

JANUARY 1975 • 75 CENTS



A HARCOURT BRACE JOVANOVIH PUBLICATION

ELECTRONIC TECHNICIAN/DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

Testing Bipolar Transistors In & Out Of Circuit / Annual Subject Reference Index

DELW57359508-P2-
10 H DEL
BOX 245
BROWNS MILLS
-AA -7763AL
AS
NJ 08015



PTS ELECTRONICS

Precision Tuner Service



now available near you

ALABAMA: 524 32ND STREET SOUTH BIRMINGHAM, ALA. 35222 TEL. 205, 323-2657	CALIFORNIA—NORTH: 4611 AUBURN BLVD SACRAMENTO, CALIF. 95841 TEL. 916, 482-6220	CALIFORNIA—SOUTH: 5111 UNIVERSITY AVE. SAN DIEGO, CALIF. 92105 TEL. 714, 280-7070	COLORADO: 4958 ALLISON ST. ARVADA, COLO. 80001 TEL. 303, 423-7080	FLORIDA—NORTH: 1918 BLANDING BLVD. JACKSONVILLE, FLA. 32210 TEL. 904, 389-9952	FLORIDA—SOUTH: 12934 N.W. 7th AVE. MIAMI, FLA. 33168 TEL. 305, 685-9811	HOME OFFICE—INDIANA: 5233 S. HWY. 37 BLOOMINGTON, IND. 47401 TEL. 812, 824-9331	KANSAS: 3116 MERRIAM LNE. KANSAS CITY, KANSAS 66100 TEL. 913, 831-1222
TEXAS—EAST: 4324-26 TELEPHONE RD. HOUSTON, TEX. 77032 TEL. 713, 644-6793	<div style="text-align: center;"> <p>... new pts products ... stop ... new 1974-1975 tuner replacement guide and parts catalog no. 4 ... stop ... 96 pages of top tuner information ... stop ...</p> <p>... blow-ups of all types of vhf and uhf tuners for easy parts identification ...</p> <p>... stop ... largest exact tuner replacement guide available in the industry</p> <p>... stop ... antenna coil replacement guide ... stop ... multifit replacement tuner shaft guide ... stop ...</p> <p>... available for \$2.00 ... stop ...</p> <p>... redeemable with min. order ... stop ...</p> <p>... pts elec ...</p> </div>					LOUISIANA: 2914 WYCHWOOD DR. METAIRIE, LOUISIANA 70033 TEL. 504, 885-2349	
TEXAS—NORTH: MOPAC LANE LONGVIEW, TEX. 75601 TEL. 214, 753-4334						MARYLAND: 1105 SPRING ST. SILVER SPRING, MD. 20910 TEL. 301, 565-0025	
TENNESSEE: 3614 LAMAR AVE. MEMPHIS, TN. 38118 TEL. 901, 365-1918						MASSACHUSETTS: 191 CHESTNUT ST. SPRINGFIELD, MASS. 01103 TEL. 413, 734-2737	
PENNSYLVANIA—WEST: 257 RIVERVIEW AVE. W. PITTSBURGH, PA. 15202 TEL. 412, 761-7648						MICHIGAN: 13709 WEST 8 MILE RD. DETROIT, MI. 48235 TEL. 313, 862-1783	
PENNSYLVANIA—EAST: 1921 S. 70th ST. PHILADELPHIA, PA. 19142 TEL. 215, 724-0999						MINNESOTA: 815 WEST LAKE ST. MINNEAPOLIS, MINN. 55408 TEL. 612, 824-2333	
OREGON: 5220 N.E. SANDY BLVD. PORTLAND, OREGON 97213 TEL. 503, 282-9636						OKLAHOMA: 3007 N. MAY OKLAHOMA CITY, OKLA. 73106 TEL. 405, 947-2013	OHIO—SOUTH: US TUNER SERVICE 8180 VINE ST. CINCINNATI, OHIO 45215 TEL. 513, 821-2298

LET US TAKE CARE OF YOUR TUNER PROBLEMS...

PTS will repair any tuner—no matter how old or new—black & white or color—transistor or tubes—varactor or electronically tuned—detent UHF. 8 hour service is a must!

...THIS IS THE SERVICE WE OFFER:

1. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located plants.
2. Best Quality—Your customers are satisfied and you are not bothered with returning tuners for rework.
3. PTS uses only ORIGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.
4. PTS is recommended by more TV Manufacturers than any other tuner company.
5. PTS is overhauling more tuners than all other tuner services combined.

Fast **8** hr. Service!

We offer you finer, faster...

... Precision
Tuner Service

1 YEAR GUARANTEE

VHF, UHF	\$10.95
UV-COMBO	17.95
IF-SUBCHASSIS	12.50

Major parts and shipping charged at cost. (Dealer net!)

Over 4000 exact tuner replacements available for \$14.95 up (new or rebuilt)



ELECTRONICS, INC....

...Number ONE and still trying harder!
(Not a Franchise Company)

Now, 23v black matrix in an economy line.

From Sylvania, of course.

Replacing a black-matrix tube has usually meant buying a brand new tube because rebuilds just didn't exist. Now, Sylvania has changed all that.

We've added five black-matrix tube types to our low-cost Color Screen 85 line, and that even includes the popular 23-inch diagonal size.

That means you can offer your customers two different price ranges.

And increase sales opportunities by offering a low-price replacement.

With Sylvania, you not only have one of the broadest lines of replacement tubes in the industry.

You also have the latest.


**Electronic Components Group,
GTE Sylvania, 100 First Ave.,
Waltham, Mass. 02154**



GTE SYLVANIA

how 80% of \$2,000 is only

\$580⁰⁰

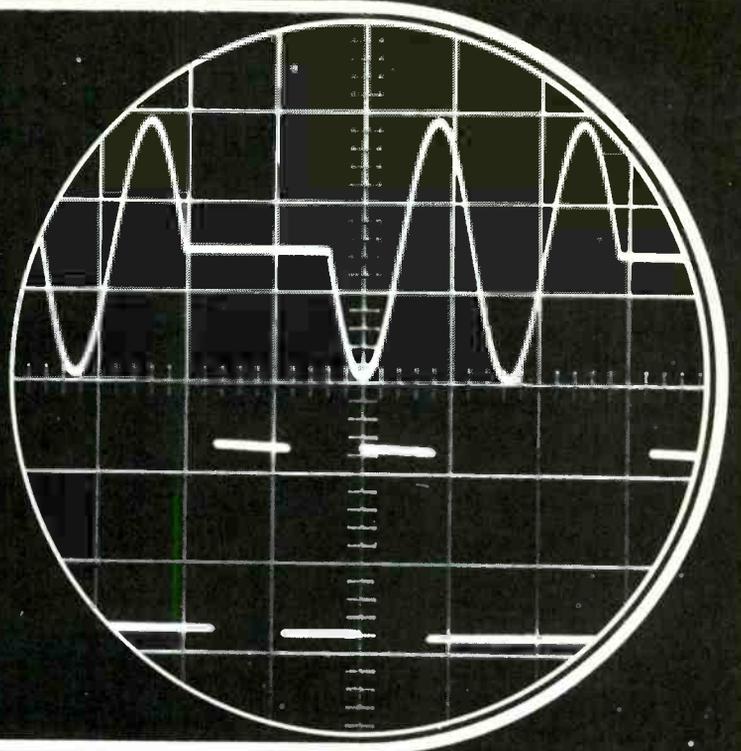

Oscilloscopes for most production, inspection, QC and lab applications are not used to their full capability.

In fact their full capability in bandwidth may even need to be limited by an external bandpass filter for easier trace readability. In one electronics manufacturing facility a survey of 22 applications discovered 19 applications which were appropriately served by our least expensive \$179.95 oscilloscope with recurrent sweep and 2MHz bandwidth. A survey of your facility may reveal similar opportunities for saving. Our triggered sweep scopes with 10MHz bandwidth and 35 nanosecond rise time answer the needs of more than 80% of all applications. Sensitivity of 10mV/cm offered by both our single and dual trace triggered sweep scopes is similarly suitable for over 80% of all applications.

Why overspecify your oscilloscopes? It's not necessary if the intent is to be sure you get the repeatability, reliability, ruggedness and versatility that is characteristic of every B&K oscilloscope. Move your ultra-wide bandwidth scopes to other applications where you need them. You'll find the B&K scopes easier to use with their simplified, human-engineered panels and controls.

10 Day Free Trial

With more than 20 years successful experience in manufacturing fine test equipment at competitive prices, Dynascan has the confidence in its new B&K instruments to offer them on a 10 day free trial basis. Just properly identify yourself, your company and your application and we'll supply a new oscilloscope that will prove our claim to quality and value. Write on your letterhead for complete specifications and Free Trial.



Model 1470

CONDENSED SPECIFICATIONS

B&K Model 1470 Dual Trace Triggered Sweep Scope
DC to 10MHz at 10mV/cm. Two separate vertical amplifiers. 35 n sec rise time. Six dual pattern modes including chopped, alternate, add and Channel 2 inverted. Auto and triggered sweep 1 usec/cm to 0.1 sec/cm. 5X magnification. **\$580.00**

B&K Model 1460 Triggered Sweep Scope
DC to 10MHz at 10mV/cm. 35 n sec rise time. 0.5 usec/cm to 0.5 sec/cm auto and triggered sweep. 5X magnification. 5V p-p 1 KHz calibration voltage. **\$450.00**

B&K Model 1431 3" Triggered "Mini-Scope"
As above, but 1/3 the size. **\$399.00**

B&K Model 1403 Portable 3" "Mini-Scope"
3" solid state scope only 5 1/4" x 7 3/8" x 11 1/4". DC to 2MHz bandwidth and 20mV/cm sensitivity. Recurrent sweep 10Hz to 100kHz. Weighs only 8 1/2 pounds. **\$189.00**



1801 W. Belle Plaine Ave. • Chicago, IL 60613 • Phone (312) 327-7270

Complete Line of Analog and Digital Multimeters, Oscilloscopes, Signal Generators, Semiconductor Testers, Power Supplies, Probes, Tube Testers and Substitution Boxes.

... for more details circle 102 on Reader Service Card

ELECTRONIC TECHNICIAN/DEALER

JANUARY 1975 • VOLUME 97 NUMBER 1

Cover photo courtesy of GTE Sylvania

J. W. PHIPPS

Editor
1 East First Street
Duluth, Minn. 55802
(218) 727-8511

ALFRED A. MENEGUS

Publisher
757 Third Avenue
New York, N.Y. 10017
(212) 754-4382

TOM GRENEY

Publishing Director

JOSEPH ZAUHAR

Managing Editor

S. J. SMITH

Production Manager

JOHN PASZAK

Graphic Design

LILLIE PEARSON

Circulation Fulfillment

GENE BAILEY

Manager, Reader Services

CONTRIBUTING EDITORS

JOSEPH J. CARR

BERNARD B. DAIEN

MANAGERS

DAVE HAGELIN

43 East Ohio Street
Chicago, Ill. 60611
(312) 467-0670

CHUCK CUMMINGS

Ad Space South/West
613 North O'Connor
Irving, Texas 75060
(214) 253-8678

KEN JORDAN

DONALD D. HOUSTON
1901 West 8th Street
Los Angeles, Calif. 90057
(213) 483-8530

CHARLES S. HARRISON

CY JOBSON
57 Post Street
San Francisco, Calif. 94104
(415) 392-6794

ROBERT UPTON

Tokyo, Japan
C.P.O., Box 1717

FEATURES

12 TESTING BIPOLAR TRANSISTORS IN AND OUT OF CIRCUIT

Practical out-of-circuit resistance and in-circuit voltage tests of silicon and germanium bipolars. By Bernard B. Daien, ET/D Contributing Editor.

22 PROFITABLE AND COMPETITIVE PRICING OF HOME SERVICE CALLS

A proven procedure for computing the flat rate you should charge for home calls. By J. W. Phipps, ET/D Editor.

26 NEW IN COLOR TV FOR 1975—Part 5

New and significantly changed features and circuits in RCA's 1975 line of color TV receivers. By Joseph Zauhar, ET/D Managing Editor.

30 DIGITAL FREQUENCY COUNTERS FOR SERVICING—Part 1

First of a two-part series which examines the theory of operation, specifications and servicing applications of digital-readout frequency counters. By Joseph J. Carr, ET/D Contributing Editor.

35 TECH BOOK DIGEST—Troubleshooting Horizontal Deflection & High-Voltage Circuits—Part 1

A two-part series which analyzes the operation of horizontal deflection and high-voltage circuits and explains how to isolate faults in them. By Ben Gaddis, TAB BOOKS, Copyright 1974.

38 ET/D 1974 SUBJECT REFERENCE INDEX

Alphabetical listing of subjects and article titles by issue and page.

TEKFAX—Airline Models GAI-12925A, GAI-11245A, B and GAI-11265A, B; General Electric Ch. XA; Quasar Ch. ATS-, CTS- and TS-942; and Sylvania Ch. E11-1.

DEPARTMENTS

- | | |
|---------------------------------|-----------------------|
| 4 EDITOR'S MEMO | 43 TECH DIGEST |
| 6 NEWS OF THE INDUSTRY | 44 NEW PRODUCTS |
| 9 ELECTRONIC ASSOCIATION DIGEST | 48 DEALER SHOWCASE |
| 10 TECHNICAL LITERATURE | 50 ADVERTISERS' INDEX |
| 42 TEST INSTRUMENT REPORT | 51 READER SERVICE |




A HARCOURT BRACE JOVANOVIICH PUBLICATION



HARCOURT BRACE JOVANOVIICH PUBLICATIONS: James Milholland, Jr., Chairman; Robert L. Edgell, President; Lars Fladmark, Senior Vice President; Richard Moeller, Treasurer; John G. Reynolds, Vice President; Thomas Greney, Vice President; Ezra Pincus, Vice President; Bruce B. Howat, Vice President; James Gherna, Vice President.

ELECTRONIC TECHNICIAN/DEALER is published monthly by Harcourt Brace Jovanovich Publications. Corporate Offices: 757 Third Avenue, New York, New York 10017. Advertising Offices: 43 East Ohio Street, Chicago, Illinois 60611 and 757 Third Avenue, New York, New York 10017. Editorial, Accounting, Ad Production and Circulation Offices: 1 East First Street Duluth, Minnesota 55802. Subscription rates: One year \$6, two years \$10, three years \$13, in the United States and Canada. Other countries: one year \$15, two years \$24, three years \$30. Single copies: 75¢ in the U.S. and Canada; all other countries \$2. Second class postage paid at Duluth, Minnesota 55806 and at additional mailing offices. Copyright © 1975 by Harcourt Brace Jovanovich, Inc. All rights reserved. No part of this publication may be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopy, recording, or any information storage and retrieval system, without permission in writing from the publisher.

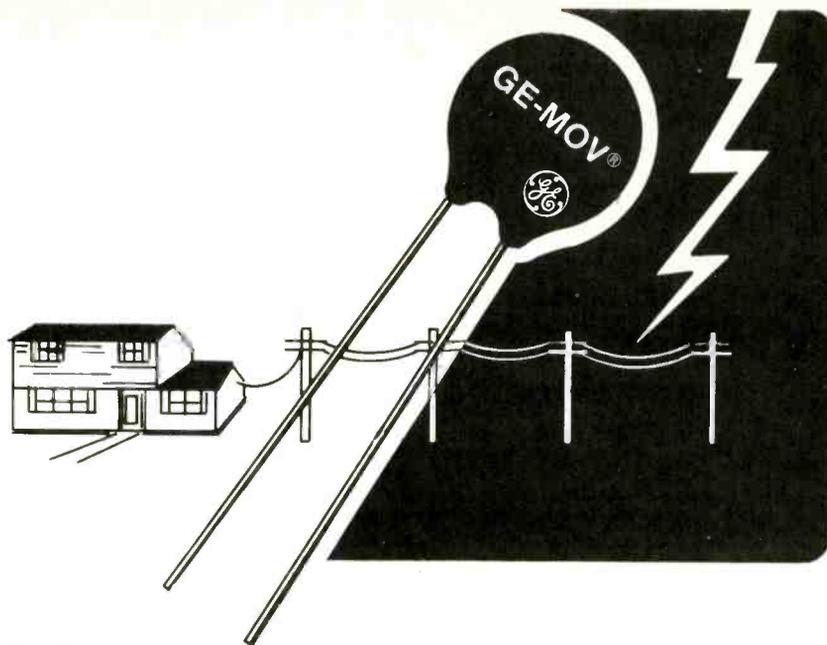POSTMASTER: Send form 3579 to ELECTRONIC TECHNICIAN/DEALER, P.O. Box 6016, Duluth, Minnesota 55806.



NOW! Protect against Transient Voltage Damage to TV, Stereo and Home Appliances with **GE-MOV[®]** Metal Oxide Varistors.

TV Set manufacturers know that many component failures are caused by voltage transients: lightning, voltage spikes and power surges. Now you can do something about it . . . economically.

Insert easy to install GE-MOV metal oxide varistors in component circuits and prevent damage from transient voltage once and for all. The varistor absorbs the dangerous transient and dissipates it as heat. The cost is low. The installation fast and easy. It's like offering your customers an insurance package . . . and it's an opportunity to make a profit!

Our GE-MOV program is ready and waiting. For all the facts about this addition to General Electric's growing replacement semiconductor line, see your authorized distributor.



TUBE PRODUCTS DEPARTMENT
GENERAL ELECTRIC COMPANY
OWENSBORO, KENTUCKY 42301

GENERAL  ELECTRIC

EDITOR'S MEMO

CONTRIBUTING EDITORS

■ Beginning with this issue, two additional names—Joseph J. Carr, CET, and Bernard B. Daien, CET—appear on the masthead of ET/D.

Articles by these two knowledgeable and experienced technicians have been published in recent issues of ET/D and, because they were so well received by ET/D readers, we asked Mr. Carr and Mr. Daien to become contributing editors for ET/D. As such, they will author one article in each issue and will function in an editorial advisory capacity as well as serving as additional "eyes and ears" in their respective areas of the country for the Duluth-based editorial staff.

Joe Carr has 15 years experience as an electronic technician and, while attending college, was an active partner in an auto radio servicing business. He has authored many books and articles about electronics and electronic servicing and is a Certified Electronic Technician (CET). Mr. Carr presently is a technician in the bioelectronics laboratory of George Washington University Medical Center in Washington, D.C.

Bernard Daien has over thirty years' experience as an electronic technician, engineer, teacher and author. He is a Certified Electronic Technician and holds commercial and amateur radio licenses. Mr. Daien previously was a senior systems engineer for Motorola Semiconductor Products Division in Tempe, Arizona, and now writes about and services electronic products in Phoenix, Arizona.

A SPECIAL "THANK YOU" TO ET/D READERS

On behalf of the entire ET/D staff, I want to thank the many readers who responded to the Reader Preference Survey in the November issue. Your cooperation in making ET/D even more responsive to your needs and interests is appreciated. Again, thank you. ■

J. W. Phipps

NEWS OF THE INDUSTRY

Audio Product Sales Up in October But Overall Sales of Entertainment Electronic Products Sagged During First 10 Months of 1974

Although total sales to dealers of all audio categories of entertainment electronic products were up in October, sales of all entertainment electronic products except home FM radios during the first ten months of 1974 were below levels achieved during the same period in 1973, as revealed by the following statistics released by the Marketing Services Department of the Electronic Industries Association:

	FIRST 10 MONTHS		% CHANGE
	1974	1973	
Television			
Monochrome	4,840,057	5,524,854	-12.4
Color	6,466,745	7,306,308	-11.5
TOTAL TELEVISION	11,306,802	12,831,162	-11.9
Radio			
AM	9,782,411	13,133,771	-25.5
FM	15,714,544	14,415,804	+9.0
TOTAL	25,496,955	27,549,575	-7.5
AUTOMOBILE	8,753,638	10,439,759	-16.2
TOTAL RADIO	34,250,593	37,989,334	-9.8
Phonograph			
Portable & Table*	3,328,513	4,463,144	-25.4
Console	641,978	676,059	-5.0
TOTAL PHONOGRAPH	3,970,491	5,139,203	-22.7

*Includes compact and component systems.

Sylvania Warranty Department at New Address

The Labor Warranty Department of GTE Sylvania has been moved to 700 Ellicott St., Batavia, N.Y. 14020. All warranty labor claims and questions about warranty labor should be sent to this new address.

New York Fair Trade Law Upheld

The New York Supreme Court, in a fair trade case involving Matsushita Electric Corporation of America (Panasonic) and three stores of the JGE retail chain, has ruled that the Fair Trade Laws of New York State are not unconstitutional.

The Court has issued injunctions against the three JGE stores, restraining them from price cutting activities which the Court felt were jeopardizing the effectiveness of Matsushita's Fair Trade program in New York state.

1975 Consumer Electronics Show in Chicago June 1-4

The ninth annual Summer Consumer Electronics Show, sponsored and produced by the Consumer Electronics Group of the Electronic Industries Association, will be held June 1-4 at McCormick Place in Chicago.

Over 400 manufacturers and marketers of consumer electronic products will exhibit their new 1976 lines at the trade show, which is open to retailers, distributors, sales representatives and manufacturers. Retail-oriented audio, video and calculator conferences will be held during the show.


OSHA Recordkeeping Forms Revised

Beginning this month, employers who have eight or more employees are required to record occupationally related injuries and illnesses on a revised form which categorizes lost work days into two types: "days away from work" and "days of restricted work activity."

"Days away from work" are defined by the U.S. Department of Labor as any days on which an employee would have worked but could not because of occupational injury or illness.

"Days of restricted work activity" are defined by the Labor Department as days during which an employee was assigned to another job on a temporary basis, or worked at his regular job less than full time, or worked at his regular job but could not perform all duties normally connected with it because of occupational injury or illness. ■

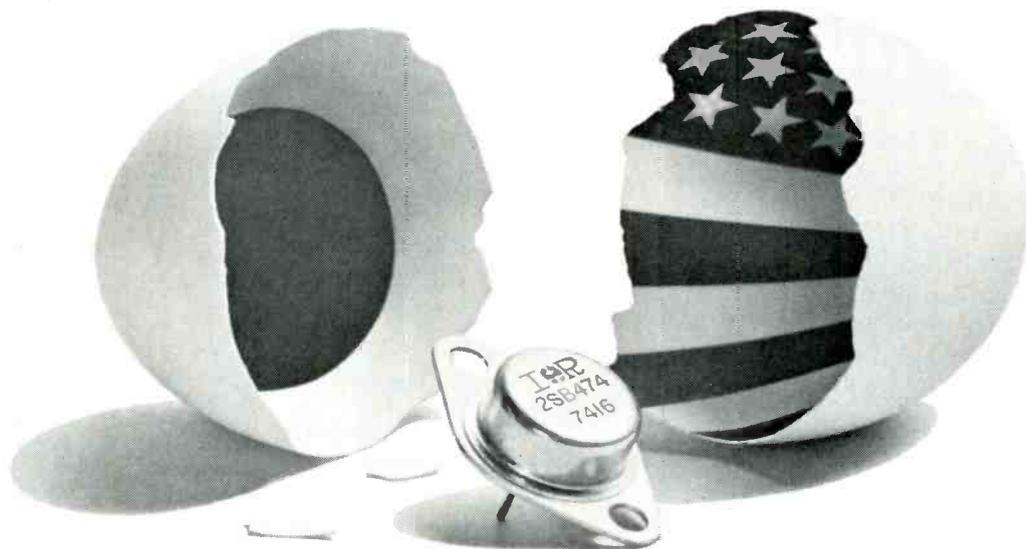How to crack the Japanese original equipment transistor problem.



Until now, there wasn't much you could do about the long delays in getting original transistor replacements for Japanese TV and audio equipment. IR has changed the picture. Now you can speed customer service with IR's DK22 Kit of 31 OEM transistors most often called out by Sony, Panasonic, Hitachi, JVC, Pioneer and Toshiba, and for many sets made in Japan for Sears, Penney's, Montgomery Ward and others.

Last year, more Japanese-built TV's were sold in this country than any single U.S. brand. And the same transistors are used in Japanese stereos, tape recorders and other entertainment equipment. Crack this fast-growing, lucrative service market with a DK22 Kit. Call your local IR Distributor today. You'll get a \$42.78 value for only \$34.23... less than the price you'd pay Japanese factory distributors.

These are not "Universal Replacements."

They are exactly the same parts used in original equipment. They're made in Japan, but are now as close to you as your local IR Distributor. Each DK22 Kit contains one each of the 31 types listed in the box at right to put exact replacements right at your fingertips.



DK22 Kit Japanese Transistors:

2SA495	2SC281B	2SC535B	2SC710
2SA564A	2SC372	2SC536	2SC717
2SB186	2SC373	2SC537B	2SC772
2SB187	2SC380AO	2SC538A	2SC828A
2SB367A	2SC403A	2SC633A	2SC829B
2SB405	2SC454B	2SC634A	2SC838
2SB474	2SC458B	2SC644	2SC945
2SB481	2SC460B	2SC682A	

INTERNATIONAL RECTIFIER
Semiconductor Division,



233 Kansas Street, El Segundo, California 90245, Phone (213) 678-6281

... for more details circle 115 on Reader Service Card

JANUARY 1975, ELECTRONIC TECHNICIAN/DEALER | 7

Now make almost all your replacements with RCA's medium-priced Colorama A's


That's the kind of socket coverage you can count on from this popular new "middle line" of RCA replacement color picture tubes. With just eight Colorama A types, you can cover almost all of the replacement market with "Grade A" performance at a price your customers can afford.

Every tube in the RCA Colorama A line is totally remanufactured. That's why they all can carry RCA's 18-month inboarded warranty plus the option for an additional 12 months. Each has a completely new gun and a completely new screen made of the latest all-new rare-earth phosphors. In addition, every "V" type is made of advanced x-ray glass.

The RCA Colorama A line includes three Matrix types: CA-21VAKP22, CA-23VALP22 and CA-25VABP22. These advanced RCA Matrix tubes are as much as 100 percent brighter than any equivalent non-Matrix picture tube in RCA history.

So why not give your customers the "Grade A" choice. Choose Colorama A at your RCA Distributor today.

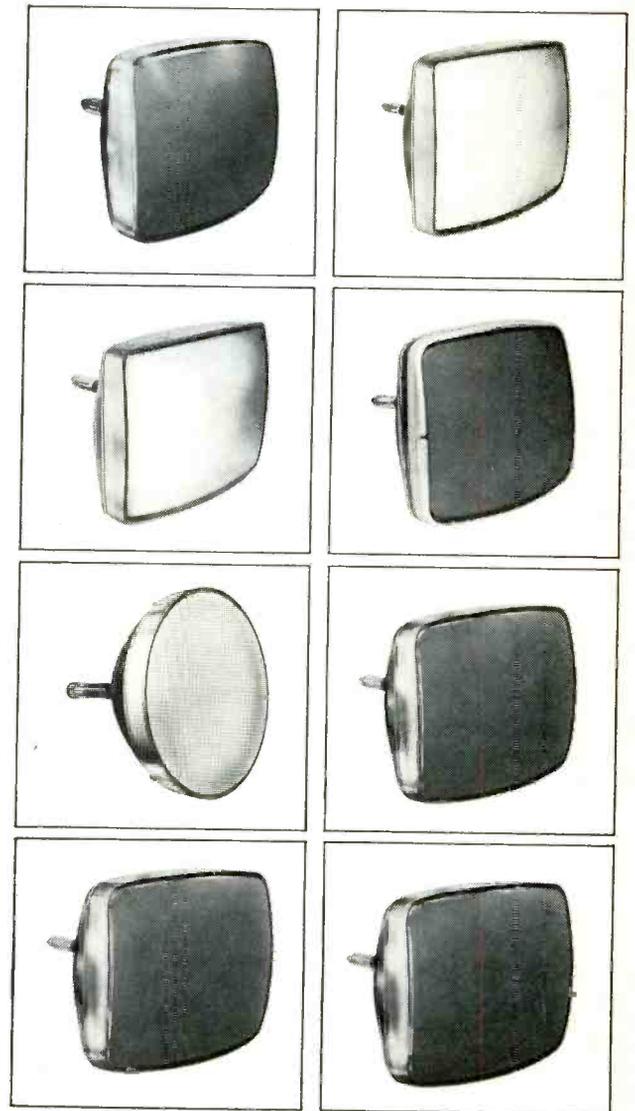Remember, RCA is the world-wide leader in picture tubes, with over 65 million produced to date.



RCA

RCA/Electronic Components/Harrison, N.J. 07029

ELECTRONIC ASSOCIATION DIGEST

Information about the activities of national, state and local associations of electronic servicers, dealers and manufacturers. Material for publication in this department should be addressed to: Service Association Digest, ET/D, 1 East First St., Duluth, Minn. 55802.

ETG of Rhode Island Elects New Officers

The Electronic Technicians Guild of Rhode Island, meeting in Pawtucket on Nov. 6, elected the following new officers, whose terms of office begin this month: Paul F. Kelley, Warwick, president; Donn C. DiBiasio, Providence, vice president; William Botelho, Warwick, secretary; Norman L. Lemieux, Attleboro, Mass., treasurer; and Thomas J. Plant, Jr., Pawtucket, corresponding secretary.

Pennsylvania IS CET Chapter Receives Charter, Elects Officers

The Pennsylvania Chapter of the International Society of Certified Electronics Technicians (ISCET) recently received its charter at a luncheon meeting in the Hilton Inn in Scranton.

Russell Scarpelli, owner of Scarpelli Electronics Service, Blakely, chairman of the new chapter, was presented the charter by John Risse of International Correspondence Schools, who represented Dick Glass, ISCET executive vice president. Other officers of the newly organized state chapter are: James Ibaugh, RCA, Lancaster, vice chairman; Ronald Lettieri, Tobyhanna Army Depot, Dunmore, secretary; and Hank Govan, Weston Instruments, Olyphant, treasurer.

FESA Chapter Sponsors Consumer "Hot line"

The Dade County Chapter of the Florida Electronics Service Association (FESA) has installed a consumer "hot line" telephone in the office of the chapter's recording secretary, John W. Dole, Dole TV & Radio, Miami.

The "hot line," which is connected to a telephone answering machine, was installed when the chapter reportedly found that the local Better Business Bureau was taking up to two months to handle consumer complaints. The "hot line" telephone number is listed in the Yellow Pages and has been publicized by local newspapers and radio and TV stations.

ESETRA Formed to Cope with Warranty-Related Problems

Elected officials of the National Appliance and Radio-Electronics Dealers Association (NARDA Inc.), the National Alliance of Television and Electronic Service Associations (NATESA), and the National Electronic Service Dealers Association (NESDA) recently met in Louisville, Kentucky to form a special "blue-ribbon" committee which will attempt to come up with solutions to warranty-related problems.

Nolan Boone, president of the Television Service Association of Arkansas, was appointed coordinating chairman of the special national committee, which has been given the name "Eastern States Electronics Technicians Regional Alliance" (ESETRA).

In addition to the chairman, the committee consists of two elected officials from each of the three national associations (NARDA, NATESA and NESDA).

Included among the warranty-related problems the committee will study are labor rates, parts availability, slow payment by manufacturers, and the additional costs of in-warranty servicing. ■

BEFORE YOU BUY A SWITCH... CONSIDER THIS—ELECTROGRAFT GIVES YOU ...


- More than 120 switches and accessories of all types and styles
- All displayed on one fixture for easy selection
- Also available in bulk put-ups for quantity users.



Attractive, easy to read bubble pack cards with specific, pertinent product information.



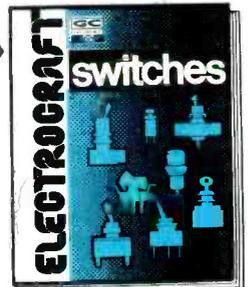48 page catalog complete with technical specs, templates and cross reference also available



GC ELECTRONICS
 DIVISION OF HYDROMETALS, INC.
 ROCKFORD, ILLINOIS 61101 U.S.A.



TECHNICAL LITERATURE

Alarm/Security Cable

A revised 12-page expanded catalog of electronic wire and cable for alarm/security applications has been published. The catalog simplifies selection of wire and cable by installers, specifications and systems engineers, systems contractors, and maintenance personnel concerned with surveillance, detection, alarm, and communications

equipment. More than 100 individual wire, cable, and cord designs are included in the catalog. Catalogued for the first time are 42 vinyl-insulated multiple-conductor control and audio cables (not paired), seven single-conductor hook-up wire designs, and three portable cord constructions. **Belden Corp.**, Advertising Dept., 2000 S. Batavia Ave., Geneva, IL. 60134.

Semiconductors and Accessories

A 148-page SK-Series Top of the Line Replacement Guide, No. SPG-202P, is now available. The guide lists

87,000 SK-Series solid-state replacements which include transistors, rectifiers, thyristors and integrated circuits. The guide is a comprehensive and accurate source of solid-state replacement information. The 87,000 semiconductor devices are cross-referenced to the SK-Series replacement semiconductors. The Replacement Program is composed of devices for uses as replacements in entertainment and industrial type equipment. Price \$90. **RCA/Distributor Products Marketing**, Route 202, Somerville, NJ. 08876.

Radio/TV Repair Course

A 6-page pamphlet describing its radio and TV service and repair course is now available. It briefly discusses course topics and career opportunities for individuals interested in working directly in radio and TV service and repair as well as in related fields. **Advance Schools, Inc.**, is a national home-study school accredited by the accrediting Commission of the National Home Study Council. **ASI Marketing Communications**, Dept. TV, 5900 Northwest Highway, Chicago, IL. 60631.

Professional Tools and Safety Equipment

An 80-page catalog of specialized professional hand tools and safety equipment is now available. The catalog is organized for easy reference and fully indexed—both alphabetically and by product number. Tools and safety equipment are illustrated with large photographs and drawings. Many illustrations utilize a second or third color for added clarity of special features. Concise product descriptions, specifications, and catalog numbers make selection simple. **Mathias Klein & Sons, Inc.**, 7200 McCormick Road, Chicago, IL. 60645.

Solid-State Product Guide

A 40-page Solid-State Product Guide No. SPG-201K is now available. This booklet contains abbreviated data for the commercial solid-state products available from the RCA Solid State Division. Data is given for Integrated Circuits (Linear and Digital) and discrete devices (power transistors, RF transistors, MOS transistors, triacs, silicon controlled-rectifiers, diacs, and rectifiers). Complete data on individual devices can be obtained by reference to the technical bulletins listed by file number or to the RCA Solid-State DATABOOK Series (SSD-2001); the publications are available from **RCA Solid State Division**, Box 3200, Somerville, NJ. 08876. ■

WHEN YOU'VE GOT
SOLID STATE SENSITIVITY
IN A 5" GENERAL SERVICE
SCOPE WITH TV-V
& TV-H... YOU'VE GOT
LEADER.



What's more, the LBO-511 delivers calibrated vertical input along with rock-like stability, recurrent sweep and automatic synchronization. This outstanding wide-band oscilloscope/vector scope is the newest in a series of solid state instruments, Leader developed to give you more for your money. Sweep frequency is in 4 ranges from 10Hz to 100Hz and we've added a versatile phasing control, continuous from 0 to 140°. Overall sensitivity is 20mVp-p/cm to 10Vp-p/cm

and vertical input is calibrated. The solid-state stability and distortion-free displays are the result of Leader's exclusive FET input stages plus DC coupling and push-pull amplifiers. Bandwidth is DC to 10MHz. And, there are special inputs to obtain vectored pattern displays for color TV circuit testing. Complete with probe, adapter and test leads, the LBO-511 weighs just 15 lbs. and is unusually compact.

\$299.95

"Put us to the test"

LEADER
INSTRUMENTS CORP.

151 Dupont Street, Plainview, L.I., N.Y. 11803 (516) 822-9300

... for more details circle 117 on Reader Service Card



Our Television Systems will sell your Televisions

Color TV sells on demonstration. The better the demonstration the quicker the sale. Nothing is more embarrassing than to demonstrate a fine TV set and find the picture rolling, the color balance changing. And it can happen, just at the wrong time.

One of the ways you can make sure that it won't happen is by using Blonder-Tongue distribution systems. Blonder-Tongue offers a wide choice of systems for color TV, black and white, and hi-fi component demonstrations. Any number of outlets, for best performance in any area—big city, suburbs

or deep fringe.

We've got the products from antennas to TV terminals. Most important we have the know-how gained through thousands of showroom system installa-

tions over the past 24 years.

We offer you a layout of a showroom TV system tailored to your store layout and reception area. It's free. Use coupon below for a survey request form.

Blonder-Tongue Laboratories, Inc.
One Jake Brown Rd. Old Bridge, N.J. 08857

Please send me a survey request so I can provide information required for a system layout for my store.

Name _____

Company _____

Address _____

City _____ State _____ Zip _____



BLONDER-TONGUE since 1950, leader in TV reception products.

... for more details circle 104 on Reader Service Card



Testing Bipolar Transistors In and Out of Circuit

By Bernard B. Daien, ET/D Contributing Editor

Tips about the simple resistance and voltage measurements you probably are using to uncover most defective transistors

■ A vacuum tube “wears out” over a period of time because the coating on its cathode becomes “depleted,” reducing the number of electrons emitted from the cathode to the plate.

Transistors do not “wear out.” If a transistor is normal when it is installed in a circuit, it usually will continue to perform within its design limits until some circuit defect or abnormal operating condition causes excessive voltage across or excessive current through one or more of its three junctions (emitter-base, base-collector or emitter-collector). The excessive voltage and/or excessive current will cause either 1) catastrophic failure of the junction (it becomes open or shorted) or 2) the transistor will develop excessive leakage or noise.

Most transistor failures are “complete” shorts or opens, either base to emitter, base to collector, or emitter to collector. (The emitter-to-collector short can exist even though the emitter-to-base and collector-to-base junctions test normal for both forward and reverse conduction. So never omit testing for shorts between collector and emitter, even if you have made the other tests.)

The incidence of leakage in most modern transistors is not as prevalent as it was in germanium devices made several years ago. Unfortunately, you may run across an older receiver which uses the early germanium transistors, or you may

have some old stock on hand. It is good practice to discard any transistors bought prior to 1965, or, at least, put them into your “private” collection or use them for “home brew” projects. It isn’t worth risking a callback for a device that can be bought today for a dollar or so.

An unusually noisy transistor should also be replaced, because there is a direct connection between noisy transistors and premature failures.

If a circuit failure subjects the transistor to a substantial overload, it is a good practice to replace the transistor, because gain, leakage, and junction voltage drops might be adversely affected.

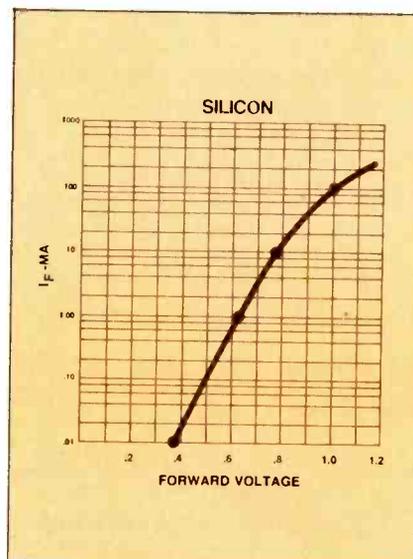


Fig. 1—Forward voltage—forward current curve of a typical silicon bipolar transistor.

OUT-OF-CIRCUIT TESTS

Although it is recommended that the voltages across the junctions of the transistor be measured before the transistor is removed from the circuit for ohmmeter tests, in this article ohmmeter tests will be discussed first because a thorough understanding of the junction characteristics involved in ohmmeter tests make it easier to understand and interpret the causes of abnormal voltages across the transistor junctions.

First, let us look at the forward voltage drop across a basic silicon junction with various levels of current through it. Fig. 1 shows that different levels of current cause different voltage drops. At 0.01 ma we read about 0.38 volts. At 1ma, 0.62 volts. At 10ma, 0.78 volts. At 100ma, 1.0 volts. Note that although the current through the junction has been increased by a factor of 10,000 (from .01ma to 100ma) the voltage drop across the junction has increased by a factor of only less than 3. This reveals that the resistance (E/I) of the junction is nonlinear; that is, an increase of current through the junction does not produce a *proportional* increase in the voltage drop across it.

The junctions of germanium transistors also exhibit nonlinear resistance characteristics, as revealed by the forward voltage-forward current curve in Fig. 2.

The nonlinear resistance charac-

TUNER SERVICE CORPORATION

SUBSTITUNER



INTRODUCING
AT JUST

\$39.95
U.S.A.
ONLY

WITH CABLES

ONE YEAR
GUARANTEE



STILL ONLY

\$9.95
U.S.A.
ONLY

ALL PARTS
INCLUDED

EXCEPT TUBES
AND TRANSISTORS

PROVIDES YOU WITH A COMPLETE SERVICE
FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.

Demonstrate the **SUBSTITUNER** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 9.95
UHF/VHF COMBINATION (U.S.A. ONLY) \$15.00

- IN THIS PRICE ALL PARTS ARE INCLUDED. Tubes, transistors, diodes, and nuvistors are charged extra. This price does not include mutilated tuners.
- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$12.95 (Canada \$15.95)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA. or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (Canada \$17.95 and \$15.95)
- Send in your original tuner for comparison purposes to Franchises listed below.



HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812-334-0411
ARIZONA	TUCSON, ARIZONA 85710	P. O. Box 4534, 1528 S. 6th St.	Tel. 602-791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213-789-2720
	BURLINGAME, CALIF. 94010	1324 Marsten Road	Tel. 415-347-5728
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209-521-8051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813-253-0324
	HIALEAH, FLORIDA 33013	906 East 25th Street	Tel. 305-836-7078
GEORGIA	ATLANTA, GEORGIA 30310	938 Gordon Street S.W.	Tel. 404-759-2232
ILLINOIS	CHAMPAIGN, ILLINOIS 61820	405 East University Street	Tel. 217-356-6400
	CHICAGO, ILLINOIS 60621	737 West 55th Street	Tel. 312-873-5556-7
	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312-675-0230
INDIANA	HAMMOND, INDIANA 46323	6833 Grand Avenue	Tel. 219-845-2676
	INDIANAPOLIS, INDIANA 46204	112 West St. Clair Street	Tel. 317-632-3493
KENTUCKY	LOUISVILLE, KENTUCKY 40208	2920 Taylor Boulevard	Tel. 502-634-3334
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Avenue	Tel. 318-861-7745
MARYLAND	BALTIMORE, MARYLAND 21215	5505 Reisterstown Rd., Box 2624	Tel. 301-358-1186
MISSOURI	ST. LOUIS, MISSOURI 63132	10530 Page Avenue	Tel. 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue No.	Tel. 702-384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	901 North Olden Avenue	Tel. 609-393-0999
	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnele Ave., Hwy. 1 & 9	Tel. 201-792-3730
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	Tel. 513-821-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216-741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Avenue	Tel. 503-222-9059
TENNESSEE	GREENVILLE, TENNESSEE 37743	1215 Snapps Ferry Road	Tel. 615-639-8451
	MEMPHIS, TENNESSEE 38111	3158 Barton Avenue	Tel. 901-458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214-327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel. 804-855-2518
CANADA	ST. LAURENT, QUEBEC H4N-2L7	305 Decarie Boulevard	Tel. 514-748-8803
	CALGARY, ALBERTA T2H-0L1	448 42nd Avenue S.E.	Tel. 403-243-0971
		P. O. Box 5823, Stn. "A"	

WATCH US
GROW

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS,
WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

teristic of transistor junctions and the fact that each range of an ohmmeter applies a different value of current to the junction are the reasons that the amount of resistance measured across a transistor junction depends on which ohmmeter range is used. This is illustrated in Tables 1, 2 and 3, which list the resistances of forward and reverse

biased junctions of typical germanium and silicon power transistors. (The resistances were measured with a Simpson Model 260 VOM, which has 20,000 ohms/volt input resistance, a 50 microamp meter, and produces about 50ma of current through the junction in the RX1 range, about .50ma in the RX100 range and 50 microamps in

the RX10,000 range.)

Note that in Table 1 the base-to-emitter and base-to-collector forward resistances are the same. Also note in Table 1 that, because of the inherently higher leakage of germanium transistors, the RX1 and RX10K ranges produced completely misleading readings for the germanium junctions (RX10K range falsely indicates shorted junctions) and less than conclusive readings for the silicon junctions. On the other hand, the RX100 range provides relatively accurate readings which would clearly reveal a shorted or open junction.

Note in Table 2, which lists the reverse bias resistances for the same junctions, that the RX100 range again produces conclusive readings which would clearly disclose open or shorted conditions, while the RX1

TABLE 1

METER RANGE	FORWARD BIASED JUNCTION RESISTANCES			
	GERMANIUM		SILICON	
	B-E	B-C	B-E	B-C
RX1	4 ohms	4 ohms	9 ohms	9 ohms
RX100	100 ohms	100 ohms	550 ohms	550 ohms
RX10K	0 ohms	0 ohms	7000 ohms	7000 ohms

TABLE 2

METER RANGE	REVERSE BIASED JUNCTION RESISTANCES			
	GERMANIUM		SILICON	
	B-E	B-C	B-E	B-C
RX1	Inf.	Inf.	Inf.	Inf.
RX100	50K ohms	50K ohms	Inf.	Inf.
RX10K	150K ohms	150K ohms	1.5 meg ohms	Inf.

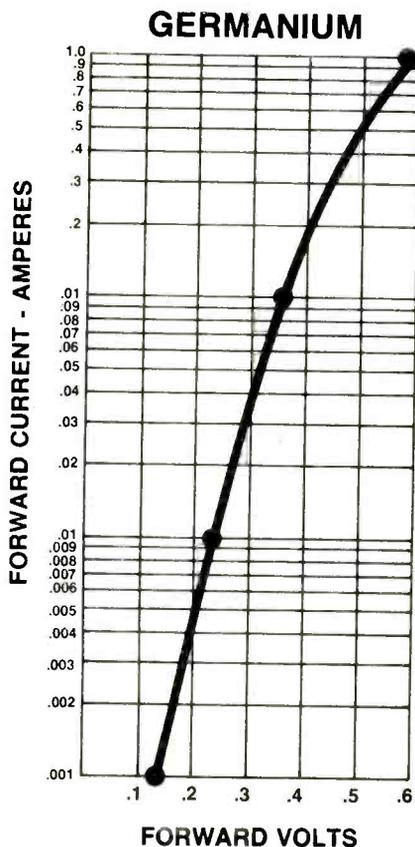


Fig. 2—Forward voltage—forward current curve of a typical germanium bipolar transistor.

TABLE 3

METER RANGE	EMITTER-COLLECTOR JUNCTION RESISTANCES (REVERSE BIAS ON COLLECTOR)	
	GERMANIUM	SILICON
	E-C	E-C
RX1	400 ohms	Inf.
RX100	50 ohms	Inf.
RX10K	0 ohms	Inf.

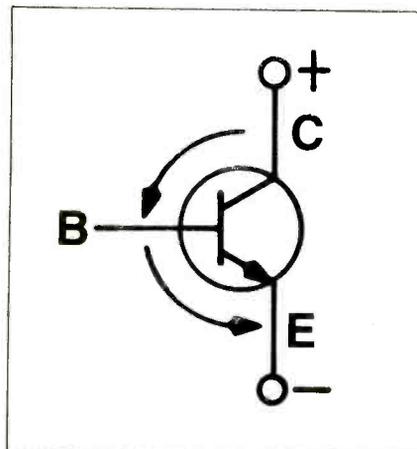


Fig. 3—The leakage current indicated by the arrows is the reason that germanium power transistors inherently have low reverse-bias emitter-to-collector resistance.

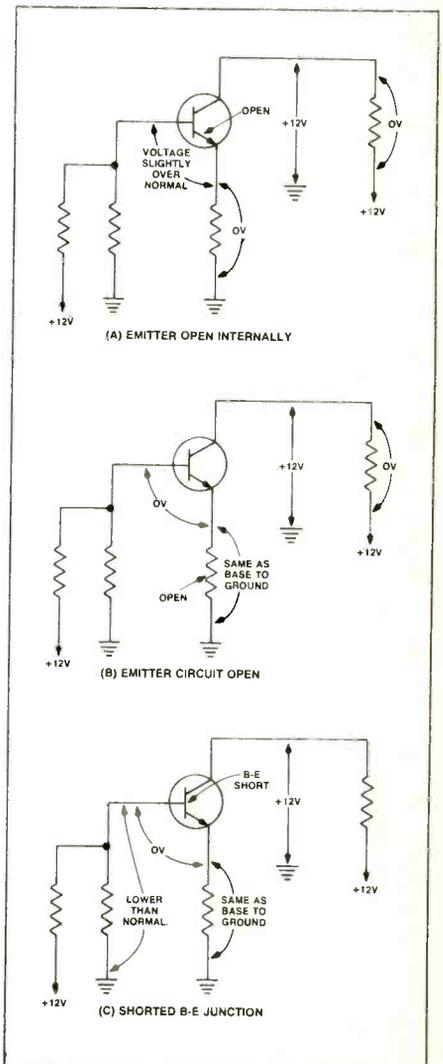


Fig. 4—Typical emitter-related defects and associated voltage symptoms in a common-emitter circuit.

and RX10K ranges again produce inconclusive or misleading readings.

Table 3 lists the emitter-to-collector resistances of the same transistors, with the collector reverse biased just as it would be during normal in-circuit operation. Note that the inherently higher leakage of the germanium transistor produced a completely misleading reading on the RX10K range, but, again, the RX100 range produced a conclusive reading which would reveal a short or open condition, if either existed.

To understand why germanium power transistors have such low emitter-to-collector resistance when reverse biased, refer to Fig. 3. Note that any leakage across the base-to-collector junction has nowhere to go if the base is open (or if there is a very high resistance between base and emitter). The leakage therefore crosses the forward-biased emitter-to-base junction in order to complete the circuit. Any current flowing through the emitter-to-base junction is amplified by the transistor,

and a larger current then flows between emitter and collector. Thus, when the base is open, the collector junction leakage is amplified by the current gain of the transistor and the emitter-to-collector path be-

comes a low resistance.

Even modern germanium transistors have higher leakage than silicon transistors, and power transistors have higher leakages than small-signal transistors. Therefore, the leakage of a germanium power transistor can be considerable. If you stick with the RX10 or RX100 ranges (whichever your meter has) you will avoid most of the leakage problems.

Semiconductors are temperature sensitive devices. Leakage doubles for every 10-degree C temperature rise. Therefore, transistors operating in circuit will have greater leakage than that measured "cold" out of circuit. Typically the junction temperature for germanium transistors may go as high as 70 degrees or more, representing an increase in "hot" leakage current of about 15 times over "cold" junction leakage.

To make matters worse, the emitter-to-base junction has a negative temperature coefficient (as the temperature increases the required forward bias decreases). Thus, for a given bias, collector current tends to increase as the temperature increases. The combination of these two effects causes significantly higher currents to flow in a leaky transistor as it heats up. If you find a transistor that appears to have more leakage than similar devices, and you are doubtful about it (remember, it's going to get worse as it heats up in the set), replace it and save yourself a callback. This applies particularly to germanium devices used in auto radios, some portable radios and in older sets. Modern silicon transistors tend not to leak. They are either normal or open or shorted, and not much else.

Another reason for using only the RX10 or RX100 range of your VOM is that the RX1 range of many VOM's applies 100ma or more of current to a junction under test. This level of current is sufficient to damage the base-to-emitter junction of some low-power transistors and the junction of signal diodes.

If you are not already thoroughly familiar with the junction resistance readings produced by your VOM, use it to make readings of the forward- and reverse-biased junction resistances of known-good germani-

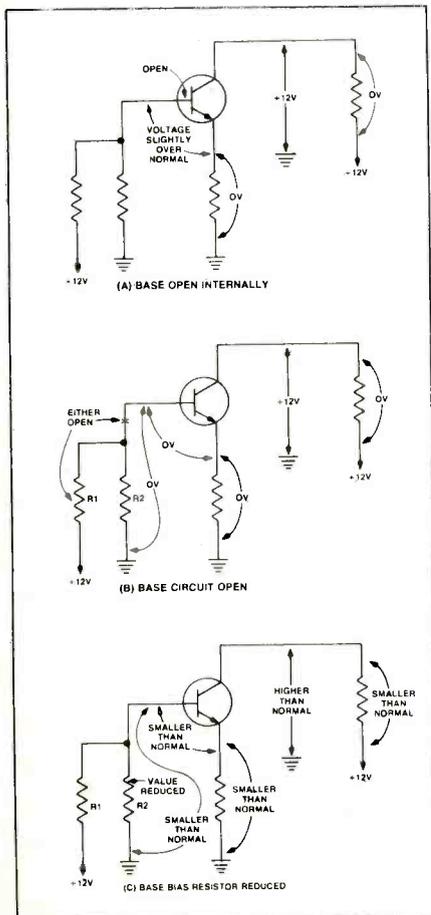


Fig. 5—Typical base-related defects and associated voltage symptoms in a common-emitter circuit.

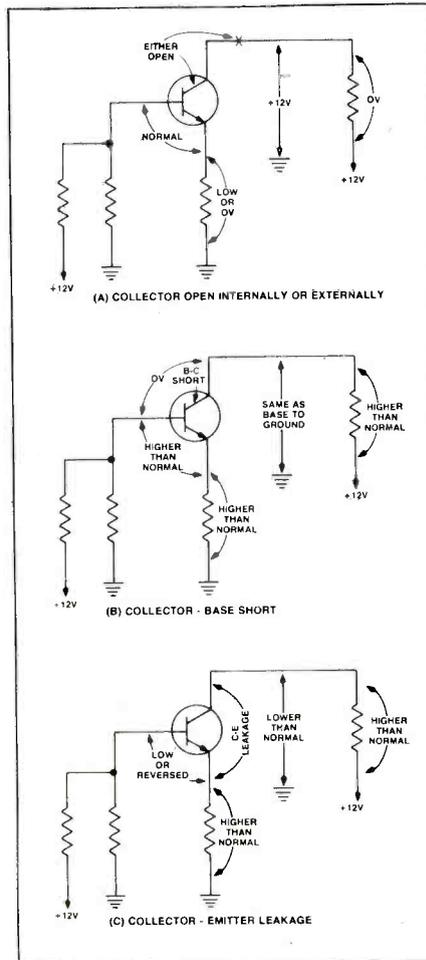


Fig. 6—Typical collector-related defects and associated voltage symptoms in a common-emitter circuit.

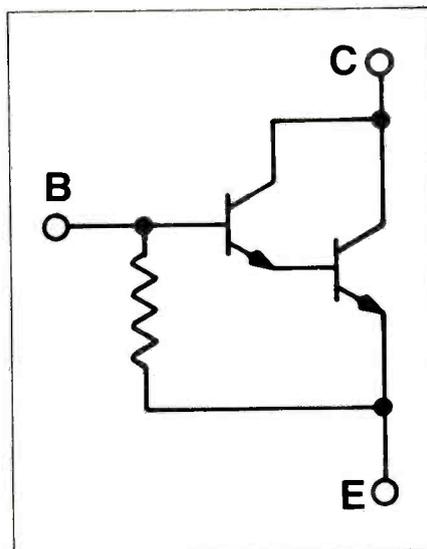


Fig. 7—Internal circuitry of a Darlington transistor.

An Extraordinary Offer

to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

for a limited time only you can obtain

ANY **3** OF THESE UNIQUE BOOKS . . . yours for only **99¢** each
...with Trial Club Membership (Combined List Price \$45.85)

May we send you your choice of any three books on the facing page as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics.

These handsome, hardbound books are indicative of the many other fine offerings made to Members . . . important books to read and keep . . . volumes with your specialized interests in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, engineering—you will find Electronics Book Club will help you.

With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your understanding of electronics, too.

How You Profit From Club Membership

This special offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Membership in the Club offers you several advantages.

1. Charter Bonus: Take any three of the books shown . . . plus the FREE Bonus book worth \$7.95 (combined values to \$53.80) for only 99¢ each with your Trial Membership.

2. Guaranteed Savings: The Club guarantees to save you at least 25% to 75% on all books offered.

3. Continuing Bonus: If you continue after this trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99, will entitle you to a valuable Book Dividend which you may choose from a special list provided members.

4. Wide Selection: Members are annually offered over 50 authoritative books on all phases of electronics.

5. Bonus Books: If you continue in the Club after fulfilling your Trial Membership, you will receive a Bonus Dividend Certificate with each addi-

SPECIAL FREE BONUS

. . . if you act now!

Yes, if you fill in and mail the Membership Application card today, you'll also get this Bonus Book, FREE!

TV TROUBLESHOOTER'S HANDBOOK

Revised Second Edition

A completely updated quick-reference source for solutions to hundreds of tough-dog troubles.

Regular List Price \$7.95

(for a total combined list price of \$53.80!)

tional Club Selection you purchase. For the small charge of only \$1.99, plus three (3) Certificates, you may select a book of your choice from a special list of quality books periodically sent to Members.

6. Prevents You From Missing New Books: The Club's FREE monthly *News* gives you advance notice of important new books . . . books vital to your continued advancement.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours . . . that it is possible to keep up with the literature published in your areas of interest . . . and to save substantially while so doing.

How the Club Works

Forthcoming selections are described in the FREE monthly *Club News*. Thus, you are among the first to know about, and to own if you desire, significant new books. You choose only the main or alternate selection you want (or advise if you wish no book at all) by means of a handy form and return envelope enclosed with the *News*. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway . . . without the substantial savings offered through Club Membership.

Limited Time Offer!

Here, then, is an interesting opportunity to enroll on a trial basis . . . to prove to yourself, in a short time, the advantages of belonging to Electronics Book Club. We urge you, if this unique offer is appealing, to act

promptly, for we've reserved only a limited number of books for new Members.

To start your Membership on these attractive terms, simply fill out and mail the postage-paid airmail card today. You will receive the three books of your choice for 10-day inspection.

SEND NO MONEY! If you are not delighted, return them within 10 days and your Trial Membership will be cancelled without cost or obligation. Electronics Book Club, Blue Ridge Summit, Pa. 17214.

Typical Savings Offered Club Members on Recent Selections

RCA Color TV Serv. Man's. Vols. 3 & 4	Ea. List Price \$8.95; Club Price \$5.95
CET License Handbook	List Price \$8.95; Club Price \$5.95
TV Bench Servicing Techniques	List Price \$7.95; Club Price \$4.95
Practical Test Instruments You Can Build	List Price \$7.95; Club Price \$4.95
Elec. Wiring & Lighting for Home/Office	List Price \$7.95; Club Price \$4.95
Modern Communications Switching Sys.	List Price \$17.95; Club Price \$13.95
Computer Technician's Handbook	List Price \$12.95; Club Price \$8.95
Color TV Trouble Factbook—2nd Ed.	List Price \$8.95; Club Price \$4.95
Solid-State Circuits Guidebook	List Price \$8.95; Club Price \$5.95
Installing TV & FM Antennas	List Price \$7.95; Club Price \$3.95
Understanding & Using the VOM & EVM	List Price \$7.95; Club Price \$4.95
Modern Applications of Linear IC's	List Price \$12.95; Club Price \$9.95
FM Stereo/Quad Recvr. Servicing Man'l	List Price \$7.95; Club Price \$4.95
Electronic Music Production	List Price \$7.95; Club Price \$3.95
Auto Stereo Service & Installation	List Price \$8.95; Club Price \$5.95
Getting Most out of Elec. Calculators	List Price \$7.95; Club Price \$4.95
Mobile Radio Handbook	List Price \$7.95; Club Price \$4.95
Elec. Test Equipment/How To Use It	List Price \$7.95; Club Price \$4.95
Indexed Guide To Modern Electr. Circs.	List Price \$7.95; Club Price \$4.95
Electronics For Shutterbugs	List Price \$8.95; Club Price \$5.95
Introduction to Medical Electronics	List Price \$9.95; Club Price \$6.95
Cassette Tape Recorders	List Price \$7.95; Club Price \$4.95
MATV Systems Handbook	List Price \$7.95; Club Price \$4.95
How to Repair Small Gasoline Engines	List Price \$8.95; Club Price \$4.95

SEND NO MONEY! Simply fill in and mail postage-paid Airmail card today!

CATV System Engineering -



Third Edition. Revised Third Edition of the accepted technical standard of the CATV industry. An expanded and revised version of the first and only authoritative book on planning, designing, and operating a CATV plant. Covers systems composed of uncorrelated components as well as fully integrated solid-state plants. Subjects covered include disadvantages of amplifier design concepts, high level distribution principles of cable powering, amplifier and system dynamic range, cascaded figure of merit, system operating levels, jumper cables, equalization and alignment, and a host of other vital subjects, including how to modernize older systems using the newest equipment available. 256 pps.

List Price \$12.95 • Order No. 298

FET Applications Handbook



This revised 2nd edition contains a wealth of data on the FET and its various applications in practical circuit designs, material prepared by some of the most capable engineers in the field. Early Chapters delve into current-voltage relationships, application areas, DC and AC amplifiers, voltage controlled attenuators, and limiter and chopper circuits. Additional Chapters deal with linear applications, chopper and switching circuits, integrated circuits and photo-FETs. Also FET oscillators, describing various types and the necessary biasing arrangements. Essential design data includes starting conditions, power output, frequency stability, and efficiency. 320 pps., 250 illus., 26 Chapters. Hardbound.

List Price \$14.95 • Order No. 240

Electronic Circuit Design Handbook



New Fourth Edition—A brand-new, enlarged edition of the ever popular circuit designer's "cookbook" now containing over 600 proven circuits, for all types of functions, selected from thousands on the basis of originality and practical application. Now you can have, at your fingertips, this carefully planned reference source of tried and tested circuits. Selected on the basis of their usefulness, this detailed compilation of practical design data is the answer to the need for an organized gathering of proved circuits... both basic and advanced designs that can easily serve as stepping stones to almost any kind of circuit you might want to build. 416 pps., 19 big sections, over 600 illus. 8 1/2" x 11". List Price \$17.95 Order No. T-101

Kwik-Fix™ TV Service Manual



By Forest Belt, all the data you need to speed color-TV diagnosis to the point where it's "Turn it on, check it out, and fix it up" just like that! Each of the 30 sections contains a circuit description, typical schematics, signal analysis, voltage charts, and waveforms—condensed into easy-to-use, step-by-step troubleshooting charts that will help solve almost any TV trouble in double-quick time. With typical photos and scope traces, this manual will lead you quickly from symptom to repair. Normal and abnormal waveforms, taken from representative TV receivers, pinpoint problems that might otherwise keep you guessing. 384 pps., hundreds of illus.

List Price \$8.95 • Order No. 611

Dictionary of Electronics



You'll find this huge volume extremely useful in whatever connection you have with electronics. This dictionary of electronic terms you will run across in your everyday reading, from alpha particles through zoom lens terms you need and use most often, including those found in radio, TV, communications, radar, electronic instrumentation, broadcasting, industrial electronics, etc. It provides full, complete and easily-understandable explanations of thousands of specific electronics terms (such as transistors, acoustic feedback, alpha particles, beat oscillator, final anode, electrostatic lens, nonlinear resistance, etc.). 420 pps., 487 illustrations. Hardbound.

List Price \$8.95 • Order No. 300

Practical Test Instruments You can build


Practical Test Instruments You Can Build



An arsenal of highly useful, economical, easy-to-build test equipment designed by the people who use it everyday. Selected for their general usefulness to the electronic and servicing professions, these projects are capable of being built and put to use in a single evening, and they make optimum use of inexpensive components. Project areas have been divided into these discrete sections: semiconductor testing devices; measuring volts, ohms, and rf watts; dip meters and wavemeters; and useful test and measurement circuits. Wherever your technical interest lies, you'll find ideal projects tailor-made to your own requirements. 204 pps., 157 illus. Hardbound.

List Price \$7.95 • Order No. 669

Understanding & Using the Oscilloscope

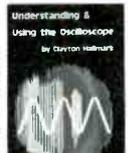

Using a scope is as easy as A-B-C, and this down-to-earth text shows how it's done. This excellent guidebook is designed especially for technicians who'd like to become more familiar with the most versatile piece of test equipment ever devised, and for the beginner who wants to get started in servicing the right way. It's packed with info on scopes of every type, with special emphasis on solid-state circuits. Describes basic functions, scope circuits, ac vs. dc inputs, differentiated and integrated waveforms, and outlines every conceivable electronic test you're likely to perform on any equipment... ever! 272 pps., 170 illus. Hardbound.

List Price \$7.95 • Order No. 664

Zenith Color TV Service Manual -- Vol. 3



Jam-packed with more information than ever before, this all-new Zenith color TV manual provides all the servicing data you'll ever need for these models: 14DC14, 15 15Z, 16 16Z; 14CC14 (and up); 18CC27, 29, and 30; 19DC11 and 12; 19DC19Z and 20; 20CC50 and 50Z; 23DC14; 25CC25, 50, and 55; 25DC58 in addition to the brand new 1974 17/19EC45; 25EC58 series just released. Contains complete alignment and service instructions, new-circuit descriptions, schematics, and complete test-point waveform photos—11 1/8" 13" full-size right-up-the-minute schematics! 180 pps., including 36-page Schematic-foldout section. Leatherette cover.

List Price \$7.95 • Order No. 668

Major Appliance Repair Guide



Everything you need to know to fix any major electrical appliance is contained in this comprehensive, up-to-date volume. The authors explain every step in great detail, and illustrate typical situations with detailed photos and drawings. Numerous troubleshooting charts help you pinpoint the cause of virtually any problem in a matter of minutes. Repair procedures are included for dishwashers, clothes washers, dryers, water heaters, garbage disposers, and ranges, using typical models and case-history data drawn from actual experience. In every case, the material is based on practical know-how, common sense reasoning, and techniques. 288 pps., over 260 illus. Hardbound.

List Price \$8.95 • Order No. 555

Industrial Electronics: Principles & Practice

INDUSTRIAL ELECTRONICS PRINCIPLES & PRACTICES

By Alfred Hahn

A comprehensive text providing an in-depth treatment of modern industrial control, processing and monitoring methods, including many of the latest innovations brought about by advances in solid-state electronics technology. You'll learn about the methods and devices used to automatically inspect, sort, and count, and about digital process control techniques that "tell" machines how to perform repetitive operations. Also covered are electronic heating, welding and machining devices, plus ultrasonic cleaning, liquid processing, and laser applications. 416 pps., 380 illus. Hardbound.

List Price \$8.95 • Order No. 583

Auto Stereo Service & Installation



An indispensable one-stop source of info (including how to get rid of interference) for all types of auto stereo equipment... plus detailed installation procedures for FM radios, 8-track cartridge units, and cassette players. Includes 48 complete schematics of 13 major manufacturers. Contains one of the most lucid descriptions of magnetic-tape theory ever published. The text on installation is very thorough and detailed—even to showing how to make a hole in carpeting; general maintenance covers the mechanical aspects—dial cord and lamp replacement, replacing controls, demagnetizing, tape splicing, etc. 252 pps., 245 illus. Hardbound.

List Price \$8.95 • Order No. 694

Commercial FCC License Handbook



A new and unique study guide and reference manual, combining theory and applications with up-to-date questions and answers for 1st, 2nd, and 3rd class radiotelephone license exams plus broadcast and radar endorsements. Everything you need to know is included—complete detailed answers to questions on any subject you may be asked when you take your exam. Numerous practical examples are used to describe the various principles you need to understand the exam questions. In each case, the author painstakingly explains the answers to questions on all subjects. Prepares you for any exam. 444 pps., 150 illustrations. Hardbound.

List Price \$9.95 • Order No. 582

Pictorial Guide to CB Radio Installation & Repair



A step-by-step approach to setting up a two-way radio in the home or car—the simple techniques outlined are equally applicable to commercial and ham systems. Complete guide to the proper installation, checkout, and maintenance of all types of modern transceivers and antennas, both mobile and fixed. Covers reducing TV interference, minimizing possible lightning damage, setting up a telephone-to-radio interconnection, and antenna setup and site selection. Shows, in pictures and text, how to optimize the coaxial line, tune the antenna, reduce cable length to increase antenna gain, etc. 256 pps. Hardbound.

List Price \$7.95 • Order No. 683

Handbook of Semiconductor Circuits



Contains 124 examples of standard transistor circuits, complete with operational data for amplifiers, oscillators, logic and switching circuits, power supplies, and various nonlinear circuits. The broad range of circuits included were selected on the basis of application and practicality. A design philosophy section is included with each group of circuits, thereby providing a basis for understanding circuits other than those selected as examples. This is a collection of practical circuits which have wide application. Each circuit description includes data concerning any unique design or operational data. Hundreds of illustrations and diagrams. 448 pps., 6" x 9". Hardbound.

List Price \$8.95 • Order No. G-30

Acoustic Techniques for Home & Studio



Complete coverage of a neglected subject! Two related areas—audio and acoustics—are neatly tied together in this single volume aimed for the hi-fi buff as well as the professional broadcaster and recording studio technician. If you can handle simple algebra and read a graph, you'll be at ease with this book's design treatment for assuring maximum fidelity—not at the loudspeaker, but at the ear, where good sound really means something. With proper application of the techniques and tests outlined, you can determine what your room acoustics lack and what to do to improve them—at minimum cost. 224 pps., 168 illus. Hardbound.

List Price \$7.95 • Order No. 646

Ten-Minute Test Techniques for PC Servicing



This new Art Margolis "classic" is a practical, easy-to-follow PC board repair guide with scores of shortcuts for the beginner or pro. You'll learn how printed-circuit boards are made and how components are mounted; replacement techniques for damaged boards; soldering and desoldering; plus the tools and chemicals needed. Reveals unique tricks used by the pros to remove and replace components without damaging fragile printed boards. The author delves into "flow chart" servicing and shows how these troubleshooting roadmaps can cut servicing time. 216 pps., 114 illus., 16-page Schematic Section for Admiral M20 and Philco 2CY91. Hardbound.

List Price \$7.95 • Order No. 698

AN EXTRAORDINARY OFFER...

... for more details circle 105 on Reader Service Card

um and silicon transistors and list them on a small chart pasted to the side of your VOM.

Two other notes of caution: 1) Check the voltage between the test leads of your ohmmeter. Some ohmmeters have 6 or more volts between their test leads in the high-ohms ranges. This amount of voltage can damage some "delicate" transistor junctions. 2) Check the polarity of your ohmmeter test leads. Some multimeters are designed so that the polarity of their input is reversed in the ohms function; the positive test lead becomes negative and the negative becomes positive.

IN-CIRCUIT TESTS

As stated previously, the very first step in testing semiconductors should be in-circuit voltage checks. When this is not possible, as in the case of power supply short circuits, or when the collector voltage is a high voltage at a high frequency (flyback circuits, etc.), ohmmeter checks should be made first.

In a normally operating circuit, there should be approximately 0.6 volts across the emitter-to-base junction of a silicon transistor and about 0.2 volts if the transistor is a germanium type. If this voltage is incorrect, do not assume that the transistor is defective until you have checked the various supply voltages. Often a voltage regulator or rectifier failure or a short elsewhere on the same supply line drastically alters supply voltages. For this reason, it is a good practice to always check supply voltages first.

Figs. 4, 5 and 6 illustrate the voltage conditions which will be present as a result of various defects in a common-emitter circuit equipped with an NPN transistor. (The same circuit equipped with a PNP transistor would display the same symptoms.) The common-emitter circuit was chosen as an example because it is used more often than the other two basic configurations. Although a few of the defects in Figs. 4, 5 and 6 will cause different voltage symptoms in common-base and common-collector circuits or if different bias and stabilizing networks are used, the causes and symptoms in Figs. 4, 5 and 6 can be "transposed" to these circuit configurations by using the

following general diagnostic guidelines:

- If the base-to-emitter junction does *not* have the correct forward-bias (about .2 volts for germanium and .6 volts for silicon) and there is *no* evidence of current flow in the collector-to-emitter circuit (lack of voltage drop across resistors in *series* with the collector-to-emitter circuit and the supply source), check for defects in the base and emitter circuits.

- If the base-to-emitter junction *is* correctly forward biased but there is *no* evidence of current flow in the collector-emitter circuit, check for an *open* in the collector circuit.

- If the base-to-emitter junction does *not* have correct forward bias and there *is* evidence of current flow in the collector-to-emitter circuit, check for a *short* or *leakage* in the collector-to-emitter circuit.

The preceding guidelines presume that supply voltages have been checked and are normal.

Some technicians short the base-to-emitter leads and look for a reduction in the collector current as an indication of a good device. There are some pitfalls in this method, not the least of which is the possibility of destroying the transistor if you short the wrong leads, and the ever present hazard of your hand slipping and shorting to adjacent circuits. For such tests, I prefer to use an insulated mini-clip with extendable hooks which can be clipped right onto the transistor leads with little danger of shorting, even in tight spots.

Occasionally, you will run across a circuit in which the *bias* is incorrect but everything else in the set is normal with the transistor removed, and the transistor itself checks normal out of the set. In such cases, look for oscillation. An oscillating IF stage is common when someone has "tweaked" an alignment adjustment. Sometimes, other stages will oscillate at any frequency from audio to UHF if a bypass capacitor in a decoupling circuit opens. Use your scope and low capacitance probe to quickly spot such oscillations.

In many sets, several transistors are DC coupled in "chains." If one transistor is defective or the bias of a stage at the front of the chain is incorrect, the entire chain will display abnormal voltages. In such cases, you can save time by removing the transistors one at a time, for individual testing. If you find a defective one do not stop. Continue testing until you have examined the entire chain. Such circuits often have more than one defective transistor, because one failure triggers more.

Some modern circuits use *Darlington* transistors, which are really two cascaded transistors in one package, as shown in Fig. 7. Because they have three terminals, as any other transistor, it is rather mystifying to find about 1.3 volts between base and emitter. In Fig. 7 you will see that there are two emitter-to-base junctions in series between the base terminal and emitter terminal, which accounts for the base-to-emitter voltage being *twice* that of the usual bipolar device.

A shorted power transistor in an audio output stage will cause blown fuses. An open device might not be so obvious because one half of a push-pull, transformer-coupled stage will still operate, although the audio will be distorted. OTL (output transformerless) complementary symmetry stages, on the other hand, do not function at all with one transistor defective.

Defective IF or RF stages might not completely eliminate a *strong local* signal, just as in vacuum tube-equipped circuits. There is enough capacitive feedthrough in a "dead" transistor to produce a degraded, snowy picture or, in the case of AM or FM radios, a weakened or noisy signal.


In resistance-coupled stages, certain defects will cause the base and collector voltages to shift significantly either above or below normal. However, in transformer-coupled RF, IF or AF stages there might not be sufficient load resistance to cause a noticeable DC voltage drop. In such cases, the voltage drop across the emitter resistor can be used as a quick and convenient means for calculating the transistor collector-to-emitter current. ■

Your VTVM is obsolete!

This may sound like a harsh claim, but it's true. Thousands of TV technicians are using instruments designed in the 1950's to troubleshoot circuits designed in the 1970's.

And now, most color TV's have solid state circuits. So use of out-of-date test equipment just compounds the problem.

The generation gap has grown too big.

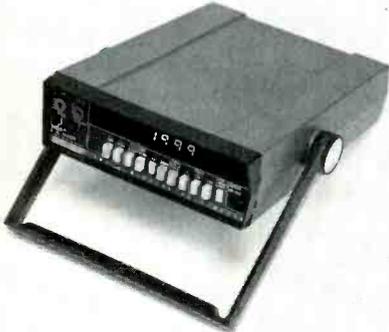

The Fluke 8000A 3 1/2 digit multimeter

Solid state calls for new performance standards.

Your "old fashioned" test equipment simply doesn't measure up to today's requirements. For example, the typical VTVM gives you 5% accuracy and 2% resolution. In the old days, that was good enough. Not so today.

Now you need an instrument to look at the voltages at each pin of an IC with sufficient accuracy and resolution to determine proper IC operation.


For example, a reading of "around 2.8 volts" is no longer sufficient. You must be able to distinguish between 2.80 and 2.82 volts.

You need a test instrument that gives you 0.1 ohm resolution so you can reliably measure resistance of switch contacts, circuit breakers, and low value resistors.

To do all this and more, you need the superior capabilities of the Fluke 8000A 3 1/2 digit multimeter.

An instrument designed specifically for testing solid state equipment.

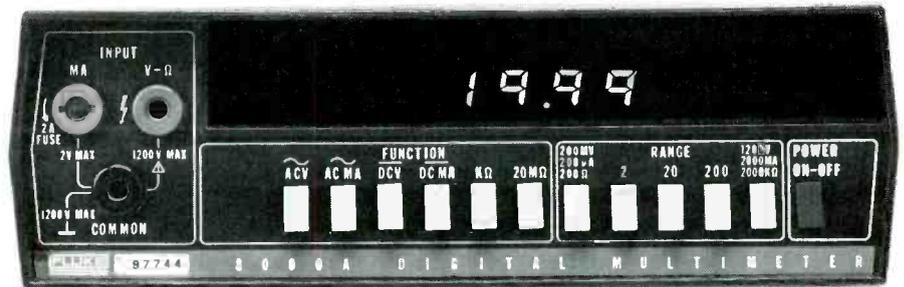The 8000A gives you up to 50 times the accuracy and 20 times the resolution of a VTVM, so you can measure the various voltage levels in a solid state chassis with absolute confidence.



Resolution is 100 microvolts, 100 nanoamps and 100 milliohms

You get the sensitivity you need for low level dc measurements. The 200 millivolt range with 100 microvolt resolution tells you *exactly* what your values are.

The 8000A has an AC frequency response from 45 Hz to 20 KHz and, with accessory probes, to 500 megahertz. Resistance measuring capability ranges from 100 milliohms to 20 megohms. It offers a 15°C to 35°C accuracy temperature span. And a 1-year accuracy time span, meaning it seldom needs calibration.

Unlike other DMM's the 8000A has fast response time — 3 readings a second. And the bright, digital readout means that no interpolation is necessary.

The 8000A measures high voltages, too.

Our 8000A is designed to answer *all* the needs of an electronic service technician.

One very important (and talked about!) safety requirement is that the picture tube anode voltage must not exceed the maximum specified by the manufacturer. Our 8000A has an optional high voltage probe that gives you guaranteed accuracy of 1% at 25,000 volts. The probe also extends the capability of the 8000A to 40,000 volts to measure the high voltage in the new 32,000 volt chassis.

No other DMM's offer this feature.



High voltage probe accessory gives you 1% accuracy at 25,000 volts

Get the most up-to-date instrument available.

Don't be caught in the typical trap. Many electronic service shops don't really update their equipment when they decide to update. Switching to a TVM or a FET voltmeter doesn't really give you the accuracy and resolution you need today, or for that matter, tomorrow.

But with the 8000A on hand, you know you have a *true* solid state testing device . . . an instrument that can do the job the way it should be done.



Carry it anywhere. Use it on line or rechargeable battery power. Note the conveniently mounted specs on the bottom decal. They're always with you.

The 8000A comes from Fluke, one of the largest instrument companies in the U.S.

It costs just \$299 (\$40 more with HV probe).* And it is far and away the largest selling, most rugged and reliable 3 1/2 digit multimeter in the world.

*Domestic only.

For data out today, dial our toll-free hotline, 800-426-0361

John Fluke Mfg. Co., Inc., P.O. Box 7428, Seattle, WA 98133

. . . for more details circle 110 on Reader Service Card



Profitable and Competitive Pricing of Home Service Calls

By J. W. Phipps

How to use your hourly service labor rate to compute the flat rate you should charge for home calls

■ Profitable pricing of both in-shop and in-home servicing requires that you determine precisely what it costs you to produce a *manhour* of service labor. Regardless of the particular *method* of service labor pricing you use—whether it is flat-rate (by the

job or function), hourly (actual time involved), or some combination of the two—the *basis* of your pricing structure is the *service labor manhour* and what it *costs you* to produce and sell it. This applies to both in-shop and in-home servicing.

TABLE 1

COSTS OF PRODUCING SERVICE LABOR	
TECHNICIAN WAGES & PAYROLL EXPENSES	
Technician Wages	\$44,720
Employer Social Security Contribution	1,230
Employer Unemployment Contribution	895
Employer Life & Medical Insurance Contribution	1,200
Employer Pension Contribution	474
	\$48,519
GENERAL AND ADMINISTRATIVE EXPENSES	
Secretary/Bookkeeper Wages	\$ 8,320
Employer Social Security Contribution	229
Employer Unemployment Contribution	166
Employer Life & Medical Insurance Contribution	300
Employer Pension Contribution	100
Building Lease	3,600
Utilities (including heating & air conditioning)	1,500
Telephone	500
Office Equipment Depreciation	100
Office Supplies	600
Advertising Expenses	1,000
Legal/Auditor Fees	400
Insurance (All other than employee)	800
Taxes (all other than Fed. & State income tax withholding)	800
Interest & Bank Charges	800
Misc. (Assoc. dues, subscriptions, license fees, etc.)	300
	\$19,515
OPERATING EXPENSES	
Owner's Salary	\$18,000
Social Security Contribution	990
Unemployment Contribution	360
Life & Medical Insurance Premiums	400
Pension Premium	300
Vehicle Operating & Maintenance Expenses	1,800
Vehicle Depreciation	2,400
Shop Equipment Depreciation	1,000
Expendable Items, Shop (cleaners, solder, tape, etc.)	400
Service Literature	100
	\$25,750
TOTAL SERVICE LABOR BUSINESS COSTS	\$93,784

The procedure for computing the hourly service labor rate you must charge to recover all business expenses and realize a specific margin of profit was outlined last month in an article titled *Profitable and Competitive Pricing of Service Labor*. This procedure involves the following steps:

- 1) Computation of the total expenses incurred in the operation of your business (Table 1)*
- 2) Computation of desired profit (Table 2)*
- 3) Computation of gross service labor income required to recover expenses and produce the desired profit (Table 2)*
- 4) Computation of the total manhours which will be available for *direct* billing to customers (Table 3)*
- 5) Computation of hourly service labor rate by dividing the required service labor income by the number of manhours available for direct billing to customers (Table 4)*.

The resultant hourly service labor rate should serve as a basis for *both* in-shop and in-home servicing. The reason for this is that many of the expenses incurred in the operation of your business are "shared" by both in-shop and in-home servicing and cannot be accurately apportioned between the two without the use of a very detailed and complex cost accounting system, which, for most shops, would be so inconvenient and time consuming that it would be self-defeating. For example, although expenses such as technician wages and payroll expenses, vehicle depreciation and vehicle operating and maintenance usually can be accurately apportioned between in-shop and in-home servicing, others such as building lease, telephone, office equipment and test instrument depreciation usually cannot be accurately apportioned between the two types of servicing. Therefore, unless you already have a *proven* cost accounting system which permits you to apportion shared expenses with an acceptable degree of accuracy and without consuming too much of your time and that of your technicians, you probably should combine *all* expenses related to service labor and compute a single service labor hourly rate based on the *combined* expenses.

APPLYING YOUR HOURLY SERVICE LABOR RATE TO IN-HOME SERVICING

After you have computed the hourly service labor rate you must charge to recover *all* business expenses and realize a specific margin of profit, you are ready to compute what *you* must charge for a home service call.

There are at least three tried-and-proven methods for flat-rate pricing of home service calls:

1) You can charge a flat rate which covers the time it takes you or your technicians to travel to the customer's door plus a specific increment of service time in the home (usually 30 minutes). Time consumed in the home in excess of the specified increment allowed by the flat-rate charge is charged the customer on an hourly basis. For example, if the technician spends an hour in the home and your flat-rate home-call charge includes only the first 30 minutes, the additional 30 minutes is charged the customer by multiplying the shop hourly service labor rate by .5 (one half hour).

2) You can flat-rate only the time it takes the technician to travel to the customer's front door and then charge *all* service labor time in the home on a straight hourly basis.

3) You can flat-rate the technician's travel time and use it as your home-call charge and then charge the customer separate flat rates for each separate function the technicians perform in the home.

You can adopt any one of the preceding methods and make it work for you if the *basis* of all three methods—*your hourly service labor rate*—accurately reflects *your* business costs and the margin of profit *you* desire.

The only other factor which will significantly affect the profitability of your home-call operation but which is not directly accounted for in your hourly service labor rate is the *travel time* between service calls. Profitable and competitive flat-rate pricing of home service calls requires that you be able to predict, with reasonable accuracy, the amount of time *typically* required for your technicians to travel from one call to the next. (Your hourly service labor rate tells you how much you must *charge* for this time, but it does not tell you *how much*

time is involved.) There are two generally accepted methods which you can use to determine how much travel time you should "build into" your flat-rate home-call charge.

The most accurate method is called *averaging*. During a period of time (the longer, the more accurate), each home-call technician maintains a log on which he records the times he leaves one call and arrives at another. At the end of the sampling period, the travel times recorded on the logs are totaled and then divided by the number of calls made. This tells you what the *average* travel time per call was during the period. You then multiply the average travel time (in increments of an hour) by your hourly service labor rate. For example, assume that the average travel time between service calls for your technicians is 20 minutes (.33 of an hour) and your hourly service labor rate is \$20.00.

Your minimum flat-rate for home service call travel then would be .33 x \$20, or \$6.60. If your home service call rate includes 30 minutes of service time in the home, you add to the \$6.60 "travel charge" an amount equal to .5 (one half hour) x your hourly service labor rate, which in this example is .5 x \$20, or \$10.00. The total of the two produces a home service call charge of \$16.60.

The other method of computing travel time is to determine the *maximum*, or worst-case, time your technicians would spend traveling from the geographical center of the area in which you offer service to the farthest point in the area. You then multiply your hourly service labor rate by this hourly increment of travel time.

The *averaging* method usually produces a more realistic and more competitive home service call charge

TABLE 2

ANNUAL SERVICE LABOR RECEIPTS REQUIRED FOR DESIRED PROFIT	
1) TOTAL SERVICE LABOR COSTS (TABLE 1)	\$93,784
2) DESIRED PROFIT EQUALS 20% GROSS SERVICE LABOR INCOME	
3) TOTAL SERVICE LABOR COSTS (TABLE 1) = DESIRED PROFIT, or	
4	
$\frac{\$93,784}{4} = \$23,446$	
4) DESIRED PROFIT + TOTAL SERVICE LABOR COSTS = REQUIRED ANNUAL GROSS SERVICE LABOR INCOME, or	
$\$23,446 + \$93,784 = \$117,230$	

TABLE 3

SERVICE LABOR MANHOURS AVAILABLE FOR DIRECT BILLING TO CUSTOMERS	
TOTAL SERVICE LABOR HOURS PER YEAR PER TECHNICIAN	2080 Hrs.
NUMBER OF FULL-TIME TECHNICIANS	× 4
TOTAL SERVICE LABOR MANHOURS PER YEAR	8320 Hrs.
MANHOURS DEDUCTED FOR PAID VACATIONS & HOLIDAYS	
Vacations (2 wks. per year per technician)	320 Hrs.
Holidays (5 days per year per technician)	160 Hrs.
TOTAL	480 Hrs.
Service Labor Manhours Per Year	8320 Hrs.
Service Labor Manhours Deducted for Vacations & Holidays	— 480 Hrs.
TOTAL Manhours Technicians on Job	7840 Hrs.
LABOR Recovery Rate (80%)	× .80
TOTAL SALEABLE MANHOURS	6272 Hrs.

TABLE 4

SERVICE LABOR HOURLY RATE REQUIRED	
SERVICE LABOR INCOME REQUIRED (TABLE 2)	\$117,230
TOTAL SALEABLE MANHOURS (TABLE 3)	6272 Hrs.
	$\frac{\$117,230}{6272 \text{ Hrs.}} = \18.70 per Hr.

than that produced by the *worst-case* method. For this reason, most shop owners prefer to use the averaging method for computing the "travel portion" of their home service call charge. The worst-case travel time then is used only as a reference against which to compare the effectiveness of their call routing and dispatching techniques, as described later.

Regardless of which method you use to compute the travel time between home service calls, it will be valid only if you establish a definite geographical area for the travel time study, and apply the resultant flat-rate home call charge only to calls made within that area. Because calls beyond this area will require additional travel time, the charge for such calls should be your flat-rate charge *plus* an extra charge based on the miles (or increments of a mile) the call is located outside your normal operating area.

PERIODIC EVALUATION OF YOUR HOME CALL RATE

Because a significant portion of your cost of producing a home ser-


vice call is attributable directly to *travel time* between calls, periodic re-evaluation of average travel time is essential for continued profitability of your home-call servicing. For this reason, it is recommended that you have your home-call technicians maintain a daily travel log on which is recorded the exact time they *leave* one home and *arrive* at the next. The log should clearly reveal the travel time between calls, the number of calls, and the time spent in the home. Weekly or monthly assessment of the logs will tell you whether or not the average travel time between calls is exceeding the average time on which your home-call charge is based. If it is, you either will have to improve your routing and dispatching techniques to reduce the travel time or you will have to recompute your home-call charge so that it is based on the *increased* average travel time. As a general rule of thumb, anytime your *average* travel time between calls exceeds one half your worst-case travel time, you should improve your routing and dispatching techniques to reduce it.

Another method of evaluating the validity of your home-call pricing structure is to: 1) Add up the travel and in-home time recorded on your technicians' travel logs during a specific period, 2) multiply this total time by your hourly service labor rate, and then 3) compare the resultant total with the gross income (minus parts income) you actually received from home call servicing during the period. If the total arrived at in step 2 does not equal or exceed the actual "service labor" income received from home-call servicing during the period, either your hourly service labor rate or your home-call rate (or both) is not adequate to recover all service-labor expenses and produce the profit you desire. You then should recompute both your hourly service labor rate and your home-call rate. ■


IN MARCH: Incentive Pay Programs for Your Technicians.

**The specific amounts listed in these tables are intended merely as examples and are not representative of those incurred in any particular business.*

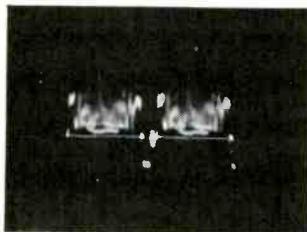
RCA's new 3-inch scope...an entire servicing system for only \$229.*



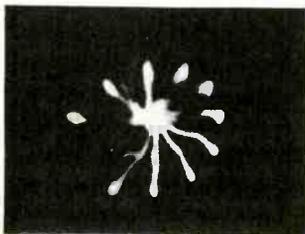
1. It's an 8 MHz general-purpose scope. Typical composite TV video signal.



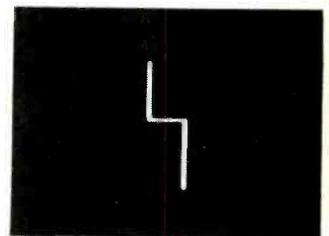3. It's a Vectorscope for color TV AFPC alignment. Color bar generator used for test signal.



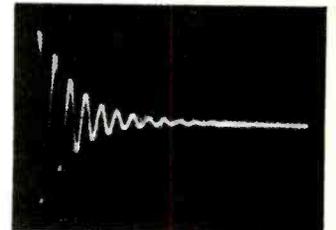2. It's a "Quicktracer" Transistor/Diode and Component Tester. Typical junction waveform.



4. It's a "ringing" tester for coils, yokes, transformers. Typical ringing test pattern.

5. It includes the WG-400A Direct/Low-Capacitance Switch Probe and Cable with BNC type connector, and a special "Quicktracer" probe.

*Optional price


For fast delivery and full information on the new WO-33B, contact any one of the more than 1,000 RCA Distributors worldwide.

Or write: RCA Electronic Instruments Headquarters, Harrison, N.J. 07029.

Specialists demand the best tools of their trade.

RCA Electronic Instruments

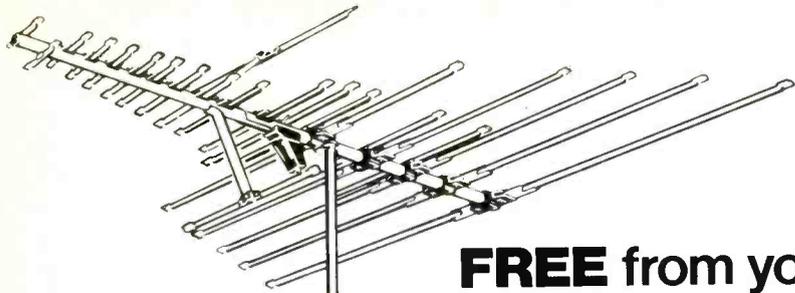... for more details circle 125 on Reader Service Card



FREE from your Winegard distributor:
New 'BIZ BOOMER UPPER KIT'
gives you 15 ways to put more
ring in your register...
more profit in your picture in '75.

Antenna sales slipping? Profits sliding? We can give you some timely, tested, proved effective help. A special Biz Boomer-Upper Kit with 15 sales-getter ideas and the materials you need to put 'em in action.

The kit's yours at no cost from your Winegard distributor. Designed so that *together* you can launch a planned program to sell replacements for all those tired old weather-beaten or damaged an-

tennas on homes in your area.

In today's competitive climate, this could be the extra promotion power you need to push profits up to—or ahead of last year's. Definitely, an offer you shouldn't refuse.

Not yet in the antenna business? There's plenty of potential going unsold right now. And your Winegard distributor can help you cash in. Why not contact him—today.



WINEGARD
TELEVISION SYSTEMS

3000 Kirkwood, Burlington, Iowa 52601



New in Color TV for 1975—Part 5

By Joseph Zauhar

Continuation of a series which analyzes the new and significantly changed circuits in 1975 color TV receivers. This month we will review RCA's T-Line Series chassis.

■ Six chassis are employed in RCA's color TV line: The CTC58, 68, 71, and 72 are all-solid-state chassis. Two continued hybrid chassis, the CTC51 and CTC53, manufactured prior to the transition of RCA to an entirely solid-state line, are used in the 14-inch and 18-inch (measured diagonally) screen sizes.

The XL-100 chassis series used in the new line have many common features: modular construction, a MOSFET mixer used in the VHF tuner, negative matrix picture tube and screen temperature setup to 6500° Kelvin, rather than the 9300° K used previously.

CTC68 CHASSIS

The CTC68 chassis was first introduced in the RCA S-Line series of color chassis but many refinements in its design have been made. The design changes include new, but compatible, audio output and kine driver modules, elimination of the standby filament power consumption, an improved tuner, digital channel indication in some models, and a different remote control system in some models.

VHF Tuner

The two-transistor, "cascode-type" mixer that was used previously in the KRK205 tuner, employed in the early S-Line chassis has been replaced by a MOSFET device using a similar circuit configuration. The KRK211 tuner shown in Fig. 1 uses a dual-gate MOSFET mixer

which provides high input impedance, a good noise figure, and low susceptibility to cross-modulation.

Low Voltage Power Supply

To conserve energy, the "Instant-Pic" has been eliminated from all T-Line color TV receivers.

A few early-production chassis will have the standby filament transformer that was used in S-Line chassis, but the wiring has been changed as shown in Fig. 2.

Two slightly different power transformer circuits are used in the CTC68 chassis. In some early production chassis the "Instant-Pic" feature is eliminated by changing the primary lead at the standby filament transformer (T104) to the off side of the line switch and the transformer is energized only when the on/off switch is switched on. In the majority of the chassis, the new design power transformer (T103) is used, providing the 6.3 volt source for the picture tube filament and transformer T104 is eliminated.

If either transformer is replaced in chassis which have both be sure to maintain the correct phasing of the filament winding (following the color coding). If the winding connections of either transformer is reversed, the two filament voltages will be out of phase and the *on* filament voltage will drop to about four volts,

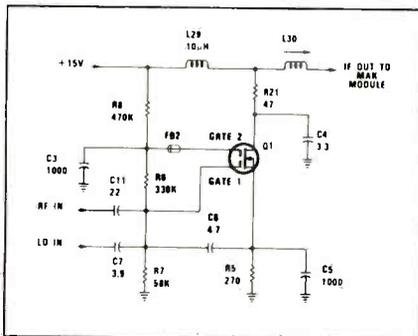


Fig. 1—The two-transistor, "cascode-type" VHF mixer has been replaced with a dual-gate MOSFET mixer. Courtesy of RCA.

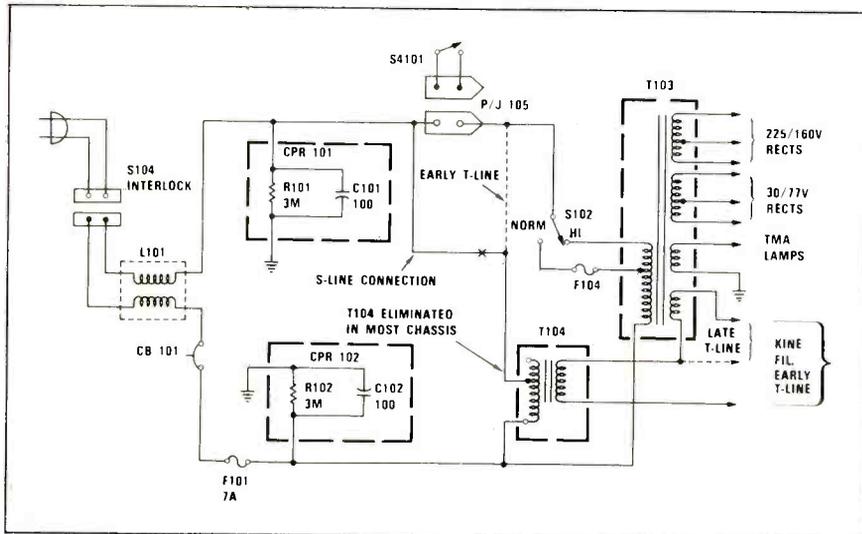


Fig. 2—Schematic diagram showing the changes made in the power supply employed in the CTC68 color TV chassis. Courtesy of RCA.

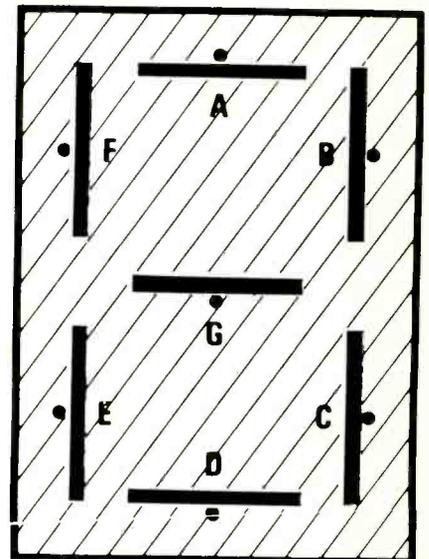


Fig. 3—The simplified illustration shows how the digits zero through nine can be formed by illuminating various sections of the seven-segment display forming channel numbers. Courtesy of RCA.

producing a symptom resembling a low-emission picture tube.

Digital Channel Indication

Various T-Line models using the CTC68 chassis have digital channel indication by using seven-segment, gas-discharge lamps, indicating both VHF and UHF channel numbers. A separate pair of neon lamps are used to indicate VHF or UHF operation.

Digits from zero through nine can be formed by illuminating various sections of the seven-segment display Fig. 3. When a particular cathode of a gas-filled indicator lamp is energized, it glows to make that segment visible and the numeral 8 is formed by energizing all seven segments.

A simple switch is shown in Fig. 4, with contacts connected to illuminate sections B and C of the lamp; the B+ input, which is common to all elements (anode connection), is supplied through a dropping resistor to the indicator lamp unit. The cathode elements B and C within the lamp are connected to ground through the switch contacts, energizing them and forming the numeral one.

Proper indication of all VHF and UHF channels requires the use of two indicator lamps encased in the same assembly and are labeled "tens" for the left-side indicator, and "units" for the right-side indicator.

UHF Indicating System

Shown in Fig. 5 is the Units section of a simplified UHF Indicating System which is an equivalent switch circuit, providing UHF channel indication. If a ground is connected to the lamp segments B and C through the isolation diodes B and C, diode CR6202 and switch S4002 we will get a numeral "1." In this position all other contacts of the switch are in the open position.

The "tens" switch and diode assembly is not shown but it is basically the same as the "units" section. Because of the VHF switching contact sequence, isolation diodes are only required for the B and C segments. The "tens" switch also uses diode CR6202 and switch S4002 to complete its path to ground in the UHF mode. This connection is indicated in the schematic by the

"common" line on the right side of the schematic.

Switch S4002 is located on the VHF tuner shaft and disconnects the common ground connections from the UHF indicator switches for VHF reception. It also operates the two neon lamps for UHF or VHF indication.

The UHF switch assembly consists of two rotating discs, each in contact with an eight-contact wiper assembly (one common and seven switched leads).

VHF Indicating System

The operation of the VHF channel indicator switch is similar to the "units" section of the UHF switch, and seven of its output leads are

connected to the "units" lamp for number indication of channels 2 through 9. The "common" side of the VHF switch (Fig. 6) connects directly to ground, and has eight switched contacts. The eighth switched lead is connected through isolating diodes to the A and B segments of the "tens" lamp. The addition of this eighth contact to the switch simplifies the system, and eliminates the need for a separate VHF "tens" switch. All contacts are open in the UHF position.

VHF/UHF Mode Indicators

The VHF/UHF Mode Indicators employ a simplified system of indication. The VHF or UHF functions operate in conjunction with switch

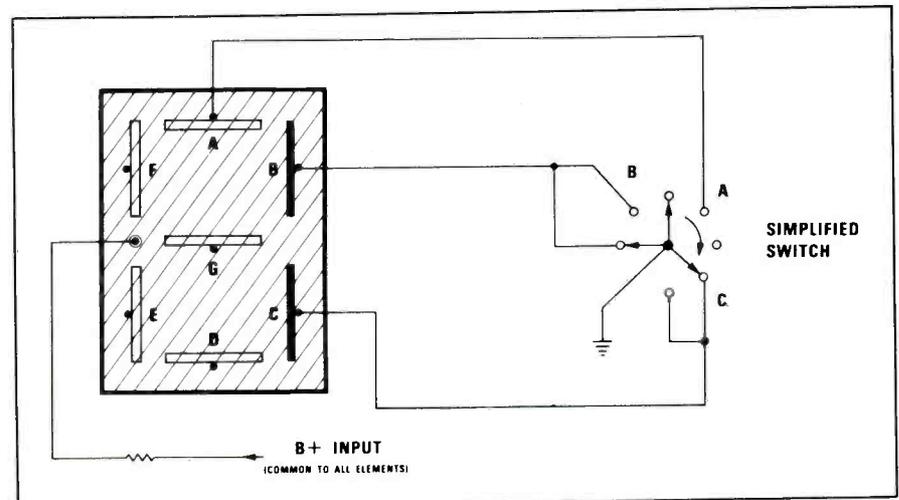


Fig. 4—A simplified indicator switch, with contacts connected to illuminate sections B and C of the lamp. Courtesy of RCA.

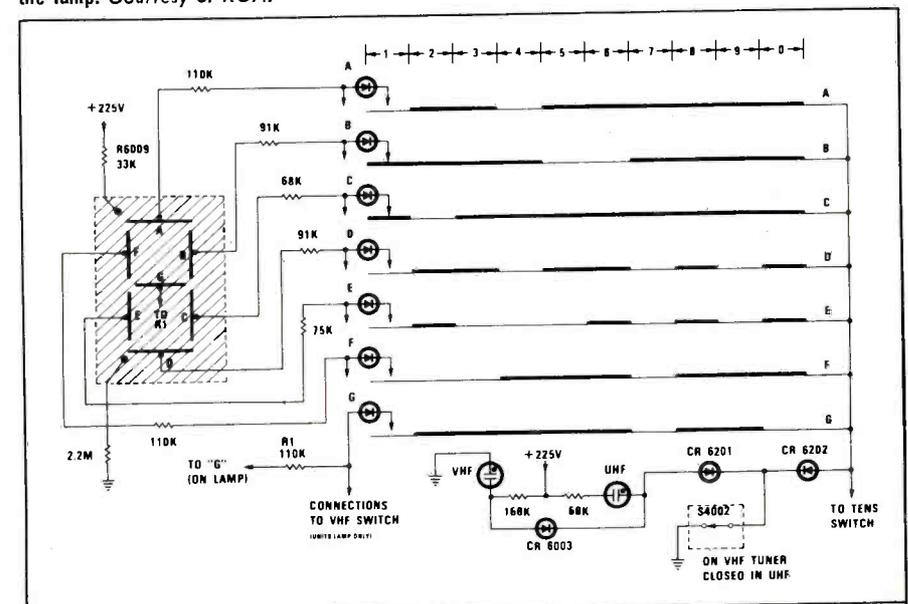


Fig. 5—Simplified illustrations showing the Units section of the UHF Indicating System. Courtesy of RCA.

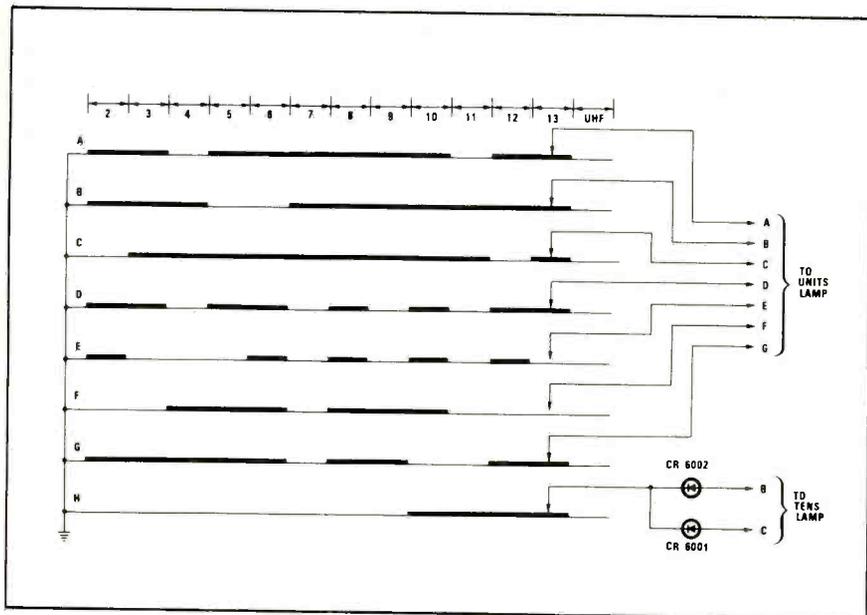


Fig. 6—Simplified schematic diagram showing the VHF Channel Indicating System. It is similar to the units section of the UHF switch. Courtesy of RCA.

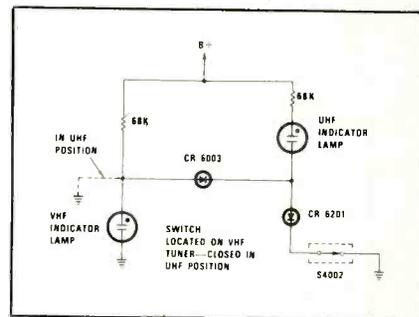


Fig. 7—Simplified schematic diagram showing the separate pair of neon lamps used to indicate VHF or UHF reception. Courtesy of RCA.

turn connection is available to diode CR6201.

CTC58 CHASSIS

Two types of the carry-over CTC58 chassis will continue in the T-Line Series for 1975. The chassis will be employed in 21- or 25-inch (measured diagonally) console and table model TV sets.

Both chassis versions are electrically identical except for changes in the section of the power transformer circuit supplying the picture tube filament voltage. This change was made because the Instant-Pic feature was eliminated.

Another significant change made in the CTC58 chassis is the removal of the ACM IV switch, but two of the AccuMatic B-Y phase angle change and the B-Y demodulator gain change functions have been retained. These functions effectively provide the optimum color demodulator characteristics of the ACM IV system used in other XL-100 color chassis, with the CTC58 chassis changes noted.

In the CTC58L and N chassis, removal of the "A" section of the ACM IV switch effectively turns on the B-Y phase shift circuit on the MAE001B module.

Removal of the "B" section of the switch, in conjunction with the new value of R315, adjusts the kine drive characteristics to yield the reduced B-Y demodulator output—as though the ACM function were turned on.

The tuners used with the CTC58 chassis will include the KRK199 VHF and KRK207 UHF units.

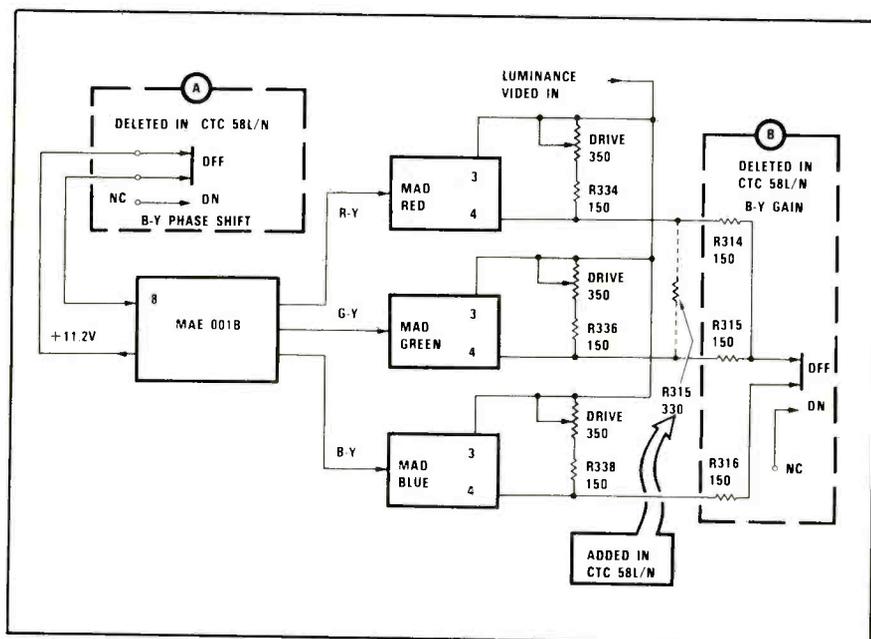


Fig. 8—Partial schematic of the ACM IV circuit used in other XL-100 color TV chassis, with the CTC58 chassis changes noted. Courtesy of RCA.

S4002 which is found on the VHF tuner. To indicate VHF or UHF reception a separate pair of neon lamps are used as shown in the simplified schematic diagram Fig. 7. The VHF/UHF Indicator Lamp Switching is shown in the UHF position. Switch S4002 is closed, completing a path from the cathode of diode CR6201 to ground. The circuit is completed to illuminate the UHF indicator lamp through the 68K resistor to B+.

The dotted line connection to ground shows the condition of the VHF lamp when in the UHF position and diode CR6003 is conducting, therefore, both sides of the VHF lamp are grounded.

As the VHF tuner is rotated from the UHF position, switch S4002 opens, and the two diodes switch off, and the ground connection is removed from the high side of the VHF indicator lamp, permitting it to illuminate. The UHF lamp is defeated because no ground re-

CTC71 CHASSIS

The CTC71 chassis is continued in the T-Line for 1975. This chassis will be used in several non-remote table models featuring a 19-inch (measured diagonally) screen.

The PW300 signal circuit board uses the same module complement as that of other current XL-100 chassis. The MAC002A Chroma-1 module has been superseded by the new MAC002B module, employing an advanced phase-locked-loop IC for the 3.58 MHz subcarrier regeneration. It is a direct replacement for the earlier "A" version. This module is common to all 1975 XL-100 chassis.

The horizontal-deflection system uses the transistorized sweep circuits first introduced in the CTC60 chassis. This chassis develops 27 kv of high voltage through a silicon tripler, the horizontal-deflection system is powered from a regulated 125-volt source and overload protected by an integral current-limiter circuit.

In comparison to its predecessor CTC60, most of the hold-down circuitry is contained on the MAH004 horizontal-oscillator module, rather than on the PW400 deflection board.

The vertical deflection system in the CTC71 uses the familiar MAG001 module and chassis-mounted vertical output transistors.

The tuners used in this is MOSFET mixer KRK199 VHF tuner and the digital-indicator KRK-207, 70-detent UHF tuner. Accu-Matic IV, AFT, and extended life neon pilot lamps are used in color TV sets employing the CTC71 chassis.

CTC72 CHASSIS

Three different versions of the CTC72 introduced in March and June will be used with portable and table model color TV receivers. The three types include the CTC72B which is used in non-remote 15-inch (measured diagonally) TV sets, and

the CTC72N for non-remote 17-inch (diagonal) screen size TV sets.

All TV models introduced in March featured a negative-matrix precision in-line (AccuLine) color picture tube, digital UHF tuning, and AFT.

In June, a remote-control 17-inch (measured diagonally) TV set, Model ET396R, was introduced. This chassis includes all of the above features plus remote control functions for channel and volume change and on/off.

The remote control used in the CTC72R chassis is the familiar two-function type, which remotely controls a 20-detent channel-selection system used previously, and a volume-stepper circuit which allows three preset volume steps and "off."

The CTC72 chassis is electrically similar to the CTC62 that it replaces, only the Instant-Pic feature has been eliminated, requiring a few minor changes in the power switching circuit. ■

Let us send you 33 proven ways to conserve energy in your business

We would like to tell you how Energy Management can help maintain your company's profitability. Send for your "33 Ways" booklet and we will send you something else: "How to Start an Energy Management Program."

To: U.S. Department
of Commerce
Office of Energy Programs
Washington, D.C. 20230

Please send me your two free booklets on "33 Ways to Conserve Energy" and "How to Start An Energy Management Program."

Name _____


Title _____

Company _____

Address _____

City _____ State _____ ZIP _____

Type of Business _____

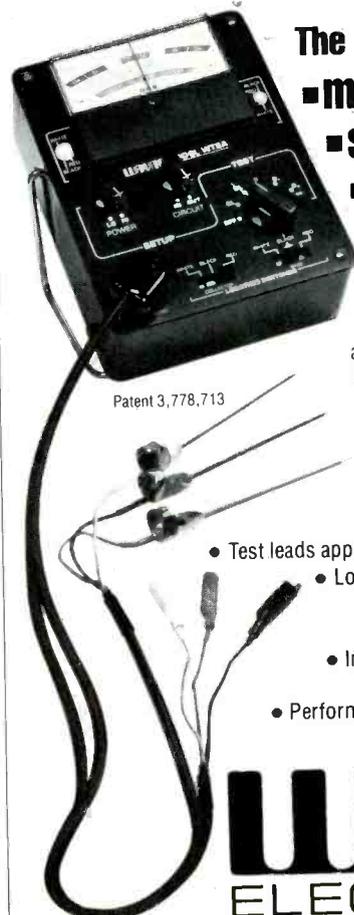

The Wayne Model WT2A
■ makes YOU money
■ saves much time
■ makes trouble-shooting easier

A new concept in transistor testing based on proven methods of circuit analysis. A current limited AC voltage is applied to each semiconductor junction under test. The resulting DC voltage is monitored while the rectifying junction is passing normal rated current. Abnormalities are easily identified.

- Indicates PNP or NPN
- Measures relative gain
- Test leads applied without prior basing knowledge
- Locates base and collector during test
 - Indicates silicon or germanium
 - Indicates transistor non-linearity
- In-circuit tests with shunt impedance down to THREE ohms
- Performs all of above and more in less than ten seconds

WAYNE ELECTRONICS

5412 Nordling St./Houston, Texas 77022

... for more details circle 132 on Reader Service Card



Digital Frequency Counters for Servicing—Part 1

By Joseph J. Carr, CET, ET/D Contributing Editor

Operation, specifications and applications

■ Until recently, digital frequency and period counters have been high-cost, exotic instruments associated with “high-dollar” communications shops, government financed R & D laboratories

and test equipment/metrology facilities.

Modern electronic technology has changed all of that, allowing manufacturers to offer, at substantially lower cost to the user, quality digital counters

whose performance often exceeds that of all but the best previous designs. As an example of this trend, consider those highly accurate, FCC-type-accepted counters often seen in mobile radio repair shops.

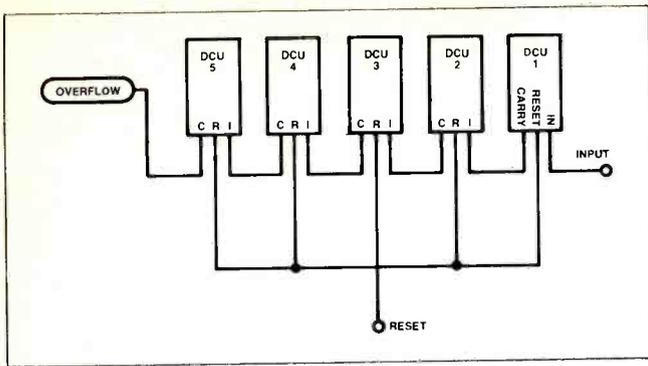


Fig. 1—A decimal counting assembly (DCA) consists of several decimal counting units (DCU's) in cascade. Each DCU counts from 0 to 9 and controls one digit of the multi-digit display.

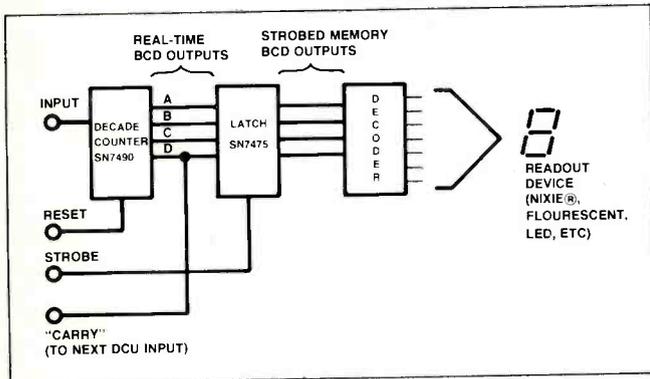


Fig. 2—Simplified block diagram of a low-cost TTL decimal counting unit capable of counting to over 20 MHz. The latch circuit keeps the display stable.

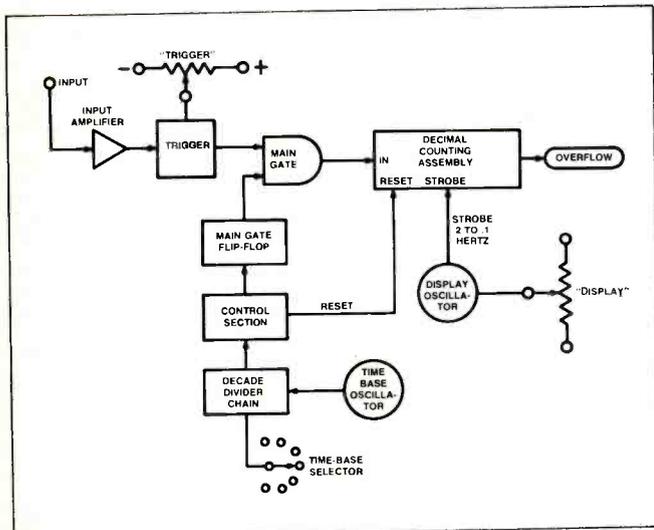


Fig. 3—Block diagram of a typical frequency counter.

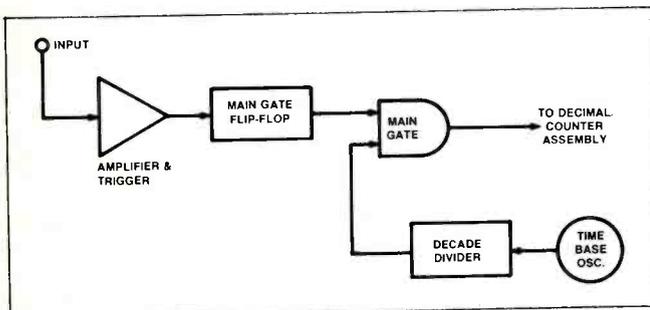


Fig. 4—Block diagram of period counting functions. Period counters measure the time interval between the beginning of successive pulses by reversing the function of the input amplifiers and the time base via a viz the control flip-flop.

Just a few years ago, such instruments carried price tags of between \$1800 and \$4000. Today, at least one instrument in that class can be purchased for less than \$800. Some non-type-approved digital counters sell for less than \$100, while a few still carry prices in the multi-kilobuck range. The cost of digital counters has decreased to the point that some top-dollar signal generators are equipped with a built-in frequency counter which functions as the dial read-out.

In this two-part series, the internal circuitry of digital counters will be examined and their utility of application around almost any electronic service shop will be demonstrated. We also will give you some insight into digital counter terminology and specifications, so that you can make intelligent purchase decisions which avoid the pitfalls of "creative spec" writing.

DECIMAL COUNTING UNITS

The real heart of the digital counter is a digital electronic circuit which accumulates pulses and drives a readout device which tells the outside world how many pulses (from 0-9) have been counted. Such circuits, called decimal counting units (DCU's), can be cascaded to provide a wider counting range (i.e., 0-99, 0-999, etc.). A bank of several DCU's in cascade, as shown in Fig. 1, is called a decimal counting assembly (DCA). One DCU is required for each digit in the DCA.

One of the factors which pushed up the price of counters in previous years was that the DCU was made of (then) very

expensive digital-logic integrated circuits. A typical digital counter IC then cost more than \$15.00. Or they were equipped with transistorized flip-flops, which were equally expensive. When the transistor design was used, four flip-flops were needed per digit. And the transistor type of DCU often proved difficult to decode, making it even more costly to use. All DCU's, incidentally, require decoding because the counters operate in *binary coded decimal* (BCD). In that number system, four "bits" (voltage levels) are presented, each on separate lines, to represent the decimal digits between 0 and 9 (i.e., 2 = 0100, 6 = 0110, 9 = 1001; where binary 0 is either "ground" or some negative voltage, and binary 1 is either a positive voltage or a negative voltage, depending upon the system).

Fig. 2 shows the partial schematic of a relatively simple common DCU using transistor-transistor digital logic (TTL) integrated circuits. At one time, these devices cost an arm and a leg, but they now are relatively cheap. The SN7490P decade counter, for example, can be purchased for \$1.00 to \$4.00, depending upon the source.

The type of decade counter used in Fig. 2 can count to speeds somewhat in excess of 20 MHz, while certain high-speed TTL chips count to 50 or even 80 MHz. The internal circuitry of the SN7490 includes all of the flip-flops and gating needed to form a decimal counter.

In many counters, especially in older designs or a few newer but very low-cost types, the decade

counter directly feeds the binary coded decimal (BCD) lines to the decoder circuit. This design produces a rolling display that is a little hard to read. You can actually see the digital readout of these instruments change as pulses are accumulated much in the same manner as the digits on a gasoline pump "roll" as price is accumulated.

To keep the display steady, most modern counters, even those of modest cost, use a four-bit memory, called a *quad latch*, between the counter and decoder circuits. A latch circuit "remembers" the BCD state which existed at its input the last time the strobe terminal was enabled (turned on). This design allows the display to be "instantly" updated at a rate determined by the repetition rate of the display multivibrator, which is set by a control on the front panel. In some low-cost designs, the display is still fed by a latch, but the display rate is *fixed*. You can tell whether or not a counter is equipped with a latch. If it is, the display update will occur all at once; the new digits seem to pop "pre-counted" onto the readout. Non-latched types will exhibit the "roll" symptom.

FREQUENCY COUNTER DESIGN

Fig. 3 is the block diagram of a typical digital frequency counter. Although this particular design is not found in *all* digital frequency counters, it is sufficiently representative to be used for explanatory purposes. The differences between the design in Fig. 3 and other designs usually involves special

features in special-purpose counters (i.e., high-resolution types) or, in low-cost types, deletion and/or automation of some of the features in Fig. 3.

In counter jargon, the term "frequency" is called *events per unit of time* (EPUT). Remember, before they changed the jargon, *frequency* was "cycles (events) per second (unit of time)." Any EPUT counter requires a *main gate*, which allows pulses being counted into the DCA. The gate is opened and closed by a train of pulses from a *time base circuit*. These pulses also are used to reset the DCA to zero state, so that a true count is obtained. Without a main gate, the DCA would simply continue to accumulate input pulses with no relationship to *time*.

PERIOD COUNTER DESIGN

A *period counter* (Fig. 4) is used to measure the amount of *time between* successive pulses. This can be accomplished by merely reversing the functions of the input amplifier and the time base. The main gate flip-flop will be enabled by a pulse from the input amplifier, and closed by the next pulse. Time base pulses are passed through the gate to the DCA. If a 1000-Hz time base signal is used, the period is measured in *milliseconds*. Many counters allow selection of the time base frequency.

There are many uses for a period counter, but the two main applications are in measuring low-frequency signals (less than 100 Hz) or higher frequencies where much greater resolution than 1 Hz is required. An example of the latter use is in electronic

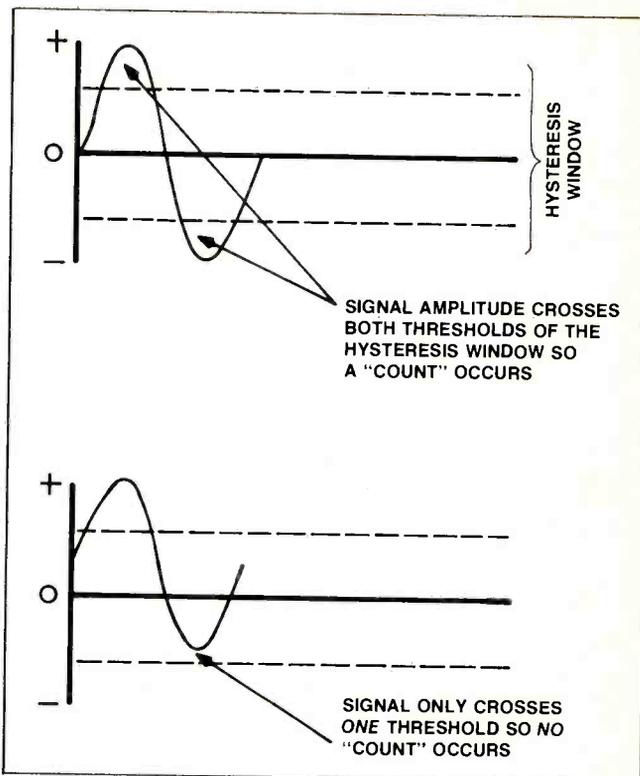


Fig. 5—A "count" can be achieved only when the input signal crosses both the upper and lower bounds of the trigger's hysteresis window.

musical instruments, in which certain of the tones are specified to within three decimal points of one hertz. In such cases, you simply choose a time base frequency high enough to give the desired resolution, and then perform this arithmetic:

$$\text{Freq. (Hz)} = \frac{1}{\text{Period (sec)}}, \text{ or}$$

$$\text{Period (sec)} = \frac{1}{\text{Freq. (Hz)}}$$

TIME BASE CIRCUITS

The *length of time* that the gate stays *open* is a function of the time base frequency. A time base is a precise crystal-controlled oscillator followed by some TTL *decade dividers* (the same SN7490P IC used in the DCU, but without decoding). Typically, 1-MHz oscillators are used, but 3-, 4-, 5- and 10-MHz types are occa-

sionally used.

Some counters provide a switch which allows the user to select time base intervals between .0000001 (.1 microsec) and 10 seconds. This is done by selecting frequency through choice of division ratio. (Each SN7490P will provide an output frequency 1/10 of the input.) Typically, 10 MHz gives gate times of .1 microsecond, 1 MHz yields 1 microsecond, 1 Hz gives 1 second, etc. Many of the lower-cost counters provide limited manipulation of the time base through a "Hz/KHz" or "KHz/MHz" switch.

One of the principal counter specs is *time base stability* and *accuracy*. Although the inclination may be to buy a counter with top time base specs, this can needlessly overprice your instrument. Where exceptional accuracy is not needed, a non-compensated, room-temperature

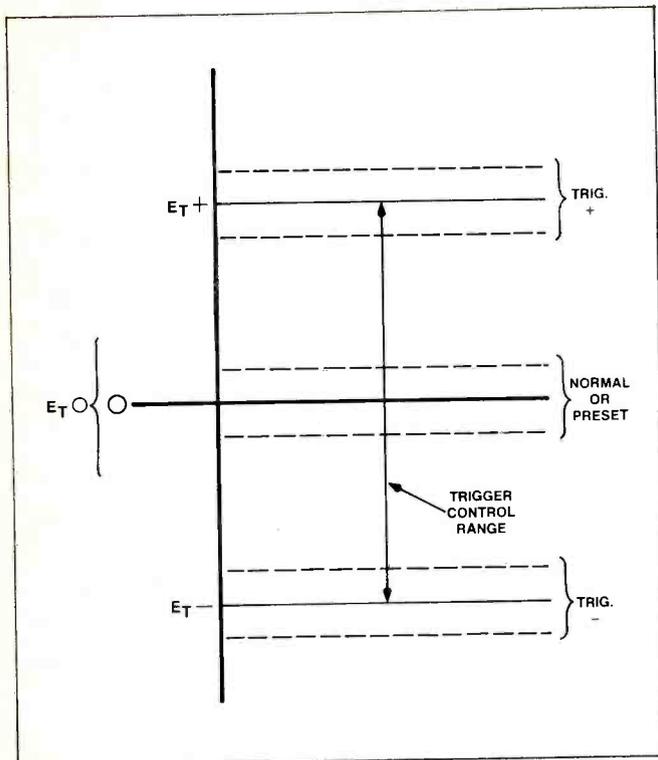


Fig. 6—Trigger controls vary the position of the hysteresis window up and down on a voltage scale so that signals of either polarity, with or without a DC component, can be counted.

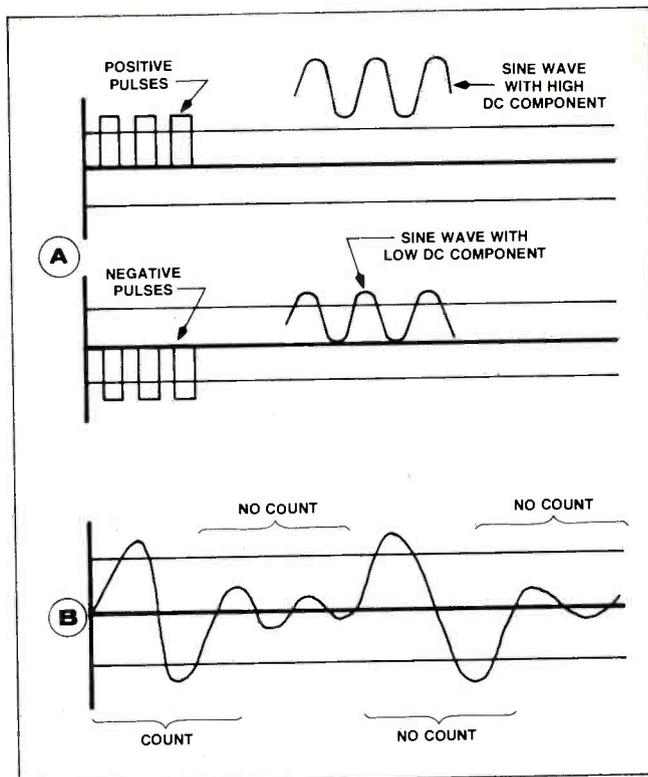


Fig. 7—Several of the waveforms which cannot be counted by a digital counter with a fixed hysteresis window.

time base usually will suffice. These circuits can offer stability figures on the order of 5×10^{-6} . A step better, offering five times the stability, are temperature-compensated crystal oscillator (TCXO) designs. In some cases, TCXO counters are accurate and stable enough to receive FCC type approval.

Oven-controlled oscillators offer the best stability. Simple thermostat-controlled oscillator ovens offer better stability but are still somewhat inferior to those using *proportional control* ovens. This design produces a more constant temperature. A single-oven proportional control oscillator can keep the frequency within $\pm 5 \times 10^{-8}$. The most stable and accurate counters use double oven oscillators, which have the actual crystal oven inside a second oven. Such arrangements are capable of maintaining crystal temperature within

$.01^\circ \text{C}$, producing a frequency stability of 5×10^{-11} . Of course, expect double-oven time base oscillators only in the most expensive counters.

TIME BASE AGING

Crystal oscillators, even high-grade types, always drift over a period of time. This slow drift is usually predictable and is expressed as an *aging rate*. This is the reason for periodic trips to the calibration laboratory or manufacturer, if it is desired to keep the instrument up to its original specs. How often calibration is needed is a function of the aging rate.

Keep in mind that even the best counters with really good stability figures have an aging rate. Also, their normal stability cannot be expected until the instrument has been on for at least 24 continuous hours. Because of this,

many counters use a special power supply for the time base oscillator. This accomplishes two things: 1) The power supply regulation is improved because the loading is essentially constant, and 2) the oscillator supply can be left on even when the counter is turned off. If you cannot keep your instrument plugged in (so that the oscillator will run continuously), it may be necessary to buy one with at least one order of magnitude better stability than would otherwise be needed. Some battery types are good in this respect because they can be left with the oscillator on during unplugged periods (i.e., in your service truck between jobs). The standard of accuracy for a counter is not less than *five times* the accuracy required of the frequency under examination. For example, a Citizens-Band transmitter must be within

$\pm 50 \text{ ppm}$ (5×10^{-5}); consequently, a counter for CB servicing should have an accuracy not worse than 10 ppm, with 5 ppm being best.

TRIGGER CIRCUITS

Most counters are equipped with Schmitt trigger circuits which have both upper and lower *threshold bounds* (see Fig. 5). An input signal must cross *both* threshold levels if the DCA count is to be affected. The difference between these limits is called the *hysteresis window*. Its function is to allow only *one pulse* to be generated for *each input cycle*. Otherwise, it would be possible for non-sinusoidal waveforms to falsely trigger the DCA. The trigger control varies the position of the window relative to a minus-zero-plus voltage scale, so that a variety of input signals not centered about zero can be counted. Other-

wise, a signal with a DC component might not be counted even though its own relative amplitude is greater than the advertised sensitivity of the counter. Fig. 6 shows the action of the trigger control. Fig. 7 shows several types of waveforms which *cannot* be counted on an instrument with a *fixed* hysteresis window.

Some counters do not have a continuously variable trigger control but, instead, are equipped with a three-position switch typically labeled either "+, 0, -" or "+, present." In many applications, this arrangement is less desirable than a continuous control, but is better than no control at all. A trigger control is almost a necessity for TV applications because the pulses encountered may have either polarity, with or without a DC component. The rarely seen *trigger amplitude* control does not affect the "center" position of the window, but does vary its "width."

COUNTER SENSITIVITY

One parameter which, like hi-fi power output, has been subjected to a lot of "creative" spec writing is *sensitivity*. On the surface, it might appear that the more sensitivity, the better. However, this is not always true. Sensitivity is the *minimum amplitude* of signal which can *reliably* trigger the counter. If the sensitivity is too great, noise might falsely trigger the instrument; if the sensitivity is too low, desired signals might be ignored.

Sensitivity is often expressed in either RMS volts or in a certain pulse amplitude (also volts). In any event, most trigger circuits have a *pulse* sensitivity that is 2.82 times the

RMS figure. If both figures are specified, be a little wary of the instrument which has a *ratio* significantly different than this value, because there might be something wrong with the sensitivity at higher frequencies.

It is difficult to state a specific optimum counter sensitivity. All that is possible are some general sensitivity guidelines, which are dependent on input impedance. Sensitivity values which usually are acceptable are 25-100 millivolts RMS for 1-megohm inputs, and 10-50 millivolts RMS for 50-ohm inputs. Generally, counters under 200 MHz have high-impedance inputs, and those over 200 MHz have a 50-ohm input.

VHF COUNTING TECHNIQUES

Common TTL digital IC's are capable of counting up to about 80 MHz. IC's in the ECL family are capable of being operated at twice this frequency, but are neither as cheap nor are they directly compatible with TTL. Very special (and expensive) ECL types can count in excess of 500 MHz. Be-

yond these limits, or even up to them if cost is a factor, other techniques must be applied. There are at least three methods for achieving a high-VHF/UHF counter: *direct counting*, *prescaled counting*, and *heterodyne counting*.

Direct counting is the normal mode of operation for digital frequency counters. Most common counters can direct count to around 80 MHz. If an ECL first stage is used, this "normal" limit is pushed to 180 MHz. Keep in mind that direct counting (also called real time counting) is possible to over 500 MHz if one wishes to pay a premium price.

A prescaled counter divides the input frequency by some integer, then counts the resulting frequency. If the selected division ratio is ten, to "read" the actual frequency you merely remember to move the decimal point on the readout one place. One reason for using this technique is that several lower-cost IC's will divide by ten up to 500 MHz, but not in a circuit that is easy to decode for display purposes. Fig. 8 shows a pop-

ular prescaled system.

The third method mentioned is the heterodyne system, shown in Fig. 9. In this type of counter, the input frequency is translated to a lower frequency within the range of the instrument. The "local" frequency source can be a separate crystal oscillator, but usually is a frequency multiplier chain or phase-locked-loop (PLL) controlled oscillator, either of which can be driven or synched by the time base oscillator.

If the "local" frequency source in a heterodyne counter is designed to produce frequencies as high as 400 MHz, and the basic counter is capable of direct counting to 80 MHz, the counter will be capable of measuring frequencies in the mobile radio bands up to 480 MHz because it will actually be measuring $F_{in} - F_{local}$. Counters well into the microwave (GHz) range are possible by use of this technique.

COUNTER ERROR

All of those pretty digits displayed by a counter might tempt one to make the same error made by high school physics students working problems with a sixteen-digit calculator: forgetting that only a *portion* of the total display is valid. For all counters in which the main gate circuitry does not synchronize the time base with the input signal (which is just about all counters), the display accuracy is \pm the last (least significant) digit. This makes the overall accuracy equal to the time base error \pm one count of the LSD.

NEXT MONTH: Specific applications of digital counters in the service shop, and what specs are desirable for each. ■

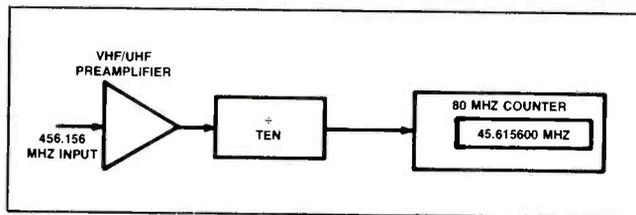


Fig. 8—Prescaling is a technique which makes it possible to measure frequencies in the VHF and UHF ranges with an instrument designed for a lower range of frequencies.

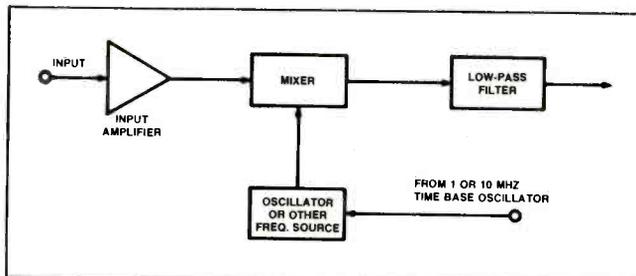


Fig. 9—Heterodyning is another method of extending the frequency range of a digital counter.

Condensed from a single chapter of a recently introduced TAB book, by permission of TAB BOOKS, Blue Ridge Summit, Pa. 17214

Troubleshooting Horizontal Deflection & High Voltage Circuits - Part I

THE DEFLECTION CIRCUITS

■ The deflection circuits are comprised of four major stages: the horizontal output stage, the horizontal output transformer, the deflection yoke, and the damper. All four of these work together to control the horizontal deflection of the electron beam.

A simplified schematic of a typical horizontal deflection system is shown in Fig. 1. The output of the horizontal oscillator drives the grid of the horizontal output tube, which is class C biased by the grid circuit. Plate voltage for the output stage is provided by the charge across C1. How this charge is developed is easier understood after looking at the operation of the four stages.

With no signal applied to the grid, V1 is cut off, and no current flows in the transformer or yoke. No magnetic field will be developed without yoke current; therefore, the beam is at the center of the screen. As the output stage is brought into conduction, current flows through V1, through the transformer, through the yoke to the positive B-boost charge on C1, from the capacitor to the B+ supply, and through the supply to ground. The corresponding CRT trace is shown as vector A in Fig. 1B. As the current through V1 and the yoke increases (shown as A in Fig. 1C), the beam is drawn farther to the right.

When the waveform at the grid of V1 starts going negative, V1 is suddenly cut off. This sudden stopping of V1 current causes the magnetic field about the transformer to collapse, inducing a current in the yoke in the same direction as that supplied by V1. However, instead of flowing into C1, the current charges the yoke capacitors. Tube V2 cannot conduct, due to the high positive potential on the cathode. When the yoke field is fully dissipated, there is no more yoke current; therefore, the beam returns rapidly to the center of the screen.

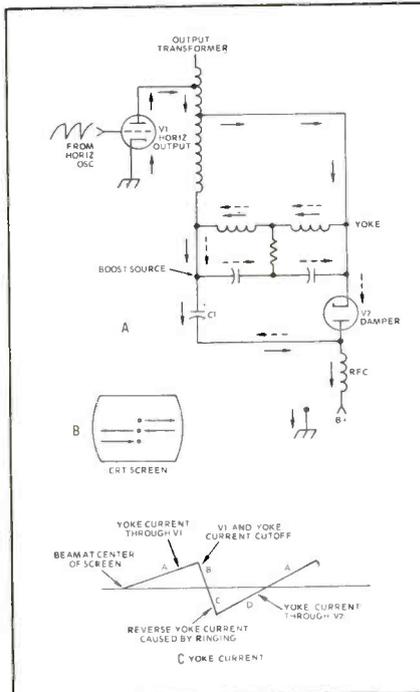


Fig. 1—Horizontal deflection circuit.

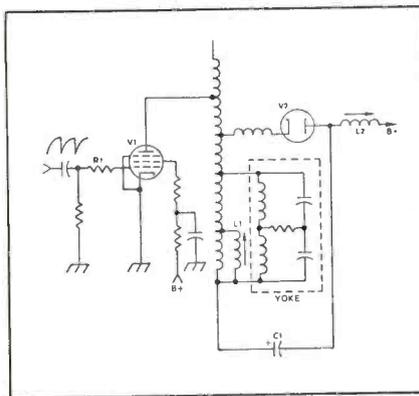


Fig. 2—Horizontal deflection circuit, showing linearity control.

As the ringing action of the yoke continues, the charge across the yoke capacitors starts to discharge through the yoke coils. This causes a reverse yoke current, and the beam is deflected to the left of the CRT, as shown by vector C in Fig. 1B. During this cycle, the cathode of

From Chapter 11, LOGICAL COLOR TV TROUBLESHOOTING, by Ben Gaddis, TAB BOOKS, Copyright 1974. A review of the complete book follows part 2 of this article.

the damper is gradually becoming less positive; and when the coils of the yoke begin to discharge into the capacitors once again, the cathode is negative with respect to the plate.

As the coils discharge back into the capacitors, yoke current flows once again, moving the beam to the center of the tube. As this current increases, V2 conduction continues to increase, gradually dampening the ringing action of the yoke (shown by dotted lines in Fig. 1A). When the beam approaches the center of the tube, the waveform at the grid of V1 is sufficiently positive to cause V1 to conduct, and the cycle starts over again.

The plate supply for V1 is the B-boost voltage across C1. Each time V2 conducts, its plate voltage drops. This AC voltage at the plate of V1 causes a charging current to flow into C1. The plate circuit sees C1 in series with the B+ supply and, therefore, the voltages are additive, resulting in a high DC voltage at the junction of C1 and the yoke. Each time V1 conducts, the charge across C1 is reduced, to be replaced each time V2 conducts.

A more complete schematic of the horizontal deflection circuits is shown in Fig. 2. Bias for V1 is developed across R1, holding V1 in cutoff until the oscillator output is sufficiently positive to cause conduction. Operation of the damper and yoke stages is the same as described earlier. Coil L1 is provided in some sets as a horizontal width control. Coil L2 is a linearity control. This control tunes the horizontal output circuit to provide minimum loading of the output stage. It is more correctly called horizontal efficiency, because it has very little control over linearity.

An example of a solid-state horizontal deflection system is shown in Fig. 3. The operation is generally the same as that of the tube-type circuits, with exception of considerations necessary for solid-state circuits. The deflection yoke coils have

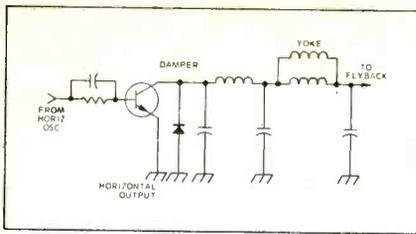


Fig. 3—Solid-state horizontal circuit.

been placed in parallel in this example to reduce to total inductive load on the output transistor. In some models, a buffer or driver transformer is located between the oscillator and the output stage to prevent loading of the oscillator. To provide the relatively high power output required of this stage, two transistors operating in parallel are sometimes used. Conduction of the output transistor causes beam deflection from the center of the screen to the right, and damper current moves the beam from the left to the center, just as in the previous circuits.

There are usually several other output taps on the flyback transformer in addition to those already presented here. The high-voltage circuit takes power from some of these taps, while others are used for horizontal blanking, AGC, AFC, and color-gating signals.

THE HIGH VOLTAGE CIRCUITS

For the purposes of our discussion here, the high-voltage circuits include two separate high-voltage supplies: the second-anode supply, and the focus supply. Some sets use one common high voltage supply with a voltage divider to produce the two DC voltages, while others make use of a high B-boost voltage as the source of focusing voltage. Two separate supplies are shown in Fig. 4.

Separate windings on the flyback transformer supply filament voltage for the two rectifiers. These circuits function similar to a conventional half-wave rectifier power supply. When oscillator action causes V1 to cut off, the collapsing magnetic field in the flyback transformer induces a voltage in the transformer winding that produces a high DC voltage pulse at the plates of the rectifiers. This pulse is stepped up by the auto-transformer action of the flyback. Rectification is achieved by the rectifiers, and a high DC voltage is produced at the cathodes. By means of L1, the impedance in the cathode

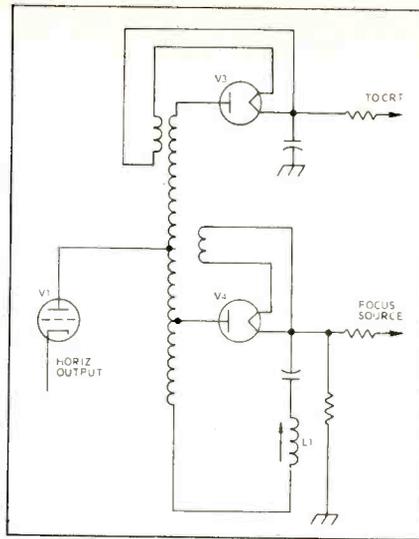


Fig. 4—High voltage supplies.

circuit of V4 can be adjusted to set the focus voltage at the prescribed level. Adjustment of the second-anode supply is usually made in the high-voltage regulator circuit, which will be discussed later.

Solid-state high-voltage diodes generally employ high-voltage solid-state rectifiers that function similar to their vacuum tube counterparts. One type of solid-state supply, shown in Fig. 5, uses a voltage tripler circuit. In this example, a high-voltage pulse is generated in the transformer and appears at the anode of X1. As X1 conducts, a charge is developed across the parallel capacitor. After several cycles, all capacitors are charged and the charges appear in series, adding to the total DC voltage available at the second anode.

In a television set, the high-voltage output of the second-anode supply will vary with the brightness of the scene. This is due to the fact that during the reproduction of high brightness areas the CRT is drawing a relatively heavy current, placing a load on the high-voltage supply. As scene brightness decreases, the load on the supply decreases, and, as a result, the high-voltage output increases. Due to the lower amount of beam current drawn by b-w receivers, this fluctuation can be tolerated. However, the heavier beam currents of the color CRT causes these variations in the high voltage to be excessive, and cause a decrease in picture width due to the loading placed on the horizontal output stage. Other circuits in the color receiver also draw DC or signal voltages from the horizontal output;

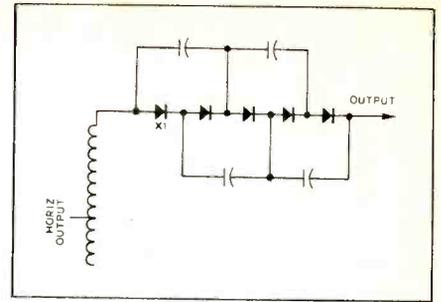


Fig. 5—Solid-state high-voltage supply.

therefore, loading of the output stage cannot be tolerated in the color set. To overcome the loading effect on the horizontal output stage, color receivers employ a regulated high-voltage supply. Basically, this supply is the same as the one just discussed except for a regulator stage placed somewhere in the high-voltage generating chain.

Regulator Stage

The shunt-type regulator has long been the most popular of the high-voltage regulators. A simplified version of this circuit is shown in Fig. 6A. Operation of this circuit is based on the premise that the output stage and flyback transformer function as a constant-current source; that is, a steady value of DC current is drawn from the transformer. The regulator tube in parallel with the load (the CRT) controls the amount of current shunted around the load, thereby regulating the voltage across the load.

In the figure, a high-voltage triode is tied between the high-voltage supply and B+. The grid is connected to the B-boost source through a voltage divider, one resistor being adjustable to furnish a high-voltage adjustment. The function of the triode is to furnish a variable load across the high-voltage output, in parallel with the CRT. As the load of the CRT decreases, the load furnished by the regulator tube increases and, as the CRT load increases, the load furnished by the regulator tube decreases. Thus, a constant load is reflected to the power supply.

Assume that the scene brightness suddenly increases, causing beam current to increase. This causes a heavier load to be placed on the flyback, and the voltage output starts to decrease. The heavier load will also cause a decrease in the boost voltage. As boost voltage decreases,

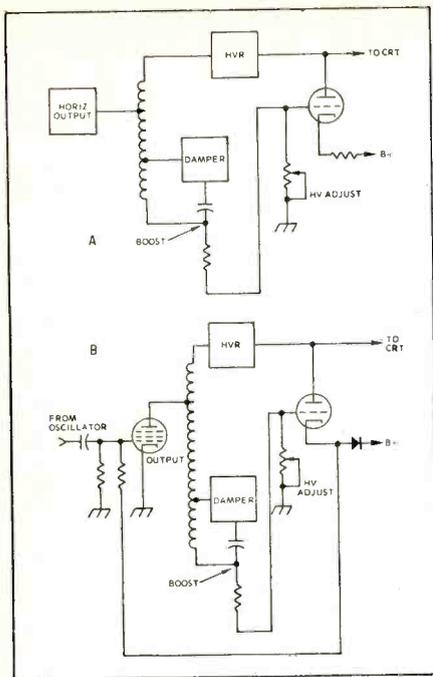


Fig. 6—Shunt-type high-voltage regulators. A) Without holddown provision. B) With holddown provision.

the bias on the regulator tube is increased (made less positive), causing the tube conduction to decrease. Conduction of the regulator tube decreases until a point is reached where the high voltage is returned to normal. Boost voltage will again be at its normal level.

If the scene brightness should decrease, the high voltage will attempt to increase due to the decrease in beam current. The decrease in load also causes an increase in boost voltage. This positive-going voltage causes the regulator tube to increase conduction, restoring the normal load on the transformer, and the high voltage and boosted B+ return to normal.

It must be remembered that this type of regulator circuit is designed to function within certain specified limits. Should the current in the load vary to a point outside these limits, as would be caused by opens in the load or a low resistance to ground, the regulator tube will not be able to control the high voltage. In cases of excessive high voltage, as could be caused by a failure of the regulator tube itself, there is the danger of X-radiation. Therefore, some modern shunt regulators use the modified circuit shown in Fig. 6.

Improved Regulator Circuit

In this example, a diode is placed between the B+ supply of the regulator and the cathode of the regula-

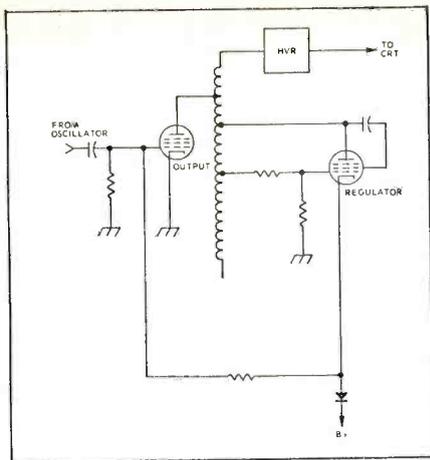


Fig. 7—A pulse-type high voltage regulator.

tor tube. The B+ for the output stage is also drawn from this same diode. In this circuit B+ will be available to bias the output tube into conduction only if the regulator tube is conducting. If the regulator fails, no current flows through the diode, and the bias on the grid of the output tube is lowered due to the absence of the B+ voltage. There will still be a high-voltage output, but it will be below normal.

One disadvantage of this circuit is that if the high-voltage regulator tube shorts—a common occurrence—the diode will probably short also. When the regulator tube is replaced to restore normal operation, all will appear well, even though the diode is shorted. However, the safety feature will now be inoperative because B+ will be available to the output stage at all times, regardless of the conduction of the regulator. When regulator tubes are replaced in this type of circuit, always check the diode for shorts.

Another disadvantage of this type of regulator is the amount of power wasted. Since operation of the shunt regulator is based on the fact that the flyback must supply a constant current, power dissipated by the regulator tube during periods of low brightness is wasted. This results in the transformer supplying a full load current at all times.

A better method would be one in which the transformer supplied only the amount of current required in any one instance. Such a circuit is shown in simplified form in Fig. 7. This circuit is called a *pulse regulator*, due to the fact that it functions on pulses from the flyback transformer. Control grid, screen grid, and plate voltages for the regulator tube are all received in the form of

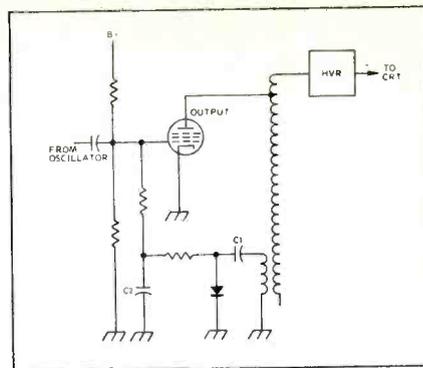


Fig. 8—Diode feedback high-voltage regulator.

positive pulses during the retrace time. If the brightness of the scene decreases, the high voltage attempts to increase. At the same time, the amplitude of the pulses at the various transformer taps also tries to increase. This increase in the positive pulses applied to the pulse regulator tube causes the tube conduction to increase and load the transformer, decreasing the transformer efficiency and current. If the high voltage decreases, so do the pulses to the regulator. The regulator conducts less, causing less loading of the flyback and an increase in efficiency. As in the shunt regulator, a protection diode is included in the cathode circuit.

Feedback Regulator

An even more efficient method of regulating the high voltage would be to regulate the current available to the transformer. Regulators using this principle employ a feedback system similar to automatic gain control. An example of the feedback regulator is shown in Fig. 8. This circuit is sometimes called a *grid regulator*, but its use with solid-state circuits as well as tube circuits makes the name *feedback regulator* more appropriate.

Normal operating bias for the tube is supplied by a grid leak circuit and the voltage divider between B+ and ground. As the high voltage tends to increase, the amplitude of the pulse applied across the diode also tends to increase. This pulse is rectified by the diode, and the filter action of C2 causes a charge to be developed across C2. With an increasing pulse, the negative voltage applied to grid resistor R1 increases, causing the tube to decrease conduction, and, consequently, the high voltage is lowered.

Continued next month in Part 2

ET/D 1974 SUBJECT REFERENCE INDEX

The first numerical group following each listing indicates the month of the issue in which it appeared, and the second numerical group indicates the page on which coverage of the topic appears or begins. The two-letter alphabetical code in parenthesis immediately following some listings indicates coverage in one of the following ET/D regular departments: COLOR-FAX (CF), Dealer Showcase (DS), New Products (NP), TEKLAB (TL), Technical Digest (TD), Test Instrument Report (TR)

ANTENNAS (Including Systems & Accessories)

Antenna, Jerrold Electronics Corp., Model TOTE-5K	(DS)	2/53
Antenna, JFD Electronics Corp., Model LPV-UC	(NP)	6/50
Antenna Matching Harness, Jerrold Model USL-U	(NP)	4/64
Antenna System Directional Coupler Taps, Jerrold Electronics, DFT/Series	(NP)	12/45
Antenna, The Finney Co.	(NP)	1/49
Antennas, Antenna Specialists Co., Models ASP-816/817	(NP)	10/48
Antennas, Channel Master Quantum Series	(NP)	12/48
Attenuation or Loss		4/33
Balancing Channels in MATV Systems		10/32
CATV Drop Cable, Belden Corp.	(NP)	8/44
CATV Midband Trap, Blonder-Tongue Model MWT-4	(NP)	3/20
Coax or Twin Lead-Making the Choice		4/32
Coax Types		4/35
Distribution Amplifier, Antennacraft Model UVF-1520		7/49
Distribution Amplifier, Jerrold Model CDA-300	(NP)	3/46
Distribution Amplifier, Winegard Co., Model DA-215	(NP)	8/43
Distribution Amplifier, Winegard Co., Model DA-825B	(NP)	1/50
Fault Finding in MATV Systems		4/36
Fields Interference and Durability		4/32
FM Antenna, Blonder-Tongue Stereo-Eight	(NP)	8/45
FM Interference Trap, Jerrold Electronics Model RFT-300	(NP)	7/49
Home Antenna/Cable TV Switch, ACA Model CM10	(NP)	11/45
Impedance		4/32
Interpreting MATV Amplifier Specs		9/38
Matching Transformer, Jerrold Model T-3789	(NP)	5/50
MATV CATV Attenuator, RCA Model WM-542A	(NP)	8/43
MATV Distribution Amplifier, ACA "Mini-Mite"	(NP)	10/48
MATV Head Ends, Jerrold Electronics	(NP)	8/46
MATV Tapoff, Blonder-Tongue Model V-4897	(DS)	9/52
MATV Taps—Selection and Use		7/22
Mobile Antenna, Antenna Specialists Co., Model ASP-800	(NP)	9/50
Mobile CB Antenna, The Antenna Specialists Co., Super Scan II	(NP)	6/51
Selling TV Antennas to CATV Subscribers		4/50
Three-Way Splitter, AEL Communications Model MSB3	(NP)	4/65
Travel Antenna, ACA Model AC800K	(DS)	5/57
TV Interference—Causes and Cures		3/27
Twin Lead Types		4/35
Two-Way VHF/UHF Splitter, RMS Electronics Model HS-20U/MM	(NP)	3/46
UHF Antenna, Antenna Specialists Co., Models ASP-820/821/822	(DS)	9/55
UHF Bandpass Filters, Jerrold Model UBPF-14 thru UBPF-70	(NP)	1/49
UHF Preamplifiers, Blonder-Tongue Model SCMA-U	(NP)	6/52
UHF/VHF/FM Antenna, RCA Model 4BG48	(NP)	11/44
VHF Cable Loss Equalizer, Q-Bit Corp., Model 4200	(DS)	9/58
VHF/FM Antenna Preamplifier, Winegard Co., Model RD-375	(NP)	2/48

AUDIO

Audio Adapters, Switchcraft 301Q "A-G"	(NP)	8/42
--	------	------

Audio/Video Tape Logger, GYR Products, Odetics, Inc. Model TL350	(DS)	1/54
Car Stereo, Aiko America Corp., Model ACS-217	(DS)	1/54
Cassette Recorder, Channel Master, Model 6392	(DS)	1/56
Cassette Recorder, General Electric, Model M8710	(DS)	5/56
Cassette Tape Deck, Sanyo Electric Inc., Model 4250	(DS)	1/55
CD-4 Demodulator, The Marantz Co., Model CD-400	(DS)	12/48
Distributor Amplifier, Ramko Research, Model DA-6BR	(NP)	2/50
Eight-Track Cartridge Record Deck, JVC Model ED-1245	(DS)	8/51
Eight-Track Player, Panasonic Dynamic 8	(DS)	9/55
Electronic Adjustments in Auto Tape Players		7/38
Erratic Tape Speed, Eight-Track Tape Player, Magnavox Model VE15-01, 02, 05, 06	(TD)	5/48
FM/AM/Radio/Cassette Recorder, Sony Model CF-310	(DS)	5/58
Four-Channel/Stereo Amplifier, Marantz Co., Model 4070	(DS)	6/56
Full Logic SQ Decoder, Superscope Model SQA-2	(DS)	10/56
Head Demagnetizer, Nortronic Co., Inc., Model QM-202	(NP)	8/47
Headphone Control Box, GC Electronics No. 30-5250	(DS)	10/53
Headphones, GC Electronics No. 30-5205	(DS)	6/56
Headphones, Panasonic Model EAH-23	(DS)	12/48
Microphone, Astatic Corp. "Trucker"		9/52
Microphone Gain Control, Shure Brothers Inc., Model M625	(NP)	7/49
Motor Failure, Admiral Tape Player Chassis 8Y6	(TD)	8/10
Motor Replacement, Magnavox, 8-Track Tape Players IK8869/701404, 05, 06, 23, 24	(TD)	10/14
Needle and Cartridge Display, Pageant/MA Miller Industries	(DS)	12/48
Needle Merchandiser, EV-Game Needle Finder	(DS)	12/48
Phone Plug Adapters, ITT Pomona Electronics Model 4043	(DS)	11/43
Phonograph Needles, EV Game No. SNK-6	(DS)	5/56
Quadraphonic Audio Console, GTE Sylvania Inc., Model QCT 4648A	(DS)	11/46
Record Cleaner, VOR Industries "VAC-O-REC"	(DS)	10/54
Recorder Erase Head, Nortronic Co., Model FD-TE4	(NP)	1/49
Recorder Test Set, 3M Model 6500	(TR)	1/41
Recording Tape Eraser, Nortronic Co., Inc., Model QM-211	(DS)	6/57
Selecting Commercial Audio Amplifiers		8/34
Selecting Speakers for Commercial Audio Systems		6/30
Speaker, Atlas Sound Model AP-15TU	(DS)	8/49
Speaker Baffle, Electro Sound Series FS	(NP)	3/48
Speakers, Benjamin Electronic Sound Co., Models CS-1/CS-20	(DS)	9/52
Speakers, Sound West Inc. "Extraspeakers"	(DS)	6/59
Speech Recognition System, Shields Products, Inc.	(NP)	2/48
Square-Wave Testing of Audio Amplifiers		9/32
Stalled or Slow Speed Turntable, Magnavox Record Changer Model W712		7/47
Stereo Amplifier, GC Electronics Cat. No. 305015	(DS)	1/56
Stereo Audio Measurements		6/24
Stereo Cassette Deck, TEAC Corp., Model 160	(DS)	2/52
Stereo Needle Lock, Se-Kure Controls, Inc., Diamond Needle Lock	(DS)	8/49
Stereo Speaker Set, RCA Model 12R403	(DS)	12/47
Stereo System, Magnavox Model E1018	(DS)	2/52
Stereo Turntable, JVC America, Inc., Model JL-B44	(DS)	9/57
System Offers Three Ways to Build Receiver Sales		1/23
Tape Deck, Sansui Electronics Corp., Model QD-5500	(DS)	2/52
Tape Deck, Sony Model TC-755	(DS)	4/66
Tape Head Cleaners, 3M Co.	(DS)	7/50
Tape Player/Recorder, 3M Co., Model 8075	(DS)	2/52
Tape Recorder, Hitachi Model TSC-8800	(NP)	1/20
Turntable, BSR Model 620AX	(DS)	3/50
Turntable, Sansui Model SR-212	(DS)	5/56

AUTO ELECTRONICS

AM/FM Auto Radio, Audiovox Corp., Model ID-200	(DS)	10/56
Antenna Coupler, Gold Line, Model GLC 1079	(DS)	7/50
Auto Alarm, Detection Systems	(DS)	11/47
Auto Cassette Player, Audiovox Corp., Model C984	(DS)	6/56
Auto Cassette Player, Pioneer Electronics, Model KP345	(DS)	11/46
Auto Cassette Tape Player, Lear Jet Stereo Model A-72	(DS)	8/50
Auto FM Amplifier, Antennacraft	(DS)	3/50
Auto FM/AM Stereo Preamplifier, ASCOM Products, Model ASC-100	(NP)	7/48
Auto Stereo Speakers, Pioneer Electronics Chameleons	(DS)	10/54
Car Stereo, Aiko America Corp., Model ACS-217	(DS)	1/54
CB Mobile Radio, EF Johnson, Model 130	(DS)	4/66
CB Transceiver, Fanon/Courier Corp., Rebel 23-	(DS)	1/56
Electronic Adjustments in Auto Tape Players		7/38
FM Transceiver, Genave, Model GTX-100	(DS)	4/67
Four Channel Car Stereo, RCA Model 12R800	(DS)	1/55
Mobile Antenna, Antenna Specialists Co., Model ASP-800	(NP)	9/50
Mobile CB Antenna, The Antenna Specialists Co., Super Can II	(NP)	6/51
SSB/AM CB Two-Way Radio, Tram Corp., Diamond 60	(DS)	5/57
Stereo Cassette, Channel Master, Model 6622	(DS)	10/55

BUSINESS MANAGEMENT

Does Servicing Have a Future?		7/20
Effective Advertising for the Service Dealer		8/26
Getting More Out of That New Sign		1/30
Going to Remodel the Store? Here's a Good Check List		2/30
Managing to Learn and Learning to Manage		1/42
Managing to Learn and Learning to Manage		2/37
Managing to Learn and Learning to Manage		3/41
Managing to Learn and Learning to Manage		5/42
Profitable and Competitive Pricing of Service Labor		12/12
Replacement Color Picture Tubes—Propping up Servicers' Profits		8/24
Retirement Programs for Owner/Employees		3/39

B-W TV

B/W TV Power Sentry System, Zenith Radio Corp.	(DS)	9/53
Circuit-Board Modifications, General Electric Chassis SF	(TD)	1/48
Console Cabinets—Lid Supports, Admiral	(TD)	2/47
Fuse and Resistor Modification, Zenith TV Chassis 12CB127X/16DB12X	(TD)	2/47

General Electric Video Display Chassis MUA Chassis Description	(TD)	3/44
How and Why—Trapezoidal		2/27
No Vertical Sweep, Admiral TV Chassis TK3	(TD)	2/47
Picture Tube Mounting Ring Removal, Philco-Ford 19-inch Models	(TD)	9/14
Picture Tube Repairs		5/33
Product Safety Maintenance, Admiral	(TD)	7/46
Service Check of Filament Diode Rectifier 34-8054-23 Philco-Ford Monochrome TV Chassis	(TD)	10/14
Servicing Solid-State AGC Circuits		11/24
Solid State Tubes, EDI	(NP)	5/54
Symptoms Caused by Shorted IC301, General Electric Chassis SF	(TD)	4/58
Troubleshooting Solid-State Multivibrators		12/28
UHF Tuner, General Electric Chassis U1/UA	(TD)	4/58
Vertical Stretch and/or Double Picture, MGA TV Models BT-120/BT-121/BT-122	(TD)	1/48

COLOR-TV

Admiral Chassis M25	(TL)	4/27
Audio Output Module, Magnavox 612046-202	(CF)	5/47
Board and Module Modifications, Magnavox Chassis T979/989	(CF)	2/44
Brightness and Contrast Control Adjustment, Admiral Chassis M10	(TD)	11/6
Buzz or Hum at Low Setting of Volume Control, Philco-Ford Chassis 22QT80, 21KT40/41	(TD)	10/14
Cleaning Precautions, Magnavox 21 Detent Tuner	(CF)	4/57
Components Kit, RCA No. 199006	(NP)	10/48
Digital Channel-Indicator Dimmer Circuit, Magnavox Chassis T989	(TD)	8/10
Dressing of Focus Capacitor, Zenith Chassis 19DC12/22/28	(CF)	2/45
Eight-Function Remote Control, Magnavox Chassis T989	(CF)	6/47
Excessive Contrast, Magnavox Chassis T989	(CF)	2/44
Failure of Resistor R742, Magnavox Chassis T924/939/950	(CF)	2/44
GTE Sylvania TV Chassis E06	(TL)	5/23
GTE Sylvania TV Chassis E06-2, Part 2	(TL)	6/18
High-Voltage Repair Kit, Tele Matic Model HVK630	(NP)	2/51
High-Voltage "Ticking/Sizzling" Sounds, General Electric Chassis "C"	(TD)	12/40
Hookup to Test Fixtures, Magnavox Chassis T989	(TD)	11/9
Horizontal Bending or Pulling in Picture, Admiral Chassis K18, K19 Series	(CF)	5/46
Horizontal Deflection Tube, RCA Triple-Boarded 6MJ6/6LQ6/QJE6C	(TD)	8/10
Horizontal Weaving, MGA Model T50	(CF)	2/43
How and Why Trapezoidal		2/27
Hum at Low Volume Level, Magnavox Chassis T989	(CF)	4/57
Hum Bar in Picture at 60 Hz Rate, Admiral Chassis K19 Series	(CF)	8/38
Hum Bar, Magnavox Chassis T948	(CF)	5/47
Intermittent Brightness Variation, Magnavox Chassis T989	(CF)	4/57
Intermittent or No Video and No Sound with White Raster, Admiral Chassis T14K10/T41K10 Series	(CF)	5/46
Loss of Sound, Admiral Models 5L5851, 5L5853, 5L5855	(CF)	8/38
Magnavox, TV Chassis T982, Part I	(TL)	2/23
Magnavox, TV Chassis T982, Part II	(TL)	3/23
Medium Level Snow on UHF Channels Using VVC Tuner, Philco-Ford Chassis 4C572/4CY91	(TD)	11/8
Modification for CATV Systems, MGA Chassis T50	(CF)	2/43
Modification for CATV Systems, MGA Chassis T50 Series	(CF)	1/46
Modifications, Magnavox Chassis CE	(TD)	8/10
Module Cross-Reference Guide, Zenith	(CF)	2/46
Module Removal, Magnavox Color TC Chassis T995	(TD)	12/41
New in Color TV for 1975—Part I		9/16
New in Color TV for 1975—Part II		10/24
New in Color TV for 1975—Part III		11/28
New in Color TV for 1975—Part IV		12/20
No Color, Admiral Chassis K10	(TD)	12/40
Noise Immunity Circuits, Motorola TV Color/Video Panel LA/MA/WA	(CF)	4/57
Panasonic Model CT-944	(DS)	3/50
Picture Tube/Deflection Yoke Replacement, Admiral Chassis M10	(TD)	10/2
Picture Tube Repairs		5/33
Power Supply Diode Failures, Magnavox Color TV Chassis T981/T982/T987	(TD)	12/40
Power Supply Module M900 (A8926-1), Admiral Chassis M25	(CF)	8/39
Quick-On Wiring, Magnavox Chassis T995	(TD)	10/12
Remote Control UHF AGC Improved, Magnavox Chassis T989	(CF)	7/47
Replacement Color Picture Tubes—Propping Up Servicer's Profile		8/24
Replacement Picture Tube, RCA "Colorama A"	(DS)	9/56
Ringed Bars on Left Side of Picture, Magnavox Chassis T989	(CF)	2/44
Sense and Nonsense Color TV "Case History" Faults Vector Diagram	(CF)	1/44
Service Hint, Admiral Chassis 3K19	(TD)	7/46
Servicing Solid State AGC Circuits		11/24
Solid-State Tubes, EDI	(NP)	5/54
Solving Sync Problems in Solid-State TV		12/25
Sony's Wide-Angle Trinitron Color TV	(TL)	8/14
Sound Problems, MGA Models CH160, CH190, CH191	(CF)	8/40
Test Rig, Tele Matic Model CJ	(NP)	3/47
The Making of a Color TV Picture Tube		4/46
Thin Vertical Line Near Left Edge of Screen, Motorola TV Chassis, TS-934	(TD)	7/47
Troubleshooting Solid-State Multivibrators		12/28
Troubleshooting the Power Supply Magnavox TV Chassis T989	(CF)	3/43
TV High-Voltage Tripler, Motorola HEP R3201	(NP)	2/18
Vector Diagrams, General Electric	(CF)	1/44
Vertical Black Line at Top and at Bottom of the Screen, Magnavox	(TD)	11/9
Vertical Line on Left Side of Raster, Magnavox Chassis T979	(CF)	8/39
Vertical Oscillator/Drive Module 703616-1, Magnavox	(CF)	2/45
Vertical-Output Transistors, Admiral Chassis, M24/M25/M30	(TD)	9/14
Vertical Problem and Yoke Capacitor C16, Magnavox "D" Panel 703505-1	(CF)	5/46
Vertical Shaded Lines, General Electric Chassis HE	(CF)	1/45
Vertical Shading Bars, Magnavox Chassis T995	(TD)	10/12
Voltage Sensor Circuit, Zenith Chassis 25DC57	(CF)	1/46

COMMERCIAL TWO-WAY

FM Transceiver, Genave Model GTX-100	(DS)	4/67
Superior Baby Foods		2/31
Transceiver, Com Data Model HT-910	(DS)	4/66
VHF High Band Monitor/Receiver, Channel Master Model 6258	(DS)	12/46

COMMUNICATIONS

CB

CB Mobile Radio, E.F. Johnson Model 130	(DS)	4/66
Servicing Two-Way Radio		2/34
SSB/AM CB Two-Way Radio, Tram Corp. Diamond 60	(DS)	5/57
SSB/CW Transceiver, Hallicrafter Model FPM-300 Mark II	(DS)	9/43
The Expansion of Citizens Band		12/34
Transceiver, Fanon/Coupler Corp., Rebel 234	(DS)	1/56
Two-Way CB Receiver, Dynascan Model CAM-89	(DS)	12/49

MERCHANDISING

Antenna Display, RCA Model MU-1937	(DS)	10/53
Car Stereo Display, Channel Master Car Stereo-Center	(DS)	9/56
Car Stereo Display RCA Model MDS-1305	(DS)	1/55
CB Parts/Accessories Program, GC Electronics No. 49-810	(DS)	12/46
Consumer Products Displays, Channel Master	(DS)	12/48
Digital Clock, General Electric Co.	(DS)	12/47
Display Advertisements, General Electric	(DS)	7/50
Effective Advertising for the Service Dealer		8/26
Electric Sign, BSR	(DS)	9/54
Electronic Products, Mallory "Desert Deal"	(DS)	9/55
Electronic Security Systems—A Natural for Electronic Servicers		10/36
MATV System Display, Jerrold Electronics	(DS)	12/46
Monitor Receiver, Electrosonic Electro-Monitor	(DS)	9/53
Needle and Cartridge Display, Pageant/MA Miller	(DS)	12/48
Needle Merchandiser, EV-Game "Needle Finder"	(DS)	12/48
Selling TV Antennas to CATV Subscribers		4/50
Stereo Speaker Merchandiser, Innovative Audio Systems "Speaker Tree"	(DS)	10/54
Stereophone Display, RCA Model MDA-1222	(DS)	3/50
System Offers Three Ways to Build Receiver Sales		1/23
Telephone Answerer Display, BSR Phone Butler	(DS)	9/57
TV Antenna Display, RCA Model MLU-1606	(DS)	6/57

RADIO

AM/FM Receiver, Superscope, Inc.	(DS)	1/54
AM/FM Weather Band Radio, Panasonic Model RC-6304	(DS)	10/53
Coils and Transformers—A Perspective for Technicians		11/16
Dial Cord Guide Replacement, RCA Tuner/Amplifier Models VZT100/VST113	(TD)	3/44
FM/AM/Radio/Cassette Recorder, Sony Model CF-310	(DS)	5/58
Four-Channel System, Panasonic Model SA-8000X	(NN)	1/20
Four-Channel Receiver, Sylvania Model RQ3746	(DS)	4/66
Multi-Band Portable Radio, Magnavox Model 3092	(DS)	11/47
Multi-Band Radio, Magnavox, Model 3090	(DS)	7/50
Portable Radio, General Electric Model P4970	(DS)	6/59
Stereo System, Magnavox Model E1018	(DS)	2/52
Volume Control, Admiral Model YH401	(TD)	7/46

OFFICE EQUIPMENT

Digital Clock/Calculator, RCA Model 3C3030	(NP)	2/49
Electronic Calculator, Texas Instruments Model TI-2550	(NP)	3/48
Phone Answering System, Channel Master Model 6000	(DS)	10/56
Telephone Answerer, Phone-Mate, Inc., Model 300	(DS)	1/55
Telephone Answering/Recorder System, Ford Industries Memory Phone	(NP)	8/45
Telephone Silencer, Diversitron Inc.	(DS)	1/54

SECURITY & SURVEILLANCE SYSTEMS

Alarm Installers' Tool Kit, Mountain West Alarm Model MW-700	(NP)	3/46
Alarm System, PLC Electronics Inc. Model 740	(NP)	1/52
Electronics in Modern Hospitals—A Varied and Vital Role		5/36
Electronic Security Systems—A Natural for Electronic Servicers		10/36
Electronic Watchman, Dytron Inc. "The Care Taker"	(NP)	2/48
Home Alarm Sets, Master Lock Co. "Snap On"	(DS)	10/53
Motion Detection System, Mountain West Alarm Model M4	(DS)	12/48
Superior Baby Foods		2/31

SEMICONDUCTORS (General)

Current Gain		6/44
Bipolar Transistors, What Every Good Technician Should Know		6/42
About Replacing Them		6/42
Collector Voltage		7/18
Conventional Bipolar Power Transistors		7/17
Darlington Power Transistors		3/30
Discrete Semiconductor Devices		8/28
FET Theory		8/28
Field-Effect Transistor Fundamentals		9/30
High-Voltage Regulators		9/31
High-Voltage Triplers		3/31
Integrated Circuits		10/50
Integrated Circuits and Modules, GTE Sylvania ECG 1000 Series	(NP)	6/45
Linearity		1/36
LASCR		1/31
LED's		9/28
Low-Voltage Power Supplies		3/32
Modules		1/31
Optoelectronics, ABC's of		6/45
Output Capacitance		1/33
Photoconductive Cell		1/36
Photo Coupler		1/34
Photodiode		1/34

Photoemissive Cell	1/33	Ignition or Powerline Interference	3/27
Photo FET	1/35	Picture Tube Repairs	5/33
Phototransistor	1/35	Product Safety Maintenance, Admiral	(TD) 7/46
Photovoltaic Cell	1/33	Servicing Solid-State AGC Circuits	11/24
Power Dissipation	6/43	Seventy Detent UHF Tuner Selector Knobs, Admiral Current TV Models	(TD) 10/12
Rectifier Replacement	5/31	"Snowy" Picture	3/29
Rectifier Theory	5/30	Sockets, Zenith Kit No. 39	(NP) 4/65
Reverse Breakdown Voltage	6/43	Solid-State Tubes, EDI	(NP) 5/54
Semiconductor Diode Theory, Testing and Replacement	5/28	Solving Sync Problems in Solid-State TV	12/25
SCR's and Power Transistors	7/14	Strong Local Channel Interferes with Distant Channel	3/28
Testing and Replacement of Discrete Semiconductor IC's and Modules	3/30	Troubleshooting Solid-State Multivibrators	12/28
The Dual-Gate JFET	8/31	TV Interference—Causes and Cures	3/27
The MOSFET	8/31	TV Remote Control, Jerrold Electronics Model TRC-12	10/54
The SCR	7/14		
Transistors, International Rectifier Corp.	10/49		
Transistors, IRC Kit DK20	(NP) 8/42		
Troubleshooting SCR Circuits	7/14		
Troubleshooting Solid-State Power Supplies	9/28		
Varactor Tests	5/29		
Varactor Theory	5/28		
Zener Diode Tests and Replacement Selection	5/30		
Zener Diode Theory	5/29		

SERVICE AIDS

A Realistic Approach to TV Tuner Trouble	10/20
Capacitor Mount Adapters, Sprague Products Inc., Type PC-8	(NP) 6/52
Chemical Cleaner, CRC Chemicals Lectra Clean	(NP) 10/48
Cleaning Aerosol, Falcon	(NP) 2/51
Contact Cleaner, CRC Chemicals Inc.	(NP) 6/49
Contact Cleaner, 3M Co., No. 1613	(NP) 8/43
Electronic Chemicals, Workman	(NP) 2/49
High-Voltage Repair Kit, TeleMatic Model HVK630	(NP) 2/51
Omni-Direction Tuner Spray Nozzle, Tech Spray "Omni-Spra"	(NP) 12/42
Service Chemical Cole-Flex Corp. CD-250	(NP) 4/63
Solder, GC Electronics No. 9132	(NP) 5/51
Tuner Cleaning Pads, PTS Electronics Inc.	(NP) 6/52
Tuner Lubricant/Cleaner, PTS Electronics, Inc., No. 108	(NP) 12/46
TV Tuner Cleaner/Lubricating Kit, General Electric	(NP) 12/42

SHOP EQUIPMENT

Alarm Installers' Tool Kit, Mountain West Alarm Model MW-700	(NP) 3/46
Bench Power Supply, Central Components Co., Model C621	(NP) 1/53
Burnishing Tool, Utica Tool Co. Inc.	(NP) 7/48
Cable Sheath Stripper, P.K. Neuses, Model N-2878	(NP) 5/54
Cable Stripper, ITT Holub Industries "Roto-Blade"	(NP) 10/49
Cordless Soldering Iron, Weller	(NP) 11/43
Desoldering Kit, Enterprise Development Corp., Model 500K	(NP) 2/50
Desoldering Tips, Enterprise Development Corp.	(NP) 12/42
Desoldering Tool, Edsyn No. DS017	(NP) 2/48
Desoldering Tool, Solder Removal Co.	(NP) 1/49
Drill Bit, Unibit Corp., Model II	(NP) 10/50
Electrical Plug Lock, Mercury Manufacturing	(DS) 5/58
Hand Tools, ITT Holub Industries	(NP) 3/48
Head Demagnetizer, Nortronics Co., Model QM-202	(NP) 10/52
Inverter, EPS Co., Model TI-250B	(NP) 8/43
Metric Hex Key Set, Vaco No. 70156	(NP) 4/62
Metric Hex Socket Screwdriver, Xcelite No. LN-8MM	(NP) 5/52
Metric Nutdriver Set, Xcelite Model PS-121MM	(NN) 3/20
Mobile Shelf Carrier, SGL Waber Electric Model Low	(NP) 5/54
Parts Case, General Electric ETRS-5980	(NP) 8/42
Parts Chest, AMP Special Industries	(NP) 6/53
Parts Rack, RCA Model QT	(DS) 8/49
Parts/Storage Bins, Kole	(NP) 9/51
Relay Service Tool Kit, P.K. Neuses, Inc., Model TK-18	(NP) 4/63
Screwdriver Sets, Xcelite Model 99-PS41MMBP	(NP) 4/60
Self-Adjusting Wire Stripper, ITT Holub No. 18-10	(NP) 5/50
Self-Adjusting Wrench, Brookstone Co.	(NN) 2/8
Service Table, RCA Model 10J107	(NP) 1/49
Socket Wrench, P.K. Neuses, Inc., Model N-311	(NP) 2/50
Solder, GC Electronics No. 9132	(NP) 5/51
Soldering Iron Accessory, Edsyn, Inc., No. HA120	(NP) 4/64
Soldering Iron Holder, Wolo Manufacturing Corp.	(NP) 9/50
Soldering Iron Tip Cleaner, Solder Removal Co., "Re-Tip"	(NP) 6/49
Soldering Iron, Ungar No. 555	(NP) 11/45
Soldering Iron, Wahl Model 7500	(NP) 4/60
Soldering Iron, Wall-Lenk Manufacturing Co.	(NP) 3/47
Temperature Probe, Edsyn, Inc., Part No. TP110	(NP) 3/48
Test Rig High-Voltage Meter, TeleMatic Model HVM 3900	(NP) 12/43
Test Rig, TeleMatic Model CJ	(NP) 3/47
Tool Case, Howe Industries	(NP) 1/52
TV Test Rig, Telematic, Model MJ-195	(NP) 10/50
Voltage Regulator, Air-Vac Engineering Co.	(NP) 7/48
Wire Unwrap Tool, O.K. Machine and Tool Corp., Model UW 2832C	(NP) 1/49
Wiring Tool and Crimper, Vaco Products Co., Wireplier	(NP) 5/55

TELEVISION (General)

A Realistic Approach to TV Tuner Troubles	10/20
Coax On Twin Lead-Making the Choice	4/32
Coils and Transformers—A Perspective for Technicians	11/16
Fault Finding in MATV Systems	4/36
Flameproof Film Resistors RCA	(NP) 12/42
Flip-Flops (Bi-Stable Multivibrator) Sylvania	(TD) 5/48
FM Interference	3/28
Ghosts and Smears	3/29
How and Why—Trapezoidal	2/27
How to Tackle a Real Dog	2/33

TEST INSTRUMENTS


AC Leakage Tester, RCA Model WT-540A	(NP) 5/50
Amplifier Checker, Sencore Model TC28	(NP) 9/49
Audio Sweep/Function Generator, Wavetek Model 30	(NP) 6/53
B & K Precision Model 1431 Oscilloscope	(NP) 4/52
Circuit Tester, Western Technical Products Safetone Tracer	(NP) 9/49
Color Bar Generator, Hickok Model 239	(TR) 2/36
Communications Counter, Anadex Model CF-710	(NP) 12/45
Continuity Checker, Thomas & Betts E-Z-Coder Tone Tracer	(NP) 10/48
Digital Multimeter, Ballantine Laboratories Model 3/24	(NP) 10/48
Digital Multimeter, B & K Precision Model 282	(TR) 6/38
Digital Multimeter, Data Technology Corp., Model 20	(TR) 3/42
Digital Multimeter, Data Technology Corp., Model 41	(NP) 9/48
Digital Multimeter, Data Technology Corp., Model 45	(NP) 4/64
Digital Multimeter, California Instruments Model DMM-51	(NP) 6/49
Digital Multimeter, Digitec's Model 2110	(NP) 9/51
Digital Multimeter, Digitec Model 2210	(NP) 9/51
Digital Multimeter, Keithley Model 168	(NP) 5/51
Digital Multimeter, MITS, Inc., Model DVM	(NP) 2/50
Digital VOM, Dana Laboratories, Inc.	(NP) 2/18
Digital VOM, Simpson Electric Co., Model 460-2	(NP) 5/50
Digital VOM, Simpson Model 360	(NP) 3/46
Distortion Analyzer, Tucker Electronics Co., Model 510A	(NP) 6/54
Dual-Channel, Triggered-Sweep Scope, Hewlett-Packard Model 1220A	(TR) 9/44
FET/Transistor Tester, Heathkit Model IT-121	(TR) 10/40
Field-Strength, Ascom Electronic Products Model ASM-105	(NP) 10/51
Field-Strength Meter, Sadelco Inc., Model FS3B VHF/UHF	(NP) 10/52
FM Alignment Generator, Sound Technology Model 1000A	1/23
FM Deviation Meter, Radio Specialty Mfg. Co., Model 1163-63-1	(NP) 11/43
Frequency Counter, Heathkit Model 1B-1103	(NP) 4/64
Frequency Counter, Hewlett Packard Model 5381A	(TR) 12/38
Frequency Counter, John Fluke Mfg. Co., Inc. Model 1980A	(NP) 1/51
Frequency Counter, Scarpa Model SC-1A	(NP) 2/50
Frequency Counter, Systron-Donner Corp., Model 6252	(NP) 2/50
Frequency Counter/Timer, Simpson Electric Co., Model 7016	(NP) 12/42
Function Generator, Datapulse Model 400	(NP) 2/48
Function Generator, Krohn-Hite Corp., Model 5200	(NP) 3/49
High-Voltage Probe, Triplett Model 79-70	(TR) 12/39
High-Voltage Test Probe, Pomona Electronics Model 4000	(NP) 5/53
Intermodulation Distortion Analyzer, Crown Model IMA	(NP) 1/20
Multi Function Counter, John Fluke Mfg. Co., Model 1900A	(NP) 10/50
Multitester, Weltron Co., Model 51-150	(NP) 4/62
Oscilloscope, Jermyn Socex 40-10	(NP) 6/52
Oscilloscope, Lectrotech Inc., Model T0-55	(NP) 6/50
Oscilloscope Probe, Valor Enterprise, Inc.	(NP) 7/48
Oscilloscope/Quicktracer, RCA Model WD-33B	(TR) 11/38
Oscilloscope, Scores Unlimited Inc.	(NP) 8/44
Oscilloscope, Sencore Inc., Model PS29	(NP) 10/52
Oscilloscope, Simpson Electric Co., Model 459	(NP) 9/48
Oscilloscope, Systems Electronic, Inc., Model 77	(NP) 8/45
Oscilloscope, Systems Model 57	(NP) 5/52
Picture Tube Tester, Sencore Inc., "Big Mack"	(NP) 2/51
Portable Tester, Lisson Electronics Model SCELBI	(NP) 8/44
Power Meter, Gold Line Model GLC 1087	(NP) 12/45
Recorder Test Set, 3M Model 6500	(TR) 1/41
Resistor Substitution Unit, Phipps O. Bird Model 236-A	(NP) 10/49
RF Signal Generator, Dynascan Corp., Model 2050	(NP) 12/42
RF Wattmeter, Bird Model 4371	(NP) 4/61
Scope, Leader Instruments Model LBO-511	(NP) 2/48
Scope, Simpson Electric Co., Model 455	(NP) 1/50
Semiconductor Curve Tracer, Heathkit Model IT-1121	(NP) 6/54
Semiconductor Tester, Krystal Kits, Jinni-1	(NP) 9/50
Signal Conditioner, Sound Technology, Model 1100A	1/23
Signal Generator, Exact Electronics Model 123 VCF	(NP) 1/52
Substitute Tuner, TeleMatic Model KT730	(NP) 5/50
Sweep/Function Generator, Exact Electronics Model 195	(NP) 8/47
TeleMatic Tuner-Mate Substi-Tuner, TeleMatic Model KT730	(TR) 5/40
Test Rig High-Voltage Meter, TeleMatic Model HVM3900	(NP) 12/43
Transistor/FET Tester, RCA Model WT-524A	(NP) 10/52
Transistor/FET Tester, Sencore, Inc., Model TF26	(NP) 3/49
Tuner Subber, Castle TV Mark IV	(NP) 3/49
Universal Color Bar Pattern Generator, Leader Model LCG-395	(TR) 7/30
VHF/UHF Portable TV Tuners, PTS Electronics Model 3001	(NP) 10/52
VOM, Mura Model FET-300	(NP) 3/20
VOM, Simpson Electric Co., Model 265	(NP) 8/42
VOM, Triplett Corp., Model 310	(NP) 9/51
VOM, Triplett Corp., Model 615	(NP) 8/47
VOM, Triplett Corp., Model 615	(NP) 2/50

VEHICLES

Commercial Vehicle, Champion Home Builders	(NP) 4/60
Truck Interior Shelf/Bin Units, Handi Van Kole Enterprises	(NP) 12/45

ARTICLE INDEX

ABC'S OF OPTOELECTRONICS	1/31
A REALISTIC APPROACH TO TV TUNER TROUBLES	10/20
BALANCING CHANNELS IN MATV SYSTEMS	10/32
COAX OR TWIN LEAD—MAKING THE CHOICE	4/32
COILS AND TRANSFORMERS—A PERSPECTIVE FOR TECHNICIANS	11/16
DOES SERVICING HAVE A FUTURE?	7/20
EFFECTIVE ADVERTISING FOR THE SERVICE DEALER	8/26
ELECTRONICS IN MODERN HOSPITALS—A VARIED AND VITAL ROLE	5/36
ELECTRONIC SECURITY SYSTEMS—A Natural for Electronic Servicers	10/36
ET/D READER PREFERENCE SURVEY	11/51
FAULT FINDING IN MATV SYSTEMS	4/36
GETTING MORE OUT OF THAT NEW SIGN	1/30
GOING TO REMODEL THE STORE? HERE'S A GOOD CHECK LIST	2/30
HOW AND WHY—TRAPEZOIDAL	2/27
HOW TO TACKLE A REAL DOG	2/33
INTERPRETING MATV AMPLIFIER SPECS	9/38
MANAGING TO LEARN AND LEARNING TO MANAGE	1/42
MANAGING TO LEARN & LEARNING TO MANAGE	3/41
MANAGING TO LEARN AND LEARNING TO MANAGE	5/42
MANAGING YOUR BUSINESS—Retirement Programs for Owner/ Employees	3/39
MATV TAPS—SELECTION AND USE	7/22
MODERN SERVICING TECHNIQUES—Bipolar Transistors—What Every Good Technician Should Know About Them	6/42
MODERN SERVICING TECHNIQUES—Field Effect Transistor Fundamentals	8/28
MODERN SERVICING TECHNIQUES—SCR's and Power Transistors	7/14
MODERN SERVICING TECHNIQUES—Semiconductor Diode Theory, Testing and Replacement	5/28
MODERN SERVICING TECHNIQUES—Testing and Replacement of Discrete Semiconductors, IC's and Modules	3/30
MODERN SERVICING TECHNIQUES—Troubleshooting Solid-State TV Power Supplies and Regulator Circuits	9/28
NEW IN COLOR TV FOR 1975—Part 1	9/16
NEW IN COLOR TV FOR 1975—Part 2	10/24
NEW IN COLOR TV FOR 1975—Part 3	11/28
NEW IN COLOR TV FOR 1975—Part 4	12/20
PROFITABLE AND COMPETITIVE PRICING OF SERVICE LABOR	12/12
REPLACEMENT COLOR PICTURE TUBES—Propping up Servicers' Profits	8/24
SELECTING COMMERCIAL AUDIO AMPLIFIERS	8/34
SELECTING SPEAKERS FOR COMMERCIAL AUDIO SYSTEMS	6/30
SELLING TV ANTENNAS TO CATV SUBSCRIBERS	4/50
SENSE AND NONSENSE COLOR-TV "CASE HISTORY" FAULTS	1/37
SERVICING SOLID-STATE AGC CIRCUITS	11/24
SERVICING TWO-WAY RADIO	2/34
SOLVING SYNC PROBLEMS IN SOLID-STATE TV	12/25
SONY'S WIDE-ANGLE TRINITRON COLOR TV	8/15
SQUARE-WAVE TESTING OF AUDIO AMPLIFIERS	9/32
SUPERIOR BABY FOODS	2/31
SYSTEM OFFERS THREE WAYS TO BUILD RECEIVER SALES	1/23
TECH BOOK DIGEST—Electronic Adjustments in Auto Tape Players	7/38
TECH BOOK DIGEST—Picture Tube Repairs	5/33
TECH BOOK DIGEST—Stereo Audio Measurements	6/24
TECH BOOK DIGEST—Troubleshooting Solid-State Multivibrators	12/28
TEKLAB Report—Admiral Color TV Chassis M25	4/27
TEKLAB Report—GTE Sylvania Color TV Chassis E06—Part 2	6/18
TEKLAB REPORT—Magnavox Color TV Chassis T982—Part 1	2/23
TEKLAB REPORT—Magnavox Color TV Chassis T982—Part 2	3/23
TEKLAB REPORT—Sylvania Color TV Chassis E06	5/23
TEST INSTRUMENT REPORT—B & K Precision Model 282 Digital Multimeter	6/38
TEST INSTRUMENT REPORT—B & K Precision Model 1431 Trigger-Sweep Scope	4/52
TEST INSTRUMENT REPORT—Data Technology Model 20 Digital Multimeter	3/42
TEST INSTRUMENT REPORT—Hewlett-Packard Model 1220A Oscilloscope	9/44
TEST INSTRUMENT REPORT—Hickok's Model 239 Color Bar Generator	2/36
TEST INSTRUMENT REPORT—Leader LCG-395 Universal Color Bar Pattern Generator	7/30
TEST INSTRUMENT REPORT—Measuring DC Beta with the Heathkit Model IT-121 FET/Transistor Tester	10/40
TEST INSTRUMENT REPORT—RCA Model WO-33B Oscilloscope	11/38
TEST INSTRUMENT REPORT—TeleMatic Tuner-Mate Substi-Tuner Model KT 730	5/40
TEST INSTRUMENT REPORT—Reviewing Specifications for 3M's Model 6500 Recorder Test Set	1/41
THE EXPANSION OF CITIZENS BAND	12/34
THE MAKING OF A COLOR PICTURE TUBE	4/46
TV INTERFERENCE—Causes and Cures	3/27

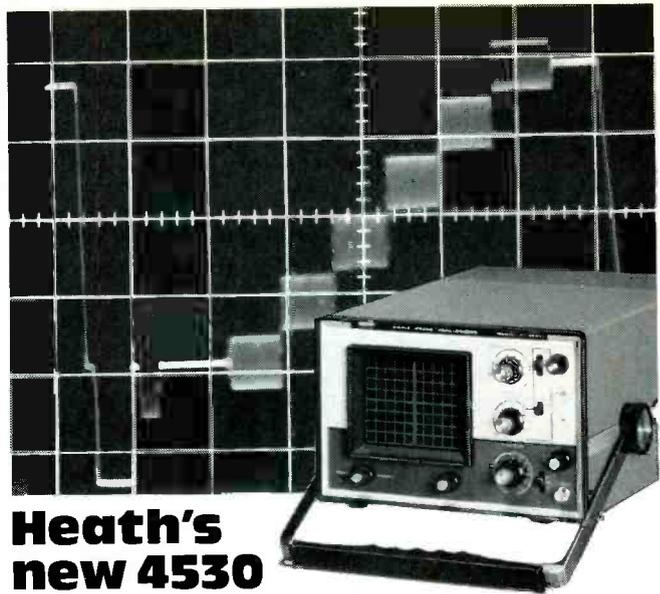

Heath's new 4530 a professional TV service scope with a practical price

It's hard to find a better TV service scope value than the new Heathkit 4530. Features like TV coupling, DC-10 MHz bandwidth, wide-band triggering capability, sensitive 10 mV/cm vertical input and calibrated X-channel input make it a versatile, easy-to-use scope every service technician will appreciate.

Trigger circuits are digitally controlled, requiring only a level control and a slope switch. Various trigger signals can be selected: a sample of the vertical input signal, a sample of the line voltage or an externally applied trigger signal. In the TV trigger coupling mode, the 4530 can be easily triggered on the vertical or horizontal signal in a composite video signal such as the one shown above. Trigger bandwidths are *guaranteed* to 15 MHz, AC and DC coupled. A low-pass filter with 1 kHz cut-off is used in the TV coupling mode.

High or low frequency waveforms are no problem since the 4530's wide range of time bases can be switched from 200 ms/cm to 200 ns/cm. And any sweep can be expanded five times.

The 4530 is one of the few single trace scopes available with two input channels. For true X-Y operation, a calibrated X-input is provided with maximum sensitivity of 20 mV/cm.

The 4530 is easy to operate, easy to service and offers a lot of performance per dollar. The IO-4530 is available in easy-to-assemble kit form for only \$299.95*. Or order the factory assembled and calibrated SO-4530, just \$420.00*.



Send for your free Heath catalogs

The latest Heath/Schlumberger Assembled Instruments Catalog features a complete line of high performance, low cost instruments for service and design applications. Our '75 Heathkit Catalog describes the world's largest selection of electronic kits — including a full line of lab and service instruments. Send for your free copies today.

HEATH COMPANY		HEATH Schlumberger	
Dept. 24-1 Benton Harbor, Michigan 49022			
<input type="checkbox"/> Please send the 1975 Heathkit Catalog. <input type="checkbox"/> Please send the latest Heath/Schlumberger Assembled Instruments Catalog.			
Name _____			
Title _____			
Company/Institution _____			
Street _____			
City _____		State _____ Zip _____	
<small>*MAIL ORDER PRICES; F.O.B. FACTORY. PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>			
			TE-316

... for more details circle 113 on Reader Service Card

take your pick

PROFESSIONAL SCREWDRIVERS

BY **Xcelite**[®]

LARGEST RANGE, GREATEST VARIETY



What are you driving? Slotted, Phillips, Frearson, Reed & Prince, Allen hex, clutch head, ScruLox[®], Bristol Spline, or Pozidriv[®] screws? Xcelite makes screwdrivers for every type and size. Metrics, too.

• from 2-1/8" miniatures to huge 2 footers.

• .040" to 7/16" tip widths.

• round or square blades.

• tough, forged alloy steel

• nickel chrome, black oxide finish, or insulation coated.

• fixed-handle or interchangeable blades.

• straight and tee handles — regular and ratcheting

• available individually or in handy kits.

• Made in U.S.A. to highest standards.

Ask your local distributor or write . . .

**Weller-Xcelite
Electronics Division**



The Cooper Group

ORCHARD PARK, N. Y. 14127

. . . for more details circle 134 on Reader Service Card

TEST INSTRUMENT REPORT



Tekelec Model TA 357 Digital Multimeter

■ Equipped with a 3½ digit, field-effect, transmissive, liquid crystal display, the Model TA 357 multimeter is capable of measuring DC and AC voltages ranging from 100 microvolts to 19.99 Kv (50 Kv with optional probe), DC and AC currents ranging from 100nA to 199.9ma, and resistances ranging from .1 ohms to 199.9 K ohms. In addition, a special + 10v DC output permits measurement of leakage currents and conductance (up to 200 x 10⁻⁶mho).

Functions and ranges are selected by eight interlocked pushbuttons on the front of the instrument. Selection of either the voltage or current measuring function is accomplished by pushing in the buttons labeled "V" or "I," respectively, and then either pushing *in* the AC/DC button for AC measurement or releasing it to the *out* position for DC measurement. Illumination of the letters "AC" or "DC" on the right of the numerical display automatically tells you whether the instrument is in the AC or DC measuring mode. In the DC mode, the polarity of the voltage or current is automatically indicated by the appearance of either a - or + sign on the left of the numerical display. In the current measuring mode ("I" button pushed in), the letters "mA" also appear to the right of the numerical display. Selection of the resistance measuring function is accomplished by pushing in the button labeled "Ω," which causes the designa-

tion "KΩ" to appear to the right of the numerical display.

Selection of one of the four ranges of the TA 357 is accomplished by pushing in either the ".2," "2," "20" or "200/LINE TEST" buttons. The decimal point in the display is automatically positioned by the range push-buttons.

Zeroing of the instrument is accomplished by a thumbwheel type control labeled "Zero" on the top of the instrument.

If the quantity being measured exceeds the full-scale capability of the range selected, the display flashes on and off, clearly indicating the over-range condition.

The TA 357 is designed to be powered by 117 VAC, 60 Hz but is available in an optional version which operates on 220 VAC, 50 Hz. The line voltage applied to the instrument is automatically measured and displayed without external probe connections when the ON/OFF/TEST switch is pushed down to the spring-loaded TEST position and the V, 200/LINE TEST and AC/DC BUTTONS are pushed in.

The multimeter is protected by a .25-amp fuse in the primary of the power supply and a .25-amp fuse in the input circuit. Both fuses plus a spare are located beneath a slide-out panel on the bottom of the instrument.

Input impedance in the voltage measuring modes is 10 megohms shunted by less than 100 pf of capacitance. The frequency range for AC voltage and current measurements is 40 Hz to 20 KHz.

Current through resistances being measured is 1 mA in the ".2" and "2" ranges, and .01 mA in the "20" and "200" ranges. The maximum voltage which can be safely applied to the input circuit in the voltage and resistance measuring modes is 480 volts p-p. In the current measuring modes, the input circuit appears as a short to input voltages in excess of 3.6 volts.

Tekelec's Model TA 357 is housed in a high-impact cyclocac case which is 2¾ inches high by 5¼ inches wide by 9½ inches deep.

Price of the TA 357 is \$179, complete with test leads and a 100:1 high-voltage (20 Kv) probe. An optional 50 Kv high-voltage probe is available for \$39.95. ■

For more information about this test instrument, circle 900 on the READER SERVICE CARD.

TECHNICAL DIGEST

The material used in this section is selected from information supplied through the cooperation of the respective manufacturers or their agencies.

MAGNAVOX

Radio Chassis R331/332—Diode Reversed

The Audio Driver modules used in these chassis, Part No. 703688-1, have diode D403 incorrectly screened on the PC board. Because of this error, the initial production of these chassis has the diode installed backwards. The symptoms that may occur are bass distortion and possible Automatic Protection Circuit Activation. Production is now installing the diode correctly. The correct polarity of the diode is cathode of D403 to emitter of Q408. These chassis are used in Model KE1570 and KE1580.

Radio Chassis R286—Schematic Correction

The schematic in Service Manual 1526 has two errors in the audio output section. Resistor R230 should be in parallel with D202 instead of D206. Resistor R231 should be in parallel with D203 instead of D207. The copper layout in the manual is correct.


Color TV Chassis—High Voltage Rectifier/Tripler Short

In cases of high voltage/tripler failure in early production TV sets using these chassis, there is a possibility that the horizontal output transformer, T302, and other associated components may be damaged. Other components to check when this type of failure occurs include: Capacitor C104, resistor R140, the power supply diodes, and the Video Delay module.

The possibility of multiple component failure can be prevented by changing R140 to a carbon film type 1K ohm resistor (Part No. 230214-1025). Whenever these early production units are in the shop, R140 should be changed to a carbon film type resistor as preventative maintenance. Elevate the resistor 1/4-inch above the PC board. Current production (identified by the numeral 2 as the last digit of the model number such as CE4360WA12) uses a carbon film resistor for R140.

Videomatic TV Sets—New LDR Holders

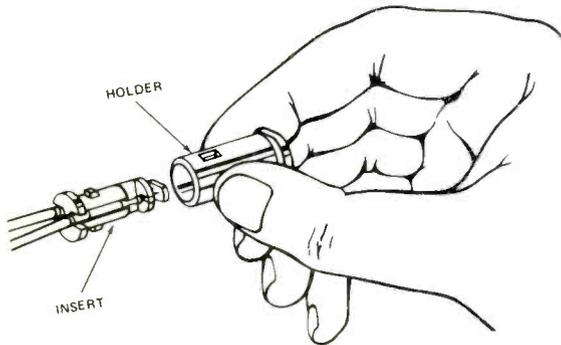A new LDR holder assembly has been developed to minimize the possibility of LDR damage from static discharges. The new assembly is made of two parts—the holder (Part No. 143593-1) and the insert (Part No. 143592-1). The entire assembly is still removable from the front of the instru-



ment as usual, but to separate the holder from the insert the holder must be gripped as shown in illustration and squeezed to unlock it. This new assembly may be used to replace all original holders with the part number 142848 or 143290. ■

the BIG ONE!

NEW IMPROVED

INSTANT-WELD Adhesive

Now a choice of 4 formulas . . . and in Big 1900 drop application container.

SAVE BIG only \$8.95
(less than 1/2¢ an application)

ORDER FROM
YOUR ONEIDA DISTRIBUTOR
OR DIRECT FROM US.



ONEIDA ELECTRONIC MFG. INC.

P.O. Box 678 — Dept. 761-D
Meadville, Pa. 16335

... for more details circle 121 on Reader Service Card

NEUSES

NUMBERING AND LETTERING KIT

Use for marking almost any type of background materials with non-fading, vivid, easy-to-read clean marking. Ideal for marking switchboard panels, junction boxes, sub-assemblies, chassis, cables, wire, etc.



Contents: Peg rubber stamps 3/4", 3/8", 1/4", 3/16", 1/8". A-Z letters, numbers and symbols. Stamp repair sets. Fuse capacity stamps 3/8" and 3/16". Ink tubes for vermillion, yellow, black, white. Inking ring, knife, brushes, cleaning fluid. Housed in sturdy steel carrying case. 12 1/4" long x 7 1/2" wide x 5" deep.

Write for new catalog on the most complete line of small tools for the telephone, communications and electronic industries.



P. K. Neuses, Inc.

Box 100 / Arlington Heights, Illinois 60006

PRECISION TELE-COMMUNICATION TOOLS

... for more details circle 122 on Reader Service Card

JANUARY 1975, ELECTRONIC TECHNICIAN/DEALER | 43

**DELUXE DIGITAL COLOR
CONVERGENCE GENERATOR**
NOW AT A PRICE EVERYONE
CAN AFFORD

ROCK SOLID PATTERNS
ALL IC COUNTDOWN CIRCUITS
QUARTZ CRYSTAL OSCILLATORS
2 FULL YEARS' WARRANTY



MODEL SG-200 \$79.95
reg. \$99.95

10 Patterns: Full & Gated Rainbow, 4 Crosshatch, 4 Dot, Die, Casted 1/8" Aluminum Case.



MODEL SG-150 \$59.95
reg. \$74.95

10 Patterns: B&W Bars, White Field, 4 Crosshatch, 4 Dot.



MODEL SG-100
ONLY \$47.95
reg. \$59.95

2 Patterns: 20 x 16 Crosshatch, 320 Dots, weight only 17 oz.

SPECIAL PRICE LIMITED TIME ONLY
FULL 15 DAYS MONEY BACK GUARANTEE

ELENCO ELECTRONICS INC.
8744 W. North Ter., Niles, Ill. 60648

312-692-6974

MODEL SG-_____

- My check or money order enclosed.
- COD—Add \$2.50 mailing & handling.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

DISTRIBUTORS' INQUIRIES INVITED


NEW PRODUCTS

Descriptions and specifications of the products included in this department are provided by the manufacturers. For additional information, circle the corresponding numbers on the Reader Service Card in this issue.

UHF MOBILE ANTENNA 700

Combines the most desired operating characteristics

The Antenna Specialists Co. has announced the development of a new antenna which combines all of the most frequently desired operating characteristics for UHF mobile antennas into one design. The Model ASP-830 features over 5 dB of gain and can handle 150 w of RF power continuously. It maintains a VSWR of less than 1.5:1 over a wide working bandwidth of at least 9 MHz, making it ideal for use in repeater systems or for broadband monitoring. It achieves its performance characteristics through the use of a pair of 5/8-wavelength radiators in a collinear design. Phasing is accomplished with a phasing coil assembly that is one-piece molded to the radiators. A threaded metal insert in the molded base provides the extra strength and durability of a metal-to-metal fitting.

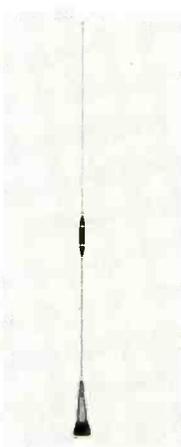

OSCILLOSCOPE 701

Compact size and lightweight

A compact 50 MHz dual-trace oscilloscope was introduced by Philips Test & Measuring Instruments, Inc., a subsidiary of North American Philips Corp. Designated the Model PM3240, the oscilloscope employs DC switching



for all functions. A magnesium alloy casting and a switching power supply

FREE EICO CATALOG

346 Ways To Save On Instruments!

EICO's Test Instruments line is the industry's most comprehensive because each instrument serves a specific group of professional needs. You name the requirement—from a resistance box to a VTVM, from a signal tracer to a scope, from a tube tester to a color TV generator, etc., you can depend on EICO to give you the best professional value. Compare our latest solid state instruments at your local EICO Electronics Distributor, he knows your needs best—and serves your requirements with the best values!

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO—283 Malta Street, Brooklyn, N.Y. 11207

30 years of service to the Professional Serviceman.




serve to reduce the size and weight. Basic specifications of the oscilloscope includes 5 mV/div. sensitivity at full bandwidth and 10 nanosecond/div. maximum sweep rate. The 50 MHz bandwidth and 7 nanosecond risetime can be displayed separate, alternate, chopped and X-Y modes. The high 1 MHz chopping rate helps to eliminate interference with displayed signals. The attenuator eliminates the need for external measuring of the X axis input. A separate delay timebase control has intensified screen indication and a 0.5 sec/div. to 10 nsec/div. range. A full 8 by 10 centimeter screen with a 10 kv accelerating potential enables easy and detailed viewing at even the narrowest one-shot pulses. Price is \$1470 without probes.

ACCOUNT COLLECTION SYSTEM 702

Simplifies follow-up and speeds payment of overdue accounts

Ever Ready Label Corp. has developed the DART (Delinquent Account Recovery Technique). The system is an extension of their line of collection stickers. In addition to the three Collection Stickers, other components of the system are: a rotary desk file with 3 by 5 Follow-Up Cards, and three small colored labels coordinated with the colors of the three Collection Stickers. When an account is overdue, basic data is entered on the Record Card and slipped onto the rotary file. Collection Sticker #1 (blue) is affixed to the statement to be mailed. The small colored label (also blue) is affixed to the edge of the card and becomes an indexed marker. The same

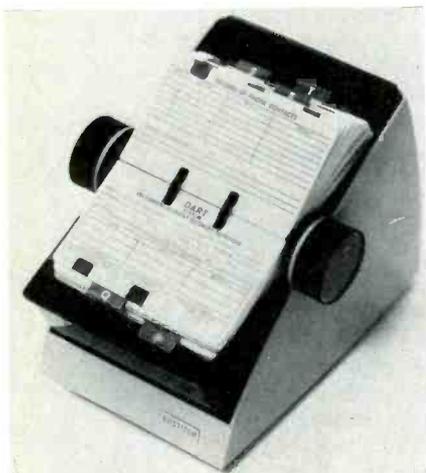

procedure is repeated with Collection Stickers #2 and #3, coordinated with the appropriate colored small labels. The Follow-Up Record Cards are printed on both sides and provide for the necessary current information. It also allows for personal phone contacts between statements. As partial

payments are made, they can be posted. And when payment is made in full, the card is easily pulled from the file. Price is \$79.95.

DIGITAL MULTIMETER 703

Features a frequency counter and can measure capacitance

A digital multimeter, featuring a 4½-digit Sperry planar display in 44 ranges has been announced by PECK/BOSS, Inc., Electronic Div. The Model 390 multimeter is a versatile bench type meter, a frequency counter and it can measure capacitance in seven ranges from 1 nano farad to 100 mi-



cro farads. The instrument has eight resistance scales from .1 ohms to 1000
continued on next page

**Pay \$9²⁵ for the PANTS.
Get a \$5⁹⁵ Shirt lettered
to advertise your business
FREE as a BONUS!**

**OFFER LIMITED:
One to a customer
and to new customers
only.**

WE WANT YOU to be our customer. And we'll do anything to make it happen! Why? Because once you've experienced the quality, value and long wear of our vast array of work garments and accessories—the business-building impact of our lettered garments—you'll do business with us for a long time. And that's the whole idea.

So, we'll give you a 65% Dacron/35% Cotton Permanent Press \$5.95 shirt free . . . lettered free . . . when you buy a pair of our Permanent Press Dacron/Cotton pants at regular price. One day's wear will convince you that we should be your work uniform source from now on!

PICK COLORS & SIZES HERE

PANTS COLORS: Navy blue, grey, green, blue or brown.


PANTS SIZES: Waist 28" thru 34";
Even 36" thru 50".
Inseams: 28" thru 35".

SHIRT COLORS: White, light grey, blue, green or tan.

NECK SIZES: Small, Med., Lg., Xlg., XXlg. (Short sleeves only with this offer). Just check exactly what you want on coupon below. Clip and mail with \$9.25. We pay all shipping charges. Satisfaction guaranteed.

ELIN MANUFACTURING CO.

Dept. 20, Rochester, Indiana 46975

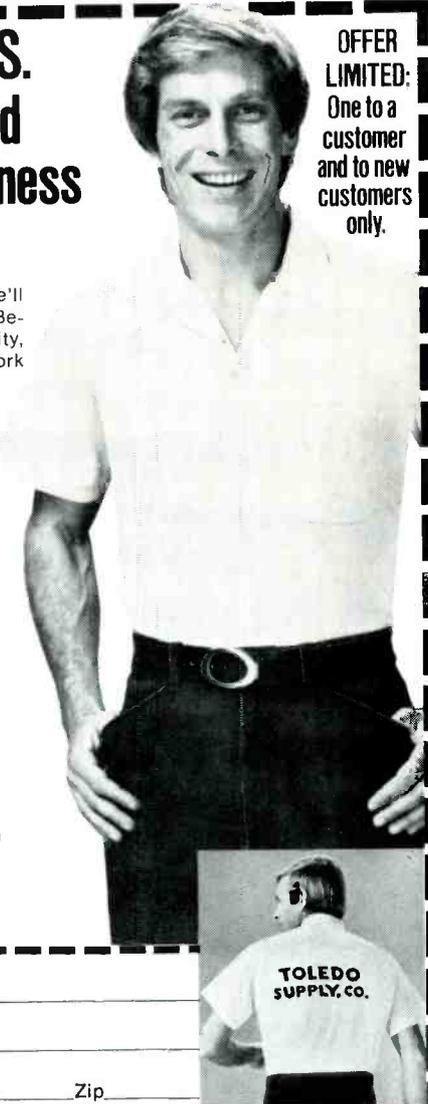

SHIP TO: _____
ADDRESS _____
CITY & STATE _____ Zip _____

Permanent Press PANTS: Color _____
Permanent Press SHIRT: Color _____
Waist _____ Size _____
Inseam _____ Short Slv. only

I enclose \$9.25. Ship postpaid
Mail entire ad and \$9.25 to
ELIN MANUFACTURING COMPANY
Dept. 20 Rochester, Ind. 46975.

Print lettering for shirt here:

Lettering color. Check one.

Red Blue Gold Green

. . . for more details circle 107 on Reader Service Card

ACA

**Chroma
POWER**


TV and FM ANTENNAS
AND ELECTRONICS

MR. DEALER — Return this ad with your letterhead for a FREE DEALER BONUS COUPON, CATALOG and the name of your nearest ACA distributor.

Mail to: P.O. Box 865, Burlington, IA 52601
Phone: 319-753-1625

... for more details circle 101 on Reader Service Card

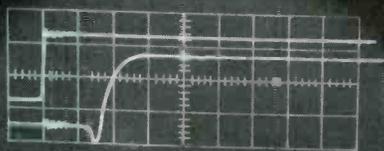Replacement Delay Lines for More Than 500 Color TV Models



Write for Cross Reference.

BELL INDUSTRIES / J. W. Miller Division

19070 REYES AVENUE • P. O. BOX 5825 • COMPTON, CALIFORNIA 90224

... for more details circle 103 on Reader Service Card

NEW PRODUCTS...

continued from preceding page

megohms full scale. Other features are 10,000 megohm input impedance on 10 v DC. Eight ranges of DC current from 1 μ a DC to 1 a full scale. The unit is overload protected by a fuse.

ANTENNA PREAMPLIFIER 704

Gain of over five times its input level

ACM has added a Model AA37, Antenna Preamplifier to its line. The unit has a 300-ohm antenna input and a 75-ohm output for use with MATV systems or in areas with high noise levels. The preamplifier boosts the signal at



the antenna where they are strongest and free from interference. The unit provides a gain of 16 dB or over five times the input level.

PORTABLE SOLDERING IRON KIT 705

Features pushbutton operation and is rechargeable overnight

General's Electric's Tube Products Dept. is making available to independent service dealers a cordless, portable soldering iron kit. Offering high wattage performance at low power, the iron's "Iso-Tip" soldering tip construction eliminates electrical leakage, need for grounding and possibility of damage to highly sensitive electronic components. Ready for use in 3-5 seconds, the iron features pushbutton operation, built-in work and pilot light and is rechargeable overnight. The kit includes case, battery charger and one regular tip. Price is \$19.95. ■



FREE ALARM CATALOG

Full line of professional burglar and fire alarm systems and supplies. 96 pages, 450 items. Off the shelf delivery, quantity prices.



mountain west alarm
4215 n. 16th st., phoenix, az. 85016

... for more details circle 118 on Reader Service Card

DISCOUNT TEST EQUIPMENT SPECIALISTS

B&K HICKOK
SENCORE RCA
TECO Leader

COMPLETE LINE OF ELECTRONIC SUPPLIES
ICC/Mullard & Raytheon Tubes
Telematic Test Rigs

FREE CATALOG

QUOTATIONS ON REQUEST

FORDHAM
Radio Supply Co., Inc.

558 Morris Ave., Bronx, N.Y. 10451
Tel: (212) 585-0330

IEC-MULLARD



88¢

MINIMUM 10
POPULAR 6GH8

ORDER No. X 114

SEND CHECK WITH
ORDER - WE PAY
SHIPPING CHARGE

"WE SELL TO THE DEALER ONLY"

FREE BIG WHOLESALE CATALOG

with thousands of money-saving audio,
electronic parts, test equipment and accessories.

FREE

QUALITONE INDUSTRIES, INC.
17 Columbus Avenue, Tuckahoe, N. Y. 10707
Please send FREE Catalog to:

Name

Address

City State/Zip

... for more details circle 124 on Reader Service Card

DEALER SHOWCASE

Descriptions and specifications of the products included in this department are provided by the manufacturers. For additional information, circle the corresponding numbers on the Reader Service Card in this issue.

4-CHANNEL TURNTABLE 706

Completely equipped
and priced at under \$100

BSR has introduced the Model 4310X 4-channel automatic turntable. The turntable comes completely equipped with a molded base with walnut trim, removable hinged tinted dust cover, and an Audio Technica AT-12S CD-4 magnetic Shibata diamond stylus cartridge and all necessary 4-channel



cables. The unit comes completely assembled, adjusted and packed in a single carton. It also features a shielded anti-magnetic steel platter, stylus force adjustment, anti-skate control, viscous-damped cue/pause control, jamproof tone arm with automatic arm lock.

COLOR TV 707

Features in-line picture tube
and all solid-state modular chassis

A new 19-inch color TV model that comes complete with super bright in-line picture tube, 100% solid-state modular chassis and matching swivel base has been added to the Magnavox line. The unit, Model 4352, comes



complete with matching swivel base. Other features include 185 square inch picture, automatic fine tuning, automatic color, 70 detent UHF tuning and 13 detent VHF tuning, sharpness control and lighted channel indicator. Price is \$449.95. ■

TROUBLED BY TRIGGERED SCOPES?



The Hickok Model 512 Dual Trace Oscilloscope eliminates the set-up and precision problems you've had to accept using other triggered scopes.

It's easy to set up

- Simplified color-coded front panel controls.
- Beam finder quickly locates off-scale traces.
- Foolproof triggering to 15 MHz.

It gives you superior performance

- 10 MHz response flat within 3dB. Excellent pulse response.
- Unique automatic VITS sync separator.

Hickok industrial lab quality and construction

Glass epoxy PC boards used throughout. Regulated power supply.

Plus, our exclusive two-year warranty.

Ask to see the Hickok Model 512 or single trace Model 511 at your Hickok distributor or contact us for more information.

\$675.00

complete with probes and accessories

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

... for more details circle 114 on Reader Service Card

CLASSIFIED

RATES: 35¢ per word; 45¢ per word Bold Face Type. Add \$3.00 if you wish Box Number. Minimum \$10.00 charge. Classified Display Rate billed \$40.00 per inch, 1 inch minimum.

For Sale

Television Service Business for Sale. In operation for nearly 25 years and we have more work than we can handle. We have several contract accounts which keep us very busy, plus a large following of regular customers. Call or write for particulars: Mr. Harry R. Johnson, VALLEY TV & APPLIANCE CENTER, 1252 North Main St., Salinas, CA 93901. (408) 449-7208.

ELECTRONIC ORGAN KITS, KEYBOARDS for organs and synthesizers. Independent and divider organ tone generators, diode keying. 35¢ for catalog. DEVTRONIX ORGAN PRODUCTS, Dept. A, 5872 Amapola Drive, San Jose, CA 95129.

LIQUID crystal. 3½ digit wristwatch display. New, with instructions for building wristwatch. Final close-out. Less than original, factory wholesale price. \$5.50 each. Two for \$10.00. TRICOUNTY WINSLOW, INC., Box 5885, Grand Central Station, New York, NY 10017.

For Sale: 72 sets of Sam's Photofact Schematics, 1218-1289. Make Offer. Contact: Mr. Wayne A. Frye, Route 2, Box 173, Edinburg, VA 22824.

LOW noise resistors—¼ W, 5%, carbon film from 10-3.3 Meg for 3½¢ each. Fifty of one value for \$1.25. 10% discount over \$50.00. 75¢ postage/handling. Free samples and specifications. COMPONENTS CENTER E, Box 134, New York, NY 10038.

EVERYTHING you always wanted to know about service contracts, but didn't know who to ask. "THE SERVICE CONTRACT COOKBOOK" only \$15.00 postpaid when you ask NATESA, Dept. SC, 5908 S. Troy, Chicago, IL 60629.

FLYBACK checker, scope adaptor. Easy to operate. Removal from circuit not necessary. \$10.95 postpaid. E. P. ELECTRONICS, 17 East El Vado, Tucson, AZ 85706.

LAKESIDE PICTURE TUBE REBUILDER—complete with many extras, e.g., neck glass, bases, pump oil, practice stems, spark coil, face plates. \$1500. FOB Oxon Hill, Md. (301) 292-2070.

FREE CATALOG

The 1974 Tucker Electronics Company General Catalog includes 180 pages of electronic test instruments, 16 lines of low cost distributor products and thousands of reconditioned instruments

TUCKER
ELECTRONICS • COMPANY
P.O. Box 1050 • Garland, Texas 75040

DYNACO-A-R, transistors, repairs—boards & units, speaker service. Send for prices and details: BEAR ELECTRONICS, 177-ET-Hillcrest Road, Mt. Vernon, NY 10552.

PRACTICAL applications of digital IC's. 100's of tips, circuits, projects on TTL. 443 pp. \$19.95, money-back guarantee. GEA, P.O. Box 285, Northfield, OH 44067.

For Sale

RCA—Solid-State Oscilloscope, type WO-505A	\$175.00
RCA—Master Chro-Bar Generator, type WR-515A	100.00
RCA—Solid-State Master Voltomist, type WV-510A	90.00
RCA—Bias supply, type WG-307B	10.00
RCA—Marker Signalyst, type WR-525A	20.00
RCA—25 inch. CTC-24 color television, with brand-new Matrix Picture Tube and flyback transformer, table model (no stand)	180.00
Jud Williams—Transistor Curve Tracer, Model A	90.00
Eico—Solid-State Signal Tracer, Model 150	35.00
Conar—Resistor-Capacitor Tester, Model 311	15.00
Conar—Communication Transmitter-Kit, assembled	15.00
Conar—Color Television Chassis, Model 600 with Cabinet, less Picture Tube	25.00
Sencore—Transistor FET Tester, Model TF17A	20.00
Electro—Transistor-Power Supply, Model-E3 0-24 @ 100 ma.	10.00
Kine—Color Circuit Analyzer, Model CA378	10.00

Contact: William D. Shevtchuk

1 Lois Avenue, Clifton, N.J. 07014. Phone: 201-471-3798

BUILD A "SPACE-AGE" TV CAMERA!

Only known solid-state camera available in kit form factory assembled. Ideal for experiments, industry, education, etc. Completely self-contained. Connects to any TV set without modification. High quality performance backed by years of lab and field testing. Fully Guaranteed. Easy-to-understand, step-by-step assembly manual. Model XT-1A, Series 0 complete with vidicon tube only \$165.00. Postpaid delivery anywhere in USA, Canada and Mexico. Optional audio subcarrier also available, \$28.95.

PHONE or WRITE for CATALOG, DIAL 402-987-3771

BOX 453-ET **ATV Research** DAKOTA CITY, NEBR. 68731

VISTA DIGITAL CROSSHATCH

For professional, accurate color T.V. convergence. Digital IC's coupled with a crystal timebase oscillator provide SYNC for precise horizontal and vertical lines.

Accurate 8 x 7 crosshatch or 56 dot pattern. A.C. power 2 x 3¼ x 6 in. Fits in tool kit completely assembled in U.S.A. \$41.95. Ready to use. Include \$2.00 for shipping and handling.

PHOTOLINE CORPORATION
118 EAST 28 STREET, NEW YORK, NY 10016

Antique radio tubes and Riders Manuals for sale. Less than dealers' prices. G. C. Goodwin, 126 W. First Ave., Rankin, IL 60960.

T.V. shop close-out sale: Common Tubes 70% off list price. 20% off list price of Heath Kit Vectorscope, Marker/sweep generator, B & K CRT Tester, Channel Master Field Strength Meter & other misc. items. Postage paid. For more information write: Ainsworth Communications, P. O. Box 23, Ainsworth, Nebr. 69210, or phone 1-402-387-1990.

Educational Courses

REPAIR TV TUNERS—High Earn-

**send a message...
...write here.**

1. Number of insertions: (circle) 1 2 3 6 12
2. Start with (month) _____ issue (Copy must be in by 1st of month preceding)
3. Amount enclosed: \$ _____

PAYMENT MUST ACCOMPANY ORDER WE'LL BILL RATED FIRMS NO AGENCY COMMISSION

NAME _____ COMPANY _____

STREET _____

CITY _____ STATE _____ ZIP _____

MAIL COPY FOR AD(S) TO: ROZ MARKHOUSE, Electronic Technician/Dealer, 757 Third Ave., New York, N.Y. 10017

RATES: 35¢ per word; 45¢ per word Bold Face Type. Add \$3.00 if you wish Box Number. Minimum \$10.00 charge. Classified Display Rate billed \$40.00 per inch, 1 inch minimum.

**ELECTRONIC
TECHNICIAN/DEALER CLASSIFIED**

ings; Complete Course Details, 12 Repair Tricks, Many Plans, Two Lessons, all for \$2. Refundable. Frank Bocek, Box 3236, Ent., Redding, CA 96001.

Wanted

WANTED—ELECTRONIC TECHNICIAN, UNUSUAL OPPORTUNITY FOR ONE WELL QUALIFIED IN COLOR TV. TOP SALES AND SERVICE SHOP HAS 40 YEAR REPUTATION. WE MUST REPLACE RETIRING PARTNERS. MUST BE HONEST, EAGER TO LEARN, AND ENJOY SERVING PEOPLE. CONTACT: WELLS & LaHATTE, VICKSBURG, MS. 39180.

COLLECTOR WANTS: Collections or dealer's stock of 78 rpm records—jazz, blues, country; 1925 to 1940. Also old comic books. Will travel. Dunner, 11 Golden Hills, Saugus, Mass. 01906.

Wanted: An extra instruction manual for Winston Electronics Corporation DYNAMIC SWEEP CIRCUIT ANALYZER Model 820, or the present address of the Winston Electronics Corporation of Philadelphia. Philip Butler, Box 581, West Brookfield, MA 01585.

Wanted: Picture tube rebuilding equipment and supplies. Call or write: George Antimisariis, 20 Coleville Road, Wayne, NJ 07470. (201) 839-4925.


BRAND NEW FROM ENDECO
the soldering iron with a light



Exclusive new safety light shows when power is on
 MODEL 540S \$10.95 NET

Two heats—20w and 40w—to handle any job
 • On-off switch • Cool, unbreakable polycarbonate handle • Ironclad tips for longer life
 • Burn-resistant neoprene cord • 8½" long, 2 oz • Converts to a desoldering iron with low cost attachment • Also desoldering irons and soldering/desoldering kits.

See your distributor or write . . .

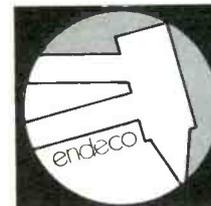

5127 EAST 65TH ST.
 INDIANAPOLIS,
 INDIANA 46220
 PHONE 317/251-1231

enterprise
 development
 corporation

. . . for more details circle 109 on Reader Service Card

**T & T
 VALUE SALE**

RAY., I.C.C., RCA, SYL.
 FAMOUS MAKE, NEW JOBBER-BOXED TUBES

- 80% Off LIST**
- | | |
|--|--|
| <input type="checkbox"/> 1B3 5 for \$5.00 | <input type="checkbox"/> 6HA5 5 for \$4.80 |
| <input type="checkbox"/> 1V2 5 for \$3.00 | <input type="checkbox"/> 6HB7 5 for \$4.85 |
| <input type="checkbox"/> 2AV2 5 for \$3.95 | <input type="checkbox"/> 6HQ5 5 for \$6.35 |
| <input type="checkbox"/> 3A3 5 for \$5.05 | <input type="checkbox"/> 6HV5 5 for \$11.80 |
| <input type="checkbox"/> 3AT2 5 for \$4.90 | <input type="checkbox"/> 6JC6 5 for \$5.65 |
| <input type="checkbox"/> 3GK5 5 for \$4.85 | <input type="checkbox"/> 6JE6 5 for \$11.15 |
| <input type="checkbox"/> 3HA5 5 for \$4.80 | <input type="checkbox"/> 6JS6 5 for \$9.30 |
| <input type="checkbox"/> 3HM5 5 for \$4.80 | <input type="checkbox"/> 6JU8 5 for \$5.55 |
| <input type="checkbox"/> 4BZ6 5 for \$4.70 | <input type="checkbox"/> 6KA8 5 for \$6.15 |
| <input type="checkbox"/> 5GH8 5 for \$5.90 | <input type="checkbox"/> 6KE8 5 for \$7.65 |
| <input type="checkbox"/> 6AX4 5 for \$5.05 | <input type="checkbox"/> 6KMG 5 for \$11.25 |
| <input type="checkbox"/> 6AY3 5 for \$5.05 | <input type="checkbox"/> 6KN6 5 for \$9.85 |
| <input type="checkbox"/> 6BK4 5 for \$9.35 | <input type="checkbox"/> 6KT8 5 for \$6.85 |
| <input type="checkbox"/> 6CG3 5 for \$4.95 | <input type="checkbox"/> 6KZ6 5 for \$5.15 |
| <input type="checkbox"/> 6CG8 5 for \$5.40 | <input type="checkbox"/> 6LB6 5 for \$10.75 |
| <input type="checkbox"/> 6CJ3 5 for \$4.70 | <input type="checkbox"/> 6LQ6 5 for \$11.15 |
| <input type="checkbox"/> 6DQ6 5 for \$6.75 | <input type="checkbox"/> 8F07 5 for \$3.75 |
| <input type="checkbox"/> 6DW4 5 for \$4.70 | <input type="checkbox"/> 12BY7 5 for \$4.50 |
| <input type="checkbox"/> 6EA8 5 for \$4.95 | <input type="checkbox"/> 12GN7 5 for \$7.00 |
| <input type="checkbox"/> 6EH7 5 for \$4.80 | <input type="checkbox"/> 17JZ8 5 for \$4.50 |
| <input type="checkbox"/> 6EJ7 5 for \$4.50 | <input type="checkbox"/> 21GY5 5 for \$6.30 |
| <input type="checkbox"/> 6FQ7 5 for \$3.75 | <input type="checkbox"/> 23Z9 5 for \$6.00 |
| <input type="checkbox"/> 6GF7 5 for \$6.65 | <input type="checkbox"/> 31LQ6 5 for \$10.15 |
| <input type="checkbox"/> 6GH8 5 for \$3.95 | <input type="checkbox"/> 33GY7 5 for \$8.05 |
| <input type="checkbox"/> 6GJ7 5 for \$3.40 | <input type="checkbox"/> 36MC6 5 for \$11.40 |
| <input type="checkbox"/> 6GM6 5 for \$5.25 | <input type="checkbox"/> 38HE7 5 for \$9.20 |
| <input type="checkbox"/> 6GU7 5 for \$5.25 | <input type="checkbox"/> 38HK7 5 for \$9.00 |
| <input type="checkbox"/> 6GY6 5 for \$4.35 | <input type="checkbox"/> 42KN6 5 for \$9.15 |
- *FREE—\$100.00 LIST OF CONTROLS WITH ANY PURCHASE OF 100 TUBES LISTED ABOVE**
 *A 6GH8 SPECIAL 100 for \$59.00
- TRANSISTORS XACT. REPLACEMENT (BOXED)**
 Up To 90% off LIST
- | | |
|--|--|
| <input type="checkbox"/> SK3004 5 for \$1.90 | <input type="checkbox"/> SK3052 5 for \$3.90 |
| <input type="checkbox"/> SK3009 5 for \$3.90 | <input type="checkbox"/> SK3054 5 for \$4.50 |
| <input type="checkbox"/> SK3010 5 for \$2.10 | <input type="checkbox"/> SK3082 5 for \$3.90 |
| <input type="checkbox"/> SK3018 5 for \$2.25 | <input type="checkbox"/> SK3103 5 for \$3.00 |
| <input type="checkbox"/> SK3021 5 for \$3.15 | <input type="checkbox"/> SK3114 5 for \$2.40 |
| <input type="checkbox"/> SK3024 5 for \$3.30 | <input type="checkbox"/> SK3124 5 for \$2.10 |
| <input type="checkbox"/> SK3025 5 for \$4.50 | <input type="checkbox"/> SK3132 5 for \$2.60 |
| <input type="checkbox"/> SK3040 5 for \$3.75 | <input type="checkbox"/> ECG155 5 for \$4.90 |
| <input type="checkbox"/> SK3041 5 for \$4.20 | <input type="checkbox"/> ECG131 5 for \$3.90 |
| <input type="checkbox"/> SK3042 5 for \$6.60 | <input type="checkbox"/> HEP707 5 for 15.00 |

- DIODES & RECTIFIERS**
- | | |
|--|--|
| <input type="checkbox"/> RCA Damper Diode Equip. To: | |
| <input type="checkbox"/> RCA 120818 \$1.95 | <input type="checkbox"/> RCA 135932 \$2.95 |
| <input type="checkbox"/> ITT 6500 PIV Color Focus Rect 10 for \$5.00 | |
| <input type="checkbox"/> 2.5 amp 1000 PIV IR170 20 for \$3.00 | |
| | 100 for \$11.00 |

- YOKES & TUNERS**
- | | |
|---|---------------|
| <input type="checkbox"/> Tuner inc. 6GS7, 6HA5 | \$1.95 |
| <input type="checkbox"/> Combo Tuners inc. tubes | \$4.95 |
| <input type="checkbox"/> Syl. Tuner 54-35055-4 inc. 3 transistors | 2 for \$15.00 |
| <input type="checkbox"/> Y105, Y94, Y130, 95-2874 | ea. \$6.95 |
| <input type="checkbox"/> Zen. Color Yoke 95-2532 repl | \$11.95 |
| <input type="checkbox"/> RCA Color Yoke 906214-501 | \$8.95 |
| <input type="checkbox"/> Syl. E01 51-29978-1 Color Yoke 2 for \$15.00 | |

- RCA - ZENITH MODULES**
- | | |
|---|------------|
| <input type="checkbox"/> 132581 | \$3.00 |
| <input type="checkbox"/> 132579, 133455 | ea. \$3.49 |
| <input type="checkbox"/> 9-50, 9-59, 9-79 | ea. \$3.95 |

- AUDIO**
- | | |
|---|-------------------------|
| <input type="checkbox"/> 60 Min. Cassette Irish | 6 for \$2.50 |
| <input type="checkbox"/> 84 Min. 8-track Irish Tape | 3 for \$3.00 |
| <input type="checkbox"/> Equip. Shure—N44, N75, N77, N91 | ea. \$2.95 |
| <input type="checkbox"/> Equip. Pickering V15 | ea. \$2.95 |
| <input type="checkbox"/> BSR Cartridges—SX5M, SX1H, SC5M | 4 for \$5.00 |
| <input type="checkbox"/> Remote Mikes Min. Plug | 4 for \$6.00 |
| <input type="checkbox"/> Stereo Head Set Min. Plug | 2 for \$5.00 |
| <input type="checkbox"/> Stereo Head Sets | ea. \$3.95 2 for \$7.50 |
| <input type="checkbox"/> Stereo Dual Mikes Ampex | \$5.95 |
| <input type="checkbox"/> Speaker Kit—incl. 2-4", 2-5" 2-4 x 6, 4-6" | All 10 for \$12.00 |

- ANTENNA SUPPLIES**
- | | |
|---|-----------------|
| <input type="checkbox"/> J.F.D. CO-14 4 Set Coupler | 10 for \$10.00 |
| <input type="checkbox"/> 72 ohm-300 ohm matching transformer | 5 for \$5.00 |
| <input type="checkbox"/> 2 Set 72 ohm Coupler | \$2.00 |
| <input type="checkbox"/> 4 Set 72 ohm Coupler | \$2.95 |
| <input type="checkbox"/> 72 ohm UHF VHF Signal Splitter | 10 for \$7.50 |
| <input type="checkbox"/> 59U F Connectors | 100 for \$10.00 |
| <input type="checkbox"/> JFD DCM101 All Channel Color Antenna | ea. \$9.95 |

- GENERAL**
- | | |
|---|----------------|
| <input type="checkbox"/> 19 & 25" 21" Color Boosters | 3 for \$11.95 |
| <input type="checkbox"/> Zen. VOLTAGE TRIPLER, 212-136 | 3 for \$12.00 |
| <input type="checkbox"/> 117V-12V DC H.D. Transformer | ea. \$1.50 |
| <input type="checkbox"/> Blue Lateral Magnets with P.R. | 10 for \$10.00 |
| <input type="checkbox"/> Jap. Phono arm incl. cartridge | 10 for \$5.00 |
- Minimum Orders \$50—F.O.B. Brooklyn, N.Y.
 Catalogs \$1—Refundable upon your order
 C.O.D.—CASH ONLY


T. & T SALES CO.

**4802 AVENUE K
 BROOKLYN, N. Y. 11234
 Phone: (212) 241-5940**

TeleMatic MJ-195

MASTER TEST RIG

FOR TUBE AND SOLID STATE SERVICING

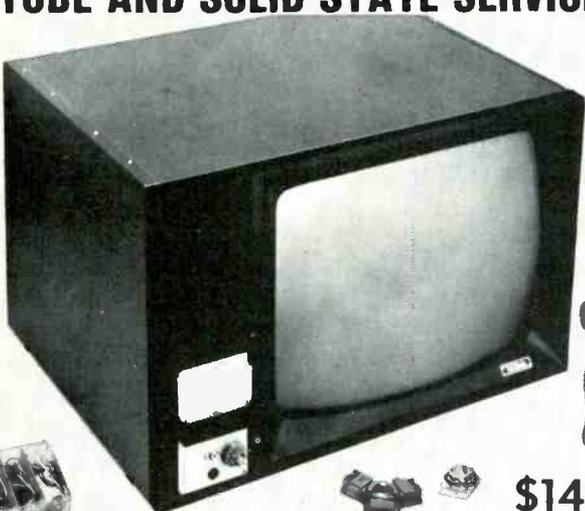

\$149.95
 less 19" picture tube

- 30 KV CAPACITY
- METAL CABINET
- SPEAKER BUILT IN
- HIGH VOLTAGE METER
- STATIC CONVERGENCE
- FRONT PANEL CONNECTIONS


TeleMatic 2245 Pitkin Ave., Brooklyn, N.Y. 11207

FREE! Adaptor Quick Reference Chart

. . . for more details circle 127 on Reader Service Card

. . . for more details circle 131 on Reader Service Card

TOUGH!

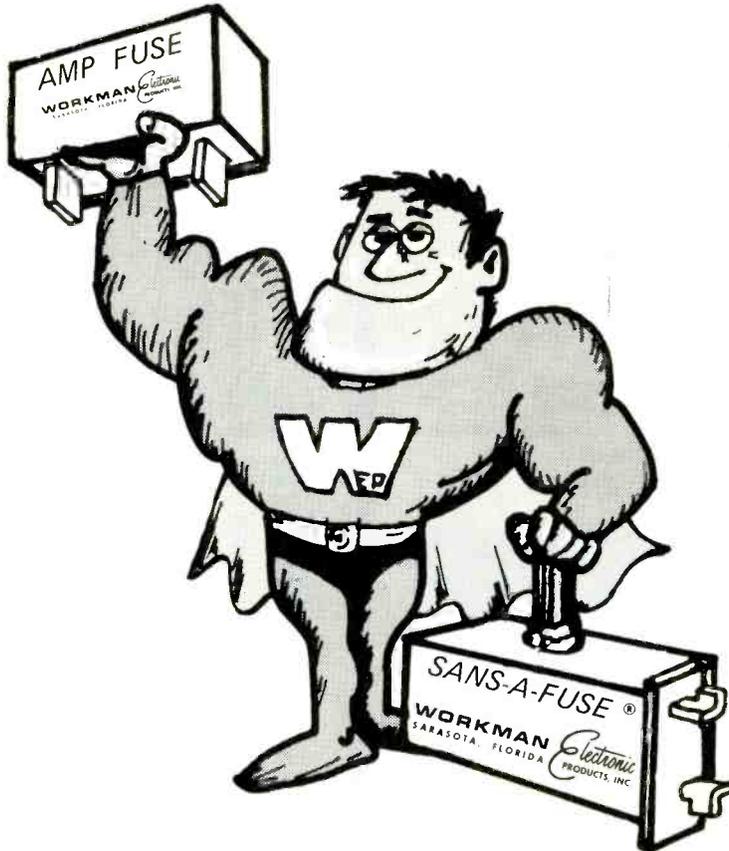

THEY HAVE TO BE. THEY'RE ENGINEERED TO PROTECT YOUR COSTLY COMPONENTS FROM A CIRCUIT OVERLOAD.

ALL our fuses are subjected to the most rigid tests before they become a *WORKMAN* Amp Fuse or Sans-A-Fuse®.

The *WORKMAN* Sans-A-Fuse® (circuit breaker with amp fuse pins) is so tough it may be reset time and time again and still maintain it's original reliability.

This is only possible because *WORKMAN* puts quality, reliability and performance into each of it's color coded Amp Fuses and Sans-A-Fuses® and both are tough as (expletive deleted)!

Workman

ELECTRONIC PRODUCTS, INC.
Subsidiary of IPM TECHNOLOGY INC.
BOX 3828 • SARASOTA, FLA. 33578

NOW, with a WEST COAST WAREHOUSE located at:
P.O. Box 5218, 817 Douglas Avenue
Redwood City, California 94063
To better serve you.

... for more details circle 135 on Reader Service Card

READERS SERVICE INDEX

ADVERTISER'S INDEX

101	Antenna Corp of America	46
102	B & K Division Dynascan Corp.	2
103	Bell Industries/J. W. Miller Division	46
104	Blonder-Tongue Laboratories, Inc.	11
105	Book Club Tab Books	16-19
106	Eico Electronic Instruments Co.	44
108	Elenco Electronics, Inc.	44
107	Elin Mfg. Co.	45
109	Enterprise Development Corp.	49
110	Fluke Mfg., John Fordham Radio Supply Co., Inc.	21 47
111	GC Electronics Co. General Electric Co. GTE Sylvania, Electronic Components	9 4 1
113	Heath, Co., The	41
114	Hickok Electrical Instrument Co.	47
115	International Rectifier Corp.	7
116	Jerrold Electronics Corp.	Cover 3
117	Leader Instruments Corp.	10
118	Mountain West Alarm Supply Co.	47
122	P. K. Neuses	43
120	Oelrich Publications	50
121	Oneida Electronic Mfg., Inc.	43
123	PTS Electronics, Inc.	Cover 2
124	Qualitone Industries, Inc.	47
125	RCA Electronic Instruments RCA Electronic Components	24 8
128	Sprague Products Co.	5
131	T & T Sales Co.	49
127	Telematic Div., UXL Corp.	49
129	Triplett Corp.	Cover 4
130	Tuner Service Corp.	13
132	Wayne Electronics	29
134	Weller-Xcelite Electronics Div. Winegard Company	42 25
135	Workman Electronic Products, Inc.	50

IT'S NO PUZZLE
TO ORDER



OELRICH SERVICE FORMS

FOR TV-RADIO & 2 WAY RADIO SERVICE LEGAL FORMS FOR CALIF. FLA.
UTAH NOW AT YOUR PARTS JOBBER OR WRITE FOR CATALOG A64

OELRICH PUBLICATIONS
4040 N. NASHVILLE AVE. CHICAGO, ILLINOIS 60634

... for more details circle 120 on Reader Service Card

COMPLETE MANUFACTURER'S CIRCUIT DIAGRAMS
AND TECHNICAL INFORMATION FOR 5 NEW SETS

GROUP
269

SCHEMATIC NO.

SCHEMATIC NO.


AIRLINE 1564
Color TV Model GAI-12925A

QUASAR ELECTRONICS CORP. 1565
Color TV Chassis ATS, CTS, TS-942

AIRLINE 1567
TV Models GAI-11245A,B/GAI-11265A,B


SYLVANIA 1566
Color TV Chassis E11-1

GENERAL ELECTRIC 1563
TV Chassis XA

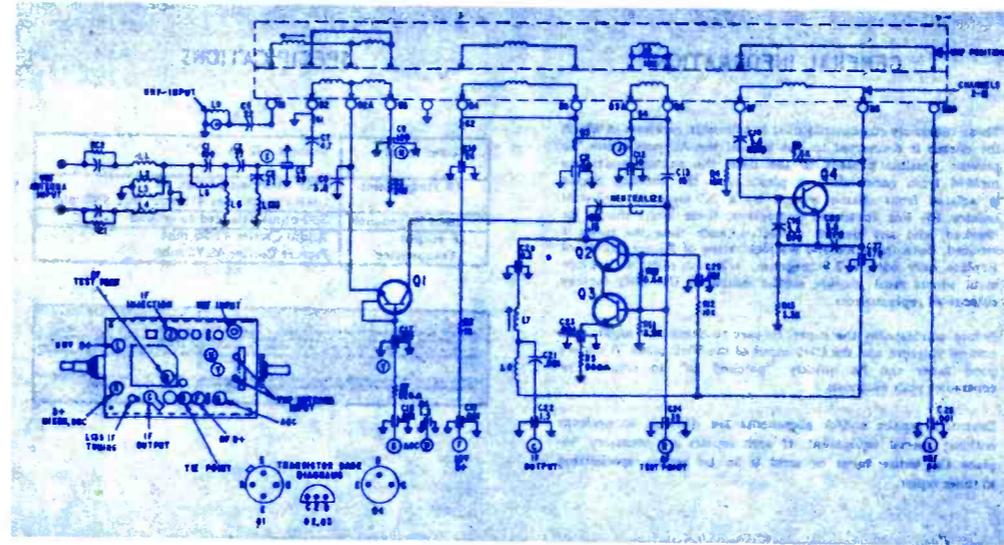







SCHEMATIC DIAGRAM


PRODUCT SAFETY SHOULD BE CONSIDERED WHEN A COMPONENT REPLACEMENT IS MADE IN ANY AREA OF A RECEIVER. THE SHADED AREA OF THIS SCHEMATIC DIAGRAM AND THE PARTS LIST INDICATE COMPONENTS IN WHICH SAFETY CAN BE OF SPECIAL IMPORTANCE. IT IS PARTICULARLY RECOMMENDED THAT GENERAL ELECTRIC CATALOGED PARTS BE USED FOR COMPONENT REPLACEMENT IN THE SHADED AREAS OF THIS SCHEMATIC. USE OF SUBSTITUTE REPLACEMENT PARTS WHICH DO NOT HAVE THE SAME SAFETY CHARACTERISTICS AS RECOMMENDED IN FACTORY SERVICE INFORMATION MAY CREATE CHOCK, FIRE OR OTHER HAZARDS.

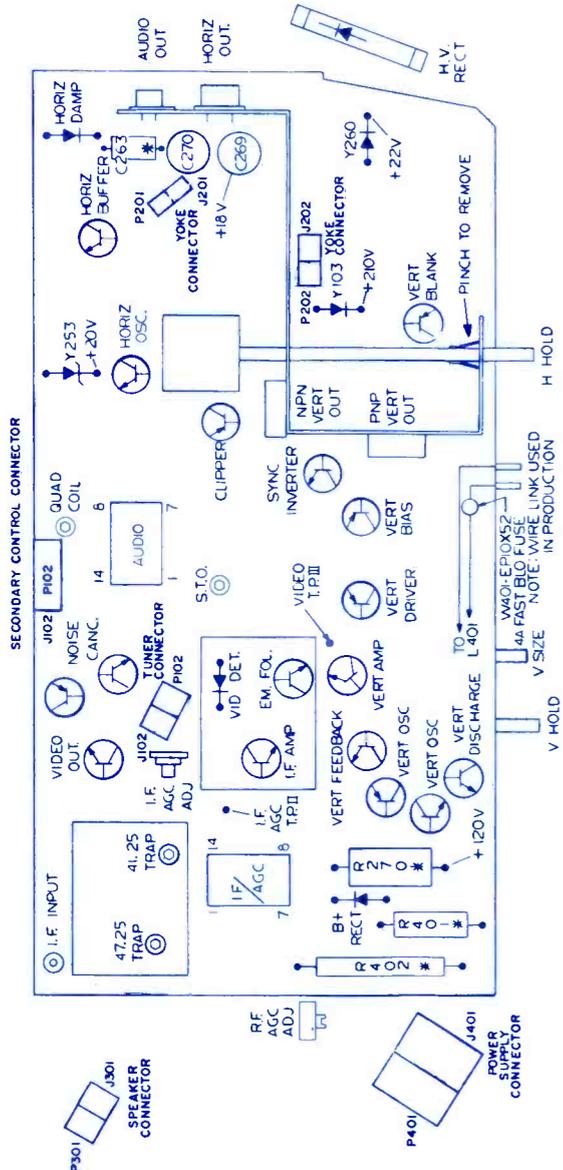

CHASSIS LAYOUT

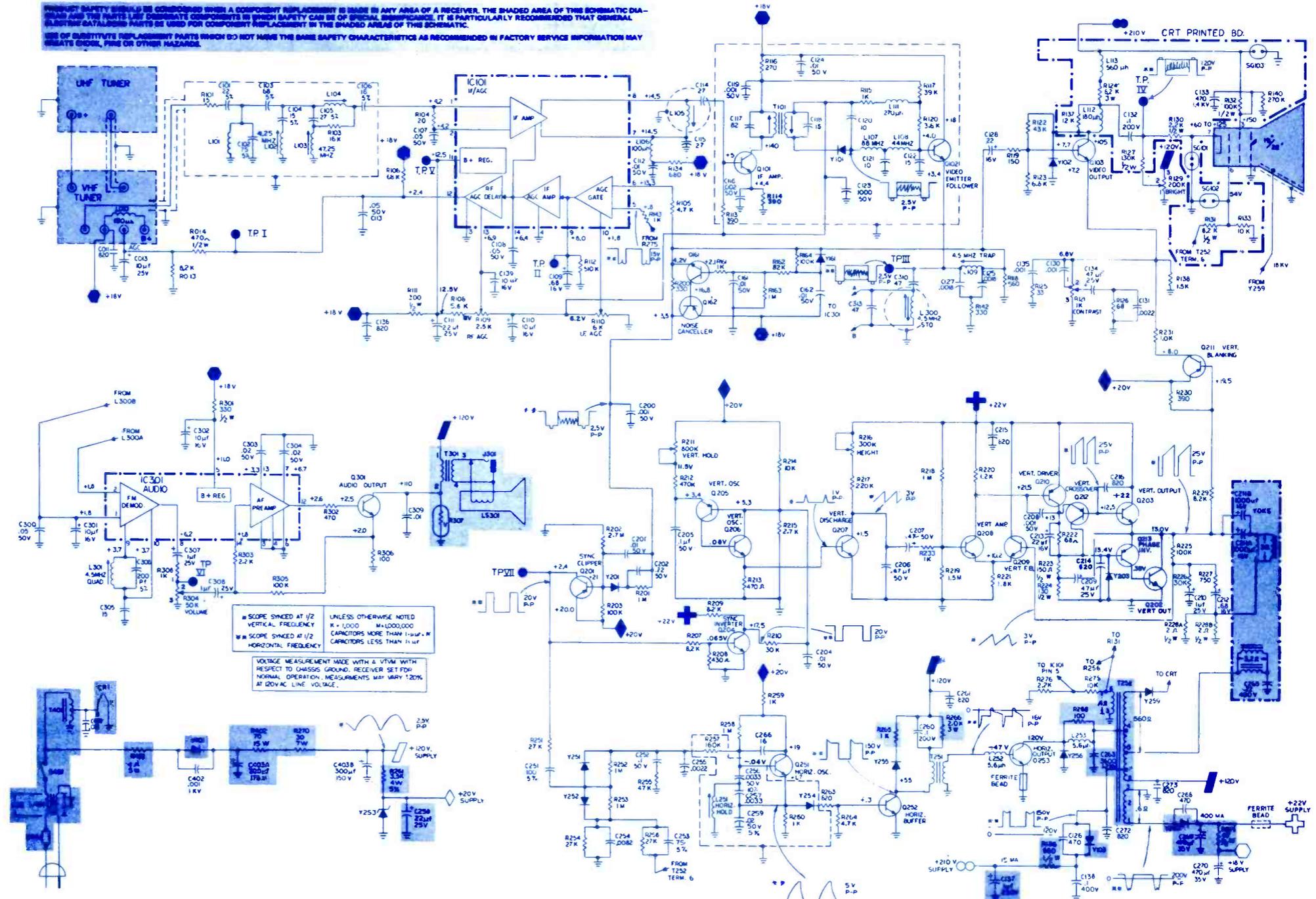

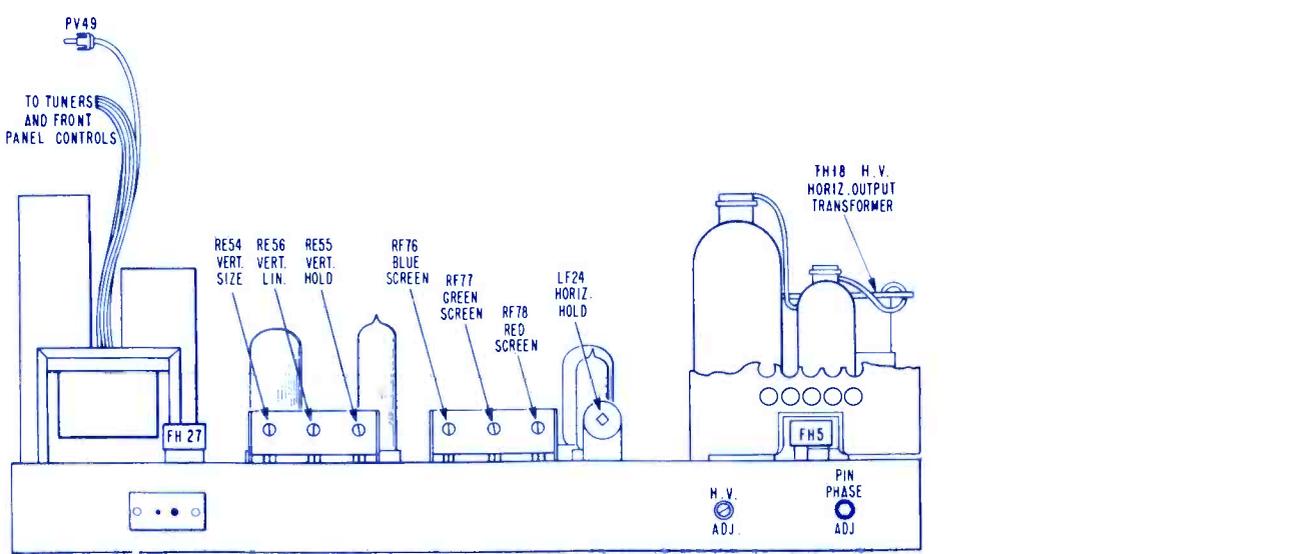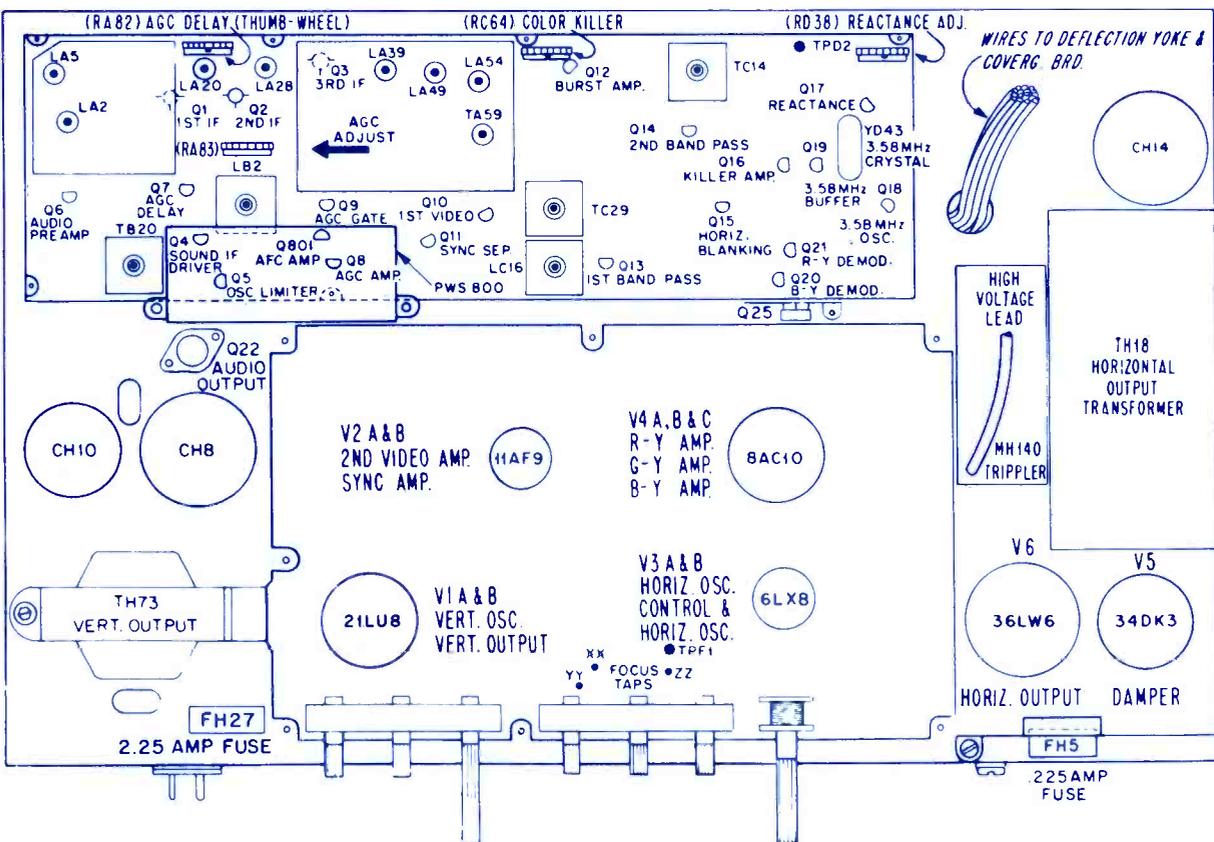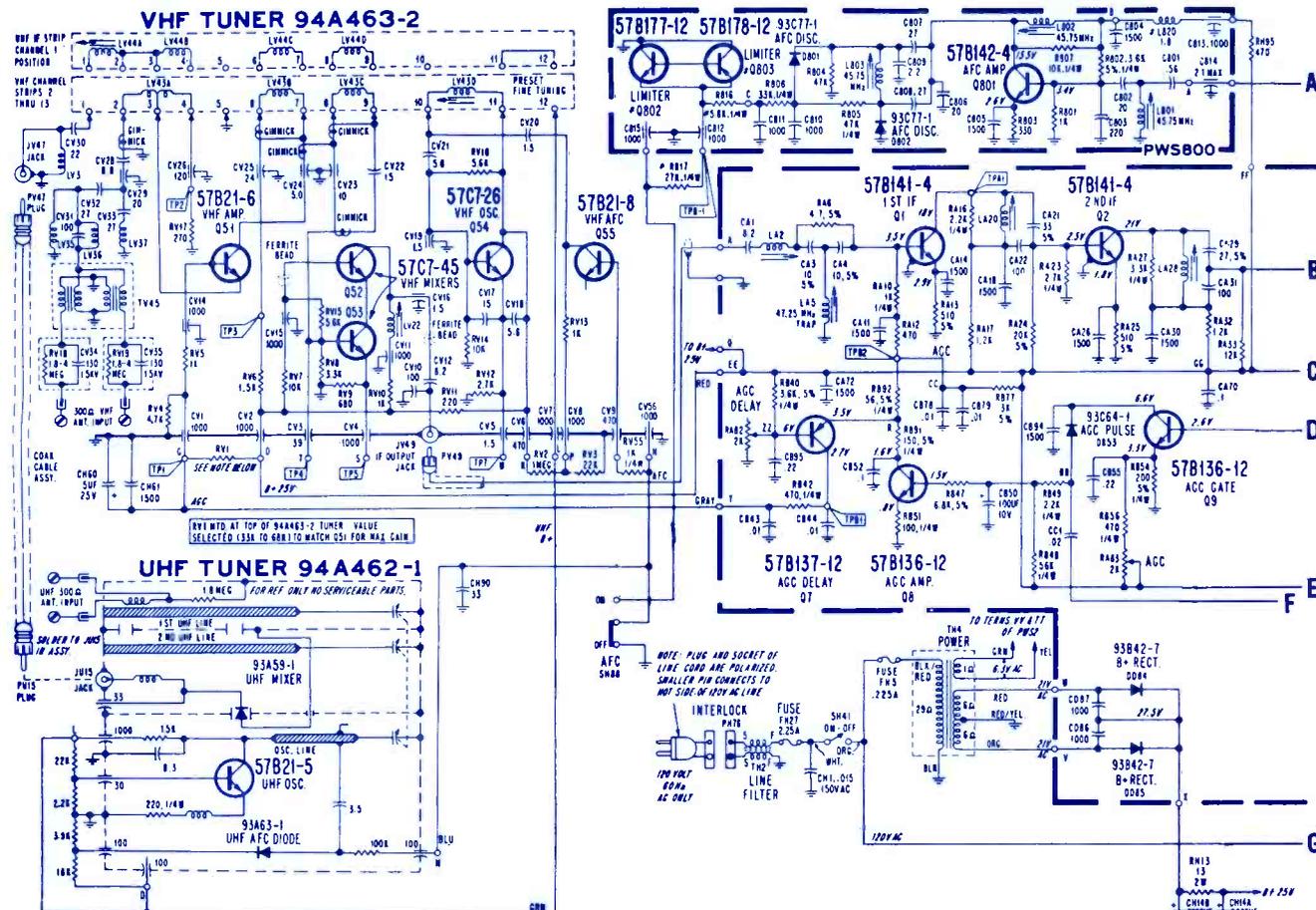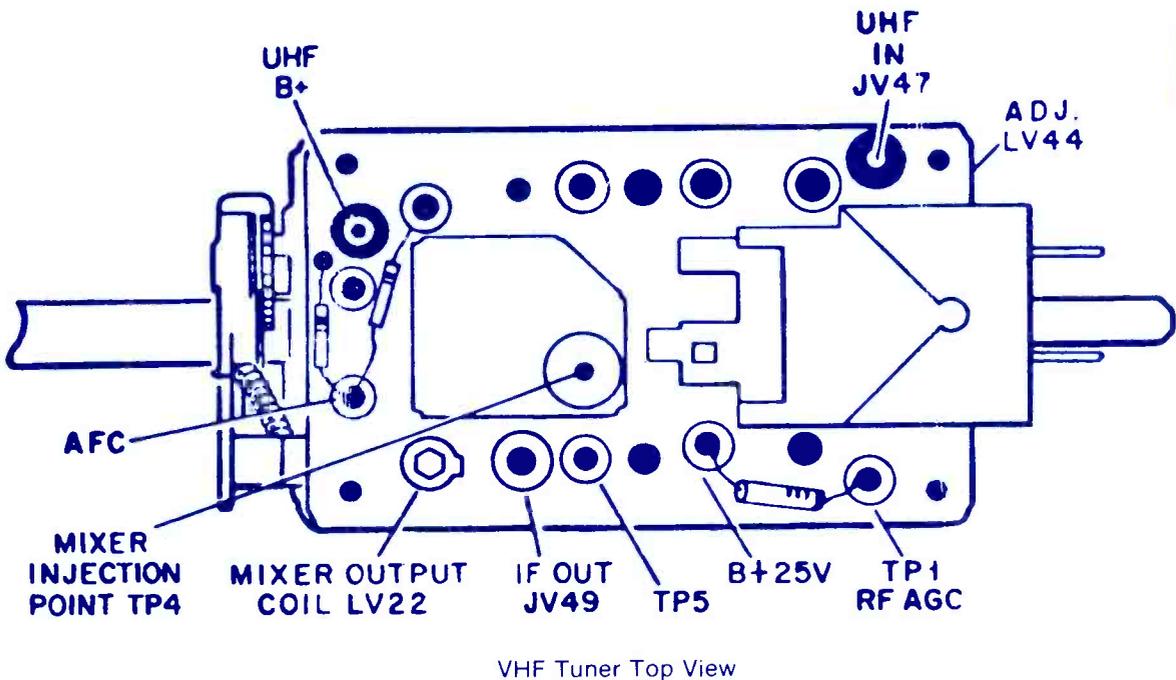
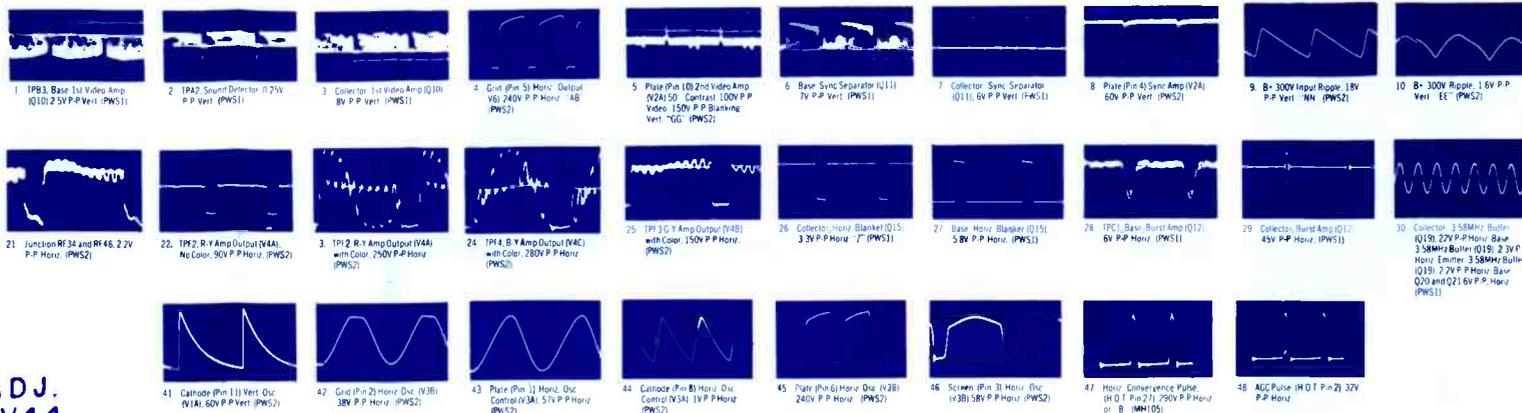


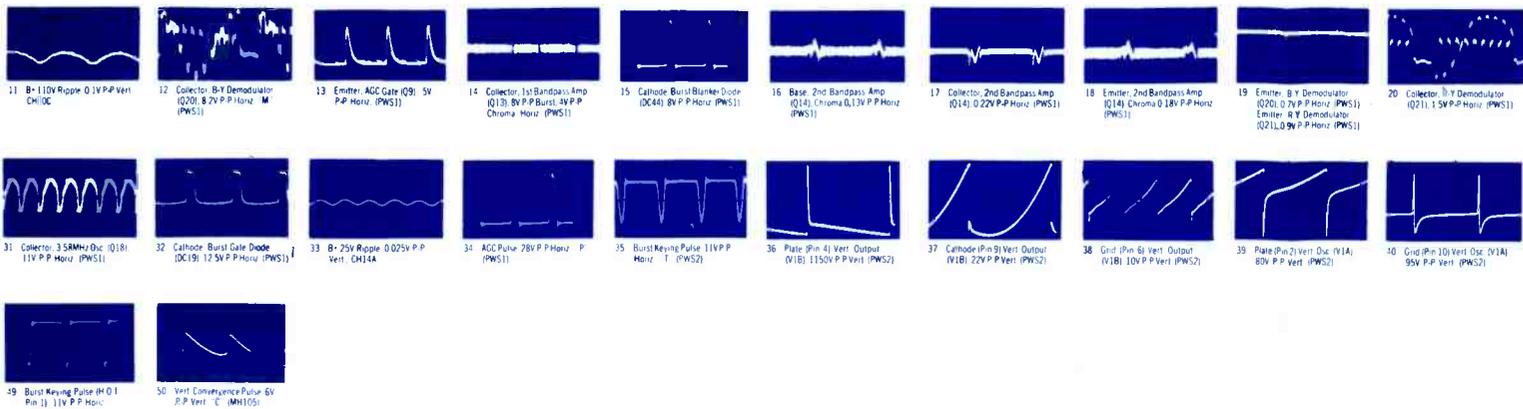

SYMBOL	DESCRIPTION	AIRLINE PART NO.
CH10A, B,	C, D—300µf/350v, 300µf/350v, 80µf/200v, 10µf/350v elect	67A15-415
CH14A, B—	2000µf/40v, 2000µf/40v elect	67A15-413
RH150A,	B—bleeder focus module	61A71-1
RA82—	2K AGC delay	75A101-31
RA83—	2K AGC	75A101-31
RC64—	10K color kill	75A101-18
RE54—	3.4M vert size	
RE55—	100K vert hold	75A95-18
RE56—	300K vert lin	
RH28—	2K brite	75A140-25
RH29—	350n contrast	75A140-26
RH39—	1K color	75A175-12
RH42—	50K vol W/SH41	75A140-31
RH125—	5M high volt adj	75A135-57
RH149—	30M chroma adj	75A108-8
LC16—	coil focus take-off	72A329-1
LD52—	coil 1µh, 3.58MHz output	73A55-37
LF24—	coil horiz adj	94A351-1

AIRLINE Color TV Model GAI-12925A

MH57—	deflect yoke	94A571-2
TA59—	x-former, 4.5MHz trap	72A216-7
TB20—	x-former ratio detect	72A318-1
TC14—	x-former burst	72A325-3
TH2—	x-former line choke	73A31-16
TH4—	x-former power	80A108-14
TH18—	x-former horiz output	79A169-3
TH44—	x-former audio output	79A141-4
TH73—	x-former vert output	79A165-1
FH5—	fuse .225a chemical	84A28-12
FH27—	fuse 2.25a chemical tuner VHF	84A28-16
		94A463-2

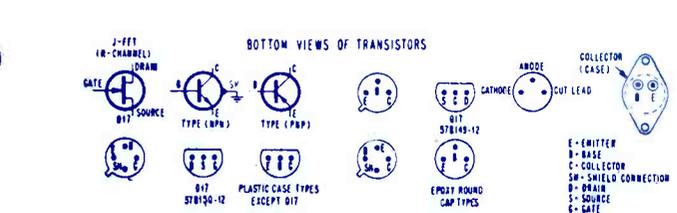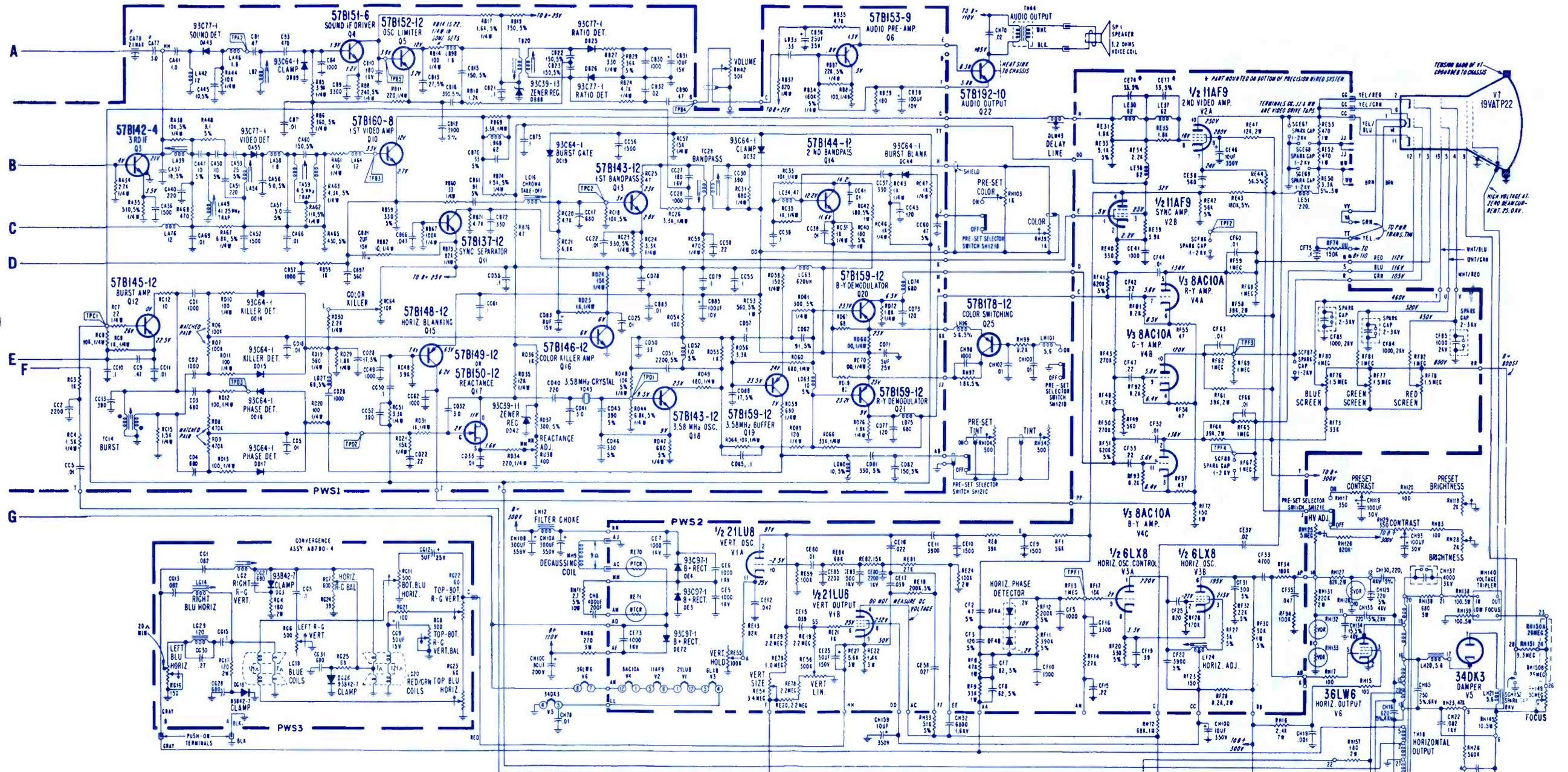

NOTES: UNLESS OTHERWISE SPECIFIED, RESISTANCE VALUES ARE IN OHMS, 10% TOLERANCE. CAPACITANCE VALUES 1 µF OR HIGHER ARE IN µF; CAPACITANCE VALUES LESS THAN 1 µF ARE IN P.F. INDICATES CYCLES PER SECOND. IN VOLTAGES ARE MEASURED WITH VTVM PLACED BETWEEN POINTS INDICATED. CHASSIS GROUND, LINE VOLTAGE SET AT 120V AC AT ALL CONTROLS SET FOR NORMAL PICTURE UNLESS OTHERWISE INDICATED. VOLTAGE READINGS ARE TAKEN WITHOUT SIGNAL, WITH VHF TUNER SET AT UNDESIRABLE CHANNEL. VOLTAGES SHOWN IN BRACKETS () ARE MEASURED WITH RECEIVER TUNED TO A COLOR SIGNAL.


WARNING: CHASSIS IS CONNECTED DIRECTLY TO ONE SIDE OF AC POWER LINE. USE AN ISOLATION TRANSFORMER WHEN SERVICING TO AVOID THE POSSIBILITY OF ACCIDENTAL ELECTRICAL SHOCK & DAMAGE TO TEST EQUIPMENT.

TRANSISTOR CAUTION: TO AVOID DAMAGE TO TRANSISTORS, DO NOT OPERATE CHASSIS WITH PICTURE TUBE DANGEROUSLY DISCONNECTED FROM CHASSIS GROUND. DO NOT TURN SET ON WITH TRANSISTOR IS. TUBE IS OFF. ALWAYS REMOVED OR UNSOLDERED. DO NOT ARC WELD TO CHASSIS GROUND. RESISTANCE AND VOLTAGE ONLY TO PICTURE TUBE AND ONE GND. USE CAUTION TO PREVENT ACCIDENTAL SHORT BY BENCH COMPONENTS OR TO CHASSIS GROUND. DO NOT APPLY EXCESSIVE HEAT TO TRANSISTOR LEADS. DO NOT USE AN ORDINARY OHMMETER FOR RESISTANCE MEASUREMENT. 1/2 VTM OR 8100 RANGE OR HIGHER.


RUN CHANGES: 10 START OF PRODUCTION

TRANSISTOR CAUTION: TO AVOID DAMAGE TO TRANSISTORS, DO NOT OPERATE CHASSIS WITH PICTURE TUBE DANGEROUSLY DISCONNECTED FROM CHASSIS GROUND. DO NOT TURN SET ON WITH TRANSISTOR IS. TUBE IS OFF. ALWAYS REMOVED OR UNSOLDERED. DO NOT ARC WELD TO CHASSIS GROUND. RESISTANCE AND VOLTAGE ONLY TO PICTURE TUBE AND ONE GND. USE CAUTION TO PREVENT ACCIDENTAL SHORT BY BENCH COMPONENTS OR TO CHASSIS GROUND. DO NOT APPLY EXCESSIVE HEAT TO TRANSISTOR LEADS. DO NOT USE AN ORDINARY OHMMETER FOR RESISTANCE MEASUREMENT. 1/2 VTM OR 8100 RANGE OR HIGHER.

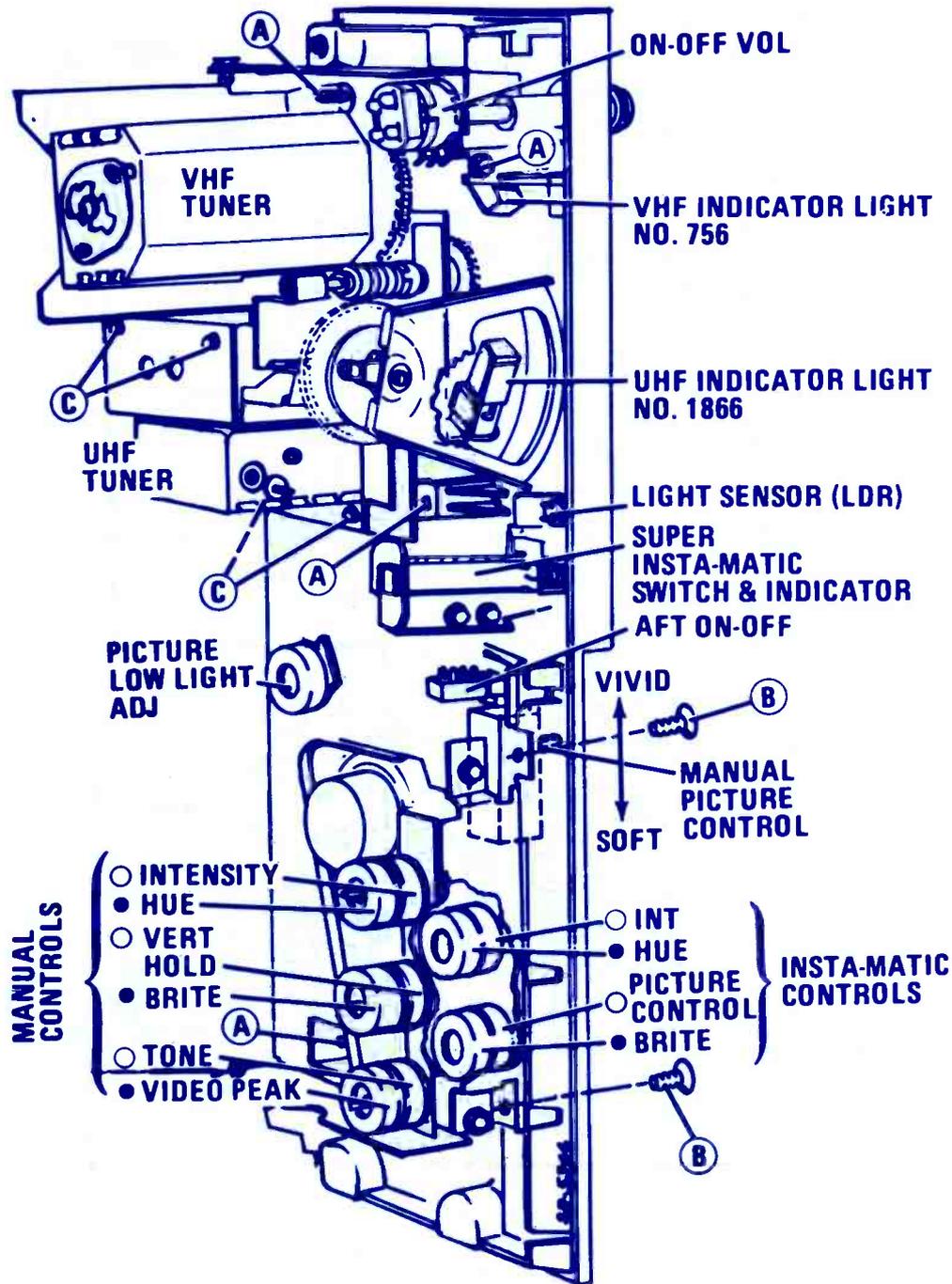
REMARKS: IDENTIFY WAVEFORM OBSERVATION LOCATIONS. CONDITIONS FOR TAKING WAVEFORM MEASUREMENTS ARE GIVEN WITH WAVEFORM PHOTOGRAPHS.



TS-942 Front Panel

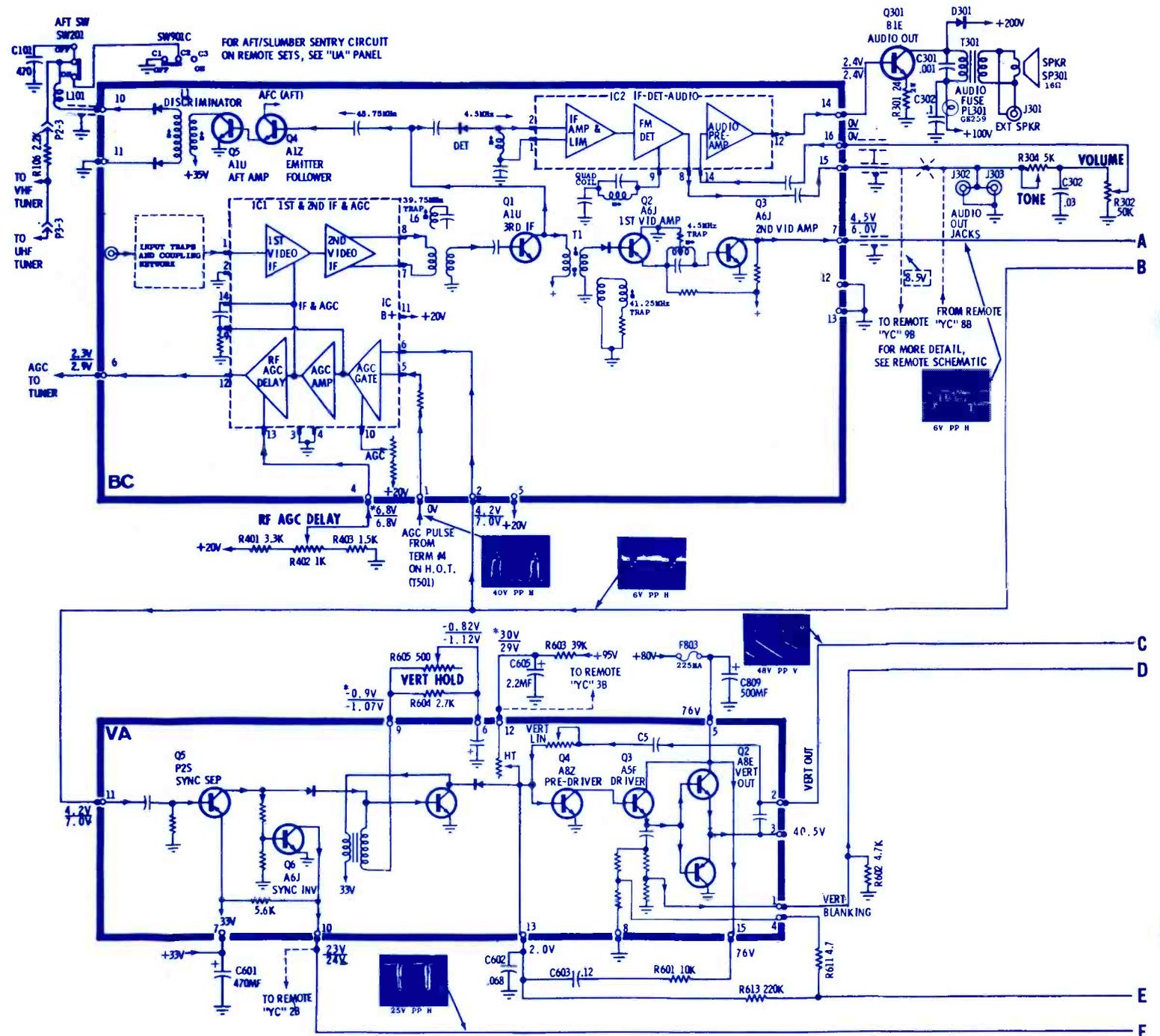

QUASAR
Color TV Chassis
ATS, CTS, TS-942

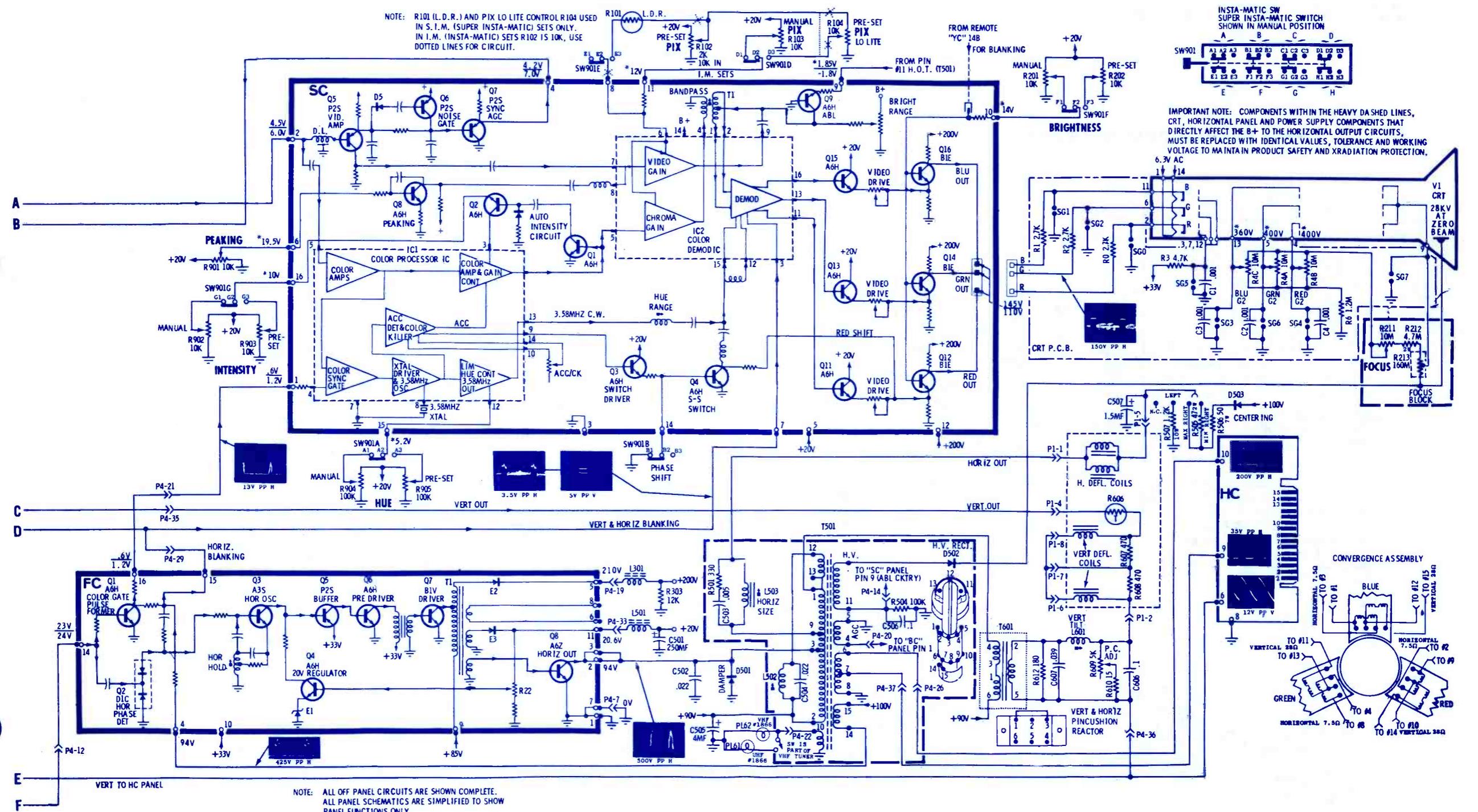



NOTE: R101 (L.D.R.) AND PIX LO LITE CONTROL R104 USED IN S.I.M. (SUPER INSTA-MATIC) SETS ONLY. IN I.M. (INSTA-MATIC) SETS R102 IS 10K, USE DOTTED LINES FOR CIRCUIT.




IMPORTANT NOTE: COMPONENTS WITHIN THE HEAVY DASHED LINES, CRT, HORIZONTAL PANEL AND POWER SUPPLY COMPONENTS THAT DIRECTLY AFFECT THE B+ TO THE HORIZONTAL OUTPUT CIRCUITS, MUST BE REPLACED WITH IDENTICAL VALUES, TOLERANCE AND WORKING VOLTAGE TO MAINTAIN PRODUCT SAFETY AND XRADIATION PROTECTION.


NOTE: ALL OFF PANEL CIRCUITS ARE SHOWN COMPLETE. ALL PANEL SCHEMATICS ARE SIMPLIFIED TO SHOW PANEL FUNCTIONS ONLY.

SYLVANIA
Color TV Chassis E11-1

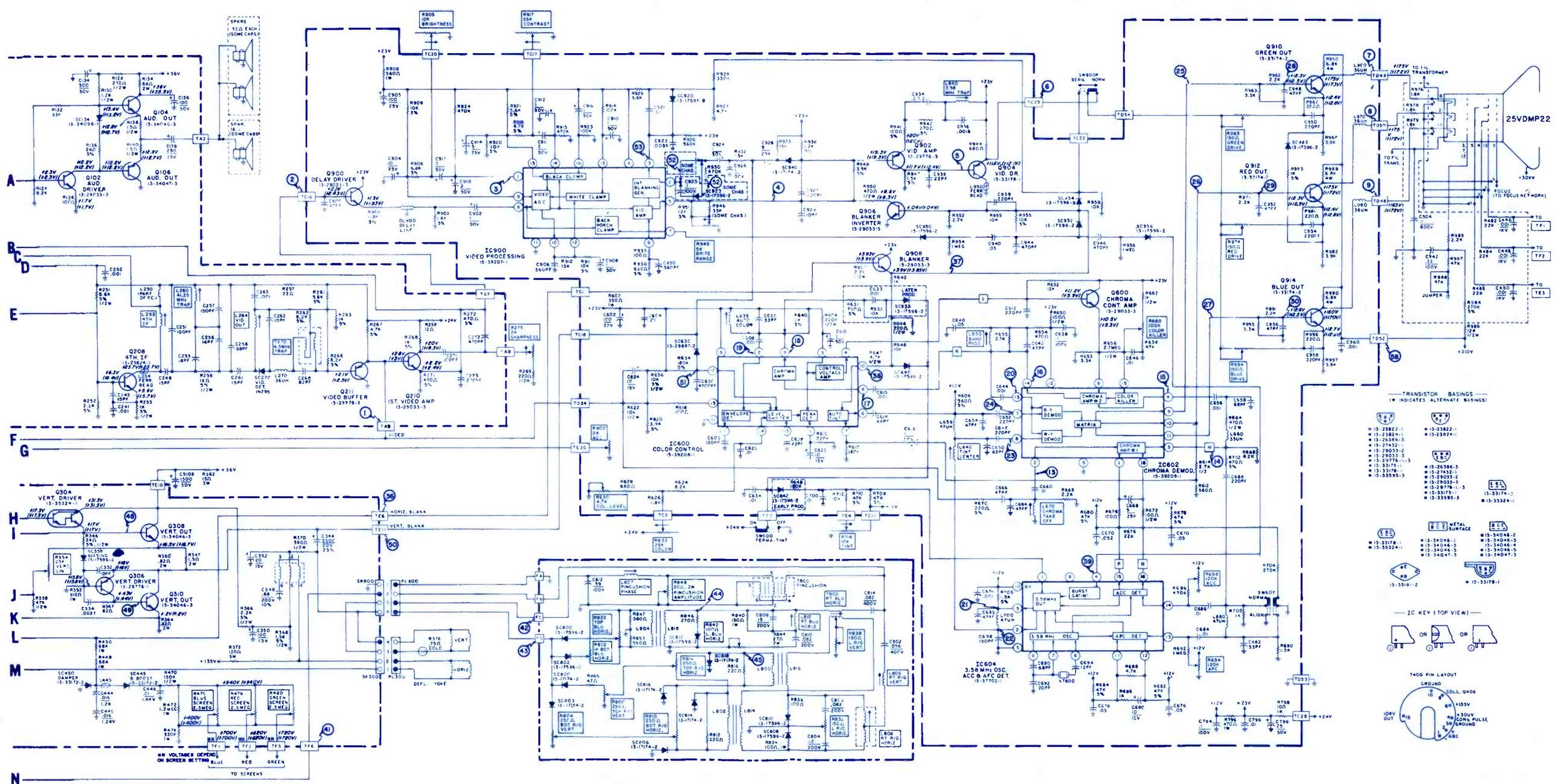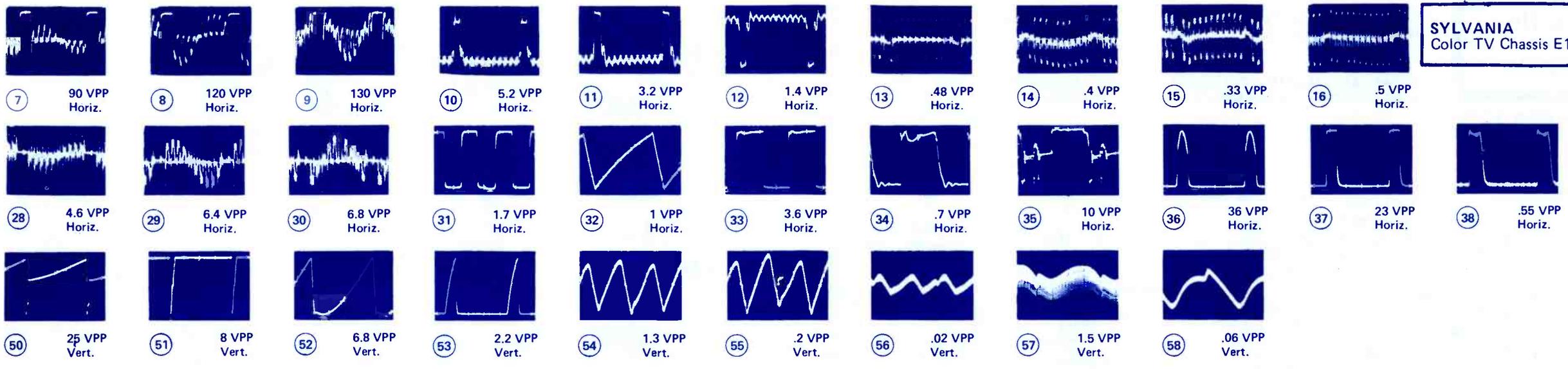


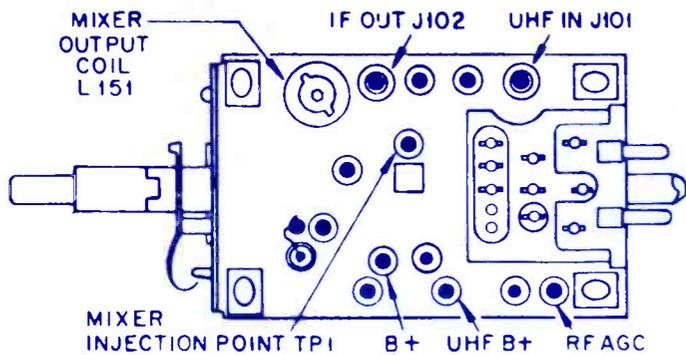



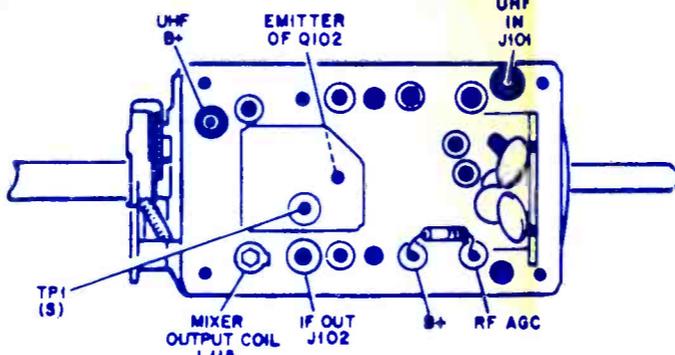
Top View of VHF Tuner (94A433-2) Showing Test Point and Alignment Locations



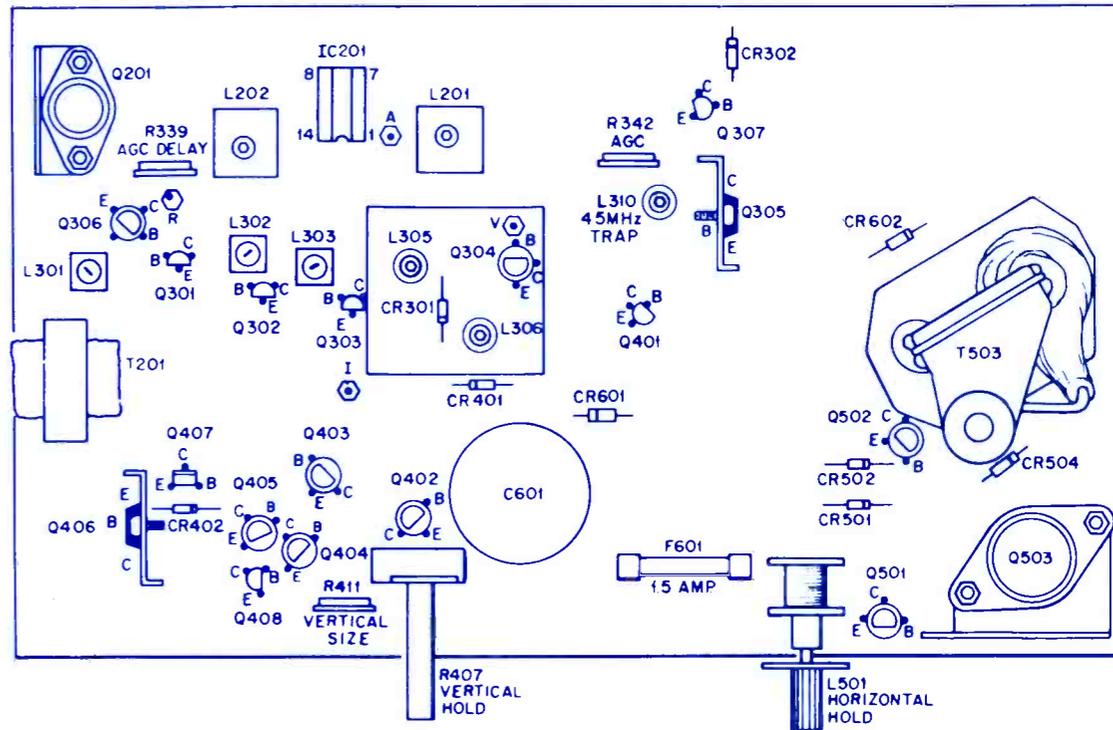Top View of VHF Tuner (94A434-2) Showing Test Point and Alignment Locations



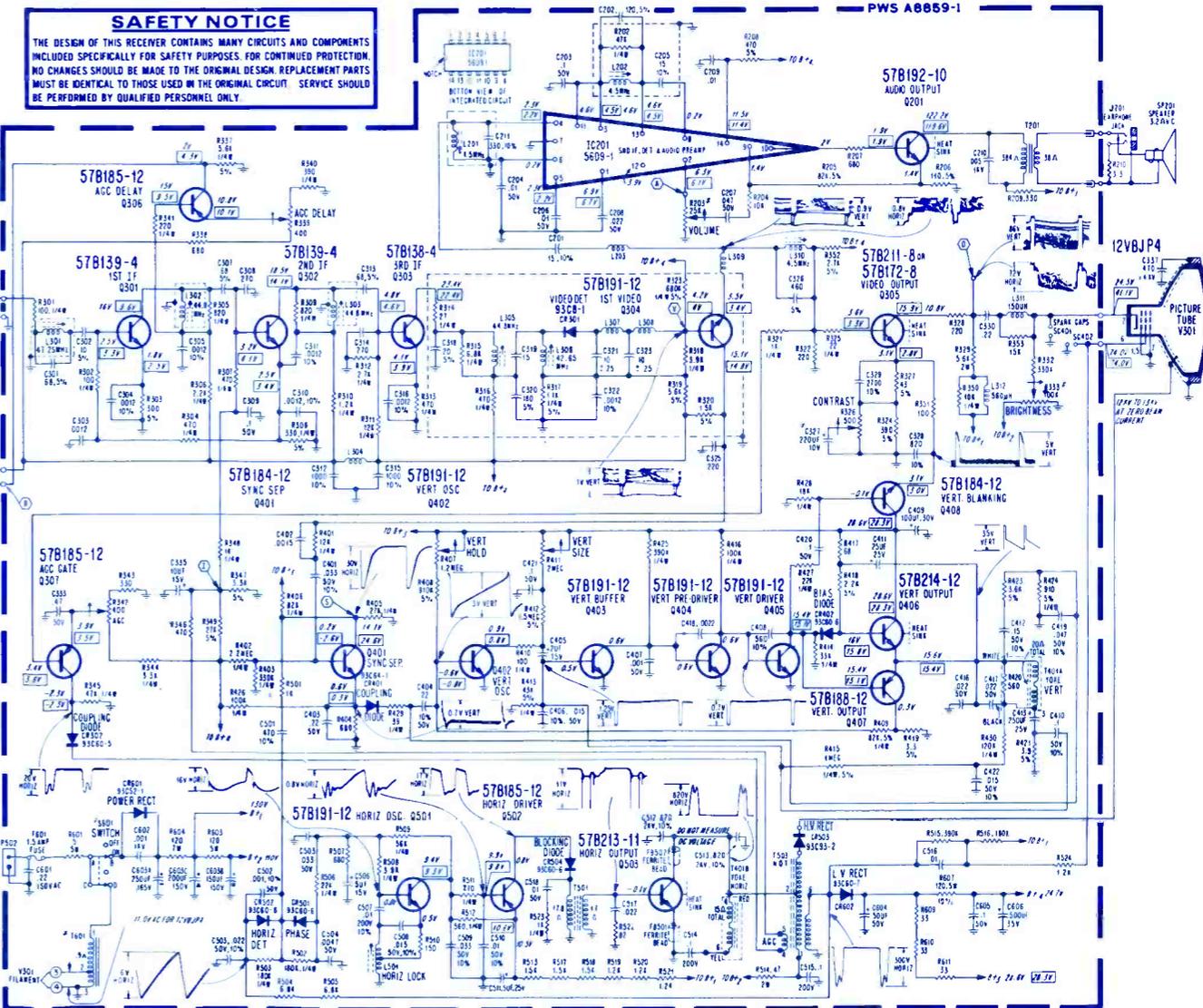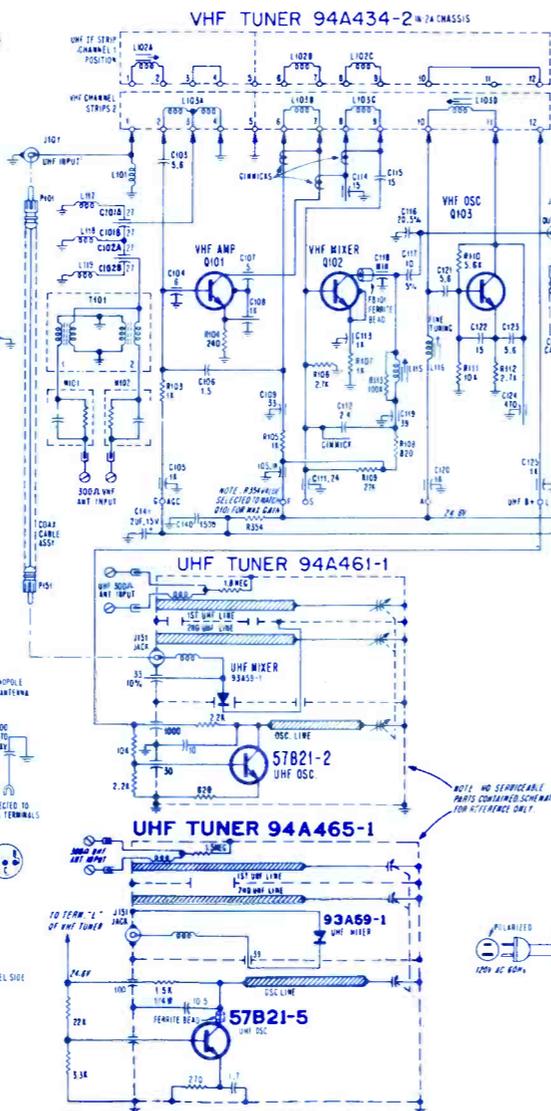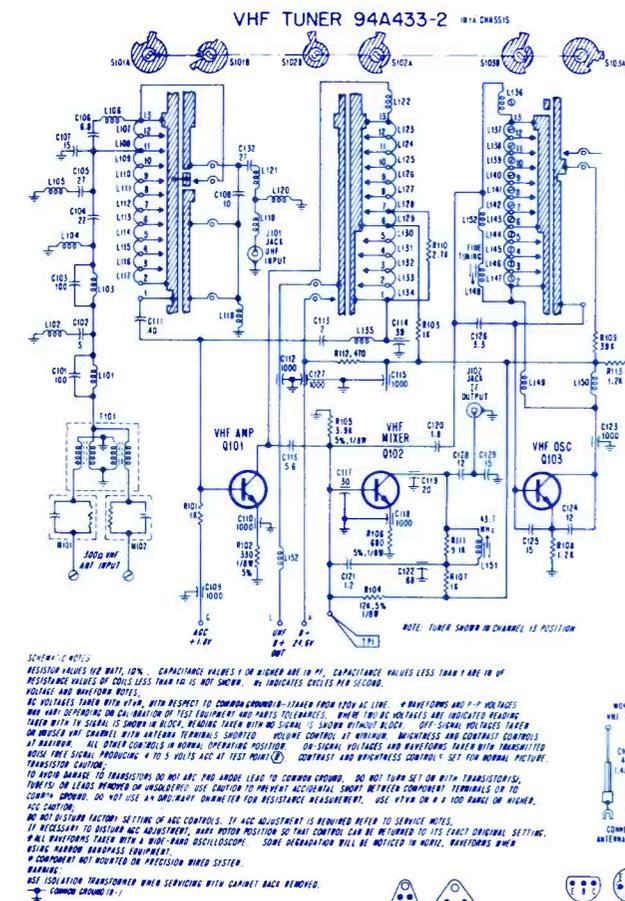Top View of Chassis Showing Alignment Locations and Test Points



SAFETY NOTICE
THE DESIGN OF THIS RECEIVER CONTAINS MANY CIRCUITS AND COMPONENTS INCLUDED SPECIFICALLY FOR SAFETY PURPOSES. FOR CONTINUED PROTECTION, NO CHANGES SHOULD BE MADE TO THE ORIGINAL DESIGN. REPLACEMENT PARTS MUST BE IDENTICAL TO THOSE USED IN THE ORIGINAL CIRCUIT. SERVICE SHOULD BE PERFORMED BY QUALIFIED PERSONNEL ONLY.

CHASSIS IDENTIFICATION

MODEL	CHASSIS
GAI-11245A	T1L6-1A
GAI-11245B	T1L6-2A
GAI-11265A	T1L6-1A
GAI-11265B	T1L6-2A

Jim is one of the busiest antenna installers in Pennsylvania. He does work for 17 major appliance dealers. But the bulk of his antenna sales come from his own advertising, yellow page listings and word-of-mouth recommendations from satisfied customers.

JERROLD 
a GENERAL INSTRUMENT company

Jim doesn't try to be the cheapest — only the best. He stresses quality of workmanship plus quality of materials. With this philosophy and a lot of hard work, Action Sales has doubled sales volume each of the four years since Jim started the business.


"My reputation means everything to me," says Jim. "That's why I'm so delighted with the performance and durability of the Jerrold Super VU-Finder line. My customers aren't much interested in the technical specifications. But, they do want excellent color quality without interference and no problems from their antenna. And that's what Super VU-Finder delivers."

For more information on the Super VU-Finder line, contact your local Jerrold Distributor or ...

JERROLD ELECTRONICS CORPORATION
Distributor Sales Division
P.O. Box 350
200 Witmer Road, Horsham, Pa. 19044

**THE JERROLD
SUPER
VU-FINDER
IS THE FINEST
ANTENNA
EVER BUILT!**

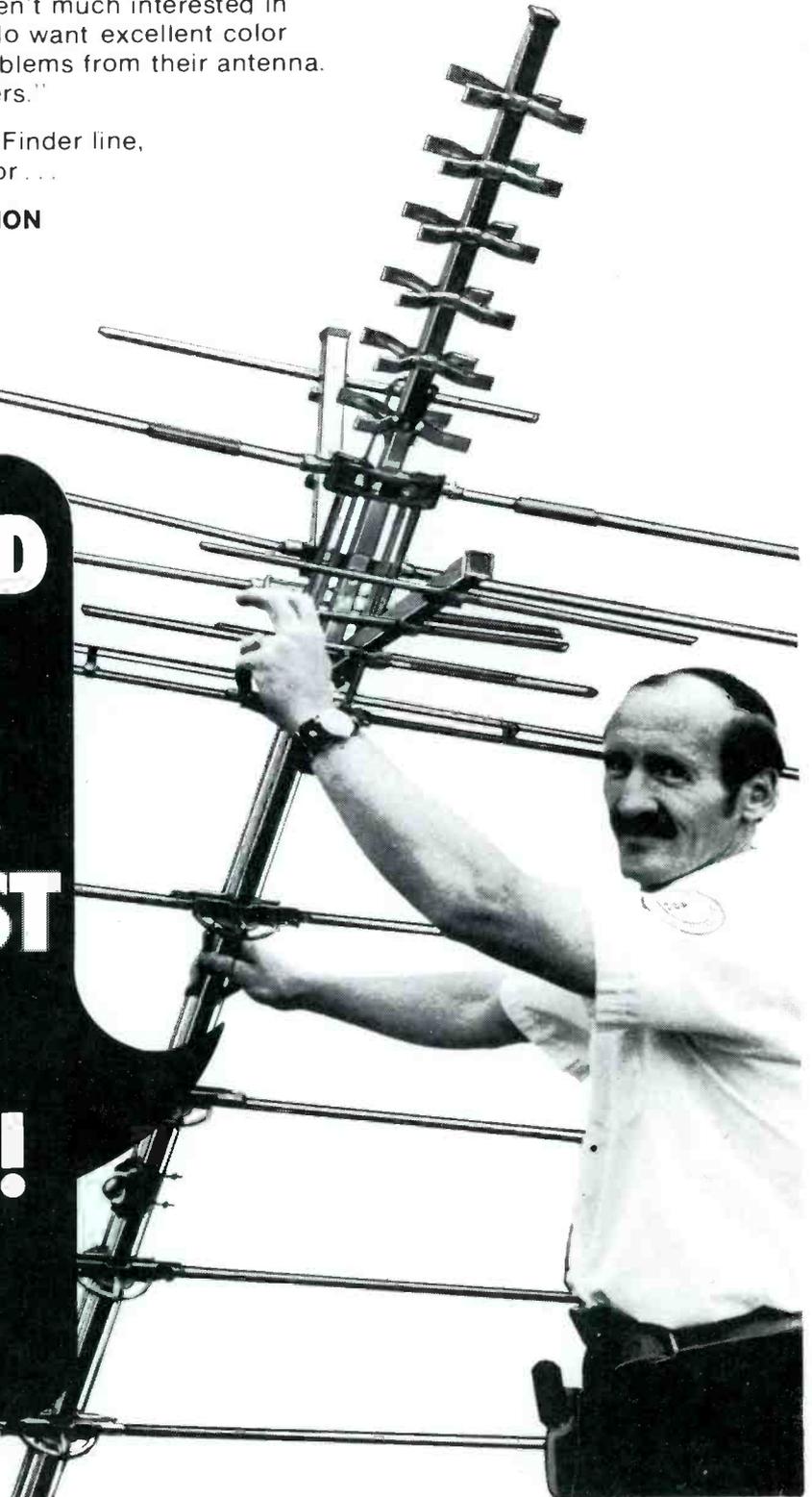**SAYS JIM WELLENER
ACTION SALES
FEASTERVILLE, PA.**



The easy-to-read 630 makes learning easy.

The Model 630 V-O-M is priced at a thrifty \$72.

The rugged, general purpose Triplet Model 630 is the kind of dependable V-O-M that both teachers and students appreciate. And for the same reasons the electronic and electrical maintenance professionals do. Uncompromising accuracy. Sturdy lightweight (only 3 lbs. with batteries). Simplified single switch operation holds errors to a minimum, and diode overload protection for the meter suspension movement reduces the chance of tester damage when mistakes do occur.

With long, clean scales covering 27 ranges in only four arcs, the Triplet Model 630 is remarkably easy-to-read.

It's packed with major features:

1. Diode overload-protected suspension movement V-O-M; single range switch minimizes error.
2. 4 Ohmmeter range with 4.4 ohms center scale.
3. Simplified scale—only 4 arcs for all 27 ranges.

Sensitivity is 20,000 Ohms per Volt DC, 5000 Ohms per Volt AC.

Accuracy is an excellent 2% on DC, and 3% on AC. Measures resistance to 100 megohms, with 6,000 Volt AC and DC capability.

Handles DC microamperes 0-60, and DC milliamperes 0-120, both at 250 mV, and can read DC amperes 0-12.

Rugged black molded plastic case with removable black leather carrying strap. All this for just **\$72**.

Get the same convenience and operating advantages plus 1½% DC accuracy and mirrored scale with the Triplet Model 630-A, priced at only **\$83**.

For more information or a free demonstration, call your Triplet

distributor or sales representative. For the name of the representative nearest you, dial toll free (800) 645-9200. New York State, call collect (516) 294-0990. Triplet Corporation, Bluffton, Ohio 45817.

TRIPLETT
ALL YOU'LL EVER NEED IN V-O-M's.



Triplet. The easy readers.

... for more details circle 129 on Reader Service Card