




SERVICE DEALER

OCTOBER
1956

50c



and ELECTRONIC SERVICING

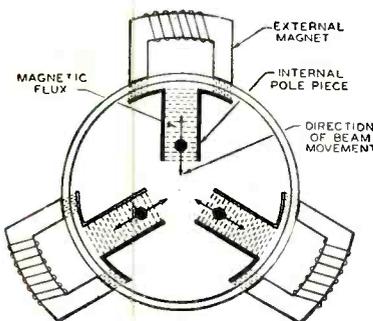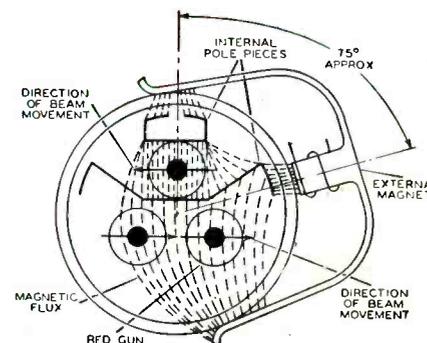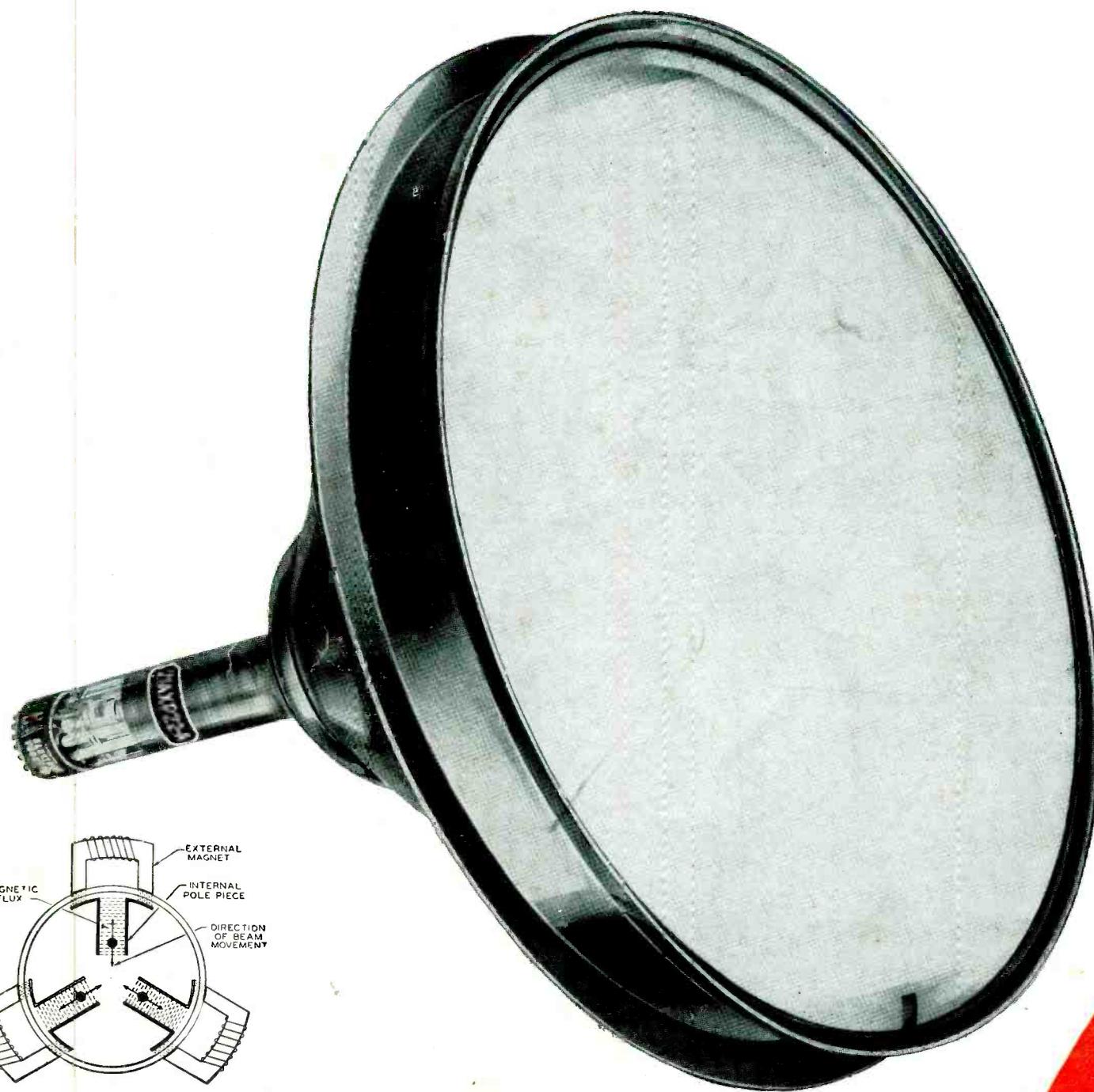

Crystal Calibrator
"Topliner" Antenna
Travelling Wave Antenna
Color Luminance Section
Tapping TV Transmission Lines

EDITORIAL STAFF

Sanford R. Cowan Publisher
 Samuel L. Marshall Editor
 Oscar Fisch Assistant Editor
 Robert T. Dargan Technical Editor
 Charles W. Gardner, Jr. Editorial Production Manager
 San D'Arcy Contributing Editor
 Paul Goldberg Contributing Editor
 Elbert Robberson Marine Communications Editor
 Lawrence Fielding Hi-Fi & PA Editor

BUSINESS STAFF

Advertising Sales

| | |
|------------------------------------|--|
| New York and East | Richard A. Cowan Jack N. Schneider 67 West 44th Street New York 36, N. Y. MUrray Hill 7-2080 |
| Chicago and Midwest | Jim Summers 400 North Michigan Ave. Chicago 11, Illinois SUperior 7-1641 |
| West Coast | Ted E. Schell 2700 West 3rd Street Los Angeles 57, Calif. DUnkirk 2-4889 |

David Saltman Advertising Production Mgr.

CIRCULATION

Harold Weisner Circulation Manager
 Carol J. Binderman Ass't Circulation Mgr.


SERVICE DEALER and ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 67 West 44th Street, New York 36, New York, MUrray Hill 7-2080. Subscription Price: \$3.00 one year, \$5.00 two years in the United States, U.S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50¢. Second Class Mail privileges authorized at New York, N. Y.

POSTMASTER: SEND FORM 3579 TO SERVICE DEALER and ELECTRONIC SERVICING, 67 WEST 44TH STREET, NEW YORK 36, N. Y.

Everything You Need for Profitable Rotor Sales


CDR ROTORS

have EVERYTHING

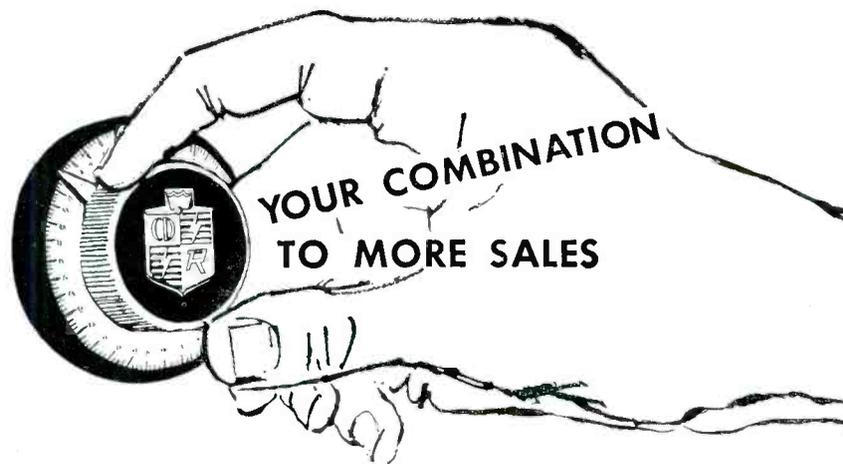


THE COMPLETE LINE
 ... a model for every need ... whatever
 the application there is a CDR Rotor that
 meets the situation best!

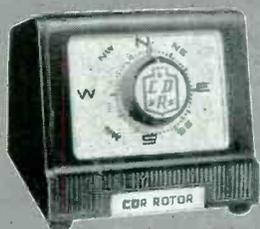
PRE-SOLD FOR YOU!
 The greatest coverage and concentration of
 full minute spot announcements on leading
 TV stations in every major rotor market is
 working for YOU...pre-selling your customers!




AR 1 and 2

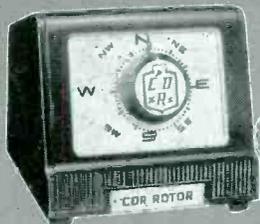

AR-22

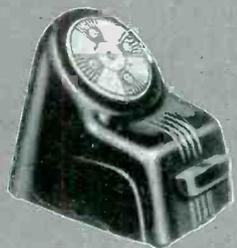

TR-2

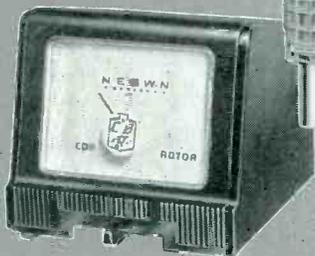

TR-4



TR 11 and 12



CORNELL-DUBILIER
 SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
 CLEVELAND 13, OHIO

SERVICE DEALER

and ELECTRONIC SERVICING

VOL. 17, NO. 10

Member

BPA

OCTOBER, 1956

FEATURE ARTICLES

- Compatible Crystal Calibrator**, by *Winston H. Starks* 6
Servicing color TV sync circuits with a compatible crystal calibrator.
- Terminated Travelling Wave Antenna**, by *Harold Harris* 8
New type of high gain antenna is described in detail.
- Color TV Luminance Section, Part 2**, by *Bob Dargan and Sam Marshall* 12
Horizontal and vertical blanking and delay circuits in luminance sections are analyzed.
- Auto Radios for 1956—Pontiac**, by *Andrew V. Dopple* 16
Installation and service notes are given on this line of car radios.
- Taco Topliner Antenna**, by *F. R. Voorhaar and Robert T. Leitner* 18
The characteristics and operation of the newest Taco antenna.
- Tapping TV Transmission Lines**, by *Ira Kamen* 24
Coaxial transmission line coupling is described.
- Pricing Index**, by *San D'Arcy* 48
Sound business procedures are given on parts pricing.

CIRCUIT AND SERVICE FORUM

- Complete Manufacturer's Schematics**
- RCA TV Portable Chassis KCS102B 27
G.E. TV Portable Chassis "T" Line 28
Emerson TV Portable Chassis 120331-H, 120332-R 29
Admiral TV Portable Chassis 14YP3B 30
- Video Speed Servicing Systems**
- Philco 440 chassis 43
G.E. "O" line 45
- The Answerman**
- Du Mont RA-340 vertical bounce 20
G.E. vertical stretch 21
Crosley 477 horizontal sync 22
- Workbench**
- CBS Color Chassis 205 32
RCA KCS48T 35

DEPARTMENTS

- S. R. Cowan Ad Libs** 2 **Buyer's Directory** 34
Association News 5 **Trade Flashes** 38
Rider Speaks 36 **Advertisers' Index** Cover III


THIS MONTH'S FRONT COVER

The 21AXP22-A RCA directly viewed picture tube of the metal-shell type for use in color TV receivers is shown. Above and to the right of the tube is a schematic of lateral-converging pole pieces while the lower left drawing shows a schematic of the radial-converging pole pieces. These converging magnets are important in adjusting the color receiver.

Entire Contents Copyright 1956, Cowan Publishing Corp.

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.

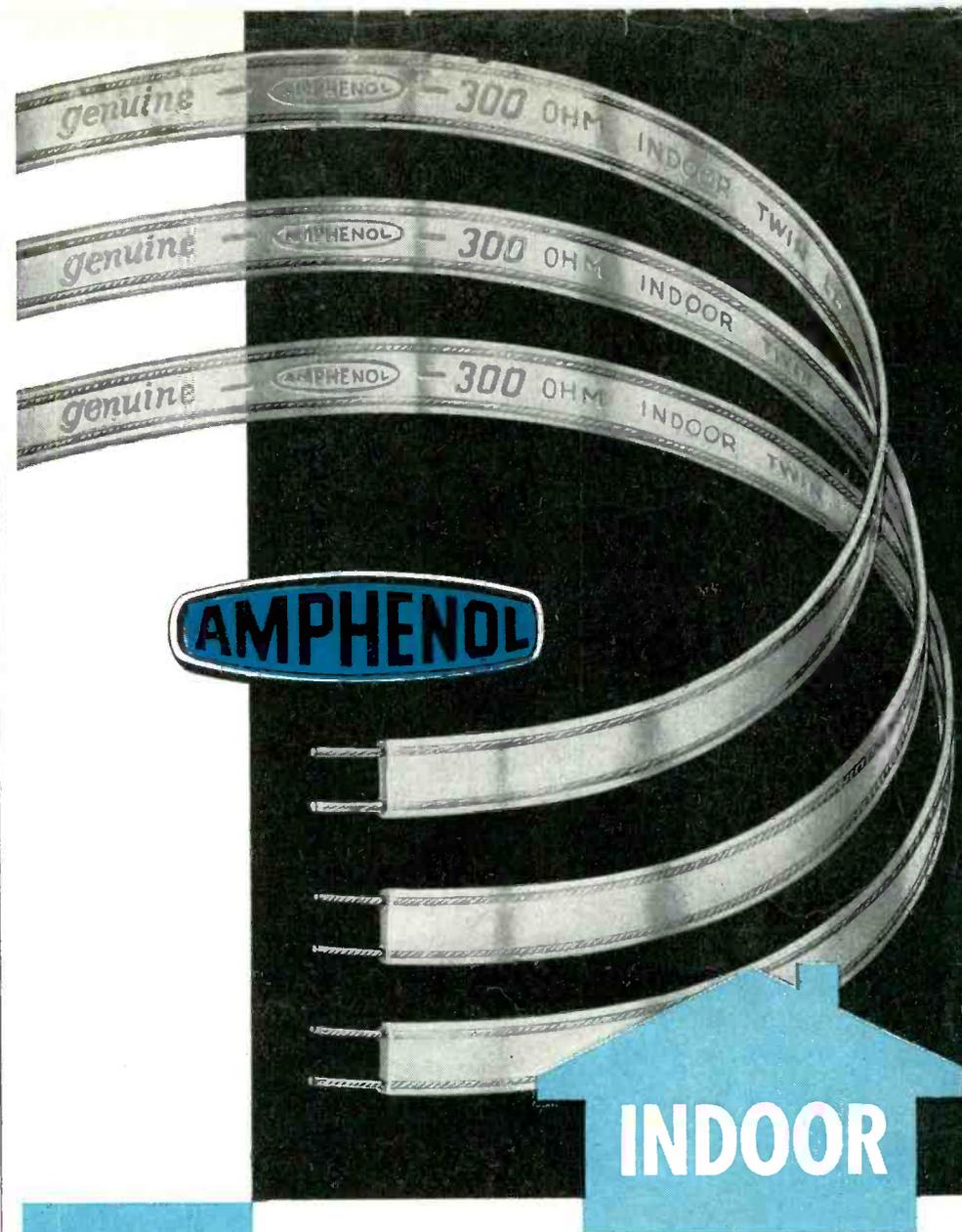SERVICE DEALER and ELECTRONIC SERVICING • OCTOBER, 1956



INDOOR

TWIN LEAD

IT'S BRAND NEW, it's quality, it's a natural—AMPHENOL Indoor Twin Lead! *Indoor* is made of pure virgin polyethylene for guaranteed performance, is extruded in beautiful, natural color to harmonize with any interior, and is available both in reels and handy hanks to make your selling job easier. Aside from its natural color, Indoor Twin Lead is a twin to famed AMPHENOL 214-056. And even though the more expensive clear natural polyethylene is used, Indoor costs you no more, and is fairly priced to give good profit margins.

 Order as 214-318. Add suffix-25, -50, -75, -100 (hanks) and -500, -1000 (reels).

AMPHENOL AMPHENOL ELECTRONICS CORPORATION
chicago 50, illinois



S. R. COWAN

Ad Libs

Industrial Electronics Servicing:

Pages 16 and 17 of September SERVICE DEALER and ELECTRONIC SERVICING each carried messages that set a precedent for the electronics service industry. Did you scan them carefully? One page carried the message that "TV and Electronics Servicemen are 'Wanted' by manufacturers of industrial electronic devices." The manufacturers referred to have sold and installed thousands of different types of industrial electronic devices to industry. These manufacturers, at the outset, provided factory service to the users of their equipment. But now the service volume has become so great—now the users of the equipment are located in so many remote places—now there is such an acute shortage of competent servicemen—these original equipment manufacturers want to "farm out" their service contracts. They want to appoint branch service depots which can and will take over all of their service work so they can concentrate on

55,000,000
ads building new
customers and sales for you!

CHANNEL MASTER PUTS NEW SELL IN

DEALERS HAVE SOLD MORE *CHANNEL MASTER* T-W AND SHOWMAN ANTENNAS DURING THE PAST 30 DAYS THAN ANY OTHER ANTENNA DURING ANY 30 DAY PERIOD IN TV HISTORY!

Isn't it time you called your Channel Master distributor?

- ★ Full-Color Ads
- ★ 2-Page Spreads
- ★ Full-page Ads


Month after month...all thru the prime TV buying months... this continuing series of sales-stimulating ads is creating loads of lively new prospects... right in your own selling area.

NATIONAL ADVERTISING TV ANTENNAS!

"Showman" INDOOR ANTENNA

This smartly styled antenna overcomes consumer objection to ugly "rabbit-ear" antennas. Exclusive "Metro-Dyne" electronic tuning brings in pictures sharp and clear on all VHF channels. Tuning knob with channel markings just like a TV set makes channel selection so easy. It's the most powerful indoor antenna ever developed . . . and it's backed with an **UNCONDITIONAL MONEY-BACK GUARANTEE**. Engineered for Black and White and **COLOR**.

| model no. | description |
|-----------|------------------|
| 3900 | Mollogany & Gold |
| 3901 | Blond & Gold |
| 3902 | Ebony & Silver |

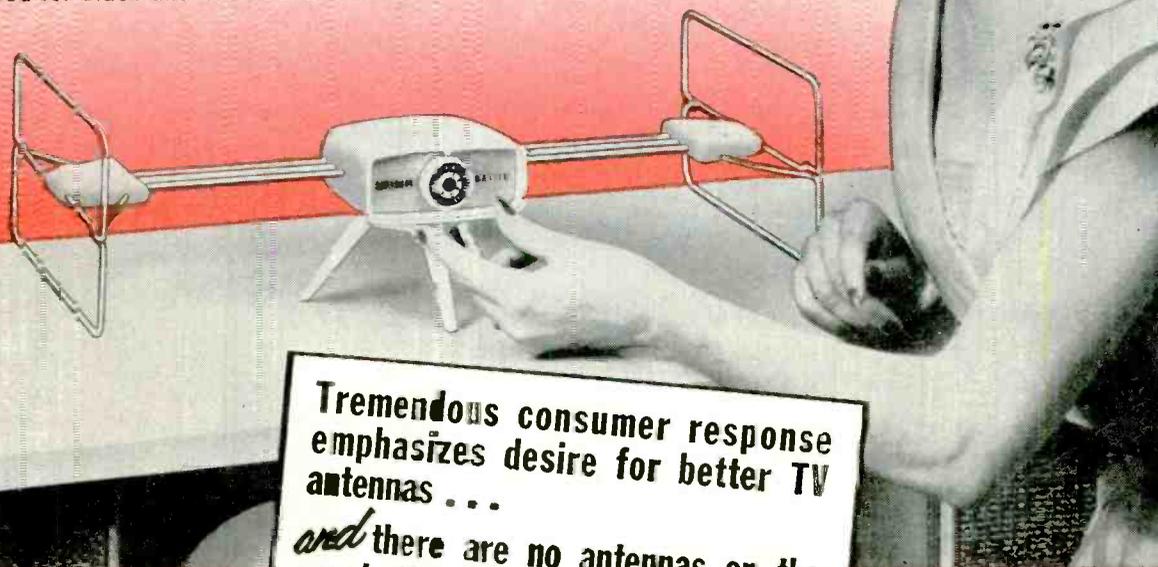

Tremendous consumer response emphasizes desire for better TV antennas . . .

and there are no antennas on the market today that compare with these fabulous new Channel Master models.

T-W OUTDOOR ANTENNA

The revolutionary new T-W is the very first TV antenna to use the "Traveling Wave" principle. This unique design electronically *reinforces* signals . . . *eliminates* "ghosts" and "snow" . . . *rejects* all unwanted signals and interference. In gain, front-to-back ratio, and mechanical strength, the T-W is unequalled by any other Broad Band antenna. Engineered for Black and White and **COLOR**.

| model no. | description |
|-----------|-------------------|
| 350 | 7-element |
| 350-2 | 7-element stacked |
| 351 | 5-element |
| 351-2 | 5-element stacked |
| 352 | 3-element |
| 352-2 | 3-element stacked |



CHANNEL MASTER CORP.

ELLENVILLE, N. Y.

WORLD'S LARGEST MANUFACTURER OF TV ANTENNAS AND ACCESSORIES

selling more new equipment to new customers. The opportunities for competent independent service firms and servicemen are magnificent!

By the same token, many of our subscribers, realizing the vast new markets and profit potential now opening to them from industrial electronic and commercial communications maintenance, have told us they would like to be put in touch with electronic equipment manufacturers who wish to set up factory service branches. Our service firm subscribers do not want to give up their present radio-TV service businesses—but they do want to expand their service activities in the industrial fields.


Now we are acting as a "Jobs Wanted" — "Jobs Offered" clearing house to bring the two groups—electronic equipment manufacturers and service firms—together so they will benefit mutually. There will be no charge or fee of any kind whatsoever for this liaison service.

Thinking Out Loud

New York, September 8th: This is an "open letter" addressed to servicemen everywhere.

In a few hours I will board a plane, destination Chicago. There, in the Windy City, next Saturday, September 15th, I will deliver an address titled "Opportunities In Industrial Electronic Servicing." My audience will be independent service shop owners, members and delegates who are attending the NATESA Convention.

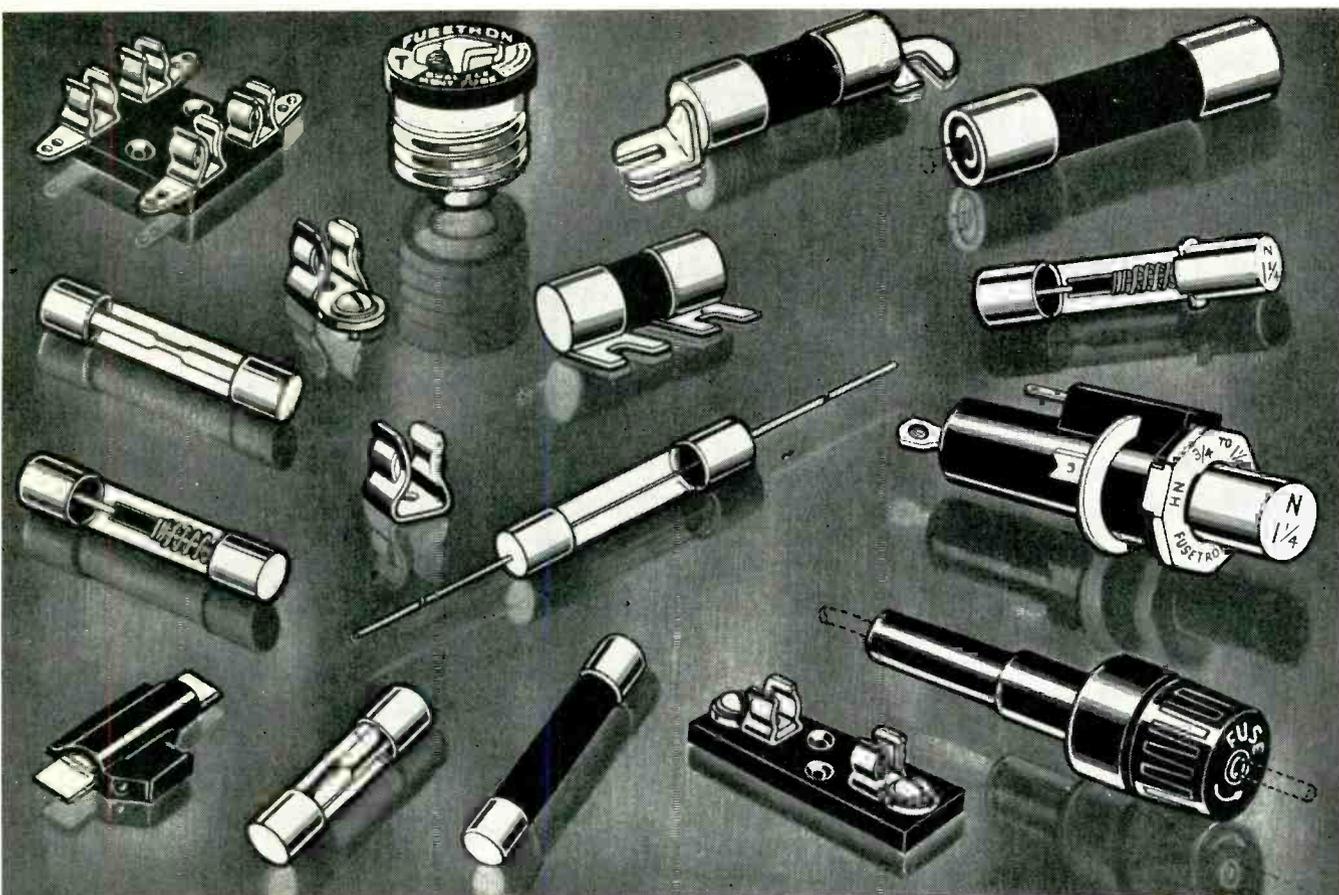NATESA is synonymous with the National Alliance of Television & Electronic Service Associations. NATESA is comprised of almost 60 independent servicemen's associations located in various



For safe electrical protection — and the elimination of needless blows, rely on BUSS FUSES . . .

When electrical faults occur, BUSS fuses open and clear the circuit. The danger of damage to equipment is reduced to a minimum.



Yet, BUSS fuses are designed and engineered so they won't blow needlessly. When you replace a blown fuse with a Fusetron or BUSS fuse, your customers are protected against useless, irritating shutdowns—and you avoid costly, time-wasting callbacks.



By relying on BUSS for all your fuse needs . . . you can help safeguard against loss of customer good will and costly troubles.

In sales and service, profit by the BUSS trademark

Millions upon millions of BUSS fuses for home, industry and automotive use have firmly established BUSS as the *Known Brand*. Handling quality products, like BUSS fuses, help you maintain your reputation for quality and service.

Be sure to get the latest information on BUSS and FUSETRON small dimension fuses and fuseholders . . . Write for bulletin SFB.

BUSSMANN MFG. CO.

(Div. McGraw Electric Co.)
University at Jefferson St. Louis 7, Mo.

Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.



1055.

sections of the country and has a gross membership of approximately 8,000 independent radio-TV service firm owners. It is too bad that NATESA's gross membership isn't 50 or 60 *thousand* because the one thing most needed by the radio-TV servicing fraternity as a whole is a spokesman.

Today NATESA is probably the largest single body of servicemen working together. There are other servicemen's associations and federations extant having memberships of varying sizes which, for one reason or another, have not found it expedient to join forces with NATESA, although they do interrelate their work with other associations. By the same token, it might be said that there are many extant servicemen's associations with which NATESA has failed to tie up for one reason or another. And, there are many thousands of independent service firm owners who have not as yet become affiliated with any servicemen's association whatever.

It is my opinion that solely and simply because many individuals and segments of the servicing fraternity have not been able to "get together" and work in harmony and unity—with a spokesman elected and authorized to voice the views of the majority—that today we find the service fraternity being "pushed around" and relegated to a much lesser status than it properly deserves.

I am sure that when I reach Chicago I will find delegates to the NATESA Convention hemming and hawing about certain present-day industry conditions which they deem are adverse to their best interests. But,—and this is a big "but"—what will the NATESA body be able to do about having those "adverse conditions" corrected? In view of the fact that at most NATESA can only claim to speak for 8,000 of this country's 53,000 service shop owners—15% of the total—well, that fact could dilute the degree of consideration their grievances will be given by those who are deemed the "offenders." How different it would be if NATESA, (or some other service industry spokesman), had the solid backing of 40 or 50,000 service shop owners and independent radio-TV servicemen. ■

ASSOCIATION NEWS

by SAMUEL L. MARSHALL

Radio and Television Guild of Long Island

The first Electronics Fair of Long Island, sponsored by the Radio and Television Guild of Long Island will be held on December 6th, 7th and 8th, 1956 at the New York State University in Farmingdale, Long Island, New York.

Thousands of dealers and technicians, together with a large segment of the general public, will attend. They will see at first hand the latest advances and newest products offered in the realm of color television, high fidelity equipment, test equipment, antennas, tools, etc. . . . in short, everything pertaining to electronics.

The lecture program committee is lining up top industry speakers to discuss technical and business problems. The following is a partial list of some of the men who have offered their time to speak at our Fair:

Mr. Miller—Vidaire Electronics Mfg. Co.

Mr. Platt—Wintronics Test Equipment

Mr. Tellis—Zenith Corporation

Mr. Dynes—R.A.M. Transformer Corporation

Mr. Dressler—Chromatic Labs

Mr. Credo—R.C.A. Service

Mr. Wendell—Service Management Magazine

Mr. Rider—Rider Publications

C.B.S. Laboratories have offered the use of their closed circuit color television camera equipment. The committee is presently negotiating with General Electric for the use of their Electronic Robot which has been demonstrated several times on television.

The Guild itself is making plans to have a large display at the Fair. In the booth will be educational material pertaining to the Television service industry in general, and to Radio and Television Guild of Long Island in particu-

lar. The Fair will offer an excellent opportunity to acquaint the general public with the fact that there is a Guild and the advantages derived from doing business with licensed Guild members.

Associated Radio-Television Servicemen of New York, Inc.

Additional information obtained from Sam Marshall, lecturer of the forthcoming color series, discloses that he will be assisted by an old friend of ARTSNY's, Bob Dargan, Technical Editor, and Oscar Fisch, Assistant Editor of Service Dealer and Electronic Servicing. Bob was former chief instructor and head of technical information and training at Philco.

NATESA, Chicago

At the Omaha, Nebraska, board of directors meeting of the National Alliance of Television and Electronic Service Association, Frank Moch, president, was named chief executive director and voted a salary plus expenses, to cover the last half of the fiscal year ending August 31, 1956. A committee was established to work out ways and means, including organizational changes, to free Moch of some of his duties, to enable him to devote more time to top level executive problems.

As steps in this direction, three governors were named. Albert C. W. Saunders will serve in dual offices, as educational director and as New England zone governor; Gordon Vrooman, Central Atlantic Zone; and Robert L. Kidd, South Atlantic Zone.

Fred Colton announced his resignation at the meeting. His post as Great Lakes governor was assigned to his former business partner, John Graham.

[Continued on page 26]

Here's why



tubular capacitors give you better performance and longer life!

All Aerovox P88N molded tubular capacitors are manufactured by a unique low-pressure, low-temperature molding process that insures perfectly centered sections with uniform wall thickness on every single unit. Only Aerovox gives you round, uniform, undistorted, coaxially-centered sections solidly imbedded in the right plastic for superb mechanical, electrical and climatic characteristics.

NOT THIS



Off-centered section

NOR THIS



Distorted section

AND NEVER THIS



Compressed section

BUT

Always THIS



Perfectly centered, undistorted, unimpaired section protected by uniform and adequate plastic wall thickness.

That's the inside story why Aerovox Duranite capacitors are recognized for their **top performance** and **utmost reliability** and **extra-generous** service life. Your local Aerovox Distributor carries a complete stock of Aerovox capacitors to meet **ALL** your service needs. Drop in soon and ask for a copy of the latest Aerovox catalog or write



AEROVOX CORPORATION

DISTRIBUTOR SALES DIVISION
NEW BEDFORD, MASS.

In Canada: AEROVOX CANADA, LTD., Hamilton, Ont.
Export: Ad. Auriema, 89 Broad St., New York, N. Y. • Cable: Auriema, N. Y.





Fig. 1—The Win-Tronix Model 120 Compatible Crystal Generator. This unit contains a precision 3.579545 mc burst frequency standard for color television.

Compatible Crystal Calibrator

Discusses the functioning and the use of an accurate test instrument for checking, aligning, and trouble shooting the reference oscillator circuits in color TV receivers

COLOR television servicing requires the use of a new frequency standard for the test and alignment of circuits which handle the color synchronizing and color modulation signals. This new frequency, 3.579545 mc, is the

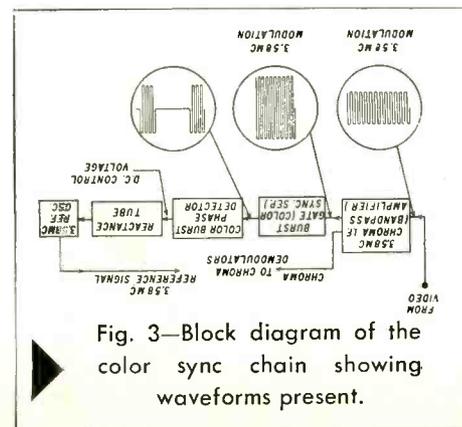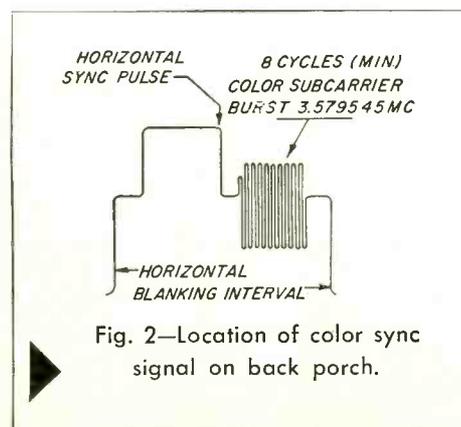color carrier, more correctly referred to as the *color subcarrier*. This color subcarrier is phase modulated by the color video, and is located precisely 3,579,545 cycles above the picture carrier, just as the sound carrier is located 4.5 mc




higher than the picture. The color carrier is a *suppressed carrier* in that it is transmitted only at the instant that some color is to be added to a certain part of the picture. It is necessary to have a 3.58 mc *color reference signal* at all times in the receiver. Therefore, it is customary to use a reference oscillator in the color TV set. This oscillator must be locked in step with the color carrier from the TV station.

In order to synchronize the receiver's reference oscillator, the station sends a short *burst* of the 3.58 mc unmodulated signal. The burst consists of about 8 cycles which appear on the back porch of the horizontal blanking pedestal. (See Fig. 2). A parallel can now be drawn between the synchronizing of the 3.58 mc reference oscillator and the synchronizing of the horizontal oscillator with which we are all familiar. Just as in the case of the horizontal oscillator,

the 3.58 mc oscillator is normally controlled by an *afc* circuit, such as a balanced phase detector.

It is also common practice to provide an adjustment, either on the front panel or on the TV chassis, which is called the *color hold* control. However, in the case of the 3.58 mc oscillator, a reactance control tube is commonly placed between the phase detector tube and the reference oscillator. The balanced phase detector develops a *dc* output voltage proportional to the amount by which the oscillator is off frequency. This *dc* correction voltage is fed to the grid of the reactance tube, which in turn reflects a change in reactance across the oscillator, causing it to change frequency and fall into synchronization. (See Fig. 3). In the light of this discussion it is apparent that the 3.58 mc color oscillator should have a definite "pull-in" range and other synchronizing charac-

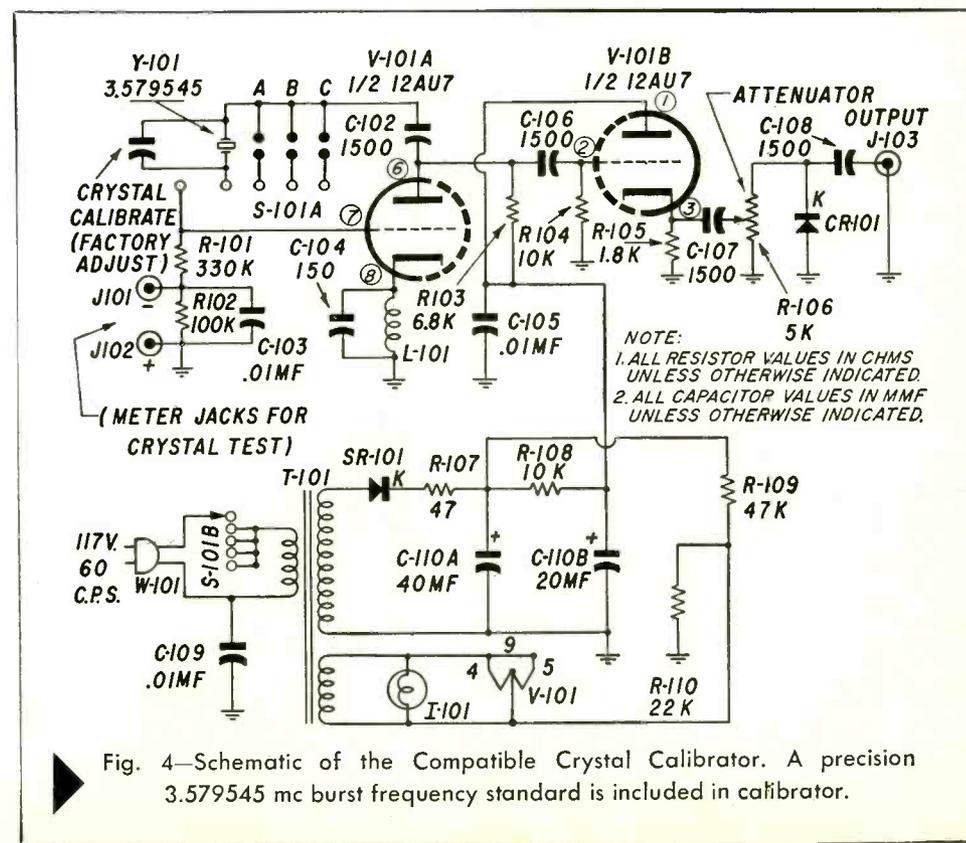

teristics similar to those of the horizontal oscillator.

One characteristic of the 3.58 *mc* oscillator is that it must be adjusted to a *high degree of accuracy*. Otherwise, the color reference oscillator may not be close enough for the phase control circuit to pull it on frequency. For example, if the phase detector circuit has a pull-in range of 358 cycles, this would represent a range of only .01% of the burst frequency. The average signal generator does not have this high degree of accuracy. The test instrument for aligning the oscillator should be at least 5 times as accurate as the required setting of .01%. Therefore, a 3.579545 *mc* standard frequency generator is needed which will have better than .002%. Without such accuracy there is no guarantee that a color receiver installed or repaired will lock in on a color program when one is received. The result would only be more call-backs and free service calls.

Description of Crystal Calibrator

The instrument shown in *Fig. 1* is the Win-Tronix Compatible Crystal Calibrator and includes a precision 3.579545 *mc* crystal standard which is calibrated to an accuracy better than .0017% or 17 parts per million, which is within 60 *cps* of 3,579,545 cycles. The drift and residual phase modulation in the unit is so small as to be negligible even in critical laboratory tests.

The color subcarrier standard crystal is mounted inside the unit and is selected by the *Function* switch. This switch will select any of three other crystals which can be conveniently plugged into the crystal sockets mounted on the front panel. Crystals from 100 *kc* to 20 *mc* can be used in the unit and selected instantly by the switch without any requirement for tuning. An output attenuator gives a range of better than 100 to 1, with a maximum output level of better than 1 volt *rms*. An internal mixer/modulator diode produces harmonics and sidebands for calibration markers and signal modulation by other generators.

Circuit Description

The schematic of the Model 120 Compatible Crystal Calibrator is shown in *Fig. 4*. The signal circuit is an extended
[continued on page 54]

IN **23,000** CITIES AND TOWNS

WESTERN UNION
"Operator 25"
is sending customers to
RAYTHEON BONDED DEALERS



Ask your Sponsoring Bonded Raytheon Tube Distributor about "Operator 25" and the many other important advantages of being a Raytheon Bonded Electronic Technician.

RAYTHEON MANUFACTURING COMPANY


Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes, Power Rectifiers and Transistors, Nucleonic Tubes, Microwave Tubes



Excellence in Electronics

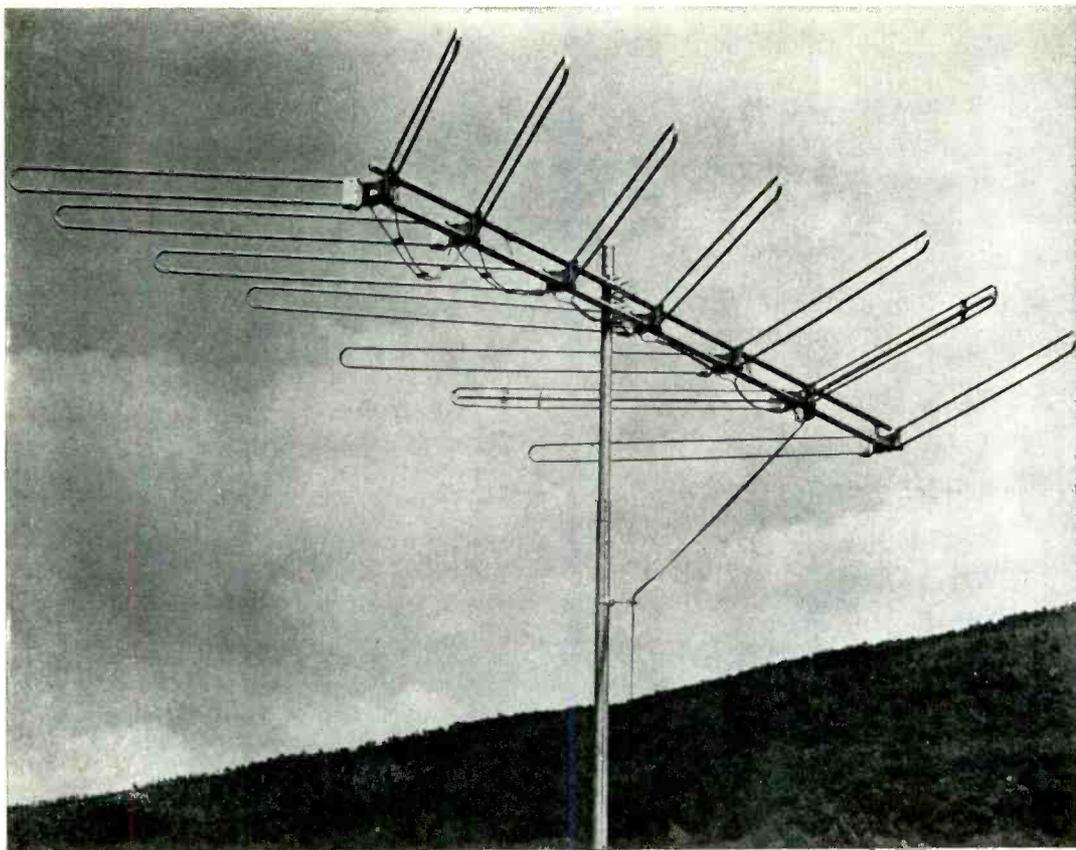

► Fig. 1—Seven element terminated travelling wave antenna.

*A discussion and explanation
of a new basic type of antenna
developed by the Channel Master Corp.*



HAROLD HARRIS

*Vice Pres. in charge of Sales & Engi-
neering, Channel Master Corp.*

TERMINATED TRAVELLING WAVE ANTENNA

by **HAROLD HARRIS**

TV ANTENNAS, over the past 10 years, represent an unusual study in swift technical progress. They actually evolved and improved more than the TV set itself, as the parade of advancing types passed by: Dipole and Reflector, Conical, Fan, Yagi, Dipole and Screen, and on up to the latest series of Broad Band VHF Yagis. This latter class has been the most powerful type of multi-channel antenna created to date, and practically every antenna manufacturer makes a version of this basic type.

The purpose of this article is to introduce and describe a new basic antenna type, which by its nature and

design represents an advance in gain, front-to-back ratio, and mechanical strength.

This new antenna, shown in *Fig. 1*, is called the "Terminated Travelling Wave Antenna." It embodies a number of important features, developed by engineers of the Channel Master Corporation. Many of these are not apparent to the casual observer. For example:

1. Six of the seven elements are "driven."
2. The phasing harness is in two sections, each with a different impedance (*Z*).
3. Despite its appearance, the antenna has no conventional folded dipoles:

- a) Five dipoles are "hairpin" or "fat" dipoles, (*Fig. 2*).
 - b) One is a 3-conductor high *Z* dipole with a shorting bar.
 - c) One is a folded reflector.
 4. All dipoles have a different length.
 5. Two different "Vee-ing" angles are used.
 6. A terminating resistor is employed.
- The configuration of this new antenna is a series of "Vee'd" dipoles. To understand the theory of its operation, it is necessary to review the basic Vee dipole. When this dipole is approximately $\frac{1}{2}$ wave on the low band, it is about 3 half waves on the high band (*Fig. 3*). Anti-phase high band opera-

tion is overcome by the fact that the center section is located 180 degrees in space behind the two outer sections. In effect, the high band dipole operates as shown in *Fig. 4*. The phase of the current changes 180 degrees as it travels to the point in space where it is abreast of the two outer dipole sections. Therefore, the current of all three sections is in phase.

It is an established and well known fact that the basic directivity patterns (and consequently, the gain) of an antenna are determined by the phase and amplitude of the current in the dipoles, as well as the position of the dipoles with respect to each other.

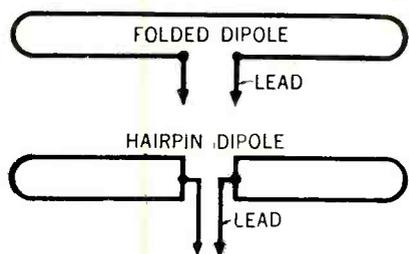


Fig. 2—Difference between folded and "hairpin" or "fat" dipole.

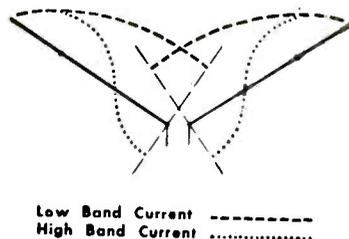


Fig. 3—High and low band current distribution of a basic Vee dipole.

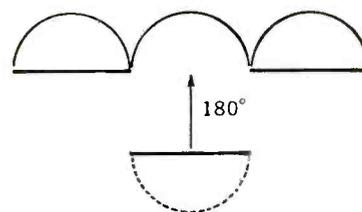


Fig. 4—Phase of current in high band dipole changes 180 degrees.

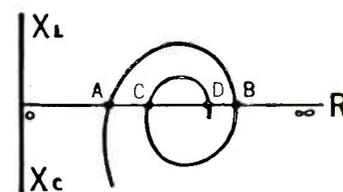


Fig. 6—Typical spiral curve of the impedance of a dipole.

Current Phase

Keeping the operation of the "Vee'd" dipole in mind, we must now think of these dipoles as impedances. Fig. 5 shows each element of the Terminated Travelling Wave Antenna as an impedance. The lines connecting the dipoles or impedances represent the phasing harness.

The harness length between each dipole is greater than the free space distance. When the total electrical harness length of the driven elements is equal to the physical spacing, plus 180 degrees, the result is termed "Increased Directivity Condition."* This produces narrower lobes and higher gain than would be obtained if the harness length and physical spacing were of equal dimensions. However, the phase relationship which produces increased directivity is not dependent on harness length alone. The phase in each dipole also depends on its impedance. Therefore, the harness must be cut to compensate for the variations in dipole impedances as described below.

Current Amplitude

By controlling the impedance of each dipole, we control the flow of current through that dipole. For maximum performance, the value of the impedances shown in Fig. 5 must be such that each dipole receives an equal amount of current. At first glance the solution would seem to be that since they are all in parallel, the impedances should be equal, and therefore, equal current would flow in each dipole. It must be borne in mind that these impedances occur in a travelling wave

antenna and each impedance is separated from its neighbor by a significant portion of a wave length.

The major achievement in the design of this antenna is the development of a series of impedances which decrease in magnitude from the feed point of the antenna to the front end, maintaining this descending series of values for every individual vhf channel.

This is best explained by considering the concept of *reciprocity*. It holds that the gain, directivity, and impedance characteristics of an antenna are the same for both receiving and transmitting. Since this is so, an understanding of this antenna will be simplified by considering it, for the time being, as a transmitting antenna.

Referring again to Fig. 5, it will be seen that the dipole of highest impedance must be at the feed point, with the impedances of the other dipoles in descending order. Since the dipole at the feed point has the highest Z , only a small controlled amount of the total current flows through it (about 1/6 of the total) and most of it continues down the harness. The impedance at the next dipole is the highest of all the remaining dipoles, and again only a small portion of the current is permitted to flow through it. The major portion of the current continues down the harness, with each impedance (dipole) getting a portion of the remaining current. The last impedance, farthest from the feed point, absorbs the remaining current.

In a travelling wave antenna any current which is not absorbed is reflected back up the harness, and this in turn, produces rear lobes. A terminating resistor, such as used on long wire rhombics, absorbs whatever power

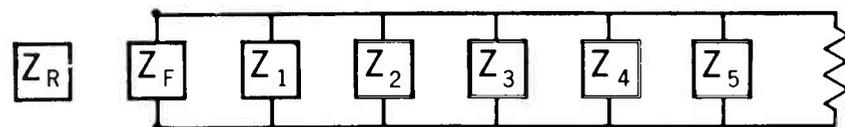


Fig. 5—Dipoles of terminated travelling wave antenna represented as impedances. Connecting lines represent phasing harness.

the dipole impedances do not. This resistor, together with the folded parasitic reflector provides front-to-back ratios higher than 10:1 (relative voltage) on all low band channels.

Methods of Maintaining Descending Impedances

A point of major importance concerns the method of controlling the descending impedance values over the entire frequency range. The solution to this problem lies in "tapering" the lengths of the dipoles so that each dipole gets progressively shorter as you go from the feed point to the terminating resistor. The theory behind this involves the basic characteristics of any dipole. Fig. 6 shows the typical spiral curve of the impedance of a dipole. The horizontal line indicates resistance of 0 to infinity. Inductive reactance is indicated by the area above the line, and capacitive reactance by the area below. Wherever the spiral crosses the horizontal line the dipole impedance is purely resistive, and the dipole is resonant. Points A, B, C, and D represent the 1st, 2nd, 3rd and 4th harmonics—or in effect, what happens when a dipole is $\frac{1}{2}$, 1, $1\frac{1}{2}$ and 2 wave lengths long. It is important to note that the dipole's characteristics are about the same between points A and B and between points C and D. The arc AB represents the impedance on the low band; arc CD, the high band.

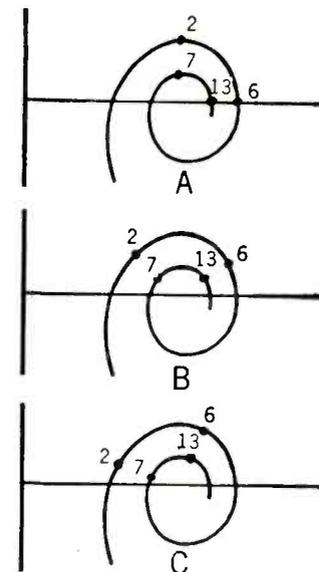


Fig. 7— Z of dipole nearest feed point is at (A); second dipole (B); and third dipole is shown at (C).


Looking at the actual antenna it will be seen that the problem of having a very high impedance at the feed point was solved by using a specially designed new type of 3-conductor dipole. The outer conductors are made of $\frac{3}{8}$ " tubing and the center conductor is $\frac{5}{8}$ " tubing. The precise impedance desired was obtained by the use of a novel shorting bar properly positioned across the 3-conductors. This new design is called the Controlled Impedance Dipole. (CID).

[Continued on next page]

*W. W. Hansen, J. R. Woodyard — "A New Principle In Directive Antenna Design," Proceedings of the Institute of Radio Engineers, 26 March 1938.

DON'T PASS UP PRINTED CIRCUIT REPAIRS!

EVERYTHING YOU NEED IS IN THE...

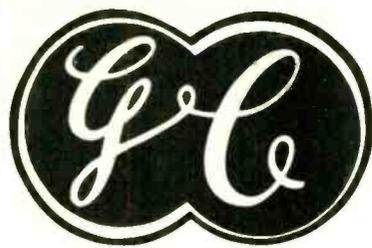

PRINTED CIRCUIT REPAIR KIT

Now you can repair any printed circuits or printed circuit wiring. This kit contains silicone resin and solvent, pure silver print, solder and tools . . . plus the G-C Printed Circuit Service Manual. Used and recommended by leading set manufacturers. Ask for G-C No. 680.



ALWAYS USE THESE G-C CHEMICAL SERVICE AIDS!



GENERAL CEMENT MFG. CO.

Division of Textron Inc.

400 South Wyman Street • Rockford, Illinois



Send 10¢ for Your G-C Printed Circuit Service Manual . . . PLUS G-C CATALOG

GENERAL CEMENT MFG. CO.

400 South Wyman Street, Rockford, Illinois

Please send me your Printed Circuit Service Manual and G-C Catalog. I am enclosing 10c (coins or stamps), to cover cost of handling and postage.

NAME _____

ADDRESS _____

CITY _____

ZONE _____

STATE _____

The next dipole is a hairpin type, which has better impedance characteristics than either a folded or straight type. It is cut so that it is a full wave on channel 6. Its characteristics, Fig. 7A, show that this dipole has its greatest low band impedance on channel 6, with the impedance decreasing with frequency. The same is true of the high band. The impedance characteristic of the second dipole from the feed point is shown in Fig. 7B and that of the third in Fig. 7C. Since the remaining dipoles are progressively shorter, the frequency points of channels 2, 6, 7, and 13 would be farther to the left. In other words, the shorter the dipole, the lower the impedance on each of the VHF channels. By comparing Fig. 7A, 7B and 7C, which represent dipoles A, B, and C in Fig. 8, it will be seen that

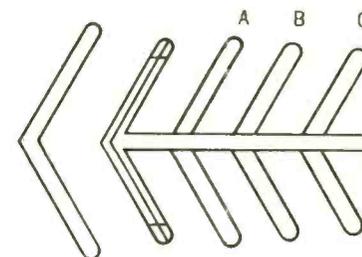


Fig. 8—Position of dipoles. Impedances decrease from feed point to shortest dipole.

no matter what channel we compare, the impedances of the dipoles decrease as we move from the feed point to the shortest dipole. This in turn creates the condition which guarantees that the current will be divided *equally* among all of the dipoles.

This is a desirable condition, since one of the basic theoretical conditions for maximum antenna performance in a multi-element antenna is that every element must receive an equal amount of current in the proper phase relationship.

This is the most basic of the limitations which cannot be overcome by the parasitic elements of a yagi. As stated earlier, both the phase and the amplitude of the current flowing in each parasite is determined by the self-impedance of the parasites and the physical spacing between them. Since there is no way to make them variable with

frequency as was accomplished with the travelling wave antenna, the broad band yagi has severe front-to-back limitations as well as major problems in broad band gain.

Mechanical Features

Since there is an apparent reawakened interest on the part of TV servicemen in the mechanical strength of antennas, this new antenna design, which Channel Master calls the T-W, should attract added attention. The antenna utilizes *folded* elements exclusively. This provides definite physical advantages. Each fold is, in effect, a truss and is actually 5 times stronger than a straight dipole of the same tubing under normal operating conditions.

The structure of the antenna is strengthened still further by an unusual type of "boom bracing." This too employs the truss principle. The "boom" actually amounts to a second full-length crossarm, joined to the basic crossarm by aluminum truss members. The entire "twin boom" unit is completely and permanently assembled in the factory by riveting.

The durability of this antenna—its exceptional resistance to excessive wind and ice loading—will appeal both to profit-conscious dealers and service-conscious consumers.

Smaller Models Developed

The original design project called for the development of an antenna for deep fringe use—very high gain and very high front-to-back ratios. This led to the development of the 7 element Travelling Wave Antenna—described and illustrated above. However, this antenna lent itself ideally to modifications for both suburban and near fringe application. As a result, 3 element and 5 element models have been developed to provide improved reception and durability for these areas as well. ■ ■

**Want to Speed Up
Your TV Servicing**

See Page 41

A MUST for Accurate TV Service at a Profit



PHILCO® Service King

Pinpoints chassis or picture tube trouble
...without removal from cabinet

At last, a multi-purpose instrument that simplifies service and saves you time and money. Completely eliminates the task of removing chassis or picture tube from the cabinet for trouble shooting. Tells whether trouble is in the chassis or picture tube. Permits checking new CR tubes without removal from original cartons. The Philco "Service King" is available now at your Philco distributor.

- Tests both color and black and white picture tubes and receivers •
- Clears picture tube shorts • Aids in setting up color purity, white balance and matrix circuits • Measures DC voltage, anode voltage and resistance.

Model 6500

PHILCO UNIVERSAL COLOR BAR AND DOT BAR GENERATOR

A single, compact instrument that puts you in the color TV service business

New, highly efficient and compact. Designed to provide the widest possible variety of functions. Unmatched for trouble shooting of circuits associated with color reproduction, and making accurate convergence adjustments in any color receiver made. In conjunction with your present monochrome equipment, it gives you complete color service facilities.



Model 7100

Write for FREE brochure on the complete line of Philco test equipment today.

PHILCO TUBES
IMPROVE THE
PERFORMANCE OF
ANY TV OR
RADIO RECEIVER

PHILCO CORPORATION
ACCESSORY DIVISION • PHILADELPHIA 34, PENNA.



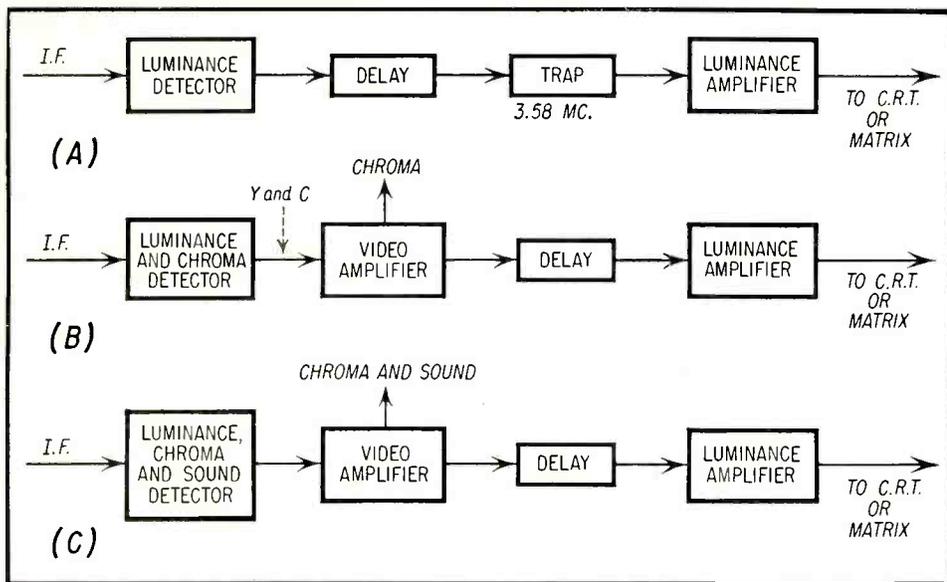


Fig. 1—Three types of luminance systems found in color TV receivers are shown in block diagram form with chroma and sound take off points.

COLOR TV LUMINANCE SECTION

THREE general types of luminance section systems are found in color TV receivers, as is shown in Fig. 1. In the first (Fig. 1A), one detector is used for the luminance signal, and another detector (not shown) is used for the chroma and sound signals. In the second (Fig. 1B), one detector is used for the sound signal (not shown) and the other is used for the chroma and luminance signals. In the third (Fig. 1C), one detector is used for the sound, chroma, and luminance signals.

Block Diagram Analysis

Referring to Fig. 1A, we observe that any chroma signals present in the luminance circuit are removed by the 3.58 mc trap located between the delay line and the luminance amplifier.

In Fig. 1B, the output of the luminance and chroma detector is fed into a video amplifier which in turn provides separate output paths for the chroma and luminance signals. In this case, the chroma information is attenuated by designing the response characteristic of

the Y channel so that there is a rapid rolloff beyond 3 mc.

In Fig. 1C, the output of the single sound, chroma, and luminance detector is fed into a video amplifier, which in turn provides separate paths for the sound, chroma, and luminance signals.

In all of the above cases the output of the luminance amplifier is fed either to a suitable matrix where the luminance and color-difference signals are combined, or are fed directly into the cathodes of the color picture tube, in which case matrixing is effected by the color tube itself.

Of the three systems shown in Fig. 1, it will be observed that only the one shown in (A) does not require an additional video amplifier. The reason for this will be explained subsequently.

Circuit Analysis

A circuit corresponding to the block diagram system of Fig. 1A is shown in Fig. 2. The signal at the output of the second detector has a positive picture polarity. Since the signal fed into the

luminance amplifier is inverted at the plate circuit, the signal fed into the picture tube cathodes will have a negative picture polarity which is correct and proper. Coils L12, L14, L23, and L31, are the usual peaking elements designed to compensate for the distributed capacities of the circuit, and to

By BOB DARGAN and
SAM MARSHALL

From a forthcoming book entitled
"Fundamentals of Color Television"

Part 2

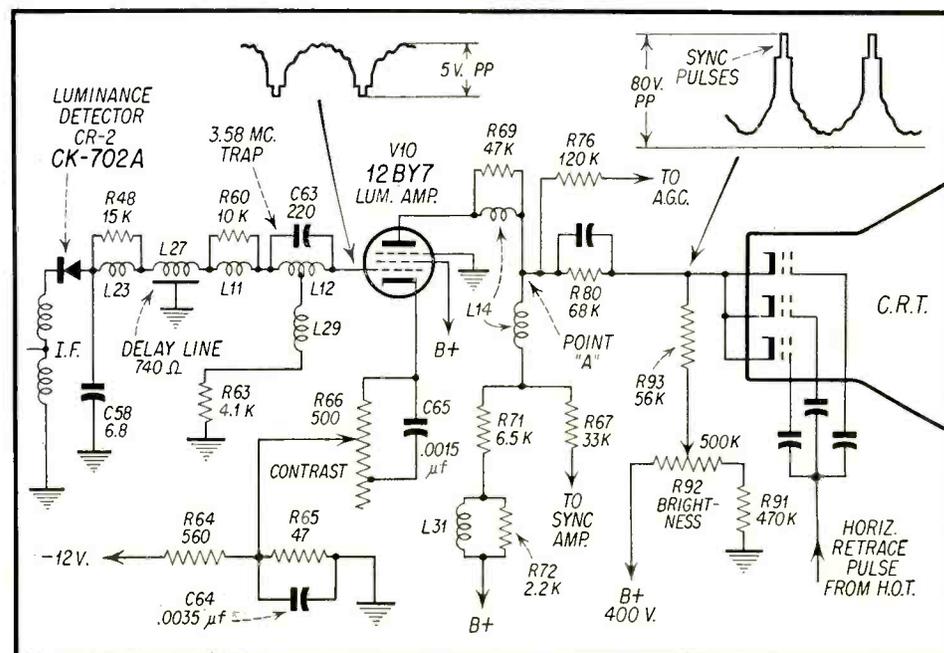


Fig. 2—Partial schematic of luminance section of Sentinel Model 1U-816.

ARE YOU COLOR-BLIND?

NOT IF YOU CAN READ THIS... BUT THE ANTENNAS YOU INSTALL COULD BE...

THE age of color ushers in your greatest challenge as well as your greatest antenna selling opportunity since the advent of television. For even the finest color TV receiver cannot deliver a satisfactory picture if the eye of the receiver—the television antenna—is “color-blind.”

Exhaustive tests by leading color receiver manufacturers have proved that an antenna must possess the following electrical characteristics to render true color reception:

1. Sufficiently high gain to override set noise and provide a clear color picture.
2. Flat response. Gain variation of not more than 1 db within 1.5 mc. below and .5 mc. above the color subcarrier.
3. Narrow unidirectional polar pattern.
4. Close impedance match to help effect a low V.S.W.R. to eliminate line reflections.

11 months ago, the JFD engineering staff undertook an intensive antenna research program. Their objective: to develop a select group of antennas that more than satisfied these stringent color requirements. The results: 8 outstanding antennas, so color-perfect in performance, that we have designated them as the NCB* Colortenna line, signifying Non Color Blind performance.

8 COLORTENNA models to choose from assure you of the right antenna answer for every location or reception problem. They spell out a great new profit opportunity for you... in replacement antenna sales... in new set sales, in trade-in sales—black and white, or color. Because now, for the first time, you can guarantee your prospects and customers both the finest black and white TV today, as well as the truest color performance possible in the future when they decide to buy.

Spearheading your antenna sales break-through will be the most spectacular sales promotion in antenna history—the NCB* COLORTENNA Sell-A-Bration!

Every COLORTENNA you sell earns you merit points for all-expense paid trips to Europe, America or any place you want to go—and a host of free valuable gifts from minks to Chris Craft cruisers. Plus newspaper advertisements, displays, streamers, direct mail, TV-radio spots, and give-aways selling you and your JFD NCB* COLORTENNA performance guarantee.



*NON COLOR-BLIND

C O L O R T E N N A S[®]



near-fringe areas.

SUPER-HELIX
Model RX511




local areas.

JUNIOR HELIX
Model JX311



fringe areas.

UHF 4-BOW HELIX
Model UX211

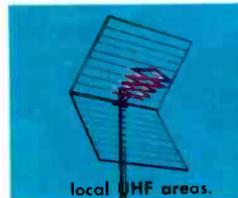

local UHF areas.

UHF CORNER-HELIX
Model UX411

American Express all-expense paid trips to Paris, Rome, Switzerland, Hawaii, Mexico, Bermuda, Havana, Miami, Las Vegas—or *any* place you name. You go *when* you want to go, *where* you want to go, *how* you want to go or...

If you prefer merchandise prizes, take your pick from over 900 of America's most wanted products—mink coats, MG sports cars, diamond rings, living room suites, Chris Craft cruisers, power mowers, and other wonderful gifts. You can't miss. *Every* point counts. *Everybody* wins.

Your JFD distributor has your NCB* **COLORTENNA SELL-A-BRATION** portfolio waiting for you. It doesn't cost you a cent—no entry blanks—no red tape. Get started *now* and *write your own ticket* in the greatest give-away in antenna history.

SALES PROMOTION EXCITEMENT FOR YOUR STORE!

- window streamers
 - displays
 - cards
- newspaper mats
 - TV film commercials
 - mailers, stickers
- TV slide commercials
 - radio commercials
 - bumper signs

JFD MANUFACTURING COMPANY, INC., BROOKLYN 4, N. Y.

world's largest manufacturer of TV antennas and accessories

International Div.: 15 Moore St., N. Y. C. • Canadian Div.: 51 McCormack St., Toronto 14, Ont.



HAVANA



LAS VEGAS



MINK COATS



CHRIS CRAFT



LIVING ROOM SUITES

tain the wideband characteristics of the detector circuit. The tapped inductance $L12$, $C63$, and $R63$ constitute a T trap producing a high rejection of 58 mc. The 4.1 K resistor $R63$ in this circuit serves a dual purpose; not only is it a part of the T trap but it also serves as the detector load.

The contrast control is connected in the cathode circuit in a manner designed to provide partial high frequency boost. Inasmuch as the cathode impedance consists of the contrast potentiometer (500 ohms) and $R65$ (47 ohms), it is obvious that $C64$ (.0035 μf) will produce an increase in stage gain for high frequencies. Capacitor $C65$ (.015 μf) is present simply to minimize the changes in circuit response as one arm of the potentiometer is moved across its range from minimum to maximum contrast.

In Fig. 3 is shown a circuit corresponding to the block diagram of Fig. 1B. The detected signal output has a positive picture polarity as it is fed into V401A the first video amplifier. A 4.5 mc sound trap is located in the plate circuit of this tube and is in series with the chroma takeoff transformer.

Note that the plate load of this tube consists of the primary of transformer T701 and the resistor that connects to B plus. The chroma signal is taken off the transformer impedance, whereas the voltage drop across the resistor provides the video signal information below 3 mc. As such, this information contains the signals required for the *agc* circuit, and the horizontal and vertical sync separator.

Note that Fig. 3 utilizes 2 tubes in the video amplifier section. This imposes the requirement that both tubes have usable gain characteristics and that the combination shall have a single phase inversion in order to provide the signal at the CRT at its proper phase. This is accomplished by designing the video detector circuit so that it is completely off ground, and its output is fed to V401A between grid and cathode. The luminance output signal from this tube is taken from $R403$ with a gain of approximately 4. This circuit is referred to as a "Bootstrap" circuit. The luminance signal is fed through the delay line and $C403$ (.1 μf) to the grid of V402, the second video amplifier. Re-

versal of the picture polarity at the plate of V402 imparts a negative signal polarity to the signal, and, as such, it is fed into the picture tube cathodes via the fixed matrix network consisting of $R418$, $R419$, and $R115$.

Contrast control is effected by $R103A$ which is connected in series with the cathode of V402, the second video amplifier, and ground. The brightness control is connected as one leg of a voltage divider between ground and the grid of the horizontal output tube which is -40 volts with respect to ground. Variation of this control produces a change of plate current, causing a corresponding increase or decrease in the voltage at the plate of V402. Since the picture tube cathodes are connected to the plate of V402, this voltage variation is transferred to the cathodes, thereby effecting an increase or decrease in brightness.

A circuit corresponding to the block diagram of Fig. 1C is shown in Fig. 4. As in Fig. 3 a bootstrap circuit is used in the detector output, the latter, in this case, containing sound, chroma, and luminance signals. Also, as in the circuit previously discussed, luminance is taken off at the cathode, and color is taken off at the plate through a chroma takeoff transformer. The sound, sync, and *agc* signals, in this circuit, are taken off at the plate return which is above rf ground by virtue of a 5K resistor ($R133$) connected between the plate return and B plus.

Connected across a portion of the secondary of the chroma takeoff transformer is a 4.5 mc sound trap. This trap effectively eliminates the 4.5 mc information and the 920 kc beat from the chrominance system.

Luminance information is fed, via the delay line, to the second video amplifier. The amplitude of the output signal is controlled by potentiometer $R134$ (contrast control) at the end of the delay line.

The brightness control consists of a potentiometer connected between ground and the -20 volt line. As in the previous circuit described (Fig. 3) variation of this control provides an increase or decrease of plate voltage which is transferred as a change of cathode potential on the picture tube, thereby increasing or decreasing its brightness.

[Continued on page 42]

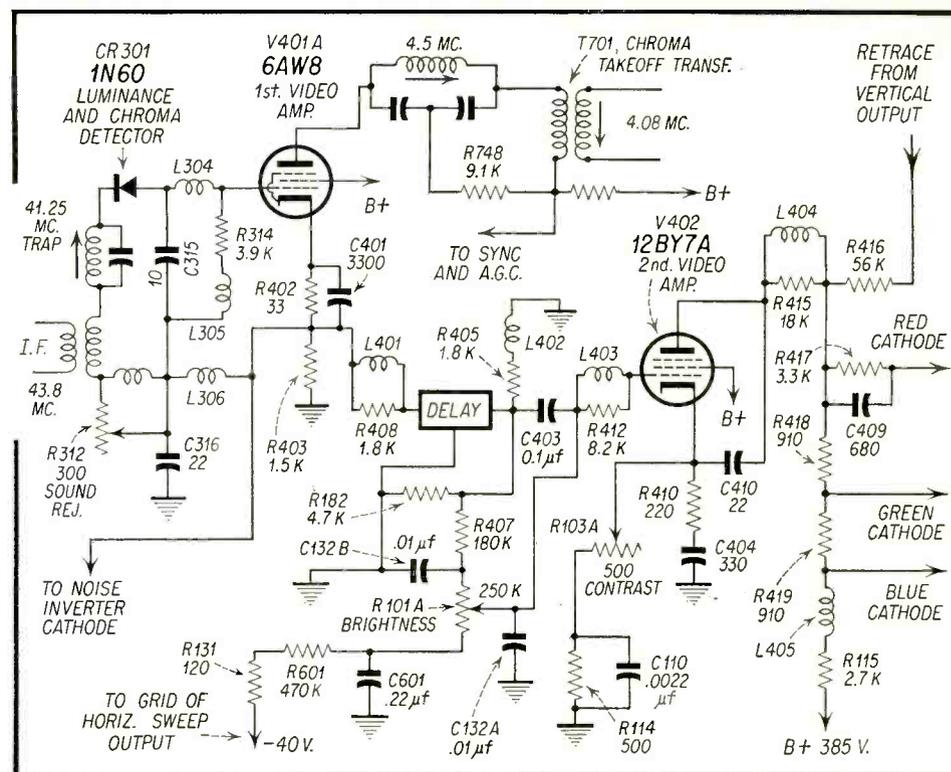


Fig. 3—The circuit diagram corresponding to the block diagram of Fig. 1B. The picture polarity is positive as applied to the first video amplifier.


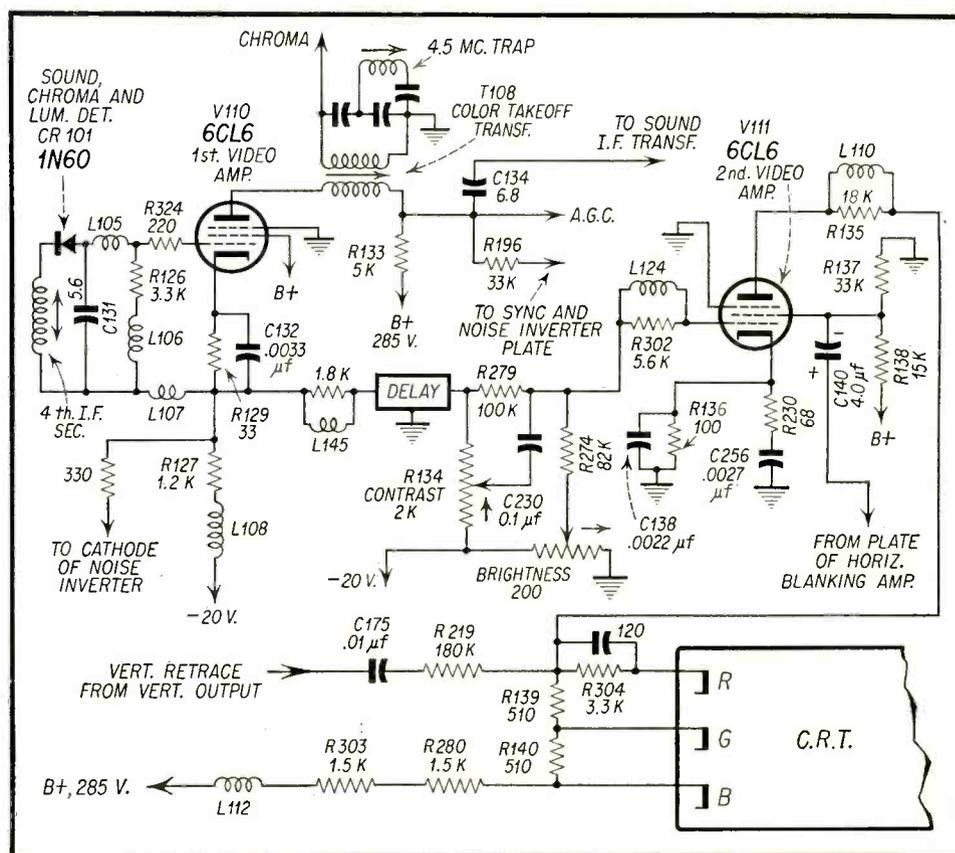


Fig. 4—The circuit diagram corresponding to the block diagram of Fig. 1C. The detector output circuit contains sound, chroma, and luminance signals.

Electro
ELECTRONIC EQUIPMENT

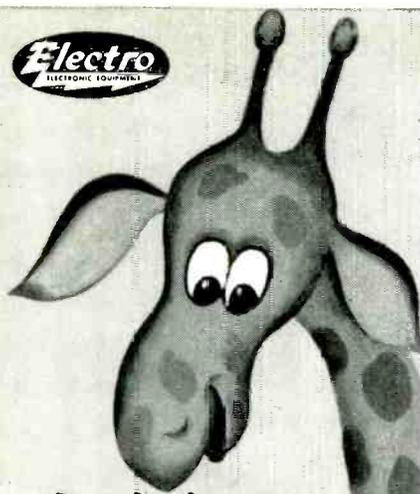

Overlooking
25%
of the profitable
radio repair
business?



Electro

MODEL D-612T

DC POWER SUPPLY

lets you service

**TRANSISTOR
AUTO RADIOS**

(services 6/12V

tube-vibrator radios, too)

* 1 out of 4 radios is an auto set

An Electro exclusive

FOR PRICES AND DATA SEND COUPON TODAY!

Electro Products Laboratories
4501-R Ravenswood Ave., Chicago 40, Ill.

Rush descriptive and technical data on MODEL
D-612T Power Supply for Transistor Auto
Radios.

Firm name _____

Address _____

City _____ Zone _____ State _____

623 Canada: ATLAS RADIO LTD., Toronto

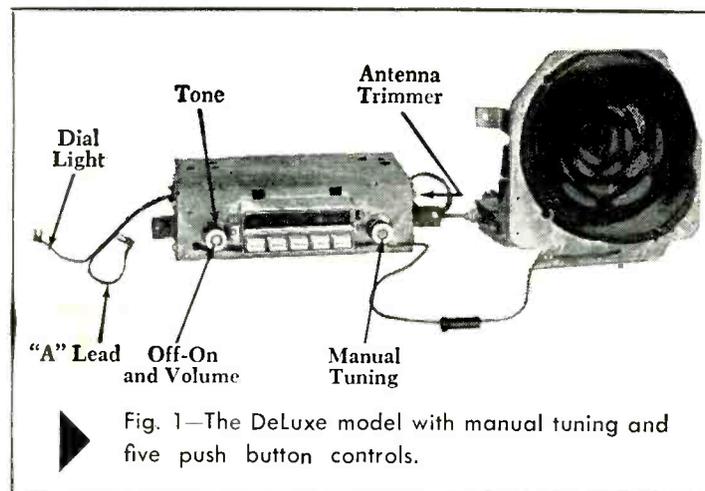


Fig. 1—The DeLuxe model with manual tuning and five push button controls.

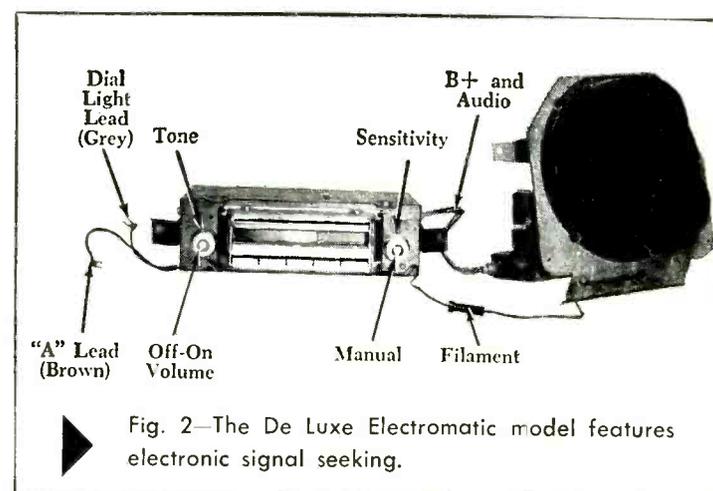


Fig. 2—The De Luxe Electromatic model features electronic signal seeking.

Auto Radios for 1956 — PONTIAC

A discussion of the important features of the two Pontiac receiver models for 1956. Tuning adjustments, removal procedures, and servicing hints are dealt with in each case.

by **ANDREW V. DOPPLE**

Auto Radio Serviceman
Frank A. Reeve Co.



THE trend in auto radio for 1956 is toward the two unit construction type, and it is this type that Pontiac offers in two 12 volt models. Both models are interchangeable in all models of Pontiac automobiles. They are custom designed and supplied by The United Motors Service Division of General Motors.

The two units consist of a tuner or rf unit which contains the complete

tuner section, and the speaker unit, which contains the complete power amplifier section with speaker.

The "De Luxe" model, part #988568, (see Fig. 1), has manual tuning plus five push-buttons, and uses six tubes in addition to a rectifier.

The "De Luxe Electromatic" model, part #988569 (see Fig. 2) features electronic signal seeking with five electronic push buttons. The tube comple-

ment is seven plus a rectifier.

The circuit of the Electronic model is identical with that of the De Luxe, except for the addition of a 12AU7 used to trigger the automatic feature. This set can be tuned manually by the right-hand control (see Fig. 2). Directly behind the manual tuning control is located the sensitivity control (see Fig. 2) which operates a four position rotary switch, which, when rotated clockwise,

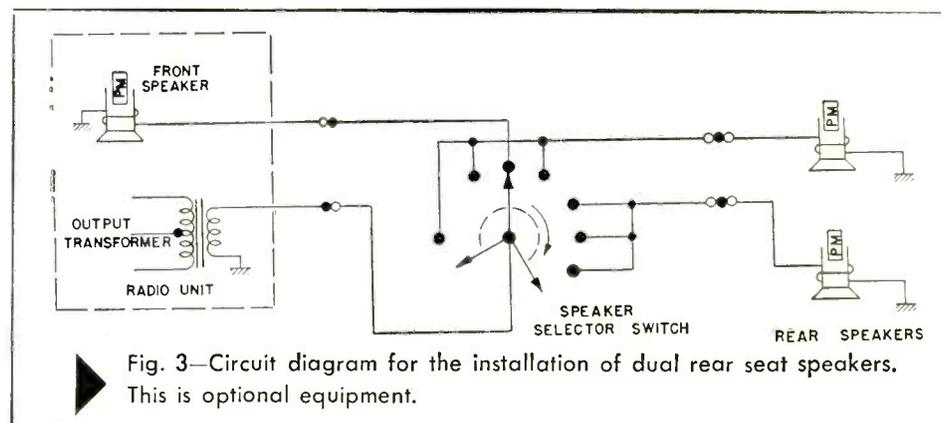


Fig. 3—Circuit diagram for the installation of dual rear seat speakers. This is optional equipment.

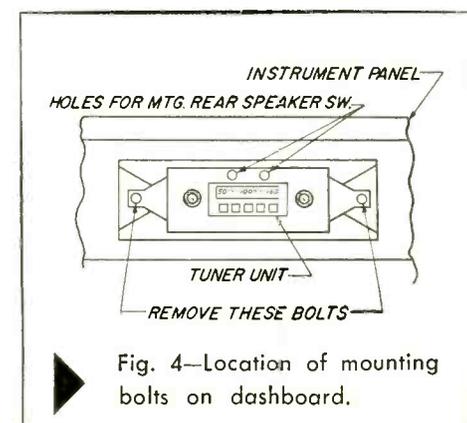


Fig. 4—Location of mounting bolts on dashboard.

increases the sensitivity of the set. Manual or automatic antennas are available.

Installation Notes

The tuner unit mounts in the center of the instrument panel directly above the glove compartment. The speaker unit mounts directly behind the speaker grille at the right-hand side of the instrument panel.

Dual rear seat speakers are optional and mount on the rear seat shelf (see Fig. 3 for installation instructions). Provision is made at the factory for ease of installation.

Antennas mount on the right front fender. Special accessory antennas are also available for rear fender mounting.

Noise suppression at the distributor is controlled by special radio type wires and no other precautions are necessary at this point. Condensers at the generator, voltage control and coil are necessary and straightforward conventional installation is followed.

The antenna trimmer condenser is located at the right side of the tuner unit (see Fig. 1) toward the speaker unit. Adjust the trimmer (after set is completely installed) for maximum volume with the radio tuned to a weak station between 600 and 1000 kc (Note: See sticker on case).

Adjustment of Push Buttons

De Luxe Model.

1. Pull push button to the right and pull out.
2. Manually tune in the desired station.
3. Push button all the way in.


De Luxe Electromatic Model.

1. Open hinged door below the tuner dial, exposing the selector tabs.
2. Tune in the nearest desired station to the left side of the dial, manually.
3. Move the first selector tab (one farthest left) until it lines up with dial pointer tip.
4. Repeat steps #2 and #3 for the remaining selector tabs, choosing stations from left to right on the dial.
5. Check the setting of each selector tab by depressing the corresponding station selector button. If

[Continued on page 50]


There is
a Difference in P.A. Speakers....
and You Can Hear it.

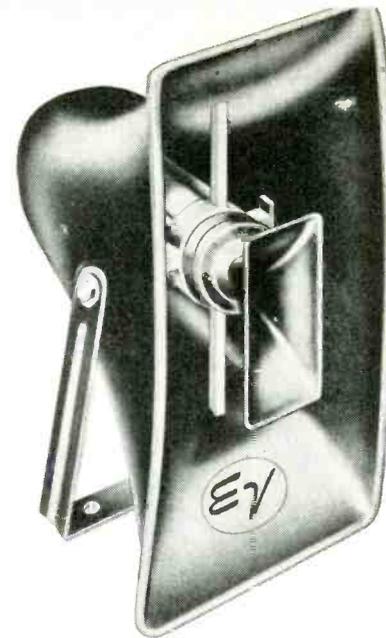Model 848 CDP for the biggest jobs. 25 watts. 16 ohms. Response, 175—10,000 cps, crossover at 1000 cps. Sensitivity rating, 52 db. Size, 10½" x 20½" x 20" Wt., 12 lbs. List \$75.00.



INTELLIGIBILITY

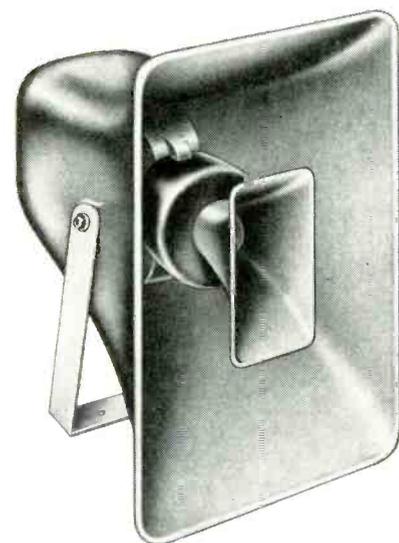Model 847 CDP for smaller areas. 12 watts. 16 ohms. Response, 250—10,000 cps, crossover at 1500 cps. Sensitivity rating, 51 db. Size, 11¾" x 7¾" x 10¾". Wt. 6½ lbs. List \$46.33.



That's What Sells the

Electro-Voice®
CDP®

See your *Electro-Voice distributor NOW*. Get the facts on sound profits with CDP—the speaker more people hear more clearly. Send for bulletin 195-SD610.

Electro-Voice

ELECTRO-VOICE, INC., BUCHANAN, MICH.

EXPORT: 13 East 40th Street, New York 16, U. S. A.


Cables: ARLAB

Canada: E-V of Canada Ltd.,
1908 Avenue Road, Toronto, Ontario

INTELLIGIBILITY and Coverage are what count in public address systems. Power alone won't do the job.

Electro-Voice tells your best prospects the CDP story. Fact-packed ads make "sales calls" on prime prospects.

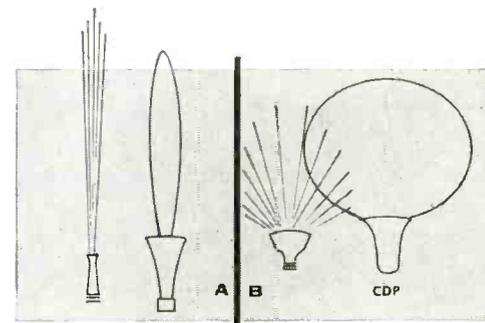Electro-Voice backs you up with informative, selling literature—printed pieces as intelligible as CDP speakers themselves!



A. This is a garden hose throwing a hard, straight beam, like a conventional P.A. horn. See how it concentrates power but sacrifices coverage.

B. This is a garden hose with a spray nozzle, covering a broad area completely, like an Electro-Voice CDP speaker. See how much more efficient the CDP pattern is.

IN THE early 1800's the suggestion was made that the United States Patent Office be closed because in the words of the legislator making the suggestion, "everything new and worthwhile has been invented." If he came back today, what a surprise he would get.

We, too, have come a long way from the earliest days of television when most TV receivers were installed in public places and used primarily to "bring in the customers." Again, the stations available were limited, with most TV sets receiving only a single channel. What a change has taken place since those days! It is almost impossible to find any part of this country where only a single channel can be received, and there are many areas where the multiplicity of signals would make satisfactory reception impossible if we had to be content with the antennas which were called "best" less than five years ago.


Engineers at TACO, for example, have devoted considerable engineering effort during the past several years to the design of new antennas. These antennas embrace a new concept in the use of driven elements. It is not enough that the elements be driven, but they must add something to performance not only from the standpoint of gain but also from that of pattern configuration. These new antennas incorporate an entirely new engineering design for coupling the elements for greater efficiency over both the high and low *vhf* bands.

Driving multiple elements in a streamlined yagi type array produces good "staying-power" in fringe and sub-fringe installations. It is only through this effective use of the elements in the antenna, that acceptable performance on a multiple number of channels is attained. Needless to say, these results are not possible without new theories which have been fully tested and developed. In the case of the popular "Trapper" series of antennas, the isolation obtained by the use of the patented traps involved new techniques. These are augmented in the "Topliner" series by a new development whereby maximum signal is transferred to the transmission line "in-phase," thereby further increasing the efficiency of the antenna.

The performance of this new *Topliner* series and the operation of the *delay line* principle is most easily analyzed by studying the electrical operation of the driven elements in conjunction with the connecting network. Since this *delay line* is designed to do its work on both the high and the low bands, it will be best to describe this combination of antenna elements in two stages. Bear in mind also, that the frequency separation between high and low band channels involves a third factor.

First Driven Element

Fig. 1 shows a schematic drawing of the "controlled drive" type of antenna which is the subject of this article. The development of this antenna begins with a basic end fed antenna made with an ordinary open

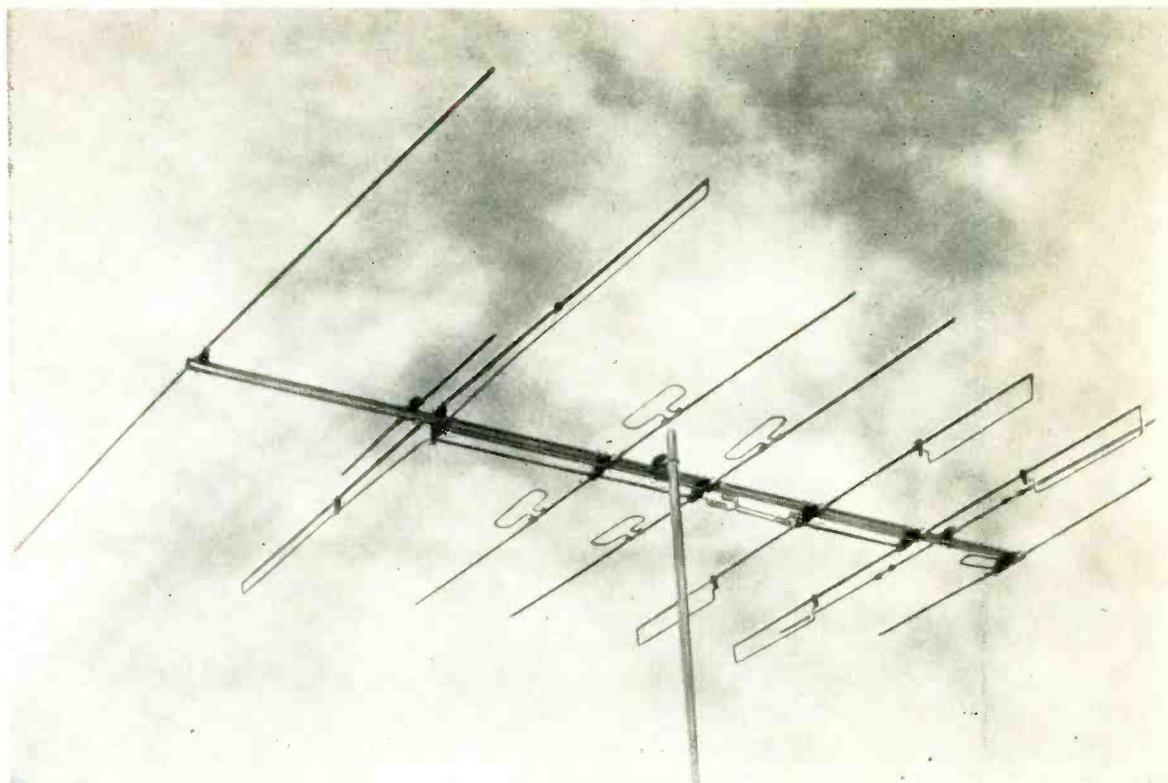

TACO TOPLINER ANTENNA



A description of the construction, operation, and characteristics of the newest TACO antenna.

by F. R. VOORHAAR and ROBT. T. LEITNER

Technical Appliance Corp., Sherburne, N. Y.



wire transmission line and illustrated in *Fig. 2a*. Here we have one wire cut shorter than the other by one halfwave length at the mean high band frequency. The instantaneous current distribution is shown by the dotted line. Let us go one step further and use two of these antennas placed end to end, feeding them in parallel. This results in the antenna shown in *Fig. 2b*, and we now have an antenna which is 3 half wave-lengths long at high band and approximately one half wavelength at the low band. However, because of the method of feeding, the operation at low band frequencies will be found to be rather inefficient.

By feeding this antenna array in series rather than in parallel, as in *Fig. 2c*, we accomplish two things. First we improve the high band characteristic by increasing the impedance and secondly we have the well known center fed half wave dipole for the low band. The short bar associated with this element becomes one conductor or a two wire transmission line, one half wavelength long at high band and because of its short length it has negligible effect at low band frequencies.

Further low band improvement is obtained by converting the element to a stepped up two diameter


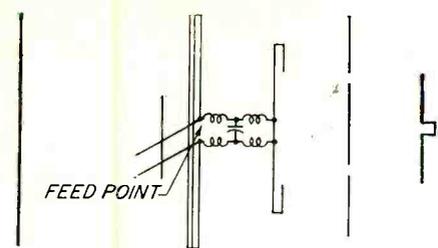


Fig. 1—Schematic drawing of a controlled drive type of antenna showing connecting delay network.

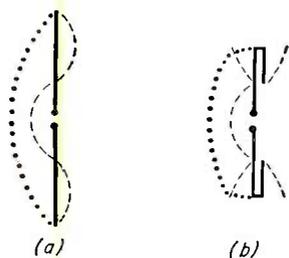

LOW BAND CURRENT
HIGH BAND CURRENT -----

Fig. 3—By folding element (a) one-sixth from ends the resultant antenna is as shown at (b).


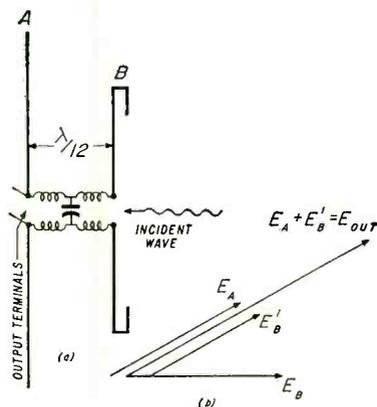


Fig. 5—The basic elements and a vector relationship for low band operation without signal delay.

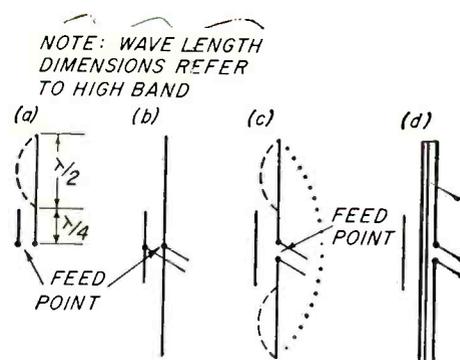

LOW BAND CURRENT
HIGH BAND CURRENT -----

Fig. 2—(a) End fed antenna. (b) Parallel fed. (c) Series fed. (d) Two-diameter dipole antenna.

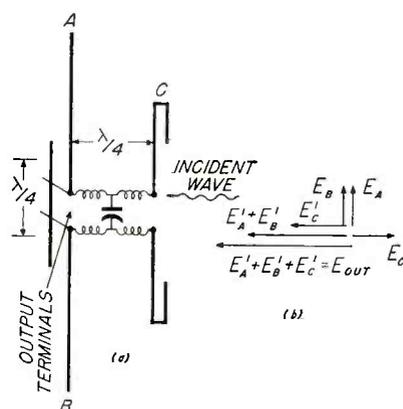


Fig. 4—The frequency selective delay line insures additive in-phase signals at the output.

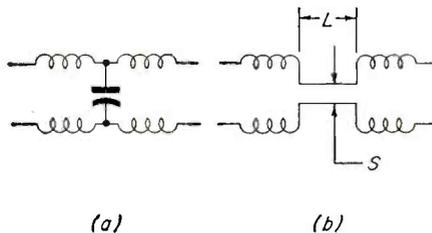


Fig. 6—(a) Delay line schematic. (b) Design considerations are length L , space S , and diameter.

dipole as shown in Fig. 2d. Here the low band impedance is improved greatly without sacrifice in operation on the high band. Furthermore, the resulting element is designed to be extremely effective at the low frequency (long wavelength) end of the low band. The effectiveness on the high band is obtained by having two end fed half wave elements whose signals add in-phase by means of the series connection. By thus improving the impedance characteristic and the resultant single lobe pattern, the two diameter dipole becomes the first major component in the *Topliner* antenna.

Second Driven Element

The second element in this combination may be considered as an end loaded dipole at the low band and a half wave center fed element at the high band. Referring to Fig. 3a, we have an element which is three half wavelengths long at the high band and one half wavelength long at the low band. By folding this element at a point approximately one-sixth from the ends there results the antenna of Fig. 3b. Because of the close coupling between the portion folded back and the original straight portion, the antenna at the low band operates as an end loaded

dipole with current distribution as shown. Its operation over the low band channels is very effective. As indicated in Fig. 3, the high current density at the center has been unaffected and the relatively small current at the ends contributes very little to the gain of the system. The out-of-phase currents at the ends of the element cancel each other resulting in an in-phase current at high band operation.

Thus we have produced a very important part of our new *Topliner* antenna—a combination of driven elements both of which are extremely effective over the entire *vhf* TV spectrum.

The Delay Line

The problem of connecting these elements so that the signals are additive, or "in-phase," over the entire *vhf* band is accomplished by the *delay line* network. This connecting network takes into account the phase shift encountered in the transmission line portion of the element shown in Fig. 2. The solution is the automatically frequency selective delay line, constructed of a combination of lumped and distributed circuit elements. Herein is illustrated the theory behind the operation of the matching network and shows how it insures additive in-phase signals.

Fig. 4a shows the basic elements for high band operation. Fig. 4b shows the vector relationship of the signals as they are induced on the elements and as they are additively combined at the output terminals by means of the delay line. The subscripts associated with the vectors refer to the individual elements upon which the signal is induced. The vectors with the prime (') designation refer to the individual signals as they appear at the output terminals. Referring to the high band operation in Fig. 4, the induced signal E_C leads E_A and E_B signal by 90 degrees, ($1/4$ wavelength), because of the space separation of the elements. E_A and E_B are further retarded in phase by 90 degrees in traveling through the transmission line path to the output terminals. If E_C is to be additive in phase at the output terminals, this signal must be delayed by 90 plus 90 or 180 degrees in traveling over a quarter wavelength transmission line path. The delay line automatically performs this job by giving the 180 degree phase shift over a 90 degree ($1/4$ wavelength) path.

Fig. 5a and 5b show the basic elements and a similar vector relationship for low band operation. For purposes of simplicity, the long element is shown as a simple dipole and the short transmission line element is omitted in this case. The constants of the delay line at low band frequencies are such that it will not act to delay the signals, therefore it will work as an ordinary straight transmission line of 30 electrical degrees, ($1/12$ wavelength), in length. Thus at low band the signals add in phase as in Fig. 5b.

[Continued on page 31]

be noted in many other manufacturers receivers and is generally corrected by either of the above changes.

Mr. Answerman:

I have a vertical problem with a G. E. receiver of the "N" chassis type. The difficulty is that the top of the picture is stretched a small amount. Adjustments of the height and vertical linearity controls will not correct or reduce the excessive stretch sufficiently. The voltages are just about what are called for and as far as I can determine every component is good. But something must be bad or the problem wouldn't exist.

C. O.
San Francisco, Cal.

More than likely the resistors and condensers in the vertical circuit have been measured and examined several times. Therefore, it is logical to suspect some component disassociated from the vertical oscillator circuit and yet connected to it. This component might very possibly be in the vertical blanking circuit as shown in Fig. 2. Quite frequently components fail in this network and cause all sorts of difficulties such as pulls at the top of the picture, bends, shading, etc. For some reason the retrace blanking circuit is often ignored in the servicing process. This case is probably another instance where the retrace elimination circuit has been overlooked. Condenser C175, 470 uuf should be tested for leakage. Only a small amount of leakage is necessary to disturb and distort the generated vertical deflection waveform. This particular 470 uuf condenser has been known to

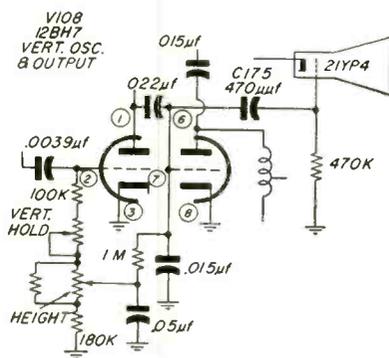


Fig. 2—Vertical output and blanking circuit of G.E. "N" chassis.

THOUSANDS OF SERVICE DEALERS

**SATISFY CUSTOMERS
SAVE REPEAT CALLS**

MAKE MONEY EVERY DAY with B&K



NET **\$109⁹⁵**

Dyna-Quik 500. Easily portable in luggage-style carrying case. Size: 15¼ x 14¼ x 5½ in. Weighs only 12 lbs. Has 7-pin and 9-pin straighteners on panel.

DYNA-QUIK MODEL 500
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Tests over 95%


OF ALL POPULAR TV TUBES*—IN SECONDS
It's easy and profitable to check all the tubes in a TV set with DYNA-QUIK—on every service call. Cuts servicing time. Creates more on-the-spot tube sales. Saves repeat calls, protects service guarantee.

DYNA-QUIK 500 measures true dynamic mutual conductance, completely checks tubes with laboratory accuracy under actual operating conditions right in the home.

Tests each tube for shorts, grid emission, gas content, leakage, dynamic mutual conductance and life expectancy. One switch tests everything. No roll charts. No multiple switching. Makes complete tube test in as little as 12 seconds. Large 4½-inch plastic meter shows tube condition on "Good-Bad" scale or in micromhos on scales calibrated 0-6,000 and 0-18,000. Used in home or shop, DYNA-QUIK is a proved money-maker!

*Including new 600 mil series tubes.

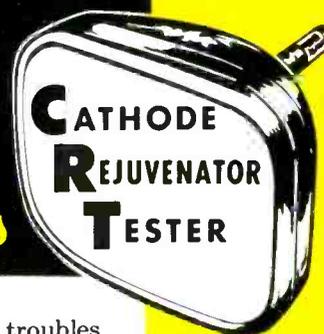DELUXE—PORTABLE
CRT MODEL 400
Tests and repairs
TV Picture Tubes



NET **\$54⁹⁵**

Deluxe CRT 400. With 4½-in. plastic meter. Weighs only 5 lbs. Luggage style carrying case. Size: 11 x 7½ x 5".

Also available in economy model CRT 200 with 3-in. meter at \$39.95 net.

Quickly spots and corrects picture tube troubles right in the home, without removing tube from set. Restores emission, stops leakage, repairs interelement shorts and open circuits. Life test checks gas content and predicts remaining useful life. Grid cut-off reading indicates picture quality customer can expect. Eliminates tube transportation, cuts service-operating costs. Also saves money on TV set trade-in reconditioning. Earns dollars in minutes—pays for itself over and over again.

Proved In Use by Servicemen Everywhere.

See your B & K Distributor or send for facts on "Profitable TV Servicing in the Home" and informative Bulletins 500-104-D.

B&K

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



get more useable power

Each of the four TOPLINER models has the Power Pack, an exclusive feature that delivers more of the signal at the receiver—where you need it, and . . . precision manufacture saves assembly and installation time. . . . dry cleaning eliminates apologies for your appearance. . . . streamlining gives the customer a better looking installation. Dollar-for-dollar, a TOPLINER gives the customer more performance, greater picture clarity for only TOPLINERS have



Ask For
Your Copy
of the Folder

"Tomorrow's
Antenna Today"

exclusive built in



TACO Distributors
Have Full Information
on The Topliner Antennas

TECHNICAL APPLIANCE CORPORATION, SHERBURNE, N. Y.
IN CANADA: Hackbusch Electronics, Ltd., Toronto 4, Ont.

develop leakage and produce the symptoms noted here by affecting the grid bias on the vertical output tube. As a result the output waveform becomes distorted. Condenser C175 should have a 1000 volt rating.

Dear Answerman:

I have an intermittent condition that has proved quite difficult to correct. After the receiver has been operated for a period of time the horizontal phase of the picture will slip so that the horizontal blanking bar is exhibited. Also, on occasion, the horizontal oscillator frequency may change so that the horizontal oscillator is out of sync.

Since the trouble is so infrequent, (although when the receiver has warmed up it occurs every minute or so), I have been having a difficult time trying to locate the intermittently defective part. One point of interest is that it takes about half an hour or more for the condition to appear. Once the receiver has been operated for that period of time the improper action continues for the balance of the period of use. When the horizontal oscillator slips out of phase the horizontal hold control does not seem to have too much effect upon the circuit.

What component would be most likely to cause this trouble? The receiver is a Crosley 477 chassis.

J. S.

Washington, D. C.

From the description of the symptoms, that of slipping out of horizontal phase intermittently, it appears that the automatic frequency control circuit is not holding or operating at these times.

As can be seen in Fig. 3 a portion of the circuit consists of a special winding on the horizontal output transformer circuit. A pulse is supplied from the winding to the horizontal *afc* stage for phase comparison action with the horizontal sync pulse. This winding on the flyback transformer is one of the first points to test and is accomplished by measuring the resistance between terminals 4 and 5 on the transformer. The resistance should be about 3.6 ohms. The check should be made after the receiver is thoroughly warmed up and is performed to determine whether the winding is open or the ground connec-



molded tubular capacitors

The C-D "Cub" capacitor has proven itself the best on the market today—by out-lasting, out-performing, out-selling any other replacement capacitor for radio or TV. For consistent high quality—always rely on C-D, the only tubulars with the built-in extras required in servicing sets today. That's why distributors *who know*, carry the complete C-D line.

Special! "Cub-Kit" with bonus plastic service dispenser. IT'S FREE!

Ask your C-D Distributor. He's listed in your local Classified Telephone Directory.

CONSISTENTLY
CORNELL-
DEPENDABLE
DUBILIER



THERE ARE MORE C-D
CAPACITORS IN USE TODAY
THAN ANY OTHER MAKE.

PLANTS IN SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND
CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS,
IND.; SANFORD AND FOUQUAY SPRINGS, N. C.; SUBSIDIARY, RADIART
CORP., CLEVELAND, OHIO.

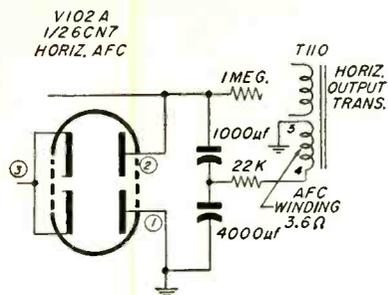


Fig. 3—Partial schematic showing Crosley 477 chassis afc circuit.

tion is intermittently open. Either condition will bring about the difficulty noted. The connections should be checked for broken leads, rosin joints, etc. More than likely the intermittently open condition is produced by the heating of the flyback transformer. The expansion of the windings during warm-up frequently results in the intermittent nature of the trouble. Since the trouble is intermittent it is possible that the resistance measurement test will prove that the winding is not open at that time. An additional means of determining whether the winding is opening is to connect a scope or a peak-to-peak reading VTVM at the flyback terminal #4. If, when the receiver slips horizontally in phase, the waveform or the VTVM reading decreases it is an indication that the winding is opening intermittently.

However, in troubleshooting this circuit with an oscilloscope it is quite possible to make an error that will considerably delay the correction of the trouble. If the winding should be open and the scope probe is brought near the transformer sufficient pulse voltage is induced into the scope probe circuit to cause a waveform to be seen, although it will not be of the correct amplitude. Even with the *afc* winding open a signal of 2.5 volts peak-to-peak or more will be found at the phase comparer circuit whereas its normal value is 15 volts peak-to-peak. Frequently, this is misleading and causes the technician to believe that the winding is good when it is open.


A final point with reference to poor horizontal lock-in action in this type of *afc* circuit is that there have been several instances where in the process of replacing a flyback transformer the ground connection has been unintentionally omitted. This produces very loose horizontal hold action with the picture slipping horizontally back and forth. ■■

a look at the latest in AUTO RADIO

Here are some typical CBS tubes and transistors you will be discovering in 1957 "hybrid" auto radios. They combine the advantages of new CBS power output transistors and modern CBS low-voltage mobile radio tubes. All power for them is drawn directly from the 12-volt battery; the vibrator power pack is eliminated. Both the tubes and transistors are especially designed for hybrid auto radio.

As the 1957 automobiles come into use this fall, you will find CBS ready to supply you with these new tubes and transistors. That's only natural. CBS pioneered the first auto radio tube kit. CBS has specialized for years in supplying auto radio tubes to leading set manufacturers. And now CBS advanced-engineering pioneers again with new hybrid auto radio components.

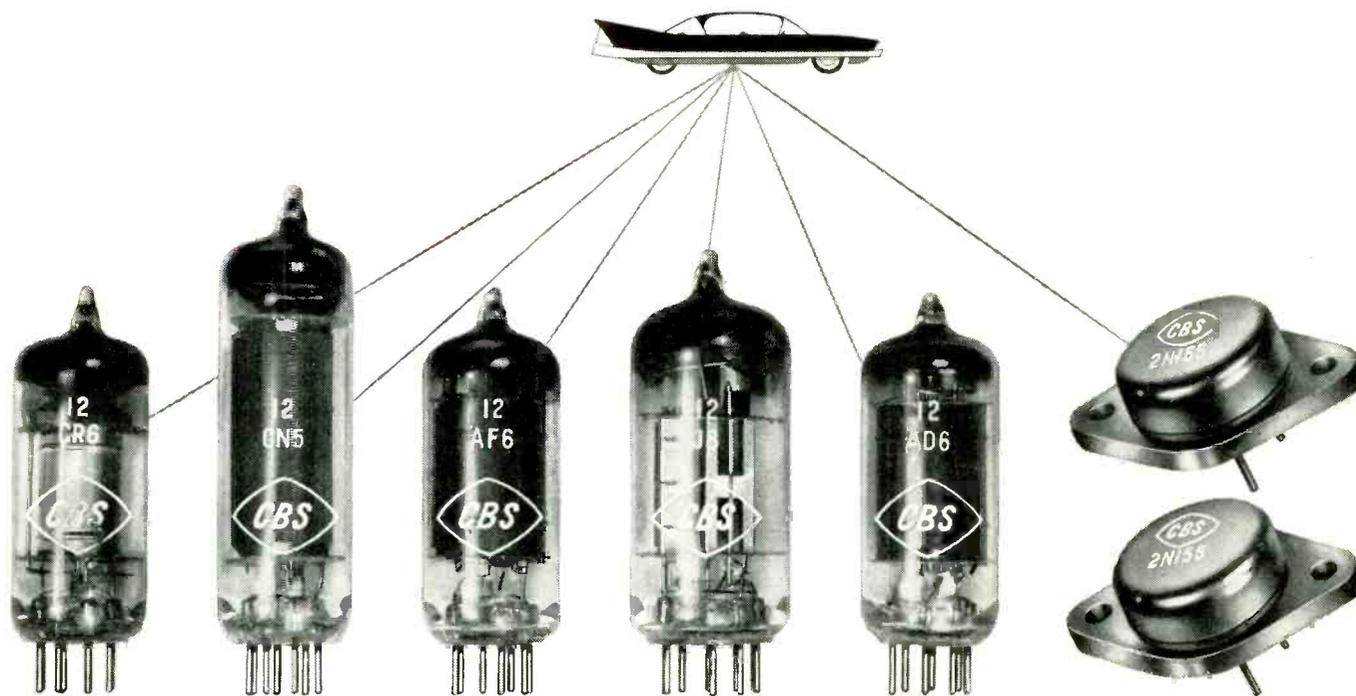Whether it's tubes or transistors — whatever you need for auto radio — old, modern, or ultramodern . . . make it CBS. Replace with the same tubes and transistors the original equipment designer specifies . . . CBS.



tubes semiconductors

Reliable products
through Advanced-Engineering

CBS-HYTRON

Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

A coupling device to connect coaxial transmission lines is presented which permits quick solderless connections without disturbing the physical or electrical characteristics of the coaxial transmission line.

TAPPING TV TRANSMISSION LINES

by IRA KAMEN

Vice President Brach Division, General Bronze Corporation

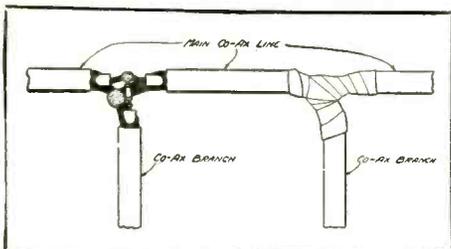


Fig. 1—Original method of tapping transmission lines.

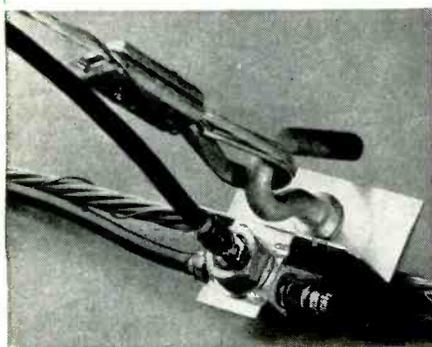


Fig. 2—Jerrold community system cable tapping device.

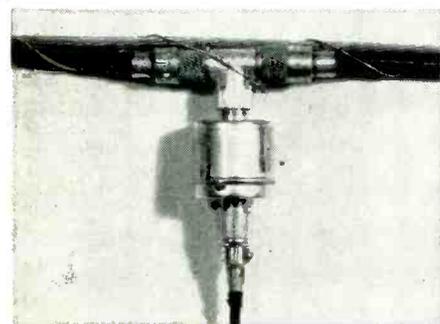


Fig. 3—Lynmar transmission line tapping device.

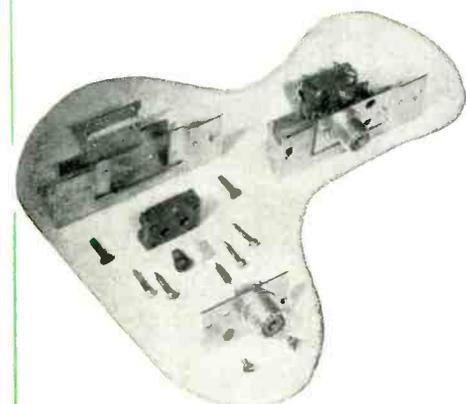


Fig. 4—Solderless coupled exploded and assembled views.

THE success of TV master antenna installations and community system installations has been based upon the proper technique of tapping TV coaxial transmission lines.

In all TV master antenna system installations where a coaxial cable transmission line must be tapped at various places along the line, to transfer the TV signals to TV receivers, the tapping must be done in such a way as not to produce a change in the concentric nature of the inner and outer conductor of the coaxial cable. If the impedance of the coaxial cable is materially changed, standing waves along the line will be developed. These standing waves dissipate the TV signal energy being transmitted along the line. The amount of energy lost depends upon the impedance changes produced by the number and nature of the taps along the line. This is especially true where the taps distort the symmetrical continuity of the conductors. In some cases, the standing waves will cause a duplicate picture on the TV screen, marring the quality of reception.

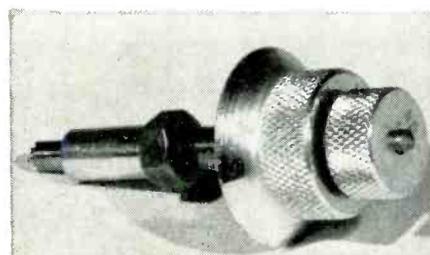


Fig. 5—RCA's tool for severing hole in coaxial transmission line.

Early Method of Tapping

When TV master antenna systems were first introduced to the market in 1948, the lines were tapped in the manner shown in *Fig. 1*, in which every effort was made to tap the transmission line with isolation resistors by a method which would distort the coaxial line to the minimum extent. This technique (*Fig. 1*) required soldering the transmission line and outlet devices and installing a resistor in an outlet box of some kind. However, this rough type of soldered connection tap-off introduced serious standing waves which produced serious signal loss on the high frequency band from channels 7 to 13. Further, with the soldered type of connection,

the coaxial lines were always in danger, for when the soldering was completed, it was necessary in rather compact quarters to make sure that the exposed inner and outer conductors of the main line and branch lines did not short circuit each other. One manner of accomplishing this was to fill the space between the conductors with a suitable insulating compound which hardened and the other was to wrap an insulating tape between and around the various conductors as shown in *Fig. 1*.

Experience has shown that when joints are made in the manner described above that they are subject to aging, resulting in a large measure from the moisture entering the transmission line at the junction points. The aging and corrosion which were produced by this solder technique developed signal losses which, in many cases, could only be

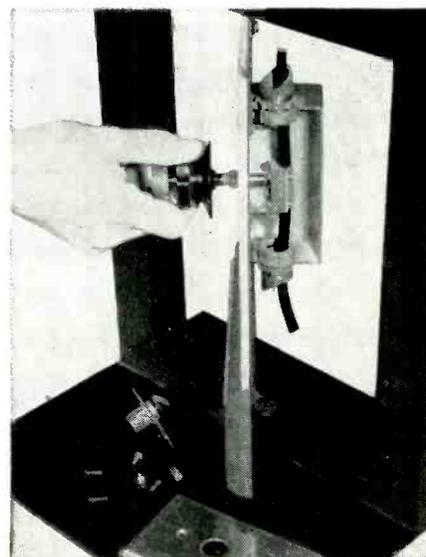


Fig. 6—Typical hole cutting procedure in tapping coaxial line.

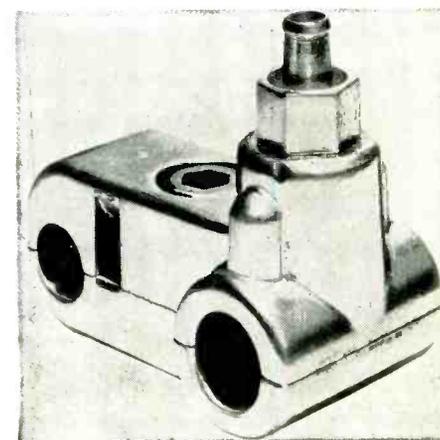


Fig. 7—Entron solderless connector for community coaxial systems.

remedied by removing the completely installed cable only a few years after its installation.

Tubular "T" Couplings

Certain manufacturers, like Jerrod and Lynmar, overcome some of the difficulties described by using tubular metallic T couplings, as shown in Figs. 2 and 3. These devices require the cable to be cut, each conductor skinned and, in some cases, carefully soldered to its respective point on the connector. With careful soldering these two unions will produce good performance in a system installation.

Solderless Couplers

One of the new trends toward solving the TV transmission line tapping problem is a device developed by the author under patent No. 2,615,948 for the Commercial Radio Sound Corporation, who have assigned it exclusively to the Radio Corporation of America. This coupler device is shown in Fig. 4 in both exploded and assembled views. It is known in the field as a solderless coupler since it has been designed for installation without the use of solder. Laboratory tests indicated that these couplers could be installed without disturbing the physical or electrical characteristics of the coaxial line. Installation of this coupler along the transmission line requires the use of only the simple tool shown in Fig. 5. This tool is used to bore a small hole through the outer conductor of the coaxial cable, as shown in Fig. 6, so that the center conductor

[continued on page 36]

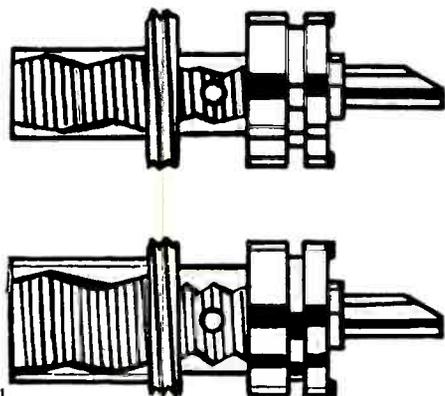


Fig. 8—Blonder-Tongue solderless cable connectors.

HANDY!

CLAROSTAT RESISTOR ASSORTMENTS...

Have the **right** resistor — **right** when you need it!

Clarostat Resistor Assortments are mounted on heavy display cards, for your convenience. In addition, the exact resistance value of each resistor is printed right on the card, and seen when the resistor is removed. Thus you always know what to reorder to keep your stock complete. A choice of assortments in most-called-for ohmage:

- GK-1** 20 ten-watt wire-wound resistors
- GK-2** 32 two-watt wire-wound flexible resistors
- GK-3** 36 five-watt wire-wound axial-lead resistors
- GK-4** 54 five-watt wire-wound resistors
- GK-5** 50 ten-watt wire-wound axial-lead resistors
- GK-6** 45 ten-watt wire-wound resistors
- GL-1, GL-2** 12 fuse-type resistors of 7.5 ohms and 5.6 ohms

CLAROSTAT

CHOOSE THE CARDS TO FILL YOUR NEEDS!

AVAILABLE AT YOUR FAVORITE CLAROSTAT DISTRIBUTOR

CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE

YOUR BEST BUY

in a UHF Converter



**B-T
LABS** Model '99'

**OFFERS TOP
PERFORMANCE
AT LOW COST**

only **\$19⁹⁵** LIST

- Tuned Input—
tracks with oscillator
- Precise Impedance Match
- One-Knob Tuning
- Drift-Free Performance

Check with your supplier
today. Also ask about
the Deluxe Ultraverter
... or write Dept. XK-7.

BLONDER-TONGUE LABORATORIES, INC.
Westfield, New Jersey

ASSOCIATION NEWS

[from page 4]

The meeting was closed with a banquet at which Friends awards were presented to several tube and component manufacturers. Dan Creato of RCA Service Co., received a personal citation for the part he has played in handling industry problems.

ESCO, Missouri

Very recently the Electronic Service Council of the Ozarks (ESCO) consisting of three associations in south Missouri, TESA of southwest Missouri, TESA of the Ozarks and the TESA South Central Mo., culminated an idea into a tangible product. The Raster will be published each month by ESCO and sent to all electronic technicians in south Missouri.

ESFETA, New York

ESFETA held their regular business meeting in the Hotel Wellington in the State Capital at Albany, New York. They had as their guests Edward M. Boor representing Doctor Persia Campbell consumer council of the governor of the State of New York. Mr. Boor spoke on the progress of the consumer council as related to the television service industry and of the investigations that have gone on in many cities of the state. He displayed several pieces of literature that the council has already published for distribution to the general public.

Publicity for ESFETA was discussed and Dan Hurley appointed as publicity and liaison chairman. Dan offered to visit all of the associations of the State (if, when, and where they meet) to offer them any assistance in the name of ESFETA. Associations wishing assistance of any sort should write to Dan Hurley, 10 Florida Rd., Syracuse 11, New York.

Movement of the manufacturer into the retail television service field was discussed with enthusiasm. Great alarm was expressed by all segments.

Syracuse Television Technicians Association, Inc.

It has come to the attention of this association of professional television technicians, who earn their livelihood at television servicing and operate from designated business zones and collect city sales taxes at the retail level, that many individuals are operating a business in a residential zone and not collecting the sales tax as required by law.

This is made apparent by the fact that more and more of our members are having difficulty collecting city sales tax from the customer who claims that other service men do not charge for this tax. We have investigated this situation and find that there are many so-called TV service men who hold jobs in factories and operate businesses from their of Syracuse to lose tax revenue from of bookkeeping or record of sales tax collections. These same men flagrantly advertise in newspapers and telephone directories.

We feel that it is unfair for the city of Syracuse to lose tax revenue from these sources while our customers have to pay this tax. We further feel that it is the duty of the tax commission to either collect these taxes or to exempt our customers from having to pay this tax.

TESA-St. Louis, Mo.

In all future phone books the telephone company has promised a committee set up by TESA to stop price advertising. This committee met with officials of the phone company at the Kingsway Hotel, to discuss price advertising in the Yellow Pages of the Telephone Directory. They have also promised a number of other things to help upgrade television service, such as: no company can advertise they are a member of a TV Service Association, unless the name of the Association is placed in the ad. Phone answering service address will not be allowed. Superlatives, such as largest in Mo., etc., will be discontinued. ■■

The Finest
.....
UHF
Converter
Ever
.....
Designed



**B-T
LABS**

Ultraverter


**OUTPERFORMS
ALL OTHERS
IN THE FIELD**

\$39⁹⁵ LIST

- ✓ Precise Impedance Match
- ✓ Higher Gain
- ✓ Lower Noise Factor
- ✓ Automatic 'on/off'
- ✓ Dual Speed Tuning

Check with your supplier today.
Also ask about the Model '99'
at \$19.95 Dept. WK-7

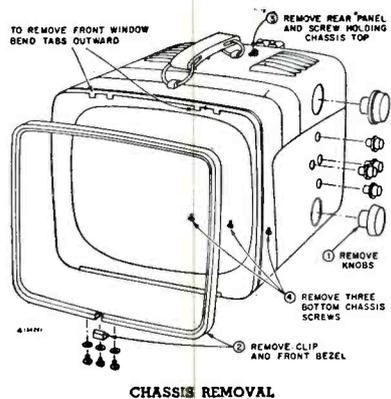BLONDER-TONGUE LABORATORIES, INC.
Westfield, New Jersey




CHASSIS REMOVAL

ANTENNA INPUT
Models 14-S-7052, 14-S-7070, 14-S-7071 and 14-S-7074
The KRK32F tuner unit is designed for VHF reception only, with a 300 ohm antenna input provided.


Model 14-S-7052U
The KRK29W tuner unit is designed for UHF-VHF reception with 300 ohm input provided for UHF and VHF use. When using a UHF antenna or a VHF antenna (or both) connect the transmission line from each antenna to the proper receiver antenna terminals.

Models 14-S-7070U, 14-S-7071U and 14-S-7074U
In these models the antenna input to the UHF and VHF tuner is connected to a crossover network to provide a single antenna input to the receiver. This provides for antenna input from a single VHF antenna, a UHF antenna, a combination UHF/VHF antenna, or the receiver cabinet antenna.

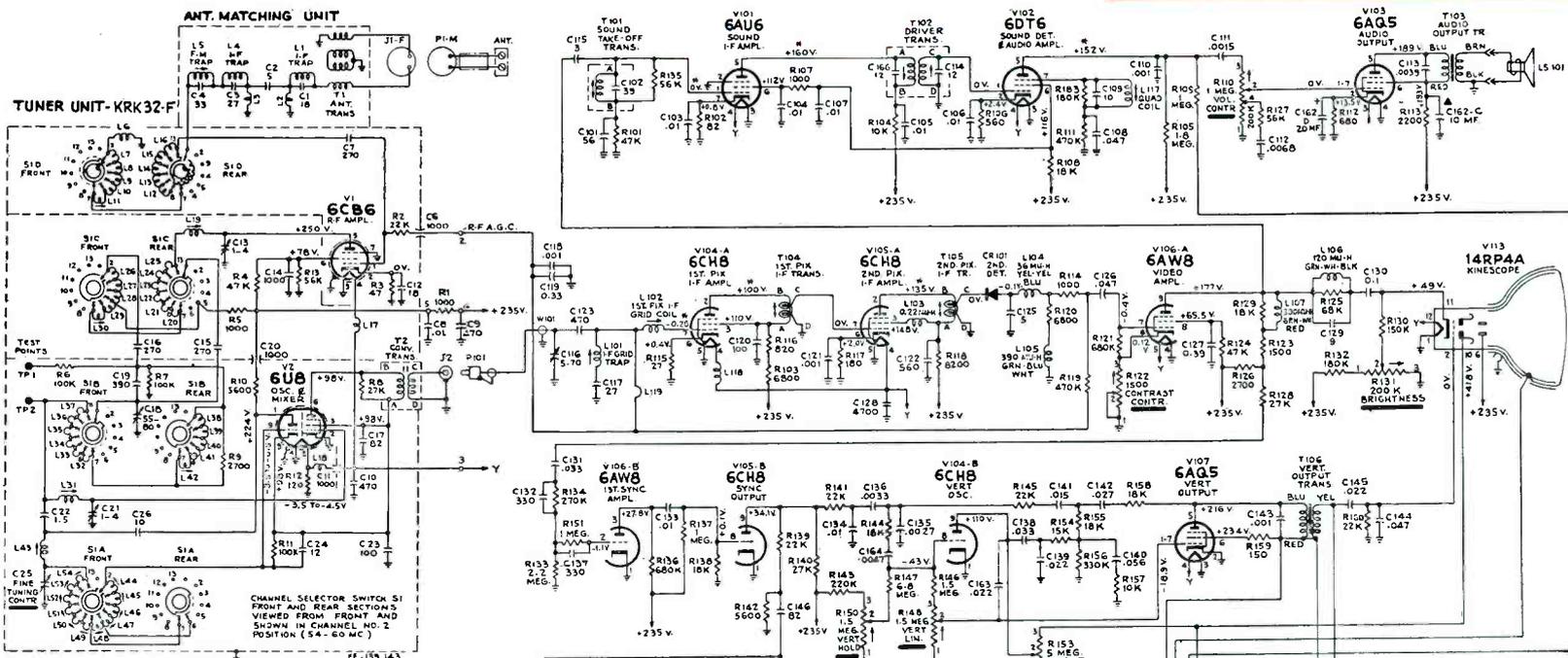
The attached cabinet antenna is automatically connected to the tuner inputs when the bottom rod sections are fully extended. When the cabinet antenna is being used disconnect the external antenna. When using the external antenna retract the rod antenna fully.



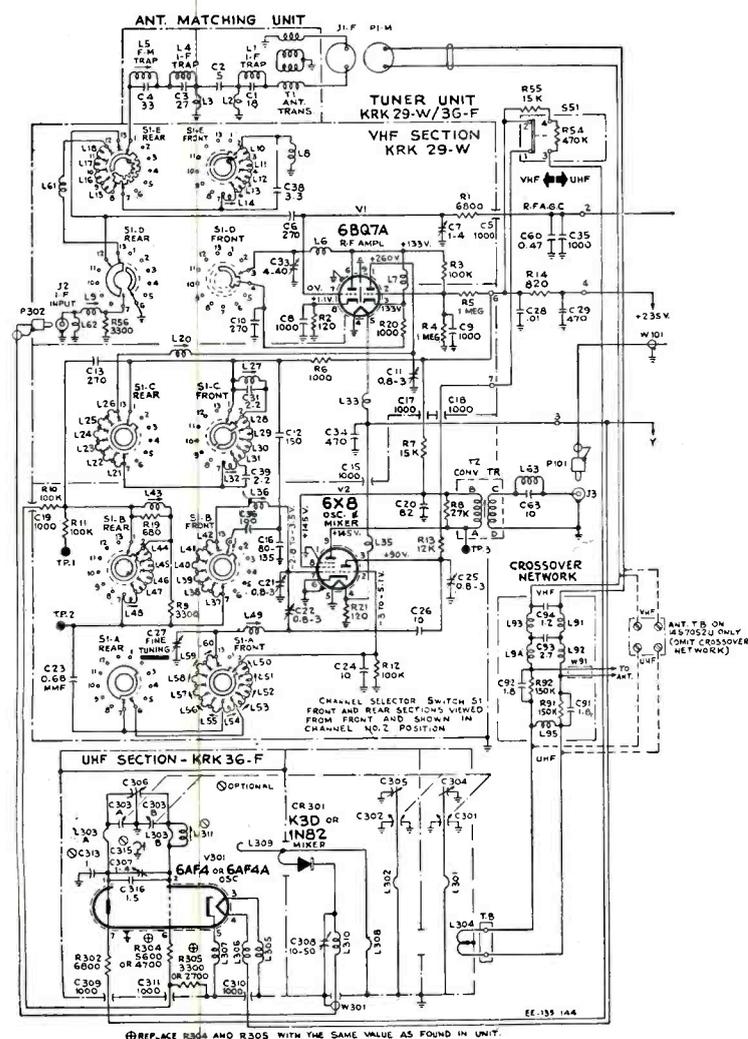*Measured with 1 megohm 1/2 watt resistor in series with meter probe.



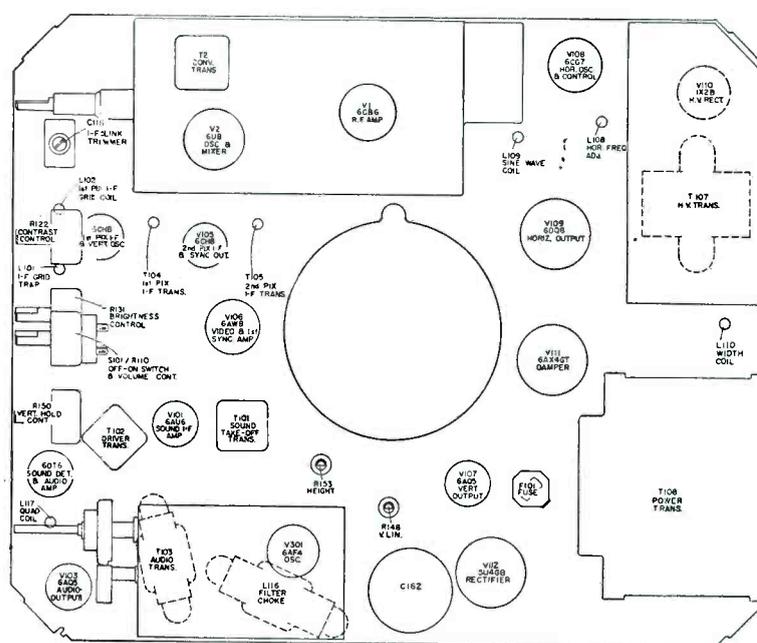Ⓢ REPLACE R504 AND R505 WITH THE SAME VALUE AS FOUND IN UNIT.



CHASSIS REAR VIEW

INSTALLATION CHECK LIST

Connect the antenna transmission line to the receiver antenna terminals.

Plug the power cord into the 117V. AC outlet and turn the receiver "ON". The receiver should operate normally. However, a check of the following adjustments should be made.

1. Check position of ion trap magnet and readjust for maximum raster brightness, if necessary.
2. Check raster for proper framing (fill) in mask. Adjust yoke position by rotating.
3. Check width and horizontal linearity, readjust width control as outlined below, if adjustment is necessary.
4. Check for normal operation of horizontal hold control. Should hold sync for two full turns or more of the control.
5. Check centering of picture. Adjustment is made with the centering lever on the focus magnet.
6. Check height and vertical linearity, reset controls where required for 1/4" overscan.
7. Check R-F oscillator adjustment on all channels. Readjust if necessary, starting at the highest frequency channel, proceeding to the lowest.

***Width and Sinewave Adjustments**

It is possible to adjust the horizontal oscillator in the field by the following method when such adjustment is indicated.

- A. Set the width coil fully counter-clockwise.
- B. Adjust width for 3/4" overscan at each side, with normal line voltage and normal brightness.
- C. Turn horizontal hold control to the left, out of sync, to the point where interrupted oscillation occurs.
- D. Adjust sinewave core, as the horizontal hold control is rotated to the left beyond the locked-in position, until 3 to 4 bars occur between the fall out point and interrupted oscillation.

RCA TV PORTABLE
Ch. KCS102B, D

Models: 14-S-7052, -7070, -7071, -7074
14-S-7052U, -7070U, -7071U, -7074U

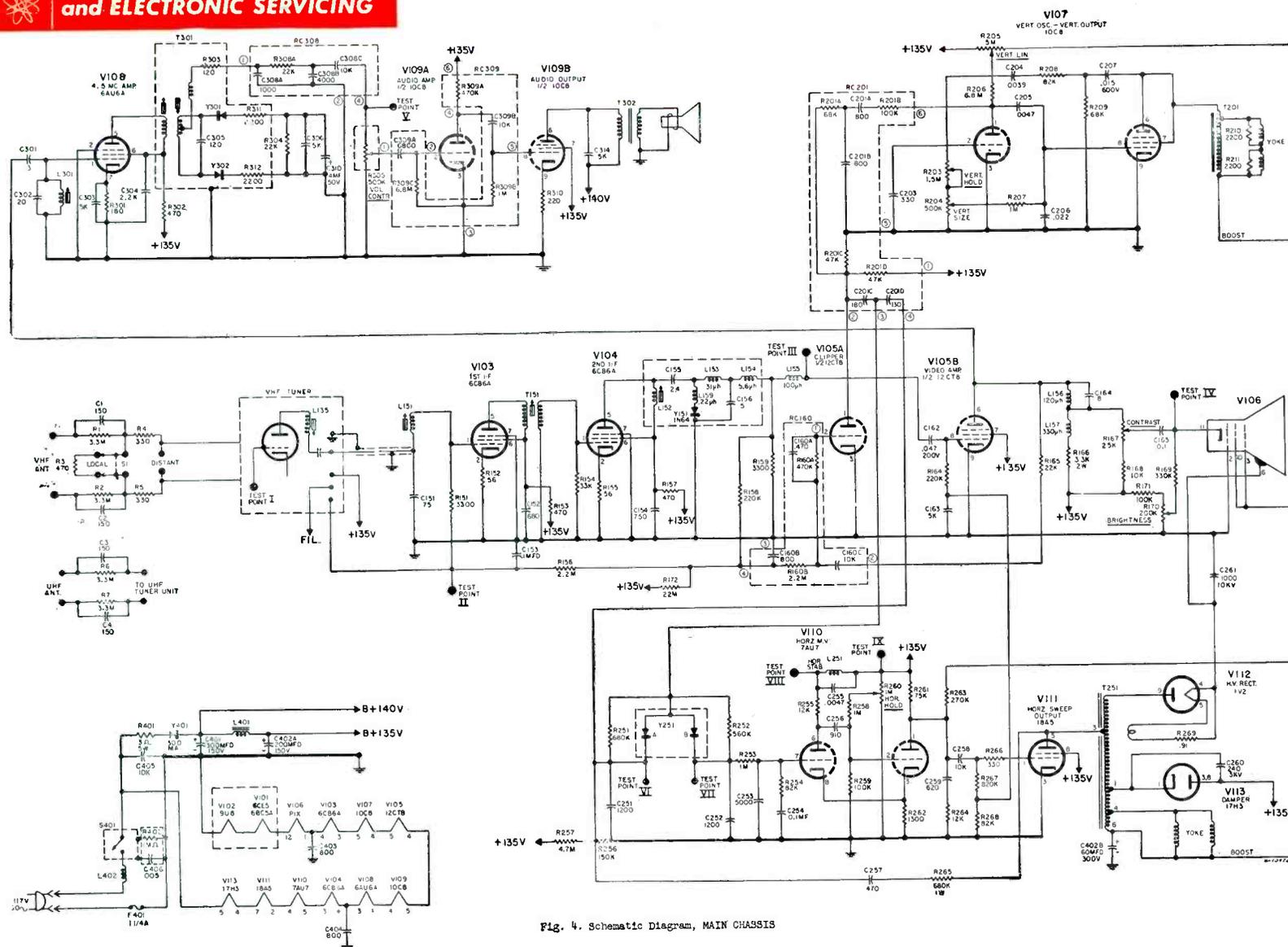


Fig. 4. Schematic Diagram, MAIN CHASSIS

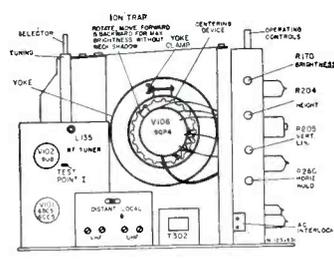
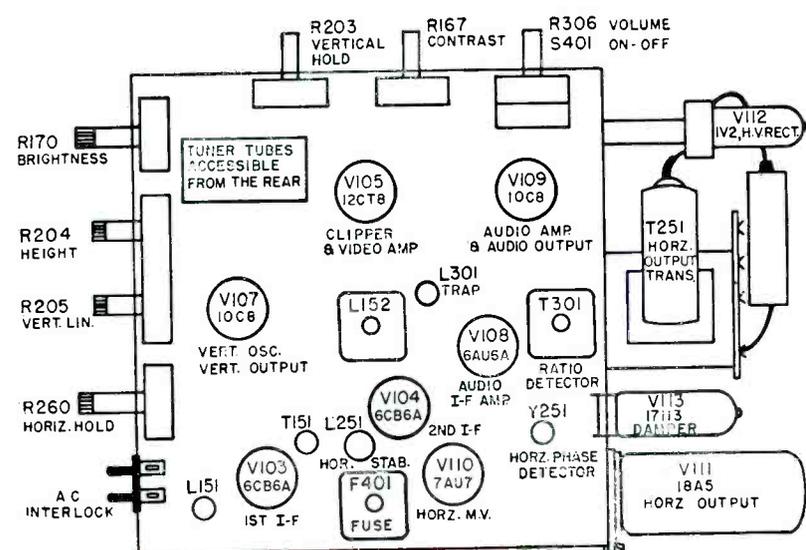


Fig. 1. Rear View of Chassis Cabinet Removed

- To Remove The Chassis From The Cabinet -In order to service the tubes or component;
1. Disconnect the line cord from the power outlet. Remove any antenna connected to the antenna terminals.
 2. Remove all knobs from the control shafts.
 3. Remove the 6 screws located on the bottom of the cabinet at the sides (3 each) and rear (2 only).

The cabinet is then removed by sliding back off the cabinet front and bottom board assembly. This leaves all components exposed with the picture tube remaining mounted to the cabinet front and bottom board assembly

Install the cabinet to the chassis in the reverse order as the disassembly.

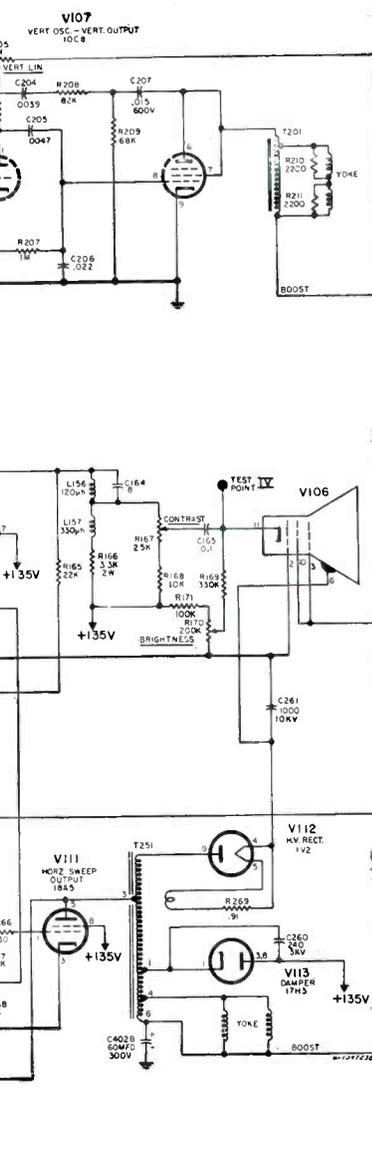


Fig. 2. Schematic Diagram VHF TUNER RX-1004

INSTALLATION ADJUSTMENTS

General -The receivers are shipped complete with the picture tube mounted and all controls pre-adjusted. After powering the receiver check the controls, as outlined in the operating manual, for proper operation.

The local-distant switch is normally left in the distant position except where overload, caused by exceptionally strong signals; or cross modulation, caused by one or more strong signals interfering with the desired signal; causes the picture to tear, roll or be distorted.

ELECTRICAL INSTALLATION

It is recommended that the receiver be permitted a 15 minute warm up period before final raster adjustments are made. A preliminary check of the ion trap should be made so as not to damage the picture tube.

Height and Vertical Linearity -These controls, R204 and R205 should be adjusted simultaneously to give proper vertical size consistent with good vertical linearity. Final adjustment should be made to allow the picture to extend approximately 1/8 inch beyond the edges of the mask.

PICTURE TUBE ADJUSTMENTS

Yoke Position -Loosen the yoke clamp wing nut. Set the yoke firmly against the bell of the picture tube and rotate the assembly to correct for any tilt of the picture, squaring the picture within the mask. Tighten the wing nut after adjustment is made.




Picture Centering - The picture tube centering device is located on the neck of the tube mounted directly on the rear of the yoke. Rotate the rings with finger tips towards and away from each other to center the picture on the face.

Focus -Focus of the picture in this set is fixed and therefore no adjustment is available. Focus should be checked when making adjustment of the ion trap and best focus consistent with maximum brightness and without neck shadow.

Ion Trap -Power should not be applied to the receiver for extended periods of time without proper adjustment of the ion trap. Rotate and slide the ion trap on the neck of the picture tube to obtain maximum picture brightness without neck shadow and consistent with good focus. Brightness should be kept moderate during the ion trap adjustment.

HORIZONTAL STABILIZER ADJUSTMENT

1. Tune receiver to a weak signal and adjust controls for normal operation.
2. Short test point VI to VII.
3. Shunt L251 (horizontal stabilizer coil) with 1000 ohms. (connect resistor between test points VIII and IX.)
4. Adjust horizontal hold potentiometer R260 so that the picture "floats" back and forth across the screen. Leave R260 set like this.
5. Remove 1000 ohm shunt across L251, and adjust L251 so that picture again "floats" back and forth across the screen. Leave L251 set like this.
6. Remove connection from test point VI and VII.

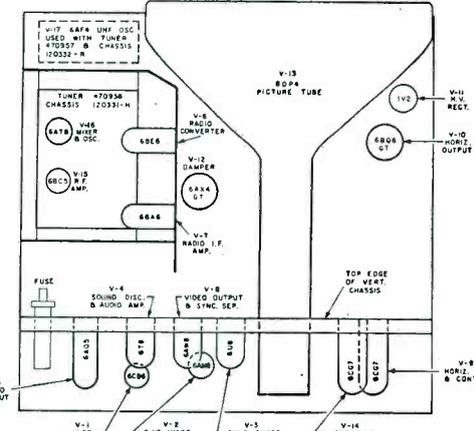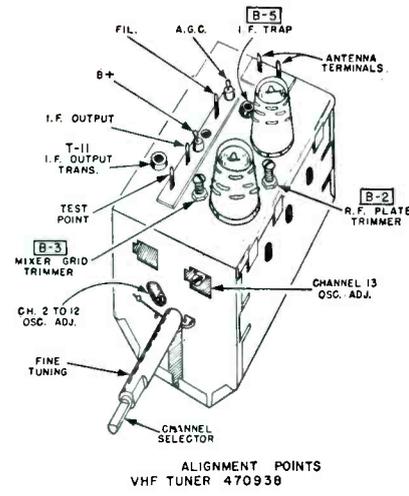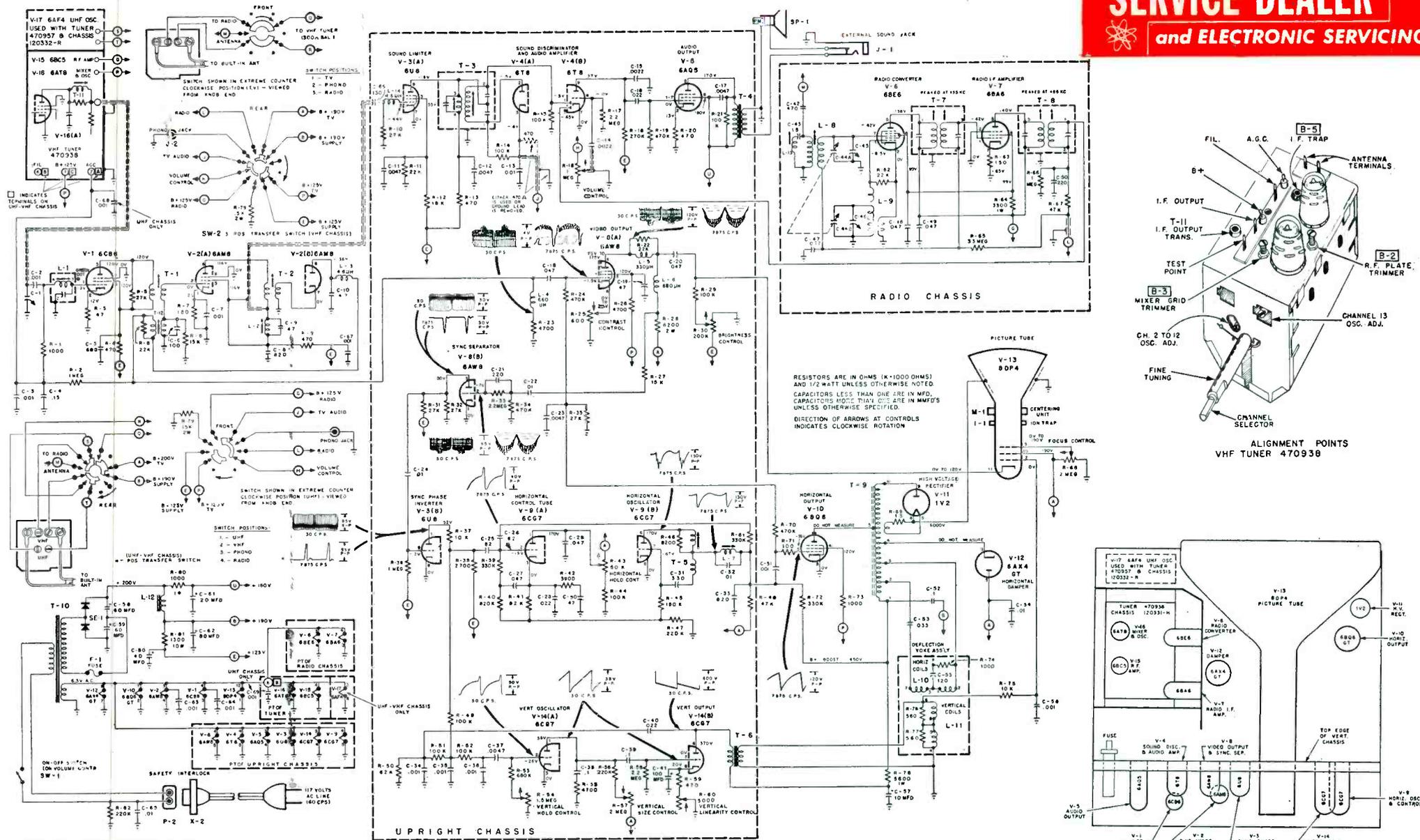

CHASSIS 120331-H & 120332-R

FIELD ALIGNMENT OF PART NO. 470938 TUNER USED IN CHASSIS 120331-H

Ordinarily the only adjustments required in the field are those necessary to compensate for variations in oscillator tube replacements. This can usually be accomplished with the channel No. 13 oscillator adjustment. If individual channel adjustments are necessary, then proceed as follows: (Since this tuner is of the incremental inductance type, all oscillator adjustments should be made commencing with the highest channel and then proceeding to the lower channels.)

1. Set channel selector to channel No. 13. Set fine tuning control to electrical center of its range.
2. Adjust channel No. 13 oscillator adjustment, (See Figure No. 1) for best picture and sound. Use a non-metallic screwdriver.
3. Channels No. 2, No. 4 and No. 6 have slug adjustments and should always be adjusted starting with the higher channel. (See Figure No. 1). It is recommended that channels No. 13, No. 6, No. 4 and No. 2 slugs, only, be adjusted in the field in that order when necessary.
4. Channels No. 12 through No. 7 can be adjusted if required by bending the hair pin inductances through the hole provided (See Figure No. 1).
5. Channels No. 3 and No. 5 (split coil windings) should not have to be compressed or separated ordinarily.

ALIGNMENT OF MIRACLE PICTURE LOCK (Horizontal Oscillator and A.F.C.)

1. Short phasing coil (L-7) by means of a jumper wire.
2. Rotate horizontal hold control (R-43) fully clockwise.
3. Starting with horizontal frequency slug (T-5) all the way "in" looking at rear of chassis, rotate "out" until picture just locks into sync (adjust "out" additional 1/4 turn).
4. Remove short from phase coil and starting with slug all the way "in" adjust "out" until picture almost locks into sync (2-3 diagonal bars).
5. Check for horizontal hold while switching channels. If this is not obtained at extreme clockwise position of horizontal hold control (R-43) turn frequency slug (T-5) "out" slightly until desired results are obtained. If excessive squedging (Christmas Tree effect) is experienced while switching channels, repeat steps No. 1 through No. 5.

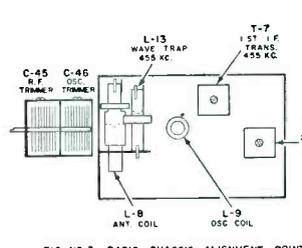


FIG. NO. 3 RADIO CHASSIS ALIGNMENT POINTS

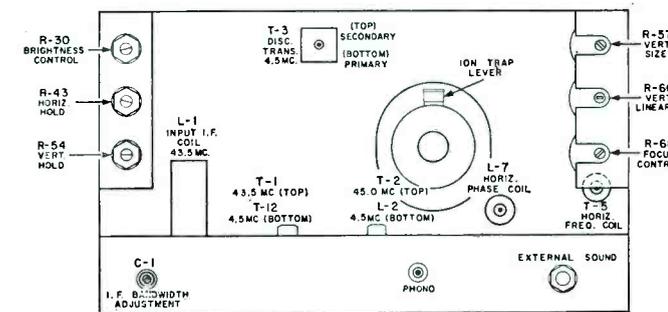


FIG. NO. 4 T.V. CHASSIS ALIGNMENT POINTS

120331-H
RESISTANCE READINGS FOR CHASSIS 120332-R


| SYMBOL | TUBE PIN NUMBERS | | | | | | | | |
|--------|------------------|-------|-------|-------|-------|-------|-------|-------|-------|
| | PIN 1 | PIN 2 | PIN 3 | PIN 4 | PIN 5 | PIN 6 | PIN 7 | PIN 8 | PIN 9 |
| V-1 | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M |
| V-2 | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M | 1.0M |
| V-3 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-4 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-5 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-6 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-7 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-8 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-9 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-10 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-11 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-12 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |
| V-13 | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K | 20K |

EMERSON TV PORTABLE

Ch. 120331-H
120332-R

Models: 1232, 1233

TUNER 94E119-1

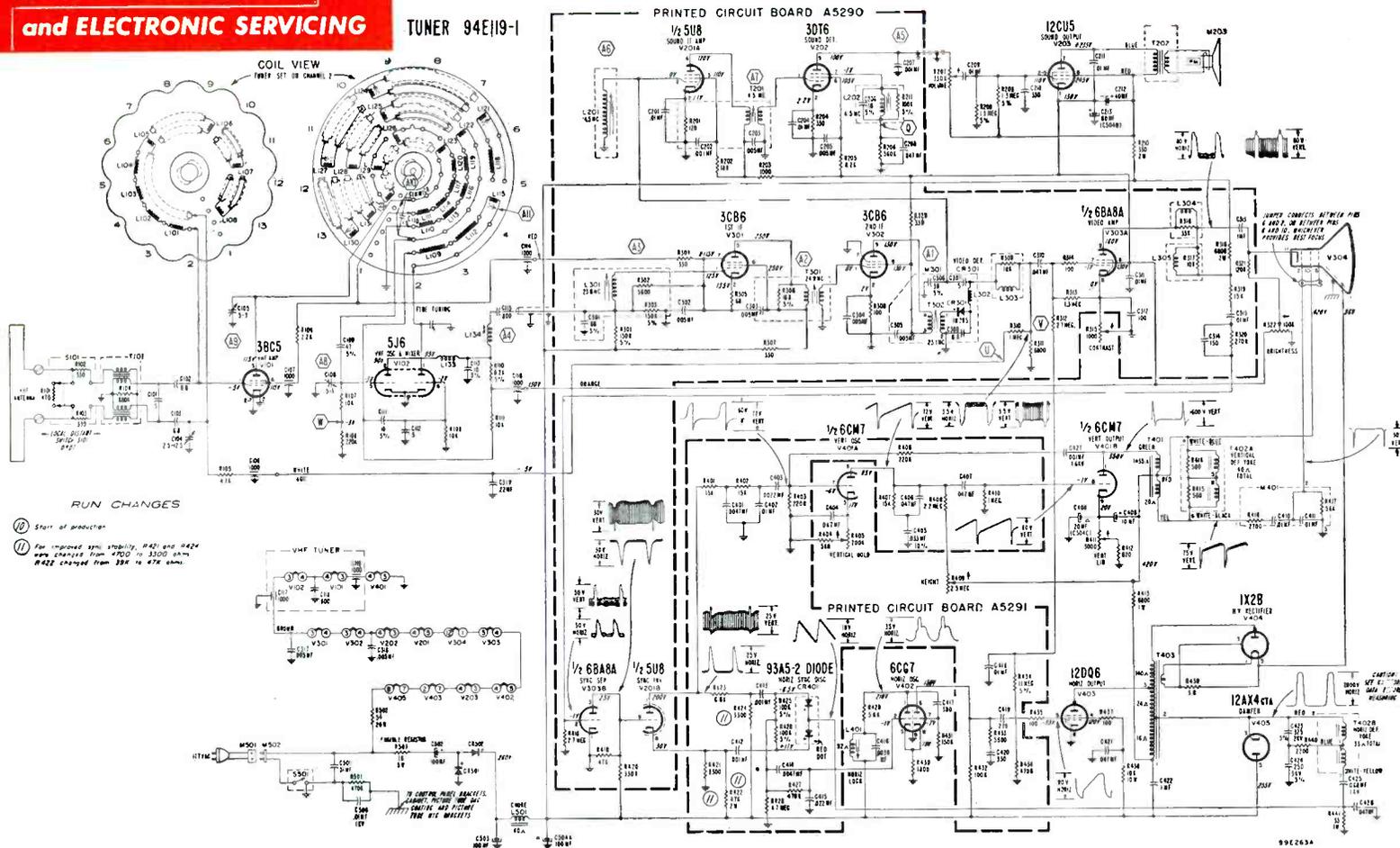

SERVICING TUBES

IMPORTANT: To prevent possibility of electric shock, do not remove or install tubes unless the set is disconnected from the power line.

Tubes in this receiver, with exception of VHF tuner, can be serviced by simply removing the cabinet back and tilting the printed circuit board. To tilt printed circuit board, remove screws mounting it to the chassis. A tube puller may be used for removing the high voltage rectifier tube (1X2B) located in the high voltage compartment.

The picture tube is accessible for replacement by removing the cabinet front, cabinet back and tilting the printed circuit board. To replace tubes in the VHF tuner, remove chassis from cabinet as instructed under "Removing Cabinet Back & Front".

LOCATING A BURNED OUT TUBE



The heaters of tubes (except V404 high voltage rectifier) are connected in a series circuit. If tubes do not light, check the interlock line cord to see that it is making good contact. Check to see that all tubes are firmly seated in sockets.

A total of 13 tubes are used in the heater circuit. The tube location diagram on the schematic page contains a simplified circuit diagram of tube heater connections. Through the use of this diagram and instructions given below, an "open" burned out tube in the heater circuit can be quickly located without the need for substituting or testing of all tubes.


A simplified procedure is given in the figure below for quickly locating an open heater tube. Checks are made with an ohmmeter from the tube socket pin to chassis ground with a tube removed. **IMPORTANT:** The picture tube mounting brackets, rear control bracket and tuner shaft are insulated from the chassis.

NOTE: Tube socket pins are counted in a counterclockwise direction when viewed from the tube side of the socket.

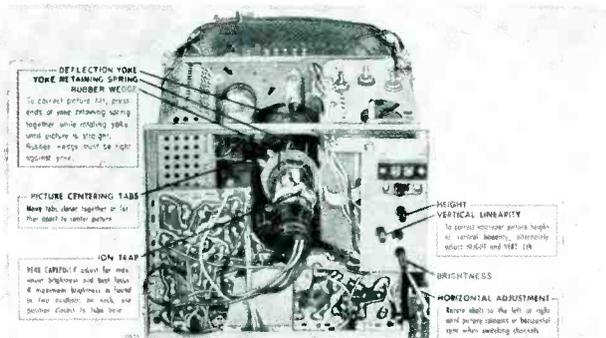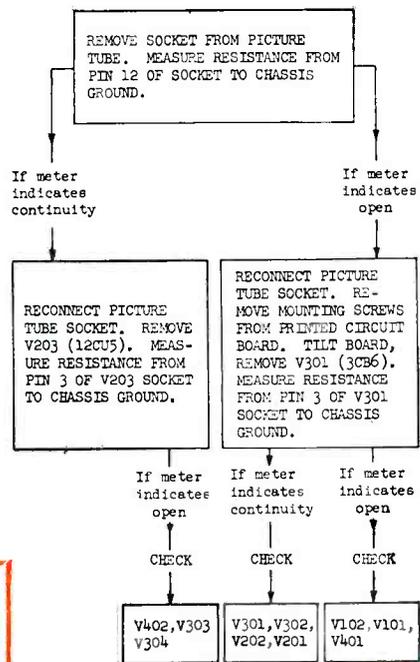Occasionally a tube heater will measure good when cold, but will "open" upon application of power. In this case, measuring continuity of the heater circuit with power applied may be necessary. An AC voltmeter or an electrician's neon test lamp can be used to circuit trace (check voltage) the heater circuit with AC power applied. However, be sure to observe the "High Voltage Warning".



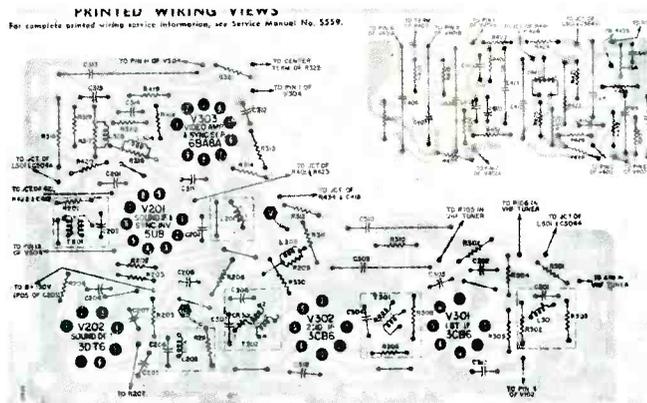Rear View of Chassis Showing Adjustment Locations.




CHANNEL ADJUSTMENT

Channel adjustment of each station should be checked upon installation and at every service call. With proper adjustment, best picture is obtained at approximately center rotation of Fine Tuning control.

IMPORTANT: Always make adjustment on lowest channel first, then work up, in order of channel number to the highest channel. (For example, if channels 2, 9, 7 and 5 are received, adjust in this order: 2, 5, 7, 9.)

Before proceeding with adjustment, see illustration for location of channel slugs, then adjust as follows:

- Turn the set on and allow 15 minutes to warm up.
- Set Channel Selector for lowest channel to be adjusted. Set other controls for normal picture and sound.
- Set Fine Tuning control at center of its range by rotating it approximately halfway between its stops.
- Remove Channel Selector and Fine Tuning knobs and the gold escutcheon under the knobs.
- Using a 1/8" blade non-metallic tool (Part No. 98A 30-19), carefully adjust the channel slug for best picture. (Note that sound is not loudest at this point.) Repeat procedure for remaining stations, adjusting them in order of their channel number (from lowest channel to highest channel).

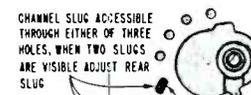

View of VHF Tuner. Knobs and Escutcheon removed.

REMOVING CABINET BACK & FRONT


The cabinet back and front are removable. Remove mounting screws; then pull away from set. In sets with carrying handle, mounting screws must be removed from handle.

To remove chassis from cabinet shell, remove back, front and screws at bottom. Remove chassis through front.

FUSIBLE RESISTOR

A pig-tail type fusible resistor (Part No. 61A22) is used as a B+ and initial surge fuse. It is located below the tuner.

TUBE LOCATIONS

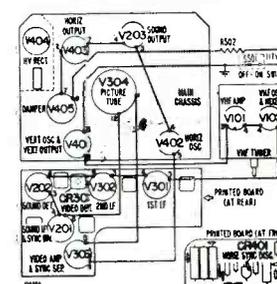

IMPORTANT CAUTION: Limited space is available when adjusting picture centering tabs and ion trap. Picture centering tabs may be adjusted using a non-metallic rod.

TACO TOPLINER ANTENNA

[from page 19]

The delay line is essentially a balanced "T" section composed of inductive series elements and a capacitive shunt element. By proper design of the elements, the transmission of signals is delayed at the high band frequencies, while at low band frequencies the reactance of the circuit is such that transmission is not retarded. Fig. 6a shows a schematic representation of the delay line. Fig. 6b is a sketch of the final delay line, where the length L , spacing S and wire diameter have been chosen to give the proper amount of distributed shunt capacity. The delay line is constructed of $\frac{1}{8}$ inch aluminum wire and special insulators to maintain the spacing, on which stable operation depends.

Parasitic Elements

The desired gain and directivity has been obtained by adding several elements to the basic driven units indicated in Fig. 1. A conventional reflector is added for increased low band gain and improved front-to-back ratio. To equalize the gain in the low band a parasitic director is added as the first element on the crossarm. This director is insulated at the center and a phase reversing loop is inserted between the two dipoles to make the unit work in both the high and the low bands. A split director is employed to give uniform increased gain on high band channels. The resulting antenna gives a unidirectional single lobed pattern over the complete high and low band channels.

Mechanical Features

To maintain consistent day-in and day-out performance of the antenna, and in order to maintain the stability of the delay line under all operating conditions, the antenna is designed for maximum mechanical strength in all its phases. Completely factory assembled, high signal strength 5052H16 aluminum alloy is used throughout. Being many times stronger than aluminum used in antennas manufactured in the early days of television, the antenna will stand up under the rigid requirements of present day reception. Wind sway, vibration, misalignment of elements and similar conditions which would not have affected the operation of a TV receiver being used on only a single channel, cannot be tolerated in the present day multi-channel era. The alloy used is many times stronger, and in addition the elements incorporate top quality mechanical support to hold them permanently in position. Insulators are of a tough durable plastic material of high dielectric quality and have excellent impact properties thus insuring consistent operation.



Radio - TV Hi Fi-Audio Communications Electronics

SERVICEMEN

SERVICE DEALER



and ELECTRONIC SERVICING

is YOUR magazine.

Subscribe to it now. Reap its benefits!

Now every serviceman engaged in every phase of radio-TV
and Industrial Electronics servicing will find:

SUBSCRIPTION RATES: 12 Issues \$3; 24 Issues \$5 (In the U.S.A., U.S. Possessions, Canada and Mexico). Elsewhere add \$1 per year.

SERVICE DEALER AND ELECTRONIC SERVICING

67 W. 44 St., New York 26, N.Y.

NEW

RENEWAL

Sirs: I remit herewith \$..... Enter a subscription for..... years as follows:

Name.....

Address.....

City..... Zone..... State.....

Name of firm.....

Firm's business address.....

City..... Zone..... State.....

CHECK YOUR CLASSIFICATION

Independent Radio-TV Serviceman

Owner

Radio-TV Service Organization

Employee

Retail Store having Service Department

Service Mgr.

Industrial Electronic Service Firm

Student

If some other type of company describe:.....

IF STUDENT, Name of School.....

A TYPICAL ISSUE COVERS

- Latest TV Installation and Maintenance Techniques for VHF and UHF
- Auto Radio Installation and Service
- Mobile Communications, 2-Way Radio, Ship-to-Shore Radio Installation and Service Techniques
- Industrial Electronics Equipment Servicing Data
- Advanced Data on New Circuitry
- Production Changes and Field Service Data on Receivers
- New Tubes
- New Test Equipment, Operation and Application Data
- P.A. Installation and Service
- Hi-Fi Installation and Service
- New Developments, Such As Transistors, Color, UHF, etc.
- News of the Trade
- Service Short Cuts and Shop Notes
- Explanation of Difficult Circuits
- M'gr's Complete Line of TV Schematics
- Video Speed Servicing Systems

"SURE, I use CLEAR BEAM Antenna Kits...they've doubled my installation business!"

Using Clear Beam Antenna Kits makes sense right from the start! Attractive packaging and do-it-yourself label creates customer interest in a new or replacement antenna—makes it a cinch to sell complete installations.

Servicemen installing Clear Beam Antenna Kits have eliminated "loose stock" inventory problems and are now able to price installation jobs accurately and profitably due to fixed material costs!

Start doubling your installation business with Clear Beam Antenna Kits now. Display them in your shop—show them from your service truck—let Clear Beam's self-selling antenna kits clinch extra installation sales for you!



Kits for Conicals, Arrows, Yagis, Dipales, UHF, VHF complete with mast, lead-in and all necessary hardware ready to install!



CLEAR ANTENNA CORP.,
BEAM CANOGA PARK, CALIF.

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Detroit, Baltimore

THE WORK BENCH

Unusual Service Problems And Their Solutions

by PAUL GOLDBERG
Service Manager

This Month's Problem:
No Color Reception,
Using HV Transformers

THIS month's installment is devoted to troubles with which a thorough knowledge of receiver circuitry is necessary.

CBS Color Receiver 205

The receiver was turned on and it was observed that the black and white picture was normal but no color was seen on the screen during color transmission. The sound was OK. In other words a black and white picture was seen at all times.

The diagram was studied and it was noted that the following tubes could cause this trouble: V16A, $\frac{1}{2}$ 6AN8, band pass amplifier, V16B, $\frac{1}{2}$ 6AN8, color killer, V43B, $\frac{1}{2}$ 6BL7, pulse

shaper. These were first replaced individually, but had no effect. V17, 6CB6 and V18, 6AL5 were also replaced but had no effect. (See Fig. 1)

The diagram was again studied. One can see that the chroma signal is fed from the first video amplifier V14, 6CL6's contrast control to the grid of V16A, $\frac{1}{2}$ 6AN8, the bandpass amplifier. The bandpass amplifier amplifies a band of frequencies of approximately 2.1 to 4.1 megacycles (chroma) which is then fed to the demodulators.

The purpose of the color killer V16B, $\frac{1}{2}$ 6AN8, is to prevent video information from passing through the bandpass amplifier and subsequent circuits when the receiver is receiving black and white

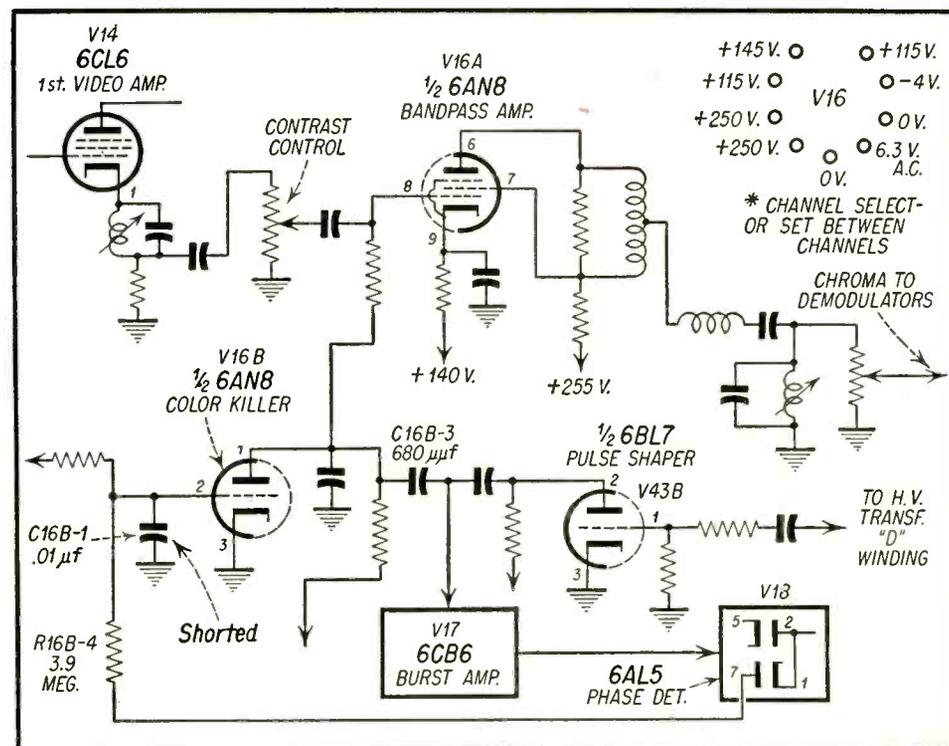


Fig. 1—Partial schematic of CBS TV receiver showing bandpass amplifier, color killer, pulse shaper, video amplifier and connecting circuitry.

AMPLIFIERS—(Audio, Hi-Fi, P. A.)

| | |
|---------------------------|---------------------------------------|
| Allied Radio Corp. | 100 N. Western Ave., Chicago 80, Ill. |
| Blonder-Tongue Labs, Inc. | 526 North Ave., Westfield, N. J. |
| Bogen & Co., Inc., David | 29 Ninth Ave., New York 14, N. Y. |
| Transvision, Inc. | 360 North Ave., New Rochelle, N. Y. |

ANTENNAS

| | |
|---------------------------------|---|
| Amphenol Electronics Corp. | 1830 S. 54th Ave., Chicago 50, Ill. |
| Channel Master Corp. | Ellenville, New York |
| Clear Beam Antenna Corp. | Canoga Park, Calif. |
| Cornell-Dubilier Electric Corp. | South Plainfield, New Jersey |
| Electrend Products Corp. | St. Joseph, Mich. |
| Finney Company, The | 4612 St. Clair Ave., Cleveland 3, Ohio |
| Hi-To TV Antenna Corp. | 3540 N. Ravenswood Ave., Chicago 13, Ill. |
| Holloway Electronics Corp. | Fort Lauderdale, Fla. |
| JFD Manufacturing Co., Inc. | 6127 16th Ave., Brooklyn 4, N. Y. |
| Philco Corp. | Philadelphia 34, Pa. |
| Radiart Corp. | 3455 Vega Ave., Cleveland 13, Ohio |
| Radio Merchandise Sales, Inc. | 2016 Bronxdale Ave., New York 60, N. Y. |
| Technical Appliance Corp. | Sherburne, New York |
| Telco Electronic Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Telrex, Inc. | Asbury Park, N. J. |
| Trio Manufacturing Corp., | Griagsville, Ill. |
| Walco Electronics Corp. | 3602 Crenshaw Blvd., Los Angeles 16, Cal. |
| Winegard Company | 3000 Scotten Blvd., Burlington, Iowa |

ANTENNA ACCESSORIES

| | |
|--------------------------------------|--|
| Alliance Manufacturing Co. | Alliance, Ohio |
| Amphenol Electronics Corp. | 1830 S. 54th Ave., Chicago 50, Ill. |
| Blonder-Tongue Labs, Inc. | 526 North Ave., Westfield, N. J. |
| Channel Master Corp. | Ellenville, New York |
| General Cement Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| I. E. Manufacturing Co. | 325 N. Hoyne Ave., Chicago 12, Ill. |
| JFD Manufacturing Co., Inc. | 6127 16th Ave., Brooklyn 4, N. Y. |
| Jontz Manufacturing Co. | 1101 E. McKinley Ave., Mishawaka, Ind. |
| Kenwood Engineering Co. | 265 Colfax Ave., Kenilworth, N. J. |
| Mosley Electronics | 8622 St. Charles Rock Rd., St. Louis 14, Mo. |
| Mueller Electric Co. | 1583 E. 31st Street, Cleveland 14, Ohio |
| Philco Corp. | Philadelphia 34, Pa. |
| Radiart Corp. | 3455 Vega Ave., Cleveland 13, Ohio |
| Radio Merchandise Sales, Inc. | 2016 Bronxdale Ave., New York 60, N. Y. |
| South River Metal Products Co., Inc. | South River, New Jersey |
| Superex Electronics Corp. | 6 Radford Place, Yonkers, N. Y. |

BATTERIES

| | |
|---------------------|----------------------|
| Burgess Battery Co. | Freeport, Illinois |
| RCA, (Tube Div.) | Harrison, New Jersey |

BOOKS & MANUALS

| | |
|-----------------------------|---|
| Cisin, Harry G. | Amagansett, N. Y. |
| Cowan Publishing Corp. | 67 West 44th Street, New York 36, N. Y. |
| Electronic Publishing Co. | 180 N. Wacker Drive, Chicago 6, Ill. |
| Rider, John F., Publisher | 480 Canal Street, New York 13, N. Y. |
| Sams, Howard W. & Co., Inc. | 2201 E. 46th Street, Indianapolis 5, Ind. |
| United Catalog Publishers | 110 Lafayette Street, New York 13, N. Y. |

BUSINESS ORDER FORMS

| | |
|---------------------------|--|
| Electronic Publishing Co. | 180 N. Wacker Drive, Chicago 6, Ill. |
| Oelrich Publications | 4308 N. Milwaukee Ave., Chicago 41, Ill. |

CAPACITORS

| | |
|---------------------------------|--|
| Aerovox Corp. | New Bedford, Mass. |
| Astron Corp. | 255 Grant Ave., East Newark, N. J. |
| Centralab, Div. of Globe-Union | 900 E. Keefe Ave., Milwaukee 1, Wisc. |
| Cornell-Dubilier Electric Corp. | South Plainfield, New Jersey |
| Erie Resistor Corp. | Erie, Pa. |
| Illinois Condenser Co. | 1616 N. Throop St., Chicago 22, Ill. |
| Planet Sales Corp. | 225 Belleville Ave., Blomfield, N. J. |
| Pyramid Electric Co. | 1445 Hudson Blvd., North Bergen, N. J. |
| Sprague Products Co. | 71 Marshall Street, North Adams, Mass. |

CHEMICALS, SPRAYS, LUBRICANTS

| | |
|----------------------------|---|
| Electronic Chemical Corp. | 813 Communipaw Ave., Jersey City 4, N. J. |
| General Cement Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Great Eastern Mfg. Co. | 165 Remsen Ave., Brooklyn 12, N. Y. |
| Krylon, Inc. | Ford & Washington Sts., Norristown, Pa. |
| Quietrol Co., Inc. | Spartanburg, South Carolina |
| Superex Electronics Corp. | 6 Radford Place, Yonkers, N. Y. |
| Telematic Industries, Inc. | 16 Howard Ave., Brooklyn 21, N. Y. |
| Walco Electronics Corp. | 3602 Crenshaw Blvd., Los Angeles 16, Cal. |

CHOKES, COILS & TRANSFORMERS (RF)

| | |
|------------------------------------|--|
| Acme Electric Corp. | 468 Water Street, Cuba, New York |
| Chicago Standard Transformer Corp. | 3501 Addison Street, Chicago 18, Ill. |
| Merit Coil & Transformer Corp. | 4427 N. Clark Street, Chicago 40, Ill. |
| Miller, J. W. Company | 5917 S. Main Street, Los Angeles 3, Cal. |
| Superex Electronics Corp. | 6 Radford Place, Yonkers, N. Y. |
| Triad Transformer Corp. | 4055 Redwood Ave., Venice, Calif. |

CHOKES, COILS & TRANSFORMERS

| | |
|--|--|
| Acme Electric Corp. | 468 Water Street, Cuba, New York |
| Chicago Standard Transformer Corp. | 3501 Addison Street, Chicago 18, Ill. |
| Delco Radio (Div. of General Motors Corp.) | Kokomo, Indiana |
| Merit Coil & Transformer Corp. | 4427 N. Clark Street, Chicago 40, Ill. |
| Perma-Power Company | 4721 N. Damen Ave., Chicago 25, Ill. |
| Triad Transformer Corp. | 4055 Redwood Ave., Venice, Calif. |

CHOKES, COILS & TRANSFORMERS

| | |
|------------------------------------|--|
| Acme Electric Corp. | 468 Water Street, Cuba, New York |
| Chicago Standard Transformer Corp. | 3501 Addison Street, Chicago 18, Ill. |
| Great Eastern Mfg. Co. | 165 Remsen Ave., Brooklyn 12, N. Y. |
| Merit Coil & Transformer Corp. | 4427 N. Clark Street, Chicago 40, Ill. |
| Perma-Power Company | 4721 N. Damen Ave., Chicago 25, Ill. |
| Ram Electronic Sales Co. | 5 Radford Place, Irvington, New York |
| Superex Electronics Corp. | 6 Radford Place, Yonkers, N. Y. |
| Triad Transformer Corp. | 4055 Redwood Ave., Venice, Calif. |

CONNECTORS, PLUGS

| | |
|-------------------------------|--|
| Blonder-Tongue Labs, Inc. | 526 North Ave., Westfield, N. J. |
| Cannon Electric Co. | P. O. Box #75, Los Angeles 31, Calif. |
| Eby Sales Co. of N. Y. | 130 Lafayette Street, New York 13, N. Y. |
| General Cement Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Mosley Electronics | 8622 St. Charles Rock Rd., St. Louis 14, Mo. |
| Radio Merchandise Sales, Inc. | 2016 Bronxdale Ave., New York 60, N. Y. |

FUSES

| | |
|-------------------|--|
| Bussmann Mfg. Co. | University and Jefferson, St. Louis 7, Mo. |
| Littelfuse, Inc. | DesPlains, Ill. |

BUYER'S DIRECTORY OF ADVERTISED PRODUCTS

• This department is an additional service to our readers and advertisers. It is not intended to cover all products in all categories, nor is it intended to cover all products made by any manufacturer.

• The classifications are broad. Under each is listed the name and address of only those manufacturers who have, in the recent past, or who are currently advertising these particular products in this publication.

• This service is not a part of the advertiser's contract. The listings may change in future issues. Every reasonable precaution is taken to avoid errors and omissions.

HARDWARE

| | |
|--------------------------------------|---|
| I. E. Manufacturing Co. | 325 N. Hoyne Ave., Chicago 12, Ill. |
| Kenwood Engineering Co. | 265 Colfax Ave., Kenilworth, N. J. |
| Mueller Electric Co. | 1583 E. 31st Street, Cleveland 14, Ohio |
| South River Metal Products Co., Inc. | South River, New Jersey |
| Television Hardware Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Walco Electronics Corp. | 3602 Crenshaw Blvd., Los Angeles 16, Cal. |

MICROPHONES, Stands & Accessories

| | |
|-------------------------|---|
| American Microphone Co. | 370 S. Fair Oaks Ave., Pasadena 3, Cal. |
| Astac Corporation | Conneaut, Ohio |
| Atlas Sound Corp. | 1446 39th Street, Brooklyn 18, N. Y. |
| Electro-Voice, Inc. | Buchanan, Michigan |
| Shure Bros., Inc. | 222 Hartrey Avenue, Evanston, Ill. |

PHONOGRAPH NEEDLES

| | |
|----------------------------|---|
| Astac Corporation | Conneaut, Ohio |
| Jensen Industries, Inc. | 342 S. Wood Street, Chicago 12, Ill. |
| Permo, Inc. | 6415 N. Ravenswood Ave., Chicago 26, Ill. |
| Recofon Corp. | 52-35 Barnett Ave., Long Island City 4, N. Y. |
| Walco-Electrovox Co., Inc. | 60 Franklin Street, East Orange, N. J. |

PHONOGRAPH PICKUPS & CARTRIDGES

| | |
|-------------------------|---|
| Astac Corporation | Conneaut, Ohio |
| American Microphone Co. | 370 S. Fair Oaks Ave., Pasadena 3, Cal. |
| Electro-Voice, Inc. | Buchanan, Michigan |
| Shure Brothers, Inc. | 222 Hartrey Avenue, Evanston, Ill. |
| Sonotone Corp. | Elmsford, New York |

POWER SUPPLIES (Converters & Inverters)

| | |
|---------------------------------|---|
| American Television & Radio Co. | 300 East First St., St. Paul 1, Minn. |
| Electro Products Labs, Inc. | 4501 N. Ravenswood Ave., Chicago 40, Ill. |
| Perma-Power Company | 4721 N. Damen Ave., Chicago 25, Ill. |
| Vokar Corporation | Dexter 2, Michigan |

RESISTORS & CONTROLS

| | |
|---|---------------------------------------|
| Aerovox Corp. | New Bedford, Mass. |
| Centralab, Div. of Globe-Union | 900 E. Keefe Ave., Milwaukee 1, Wisc. |
| Claroat Mfg. Co., Inc. | Dover, New Hampshire |
| Delco Radio, Div. of General Motors Corp. | Kokomo, Indiana |
| Erie Resistor Corp. | Erie, Pa. |
| International Resistance Co. | 401 N. Broad St., Philadelphia 8, Pa. |

SEMI-CONDUCTORS

| | |
|---------------------------------|--|
| CBS-Hytron | 100 Endicott Street, Danvers, Mass. |
| Federal Telephone & Radio Corp. | 100 Kingsland Road, Clifton, N. J. |
| General Electric Co. | Schenectady, New York |
| Philco Corp. | Philadelphia 34, Pa. |
| RCA, (Tube Div.) | Harrison, New Jersey |
| Raytheon Mfg. Company | Newton, Mass. |
| Tarzian Inc., Sarkes | 415 N. College Ave., Bloomington, Ind. |
| Tung-Sol Electric, Inc. | 95 Eighth Ave., Newark 4, N. J. |

SERVICING AIDS

| | |
|---|---|
| Allied Radio Corp. | 100 N. Western Ave., Chicago 80, Ill. |
| American Phenolic Corp. | 1830 S. 54th Ave., Chicago 50, Ill. |
| Belden Manufacturing Co. | 4647 W. Van Buren St., Chicago 80, Ill. |
| Blonder-Tongue Labs, Inc. | 526 North Ave., Westfield, N. J. |
| Colman Tool & Machine Co. | P. O. Box 7026, Amarillo, Tex. |
| Columbia Wire & Supply Co. | 2850 Irving Park Road, Chicago 18, Ill. |
| Electric Soldering Iron Co. | Deep River, Conn. |
| Electronic Publishing Co. | 180 N. Wacker Drive, Chicago 6, Ill. |
| General Cement Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Mall Tool Company | 7740 South Chicago Ave., Chicago 19, Ill. |
| Multicore Solder Div., Brit. Ind., Inc. | 80 Shore Rd., Pt. Wash., N. Y. |
| Quietrol Co., Inc. | 4308 N. Milwaukee Ave., Chicago 41, Ill. |
| Ram Electronic Sales Co. | Spartanburg, South Carolina |
| Tele-Scopic Products, Inc. | Irvington, New York |
| Ungar Electric Tools, Inc. | 215 W. 33rd Street, New York 1, N. Y. |
| United Catalog Publishers | 110 Lafayette Street, New York 13, N. Y. |
| Vaco Products Co. | 317 E. Ontario Street, Grove City, Pa. |
| Wall Mfg. Co. | Grove City, Pa. |
| Weller Elec. Corp. | 160 N. 15 St., Phila., Pa. |
| Wen Products, Inc. | 5806 Northwest Highway, Chicago 31, Ill. |
| Xcelite, Inc. | Thorne Ave. and Bank St., Orchard Park, N. Y. |
| Yeats Appliance Dolly Sales Co. | 2133 N. 12th Street, Milwaukee 5, Wisc. |

SPEAKERS (including phones)

| | |
|---|--|
| Delco Radio, Div. of General Motors Corp. | Kokomo, Indiana |
| Electro-Voice, Inc. | Buchanan, Michigan |
| Jensen Mfg. Company | 6601 S. Laramie Ave., Chicago 38, Ill. |
| North American Philips Co., Inc. | 100 East 42nd Street, New York 17, N. Y. |

| | |
|-------------------------------|--|
| Oxford Electric Corp. | 3911 S. Michigan Ave., Chicago 15, Ill. |
| Philco Corp. | Philadelphia 34, Pa. |
| Quam-Nichols Company | Marquette Rd. & Prairie Ave., Chicago 37, Ill. |
| Telex | Telex Park, St. Paul, Minn. |
| University Loudspeakers, Inc. | 80 S. Kenzie Ave., White Plains, N. Y. |

SPEAKER ENCLOSURES

| | |
|-------------------------------|---|
| Electro-Voice, Inc. | Buchanan, Michigan |
| Jensen Mfg. Company | 6601 S. Laramie Ave., Chicago 38, Ill. |
| Transvision, Inc. | 460 North Ave., New Rochelle, N. Y. |
| University Loudspeakers, Inc. | 80 S. KENSICO AVE., White Plains, N. Y. |

TEST EQUIPMENT & INSTRUMENTS

| | |
|--|--|
| Allied Equipment & Instrument Corp. | 100 N. Western Ave., Chicago, Ill. |
| American Scientific Development Co. | 334 S. Main St., Fort Atkinson, Wisc. |
| B & K Manufacturing Co. | 3731 N. Southport, Pasadena, Calif. |
| Central Electronics, Inc. | 1247 Belmont Ave., Chicago, Ill. |
| Century Electronics | 111 Roosevelt Ave., Mineola, N. Y. |
| Electronic Instrument Company (EICO) | 84 Withers Street, Brooklyn 11, N. Y. |
| Electronic Test Instrument Corp. | 13224 Livernois Avenue, Detroit 38, Mich. |
| General Electronic Research Co. | Whitewater, Wisc. |
| Heath Company, The | Benton Harbor, Michigan |
| Hickok Electrical Instrument Co. | 10533 Dupont Ave., Cleveland 8, Ohio |
| Hycon Electronics, Inc. | 320 S. Arroyo Parkway, Pasadena, Calif. |
| Jackson Electrical Instrument Co. | 16 S. Patterson Blvd., Dayton 2, Ohio |
| Leitch Engineering Co. | 326 Lincoln St., Manchester, N. H. |
| Moss Electronic Distributing Co., Inc. | 38 Murray Street, New York 7, N. Y. |
| Phaestron Company | 151 Pasadena Ave., South Pasadena, Calif. |
| Philco Corp. | Philadelphia 34, Pa. |
| Precision Apparatus Co., Inc. | 70-31 84th Street, Glendale 27, L. I., N. Y. |
| Protosound Electronics, Inc. | 44-05 30th Ave., Long Island City 3, N. Y. |
| Radio City Products Co., Inc. | Centre & Glendale Sts., Easton, Pa. |
| Research Inventions & Mfg. Co. | 617 F Street, N. W., Washington 1, D. C. |
| Seco Mfg. Co. | 5015 Penn Avenue South, Minneapolis, Minn. |
| Simson Electric Company | 5200 W. Kinzie Street, Chicago 44, Ill. |
| Superior Instruments Co. | 2435 White Plains Rd., New York 67, N. Y. |
| Telematic Industries, Inc. | 16 Howard Ave., Brooklyn 21, N. Y. |
| Teletest Instrument Corp. | 31-01 Linden Place, Flushing 54, N. Y. |
| Triplet Electrical Instrument Co. | Bluffton, Ohio |
| Weston Electrical Instrument Corp. | 614 Freilighuyser Ave., Newark 5, N. J. |
| Winston Electronics, Inc. | 4312 Main Street, Philadelphia 27, Pa. |

TOOLS

| | |
|---|---|
| Electric Soldering Iron Co. | Deep River, Conn. |
| General Cement Mfg. Co. | 418 S. Wyman St., Rockford, Ill. |
| Ohmite Manufacturing Co. | 3640 W. Howard Street, Skokie, Illinois |
| Philco Corp. | Philadelphia 34, Pa. |
| Krauter & Co., Inc. | 583 18th Avenue, Newark, N. J. |
| Mall Tool Company | 7740 S. Chicago Ave., Chicago 19, Ill. |
| Multicore Solder Div., Brit. Ind., Inc. | 80 Shore Rd., Pt. Wash., N. Y. |
| Tele-Scopic Products, Inc. | 215 W. 33rd Street, New York 1, N. Y. |
| Ungar Electric Tools, Inc. | P. O. Box 312, Venice, Calif. |
| Vaco Products Co. | 317 E. Ontario St., Chicago 11, Ill. |
| Wall Mfg. Co. | Grove City, Pa. |
| Walco Electronics Corp. | 3602 Crenshaw Blvd., Los Angeles 16, Cal. |
| Weller Elec. Corp. | 160 N. 15 St., Phila., Pa. |
| Wen Products, Inc. | 5806 Northwest Highway, Chicago 31, Ill. |
| Xcelite, Inc. | Thorne Ave. and Bank St., Orchard Park, N. Y. |

TUBES—CRT & RECEIVING

| | |
|---|---|
| Barry Electronics Corp. | 512 Broadway, New York 12, N. Y. |
| CBS-Hytron | 100 Endicott St., Danvers, Mass. |
| Ceco Electronics Co. | Columbia Ave. and 18th, Irvington 11, N. J. |
| Delco Radio, Div. of General Motors Corp. | Kokomo, Indiana |
| Federated Television Mart | 513 Rogers Ave., Brooklyn 25, N. Y. |
| General Electric Co. | Schenectady, N. Y. |
| Philco Corp. | Philadelphia 34, Pa. |
| RCA, (Tube Div.) | Harrison, N. J. |
| Raytheon Mfg. Company | Newton, Mass. |
| Tung-Sol Electric, Inc. | 95 Eighth Ave., Newark 4, N. J. |

TV RECEIVERS

| | |
|-------------------------|---------------|
| Hotpoint Division of GE | Chicago, Ill. |
|-------------------------|---------------|

VIBRATORS

| | |
|---|--|
| American Television & Radio Co. | 300 E. First Street, St. Paul 1, Minn. |
| Cornell-Dubilier Electric Corp. | South Plainfield, New Jersey |
| Delco Radio, Div. of General Motors Corp. | Kokomo, Indiana |
| Radiart Corp. | 3455 Vega Ave., Cleveland 13, Ohio |
| Vokar Corporation | Dexter 2, Michigan |

WIRE—CABLE—HARNESSES

| | |
|---------------------------------|---|
| American Phenolic Corp. | 1830 S. 54th Ave., Chicago 50, Ill. |
| Belden Manufacturing Co. | 4647 W. Van Buren St., Chicago 80, Ill. |
| Columbia Wire & Supply Co. | 2850 Irving Park Road, Chicago 18, Ill. |
| Eby Sales Co. of N. Y. | 130 Lafayette St., New York 13, N. Y. |
| Federal Telephone & Radio Corp. | 100 Kingsland Road, Clifton, N. J. |
| Jersey Specialty Co. | Burgess Place, Mountain View, N. J. |

Don't just say
capacitors

Ask For Sprague By
Catalog Number
Know what you're getting... get
exactly what you want. Don't be
vague... insist on Sprague. Use
complete radio-TV service cata-
log C-610. Write Sprague Prod-
ucts Company, 71 Marshall
Street, North Adams, Mass.

SPRAGUE
WORLD'S LARGEST
CAPACITOR MANUFACTURER

SHOW ANY PICTURE or PATTERN


at any time—ON ANY TV SET



- For Servicing Black & White and Color TV
- For Merchandising and Advertising Promotions
- For Paging, Educational and Industrial Use

New
MODEL 1000

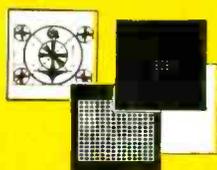B&K DYNA-SCAN PICTURE AND PATTERN VIDEO-GENERATOR



**3 SLIDE
TRANSPARENCIES
ARE SUPPLIED**

1. Indian Head Pattern
2. White Dot Pattern
3. White Line Crosshatch
Plus One Clear Acetate

These are broadcast quality and assure high-definition TV images. You can also transmit slides of any subject you wish.



MODEL 950

See Your Distributor or Send For Bulletin 1000-D

B&K MANUFACTURING CO.

3726 N. Southport Ave. • Chicago 13, Illinois

Makers of DYNA-QUIK, CRT, CALIBRATOR and DYNA-SCAN



Simplify and speed servicing with this unique, new, COMPLETE FLYING SPOT SCANNER. Produces composite video and sync signal that operates any standard VHF black and white or color TV receiver. Easily reproduces standard Indian Head test pattern or any other pattern—in home, shop or store—for proper TV set alignment; enables you to make all color TV static and dynamic convergence adjustments with stable White Dot and White Line patterns. Can be used with one or more standard TV receivers or fed into master antenna system. Reproduces from any film transparency. Transmits messages typed or written on clear acetate. Size: 16½ in. long, 10¾ in. high, 9½ in. wide. Net wt. 28 lbs. **\$199.95** NET

Model 950 Dyna-Scan Pickup and RF Generator Only

Make your own picture and pattern generator. Just connect Model 950 to any properly modified 10-inch TV set which acts as your external flying spot scanner. Size: 3½ in. high, 10½ in. wide, 5 in. deep. Complete with 3 slide transparencies and 1 clear acetate. Net wt. 5 lbs. **\$69.95** NET

TAPPING TV TRANSMISSION LINES

[from page 25]

may be contacted by the resistor which is subsequently inserted through the hole created by the cutting tool. This "doughnut hole" cutter requires only a few easy turns to clear the outer sheath, the shield, and the small portion of polyethylene between the inner and outer conductors. The ground connection to the cable is made by means of an insert ground screw which is threaded all the way down and cuts its way

through the cable sheath to establish the ground contact with the shield. Making the ground connection applies the tapped TV voltages to the coaxial outlet. Regular inspection of the boring tool is required to make certain that it is in good working order. Special attention to the proper depth setting is important to make certain that the correct amount of metal and plastic is removed from the cable. 

RIDER SPEAKS

by JOHN F. RIDER

"Dean of America's Radio Servicemen"



THE BIG problem in the minds of servicing dealers and technicians is factory service. Two prominent receiver manufacturers have recently announced their intention to open a number of factory service branches in major population centers of the United States—this in addition to the one manufacturer who has had a great number of these stations in operation for the past 10 years.

Looking at the situation without rose colored glasses and analyzing its effects without emotion we do *not* foresee the end of the electronic servicing industry. As a matter of fact this conclusion is reached even after consideration of the possibility that other receiver manufacturers will do the same thing.

Some of the receiver manufacturers who will remain in the home electronic equipment field after the present battle between the giants of the industry is finished are not too happy about the prospect of direct service contact with the receiver buying public, but the likelihood is that a factory service program of some sort will be conducted by most of them. The thinking is dictated by the sales departments, which maintain that an advantage in receiver sales accrues to any organization that eases the mind of the buying public on the question of service.

A not insignificant factor in this thinking is the possibility of making the factory service branches a profitable operation, since they would service all the products made by the parent concern. As things look now it is reasonable to presuppose that the sales programs of those who stay in the manufacturing business will encompass home electronic and home white goods equipment. So, opening factory service

branches is a pattern which will without doubt be adopted by most producers of TV receivers and white goods—including those concerns which at present say they'll do nothing. Competition is a powerful influence in making manufacturers change their minds.

Interestingly enough, quite a few manufacturers who have not yet declared themselves broadly on the issue of factory service have, during the past few years, operated a few scattered installations.

Let us for the moment assume the worst; that makers of the equipment *will* operate factory service branches. Experience in the past has illustrated that operating a service branch is not cheap. It costs money and we must accept the premise that factory service branches which lose money will not be continued for long. Naturally, every effort will be expended to make them profitable. The reasoning behind this statement is that sales competition between the producers is keen, and while profits can be earned even the big manufacturers question the advisability of maintaining service branches which are draining off profits earned on sales. In a limited way this has been proven; TV receiver manufacturers *have* closed down unprofitable service branches.

The factory service branch has advantages over the independent servicing facility. More money is available for advertising and there is great public trust in the words "factory service" or "service by factory trained personnel." Whether the factory service is better than that given by a technically competent service facility is debatable; a fact that is, unfortunately, not generally known.

However, let's not lose sight of the

vulnerable point—profitable operation of the factory service branch—it must operate profitably or close down. Advertising sells brand names, but the dealer who carries the line is in direct contact with the public. If he is a servicing dealer he need worry very little about factory service, because he can sell his service to his customers. After all, the dealer sold the original product, and the path of least resistance, when service is required by the customer, is back to the organization which sold him equipment.


What about the service shop which doesn't sell receivers? How does this new approach to service affect it? If the shop is located in an area of relatively low population density (which also means relatively low receiver population) it may not pay for a factory to establish a local competing service facility. Even the manufacturer with the greatest number of factory service branches presently in operation is not active in many areas, except perhaps by arrangement with a local service shop. It is doubtful that any other manufacturer can spread his service branches as widely as this one.

Widespread activity is dependent on diversification of products to be serviced. The greater the variety of products being manufactured by the organization the greater the possibility of making a factory service branch pay, because the categories of product owners who call for service are more numerous.

The ability to finance a great many factory service branches is not equal for all electronic equipment manufacturers. This statement does not reflect adversely on the financial standing of any concerns; it simply means that some manufacturers have greater financial power than others and can afford to do things which others can't.

Thus the service shop owner who is not engaged in equipment sales is not doomed to extinction. He will have the opportunity to compete to an extent which offers greater possibilities than that of mere existence. In next month's issue we'll describe the things which are being done and can be done by servicing facilities not only to maintain their standing, but to grow in spite of factory service. ■ ■

AS MODERN AS TOMORROW...

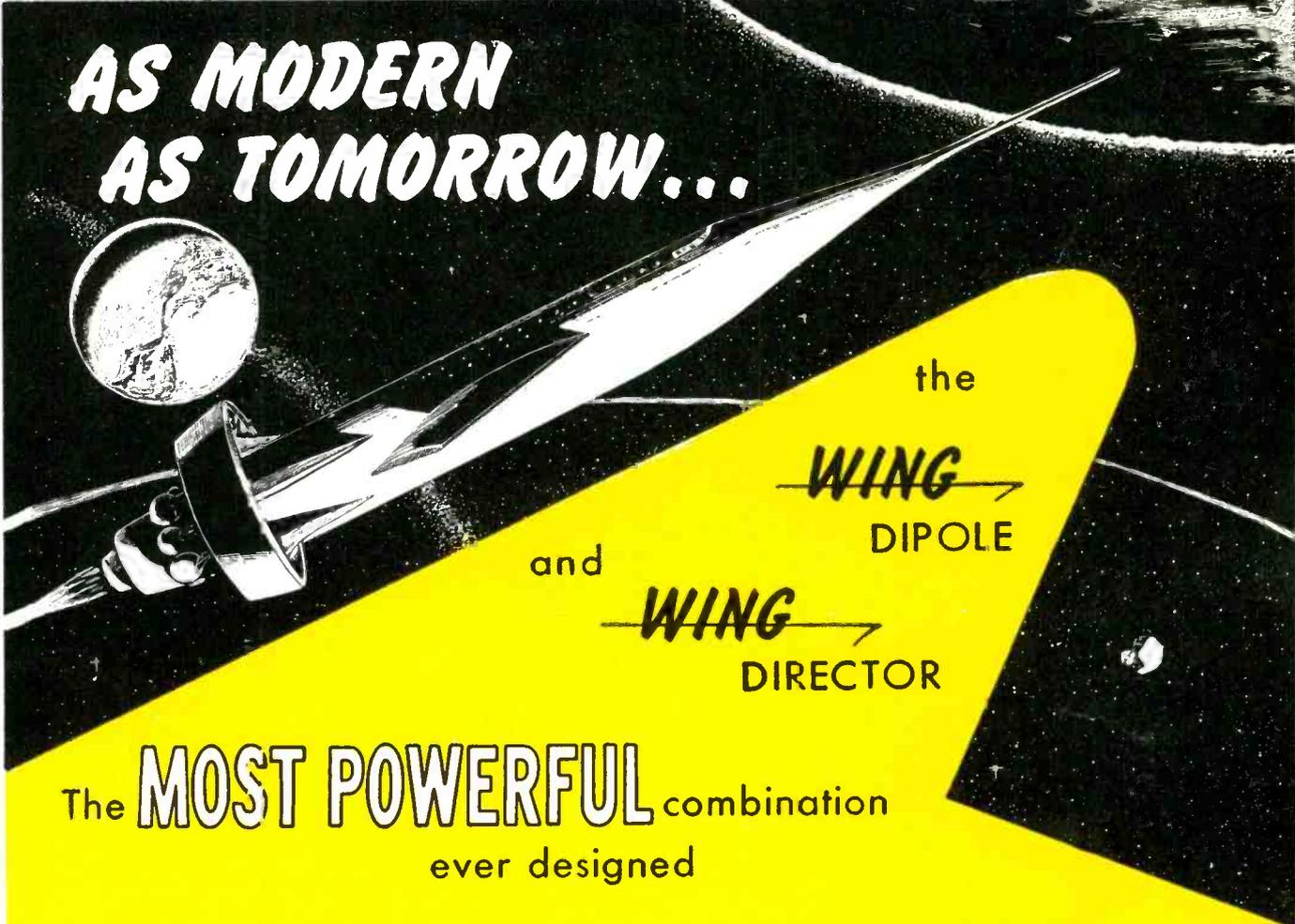

the
WING →
DIPOLE

and
WING →
DIRECTOR

The **MOST POWERFUL** combination
ever designed

FOUND ONLY IN THE TRIO ZEPHYR LINE



ZEPHYR
MITE
POWER PACKED PAIR



FOR DISTANCE



Zephyr
POWER PACKED THREESOME



ZEPHYR ROYAL
POWER PACKED FOURSOME

Trio's Zephyr and Zephyr Royal, the leaders of the 1956 season, are brought to you in the 1957 models improved and perfected, and destined to remain the champions. This famous antenna family is expanded by the Zephyr-Mite, newest addition to the Zephyr family. Trio's Zephyr family features the "Wing" dipole—the composite dipole that brought the power of the Yagi to every channel! Add to this the "Wing" director, the revolutionary new director specifically

designed to enhance the power and sensitivity of the "Wing" dipole—and you have a combination that is unequalled in the TV antenna field today for the maximum in performance. The "Wing" dipole and "Wing" director are exclusive features of the Trio Zephyrs—features that make Trio "the choice antenna line."


Trio's recognized quality construction features the internationally famous Insta-Lok clamps—the clamps that 'protect' the element!

TRIO[®]

Manufacturing Company
GRIGGSVILLE, ILLINOIS

COPYRIGHT 1956 TRIO MFG CO. EXPORT SALES DIV., SCHEEL INTERNATIONAL INC., 4237 N. Lincoln Ave., Chicago, U.S.A. Cable Address: HARSHEEL

BEST IN

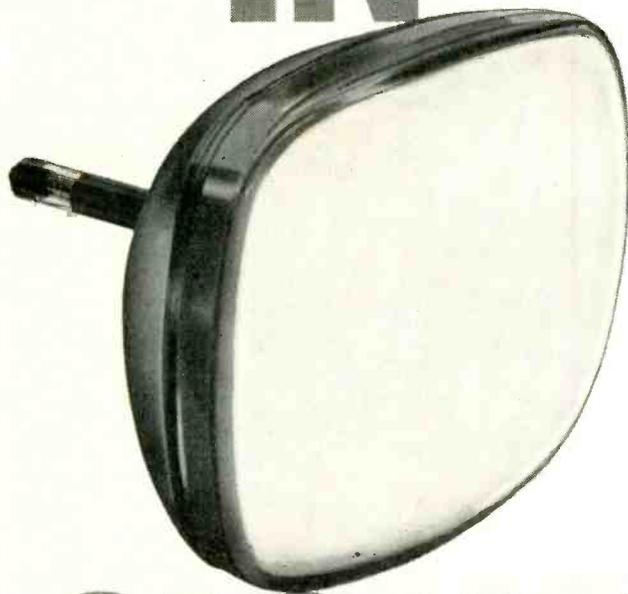

SIGHT

The Tung-Sol Magic Mirror Aluminized Picture Tube captures every tone, every detail brilliantly to bring out the best in every set. It's your best insurance for loyal, satisfied customers. Tell your supplier you'd rather have Tung-Sol tubes.

Blue Chip Quality


TUNG-SOL®
Magic Mirror Aluminized
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Columbus, Culver City, Dallas, Denver, Detroit, Melrose Park (Ill.), Newark, Seattle.

Radio set shipments to dealers during June, excluding automobile receivers, increased over the June 1955 level by 47 per cent and over the first six months of 1955 by 23 per cent, the Radio-Electronics-Television Manufacturers Association announced. Radio shipments in June also increased substantially over the May shipments, it was reported. Radio receiver shipments to dealers in June totaled 798,414 compared with 551,712 sets shipped in May and 542,382 receivers shipped in June of last year. First six months of 1955 shipments had totaled 2,515,807 radios compared with 3,270,809 radios shipped to dealers during the first half of this year.

Allen B. Du Mont Laboratories, Inc., and Chromatic Television Laboratories, Inc., have reached an agreement whereby Du Mont will undertake immediately a program aimed to get the Chromatic single-gun color tube and the color television set using the Chromatron into production.

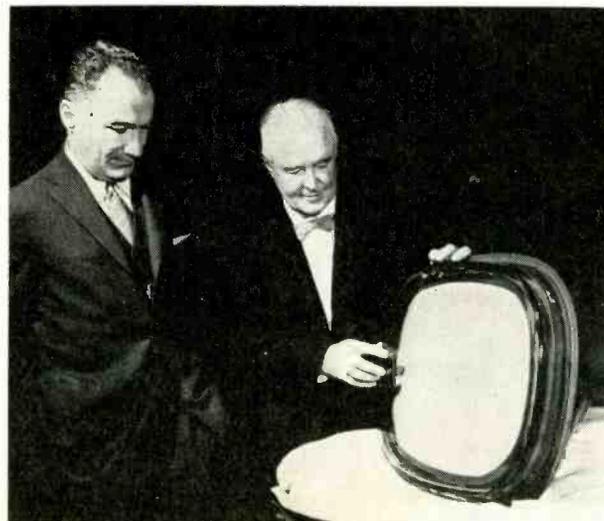The announcement was made jointly by David T. Schultz, President of Du Mont, and Paul Raibourn, (Right) Chairman of Chromatic.



It is anticipated, according to Messrs. Schultz and Raibourn, that preparatory work leading to mass production of the tube and color receivers will be completed within a year. When production begins, it was stated, the Chromatic tube will be available to all set manufacturers as well as for Du Mont receivers.

Appointment of Kenneth C. Kleidon to the newly-created post of National Color Television Manager for

trade

Hycon Electronics, Inc., Pasadena, Calif., was announced. Harry A. Kirkpatrick, general manager, said that Kleidon's chief responsibility will be to help familiarize television manufacturers, distributors, dealers, and service organizations with new techniques and equipment developed for testing and servicing color TV receivers. Kleidon will conduct color television symposiums in cities across the nation, Kirkpatrick said.

Automation, semiconductor applications, television receiver developments are but a few of the topics to be discussed when some of the nation's top electronic engineers and scientists gather in Syracuse, N. Y., Oct. 15-17 for the annual Radio Fall Meeting, the Radio-Electronics-Television Manufacturers Association announced.

A session of invited papers on "Recent Developments in Electron Devices" will be a feature of the Second Annual Technical Meeting of the IRE Professional Group on Electron Devices, to be held at the Shoreham Hotel, Washington, D. C., Thursday and Friday, October 25-26, 1956.

The marine telephone industry is ringing up record sales. Next year, if the present rate of sales holds up, 30,000 pleasure and commercial vessels will be equipped with marine-radiotelephone units, compared to 3,282 in 1945. Statistics of the American Telephone & Telegraph Co. show that registrations had jumped to 15,917 by 1950, and in 1955 reached 27,343.

The General Electric Company has announced its intention to make direct factory television service available in all areas where dealers and customers demand it. The announcement was made by William L. Parkinson, planning study manager of the General Electric Appliance and Television Receiver Division's product planning section during an address before the annual meeting of the Texas Servicemen's Association. Mr. Parkinson explained that service to customers is considered a major function of his division's marketing operation and, he said, "we are going to do whatever it takes in regard to service to sell the maximum number of goods".

flashes

"Service Dealer & Electronic Servicing" magazine and the CBS-Hytron Tube Division were honored by being given, for the first time, the Friends of Service Management Award for 1956 by NATESA at their annual convention held at Chicago September 14-16, 1956. Due to unsettled conditions in the set division, as it pertains to service, no awards were voted in the set division.

• • •

Channel Master Corp. has introduced two new television antennas which will be backed by a \$50,000 national consumer advertising campaign. This is the first national consumer advertising campaign in the history of the industry. It has been announced that the New York advertising agency of Balton, Barton, Durstine & Osborn have been appointed to introduce the new Channel Master T-W outdoor antenna and the smartly styled Showman indoor antenna to the American public.



Discussing these new antennas, Mr. Harold Harris, Channel Master Vice-President in charge of Sales and Engineering, recently addressed a conference of Channel Master distributors. Checkered boxes on the tables contain miniature versions of the revolutionary new T-W outdoor antenna—only antenna to employ the "Traveling Wave" principle.

• • •

The New England Radio-Electronics Meeting jointly sponsored by the Boston and Connecticut Valley sections of the I.R.E. will henceforth be held each fall instead of in the spring as in the past decade. The decision to shift the timing was made in order to make the meetings, which have grown steadily in importance and attendance in recent years, of even greater usefulness by moving them to a time halfway between the national conventions at New York each spring. The first fall meeting of NEREM will take place this November 15 and 16 at the Hotel Bradford in Boston.

Don Cain, Admiral Distributors-Chicago Division flying serviceman, made use of Polk Brothers' courtesy helicopter service when going to the International Amphitheatre to check the TV sets installed in the work



rooms of newspapers, news magazines and press associations for the Democratic National Convention.

• • •

A new dealer-aid, to assist distributors and dealers in selling and servicing color television, has been announced by E. P. Atcherly, merchandising manager, of Sylvania Electric Products, Inc. The new item is a 10-minute film strip entitled "Make Way for Color" and has been made available to all Sylvania's electronic products district sales offices. The film will be shown in the next few months to electronic products distributors and dealers at meetings from coast-to-coast by Sylvania sales representatives and sales engineers. The color film and recorded narrative points up selling reasons and outlines major differences in the composition of black-and-white and color television sets. It also touches on some of the new terms added to the technical vocabulary as a result of the impact of color television. According to Mr. Atcherly, the film may be requested for distributor or dealer meetings through the local Sylvania electronic products sales representative.

• • •

Walter W. Watts, Executive Vice-President of the Radio Corporation of America, said that new electronic developments—now in the laboratory or just emerging—will have a decisive impact on American living. Speaking to a luncheon meeting of Findlay civic and business leaders, the RCA executive foresaw such devices as magnetic TV tape recording for replay at home of favorite television programs, electronic refrigeration and air conditioning, mural television and a variety of new devices for industry, medicine and education. As a result of these and other developments, Mr. Watts said that the electronics industry would increase its present sales volume by more than 50 per cent by the next decade, exceeding 18 billion dollars by 1964. ■■

BEST IN




SOUND

Made to the highest requirements of leading set manufacturers, Tung-Sol Tubes are perfect replacements for all sets. Bank on Tung-Sol's brand of quality—tops in the industry. It's the sure way to avoid callbacks that eat into profits. Tell your supplier you'd rather have Tung-Sol tubes.

Blue Chip Quality

TUNG-SOL®
RECEIVING TUBES

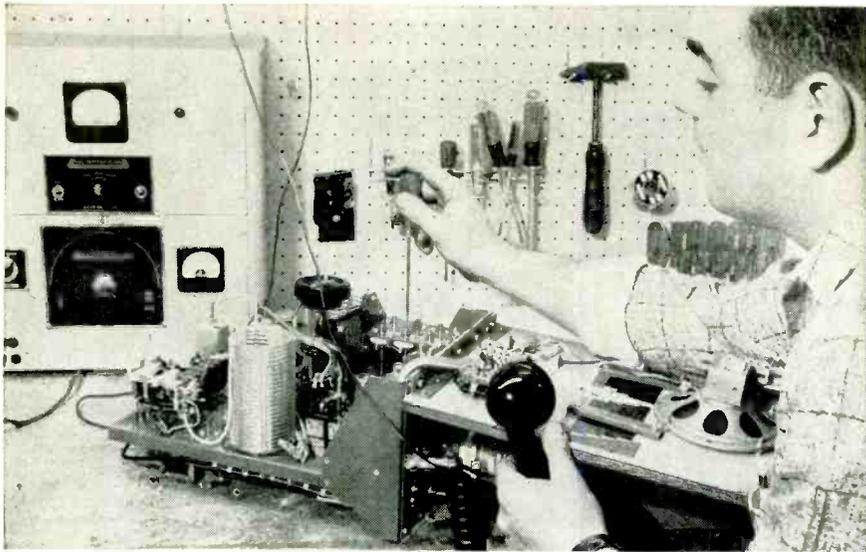TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.



► Fig. 1—Compromise measures such as coil-clip tuning are still used, as seen in this photograph, for reasons of economy.

MARINE ELECTRONIC BUSINESS

RADIO TELEPHONE CHARACTERISTICS

Part 4

No matter how experienced a service engineer may be with other types of radio equipment, he is likely to find marine radiotelephone a peculiar breed of cat. In fact, I've heard expressions of astonishment from technicians in practically every other electronic field, and even from amateur radio operators, over various design and constructional features of marine radio communications equipment. From some of the criticism and comment, one might think that the designers of marine equipment were out in the boondocks when the brains were passed around.

Actually, however, there is a sound reason for the way marine radiotelephones are built. This will be easily understandable after a look into the background, and the technical and economic requirements.

The first commercial marine radiotelegraph transmitter I ever worked on gave me the "willies." It was a self-excited oscillator, covering the band between 300 and 500 kc, and the transmitting frequency was adjusted by changing the position of clips and flexible leads on the oscillator tank coil. Fine tuning was performed by bending the flexible leads slightly. When the tuning for one channel was changed, of course, it affected the adjustment on the other channels as well. This was a trying trick, especially with an FCC inspector looking over your shoulder, wave-meter "at the ready." Mind you, this set was a first-line commercial outfit.

The author talks of early marine transmitter design, and discusses modern trends.

by **ELBERT ROBERSON**
Marine Electronics Consultant

Later, when radiotelephony arrived on the maritime scene, I tuned up my first marine radiotelephone. Again I was aghast to find that transmitter tuning was accomplished by changing the position of clips on coils. This also was a first-line commercial product. Not only would no self-respecting amateur have had it in his shack, but the FCC would have prohibited him from putting it on the air.

This is not meant to imply, by any means, that all radiotelephones are designed in this fashion. However, it would be a very rare instance in which factors, other

than excellence of design, did not, in a somewhat similar manner, alter the final outcome of the designer's dream.

The market for marine radiotelephones is very limited, compared to that for television or table-model radios. A run of a few-hundred radiotelephones is a substantial one. From this standpoint it is not so amazing that marine radiotelephones may possibly be deficient in some theoretical respect. Indeed, it is amazing that they have as many excellent features as they do at such a comparatively low price. Competition, and the roving ear of the FCC, which has just recently noticed a little splatter and a few harmonics around marine frequencies, have served to shake out most of the "bugs," and today's equipment is about as cleanly designed and as reliably put together as one could hope. This has been made possible only by a

step-by-step evolutionary development, bringing out small improvements from time to time on the old ideas and traditional designs, and not from any dazzling and expensive exploitation of brand-new concepts. Therefore, to understand what we have today, it helps to look back a little.

One of the first and most popular pieces of equipment for this service consisted of a "Vibrapak" power supply, to change the 6 or 12-volt battery input to as high as 300-volts *dc*; a 4-tube superheterodyne receiver, and a 2-tube transmitter.

Circuits of this early telephone were simple and straightforward and designed to operate with pre-set adjustments. The operator needed no technical knowledge. A knob on the front panel changed operation of both transmitter and receiver to any one of four different operating frequencies, which provided for two ship-to-ship channels, one channel to the Coast Guard, and one channel for shore-telephone communications.

Inside the cabinet, the receiver was entirely conventional, with the exception that the superheterodyne mixer circuit was crystal controlled. The bandswitch selected the proper crystal for the channel to be received, and also selected pre-set input trimmer capacitors, which on installation of the equipment were peaked for best reception on the different frequencies. Loudspeaker reception was provided, or the receiver

output could be switched to a conventional telephone handset earpiece.

The transmitter consisted of a single oscillator tube in a tuned-plate crystal-controlled circuit. The band-switch selected the crystal for the desired transmitting channel. A single coil was used in the transmitter output circuit, and the capacitance of the antenna itself was used to establish plate resonance. Different coil taps for the antenna and the plate of the oscillator tube were selected by the bandswitch for tuning, and at the same time established some sort of impedance match.

The modulator used a single tube of the same type as the *rf* oscillator, and was transformer coupled to its plate. Audio from the carbon microphone was impressed on the modulator-tube grid through a step-up transformer. The high level output of the single-button carbon microphone obviated the need for a speech amplifier, and sufficient output was obtained for a high degree of modulation under optimum transmitter loading adjustments.

A push button on the handset operated a multi-contact control relay, which transferred "B" voltage from the receiver to the transmitter circuits, and switched the antenna likewise.

With all due respect for the dead, and for the fact that this type of equipment gave long and faithful service in its time, it possessed several features which have fortunately passed out of favor. For example, it has since been determined that the direct modulation of an oscillator tube is bad practice, since on negative modulation peaks oscillation may cease entirely, giving rise to serious distortion products.

Using the antenna as a reactive element in the transmitter tuning circuit was bad enough, and direct connection of the antenna to the plate circuit of the oscillator tube compounded the probability of spurious emanations from this type of rig. Not only was such a circuit potentially a source of interference, but it was also difficult to tune if the antenna did not have the proper impedance to serve its multiple purpose on a number of different frequencies. Accord-

[Continued on page 51]



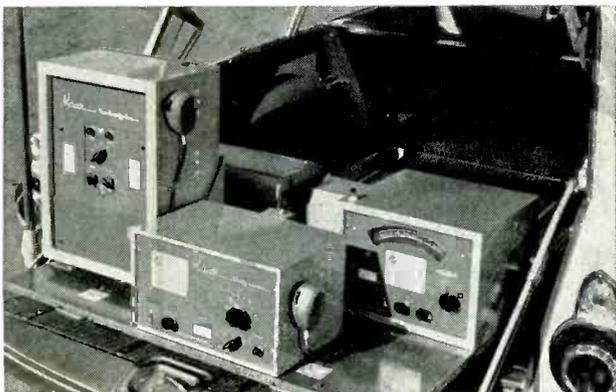


Fig. 2—A display showing the Kaar line of radiotelephones—low to high power.

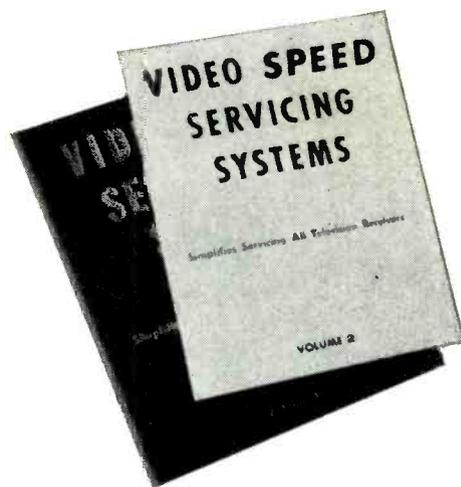

VIDEO SPEED SERVICING SYSTEMS

CUT SERVICING TIME

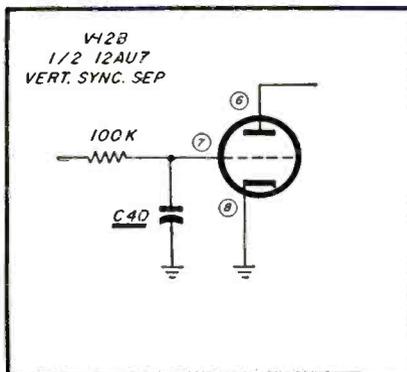

Mfg: Emerson

Chassis No. 120162-A

Card No. EM162-6

Section Affected: Sync.

Symptom: Horizontal pulling, and vertical rolling.

Cause: Defective component.

What To Do:

Replace: C40 (47 μ f), which is leaking.

Time is money to servicemen. Thousands of servicemen who have bought Vol. 1 VSSS report that it is a time-saver—and more important—it helps them pinpoint their trouble-shooting so they can service sets more efficiently.

Here is one typical VSSS data sheet. VSSS Vol. II contains more than 600 and covers all the most-serviced TV models now in use.

- Volume 2 of VSSS is completely new and does not cover any of the items published in volume 1.
- Volume 2 of VSSS contains most of the data sheets published since May 1953 plus several hundred new data sheets that have not been published heretofore and which will not be published anywhere else.
- Although published as a hard paper cover bound volume each page in VSSS Vol. 2 is marked so the pages can be inserted into a loose leaf ring binder or into our VSSS Vol. 1 cloth-covered ringbinder edition.

Order Your Copy Today

CUT OUT AND MAIL

COWAN PUBLISHING CORP., 67 WEST 44TH STREET, NEW YORK 36, N. Y., DEPT 9

Please send me postpaid Video speed Servicing Systems Vol. 1 in Paper Bound Edition for \$2.95
 " " " " " " " " " " Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95
 " " " " " " " " " " Vol. 2 in Paper Bound Edition for \$2.95


My Check for \$..... is enclosed. (If you reside in New York City add 3% to cover city sales tax.)

Name _____

Address _____

City _____ Zone _____ State _____

Send today
for your complete
catalog

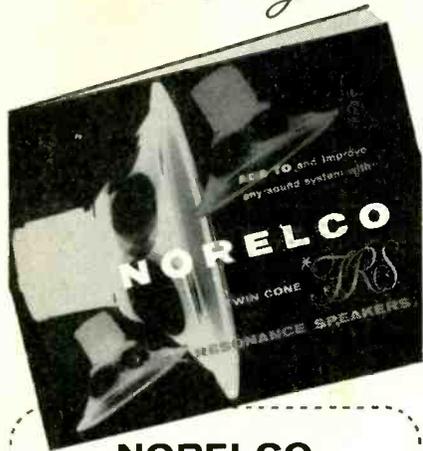

NORELCO
**F.R.S. SERIES*
**FULL RESONANCE
TWIN-CONE
SPEAKERS**



Norelco's twin-cone speakers are designed to meet the problem of high and low frequency dispersion in a single speaker. The large (heavy) cone is designed to produce good bass while the small (light) cone radiates higher frequencies.

Eliminating operating inefficiency experienced in multiple speaker cross over systems, Norelco's twin-cone is driven by a single voice coil—producing a flat response with exceptional reproduction of transients. Based on economy and value any one of the Norelco FRS twin-cone speakers is your best choice. If your neighborhood dealer does not stock Norelco write direct to North American Philips Company, Inc. giving your dealer's name and address.

ADD TO... and improve any
sound system with **Norelco**[®]
*FULL RESONANCE SPEAKERS



Write today to Dept. E-10 for brochures and prices of these unique speakers.

North American Philips Co., Inc.
100 E. 42nd Street, New York 17, N. Y.

Color TV Luminance Sections

[from page 15]

Retrace Elimination

Retrace, both horizontal and vertical, presents problems in color TV reception. Although the vertical retrace problem is the same in color receivers as in black and white, horizontal retrace presents additional problems in color receivers.

In receivers using *dc* restorers, such as the CBS 205, the presence of a burst at the demodulator will produce a recovered square wave not unlike a second horizontal sync pulse. Should this pulse exceed the horizontal sync pulse in amplitude (and the FCC specifications allow this to happen) the restoration action on the blue gun will be in error because the restorer sets up at the recovered burst amplitude instead of the horizontal sync pulse amplitude. The consequence of this action is that the picture will appear too blue. The reason that the blue color is affected more than red and green during this sequence of events is that the burst phase is recovered at greatest amplitude along the B-Y axis as compared to any other axis. This is overcome by removing the burst from the chroma signal prior to demodulation. This removal is effected by adding a horizontal blanking pulse to the chroma amplifier.

In direct coupled systems which do not require *dc* restorers, and where horizontal retrace blanking is not employed, the burst is recovered as a strip of color information in the demodulator section, and will show up as a faint greenish yellow strip occupying about 25% of the raster to the left of center. On bright scenes this coloration is effectively masked; however, on dark scenes it becomes faintly perceptible.

Horizontal blanking may be performed either by the addition of a blanking pulse to the screen grid of the video amplifier or to the screen grids of the picture tube.

In the circuit used in *Fig. 2* horizontal blanking is effected by applying a horizontal pulse to the screen grids of the picture tube. No vertical blanking is used because a resistive matrix applying both horizontal and vertical blanking pulses to the picture tube screens results

in a seepage of horizontal information into the vertical sweep system, which in turn produces poor interlace.

In *Fig. 3* vertical retrace blanking is performed by feeding a positive pulse from the vertical output transformer to the CRT cathodes, thus biasing the picture tube beyond cutoff during the vertical retrace time.

Horizontal retrace blanking is obtained by feeding horizontal pulses into the chroma channel for this purpose. A more detailed explanation of this circuit will appear in a subsequent circuit analysis of this section.

In *Fig. 4* horizontal blanking is accomplished by connecting the screen grid of the second video amplifier to the output of a blanking amplifier. The latter provides a high negative horizontal pulse derived from a tap on the horizontal output transformer. This high negative pulse cuts off the tube, causing the CRT cathodes to go positive enough to produce picture tube cutoff. Vertical retrace blanking is effected by feeding a positive vertical pulse from the vertical output circuit to the CRT cathodes.

Delay Line Circuits

One of the interesting aspects of video amplifiers in color TV receivers is the manner in which a delay line is connected into the circuit. At first glance it might seem that this component is merely connected into the luminance signal path (as shown in *Figs. 2, 3 and 4*) with no regard to the impedance characteristics of the input and output circuits. This is not so, for the delay line is essentially a transmission line, and as such, its impedance characteristics, as well as the source and load impedances to which it is connected, must ideally be taken into consideration if line reflections are to be avoided.


As a practical consideration some receivers (CBS 205) have been built using a proper termination only at the load end. Terminating in this manner prevents reflections from the load end and obviously there can be no subsequent

[Continued on page 47]

ONE SPEAKER THE NORELCO

**F.R.S.*

for improving
audio quality

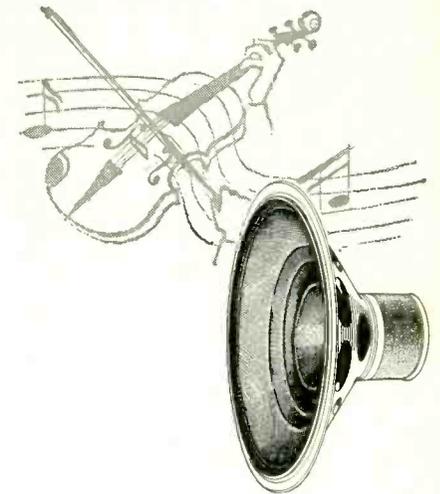


Unexcelled performance at a moderate price. Here is your invitation to a treat in superior performance.

Features which make these Norelco FRS speakers distinctive are based on faultless design, quality materials and the best in workmanship.

Exclusive alloy magnet steels, select cone materials, hand wound voice coils and individual alignment—all contribute to "Living Sound", the luxury of listening to realistic reproduction through Norelco Full Resonance Speakers.

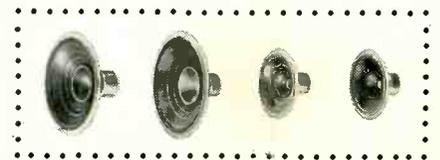Priced from \$59.98 to \$6.75 in all standard impedances and sizes from 12 inches to 5 inches.



ADD TO... and improve any
sound system with **Norelco**[®]
*FULL RESONANCE SPEAKERS



Send to Dept. E6 for more details

North American Philips Co., Inc.
100 East 42nd Street
New York 17, N. Y.

MERIT

first in exact replacement



MDF-77 for exact replacement in 32 Admiral chassis, over 220 models; provides exact lead color coding and exact network. Another in the complete line of exact transformers, yokes and coils. Merit is the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.

MERIT

MERIT COIL AND TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 40, ILLINOIS

Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-1


Section Affected: Pix

Symptoms: Range of lock-in action of horizontal hold control is too small and thus requires more or less critical adjustments.

Reason For Change: Circuit improvement.

What To Do:

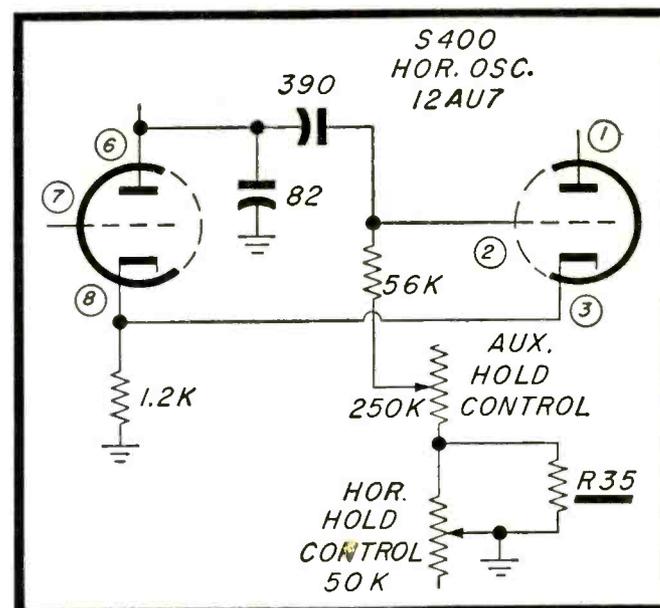Change: Resistor R35 (39K) across the horizontal hold control to 82K.



Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-2


Section Affected: Pix

Symptoms: Range of contrast control is too small requiring too exact an adjustment.

Reason For Change: To improve circuit operation.

What To Do:

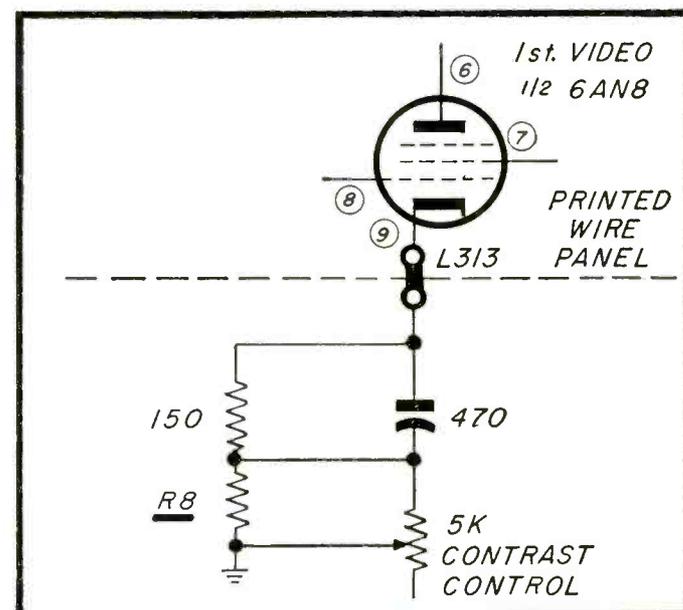Remove: Resistor R8, 2200 ohms.
Change: Contrast from 5000 ohms to 1500 ohms. (Philco Pt. No. 33-5572-31).



Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-3


Section Affected: Raster and picture


Symptoms: When picture information is removed by station or channels are changed a motorboating takes place. The picture sometimes loses horizontal and vertical sync.

Reason For Change: Circuit improvement. The changes are incorporated to produce a more stable in-sync raster by altering age filtering time constants.

What To Do:

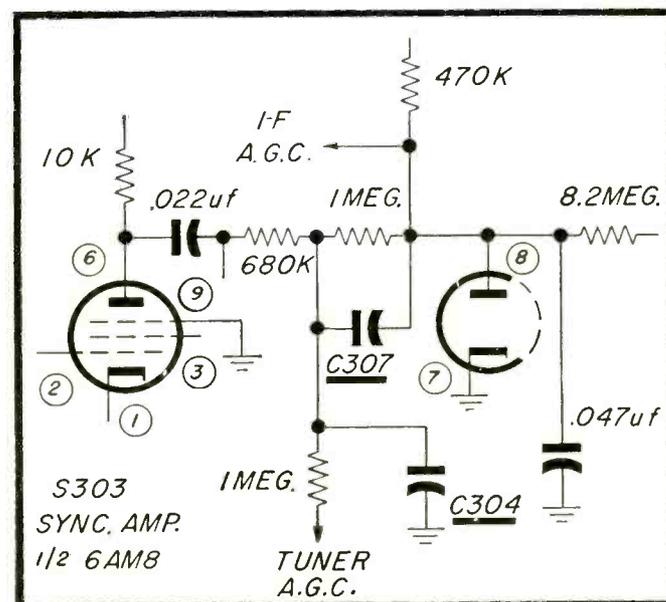Change: C307 from .01 μ f, to .006 μ f, 400 volts, C304 from .1 μ f to .15 μ f, 200 volts.



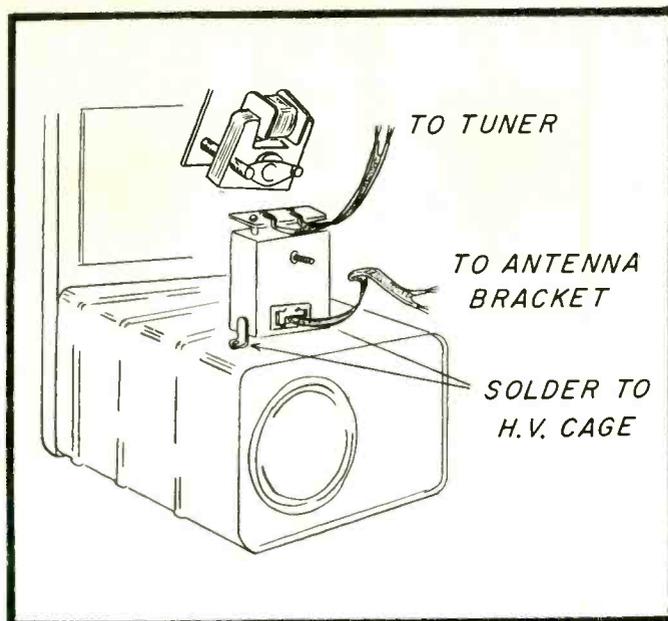

Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-4

Section Affected: Pix


Symptoms: Beat patterns and interference in picture in areas where 40 mc police or doctor call transmitter interference is present.

Reason For Change: Circuit improvement.

What To Do:

Install: Tunable vhf antenna trap, Philco Pt. No. 420-0015. Solder the trap to the high voltage cage using the mounting tabs provided.

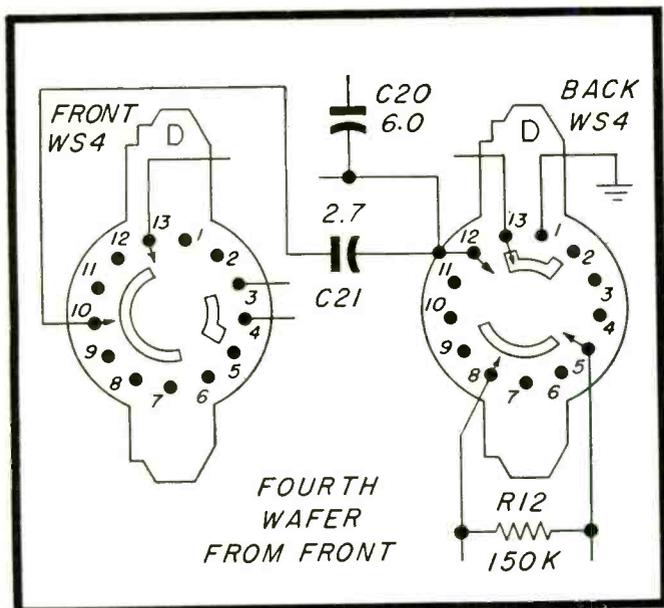Note: The traps are pre-tuned to 42.5 mc. Tune the trap if necessary to obtain minimum interference while the interfering signals are being experienced. It is suggested that a plastic tuning tool be employed.



Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-5

Section Affected: Pix


Symptoms: A broad overshoot in picture on Channel 2, 3 or 4. To reduce the overshoot it is possible to tune the picture into the smear condition, but this produces a lack of sharp detail.

Cause: Improper impedance match between tuner and antenna.

What To Do:

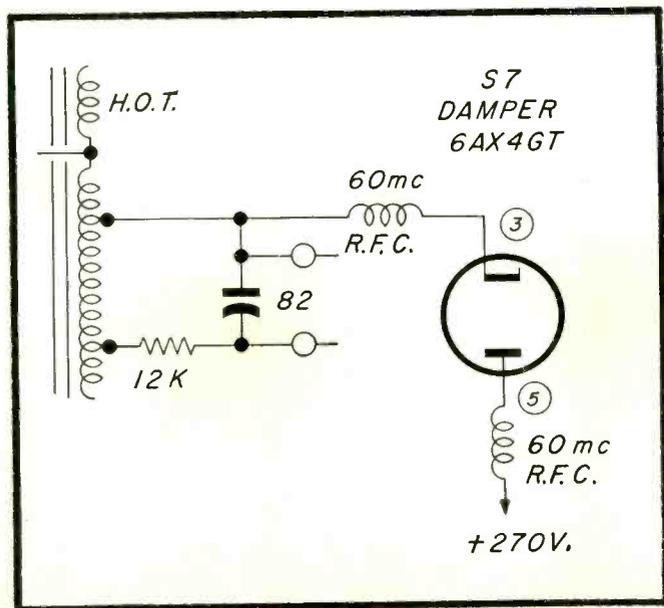1. If the condition is moderate reduce the length of lead-in from the antenna to the set by an $\frac{1}{8}$ of a wave length of the channel most affected. Removal of an additional $\frac{1}{8}$ of wave-length may provide further improvement, allowing the receiver to tune smoothly to a point where no overshoot is present.
2. In extreme cases, to improve the match between the antenna and the tuner install a 1000 ohm resistor across the low channel coils. Remove the tuner cover and wire the 1000 ohm resistor across C21, the 27 μmf low band matching capacitor.

Note: Be sure to use short leads in wiring the resistor across the condenser.



Mfr. Philco Chassis No. TV-440, 444

Card No. PH 440-6

Section Affected: Pix and raster

Symptoms: No high voltage, no picture or raster, boost voltage is not normal. There is usually repeated failures of 6AX4GT damper tube.


Cause: 6AX4 damper tube breaks down (shorts internally).

What To Do:

Change: Damper tube from a 6AX4 tube to a 6AU4GT for more reliable operation and less frequent tube failures.

LOOK FOR THIS RACK

at your Jobber . . .

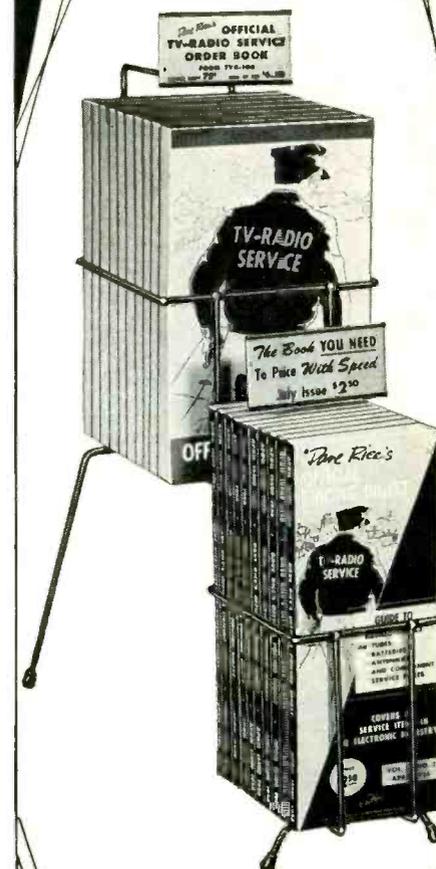


In this rack you will find
The Biggest Service Help
The Largest Value
In These Perfect Partners

Dave Rice's Official Pricing Digest—a quick check for over 60,000 prices—revised 4 times every year. Pocket sized.

and Dave Rice's Official TV-Radio Service Order Book which provides separate listings for picture tubes, receiving tubes, parts and components, serial numbers, labor and state and local taxes. 5½x8½—50 sets of triplicate orders—carbons bound in.

ELECTRONIC PUBLISHING CO. INC.
180 North Wacker Drive Chicago 6, Illinois

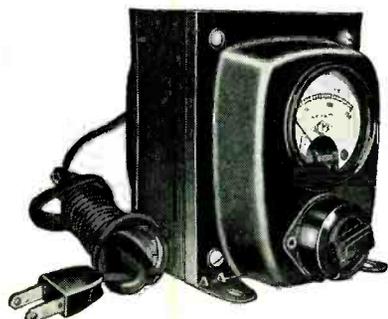**WHEN
PERFORMANCE
IS
AFFECTED BY
LOW VOLTAGE
CONDITIONS**



**SELL THIS
ACME ELECTRIC
VOLTAGE
ADJUSTOR**

TV sets are designed to operate best when voltage holds closely to 115-117 volts. Overloaded supply lines (the power industries greatest problem) may result in a voltage drop of 10 to 15% at certain times of day. Usually the TV set will function in a fashion under such low voltage conditions but with a great strain on its components. For example; narrowing of picture, output stage tube life shortened, frequent burn-out of filaments, fuzzy focus have been traced to lack of proper voltage.

These conditions can be corrected with an Acme Electric T-8394M Voltage Adjustor. Simply plug-in to convenient outlet. Plug-in television set cord into female receptacle built into adjustor. Voltmeter indicates output voltage. If voltage is incorrect turn regulating control until proper voltage is reached for best performance. Voltage range 95 to 125 volts. Tell your supply dealer you want the Acme Electric T-8394M. No other so compact, practical, inexpensive.

ACME ELECTRIC CORPORATION
4610 WATER ST. CUBA, NEW YORK

Acme Electric
TRANSFORMERS

Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-1


Section Affected: Pix

Symptoms: Horizontal jitter.

Cause: Defective component.

What To Do:

Replace: C257 (.1 μ f) which is open.

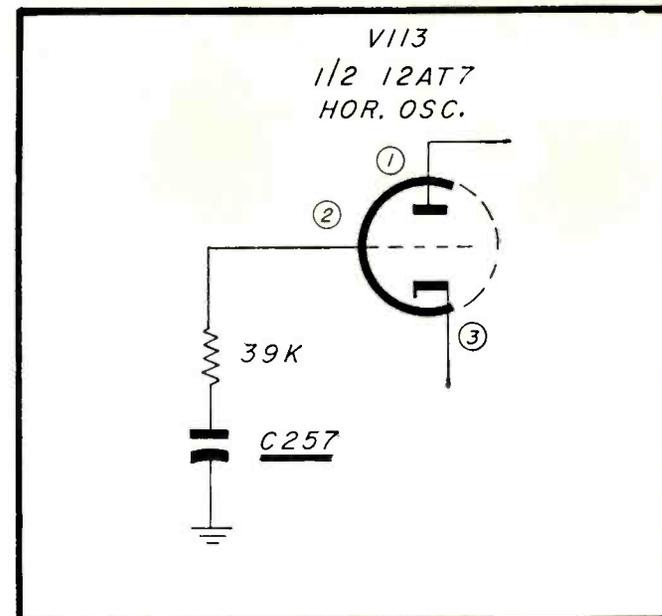

Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-2


Section Affected: Raster

Symptom: Excessive height.

Cause: Defective component.

What To Do:

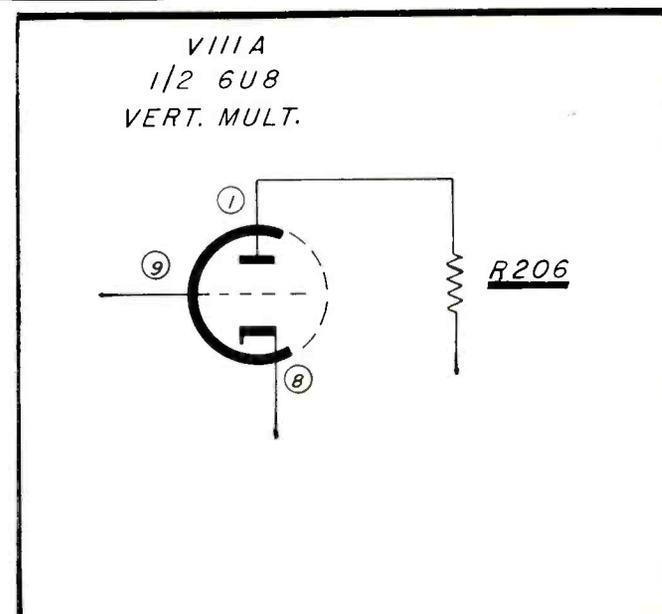Replace: R206 (5.6 meg.) which has decreased in value.



Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-3


Section Affected: Pix and sound.


Symptoms: Pix and sound flutters.

Cause: Defective component.

What To Do:

Replace: C213 (.5 μ f) which is open.

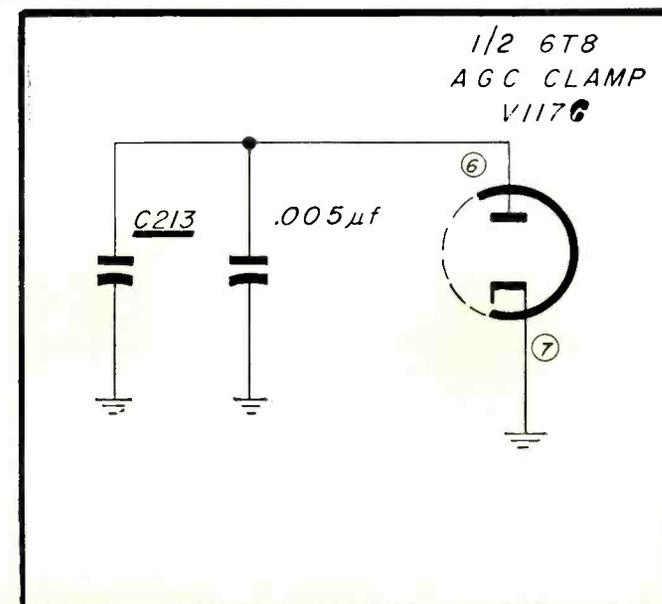

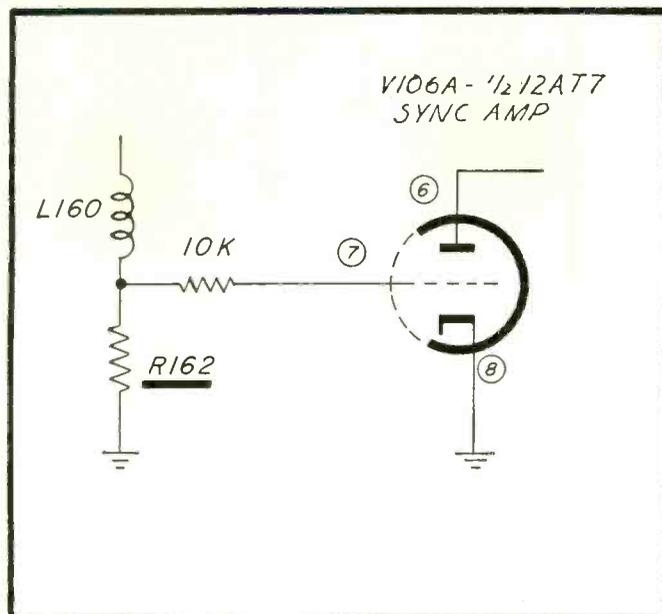

Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-4


Section Affected: Pix

Symptom: Wiggles in background.

Cause: Defective component.

What To Do:

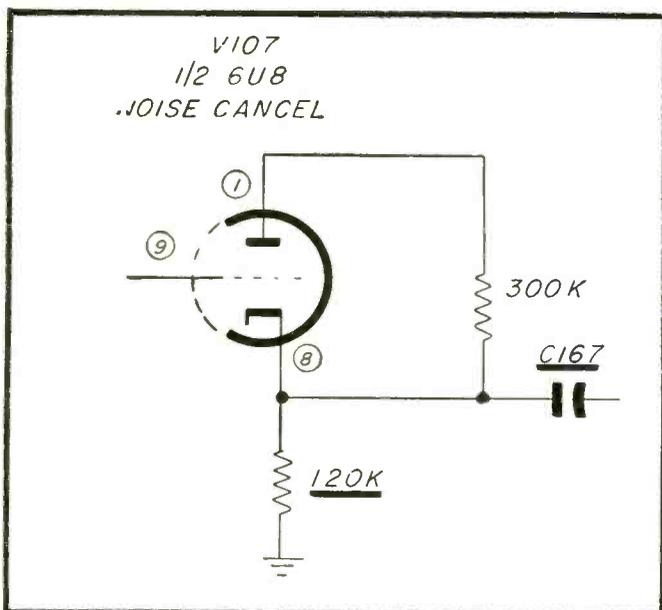Replace: R162 (3.3K) which has decreased in value.



Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-5


Section Affected: Sync

Symptom: Weak composite sync.

Cause: Defective component.

What To Do:

Replace: C167 (.15 μ f) which is leaky.

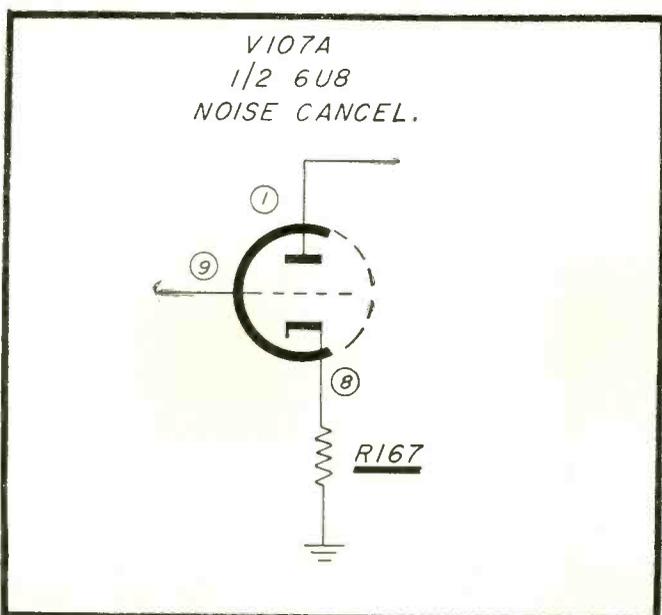

Mfr. GE Chassis No. 21C130—"O" Line

Card No. GEO-6

Section Affected: Pix


Symptom: Picture tearing.

Cause: Defective component.

What To Do:

Replace: R167 (120K) increased in value.

COMING NOV. 15

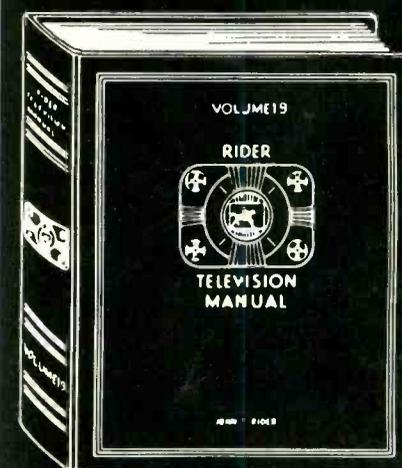

RIDER'S TV 19

only \$19.80

tell your jobber to
reserve your copy now!

IF YOU WANT THE BEST IN TV SERVICE INFORMATION

| | | |
|---------|----|----------|
| RCA | ON | EMERSON |
| PHILCO | | MOTOROLA |
| ADMIRAL | | CROSLEY |
| GE | | ZENITH |

ASK YOUR JOBBER ABOUT

RIDER'S **SDO**
("single diagram only")

ONLY 50¢ PER CHASSIS

JOHN F. RIDER Publisher, Inc.
480 Canal Street, New York 13, N. Y.

Luminance Sections

[from page 42]

reflections from the incorrectly terminated receiving end.

An analysis of the impedance elements connected to the input and output terminals of a delay line will reveal that these input and output load components are generally selected to provide an impedance match to the voltage sources and input circuits to which they are connected. The delay line must then have a characteristic impedance equal to these input and output loads. Failure to adhere to these conditions will result in a waste of available signal strength, and unstable circuit operation due to reflections.

It is for the above reasons that various components are seen connected in color video amplifiers that are not otherwise seen in black and white video systems. The typical impedance range of delay lines commonly used in TV sets today is between 1500 and 4100 ohms. Although the higher impedance lines make for greater gain characteristics they are more difficult to make and harder to compensate for the bandwidths required (approximately 3.5 mc).

In Fig. 3, the input load to the delay line is shown as $R403$ (1.5K), and the output load as $R405$ (1.8K) in parallel with $R182$ (4.7K), the combination of which is equal to 1.3K ohms. In Fig. 4 the input load is shown as $R127$ (1.2K), and the output load is the contrast control, $R134$ (2K).

In Figs. 3 and 4, low impedance lines are used and the resultant lower gains realized necessitate the use of a 2 stage amplifier.

The need for an additional stage of video amplification is overcome by the insertion of a high Z delay line (4.1K) in the detector circuit as shown in Fig. 2. Here the detector impedance matches the source requirements of the line, and the terminating line resistance becomes the effective detector load. In this manner, insertion of a delay line into the video system introduces negligible loss of the Y signal. Thus, systems using this design can employ a single video amplifier to adequately drive the picture tube. [To Be Continued]

Burton Brown / New York



Examine it today

Being introduced by leading Electronic Parts Distributors

PYRAMID ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, New Jersey

Bull's-eye every time!



We hit the target again . . .
with this new, modern version of the
most wanted service-test instrument.

Pyramid introduces the CRA-2 Capacitor-Resistor Analyzer, a versatile, up-to-date, moderately priced test instrument. The CRA-2 is the perfect multi-purpose analyzer for the technician, serviceman and engineer, in industrial and military electronics, black and white, and color television, and all related fields.

The guesswork has been removed from circuit trouble shooting. When making leakage-current measurements, the values are read directly from the meter while the rated operating voltage is applied to the capacitor. A vacuum-tube ohmmeter circuit displays accurate insulation-resistance values on the meter for many types of capacitors. The extended range calibrated power factor control permits power factor measurements of electrolytic capacitors rated as low as 6 volts DC working and as high as 600 volts DC working. This special "QUICK CHECK" circuit performs rapid "IN CIRCUIT" test for short, open, intermittent high RF impedance and high power factor without removing or disconnecting the component from its operating circuit.

FEATURES

- "Quick Check" in circuit test for Open Circuits. Short Circuits. Intermittents. High RF Impedance. High Power Factor.
- Speedily and accurately checks: Capacitance. Power Factor. Resistance. Insulation-Resistance. Leakage Current.
- Precision meter for accurate readings of leakage current, applied voltage and insulation resistance.
- Combination Wien and Wheatstone bridge.
- Accurate vacuum-tube meter circuit.
- Parts of the highest quality are used. Wire and wiring meet military specifications.

list prices of tube type 6BA7 vary considerably. One of the eight brands has a list of \$2.60, one lists at \$2.80, two list it at \$2.90 and four list price it at \$2.95.

It is quite possible and very probable that a serviceman will have several different brands of tubes in his caddy—and should he happen to use the brand of 6BA7 that lists at \$2.60 and charge \$2.95 for it, he is in effect over-charging the customer by \$.35. By the same token, if he uses one of the 6BA7 brands that lists at \$2.95 and charges the customer only \$2.60, then he is gypping himself. When customers are over-charged, even unwittingly, grave consequences can result and the serviceman will probably be labeled

a “gyp.” When servicemen undercharge because they rely on memory or do not refer to accurate price tables, they lose profits they should not lose.

All tube makers list price their 6SJ7 tubes at \$2.25, but not so 6SJ7GT's. Six of them list the latter type at \$2.15 while two list it at \$2.25. The 6SJ7 and 6SJ7GT types, so similarly numbered, can easily confuse a serviceman and get him “in dutch” with a customer who is overcharged because the serviceman carelessly relied on memory and charged \$2.25 when using a brand and type which actually lists at \$2.15.

Refer to Rice's “Official Pricing Index” and you'll
[Continued on page 52]

The Best Thing About the “Cure-all”



...was the Professor's pitch!

Yes, sir, the old time medicine showman sure made some high, wide and handsome claims about his particular brand of “cure-all”. Trouble was, his elixir's performance rarely matched his claims. That didn't matter to the Professor, though, he'd made his pitch and was miles away by the time the customer found he needed a specialist. Now, today, most of us try to keep our customers happy — keep them coming back. And most of us realize that today's “cure-all” claims are just as hard to swallow as the old timer's snake oil . . . nobody really profits from a “cure-all” substitute except the “Professor”! It stands to reason that when a phonograph manufacturer, for instance, puts a pickup cartridge into his product, it's because *that particular cartridge* is best for the job. No substitute is *exactly* the same. So, for highest performance, for full profit markup, for complete customer satisfaction, don't rely on “cure-all” substitutes! *Always* replace with *Astatic original and direct replacement cartridges.*

**ASTATIC IS THE WORLD'S ONLY COMPLETE
LINE OF PICKUP CARTRIDGES!**

Leader with Originals, First with Replacements.

NEW! Ask your distributor for the latest Astatic Cartridge Cross Reference and Needle Listing CRC-56.

THE **Astatic** CORPORATION, CONNEAUT, OHIO
KNOWN THE WORLD OVER
IN CANADA CANADIAN ASTATIC LIMITED, TORONTO, ONTARIO
Export Sales Representative: 401 Broadway, N.Y. 13, N.Y. • Cable — ASTATIC, N.Y.



Manufacturers, Distributors and Users of Electronic Equipment

Thousand of financially sound, qualified electronic servicemen and service organizations are desirous of affiliating themselves with manufacturers as official service depots or service representatives. If you are interested in employing the services of these capable experienced technicians on a permanent or contract basis, please advise us of your needs and requirements, and we will forward you the names and addresses of such individuals and organizations in any area you specify.

This is a free service of Service Dealer and Electronic Servicing.


Service Dealer and Electronic Servicing

COWAN PUBLISHING CORP.

67 W. 44 ST., DEPT. S, N.Y. 36, N.Y.

*ANOTHER COWAN PUBLISHING SERVICE

**W
A
N
T
E
D**

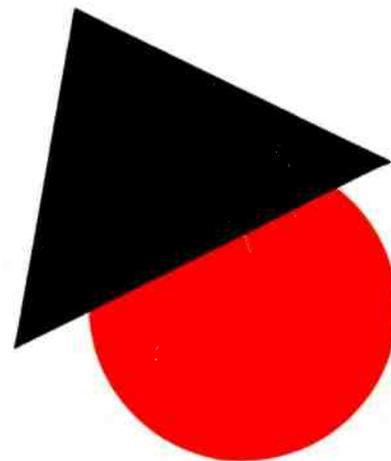

AUTO RADIOS—PONTIAC

[from page 17]

the correct station is not tuned accurately readjust the selector tab as needed.

Removal of Tuner Section

1. Disconnect the "A" battery and dial light leads from the fuse block located under the steering column. (Current is supplied through a 7½ amp. AGW type fuse.)

2. Remove the antenna lead located on the righthand side.

3. Disconnect the three prong plug from the speaker unit.

4. Disconnect the single filament lead at the plastic connector.

5. With a 7/16" wrench remove the bracket mounting bolt, located at the right side directly above the glove compartment.

6. With an allen wrench, loosen the set screws in the front panel control knobs; remove the knobs and controls.

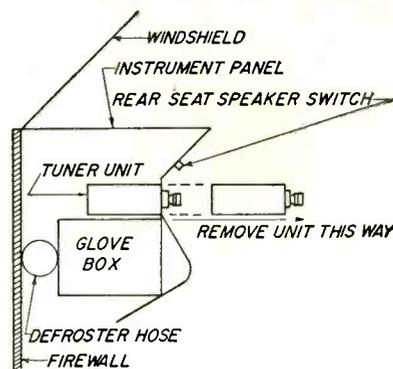


Fig. 5—Tuner unit is removed by bringing it forward and out.

NOTE: On the De Luxe push button tuner jobs, the dummy knob (right side behind manual tuner) is threaded and screws on the control.

7. With a 7/8" deep socket remove the two mounting nuts.

8. Open the glove compartment door and remove the front mounting panel.

9. With a 7/16" wrench remove the two front mounting bolts (see Fig. 4).

NOTE: If the car is equipped with rear speakers, remove the two screws holding the switch to the unit and hold aside for removal of the tuner unit.

10. Bring unit forward and out though the front (see Fig. 5).

Removal of Speaker Amplifier Section

1. Remove the two phillips head screws in the lower edge of the instrument panel.

2. Remove the single phillips head screw in the left side near the glove compartment.

3. Push unit forward, down and out.

Service Hints

Complaints of excess fading, or decrease of volume when the antenna is held have been traced to broken wires in the antenna, r. f., or oscillator coils. The wires occasionally break at the output junction. Disconnect the output leads and test for continuity with an ohmmeter. If open, remove the screws and leads at the fibre board holding the coils and slide out. Complete coil should be replaced.

If a machine gun-like action is produced when the selector bar in electronic tuners is depressed, look for trouble in the gear train of the tuner. These gears become worn or loose on shafts. Remove and replace the gear train unit. Do not try to repair it. ■■

TOP QUALITY PARTS

FOR RADIO AND T.V. SERVICEMEN

SELENIUM RECTIFIERS

300 M.A.—79c ea. 400 M.A.—1.19 ea.
350 M.A.—99c ea. 500 M.A.—1.39 ea.

FILTER CONDENSERS

RADIO PACKS:

40-20-20 MFD-150V, 100-25V 29c
50-30 MFD-150V 20 MFD, 25V 29c
40-40 MFD-150V, 250-25V 29c
60-40-40 MFD-150V, 20-25V 29c

T. V. PACKS:

250 MFD-150V, 50 MFD-150V 29c
250 MFD-150V, 120 MFD-150V 50-25V 29c
140 MFD-300V, 40 MFD-250V, 100-50V 39c
140 MFD-350, 5 MFD-30CV,
200-200V, 30-150V 39c

SERVICEMAN'S SPECIALS

50 ea. Carbon, ¼ & 1 watt resistors 49c
12 ea. W.W. resistors, 5 to 15 W. 98c
10 ea. assorted pots 49c
25 ea. Assorted Condensers 49c

TUBE SPECIALS

| | | |
|------------|------------|------------|
| 6AC7 —.65 | 6SJ7 —.55 | 6C4 —.28 |
| 6AK5 —.49 | 6AG7 —.49 | 6V6G —.29 |
| 6SN7 —.69 | 12SH7 —.39 | 6SL7 —.69 |
| 2AF4A —.98 | 6J6W —.64 | 6AF4A —.98 |

SPEAKERS

4" P.M. SPEAKER98
10" P.M. HEAVY SLUG, INDIVIDUAL
BOXED, R.C.A. BRAND 2.49

No order Too Small. Merchandise shipped within 24 hours of receipt of order. 25% deposit required with order. F.O.B. Brooklyn.

FEDERATED TELEVISION

MART, INCORPORATED
513 Rogers Ave., Dept. R, Brooklyn 25, N. Y.

NEW PROFIT MAKER...

Electenna

AUTO RADIO REPLACEMENT ANTENNA

Here's sales potential! Millions of car owners will welcome new Electenna... first and only replacement antenna that installs fast, using present mounting and wiring. Boosts radio reception; up to 100% gain over standard 54" antenna fully extended. Beautiful design, chrome finish. Short height avoids damage.

Retails profitably for you at..... **\$5.95**

COILTENNA
Coil only without antenna. Easily installed. Gives same improved performance. Packed in colorful self-service counter display container. Retails at only \$3.95.

Dealers! Jobbers! Write today!

ELECTENNA DISPLAY BOARD
Large, colorful counter display given to dealer does outstanding self-service selling job!

Another Quality Product of **Electrend** **PRODUCTS CORPORATION**
St. Joseph, Mich.
Electronic Division

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF SERVICE DEALER and ELECTRONIC SERVICING, published monthly at New York, N. Y. for October 1, 1956.

1. The names and addresses of the publisher, editor and business manager are: Publisher, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y. Editor, Samuel L. Marshall, 262 Sullivan Place, Brooklyn 25, N. Y.; Managing Editor: None; Business Manager, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

2. The owner is: (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.) COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.; Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and beliefs as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

(Signed) S. R. COWAN, Publisher
Sworn to and subscribed before me, this 18th day of September, 1956.

EMANUEL M. VIRSHUR, Notary Public

Sandy Says!
Be Modern with an

Anchor V-500-VTVM!

- Simpler to operate
- Easier to maintain
- No battery

SIZE: 6½" x 9¼" x 4½"

Latest type tubes and circuitry. Single control selects range and function. Has 4½" full view meter, separate 3-volt AC scale, zero centering for TV and FM alignment, DB scale and burnout proof meter circuit, housed in durable carrying case. Completely factory wired, tested and warranted.

only **\$47.50** net
AT YOUR
DISTRIBUTOR

anchor products co.
ELECTRONIC COMPONENTS
2712 W. Montrose • Chicago 18, Ill.

MARINE ELECTRONICS

[from page 41]

ingly, many of these transmitters would modulate upward on one channel, and downward on the next, and there wasn't much that could be done about it.

Since then, transmitters have all become more or less respectable. Among the refinements are that separate oscillator and *rf* amplifier tubes are used in the transmitter, and antenna-tuning and coupling circuits are separate from the *rf* amplifier plate tuning circuit. Negative modulation peaks are limited



Fig. 3—Ray Jefferson Model 460

by one means or another, harmonic radiation is reduced to a level comparable to that for other services, and audio band width has been drawn into the limits necessary for voice transmission. However, there is still a tendency toward impressing microphone voltage directly on the modulator tubes, with speech amplifiers being used only in more elaborate sets.

While the receiver design in modern inexpensive radiotelephones is basically the same as that originally used, except for new miniature tubes, more efficient *if* transformers, printed circuits, and compact components, the larger outfits have several improvements. Such improvements are squelch circuits, which mute the speaker thus cutting out noise between reception periods; and noise

[Continued on page 53]



3 big reasons why QUIETROLE
Reg. U. S. Pat. Off.

is "The Choice of Better Service Dealers Everywhere"

- 1 MERIT
- 2 QUALITY
- 3 RELIABILITY

The original product for quieting noisy controls and switches . . . the universal lubri-cleaner for TV and radio . . .

Say "QUIETROLE" to your distributor . . . be sure you get it.

**NO GUM!
NO GOO!
NO GRIME!**

Carried by recognized jobbers . . . everywhere!

manufactured by

QUIETROLE

COMPANY INC.
Spartanburg, South Carolina

IN CANADA: Active Radio & TV Distributors
58 Spadina Ave., Toronto 2B, Ont.

DON'T JUST SAY CAPACITORS


Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 71 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

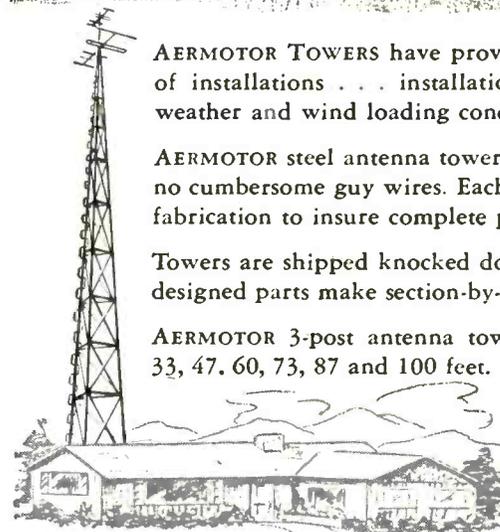When signal conditions demand a TOWER... choose one built by AERMOTOR



AERMOTOR TOWERS have proven their excellence in thousands of installations . . . installations exposed to the most severe weather and wind loading conditions.

AERMOTOR steel antenna towers are self supporting . . . require no cumbersome guy wires. Each part is heavily galvanized after fabrication to insure complete protection from exposure.

Towers are shipped knocked down in convenient bundles; well designed parts make section-by-section assembly easy.

AERMOTOR 3-post antenna towers are available in heights of 33, 47, 60, 73, 87 and 100 feet.

WRITE FOR ADDITIONAL INFORMATION ABOUT THE AERMOTOR TOWERS AND A DEALER FRANCHISE IN YOUR TERRITORY.

SINCE 1888, MANUFACTURERS OF QUALITY BUILT TOWERS

• AERMOTOR COMPANY •

2500 W. ROOSEVELT RD.—CHICAGO 8, ILLINOIS U.S.A. DEPT. 33U10

for service and lab. work

Heathkit PRINTED CIRCUIT OSCILLOSCOPE KIT FOR COLOR TVI

① Check the outstanding engineering design of this modern printed circuit Scope. Designed for color TV work, ideal for critical Laboratory applications. Frequency response essentially flat from 5 cycles to 5 Mc down only 1½ db at 3.58 Mc (TV color burst sync frequency). Down only 5 db at 5 Mc. New sweep generator 20-500,000 cycles, 5 times the range usually offered. Will sync wave form display up to 5 Mc and better. Printed circuit boards stabilize performance specifications and cut assembly time in half. Formerly available only in costly Lab type Scope. Features horizontal trace expansion for observation of pulse detail — retrace blanking amplifier — voltage regulated power supply — 3 step frequency compensated vertical input — low capacity nylon bushings on panel terminals — plus a host of other fine features. Combines peak performance and fine engineering features with low kit cost!



Heathkit TV SWEEP GENERATOR KIT ELECTRONIC SWEEP SYSTEM

② A new Heathkit sweep generator covering all frequencies encountered in TV service work (color or monochrome). FM frequencies too! 4 Mc — 220 Mc on fundamentals, harmonics up to 880 Mc. Smoothly controllable all-electronic sweep system. Nothing mechanical to vibrate or wear out. Crystal controlled 4.5 Mc fixed marker and separate variable marker 19-60 Mc on fundamentals and 57-180 Mc on calibrated harmonics. Plug-in crystal included. Blanking and phasing controls — automatic constant amplitude output circuit — efficient attenuation — maximum RF output well over .1 volt — vastly improved linearity. Easily your best buy in sweep generators.



Heath
COMPANY
A SUBSIDIARY OF DAYSTROM, INC.
BENTON HARBOR 29, MICH.

WRITE FOR FREE CATALOG
...COMPLETE INFORMATION

EICO 84 Withers St., Brooklyn 11, N. Y. D-10

SAVE ME 50% on precision instruments—
send **FREE CATALOG** on EICO's 46 models
in factory-wired and kit form.

My Name.....
Address.....
City..... Zone..... State.....



NEW! COLOR

and Black-&White
DC to 5 MC LAB & TV
5" OSCILLOSCOPE

#460
Factory-wired
and tested **\$129.50**
Also available as kit **\$79.95**

• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; 2 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions (30 & 7875 cps); auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.

BEFORE you buy ANY instruments—get the FACTS on the money-saving, high-precision EICO line. Fill in coupon for FREE catalog & name of your nearby distributor.

EICO 84 Withers St., Brooklyn 11, N. Y.
Prices 5% higher on West Coast

FREE! JUST OUT!
LEKTRON'S LARGEST-EVER

FLYER!

WRITE TODAY! BIGGEST BUYS IN
RADIO • TV • HI-FI • ELECTRONICS
PARTS ASSORTMENTS & EQUIPMENT

FAMOUS **KIT KING** DOLLARKITS

sold only by Lektron!

\$1

- 65 TUBULAR CONDENSERS.
Popular makes. 30 types. .0005 to 0.5mf to 1500 V. Wt. 2 lbs. \$1 Reg. \$12
- 75 CERAMIC CONDENSERS!
Scoop! 35 asstd. values. tubulars and discs. 5 mmf to .01 mf up to 3 Kv. Wt. ½ lb. Reg. \$11
- 70 RESISTORS. Insulated IRC. Allen-Bradley, etc. 5 ohms to 10 megs. ½, 1 & 2 w; 1% & 5%. \$1 Wt. ½ lb. Reg. \$11.
- 15 VOLUME CONTROLS. 10 types; values to 0.5 megs. Wt. 1 lb. Reg. \$9.

FREE! ANY \$1 ITEM FREE WITH \$10 ORDER!
Above are typical of parts assortments regularly stocked by WORLD'S LARGEST SUPPLIER OF PARTS ASSORTMENTS.

Exclusive! LEKTRON "CREDIT-BONUS" PLAN!
\$2.69 ORDER — \$2.69 BONUS CREDIT —
\$14.00 ORDER — ONE FREE \$1 ITEM — PLUS
\$4 BONUS CREDIT

\$10 IN BONUS CREDITS ENTITLES YOU TO
ANY \$1 ITEM... FREE!

HOW TO ORDER } Check items wanted. Return entire ad with check or M.O. Include sufficient postage, excess returned. C.O.D. orders, 25% down. Rated, net 30 days. Print name, address, amount money enclosed in margin. SD-10

LEKTRON

27 GARDNER ST., CHELSEA 50, MASS.

PRICING INDEX

[from page 49]

see scores of instances where components of similar characteristics produced by different manufacturers list at prices which vary greatly. For example, one leading capacitor manufacturer has a list price of \$.85 (while a competitor has a list of \$.90) for a 3V. 25 uf miniature metal capacitor and a still different manufacturer lists his unit, with the same ratings, at only \$.25. Strangely enough all three of these capacitor manufacturers list price their 6V. 5 uf capacitors at \$.90. You figure it out! A serviceman must constantly refer to a current, reliable pricing source if he wants to operate on a proper and businesslike basis. It could happen that, failing to refer to a pricing guide, a serviceman might charge \$.25 for a capacitor that actually cost him over \$.40—and such a careless serviceman won't be able to stay in business long.

Despite what the politicians say, prices of most commodities have been rising constantly. In other words, every serviceman's operating costs have been going up and up. It is incumbent upon all businessmen and particularly radio-TV servicemen who work on a nominal margin to realize this and they must take advantage of it when possible. Here's an example of what I mean. According to Dave Rice's "Official Pricing Index" Vol. 1 No. 2, issued in January of this year the five picture tube manufacturers who make them had a list price of \$44.75 for type 16AP4A CRT's. However, the July 1956 issue of "Official Pricing Index," Vol. 1 No. 4 shows that while two manufacturers still list the 16AP4A at \$44.75 two others now list it at \$46.40 and the fifth manufacturer now list prices it at \$46.72. When Rice's next issue is released in October, other price changes like this will undoubtedly be recorded.

I checked with Dave Rice about his "Official Pricing Digest" and concur with his theories about it. To begin with, the "Digests" are published four times a year, January, April, July and October. They have a list price of \$2.50 but a great many parts distributors buy them in large lots and gladly give them away free to their regular servicemen customers for several reasons. For example, "Digests" save the distributors much time answering servicemen's queries regarding new list prices of items. And distributors realize that it helps them when their servicemen customers charge the right prices. As for servicemen themselves, I personally feel that even if they have to buy a copy of the Pricing Index for the nominal sum involved they will get that investment back many times by making certain that they can quickly price any item, that they will neither gyp themselves, nor will they improperly charge their customers. In fact, when itemizing a bill for a customer, it's wise to refer to the index and thus show the customer that you did not guess at the prices you charged. ■ ■

Mr. Electronic Service Technician



You have seen and will continue to see, in the chassis of TOP-NAME Radio and TV sets, an increasing number of Planet electrolytic capacitors — conspicuous because of their shiny red cardboard jackets. They are in those quality sets because components engineers have proven for themselves that PLANET condensers are "ENGINEERED FOR QUALITY".

You can take advantage of their findings by purchasing from your distributor Planet universal replacement types of the same high standard of quality. Ask for PLANET by name.

Write now for "ENGINEERED FOR QUALITY"
latest FREE catalog. GUARANTEED FOR ONE YEAR

PLANET


PLANET SALES CORPORATION

225 BELLEVILLE AVENUE
BLOOMFIELD, N. J.

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

SOMETHING NEW (AND BETTER) IN FLUSH CUTOFF!

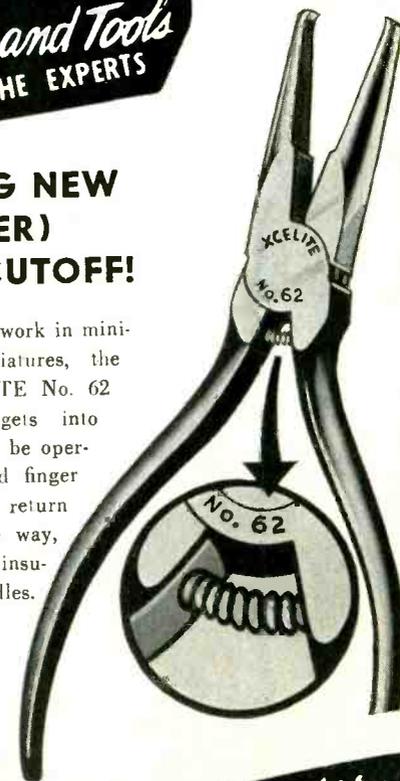For your flush cutoff work in miniatures and sub-miniatures, the popular new XCELITE No. 62 Transverse Cutter gets into small spaces and can be operated with thumb and finger only. Its new coil return spring is out of the way, and permits sliding insulating sleeves on handles. Ask your supplier!



XCELITE
INCORPORATED
Dept. R
Orchard Park
New York

For Originality
LOOK TO **XCELITE**

HICKOK

Model 605A



DYNAMIC MUTUAL
CONDUCTANCE

Tube Tester

Handy Size Portable

- Popular—Accurate—Dependable.
- Large 5" easy-to-read meter.
- Accurately tests tubes in micromhos.
- Built-in 20,000 ohms per volt DC multimeter measures capacitance, inductance, volts, current and decibels.
- Write for technical details . . .

THE HICKOK ELECTRICAL INSTRUMENT CO.

10533 DUPONT AVE., CLEVELAND 8, OHIO

MARINE ELECTRONICS

[from page 51]

limiting circuits, which remove sharp peaks of interference, such as those from static and engine ignition.

The relatively costly handset has been done away with in all but the luxury models, in favor of a hand microphone, with reception over the loudspeaker, which is just as practical and a great deal less expensive.

When I looked inside my first marine radiotelephone, I was very much disturbed at seeing *rf* leads, especially in

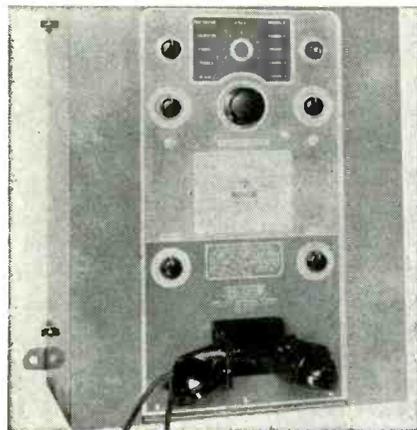


Fig. 4—Radiomarine ET-8050-HF

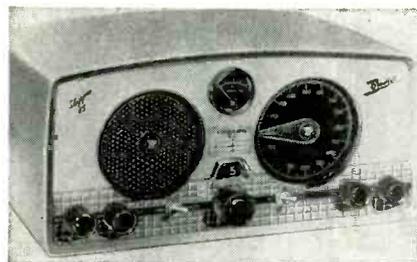


Fig. 5—The Bendix Skipper 45

the transmitter circuits, cabled together as if they were *dc* circuits. Look inside many radiotelephones built this year, and you will still see *rf* leads cabled as if they were carrying filament current. I suppose it is all right, as long as the insulation is good, for practices such as this to continue. Actually, loaded *rf* circuits are low *Q*, and using cabled wires and other distributed capacitances as part of the circuit reactance is permissible, if the insulation is not too muddy. Marine radiotelephones have not changed a great deal since their inception, but I'm happy to state that in the past few years things have taken a turn for the better. ■■

CORNING LOW-POWER RESISTORS


available now through

ERIE
distributors

for Service Replacements

Corning Low-Power Resistors Types LP-4 and LP-5 have been especially designed for radio, TV, and similar applications. They have the highest resistance range of any low-power resistors on the market, and are used by leading manufacturers. They are stable and non-inductive, and impervious to moisture and dirt. Resistance spiralling is automatic and is electronically controlled.

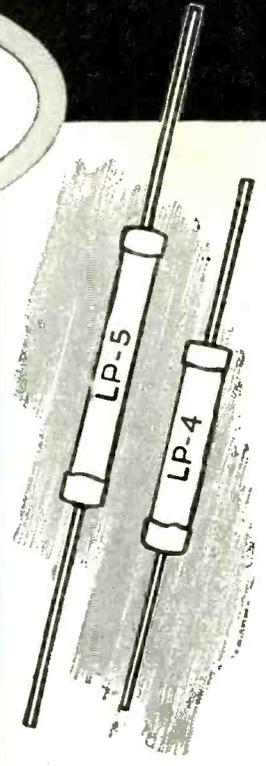For complete service information and prices . . . see your Erie Distributor.



ERIE
electronics

ERIE ELECTRONICS DISTRIBUTOR DIVISION

ERIE RESISTOR CORPORATION
Main Offices: ERIE, PA.

Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO



SERVICEMEN
WHO PUT PRIDE
IN THEIR WORK
"ALWAYS
SPECIFY
STANCOR"




CHICAGO STANDARD TRANSFORMER CORPORATION

3511 Addison Street • Chicago 18, Illinois

QUICK-CHANGE 5AXP4 HOLDER


Permits
Speedy
Yoke
Changing

\$3.25
each

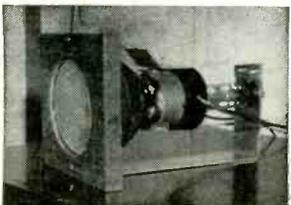

TELE-SCOPIC PRODUCTS, INC.
215 W. 33rd St. New York 1, N. Y.

IDEA OF THE MONTH

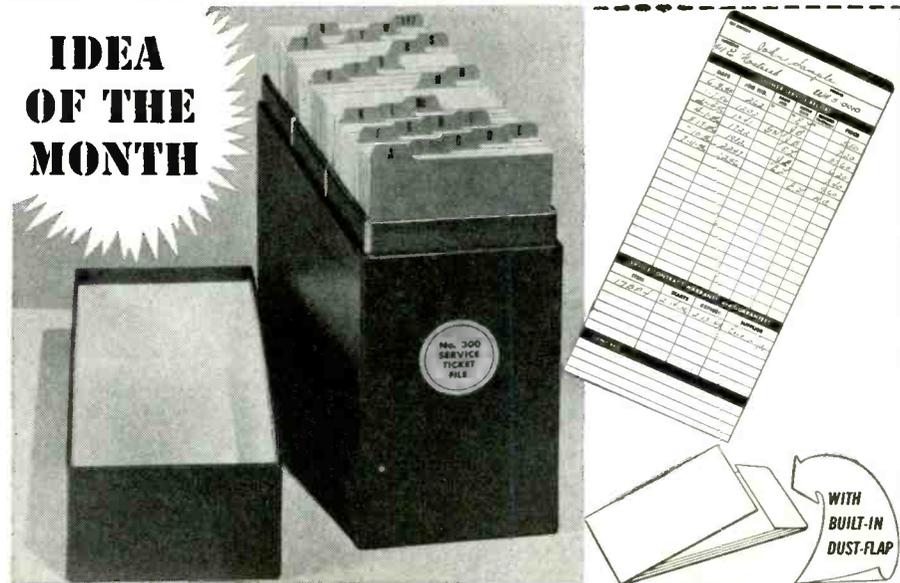

#300 SERVICE TICKET FILE

(200 FOLDER CAPACITY)

A new practical low cost system for filing customers service call and shop job tickets alphabetically in individual file folders. For instant reference a form is printed on the face of each folder for summarizing contents. File case is of heavy cardboard construction in attractive brown simulated leather finish. File folders are of heavy cream tag stock with extra flap feature for fast reference (see inset) . . . smartly printed in brown. A to Z file guides are heavy press board. FILE CASE SIZE 4 7/8" x 10 7/8" x 12 1/2"

AT YOUR ELECTRONIC PARTS JOBBER

#300 SERVICE TICKET FILE SYSTEM . . . \$7.40
(includes case, guides and 100 folders)
#301 BOX OF 100 FILE FOLDERS . . . \$2.95
#302 SET OF FILE GUIDES . . . \$1.95

DELRICH PUBLICATIONS
4308 N. MILWAUKEE AVE. • CHICAGO 41, ILL.
Send me FREE sample file folder and catalog.

Name _____
Address _____
City _____ Zone _____ State _____

Only the 5 TOP-QUALITY brands of

STANDARD BRAND TUBES

AT SENSIBLE PRICES

• 90 Day RETMA Guarantee • Brand New
• 1st quality only • Individually boxed

FREE! Newest handy air-mail order form for your ordering convenience.—Free!
• Lists ALL popular TV & radio types.
• Makes mail-ordering a real pleasure.
• Orders over \$25.00 (with remittance) postpaid

| | | | | | |
|--------|-------|-----------|------|----------|------|
| 0Z4 | \$.60 | 6AS6 | 2.25 | 7F8 | 1.20 |
| 1AX2 | 1.15 | 6AS8 | 1.20 | 7G7 | 1.85 |
| 1B3GT | .95 | 6AT6 | .60 | 7B7 | .85 |
| 1H5GT | .80 | 6AT8 | 1.10 | 7J7 | 1.35 |
| 1L4 | .85 | 6AU4GT | 1.10 | 7K7 | 1.20 |
| 1L6 | 1.10 | 6AU5GT | 1.25 | 7L7 | 1.15 |
| 1LA4 | 1.00 | 6AU6 | .75 | 7N7 | .95 |
| 1LA6 | 1.00 | 6AU7 | .90 | 7Q7 | 1.00 |
| 1LB4 | 1.00 | 6AV5GT | 1.20 | 7R7 | 1.30 |
| 1LC5 | 1.00 | 6AV6 | .60 | 7V7 | 1.30 |
| 1LC6 | 1.00 | 6AW8 | 1.20 | 7W7 | 1.30 |
| 1LD5 | 1.00 | 6AX4GT | .90 | 7X7 | 1.00 |
| 1LE3 | 1.00 | 6AX5GT | .90 | 7Y4 | .70 |
| 1LG5 | 1.00 | 6BA5 | .70 | 7Z4 | .75 |
| 1LH4 | 1.00 | 6B47 | .90 | 12A4 | .85 |
| 1LN5 | 1.00 | 6BC4 | 1.60 | 12AL5 | .70 |
| 1NSGT | .95 | 6BC5 | .75 | 12AQ5 | .75 |
| 1Q5GT | 1.15 | 6BC7 | 1.25 | 12AT6 | .65 |
| 1R4 | 1.00 | 6BD5 | 1.40 | 12AT7 | 1.00 |
| 1R5 | .85 | 6BD6 | .75 | 12AU6 | .70 |
| 1S4 | .90 | 6BE6 | .75 | 12AV7 | .85 |
| 1S5 | .75 | 6BF3 | .70 | 12AV6 | .65 |
| 1T4 | .85 | 6BF6 | .70 | 12AV7 | 1.05 |
| 1T5GT | 1.05 | 6BG6G | 1.85 | 12AW6 | 1.00 |
| 1U4 | .80 | 6BH6 | .90 | 12AX4GT | 1.00 |
| 1U5 | .75 | 6BJ6 | .85 | 12AX7 | .90 |
| 1V | .95 | 6BK5 | 1.15 | 12AY7 | 1.75 |
| 1V2 | .70 | 6BK7A | 1.15 | 12AZ7 | .95 |
| 1X2B | 1.00 | 6BL7GT | 1.25 | 12BA4 | .90 |
| 2AF4A | 1.40 | 6BN6 | 1.15 | 12BA6 | .70 |
| 2D21 | 1.00 | 6BQ6GTA | 1.45 | 12BA7 | .95 |
| 2X2 | .50 | 6BQ7A | 1.30 | 12BD6 | .75 |
| 3A3 | 1.10 | 6BX7GT | 1.25 | 12BE6 | .75 |
| 3A4 | .55 | 6BY5G | .30 | 12BF5 | .70 |
| 3A5 | .75 | 6BZ6 | .80 | 12BH7A | 1.00 |
| 3AL5 | .70 | 6BZ7 | 1.35 | 12BK5 | 1.10 |
| 3AU6 | .75 | 6C4 | .60 | 12BQ6GTB | 1.45 |
| 3AV6 | .65 | 6C5 | .80 | 12BX7 | .90 |
| 3BA6 | .75 | 6CB3 | 4.90 | 12B7A | 1.05 |
| 3BC5 | .80 | 6CB7 | .75 | 12C7 | 1.10 |
| 3BE6 | .75 | 6CD6G | .90 | 12CA5 | .80 |
| 3BN6 | 1.05 | 6CF6 | .90 | 12CU6 | 1.45 |
| 3BY6 | .90 | 6C7 | .90 | 12L6 | .80 |
| 3BZ6 | .80 | 6CL6 | 1.20 | 12SA7GT | 1.00 |
| 3CB6 | .85 | 6CM6 | .85 | 12SC7 | .80 |
| 3CF6 | .85 | 6CS6 | .75 | 12S7 | .75 |
| 3CS6 | .80 | 6CU6 | 1.45 | 12SK7GT | .80 |
| 3LF4 | 1.20 | 6DC7 | .95 | 12SL7GT | 1.00 |
| 3Q4 | .85 | 6DE6 | .80 | 12SN7GTA | .85 |
| 3Q5GT | 1.00 | 6F5 | .85 | 12SQ7GT | .75 |
| 3S4 | .80 | 6FF6G | .80 | 12V6GT | .80 |
| 3V4 | .85 | 6H6 | .75 | 12W6GT | .95 |
| 4BQ7A | 1.30 | 6J4 | 3.95 | 14A4 | 1.00 |
| 4BZ7 | 1.35 | 6J5 | .75 | 14A5 | 1.50 |
| 5AM8 | 1.05 | 6J6 | .70 | 14A7 | .85 |
| 5AN8 | 1.10 | 6K6GT | .75 | 14AF7 | 1.00 |
| 5AQ5 | .75 | 6K7 | .90 | 14B6 | .85 |
| 5AS8 | 1.10 | 6K8 | 1.25 | 14C7 | 1.00 |
| 5AT8 | 1.10 | 6L6GA | 1.30 | 14E6 | 1.20 |
| 5AY8 | 1.15 | 6L6M | 1.75 | 14E7 | 1.30 |
| 5AW4 | 1.15 | 6N7 | 1.20 | 14F7 | 1.00 |
| 5AZ4 | .60 | 6Q7 | 1.00 | 14F8 | 1.30 |
| 5B7 | 1.10 | 6S4 | .70 | 14H7 | 1.00 |
| 5B8 | .95 | 6S6GT | 1.10 | 14N7 | 1.00 |
| 5T4 | 1.75 | 6SA7GT | .90 | 14Q7 | .95 |
| 5T8 | 1.10 | 6SC7 | 1.00 | 14R7 | 1.30 |
| 5U4G | .70 | 6SF5 | .75 | 14S7 | 1.25 |
| 5U4GB | .75 | 6SF7 | .95 | 14W7 | 1.35 |
| 5U8 | 1.10 | 6SG7 | 1.00 | 19T8 | 1.20 |
| 5V4G | 1.00 | 6SH7 | .95 | 25AV5GT | 1.30 |
| 5V6GT | .70 | 6S17M | .85 | 25AX4GT | 1.10 |
| 5W4GT | .70 | 6SK7GT | .85 | 25BK5 | 1.10 |
| 5X4G | .80 | 6SL7GT | 1.00 | 25BQ6GTB | 1.45 |
| 5X8 | 1.05 | 6SN7GTA/B | 1.90 | 25CD6GA | 1.85 |
| 5Y3GT | .60 | 6SQ7GT | .75 | 25CU6 | 1.45 |
| 5Y4G | .65 | 6SR7 | .75 | 25LRGT | .75 |
| 5Z3 | .90 | 6T4 | 1.30 | 25V6GT | .80 |
| 5Z4 | 1.25 | 6T8 | 1.10 | 25Z5 | .80 |
| 6A8GT | 1.10 | 6U8 | 1.10 | 25Z6GT | .85 |
| 6AB4 | .70 | 6V3A | 1.50 | 35A5 | .75 |
| 6AC5GT | 1.15 | 6V6GT | .75 | 35B5 | .70 |
| 6AC7 | 1.15 | 6V6M | 1.35 | 35C5 | .70 |
| 6AD7G | 1.55 | 6W4GT | .80 | 35LRGT | .65 |
| 6AF4 | 1.35 | 6W6GT | .95 | 35W4 | .55 |
| 6AF6G | 1.20 | 6X4 | .55 | 35Y4 | .75 |
| 6AG5 | .80 | 6X5GT | .55 | 35Z5 | .60 |
| 6AG7 | 1.35 | 6X8 | 1.20 | 41 | .85 |
| 6AH4GT | 1.00 | 6Y6G | .95 | 42 | .75 |
| 6AH6V | 1.25 | 7A5 | .95 | 43 | .85 |
| 6AJ5 | .75 | 7A6 | .80 | 50A5 | .75 |
| 6AK5 | .80 | 7A7 | .85 | 50B5 | .75 |
| 6AK6 | .80 | 7A8 | .80 | 50C5 | .75 |
| 6AL5 | .65 | 7AG7 | 1.00 | 50L6GT | .75 |
| 6AL7GT | 1.65 | 7AH7 | 1.00 | 50X8GT | .90 |
| 6AM4 | 1.55 | 7B4 | .80 | 50Y6GT | 1.00 |
| 6AM8 | 1.15 | 7B5 | .70 | 50Y7GT | .90 |
| 6AN4 | 1.50 | 7B6 | .80 | 70L7GT | 1.55 |
| 6AN5 | 3.50 | 7B7 | .80 | 80 | .65 |
| 6AN8 | 1.20 | 7B8 | .90 | 117L7GT | 2.50 |
| 6AQ5 | .75 | 7C5 | .80 | 117N/P7 | 2.00 |
| 6AQ6 | .60 | 7C6 | 1.00 | 117Z4GT | 1.15 |
| 6AQ7GT | 1.25 | 7C7 | .85 | 117Z6GT | 1.15 |
| 6AR5 | .75 | 7E7 | 1.20 | 117Z6GT | 1.15 |
| 6AS5 | .80 | 7F7 | .90 | 5642 | 1.00 |

We stock over 1000 types including Diodes, Transistors, transmitting and Special Purpose types.

TERMS: 25% with order, balance C.O.D. All merchandise guaranteed. F.O.B., N.Y.C.

BARRY ELECTRONICS CORP.
Dept. SD

512 Broadway, N. Y. 12, N. Y.

Call us day or night
24-hour telephone service
WAlker 5-7000

COMPATIBLE CRYSTAL CALIBRATOR

[from page 7]

range Pierce type oscillator requiring no adjustment for crystals having fundamentals over the range of 100 kc to 20 mc. The cathode coil and condenser *L101* and *C104* form a resonant circuit to extend the range of the oscillator to the low frequencies. The oscillator *V101A* is isolated from the output by a cathode follower *V101B*. The crystal *CR101* serves as the harmonic generator, modulator and signal mixer in the output. *Y101* is the precision color carrier crystal which is calibrated to its high degree of accuracy by the ceramic trimmer across it. This is adjusted at the factory. A selenium rectifier and isolation transformer are used with a long time constant *RC* filter to provide a hum-free power supply. Test jacks *J101* and *J102* permit the use of a 0 to 100 microampere meter or multimeter to read oscillator grid current, providing an *activity test* for checking and comparing quartz crystals.

Use of the Crystal Calibrator

The front panel accessibility of the crystal sockets in conjunction with the crystal selector switch gives the instrument universal applications in both the service shop and the laboratory. When a 4.5 mc crystal is used in a front panel socket the instrument may be used for troubleshooting and alignment of intercarrier sound I.F. amplifiers, sound IF discriminators, 4.5 mc trap alignment and sideband marking for alignment sweep curves. It can be used with appropriate crystals as a frequency standard or band limit marker since the accuracy with a good crystal is better than that of the average frequency meter.

In color television the 3.579545 mc standard is useful not only in servicing but also in laboratory work, television transmitter testing and community antenna systems testing for color operation.

Figure 5 shows the hookup used with a color TV receiver to check and align the frequency of the 3.579545 mc reference oscillator. The slanting lines of color appear when the 3.58 MC reference oscillator is not on the correct frequency. These lines are analogous to the ones seen on the screen when the horizontal oscillator is not synchronized.

SLANTING LINES OF COLOR INDICATE 3.58MC TV OSCILLATOR IS OFF-FREQUENCY

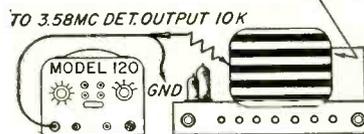


Fig. 5—Hookup to check and align reference oscillator.


In like manner, if we count the number of slanting lines of color and multiply by 60 (the vertical sweep frequency) we have the amount by which the oscillator is off frequency. Also, as we adjust the color hold or reference oscillator frequency, counting the number of lines on the screen when the phase detector circuit starts to pull the oscillator in to synchronization will give the "pull-in" range of the circuit, thus determining whether the phase detector circuit is operating properly. For example, if pull-in starts at 10 lines this shows that the pull-in range of the color phase detector circuit is 10 x 60 or 600 cycles.

Another possibility in the servicing of color receivers is that the color circuits will not function and no color can be produced because the 3.58 mc reference oscillator will not operate. In this case, the Model 120 can be used to substitute for the reference oscillator to determine the exact nature of the trouble. This is a form of troubleshooting by signal substitution.

The entire burst and chroma chain can be tested by signal tracing the 3.58 mc signal produced by the Model 120. The signal from the Model 120 is fed to the video detector test point of the color receiver, ahead of the color take-off points. Then a broad band scope is used to trace the 3.58 mc signal through the chroma circuits to the chroma detectors, or through the burst gate (equivalent to a sync separator), burst amplifiers, etc, up to the color phase detector circuit. The defective stage would be located when the oscilloscope tracing reaches a point in the sync or chroma chain beyond which the signal cannot pass or is excessively low.

ask the
"Man-on-the-Roof"
why he prefers

South River

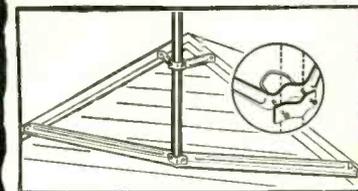

EAVE MOUNT Model EM-48

One piece construction of heavy gauge, embossed steel, Hot-Dip galvanized to prevent corrosion. Unique design of lower bracket gives extra strength and rigidity. Extended lip supports mast during installation. 48" spread permits generous spacing between brackets for excellent mechanical mast support. Both 3" embossed steel upper bracket and lower bracket have new "reversed" U bolt and clamp feature or Spintite fastening. Also available with 30" spread: EM-60

WRITE FOR NEW 1956 CATALOG

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey

pioneer & outstanding producer of finest line of antenna mounts

DON'T JUST SAY CAPACITORS


Ask For Sprague By Catalog Number

Know what you're getting get exactly what you want. Don't be vague. Insist on Sprague. Use Complete radio-TV service catalog C-610. Write Sprague Products Company, 71 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

DON'T JUST SAY CAPACITORS

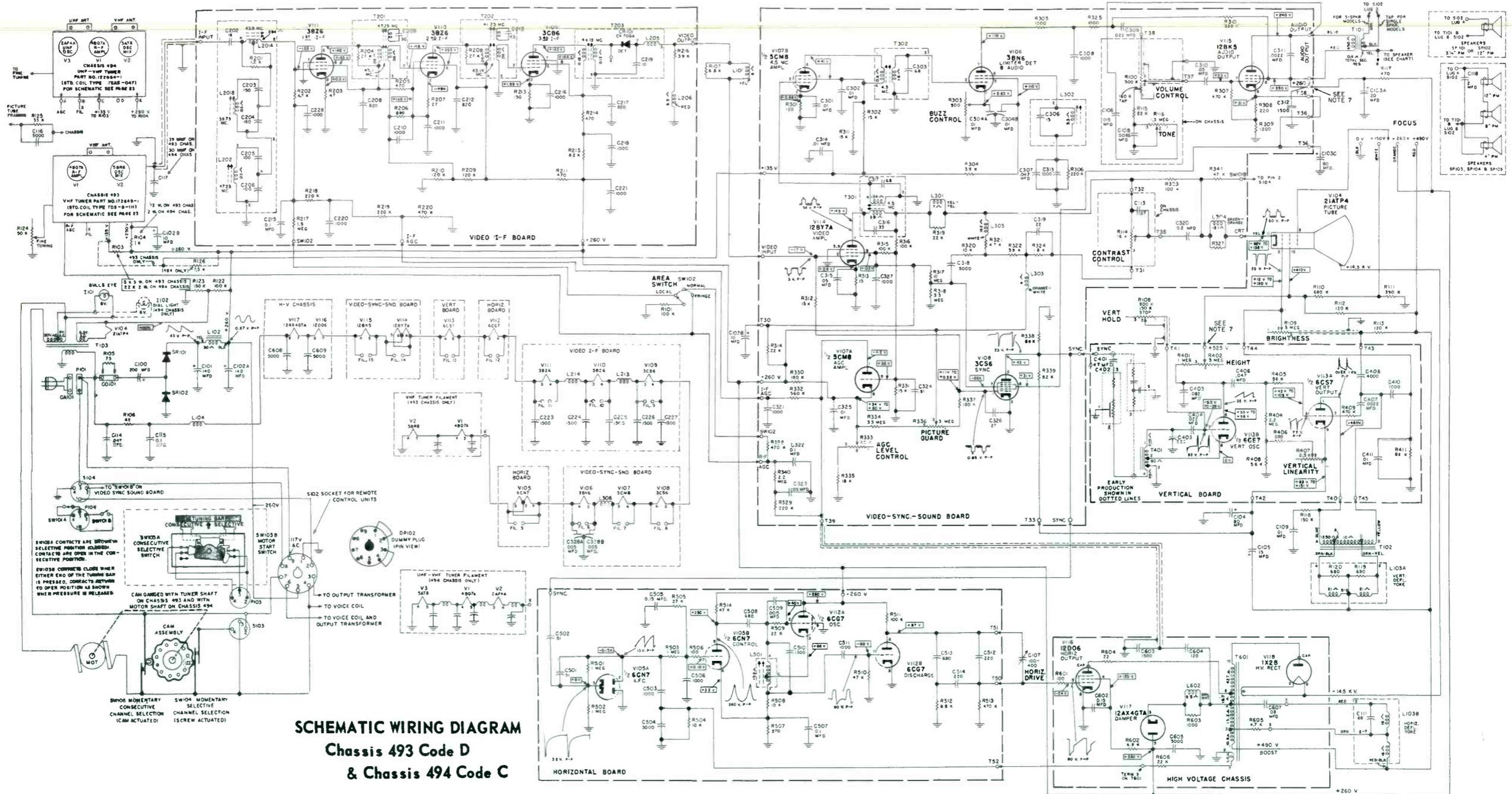

SCHEMATIC WIRING DIAGRAM
Chassis 493 Code D
& Chassis 494 Code C

TABLE OF SOCKET VOLTAGES 494 Chassis

| Symbol | Type | Pin 1 | Pin 2 | Pin 3 | Pin 4 | Pin 5 | Pin 6 | Pin 7 | Pin 8 | Pin 9 |
|---|----------|-------|-------|-------|-------|-------|-------|--------|--------|--------|
| V1 | 4BQ7A | +1.0 | -6 | 0 | *4.7 | *9.0 | -215 | -110 | -110 | 0 |
| V2 | 5AT8 | -1.5 | +88 | 0 | *0 | *4.7 | +175 | +100 | 0 | -1.55 |
| V104 | 21ATP4 | +150 | +8 | 0 | 0 | 0 | 0 | Pin 10 | Pin 11 | Pin 12 |
| (Filament voltage measured across Pins 1 & 12 = 6.3 V.) | | | | | | | | | | |
| V105 | 6CN7 | 0 | +25 | +5.5 | *14.5 | *14.5 | +1.95 | +25 | +173 | *11.2 |
| V106 | 3BN6 | +1.8 | 0 | *17.5 | *14.5 | +94 | 0 | +105 | --- | --- |
| V107 | 5CM8 | -1 | 0 | +4 | *22.2 | *17.5 | +40 | +40 | +40 | +23.5 |
| V108 | 3C8 | +55 | 0 | *25.3 | *22.2 | +45 | +28.5 | -5 | --- | --- |
| V109 | 3CB6 | 0 | +2.0 | *28.5 | *25.3 | +135 | +135 | 0 | --- | --- |
| V110 | 3BZ6 | +125 | +126 | *31.6 | *28.5 | +240 | +242 | +120 | --- | --- |
| V111 | 3BZ6 | -1 | +0.75 | *34.8 | *31.6 | +115 | +213 | 0 | --- | --- |
| V112 | 6CG7 | +250 | +43 | +71 | *34.8 | *41.1 | +78 | -66 | 0 | 0 |
| V113 | 6CS7 | +480 | +70 | +70 | *47.4 | *41.1 | +66 | -21.5 | 0 | +115 |
| V114 | 12BY7A | +45 | -2 | 0 | *47.4 | *47.4 | +53.7 | +105 | +110 | 0 |
| V115 | 12BK5 | +222 | 0 | +22.5 | *66.3 | *53.7 | +29 | +22.5 | +235 | 0 |
| V116 | 12DQ6 | 0 | *79.0 | 0 | +132 | -24 | +66.3 | 0 | --- | --- |
| V117 | 12AX4GTA | 0 | +550 | 0 | +245 | 0 | *79.0 | *91.5 | --- | --- |
| V118 | 1X2B | --- | --- | --- | --- | --- | --- | --- | --- | H. V. |

D. C. voltages listed below measured with VHF channel selector in UHF position. UHF channel selector set to low frequency end.

| | | | | | | | | | | |
|----|-------|-----|----|------|-------|---|----|-----|-----|-----|
| V3 | 2AF4A | +68 | -3 | *9.0 | *11.2 | 0 | -3 | +68 | --- | --- |
|----|-------|-----|----|------|-------|---|----|-----|-----|-----|

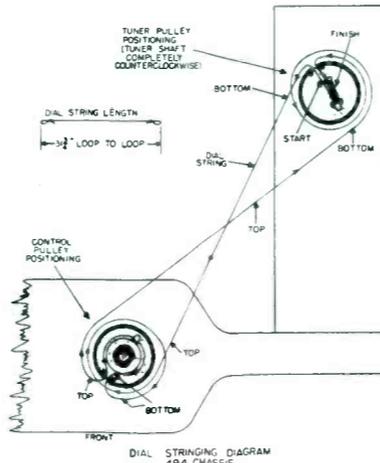



TABLE OF SOCKET VOLTAGES 493 Chassis

| Symbol | Type | Pin 1 | Pin 2 | Pin 3 | Pin 4 | Pin 5 | Pin 6 | Pin 7 | Pin 8 | Pin 9 |
|--|----------|-------|-------|-------|-------|-------|-------|--------|--------|--------|
| V1 | 4BQ7A | +215 | +120 | +120 | *4.7 | *8.9 | +120 | -3 | 0 | 0 |
| V2 | 5BR8 | -1.6 | +85 | 0 | *0 | *4.7 | +88 | +72 | 0 | -1.6 |
| V104 | 21ATP4 | +150 | +8 | 0 | 0 | 0 | 0 | Pin 10 | Pin 11 | Pin 12 |
| (Filament voltage measured across Pin 1 & 12 = 6.3 V.) | | | | | | | | | | |
| V105 | 6CN7 | 0 | +25 | +5.5 | *12.0 | *12.0 | +1.95 | +25 | +173 | *8.9 |
| V106 | 3BN6 | +1.8 | 0 | *15.3 | *12.0 | +94 | 0 | +105 | --- | --- |
| V107 | 5CM8 | -1 | 0 | +4 | *20.0 | *15.3 | +40 | +40 | +40 | +23.5 |
| V108 | 3C8 | +55 | 0 | *23.1 | *20.0 | +45 | +28.5 | -50 | --- | --- |
| V109 | 3CB6 | 0 | +2.0 | *26.3 | *23.1 | +135 | +135 | 0 | --- | --- |
| V110 | 3BZ6 | +125 | +126 | *29.4 | *26.3 | +240 | +242 | +120 | --- | --- |
| V111 | 3BZ6 | -1 | +75 | *32.6 | *29.4 | +115 | +213 | 0 | --- | --- |
| V112 | 6CG7 | +250 | +43 | +71 | *32.6 | *38.9 | +78 | -66 | 0 | 0 |
| V113 | 6CS7 | +480 | +70 | +70 | *45.2 | *38.9 | +66 | -21.5 | 0 | +115 |
| V114 | 12BY7A | +45 | -2 | 0 | *45.2 | *45.2 | +51.5 | +105 | +110 | 0 |
| V115 | 12BK5 | +222 | 0 | +22.5 | *64.0 | *51.5 | +29 | +22.5 | +235 | 0 |
| V116 | 12DQ6 | 0 | *76.7 | 0 | +132 | -24 | +64.0 | 0 | --- | --- |
| V117 | 12AX4GTA | 0 | +550 | +550 | 0 | +245 | 0 | *76.7 | *89.3 | --- |
| V118 | 1X2B | --- | --- | --- | --- | --- | --- | --- | --- | H. V. |


The following voltages were measured with an electronic voltmeter while the set was operating on 117 volts, 60 cycle a.c. with no signal input, antenna terminals shorted, Station Selector set to channel 3. The Brightness, Contrast and Picture Guard controls set at minimum, Area Switch set in NORMAL position. Electronic voltmeter connected between socket lug and chassis; * = A-C voltages. Voltages may vary depending upon the setting of other controls.

TV CHASSIS 493
 Models DT-12M DC-12M
 DT-12B DC-14M
 DC-10M DC-16B
 DC-10B DC-18N

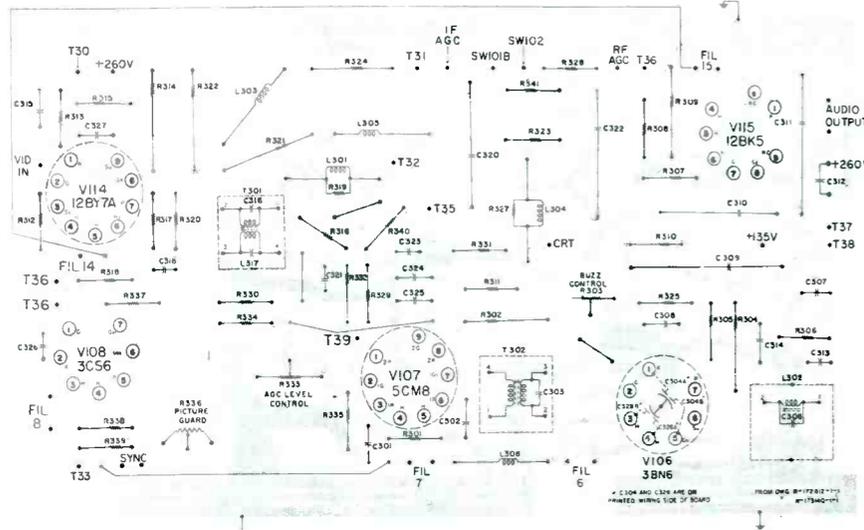
TV CHASSIS 494
 Models DT-13M DC-13M
 DT-13B DC-15M
 DC-11M DC-17B
 DC-11B DC-19N




VIDEO-SYNC-SOUND BOARD

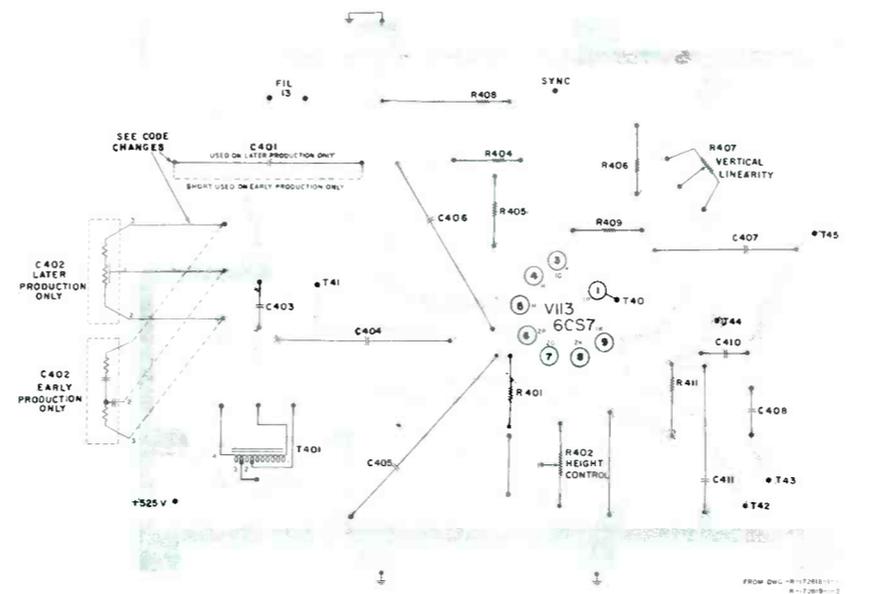


VERTICAL BOARD

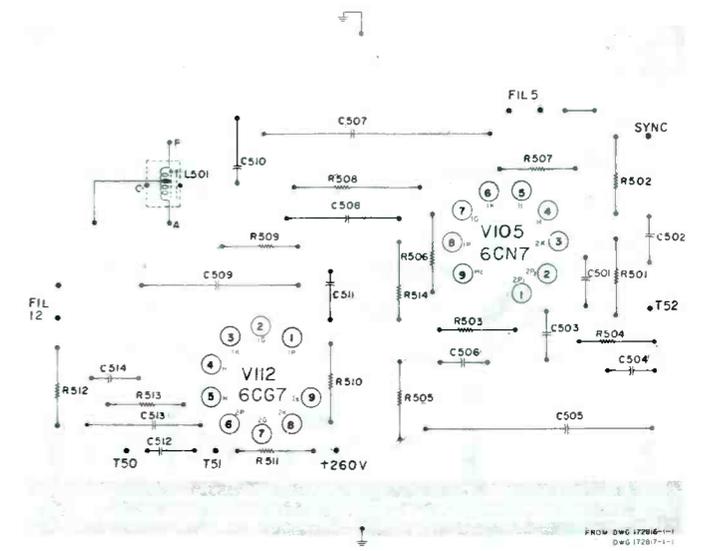

HORIZONTAL BOARD

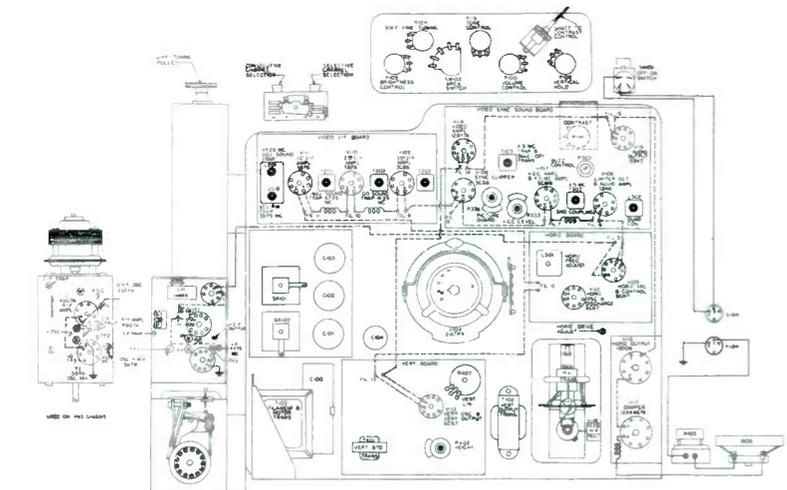

REAR VIEW OF CHASSIS 493 and 494
 (Tube and Alignment Locations and Tube Filament Wiring)

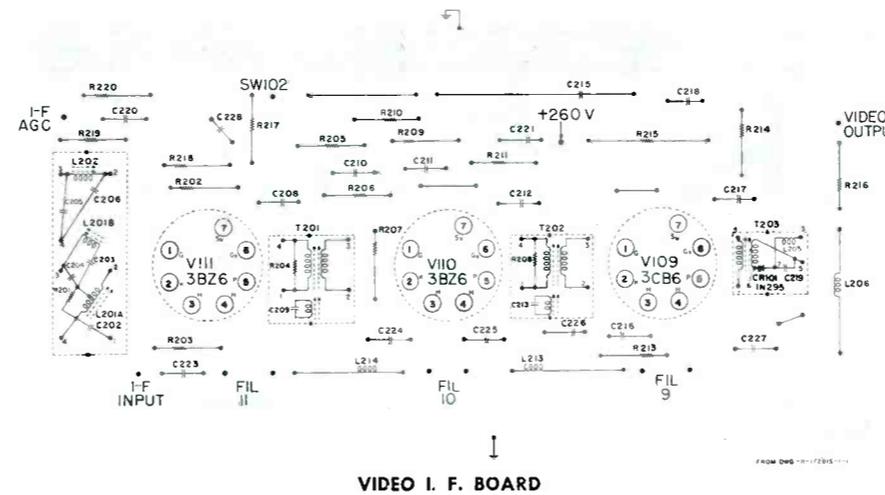


VIDEO I. F. BOARD

PRINTED CIRCUIT BOARDS

The printed circuit boards shown below are viewed from the component side of board. The shaded area represents the printed wiring. Components mounted on the board and other connections are shown in black.

| SYMBOL NUMBER | SPEAKER SIZE | USED ON MODELS |
|---------------|--------------|--|
| SP101 | 5 1/4" | DT-12M, DT-12B, DT-13M, DT-13B |
| SP102 | 12" | DC-10M, DC-10B, DC-11M, DC-11B, DC-12M, DC-12B, DC-13M, DC-13B |
| SP103 | 12" | DC-14M, DC-14B, DC-15M, DC-15B, DC-16M, DC-16B, DC-17M, DC-17B, DC-18M, DC-18B |
| SP104 | 8" | DC-16B, DC-17B |
| SP105 | 4" | DC-18M, DC-18B |

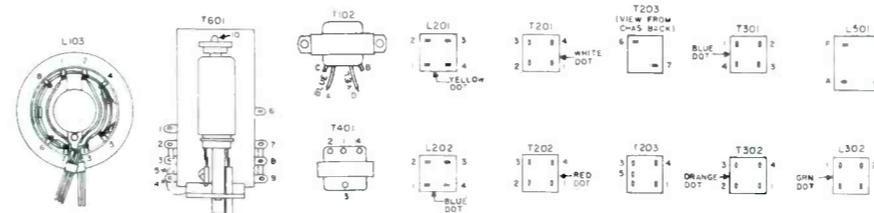


| Symbol No. | Part No. | Description |
|------------|-----------|--|
| R-101 | 172689-1 | Control, Volume (500,000 ohm, 150,000 ohm Tap) |
| R-104 | 39374-201 | 1000 ohm, 10%, 2 w, (494 chassis only) |
| R-105 | 154089-1 | 7.5 ohm, 5w, Fusistor |
| R-106 | 158230-3 | 45 ohm, 20 w |
| R-109 | 171716-1 | Control, Brightness, 5 megohm |
| R-114 | 172172-1 | Control, Contrast, 16,000 ohm |
| R-116 | 172724-1 | Control, Tone (1.5 megohm) |
| R-117 | 39374-109 | 470 ohm, 10%, 1 w |
| R-124 | 172725-1 | Control, Fine Tuning (50,000 ohm) |
| R-125 | 39374-131 | 33,000 ohm, 10%, 1 w |
| R-126 | 170773-7 | 7500 ohm, 10%, 3 w (494 chassis only) |
| R-215 | 170773-4 | 8200 ohm, 10%, 3 w |
| R-303 | 172171-1 | Control, Buzz, 500 ohm |
| R-321 | 39374-209 | 4700 ohm, 10%, 2 w |
| R-322 | 39374-208 | 3900 ohm, 10%, 2 w |
| R-333 | 172236-1 | Control, AGC Level, 40,000 ohm |
| R-336 | 172235-1 | Control, Picture Guard, 5 megohm |
| R-402 | 172235-1 | Control, Height, 5 megohm |
| R-407 | 172275-1 | Control, Vertical Linearity, 2500 ohm |
| R-408 | 170773-1 | 5600 ohm, 10%, 3 w |
| R-602 | 170773-2 | 6800 oh, 10%, 3 w |
| R-604 | 39374-93 | 22 ohm, 10%, 1 w |
| R-606 | 39374-129 | 22,000 ohm, 10%, 1w |
| L-102 | 155529-5 | Choke, Filter, (50 ohm, 1 henry, 300 ma.) |
| L-103A | 172388-1 | Deflection Yoke Assem., Less Cover |
| L-302 | 172452-1 | Coil, Quadrature |
| L-501 | 172339-1 | Transformer, Horizontal Frequency |
| T-101 | 172978-1 | Transformer, Audio Output |
| T-102 | 158726-2 | Transformer, Vertical Output |
| T-103 | 172148-1 | Transformer, Filament and Motor |
| T-201 | 172299-1 | Transformer, 1st. I. F. |
| T-202 | 172306-1 | Transformer, 2nd. I. F. |
| T-203 | 173346-1 | Transformer, 3rd. I. F. (less Xtal and Cap) |
| T-301 | 172454-1 | Transformer, Sound Take-Off |
| T-302 | 172457-1 | Transformer, Sound Coupling |
| T-401 | 172249-1 | Transformer, Vertical B. F. O. |
| T-601 | 172387-2 | Transformer, Horizontal Deflection |
| CR-101 | 157465-5 | Crystal, IN295 |
| P-101 | 154125-1 | Receptacle, Line Cord |
| SR-101 | 155575-1 | Rectifier, Selenium (350 ma.) |
| SR-102 | 155575-1 | Rectifier, Selenium (350 ma.) |
| SW-101A | 172671-1 | Switch, Off-On |


TV COLOR RECEIVER

CHASSIS DESIGNATIONS

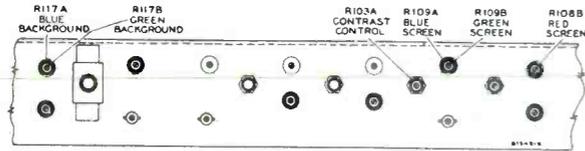
- CTCS Models 21-CS-7815 & 21-CS-7817
- CTCSA Models 21-CS-7815U & 21-CS-7817U
- CTCSB Models 21-CT-7835 & 21-CT-7837
- CTCSC Models 21-CT-7835U & 21-CT-7837U
- CTCSD Models 21-CT-7855, 21-CT-7857, 21-CT-7865, 21-CT-7866 & 21-CT-7867
- CTCSE Models 21-CT-7855U, 21-CT-7857U, 21-CT-7865U, 21-CT-7866U & 21-CT-7867U





SCREEN AND BACKGROUND CONTROLS

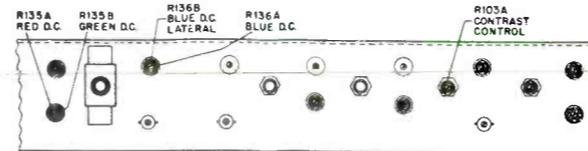


STATIC CONVERGENCE CONTROLS

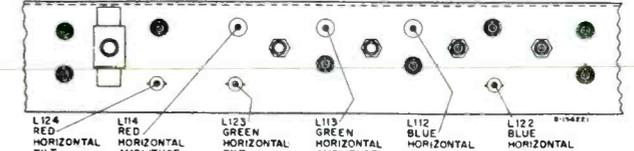

HORIZONTAL DYNAMIC CONTROLS

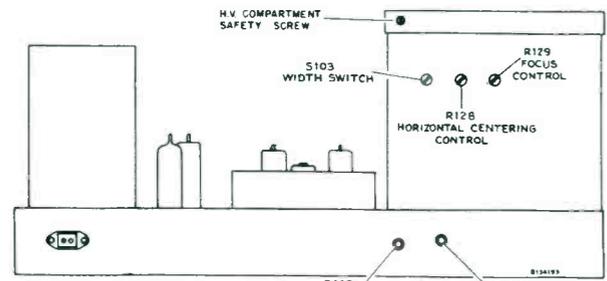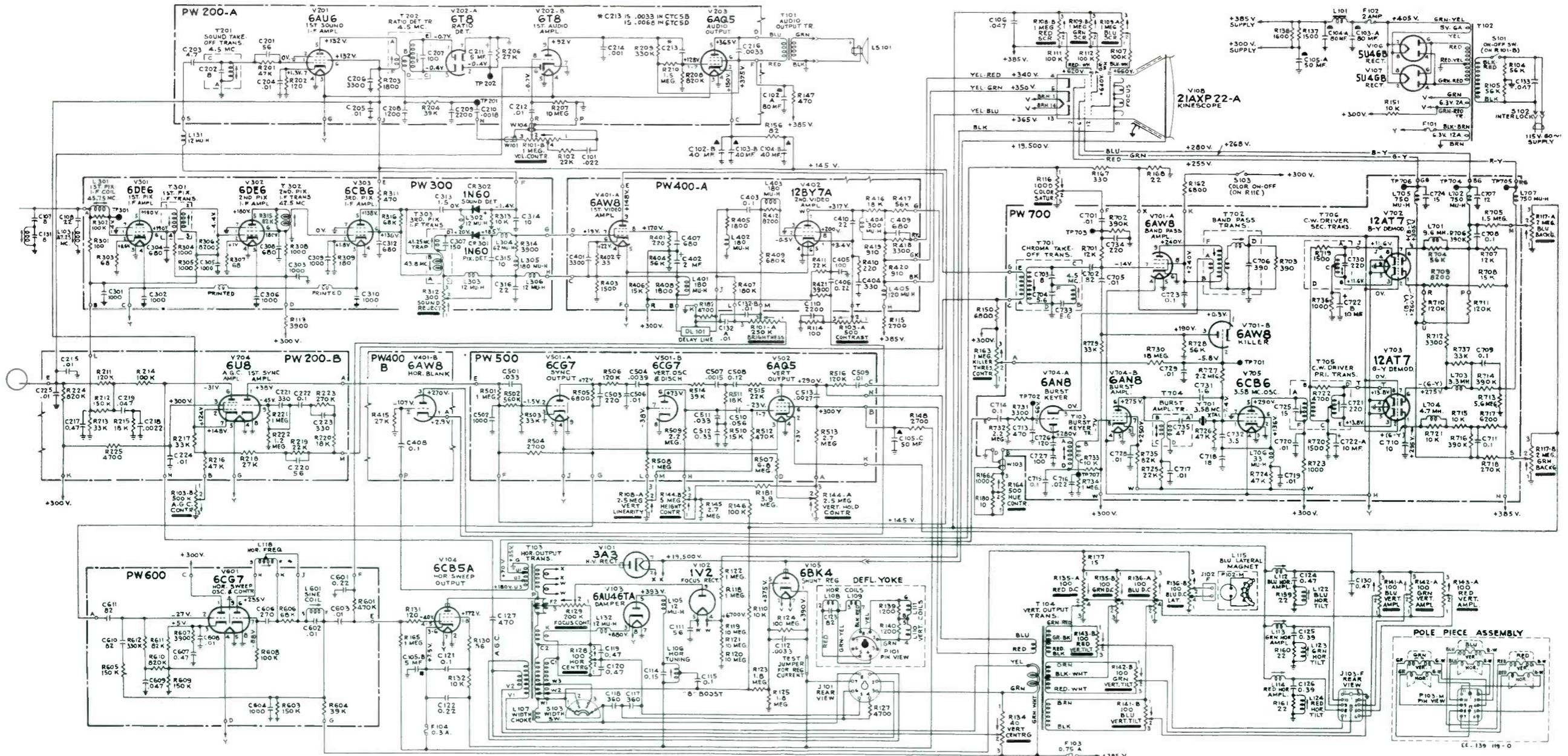

REAR CHASSIS ADJUSTMENTS

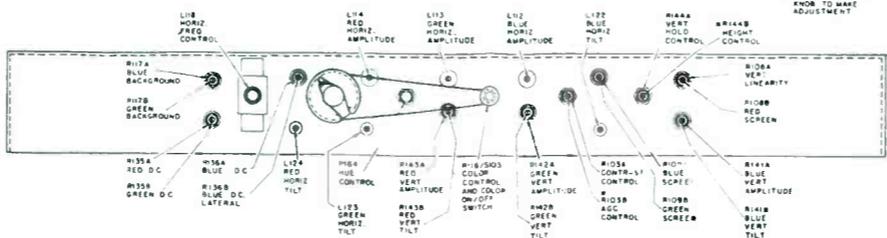

VERTICAL DYNAMIC CONTROLS






Models 21T101B, 107A, 107B, 108A, 112A
 21K112B, 113B
 21KE113A, 115A, 116A
 21KU112A, 112B, 113A, 114A, 114B, 115A, 116A
 21TU101A, 107A, 107B, 108B
 24KR126A
 24KU126A

TV CHASSIS
 V-2346
 V-2347
 V-2356
 V-2357


| Ref. No. | Part No. | Description | Function |
|----------|------------|--|-----------------------|
| C427 | 215V300M24 | Capacitor, 100 mmf 5KV | Boost |
| C505 | V15329-1 | Capacitor, elec. 160 mf 200V | Surge input |
| C506A | 218V007M01 | Capacitor, elec. 160 mf 350V (includes C402A, C419A, C506A) | Input filter |
| C507B | 218V008M01 | Capacitor, elec. 30 mf 300V (includes C507B, C508B, C509B) | Lo B \neq filter |
| C508B | 218V008M01 | Capacitor, elec. 30 mf 300V (includes C507B, C508B, C509B) | Audio B \neq filter |
| C509B | 218V008M01 | Capacitor, elec. 150 mf 300V (includes C507B, C508B, C509B) | Hi B \neq filter |
| C510 | 215V300M20 | Capacitor, 470 mmf 1.4 KV | Heater bypass |

| Ref. No. | Part No. | Description | Function |
|----------|------------|------------------------------|-------------------|
| R202 | V12709-16 | Control, 600 ohms, 1/4 W. | Quieting |
| R207 | 270V002M02 | Control, 1 megohm | Volume |
| R318 | 270V002M02 | Control, 15,000 ohms | Picture |
| R324 | 270V003M03 | Control, 100,000 ohms 1/2 W. | Brightness |
| R403A | 270V010M01 | Control, 5 megohms triplex | Sync |
| R410 | 250V421A03 | Resistor, 10,000 ohms 2W | B \neq drooping |
| R421A | 270V019M01 | Control, 5 megohms triplex | Height |
| R413 | 270V003M04 | Control, 2 megohm | Vert. hold |
| R420 | 250V224A74 | Resistor, 470,000 ohms 1/2W | Plate load |
| R436 | 270V003M02 | Control, 60,000 ohms | Horiz. hold |
| R500 | 251V011M01 | Resistor, 59 ohms 25W | Filament drooping |
| R500 | 251V015M02 | Resistor, 25W A-B-24 ohms, | Filament drooping |

| Ref. No. | Part No. | Description | Function |
|----------|------------|--|------------------------|
| R502 | 259V002M01 | Resistor, 7.5 ohms | Fusible |
| R503 | 251V017M02 | Resistor, 2,000 ohms 15W | Filter |
| R503 | 251V017M06 | Resistor, 1,800 ohms 15W (V2346-25 chassis only) | Lo B \neq decoupling |
| R504 | 251V020M01 | Resistor, 1,500 ohms 4W | Filter |
| R505 | 251V017M01 | Resistor, 180 ohms 10W | Filter |
| R507 | 251V013M01 | Thermistor, 85 ohms Cold 2W 500 ohms hot (used only on UHF receivers equipped with pilot light) | Protection On-Off |
| SW500 | 270V002M02 | Switch, (includes R207, R318, SW300, SW500) | On-Off |
| X500 | V-15920-2 | Rectifier, selenium 350 MA | Rectifier |
| X501 | V-15920-2 | Rectifier, selenium 350 MA | Rectifier |

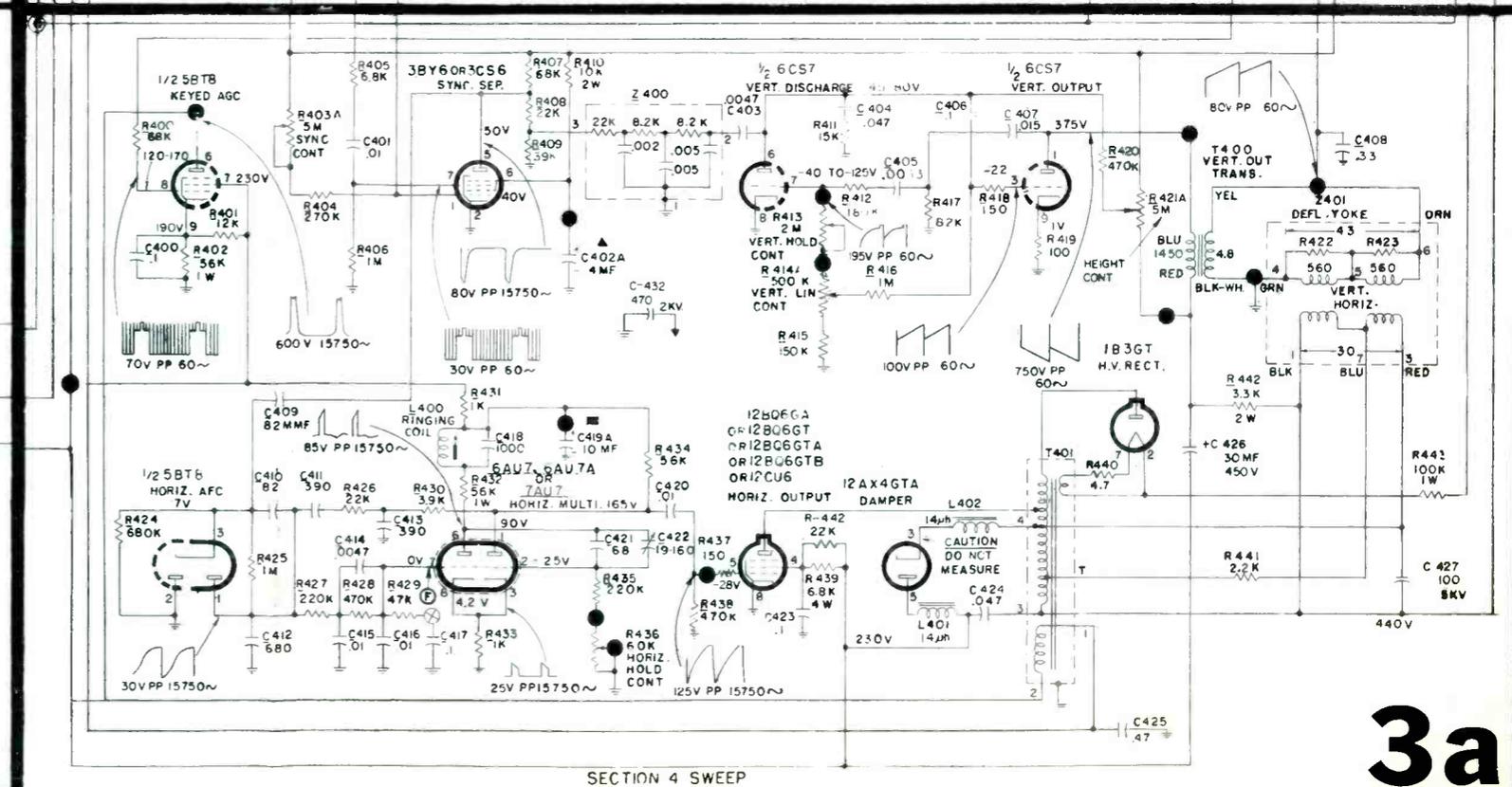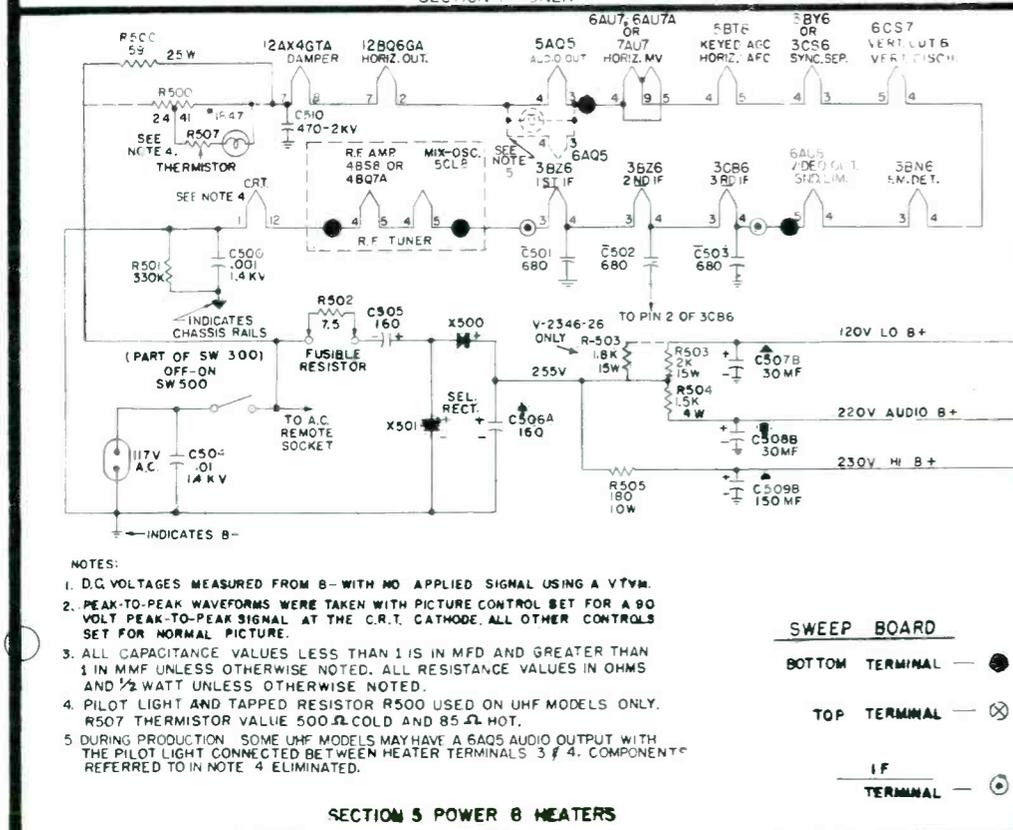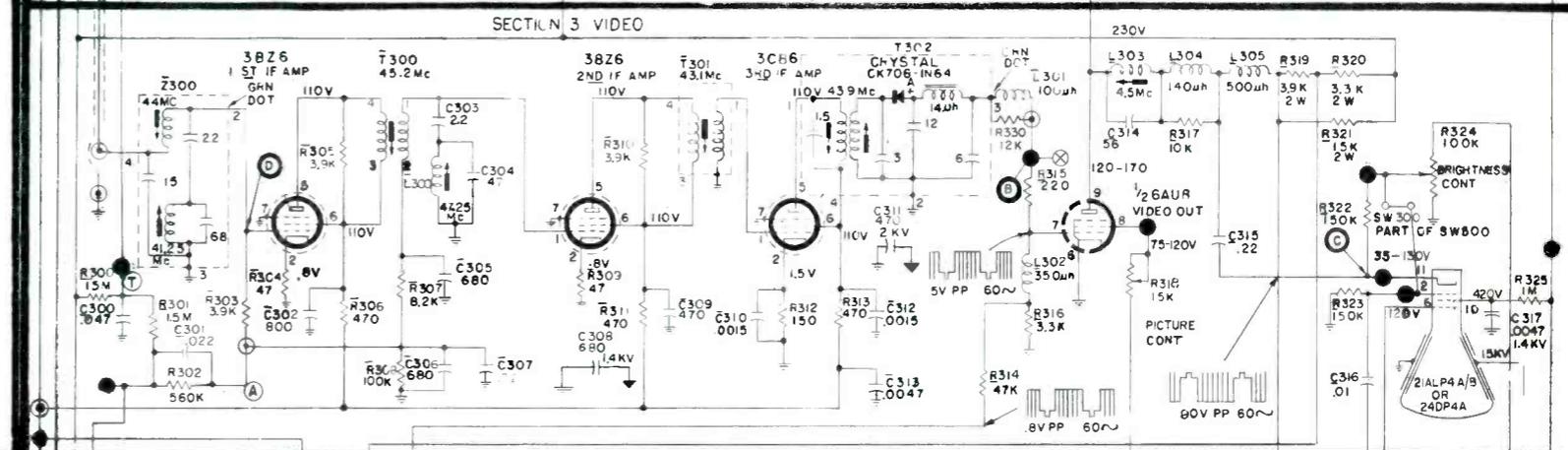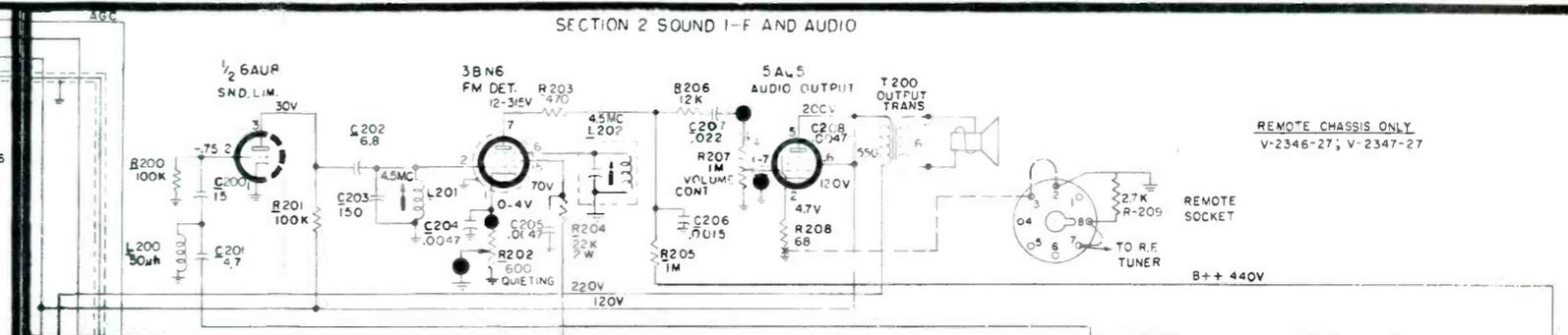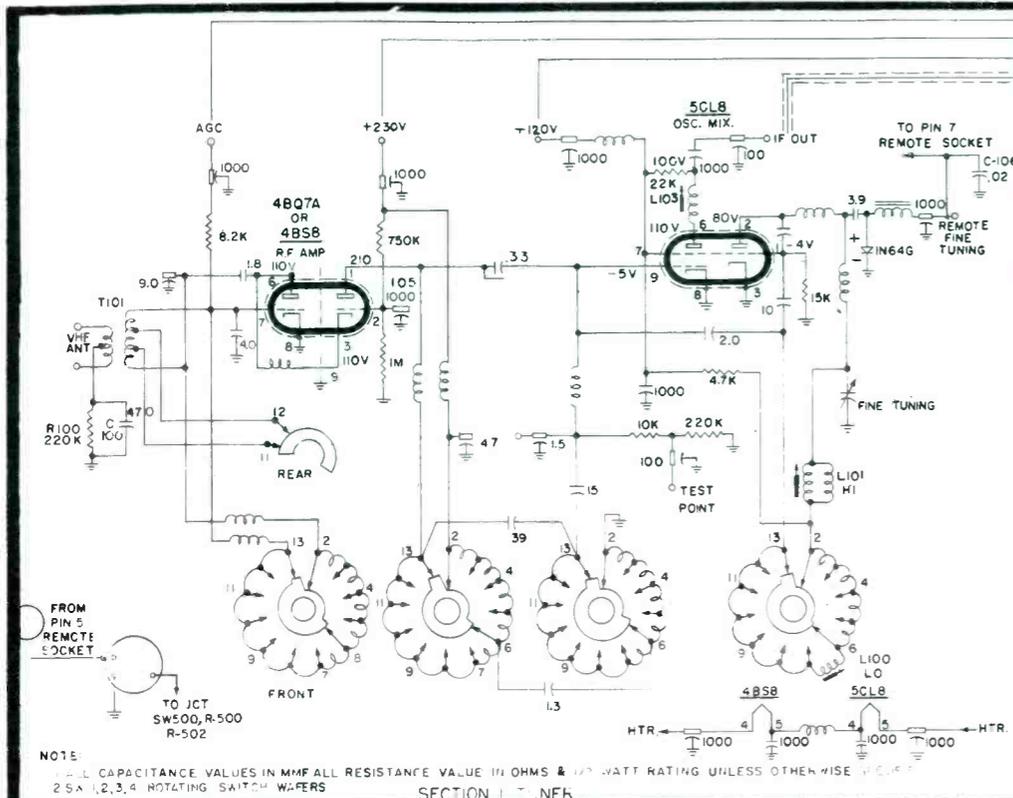




- NOTES:
- D.C. VOLTAGES MEASURED FROM B- WITH NO APPLIED SIGNAL USING A VTVM.
 - PEAK-TO-PEAK WAVEFORMS WERE TAKEN WITH PICTURE CONTROL SET FOR A 90 VOLT PEAK-TO-PEAK SIGNAL AT THE CRT. CATHODE. ALL OTHER CONTROLS SET FOR NORMAL PICTURE.
 - ALL CAPACITANCE VALUES LESS THAN 1 IS IN MFD AND GREATER THAN 1 IN MMF UNLESS OTHERWISE NOTED. ALL RESISTANCE VALUES IN OHMS AND 1/2 WATT UNLESS OTHERWISE NOTED.
 - PILOT LIGHT AND TAPPED RESISTOR R500 USED ON UHF MODELS ONLY. R507 THERMISTOR VALUE 500 Ω COLD AND 85 Ω HOT.
 - DURING PRODUCTION, SOME UHF MODELS MAY HAVE A 5AQS AUDIO OUTPUT WITH THE PILOT LIGHT CONNECTED BETWEEN HEATER TERMINALS 3 & 4. COMPONENT REFERRED TO IN NOTE 4 ELIMINATED.

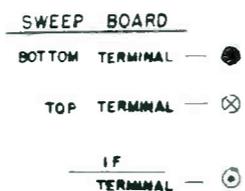


| Item No. | Part No. | Description | Power |
|----------|----------|-------------------------------------|-------|
| A1 | 87-5 | Integrator | |
| A2 | 87-4 | Integrator | |
| X1 | 103-18 | Diode Crystal | |
| R3 | 63-3609 | 7K Ohm Contrast Control | |
| R4 | 63-3264 | 500K Ohm Brightness Control | |
| R5 | 63-3284 | 750 Ohm Buzz Control | |
| R9 | 63-3625 | 350K Ohm Potentiometer A.G.C. | |
| R10 | 63-3263 | 7.5 Megohm Vertical Size Control | |
| R11 | 63-3262 | 750K Ohm Vertical Hold Control | |
| R12 | 63-3266 | 3.5K Ohm Vertical Linearity Control | |
| R14 | 63-3680 | 17 Ohm I.R.C. $\pm 10\%$ | 7 W |
| R15 | 63-3644 | 6 Ohm Fuse Type $\neq 10\%$ | 5 W |
| R16 | 63-1194 | 47K Ohm $\neq 10\%$ | 1 W |
| R17 | 63-2145 | 10K Ohm | 2 W |
| R18 | 63-2313 | 180K Ohm $\neq 10\%$ | 1 W |
| R19 | 63-3623 | 10K Ohm $\neq 10\%$ | 4 W |
| R20 | 63-3631 | 2.7 Ohm \bar{W} | 1/2 W |
| R23 | 63-3696 | 1 Megohm Volume Control | |
| T6 | 95-1534 | Audio Output Transformer | |
| T7 | 95-1535 | Vertical Output Transformer | |
| T8 | 95-1527 | Deflection Coil | |
| T10 | S-40284 | Horizontal Sweep Transf. | |
| T11 | 95-1543 | Filter Choke | |
| SE1 | 212-19 | Selenium Rectifier | |
| SE1 | 212-14 | Selenium Rectifier (Alt) | |
| SE2 | 212-19 | Selenium Rectifier | |
| SE2 | 212-14 | Selenium Rectifier (Alt) | |

VHF BAND SWITCH TUNER S-40282

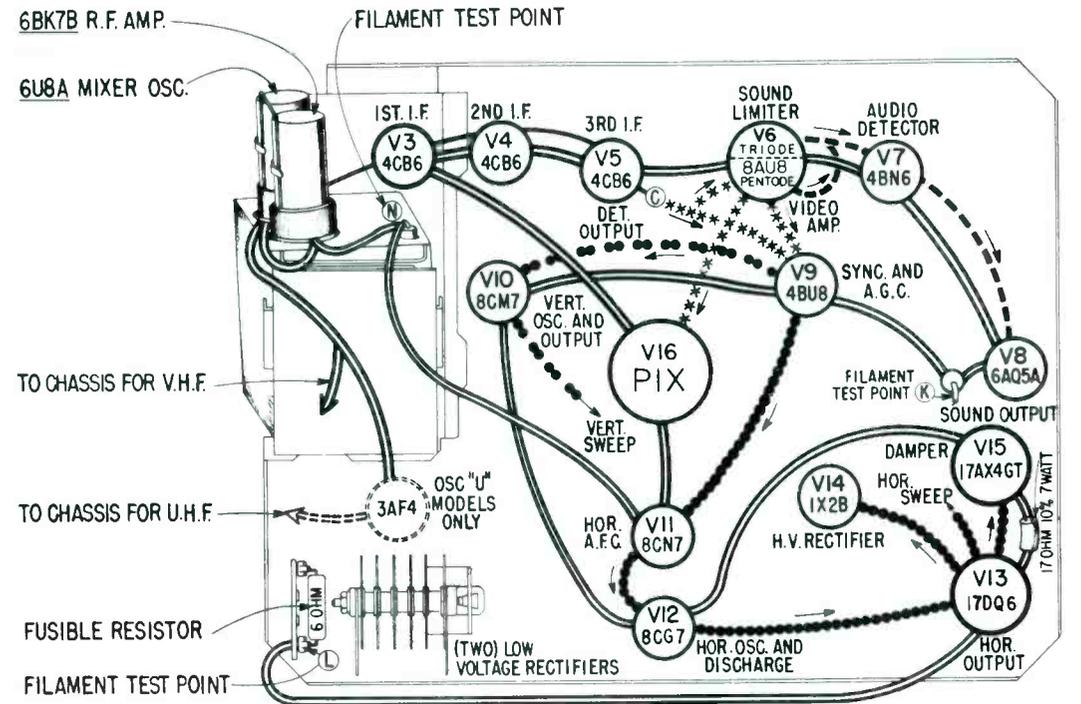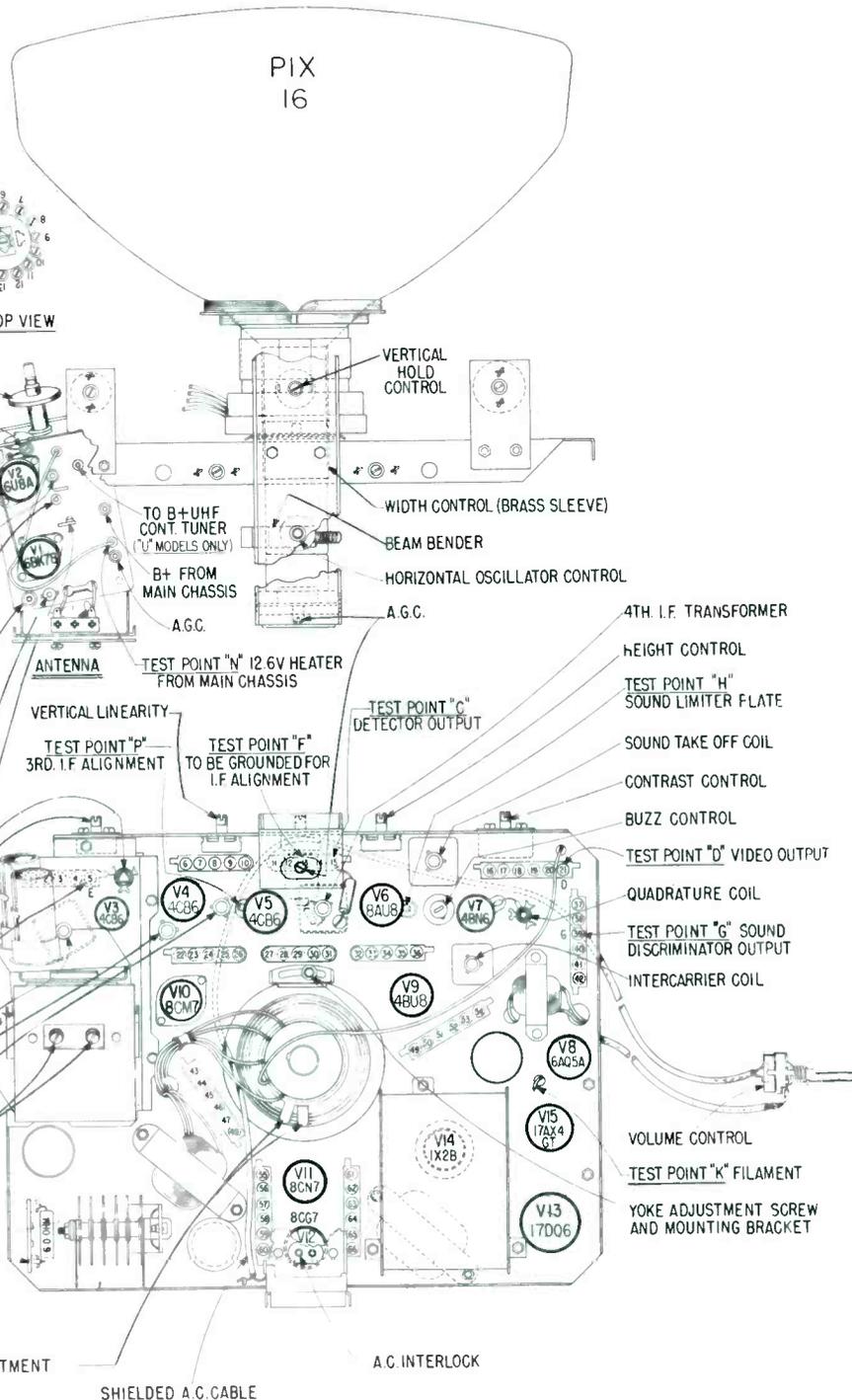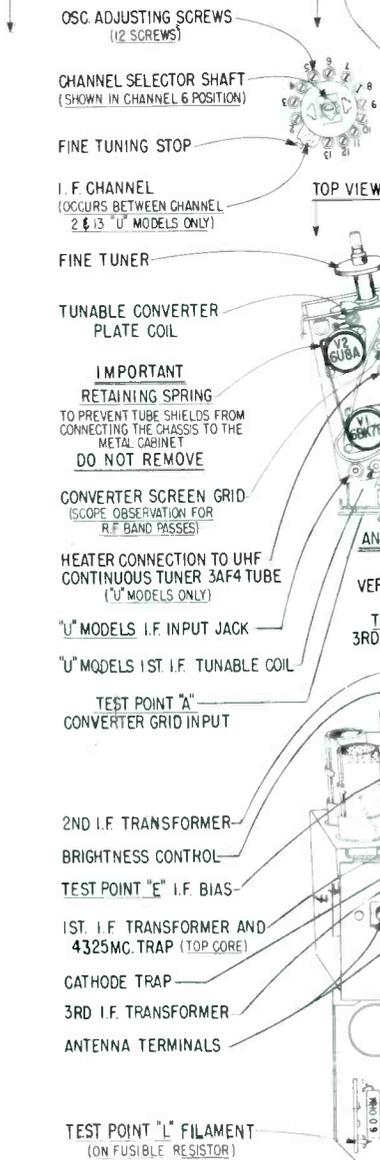AS SHOWN BELOW.
NOTE: "U" MODEL INCORPORATE A UHF CONTINUOUS TUNER S-40504 AND A S-40283 VHF TUNER. REFER TO 16Z20U CHASSIS FOR ADJUSTMENTS



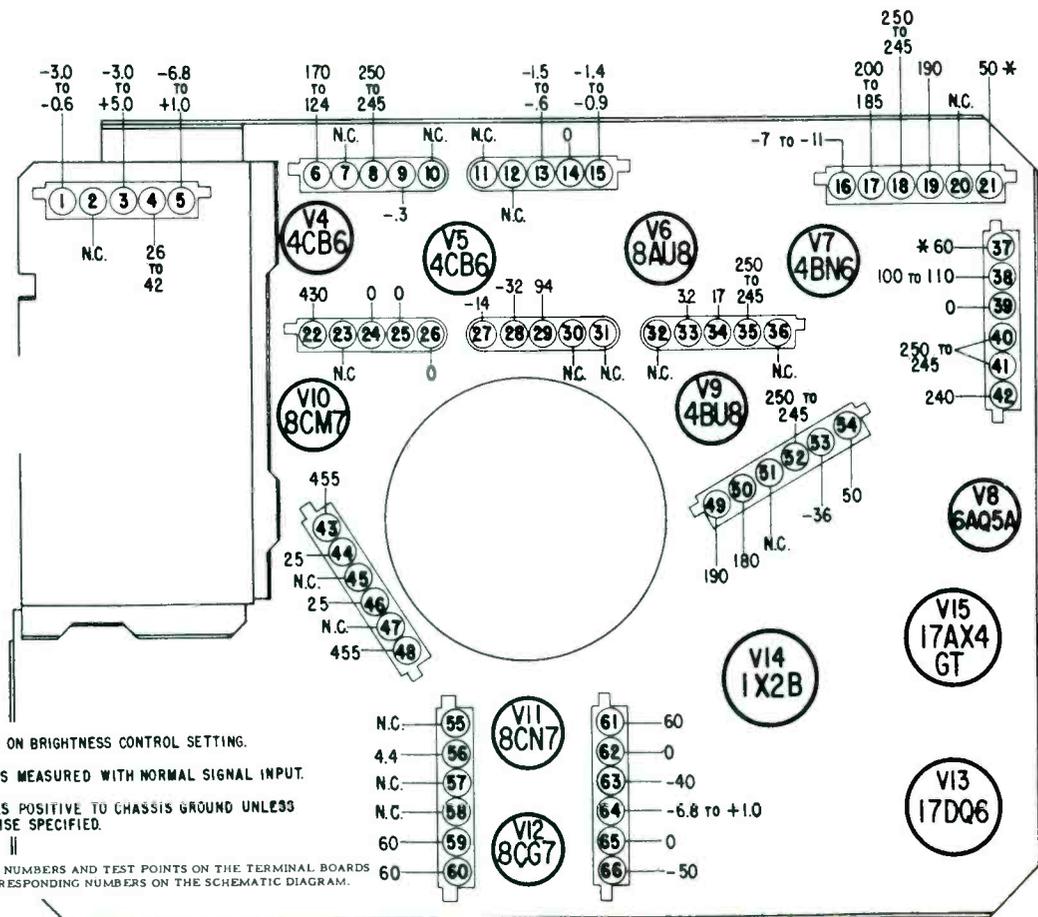FILAMENTS
SOUND CIRCUIT
COMPOSITE VIDEO *****
60 CYCLES
VERTICAL CIRCUIT
HORIZONTAL CIRCUIT
INTERMEDIATE FREQUENCY
VOLTS 117 AC
WATTS 160



Advertisers Index

| | |
|--|-------------|
| Acme Electric Corporation | 45 |
| Aermotor Company | 51 |
| Aerovox Corporation | 5 |
| Amphenol Electronics Corporation | 1 |
| Anchor Products Company | 50 |
| Astatic Corporation | 49 |
| | |
| B, & K Manufacturing Co. | 21, 36 |
| Barry Electronics Corp. | 54 |
| Belden Manufacturing Co. | Cover 3 |
| Blonder-Tongue Laboratories, Inc. | 26 |
| Bussmann Manufacturing Co. | 4 |
| | |
| CBS-Hytron | 23 |
| Channel Master Corp. | 2, 3 |
| Chicago Standard Transformer Corp. | 53 |
| Clarostat Manufacturing Co., Inc. | 25 |
| Clear Beam Antenna Corp. | 32 |
| Cornell-Dubilier Elec. Corp. | 22, Cover 2 |
| | |
| Eico | 52 |
| Electrend Products Corp. | 50 |
| Electronic Publishing Co. | 44 |
| Electro Products Labs, Inc. | 16 |
| Electro-Voice, Inc. | 17 |
| Erie Resistor Corp. | 53 |
| | |
| Federated Television Mart | 50 |
| | |
| General Cement Mfg. Co. | 10 |
| | |
| Heath Company | 51 |
| Hickok Electrical Instrument Co. | 53 |
| Hotpoint Company, Div. of General Electric Co. | 33 |
| | |
| Jensen Manufacturing Company | 35 |
| JFD Manufacturing Co., Inc. | 13, 14 |
| Lektron Specialties | 52 |
| Merit Coil & Transformer Corp. | 43 |
| North American Phillips Co., Inc. | 42 |
| Oelrich Publications | 53 |
| | |
| Philco Corporation | 11 |
| Planet Sales Corp. | 52 |
| Pyramid Electric Company | 47 |
| | |
| Quietrol Company | 51 |
| | |
| RCA Tubes | Cover 4 |
| Radiart Corporation | Cover 2 |
| Raytheon Manufacturing Co. | 7 |
| Rider, John F., Publisher | 46 |
| | |
| Sonotone Corporation | 20 |
| South River Metal Products Co. | 54 |
| Sprague Products Company | 34, 51, 54 |
| | |
| Technical Appliance Corp. | 22 |
| Trio Manufacturing Co. | 37 |
| Tung-Sol Electric, Inc. | 38, 39 |
| | |
| Xcelite, Inc. | 52 |



If it's worth the cost of installation...



...it's worth the cost of engineered cable



Belden

**TRANSMISSION
LINES**

**•
ROTOR CABLES**

Superior Cables engineered for the job—
In a complete line for every requirement.
Packaged for easy handling.

"More items from the Complete Belden Line"

Belden

WIREMAKER FOR INDUSTRY
SINCE 1902
CHICAGO

9-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable

Win bigger
picture-tube profits

Join the RCA

Silverama

CRUSADE FOR PROFITS

The top picture-tube line on the market . . . Compelling national advertising . . . The most forceful promotional material in picture-tube history . . . These join forces now to spearhead your CRUSADE FOR PROFITS in RCA's newest selling campaign for Silverama Super-Aluminized Picture Tubes.

RCA paves the way with a barrage of national advertising in *Life*, *TV Guide*, the *Saturday Evening Post*, and on the N.B.C. TV and Radio Networks.

And, to help you cash-in on this CRUSADE FOR PROFITS, your RCA Distributor is ready now with a winning array of RCA Silverama sales promotion material—window displays, decals, streamers, local spot commercials by Vaughn Monroe, direct-mailers, and consumer give-away items.

So, join the Crusade now. There's a selling-season of profits waiting to be won over by you. See your RCA Distributor immediately.



PICTURE TUBES

RADIO CORPORATION OF AMERICA, HARRISON, N. J.



CHWAN PUBLISHING CORP., 67 West 44th St. el., New York 36, N. Y.



SERVICE DEALER
and ELECTRONIC SERVICING

A CT 244
MERB'S TV
M A KAURANEN
11666 HUBBELL
DETROIT 27 MICH