

**SCIENCE and
MECHANICS**

33 Construction Projects • SWL

RADIO-TV EXPERIMENTER

75c No. 576

- VHF RECEIVER
- TRANSISTOR TESTER
- VOLT-OHMMETER
- MULTI-LAB
- TELEPHONE SENTRY
- OPINION METER
- MAKING TRANSFORMERS
- PARABOLIC MIKE
- BATTERY RECHARGER
- FIELD STRENGTH INDICATOR
- CODE PRACTICE EQUIPMENT

and

**WHITE'S
RADIO
LOG**

500 Changes • New, Up-to-Date
AM-FM-TV STATICS
WORLD-WIDE SHORT WAVE

**Amplifier Input / Output Comparison
with 'Scope Attachment, page 47**



SPRING 1961

THE SIGN OF RAD-TEL'S QUALITY PERFORMANCE

**BUY DIRECT FROM
RAD-TEL!!**

**ORDER RAD-TEL'S
FIRST QUALITY TUBES TODAY!
NOT USED!! NOT PULLED OUT OF SETS!!**

**SERVICEMEN: HUGE SAVINGS!! COMPARE!!
FAST ONE DAY SERVICE.**



GUARANTEED ONE FULL YEAR UP TO 75% OFF ON BRAND NEW TUBES

**SEND FOR FREE TROUBLE SHOOTER
GUIDE AND NEW TUBE & PARTS CATALOG**

TRANSISTORS — AT FABULOUS DISCOUNTS

PRICE	TYPE	RATING	ELECTRICAL CHARACTERISTICS		hfe
RF 49¢ AF 39¢	GE PNP ALLOY JUNCTION GENERAL PURPOSE RF/AF	200 MW	1CBO max. 20 μa VCB -3V	1EBO max. 20 μa VEB -3V	VCE -1.5 Ib 5 ma 20 min
80¢ ea.	Power AF Mgd. Freq. to -3		20 ma VCB -16V	20 ma VEB -16V	VCE -1.5 Ib 1 ma 40 min
140¢ ea.	Hi Power 15 AMP to 36	MIN. POWER OUTPUT 2 25 W	40 ma VCB -100	40 ma VEB -100	VCE -1.5 Ib 1 ma 30 min

**SILICON
RECTIFIER**

35 AMP
50 PIV
(max. 20 ma)

\$2.50 ea.

Lots of 10
\$2 25 ea.
(No Hardware)



NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY

RAD-TEL TUBE CO.

55 CHAMBERS STREET, NEWARK 5, N. J. DEPT. RTV-261

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. No COO's outside continental USA.

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	024M	.79	—	6AW8	.89	—	12AF6	.49
—	1AX2	.62	—	6AX4	.65	—	12AI6	.46
—	1B3GT	.79	—	6AX7	.64	—	12AL5	.45
—	10N5	.55	—	6BA6	.49	—	12AL8	.95
—	1G3	.73	—	6BC5	.54	—	12A05	.52
—	1J3	.73	—	6BC7	.94	—	12AT6	.43
—	1K3	.73	—	6BC8	.97	—	12AT7	.76
—	1L6	1.05	—	6BD6	.51	—	12AU6	.50
—	1LN5	.59	—	6BE6	.55	—	12AU7	.60
—	1R5	.62	—	6BF6	.44	—	12AV5	.97
—	1S5	.51	—	6BG6	1.66	—	12AV6	.41
—	1T4	.58	—	6BM6	.65	—	12AV7	.75
—	1U4	.57	—	6BH8	.87	—	12AX4	.67
—	1U5	.50	—	6BI6	.62	—	12AX7	.63
—	1X2B	.82	—	6BK7	.85	—	12AZ7	.86
—	2AF4	.96	—	6BL7	1.00	—	12B4	.63
—	3AL5	.42	—	6BN4	.57	—	12BA6	.50
—	3AUG	.51	—	6BN6	.74	—	12B06	.50
—	3AV6	.41	—	6BQ5	.65	—	12BE6	.53
—	3BA6	.51	—	6BQ6GT	1.05	—	12BF6	.44
—	3BC5	.54	—	6BQ7	.95	—	12BM7	.73
—	3BE6	.52	—	6BR8	.78	—	12BL6	.56
—	3BN6	.76	—	6BU8	.70	—	12BQ6	1.06
—	3BU8	.78	—	6BY6	.54	—	12BY7	.74
—	3BY6	.55	—	6BZ6	.54	—	12BZ7	.75
—	3BZ6	.55	—	6C27	.97	—	12C5	.56
—	3CB6	.54	—	6C4	.43	—	12CA5	.59
—	3CF6	.60	—	6CB6	.54	—	12CN5	.56
—	3CS6	.52	—	6CD6	1.42	—	12CR6	.54
—	3CY5	.71	—	6CF6	.64	—	12CU5	.58
—	3OK6	.60	—	6CG7	.60	—	12CU6	1.06
—	3OT6	.50	—	6CG8	.77	—	12CX6	.54
—	3Q5	.80	—	6CM7	.66	—	12DB5	.69
—	3S4	.61	—	6CN7	.65	—	12DE8	.75
—	3V4	.58	—	6CR6	.51	—	12DL8	.85
—	4BC5	.56	—	6CS6	.57	—	12DM7	.67
—	4BC8	.96	—	6CU5	.58	—	12DQ6	1.04
—	4BN6	.75	—	6CU6	1.08	—	12DS7	.79
—	4BQ7	.96	—	6CY5	.70	—	12DZ6	.56
—	4BS8	.98	—	6CY7	.71	—	12EL6	.50
—	4BU8	.71	—	6DA4	.68	—	12EG6	.54
—	4BZ6	.58	—	6DB5	.69	—	12E76	.53
—	4BZ7	.96	—	6DE6	.58	—	12F5	.66
—	4CS6	.61	—	6DG6	.59	—	12F8	.66
—	4OE6	.62	—	6DQ6	1.10	—	12FM6	.45
—	4DK6	.60	—	6DTS	.76	—	12K5	.65
—	4DT6	.55	—	6DT6	.53	—	12SA7M	.86
—	5AM8	.79	—	6EUB	.79	—	12SK7GT	.74
—	5AN8	.86	—	6EAB	.79	—	12SN7	.67
—	5AQ5	.52	—	6H6GT	.58	—	12SQ7M	.73
—	5AT8	.80	—	6J5GT	.51	—	12U7	.62
—	5BK7A	.82	—	6J6	.67	—	12V6GT	.53
—	5BQ7	.97	—	6K6	.63	—	12W6	.69
—	5BR8	.79	—	6S4	.48	—	12X4	.38
—	5CG8	.76	—	6SA7GT	.76	—	17AX4	.67
—	5CL8	.76	—	6SK7	.74	—	17BQ6	1.09
—	5EA8	.80	—	6SL7	.80	—	17C5	.58
—	5EU8	.80	—	6SN7	.65	—	17CA5	.62
—	5I6	.68	—	6SQ7	.73	—	17D4	.69
—	5I8	.81	—	6T4	.99	—	17DQ6	1.06
—	5U4	.60	—	6U8	.78	—	17L6	.58
—	5U8	.81	—	6V6GT	.54	—	17W6	.70
—	5V6	.56	—	6W4	.54	—	19AU4	.83
—	5X8	.78	—	6W6	.69	—	19BQ6	1.39
—	5Y3	.46	—	6X4	.39	—	19T8	.80
—	6AB4	.46	—	6X5GT	.53	—	21EX6	1.49
—	6AC7	.96	—	6X8	.77	—	25BQ6	1.11
—	6AF3	.73	—	7AU7	.61	—	25C5	.53
—	6AF4	.97	—	7A8	.68	—	25CA5	.59
—	6AG5	.65	—	7B6	.69	—	25C06	1.44
—	6AH6	.99	—	7Y4	.69	—	25C06	1.11
—	6AK5	.95	—	8AU8	.83	—	25ON6	1.42
—	6ALS	.47	—	8AW8	.93	—	25EH5	.55
—	6AM8	.78	—	8BQ5	.60	—	25L6	.57
—	6AN4	.95	—	8CG7	.62	—	25W4	.68
—	6AN8	.85	—	8CM7	.68	—	25Z6	.66
—	6AQ5	.50	—	8CN7	.97	—	35C5	.51
—	6AR5	.55	—	8CX8	.93	—	35L6	.57
—	6AS5	.60	—	8E88	.94	—	35W4	.52
—	6AT6	.43	—	11CY7	.75	—	35Z5GT	.60
—	6AT8	.79	—	12A4	.60	—	50B5	.60
—	6AU4	.82	—	12AB5	.55	—	50C5	.53
—	6AU6	.50	—	12AC6	.49	—	50C4	.37
—	6AU7	.61	—	12AD6	.57	—	50EH5	.55
—	6AU8	.87	—	12AE6	.43	—	50L6	.61
—	6AV6	.40	—	12AF3	.73	—	117Z3	.61

RADIO-TV EXPERIMENTER

Spring 1961 Edition

Sloyd D. Parkell

Now Amateurs Are Working Meteor Trails	14	Amplifier that Drives Speaker Directly....	83
Needles Aid Communication.....	18	Wind-It-Yourself Brightener.....	86
Acce-Deucey VHF Receiver.....	23	Ham Radio Anagram.....	88
Transistor Tester.....	27	Nerve Tester.....	89
Printed Circuit Phono Amplifier.....	29	Trouble-Shooting Interference.....	91
Transistor Circuit Designer.....	32	Curing Tape Recorder Noise.....	94
The Little Cub Receiver.....	35	Fishing Thermometer.....	95
Beginner's Volt-Ohmmeter.....	37	Portable Record Player.....	99
What Is It?.....	38	Add a Speaker System to Your TV.....	104
Field-Strength Indicator.....	39	Versatile Code Practice Equipment.....	107
Multi-Testing Lab.....	41	Quintuplet Duty for Radio.....	111
What to Listen for on Short Wave.....	45	The DX Strip.....	113
'Scope Electronic Switch and Voltage Calibrator.....	47	Transistorized Audio Amplifier.....	115
Battery Eliminator.....	52	Analog Computer Theory.....	118
Five Transistor Audio Amplifier.....	54	Plug-in TV Antennas.....	121
AC Line Voltage Regulator.....	57	Electronics—Father and Son Hobby.....	125
Amateur Radio Numbersgram.....	59	Using Positive Feedback.....	127
Sound Searching Parabolic Mike.....	60	Code Practice Oscillator.....	131
Opinion Meter.....	63	Transistorized Electronic Megaphone.....	133
Dual Capacitor Substitution Box.....	65	Grandpappies of the Call Books.....	139
Antenna Switchboard.....	67	Transistor Hybrid Parameters.....	142
Telephone Sentry.....	68	Recharger for Dry Batteries.....	143
Electrical Right-Wrong Game.....	73	Door Bell Silencer.....	147
Low-Voltage Power Supply.....	75	Noise Filter for Record Playing.....	148
Adapting Meters for Test Equipment.....	77	Short Wave Receiver.....	149
Radio Hobbyist Anagram.....	80	Custom-Making Transformers.....	153
Variable DC Power Supply.....	81	Remote TV-Radio Sound Silencer.....	162
		WHITE'S RADIO LOG.....	163

Cover by Harold R. Stluka

B. G. DAVIS
Publisher

JOEL DAVIS
Assistant Publisher

HERB SIEGEL
Editor

LYNELL A. JOHNSON
Assistant Editor

LEROY R. KIETZMAN
Editorial Assistant

BILL WADKINS
Art Director

RAY FORSBERG
Advertising Manager

Published and Copyrighted 1961 by
SCIENCE AND MECHANICS PUBLISHING COMPANY

A Subsidiary of Davis Publications, Inc.

450 East Ohio Street

Chicago 11, Illinois

The Radio-TV Experimenter contains a selected few of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subjects appearing for the first time.

Science and Mechanics Handbook Annual No. 5, 1961—No. 576

Advertising Offices: Chicago: 450 E. Ohio St., WH 4-0330; New York: 527 Madison Ave., PL 3-9377; Los Angeles: 560 N. Larchmont Blvd., HO 6-2854; Detroit: 2755 Woodstock, UN 3-5267.

COMPLETE SERVICE TRAINING
... written so you can understand it!



Fix any TV or Radio Ever Made

EASIER - BETTER - FASTER!

No complicated theory or mathematics! These famous Ghirardi books get right down to brass tacks in showing you how to handle all types of AM, FM and TV service work by approved professional methods. Almost 1500 pages and over 800 clear illustrations show how to handle every phase of troubleshooting and servicing. Each book is co-authored by A. A. Ghirardi whose manuals have helped train more servicemen than any other books of courses of their kind!

1—Radio and Television Receiver TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the beginner, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" troubleshooting charts that show what to look for and where. 820 pages, 417 illustrations, price \$10.00 separately.

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$9.00.

Special low price . . . you save \$2.00

If broken into lessons and sent to you as a "course," you'd regard these two great books as a bargain at \$100 or more! Under this new offer, you buy both books for only \$17.00. No lessons to wait for. You learn fast—and right!

STUDY 10 DAYS FREE!

Dept. MH-31, HOLT, RINEHART & WINSTON, Inc.
Technical Div., 383 Madison Ave.,
New York 17, N. Y.

Send books below for 10-day FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$10.00 separately)

Radio & TV CIRCUITRY & OPERATION (Price \$9.00)

Check here for MONEY-SAVING COMBINATION OFFER. Save \$2.00. Send both of above big books at special price of only \$17.00 for the two. (Regular price \$19.00 . . . you save \$2.00.)

SAVE! Send cash with order and we pay postage. Same return privilege with money promptly refunded.

Name

Address

City, Zone, State

Outside U.S.A.—\$10.50 for TROUBLESHOOTING & REPAIR; \$9.50 for CIRCUITRY & OPERATION; \$18.00 for both. Cash only, but money refunded if you return books in 10 days.



ROCKHOUNDS! *It's finally available again!*
Gem Hunter's Guide!

• Russ MacFall's new and completely revised guide to North American gem locations, the *Gem Hunter's Guide*, in addition to its comprehensive listing of locations, contains 81 maps pinpointing rich and secluded native gemstone sites . . . Plus full-color, natural-size photos of 53 different gems shown as they occur in nature . . . Plus a detailed text explaining hunting methods, field testing and identification techniques and special chapters devoted to the most valuable gems. To get your copy, send \$3.95 to Dept. 126, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois. Money-back guarantee. No C.O.D.'s or stamps, please.

- 53 Natural Color Gem Photos!**
- 81 Detailed Maps!**
- 1034 Gem Mineral Locations!**

Back-Issue Treasures!




VERY LIMITED QUANTITY, 6 FOR \$1.00

We've been housecleaning. And what do you think we've found? A rare treasure-lode of back issues of SCIENCE AND MECHANICS. Hundreds and hundreds of copies in good condition, all issues from 1959 and 1960. Would you like to share this find with us? Send us \$1.00. We'll send you 6 (yes, six) assorted back issues. First come, first served—offer good until supply is exhausted.

SCIENCE and MECHANICS Magazine
450 East Ohio Street, Dept. 733, Chicago 11, Illinois

HOW TO BREAK INTO RADIO-TV-ELECTRONICS

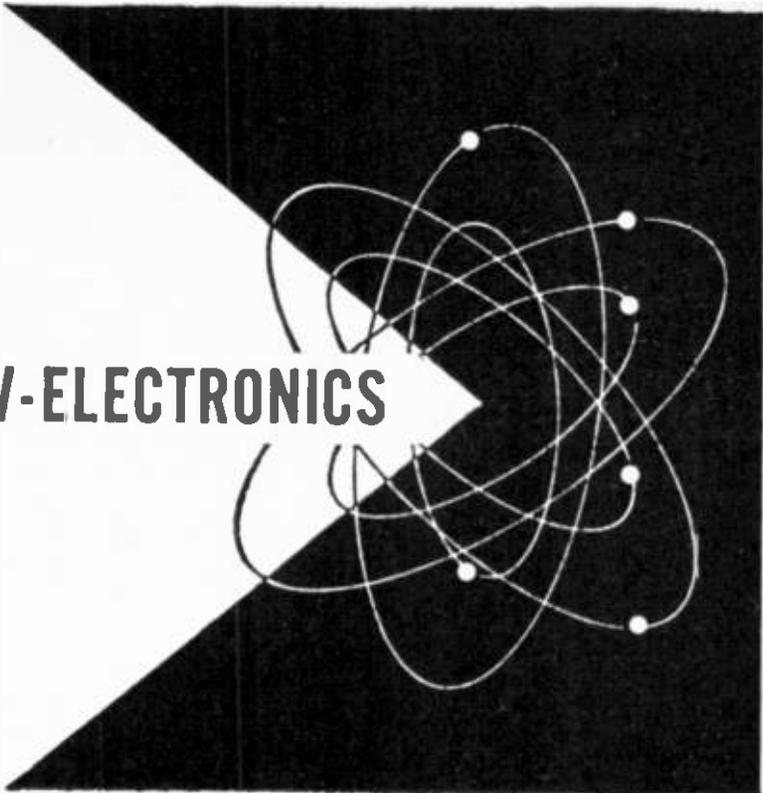

A good paying career in Radio-TV-Electronics may be closer than you think—regardless of your age, education or present job experience.

You know about the tremendous demand for radio-TV and electronics technicians. But something perhaps you didn't know is how easy it is to get the training that will qualify you for this vital work, and how quickly you can advance.

From the very beginning you will find that your I.C.S. course is preparing you thoroughly—at your own pace—for an exciting new career. I.C.S. Radio-TV-Electronics courses make electronic fundamentals clear, easy to follow. You get *personalized* guidance from people who know—and can tell you—what it takes to succeed along every step of the way.

The I. C. S. method makes it possible to learn while you earn. You study at home—in your spare time. Everything you learn is practical, usable. Your mastery of Radio-TV-Electronics assures you of top

pay and real job security in one of today's fastest growing fields.

So if you would like to break into Radio-TV-Electronics—your first step is to send for your FREE I.C.S. Career Kit. There's no obligation... and there's a whole new future to gain.

Send coupon below for your free I.C.S. Career Kit!

- 1 "How to Succeed" career guide
- 2 "Career Catalog" of job opportunities in your field of interest
- 3 "Sample Lesson" (math) to demonstrate the famous I.C.S. method



For Real Job Security—Get an I.C.S. Diploma!

I. C. S., Scranton 15, Penna.

Accredited Member, National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 45115B, SCRANTON 15, PENNA.

In Hawaii reply P.O. Box 418, Honolulu

(Partial list of courses)

Without cost or obligation, send me "How to Succeed" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

RADIO TELEVISION ELECTRONICS

- General Electronics Tech.
- Industrial Electronics
- Practical Radio-TV Eng'r'g
- Practical Telephony
- Radio-TV Servicing

BUSINESS

- Cost Accounting
- Managing a Small Business
- Purchasing Agent

DRAFTING

- Electrical Drafting

HIGH SCHOOL

- High School Diploma
- Good English
- High School Mathematics

ELECTRICAL

- Electrical Engineering
- Elec. Engr. Technician
- Elec. Light and Power
- Practical Electrician
- Professional Engineer (Elec.)

LEADERSHIP

- Industrial Foremanship
- Industrial Supervision
- Personnel-Labor Relations
- Supervision

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to _____ P.M. _____

Occupation _____

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special low monthly tuition rates to members of the U. S. Armed Forces.

Abraham Marcus, co-author of famous best-seller "Elements of Radio" makes amazing offer!



TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books get right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls.

DON'T WAIT! You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.



WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned radio-frequency tuner—AC-DC superheterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and re-adjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments, such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.

MAIL THIS COUPON

Prentice-Hall, Inc., Dept. 5747-82
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.60, plus a few cents postage. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.60 a month for two months.

Name
Address
City Zone State

TAACD TV ACCESSORIES

Multi-set couplers, multi-antenna couplers and every accessory for an A-1 installation for TV or FM.

TECHNICAL APPLIANCE CORPORATION
SHERBURNE, N. Y.

INVENTIONS WANTED

140 Wealthy Manufacturers Ready to Pay Top Prices

Do you have an idea for a new product or a way to improve a product already in use—patented or unpatented—you would like to sell for cash or lease on royalty? If so, send your name and address on a post card—NOW—for FREE details explaining how you can turn your "Big Ideas" into big money.

SCIENCE AND MECHANICS MAGAZINE
450 East Ohio Street • Dept 432 • Chicago 11, Illinois

new! 7-Band SWL/DX Dipole Kit for 11·13·16·19·25·31·49 meters

Here's a low cost 7-band receiving dipole antenna kit that will pick up those hard-to-get DX stations. Everything included . . . just attach the wires and you're on the air! Weatherproof traps enclosed in Poly-Chem for stable all-weather performance. Overall length of antenna - 40 feet.

Complete with
8 Trap Assemblies
Transmission Line Connector
Insulators
45 ft. No. 16 Tinned Copper Wire
100 ft. of 75 ohm twin lead

WRITE FOR NAME OF NEAREST DISTRIBUTOR **SWL-7 \$14.75**

Mosley Electronics, Inc. 4610 N. Lindbergh • Bridgeton, Missouri


These men are getting practical training in **NEW Shop-Labs of**

ELECTRICITY

ELECTRONICS

ON REAL

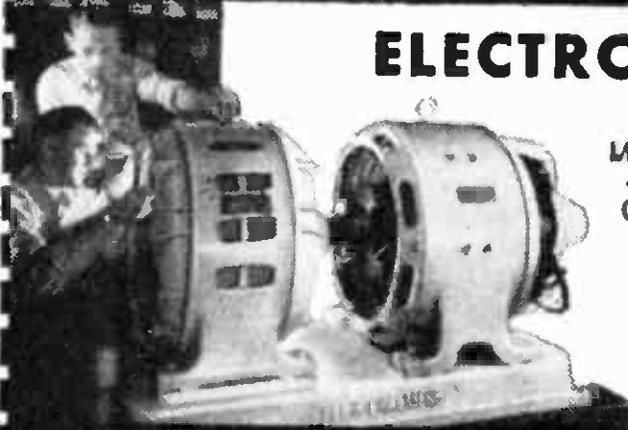- Motors—Generators
- Switchboards—
- Controls—Modern
- Appliances—
- Automatic
- Electronic
- Control Units



TELEVISION

RADIO ELECTRONICS

ON REAL

- TV Receivers—
- Black and White
- and Color
- AM-FM and
- Auto Radios
- Transistors
- Printed Circuits
- Test Equipment



COYNE

in Chicago—prepare for today's **TOP OPPORTUNITY FIELD**. Train on real full-size equipment at **COYNE** where thousands of successful men have trained for over 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. **Employment Service to Graduates.**

START NOW—PAY LATER—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK—**"Guide to Careers" which describes all training offered in **ELECTRICITY** and **TELEVISION-RADIO ELECTRONICS**—no obligation; **NO SALESMAN WILL CALL.**

Coyne Electrical School, 1501 W. Congress Parkway
Chartered Not For Profit • Chicago 7, Dept. 31-7C

MAIL COUPON OR WRITE TO ADDRESS BELOW

COYNE ELECTRICAL SCHOOL
Dept. 31-7C—New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **BIG FREE** book and details of all the training you offer. However, I am especially interested in:

- Electricity Television Both Fields

Name _____

Address _____

City _____ State _____



COYNE offers
LOW COST

TELEVISION

RADIO-COLOR TV

Training in
Spare Time AT HOME

The future is **YOURS** in **TELEVISION!**

A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost —you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including Radio, UHF and Color TV. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—*make money early in course.* Free Lifetime Employment Service to Graduates.

COYNE ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION
NOT FOR PROFIT
1501 W. Congress Parkway • Chicago 7, Dept. 31-H7



B. W. COOKE, Jr., President
Coyne—the Institution behind this training... the largest, oldest, best equipped residential school of its kind. Founded 1899.



Send Coupon or write to address below
for Free Book

and full details,
including easy
Payment Plan.
**No obligation, no
salesman will call.**



COYNE Television Home Training Division

Dept. 31-H7, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____

Address _____

City _____ State _____

AMERICAN BASIC SCIENCE CLUB

Sensational LOW COST SCIENCE LAB

NOW over 110 fascinating projects with



These Kits Developed with World Famous SOUTHWEST RESEARCH INSTITUTE and are a TRUE BASIC SCIENCE COURSE

NO EXPERIENCE NECESSARY

- The 8 instruction manuals are expertly written, clearly illustrated — exciting, interesting.
• Without previous experience you can complete every project and gain a comprehensive science background.

CHALLENGING - STIMULATING - REWARDING



Analyzing Glowing Gases with the SPECTROSCOPE

Trouble Shooting with the SIGNAL TRACER

PHOTOMICROGRAPH of a Fly's Wing made with Microscope and Photo Lab (Actual Size 5" diameter)

A VALUABLE SCIENCE LAB

8 Versatile Kits Containing Parts by RCA, MALLORY, G.E., PYRAMID, STACKPOLE, TRIM and other reliable manufacturers. Retail Value of Parts Alone is OVER FIFTY DOLLARS

MEMBERS ARE ENTHUSIASTIC!

I wish I could provide each of my Physics students with all of your enjoyable kits. You are doing a wonderful job. Allen T. Ayers, Physics Dept., Jamestown High School, Jamestown, New York

Designing and offering this complete laboratory to the public at such a low price is a notable service to our society.

R. M. Helm, Professor of Physics, East Carolina College, Greenville, N. C.

FOR SAFETY!

Circuits are low voltage supplied by isolation transformer that comes with first kit.

FREE! These 6 Auxiliary Textbooks



COMPLETE LABORATORY COMES IN 8 KITS... ONE A MONTH SUPPLIES ALL THE EQUIPMENT FOR ALL THE FOLLOWING:

Table listing 8 kits: ELECTRICAL EXPERIMENTS, RADIO RECEIVER, DC POWER SUPPLY, PHOTOELECTRIC EYE, MICROPHONE, ELECTRONIC EXPERIMENTS, CODE PRACTICE SET, STROBE LIGHT, BROADCAST TRANSMITTER, RADIO SERVICE EQUIPMENT, SOUND EXPERIMENTS, TELESCOPE, PHOTOGRAPHY LAB, SLIDE PROJECTOR, MICROSCOPE, SPECTROSCOPE, ATOMIC RADIATION EXPM., ATOMIC CLOUD CHAMBER, ULTRAVIOLET LAMP, HEAT EXPERIMENTS, WEATHER STATION.

ALL THE EQUIPMENT FOR ALL THE ABOVE-ONLY \$29.60

SEND \$2.00 WITH ONLY COUPON PAY \$3.45 FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 8 MONTHS) FREE SOLDERING IRON with second Kit

Your Satisfaction or Your Money Back... AND you may cancel at any time without obligation. These "no risk" assurances because we know you will be...

SURPRISED! AMAZED! DELIGHTED!

AMERICAN BASIC SCIENCE CLUB 501 E. Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Home Science Labs" in eight kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose plan checked.)
() I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
() I enclose \$29.60 as full payment, Postage Paid, for all 8 kits. I may cancel any time and get full refund on unshipped kits.

NAME, STREET, CITY, STATE, MAIL COUPON TODAY

AMERICAN BASIC SCIENCE CLUB, Inc. San Antonio, Texas

Now! Work Over 300 PRACTICAL PROJECTS with these PARTS AT HOME!

to help You learn ELECTRONICS RADIO-TELEVISION-RADAR

NOW . . . at home in your spare time you can get the very kind of training and subsequent Employment Service you need to get started toward real earnings in one of today's brightest opportunity fields—TELEVISION-RADIO-ELECTRONICS. Now that Electronics is entering so many new fields, here is a chance of a lifetime to prepare to cash in on its remarkable growth.

DeVry Tech's amazingly practical home method enables you to set up your own HOME LABORATORY. You spend minimum time to get maximum knowledge from over 300 practical projects, using the same type of basic equipment used in our modern Chicago and Toronto Training Centers!

DeVry Tech Provides EVERYTHING YOU NEED . . .

—to help you master TV-ELECTRONICS. In addition to the home laboratory and easy-to-read lessons, you even use HOME MOVIES—an exclusive DeVry Tech advantage. You watch hidden actions . . . see electrons on the march. Movies help you to learn faster . . . easier . . . better.

LABORATORY TRAINING

Full time day and evening training programs in our modern Chicago and Toronto Laboratories are also available. MAIL COUPON TODAY for facts.

BUILD and KEEP Valuable TEST EQUIPMENT

As part of your training, you build and keep a fine Jewel-Bearing Vacuum Tube VOLTMETER and a 5-inch COLOR OSCILLOSCOPE—both high quality, needed test instruments.

EFFECTIVE EMPLOYMENT SERVICE

Get the same Employment Service that has helped so many DeVry Tech graduates get started in this fast-growing field.

"One of North America's Foremost Electronics Training Centers"

Accredited Member
of National Home
Study Council

EARN WHILE YOU LEARN

DeVry Tech's practical training helps you toward spare time income—servicing Radio and Television sets.

CHECK
These Exciting
Job
Opportunities:

- TV-Radio Broadcast Technician
- Color Television Specialist
- Radar Operator
- Laboratory Technician
- Airline Radio Man
- Computer Specialist
- Quality Control Manager
- Your Own Sales & Service Shop
- ... PLUS MANY OTHERS

MAIL COUPON TODAY!

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RTE-1-R

Please give me your FREE booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.


Name _____ Age _____
PLEASE PRINT
Street _____ Apt. _____
City _____ Zone _____ State _____

2045 Canadian residents address: DeVry Tech of Canada, Ltd.
970 Lawrence Avenue West, Toronto, Ontario



DeVRY TECHNICAL INSTITUTE
CHICAGO 41, ILLINOIS

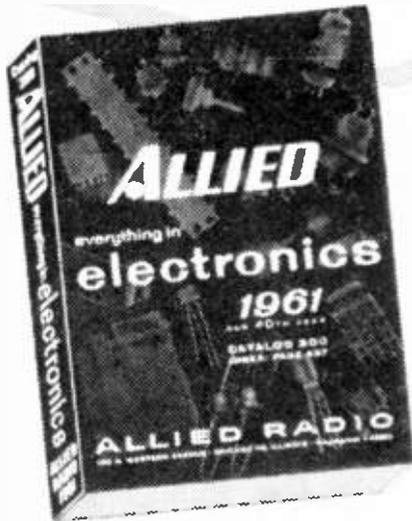Simply Great! **k**
ELECTRONIC
knight-kits[®]
 A PRODUCT OF ALLIED RADIO
A PLEASURE TO BUILD
and YOU OWN THE BEST



featured in the
 big 444-page 1961

ALLIED
ELECTRONICS
CATALOG

free



KITS FOR EVERY NEED
 Stereo Hi-Fi
 Hobby
 Instrument
 Amateur

BIGGEST SAVINGS
 Know the thrill of building your own money-saving electronic equipment. Make your selection from the complete KNIGHT-KIT line—available only from ALLIED. Lowest in cost, convenience-engineered for easiest assembly, best for performance; satisfaction guaranteed or your money back. Send today for the 1961 ALLIED Catalog—select exciting KNIGHT-KITS—and...

SAVE ON EVERYTHING
IN ELECTRONICS



Get more for your money in: Stereo hi-fi systems and components • Recorders and tape • Citizen's 2-way radio • Amateur station equipment • TV tubes, antennas, accessories • Test instruments • Electronic parts, tubes, transistors, tools. Send today for your FREE 444-page Allied Catalog!

only \$2 down
 on orders up to \$50

FREE
catalog



ALLIED RADIO

ALLIED RADIO, Dept. 64-C1
 100 N. Western Ave., Chicago 80, Ill.

Rush FREE 1961 Allied Catalog No. 200

Name _____
 PLEASE PRINT

Address _____

City _____ Zone _____ State _____

TACO
FM
ANTENNAS
 FOR MORE STATIONS
 AND HIGHER FIDELITY
TECHNICAL APPLIANCE CORPORATION
SHERBURNE, N. Y.



Inventors!
IS YOUR
SALES
PITCH
MISSING
SOMETHING?

If you want to SELL your invention to the next manufacturer you contact, use our NEW INVENTION FOR SALE form, designed to assist you in presenting ALL the pertinent, selling facts. A packet of six forms for \$1.00.

SCIENCE and MECHANICS MAGAZINE, Dept. 734
450 East Ohio Street, Chicago 11, Illinois

WHERE TO FIND



GEM HUNTER'S GUIDE

SCIENCE and MECHANICS, Dept. 127
450 East Ohio St., Chicago 11, Illinois

Please send me for 5 days' FREE EXAMINATION—a copy of the "Gem Hunter's Guide," your 188-page hardbound book packed with maps, full-color photos and expert advice on how and where to find gems. Unless completely satisfied with book I may return it in 5 days and owe nothing. Otherwise I will keep it and send you \$3.95, plus 50¢ to cover postage and handling.

NAME

ADDRESS



CITY ZONE.....

STATE

SAVE Money! Enclose only \$3.95 WITH this coupon. Then we prepay delivery charges. Same 5-day return privilege for full refund applies if not satisfied.

This is all you need to know, to TEST FOR REPAIR, ALL ELECTRICAL APPLIANCES, AUTOMOBILES, TV TUBES

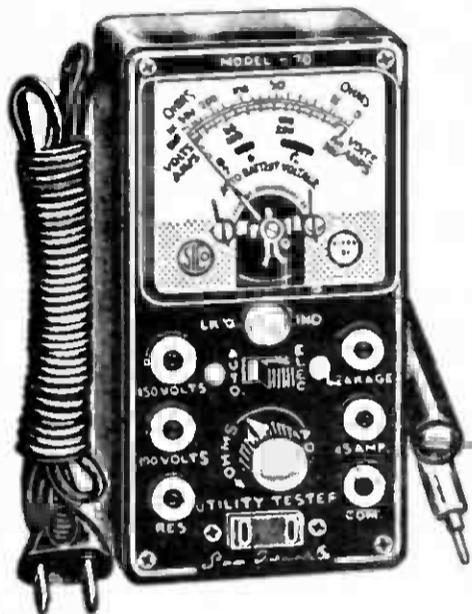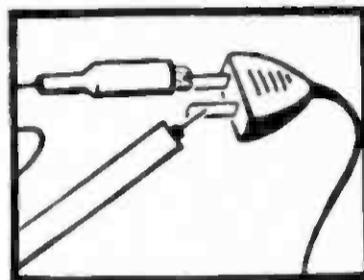This simple outlet is typical of 2 points of contact on all electrical appliances →



All electricity is measured by (1) voltage, (2) current, (3) resistance. You can test either, any or all by merely touching 2 points of contact on any electrical device with our prod and clip. Results are indicated on the meter of our new Model 70 Utility Tester. Repair procedure is outlined in our Tester Use Book.

Even if you don't know a male plug from a female socket, you should be able to test household appliances within 10 minutes. You can repair electrical appliances yourself, do it for others (as a favor or spare time business) or merely protect yourself by knowing what needs fixing, which TV tubes have open or burned out filaments. In this respect alone you can save yourself many times the small cost of this Utility Tester.

JUST TOUCH TO TEST!
It's as simple and easy and fool-proof as this.

Condensed Course in Electricity

Along with your Utility Tester, you receive a FREE 64-page, fully illustrated course of facts, tests, instructions and electrical repairs. It has been proven that this course simplifies the subject of electricity, and is in fact superior to most comparable courses, texts, volumes or encyclopedia on the subject. In 10 minutes, you will be testing household appliances of every kind (and you learn how to repair them). In one hour, you will know more about electricity in its relation to your personal living, than many folks learn in a full course. This book is included at no extra charge with your Model #70 Utility Tester. Complete with Condensed Course in Electricity and Tests Leads.

\$15⁸⁵ PAY NOTHING NOW
Only

A.A.A. REPORTS BATTERY AND ELECTRICAL FAILURES MAJOR CAUSE OF HIGHWAY FAILURES AND BREAKDOWNS

Model #70 tests appliances, motors, car batteries and circuits, TV tubes. Measures A.C. and D.C. voltages, current, resistance, leakage, etc. Tests: Toasters • Irons • Broilers • Heating Pads • Clocks • Fans • Vacuum Cleaners • Refrigerators • Lamps • Fluorescents • Switches • Thermostats and other items. Tests all TV tubes for open or burned out filaments.

Tests both 6- & 12-volt Storage batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Lamps & Bulbs • Directional Signal Systems • Fuses • Horns • Heating Systems. Also locates Poor Grounds, Breaks in wiring, Poor connections, etc.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try it for 10 days before you buy. If completely satisfied then send \$3.85 and pay balance at rate of \$4.00 per month for 3 months—No Interest or Finance Charges Added! If not completely satisfied, return to us, no explanation necessary.

MOSS ELECTRONICS, INC.
Dept. D-862, 3849 Tenth Avenue, New York 34, N. Y.
Please rush me one Model #70. If satisfactory, I agree to pay \$3.85 within 10 days, and balance at rate of \$4.00 monthly until total price of \$15.85 plus postage is paid. If not satisfactory, I may return for cancellation of account. Include my Free Course.

Name

Address

City Zone State

All Prices Net, F.O.B., N. Y.

New "Mechanical Educator" to IMPROVE MEMORY

Inability to recall names, places, facts quickly is a common, often costly, shortcoming that can now be easily overcome with the aid of a new device for mental training. This versatile new educational tool can also be used effectively in language learning, speech correction and improvement, in mastering tables, formulae—anything to be memorized—faster than ever while you sleep.

DORMIPHONE Memory Trainer Works for you—You Learn While You Sleep

- Speeds up learning processes
- Aids concentration
- Provides entertainment



Using a new recording principle, the Memory Trainer records, instantly plays back, and automatically repeats speech, music, or any spoken or broadcast material by clock control. No reels of tape to snarl or rewind. Completely portable. Ideal aid for home, school, industrial safety training use. So simple to use, children benefit—so helpful and practical, it is used by educators, psychologists, people of all ages and professions.

SELF-CONTAINED RECORDING CARTRIDGES

from 30 seconds to 55 minutes. Easily removed. Can be stored or "erased" instantly and re-used repeatedly. Just record, flip a switch for play-back and listen! Write TODAY for FREE folder with complete information. Modernophone, Inc. 396-021 Radio City, New York 20, N.Y.

MODERNOPHONE, INC. Circle 7-0830

396-021 Radio City, New York 20, N. Y. Gentlemen: Please send me your FREE Booklet. I am interested in finding out all about Scientific Sleep Learning and what the Dormiphone Memory Trainer can do for me. No obligation—no salesman will call.

Name

Address

City Zone State

My main interest in the Memory Trainer is for:

Language Learning Speech Improvement

Memorization School or College Work

Sleep Learning Bridge Rules

Now... Build 35 ELECTRONIC PROJECTS with these amazing kits!



LESS THAN 75¢ A PROJECT!

- ★ ONLY A SCREWDRIVER NEEDED!
- ★ PARTS CAN BE USED AND REUSED!
- ★ NO PREVIOUS ELECTRONIC EXPERIENCE REQUIRED!

ELECTRONICS LAB

Model LAB-18

18 ELECTRONIC PROJECTS FOR ALL HOBBYISTS! Build useful equipment... work with SOLAR ENERGY—SPACE COMMUNICATIONS—RADIOS—TRANSISTORS—OSCILLATORS. This fascinating kit will amaze you... start you on your way to a successful electronics career. Kit comes complete with all parts and simple picture instructions that even a beginner can follow! A fabulous buy at only \$12.95 ppd.

Model LAB-35

35 EXCITING SCIENTIFIC PROJECTS! Contains all parts & simple illust. instruct. to build useful projects as PHOTO ELECTRIC RELAYS—SIGNAL GENERATOR—STEREO PREAMP—BROADCAST STATION—SOLAR POWERED RADIOS—RAIN ALARM—INTERCOM—VOICE OPERATED RELAY—TV COMMERCIAL KILLER—CAPACITY RELAY—BURGLAR ALARM—FIRE ALARM—FLASHER—WIRELESS CODE TRANSMITTER—TIMER & many more. A virtual electronics treasure chest, only \$18.95 ppd.

ORDER TODAY! And we will rush your kit to you by return mail! Send check or money order (no C.O.D.).

TV SALES CO., Dept. RE, P.O. Box 44, Yonkers, N.Y.



SO EASY IT'S SHOCKING, IF YOU USE ENLARGED PLANS

to build electronic projects. Enlarged size, step-by-step craft print plans—complete with detailed materials lists—are available for the following:

- 191. TESLA COIL. Produces 70,000 volts at 500,000 cps. Spectacular but safe.....\$1.00
- 227. REPULSION COIL. Defies law of gravity—electromagnetically.....\$1.00
- 243. DEMO ELECTRIC MOTORS. Plans for both windmill and engine types.....\$1.50
- 251. SOLAR BATTERY AND MOTOR. Battery's volt at 180 ma drives motor.....\$1.50
- 258. SUN-POWERED RELAY. Light-activated control with a variety of practical applications.....\$1.00
- 264. HI-FI FM RECORD PLAYER. Phono oscillator, arm and turntable for hi-fi reproduction.....\$1.00
- 265. ELECTRICAL COIL-WINDING MACHINE. Motor-powered with foot-controlled reactor.....\$1.00
- 279. WIMSHURST STATIC MACHINE. Constant source of static electricity.....\$1.50
- 283. VAN DE GRAAFF GENERATOR. Costs \$30 to build. Produces up to 250,000 volts.....\$1.50
- 301. VAN DE GRAAFF GENERATOR. Produces up to 400,000 volts. This is the apparatus that can stand your hair on end!.....\$1.50

... SAVE MONEY! If you order two or more craft prints, deduct 25¢ from the regular price of each print. Thus, for two prints, deduct 50¢; three prints, 75¢, etc. Use handy coupon below. Satisfaction guaranteed or money back.

SCIENCE and MECHANICS, Dept. 298

450 East Ohio St., Chicago 11, Illinois

Enclosed is \$..... Please send me the circled plans.

These plans are \$1.00 each

191 227 258 264 265

These plans are \$1.50 each

243 251 279 283 301

NAME.....


ADDRESS.....

CITY & ZONE.....

STATE.....

Here's 20¢. Please send me your illustrated catalog of 196 craft print plans.

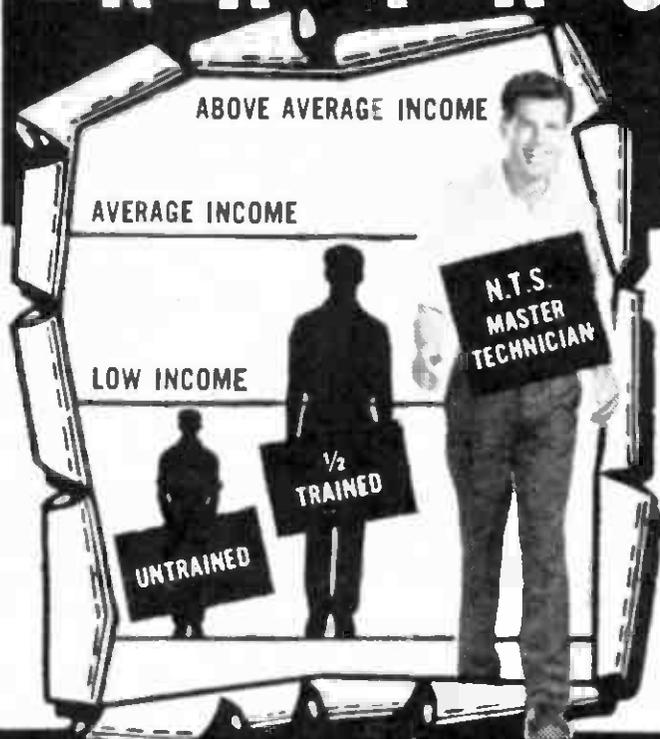BREAK THROUGH TO HIGHER PAY in ELECTRONICS TV-RADIO



START NOW! Break through the Earning Barrier that stops half-trained men. N.T.S. "All-Phase" training prepares you — at home in spare time — for a high-paying CAREER in Electronics — TV — Radio as a MASTER TECHNICIAN. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: Servicing, Communications, Preparation F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.


A more rewarding job... a secure future... a richer, fuller life can be yours! As an N.T.S. MASTER TECHNICIAN you can go straight to the top in industry... or in your own profitable business.

You work on actual job projects

SUCCEED IN MANY HIGH-PAYING JOBS LIKE THESE...

- TV-Radio Sales, Service and Repair
- Profitable Business of Your Own
- Communications Technician — F.C.C. License
- Hi-Fi, Stereo & Sound Recording Specialist
- TV-Radio Broadcasting Operator
- Technician in Computers & Missiles
- Electronics Field Engineer
- Specialist in Microwaves & Servomechanisms
- Expert Trouble Shooter
- All-Phase Master Technician

19 BIG KITS YOURS TO KEEP

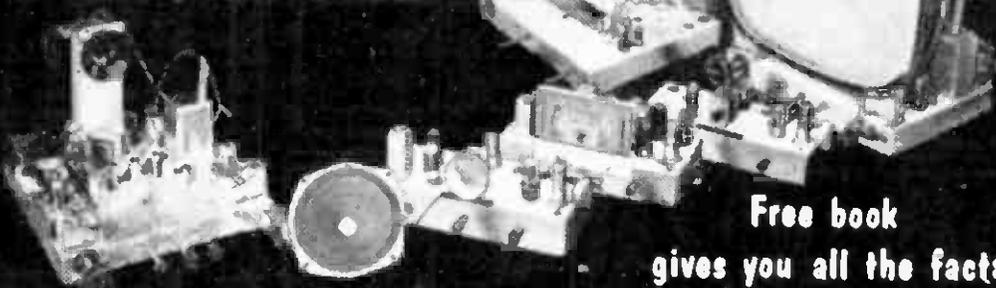

Free book gives you all the facts

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1924

4000 SO. FIGUEROA ST., LOS ANGELES 32, CALIF., U.S.A.

Write Dept. RKK-31



RESIDENT TRAINING AT LOS ANGELES
If you wish to take your training in our Resident School at Los Angeles, start NOW in our big, modern Shops and Labs. Work with the latest Auto and Diesel engines — all types — fuel injection, automatic transmissions, all power equipment — most complete facilities offered by any school. Expert, friendly instructors. Graduate Employment Service. Help in finding home near school — and part-time job while you learn.

WRITE FOR SPECIAL RESIDENT SCHOOL CATALOG AND INFORMATION



ACCREDITED MEMBER
... the only nationally recognized accrediting agency for private home study schools.

N.T.S. Shop-Tested HOME TRAINING is Better, More Complete, Lower Cost... and it is your key to the most fascinating, opportunity-filled industry today!

YOU LEARN QUICKLY AND EASILY THE N.T.S. SHOP-TESTED WAY

You get lessons, manuals, job projects, unlimited consultation, graduate advisory service.

You build a Short Wave-Long Wave Superhet Receiver, plus a large-screen TV set from the ground up, with parts we send you at no addi-

tional cost. You also get a Professional Multimeter for your practical job projects.

EARN AS YOU LEARN... WE SHOW YOU HOW!

Many students pay for entire tuition — and earn much more — with spare time work they perform while training. You can do the same... we show you how.

SEND FOR INFORMATION NOW... TODAY! IT COSTS YOU NOTHING TO INVESTIGATE.

N.T.S. HOME TRAINING is

- Classroom Developed
- Lab-Studio Planned
- Shop-Tested
- Industry-Approved
- Specifically Designed for Home Study



MAIL COUPON NOW

for **FREE BOOK** and **ACTUAL LESSON**

**NO OBLIGATION!
NO SALESMAN WILL CALL**

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1924

Mail Now To
National Technical Schools, Dept. RKK-31
4000 S. Figueroa St., Los Angeles 32, Calif.

Please rush FREE Electronics-TV-Radio "Opportunity" Book and Actual Lesson. No Salesman will call.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if interested ONLY in Resident Training at Los Angeles.
VETERANS: Give date of discharge _____



FREE **GIANT 1961 204 PAGE CATALOG**

BA 1961
ANNUAL CATALOG #11

SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

RADIO TV ELECTRONICS

BURSTEIN-APPLEBEE CO.

Dept. RE, 1012 McGee St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

Name

Address

City..... State.....

SEND FOR IT TODAY

GET THE BEST

T-T-A-C-O-O

T-BIRD

TECHNICAL APPLIANCE CORPORATION
SHERBURNE, N. Y.

INVENTORS


PROTECT YOUR PATENT
With NEW PATENT SALES AGREEMENT

Now you can sell your patent and be SURE you are protecting your interests 100 percent. Prepared by the Dean of a leading law school, this S&M Patent Sales Contract will help you protect yourself and make sure you or your attorney overlooks no detail. Not a blank, but a true, TESTED Sales Contract that will protect your earnings and interests. Send today for a copy of our Patent Sales Agreement.

Only \$1.00

SOLD EXCLUSIVELY BY
SCIENCE & MECHANICS MAGAZINE
450 East Ohio Street, Dept. 433, Chicago 11, Illinois

FARM TELEPHONE CABINETS

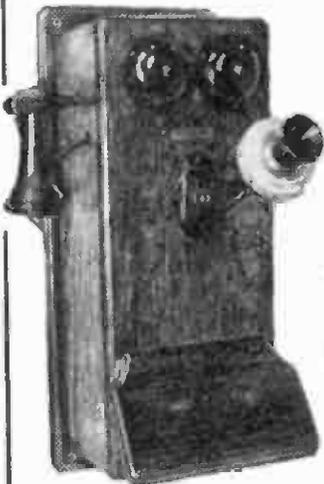

Slightly used crank style CABINETS (once used everywhere) for Home Hobby Shops. Complete with transmitter, receiver, bells, crank and shelf (Less Generator). Has all of the outside parts. Make beautiful, unique Radio Cabinets, Liquor Chests, Spice Cabinets, Flower Planters, etc. Immediate deliveries assured. \$10.00, F.O.B. Chicago.

TELEPHONE HANDSETS




Use as inter-house phone, talk house to garage, as loud speaker system, etc. You receive transmitter, receiver, 3 conductor cord and simplified, illustrated installation diagrams. Handsets are guaranteed to be the same as used in our great National Telephone System. Price delivered \$2.95. Two for \$5.00!

TELEPHONE REPAIR AND SUPPLY CO.
Dept. BB-6 1760 Lunt Ave., Chicago 26

Short Supply Sale of CRAFTPRINTS

Very Limited Stock

6 PLANS for \$1.00

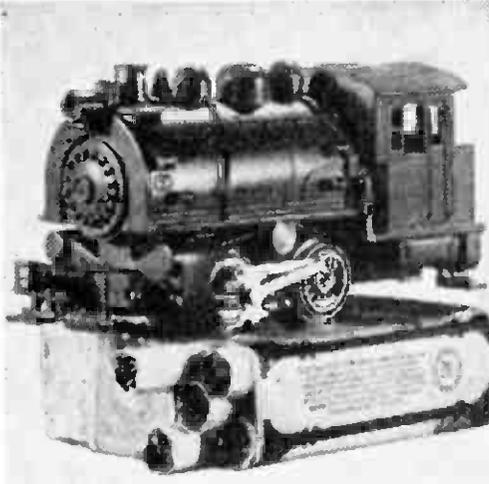

We've been housecleaning. And what do you think we've found? A rare treasure-lode of enlarged-size Craftprints for building wall shelves, tie racks, model trains, planes and cars, shoe racks, toys, smoking stands, etc., etc. Of some we have only 10 in stock, of none have we more than 150. These plans do not appear in our latest Craftprint catalog; we are not going to print them again. To run them out, we offer them to you pre-packaged, our assortment, six (6) for \$1.00. First come, first served—offer good until supply is exhausted. Send your \$1.00 for six assorted Craftprints to:

SCIENCE AND MECHANICS, Dept. 299
450 East Ohio Street Chicago 11, Illinois

BUILD 20 RADIO

CIRCUITS AT HOME

with the New Deluxe

PROGRESSIVE RADIO "EDU-KIT"®

A Practical Home Radio Course

ONLY
\$26⁹⁵



Reg. U.S. Pat. Off.

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Sold in 79 Countries

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$26.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tester and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special Insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name

Address

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 508NN, Hewlett, N. Y.

Now Amateurs Are Working Meteor Trails



Here Walter Bain demonstrates the equipment needed to get into meteor trail work: A) transmitter; B) transmitter power supply; C) frequency marker; D) communications receiver; E) crystal controlled converter; F) clock with sweep second hand; G) tape recorder (optional).

By S. DAVID PURSGLOVE

RADIO amateurs have joined communications engineers and military planners in looking at meteors with a new interest. These tiny fragments burning as they whiz through the atmosphere make possible communication over longer distances and at lower power than can normally be achieved by conventional radio techniques.

A transmitter constantly directs a radio signal at a portion of the sky known to exhibit good meteor activity for that time of day. A receiver up to 1,400 miles away listens for a reflected signal from that part of the sky.

When a meteor trail crosses the transmitted signal and reflects the signal to the intended receiver, the receiving station's own transmitter notifies the sending station.

As soon as the station wanting to send a message receives confirmation that its signal is being received, it releases a high-speed taped message in a rapid burst (hence the name often applied to the technique—"meteor burst").

The use of meteor trail communication on VHF bands means there will be more channels available. This is especially important in the near future, since we are in the fifth year of an 11 year sun spot cycle. Six years from now there will be only about $\frac{1}{2}$ to $\frac{2}{3}$ as many high frequency channels available.

Walter F. Bain operates W4LTV on 144 mc from his home in Springfield, Va. Like most meteor trail amateurs, he usually has ar-

rangements made with another station to go into operation during one of the larger meteor showers.

What does an amateur need for meteor trail work? Here is Bain's answer:

1. Transmitter. A VHF transmitter of at least 100 watts, 500 is better (although some amateurs have operated over long distances with as little as 25 watts when the meteors have been large). It should have good frequency stability, and the operator must be able to measure the frequency accurately so he can notify his intended listener exactly of the frequency to monitor.

2. Receiver. Don't pinch pennies—get a good communications receiver with a low noise converter. The receiver also should have good frequency stability since the receiving operator will be listening for a message that usually will last only five to 15 seconds. Frequencies at both ends of the system must be accurate—there is no way to search for the sender.

3. Switch. Each rig should be equipped to switch easily and rapidly from transmitting to sending and *vice versa* since each station's function will alternate usually four times per minute.

4. Antenna. The antenna must have at least 10 db actual gain. It can always be simple, such as Bain's four sets of 12 element Yagis, each mounted on an 18 ft. boom. W2NLY set the 144 mc distance record with eight 12-element Yagi stacked four high and two wide. It does not have to be a Yagi antenna. Another good configuration is a 16-element broadside colinear antenna. Any of these will give a 13 db gain or better.

5. Clock. An accurate clock—the larger the face the better—with a sweep second hand so you can accurately time the alternating 15 seconds transmitting and listening periods.

6. Key. Any standard or semi-automatic key will suffice, just so it permits the highest keying speed that can be copied conveniently.

7. Optional Equipment. The only major equipment you may want to use beyond the essentials would be some automatic aid to message transmitting and copying since the message period of a meteor reflection is so brief and since you will be repeating messages over and over every 15 seconds. An automatic key or a toothed wheel coded with a standard message helps. Probably best is a tape recorder that rapidly plays a message that was recorded slowly and that can record

MAKE MORE MONEY



RAIN FOR ELECTRONICS . . .

In RESIDENT CLASSES

Grantham *resident* schools are located in four major cities—Hollywood, Seattle, Kansas City, and Washington, D. C. Regularly scheduled classes in F. C. C. license preparation are offered at all locations. New *day* classes begin every three months, and new *evening* classes begin four times a year. The day classes meet 5 days a week and prepare you for a first class F. C. C. license in 12 weeks. The evening classes meet 3 nights a week and prepare you for a first class license in 20 weeks. For more information about the Grantham resident schools, indicate in the coupon the city of your choice and then mail the coupon to the School's home office in Hollywood, Calif. Free details will be mailed to you promptly.

Through HOME STUDY

Grantham training is the easy way to learn more quickly—to prepare more thoroughly—for F. C. C. examinations. And your first class license is the quick, easy way to prove to your employer that you are worth more money.

This correspondence course is directed toward two major objectives—(1) to *teach* you a great deal about electronics, and (2) to prepare you to *pass* all of the F. C. C. examinations required for a first class commercial operator's license. We teach you step by step and have you practice with FCC-type tests which you send to the school for grading and comment. You prepare for your F. C. C. examinations under the watchful direction of an instructor who is especially qualified in this field.

GET your first class commercial F.C.C. LICENSE

To get ahead in electronics—first, you need the proper training; then, you need "proof" of your knowledge. Your first class commercial F. C. C. license is a "diploma" in communications electronics, awarded by the U. S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to earn this diploma.

Grantham training is offered in resident classes or by correspondence. Our free booklet gives complete details. If you are interested in preparing for your F. C. C. license, mail the coupon below to the School's home office at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. No charge—no obligation.

Get your First Class Commercial F. C. C. License by training at

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD


SEATTLE

KANSAS CITY

WASHINGTON

This booklet FREE!

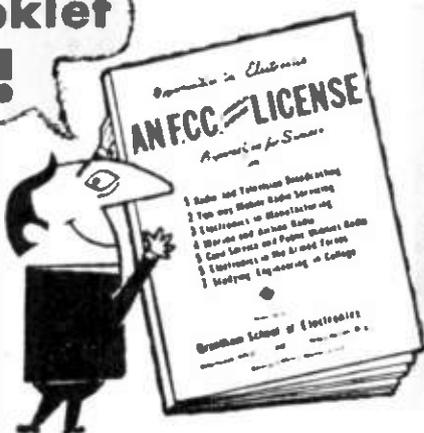This free booklet gives details of our training and explains what an F. C. C. license can do for your future. Send for your copy today.



for **FREE Booklet CLIP COUPON** and mail in envelope or paste on postal card.

for **FREE** Booklet CLIP COUPON and mail in envelope or paste on postal card.

To: GRANTHAM SCHOOL OF ELECTRONICS
1505 N. Western Ave., Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Kansas City classes, E-1C
 Hollywood classes, Seattle classes, Washington classes

the other party's messages for slower playback and copying later.

Bain believes an ingenious amateur who is able to buy items from surplus stocks or make much of his own equipment can get well into VHF meteor trail work for under \$500. The largest single expense will be \$200 or more for a good receiver. Bain's antenna cost only \$120: \$50 for aluminum pipes and rods, \$80 for a tower for which other operators might find a substitute.

The time of day, the season and the latitude dictate the number of meteors that will pass through a portion of the atmosphere per minute. In the Northern hemisphere, Fall is the most active time, while Spring is the least active. Meteoric bombardment is 20 times as high at sunrise as it is at sunset.

Meteors are far more common during several annual meteor showers. It is during these widely publicized showers that amateurs have their greatest success. Table A lists the major showers, their dates, the times during which they are faced by North America, and the times during which an operator should transmit to get the best results in various directions. The shower in August which appears to come from the constellation Perseids is the best shower for ham operation. Nearly as good, though, is the December

shower that appears to come from the Geminids. The Perseids offer about 100 meteors per hour. When meteors collide with molecules of the atmosphere, they leave a trail of metallic ions and free electrons. Radio signals can be reflected from these ionized trails just as they reflect from ionized layers of the atmosphere.

The direction from which a meteor or shower of meteors seems to be coming is called the radiant. For the Perseids shower, the constellation Perseids is the radiant since the shower appears to be coming from that direction. The large meteors will scatter a radio signal in all directions and the operator need only transmit during a good shower to be sure of hitting a few large meteors. However, the small meteors call for a special meteor trail geometry to be applied for communications. Stated most simply, the geometric rule is this: Work on a path at a right angle to the radiant.

This rule has been taken into account by Walter Bain who prepared Table A. For example, if you wish to contact a station Northwest of you during the October Orionids shower, consult the table and you will see that the earth will be so located between 4:30 and 6:00 a.m. that your SE-NW transmission direction will be at right angle to the shower's apparent direction.

Here is another example. You are in New York and wish to contact Chicago late in July. This is during the Aquarids shower. Your path is East-West, so the information in column 3 is applicable. The best activity is between 1:00 and 3:00 a.m., local standard time. Remember that there is a one-hour time difference between New York and Chicago. If the peak of activity is 2:00 local time (this is not necessarily true) this means that so far as you in New York are concerned, the peak for New York is 2:00 a.m., New York time, but, also in New York time the peak for Chicago is 3:00 (2:00 Chicago time).

Once you have selected the day and time for communication, arrange for one station to transmit the first and third 15 seconds of each minute while the other listens. The second station transmits the second and fourth 15 second period while the first station listens.

TABLE A—THE METEOR SHOWERS

Date and Shower	Time Visible	Best Times for Transmission Over Various Paths			
		E-W	NW-SE	SW-NE	N-S
January 1-4 Quadrantids	11am-6pm	8-9pm	3-8am	9am-2pm	—
April 19-23 Lyrids	9pm-11am	—	11:30pm-1am	7-8:30am	2:30-5:30am
May 1-6 Aquirids	3am-12noon	6:30-8:30am	8:30-10am	5-6:30am	—
July 26-31 Aquirids	10pm-6am	1-3am	3-5am	mid-1am	—
August 10-14 Perseids	at all times	3-8am	11:30pm-3am	6-11:30am	—
October 9 Giacobinids	6am-3am	4-5pm	11am-4pm	5-10pm	—
18-23 Orionids	11:30pm-9:30am	3:30-4:30am	4:30-6am	2-3:30am	mid-8am
November 14-18 Leonids	mid-12:30pm	—	—	—	3-5am and 8-10am
December 10-14 Geminids	7pm-9am	—	9:30-11pm	5-6:30am	mid-3:30am
DAYLIGHT METEOR SHOWERS					
May 19-21 Cetids	5:30am-2:30pm	9-11am	11am-2:30pm	7:30-9am	—
June 4-6 Perseids	5am-5:30pm	—	—	—	8-10am and 1-3pm
8 Arietids	3:30am-3:30pm	—	—	—	6-8am and 11am-1pm
June 30- July 2 Taurids	5am-5pm	10:30-11:30am	11:30am-1pm	9-10:30am	7-9am and 1-3pm

**NOW
HEAR
THIS**

**OPPORTUNITY
INTENSIVE RESEARCH BRINGS YOU NEW FACTS—NEW THEORIES
—AN ENTIRELY NEW CONCEPT NEVER BEFORE REVEALED ABOUT
ELECTRICITY, ELECTRONICS AND HEAT**

Amazing new discoveries and inventions in electricity, electronics and heat are utilizing the facts and theories set forth by James Roe, long-time Chicago scientific investigator. One of the most unusual applications is the obtaining of electricity from gases (Oxygen and Hydrogen) via fuel cells. The improvement of storage batteries, the development of maximum thrust rocket fuels, and many other knotty problems can find a basis for their solution in Mr. Roe's works. After reading and studying these works you will understand why and how the fuel cells work, why and how batteries can be improved, why and how heat can be converted directly into electricity. It may well be that through the information you gain from Mr. Roe's writings you may find yourself sparked to a point of originating new ideas and achievements that will benefit all mankind.

Fabulous riches may be yours if your ideas spark a new invention, and this is truly very possible for the field for new ideas is very extensive, and is wide open to all. Every day brings reports of new advancements in the sciences of electricity, electronics and heat. LET MR. ROE'S WRITINGS HELP YOU HAVE A PART IN THESE ADVANCES. Before turning the page fill in the order below for your copy of these works.



Partial Contents

"WHAT ELECTRICITY IS"

WHERE ELECTRICITY COMES FROM
WHERE ELECTRICITY GOES
WHAT ELECTRICITY IS—(ROE'S DEFINITION AND PROOFS)
USE, AND ACTION OF ELECTRONS
LIGHTNING—WHAT IT IS
ROE'S LAWS OF ELECTRICITY
THE LODESTONE (OR MAGNETITE)
ELECTROLYTES—OZONE, ETC.

"WHAT HEAT IS"

THE KINETIC THEORY
WHAT HEAT IS—(ROE'S DEFINITION AND PROOFS)
TEMPERATURE, WEIGHT, VOLUME, MASS
COMBUSTION, FLAME, FIRE. ROE'S EXPLANATIONS.
ROE'S RULES FOR ELECTRONS AND HEAT
COMPARISON OF CONDUCTIVITY OF ELECTRICITY AND HEAT, ETC.

ONLY AVAILABLE BY MAIL · SEND COUPON TODAY

J A R PUBLICATIONS, 2122 E. 75th St., Chicago 49, Ill.

Enclosed is (check or M.O.) for \$.....

Please send by return mail, postpaid, the following:

- "What Electricity Is" @ \$1.95
- "What Heat Is" @ \$1.95
- Both Books for \$3.75

NAME

ADDRESS

CITY ZONE STATE

(Please print)

Study Programs in...

**APPLIED SCIENCE
AND ENGINEERING**

Associate in Applied Science degrees — 2 years

- Electronics Communications Technology
- Electrical Power Technology
- Computer Technology
- Air Conditioning Technology
- Industrial Technology
- Metallurgical Technology

Bachelor of Science degrees — 4 years

- Electrical Engineering
 - Communications option
 - Electrical power option
- Mechanical Engineering

At MSOE, new classes begin quarterly. Pre-technology program, scholarships, financial aid, and placement service available.



New! FREE "Your Career" booklet. Send coupon today.

MILWAUKEE SCHOOL OF ENGINEERING
1025 N. MILWAUKEE STREET • MILWAUKEE 1, WIS.



MILWAUKEE SCHOOL OF ENGINEERING
Dept. RTV-62, 1025 N. Milwaukee St., Milwaukee 1, Wis.


Name..... Age.....

Address.....

City..... State.....

Course Interest.....

(Please Print)

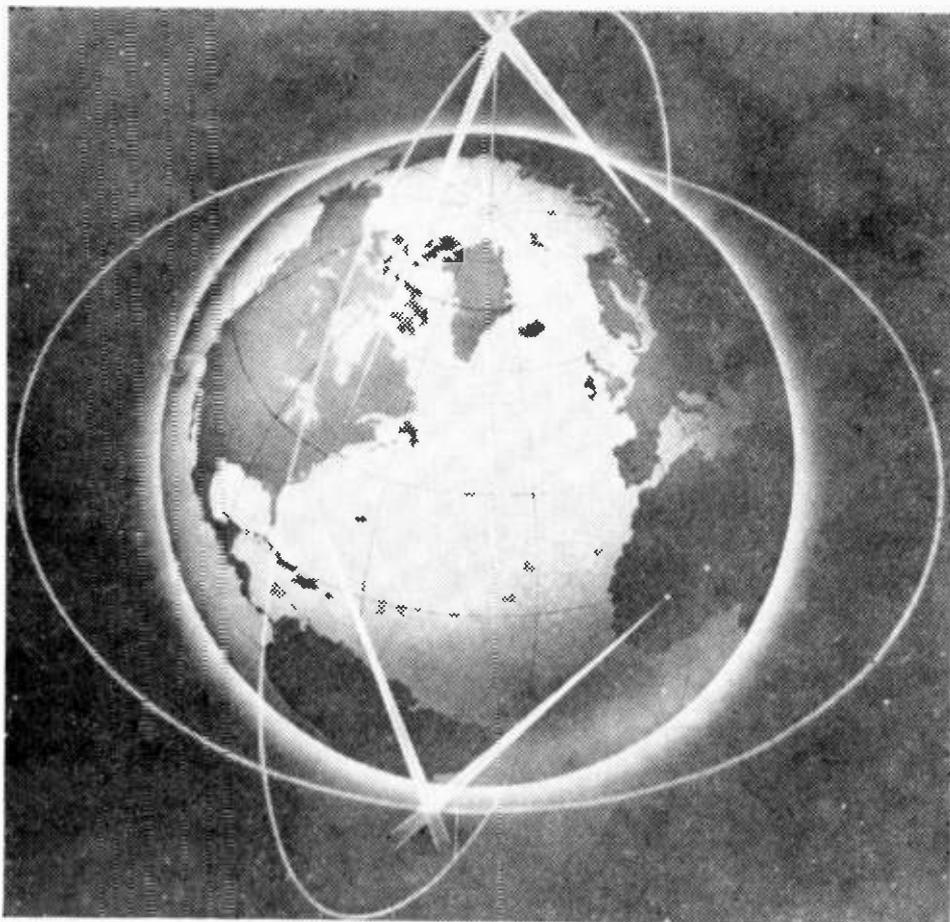

Two orbital scatter belts placed east-west over the equator and north-south over the poles will relay world-wide long-distance radio messages under a new communication system that will replace the presently used ionized layer of atmosphere.

time reliable, high-quality and low-cost, television, voice radio and teletype communication between any two points on Earth.

Unlike the natural ionosphere, the bands will stay at the same distance from Earth, have a constant density and the same radio-reflecting qualities undisturbed by storms and sunspots. The system has been developed by the Massachusetts Institute of Technology and the Air Force Air Research and Development Command.

The metal fibers are about $\frac{1}{2}$ in. long and $\frac{1}{3}$ the thickness of a human hair. They will work in space much as conventional dipole antennas.

When "Project Needles" goes operational the dipole needles will be made of copper and will last for two to three years before they have to be replaced. However, the needles orbited in a test early in 1961 probably will be made of white tin so they will disintegrate within a year. This is to meet the

objections of some astronomers who believe the artificial ionosphere bands will hamper optical and radio telescopes.

The system's developers though, W. E. Morrow, Jr., of MIT and Harold Meyer of Thompson-Ramo-Wooldridge Corp., say there will be no interference. The tiny particles will be hundreds of feet apart in orbit. The bands will be only five miles wide and 20 miles thick. They will reduce the light from stars (in the few instances when the band lies between a star and the telescope) by only one ten-billionth. Radio telescope reception will be reduced by only a millionth.


Orbital scatter has several additional advantages over other long distance communications techniques being tried. Two small rockets can orbit the cannisters that will dispense the dipole needles.

Also, just 9 oz. of the metallic fluff has the same radio wave reflection quality as the 100-ft. dia. Echo balloon. Moreover, communications satellites have to be tracked steadily by special rotating transmitters and receivers; orbital scatter calls for just a few degrees of predictable shift each day. And a single belt of dipole needles can handle many more channels than can a communications satellite.—S. DAVID PURSGLOVE.

ORBITING NEEDLES To Aid Communication

A MAN-MADE ionosphere—composed of millions of tiny metal needles—soon may replace the ionized layer of atmosphere presently used in radio communication.

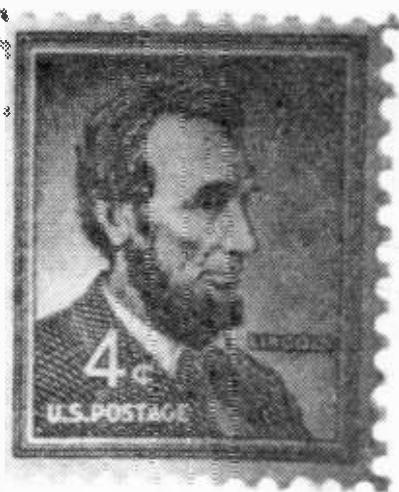The artificial ionosphere, actually two narrow bands of needles, 3,000 to 6,000 miles from Earth, will make possible for the first



Fine metallic fibers like these at the right of the postage stamp will be placed in orbit around the earth to relay radio messages. Two of these fibers will reflect as much radio energy as a flat surface the size of the stamp.

Learn TELEVISION RADIO · RADAR SONAR · ELECTRONICS



THE MOST COMPLETE ELECTRONIC COURSE

Get **COMPLETE** training in all phases of Electronics. Why be satisfied with less? **CHRISTY** Shop Method Home Training System speeds your progress, makes learning fun.

HOME LABORATORY SENT 19 TRAINING INSTRUMENTS INCLUDED

Christy's Complete Course includes your receiving a Multi-Tester, Oscillator, Signal Generator, Electronic Timer, Regenerative Radio, Giant-sized Television Receiver (Optional). Do hundreds of exciting experiments and Earn as You Learn.

FREE BOOK—TWO SAMPLE LESSONS

together with Pay Later form sent on request.

SIGN, MAIL FOR THREE BOOKS

Send for
**FREE
BOOK**



**CHRISTY TRADES SCHOOL, Dept. T-411
3214 W. Lawrence, Chicago 25**

Please send two **FREE** lessons and new 24 Page Illustrated Book telling how I can get started right away in the big money field of Electronics.

Name Age.....
Address
City Zone.... State.....

Experimental ELECTROSTATIC GENERATORS



150,000 V...\$27.95
250,000 V...\$32.95
Special
400,000 V — Write

Build your own Laboratory model electrostatic generator described in Science & Mechanics. These generators have been scientifically tested and produce charges up to 150,000, 250,000, or 400,000 volts depending on the kit. More powerful than units many times larger. Ideal for Schools, Laboratories, Physics and Science

projects and all experimental purposes using static electricity. Used by many leading companies and colleges. Kit, complete and ready for easy assembly, all parts machined and drilled. Includes base, column, sphere, motor, pulleys, belt and all electrical parts and hardware. (For information on 400,000 volt kit, write for circular.) 150,000 volt kit — \$27.95 postpaid. 250,000 volt kit—\$32.95 postpaid. Send U. S. Postal Money Order or check. Please, No. C.O.D.s.

ALSO PLASTIC MATERIALS FOR:

- Repulsion Coil, \$4.00
- Miniature Tesla Coil, \$21.00
- Souped-Up Tesla Coil, \$24.00
- Wimshurst Static Machine, \$20.00
- Sun Battery Kit, \$4.00
- Opaque Projector, \$4.50
- Wilson Cloud Chamber, \$9.50

- 380,000 Volt Electrostatic Generator (Van de Graaf type), \$14.00 Postage Postpaid

**FOREST PRODUCTS, Inc.
Dept. RT-10
145 Portland Street,
Cambridge, Mass.**

FOREST PRODUCTS, Inc., Dept. RT-10
145 Portland Street, Cambridge, Mass.

- 150,000 Volt Kit only \$27.95
- 250,000 Volt Kit only \$32.95

Name.....
Address.....

CUT OUT AND MAIL TODAY



8 FREE OLSON CATALOGS

TYPICAL VALUE

**DIAL TELEPHONE
\$7.93**

No. PH-31
Standard phone company model.



We will send you a new issue every 6 weeks for a full year—**NO CHARGE!** Compare our World Famous Values.

SEND FREE CATALOGS | MAIL TO: **OLSON ELECTRONICS**
(Formerly Olson Radio)
904 S. Forge St., Akron 8, Ohio

Send Dial Telephone @ \$7.93, plus postage | NAME.....
ADDRESS.....
CITY..... ZONE..... STATE.....

FREE Catalog

OF THE WORLD'S FINEST ELECTRONIC GOV'T SURPLUS BARGAINS



MAGNAVOX AUDIO AMPLIFIER

Mfg. for the Navy for intercommunication and amplification of radio signals. Uses 2/12A6 tubes in push-pull; also high quality input transformer for carbon microphone, and Receiver input-output transformer has variable control for headset or speaker. Also mounting for 12 Volt Dynamotor, and instruction book. Voltage required for operation 12 VDC and 250 VDC 60



MA. Can be used for mobile or home use. Size: 7 1/2 x 7 x 10". Wt. 15 lbs. Navy #CMX-50128. Price—Complete with 3/12A6 Tubes (1 spare), less Dyn. **\$2.95** Price—With 12 Volt Dynamotor. \$6.95 Address Dept. 16—Prices F.O.B., Lima, Ohio. 25% Deposit on All C.O.D. Orders

MAIL COUPON FOR CATALOG!

FAIR RADIO SALES

2133 ELIDA RD. • Box 1105 • LIMA, OHIO

FAIR RADIO SALES

Dept. 16—P. O. Box 1105—Lima, Ohio—U.S.A.

Please rush me your current FREE CATALOG:

NAME:

ADDRESS:

CITY: STATE:

New Isotronic Training Method!

LEARN TV REPAIR IN ONE SHORT WEEK

Now, after 5 years research—a dynamic TV training technique that makes others obsolete! If you've waited for a chance to have your own prosperous business, here's an opportunity to make up to \$150 weekly, almost immediately! **NO EXPENSIVE TRAINING - NO LONG STUDY!**

You want to get started servicing TV sets - not building them! So, why pay up to \$250 for high-priced lessons and equipment... study long months? Our revolutionary ISOTRONIC method qualifies you to handle any make TV set right away! All the complicated technical theory is already taken care of by our Scientists! This new technique - hailed the most practical in the field - was developed by two of the industry's most respected scientists, in cooperation with every major American TV manufacturer!

PUT YOUR "KNOW HOW" TO WORK FOR PROFIT!

In addition to the most streamlined training program of its type, you also benefit from a complete Business Plan that explains fully how to start, conduct, and expand your own TV Service business. Written by expert business consultants. Packed solid with practical know-how instead of theory! Yes, a complete "Business Package" designed to quickly bring you the good things in life that come with your own successful business.

FREE LESSON PROVES ISOTRONIC METHOD WORKS!

For conclusive proof, send now for full details and FREE SAMPLE LESSON. Apply it to your own ailing set or a friend's - repair it without a single tool or testing device - convince yourself that the amazing Isotronic method can put you in a profitable TV business of your own, in one short week! Write today - free lesson supply limited! (No obligation, no salesman will call.)

TV SERVICING SYSTEMS, Dept. E-872
1038 So. La Brea, Los Angeles 19, California

FREE! Sample Lesson

Take Your Pick OF THESE ILLUSTRATED "HOW-TO-DO-IT" BOOKS

only **75¢ each**



Here's a bargain you don't want to miss! 5 Big handbooks jam packed with plans and instructions for building hundreds of projects—75c each, or less if you buy two or more. Order copies NOW for your library.

573 NEW CARS 1961

In the market for a new car? Then here's a handbook you can't afford to miss. NEW CARS 1961 tells you everything you'll want to know about the '61s—prices, interiors, horsepower, fuel capacity, and dozens of specifications. Specifications of all cars are placed side by side for quick comparison. Every American car and wagon is pictured. 75¢

572 WOODWORKER'S ENCYC'EDIA

Everything the home craftsman needs to know about woodworking can be found in this comprehensive volume. Over a thousand illustrations help explain every operation in basic woodworking. Tells what tools to buy and how to buy wood. Explains how to joint, miter, mold, bevel, dowel and chamfer plus dozens of woodworking projects. 75¢

571 SCIENCE EXPERIMENTER

Wonders of science now explained with 37 fascinating projects you can build—a model hydroelectric plant, a vacuum chamber for making experiments on sound and electricity, a transistor thermometer, a radiation measurer, a logic circuit board, a pure fluid amplifier, a sonic shake table and a force table. 75¢

570 HOME WORKSHOP HANDBOOK


More than 50 shop projects are included in the 1961 edition of this handbook. Projects for the shop include a spot welder, saber saw, lathe face-plate adapter, powered edge planer and drill press sanding table. 75¢

569 RADIO-TV EXPERIMENTER

Includes 37 electronic projects, among them—a complete two meter ham station, a transistor analyzer, an economy frequency standard, a two tube long wave receiver, a musical annunciator, a typacode and a wireless intercom. All of these plus the latest revision of White's Radio Log. 75¢

SAVE MONEY!

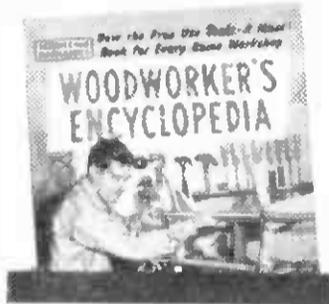Price of first handbook, 75¢; each additional handbook ordered at same time only 50¢ each. Rush coupon!



RUSH THIS ORDER FORM

Science and Mechanics Magazine, Dept. 3005

450 East Ohio Street, Chicago 11, Illinois

Enclosed is \$..... Please send the books whose numbers I have circled below:

569 570 571 572 573

Name

Address

City, Zone & State

SATISFACTION GUARANTEED OR YOUR MONEY BACK

Experimenters! Take Your Pick

SPECIAL OFFER! **BACK-ISSUE BARGAINS!**
FIVE FOR ONLY \$2.50

These back issues of the **RADIO-TV EXPERIMENTER** are still available:



551 Includes sun-cell TRF receiver, plans for experimenter's test bench, decade chm box, electronic tic-tac-toe, split-powered oscillator, photoelectric controls, signal tracer, portable hi-fi record player, single-tube organ. Single copy, 75¢



559 Has 43 different project plans including 15-meter ham rig, simple signal mixer, electronic moisture tester, finger-clip radio, telethermoscope, portable phonograph, hi-fi tone arm, strobe-flash unit. Single copy, 75¢



562 Contains 53 make-it-yourself projects: transistorized intercom, Citizens Band 2-way radio, 7-tube FM tuner, 6-meter ham rig, sun-celled motor, stereo music center. Single copy, 75¢



Also available, these **SCIENCE EXPERIMENTERS**

557 Plans for 40 projects including Van de Graaff generator, Tesla coil, Wimshurst static machine, cloud chambers, light ray tracer, satellite scope, solar furnace. Single copy, 50¢

563 Contains over 50 science projects including repulsion coil satellite camera, tone generator, atmospheric voltmeter, infrared detector. Single copy, 75¢

RUSH COUPON TODAY
Satisfaction guaranteed

Two for \$1.00

SCIENCE and MECHANICS, Dept. 3006
450 East Ohio St., Chicago 11, Illinois

- Enclosed is \$..... Please send me:
- All FIVE of the Experimenters for \$2.50.
 - The TWO RADIO-TV Experimenters circled for \$1.00.
 - Both SCIENCE Experimenters for \$1.00.
 - The circled issues at single-copy prices:

551 559 562 557 563

NAME

ADDRESS

CITY..... ZONE.....

STATE

save more with

SONAR TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
0Z4	.42	6AT8	.48	6SL7GT	.50	12Q7	.45
1A7GT	.45	6AU4GT	.40	6SN7GT	.40	12SA7	.44
1B3GT	.52	6AU5GT	.50	6SQ7	.40	12SG7	.48
1H4G	.39	6AU6	.40	6SS7	.62	12SJ7	.48
1H5GT	.45	6AU8	.49	6T4	.62	12SK7	.44
1L4	.39	6AV5GT	.49	6T8	.61	12SN7GT	.46
1L6	.42	6AV6	.42	6U8	.66	12SQ7	.44
1N5GT	.52	6AW8	.40	6V6	.44	12V6GT	.40
1Q5GT	.44	6AX4GT	.50	6W4GT	.39	12W6GT	.40
1R5	.41	6AX5GT	.49	6W6GT	.43	12X4	.46
1S5	.39	6B8	.44	6X4	.37	12Z3	.46
1T4	.41	6BA6	.46	6X5	.40	14A7/12B7	
1U4	.41	6BC5	.44	6X8	.65	14B6	.48
1U5	.42	6BC8	.49	6Y6G	.69	14Q7	.48
1V2	.49	6BD6	.40	7A4/XXL	.44	19	.48
1X2	.52	6BE6	.44	7A5	.42	19A4GT	.49
2A3	.95	6BF5	.45	7A6	.44	19B6G6	1.00
2AF4	.88	6BF6	.40	7A7	.42	19J6	.48
3BC5	.48	6BG6G	.99	7A8	.45	19T8	.58
3BN6	.80	6BH6	.41	7B4	.42	24A	.48
3BZ6	.40	6BJ6	.41	7B5	.41	25AV5	.75
3CB6	.41	6BK5	.65	7B6	.46	25BQ6	.79
3CF6	.42	6BK7	.68	7B7	.48	25DN6	.99
3CS6	.42	6BL7GT	.68	7B8	.44	25L6GT	.40
3LF4	.49	6BN6	.70	7C4	.39	25W4GT	.41
3Q4	.44	6BQ6GT	.73	7C5	.44	25Z5	.44
3S4	.44	6BQ7	.68	7C6	.46	25Z6	.44
3V4	.44	6BY5	.60	7C7	.48	26	.40
4BQ7A	.65	6BZ6	.42	7E6	.46	35A5	.45
4BZ7	.65	6BZ7	.68	7E7	.44	35B5	.44
5AS8	.52	6C4	.39	7F7	.42	35C5	.46
5AT8	.44	6C5	.60	7F8	.42	35L6GT	.48
5AV8	.44	6C6	.60	7H7	.40	35W4	.43
5AW4	.49	6CB6	.44	7N7	.48	35Y4	.39
5BK7	.58	6CD6G	.99	7Q7	.48	35Z5GT	.47
5J5	.51	6CF6	.42	7X7/XXFM	.44	37	.48
5T8	.49	6CG7	.40	7Y4	.39	39/44	.35
5U4G	.39	6CL6	.59	7Z4	.38	42	.45
5U8	.49	6CM6	.59	12A8	.42	43	.45
5V4G	.49	6CM7	.40	12AQ5	.52	45	.47
5V6GT	.45	6CN7	.40	12AT6	.42	50A5	.45
5X8	.45	6CS6	.42	12AT7	.61	50B5	.48
5Y3GT	.42	6DE6	.44	12AU6	.40	50C5	.48
5Y4G	.55	6DQ6	.79	12AU7	.44	50L6GT	.48
6A7	.60	6F6	.69	12AV6	.42	50X6	.51
6A8	.60	6H6	.37	12AV7	.63	56	.43
6AB4	.40	6J4	1.00	12AX4GT	.50	57	.43
6AC7	.55	6J5	.44	12AX7	.51	58	.43
6AF4	.82	6J7	.59	12A27	.55	71A	.59
6AG5	.40	6K6GT	.33	12B4	.42	75	.60
6AG7	.44	6K7	.48	12BA6	.44	76	.45
6AH4GT	.55	6K8	.58	12BA7	.69	77	.45
6AH6	.42	6L7	.49	12BE6	.44	78	.60
6AK5	.43	6N7	.59	12BF6	.44	80	.52
6AL7	.45	6Q7	.59	12BH7	.51	84/6Z4	.48
6AM8	.49	6S4	.40	12BQ6	.53	117Z3	.44
6AN8	.54	6E8GT	.40	12BR7	.48	117Z6	.90
6AQ5	.44	6SA7	.40	12BY7	.55	117L7	1.95
6AQ6	.42	6SC7	.44	12CA5	.46	117M7	1.95
6AQ7GT	.48	6SF5	.49	12J5	.45	117P7	1.95
6AR5	.48	6SF7	.55	12K7	.40		
6AS5	.42	6SJ7	.55	12L6	.40		
6AT6	.42	6SK7	.40				

6-12 VIBRATORS.....89¢ each

Write Dept. RT-61 for complete list of tubes and special purpose tubes.

All advertised tubes not necessarily new but may be electrically perfect factory seconds or used tubes. Each is clearly marked. All tubes postage paid. Include 25¢ handling for orders under \$5. Include 25% deposit on C.O.D.'s. Send approx. postage on Canadian and foreign orders.

SONAR

ELECTRONIC TUBE CO.
112 MARTIN ST., PATERSON 3, N. J.

**SCIENCE and
MECHANICS'
DO-IT-YOURSELF
LIBRARY**

Boat Builder's Handbook

Car Repair Handbook

Craftsman's Handbook

Craftwork

Do-It-Yourself Handbook

Home Electrical Handbook

Home Repair Handbook

Home Workshop Handbook

Income Opportunities

Model Craft Handbook

New Cars Handbook

1001 How-to Ideas

Photo Craftsman

Science Experimenter

Sportsman's Handbook

Toys and Games

You Can Make

25 Projects on Wheels

Woodworker's Encyclopedia

Copyright 1961 by
SCIENCE AND MECHANICS
A Davis Publication
450 East Ohio Street
Chicago 11, Illinois

Acey-Deucey, A VHF Receiver

BY C. F. ROCKEY, W9SCH/W9EDC

THE ordinary SW frequencies below 30 mc. are becoming more crowded with routine operations every day, so these are now largely old hat. The VHF's the thing today, and this little receiver will introduce you to an interesting slice of the VHF at modest cost. With it you can eavesdrop upon aircraft communications, taxicab dispatchers, police-calls, industrial communications, and that great source of interest to all experimenters, the 144-mc, 2-meter amateur band.



While it can hardly compare with a good VHF superheterodyne, you will be pleasantly surprised with its performance, especially as you grow more proficient in tuning. And you can build it for only about \$20. The RF amplifier minimizes interfering radiation to other sets.

Begin construction by bending-up the aluminum chassis (Fig. 3) from a flat cookie-sheet or sheet aluminum. Or you can buy a 5 x 7-in. chassis. Punch the socket hole in the chassis with a 3/4-in. socket punch, and drill the holes for the potentiometer, 'phone jack and tuning capacitor shaft with a 1/8-in. drill, and ream to 3/8 in. with the tang of a mill file or a taper-reamer. Drill the jack and pot holes in the front panel, then use the panel as a template to drill the chassis. This will assure proper matching. Do not mount the panel upon the chassis until the very last; it will get in the way of wiring and assembly.

Mount the power transformer under the chassis (Fig. 5) using the transformer as template for drilling holes to take the 6-32 screws. Then mount the 4-terminal Cinch-Jones strip. Deburr the holes for the power line leads. Now, mount the tube (AF) socket with 4-36 screws and nuts using the socket as guide for drilling. Put a lug under one of the screws to be used as a ground.


Now mount the selenium rectifier by its mounting screw in the position shown in Fig. 5. Also mount the 100K regeneration control potentiometer temporarily in its hole, as you'll need to make connections to its switch

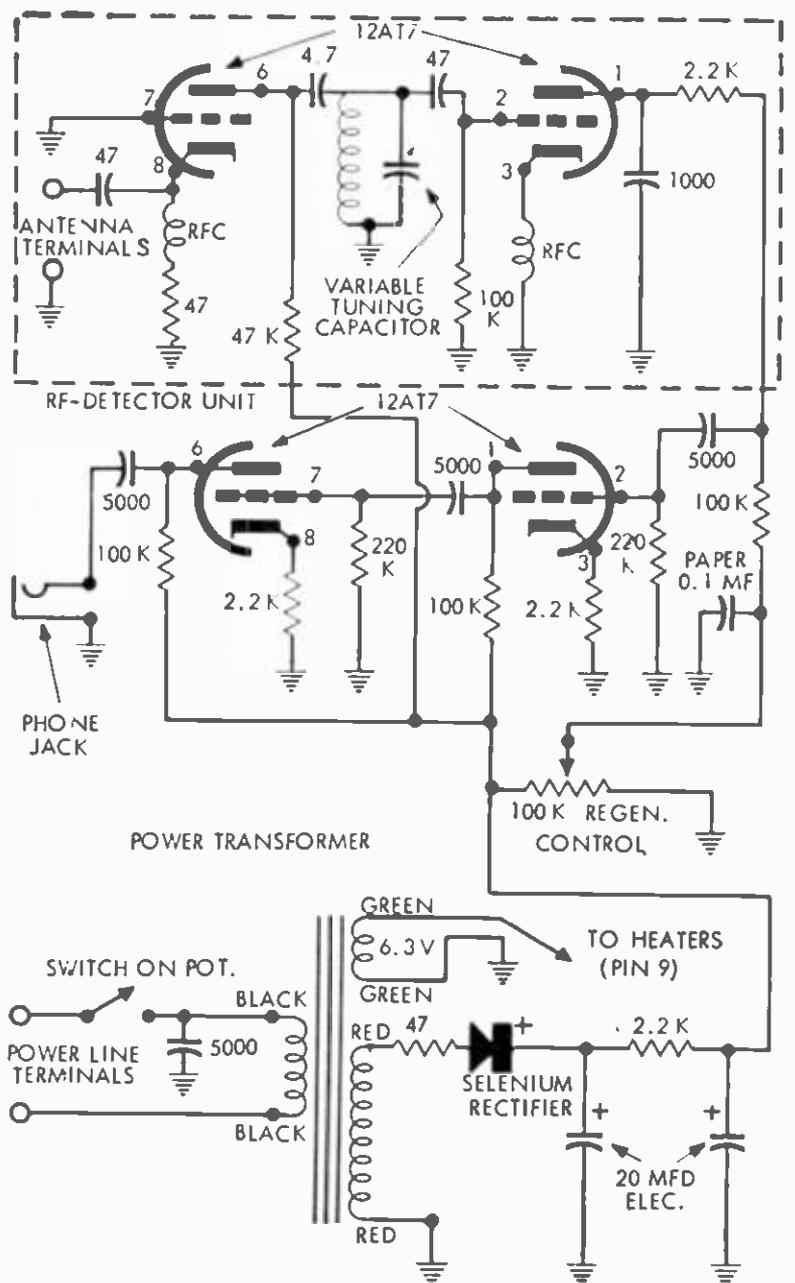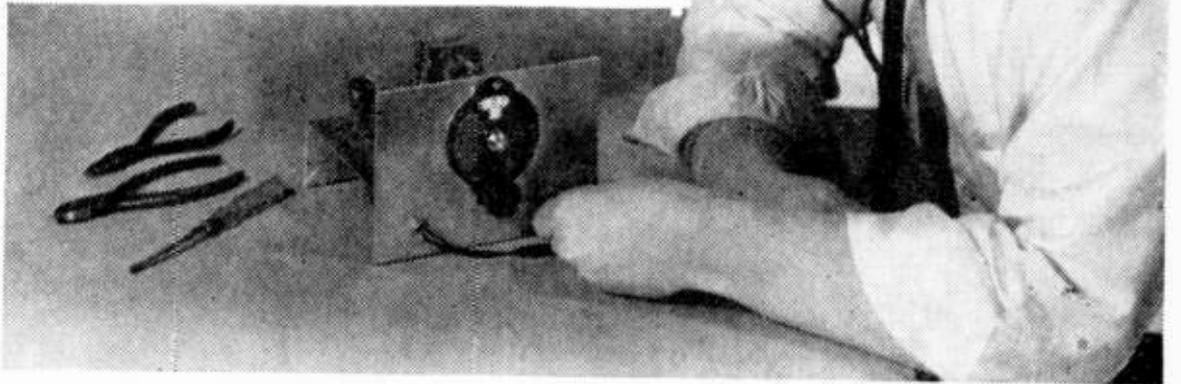This super-regenerative VHF receiver brings in many types of utility calls and the 2-meter amateur band.



ALL RESISTORS IN OHMS
ALL CAPACITORS IN MMF, UNLESS OTHERWISE STATED

2 SCHEMATIC

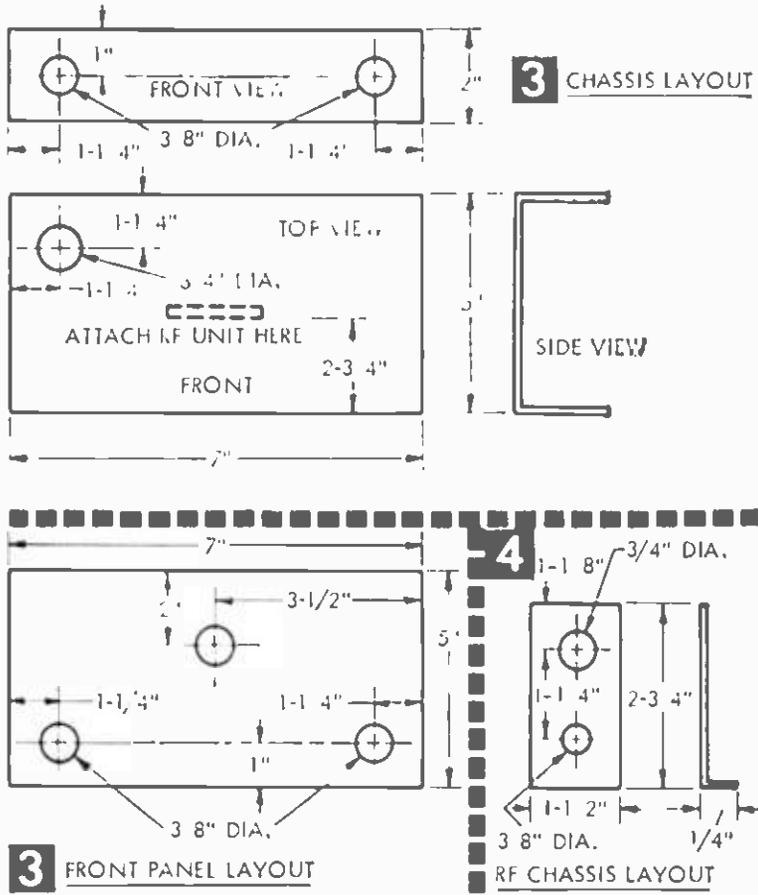


Under chassis view of receiver shows parts layout and wiring.

right away. Next, wire the power supply, using the schematic (Fig. 2) as a guide. Start with the power leads associated with the primary (black) leads of the power transformer. Connect these through the potentiometer switch to the power line terminals on the terminal strip. Don't forget the 5000 mmfd capacitor (filters line hum) from one side of the line to ground. Use insulated tie-lugs to hold the wiring in place.

Next, connect in the selenium rectifier and the electrolytic filter capacitors. Be extremely careful to observe polarity of both the rectifier and of the electrolytics. Hold the filter capacitors in place by their brackets and by fastening their hot leads to an insulated tie lug. When the power supply is wired, with an ohmmeter measure the resistance from the hot terminals of each electrolytic to chassis ground. Readings of at least 10,000 ohms indicates no shorts.

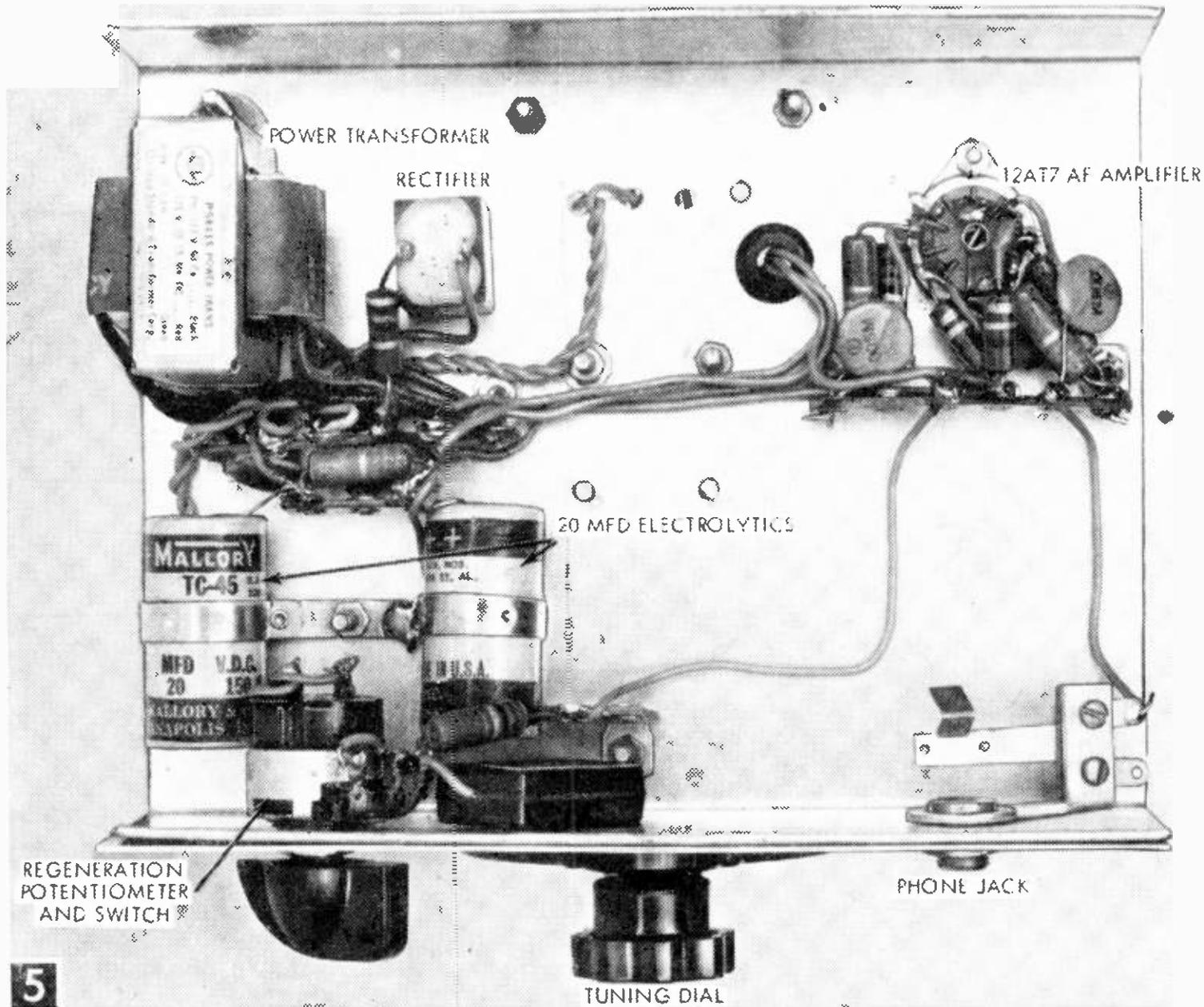Connect the line cord to the line terminals upon the terminal strip. Plug the cord into a power outlet and turn on the pot switch. A voltmeter connected from the hot side of the output (farthest from rectifier) filter capacitor should indicate a dc voltage of 100-200 v., usually about 150.



Now, wire the audio amplifier. Temporarily install the 'phone jack, and wire the output audio amplifier stage.

Tie lugs 4 and 5 together and connect to ground. Connect the ungrounded green (6.3 v.) lead from the transformer to pin 9 (the heater connection). Then wire in the grid, plate and cathode circuits. Use insulated tie lugs as needed.

Plug in a good 12AT7 tube. Connect the power cord to the line, turn on the switch, and plug a pair of headphones into the 'phone jack. Holding onto the blade, touch a screwdriver tip to pin No. 7. A buzzy click indicates that the stage is OK.

Now complete wiring the first stage of the audio amplifier. Use insulated tie lugs as needed.

When done and checked, insert tube, 'phone plug and line cord. When tube is warm, touch screwdriver blade to pin Number 2. A much louder clicky buzz should come from the 'phones, indicating success.

Next, wire in the connections to the potentiometer, the 100K detector load resistor and the coupling capacitor (5000 mmfd) to the grid of the first audio amplifier.

The rf-detector unit is built upon a 1½ x 3-in. aluminum angle piece, cut, bent and drilled according to Fig. 4. The 3/8-in. hole is for the tuning capacitor, the 3/4-in. hole is for the 12AT7 socket. Fasten a double insulated tie lug under each socket mounting screw to serve as terminals for the leads to the rest of the circuitry and to hold small parts firmly in place. Mount the tuning capacitor last.


Wire the rf-detector unit. All of the circuitry enclosed within the dotted enclosure on the schematic is on the rf-detector unit.

Remove one rotor plate from the variable capacitor by grasping it firmly with long-nose pliers, leaving only one rotary plate in the unit. Check carefully to see that this plate does not touch the stator plates at any point of its rotation, and then mount it and wire it into the unit.

Complete the unit by winding and installing the coil (Fig. 7) between the rotor and stator connection lugs of the variable capacitor. This coil consists of three turns of #14 wire. Wind the turns around a 3/8-in. twist drill shank or a fountain pen. Keeping the leads as short as possible, connect this coil directly across the tuning capacitor.

Fasten the rf unit to the chassis with 6-32 screws. Then complete the connections to the power supply and audio amplifier. Bring these leads through a 1/2-in. grommeted hole. Loosely twist two pieces of hookup wire together and connect this twisted pair to the antenna terminals. One side of the other end of this pair goes to the 47 mmfd capacitor, the other to ground, as close by the input circuit as possible. This completes the wiring.

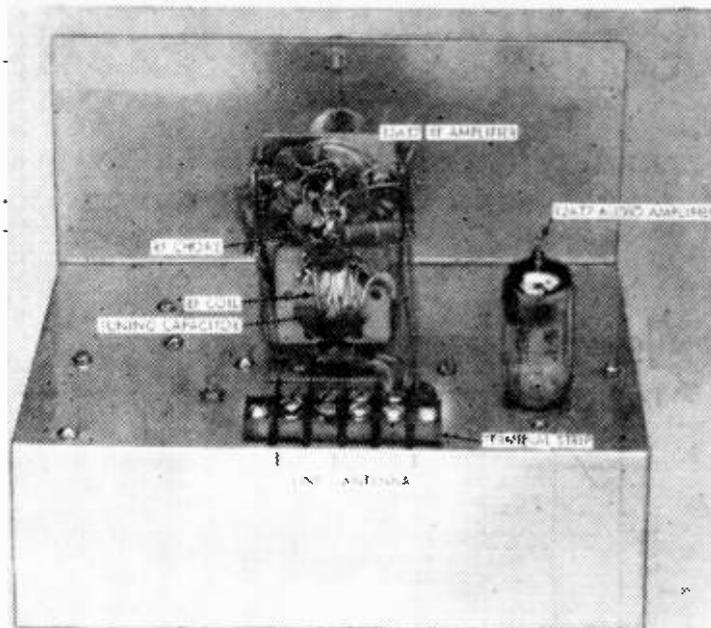Insert the tubes, connect power, and plug



6

The RF detector unit is in the center in this top-chassis view. This unit is wired in late in construction.



3 TURNS # 14 WIRE 3/8" INSIDE DIAMETER

7


COIL:

in phones. As the regeneration control potentiometer is advanced, the circuit breaks into superregeneration, as indicated by a smooth, strong hiss. As the regeneration control is adjusted throughout its range, it is possible to vary the strength of this hiss from inaudible through medium level to strong.


Drill the mounting holes in the front panel

MATERIALS LIST—VHF RECEIVER

No.	Req'd.	Size and Description
1	pc	16 ga. x 7 x 9" aluminum for chassis
1	pc	16 ga. x 5 x 7" aluminum for panel
1	pc	16 ga. x 1½ x 3" aluminum for rf unit
1		venier dial (National type BM)
1		bar knob
1		100K linear-taper potentiometer with switch (IRC)
1		single-circuit 'phone jack (Mallory)
1		shaft coupling, 1/4" to 1/4"
1	pc	plastic, rod, 1/4" dia. x 2½" long
2		9-pin miniature sockets (Amphenol)
1		Cinch-Jones 4-terminal barrier strip, about 1" wide
1		variable capacitor (Hammarlund type HF-15)
1		power transformer (Stancor No. PS-8415)
1		selenium rectifier (Sarkes-Tarzian Model 50)
2		electrolytic capacitors, 20 mfd., 150 W.V. (Mallory type TC-45)
1		0.1 mfd., 200 W.V. paper capacitor (Mallory)
1		line cord and plug
1		pair headphones (Trimm "Dependable")
1		phone plug
2		12AT7 vacuum tubes
2		Miller type 4605, 2.5 microhenry, RF chokes (or can use Ohnite Z-144 1.8 microhenry)
4		2.2K ohm, 1-w. carbon resistor
1		47K ohm, 1-w. carbon resistor
4		100K ohm, 1-w. carbon resistor
2		220K ohm, 1-w. carbon resistor
2		47 ohm, 1-w. carbon resistor
2		47 mmfd disc ceramic capacitor
1		4.7 mmfd disc ceramic capacitor
1		1000 mmfd disc ceramic capacitor
4		5000 mmfd disc ceramic capacitor
		300-ohm twin-lead for antenna, if needed
		hook-up wire, rosin-core solder, screws and nuts,
		No. 14 tinned wire, 3 and 4-point insulated tie lugs,
		soldering lugs, rubber grommet.

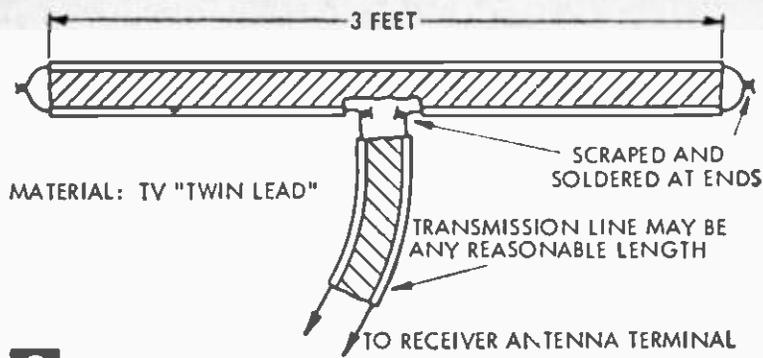

8 FOLDED DIPOLE ANTENNA

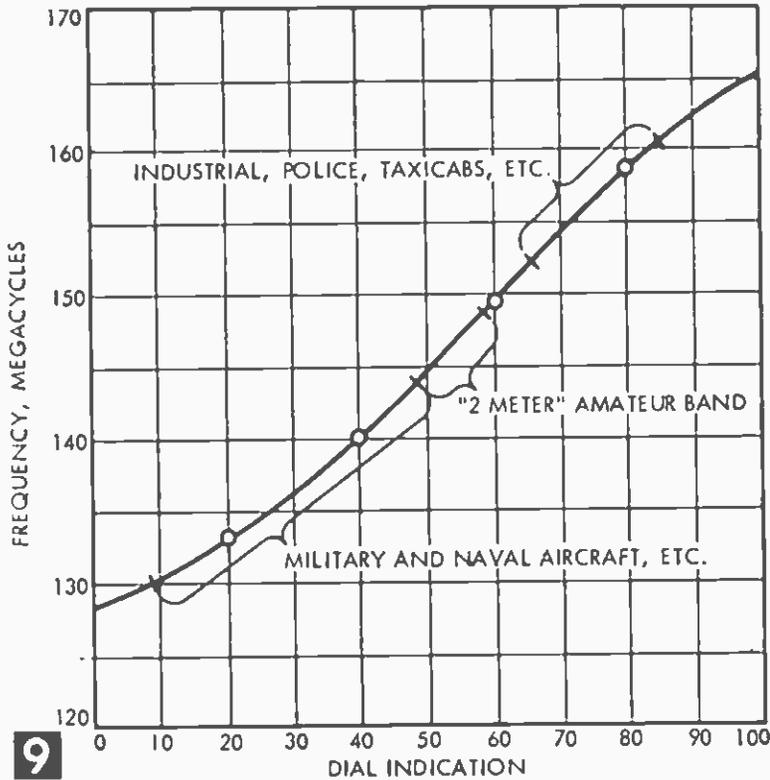

9

Approximate calibration curve of author's receiver.

for the tuning dial using the template supplied by the manufacturer. Then, install the panel. It is held firmly in place by clamping tightly under the potentiometer and 'phone jack binding nuts.

Place the shaft coupler upon the capacitor shaft, then pass a length of plastic or fiber rod through the hole in the dial and into the coupler. Tighten down all setscrews firmly, setting the dial so that the indicator points to 100 when the tuning capacitor plates are fully unmeshed (all the way out) then saw off the plastic rod flush with the end of the dial bushing and insert the bushing cover.

If your present TV antenna is high and pointed in the right direction, you will probably have fairly good results when used with this receiver. Or, you may make a suitable antenna by following Fig. 8. Be sure that your antenna is high, as your receiving range depends directly upon its height.

As in the case with all simple receivers, the number of and distance of signals you hear will depend directly upon the skill with which you use this little set.

Correct use of the regeneration control is often a key to good results. Always adjust the regeneration to the lowest possible level consistent with signal clarity. This is particularly true when receiving the narrow-

band FM transmitters, widely used by police and industrial services. If the regeneration control is advanced too far, all you'll hear is an unmodulated, blank carrier.


If you particularly wish to hear 2-meter amateur signals, you may spread-out the number of dial divisions occupied by the amateur band, if you remove all but one rotary and one stationary plate from the variable capacitor. This will demand some readjustment of the coil. In this case, make final tuning-range adjustments with a grid-dip meter.

Figure 9 represents the frequency calibration of the author's receiver. Yours will be somewhat near, but probably not exactly the same, due to minor construction differences. You may calibrate your receiver by use of the grid dip meter.

You may alter the tuning range of this receiver by soldering-in coils of either more or less turns than those specified. Due to differences in lead length, etc., it is impractical to predict just how many turns would be required to tune over a specified range with your layout; a grid dip meter will enable you to make these determinations in your own individual case. By such coil changes it should be possible to cover from about 100 to about 200 mc. Do not try to incorporate coil switching into this circuit; the increased capacity and inductance introduced by the switch will probably completely spoil the set's operation, particularly at higher frequencies.

Eraser Cleans Terminals

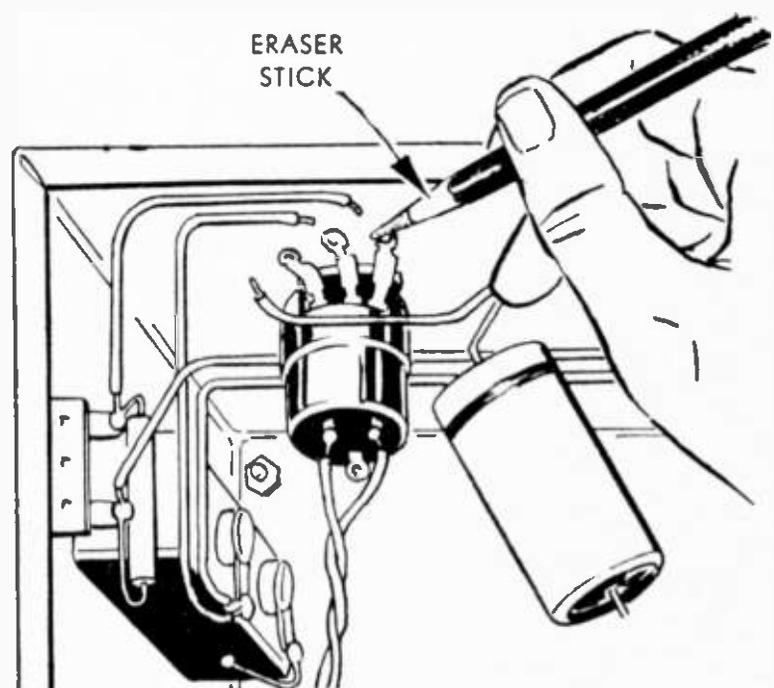- If the terminals or lugs in a radio circuit are scoured clean of dirt and oxidation before wires are soldered to them, there's less likeli-



hood of obtaining a troublesome cold solder joint. To clean terminals deep down among wiring where sandpaper cannot reach, use a pencil-shaped eraser.—JOHN A. COMSTOCK.


Transistor Tester

Compact unit indicates leakage current and beta

By FORREST H. FRANTZ, Sr.

If you experiment with electronics you have or you will get into transistor circuit experimentation and construction. The condition of the transistor which you use in your circuits will determine the quality of the operation of your circuits. It's heartbreaking to search for circuit troubles only to find a bad transistor after a considerable expenditure of time. Many difficulties can be avoided by testing transistors before you place them in circuits. This transistor tester will do the job.


Not all transistor testers are alike. There are desirable features which transistor testers should possess to be most useful. One important feature is provision for universal connection of any type of transistor. Testing under collector current conditions approximating those under which transistor characteristics are compiled (most often 1 ma.) is another desirable feature. The tester should be off unless the on-off switch is depressed. Other desirable features (most transistor testers have these) are npn-pnp selector switch, range-leakage switch, and direct reading beta scale.

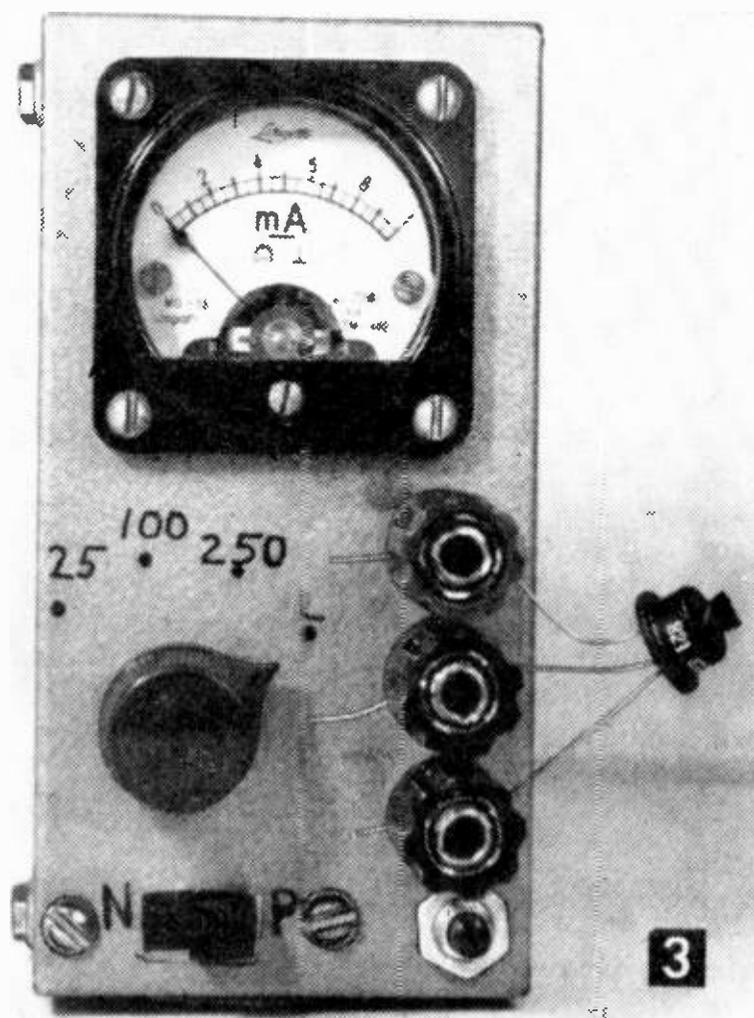

Front view of the tester with a transistor connected for test.



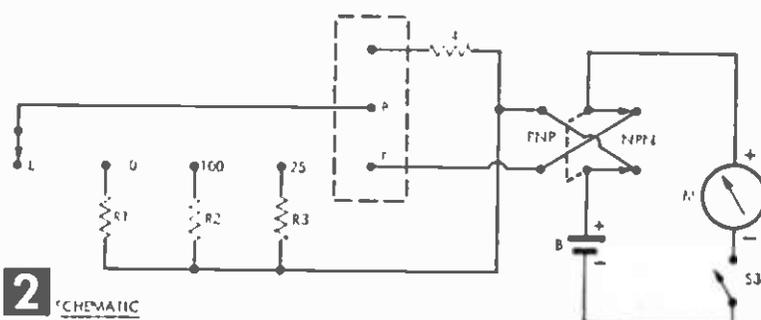
Many of the features of larger units are to be found in this transistor tester.



This compact transistor tester has these features, and in addition is small enough to fit in your pocket (case is only $1\frac{5}{8} \times 2\frac{1}{8} \times 4$ in.). The case is a rugged aluminum box that can stand rough handling. And the batteries are penlite cells—easy to obtain anywhere.

The hole layout for the case is shown in Fig. 5. All holes except the meter and switch hole are made with a $\frac{1}{8}$ -in. drill. A taper reamer may be used to enlarge holes where greater diameters are required. The large meter hole may be made with a hole punch, a fly cutter or by drilling a series of holes with a small drill and smoothing to size with a small file. The rectangular hole for the npn-pnp switch can be made by drilling several $\frac{1}{8}$ -in. holes and smoothing to size with a small file. It's a good idea to fasten the back to the case for extra support before drilling holes.

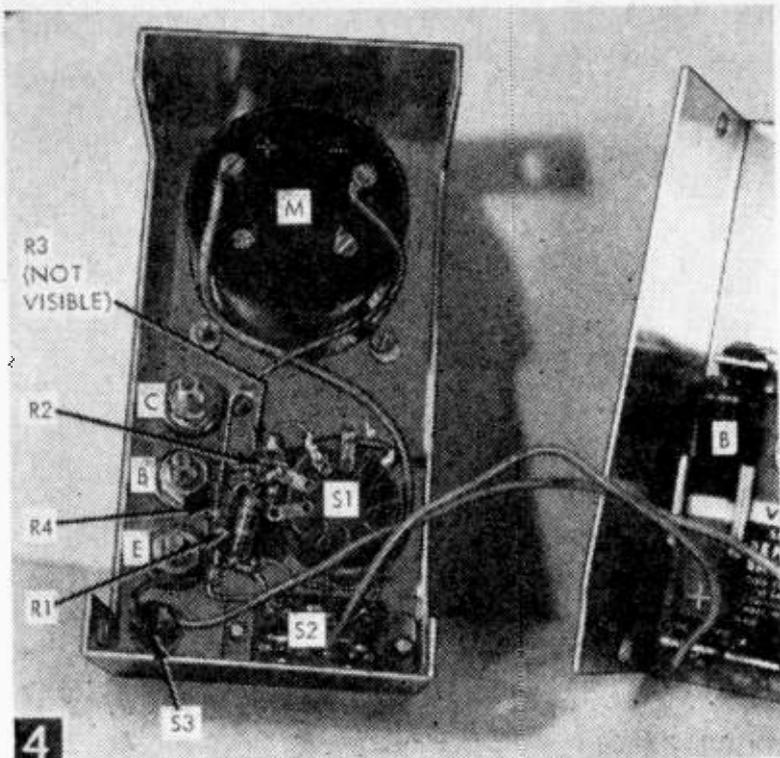
Mount the switches, terminal posts and meter on the front of the case, following Figs. 3 and 4. Mount the battery holder on the case back. Turn the battery holder lugs over till they touch, and solder for series connection. Fill the battery holder eyelets with solder to assure good connection to the batteries. Then



4 This inside panel view shows parts mounting and wiring.

MATERIALS LIST—COMPACT TRANSISTOR TESTER

Desig.	Description
R4	2.2K, 1/2-w. carbon resistor (10%)
R3	15K, 1/2-w. carbon resistor (10%)
R2	600K (680K and 4.7 meg. 1/2-w. carbon in parallel)
R1	1.5 meg. (3.3 meg. and 2.7 meg. 1/2-w. carbon in parallel)
S1	SP4T miniature rotary switch (Grayhill 5001-4)
S2	DPDT slide switch (Lafayette SW-17)
S3	SPST normally open momentary contact sw. (Grayhill 30-1)
M	0-1 ma. dc meter (Lafayette TM-400)
B	four 1.5 v. penlite cells in series (Burgess #7) battery holder (Lafayette MS-170) binding posts (Grayhill, 1 red 29-3R and 2 black 29-3B) 1 5/8 x 2 1/8 x 4" aluminum case (Bud CU-2102-A) knob (Lafayette KN-19)

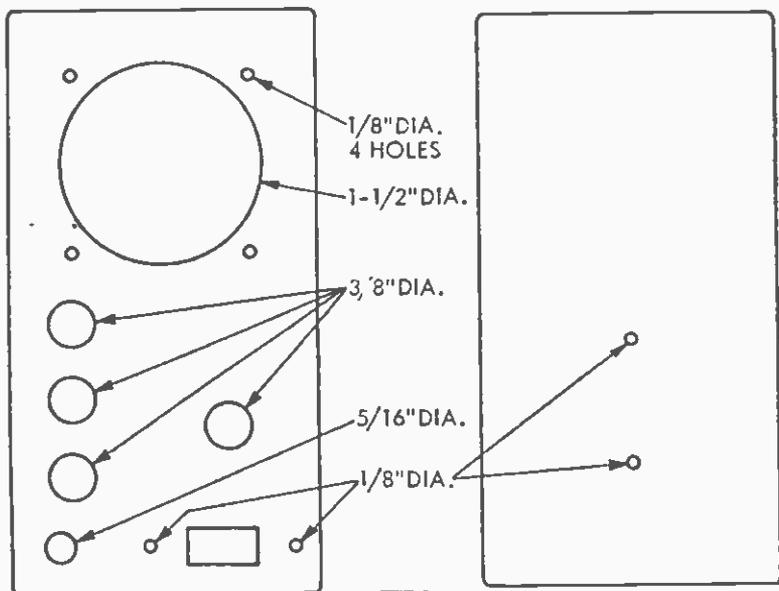

REAR VIEW OF FRONT PANEL

5

REAR VIEW OF BACK PANEL

proceed with the wiring of the tester according to the schematic (Fig. 2) and Fig. 4.

Note that a 3.3 megohm and a 2.7 meg. resistor are connected in parallel to produce a resistance of 1.5 megs. (R1). A 680K and 4.7 meg. resistor are connected in parallel to obtain a resistance of 600K (R2). If you com-

pute the actual values of these parallel combinations, you'll find that they differ slightly from the values cited, but they're sufficiently close for all practical purposes.

Markings may be made on the front of the transistor tester case with India ink. Cement four small rubber grommets to the back of the case to serve as feet for the tester.

Operation. To use the transistor tester align the transistor leads and insert them in the terminal posts. The red (top) terminal post is the collector terminal. The base connects to the middle terminal, and the emitter connects to the lower terminal.

Set the npn-pnp switch for the type of transistor to be tested. Set the range switch to the leakage (L) position. Depress the on-off switch. The meter reading is the leakage current for the common emitter configuration.

Next, rotate the range switch to the range which gives the fullest scale reading when the on-off switch is depressed without deflecting the meter off scale. The beta of the transistor is the meter reading the range switch multiplier.

Example 1: A GE 2N107 transistor was tested. Leakage current was .1 ma. (100 microamperes). On the 100 range, the meter read .35. Beta was $.35 \times 100$ or 35. The beta was relatively low in this case.

Example 2: A GE 2N508 transistor was tested. Leakage was .15 ma. The meter read .5 on the 250 scale. Beta was $.5 \times 250$ or 125. Beta was relatively high in this case, a good argument for using the better entertainment grade transistors in preference to experimenter grade transistors.


Your compact transistor tester will help you to get the most out of your transistor work. It will emphasize transistor qualities that make transistor circuits perform well or otherwise. This tester will save you time and trouble.

The figure of merit of a transistor that is most commonly recognized is Beta. Beta is collector current divided by base current in the common emitter circuit configuration. Resistors R1, R2 and R3 provide base currents of 40, 10 and 4 microamps respectively for full meter deflection on the 25, 100 and 250 beta ranges. The base is left open for the leakage measurement. Leakage current for the common base configuration, frequently referred to as I_{co} , may be computed by dividing leakage current by beta. Thus, I_{co} in example 1 was $100/35$ or approximately 3 microamps. In example 2, I_{co} was $150/125$ or approximately 1 microamp.

The 2.2K resistor in series with the collector terminal limits meter current to a safe value if a short circuited transistor is placed in the tester. The double-pole double-throw switch reverses battery polarity to provide proper biases for npn or pnp transistors.

PRINTED CIRCUIT

Phono Amplifier

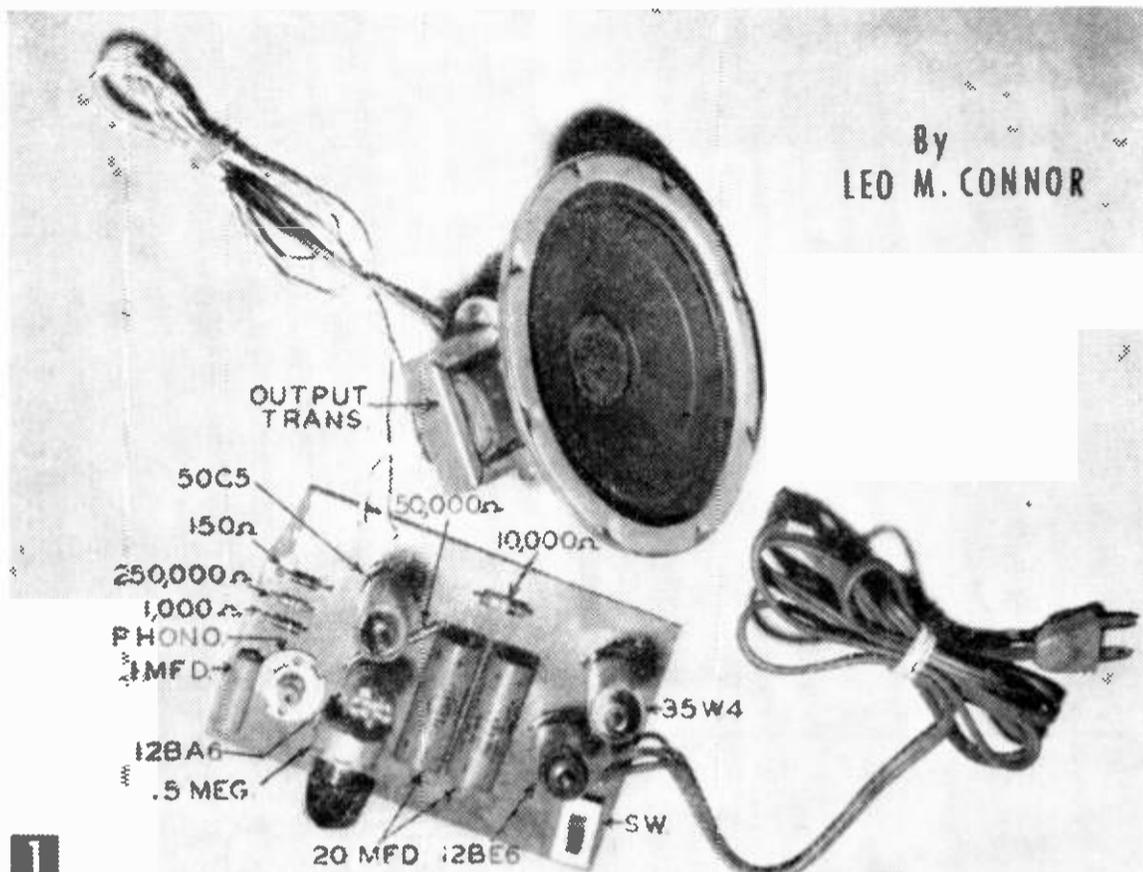

You can play your crystal-cartridge record player through this printed circuit phono amplifier. Or, with a crystal mike it makes a dandy PA system.


WANT to try your hand at making a printed circuit? Here's an easy one to start out with. Figure 3 shows the phono amplifier etched circuit pattern actual size. Try your parts on the pattern to make sure they will fit. The parts will be on top of the board and the pattern under the board.


You will need pencil carbon (not typewriter carbon) to trace the circuit. This paper is coated on both sides and feels soft. Place the circuit board, copper side up, under the carbon paper, the drawing over the carbon and Scotch-tape all together.

Use a 4H pencil with a sharp point. Outline all the dark areas of Fig. 3. For the long, straight lines, place a ruler along the line as a guide for the pencil. Use plenty of pressure on the pencil. First, trace all horizontal marks using a straightedge as a guide. Next trace the vertical lines and then all lines that are at an angle. The circles are traced last. The small circles centered throughout the drawing are hole centers. These may be traced or a small prick punch may be used to mark through the paper and into the copper. In either case, the centers must be accurately located so that the tube socket pins will line up properly.

After all lines have been traced and the hole centers marked, loosen the drawing and carbon paper at one end so you can check

and make sure you have not left out any connections. The board is now ready for inking with acid resistant. Apply it to the copper with a pen or small brush. Completely cover all copper that is to be preserved (the dark areas of Fig. 3). The sharpness of the finished pattern will be determined by the sharpness of the ink work, so use care in getting smooth lines. Should you make an error, wait until the ink dries and then erase the line with a hard eraser. For small patterns, ordinary wax crayon can be used instead of acid resistant ink. If this method is used, the pattern can be made like a stencil and the crayon rubbed over the openings. It is advisable to warm the board slightly if you use crayon as an acid resist.

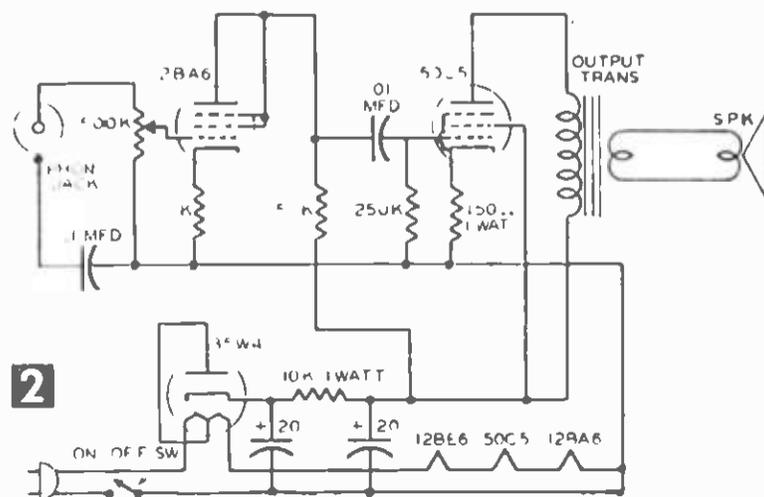

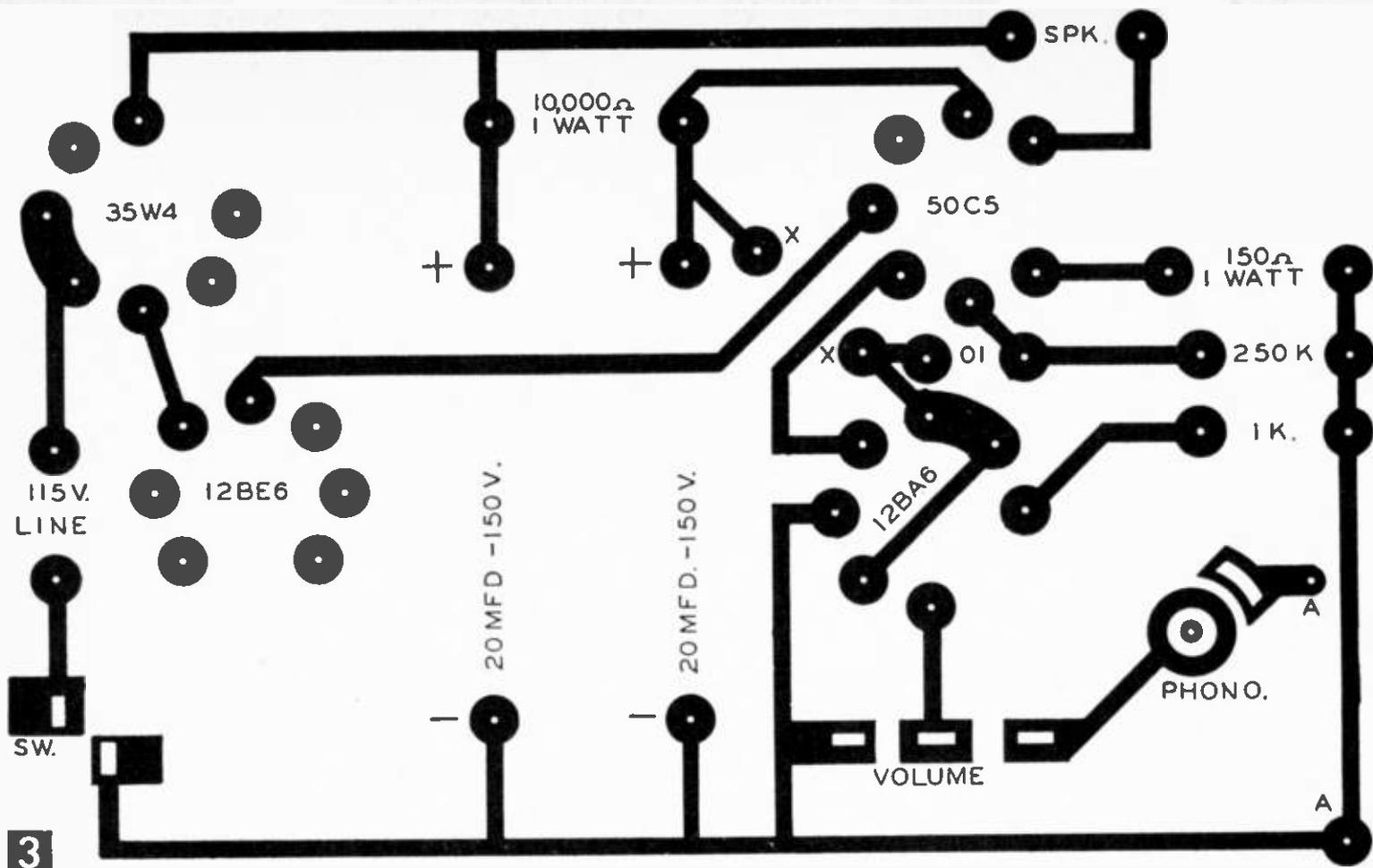

MATERIALS LIST—PHONO AMPLIFIER

No. Reqd.	Description
1	1,000 ohm, 1/2-watt resistor
1	50,000 ohm, 1/2-watt resistor
1	250,000 ohm, 1/2-watt resistor
1	150 ohm, 1-watt resistor
1	10,000 ohm, 1-watt resistor
2	20 mfd, 150 v electrolytic capacitor
1	.01 mfd, disc ceramic capacitor
1	.1 mfd, 400 v paper capacitor
1	12BA6 tube
1	12BE6 tube
1	35W4 tube
1	50C5 tube
1	phono connector and plug
1	500,000-ohm audio taper volume control
1	SPST slide switch
1	power cord and plug
1	5" PM speaker
1	output transformer
4	printed circuit tube sockets (Allied 42H411)
	Circuit board and etching materials (Allied 43N069 kit contains all materials, costs \$3.38)

If you have punched the hole locations (white dots) be sure that the punch marks are filled with ink. Otherwise, the acid will work there.

The unwanted copper is removed with etchant. Wear rubber gloves and old clothes when working with this acid. Place the etching solution in a glass or enamel pan which is slightly larger than the circuit board.

Etching can be speeded by holding the board in the gloved hand and rocking it so that the acid runs back and forth over the board.

Remove the board from the acid and rinse it in cold running water. Then remove the ink with scouring powder.

The holes for tube socket pins and wire leads are drilled with a #40 drill. Use the centering holes as starting marks for the drill.

The only larger hole is for the center connection of the phono jack. Use a 1/8-in. bit after first drilling a pilot hole with the small drill.

The slots for the switch contacts, the volume control and the phono jack ground connection are made by first drilling #40 holes at the ends of the slots and then drilling as many holes as possible between the end holes. Finish the slots with a rat-tail file.

Figure 1 shows all parts except the .01 mfd ceramic coupling capacitor. This part is between the 50C5 tube and the 12BA6 tube. Note that all parts are on the side of the board opposite the pattern. Start by mounting the tube sockets. To mount the socket, line up the holes and pins and push the pins through the holes from the top of the board. Solder the pins to the pattern using a light iron, preferably 25 watts, and rosin core solder. Work carefully because too much heat will loosen the foil from the board.

Push filter capacitor leads through, observing polarity, and solder leads to pattern. The mounting flaps of the on-off switch may be cut off with a hack saw and the rough edges removed with a file before mounting the switch. Push switch lugs through the slots in the board. Bend the lugs down against the copper and solder.

Mount the phono jack next. After pushing the terminals through the board, flow solder around the flat part of the center connection but leave the angled sides of this terminal free to expand so that the plug can be inserted later. Now, mount the volume control.

Mount the resistors. The 50,000 ohm plate load resistor for the 12BA6 tube should be mounted in the holes marked X-X.

The .01 mfd disc ceramic capacitor is mounted in holes A-A standing on edge.

The output transformer is mounted on the speaker. The voice coil leads are connected to the secondary of the transformer and the transformer primary is connected, by a pair of stranded wires, to the holes marked SPK on the drawing.

The power cord is connected last. Push the bare ends of the leads through the holes in the board until the rubber insulation is tight against the board. Solder the leads to the pattern and cut off the excess length.

The mounting of parts is now completed and the tubes can be placed in their sockets. The 12BE6 tube is used solely as a filament dropping resistor. It costs no more than a high wattage resistor and generates less foiling heat.

Before applying power to the circuit, block the board up so that the circuit cannot come in contact with something on the work bench. After plugging the cord into an outlet, turn the switch ON. All tubes should light up. The volume control should then be advanced about half way and the center terminal of the phono jack touched with the finger. You should hear a loud buzz when this is done.

If the amplifier checks out this far, you are

ready to connect a crystal type record player to the input. It is also possible to connect a crystal microphone to the input and use the amplifier as a small PA system.

The amplifier may be mounted in any convenient manner provided there is enough ventilation to carry away the heat generated by the tubes. Any mounting can be used for the speaker. A 5-in. speaker mounted in a scaled down Carlson enclosure and this amplifier will provide surprisingly good quality.

Wire Soldering Technique

- When joining electrical wires or wires in electronic circuits, it is frequently difficult to hold two wires and the soldering iron or gun in position for a good solder joint. This problem can be considerably eased by tinning both wires before placing in contact. This then becomes a sweating rather than a soldering technique, which takes less heat for less time because the work does not have to be brought up to soldering temperature. Touch the wires lightly and apply the iron for just an instant to melt the solder and complete the joint. The joint will have sufficient mechanical strength and, if the resin core type of solder is used, it will carry current efficiently.




"Man out here with the latest bookshelf equipment, dear."

The circuit designer with a test amplifier on the board. The voltmeter aids voltage setting. A head-phone is the amplifier load.

Transistor Circuit Designer

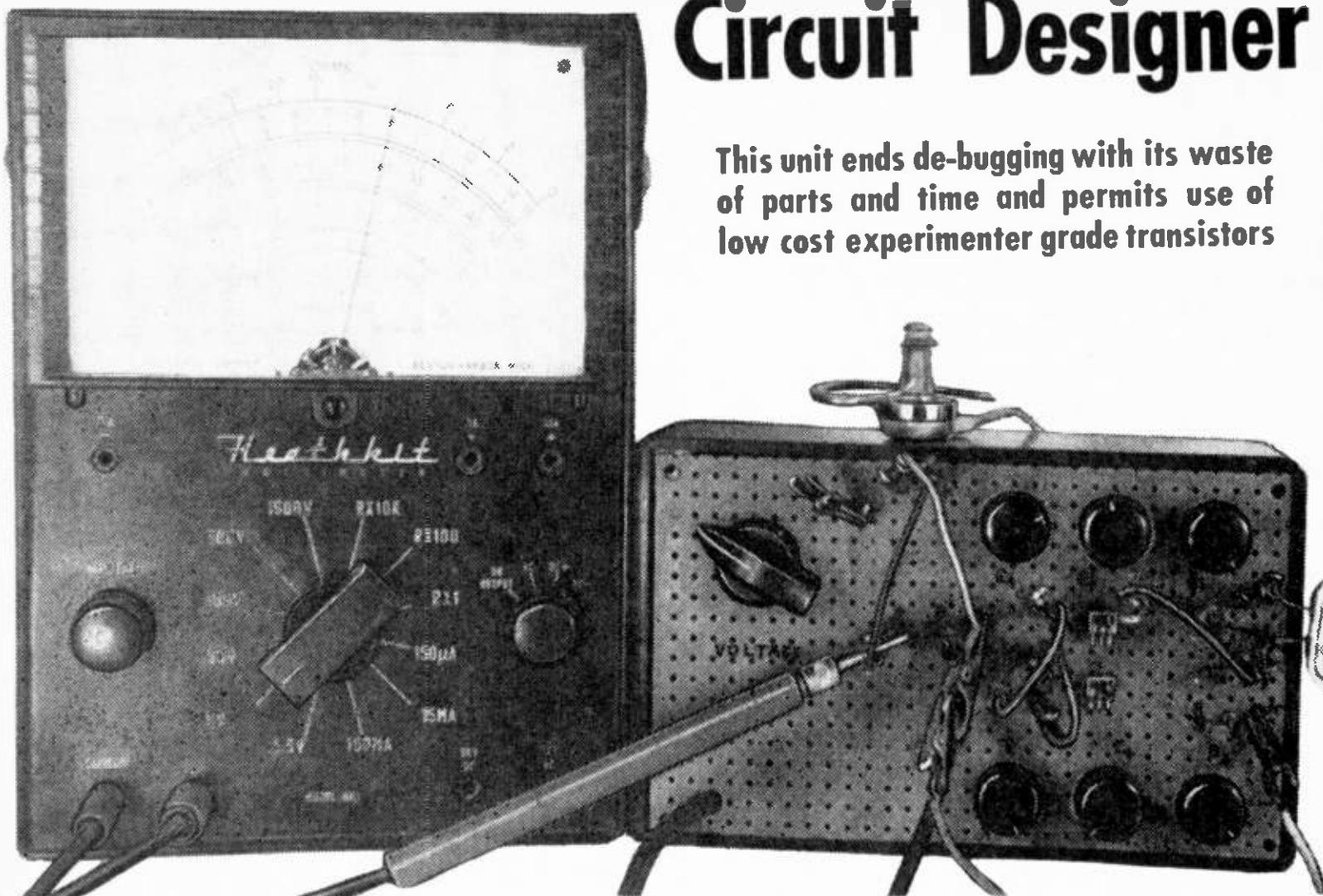This unit ends de-bugging with its waste of parts and time and permits use of low cost experimenter grade transistors




By FORREST H. FRANTZ, Sr.


THIS instrument permits the design of one and two stage transistor amplifiers and facilitates rapid measurement of their characteristics. The unit, costing \$10 to build, is also useful as an auxiliary power supply and amplifier for other transistor equipment.

The unit is enclosed in a 2 x 3 3/4 x 6 1/4-in. Bakelite case. The circuit is constructed on the perforated Bakelite board front panel.

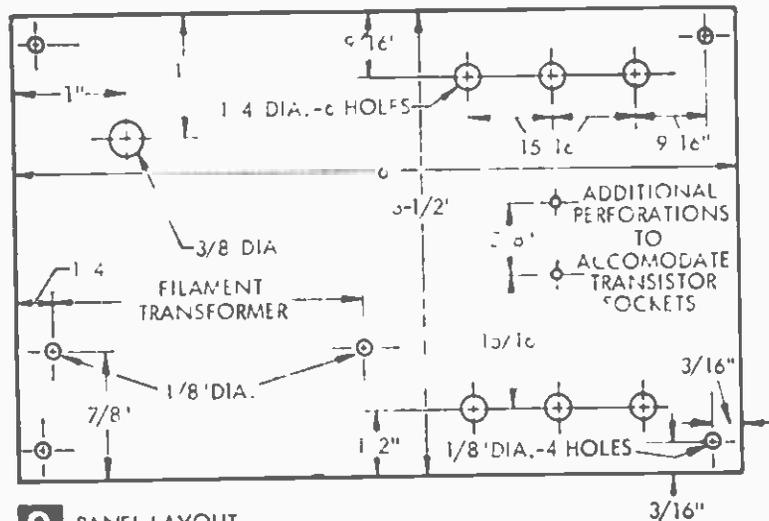The power supply is a 6.3 v. filament transformer, two diodes in a voltage doubler circuit.



2 PANEL LAYOUT

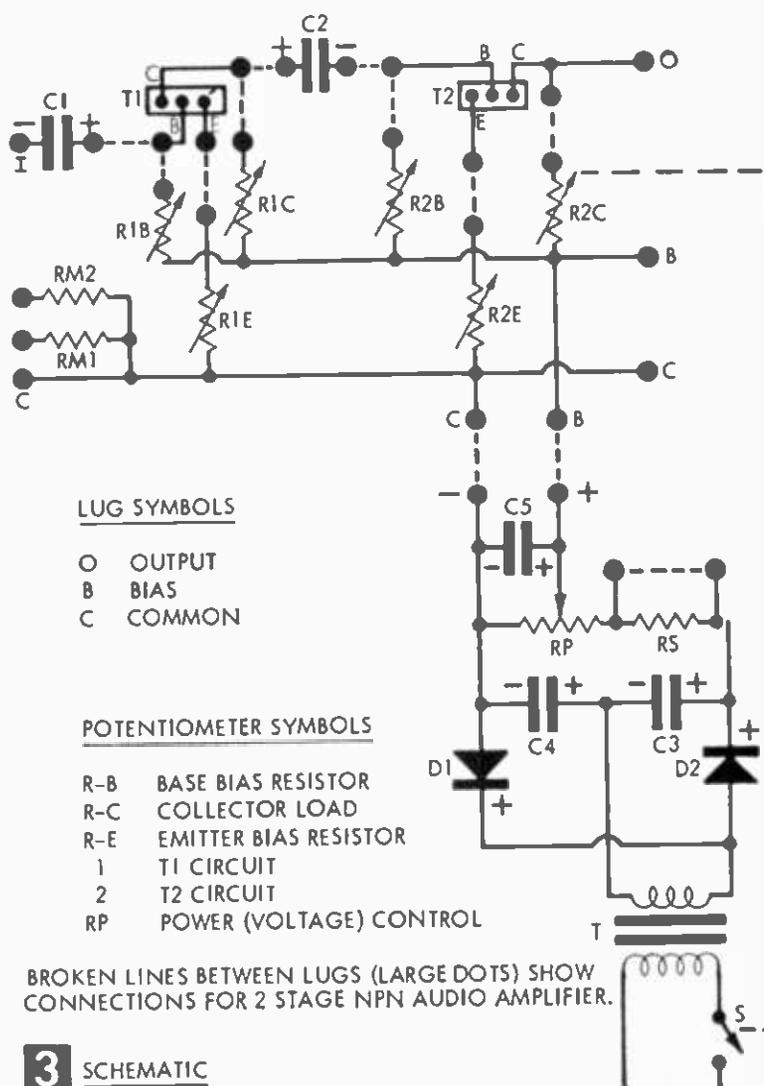

LUG SYMBOLS


- O OUTPUT
- B BIAS
- C COMMON

POTENTIOMETER SYMBOLS


- R-B BASE BIAS RESISTOR
- R-C COLLECTOR LOAD
- R-E EMITTER BIAS RESISTOR
- 1 T1 CIRCUIT
- 2 T2 CIRCUIT
- RP POWER (VOLTAGE) CONTROL

BROKEN LINES BETWEEN LUGS (LARGE DOTS) SHOW CONNECTIONS FOR 2 STAGE NPN AUDIO AMPLIFIER.


3 SCHEMATIC

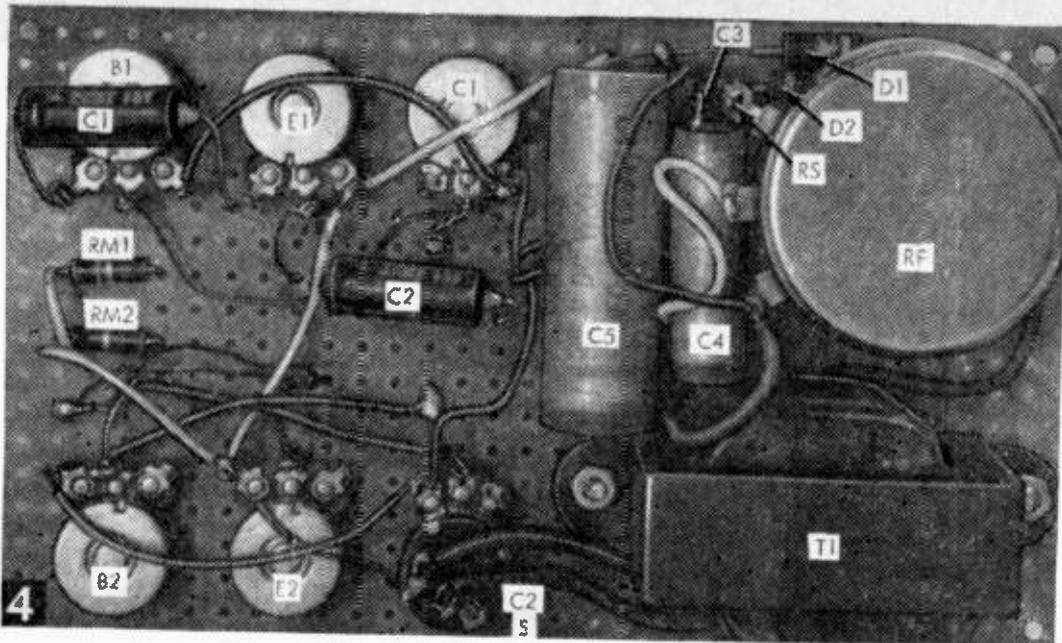

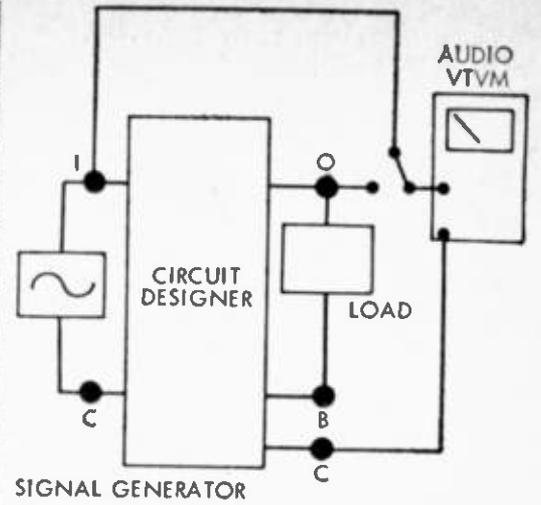Under-panel view, showing parts and wiring.



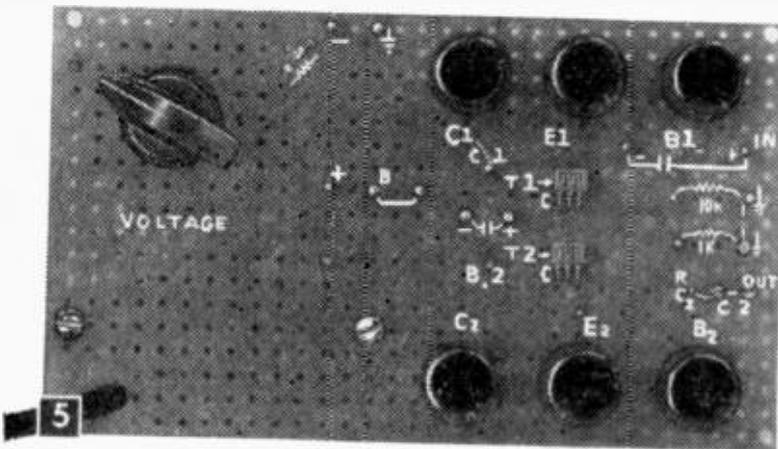INPUT - OUTPUT
CIRCUIT INSTRUMENTATION FOR
HIGH GAIN AMPLIFIER DESIGN AND
FREQUENCY RESPONSE MEASUREMENTS



Top-panel view. Experimental component connections are marked.

cuit, a voltage output control and filters.

On the top of the front panel are the two test circuit transistor sockets and leads from two electrolytics for the test circuit and two resistors to determine input impedance. The six potentiometers adjust collector load, emitter bias and base bias for the test transistors.

The transistor sockets are connected for the common emitter configuration, but other configurations may be readily investigated by switching transistor leads in the sockets. The power supply may be connected for either pnp or npn transistors. Connections between experimental components are made with mini-gator clip leads.

The front panel is cut and drilled as in Fig. 2. Mount power transformer and pots first. Then wire the power supply according to schematic (Fig. 3) and Fig. 4. Push leads through board holes and solder. Some lead ends will serve as lugs for attachment of test clips and are shown in schematic. Splice on #18 wire if leads aren't long enough.

Attach transistor sockets to panel with Duco cement. Solder leads to the transistor sockets and pass them through the panel and wire in.

Operation. We will use a grounded emitter circuit. Resistor RS in the power supply

is shorted with a jumper wire, except when control of voltages of less than a volt is required. When this resistor is shorted, the power supply provides about 10 v. for a load drawing 20 ma. and about 5 v. for a 50 ma. load. The voltage may be monitored with a voltmeter.

This power supply may be used with npn transistors by connecting the - power supply lug to the adjacent ground lug and the + lug to the adjacent B lug. Reverse the connections for pnp transistors. The power supply may also be used as a power supply for other transistor equipment.


The circuit to be designed is wired up on the designer with clip heads, and best bias and load resistance values are found by adjusting the dials. In the schematic (Fig. 3) a two-transistor stage audio amplifier is on the designer.

The emitter bias pots which stabilize the transistor dc operating points also introduce negative feedback. This flattens the amplifier frequency response, but also decreases amplifier gain. If frequency response is unimportant, the emitter bias pots (R1E and R2E)

MATERIALS LIST—CIRCUIT DESIGNER

Desig.	Description
RP	500 ohm, 3 w. potentiometer (Clarostat 58-500)
R1E, R2E	1K potentiometer (Lafayette VC-32)
R1C	10K potentiometer (Lafayette VC-34)
R2C, S	10K potentiometer with switch (Lafayette VC-28)
R1B, R2B	1 megohm potentiometer (Lafayette VC-38)
RS, RM1	1K, 1/2-w. carbon resistors
RM2	10K, 1/2-w. carbon resistor
C1, C2	20 mfd., 15 v. electrolytic capacitor (Lafayette CF-123)
C3, C4	100 mfd., 15 v. electrolytic capacitor (Lafayette CF-126)
C5	160 mfd., 25 v. electrolytic capacitor (Lafayette CF-145)
D1, D2	germanium diodes (General Electric 1N64)
T	6.3 v. filament transformer (Lafayette TR-11)
6	knobs (Lafayette MS-185)
T1, T2	transistor sockets (Lafayette MS-149)
1	perforated Bakelite board (cut from Lafayette MS-305)
1	Bakelite case (Lafayette MS-216)

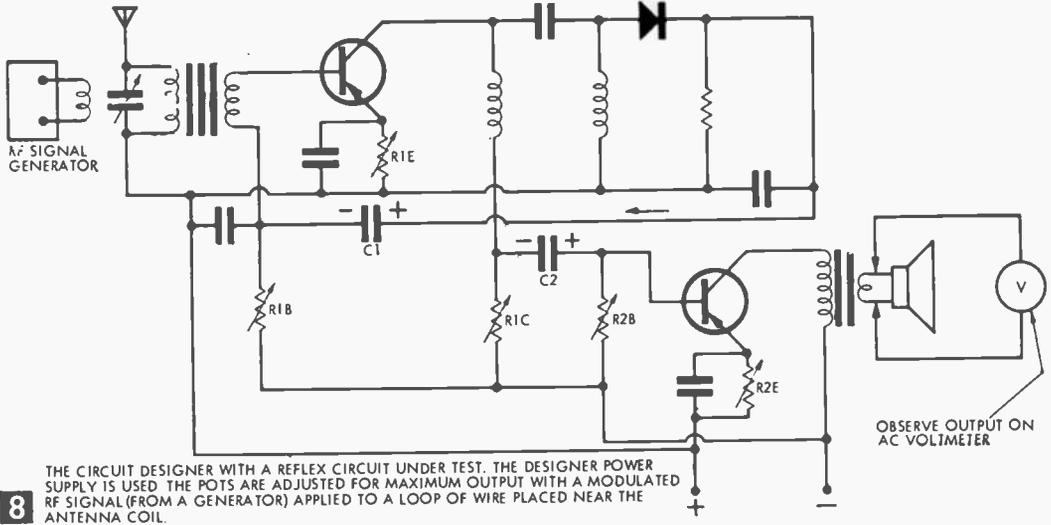Parts are available from Lafayette Radio Co., Dept. SM, 165-08 Liberty Ave., Jamaica 33, N. Y.



8

THE CIRCUIT DESIGNER WITH A REFLEX CIRCUIT UNDER TEST. THE DESIGNER POWER SUPPLY IS USED. THE POTS ARE ADJUSTED FOR MAXIMUM OUTPUT WITH A MODULATED RF SIGNAL (FROM A GENERATOR) APPLIED TO A LOOP OF WIRE PLACED NEAR THE ANTENNA COIL.

may be bypassed with electrolytic capacitors (about 10 mfd) for increased gain. The desired dc stabilization will be retained.


Note that the actual load, say a headphone or a loudspeaker and output transformer, may be connected to lugs O and B for the design adjustments. Furthermore, the device which is to drive the amplifier, a broadcast tuner for example, may be connected to the input terminals for performance checks.

For more critical circuit design where highest gain is desired, the input-output circuit arrangement of Fig. 6 should be used. With a 1000-cycle signal input, adjust the designer pots for maximum output indication on the audio voltmeter.

This circuit is also used for obtaining the desired frequency response if this characteristic is of importance to you. Frequency response is improved by increasing the emitter resistances R1E and R2E. Simply record the output for various frequencies as you vary the audio signal generator frequency—then plot the frequency response. If you want to do a fast design job, though, you can check the output only at the lowest and the highest frequency to which the amplifier is to be flat against the output at 1,000 cycles.

The resistors RM1 and RM2 were provided for determining input impedance of an amplifier under design or for designing an amplifier with a given input impedance. Figure 7 shows the circuit and calculations. Input impedance may be increased by increasing emitter bias resistance of the first transistor.

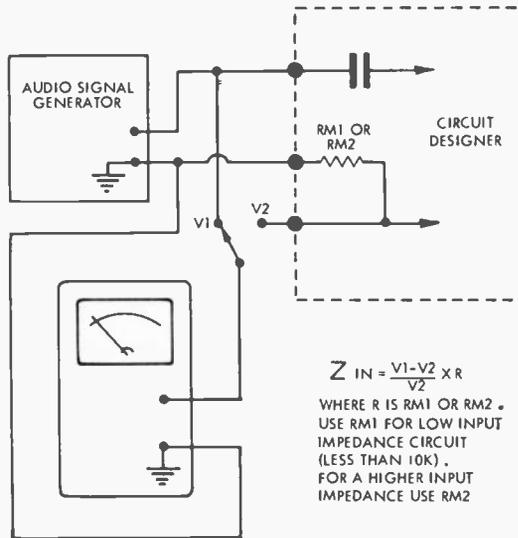The designer may also be used for designing RF, IF, and reflex circuits. The instrument shown in the photographs does not have this provision. This instrument was designed primarily for evaluating audio amplifiers and does not contain all of the connection lugs shown in the schematic (Fig. 3). But, if



7

INPUT IMPEDANCE MEASURING CIRCUIT AND CALCULATIONS

$$Z_{IN} = \frac{V1 - V2}{V2} \times R$$

WHERE R IS RM1 OR RM2 .
USE RM1 FOR LOW INPUT
IMPEDANCE CIRCUIT
(LESS THAN 10K) .
FOR A HIGHER INPUT
IMPEDANCE USE RM2

you'll provide all of the lugs shown in Fig 3, you can evaluate RF, IF and reflex circuits. The circuit arrangement for a typical reflex receiver is shown in Fig. 8. External coils and capacitance must be used, and the arrangement becomes quite crowded.

One note of caution: The miniature potentiometers that I used in the circuit designer are of the audio taper type. To obtain bias and load resistance values for the equipment which is to be constructed, measure resistance values of all controls after optimum settings have been made. Linear resistance scales for these controls would be misleading, but you can provide these pots with scales by calibrating with an ohmmeter.



The Little Cub Receiver


By HOMER L. DAVIDSON

Transistorized printed circuitry combined with simple construction makes the Little Cub receiver an ideal project for boys, individually or in groups.




THE circuit of this small receiver is very simple; technically it is nothing more than a tuned grid and tuned plate feedback circuit, and youngsters will have a lot of enjoyment building it and using it. The antenna is capacity-coupled to a tuned tank circuit with a 50-turn secondary wound over a commercial ferrite coil. This output is coupled through a tuning capacitor to the base terminal of the first transistor (TR 1). Feedback is also obtained through this capacitor and transistor, and a second tuned circuit is found in the collector circuit of TR 1. A small audio transistor (TR 2) stage adds volume to the receiver's operation, and a phone jack enables record playing through it. Both emitter terminals of the transistors are tied to the positive terminals of the battery (See Figs. 2 and 3).


Construction. The front panel is constructed from a 6x10-in. printed-circuit board. First, roughly lay out the lines and hole dimensions on the copper plate. Make sure that the plate is clean. If not, wash it with soap and water. All straight lines were made with the black resist tape and joined with liquid paint resist. The PRLT pens (see materials list) are of the ball-pen type. Simply hold the pen in the hand and push down on the ball of the pen and liquid will start to flow. You can use any color of resist you wish, although black shows up the best. Let circuits dry for several hours before placing in the etching solution.

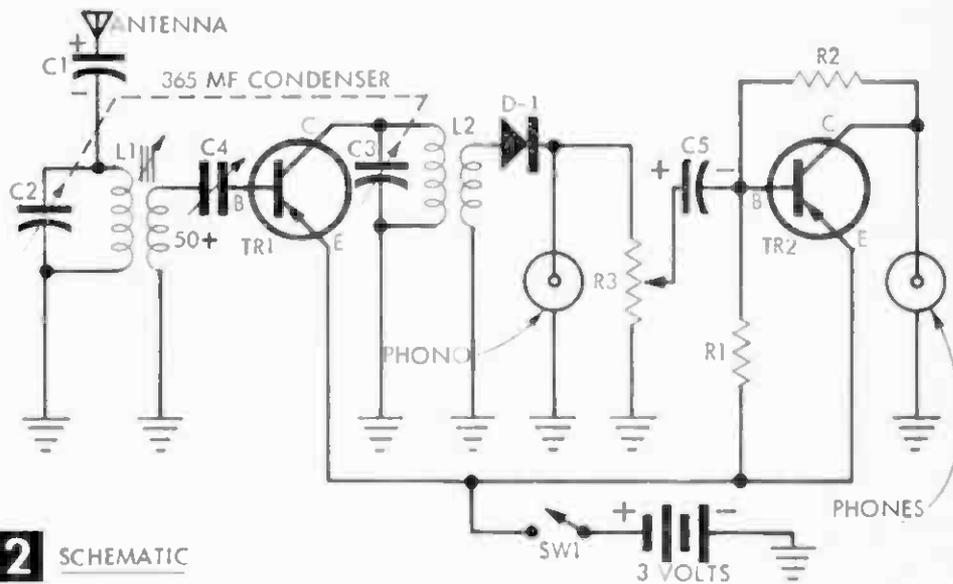

2 SCHEMATIC

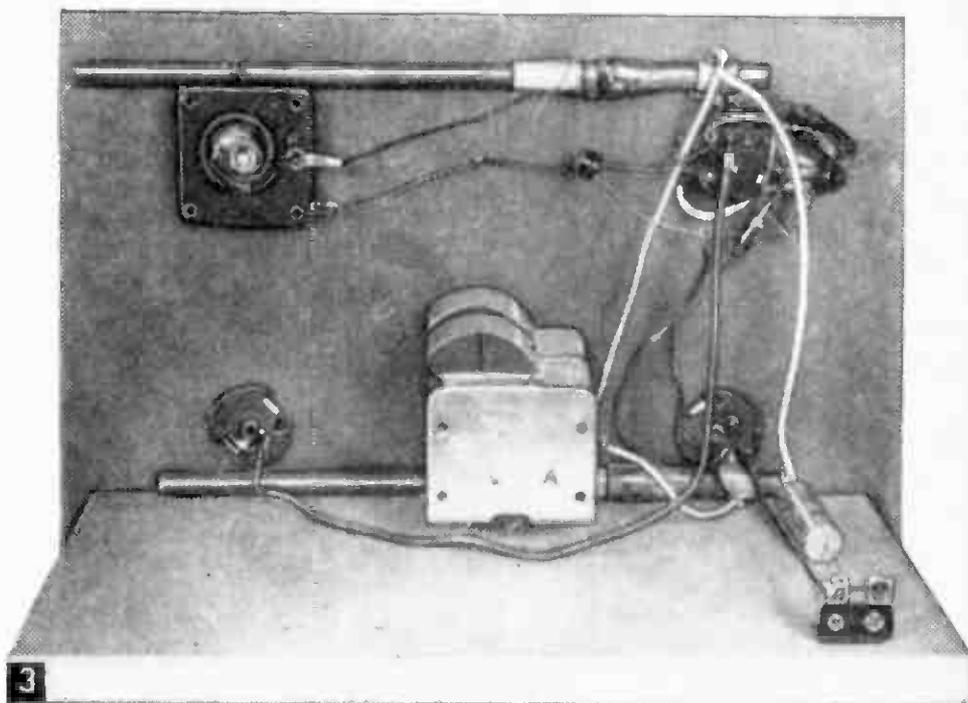

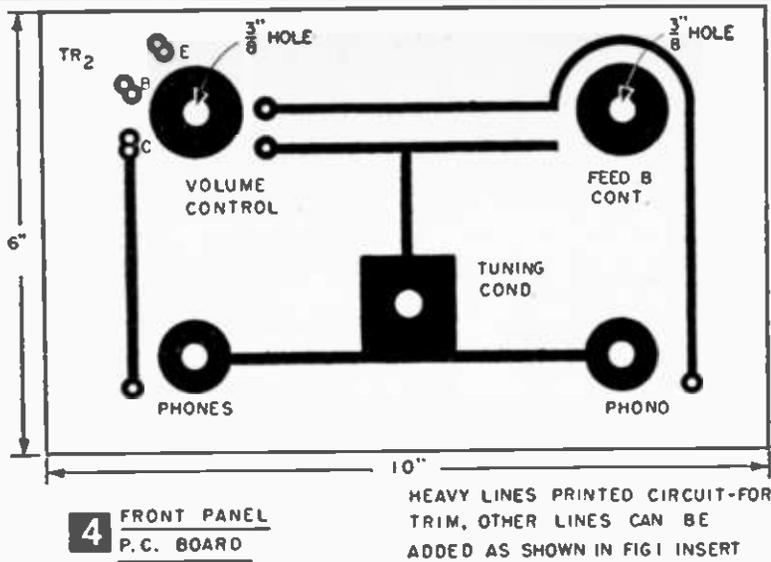As an etching container, use a large flat glass baking dish. Place the copper board in the bottom of the dish and pour just enough liquid etchant solution over it to cover. (If the solution gets on your hands, wash it off with soap and water. Clothing will be



MATERIALS LIST—LITTLE CUB

Desig.	Description
C1	.01 capacitor, 200 V
C2, C3	365 mfd variable capacitor, two-gang TRF (Lafayette MS142)
C4	365 mfd, variable capacitor (Lafayette MS215)
C5	10 mfd, 50 V elect. capacitor
R1	12,000 ohm carbon fixed resistor
R2	220,000 ohm carbon fixed resistor
R3	10,000 ohm variable resistor with S.P.S.T. switch (SW1)
TR1	2N414A Raytheon transistor
TR2	2N107 GE transistor
D1	1N64 fixed diode
L1, L2	Superex 7" loopstick with 50 turns of 28EN wire over original winding
2	phono jacks
2	penlite cells
Printed Circuit Materials	
1	Technicians Kit #5002P. or
1	PCA copper-laminated board 9 x 12 in.
1 pt.	PE5 etchant liquid
1 roll	tape resist PRT-1
1	liquid ball-point pen PRLT

There will be a quantity of tape, etchant liquid and pen resist left over from this experiment so all that would be needed to construct other experiments would be to purchase extra copper-laminated boards.

Printed circuit material available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, New York, or direct from Techniques, Inc., Dept. C, P. O. Box 85, Hackensack, N. J.

soiled with a brownish color if the solution comes in contact with it, but this solution is not dangerous in any form.)

To help the solution etch the copper plate more rapidly, rock the container. The etching process takes about 45 minutes. Pull the board up every few minutes and view the etching process. All of the copper will be gone when the process is complete. The only remaining copper will be under the paint resist.

When etching is complete, wash the board in clear water, pour the etchant liquid back into its bottle (it can be used over and over again) and wash the glass container in soap and water. Pull off the resist tape and, with any kind of cleaning solution such as carbon-tet, or by scraping, remove the resist paint. Be extremely careful that you do not injure the copper circuit lines. Now, drill all of the holes required (See Fig. 4).

After the front panel has been etched, mount components. The large parts, such as the variable capacitor and volume control,

are mounted first. TR1 is wired directly to the feedback capacitor and then On-Off switch. Mount coil L1 at the top of the panel with the grounded side soldered to the ground lug of the volume control. The collector tank coil (L2) is mounted at the bottom of the chassis with its grounded side soldered to one side of the phone jack. A two-lug insulator is screwed to the plywood base, for antenna and ground connections, as is the battery holder. Finally solder small components in place.


The coils are the 7-in. superex ferrite type with an extra winding of 50 turns of No. 28 enameled wire added over the original winding.

Operation. To test, plug in phones and record player. Turn set on and with recording on turntable, it should be heard. (The volume can be raised or lowered with the volume control.) Unplug record player and hook up the long-wire antenna system. Tune for a station in the middle of the band. When a station is located, turn up the feedback control and a loud squeal will result. Lower this control's setting until the station is audible. Now tune L1 by pushing its core in and out. The station will get louder—and oscillation may occur. If it does, turn the feedback control down. Next, adjust L2 for maximum signal. (This adjustment is not as critical as L1.) Go over adjustments again until the best signal is heard and stations can be received at both ends of the band. Feedback should occur over all of the band.




Beginner's Volt-Ohmmeter

By FORREST H. FRANTZ, SR.

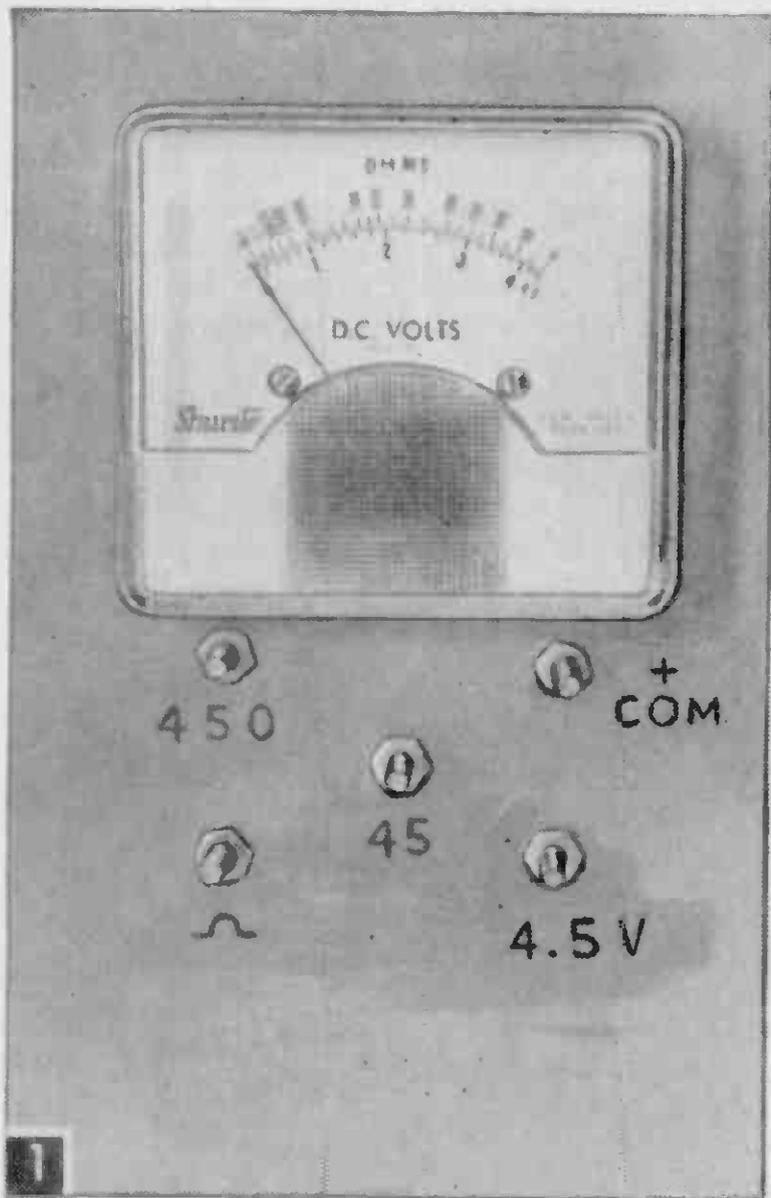

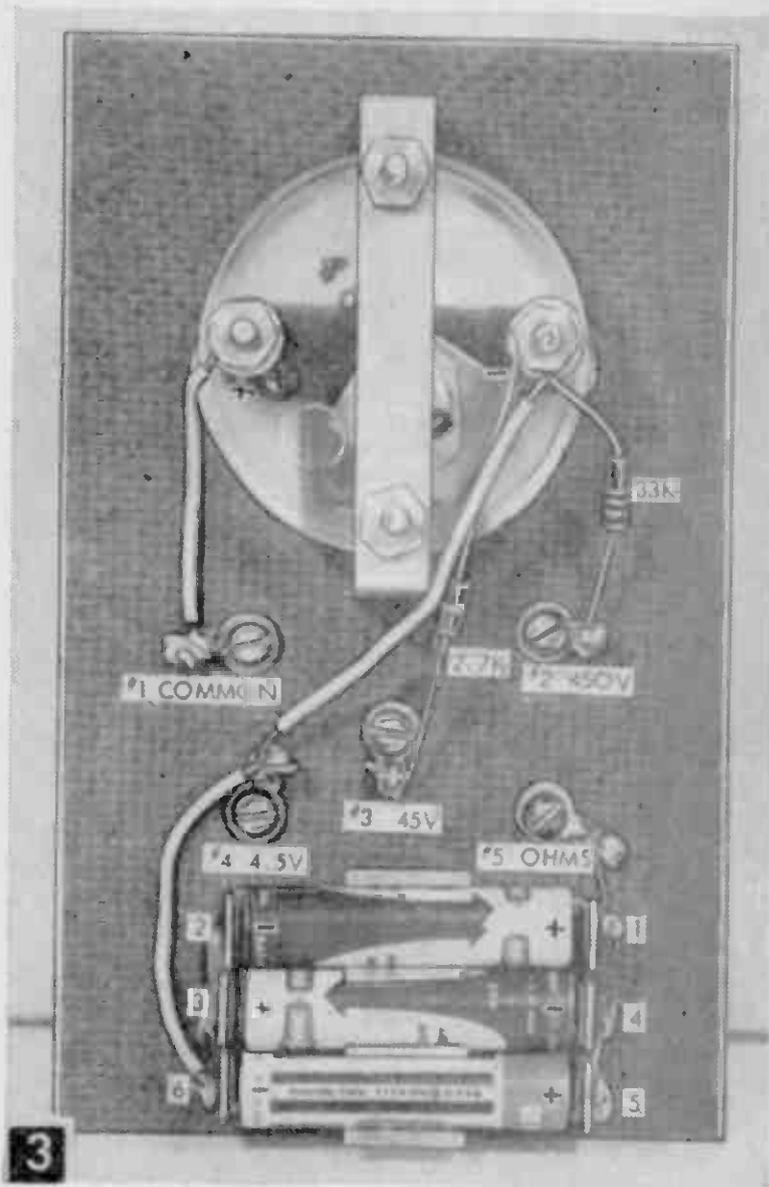This inexpensive volt-ohmmeter employs machine screws as terminals for Mini-Gator clips on test leads.



Parts mounting. Piece of #18 wire (arrow) supports battery holder.

THIS DC volt-ohmmeter costs about \$3.50 to make. It will serve to introduce the beginner to the use of volt-ohmmeters.


All parts are mounted on a panel made of a scrap piece of Masonite 3½ x 5½ in. or larger.

The panel layout is shown in Fig. 2. Cut the 2¼-in. meter hole with a coping saw or hacksaw after drilling starting holes. Smooth with a round file. Give the panel a coat of gray enamel.


Mount the meter, first removing the U-shaped panel clamp fastened to the back of the meter. Push the meter through the hole on the panel and replace the U-clamp on the back of the meter. Before you tighten it all the way against the back of the panel, be sure you have the meter lined up properly on the front of the panel. Next, mount the five machine screws on the panel. Place soldering lugs under the screws.

Wire according to Fig. 3 and the schematic, Fig. 4.

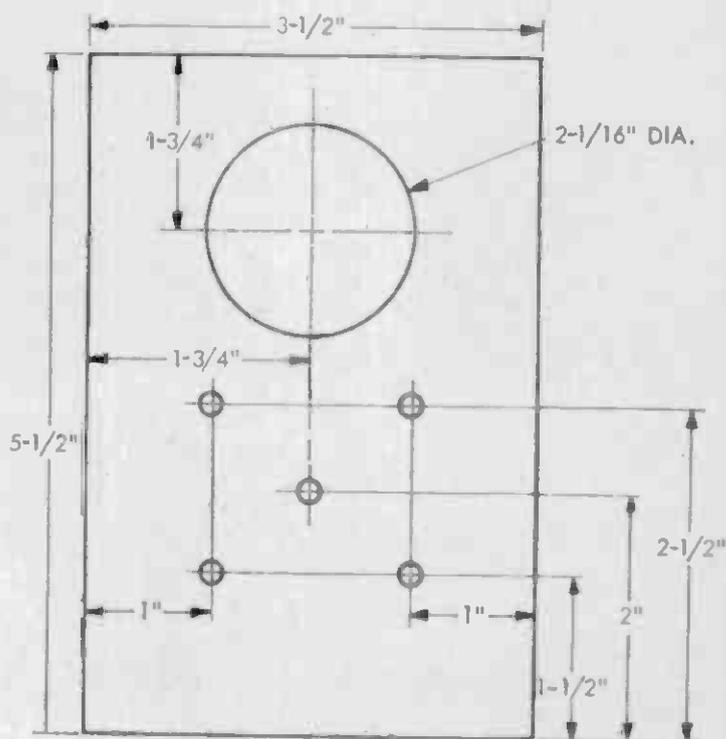The connections to the meter are not sol-



2 PANEL LAYOUT

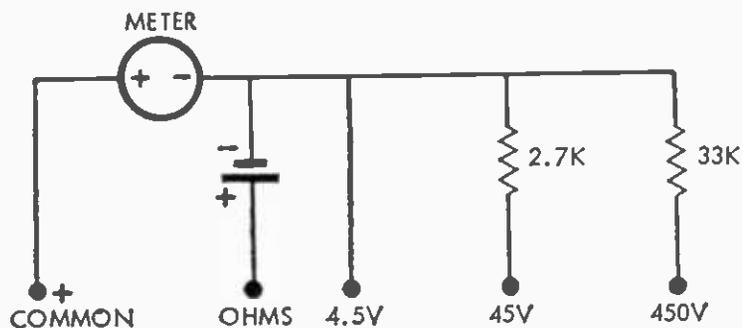

4 SCHEMATIC

MATERIALS LIST—VOLT-OHMMETER

No. Req'd	Description
1	ohms-volts meter (Shurite 8701)
1	3 cell battery holder (Lafayette MS169)
3	pen lite cells (Burgess #7 or equivalent)
1	2.7K, 1/2 W carbon resistor ($\pm 10\%$)
1	33K, 1/2 W carbon resistor ($\pm 10\%$)
	machine screws, hook up wire, rosin core solder

plus to minus. Therefore, the three 1.5 v. batteries will deliver 4.5 v. This is the full scale deflection voltage of the basic meter and the lowest voltage range of your instrument.

To use the meter, clip a lead to the common terminal and connect the other lead to the terminal which identifies the range you want to use. Mueller Mini-Gator clips work nicely for this purpose. Make a set of leads 6-in. long and another set 24-in. long. To measure volts with the meter, connect lead from common (+) to high (+) side of voltage to be measured. Connect negative lead to the highest range first, and move progressively down until you're on the proper range.

Measure ohms only when there is no electrical energy being applied to the resistance being measured. When you measure volts, do not touch terminals or uninsulated leads with your body, at risk of a bad shock.

Don't lay the meter on a metal object when you make measurements, because the back terminals are exposed. It would be a good idea to place the meter in a wood case or a small cardboard box.

And a final precaution: The volt ranges are dc voltage ranges. Don't attempt to measure ac volts with this meter.

dered. Be careful not to let your soldering iron touch the plastic meter case accidentally while you're working.

Mark the front panel with india ink. Or you may type labels and fasten them to the panel with Scotch tape.

To wind up the job, insert the batteries in the holder observing the polarities shown in Fig. 3. The batteries are connected in series—

What-Is-It?

By JOHN A. COMSTOCK

Do you think you can correctly identify the objects in the photos? Try your luck, and then check your answers with those on page 53.

1. _____


3. _____

5. _____


2. _____

4. _____


6. _____

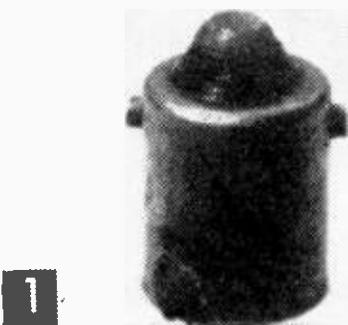


1

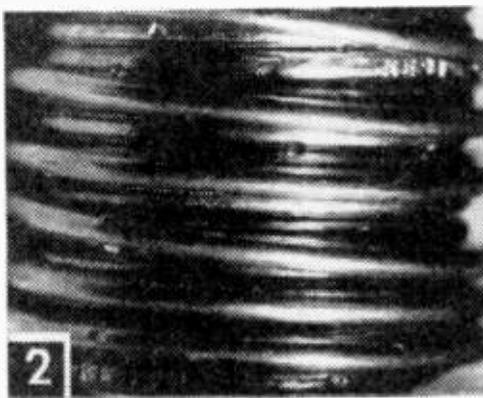


2

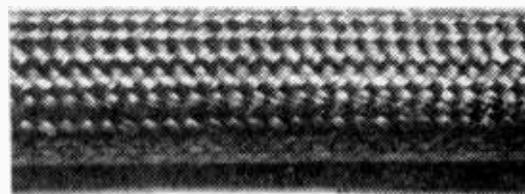


3

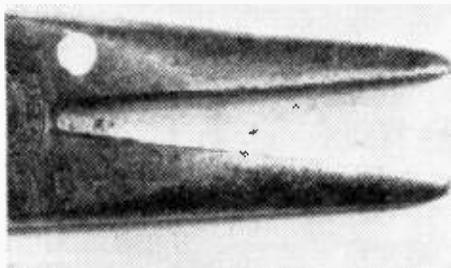

4

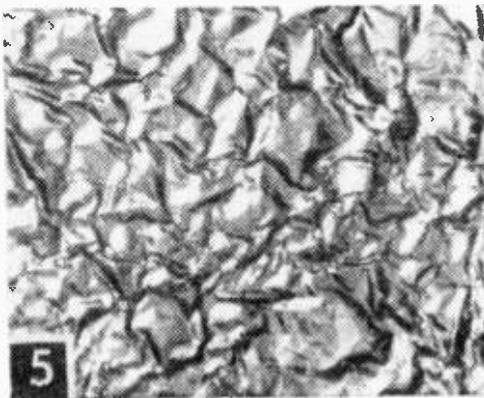


5

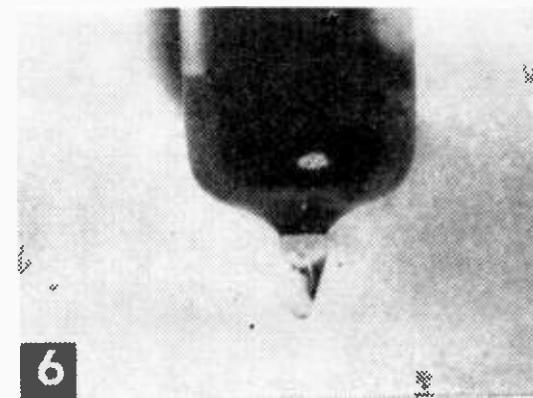

6

Hams: convert that rabbit-ears into a Field Strength Indicator

By C. F. ROCKEY, W9SCH

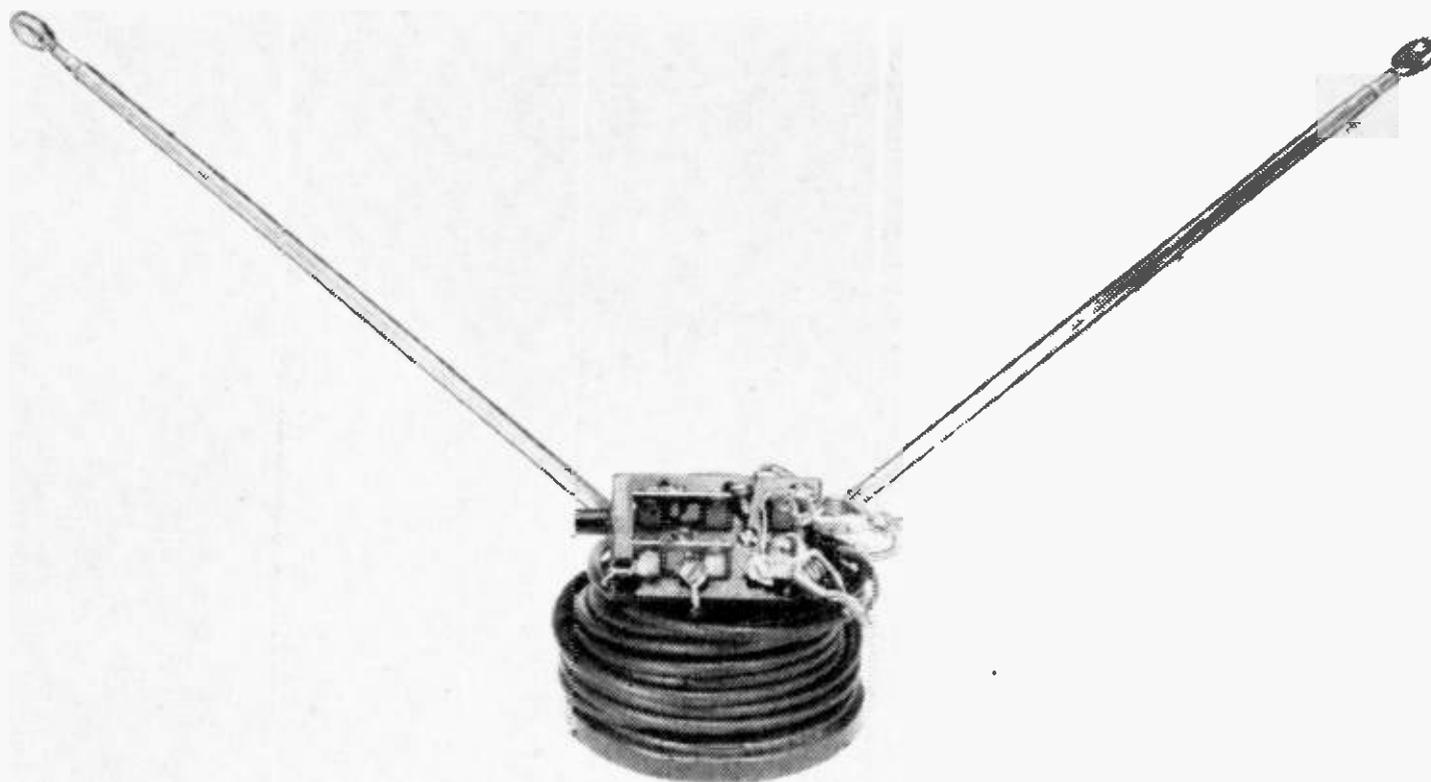

1

You can easily check the radiation of your station with this field-strength indicator.

EVERY amateur knows how convenient it is to tune a transmitter for maximum radiated output with a field strength indicator. And one cannot make significant adjustments upon a directional, "beam" antenna without one.

If you have an old rabbit-ears indoor TV antenna, you can convert it for field-intensity indications for a dollar or two. Furthermore, at the flick of a switch, you have the rabbit-ears available for its original use.

We used a *Radion* indoor TV receiving antenna for our model. Any similar antenna will work as well, as long as it is a true rabbit-ears, that is, not one of those fancy things sometimes sold with tuning stubs or other similar gimmicks attached.

First, disassemble the unit by removing the long machine screw which passes horizontally through the support. Then remove the felt from the base with a razor blade. Remove the ceramic weight within the base by running the razor blade around the weight. The two halves of the base will then come apart, freeing the two antenna rods.


One of the halves has two cast recesses in it to receive the antenna support rods. Mount the DPDT knife switch upon the "forehead" of the piece with two 6-32 x 3/4-in. machine screws, first drilling two 1/8-in. holes 3/4-in. apart (each 3/8 in. from center) and 7/8 in. down from the antenna rod slot. Then drill

three 1/4-in. holes, two near the ends of the rod slots, and one near the base (Fig. 3).


Complete wiring, leaving connections to dipole elements till last (Fig. 2). Pass the coax cable through the hole near bottom of base.

Insert the antenna element support rods into their recesses and make connections by soldering directly to these rods. Be sure to make the leads to these rods flexible enough to allow easy adjustment of the antenna rod angle after assembly.

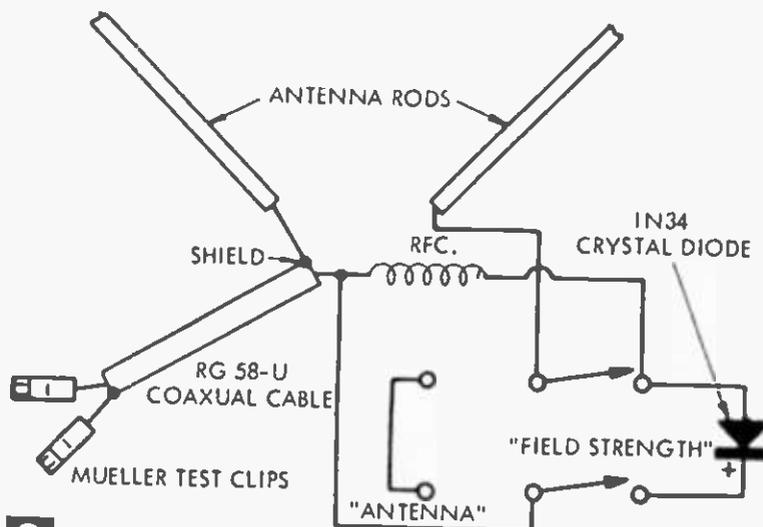
Reassemble the two base halves, insert the ceramic weight and replace screw and nut. Fasten clips on far end of coax cable.



2 SCHEMATIC

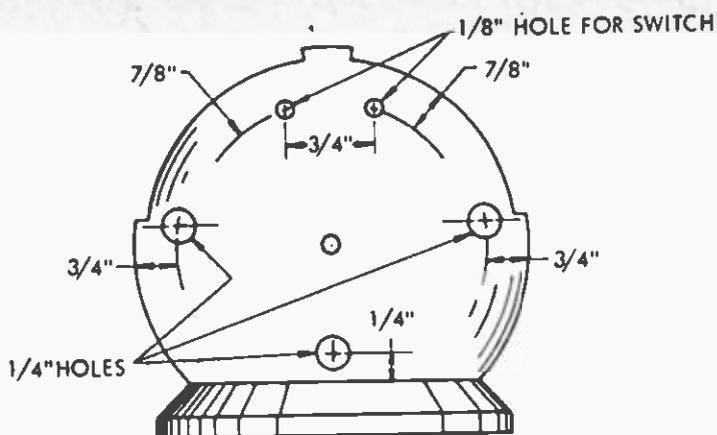

3 DRILLING DIAGRAM

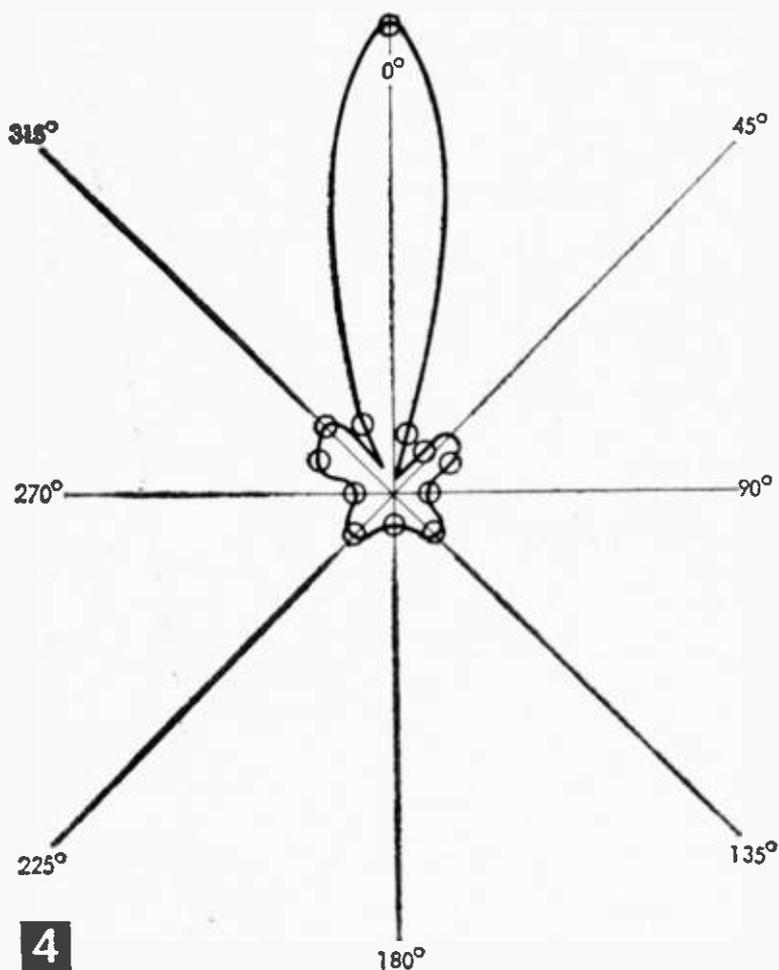

4

MATERIALS LIST—FIELD STRENGTH INDICATOR

No. Reqd.	Description
1	Radion or similar indoor rabbit-ears TV antenna
10 ft	RG 58-U or RG 58-AU coax cable
1	2.5 millihenry RF choke (National Type R-100)
1	DPDT, plastic base, knife switch
1	1N34 crystal diode
2	Mueller spring clips
	machine screws and nuts, rosin core solder, hookup wire, microammeter or VOM (see text)

Throw the switch into "antenna" position and connect to your TV set as a test. Now throw the switch into "field strength" position and connect the coax to a microammeter or low-range milliammeter. Set the unit near your transmitting antenna, and bring the coax and meter away so that you do not get into the RF field, and put the transmitter into operation. You should get a definite reading on the micro- or milliammeter. For low-frequency operation (below 50 mc) extend the antenna rods as long as possible; for 50 mc or 144 mc use, adjust the two rods to give

maximum indication, keeping both rods equal in length. If you have a vertical transmitting antenna, put one rod as nearly vertical and the other as nearly horizontal as possible. If your transmitting antenna is horizontal, put both rods as near horizontal as possible. If meter swings backward, reverse leads.

The amount of indication you will get depends upon the power output of your transmitter and the distance between the transmitting antenna and the ears. With a low power 144-mc transmitter connected to a directional antenna, the author was able to get a deflection of over 100 microamperes at a distance of over 100 ft. from the antenna. Of course, at this frequency it is necessary to elevate the ears above ground (for instance, on top of a 6-ft. stepladder) to get a representative indication.


Such technique would be proper for the adjustment of a directional beam antenna. Use a 0-200, or smaller, microammeter; set the rabbit-ears on the stepladder, placed at least 100 ft. from the antenna, and run the coax down and away so the observer's presence does not affect the field distribution appreciably. Station an observer at the meter and, with transmitter running at low power (50 watts input or less), adjust the beam antenna to produce maximum deflection on the meter. When this deflection is a maximum, you can be reasonably sure that your beam antenna is operating at or near optimum effectiveness.

If you do not have a microammeter you can use the fundamental movement of your VOM. Most VOMs have a pair of terminals or a switch position which will make this movement directly usable in this manner.

You can use this device to determine the radiation pattern of your directive antenna system by setting up as described above. Then, keeping the power input to your transmitter constant, rotate your antenna through 360° and have the observer write down the meter reading each 15 or 20° as you go around. Then, using polar-coordinate graph paper (available at draftsmen's supply stores), plot the meter reading at each angle as a distance outward from the center. Choose a reasonable scale, of course. Then connect the points with a smooth curve and you have the radiation pattern of your antenna. This will prove handy in correctly aiming it at that distant station you wish to work. A directional pattern, drawn for the author's antenna, appears as Fig. 4.

Removing Radio Knobs

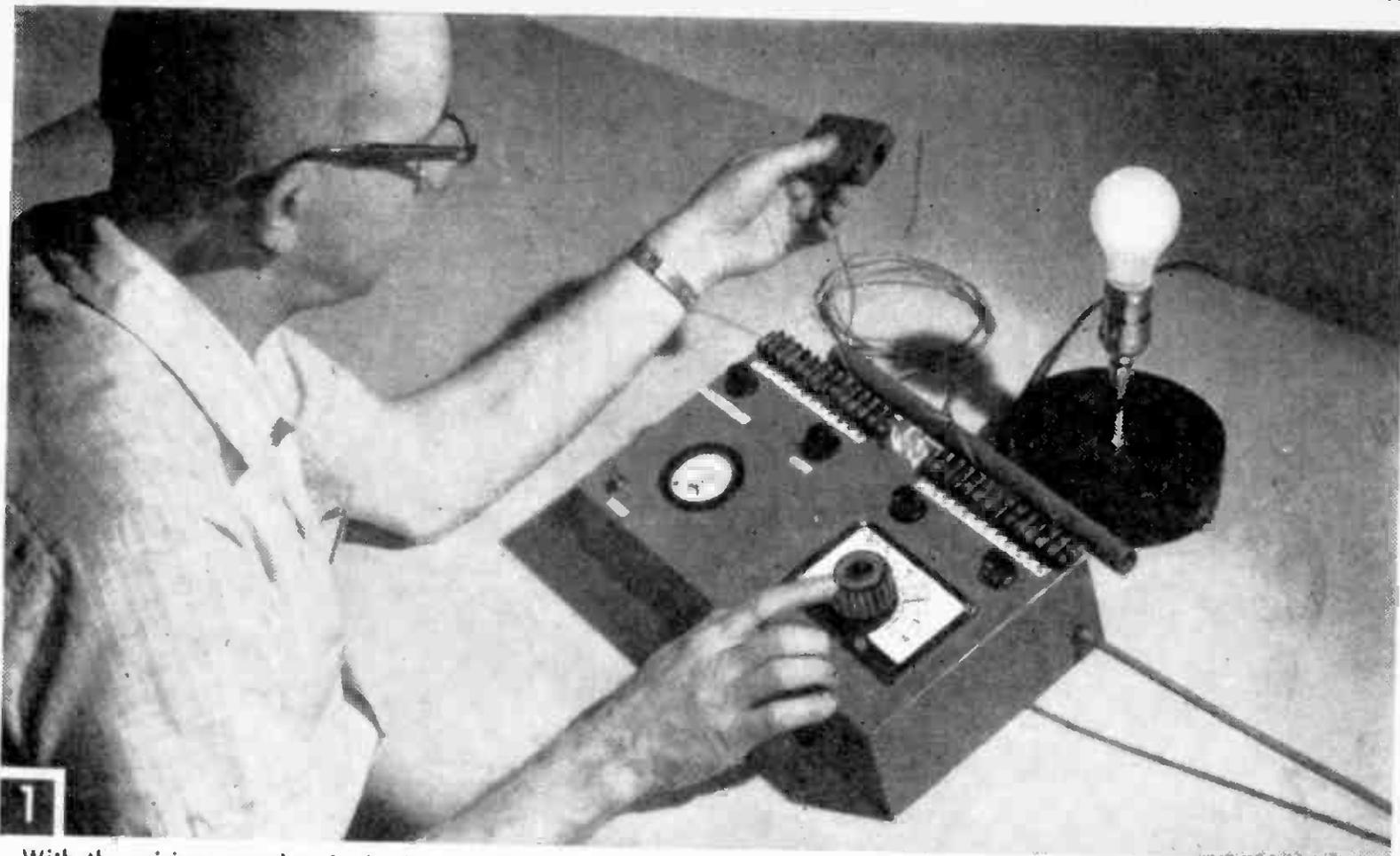- To remove obstinate radio knobs of the "pull-off" variety, hook a handkerchief back of the knob and rest your fore-finger against the cabinet as a fulcrum. Pull on remainder of handkerchief, held firmly in your hand.



With the wiring completed, check operation with a Polaris photocell. The circuitry also doubles duty as a burglar alarm and electronic counter.

All-Purpose Multi-Testing Lab

THOUGH designed by inventor Gus Wesenfeld primarily as a science lab, the Multi-Lab is also a workhorse around the home, shop, garage and photo-darkroom. For instance, after we describe construction of the Multi-Lab, we explain how to use thermistors to read temperatures from 0 to 600°F. Or with a photocell and lamp attachment, you can set up a smoke monitor on your chimney that tells you how to set the controls of your furnace for best combustion.

With Multi-Lab, you can read the condition of each cell of your car battery separately under actual load conditions. An optional relay circuit with Multi-Lab's built-in power supply and sensitivity control gives you a dependable light beam annunciator, an emergency fire alarm, or burglar alarm. The experimenter can read electrical resistance down to 1%, and use the bridge circuit to check impedance of loudspeakers, and test radio and TV tubes.

The chassis is a core unit to which you can add attachments. You use the terminal strips at the top of the panel to connect photocells, temperature detectors, strain gages, etc.







While Multi-Lab is a measuring device, unlike a scale or micrometer, it does not indicate a direct reading in units. Rather, it compares. The null meter tells you whether the electrical input is more, less, or equal to a

predetermined "standard."

Use a combination square to lay out the hole centers (Fig. 2) and then drill all the holes except those behind the terminal strips. Your only tough steps are the large holes for the meter and the vernier dial. If you are working without a drill press and hole saw, just outline the circles with a compass. Then drill starting holes and finish the job with a coping saw and file.

Temporarily mount the terminal strips with 4-40 screws and nuts. Then remove the terminal screws (those to which inside wiring feeds) and use the terminal strip's holes as a template to drill $\frac{3}{32}$ -in. pilot holes through the steel box. Remove the terminal strips and re-drill the holes to enlarge them up to $\frac{3}{16}$ in. Clean up any remaining burrs and then mount all parts and terminal strips. The National Co. type MCN vernier dial comes packed with a mounting template. Follow this pattern exactly except for drilling the top two holes $\frac{1}{16}$ in. instead of $\frac{1}{8}$ in. Then, using sheet metal screws in place of the machine screws ordinarily used, you'll be able to easily interchange the cardboard dials.

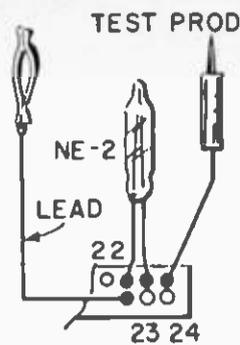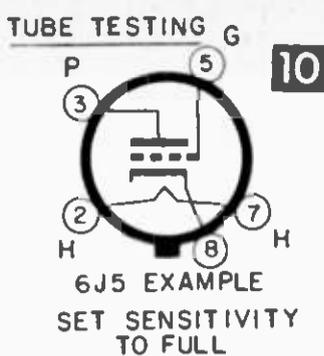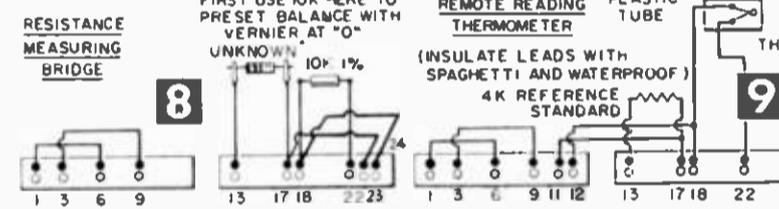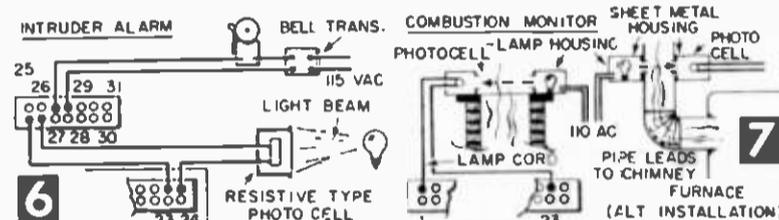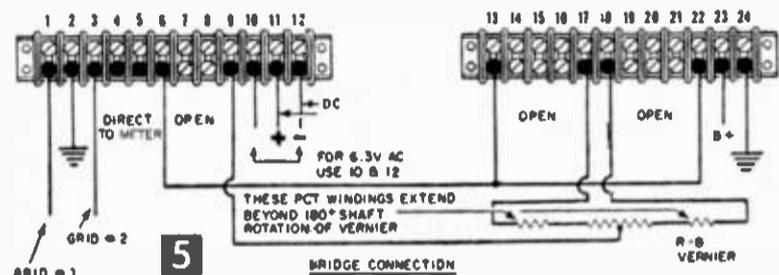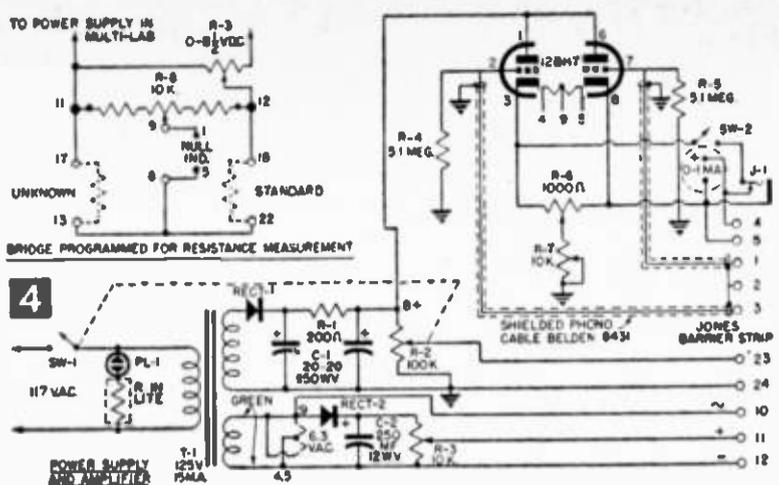Assemble the Power Supply and amplifier circuit on the perforated Vectorboard (Fig. 3B). A few of the Vectorboard holes will need enlarging with a $\frac{1}{8}$ -in. drill. Use the parts to be mounted themselves as templates.



TUBE TESTING PROCEDURE

1. Turn sensitivity to full right position. (This also turns Multi-Lab power on)
2. Clip lead to pin #2 of tube.
3. Touch test prod to pin #7. If filament is good, NE2 will glow brightly.
4. With clip lead attached to pin #2, touch test prod to pin #8. NE-2 might glow softly. If NE2 glows bright, tube has heater-cathode short.
5. Move clip lead to pin #8. Touch pin #5. If NE2 glows, tube is either shorted or gassy.
6. With clip lead on pin #8, touch pin #3. If NE2 glows, tube is either shorted or gassy.

As you wire, you'll note that the toggle switch beneath the meter is arranged to cut the meter off for safety during setting up and standby. The tube filament stays on since it is controlled by the switch mounted on the sensitivity control pot, R2. The 100K potentiometer R2 is used as a voltage divider and provides a 0-150 variable DC voltage to #23 and #24 on the external terminal strip. Pot R6 acts (zero adjust) as a balance control between the two cathodes of tube 12BH7. Pot R3 delivers 0 to 8.5 volts DC to the bridge. R8, is the "slide wire" of the Wheatstone bridge and is operated by the vernier dial.

Check Your Completed Chassis as follows:

MATERIALS LIST MULTI-LAB

No. Req'd	Size and Description
1	R1—200 ohm, 1 watt 5% resistor
1	R2—100M Mallory type U-41 Midgetrol w. #4 linear taper (Lafayette*)
1	SW1—attachable switch for R2, Mallory type US 26 (Lafayette*)
3	R3, R7, R8—10K 2 watt wirewound pot, Mallory type R10 ML, linear (Lafayette*)
2	R4, R5—5.1 meg, 1/2 watt 1% carbon precision resistors Aerovox type CPL 1/2 (Lafayette*)
1	R6—1K, 2 watt wirewound pot, linear Mallory type R1000L (Lafayette*)
1	C1—250 mfd/12 wv Sprague dry electrolytic type TVA or equal (Lafayette #Z70)
1	C2—20-20 mf, 150 wv tubular electrolytic
1	Rect 1—50 ma. Silicon rectifier, Sarkes Tarzian M-150
1	Rect 2—65 ma. 130 VAC selenium rectifier (Lafayette #RE12)
1	SW2—SPST Toggle Switch (Lafayette #SW21)
1	T1—125 Vct. 15 ma. Stancor type PS 8415 (Lafayette*)
1	PL1—Neon lamp, Drake Type 105 Postlite (Lafayette*)
1	M1—0.1 DC milliammeter, Shurite panel type (Lafayette #MT-100)
1	Vernier dial—5 to 1 drive for 1/4" shaft, with removable scales National type MCN (Lafayette*)
1	Perforated board chassis, 2 7/16 x 8 1/2", Vector type 32AA9 (Newark #38F420)
1	Term strip, 6 screw type (Newark #28F664)
1	Term strip, 3 screw type (Newark #28F661)
2	Term strips, 12 double terminals ea. Jones Barrier type 12-140 (Newark #28F710)
1	7 x 12 x 3" Black wrinkle steel chassis, Bud No. CB 792 (Lafayette*)
1	Bottom cover plate, steel, for above Bud No. BP-539 (Lafayette*)

(Note: Order aluminum chassis, same size as above if working without electric drill, etc.)

No. Req'd	Size and Description
1	9 pin miniature tube socket
1	V1—12BH7 tube
4	Knobs, black plastic, 1/4" (Lafayette KN-37)
Misc.	AC power cord, hardware, scrap aluminum bracket, bus bar, or hookup wire, alligator clips, test prod wire, 1/2 x 11" elec. conduit handle, shielded cable for grid leads.

AUXILIARY METER

1	R9—120 ohm/ 1 W 10% Carbon (Lafayette* RS11*)
1	SW3—Push button, N.C. Grayhill type 4002 (Lafayette*)
1	SW4—Toggle switch, SPST (Lafayette #SW21)
1	S01—Socket, Cinch Jones type P-302-AB (Newark #39F220)
1	S02—Plug, Cinch Jones type S-302-CCT (Newark #39F200)
1	P1—Phone plug (Newark #39F792)
1	Meter case, Bud type CM-1935 with center hole knockout (Newark #91F598)
1	M2—0-S0 D.C. Microammeter (Lafayette #TM70)

STANDARDS AND ATTACHMENTS

1	Photocell, Polaris "Maji" cadmium sulphide resistor type (Allied #78E711)
1	TH1 2000 ohm Probe style Thermistor Fenwal #GB32P2 (Allied #9E927)
1 ea.	1K, 2K, 4K, 8K, 100K 1% precision resistors IRC type DCC or equiv. (Allied #1MM493)
2 ea.	10K 1% precision resistors, as above.

SOURCES*

(Lafayette*) Order using Mfrs. numbers listed. Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y. (Newark) Use Newark nos. Newark Electronics Corp., 223 W. Madison, Chicago 6, Ill. (Allied) Allied Radio, 100 N. Western Ave., Chicago 80, Ill.

close switch SW2 to put the meter switch in the circuit, and then turn on the power. As the amplifier warms up, turn calibration control R7 clockwise up to full, and slowly rock the zero adjust control back and forth. You should get a meter deflection. If not, turn switch SW2 on and off to make sure the meter circuit is operative. Then turn R7 to the other extreme. If there still is no reading on the meter, turn power off and recheck your wiring.

All controls, with the exception of vernier R8 are "polarized." This means that you turn a knob to the right, the attached control either causes an increase in voltage or current, or the meter increases its reading.

Now take part R8 and fasten it tightly to the sheet metal bracket with the mounting nuts (Fig. 3D). Set your vernier dial exactly to #50 on the dial, and then center the pot's slider electrically. You can do it with a VOM set to a 10K range. Read the resistance from center tap to one side, and then to the other side. If necessary, turn the shaft slightly to equalize the resistance legs, and then bolt the bracket into the case, and tighten the shaft setscrews.

Testing Multi-Lab with Photocell. With wiring and construction completed, you're ready to test operating controls. Connect a resistive type photocell (not the sun battery type) such as the *Polaris* cell in the Materials List, across terminals 1 and 23 as in Fig. 6. Arrange a light as in Fig. 1. Turn the sensitivity control R2 to its minimum setting, and then cut the meter into the circuit with switch SW2. If the needle swings off scale, turn the zero adjust until the needle centers. Now slowly turn R2 until it's about three-quarters up, continuing to center the meter needle with the zero adjust.

Now block the light from the photocell. The meter should swing down scale. If it swings up scale, switch the lead from terminal 1 to terminal 3. Remember, whenever you are making changes or adjustments, switch your meter to prevent a burn out.

This photocell setup not only demonstrates the basic Multi-Lab adjustments, but you can easily use it as a temporary burglar alarm or light-beam annunciator as in Fig. 6. A bell or light will serve as a signaling device, and sensitive relay RLY 1 instead of your meter does the work.

The Smoke Monitor (Fig. 7) is a timesaver when you want to adjust your draft or stoker controls to save fuel, prevent smog, etc. All you need is a lamp housing made of scrap metal, and a holder for the photocell. When the best furnace adjustment is obtained, disconnect the cell from your stack and insert a metal cover in its place.

Now The Bridge Unit. Set it up with two 10K resistors as in Fig. 8. With the vernier dial on 0, R7 full up and R2 three-quarters

up, switch in the meter and center the needle with the zero adjust. These steps are basic to the operation of Multi-Lab. Practice until you can do them fast. *From here on, remember that you'll be working only with the vernier. Don't touch the calibration control or the sensitivity control.*

Then turn off the meter switch, and replace the 10K resistor across terminals 13 and 17 with a smaller resistor, say 560 ohms. Switch the meter back on briefly. Now readjust the vernier until the meter is again exactly centered. Your reading on the vernier now represents the value of the unknown resistor. If you get no meter response as you adjust the vernier, check the bridge and setup to find your mistake.

The Resistance Measuring Method detailed under Fig. 8 is typical of most operations that you will want to do later on with Multi-Lab. Following the instructions, program the bridge, connect in your standard resistors, center the meter, and mark the dial. Repeat the procedure to get a series of calibration points on the dial. By connecting your resistor standards in series-parallel combinations you can obtain more intermediate points. This bridge performs best in the 200 ohm 2M range; however, any calibration range will cover only a 1 to 10 resistance ratio. Remember not to upset any of the controls while calibrating or measuring—work only with the vernier.

The 0-1 ma. meter on the Multi-Lab panel is sensitive enough for most preliminary experiments. For example, it gives you about 4% accuracy with the bridge. The auxiliary meter (Fig. 3F) is a 0-50 microamp meter that can increase your accuracy within 1/2 of 1%. Of course, your readings are always only as accurate as your standards. You can use any precise microammeter with the Multi-Lab. But until you are completely familiar with operation, it's best to protect expensive instruments by starting the experiment with the panel meter.

With a Thermistor, (Fig. 9) you can read outdoor temperatures from 20 below up to 100°F. Calibrate your dial by immersing the thermistor—it must be waterproofed with varnish—in ice water. Set the vernier at 32 and balance the bridge with the zero adjust. Then place the thermistor outdoors next to an accurate thermometer. A range of readings will establish the scale on your dial. You can also use thermistors to read oven temperatures up to 700°F, provided that you use asbestos wire leads.

The Tube Checking Circuit, (Fig. 10), takes advantage of Multi-Lab's built-in power supply to give you a high voltage-through-resistance check for filament continuity, interelement shorts and gas. Manufacturer's tube manuals will give you pin connections for all tube types.

What To Listen For On Short Wave

Spring and Summer 1961

By C. M. STANBURY II

July 12, 1960. The Belgian Congo has just gained its independence, the army mutinies and attacks the formerly elite European. In the States, an SWL tunes to 9835 kc for Leopoldville. Instead he hears a jammer and a quick check of reference lists reveals that it could only be intended for the Congo transmitter. Obvious question, who and why?

It could have come from the secessionist Katanga province but this was a real jammer and the rebel Elizabethville government did not have time to set up such equipment. Which left the Russians and a tipoff that Mr. K was going to jump into the mess with both feet. And this SWL's guess was right. First premier Lumumba requested American troops, the Soviets opened fire propagandawise, and Washington discreetly turned down the request. Then the Congo government switched to the Soviet side of the fence and what do you think happened? That's right, the jamming disappeared.

The above illustrates the most effective method of SWLing. With the help of a good reference log such as *White's*, tune to the world's hot spots and interpret what you hear via comparison and logic rather than be hand-fed propaganda.

Of course, not every international broadcast is pure propaganda, in fact most propaganda is mixed with truth, and a few stations come close to painting an unbiased picture. Such a station is Radio Brazzaville, operated by the French government in the Congo Republic (formerly French Equatorial Africa). The Congo Republic which should not be confused with the Republic of the Congo, is an independent state but within the French community. Possibly this dual control is responsible for its almost objective approach to the news. During the Congo emergency, this station just across the river from Leopoldville appeared to provide complete, often first hand information.

This policy contrasts sharply with the propaganda blasts coming from Brussels on 11855 kc and other frequencies. While the Belgian attitude may have its merits, propaganda is propaganda and of little use to the SWL.

Radio Brazzaville illustrates another important point. Its signal on 11970 kc consistently topped those of Radio Moscow, which used the same channel. Both transmitters were beamed to North America, so what's the difference? Answer, the Auroral Zone. Signal from Russia must pass near the North



QSL card from Radio Brazzaville. In French and Belgian both Congo Republic and Republic of the Congo are written République du Congo.

pole and Northern lights (Aurora Borealis) before reaching us. Tropical stations do not. The Aurora Borealis increases absorption, weakening signals, even under normal reception conditions. During ionospheric disturbances (magnetic storms) the signal drop becomes severe. Thus Brazzaville's advantage over Moscow.

But is this polar block always advantageous? No, it is frequently a major short


TABLE A WHEN TO LISTEN WHERE

KC/S AND METER BAND	TIME				
	MIDNIGHT	SUNRISE	NOON	SUNSET	MIDNIGHT
5950 - 6200 (49)	█	█		█	█
7100 - 7300 (41)	█	█		█	█
9500 - 9775 (31)	█	█		█	█
11700 - 11975 (25)	█	█		█	█
15100 - 15450 (19)		█	█	█	
17700 - 17900		█	█	█	

wave problem. Since 1958 the number of tropical transmitters on 25 and 31 meters has at least doubled, making pleasant listening from Europe increasingly difficult with many broadcasts to North America blocked or seriously impaired. To mention just a few, Radio Ankara and Radio Denmark.

What does seriously impaired mean? Well, that's up to you as a listener—how much interference will you tolerate? Apparently the average SWL won't stand for much because even with an advantageous location, Radio Brazzaville still found it necessary to switch back to 11725 kc, clear of Moscow. To sum this technical dilemma up, either there will have to be better use of channels in these key night-time bands, or SWLs will have to become better DXers.

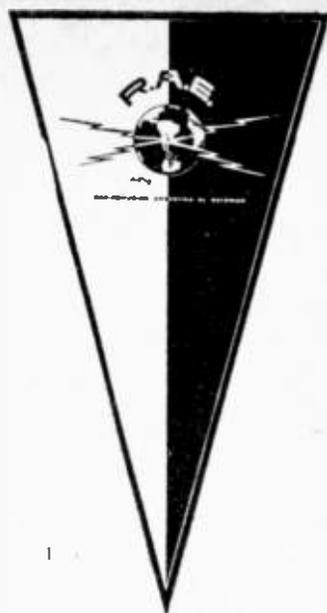But let's look and see what, band by band, the listener can expect this spring and summer. First, 16 and 19 meters will be open to Europe and Africa during daylight hours on the east coast, and to Asia in the morning and early evening. Out west these bands will be open to all continents around 9 am PST, to Asia and the Pacific from late afternoon until



Pennant from RAE
(Argentina).

past midnight. In every part of the U.S. there will be a scattering of Latin American signals anytime these bands are open except after 1 am EST when such stations have gone to bed.

Twenty-five and 31 meters are primarily night-time bands, open to every part of the world and subject to that tremendous interference we mentioned. Europe and Africa will be clearest late afternoons and early evenings with Asia and the Pacific gradually taking over after midnight.

Forty-one meters, not used for broadcasting in the Americas, will provide limited European reception evenings, equally limited Oriental DX toward dawn. Forty-nine meters will provide good Latin American reception during the hours of darkness until such stations sign off.


As you've undoubtedly gathered from this rundown, there is no single peak period for transmission to North America from either Eurafica or the Orient. Usually two broadcasts are required, one for our east coast, a second for the Pacific and Rocky Mountain areas. Here, the Westerner has an advantage. Most Europeans have dual broadcasts, Asians only one, and shortly after 9 pm PST, a much better time for the West than the East. A major exception is Radio Japan (see Table A) and even this powerful station's signals are often weak in the Eastern U.S. There is not too much the Asiatic broadcaster can do about this because ideal conditions over such a path only prevail between 3 and 6 am EST and the SWL can't do much listening while asleep.

TABLE B—STATIONS TO START WITH

COUNTRY	FREQUENCY IN KC/S	TIME (EST)*	PROGRAM
CONGO REPUBLIC	11725	2015-2100	African news (see text), World news from a French viewpoint, French language lessons and once a week, Congolese music.
UNITED ARAB REPUBLIC	15475	Daylight hours until 1830	This listing is an experiment. No English is transmitted here, and if there were any, it would be propaganda. But you will hear a fine selection of Near East music, probably reflecting the mood of this area quite accurately.
MOZAMBIQUE	11760	2230 until fadeout	This is a semi-local broadcaster on an international frequency. Take a listen and see what the Dutch, English-speaking inhabitants of Southern Africa consider entertainment.
SWITZERLAND	11865, 9535	2030-2215, 2315-2400	News (governmental) and newspaper editorials from the world's one neutralist nation.
GREAT BRITAIN	Many frequencies	1600-2200	This is the best of conservative Western thought and programming.
NETHERLANDS	15220 11855, 9715	1615-1705 2130-2210	International news and topical talks, from a leading West European Nation.
WINDWARD ISLANDS	15395 11715	1600-1745 1800-2115	A chance to observe programming in the West Indies which blend Caribbean, British and American.
ARGENTINA	9690	2200-2300, 0000-0100	South American news from at least a different viewpoint. Also covers Argentine literature.
JAPAN	11800, 15235, 17825	1930-2015	News and commentary from Asia's number one democracy. Limited amount of Japanese music.
AUSTRALIA	11710 11810	0714-0845 1014-1145	This is the only station in the Pacific actually beamed to North America. Best here is news. Remainder of program is primarily entertainment.

* Time is given on the 24-hour clock. 1200 is 12 noon, 1300 is 1 pm, 2400 is midnight, and so on. In other words, for times past noon subtract 1200 to get Eastern Standard Time.

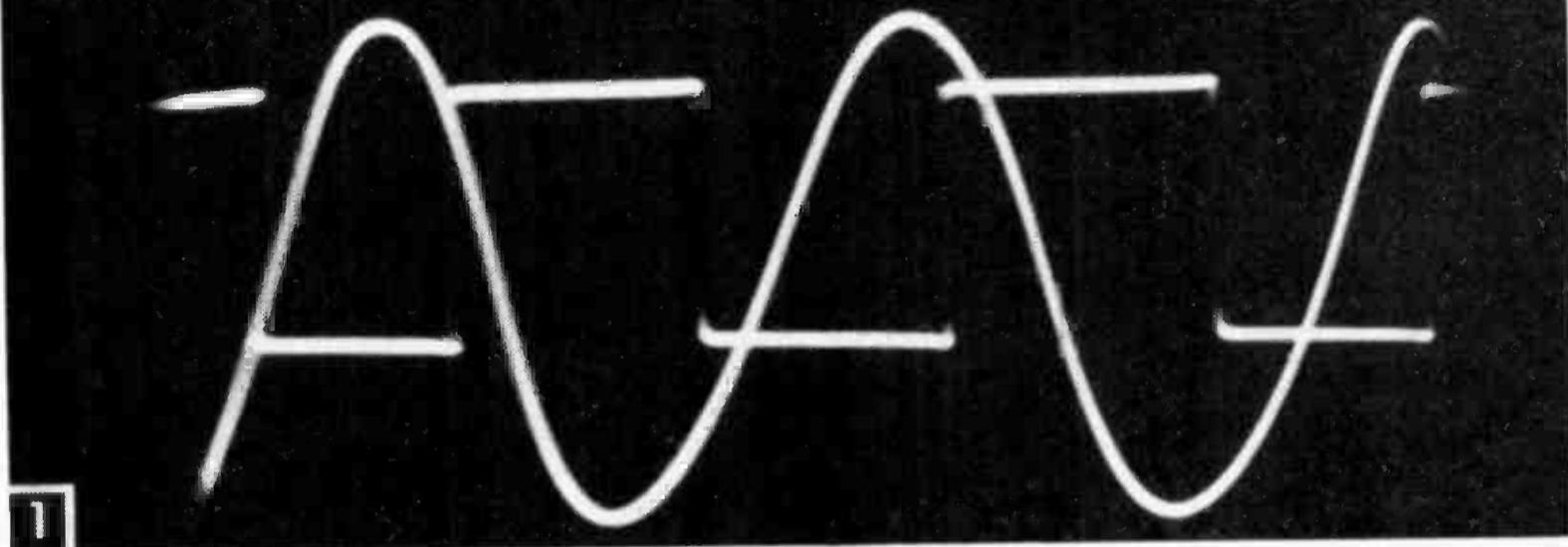Combined Voltage Calibrator And Electronic Switch



Sine and square wave seen simultaneously with aid of electronic switch unit.

Single unit multiplies oscilloscope usage

By W. F. GEPHART


THE unit shown in Fig. 2 combines two useful 'scope accessories: 1) an electronic switch which permits viewing of two signal patterns simultaneously (Fig. 1), and 2) a voltage calibrator, allowing the 'scope to be used for ac voltage measurements. The first accessory, the switch, permits both the input and output of an amplifier to be viewed together to check fidelity, for example. The second accessory, the voltage calibrator, gives the magnitude of a signal as the wave form is viewed.

Our unit has a special switching system that permits the calibrated voltage signal to be one of the signals seen simultaneously.


An electronic switch switches signals so fast that both images appear on the oscilloscope together, due to the persistence of the cathode ray tube. A multivibrator type oscillator switches amplifier tubes "on" and "off" so they conduct alternately. Separate signals are fed into each amplifier tube, whose output is common. This output is actually both signals, presented alternately.

Figure 3 shows the schematic, in which V1 is a twin triode multivibrator. It generates square waves, with frequencies between about 20 and 2000 cycles, as set by SW1 and R15, the frequency controls. The multivibrator drives the grids of a second twin triode (V2), which acts as a switching tube. The two plates of the multivibrator are connected to the two grids of the switching tube. Since the signals on the plates of V1 are 180° out of phase, the two halves of V2 conduct alternately. The output of the multivibrator is a square wave and quite high. Thus, when the


plate of V1a is positive, the grid of V2a is positive and V2a conducts. At the same time, the plate of V1b and grid of V2b are negative,

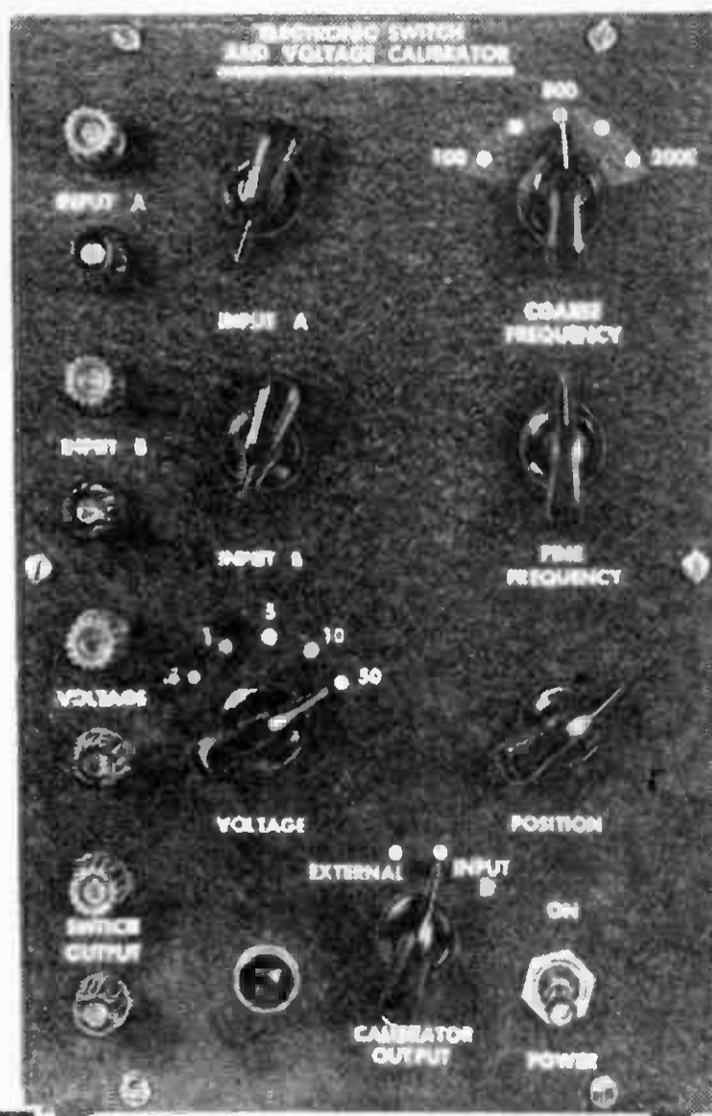

Front view of the completed unit.

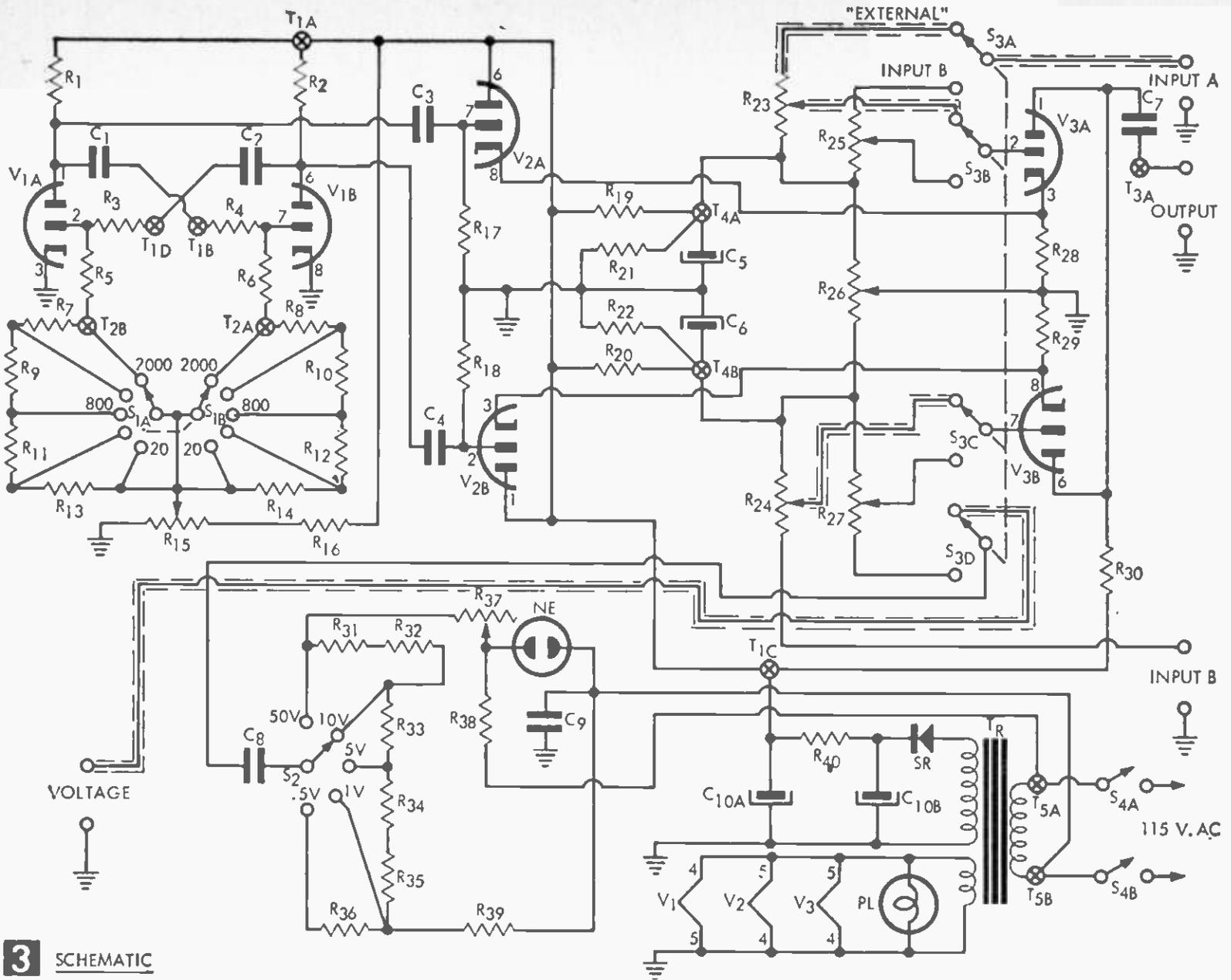


3 SCHEMATIC

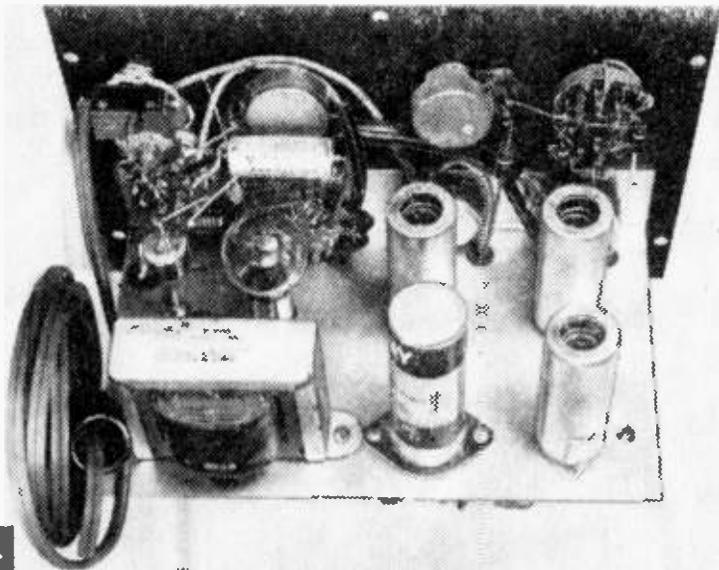

4 Back-of-panel view shows miniature pots mounted by stiff wire leads.


which prevents V2b from conducting. At the half-cycle point, the situation instantly reverses (since the multivibrator is a square wave generator), and V2b conducts and V2a cuts off.

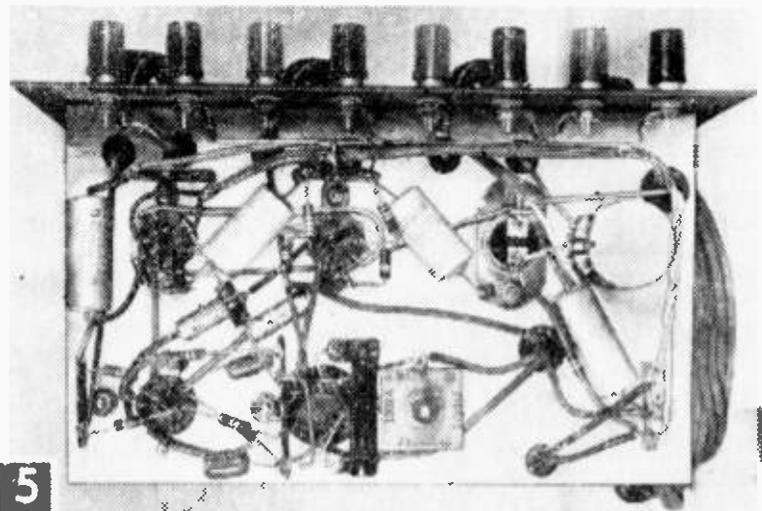As the two halves of V2 alternately conduct, the current they draw flows through the cathode resistors (R28 and R29) of V3a and V3b. The twin triode amplifier (V3) is two ordinary amplifiers, biased at a normal op-




5 Under-chassis view shows shielded lead attached to common negative lead of binding posts.

erating point by cathode bias. If the cathodes of the switching tube were not connected to their cathodes, both halves of V3 would amplify equally. However, as the two halves of V2 draw current, this current flowing through the related cathode resistor of V3a or V3b biases that half of the amplifier tube (V3) to cut-off. In this way, the two halves of the amplifier tube (V3a and V3b) are alternately switched on and off at a rate equal to the multivibrator frequency. Therefore, the two input signals take turns appearing at the out-

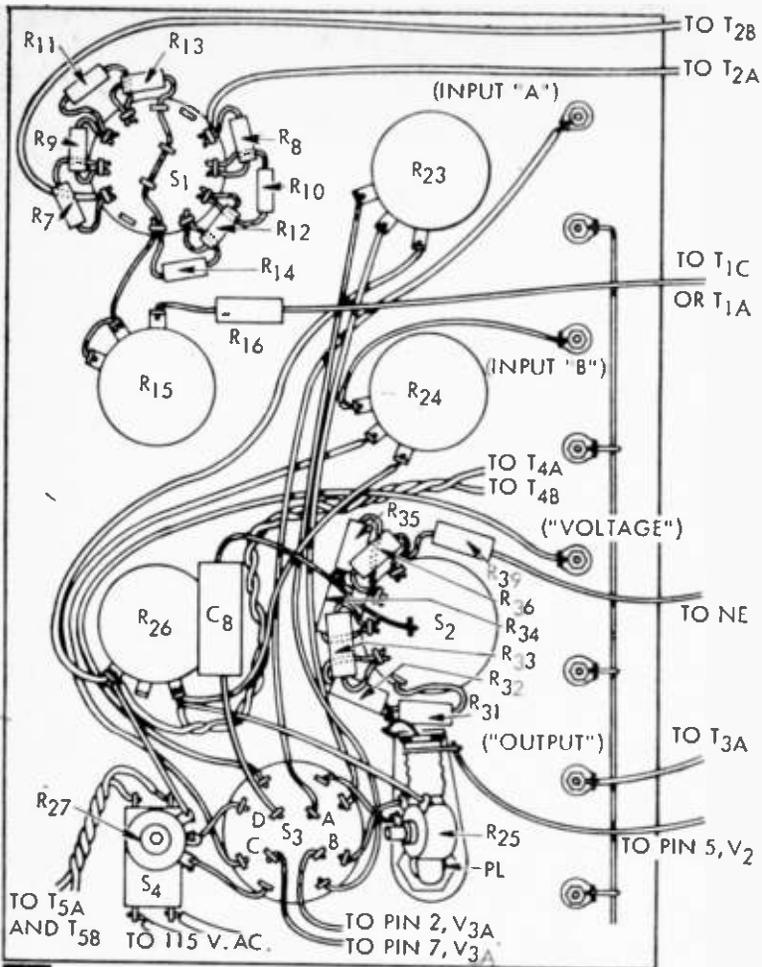

8 PANEL WIRING

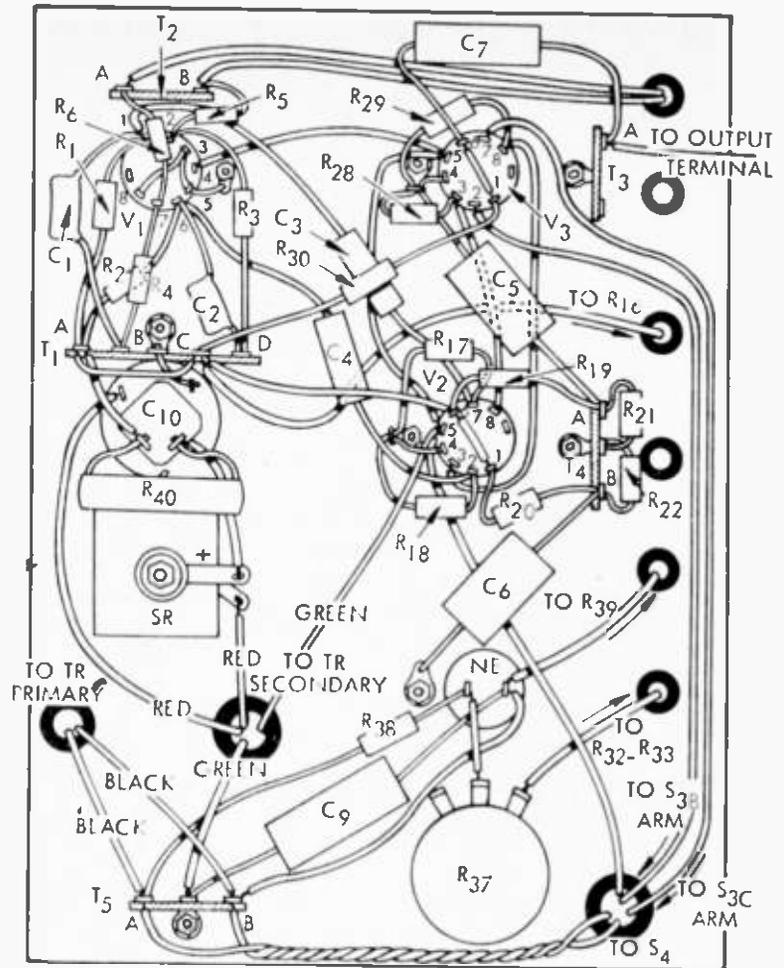

9 CHASSIS WIRING

by stiff (#16) wire leads.

The power supply and filaments are wired first, followed by the neon bulb circuit. In mounting resistors on the voltage switch (S2), be sure they will clear the neon bulb. No particular care is required in wiring, except that certain leads (as shown on the schematic) should be shielded, and care used that the grounded shield does not short out any terminals.

After wiring, output of the calibrator must be set. Connect a vacuum tube voltmeter be-

tween R37 and ground, and set the voltage switch S2 on 50. Calibration should be for peak-to-peak voltages, so the reading on the VTVM should be .3535 of the values shown on S2. Turn the unit on, and adjust R37 so the voltmeter reads 17.7 v., which is .3535 of the 50 v. indicated on S2. Due to the divider, other readings will be appropriate.

Next, potentiometer R27 should be set. With Calibrator Output S3 on External, set Voltage S2 on 5, and connect the Voltage terminals to the vertical input of the 'scope.

MATERIALS LIST—SCOPE CALIBRATOR AND SWITCH

(All resistors 1/2 watt and 10% unless shown)

Desig.	Description	Desig.	Description
R1, R2	51K, 5%	C1, C2	.001 mfd., 200 v.
R3, R4	12K	C3, C4	.047 mfd., 200 v.
R5, R6	.22 meg.	C5, C6	25 mfd., 25 v. electrolytic
R7, R8	1 meg.	C7, C8, C9	.5 mfd., 200 v.
R9, R10	3.3 meg.	C10	40-40 mfd., 150 v. electrolytic (Mallory FP-221 or equiv.)
R11, R12	4.3 meg., 5%	S1	2-pole, 5-pos. rotary switch (Coarse Freq.) Mallory 3226J
R13, R14	5.1 meg., 5%	S2	1-pole, 5-pos. rotary switch (Voltage) Mallory 3215J
R15	.1 meg. potentiometer (Fine Frequency)	S3	4-pole, 2-pos. rotary switch (Calibrator Output) Mallory 3242J
R16	.15 meg.	S4	DPST toggle switch (Power)
R17, R18	.1 meg.	PL	6.3 v., .15 amp. pilot light (#40 or #47)
R19, R20	.33 meg.	SR	65 ma. selenium rectifier
R21, R22	15K	T	power transformer, 120 v. @ 50 ma., 6.3 v. @ 1 amp. (Merit P-3045)
R23, R24	.1 meg. potentiometer (Input A and Input B)	NE	NE 32 neon bulb
R25, R27	1 meg. miniature potentiometer (Clarostat Series 48)	V1, V2, V3	6CG7 vacuum tubes
R26	50K potentiometer (Position)		5 x 6 x 9' utility cabinet (Bud CU-1099)
R28, R29	1000 ohm		three 9-pin miniature sockets
R30	33K, 1 watt		neon bulb socket
R31	68K, 1%		pilot light holder
R32	12K, 1%		8 binding posts
R33	10K, 1%		7 knobs
R34, R35	4K, 1%		miscellaneous hardware
R36, R39	1K, 1%		
R37	50K potentiometer		
R38	10K		
R40	250 ohm, 10 watt, wirewound		

Turn both units on, and adjust the vertical gain control on the 'scope to give a pattern of convenient height, and note the height of the image on the CRT. Do not touch the vertical gain control on the 'scope after this.

Move the leads from the 'scope to the Output terminals, set Frequency controls S1 and R15 to mid-position, and adjust Position R26 so a single trace appears on the CRT. Switch Calibrator Output to Input-B and adjust R27 so that the trace height on the CRT is the same as the voltage trace height found above. Seal R27 shaft with nail polish.

To set R25, feed a low gain signal from an AF oscillator or other unit into the vertical input of the 'scope, adjust the vertical gain for a convenient height, and note the trace height. Then connect the 'scope to the Output Terminals instead of the signal source and adjust the Position control to get a single trace on the CRT.

Remove the neon bulb and set S3 to Input-B. Connect the AF oscillator to Input-A terminals, and adjust R25 to give the same trace height as given when the signal was connected directly to the 'scope. Seal R25 shaft with nail polish and replace the neon bulb.


It will be found that adjustment of the position control will affect signal magnitudes somewhat, so the voltage calibrator section

should be used through the electronic switch section only when approximate results are sufficient. When using the unit in this manner, the Position control should be set so the signal pattern is superimposed over the voltage calibrator pattern, and ready comparison can be made. Also, most accurate results can be obtained when the two signals are superimposed. For more precise work, the electronic switch section is not used. Output from the Voltage terminals is connected to the 'scope, the vertical gain set, and trace height noted. The leads from the Voltage terminals are removed, and the signal is then connected directly to the 'scope. A comparison of the trace height produced by the signal, with the noted height of the voltage calibrator trace will then give a precise peak-to-peak voltage measurement.

In using the electronic switch, the two signals to be viewed are connected to Input A and Input B, and the Output is connected to the vertical input of the 'scope. The frequency controls of both the 'scope and the electronic switch are adjusted for proper frequency, and the gain controls on the switch adjust the individual trace heights. By use of the Position control on the switch, the two patterns can be shown separately or superimposed (as in Fig. 1).

Improved Razor-Blade Detector


• Here is a more rugged version of the familiar fox-hole razor-blade "crystal" detector. The original was a piece of pencil lead bridged across the edges of two razor-blades and sometimes used by G.I.'s in fox-holes to pick up local broadcasting stations. This was fairly sensitive, but it was very difficult to hold an adjustment, as the least vibration or jar caused the lead to rock and roll on the blade edges, resulting in erratic and noisy reception. For the arrangement shown, blue steel single edge or double edge blades (such as *Pal* razors) seem to be the most sensitive, but many other blades also have sensitive spots on them. Use with a conventional circuit and a good antenna and ground.—ARTHUR TRAUFFER.

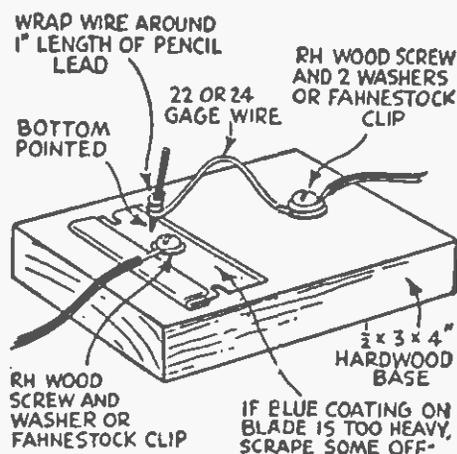

Pointed-End for Radio Ground Pipe

• A simple pointed end makes it easier to drive a radio ground pipe. Insert the lathe-turned point into the bottom end of the pipe to keep dirt from plugging the pipe. Holes drilled through the pipe for soil wetting reduce electrical resistance between ground pipe and soil.—ARTHUR TRAUFFER.

Solderless Tube Sockets

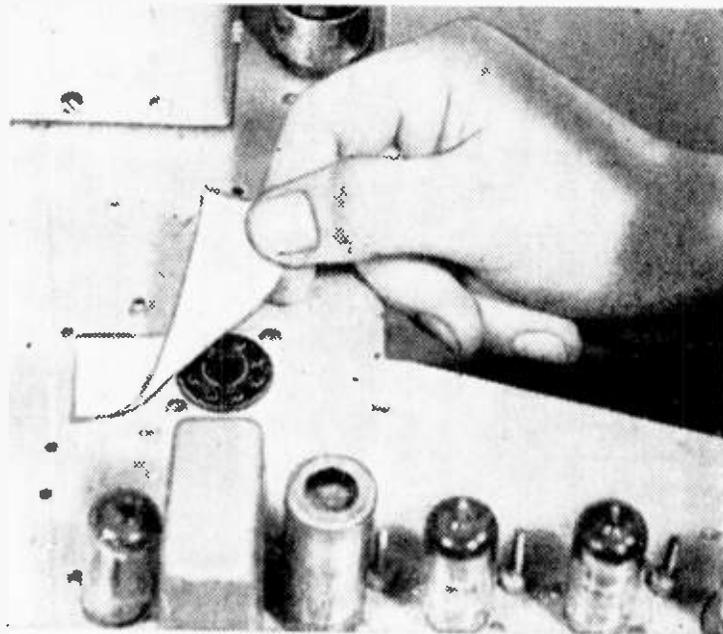


• When soldering on top side of radio or TV chassis, dropping solder in an open tube socket can cause trouble. Eliminate this possibility by placing a strip of wide adhesive tape over the open socket.—H. LEPPER.

Removing Enamel Wire Insulation

• To remove enamel insulation on magnet and hook-up wire quickly and cleanly, wrap a piece of sandpaper around the wire and give a twisting, rotary motion.—E. L. BURNER.

Transistor Radio "B" Eliminator and Battery Charger

By GEORGE D. PHILPOTT

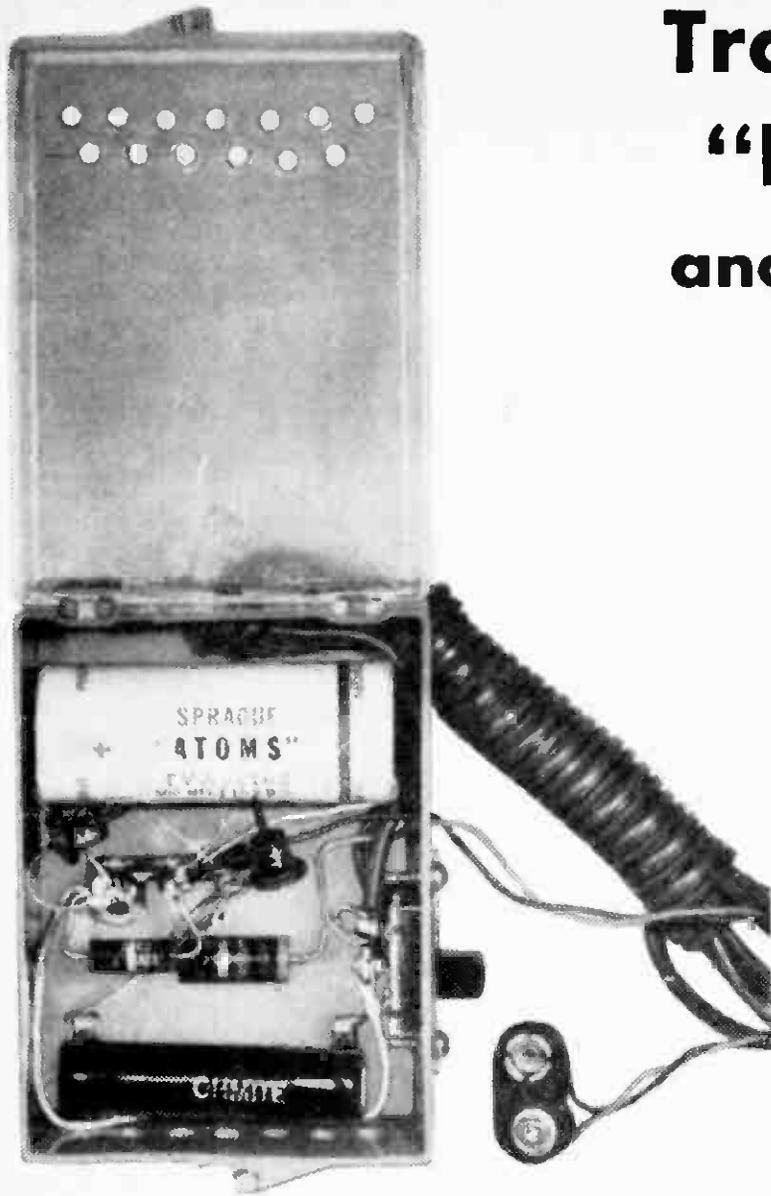

House-current is converted by this unit to power transistor radios. If battery is left in radio, unit will charge it while powering the radio.

ONE hour of your spare time, a few inexpensive components, and you will have not only a reliable transistor power supply capable of operating a 6-8 transistor receiver from house-current, but a means of recharging batteries for extra hours service. The set may be off while recharging.

There is no chance of damage to the radio from too much voltage because of these design features: low current rectifiers, a low operating voltage filter capacitor, and a resistor voltage dividing network at the input to the rectifiers.

Necessarily this means a 20-watt resistor must be used (R1, 3500 ohms) in the top leg


of the divider. During operation this resistor gets warm and should be mounted slightly apart from other components in the plastic case (as from the case itself) and several small holes for ventilation should be drilled in the case near this component.

Resistor R2, electrically connected as the bottom half of the input voltage divider, operates coolly. Current flows here only on the half-cycle when rectifier D2 is not conducting. By changing the value of this resistor a few hundred ohms the voltage output of the power supply can be varied sufficiently to meet most 9-v. receiver current-voltage demands.


The rectifiers must be capable of supplying at least a 5-ma continuous load. International 1V1 diodes are satisfactory, but larger capacity units such as the GE 1N91, or Sylvania SR 200 silicons will give better voltage regulation under most class A loads.

The 500 mmfd electrolytic provides filtering action at the output, limiting ac ripple to approximately 0.1%, more than adequate for transistor usage. Its low (15 V.) operating voltage is a form of insurance to prevent damage to the radio in case of resistor or rectifier failure in the voltage divider network. The battery is a definite load across the output line until the power supply output is equal to, or slightly above, battery voltage (the latter condition that of recharging the battery) thus keeping the load current to an approximate constant value, preventing possible damaging surges.

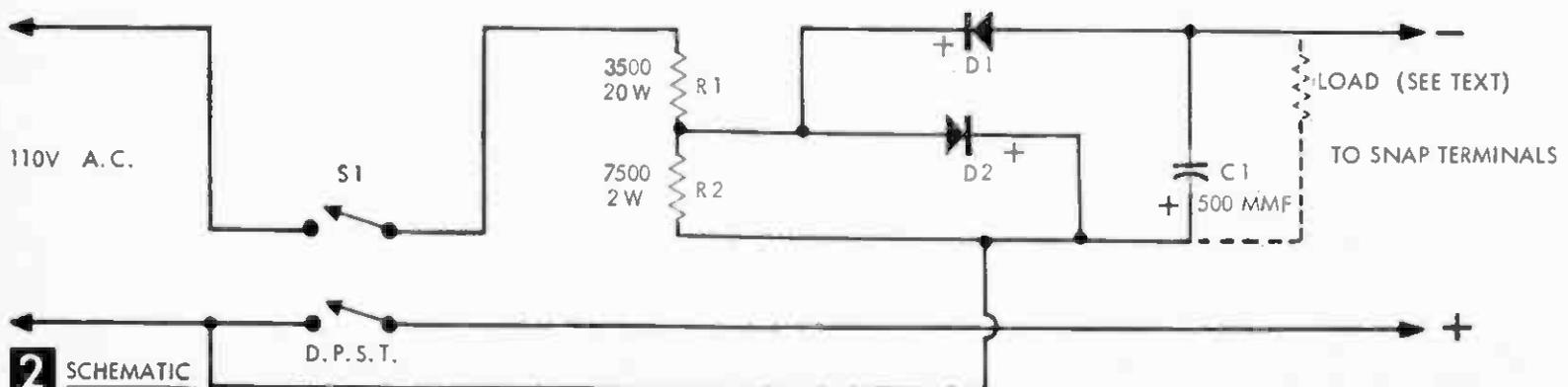As shown by the schematic, a DPST switch disconnects the output of the power supply from the receiver as well as the input voltage, preventing unnecessary battery drain by the relatively high internal resistance of the filter



2 SCHEMATIC

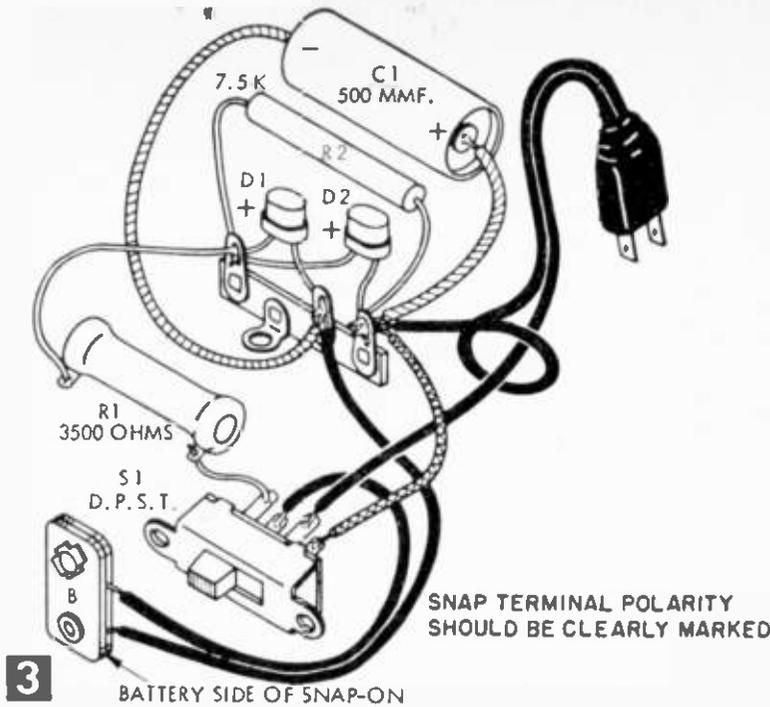

MATERIALS LIST—TRANSISTOR "B" ELIMINATOR

Desig.	Description
R1	3500-ohm, 20-w. wire-wound resistor—IRC 2D (DG)
R2	7500-ohm, 2-w. metalized resistor (IRC BTB-2)
C1	500 mmfd., 15-v. capacitor (Sprague "Atom" TVA 1162, or equiv.)
D1, D2	silicon, selenium or germanium rectifiers (GE 1N91, Sylvania silicon SR 200, or International type 1V1 selenium)
SW	DPST slide switch (Wirt SW725, Allied Radio Co.)
	one 3-terminal tie-point
	two battery snap-on's (salvaged from used batteries)
	plastic case (Sprague Difilm .5-600 v. cap. 4 unit package container, or equiv.)
	ac line cord and plug

where the hand might contact either side of the line. Do not connect any mounting bolts extending through the case to the internal circuitry. One last word. Transistor radios are usually small and light—easily toppled from a chair or table. Tuck your extending earphone and power supply wires well away from the reaches of small feet. A trip through the air may take the pep out of your pet receiver.

capacitor and diode rectifiers when the receiver is not operating.

Locate parts to fit the plastic box that you have. Wiring is shown in Fig. 3. A typical box layout is shown in Fig. 1.


The battery-receiver snap-ons (Fig. 4) which fasten to the battery inside of the receiver must be marked to avoid placing the wrong voltage potential from the power supply across the receiver and battery effectively canceling the voltage output.

If it is necessary to operate the receiver without a battery across the load, thus stabilizing the current output of the power supply, a 2200-ohm, 1-watt resistor (as shown by the dotted lines in the schematic) must be inserted across the "B" eliminator output. However, for a 2- or 4-transistor radio use a 1200-ohm resistor in this position at all times, even when using while batteries are in the radio.


A word of caution before closing: Necessarily, such an economy power supply is not electrically isolated from the ac line. A lethal shock hazard is thus present at any point

Marking Your Radio for CD Bands

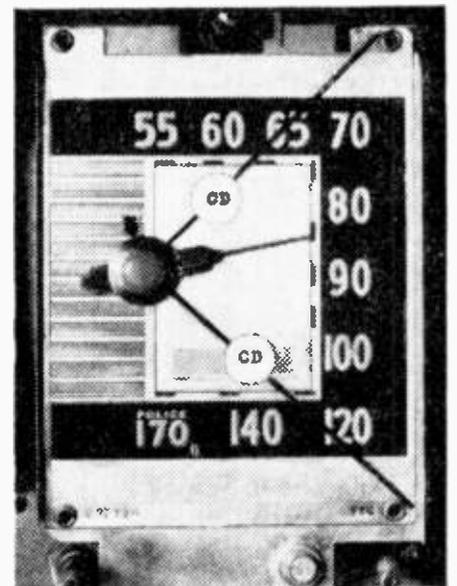• In the event of an enemy attack on the U. S., the only radio broadcasts will be made by Civil Defense on a frequency of 640 or 1240 kc. To mark your radio now for pinpoint emergency tuning, first remove the knobs and chassis-holding screws and slide chassis out of cabinet, being careful not




to ground an ac-dc chassis. Using a signal generator (your radio serviceman can do this) mark the exact 640 and 1240 kc spots on the dial with a sharp-pointed pencil. Pull the line plug for safety, and draw the lines across the face of the dial with black India ink, or white ink if dial is black, or you can stretch threads secured at each end with Duco cement across dial. Type the letters "CD" on white paper, cut out and cement on top of lines, or post a typed notice such as "Civil Defense, 640 kc, 1240 kc" on cabinet.—ARTHUR TRAUFFER.

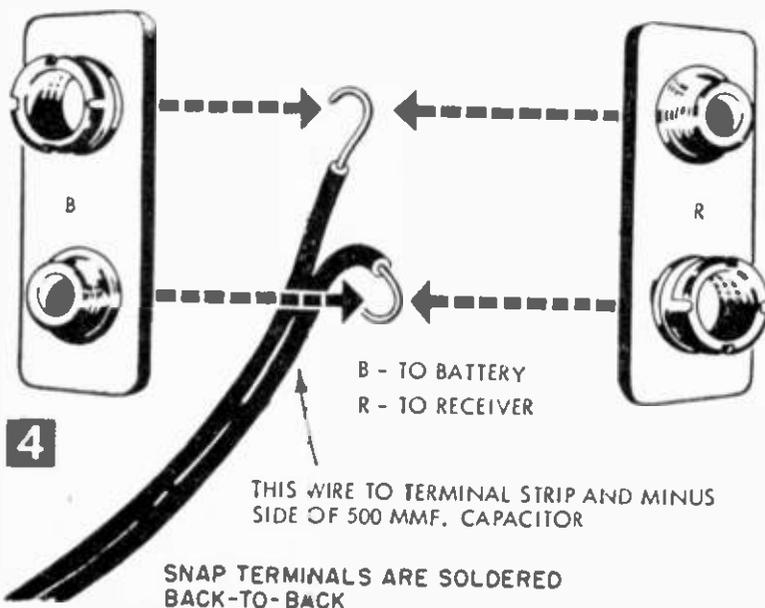

**Solution to What-Is-It?
Photo Quiz on Page 38**

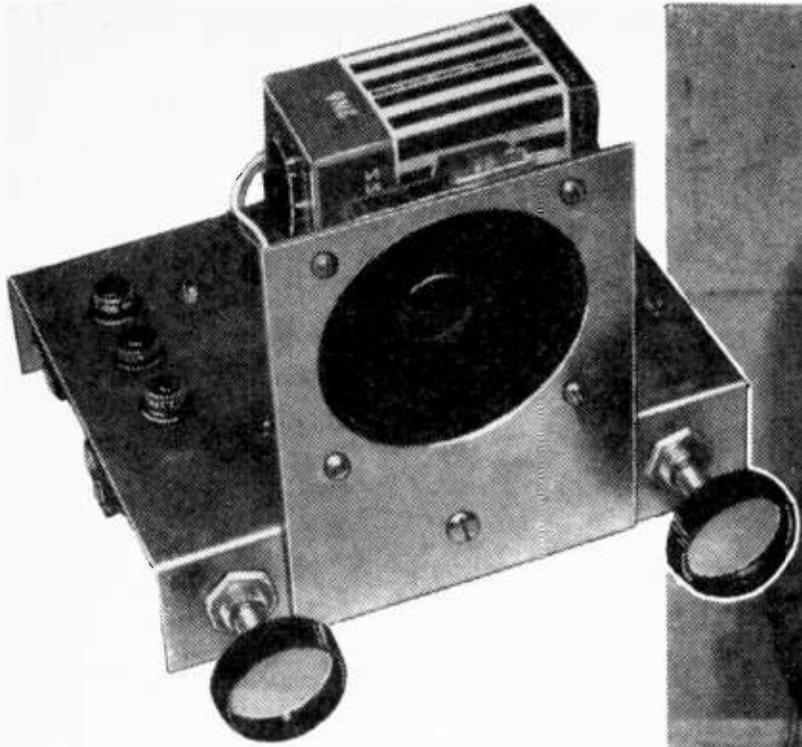- 1) Bayonet base of pilot lamp
- 2) Spool of wire solder
- 3) Spaghetti
- 4) Sharp nose pliers
- 5) Aluminum foil
- 6) Top of miniature tube



Here's a complete sound system that operates without a-c power. A built-in pre-amp permits use of dynamic mikes, reluctance type pickups as well as crystal phono pickups.

By THOMAS A. BLANCHARD





5-Transistor Audio Amplifier

It weighs only 18 ounces complete, and yet this tiny amplifier delivers loudspeaker volume and has inputs for both low and high impedance pickups.

You can bend the 5 1/8 x 4 x 1-in. chassis from a 5 1/8 x 6-in. of sheet aluminum, or use a Bud miniature chassis (see Materials List). A 3 x 4-in. aluminum panel supports a tiny 2 1/2-in. PM speaker (Fig. 1). Omit this panel if you intend to use the amp with larger speakers.

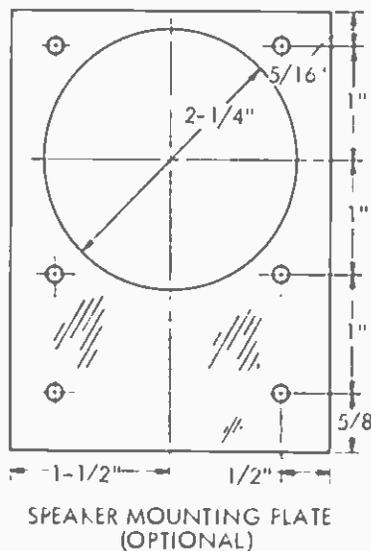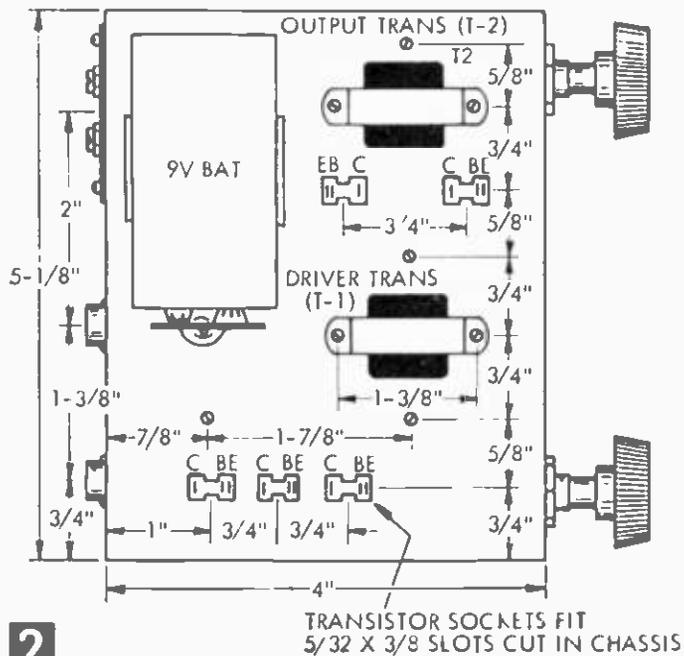Drill all chassis holes according to the layout (Fig. 2). Mount the driver and audio output transformers on top of the chassis with 4-40 x 1/4-in. machine screws and nuts. Then fasten the three 8-lug tie strips to the inside of the chassis. These strips support the resistors, capacitors and wiring in a neat un-




2

crowded way. Color code the tie lugs, and you'll have a chassis that is ideal for class or lab demonstration.


Mount the 5K tone control at the left side of the chassis, and the 10K volume control at the right. Fit the two RCA type phono jacks to the rear of the chassis. The shells of these jacks are self-grounding, so they require only one connection to the center pin.

Next complete all of the lead connections as shown in Fig. 3. Lugs #2 and #7 on each strip are your terminals for all grounded leads. Then, wire in the capacitors and resistors (Fig. 4). You can use either the rectangular type of 9-volt battery shown in Fig. 1A with connector clips at one end, or the round type with a connector snap at each end. Fasten the battery to the chassis with a strip of aluminum.

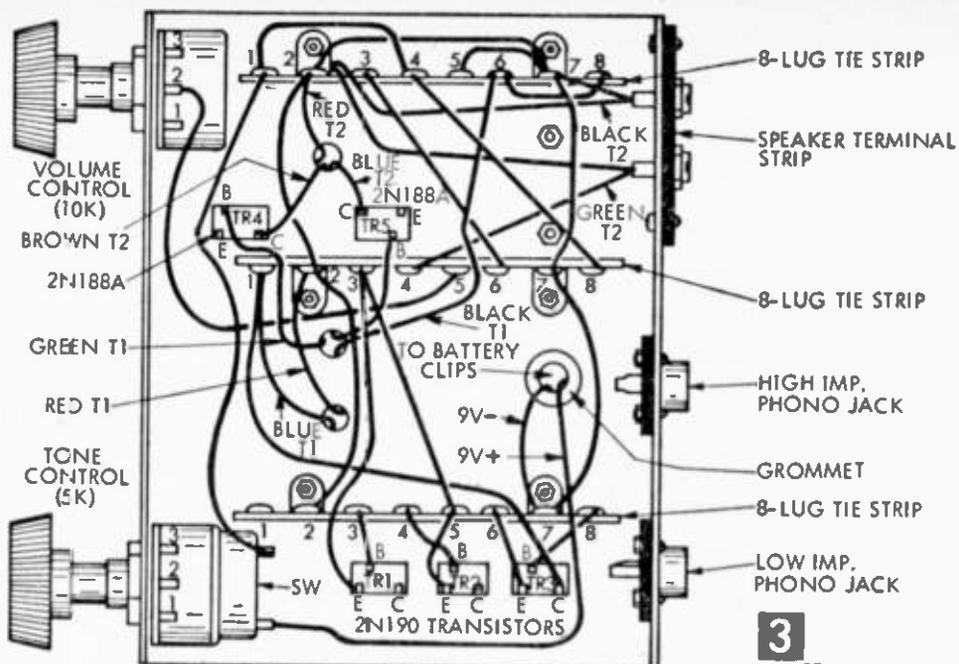
Operation. The low impedance input jack is intended for use with magnetic mikes or phono pickups. As shown in Fig. 5, TR1



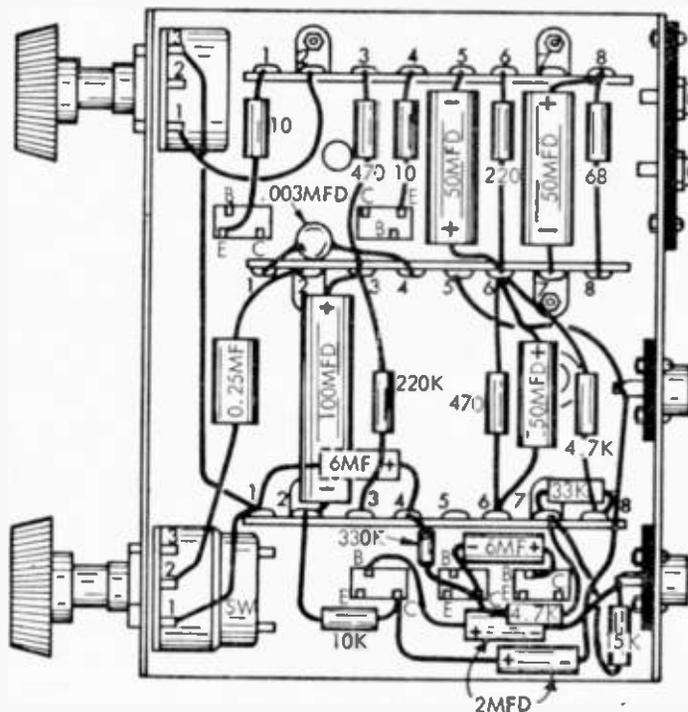3
NOTE:
MAKE ALL CONNECTIONS SHOWN HERE FIRST, THEN ADD PARTS SHOWN IN FIGURE 4. COLOR CODED T1 AND T2 LEADS FEED TO TRANSFORMERS.



4

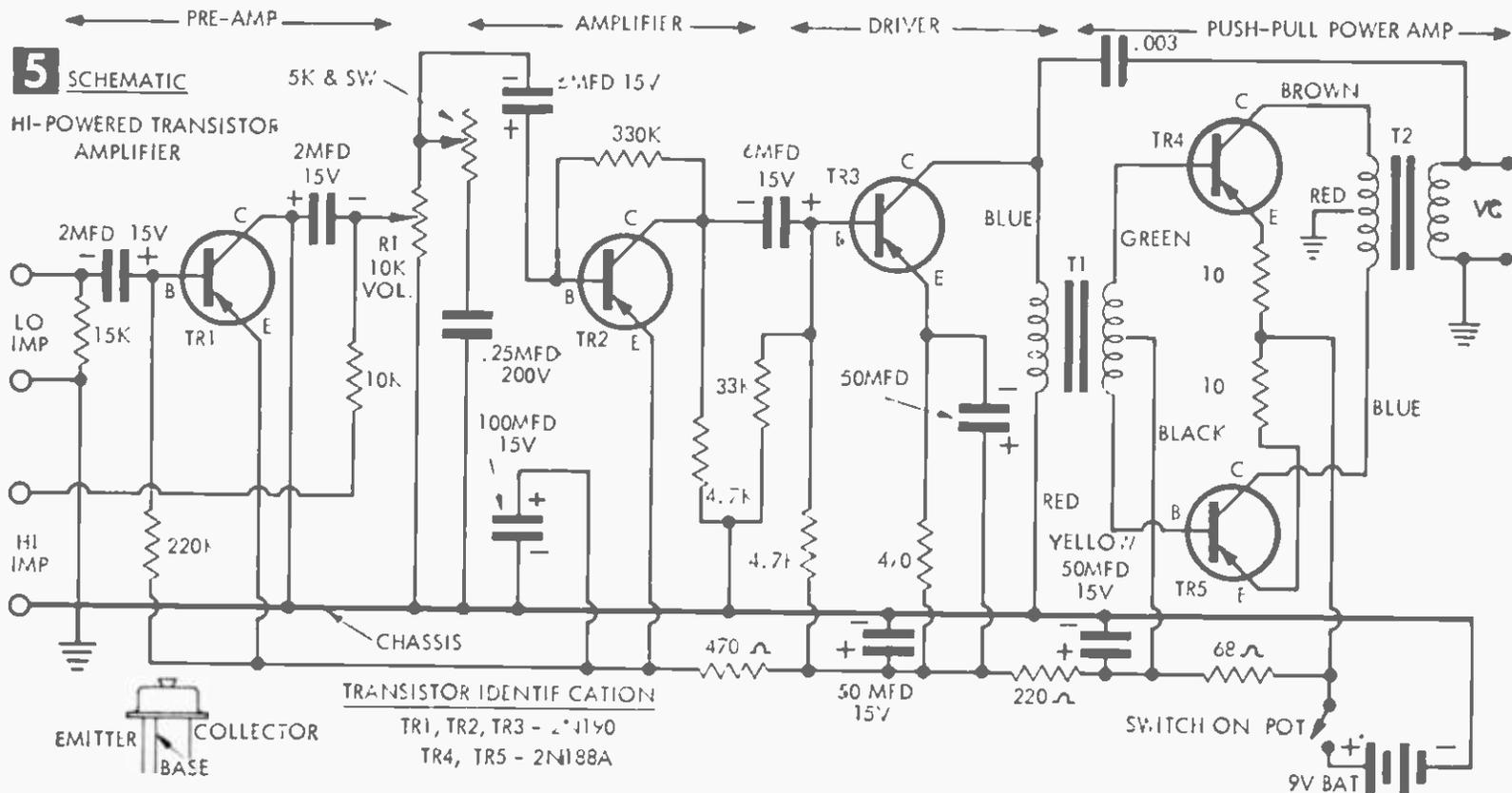

MATERIALS LIST—AUDIO AMP.

- | Amt. Req'd. | Size and Description |
|-------------|--|
| 1 | 5/8 x 4 x 1" aluminum chassis (Bud #CB-1619)* |
| 1 | 3 x 4" aluminum plate for speaker |
| 1 | 2 1/2" dia. 3.2 ohm PM speaker (Argonne #SK-65)* |
| 1 | T1 audio driver transformer, 5K primary impedance, 3K CT sec. impedance (Argonne #AR 173)* |
| 1 | T2 audio output transformer, 125 ohm C.T. pri 3.2 ohm sec. (Argonne #AR 174)* |
| 3 | TR1, TR2, TR3-GE 2N190 transistors (or equiv. type 2N189)* |
| 2 | TR4, TR5-GE 2N188A transistors (or equiv. types 2N186A or 2N187A)* |
| Capacitors | |
| 2 | 2mfd./15 V midget electrolytics |
| 2 | 6mfd./15 V midget electrolytics |
| 3 | 50mfd./15V midget electrolytics |
| 1 | 100mfd./15V midget electrolytic |
| 1 | .003mfd. ceramic capacitor |
| 1 | .25mfd./200 V miniature paper capacitor
Aerovox type P82Z or equal* |
| Resistors | |
| 1 | R1—10K pot, linear (for vol. control) |
| 1 | R2—5K pot, linear with switch (for tone control) |
| 2 | 10 ohm/1/2 watt carbon resistors |

- | Amt. Req'd. | Size and Description |
|---------------|---|
| 1 | 68 ohm/1/2 watt carbon resistor |
| 1 | 220 ohm 1/2 watt carbon resistor |
| 2 | 470 ohm/1/2 watt carbon resistors |
| 2 | 4.7K/1/2 watt carbon resistors |
| 1 | 10K/1/2 watt carbon resistor |
| 1 | 15K/1/2 watt carbon resistor |
| 1 | 33K/1/2 watt carbon resistor |
| 1 | 220K/1/2 watt carbon resistor |
| 1 | 330K/1/2 watt carbon resistor |
| Miscellaneous | |
| 3 | 8-lug tie strips |
| 1 | 2-screw terminal strip |
| 2 | RCA type phono jacks |
| 1 | Burgess 2N6 (or equal)
9V battery |
| 1 pr. | snap connectors for above |
| 1 | battery mtg. clip |
| 5 | retainer mtg. ring
transformer sockets |
| 2 | push-on knobs for 1/4" shaft |
| 1 | rubber grommet |

* These parts are listed in the mail-order catalog of Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

acts as a pre-amp. When you plug high impedance reproducers such as crystal type phono pickups into the high impedance jack, they feed directly into the TR2 amplifier stage.

Transistor TR3 acts as a driver, with transistors TR4 and TR5 operating as a push-pull power amp. All of the transistors are low-

priced types, and your circuit will perform equally well with the substituted transistors shown in the materials list.

Any PM speaker with a 3.2 ohm voice-coil can be connected to the amplifier output terminals. To use speakers with 8 ohm voice coils, substitute an Argonne #176 output transformer for the #174 shown.

Reserve Your Copy NOW!

RADIO-TV EXPERIMENTER



ON SALE SEPTEMBER 1, 1961

SPECIAL BONUS OFFER—Send in coupon now and receive at no additional charge a special set of enlarged blueprint plans for the exclusively designed battery powered transistorized portable tape recorder.

Here is your chance to make sure that you don't miss the next exciting edition of the RADIO-TV EXPERIMENTER. Our editors have already begun work on this edition and it promises to be one of our very best. There's more new electronic projects, more new challenging electronic experiments—more of everything that has made the RADIO-TV EXPERIMENTER the outstanding do-it-yourself book in the electronics field. Mail this handy coupon in now. We'll reserve your copy for you and send it to you as soon as it is off the press.

RUSH COUPON TODAY

RADIO-TV EXPERIMENTER, Dept. 3002
450 East Ohio Street
Chicago 11, Illinois

Enclosed is 75¢. Please reserve my copy of Vol. 11 of RADIO-TV EXPERIMENTER which I understand will be sent to me by September 1, 1961.

Name

Address

CityZone.....

State

AC Line Voltage Regulator


By FORREST H. FRANTZ, Sr.

THE experimenter faces a difficult challenge in attempting to provide a constant ac line voltage for critical experiments. The line voltage varies considerably due to variations in load with time, variation in loads over small segments of the power distribution system, and the voltage drop in the wiring from the line service connection. Variations from 110 to 120 v. are common, and variations from 105 to 130 v. sometimes occur during the course of a day.

This situation is not healthy because it causes you to lose control of your test and experiment procedures. A regulated line voltage is essential for certain work. I developed an inexpensive scheme for first approximation regulation that will work beautifully and meet the requirements of most experimenters.


The regulating heart of the device is an Amperite ballast regulating tube. This tube is a non-linear resistor that maintains current constant over a considerable range of input voltage regulation. It may be thought of as a rheostat that automatically adjusts itself to a high resistance value when input voltage increases and to a lower resistance value when voltage decreases.

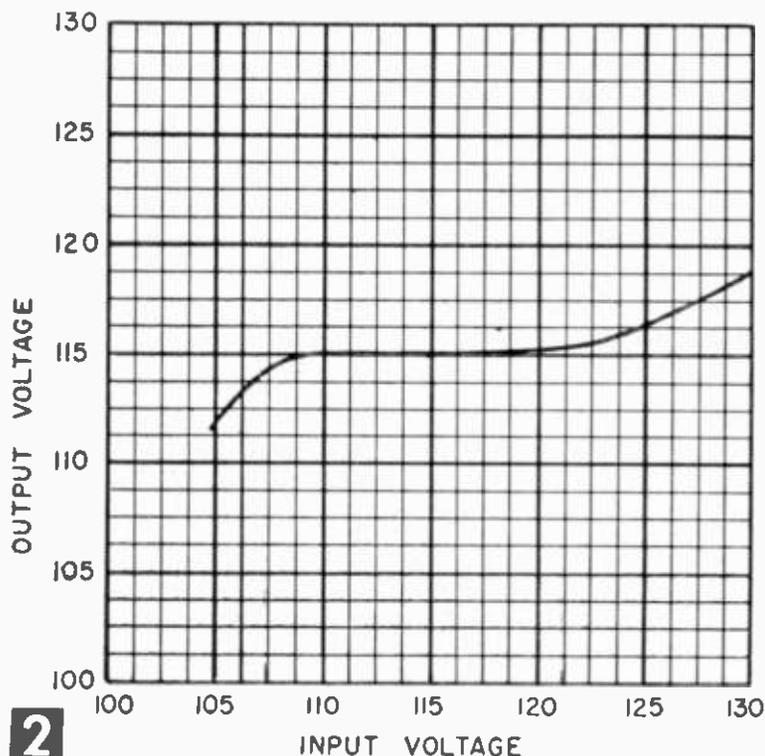The use of the ballast tube, with the attendant voltage drop and the fact that for low voltage a greater output voltage is required, necessitates the employment of a step-up device. A 25-v. filament transformer connected series aiding is employed for this purpose. The internal parallel resistance loading network allows the total load to be adjusted to



2

OUTPUT VS. INPUT VOLTAGE FOR REGULATOR

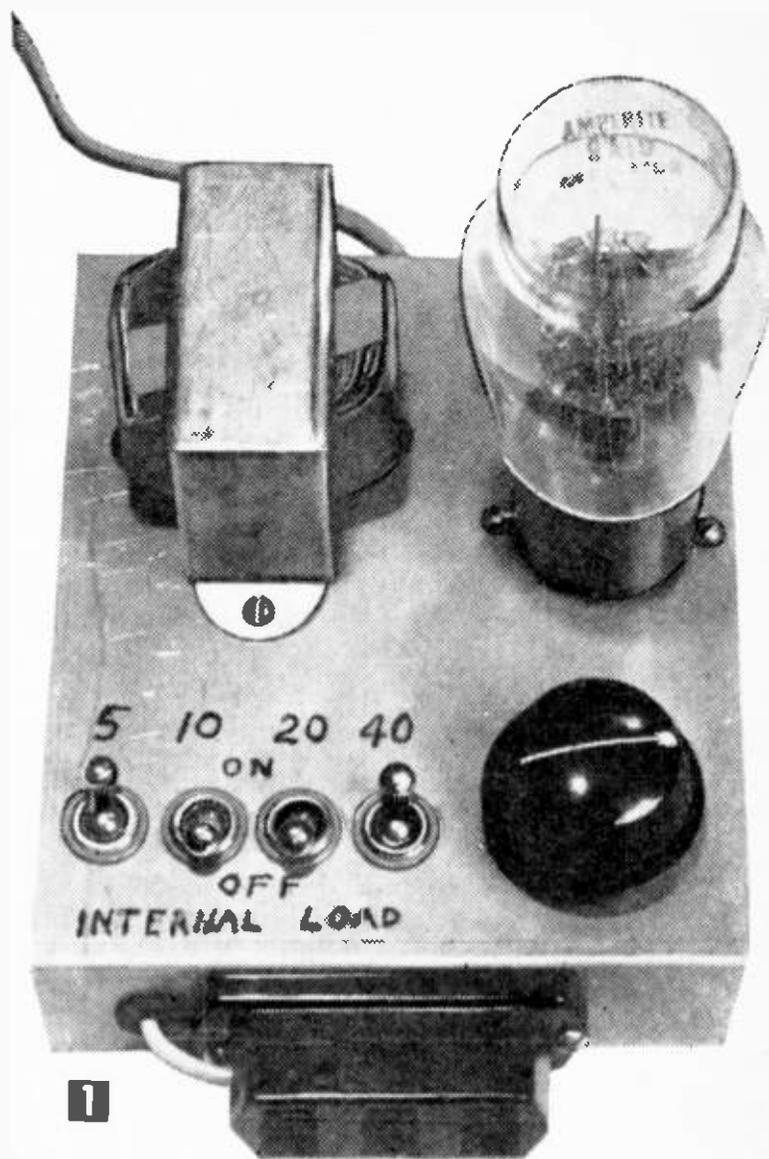

This line voltage regulator assures constant voltage for experiments.



the proper ballast regulator tube operating current. Fig. 2 shows the voltage output vs. input curve of the regulator for the circuit shown in Fig. 3.

The circuit of Fig. 3 employs an Amperite 9A10 ballast and can handle loads rated from 30 to 100 watts. If loads no greater than 45 watts are to be handled, an Amperite 5H10 ballast regulator tube should be used, and the 400-ohm, 50-W resistor and associated switch may be eliminated.

Follow Figs. 1, 3 and 4 in constructing the 100-watt regulator. Any available chassis may be used. The tube socket hole may be cut with a hole punch, fly cutter, or by drilling a series of small holes and completing the job with a file. The switch holes are $\frac{1}{2}$ -in. dia., the outlet wire and transformer lead holes are $\frac{3}{8}$ -in. dia., and all other holes are $\frac{1}{8}$ -in. dia.

Make firm mechanical connections and use a large soldering iron and rosin core solder.

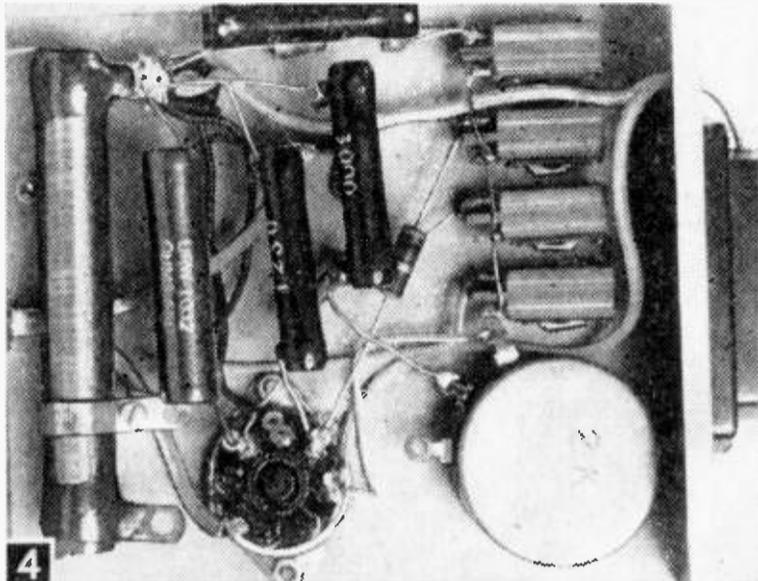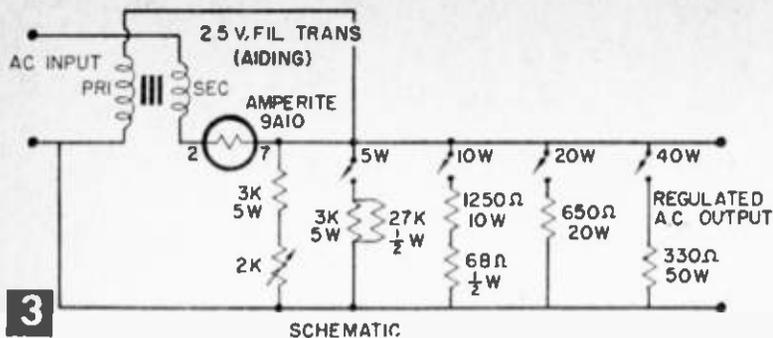The internal loading system provides loads of 5, 10, 20 and 40 watts controlled by individual switches so that internal loading may be varied from 5 to 75 watts in 5-watt incre-



Completed voltage regulator shows ports mounting and wiring.

ments. The potentiometer provides a small continuously variable increment. This potentiometer and the associated 3K resistor may be omitted for reasons of economy on the 100 watt version without serious limitations. The loading system is used in this way: if a 55-watt device is connected to the regulator, an internal load of 100—55 watts must be provided. This value is 45 watts. The photo (Fig. 1) shows the switch settings for this condition.

The regulator is used in the following way: Observe the power rating marked on the device to be operated, and add enough internal load to bring the total load to 100 watts. Plug the regulator in, and measure the line input voltage. If it is 115 v., adjust the internal load until the 9A10 ballast regulator has a slight glow. If the input line voltage is greater than 115 v., the load should be adjusted for a brighter regulator tube glow. If the input line voltage is less than 115 v., internal load should be increased until the ballast tube just starts to glow, and then decreased a small amount. This procedure is simple, and the adjustment need only be made once for a given load. The purpose of this adjustment is to establish the current at a value that will be maintained constant through the input line voltage variation range.


It should be noted that there is a small time lag in the operation of the regulator. A large change in line voltage, for example, an instantaneous jump from 110 v. to 125 v. will not be regulated instantaneously. The output voltage may rise from 115 v. to 120 v. and re-

quire a second or two to settle to the regulated value. Since most line voltage changes are not this large in a given instant, the small time lag is not detrimental to regulation.

The 100-watt regulator may be built for about \$10, the 45-watt for \$8. With surplus parts, the cost may be cut in half. This is the lowest cost line voltage regulator scheme available at this time. To increase the capacity of the unit to handle television sets, several tubes may be used in parallel in conjunction with a transformer capable of supplying a greater current demand.

A disadvantage is apparent in this scheme. The regulation, although it is automatic, requires an initial regulator setting for the load to be handled. And if the load demand changes substantially with time, regulation may not be too good. To overcome this objection, a saturable transformer may be employed in the regulator.

One commercial unit, the Microtran LVS-153 employs this idea. This unit is capable of maintaining the voltage within $\pm 3\%$ for line voltage variations from 100 to 125 v. and within $\pm 5\%$ for line voltages of 95 to 130 v. This regulator will handle loads up to 300 watts. The circuit is shown in Fig. 5. There are no preliminary adjustments for loads required except that one of the regulator tubes must be removed for loads of less than 200 watts. The cut out relay shown in the circuit automatically turns the regulator off when there is no load.

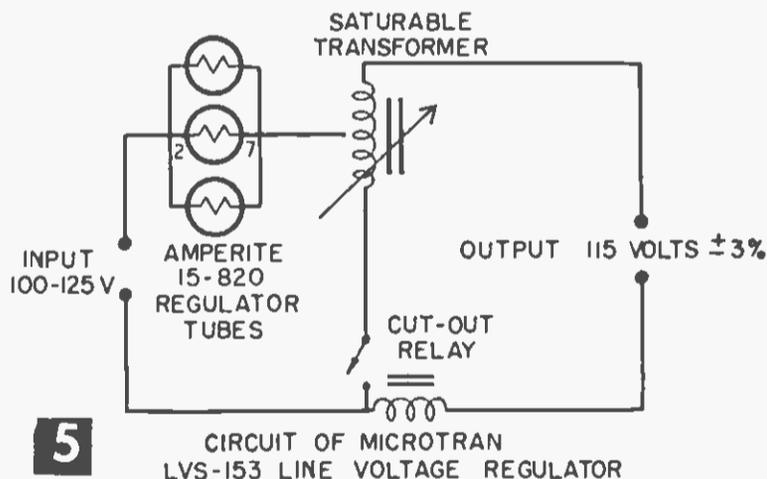


MATERIALS LIST—LINE VOLTAGE REGULATOR

No. Req'd.	Description
1	68-ohm resistor, 1/2 w., 10%
1	27K resistor, 1/2 w., 10%
2	3K resistors, 5 w., wirewound
1	1250-ohm resistor, 10 w., wirewound
1	650-ohm resistor, 20 w., wirewound
1	450-ohm adjustable resistor, 50 w., wirewound (adjusted to 330 ohms)
1	2K potentiometer, 3 w.
4	SPST switches
1	octal socket
1	25-v. filament transformer (Stancor P-6469)
1	9A10 ballast regulator tube (Amperite)
1	triple outlet (Monowatt 1240)
1	1 1/2 x 4 3/4 x 5 3/4" chassis

Parts available from Allied Radio Co. or Lafayette Radio Co.

Another scheme (Fig. 6), uses two gas-filled VR tubes such as the OC3 (VR105). The tubes are wired in parallel in opposite conduction directions. The OC3 fires at 133 v. and extinguishes at 105 v. An rms line voltage of 110 v. has a peak value of 156 v. The effect of the voltage regulator tubes on the ac line voltage is shown. The output voltage is reduced, and a step-up transformer is needed. Since the ac waveform is distorted with a gaseous discharge regulator tube, this arrangement cannot be used where observation of the sine waveform is essential. A further disadvantage is that regulation is limited to a small range.

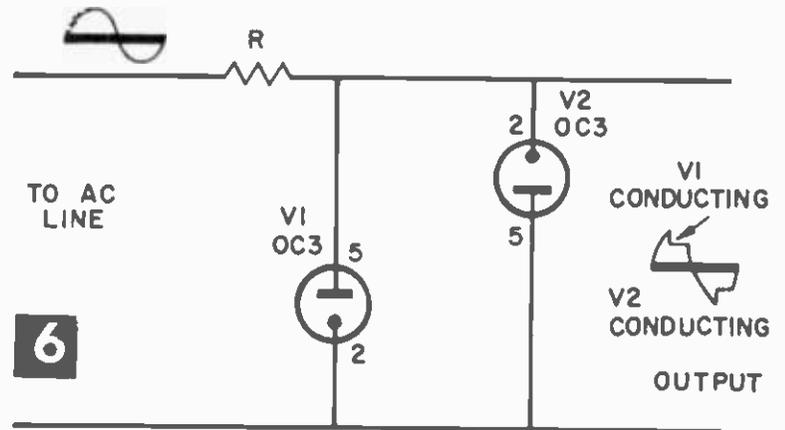

AC REGULATOR SCHEME EMPLOYING GASEOUS VR TUBES. R IS DETERMINED BY LOAD OUTPUT IS APPROXIMATELY 95 VOLTS

Amateur Radio Numbersgram

1	2		3	4	5	6	7
8	0		9	3		10	
		11	0	13	0	0	
	14	4	15		16		17
18	8	8	19		20	2	22
23			24	25	26	5	0
		27	8	28	0	0	30
32	33	3	0	1		34	1
	35	3	0		36	5	37
38			39		40		41
		42	4	43	5		44
46		0	0				45
					47		5

ACROSS:

- 1) The amateur band between 1.8 and 2 mc.
- 3) Total voltage of eight 1½-v. batteries in series.
- 5) To find the average value of an ac current or voltage, we multiply the effective value by this decimal.
- 8) Amateur band between 7 and 7.3 mc.
- 9) Inductive reactance of a .1 henry inductor at 15 kc.
- 10) The peak value of a sine wave is equal to — times the average value.
- 11) Unmodulated carrier (letter and number).
- 12) The number of zeros represented by "k" in designating resistor values.
- 14) To obtain a General License you have to transmit code at this WPM.
- 18) Lower limit of the FM broadcast band in mc.
- 19) Ham band between 14 and 14.35 mc.
- 20) One dit-four dahs, two dits-three dahs, five dahs.
- 22) The filament voltage of a 50L6.
- 23) The number of digits represented by red in the resistor color code.
- 24) The resistance of a circuit when applied voltage is 475 v., current flow 1 amp.
- 26) Total resistance of two 25-ohm resistors in series.
- 27) The ham band which has an upper limit of 3.8 mc.
- 28) The frequency of a 750-meter signal.
- 32) Decimal multiplier used when converting from cycles to kc.
- 34) One-kilowatt in watts.
- 35) Upper limit of VHF band.
- 36) A common am superhet if frequency.


- 39) Maximum wattage output permitted the holder of a Novice License.
- 40) Total capacitance of 20 mfd and 30 mfd in parallel.
- 42) The current flowing in an ac circuit when applied voltage is 450 v., impedance 10 ohms.
- 44) 245,000 cps converted to kc.
- 46) Upper limit in mc. of the SHF band.
- 47) Upper limit of the 20-meter ham band.

DOWN:

- 1) Upper frequency limit of the 2-meter ham band.
- 2) Ripple frequency output of a ½-wave single phase rectifier.
- 3) Lower frequency limit of the 20-meter amateur band.
- 4) The voltage dropped when 1 amp. flows through 230-ohms resistance.
- 5) The wavelength in meters of a 500-kc signal.
- 6) The total resistance of 10-ohms in parallel with 12 ohms, in series with 66 ohms.
- 7) The wavelength of a 800-kc transmitter.
- 9) The number of electrical degrees in ¼ cycle of an ac signal.
- 11) Am radiotelephony.
- 13) To convert kc to mc, we must multiply by this decimal.
- 14) The number of electrical degrees that plate current flows in a class B amplifier.
- 15) The effective to peak value of a sine wave.
- 16) International distress frequency used by ships and aircraft.
- 17) The difference frequency produced when a 1,000-kc signal is mixed with a 50-kc signal.
- 18) The output frequency of a transmitter having a basic frequency of 2017.5 and two frequency doubler stages.
- 19) The output ripple frequency of a full-wave 2-phase rectifier.
- 21) The total voltage dropped across a series circuit when applied voltage is 250 v., current flow 1 amp.
- 25) The upper limit of the 6-meter ham band.
- 27) The value of a resistor color-coded gray-brown-brown.
- 29) 5 milliamps converted to amps.
- 30) The maximum modulation permitted in am transmission.
- 31) The frequency in kc of a 375-meter transmitter.
- 33) 30,000 mmfd converted to mfd.
- 36) The impedance of an ac circuit when applied voltage is 450 v., current flow 1 amp.
- 37) The voltage applied to an ac circuit when total impedance is 65 ohms, current flow 10 amps.
- 38) The total inductance of 60 and 80 microhenries in parallel (no mutual coupling).
- 41) The conductance of a circuit when current flow is 0.86 amps, applied voltage 2 v.
- 42) The total wattage dissipated by two 20-ohm, 20-watt resistors in series.
- 43) The amount of voltage that will send a current of 1 amp through 50-ohms resistance.
- 44) Two dozen decibels.
- 45) .055 millihenries converted to microhenries.

Solution on Page 62.

Sound-Searching Parabolic Mike

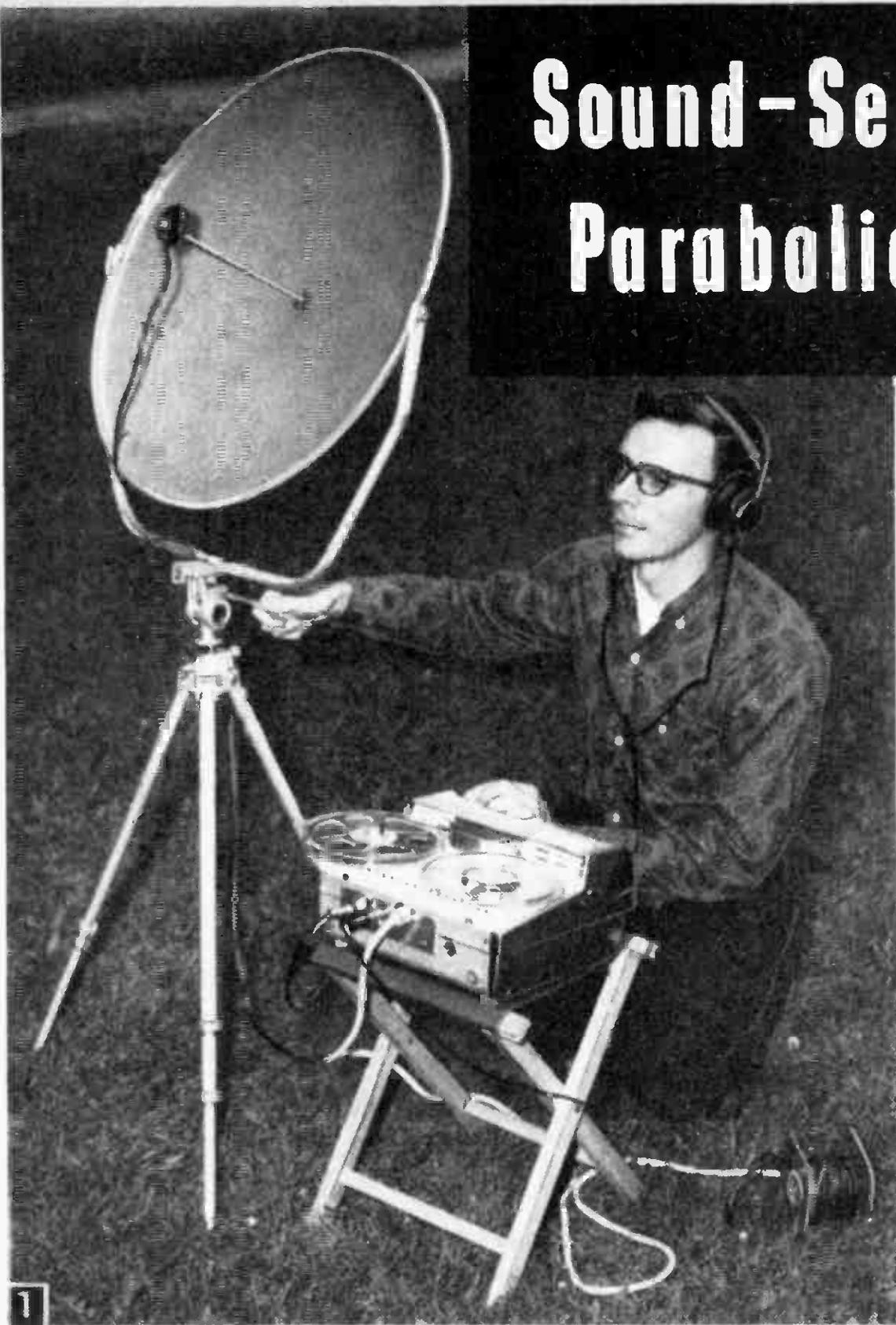

With earphones plugged into the output jack of a recorder, you can monitor the incoming sound. A disc (not shown) should be mounted in front of the mike to absorb unwanted sound.

although the disc is not selective enough to pick out a single bird call among many. For broadcast use, the unit was set up on top of the grandstand at a football game, and allowed radio broadcast of band music from the other side of the field which was almost drowned out by other noise picked up by a standard microphone.

The bright orange sled, with the station call letters painted on, was quite an attention getter. The operator wears phones connected to the broadcast amplifier so he can monitor the aiming of the dish, pointing it in any direction the announcer may call for.

This dish gives a definite boost to mike sensitivity. Gear was not available to determine exactly how much, but

tests run by Electro-Voice indicated that a good 3-ft. parabola gave a 10 DB gain, or a voltage gain of 3.16 times; and a 10 times boost in power output.


The Reflector is Made of a "Flying Disc" fiberglass sled manufactured by Kalamazoo Sled Company. You can order one through Sears Roebuck for under \$4. Remove the

Whispers 100-feet away, bird calls 150 feet away—these are only two of many fascinating experiments you can try with this unit

By JACK B. THORNTON

A PARABOLIC reflector made of a \$4 disc sled performs like equipment used in broadcast and detective work to pick up sounds hundreds of feet away.

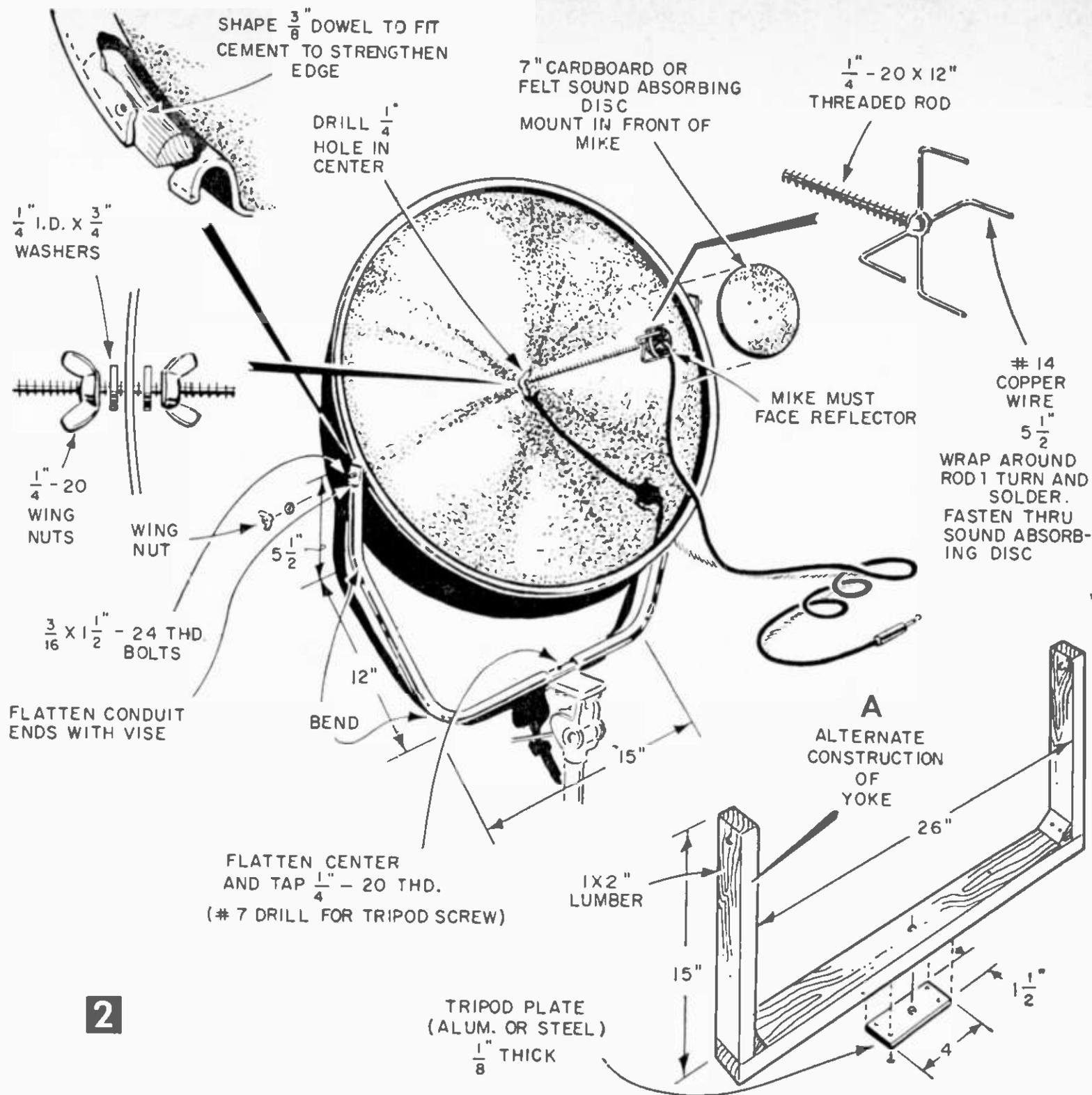With a VM tape recorder and an Astatic JT-30 mike this parabolic mike detected whispers at 100 feet and normal speech at 150 feet. Bird calls were recorded at 150 feet,



2

handles, and locate the center of the 26-in. dish by laying a yardstick across at the widest point and drawing a line. Then lay the yardstick across again, at a right angle to the first line and mark an X at the disc's center. Drill a $\frac{1}{4}$ -in. hole for the threaded microphone support rod.


Make the U-shaped yoke by bending a 4-ft. length of $\frac{1}{2}$ -in. electrical conduit (Fig. 2). An electrician's conduit bender makes the job easy. (You can also make the yoke of three lengths of 1 x 2-in. lumber, Fig. 2A) Flatten the bottom center part of the U and tap a $\frac{1}{4}$ -20 thread

EDITOR'S NOTE: Testing the 26-in. dish in our backyard (Fig. 1) we found the author's claims ultra-conservative. We picked up a neighbor's whisper four houses away, and a baby crying a block and a half away. With our setup out in the back alley, our helper paced out a hundred yards counting each pace in a normal tone of voice. At first the sound level decreased rapidly. Then from 20 paces out to about 100, there was very little change. At 110 paces out, his voice started to fade until he got to about 130. Then strangely, he came in loud and clear all the way out to 220 yards.

We found we could vary the performance by making minor adjustments on the mike mounting screw, and also that we could beam sound out almost 150 yards by playing the tape recorder through a small 3-in. loudspeaker substituted for the mike.

for camera tripod mounting. Also flatten the top ends of the U and drill the $\frac{3}{16}$ -in. holes for the swivel screws. Attach the yoke to the disc by drilling $\frac{3}{16}$ -in. holes on each side for $\frac{3}{16}$ -14 thread x $1\frac{1}{2}$ -in. bolts and wingnuts. Tighten these nuts just enough so that the assembly is free enough to swivel.

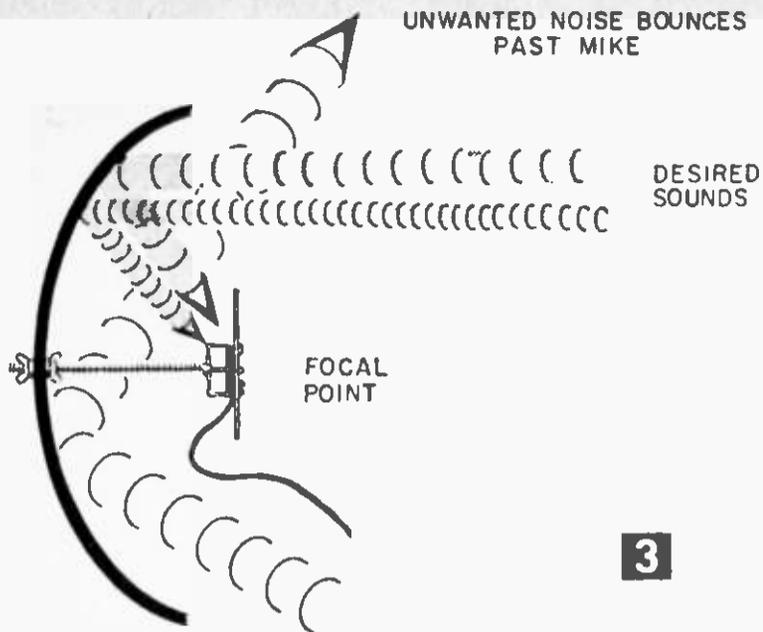Your Microphone and Amplifier should have as much gain as possible. Most tape recorders will work, and allow recording while you monitor with earphones plugged into the output jack or the monitor jack. A PA amplifier will work if it has



3

MATERIALS LIST—PARABOLIC MICROPHONE

- | | |
|----------|--|
| No. Req. | Size and Description |
| 1 | "Flying Disc" sled, 26" dia. Sears Roebuck catalog #8317 (\$3.72) |
| 4 | 1/2" electrical conduit |
| 12" | 1/4"—20 threaded rod with wingnuts and 2 washers. Available hardware stores. |
| 2 | 1 1/2 x 3/16"—24 thread bolts with wingnuts |
| 16" | #14 bare copper wire |
| Misc. | Electrical tape, 1/4"—20 tap, #7 drill, 7" sound absorbing disc of cardboard, felt or fiberglass |
| | Suggested Microphones |
| | Lapel Microphone PA-9, high impedance type. \$1.95* |
| | or |
| | 3-way Crystal Microphone #PA-31, high impedance type, \$3.95* |
| | *These microphones are listed in the 1960 Lafayette Radio Catalog, Box 1000, Jamaica 31, New York. |

Screw a wingnut on the mike support rod to about 4 in. from the mike. Place a washer on the rod, and push it through the hole in the disc. Mount another washer and nut on the back side. Set up your amplifier and listen on earphones as you point to a constant sound source about 50 feet away, such as a code oscillator or someone counting in a normal voice. Slowly adjust the threaded rod in and out until you find the point at which the sound is clearest.

You'll find that the sound is more brilliant at the focus, becoming slightly "bassy" on either side of the focal point. When you find it, lock the rod assembly. No further adjustment is needed unless you change microphones. Many mikes can be improved a bit in some locations by adding a 6- or 7-in. disc of felt or fiberglass to the dead side to block out unwanted sound (Fig. 2).

The Principle of the Sound Detecting mike is that the curved surface reflects sound waves from directly in front to a focal point (Fig. 3). Unwanted noise from angles to the side is bounced back out. The dead side of the microphone is toward the source of sound, so what you record is only by reflection.

Parabolic microphones have been also made from surplus radar reflectors which use a similar principle. Also, small pickups can be made from old style automobile headlight reflectors as well as from electric heater reflectors—the old type that had a bowl at least a foot in diameter.

provision for earphones instead of a loudspeaker. Your regular recorder mike can be used unless it is unusually large or heavy. Lapel mikes (see Materials List) will also do the job.

If you decide to order a mike, be sure to specify the proper impedance for your tape recorder or amplifier. Most tape recorders are high impedance, and if the figure is not mentioned in your instruction book, take the unit to an expert, or to your dealer for matching.

Make the mike support rod (Fig. 2) of a 12-in. length of threaded rod obtainable at hardware stores. Solder two 8-in. lengths of #12 or #14 bare copper wire in an X across the end of the rod. Bend the wires forward and tape them to four points around the edge of the mike, keeping the mike's face an inch or two from the end of the rod with the live side facing the disc. Then you can bend the copper wires to center the mike on the rod.

Mount the yoke on a photographer's tripod, or improvise a pipe stand and you're ready for a test. Set up the gear in a quiet location outdoors. Remember to take safety precautions in using no equipment that has a hot chassis that can be connected to either side of the 120 volt supply cord. Also avoid working on damp ground.

Invert Aerial to Speed Installation


- The neighbors may think you're crazy if you start the installation of a TV or radio aerial upside down, but doing this will help you to quickly and easily align a bracket on the edge of your house. By having the mast parallel a corner of the building, one of the windows, or some other vertical part, it is easy to sight the alignment while adjusting the mounting bracket. Then you need only reverse the mast to finish the job.

Solution to Amateur Radio Numbersgram, Page 59

1	6	0		1	2		6	3	7		3
4	0		9	4	3		0		1	5	7
8		1	A	0		2	0	0		4	5
	1	3		7			0		5		9
8	8		2	0		1	2	0		5	0
0	0		2	4	7	5		5	0		0
7		2	8	0		2	6	0		0	1
0	0	1				0		1	0	0	0
	3	0	0			3	4	5	6		0
3					7	5		5	0		0
4		4	5		0		0		2	4	5
3	0	0	0	0				1	4	3	5

Opinion Meter

By C. F. ROCKEY

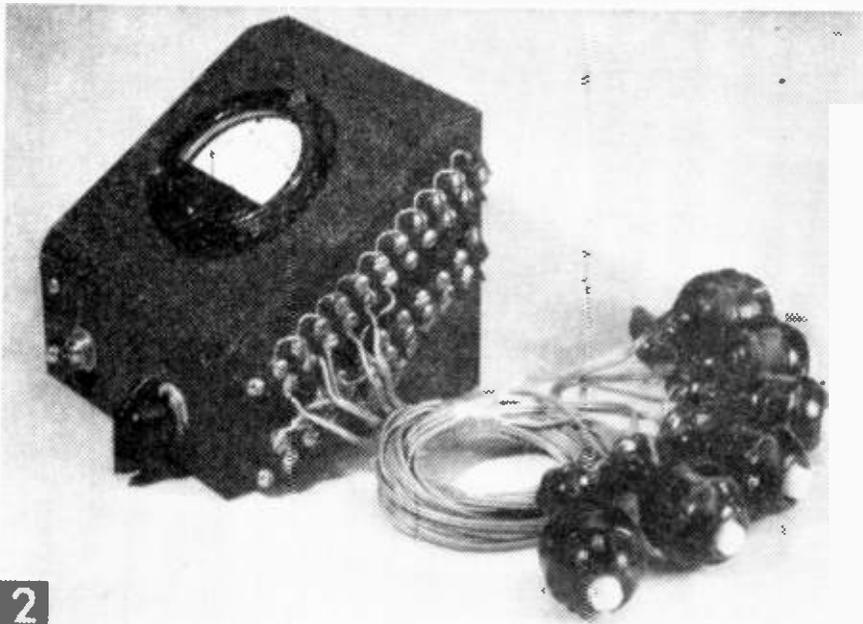

2

CALLED the *Group Thinkometer* by its inventors, this electronic device registers your opinion. You can vote against the boss, and nobody will be the wiser.

Let's say that around a conference table are gathered engineers, scientists, test pilots and designers. The project leader points to a chart and says, "All those in favor of this nozzle design vote Yes by pressing the button." Instantly, the total vote in favor is indicated on a dial.

This idea was developed and experimentally marketed by the Harwald Company of Evanston, Ill., and it was found that the "Thinkometer" does more than just speed up a voting procedure. The chairman can instantly determine the group opinion at any moment during a discussion. And of course, the vote is completely secret, as long as each person conceals the button in his hand. The "personality factor" in voting is eliminated, and each person is free to express his opinion,

in favor or against, without fear of offending a friend, a co-worker, or a boss.

We suggest that you build a Thinkometer and try it at a club meeting, or in a class discussion. You may find that it gives you a much more accurate reflection of what people think about controversial issues. Someday perhaps, legislatures may vote electronically, with equipment much like the Thinkometer.

Construction can be completed in an evening if you use the Premier metal case (Fig. 2). It comes pre-drilled with a 2-in. hole that needs only a little filing to fit the body of the meter. Drill $\frac{7}{64}$ -in. holes for mounting the meter and outside terminal strips, using these parts themselves as drilling templates.

Now take two of the five-point tie strips and make a 5-rung ladder, using 10,000-ohm resistors as each rung (Fig. 3). Solder each resistor lead carefully at each end. At one side of the ladder, tie all of the resistors together and bring out one lead. At the other side solder a 6-in. lead to each resistor.

Next make another ladder assembly just like the first one, so that you have two assemblies of five resistors each. Fasten these assemblies to the inside rear of the case using 6-32 x $\frac{1}{2}$ -in. machine screws and nuts. Lace the 10 individual resistor leads together into a cable and pass it out through the $\frac{3}{8}$ -in. grommets hole on the right side of the case.

On the front of the case, you will find two pre-stamped knockouts for the switch and pot. Pry the holes out with a screwdriver and mount the SPDT switch with the two-lug end downwards. Then assemble the on-off switch on the pot following manufacturer's directions, and mount it on the right. Next fasten the two 10 terminal strips on the right side of the case. Mount the battery clip inside with the positive end facing the switches. Temporarily insert the meter so you can arrange enough clearance while you complete


TABLE A

Dial Marking	Scale Reading in. ma.
0	0
1	0.13
2	0.27
3	0.39
4	0.50
5	0.60
6	0.69
7	0.77
8	0.86
9	0.93
10	1.0


wiring (Fig. 4). Since all of the resistors are 10,000 ohms, there is no need to connect them in order on the terminal strips. When all the wiring is complete, check each connection carefully. Then temporarily connect the meter, and test the operation.

How It Works. As you press more buttons, more current flows through the milliammeter, but not quite in direct proportion, since there is a constant resistance of about 500 ohms in series with the meter at all times. To test the meter, you connect the cables to the terminal strips and insert a fresh battery (polarity must be correct).

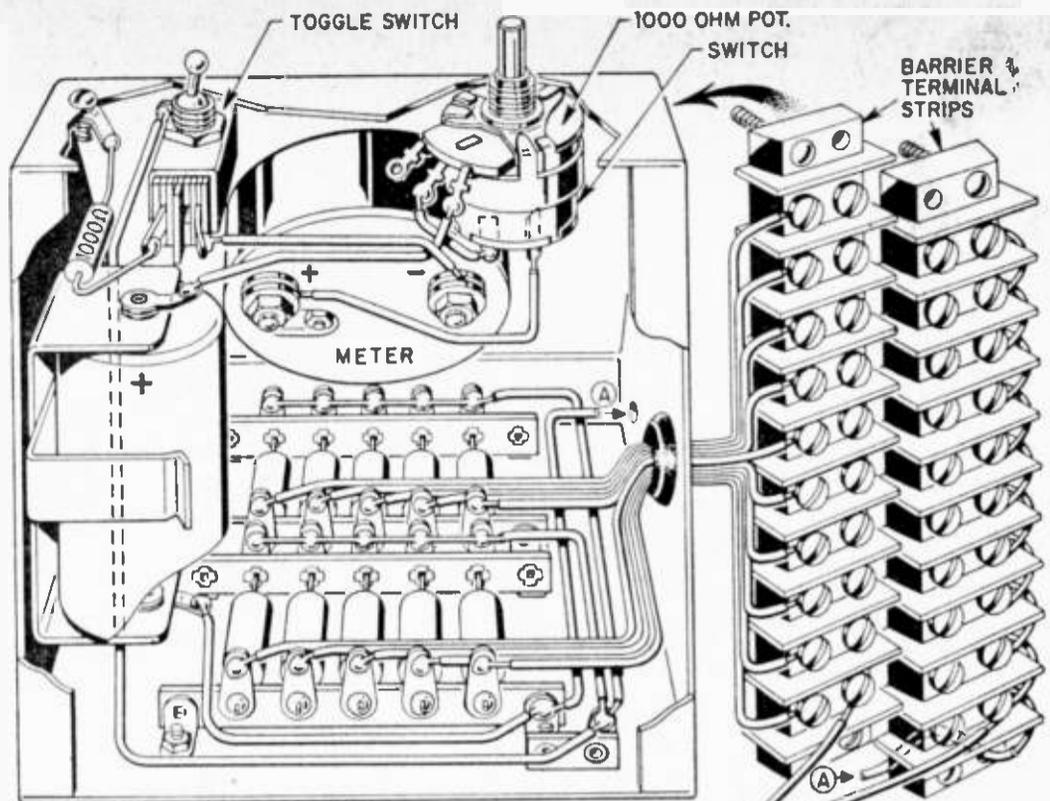With the power switch on, throw the toggle switch to *Calibrate*, its down position.



3 PICTORIAL

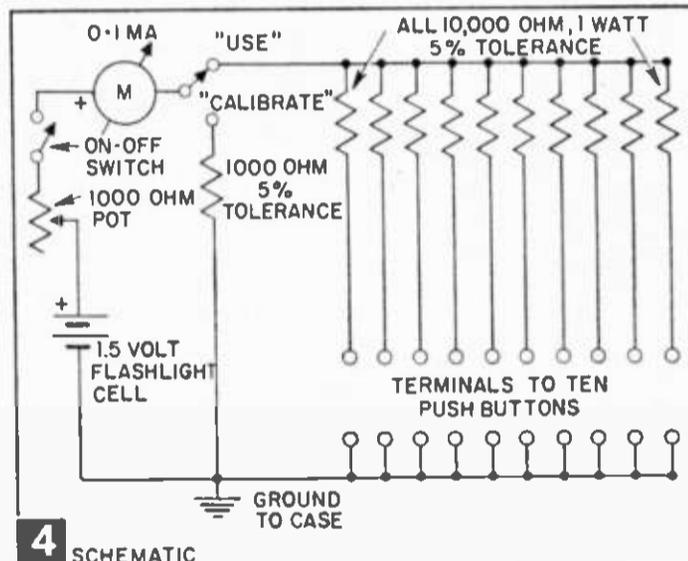

4 SCHEMATIC

MATERIALS LIST—OPINION METER

Amt. Req.	Size and Description
1	meter case, Premier No. SPC-23 (NE #91F861)*
1	0-1 ma. milliammeter, Triplett #221-T, 2" round (NE #55F1691)
1	1,000 ohm pot with switch, Mallory type U-4 Midgetrol (NE #9F134 and 9F194)
1	battery clip, 1 cell, Keystone #175 (NE #28F858)
1	toggle switch SPDT, AH&H (NE #23F024)
2	10 position Jones Type 10-140 barrier terminal strips (NE #28F708)
10	10,000 ohm, 1 watt, 5% resistors
1	1,000 ohm, 1 watt, 5% resistor
4	5 lug insulated Jones #2000 Terminals (NE #28F683)
1	knob, bar type, bakelite Davies #2300 (NE #26F100)
50 ft	#24 double strand speaker extension wire, Belden #8782 (NE #36F105B)
10	push buttons Eagle Electric Type 185B. Available local electric dealers or mail order from Contact Electric Supply Inc., 2030 N. Milwaukee Ave., Chicago 47, Ill. Cost post-paid, \$6.50.
Misc.	1 doz. 6-32 x 1/2" machine screws and nuts, 10' hookup wire, solder, rubber grommet, battery

* NE nos. refer to catalog items, Newark Electronics, 223 W. Madison, Chicago 6, Ill., and 4747 W. Century Blvd., Inglewood, Calif.

Now turn the pot clockwise until the meter reads exactly full scale. Then throw the switch to the *Use* position. The meter should now indicate the number of buttons pressed as in Table A. If there is serious error, recheck your wiring. If you used parts other than those in the Materials List, you may have to do your own calibration.

After testing the opinion meter, you are ready to add the scale markings to the meter face. Working in a clean dry room, remove the meter from its housing by taking out the three tiny screws near the back and pulling the movement straight back. Remove the two screws which hold the meter dial in place, and taking care not to damage the needle, remove the dial and add the markings (Table A). You can use pencil, or India Ink and a fine lettering pen. Then reassemble. If you used the parts in the Materials List, especially the 5% tolerance resistors, your calibration will remain accurate as long as the battery is reasonably fresh.

Dual Capacitor Substitution Box

Simple unit provides over 600 values
with only 36 capacitors

By W. F. GEPHART

IN SERVICING work, it is often necessary to replace a capacitor whose markings are illegible, and unless manufacturer's data is available, replacement must be made by trial and error until the correct value is found. In experimental and design work, various size capacitances must be tried for optimum results, and often matched pairs are required for multivibrator and bridge circuits. The capacitor substitution box shown in Fig. 1 will provide virtually all values needed and provides matched pairs for the most common values.

Two sets of 18 bypass capacitors are used, with separate switches, providing 18 values in matched pairs for multivibrator and bridge work. By the use of a switch, however, any two capacitors can be connected in series or in parallel, which gives a total of over 600 different capacity values that can be obtained with the 36 capacitors. Table A shows how 76 normally-needed capacity values are secured. In addition to the bypass values, the box also includes two sets of electrolytics, of voltage rating and capacity most often needed, for power supply substitution or experimentation.


As can be seen by the schematic (Fig. 2), the box consists of two 23-position switches, which select the capacitor required. Normally, capacitors for each rotary switch are connected to a separate set of binding posts, so two isolated values can be used simultaneously. If desired, the negative side of the two values may be made common by switch S4. When a value other than that included in the unit is needed, the two sections are connected together, either in series or parallel, by S1, which is a 3-position switch. When this switch is used, S4 must be in the "Separate" position, and the top and bottom binding posts must be used.

If at all possible, similar capacitor values for each switch assembly should be matched, so they can be used in matched pairs. High tolerance capacitors are quite expensive, but reasonably well-matched values can be secured in two ways. If you have access to a capacity bridge, capacitors from your junk box (or dealer's stock) can be checked for


matching. Another means is to order the capacitors together, specifying manufacturer and type. While the values furnished may not be the exact value labeled, they will tend to be equally high or low, and therefore fairly well matched.

Unless special precautions are taken, and a low capacity bridge is available for checking, the lower values (below 100 mmf) should be omitted, or it should be recognized that such values will not be wholly accurate. Any instrument has certain inherent capacity, and a box such as this could have an internal capacity up to 60 or 70 mmf, which precludes a setting below that. To minimize internal capacity, special precautions, such as using porcelain insulators for the binding posts, use of a special switch in the series-parallel circuit, and careful wiring techniques must be taken. All leads should be as short as possible, and the low-capacity capacitors should not touch each other.


Even with special precautions, the minimum internal capacity of the box will be somewhere from 3 to 10 mmf per section, primarily due to the capacity of the rotary switches. If a low-capacity capacitance bridge is available, the internal capacity of each section can be checked, and allowances made in selecting capacitors for the low values. In the unit shown, undersize or odd values had to be used for the 10, 15 and 22 mmf capaci-

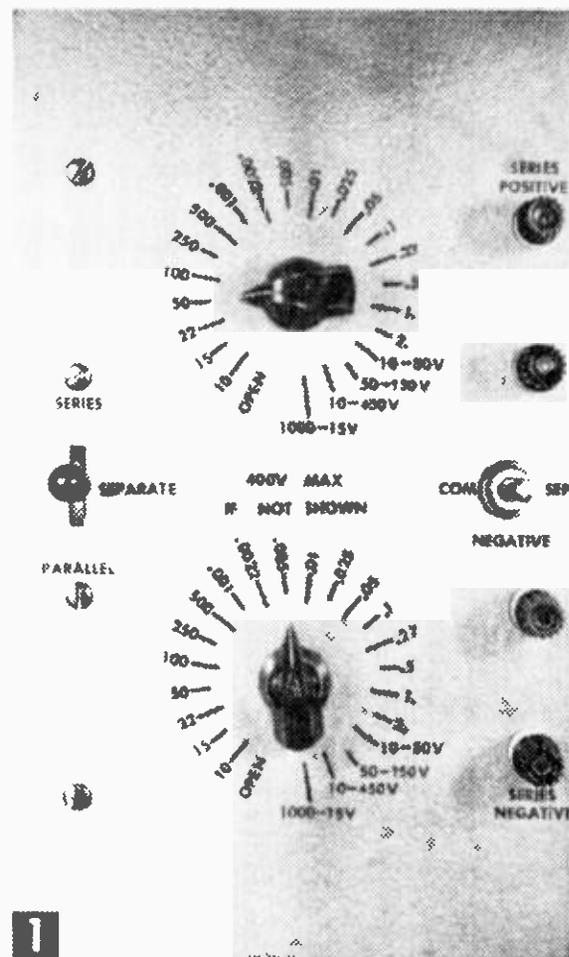

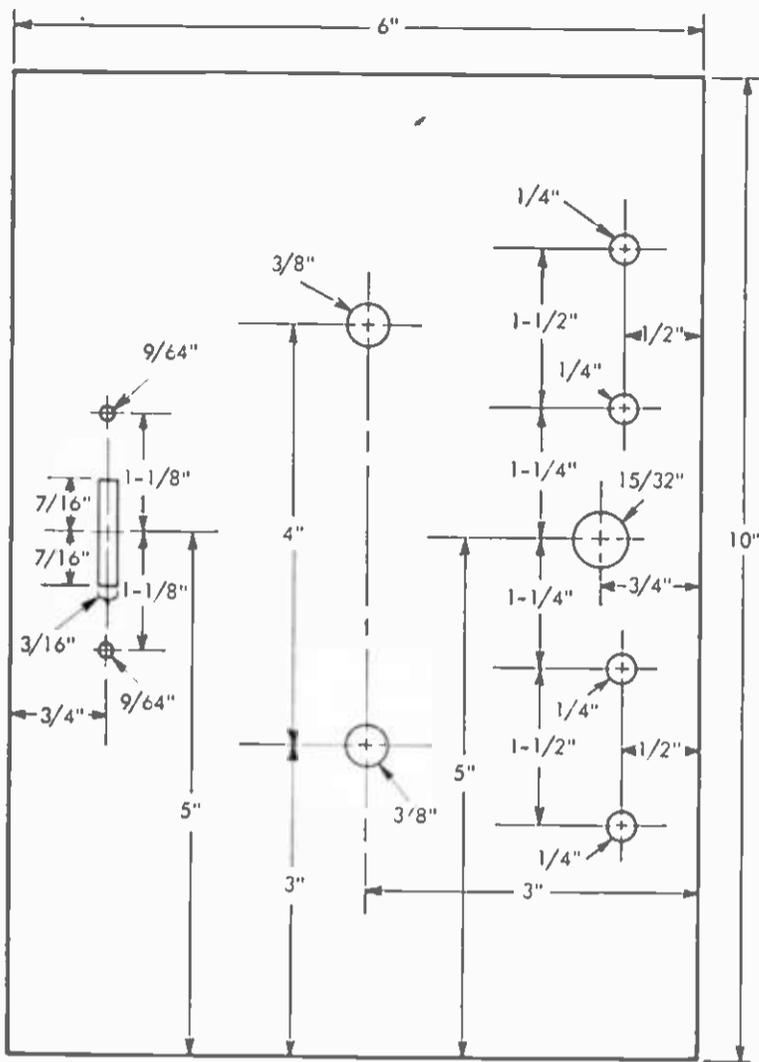A must for the service man, the capacitor substitution box tells the value when markings are illegible.



3 PANEL LAYOUT

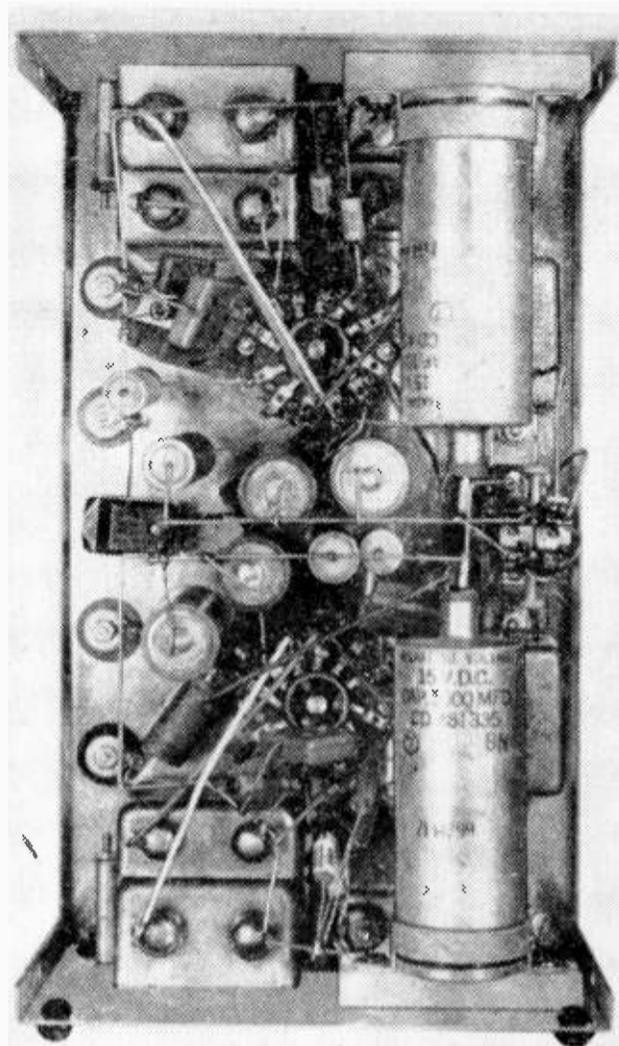


4

Back-of-panel view of the capacitor substitution box.

TABLE A—SECURING VALUES

Value MMF	Series Conn.	Parallel Conn.	Value MFD	Series Conn.	Parallel Conn.
5	10 & 10		.001	Included in Unit	
10	Included in Unit		.0011	.0022 & .0022	
12	15 & 100		.0015		500 & .001
15	Included in Unit		.0018	.0022 & .01	
20		10 & 10	.002	.0022 & .025	
22	Included in Unit		.0022	Included in Unit	
25	50 & 50	10 & 15	.0025	.005 & .005	
30		15 & 15	.0027		.0022 & 500
33	50 & 100		.0033	.005 & .01	
37		15 & 22	.005	Included in Unit	
40	50 & 250		.0051		.005 & 100
47	50 & .001		.0055		.005 & 500
50	Included in Unit		.006		.005 & .001
60		50 & 10	.0082	.01 & .05	
65		50 & 15	.01	Included in Unit	
70	100 & 250		.015		.005 & .01
83	100 & 500		.02		.01 & .01
91	100 & .001		.025	Included in Unit	
100	Included in Unit		.035		.01 & .025
110		100 & 10	.05	Included in Unit	
125	250 & 250		.068	.1 & .27	
150		50 & 100	.1	Included in Unit	
160	250 & 500		.15		.05 & .1
200	250 & .001		.2		.1 & .1
220	250 & .0022		.25	.5 & .5	
240	250 & .005		.27	Included in Unit	
250	Included in Unit		.33	.5 & 1.0	
272		250 & 22	.5	Included in Unit	
300		250 & 50	.68	1.0 & 2.0	
330	500 & .001		1.0	Included in Unit	
350		250 & 100	1.5		.5 & 1.0
400	500 & .0022		2.0	Included in Unit	
470	500 & .01		2.5		.5 & 2.0
500	Included in Unit		3.0		1.0 & 2.0
510		500 & 10	4.0		2.0 & 2.0
522		500 & 22			
550		500 & 50			
600		500 & 100			
680	.001 & .0022				
750		500 & 250			
820	.001 & .005				

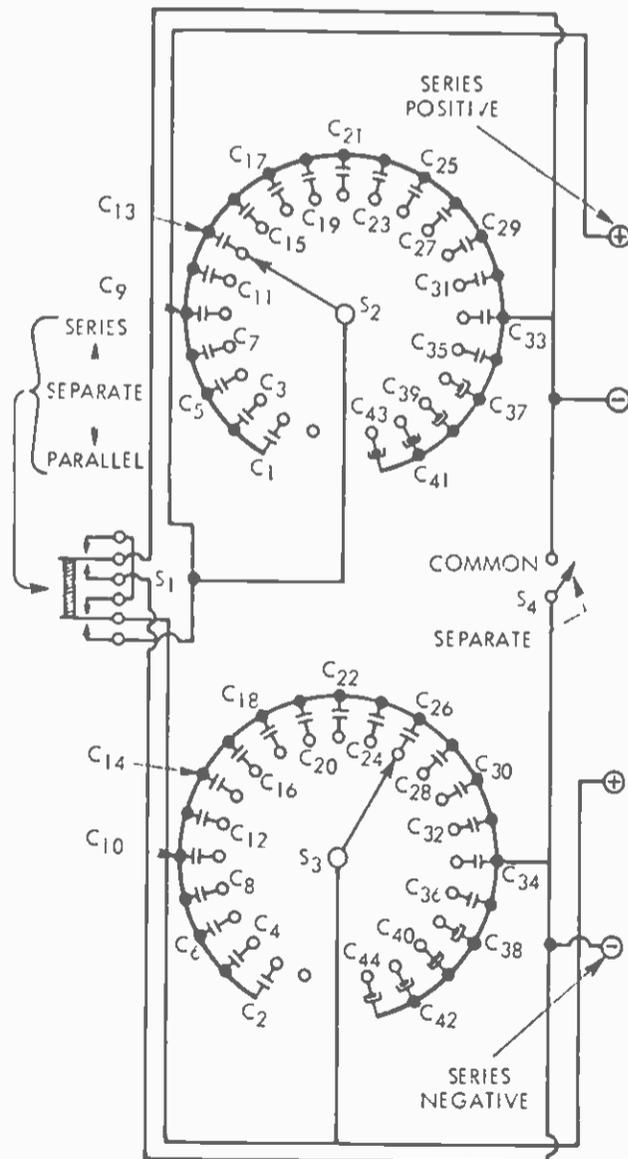

2 SCHEMATIC

MATERIALS LIST—CAPACITOR SUBSTITUTION BOX

DESIG.	Description
C1, C2	10 mmf ceramic or disc
C3, C4	15 mmf ceramic or disc
C5, C6	22 mmf ceramic or disc
C7, C8	50 mmf ceramic or disc
C9, C10	100 mmf mica
C11, C12	250 mmf mica
C13, C14	500 mmf mica
C15, C16	.001 mfd mica
C17, C18	.0022 mfd mica
C19, C20	.005 mfd mica
C21, C22	.01 mfd mica
C23, C24	.025 mfd metallized
C25, C26	.05 mfd "bathtub"
C27, C28	.1 mfd "bathtub"
C29, C30	.27 mfd metallized
C31, C32	.5 mfd "bathtub"
C33, C34	1.0 mfd "bathtub"
C35, C36	2.0 mfd "bathtub"
C37, C38	10 mfd 50 v. electrolytic
C39, C40	50 mfd 150 v. electrolytic
C41, C42	10 mfd 450 v. electrolytic
C43, C44	1000 mfd 15 v. electrolytic
S1	DPDT anti-capacity lever switch (Federal 1425) or DPDT center-off toggle switch (see text)
S2, S3	23-position (Centralab 1443) or 17-position (Mallory 32117J) single pole rotary switch (see text)
S4	SPST toggle switch

NOTE: This list specifies capacitors actually used. Similar values in paper capacitors will also work. All ratings should be 400 v. or higher.

3 1/2 x 6 x 1 1/2 in. Minibox (Bud CU-2110). 2 knobs, 4 binding posts, porcelain insulators for binding posts (see text), rubber feet, miscellaneous hardware as required.


tors to offset the internal capacity of the section. If this cannot be done, it is best to eliminate the values of "Open," 10, 15, 22, 50 and 100 mmf, and use the 17 position switches al-

ternately specified in the Materials List. In the box shown, a number of "bathtub" capacitors were used because they were available in surplus stocks. Paper capacitors will work satisfactorily, and are easier to mount. In wiring, a heavy negative bus wire should circle the area for each switch section, to permit short leads and to support the capacitors. This negative bus cannot touch the chassis, since all wiring must be isolated from the chassis to allow switching the negative leads as required. Any metal can capacitor (where the can is negative) must be insulated from the chassis also.

Figure 3 shows the drilling diagram for the front panel, using the anti-capacity lever switch for S1. If low values are not used, an ordinary DPDT center-off switch may be used, and a 1 5/32-in. hole drilled on the left side of the panel to match the one on the right side. Also, mounting holes for the bathtub capacitors used in this unit are not shown, since the capacitors actually used may vary in individual cases.

To save bench space, the unit is designed vertically, and has four rubber feet on the bottom. A small-scale copy of Table A is pasted on the back to give the intermediate values usually required.

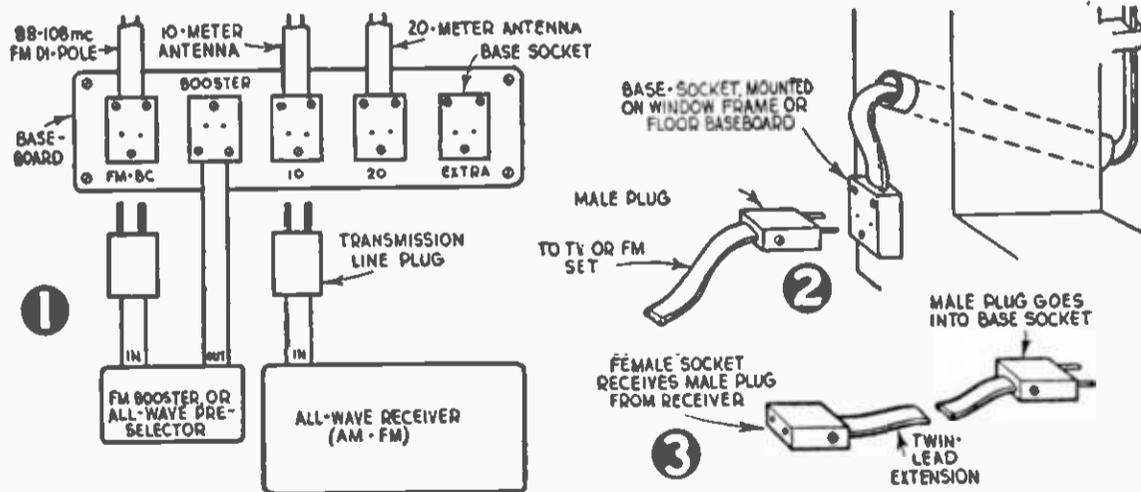Low-Loss Uniform-Impedance Antenna Switchboard



DX radio hobbyists, hams and experimenters can solve the problem of antenna switching and booster in-and-out switching by the use of Mosley polystyrene 300-ohm twin-lead male plugs, and female base-sockets (Fig. 1). This switchboard does away with the common hay-wire switching arrangements using knife-switches or toggle switches, which often result in UHF losses and impedance changes due to poor insulation and capacitances in the switches. By this method, many different combinations are possible whereby boosters, ham-band preselec-


tors, AM-FM receivers and transmitters may be plugged in or out of various dipole antennas for highest efficiency. Mount sockets on a hardwood base board and label sockets as shown. Place the switchboard for shortest leads to apparatus. Use 300-ohm ribbon twin-lead for all connections shown.

Low-Loss Uniform-Impedance Antenna Connectors for TV Sets

When connecting outdoor antennas to TV

sets, insert a pair of Mosley 300-ohm transmission line connectors in the twin-lead between window and set. Mount a 311 socket on window frame or floor baseboard, and connect a 301 plug to lead going to receiver (Fig. 2). Thus, the set may be quickly disconnected when the housewife wants to move the receiver for cleaning, or a twin-lead extension may be added easily when you want to move the receiver to another place in the room. In the latter case, connect a female socket to one end of extension, and a male plug to other (Fig. 3).—A. T.

Telephone Sentry

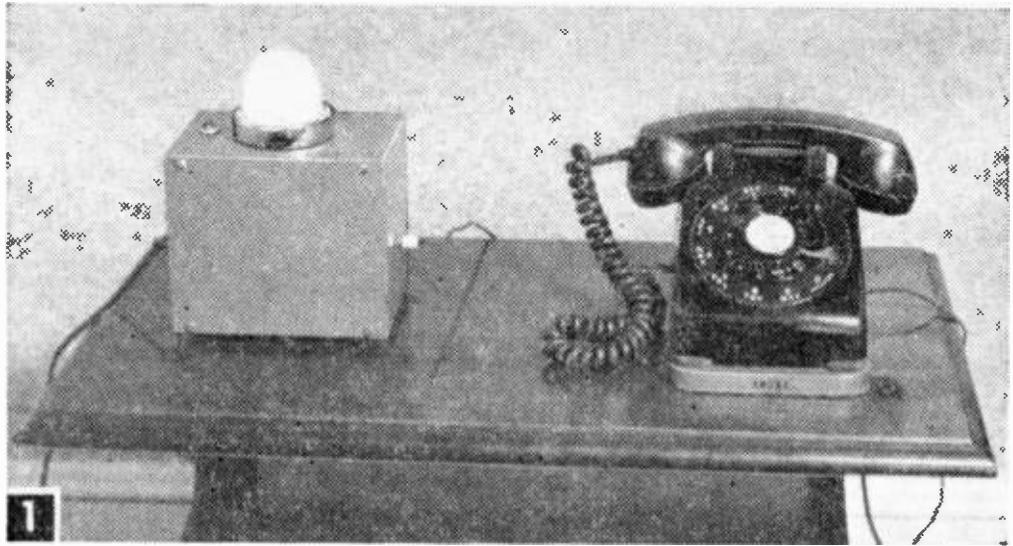


Transistorized telephone sentry lights with each ring of the bell and ignores other line disturbances if pick-up coil is properly located.

Now you can "see" the rings, if you can't hear them.
And baby doesn't need to be awakened by the bell

By HAROLD P. STRAND

If faulty hearing or noisy quarters cause you to miss incoming phone calls, a telephone sentry installed wherever you're most likely to see it will eliminate much of the difficulty.

The compact unit in Fig. 1 flashes brightly for the duration of each ring of your phone and is always ready to signal you since there is no battery to run down. When the bell rings, an inductive pick-up unit placed under the phone base receives a low energy current and passes it along to a special transistorized amplifier. This activates a relay to operate a 7½-watt, 125-volt lamp which produces a strong light signal when installed in an automobile backup light.


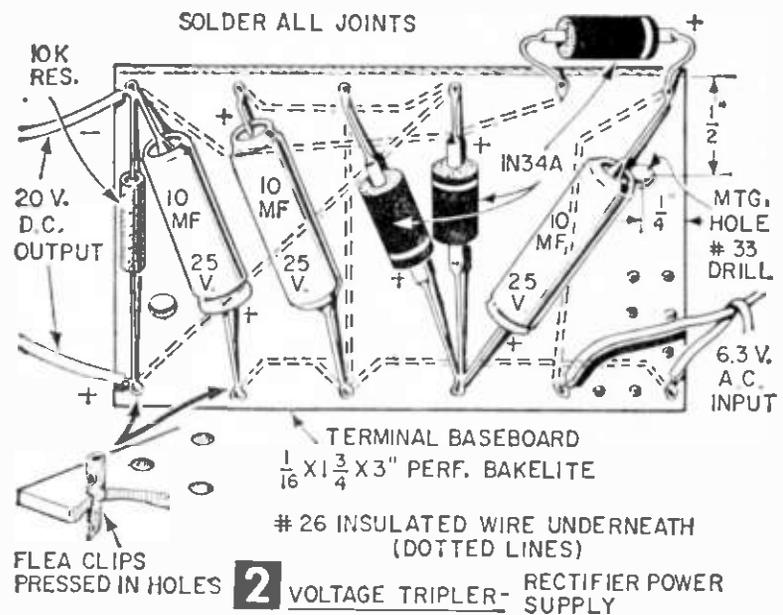


For increased versatility, the unit has a side outlet. You may expect a call while working in your yard or relaxing on your terrace some distance from the phone. An ex-

MATERIALS LIST—TELEPHONE SENTRY

No. Req'd	Size and Description
1	4 x 5 x 6" gray hammertone aluminum cabinet (Bud AU-1029-HG)
1	flush power outlet receptacle with mounting plate (Amphenol 61-F1)
1	3-amp, SPST toggle switch
1	miniature plug and jack set (MS370)
1	flat rubber or plastic-covered line cord with attached plug
1	angle bracket-type pilot lamp assembly for miniature screw base lamp, with ½" red jewel (Dialco series 510-121)
1	6-8-volt miniature base pilot lamp (#46)
1	120-volt primary and 6.3 volts at 1 amp secondary filament transformer (Thordarson 21F08)
1	8,000-ohm sensitive relay (Sigma 4-F)
4	diodes (CBS 1N34-A or equivalent)
2	transistors (RCA 2N-109)
2	transistor sockets (MS-275)
2	2-terminal barrier strips (Cinch-Jones 2-140)
1	8-terminal chassis strip (Cinch-Jones 56-C)
1	3-terminal chassis strip (Cinch-Jones 53-E)
2	2-terminal chassis strip (Cinch-Jones 51-A, 52)
1 pc	1/16" perforated Bakelite board cut to 1 3/4 x 3" (MS-304)
12	flea clips for above board (1 pkg. MS-263)


No. Req'd	Size and Description
1	100,000-ohm ½-watt resistor (Ohmite)
1	10,000-ohm ½-watt resistor (Ohmite)
3	10 mfd 25-volt miniature electrolytic capacitors (CF-142)
1	6 mfd 25-volt miniature electrolytic capacitor (CF-141)
1	.1 mfd 200-volt midget capacitor (Sprague 68-F17 or Cornell-Dubilier MP2P1)
1	telephone pick-up coil (MS-16)
All parts above are available from Lafayette Electronics, 165-08 Liberty Ave., Jamaica 33, N. Y.	
1	auto backup light (auto supply store—see photos for type wanted)
1	sign-type receptacle for lamp (H&W #9154, Leviton #9885 or similar-electrical supply store)
1 pc	.050 x 5 3/16 x 6 7/16" sheet aluminum ¼ or ½ hard for chassis (Try for scrap piece at sheet metal or metalworking shop)
Misc.	7½-watt 125-volt lamp, ½" wood stock for base, 1/16" felt for pick-up base and recess, small piece ¼" Bakelite, 3/16" dia. metal tubing for 2 3/8" collars, 8' plastic-covered #26 stranded hookup wire (small size for transistor circuit wiring), grommets for six ¼" holes and two 3/8" holes, 4 1/2"-dia. rubber mounting feet, miscellaneous screws and nuts

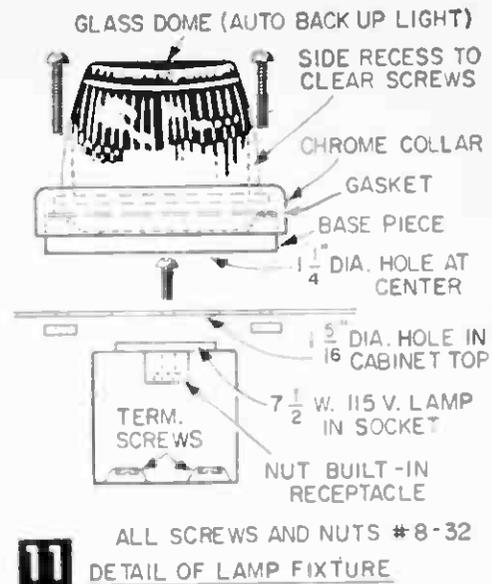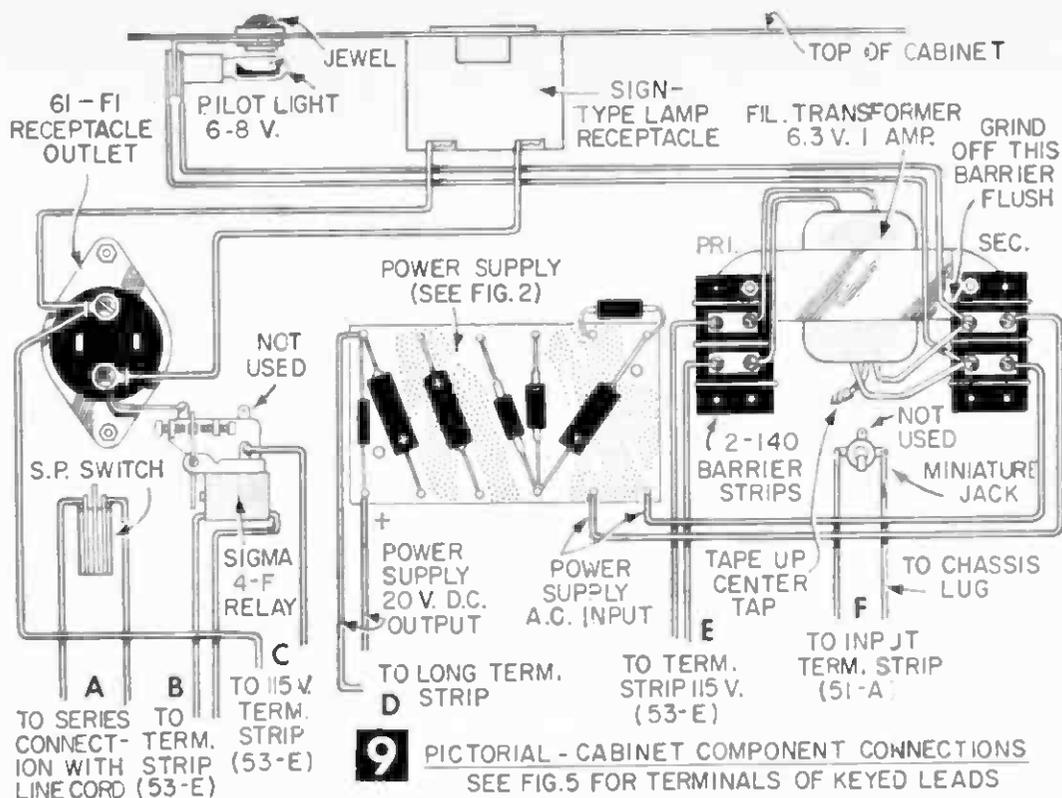

Finish top and edge of base to blend with unit or phone, after first masking bottom of recess to keep paint out. We used a ham-

mertone variety of gray enamel from a spray can. When dry, remove masking tape and glue felt to bottom of base and in recess.

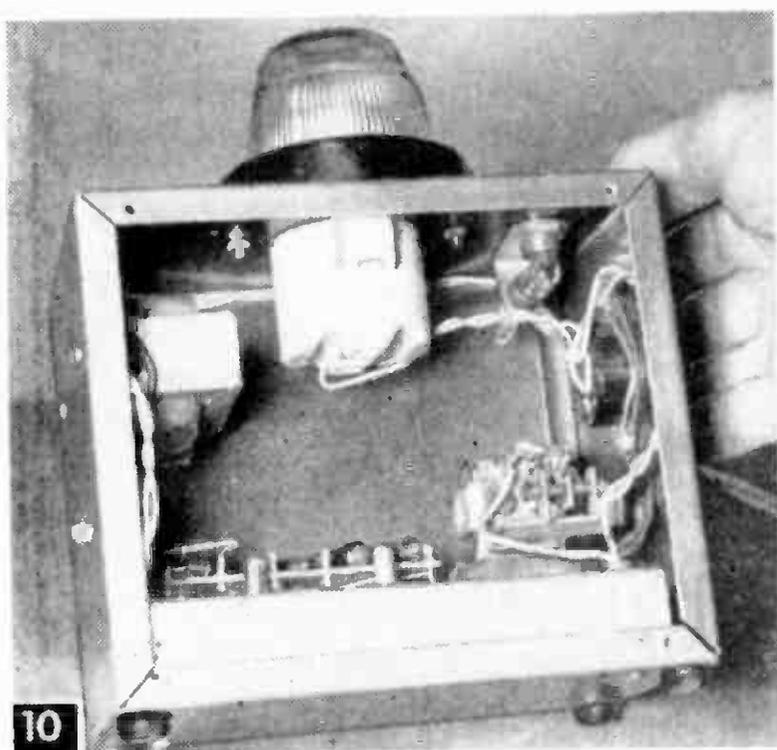Attach the miniature plug to pick-up coil leads as in Fig. 14. Ream a hole through head of the removable plastic cap large enough to accommodate cord, using a small rat-tail file or, with extreme care, a twist drill. Thread cord through hole. Bare wire ends but 1/16




Looking toward outlet end with chassis in place and all leads attached to components. Transistors are in front of terminal board at left.


where along the telephone line or instrument case. But unless the coil is located at one particular point, the voice as well as dial calls made from your phone will also cause the light to flash.

To eliminate this problem, you can make an attractive, permanent pick-up base of 1/2-in. hardwood plywood as in Fig. 1. If your phone is the new type shown, cut plywood to size, round corners and dress smooth as in Fig. 12. Cut recess with a sharp chisel to fit coil as in Fig. 13 and place pick-up under the bell magnets for least interference.

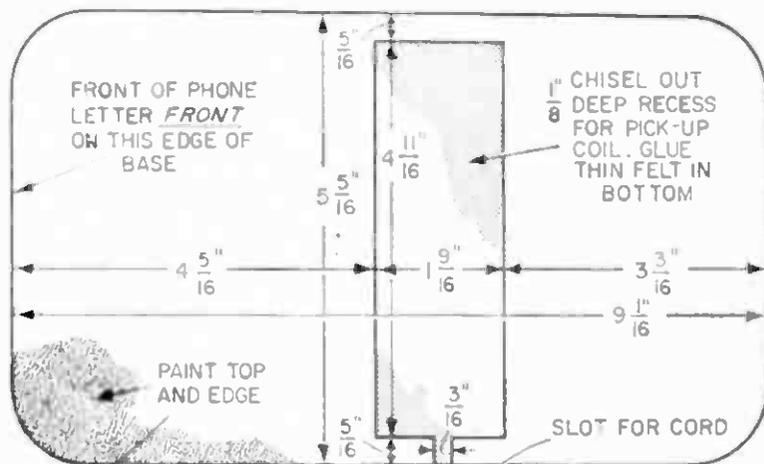
If your phone is an older type with a shorter rectangular base, shorten length to 7 5/8 in. and start recess cut exactly 4 in. back from front. Also shape corners to a 1/4-in. radius. If your phone is a wall type, tape pick-up to right side of the case, near the bottom.



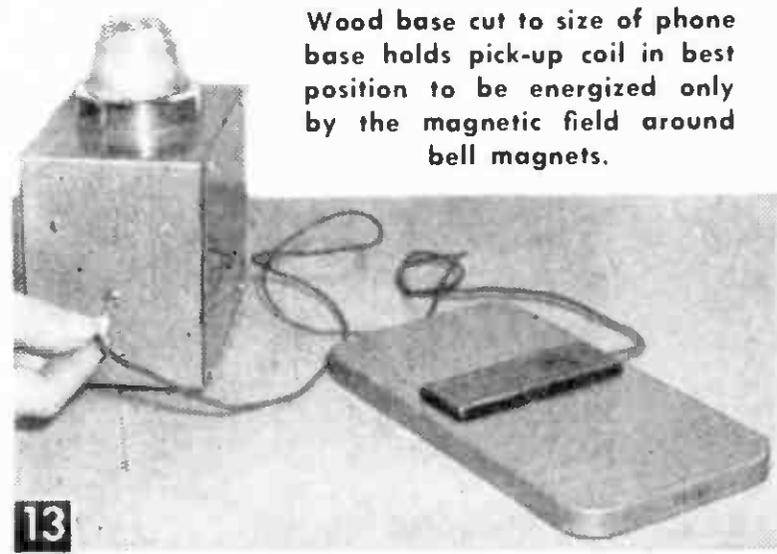PICK-UP BASE TO FIT NEW STYLE PHONES THIN FELT GLUED ON BOTTOM



13

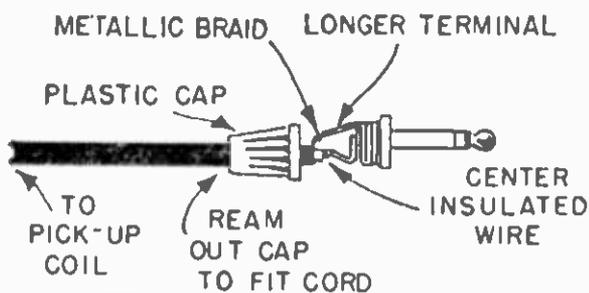

14 MINIATURE PLUG CONNECTION

in., then solder insulated center wire to short terminal connected to end of plug. Solder metallic braid to the longer terminal, which is grounded. Snip off any stray ends to prevent touching the wrong terminal and screw cap in place over connections.

Tuning Up the Completed Sentry. When unit is turned on and line cord plugged in, the pilot lamp should light and remain on. Remove pick-up coil from base and hold it near transformer as in Fig. 15. If unit is working correctly, the field surrounding the transformer will energize the coil and light the lamp. Move coil away and the light should go out.

For more positive action, some adjustment of the relay may be desirable, but *pull the line cord out before making any changes*. You can receive a severe shock working around 115-volt current, especially on a grounded floor such as in a basement. Adjust side contact terminal screws to allow sufficient motion for relay armature. Allow about $\frac{1}{16}$ in. between armature and fixed contacts when moving the armature with your fingers.


If you want the relay to pull in with less current, reduce tension by turning adjustment on top of the relay in a counterclockwise direction. Retain just enough tension so that the armature will pull away positively when coil is drawn away from transformer. After a little experimentation, the relay should operate perfectly.

If the unit does not operate, you may have a defective component. A leaking capacitor across the relay would short out the relay coil and make it inoperative.


A high resistance multimeter such as a Simpson Model 260 is a handy trouble shooter. Using its 50-volt d-c range, a test across output terminals on power supply board should read a little over 20 volts. The a-c reading at input should be about 6.5 volts. If you don't get such readings, one or more diodes and capacitors are either misplaced, wrongly wired or defective.

Move the relay armature with cord plugged in, using a thin piece of *dry wood*. If lamp turns on and off, the 115-volt circuit checks OK.

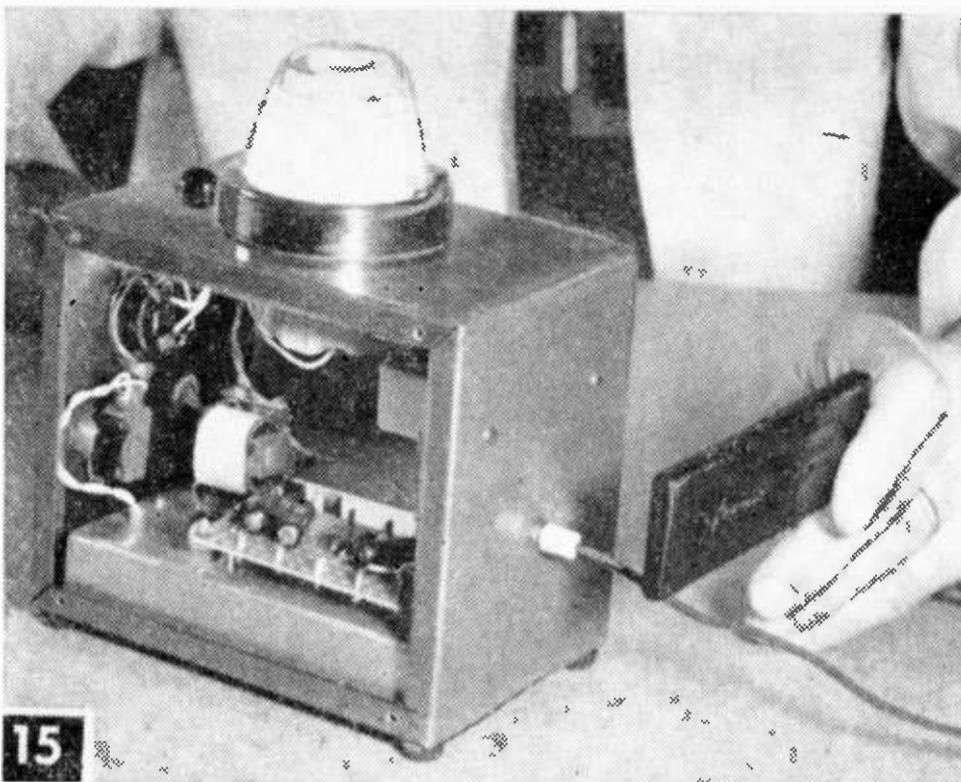Once the light appears to flash normally,



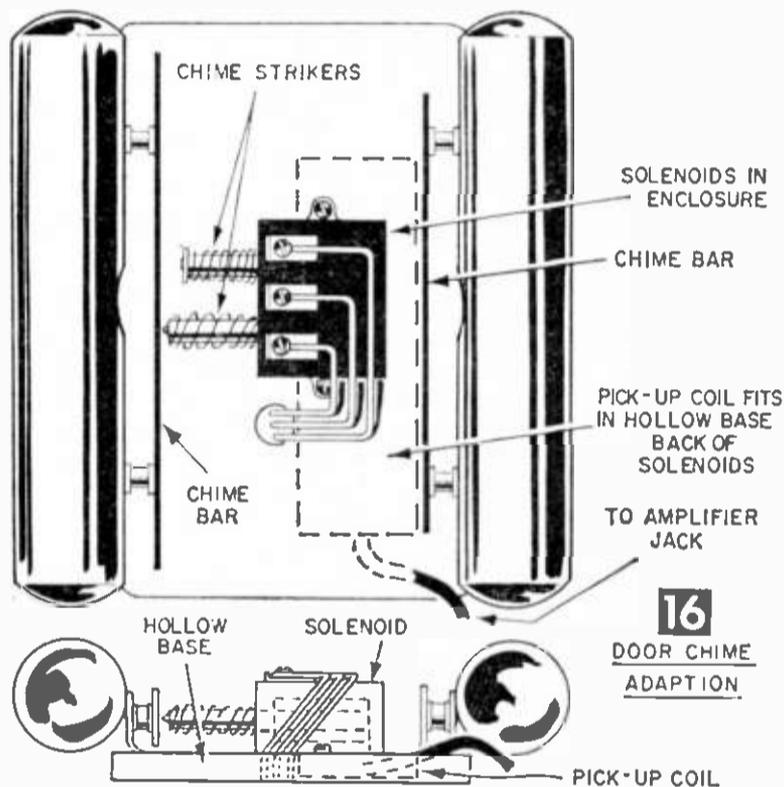15 To test sentry, magnetic field around transformer will operate light upon approach of pick-up coil.



you are ready for the final test. Place the pick-up baseboard in position, telephone a friend and ask him to call you back. Then stand aside and see your first call come in. If light does not operate properly, experiment by moving pick-up coil baseboard a bit.


Signals Door Chimes Too. The sentry works equally well on door chimes whereas signaling attempts through direct wiring from chimes to a nearby lamp socket are largely unsuccessful because of the low current output of transformer. The lamp either robs the chimes of current or vice versa, depending on size of the lamp used.

The sentry light, however, flashes brightly when the inductance pick-up unit is fitted into the hollow base of the chime fixture as in Fig. 16 immediately behind and slightly below the solenoid.

Electrical Right-Wrong Game

A homemade computer with planned decisions that is simple to make and fun to use

By FORREST H. FRANTZ, Sr.

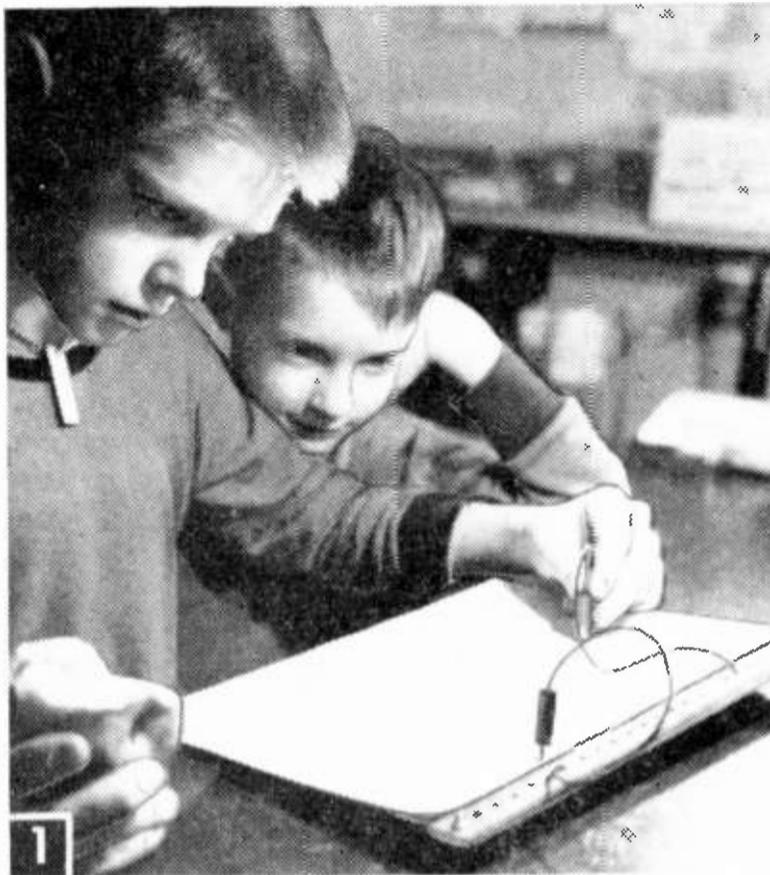

1 A project that youngsters will want to undertake—and simple enough so that they can—the Electrical Right-Wrong Game is both entertaining and educational.

THIS game can be constructed and assembled, complete with a number of question-answer sheets in a single evening. The only tools required are a pair of diagonal pliers, a soldering iron and a screwdriver. But before more is said about the construction of this interesting game, a few illustrations will help to bring out the principle of operation and the idea behind it.

Figure 2 is the circuit for a battery and flashlight bulb short circuit tester. If the banana plugs are touched together, the bulb lights. In effect you turn on a switch when you allow the plugs to touch. If you allow both plugs to touch a copper wire (or any other good conductor of electricity), the bulb will also light. The conductor becomes a part of a switch which controls the light bulb.

Now, visualize a board with six jacks connected as shown in Fig. 3. Suppose each jack is labelled on the left with a problem and each jack on the right with the corresponding answer. If you insert one plug of the short tester of Fig. 2 in the 2-plus-1 jack and the other plug in the 3 jack, the bulb will light. But, if you insert the second plug in the 7 or the 12 jack, the bulb will not light. Similar observations apply to the two pairs of jacks.




Going a step further, and changing the wir-

ing sequence of the jacks to that shown in Fig. 4, you have a simple three-question Right-Wrong Game.

But we want to make it possible to vary the questions. This is done by preparing removable sheets with a varied menu of problems and questions. To change the questions, you simply change the problem sheet. Still, the game would become dull—

even for a child—with only three problems, because he would soon memorize the board arrangement. This means that there should be at least 12 questions instead of the original three. This would require 24 jacks, and construction of the game could become expensive as well as time consuming. Here's where perforated Masonite board comes in. It has holes spaced 1 in. apart that are just the right size for radio banana plugs.

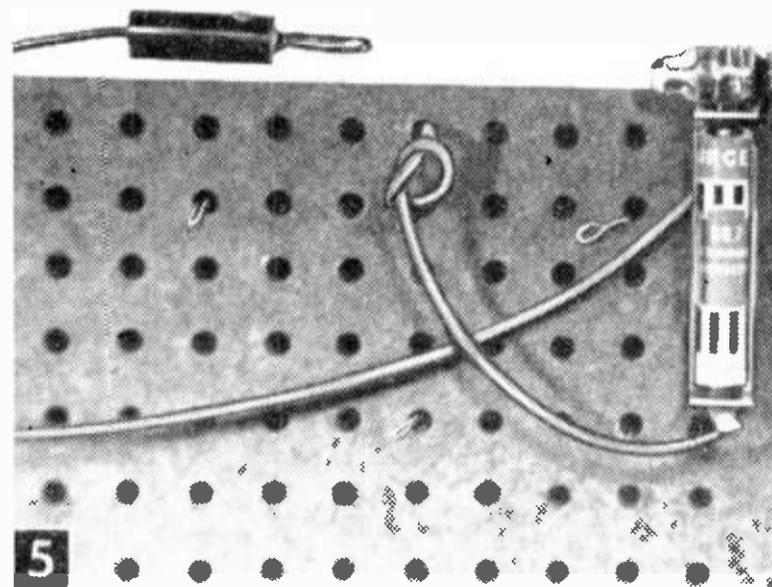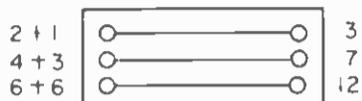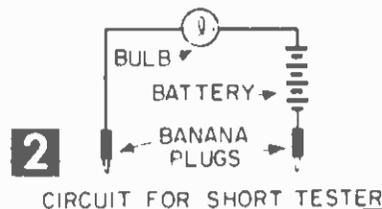To prepare the board, rule it off with nine holes to each square. Then choose a wiring sequence that uses the upper left hand hole in each square for the connection. Use #28 dcc magnet wire for the wiring, pushing the insulation back so that about 1½-in. of wire is bared at each end. Double the wire back over itself and insert through the appropriate holes. Bend the wire over in back to hold it



5 Short checker (indicator of right answers) mounts on the back of the board with bulb visible from front.

$4+7$	$7\sqrt{140}$	$31+26$	30	13	$\frac{39}{4}$
12×3	9×8	$\frac{7}{2} + \frac{3}{4}$	$\frac{17}{4}$	36	20
$6+2$	$3+4+6$	$12 + \frac{2}{3}$	11	8	$\frac{38}{3}$
6×2	$(9+6) \times 2$	$9 + \frac{3}{4}$	72	12	57

SAMPLE Q-A SHEET


MATERIALS LIST—RIGHT-WRONG GAME	
No. Req'd	Description
2	perforated Masonite sheets $7\frac{1}{2} \times 11\frac{1}{2}$ " (Lafayette ML-81)
2	insulated banana plugs (Lafayette MS-209)
1	battery holder (Lafayette MS-137)
1	type 112 flashlight bulb
(Use flexible hook-up wire for short tester leads)	

mounted on the back of the board with its bulb extending far enough above to be visible from the front. The bulb's brass threading is soldered to the terminal of the battery holder, a wire lead is soldered to the center contact of the bulb. Note that the leads pass through perforations to emerge at the top of the board. The knots in the wire leads prevent strain on the soldered connections.

in place. It is important to have bare copper wire against the side of the hole so that the banana plug will make contact with it.

Next, bolt another perforated Masonite to the first to form a double thickness. This holds the wiring in place and conceals the wiring sequences. Be sure that holes are clear of cross wiring before you tighten the bolts. Now the switch circuit is in order, and the mounting of the short checker of Fig. 2 will complete the electrical work for the game. Figure 5 shows the short checker

Make problem sheets by fastening a sheet of paper to the front of the board with cellophane tape. Use a pencil to punch the paper from the rear of the board where the active holes are apparent from the wire ends (see Fig. 5). After the holes are punched, rule off the sheet. Then enter the questions and correctly placed answers on the sheet (see Fig. 6). If you want to make a 30-question game, use two sets of perforated boards.

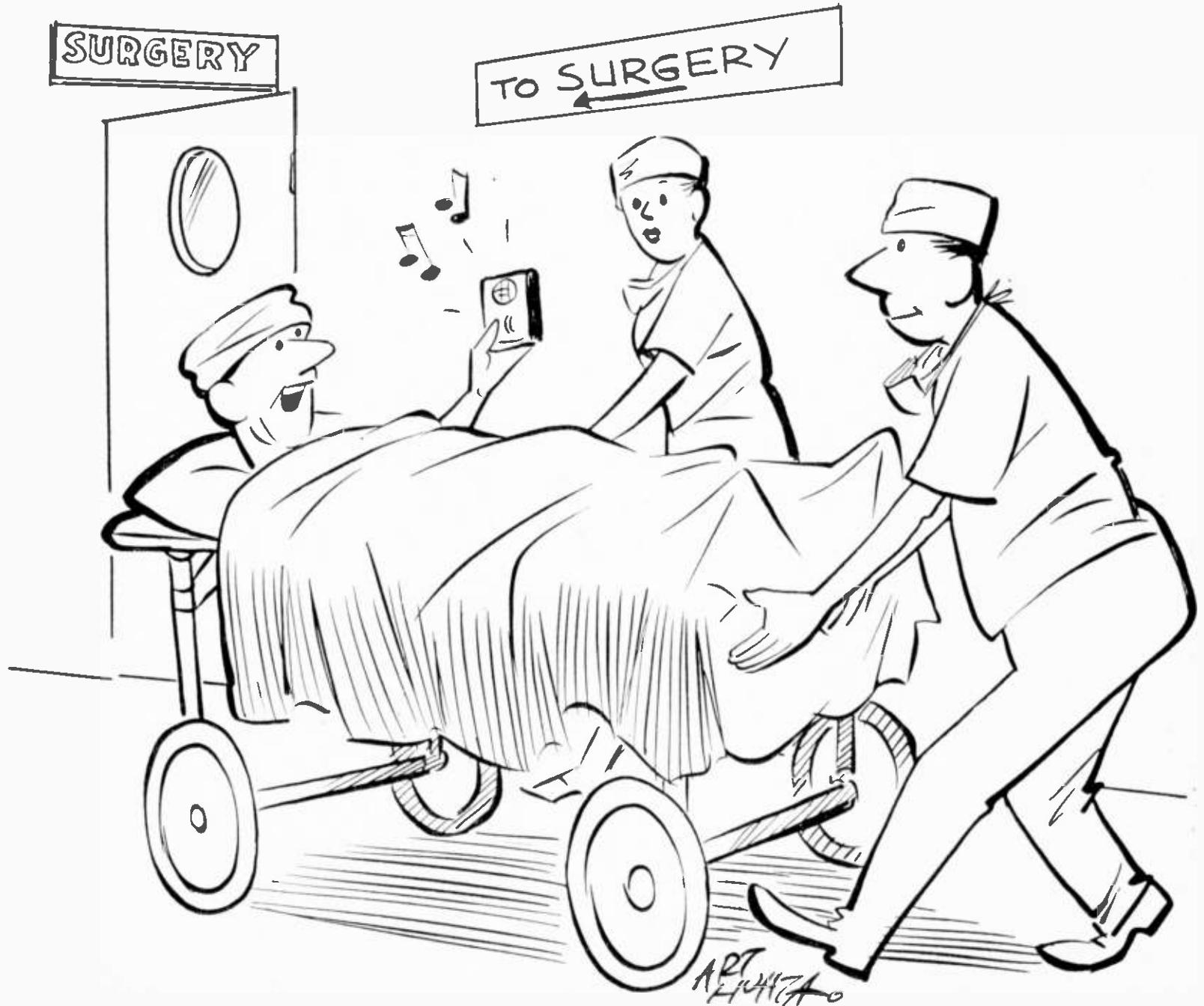

"I always go to sleep with music."

Low Voltage Power Supply

This low voltage power supply is useful for testing transistor circuits, small motors and relays


By FORREST H. FRANTZ, SR.

THE experimenter's instrument inventory is incomplete without a variable low voltage power supply. This unit will supply 0 to 8 v. dc or 6 v. ac. The cost of parts is less than \$10, and the unit may be constructed in a few hours. The saving in battery costs and the versatility afforded by a variable control readily compensate for the cost and effort involved in the construction.

Converting ac line voltage to dc voltage involves two basic tasks: rectification and filtering. These are done after the transformer has set the voltage level.

In Fig. 2, A is ac from the transformer (represented by the sinusoidal wave), B is the polarized, but pulsating dc after rectification and C is the non-pulsating dc after filtering.

The filter in Fig. 2 consists of an inductance and a capacitance. The inductance is series connected in one of the power supply legs and introduces inertia into the circuit to smooth the voltage just as a flywheel smooths energy impulses from an engine to a rotating shaft. The capacitor (C1) action is similar to that of a spring in that it alternately stores and releases energy. The capacitor charges when voltage is increasing and discharges when voltage is decreasing or zero. Although the filtered voltage may not appear a straight line scope trace after filtering, it will be smoothed considerably (C in Fig. 2). The

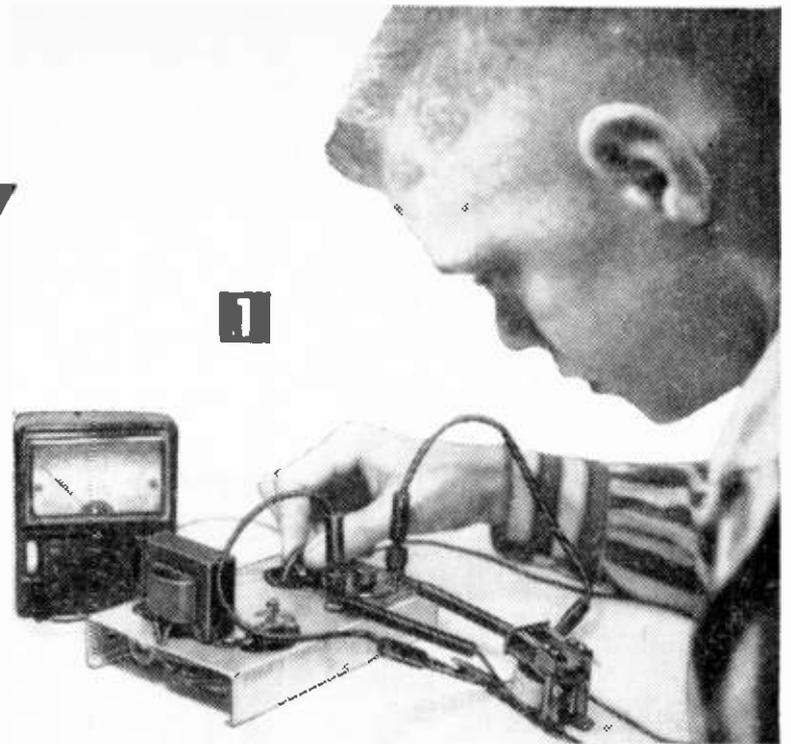


The low voltage power supply being used to determine operating voltage of a relay.

output voltage would be a straight line if filtering action were perfect.

It was previously noted that the transformer sets a basic level. If the output level of the power supply is to be varied, the variable voltage divider scheme shown in Fig. 2 can do the job. The capacitor C2 provides additional filtering.

These features are apparent in the experimenter's inexpensive power supply, although some novel features have been incorporated in the circuit (Fig. 3). A 6.3 v. filament transformer (TRANS) sets the basic voltage level. A Sylvania 2N307 power transistor (T1) is employed as a rectifier by connecting the base and collector terminals together. This arrangement provides an efficient low voltage, high current rectifier. The heavy, expensive choke of Fig. 2 is eliminated, and a large but relatively inexpensive filter capacitor C1 performs the first filter action. R1, R2 and C2 provide additional filter action for the voltage applied to the base of T2.

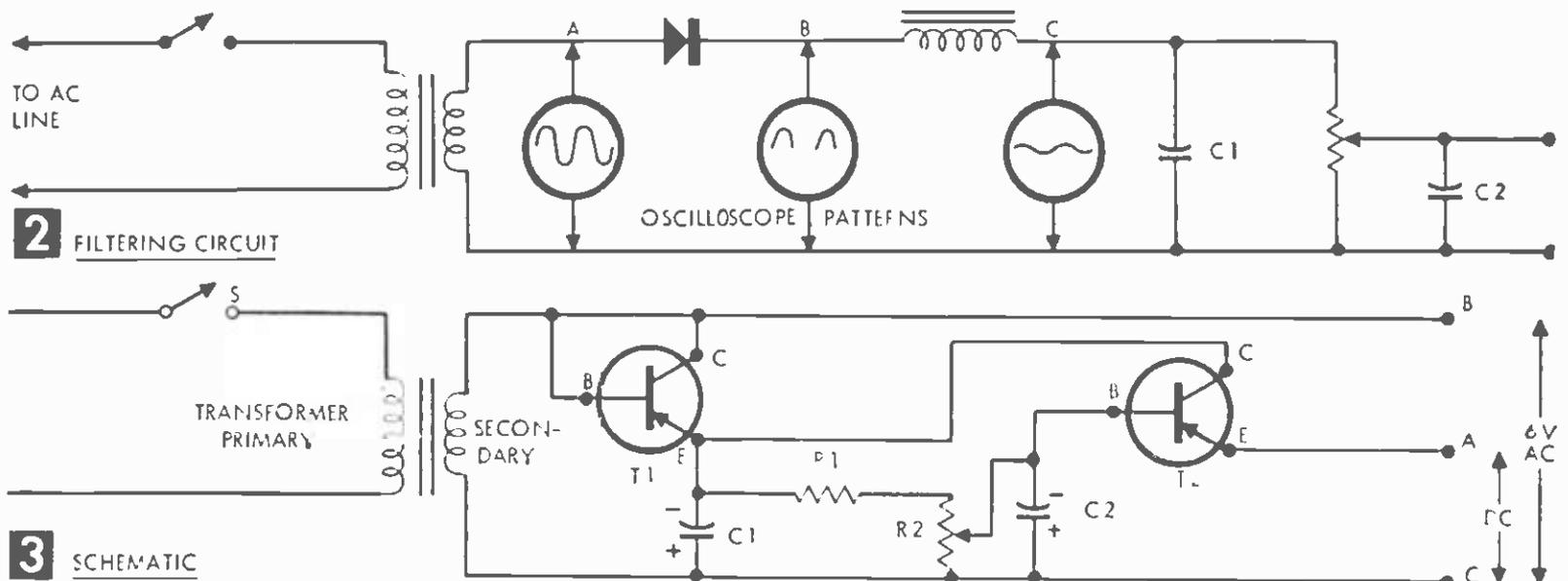
T2 is connected in an emitter follower cir-



Adapting Meters for Test Equipment

How to provide built-in volt-milliammeters
in test equipment

By W. F. GEPHART

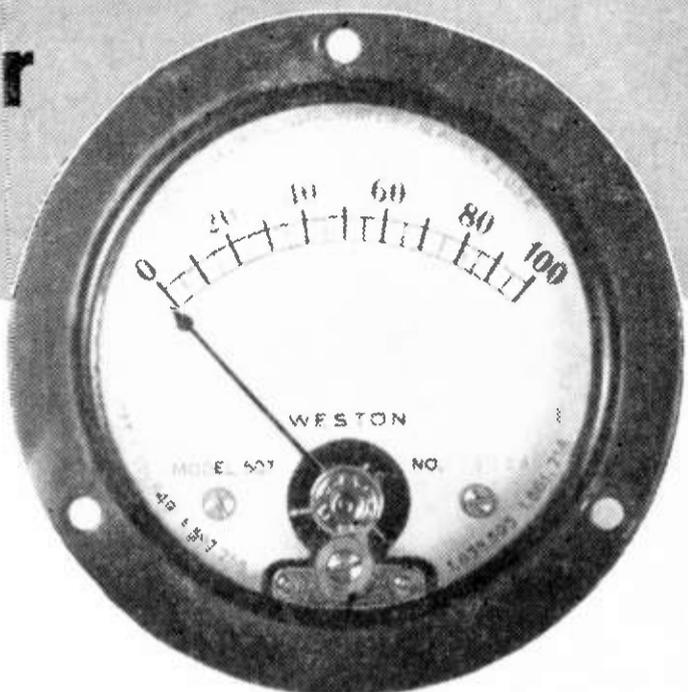

The surplus meter (above) is adapted for specific ranges (below) with the resistors shown.

IN BUILDING test equipment, such as power supplies, oscillators, and so on, it is often desirable to include a built-in meter to measure output voltages and currents. This usually involves providing the correct shunt and multiplier resistances and re-calibrating the meter dial.


The minimum current that will give full-scale deflection on a meter is referred to as the basic movement. For most purposes, a 0-1 ma. basic movement is satisfactory, although higher or lower values can be used. The lower values are more expensive, and the higher values will draw more current from the circuit. Since any directly-connected meter draws current, there may be a slight variation in the output voltage of a circuit when a meter is connected or disconnected. For that reason, meters should be left in the circuit at all times when critical work is involved.

Many surplus meters are available that can be used for test equipment. If the basic meter movement is not known, it can be determined accurately with a precision resistor, vacuum tube voltmeter and a variable voltage source, as shown in Figure 2A. The voltage is adjusted to give full-scale deflection on the meter, and the voltage drop across the resistor is measured. By knowing the value of the resistor and the voltage drop across it, the current through it (hence, through the meter) can be determined by:


(Formula 1)

$$\text{full scale } (I_d) = \frac{\text{voltage drop across resistor}}{\text{value of } 1\% \text{ resistor}} \times \text{current}$$

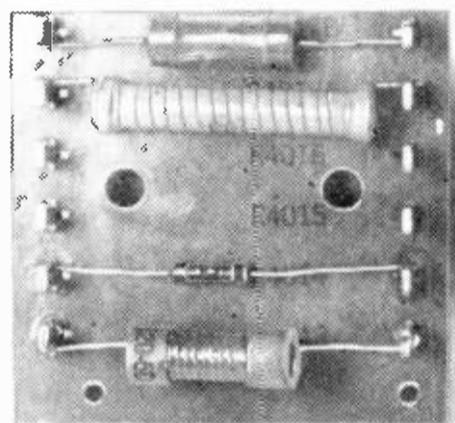To determine proper voltage multiplier and current shunt resistances, the internal resistance of the meter must be known. This data is usually not furnished with meters, but can



B

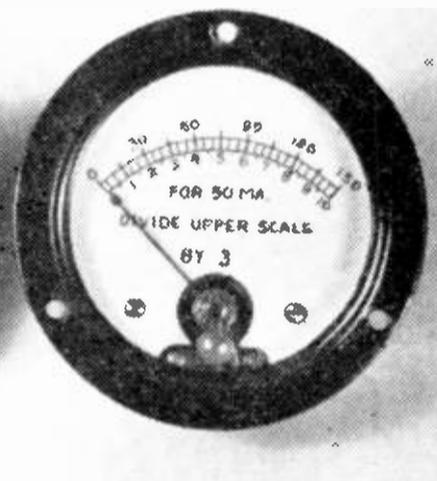


be determined as shown in Fig. 2B. With the switch open, the voltage is adjusted to give full-scale deflection on the meter. (Unless extremely small voltages are available, a dropping resistor will probably be required.) Then the switch is closed, and the resistance adjusted to give exactly half-scale reading (without altering the input voltage). The value of the resistance in the circuit is then equal to the internal resistance of the meter, which will be referred to as R_i . By knowing the full-scale deflection (I_d) and the internal resistance (R_i), the voltage rating of the basic meter can be determined by:

$$\text{(Formula 2) meter voltage rating } (E_m) = I_d \times R_i$$

The meter voltage rating is always very small, and to provide for measurement of the voltages normally used, a voltage multiplier resistor (R_m) must be connected in series with the meter (Fig. 2C). The voltage drop across this resistor must be the difference between the meter voltage rating (E_m) and the total voltage to be measured (E_t):
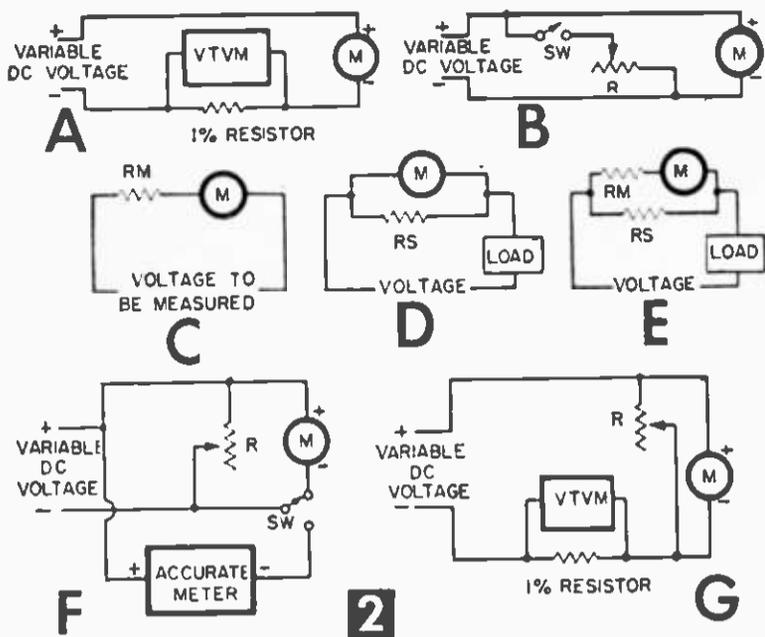
$$\text{(Formula 3) multiplier resistor } (R_m) = \frac{E_t - E_m}{I_d}$$



Schematics (A) for determining the basic meter movement, if unknown, (B) for determining internal resistance of a meter, (C) for determining a meter's voltage rating, (D) showing connection of meter shunt, (E) showing how to increase meter voltage rating by using a multiplier and current shunt, and (F and G) circuits for determining the amount of resistance wire to use in making meter shunts.

Since the meter voltage rating is very small, it can be ignored for higher voltage readings. When E_t is greater than 1000 times E_m , use this formula:

$$\text{(Formula 4)} \quad R_m = \frac{E_t}{I_d}$$

Current shunts are resistors that bypass all current in excess of the basic meter's range, to permit measurement of higher currents, and are connected as shown in Figure 2D. The value of a current shunt (R_s) to read a maximum current of I_t is:

$$\text{(Formula 5) shunt resistor } (R_s) = \frac{E_m}{I_t - I_d}$$

Where the value of I_t is greater than 100 times I_d :

$$\text{(Formula 6)} \quad R_s = \frac{E_m}{I_t}$$

In applying these formulas for high current values, quite often the shunt resistor will be a small fraction of an ohm. It is sometimes easier to increase the meter voltage rating (E_m) by the addition of a multiplier, and then connect a current shunt across both the multiplier and meter, as shown in Fig. 2E. Using Formula 3 to determine a suitable multiplier resistor, and to establish an E_t , the value of the shunt for the combination resistor and meter can be determined by using Formula 5 or Formula 6, substituting the new E_t for the E_m in these formulas.

It will be found that voltage multiplier resistors will usually be values that are readily obtainable in 1% precision resistors, but that current shunts are often low, odd values. Sometimes it is desirable to wind your own


low-value current shunts, using resistance wire, and a small rod or miniature coil form. The exact length of resistance wire can be obtained by either of the circuits shown in Figures 2F and 2G. Solder one end of the wire to one end of the form, and fasten this end to one meter terminal. Run the wire through a screw-type binding post which is connected to the other side of the circuit (the switch in 2F or the other side of the meter in 2G). Have only a short section of wire at the start, and adjust the voltage to set up the desired current in the circuit, as determined by the accurate meter in 2F (with switch "down") or by the voltage drop across the resistor in 2G. Then, by adjusting the length of the wire (turning the voltage off and tightening the binding post screw each time), the exact resistance required to give full-scale reading with the desired current can be found. The wire can then be wound around the form and soldered at the other end to give the proper low-resistance shunt.

To illustrate the use of these formulas, assume we have a meter with a basic movement of 0-1 ma., and we have determined the internal resistance to be 50 ohms. With I_d .001 amp. and R_i 50 ohms, we find, substituting in Formula 2,



$$E_m = I_d \times R_i$$

$$E_m = .001 \times 50 = .05\text{v.},$$

Assume we want to make this meter read

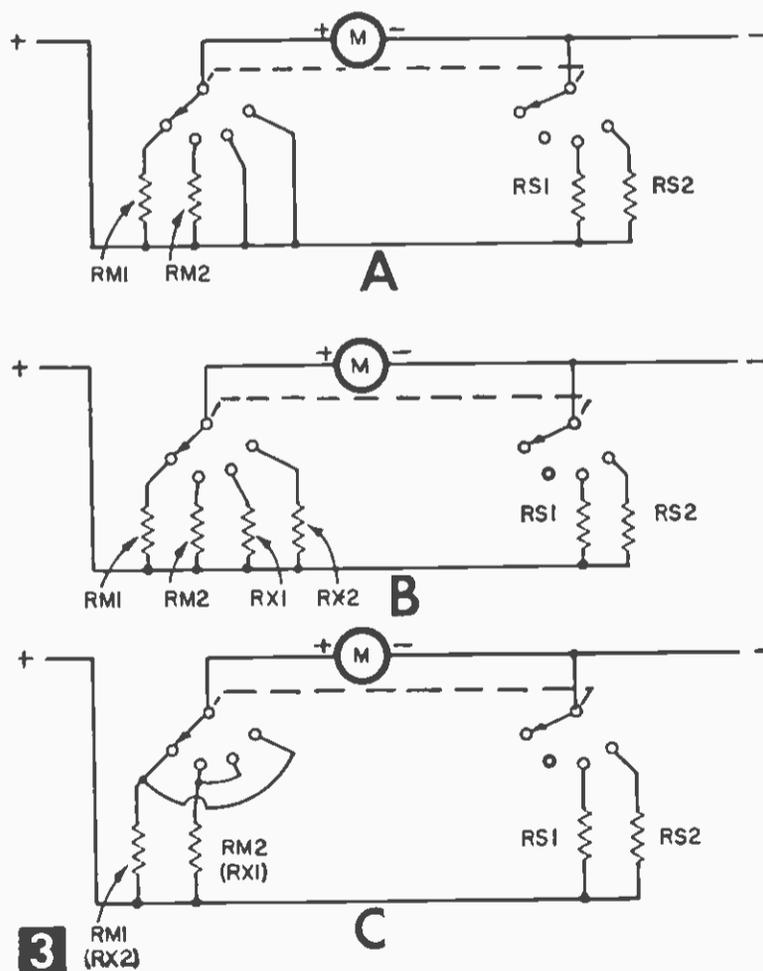

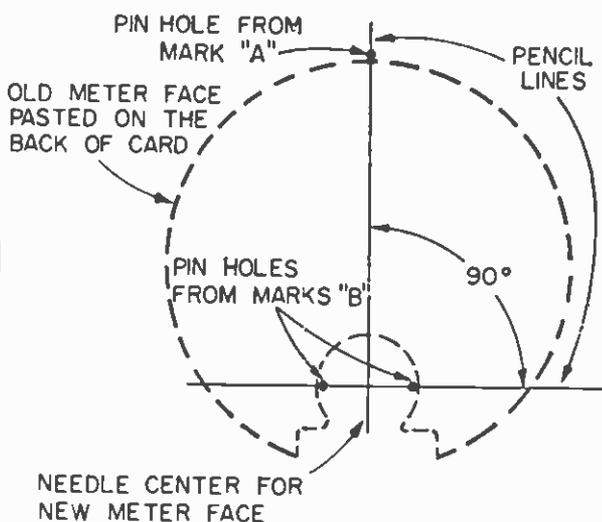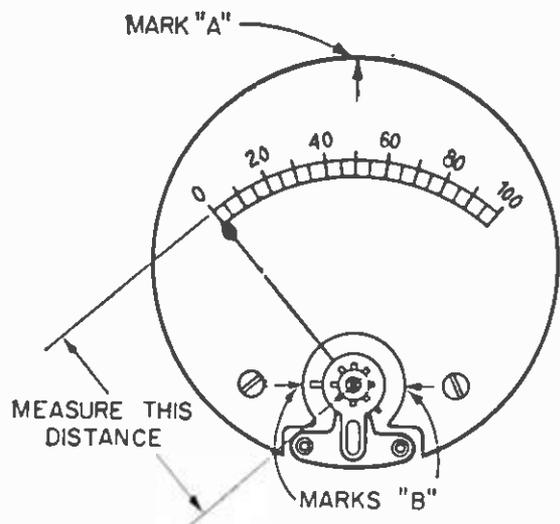3 Means of switching various multipliers and shunts into meter circuits: (A) when only multipliers and shunts are used, (B) for extending the voltage rating by using special multipliers, and (C) for extending voltage by using the voltage multipliers themselves.



4 **A** MARKING METER FACE

How the radius and length of the meter scale can be transferred to the card stock pasted on the back of the dial plate.

0 to 10 v., 0 to 150 v., 0 to 50 ma., and 0 to 150 ma. To get the multiplier for the 10-volt scale, applying Formula 3:

$$R_m = \frac{E_t - E_m}{I_d}$$

$$R_m = \frac{10 - .05}{.001} = \frac{9.95}{.001} = 9950 \text{ ohms}$$

Since 150 v. is more than 1000 times the E_m of .05 v., Formula 4 is used for the 150 v. multiplier:

$$R_m = \frac{E_t}{I_d}$$

$$R_m = \frac{150}{.001} = 150,000 \text{ ohms}$$

For the 50 ma. shunt, applying Formula 5:

$$R_s = \frac{.05}{.050 - .001} = \frac{.05}{.049} = 1.02 \text{ ohms}$$

This is an odd value, but the use of 1 ohm would only give a 2% error, so it could be used.

Since 150 ma. is more than 100 times the I_d of 1 ma., Formula 6 can be used for the 150 ma. shunt:

$$R_s = \frac{E_m}{I_d}$$

$$R_s = \frac{.05}{.150} = .33 \text{ ohm}$$

Since this is a fractional value (that could be wound or secured by connecting three 1 ohm resistors in parallel), it might be well to see what value would be obtained in combination with the multiplier resistors we have calculated for the two voltage ranges. Applying Formula 6 again, using E_t 's (total voltages) of 10 and 150 v. instead of E_m (meter voltage ratings), we substitute as follows:

$$R_s = \frac{10}{.15} = 66.67 \text{ ohms}$$

$$R_s = \frac{150}{.15} = 1000 \text{ ohms}$$

B ESTABLISHING NEW NEEDLE CENTER POINT

If it doesn't seem practical to wind the .33 ohm shunt for this range, the best method would be to measure the 150 ma. current with a 1000 ohm shunt across the meter and multiplier used for the 150 volt range, wired as in Figure 2E.

The means of switching various multipliers and shunts into the meter circuit are shown in Figure 3. In 3A, where only multipliers and shunts are used, the multipliers are on the left and the

shunts on the right. In 3B, the voltage rating of the meter is extended by special multipliers (R_{x1} and R_{x2}) to get more reasonable values for shunt resistances. In 3C, the voltage multipliers themselves are used for the same purpose, similar to the case above, where it was possible to use the 150 v. multiplier in conjunction with a reasonable value 150 ma. shunt.

After determining the resistance values and switching circuit to be used, there remains only the matter of recalibrating the meter dial. The primary problem here is transferring the length and radius of the original scale to a new face. The new face may be made on a piece of light card stock glued to the back of the metal dial plate of the meter, mounted on the meter, reversed. Figure 4 shows how the radius and length of the meter scale can be transferred to the card stock pasted on the back of the dial plate.

Before removing the dial plate from the meter body, make three marks on the front of the dial, as shown in Figure 4A. The mark "A," at the top of the plate, should be in line with the center of the existing scale and the needle pivot point. The other marks ("B") should be on either side of the pivot point, making an imaginary line through the pivot point, at right angles to the line to mark A. The distance from the needle pivot to the outer line of the scale is measured, and a pair of dividers set to the distance between major markings (usually tenths) of the existing scale. The dial plate is then removed from the base, and a white index card is glued to its back.

When the glue has dried, carefully punch a small needle hole through the card at points A and B, right up against the plate. Turn the card over and draw a line between the two B needle holes, and another line at right angles to the first line, from the A needle hole, as shown in Fig. 4B. The intersection of these

lines will be the needle pivot point. Using the distance measured, an arc can be swung from this point, giving a new scale. The center of the new scale will be where it crosses the line from needle hole A, and from this point the limits of the scale can be determined by stepping off the proper number of spaces with the preset dividers. Once the scale length and radius has been established, it can be divided into any convenient divisions, according to the value represented.

In the finished meter shown in Figure 1, the main scale is divided into ten parts, and each tenth is divided into thirds. This scale

is used for 150 v. and 150 ma. ranges, and can be used for the 50 v. range by dividing readings by 3. A secondary scale is set below, divided into tenths, for the 10 v. range. Between each tenth mark, there is a small mark down from the major scale, so this scale for the 10 v. range can be read to .5 v.

The resistor board shown beside the finished meter in Figure 1 is a convenient means of mounting multiplier and shunts. It fastens to the back of the meter, the two large holes fitting over the meter terminals. The bottom resistor is a .33 ohm, wound on a uhf coil form.

Radio Hobbyist Anagram

How good is your radio-electronics word vocabulary? This anagram puzzle will put your radio lingo to the test. Many of the words, terms, and abbreviations

have something to do with radio parts; others with circuits or tools used for making repairs or building circuits. Solution on page 142.

By JOHN A. COMSTOCK

ACROSS

- 1) Wire wound on an insulator form.
- 3) This type circuit can, and often does, blow fuses.
- 8) Captures passing radio waves from the atmosphere. Also, may transmit radio waves into the atmosphere.
- 9) Electronic switch controlled by current.
- 10) A group of radio frequencies.
- 14) Amateur radio operator.
- 15) Electron coupled oscillator (abbr).
- 18) Used for soldering.
- 19) Most radio parts give off — — — —.
- 22) Meaning to cut the top off a radio wave as done in a noise-limiter circuit.
- 23) The organization that regulates radio transmission in the United States.
- 25) Device used to measure current, voltage, power, etc.
- 27) Electromotive force (abbr).
- 28) Automatic volume control (abbr).
- 29) Voltage regulator (abbr).
- 30) The effect of capacitance to ground at the end of an antenna.
- 31) The — — — — on which all radio parts are mounted is called the chassis.
- 32) Broadcast (abbr.)
- 34) A conductor used


- to carry electric current from point to point.
- 36) Continuous wave (abbr).
- 37) Television interference (abbr).
- 39) Pole on which an antenna or aerial is mounted.
- 41) Movable iron core of a coil.
- 42) Unit of length equal to 1,000th of an inch.
- 43) A bulb.
- 46) A two-element vacuum tube.
- 47) A vacuum tube or


transistor and all other parts necessary to make up a circuit having one input and output.

DOWN

- 1) Something that flows in electronic circuits and wires.
- 2) A length of wire.
- 3) Switch (abbr).
- 4) A circuit that is not continuous.
- 5) Connection to a coil or resistor.
- 6) Electrical discharge through the air.
- 7) Unit of capacitance.

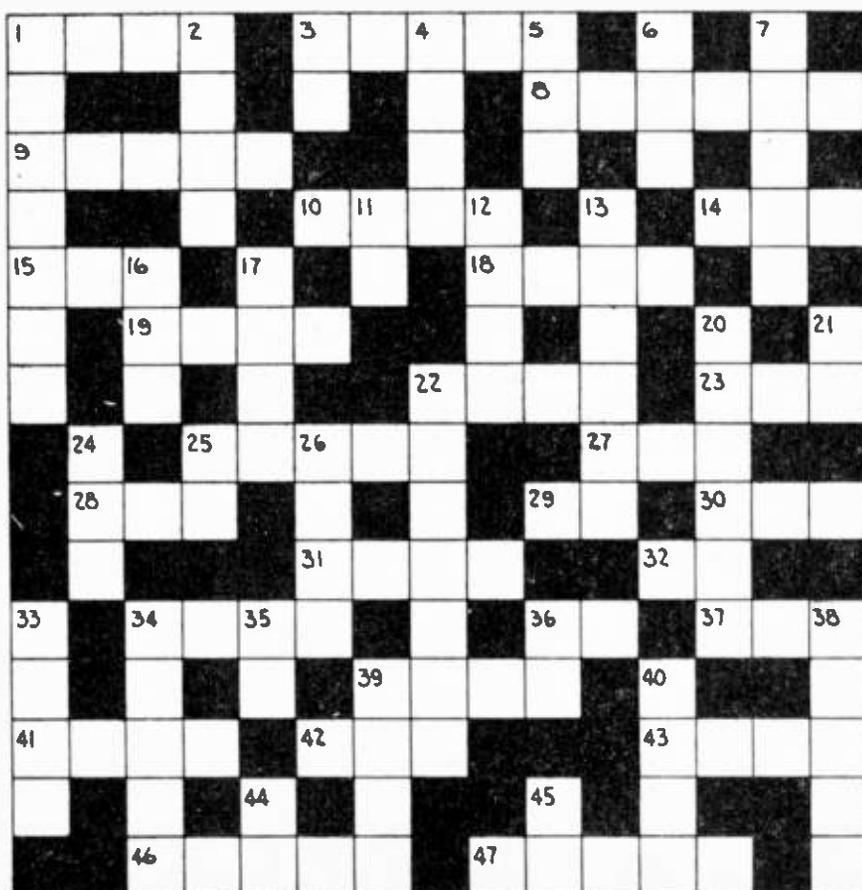- 11) Alternating current (abbr).
- 12) Used to select stations.
- 13) Metal used in wires.
- 16) Unit of resistance or opposition to current flow.
- 17) Often used to insulate bare wire splices.
- 20) The Edison — — — — is the flow of negative particles of electricity (electrons) between the cathode and plate in a vacuum tube.
- 21) Direct current (abbr).
- 22) Some part used in a crystal radio set.
- 24) Part of an antenna array.
- 25) Megacycle (abbr).
- 26) In the year 1904, Alexander Fleming invented the diode vacuum — — — — detector.
- 33) Circuit protector.
- 34) Wire — — — — on a suitable insulated form is called a coil.
- 35) Radio frequency (abbr).
- 36) Center tap (abbr.)
- 38) The control grid is the — — — — element of a vacuum tube.
- 39) Short for microphone.
- 40) A type of wire connector.
- 44) Power output (abbr).
- 45) Vacuum tube (abbr).



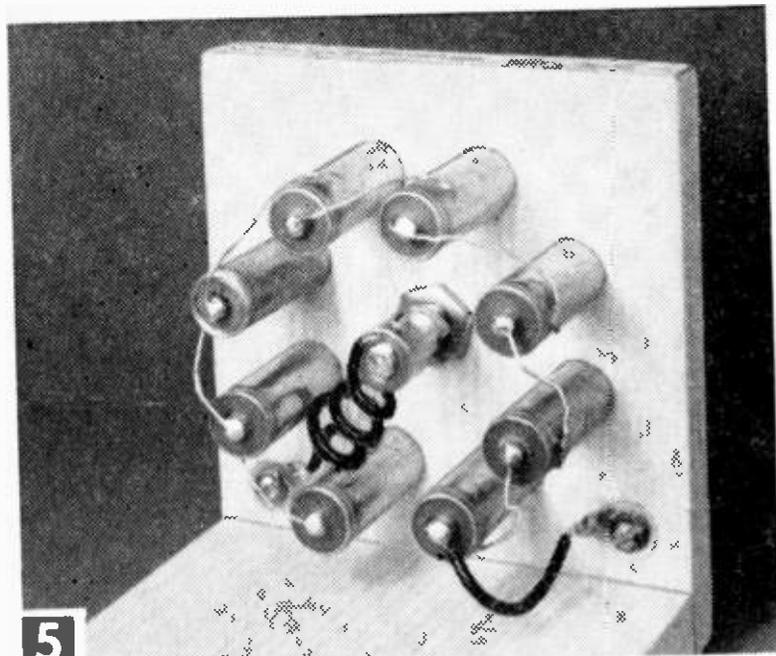

5 Flexible pigtail lead to end of switch assures reliable contact. A more rigid wire soldered to bearing might deliver unstable voltage due to corrosion between bearing and shaft.

MATERIALS LIST—DC POWER SUPPLY


No. Req.	Size and Description
1 pc	$\frac{1}{2}$ x 4 x $4\frac{1}{2}$ " hardwood for panel
1 pc	$\frac{1}{2}$ x 3 x 4" hardwood for base
8	AA flashlight cells
2	binding posts
1	brass $\frac{1}{8}$ -pipe nipple 1" long, threaded full length (available at electrical parts dealers)
2	brass $\frac{1}{8}$ -pipe hexagon nuts, to fit nipple
1	$\frac{1}{4}$ x $2\frac{1}{2}$ " brass rod, threaded one end with $\frac{1}{4}$ "-20 N.C. die
1	radio knob with $\frac{1}{4}$ " socket (2 setscrews preferred)
1 pc	$\frac{1}{32}$ x 1 x 2" brass or hard aluminum
1	$\frac{1}{4}$ "-20 N.C. brass hexagon nut
1	compression spring about $\frac{3}{4}$ " long, to fit $\frac{1}{4}$ " shaft
1	collar with setscrew, to fit $\frac{1}{4}$ " shaft (see text)
1	$\frac{5}{8}$ " O.D. washer to fit $\frac{1}{4}$ " shaft
2	washers to fit binding post screws
2	soldering lugs to fit binding post screws
2	flathead or ovalhead wood screws about $1\frac{1}{4}$ " long
	24" hook-up wire (insulated), solder, soldering paste

The Rotary Switch. Assembly shown in Fig. 3 includes a 1-in.-long bearing of brass $\frac{1}{8}$ -pipe nipple having a bore of slightly over $\frac{1}{4}$ in. Mount the nipple securely in the $\frac{3}{8}$ -in. hole, using two brass hexagon nuts.

Cut the metal rotary-switch blade from brass or hard aluminum about $\frac{1}{32}$ -in. thick, then bend and drill as shown in Fig. 4. Make the right-angle bend on the end of the blade with a slant; this gives the blade a wider sweep which prevents the contact edge from wearing a groove in the soft metal ends of the cells.

Clamp the blade on threaded end of $\frac{1}{4}$ x $2\frac{1}{2}$ -in. brass shaft, securing it between a brass hexagon nut and a radio knob (Fig. 3), then slip the shaft into the bearing. Over the free end of the shaft, slip a $\frac{5}{8}$ -in. O.D. metal washer having a hole slightly over $\frac{1}{4}$ in.; a $\frac{3}{4}$ in.-long compression spring and a collar with setscrew. Adjust the collar against the spring for proper tension on the switch blade.

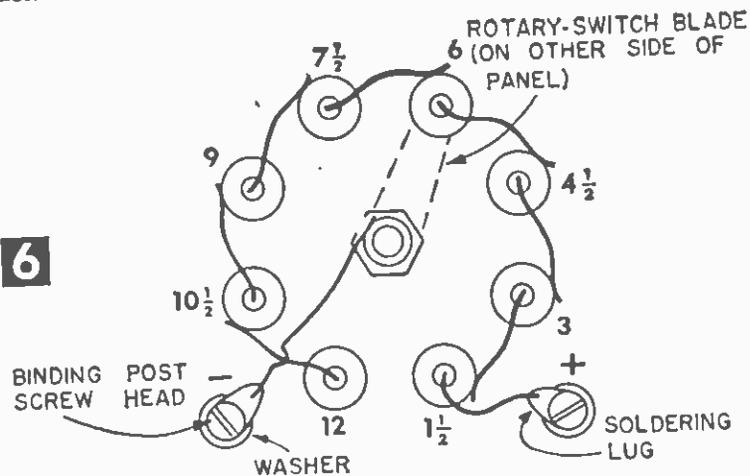If you have difficulty in obtaining the collar, you can buy a brass coupling made for joining two $\frac{1}{4}$ -in. shafts for about 15¢ at radio parts houses; then saw it in half. Or, as a sub-



stitute, simply thread the end of the shaft with a $\frac{1}{4}$ "-20 N.C. die and tighten two hexagon nuts against each other.

Paper labels do not have to be removed from the cells as shown in Fig. 5. You need only scrape off enough around the bottoms to push the batteries into the holes and leave some of the metal jacket exposed for direct soldering of wire leads. If labels are the "leakproof" type with plastic top, foil and waxpaper tube and metal disc bottom, remove bottom half with a sharp penknife blade.

Wiring Up. Figures 5 and 6 show how cells, switch, and binding posts are wired together with soldered leads. Mount the two binding posts in their $\frac{3}{32}$ -in. holes, using soldering lugs and washers under the screw heads, as shown. If screws that come with the binding posts are too short for the $\frac{1}{2}$ -in. wood panel, replace with longer brass screws.

Looking at the panel from the back, connect the left-hand ("minus") binding post directly to the end of the $\frac{1}{4}$ -in. brass shaft of the rotary switch (Figs. 3 and 5), using a very flexible pigtail lead. Then connect the right-hand ("plus") binding post to the center electrode of the cell nearest to the corner of the panel, using most any insulated or spaghetti-covered wire.



Solder all the cells in series, doing the job as quickly as possible because it doesn't do the cells any good to overheat them in spots. To speed the work cut the wire leads to right length and then "tin" the ends with solder. Scrape cells clean at places where you are going to solder and apply a little soldering paste to the spots. The paste makes the solder "hold" quickly, without overheating.

For the base, use a 3 x 4-in. piece of the same kind of wood used for the panel. Attach panel to base with two flathead or ovalhead wood screws.

When the batteries wear out, you will have to unsolder the wire leads and hook up a new set of cells. However, transistors put such a small drain on the cells that they should last nearly as long as their shelf life.

The soldered joints and the wiping action of the switch blade, which cleans the cell bottoms, assure steady voltages.

Amplifier that Drives Speaker Directly

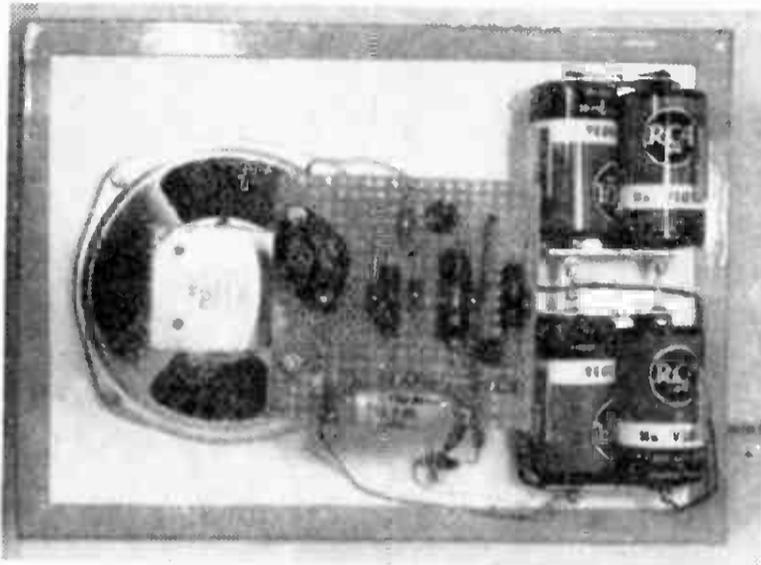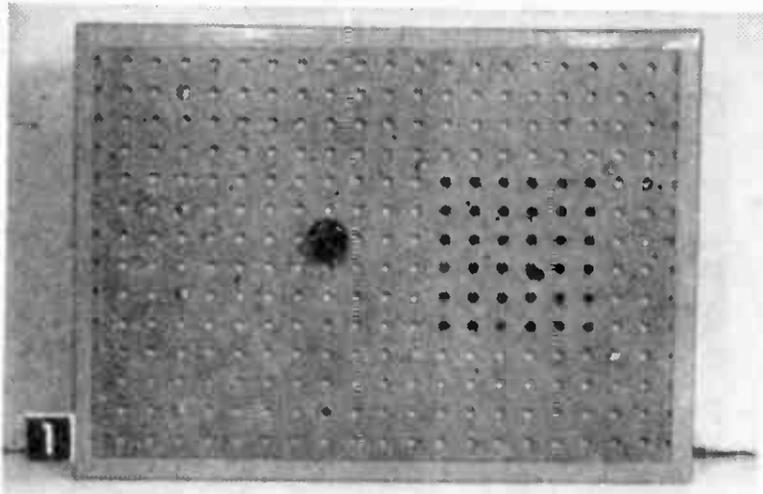

Front (top) and rear of amplifier. Weight saved by omission of output transformer makes unit easily portable.

By FORREST H. FRANTZ, Sr.

THIS transistorized amplifier drives a speaker without an intervening transformer. It may be used as a phonograph or microphone amplifier, with a tuner as the audio end of a receiver. The input may be high impedance or medium impedance. This amplifier uses only 3 transistors and costs under \$15.



The secret of direct speaker drive from a

single low cost power transistor is this: An intercom speaker is used, which has an impedance of 45 ohms—close to the 48 ohm output transformer impedance of the transistor. Thus steady dc flows through the speaker voice coil. The amplified output is a superimposed ac signal. The dc through the speaker voice coil displaces the speaker slightly from its normal center rest position. But this displacement is small.

The output is 50-75 milliwatts. You can get 150 milliwatts by using a 48 ohm to 3.2 ohm transformer such as the AR-503 and a speaker with a 3.2 ohm voice coil.

This heavier (by 3 lbs.) set-up requires mounting the transformer on the back of the panel. The transformer primary leads connect to 2N255 collector and -6 v.; the secondary leads connect to the speaker terminals. Otherwise construction is as outlined below for the direct speaker drive amplifier.

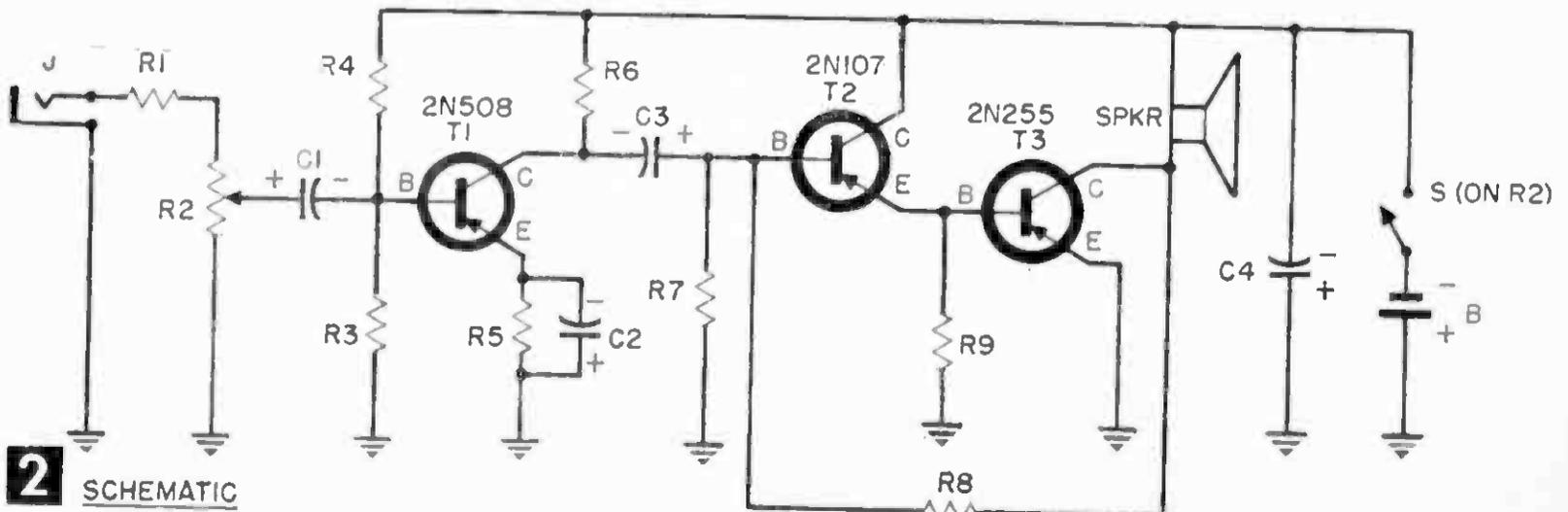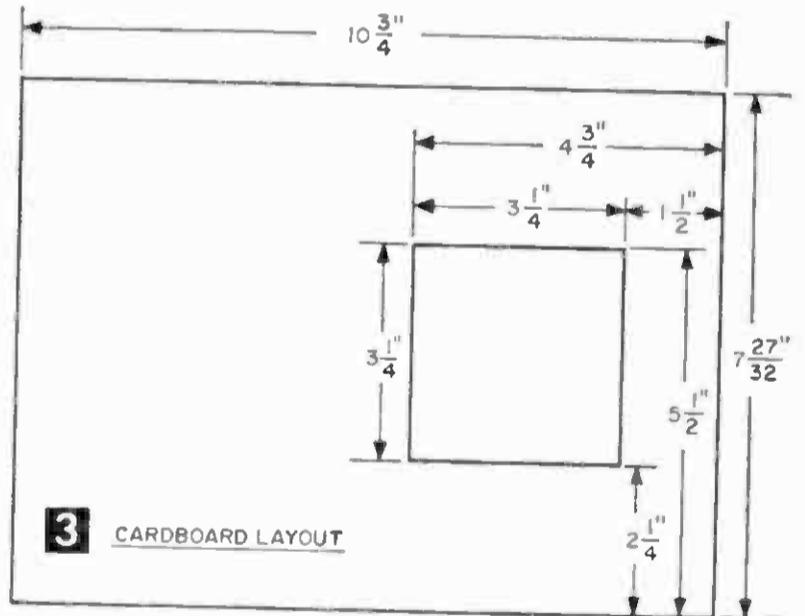
The preamplifier transistor is a high gain pnp GE 2N508 in a common emitter circuit. C2 bypasses ac to keep the emitter at ac ground without affecting the dc stabilization. The preamp output is fed to the driver, a GE 2N107 in a common collector circuit, through C3. This stage keeps the low input impedance



of the 2N255 from overloading the preamp. The driver output from the emitter of the 2N107 is directly coupled to the 2N255. R8 provides dc stabilization and a considerable amount of audio feedback.

As for the amplifier input circuit, the value of R1 depends on the application: If the amplifier is to be used with a crystal mike (Lafayette PA-9) R1 is 27K. For a crystal phono pickup, R1 should be between 27K and 68K.

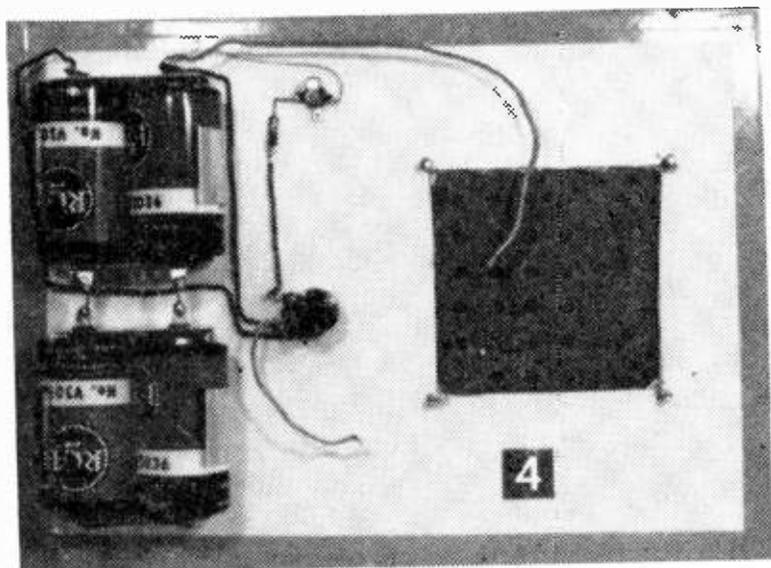If the amplifier is to be used with a vacuum tube tuner, R1 should be 27K to 68K and a capacitor of .1 mfd, 600 v. should be provided in series with the jack and R1 if there's dc across the tuner output terminals. R1 is omitted when the amplifier is used with a




Panel-mounted components in place and wiring done, awaiting speaker and amplifier mounting.


transistorized tuner, and no capacitor is needed if the tuner has a decoupling capacitor in the output circuit. Otherwise, provide a

MATERIALS LIST—AMPLIFIER

R9	270 ohms, 1/2-watt carbon resistor, 10%
R5	1K ohms, 1/2-watt carbon resistor, 10%
R6	4.7K ohms, 1/2-watt carbon resistor, 10%
R7	6.8K ohms, 1/2-watt carbon resistor, 10%
R3	10K ohms, 1/2-watt carbon resistor, 10%
R8	27K ohms, 1/2-watt carbon resistor, 10%
R4	47K ohms, 1/2-watt carbon resistor, 10%
R1	required for certain mike, phono or tube tuner applications (see text)
R2-S	10K volume control with switch (Lafayette VC-28)
C1, C3	30 mf. 6 v. miniature electrolytic capacitor (Lafayette CF-104)
C2	100 mf. 6 v. miniature electrolytic capacitor (Lafayette CF-106)
C4	160 mf. 15 v. miniature electrolytic capacitor (Lafayette CF-127)
T1	2N508 transistor (G E)
T2	2N107 transistor (G E)
T3	2N255 transistor (CBS)
SPKR	45 ohm intercom speaker (Quam 5A1Z45)
J	subminiature jack (Lafayette MS-282)
B	four 1.5 v. size D flashlight batteries, series connected (RCA VSO 36) two double battery holders (Lafayette MS-176) 7 7/32 x 11 7/32 x 1/8 in. perforated Masonite Board (Lafayette ML-181) 3 1/16 x 6 3/4 in. perforated bakelite board, cut to 3 1/16 x 3 1/2" (Lafayette MS-305) miniature knob (Lafayette MS-185) rosin core solder, hookup wire Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y., stocks all parts except the loudspeaker. Allied Radio, 100 N. Western Ave., Chicago 80, Ill., stocks all parts except those designed by Lafayette numbers.

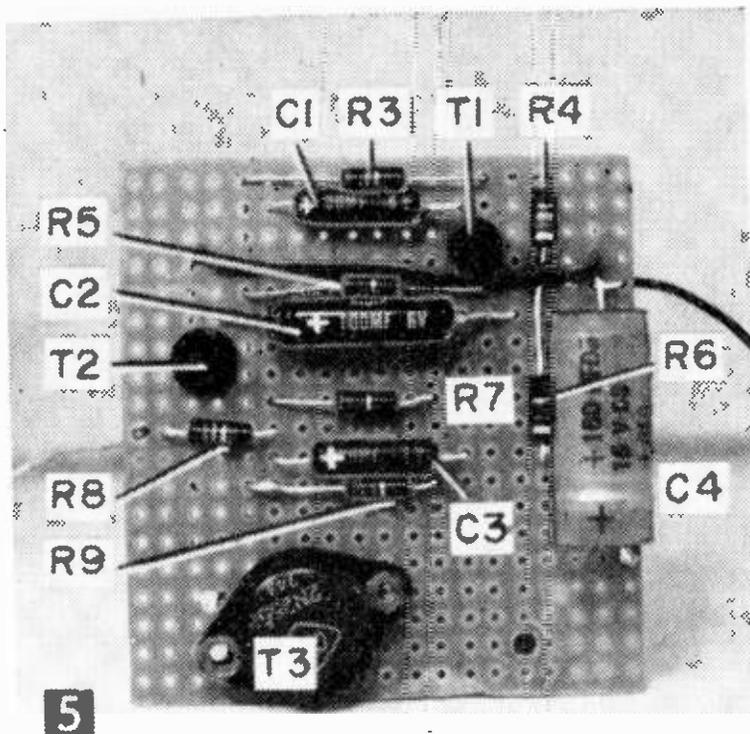

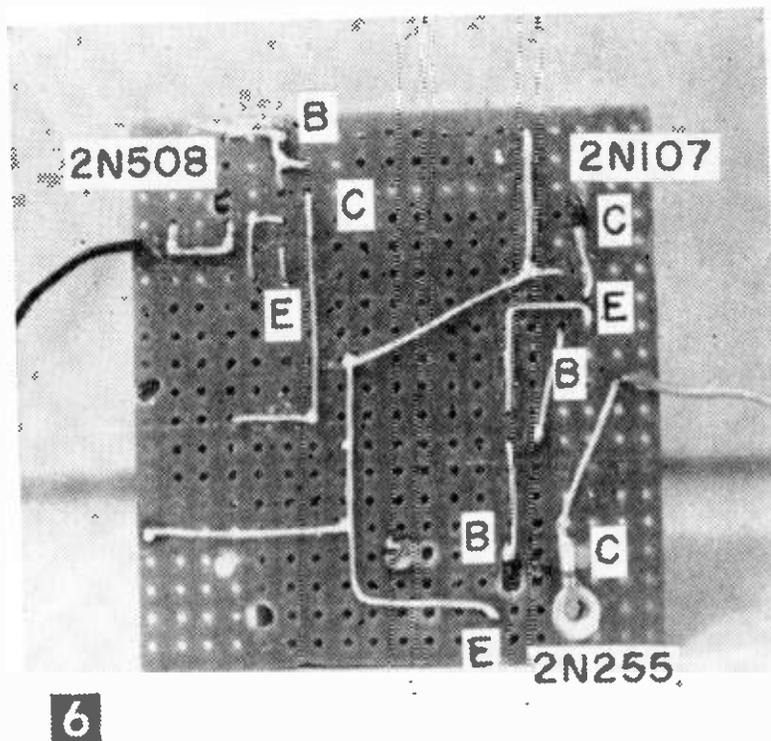
Amplifier parts are mounted on Bakelite piece.



Underside view of amplifier chassis shows wiring.

series coupling capacitor of 10 to 30 mfd with a voltage rating equal to at least 6 v. if the tuner battery is less than 6 v. If the tuner battery voltage is greater than 6 v., select a capacitor with a voltage rating equal to or greater than the tuner battery voltage.

Cut a piece of stiff cardboard according to the layout in Fig. 3. Glue it to the back of the perforated Masonite board (shortened to 10 3/4 in.). The perforations in the Masonite are centers for all of the required holes except 2 speaker holes. Locate these by fastening the speaker on the panel through the two existing holes. The input jack and volume control holes must be enlarged to 1/4 in. dia. Use the front panel view of the amplifier (Fig. 1) as a guide for your layout. After the panel drilling has been completed, fasten the

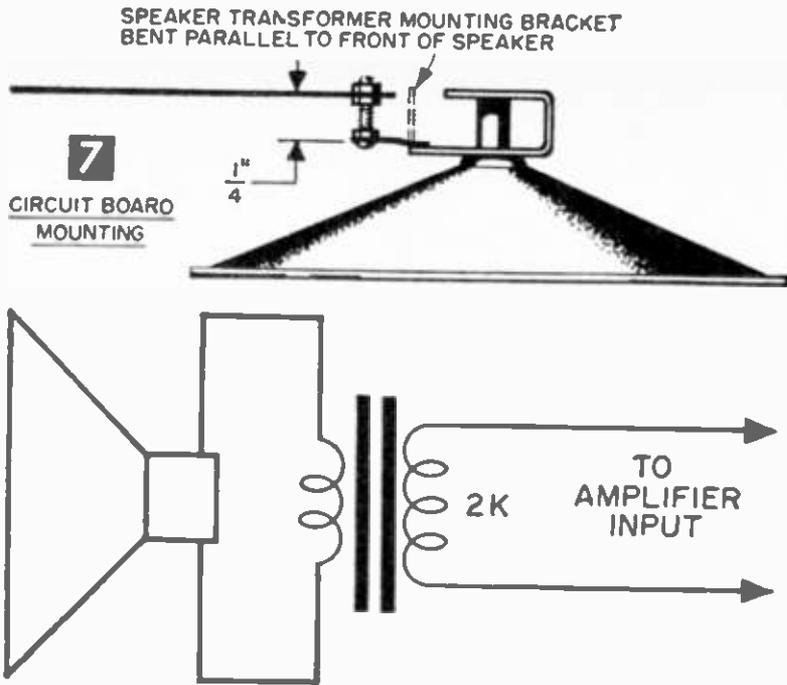

8 MICROPHONE MADE OF LOUDSPEAKER AND OUTPUT TRANSFORMER

battery holders, volume control (with shaft length cut to 1/4 in.) and jack on the panel and wire as shown in Fig. 4.

The transistor amplifier circuit is constructed on a miniature perforated Bakelite board (Fig. 5). Drill three 3/32 in. dia. holes—T3 mounting holes and holes to mount the board on the speaker (one hole does double-duty). The components are wired on the board by pushing the component pigtailed


through the perforations and soldering.

Bend the transformer mounting bracket on the speaker parallel to the front of the speaker. Fasten a 6-32 x 3/4-in. machine screw with a nut in each of the two holes on the transformer mounting bracket. Set another nut on each of these screws so that the circuit board will be supported about 1/4 in. above the bracket (Fig. 7). Make the final connections between the circuit board, front panel wiring and the loudspeaker.

If you want good volume with microphone, use one with an impedance of 1K to 2K. The Shure MC11 (about \$7) is ideal. Or a microphone can be made of a loudspeaker connected through an output transformer (Fig. 9). If either of these microphones is used with the amplifier, omit R1.


Quick Wire Connections

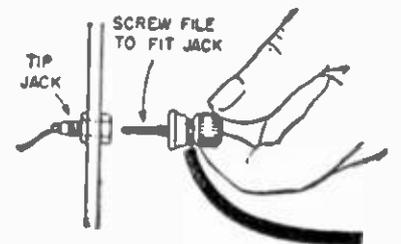• Almost any wire can be quickly plugged into a pin jack in radio and electronics test and experimental work by altering binding post as shown below. Using a binding post with non-removable tops and molded-in screw-shanks (such as made by Eby), simply file the screw-shank to the same diameter as a phone cord tip.—A. TRAUFFER.



TV-RADIO Servicemen or Beginners...

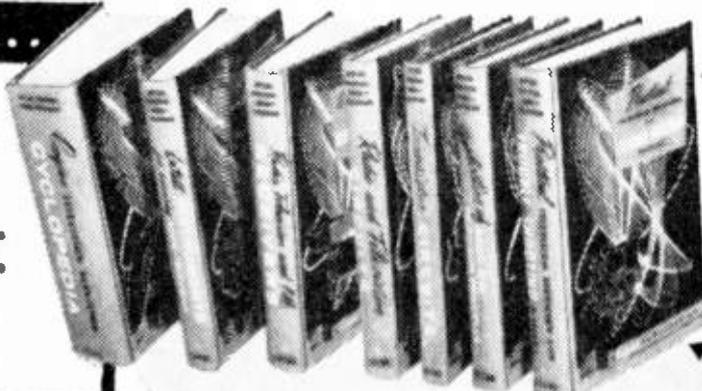Send for *Coyne's* 7-Volume Job-Training Set on 7-Day **FREE TRIAL!**



The First Practical TV-RADIO-ELECTRONICS Shop Library!

Answers ALL Servicing Problems QUICKLY . . . Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."

—Guy Bliss, New York
"Swell set for either the serviceman or the beginner. Every serviceman should have one."—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS; 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. 31-RE, Chicago 7, Illinois

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per offer. Include "Patterns & Diagrams" book FREE!

Name Age

Address

City Zone State


Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

Coyne Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. 31-RE Chicago 7, Illinois

Wind-It-Yourself Brightener

You can make this picture tube brightener in an hour, install it and have plenty of time left to enjoy those late shows on a brighter TV

By GEORGE D. PHILPOTT

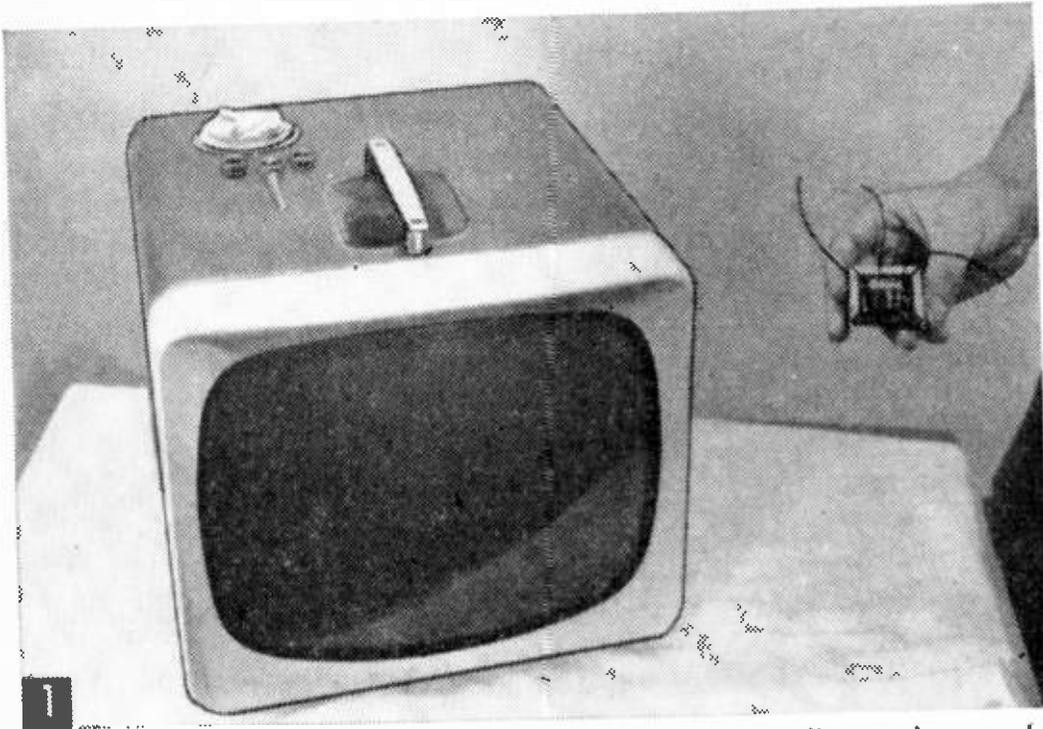

The CR tube brightener usually cures dimness, when the dimness is caused by low cathode emission.

THIS autotransformer-type brightener is made by winding a few hundred turns of magnet wire on the core-form from a small, audio output transformer. After a tube has 1000 or more hours service, cathode emission drops, and the required number of electrons fail to reach the phosphorous screen. Emission from a spent cathode can be increased by raising the filament temperature of the tube. The brightener does this by raising the CRT filament voltage from 6.3 v. to 8 v.

There is a risk, depending on the applied voltage increase, age of the tube, gas content (leakage), and the condition of the tungsten filament wire. Many tubes give a year of highly satisfactory service after a brightener has been installed. One tube out of twenty, will give a disappointing few hours or days of brightness. The brightener should be used only when causes of failure other than lowered emission are ruled out.

For example, troubles originating in the high-voltage section, such as an open current-limiting resistor in the anode lead, often are responsible for dimness. A weak rectifier will cause dimness and can be verified by advancing brightness control—if picture enlarges, rectifier is bad. Another cause of dimness is a gassy picture tube, which can be discovered by adjusting ion trap and checking picture for distortion and defocusing



effects as trap is moved slowly.


Many series-string TV's use a thermistor (Glo-Bar) component to prevent filament burn-out from warm-up surges. Failing in its thermal function, this protective device may be the cause of sub-normal filament voltages throughout the receiver, resulting in dimness. If possible, check filament voltages when this part is suspected.

If you've ruled out the foregoing causes of dimness, low emission may be the cause of dimness and you can try a brightener.


First, find out whether your TV is a series-string job, or has parallel-wired

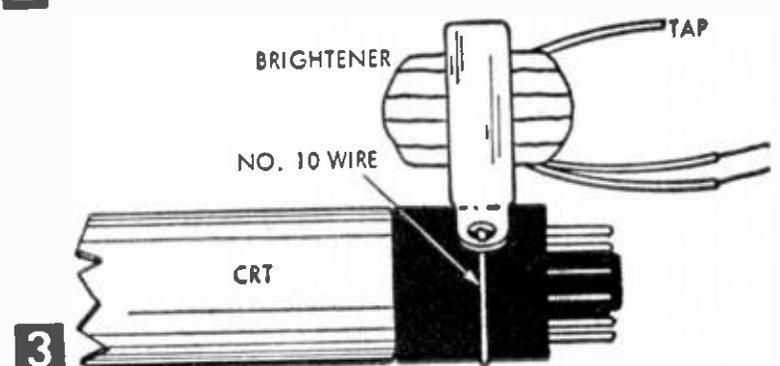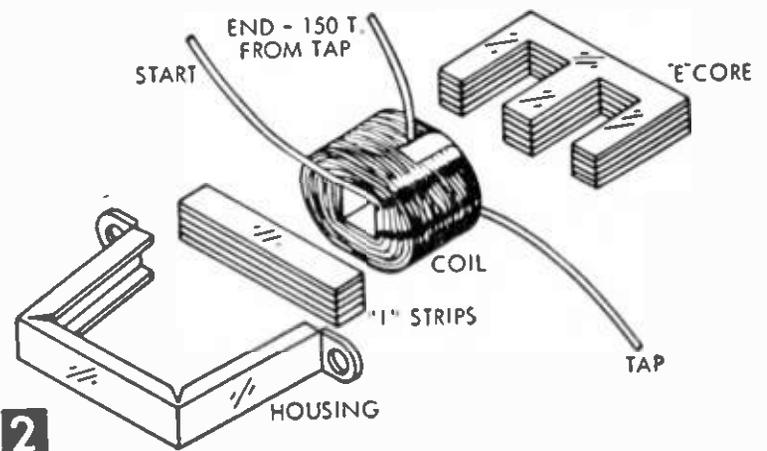tube filaments. The coil specifications of the brightener depend on the filament arrangement. If in doubt, check the tube-chart pasted on the back or inside panel of the receiver, and compare tube prefix numbers. The first number designates tube filament voltage. 6W4, 6BG6, 6K6, 6BC5, 6AL5 are tubes with 6.3 v. filaments. If set uses mostly




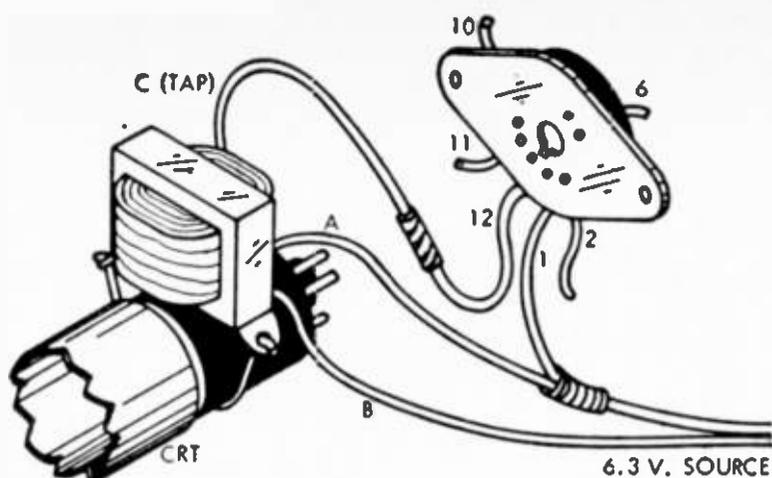

4 SERIES - STRING WIRING

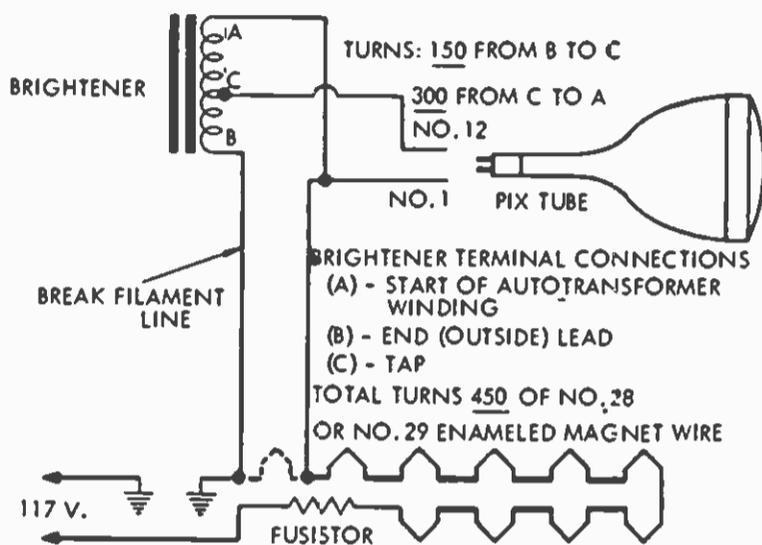

5 SERIES - STRING SCHEMATIC

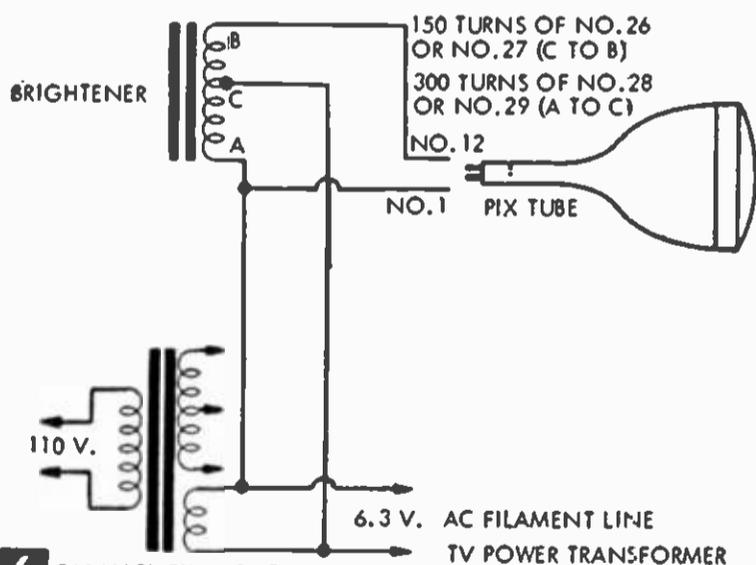

6 PARALLEL FILAMENTS SCHEMATIC

these types, it probably is a parallel type receiver. TV's with mixed filament-voltage prefixes—3AU6, 5U8, 25W6, 17BQ6—are series-string. Receivers with a power transformer are always parallel connected.

Next, locate a small audio output transformer that has been salvaged (preferably $1\frac{1}{4} \times 1 \times \frac{5}{16}$ in. lamination size) and begin. First, remove the core from its housing and slip the coil from the iron. Strip, or unwind coil down to the inside form. With this insulated sleeve fastened over a small tapered stick (winding handle), secure a 5-in. #28

TRANSFORMER THEORY

An autotransformer is basically the simplest type of transformer. Primary and secondary windings are combined and form a single, tapped coil. By reversing two leads, an auto-transformer may be used either as a step-up voltage device or a step-down transformer. One disadvantage is that it will not provide complete isolation between the primary and secondary circuits, because of the single winding. In Fig. 6, parallel operation, the 300 turn coil section is the primary. As voltage is applied to this winding, a magnetic flux builds in the primary and induces a voltage into the secondary, in direct proportion to the number of turns of the secondary. Because the single winding is, in effect, two coils coupled together and series-aiding insofar as voltage is concerned at the secondary terminals, this induced voltage adds to the input voltage of 6.3 v. and, being approximately half of 6.3 v. (less transformer losses which run comparatively high for this type unit) we get about 8 v. output.

If transformer is connected to a series-string receiver, Fig. 5, a different induction arrangement becomes apparent. Effectively in series only with the resistance of the picture tube filament, our small, 150-turn coil section now becomes the transformer primary. The larger, higher impedance winding (but having considerably less inductive reactance because of this filament resistance) now becomes the secondary. Induction from the primary adds to the voltage flowing through the 300 turns and thereby supplies the tube with a required voltage increase.

If possible, test the applied AC filament voltage from the brightener. It should not exceed 8.5 v. AC. The possibility of winding error or high line voltage makes it important to tube life that you lower too-high voltage by removing turns from the 150 turn coil section. Usually, 20 or 30 turns is sufficient. If voltage seems lower than expected, a few turns may be added to the same winding.

If you care to check the dc resistance of the coil sections before connecting to receiver, the parallel-type winding (#27) measures approximately .8 ohm; primary, 3.5 ohms. The series-string coils are: primary, 2.5 ohms, secondary 3.5 ohms.

or #29 enamel-covered magnet wire lead to the form with Scotch tape and start the winding. Scramble-wind 300 turns neatly without actually layer-winding, then make a loop-tap 5 in. long (C lead, Fig. 3). At this point, if brightener is to be used on a series-string type receiver, continue and wind another 150 turns and bring out the end lead. However, if unit is for a parallel filament hook-up, the wire size is changed at the tap to the slightly larger #26 or #27, insuring adequate current-carrying capacity of the coil. Depending on the actual wire-sizes involved, coil-form width, and neatness of turns, you may have to secure the winding bulk with cement to

MATERIALS LIST—CRT BRIGHTENER

No. Req.	Description
1	Used audio output transformer. Lamination size, approx. 1 1/4 x 1 x 5/16" (50L6GT type)
For Series Brightener:	
100 ft.	#28 or #29 enameled copper magnet wire
For Parallel Brightener:	
75 ft.	#28 or #29 enameled copper magnet wire
50 ft.	#26 or #27 enameled copper magnet wire
Scotch tape, coil dope, speaker cement, etc.	

overcome a tendency of underneath turns of slipping loose at the sides. After completing the required number of turns (450 total, tapped at 300), tape end lead to winding body and apply insulating varnish, coil dope or speaker cement.

Figure 2 shows a completed coil ready for insertion on the center-leg core laminations. The assembled transformer should be inspected to make sure that the outside housing clamps the I laminations securely to the E core pieces. A few additional drops of cement between the coil and laminations will prevent vibration-hum during operation.

A satisfactory method of mounting the brightener is shown in Fig. 3. When convenient, the brightener may be taped to the picture tube base by wrapping several turns around each. Figs. 4 and 5 show brightener wiring details and schematic for series-string operation. Sets with a power transformer are connected according to the schematic, Fig. 6.

Ham Radio Anagram

Calling all hams, SWL's and everyone interested in amateur radio. Think you can chop through the QRM and work this anagram puzzle? Read each

clue very carefully—some are sure to give you some static! The empty blocks are to be filled with words, abbreviations or Q-signals.

Solution on Page 120

By JOHN A. COMSTOCK

ACROSS:

- 1) Something every ham must learn to send before he can obtain his ticket.
- 3) A type of antenna commonly used by amateurs.
- 6) A type of CW key.
- 8) Capacitive reactance.
- 10) A combination of antenna elements.
- 11) A type of transmitter circuit often used in ham rigs.
- 12) A tap in the center.
- 14) Opposite of high-voltage.
- 16) A directly excited antenna element.
- 19) CW that is interrupted.
- 20) A grid that's floating.
- 22) It flows in a vacuum-tube's plate circuit.
- 24) The oscillator found in a superhet.
- 25) Entries are made in it.
- 27) Plate load resistor.
- 28) "From."
- 30) Phase modulation.
- 31) Not an old lady.
- 32) Calling all stations.
- 33) A rig moved about by automobile.
- 34) The letter "A" in code is dit- — — (supply missing letters).
- 36) A type of modulation.
- 38) A point of minimum voltage or current.
- 40) An international time standard.
- 42) Break.
- 43) Sent three-times,

it's the CW safety signal.


- 44) A national defense organization.
- 49) A type of oscillator.
- 51) An interference which modulates a signal undesirably.
- 52) Grid potential.
- 55) Part of an antenna array.
- 56) Not desirable in the output signal of a transmitter.
- 57) Three times, dah dit dit dah.

DOWN:

- 1) A type of transmission line.
- 2) A current that flows in only one direction.
- 3) Abbreviation for the kind of current described in No. 2 down.
- 4) Some hams work — — — — —, others work CW.
- 5) The power that a

transmitter delivers to its antenna.

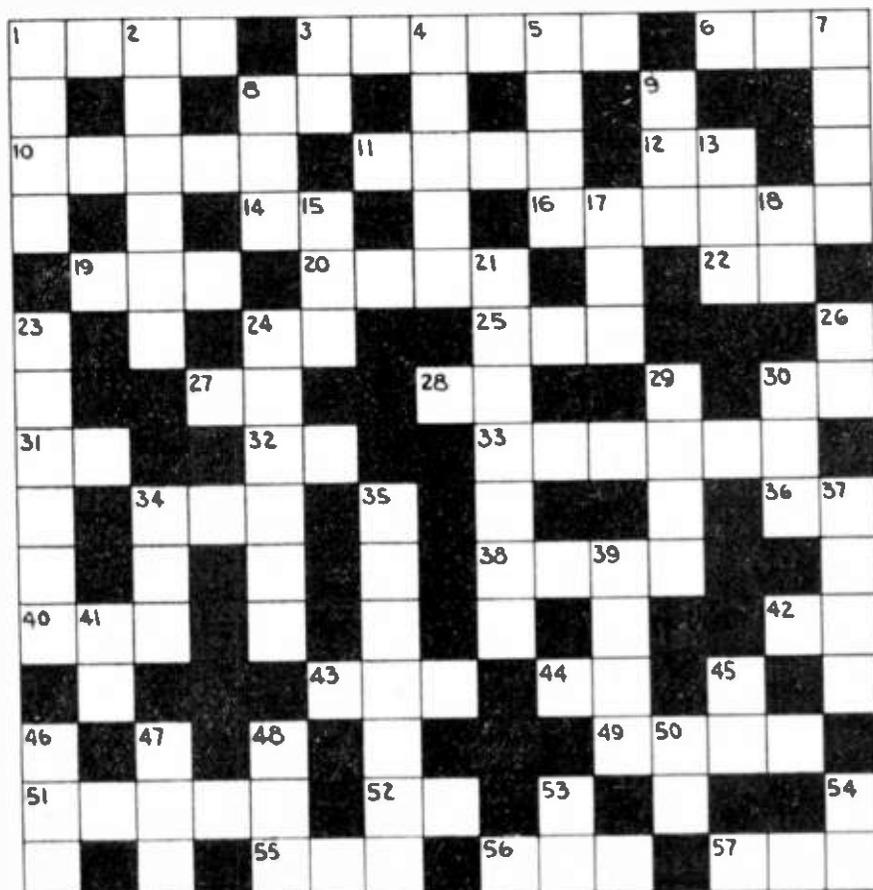- 7) An antenna with high — — — is better for DXing than one with low — — — — —.
- 8) A ham's wife.
- 9) Interference to standard broadcasts.
- 13) Interference to television.
- 15) When you want to work several bands easily, a — — — is a must.
- 17) Amateur radio gear.
- 18) Plate potential.
- 21) Part of an antenna.
- 23) What you are doing when you pound a bug.
- 24) Wires used to measure short wavelengths.
- 26) Not a young man (but could be).
- 29) A pure waveform.
- 30) A low-voltage lamp the size of a certain green vegetable.
- 34) What a dot (•) sounds like.
- 35) A type of oscillator.
- 37) Hams talk into one.
- 39) A type of switch.
- 41) A definite length of time.
- 45) Tube with a breakable envelope.
- 46) A broadcast listener.
- 47) Often it is used as a volume or tone control.
- 48) Transmitting only one sideband.
- 50) An amplifier that boosts power.
- 53) Thank you.
- 54) Long distance communication.



Nerve Tester

Here's a gadget that'll find who's got the steady nerves in your crowd

By FORREST H. FRANTZ, Sr.


THE principle of operation of the nerve tester is extremely simple. The circuit is shown in Fig. 2. A weight is suspended on a short length of bare wire, forming a pendulum. The wire passes through a hole in a small metal bracket. This bracket and the wire which hold the weight form the two terminals of a switch. The pendulum will make contact with the bracket if the person holding the case is the least bit unsteady.

The pendulum switch is connected in series with a battery and a light bulb. The battery consists of two penlite cells connected in series so that the bulb will light brilliantly whenever the pendulum makes contact. The pendulum is skewed away from the case sides (Fig. 3) to make the correct orientation of the case more challenging. The lower bracket may be turned to decrease the effective size of the hole through which the pendulum passes and thus increase the sensitivity of the tester. The switch CS is a clip-switch consisting of a Mueller Minigator clip which is fastened to the positive battery holder terminal when the tester is not in use. The stiffness of the hook-up wire is sufficient to keep the clip from touching the battery when it is disconnected even under severe jostling.


The unit can be constructed from parts costing about 75¢. The cost can be cut to about 25¢ if only one penlite cell is used and no battery holder. This may be done if the connections to the penlite cell are soldered. In this event, the minigator clip lead is soldered to the battery, and the clip connects and disconnects on the lower bracket.

Place the battery holder in the case in the approximate position indicated in Fig. 4, and make mounting holes by passing a heated ice pick through the case. The holes for the pendulum supporting bracket and the lower contact bracket are made the same way. (Drilling may crack case.) The positions for the bracket holes are not critical, but try to place them $1\frac{1}{2}$ to $1\frac{3}{4}$ in. apart. After the plastic around the case holes has hardened, trim the edges with a pocket knife.

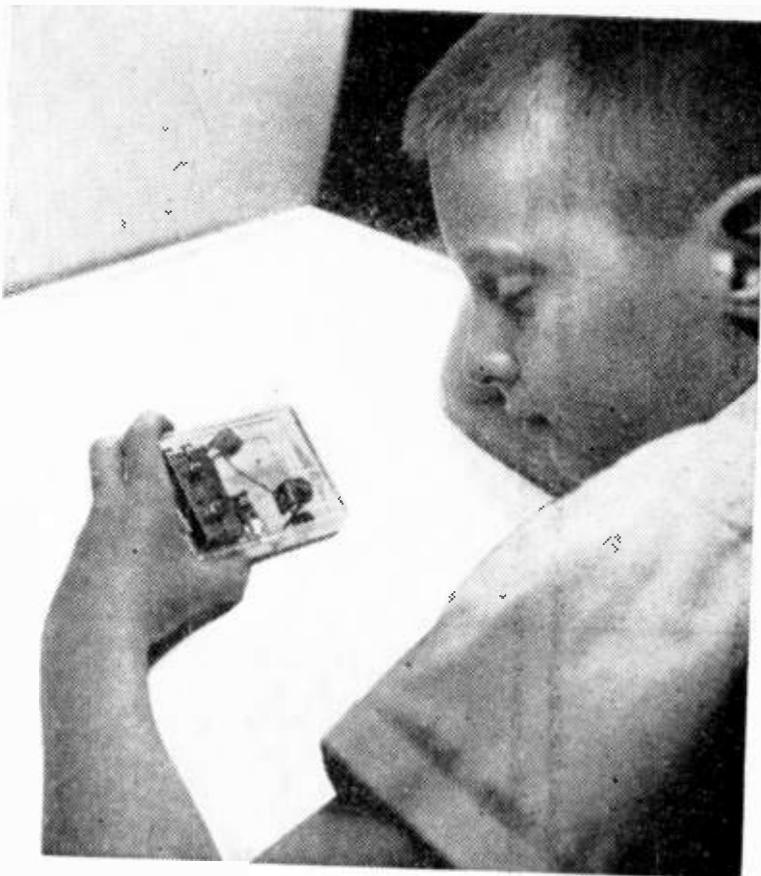
Next, fasten the battery holder and the brackets to the case. The heads of the mounting screws can be placed on the inside of the case to prevent screws' interference with the pendulum. The brackets are available at hardware or radio stores, or you can make your own. They should be $\frac{1}{4}$ - to $\frac{1}{2}$ -in. wide with each side of the angle $\frac{1}{2}$ - to $\frac{3}{4}$ -in. long.



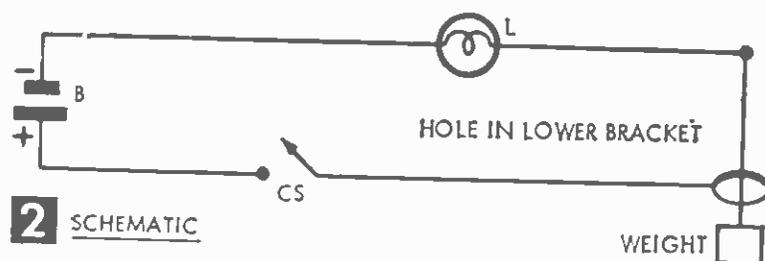The nerve tester—challenge to the young in heart.



2 SCHEMATIC

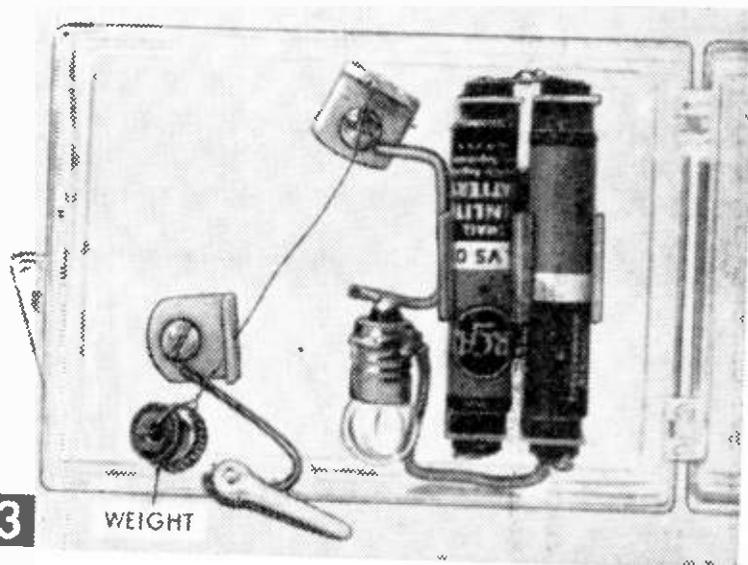


3

The weight is suspended on the bare wire, which passes through the hole in the lower bracket. If wire touches bracket, bulb lights.

The holes should be $\frac{1}{8}$ -in. dia. or smaller, for best results.

Now, solder a piece of wire about $1\frac{1}{2}$ -in. long to one of bulb's terminals and a similar length to the other terminal. Connect one of these leads to the battery holder; connect the other to the pendulum support bracket. Turn the battery holder connection lugs at the other end of the battery holder toward each other and solder them together. Solder a 2-in. length of hookup wire to the Minigator clip

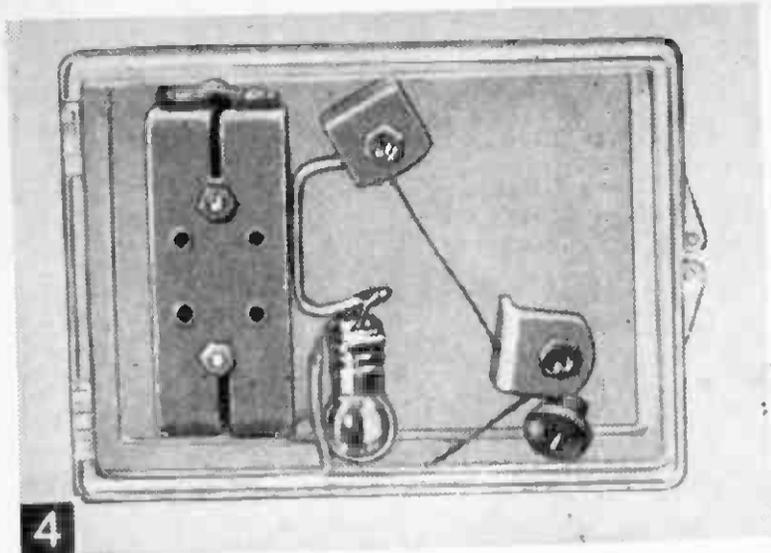

4 Back view shows mounting details.

MATERIALS LIST—NERVE TESTER


Desig.	Description
L	* flashlight bulb (GE #14)
B	2 penlite cells series connected (RCA VS0-74)
	2-cell battery holder (Lafayette MS-138)
	plastic case 3 5/8 x 2 5/8 x 1 in. (Lafayette MS-159)
CS	minigator clip (Mueller 30)
	2 brackets and hardware (see text)
	* Get a bulb with a brass base. Some bulbs have aluminum bases and cannot be soldered readily.

and fasten the other end under the lower contact bracket mounting screw.

The pendulum wire should be sufficiently stiff and rugged to allow easy fastening and to assure long trouble-free operation—#28 is a good gauge. Solder a 3 1/2-in. length to the suspending bracket, but go easy on the heat, or you'll melt the plastic case. Pass the wire through the lower contact bracket, and fasten the weight. This weight could be a nut, a washer or a fishing sinker. Insert the batteries in the holder and adjust the lower bracket for the desired sensitivity. Shut the case and you're ready to test your nerve.

Which Bulb Burns Brighter?

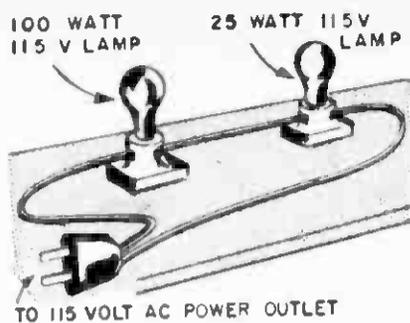• Connect two ordinary cleat-type lamp sockets in series as shown in diagram, then screw a 100-watt bulb into one, a 25-watt bulb into the other. Now, before you connect the setup to a 115 volt a-c outlet, which of the bulbs do you think will burn brighter?



Most people instinctively choose the larger lamp, but the experiment proves otherwise. A bit of thought reveals the reason. In a series circuit, the identical stream of current flows through all parts. Thus, whether the current is large or small, it will be the same through both bulbs. However, the voltage across each lamp will be proportional to its resistance. The 25-watt bulb must have the higher resistance, since normally it consumes less current than the 100-watt when supplied by the same line voltage. Therefore, in a series circuit, the lowest-rated lamp burns more brightly since it receives the greater voltage.—C. F. ROCKEY.

Kink for Soldered Joints

• When soldering wires and cables in a radio receiver, immediately after the iron is removed from the soldered joint, paint the joint with lacquer-thinner, using a small brush. The rosin flux will evaporate immediately, leaving a clean joint. Using this kink, a cold-soldered joint will immediately show up, preventing future trouble.



"Would your ears mind listening in another spot—the carpet's wearing out!"

Trouble-Shooting Interference




How to discover the source and eliminate noise in a radio or amplifier

By FORREST H. FRANTZ, Sr.

PUT a new LP on the phono and slump into the easy chair. The music is fine, but what's that d— hum? The disturbing sizzle of a TV, the gasping of a hoarse, distorted radio or TV and the whine of a humming radio are other manifestations of interference. Fortunately, most of these troubles are easily recognized and fixed.

We usually differentiate interference as either hum, buzz, squeal, noise, distortion or station interference. Sometimes these are due to faults in the gear, sometimes to external sources. Frequent internal causes are: open, shorted or leaky capacitors, intermittent connections, intermittent short circuits, defective tubes and dampness. The antenna-ground system is also a frequent trouble spot. Externally caused disturbance is often traced to switches, thermostats, advertising signs, motors, radio stations and high voltage lines.

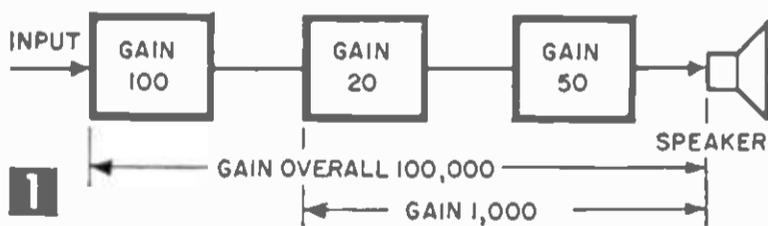Let us look, first, at hi-fi audio amplifiers, remembering that this discussion is applicable also to the AF section of radios. Then we will cover radios specifically.



Hum introduced in first stage is amplified more than hum introduced in subsequent stages.


Audio Amplifiers. Amplifiers may exhibit interference in the form of hum, buzz, squeal, noise or distortion.

Hum in an amplifier is usually caused by insufficient shielding of the amplifier input circuit. The various stages of an amplifier have individual gains, which multiply as shown in Figure 1. The first stage usually has the highest gain. Thus, the gain from the first stage to the loudspeaker is much greater than the gain from any succeeding stage to the loudspeaker. If even a small portion of an amplifier input lead is unshielded, it acts as a capacitor to the ac line though it may be many feet away. A small amount of alternat-


ing current can therefore feed into the amplifier. The high gain of the amplifier multiplies this minute voltage into a sizeable signal at the loudspeaker.

Hum due to poor input shielding is easily recognized, since the loudness of the hum will decrease as the volume control setting is decreased. There are several steps to pinpointing and curing this. First, dress the input lead close to the chassis. The input lead can be traced from the input connector and usually goes to the high volume control terminal (possibly through a capacitor) as shown in Figure 2. The center terminal of the volume control goes to the grid of the input tube (possibly through a capacitor). In some amplifiers, a preamp stage precedes the volume control. If the input tube is glass, a shield may cure hum. Next, check the shell to chassis ground connection of the input connector. Then check the connection from the external input plug to the braided shield which encircles the unit's input lead (Figure 3). An open can cause hum.

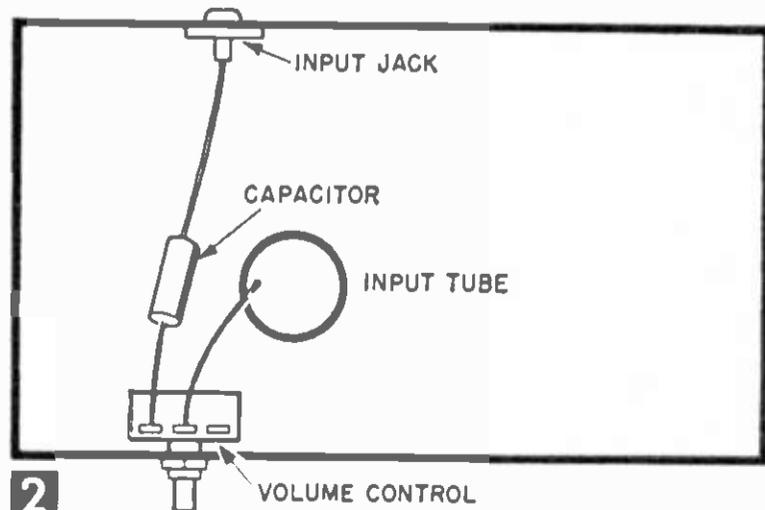Sometimes, in cheap construction, unshielded leads are used, and should be replaced. An open from shield to ground or at the chassis connector will result in loss of gain, because the shield is frequently the chassis ground return conductor. Finally, check the ground connection at the remote input device and look for short lengths of



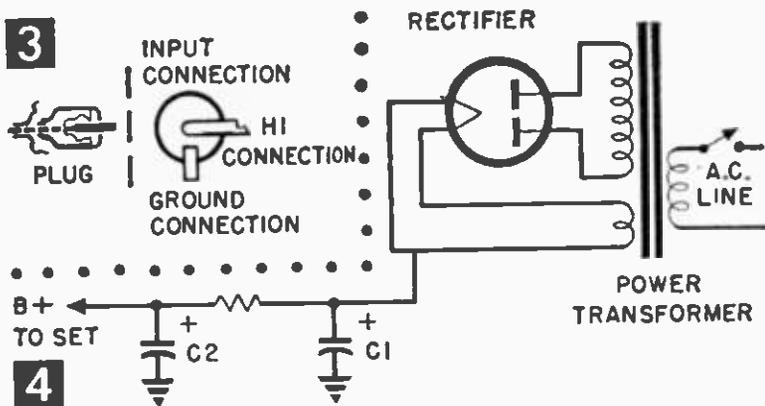Leads likely to pick up hum. Remedy is to substitute shielded cable, dressed close to chassis.



3. A broken shield or disconnection from plug ground or a faulty or open input jack can cause hum pickup.
 4. Filter capacitor (C1), which if open, causes hum in amplifier power supply. Leaky power supply output filter capacitor (C2) will cause hum or squeal.

input lead which may be unshielded.

Hum which occurs at all volume settings is often due to defective filter capacitors in the amplifier power supply, as shown in Figure 4. (The rectifier tube is connected to the power transformer and the high voltage electrolytic capacitors.) To test the filtering, bridge a 10 mfd. electrolytic (watch the polarity) across C1. The voltage rating should be equal to or greater than that of C1. If hum decreases, you're on the right track. Disconnect C1, and connect a replacement capacitor of the same or greater voltage and the same capacity in the circuit. If the hum is substantially reduced, replace C1 permanently. Otherwise, connect the original C1 back into the circuit, and bolster the filtering action with the 10 mfd. capacitor that scored the original improvement. If this isn't enough, try a 40 mfd. capacitor of adequate voltage rating across C2.

Caution! Don't work on an amplifier that has been used in the last few minutes—wait until capacitors discharge.

If you still haven't cured the hum, check for cathode to heater leakage in tubes, poor connections to chassis ground within the amplifier, and open or partially open capacitors elsewhere in the circuit (can usually be found by bridging with another capacitor).

Squeal in amplifiers may be due to open filter or bypass capacitors, which can be traced by employing the capacitor bridging technique described previously. Another cause of squeal is feedback caused by a high level signal lead being too close to an early amplifier stage lead—shorten the lead and dress it close to the chassis.

Noise may be due to a bad volume control, a microphonic, shorted or intermittent tube (which can often be located by tapping with a pencil eraser) or a rubbing loudspeaker voice coil (most readily checked by substitution of another speaker). Noise can also be caused by an intermittent capacitor (thump and jiggle the suspect), by poor connections which may be loose or intermittently shorted,

by intermittently shorting output or inter-stage transformer windings or by arcs across rectifier or output tube sockets (usually indicated by a charred section of tube socket or a visible arc during operation).

Distortion in amplifiers is usually caused by leaky coupling capacitors (C4 in Figure 5). Coupling capacitors may be checked by substitution, but this requires disconnecting one end of the original capacitor. Other sources

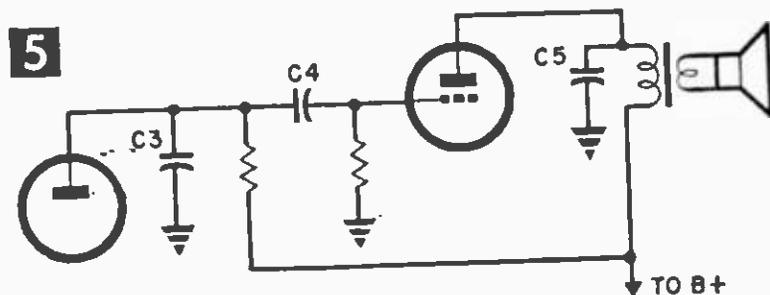


Plate bypass capacitors (C3 and C5) or coupling capacitor (C4) if leaky can cause distortion.

of distortion are leaky power supply output filter capacitors (C2 in Figure 4) and leaky bypass capacitors. Plate bypass capacitors (C3 and C5 in Figure 5) are likely offenders. In each of these cases, one end of the original capacitor must be disconnected before substitution of a similar capacitor is attempted. Another frequent cause of distortion in amplifiers is a gassy tube. Output tubes are the usual offenders.

Radios. Radios are subject to all the amplifier disturbances described, and the same solutions apply. In addition to amplifier troubles there are other possibilities.

Hum caused by some strong local radio station can usually be cured by connecting a 0.05 mfd., 600 v. capacitor from one side of the ac line to chassis ground as shown in Figure 6A. If the set is ac-dc (no power transformer), the capacitor should be connected from the set side of the switch to the opposite side of the line as shown in Figure 6B.


Buzzing is due to external sources such as neon signs, motors, or high voltage lines.

Squeals may be caused by any of the things already discussed under audio amplifiers or may be due to open bypass capacitors, long unshielded RF or IF leads or other causes. Long leads on IF transformers are frequent causes of squealing.

Noise may be due to internal or external trouble. If the set uses an external antenna,



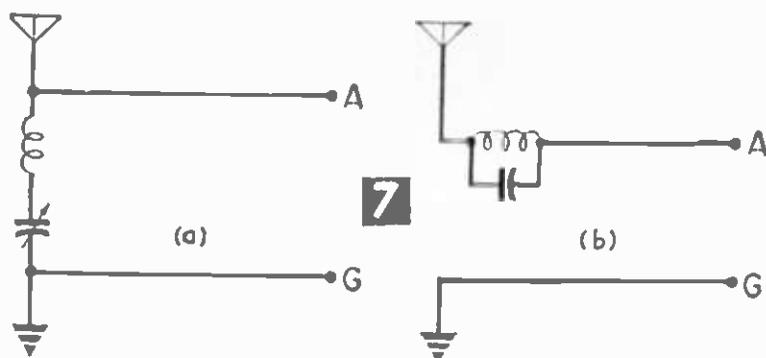Suppressing a strong local station by connecting .05 mfd capacitor from one side of line to chassis ground for ac radio (a) and from set side of the switch to opposite side of line for AC-DC radio (b).



Suppressing an unwanted station with a wave trap, a tuned circuit across the antenna ground terminals (a) or in series with the antenna terminal (b).

disconnect it, and short the antenna terminal to ground. If the noise persists, it's in the receiver. Arc in the power supply, intermittent connections almost anywhere in the set or defective tubes are possibilities. Next, check the antenna by disconnecting it and connecting 20 ft. of wire to the antenna terminal. Noise in an antenna may be due to poor or corroded connections at the antenna, lightning arrestor, feed-in to the building, a break in the lead-in under the insulation or to the antenna or lead-in contacting metal such as the storm gutter.

Assuming noise to be external to the receiver, a capacitor connected as shown in Figure 6A or 6B may be helpful if your receiver doesn't already have one. If this doesn't help, try tracking down the external causes

which were mentioned early in this article. For example, if noise occurs around meal times, it may be an electric stove or other appliance. Or, say the noise occurs only in winter—could be the thermostat.

The type of noise your receiver picks up is also a clue to its origin. Switches, relays, thermostats and poor electrical connections cause intermittent noise. Motors and industrial and medical electronic equipment produce a buzz or whine in nearby radios. High voltage lines produce a hum or buzz with a super-imposed crackle in radios. High voltage line noise is continuous, and the crackling is worse in damp weather.

A battery receiver, that has automatic volume control (which you must disconnect for this purpose) and a directional loop antenna, is helpful in tracking down noise.

When the source of noise is located, a commercial filter installed at the source of the noise will usually cure the trouble. These filters usually consist of capacitors or capacitors and inductors.

Distortion is usually due to AF section trouble. Refer to the previous discussion of distortion in connection with audio amplifiers.

An interfering radio station can be eliminated by a wave trap, a tuned circuit across the antenna-ground terminals (Figure 7A) or in series with the antenna terminal (Figure 7B) tuned to the frequency of the interfering station.



Curing Tape Recorder Noise

CHATTER, squeals, hum and fading are the symptoms of minor mechanical ills that you can cure without taking your tape recorder in for repairs.

Mystery Chatter. Here's an example of trouble that had both the owner and a service technician stumped. Whenever the tape was running they heard a mysterious chatter, but when the machine ran without tape on the reels the noise ceased. Finally, with an improvised "stethoscope" made of a cardboard mailing tube, they pinpointed the sound in the counter. Even though the moving parts were plastic, they rattled and chattered until the steel counter shaft was smeared with a bit of Vaseline petroleum jelly.


Poor Tape Gums Head. Sometimes the trouble may not even be in your recorder. The culprit may be poor tape, hard to spot when spliced in between lengths of superior quality tape. Some bargain tapes shed their red-colored coating, and gradually your recording heads gum up with a deposit. The effect is a gradual drop in recorded volume until you may not be able to record at all. The same tape coating residue deposited on the pressure pads and roller may cause squeaks. If the dirt won't come off with a clean, moist cloth, use alcohol or tape-head cleaning liquid (Fig. 1).

Pad Squeak. Dry pressure pads, even if they are clean, can cause squeaks. Isolate your noise by gently lifting the pad away from the tape as it passes the recording head. If the pad was causing it, touch it lightly with a tiny bit of petroleum jelly.

Ratio Flutter. Sometimes the difference in ratio between the O.D. and hub diameter of a 7-in. reel may cause a speed variation as you wind from a full reel down to an almost empty one. The effect is flutter and wow, and the answer is either to use a lot of leader ahead of your recording, or the new "flutter-free" reels that have larger hubs.

Rubbing, Stalling, Spilling. Bits of broken tape, dust and dirt will collect around the head and top mechanism to cause soft rubbing noises. A remedy is to cautiously take off the top cover plate and remove dust and tape chips with a small brush.

Most machines are permanently lubricated at the factory. But after a lot of heavy duty use, you may find dry bearings on the motor, flywheel, pressure roller or idler assemblies. These bearings can take an additional drop of #10 motor oil once a year if your machine is used a lot. But don't over oil. Oil that transfers to rubber belts, wheels and your flywheel can cause all kinds of braking, rewind, and fast forward troubles. Tape spill and a stall-

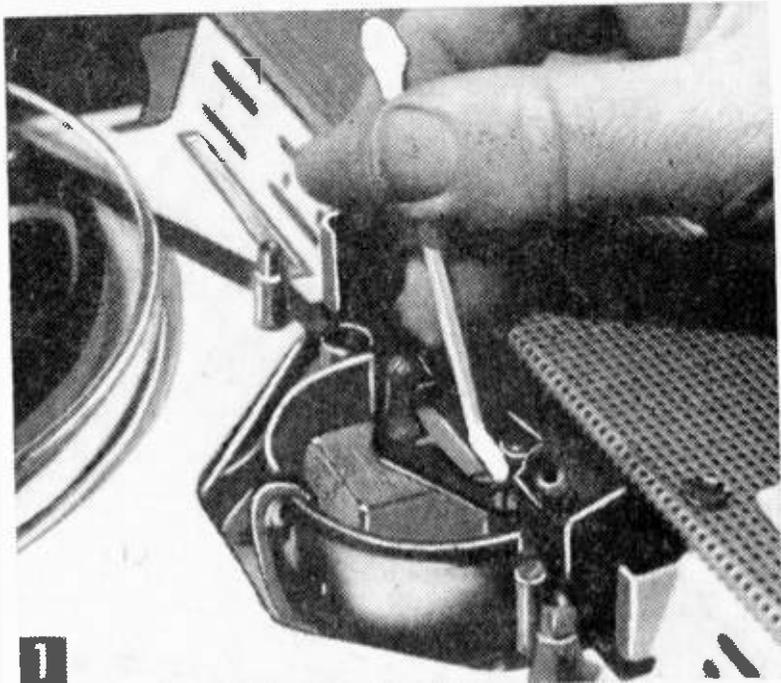


1 Every so often, clean your recording head, rollers and pads with a cotton medical swab. Use alcohol or tape-head cleaner to dissolve deposits of tape oxide.

ing of the take-up reel when it's almost full are common symptoms. Remove oil on belts and wheels with an alcohol dampened cloth.

If your recorder is stored away for months at a time, don't worry about noise problems or adjustments until after you run it a few hours. Rubber drive wheels, belts, etc., particularly if the recorder is accidentally left in forward or rewind for a long time, will develop bumps or flat spots which will disappear after a good warmup. Even your plastic spools will warp if stored improperly, and tape wound too tightly will "set."

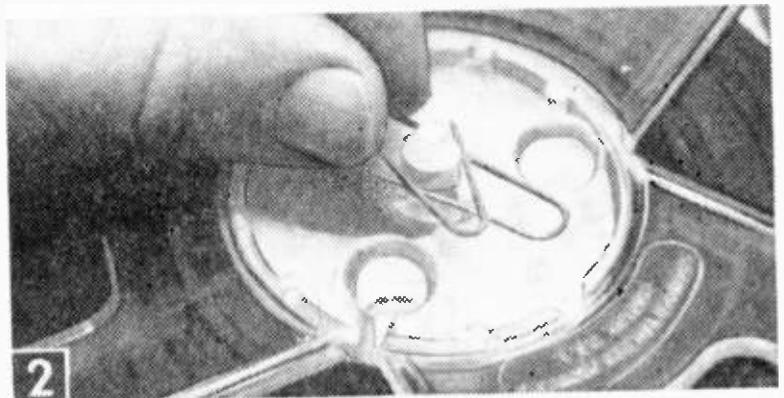If internal noises persist, remove bottom covers and look for loose set screws, scraping motor fan blades and rubbing shafts on the inside. Tie your tape reels in place with paper clips and run the recorder at various angles to spot vibration trouble. More advanced servicing steps are covered in service sheets usually supplied free on request from recorder manufacturers.—GLEN F. STILLWELL.



2 With the reels clipped in place, you can run the recorder tipped at various angles to pin down the source of rattles and vibrations.

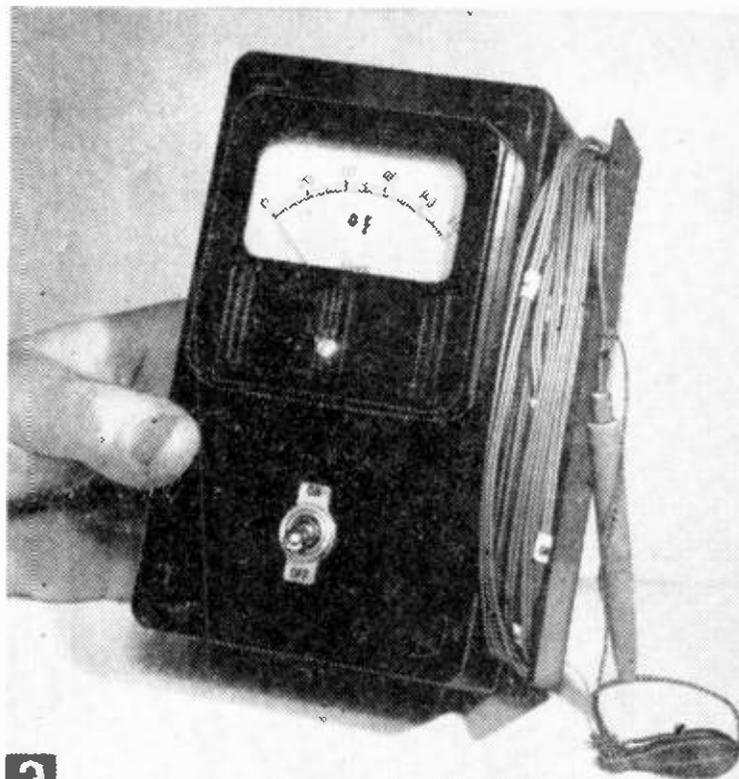


Fig 1. Lower the probe into the water, flip the switch, and the meter instantly reads the temperature.

Fig. 2. The meter scale is labeled to read directly in degrees F. Left-handed fishermen will want to mount the wire reel on the opposite side.

Remote Reading

Electronic Fishing Thermometer

Because the fish play it cool,
this will help you locate the
spots where they bite

By JAMES E. PUGH

THE sensitive thermistor in the probe of this \$11 instrument will give you temperature readings down to 50 or more feet below the surface of your favorite fishing waters. That is why you can use it to answer the question, "Where are they biting today?"

Fishing experts know that fish prefer waters within a certain temperature range; the exact range depending on the species (Table A). When the fish are in a level of water at the temperature they prefer, they are lively and will take lures readily. In warmer zones, they are more listless, often

refusing bait altogether. The principle behind this fishy behavior is that any one kind of fish will seek water with the certain oxygen content that is most comfortable for him. Since the amount of absorbed oxygen in water depends largely on the water temperature (warm water holds less oxygen than cold water), the electronic remote thermometer will guide you to where your favorite fish are most likely to be found.

Preparing the Case. First lay out the hole locations on the black plastic case (Fig. 3). The arrangement of the wire reel shown in Fig. 2 is for right-handed fishermen. South-paws should simply change the reel to the left side and the battery to the right. When you drill the holes, back up the underside of the case with a wooden block to prevent chipping. Use a circle cutter on a drill press to make the 2 $\frac{5}{8}$ -in. hole for the meter. Without a circle cutter, scribe the hole and drill a $\frac{3}{16}$ -in. hole just inside the circle. Then cut this section with a fine coping saw, and trim the hole with a fine half round file to fit the meter case exactly.

Next solder the junction of rivets and lugs on the battery holder (Fig. 4) to avoid possible trouble with a high resistance joint in the future. Also coat the inside surface of


the rivet with solder where it contacts the battery, to avoid corrosion from battery leakage. Then mount the other parts and solder all connections (Fig. 5).

Be sure that your soldering iron is hot and clean, and use only rosin core solder. Apply the hot iron and a very small bit of solder to the joint at the same time. The layer of solder provides heat contact with the joint. After a moment when the joint is hot apply more solder. Remove the meter lugs when soldering to prevent damage to the meter, and use heat sinks to keep the small resistors cool.

Although our model is shown with 50 feet of cable you can use any length to suit local needs. Tie one end of the cable to one of the reel spacers (Fig. 5A) allowing about 1-ft., to pass through the grommet into the case. Solder the connections and wind up the length of cable on the reel.

Testing Meter Wiring. To check the work so far, strip about 1/4-in. of insulation from the probe end of the cable. Place the battery in its holder and with the bare ends of the probe wire well separated, immerse them in a glass of water. The meter pointer should move upward on the scale, the amount of movement depending on the impurity of the water. If the meter reads backward, your battery is reversed in the holder. Remember that the positive terminal of this battery is not the same as that of a flashlight cell. Mercury cells have a positive shell and a negative center. Mark the positive terminal lug of the battery holder with a dab of nail polish, or red paint.

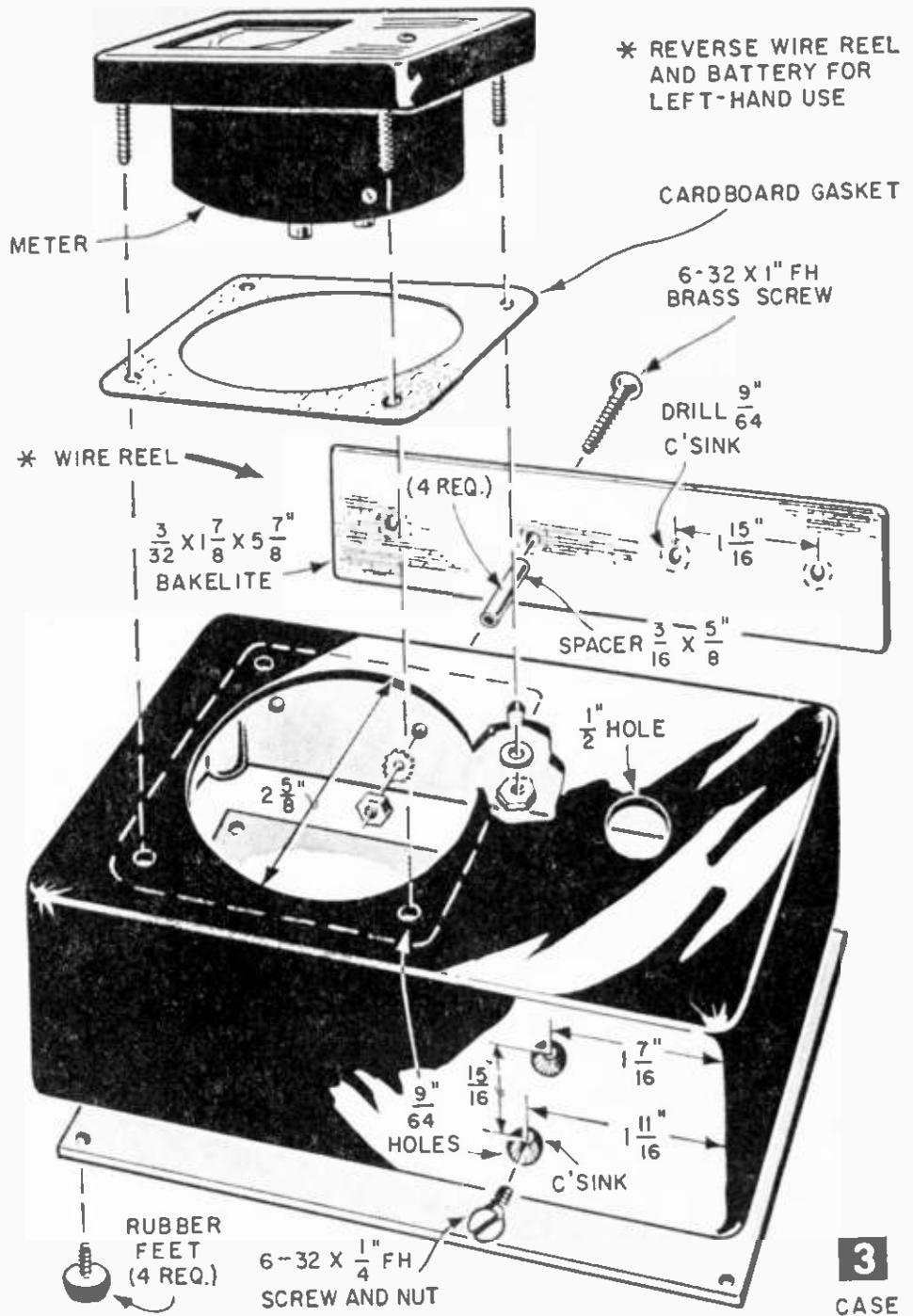Making the Probe. With a fine coping saw,




MATERIALS LIST—ELECTRONIC FISHING THERMOMETER

Part/No. Req.	Size and Description
B1	1.34-volt mercury cell, Mallory RM-401R (Lafayette BA-239)
M1	0-1 ma. D.C. Milliammeter (Lafayette TM-60)
R1	100 ohm, 1/2 watt, 10% carbon resistor (Lafayette RS-10)
R2	470 ohm, 1/2-watt, 10% carbon resistor (Lafayette RS-10)
S1	SPDT toggle switch (Lafayette 8282k14)
TH	1250 ohm thermistor, Veco 31A1 (Lafayette 31A1)
1	6 1/4 x 3 3/4 x 2" Bakelite case (Lafayette MS-216)
1	panel for Bakelite case (Lafayette MS-217)
1	holder for RM-401R Mercury cell (Lafayette MS-388)
50'	miniature parallel cable, Belden 8782 (Newark Electronics 36F105B)
4	1/2" rubber feet (Lafayette P-249)
1	On-Off switch plate (Lafayette 827-228F3)
1	#1-33 wire markers, Brady B-500 (Newark 30F200)
1	#34-66 wire markers, Brady-500 (Newark 30F201)
Misc	machine screws, nuts, metal spacers, wood dowel, ball point pen casing, cement, sheet Bakelite, cardboard gasket, plastic electrical tape, wire and rosin core solder

cut the threaded end off the lower half of a plastic ball point pen casing. Drill eight 1/16-in. holes around the pointed end (Fig. 6). Then shape a 2 1/8-in. length of wood dowel so it fits snugly into the casing with about 1/2-in. projecting. You can turn a dowel down to the diameter needed by chucking it in an electric drill and removing excess wood with sandpaper. Carefully drill a 1/8-in. hole through the dowel, working from both ends to keep the hole centered. Notch the tapered end of the dowel (Fig. 6) to seat the plastic probe cable. Push the cable through, tie a single knot and dress the ends, tinning them with solder.


Handle Thermistor Carefully. Remove the thermistor from its shipping box and place it on a clean white paper so it can be seen. It is so small it can easily be lost. With the thermistor laying on the paper, hold one of the cable ends against one of the tiny leads. Use a small tweezers as a heat sink to keep soldering heat from damaging the thermistor, carefully touching your clean soldering iron tip to the wire until the solder melts.

Fig. 4. Solder the terminal rivets and also coat the contacts to prevent corrosion. Mark the positive terminal to insure correct battery polarity.

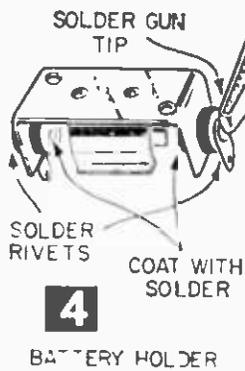


BATTERY HOLDER


Fig. 5. Because the ohmage of thermistors varies in manufacture, you may need to alter the values of R1 and R2. See text.

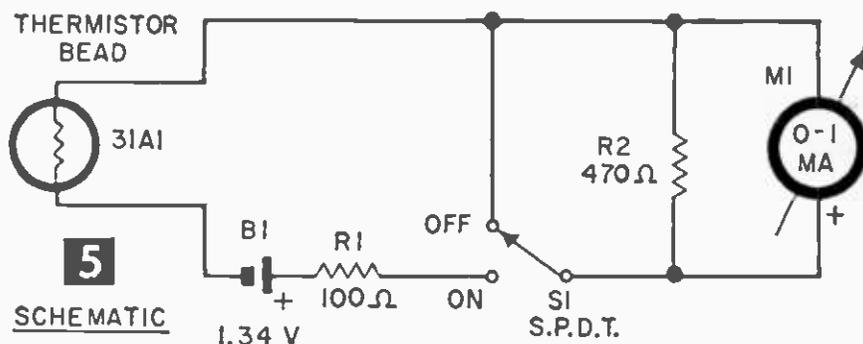

5 SCHEMATIC

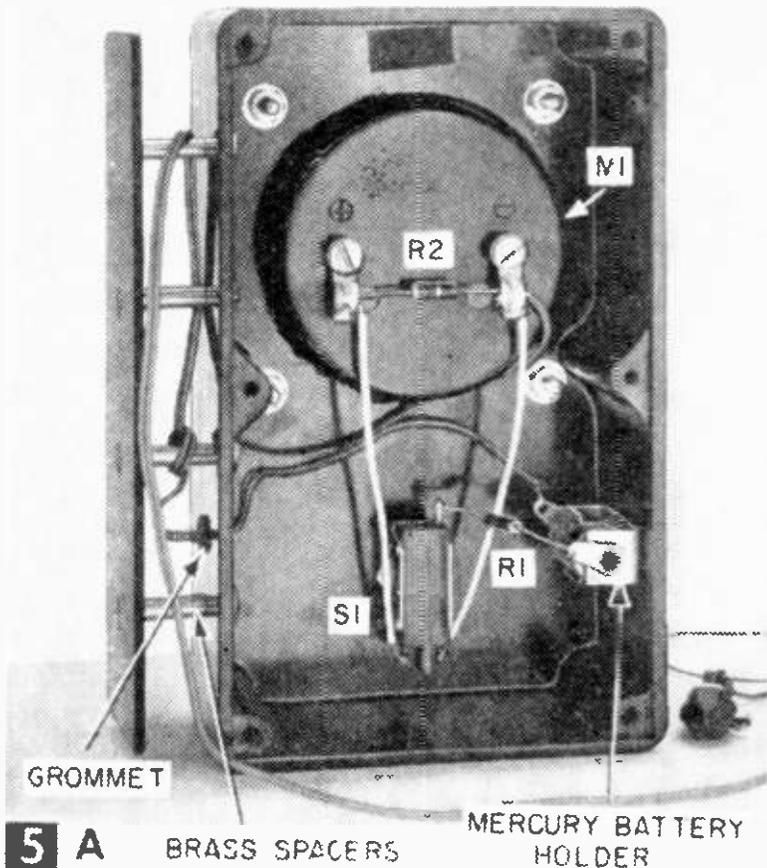

5 A

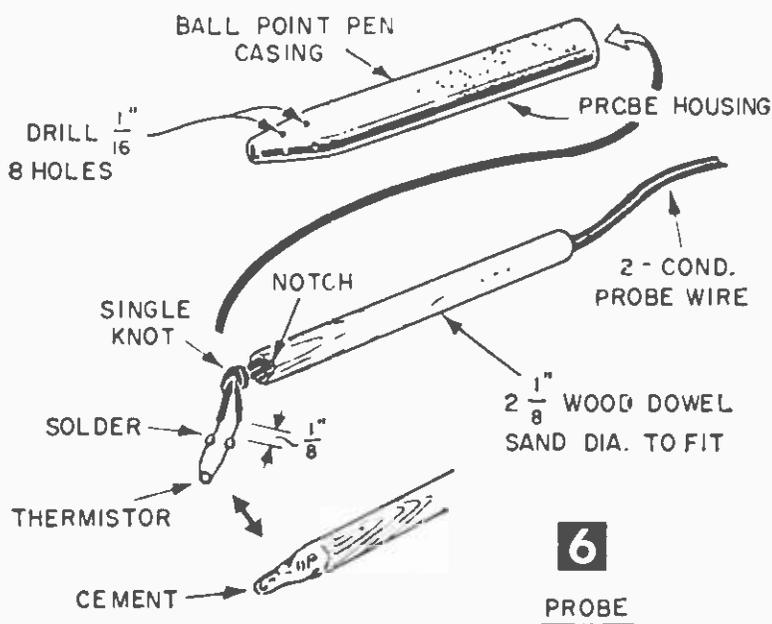

6 PROBE

After the joint is cool, with a needle or small probe gently bend the other thermistor lead until it lays parallel to the first one. Solder as before. Then carefully ease the bead end of the thermistor into a point about 1/8-in. across, so it projects straight forward from the section of wire feeding into the wood dowel.

Testing the Thermistor. Now with the battery in the holder and the switch on, the meter should read about 3/4 full scale. If the pointer

doesn't move, one of your leads is not perfectly soldered. Resolder, noting that the meter should deflect when a good joint is obtained. Blow lightly on the thermistor and the reading should change.

Waterproofing Probe. Coat about 3 inches of the probe cable with polystyrene coil dope, or model cement. Pull the cable, wet with the cement, back into the dowel until the knot rests firmly against the notched end and allow to dry for several hours. Then dip the thermistor and connections in the cement and dry for at least an hour. Apply additional coats and dry overnight. Then rub paraffin or beeswax on the wood dowel and insert gently into the plastic casing, so that the thermistor tip is slightly below the upper four holes in the tapered end. Now apply the adhesive wire markers to indicate each foot of depth on the cable.

Calibrating the Meter. Take the meter out of the plastic case, and remove the four tiny screws from the rear of the front flange. Working in a clean dust-free place, carefully take the cover off and apply numbers left over from the wire marker set, to the dial, so that your meter reads from 0 to 100. Then letter "degrees F." on a narrow strip of white adhesive tape and place it over the MA label on the meter face. Replace meter in case and reinstall using the waterproofing gasket (Fig. 3).

Remove the plastic probe cover and gently lay the tip of the probe against an ice cube. The meter should read 32. Now heat some water to 90° F, immerse the probe in it, and note the meter reading. Cool the water to 80° and check the meter reading. Repeat at each 10° step down to 40. The meter should indicate the correct water temperature within ± 2° from 32 to 80°. Above 80° the error becomes slightly higher.

If the meter reading is more than 1° off at 32 and 70° it can be corrected by changing the value of R1 and R2. To do this, simply change R2 to cause the reading to be correct at 32°, and R1 to give a correct reading at 70°. Use a smaller value R2 to decrease the reading near 32° and a larger value R1 to decrease the reading near 70°.

Since these two resistors interact it may be necessary to change them alternately until the correct readings are obtained. If you



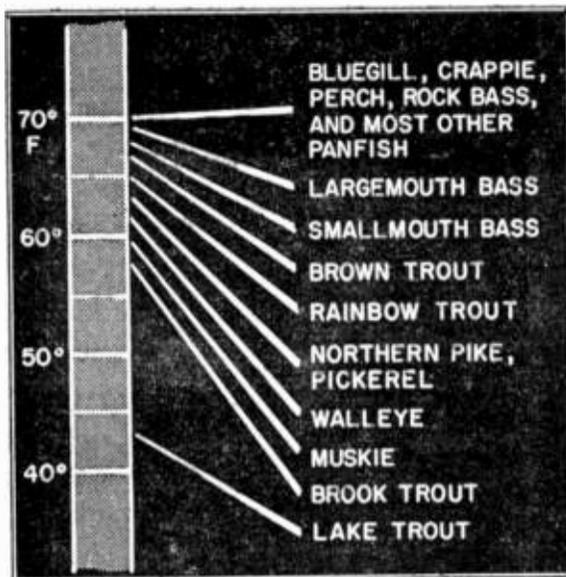


TABLE A.

Typical feeding temperatures.

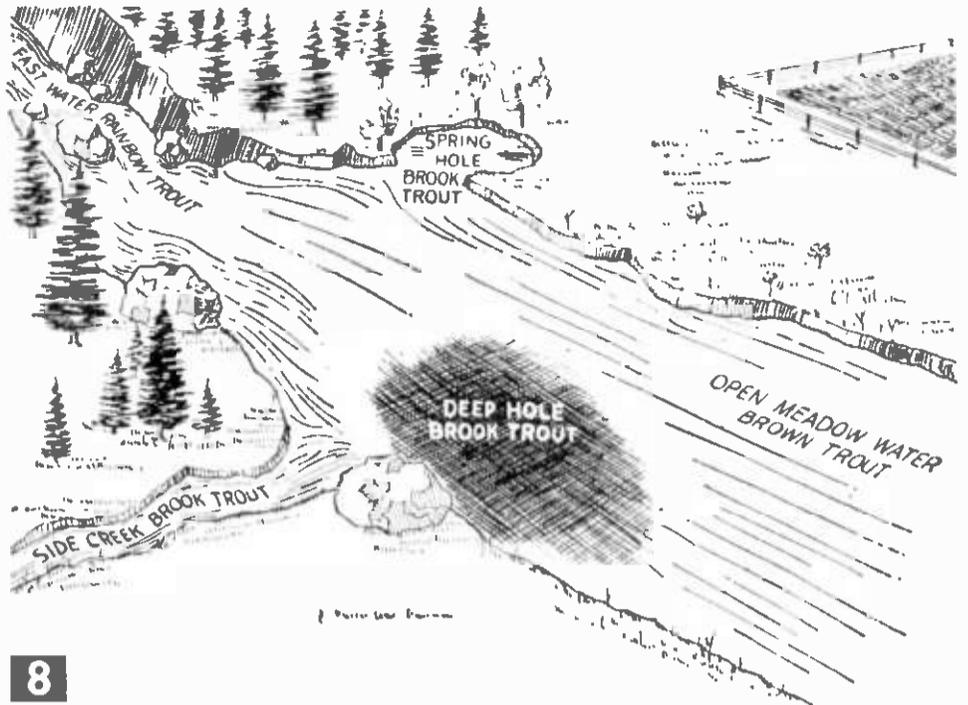

8

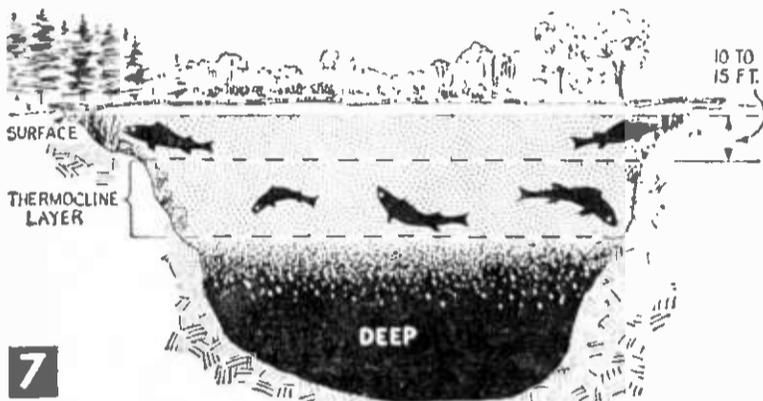

7

wish, these two fixed resistors can be replaced with variable controls. Replace R1 with a Mallory Type U-2, 500 ohm control, and R2 with a Mallory Type U-4, 1000 ohm control—both available at Lafayette Radio.

Seal the rear surface of the meter flange and the bottom cover of the case with plastic tape. Cement the meter movement adjustment screw on the front and the instrument is completed.

How Circuit Works. The temperature sensing probe is a special kind of resistor known as a thermistor. When this fast-acting thermistor is heated its resistance goes down, and when it is cooled its resistance goes up. Wired in series with the meter and battery it will cause the meter to read lower as the temperature becomes lower, and higher as the temperature becomes higher. The meter reading therefore shows the temperature at the probe.

Resistors R1 and R2 proportion the current so as to give a convenient meter reading, and switch S1, in the Off position, damps the meter movement to prevent damage to the pointer while the unit is being carried.

Fishing Hints. Tie several fishing sinkers to the cable just above the probe. Allow enough string so they hang below the probe to prevent damaging it. Lower the probe into the water and turn the switch on. Almost immediately the meter will indicate temperature. As the probe sinks down, temperature will normally decrease gradually for the first 10 to 15 feet. Then, you'll go through a second

thermocline layer where the temperature drops more rapidly, followed by a third layer which reaches to the bottom and again decreases slowly in temperature (Fig. 7). This is the normal pattern for quiet lakes, ponds and rivers. Near currents, springs and disturbed water, the pattern will take another form.

Now you can make a plot of your fishing spot, being on the lookout for cool springs that can easily be tracked down to their point of entry by following colder than normal areas back to their origin. Near such cool springs, many fish such as muskie gather on hot days. Drop your line in such a spot and they'll bite often.

Other places to check are river openings and spots where deep depressions have been formed on the bottom by currents (Fig. 8). Such deeper water will be cooler and thus more attractive to fish on hot days. After you plot your spots, noting the temperature where fish bite the best, you'll be able to go back any day, hot or cool, and get results after spot checking the temperature.

The exact temperature range preferred by various species will vary from Table A when local conditions are unusual. For example, rushing water will contain more oxygen than still water, and therefore, the fish will seek a warmer temperature. Also, when barometric pressure is high, the water will absorb more oxygen. When the barometer is high, the fish will seek a warmer range and when the pressure is heavy and depressing, they will prefer a cooler temperature.

Clip the chart from the page, and fasten it to the back of your thermometer case with tape and a few coats of varnish. The tiny mercury battery should last for over 800 hours, and since its output is constant at 1.34 volts, your readings should remain accurate throughout the season. But at season's end remove the battery to avoid damage due to battery leakage.

Battery-Powered Portable Record Player

By FORREST H. FRANTZ, Sr.

A PORTABLE record player adds zest to picnics, barbecues, beach trips and other outdoor activities. With the younger set, a portable record player has always been symbolic of good times. But, till the mighty miniature electronic marvel—the transistor—came along, the outdoor record playing crowd squeaked along with low volume, non-electronic amplifiers or went broke buying B batteries. And, generally, you cranked a spring type motor by hand.


Today, however, you can get plenty of volume with reasonable fidelity from a transistor amplifier, and low current 6-v. motors are available to relieve the strain on your cranking arm. The record player described in this article can be built for approximately \$25. (You can cut the cost to about \$20 by making some compromises that I'll describe.) Construction time is six to 20 hours depending on your skill and the tools you work with. Operating energy for the record player is supplied by four inexpensive regular size D (#2) flashlight batteries. You can expect a set of batteries to last for roughly 40 hours of playing under ordinary interrupted usage.

There are five major electrical and electronic components in a record player system (Fig. 2). The turntable imparts the "timing" and the mechanical forcing of the record grooves for transfer to the pick-up. This me-




1

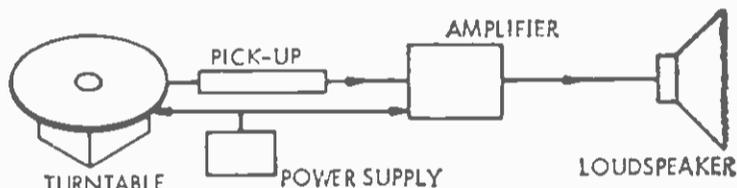This record player will provide many hours of outdoor entertainment.



2 RECORD PLAYER SYSTEM

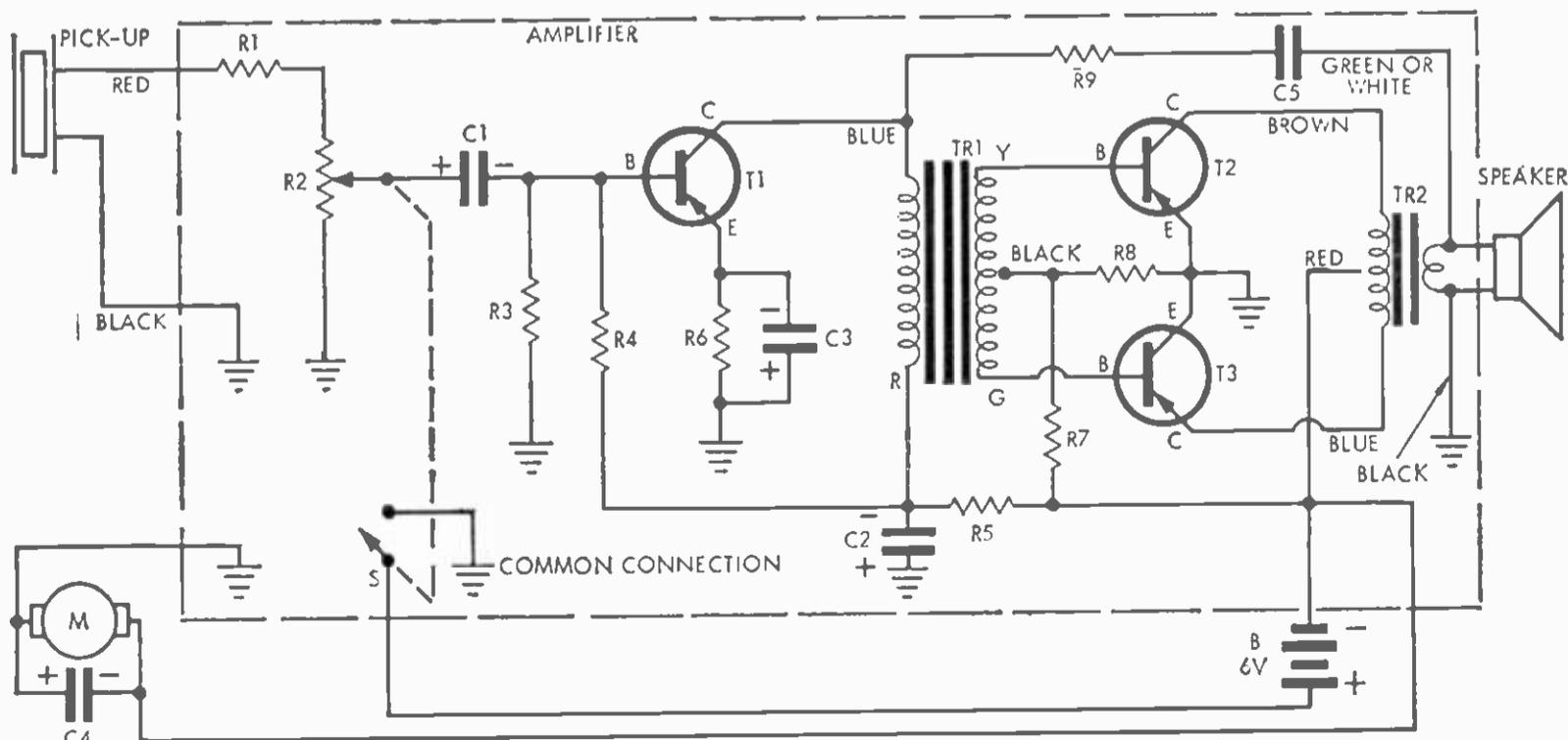chanical energy is changed to electrical voltage by the crystal. The voltage is applied to the amplifier (powered by the power supply) which supplies amounts of this power to the speaker in proportion to the pick-up voltage.



3 SCHEMATIC

In this record player, the turntable speeds are 16, $33\frac{1}{3}$, and 45 rpm. The turntable is operated by a small 6-v. dc motor. The motor and turntable assembly are obtained as a single complete unit.

The pick-up should contain a high output crystal cartridge (1 v. or more) and it should be of the turnover variety, which contains a large needle for 78 rpm records, a smaller needle for slower speed records. A pick-up of this type can be obtained more readily and at a lower cost than a slow speed pick-up, and in addition the cartridge may be turned to the 78 rpm position to prevent damage to the slow-speed needle while transporting the record player.

The first transistor in the amplifier (see schematic, Fig. 3) is the driver stage for a pair of transistors in the output stage. The output stage is designed so that the power that the batteries must supply is approximately proportional to the signal. This feature conserves battery power.


I used a 3-in. speaker, but left enough room on the panel for a larger speaker if desired.

Panel and Mounting Base. The panel layout is shown in Fig. 6. The panel material is $\frac{1}{8}$ -in. tempered Masonite, both surfaces smooth. Lay out the dimensions on the panel before you start drilling and sawing. When you drill the holes, place a piece of scrap Masonite or hardwood under the panel so that the back edges of the holes come out clean without burring or flaking. Use a $\frac{5}{32}$ -in. drill for all the holes and enlarge these to other dimensions where required with a taper reamer.


Cut the turntable opening by drilling several starter holes and sawing with a hacksaw blade. If you have a jig saw or a band saw, you can save some time by using it to cut this hole. The edges of the turntable hole may be dressed down with a file.

The mounting base is made from 1-in. pine which has a dressed thickness of $\frac{3}{4}$ -in. It is ripped to a width of $2\frac{1}{4}$ in. Two pieces are cut to a length of 14 in. and two pieces are cut to a length of $7\frac{1}{4}$ in. They are nailed together as in Fig. 7 to form the base.

The Amplifier. The circuit diagram is shown in Fig. 3. Pictorial views of the wiring are shown in Fig. 8 (top of wiring board) and 9 (bottom of wiring board). The wiring board is the right size as purchased. Two holes must be drilled in this perforated board. One is for mounting the volume control and the other two are to mount the wiring board on the record player panel. These holes are $\frac{1}{4}$ -in. in dia. and may be located from Fig. 8. The centers of these holes coincide with perfora-

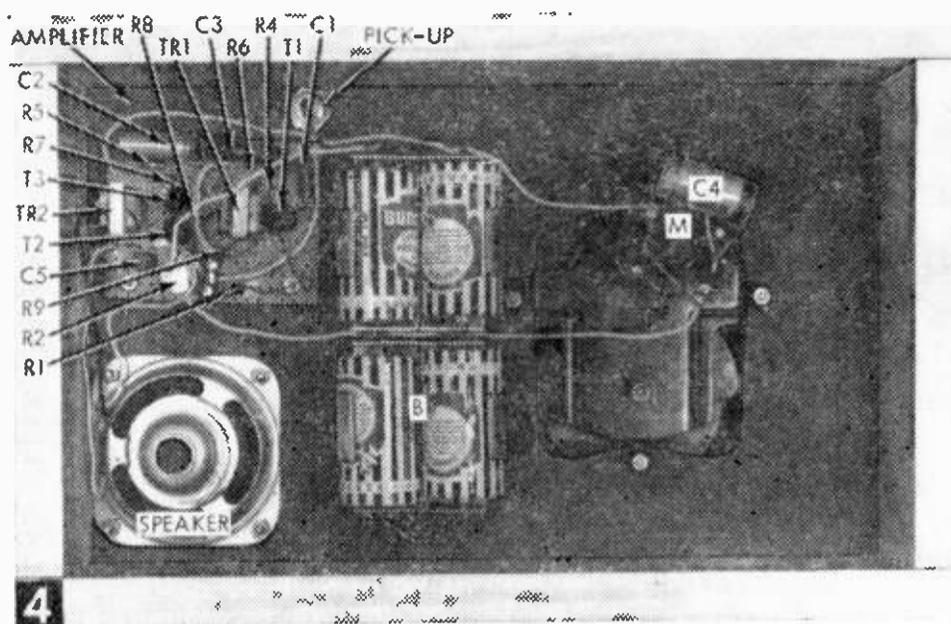

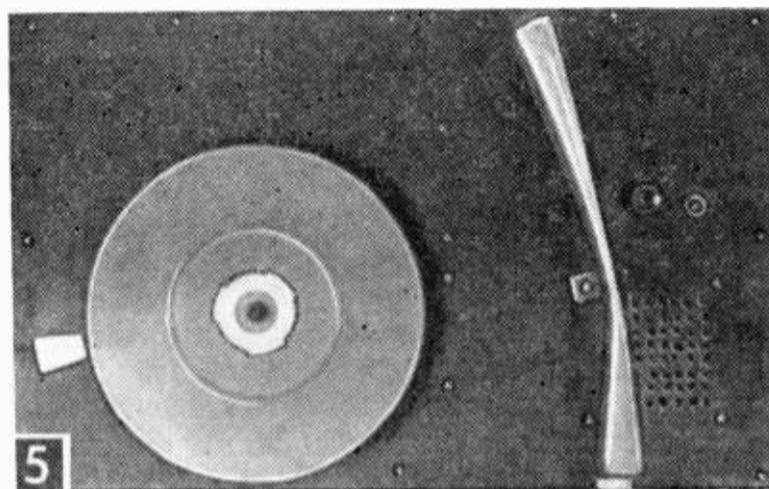Bottom view of the completed record player.



Top view of the record player panel.

tions on the wiring board.

You may also want holes to mount the two transformers instead of the slots shown in Fig. 4. The choice will depend on whether you obtain transformers with tabs designed for mounting in slots or with holes for fastening with small screws and bolts. My output transformer was equipped with tabs. But, you'll note that the driver transformer which I used was equipped for screw mounting, and I bent mounting lugs down so that it could be tab mounted. If you tab mount the transformer, cut the slots with a hacksaw blade.

Mount the volume control (R2) and the transformers (TR1 and TR2) first. Next, mount capacitors C1, C2, and C3 and resistors R1, R3, R4, R5, R6, R7, R8 and R9. These components are mounted by pushing the pig-tails through the wiring board perforations. The same applies to transistors T1, T2 and T3. Now wire the amplifier. The only additional part which will have to be mounted on the wiring board is C5. Mount it when you get to it in the wiring. Some of the connections were made by passing the component pig-tails through the same perforation. Other connections were made by twisting pig-tails together. The leads were soldered together to complete the connection work. Protect transistors with heat sinks.

The lead to the — battery terminal is about

turntable in the 45 rpm position and raise the 45 rpm center adapter by turning it counter-clockwise.


Place the record player with the end containing the amplifier protruding out over the edge of a table. Place your fingers on T2 and T3 and turn the switch on. The turntable should rotate and T2 and T3 should not get hot. Then feel T1. If any of these 3 transistors gets hot, turn the switch off, and look for trouble in the wiring. If the transistors don't get hot, turn the cartridge to the 33-45 position in the tone arm and place the tone arm on the record. If you did everything right, there should be music.

To play 33 $\frac{1}{3}$ rpm records, change the speed lever to 33 $\frac{1}{3}$ rpm. Let the turntable get up speed before you place the arm on the record. The 33 $\frac{1}{3}$ rpm records are heavy by comparison to the 45 rpm records. And because of the larger diameter of the 33 $\frac{1}{3}$ rpm records, there's more torque on the turntable bushing due to the tone arm pressure.


If the 45 rpm record sounds slow or seems to play at variable speed, check the speed change lever to be sure that it's in the correct position. If this isn't the cause of the difficulty, remove the turntable retaining pin and turntable, and put a few drops of household oil on the turntable spindle. Also check the vertical position of the rubber turntable rim drive wheel with respect to the plastic drive on the motor (see Fig. 10). This should clear up any difficulty that you might have.

Bear in mind however, that as the batteries go down, some reduction in speed will occur. It may be noticeable at 33 $\frac{1}{3}$ rpm while it may not be noticeable at 45 rpm because of the difference in record size and weight.

You can economize on the parts cost of the record player. GE 2N107 or RCA 2N109 transistors may be used in place of those specified. C3 may be eliminated if R6 is changed to 100 ohms and R1 is decreased to 47K. Almost any crystal pick-up may be used in place of the 2-v. unit specified, as long as it has an output of 1 v. or more. For lower output units, you may have to decrease the value of R1. The really ambitious economy-minded builder might want to make his own turntable unit. You can buy the required motor for a dollar or two. I didn't have such

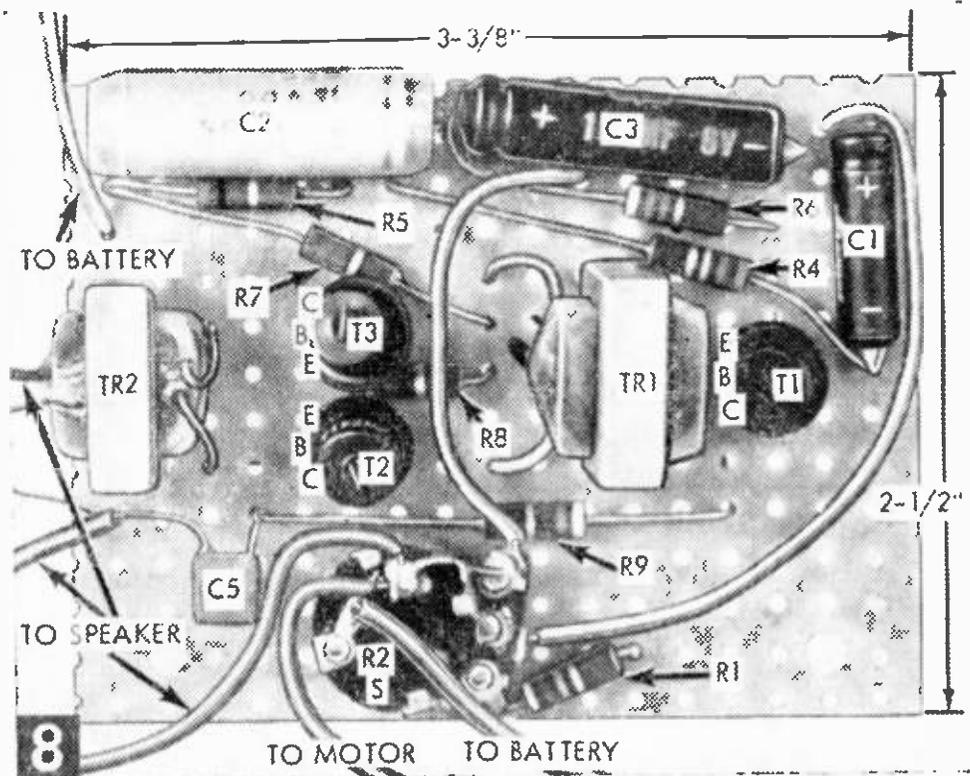

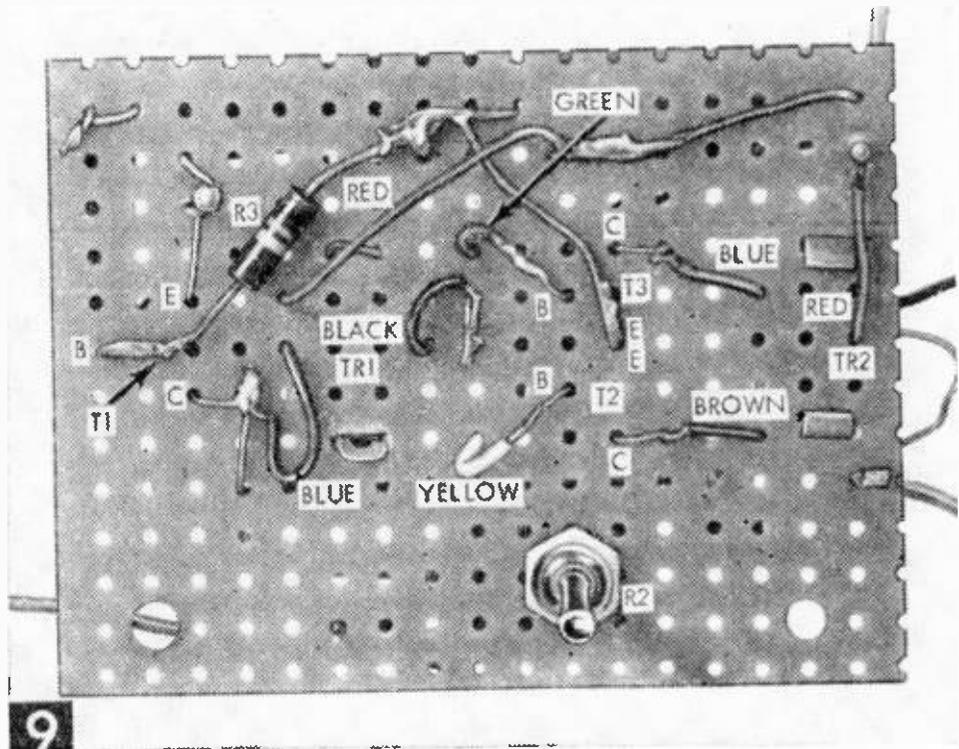Top view of amplifier shows parts mounting and wiring.




Bottom view of amplifier shows wiring.

extremes in mind of course, when I suggested that you could cut the cost to \$20. If you go that far, you can probably get down close to \$10!


On the luxury improvement side, you can add a tone control by replacing R9 with a 10K volume control. Use one of the end and the center terminals. Another improvement would be a larger speaker.

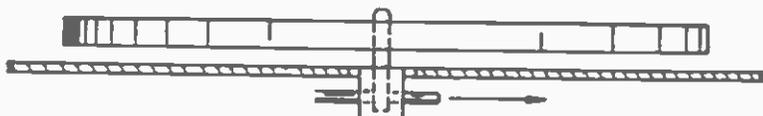To make the record player look its best, the base may be painted or upholstered with cloth or plastic. Do this before you mount the parts. Or, you can staple the material on corrugated cardboard panels and cut them to fit over the panel and sides. This way, the screws will be hidden. The panels can be fastened with a sparing amount of glue so that they can be removed and replaced as



10

TO REMOVE TURNTABLE, PULL RETAINING PIN

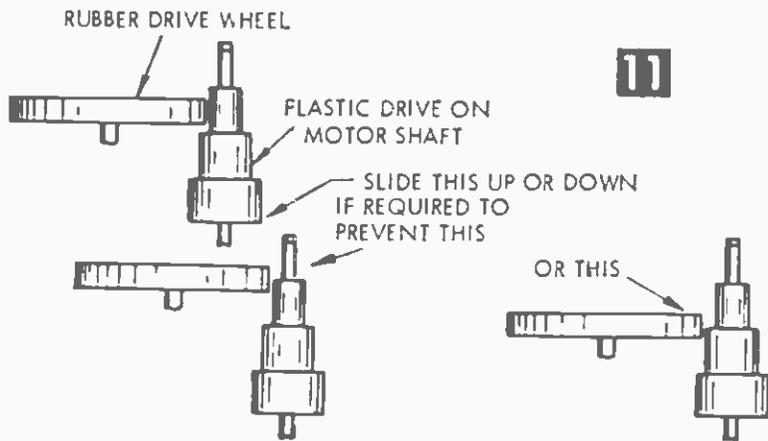


11

required for maintenance.

To make the record player truly portable, you need a case. I found an old beat-up overnight case in the attic that was just right. Note that the base is fastened to the original lid of the case. This allows freedom to play larger records; you couldn't play them if you mounted the base on the actual bottom of the case which has high sides.


If the case does not come down against the pick-up when it is closed, add a piece of wood in the top of the case that will come down snugly on the arm when the case is closed. This will prevent the arm from swinging off of the rest and being damaged when the record player gets rough treatment en route to your favorite picnic spot.

Emergency Battery Clip

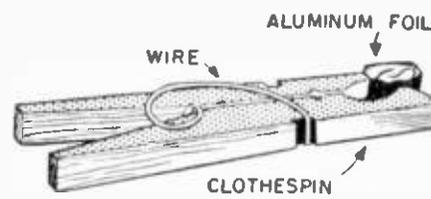

• If you run out of battery clips while doing an electrical project, make a substitute clip by wrapping aluminum foil around the tips of a spring-type clothespin. Wrap wire around foil.—J. HARVEY.

Insulation Scraping Tool

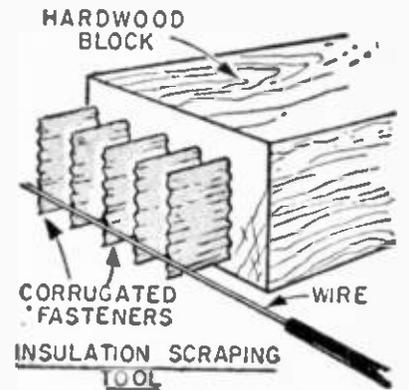

• This simple and long-lasting tool is practical for scraping and cleaning insulated wire to make firm solder connections. To make it, simply drive several corrugated fasteners into the end of a hardwood block.—G. E. HENDRICKSON.


Miniature Plugs and Jacks

• Those tiny snap-fasteners used on clothing make good miniature plugs and jacks for pocket radios, hearing aids, and the like. You can mount either the plug or jack on the set's case with plastic cement or you can fuse the connector in place by heating it with a soldering iron. The connectors can be used for either external headphone or antenna lead connections.



"It's just until I get the kit assembled, Honey."

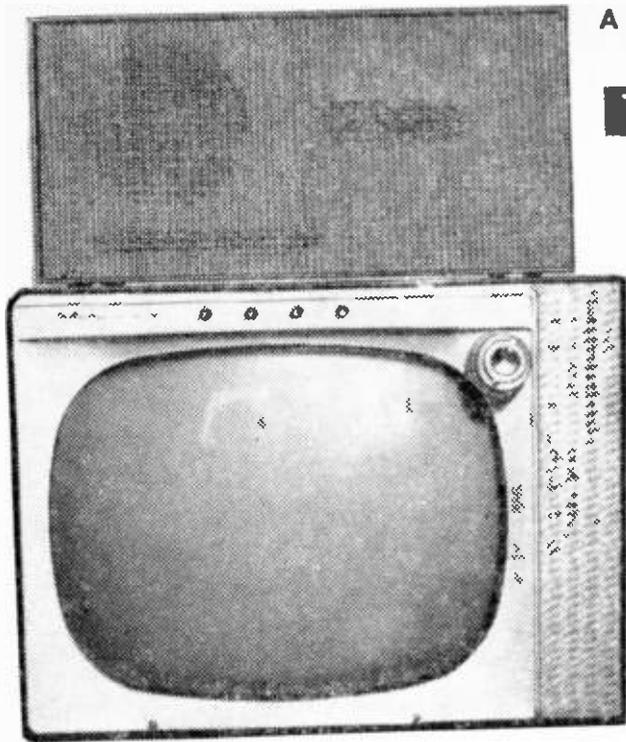A typical hi-fi speaker addition to a TV set.



1

Add A Speaker System to Your TV

Hi-fi reception from your TV or radio! It's yours by adding a speaker system and inverse feedback


By FORREST H. FRANTZ, Sr.

MOST of the TV sets selling for \$300 or less contain a small 4-6 in. loudspeaker. You can't expect good quality sound from such a small speaker. Even if you have a larger speaker it may not sound good on high frequencies. Also, few low-price TVs and radios have speaker enclosures designed for best fidelity.


You can buy a speaker system kit that will put you in the hi-fi business. One of the least expensive (\$29.50) ducted port bass reflex speaker systems available is the handsome Windhaven System (Windhaven Radio Co., Box 74, Baroda, Michigan). This has an impedance of 3-4 ohms which matches most inexpensive radio and TV set output transformers. The frequency response is ± 5 db from 60 to 8000 cycles.

For better frequency response you have to pay more in dollars and time. The Heathkit SS-3 at \$34.95 is within ± 5 db from 50 to 12,000 cycles. This speaker system contains an 8-in. woofer and a tweeter. A little work on the cabinet and fifty cents worth of grille cloth and trim will produce a neat piece of equipment.

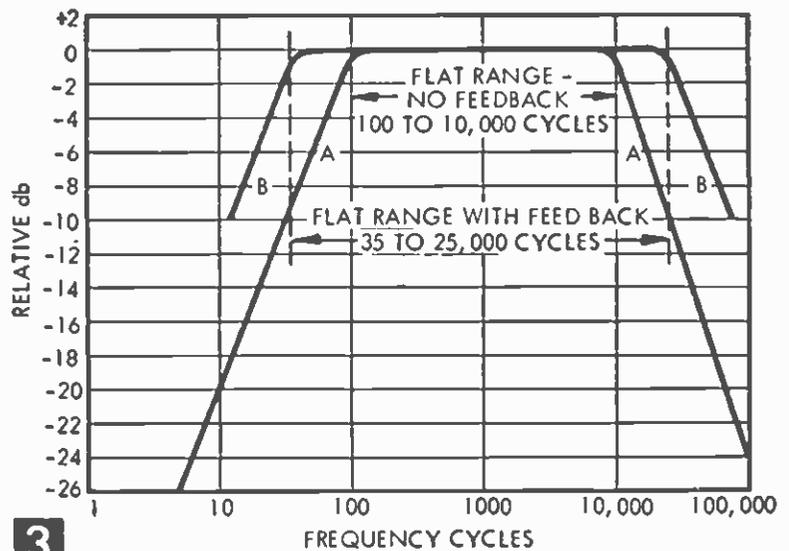The SS-3 is intended for hi-fi systems and has 16 ohms impedance, so you will have to replace the 3-4 ohm impedance output transformer on a low-price TV. At the same time you can improve the quality of the amplifier



3

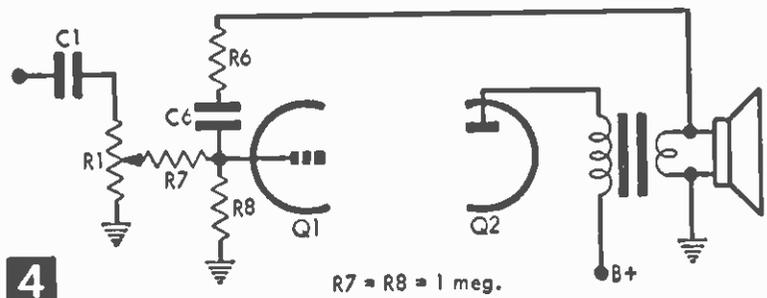


4

on your TV set or radio by incorporating inverse feedback into it.


Figure 2 shows a typical TV or radio audio amplifier stage. The amplifier is resistance-capacitance coupled. Capacitor C1 transfers the signal from the detector tube (usually a diode, and frequently within the same envelope as tube Q1) to the volume control R1. The setting of R1 determines the amount of signal voltage that is applied to the grid of Q1. Q1 is a high gain amplifier tube which usually has a voltage gain of about 50. The signal, amplified about 50 times, appears at the plate of Q1.

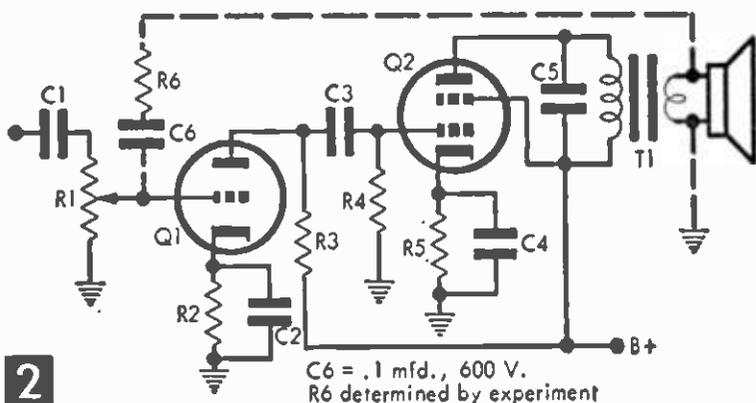This signal is fed to Q2 thru capacitor C3 which passes only the audio signal but iso-



2

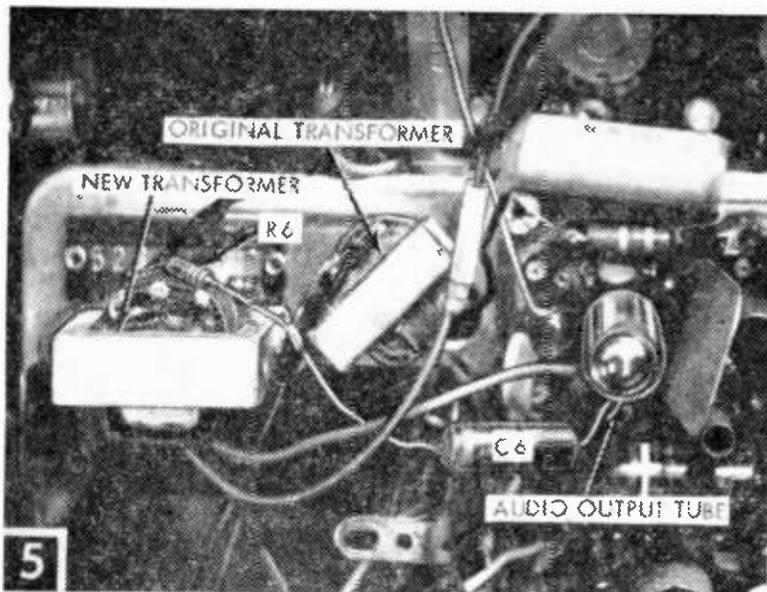C6 = .1 mfd., 600 V.
R6 determined by experiment



Mounting details of the substitution of a higher impedance output transformer to match the 16-ohm impedance of the hi-fi speakers.


lates the dc grid bias voltage for Q2 from the high plate voltage of Q1. Q2 amplifies the signal voltage about 30 times. But, the load impedance of Q2 is much less than the input impedance, and there is therefore a large current gain in this stage too. Power gain is voltage \times current gain, and this stage is therefore usually referred to as the power output stage.

The impedance of dynamic loudspeakers is very low in contrast to the load impedance required for a vacuum tube, so the speaker is coupled to the output stage through an output transformer (T2).

A good speaker and output transformer are expensive, so most inexpensive TV's and radios don't have good ones. To get good fidelity you have to replace both.

Then only the fidelity of the amplifier limits the fidelity of the system. The coupling capacitors C1 and C3 and the cathode by-pass capacitors C2 and C4 (usually electrolytics) limit the low frequency response. Capacitors that are in parallel with the signal (such as C5) limit the high frequency response. The capacitance of C1, C2, C3 and C4 should be increased to improve the low frequency response, and C5 should be decreased or removed entirely to increase the high frequency response.

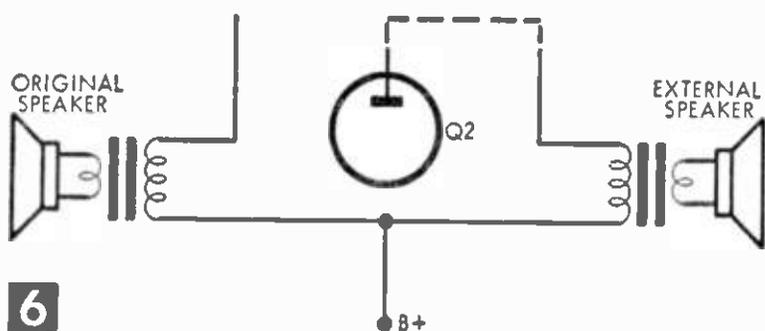
But you can improve fidelity more than this by incorporating inverse feedback. In most cases you can get away with merely increasing C1 and C3 by a factor of 10 and



by removing C5 if you incorporate inverse feedback.

Inverse feedback is graphed in Fig. 3. Curve A is a typical response curve for a low quality amplifier. If a part of the output signal is fed back to the input of the amplifier in opposition to the input signal, it will flatten the curve out to curve B. More signal feeds back at the mid-frequency range than at the high or low frequency ends of the curve where gain drops off. This flattening action gives better frequency response. Also, distortion which occurs during the amplification process is cancelled.

How do you incorporate inverse feedback in your amplifier? The dotted lines in Fig. 2 show a simple scheme for incorporating inverse feedback in an amplifier that does not already have it. One side of the output transformer secondary is grounded. The other side of the secondary is connected via C6 and R6 to the grid of Q1. The value of C6 should be about 0.1 mfd. at 600 v. The value of R6 and the value and setting of R1 determine the

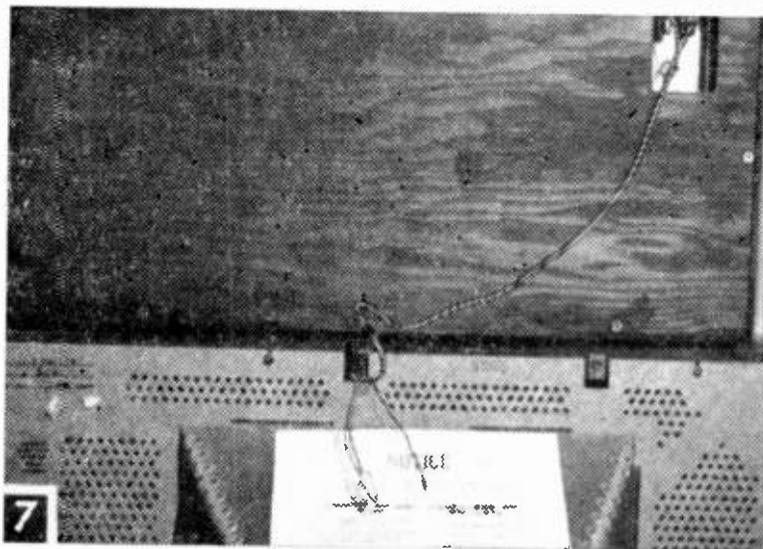

Showing the lamp cord used to connect the substitute output transformer to the crossover network of the hi-fi speaker cabinet.

amount of feedback that will be obtained.

Choose R6 so that you can get sufficient volume to meet your requirements on the weakest station when R1 is set to full volume.

The matter of which side of the speaker to connect to ground and which side to use for feedback doesn't present a problem. If you connect it the wrong way, you'll have positive feedback and the result will be an increase in volume or squealing. When the proper connections are made, volume with feedback is lower than volume without feedback.

It is desirable to have inverse feedback independent of the volume control setting. In Fig. 4 two fixed 1 meg. resistors (R7 and R8) have been added to the input circuit. R7 reduces the variations in input resistance from the grid of Q1 to ground. R8 performs as part of the feedback voltage divider which includes R6.

Typical Installation. Figure 5 shows a typi-

cal set of changes made in a TV set to incorporate inverse feedback and permit the connection of a 16-ohm speaker system to the set. The transformer that was added in the set in this case was a relatively inexpensive Lafayette TR-12 universal replacement transformer.

A piece of lamp cord connects from the secondary to the external speaker (Fig. 7). The feedback resistor is connected to one of the transformer secondary taps. The other end of the feedback resistor connects through capacitor C6 to the grid of the output stage. Feedback in this case is only around one tube since the detector output drives the single audio stage in this set.

The transformer primary can be connected to the same points where the original output transformer leads were connected. The original transformer primary leads should be disconnected in this event.

However, you'll be able to change from the external to the internal speaker without having to remove the back of the set if you use the arrangement of Fig. 6. A lead from the plate of the output tube and the plate end of each transformer is brought out through the rear cover. The plate lead and the new transformer lead are twisted together and taped. The original transformer plate lead is taped.

If at any time you wish to disconnect the external speakers and use the internal speaker, you simply disconnect the plate lead of

the new transformer from the TV set output tube plate lead, and connect the output tube plate lead to the other transformer lead. The leads should of course be taped.

When you install the new output transformer you'll have to select secondary taps that meet the impedance matching requirements between the output stage and the speaker. If you don't know the load impedance that the output stage has been designed for, assume it to be 2000 ohms. Then select the transformer connections that match 2000 ohms to the impedance of the new speaker according to the connection sheet furnished with the transformer. This will generally do the trick. You can do some experimenting then to see if another connection arrangement affords any improvements.

Eliminating Power Hum

- An extra 10-mfd., 450-v. electrolytic capacitor connected in parallel with the input filter capacitor of a radio receiver will often reduce or eliminate an annoying power hum. Capacitor values add when in parallel, so you are adding 10 mfd. to whatever capacity value is already in the set. Be sure to observe correct polarity of connections—plus to plus, and minus to minus. The black lead is usually minus.



"It's not often a soap-box orator can hold a crowd like that."

Versatile Code Practice Equipment

By
HOWARD S. PYLE


THE teaching of code to a group of students is made easy with this control unit. The control unit (Fig. 1) with connections to a key and an ac supply line, is a keyed audio oscillator of variable tone and volume, with the resultant tone reproduced in a loud speaker with sufficient audibility to handle a group of up to thirty students.

The control unit is housed in a Hamcab #12. Layout the front panel, chassis and the rear panel according to Fig. 2 and cut the holes for the components. Several holes in the sides of the cabinet are also required. Mount the components (see Materials List). Wire the unit according to the schematic, Fig. 3. The isolation transformer is mounted inside the cabinet.

When you have completed the control unit and have selected a space for the students' table (Fig. 4), make the table of plywood, suitably supported. Wire the table in accordance with schematic (Fig. 5) and Fig. 6.

Through the plug P-1, provided on the table cord, connect the table wiring to the instructor's control unit through the multi-terminal jack, J-2. With the instructor's switch S-2 in the LOCAL position, the audio oscillator is keyed and the reproduction emanates from the loud speaker. All of the table circuits are now connected to the control unit through the cord and plug. Any student whose toggle switch SX is placed in the A position, now has his key in parallel with the instructor's and he, too, may then key the oscillator.

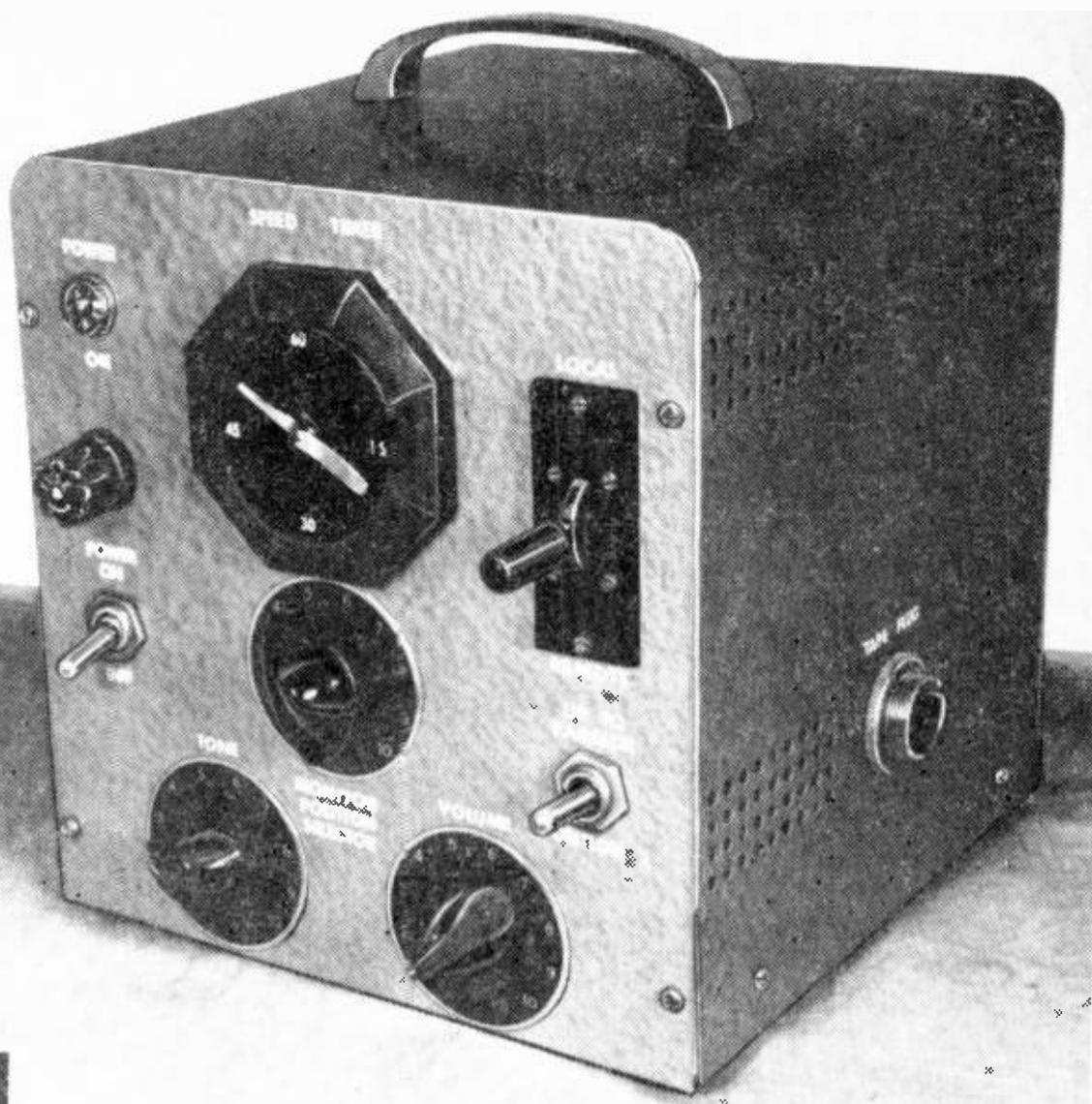One or all students may be so switched in through their SX switches and have keying control of the oscillator, with loud speaker reproduction. The instructor may then send to all students or work with any one or more students two-way, with the rest of the class monitoring.




This control panel is a versatile aid in group code instructions.


Any two or more students may work each other, simulating on-the-air operation and, as the reproduction is still from the loud speaker, the remainder of the class may still monitor all sending and, if desired, may break in on the communication as can the instructor.

Now let's throw the instructor's switch S-2, to the REMOTE position. This immediately disconnects the loud speaker from the circuit and at the same time shorts the instructor's key, thereby producing a continuous, steady audio tone which is fed through J-2 and P-1 to the tables and made available to all students through their keys and head telephone receivers, provided each student has thrown his toggle switch SX to the B position. The second switch S at each student position, if all thrown to the ON position, will parallel all positions, and the same conditions existing when the instructor's switch S-2 was in the LOCAL position will appear except that reproduction will now be in the head telephone receivers rather than through the loud speaker.

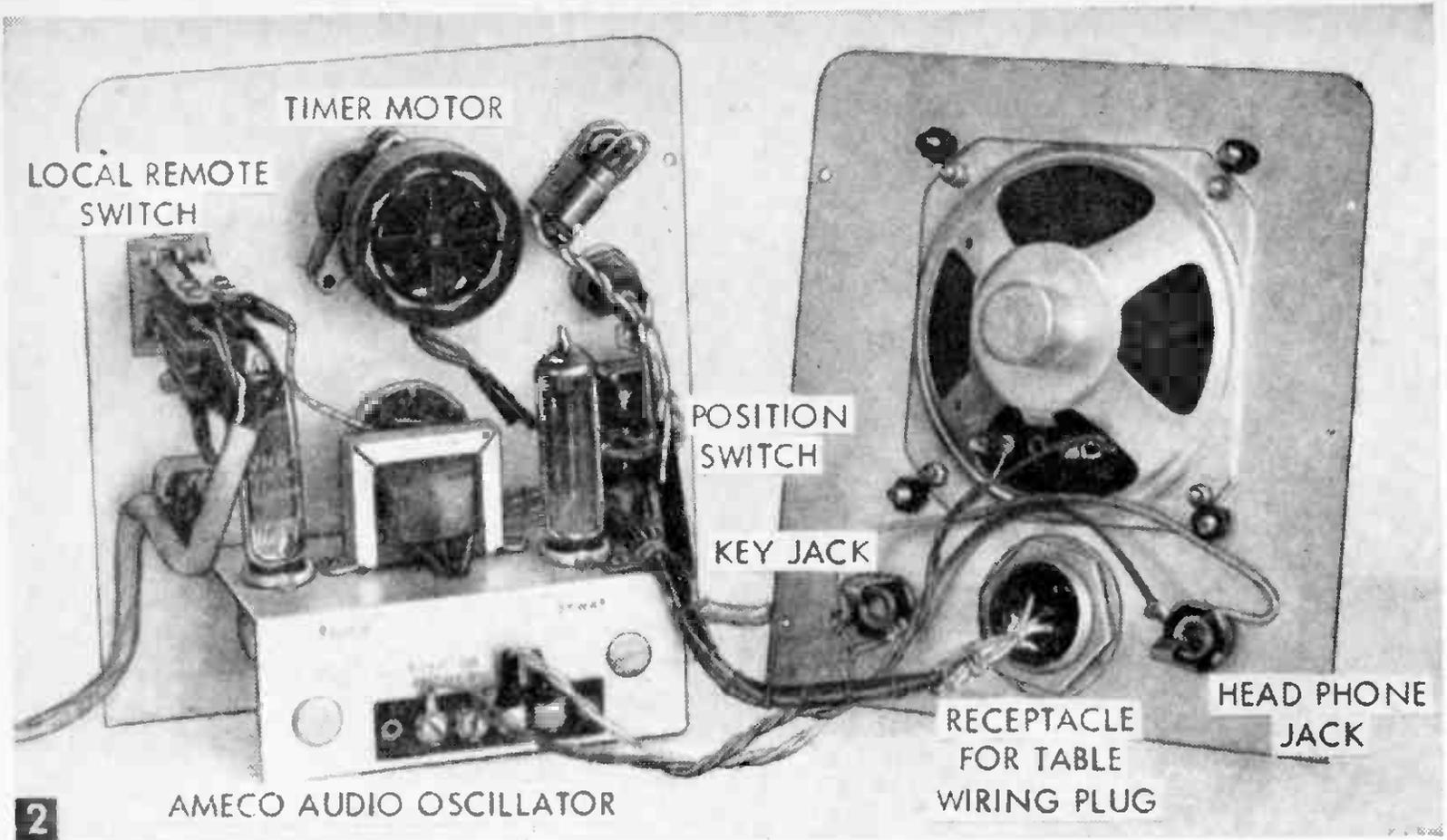Suppose now that we leave the instructor's switch, S-2, in the Remote position and that



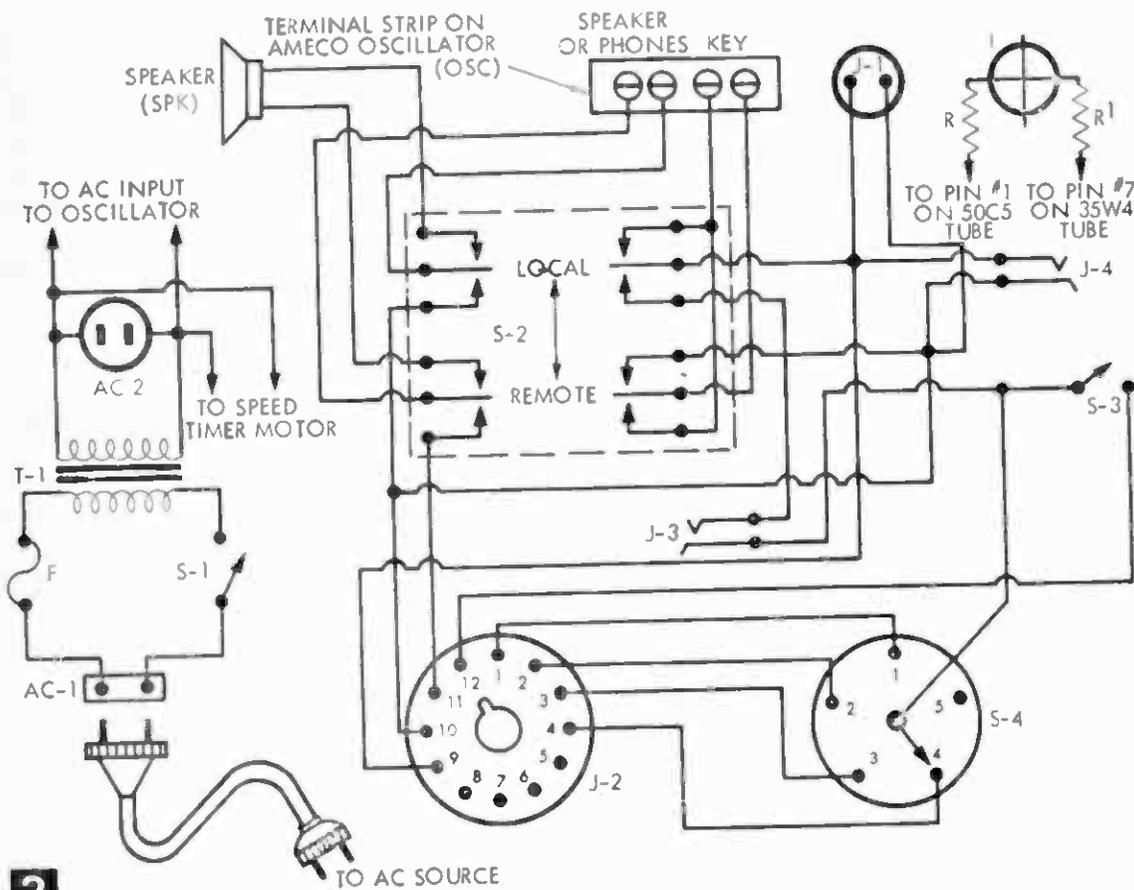Parts layout and wiring of instructor's control panel



two-way with student #3 at the same time that all of the others are engaged in independent individual sending practice. Student #2 need merely throw his switch S to the ON position which will parallel him with student #3 and they may then work together without causing or receiving interference from any of the others! Perhaps student #4 wants to join this group (#2 and #3). He merely asks student #3 to close his S switch to the ON position and he, too, is in!

Student #1 may come in also, if desired, merely by closing his

all student switches S are placed in the open position. Each student may then practice sending by himself with reproduction in only his own headphones and without interfering with any other student who may be engaged the same way. In other words, each and every student may conduct sending practice and listen to himself in his headphones while all other students are doing likewise simultaneously and with no inter-position interference.

Now, suppose student #2 wants to work

S switch to ON.


And the instructor may listen to any individual student, any pair or more who may be working together and may break in on any position or any group of paralleled positions by merely placing his monitor position selector switch S4 on the single position he wishes to monitor or work, or to any of the positions which are paralleled.

The speed timer is a standard electric clock movement and motor—in this case a new Telechron from one of the mail order


electronic supply houses (cost \$1.95) without hands or face. The octagon shaped dial shown in the photos is made by removing the clear plastic cover from a box of dressmaker's pins purchased at the local variety store. Give it a coat of black enamel and fit small white decals, procurable at any amateur radio supply store, to indicate the 15, 30, 45 and 60 second points. A light strip of aluminum is cut and fitted to the central shaft of the clock driving mechanism or a standard sweep hand may be procured from a local watchmaker. This makes one revolution every 60 seconds; five times around equals five minutes and enables the instructor to time code speed.

The audio oscillator is an Ameco or other brand purchased in kit form and the cabinet discarded after removing the speaker. Unfortunately these oscillators are of the ac-dc type and require installation of a small 1/1 ratio isolation transformer on the inside of the control cabinet, feeding the oscillator, clock motor and an ac outlet from the secondary side and with the primary connected externally to the 115 ac line through the power switch and fuse on the control panel. The ac outlet AC-2, of conventional chassis mounting type, is installed on the side of the cabinet to provide a convenient point at which to plug in the ac supply to an automatic tape transmitter, if one is used. If you use a tape transmitter (such as Instructograph) the contacts of the tape transmitter are paralleled across the instructor's key through a two conductor cord and plug with a matching socket mounted on one side of the control cabinet.

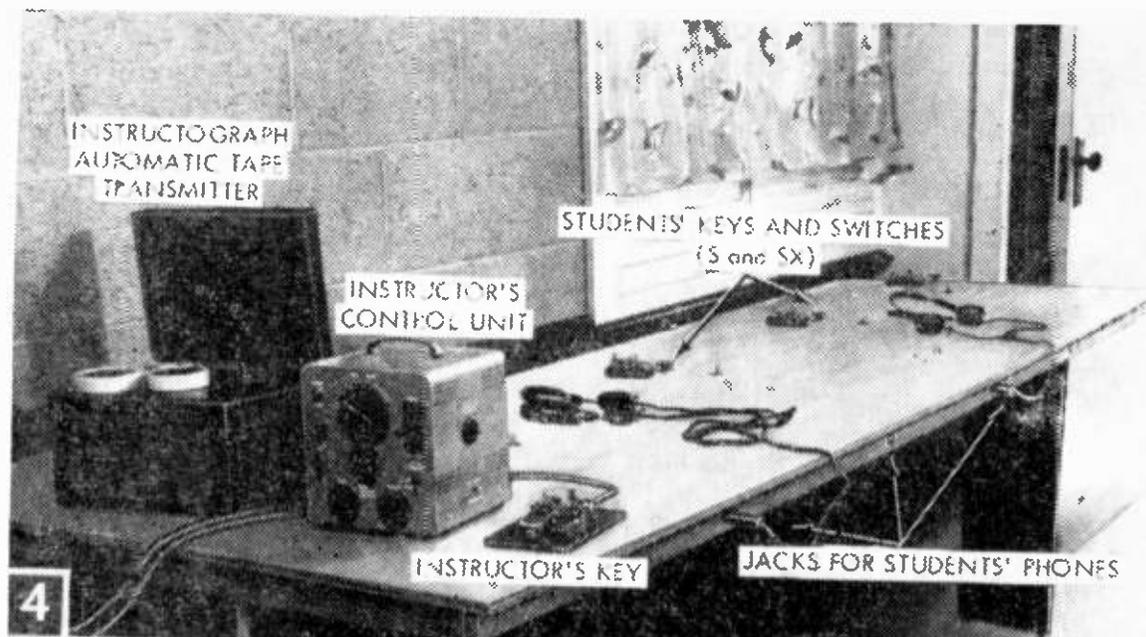For the indicator lamp (I) use an NE-51 neon bulb connected through a 47 K resistor



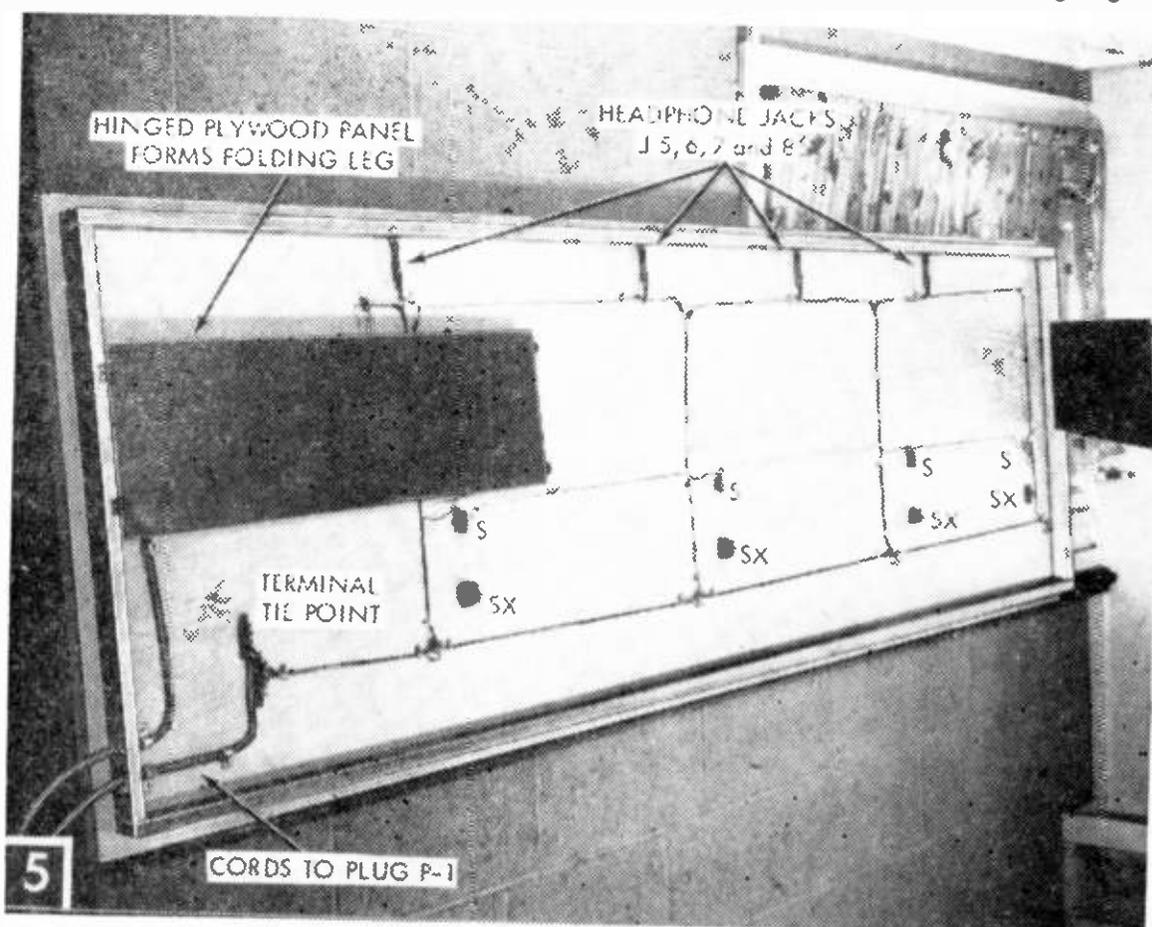Complete equipment as set up in the author's home classroom. This arrangement uses a four position table hinged to wall and with folding plywood wing legs.



Wiring of the students' table.

in each leg, to pin 1 of the 50C5 tube and to pin 7 of the 35W4. The NE-51 element will not fire until the neon gas has become sufficiently heated, which will take a few seconds. Conversely, the bulb will also require a few seconds to extinguish after the ac switch is placed in the off position. This is an added safety factor in that the false indication that the unit is still hot allows any stray high voltage in the oscillator to bleed off before you touch exposed terminals.


If, due to use of high impedance headphones (2000 ohms) with the oscillator, there is an annoying undertone of audio feed-back when unkeyed, place a 670-ohm (not critical value) 1/2 watt resistor across each headphone jack.

MATERIALS LIST—GROUP CODE EQUIPMENT INSTRUCTOR'S CONTROL UNIT

- | | |
|--|---|
| Design. | Description |
| AC-2 | 110 V. AC chassis type receptacle (Amphenol 61-F) |
| T-1 | 115/115 V. isolation transformer (Triad N-51X) |
| F | panel mounted fuse holder, insert type (Buss HKP) |
| S-1/S-3 | SPST bat-handled toggle sws. (Cutler-Hammer 8098) |
| AC-1 | recessed 115 V. AC plug (Cinch-Jones 2RP) |
| SPK | 4" PM dynamic speaker (incl'd. in Ameco oscil. kit) |
| OSC | code practice oscillator (Ameco CPS-KL Deluxe) |
| S-2 | locking type lever switch (Switchcraft 60012-L) |
| J-3/J-4 | open circuit phone jacks (Mallory LA-1 Midget) |
| J-2 | terminal jack (Amphenol Military type AN 12 for up to 8 students or Cinch-Jones Series 300) |
| J-1 | single contact, male microphone receptacle. Insulate from cabinet with extruded fibre washers. (Walsco 1882 or equivalent) |
| S-4 | rotary switch (Mallory 3215J for 4 students, 32112J for 8 students) |
| I | jewel light assembly with NE-51 neon bulb (Drake 10) |
| R-R1 | 47K-ohm resistors, 1/2-watt cabinet with chassis—mount chassis upside down in cabinet to form rigid base plate. (Hamcab 12, L. M. Bender Co., 2528 W. 9th St., L. A. 6, Calif. or supplier) |
| SPEEDTIMER | Telechron electric clock motor with sweep hand |
| PRACTICE TABLE EQUIPMENT (FOR 4 STUDENTS) | |
| P-1 | plug to match J-2 on Instructor's control unit. |
| S | SPST toggle switches—1 for each student (Cutler-Hammer 8098) |
| Sx | SPDT toggle switches—1 for each student (Cutler-Hammer 7140) |
| KEYS | military surplus or builder's choice |
| J-5, J-6, etc. | midget open-circuit phone jacks (Mallory LA-1) |
| R | 670-ohm, 1/2-watt swamping resistors, one for each student |
| CABLE | 12-conductor (for up to 8 students) flexible cable to reach from table to J-2. Conductors may be unshielded. (Belden 8747 intercom cable) |

P-1 PLUGS INTO J-2 ON INSTRUCTOR'S CONTROL UNIT

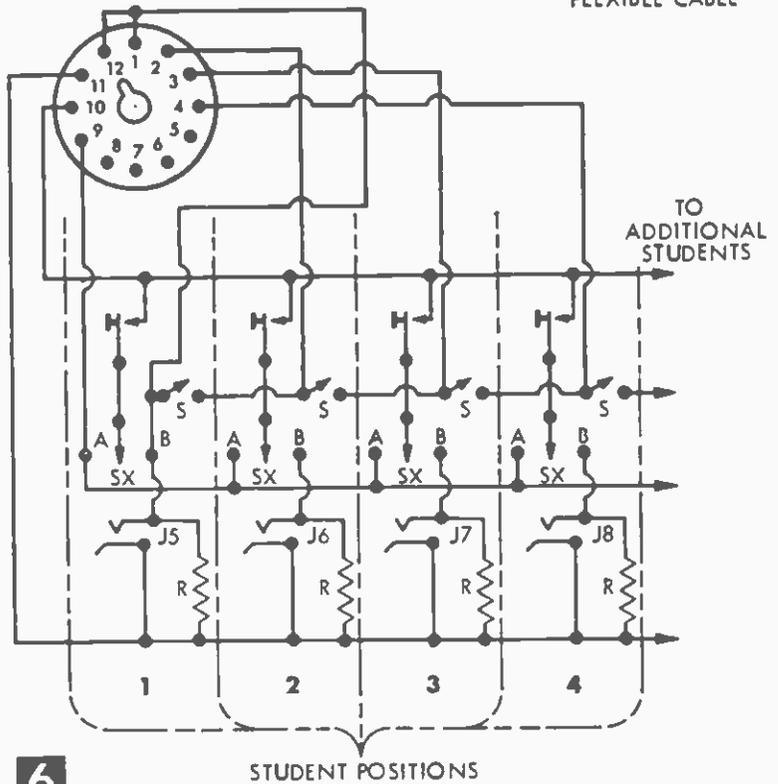ALL WIRES TO P-1 IN 12-CONDUCTOR FLEXIBLE CABLE



6

Wiring for one four-position table; additional tables are wired identically.



"I feel sure that your circuit has not been already patented!"

Quintuplet Duty For Your Radio



How to modify your a-c radio for 20¢ to produce a crystal set amp, earphone radio, AM/FM tuner, record amp, or signal tracer


By ART TRAUFFER

A half hour's work, a 20¢ terminal strip, and the changing of a few connections make it possible for your radio to take on any one of five different jobs.

Run two leads from your volume control out to the terminal strip (Fig. 1) and in effect, you cut your radio in half so you can use either the tuner section or the amplifier-speaker as separate useful devices.

You will need a 3-terminal strip, (Fig. 2) and can get it at any radio supply store or mail order house. Mount it in an uncrowded place on the back of your radio chassis. Protect the chassis wiring with paper taped in place, and cut the slot away with a hand nibbler, or tin snips. You can simply cut narrow strips of the chassis metal, and break them away with pliers. Then drill two holes for the mounting screws. Letter or type the paper terminal label, and cement to the chassis.

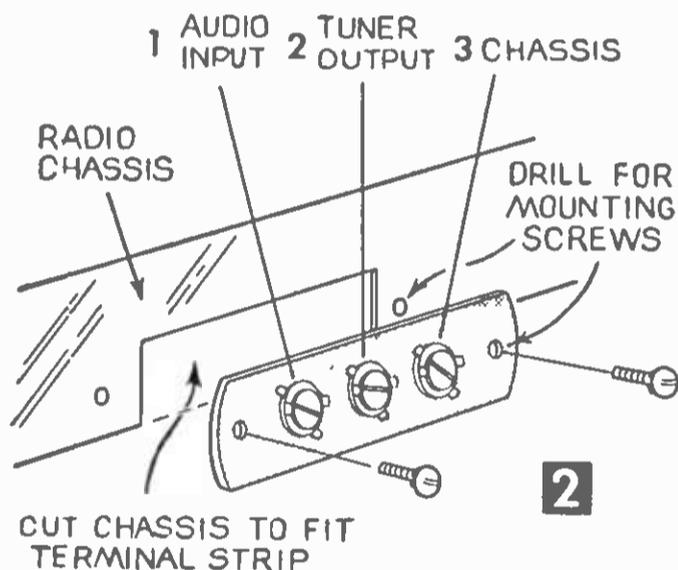
Wire the Terminal Strip into the volume control circuit (Fig. 3). These instructions apply mainly to the better-built type of a-c



radios—that have power transformers instead of the line resistors and “hot chassis” type of construction. But more about this later.

Unsolder the r-f lead from the high side lug of the volume control (Fig. 3) and solder it to the lug on the “tuner output terminal.” Then solder one end of a length of insulated hook-up wire to the audio input terminal lug and the other end of the wire to the high side lug of the volume control.

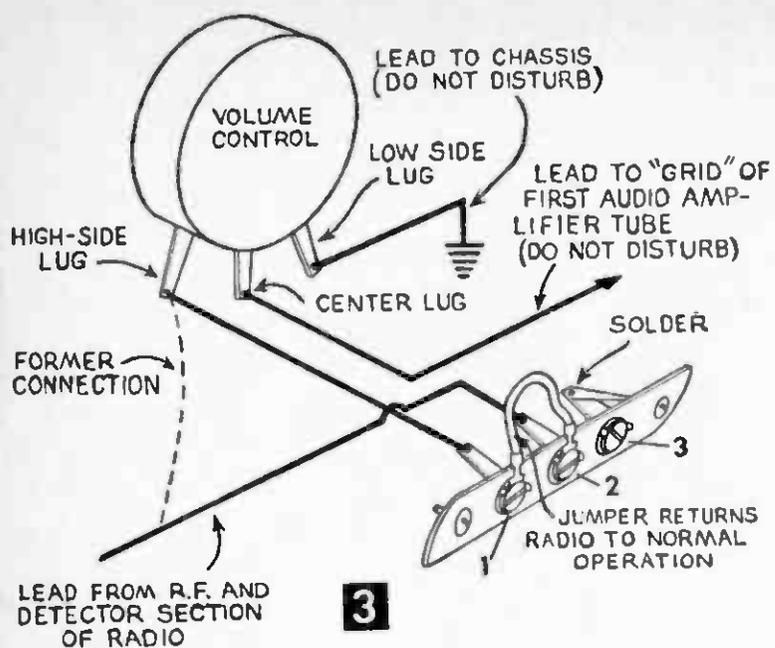Solder the chassis terminal lug to a second soldering lug placed under the nut of the terminal strip mounting screw. This completes the wiring, except for a jumper. Make it by soldering a short wire to two spade lugs. Connected across the Audio and Tuner terminals, it puts the radio back into normal operation.



shielded phono cable to make the connections, with the shield running to the chassis terminal. *Caution.* If you use an a-c/d-c type table radio with a hot chassis, connect a .05 mfd. 600-volt blocking capacitor at X (Fig. 4) in series with the chassis lead. This will isolate the phono pickup from the a-c line voltage.



Tuner Section Can Feed Hi-Fi. With the jumper removed and the connections in Fig. 5, you can route the radio's output into your hi-fi amp and speaker for real volume. If the radio has an FM band, you'll have fine static-free music. Connect the chassis terminal to the chassis terminal on the hi-fi amplifier, and the tuner output to your amplifier's tuner input. If you get hum, use shielded cable, grounded to the chassis terminals of both units.

Radio Now Works as Phono Amp. Connect the leads of a crystal or ceramic phono pickup to the Audio and Ground terminals (Fig. 4); if your radio has a good a-f section and a respectable speaker, you'll get quality music. If your amp section is low gain, use a high output crystal, or ceramic phono cartridge. Otherwise, if your amp section has plenty of gain, you can use the higher quality low voltage crystals, or ceramic cartridges as are made by Ronette, Electro-Voice and Sonotone.

Crystal Input for AM Fidelity. Run the output of a crystal radio through the audio amplifier and speaker (Fig. 6) and you'll get better quality sound because the detector tube element noises has been eliminated. Also a crystal radio has a wider bandpass and less distortion than a superhet radio. If your amp section has high gain, a short antenna on the crystal set will do the job. No ground connection is needed, because the crystal set is automatically grounded by capacitance when connected to an a-c type radio. With an a-c/d-c type radio, use a .05 600-volt blocking capacitor to get line isolation.

Record Player. Since the radio already has a volume control, none is needed on the record player. If you get a-c hum pickup, use

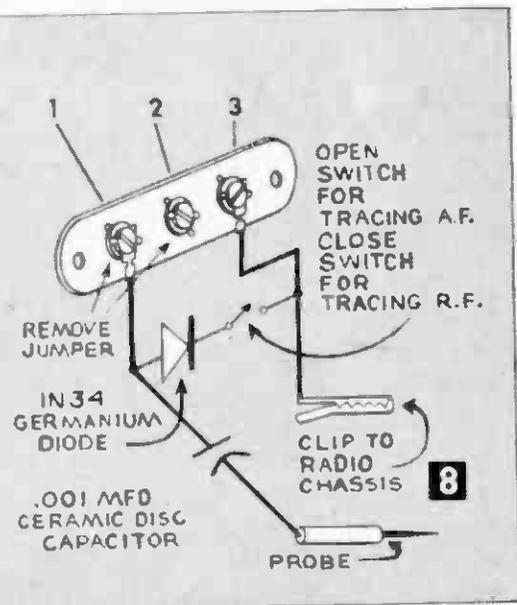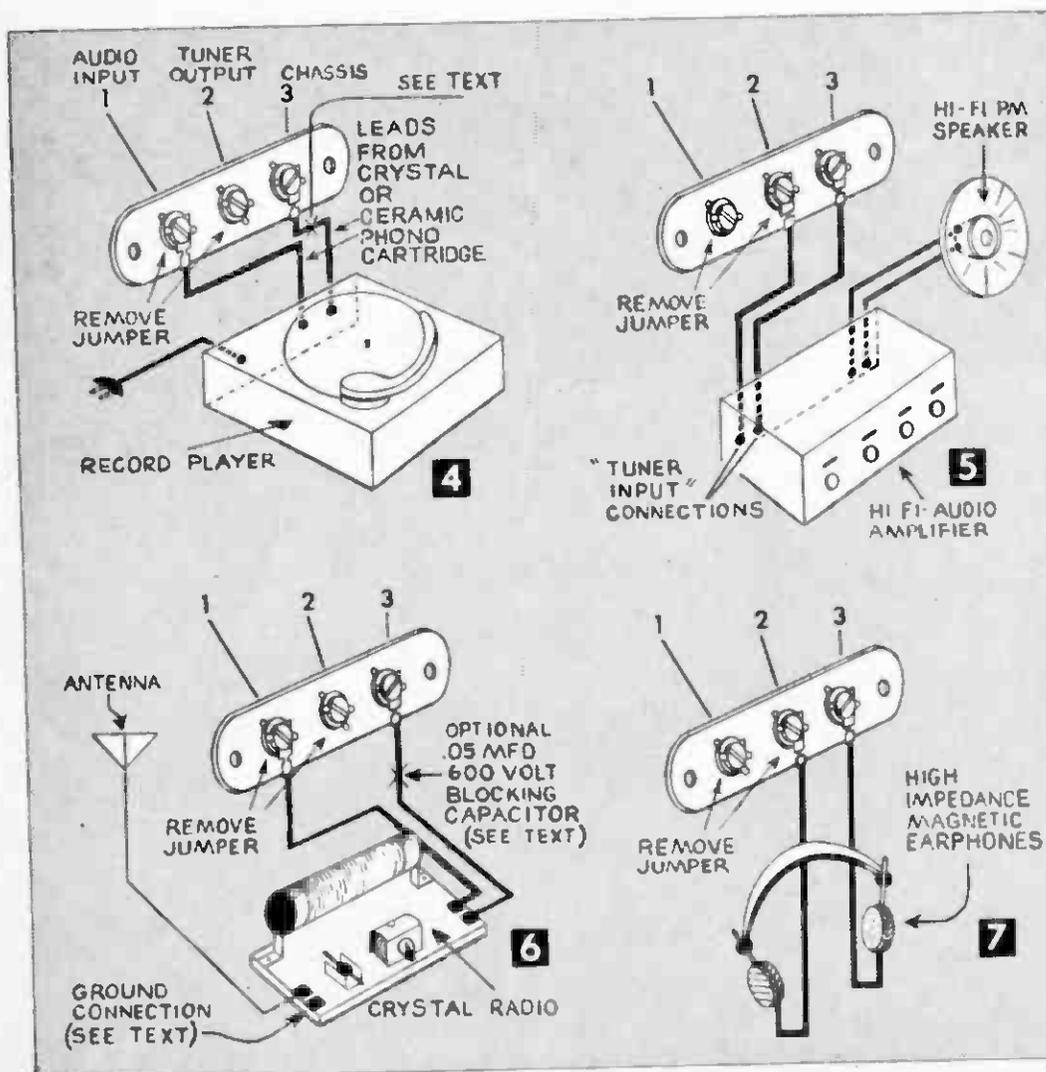Tuner Is Right for Earphones. Late listening will be a pleasure because you'll get less hum and distortion than with the common across-the-speaker method of connecting phones. Use a pair of high impedance magnetic or dynamic earphones. Of course, the radio volume control will not function because the connection is ahead of it in the circuit. Don't try this on an a-c/d-c type radio be-



cause a shock hazard would be involved unless you observe precautions noted later.

Radio as Signal Tracer. Less than \$2 worth of parts that you may have in the scrap box will give you an *rf/af* signal tracer (Fig. 8). You can mount the parts on a block of wood, or in a small plastic case. Use insulated flexible wire for the probe and clip. When tracing *af*, open the switch to take the diode out of the circuit. Close the switch for tracing *rf*. Your radio volume control will regulate the speaker volume to a comfortable level. If your radio is an *ac-dc* model, note precautions given in next paragraphs.

Using AC-DC Type Radios. The reason for avoiding the use of *a-c/d-c* radios for these applications is the danger of shock hazard. If you are not sure of your connections,

ask a radio expert. The *a-c* radio has a transformer which completely isolates the chassis from the line voltage, and so it is safe. But the *a-c/d-c* set usually is wired with the tube filaments in series, and thus when the plug is one way in the wall, the metal chassis is connected directly to the "hot" line voltage. You can test by connecting a voltmeter, or lamp between the chassis and any grounded water pipe. Correct this situation by reversing the plug so the chassis is on the ground side of the power line. Plug and outlet can be marked, or you could use a polarized plug and outlet so it will always be correct. Another remedy is to isolate the hot *ac-dc* chassis from the power line with an isolation transformer. (A 50-watt size is available from radio dealers for about \$6.)

The DX Strip

The Bahaman waterways offer exciting listening

By C. M. STANBURY II

APRIL 24, 1960 and the 42-ft. cabin cruiser "White Star" is grounded on Elbow Cay. Signaling with a mirror, it attracts the attention of the "Muriel III" who comes to the rescue. Only this script wasn't written that way because when it arrives the White Star's one man crew seizes her, disposes of the captain and sails away in the plundered vessel. Who said piracy is dead?

Where did it happen? The China Sea or maybe the Indian Ocean? No, right next door in the Bahamas, in the DX strip extending from Little Bimini (less than 50 miles east of Fort Lauderdale, Florida) to Inagua, approximately 50 miles from Haiti and Cuba. While such locals as Nassau and Bimini are well civilized, much of this territory consists of rocky uninhabited islets accessible only by boat. Elbow Cay is such a place.

Have you heard this first class DX target yet? Chances are, unless you happen to be an eastern BCB DXer, these fine loggings have escaped you.

The only broadcasting station in the Bahamas is ZNS at Nassau (Z is pronounced Zed outside of the U.S.). It operates on 1540 kc and according to international treaty (the North American Radio Broadcasting Agreement) is supposed to use only 5000 watts. Instead ZNS has boosted power to 20,000 watts. The increase has been protested via the State Department by U.S. stations which share this channel at night. Indications are that ZNS is getting out, certainly good news

for DXers.

The best way to log this station is via "Sunset skip," that mysterious process by which signals, particularly those from Latin America, appear with unusual signal strength for a brief period, either at sunset or during the three hours following, depending upon frequency and conditions. ZNS is usually best between 6 and 7 at this time of year in the east and a little earlier (local time) in the Midwest.

Reports should go to the Chief Engineer and at last report he was verifying by letter. Return postage which must always be enclosed, may be sent via International Reply Coupon obtainable at any post office for 15¢.

Above the Broadcast Band. Now if you live out west, for some reason don't like BCB DXing or just plain want to stick to short-wave, the frequencies for you are those used by aeronautical services in the Bahamas. Daytime this means 13344.5 and 8871 kc., during the first couple hours past sunrise, the hour before sunset and early evening period, you should monitor 6537 and 5566.5. The night channel is 2966, a fine medium-wave DX spot except during the static laden summer.

Call letters for Nassau Aeradio are ZQA but it identifies simply as Nassau. At last report, the station, which is government owned and operated, verified by letter and reports should go to Officer in Charge, Nassau Aeradio, International Aerodrome, Nassau.

But there is no reason to limit your aero-

Transistorized Audio Amplifier

THIS two-pound battery-operated amp will add loudspeaker volume to a phono pickup or portable tape recorder (Radio-TV #569). Or it will put more "reach" into earphone radio reception. It can be built for about \$13.

While the $\frac{1}{4}$ -watt output would never win a hi-fi volume contest, with a good crystal phono pickup (Fig. 2) and an efficient speaker, you get enough volume to fill a room. Frequency response is excellent and the transformerless design means that money saved can be spent on high quality entertainment-type transistors.

How It's Built. First bend a 7 x 7½-in. piece of 20-gage aluminum for the chassis (Fig. 3). For a "pro" look, have your local tinsmith make the bend on a brake. You can also use anodized store front aluminum, available from window glass dealers. Its smooth matte surface is ideal for panels provided that you remember to scrape off the surface at every point where the parts must connect electrically to the chassis.


The location of the mounting holes (Fig. 3A) is not critical, but be sure to allow enough room on the edges for the wood cabinet fit. Make the opening for the slide switch by drilling two $\frac{3}{16}$ -in. holes and filing the opening with a small square file.

Make the wooden case (Fig. 4), using small wire brads and cabinet glue to fasten the parts together. File and sand the edges of the case and chassis round and drill holes for the *rh* wood screws which hold the chassis and cabinet together. Three rubber feet in triangular arrangement will permit the amplifier to rest solidly on uneven surfaces. Drill small holes in the chassis, and use three rubber tack bumpers fastened with Duco cement.


Mount the panel parts, using lock washers under nuts and screw heads. Scrape away the aluminum coating at each connection to chassis. Make the transistor socket bracket

Lightweight battery-operated amp delivers
loudspeaker volume

By ART TRAUFFER

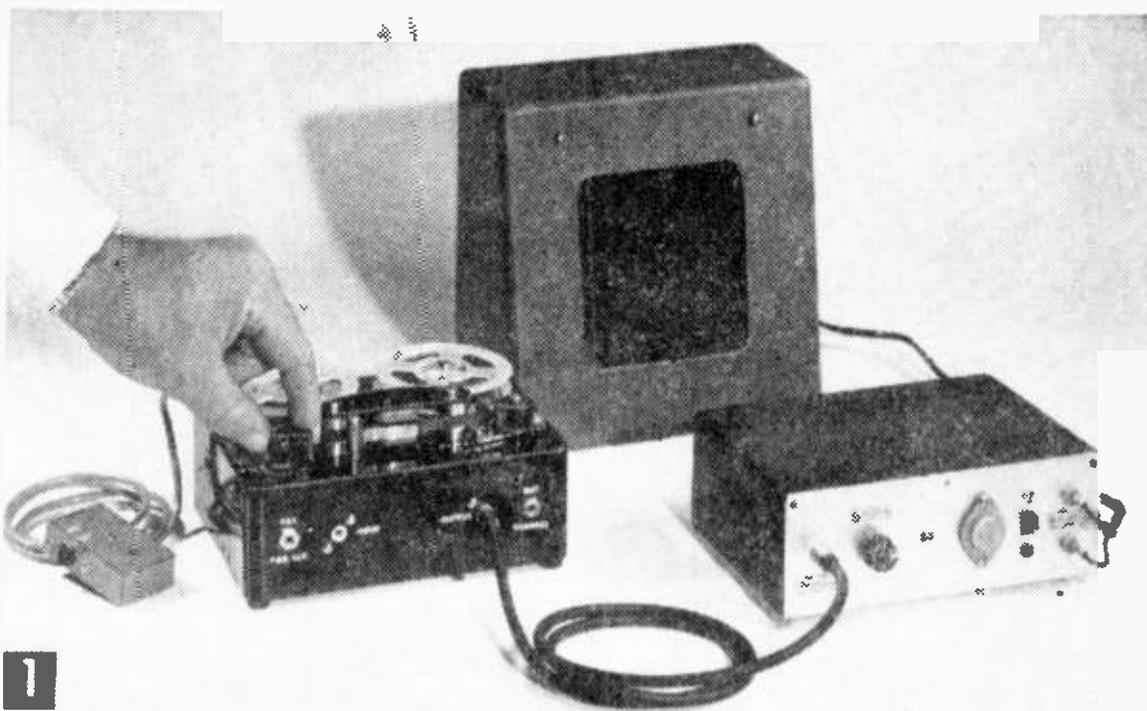

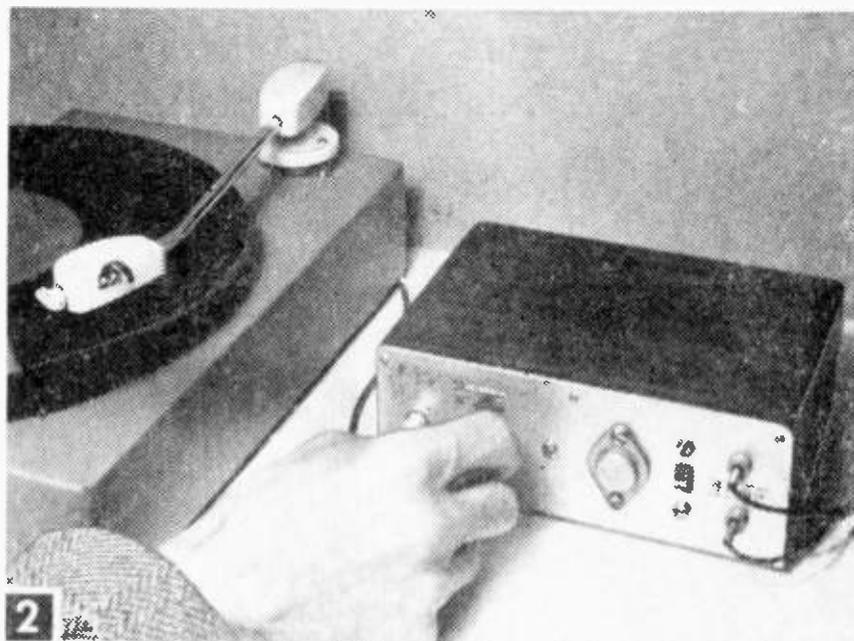1 Plug in the transistorized amplifier and you boost the tape recorder output up to loudspeaker volume.



2 With a crystal pickup and an extended range 8 or 12-in. speaker, reproduction is crisp and clear with volume to fill a room.


(Fig. 5) of thin aluminum. File each slot for a tight clamp fit around the transistor socket, and fasten with cement. Mount the 2N301 power transistor to the chassis with a layer of thin mica (Fig. 6). The mica and the insulating washers which are cemented to the inside of the panel serve to insulate the mounting screws and the transistor case (collector). Yet the thin mica permits the chassis to act as a heat sink to keep the transistor

tion, improved frequency response, and less cost in the circuit.


A 16-ohm speaker will give the best results with your amplifier. A second choice would be a Jensen P12-RX (\$12.40) 12-inch extended range speaker. Otherwise any 8-ohm speaker also will work well, and you will get fair results with even a 4-ohm speaker. The 560-ohm resistor (R9) across the speaker terminals protects the transistors in case power is turned on with speaker disconnected.

Any good crystal or ceramic phono cartridge mounted on a free-moving arm can be used. The cartridge shown in Fig. 2 is a Ronette TO-284-P mounted on a Ronette 12-in. arm. This kind of pickup has relatively low output, with very low intermodulation distortion. Turntable selection depends on how much quality you want to buy. For a low budget system, 3-speed turntables such as Alliance Model JPT8 and General Industries Model-SS are offered in the \$6 bracket.

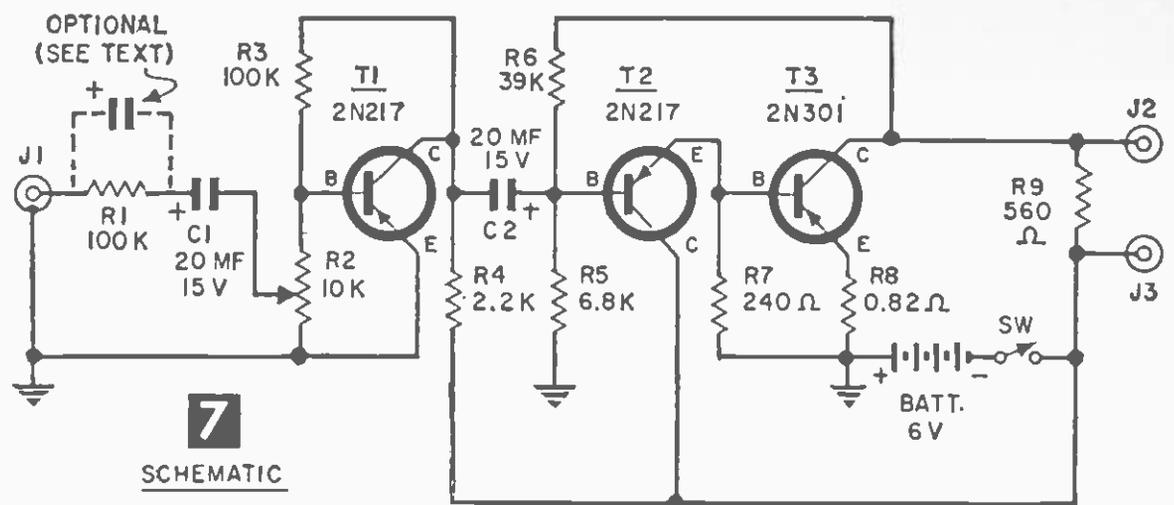
The amplifier was designed to use the high quality entertainment transistors specified. If you use the lower-priced experimental transistors, performance will suffer. You may



7 SCHEMATIC

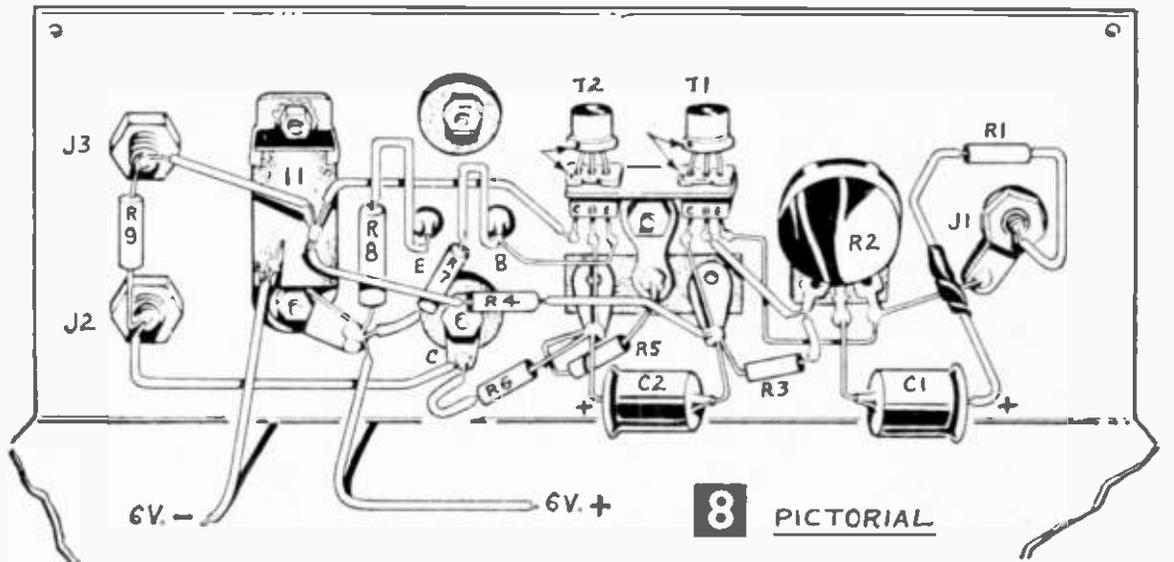


8 PICTORIAL

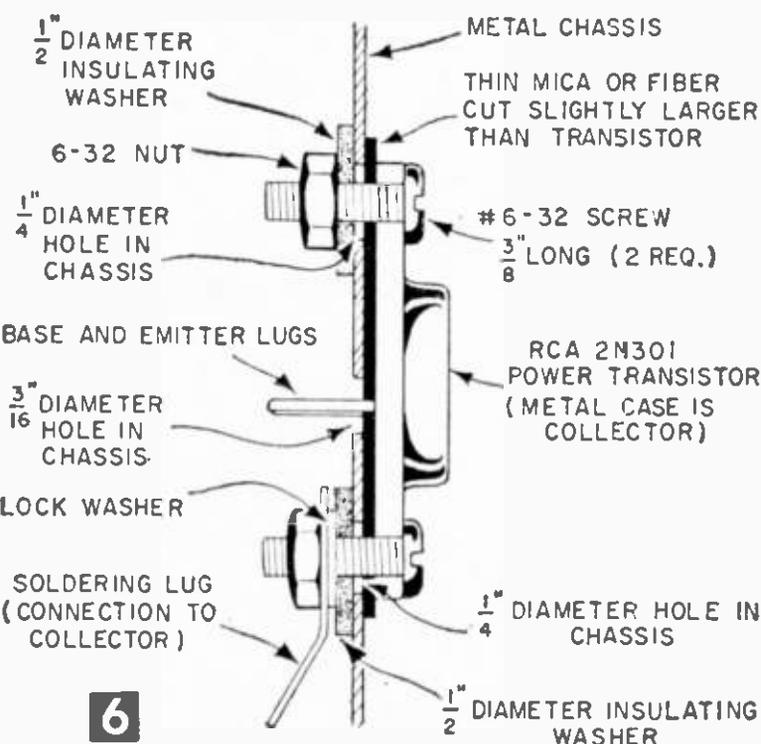

6

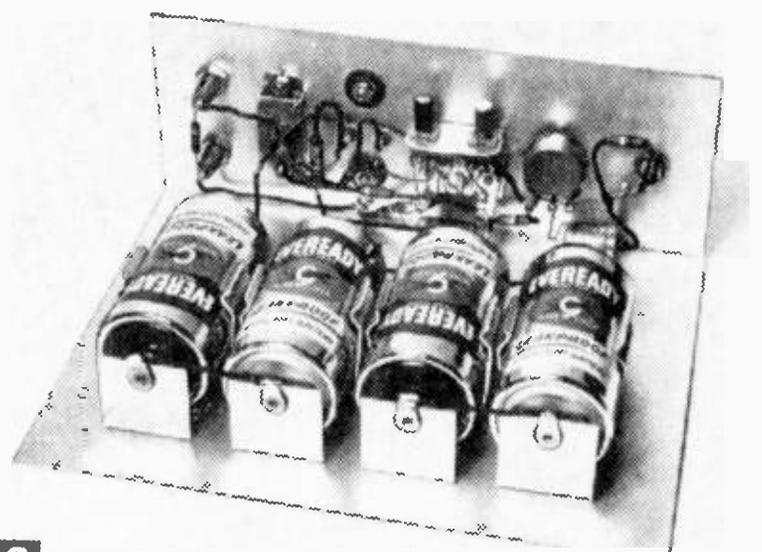HOW TO MOUNT POWER TRANSISTOR TO METAL CHASSIS




9

Four D-size flashlight batteries wired in series give you 6 volts of power. Battery life is 100 to 200 hours.


want to experiment with the size of input resistor R1. The higher its resistance, the more it attenuates the high frequency response. You can try values between 10K and 1 meg-ohm. A 10K resistor worked best with the S&M portable tape recorder.

When the amplifier is used to boost the output of a crystal set or a single transistor radio, you will get bell-like clarity from local AM stations. It works well with good FM tuners, and you could also use two of the units for stereo.

Analog Computer Theory

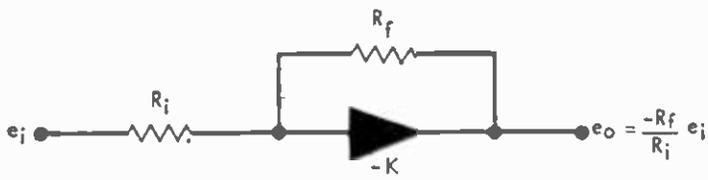


A CONSTANT MULTIPLIER

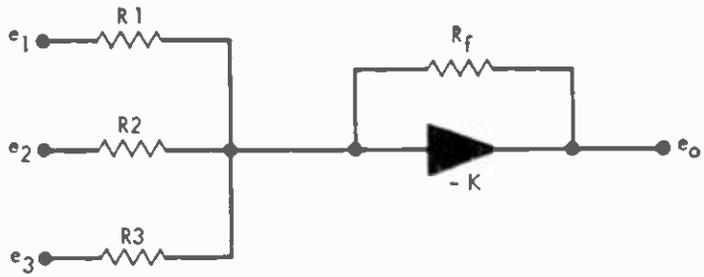

B ADDER
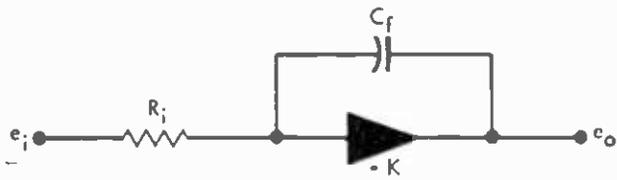
$$-e_o = e_1 \frac{R_f}{R_1} + e_2 \frac{R_f}{R_2} + e_3 \frac{R_f}{R_3}$$



C INTEGRATOR

$$e_o = \frac{-1}{R_i C_f} \int e_i dt$$

∫ MEANS INTEGRAL OF

1

KEY

- R_f - FEEDBACK RESISTOR
- C_f - FEEDBACK CAPACITOR
- R_i - INPUT RESISTOR



THE "K" REFERS TO THE VOLTAGE GAIN
MINUS SIGN INDICATES AN INVERTED SIGNAL

By FORREST H. FRANTZ, SR.

ELECTRONIC analog computers are valuable tools in product research and development. Scientists and engineers use them to study the mathematics and behavior of physical phenomena and physical systems. The analog computer is favored over the digital computer for programming simplicity and for the ease with which results may be interpreted.

Digital computers are used when extreme accuracy is required or exceedingly complex problems are to be solved. Several manufacturers offer small desk top electronic analog computers that cost in the vicinity of a thousand dollars. One of these computers, properly used, can pay for itself in a month in many industries.

The main components of an analog computer are operational amplifiers, coefficient potentiometers, reference and initial conditions power supplies, function generators, and computing resistors and capacitors.


The operational amplifier is the basic analog computer building block. In the Heathkit ES-400 it is a high gain (50,000) direct coupled (dc) amplifier. This amplifier must be able to amplify very small signals, and at the same time must be able to handle large signals without overloading. The amplifier must have very low drift. Drift is a problem in dc amplifiers because a very small voltage change in the input tube is amplified and appears as a signal voltage at the output tube.

The input impedance must be high, the

output impedance low. And the operational amplifier must be linear over its operating range.


The principal difference between this type of amplifier and an audio amplifier is the direct coupling, the more elaborate precision voltage dividers, and the output arrangement to allow negative as well as positive dc outputs.

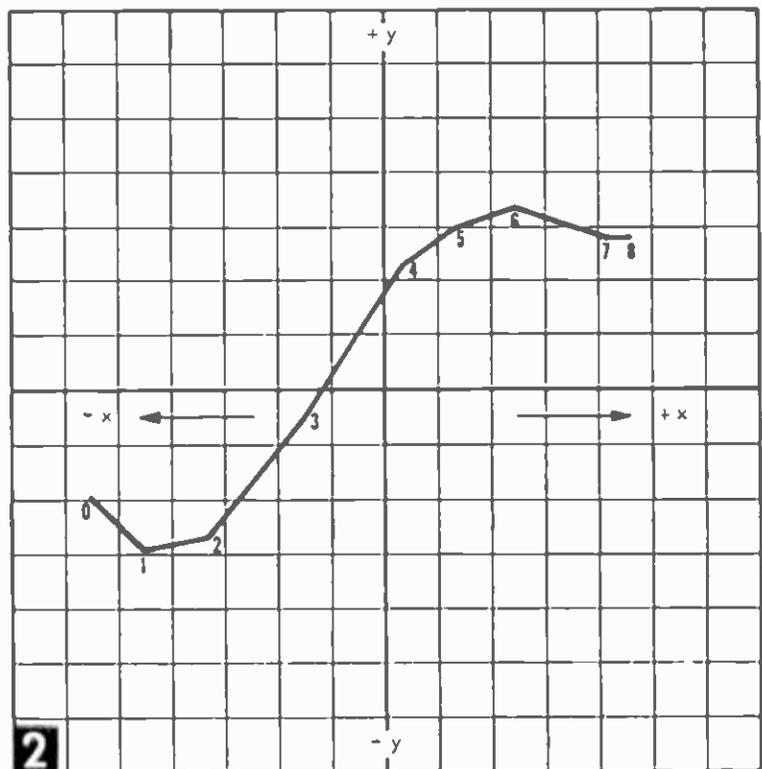Operational amplifiers are used with feedback resistors and capacitors and input resistors. Appropriate combinations form con-



2

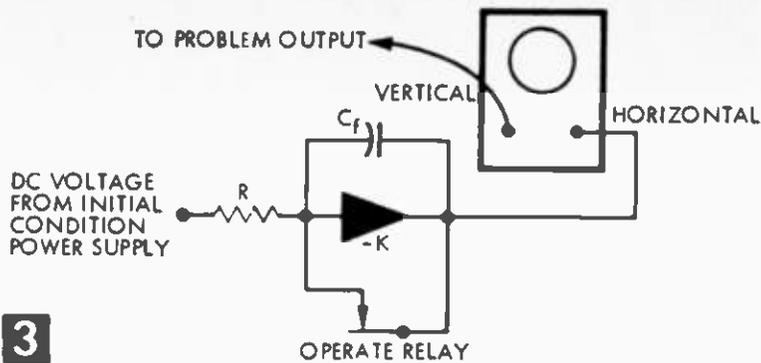Finding the curve of a non-linear function. If more points were known, an even curve would result.




3 An integrator can generate sweep voltage for CRO display.

stant multipliers (Fig. 1a), adders (1b), and integrators (1c). Note that the ratio of the feedback and input components can be chosen to reduce the overall gain to 1 or less. The operation and use of the constant multipliers, adders, and integrators will be discussed later.

The coefficient potentiometers are used to set constant multipliers into problems and to keep signal levels within the operational amplifier linearity limits.

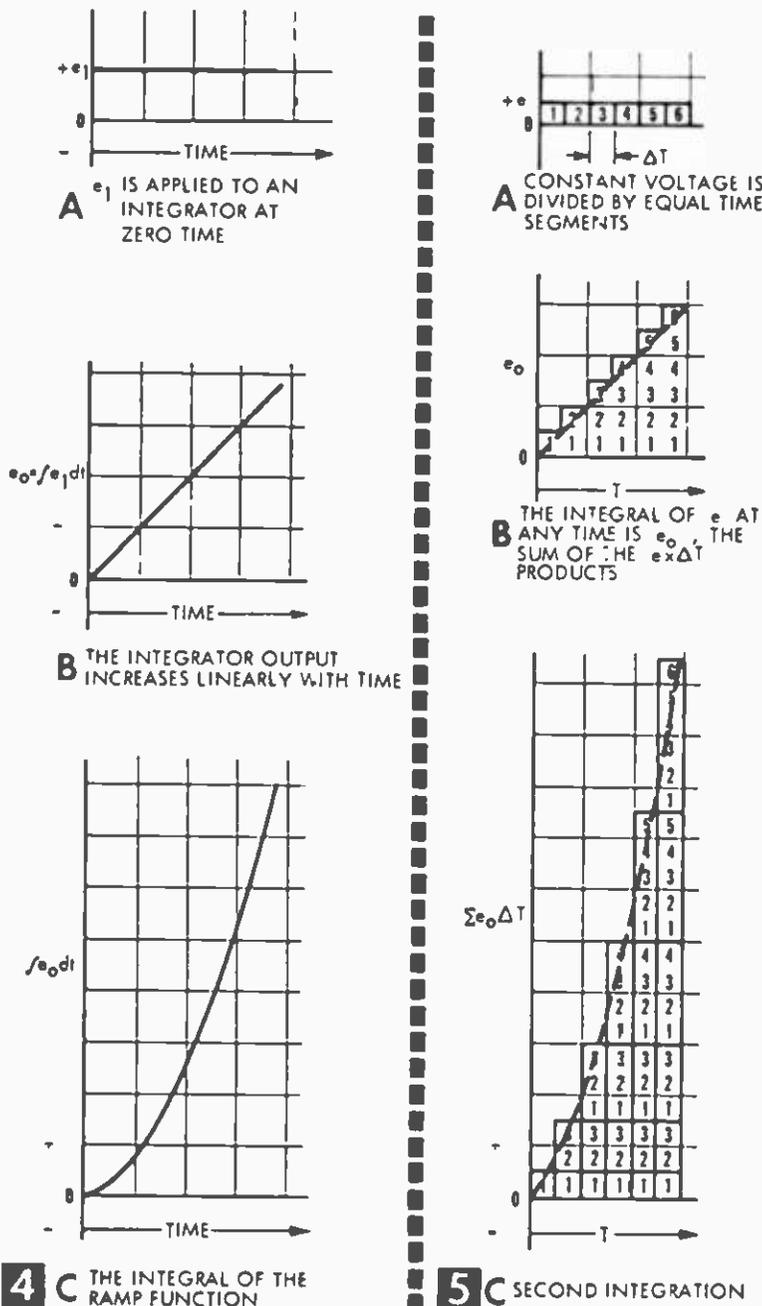The coefficient potentiometers, amplifier inputs and outputs, reference and initial condition voltages, relays, diodes and function generator are terminated on a patch board.



4 C THE INTEGRAL OF THE RAMP FUNCTION

5 C SECOND INTEGRATION

The problem is entered into the computer by interconnecting the various components on the patch board. The computing resistors and capacitors are mounted on plugs that fit these jacks.

Separate power supplies furnish the heater and B voltages for the operational amplifiers, reference power (plus and minus voltages), and initial condition power (plus and minus).

A function generator is used to generate non-linear response functions. Mathematical functions such as logarithms, sines, and co-sines, can be approximated with this unit. These non-linear functions cannot be produced too readily. But their curves may be approximated by setting the slope and break points of 8 straight line segments as shown in Fig. 2. Diodes and bridge circuits form the basic function generator set-up.

If a problem is to run a long time, a pen recorder is generally employed with an analog computer. Another approach to display and recording is to solve the problem in a short time (less than a second), and repeat the solution continuously for display on an oscilloscope. A repetitive oscillator is used to reset initial problem conditions and the horizontal sweep for the scope. The horizontal sweep may be derived from an integrator as shown in Fig. 3. Subsequent discussion will explain the operation.


Computation Building Blocks. The operational amplifier is the basis of the computation building blocks which are basically adders and integrators. The classification can be broken down further to include sign changers and constant multipliers. The constant multiplier is simply a special case of the adder with only one input resistor. The sign changer is a special case of the constant multiplier where R_f/R_i equals 1. Note that there is always a change of sign when a signal passes through an operational amplifier.

The mathematics behind the computer building blocks shown in Fig. 1 is based on feedback theory. The gain from input to output may be readily adjusted to very low values by the choice of the ratio of R_f/R_i . For best results, this ratio should never exceed 50, and upper limits of 20 or 30 are preferable. Since problems are readily scaled to convenient numbers, these limits don't impose any problem restrictions.

The adder of Fig. 1b has more than one input resistor (R_i). The several input re-

TABLE A—BIBLIOGRAPHY

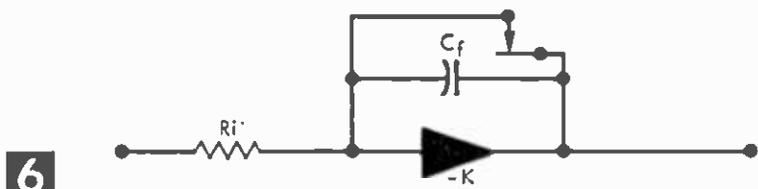Johnson, C. L., Analog Computer Techniques, McGraw-Hill, 1956.
 Korn, G. A., and Korn, T. M., Electronic Analog Computers, McGraw-Hill, 1956 (2nd Ed.).
 Soroka, W. W., Analog Methods in Computation and Simulation, McGraw-Hill, 1954.
 Wass, C. A. A., Introduction To Electronic Analog Computers, McGraw-Hill, 1955.



6 When initial condition is zero, the integrator capacitor is shorted by a relay until computation begins.

sistors are designated as R1, R2, R3, etc., for convenient identification. If any of the inputs is to be subtracted, it is introduced in the negative form. Thus the adder is also a subtractor. Note that the choices of R1, R2, R3 etc. allows multiplication of each of the adder inputs by a different constant. Or, the same result may be accomplished by setting all of input resistors equal and using a coefficient pot to adjust the constant multiplier at each of the inputs.

Integration warrants some explanation. Figure 4a shows the plot of a voltage that is constant with respect to time. If a constant voltage is applied to an integrator input, the output plotted against time is the sloped straight line of Fig. 4b. A simplified way of explaining an integrator is to say that the input is multiplied by small segments of time, and the resulting products are added to all others (Figs. 5a and b). The analog integrator is continuous of course, and the small time segments or increments approach zero. If you didn't study calculus in college, don't be too alarmed if you find integration hard to understand.


If the integrator output of Fig. 4b is the input to a second integrator, a second integration is performed. The integral of the ramp voltage of Fig. 4b is shown in Fig. 4c. Figure 5c shows the incremental representation.

Integration is begun by opening a relay which has the integrator initial condition set on the feedback capacitor and by applying the input voltage to the integrator. If the initial condition is zero, the capacitor is shorted till integration is to begin as shown in Fig. 6. If the initial condition is some value other than zero, this voltage is connected across the capacitor till integration is to begin.

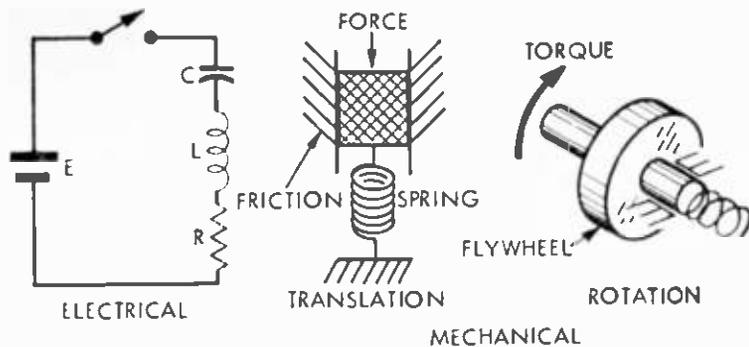
Problem Solving. Electronic analog computers solve differential equations. Differential equations describe the behavior of many physical systems. Figure 7 shows the electrical LCR circuit, a mechanical translational, and a mechanical rotational system. All of these systems are described by the same differential equation describing that input = reactions + losses:

$$\text{Input} = A \frac{d^2x}{dt^2} + B \frac{dx}{dt} + Cx$$

The computer hook-up is the same for all three systems. The constants A, B, and C are not the same but there are simple different coefficient potentiometer settings or different



7

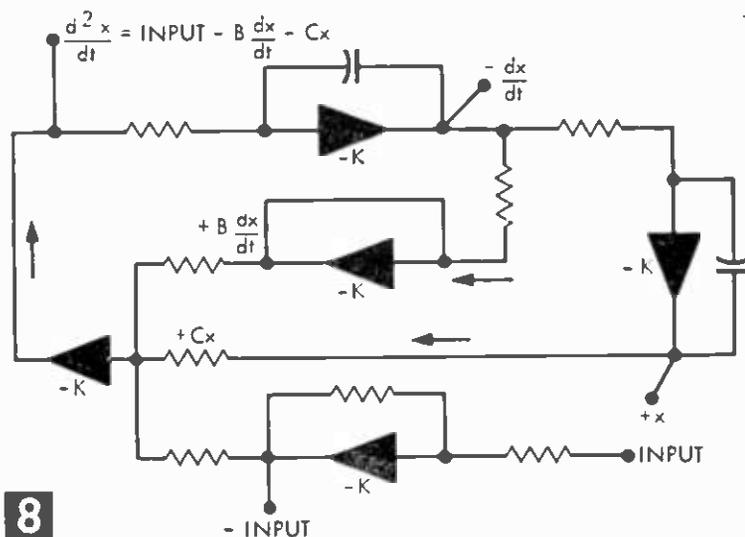

8

ratios of input and feedback resistors and capacitors in the hook-up. The computer hook-up for solving this differential equation is shown in Fig. 8. The initial conditions are assumed to be zero at the beginning of the problem in this case, and A equals 1.


To set up any problem for computer solution, you begin by assuming you have the highest derivative term, d^2x/dt^2 in this case or this term and its coefficient A (d^2x/dt^2) in this case. Isolate this term, i.e., find out what it's equal to. Then integrate this term to form the lower derivatives. Thus the integral of d^2x/dt^2 is dx/dt ; the integral of dx/dt is x . Again, this is college level math. If you have trouble understanding it, try to get help from an engineer or math teacher.

Space limitations do not permit a thorough treatment of dc electronic analog computers in this article. Many books and papers have been written on the subject. For those who are interested in learning more about analog computers, a bibliography is presented (Table A).

Solution to
Ham Radio
Anagram,
Page 88



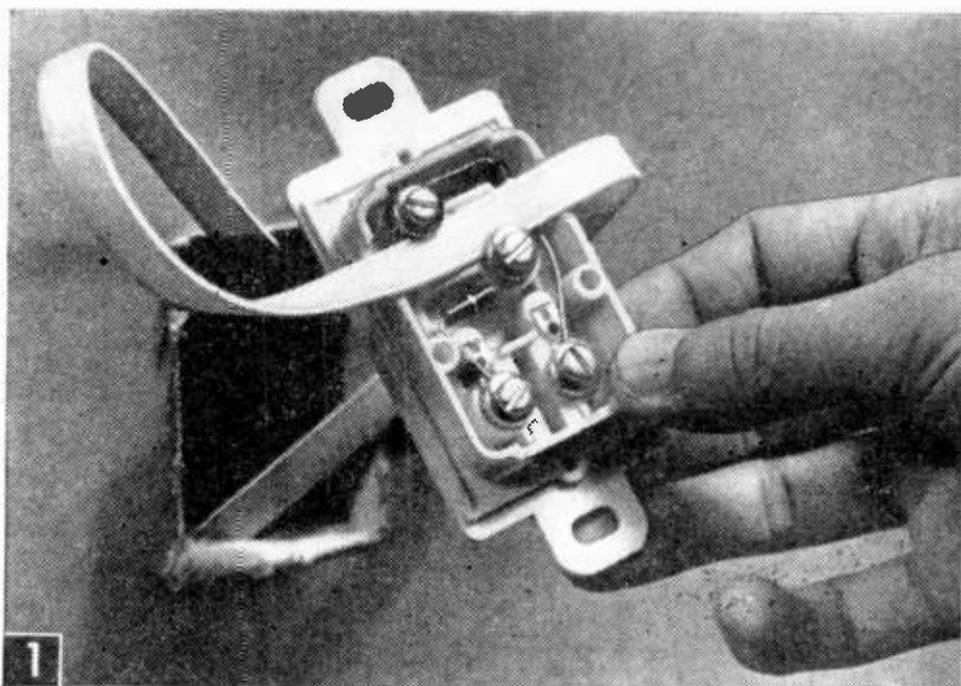Installing Plug-In TV Antenna and Booster Systems



You can install TV line outlets in any kind of wall, or along the baseboard. No soldering is required.

This type of antenna system lets you move your TV from room to room; it also banishes signal traps and improves picture quality

By **ELMER A. WOLFORD**

INSTALL a wired-in-the-wall type of antenna line system, and you'll get rid of TV signal traps, improve picture quality, and be able to use your portable TV and FM receivers in any room. Also, you'll eliminate unsightly indoor antennas and dust collecting coils of wire that have been plaguing your wife.

Cost of the system depends on the number of outlets (also called taps or plates) that you decide to use. These outlets range in price from \$1.50 to \$2.81 each. The typical layout (Fig. 2) cost \$8.20 for parts (available any electronic supply house) and took a few hours to install.

First, sketch exactly where you want your outlets. The 2- or 4-set couplers (Fig 2) will allow you to use all of the outlets at the same time with no interference. An FM radio in your den will not dis-

turb the TV sets in the living room and recreation room, or the FM-AM hi-fi combination.







You can choose one of three ways to bring an antenna lead into your house: (1) through the basement to all locations, (2) into the attic and down the walls, or (3) through the outside wall to the antenna wire coming down the side of the building. Pick the route that requires the shortest leads. For example, if you have a tri-level, bring the wires in through the basement.

Let's run through a typical basement installation. Start by drilling a 1/2-in. hole through the wall. Slant the hole upward as you drill from the outside to keep water from running in. Use a masonry drill on brick, stone, or cement walls. Either use an extra-long electrician's type bit, or have a welding shop add a 12-in. extension to your drill bit.

Next bring the wires through a feed-in tube and connect them to your antenna coupler. At no point should the

EDITORS NOTE: The plug-in antenna systems described in this article are not to be confused with the plug-in "antenna eliminators" which are claimed to turn your house wiring into a giant antenna system. Such TV "antenna eliminators" do not always provide consistently strong signals for good viewing on all channels, though some people living close to transmitter have installed the units and effected an improvement, often particularly on sets that previously were running with no antenna, or with standard antennas in poor repair.

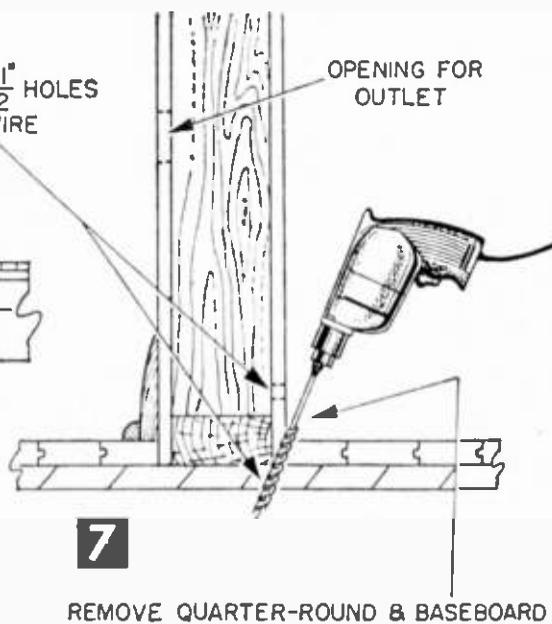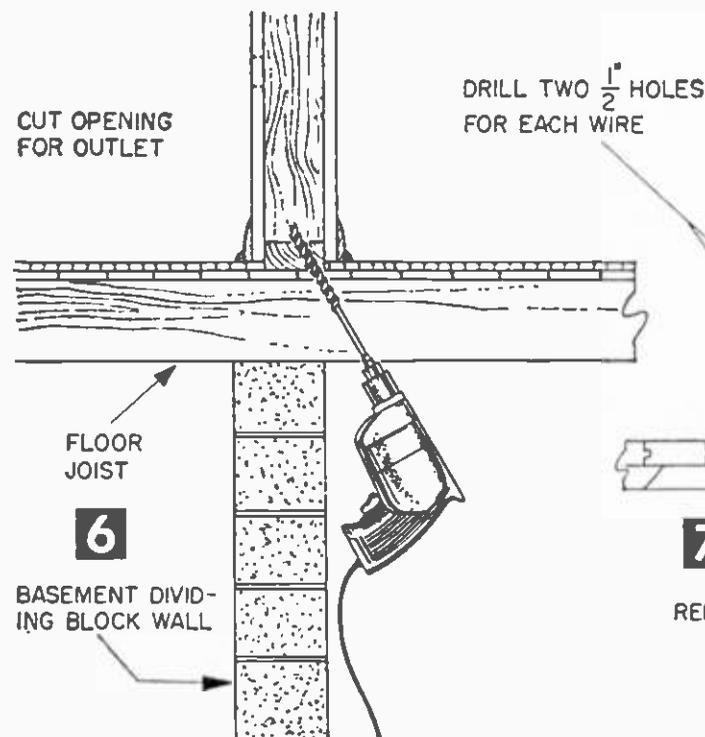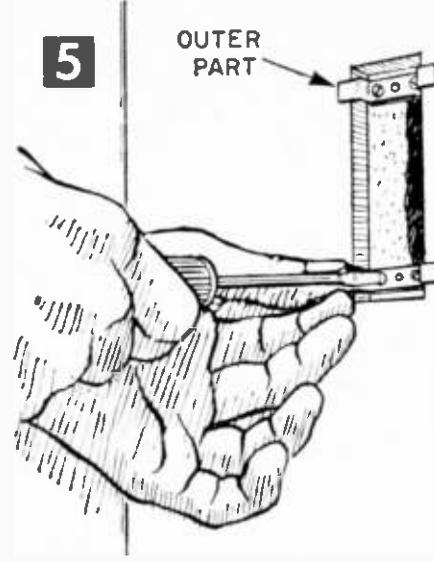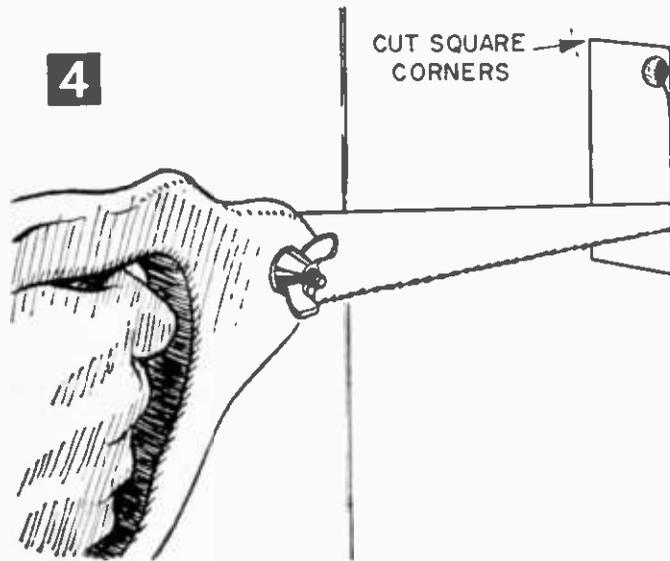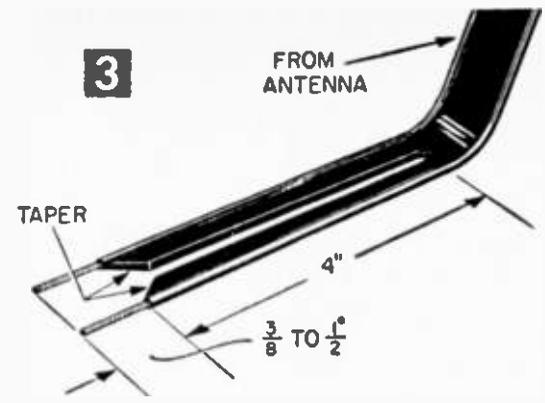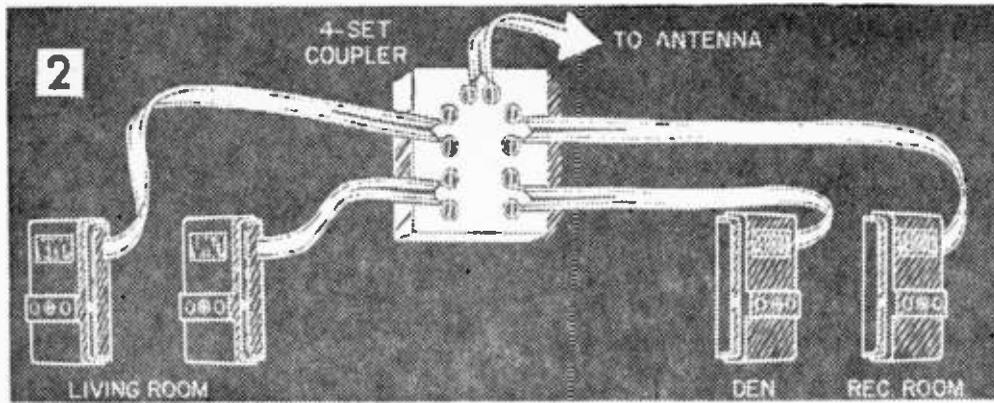Antenna eliminators can also become a shock hazard, in those instances where they include a capacitor circuit that isolates the TV set from the line. In such cases, if one of the capacitors shorts out while the antenna circuit of your TV is plugged into one leg of the house a-c line, it may make all metal chassis and cabinet parts, "hot."



trical outlets for neat appearance. Tap sharply on the wall to be sure you won't hit a stud, and then drill a starting hole and cut the wallboard or plaster with a keyhole saw (Fig. 4). Mount the brackets (Fig. 5), spacing them to match the holes in the outlet plate.

To spot the holes feeding into the basement, use electrical conduits or heating ducts as guides to find your partition centers. Drill a $\frac{1}{2}$ -in. hole directly beneath your outlet opening. Or temporarily remove the baseboard (Fig. 7) and drill through.

Trim the wire end (Fig. 3) and connect to terminals marked SET 1, on the coupler. Follow the most direct route possible between the coupler and the outlet holes, tacking the wire to the joists with wall stand-off insulators. When the wire is up to your hole

TV transmission line run through pipe, metal conduit, or jacket, since metal around the line will cause a loss in signal strength.

If you follow the Fig. 2 layout, but live in a fringe area where you use two antennas, you will need two 4-set couplers and two line outlet plates. Pick a spot in the basement where the wires from the coupler will be as nearly equal in length as possible. Trim the incoming antenna lead as in Fig. 3. Connect to the coupler terminals marked ANT, and fasten the coupler to the floor joist with wood screws.

Making the Wall Openings is next. In the living room, mark a $1\frac{3}{4} \times 4$ -in. rectangle for each outlet, at the same height as your elec-

under the outlet, clip it off with about 4 feet extra remaining. Straighten a metal coat hanger, tape the wire to it, and have your helper pull the line up through the outlet hole in the wall. Again trim the wire end as in Fig. 3, and connect to the terminals on back of the outlet plate. Follow the same procedure installing the outlets in the other rooms.

For a Double Antenna System, locate the second coupler near the first, and run all four outlet lines as before, bringing them up to your two-line outlet plates. Whenever more than one line is connected to an antenna, there is some loss of signal due to stub effect. If you do not need the convenience of using two or more outlets at the same time,

you can save money by using polarized plugs (Fig. 8) with which you can quickly connect any desired outlet.

When a TV set is connected into any outlet other than the last of several outlets wired in series, the antenna wire beyond that outlet produces a signal loss. A new kind of switching outlet (Mosley) automatically disconnects the system beyond the outlet in use.


Where TV Signal Strength Is Low, multiple outlets may weaken reception to the extent that pictures are snowy and dull, with poor sound at the receiver. One home system kit (Jerrold \$43.98) provides for five TV or FM outlets, and includes an amplifier (Fig. 9). Another system (Blonder-Tongue Co. \$57.33) which includes an amplifier and provides for up to eight TV sets, is the answer for apartment buildings, motels and rooming houses. Even larger systems providing for up to 500 outlets are available, but require experienced installers.

Through the Attic Installation is the answer if you have no basement. Drill a ½-in. hole through the roof for each wire and push the wires inside. Mosely Roof-Thru or Javex Tenna-Shingles permit feeding the antenna wire directly through the roof for short direct connections with less signal loss. Copper flashing inserts (Fig. 10) under the roof shingles prevent water from running into the attic. Black plastic roof cement can also be used to seal these fittings and guarantee no leaks.

For through-the-attic installation, connect your antenna lighting arrestors near the entrance holes and run a ground wire as in Fig. 10. An important advantage of plug-in TV antenna systems is that you can disconnect your TV sets during electrical storms. Lightning has been known to split open the finest arrestors and then the TV set. While you are away on vacation, you can be worry-free knowing that your TV is completely disconnected.


Select the locations for your outlets and drill ½-in. holes above each (Fig. 11). Tie a string to a nut and drop it through the hole to check for obstructions in the walls. If the nut hits bottom, there is no problem, but if there is an obstruction, try another location. Or run the wire through a closet on the other side of the wall, and then out the wall opening. Complete the outlet installations as described before.

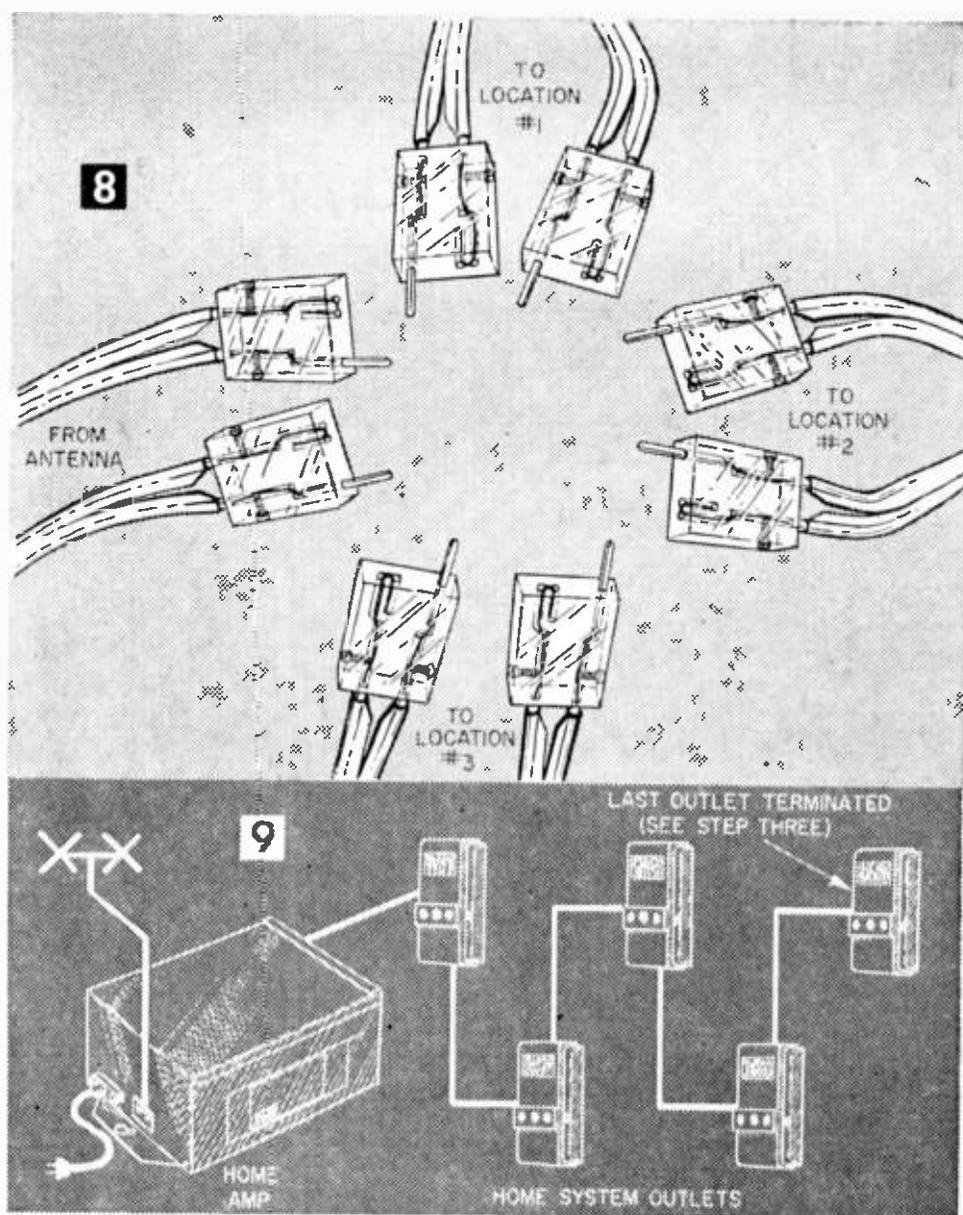The Magic Carpet antenna (Jerrold Electronics Corp.) is a 2½ x 6-ft. flat flexible



printed circuit (Fig. 12). You can staple it to the attic floor or joists, to the ceiling of a utility room or closet, or even slip it under a rug. But remember that metal will shield an antenna. If there are large areas of your roof or walls covered with aluminum insulation, particularly along a line between your antenna and the TV station, your signal strength will suffer.

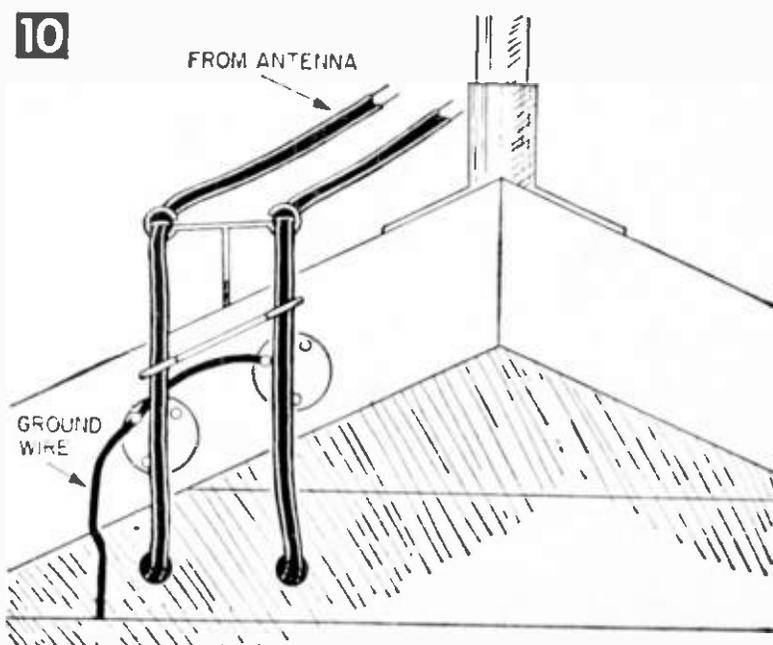
Through the Wall Installation may be the only answer in some homes. Drill a ¾-in.





hole through the wall all the way. Insert the Wall-Thru fitting (Mosley Electronics, Inc.) mark it for length, and cut off the excess. A socket mounts directly to the fitting on the inside wall. Re-insert the wall-thru, run the wire through and trim as in Fig. 3. Connect the wires to the socket, and then mount the socket to plate of the wall-thru fitting. Connect to your outlet plug.

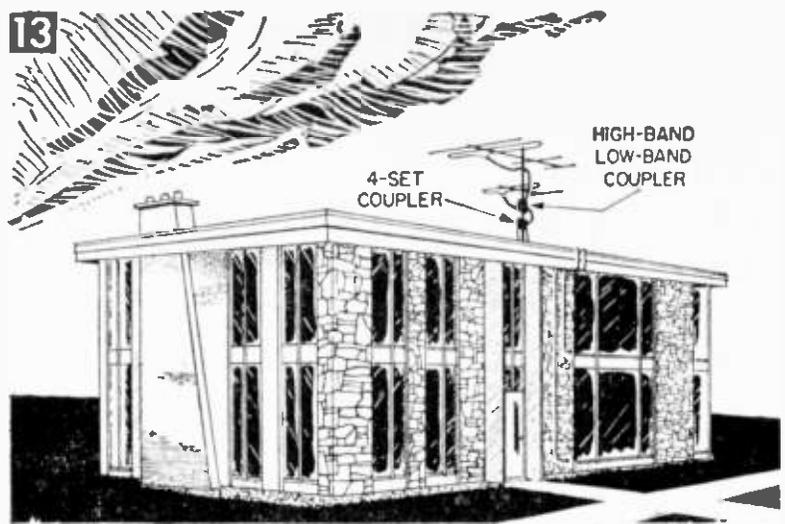Multiple Family Dwellings can be spared the "forest" of many antennas littering the roof top, if multi-set arrangements are used. All-weather TV set couplers can be mounted on the antenna mast or at the eaves. If your area has both low band (channels 2-6) and high band (channels 7-13) stations transmit-




ting, you can couple the two lines together and run one line only by using a high-band, low-band VHF coupler (Fig. 13). This requires that you bring in only one wire to the 2-set or 4-set couplers in various apartments. Cost per outlet will be less. Also, couplers are available for connecting separate VHF and UHF antennas to a single line. These couplers are also excellent for homes.

Use either double or single stand-off insulators as you run the wire down the antenna mast, across the roof and down the sides to the apartments. Insert the insulators about every 10 feet. Apply a dab of black plastic roof cement around the stem of each to prevent leaks. Also, install a lightning arrester on each wire at the point where it enters the building, and run a line down to a ground rod as close as possible to the building.

Custom TV Wiring. New home builders can save money by installing custom TV wiring while the house is under construction. By planning ahead, you can also install your telephone wires and terminate the lines in wall sockets. Install a plaster ring for each outlet location so it will be flush with the plaster board or plaster. In some areas, the code may require a plastic wall box. Also, wall plates are available which provide for both power and antenna connections. A metal barrier plate in the box separates the antenna socket from house wiring to comply with the code, and the plugs are polarized to prevent improper insertion.

Antenna Rotor Controls can also be fed to TV outlet plates. You'll find either four, five or eight wires in the rotor cable. Connections must be correct or you'll burn up the control box, so sketch the hookup and note the color of wire at each terminal before you disconnect anything. Connect the sockets and plugs so that each wire mates color to color.

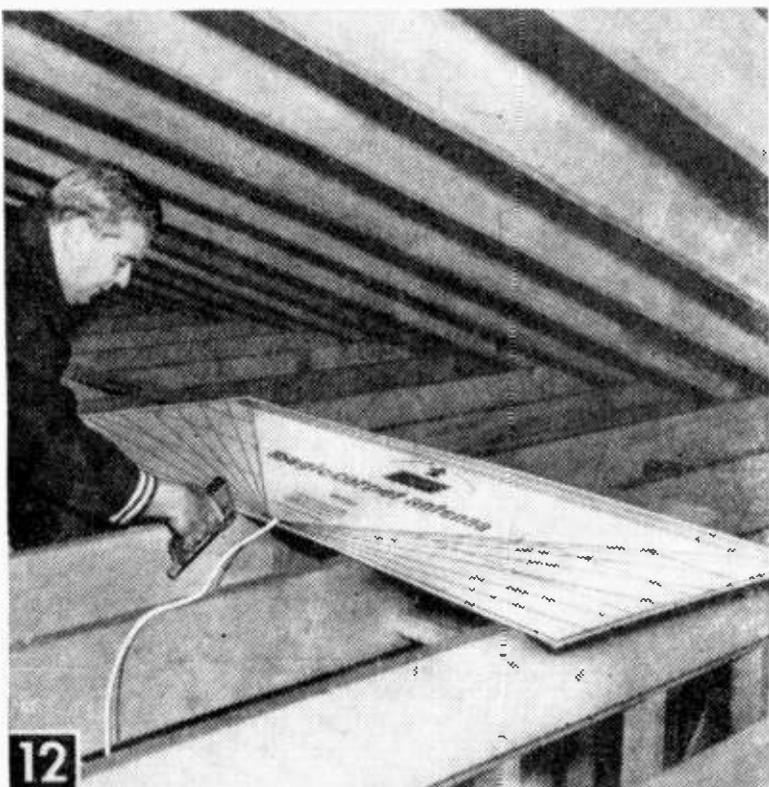Chromed outlet plates are also available but are not recommended for fringe area installations. Instead use low-loss polystyrene wall plates. Always, the wire between outlet plates and the TV set should be as short as possible, preferably under 4-ft. in length, for optimum reception.



Performance of this printed circuit antenna is comparable to outdoor antennas up to 35 miles from the TV station.

Electronics Father and Son Hobby

By FORREST H. FRANTZ, SR.

SOME people tell us that modern family life has been torn to shreds. Too many cars, too many television sets, too many widely scattered activities and hobbies shoot the members of a family in different directions, they say.

Bunk! In our family, we benefit from these activities and find them a mutual basis for enjoyment. The hobby? Well, that's one of the best friendship cements there is. And I don't know of any hobby that tends to keep a father and son as close to each other as electronics.

Why electronics? While he certainly can profit from your wisdom in matters of sportsmanship, your son probably can do fine on his own from the standpoint of athletic skill. When it comes to electronics and other scientific-engineering hobbies, however, he will need your help. And activities such as these can lead your son to a career in which he can one day support his family very comfortably. More important, an interest in electronics stimulates an understanding of science that is essential in our technological age.

There's another important angle to electronics as a father and son hobby: it will keep *you* interested, too. If your son engages exclusively in activities that don't appeal to you, it's hard for you to be the kind of buddy you should be. You've got to be an enthused participant rather than a tolerating one.


Incidentally, Junior, if you're reading this, there's a good reason for getting Dad in on your electronics hobby, in addition to the obvious one that you like the guy and want to do things with him. Although you can do a lot in electronics with a limited budget, you can do a great deal more if the purse strings aren't too tight. Get Dad interested in electronics, and he'll soon realize this.

As a matter of fact, you can show him how he can make some big savings by letting you build home intercoms, hi-fi amplifiers, receivers, battery chargers, and other modern living essentials from kits. Chances are he'll be wrestling with you for the soldering iron when the kits arrive. If that's the case, give him a chance because it's your opportunity to get him into electronics in a solid way.




An electronic lab type kit which features a number of construction projects is a good investment for beginners.

Assuming we want to get started on a father and son basis, what are the ground rules? In the first place, you can't cram a hobby down someone's throat. Create interest by exciting curiosity and enthusiasm. A boy who can show his father a clever electronic device that he built for a few dollars will usually find his father's interest and pocketbook available. A father who can show his son a very compact radio or other elec-

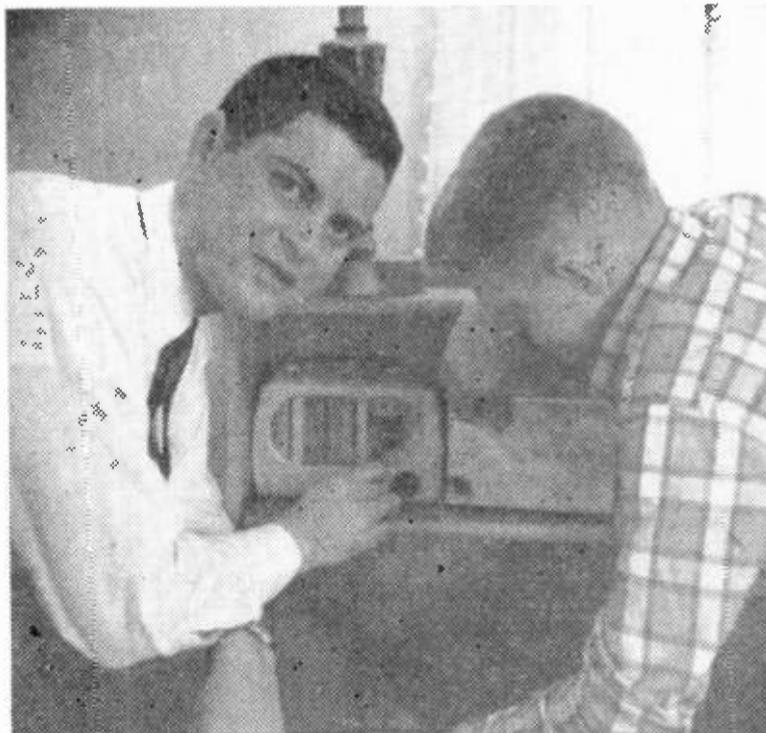

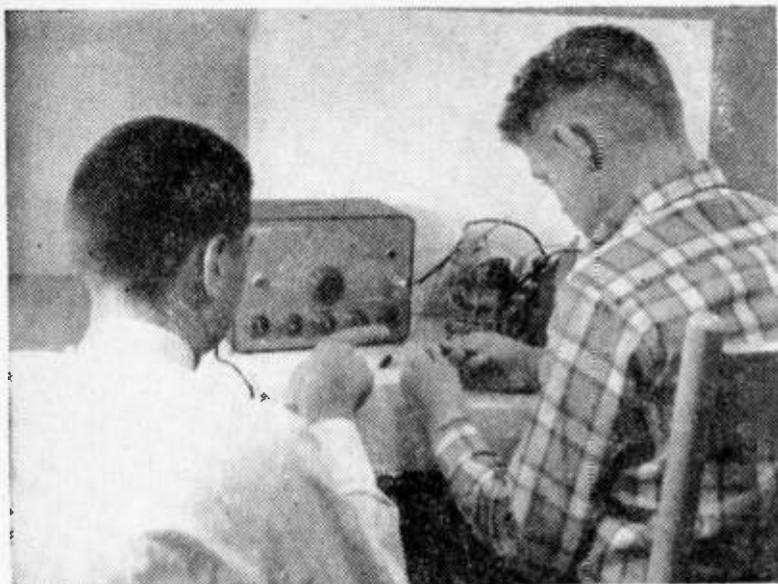Short wave converters and radios are excellent projects after the beginner has acquired some know-how.



Learning how to build test equipment for use in trouble shooting radios and construction projects is important.

tronic device usually has a ready and willing partner for the next construction project.

Where do you start? Age and "do-it-yourself" know-how have considerable bearing on this question. A boy under ten years of age might well start on a crystal set such as the Allied-Knight 83Y261 (\$2.50) and then progress to a code practice set such as the Lafayette KT-72 (\$2.99) or the Knight 83Y239 (\$3.95), which provide an opportunity to learn code. After this he may progress to the point where an older boy might start—the experimental stage. An experimental kit may be a home-rolled job or a professional one such as the Allied-Knight 83Y299 Transistor Lab Kit (\$15.75).

A project that is usually best reserved till after the Lab Kit is a short wave converter kit such as the Lafayette KT-123 (\$9.80). This converter brings in short wave on a broadcast receiver without any receiver changes. In lieu of the converter a simple short wave receiver such as the Knight 83YX259 "Space Spanner" (\$19.95) might go well. The short wave converter or receiver approach is a good one because it creates an extracurricular electronics interest that is broadening and doesn't eat up additional kit or parts dollars.

At this stage of the game, you're ready to go on to test equipment. A multimeter is a must for the serious electronics hobbyist. The Lafayette TK-10 Kit (\$11.95) or the Heathkit MM-1 (\$29.95) are representative kits. A signal generator such as the Knight 83Y145 RF Signal Generator (\$19.75) is also an important instrument to acquire.

If the kit prices seem to amount to a lot of money when you add them up, bear in mind that this number might represent a year's investment.

In some cases, of course, the father and son team will want to move faster. Regardless of the rate at which you pursue your electronics hobby, remember that every dollar you spend


for kits or construction parts is buying know-how, skill and experience, as well as equipment for future use.

At this point in the father-son electronics pursuit, you're ready to tackle magazine construction projects. Generally speaking, this kind of construction is more educational than kit construction. But kits are recommended for earliest projects because construction success comes easily with a minimum amount of know-how and time.

One word of caution. Don't get so wrapped up in turning out construction projects that you neglect to learn electronic principles. To get the most out of your hobby, back the construction with reading in electronic theory. Some good books on the fundamentals will help considerably. Try to understand how circuits work. This will give you a fuller understanding of your hobby and a better basis for a future in electronics.

Good luck to both of you on your electronic hobby. And by the way—maybe mother and sister would like to get in on the fun, too.

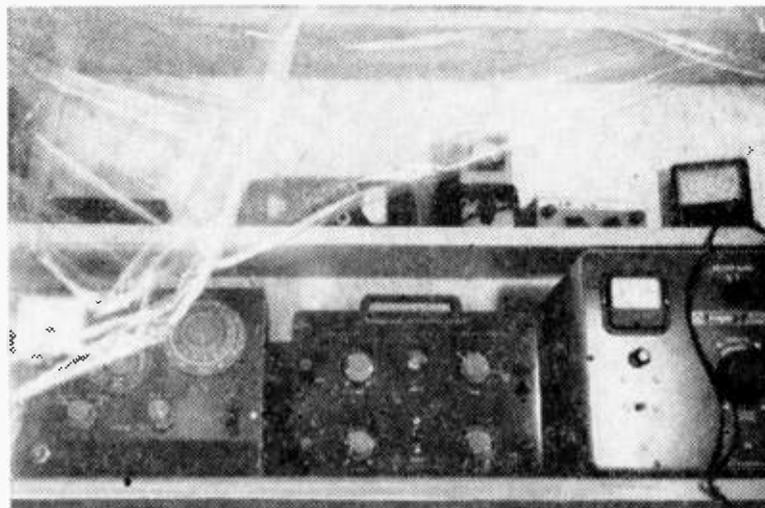Protect Instruments with Polyethylene Film




- Dust and other air pollution poses a threat to instruments. This pollution readily enters ventilation openings and can eventually cause trouble. But the more visible effects on the exterior of instruments are likely to become annoying in a much shorter time. Greasy particles tend to make dirt stick to instruments and cause a film to form. In a short time the once shiny instrument has lost its luster. This dirt film is not easy to remove, and sometimes the required cleaning will damage the instrument finish.

A sheet of polyethylene film fastened to the front of your instrument shelf will protect your instruments and minimize the effects of pollution in the air. The polyethylene film protects the instruments and yet allows you to see them. Simply throw it back to use the instruments.

The polyethylene film may be obtained from Sears-Roebuck or it may be salvaged by splitting a polyethylene clothing bag.

Using Positive Feedback

By C. F. ROCKEY

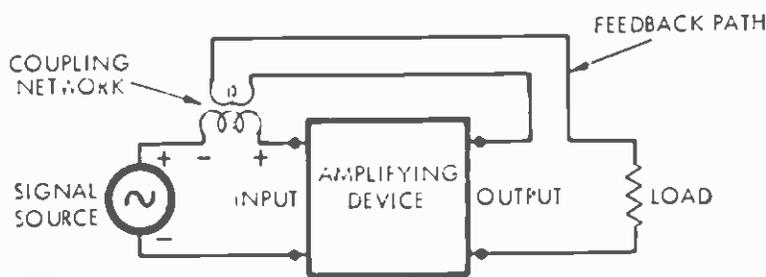

1 DIAGRAM OF AMPLIFIER EMPLOYING FEEDBACK

ONE of the truly valuable techniques available to the small-receiver designer is positive feedback, or regeneration. Most small receiver projects utilize it; in fact, all truly sensitive receivers using less than five tubes or transistors probably apply this principle.

Positive feedback owes its effectiveness to the reduction of circuit losses which it accomplishes. All apparatus contributes some loss of energy to a radio signal as it passes through; even one inch of hookup wire has measurable resistance. This unavoidable extraction of signal energy reduces both the available amplification and the selectivity of a receiver. Positive feedback takes a little of the relatively strong signal appearing in the output of an amplifier and transfers it around to the input, overcoming some of the losses in the circuit (Fig. 1).

Thus the losses of the circuit are reduced, and in effect the resistance of the tuning circuit or other circuit is reduced. In the case of the tuning circuit, since selectivity is an inverse function of its resistance, the tuning curve will be sharpened considerably (Fig. 2).

By "positive" feedback is meant that the feedback path and coupling network are arranged to make the feed-back voltage add to the original signal voltage at any instant. Such a connection enhances the gain and reduces the bandwidth of the circuit involved.

The additional gain is expressed in this formula:

$$\text{Gain with Positive Feedback} = \frac{\text{Normal gain}}{1 - \text{Normal gain} \times \text{Feedback Ratio}}$$

The feedback ratio is the ratio of the voltage fed back over the output voltage. It is always a number smaller than one.


Even though you've let your algebra slip, you can still see that as the feedback ratio (amount of voltage fed-back, in effect) is increased the denominator of the fraction grows smaller. And as the denominator grows smaller, you will recall, the whole quantity becomes larger, since the numerator remains constant. This means that a comparatively small amount of feedback will give a large increase in gain.

Suppose we have an amplifier with a normal, non-feedback gain of five. Now, let us arrange that 1/10 of the amplifier's output voltage will be additively (positively) fed-back into the input. Substituting these values into our equation we see that:

$$\text{Gain with Feedback} = \frac{5}{1 - (5 \times 1/10)} = \frac{5}{1/2} = 10$$

Thus we see that even this comparatively small amount of feedback has doubled the actual amplification of our system. Some calculated gain values obtained from this same hypothetical amplifier with various values of feedback are tabulated below:


Ratio $\left(\frac{\text{Feedback Voltage}}{\text{Output Voltage}}\right)$	Effective Circuit Amplification
Without Feedback	5.0
0.05	6.7
0.10	10.0
0.125	13.7
0.150	20.0
0.175	40.0
0.195	200.0

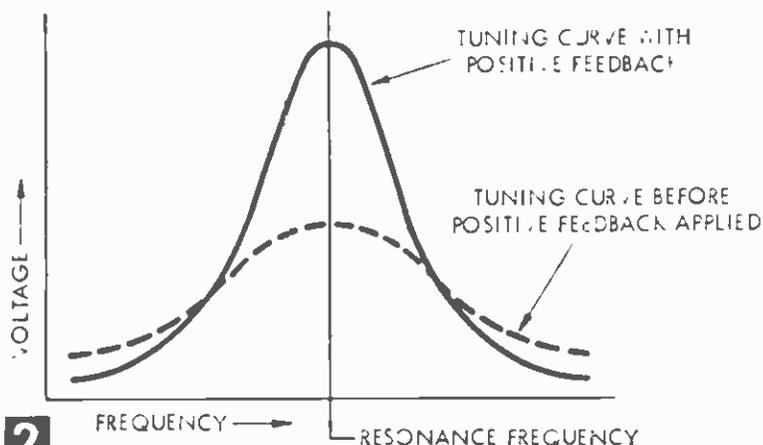

2

The value of feedback is limited by the fact that when the product of the normal gain times the feedback ratio becomes equal to one, the system breaks into oscillation. As the feedback is increased toward the maximum value, the circuit adjustment becomes exceedingly critical. But positive feedback makes it possible to obtain as much amplification from one tube or transistor as would be gotten from two or three without it, so it is well worth the drawbacks.

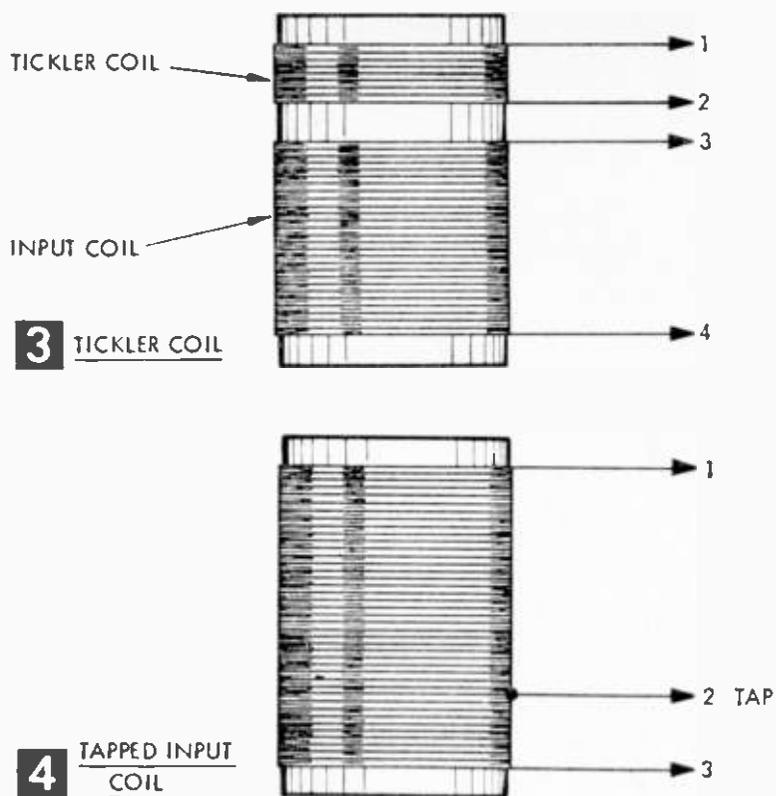Positive feedback is always employed in the



higher frequency circuitry of a receiver, since the bandwidth-limiting action makes its use in the audio section inadvisable. While most often employed in the detector circuit, regeneration often also improves the operation of if or rf amplifiers; here it increases both sensitivity and sharpness of tuning to a marked degree.

In any case, the requirements for successful application of positive feedback may be summarized as follows:

1. The feedback must add to the signal input voltage at all times. This means the phasing or polarity of the coupling circuit must be correct.
2. The magnitude of the feedback's effect must be under perfect control and smooth at all times.
3. Normal control of feedback must have a minimum effect upon the frequency to which the circuit is tuned.

Most often, an inductive feedback system is used wherein the energy is transferred via a magnetic field.

The first method of inductive feedback employs a tickler coil, connected in series with the output circuit and coupled magnetically to the tuned input coil. If the two coils, tickler and input coil are wound in the same direction and on the same form, they must be connected according to Fig. 3 and Table A.

The tickler coil should be spaced as closely to the input coil as possible, and should contain the fewest possible turns, determined by experiment.

Another commonly-used arrangement for providing positive feedback is by the use of a tapped input coil. This is shown in Fig. 4, connections in Table B.

Again, exact placement of the tap along the coil must be determined experimentally in new designs; in most cases, however, the

TABLE A—TICKLER COIL CONNECTIONS

Type of Circuit	Connection Numbers			
	1	2	3	4
Vacuum Tube Grounded Cathode	Plate	B+	Ground	Grid
Vacuum Tube "Hot" Cathode	Ground	Cathode	Ground	Grid
Grounded Emitter Transistor	Emitter	Battery	Ground	Base
Grounded Base Transistor	Battery	Collector	Ground	Emitter

TABLE B—TAPPED INPUT COIL CONNECTIONS

Type of Circuit	Connection Numbers		
	1	(Tap)2	3
Vacuum Tube Grounded Cathode	Plate	Cathode	Grid
Vacuum Tube "Hot" Cathode	Grid	Cathode	Ground
Grounded Emitter Transistor	Collector	Emitter	Base
Grounded Base Transistor	Collector	Emitter	Base

number of turns between connections one and two will be appreciably greater than between two and three.

Although physical arrangements may vary, other taps may be used in certain applications, particularly with transistors, but the identical principles apply in coil connections.

Control of the effects of feedback is most often accomplished by controlling the gain of the circuit rather than by varying the feedback coupling. This is because most feedback variations tend to influence the tuning of the circuit at the same time.

The most widely-used method for controlling the effect of feedback involves varying of either the dc plate voltage (with triodes) or the screen-grid voltage (with pentode tubes). With transistors, current practice involves variation of the dc base bias in most instances. This is practically done with a well-bypassed volume control potentiometer. When set up properly, these means provide absolutely smooth and reproducible control of the effects of feedback with a minimum of influence upon circuit tuning. This, along with a little circuit savvy and shielding, suffices for requirement three that we stated earlier.

From the operational standpoint, these two rules should be observed:

1. For maximum gain, adjust the effective feedback as closely to the oscillation point as possible. The oscillation-point is manifested by a click or plunk, followed by evidences of instability or reduction or gain as the feedback is advanced.

2. If for any reason it is desirable to operate the circuit in an oscillating condition; as for CW radiotelegraph reception with the simple receiver, for instance, again always operate as close to the oscillation-point as expedient.

RCA training at home can be the smartest investment you ever made

Look what you get in the Course in Radio and Electronic Fundamentals

40 Fascinating THEORY LESSONS




Containing all the basic principles of radio and electronics in easy-to-understand form.

40 EXPERIMENT LESSONS



Each containing absorbing, practical experiments bound together in 20 books.

40 SERVICE PRACTICES

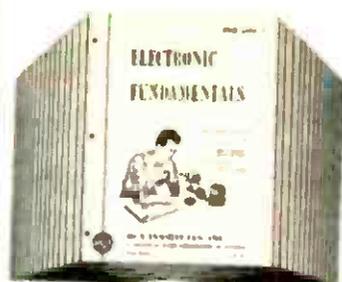

Full of practical, time-saving and money-saving servicing tips, bound into 20 books.

PLUS ALL THIS AT NO EXTRA COST...

15 KITS


to build a Multimeter, AM Receiver and Signal Generator. Kits contain new parts for experiments, integrated so as to demonstrate what you learn in the lessons and to help you develop technical skills. Each kit is fun to put together!

MULTIMETER



A sensitive precision measuring instrument you *build* and *use* on the job. Big 4½" meter with 50 micro-amp meter movement. 20,000 ohms-per-volt sensitivity d-c, 6,667 a-c.

AM RECEIVER

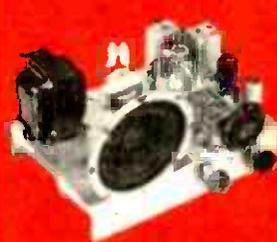

Have the satisfaction of building your own radio receiver with this high-quality 6-tube superheterodyne set. Big 5" speaker, fine tone!

SIGNAL GENERATOR



A "must" for aligning and trouble-shooting receivers. Build it for your own use. 170 KC to 50 MC fundamental frequencies for all radio and TV work.

Practical work with the very first lesson! Pay-only-as-you-learn! No long-term contracts to sign! No monthly installment payments. Pay only for one study group at a time if and when you order it!

Stake out your future in electronics now!

SEND FOR OUR FREE HOME STUDY CATALOG TODAY!



Just fill out this card and drop it in the mail—no postage needed. ▶

RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

RCA INSTITUTES INC. Home Study School, Dept. RX-21

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, rush me the FREE 64-page illustrated book describing your electronic training program (check one). No salesman will call.

Home Study Los Angeles Resident School New York Resident School

Name

(Please Print)

Address

City Zone State

Veterans: Enter discharge date.....

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Enclose this card in envelope and mail to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

HOME STUDY SCHOOL



RCA TRAINING CAN BE THE SMARTEST INVESTMENT YOU EVER MAKE

With RCA Institutes Home Study training you set your own pace in keeping with your own ability, finances and time. You get prime quality equipment as a regular part of the course . . . and you never have to take apart one piece to build another. Perhaps most important, RCA's liberal Pay-As-You-Learn Plan is the most economical home study method *because you pay only for lessons as you order them . . . one study group at a time!* If you drop out at *any* time, for *any* reason, you do not owe RCA one penny! No other obligations! No installment payments required! Licensed by New York State Education Department.

Choose **YOUR FUTURE** from this list of courses:

- Radio and Electronic Fundamentals (see reverse side)
- Television Servicing
- Color Television
- Electronics for Automation
- Transistors

RESIDENT SCHOOLS

START YOUR CAREER IN ELECTRONICS NOW AT RCA INSTITUTES in Los Angeles - New York City

CHOOSE FROM THIS LIST . . .

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad, with Algebra, Physics or Science	Day 2 1/4 yrs. Eve. 6 3/4 yrs.
B	TV and General Electronics (V-7)	2 yrs. High School, with Algebra, Physics or Science	Day 1 1/2 yrs. Eve. 4 1/2 yrs.
C	Radio & TV Servicing (V-3)	2 yrs. High School with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs.
D	Transistors	V-3 or equivalent	Eve. 3 mos.
E	Electronic Drafting (V-9)	2 yrs. High School, with Algebra, Physics or Science	Eve. Basic: 1 yr. Advanced: 2 yrs.
F	Color TV	V-3 or equivalent	Day 3 mos. Eve. 3 mos.
G	Audio-HI Fidelity	V-3 or equivalent	Eve. 3 mos.
H	Video Tape	V-3 or equivalent	Eve. 3 mos.
I	Technical Writing (V-10)	V-3 or equivalent	Eve. 3-18 mos.
J	Computer Programming	High School grad	Day 6 weeks Eve. 24 weeks Sat. 30 weeks
K	Radio Code (V-4)	8th Grade	Eve. as desired
L	Preparatory Math & Physics (P-C)	1 yr. High School	Day 3 mos.
M	Preparatory Mathematics (P-0A)	1 yr. High School	Eve. 3 mos.

BUSINESS REPLY MAIL

No Postage Stamp Necessary if mailed in U. S.

Postage will be paid by —

RCA INSTITUTES, INC., Dept. RX-21
350 West Fourth Street
New York 14, N. Y.


FIRST CLASS
PERMIT NO.
10662
NEW YORK, N. Y.



RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Co-educational Day and Evening classes. Free Placement Service. Applications now being accepted.

SEND FOR THIS FREE ILLUSTRATED BOOK TODAY

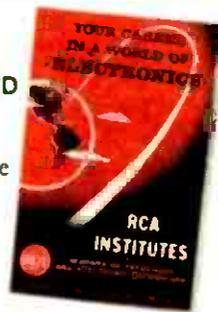Fill in the other side of the postage-free card and check Resident School.




RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

Code Practice Oscillator

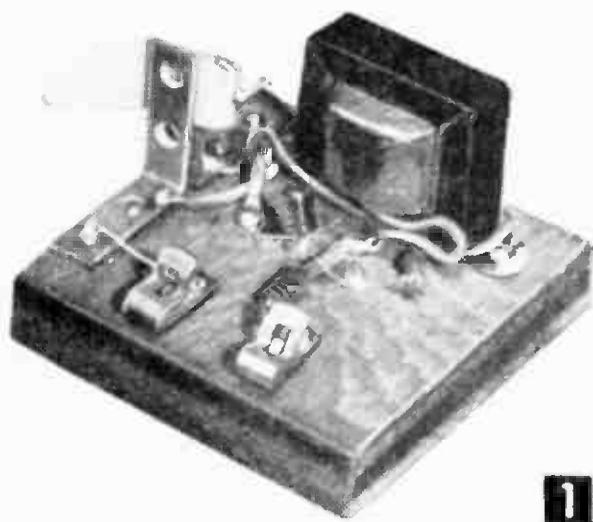

By C. F. ROCKEY

AYE, LADDIE, if you've got a bit of the Scots in you—or even if you haven't—you'll ken this thrifty little oscillator. Its source of power is tap water—or spit—and it's just the thing for code practice, for circuit continuity testing, for capacitor checking, and for use as a signal source when adjusting hi-fi or public address amplifiers.

To build it, first saw, sand smooth and shellac a $\frac{3}{4}$ -in. piece of soft pine or plywood to a 4 x 4 in. block. This is your oscillator's chassis. Next, physically modify the driver transformer by bending the bottom fastening lugs away from the core and removing the mounting frame, finding the dividing point between the "E" and the "I" sections of the core (see Fig. 3) and—carefully—prying up and removing the "I" section. Set the "I" section aside, re-insert the modified core in the transformer's frame and bend the fastening lugs in place.

We used a Thordarson 14-D-93 interstage audio coupling transformer (4:1) that we had on hand, but this type has been discontinued by the manufacturer. Its closest present Thordarson equivalent is the 20-A-16 interstage transformer. This—or any similar transformer made by any other manufacturer—will work just as well in the oscillator's ultra-simple circuit.

When transformer is modified, mount it and all other circuit components except the angle brackets on the wood-block chassis (see Fig. 4), with $\frac{1}{2}$ -in. #6 r.h. wood screws. Before mounting the two angle brackets, clean their facing surfaces carefully with sandpaper or steel wool. Mount them with faces about $\frac{1}{16}$ in. apart.


Make all connections to the transistor connecting lugs before mounting the transistor to avoid




A quick dip of the blotting paper, place it between the brackets, and you've set the set to buzzing, ready to key off for code practice.


any possibility of damaging the transistor with soldering heat. When all wiring is complete (see Fig. 2) and checked, put the transistor into the circuit by clamping its leads under the appropriate soldering lugs and screwing them tight. (The transistor lead adjacent to the red dot is the Collector, the center lead is the Base, the remaining lead is the Emitter.)

Spit Power. Strictly speaking, the source of power for this oscillator is not spit or water. Water is simply the electrolyte of a simple voltage generating cell whose plates are the dissimilar metal faces of the iron and brass brackets. Immerse a piece of blotting paper (about $\frac{1}{2}$ x $1\frac{1}{2}$ in.) in tap water, or moisten the paper with saliva, insert it between the bracket faces and you will have a source of power for your oscillator. What you're doing, is duplicating one of the first steps taken by Alessandro Volta (1755-1837) in developing the world's first battery (or *pila*, as Volta called it). Volta found that if two dissimilar metal plates (he used copper and zinc) were separated by moist paper, a current would

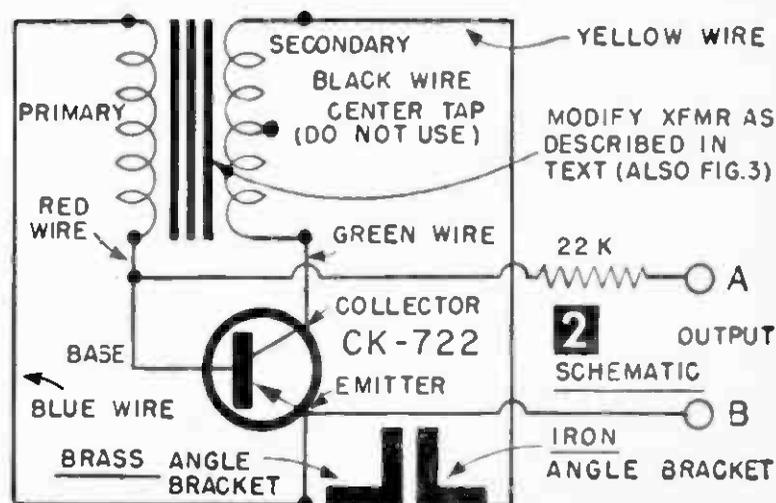


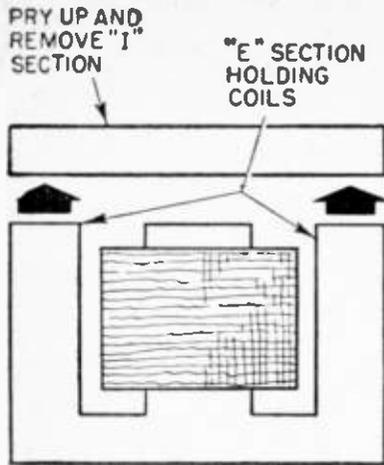

3 MODIFICATION OF TRANSFORMER

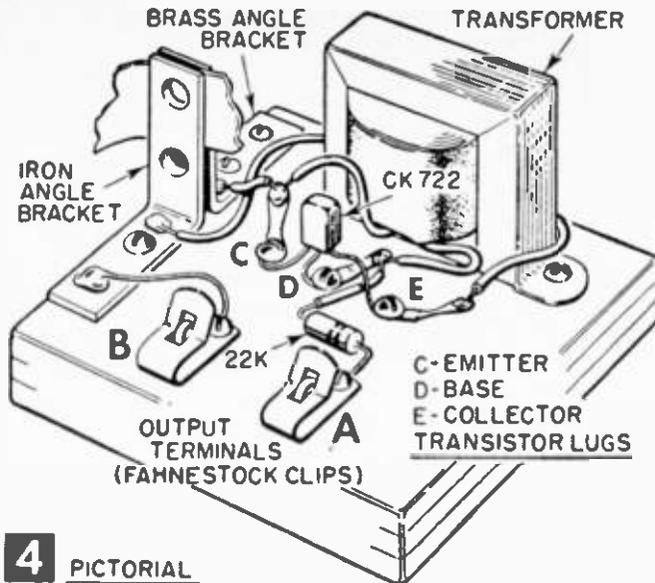

4 PICTORIAL

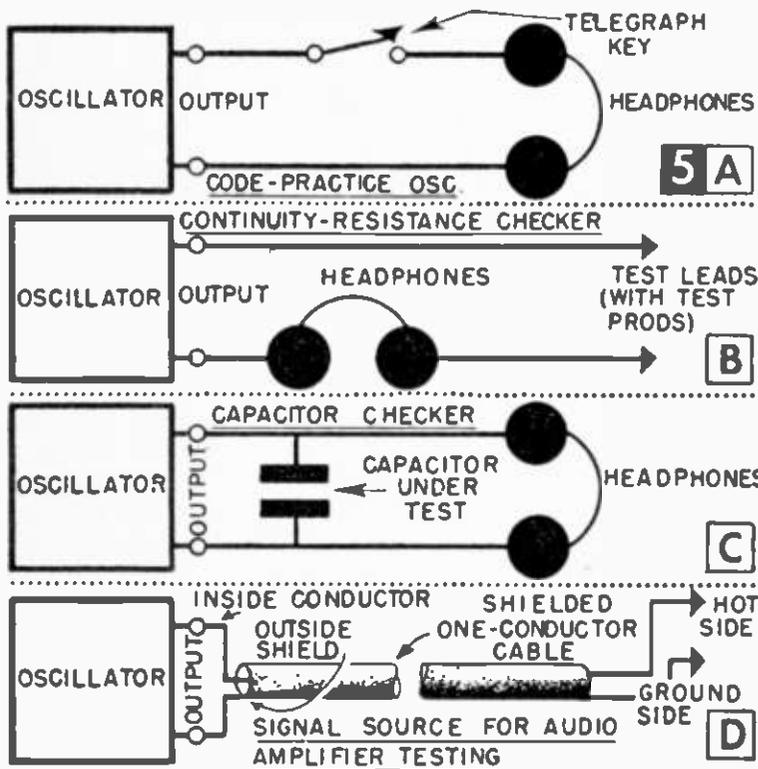

MATERIALS LIST—SCOTSMAN'S DELIGHT

No.	Req'd	Description
1	pc	3/4x4x4" pine or plywood
9		#6x1/2" r.h. wood screws
1		brass angle bracket, 1 1/2" arms
1		iron angle bracket, 1 1/2" arms
2		Fahnestock clips
1		CK722 Raytheon transistor
1		Thordarson 20-A-16 transformer (or Stancor A-53 or Triad A-31X)
1		22,000 ohm, 1/2 watt resistor
1	pr	2000-4000 ohm headphones (Trimm "Featherweight" standard or "Professional"—Allied cat. no's. 59J000, 59J020, or 59J021)
1	pc	blotting paper

flow between them when their outer surfaces were connected together.

Ordinary tap water usually contains enough impurities to act as an electrolyte; saliva, too. But if you don't get oscillation with either used as an electrolyte, do as Volta did, use a dilute salt solution, 1/2 teaspoonful of table salt in a small glass of water.

To test the unit for oscillation, connect a high-impedance (2000 to 4000 ohms) pair of earphones across the output terminals and listen for a clear, smooth tone of about 500-1500 c.p.s. If you


don't hear such a tone, check the wiring and transistor connections for correctness and if these are as they should be insert a 1 1/2v. dry cell temporarily across the brackets (plus side of cell to the brass bracket). This will give you a check on the transistor's condition. If it's good, oscillation will certainly occur. If not, substitute a new transistor in the circuit. (CK722's have proved unusually reliable in this simple circuit, but any other good PNP transistor may also be

used.) Also, if you have used a transformer other than those specified in the Materials List, see if reversing its primary connections helps the tone.

With the unit operating, it can be used as a code-practice oscillator (see Fig. 5A); as a continuity-resistance checker to locate open circuits (Fig. 5B)—in circuits up to 10-megohms resistance if you use sensitive phones; as a capacitor checker (Fig. 5C); and as a signal source for audio amplifier testing (Fig. 5D). If too much hum is present for best audio amplifier testing, put the oscillator in a grounded coffee can and bring the shielded cable out through a hole in the can's top cover.

In capacitor testing, a good paper or mica capacitor in the capacity range of .001 mfd to .1 mfd will slightly weaken the signal and noticeably change its frequency. An open capacitor will have no effect on the signal, a shorted capacitor will kill it. (It is not recommended that you test electrolytic capacitors with the oscillator.)

Heavy Current Relay

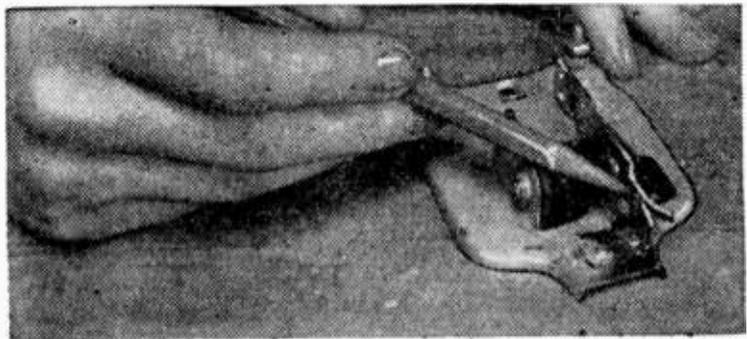

• This little relay will handle as much as two amps. without trouble. Remove stationary contact of an electric bell or buzzer and turn it around. When current flows through coil, armature is pulled in and it makes contact with stationary member.—R.F.Y.


Better Soldering

• When using non-corrosive soldering paste flux for radio work, first warm the joint slightly with the soldering iron, then apply the paste with a piece of wire. The small amount of flux which melts on the joint is entirely adequate. Excessive flux spreads to adjacent insulation, causing leakage.

Transistorized Electronic Megaphone

Highly portable, self-contained P.A. with a 500-ft. plus range

By HAROLD P. STRAND

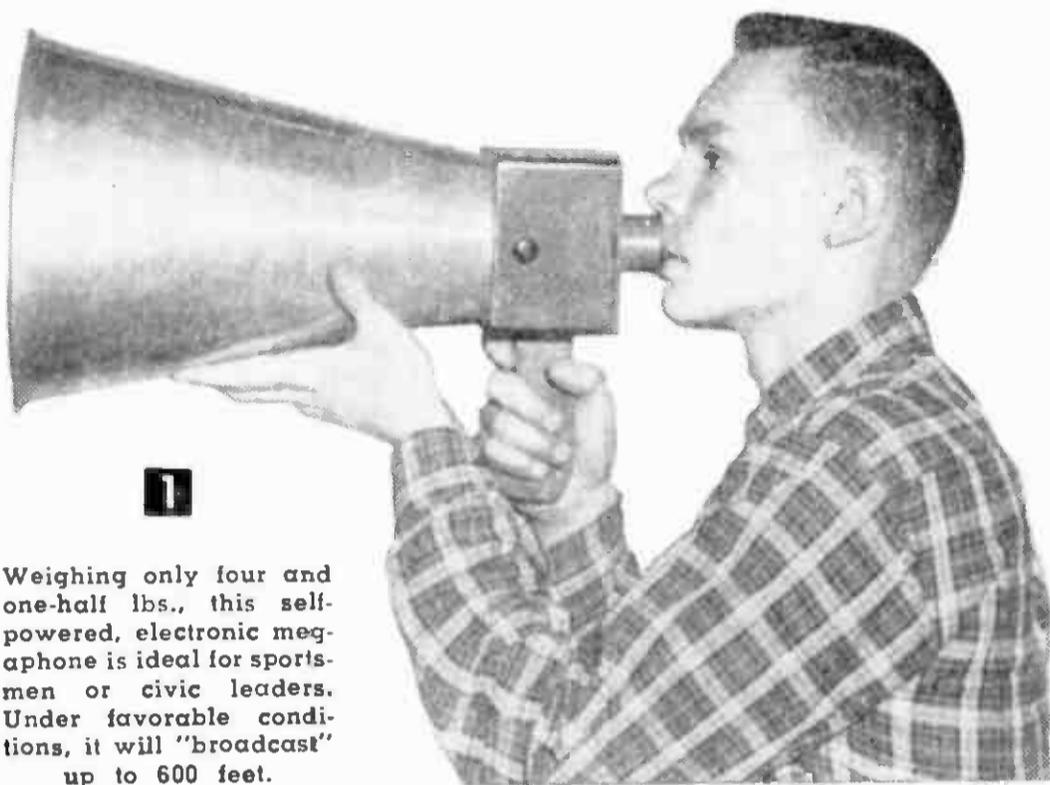

Weighing only four and one-half lbs., this self-powered, electronic megaphone is ideal for sportsmen or civic leaders. Under favorable conditions, it will "broadcast" up to 600 feet.

amplification. Transistors employed in an amplifier circuit allow the use of small, light batteries contained in an attached housing back of the horn (Fig. 2). It has a volume control, although raising or lowering the voice level usually serves to control the output volume. A push-button switch on the pistol grip handle is controlled by the forefinger. Holding the switch closed turns the power on from the 22½ volt battery and the 3 volt bias battery.

Releasing the switch eliminates power drain when megaphone is not in use.

Since the *in-use* maximum current drain at the loudest volume level is about 40-50 milliamperes from the 22½ volt battery, and about 2.5 from the 3 volt battery (used as


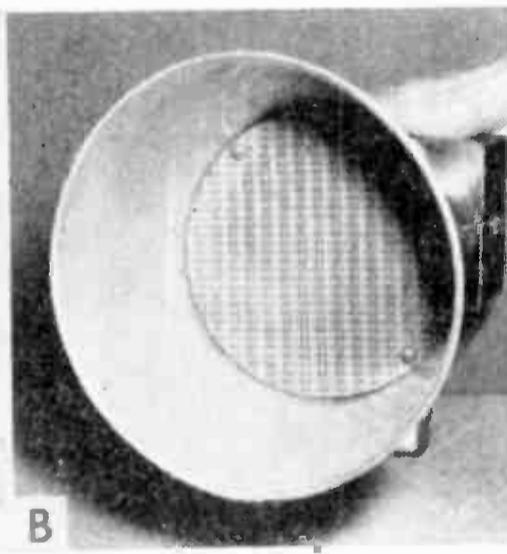
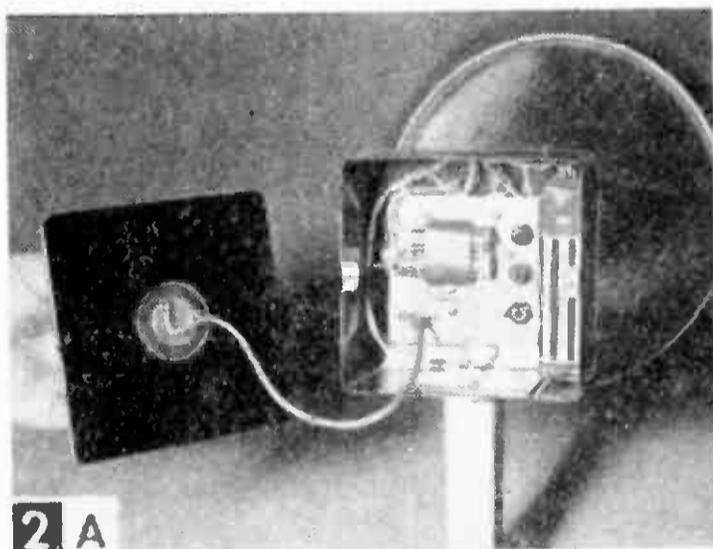


Fig. 2A (Left) Cover removed to show housing components (detailed in Figs. 3 and 4). Note small microphone mounted in cover plate at left, with its leads plugged into amplifier chassis. Fig. 2B (Right) Front of megaphone, showing how grille cloth mounted over wooden ring holding speaker presents neatly finished appearance.

WHETHER you skipper your own cabin cruiser, or are active in local civic groups which hold or sponsor sports events, public meetings or rallies, you'll find this highly portable, self-contained "public address" system mighty handy for long distance hollering. Come to think of it, this megaphone might be just what your wife would like to have for summoning the children for supper. It will "broadcast" intelligible speech from 500 to 600 feet, depending on weather conditions.

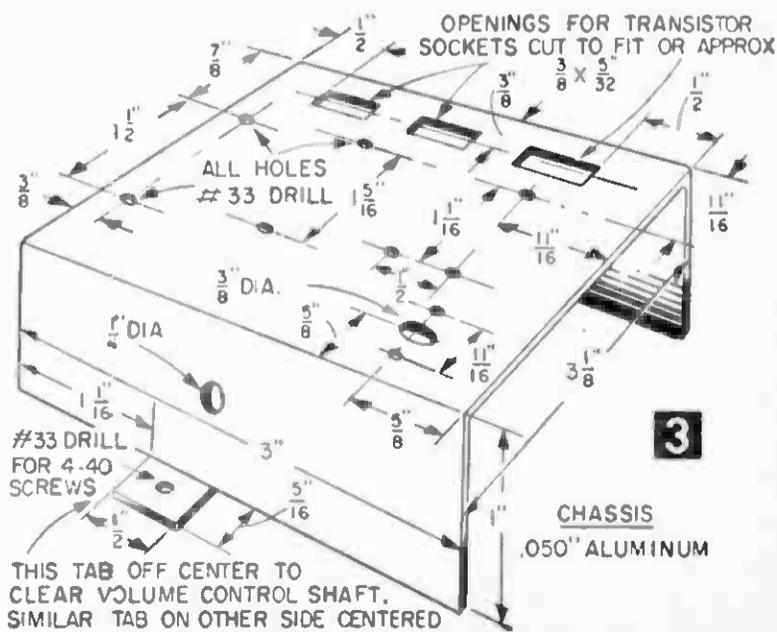This unit is designed for medium level voice



THIS TAB OFF CENTER TO CLEAR VOLUME CONTROL SHAFT. SIMILAR TAB ON OTHER SIDE CENTERED

MATERIALS LIST—ELECTRONIC MEGAPHONE

Electronic parts listed below were supplied by Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

- 1 6" P.M. speaker, 2.15 oz., magnet. Oxford 6EVS 3.2 ohm voice coil or Utah equivalent, with 4-6 watts rating
- 1 Shure microphone, MC-11 controlled reluctance type, 1" diameter
- 3 transistor sockets MS-275
- 3 G. E. 2N44 transistors
- 1 RCA type phono jack and plug
- 10' shielded cable, small diameter (about 1/8" O.D.)
- 1 10,000 ohm miniature volume control VC-34
- 1 Burgess XX15 B battery, 22 1/2 volt
- 2 Burgess #Z penlight cells
- 1 three-prong plug to fit XX15 battery
- 1 AR-109 driver transformer
- 1 AR-138 output transformer
- 1 Argonne 8 mfd 15 volt capacitor, 15v
- 1 47 ohm 1/2 watt resistor
- 1 22,000 ohm 1/2 watt resistor
- 1 1200 ohm 1/2 watt resistor
- 1 #6 solder lug or more if needed for ground conn. (see below)
- 1 Bakelite terminal strip 7 terminals, two grounded, Jones 55-C
- 2 Bakelite terminal strips 2 terminals, one grounded, Jones 51-A (Note: You can use 5 terminals on first and 1 terminal on second strip mentioned above, all lugs to be insulated and use solder lugs under chassis screws for ground connections)
- 1 miniature knob for 1/8" shaft MS-185
- 1 piece plastic grille cloth about 7 x 7"
- 1 D.P.S.T. push leaf switch, Switchcraft 1004 or Mallory 1014
- 1 speaker cone made of half-hard .032 sheet alum., riveted or with lock seam, front end rolled bead, 12 3/4" long, 9 1/2" O.D. large end, 4" O.D. small end. Robert Towne, 49 Abbott Avenue, Everett, Mass., will make them for our readers for \$7.25 P.P. in U.S., express or money order


BAKELITE—supplied by Forest Products Co., 131 Portland Street, Cambridge, Mass., for \$3.00 P.P. in U.S., express or money order.

- 1 pc black paper base 1/4 x 5 x 5". Cut and dress to tightly fit inside housing
- 1 pc black paper base 1/8 x 5 x 5". Cut and dress to fit on outside front of housing
- 2 pcs linen base natural finish 1/8 x 5 x 2 1/4" (handle sides)
- 1 pc paper base natural finish tubing 1 1/2" O.D., 1/16" wall, 1 7/8" long (mouthpiece)

MISCELLANEOUS METAL AND WOOD STOCK (Try local metal-working and cabinet shops)



- 1 pc aluminum about .050 x 3 x 5 3/4" (chassis)
- 1 pc aluminum half-hard alloy or material that can be bent but has reasonable rigidity, 1/8" x 1 3/16" x about 11 3/4" (handle frame)
- 1 pc aluminum half-hard alloy about .040-.045 x 3 9/16 x 18 1/2" (housing) can also use soft sheet steel about .034"
- 1 pc aluminum half-hard alloy 3/32 or 1/8" x 5/8" x about 17". Bend to form speaker U bracket support
- 1 pc hard brass or phosphor bronze about .010 x 2 3/8 x 7/8" (clip for bias battery)
- 1 pc dry maple or birch 3/4 x 4 1/2 x 4 1/2". Turn to tapered disc to fit tightly in small end of cone
- 1 pc hardwood plywood such as birch 1/4 x 7 x 7". Cut-out ring to hold speaker in cone

Misc. hook-up wire, screws, nuts, paint, Pliobond cement, etc.
 Note—Pure aluminum bends too easily for our purpose. What is commonly called half-hard can be formed or bent but is strong and rigid. Some trade numbers are 3003H14 half-hard, 11H14 half-hard and 5052H34 quarter-hard. Any similar type could be used where a test shows it workable for bending but as rigid as soft steel. Lightness of aluminum makes it ideal for keeping megaphone light. Usually supply houses do not sell small quantities so it has to be picked up in shops using this stock.

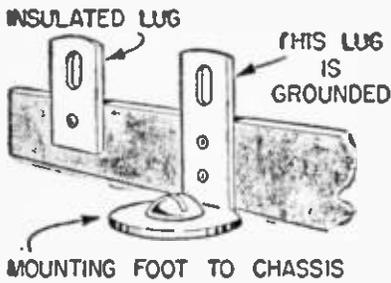

Terminal strips 55-C and 51-A have grounded lugs as shown above for connection of leads going to ground. If strips with all lugs insulated are used, simply use solder lugs under chassis screws for ground connections, as at AR-109 transformer feet.

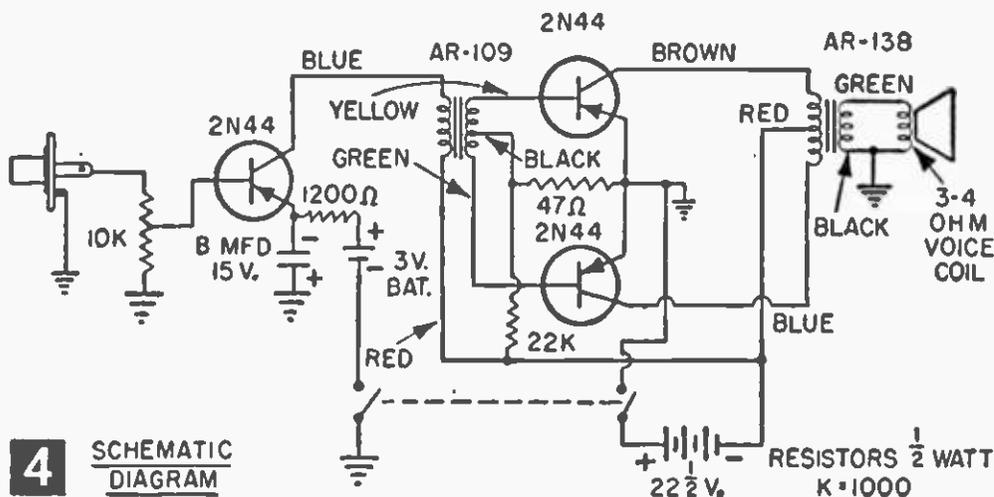
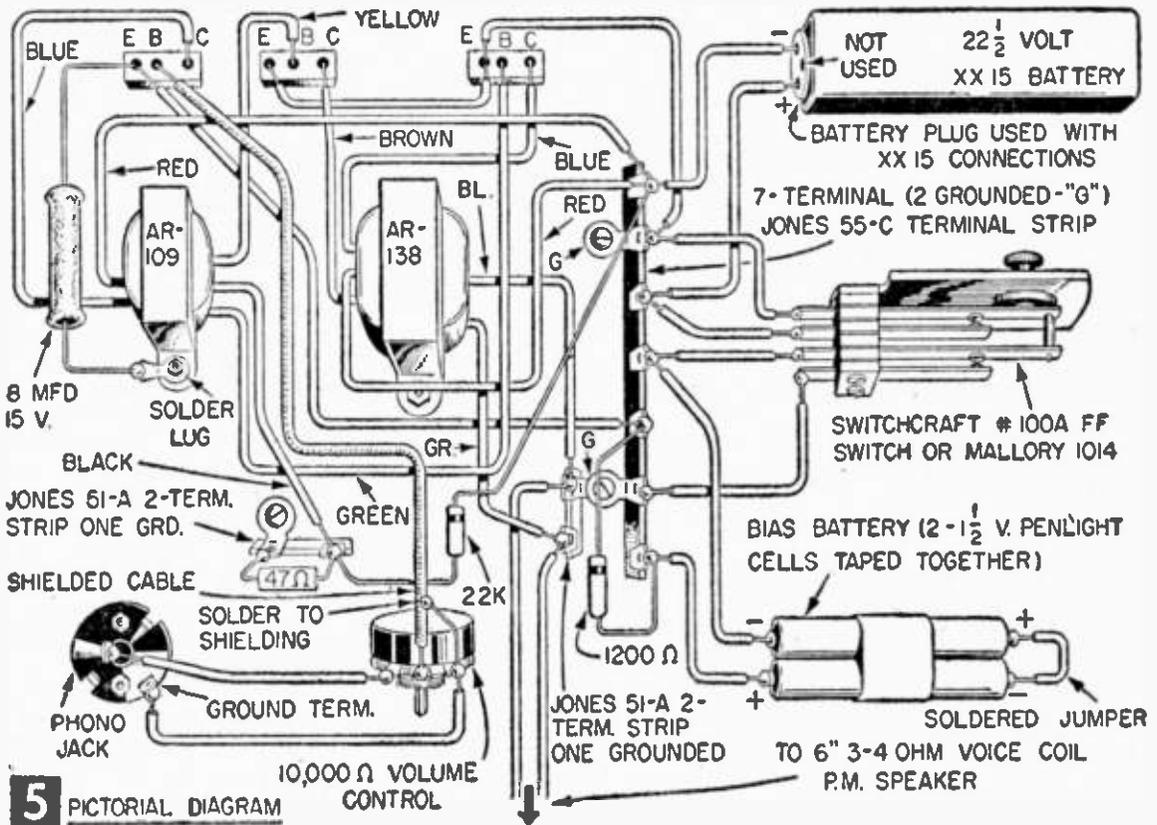
bias in the emitter of the driver stage), battery life should be quite high. The Shure controlled-reluctance type microphone has an output level of -71 db below




one volt per microbar, and an impedance of 1000 ohms. It is only one inch in diameter. It is mounted in a Bakelite tube, which also serves as the mouthpiece (Fig. 2).

The 6 in. permanent magnet type speaker with its 2.15 ounce Alnico magnet is fixed part way down in the cone as in Fig. 2. The three G.E. 2N44 transistors in a push-pull circuit which power

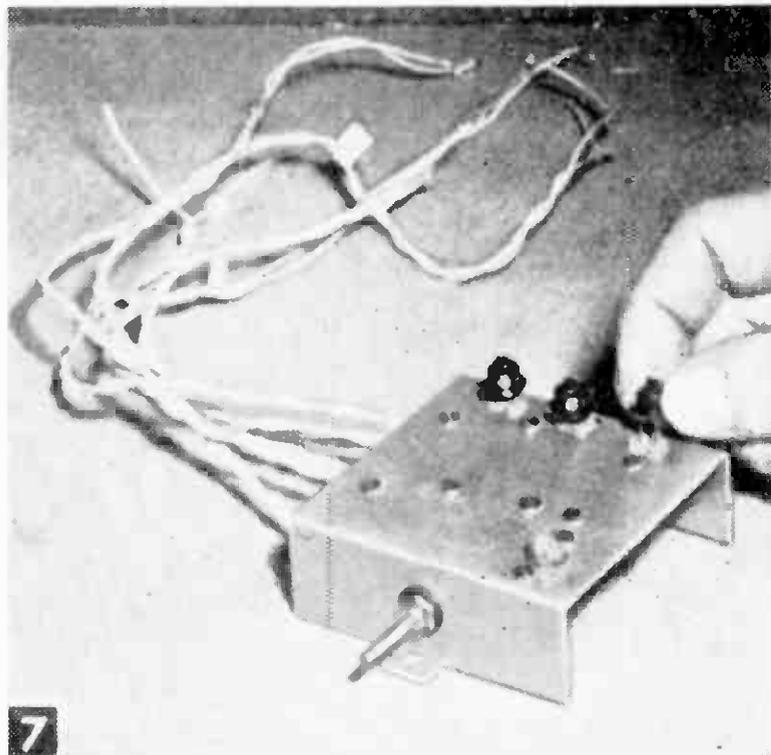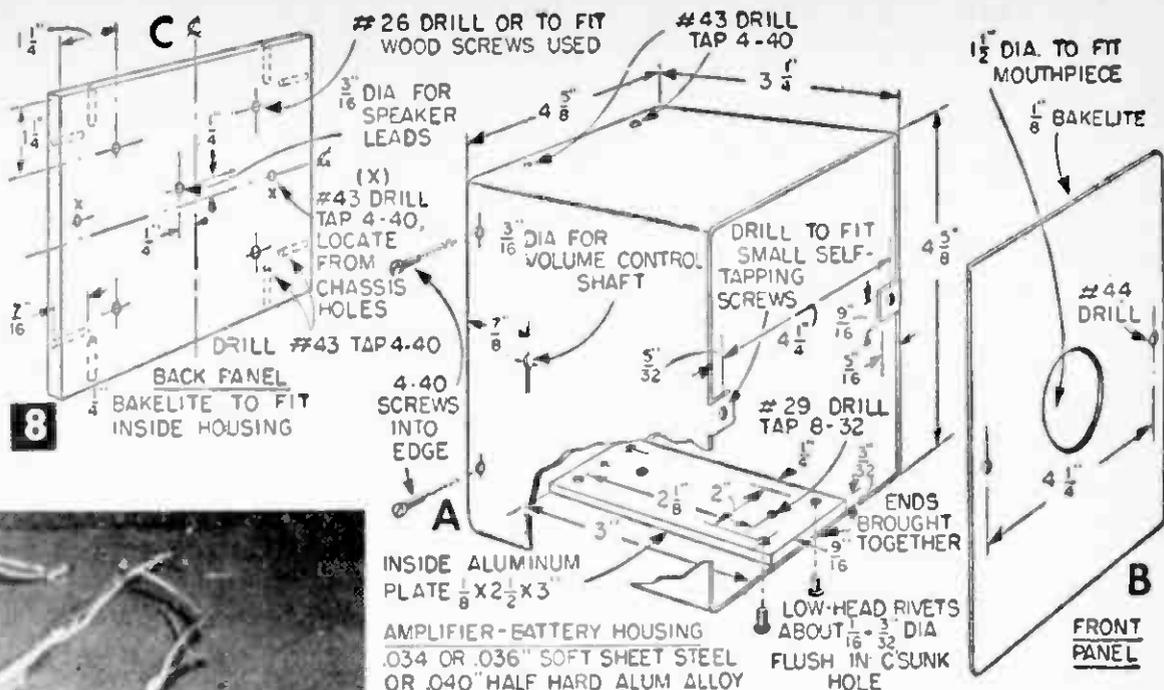the unit, have much higher collector power dissipation than ordinary transistor radio types, such as the 2N107. In addition, the AR-138 output transformer, used can handle more power than the AR-119 or 120 as usually used in radios. Thus you get a surprising volume from this miniature equipment.



7 Test-mounting three audio transistors in their sockets. Leads from these transistors will need to be cut off to about 7/16-in. length with diagonal pliers, but transistors should not be permanently placed in sockets until megaphone assembly is complete, ready for cover plate to be put on (Fig. 2A). Wire leads to batteries, switch and speaker are identified with marked tabs of white tape to assure correct connections. Plus battery lead is also marked to avoid error.

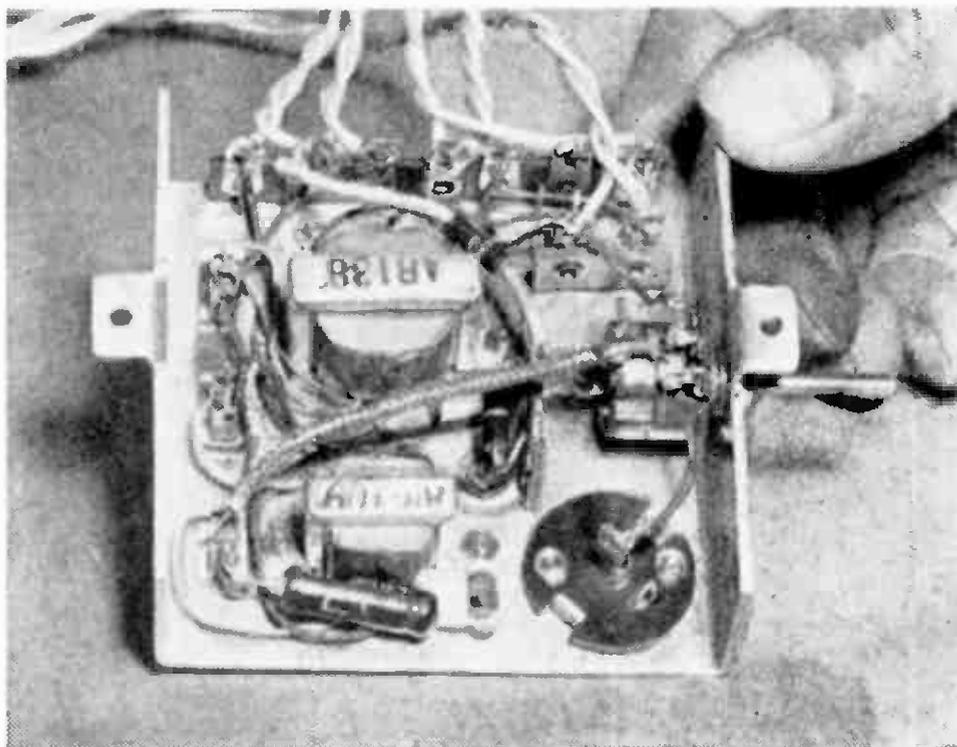

6 Underside of amplifier chassis, with parts mounted and wired according to Figs. 4 and 5.

Parts for this megaphone should cost you from \$35 to \$40, which is only about two-thirds the cost of a typical commercial unit.

Building the Amplifier. Bend up the chassis from sheet aluminum and drill openings for components as in Fig. 3. Figs. 6 and 7 show both sides of this chassis with all parts mounted. Note terminal strip at one end (Fig. 6) for leads to battery, speaker and switch. The input from the mike is at a phono jack in the top of the chassis and the volume control is placed in a side opening, where its shaft will project through the housing for an outside control with a knob.

Use a short piece of shielded wire from volume control to base of first transistor, since this is a sensitive input lead and grounding the shield prevents or minimizes possible hum. Place two small terminal strips in the chassis as in Fig. 5, to provide tie points for soldering leads.

You won't need much hook-up wire in this circuit as the transformers come equipped with leads that are carried to the proper points and soldered. Use only rosin-core solder and apply enough heat from a small iron or soldering gun to fully flow the solder. In making connections to terminal strips, make sure the lugs grounded to the chassis are used for ground connections *only*, as indicated in Fig. 5. If you use other types of terminals by the way, where all lugs are insulated, provide small solder lugs under chassis screws for ground connections.

Next lay out pattern for the amplifier housing (Fig. 8) on sheet aluminum or soft sheet steel (about .034 in.). Housing can be bent over a piece of angle iron in the vise (Fig. 9). Make sure the box is square.




After bending up the housing, bring its two edges together and rivet a piece of 1/8 in. thick aluminum placed inside over the joint (Fig. 10). Drill holes for the short 3/32 in. brass

Forming the amplifier's sheet metal housing, using the rounded edge of a piece of angle iron held in the vise.

Edges of shaped housing are brought together and riveted to an aluminum plate.

rivets, and head the rivets over on the inside in countersunk holes so that the rivets will come flush.

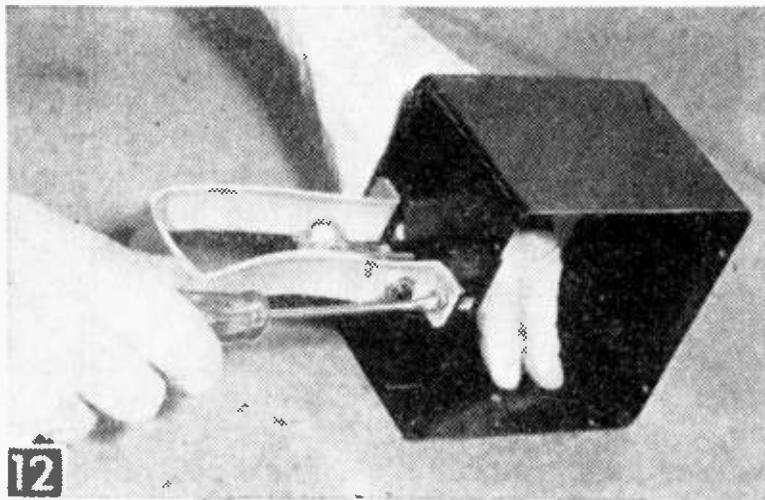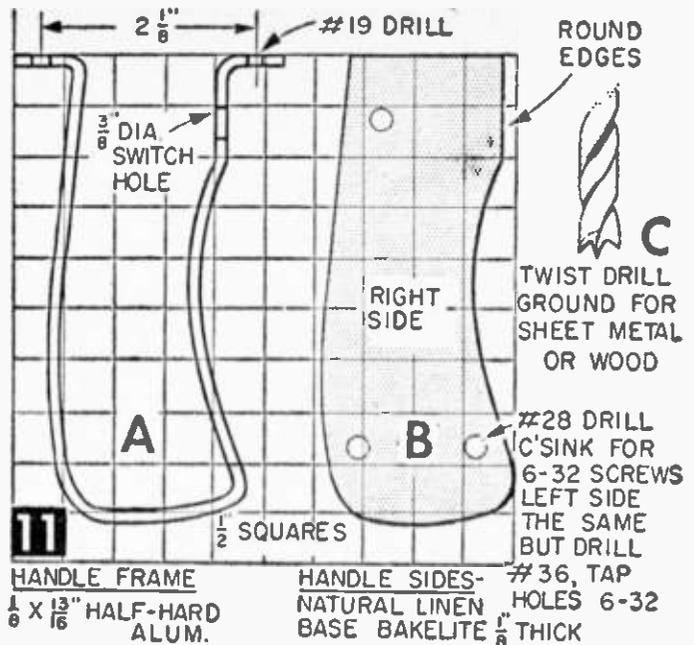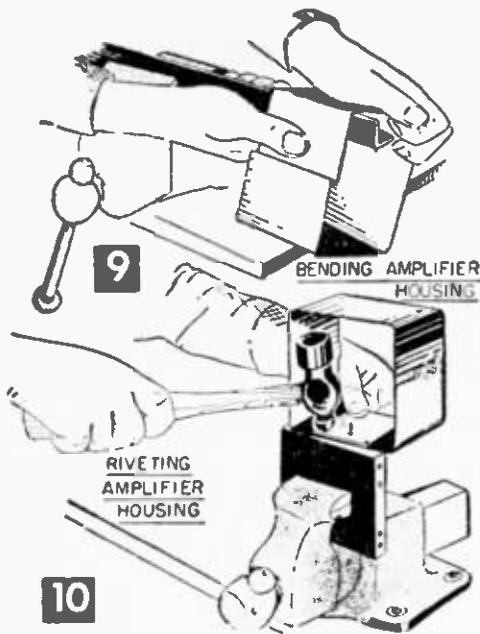To form the frame for the pistol grip handle



12 After fastening switch through its hole in handle with locknuts, attach handle frame to amplifier housing. Note that housing has been finished with primer, then black enamel lightly rubbed with steel wool.

which is of aluminum stock about 3/32 to 1/8 in. thick and soft enough to be bent, lay out the pattern (Fig. 11A) on paper with 1/2 in. squares. Then, carefully bend the aluminum stock to its proper shape over various forming pieces held in the vise.

Install the switch in its hole with locknuts and attach the handle frame to the housing, using two 8-32 machine screws in holes drilled and tapped into the housing and inside plate (Fig. 12).



Because the aluminum cone could be difficult for an amateur to make we recommend you purchase one as indicated in the materials list, or have your local tinsmith make one up for you (Fig. 1). These commercial ones have a neat rolled bead at the front end which helps to stiffen the cone.


To assemble the speaker, you'll need a hardwood disc which fits tightly in the 4 in. end of the cone (Fig. 14). Turn this from maple in any woodturning lathe, giving it a taper to properly fit and come flush with the end. Insert it from the large end of the cone, tapping it down into place. Fasten it with four 3/8 or 1/2 in. #7 flat-head brass wood screws, inserted through the aluminum and into the wood disc in holes spaced and drilled equally around the circumference.

Pliobond cement on the disc edges will further insure its remaining in place.

Figure 14 shows how a piece of 1/4 in. thick black Bakelite, which was carefully cut and fitted to the inside dimensions of the housing as in Fig. 8E, is attached to the maple disc in the end of the cone, using four 3/4 in. #9 roundhead wood screws. Holes for these screws must also be drilled in the maple block so you won't split the wood. Next fit the Bakelite panel into the amplifier housing until it is flush with the edge, and use 4-40 machine screws in drilled and tapped holes to secure it.

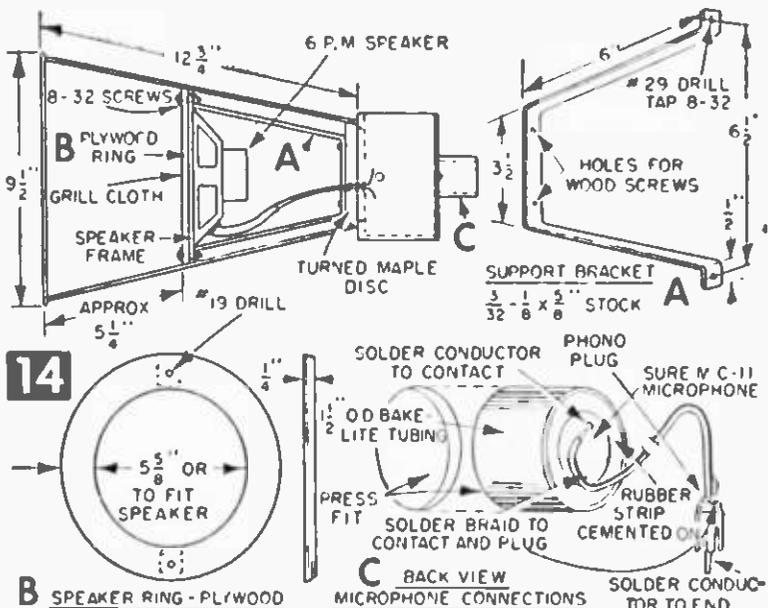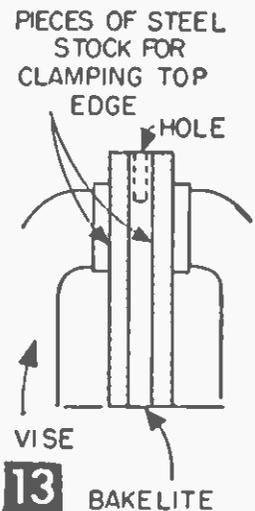Make sure when doing this fitting the switch button is on side of housing nearest speaker cone, and tabs on housing are on the end of housing away from cone. When drilling and tapping Bakelite in its edge, by the way, clamp the Bakelite in a vise so the tap will not tend to split the material, since it splits rather easily in end grain. You can drill the required holes in the metal with



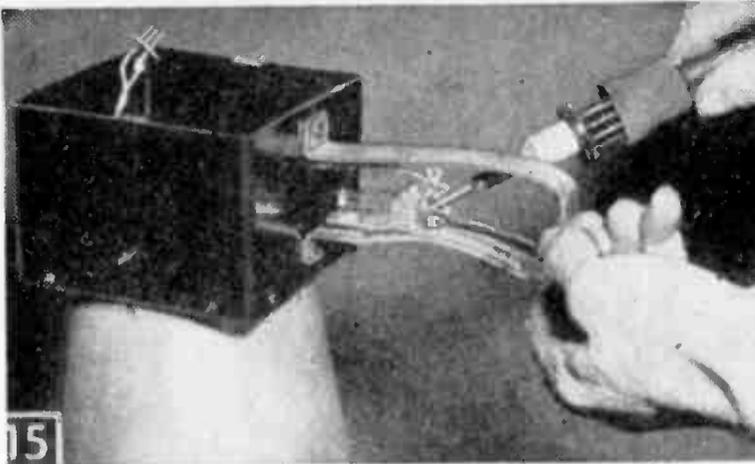

15 Soldering connections to switch terminals in handle of megaphone—see Fig. 5.


Bakelite in place, but only allow drill enough of a depression in the Bakelite to mark where to drill for tapping. Use a #33 drill through the metal and then change to a #43 drill for making the holes in the piece of Bakelite. Then use a 4-40 tap in each drilled hole.

Before fitting the amplifier to the Bakelite piece you have already attached to the cone, first drill a #29 drill hole through the Bakelite and also the wood disc in the cone just off the center (Fig. 8E), for the speaker wires. Pass the speaker leads through this hole and then fit the amplifier chassis against the Bakelite piece and secure it (Figs. 2A and 3), making sure the control knob shaft is allowed to project through the hole for it drilled in the side of the housing. The chassis should also be so located in the housing so that the 22½ volt XX15 battery will fit between the chassis and the housing (Fig. 2A) when wedged with a folded piece of cardboard.

The switch contact wires are brought through their hole (Fig. 8C) in bottom of the case, and connected as shown in Fig. 5 and Fig. 15. Solder a plug to the two leads that go to the battery and make a knot in one of them which will easily identify the plus lead for you. Examination of the way the three-prong plug fits in the battery quickly shows which terminal of the plug is plus.


Mounting the Speaker. Figure 14 shows how the speaker is held part way down in the cone by mounting it to a support that is bent up from any light metal, as in Fig. 14A. Since the size of the cone and the speaker size may vary a little, the exact length of the bracket is not given.

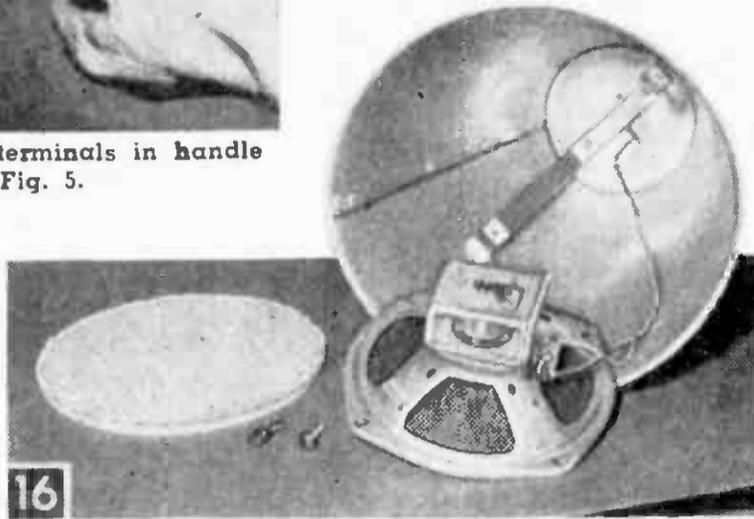But it should be such that the screws used to secure the speaker ring (Fig. 14) will pull the ring down tightly in the taper of the cone, coming to rest with the speaker against the support at two of its mounting holes. Fig. 16 shows the bracket support attached to the wood disc at the base of the cone. Note that the leads have already been soldered to the speaker terminals.




16 Note speaker supporting U-bracket attached to wood disc at far end of horn. Speaker will mount against this bracket and grille cloth-covered wood ring at left will cover front of speaker. Note connected speaker leads going back through wood disc to amplifier.

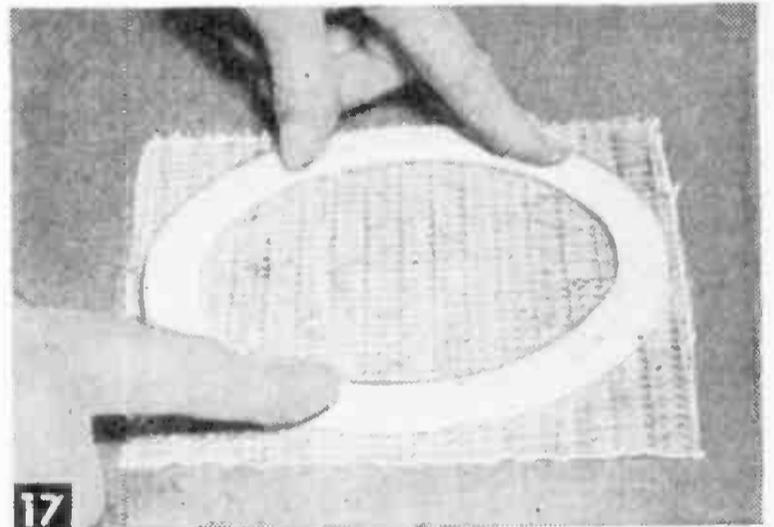
After jigsawing out the plywood ring which fits over the front of the speaker (Fig. 14), cement plastic grille cloth to the ring with Pliobond cement (Fig. 17). After this dries, trim off cloth around the ring with scissors. Make two holes in the ring for the two 8-32 machine screws that turn into the ends of the speaker support in tapped holes.



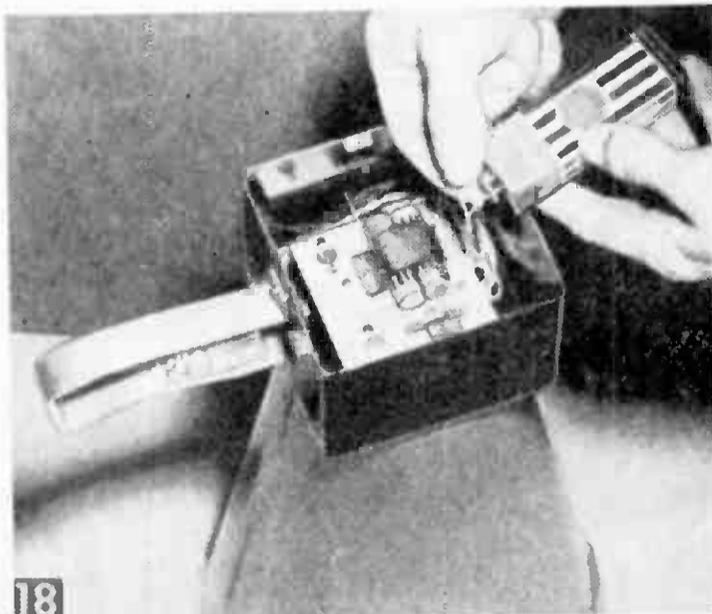17 Pressing plywood ring, coated with Pliobond cement, down firmly onto square of grille cloth.



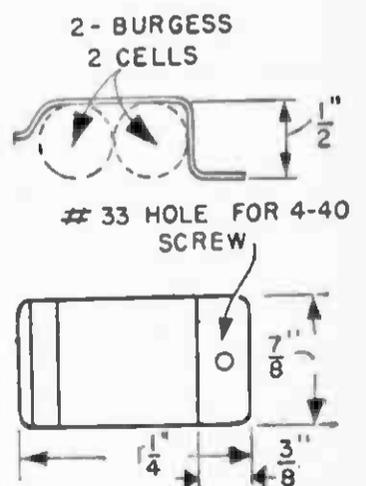18 Installing 22½ volt B-battery in amplifier housing. See Fig. 2A for battery position in housing.




CLIP HOLDER FOR BIAS BATTERY MATERIAL—010" HARD BRASS OR PHOSPHOR BRONZE

You can now connect the 22½ volt battery and place it between the chassis and the housing (Fig. 18) using folded cardboard to wedge it tightly in place. You can also place the transistors in their sockets now.

Mounting the Mike. The microphone mounts in a rubber strip which in turn is cemented into a 1½ in. diameter Bakelite tubing mouthpiece (Fig. 2A, 14A and C, and 19). The mouthpiece then fits tightly in a hole made in the front Bakelite housing cover, using a fly cutter in the drill press. Before installing mike in the mouthpiece tube, connect a 6 in. length of shielded flexible wire to the terminals and a phonoplug to the other end (Fig. 2A and 14C). Make up the strip into which the mike will mount from the type of sponge rubber used to seal car trunks and doors; it is sold in auto supply stores. This rubber should be about ¼ in. thick, ½ in. wide and long enough to be formed around the mike and have its ends meet. Apply Pliobond cement to outside edge of mike and one surface of the rubber. Then, after a few seconds wrap the piece around the mike, tie with string and let dry for about an hour. Then untie string, apply cement to outside surface of rubber, and press the assembly of mike and rubber in mouthpiece tube until about flush with the end (Fig. 20).


Attach the 3-volt bias battery, consisting of two penlight cells in series, to the chassis under a spring clip bent up from thin hard brass or phosphor bronze (Fig. 18A). The leads were soldered to the battery terminals (Fig. 5). To enclose the megaphone handle, make up Bakelite sides as shown in Fig. 11C, and attach to handle frame with screws and Pliobond cement.

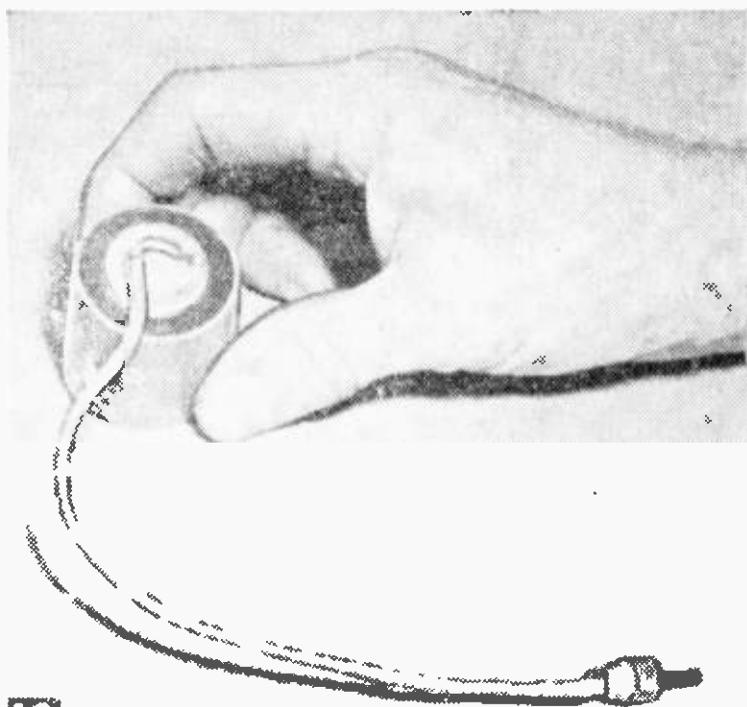Using the Megaphone. If you test the megaphone indoors in a small room, you may find a whistle will develop when you press the push-button and try to talk. This is because sound bounces from walls and enters the microphone to



19

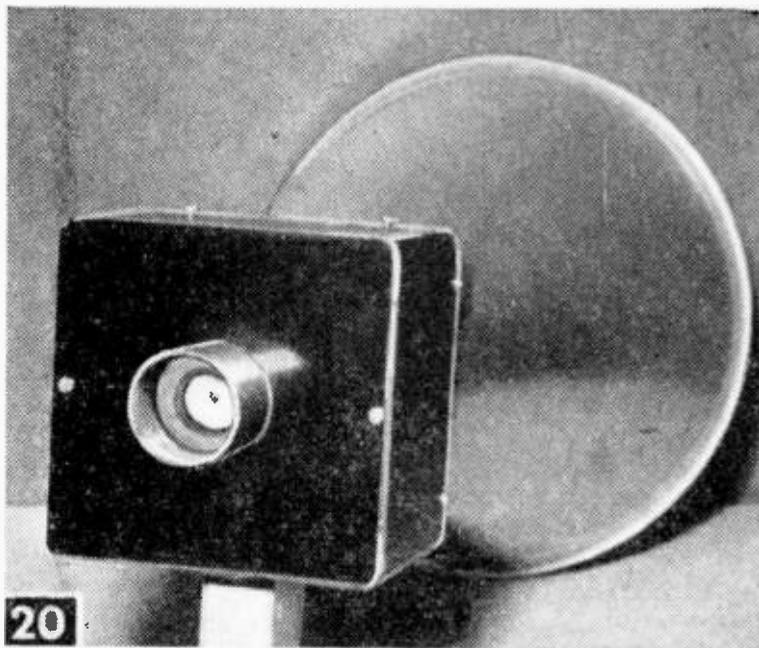Microphone mounted in insulating rubber ring, which in turn is fitted into Bakelite tubing mouthpiece.



Mouthpiece with mike and its rubber ring inserted, mounted to Bakelite panel.

set up a series of oscillations—a common occurrence where a high-gain amplifier, a mike and a speaker are in close proximity to each other. When used outdoors or in large areas, however, this sound has less chance to rebound and there should be little tendency to whistle.

You can use the volume control setting to keep the gain down enough to eliminate whistle when testing indoors. Or, if you want to cut down any tendencies to whistle, line the space inside the cone back of the speaker, and the interior of the box housing the amplifier, with felt. Also cement a piece of felt to the inside surface of the cover. I used a standard dress goods or fabric store type of felt and Permatite Liquid Adhesive R-6229 (from Sears).

For longer battery life, you can place a second XX15 battery in the housing and connect it in parallel with the other one. Simply splice on two leads from the original two battery wires and connect a plug to them, making connections so that the batteries will be plus to plus and minus to minus or parallel. You'll get the same 22½ volts but double the current capacity. The second battery can be taped in place where convenient in the roomy housing.


When using the megaphone, talk close to the mike, even placing the lips directly up to the mouthpiece. This will give maximum volume and also help to prevent stray sounds from entering to cause undesirable oscillations. Avoid taking deep breaths through the mouth while it is close to the mike but rather breathe through the nose. With a little practice, you'll be able to transmit intelligible speech under good atmospheric conditions for distances of 500 to 600 feet, depending on the direction and force of the wind.

Draftsman's Tape Holds Tight

• Draftsman's tape makes an excellent "third hand" to hold electronic components together during assembly or soldering. Due to its high insulation, the tape can be left on permanently, or can be peeled off easily.—J. A. McROBERTS.

Grandpappies of the Call Books

By HOWARD S. PYLE

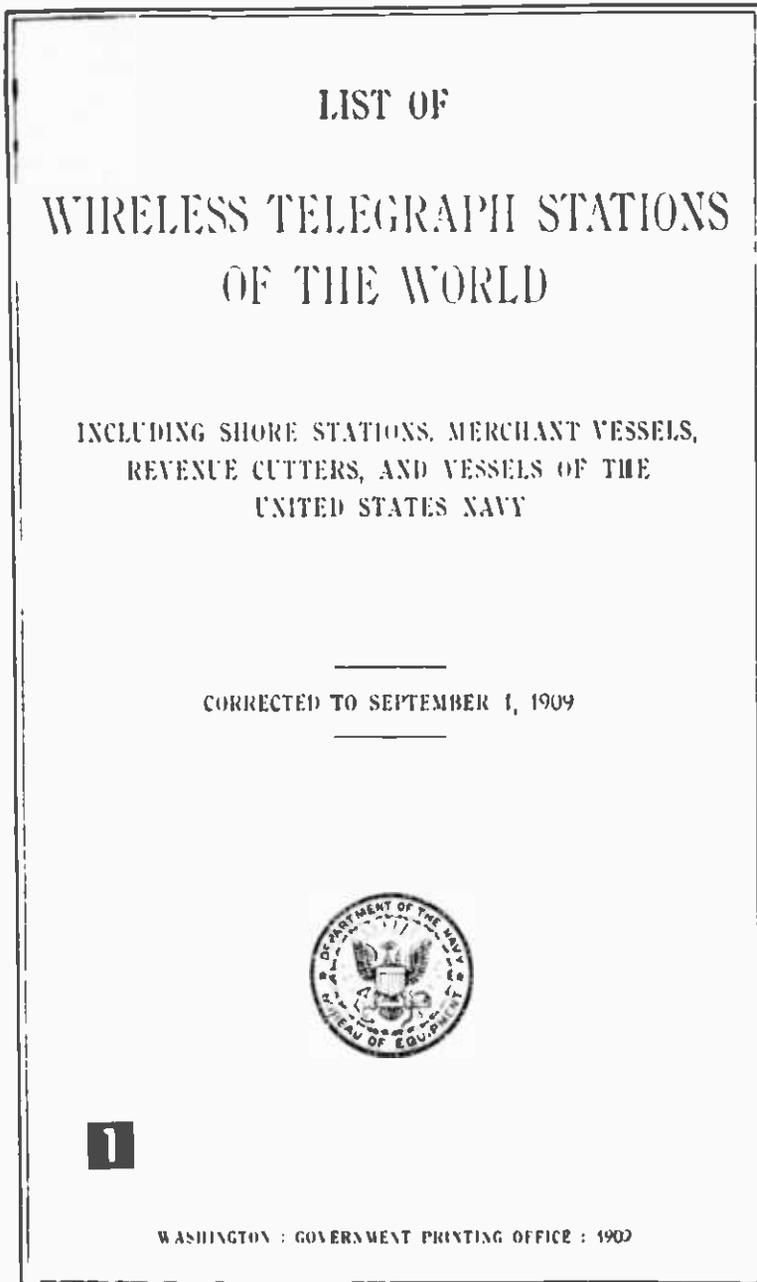

One of the earliest official lists of call letters of merchant vessels and shore stations of the world, as well as naval and other government vessels of the United States.

IMAGINE, if you can, a telephone in your home but no directory—aside from the numbers which you have memorized or jotted down, your phone would be of little value to you. Yet not too long ago this situation existed.

About the time the Spanish-American War ended, Bell's "magic box" was a thrilling novelty. Two hand-cranked long rings brought almost instant response from the widow Sprightly. A short and a long put you in touch with gruff Doc Grouch. The thing caught on.

But it wasn't long before even the keenest memories became confused in attempting to recall what ring for who(m). Scribbled lists were soon replaced by printed pages. And to-

day? Today in any metropolitan center it almost calls for two hands to lift the telephone directory.

When Guglielmo Marconi popularized the use of "wireless" telegraphy, the same problem soon arose. Ships were being rapidly equipped with this new marvel; wireless telegraph stations were being established ashore to provide a link with land.

Early wireless operators kept pencilled notes of the names of various vessels equipped with Marconi's apparatus and the locations of stations ashore. It immediately became evident that the slow and laborious process of calling a ship or land station by spelling out its name in the characters of the Morse code was inadequate; such calls must be shortened. Vessels and wireless stations ashore followed the pattern of the older Morse telegraph lines and adopted two and three letter designations for calling each other.

On the surface it appeared that the problem had been satisfactorily solved, but soon chaos developed. Wireless operating companies discovered that much duplication of these "call letters," as they became known, had developed between the various companies as well as between independent operators. It became immediately apparent that some orderly selection of non-duplicating calls must be adopted and that published lists, similar to telephone directories, must be arranged for.

But individual operating companies were reluctant to absorb the expense of listing call letters and other identifying characteristics of competing interests. Consequently, each operating company published printed lists which included only the ships and shore stations using their system and under their control. A United Wireless Telegraph Co. operator aboard a sea-going vessel could identify only the stations on shore which were also under UWT control. Out of range of a United station, the United operator had no communication with land except perhaps, by the then laborious method of "relaying" through other United equipped ships, if available.

Wireless telegraphy, during its inception and early development years, was primarily a marine communication system. It not only made the sea-lanes safer by enabling a vessel in distress to call for assistance, but it gave the ship-owner an economic advantage in that he had contact with the vessels of his fleet while they were at sea and could divert them to his economic advantage. Very early in the development of wireless signalling it also be-

Wireless Telegraph Call List of the Pacific

NOVEMBER 20, 1913

PRICE 25 CENTS

SOS DISTRESS CALL R I RADIO INSPECTOR, Pacific Coast, San Francisco

DSQ Hiramia	KPD Friday Harbor, Wash.	VDS Rainbow	WRA Henry T. Meutt
DMG Harbor	KPH San Francisco, Cal.	VDE Quadra	WRB Berlin
DMP Harport	KPI Avalon, Cal.	VFA Princess Adelaide	WRD J. H. Metson
DMX Hesperus	KPJ San Pedro, Cal.	VFB Princess Mary	WRP Field
DIP Hesperus	KPK Eureka, Cal.	VFO Princess Beatrice	WRN Harrod
DBR Mecca	KPL Marshfield, Oregon	VFL Princess Alice	WRI Harrod
DBP Memphis	KTM El Segundo	VFE Princess Charlotte	WRJ Arline
DBY Vera	KYD Yacht Cyprus	VFF Princess Victoria	WRK Helena
	KYV Yacht Adventure	VFG Princess Moral	WRM Some City
	KAD Musiris	VFH Princess Mar	WRP Mosko
		VFI Princess Sophia	WRS Santa Clara
			WRT Geo. W. Elder
			WRU Alburn
KNE Kona, T. H.	ROT (Ship)	WPS Pioneer	(P)HU Honolulu, T. H.
KNF Kahuia, T. H.	RPK Petropavlovsk, Siberia	WPO Zepora	(P)IN Phoenix, Arizona
KNH Lihue, T. H.	VAG Point Grey, B. C.	WPI Starr	(P)KE Kansas City, Mo.
KNI Kaulaheo, T. H.	VAD Parkers, B. C.	WPK Columbia	(P)LA Los Angeles, Cal.
KNT Nekeah, Alaska	VAE Estevan, B. C.	WPL Ontario	(P)SF South San Francisco, Cal.
KIT Koko, Alaska	VAF Alert Bay, B. C.	WPM Wallula	(P)SD San Diego, Cal.
KIU Burnett Inlet, Alaska	VAG Triangle Island, B. C.	WPN Joseph Phyllis	(P)SP San Francisco, Cal.
KJA Juchia, Alaska	VAN Dead Tree Point, B. C.	WPP Camie	(P)ST Portland, Oregon
KKA Seattle, Wash.	VAI Ikeda Head, B. C.	WPS Edgar H. Vance	(P)TX El Paso, Texas
KKB Ketchikan, Alaska	VAJ Prince Rupert, B. C.	WPT Speedwell	
KKC Astoria, Oregon	VAR Victoria, B. C.	WPU Yosemite	

2

PUBLISHED BY
AYLSWORTH AGENCIES CO.
149 NEW MONTGOMERY ST., SAN FRANCISCO, CAL.

WESTERN AGENTS FOR
CLAPP EASTHAM CO. RADIO TELEPHONE CO.
C. BRANDES, INC.

This 1913 list contained the call letters and names of ships and shore stations under United States control, as well as the Japanese and Canadian stations both afloat and ashore.

came increasingly apparent to the navies of the world that a strategic military advantage was evident in this method of communication with war vessels. The United States Navy was one of the first to recognize what a tremendous advantage this would be to naval strategy.

With this in mind, the U. S. Navy Department decided to publish a consolidated list of naval vessels and their associated wireless call letters. They felt that the wireless call letters together with the names of merchant vessels which plied the high seas should be included as well, as such ships would probably become auxiliary naval vessels in the event of hostilities. The final result was a complete listing of the wireless communication facilities not only of the U. S. Navy, afloat and ashore, but of all of the sea-going vessels of United States as well as foreign registry, and their companion stations ashore (see Fig. 1).

Such a listing proved of immeasurable benefit not only to U. S. naval vessels and shore stations and the U. S. merchant marine, but to other countries of the world as well whose merchant vessels frequently entered U. S. ports. Other countries rapidly made their publications available to U. S. ship-owners without regard to the particular system of wireless telegraphy employed.

And now, how about the "amateurs" . . . the several hundred experimenters who were enjoying daily the thrill of communication through space without a visible connecting medium? It had become necessary for them too to adopt some brief identification for their equipment. Many of them simply used the initials of their name. Again, "who is who and where are you located?" became an immediate problem. Again a publication of some kind was dictated which contained the answer to both questions.

Recognizing this, Hugo Gernsback, then publisher of *Modern Electrics*, the world's first wireless magazine, published his *Wireless Blue Book* as an adjunct to his *Wireless Association of America*. In this booklet were included the self-chosen call letters of amateur stations.

From the author's records and information from other sources, it appears that Hugo Gernsback's *Blue Books* were the first listing of amateur radio stations to appear in printed form (see Fig. 3).

With the passage of the Radio Act of 1912, control of radio communication in the United States, both amateur and commercial, passed from the Navy Department to the Department of Commerce. As a result, naval and military call letters, although chosen by the Army and Navy, were of necessity co-ordinated with the Commerce Department to insure that they were non-conflicting with other services.

With transfer of jurisdiction over radio services from the Navy Department to the Department of Commerce, it became the responsibility of the Department of Commerce to publish radio call books. These new call books confined the commercial and military listings to United States vessels and shore stations only, and in place of foreign ships and stations they included amateur listings. This was, of course, a boon to the U. S. amateur and, together with issuance of formal licenses to qualified persons, gave the amateur Government recognition (see Fig. 3).

The growth of radio was phenomenal. Installation of equipment on sea-going vessels progressed rapidly. Keeping pace, the number of shore stations with which to communicate with such ships grew by leaps and bounds. Experimenters increased proportionately as this fascinating science caught on.

Soon it became obvious to the Commerce



Left to right, title page of the first formally published call book of amateur wireless telegraph stations, the Department of Commerce list of all radio stations of the United States, and the "Berne-list," in three languages.

Department that to include the names, addresses and call letters of all of the radio services in one publication was impractical. The result was a splitting of the initial call books into two parts, one listing only the commercial and military vessels and shore stations, the other only the amateur class. Such an arrangement served for some time in a satisfactory manner, but with the continued expansion of radio services it soon became a monumental task to compile, revise and publish the call books. Departmental appropriations and staffing were inadequate.

For several years it had been recognized that wireless communication was no longer a local problem. Wireless signals knew no boundaries; vessels of foreign nations habitually sailed in U. S. waters and vice versa. Even shore stations overlapped with their signals between countries. The problem was international.

International Radio Telegraph conferences developed and from them it was determined that publication of an international call book, listing the ships, both naval and commercial, of the world, together with their companion shore stations, was a vital need. A Bureau, agreed on by all nations participating in the conference, was set up in Berne, Switzerland and was charged with the publication of an *International* list of ship and shore stations of the world, both commercial and military. The Berne Bureau discharged its obligation to international agreements, and the annual issues of the Berne Bureau are now of such bulk and contain so many listings that they are published in *three* massive volumes and in three languages (see Fig. 3).

But what about the amateur? Growth of this hobby in the United States alone has reached such phenomenal proportions that it was evident that the Department of Commerce, with its limited facilities and funds, would be unable to continue publication of even the amateur call book for much longer. Radio broadcasting had also entered the picture both in the United States and abroad. They, like the amateur, deserved a separate listing.

In 1924, Charles deWitt White assembled

and published "The Rhode Island Call Book" in Providence, R. I., a compilation of radio broadcast stations in that area. This was shortly followed by a more comprehensive publication which he called "White's Triple List of Radio Broadcast Stations." He soon introduced a number of related publications and they were shortly combined into one which appeared under various titles from time to time. They retained, however, the basic "log" or listing of radio broadcasting stations, both domestic and foreign. Eventually titled "White's Radio Log," this listing was published annually for 34 continuous years. Shortly after White's death his daughter Mrs. W. R. Washburn, disposed of all right in this publication to Science and Mechanics Publishing Company, who were entrusted with continuance of her father's work.

While the excellent listings appearing in "White's Radio Log" adequately cover its field, what about the *amateur* stations? In the fall of 1920, Charles O. Stimpson, himself an active amateur founded the "Citizen's Amateur Call Book." Today the Radio Amateur Call Book, as it has been re-titled is still a quarterly publication. In 1956 an IBM electronic system was installed to speed up the processing of an average of 100 new call letters issued each week.

In 1959 the size of the volume began to approach the bulk of a telephone directory in a large metropolitan city, and it became necessary to split the book into *two* volumes, each of impressive size. The American section, containing over 500 pages, lists some 200,000 U. S. amateur stations. The second section, which lists some 50,000 foreign amateur stations, is issued semi-annually rather than quarterly. The Radio Amateur Call Book remains the only publication in the field listing licensed radio amateurs throughout the world.

A history of the evolution of the call book is a chronological history of the growth of wireless, radio and TV. Without the call letter directories for the various services, radio communication and broadcasting as well as television would be a chaotic groping in the dark.

Transistor Hybrid Parameters

WHEN an experimenter builds a piece of gear, he can play around with component values to his heart's content. If the gadget doesn't work right, he can change the circuit until it does. Not so the professional engineer. If he wants to hold his job, he'd better have a darn good idea of just how the circuit will work long before the fumes of rosin arise.

The best engineer is helpless without adequate performance data for the transistors with which he works, and an effective design method. One of the most effective designing tools is the *equivalent* circuit. When an engineer designs a transistor circuit, he usually forgets about the exact details of the transistor's innards, thinking instead in terms of a simplified device that behaves in the same way. The useful numerical properties of this equivalent circuit are called its *parameters*.

There are a number of possible equivalent circuits from which an engineer may choose

This is symbolized by h_{re} and called, "Reverse Voltage Transfer Ratio."

4) The *current gain* of the transistor, a ratio between input and output signal currents. This is often also called "beta" in the literature, or h_{fe} , as a hybrid parameter.

Why "hybrid" parameters? Well, you'll observe that there are three *different* electrical quantities involved; a resistance, a conductance, and two pure ratios, without units. Hybrid means mixed, the philologists tell us, and these certainly represent a mixture of quantities.


Of what significance are these parameters to the circuits engineer? The first parameter tells the engineer whether he can connect his signal source directly into the transistor, or whether some sort of an impedance-matching or coupling network is necessary. The second tells him much as to the proper load resistor necessary to obtain maximum performance from this particular transistor. For instance, one theoretically gets the best output when

the load resistance is made equal to $\frac{1}{h_{oe}}$. The

third, "reverse voltage ratio," tells the engineer what effect the load circuit will have upon input circuit conditions, and also often whether he may anticipate oscillation troubles in a particular circuit.

The fourth parameter is perhaps the most important of all, for this tells the circuit designer directly how much amplification he may expect in the circuit he contemplates. Will it be sufficient to meet "the specs"? The parameter h_{fe} will tell him. It is actually the "figure of merit" of the transistor.

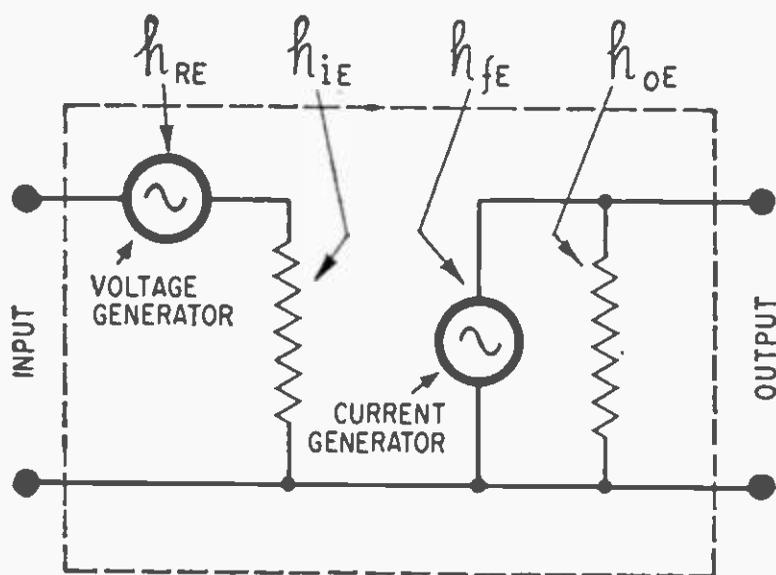Of course, electronics is still an art as well as a science. No human can predict the exact performance of any circuit; a prototype must be built for the final checks. But the parameters will tell the engineer whether the prototype will be worth building, and this is a prediction that can save thousands of dollars.



A EQUIVALENT INTERNAL CIRCUIT OF GROUNDED-EMITTER CONNECTED, JUNCTION TRANSISTOR

but the one shown in Fig. A is one of the most popular.

Obviously the inside of a grounded-emitter connected junction transistor does not look like this, but it acts as if it does.

The important quantitative properties, or parameters of this particular circuit are:

1) The resistance between the input terminals, A and B, as "seen" by the input signal source. This is often called h_{ie} .

2) The internal *conductance*, seen by the output, or load circuit, called h_{oe} .

3) The ratio between the output voltage across the load and the voltage internally fed-back from the output to the input circuit, through interaction within the transistor.

Solution to

Radio Hobbyist


Anagram on

Page 80



Recharger for Dry Batteries

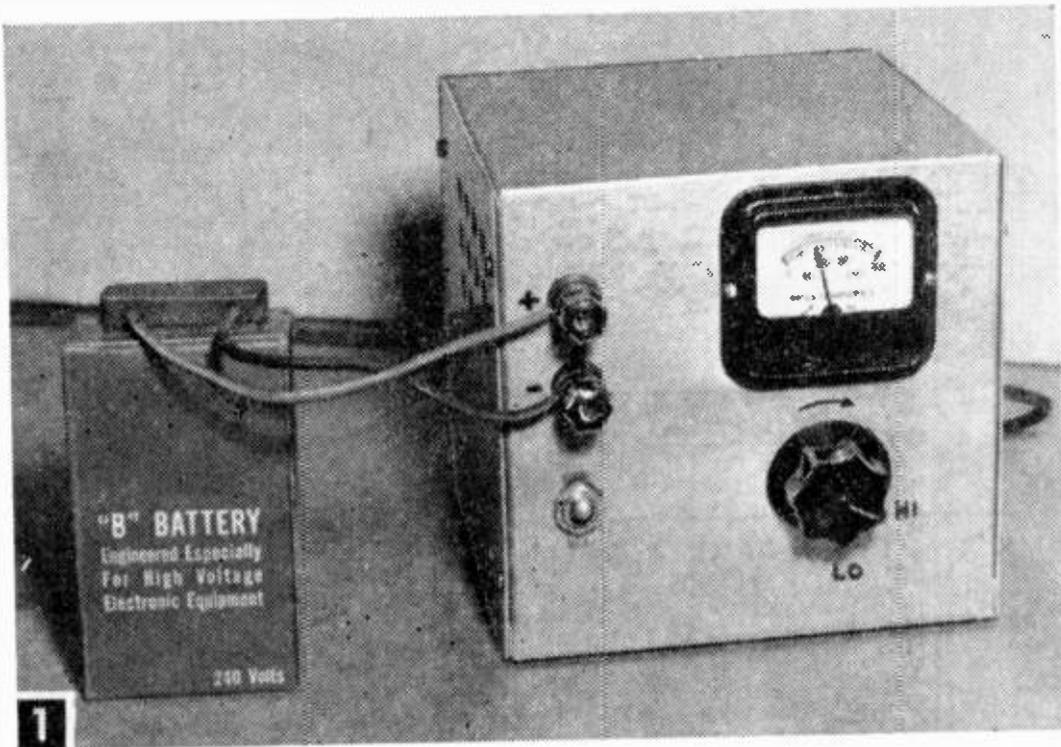Timely booster shots from this quick-charging power unit will renew B-batteries and strobe batteries



In just two minutes, the d-c power supply unit stepped up the charge in this 240-volt photo strobe dry battery from 200 to a steady 230 volts at 100 milliamperes. Connector was adapted to fit battery.

By HAROLD P. STRAND

PROLONGING the useful life of dry cell batteries is not only possible but very practical these days if you have several pieces of battery-powered equipment.

You can revive the expensive, high voltage "B" batteries used in portable radios and industrial laboratories with the 350-400-volt power supply in Fig. 1—if you don't wait too long. In a matter of minutes, this simply-made charging unit will boost the slipping output of the popular 240-volt batteries used in pairs in battery-operated electronic flash outfits and retailing for about \$7.50 each.

The same power supply can also be used for numerous lab test applications where up to 400-volt d-c at 70-90 milliamperes (ma)


may be required.

You can use a healthy 6- or 12-volt storage battery, in place of the power unit, to recharge standard 1½-volt dry cells or other batteries rated at substantially less voltage than that of the source of your charge.


How Long Will the Boost Last? Success of the job depends almost entirely on condition of the batteries when treated. Old units with bulging walls or corroded zinc casings are beyond hope, but many appearing in good shape are simply in a state of partial exhaustion and can be boosted to near-original voltage.

Generation of electrical energy, or a voltage in a primary cell is accomplished by a basic law stating that when two dissimilar materials (such as the two metal elements or metal and carbon in a battery) are placed in an electrolyte or chemical solution, an electro-motive force will be developed.

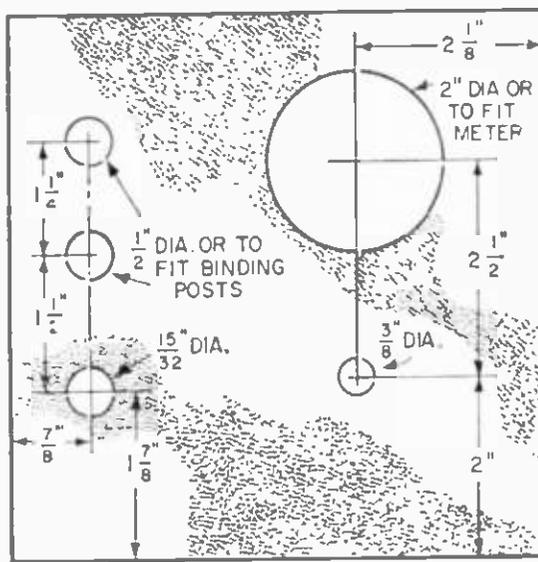
When a battery is delivering current, the chemical reaction in theory, frees hydrogen gas which collects around the carbon rod or positive electrode. Since this gas is an insulator, electrical output is substantially re-



FRONT PANEL LAYOUT

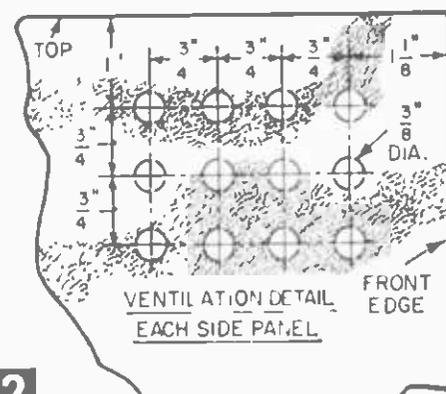

2

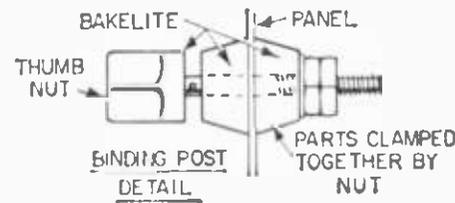


duced as it continues to build up on the rod and increase resistance. To slow down this polarization, the electrolyte paste filler within the battery case includes manganese dioxide, a substance with which hydrogen readily combines. Whenever the battery stands idle after use, some gas is drawn away from the carbon pole by the attraction of the electrolyte. As the resistance declines, the battery gradually recovers its strength. This action continues until the cell has become chemically exhausted, or severely polarized, or both.

In cases where service demands for current cause appreciable voltage drop due to excessive polarization, and chemical decomposition is only minor, you can save the battery by recharging or—more accurately—depolarizing it.



Recharging reverses d-c current flow through the cells to drive the hydrogen off of the carbon electrode and back into the electrolyte mixture. As the internal resistance is lowered, voltage immediately rises and the ability of the depolarizing agent to “take care of it” is resumed.

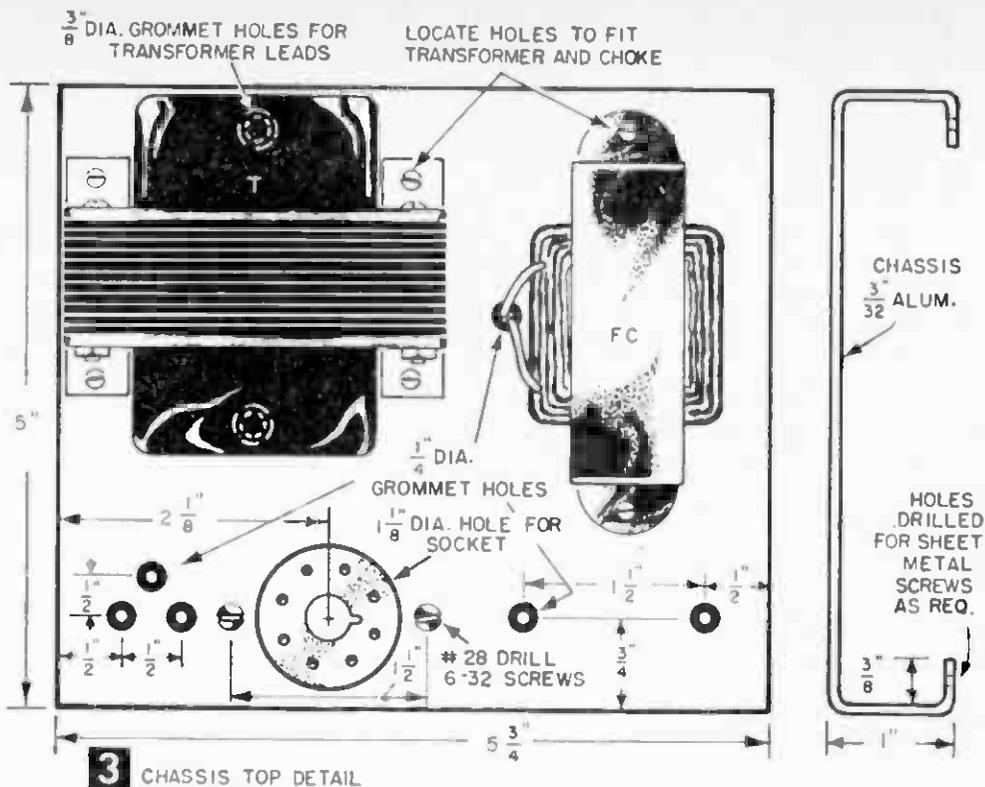In any event, recharging can be repeated as often as




MATERIALS LIST—BATTERY CHARGER

Desig. or No. Req.	Size and Description
C1, C2	8 mfd, 500 v electrolytic capacitors, Cornell #850 (Allied #14L000)
R1	2,500-ohm, 25-watt power rheostat, Ohmite type H-0160 (A #74M334)
R2	150,000-ohm, 1-watt bleeder resistor, IRC GBT-1 (A #1MM020) (optional—see text)
T	700 v at 90 ma power transformer with 5 v 2 amp and 6.3 v 3 amp filament supply, Stancor PC-8409 (A #64G185)
FC	3 hy, 150 ma, 90-ohm filter choke, Stancor C2309 (A #64G457)
M	0-300 scale panel d-c milliammeter, Shurite MT-314
S1, CS2	two terminal chassis strips (A #41H500)
CS3	three-terminal chassis strip (A #41H501)
S	SPST toggle switch, Arrow H&H #20994EW (A #34B195)
1	indicating toggle switch plate for above (A #34B157)
1	black binding post, Superior type DF30BC (A #41H177)
1	red binding post, Superior type DF30RC (A #41H178)
1	6 x 6 x 6" gray hammertone aluminum cabinet, Bud AU1039 (A #88P551)
1 pc	Above items available at Allied Radio, 100 N. Western Ave., Chicago 80, Ill.
V	3/32 x 5 3/4 x 8" sheet aluminum
	5Y3GT rectifier tube
Misc	7' #18 flat rubber or plastic lamp cord, a-c power plug, octal socket, 2 rubber grommets for 3/8" hole, 6 rubber grommets for 1/4" hole, solder, hookup wire

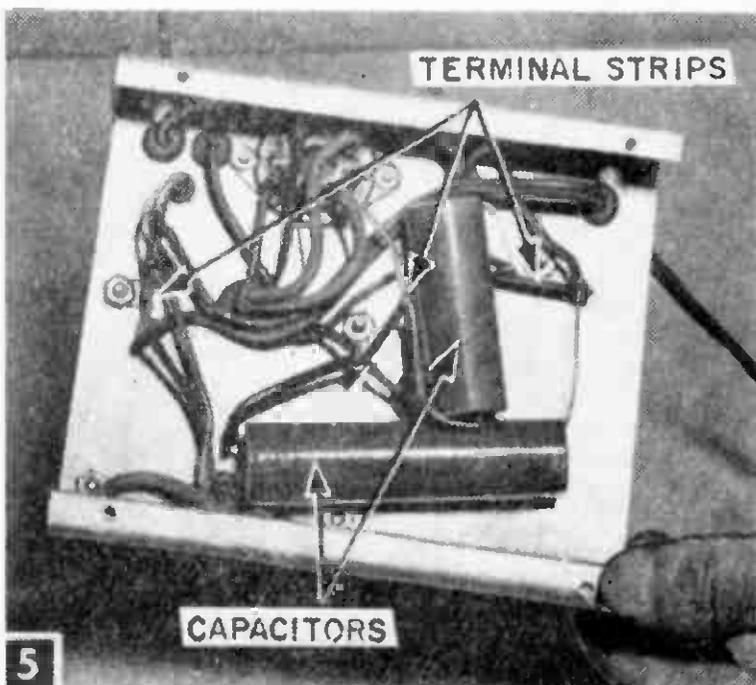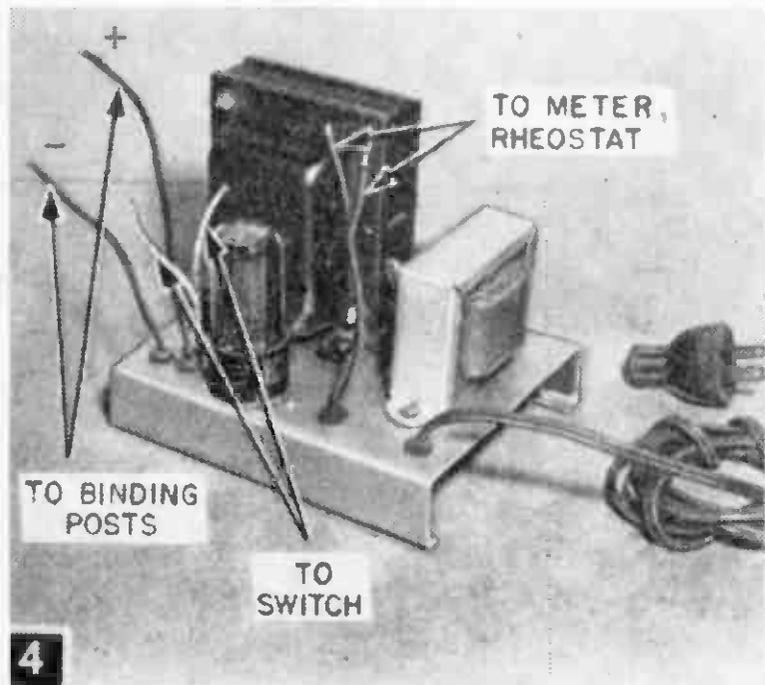

Top view of power supply shows components used. Wires through grommets lead to panel mountings.

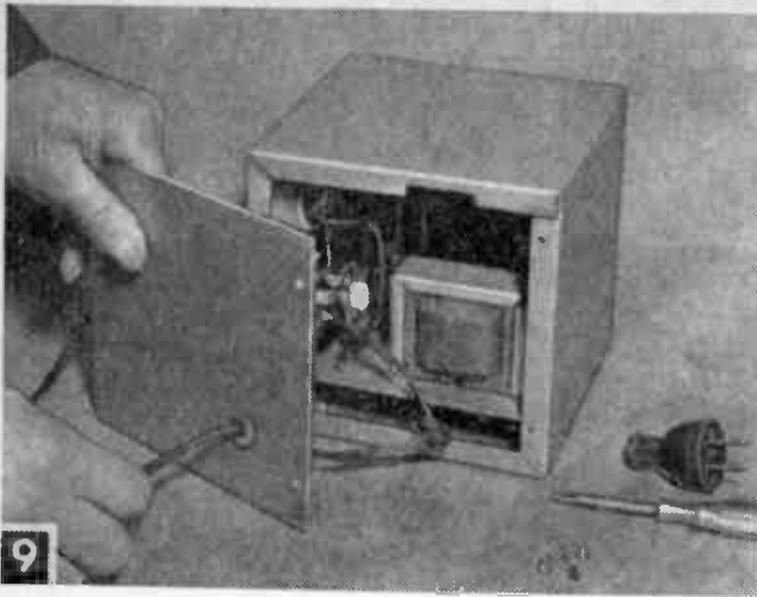All normally grounded leads go to insulated terminal strip at right. No leads should touch chassis.



9 Notch in cabinet to clear transformer will be covered when side panel is attached. Note knot in line cord to prevent any unintentional strain from loosening input connections.

turn on the line switch, the meter should read but a few *ma*. Advance the rheostat towards "HI," cutting out some of the resistance and the *ma* value will rise. If battery is badly exhausted, this reading may be about 50 or 60 *ma* at the start, but in about two minutes 100 *ma* should be indicated with the rheostat further advanced. Turn off the switch and disconnect battery. You can now test it with a high-resistance voltmeter to compare with pre-charging voltage.


Carefully feel the battery during charging. If it seems more than just slightly warm, either discontinue charging or reduce the rate until it has cooled down.

Batteries that are quite well up and only being given a boost will read about 80-90 *ma* at the start and need but a half-minute or so of charging to advance to 100 *ma*.


You can charge B batteries with this unit in similar fashion, but for 45-volt and smaller sizes you will first have to reduce the current to a reasonable level. This can be done without disturbing the unit by mounting another 2,500-ohm, 25-watt variable resistance on a stand and connecting it in series between positive terminals of the unit and the battery.

Remember to test B batteries and photo-flash batteries with a voltmeter only. When we tested the one in Fig. 10, voltage had dropped from a normal 240 to 200. After the two-minute charging period, voltage jumped to 245, then quickly dropped to 240. The next day, it had leveled out to 230 volts. Some batteries may not respond so well if they have one or more cells that have depreciated chemically, and milliammeter readings will vary, too. While it may not be possible to get voltage past 225, even that will allow some extra service.

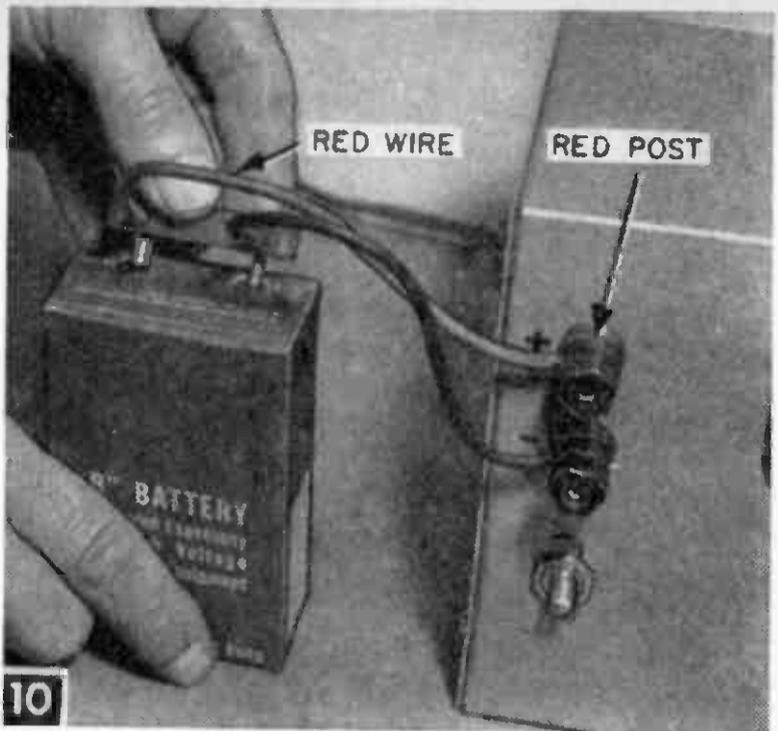Low-Voltage Charging is adequately accomplished with the aid of storage batteries, using the hookup in Fig. 11. To revive 6-volt "hot shot" ignition and electric fence bat-




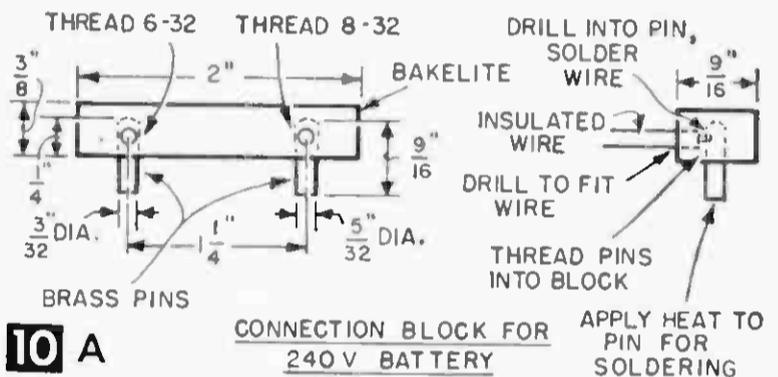10 Difference of pin diameters insures right hookup for high voltage charge. As further safety measure, positive lead has red covering, matching color of positive terminal on panel.



10 A

CONNECTION BLOCK FOR 240 V BATTERY

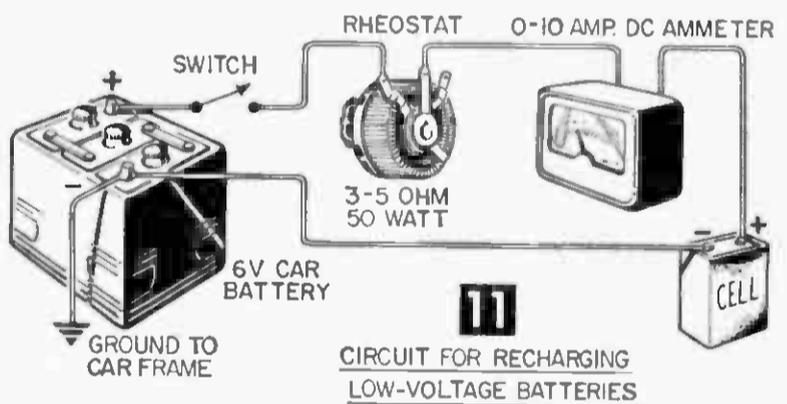

11

CIRCUIT FOR RECHARGING LOW-VOLTAGE BATTERIES

teries, substitute a 12-volt storage battery.

Adjust the rheostat to apply 1 to 3 amperes, since these large batteries can stand such current for a short time without heating. Disconnect after two or three minutes and test momentarily with an 0-25 scale ammeter. Check with a quick touch of the terminals since this meter short circuits the battery and will quickly drain it if left in contact. If less than 15-20 *amps* are indicated, put it back on charge. It may take as long as five or six minutes to bring the battery up sufficiently for good service.

Here's what happened when we charged a well-used #6 dry cell testing 1.4 volts but only 2-3 *amps*! After a minute at 3 *amps*, voltage measured 1.6 and the current was 4½ *amps*. Put back on charge for two more min-

utes, the readings were 1.7 volts and 17 amps, quite satisfactory for such a depleted cell and enough to team up with another recharged cell to ring the door bells again.

Caution: Do not permit the battery to get very warm to the touch. Current tends to heat the cells if its value is too large or charging continues for too long a time. The smaller the battery, the less current should be put through it. Overheating will dry out the electrolyte and build up pressure which may blow out the internal mixture at the sealed end.

Generally, the voltage value used in charging should be nearly twice that rated for the battery, applied through a variable resistance. More voltage may be needed, however, to force a satisfactory current through at the start where the battery is heavily polarized.



To prolong life in batteries, it's a good idea to apply a short charge at frequent intervals to depolarize them and thus keep them in fresher condition. Such a boost may require only a half minute or so—just long enough for the meter to rise up to 100-125 ma. And while voltage will always drop a bit right after the battery is removed from the charger, it should remain substantially higher than before.

After the unit is turned off and before touching the binding posts, be sure to dis-

charge the capacitors by shorting across the posts with a well-insulated screwdriver. If you change connections often, it's a good idea to eliminate this potential shock hazard permanently by connecting a 150,000-ohm, 1-watt bleeder resistor across the output posts just inside the cabinet. With this setup (Fig. 7), the resistor will drain off the charge in a minute or two.

Capacitor Modified for Printed Circuit

• When you need a single-ended capacitor for a printed circuit and none is available, modify a regular double-ended capacitor of the same value to serve the purpose. Bend the lead at one end over, and down the outside of the capacitor housing. If necessary, solder on an extra length of wire to extend the lead. Wrap the capacitor body with electrical tape to avoid any possibility of the bare wire lead accidentally shorting out to other adjacent components. This modification brings both leads out at one end, thus converting the component into a single-ended one, useable in printed circuits.—JOHN A. COMSTOCK.

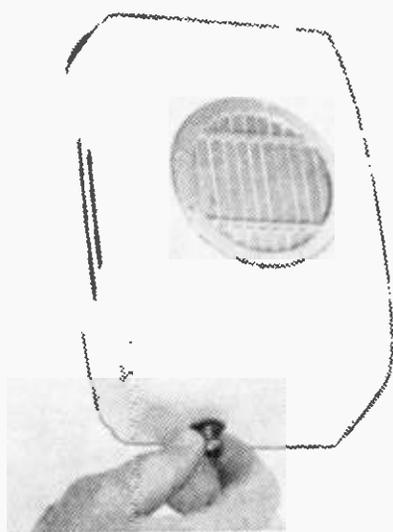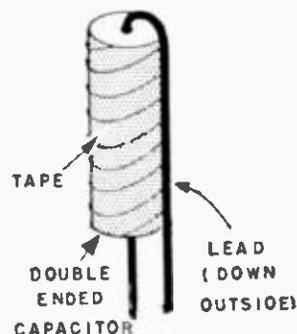


1

Door Bell Silencer

HERE'S a simple way of silencing that door bell so that it won't wake babies taking afternoon naps.

Obtain a small twist switch with threaded shaft and nut for mounting from your hardware store. Remove the cover or housing from your door bell and drill a hole through it large enough to pass the threaded shaft on the switch (Fig. 2). Make sure the switch parts inside the housing won't interfere with the bell mechanism.

Remove the wire coming from the bell

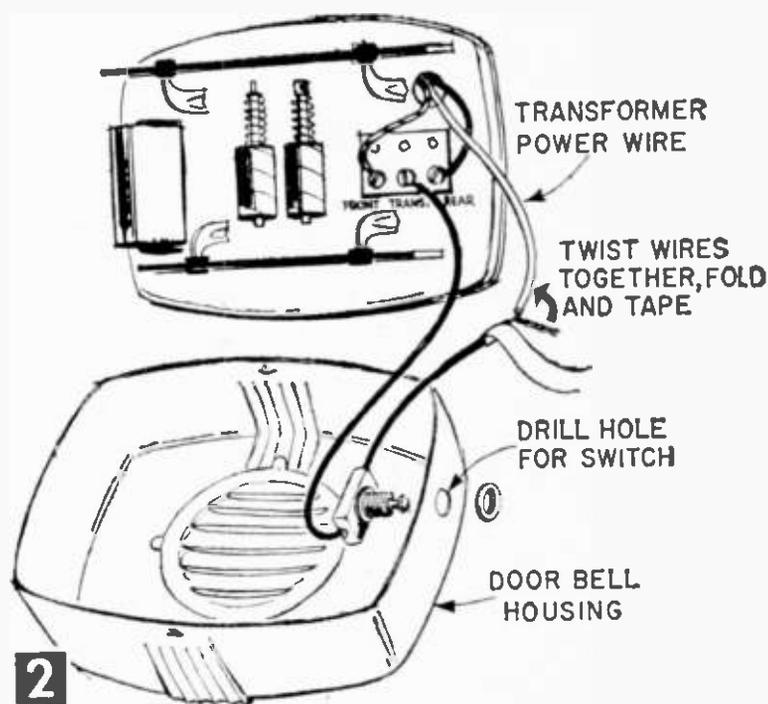


2

transformer from its terminal and connect one of the pigtail wires on the switch to the transformer terminal. Then connect the transformer wire to the other pigtail wire on the switch by twisting them together and taping.

You don't have to turn off the house current for this job—house bell circuits carry only 6 volts.

Replace bell housing, and have someone press door bell button so you will know if the switch is in the "on" or "off" position.

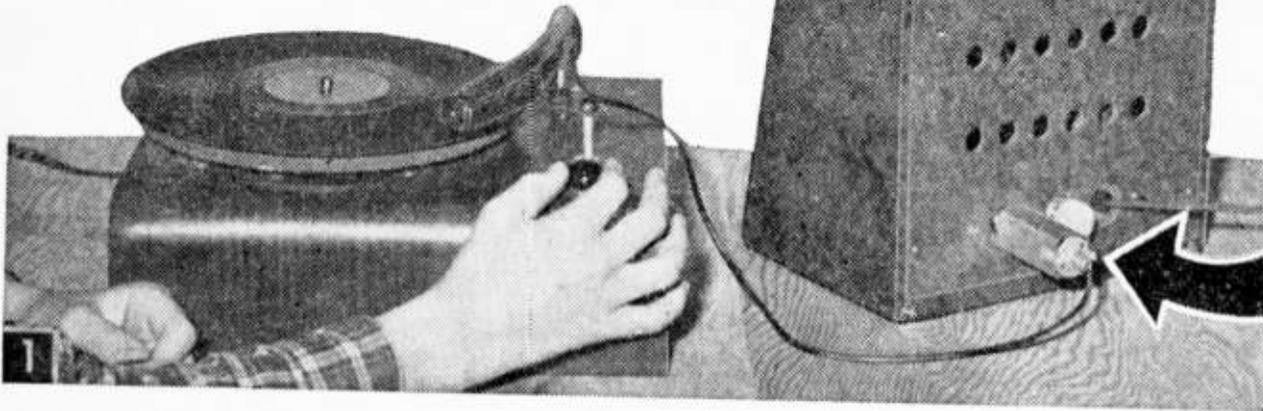A midget IF transformer can (inset) housed the original phono surface noise and scratch filter, but other more common types of tin containers can be used. To use filter, merely plug unit into line between record player and amplifier or radio phono jack.



Noise Filter for Record Playing

RECORDS, both old and new, frequently suffer a common disease—surface noise. Here's a filter that should help to cut down that distracting scratching, so that you can enjoy even those old favorite records made before the advent of electronic recording.


This record filter plugs into the input line of the phono amplifier (Fig. 1) so that in most instances no internal circuit changes are required, either at the record player or amplifier. The original unit was housed in a miniature IF transformer can (Fig. 1A), but any small metal container may be used.

Drill a $\frac{7}{32}$ -in. hole in one end of the can; this hole will be just large enough for you to insert the neck of the ICA-type phono plug shell. Solder the shell to the can. If the housing is made of aluminum, first "tin" the areas around the $\frac{7}{32}$ -in. hole with aluminum solder. You can then solder the shell to the aluminum with regular lead/tin alloy radio solder.


Drill a $\frac{3}{8}$ -in. hole in the opposite end of the can, along with two $\frac{1}{8}$ -in. holes for mounting an ICA-type phono jack. When screwed down with $\frac{1}{4}$ x 4-40 machine screws, the jack shell is automatically grounded to the metal container.

The filter network (Figs. 2 and 3) consists of two 470k (470,000) ohm $\frac{1}{2}$ -watt resistors and two ceramic capacitors with an identical capacity of 100 to 500 *mmf* each. Where surface noise is only slight, use capacitors of 100 *mmf* to 250 *mmf*. For old, scratched discs, use capacitors of about 500 *mmf*. The larger capacitors will somewhat increase the bass response of records, and suppress the highs, but at least you'll be able to hear both bass and treble far better with the annoying surface noise suppressed.

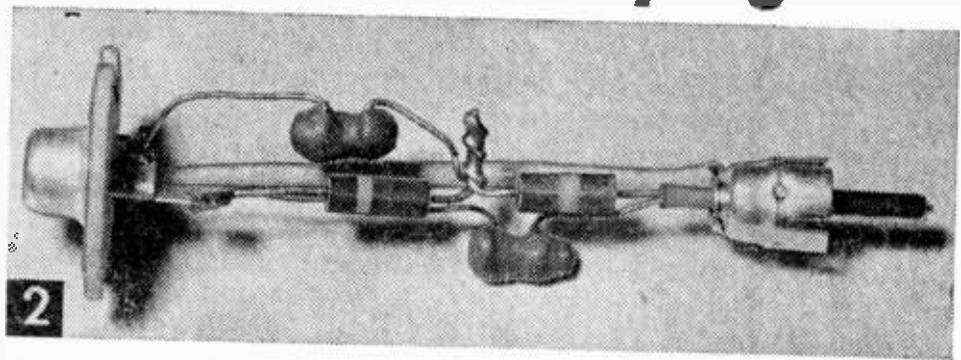If you are very ambitious, substitute a pair of



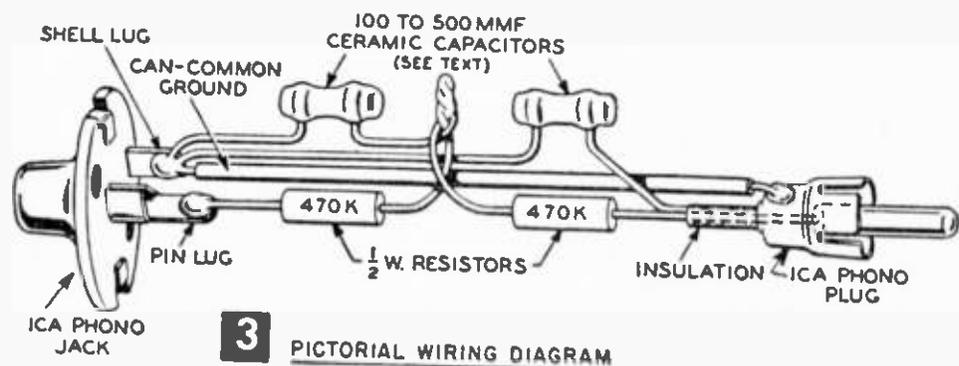The noise filter consists of six inexpensive radio components listed in Fig. 3.



3 PICTORIAL WIRING DIAGRAM

MATERIALS LIST—RECORD NOISE FILTER

- 1 small friction lid can, or IF transformer shell
- 1 ICA type phono plug
- 1 ICA type phono jack
- 2 470k (470,000) ohm, $\frac{1}{2}$ -watt composition resistors
- 2 fixed ceramic capacitors or adjustable trimmers (see text)
- 2 $\frac{1}{4}$ x 4-40 rh machine screws and nuts

adjustable mica trimmer capacitors with a range of about 100-500 *mmf* for the fixed ceramic types. Then with a screwdriver, you can adjust the capacitances to suit the condition of the record.

When wiring up the filter, be sure the resistor and capacitor lead to the phono-plug pin does not accidentally ground to the shell since this would render the phono inoperative. A short length of radio "spaghetti" or other insulation will prevent this.—T. A. BLANCHARD.



Designed primarily for use by the student ham who wants to keep up his code speed, the Student's Special can be modified to receive the standard broadcast band.

SW Receiver

By C. F. ROCKEY

Here's a project for the radio-minded high school or college student, or for the man whose son is such a student—an inexpensive short-wave receiver for the study desk

THIS receiver employs an untuned radio frequency amplifier, a regenerative detector, and an audio amplifier. In addition to increasing the unit's sensitivity, the RF amplifier isolates the detector from the antenna, thus minimizing hand-capacity effects. A voltage regulator tube also makes a big contribution to overall stability. This circuit thus offers the maximum in short-wave receiving satisfaction at minimum cost. And, since a large resistance unit is required to drop the heater voltage, a lamp bulb is used for this purpose, a lamp that normally burns only slightly less brightly than normal and does double duty as a close-in reading lamp. In addition, a sturdy book trough, capable of holding half a dozen textbooks, is included.

Build the receiver unit itself first; then, the book trough and lamp assembly. Begin by lay-

ing out the chassis as shown in Fig. 2. Set the tubes and coil in position in order to assure proper clearance, then drill all small holes with a No. 27 drill, large enough to clear the body of a 6-32 screw. Punch socket holes with a $1\frac{1}{16}$ -in. Greenlee socket punch (available from any large radio supply house).

Next, take the 7 x 10-in. front panel (see Materials List) to your neighborhood sheet-metal shop and have the tinsmith cut exactly 1 in. from it, making it 7 x 9 in. He can do this on his foot-powered shear much more neatly than you can with a hacksaw. If no such facilities are available, however, you'll have to use the saw; this metal is too tough for hand tin shears. Finish the raw edge of the panel with black automobile "touch-up" enamel.

Now lay out and drill holes for the front-panel mountings (Fig. 3). Consult the instructions and template enclosed with the tuning dial when drilling mounting holes for it. Then fasten the sockets, terminal strip and selenium rectifier to the chassis, using 6-32 steel machine screws and hex nuts (buy 1-in. screws, cutting them shorter where too long with diagonal cutters and pliers) and secure to the chassis the insulated tie points for holding the electrolytic filter capacitors. Insert other tie points as the wiring progresses.


Figure 4 gives the schematic for the wiring; Fig. 5, the pictorial. Heater and plate-supply leads can be as long as convenient; you can even group these together cable-like if you wish. Keep these wires close to the chassis, however, in order to avoid hum troubles later.

Keep plate, grid and other signal-carrying leads as short and direct as possible. Except for the electrolytic and large paper capacitors (which should be hung between tie points) the resistors and capacitors can be wired-in directly without other mounting precautions.

Care is the only preventer of wiring errors. Mark over the schematic as wires are inserted; check each stage or circuit as it is completed. Carefully observe polarity on electrolytic capacitor and selenium rectifier connections. Finally, have one of your radio-minded friends recheck the wiring for you, before plugging-in to eliminate those annoying mistakes a person misses when checking his own work.

When you are sure that the under-chassis wiring is complete and correct, mount the variable capacitors, dial, potentiometer and phone jack securely on the panel. Then fasten the chassis and panel together, and complete the wiring.

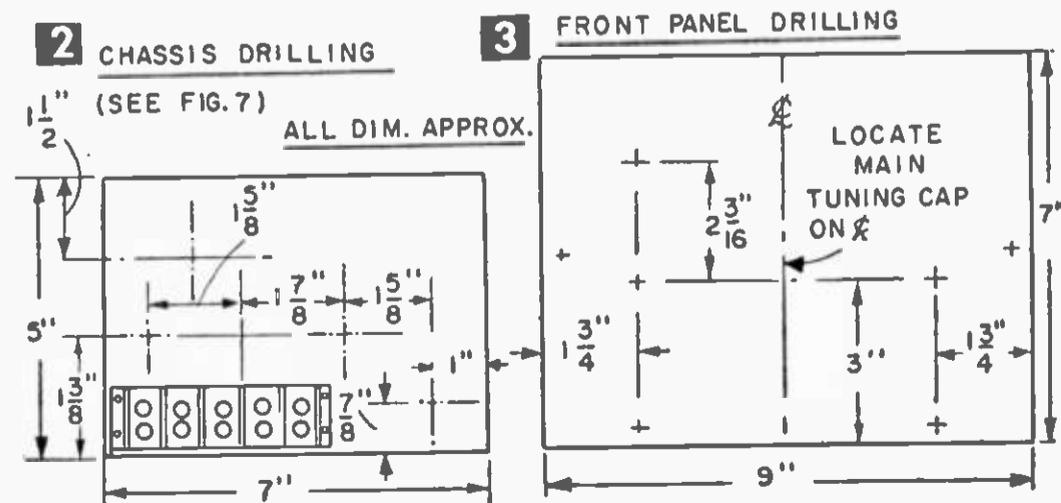
When all wiring has been completed and checked, insert



MATERIALS LIST—SHORT-WAVE RECEIVER

- | No. | Description |
|-----|--|
| 1 | 7 x 10" steel panel (Bud Radio Corp.) |
| 1 | chassis, steel, 1 1/2 x 5 x 7" (Bud Radio Corp.) |
| 1 | terminal strip, 5-terminal barrier type (Allied Radio Corp., catalog no. 41-H-673) |
| 1 | vernier tuning dial, national type BM |
| 2 | knobs, 1/4" shaft |
| 1 | 100 mmf variable band-set capacitor (Bud Radio Corp., type #1855) |
| 1 | 33 mmf variable main tuning capacitor (Bud Radio Corp., type #1852) |
| 1 | 100K linear taper potentiometer, with S.P.S.T. switch |
| 4 | 8-prong (octal) socket, amphenol, type "MIP" |
| 1 | 4-prong socket, amphenol, type "MIP" |
| 1 | single circuit headphone jack (Mallory type 701) |
| 1 | phone plug (Mallory type 75) |
| 1 | selenium rectifier, half-wave, 65 ma (Selectron) |
| 6 | insulated tie-points, 2 insulated lugs
coil forms, 4-prong (I.C.A. type 2158) one for each coil desired |
| 2 | 6SK7 tubes (metal type preferable; "GT" type may be used)
6SG7 tubes may be used instead of 6SK7's if available |
| 1 | 6J5 tube (a 6L5 may be used; metal type preferred) |
| 1 | VR 90 tube (sometimes called OB-3)
wire, screws and solder as required |

- | No. | Description | |
|---|---|------------------|
| Capacitors Required | | |
| | Mica ("postage stamp" type) | |
| 3 | 100 mmf | |
| 5 | 6000 mmf | |
| 1 | 25 mmf | |
| | Paper (200 v. working voltage) | |
| 2 | 0.25 mf tubular | 1 1.0 mf tubular |
| | Electrolytic (150 v. working voltage, tubular type) | |
| 2 | 30 mfd | |
| Resistors Required | | |
| Carbon type (all 1-watt size unless otherwise stated) All values in ohms (K-1000 ohms) | | |
| 2 | 22K | 1 8.2 megohm |
| 2 | 100K | 1 270K |
| 1 | 470 | 1 47K |
| 1 | 100 | 1 5K, 2-watt |
| Wire-wound type: | | |
| 1 | 2K, 10 watt | |
| 1 | 40-watt, Mazda lamp, 110 volt, with socket. | |
| Headphones required: Trimm "dependable," or any other good high-impedance double headset. Crystal phones may be used, but are expensive and not necessary here. | | |
| 1 | line cord and plug | |

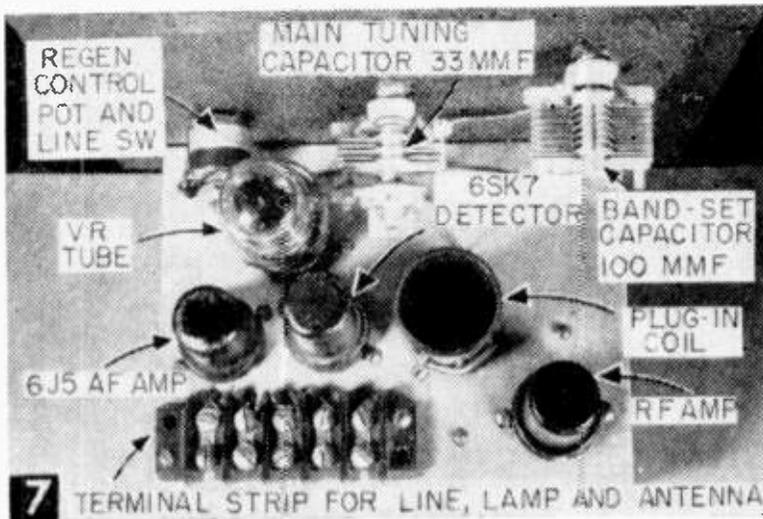

Top of chassis view.

post on the terminal strip. With the potentiometer set just above the oscillation point (slightly on the "hiss" side), rotate the band-set capacitor. Whistling, indicating the presence of signals, should be heard. For best reception of code signals, the potentiometer should be set just on the oscillating point; for voice signals, just below the oscillation point.

The correct technique for tuning-in a voice signal is first to tune for the steady whistle, indicating the presence of the "carrier wave,"


then gradually back down the potentiometer until the whistle just stops. Finally, carefully and slowly readjust the tuning control until the voice or music comes in the best. Much as with playing the violin, a little practice is prerequisite to good results.

The band-set, band-spread tuning system used in this receiver enables you to spread a narrow section of the spectrum, such as an amateur or a short-wave broadcasting band, over the whole dial. When used properly, this vastly improves tuning, and enables you to hear many stations which otherwise would be missed completely.

As designed, this receiver is for use with headphones. This is to avoid barraging a non-radiotic roommate with irritating "noise." However, many strong amateur and short-wave broadcasting stations (the Voice of America, the British Broadcasting stations, and occasionally Russia) come in strong enough to work a small PM speaker when coupled through a plate-to-voice coil output transformer. Stick to the 'phones for regular work, however. You'll hear many more stations with them.

Oh yes, the set is automatically grounded through the power line. Do not use an outside ground (you may blow a line fuse). And, if the hum-level seems high, reverse the plug. If you want to use a doublet antenna instead of the straight wire, connect one side to the antenna terminal and the other to the chassis.

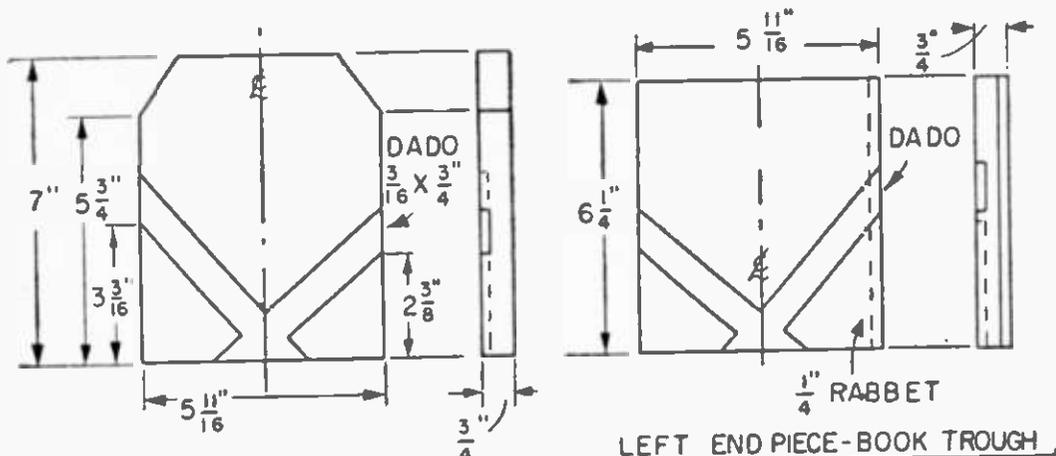Building the Book Trough Unit. Make this unit from clear white pine unless you are equipped for and experienced in working with hard woods. Begin by cutting and dading the book trough end pieces (see Fig. 8). Then make



8 RIGHT END PIECE - BOOK TROUGH (RIGHT END PIECE - RCVR. CABINET)

MATERIALS LIST—BOOK TROUGH

No.	Description
7 linear ft.	$\frac{3}{4}$ x 5 and $1\frac{1}{16}$ " white pine stock, clear
11"	1 x 1" white pine
3'	rubber covered lamp cord
$12\frac{1}{4}$ "	lamp tubing, threaded
1	nut to fit lamp tubing
1	keyless lamp socket
1	clip-on-bulb lamp shade, 8" dia. at bottom
Nails, insulated staples, finishing materials	

the front and back pieces for the book trough (Fig. 9A). If you don't have dadoing equipment, nail the book trough directly to the ends, shortening the back and front pieces by about $\frac{1}{2}$ in. in order to keep the overall proportions correct and omit the panel recess shown in Fig. 9A in the book trough front piece. Sand these parts and assemble, using 3d finishing nails.

Next, make the left-hand receiver cabinet end pieces, and the top piece for the receiver cabinet (Fig. 9B). You can simplify this part of the project by not recessing the cabinet back or by omitting the back entirely if you don't need its dust-proofing protection.

Now cut off 25 in. of the $5\frac{1}{16}$ -in. stock for the base (Fig. 10A), drill the $\frac{1}{2}$ -in. and $\frac{1}{4}$ -in. holes, and groove the bottom for the lamp cord.


Begin the general assembly (Fig. 11) by first nailing the left-hand cabinet end to the baseboard, with its outside edge $\frac{3}{4}$ -in. from the left end of the baseboard. Then nail the left-hand end of the book trough (right-hand end of the cabinet) to the base with its right-hand edge exactly 9 in. from the outside edge of the previously nailed end piece. Then nail down the right-hand end of the book trough.

After the cabinet top has been nailed on, make the lamp stand (Fig. 10B) from an 11-in. piece of 1x1 stock. Carefully drill a $\frac{1}{2}$ -in. hole (lengthwise) through this piece, using a long, electrician's auger bit, or drill halfway from each end with a regular auger bit. Round the corners at the upper end.

From your local electrical supply store get $12\frac{1}{4}$ -in. of lamp tubing (long, threaded steel pipe through which the cord is passed in nearly every table lamp), and a nut to fit. Pass this lamp tubing through the lampstand and through the $\frac{1}{2}$ -in. hole at the right-hand end of the base. Screw the nut on to the bottom of the lamp tubing, thus fastening the lampstand on to the base. Next, screw the shank of a lamp socket on to the upper end of the lamp tubing until it presses firmly on the upper end of the wooden lampstand. Now nail the lampstand to the right-hand end of the book trough. Remove the lamp socket to facilitate finishing the woodworking. Cutting, drilling and installing the back of the cabinet completes the woodwork.

This unit may be finished either by painting or by staining and varnishing.

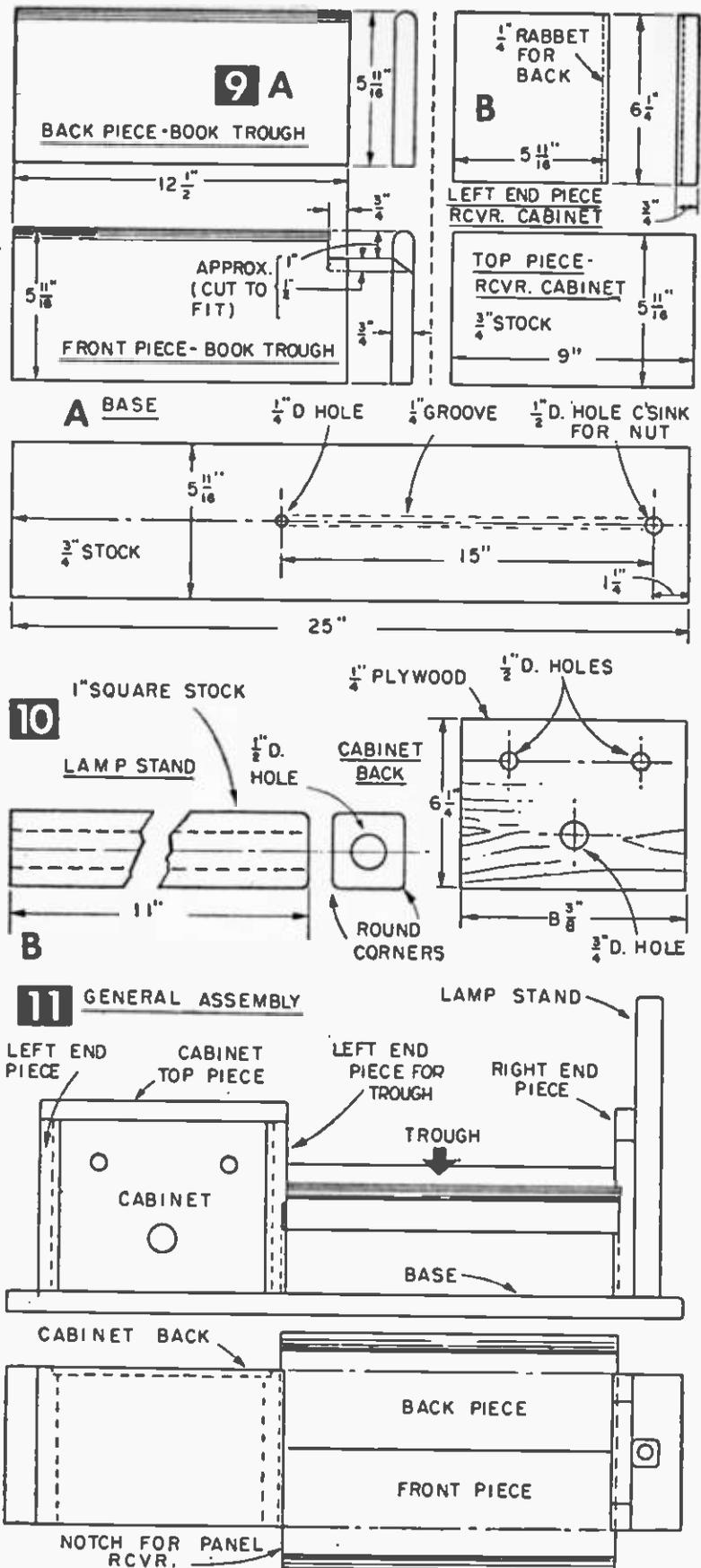When the finish is dry, screw the lamp socket back on the upper end of the lamp tubing, con-




nect about 3 ft. of rubber-covered lamp cord to the socket and assemble after passing the cord down through the lamp tubing to the bottom of the base. Run the lamp cord through the groove and pass it up through the $\frac{1}{4}$ -in. hole into the cabinet.

Fasten the cord into the groove with small insulated staples, at several places, being careful not to pierce the insulation on the lamp cord.

Now make lamp, power line, and antenna connections to the terminal strip on the back of the receiver chassis and fasten the receiver panel to the front of the cabinet. Screw a 40-watt lamp bulb into the lamp socket, put an appropriate shade on this bulb, and your *Student's Special* is complete.

Custom-Making TRANSFORMERS

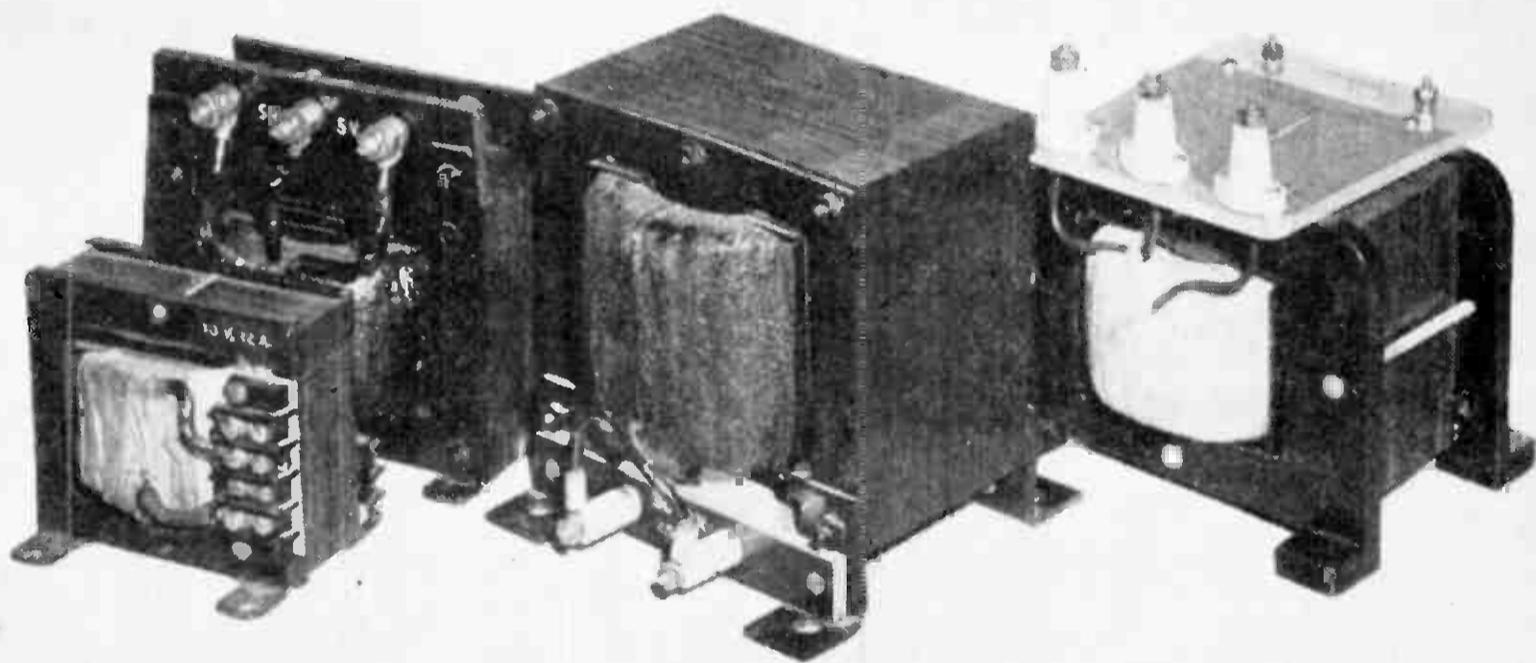

Transformers built using methods described in this two-part article. Left to right: a 10 V 12 amp filament transformer; a 10 V 25 amp filament transformer; a 3000 V 400 ma. plate transformer; a 2000 V 350 ma. transformer for large Tesla coil.

How to make your own special transformers for ham radio, high voltage experiments, welding, plating, and special electronic equipment

By HAROLD P. STRAND


IF YOU need a certain voltage and amperage not available in a stock transformer, you can get exactly what you need by salvaging core metal from a discarded transformer. Then, by winding your own coils, you have a tailor-made job, at a fraction of the cost of having a special transformer made to order.

A transformer consists of a laminated core of special silicon steel (Fig. 2) on which is placed a primary and secondary coil. Depending on design needs, primary and secondary windings can be wound on top of one another as a unit, or placed side by side on the core.


Your first step in design is to decide exactly what transformer output voltage and amperage you need. You determine what size laminated metal core to use, by means of Table A. A formula gives you the wire size and number of turns for the windings. Varnishing, baking and testing completes the job.

Obtaining Laminations. Let's start with the transformer's metal core. We'll assume that you want to get set to make up practically any type of transformer. Usually, large metal stamping companies are not anxious to handle orders for transformer laminations in small lots. But you can pick up old transformers from electrical equipment, radio and TV sets, sometimes for the asking, in repair shops and junk yards. We suggest that you obtain a variety of used or burned out transformers in all sizes.

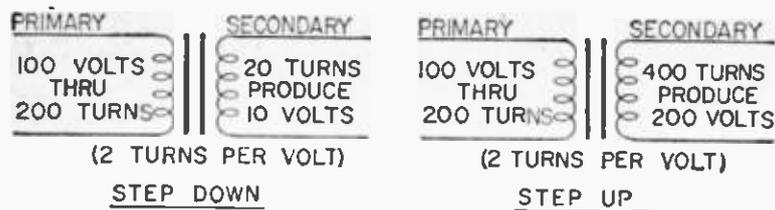Suspend the transformers over an incinerator or steel drum, with wires attached to a 1/2-in. steel rod (Fig. 3). If the transformers have side enclosures, they should be removed before burning, but brackets and clamping parts can be left on. Work away from buildings because the fumes and odor are objectionable. A little fuel oil sprinkled over paper



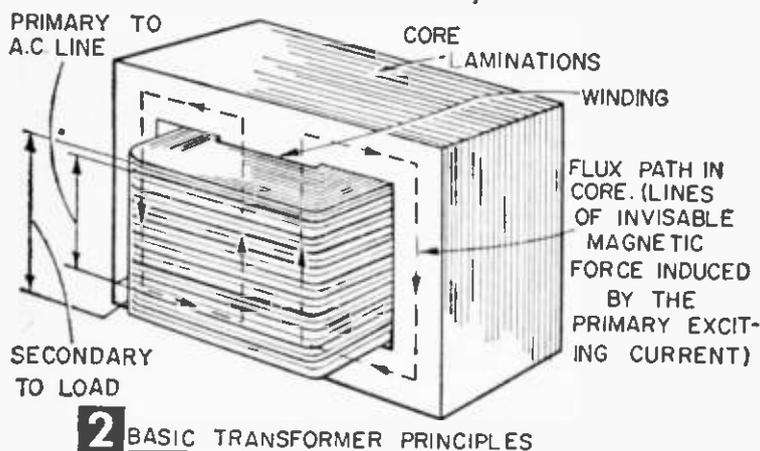(WITHOUT ALLOWANCE FOR LOSSES AND REGULATION)



will get a good fire started. Keep the heat up for a half hour by adding more paper and scrap wood. The heat will burn away all old insulation and wrapping material, but will not harm the laminations. In fact, it will tend to anneal the steel, resulting in lower magnetic losses, an important factor in good quality transformers. Quench the fire with a garden hose, and cool the transformers so they can be handled.

Now you can remove the laminations (Fig. 4). If you have an "E and bar" type transformer, pull alternately from each side. Another kind of core has one-piece laminations (Fig. 5B) with a joint open at one side. Take it apart by carefully lifting the side pieces first. Then pull the laminations alternately from each side, one at a time. Clean the metal with a stiff brush, and wipe clean with cloth.

Planning Core Size is easy. You need a mass of metal in the center big enough to provide an adequate path for the magnetic flux in relation to the volt-ampere rating of the transformer. The window opening must be big enough to take the wound coil. Table A lists transformers from 5 to 500 volt amperes. The core area minimum figures refer to the width of the center leg, times the thickness of the stacking in inches (Fig. 5A). You need not follow the table exactly. A variation of 20% plus or 5% minus is allowable.

Theoretically, the best core would have a square cross-sectional area, for example 1.5 x 1.5-in. In practice, many coils will not fit in such a stack. Your core should not vary from the square more than by a factor of 1.75 for the best designs. For example, it would measure 1-in. by a maximum of 1.75 in. But if a certain required coil size would not fit into such a stacking, you might have to exceed the 1.75 ratio.

This will happen when your coils have un-

TABLE A—TRANSFORMER CORE AREAS
Approximate cross sectional area in inches for Silicon steel transformer laminations.

Output in volt-amperes	25 cycles	50 cycles	60 cycles
5	0.6	0.3	0.25
10	1.0	0.5	0.4
15	1.2	0.6	0.5
20	1.4	0.7	0.6
25	1.8	0.8	0.7
50	2.8	1.4	1.2
75	4.0	2.0	1.8
100*	4.8*	2.4*	2.2*
125	5.2	2.6	2.4
150	5.6	2.8	2.6
200	6.0	3.0	2.8
250	6.8	3.4	3.2
300	7.6	3.8	3.6
350	8.0	4.0	3.8
400	8.4	4.2	4.0
500	9.6	4.8	4.6

* Text example.

usually large numbers of turns, or where large size wire is being used. In such cases, use more stacking or larger laminations and then recalculate the winding with the larger core area; this in turn will result in a smaller coil with less turns. When designing transformers, you may have to recalculate several times with different core dimensions, before you can be certain that the finished coil will fit into the core space.

Window Opening. The second important design factor to consider is the length times the width of one of the rectangular openings in a lamination (Fig. 5A). A good transformer design is thus the best combination of three factors: core size, window opening area, and coil size. Common rectangular cores can be mounted either horizontally or vertically (Fig. 7A, B). In some amplifier circuits where two transformers are to be mounted close together on a chassis, their cores are placed at right angles to each other. This reduces the flux linkage between them to minimize hum and other bad effects.

Building a Transformer. Let's run through a typical design problem and build a transformer. We're making a rectifier unit that runs on 120-ac line voltage. The circuit requires 16.5 volts at 5 amps. So we multiply secondary voltage (16.5) times secondary amperage (5), to get the volt-amp rating (82.5 v.a.), which is equal to watts. This, of course, is provided that the future load of the equipment is non-inductive.

In Table A you will find that the nearest core size is 100 v.a., calling for 2.2-sq. in. core area. This area is an average and we can be under 5% or over 2%. From our stock of salvaged laminations, we select a suitable group with a center leg width of the "E", 1.25-in. Stacking these laminations to 1.75-in. thick, and multiplying the two dimensions, (Fig. 5A) we get 2.18 sq. in. The window opening measures $\frac{5}{8}$ -in. x $1\frac{7}{8}$ -in. or an area of 1.17 sq. in.—the space into which the coil cross section must fit.

Now calculate the coil windings (Fig. 7C).

TABLE B—WIRE SIZES AND TURNS PER SQUARE INCH

Heavy Formvar Diameter (Nominal)	Wire size in B&S Gage	Cross-sectional area (bare) in circular mils	Turns per square inch with average insulation, layer wound
.1055	10	10,380	90
.0942	11	8,226	112
.0842	12	6,529	140
.0753	13	5,184	177
.0673	14	4,109	220
.0602	15	3,260	276
.0538	16	2,580	346
.0482	17	2,052	428
.0431	18	1,624	534
.0386	19	1,289	665
.0346	20	1,024	835
.0310*	21*	812*	1,042*
.0277	22	640	1,310
.0249	23	511	1,600
.0223	24	404	1,980
.0200	25	320	2,470
.0179	26	253	3,090
.0161	27	201.6	3,870
.0145	28	158.8	4,830
.0131	29	127.7	5,920
.0116	30	100	7,430
.0104	31	79.21	9,120
.0094	32	64	10,000
.0084	33	50.41	13,900
.0075	34	39.69	17,700
.0067	35	31.36	22,200
.0060	36	25	27,700

* Text example.

Volt-amperes required (83) are divided by line voltage (120), to get the amperage which must flow through the primary circuit. But since small transformers usually operate at 85% efficiency in transferring electromagnetic energy from primary to secondary, we must add 15% more current to compensate. This totals .79, or .8 amp (with decimal rounded off).


Figuring for constant duty, a value of 1,000 circular mils per ampere is satisfactory. In wire Table B, #21 wire has 812 c.m. area. Therefore you point off three decimal places to the left for the current carrying capacity, .812. For intermittent duty, or if the transformer is to be used only at partial load, one smaller size wire, #22, can be used.

Your next step is to find out how many turns of wire will be required for the primary. The formula is:


$$N = \frac{10^8 \times E}{4.44 \times f \times A \times B_m}$$

N is number of turns, E is counter electromotive force (line volts), 4.44 is a multiplying factor, f is frequency in cycles per second, B_m is maximum flux density in lines per sq. in., A is area of core in sq. in.

B_m (maximum flux density) is the value of the flux or magnetic lines of force set up in the core by the primary exciting current (Fig. 8). If the density is too high, the transformer will heat excessively and waste power. Various values are selected by a designer according to the use. In some electronic transformers it may be as low as 20,000; in some cases a density of 80,000 has been used, especially for intermittent duty. A value of 60,000 lines is a good average for

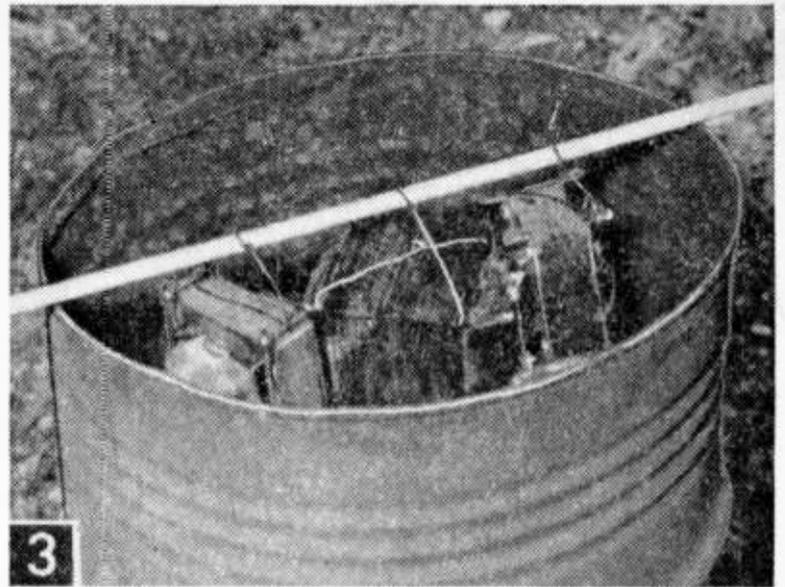

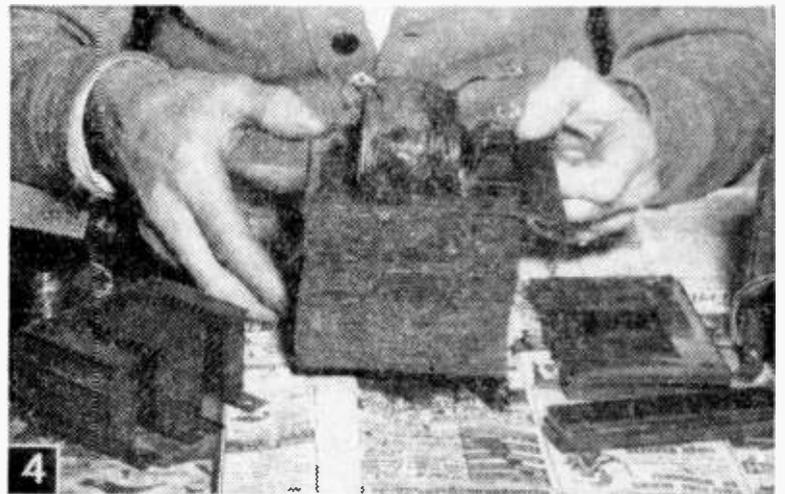Burning a half hour will loosen the insulation and wrappings so that core laminations can easily be removed.





The heat has reduced the insulated wire to bare copper and laminations that are easily pulled out.

small power transformers.


$$\text{Thus turns} = \frac{100,000,000 \times 120}{4.44 \times 60 \times 2.18 \times 60,000} = 344$$

We now have the primary winding calculated as having 344 turns of #21 wire which would operate with little temperature rise.

Now figure the turns-per-volt in the primary to determine how many turns will be required in the secondary. Divide primary turns (344) by line voltage (120), which is 2.87 turns per volt. As 16.5 secondary volts are required, multiply by 2.87, resulting in 47.3 turns. There will be some iron and copper losses, however, which average about 4%, and there will also be a normal voltage drop when the load is added so, if we want the stated voltage at full load, about 2% more turns must be added—or a total of 6% additional turns. The exact values of losses and regulation (the % difference between no load voltage and full load voltage) are difficult to estimate in advance. In commercial applications where the voltage under load must be exact, it is often necessary to construct a second pilot model after tests on the first one show more or less is involved in the loss and regulation factors. In our case the

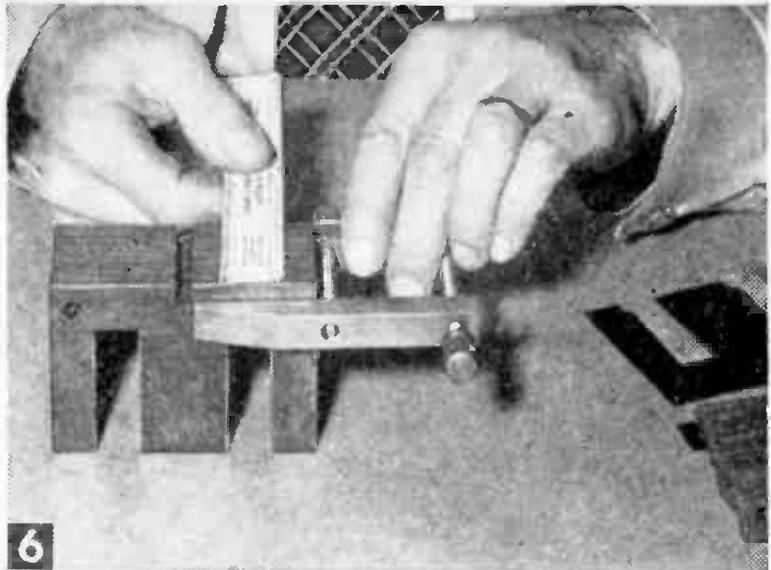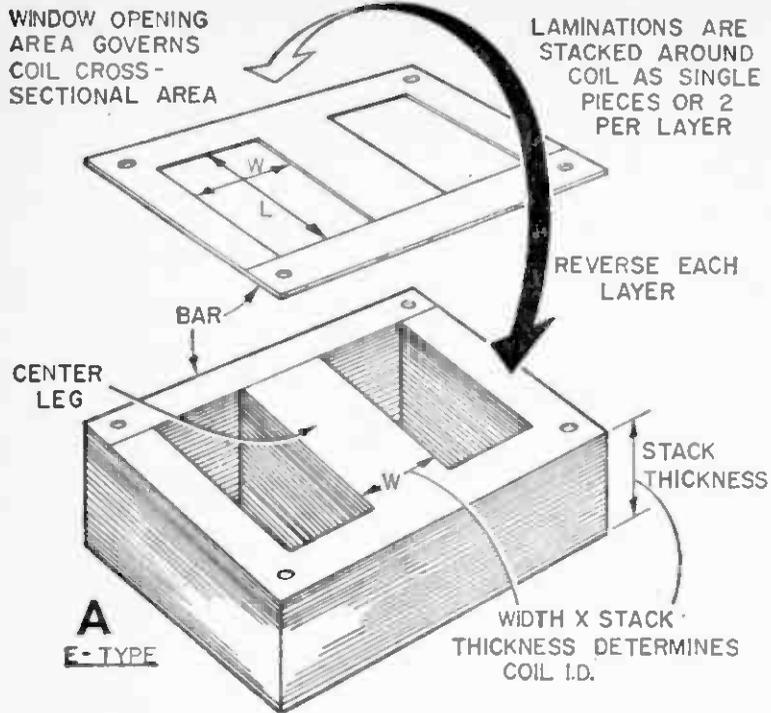

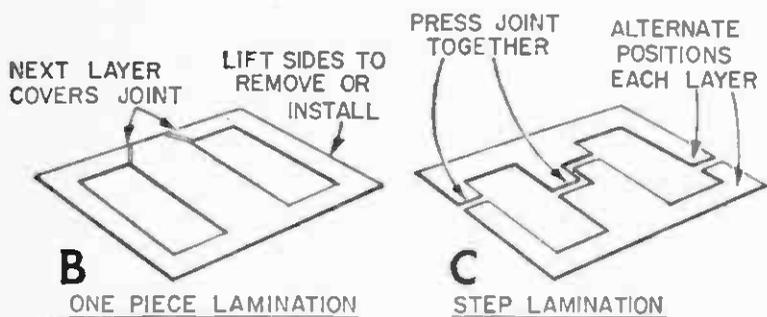Clamp the stack of transformer laminations tightly together when you measure thickness. The thickness x the center leg width is the cross sectional area of core.



5 PUNCHED TRANSFORMER LAMINATIONS

STACKED LAMINATIONS ARE #26-#29 GAGE, SILICON TRANSFORMER STEEL. FOR 60-400 CYCLES, USE #29 GAGE TO LOWER LOSSES. (#29 MAY BE USED ON LOWER FREQUENCIES)



voltage is not too critical, so the addition of 6% is sufficient in the calculated turns, making 50.1 (50) turns for the secondary winding. This winding will be tapped at 25 turns.

The wire size of this winding is the next consideration. The transformer winding is to carry a current of 5 amperes. Table "B" lists #13 wire with 5184 circular mils, or as having 5.184 amp capacity at 1000 circular mils per amp. Since this is heavy wire to wind, use two wires wound on together, three sizes smaller, or #16, which will have the same


area and be easier to wind. (For intermittent duty, you could use one #15 wire.) Formvar magnet wire is recommended for its tough enamel insulation and minimum required space.

The final problem is to estimate the size of the finished coil to make sure it will fit in the lamination window openings (Fig. 7C). To do this, refer to Table "B" in the "turns per sq. in." column. We are using 344 turns of #21, so divide 344 by 1042, resulting in .33. Figure the 50 turns of double #16 singly first, then the result doubled: 50 divided by 344 is .14 times 2 equals .28. Add this to .33 for a total of .61. To this must be added a figure which represents the approximate space taken by the insulation between primary and secondary, between secondary turns if any, and out-

7 SMALL TRANSFORMER DESIGN

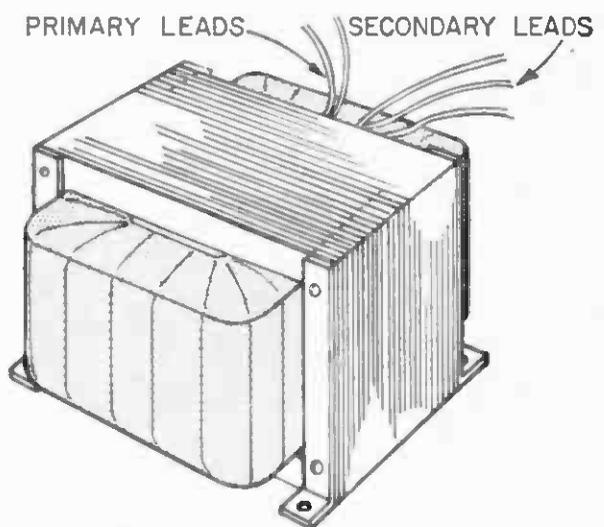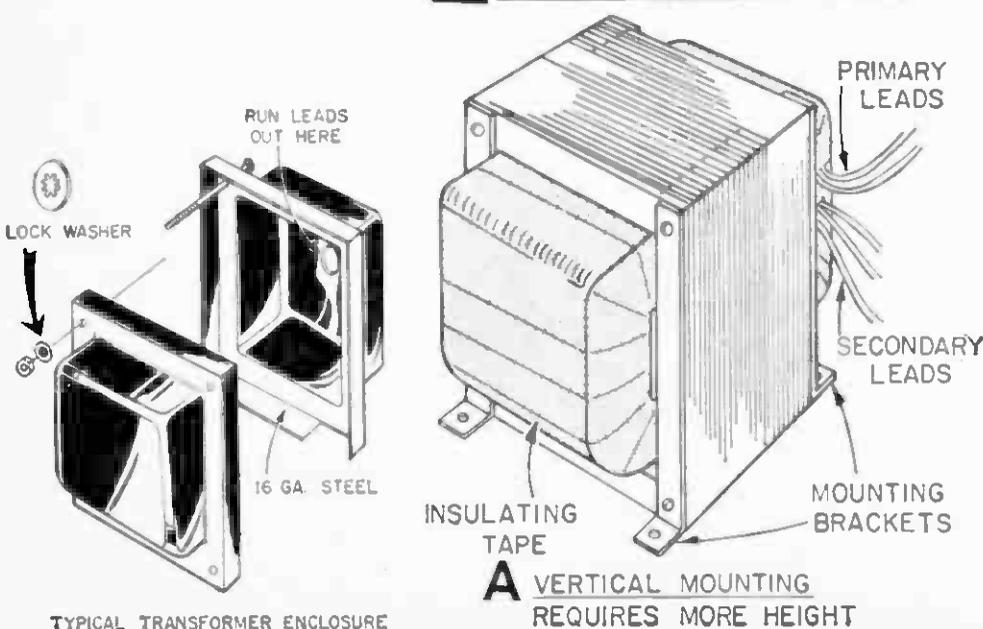


TYPICAL TRANSFORMER ENCLOSURE

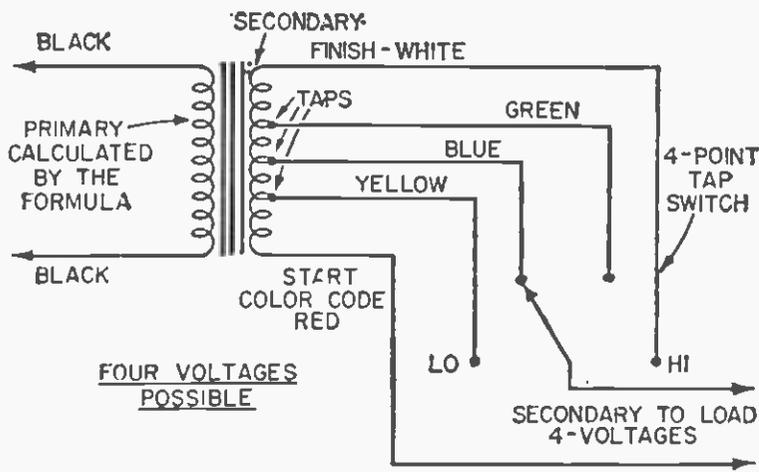

A TAPPED SECONDARY WINDING

FIGURE EACH TAP FOR A SINGLE VOLTAGE
 TURNS = DESIRED VOLTS X TURNS PER VOLT
 RATIO - 6% FOR LOSSES. (SEE TEXT)

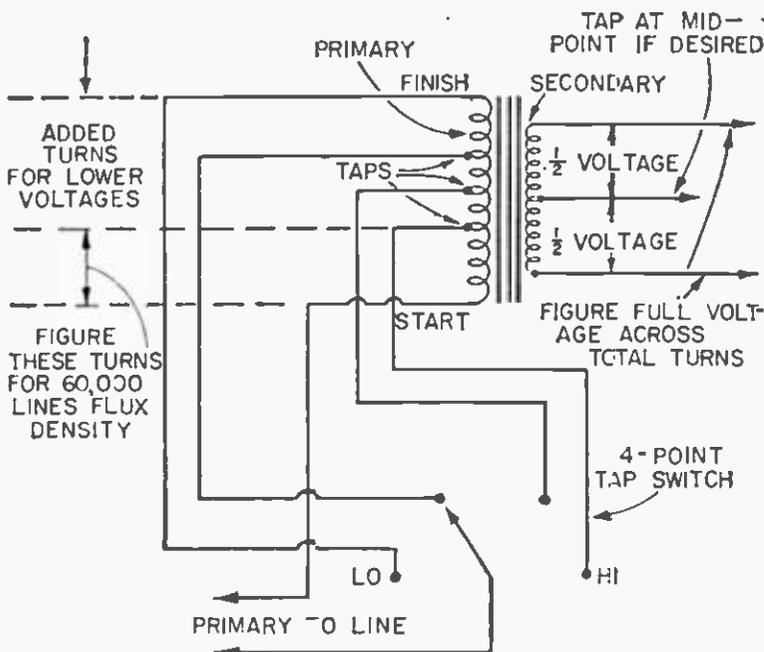

B TAPPED PRIMARY WINDING

FIRST CALCULATE PRIMARY AND SECONDARY FOR HIGHEST VOLTAGE. THEN ADD TURNS TO PRIMARY FOR LOWER VOLTAGES

8 VARIABLE VOLTAGE TAPS.

side taping of coil. Another factor is that the turns may not be wound in flat layers, but may be "random" wound, which is easier for the amateur. This type of winding, while satisfactory, takes up more space. Therefore, an estimate of 25% must be added to the figures previously obtained as the probable total space required for the finished coil. This totals .76 sq. in. As the window opening in the core ($\frac{5}{8} \times 1\frac{1}{8}$ in) is 1.17 sq. in., the coil should fit in place if it is neatly and tightly wound.

Transformer designs which must be quite exact, usually include a stacking factor for the core, since a stack of laminations 2-in. high does not necessarily have the same area as 2-in. of solid steel. Therefore, .9, another multiplier, is added to the row of figures below the line in the formula. For practical purposes, however, this figure can be omitted in most cases.

A transformer is often needed which has

several output voltages, obtained with a multi-point switch or so-called tap switch. There are two ways of doing this. You can design the secondary winding with taps at the turns to deliver the desired voltages, each of which can be calculated by the methods already described, and bring out leads at these points (Fig. 8). Or the primary winding can be tapped. This is especially desirable when the size wire in the secondary is large and it is impossible to make taps there without adding considerable bulk. To tap the primary, first calculate the primary winding by the method described for single-voltage transformers.

Then, figure the number of turns for the secondary for the *highest* voltage required, using the primary turn-per-volt ratio as the multiplier plus the added percentage for losses and regulation. This will establish the number of secondary turns. In order to get several lower voltages, more turns must be added to the primary with taps at each of the points to be determined.


Supposing that we wish to have 24, 18, 12 and 10 volts through the use of a tap switch on the primary. A particular transformer with a certain core, for example, is figured to require 350 primary turns for a 60,000 flux density.

Dividing this by the line voltage (120), we get a turn-per-volt ratio of 2.9. Multiplying this by the highest secondary voltage (24), the turns for the secondary—with 6% added for losses and regulation—will be 73.77 (74) turns. Eighteen volts will be the next objective, so 70 is divided by 18 which is 4.1. Multiply this by line voltage (120) and the result is 492 primary turns as the next tapping point.

Repeat this procedure for each secondary voltage and the last figure obtained will be the total primary turns required, with the point for each tap indicated.

With so many primary turns, the coil when wound will be comparatively large, so careful selection of the laminations must be considered to provide a suitable space for the coil. When the transformer is operating on the tap which produces the highest secondary voltage (24), the flux density in the core will be at its highest—60,000 lines.

The taps which cut in *more* primary turns will *reduce* the secondary voltage and the exciting current and hence the flux, so the transformer will not be in danger of overheating on any of the taps. If you tapped the basic 350 turns in an attempt to get variable secondary voltage, the result would be an increase in flux density for each tap used, and the flux density would reach a point where the core would overheat, and the line current become excessive.

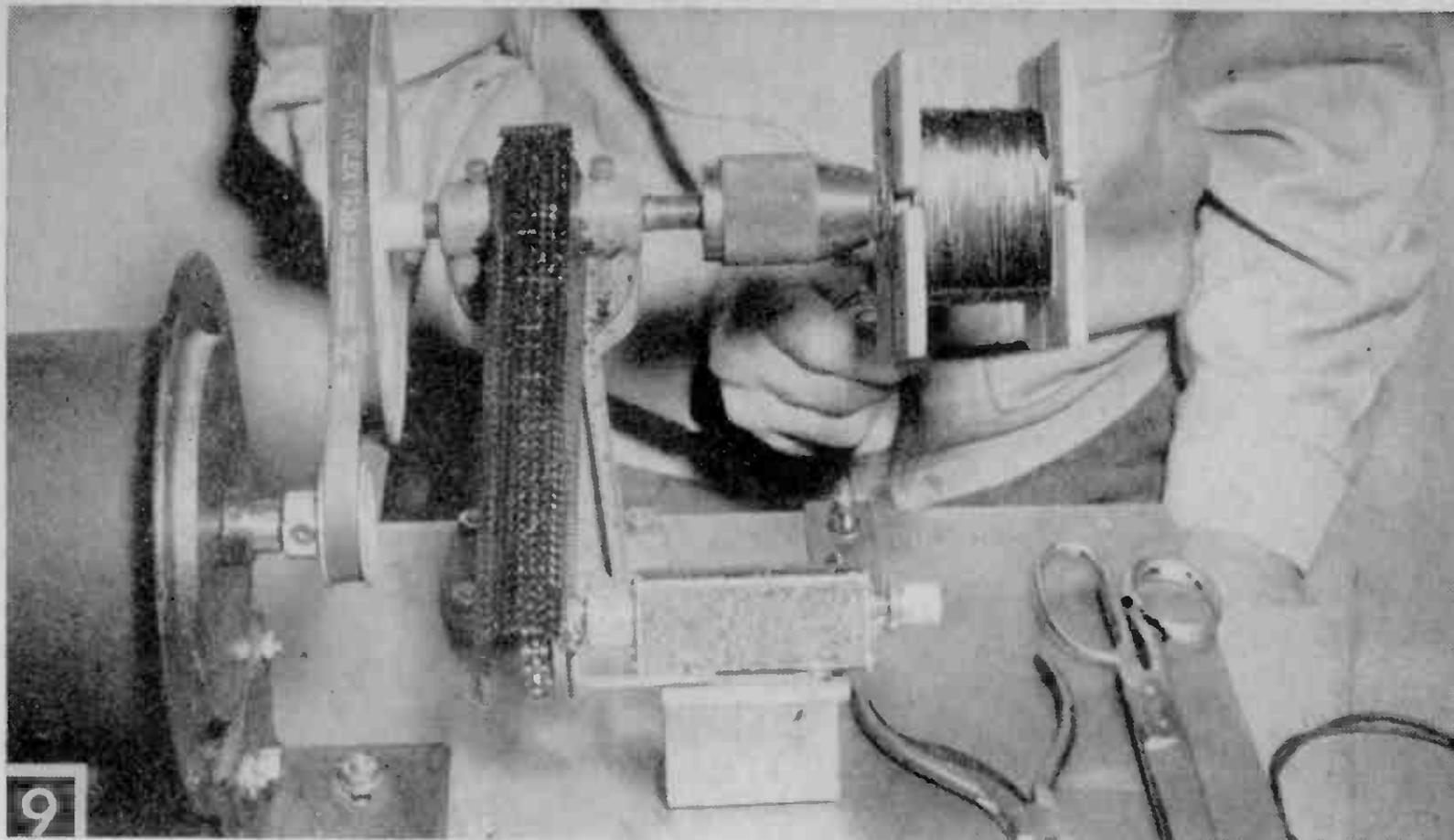

This homemade machine makes transformer and coil winding easy. Speed is controlled by a foot pedal.

We have described the steps in designing cores and coils for making your own special transformers for rectifiers, plating, ham radio as well as high voltage and electronic experiments.


Laminations were salvaged from discarded transformers, and complete calculations were shown for designing a special rectifier transformer which is to step down 120 line voltage to 16.5 volts at 5 amperes. The continuous duty primary coil was calculated to require 344 turns of #21 Formvar magnet wire; the secondary winding requires 50 turns of two #16 Formvar magnet wires wound together in parallel, with a center tap at the 25th turn. The basic procedure which follows can be used to wind any kind of similar transformer.

Start by making the winding form (Fig. 9) with a center block cut slightly larger than the core center of your transformer laminations. The grooves and the slots in the coil form (Fig. 10) are used for temporarily binding completed turns of wire with cord. Sand the wood smooth, slightly rounding the corners, and then coat with shellac. When dry, sand lightly and apply paste wax to make it easy to remove the coil after winding.

The home-made machine (Fig. 9) includes a variable-speed foot pedal which controls a vacuum cleaner motor. If you plan to make a number of transformers, or coils, you will save time by building an electrical coil winding machine (such as the one shown in Craftprint 265, \$1). Otherwise, you can chuck the winding form in a lathe that has slow speeds, or rig up a hand crank. For any winding method, you need a positive way to


count turns, such as a mechanical counter tied in with sprockets and chain.

To insulate the coil from the laminations first place a turn of lapped .007 Duro insulating paper around the form. Fit the paper tightly with $\frac{1}{16}$ -in. brought up on all sides (Fig. 12). Secure with a strip of Scotch masking tape. Then slip a length of spaghetti tubing over the end of your #21 Formvar magnet wire, for the starting lead of the primary. Allow at least a foot of this wire and bring the spaghetti in through a side slot into the coil form about $\frac{1}{4}$ -in. Secure the end of the

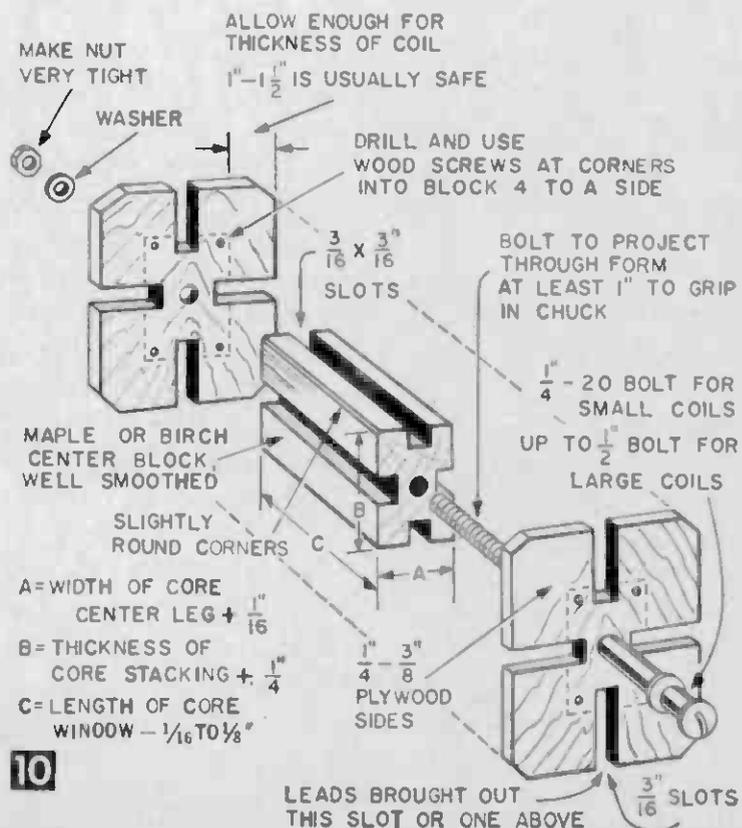


wire by taking a few turns around the bolt on the chuck side of the form. Set your counter at zero and wind back and forth as evenly as possible to avoid unnecessary wire crossings. When the counter reads 344, cut about a foot beyond the last turn, slip on spaghetti tubing, and bring the lead out through the same slot used at the start. Again, secure the lead with paper Scotch tape and a few turns taken around the bolt.


Start the secondary winding with a turn of .007 Duro insulating paper placed over the primary. Follow the same procedure as before (Fig. 11). But after you slip the spaghetti tubing over the lead of your pair of #16 secondary wires, run them through the opposite slot on the coil winding form. Set counter to zero and wind 25 turns, flat and even because your space in the laminations is limited. After the 25th turn, use tape around the turns to temporarily hold them in place. Scrape $\frac{5}{8}$ -in. insulation from both wire ends and solder on a flexible #16 insulated lead (Fig. 13). Insulate with a folded piece of the .007 Duro paper and secure with paper

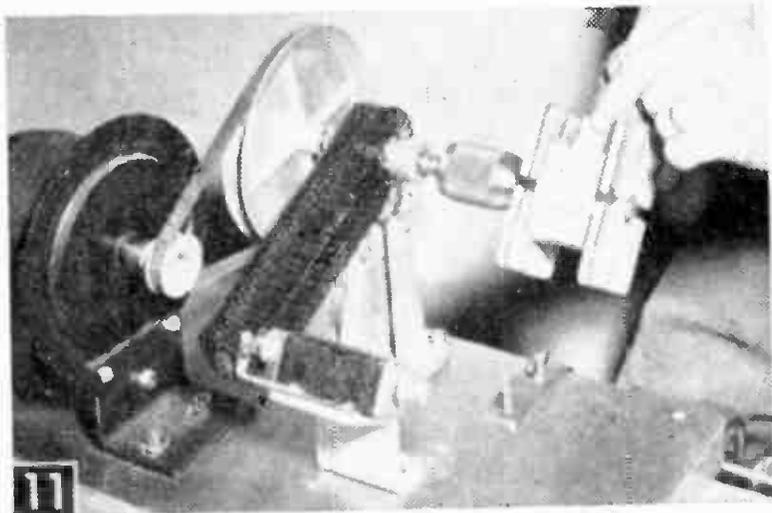

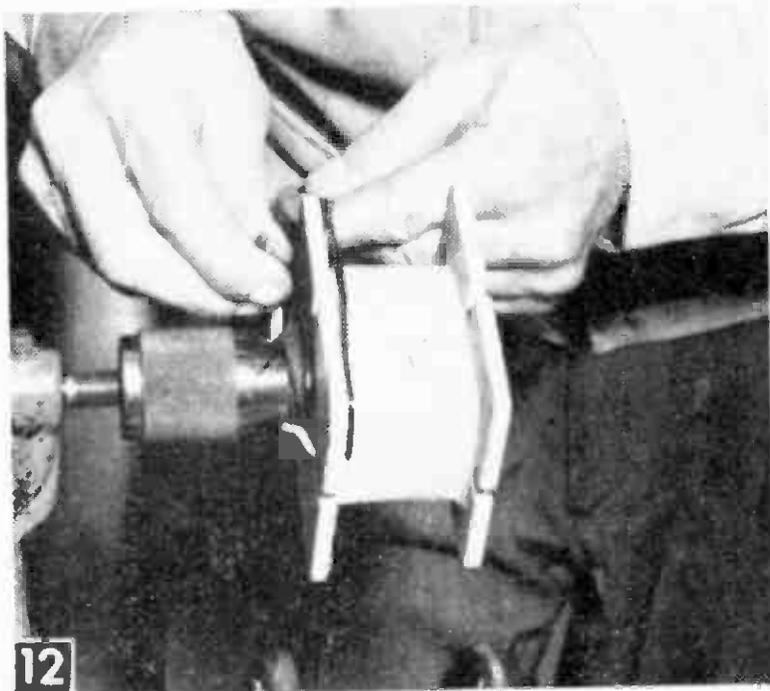Use Duro insulating paper, brought up at the sides and fastened with tape to insulate the coil from the laminations.



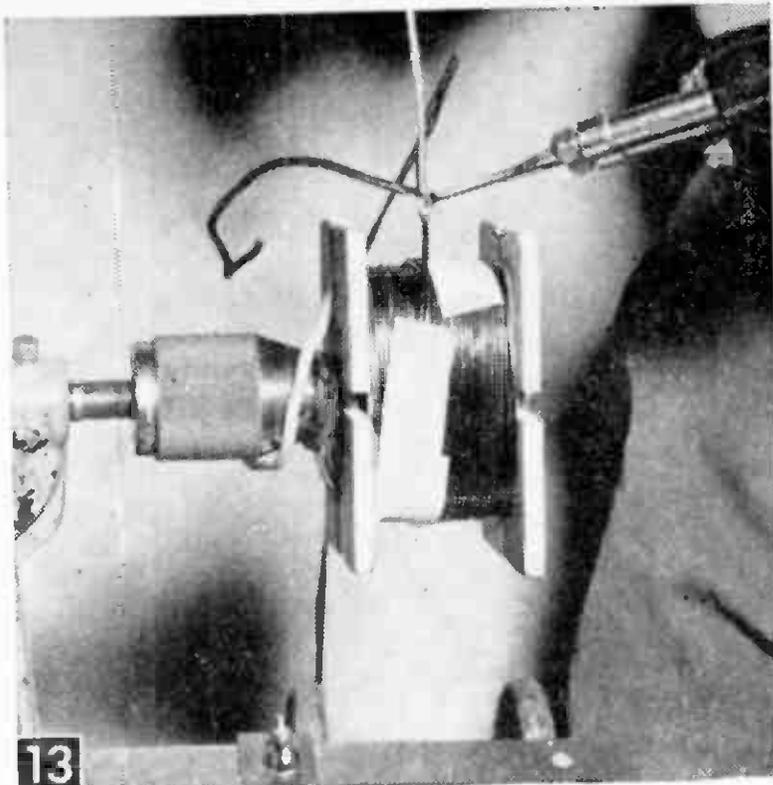When primary winding is finished, bring out the leads end wrap around the mounting bolt. The paper insulates primary from secondary winding.



With tape temporarily holding the windings, solder a flexible lead wire to make your first tap.

masking tape. Then wind another 25 turns, cut the wires, slip on spaghetti, and bring the last lead out the same slot used to start the secondary winding.

Now you are ready to remove the coil from the form. Make a fish wire and thread some strong cord through the slots (Fig. 14). Gently tap the windings with a block of wood and tightly bind the coil with secure knots. Unchuck, tap out the coil block, and check the coil size with a lamination. Coils have a tendency to spread out at the center after removal from the form, but can be compressed slightly with tape, or in a vise with two blocks of wood.

Use cotton coil tape, the kind specially sold for this purpose, to wrap the coil. Pull it tight each turn, and overlap the tape half its' width. Avoid bunching tape excessively at the corners, which might interfere with the laminations. When you come to a tie cord, cut it, and continue taping (Fig. 15). Run the cotton tape tightly around the leads and sew with needle and thread to keep tight. Also secure the ends of the tape with sewing.

COIL WINDING—SOURCES OF SUPPLY

Formvar Magnet Wire*


1-lb. spools; Allied Radio, 100 N. Western Ave., Chicago 80, Ill.
5 lb. #21, 10-lb., #16 minimum orders; Huse Liberty Mica Co.,
Lynfield Street, Peabody, Mass.

Insulation*

Duro insulating paper .007 or .010" thick in 24 x 46" sheets;
cotton coil tape, .007 x $\frac{3}{4}$ " wide rolls; clear baking varnish,
1 gal. cans.; Huse Liberty Mica Co.
Spaghetti tubing, heat-resistant; assorted sizes available most elec-
tronic supply houses. Assorted bundle, 8" lengths, Allied Radio
Cat. No. 49 T220. (\$.25)
Scotch masking tape, paper; hardware and paint stores.

Flexible Insulated Lead Wire

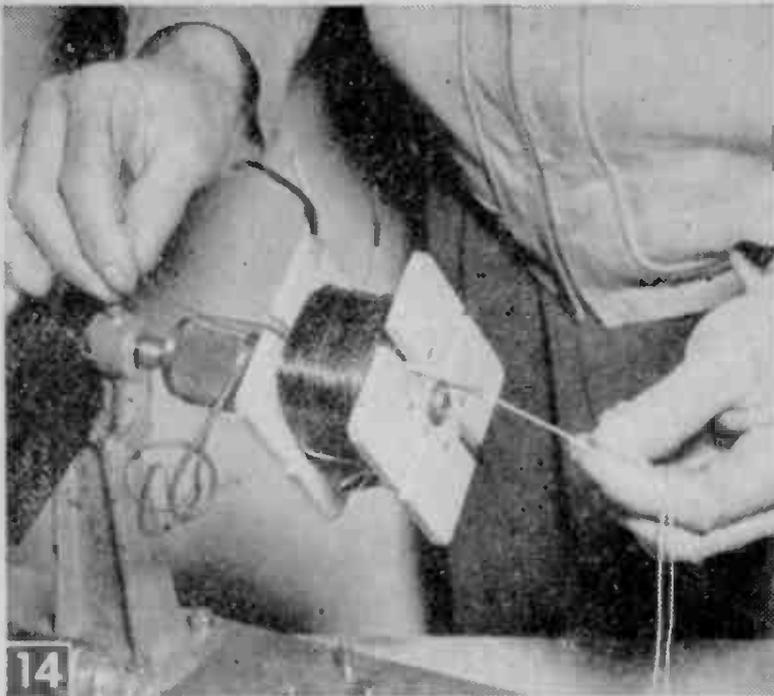Braided, heat resisting type; electrical and electronic supply houses.
*Many of these items in small quantities can be purchased through
motor winding shops.




14 Use a small fish made of a short piece of wire to thread through the slots to tie the finished windings.

Before you can install the laminations, the coil must be dipped in heat-reactive clear coil baking varnish, and baked. First be sure the coil is free of moisture, dirt etc. Use a can with enough varnish to completely submerge the coil. Wait 20 minutes or until all bubbling ceases, and then hang it up over the can to drain.

The Baking Oven (Fig. 16) uses two 250-watt infra-red lamps and has a hook fitted through the center of the large galvanized stove pipe for turning the coil during baking. Use asbestos cord for the leads to the lamps, and bind the asbestos fibers with carpet thread to prevent fraying. The infra-red heat rays penetrate down through the windings to the bottom layer, and so baking time will vary with the size of coil and make of varnish. Two or three hours should be enough, provided that you turn the coil a few times.

Assemble the laminations as soon as the

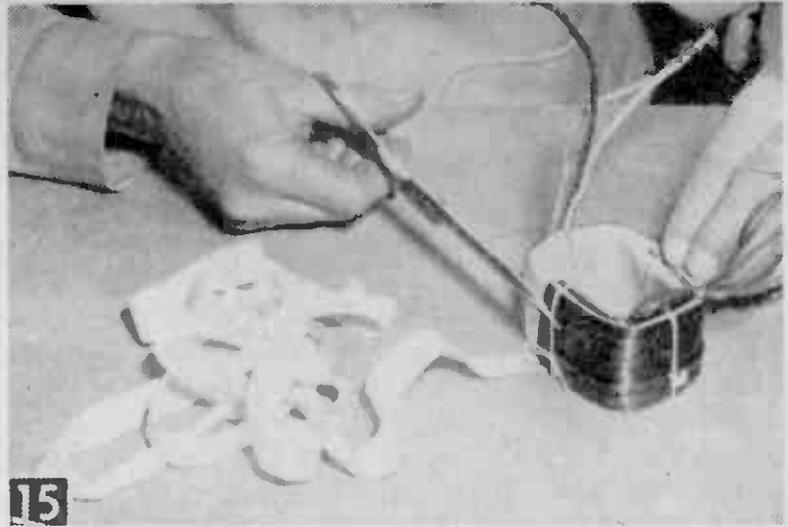



15 Pull each turn of the cotton coil tape tightly, and avoid bunching the tape at the corners.

coil is cool. You can insert two laminations per layer at once, but be sure to alternate the direction of the "E" for each layer (Fig. 17). When the stack is complete, insert the longer "E" pieces (keepers) which generally are used to cover the last laminations. If such keepers were not part of your original core assembly, disregard. They are not essential.

Now insert core assembly bolts through the laminations and tighten temporarily. Drive Bakelite or fiber wedges into the spaces between the winding and "E" legs to pre-

MATERIALS LIST—BAKING OVEN

Amt. Req.	Size and Description
1	10 x 24" length, galvanized stove pipe
2	1 x 25 x 1/8" strips, mild steel (legs)
2	1/16 x 6 x 18" pieces aluminum, or galv. sheet steel. (bend 90° for lamp brackets)
1	1/8 x 6" steel rod (coil support)
1	3/4 x 1" Bakelite rod (coil support knob)
4	6-32 x 1/2" rh machine screws and nuts (leg stove pipe assembly)
4	6-32 x 3/4" rh machine screws, washers and nuts (lamp socket assembly)
4	8-32 nuts, (rod-hook assembly)
2	250-watt infra-red lamps
2	lamp sockets, porcelain surface type
12'	#16 braided asbestos-covered appliance cord
1	a-c plug

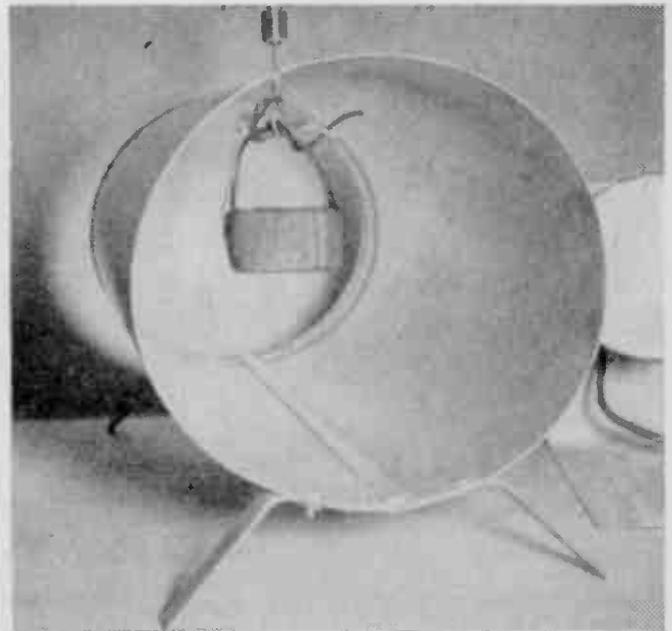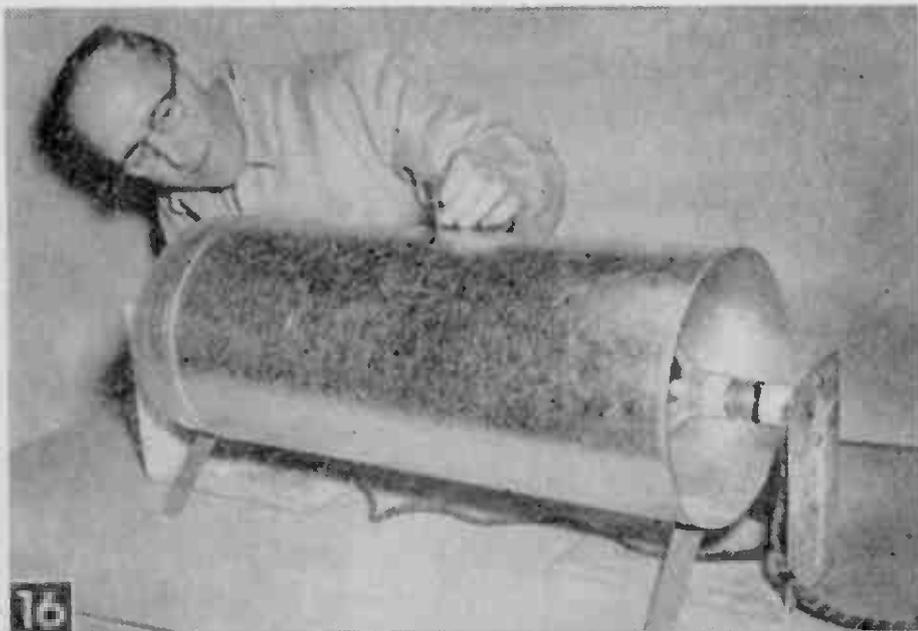

16 Use a 10-inch stovepipe and two 250-watt infrared lamps to make the oven. With the knob you can turn the coil during baking.

vent the laminations from vibrating. Square up your laminations and drive the joints together with a hammer, with the assembly resting on a steel block (Fig. 18).


Terminal strips are a practical necessity on this type of experimental transformer (Fig. 19), because you can make and break connections quickly. Use Jones #3-140 barrier terminal strips, and make two sheet metal brackets that just clear the top of the laminations. Complete construction by bolting the terminal assembly, the laminations, and transformer mounting brackets together. Carefully clean the ends of your lead wires and loop around the terminal screws, or solder permanently.

Insulation Tests. A high voltage transformer is generally used to check for grounds, or electrical leakage to core. A commercial "Megger" insulation tester, will also tell you whether you have perfect insulation. Make the test by applying the high voltage between one primary terminal and frame, and one secondary terminal and frame. Also test across one primary terminal and one secondary terminal.


Apply the high voltage for only an instant and of course, never between terminals of either winding. The leakage will show on the test transformer lamp, or on a megger, the meter will register value of insulation resistance.

Make the No-Load Test by connecting an ammeter in series with one line wire to the primary. A well designed transformer should draw hardly any current with no load on the secondary. Our transformer read .160 amps, which is a satisfactory value. A high current would indicate insufficient primary turns, or that there are shorts between turns. Either of these faults will require rewinding of the coil.

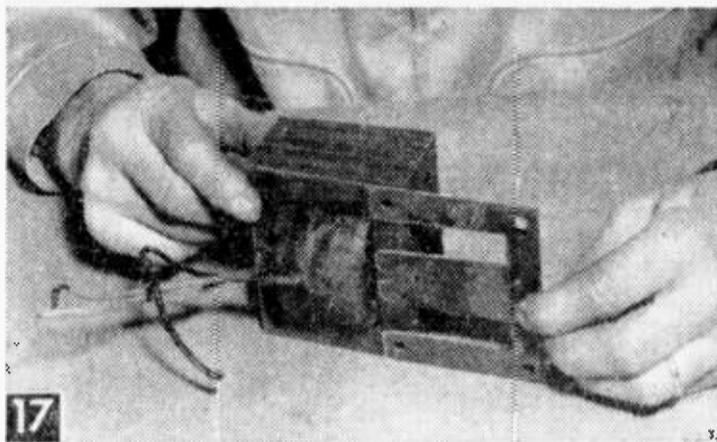A final test is with a secondary load. For our model, we used an adjustable 100-watt resistor (Fig. 19) capable of carrying the output amperage (5 amps) with a 4-ohm resistance. Connect the resistor with an ammeter in series with one side of the secondary, and



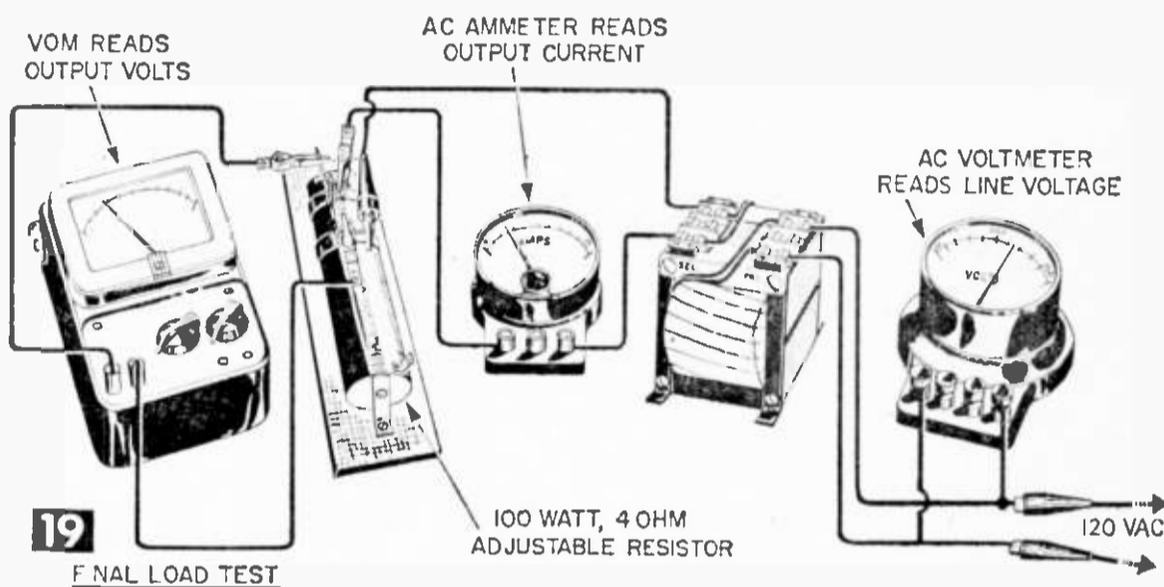Left. Assemble the laminations alternating the E each layer. Usually longer E pieces cover the ends. Right. Fiber wedges driven into the open center spaces prevent vibration of the laminations.



a voltmeter in parallel. Also connect a voltmeter across the line. An a-c ammeter to indicate line current, connected in series with one of the primary leads, would also be helpful. Adjust resistor band so secondary ammeter reads exactly 5 amps. Secondary voltage on our model read 16.4 volts, and reading primary amps, we found that full load current was exactly .75 amps. We found the finished transformer voltage was within 1% of our original calculations (using the right line voltage for the test).

You can use the method demonstrated in this article to wind any low voltage transformer. When you build high voltage transformers, you will need to use many turns of fine wire, which usually require insulation between layers to prevent breakdown. On factory winding machines, the insulation is applied automatically over perfectly even layers. On a hand winding machine, use a turn of paper every 500 turns to break up the otherwise continuous winding. Transformers up to 3,000 volts can be built by this method. As an added precaution with high-voltage types, thoroughly impregnate the coils and bake and varnish twice. Also, especially with high voltage transformers, use your infra-red oven to pre-bake the coil for 10 minutes to dry out any moisture that otherwise might be sealed in by the varnish.

WHITE'S RADIO LOG

QUICK REFERENCE INDEX

U. S. and Canadian AM Stations by Frequency.....	163
U. S. and Canadian AM Stations by Location.....	172
United States FM Stations.....	180
Canadian FM Stations.....	183
United States Television Stations.....	183
Canadian Television Stations.....	184
World-Wide Short-Wave Stations.....	185

Remote TV- Radio Sound Silencer

You won't need to dash madly to the TV before answering the phone, nor smash the picture tube when a hammy huckster goes into his commercial pitch

FOR no more than the cost of a push button from your dime store and some fixture wire, you can squelch the TV sound or a radio from your telephone stand or table near your favorite chair. The installation takes only a moment, and the silencer neither shuts off the radio or TV set requiring it to warm up when turned *On* again, nor connects to any 110-volt power line or high voltages within the set.



Because there are no high voltages involved, you can run the squelcher's cord under a carpet without worrying about fire or shock. TV twin-wire lead-ins are excellent because they lay flat.

Mount a doorbell push button with two #4-40 x 1/2-in. machine screws and nuts on a plastic coaster (Fig. 2) after cutting a hole in the side to let the cord through. Determine the required run of connecting fixture cord or TV lead-in and attach alligator clips to the ends opposite the push-button.

To install the squelcher, merely attach a clip to each of the lugs on the set's speaker (Fig. 3). Do not disturb any wires already soldered to these lugs. When the push-button is depressed, it shorts out the secondary (voice coil) of the set's output transformer. Voltages are too slight to feel. In some instances this device may not completely kill



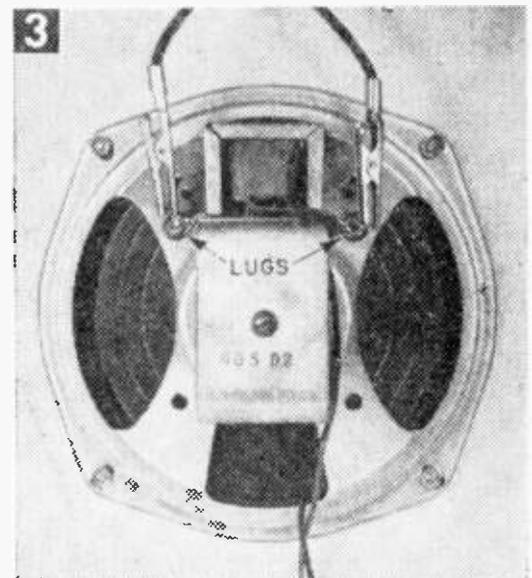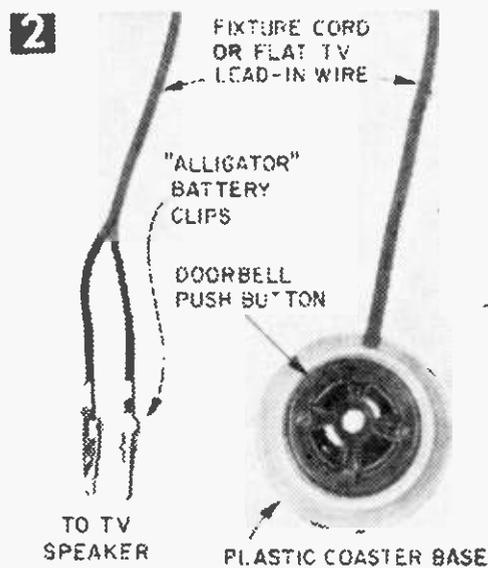1 Silencer button by telephone eliminates conversation being drowned out by radio or TV set.



Left, doorbell button, plastic coaster and cord are dime store items. Auto shops have clips. Right, Some sets have output transformer mounted on speaker; concealed in others. Regardless, attach clips to the lugs on speaker.

the sound, but will reduce it to a whisper.—T.A.B.



WHITE'S RADIO LOG

An up-to-date broadcasting directory
AM, FM, TV and Short-Wave Stations

Vol. 38

No. 1

Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and, of course, only information available up to press-time could be included. Copyright 1961 by Science and Mechanics Publishing Co., a subsidiary of Davis Publications, Inc., 450 East Ohio St., Chicago 11, Ill.

U. S. and Canadian AM Stations by Frequency

U.S. stations listed alphabetically by states within groups, Canadian stations precede U.S. Abbreviations: Kc., frequency in kilocycles; W.P., watt power; d—operates daytime only. Wave length is given in meters

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
540—555.5			CKCQ	Quesnel, B.C.	1000	600—499.7			WVNR	Beckley, W.Va.	1000
CBK	Regina, Sask.	50000	CFCB	Corner Brook, N.F.	1000	CFCF	Montreal, Que.	5000	WTMJ	Milwaukee, Wis.	5000
KVIP	Redding, Calif.	1000d	CJEM	Edmundston, N.B.	1000	CFCB	North Bay, Ont.	1000d	630—475.9		
KFMB	San Diego, Calif.	5000	WAAX	Gadsden, Ala.	5000	CFQC	Saskatoon, Sask.	5000	CFCO	Chatham, Ont.	1000
WGTO	Cypress Gardens, Florida	50000d	WCNO	Alturas, Calif.	1000	CJOR	Vancouver, B.C.	5000	CHLT	Sherbrooke, Que.	1000d
WDAK	Columbus, Ga.	5000	KLAC	Los Angeles, Calif.	5000	CKCL	Truro, N.S.	1000	CFCY	Charlottetown, P.E.I.	5000
KBRV	Soda Springs, Idaho	500d	WGMS	Washington, D.C.	5000	WIRB	Enterprise, Ala.	1000	CJET	Smith Falls, Ont.	1000
KWMT	Ft. Dodge, Iowa	1000d	WACL	Waycross, Ga.	5000	KCLS	Flagstaff, Ariz.	5000	CKRC	Winnipeg, Man.	5000
WDMV	Pocomoke City, Md.	500d	WKYB	Paducah, Ky.	1000	KVCV	Redding, Calif.	1000	CKOV	Kelowna, B.C.	1000
WBIC	Islip, N.Y.	250d	WVMI	Biloxi, Miss.	1000d	KFSD	San Diego, Calif.	5000	CKYL	Peace River, Alta.	1000
WETC	Wendell-Zebulon, N.C.	250d	KGRT	Las Cruces, N. Mex.	5000d	WICC	Bridgeport, Conn.	1000	WAVU	Albertville, Ala.	1000d
WCNG	Canonsburg, Pa.	250d	WMCA	New York, N.Y.	5000	WPDQ	Jacksonville, Fla.	5000	WJDB	Thomasville, Ala.	1000d
WYNN	Florence, S.C.	250	WSYR	Syracuse, N.Y.	5000	WMT	Cedar Rapids, Iowa	5000	KJNO	Juneau, Alaska	1000
WDXN	Clarksville, Tenn.	1000d	WNWC	Asheville, N.C.	5000	KSCB	Liberal, Kans.	500	KVMA	Magnolia, Ark.	1000d
WRIC	Richlands, Va.	1000d	WSHE	Raleigh, N.C.	500d	WFOM	New Orleans, La.	1000d	KIDD	Monterey, Calif.	1000
550—545.1			WKBN	Youngstown, Ohio	5000	WFST	Caribou, Maine	5000d	KHOW	Denver, Colo.	5000
CFNB	Fredericton, N.B.	50000	WNAX	Yankton, S.Dak.	5000	WCAO	Baltimore, Md.	5000	WMAL	Washington, D.C.	5000
CFBR	Sudbury, Ont.	1000	WFAA	Dallas, Tex.	5000	WLST	Escanaba, Mich.	1000d	WSAV	Savannah, Ga.	5000
CHLN	Three Rivers, Que.	5000	WBAP	Ft. Worth, Tex.	5000	WTAC	Flint, Mich.	1000	KIDO	Boise, Idaho	5000
CKPG	Prince George, B.C.	250	KLUB	Salt Lake City, Utah	5000	KGEZ	Kalispell, Mont.	2000	WLAP	Lexington, Ky.	5000
KENI	Anchorage, Alaska	5000	KV	Seattle, Wash.	5000	WCVP	Murphy, N.C.	1000d	KTIB	Thibodaux, La.	500
KOY	Phoenix, Ariz.	5000	WMAM	Marinette, Wis.	5000	WSJS	Winston-Salem, N.C.	5000	WJMS	Ironwood, Mich.	1000
KAFY	Bakersfield, Calif.	1000	580—516.9			KSJ	Jamestown, N.D.	5000	KDWB	So. St. Paul, Minn.	5000
KRAI	Craig, Colo.	1000	CJFX	Antigonish, N.S.	5000	WFRM	Coudersport, Pa.	1000d	KXOK	St. Louis, Mo.	5000
WAYR	Orange Park, Fla.	1000d	CKEY	Toronto, Ont.	5000	WAEL	Mayaguez, P.R.	1000	KGWV	Belgrade, Mont.	1000d
WGA	Gainesville, Ga.	5000	CKPR	Ft. William, Ont.	5000	WREC	Memphis, Tenn.	5000	KOH	Reno, Nev.	1500
KMVI	Walluku, Hawaii	1000	CKUA	Edmonton, Alta.	10000	KROD	El Paso, Tex.	5000	KLEA	Livingston, N. Mex.	500
KFRM	Concordia, Kansas	5000d	CKY	Winnipeg, Man.	50000d	KERB	Kernit, Tex.	1000d	WIRC	Hickory, N.C.	1000d
WCB	Columbus, Miss.	1000	WABT	Tuskegee, Ala.	500d	KTBB	Tyler, Tex.	1000	WMFD	Wilmington, N.C.	1000
KSD	St. Louis, Mo.	5000	KTAN	Tucson, Ariz.	5000	610—491.5			KWRO	Coquille, Oreg.	5000d
KOPR	Butte, Mont.	1000	KMJ	Fresno, Calif.	5000	CHNC	New Carlisle, Que.	5000	WEJL	Scranton, Pa.	500d
WGR	Buffalo, N.Y.	5000	KUBC	Montrose, Colo.	5000	CJAT	Trail, B.C.	1000	WKYN	Rio Piedras, P.R.	1000d
WDBM	Statesville, N.C.	500d	WDBO	Orlando, Fla.	5000	CKKL	Thompson, Man.	1000	WPRO	Providence, R.I.	5000
KFYR	Bismarek, N. Dak.	5000	WGC	Augusta, Ga.	5000	CKTB	St. Catharines, Ont.	5000	KGFX	Pierre, S. Dak.	250
WKRC	Cincinnati, Ohio	5000	KFXD	Nampa, Idaho	5000	WGSN	Birmingham, Ala.	5000	KMAC	San Antonio, Tex.	5000
KOAC	Corvallis, Oreg.	5000	WILL	Urbana, Ill.	5000d	KAVL	Lancaster, Calif.	1000	KSXX	Salt Lake City, Utah	1000d
WHLM	Bloomsburg, Pa.	1000	KSAC	Manhattan, Kans.	5000	KFRS	San Francisco, Calif.	5000	KGDN	Edmunds, Wash.	5000d
WPAB	Ponce, P.R.	5000	WIBW	Topeka, Kans.	5000	WCKR	Miami, Fla.	5000	KZUN	Opportunity, Wash.	500d
WPAW	Pawtucket, R.I.	500	KALB	Alexandria, La.	5000	WDEB	Pensacola, Fla.	500d	640—468.5		
KCRS	Midland, Tex.	5000	WTAG	Worcester, Mass.	5000	WCEH	Hawkinsville, Ga.	500d	CBN	St. John's, N.F.	10000
KTSA	San Antonio, Tex.	5000	WELO	Tupelo, Miss.	1000	WRUS	Russellville, Ky.	500d	KFI	Los Angeles, Calif.	50000
WDEV	Waterbury, Vt.	5000	WAGR	Lumberton, N.C.	500d	KDAL	Duluth, Minn.	5000	WOI	Ames, Iowa	5000d
WSVA	Harrisonburg, Va.	5000	WHP	Harrisburg, Pa.	5000	WDAF	Kansas City, Mo.	5000	WHLO	Akron, Ohio	1000
KARI	Blaine, Wash.	500d	WKAQ	San Juan, P.R.	5000	KOJM	Havre, Mont.	1000	WNAD	Norman, Okla.	1000d
WSAU	Wausau, Wis.	5000	KOBH	Hot Springs, S. Dak.	500d	WGIR	Manchester, N.H.	5000	650—461.3		
560—535.4			WRKH	Rockwood, Tenn.	1000d	KGGM	Albuquerque, N. Mex.	5000	KKAA	Honolulu, Hawaii	10000
CBY	Corner Brook, N.F.	1000	KDAV	Lubbock, Tex.	500d	WAYS	Charlotte, N.C.	5000	WSM	Nashville, Tenn.	50000
CFRA	Ottawa, Ont.	5000	WLES	Lawrenceville, Va.	500d	WTVN	Columbus, Ohio	5000	KRCT	Baytown, Texas	2500
CJKL	Kirkland Lake, Ont.	5000	WCHS	Charleston, W. Va.	5000	WIP	Philadelphia, Pa.	5000	660—454.3		
CFOS	Owen Sound, Ont.	1000	WKTY	LaCrosse, Wis.	5000	KILT	Houston, Tex.	5000	KFAR	Fairbanks, Alaska	10000
WOOF	Dothan, Ala.	5000d	590—508.2			KVNU	Logan, Utah	1000	KMEO	Omaha, Nebr.	500d
KYUM	Yuma, Ariz.	1000	CFAR	FlinFlon, Man.	1000	WLSL	Roanoke, Va.	5000	WNBC	New York, N.Y.	50000
KSFO	San Fran., Calif.	5000	CKAR	Huntsville, Ont.	1000	KEPR	Kennewick, Wash.	5000	WESC	Greenville, S.C.	40000d
KLZ	Denver, Colo.	5000	CKRS	Jonquiere, Que.	1000	620—483.6			KSKY	Dallas, Tex.	1000
WQAM	Miami, Fla.	5000	VOCM	St. Johns, N.F.	10000	CFCL	Timmins, Ont.	10000	670—447.5		
WIND	Chicago, Ill.	5000	WRAG	Carrollton, Ala.	1000d	CKCK	Regina, Sask.	5000	WMAQ	Chicago, Ill.	50000
WMIK	Middlesboro, Ky.	500d	KBHS	Hot Springs, Ark.	5000d	KTAR	Phoenix, Ariz.	5000	680—440.9		
WGAN	Portland, Maine	5000	KFXM	San Bernardino, Cal.	1000	KNGS	Hanford, Calif.	1000	CHFA	Edmonton, Alta.	5000
WHYN	Springfield, Mass.	1000	KCSJ	Pueblo, Colo.	1000	KWSD	Mt. Shasta, Calif.	1000d	CHLO	St. Thomas, Ont.	1000
WQTE	Monroe, Mich.	500d	WDLP	Panama City, Fla.	1000	KSTR	Grand Junction, Colo.	5000d	CJOB	Winnipeg, Man.	10000
WEBC	Duluth, Minn.	5000	WPLO	Atlanta, Ga.	5000	WSUN	St. Petersburg, Fla.	5000	CKGB	Timmins, Ont.	10000
KWTO	Springfield, Mo.	5000	KID	Idaho Falls, Idaho	5000	WTRP	LaGrange, Ga.	1000d	KNBC	San Fran., Calif.	50000
KMON	Great Falls, Mont.	5000	WVLC	Lexington, Ky.	5000	KWAL	Wallace, Idaho	1000	WPIN	St. Petersburg, Fla.	1000d
WGAI	Elizabeth City, N.C.	1000	WEEI	Boston, Mass.	5000	KMNS	Sioux City, Iowa	1000	WCTT	Corbin, Ky.	1000
WFIL	Philadelphia, Pa.	5000	WKZO	Kalamazoo, Mich.	5000	WTMT	Louisville, Ky.	500d	WCBM	Baltimore, Md.	10000
WIS	Columbia, S.C.	5000	WOW	Omaha, Nebr.	5000	WLBZ	Bangor, Maine	5000	WNAC	Boston, Mass.	50000
WHBQ	Memphis, Tenn.	5000	WROW	Albany, N.Y.	5000	WJDX	Jackson, Miss.	5000	WDBC	Escanaba, Mich.	1000
KFDM	Beaumont, Tex.	5000	WGTM	Wilson, N.C.	5000	WVNJ	Newark, N.J.	5000	WHITE'S RADIO LOG 163		
KPQ	Wenatchee, Wash.	5000	KUGN	Eugene, Oreg.	5000	WHEN	Syracuse, N.Y.	5000			
WJLS	Beckley, W. Va.	5000	WARM	Scranton, Pa.	5000	WDNC	Durham, N.C.	5000			
570—526.0			WMBS	Uniontown, Pa.	1000	KGW	Portland, Oreg.	5000			
CKEK	Cranbrook, B.C.	1000	KTBC	Austin, Tex.	5000	WHJB	Greensburg, Pa.	1000			
			KSUB	Cedar City, Utah	1000	WCAY	Cayce, S.C.	500d			
			WLVA	Lynchburg, Va.	1000	WATE	Knoxville, Tenn.	5000			
			KHQ	Spokane, Wash.	5000	KWFT	Wichita Falls, Tex.	5000			
						WCAX	Burlington, Vt.	5000			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WCTA	Adalusia, Ala.	5000	KLER	Orofino, Idaho	5000d	WIVI	Christianstiel, V.I.	1000	WCNU	Crestview, Fla.	1000d
WWWR	Russellville, Ala.	1000d	WAAF	Chicago, Ill.	1000d	WDTI	Danville, Va.	500d	WZRO	Jacksonville Beach, Fla.	1000d
KARK	Little Rock, Ark.	5000	WXLW	Indianapolis, Ind.	5000d	KREM	Spokane, Wash.	5000	WINQ	Tampa, Fla.	50000d
KDES	Palm Springs, Calif.	1000d	KOEL	Oelwein, Iowa	1000	WYVO	Pineville, W.Va.	1000d	WGUN	Decatur, Ga.	50000d
KVEC	San Luis Obispo, Cal.	1000	KJRG	Newton, Kans.	500d	WHA	Madison, Wis.	5000d	WCSI	Columbus, Ind.	500d
KREX	Grd. Junction, Colo.	5000	WBVL	Barbourville, Ky.	1000d				KSMN	Mason City, Iowa	1000d
KLMR	Lamar, Colo.	1000	WAGM	Presque Isle, Maine	5000				KIND	Independence, Kans.	250d
WMEG	Eau Gallie, Fla.	1000d	WORL	Boston, Mass.	5000d				KDLA	DeRidder, La.	1000d
WGST	Atlanta, Ga.	5000	WWJ	Detroit, Mich.	5000				WSDI	Baltimore, Md.	1000d
KAHU	Walpahu, Hawaii	1000	KRSI	St. Louis Park, Minn.	1000d				KCHI	Chillicothe, Mo.	250d
WMOK	Metropolis, Ill.	1000d	WBKH	Hattiesburg, Miss.	5000d				KXEN	Festus, Mo.	50000d
WBAA	W. Lafayette, Ind.	5000	KLIK	Jefferson City, Mo.	5000d				KRVN	Lexington, Nebr.	25000d
KFNF	Shenandoah, Iowa	1000	WBBF	Rochester, N.Y.	1000				WCNL	Newport, N.H.	250d
WTCW	Whitesburg, Ky.	1000d	WIBX	Utica, N.Y.	500d				WINS	New York, N.Y.	50000d
WBOX	Bogalusa, La.	1000d	WPET	Greensboro, N.C.	500d				WABZ	Albermarle, N.C.	1000d
KTOC	Jonesboro, La.	500d	WNCC	Barnesboro, Pa.	500d				WELS	Kinston, N.C.	1000d
WPTX	Lexington Pk., Md.	500d	WPEN	Philadelphia, Pa.	5000				WIOI	New Boston, Ohio	1000d
WMPL	Hancock, Mich.	1000d	WSPA	Spartanburg, S.C.	5000				KBEV	Portland, Oreg.	1000d
KDHL	Faribault, Minn.	1000	KWAT	Watertown, S.Dak.	1000				WITT	Lewlsburg, Pa.	250d
KWAD	Wadena, Minn.	1000	WAGG	Franklin, Tenn.	1000d				WHIN	Gallatin, Tenn.	1000d
KRAM	Las Vegas, Nev.	1000	KOSX	Oenison, Tex.	500				WORM	Savannah, Tenn.	250d
KOLO	Reno, Nev.	1000	KPRC	Houston, Tex.	5000				KBUY	Amarillo, Tex.	5000
KQEO	Albuquerque, N.Mex.	1000	KSEL	Lubbock, Tex.	5000				KMLW	Marlin, Tex.	250d
WTTM	Trenton, N.J.	1000	WXGI	Richmond, Va.	1000d				WELK	Charlottesville, Va.	1000d
WKRT	Cortland, N.Y.	1000	KJR	Seattle, Wash.	500d				WMEV	Marion, Va.	1000d
WGHO	Saugerties, N.Y.	1000d	WERL	Eagle River, Wis.	1000d				WCST	Berkeley Sprgs., W.Va.	250d
WBBB	Burlington, N.C.	5000d	WKAZ	Charleston, W.Va.	5000				WSPT	Stevens Pt., Wis.	1000d
WMNI	Columbus, Ohio	500	WKTL	Sheboygan, Wis.	500d						
KGAL	Lebanon, Oreg.	1000									
WKVA	Lewistown, Pa.	1000d									
WJAR	Providence, R.I.	5000									
WTND	Orangeburg, S.C.	1000d									
KEZU	Rapid City, S.Dak.	1000d									
WLIV	Livingston, Tenn.	1000d									
KELP	El Paso, Tex.	1000									
KECK	Odessa, Tex.	1000									
KTLW	Texas City, Tex.	1000d									
KITN	Olympia, Wash.	1000d									
KXYL	Spokane, Wash.	5000									
WMMN	Fairmont, W.Va.	5000									
WOKY	Milwaukee, Wis.	1000									
930—322.4			960—312.3			980—305.9			1020—293.9		
CFBC	Saint John, N.B.	5000	CFAC	Calgary, Alta.	10000	CKNW	New Westminster, Brit. Columbia	10000	WJTY	Danville, Ill.	1000
CJCA	Edmonton, Alta.	1000d	CHNS	Halifax, N.S.	10000	KOKA	Shreveport, La.	5000d	WCAP	Lowell, Mass.	1000d
CJON	St. John's, N.F.	10000	CKWS	Kingston, Ont.	5000	WPBC	Minneapolis, Minn.	1000d	WAPP	McComb, Miss.	1000d
WETO	Gadsden, Ala.	1000d	WBRC	Birmingham, Ala.	5000	WAPF	McComb, Miss.	1000d	KMBC	Kansas City, Mo.	5000
KTKN	Ketchikan, Alaska	1000	WMOZ	Mobile, Ala.	1000	KMGB	Ste. Genevieve, Mo.	500	KVER	Clovis, N.Mex.	1000
KAPR	Douglas, Ariz.	1000d	KOOL	Phoenix, Ariz.	5000	KMIN	Grants, N. Mex.	1000d	KMIN	Grants, N. Mex.	1000d
KHJ	Los Angeles, Calif.	5000	KAVR	Apple Valley, Calif.	5000d	WTRY	Troy, N.Y.	5000	WKLM	Wilmington, N.C.	5000d
KMET	Paradise, Calif.	500d	KNEZ	Lompoc, Calif.	500	WAAA	Win.-Salem, N.C.	1000d	WONE	Dayton, Ohio	5000
KIUP	Durango, Colo.	5000	KABL	Oakland, Calif.	1000	WONE	Dayton, Ohio	5000	WILK	Wilkes-Barre, Pa.	5000
WKSB	Milford, Del.	500d	WELI	New Haven, Conn.	5000	WILK	Wilkes-Barre, Pa.	5000	KDSJ	Deadwood, S.Dak.	1000
WHAN	Haines City, Fla.	500d	WGRO	Lake City, Fla.	500d	WSIX	Nashville, Tenn.	5000	KFRD	Rosenberg, Tex.	1000d
WJAX	Jacksonville, Fla.	5000	WJCM	Sebring, Fla.	1000d	KSVK	Richfield, Utah	5000	WFHG	Bristol, Va.	5000
WKXY	Sarasota, Fla.	1000	WJAZ	Albany, Ga.	5000d	WMEK	Chase City, Va.	500d	KUTI	Yakima, Wash.	5000d
WMGR	Bainbridge, Ga.	5000d	WRFC	Athens, Ga.	5000	WHAW	Weston, W.Va.	1000d	WHAW	Weston, W.Va.	1000d
KSEI	Pocatello, Idaho	5000	KSRA	Salmon, Idaho	1000d	WCUB	Manitowoc, Wis.	1000d	WPRE	Prarie du Chien, Wis.	500d
WTAD	Quincy, Ill.	5000	WDLM	E. Moline, Ill.	1000d						
WKCT	Bowling Green, Ky.	1000	WSBT	South Bend, Ind.	5000						
WFMD	Frederick, Md.	1000	KMA	Shenandoah, Iowa	5000						
WREB	Holyoke, Mass.	500d	WPRT	Prestonsburg, Ky.	1000d						
WBCK	Battle Creek, Mich.	1000	KROF	Abbeville, La.	1000d						
WSLI	Jackson, Miss.	5000	WBOC	Salisbury, Md.	5000						
KWOC	Poplar Bluff, Mo.	1000	WFGM	Fitchburg, Mass.	1000						
KOFI	Kalispell, Mont.	5000d	WHAK	Rogers City, Mich.	5000d						
KOGA	Ogallala, Nebr.	500d	KLTF	Little Falls, Minn.	500d						
WVNH	Rochester, N.H.	5000d	WABG	Greenwood, Miss.	1000						
WPAT	Paterson, N.J.	5000	KFVS	Cape Girardeau, Mo.	1000						
WBEN	Buffalo, N.Y.	5000	KNEB	Scottsbluff, Nebr.	1000						
WSOC	Charlotte, N.C.	5000	KWYK	Farmington, N.Mex.	1000d						
WRRF	Washington, N.C.	5000	WEAV	Plattsburg, N.Y.	5000						
WEOL	Elyria, Ohio	1000	WCFT	Dallas, N.C.	1000d						
WKY	Oklahoma City, Okla.	5000	WFTC	Kinston, N.C.	5000						
KAGI	Grants Pass, Oreg.	1000	WWST	Wooster, Ohio	1000d						
WCNR	Bloomsburg, Pa.	1000d	KGWA	Enid, Okla.	1000						
KSDN	Aberdeen, S.D.	1000	KLAD	Klamath Falls, Oreg.	5000d						
WSEV	Sevierville, Tenn.	5000d	WHYL	Carlisle, Pa.	5000d						
KDET	Center, Tex.	1000d	WADP	Kane, Pa.	1000d						
KITE	San Antonio, Tex.	5000	WATS	Sayre, Pa.	1000d						
KENY	Bellingham-Ferndale Wash.	1000d	WBEU	Beaufort, S.C.	1000d						
WSAZ	Huntington, W.Va.	5000	WBMC	McMinnville, Tenn.	500d						
WLBL	Stevens Point, Wis.	5000d	KIMP	Mt. Pleasant, Tex.	1000d						
940—319.0			970—309.1			990—302.8			1030—291.1		
CBM	Montreal, Que.	5000d	CKCH	Hull, Que.	5000	CBW	Winnipeg, Man.	5000d	WBZ	Boston, Mass.	50000
CJGX	Yorkton, Sask.	10000	WERH	Hamilton, Ala.	5000d	CBT	Grand Falls, N.F.	1000	WBZA	Springfield, Mass.	1000
CJIB	Vernon, B.C.	1000	WTBF	Troy, Ala.	5000	WVWF	Fayette, Ala.	1000d	KOB	Albuquerque, N.Mex.	10000
KMBO	Tucson, Ariz.	250	KNEA	Jonesboro, Ark.	1000d	WVWB	Flomaton, Ala.	500d	KCTA	Corpus Christi, Tex.	50000d
KFRE	Fresno, Calif.	50000	KBIS	Bakersfield, Calif.	1000	WVWB	Flomaton, Ala.	500d			
WINZ	Miami, Fla.	5000d	KCHV	Coachella, Calif.	1000d	KTCT	Tucson, Ariz.	1000			
WMAZ	Macon, Ga.	50000	KFEL	Pueblo, Colo.	1000d	KKIS	Pittsburg, Calif.	5000			
WMIX	Mt. Vernon, Ill.	1000	WFLA	Tampa, Fla.	5000	KGUO	Santa Barbara, Calif.	1000d			
KIOA	Des Moines, Iowa	10000	WVIN	Atlanta, Ga.	5000d	KLIR	Denver, Colo.	1000d			
WYLD	New Orleans, La.	1000	WVOP	Vidalia, Ga.	5000d	WBZY	Torrington, Conn.	1000d			
KGRL	Bend, Oreg.	1000d	KHBC	Hilo, Hawaii	1000	WFAB	Miami, Fla.	500			
WESA	Charleroi, Pa.	250	KAYT	Rupert, Idaho	1000d	WHOO	Orlando, Fla.	10000			
WGRP	Greenville, Pa.	1000d	WMAY	Springfield, Ill.	1000	WDWD	Dawson, Ga.	1000d			
WIPR	San Juan, P.R.	10000	WAVE	Louisville, Ky.	5000	KOOD	Honolulu, Hawaii	1000			
KIXZ	Amarillo, Tex.	5000	KSYL	Alexandria, La.	1000	WCAZ	Carthage, Ill.	1000d			
950—315.6			1000—299.8			1010—296.9			1040—288.3		
CKNB	Campbellton, N.E.	1000	WNTA	Newark, N.J.	5000	CBX	Edmonton, Alta.	50000	KHMH	Honolulu, Hawaii	5000
CKBB	Barrie, Ont.	10000	WEBR	Buffalo, N.Y.	5000	CFRB	Toronto, Ont.	50000	WHO	Des Moines, Iowa	50000
WRMA	Montgomery, Ala.	1000d	WCHN	Norwich, N.Y.	500d	KINK	Phoenix, Ariz.	500d	KIXL	Dallas, Tex.	1000d
KXJK	Forrest City, Ark.	5000d	WRCS	Ahoskie, N.C.	1000d	KVNC	Winslow, Ariz.	1000			
KFSA	Ft. Smith, Ark.	1000	WWIT	Canton, N.C.	1000d	KLRA	Little Rock, Ark.	10000			
KAHI	Auburn, Calif.	1000d	WDAY	Fargo, N.Dak.	5000	KCHJ	Delano, Calif.	5000			
KIMN	Denver, Colo.	5000	WREO	Ashtabula, Ohio	5000	KCMJ	Palm Sprgs., Calif.	1000			
WNUE	Ft. Walton Sch., Fla.	1000d	WATH	Athens, Ohio	1000d	KSAY	San Fran., Calif.	10000d			
WLOF	Orlando, Fla.	5000	KAKC	Tulsa, Okla.	1000						
WGTA	Summerville, Ga.	1000d	KOIN	Portland, Oreg.	5000						
WGOV	Valdosta, Ga.	5000	WWSW	Pittsburgh, Pa.	5000						
KBOI	Boise, Idaho	5000	WJMX	Florence, S.C.	5000						
			KASE	Austin, Tex.	1000d						
			KNOK	Ft. Worth, Tex.	1000d						

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
1060—282.8			WJRD Tuscaloosa, Ala.	5000	KKAR Pomona, Calif.	250d	WITH Baltimore, Md.	250			
CFCN Calgary, Alta.	10000		KCKY Coolidge, Ariz.	1000	KFSC Denver, Colo.	1000d	WCUM Cumberland, Md.	250			
CJLR Quebec, Que.	5000		KXLR No. Little Rock, Ark.	5000	WDEE Hamden, Conn.	1000d	WNNB No. Adams, Mass.	250			
KUPD Tempe, Ariz.	500		KFSG Los Angeles, Calif.	2500	WQTY Arlington, Fla.	250d	WESX Salem, Mass.	250			
KPAY Chico, Calif.	10000		KRKD Los Angeles, Calif.	5000	WKBX Kissimmee, Fla.	250d	WNEB Worcester, Mass.	250			
WNOE New Orleans, La.	50000		KJAX Santa Rosa, Calif.	5000	WFEC Miami, Fla.	250d	WJEF Grand Rapids, Mich.	500			
WHFB Benton Harbor, Mich.	1000d		KGMC Englewood, Colo.	1000d	WCLB Camilla, Ga.	1000d	WIKB Iron River, Mich.	250			
WMAP Monree, N.C.	250d		WCNX Middletown, Conn.	500d	WPLK Rockmart, Ga.	250d	WMPC Lapeer, Mich.	250			
WCMW Canton, Ohio	1000d		WDEL Wilmington, Del.	5000	WSFT Thomaston, Ga.	250d	WSOO St. Ste. Marie, Mich.	1000			
WRCV Philadelphia, Pa.	50000		WNOB Daytona Bch., Fla.	1000	WLPO LaSalle, Ill.	1000d	WSTR Sturgis, Mich.	250			
1070—280.2			WTMP Tampa, Fla.	5000d	WKRS Waukegan, Ill.	1000d	WKLK Cloquet, Minn.	250			
CBA Sackville, N.B.	50000		WFPM Fort Valley, Ga.	1000d	WSLM Salem, Ind.	1000d	KGHS Internat'l Falls, Minn.	100			
CHOK Sarnia, Ont.	5000		WJEM Valdosta, Ga.	1000d	KJAN Atlantic, Iowa	250d	KYSM Mankato, Minn.	250			
WAPI Birmingham, Ala.	50000		WGGH Marion, Ill.	5000d	KOUR Independence, Iowa	250d	KTRF Thief Riv. Falls, Minn.	250			
KNX Los Angeles, Calif.	50000		WJRL Rockford, Ill.	500d	KOFO Ottawa, Kans.	250d	KWNO Winona, Minn.	250			
WVCG Coral Gables, Fla.	1000d		KWKY Des Moines, Iowa	1000	WFKN Franklin, Ky.	250d	WCMA Corinth, Miss.	250			
WIBC Indianapolis, Ind.	50000		KSAL Salina, Kans.	5000	KBCL Shreveport, La.	250d	WHSY Hattiesburg, Miss.	250			
KIRL Wichita, Kans.	10000		WMST Mt. Sterling, Ky.	500d	WLB1 Denham Springs, La.	250d	WSSO Starkville, Miss.	250			
KHMO Hannibal, Mo.	5000		WL0C Mumfordsville, Ky.	1000d	WSME Sanford, Maine	1000d	WAZF Yazoo City, Miss.	250			
WHPE High Point, N.C.	1000d		WJBO Baton Rouge, La.	5000	WBCH Hastings, Mich.	250d	KODE Joplin, Mo.	250			
WFLI Lookout Mtn., Tenn.	10000		WGMM Skowhegan, Maine	5000d	WAVN Stillwater, Minn.	1000d	KLWT Lebanon, Mo.	250			
W0IA Memphis, Tenn.	50000		WCOP Boston, Mass.	5000	WMDG Hazlehurst, Miss.	250d	KNCM Moberly, Mo.	250			
KOPY Alice, Tex.	1000		WCEN Mt. Pleasant, Mich.	1000	KBHM Branson, Mo.	1000d	KANA Anaconda, Mont.	250			
WKOW Madison, Wis.	10000		KASM Albany, Minn.	1000d	KGMO Cape Girardeau, Mo.	250d	KBMN Bozeman, Mont.	250			
1080—277.6			WXTN Lexington, Miss.	500d	KLWP Union, Mo.	1000d	KXLO Lewiston, Mont.	250			
CHED Edmonton, Alta.	10000		KRMS Osage Beach, Mo.	1000d	WKBK Keene, N.H.	1000d	KLCB Libby, Mont.	250			
KSCO Santa Cruz, Calif.	1000		KSEN Shelby, Mont.	1000	WGNV Newburgh, N.Y.	1000d	KTNC Falls City, Nebr.	100			
WTIC Hartford, Conn.	50000		KDEF Albuquerque, N.Mex.	1000d	WSOQ N. Syracuse, N.Y.	1000d	KHAS Hastings, Nebr.	250			
WKLO Louisville, Ky.	5000		WRUN Utica, N.Y.	5000	WKMT Kings Mtn., N.C.	1000d	KELY Ely, Nev.	250			
WOAP Owosso, Mich.	250d		WBAG Burlington, N.C.	1000d	WREV Reidsville, N.C.	250d	KLAS Las Vegas, Nev.	250			
WYSL Kenmore, N.Y.	1000d		WGBR Goldsboro, N.C.	5000	WENC Whiteville, N.C.	1000d	KDOT Reno, Nev.	250			
WEWO Laurinburg, N.C.	1000d		WCUE Akron, Ohio	1000d	KEYD Oakes, N.Dak.	1000d	WMOU Berlin, N.H.	250			
KWJJ Portland, Oreg.	10000		WIMA Lima, Ohio	1000	WGAR Cleveland, Ohio	50000	WTSV Claremont, N.H.	250			
WEEP Pittsburgh, Pa.	1000d		KNED McAlester, Okla.	1000	WERT Van Wert, Ohio	250d	WCMC Wildwood, N.J.	100			
KRLD Dallas, Tex.	50000		KAGO Klamath Falls, Oreg.	5000	KGYN Guymon, Okla.	1000d	KALG Alamogordo, N.Mex.	250			
1090—275.1			WHUN Huntingdon, Pa.	1000d	WJUN Mexico, Pa.	250d	KOTS Deming, N.Mex.	250			
CHEC Lethbridge, Alta.	5000		WLPS Lehigh, Pa.	1000d	WRIB Providence, R.I.	1000d	KYVA Gallup, N.Mex.	250			
CHIC Brampton, Ont.	250		WKPA New Kensington, Pa.	1000d	WALD Walterboro, S.C.	1000d	KFUN Las Vegas, N.Mex.	250			
CHRS St. Jean, Que.	1000		WRNO Orangeburg, S.C.	5000	WFWL Camden, Tenn.	250	KSWS Roswell, N.Mex.	250			
KTHS Little Rock, Ark.	50000		WTYC Rock Hill, S.C.	1000d	WCPH Etowah, Tenn.	1000d	WNIA Cheektowaga, N.Y.	250			
WCRA Evingham, Ill.	250d		WSNW Seneca Township, South Carolina	1000d	WHEY Millington, Tenn.	250	WENY Elmira, N.Y.	1000			
KNWS Waterloo, Iowa	1000d		WAPD Chattanooga, Tenn.	5000	KVLL Livingston, Tex.	250d	WHUC Hudson, N.Y.	250			
WBAL Baltimore, Md.	50000		WCRK Morrilton, Tenn.	1000	KZEE Weatherford, Tex.	250d	WLFH Little Falls, N.Y.	250			
WILD Boston, Mass.	1000d		WTAW Bryan, Tex.	1000d	WLSO Big Stone Gap, Va.	1000d	WFAS White Plains, N.Y.	250			
WMUS Muskegon, Mich.	1000d		KCCT Corpus Christi, Tex.	1000d	WFAJ Falls Church, Va.	1000d	WASKY Asheville, N.C.	250			
KING Seattle, Wash.	50000		KIZZ El Paso, Tex.	1000d	KASY Auburn, Wash.	250d	WFAI Fayetteville, N.C.	250			
1100—272.6			KVIL Highland Park, Tex.	500d	KOZI Chelan, Wash.	1000d	WMFR High Point, N.C.	250			
KFAX San Francisco, Calif.	1000d		KJBC Midland, Tex.	1000d	1230—243.8		WISP Kingston, N.C.	250			
WLBB Carrollton, Ga.	250d		KPNG Port Neches, Tex.	1150	CFCW Camrose, Alta.	1000	WNNC Newton, N.C.	250			
WHLI Hempstead, N.Y.	10000d		KOLJ Quanah, Tex.	500d	CHFC Churchill, Man.	250	WCBT Roanoke Rap., N.C.	250			
KYW Cleveland, Ohio	50000		KOFE Pullman, Wash.	1000d	CFKL Schefferville, Que.	250	KOIX Dickinson, N.Dak.	250			
WGPA Bethlehem, Pa.	250d		KAYO Seattle, Wash.	5000	CFGR Gravelbourg, Sask.	250	WCPO Cincinnati, Ohio	250			
1110—270.1			KKEY Vancouver, Wash.	1000d	CFYT Dawson City, Yukon T.	100	WCOL Columbus, Ohio	250			
CFML Cornwall, Ont.	1000		WELC Welch, W.Va.	1000d	CFPA Port Arthur, Ont.	1000	WIRO Ironton, Ohio	250			
CFTJ Galt, Ont.	250		WAXX Chippewa Falls, Wis.	5000d	CKLO Thorford Mines, Que.	250	WTOL Toledo, Ohio	250			
KRLA Pasadena, Calif.	10000		WISN Milwaukee, Wis.	5000	CKMP Midland, Ont.	250	KAOA N. of Ada, Okla.	250			
WALT Tampa, Fla.	50000d		1160—258.5		VOAR St. John's, Nfld.	100	WBBZ Ponca City, Okla.	250			
KIPA Hilo, Hawaii	1000		WJJD Chicago, Ill.	50000	CKVD Val D'Or, Que.	250	KVAS Astoria, Oreg.	250			
WMBI Chicago, Ill.	5000d		KSL Salt Lake City, Utah	50000	WAUD Auburn, Ala.	250	KRNS Burns, Oreg.	250			
KFAB Omaha, Nebr.	50000		1170—256.3		WJBB Haleyville, Ala.	250	KDOS Coos Bay, Oreg.	250			
WBT Charlotte, N.C.	50000		CFNS Saskatoon, Sask.	1000	WBHP Huntsville, Ala.	250	KGRO Gresham, Oreg.	250			
KBND Bend, Oreg.	5000		WCOV Montgomery, Ala.	10000	WNUZ Talldega, Ala.	250	KYJC Medford, Oreg.	1000			
WNAR Norristown, Pa.	500d		KCBQ San Diego, Calif.	50000	WTBC Tuscaloosa, Ala.	250	KQIK Lakeview, Oreg.	250			
WVJP Caguas, P.R.	250		KLOK San Jose, Calif.	10000	KIFW Sitka, Alaska	250	KLUU Toledo, Oreg.	250			
WHIM Providence, R.I.	1000d		KOH0 Honolulu, Hawaii	1000	KSUN Bisbee, Ariz.	250	WBVP Beaver Falls, Pa.	250			
1120—267.7			WLBH Mattoon, Ill.	250d	KAAA Kingman, Ariz.	250	WEEX Easton, Pa.	250			
WUST Bethesda, Md.	250d		KSTT Davenport, Iowa	1000	KRIZ Phoenix, Ariz.	250	WKBO Harrisburg, Pa.	250			
KMDX St. Louis, Mo.	50000		KVOO Tulsa, Okla.	50000	KCON Conway, Ark.	250	WCRO Johnstown, Pa.	250			
WWOL Buffalo, N.Y.	1000d		WLEO Ponce, P.R.	250	KFPW Ft. Smith, Ark.	250	WBPZ Lock Haven, Pa.	250			
KCLE Cleburne, Tex.	250d		KPUG Bellingham, Wash.	1000	KBTM Jonesboro, Ark.	250	WNIC Arcibo, P.R.	250			
1130—265.3			WVVA Wheeling, W.Va.	50000	KGEE Bakersfield, Calif.	250	WERI Westerly, R.I.	250			
CKWX Vancouver, B.C.	50000		1180—254.1		KWTC Barstow, Calif.	250	WAIM Anderson, S.C.	250			
KSDO San Diego, Calif.	5000		WLDS Jacksonville, Ill.	1000d	KIBS Bishop, Calif.	250	WNOK Columbia, S.C.	250			
KWKH Shreveport, La.	50000		WHAM Rochester, N.Y.	50000	KXO El Centro, Calif.	250	WOLS Florence, S.C.	250			
WCAR Detroit, Mich.	50000		1190—252.0		KDAC Ft. Bragg, Calif.	250	KISD Sioux Falls, S.Dak.	250			
WDGY Minneapolis, Minn.	50000		KEZY Anahelm, Calif.	1000	KGFI Los Angeles, Calif.	250	WMMT McMinnville, Tenn.	250			
WNEW New York, N.Y.	50000		KNBA Vallejo, Calif.	250d	KPRL Paso Robles, Calif.	250	KSIX Corpus Christi, Tex.	250			
1140—263.0			WOWO Ft. Wayne, Ind.	50000	KRDG Redding, Calif.	250	KDLK Del Rio, Tex.	250			
CFTK Terrace, B.C.	1000		WANN Annapolis, Md.	10000d	KWG Stockton, Calif.	250	KNUZ Houston, Tex.	250			
CKXL Calgary, Alta.	10000		WKOX Fram'gham, Mass.	1000d	KEXO Grand Junc., Colo.	250	KERV Kerrville, Tex.	250			
KRAK Sacramento, Calif.	5000		WLIB New York, N.Y.	1000d	KLVC Leadville, Colo.	250	KLVT Levelland, Tex.	250			
WMIE Miami, Fla.	10000		KLIF Dallas, Tex.	50000	KDZA Pueblo, Colo.	250	KEEE Nacogdoches, Tex.	250			
KGEM Boise, Idaho	10000		1200—249.9		KGEK Sterling, Colo.	250	KOSA Odessa, Tex.	250			
WSIV Pekin, Ill.	1000d		WOAI San Antonio, Tex.	50000	WINF Manchester, Conn.	250	KHHH Pampa, Tex.	250			
KLPR Oklahoma City, Okla.	1000d		KDWT Stamford, Tex.	250	WGGG Gainesville, Fla.	250	KSEY Seymour, Tex.	250			
WITA San Juan, P.R.	500		1210—247.8		WONN Lakeland, Fla.	250	KCMC Texarkana, Tex.	250			
KS00 Sioux Falls, S.Dak.	10000		WCNT Centralia, Ill.	1000d	WMAF Madison, Fla.	250	KSST Sulphur Sprags., Tex.	250			
KORC Mineral Wells, Tex.	250		WKNX Saginaw, Mich.	10000d	WSBB New Smyrna Bch., Fla.	250	KWTX Waco, Tex.	250			
WRVA Richmond, Va.	50000		WADE Wadesboro, N.C.	1000d	WNVV Pensacola, Fla.	250	KMUR Murray, Utah	250			
1150—260.7			WAVI Dayton, Ohio	250d	WCNH Quincy, Fla.	250	KOAL Price, Utah	250			
CKSA Lloydminster, Alta.	1000		WCAU Philadelphia, Pa.	50000	WJNO W. Palm Beach, Fla.	250	WJOY Burlington, Vt.	250			
CKSJ Saint John, N.B.	10000		1220—245.8		WBIA Augusta, Ga.	250	WBI Abingdon, Va.	250			
CKOC Hamilton, Ont.	10000		CJOC Lethbridge, Alta.	10000	WBLJ Dalton, Ga.	250	WCFV Clifton Forge, Va.	250			
CKX Brandon, Man.	10000		CKDA Victoria, B.C.	10000	WCLI Dublin, Ga.	250d	WFVA Fredericksburg, Va.	250			
CKTR Three Rivers, Que.	5000		CJRL Kenora, Ont.	1000	WFOM Marietta, Ga.	250	WNOR Norfolk, Va.	250			
WBCA Bay Minette, Ala.	1000d		CKCW Moneton, N.B.	10000	WSOK Savannah, Ga.	250	KQTY Everett, Wash.	1000			
WGEA Geneva, Ala.	1000d		CJSS Cornwall, Ont.	1000	WAYX Waycross, Ga.	250	KLYK Spokane, Wash.	250			
			CKSM Shawinigan, Quebec	1000	KBAR Burley, Idaho	250	KREW Sunnyside, Wash.	250			
			WEZB Birmingham, Ala.	1000d	KORT Grangeville, Idaho	250	WLOG Logan, W.Va.	250			
			WPRN Butler, Ala.	1000d	KRXX Rexburg, Idaho	250	WTAP Parkersburg, W.Va.	250			
			KVSA McGee, Ark.	1000d	WJBC Bloomington, Ill.	250	WHBY Appleton, Wis.	250			
			KIBE Palm Alto, Calif.	1000d	WQUA MoLine, Ill.	250	WCLO Janesville, Wis.	250			
					WHCO Sparta, Ill.	250	WHVF Wausau, Wis.	250			
					WJOB Hammond, Ind.	250	KVOC Casper, Wyo.	250			
					WSAL Logansport, Ind.	250	1240—241.8				
					WTCJ Tell City, Ind.	250	CFLM La Tuque, Que.	1000			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KYNO	Fresno, Calif.	5000	KWHN	Fort Smith, Ark.	5000	CKAR-I	Parry Sound, Ont.	250	WKRZ	Oil City, Pa.	250
KWKW	Pasadena, Calif.	1000	KRLW	Walnut Ridge, Ark.	1000d	CKOX	Woodstock, Ont.	250	WHAT	Philadelphia, Pa.	250
KVOR	Colo. Sprgs., Colo.	1000	KHSJ	Hemet, Calif.	500d	WKUL	Cullman, Ala.	250	WRAP	Reading, Pa.	250
WAVZ	New Haven, Conn.	1000	KLAN	Lemoore, Calif.	1000d	WJ01	Florence, Ala.	250	WTRN	Tyrone, Pa.	250
WRKT	Cocoa Beach, Fla.	500d	KUDE	Oceanside, Calif.	500	WGCW	Selma, Ala.	250	WBRE	Wilkes-Barre, Pa.	250
WFFG	Marathon, Fla.	500d	KCRA	Sacramento, Calif.	5000	WFEB	Sylacauga, Ala.	250	WWPA	Williamsport, Pa.	250
WSOL	Tampa, Fla.	5000d	KAVI	Rocky Ford, Colo.	1000d	KIBH	Seward, Alaska	250	WGRF	Aguadilla, P.R.	250
WMTM	Moultrie, Ga.	5000d	WATR	Waterbury, Conn.	5000	KIKO	Miami, Ariz.	250	W0KE	Charleston, S.C.	250
WIMO	Winder, Ga.	1000d	WGMA	Hollywood, Fla.	1000d	KNOG	Nogales, Ariz.	250	WRHJ	Rock Hill, S.C.	250
KOZE	Lewiston, Idaho	5000	WZOK	Jacksonville, Fla.	5000	KPGE	Page, Ariz.	250	WSSC	Sumter, S.C.	250
WTAQ	LaGrange, Ill.	500	WAMR	Venice, Fla.	500d	KZOK	Prescott, Ariz.	250	KIJV	Huron, S.D.	250
WFRX	W. Frankfort, Ill.	1000d	WHIE	Griffin, Ga.	5000d	KBTA	Batesville, Ark.	250	KRSD	Rapid City, S.Dak.	250
WHLT	Huntington, Ind.	500d	WNEG	Toccoa, Ga.	1000d	KBRS	Springdale, Ark.	250	WBAC	Cleveland, Tenn.	250
WMFT	Terre Haute, Ind.	500d	WKAN	Kankakee, Ill.	1000d	KENL	Arcata, Calif.	250	WKRM	Columbia, Tenn.	250
KGLO	Mason City, Iowa	5000	KNIA	Knoxville, Iowa	500d	KMAK	Fresno, Calif.	250	WGRV	Greeneville, Tenn.	250
WBLG	Lexington, Ky.	1000	KMAQ	Maquoketa, Iowa	500d	KDOL	Mojave, Calif.	250	WKGN	Knoxville, Tenn.	250
WIBR	Baton Rouge, La.	1000	KLWN	Lawrence, Kans.	500d	KSFE	Needles, Calif.	250	WHHM	Memphis, Tenn.	250
KANB	Shreveport, La.	1000d	WBRT	Bardstow, Ky.	1000d	KATY	San Luis Obispo, Calif.	250	WCDT	Winchester, Tenn.	250
WFBR	Baltimore, Md.	5000	WNGO	Mayfield, Ky.	1000d	KIST	Santa Barbara, Calif.	250	KWKC	Abilene, Tex.	250
WJDA	Quincy, Mass.	1000d	KVHL	Homer, La.	1000d	KOMY	Watsonville, Calif.	250	KAND	Corsicana, Tex.	250
WOOD	Grand Rapids, Mich.	5000	WICO	Salisbury, Md.	1000d	KDEN	Denver, Colo.	250	KSET	El Paso, Tex.	250
WRBC	Jackson, Miss.	5000	WARA	Attleboro, Mass.	1000	KVRH	Salida, Colo.	250	KDUB	Lubbock, Tex.	250
KMMO	Marshall, Mo.	1000d	WILS	Lansing, Mich.	5000	WNHC	New Haven, Conn.	250	KRBA	Lufkin, Tex.	250
KBRL	McCook, Nebr.	1000d	WDMJ	Marquette, Mich.	1000	W00K	Washington, D.C.	250	KPDN	Pampa, Tex.	250
KPTL	Carson City, Nev.	5000	WCPC	Houston, Miss.	5000d	WTAN	Clearwater, Fla.	250	KOLE	Port Arthur, Tex.	250
WAAT	Trenton, N.J.	250d	WRJW	Picayune, Miss.	5000d	WROD	Daytona Bch., Fla.	250	KTXL	San Angelo, Tex.	250
WOSC	Fulton, N.Y.	1000d	KXLW	Clayton, Mo.	1000d	WDSR	Lake City, Fla.	250	KVIC	N. of Victoria, Tex.	250
WGOL	Goldsboro, N.C.	1000d	KOLT	Scottsbluff, Nebr.	5000	WTYS	Marlanna, Fla.	250	WTWN	St. Johnsbury, Vt.	250
WSYD	Mt. Airy, N.C.	5000	WWHG	Hornell, N.Y.	5000d	WQXT	Palm Beach, Fla.	250	WKEY	Covington, Va.	1000
WERE	Cleveland, Ohio	5000	WAGY	Forest City, N.C.	500d	WSEB	Sebring, Fla.	250	WHAP	Hopewell, Va.	250
WMVO	Mt. Vernon, Ohio	500	WCOG	Greensboro, N.C.	5000	WNSM	Valparaiso-Niceville, Fla.	250	WJMA	Orange, Va.	250
KOME	Tulsa, Okla.	5000	KQDY	Minot, N.Dak.	1000d	WGAU	Athens, Ga.	250	KAGT	Anacortes, Wash.	250
KDOV	Medford, Oreg.	5000d	WHOK	Lancaster, Ohio	1000d	WAKE	Atlanta, Ga.	250	KPKW	Pasco, Wash.	250
KACI	The Dalles, Oreg.	1000d	KW0E	Clinton, Okla.	1000d	WBBQ	Augusta, Ga.	250	KAPA	Raymond, Wash.	250
WWCH	Clarion, Pa.	500d	WKAP	Allentown, Pa.	1000	WGAA	Cedartown, Ga.	250	KMEL	Wenatchee, Wash.	250
WTLI	Mayaguez, P.R.	1000	WGET	Gettysburg, Pa.	250	W0KS	Columbus, Ga.	250	WHAR	Clarksburg, W.Va.	250
WCKI	Greer, S.C.	1000d	WAMP	Pittsburgh, Pa.	5000	WBBT	Lyons, Ga.	250	WEPM	Martinsburg, W.Va.	250
KOLY	Mobridge, S.Dak.	1000d	WSCR	Scranton, Pa.	1000	WTIF	Tifton, Ga.	250	WMON	Montgomery, W.Va.	250
WMTN	Morristown, Tenn.	5000d	WRIO	Rio Piedras, P.R.	5000	KPST	Preston, Idaho	250	W0VE	Welch, W.Va.	250
WMAK	Nashville, Tenn.	5000	WMSC	Columbia, S.C.	1000	KSKI	Sun Valley, Idaho	250	WLDY	Ladysmith, Wis.	1000
KVET	Austin, Tex.	1000	KELO	Sioux Falls, S.Dak.	5000	WSOY	Decatur, Ill.	250	WRIT	Milwaukee, Wis.	250
KTFY	Brownfield, Tex.	1000d	WKIN	Kingsport, Tenn.	5000d	WJPF	Herrin, Ill.	250	KWOR	Worland, Wyo.	250
KKAS	Silsbee, Tex.	500d	WMSR	Manchester, Tenn.	1000d	WJOL	Joliet, Ill.	250			
KOL	Seattle, Wash.	5000	KVMC	Colo. City, Tex.	1000d	WBIW	Bedford, Ind.	250	1350-222.1		
WCLG	Morgantown, W.Va.	1000d	KXYZ	Houston, Tex.	5000	WTRC	Elkhart, Ind.	250	CHOV	Pembroke, Ont.	1000
WKLC	St. Albans, W.Va.	1000d	KCPX	Salt Lake City, Utah	5000	WLBC	Muncie, Ind.	250	CJDC	Dawson Creek, B.C.	1000
			WEET	Richmond, Va.	1000d	KROS	Clinton, Iowa	250	CJLM	Joliette, Que.	1000
			KXRO	Aberdeen, Wash.	1000	KLIL	Estherville, Iowa	250	CHGB	St. Anne de la Pocatiere, Que.	1000
			KHIT	Walla Walla, Wash.	1000d	KCKN	Kansas City, Kans.	250	CKLB	Oshawa, Ont.	1000d
			WQMN	Superior, Wis.	1000d	KSEK	Pittsburg, Kans.	250	CKEN	Kentville, N.S.	1000
			WFHR	Wisconsin Rapids, Wis.	5000	W0MI	Ashland, Ky.	250	WELB	Elba, Ala.	1000d
1310-228.9						W0BN	Bowling Green, Ky.	250	WGAD	Gadsden, Ala.	5000
CKOY	Ottawa, Ont.	5000	1330-225.4			W0BS	Murray, Ky.	250	KAAB	Hot Springs, Ark.	1000
CJRH	Richmond Hill, Ont.	1000	WROS	Scottsboro, Ala.	1000d	W0KY	Richmond, Ky.	250	KLYD	Bakersfield, Calif.	1000d
WHEP	Foley, Ala.	1000d	KMOP	Tucson, Ariz.	500d	KV0B	Bastrop, La.	250	KCKC	San Bernardino, Calif.	500
WJAM	Marion, Ala.	5000d	KFAC	Los Angeles, Calif.	5000	KRMD	Shreveport, La.	250	KSRO	Santa Rosa, Calif.	1000
KBUZ	Mesa, Ariz.	5000	WARN	Ft. Pierce, Fla.	1000d	WFAU	Augusta, Maine	1000	KGHF	Pueblo, Colo.	5000
KBOK	Malvern, Ark.	1000d	WYSE	Lakeland, Fla.	1000d	WHOU	Houlton, Maine	250	WNLK	Norwalk, Conn.	500
KPOD	Crescent City, Calif.	1000d	W0BY	Milton, Fla.	5000d	WGAW	Gardner, Mass.	250	WINY	Putnam, Conn.	1000d
KDIA	Oakland, Calif.	1000	WMEN	Tallahassee, Fla.	5000d	WNBH	New Bedford, Mass.	250	WEZY	Cocoa, Fla.	1000
KTKR	Taft, Calif.	500d	WMLT	Dublin, Ga.	5000d	WBRK	Pittsfield, Mass.	250	WDCF	Dade City, Fla.	1000d
KFKA	Greeley, Colo.	1000	WEAW	Evanston, Ill.	1000d	WLEW	Bad Axe, Mich.	250	WRPB	Warner Robins, Ga.	1000d
WICH	Norwich, Conn.	1000	WRAM	Monmouth, Ill.	1000d	WLAV	Grand Rap., Mich.	250	KRLC	Lewiston, Idaho	5000
W000	Deland, Fla.	5000d	WRRR	Rockford, Ill.	1000d	WCSR	Hillsdale, Mich.	100	WAAP	Peoria, Ill.	1000
WAUC	Wauchula, Fla.	500d	WJPS	Evansville, Ind.	5000	W0TE	Manistee, Mich.	250	WJBD	Salem, Ill.	500d
WBRO	Waynesboro, Ga.	1000d	KFWL	Waterloo, Iowa	5000	WAGN	Menominee, Mich.	250	WIOU	Kokomo, Ind.	1000
WBMK	West Point, Ga.	1000	W0HL	Wichita, Kans.	5000	WMBN	Potosky, Mich.	250	KRNT	Des Moines, Iowa	5000
KLIX	Twin Falls, Idaho	5000	WMOR	Morehead, Ky.	1000d	WEXL	Royal Oak, Mich.	250	KMAN	Manhattan, Kans.	500d
WISH	Indianapolis, Ind.	5000	KVOL	Lafayette, La.	1000	KDLM	Oetroit Lakes, Minn.	250	WLOU	Louisville, Ky.	5000d
K0KX	Keokuk, Iowa	1000	WASA	Harve deGrace, Md.	1000d	WEVE	Eveleth, Minn.	250	WSMB	New Orleans, La.	5000
WTTL	Madisonville, Ky.	500d	WCRB	Waltham, Mass.	5000	KROC	Rochester, Minn.	1000	WDEA	Ellsworth, Me.	1000d
W00C	Prestonsburg, Ky.	5000d	WTRX	Flint, Mich.	5000	KWLM	Willmar, Minn.	250	WHMI	Howell, Mich.	500
KIKS	Sulphur, La.	500	WL0L	Minneapolis, Minn.	5000	WJMB	Brookhaven, Miss.	250	KDIO	Ortonville, Minn.	1000d
KUZN	W. Monroe, La.	1000d	WCRR	Corinth, Miss.	500d	WAML	Laurel, Miss.	250	WCMP	Pine City, Minn.	1000d
WLOB	Portland, Maine	1000d	WJPR	Greenville, Miss.	1000	KX0E	Mexico, Mo.	250	WKOZ	Kosciusko, Miss.	5000d
W0RC	Worcester, Mass.	5000	WDAL	Meridian, Miss.	1000d	KSMO	Salem, Mo.	250	KCHR	Charleston, Mo.	1000d
WKMH	Dearborn, Mich.	5000	KUKU	Willow Springs, Mo.	500d	KICK	Springfield, Mo.	250	KBRX	O'Neill, Nebr.	1000d
WCCW	Traverse City, Mich.	1000d	KGAK	Gallup, N.Mex.	5000	KCAP	Helena, Mont.	250	WLNH	Laconia, N.H.	5000d
KRBI	St. Peter, Minn.	1000d	WEVD	New York, N.Y.	5000	KPRK	Livingston, Mont.	250	KABQ	Albuquerque, N.M.	5000
WXXX	Hattiesburg, Miss.	1000d	WPOW	New York, N.Y.	5000	KATL	Miles City, Mont.	250	WCBA	Corning, N.Y.	1000d
KFSB	Joplin, Mo.	5000	W0BO	Owego, N.Y.	1000d	KQTE	Missoula, Mont.	250	WRNY	Rome, N.Y.	500d
KFBB	Great Falls, Mont.	5000	WHAZ	Troy, N.Y.	1000	KFGT	Freemont, Nebr.	100	WHIP	Mooreville, N.C.	1000d
WJLK	Asbury Park, N.J.	250	WFIN	Findlay, Ohio	1000d	KGFW	Kearney, Nebr.	250	WLLY	Wilson, N.C.	1000d
WCAM	Camden, N.J.	250	WK0V	Wellston, Ohio	500d	KSID	Sidney, Nebr.	250	KQDI	Bismarck, N.D.	500d
KARA	Albuquerque, N.M.	1000d	KPOJ	Portland, Oreg.	5000	K0BK	Reno, Nev.	250	WADC	Akron, Ohio	500d
WVIP	Mt. Kisco, N.Y.	1000d	WBLF	Bellefonte, Pa.	500	WDCR	Hanover, N.H.	250	WCHI	Chillicothe, Ohio	500d
WTLB	Utica, N.Y.	1000	WICU	Erie, Pa.	5000	WMID	Atlantic City, N.J.	250	KRHD	Duncan, Okla.	250
WISE	Asheville, N.C.	5000	WLAT	Conway, S.C.	5000d	KNDE	Aztec, N.M.	250	KTLO	Tahlequah, Okla.	1000d
WKTC	Charlotte, N.C.	1000	WFBC	Greenville, S.C.	5000	KYAP	Ruidoso, N.M.	250	WORK	York, Pa.	5000
WTKI	Durham, N.C.	1000	WAEW	Crossville, Tenn.	1000d	KSIL	Silver City, N.Mex.	1000	WDAR	Darlington, S.C.	500d
KNOX	Grand Forks, N.Dak.	5000	WTRO	Dyersburg, Tenn.	500d	WMBO	Auburn, N.Y.	1000	WGSW	Greenwood, S.C.	1000d
WFAH	Alliance, Ohio	1000d	KMIL	Cameron, Tex.	500d	WENT	Groversville, N.Y.	250	WRKM	Carthage, Tenn.	500d
KNPT	Newport, Oreg.	5000	KSWA	Graham, Tex.	500d	WJOC	Jamestown, N.Y.	250	KCAR	Clarksville, Tex.	500d
WBFD	Bedford, Pa.	1000d	KINE	Kingsville, Tex.	1000d	WUSJ	Lockport, N.Y.	250	KTJX	Jasper, Tex.	1000d
WGSA	Ephrata, Pa.	1000d	KVKM	Monahans, Tex.	1000	WMSA	Massena, N.Y.	250	KCOR	San Antonio, Tex.	5000
WNAE	Warren, Pa.	5000d	KDKK	Tyler, Tex.	1000d	WALL	Middletown, N.Y.	250	WBLT	Bedford, Va.	1000d
WDKD	Kingstree, S.C.	5000d	WBTM	Danville, Va.	5000	WIRY	Plattsburg, N.Y.	250	WFLS	Fredericksburg, Va.	500d
W00D	Chattanooga, Tenn.	5000	WESR	Tasley, Va.	1000d	WJRI	Lenoir, N.C.	250	WNVA	Norton, Va.	5000d
WDXI	Jackson, Tenn.	5000	KFKF	Bellevue, Wash.	1000d	WTSB	Lumberton, N.C.	250	WAVY	Portsmouth, Va.	5000
WBNT	Oneida, Tenn.	1000d	K0FA	Spokane, Wash.	5000d	W0XF	Oxford, N.C.	250	WPDR	Portage, Wis.	1000d
KZIP	Amarillo, Tex.	1000d	WETZ	New Martinsville, W.Va.	1000d	W00W	Greenville, N.C.	250			
WRR	Dallas, Tex.	5000	WHBL	Sheboygan, Wis.	1000	WGNI	Wilmington				

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WINT	Winter Haven, Fla.	1000d	WLCY	St. Petersburg, Fla.	5000	KXIV	Phoenix, Ariz.	250	WHAL	Shelbyville, Tenn.	250
WAZA	Bainbridge, Ga.	1000d	WAOK	Atlanta, Ga.	5000	KTUC	Tucson, Ariz.	250	KRUN	Ballinger, Tex.	250
WLaw	Lawrenceville, Ga.	1000d	WRWH	Cleveland, Ga.	5000	KVOY	Yuma, Ariz.	250	KBYG	Big Spring, Tex.	100
WLBK	DeKalb, Ill.	500d	KPOI	Honolulu, Hawaii	5000	KELD	El Dorado, Ark.	250	KUNO	Corpus Christi, Tex.	250
WVMC	Mt. Carmel, Ill.	500d	WITE	Brazil, Ind.	5000	KCLA	Pine Bluff, Ark.	250	KILE	nr. Galveston, Tex.	250
KHAK	Cedar Rapids, Iowa	1000d	WKJG	Ft. Wayne, Ind.	5000	KWYN	Wynne, Ark.	250	KGVL	Greenville, Tex.	250
KXGI	Ft. Madison, Iowa	1000d	KCIM	Carroll, Iowa	1000	KRE	Berkeley, Calif.	250	KEBE	Jacksonville, Tex.	250
KSCJ	Sioux City, Iowa	5000	WMTA	Central City, Ky.	500d	KREO	Indio, Calif.	250	KIUN	Pecos, Tex.	250
KBTO	El Dorado, Kans.	500d	WWKY	Winchester, Ky.	1000d	KSDA	Redding, Calif.	250	KEYE	Perryton, Tex.	250
WFLW	Monticello, Ky.	1000d	WYNK	Baton Rouge, La.	500d	KSLY	San Luis Obispo, Cal.	250	KVOP	Plainview, Tex.	250
KOBC	Mansfield, La.	1000d	WKTJ	Farmington, Me.	1000d	KSPA	Santa Paula, Calif.	250	KTEM	Temple, Tex.	250
KVIM	New Iberia, La.	1000d	WTTH	Port Huron, Mich.	1000	KHOE	Truckee, Calif.	1400	KTFS	Texarkana, Tex.	250
KTLD	Tallulah, La.	500d	WPLB	Greenville, Mich.	500d	KUKI	Ukiah, Calif.	250	KVOU	Uvalde, Tex.	250
WEBB	Dundalk, Md.	5000d	KLIZ	Brainerd, Minn.	1000d	KONG	Visalia, Calif.	250	KIXX	Provo, Utah	250
WLYN	Lynn, Mass.	1000d	KAGE	Winona, Minn.	1000d	KRLN	Canon City, Colo.	250	WDOT	Burlington, Vt.	250
WKMI	Kalamazoo, Mich.	5000	WDLT	Indianola, Miss.	500d	KDTA	Delta, Colo.	250	WINA	Charlottesville, Va.	250
KLRS	Mountain Grove, Mo.	1000d	KUDL	Kansas City, Mo.	1000d	KFTM	Ft. Morgan, Colo.	250	WLOW	Portsmouth, Va.	250
WNNJ	Newton, N.J.	1000d	KWK	St. Louis, Mo.	5000	KBZZ	La Junta, Colo.	250	WHLF	So. Boston, Va.	1000
WVWZ	Vineand, N.J.	1000	KUVR	Holdrege, Nebr.	500d	WSTC	Stamford, Conn.	250	WINC	Winchester, Va.	250
WKOP	Binghamton, N.Y.	5000	WBBX	Portsmouth, N.H.	1000d	WILI	Willimantic, Conn.	250	KWLK	Longview, Wash.	250
WMNS	Olean, N.Y.	1000d	WAWZ	Zarephath, N.J.	5000	WFTL	Ft. Lauderdale, Fla.	250	KRSC	Othello, Wash.	250
WCHL	Chapel Hill, N.C.	1000d	WBNX	New York, N.Y.	5000	WIRA	Ft. Pierce, Fla.	250	KTNT	Tacoma, Wash.	250
KEYZ	Williston, N.D.	5000	WLOS	Asheville, N.C.	5000	WRHC	Jacksonville, Fla.	250	WCAW	Charleston, W.Va.	250
WSAI	Cincinnati, Ohio	5000	WTOB	Winston-Salem, N.C.	5000	WPRY	Perry, Fla.	250	WBOY	Clarksburg, W.Va.	250
WVOW	Conneaut, Ohio	500d	WWIZ	Lorain, Ohio	500d	WTRR	Sanford, Fla.	250	WRON	Clarksburg, W.Va.	250
KUIK	Hillsboro, Oreg.	1000d	WPKO	Waverly, Ohio	1000d	WCQS	Alma, Ga.	250	WKWK	Wheeling, W.Va.	250
WMCK	McKeesport, Pa.	1000	KSWO	Lawton, Okla.	1000	WSGC	Elberton, Ga.	250	WBTH	Williamson, W.Va.	250
WPPA	Pottsville, Pa.	1000	KMUS	Muskogee, Okla.	1000	WNEX	Macon, Ga.	250	WATW	Ashland, Wis.	250
WELP	Easley, S.C.	1000d	KBCH	Ocean Lake, Oreg.	1000d	WMGA	Moultrie, Ga.	250	WBIZ	Eau Claire, Wis.	250
WLCM	Lancaster, S.C.	1000d	KSRV	Ontario, Oreg.	5000	WCOH	Newnan, Ga.	250	WDUZ	Green Bay, Wis.	250
WNAH	Nashville, Tenn.	1000d	WACB	Kittanning, Pa.	1000d	WGSA	Savannah, Ga.	250	WRJN	Racine, Wis.	250
KRAY	Amarillo, Tex.	500d	WARC	Milton, Pa.	1000d	KART	Jerome, Idaho	250	WRDB	Reedsburg, Wis.	250
KACT	Andrews, Tex.	1000d	WAYZ	Waynesboro, Pa.	1000d	KRPL	Moscow, Idaho	250	WRIG	Wausau, Wis.	250
KWBA	Baytown, Tex.	1000	WNRI	Woonsocket, R.I.	1000d	KSPT	Sandpoint, Idaho	250	KATI	Caspar, Wyo.	250
KRYS	Corpus Christi, Tex.	1000	WAGS	Bishopville, S.C.	1000d	WDSW	Champaign, Ill.	250	KODI	Cody, Wyo.	250
KXOL	Ft. Worth, Tex.	5000	WGUS	N. Augusta, S.C.	500	WGIL	Galesburg, Ill.	250			
WBOB	Galax, Va.	1000d	KOTA	Rapid City, S.Dak.	5000	WEOA	Evansville, Ind.	250			
WHBG	Harrisonburg, Va.	5000d	KJET	Beaumont, Tex.	1000d	WBAT	Marion, Ind.	250			
KFDR	Grand Coulee, Wash.	1000d	KBWD	Brownwood, Tex.	1000	KCOG	Centerville, Iowa	100			
KMO	Tacoma, Wash.	5000	KCRN	Crane, Tex.	1000d	KVFD	Fort Dodge, Iowa	250	CFUN	Vancouver, B.C.	1000d
WHJC	Matawan, W.Va.	1000d	KTSM	El Paso, Tex.	1000	KVOE	Emporia, Kans.	250	CHLP	Montreal, Que.	1000d
WMOV	Ravenswood, W.Va.	1000d	KMUL	Muleshoe, Tex.	500d	KAYS	Hays, Kans.	250	WALA	Mobile, Ala.	5000
WBAY	Green Bay, Wis.	5000	KBOP	Pleasanton, Tex.	1000d	WCYN	Cynthiana, Ky.	100	WCHP	Tuscumbia, Ala.	500d
WISV	Virouqua, Wis.	500d	WSYB	Rutland, Vt.	5000	WIEL	Elizabethtown, Ky.	250	KTCS	Fort Smith, Ark.	500d
WMNE	Menomonie, Wis.	1000d	WMBG	Richmond, Va.	5000	WFTG	London, Ky.	250	KERN	Bakersfield, Calif.	500
KVRS	Rock Springs, Wyo.	1000	KRKO	Everett, Wash.	1000	WFPR	Hammond, La.	250	KRML	Carmel, Calif.	500d
			WBEL	Beloit, Wis.	5000	KAOK	Lake Charles, La.	250	KMYC	Marysville, Calif.	5000

1370—218.8

WBYE	Calera, Ala.	1000d
KTPA	Prescott, Ark.	500d
KBUC	Corona, Calif.	1000
KEEN	San Jose, Calif.	5000
KGEN	Tulare, Calif.	1000d
WHYS	Ocala, Fla.	1000d
WCOA	Pensacola, Fla.	5000
WAXE	Vero Beach, Fla.	1000d
WBGR	Jesup, Ga.	1000d
WFDR	Manchester, Ga.	1000d
WKLE	Washington, Ga.	1000d
WPRC	Lincoln, Ill.	500d
WTTS	Bloomington, Ind.	5000
WGRY	Gary, Ind.	500d
KDTH	Dubuque, Iowa	1000
KGNO	Dodge City, Kans.	5000
WGOH	Grayson, Ky.	5000d
WTKY	Tompkinsville, Ky.	1000d
KAPB	Marksville, La.	1000d
WKIK	Leonardtown, Md.	1000d
WGHN	Grand Haven, Mich.	500d
KSUM	Fairmont, Minn.	1000
WDOB	Canton, Miss.	1000d
KWRT	Boonville, Mo.	1000d
KCRV	Caruthersville, Mo.	1000d
KXLF	Butte, Mont.	5000
KAWL	York, Neb.	500d
WFEA	Manchester, N.H.	5000
WALK	Patchogue, N.Y.	500d
WSAY	Rochester, N.Y.	5000
WLTC	Gastonia, N.C.	1000d
WTAB	Tabor City, N.C.	5000d
KFJM	Grand Forks, N.D.	1000d
WSPD	Toledo, Ohio	5000
KAST	Astoria, Oreg.	1000
WOTR	Corry, Pa.	1000
WPAZ	Pottstown, Pa.	1000d
WKMC	Roaring Spgs., Pa.	1000d
WIVV	Vieques, P.R.	1000
WDEF	Chatanooga, Tenn.	5000
WDXE	Lawrenceburg, Tenn.	1000d
WRGS	Rogersville, Tenn.	1000d
KOKE	Austin, Tex.	1000d
KFRO	Longview, Tex.	1000
KUKO	Post, Tex.	500d
KSOP	Salt Lake City, Utah	1000d
WBTN	Bennington, Vt.	500d
WHEE	Martinsville, Va.	5000d
WJWS	South Hill, Va.	5000d
KPOR	Quincy, Wash.	1000d
WMOD	Moundsville, W.Va.	1000d
WCCN	Neillsville, Wis.	5000d
KVWO	Cheyenne, Wyo.	1000

1380—217.3

CFDA	Victoriaville, Que.	1000
CKPC	Brantford, Ont.	1000d
CKLC	Kingston, Ont.	5000
WGYV	Greenville, Ala.	1000d
KDXE	N. Little Rock, Ark.	1000d
KBYM	Lancaster, Calif.	1000d
KGMS	Sacramento, Calif.	1000
KSBB	Salinas, Calif.	5000
KFLJ	Walsenburg, Colo.	1000d
WAMS	Wilmington, Del.	1000
WLIZ	Lake Worth, Fla.	500d
WQXQ	Ormond Beh., Fla.	1000d

1390—215.7

CKLN	Nelson, B.C.	1000
WHMA	Anniston, Ala.	5000
KDQN	DeQueen, Ark.	500d
KAMO	Rogers, Ark.	1000d
KGER	Long Beach, Calif.	5000
KTUR	Turlock, Calif.	1000
KFML	Denver, Colo.	1000d
WAVP	Avon Park, Fla.	1000d
WGES	Chicago, Ill.	5000
WFIV	Fairfield, Ill.	500d
WJCD	Seymour, Ind.	1000d
KCLN	Clinton, Iowa	1000d
KCBC	Des Moines, Iowa	1000
KNCK	Concordia, Kans.	500d
WANY	Albany, Ky.	1000d
WKIC	Hazard, Ky.	5000d
KFRA	Franklin, La.	500d
KNOE	Monroe, La.	5000
WEGP	Presque Isle, Me.	5000d
WCAT	Orange, Mass.	1000d
WPLM	Plymouth, Mass.	5000d
WCER	Charlotte, Mich.	1000d
KRFO	Owatonna, Minn.	500d
WROA	Gulfport, Miss.	1000d
WQIC	Meridian, Miss.	5000d
KENN	Farmington, N.Mex.	5000
KHOB	Hobbs, N.Mex.	5000d
WEOK	Poughkeepsie, N.Y.	5000d
WRIV	Riverhead, N.Y.	1000d
WFBL	Syracuse, N.Y.	5000
WFNC	Fayetteville, N.C.	5000
WKRK	Murphy, N.C.	1000d
WEED	Rocky Mount, N.C.	5000
WADA	Shelby, N.C.	500d
KLPM	Minot, N.Dak.	5000
WHPH	Bellefontaine, Ohio	5000
WMPO	Middleport-Pomroy, Ohio	1000d
WFMJ	Youngstown, Ohio	5000
KCRC	Enid, Okla.	1000
KSLM	Salem, Oreg.	5000
WLAN	Lancaster, Pa.	1000
WHPB	Belton, S.C.	500d
WCSC	Charleston, S.C.	5000
KJAM	Madison, S.D.	1000d
WTJS	Jackson, Tenn.	5000
KULP	El Campo, Tex.	500d
KBEC	Waxahachie, Tex.	500d
KLGN	Logan, Utah	500
WEAM	Arlington, Va.	5000
WVOD	Lynchburg, Va.	5000
KLOQ	Yakima, Wash.	1000
WTMB	Tomah, Wis.	500d

1400—214.2

CKBC	Bathurst, N.B.	250
CKDH	Amherst, N.S.	250
CKCY	Sault Ste. Marie, Ont.	250
CJFP	Riviere-du-Loup, Que.	1000
CKRN	Rouyn, Que.	250
CKSW	Swift Current, Sask.	250
WMSL	Decatur, Ala.	250
WXAL	Demopolis, Ala.	250
WFPA	Ft. Payne, Ala.	250
WJLD	Homewood, Ala.	250
WJHO	Opelika, Ala.	250
KSEW	Sitka, Alaska	250
KCLF	Clifton, Ariz.	250

KXIV	Phoenix, Ariz.	250
KTUC	Tucson, Ariz.	250
KVOY	Yuma, Ariz.	250
KELD	El Dorado, Ark.	250
KCLA	Pine Bluff, Ark.	250
KWYN	Wynne, Ark.	250
KRE	Berkeley, Calif.	250
KREO	Indio, Calif.	250
KSDA	Redding, Calif.	250
KSLY	San Luis Obispo, Cal.	250
KSPA	Santa Paula, Calif.	250
KHOE	Truckee, Calif.	1400
KUKI	Ukiah, Calif.	250
KONG	Visalia, Calif.	250
KRLN	Canon City, Colo.	250
KDTA	Delta, Colo.	250
KFTM	Ft. Morgan, Colo.	250
KBZZ	La Junta, Colo.	250
WSTC	Stamford, Conn.	250
WILI	Willimantic, Conn.	250
WFTL	Ft. Lauderdale, Fla.	250
WIRA	Ft. Pierce, Fla.	250
WRHC	Jacksonville, Fla.	250
WPRY	Perry, Fla.	250
WTRR	Sanford, Fla.	250
WCQS	Alma, Ga.	250
WSGC	Elberton, Ga.	250
WNEX	Macon, Ga.	250
WMGA	Moultrie, Ga.	250
WCOH	Newnan, Ga.	250
WGSA	Savannah, Ga.	250
KART	Jerome, Idaho	250
KRPL	Moscow, Idaho	250
KSPT	Sandpoint, Idaho	250
WDSW	Champaign, Ill.	250
WGIL	Galesburg, Ill.	250
WEOA	Evansville, Ind.	250
WBAT	Marion, Ind.	250
KCOG	Centerville, Iowa	100
KVFD	Fort Dodge, Iowa	250
KVOE	Emporia, Kans.	250
KAYS	Hays, Kans.	250
WCYN	Cynthiana, Ky.	100
WIEL	Elizabethtown, Ky.	250
WFTG	London, Ky.	250
WFPR	Hammond, La.	250
KAOK	Lake Charles, La.	250
WRDO	Augusta, Maine	250
WIDE	Biddeford, Maine	250
WWIN	Baltimore, Md.	250
WALE	Fall River, Mass.	250
WLLH	Lowell, Mass.	250
WHMP	Northampton, Mass.	250
WELL	Battle Creek, Mich.	250
WJLB	Detroit, Mich.	250
WHDF	Houghton, Mich.	250
WMAB	Munising, Mich.	250
WSAM	Saginaw, Mich.	250
WSTM	St. Joseph, Mich.	250
WTCM	Traverse City, Mich.	250
KEYL	Long Prairie, Minn.	250
KMHL	Marshall, Minn.	250
WMIN	Mpls.-St. Paul, Minn.	250
WHLB	Virginia, Minn.	250
WBIP	Booneville, Miss.	250
WNAG	Grenada, Miss.	250
WFOR	Hattiesburg, Miss.	250
WJQS	Jackson, Miss.	250
WMBC	Macon, Miss.	250
KFRU	Columbia, Mo.	250
KSIM	Sikeston, Mo.	250
KTTG	Springfield, Mo.	250
KXGN	Glendive, Mont.	250
KARR	Great Falls, Mont.	1000
KCOV	Allamore, Nebr.	250
KLIN	Lincoln, Nebr.	250
KBMI	Henderson, Nev.	250
KWNA	Winnemucca, Nev.	250
WTSL	Hanover, N.H.	250
KGFL	Roswell, N. Mex.	250
KTRC	Santa Fe, N. Mex.	250
KCHS	Truth or Consequences, New Mexico	250
KTNM	Tucumcari, N. Mex.	250
WOND	Pleasantville, N.J.	250
WABY	Albany, N.Y.	1000
WBNY	Buffalo, N.Y.	250
WLSB	Ogdensburg, N.Y.	1000
WBMA	Beaufort, N.C.	250
WGBG	Greensboro, N.C.	250
WKDX	Hamlet, N.C.	250
WSIC	Statesville, N.C.	250
WLSE	Wallace, N.C.	250
WHCC	Waynesville, N.C.	250
WCNF	Weldon, N.C.	250
KEYJ	Jamestown, N.Dak.	250

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KLMS	Lincoln, Nebr.	1000	WCSS	Amsterdam, N.Y.	250	1540—195.0			KOLS	Pryor, Okla.	1000d
KLEW	Hobbs, N. Mex.	5000	WBTA	Batavia, N.Y.	250	ZNS	Nassau, B.W.I.	5000	KWAY	Forest Grove, Oreg.	1000d
WLEA	Hornell, N.Y.	1000d	WKNY	Kingston, N.Y.	250	KPOL	Los Angeles, Calif.	10000	KOHU	Hermiston, Oreg.	1000d
WHOM	New York, N.Y.	5000	WICY	Malone, N.Y.	250	WSMI	Litchfield, Ill.	1000d	WBUX	Doylstown, Pa.	1000d
WREM	Remsen, N.Y.	1000d	WDLG	Port Jervis, N.Y.	250	WBNL	Boonville, Ind.	250d	WSHH	Latrobe, Pa.	1000d
WWOK	Charlotte, N.C.	1000d	WOLF	Syracuse, N.Y.	250	WLOI	LaPorte, Ind.	250d	WFGN	Gaffney, S.C.	250d
WYRN	Louisburg, N.C.	500d	WSSB	Durham, N.C.	250	WXEL	Waterloo, Iowa	5000d	WLSG	Coris, S.C.	1000d
WMSJ	Sylva, N.C.	5000d	WFLB	Fayetteville, N.C.	250	KNEX	McPherson, Kans.	250d	WHLR	Centerville, Tenn.	1000d
WHBC	Canton, Ohio	5000	WLOE	Leaksville, N.C.	250	KLKC	Parsons, Kans.	250d	WCLE	Cleveland, Tenn.	1000d
WCIN	Cincinnati, Ohio	5000	WRNB	New Bern, N.C.	250	WDOH	Wheaton, Md.	250d	WTRB	Ripley, Tenn.	1000d
WTRA	Latrobe, Pa.	500d	WRMT	Rocky Mount, N.C.	250	WPTR	Albany, N.Y.	50000	KZOL	Farwell, Tex.	250d
WDAS	Philadelphia, Pa.	5000	WSTP	Salisbury, N.C.	250	WIFM	Elkin, N.C.	250d	KVLG	La Grange, Tex.	250d
WISL	Shamokin, Pa.	1000	KNDC	Hettinger, N.Dak.	250	WABQ	Cleveland, Ohio	1000d	KTER	Terrell, Tex.	250d
WLOK	Memphis, Tenn.	5000d	KOVC	Valley City, N.Dak.	250	WJMJ	Philadelphia, Pa.	50000d	WKIC	Salt Lake City, Utah	500d
KBOX	Dallas, Tex.	5000	WBEX	Chillicothe, Ohio	250	WPTS	Pittston, Pa.	1000d	WSWV	Pennington Gap, Va.	1000d
KLYL	Pasadena, Tex.	1000	WJMO	Cleveland Hgts., Ohio	250	WPME	Punxsutawney, Pa.	1000d	WYTI	Rocky Mount, Va.	1000d
KAPE	San Antonio, Tex.	500d	WOHI	E. Liverpool, Ohio	250	WADK	Newport, R.I.	1000d	WEER	Warrenton, W.Va.	500d
KONI	Spanish Fork, Utah	1000d	WMOA	Marietta, Ohio	250	KCUL	Ft. Worth, Tex.	10000	WAPL	Appleton, Wis.	1000d
WCFR	Springfield, Vt.	1000d	WMRN	Marion, Ohio	250	KGBC	Galveston, Tex.	1000			
WBBL	Richmond, Va.	5000	KWRW	Guthrie, Okla.	100	WTKM	Hartford, Wis.	500d			
WLEE	Richmond, Va.	5000	KBIX	Muskogee, Okla.	250						
WBLU	Salem, Va.	5000d	KBKR	Baker, Oreg.	250						
KVAN	Camas, Wash.	1000d	KRNR	Roseburg, Oreg.	250						
KAYG	Lakewood, Wash.	1000d	KBZY	Salem, Oreg.	250						
WISM	Madison, Wis.	5000	WESB	Bradford, Pa.	250						
KRAE	Cheyenne, Wyo.	1000d	WAZL	Hazleton, Pa.	250						

1490—201.2

CFRC	Kingston, Ont.	100	WMB	Wilmington, N.C.	250
CKCR	Kitchener, Ont.	250	WMD	Wilmington, N.C.	250
CKBM	Montmagny, Que.	250	WGCD	Chester, S.C.	250
WANA	Anniston, Ala.	250	WMRB	Greenville, S.C.	250
WAJF	Decatur, Ala.	250	KORN	Mitchell, S.Dak.	250
WRLD	Lawlett, Ala.	250	WOPI	Bristol, Tenn.	250
WHBB	Selma, Ala.	250	WDXB	Chattanooga, Tenn.	250
KYCA	Prescott, Ariz.	1000	WROL	Fountain City, Tenn.	250
KAIR	Tucson, Ariz.	250	WJMJ	Lewisburg, Tenn.	250
KXAR	Hope, Ark.	250	WDXL	Lexington, Tenn.	250
KTLO	Mtn. Home, Ark.	250	KNOW	Austin, Tex.	250
KDRS	Paragould, Ark.	250	KIBL	Beeville, Tex.	250
KOTN	Pine Bluff, Ark.	250	KBST	Big Spring, Tex.	250
KXRJ	Russellville, Ark.	250	KHUZ	Borger, Tex.	250
KMAP	Bakersfield, Calif.	250	KNEL	Brady, Tex.	250
KPAS	Banning, Calif.	250	KSAM	Huntsville, Tex.	250
KBLA	Burbank, Calif.	250	KVOZ	Laredo, Tex.	250
KICO	Calxico, Calif.	250	KZZN	Littlefield, Tex.	250
KOWL	Lake Tahoe, Calif.	250	KPLT	Paris, Tex.	250
KAFP	Petaluma, Calif.	250	KGKB	Tyler, Tex.	250
KBLF	Red Bluff, Calif.	250	KVWC	Vernon, Tex.	250
KDB	Santa Barbara, Calif.	250	KVOG	Ogden, Utah	250
KSYC	Yreka, Calif.	250	WKVT	Brattleboro, Vt.	250
KBOL	Boulder, Colo.	250	WKE	Newport, Vt.	250
KRUC	Gunnison, Colo.	250	WCVA	Culpeper, Va.	250
KCMS	Manitou Sprgs., Colo.	100	WVEC	Hampton, Va.	250
KOLR	Sterling, Colo.	250	WAYB	Waynesboro, Va.	250
WNLC	New London, Conn.	250	KBRO	Bremerton, Wash.	250
WTOR	Torrington, Conn.	250	KLOG	Kelso, Wash.	250
WTRL	Bradenton, Fla.	250	KENE	Toppenish, Wash.	250
WJBS	DeLand, Fla.	250	KTEL	Walla Walla, Wash.	250
WMET	Miami Beach, Fla.	250	WHMS	Charleston, W.Va.	250
WSRA	Milton, Fla.	250	WTCS	Fairmont, W.Va.	250
WRGR	Starke, Fla.	250	WLOH	Princeton, W.Va.	250
WTTB	Vero Beach, Fla.	250	WGEZ	Belolt, Wis.	250
WSIR	Winter Haven, Fla.	250	WLCX	LaCrosse, Wis.	250
WMOG	Brunswick, Ga.	250	WIGM	Medford, Wis.	250
WMJM	Cordele, Ga.	250	WOSH	Oshkosh, Wis.	250
WMRE	Monroe, Ga.	250	KIML	Gillette, Wyo.	250
WSFB	Quitman, Ga.	250	KRTR	Thermopolis, Wyo.	250
WSNT	Sandersville, Ga.	250	KGOS	Torrington, Wyo.	250
WSYL	Sylvania, Ga.	250			
KTOH	Lihue, Hawaii	250			
KCID	Caldwell, Idaho	250			
WKRO	Cairo, Ill.	250			
WOAN	Danville, Ill.	250			
WAMV	East St. Louis, Ill.	250			
WOPA	Oak Park, Ill.	250			
WKBY	Richmond, Ind.	250			
WNUD	South Bend, Ind.	250			
KBUR	Burlington, Iowa	250			
WDBQ	Dubuque, Iowa	250			
KRIB	Mason City, Iowa	250			
KKAN	Phillipsburg, Kans.	250			
KTOP	Topeka, Kans.	250			
WFKY	Frankfort, Ky.	250			
WKAY	Glasgow, Ky.	250			
WOMI	Owensboro, Ky.	250			
WSIP	Paintsville, Ky.	1000			
WIKC	Bogalusa, La.	250			
KEUN	Eunlee, La.	250			
KCIL	Houma, La.	250			
KRUS	Ruston, La.	250			
WPOR	Portland, Maine	250			
WTVL	Waterville, Maine	250			
WARK	Hagerstown, Md.	250			
WHAV	Haverhill, Mass.	250			
WMRC	Milford, Mass.	250			
WTXL	W. Springfield, Mass.	250			
WABJ	Adrian, Mich.	250			
WCBQ	Fremont, Mich.	250			
WMDN	Midland, Mich.	250			
KXRA	Alexandria, Minn.	250			
KOZY	Grand Rapids, Minn.	250			
KLGR	Redwd. Falls, Minn.	100			
WLOX	Biloxi, Miss.	250			
WCLD	Cleveland, Miss.	250			
WHOC	Philadelphia, Miss.	250			
WTUP	Tupelo, Miss.	250			
WVIM	Vicksburg, Miss.	250			
KDMO	Carthage, Mo.	250			
KTTR	Rolla, Mo.	250			
KDRO	Sedalia, Mo.	250			
KBOW	Butte, Mont.	1000			
KBON	Omaha, Nebr.	250			
WEMJ	Laconia, N.H.	250			
WLDB	Atlantic City, N.J.	250			
KRSN	Los Alamos, N.Mex.	250			
KRTN	Raton, N.Mex.	250			

WCSB	Wilmington, N.C.	250	WMB	Wilmington, N.C.	250
WMD	Wilmington, N.C.	250	WGCD	Chester, S.C.	250
WVBC	Wilmington, N.C.	250	WMRB	Greenville, S.C.	250
WVBC	Wilmington, N.C.	250	KORN	Mitchell, S.Dak.	250
WVBC	Wilmington, N.C.	250	WOPI	Bristol, Tenn.	250
WVBC	Wilmington, N.C.	250	WDXB	Chattanooga, Tenn.	250
WVBC	Wilmington, N.C.	250	WROL	Fountain City, Tenn.	250
WVBC	Wilmington, N.C.	250	WJMJ	Lewisburg, Tenn.	250
WVBC	Wilmington, N.C.	250	WDXL	Lexington, Tenn.	250
WVBC	Wilmington, N.C.	250	KNOW	Austin, Tex.	250
WVBC	Wilmington, N.C.	250	KIBL	Beeville, Tex.	250
WVBC	Wilmington, N.C.	250	KBST	Big Spring, Tex.	250
WVBC	Wilmington, N.C.	250	KHUZ	Borger, Tex.	250
WVBC	Wilmington, N.C.	250	KNEL	Brady, Tex.	250
WVBC	Wilmington, N.C.	250	KSAM	Huntsville, Tex.	250
WVBC	Wilmington, N.C.	250	KVOZ	Laredo, Tex.	250
WVBC	Wilmington, N.C.	250	KZZN	Littlefield, Tex.	250
WVBC	Wilmington, N.C.	250	KPLT	Paris, Tex.	250
WVBC	Wilmington, N.C.	250	KGKB	Tyler, Tex.	250
WVBC	Wilmington, N.C.	250	KVWC	Vernon, Tex.	250
WVBC	Wilmington, N.C.	250	KVOG	Ogden, Utah	250
WVBC	Wilmington, N.C.	250	WKVT	Brattleboro, Vt.	250
WVBC	Wilmington, N.C.	250	WKE	Newport, Vt.	250
WVBC	Wilmington, N.C.	250	WCVA	Culpeper, Va.	250
WVBC	Wilmington, N.C.	250	WVEC	Hampton, Va.	250
WVBC	Wilmington, N.C.	250	WAYB	Waynesboro, Va.	250
WVBC	Wilmington, N.C.	250	KBRO	Bremerton, Wash.	250
WVBC	Wilmington, N.C.	250	KLOG	Kelso, Wash.	250
WVBC	Wilmington, N.C.	250	KENE	Toppenish, Wash.	250
WVBC	Wilmington, N.C.	250	KTEL	Walla Walla, Wash.	250
WVBC	Wilmington, N.C.	250	WHMS	Charleston, W.Va.	250
WVBC	Wilmington, N.C.	250	WTCS	Fairmont, W.Va.	250
WVBC	Wilmington, N.C.	250	WLOH	Princeton, W.Va.	250
WVBC	Wilmington, N.C.	250	WGEZ	Belolt, Wis.	250
WVBC	Wilmington, N.C.	250	WLCX	LaCrosse, Wis.	250
WVBC	Wilmington, N.C.	250	WIGM	Medford, Wis.	250
WVBC	Wilmington, N.C.	250	WOSH	Oshkosh, Wis.	250
WVBC	Wilmington, N.C.	250	KIML	Gillette, Wyo.	250
WVBC	Wilmington, N.C.	250	KRTR	Thermopolis, Wyo.	250
WVBC	Wilmington, N.C.	250	KGOS	Torrington, Wyo.	250

1500—199.9

CHUC	Port Hope, Ont.	1000	WMB	Wilmington, N.C.	250
KXRX	San Jose, Calif.	1000	WGCD	Chester, S.C.	250
WTOP	Washington, D.C.	50000	WMRB	Greenville, S.C.	250
WKIZ	Key West, Fla.	250	KORN	Mitchell, S.Dak.	250
WJBK	Detroit, Mich.	10000	WOPI	Bristol, Tenn.	250
KSTP	St. Paul, Minn.	50000	WDXB	Chattanooga, Tenn.	250
WMNT	Manati, P.R.	250	WROL	Fountain City, Tenn.	250
KTXX	Sherman, Tex.	250	WJMJ	Lewisburg, Tenn.	250

1510—199.1

CKOT	Tillsonburg, Ont.	1000d	WMB	Wilmington, N.C.	250
KASK	Ontario, Calif.	1000	WGCD	Chester, S.C.	250
KTIM	San Rafael, Calif.	1000d	WMRB	Greenville, S.C.	250
KMOR	Littleton, Colo.	1000	KORN	Mitchell, S.Dak.	250
WKAI	Macon, Ill.	250d	WOPI	Bristol, Tenn.	250
WMEX	Boston, Mass.	5000	WDXB	Chattanooga, Tenn.	250
KANS	Independence, Mo.	1000d	WROL	Fountain City, Tenn.	250
WRAN	Dover, N.J.	1000	WJMJ	Lewisburg, Tenn.	250
WLAC	Nashville, Tenn.	50000	WDXL	Lexington, Tenn.	250
KCTX	Childress, Tex.	250d	KNOW	Austin, Tex.	250
KSTV	Stephenville, Tex.	250d	KIBL	Beeville, Tex.	250
KGA	Spokane, Wash.	50000	KBST	Big Spring, Tex.	250
WAUX	Waukesha, Wis.	250d	KHUZ	Borger, Tex.	250

1520—197.4

KACY	
------	--

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Berkeley, Calif.	KRE 1400	Bridgeton, N.J.	WSNJ 1240	Cedar Falls, Iowa	KCFI 1250	Clarksdale, Miss.	WROX 1450 M
Berkeley Springs, W.Va.	WCST 1010	Bridgewater, N.S.	CKBW 1000	Cedar Rapids, Iowa	KCRG 1600 M	Clarksville, Ark.	WKOL 1600
Berlin, N.H.	WMOU 1230	Brigham City, Utah	KBUH 800		KHAK 1360	Clarksville, Tenn.	KLYR 1360
Berry Hill, Tenn.	WVOL 1470	Brighton, Colo.	KBRN 800		KPIG 1450		WJZM 1400 M
Berryville, Ark.	KTCN 1480	Brinkley, Ark.	KBRI 1570		WMT 600 C		WDXN 540
Berwick, Pa.	WBRX 1280	Bristol, Conn.	WBIS 1440	Cedartown, Ga.	WGAA 1340	Clarksville, Tex.	KCAR 1350
Bessemer, Ala.	WYAM 1450	Bristol, Tenn.	WOPI 1490 N	Center, Tex.	KDET 930	Claxton, Ga.	WCLA 1470
Bethesda, Md.	WUST 1120	Bristol, Va.	WOCY 690 A	Centerville, Calif.	KBIF 900	Clayton, Ga.	WGHC 1570
Bethlehem, Pa.	WGPA 1100		WFHG 980 M	Centerville, Iowa	KCOG 1400	Clayton, Mo.	KXLU 1320
Biddeford, Maine	WIDE 1400 M	Brockton, Mass.	WBET 1460	Centerville, Tenn.	WHLP 1570		KFUO 850
Big Lake, Tex.	KBLT 1290	Brockville, Ont.	CFJR 1450	Centerville, Utah	KBBC 1600	Clayton, N.Mex.	KLMX 1450
Big Rapids, Mich.	WBRN 1460	Broken Bow, Nebr.	KCNI 1280	Central City, Ky.	WNES 1050	Clearfield, Pa.	WCXA 900
Big Sprg., Tex.	KBST 1490 A	Brookfield, Mo.	KGHM 1470		WMTA 1380	Clearwater, Fla.	WTAN 1340
	KHEM 1270	Brookhaven, Miss.	WCHJ 1470	Centralia, Ill.	WCNT 1210		WAZE 860
	KBYG 1400 M		WJMB 1340 M	Centralia & Chehalis, Wash.	KELA 1470	Cleburne, Tex.	KCLE 1120
Big Stone Gap, Va.	WLSD 1220	Brookings, Oreg.	KURY 910		WGLC 1580	Cleveland, Ga.	WRWH 1380
Biloxi, Miss.	WLOX 1490 M	Brookings, S.Dak.	KBRK 1430	Centerville, Miss.	KCSR 1450	Cleveland, Miss.	WCLD 1490
	WMI 570	Brookline, Mass.	WBOS 1600	Chadron, Nebr.	WCHA 800		WDSK 1410
Billings, Mont.	KBMY 1240 M	Brooksville, Fla.	WVJB 1450	Chambersburg, Pa.	WCBG 1590	Cleveland, Ohio	KYW 1100
	KGHL 790 N	Brownfield, Tex.	KTFY 1300		WDWS 1400 C		WDOK 1260 M
	KOOK 970 C	Brownsville, Tex.	KBOR 1600 A	Champaign, Ill.	KCRB 1460		WERE 1300
	KOYN 910	Brownwood, Tex.	KBWD 1380 M	Chanute, Kans.	WCHL 1360		WGAR 1220 C
	KURL 730		KEAN 1240	Chapel Hill, N.C.	WESL 940		WHK 1420
Binghamton, N.Y.	WINR 680 N	Brunswick, Ga.	WGIG 1440 A	Charleroi, Pa.	KCHA 1580		WABQ 1540
	WKOP 1360 M		WMOG 1490	Charles City, Iowa	WEIC 1270	Cleveland, Tenn.	WJW 850 N
	WNBF 1290 C	Brunswick, Maine	WCME 900	Charleston, Ill.	KCHR 1350		WBAC 1340 M
	WAPI 1070 N	Bryan, Tex.	KORA 1240 M	Charleston, Mo.	WCSC 1390 C	Cleveland, Tex.	KVLB 1410
Birmingham, Ala.	WBRC 960 A		WTAW 1150	Charleston, S.C.	WOKS 1340 A-M	Cleve. Hgts., Ohio	WJMO 1490 A
	WCRT 1260 A	Buckhannon, W.Va.	WBUC 1460		WPAL 730	Clewiston, Fla.	WSUG 1050
	WEZB 1220	Buffalo, N.Y.	WBEN 930 C		WQSN 1450		WOWY 1590
	WENN 1320 M		WBNY 1400	Charleston, W.Va.	WTMA 1250 N	Clifton, Ariz.	KCLF 1400 A
	WATV 900		WEBR 970 M		WCAW 680	Clifton Forge, Va.	WCFV 1230
	WGSN 610		WGR 550		WCHS 580 C	Clifton, Ill.	WHOW 1520
	WYDE 850		WKBW 1520 N		WHMS 1490 A	Clinton, Iowa	KCLN 1390
	WVOK 690		WWOL 1120 A		WKAZ 950 N		KROS 1340 M
Bisbee, Ariz.	KSUN 1230 A	Buffalo, Wyo.	KBBS 1450		WTIP 1240 M	Clinton, Mo.	KDKD 1280
Bishop, Calif.	KIBS 1230 A	Bufoed, Ga.	WDMF 1460		WCER 1390	Clinton, N.C.	WRRZ 880 A
Bishopville, S.C.	WAGS 1380	Burbank, Calif.	KBLA 1490		WBT 1110 C	Clinton, Okla.	KWOE 1320
Bismarck, N.Oak.	KFYR 550 N	Burley, Idaho	KBAR 1230 A-M	Charlotte, Mich.	WAYS 610 A	Clinton, S.C.	WPCC 1400
	KQDI 1350	Burlington, Iowa	KBUR 1490 A	Charlotte, N.C.	WGIV 1600	Cloquet, Minn.	WKLK 1230
		Burlington, N.C.	WBBB 920 M		WKTC 1310	Clovis, N.Mex.	KCLY 1240
Bismarck-Mandan, N.Dak.	KBOM 1270		WBAG 1150		WSOC 930 M		KVER 980
		Burlington, Vt.	WCAX 620 N		WIST 1240 N	Coachella, Calif.	KCHV 970
Black River Falls, Wis.	WWIS 1260		WDOT 1400	Charlottesville, Va.	WVOK 1480	Coalinga, Calif.	KBMX 1470
	KBLI 690	Burns, Oreg.	KRNS 1230		WCHV 1260 A	Coatesville, Pa.	WCOJ 1420
Blackfoot, Idaho	WKLK 1440	Butler, Ala.	WPRN 1220		WELK 1010	Cocoa, Fla.	WKKO 860
Blackstone, Va.	KLTR 1580	Butler, Pa.	WBUT 1050		WINA 1400 M	Cocoa Beach, Fla.	WRKT 1300
Blackwell, Okla.	KARI 550		WISR 680		WMEK 980	Cody, Wyo.	KODI 1400 A
Bfaine, Wash.	WBBK 1260	Butte, Mont.	KBDW 1490 C	Charlottetown, P.E.I.	WCFY 630	Coeur d'Alene, Ida.	KVNI 1240 M
Blakely, Ga.	KUTA 790		KOPR 550 M	Chase City, Va.	WMEK 980		KZIN 1050
Blanding, Utah	CJNR 730		KXLF 1370 N	Chatham, Ont.	CFCO 630	Coffeyville, Kans.	KGGF 690 A
Blind River, Ont.	WJBC 1230 A	Cabano, Que.	CJAF 1340	Chattanooga, Tenn.	WOGA 1450 M	Colby, Kans.	KXXX 790
Bloomington, Ill.	WTTS 1370 A	Cadillac, Mich.	WATT 1240 M		WAO 1150 A	Coldwater, Mich.	WTVB 1590
Bloomington, Ind.	WCNR 930	Caguas, P.R.	WNEL 1450		WDEF 1370 N	Coleman, Tex.	KSTA 1000
Bloomsburg, Pa.	WHLM 550		WVJP 1110		WDXB 1490	Colfax, Wash.	KCLX 1450
	WHIS 1440 N	Cairo, Ga.	WGRA 790		WNOO 1260	College Park, Ga.	WEAS 1570
Bluefield, W.Va.	WKOY 1240 M	Cairo, Ill.	WKRO 1490		WNOO 1260	Colonial Heights, Va.	WPVA 1290
	KYOB 1450 A	Calais, Maine	WQDY 1230 N	Cheboygan, Mich.	WCBY 1240		WPVA 1290
Blythe, Calif.	KLCM 910	Caldwell, Idaho	KCID 1490	Cheektowaga, N.Y.	WNIA 1230	Colorado City, Tex.	KVMC 1320
Blytheville, Ark.	WAVC 1300		KBGN 910	Chehalis, Wash.	KITI 1420	Colo. Sprgs., Colo.	KRDO 1240
Boaz, Ala.	WIKC 1490 N	Calera, Ala.	WBYE 1370	Chelan, Wash.	KOZI 1220		KPIK 1580
Bogalusa, La.	WBOX 920	Calixico, Calif.	KICO 1490 A	Cheraw, S.C.	WCRE 1420		KVOR 1300 C
	KBOI 950 C	Calgary, Alta.	CFAC 960	Cherokee, Iowa	KCHE 1440		KSSS 740
	KEST 790		CFCN 1060	Chester, Pa.	WEEZ 1590		KYSN 1460 M
	KGEM 1140 M		CKXL 1140		WVCH 740	Columbia, Ky.	WAIN 1270
	KIOO 630 N	Calhoun, Ga.	WCGA 900	Chester, S.C.	WGCD 1490	Columbia, Miss.	WCJU 1450 M
	KYME 740	Camas, Wash.	KVAN 1480	Cheyenne, Wyo.	KFCB 1240 A	Columbia, Mo.	KFRU 1400 A
Bonham, Tex.	KFYH 1420	Cambridge, Md.	WCEM 1240		KCHY 1590		KBIA 1580
Boone, Iowa	KFGQ 1260	Cambridge, Mass.	WTAO 740 A		KRAE 1480	Columbia, Pa.	WCOY 1580
	KWBG 1590	Cambridge, Ohio	WILE 1270		KVWO 1370 M	Columbia, S.C.	WCOS 1400 A
Boone, N.C.	WATA 1450	Camden, Ark.	KAMO 910	Chicago, Ill.	WAAF 950		WIS 560 N
Boonville, Ind.	WBNL 1540	Camden, N.J.	WCAM 1310		WAIT 820		WMSC 1320 C
Boonville, Mo.	KWRT 1370		WKDN 800		WBBM 780 C		WNOK 1230
Booneville, Miss.	WBIP 1400 A	Camden, S.C.	WACA 1590		WCFL 1000		WQIC 1470
Boonville, N.Y.	WBRV 900	Camden, Tenn.	WFWL 1220		WCRW 1240	Columbia, Tenn.	WMCP 1280
Borger, Tex.	KHUZ 1490 M	Cameron, Tex.	KMIL 1330		WEDC 1240		WKRM 1340
	KBBB 1600	Camilla, Ga.	WCLB 1220		WGES 1390	Columbus, Ga.	WDAK 540 N
	WBZ 1030	Campbell, Ohio	WHOT 1570		WGN 720 M		WRBL 1420 C
Boston, Mass.	WCOP 1150	Campbellsville, Ky.	WTCO 1450		WIND 560		WGBA 1270 M
	WILD 1090	Campbellton, N.B.	CKNB 950		WJJD 1180		WCLS 1580
	WNAC 680	Camrose, Alta.	CFCW 1230		WLS 890 A		WOKS 1340
	WEZE 1260 N	Canon City, Colo.	KRLN 1400 M		WMAQ 670 N		WCSI 1010
	WEEI 590 C	Canonsburg, Pa.	WCNG 540		WMBI 1110	Columbia, Ind.	WACR 1050
	WHOH 850	Canton, Ga.	WCHK 1290		WWSB 1240	Columbia, Miss.	WCBI 550 M
	WMEX 1510	Canton, Ill.	WBYS 1560		WCO 1600		KJSK 900
	WORL 950 M	Canton, Miss.	WDOB 1370	Chicago Hgts., Ill.	KWCO 1580	Columbia, Nebr.	WBNS 1460 C
Boulder, Colo.	KBOL 1490	Canton, N.C.	WWIT 970	Chickasha, Okla.	KHSL 1290	Columbia, Ohio	WCOL 1230 A
Bowie, Tex.	KBAN 1410	Canton, Ohio	WAND 900	Chico, Calif.	KPAY 1060		WMNI 920 A
Bowling Green, Ky.	WKCT 930 A		WCMW 1060	Chicago, Mass.	WACE 730		WOSU 820
	WBGN 1340		WHBC 1480 A	Chicoutimi, Que.	CBJ 1580		WTVN 610
	WLBJ 1410 M	Cape Girardeau, Mo.	KFVS 960		CJMT 1420		WVKO 1580
Bowl, Green, Ohio	WHRW 730		KGMO 1220	Childress, Tex.	KCTX 1510	Colville, Wash.	KCVL 1270
Bozeman, Mont.	KXXL 1450 N	Carbondale, Ill.	WCIL 1020	Chillicothe, Mo.	KCHI 1010	Commerce, Ga.	WJJC 1270
	KBMN 1230	Carbondale, Pa.	WCDL 1440	Chillicothe, Ohio	WBEX 1490	Concord, N.H.	WKXL 1450 C
Bradbury Hgts., Md.	WP6C 1580	Caribou, Maine	WFST 600		WCHI 1350	Concord, N.C.	WEGO 1410
Braddock, Pa.	WLOA 1550	Carlisle, Pa.	WHYL 960	Chilliwack, B.C.	CHWK 1270	Concordia, Kans.	KNCK 1390
Bradenton, Fla.	WTRL 1490	Carlsbad, N.Mex.	KAVE 1240 C	ChIPLEY, Fla.	WBGC 1240		KFRM 550 A
	WBRD 1420		KPBM 740	Chippawa Falls, Wis.	WAXX 1150	Conneaut, Ohio	WWOW 1360
Bradford, Pa.	WESB 1490 M		KRML 1410		WBCR 1260	Connellsville, Pa.	WCVI 1340
Brady, Tex.	KNEL 1490	Carmel, Calif.	WROY 1460	Christiansburg, Va.	WVIV 970	Connorsville, Ind.	WCNB 1580
Brainerd, Minn.	KLIZ 1380	Carmi, Ill.	WROY 1460	Christiansted, V.I.	WMCH 1260	Conroe, Tex.	KMCO 900
Brampton, Ont.	CHIC 1090	Carrizo Springs, Tex.	KBEN 1450	Church Hill, Tenn.	CHFC 1230	Conway, Ark.	KCON 1230
Brandon, Man.	CKX 1150	Carroll, Iowa	KCIM 1380	Churchill, Man.	WHFC 1450	Conway, N.H.	WBNC 1050
Branson, Mo.	KBHM 1220	Carrollton, Ala.	WRAG 580	Cicero, Ill.	WCKY 1530	Conway, S.C.	WLAT 1330 M
Brantford, Ont.	CKPC 1380	Carrollton, Ga.	WLBB 1100	Cincinnati, Ohio	WCIN 1480	Cookeville, Tenn.	WHUB 1400 C
Brattleboro, Vt.	WTSA 1450	Carrollton, Mo.	KAOL 1430		WCPO 1230	Coolidge, Ariz.	KCKY 1150 C
	WKYT 1490	Carson City, Nev.	KPTL 1300		WKRC 550 C	Coos Bay, Oreg.	KOOS 1230 M
Brawley, Calif.	KROP 1300 A	Cartersville, Ga.	WBHF 1450 M		WLW 700 N-A		KYNG 1420
Brazil, Ind.	WITE 1380	Carthage, Ill.	WCAZ 990	Christiansburg, Va.	WBSR 1260	Copper Hill, Tenn.	WLSB 1400
Breckenridge, Minn.	KBMW 1450	Carthage, Mo.	KDMO 1490	Christiansted, V.I.	WVIV 970	Codville, Oreg.	KWRO 630
Breckenridge, Tex.	KSTB 1430	Carthage, Tenn.	WRKM 1350	Church Hill, Tenn.	WMCH 1260	Coral Gables, Fla.	WVCG 1070
Bremen, Ga.	WWCC 1440	Carthage, Tex.	KGAS 1590	Churchill, Man.	CHFC 1230	Corbin, Ky.	WCTT 680 M
Bremerton, Wash.	KBRO 1490	Caruthersville, Mo.	KCRV 1370	Cicero, Ill.	WHFC 1450	Cordele, Ga.	WMJM 1490 M
Brenham, Tex.	KWHI 1280	Casa Grande, Ariz.	KPIN 1260		WCKY 1530	Cordova, Alaska	KLAM 1450
Brevard, N.C.	WPNF 1240 M-N	Casper, Wyo.	KTWO 1470		WCIN 1480		
Brewton, Ala.	WEBJ 1240 M		KATI 1400		WCPO 1230		
Bridgeport, Conn.	WICC 600 M		KVOC 1230 A-M	Clanton, Ala.	WKLF 980		
	WNAB 1450 A	Cayce, S.C.	WCAY 620	Ciarc, Mich.	WCRM 990		
		Cedar City, Utah	KSUB 590 C	Claremore, Okla.	KWPR 1270		
				Claremont, N.H.	WTSV 1230		
				Clarion, Pa.	WVCH 1300		
				Clarksburg, W.Va.	WBOY 1400 N		
					WHAR 1340 M		
					WPOX 750		

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.		
Corinth, Miss.	WCMA 1230 WCRR 1330	De Kalb, Ill.	WDSP 1280 WZEP 1460	Edmonton, Alta.	CBX 1010 CBXA 740	Farmville, N.C.	KZUM 1280 WBTL 1050		
Cornelia, Ga.	WCOR 1450	De Land, Fla.	WLKB 1360 WJBS 1490		CFRN 1260 CHED 1080	Farmville, Va.	WFLAG 1250 WFLO 870		
Corner Brook, Nfld.	CBY 560 CFCB 570	Delano, Calif.	WODD 1310 KCHJ 1010		CHFA 680 CJCA 930	Farrell, Pa.	WFAI 1470 KZDL 1570		
Corning, Ark.	KCCB 1260	Delaware, Ohio	WDLE 1550 WDBF 1420	Edmundston, N.C.	CKUA 580 CJEM 570	Farwell, Tex.	WWWF 990 KHOG 1440		
Corning, N.Y.	WCBA 1350 WCLI 1450 A	Delray, Beh., Fla.	KDLK 1230 Delta, Colo.	El Elngham, Ill.	WCRA 1090 WELB 1350	Fayetteville, Ala.	WFAI 1250 M WFNC 1390 M		
Cornwall, Ont.	CJSS 1220 CFML 1110	Deming, N.Mex.	KOTS 1230 Demopolis, Ala.	Elba, Ala.	WELB 1350 WSGC 1400	Fayetteville, Ark.	WFAI 1250 M WFNC 1390 M		
Corona, Calif.	KBUC 1370	Denham Sprgs., La.	WLBI 1220 Denison, Iowa	Eibertson, Ga.	KDEO 910 A El Cajon, Calif.	Fayetteville, N.C.	WFAI 1250 M WFNC 1390 M		
Corpus Christi, Tex.	KCTA 1030 M KCCT 1150 KEYS 1440 KRYS 1360 N KSIX 1230 A-C KUNO 1400	Denison, Iowa	KDSN 1580 Denison, Tex.	El Centro, Calif.	KULP 1390 KXO 1230 M KAMP 1430	Fayetteville, Tenn.	WEKR 1240 M		
Corry, Pa.	WOTR 1370	Denton, Tex.	KDSX 950 KDNT 1440 Denver, Colo.	El Dorado, Ark.	KDMS 1290 KELD 1400 A KBTO 1360	Fergus Falls, Minn.	KOTE 1250 M		
Corsicana, Tex.	KAND 1340	Des Moines, Iowa	KFML 1390 KHOW 630 A KIMN 950 M KLIR 990 KLZ 560 C KICN 710 KOA 850 N KPOF 910 KFSC 1220 KTLN 1280 KDQN 1390 KDLA 1010	Eldorado, Kans.	WRMN 1410	Fernandina Beach, Fla.	WPAP 1570 KFNV 1600 KXEN 1010 WFIN 1930 WELD 890 A WEIM 1280 M WFGM 960 WBHB 1240 M KCLS 600 N KVNA 690 A KEOS 1290		
Cortez, Colo.	KVFC 740	Des Moines, Iowa	KCBC 1390 A KIOA 940 KRNT 1350 C KSO 1460 KWKY 1150 M WHO 1040 N	Elgin, Ill.	WCNC 1240 WGAJ 560 WBEJ 1240 WIEL 1400	Ferriday, La.	WFMD 1240 M CFAR 590 WDFD 910 N WTRX 1330 A WAMM 1420 WMPR 1370 WKM 1470 WTAC 600 A WTCB 990 WJOI 1340 M WOWL 1240 A WJMX 970 A WOLS 1230 WYNN 540 KFLD 900 WHEP 1310 KFIZ 1450 M KBJT 1570 WMAG 860 WBBO 780 WAGY 1320 KWAY 1570 KXJK 950 KDAC 1230 KCOL 1410 KVFD 1400 M KWMT 540 A CFDB 800 WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Cortland, N.Y.	WKRT 920	Detroit, Mich.	WCAR 1130 WJBK 1500 WJLB 1400 WJR 760 WVJ 950 N WXYZ 1270 A	Elkhart, Ind.	WTRC 1340 N WCMR 1270 WIFM 1540 WDNE 1240 KELK 1240 M KXLE 1240 WDEA 1350 WELM 1410 A-C WENY 1290 N	Flat River, Mo.	WFMD 1240 M CFAR 590 WDFD 910 N WTRX 1330 A WAMM 1420 WMPR 1370 WKM 1470 WTAC 600 A WTCB 990 WJOI 1340 M WOWL 1240 A WJMX 970 A WOLS 1230 WYNN 540 KFLD 900 WHEP 1310 KFIZ 1450 M KBJT 1570 WMAG 860 WBBO 780 WAGY 1320 KWAY 1570 KXJK 950 KDAC 1230 KCOL 1410 KVFD 1400 M KWMT 540 A CFDB 800 WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Corvallis, Oreg.	KOAC 550 KFLY 1240 KLOO 1340	Detroit Lakes, Minn.	KOLM 1340	Elmira Heights-Horseheads, N.Y.	WEHH 1590 M KROD 600 KELP 920 KHEY 690 KINT 1590 KIZZ 1150 KSET 1340 M KTSM 1380 N WELY 1450 M KELY 1230 WEOL 930 WSTL 1600 WVOW 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Elmira, N.Y.	WELM 1410 A-C	Florence, Ala.	WJMI 1340 M WOWL 1240 A WJMX 970 A WOLS 1230 WYNN 540 KFLD 900 WHEP 1310 KFIZ 1450 M KBJT 1570 WMAG 860 WBBO 780 WAGY 1320 KWAY 1570 KXJK 950 KDAC 1230 KCOL 1410 KVFD 1400 M KWMT 540 A CFDB 800 WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150
Coshocton, Ohio	WTNS 1560	Devils Lake, N.Dak.	KDLR 1240 M KDEX 1590 KSPL 1260 KDIX 1230 WKN 1260 KDBM 800 WDSO 800 A KRDU 1240 KGNO 1370 WAGF 1320 WDIG 1450 M WDF 560 KAWT 1450 M KAPR 930 WDMG 860 KWIV 1050 WDOV 1410 WKEN 1600 WTSN 1270 WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	El Paso, Tex.	KROD 600 KELP 920 KHEY 690 KINT 1590 KIZZ 1150 KSET 1340 M KTSM 1380 N WELY 1450 M KELY 1230 WEOL 930 WSTL 1600 WVOW 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Florence, S.C.	WJMI 1340 M WOWL 1240 A WJMX 970 A WOLS 1230 WYNN 540 KFLD 900 WHEP 1310 KFIZ 1450 M KBJT 1570 WMAG 860 WBBO 780 WAGY 1320 KWAY 1570 KXJK 950 KDAC 1230 KCOL 1410 KVFD 1400 M KWMT 540 A CFDB 800 WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Cottage Grove, Ore.	KNND 1400	Douglas, Ariz.	KAWT 1450 M KAPR 930 WDMG 860 KWIV 1050 WDOV 1410 WKEN 1600 WTSN 1270 WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	El Paso, Tex.	KROD 600 KELP 920 KHEY 690 KINT 1590 KIZZ 1150 KSET 1340 M KTSM 1380 N WELY 1450 M KELY 1230 WEOL 930 WSTL 1600 WVOW 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Frances, Ont.	CFDB 800 WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Coudersport, Pa.	WFRM 600	Douglas, Ga.	WDMG 860 KWIV 1050 WDOV 1410 WKEN 1600 WTSN 1270 WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Enterprise, Ala.	WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Knox, Ky.	WSAC 1470 WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Council Bluffs, Iowa	KSWI 1560 M-A	Dover, Del.	WDOV 1410 WKEN 1600 WTSN 1270 WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Enterprise, Oreg.	KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Lauderdale, Fla.	WFTL 1400 WWIL 1580 KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Courtenay, B.C.	CFCP 1440	Dover, N.H.	WTSN 1270 WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Ely, Minn.	WELY 1450 M KELY 1230 WEOL 930 WSTL 1600 WVOW 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Madison, Iowa	KXGI 1360 KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Covington, Ga.	WGFS 1430	Dover, N.J.	WRAN 1510 WJER 1450 WDOW 1440 WBUX 1570 CJDV 910 CHR 1340 WMLT 1330 WXL 1230 WCED 1420 C KDT 1870 WDBQ 1490 KDAL 610 C WEBC 560 KDD 800 KRHD 1350 M WAYE 860 WEBB 1360 WFLR 1570 WDOE 1410 WCKB 780 WDQN 1580 KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Ely, Nev.	KELY 1230 WEOL 930 WSTL 1600 WVOW 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Morgan, Colo.	KFTM 1400 WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Covington, Ky.	WZIP 1050 M	Durango, Colo.	KIUP 930 KGO 1240 KSFO 750 WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Emporia, Kans.	KVOE 1400 WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Myers, Fla.	WINK 1240 C WMYR 1410 WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Covington, La.	WARB 730	Durham, N.C.	WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Emporia, Va.	WEVA 860 WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Payne, Ala.	WFPA 1400 WZOB 1250 WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Covington, Tenn.	WKBL 1250	Durham, N.C.	WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Emporium, Pa.	WLEM 1240 WENE 1430 A KGMG 1150 KCRC 1390 A KGWA 960 M WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340 WCPH 1220 WULA 1240 M KORE 1450 M KASH 1600 A KERG 1280 C KUGN 590 N KEUN 1490 M KINS 980 C KDN 790 KIEM 1480 M WLCO 1240 WEAW 1330 WNMP 1590 KLUK 1240 WEOA 1400 C WGBF 1280 N WIKY 820 WJPS 1330 A WEVE 1340 M KRKO 1360 KQTY 1230 WBLO 1470	Ft. Pierce, Fla.	WARN 1330 WIRA 1400 KMDO 1600 KFPW 1230 C KFSA 950 A KTCS 1410 M KWHN 1320 KFST 860 WFFM 1150		
Cowan, Tenn.	WZYX 1440	Durham, N.C.	WDNC 620 C WSRC 1410 WSSB 1490 WTK 1310 A WDSG 1450 WTRO 1330 KEPS 1270 WERL 950 WELP 1360	Enterprise, Ala.	WIRB 600 KWVR 1340 WGSA 1310 KULF 730 WERC 1260 A WICU 1330 N WJET 1400 WLEU 1450 WEMB 1420 WDBC 680 M WLST 600 A KOWN 1450 KLIL 1340				

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Millington, Tenn.	WHEY 1220	Mt. Pleasant, Mich.	WCEN 1150	New Richmond, Wis.	WIXK 1590	O'Neill, Nebr.	KBRX 1350
Millville, N.J.	WMBV 1440	Mt. Pleasant, Tex.	KIMP 960	New Rochelle, N.Y.	WVOX 1460	Oneonta, Ala.	WCRL 1570
Milton, Fla.	WEBC 1330 M	Mt. Shasta, Calif.	KWSD 820	New Smyrna Beach, Fla.	WSBB 1290 M	Ontario, N.Y.	WDOS 730
Milton, Pa.	WSRA 1490	Mt. Sterling, Ky.	WMST 1150	Newton, Iowa	WJRG 1280	Ontario, Calif.	KASK 1510
Milwaukee, Wis.	WMLP 1570	Mt. Vernon, Ill.	WMIX 940	Newton, Kans.	KJRG 950	Ontario, Oreg.	KSRV 1380
	WARC 1380	Mt. Vernon, Ind.	WPCO 1590	Newton, Miss.	WBKN 1410	Opelika, Ala.	WPHO 1400 M
	WEMP 1250	Mt. Vernon, Ky.	WRVK 1460	Newton, N.J.	WNNJ 1360	Opelousas, La.	KSLO 1230 A
	WFOX 860 M	Mt. Vernon, Ohio	WMVO 1300	Newton, N.C.	WNNC 1230	Opp, Ala.	WAMI 860
	WRIT 1340	Mt. Vernon, Wash.	KBRC 1430	New Ulm, Minn.	KNUJ 860	Opportunity, Wash.	WZUN 630
	WISN 1150 A	Muleshoe, Tex.	KMUL 1380	New Westminster, B.C.	CKNW 980	Orange, Mass.	WCAT 1890
	WMIL 1290	Mullins, S.C.	WJAY 1280			Orange, Tex.	KOGT 1600-
	WOKY 920	Muncie, Ind.	WLBC 1340 C			Orange, Va.	WJMA 1340
	WTMJ 620 N	Munfordville, Ky.	WLOC 1150			Orangeburg, S.C.	WDIX 1150 A
Minden, La.	KASO 1240	Munising, Mich.	WMAB 1400	New York, N.Y.	WABC 770 A		
Mineral Wells, Tex.	KORC 1140	Murfreesboro, Tenn.	WGNS 1450		WBNX 1380	Orange Park, Fla.	WAYR 550
Minneapolis, Minn.	WFYI 1520	Murphy, N.C.	WMTS 860		WBCS 880 C	Orange City, Oreg.	KGON 1520 M
	WCCO 830 C		WCVF 600		WEVD 1330	Orillia, Ont.	CFOR 1570
	WLLO 1330		WKRK 1390		WHOM 1480	Orlando, Fla.	WDBO 580 C
	WMIN 1400	Murphysboro, Ill.	WINI 1420		WINS 1010		WHOO 990 M
	WDGY 1130	Murray, Ky.	WNBS 1340		WLIB 1190		WHIY 1270
	WPBC 980	Murray, Utah	KMUR 1230		WMCA 570		WLOF 950
	WTCN 1280 A	Muscatine, Iowa	KWPC 860		WMGM 1050		WKIS 740 N
	KTIS 900	Muskegon, Mich.	WLAB 1450		WNEW 1130	Ormond Bch., Fla.	WQXQ 1380
	KUOM 770		WKBZ 850 A		WNYC 830	Orofino, Idaho	KLER 950
Minot, N.Dak.	KLPM 1390 M		WTRU 1600		WOR 710 M	Ortonville, Minn.	KDIO 1350
	KQDY 1320		WMUS 1090		WADO 1280	Osage Bch., Mo.	KRMS 1150
	KCJB 910 C	Muskogee, Okla.	KBIX 1490 A		WPOW 1330	Osceola, Ark.	KOSE 860
Mission, Kans.	KBKC 1480		KMUS 1380		WQXR 1560	Oshawa, Ont.	CKLB 1350
Mission, Tex.	KIRT 1580	Myrtle Beach, S.C.	WMYB 1450		WNBC 660 N	Oshkosh, Wis.	WOSH 1490 A
Missoula, Mont.	KGVO 1290 C	Nacogdoches, Tex.	KEEE 1230 A	Niagara Falls, N.Y.	WHLI 1270	Oskaloosa, Iowa	KBOE 740
	KXLL 1450 N		KSFA 860		WJLL 1440	Othello, Wash.	KRSC 1400
	KQTE 1340 M	Nampa, Idaho	KFXD 580	Niagara Falls, Ont.	CHVC 1600	Ottawa, Ill.	WCMY 1430
	KYSS 910	Nanaimo, B.C.	CHUB 1570	Niles, Mich.	WNIL 1290	Ottawa, Kans.	KOFO 1220
Mitchell, S.Dak.	KORN 1490 M	Nanticoke, Pa.	WNAC 730	Nogales, Ariz.	KNOG 1340 A	Ottawa, Ont.	CBO 910
Moab, Utah	KURA 1450	Napa, Calif.	KVON 1440	Nome, Alaska	KICY 850		CFRA 560
Moberly, Mo.	KNCM 1230	Naples, Fla.	WNOG 1270	Norfolk, Nebr.	WJAG 780		CKOY 1310
Mobile, Ala.	WALA 1410 N	Narrows, Va.	WNRV 990	Norfolk, Va.	WTAR 790 C	Ottumwa, Iowa	KBIZ 1240 A
	WABB 1480 A	Nashua, N.H.	WOTW 900		WCMS 1050		KLEE 1480
	WGOK 900		WSMN 1590		WNOR 1230	Owatonna, Minn.	KRFO 1390
	WKAB 840	Nashville, Ark.	KBHC 1260		WRAP 850	Owego, N.Y.	WEBO 1330
	WKRK 710 C	Nashville, Ga.	WNGA 1600	Norman, Okla.	WNAD 640	Owensboro, Ky.	WOMI 1490 M
	WLIQ 1360	Nashville, Tenn.	WKDA 1240		KNOR 1400		WVJS 1420 A
	WMOZ 960		WLAC 1510 C			Owen Sound, Ont.	CFOS 560
Mobridge, S.Dak.	KOLY 1300		WMAK 1300	Norman Wells, North-	CFNW 1240	Owosso, Mich.	WOAP 1080
Modesto, Calif.	KTRB 860		WNAH 1360 M	west Territory	WNAR 1110	Oxford, Miss.	WSUH 1420
	KBEE 970		WSIX 980 A	N. Adams, Mass.	WMNB 1230	Oxford, N.C.	WOXF 1340
	KFIV 1360 A		WSM 650 N	N. Augusta, S.C.	WGUS 1380	Oxnard, Calif.	KOXR 910
Mojave, Calif.	KDOL 1340		WNAT 1450 M		WESN 1550	Ozark, Ala.	WOZK 900
Moline, Ill.	WQUA 1230 A	Natchez, Miss.	WMIS 1240 N	N. Battleford, Sask.	CJNB 1460	Paducah, Ky.	WKYB 570 N-M
Monahans, Tex.	KVKM 1330 M		WNAT 1450 M	North Bay, Ont.	CFCH 600		WDXR 1580
Moncton, N. B.	CBFA 1330		KNOC 1450 M	North Bend, Oreg.	KBBR 1340 C		WPAD 1450 C
	CKCW 1220	Natchitoches, La.	KNOC 1450 M	Northfield, Minn.	WCAL 770		KPGE 1340
Monett, Mo.	KRMD 390	Naugatuck, Conn.	WOWW 860	Northampton, Mass.	WHMP 1400 M	Page, Ariz.	WRIM 1250
Monmouth, Ill.	WRAM 1330	Nebraska City, Nebr.	KNCY 1600		WHLI 1270	Pahokee, Fla.	WRIM 1250
Monroe, Ga.	WMRE 1490		KSFE 1340		WJLL 1440	Painesville, Ohio	WPVL 1460
Monroe, La.	KMLB 1440 A-N	Needles, Calif.	KSFE 1340		WJLL 1440	Paintsville, Ky.	WSIP 1490 M
	KLIC 1230 M	Neenah, Wis.	WNAM 1280		WJLL 1440	Palatka, Fla.	WVWF 1280
	KNOE 1390	Neillsville, Wis.	WCCN 1370		WJLL 1440		WSUZ 800
	WQTE 560	Nelson, B.C.	CKLN 1390		WJLL 1440	Palestine, Tex.	KNET 1450
Monroe, Mich.	WMAP 1060	Neon, Ky.	WNKY 1480		WJLL 1440	Palm Bch., Fla.	WQXT 1340 A
Monroe, N.C.	WEKZ 1260	Neosho, Mo.	KBTN 1420		WJLL 1440	Palm Sprgs., Calif.	KCMJ 1010 C
Monroe, Wis.	WEKZ 1260	Nevada, Mo.	KNEM 1240		WJLL 1440		KDES 920
Monroeville, Ala.	WMFC 1360	New Albany, Ind.	WOWI 1570		WJLL 1440		KPAL 1450
Monterey, Calif.	KIDD 630	New Albany, Miss.	WNAU 1470		WJLL 1440		KUTY 1470
	KMBY 1240 C	Newark, N.J.	WNTA 970		WJLL 1440		KIBE 1220
	KDMA 1460 A		WHBI 1280		WJLL 1440		KPDN 1340 M
Montevideo, Minn.	KSLV 1240		WNJR 1430		WJLL 1440		KHHH 1230
Monte Vista, Colo.	WBAW 740		WVNJ 620		WJLL 1440		WDLF 590
Montgomery, Ala.	WCDV 1170 C	Newark, N.Y.	WACK 1420		WJLL 1440		WPCF 1430 M
	WAPX 1500 A	Newark, Ohio	WCLT 1430		WJLL 1440		WTHR 1480
	WHYH 1440 N	New Bedford, Mass.	WBSM 1420		WJLL 1440		WSCM 1290
	WRMA 950		WNBH 1340 M		WJLL 1440		KMET 930
Montgomery, W.Va.	WMON 1340 M		WRNB 1490		WJLL 1440		KDRS 1490
	WMBL 740	New Bern, N.C.	WHIT 1450 M		WJLL 1440		KCCL 1460
Monticello, Ark.	KHBM 1430		WRNB 1490		WJLL 1440		WPRS 1440
Monticello, Ky.	WFLW 1360	Newberry, S.C.	WKDK 1240		WJLL 1440		WKLX 1440
Montmagny, Que.	CKBM 1490	New Boston, Ohio	WIOI 1010		WJLL 1440		WTPR 710
Montpelier-Barre, Vt.	WSKI 1240 A	New Braunfels, Tex	KGNB 1420		WJLL 1440		KPLT 1490 A
	CBF 690 N	New Britain, Conn.	WHAY 910 A		WJLL 1440		KFTY 1250
	CBM 940 N		WKNB 840		WJLL 1440		WCEF 1050
	CFCF 600 A	New Brunswick, N.J.	WCTC 1450		WJLL 1440		WPAP 1450
	CHLP 1410	New Brunswick, N.Y.	WGNV 1220		WJLL 1440		WTAP 1230 A
	CJAD 800	Newburyport, Mass	WNBV 1470		WJLL 1440		WPF 1450
	CJMS 1280	New Carlisle, Que.	CHNC 610		WJLL 1440		CKAR-1 1340
	CKAC 730 C	New Castle, Ind.	WCTW 1550		WJLL 1440		KLKC 1540
	CKGM 980	Newcastle, N.B.	CKMR 790		WJLL 1440		KALI 1430
	KUBC 580	New Castle, Pa.	WKST 1280 M		WJLL 1440		KPPC 1240
Montrose, Pa.	WPEL 1250	Newcastle, Wyo.	KASL 1240		WJLL 1440		KRLA 1110
Mooreville, N.C.	WHIP 1350	New Glasgow, N.S.	KCEC 1320		WJLL 1440		KWKW 1300
Moorhead, Minn.	KVOX 1280 M	New Haven, Conn.	WAVZ 1300		WJLL 1440		KLVL 1480
Moosejaw, Sask.	CHAB 800		WELI 960		WJLL 1440		WPMP 1580 A
Morehead, Ky.	WMOR 1330		WNHC 1340 A		WJLL 1440		KORD 910
Morehead City, N.C.	WMBL 740		KANE 1240		WJLL 1440		KPKW 1340
Morgan City, La.	KMRC 1430 M		KVIM 1360		WJLL 1440		KPRL 1230 M
Morgantown, N.C.	WMNC 1430		WVETZ 1330 M		WJLL 1440		WALK 1370
Morgantown, W.Va.	WAJR 1440 N		WCOH 1400 M		WJLL 1440		WPAC 1580
	WCLG 1300		WDSU 1280 N		WJLL 1440		WPAT 930
Morrilton, Ark.	KVOM 800		WJBW 1230		WJLL 1440		KVLH 1470
Morris, Minn.	KMRS 1570		WJMR 990		WJLL 1440		WPAW 550 A
Morristown, N.J.	WMTR 1250		WJMR 990		WJLL 1440		KEOK 1450
Morristown, Tenn.	WCRK 1150 M		WJMR 990		WJLL 1440		CKYL 630
	WMTN 1300		WJMR 990		WJLL 1440		KIUN 1400 M
Moscow, Idaho	KRPL 1400		WJMR 990		WJLL 1440		WLNA 1420
Moses Lake, Wash.	KSEM 1470		WJMR 990		WJLL 1440		WSIV 1140
	KWIQ 260		WJMR 990		WJLL 1440		WFHK 1430
Moultrie, Ga.	WMGA 1400 A		WJMR 990		WJLL 1440		CHOV 1350
	WMTM 1300		WJMR 990		WJLL 1440		KKID 1240 A
Moundsville, W.Va.	WMOD 1370		WJMR 990		WJLL 1440		KUBE 1050
Mountain Grove, Mo.	KLRS 1360		WJMR 990		WJLL 1440		KUMA 1290 A
Mountain Home, Ark.	KTLO 1490		WJMR 990		WJLL 1440		WSWV 1570
Mt. Airy, N.C.	WPAQ 740		WJMR 990		WJLL 1440		
	WSYD 1300 M		WJMR 990		WJLL 1440		
Mt. Carmel, Ill.	WVMC 1360		WJMR 990		WJLL 1440		
Mt. Clemens, Mich.	WBRB 1430		WJMR 990		WJLL 1440		
Mt. Dora, Fla.	WMDP 1580		WJMR 990		WJLL 1440		
Mt. Jackson, Va.	WSIG 790		WJMR 990		WJLL 1440		
Mt. Kisco, N.Y.	WVIP 1310		WJMR 990		WJLL 1440		

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Pensacola, Fla.	WBOP	980		Port Arthur, Ont.	CFPA	1230		Reading, Pa.	WEEU	850	A	Roswell, N. Mex.	KSWS	1230	
	WDEB	610		Port Arthur, Tex.	KOLE	1340			WHUM	1240	C		KGFL	1400	M
	WBSR	1450	C		KPAC	1250	M	Redding, Calif.	WRAW	1340	N		KBIM	910	
	WNVY	1230	A	Porterville, Calif.	KTIP	1450	A		KROG	1280	M	Rouyn, Que.	CKRN	1400	
	WCOA	1370	N	Port Hope, Ont.	CHUC	1500			KPAP	1270		Roxboro, N.C.	WRXO	1430	
	WPFA	790		Port Hueneme, Calif.	KACY	1520			KSDA	1400		Royal Oak, Mich.	WEXL	1340	
Pentleton, B.C.	CKOK	800		Port Huron, Mich.	WHLS	1450			KVCV	600	C	Ruidoso, N.M.	KYAP	1340	
Peoria, Ill.	WAAP	1350	N		WTTT	1380	A	Red Bluff, Calif.	KVIP	540		Rumford, Me.	WRUM	790	
	WMBD	1470	C	Port Jervis, N.Y.	WDLC	1490		Red Deer, Alta.	KBLF	1490		Rupert, Idaho	KAYT	970	
	WIRL	1290	M	Portland, Ind.	WPGW	1440		Redlands, Calif.	CKRD	850		Rushton, La.	KRUS	1490	
	WPEO	1020		Portland, Maine	WCSH	970	N	Red Lion, Pa.	KCAL	1410		Rusk, Texas	KTLU	1580	
Perry, Fla.	WPRY	1400			WGAN	560	C	Redmond, Oreg.	WGCB	1440		Russell, Kans.	KRSL	990	
Perry, Ga.	WPGA	980			WLOB	1310		Red Wing, Minn.	KPRB	1240		Russellville, Ala.	WWWR	920	
Perryton, Tex.	KEYE	1400	M		WPOR	1490	A-M	Redwood Falls, Minn.	KCUE	1250		Russellville, Ark.	KXRJ	1490	
Peru, Ind.	WARU	1600		Portland, Oreg.	KBPS	1450		Reedsburg, Wis.	KLGR	1490		Russellville, Ky.	WRUS	610	
Petaluma, Calif.	KAFP	1490			KBEV	1010		Reedsport, Oreg.	WRDB	1400		Rutland, Vt.	WHWB	1000	
Peterborough, Ont.	CHEX	980			KLIQ	1290		Regina, Sask.	KROP	1470			WSYB	1380	M
	CKPT	1420			KEX	1190			CBK	540		Sackville, N.B.	CBA	1070	
Petersburg, Va.	WSSV	1240	M		KGW	620	N		CJME	1300		Sacramento, Calif.	KCRA	1320	N
Petoskey, Mich.	WMBN	1340			KOIN	970	C		CKCK	620			KFBK	1530	A
Phenix City, Ala.	WPNX	1460	A		KPAM	1410			CKRM	980			KGMS	1380	M
Philadelphia, Miss.	WHOC	1490			KPDQ	800		Reidsville, N.C.	WFRC	1600	A		KRAK	1140	
Philadelphia, Pa.	WCAU	1210	C		KPOJ	1330			WREY	1220			KROY	1240	C
	WDAS	1480			KWJJ	1080	A	Remsen, N.Y.	WREM	1480			KXOA	1470	
	WFIL	560	A		KXL	750		Reno, Nev.	KOH	630	N	Safford, Ariz.	KGLU	1480	A
	WFLN	900		Port Neches, Tex.	KPNG	1150			KBET	1340	M	Saginaw, Mich.	WKNX	1210	
	WHAT	1340		Portsmouth, N.H.	WBBX	1380			KOLO	920	C		WSAM	1400	N
	WIBG	990			WHEB	750			KONE	1450			WSGW	780	M
	WIP	610		Portsmouth, Ohio	WPAY	1400	C		KDOT	1230			WWSR	1420	
	WJMJ	1540			WNXT	1260	A	Renton, Wash.	KUDY	910		St. Albans, Vt.	WWSR	1420	
	WPEN	950		Portsmouth, Va.	WLOW	1400	A	Rexburg, Idaho	KRXK	1230		St. Albans, W.Va.	WKLC	1300	
	WRCV	1060	N		WAVY	1350	N	Rhineland, Wis.	WOBT	1240		St. Augustine, Fla.	WFOY	1240	C
	WTEL	860		Post, Tex.	KUKO	1370		Rice Lake, Wis.	WJMC	1240			WSTN	1420	
Phillipsburg, Pa.	WPHB	1260		Poteau, Okla.	KLCO	1280		Richfield, Utah	KSVQ	980		St. Boniface, Man.	CKSB	1050	
Phillipsburg, Kans.	KKAN	1490		Potosi, Mo.	KYRO	1280		Richland, Wash.	KALE	960		St. Catharines, Ont.	CKTB	610	
Phoenix, Ariz.	KIFN	860		Potsdam, N.Y.	WPDM	1470		Richland, Wis.	WRCO	1450		St. Charles, Mo.	KADY	1460	
	KXIV	1400		Pottstown, Pa.	WPAP	1370		Richlands, Va.	WRIC	540		St. Cloud, Minn.	KFAM	1450	N
	KHAT	1480		Pottsville, Pa.	WPAM	1450		Richmond, Ind.	WKBV	1490	A		WJON	1240	
	KHEP	1280		Poughkeepsie, N.Y.	WPPA	1360	M	Richmond, Ky.	WEKY	1340	M	Ste. Anne de la Pocatiere, Que.	CHGB	1350	
	KINK	1010			WEOK	1390		Richmond, Va.	WANT	990		St. George, Utah	KDXU	1450	
	KOY	550	A	Powell, Wyo.	WKIP	1450	A		WBBL	1480		St. Genevieve, Mo.	KSGM	980	
	KOOL	960	C	Poynette, Wis.	KPOW	1260	M		WEZL	1590		St. Helen, Mich.	WMIC	1590	
	KPHO	910	A	Prairie du Chien, Wis.	WIBU	1240			WLEE	1480	N	St. Helens, Oreg.	KOHI	1600	
	KUEQ	740			WPRE	980			WEET	1320		St. Hyacinthe, Que.	CKBS	1240	
	KRIZ	1230		Pratt, Kans.	KWSK	1570			WMBG	1380	A	St. Jean, Que.	CHRS	1090	
	KTAR	620	N	Prescott, Ariz.	KYCA	1490	N		WRNL	910	M	St. Jerome, Que.	CKJL	900	
Pleayunc, Miss.	WRJW	1320			KNOT	1450	A		WRVA	1140	N	Saint John, N.B.	CFBC	930	
Piedmont, Ala.	WPID	1280			KTPA	1370			WXGI	950			CHSJ	1150	
Pierre, S.Dak.	KGFX	630		Presque Isle, Me.	WAGM	950		Richmond Hill, Ont.	CJRH	1310		St. Johns, Mich.	WJUD	1580	
	KCCR	1590			WEGP	1390		Richwood, W.Va.	WVAR	1280		St. John's, Nfld.	CBN	640	
	WLSI	900		Preston, Idaho	KPST	1340		Ridgecrest, Calif.	KRCK	1360			CJON	930	
	WPKE	1240	M	Prestonsburg, Ky.	WPRT	960			KRKS	1240			VOAR	1230	
Pine Bluff, Ark.	KCLA	1400			WDOC	1310		Rimouski, Que.	CJBR	900			VOCM	590	
	KADL	1270		Pricce, Utah	KOAL	1230	M	Rio Piedras, P.R.	WRIO	1320			VOWR	800	
	KOTN	1490	M	Prichard, Ala.	WAIP	1270			WKYN	630		St. Johnsbury, Vt.	WTWN	1340	
	KPBA	1590		Prince Albert, Sask.	CKBI	900			WWWW	1520		St. Joseph, Mich.	WSJM	1400	
Pine City, Minn.	WCMP	1350		Prince George, B.C.	CKPG	550		Ripley, Tenn.	WTRB	1570		St. Joseph, Mo.	KFEQ	680	
Pineville, Ky.	WMLF	1230		Prince Rupert, B.C.	CFPR	1240		Ripon, Wis.	WCWC	1600			KRES	1550	M
Pineville, W.Va.	WWYO	970		Princeton, Ind.	WRAY	1250		Riverhead, N.Y.	WRIV	1390			KUSN	1270	
Pipestone, Minn.	KLOH	1050		Princeton, Ky.	WPKY	1580			WAPC	1570		St. Joseph d'Alma, Que.	CFGT	1270	
Piqua, Ohio	WPTW	1570		Princeton, W.Va.	WLOH	1490	A		KPRO	1440		St. Louis, Mo.	KATZ	1600	
Pittsburg, Calif.	KKIS	990		Prineville, Oreg.	KRCO	690		Riverton, Wyo.	KACE	1570			KFUO	850	
Pittsburg, Kans.	KOAM	860	N	Prosser, Wash.	KARY	1310		Riviera Beach, Fla.	WHEW	1600			KMOX	1120	C
	KSEK	1340		Providence, R.I.	WEAN	790	C	Rochester, N.Y.	CJFP	1400			KSD	550	N
	KDKA	1020			WHIM	1110		Roanoke, Ala.	WELR	1360			KSTL	690	
	KQV	1410	C		WICE	1290		Roanoke, Va.	WDBJ	960	C		KWK	1380	
	WCAE	1250			WJAR	920	N		WRIS	1410	M		KXOK	630	
	WEEP	1080			WLKW	990			WHYE	910			WEW	770	M
	WAMO	860			WPRO	630			WROV	1240	A		WIL	1430	A
	WAMP	1320	N		WRIB	1220	M	Roanoke Rapids, N.C.	WLSL	610	N				
	WPIT	730			KIXX	1400	A		WCBT	1230	M	St. Louis Park, Minn.	KRSI	950	
	WWSW	970		Provo, Utah	KEYY	1450			WKMC	1370		St. Mary's, Pa.	WKBI	1500	
Pittsfield, Ill.	WBBA	1580			KOVO	960	M	Roaring Sprgs., Pa.	CHRL	910		St. Paul, Minn.	KSTP	1400	N
Pittsfield, Mass.	WBEC	1420	A	Pryor, Okla.	KOLS	1570		Roberval, Que.	WTAY	1570			KDWB	630	M
	WBRK	1340	M	Pueblo, Colo.	KDZA	1230		Robinson, Ill.	KROC	1340	N	St. Peter, Minn.	KRBI	1310	
Pittston, Pa.	WPTS	1540			KAPL	690		Rochester, Minn.	KWEB	1270		St. Petersburg, Fla.	WPIN	680	
Plainfield, N.J.	WERA	1590			KFEL	970			WVNH	930			WSUN	620	A
Plainview, Tex.	KVOP	1400	M		KGHF	1350	A-M	Rochester, N.H.	WBBF	950	M		WLCY	1380	M
	KPLA	1050			KCSJ	590		Rochester, N.Y.	WHAM	1180	N	St. Petersburg Beach, Fla.	WILZ	1590	
Plant City, Fla.	WPLA	910			KTUX	1480			WHEC	1460	C	St. Thomas, Ont.	CHLO	680	
Platteville, Wis.	WSWW	1590		Pulaski, Tenn.	WKSR	1420	A		WRVM	680		Salamanea, N.Y.	WGGO	1590	
Plattsburg, N.Y.	WEAV	960	A-N	Pulaski, Va.	WPUV	1580			WSAY	1370		Salem, Ill.	WJBD	1350	
	WIRY	1340	M	Pullman, Wash.	KWSC	1250			WVET	1280	A	Salem, Ind.	WSLM	1220	
Pleasanton, Tex.	KBOP	1380			KOFE	1150		Rockford, Ill.	WROK	1440	A	Salem, Mass.	WESX	1230	M
Pleasantville, N.J.	WOND	1400			WCCF	1580			WJRL	1150		Salem, Mo.	KSMO	1340	
Plymouth, Mass.	WPLM	1390		Punta Gorda, Fla.	WPME	1540			WRRR	1330		Salem, Oreg.	KSLM	1390	A
Plymouth, N.C.	WPNC	1470		Punxsutawney, Pa.	WINY	1350			WRHI	1340	M		KBZY	1490	N
Plymouth, Wis.	WPLY	1420		Putnam, Conn.	KAYE	1450		Rock Hill, S.C.	WTYC	1150			KGAY	1430	
Poehontas, Ark.	KPOC	1420		Puyallup, Wash.	KOLJ	1150			WAYN	900		Salem, Va.	WBLU	1480	
Pocatello, Idaho	KSEI	930	N	Quanah, Tex.	CBV	980			WHBF	1270	C	Salida, Colo.	KVRH	1340	M
	KWIK	1240	M	Quebec, Que.	CHRC	800		Rock Island, Ill.	WRKD	1450	A	Salina, Kans.	KSAL	1150	M
	KYTE	1290			CJLR	1060		Rockland, Maine	WPLK	1220		Salinas, Calif.	KDON	1460	
Pocomoke City, Md.	WDMV	540			CJQC	1340									

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
San Antonio, Tex.	KAPE 1480 KCOR 1350 KENS 680 C KIKK 1150 KITE 930 KUKA 1250 KUBO 1310 KMAC 630 A KONO 960 KTSA 550 WOAI 1200	Seaford, Del.	WSUX 1280	Springdale, Ark.	KXLY 920 C KCFA 1330	Temple, Tex.	KTEM 1400
San Bernardino, Calif.	KCKC 1350 KFXM 590 KRNO 1240 KITO 1290 M WSNT 1490 KCBQ 1170 KFMB 540 C KFSD 600 N KGB 1360 A KSON 1240 KSDO 1130 KSPT 1400 WLEC 1450 M KGIL 1260	Seaside, Oreg.	KWCB 1300	Springfield, Ill.	KBRS 1340 A WCVS 1450 A-M WMAY 970 N WTAX 1240 C WBZA 1030 C WHYN 560 C WMAS 1450 M WSPR 1270 KGBX 1260 N KICK 1340 KTTS 1400 C KWTO 560 A WIZE 1340 A WBLY 1600 KEED 1050 WDBL 1590 WCFR 1480 KBSF 1460 WTOE 1470 WSTC 1400 A KDWT 1200 WRGR 1490 WSSO 1230 WMAJ 1450 M WWSN 1240 WSIC 1400 WDBM 550 WTDN 1240 A WAFG 900 KSTV 1510 KGEK 1230 KOLR 1490 WSDR 1240 WSTV 1340 M WSPT 1010 WLBL 930 WAVN 1220 KSPI 780 KJOY 1280 KSTN 1420 KWG 1230 A-M KAYL 990 CJCS 1240 WIZZ 1250 WVPO 840 WSTU 1450 M WHEO 1270 WUOR 910 WSTR 1230 KWAK 1240 M CKSO 790 CFBR 550 CHNO 900 WLPM 1460 A KIKS 1310 KSST 1230 CJRW 1240 WGTA 950 WFIG 1290 M WDXY 1240 WSSC 1340 A WKOK 1240 C KREW 1230 KSKI 1340 KRFS 1600 WDSM 710 N WQMN 1320 KSUE 1240 WJAT 800 WDEH 800 KXOX 1240 CKSW 1400 CBI 1570 CJCB 1270 WFEB 1340 M WMLS 1290 WMSJ 1480 WSYL 1490 WHEN 620 C WFBL 1390 WNRD 1260 WOLF 1490 A WSYR 570 N WTAB 1370 KMO 1360 KTAC 850 KTNT 1400 KVI 570 M KTKR 1310 KTLQ 1350 WJHB 1580 WNUZ 1230 M WMEN 1330 WRFB 1580 WTAL 1270 WTNT 1450 A-M-C WTLN 1300 KTLD 1360 WALT 1110 WQAE 1250 C WZST 1550 WFLA 970 N WHBO 1050 WBNQ 1010 WTMP 1150 WSOL 1300 WCPS 760 WDCL 1470 WESR 1330 WPEP 1570 WIOS 1480 KTAE 1260 WTIM 1410 WNTT 1250 WTCJ 1230 KUPD 1060 KYND 1580	Terre Haute, Ind.	WBOW 1230 N WMFT 1300 WTHI 1480 C KTER 1570 KOSY 790 M KCMC 1230 A KTFS 1400 KTLW 920 KALM 1290 KODL 1440 KRMW 1300 KRTR 1490 M KTHE 1240
San Diego, Calif.	KCBQ 1170 KFMB 540 C KFSD 600 N KGB 1360 A KSON 1240 KSDO 1130 KSPT 1400 WLEC 1450 M KGIL 1260 WTRR 1400 WFSR 1360 WSME 1220 WEYE 1290 WGGP 1050	Seattle, Wash.	KAYO 1150 KING 1090 A KIRO 710 C KJR 950 KOL 1300 KOMO 1000 N KTIX 1590 KTW 1250 KVI 570 KXA 770 WJCM 960 WSEB 1340 KDRO 1490 KSIS 1050 KWED 1580 WGWC 1340 C WHBB 1490 WRWJ 1570 KSML 1250	Thief River Falls, Minn.	KTRF 1230		
Sandusky, Ohio	KGIL 1260	Sebring, Fla.	WJCM 960	Thetford Mines, Que.	CKLD 1230		
San Fernando, Calif.	KGIL 1260	Sedalia, Mo.	KDRO 1490	Thibodaux, La.	KTIB 630		
Sanford, Fla.	WTRR 1400 WFSR 1360 WSME 1220 WEYE 1290 WGGP 1050	Seguin, Tex.	KSIS 1050	Thomaston, Ga.	WSFT 1220		
Sanford, Me.	WSME 1220	Selma, Ala.	WGWC 1340 C	Thomasville, Ala.	WJDB 630		
Sanford, N.C.	WEYE 1290 WGGP 1050	Seminole, Tex.	KSML 1250	Thomasville, Ga.	WPAX 1240 WKTG 730 WTNC 790 WTWA 1240 M CHLN 550 CKTR 1150 WIPS 1250 WTF 1600 WTFI 1340 WWSG 1430 KTIL 1590 CKOT 1510 CFCL 620 CKGB 680 WRMF 1050 WLET 1420 M WNEG 1320 WUHO 1470 M WSPD 1370 N WTD 1560 C WTOL 1230 A KLUU 1230 WTMB 1460 WTKY 1370 KOYL 990 WIBW 580 C KJAY 1440 WREN 1250 A KTOP 1490 M KENE 1490 CBL 740 N CFRB 1010 C CHUM 1050 CJBC 860 CKEY 580 M CKFH 1430 WBZY 990 WTOR 1490 M KGOS 1490 WTTT 1550 WAQE 1570 CJAT 610 WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
San Francisco, Calif.	KFRC 610 M KCBS 740 C KFAX 1100 KGO 810 KNBC 680 N KQBY 1550 M KSAY 1010 KSN 1450 KSFO 560 KYA 1260 WRJS 1050 KLOK 1170 KLIV 1590 KEEN 1370 KXRX 1500	Shelby, Mont.	WSEV 930	Thomasville, N.C.	WTWA 1240 M		
San German, P.R.	WRJS 1050	Shelby, N.C.	WJCD 1390 KSEY 1230 WISL 1480 KBYP 1580 WPIC 790 WTCM 960 CKSM 1220 KGFF 1450 M WHBL 1330 A WKT 950 KSEN 1150 M WHS 730 M WADA 1390 WHL 1400 WLIJ 1580	Thomson, Ga.	CHLN 550		
San Jose, Calif.	KLOK 1170 KLIV 1590 KEEN 1370 KXRX 1500	Shelbyville, Tenn.	WHL 1400	Three Rivers, Que.	CKTR 1150		
San Juan, P.R.	WAPA 680 M WHA 870 WIAC 740 WIPR 940 WKAQ 580 C WKVM 1230 WITA 1140	Shenandoah, Iowa	WLIJ 1580	Ticonderoga, N.Y.	WIPS 1250		
San Luis Obispo, Calif.	KATY 1340 KCJH 1280 KSLY 1400 KVEC 920 M KCNV 1470 KOFY 1050 KTIM 1510 KBAL 1410 KWIZ 1480 KDB 490 KGD 990 KIST 1340 KTMS 1250 A-M	Sherbrooke, Que.	KFNF 920 KMA 960 A CHLT 630 CKTS 900 KWYO 1410 M KRRV 910 M KTXO 1500 KVWM 1050 KANB 1300 KBCL 1220 KCIJ 1050 KEEL 710 KREB 1550 M KJOE 1480 KOKA 980 KRMD 1340 A KWKH 1130 C KGCX 1480 M KSID 1340 A KHFH 1420 A KSIM 1400 WNCA 1570 KUOA 1290 M KKAS 1300 KSIL 1340 C WQMR 1050 CFRS 1560 KTOO 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KISD 1230 KELO 1320 KHO 1270 KSOO 1140 A KIFW 1230 C-A KSEW 1400 WGHM 1150 WMPM 1270 CJET 630 KSNY 1450 M KSRC 1290 KBRV 540 WSFC 1240 M WTLO 1480 WVSC 990 KROG 1450 CJSO 1320 WNU 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WEEB 990	Tiffin, Ohio	WTFI 1340		
San Marcos, Tex.	KCNV 1470	Sheridan, Wyo.	WVPO 840	Tifton, Ga.	WWSG 1430		
San Mateo, Calif.	KOFY 1050	Sherman, Tex.	WVPO 840	Tillamook, Oreg.	KTIL 1590		
San Rafael, Calif.	KTIM 1510	Show Low, Ariz.	KVWM 1050	Tillsonburg, Ont.	CKOT 1510		
San Saba, Tex.	KBAL 1410	Shreveport, La.	KANB 1300 KBCL 1220 KCIJ 1050 KEEL 710 KREB 1550 M KJOE 1480 KOKA 980 KRMD 1340 A KWKH 1130 C KGCX 1480 M KSID 1340 A KHFH 1420 A KSIM 1400 WNCA 1570 KUOA 1290 M KKAS 1300 KSIL 1340 C WQMR 1050 CFRS 1560 KTOO 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KISD 1230 KELO 1320 KHO 1270 KSOO 1140 A KIFW 1230 C-A KSEW 1400 WGHM 1150 WMPM 1270 CJET 630 KSNY 1450 M KSRC 1290 KBRV 540 WSFC 1240 M WTLO 1480 WVSC 990 KROG 1450 CJSO 1320 WNU 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WEEB 990	Timmins, Ont.	CFCL 620		
Santa Ana, Calif.	KWIZ 1480	Sidney, Mont.	WSEV 930	Titusville, Fla.	WRMF 1050		
Santa Barbara, Cal.	KDB 490 KGD 990 KIST 1340 KTMS 1250 A-M	Sidney, Nebr.	WJCD 1390	Toccoa, Ga.	WLET 1420 M		
Santa Cruz, Calif.	KSCO 1080	Sierra Vista, Ariz.	KHFH 1420 A	Toledo, Ohio	WUHO 1470 M WSPD 1370 N WTD 1560 C WTOL 1230 A KLUU 1230 WTMB 1460 WTKY 1370 KOYL 990 WIBW 580 C KJAY 1440 WREN 1250 A KTOP 1490 M KENE 1490 CBL 740 N CFRB 1010 C CHUM 1050 CJBC 860 CKEY 580 M CKFH 1430 WBZY 990 WTOR 1490 M KGOS 1490 WTTT 1550 WAQE 1570 CJAT 610 WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Santa Fe, N.Mex.	KTRC 1400 A KVSF 1260 C KCOY 1400 KSMA 1240 KDAY 1580 KSPA 1400 KSRO 1350 KJAX 1150 KSYX 1420	Sikeston, Mo.	KSIM 1400	Toledo, Oreg.	KLUU 1230		
Santa Maria, Cal.	KCOY 1400 KSMA 1240 KDAY 1580 KSPA 1400 KSRO 1350 KJAX 1150 KSYX 1420	Siler City, N.C.	WNCA 1570	Tomah, Wis.	WTMB 1460		
Santa Monica, Cal.	KDAY 1580	Siloam Spgs., Ark.	KUOA 1290 M	Tompkinsville, Ky.	WTKY 1370		
Santa Paula, Calif.	KSPA 1400	Silsbee, Tex.	KKAS 1300	Tooele, Utah	KOYL 990		
Santa Rosa, Calif.	KSRO 1350 KJAX 1150 KSYX 1420	Silver City, N.Mex.	KSIL 1340 C	Topeka, Kans.	WIBW 580 C KJAY 1440 WREN 1250 A KTOP 1490 M KENE 1490 CBL 740 N CFRB 1010 C CHUM 1050 CJBC 860 CKEY 580 M CKFH 1430 WBZY 990 WTOR 1490 M KGOS 1490 WTTT 1550 WAQE 1570 CJAT 610 WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Santa Rosa, N.Mex.	KSYX 1420	Silver Spgs., Md.	WQMR 1050	Toronto, Ont.	CBL 740 N CFRB 1010 C CHUM 1050 CJBC 860 CKEY 580 M CKFH 1430 WBZY 990 WTOR 1490 M KGOS 1490 WTTT 1550 WAQE 1570 CJAT 610 WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Saranac Lake, N.Y.	WNBZ 1240 A	Sioux City, Iowa	KSCJ 1360 A KMNS 620 KTRI 1470 KISD 1230 KELO 1320 KHO 1270 KSOO 1140 A KIFW 1230 C-A KSEW 1400 WGHM 1150 WMPM 1270 CJET 630 KSNY 1450 M KSRC 1290 KBRV 540 WSFC 1240 M WTLO 1480 WVSC 990 KROG 1450 CJSO 1320 WNU 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WEEB 990	Torrington, Conn.	WBZY 990 WTOR 1490 M KGOS 1490 WTTT 1550 WAQE 1570 CJAT 610 WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Sarasota, Fla.	WKXY 930 WSPB 1450 C WYND 1280	Sloux Falls, S.Dak.	KELO 1320 KHO 1270 KSOO 1140 A KIFW 1230 C-A KSEW 1400 WGHM 1150 WMPM 1270 CJET 630 KSNY 1450 M KSRC 1290 KBRV 540 WSFC 1240 M WTLO 1480 WVSC 990 KROG 1450 CJSO 1320 WNU 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WEEB 990	Torrington, Wyo.	KGOS 1490		
Saratoga Springs, N.Y.	WSPN 900 WRSA 1280 CHOK 1070 CFQC 600 CFNS 1170 CKOM 1420 WGHQ 920	Sitka, Alaska	KIFW 1230 C-A	Towson, Md.	WAQE 1570		
Sarnia, Ont.	CHOK 1070	Skowhegan, Maine	WGHM 1150	Trail, B.C.	CJAT 610		
Saskatoon, Sask.	CFQC 600 CFNS 1170 CKOM 1420 WGHQ 920	Smithfield, N.C.	WMPM 1270	Traverse City, Mich.	WTCM 1400 WCOW 1310 WCCW 1310 KTTN 1600 WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Saugerties, N.Y.	WGHQ 920	Smiths Falls, Ont.	CJET 630	Trenton, Mo.	KTTN 1600		
Sault Ste. Marie, Mich.	WSOO 1230	Snyder, Tex.	KSNY 1450 M	Trenton, N.J.	WAAT 1300 WBUD 1260 WTTM 920 N KCRF 1240 M WTBF 970 M WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Sault Ste. Marie, Ontario	CJIC 1050 CKCY 1400 WCCP 1450 M WJIV 900 WSAV 630 N WSGA 1400 WTOC 1290 C WSOK 1230 A WORM 1010 WATS 960 CFKL 1230 WGY 810 N WSNY 1240 WYAL 1280 KNEB 960 M KOLT 1320 C WCRI 1050 WROS 1330 KPOK 1440 WLCK 1250 WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	Socorro, N.Mex.	KSRC 1290	Trinidad, Colo.	KCRF 1240 M		
Savannah, Ga.	WCCP 1450 M WJIV 900 WSAV 630 N WSGA 1400 WTOC 1290 C WSOK 1230 A WORM 1010 WATS 960 CFKL 1230 WGY 810 N WSNY 1240 WYAL 1280 KNEB 960 M KOLT 1320 C WCRI 1050 WROS 1330 KPOK 1440 WLCK 1250 WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	Soda Spgs., Idaho	KBRV 540	Troy, Ala.	WTBF 970 M		
Savannah, Tenn.	WORM 1010	Somers, Ky.	WSFC 1240 M	Troy, N.Y.	WHAZ 1330 WTRY 980 KHOE 1400 CKCL 600		
Sayre, Pa.	WATS 960	Somerset, Pa.	WVSC 990	Truckee, Calif.	KHOE 1400		
Schefferville, Que.	CFKL 1230	Sonora, Calif.	KROG 1450	Truro, N.S.	CKCL 600		
Schenectady, N.Y.	WGY 810 N WSNY 1240 WYAL 1280 KNEB 960 M KOLT 1320 C WCRI 1050 WROS 1330 KPOK 1440 WLCK 1250 WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	Sorel, P.Q.	CJSO 1320	Truth or Consequences, New Mexico	KCHS 1400		
Scotland Neck, N.C.	WYAL 1280	So. Bend, Ind.	WNU 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WEEB 990	Tryon, N.C.	WTYN 1550 M		
Scottsbluff, Nebr.	KNEB 960 M KOLT 1320 C WCRI 1050 WROS 1330 KPOK 1440 WLCK 1250 WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	So. Boston, Va.	WHLF 1400 A	Tucson, Ariz.	KTUC 1400 A KAIR 1490 KCEE 790 KTAN 580 A KCUB 1290 N KEVT 690 KMBO 940 KMOP 1390 KSWC 1550 KTKT 990 KOLD 1450 C KTNM 1400 M CKOK 1270 M KGEN 1370 KTUE 1260 WJIG 740 KAKC 970 KOME 1300 KRMG 740 KTUL 1430 C KVOO 1170 N KFMJ 1050 WELO 580 M WTUP 1490 A KTUR 1390 WJRD 1150 WACT 1420 WNPT 1280 A WTUG 790 WTBC 1230 M WVNA 1590 WCHP 1410 WABT 580 KTFI 1270 N KLIX 1310 M KEEP 1450 WTRW 1590		
Scottsboro, Ala.	WCRI 1050 WROS 1330 KPOK 1440 WLCK 1250 WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	So. Daytona Beach, Florida	WELE 1590	Tulsa, Okla.	KAKC 970 KOME 1300 KRMG 740 KTUL 1430 C KVOO 1170 N KFMJ 1050 WELO 580 M WTUP 1490 A KTUR 1390 WJRD 1150 WACT 1420 WNPT 1280 A WTUG 790 WTBC 1230 M WVNA 1590 WCHP 1410 WABT 580 KTFI 1270 N KLIX 1310 M KEEP 1450 WTRW 1590		
Scottsdale, Ariz.	KPOK 1440	So. Gastonia, N.C.	WGAS 1420	Tulsa, Okla.	KAKC 970 KOME 1300 KRMG 740 KTUL 1430 C KVOO 1170 N KFMJ 1050 WELO 580 M WTUP 1490 A KTUR 1390 WJRD 1150 WACT 1420 WNPT 1280 A WTUG 790 WTBC 1230 M WVNA 1590 WCHP 1410 WABT 580 KTFI 1270 N KLIX 1310 M KEEP 1450 WTRW 1590		
Scottsville, Ky.	WLCK 1250	So. Paris, Me.	WKTQ 1450	Tupelo, Miss.	WTUP 1490 A		
Scranton, Pa.	WARM 590 A WEJL 630 WGBI 910 C WICK 1400 WSCR 320 N	So. Pittsburg, Tenn.	WEPG 910	Turlock, Calif.	KTUR 1390		
		So. St. Paul, Minn.	WISK 630 M	Tuscaloosa, Ala.	WJRD 1150 WACT 1420 WNPT 1280 A WTUG 790 WTBC 1230 M WVNA 1590 WCHP 1410 WABT 580 KTFI 1270 N KLIX 1310 M KEEP 1450 WTRW 1590		
		So. Williamsport, Pa.	WMPT 1450 KONI 1480 KBUB 1270 WHCO 1230 WSMT 1050 WKLJ 990 WTHE 1400 M WORD 910 N WSPA 950 C KICD 1240 KGA 1510 A KLYK 1230 KPEG 1380 KHQ 590 N KNEW 790 M KREM 970	Tuskegee, Ala.	WABT 580		
		Spokane, Wash.	KLYK 1230 KPEG 1380 KHQ 590 N KNEW 790 M KREM 970	Twin Falls, Idaho	KTFI 1270 N KLIX 1310 M KEEP 1450 WTRW 1590		

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Tyler, Tex.	KDOK	1330		Walnut Ridge, Ark.	KRLW	1320		Wendell-Zebuion, N.C.				Winchester, Tenn.	WCDT	1340	
	KGJB	1490	M	Walsenburg, Colo.	KFLJ	1380			WETC	540		Winchester, Va.	WINC	1400	A
	KTBB	600	A	Walterboro, S.C.	WALD	1220	A	Westlaco, Tex.	KRGV	1290	N	Winder, Ga.	WIMO	1300	
	KZEY	690		Waltham, Mass.	WCRB	1330		W. Bend, Wis.	WBKV	1470		Windom, Minn.	KDOM	1580	
Tyrone, Pa.	WTRN	1340		Walton, N.Y.	WDLA	1270		Westbrook, Me.	WJAB	1440		Windsor, Conn.	WSOR	1480	
Ukiah, Calif.	KUKI	1400		Ward Ridge, Fla.	WJOE	1570		W. Frankfort, Ill.	WFRX	1300		Windsor, N.S.	CFAB	1450	
Union, Mo.	KLPW	1220		Ware, Mass.	WARE	1250	M	West Jefferson, N.C.				Windsor, Ont.	CBE	1550	
Union, S.C.	WBCU	1460		Warner Robbins, Ga.	WRPB	1350			WKSJ	1600			CKLW	800	M
Union City, Tenn.	WENK	1240		Warren, Ark.	KWRF	860		W. Monroe, La.	KUZN	1310		Wingham, Ont.	KKNX	920	
Uniontown, Pa.	WBMS	590	C	Warren, Ohio	WHHH	1440		W. Palm Beach, Fla.				Winnemucca, Nev.	KWNA	1400	
Urbana, Ill.	WILL	580		Warren, Pa.	WNAE	1310			WEAT	850	N	Winnfield, La.	KVCL	1270	
	WKID	1580		Warrensburg, Mo.	KOKO	1450			WJNO	1230	C	Winner, S.Dak.	KWYR	1260	
Utica, N.Y.	WIBX	950	C	Warrenton, Mo.	KWRE	730			WIRK	1290	M	Winnipeg, Man.	CBW	990	
	WRUN	1150		Warrenton, Va.	WEER	1570		West Plains, Mo.	KWPM	1450			CKRC	630	
	WTLB	1310	A	Warsaw, Ind.	WRSW	1480		West Point, Ga.	WBMK	1310			CKY	580	
Uvalde, Tex.	KVOU	1400		Warsaw, Va.	WNNT	690		West Point, Miss.	WROB	1450	M		CJOB	680	
Val D'Or, Que.	CKVD	1230		Warwick-E.Greenwich, R.I.	WYNG	1590		Westport, Conn.	WMMM	1260		Winnsboro, La.	KMAR	1570	
Valdosta, Ga.	WGOV	950	M		WYNG	1590		W. Springfield, Mass.	WTXL	1490	A	Winona, Minn.	KWNO	1230	A
	WGAF	910	A	Waseo, Calif.	KWSO	1050							KAGE	1380	
	WJEM	1150		Washington, D.C.	WGMS	570		W. Yarmouth, Mass.				Winona, Miss.	WONA	1570	
	WVLD	1450			WMAL	630	A		WOCB	1240	M	Winslow, Ariz.	KVNC	1010	A
Vallejo, Calif.	KNBA	1190			WOL	1450	M	Westerly, R.I.	WERI	1230	M	Winston-Salem, N.C.			
Valley City, N.Dak.	KOVC	1490	M		WOL	1450	M	Westfield, Mass.	WDEW	1570			WAAA	980	
Valparaiso-Niceville, Fla.	WNMS	1340			WOOB	1340		Westminster, Md.	WTTR	1470			WAIR	1340	
	KDFD	1580			WVOC	1240	M	Weston, W.Va.	WHAW	980	M		WSJS	600	N
Van Buren, Ark.	WMTA	730			WVOC	1240	M	W. Warwick, R.I.	WVRI	1450			WTOB	1380	M-C
Van Cleve, Ky.	WERT	1220			WVOC	1240	M	Wetumpka, Ala.	WETU	1250			WOKB	1600	
Van Wert, Ohio	WKKS	1570			WVOC	1240	M	Wewoka-Seminole, Okla.	KWSH	1260	A	Winter Garden, Fla.	WSIR	1490	M
Vanceburg, Ky.	CBU	690			WVOC	1240	M		CFSL	1340		Winter Haven, Fla.	WSIR	1490	M
Vancouver, B.C.	CFUN	1410			WVOC	1240	M	Weyburn, Sask.	WDON	1540			WINT	1360	
	CHQM	1320			WVOC	1240	M	Wheaton, Md.	WHLL	1600		Winter Park, Fla.	WABR	1440	M
	CJOR	600			WVOC	1240	M	Wheeling, W.Va.	WKWK	1400	A	Wisconsin Rapids, Wis.	WFHR	1320	M
	CKWX	1130	M		WVOC	1240	M		WVVA	1170	C		WVCK	1450	M
Vancouver, Wash.	KKEY	1150			WVOC	1240	M	White Castle, La.	KEVL	1590		Wolf Pt., Mont.	WVLR	1600	
	KISN	910			WVOC	1240	M	White Plains, N.Y.	WFAS	1230		Woodside, N.Y.	CJCJ	920	
Venice, Fla.	WAMR	1320			WVOC	1240	M	White River Junc., Vt.			Woodstock, N.B.	CKOX	1340		
Ventura, Calif.	KVEN	1450	M		WVOC	1240	M		WWRJ	910		Woodstock, Ont.	KSIW	1450	
	KUDU	1590			WVOC	1240	M	Whitehorse, Y.T.	CFWH	1240		Woodward, Okla.	WNRI	1380	
Verdun, Que.	CKVL	850			WVOC	1240	M	Whitesburg, Ky.	WTCW	920		Woonsocket, R.I.	WWON	1240	
Vermillion, S.Dak.	KUSD	690			WVOC	1240	M	Whiteville, N.C.	WENC	1220			WWST	960	
Vernal, Utah	KVEL	1250			WVOC	1240	M	Wichita, Kans.	KAKE	1240	M		WAAB	1440	M-N-A
Vernon, B.C.	CJIB	940			WVOC	1240	M		KLEO	1480			WNEB	1230	
Vernon, Tex.	KVWC	1490			WVOC	1240	M		KIRL	1070	N		WROC	1310	
Vero Beach, Fla.	WAXE	1370			WVOC	1240	M		KFH	1330	C		WTAG	580	C
	WTTB	1490	A		WVOC	1240	M		KSIR	900			WVOR	1340	M
Vicksburg, Miss.	WQBC	1420	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
	WVIM	1490			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Victoria, B.C.	CJVI	900			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	CFAX	810			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	CKDA	1220			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	KNAL	1410			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	KVIC	1340	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Victoriaville, Que.	CFDA	1380			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Vidalia, Ga.	WVOP	970			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Vieques, P.R.	WIVV	1370			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Ville Marie, Que.	CKVM	710			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Ville Platte, La.	KVPI	1050			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Ville St. Georges, Que.	CKRB	1460			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Vincennes, Ind.	WAOV	1450	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Vineland, N.J.	WBZB	1360			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	WDVL	1270			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Vinita, Okla.	KVIN	1470			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Virginia, Minn.	WHLB	1400	N		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Virginia Beh., Va.	WBOF	1550			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Virouqua, Wis.	WISV	1360			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Visalia, Calif.	KONG	1400			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Waco, Tex.	WACO	1460	A		WVOC	1240	M		KWBB	1410			WVOR	1340	M
	KWTX	1230	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Wadena, Minn.	KWAD	920	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Wadesboro, N.C.	WADE	1210			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Wailuku, Hawaii	KMVI	550	N		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Waipahu, Hawaii	KAHU	920			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Walhalla, S.C.	WGOG	1460			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Wallace, Idaho	KWAL	620	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
Wallace, N.C.	WLSE	1400			WVOC	1240	M		KWBB	1410			WVOR	1340	M
Walla Walla, Wash.	KHIT	1320			WVOC	1240	M		KWBB	1410			WVOR	1340	M
	KUJ	1420	M		WVOC	1240	M		KWBB	1410			WVOR	1340	M
	KTEL	1490	A		WVOC	1240	M		KWBB	1410			WVOR	1340	M

United States FM Stations

Abbreviations: Mc., megacycles, asterisk (*) indicates educational station

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	
ALABAMA												
Albertville	WAVU-FM	105.1	Mesa	KBUZ-FM	104.7	Claremont	KSPC	*88.9			KXLU	*88.7
Alexander City	WRFS-FM	106.1	Phoenix	KELE	95.5	El Cajon	KUFM	93.3			KHOF	99.5
Andalusia	WCTA-FM	98.1		KFCA	*88.5	Eureka	KRED-FM	96.3	Marysville	KMYC-FM	99.9	
Anniston	WHMA-FM	100.5		KOOL-FM	94.5	Fresno	KARM-FM	101.9	Modesto	KBEE-FM	103.3	
Athens	WJOF	104.3		KYEW	93.3		KMJF-FM	97.9		KTRB-FM	104.1	
Birmingham	WAPI-FM	99.5	Tempe	KUPD-FM	97.9		KRFM	93.7	Mountain View	KFJC	*88.5	
	WBRC-FM	106.9	Tucson	KFMM	99.5	Glendale	KFMU	97.1	Oakland	KAPE	98.1	
	WSFM	93.7					KUTE	101.9	Ontario	KASK-FM	93.5	
Clanton	WKLF-FM	100.9	ARKANSAS									
Cullman	WFMH-FM	101.1	Blytheville	KLCN-FM	96.1	Hayward	KTYM-FM	103.9	Oxnard	KAAR	104.7	
Decatur	WHOS-FM	102.1	Ft. Smith	KFPW-FM	94.9	Inglewood	KCVR-FM	97.7	Palm Springs	KPSR	92.1	
Homewood	WJLN	104.7	Jonesboro	KBTM-FM	101.9	Lodi	KFOX-FM	102.3	Pasadena	KPCS	89.3	
Huntsville	WAHR	99.1		KASU	91.9	Long Beach	KLON	*88.1	Riverside	KPLI	99.1	
Mobile	WKRQ-FM	99.9	Mammoth Springs	KAMS	103.9		KNOB	97.9		KACE-FM	92.7	
Sylacauga	WMLS-FM	98.3	Osceola	KOSE-FM	98.1	Los Angeles	KABC-FM	95.5	Sacramento	KDUO	97.5	
Tuscaloosa	WTBO-FM	95.7	Pine Bluff	KOTN-FM	92.3		KBBI	107.5		KCRA-FM		

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.			
San Francisco	KGB-FM	101.5	Savannah	WTOC-FM	97.3	KANSAS						WJBK-FM	93.1	
	KITT	105.3	Swainsboro	WJAT-FM	101.7	Emporia	KSTE	*88.7	E. Lansing	WFRS	92.5			
	KSDS	*88.3	Toccoa	WLET-FM	106.1	Kansas City	KCJC	98.1	Flint	WFSM	99.1			
	KALW	*91.7	HAWAII						Lawrence	KANU	*91.5	Grand Rapids	WFUR-FM	102.9
	KBAY-FM	104.5	Honolulu	KAIM-FM	95.5	Manhattan	KSDB-FM	*88.1	Henderson	WSON-FM	99.5	Highland Pk.	WHPR	*88.1
	KCBS-FM	98.9		KVOK	*88.1	Newton	KJRG-FM	92.1	Hopkinsville	WRLX	98.7	Jackson	WBBC	94.1
	KDFC	102.1	ILLINOIS						Ottawa	KTJO-FM	*88.1	Kalamazoo	WMCR	*102.1
	KEAR	97.3	Anna	WRAJ-FM	92.7	Parsons	KPPS-FM	*91.1	Lexington	WBKY	*91.3	Lansing	WJIM-FM	97.5
	KGO	103.7	Arlington Heights	WNWC	92.7	Wichita	KFH-FM	100.3	Louisville	WLP-FM	94.5	Oak Park	WLOM	95.5
	KNBC-FM	99.7	Bloomington	WJBC-FM	101.5		KMUW	*89.1	Madisonville	WFPK	*91.9	Royal Oak	WOAK	*89.3
	KHIP	106.9	Carmi	WRDY-FM	97.3	KENTUCKY						Saginaw	WSAM-FM	98.1
	KRON-FM	96.5	Champaign	WDWS-FM	97.5	Ashland	WCMI-FM	93.7	Sturgis	WSTR-FM	103.1			
	KSFR	94.9	Chicago	WBBM-FM	96.3	Central City	WNES-FM	101.9						
	KQBY-FM	95.7		WBEZ	*91.5	Fulton	WFUL-FM	104.9						
San Jose	KYA-FM	93.3		WCLM	101.9	Hazard	WKIC-FM	96.5						
	KSJO-FM	92.3		WDFH	95.5	Henderson	WSON-FM	99.5						
San Luis Obispo	KRPM	98.5		WEBH	93.9	Hopkinsville	WRLX	98.7						
San Mateo	KATY-FM	96.1		WEFH	99.5	Lexington	WBKY	*91.3						
Santa Ana	KCSM	*90.9		WEHS	97.9	Louisville	WLP-FM	94.5						
	KWIZ-FM	96.7		WENR-FM	94.7	Madisonville	WFPK	*91.9						
Santa Barbara	KFIL	106.3		WFMF	100.3	Owensboro	WNGO-FM	94.7						
Santa Clara	KRCW	97.5		WFMQ	107.5	Paducah	WVJS-FM	96.1						
Santa Maria	KSCU	*90.1		WFMT	98.7		WPAO-FM	96.9						
	KEYM	89.1		WKFM	103.5		WKYB-FM	93.3						
Santa Monica	KSMF-FM	102.5		WMAQ-FM	101.1	LOUISIANA								
Stockton	KCRW	*89.9		WMBI-FM	*90.1	Alexandria	KALB-FM	96.9						
Walnut Creek	KCVN	*91.3		WNIB	97.1	Baton Rouge	WJBO-FM	98.1						
West Covina	KSGV	98.3		WSBC-FM	93.1	Monroe	KMLB-FM	104.1						
COLORADO				WSEL	104.3	New Orleans	WBEH	89.3						
Boulder	KRNW	97.3		WSOY-FM	102.9	Shreveport	WDSU-FM	105.3						
Colorado Springs	KRCC	*91.3		WNIC	*91.1		WRCM	97.1						
	KFMH	96.5		WAMY-FM	101.1		WMMT	95.7						
	KSHS	*90.5		WELG	103.9		KRMD-FM	101.1						
Denver	KVOR-FM	92.9		WELG	103.9		KBCL-FM	96.5						
	KFML-FM	98.5		WRMN-FM	94.3		KWKH-FM	94.5						
	KDEN-FM	99.5		WEPS	*88.1									
	KLIR-FM	100.3		WTFM	105.9									
	KTGM	105.1		WEAW	105.1									
Grand Junction	KREX-FM	92.3		WNUR	*89.3									
Manitou Springs	KCMS-FM	102.7		WEBQ-FM	99.9									
CONNECTICUT				WLDS-FM	100.5									
Brookfield	WGHF	95.1		WAJP	93.5									
Danbury	WLAD-FM	98.3		WJOL-FM	96.7									
Hartford	WHCN	105.9		WSMI-FM	106.1									
	WDRC-FM	102.9		WWKS	*91.3									
	WRTC-FM	*89.3		WLBH-FM	96.9									
	WTIC-FM	96.5		WMIX-FM	94.1									
Meriden	WBMI	95.7		WOPA-FM	102.7									
New Haven	WNHC-FM	99.1		WVLN-FM	92.9									
Stamford	WSTC-FM	96.7		WPRF-FM	98.3									
Storrs	WHUS	*90.5		WMTM	*88.5									
DELAWARE				WMBD-FM	92.5									
Dover	WDOV-FM	94.7		WGEN-FM	105.1									
Wilmington	WDEL-FM	93.7		WTAD-FM	99.5									
	WJBR	99.5		WROK-FM	97.5									
				WHBF-FM	98.9									
				WTAX-FM	103.7									
				WILL-FM	*90.9									
D. C.				INDIANA										
Washington	WASH-FM	97.1		Bloomington	WFIU	*103.7								
	WFAN	100.3			WTTV-FM	92.3								
	WGMS-FM	103.5			WCSI-FM	98.3								
	WMAL-FM	107.3			WCNB-FM	100.3								
	WOL-FM	98.7			WBBS-FM	106.3								
	WRC-FM	93.9			WCMR-FM	95.1								
	WTOP-FM	96.3			WTRC-FM	100.7								
	WVDC-FM	101.1			WIKY-FM	104.1								
FLORIDA					WEVC	*91.5								
Coral Gables	WVCG-FM	105.1			WPSR	90.7								
Daytona Beach	WNOB-FM	94.5			WPTH	95.1								
Fort Lauderdale	WWIL-FM	103.5			WQVE	*88.1								
	WFLM	105.9			WGCS	91.1								
Gainesville	WRUF-FM	*104.1			WGRE	*91.7								
Jacksonville	WJAX-FM	95.1			WIOB-FM	92.3								
	WZFM	96.9			WHCI	*91.9								
	WMBR-FM	96.1			WVSH	*91.9								
Miami	WAFM	93.1			WJJC	*104.5								
	WCKR-FM	97.3			WFBM-FM	94.7								
	WGBS-FM	96.3			WFMS	95.5								
	WTHS	*91.7			WIAN	*90.1								
	WWPB-FM	101.5			WITZ-FM	104.7								
Miami Beach	WKAT-FM	93.1			WGRX-FM	96.7								
	WMET-FM	93.9			WMRI-FM	106.9								
Orlando	WDBO-FM	92.3			WVST	*90.7								
	WHOO-FM	96.5			WMUN	104.1								
	WKIS-FM	100.3			WVHI	*91.5								
Palm Beach	WQXT-FM	97.9			WNAS	*88.1								
Tallahassee	WFSU-FM	*91.5			WCTW-FM	102.5								
Tampa	WDAE-FM	100.7			WYSN	*91.1								
	WFLA-FM	93.3			WETL	*91.9								
	WPKM	104.7			WTHI-FM	99.9								
Winter Park	WTUN	*88.9			WSKS	*91.3								
	WPRK	*91.5			WRSW-FM	107.3								
GEORGIA					WFML	106.5								
Athens	WGAU-FM	102.5		IOWA										
Atlanta	WABE	*90.1		Ames	WOI-FM	*90.1								
	WPLO-FM	103.3		Boone	KFGQ	*99.3								
	WGKA-FM	92.9		Cedar Falls	KTCF	*88.1								
	WSB-FM	98.5		Clinton	KROS-FM	96.1								
Augusta	WAUG-FM	105.7		Davenport	WOC-FM	103.7								
	WBBQ-FM	103.7		Des Moines	KOPS	*88.1								
	WRBL-FM	93.3			WHO-FM	100.3								
Columbus	WOUN-FM	103.9			WDBQ	103.3								
Gainesville	WLAG-FM	104.1			KSUI	*91.7								
Lagrange	WMAZ-FM	99.1			KGLO-FM	101.1								
Macon	WMAZ-FM	99.1			KWPC-FM	99.7								
Marietta	WMAZ-FM	101.5			KAYL-FM	101.5								
Newnan	WCOH-FM	96.7			KWAR	89.1								

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Cherry Valley	WRRC	101.9	Cincinnati	WCPO-FM	105.1	Palmyra	WJWR	92.1	San Antonio	KISS	99.5
Corning	WCLI-FM	106.1		WAEF-FM	104.3	Philadelphia	WCAU-FM	98.1		KEEZ	97.3
Cortland	WKRT-FM	99.9		WKRC-FM	101.9		WDAS-FM	105.3		KITY	92.9
DeRuyter	WRRD	105.1		WSAI-FM	102.7		WFIL-FM	102.1	Texaskana	KCMC-FM	98.1
Elmira	WECW	*88.1	Cleveland	KYW-FM	105.7		WFLN	95.7	Waco	KEFC	95.5
Floral Park	WSHS	*90.3		WABQ-FM	106.5		WHAT-FM	96.5	Waxahachie	KBEC-FM	93.5
Hempstead	WHLI-FM	98.3		WBOE	*90.3		WHYY	*90.9			
Hornell	WWHG-FM	105.3		WCRF-FM	103.3		WIBG-FM	94.1			
Ithaca	WHCU-FM	97.3		WDOK-FM	102.1		WIP-FM	93.3			
	WICB	*91.7		WERE-FM	98.5		WPEN-FM	102.9			
	WRRR-FM	103.7		WGAR-FM	99.5		WPWT	*91.7			
	WVBR-FM	101.7		WHK-FM	100.7		WQAL	106.1	Ephraim	KEPH	*88.9
	WJTN-FM	93.3		WJW-FM	104.1		WRTI-FM	*90.1	Logan	KVSC	*88.1
Jamestown	WYSL-FM	103.3		WNOB	107.9		WXPB	*88.9	Provo	KBYU-FM	*88.9
Kenmore	WMSA-FM	105.3	Cleveland Hts.	WCUY-FM	95.3	Pittsburgh	KDKA-FM	92.9	Salt Lake City	KCPX-FM	98.7
Massena	WRNW	107.1	Columbus	WCBE	*90.5		WCAE-FM	96.1		KSL-FM	100.3
Mt. Kisco	WVOX-FM	93.5		WBNS-FM	97.1		WDOQ	*91.5			
New Rochelle	WABC-FM	95.5		WCOL-FM	92.3		WFMP	99.7			
New York	WBAI	99.5		WOSU-FM	*89.7		WKJF	93.7			
	WBFM	101.9		WTVN-FM	96.3		WPIT-FM	101.5			
	WCBS-FM	101.1		WVOK	94.7		WWSW-FM	94.5			
	WEVD-FM	97.9	Dayton	WHIO-FM	99.1	Pottsville	WPPA-FM	101.9	Arlington	WARL-FM	105.1
	WFUV	*90.7		WIFE	104.7	Red Lion	WGCB-FM	96.1		WCCV-FM	95.7
	WHOM-FM	92.3	Delaware	WISL	*91.1	Scranton	WGBI-FM	101.3	Charlottesville	WINA-FM	95.3
	WKCR-FM	*89.9	East Liverpool	WOHI-FM	104.3		WUSV	*88.9		WTJU	91.3
	WNCN	104.3	Elyria	WEOL-FM	107.3		WPIC-FM	102.9	Crewe	WSVS-FM	104.7
	WNEW-FM	102.7	Findlay	WFIN-FM	100.5	State College	WDFM	*91.1	Fredericksburg	WFVA-FM	101.5
	WNYC-FM	93.9	Fostoria	WFOB	96.7	Sunbury	WKOK-FM	94.1	Harrisonburg	WEMC	*91.7
	WNYE	91.5	Fremont	WFRO-FM	99.3	Towanda	WTTC-FM	92.7		WSVA-FM	100.7
	WOR-FM	98.7	Hamilton	WQMS	96.7	Warren	WRRN	92.3	Lynchburg	WWOD-FM	100.1
	WQXR-FM	96.3		WHOH	103.5	Washington	WJPA-FM	104.3	Martinsville	WMVA-FM	96.3
	WNBC-FM	97.1		WKSU-FM	*88.1	Waynesboro	WAYZ-FM	101.5	Newport News	WGH-FM	97.3
	WRFM	105.1	Kent	WHOK-FM	95.5	Wilkes-Barre	WBRE-FM	98.5	Norfolk	WMTI	*91.5
	WHLI-FM	98.5	Lancaster	WIMA-FM	102.1		WYZZ	103.3		WRVC	102.5
	WHOL-FM	95.7	Lima	WCMO	*89.3	Williamsport	WLYC-FM	105.1		WYFI-FM	99.7
	WALK-FM	97.5	Marietta	WMRN-FM	106.9	York	WRAC-FM	100.3	Richmond	WCOD	98.1
	WPAC-FM	106.1	Marion	WPFB-FM	105.9		WNOW-FM	105.7		WRFK	91.1
	WLNA-FM	100.7	Middletown	WMVO-FM	93.7					WRVA-FM	94.5
	WKIP-FM	104.7	Mt. Vernon	WCLT-FM	100.3					WRNL-FM	102.1
	WHFM	98.9	Newark	WMUB	*88.5					WDBJ-FM	94.9
	WIRQ	*90.9	Oxford	WOXR	97.7					WROV-FM	103.7
	WROC-FM	97.9	Portsmouth	WPAY-FM	104.1					WLSL-FM	99.1
	WGFM	99.5	Salem	WSOM-FM	105.1					WHLF-FM	97.5
	WRRE	95.1	Sandusky	WLEC-FM	102.7					WFOS	*90.5
	WSPE	*88.1	Springfield	WBLY-FM	103.9					WAFB-FM	93.3
	WAER	*88.1	Staubenville	WSTV-FM	103.5					WCWM	89.1
	WDDS-FM	93.1	Toledo	WSPD-FM	101.5					WRFL	92.5
	WONO	100.9		WMHE	92.5					WBVA	105.9
	WSYR-FM	94.5		WTDS	*91.3						
	WFLY	92.3		WTOL-FM	104.7						
	WRPI	91.5		WTRT	99.9						
	WRUN-FM	105.7	Wooster	WWST-FM	104.5						
	WRRL	107.7	Youngstown	WKBN-FM	98.9						
	WFAS-FM	103.9		WBBW-FM	93.3						
				WRED	101.1						

UTAH

VIRGINIA

RHODE ISLAND

WASHINGTON

SOUTH CAROLINA

WEST VIRGINIA

TENNESSEE

TEXAS

WISCONSIN

NORTH CAROLINA

OKLAHOMA

OREGON

PENNSYLVANIA

OHIO

Canadian FM Stations

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Brampton, Ont.	CHIC-FM	102.1	Kingston, Ont.	CFRC-FM	91.9	Oshawa, Ont.	CKLB-FM	93.5	Vancouver, B.C.	CFRB-FM	99.9
Brantford, Ont.	CKPC-FM	92.1		CKLC-FM	99.5	Ottawa, Ont.	CBO-FM	103.3		CHFI-FM	98.1
Cornwall, Ont.	CJSS-FM	104.5		CKWS-FM	96.3		CFRA-FM	93.9		CJRT-FM	91.1
Edmonton, Alta.	CFRN-FM	100.3	Kitchener, Ont.	CKCR-FM	96.7	Quebec, Que.	CHRC-FM	96.1		CBU-FM	105.7
	CJCA-FM	99.5	Lethbridge, Alta.	CHEC-FM	100.9	Rimouski, Que.	CJBR-FM	101.5		CHQM-FM	103.5
	CKUA-FM	98.1	London, Ont.	CFPL-FM	95.9	St. Catharines, Ont.				CKVL-FM	98.9
Ft. William, Ont.	CKPR-FM	94.3	Montreal, Que.	CBF-FM	95.1	Timmins, Ont.	CKTB-FM	97.7	Verdun, Que.	CKDA-FM	98.5
Halifax, N.S.	CHNS-FM	96.1		CBM-FM	100.7	Toronto, Ont.	CKGB-FM	94.5	Victoria, B.C.	CKLW-FM	93.9
				CFCF-FM	106.5		CBC-FM	99.1	Windsor, Ont.	CKLW-FM	93.9
									Winnipeg, Man.	CJOB-FM	103.1

United States Television Stations

(Territories and possessions follow states). Chan., channel number; asterisk (*) indicates educational station.

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.
ALABAMA			CONNECTICUT			INDIANA			Springfield		
Andalusia	WAIQ	42	New Britain	WNHB-TV	30	Bloomington	WTTV	4		WHYN-TV	40
Birmingham	WAPI-TV	13	New Haven	WNHC-TV	8	Elkhart	WSJV-TV	26	Worcester	WWLP	22
	WBIQ	*10	Waterbury	WATR-TV	53	Evansville	WFIE-TV	14		WWOR-TV	14
	WBRC-TV	6	DIST. OF COLUMBIA				WEHT	50	MICHIGAN		
Decatur	WMSL-TV	23	Washington	WMAL-TV	7	Ft. Wayne	WTVW	7	Bay City	WNEM-TV	5
Dothan	WTVY	9		WRC-TV	4		WANE-TV	15	Cadillac	WWTW	13
Florence	WOWL	15		WTOV-TV	9		WKJG-TV	33	Cheboygan	WTOM-TV	4
Huntsville	WAFG-TV	31		WTTG	5	Indianapolis	WPTA	21	Detroit	WJBK-TV	2
Mobile	WALA-TV	10	FLORIDA				WFBM-TV	6		WTVS	*56
	WKRQ-TV	5	Daytona Beach	WESH-TV	2		WLWI	13		WWJ-TV	4
Montgomery	WCOV-TV	20	Fort Pierce-Vero Beach	WFTS-TV	28	Lafayette	WISH-TV	8	(Windsor, Ont.)	WXYZ-TV	7
	WSFA-TV	12	Fort Myers	WINK-TV	11	Muncie	WFAM-TV	18	Flint	CKLW-TV	9
Munford	WCIQ	*7	Gainesville	WUFT	*5	South Bend	WLBC-TV	49	Grand Rapids	WJRT	12
Selma	WSLA	8	Jacksonville	WFGA-TV	12	Terre Haute	WNDU-TV	16	Kalamazoo	WOOD-TV	8
ALASKA				WJCT	*7		WSBT-TV	10	Lansing	WKZO-TV	3
Anchorage	KENI-TV	2		WJXT	4	IOWA			Marquette	WJIM-TV	6
Fairbanks	KFAA-TV	2	Miami	WCKT	7	Ames	WOI-TV	5	Onondaga	WLUC-TV	6
	KTVF	11		WLBW-TV	10	Cedar Rapids	KCRG-TV	9	Saginaw	WILX-TV/WMSB	10
Juneau	KINY-TV	8		WTHS-TV	*2	Davenport	WMT-TV	2	Traverse City	WKNX-TV	57
ARIZONA				WTVJ	4	Des Moines	WOC-TV	6	MINNESOTA		
Phoenix	KOOL-TV	10	Orlando	WDBO-TV	6		KRNT-TV	8	Alexandria	KCMT	7
	KPHO-TV	5	Palm Beach	WLOF-TV	9	Fort Dodge	KDPS-TV	*11	Austin	KMMT	6
	KTVK	3	Panama City	WPTV	5	Mason City	WHO-TV	13	Duluth	KDAL-TV	3
	KVAR	12	Pensacola	WJDM-TV	7	Ottumwa	KQTV	21		WDSM-TV	6
Tucson	KGUN-TV	9	St. Petersburg	WEAR-TV	3	Sioux City	KGLO-TV	3	Mankato	KEYC-TV	12
	KOLD-TV	13	Tallahassee	WSUN-TV	38	Waterloo	KTVO	3	Minneapolis	KMSP	9
	KVOA-TV	4	Tampa	WFSU-TV	*11		KTIV	4		WCCO-TV	4
	KUAT	*8		WFLA-TV	6		KVTV	9	Rochester	WTCT-TV	11
Yuma	KIVA	11		WEDU	*3		KWWL-TV	7	St. Paul	KROC-TV	10
ARKANSAS				WTVT	13	KANSAS				KSTP-TV	5
El Dorado	KTVE	10	W. Palm Beach	WEAT-TV	12	Ensign	KTVC	6		KTCA-TV	*2
Ft. Smith	KFSA-TV	5	GEORGIA			Goodland	KGLD	11	MISSISSIPPI		
Little Rock	KARK-TV	4	Albany	WALB-TV	10	Garden City	KBLR-TV	10	Columbus	WCBI-TV	4
	KTHV	11	Athens	WGTW	*8	Great Bend	KCKT	2	Greenwood	WABG-TV	6
	KATV	7	Atlanta	WAGA-TV	5	Hays	KAYS-TV	7	Jackson	WJTV	12
Texarkana	KCMC-TV	6		WSB-TV	2	Hutchinson	KTVH	12	Laurel	WDAM-TV	7
CALIFORNIA				WETV	*30	Pittsburg	KOAM-TV	7	Meridian	WTOK-TV	11
Bakersfield	KBAK-TV	29		WLW-A	11	Topoka	WIBW-TV	13	Tupelo	WCOC-TV	30
	KERO-TV	10	Augusta	WJBF	6	Wichita	KAKE-TV	10		WTWV	9
Chico	KLYD-TV	17		WRDW-TV	12	KENTUCKY			MISSOURI		
El Centro	KHSL-TV	12	Columbus	WRBL-TV	3	Lexington	WLEX-TV	16	Cape Girardeau	KFVS-TV	12
Eureka	XEM-TV	3		WTVM	9	Louisville	WKYT	27	Columbia	KOMU-TV	8
	KIEM-TV	3	Macon	WMAZ-TV	13		WAVE-TV	3	Hannibal	KHQA-TV	7
Fresno	KVIQ-TV	6	Savannah	WESA-TV	*9		WFPK-TV	*15	Jefferson City	KRCG-TV	13
	KFRE-TV	30		WTOC-TV	11	Paducah	WHAS-TV	11	Joplin	KODE-TV	12
	KJEO	47	Thomasville	WCTV	6		WQXL-TV	41	Kansas City	KCMO-TV	5
Los Angeles	KMJ-TV	24	Waycross	WEGS-TV	*8		WPSD-TV	6		KMBC-TV	9
	KABC-TV	7	HAWAII							WDAF-TV	4
	KCOP	13	Hilo	KHBC-TV	9	LOUISIANA			Kirkville	KTVO	3
	KHJ-TV	9	Honolulu	KHJK	13	Alexandria	KALB-TV	5	St. Joseph	KFEQ-TV	2
	KNXT	2		KGMB-TV	9	Baton Rouge	WAFB-TV	28	St. Louis	KETC	*9
	KRCA	4		KONA	2		WBRZ	2		KMOX-TV	4
	KTLA	5	Walluku	KULA-TV	4	Lafayette	KLFY-TV	10		KSD-TV	5
	KTTV	11		KMAU	3	Lake Charles	KPLC-TV	7		KTVI	2
Oakland	KTVU	2		KALA	7	Monroe	KTAG-TV	25	Sedalia	KPLR-TV	11
Redding	KVIP-TV	7		KMVI-TV	12	New Orleans	KNOE-TV	8	Springfield	KMOS-TV	6
Sacramento	KXTV	10	IDAHO				KLSE	*13		KTTS-TV	10
	KCRA-TV	3	Boise	KBOI-TV	2		WVUE	13		KYTV	3
	KVIE	*6		KTVB	7	MAINE			MONTANA		
Salinas	KSBW-TV	8	Idaho Falls	KID-TV	3	Bangor	WABI-TV	5	Billings	KOOK-TV	2
San Diego	KFMB-TV	8	Lewiston	KLEW-TV	3	Poland Spring	WLBZ-TV	2		KGHL-TV	8
	KFSD-TV	10	Nampa	KCIX-TV	6	Portland	WMTW-TV	8	Butte	KXFL-TV	4
(Tijuana, Mex.)	XETV	6	Pocatello	KTLE	6	Presque Isle	WCSH-TV	13	Glendive	KXGN-TV	5
San Francisco	KGO-TV	7	Twin Falls	KLIX-TV	11		WGAN-TV	8	Great Falls	KFBB-TV	5
	KPIX	5	ILLINOIS				WAGM-TV	8		KRTV	3
	KQED	*9	Champaign	WCIA	3				Helena	KXLJ-TV	12
	KRON-TV	4	Chicago	WCHU	33	Baltimore	WJZ-TV	13	Kalspell	KULR	9
San Jose	KNTV	11		WBBM-TV	2	Salisbury	WBAL-TV	11	Missoula	KMSO-TV	13
San Luis Obispo	KSBJ-TV	6		WBKB	7		WMAR-TV	2	NEBRASKA		
Santa Barbara	KEY-TV	3		WGN-TV	9		WBOC-TV	16	Hastings	KHAS-TV	5
Stockton	KOVR	13		WNBQ	5				Hay Springs	KDUH-TV	4
COLORADO				WTTW	*11				Hayes Center	KHPL-TV	8
Colorado Springs	KKTV	11		WICD	24				Kearney	KHOL-TV	13
	KRDO-TV	13	Danville	WTVP	17				Lincoln	KOLN-TV	10
Denver	KBTU	9	Decatur	WSIL-TV	3	Baltimore	WBZ-TV	4		KUON-TV	*12
	KLZ-TV	7	Harrisburg	WEEQ-TV	35	Boston	WBZ-TV	4	McCook	KOMC	8
	KOA-TV	4	La Salle	WEEK-TV	43		WGBH-TV	*2	North Platte	KNOP	2
	KRMA-TV	*6	Peoria	WMBD	31		WHDH-TV	5	Omaha	KMTV	3
	KTVR	2		WTVH	19		WNAC-TV	7		KETV	7
Grand Junction	KREX-TV	5	Quincy	WGM-TV	10					WOW-TV	6
Montrose	KREY-TV	10	Rockford	WREX-TV	13				Scottsbluff	KSTF	10
Pueblo	KCSJ-TV	5		WTVO	39				NEVADA		
Bridgeport	WICC-TV	43	Rock Island	WHBF-TV	4				Henderson	KLRJ-TV	2
Hartford	WTIC-TV	3	Springfield	WICS	20						
	WHGT	18	Urbana	WILL-TV	*12						

Location	C.L. Chan.
Las Vegas	KLAS-TV 8
Reno	KSHO-TV 13
Reno	KOLO-TV 8
NEW HAMPSHIRE	
Durham	WENH-TV 11
Manchester	WMUR-TV 9
NEW JERSEY	
Newark	WNTA-TV 13
NEW MEXICO	
Albuquerque	KGGM-TV 13
	KNME-TV 5
	KOAT-TV 7
	KOB-TV 4
Carlsbad	KAVE-TV 6
Clovis	KVER-TV 12
Roswell	KSWV-TV 8

NEW YORK	
Albany	WTEN 10
	WAST 13
	WTRI 35
	WCDA 41
Binghamton	WINR-TV 40
	WNBF-TV 12
Buffalo	WBEN-TV 4
	WNED-TV 17
	WGR-TV 2
	WKBW-TV 7
Carthage	WCNY-TV 7
Elmira	WSYE-TV 18
New York	WABC-TV 7
	WNEW-TV 5
	WCBS-TV 2
	WOR-TV 9
	WPIX 11
Plattsburg	WNBC-TV 4
Rochester	WPTZ-TV 5
	WHEC-TV 10
	WROC-TV 5
	WVET-TV 10
Sehenectady	WRGB 6
Syracuse	WHEN-TV 8
	WSYR-TV 3
Utica	WKTV 2

NORTH CAROLINA	
Asheville	WISE-TV 62
	WLOS-TV 13
Chapel Hill	WUNC-TV 4
Charlotte	WBTV 3
	WSOC-TV 9
Durham	WTVD 11
Greensboro	WFMY-TV 2
Greenville	WNCT 9
Raleigh	WRAL-TV 5
Washington	WITN 7
Wilmington	WECT 6
Winston-Salem	WSJS-TV 12

NORTH DAKOTA	
Bismarek	KBMB-TV 12
	KFYR-TV 5
Dickinson	KDIX-TV 2
Fargo	WDAY-TV 6
	KXGO-TV 11
Grand Forks	KNOX-TV 10
Minot	KXMC-TV 13
	KMOT 10
Pembina, N.D.	12
Valley City	KXJB-TV 4
Williston	KUMV-TV 8

OHIO	
Akron	WAKR-TV 49
Cincinnati	WCET 48
	WCPO-TV 9
	WKRC-TV 12

Location	C.L. Chan.
Cleveland	WLW-TV 5
	WCIN-TV 54
	KYW-TV 3
	WEWS 5
	WJW-TV 8
Columbus	WBNS-TV 10
	WLW-C 4
	WOSU-TV 34
	WTVN-TV 6
Dayton	WHIO-TV 7
	WLW-D 2
Lima	WIMA-TV 35
Dxford	WMUB-TV 14
Steubenville	WSTV-TV 9
Toledo	WSPD-TV 13
	WGTE-TV 30
	WTOL-TV 11
Youngstown	WFMJ-TV 21
	WKBN-TV 27
	WKST-TV 33
	WXTV 45
Zanesville	WHIZ-TV 18

OKLAHOMA	
Ada	KTEN 10
Ardmore	KXII 12
Enid	KOCO-TV 5
Lawton	KSWO-TV 7
Oklahoma City	KETA 13
	KOKH-TV 25
	KWTU 9
	WKY-TV 4
Tulsa	KOTV 6
	KOED-TV 11
	KTUL-TV 8
	KV00-TV 2

OREGON	
Coos Bay	KCBY-TV 11
Corvallis	KOAC-TV 7
Eugene	KVAL-TV 13
Klamath	KOTI 2
Medford	KBES-TV 5
Portland	KGW-TV 8
	KHTV 27
	KOIN-TV 6
	KPTV 12
Roseburg	KPIC 4

PENNSYLVANIA	
Altoona	WFBG-TV 10
Erie	WICU 12
	WSEE-TV 35
Harrisburg	WHP-TV 55
	WTPA 27
Johnstown	WARD-TV 56
	WJAC-TV 6
Lancaster	WGAL-TV 8
Lebanon	WLVI-TV 15
Lockhaven	WBPZ-TV 32
New Castle	WKST-TV 45
Philadelphia	WCAU-TV 10
	WFIL-TV 6
	WHYY-TV 35
	WPCA-TV 17
	WRCV-TV 3
Pittsburgh	KDKA-TV 2
	WIBC 11
	WQED 13
	WQEX 16
	WTAE 4
Seranton	WNEP-TV 16
	WDAU-TV 22
Wilkes-Barre	WBRE-TV 28
York	WSBA-TV 43

RHODE ISLAND	
Providence	WJAR-TV 10
	WPRO-TV 12

SOUTH CAROLINA	
Anderson	WAIM-TV 40
Charleston	WCSC-TV 5

Location	C.L. Chan.
Columbia	WUSN-TV 2
	WIS-TV 10
	WNOK-TV 67
Florence	WBTW 8
Greenville	WFBC-TV 4
Spartanburg	WSPA-TV 7
SOUTH DAKOTA	
Aberdeen	KXAB-TV 9
Deadwood	KDSJ-TV 5
Florence	KDLO-TV 3
Mitchell	KORN-TV 5
Rapid City	KOTA-TV 3
	KRSD-TV 7
Reliance	KPLO-TV 6
Sioux Falls	KELO-TV 11
	KSOO-TV 13
Vermillion	KUSD-TV 2

TENNESSEE	
Chattanooga	WDEF-TV 12
	WRGP-TV 3
	WTVG 9
Jackson	WDXI-TV 7
Johnson City	WJHL-TV 11
Knoxville	WATE-TV 6
	WBIR-TV 10
	WTVK 26
Memphis	WHBQ-TV 13
	WKNO 10
	WMCT 5
	WREC-TV 3
Nashville	WLAC-TV 5
	WSIX-TV 8
	WSM-TV 4

TEXAS	
Abilene	KRBC-TV 9
Amarillo	KFDA-TV 10
	KGNC-TV 4
	KVII 7
Austin	KTBC-TV 7
Beaumont	KFDM-TV 6
Big Spring	KEDY-TV 4
Bryan	KBTX-TV 3
Corpus Christi	KRIS-TV 6
	KZTV 10
Dallas	KRLD-TV 4
	KERA-TV 13
	WFAA-TV 8
El Paso	KELP-TV 13
	KROD-TV 4
	KTSM-TV 9
(Ciudad Juarez, Mex.)	XEJ-TV 5
Ft. Worth	KTVT 11
	WBAP-TV 5
Harlingen	KGBT-TV 4
Houston	KPRC-TV 2
	KHOU-TV 11
	KTRK-TV 13
	KUHT 8
Laredo	KGNS-TV 8
Lubbock	KCBD-TV 11
	KDUB-TV 13
Lufkin	KTRE-TV 9
Midland	KMID-TV 2
Monahans	KVKM-TV 9
Odessa	KOSA-TV 7
Port Arthur-Beaumont	KPAC-TV 4
	KRET-TV 23
Richardson	KCTV 8
San Angelo	KCOR-TV 41
San Antonio	KENS-TV 5
	KONO-TV 12
	WOAI-TV 4
	KPAR-TV 12
	KCEN-TV 6
	KCMC-TV 6
	KLTV 7
	KWTX-TV 10
	KRGV-TV 5

Location	C.L. Chan.
Wichita Falls	KFDX-TV 8
	KSYD-TV 8
UTAH	
Ogden	KVOG-TV 9
	KWCS-TV 18
Provo	KLOR-TV 11
Salt Lake City	KSL-TV 5
	KCPX-TV 4
	KUED 7
	KUTV 2

VERMONT	
Burlington	WCAX-TV 3

VIRGINIA	
Bristol	WCYB-TV 5
Hampton	WVEC-TV 13
Harrisonburg	WSVA-TV 3
Lynchburg	WLVA-TV 13
Norfolk	WTAR-TV 3
Petersburg	WXEX-TV 8
Portsmouth	WAVY-TV 10
Richmond	WRVA-TV 12
	WTVR 8
Roanoke	WDBJ-TV 7
	WSLS-TV 10

WASHINGTON	
Bellingham	KVOS-TV 12
Ephrata	KBAS-TV 16
Pasco	KEPR-TV 19
Seattle	KCTS-TV 9
	KING-TV 5
	KIRO-TV 7
	KOMO-TV 4
	KHQ-TV 6
	KREM-TV 2
	KXLY-TV 4
Tacoma	KTNT-TV 11
	KPEC-TV 56
	KTPS 62
	KTVW 13
Walla Walla	KNBS 22
Yakima	KIMA-TV 29
	KNDO-TV 23

WEST VIRGINIA	
Bluefield	WHIS-TV 6
Charleston	WCHS-TV 8
Clarksburg	WBOY-TV 12
Huntington	WHTN-TV 13
	WSAZ-TV 3
Oak Hill	WDAY-TV 4
Parkersburg	WTAP-TV 15
Wheeling	WTRF-TV 7

WISCONSIN	
Eau Claire	WEAU-TV 13
Green Bay	WBAY-TV 2
	WFRV 5
	WKBT 8
La Crosse	WHA-TV 21
Madison	WISC-TV 3
	WKOW-TV 27
	WMTV 33
Marinette	WMBV-TV 11
Milwaukee	WISN-TV 12
	WITI-TV 6
	WMVS-TV 10
	WTMJ-TV 4
	WXIX 18
Wausau	WSAU-TV 7

WYOMING	
Casper	KTWO-TV 2
Cheyenne	KFBC-TV 5
Riverton	KWRB-TV 10

PUERTO RICO	
Aquadilla	WOLE-TV 12
Caguas	WKBM-TV 11

Canadian Television Stations

Location	C.L. Chan.
ALBERTA	
Calgary	CHCT-TV 2
	CFCN-TV 4
Edmonton	CFRN-TV 3
Lethbridge	CJLH-TV 7
Lloydminster	CHSA-TV 2
Medicine Hat	CHAT-TV 6
Red Deer	CHCA-TV 6
BRITISH COLUMBIA	
Dawson Creek	CJDC-TV 5
Kamloops	CFCR-TV 4
Kelowna	CHBC-TV 2
	CHGP-TV-1 72
Oliver	CHBC-TV-3 8
Penticton	CHBC-TV 13
Vancouver	CBUT 2
Vernon	CHBC-TV 7
Victoria	CHEK-TV 6
LABRADOR	
Goose Bay	CFLA-TV 8

Location	C.L. Chan.
MANITOBA	
Baldy Mountain	CKOS-TV-1 8
Brandon	CKX-TV 5
Winnipeg	CBWT 3
	CBWFT 6
NEW BRUNSWICK	
Campbellton	CKAM-TV 12
Moneton	CKCW-TV 2
	CBAFT 11
Saint John	CHSJ-TV 4
NEWFOUNDLAND	
Argentia	CJOX-TV 10
Corner Brook	CBYT 5
	CHEK-TV 6
Grand Falls	CJCN-TV 4
St. John's	CJON-TV 6
Stephenville	CFSN-TV 8
NOVA SCOTIA	
Hallfax	CBHT 3
Inverness	CJCB-TV-1 6
Liverpool	CBHT-1 12

Location	C.L. Chan.
New Glasgow	CFCY-TV-1 7
Shelburne	CBHT-2 8
Sydney	CJCB-TV 4
Yarmouth	CBHT-3 11
ONTARIO	
Barrie	CKVR-TV 3
Cornwall	CJSS-TV 8
Elk Lake	CFCL-TV-2 2
Elliot Lake	CKSO-TV-1 3
Hamilton	CHCH-TV 11
Kapuskasing	CFCL-TV-1 3
Kenora	CBWAT 8
Kingston	CKWS-TV 11
Kitchener	CKCO-TV 13
London	CFPL-TV 10
North Bay	CKGN-TV 10
Peterborough	CHEX-TV 12
Ottawa	CBFT 9
	CBOT 4
Port Arthur	CFCJ-TV 2
Sault Ste. Marie	CJIC-TV 2
Sudbury	CKSO-TV 5
Timmins	CFCL-TV 6
Toronto	CBLT 6
Windsor	CKLW-TV 9
Wingham	CKNX-TV 8

Location	C.L. Chan.
PRINCE EDWARD ISLAND	
Charlottetown	CFCY-TV 13
QUEBEC	
Carleton	CHAU-TV 5
Clermont	CFCV-TV-1 75
Estcourt	CJES-TV-1 70
Jonquiere	CKRS-TV 12
Matane	CKBL-TV 9
Montreal	CBFT 2
	CBMT 6
Quebec	CFCM-TV 4
	CKMI-TV 5
Rimouski	CJBR-TV 3
Rouyn	CKRN-TV 4
Sherbrooke	CHLT-TV 7
Three Rivers	CKTM-TV 13
SASKATCHEWAN	
Moose Jaw	CHAB-TV 4
Prince Albert	CKBI-TV 5
Regina	CKCK-TV 2
Saskatoon	CFQC-TV 8
Saskatoon	CFJB-TV 5
Swift Current	CFQC-TV 8
Yorkton	CKOS-TV 3

World-Wide Short-Wave Stations

Most international broadcasting is done within frequency limits agreed upon at international conventions. These frequency ranges are listed here, at the right, expressed both in frequency and by meter bands (wave-length).

Reception in the various bands varies according to the time of day and season of the year. Reception in the 60, 49 and 41 meter bands is best at night during the winter months. Reception in the 31 and 25 M. bands is best at night, but all year. Reception in the 19, 16, 13 and 11 M. bands is best during the day, also at night during the summer in the 16 and 19 M. bands.

Abbr.: AIR—All India Radio; RAI—Radiotelevisione Italiana; RTF—Radiodiffusion Television Francaise; VOA—Voice of America; RFE—Radio Free Europe. • denotes stations beaming evening (U.S.) broadcasts to the U.S., † morning or afternoon broadcasts.

METER BANDS

- 4750 to 5060 kc/s (60 meter band)
- 5950 to 6200 kc/s (49 meter band)
- 7100 to 7300 kc/s (41 meter band)
- 9500 to 9775 kc/s (31 meter band)
- 11700 to 11975 kc/s (25 meter band)
- 15100 to 15450 kc/s (19 meter band)
- 17700 to 17900 kc/s (16 meter band)
- 21450 to 21750 kc/s (13 meter band)
- 25600 to 26100 kc/s (11 meter band)

Kcs. Call and Location

- 4630 HCGBI, Quito, Ecu.
- 4765 HJEF, Cali, Col.
- 4770 ELWA, Monrovia, Lib.
- 4770 YVMW, Puntó Fiji, Ven.
- 4775 Libreville, Gabon Rep.
- 4780 YVLA, Valencia, Ven.
- 4790 YVQN, Puerto La Cruz, Ven.
- 4795 Rangoon, Burma
- 4805 ZYS8, Manaus, Braz.
- 4810 YVMG, Maracaibo, Ven.
- 4830 YVOA, San Cristobal, Ven.
- 4835 HJKE, Bogota, Col.
- 4840 Lourenco Marques, Moz.
- 4840 YVOI, Valera, Ven.
- 4845 HJGF, Bucaramanga, Col.
- 4850 YVMS, Barquisimeto, Ven.
- 4870 Cotonou, Dahomey Rep.
- 4880 YVKF, Caracas, Ven.
- 4893 Dakar, Mali Fed.
- 4895 PRF6, Manaus, Braz.
- 4898 HJAG, Barranquilla, Col.
- 4900 YVKP, Caracas, Ven.
- 4905 HRQN, Puerto Cortes, Hon.
- 4910 HCIMI, Quito, Ecu.
- 4910 Conakry, Guinea
- 4915 Accra, Ghana
- 4920 VLM4, Brisbane, Aus.
- 4920 YVKR, Caracas, Ven.
- 4930 HCIRC, Quito, Ecu.
- 4935 HJLF, Ibaguè, Col.
- 4940 Abidjan, Ivory Coast
- 4940 YVMO, Barquisimeto, Ven.
- 4945 HJCV, Bogota, Col.
- 4945 Paradys, So. Afr.
- 4950 Dakar, Mali Fed.
- 4950 YVMM, Coro, Ven.
- 4955 CR6RZ, Luanda, Ang.
- 4960 YVQA, Cumana, Ven.
- 4970 YVLK, Caracas, Ven.
- 4975 Yaounde, Cameroun
- 4990 Lagos, Nigeria
- 4990 YVMQ, Barquisimeto, Ven.
- 5010 HCRCX, Quito, Ecu.
- 5010 St. George, Grenada, B.W.I.
- 5020 HJFW, Manizales, Col.
- 5020 Niamey, Niger Rep.
- 5030 YVKM, Caracas, Ven.
- 5040 YVMA, Maracaibo, Ven.
- 5045 Lome, Togo
- 5050 YVKD, Caracas, Ven.
- 5075 HJGC, Bogota, Col.
- 5873 HRN, Tegucigalpa, Hond.
- 5940 Moscow, U.S.S.R.
- 5952 TUNA, Guatemala, Guat.
- 5954 TIQ, Puerto Limon, C. R.
- 5960 HJCF, Bogota, Col.
- 5965 YNWW, Granada, Nie.
- 5980 TGAR, Guatemala, Guat.
- 5981 Georgetown, Br. Guiana
- 5982 4VB, Port-au-Prince, Haiti
- 5990 Andorra, Andorra
- 5990 TGJA, Guatemala, Guat.
- 5995 Fort-de-France, Mart.
- 6002 4VEC, Cap Haitien, Haiti
- 6005 RIAS, Berlin, Ger.
- 6006 TIHBG, San Jose, C. R.
- 6010 XEOL, Mexico City, Mexico
- 6015 PRA8, Recife, Braz.
- 6020 Amman, Jordan
- 6020 Kiev, Ukrainian S.S.R.
- 6025 Kuala Lumpur, Malaya
- 6025 Hilversum, Neth.
- 6030 Baghdad, Iraq
- 6035 Rangoon, Burma
- 6035 HRTL, Tegucigalpa, Hond.
- 6037 TIFC, San Jose, C. R.
- 6037 Monte Carlo, Mon.
- 6040 HJLB, Ibaguè, Col.
- 6045 YOF, Jakarta, Indon.
- 6045 HOU3I, David, Pan.
- 6050 HCJB, Quito, Ecu.
- 6050 BBC, London, Eng.
- 6055 HJEX, Cali, Col.
- 6055 JOZ2, Tokyo, Japan

Kcs. Call and Location

- 6060 RAI, Caltanissetta, It.
- 6065 XEXG, Leon, Mex.
- 6065 Horby, Sweden
- 6070 Sofia, Bulgaria
- 6070 BBC, London, Eng.
- 6075 Norden, Ger.
- 6080 ZL7, Wellington, N.Z.
- 6082 OAX4Z, Lima, Peru
- 6085 Munich, Ger.
- 6090 VLI6, Sydney, Aus.
- 6090 Luxembourg, Lux.
- 6090 XECMT, C. El Mante, Mex.
- 6095 ZYB7, Sao Paulo, Braz.
- 6100 VOA, Munich, Ger.
- 6100 Belgrade, Yugo.
- 6103 Peking, China
- 6105 XEQM, Merida, Mex.
- 6105 Tunis, Tunisia
- 6110 BBC, London, Eng.
- 6115 ZYC7, Rio de Jan., Braz.
- 6115 Khabarovsk, U.S.S.R.
- 6120 LRXI, Buenos Aires
- 6120 BBC, Limassol, Cyprus
- 6130 Port Moresby, New Guinea
- 6130 Madrid, Spain •
- 6135 HRMF, La Ceiba, Hond.
- 6135 Papeete, Tahiti
- 6135 Singapore, Sing.
- 6140 HCOV5, Azogues, Ecu.
- 6140 VLW6, Perth, Aus.
- 6145 Algiers, Algeria
- 6147 PRL9, Rio de Jan., Braz.
- 6150 VLR6, Melbourne, Aus.
- 6150 BBC, London, Eng.
- 6155 4VWA, Cap Haitien, Haiti
- 6155 VOA, Salonika, Greece
- 6160 HJKJ, Bogota, Col.
- 6160 FEN, Tokyo, Japan
- 6165 HER3, Bern, Switz. •
- 6165 XEWW, Mexico City, Mex.
- 6165 Saigon, Vietnam
- 6170 BBC, Limassol, Cyprus
- 6170 Cayenne, Fr. Guiana
- 6175 RTF, Paris, France
- 6180 BBC, London, England
- 6185 HJCT, Bogota, Col.
- 6190 VOA, Munich, Ger.
- 6190 HVJ, Vatican City
- 6195 HJEZ, Cali, Col.
- 6195 HRD2, La Ceiba, Hond.
- 6195 Pyongyang, N. Korea
- 6200 H2LR, C. Trujillo, D.R.
- 6200 4VHW, Port-au-Prince, Haiti
- 6208 TGHC, Guatemala, Guat.
- 6215 Pyongyang, N. Korea
- 6225 Peking, China
- 6305 Andorra, Andorra
- 6327 COCF, Havana, Cuba
- 6345 Ulan Bator, Mong.
- 6373 Lisbon, Port.
- 6790 BBC, Limassol, Cyprus
- 7105 Madrid, Spain
- 7110 VOA, Colombo, Ceylon
- 7110 BBC, London, England
- 7115 Rabat, Morocco
- 7115 RFE, Germ.
- 7120 BBC, London, England
- 7120 BBC, Singapore
- 7125 Warsaw, Poland
- 7140 Monte Carlo, Monaco
- 7145 RFE, Ger.
- 7150 Khabarovsk, U.S.S.R.
- 7160 RTF, Paris, France
- 7160 VOA, Tangier, Mor.
- 7165 RFE, Germ.
- 7170 Algiers, Alg.
- 7180 Baghdad, Iraq
- 7185 BBC, London, Eng.
- 7200 BBC, London, Eng. •
- 7200 R. Malaya, Sing.
- 7200 Omdurman, Sudan
- 7205 VOA, Salonika, Gr.
- 7210 BBC, London, Eng.
- 7210 Dakar, Mali Fed.
- 7210 Khabarovsk, U.S.S.R.
- 7220 VLD7, Melbourne, Aus.
- 7220 Budapest, Hung.
- 7230 BBC, London, Eng.
- 7235 Taipei, Taiwan, China
- 7235 VOA, Munich, Ger.

Kcs. Call and Location

- 7240 RTF, Paris, France
- 7250 BBC, London, Eng.
- 7255 Sofia, Bulg.
- 7260 Saigon, Vietnam
- 7270 Metola, Sweden
- 7270 Magadan, U.S.S.R.
- 7275 RAI, Rome, It.
- 7280 Teheran, Iran
- 7280 HVJ, Vat. City
- 7285 Ankara, Turk.
- 7290 RAI, Rome, It.
- 7295 Makassar, Celebes
- 7295 RFE, Ger.
- 7320 BBC, London, Eng.
- 7398 Damascus, U.A.R.
- 7505 Peking, China
- 7650 YNMS, Leon, Nic.
- 7670 Sofia, Bulg.
- 7850 Tirana, Alb.
- 8002 Beirut, Leb.
- 8900 HCJG3, Zaruma, Ecu.
- 9009 Tel Aviv, Israel
- 9026 COBZ, Havana, Cuba
- 9065 Peking, China
- 9210 Leopoldville, Congo
- 9360 Madrid, Spain •
- 9363 COBC, Havana, Cuba
- 9380 Alma Ata, Kazakh S.S.R.
- 9385 Leopoldville, Congo
- 9410 BBC, London, Eng.
- 9440 CP38, La Paz, Bol.
- 9458 Peking, China
- 9500 XEWW, Mexico City, Mex.
- 9500 Magadan, U.S.S.R.
- 9500 Moscow, U.S.S.R.
- 9505 PRB22, Sao Paulo, Braz.
- 9505 Rabat, Mor.
- 9505 HDLA, Colon, Pan.
- 9510 Peking, China
- 9510 VOA, Tangier, Mor.
- 9515 RAI, Caltanissetta, It.
- 9515 Ankara, Turkey •
- 9520 Colombo, Ceylon
- 9520 Copenhagen, Den. •
- 9520 VOA, Salonika, Gr.
- 9520 OAX8E, Iquitos, Peru
- 9523 Paradys, S. Afr.
- 9525 BBC, London, Eng.
- 9525 JOB9, Tokyo, Japan
- 9525 Warsaw, Poland
- 9530 COCO, Havana, Cuba
- 9530 VOA, Munich, Ger.
- 9530 AIR, Delhi, India
- 9530 VOA, Courier, Rhodes
- 9530 YVMZ, Maracaibo, Ven.
- 9535 Lagos, Nigeria
- 9535 VOA, Manila, P.I.
- 9535 HER4, Bern, Switz. •
- 9540 ZL2, Wellington, N.Z.
- 9540 Warsaw, Poland
- 9540 Omdurman, Sudan
- 9545 ZYS43, Curitiba, Braz.
- 9545 HED5, Bern, Switz.
- 9550 Prague, Czecho. •
- 9550 AIR, Bombay, India
- 9550 OAXIZ, Tumbes, Peru
- 9555 CP6, La Paz, Bol.
- 9555 BBC, London, Eng.
- 9555 XETT, Mexico City, Mex.
- 9560 RTF, Paris, France
- 9560 Tokyo, Japan
- 9563 OAX4R, Lima, Peru
- 9565 ZYK3, Recife, Braz.
- 9565 Radio Liberty, Ger.
- 9565 Khabarovsk, U.S.S.R.
- 9570 Bucharest, Rom. •
- 9575 ZYZZ7, Rio de Jan., Braz.
- 9575 Taipei, Formosa
- 9575 RAI, Rome, Italy •
- 9580 VLA9, Melbourne, Aus.
- 9580 BBC, London, Eng.
- 9585 ZYR56, Sao Paulo, Braz.
- 9585 RTF, Paris, France
- 9588 Peking, China
- 9590 Djakarta, Indon.
- 9590 Hilversum, Neth.
- 9590 Bucharest, Rom. •
- 9595 JOZ3, Tokyo, Japan
- 9598 CE960, Santiago, Chile
- 9600 BBC, London, Eng.
- 9605 Cologne, Ger.
- 9607 Athens, Greece
- 9610 VLX9, Perth, Aus.

Kcs. Call and Location

- 9610 ZYC8, Rio de Jan., Braz.
- 9610 Oslo, Norway •
- 9610 OAX8C, Iquitos, Peru
- 9615 VOA, Tangier, Morocco
- 9620 ZYR98, Sao Paulo, Braz.
- 9620 Peking, China
- 9620 VOA, Tangier, Mor.
- 9620 Saigon, Vietnam
- 9625 Brazzaville, Equat. Un.
- 9625 BBC, London, Eng.
- 9625 OAX8K, Iquitos, Peru
- 9625 Moscow, U.S.S.R.
- 9630 CR6RL, Luanda, Ang.
- 9630 VLG9, Melbourne, Aus.
- 9630 RAI, Rome, Italy
- 9630 Komsomolsk, U.S.S.R.
- 9635 ZYR83, Aparecida, Braz.
- 9635 VOA, Munich, Ger.
- 9635 Lisbon, Portugal •
- 9640 BBC, London, Eng.
- 9640 Cologne, Germany •
- 9640 Accra, Ghana
- 9640 HLK5, Seoul, Korea
- 9640 Moscow, U.S.S.R.
- 9645 TIFC, San Jose, C.R.
- 9645 HVJ, Vatican City
- 9650 BBC, Limassol, Cyprus
- 9655 Radio Free Europe, Ger.
- 9660 LRX, Buenos Aires, Arg.
- 9660 VLQ9, Brisbane, Aus.
- 9660 Radio Liberty, Ger.
- 9660 Teheran, Iran
- 9660 Komsomolsk, U.S.S.R.
- 9665 Moscow, U.S.S.R.
- 9667 Hargeisa, Somalia
- 9667 TUNA, Guatemala, Guat. •
- 9670 COCQ, Havana, Cuba
- 9670 Prague, Czecho.
- 9675 BBC, London, Eng.
- 9675 RTF, Paris, France
- 9675 JOB9, Tokyo, Japan
- 9675 Warsaw, Poland •
- 9680 VLH9, Melbourne, Aus.
- 9680 XEQQ, Mexico City, Mex.
- 9680 VOA, Tangier, Mor.
- 9680 Paradys, S. Afr.
- 9685 Algiers, Algeria
- 9690 LRA, Buenos Aires, Arg. •
- 9690 BBC, London, Eng.
- 9690 BBC, Singapore
- 9700 Sofia, Bulgaria •
- 9700 Rabat, Morocco
- 9705 Kabul, Afghan.
- 9705 Brussels, Belg.
- 9705 AIR, Delhi, India
- 9705 Radio Free Europe, Port.
- 9710 BBC, London, Eng.
- 9710 RAI, Rome, It.
- 9715 Hilversum, Neth. •
- 9715 Radio Free Europe, Ger.
- 9720 Paradys, S. Afr.
- 9725 Tel Aviv, Israel
- 9725 RFE, Port.
- 9725 BBC, Singapore
- 9730 Brazzaville, Equat. Un.
- 9730 Leipzig, E. Ger.
- 9730 DZH7, Manila, P.I.
- 9735 Peking, China
- 9735 BBC, London, Eng.
- 9735 Cologne, Germany
- 9735 AIR, Madras, India
- 9740 VOA, Tangier, Mor.
- 9742 LRSI, Buenos Aires, Arg.
- 9745 Brussels, Belg.
- 9745 HCJB, Quito, Ecu. •
- 9745 Ankara, Turk.
- 9745 Moscow, U.S.S.R.
- 9750 BBC, London, Eng.
- 9750 Radio Free Europe, Port.
- 9750 Khabarovsk, U.S.S.R.
- 9755 ZYW29, Goiania, Braz.
- 9755 RTF, Paris, France
- 9755 Saigon, Vietnam
- 9760 BBC, London, Eng.
- 9762 Hanoi, N. Vietnam
- 9765 Moscow, U.S.S.R.
- 9770 Brazzaville, Equat. Un.
- 9770 BBC, London, Eng.
- 9775 Moscow, U.S.S.R.

Kcs. Call and Location

9795 Cairo, U.A.R. ●
 9800 Peking, China
 9800 Moscow, U.S.S.R.
 9805 Cairo, U.A.R.
 9825 BBC, London, Eng. ●
 9833 Budapest, Hung. ●
 9840 Hanoi, N. Vietnam
 9850 AIR, Delhi, India
 9860 Peking, China
 9870 Djakarta, Indon.
 9895 Bengazi, Libya
 9915 BBC, London, Eng.
 9973 Peking, China
 10335 Ulan Bator, Mong.
 10530 Alma Ata, Kazakh S.S.R.
 11290 Peking, China
 11570 Moscow, U.S.S.R.
 11600 Peking, China
 11630 Moscow, U.S.S.R.
 11650 Peking, China
 11665 Cairo, U.A.R.
 11675 Peking, China
 11675 Karachi, Pak.
 11680 BBC, London, Eng.
 11685 HVJ, Vat. City
 11690 Moscow, U.S.S.R. ●
 11700 RTF, Paris, France
 11705 JOAII, Tokyo, Japan
 11705 Horby, Sweden
 11705 Moscow, U.S.S.R.
 11710 VLBII, Melbourne, Aus. †
 11710 AIR, Delhi, India
 11710 WBOU, New York, N.Y.
 11715 VOA, Munich, Ger.
 11715 Moscow, U.S.S.R.
 11717 Athens, Greece
 11720 Brazilia, Brazil
 11720 BBC, Limassol, Cyprus
 11725 Brazzaville, Equat. Un.
 11725 Prague, Czecho.
 11725 BBC, Singapore
 11730 Hilversum, Neth. ●
 11735 Rabat, Morocco
 11735 Moscow, U.S.S.R. ●
 11740 VLCII, Melbourne, Aus.
 11740 CEI174, Santiago, Chile
 11740 Peking, China
 11740 VOA, Tangier, Mor.
 11745 RFE, Germ.
 11750 BBC, London, Eng.
 11750 FEN, Tokyo, Japan
 11755 RFE, Port.
 11755 Hilversum, Neth. ●
 11755 Komsomolsk, U.S.S.R.
 11760 VLBII, Melbourne, Aus.
 11760 VOA, Munich, Ger.
 11760 VOA, Tangier, Mor.
 11760 Lourenco Marques, Moz.
 11760 Hanoi, N. Vietnam
 11765 ZYB8, Sao Paulo, Braz.
 11765 Berlin, E. Germany
 11770 Colombo, Ceylon
 11770 BBC, London, Eng.
 11775 ZYZ28, Rio de Jan., Braz.
 11775 Moscow, U.S.S.R.
 11780 BBC, London, Eng. ●
 11785 Djakarta, Indon.
 11785 VOA, Tangier, Morocco
 11790 BBC, London, Eng.
 11790 VOA, Manila, P.I.
 11790 Moscow, U.S.S.R.
 11795 Cologne, Ger. ●
 11795 Djakarta, Indon.
 11800 BBC, London, Eng.
 11802 Warsaw, Poland ●
 11805 RAI, Rome, It.
 11805 VOA, Courier, Rhodes
 11810 VLBII, Melbourne, Aus. †
 11810 RAI, Rome, It.
 11810 Amman, Jordan
 11810 Bucharest, Rom. ●
 11810 Horby, Sweden ●
 11815 Madrid, Spain
 11820 Peking, China
 11820 BBC, London, Eng.
 11820 XEBR, Hermosillo, Mex.
 11825 ELWA, Monrovia, Lib.
 11830 WRUL, Boston, U.S.A.
 11830 Moscow, U.S.S.R.
 11835 Algiers, Alg.
 11835 VOA, Colombo, Ceylon
 11835 CXA19, Montevideo, Urug.
 11840 Prague, Czecho.
 11840 VOA, Tangier, Mor.
 11840 Lisbon, Port. ●
 11840 Khabarovsk, U.S.S.R.
 11840 Hanoi, N. Vietnam
 11845 RTF, Paris, France
 11845 Karachi, Pak.
 11850 Sofia, Bulg.
 11850 AIR, Bombay, India
 11850 Oslo, Norway ●
 11855 Brussels, Belg. ●
 11855 Radio Free Europe, Ger.
 11855 DZH8, Manila, P.I.
 11860 Peking, China
 11860 BBC, London, Eng.
 11860 Moscow, U.S.S.R.
 11865 PRA8, Recife, Braz.
 11865 VOA, Tangier, Mor.
 11865 HER5, Bern, Switz. ●
 11865 Tunis, Tun.
 11870 Moscow, U.S.S.R.
 11875 ZYN32, Salvador, Braz.

Kcs. Call and Location

11875 VOA, Colombo, Ceylon
 11875 VOA, Tangier, Mor.
 11880 BBC, London, Eng.
 11880 XEHH, Mexico City, Mex.
 11885 Peking, China
 11885 Karachi, Pak.
 11885 Radio Free Europe, Ger.
 11890 Moscow, U.S.S.R.
 11895 Dakar, Mali Fed.
 11895 VOA, Tangier, Mor.
 11895 VOA, Manila, P.I.
 11900 Bucharest, Rumania ●
 11900 CXA10, Montevideo, Ur.
 11900 Moscow, U.S.S.R.
 11905 RAI, Rome, Italy ●
 11905 WDSI, New York, U.S.A.
 11910 BBC, London, Eng.
 11910 Budapest, Hung. ●
 11910 Bangkok, Thai.
 11915 HCJB, Quito Ecua. ●
 11915 Hilversum, Neth.
 11920 RAI, Paris, France
 11920 DXF2, Manila, P.I.
 11920 WLWO, Cincinnati, U.S.A.
 11925 ZYR78, Sao Paulo, Braz.
 11925 HLK6, Seoul, Korea †
 11925 Warsaw, Pol.
 11925 Moscow, U.S.S.R.
 11930 BBC, London, Eng.
 11930 BBC, Singapore
 11935 Radio Liberty, Ger.
 11940 CEI190, Valparaiso, Chile
 11940 JOBII, Tokyo, Japan
 11945 Peking, China
 11945 BBC, London, Eng.
 11945 Cologne, Germany ●
 11950 Warsaw, Poland
 11950 Jidda, Saudi Arab.
 11950 Moscow, U.S.S.R.
 11955 BBC, London, Eng.
 11955 BBC, Singapore
 11960 CEI196, Santiago, Ch.
 11960 Moscow, U.S.S.R. ●
 11965 Radio Liberty, Ger.
 11970 Caracas, Ven.
 11972 Brazzaville, Equat. Un. ●
 11975 Peking, China
 11975 Moscow, U.S.S.R. ●
 11985 Moscow, U.S.S.R.
 11985 ELWA, Monrovia, Lib. ●
 11990 Prague, Czecho.
 12000 Moscow, U.S.S.R.
 12010 Hanoi, Vietnam
 12020 AIR, Delhi, India
 12020 Moscow, U.S.S.R.
 12040 BBC, London, Eng.
 12050 Cairo, U.A.R.
 12095 BBC, London, Eng.
 15020 Hanoi, N. Vietnam
 15030 Peking, China
 15060 Peking, China
 15070 BBC, London, Eng.
 15085 Grenada, Windward Is., BWI
 15095 Peking, China
 15100 Lisbon, Port.
 15100 Moscow, USSR
 15105 ZYZ32, Rio de Jan., Braz.
 15105 AIR, Delhi, India
 15110 BBC, London, Eng.
 15110 Moscow, USSR ●
 15115 HCJB, Quito, Ecuador ●
 15115 Peking, China
 15120 Colombo, Ceylon
 15120 RAI, Rome, Italy
 15120 Warsaw, Poland †
 15120 HVJ, Vatican City
 15125 ZYN31, Salvador, Brazil
 15125 Prague, Czecho.
 15125 Seoul, Korea ●
 15125 VOA, Manila, P.I.
 15125 Lisbon, Portugal ●
 15130 RTF, Paris, France
 15130 VOA, Manila, P.I.
 15130 KCBR, Delano, Calif.
 15130 WBOU, New York, USA
 15130 Moscow, USSR
 15135 PRB23, Sao Paulo, Braz.
 15135 JOB15, Tokyo, Japan
 15135 Radio Free Europe, Port.
 15140 Peking, China
 15140 BBC, London, Eng.
 15140 AIR, Delhi, India
 15140 Komsomolsk, USSR
 15145 ZYK33, Recife, Brazil
 15145 Radio Free Europe, Port.
 15148 CEI515, Santiago, Chile
 15150 Djakarta, Indonesia
 15150 Lourenco Marques, Moz.
 15150 Lisbon, Portugal
 15150 Moscow, USSR ●
 15153 OAX4T, Lima, Peru
 15155 ZYB9, Sao Paulo, Brazil
 15155 Karachi, Pakistan
 15155 VOA, Manila, P.I.
 15155 WBOU, New York, USA
 15155 Moscow, USSR
 15160 VLA15, Melbourne, Aus.
 15160 RTF, Paris, France
 15160 XEWW, Mexico City, Mex.
 15160 Ankara, Turkey
 15160 Moscow, USSR
 15165 ZYN7, Fortaleza, Braz.
 15165 Copenhagen, Denmark
 15165 Damascus, UAR
 15170 Tromse, Norway

Kcs. Call and Location

15170 DBX4C, Lima, Peru
 15170 Radio Free Europe, Port.
 15175 Peking, China
 15175 Oslo, Norway ●
 15180 BBC, London, Eng.
 15180 AIR, Delhi, India
 15180 Moscow, USSR
 15185 VOA, Manila, P.I.
 15185 Radio Free Europe, Port.
 15185 WDSI, New York, USA
 15190 Brazzaville, Congo Rep.
 15190 Helsinki, Finland †
 15190 Komsomolsk, USSR
 15190 Moscow, USSR
 15195 Prague, Czecho.
 15195 Radio Free Europe, Ger.
 15195 Ankara, Turkey
 15200 Paradys, South Africa
 15200 WDSI, New York, USA
 15200 Moscow, USSR
 15205 XESC, Mexico City, Mex.
 15205 WDSI, New York, USA
 15210 VLG15, Melbourne, Aus.
 15210 VOA, Manila, P.I.
 15210 KCBR, Delano, Calif., USA
 15210 Moscow, USSR
 15215 Radio Free Europe, Port.
 15215 VOA, Okinawa, Ryukyu Is.
 15220 Hilversum, Neth. †
 15225 Taipei, Taiwan, China
 15225 Radio Liberty, Germany
 15225 Moscow, USSR
 15230 VLBII, Melbourne, Aus.
 15230 VOA, Colombo, Ceylon
 15230 BBC, London, Eng.
 15235 JOB15, Tokyo, Japan
 15235 VOA, Tangier, Morocco
 15235 Komsomolsk, USSR
 15240 VLA15, Melbourne, Aus.
 15240 Horby, Sweden
 15240 Moscow, USSR
 15240 Belgrade, Yugoslavia
 15245 ZYE21, Belém, Brazil
 15250 VOA, Manila, P.I.
 15250 Bucharest, Rumania ●
 15250 WLWO, Cincinnati, USA
 15255 Radio Free Europe, Port.
 15257 FEN, Tokyo, Japan
 15260 BBC, London, England
 15265 Colombo, Ceylon
 15265 Moscow, USSR
 15270 Peking, China ●
 15270 AIR, Bombay, India
 15270 VOA, Tangier, Morocco
 15270 WBOU, New York, (VOA)
 15270 WDSI, New York, USA
 15275 Cologne, Germany
 15275 Karachi, Pakistan
 15275 VOA, Manila, P.I.
 15275 Warsaw, Poland ● †
 15280 ZL4, Wellington, N.Z.
 15280 Moscow, USSR
 15285 Brussels, Belgium
 15285 Prague, Czecho.
 15285 AIR, Bombay, India
 15285 WBOU, New York, USA
 15290 LRU, Buenos Aires, Arg.
 15290 Peking, China
 15290 KCBR, Delano, Calif., USA
 15290 WLWO, Cincinnati, USA
 15295 Rio de Janeiro, Brazil
 15295 RTF, Paris, France
 15295 VOA, Tangier, Morocco
 15295 Moscow, USSR ●
 15300 BBC, London, Eng. †
 15300 DZH9, Manila, P.I.
 15305 Dacca, Pakistan
 15305 Moscow, USSR
 15310 BBC, London, England ●
 15310 BBC, Singapore
 15310 KCBR, Delano, Calif., USA
 15315 VLC15, Melbourne, Aus.
 15315 Peking, China
 15315 HEU6, Bern, Switz. ●
 15315 Moscow, USSR
 15320 VLC15, Melbourne, Aus.
 15320 AIR, Delhi, India
 15320 VOA, Tangier, Morocco
 15325 ZYR228, Sao Paulo, Braz.
 15325 RAI, Rome, Italy
 15325 JOB15, Tokyo, Japan ●
 15330 VOA, Munich, Germany
 15330 VOC, Salonika, Greece
 15330 WBOU, New York, USA
 15330 WGO, Schenectady, USA
 15335 Brussels, Belgium †
 15335 ZYU68, Porto Alegre, Braz.
 15335 Karachi, Pakistan
 15335 VOA, Manila, P.I.
 15335 Komsomolsk, USSR
 15340 Radio Liberty, Germany
 15340 Moscow, USSR
 15345 LRA, Buenos Aires, Arg.
 15345 Taipei, Taiwan, China
 15345 Athens, Greece
 15345 Rabat, Morocco
 15350 RTF, Paris, France
 15350 WLWO, Cincinnati, USA
 15355 Radio Free Europe, Port.
 15360 BBC, London, England
 15360 Moscow, USSR
 15365 WLWO, Cincinnati, Ohio
 15370 ZYC9, Rio de Jan., Braz.
 15370 Radio Liberty, Germany
 15375 BBC, London, Eng.
 15375 Cologne, Germany †
 15380 VOA, Tangier, Morocco

Kcs. Call and Location

15380 VOA, Okinawa, Ryukyu Is.
 15380 WRUL, Boston, USA
 15385 DZF3, Manila, P.I.
 15385 CXA60, Montevideo, Urug.
 15385 Moscow, USSR
 15390 BBC, London, Eng.
 15390 Moscow, USSR
 15395 Radio Liberty, Germany
 15400 RTF, Paris, France
 15400 RAI, Rome, Italy
 15405 Cologne, Germany
 15405 Moscow, USSR
 15407 Paramaribo, Surinam
 15410 Prague, Czecho. ●
 15410 Radio Liberty, Germany
 15410 VOA, Tangier, Morocco
 15415 AFRS, Munich, Germany
 15415 Budapest, Hungary ●
 15417 Peking, China
 15420 Brazzaville, Congo Rep.
 15417 BBC, London, Eng.
 15420 Madrid, Spain
 15420 Moscow, USSR
 15425 VLX15, Perth, Aus.
 15425 Hilversum, Neth.
 15430 Peking, China ●
 15430 Cairo, UAR
 15430 Moscow, USSR
 15435 BBC, London, Eng.
 15435 BBC, Singapore
 15440 VOA, Munich, Germany
 15440 Moscow, USSR
 15445 Brazzaville, Congo Rep.
 15445 Hilversum, Neth.
 15447 BBC, London, Eng.
 15450 Komsomolsk, USSR
 15465 Paramaribo, Surinam
 15470 Moscow, USSR
 15475 Cairo, UAR
 15480 Peking, China
 15480 AIR, Delhi, India
 15520 Peking, China
 15555 Peking, China
 15610 Peking, China
 17605 Peking, China
 17675 Peking, China
 17690 Cairo, UAR
 17695 BBC, London, Eng.
 17700 BBC, London, Eng.
 17700 Moscow, USSR
 17705 AIR, Delhi, India
 17705 VOA, Tangier, Morocco
 17710 VLG17, Melbourne, Aus.
 17710 WLWO, Cincinnati, USA
 17710 Moscow, USSR
 17715 BBC, London, Eng. ●
 17715 VOA, Colombo, Ceylon
 17720 Peking, China ●
 17720 Brazzaville, Congo Rep.
 17720 Radio Liberty, Germany
 17720 Moscow, USSR
 17722 San Jose dos Campos, Braz.
 17725 Radio Free Europe, Port.
 17725 AIR, Delhi, India
 17730 BBC, London, Eng.
 17730 Radio Liberty, Germany
 17735 Radio Free Europe, Port.
 17735 KCBR, Delano, Calif.
 17735 HVJ, Vatican City
 17740 WLWO, Cincinnati, USA
 17740 BBC, London, Eng.
 17740 Moscow, USSR
 17745 BBC, London, Eng.
 17745 Karachi, Pakistan
 17745 VOA, Manila, P.I.
 17747 Peking, China ●
 17750 WRUL, Boston, USA
 17750 VOA, Tangier, Morocco
 17750 Moscow, USSR
 17755 Prague, Czecho.
 17755 BBC, Singapore
 17760 WGO, Schenectady, USA
 17760 AIR, Delhi, India
 17760 Moscow, USSR
 17765 RTF, Paris, France
 17765 Peking, China ●
 17770 RAI, Rome, Italy
 17770 Radio Free Europe, Port.
 17770 KCBR, Delano, Calif., USA
 17773 Athens, Greece
 17775 Hilversum, Neth.
 17780 WBOU, New York, USA
 17780 VOA, Manila, P.I.
 17780 Moscow, USSR
 17785 HER7, Berne, Switz.
 17785 AIR, Delhi, India
 17788 Taipei, Formosa, China
 17790 BBC, London, Eng.
 17790 Prague, Czecho.
 17790 AIR, Delhi, India
 17795 KGEI, San Fran., USA
 17795 WLWO, Cincinnati, USA
 17795 Moscow, USSR
 17795 CR6RZ, Luanda, Angola
 17800 Helsinki, Finland †
 17800 RAI, Rome, Italy
 17800 Warsaw, Poland †
 17805 Radio Free Europe, Port.
 17805 DZ16, Manila, P.I.
 17810 BBC, London, Eng. †
 17810 AIR, Delhi, India
 17810 Hilversum, Neth.
 17810 Moscow, USSR
 17815 Prague, Czecho.
 17815 Cologne, Germany
 17815 KCBR, Delano, Calif.



JOB COUNSELORS ADVISE LEARN ELECTRONICS

NEW Home Study Course in **ELECTRONICS** Principles-Practices-Maintenance **NOW READY**

This is the Electronic Age. Electronic equipment is already being used to count and control flow of liquids, solids, gases. Electronics is employed to search for oil, make surveys, control traffic, machine complex parts and in atomic installations. Military uses of Electronics are great and expanding rapidly. In business, Automation with Electronics plays an important part, prepares payrolls, calculates engineering formulas.


Learn More to Earn More

Now, to meet the growing demand for trained Electronic Technicians NRI has developed a comprehensive, complete course in Electronics Principles, Practices, Maintenance. This training stresses fundamentals. It is a course specially prepared for beginners and for Technicians. You get both theory and practical experience in an interesting, exciting way.

Ten Special Training Kits Give Practical Experience

You get practical experience with Thyatron Tube circuits, Multivibrators, build a D'Arsonval type Vacuum Tube Voltmeter (Kit 2); work and experiment with pentode tubes, selenium resistors, oscillators, transistors, magnetic amplifiers; and get practical experience in telemetry circuits as used in earth satellites, digital and analog computers (Kit 9).

SPECIAL TRAINING KITS NO EXTRA COST

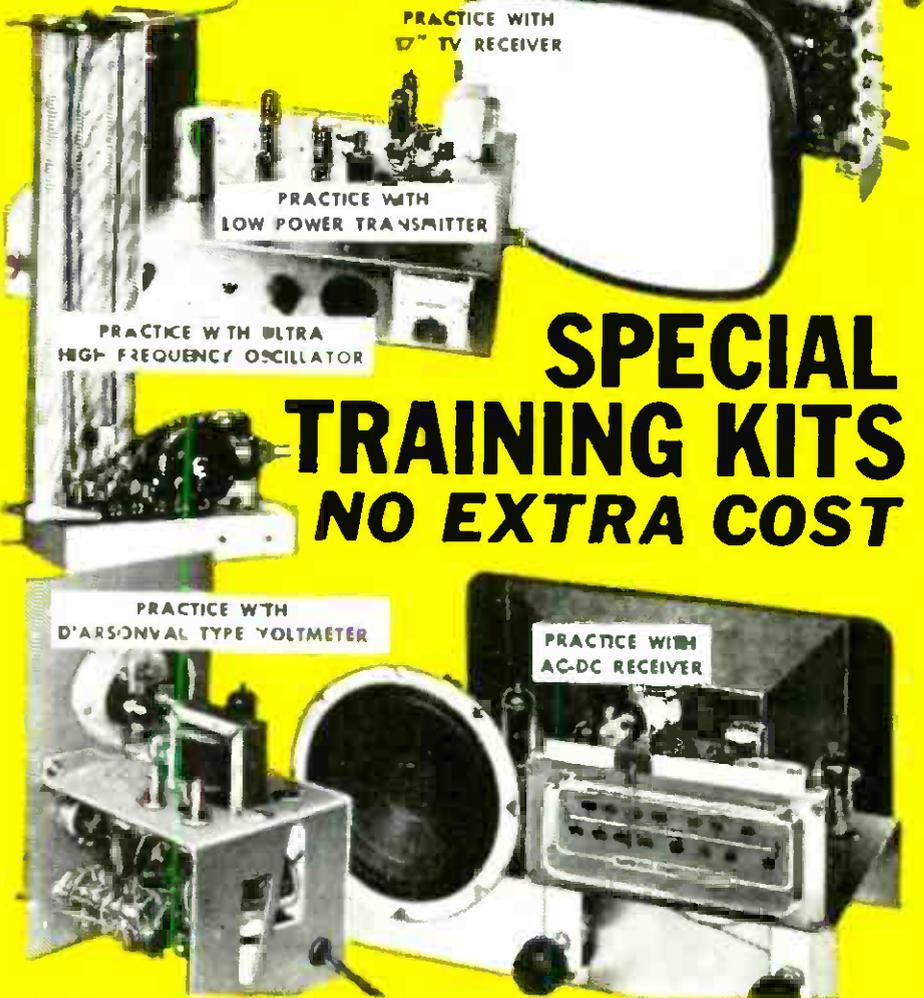

NRI Oldest, Largest School  **SEE OTHER SIDE** 

Wishing for success won't bring success. You must act. Get FREE 64-page Catalog from America's oldest and largest home study Electronic-Radio-Television school. It gives facts, opportunities in Industrial and Military Electronics careers, also shows what you learn, tells about NRI's other courses in Radio Television Servicing and Radio Television Communications. Monthly payments plan. Mail Postage Free Card for 64-page Catalog. NATIONAL RADIO INSTITUTE, Washington 16, D.C.



**POSTAGE FREE CARD
MAIL NOW**

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.

BUSINESS REPLY CARD
No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY
National Radio Institute
3939 Wisconsin Avenue
Washington 16, D.C.



Learn RADIO, TELEVISION

AND ELECTRONICS

by Practicing at Home in Your Spare Time

At No Extra Cost you get specially developed Electronic Training Kits for practical experience. Shop and laboratory practice at home make learning easier, interesting, faster. You do not need a high school diploma or previous experience.


Increasing Demand for Trained Men

This is the Electronics age. Men with Electronic know-how are in demand. They enjoy high pay and growing opportunities for advancement. Satellites, Radar, Automation in Industry; Missiles, Rockets, Planes, Stereo, TV, Radio, Two Way Communications for transportation are a few of the fantastic developments in the fast growing Electronics industry. If you are not completely satisfied with your work; if you are doubtful about your future, investigate Electronics.



High Pay, Prestige, Bright Future

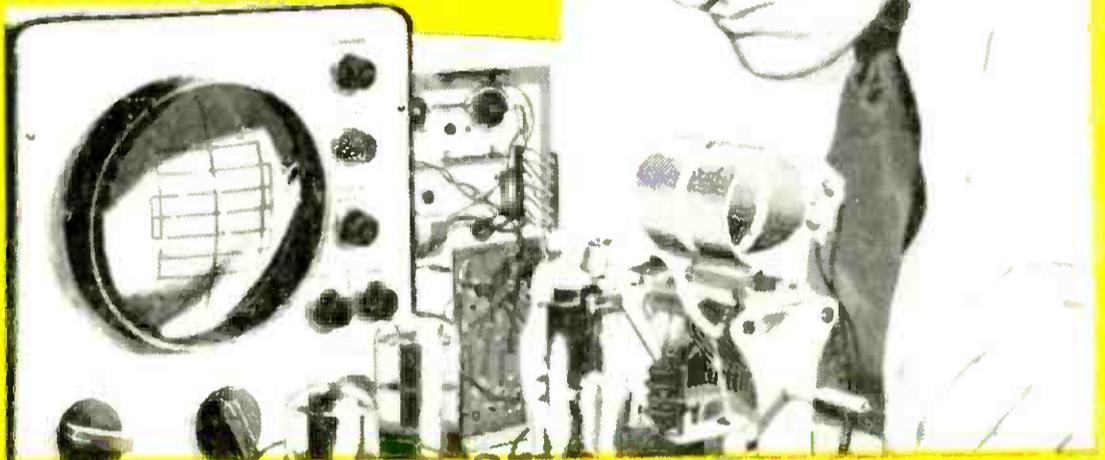What branch of Electronics interests you? Thousands of successful NRI graduates prove that NRI's learn-by-practice method is the way to success. You start in your chosen career way ahead of the man who only learns from books. You do not need to give up your job. You do not need to go away to school. You learn at home, get practical knowledge from training kits NRI provides.



NRI Has Trained Thousands for Success



"I get over twice the salary I made before enrolling. NRI training gave me a thorough understanding." H. ATKINSON, Austin, Tex.



"Now in charge of sound effects for CBC. NRI opened doors to greater opportunity for me." F. TUDOR, Toronto, Ontario.



"Averaged \$150 a month spare time before I graduated. Now have my own full time business." F. W. COX, Hollywood, Cal.

NEW COURSE IN ELECTRONICS TURN PAGE

Cut Out and Mail—No Stamp Needed

64-PAGE CATALOG FREE

No Salesman will call. (Please PRINT) 1BB 3

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
 WASHINGTON 16, D. C.

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL



Train With the Leader

NRI is the world's oldest and largest home study Electronics school. You benefit from the experience NRI has gained from training men for 45 years. NRI offers you proven courses; Principles, Practices and Maintenance—Radio Television Communications—Radio Television Servicing.

Start Soon, Earn More

Soon after enrolling NRI shows you how to apply your knowledge to earn extra money doing Electronic repairs or servicing Radio and Television sets for friends and neighbors. Take the first step toward success now. Find out what NRI offers you. Mail the postage-free card. No obligation. Cost of NRI training is low. Monthly payment plan available. NATIONAL RADIO INSTITUTE, Washington 16, D.C.

