

UP-TO-DATE LIST OF BROADCASTERS

MORE ABOUT THE WHITE SUPER-AMPLIFIER—(See Inside)

15c. a Copy

Vol-4 No-99

February 16

1924

RADIO

Title Reg. U. S. Pat. Off.

WORLD

ILLUSTRATED

EVERY WEEK

GENERAL BUTLER ENLISTS RADIO IN PHILADELPHIA CRUSADE




(C. Keystone View Co.)

Brig.-Gen. Smedley D. Butler, of the Marine Corps, who is on a year's leave of absence to serve as Director of Public Safety of Philadelphia, has made a great "clean-up" in the City of Brotherly Love since January 1. His latest move was to broadcast an address from Station WDAR asking the public's co-operation. Gen. Butler is shown at the right. His assistant, George W. Elliott, is at the left.

FURTHER DETAILS OF THE ULTRADYNE RECEIVER—(See Inside)

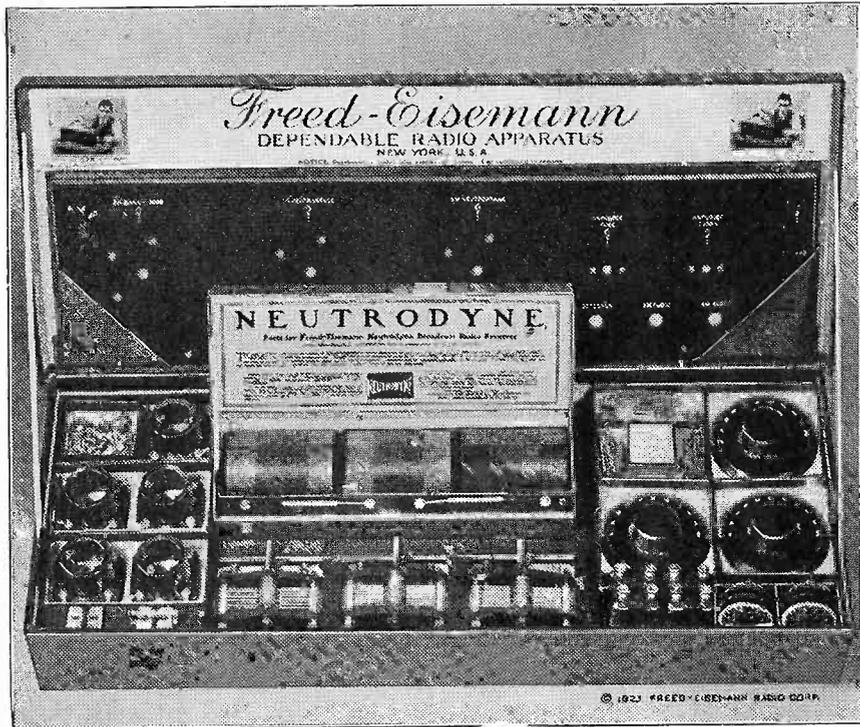A *Freed-Eisemann* KNOCKDOWN NEUTRODYNE RECEIVER



Unassembled, Model KD-50
Freed-Eisemann Neutrodyne Receiver

NOW the opportunity is presented to obtain a complete set of parts, recommended by the manufacturer, to work with each other in building your Neutrodyne set. An illustrated 32-page book on how to build the Neutrodyne with full-sized diagrams and templates included.

Complete
With Full Instructions

\$80

DEALERS! Write for Name
of Nearest Distributor.



Front View KD-50 Neutrodyne Being Assembled

NEUTRODYNE has taken the country by storm. It is the remarkable distance getting, powerful, non-oscillating and non-whistling receiver.


A 32-page book answers every question. The panel is accurately drilled. A baseboard is furnished; in fact, everything down to the very last screw and nut, including all necessary parts excepting the cabinet.

Besides the book there is furnished schematic blueprints and template for drilling the baseboard, also full-size pictorial perspective

wiring diagram, so that it will hardly be possible for the amateur with ordinary care and skill to make an error.

Remember that here are licensed parts—not a collection of apparatus trusting to luck that they will assemble properly. Each part is designed and fitted to work with each other part in this particular set. The instructions are so complete and the parts so accurately matched that you will be grateful for the manner in which we have eliminated guess work in the amateur construction of this receiver.

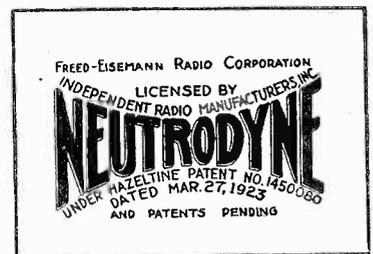For sale by dealers of the better class throughout the country, for amateur and experimental building. Builders are cautioned against attempting to build a Neutrodyne Set with parts which are not recommended and designed by the manufacturer to work with each other.



32-page illustrated book of instructions on "How to Build the Neutrodyne," with full size pictorial wiring diagram and full size panel and baseboard templates, \$1. At your Radio Dealers.

Freed-Eisemann Radio Corporation

RADIO WORLD

[Entered as second-class matter, March 28, 1922, at the Post Office at New York, N. Y., under the Act of March 3, 1879]

A Weekly Journal Published Every Wednesday and Dated Saturday, by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawana 6976 & 2063.

Vol. IV, No. 21. Whole No. 99

February 16, 1924

15c. per copy, \$6.00 a year

Further Notes on the Ultradyne Receiver

By B. C. Caldwell

SINCE the publication of the Ultradyne receiver the writer has literally been flooded with letters from the builders. Almost every one commented on the fact that the Ultradyne was the ideal set. Among all of the letters, I have found but three who have had trouble. In the first case, the builder could not tune the set to the higher wave lengths. If this happens to be the case with you, wind about 25 per cent. more wire on each secondary coil.

pairs, you will see that this is a good evening's work in itself. However, don't let this bother you, for the Ultradyne is a wonderful receiver when once these coils have been placed together properly.

The inside diameter of the coils used by the writer is $1\frac{1}{2}$ ". They were wound with No. 22 double silk covered wire.

The paper that is placed between the coils need be of no particular kind, brown or heavy wrapping paper will suffice. If double silk covered wire is used, no paper is necessary.

The best forms to be used are radion or formica. These come in the standard size, with a center of approximately $1\frac{1}{2}$ ". These may be cut down to an outside diameter of about $3\frac{1}{2}$ ". Cardboard forms in this size may also be

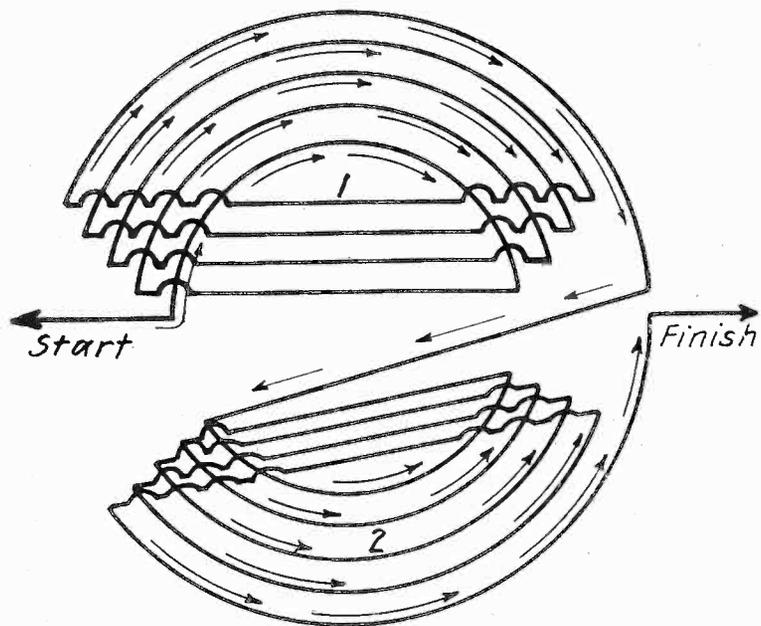


Fig. 1. Diagram showing the manner in which the wire is wound on the forms to make the transformers for the Ultradyne circuit. Arrows show direction of winding wire.

In the other two cases, the sets would not work at all, except for a rushing or a clicking sound. The trouble here is simple. The primary coils are not placed in the proper relation to the secondary coils. In the first description of the set, I stressed this point. However, I will admit, that it is a hard task to get them right the first time, as even if you do get the wires running in the same direction on each coil, there is a chance that the opposite fields will be placed together. In this case, of course, there will be absolutely no sound in the phones. Placing these coils together is very much like getting the proper connection for a honeycomb coil. When you buy one of these, there is a fair chance that you will have to take the coil apart and change the connections yourself. Getting these coils placed properly is the only difficult thing about the Ultradyne, and when you realize that there are three

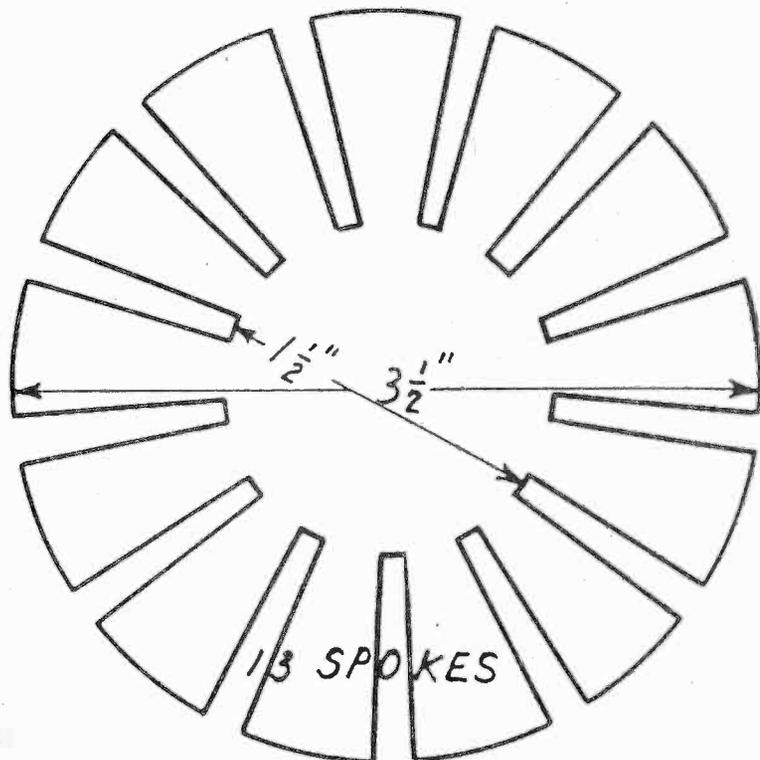


Fig. 2. Former to be used for winding coils for the Ultradyne circuit. This illustration may be used as a cutting template.

obtained in most localities and will work satisfactorily. The original coils made by the writer were wound on cardboard, so if you cannot obtain radion forms, do not be afraid to cut them from heavy cardboard.

One question that cannot be answered by writing, is
(Concluded on next page)

This Receiver is Compact and Highly Efficient

By Charles Bucher

PROBABLY the greatest fun of radio is realized by the man who constructs his own receiver. Many fans who never thought that they had mechanical ability in any line are now surprising themselves and others by building highly satisfactory and powerful receivers. However, no matter what circuit is used, the general rule of construction seems to lie in spreading a little apparatus over a great big panel, and using leads that could almost wire up a house for electricity. This is basically and electrically wrong. You can limit your leads and place your apparatus so that it will not inter-


is a positive wonder. Electrically it is a marvel of careful placement of apparatus and wiring. Besides that, the builder included several points novel in themselves which it would do well for other amateur builders to observe.

The foremost point is the arrangement of the apparatus. Note the manner in which the entire set was planned. The panel is just a little larger than the wood forms of the variometer in width and depth. It is just twice the height of the UV199 and socket, or 6", which makes the entire panel square. Some of the leads are but 1½" in length, and the longest lead used is not over 7". This cuts down the internal resistance of the circuit wonderfully, and makes much louder and clearer signals possible. If people who construct home-made sets would only realize this point, as Chassevent surely must have before making the receiver, there would be far less complaints from disappointed builders of receivers.

One other novel point is the method used in tuning. The receiver is not regenerative, and simply uses the variometer across the grid and filament leads of the tube as an inductance. However it was found necessary to incorporate a condenser or rather a variable bank of fixed condensers to give sharp tuning. On the lower right hand corner of the panel, directly in front of the tube will be seen three fixed condensers. If you look real sharp, you will see that they are joined to switch points or taps, which lead through the panel to the front of the set. They are of different capacities, which were first tested out. One condenser allows perfect reception from WHN the second from WOR and WJZ and the third from WEA and higher. Another good point about the circuit is that it is only necessary to attach a good ground, and no antenna, and signals can be plainly received.

A single 22½ volt dry cell supplies the B battery voltage, and a three-cell flashlight battery supplies the current necessary for the filament. These are neatly placed on the base under the variometer as shown. Directly in front of these, and under the variometer, can be seen the grid leak of the small variable type which is used. Back of that is the 30 ohm rheostat necessary to control the filament of the tube.

This should prove a good example for some of the amateur fans who like to "roll their own." The point that should be stressed, and *which is not in most home made receivers*, is to make your leads short, and of good heavy wire. Resistance in any part of a circuit that connects apparatus cuts down the efficiency to a great extent, so build it over now, using this as a model for the wiring, and make your leads short, of good heavy bus wire, and do not bring leads 18" in length around a tuning coil, with nice right angle bends, to reach across a 6" space.

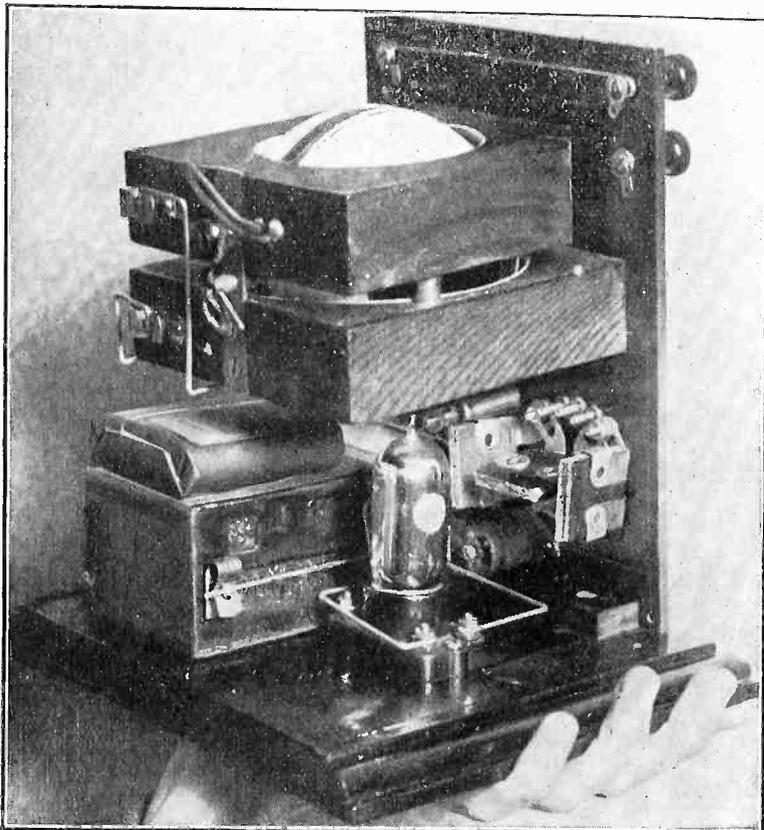

(C. Kadel and Herbert)

Interior view of an interesting little one-tube receiver which is so small that it can be easily held in the palm of the hand. Note the very exact and neat construction.

ferre electrically and yet will be small or compact to a high degree.

A good example of this compact arrangement is shown by the accompanying illustration, which depicts a single UV199 receiver built by Raymond Chassevent, a Bronx, N. Y., amateur who, to say the least, is a very good workman and a most careful observer. Mechanically the set

(Concluded from preceding page)

the manner of actually winding the coils. This is easily shown in the diagram accompanying this article. It is the five-turn coil, and to make things clearer, the direction of the wires is shown by arrows, with the start and finish clearly marked. Wind the large or secondary coils in the same manner, being sure that no binding material of any sort is used on either the coils themselves or the formers.

Like most of all supersensitive circuits, this one is critical, and in most cases is more critical than the well

known neutrodyne. By this I mean that it is critical as to the wiring of the leads. In the neutrodyne, there are the neutrodons to neutralize the internal tube capacitance that causes the oscillations. In this receiver we rely upon the turns ratio and the manner of winding and connecting the coils to do the same thing. This makes the coils the one factor that determines the correct operation of the circuit, and if they are not wired up just so, there will be no results at all. It is not a circuit that can be wired up in an hour or five hours, as time and care must be taken. Wires should be short as possible.

How to Make a CW or Radiophone Transformer

By Leroy Western

TO the experimenter who has available 110 volts 60 cycle A. C., a step-up transformer capable of delivering both a high voltage and a low voltage is invaluable. Such a transformer is useful in both radio

ance will accomplish the feat quite satisfactorily. Any of these strips which are bent can be readily brought back to shape by careful manipulation. The steel used should be of two sizes, 8" and 6". The actual assembling of the approximately .014" thick, and should be cut into lengths the core is done after the coils are wound, but beforehand the core should be assembled by overlapping the corners of the strips which can be readily seen by referring to Fig. 1.

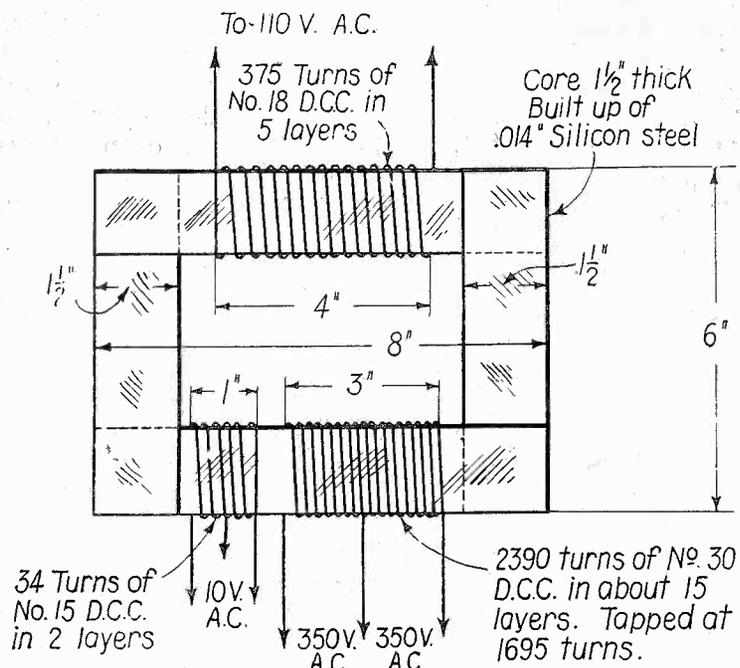


Fig. 1. Diagram showing location and winding of coils on the transformer. The manner of constructing the core is also shown.

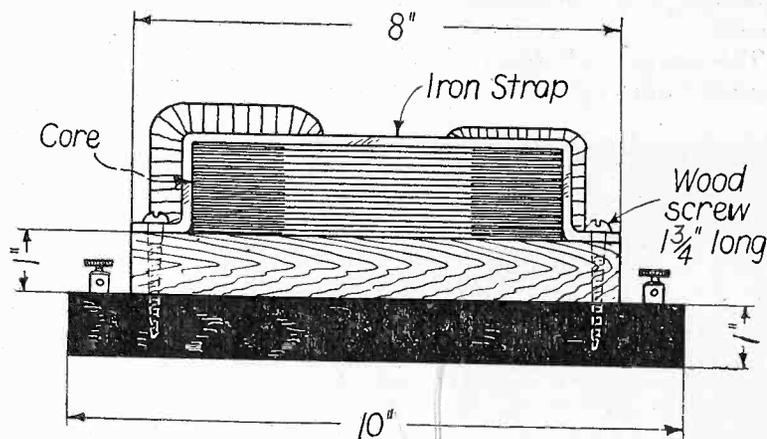


Fig. 3. Side view of the completed transformer showing manner of mounting.

telephone and CW or ICW transmitting sets. The manufactured ones are quite expensive, although those made by reliable companies are very efficient. Still the amateur with the construction "bug" often desires to make his own but hesitates because of lack of definite and authentic data.

To supply this want and furnish the required information, the transformer described below and illustrated herewith was designed. It was made after standard engineering practice using the regular formulas which can be found in any electrical engineering handbook and when completed was found to be equal in performance to a standard manufactured transformer which unfortunately had been burned out.

In order to make the transformer operate at as low a temperature as possible, a core of generous dimensions was

It should be assembled in this manner just for practice so that the builder will be able to go ahead and place the core within the coils in the easiest possible manner.

Wood - 10" x 1 1/2" x 1 1/2"

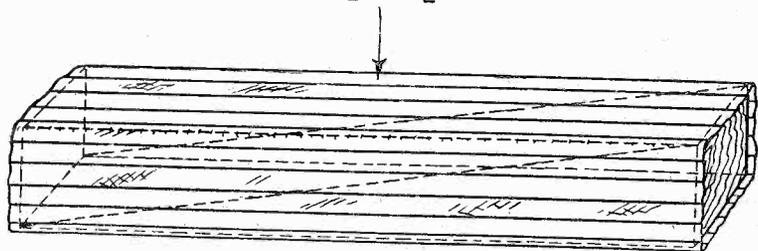


Fig. 2. Wood former used to wind the coils of the transformer. It is easier to wind it on the wood block than on the laminated leg.

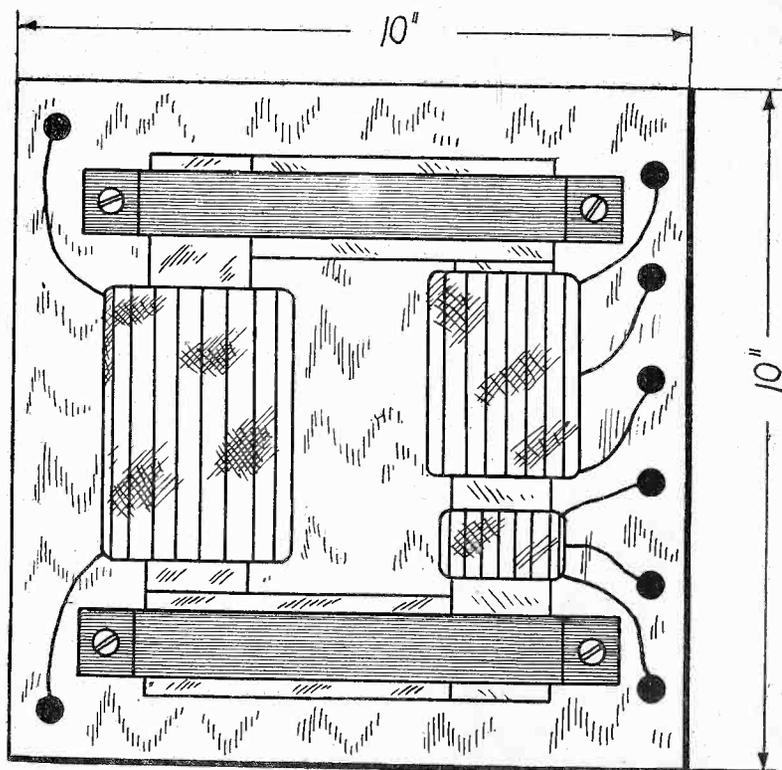


Fig. 4. Top view of the completed transformer showing location of binding posts and also the final placement of the coils.

used. Furthermore, it was made up of the best quality of silicon steel obtainable and it is advisable to procure this material from a company specializing in the sale of transformer steel. The material can in some cases be bought already cut in 1 1/2" strips, but if not, it should be bought in sheets and cut up. This will require a little careful work in order to get the edges smooth and to prevent bending the metal when cutting. However, a little persever-

The next step is the winding of the coil. The primary or input winding is to consist of 375 turns of No. 18 DCC or asbestos insulated wire. The actual winding should cover a space of 4" of the core and five layers will be required. This winding is to be placed on one leg of the transformer as indicated in Fig. 1 while the other leg is to have wound thereon two windings, one of sufficient size

(Concluded on next page)

Here Is a Mexican Station You Can Get in the U. S.

By G. Obregon, Jr.


AMATEURS and broadcast listeners throughout the United States have seen the interiors of the larger broadcasting stations, through the columns of *RADIO WORLD*. The illustrations herewith show one of most powerful broadcasting stations in Mexico. It has been heard in every state in the United States and has also received cards from Canada, Cuba, Central and South America, and numerous ships on both the Atlantic and Pacific.

The station, whose call is CYL, is operated by "El Universal," one of Mexico's leading newspapers, and La

Casa del Radio, the house of radio. It is situated at Av. Juarez 62, Mexico, D. F.

The transmitter is a 500-watt tube set constructed especially for this station by a Texas radio manufacturer. It operates on 500 meters (600 kilocycles) on Tuesdays and Fridays from 9:00 to 10:30 P. M. It is the most complete and powerful station used for the broadcasting of entertainment south of the Rio Grande and enjoys a wide popularity due to the interesting type of programs that it transmits.

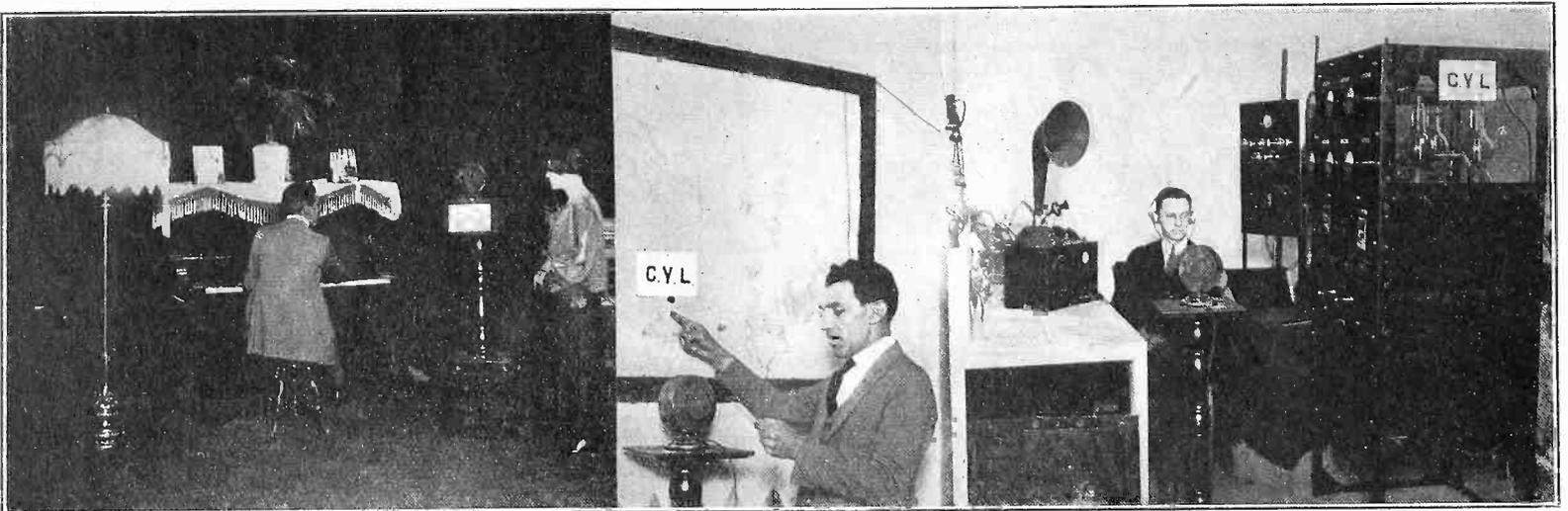Programs in both English and Spanish are broadcast.



Three views of the powerful Mexican broadcasting station CYL. On the left is shown the interior of the studio, with a performer singing before the microphone. In the center is shown the announcer (who is also the pianist, by the way) acknowledging some telegraph and telephone calls from the station. The announcer has to be somewhat of a linguist, as the range of the station makes announcements in both Spanish and English necessary. On the right is shown the operating room, with the chief operator listening in and checking up on the programs.

(Concluded from preceding page)

to supply the necessary current for two 5-watt tubes and the other to supply a total of 700 volts in sections of 350 volts each. Such windings will readily take care of two 5-watt tubes and may be used either for placing voltage directly on the plates of the tubes or it may be fed through a 10 or 12 jar electrolytic rectifier and thence to the plates.

For winding the coils, the writer found it advisable to obtain a strip of wood 10" long by 1½" square. The corners were first rounded off slightly and then the block was cut diagonally from end to end so as to form two long wedge-shaped pieces. The pieces are to be placed so as to form a 1½" square block and a couple of turns of cord or fine wire may be put around each end to hold the blocks in position. Strips of tape about 10½" long are then cut and placed overlapping each other lengthwise on the block as illustrated in Fig. 2. As an example in winding we take the primary. Measure off 4" at about the center of the coil and start the winding leaving about 8" of wire for a connection. Proceed with the winding, placing on the required number of turns. Cut the wire, leaving another 8" or so for the other terminal. The winding should be done smoothly and evenly. Now fold back one end of one strip of the tape over the winding and bring over the other end of the same strip so as to overlap. Proceed in this manner all the way around in this coil. The wooden blocks can now be removed and a perfectly formed and insulated coil will be found. It is advisable before placing the tape on the wooden blocks to coat the latter

with talcum so as to allow them to slide out of the form.

This same procedure is followed for the winding of the other two coils, the data on the number of turns being given in Fig. 1. It is advisable when winding the filament coil, to take off a tap at the center, as it will be found useful in many circuits.

When the coils are all wound and formed, the core is built up within the winding. First a strip of steel is inserted within the primary and another within the two secondaries. Elevating the coils on two blocks two 6" side pieces are placed, overlapping as illustrated in Fig. 1. Two other 8" strips are then placed within the coils and another pair of strips added. In this manner the core is built up to the required size. It should be seen that the core is quite rigid in construction and that the coils are not loose.

After constructing the transformer it will be necessary to mount it in some manner so as to at least partially protect the windings. This can be accomplished by providing a base of hard wood thoroughly boiled in paraffin or a slate or marble slab 1" thick by 10" square. Two strips of wood are also required, each being 8" long by 1" square. These are to be the supporting blocks for the core. Two pieces of scrap iron are then cut and formed, as yokes as illustrated in Fig. 3. Holes are drilled in each end of the two yokes and the entire assembly is made as shown in Figs. 3 and 4. In the base-board are drilled eight holes for mounting binding posts. The connections from the three coils are brought out as shown in Fig. 4. The entire unit is then rigidly assembled and can be handled quite roughly.

Navy Thanks WOR for Assisting "Shenandoah"

TWO highly prized letters addressed to Louis Bamberger, president of L. Bamberger & Company, who operate Station WOR, Newark, N. J., have been received from Hon. Edwin Denby, Secretary of the Navy and Commander J. H. Klein, Jr., U. S. N. They were sent in official commendation of the service rendered by Joseph M. Barnett, studio manager, and Jack Poppele, chief operator, on the night of January 16, 1924, when the giant air craft "Shenandoah" after breaking away from its moorings at Lakehurst, New Jersey, hung suspended in midair and storm-tossed over the control room of Station WOR on the roof of the Bamberger Building.

The dramatic scene enacted at that time with Barnett and Poppele broadcasting to the crew of the "Shenandoah," giving them location and reassuring words, following which hundreds of thousands of radio listeners in were kept informed of the progress of the runaway airship has been epitomized by Secretary Denby as "unselfish and patriotic service."

Barnett with tense nerves and voice quivering with emotion broadcast to the crew of the "Shenandoah": "You are now over Newark, New Jersey. The lights you see below are on the tower of the Prudential Building." The answer came back. "Thanks, old man." This thrilling conversation marked the beginning of the safe return of the "Shenandoah" to its hangar at Lakehurst. Secretary Denby wrote:

"I desire to express to you the appreciation of the Navy Department and of the Naval Service for your valued assistance on the occasion when the 'Shenandoah' was cast adrift from her mooring on the night of January 16th.

"The ready response with which Station WOR met the request of the officers at Lakehurst to broadcast the fact of the 'Shenandoah's' escape, and the close cooperation that was maintained by your station throughout the night are worthy examples of unselfish and patriotic service."

Commander Klein, who is executive officer at the Naval Air Station at Lakehurst, N. J., sent this letter:

"On behalf of the officers and crew of the U. S. S. 'Shenandoah' I wish to express my appreciation to you and the operating force of WOR for the assistance given us on the night of January 16, when the 'Shenandoah' broke away from her mast and sailed out over New Jersey.

"I understand that you ceased operations entirely during this period and devoted your entire attention to getting in touch with the 'Shenandoah'

and thereafter maintained uninterrupted communication from us to the ship. As a result of your efforts we were constantly notified in regard to the ship.

"Will you please also express to your radio audience our appreciation for the many telephone and telegraphic communications sent during the night from those who saw the ship in flight?"

"This cordial cooperation and unselfish devotion to the air forces is something which we particularly appreciate because should any misfortune ever overtake us in the air, we shall always feel that we have a multitude of friends on the ground who are constantly helping us as you and your people did.

"Captain McCrary, commanding the 'Shenandoah,' is absent from the station at this time and I know that he, as well as all the officers and men on the station, subscribes to these views and we all hope that if we can be of any assistance to you that you will not hesitate to let us know."

Radio at Palm Beach Interests the Dog



(C. International Newsreel)

Miss Betty Queen, of New York City, and her Pekinese "Ming Toy" listening in to a radio program at Palm Beach, Florida. Judging by "Ming's" expression, something to eat is being discussed over the air.

A Radio Rhapsody

By Henry D. Cheney

UPON a crystal mounted high,
In a box all by itself,
A lordly tube with brilliant eye
Gazed from off a shelf.

"Behold my wonder plate!" said he,
"And filament and grid,
And tell me, crystal, what you see
Of greatness in me hid."

The crystal scratched his shining head,
With a wire short and stout,
And in a tiny voice he said:
"O royal bulb, don't shout!

"Of greatness much there is no doubt,
And mystery galore,
Concealed in you and round about,
Especially your roar.

"But look at me, O prideful one,
Who also secrets hold,
And see what great things I have done
In the many years that rolled!

"Clear as crystal, like my name,
I snatch the ether wave,
And ride upon the wings of fame,
That history to me gave.

"Admit I will that you are grand,
Most noble of detectors,
And in DX or broadcast band
The king among reflectors.

"So let us both go hand in hand,
Reflex or otherwise,
And see how much we can command
Of this ether of the skies."

Amateurs Radio Alarm While Convicts Flee

BALTIMORE, Md. — Amateur radio stations all over the United States and remote sections of Canada recently sent out on the air the description of two convicts who escaped from the local penitentiary soon after the police and the radio department of the "Baltimore American" had been notified of their disappearance.

The first alarm was sent by Martin Porter, operator of amateur station 3DQ. Immediately the message was picked up by other operators in the vicinity and in a few minutes had spread throughout the East, amateurs in each city notifying their local police authorities and turning in the descriptions.

Far into the night, while the two fugitives were fleeing, amateurs here listening at their receiving sets heard stations connected with the American Radio Relay League in the Mississippi Valley and on the West Coast sending the alarm one to another by telegraph code and amateur phones. Within four hours the entire country had been completely covered.

Referring to the incident, the "Baltimore American" said: "A tribute, indeed, to A. R. R. L. efficiency, organization and co-operation and a real joy to the amateur."

The Captain and Four Radiomen "Stand By"

WASHINGTON, D. C.—Captain Herbert G. Sparrow, U. S. N., commander of the U. S. S. "Tacoma," and four radio men were the last to leave this vessel wrecked off Vera Cruz recently—and, at the end, four of them were dead and the other injured. Old naval traditions obtained, not alone through the action of the gallant skipper, but through the four radiomen who stood by with him in an effort to keep radio communication open.

While the details of the accident which killed Captain Sparrow, Radiomen Lusser, Herrick and Sivin, and injured Chief Radioman J. V. Cooper are not available, Admiral Eberle, Chief of Operations, says he believes all five men were in the radio shack trying to maintain radio-telephone communication with the U. S. Consulate on shore, which had been established the preceding day on batteries, as the dynamos were out of action. Then the hurricane struck the old cruiser, whose bow was on a reef, and threshed her unmercifully, washing her with terrific seas

and pounding her to pieces. Either a falling mast or an extremely heavy sea is believed by the admiral to have crushed in the radio shack, formerly the captain's emergency cabin, located on the main deck just below and aft of the bridge. The only dispatch bearing on the death of these four men states: "They were all killed on the main deck on January 21, having been struck by heavy wreckage and seas."

Naval officers picture the captain, who was an authority on electrical matters and a radio enthusiast, and the radio operators, as crowded around the ship's radio apparatus trying to send a last message to the Vera Cruz Consulate, when the crash came.

Investigations, scheduled as soon as the "Prometheus" reaches Charleston with the survivors, may reveal that the navy has developed a new type of hero, the radioman, who remains aboard even in extreme danger, continuing to "stand by" with his skipper until ordered over the side or relieved by a Higher Power.

Radio to Be Used Only on Last Leg of Army Plane World Flight

WASHINGTON, D. C.—The army aerial world tour will be attempted without the use of radio, except on the last leg, across the Atlantic from Hull, England, due to the conservation of weight, the Chief of the Army Air Service has announced.

Radio experts and some fliers believe that this is an unfortunate decision, since through the use of radio in connection with aviation, greater assurance of successful flights and the safety of pilots has resulted generally. But the projectors of the flight do not consider radio essential.

Weather conditions, orders, and emergency calls can be received immediately by pilots on radio-equipped craft, and they, in turn, can send messages as to progress, position, and changes in routes, as well as requests for assistance, position reports, and desired information.

One plane, it is now planned, will be equipped with a transmitter and a receiving set at Hull, England, but what would happen if that plane should crash is not announced.

The radio-telegraph transmitting set is a 200-watt non-synchronous, rotary spark, with a plane-to-ground range of about 100 miles. The antenna will be a single weighted trailing wire, and the whole set will weigh approximately 100 pounds. Six hundred meters will be the wave used.

A super-heterodyne receiving set will also be carried in the communication plane but no radio compass. The transmitting set is capable of being transferred to another plane if necessary. Spares and some replacement apparatus will be carried across the Atlantic.

While the country at large, particularly radio fans, are interested in the flight scheduled to leave Los Angeles, Cal., on March 15, and circumnavigate the globe westward, some anxiety for the fliers is felt by those who have come to place great confidence in radio communication and position finding, such as will be possible when the naval airship "Shenandoah" sails north to the Pole, fully equipped with all radio facilities.

White's Radio Bill Ready to Submit

By Washington R. Service

WASHINGTON, D. C.—The revised White Radio Bill is now understood to have been generally approved by the Department of Commerce, except that the final draft has not been read by radio officials there. A last conference between Congressman White, of Maine, and Solicitor Davis of the Commerce Department is expected in a few days, following which the bill will be introduced in the House and referred to the Merchant, Marine and Fisheries Committee. Public hearings will then be held, for suggestions and complaints from the interests affected. It is also believed a similar bill will be presented in the Senate.

In general, the bill will provide for the continued inspection and licensing of all American ship and shore transmitting stations, including commercial, private, broadcast-

ing and amateur stations, as well as the examination and licensing of all operators by the Department of Commerce. General regulations of all sending stations and operators, together with license fees, location of stations, the assignment of wave lengths, power and hours, will be placed in the hands of the Secretary of Commerce. Existing licenses, however, will be permitted to run until they expire. An advisory committee of 15 experts, commercial and governmental officials will also be authorized to aid the Commerce Secretary. Assurance is given that receiving stations will now be required to secure licenses.

In view of the recent action by the Federal Trade Commission, some advocates of the bill do not believe the "monopoly" question should be included in the projected legislative measure, but others say it may be.

The C. White Super-Power Amplifier

More About a Device Which Appealed to 10,741
"Radio World" Readers

By C. White, Consulting Engineer

IN RADIO WORLD for June 9, 1923, I wrote up the "Super Amplifier." At that time I had no idea that the circuit would be so widely adopted. Almost instantly, however, I received letters from nearly every part of the world asking for more information concerning this amplifier. Letters concerning this amplifier have never ceased to come in and at the request of more than 10,741 readers, by actual count, I have decided to repeat the original article in a slightly different form.


Push-pull amplification was by no means new when it was first introduced for amateur use, and it was through the efforts of the author that the Como Apparatus Company of Boston, decided to build a pair of duplex transformers for amateur use. The only transformers of this type that were on the radio market were not available for home construction and were not designed to go with the amateur tubes now in common use. The actual design of these transformers for amateurs was not an easy problem. Many calculations were involved as well as a great deal of careful laboratory research to bear out conclusions reached on paper. The problem of coil insulation, moreover, was a serious one. These transformers to be of any value must be able to withstand high voltage surges such as are very common in the third stage of audio-frequency amplification when high plate voltages are employed.

What is the advantage of duplex amplification? This is a most common and regular question that is being asked almost daily in radio stores and elsewhere. Push-pull amplification is the only well known method of amplifying a loud signal to a great extent. If a signal is fairly loud and it is desired to boost it up to still greater volume without adding an undue amount of distortion, a stage of duplex amplification is the logical thing. It is the one form of amplification for audio frequencies that can be successfully applied to act as a third stage. The reason for this is that there is an actual push and pull action of the two tubes, similar to that of a double action steam engine. As the plate current of tube No. 1 in the push-pull stage increases, the plate current of No. 2 is decreasing. This causes a filtering out of a large amount of tube noise and distortion. Then again the output transformer of the duplex stage effectively prevents any of the direct current plate supply from passing through the field coils of the loud speaker. The passing of a high value of direct current through the coils of a loud speaker causes it to be biased in one direction, thus putting a stronger pull on the diaphragm in one direction than in the other. This means that the diaphragm more readily responds to an impulse in one direction than an impulse in the opposite direction. In turn, this means that distortion of a certain degree is introduced into the reproducing mechanism, making the loud speaker sound "raspy" although the fault is really in the use of a high plate current passing through the coils.

As I have stated, push-pull amplification is more effective to swell the volume of a signal that is already audible to a good degree; therefore it is used, for example, as the third stage of an audio-frequency amplifier. Many radio fans will place a duplex stage right after their detector tube and expect the loud speaker to pour forth a marvelous volume on a signal that is extremely weak. They are disappointed because a stage of ordinary ampli-

fication should be used on a weak signal before it is fed into the duplex stage. Good transformer-repeated cascade (ordinary AF) amplification is better suited to the amplification of a weak signal, but it falls down when it comes to amplifying a strong signal to a still greater extent. Some radio fans have found that they can secure more volume as well as distance by using this super amplifier after two stages of ordinary audio amplification. On a distant station excellent results can be so obtained, but when a good set is used and such a combination is employed for the reception of a loud or local station they are apt to seriously injure the loud speaker. I have seen and heard the diaphragm of one of the strongest power type of loud speakers permanently damaged in a test of this nature.

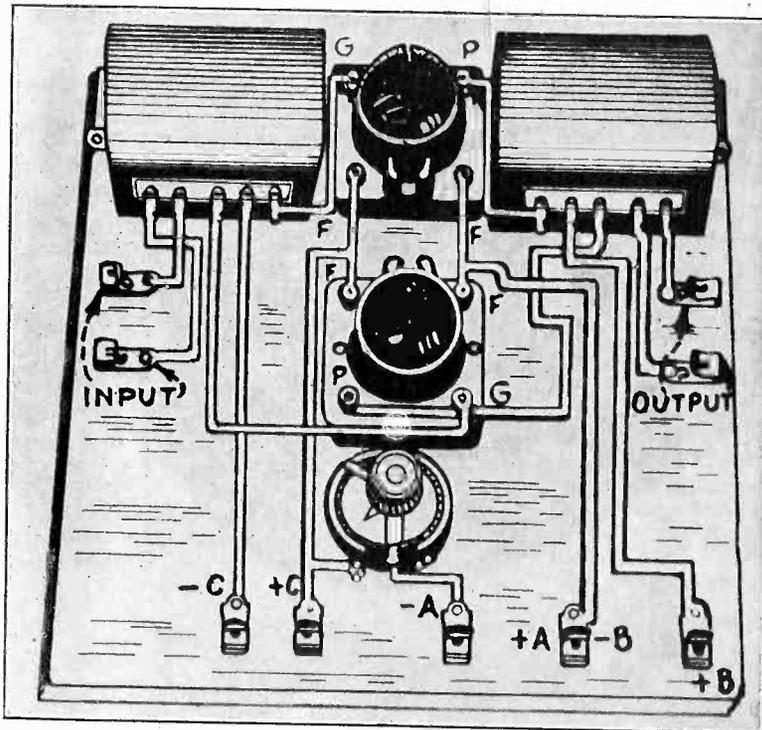The diagram herewith clearly shows the actual wiring connections. It is plain to see that there is very little wiring to the job and the assembly is extremely easy; the



Plan view of a completed power amplifier. The wiring is plainly shown and the terminals are all marked for ease in hooking up.

wires almost fall into place after the apparatus has been properly located on a suitable baseboard.

After assembling this amplifier do not be afraid to apply heavy "B" battery voltage to the tubes in the duplex stage and for every 45 volts of "B" battery about 1.5 volts of "C" battery must be used. The "C" battery can be made up of small flashlight cells, or an Eveready "Three" battery can be used. Although this amplifier functions best when UV201A or C301A tubes are used, still very excellent results are obtainable with the UV199 or C299. I would not recommend this unit for use with the WD11 or the WD12 owing to the fact that this type of tube is a very poor audio-frequency amplifier for super or power amplification.

If you are building a new set the super amplifier can be mounted in the cabinet with the other parts of the set,
(Concluded on next page)

Radio Primer

MAKING YOUR RECEIVER MORE EFFICIENT: Lately there has been much to do about "efficient" receivers. One circuit will be bruted about as "the most wonderfully efficient" and the next one as the "most efficient circuit using steeny-umph tubes ever perfected." Needless to say such statements should all be taken with a good deal of salt. Because a circuit is as efficient as its wiring and the apparatus used in its construction. Efficiency means one thing—using the energy that is collected in the antenna circuit to the best advantage, with the least amount of loss in the circuits that eventually lead the currents to the audible circuits (phone or loud speaker circuit).

A simple crystal circuit can be made more efficient than the most complex heterodyne receiver, which is not properly or efficiently constructed, if you take the word efficiency correctly. It will not give louder signals, but will put the received energy to the best use. Efficiency does not mean the use of six or eight tubes, or complex filtering circuits or double, triple or quadruple tuners. It means getting the most good out of the current received. the loudest possible response in the phones with the least amount of loss in the circuit.

One of the points that leads to the efficient working of a receiver is the cutting down of losses in the circuit itself. Most receivers, both home constructed and factory made, use long leads, with pretty and fancy bends in the wires. This looks right, but is absolutely wrong. To convince yourself of this fact, do the following: Take two crystal receivers, identical as to apparatus, and wire one up with nice bends in the wire, long leads, and few soldered connections. The second, wire up with heavy copper wire (No. 12 if possible) and make the leads as short as possible. Where two leads go to one piece of apparatus, arrange the parts so that one lead will suffice. Then hook up first the nicely constructed one to the antenna and tune in on some medium strength signal. If possible, get an audibility meter and test the strength. Then test the other one, under the same conditions. The one that uses the short leads with the heavy wire will surprise you in its increase of audibility over the second or nicely wired one. This will give the "wire bending fans" something to think over, if they will only test the thing out.

Now, not getting away from the point, two receivers using identical apparatus and the same circuit, which by the way was the Superdyne, were tested out under the same conditions. Care was taken, of course, not to run the plate and grid leads too close, but the other wires were run every which way, short and direct. An increase in audibility of over 30 per cent. on the detector alone, and a lessening of the disturbing howling noises was imme-

diately apparent in the direct wire receiver. To prove this to the average builder would be simple, as all he has to do is to rewire his set, making his leads short, direct and of heavy, low resistance wire.

The ideal receiver would be one that could use wire as heavy as No. 6 or No. 8, but this is a physical impossibility, as this wire is as thick as a thin lead pencil, and costs too much.

The next point to consider is the spacing of the parts. Do not use a 27" or 30" panel just because you happen to have that size cabinet at home. You can easily and cheaply buy a new cabinet, but you cannot chase resistance out of a circuit by laying a half dollar down in front of the set.

Then make sure that every connection (and that doesn't mean almost every one) is firmly soldered with a *resin flux solder*. A handy flux can be made by making a paste of powdered resin in alcohol and placing a tiny bit on each connection before applying the solder. Have the iron good and hot, and the point well tinned.

The next thing, when using tubes is to use good sockets. In most cases, the sockets of today depend upon the nibs of the tubes making contact with the springs by pressing down on them. They lose their springiness and consequently relax, causing a poor contact. There are sockets made which due to their peculiar construction always make a perfect contact, which is always wiped clean. These sockets are harder to obtain than most, as they are not as widely distributed as the cheap ones, but it is worth while to wait three weeks to get one and be sure of good contacts than it is to use a poor one and wonder where the trouble lies.

Finally, do not use coils that cover too great a wave length range, or that use a great number of taps to vary the wave length. A single coil correctly proportioned, the wave length of which is varied by a 23 plate condenser, should be the standard for the average amateur. Bank wound coils because of distributed capacity and dead end loss will sometimes cut the volume of the signals down 25 per cent. on local stations and even more on the distant signals. A single coil of from 30 to 40 turns shunted by a 23 plate condenser on a 4" tube will allow a receiver to respond to all the broadcast waves, with the probable exception of the very lowest around 200 meters. It is better to have a receiver which is very efficient over a wave length of from 250 to 500 meters than one that will respond with lessened efficiency from 150 to 1,000 meters.

Plan your receiver carefully, wire it with heavy wire, use straight connections, solder every one, and use inductances that cover just the band you wish to receive. Use the best of parts, pay especial attention to your sockets and condensers, and you will find that every receiver you hear about, read about or build will prove itself a success as far as received signals and distance go.

(Concluded from preceding page)

but the wiring should be so arranged that the input to this duplex stage can be connected to the detector, first stage or second stage, in order to control the volume output. This is readily done by having a flexible phone cord with a plug on one end and the other end permanently connected to the input coil of the push-pull stage. This will allow the input of the duplex stage to be connected into the detector jack, the first stage jack, or the second stage jack.

Another fact to bear in mind is that the "C" battery voltage is important. Failure to apply sufficient "C" voltage will mean a noisy amplifier, while with the correct amount of grid bias ("C") voltage the tone will be loud and pure. Then again, the "C" battery aids to conserve the "B" battery, since when the correct "C" voltage is ap-


plied to the grid, the minimum plate current is drawn from the plate potential supply.

All in all, there has been no more important addition to the audio-frequency field than the introduction of push-pull amplification. It has accomplished what had heretofore been considered as impossible; that is, more volume with less distortion by the use of an extra stage of audio-frequency.

In conclusion, I want to thank all those who have written me in care of RADIO WORLD, Como Apparatus Company, and personally for their kind appreciation of my humble efforts to serve them, and I regret the fact that personal physical limitations alone prevented me from giving all letters a personal answer, such as is my general rule. However, I am sure they will understand what it means to receive so many letters on one subject.

RADIOGRAMS

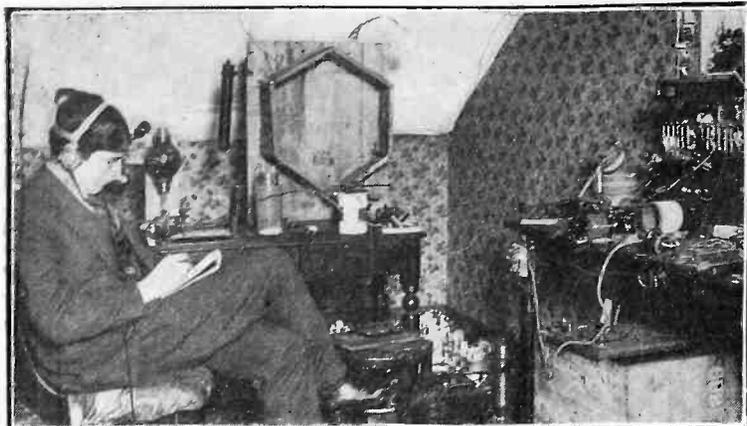WORLD NEWS HAPPENINGS BRIEFLY
PHRASED FOR OUR BUSY READERS



(C. P. & A. Photos)

Frederick L. Hogg, of Highgate, London, England, who kept up a two hours' back-and-forth talk with an amateur in Canada. Low waves around 150 meters were used, with comparatively low power. Hogg is shown copying messages from American and Canadian amateurs. He has a licensed station—a rarity in England.

Lives of great men all remind us we should broadcast as we go, and, departing, leave behind us echoes from the radio.—New York Tribune.

* * *

Cook: What are we having tonight, m'm?
Mistress: Why, I've just told you; clear soup; fillet of sole; cutlets; cabinet pudding.
Cook: I meant on the wireless, m'm.—Punch.

* * *

Students in the classes to be taught by radio planned by some of the Western universities will have no difficulty in walking out on the professor whenever his discourse bores them.—The New York Herald.

* * *

In a recent radio contest from Station WLW, Cincinnati, the broadcasting station of the Crosley Radio Corporation, a number of hams were given away. Several letters have been received asking when the eggs will be offered in a contest.

* * *

E. F. W. Alexanderson, consulting engineer of the General Electric Company, and chief consulting engineer of the Radio Corporation of America, has been awarded the Order of the Polonia Restituta by the Polish Government, in recognition of his meritorious service in connection with the building of Poland's new radio station near Warsaw.


* * *

The Postmaster General of Ireland is reported to have decided upon a method of broadcasting control and a group of Irish firms have agreed to work the scheme together. There is to be a main station at Dublin. Radio sets will be imported and manufactured locally. The license for an amateur will cost \$5; hotels and restaurants will pay \$25. News, music and advertising will be broadcast.



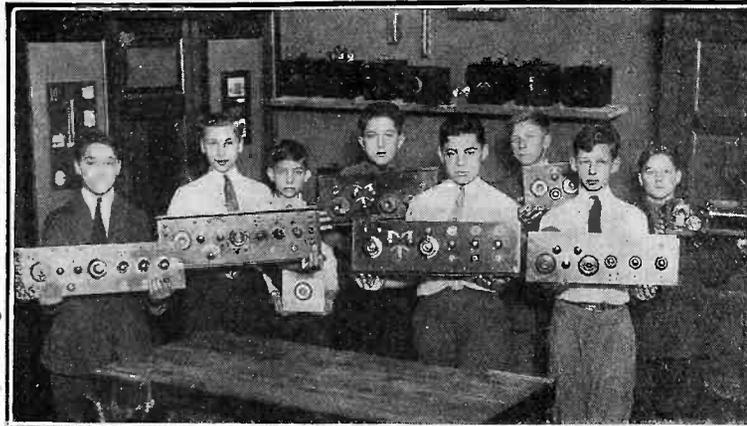(C. P. & A. Photos)

Bartholomew Molinari, San Francisco amateur, who is one of the few American amateurs in communication with WNP, the MacMillan Expedition at the North Pole. A 250-watt tube set is used for transmitting, with a home constructed regenerative set for receiving. Direct two-way communication was established without the necessity of any relays or aid from other amateurs. The fading of WNP was bothersome, though.



(C. P. & A. Photos)

Making radio receivers in school shops now takes the place of making the old-time taboret and knife box or candle-stands. The illustration shows a group of New York school boys with the finished receivers they constructed during their manual training periods in school. While all the sets bear some resemblance to one another, no two are the same.

Remember, we never know how many receivers catch something of the influence we radio daily.—Forbes Magazine.

* * *

Jazz music and radio loud-speakers have rendered great service to the deaf. Deafness isn't the curse that it once was.—San Diego Union.

* * *


Almost everything but thinking may be artificially done, but knowledge and understanding must be actively sought and acquired. Man is the only animal who can do this.—Dr. W. R. Whitney.

* * *

Islands of the Southern Pacific Ocean have been brought within range of American radio broadcasting. KGO, the new 1,000-watt station of the General Electric Company at Oakland, California, was heard two evenings out of five at Apia, Samoa, a distance of 4,750 miles from Oakland.

* * *

At the Great Lakes Naval Training Station, where radio operators are trained, the new fangled psychological method of increasing speed in code reception, while the partly trained gobs sleep, is being used with as great success as met the initial sleep instruction tests at Pensacola. One night, after sending at high speed to seventeen sleeping embryo operators equipped with "ear-muffs," a petty officer ended his watch with the code message: "Hey, gobs! Get up, it's five-fifty-five!" Much to his surprise, the snoring ceased, three of the men awoke, and in a few minutes the other fourteen rolled out, asking what was the matter. The flabbergasted petty officer now admits night code practice may increase receiving speed, but he knows it will get the students up at four bells.

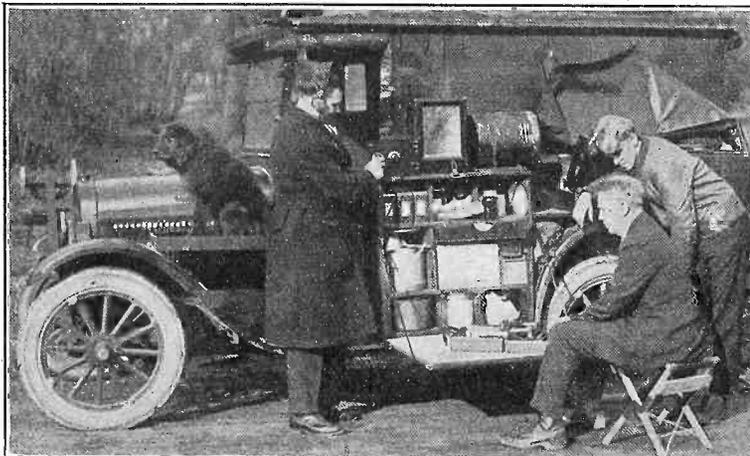

(C. Wide World Photos)

The unique automobile in which four New Yorkers are to cross the country. The car is equipped with every household necessity, and even boasts a loop receiver, with which they may while away their idle moments while traveling. The receiver is of the duo-control type, operating on the battery of the car, and uses a small loop located inside the body to keep it dry in case of damp or rainy weather.

Complete List of U. S. Broadcasters

Includes Stations in Canada, Cuba, Porto Rico and Mexico

Corrected to February 8, 1924

Call	Owner	Location	Meters	Kcys.	Call	Owner	Location	Meters	Kcys.
KDKA	West'ghouse Elec. & Mfg. Co.	E. Pittsburgh, Pa.	326	920	KFKQ	Conway Radio Lab.	Conway, Ark.	224	1340
KDPM	West'ghouse Elec. & Mfg. Co.	Cleveland, Ohio	270	1110	KFKV	F. Gray	Butte, Mont.	283	1060
KDYL	Southern Electrical Co.	San Diego, Cal.	244	1230	KFKX	West'ghouse Elec. & Mfg. Co.	Hastings, Neb.	286	1050
KDYL	Telegram Publishing Co.	Salt Lake City, Utah	360	830	KFKZ	Nassour Bros.	Colorado Springs, Colo.	234	1250
KDYM	Savoy Theatre	San Diego, Cal.	280	1070	KFLA	A. R. Willson	Butte, Mont.	248	1210
KDYO	Oregon Inst. of Tech.	Portland, Oregon	360	620	KFLB	Signal Mfg. Co.	Menominee, Mich.	248	1210
KDYW	Smith, Hughes & Co.	Phoenix, Ariz.	360	830	KFLD	P. E. Greenlaw	Franklinton, La.	234	1280
KDYX	Star Bulletin	Honolulu, Hawaii	360	620	KFLE	Nat'l Educational Service	Denver, Colo.	268	1120
KDZB	Frank E. Siefert	Bakersfield, Cal.	240	1250	KFLH	Errickson Radio Co.	Salt Lake City, Utah	261	1150
KDZE	The Rhodes Co.	Seattle, Wash.	270	1110	KFLP	E. N. Foster	Cedar Rapids, Iowa	240	1250
KDZF	Auto Club of So. California	Los Angeles, Cal.	278	1080	KFLQ	Bizzell Radio Co.	Little Rock, Ark.	261	1150
KDZI	Electric Supply Co.	Wenatchee, Wash.	360	830	KFLR	University of New Mexico	Albuquerque, N. M.	254	1180
KDZO	Nichols Academy of Music	Denver, Colo.	360	830	KFLU	Rio Grande Radio Co.	San Benito, Texas	236	1270
KDZR	Bellingham Publishing Co.	Bellingham, Wash.	261	1150	KFLV	Rev. A. T. Frykman	Rockford, Ill.	229	1310
KFAD	McArthur Bros. Merc. Co.	Phoenix, Ariz.	360	830	KFLW	Missoula Elec. Supply Co.	Missoula, Mont.	234	1280
KFAE	State College of Washington	Pullman, Wash.	330	910	KFLX	Geo. R. Clough	Galveston, Texas	240	1250
KFAF	Western Radio Corp.	Denver, Colo.	360	830	KFLY	Fargo Radio Co.	Fargo, N. D.	231	1300
KFAJ	University of Colorado	Boulder, Colo.	360	830	KFLZ	Atlantic Auto Co.	Atlantic, Iowa	273	1100
KFAN	The Electric Shop	Moscow, Idaho	360	830	KFMQ	University of Arkansas	Fayetteville, Ark.	263	1140
KFAR	Studio Lighting Service Co.	Hollywood, Cal.	280	1070	KFMR	Morningside College	Stoux City, Iowa	261	1150
KFAU	Daily Sun	Boise, Idaho	270	1110	KFMS	Freimuth Dept. Store	Duluth, Minn.	275	1090
KFAW	The Radio Den	Santa Ana, Cal.	280	1070	KFMT	Dr. G. W. Young	Minneapolis, Minn.	231	1300
KFAZ	W. T. Virgin Milling Co.	Medford, Ore.	283	1060	KFMU	Stevens Bros.	San Marcos, Tex.	240	1250
KFBB	F. A. Buttrey & Co.	Havre, Mont.	360	830	KFMV	M. G. Sateren	Houghton, Mich.	266	1130
KFBC	W. K. Azbill	San Diego, Cal.	278	1080	KFMW	Carleton College	Northfield, Minn.	283	1060
KFBE	Reuben H. Horn	San Luis Obispo, Cal.	360	380	KFMY	Boy Scouts of America	Long Beach, Cal.	229	1310
KFBG	First Presbyterian Church	Tacoma, Wash.	360	830	KFMZ	Roswell Bdstg. Club	Roswell, N. M.	250	1200
KFBH	Kimball-Upson Co.	Sacramento, Cal.	283	1060	KFNC	Echo Pk. Evang'ic As., Inc.	Los Angeles, Calif.	278	1080
KFBL	Leise Bros.	Everett, Wash.	224	1340	KFNG	Wooten's Radio Shop	Coldwater, Miss.	254	1180
KFBS	Trinidad Gas & Elec. Co.	Trinidad, Colo.	360	830	KFNH	State Teachers' College	Springfield, Mo.	236	1270
KFBU	The Cathedral	Laramie, Wyo.	283	1060	KFNJ	Warrensburg Elec. Shop	Warrensburg, Mo.	234	1280
KFCB	Nielsen Radio Supply Co.	Phoenix, Ariz.	238	1260	KFZ	Doerr-Mitchell Elec. Co.	Spokane, Wash.	283	1060
KFCF	Frank A. Moore	Walla Walla, Wash.	360	830	KGB	Tacoma Daily Ledger	Tacoma, Wash.	252	1190
KFCH	Electric Service Sta., Inc.	Billings, Mont.	360	830	KGG	Hallock & Watson Radio Ser.	Portland, Ore.	360	830
KFCM	Richmond Radio Shop	Richmond, Cal.	244	1230	KGN	Northwestern Radio Mfg. Co.	Portland, Ore.	360	830
KFCP	Ralph W. Flygare	Ogden, Utah	360	830	KGO	General Electric Co.	Oakland, Cal.	312	960
KFCV	Fred Mahaffey, Jr.	Houston, Texas	360	830	KGU	Marion A. Mulrony	Honolulu, Hawaii	360	830
KFCY	Western Union College	Le Mars, Iowa	360	830	KGW	Portland Morning Oregonian	Portland, Ore.	492	610
KFCZ	Omaha Central High School	Omaha, Neb.	258	1160	KGY	St. Martin's College	Lacey, Wash.	258	1160
KFDA	Adlers Music Store	Baker, Ore.	360	830	KHJ	Los Angeles Times	Los Angeles, Cal.	395	760
KFDD	St. Michael's Cathedral	Boise, Idaho	252	1190	KHQ	Louis Wasmer	Seattle, Wash.	360	830
KFDE	University of Arizona	Tucson, Ariz.	360	830	KJQ	C. O. Gould	Stockton, Cal.	360	830
KFDJ	Oregon Agricultural College	Corvallis, Ore.	360	830	KJR	Northwest Radio Service	Seattle, Wash.	283	1060
KFDO	H. Everett Cutting	Rozeman, Mont.	248	1210	KJS	Bible Inst. of Los Angeles	Los Angeles, Cal.	360	830
KFDR	Bullock's Hdw. & Spt. Goods	York, Neb.	360	830	KLS	Warner Bros. Radio Co.	Oakland, Cal.	360	830
KFDV	Gilbrech & Stinson	Fayetteville, Ark.	360	830	KLX	Tribune Publishing Co.	Oakland, Cal.	509	590
KFDX	First Baptist Church	Shreveport, La.	360	830	KLZ	Reynolds Radio Company	Denver, Colo.	360	830
KFDY	S. D. State Col. of Agric.	Brookings, S. D.	360	830	KMJ	San Joaquin Lt. & Pr. Corp.	Fresno, Cal.	273	1100
KFDZ	Harry O. Iverson	Minneapolis, Minn.	231	1300	KMO	Tacoma Times	Tacoma, Wash.	360	830
KFEC	Meier & Frank Co.	Portland, Ore.	360	830	KNT	Gray's Harbor Radio Co.	Aberdeen, Wash.	263	1140
KFEL	Winner Radio Corp.	Denver, Colo.	360	830	KNV	Radio Supply Co.	Los Angeles, Cal.	256	1180
KFEO	J. L. Scroggin	Oak, Neb.	270	1110	KNX	Elec. Lighting Supply Co.	Los Angeles, Cal.	360	830
KFER	Auto Electric Service Co.	Fort Dodge, Iowa	231	1300	KOB	N. M. Col. of Ag. & Mec. Arts	State College, N. M.	360	620
KFEV	Radio Electric Shop	Douglas, Wyo.	263	1140	KOP	Detroit Police Department	Detroit, Mich.	286	1050
KFEY	Augsburg Seminary	Minneapolis, Minn.	261	1150	KPO	Hale Bros.	San Francisco, Cal.	423	710
KFEZ	Bunker Hill & Sull. Mng. Co.	Kellogg, Idaho	360	830	KQV	Apple City Radio Club	Hood River, Ore.	360	830
KFFB	Am. Soc. of Mech. Engineers	St. Louis, Mo.	360	830	KQW	Doubleday-Hill Elec. Co.	Pittsburgh, Pa.	360	830
KFFC	Jenkins Furniture Co.	Boise, Idaho	273	1100	KRE	Chas. D. Herrold	San Jose, Cal.	360	830
KFFE	Eastern Oregon Radio Co.	Pendleton, Ore.	360	830	KSD	Berkeley Daily Gazette	Berkeley, Cal.	270	1080
KFFO	Dr. E. H. Smith	Hillsboro, Ore.	229	1310	KSL	Post Dispatch	St. Louis, Mo.	546	550
KFFQ	Marksheffel Motor Co.	Colorado Springs, Colo.	360	830	KSS	The Emporium	San Francisco, Cal.	360	830
KFFR	Jim Kirk	Sparks, Nev.	226	1330	KTW	Prest & Dean Radio Co.	Long Beach, Cal.	360	830
KFFV	Graceland College	Lamoni, Iowa	360	830	KUO	First Presbyterian Church	Seattle, Wash.	360	830
KFFX	McGraw Company	Omaha, Neb.	278	1080	KUS	Examiner Printing Co.	San Francisco, Cal.	360	830
KFFY	Pincus & Murphey	Alexandria, La.	275	1090	KUY	City Dye Wks. & Laun. Co.	San Francisco, Cal.	360	830
KFFZ	Al. G. Barnes Amuse. Co.	Dallas, Texas	226	1330	KWG	Coast Radio Company	El Monte, Cal.	256	1170
KFGC	Louisiana State University	Baton Rouge, La.	254	1180	KWH	Portable Wireless Tel. Co.	Stockton, Cal.	360	830
KFGD	Chickasha Radio & Elec. Co.	Chickasha, Okla.	248	1210	KXD	Los Angeles Examiner	Los Angeles, Cal.	360	830
KFGH	Leland Stanford University	Stanford Univ., Cal.	226	1330	KYW	Herald Publishing Company	Modesto, Cal.	252	1190
KFGJ	Mo. Nat. Guard, 138th Inf.	St. Louis, Mo.	226	1130	KYO	West'ghouse Elec. & Mfg. Co.	Chicago, Ill.	316	560
KFGL	Arlington Garage	Arlington, Ore.	234	1250	KZM	Electric Shop	Honolulu, Hawaii	360	830
KFGQ	Crary Hardware Co.	Boone, Iowa	226	1330	KZN	Preston D. Allen	Oakland, Cal.	360	830
KFGV	Heidbreder Radio Sup. Co.	Utica, Neb.	224	1340	KZV	The Deseret News	Salt Lake City, Utah	360	830
KFGX	First Presbyterian Church	Orange, Texas	250	1200	WAAB	Wenatchee Bat. & Motor Co.	Wenatchee, Wash.	360	820
KFGY	Gjelhaug's Radio Shop	Baudette, Minn.	224	1340	WAAC	Valdemar Jensen	New Orleans, La.	268	1120
KFGZ	Emmanuel Missionary Col.	Berrien Springs, Mich.	268	1120	WAAD	Tulane University	New Orleans, La.	463	650
KFHA	Colo. State Normal School	Gunnison, Colo.	252	1190	WAAF	Ohio Mechanics Inst.	Cincinnati, Ohio	360	830
KFHB	Rialto Theatre	Hood River, Ore.	280	1070	WAAG	Daily Drivers Journal	Chicago, Ill.	284	1050
KFHD	Utz Elec. Shop Company	St. Joseph, Mo.	226	1330	WAAM	Gimbel Bros.	Milwaukee, Wis.	380	1070
KFHF	Central Christian Church	Shreveport, La.	266	1130	WAAN	I. R. Nelson Company	Newark, N. J.	263	1140
KFHH	Ambrose A. McCue	Neah Bay, Wash.	261	1150	WAAP	University of Missouri	Columbia, Mo.	754	1180
KFHI	Fallon & Company	Santa Barbara, Cal.	360	830	WAAB	Omaha Grain Exchange	Omaha, Neb.	360	830
KFHR	Star Electric & Radio Co.	Seattle, Wash.	270	1110	WABB	Dr. John B. Lawrence	Harrisburg, Pa.	266	1130
KFHS	Clifford J. Dow	Linue, Hawaii	275	1090	WABD	Parker High School	Dayton, Ohio	283	1060
KFHX	Robert W. Nelson	Hutchinson, Kan.	229	1310	WABE	Y. M. C. A.	Washington, D. C.	283	1060
KFI	Earle C. Anthony, Inc.	Los Angeles, Cal.	469	640	WABG	Arnold Edwards Piano Co.	Jacksonville, Fla.	248	1210
KFID	Ross Arbuckle's Garage	Iola, Kan.	246	1220	WABH	Lake Shore Tire Co.	Sandusky, Ohio	240	1250
KFIF	Benson Poly. Institute	Portland, Ore.	360	830	WABI	Bangor Railway & Elec. Co.	Bangor, Me.	240	1250
KFIL	Windisch Elec. Farm Eqp. Co.	Louisburg, Kan.	234	1280	WABK	First Baptist Church	Worcester, Mass.	252	1190
KFIO	North Central High School	Spokane, Wash.	252	1190	WABL	Conn. Agricultural College	Storrs, Conn.	283	1060
KFIQ	Yakima Valley Radio Broad- casting Association	Yakima, Wash.	224	1340	WABM	F. E. Doherty Radio Sup. Co.	Saginaw, Mich.	254	1180
KFIU	Alaska Elec. Light & Pr. Co.	Juneau, Alaska	226	1330	WABN	Waldo C. Grover	La Cross, Wis.	234	1280
KFIX	Church of Latter Day Saints	Independence, Mo.	240	1250	WABO	Lave Ave. Baptist Church	Rochester, N. Y.	282	1190
KFIZ	Daily Commonwealth	Fond du Lac, Wis.	273	1100	WABP	Haverford Col. Radio Club	Haverford, Pa.	261	1150
KFJB	Marshall Electrical Co.	Marshalltown, Iowa	248	1210	WABR	Scott High School	Toledo, Ohio	270	1180
KFJC	Seattle Post-Intelligencer	Seattle, Wash.	233	1290	WABS	Essex Mfg. Co.	Newark, N. J.	244	1230
KFJD	National Radio Mfg. Co.	Oklahoma City, Okla.	252	1190	WABT	Holiday Hall	Washington, Pa.	252	1190
KFJE	Liberty Theatre	Astoria, Ore.	252	1190	WABU	Victor Talking Machine Co.	Camden, N. J.	226	1330
KFJK	Delano Radio & Elec. Co.	Bristow, Okla.	233	1290	WABV	John H. De Witt	Nashville, Tenn.	263	1140
KFJL	Hardsack Mfg. Company	Ottumwa, Iowa	242	1240	WABW	College of Wooster	Wooster, Ohio	234	1280
KFJM	University of North Dakota	Grand Forks, N. D.	229	1310	WABX	H. B. Toy	Mt. Clemens, Mich.	270	1110
KFJO	Valley Radio Co.	Grand Forks, N. D.	280	1070	WABY	John Magaldi	Philadelphia, Pa.	242	1240
KFJR	Ashley C. Dixon & Son	Stevensville, Mont.	288	1160	WABZ	Coliseum Pl. Baptist Church	New Orleans, La.	263	1140
KFJV	T. H. Warren	Dexter, Iowa	224	1340	WBAW	Purdue University	W. Lafayette, Ind.	360	830
KFJW	Le Grand Radio	Tonawanda, Kan.	226	1320	WBAH	The Dayton Company	Minneapolis, Minn.	360	830
KFJX	Iowa State Teachers' Col.	Cedar Falls, Iowa	229	1310	WBAK	Pennsylvania State Police	Harrisburg, Pa.	400	750
KFKA	Tunwall Radio Co.	Fort Dodge, Iowa	246	1220	WBAN	Wireless Phone Corp.	Paterson, N. J.	246	1220
KFVJ	Texas National Guard	Fort Worth, Texas	254	1180	WBAO	James Millikin University	Decatur, Ill.	360	830
KFJZ	Colo. State Teachers' College	Greeley, Colo.	248	1210	WBAP	Star-Telegram	Fort Worth, Texas	476	620
KFKB	Brinkley-Jones Hospital	Milford, Kan.	286	1050	WBAU	Republican Publishing Co.	Hamilton, Ohio	258	1160
					WBAV	Erner & Hopkins Co.	Columbus, Ohio	390	770

Call	Owner	Location	Meters	Kcys.	Call	Owner	Location	Meters	Kcys.
WBAX	John H. Stenger, Jr.	Wilkes-Barre, Pa.	360	830	WJAD	Jackson's Radio Eng. Lab.	Waco, Tex.	360	830
WBAY	American Tel. & Tel.	New York, N. Y.	492	610	WJAF	Muncie Press	Providence, R. I.	360	830
WBBA	Newark Radio Laboratories	Newark, Ohio	240	1250	WJL	Continental Elec. Supply Co.	Washington, D. C.	360	830
WBBB	Barbey Battery Service	Reading, Pa.	234	1280	WJAG	Norfolk Daily News	Norfolk, Neb.	283	1060
WBBE	Alfred R. Marcy	Syracuse, N. Y.	246	1220	WJAK	C. L. White	Norfolk, Neb.	360	830
WBBF	Petoskey High School	Petoskey, Mich.	246	1220	WJAM	D. M. Perham	Greentown, Ind.	254	1180
WBBG	Irving Vermilya	Mattapoisett, Mass.	240	1250	WJAN	Peoria Star	Cedar Rapids, Iowa	268	1120
WBBH	J. Irving Bell	Port Huron, Mich.	246	1220	WJAO	Capper Publications	Peoria, Ill.	280	1070
WBBI	The Indianapolis Radio Club	Indianapolis, Ind.	234	1280	WJAR	The Outlet Co.	Topeka, Kans.	360	830
WBBJ	Neel Electric Co., P. E. Neal,	West Palm Beach, Fla.	258	1160	WJAS	Pittsburgh Radio Sup. House	Pittsburgh, Pa.	250	1200
WBBK	Kaufmann & Baer Co.	Pittsburgh, Pa.	254	1180	WJAT	Kelly-Vawter Jewelry Co.	Marshall, Mo.	360	830
WBBM	Frank Atlas Prod. Co.	Lincoln, Ill.	226	1330	WJAZ	Union Trust Co.	Cleveland, Ohio	390	760
WBBN	Blake, A. B.	Wilmington, N. C.	275	1090	WJZ	Chicago Radio Laboratory	Chicago, Ill.	448	670
WBBQ	Mich. Limestone Co.	Rogers, Mich.	250	1200	WJD	Dennison University	Granville, Ohio	229	1310
WBBR	Frank Crooke,	Pawtucket, R. I.	275	1090	WJH	Wm. P. Boyer Company	Washington, D. C.	273	1100
WBL	People's Pulpit Asso.	Rossville, N. Y.	244	1230	WJX	De Forest Radio T. & T. Co.	New York, N. Y.	360	830
WBR	T. & H. Radio Company	Anthony, Kan.	261	1150	WJY	Radio Corp. of America	New York, N. Y.	405	744
WBS	Penna. State Police	Butler, Pa.	286	1050	WJZ	Radio Corp. of America	New York, N. Y.	455	660
WBT	D. W. May, Inc.	Newark, N. J.	360	830	WKAA	H. F. Paar	Cedar Rapids, Iowa	360	830
WBZ	Southern Radio Corporation	Charlotte, N. C.	360	830	WKAD	Charles Loeff	E. Providence, R. I.	240	1250
WBZ	Westinghouse Elec. & Mfg. Co.	Springfield, Mass.	337	890	WKAF	U. S. Radio Supply Co.	Wichita Falls, Texas	360	830
WCAC	J. Finke Jewelry Mfg. Co.	Fort Smith, Ark.	360	830	WKAN	United Battery Co.	Montgomery, Ala.	226	1330
WCAD	St. Lawrence University	Canton, N. Y.	360	830	WKAP	Dutee W. Flint	Cranston, R. I.	360	830
WCAE	Kaufman & Baer Company	Pittsburgh, Pa.	462	650	WKAQ	Radio Corp. of Porto Rico.	San Juan, P. R.	360	830
WCAH	C. R. Randall	New Orleans, La.	268	1120	WKAU	Mich. Agricultural College	E. Lansing, Mich.	280	1070
WCAI	Entrekin Electric Company	Columbus, Ohio	286	1050	WKAY	Laconia Radio Club	Laconia, N. H.	254	1180
WCAJ	Nebraska Wesleyan Univ'ty	University Place, Neb.	360	830	WKY	Brenau College	Gainesville, Ga.	280	1070
WCAK	Alfred P. Daniel	Houston, Texas	263	1140	WLA	WKY Radio Shop	Oklahoma City, Okla.	360	620
WCAL	St. Olaf College	Northfield, Minn.	360	830	WLAG	Cutting & Wash. Radio Corp.	Minneapolis, Minn.	417	720
WCAM	Villanova College	Villanova, Pa.	360	830	WLAH	Samuel Woodworth	Syracuse, N. Y.	234	1250
WCAN	Sanders & Stayman Company	Baltimore, Md.	360	830	WLAJ	Waco Elec. Supply Co.	Waco, Texas	360	830
WCAP	Chesapeake & Potomac Tel. Co.	Washington, D. C.	469	640	WLB	Vt. Farm Machine Corp.	Bellevue Falls, Vt.	360	830
WCAR	Alamo Radio Elec. Co.	San Antonio, Texas	360	830	WLB	Naylor Elec. Co.	Tulsa, Okla.	360	830
WCAS	Wm. Hood Dunwoody Ind. Inst.	Minneapolis, Minn.	246	1220	WLB	W. V. Jordan	Louisville, Ky.	360	830
WCAT	S. D. School of Mines	Rapid City, S. D.	240	1250	WLB	A. E. Schilling	Kalamazoo, Mich.	283	1060
WCAU	Durham & Company	Philadelphia, Pa.	286	1050	WLB	Electric Shop	Pensacola, Fla.	254	1180
WCAV	J. C. Dice Elec. Co.	Little Rock, Ark.	360	830	WLB	Police Dept. of N. Y. City	New York, N. Y.	360	830
WCAW	Kesselman O'Driscoll Co.	Milwaukee, Wis.	261	1150	WLB	Putnam Electric Company	Greencastle, Ind.	231	1300
WCBA	Charles W. Heimbach	Allentown, Pa.	280	1070	WLB	University of Minnesota	Minneapolis, Minn.	360	830
WCBC	University of Michigan	Ann Arbor, Mich.	280	1070	WLB	Crosley Mfg. Co.	Cincinnati, Ohio	309	970
WCBD	Wilbur G. Voliva	Zion, Ill.	345	870	WLB	Clive B. Meredith	Cazenovia, N. Y.	261	1150
WCK	Stix-Baer & Co. & Fuller Co.	St. Louis, Mo.	360	830	WLB	Round Hills Radio Corp.	Dartmouth, Mass.	360	830
WCM	University of Texas	Austin, Texas	360	830	WLB	General Supply Company	Lincoln, Neb.	254	1180
WCX	Detroit Free Press	Detroit, Mich.	517	580	WLB	Drovers Telegram Company	Kansas City, Mo.	275	1090
WDAE	Tampa Daily Times	Tampa, Fla.	360	830	WLB	Norton Laboratories	Lockport, N. Y.	360	830
WDAF	Kansas City Star	Kansas City, Mo.	411	730	WLB	Trenton Hardware Company	Trenton, N. J.	256	1170
WDAG	J. Lawrence Martin	Amarillo, Texas	263	1140	WLB	Broad St. Baptist Church	Columbia, Ohio	286	1050
WDAH	Trinity Meth. Church (So.)	El Paso, Texas	268	1120	WLB	Utility Battery Service	Easton, Pa.	246	1220
WDAJ	Atlanta & West Point R.R. Co.	College Park, Ga.	360	830	WLB	Chicago Daily News	Chicago, Ill.	448	672
WDAK	The Courant	Hartford, Conn.	261	1150	WLB	Alabama Poly. Inst.	Auburn, Ala.	250	1200
WDAO	Automotive Electric Co.	Dallas, Texas	360	830	WLB	Walshpeton Electric Co.	Walshpeton, N. D.	254	1180
WDAP	Board of Trade	Chicago, Ill.	360	830	WLB	Kingshighway Pres. Church	St. Louis, Mo.	280	1070
WDAR	Lit Bros.	Philadelphia, Pa.	395	760	WLB	Mercer University	Macon, Ga.	268	1120
WDAS	Samuel A. Waite	Worcester, Mass.	360	830	WLB	Commercial Appeal	Memphis, Tenn.	500	600
WDAU	Slocum & Kilburn	New Bedford, Mass.	360	830	WLB	Doubleday-Hill Elec. Co.	Washington, D. C.	261	1150
WDAY	Fargo Radio Electric Co.	Fargo, N. D.	244	1280	WLB	Shepard Stores	Boston, Mass.	278	1080
WDBC	Kirk, Johnson & Company	Lancaster, Pa.	258	1160	WLB	University of Oklahoma	Norman, Okla.	360	830
WDM	Church of the Covenant	Washington, D. C.	234	1280	WLB	R. J. Rockwell	Omaha, Neb.	242	1240
WDZ	James L. Bush	Tuscola, Ill.	248	1210	WLB	Syracuse Radio Telephone Co.	Syracuse, N. Y.	286	1050
WEAA	Fallain & Lathrop	Flint, Mich.	280	1070	WLB	Wittenberg College	Springfield, Ohio	230	1300
WEAF	West. Elec. Co. (A. T. & T.)	New York, N. Y.	492	610	WLB	Charleston Radio Elec. Co.	Charleston, S. C.	360	830
WEAH	Wichita Board of Trade	Wichita, Kan.	244	1230	WLB	C. C. Rhodes	Butler, Mo.	231	1300
WEAI	Cornell University	Ithaca, N. Y.	286	1050	WLB	Austin Statesman	Austin, Tex.	360	830
WEAJ	University of South Dakota	Vermilion, S. D.	280	1070	WLB	Lenning Bros. Co.	Philadelphia, Pa.	360	830
WEAM	Borough of North Plainfield	North Plainfield, N. J.	252	1190	WLB	Peoples Tel. & Tel. Co.	Knoxville, Tenn.	236	1270
WEAN	Shepard Company	Providence, R. I.	273	1100	WLB	Peninsular Radio Club	Ft. Monroe, Va.	360	830
WEAO	Ohio State University	Columbus, Ohio	360	830	WLB	Dakota Radio Apparatus Co.	Yankton, S. Dak.	244	1280
WEAP	Mobile Radio Company	Mobile, Ala.	360	620	WLB	Shotton Radio Mfg. Co.	Albany, N. Y.	360	830
WEAR	Balto. Am. & News Pub. Co.	Baltimore, Md.	360	830	WLB	Valley Radio	Grand Forks, N. D.	280	1070
WEAS	Hecht Company	Washington, D. C.	360	830	WLB	Maus Radio Co.	Lima, Ohio	266	1130
WEAU	Davidson Bros. Company	Sioux City, Iowa	360	830	WLB	Friday Battery & Elec. Corp.	Sigourney, Iowa	360	830
WEAY	Will Horowitz, Jr.	Houston, Texas	360	830	WLB	Midland College	Fremont, Neb.	360	830
WEB	Benwood Company	St. Louis, Mo.	360	830	WLB	Tyler Commercial College	Tyler, Tex.	360	830
WEV	Hurlburt-Still Electrical Co.	Houston, Texas	360	830	WLB	Apollo Theatre	Belvidere, Ill.	224	1340
WEW	St. Louis University	St. Louis, Mo.	261	1150	WLB	Palmetto Radio Corp.	Charleston, S. C.	360	830
WFAA	Dallas News & Dallas Journal	Dallas, Texas	476	620	WLB	Evening News & Express	San Antonio, Tex.	385	780
WFAB	Carl F. Woese	Syracuse, N. Y.	234	1280	WLB	Em. E. Woods	Webster Groves, Mo.	286	1050
WFAF	H. C. Spratley Radio Co.	Poughkeepsie, N. Y.	360	830	WLB	Vaughn Conservat'y of Music	Lawrenceburg, Tenn.	360	830
WFAH	Electric Supply Company	Port Arthur, Texas	360	830	WLB	Lyradion Mfg. Co.	Mishawaka, Ind.	360	830
WFAJ	Hi-Grade Wireless Inst. Co.	Asheville, N. C.	360	830	WLB	Kalamazoo College	Kalamazoo, Mich.	240	1250
WFAM	Times Publishing Company	St. Cloud, Minn.	485	620	WLB	Henry P. Lundskow	Kenosha, Wis.	229	1310
WFAN	Hutchinson Elec. Ser. Co.	Hutchinson, Minn.	360	830	WLB	Boyd M. Hamp	Wilmington, Del.	360	830
WFAQ	Wo. Wesleyan College	Cameron, Mo.	360	830	WLB	Penn. National Guard	Erie, Pa.	248	1240
WFAV	U. of Neb. Dept. of Elec Eng.	Lincoln, Neb.	275	1090	WLB	Woodmen of the World	Omaha, Neb.	526	570
WFI	Strawbridge & Clothier	Philadelphia, Pa.	395	760	WLB	Franklin J. Wolff	Trenton, N. J.	240	1250
WGAL	Lancaster Elec. Supply Co.	Lancaster, Pa.	248	1210	WLB	Palmer Sch. of Chiropractic	Davenport, Iowa	484	620
WGAN	Cecil E. Lloyd	Pensacola, Fla.	360	830	WLB	Iowa State College	Ames, Iowa	360	830
WGAO	Glenwood Radio Corp.	Shreveport, La.	360	830	WLB	John Wanamaker	Philadelphia, Pa.	509	590
WGAW	Ernest C. Albright	Altoona, Pa.	261	1150	WLB	Western Radio Company	Kansas City, Mo.	360	830
WGAZ	South Bend Tribune	South Bend, Ind.	360	830	WLB	L. Bamberger & Co.	Newark, N. J.	405	740
WGI	Amer. Radio Research Corp.	Medford Hillside, Mass.	485	620	WLB	Mo. State Marketing Bureau	Jefferson City, Mo.	441	680
WGR	Federal Tel. & Tel. Co.	Buffalo, N. Y.	360	830	WLB	Penn. State College	State College, Pa.	283	1060
WGV	Interstate Electric Co.	New Orleans, La.	242	1240	WLB	Donaldson Radio	Okmulgee, Okla.	360	830
WGY	General Electric Co.	Schenectady, N. Y.	380	760	WLB	Wis. Dept. of Markets	Waupaca, Wis.	360	830
WHA	University of Wisconsin	Madison, Wis.	360	830	WLB	Doolittle Radio Corp.	New Haven, Conn.	268	1120
WHAA	State University of Iowa	Iowa City, Iowa	283	1060	WLB	N. Dak. Agricultural College	Agricultural Col., N. D.	360	620
WHAB	Clark W. Thompson	Galveston, Texas	360	830	WLB	Superior Rad. Tel. & Eq. Co.	Columbus, Ohio	286	1050
WHAD	Marquette University	Milwaukee, Wis.	280	1070	WLB	Auerbach & Guettel	Topeka, Kans.	360	830
WHAG	University of Cincinnati	Cincinnati, Ohio	222	1350	WLB	Theodore D. Philips	Winchester, Ky.	360	830
WHAH	Hafer Supply Co.	Joplin, Mo.	283	1060	WLB	Gen. Sales & Engineering Co.	Frostburg, Md.	360	830
WHAK	Roberts Hardware Co.	Clarksburg, W. Va.	360	830	WLB	St. Patrick's Cathedral	El Paso, Tex.	360	830
WHAM	University of Rochester	Rochester, N. Y.	283	1060	WLB	Concordia College	Moorhead, Minn.	360	620
WHAP	Otta & Kuhns	Decatur, Ill.	360	830	WLB	Dr. John R. Koch	Charleston, W. Va.	273	1100
WHAR	Paramount Radio & Elec. Co.	Atlantic City, N. J.	231	1300	WLB	Nushagwa Poultry Farm	New Lebanon, Ohio	234	1280
WHAS	Courier-Journal & Lo. Times	Louisville, Ky.	400	750	WLB	Horace A. Beale, Jr.	Parkesburg, Pa.	360	830
WHAV	Wilmington Elec. Spec. Co.	Wilmington, Del.	360	830	WLB	E. B. Gish	Amarillo, Tex.	360	830
WHAZ	Rensselaer Poly. Inst.	Troy, N. Y.	380	760	WLB	Whithall Electric Co.	Waterbury, Conn.	242	1240
WHB	Sweeney School Co.	Kansas City, Mo.	411	730	WLB	Moore Radio News Sta.	Springfield, Vt.	275	1090
WHK	Radio Box Co.	Cleveland, Ohio	283	1060	WLB	Sandusky Register	Sandusky, Ohio	240	1250
WHN	Loew's State Theatre	New York, N. Y.	360	830	WLB	Brock-Anerson Elec. Eng. Co.	Lexington, Ky.	254	1180
WHT	Mich. Limestone & Chem. Co.	Rogers, Mich.	300	1000	WLB	Coles Co. Tel. & Tel. Co.	Mattoon, Ill.	258	1160
WIAB	Joslyn Automobile Co.	Rockford, Ill.	252	1190	WLB	Electrical Equipment Co.	Miami, Fla.	283	1060
WIAC	Galveston Tribune	Galveston, Texas	360	830	WLB	Scranton Times	Scranton, Pa.	280	1070
WIAD	H. R. Miller	Philadelphia, Pa.	254	1180	WLB	Calvary Baptist Church	New York, N. Y.	360	830
WIAF	Gustava DeCortin	New Orleans, La.	234	1250	WLB	West Texas Radio Co.	Abilene, Tex.	285	1050
WIAI	Heer Stores Company	Springfield, Mo.	252	1190	WLB	Prince-Walter Company	Lowell, Mass.	266	1130
WIAJ	Fox Riv. Val. Radio Supply Co.	Neenah, Wis.	224	1340	WLB	Huntington & Guerry, Inc.	Greenville, S. C.	258	1160
WIAK</									

Call	Owner	Location	Meters	Kcys.	Call	Owner	Location	Meters	Kcys.
WRAL	Northern States Power Co.	St. Croix Falls, Wis.	248	1210	CFCR	Laurentide Air Service	Sudbury, Ont.	410	730
WRAN	Black Hawk Electrical Co.	Waterloo, Iowa	236	1270	CFCW	The Radio Shop	London, Ont.	420	710
WRAO	Radio Service Co.	St. Louis, Mo.	360	830	CFDC	Sparks Co.	Nanaimo, B. C.	430	700
WRAV	Jacob C. Thomas	David City, Neb.	226	1330	CFOC	Electric Shop, Ltd.	Saskatoon, Sask.	400	750
WRAW	Antioch College	Yellow Springs, O.	242	1240	CFRC	Queen's University	Kingston, Ont.	450	670
WRAX	Avenue Radio Shop	Reading, Pa.	360	830	CFUC	University of Montreal	Montreal, Que.	400	730
WRAY	Flaxon's Garage	Gloucester City, N. J.	268	1120	CHAC	Radio Engineers, Ltd.	Halifax, N. S.	400	750
WRBZ	Radio Sales Corporation	Scranton, Pa.	280	1070	CHBC	The Albertan Pub. Co.	Calgary, Alta.	410	730
WRZ	Radio Shop of Newark	Newark, N. J.	233	1290	CHCB	Marconi Company	Toronto, Ont.	440	680
WRC	Radio Corp. of America	Washington, D. C.	469	640	CHCC	Canadian Westinghouse Co.	Edmonton, Alta.	400	730
WRK	Doron Bros. Elec. Co.	Hamilton, Ohio	360	830	CHCD	Canadian Wireless & Elec. Co.	Quebec, Que.	410	730
WRL	Union College	Schenectady, N. Y.	360	830	CHCE	W. Canada Radio Supply, Ltd.	Victoria, B. C.	400	750
WRM	University of Illinois	Urbana, Ill.	360	830	CHCL	The Vancouver Merchants Exchange, Ltd.	Vancouver, B. C.	440	680
WRR	City of Dallas	Dallas, Tex.	360	620	CHYC	North Electric Co., Ltd.	Montreal, Que.	410	730
WRW	Tarrytown Radio Research	Tarrytown, N. Y.	273	1100	CJCA	The Edmonton Journal, Ltd.	Edmonton, Alta.	450	670
WSAB	S. E. Mo. State Teachers Col.	Cape Girardeau, Mo.	360	830	CJCC	London Free Press	London, Ont.	430	700
WSAC	Clemson Agricultural College	Clemson College, S. C.	360	830	CJCD	T. Eaton Company	Toronto, Ont.	410	730
WSAD	J. A. Foster Company	Providence, R. I.	261	1150	CJCE	Sprott-Shaw Radio Co.	Vancouver, B. C.	420	710
WSAG	City of St. Petersburg	St. Petersburg, Fla.	244	1230	CJCF	Maritime Radio Corp., Ltd.	St. John, N. B.	400	750
WSAH	A. J. Leonard, Jr.	Chicago, Ill.	248	1210	CJCN	Simons, Agnew & Co., Ltd.	Toronto, Ont.	410	730
WSAI	U. S. Playing Card Co.	Cincinnati, Ohio	309	970	CJCS	Percival Wesley Shackleton	Olds, Alta.	400	750
WSAJ	Grove City College	Grove City, Pa.	360	830	CKAC	The Evening Telegram	Toronto, Ont.	430	700
WSAL	Franklin Electric Co.	Brookville, Ind.	246	1220	CKAD	La Presse Pub. Co., Ltd.	Montreal, Que.	430	700
WSAN	Allentown Radio Club	Allentown, Pa.	229	1310	CKAE	Vancouver Daily Province	Vancouver, B. C.	410	730
WSAR	Doughty & Welch Elec. Co.	Fall River, Mass.	254	1180	CKAF	Canadian Independent Tel. Co.	Toronto, Ont.	450	670
WSAT	Donohoe-Ware Co.	Plainview, Tex.	268	1120	CKAG	Leader Publishing Co., Ltd.	Regina, Sask.	420	710
WSAU	Camp Marienfeld	Chesham, N. H.	229	1310	CKAH	Wentworth Radio Supply Co.	Hamilton, Ont.	410	730
WSAW	J. J. Long	Canandaigua, N. Y.	275	1090	CKAI	Manitoba Telephone System	Winnipeg, Man.	450	670
WSAX	Chicago Radio Laboratory	Chicago, Ill.	268	1120	CKAJ	C. P. Edwards	Ottawa, Que.
WSAY	Irving Austin	Portchester, N. Y.	230	1300	OA				
WSAZ	Chase Radio Co.	Pomeroy, Ohio	258	1160					
WSB	Atlanta Journal	Atlanta, Ga.	429	700					
WSL	J. & M. Electric Co.	Utica, N. Y.	273	1100					
WSY	Alabama Power Company	Birmingham, Ala.	360	830					
WTAB	Fall River Daily Herald	Fall River, Mass.	248	1210					
WTAC	Penn. Traffic Company	Johnstown, Pa.	360	830					
WTAF	Lewis J. Gallo	New Orleans, La.	268	1120					
WTAG	Kern Music Company	Providence, R. I.	258	1160					
WTAH	Carmen Ferro	Belvidere, Ill.	236	1270					
WTAJ	The Radio Shop	Portland, Me.	236	1270					
WTAK	Swan-Bower Company	Steubenville, Ohio	266	1130					
WTAL	Toledo Radio & Elec. Co.	Toledo, Ohio	252	1190					
WTAM	Willard Storage Battery Co.	Cleveland, Ohio	390	770					
WTAN	Orendorff Radio Co.	Mattoon, Ill.	240	1250					
WTAP	Cambridge Radio Elec. Co.	Cambridge, Ill.	242	1240					
WTAQ	S. Van Gorden	Oseo, Wis.	226	1330					
WTAR	Reliance Radio & Elec. Co.	Norfolk, Va.	280	1070					
WTAS	Geo. D. Carpenter	Elgin, Ill.	275	1090					
WTAU	Ruegg Battery & Elec. Co.	Tecumseh, Nebr.	360	830					
WTAW	Agricultural & Mech. College	College Stations, Tex.	254	1180					
WTAX	Williams Hardware Mfg. Co.	Streator, Ill.	231	1300					
WTAY	The Oak Leaves	Oak Park, Ill.	226	1330					
WTAZ	T. J. McGuire	Lambertville, N. J.	280	1070					
WTG	Kans. State Agr. College	Manhattan, Kans.	360	830					
WWAC	Sanger Bros.	Waco, Tex.	360	830					
WWAD	Wright & Wright, Inc.	Philadelphia, Pa.	360	830					
WWAW	Mich. College of Mines	Houghton, Mich.	244	1230					
WWI	Ford Motor Company	Dearborn, Mich.	273	1100					
WWJ	Detroit News	Detroit, Mich.	517	580					
WWL	Loyola University	New Orleans, La.	280	1070					
WWT	McCarthy Bros. & Ford	Buffalo, N. Y.	360	830					

CANADA				
Call	Owner	Location	Meters	Kcys.
CFAC	The Calgary Herald	Calgary, Alta.	430	700
CFCA	Star Pub. & Printing Co.	Toronto, Ont.	400	750
CFCF	Marconi Wireless Tel. Co. of Canada	Montreal, Quebec	440	680
CFCH	Abitibi Pow. & Paper Co., Ltd.	Iroquois Falls, Ont.	400	750
CFCI	La Cie de L'Evenement	Quebec, Que.	410	730
CFCK	Radio Supply Co., Ltd.	Edmonton, Alta.	410	730
CFCL	Centennial Methodist Church	Victoria, B. C.	400	750
CFCN	W. W. Grant Radio, Ltd.	Calgary, Alta.	440	680
CFCO	Semmelhaack-Dickson, Ltd.	Bellevue, Que.	450	670
CFQ	Radio Specialties, Ltd.	Vancouver, B. C.	450	670

CUBA				
Call	Owner	Location	Meters	Kcys.
PWX	Cuban Telephone Co.	Habana	400	750
2DW	Pedro Zayas	Habana	300	1000
2AB	Alberto S. de Bustamante	Habana	240	1250
2OK	Mario Garcia Velez	Habana	360	830
2BY	Frederick W. Borton	Habana	260	1150
2CX	Frederick W. Borton	Habana	320	940
2EV	Westinghouse Elec. Co.	Habana	220	1360
2TW	Roberto E. Ramires	Habana	230	1300
2HC	Heraldo de Cuba	Habana	275	1090
2LC	Luis Casas	Habana	250	1200
2KD	E. Sanchez de Fuentes	Habana	350	860
2MN	Fausto Simon	Habana	270	1110
2MG	Manuel G. Salas	Habana	280	1070
2JO	Raul Perez Falcon	Habana	150	1990
2KP	Alvira Daza	Habana	200	1500
2HS	Julio Power	Habana	180	1660
2OL	Oscar Collado	Habana	290	1030
2WW	Amadeo Saenz	Habana	210	1430
5EV	Leopoldo V. Figueroa	Colon	360	830
6KW	Frank H. Jones	Tuinucu	340	880
6KJ	Frank H. Jones	Tuinucu	275	1090
6CX	Antonio T. Figueroa	Cienfuegos	170	1760
6DW	Eduardo Terry	Cienfuegos	225	1330
6BY	Jose Gandux	Cienfuegos	300	1000
6AZ	Valentin Ullivarri	Cienfuegos	200	1500
6EV	Josefa Alvarez	Caibarien	225	1330
8BY	Alberto Ravelo	Stgo. de Cuba	240	1250
8AZ	Alfredo Brooks	Stgo. de Cuba	250	1200
8FU	Andres Vinnat	Stgo. de Cuba	225	1330
8DW	Pedro C. Anduz	Stgo. de Cuba	275	1090
8EV	Eduardo Mateos	Stgo. de Cuba	180	1660

PORTO RICO				
Call	Owner	Location	Meters	Kcys.
WGAD	Sp. Am. Sch. of Radio Tel.	Ensenada	300	1800
WKAQ	Radio Corp. of Porto Rico	San Juan	360	830

MEXICO				
Call	Owner	Location	Meters	Kcys.
CYL	La Casa del Radio	Mexico City, Mexico	500	600

Canary's Obligato Keeps Sailors in Jail

By Washington R. Service

ONE would scarcely think the sweet song of a canary would in any way affect the prolongation of the incarceration of three of Uncle Sam's sailors in a Japanese prison, but so the tale of an ex-Navy radio operator goes. Three firemen from the good ship "Orion" got themselves in wrong with the Nagasaki authorities, and were detained ashore, although their ship was sailing. Upon the request of his captain, the "Orion" operator called the flag ship to ask that steps be taken to secure the firemen's release and return to the United States.

Sparks got his message off, despite the fact that a canary he was bringing home sang in harmony with the ship's radio wave note. As soon as the operator started to listen in for his O.K., the bird redoubled its efforts in a key

which interfered so seriously with the reception of the flag ship's answer that it made impossible to get the message. Sparks couldn't leave his key to put the bird out of the shack, so he threw spare parts and tools in its general direction, without effect. Again he called the flag ship; again the dicky bird, now exceedingly unpopular with its temporary owner, began its lusty song. As the ship steamed out to sea, the operator gave up in despair; he couldn't get his answer through the canary's QRM. It developed later that "Orion's" message was not received correctly, and the unlucky firemen were held in the Japanese "brig" several months, all because of the canary's sweet obligato. The bird finished the voyage in a stateroom, but when delivered to its ultimate owner ashore, it refused to sing again.

Every State Now Has a Broadcasting Station

WITH the recent licensing of KFNG, at Coldwater, Miss., every state in the Union had one or more broadcasters, it was learned at the Bureau of Navigation, Department of Commerce. This is not the

first time, however, that each state has been listed; last year a broadcasting station opened up in Corinth, Mississippi, which completed the roster, but this station later dropped out, leaving one of the 48 states unrepresented.

The Radio University

A Question and Answer Department conducted by the Technical Staff of RADIO WORLD for the information and instruction of its subscribers. A "trouble shooter" is always ready here to help new radio fans.

I have constructed the Superdyne receiver, using the very best parts, such as Hammerlund condensers, Condensite sockets, and coils wound on latticed bakelite tubes, which I tooled out myself, so as to have the least amount of insulating material necessary to support the coils. I use Bradleystats to control the filament current, and the rest of the parts are all of really high quality. My trouble is this. I can tune in the local stations fine with wonderful clarity and clearness, and no distortion, but after fooling with it a week and a half cannot tune in anything more distant than KDKA, which I can bring in on a single tube set without any antenna. Is this a good distance receiver? Are there any models made up which will back up the claims made for them? What can the trouble be, seeing as the receiver works to perfection on all the nearby stations, even cutting the powerful WEAf out entirely and listening to WIP with absolutely no interference?—Kenneth Halper, 1600 Broadway, N. Y. C.

Your trouble can be easily diagnosed. You do not know how to tune the distant stations, or signals in. This receiver, while wonderfully clear and distinct, and sharp in tuning, must be operated in a certain manner. It is also of advantage in

Where can the flat spiderweb variometers used in the "autoplex," as described by B. C. Caldwell, be obtained?—C. H. Karuts, 1104 Broadway, N. Y. C.

They may be obtained from the Biltmore Radio Co., 238 Lamartine Street, Boston 30, Mass. The complete set may be purchased from these people.

Please publish a diagram of a detector and two stage amplifier, using "C" batteries in the grid leads of the audio frequency tubes. Can selective, stable and satisfactory results be secured with a set using transformer coupled radio frequency and regeneration?—Kenneth H. Jones, London Mills, Ill.

The diagram you desire is herewith published. The minus side of the "C" battery goes to the grid of the tubes, the plus going to the transformer grid secondary. For your information, if you use over 60 volts it is desirable to use 3 volts minus bias on the tube. If not over 60, a single 1½-volt cell in each tube will suffice, although a little experimentation on this value especially in the second tube should prove the best value in a short space of time. Tune in a strong signal, and vary the value of "C" battery with a slightly

ization of tube capacity without the necessary neutrotons. The illustration shows a regulation air-core coupler such as the neutrodyne receivers use. How does he make a D coil out of a round tube? What is the size of the tube used? What is the size of the wire? How is the primary arranged, so that it may also be a D coil? Will these coils work equal to a regulation neutralized radio frequency coil set? Is it possible to neutralize tube capacity by means such as he outlines?—Otto Bank, 908 Ottwards Building, Cincinnati, Ohio.

The D coils may be wound on a regulation tube by doing the following: Obtain a 3½" tube (radion, bakelite, formica) and cut two ¼" slots, one on either side of the coil. Cut these down to within 1" of the end of the tube. You will then be enabled to wind the D form coil on this. You may use either No. 22 or 24 DSC wire—do not use shellac or binder. Wind the primary at the beginning of the slot (1 near the 1" solid end and then leave a space of about ¼" and begin the winding of the secondary. These coils will work in the set mentioned, using the hookup given in the book you mention. Set them at the same angle as those of the Neutrodyne, namely 60° off vertical. It is perfectly possible and highly plausible to do this, providing the correct wiring is used, and the leads do not interfere in any manner. Be careful when using a coil of this sort that the insulation of the coils is not "stripped" when bringing it around the sharp corner of the D form. For this purpose it is best to file the corners round, and to wind the wire just tight enough to hold, but not so tight that the form will cut through the insulation and bare the wire. More care is necessary in constructing a set of this type than of the neutrodyne type, as you are dealing with very fine balances which is one of the reasons that the neutrodyne is so nearly fool proof—it is not so severely critical.

I have just purchased a receiver which I know from other's experience is a good set. My trouble is that I cannot seem to get the third tube to work properly. I get good results on two tubes, but when I plug it in the third, the sound is reduced and sandy. When I place my hand on the tube and push it to the left side, facing the slot in the socket it works fine, but the moment I remove my hand, the amplification falls and it gets sandy again.—Myron Cohen, 1640 Park Ave., New York City.

You evidently have a socket which is making imperfect contact with the tube. Remove the tube from the socket, and see if there is something interfering with the contact of the tube prongs. It may be that the prongs are loose. Pry them up so that they have a slight spring to them when the tube is inserted in the socket.

I have constructed the Superdyne receiver and it works fine, giving all the volume that my five tube neutrodyne did on distance, and even more when tuned to exact resonance. How can I eliminate the shrill whistle that lasts for about two seconds when the set is tuned? The receiver is very quiet otherwise, but this short whistle makes it impossible to use the loud speaker late at night.—K. M. Kalbe, New York City.

This whistle as you term it should present itself as a rather high hiss. Suggest that you use a slightly larger size of grid condenser in the detector tube circuit. It is not possible to do away with this hiss, if the receiver is working properly, but as it does not last long it should not prove annoying.

Please advise me of some minor details of the Superdyne. What length of tubing (4" OD) should be necessary for the construction of the coupler and coil? What does "OD" mean?—A. Miller, Rosedale, L. I., N. Y.


As each winding takes up 1¼", you will need a 2" piece for the tuned impedance coil, and a 2½ or 3" piece for the coupler. OD is a mechanical term, meaning outside diameter, or outside dimension. This means that the tube should be 4" in diameter measured from the outside.

Does the proximity of the radio frequency coil to L1 and LF1 and tickler coils have any effect on the efficiency of the superdyne?—C. C. Seymour, P. O. Box 591, Barrington, N. J.

This coil is to be wound in the opposite direction to the ones mentioned, and should be set at an angle of 90 degrees to them. This will stand it upright, with its windings vertical. It should be located at least 2" distant from the coil.

What is the wave length of PWX? I have tried to get him every time I see his call letters in the papers, but have had no success. Is he powerful enough to be heard by amateurs in this section?—M. Fleischer, Bradford, Pa.

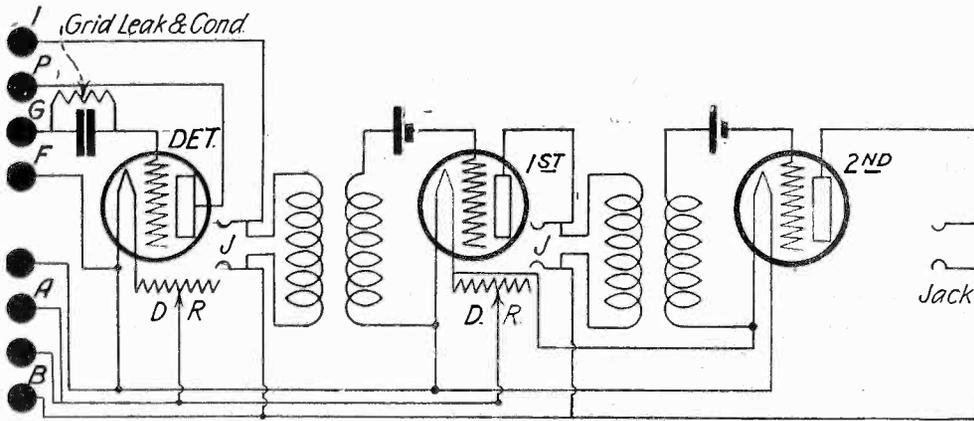This station operates on a wave length of 400 meters. It is a rather hard station to tune in on anything less than a very selective and sensitive receiver, seeing as it is so distant and is also operating on a wave band that is rather crowded. He has been received in the vicinity you mention, but not as a regular performance.



Detector and two stages of audio-frequency amplification with "C" batteries asked for by Kenneth H. Jones.

some receivers to include a grid leak (variable—of very high manufacture such as Bradleyleak, or Variotom or some similar make) from the grid side of the condenser to the filament of the tube. Tuning in weak signals in this receiver is much harder than on the other makes, and for this reason it is known as a "tricky set." Patience and lots of practice on tuning weak signals, will do wonders for the receiver. Vernier controls are absolutely necessary.

I have constructed the Superdyne as per the articles in RADIO WORLD for Dec. 15, 22 and 29, using the following apparatus: One Murdock condenser; one unknown make; Workrite sockets; Franco B battery two UV199 tubes; Dubilier grid condenser. The tubes for the windings are cardboard. Have you any suggestions in regard to the apparatus used? How far above the top of the secondary should the center of the rotor be? Why does my detector rheostat have more to do with the tuning than the radio frequency tube? Which terminals of a UV199 is the filament minus? Should the primary be wound in the same direction as the secondary? What causes a steady click in the receiver which stops if I touch the grid circuit of the detector tube?—Robert Reynolds, Cumming, Ia.

The condensers you mention would do for a purely experimental receiver, but for a receiver that is to give constant use would suggest that you use better ones. Condensers were specified in the article; if possible obtain them and use them. Use either radion or formica tubing instead of cardboard. Cardboard is hygroscopic and is poor material to use when constructing a super sensitive set of the type described. We note you have constructed a two-tube receiver, so if you intend to incorporate audio frequency in it, suggest that you use the best of everything when you rebuild it. The bottom of the rotor should be so located that the last turn is about 1" above the top of the secondary winding. The detector tube will have most to do with the reception in any receiver, but in this receiver if it is properly constructed it should not be critical. This depends upon how you wire it up—it makes no difference which side of the filament itself is connected to the minus or plus side as long as the wiring in the circuit is correct. No. The click is caused by too small a grid condenser; use one size larger and incorporate a small grid leak from the grid side of the condenser to the filament-grid return.

higher filament current than you normally use, and the best value will show itself in a distortionless signal. The results you desire may be had if a variable transformer of the Ballantine type is used. However, at its best, it will prove unstable, and tricky to handle, so suggest that you use the radio frequency without the regeneration. Two stages of good tuned radio frequency amplification if constructed carefully should prove far more satisfactory than any regenerative set made. Use the best apparatus, however, if good results are wanted.

In regard to the superdyne, would it be possible to get the American stations on one properly constructed and following directions? What distance has been covered on it consistently? Does it regenerate or is it non-regenerative? Can the Ediswan Dull emitter type A. R. 06 valve be used in this circuit?—C. Bell, Hull, England.

While this is a good receiver and capable of extremely good work as far as distance is concerned it is a matter of conjecture if the circuit will consistently work under the conditions you name. Under practical test conditions the circuit has showed a consistent range of 2,000 miles, with much better range, conditions of course favoring such work. However as reception over water is much better than over land, you should have no trouble in getting the American coastal stations such as WJZ, WEAf, KDKA and others, under good conditions. This valve is identical to the UV199, which is a high emission thoriated filament tube. You may use his valve.

In Kenneth Harkness' book "Radio Frequency Amplification" the writer mentions a D coil, made by himself, in which he was able to obtain neutral-

Join RADIO WORLD'S University Club

And Get Full Question and Answer Service for the Coming 52 Weeks.

RADIO WORLD, 1493 Broadway, New York City:

Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also consider this as an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year.

Name
 Street
 City and State

RADIO WORLD

TELEPHONES:

LACKAWANNA 6976 and LACKAWANNA 2063
 PUBLISHED EVERY WEDNESDAY (Dated
 SATURDAY OF SAME WEEK)
 FROM PUBLICATION OFFICE,
 1493 BROADWAY, NEW YORK, N. Y.
 BY HENNESSY RADIO PUBLICATIONS
 CORPORATION
 ROLAND BURKE HENNESSY, President
 M. B. HENNESSY, Vice-President
 FRED S. CLARK, Secretary and Manager
 1493 BROADWAY, NEW YORK, N. Y.
 Boston Representative: Chas. H. M. White, 1367 Com-
 monwealth Avenue, Allston, Mass.
 Chicago Representative: Mat H. Friedman, 519 East 60th
 St., Chicago, Ill.
 Philadelphia Representative: J. M. Lane, 765 South Fifth
 Street, Philadelphia, Pa.
 San Francisco Representative: Conger & Johnston, Hol-
 brook Building.
 Los Angeles Representative: Conger & Johnston, Higgins
 Building.
 European Representatives: The International News Co.,
 Brema Bldgs., Chancery Lane, London, Eng. Paris,
 France: Brentano's 38 Avenue de l'Opera.

Editor

Roland Burke Hennessy

Managing Editor
 Stephen L. Coles

Technical Editor
 Robert L. Dougherty

SUBSCRIPTION RATES

Fifteen cents a copy, \$6.00 a year. \$3.00 for six
 months. \$1.50 for three months. Add \$1.00 a year
 extra for foreign postage. Canada, 50 cents.

Receipt by new subscribers of the first copy of RADIO
 WORLD mailed to them after sending in their order, is
 automatic acknowledgement of their subscription order.
 Changes of address should be received at this office two
 weeks before date of publication. State whether sub-
 scription is new or a renewal.

ADVERTISING RATES

One page: One time—\$150.00.
 Half, Quarter, Third and Two-thirds pages at propor-
 tionate rates.

One inch, one time—\$5.00. Per agate line \$0.40.

On four consecutive issues, 10% discount.

On thirteen consecutive issues, 15% discount.

Cover and preferred-position rates made known on
 application.

Terms: 30 days net. 2% 10 days.

CLASSIFIED ADVERTISEMENTS

Five cents per word. Minimum, 10 words. Discount
 of 10% on 4 consecutive issues—15% on thirteen consecu-
 tive issues. Cash with order.

Entered as second-class matter, March 28, 1922, at
 the Post Office at New York, New York, under the act
 of March 3, 1879.

IMPORTANT NOTICE

While every possible care is taken to state correctly
 matters of fact and opinion in technical and general writ-
 ings covering the radio field, and every line printed is
 gone over with a scrupulous regard for the facts, the
 publisher disclaims any responsibility for statements re-
 garding questions of patents, priority of claims, the proper
 working out of technical problems, or other matters that
 may be printed in good faith and on information furnished
 by those supposed to be trustworthy. This statement is
 made in good faith and to save time and controversy in
 matters over which the publisher cannot possibly have
 control.

FEBRUARY 16, 1924

Woodrow Wilson

WOODROW WILSON, twenty-
 eighth President of the United
 States, passed on peacefully and pain-
 lessly, after four years of ill health,
 at his home in Washington on Feb-
 ruary third. His death brought to his
 family literally thousands of messages
 of condolence from all over the civil-
 ized globe. They came from those
 who admired him and from those who
 were opposed to his policies. History
 will accord him a place among the
 idealists who gave their all, including
 life itself, to the causes which they un-
 selfishly championed. A great Ameri-
 can is dead.

Radio played its part in the solemn
 event. The naval radio station at Ar-
 lington, Va., flashed the news around
 the world. As it was received, Ameri-
 can vessels upon the seven seas dipped
 the flag in salute and then half-masted
 it in official mourning. Stations WJZ
 and WEA, in New York City, also
 broadcast the sad news. Many other
 stations stayed off the air or revised
 their programs to include tributes to
 Mr. Wilson.

Alleged Radio Monopoly

A CAREFUL study of the com-
 plaint filed by the Federal Trade
 Commission against the Radio Corpora-
 tion of America and its component
 companies, alleging that certain acts and
 practices charged are to the prejudice
 of the public and of the corporation's
 competitors and constitute unfair
 methods of competition in commerce,
 leaves one confused and bewildered.
 The basis of the charges seems to be
 that the respondents have acquired a
 large number of patents, some 2,000,
 and that through these and others
 which they may acquire by purchase
 or by grant, they intend to perpetuate
 their control of the patent situation be-
 yond the life of the patents they now
 own. A patent is a monopoly. The
 government says so when it grants it.
 The patentee is entitled for seventeen
 years to all the benefits he may be able
 to derive from it. The argument of the
 Federal Trade Commission in this in-
 stance would seem to be that when a
 group of companies acquires a group of
 patents the monopolies inherent to each
 of the patents become a menace to the
 public when operated as a group. And
 that naturally might bring up the ques-
 tion "When is a patent not a patent?"

The radio industry is to a greater ex-
 tent than almost any other built upon
 patents. And the Radio Corporation
 of America does not own them all by
 any means. Could the commission's
 reasoning be applied to a manufactur-
 ing company owning a little group of
 ten or twelve patents which gave it an
 absolute monopoly in its particular line
 of goods?

The Radio Corporation of America
 was formed in 1919 practically at the
 request of the government. A Navy
 Department report recording the orga-
 nization of the corporation says:
 "Probably the most important single
 act affecting the communications of
 the United States, was directly origi-
 nated and fostered by representatives
 of the Navy Department." The new
 corporation acquired the interests of
 all foreign owners in the then existing
 radio stations of any importance.
 Thus was established what Naval
 Communication officers believed to be
 "a 100 per cent. American company
 for the operation of the high powered
 radio stations of this country."

If the allegations of the Federal
 Trade Commission that the respond-
 ents have conspired to create a monop-
 oly in the manufacture, purchase and
 sale of radio devices and apparatus
 can be sustained, then the restraint
 exercised by the Radio Corporation
 of America in the enforcement of
 what it now believes are its rights will
 be a matter for wonder. Few, if any,
 of the millions of receiving sets built
 by amateurs all over the country fail
 to infringe one or more of the patents

controlled by the corporation. In-
 stead of pursuing these infringers in
 the courts, the corporation has, at
 least indirectly, encouraged the wid-
 est possible use of radio by the people.

The Federal Trade Commission is
 not always right, either in its premises
 or in its conclusions, as its record
 clearly shows. According to statistics
 quoted by the New York "Times" it
 has issued 1,062 complaints with the
 result of final action in only 563. The
 courts have reviewed 35 cases and
 found in 23 that the orders of the
 commission were wholly void. Only
 in seven were they valid. On the bal-
 ance of presumptions the respondents
 would stand a three to one chance of
 being right and the commission wrong.
 The commission made a report to Con-
 gress on the respondents' activities in
 the radio industry and expressed no
 adverse opinion. The respondents
 maintain that their intentions were
 made known to the government, that
 for a time a representative of the gov-
 ernment sat on their board of direc-
 tors, that their contractual relations
 are in the public interest rather than
 against it and that they are advised
 that these contracts are legal.

Only when the evidence is heard
 and the courts pass upon the law can
 it be asserted that the respondents are
 in restraint of trade. Now, while the
 radio industry is comparatively young,
 is an excellent time to have this im-
 portant matter resolved. While RADIO
 WORLD holds no brief for any of the
 respondents, especially if it can be
 demonstrated that they are acting in
 restraint of trade and thereby retard-
 ing the progress of what promises to
 be one of the greatest of all industries,
 we are of the opinion that the Federal
 Trade Commission will be unable to
 maintain its allegations in this in-
 stance.


A GAIN we call attention to the fact
 that instructions for the con-
 struction of circuits as published from
 time to time in our columns must be
 followed to the letter. If this is not
 done it is useless to complain that the
 circuit won't work and to bombard
 RADIO WORLD with questions as to
 why it doesn't. Often legitimate
 questions arise even when instructions
 are followed and these we are glad to
 answer.

THE most satisfactory definition
 of man is that credited to Benja-
 min Franklin: "Man is a tool-using
 animal." Although possessing re-
 markable vision this patron saint of
 the electrical arts little dreamed that
 his definition not only included all the
 males of the species but that it would
 apply with especial aptitude, 150 years
 after his death, to the amateur radio
 constructor.

All Kinds of Radio News Pictured Here



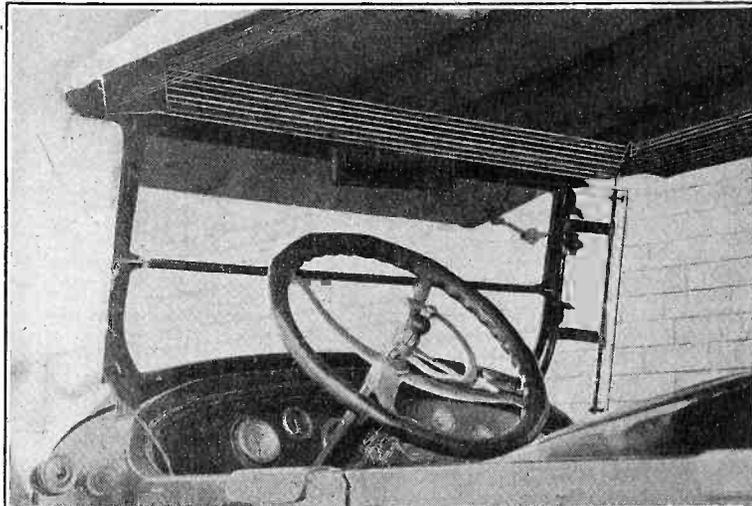
(C. Underwood and Underwood)
 Bevy of English chorus girls rehearsing one of their intricate dance steps at the Selwyn Theatre, N. Y., to the tune of a jazz band broadcasting from WJAZ, Chicago.




The way a radio enthusiast fixed his antenna. It is arranged so that it can form a closed loop or a straight antenna, using the frame of the car as the counterpoise.



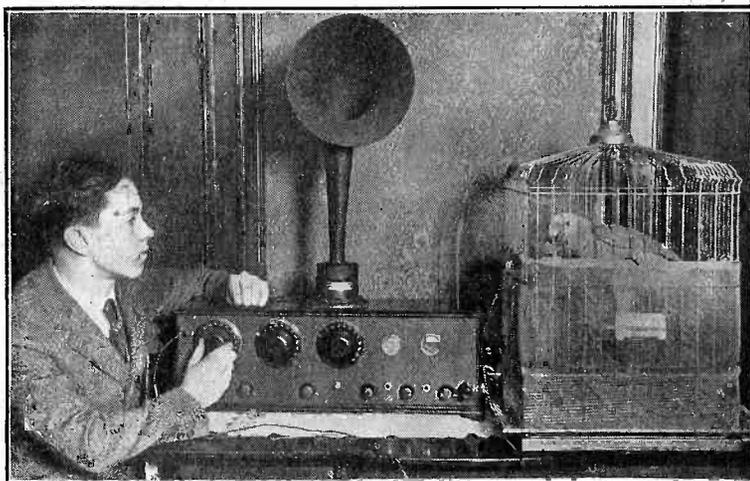
(C. Foto Topics)
 Paul Specht, who broadcasts from the Alamac Hotel, New York City, through WJZ, looking over a day's receipts of manuscripts, sent in at his request. In one week he received over 6,000 pieces.



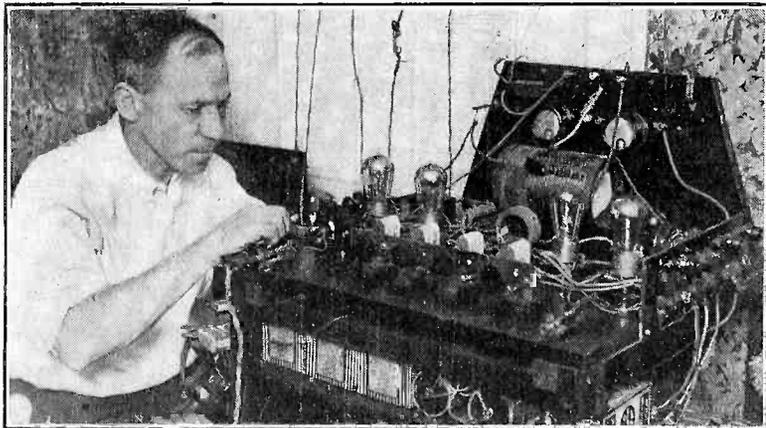
(C. Kadel and Herbert)
 Robert McAfee, New York radio enthusiast, and his pet parrot "Jake," who imitates all the announcers perfectly, and mimics them when they start to broadcast.



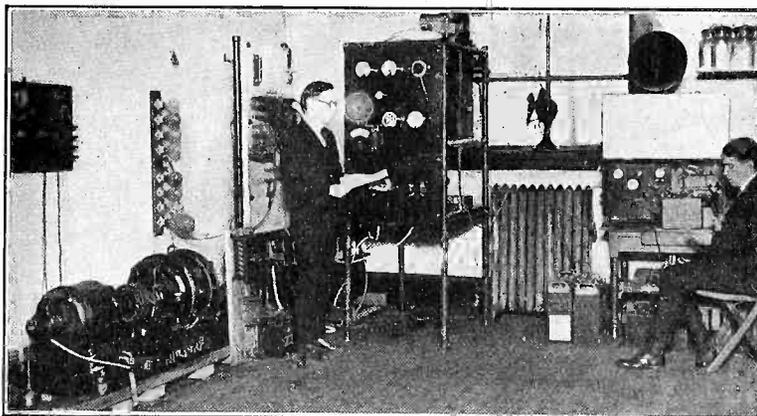
(C. Kadel and Herbert)
 Leo Johnson and his station 2CTQ, which has established some wonderful records. When he gets the best system of modulation he will put it in a cabinet—maybe!



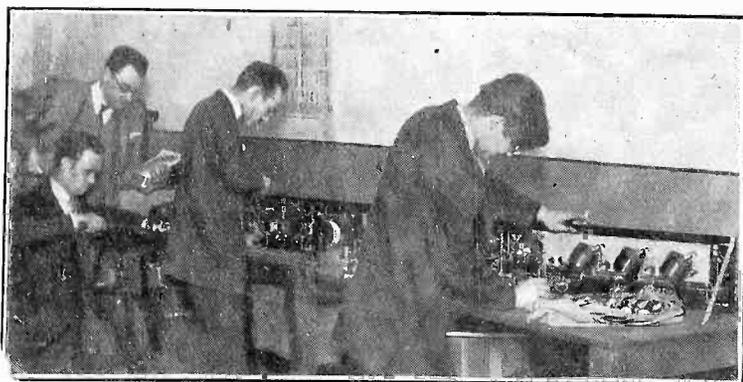(C. Underwood and Underwood)
 The broadcasting station of the University of Illinois, showing the transmitter and controls. Here the students study advanced radio and broadcasting methods.



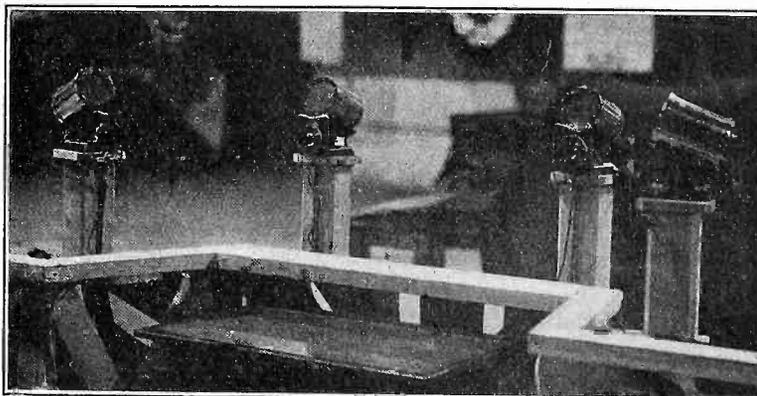(C. Photonews)
 The Radio Association of Greater New York maintains a shop and laboratory where members make and test receivers. A few members snapped on a Saturday afternoon, finishing their work.



Temporary installation of microphones in Montreal through which prominent parliamentary members spoke recently. The talks were broadcast through CKAC, the broadcasting station of "La Presse," Montreal.

Here Are Good Broadcast Programs

Station KDKA, East Pittsburgh, Pa.

326 Meters (920 Kcys.) E. S. T. Feb. 15—9:45 A. M.—Union live stock market reports. 11:55 A. M.—Arlington time signals. 12 M.—Weather forecast. United States Bureau of Market Reports. 12:10 P. M.—Concert by Brody's Orchestra, from the dining room of Kanfmann's, Pittsburg, Pa. 6:15 P. M.—Organ Recital by Lucile Hale, from the Cameo Motion Picture Theater, Pittsburgh, Pa. 7:15 P. M.—Radio Boy Scout meeting conducted by Richard Victor. 7:45 P. M.—The Children's Period. 8 P. M.—Market reports. 8:15 P. M.—"Joshua and the Conquest of Canaan," the Sunday School lesson for February 17, presented by Dr. R. L. Lanning. 8:30 P. M.—Address by S. M. Kintner, Westinghouse Electric & Mfg. Co. 8:45 P. M.—Concert by artists from the LeSueur Studios, assisted by Leo Kruczek, violin. 9:55 P. M.—Arlington time signals; weather forecast.

Feb. 16—9:45 A. M.—Union live stock market reports. 11:55 A. M.—Arlington time signals. 12 M.—Weather forecast. United States Bureau of Market Reports. 1:30 P. M.—Concert by Daugherty's Orchestra from the dining room of McCreey's Company. 6:15 P. M.—Dinner concert by the Westinghouse Band, T. J. Vastine, conductor. 7:30 P. M.—"Bringing the World to America," prepared by "Our World." 7:45 P. M.—The Children's Period. 8 P. M.—Feature. 8:15 P. M.—"Personal Income Tax Returns for Small Incomes," Robert D. Ayers, Assistant Professor of Accounting, University of Pittsburgh. 8:30 P. M.—Concert by the Westinghouse Band, T. J. Vastine, conductor, assisted by "An Unknown Tenor." 9:55 P. M.—Arlington time signals. Weather forecast.

Station WGI, Medford, Mass.

360 Meters (830 Kcys.) E. S. T. Feb. 15—12:00 Noon—Selection on the Ampico in the Chickering; Amrad Round Table; Selections on the Brunswick Console. 12:40 P. M.—New England weather forecast. 12:45 P. M.—Closing report on farmers' produce market. 3:00 P. M.—Amrad Women's Club program; Talk by Miss Dorothy H. Goodwin; Musicals by the Brunswick Console. 3:30 P. M.—Talk by Miss Dorothy Dean, Girl Scouts. 5:30 P. M.—Closing stock market reports; Live stock markets report. 6:15 P. M.—Code practice, lesson No. 234. 6:30 P. M.—Meeting of the Big Brother Amrad Club. 7:00 P. M.—Boston police reports. 7:30 P. M.—Selected verses by Mr. Charles L. H. Wagner, radio poet; Red Cross health talk by Henry Copley Green, "Your Milk Supply"; Musicals. 8:15 P. M.—Reading of Boy Scout Oath.

Feb. 16—6:30 P. M.—Meeting of the Big Brother Amrad Club. 6:45 P. M.—Code practice, lesson No. 235. 7:05 P. M.—New England weather forecast; New England crop notes. 7:30 P. M.—Third of a series of talks on New England Business Industry by Arthur R. Curnick; Arthur Murray's course in Ball Room Dancing; Musicals.

Feb. 17—4:00 P. M.—"Adventure Hour" by the Youth's Companion; Musicals. 8:30 P. M.—Talk on "World Unity," under the auspices of the Greater Boston Federation of Churches; Musicals.

Station WFAA, Dallas, Texas

476 Meters (630 Kcys.) C. S. T. Feb. 15—12:30-1 P. M.—Address, Dr. Robert Stewart Hyer, Southern Methodist University, on the Sunday School lesson, "Joshua and the Conquest of Canaan." 8:30-9:30 P. M.—Musical variety program presenting the orchestra and assisting performers from Kerens, Texas.

Feb. 16—12:30-1 P. M.—Address, Dr. Edward H. Jones, Southern Methodist University, on "The Science of Numbers." 8:30-9:30—Faculty recital by music department of Southern Methodist University. 11-12 P. M.—Dance music, Adolphus Hotel Orchestra, broadcast from the junior ballroom of the hotel.

Feb. 17—6-7 P. M.—Radio Bible Class, Dr. William M. Anderson, Jr., pastor First Presbyterian Church, teacher; half hour of Bible study and half hour of gospel song. 9:30-10 P. M.—Address by the Rt. Rev. Harry T. Moore, bishop of Dallas, American Protestant Episcopal Church, on "Worship and Christianity." 10-11 P. M.—Popular music recital by Jimmy Allen's Serenaders, S. A. E., Fraternity, Southern Methodist University.

Station WRC, Washington, D. C.

469 Meters (640 Kcys.) E. S. T. Feb. 15—5:15 P. M.—Instruction in international code. 6:00 P. M.—Stories for children by Peggy Albion. 6:20 P. M.—"The Question Box." 7:45 P. M.—Bible talk by Homer J. Councilor, chairman of Men's Organized Bible Class Association. 8:00 P. M.—Song recital to be announced. 8:15 P. M.—A talk on the Coast Guard by Oliver M. Maxam, chief of the Division of Operations of the United States Coast Guard. 8:30 P. M.—Piano recital to be announced. 8:45 P. M.—A talk on the Navy by Admiral E. W. Eberle, chief of naval operations. 9:00 P. M.—Concert by the United States Navy Band under the direction of Charles Benter.

Feb. 16—3:00 P. M.—Fashion developments of the moment. 3:10 P. M.—Song recital to be announced. 3:25 P. M.—Current events by the editor of the "Review of Reviews." 3:35 P. M.—Piano recital by Edwina Greene. 4:00 P. M.—The Magazine of Wall Street. 5:15 P. M.—Instruction in international code. 6:00 P. M.—Stories for children by Peggy Albion.

Station WJZ, New York City

455 Meters (660 Kcys.) E. S. T. Feb. 15—12:15 P. M.—Music from the Brick Presbyterian Church. 3:00 P. M.—Organ recital by Leo Riggs on Hotel Astor organ. 5:00 P. M.—"The Larger Aspect of World Affairs" by the International Interpreter. 5:30 P. M.—Closing reports of the New York State Department of Farms and Markets; Farm and Home reports; closing quotations of the New York Stock Exchange; foreign exchange quotations; "The Condition of the Leading Businesses" by the "Magazine of Wall Street"; "Evening Post" news. 7:00 P. M.—MacDowell program, under the auspices of the Music Study Club of Newark. 7:30 P. M.—Burr McIntosh, the Cheerful Philosopher. 7:50 P. M.—MacDowell program, under the auspices of the Music Study Club of Newark. 8:15 P. M.—"Looseleaf" current lege Musical Clubs direct from the Grand Ballroom topics. 8:30 P. M.—Concert by the Amherst College Ritz-Carlton Hotel. 10:30 P. M.—Dance program by Paul Specht and his Alamac Hotel Orchestra, direct from the Congo Room of the Alamac Hotel.

Feb. 16—3:00-3:30 P. M.—Charles Phillips, pianist. 4:00 P. M.—Tea concert by the Hotel Belmont Stringed Ensemble, Harry Lerner, leader; direct from the Balcony of the Tea Room of the Hotel Belmont. 5:00 P. M.—Famous Fain Orchestra. 5:30 P. M.—Closing reports of the New York State Department of Farms and Markets; Farm and Home reports; closing quotations of the New York Stock Exchange; foreign exchange quotations; "Bradstreet's" financial report; "Evening Post" news. 7:00 P. M.—"Uncle Wiggily Stories" by Howard Garis. 8:00 P. M.—"The Asset Value of the Ocean Liner to a Port" by Emerson E. Parvin, secretary of the International Mercantile Marine. 8:40 P. M.—Dr. Alfred N. Goldsmith, director of research of the Radio Corporation of America; "Applying the Golden Rule in Radio"; one of the "Highlights of Modern Radio Broadcasting" series of talks. 9:15 P. M.—"In a Persian Garden" (Quartet), accompanied by Creighton Allen. 9:45 P. M.—Harold Lieberman, violinist, accompanied by C. Allen. 9:55 P. M.—Time signals and weather forecast from Station NAA at Arlington. 10:00 P. M.—Harold Lieberman, violinist, accompanied by C. Allen. 10:20 P. M.—"English Folk Songs," Kenneth K. Wheeler. 10:45 P. M.—Recital by Alphonse Bohrer, pianist, directly from Aeolian Hall.

Feb. 17—11:00 A. M.—1:00 P. M.; 7:00-10:30 P. M.

Station KYW, Chicago, Ill.

536 Meters (560 Kcys.) C. S. T. Feb. 15—9:30 A. M.—Late news and comment of the financial and commercial markets. (This service is broadcast from KYW every half hour during the twenty-four). 11:35 A. M.—Table talk by Mrs. Anna J. Peterson. 12:30 P. M.—"The Progress of the World," by Review of Reviews. 6:30 P. M.—News, financial and final market and sport summary. 6:50 P. M.—Children's bedtime story. 7:7-10 P. M.—Joska DeBabary and his orchestra playing in the Louis XVI room, Congress Hotel. 7:10-7:20 P. M.—Clyde Doerr and his orchestra playing in the Pompeian room. 7:20-7:30 P. M.—Joska DeBabary and his orchestra playing in the Louis XVI room. 10-2 P. M.—Midnight revue, artists and program to be announced.

Feb. 16—9:30 A. M.—Late news and comment of the financial and commercial markets. (This service is broadcast every half hour during the twenty-four). 10:30 A. M.—Farm and home service. 11:35 A. M.—Table talk by Mrs. Anna J. Peterson. 6:30 P. M.—News, financial and final market and sport summary. 6:50 P. M.—Children's bedtime story. 7:7-10 P. M.—Joska DeBabary and his orchestra from the Louis XVI room, Congress Hotel. 7:10-7:20 P. M.—Clyde Doerr and his orchestra from the Pompeian room. 7:20-7:30 P. M.—Joska DeBabary and his orchestra from the Louis XVI room. 8-8:58 P. M.—Musical program. 9:05 P. M.—"Under the Evening Lamp." 10-12 P. M.—Midnight revue to be broadcast from the KYW studio in the Congress Hotel.

Feb. 17—11 A. M.—Central Church Service, Orchestra Hall, Chicago, Dr. F. F. Shannon, pastor. 6:30 P. M.—Excerpts from the New Testament—An American Translation by Prof. Edgar J. Goodspeed, read by William Ziegler Nourse. 7 P. M.—Chicago Sunday Evening Club service from Orchestra Hall, Chicago. Speaker, Hon. Frank O. Lowden.

Station WBZ, Springfield, Mass.

337 Meters (890 Kcys.) E. S. T. Feb. 15—11:55 A. M.—Arlington time signals; weather reports; Boston and Springfield market reports. 6 P. M.—Dinner concert by the WBZ Quintet. 7 P. M.—"A Tale of the Poplar," a dramatized story by the Youth's Companion. Talk by Herbert Myrick, Editor of Farm and Home, a Mrs. Mary R. Reynolds, Household Editor of Farm and Home. 7:30 P. M.—Bedtime story for the kiddies. Current book review by H. A. MacDonald. Story for grown-ups by Orison S. Marden. 9:55 P. M.—Arlington time signals.

Feb. 16—11:55 A. M.—Arlington time signals; weather reports; Boston market report. 7 P. M.—Dinner concert by the Hotel Kimball Trio transmitted from the Hotel Kimball Dining Room Jan Geerts, director. 7:30 P. M.—Bedtime story for the kiddies. "Bringing the World to America," prepared by "Our World" Magazine. 8 P. M.—Concert by Harry Knight, saxophone and clarinet. 9 P. M.—Bedtime story for grown-ups by Orison S. Marden. 9:55 P. M.—Arlington time signals.

Station WFAF, New York City

492 Meters (610 Kcys.) E. S. T. Feb. 15—11:00 A. M.—Lecture by Dr. Walter Damrosch, conductor of the New York Symphony Orchestra, under the auspices of the League for Political Education, direct from Town Hall, New York City. 11:50 A. M.—Consolidated market and weather reports by the U. S. and N. Y. State Departments of Agriculture. 4:00-5:30 P. M.—Marguerite Eckenroth, soprano, accompanied by Katherine Eckenroth. Recital by "The Banjo Trio." Children's Hour Stories and Songs. 7:15-10:00 P. M.—Beatrice Lilly and Jack Buchanan, singing comedians. Daily sport talk by Thornton Fisher; Ted Schmidt and Harry Regan, popular singers; Battery instruction talk by George Furness, radio head of the National Carbon Company. "The Happiness Boys" Billy Jones and Ernest Hare; Music by the World Mutual Instrumental Trio, and a talk on the "Care and Safe Operation of Automobiles" by Major A. A. Stewart. B. Fischer & Company's "Astor Coffee" Dance Orchestra.

Feb. 16—1:45-3:30 P. M.—Foreign Policy Association luncheon direct from Hotel Astor, New York City. 4:00-5:30 P. M.—Dance program by the Carolinians Orchestra, Charles M. Koch, director; Helen Albus, dramatic soprano. 7:30-12:00 P. M.—W. C. Fields, comedian monologist; David Franklin, pianist, and Tom Butler, baritone; "The Chiclet Trio" assisted by the "Chiclet Quartette"; Myra Purts Bindenberger, contralto, accompanied by George Vause. Recital by George Vause, pianist; Bernard Ahrens, baritone. Gimbel Brothers' program. Vincent Lopez and his orchestra direct from the Grill of the Hotel Pennsylvania.

Station KFI, Los Angeles, Cal.

469 Meters (640 Kcys.) P. T. Feb. 17—10:00-10:45 A. M.—L. A. Church Federation Service. 4:00-5:00 P. M.—Federated Church Musicians Vesper Service. 6:45-7:30 P. M.—Bedtime story and concert. 8:00-9:00 P. M.—Ambassador Hotel concert. 9:00-10:00 P. M.—Examiner concert. 10:00-11:00 P. M.—Theron Bennett's Packard Six.

Feb. 18—4:45-5:15 P. M.—Evening Herald news bulletin. 5:15-5:45 P. M.—Examiner news bulletins. 8:00-9:00 P. M.—Evening Herald concert. 9:00-10:00 P. M.—Examiner concert. 10:00-11:00 P. M.—Ambassador-Lyman's Coconut Grove Orchestra.

Feb. 19—4:45-5:15 P. M.—Evening Herald news bulletins. 5:15-5:45 P. M.—Examiner news bulletins. 6:45-7:30 P. M.—Geo. J. Birkel concert. 8:00-9:00 P. M.—Ambassador-Lyman's Coconut Grove Orchestra. 9:00-10:00 P. M.—Examiner concert. 10:00-11:00 P. M.—Sol Cohen and associates.

Feb. 20—4:45-5:15 P. M.—Evening Herald news bulletins. 5:15-5:45 P. M.—Examiner news bulletins. 6:45-7:30 P. M.—Nick Harris detective stories and concert. 8:00-9:00 P. M.—Evening Herald concert. 9:00-10:00 P. M.—Examiner concert. 10:00-11:00 P. M.—Hollywood Community Orchestra. 11:00-12:00 P. M.—Ambassador-Lyman's Coconut Grove Orchestra.

Feb. 21—4:45-5:15 P. M.—Evening Herald news bulletins. 5:15-5:45 P. M.—Examiner news bulletins. 6:45-7:30 P. M.—Y. M. C. A. concert and bedtime story. 8:00-9:00 P. M.—Ambassador Hotel concert. 9:00-10:00 P. M.—Examiner concert. 10:00-11:00 P. M.—Mrs. William Barber concert.

Station WOR, Newark, N. J.

405 Meters (740 Kcys.) E. S. T. Feb. 15—2:30 P. M.—Musical program by the combined musical clubs of Lafayette College of Easton, Pa. 6:15 P. M.—"Music While You Dine," Ben Friedman Entertainers, augmented by George Perry's Singing Orchestra. 6:30 P. M.—"Man in the Moon Stories for the Children." 7-7:30 P. M.—"Music While You Dine," by Ben Friedman Entertainers, augmented by George Perry's Singing Orchestra.

Feb. 16—Between 2:30 and 4:00 P. M.—Broadcasting from Radio Exposition, 6th floor, L. Bamberger & Co. 2:30 P. M.—Frank Dailey's Meadowbrook Dance Orchestra. 3:10 P. M.—Baroness Leja de Torinoff, on "The Russian Revolution from a Woman's Viewpoint." Followed by Russian Folk Songs. 3:30 P. M.—Frank Dailey's Meadowbrook Dance Orchestra. 6:15-7:15 P. M.—"Music While You Dine," Paul Van Loan and his Cinderella Dance Orchestra of New York. 7:15 P. M.—Fred J. Bendel, on "Sporting News-Uu-to-the-Minute." 8:00-9:00 P. M.—Gene Ingraham and his Bell Record Orchestra. 9:00 P. M.—"The Law and Income Tax," by John Armstrong, C. P. A. 9:15 P. M.—J. Bernard Walker, Editor Scientific American, on "What America Owes Europe." 9:45 P. M.—Joint program by Mary Dell Downman, Lorraine Boardman and International Trio.

Station WOS, Jefferson City, Mo.

441 Meters (680 Kcys.) C. S. T. Feb. 15—8:00 P. M.—Program by the students of the Missouri Military Academy, Mexico, Missouri.

Feb. 17—7:30 P. M.—Services of the First Christian Church, Jefferson City, Robert M. Talbert, pastor. Professor Siebert Price, organist. Robed choir of twenty-four voices. Mrs. Fred Reagle, violinist.

Feb. 18—8:00 P. M.—Dance program by the Missouri State Prison Dance Orchestra, Hugh C. French, director. Piano numbers by Harry M. Snodgrass.

Feb. 20—8:00 P. M.—Address on agricultural topic by a faculty member of the Missouri College of Agriculture. 8:20 P. M.—Dance program by S. C. Stancil's Novelty Six Dance Orchestra.

Station WHAS, Louisville, Ky.

400 Meters (750 Kcys.).—C. S. T. Feb. 15.—4:00 to 5:00 P. M.—Selections by the Walnut Theatre Orchestra; Walter Davison, conductor; police bulletins; weather forecast; "Just Among Home Folks," a daily humorous column appearing in the "Courier-Journal"; selections by the Strand Theatre Orchestra; Harry S. Currie, conductor; late important news bulletins. 4:50 P. M.—Local live stock, produce and grain market reports. 5:00 P. M.—Official Central Standard time announced. 7:30 to 9:00 P. M.—Concert, visiting students of Louisville Conservatory of Music, who will sing especially to their own home towns, under the direction of Miss Laura Butler, Marion, Ky.; late important news bulletins; official Central Standard time announced.

Feb. 16.—4:00 to 5:00 P. M.—Selections by the Strand Theatre Orchestra; Harry S. Currie, conductor; police bulletins; weather forecast; old-fashioned fiddler, Charles Elder, accompanied by Miss Sue Elder; "Just Among Home Folks," a daily humorous column appearing in the "Courier-Journal"; selections by the Walnut Theatre Orchestra; Walter Davison, conductor; late important news bulletins. 4:50 P. M.—Local live stock, produce and grain market reports. 5:00 P. M.—Official Central Standard time announced. 7:30 to 9:00 P. M.—Concert by the Delta Omicron Sorority of the Louisville Conservatory of Music, under the direction of Miss Elizabeth Shelton, president; late important news bulletins; official Central Standard time announced at 9 o'clock.

Station WOC, Davenport, Iowa

484 Meters (620 Kcys.). C. S. T. Feb. 15.—10 A. M.—Opening market quotations and household hints. 10:55 A. M.—Time signals. 11 A. M.—Weather and river forecast. 11:05 A. M.—Market quotations. 12 M.—Chimes concert. 2 P. M.—Closing stocks and markets. 3:30 P. M.—Lecture by R. G. Maybach, P. S. C. Dept. of Anatomy, "The Teeth, Their Function and Care." 5:45 P. M.—Chimes concert. 6:30 P. M.—Sandman's Visit. 6:50 P. M.—Sport news and weather forecast. 7:20 P. M.—International lesson for next Sunday discussed by Dr. Frank Willard Court, pastor St. John's Methodist Episcopal Church, Davenport, Iowa. 8 P. M.—Musical program, Erwin Swindell, musical director. Program under the auspices of the Scott County Farm Bureau. Feb. 16.—10 A. M.—Opening market quotations and household hints. 10:55 A. M.—Time signals. 11 A. M.—Weather and river forecast. 11:05 A. M.—Market quotations. 12 M.—Chimes concert. 12:30 P. M.—Closing stocks and markets. 3:30 P. M.—Lecture by C. C. Hall, P. S. C. Dept. of Chemistry, "Preparation and Uses of Rubber." 5:45 P. M.—Chimes concert. 6:30 P. M.—Sandman's visit. 6:50 P. M.—Sport news and weather forecast. 7 P. M.—"Our National Guard," by Lieut. Ralph A. Lancaster, Iowa National Guard. 9 P. M.—P. S. C. Orchestra, Gerald M. Barrow, director. (Popular selections released through the National Association of Broadcasters, of which WOC is a member.) V. B. Rochte, baritone soloist.

Station WDAR, Philadelphia

395 Meters (760 Kcys.). E. S. T. Feb. 15.—11:45 A. M.—Daily almanac. 12:02 P. M.—Organ recital from the Stanley Theatre features from the studio; Arcadia Concert Orchestra, Fery Sarkozi, director. 2:00 to 3:00 P. M.—Arcadia Concert Orchestra; Artist recital. 4:30 P. M.—Program of dance music by the Scranton Sirens. 7:30 P. M.—Dream Daddy with the Boys and Girls. 7:50 P. M.—An Evening with Betsy Logan. 10:10 P. M.—Howard Lanin's Dance Orchestra; Artie Bittong's Elk Frolic; Harry Glynn and others. Feb. 16.—11:45 A. M.—Daily almanac. 12:02 P. M.—Organ recital from the Stanley Theatre. features from the studio; Arcadia Concert Orchestra. 2:00 to 3:00 P. M.—Arcadia Concert Orchestra; Artist recital; 4:30 P. M.—Bobbie Lee and his Cotton Pickers. 7:30 P. M.—Dream Daddy with Boys and Girls.

Station KGO, Oakland, Cal.

312 Meters (960 Kcys.). P. T. Feb. 14—8 P. M.—Musical program. Feb. 16—8 P. M.—Musical program.

Station KHJ, Los Angeles, Calif.

395 Meters (760 Kcys.). P. T. Feb. 15.—12:30 to 1:15 P. M.—Music; news items. 2:30 to 3:30 P. M.—Matinee musicale. 6:40 P. M.—Live stock and vegetable reports. 6:45 to 7:00 P. M.—Children's program presenting Richard Headrick; screen juvenile. Bedtime story by "Uncle John." 8:00 to 10:00 P. M.—Program arranged by Floryane Thompson, soprano. "An Evening of Old Fashioned Songs." 10:00 to 12:00 P. M.—Broadcasting Art Hickman's Orchestra by line telephony from the Los Angeles Biltmore Hotel.

Feb. 16.—12:30 to 1:15 P. M.—Program presented by the Rainbow Melody Makers. 2:30 to 3:30 P. M.—Matinee musicale. 6:40 P. M.—Live stock and vegetable reports. 6:45 to 7:30 P. M.—Children's program presenting Helene Pirie, screen juvenile, and John M. Trimbur, flutist. Bedtime story by "Uncle John." 8:00 to 10:00 P. M.—Program presented by the Los Angeles Federation of P. T. A. N. E. Brown, Electrical Engineer, will speak. 10:00 to 12:00 P. M.—Broadcasting Art Hickman's Orchestra by line telephony from the Los Angeles Hotel.

Station WGY, Schenectady, N. Y.

380 Meters (790 Kcys.). E. S. T. Feb. 15.—11:55 A. M.—Time signals. 12:30 P. M.—Stock market report. 12:40 P. M.—Produce market report. 12:45 P. M.—Weather forecast. 2 P. M.—Music and fashion talk. "Dress Accessories," Ralph L. Smith. 6 P. M.—Produce and stock market quotations; news bulletins. 6:30 P. M.—Children's program. 7:35 P. M.—Health talk, N. Y. State Department of Health. 7:45 P. M.—Radio drama, comedy, "Anne," by WGY players. Instrumental selection, WGY Orchestra. 10:30 P. M.—Musical program.

Feb. 16.—11:55 A. M.—U. S. Naval Observatory time signals. 12:30 P. M.—Stock market report. 12:40 P. M.—Produce market report. 9:30 P. M.—Dance music by Jack Symonds' Orchestra, Hampton Hotel, Albany, N. Y.

Station WLW, Cincinnati, Ohio

309 Meters (970 Kcys.) C. S. T. Feb. 15.—10:30 A. M.—Weather forecast and business reports. 1:30 P. M.—Market reports. 3:00 P. M.—Stock quotations. 4:00 P. M.—Half hour lecture recital. Feb. 16.—10:30 A. M.—Weather forecast and business reports. 1:30 P. M.—Business reports. Feb. 17.—9:30 A. M.—Sunday school conducted by the Editorial Staff of Sunday School Publication of the Methodist Book Concern. 11A. M.—Services of the Church of the Covenant, Dr. Frank Stevenson, minister. 7:45 P. M.—Services of the First Presbyterian Church, Walnut Hills, Cincinnati.

Station KPO, San Francisco, Cal.

423 Meters (770 Kcys.) P. T. Feb. 14.—6:00-7:00 P. M.—Dinner concert by George Lipschultz and Music Masters from the Loew's Warfield Theatre. 8:00-9:00 P. M.—Theodore J. Irwin at the console of the Robert Norton organ. 9:00-10:00 P. M.—Program by the San Lorenzo Improvement Association. 10:00-11:00 P. M.—Palace Hotel Dance Orchestra. Feb. 15.—Silent. Feb. 16.—Art Weidner and the Fairmont Hotel Dance Orchestra. 8:00-12:00 P. M.—During intermissions the KPO Trio will sing popular songs.

Station WJY, New York City

405 Meters (740 Kcys.) E. S. T. Feb. 15.—7:30 P. M.—Frank Shevitt, "Income Taxes." 7:45 P. M.—Program by the Brooklyn Edison Orchestra. 8:15 P. M.—The Honorable Julius Berg, "The Work of the New York Assembly." 8:30 P. M.—Program by the Brooklyn Edison Orchestra. 9:00 P. M.—"Father & Son." 9:30 P. M.—General Chas. H. Sherrill. 10:00 P. M.—Popular program by Breaud and Tobias.

Station KSD, St. Louis, Mo.

546 Meters (550 Kcys.). C. S. T. Feb. 14.—8 P. M.—Program by Glee Club of Shurtleff College, Mrs. D. Jones, director. Feb. 15—8 P. M.—Concert by the Civic Orchestra, Ellis Levy, conductor, at Central High School. Feb. 16—Silent.

MAGNAVOX Radio Products



A1-R—\$59.00

THIS combination of electro-dynamic Reproducer and one-stage Power Amplifier gives the user the utmost in adaptability, convenience and efficiency.

Magnavox Reproducers

- R2 with 18-inch curvex horn \$60.00
- R3 with 14-inch curvex horn \$35.00
- M1 with 14-in. curvex horn. Requires no battery for the field \$35.00

Magnavox Combination Sets

- A1-R consisting of electro-dynamic Reproducer with 14-inch curvex horn and 1 stage of amplification \$59.00
- A2-R consisting of electro-dynamic Reproducer with 14-inch curvex horn and 2 stages of amplification \$85.00

Magnavox Power Amplifiers

- A1—new 1-stage Power Amplifier \$27.50
- AC-2-C—2-stage Power Amplifier \$55.00
- AC-3-C—3-stage Power Amplifier \$75.00

Magnavox products can be had at Registered Magnavox Dealers everywhere. Write for new 32-page catalogue.

The Magnavox Company
Oakland, California

New York Office: 370 Seventh Avenue
Canadian Distributors
Perkins Electric, Limited, Montreal

Who Is America's Most Popular Radio Entertainer?

Everybody is interested in this query: Who is America's most popular radio entertainer? You have your favorite. Who is she or he? Let us know your choice, whether a comedian, an opera singer, a jazz band, or a story-teller.

RADIO WORLD wants to be able to tell the world the name of the entertainer who stands highest in the regard of listeners-in.

Use the accompanying blank and mail to Broadcasting Manager, RADIO WORLD. Cut off. Fill out. Mail today.

BROADCASTING MANAGER, RADIO WORLD,
1493 Broadway, New York City.

Dear Sir:

My favorite entertainer is.....Station.....

My second choice is.....

Name.....

Street Address.....

City and State.....


Latest Radio Patents

Method of Delivering Illustrated Lectures or Songs

No. 1,478,806: Patented December 25, 1923. Patentee: A. F. Victor, New York City.

My invention relates to the method of delivering illustrated lectures or songs by means of wireless telephony.

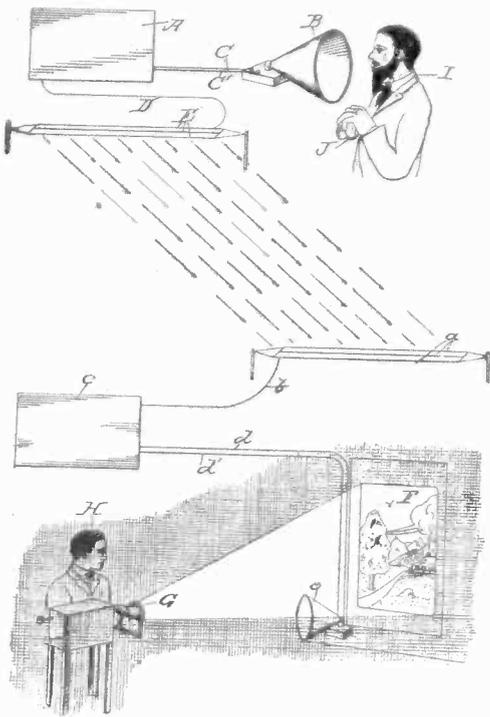The object of my invention is to project radiogram lectures or songs or anything else, to audiences or persons having wireless receiving stations, and to illustrate the same by pictures projected upon a screen



Method of utilizing radio telephony so a speaker may give illustrated lectures at a distance from the place they are being shown. It is also applicable to give the same lecture at two or more places.

at the place where the lecture is presented. This I accomplish by the means hereinafter fully described and as particularly pointed out in the claims.

The drawing illustrates a diagrammatical layout of the invention.

In the drawings A represents a transmit-

ting apparatus that has a receiving horn B, of the usual construction, that is attached thereto by wires C, C' and this transmitting apparatus A is connected by wires D to a wireless transmitting set of wires E.

At the receiving end of the invention, there is a receiving set of wires a, that is connected by a wire b to the receiving apparatus c, and this receiving apparatus, c, is connected by wires d and d' to the horn or amplifier e.

At the receiving end of the method, preferably in the same room as the amplifier e, there is a stereopticon screen F, upon which pictures are projected from a stereopticon G by the operator H, during the lecture, that is being delivered by a lecturer, I, into horn B.

The lecturer, I, has a castanet J in his hand, and when he desires the picture changed he simply claps the castanets together, and thus signals the operator for a change. Of course the lecturer could snap his fingers, or could speak his desire for a change. Any means that made a sound that would convey a signal could be satisfactorily employed.

The sound transmitted is preferably of a different timbre from vocal sounds so that the same will not be noticed by the audience, or if heard, will be taken to be interference that is common particularly from signals in code or the like.

It will be understood that, before the lecture, the slides to be displayed by the stereopticon, could be collected and arranged in the order in which they are to be used at a school, or a church, or at home, or other auditorium, where the lecture is to be presented to an audience.

The foregoing method can be used by any number of receiving stations at the same time, and, could be received by radio stations that were not supplied with the picture apparatus. Such lectures, however, would be enjoyed by audiences to a much less extent, than when illustrated by pictures.

It will be understood that where I refer to lectures I intend to include therein songs, or anything else that can be used by my invention.

Electric Oscillator

No. 1,478,638: Patented December 25, 1923. Patentee: H. G. Cordes, Bremerton, Wash.

My invention relates to improvements in arrangements for starting, sustaining, utilizing and studying a particular class of oscillations of a direct current arc oscillator. As to common subject-matter this application is a continuation in part of application 43,436.

The object of my invention is to attain greater efficiency in converting direct current into oscillating current energy, to permit the efficient use of a lower potential direct current in a radio transmitter, to secure greater stability of the apparatus, to adapt an arc oscillator to the production of variable frequency oscillations for radio telephony and to efficiently transform the potential of direct current energy by means of oscillating current.

These improvements are attained by applying a principle well known in the production of oscillations in mechanical devices to the production of electrical oscillations.


My invention can be best explained by considering the direct current arc oscilla-

tor as the basis of my improvements. My improvements pertain to class 2 oscillations which are defined by the committee on standardization for 1915 of the Institute of Radio Engineers as those oscillations in which the amplitude of the oscillation circuit current is at least equal to the direct current, but in which the direction of the current through the arc is never reversed. In other words, in this class of oscillations the arc acts as an electric check valve.

A class 2 oscillation involves three circuits and two time intervals. The circuits will be referred to as the direct current charging circuit, the direct current arc circuit and the discharge circuit. The time intervals will be referred to as the primed and unprimed intervals. During the primed interval current flows through the arc and during the unprimed interval no current flows through the arc. The direct current arc and discharge circuits are only closed during the primed interval. With the usual large inductance in series with the direct current source the direct current amplitude varies a little and consists of an oscillating current of comparatively small amplitude superposed upon a direct current. The discharge cir-

cuit consists of a capacitance discharging through an inductance; the inductance may be either in series with the arc or in series with the capacitance across the direct current line.

The potential of the capacitance varies practically as a linear function of the time during the unprimed interval or period while the potential varies as a sinusoidal function of the time during the primed period of each cycle. Similarly, the graph of the current is also a straight line and a damped sine wave. Oscillations having the characteristics above described will be referred to by the general term "linear-sinusoidal oscillations."

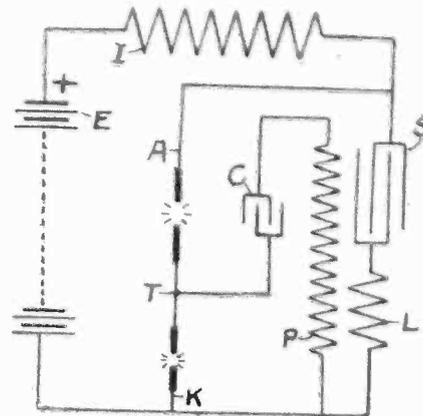

Means and apparatus used to produce sustained oscillations in a circuit.

During the primed period electromagnetic energy is stored in the direct current arc-circuit inductance while during the unprimed period the discharge circuit capacitance is charged simultaneously with the discharge of this energy and the energy due to the flow of direct current during the unprimed period.


Radio Receiving Sets

No. 1,477,413: Patented December 11, 1923. Patentee: E. F. W. Alexanderson, Schenectady, N. Y.

My present invention relates to radio receiving systems, and more particularly to means for preventing interference in such systems with the reception of desired signals.

The object of my invention is to provide in a radio receiving system a means for preventing interference with the reception of desired signals from a near-by transmitting station having a different wave length.

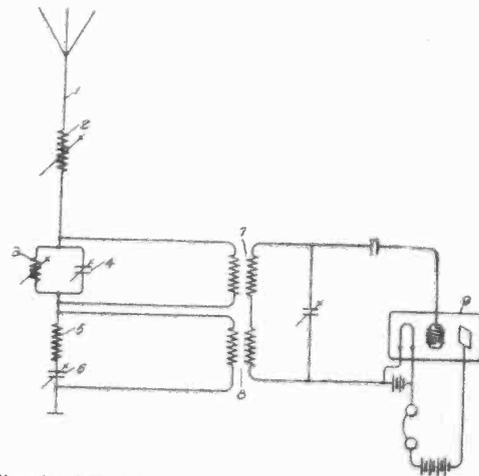In carrying my invention into effect I provide in connection with a receiving antenna means for impressing upon the receiving circuit two equal and opposing potentials produced in the antenna by



Circuit for the prevention of interference by means of double tuned inductances.

the interfering wave. This means is so arranged that it will also impress upon the receiving circuit two potentials produced by the desired signaling waves, but these two potentials will be of different magnitude and of the same phase or will have such phase relation to each other that they will add in the receiving circuit and will not neutralize one another.

Complete Receiving Set—\$8.50

Panel mounted crystal sets in mahogany finished cabinet. Variable condenser used for tuning, very sensitive and efficient due to the special crystals used in detector. Comes to you complete with one 2,000 ohm double headset, aerial and ground wires, insulators, lead-in wires, etc. Send Money Order or check for \$8.50 at once.

Money back if not satisfied.

FLOYD HILL, LIBERTYVILLE, IOWA

For Maximum Amplification Without Distortion and Tube Noises use the well known

Como Duplex Transformers

Push-Pull
Send for literature

COMO APPARATUS COMPANY

446 Tremont St. Boston, Mass.

GUARANTEED Dry B Batteries


Shipment prepaid at the following prices direct to consumer:

	large	medium	small
22½ volt variable.....	\$1.55	\$1.25	\$0.80
45 volt variable.....	2.85	2.55	

Guaranteed money back if you're not satisfied.

Sidbenel Radio—Premium Dept.
25 W. Mt. Eden Avenue New York City

DOUBLE THE LIFE AT HALF THE COST

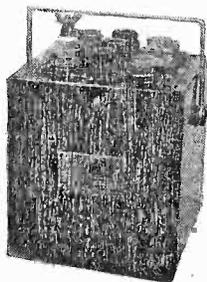

Arrow Radio Batteries

are guaranteed two years in writing.

Will ship C. O. D. or allow 5% discount for cash with order. Order shipped same day received. Write today.

We specialize in Storage Batteries only.

Arrow Battery Co.
8 St. Clara Place
New York City

6 V., 60 amps.	\$8.50
6 V., 80 amps.	10.00
6 V., 100 amps.	12.50

Hovey First with News of Wilson's Death

EDITOR, RADIO WORLD: I am wondering how many radiophans made the most of their opportunities today. At 10:32 this morning I received a radiogram saying "Former President Wilson passed away at 10:27." At 10:35 (although in working clothes) I was at the pulpit of the nearest church, and the announcement was made. Three minutes later I was in the pulpit of another church with the announcement, and I followed at the same speed until every church in the city was visited. Although in each case services were in progress, I felt justified in intruding, and in each case was heartily thanked by the pastor.

The sad news was thus given to our people just 19 hours ahead of the daily papers which will reach here tomorrow morning.

They are talking radio in this town today all right. I might add, too, that for the past 48 hours I have worked and slept within six feet of a set all tuned in and lit up, ready to hear the first announcement of the death of this great and good man.

If you know of a radiophan in this entire country who goes to it stronger than I do I want to see what he looks like. I am still going on 70 years young and then some.

O. H. Hovey.

Perry, Oklahoma, Feb. 3, 1924.

RADIO FANS

Would you like to get a start as salesman or dealer in the Radio Field? We manufacture one of the best receiving sets and parts on the market. We want local representatives in your district. We show you how to get started in the radio business. If you are familiar with radio you can earn a big income immediately. This is open to part time men.

Write to MR. GAY

4684 North Clark Street Chicago, Ill.

MORRISON STANDARD RADIO SUPPLIES

Wholesale Only
Kellogg Switchboard & Supply Co.
Bristol Audiophones
Gilfillan Bros.
Morrison B Batteries
Panelyta
Valley Chargers
Franco Chargers
CLARENCE E. MORRISON
2 STONE STREET NEW YORK CITY

PATENTS Domestic and Foreign, Trade Marks and Copyrights, Infringement Suits and Interference Cases.

Booklet "More Light on Patents" Sent Free

MAX D. ORDMANN

Reg. Pat. Lawyer
Mech. and Elect. Engineer


Specializing in Radio
1808 Woolworth Bldg., N.Y. City Tel. Whitehall 7640-4

Coast to Coast on One Tube and No Body Capacity

These popular hook-ups use UV-199, WD-11 or WD-12 Tubes. One hook-up gives selectivity and 1,500 miles with absolutely no body capacity, while the other gives the remarkable distance of coast to coast. Both prints postpaid for 50 cents or any of the above tubes postpaid \$4.95. No stamps accepted.

Radio Outfitting & Supply Co.
Box 1107 LANCASTER, PA.

18 times more

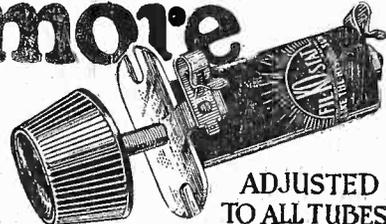

ADJUSTED TO ALL TUBES

FILKO-STAT has a fine adjustment area many times greater than any other rheostat. It is the only rheostat assuring minute control over the maximum audibility range of the vacuum tube; bringing in DX stations you never heard before and eliminating tube noises.

30 ohms full resistance.
No adjustment to puzzle.
No discs to break.
No Carbon Powder.



FILKO-STAT

Made and Guaranteed by
DX Instrument Co. Harrisburg, Pa.
Radio Stores Corp., 218 W. 34th St., New York
Sole International Distributors

If you see it in RADIO WORLD you know it's so. If you hear about it somewhere else, you can find it in last month's issues of RADIO WORLD. Start keeping that file now

RADIO BY MAIL

- UV200, UV201A, UV199, WD11, WD12
- GENUINE RCA RADIOTRON TUBES.....\$4.24
- "ACME" AUDIO & RADIO TRANSFORMERS 3.94
- "ERLA" AUDIO & REFLEX TRANSFORMERS 3.89
- "COMO" PUSH-PULL TRANSFORMERS (PR) 9.38
- ALL AMER. TRANS. (ALL RATIOS)..... 9.87
- 2 Amp. BATTERY CHARGER WITH "TUNGAR" BULB..... \$9.38
- \$6.00 BRANDES "SUPERIOR" PHONES..... 4.69
- \$10.00 BRANDES "TABLE TALKER"..... 8.29
- \$5.00 BREMER-TULLY "VER. TUNER"..... 3.94
- WORK-RITE NEUTRODYNE TRANS..... 4.76
- \$3.00 SIZE 22½-VOLT "B" BATTERY..... 1.49
- \$5.50 SIZE 45-VOLT "B" BATTERY..... 3.19

VARIABLE CONDENSERS

- 11-PLATE..\$0.94 VERNIER WITH DIAL..\$1.89
- 23-PLATE.. 1.19 VERNIER WITH DIAL.. 2.19
- 43-PLATE.. 1.34 VERNIER WITH DIAL.. 2.49
- \$25.00 SET "FADA" NEUTRODYNE PARTS.. 19.95
- \$65.00 SET "FADA" NEUTRODYNE PARTS.. 51.95
- 6E "TUNGAR" 2-AMP. BAT. CHARGER 15.69

Cash or C. O. D. Send for Complete List.

SIMPLEX RADIO COMPANY
1806 Lafayette Avenue St. Louis, Mo.

SPECIAL \$ SAVERS

Satisfaction or money back

- \$65.00 Set "Fada" Neutrodyne parts.....\$48.85
- 25.00 Set "Fada" Neutrodyne parts..... 19.65
- 4.50 Thorndarson Transf. 3½-1 (new type)..... 2.95
- 6.00 Supertran Transf. 6-1..... 3.95
- 12.00 "All American" Push Pull (per set)..... 9.77
- 3.00 Set of Reflex Coils..... 2.15
- 3.50 23 Plate "Signal" Cond..... 1.95
- 4.50 43 Plate "Signal" Cond..... 2.25
- 2.00 Filkostats..... 1.65
- 2.00 Spring Aerial..... 1.48
- 5.00 Turney 3000 ohm Phones..... 2.85
- 6.00 Brandes Superior..... 4.45
- 12.00 Baldwin Type C Phones..... 7.90
- 6.00 Little Tattler Phones..... 2.69
- 10.00 Brandes Table Talker..... 8.65
- 18.50 Tungar or Rectigon Charger..... 14.95
- 20.00 Crosley V..... 14.75
- 20.00 Crosley Two Stage Amplifier..... 14.75


Everything guaranteed as firsts. Don't delay getting price list No. 9.
RADIO SUPPLY STORES
254 W. Stiegel St., Manheim, Pa.

The Marvel - Switch

THREE-WAYS

Series, Parallel, Direct-Ground

Dial-Mounted

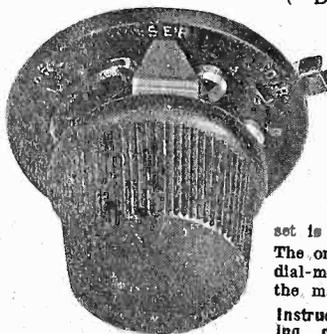

Strictly anti-capacity. Without a switching arrangement for changing from one wave length to another, your set is inefficient.

The only three-way and dial-mounted switch in the market.

Instructions for mounting given with each instrument.


List Price \$1.25

Attractive discounts for dealers and jobbers. Write for descriptive circular.

IF YOUR DEALER CANNOT SUPPLY YOU, SEND PURCHASE PRICE TO
MARVEL-SWITCH COMPANY
28 WEST 25TH STREET NEW YORK

GET A REAL "B" BATTERY!

Powerful—Durable—Rechargeable

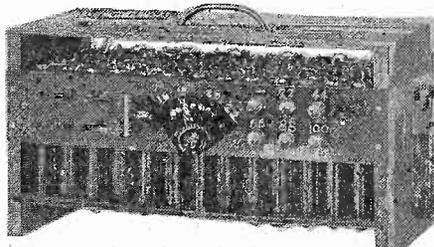

A swing of the switch lever gives instant voltage.

BATTERY SATISFACTION AT LAST. Hundreds of enthusiastic owners of Roberts "B" Batteries tell us: "Positively the best battery on the market—I have tried them all." "All my battery troubles are over!" "Not only a wonderful battery, but handsome, also." "The best investment I ever made!" "Now, I get real radio enjoyment!"

W. ROBERTS STORAGE "B" BATTERY COMPANY

1120 MYRTLE AVENUE, NEAR BROADWAY, BROOKLYN, N. Y.

Telephone Bushwick 6753

Batteries can be obtained from the following dealers: Brooklyn Radio Service, 573 Myrtle Avenue; Smith and Livingston Streets, Brooklyn; 17 John Street, New York City. Brooklyn Radio Supply, Broadway and Reid Avenue, Brooklyn. Romcho Storage Battery, 146 West 68th Street, New York City. Conroy Storage Battery Co., 147 East 76th Street. Stephan Radio, 6 Nassau Street, Roosevelt, L. I. Autoelectric Storage Battery & Supply Co., 201 Paterson Street, Paterson, N. J. DEALERS WRITE FOR TERMS.

Roberts Rechargeable "B" Battery
LASTS A LIFETIME
MADE OF EDISON ELEMENTS
SATISFACTION GUARANTEED

No Change of Wiring Necessary

- Only Three (3) Main Terminals to Connect
- Type A—100 volt, with variable detector, from 16-22 volts, \$20.50.
- Type B—100 volt, with variable detector, from 16-22 volts and variable voltage from 44 to 100 volts for amplifier, \$23.50.
- Type C—140 volt, with variable detector, from 16-22 volts, \$26.50.
- Type D—140 volt, with variable detector, from 16-22 and variable voltage, from 44-140 volts for amplifier, \$30.00.

Open Till 9 P. M. Daily

BUSINESS NEWS OF THE INDUSTRY

My Bristol Single Control Receiver

By David Grimes

CONTRARY to general belief, most things in this world do not "just happen." There is usually a series of prior events which predetermine the final result. The person on the outside is not familiar with the earlier moves and he assumes the completed article is just "dumb luck." The Bristol Grimes combination is one of those things which doesn't just happen.

Some time ago when my Inverse Duplex was still in its infancy, I bought a power amplifier, which strange as it may seem required no "C" battery. Upon combining it with my circuit, I was surprised at the volume and the quality. It was the missing link in my development. No other set could produce that volume without sacrificing that quality. That power amplifier was made by the Bristol Company. Negotiations were immediately started with them which led to their purchase of the remaining ten licenses under the Grimes Inverse Duplex System, an ideal combination which permitted the high efficiency of the Grimes circuit to be fully realized through the quality reproduction of the Bristol power amplifier.

The next efforts were devoted toward simplicity. It was realized that a radio set was merely a means to an end and therefore should not require a correspondence school diploma for successful operation. The final result was a single control set which even a five-year-old child can operate and which has stood the extreme test of perfect performance in the hands of the blind. Several invalids confined to their beds are also satisfied owners of this single control set.

Many years of radio experience taught us that satisfactory reception depended a great deal on local surroundings. No one given set will operate equally well under all conditions. The Bristol set was therefore designed to be readily adaptable to these many conditions by flexibility in the methods of reception. By merely throwing a switch the set may be operated by loop or by an-

tenna. A single connection in the rear adapts it most effectively to a long or short aerial. In many localities, it may operate with a ground connection only. No other set has the many possibilities for correct installation in particular receiving locations and with these determined, one knob does all the tuning.

Other refinements have been added, such as a protecting cover over the entire set, capable of being locked! A special jack has been installed for phone operation and



The Bristol single control receiver.

when tuning in, automatically reduces the volume on the loud speaker. A meter is used to permit most efficient operation of the amplifier tubes—greatly increasing their length of life as well as the life of the batteries. In every way possible this set has been made the latest word in radio and is one of the best adaptations of my Inverse Duplex principle. This set is now being manufactured and placed on the market by the Bristol Company, of Waterbury, Conn.

Rumors of a New Radio Corporation

RUMORS were current in New York City last week that a new radio patent holding company was about to be formed, with several million dollars capital, to be known as the Hazeltine Corporation. Its revenue was to be derived from royalties paid by manufacturers of radio products under patents controlled by the new company.

Prof. L. A. Hazeltine, inventor of the neutrodyne circuit, was named in the rumors as a director of the company to be formed. W. H. Taylor, Jr., of Pennie, Davis, Marvin & Edwards, patent attorneys of New York City, was said to be slated for the presidency.

When interviewed by RADIO WORLD Mr. Taylor declined to comment on the rumors and insisted that the matter was not in shape to be discussed, that he had authorized no statement in regard to it and that, so far as he knew, no announcement was forthcoming in the near future.

In the record of incorporations for which charters were granted at Dover, Delaware, last week, appears the following: "Hazeltine Corporation, New York, research and experimental work; \$20,000,000."

R. C. A. vs. DeForest

SEVERAL months ago the Radio Corporation of America, of New York, City, secured an injunction against the De Forest Telephone & Telegraph Co., of Jersey City, N. J., restraining the latter from manufacturing certain radio tubes, the patents on which were claimed to be owned by the Radio Corporation of America. It is alleged that the De Forest Company has continued to manufacture the tubes in violation of the injunction.

Vice-Chancellor Lewis, at Paterson, N. J., on February 5, called a hearing to compel the De Forest Company to show why it should not be held in contempt of court for alleged violation of the injunction. The hearing was adjourned to February 25, when the De Forest Company will put forward evidence in support of its continued production of the tubes in question.

John W. Griggs, former U. S. Attorney-General, is counsel for the Radio Corporation. Thomas Haight, former U. S. District Judge, represents the De Forest Company.

Horace E. Genge, 125 Marquette Ave., South Bend, Ind., has gone into the radio business.

Radio Literature Wanted

Manufacturers of and dealers in radio apparatus and accessories are notified that literature and catalogues describing their products have been requested, through the Service Editor of RADIO WORLD, by the following:

Dr. C. L. Harmer, Danville, Ohio.
John A. Sokol, 2117 So. Ridgeland Ave., Berwyn, Ill.
Horace E. Genge, 125 Marquette Ave., South Bend, Ind.
Albert H. Savage, 307 Hudson Ave., Albany, N. Y.
Burman C. Diddle, Chapin, Ill.
Harry A. Thomas, 1202 French street, Wilmington, Del.

Ajax Sued For Infringement

THE Ajax Radio Corporation, 367 Verona avenue, Newark, N. J., defendant in a suit brought by five other radio corporations, charging infringement on radio patent rights, was ordered on February 5 by Federal Judge John Rellstab in the United States Court in Newark to show cause, on February 18, why an injunction sought against it by the five companies should not be issued. Suit is brought by the Radio Corporation of America, De Forest Radio Telephone & Telegraph Co., General Electric Co., Westinghouse Electric & Manufacturing Co. and the American Telephone & Telegraph Co.

Broadcasting a Radio Show

F. P. GUTHRIE, district manager of the Radio Corporation of America, has pledged the cooperation of Station WRC in broadcasting to the country information regarding the First Annual Radio Show to be held at Washington, D. C., March 19-26. In line with this, Fred S. Lincoln, general chairman of the show committee, will deliver a series of addresses to the radio audience from WRC, the first of which will be broadcast in the near future.

Error in Telephone Number

THE telephone number of the Bel-Canto Manufacturing Co., Inc., 417 East 34th Street, New York City, is Vanderbilt 8959. As this company is advertising to sell a \$25.00 loud speaker for \$10.00 direct from manufacturer to consumer, and receives a large number of telephone orders, it is to be regretted that an error in the telephone number appeared in their advertisement in last week's RADIO WORLD.

Coming Events

INTERNATIONAL RADIO & ELECTRIC SHOW, Baltimore, Md., March, 1924.

RADIO will be featured at the electrical exhibition to be held at Melbourne, Australia, in September, 1924.

FIRST ANNUAL RADIO SHOW, Convention Hall, Washington, D. C., March 19-26, 1924.

FOURTH ANNUAL RADIO SHOW, EXECUTIVE RADIO COUNCIL, SECOND DISTRICT, INC., Hotel Pennsylvania, New York City, March 3-7, 1924.

USE
EVEREADY
Radio Batteries
-they last longer

YOU to hear programs from stations 400 to 1000 Miles Away. I can show you how to get them on YOUR CRYSTAL SET. Changes often cost Less Than One Dollar. Send self-addressed envelope for picture of my set.
LEON LAMBERT
567 So. Volusia, Wichita, Kansas


NOW is the TIME to USE
"Where I Go by Radio"
This New Unique RADIO RECORD BOOK Enables You to Keep for Reference What You Hear and How You "Tune In." Increases Radio Pleasure at Small Cost.
POPULAR EDITION, 2 Copies, \$1.00
Each Book Space for 300 Complete Records
HOLIDAY EDITION, 1 Copy, \$1.00
Space for 700 Complete Records
Each Book also contains Accurate List of U. S. Broadcasting Stations to Nov. 15, 1923, alone worth the price of book.
Size of Book 8x11 inches. Record Pages good paper, suitable either pen or pencil. Cover, heavy, flexible cover stock.
"Ra-Owls" Everywhere Like It, However.
Your Money Back if Not Satisfied.
But Don't Expect the World for \$1.00.
PROGRESS PRESS, Radio Dept.
Union, South Carolina, U. S. A.

1500 MILE RANGE
VACUUM TUBE RADIO SET READY BUILT
1,500-mile range attained in favorable weather with Atlas Wizard Single Tube Radio Set. Wonderful selectivity—clear tone reproduction—brings you melodies, music and market reports. Dials log with accuracy of a Neutrodyne.
One ATLAS WIZARD Radio Set completely built, **nothing else to buy**, to one person in each community, only **\$19.95**. Don't fail to take advantage of this amazing offer. Name and address brings set complete by express C. O. D. You take no risk so order this Radio wonder today.
ATLAS CUT RATE RADIO STORES
Div. 23, 345 S. Clark St., Chicago
Send 5c in stamps for Atlas Wizard Blue-print. Big Radio Catalog FREE.

1925 REG. VALUE \$57.50

WHAT YOU GET
Atlas Wizard Receiver, mahogany finish; Head Phones; Vacuum Tube; A & B Batteries; Aerial; Ground Wire; Instructions.
READY BUILT

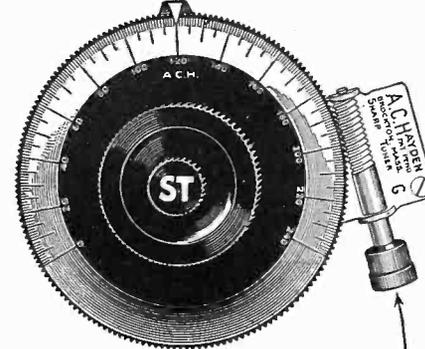A Pleasant Surprise Awaits the User of the A. C. H. Sharp Tuner Dials



Why the A.C.H. is different
3 in. DIAL (156-TO-1)
4 in. DIAL (215-TO-1)

Will improve any receiving set, making difficult tuning easy
Money Back Guarantee
Price 3-inch size, \$2.50 Price 4-inch size, \$5.00
Regular fitting 5/16 shaft 3/4 and 3/16, 5c each extra

Extra Advantage of the A C H

1. Can be attached or removed from any instrument.
2. Rough tuning same as any dial.
3. Movement so fine that the eye cannot detect but the ear can.
4. Automatically locks instrument so no jar can disturb it.
5. Dial grounded reducing the body capacity to a minimum.
6. Special dial 2 graduations where ordinarily one.

MAIL ORDERS SENT PREPAID IN U. S. A.
A. C. Hayden Radio & Research Co.
BROCKTON, MASS., U. S. A.

LONDON **TURN-IT** **PHIL.**
ADJUSTABLE **GRID LEAK**

"- did YOU get London?"

We have authentic reports proving that two of the three Philadelphia stations that tuned in London were equipped with "Turn-It" Adjustable Grid Leak—the perfect grid control.
Varies 1/2 to 5 Megohms! No Carbon or Graphite! No Sliding Contacts! Eliminates Microphone Noises on DX Stations!

Sole Distributors for Charles E. Bonime
TURN-IT RADIO SALES, Inc.
30 CHURCH STREET NEW YORK

\$1.00 At your dealer or direct on receipt of price.

Turn-it 

2,000 MILES
ON TRIPLE CIRCUIT with ONE TUBE
READ THE EXPERIENCE OF OTHERS

Gentlemen:—I completed making the SX-DX radio set which I bought from you while in New York on the 10th, and wish to state to you that after hearing quite a number of other one-tube sets this one is far superior to any one I have heard. Not only does this set enable me to tune in distant stations, but same does not fade, but holds the stations for any length of time and all the time very clear and with great volume.

I am unable to express my appreciation in this letter of how highly I am pleased with your set, but only wish I could be in personal conversation with you to tell you all the great things I have been able to do with my set.

Below are a few of the stations I have tuned in and have received very clear and distinct and with two sets of phones attached:


KDKA, WOR, WEAJ, WCBF, KFKX, WHAS, WJAS, WCAP, WHAI, WJAZ, WTAM, and last night I was very much surprised to tune in PWX, Havana, Cuba.

I am thinking of adding a two-step amplifier to my set so that I will be able to use a loud speaker, and will you kindly quote me your prices on parts for same, including tubes and batteries?

Two of my friends are considering the purchase of one of your sets, and I will do all I can to secure the order for you.

If this letter will be of any value to you, you have my consent to use same.

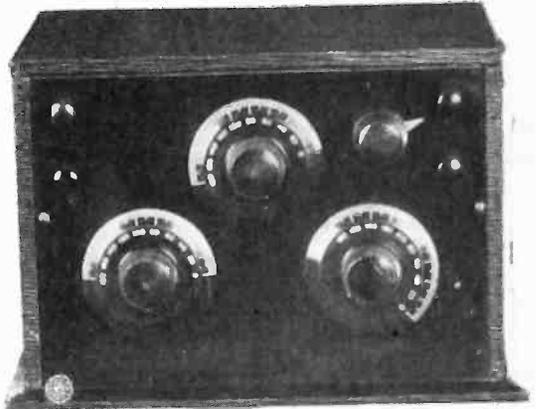Yours very truly,
B. H. M. CLARK.
375 Main Street,
Danbury, Conn.



ESSEX RADIO
AS SET LOOKS WHEN COMPLETED
\$15.00

THIS SET COMES TO YOU WITH COMPLETE BOOK OF INSTRUCTIONS COVERING ASSEMBLING, REQUIRING NOT OVER ONE HOUR OF YOUR TIME EVEN IF YOU NEVER PUT A SET TOGETHER BEFORE.

COMPLETE SET INCLUDES—


Vario-Coupler, Special Winding, 23 Plate Essex Condenser, 17 Plate Essex Condenser, Leatherette Cabinet, Standard Essex Socket, Rheostat, 6 ohms, will work with any tube, 4 Binding Posts. Hard Rubber, 7x10 Hard Rubber Panel, 3-3" Dials, 4 Pieces Bus Wire, 1 Length Spaghetti.

This Set with Tube and Batteries Will Cost \$20.00.
(PLUS POSTAGE)

These Prices Will Save You from \$15.00 to \$125.00.

MAIL ORDERS ONLY
MONEY ORDER—PREFERRED

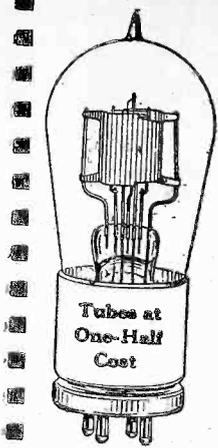ESSEX RADIO SERVICE
615 West 125th Street, NEW YORK CITY, N. Y.
Telephone: Morningside 0282



Save
1/2 Price
of
New Tubes

Burned out or
broken tubes re-
paired and guar-
anteed equal to
new.

Harvard Radio
Laboratories
200 Old Colony Ave.
South Boston, Mass.

PATENTS

promptly procured. Trade
Marks designed & registered
**FREE INVENTION RE-
CORDING BLANK**
Phone Vanderbilt 7212

**FREE MANUFACTURERS
PATENT CO., INC.**
800K 520 FIFTH AVE
NEW YORK

Nath.
Baldwin Phones
with

**SHELTONE
LOUD SPEAKER**

COMPLETE \$10.00

Postpaid. Use your head-
set for 2 purposes—Exceptional
combination value—Every
pair of phones tested—Guaran-
teed to give results.

WALTER SCOTT
1157 E. Broad St.
Newark, N. J.

OUT OF THE ETHER
Chats About Broadcasting
Stations


By Hirsch M. Kaplan

Proceeding up the scale we encountered station WPAB which was entertaining its listeners with a program of popular selections by the Nittany Nine, a musical group attending Penn State College. No doubt many of you remember the famous basketball team which this school once supported. Well, this musical team is making itself just as famous with its splendid efforts offered through this station.

Moving up the scale a few notches we next heard a splendid array of music as played by a very distinguished group known as the Shrine Band. Between numbers the individual members offered their own personal entertainment in the way of wise cracks. All in all their splendid offerings were greatly appreciated and let's hope that we will have the pleasure of hearing them again.

Station WGR, located in "The City of Opportunity" was next heard as they were offering a program of dance music by the well known Vincent Lopez Orchestra. No, they are not the original Vincent Lopez combination which plays through station WEAJ every Wednesday and Saturday evening, but they are every bit as good. That says a great deal for, in our estimation, of all the dance orchestras we have

(Concluded on next page)

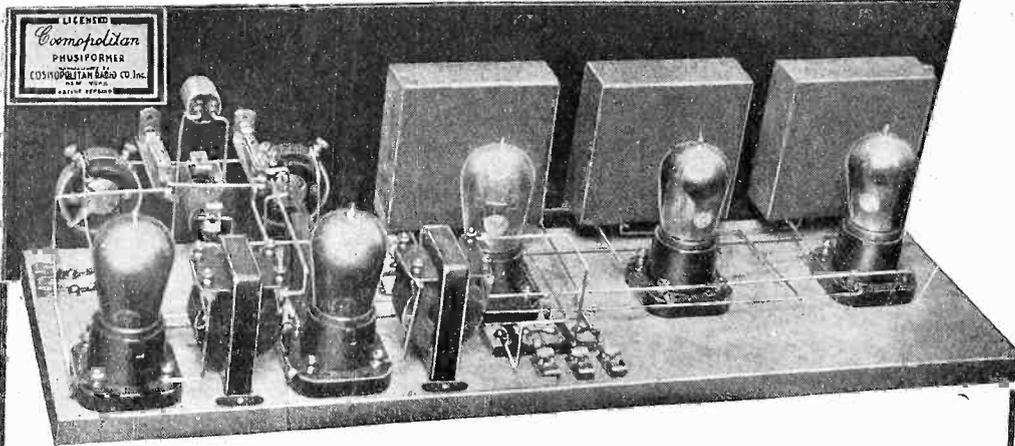

COSMOPOLITAN PHUSIFORMER

Converts any set to the equivalent of a Neutrodyne and then some.

More satisfactory than any instrument heretofore given to the public.
It meets the following requirements:

- 1—Non-oscillation
- 2—Non-reradiation and non-interference
- 3—Sensitive to distant stations
- 4—Freedom from hand capacity
- 5—Synchronized and calibrated tuning
- 6—Simple operation and construction
- 7—Inexpensive
- 8—Wave Trap

LIST PRICE \$8.50

For further particulars apply to any radio dealer or write to address below.

COSMOPOLITAN PHUSIFORMER COMPANY, INC.

GROVER C. DAHLBENDER, Secretary and Treasurer
Factory: 151 East 126th Street, New York City Office: 2255 Broadway, New York City

**WE REPAIR
RADIO TUBES**

WD-11 ... \$3.00	DV-2 ... \$3.00
WD-12 ... 3.00	DV-6A ... 3.00
UV-200 ... 2.75	UV-199 ... 3.00
UV-201 ... 3.00	C-299 ... 3.00
C-300 ... 2.75	UV-201A ... 3.00
C-301 ... 3.00	C-301A ... 3.00
DV-6 ... 3.00	Marconi ... 3.00
DV-1 ... 3.00	Moorhead ... 3.00
6 v. Plain Detector ... 2.75	
6 v. Plain Amplifier ... 3.00	

Mail orders solicited and promptly attended to.
Dealers and agents write for special discounts.


H. & H. RADIO CO.
P. O. Box 22-B
Clinton-Hill Station Newark, N. J.

THE TRINITY LOUD SPEAKER



TYPE "A1"
21" FIBER
HORN
\$25.00

TYPE "B"
(For Phonographs)
\$12.50

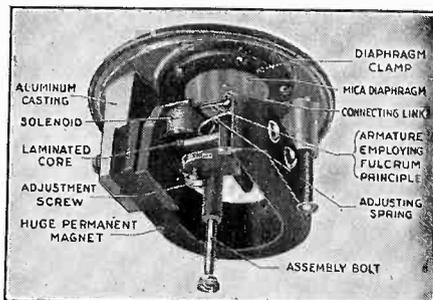

INTERIOR CONSTRUCTION

An ear phone is an ear phone no matter how fancy the horn that covers it may be, and, due to the delicate construction of an ear phone it is utterly incapable of giving true tone reproduction, especially when relatively large currents are passed thru its coils, such as the output of a two-stage or power amplifier.


The Trinity Loud Speaker element embodies the well-proven and tested principles of the phonograph reproducer with the soundest principles of electromagnetic design best adapted for loud speaker operation. It is not an ear phone when placed on a head band and a loud speaker when covered with a horn. It is a sturdy loud-speaking element ALWAYS.

SEND FOR LITERATURE.

TRINITY RADIO CORPORATION

446 TREMONT STREET, BOSTON, MASS.

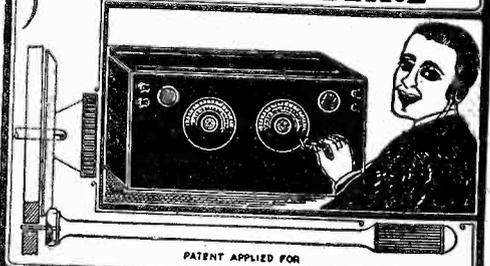**HUNT'S UNIVERSAL HAIR-LINE
RADIO TUNING DEVICE**



PATENT APPLIED FOR

**ONE VERNIER
FOR ALL DIALS**

Gives micrometric adjustment outside the field of inductivity.

Tested and approved by amateurs and experts. Enables you to tune distant stations easier and more clearly. Simple as A B C. Installed from outside, no dismantling of your set necessary. Audibility made more natural or less distorted by the fine adjustments obtained. One Hunt's Device handles all dials on set or several sets. Costs only one dollar on guarantee of money refunded if not satisfied. Ask your dealer or order direct from Hunt Co., 486 Shrine Bldg., Memphis, Tenn.

Out of the Ether

(Concluded from preceding page)

heard via radio, Vincent Lopez and his Hotel Pennsylvania Orchestra rank third to Paul Specht and his Hotel Alamac jazz boys whom we consider as the leaders of their class.

We next jumped to 429 meters on which wave WSB sprung a surprise by offering the fistic combat between Young Stribling and Billy Shade. The combat itself, from what we heard, was great, but the announcing of the clash was not up to the standard set by those who perform this feature

through station KDKA and WJZ. So ended one evening of experimenting.

The male folks may have the reputation of being the whistlers, but you should have heard Miss Mary McKee whistle. Boy, oh boy! The canaries have nothing on her. She whistled a couple of classical selections and it was great stuff. Miss McKee was part of the Capitol's program rendered through station WEAf and we hope that Roxy will give us the pleasure of hearing her a few more times.

RADIO

SEND FOR OUR COMPLETE
MONEY SAVING CATALOG
TIMES SQ. AUTO SUPPLY CO. INC.
MAIL ORDER DEPT.
1745 BROADWAY AT 56th STREET
NEW YORK, N. Y.

FORMICA
A Laminated Phenolic Condensation Product
SHEETS TUBES RODS

PANELS CUT-DRILLED
Neatly—Lowest Prices

For quick service and high class work see us.

TRIPLE PANEL MOUNTING SOCKETS

This scarce item ready for instant delivery.

The Best Made—BACK MOUNTING INDUCTANCE SWITCH—See Them

UNITED RADIO MFG. CO.

Phone Cort. 4885 Dept. R. W.
191 GREENWICH STREET, N. Y. CITY

Lattice Coil Specialties




Varimeters
Variocouplers
R.F. Transformers
Micro-Mike
Condensers
Plain Coils
Tapped Coils

ESTRU LATTICE COIL PRODUCTS have been designed so as to produce as nearly as possible IDEAL INDUCTANCE in various forms. It was not the intention in designing, to produce Miniature Apparatus, the small size being the result of careful electrical design with no UNNECESSARY Mechanical parts which would detract from the electrical efficiency.

YOU will appreciate these facts as set forth in our COMPLETE DESCRIPTIVE LITERATURE, which will be sent on request and in reading our GUARANTEE which goes with all ESTRU PRODUCTS.



2905 WEST MADISON STREET

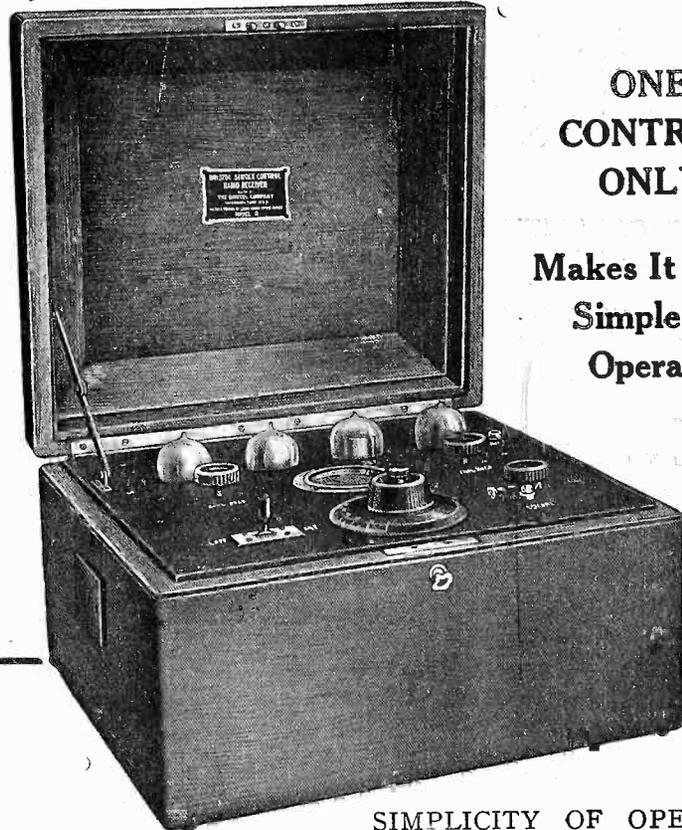

ONE
CONTROL
ONLY

Makes It Most
Simple to
Operate

BRISTOL SINGLE CONTROL RADIO RECEIVER

(Non Regenerative)

Using Grimes Inverse
Duplex System

SIMPLICITY OF OPERATION is the outstanding feature of this Receiving Set. One Control Dial includes every adjustment. To tune in, turn this Dial. A station once located can always be brought in again at the same setting.

NOT CONFINED TO LOCAL BROADCASTING—this four-tube set has power equal to six. Because the Grimes Inverse Duplex System utilizes the first two tubes for both Radio and Audio Amplification.

FULLY EQUIPPED FOR LOUD SPEAKER—no additional amplification is necessary—the patented Bristol One Stage Power Amplifier is incorporated as the last stage of amplification.

ANTENNA OR LOOP—either may be used to suit conditions.

SOLID MAHOGANY CASE with walnut finish encloses the complete Receiving Set. It is a beautiful piece of furniture fully in keeping with the most luxurious room.


The price—Bristol Single Control Radio Receiver, \$190.00.

Ask for copy of Bulletin 3013-BT describing this set.

THE BRISTOL COMPANY
Waterbury, Connecticut

1924's BEST RECEIVER

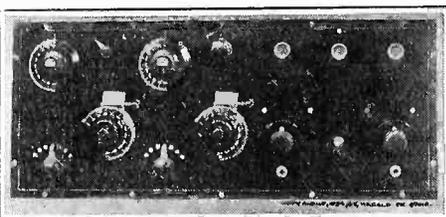Works on Aerial or Loop
Regenerative — Highly Selective
— Non-Reradiative
Radio Satisfaction at Last



Copyright, 1924, by Harold De Jong

Build It Yourself at Low Cost

Complete Engineering Plans anyone can understand, showing construction in detail of set, wiring, cabinet, bill of material, specifications, assembly, operation and instructions.

Blueprints, 16x20; Photo-diagram, 8x10

Standard parts of all manufacturers can be used. Volume, Distance, Clearness and Non-Interference are the features of this set. Reliability and value guaranteed or money back.

COMPLETE PLANS AS STATED FOR

- Three Tube Set, \$2.00
- One Tube Detector, \$1.50
- Two Step Amplifier, \$1.00

Check plans wanted—cut out end mail with cash or money order.


NAME.....
STREET.....
CITY.....
STATE.....

HAROLD DE JONG
118 INDIA STREET
BROOKLYN, NEW YORK
Consulting Engineer, Jr., Am. Soc. M. E.

Are You Building A Radio Set?


Then Use A

STAR SINGLE SLIDE COUPLER

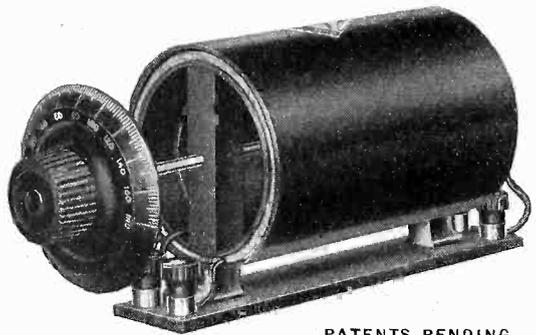

TYPE
1C1

END
VIEW

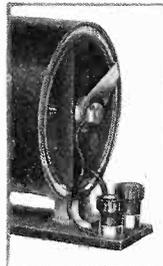

NO BODY CAPACITY
EXTRA KNOBS

PATENTS PENDING


NO SOLDERING
DUSTY PARTS

PERFECT CONTROL AND TUNING

Note:—

WE have tested type 1C1 on this circuit, get coast to coast receiving. Type 1C1 on this circuit will give surprising results to you. Let us tell you about Better Radio Receiving.

**OUR STAR
COUPLE
TYPE 1C1**

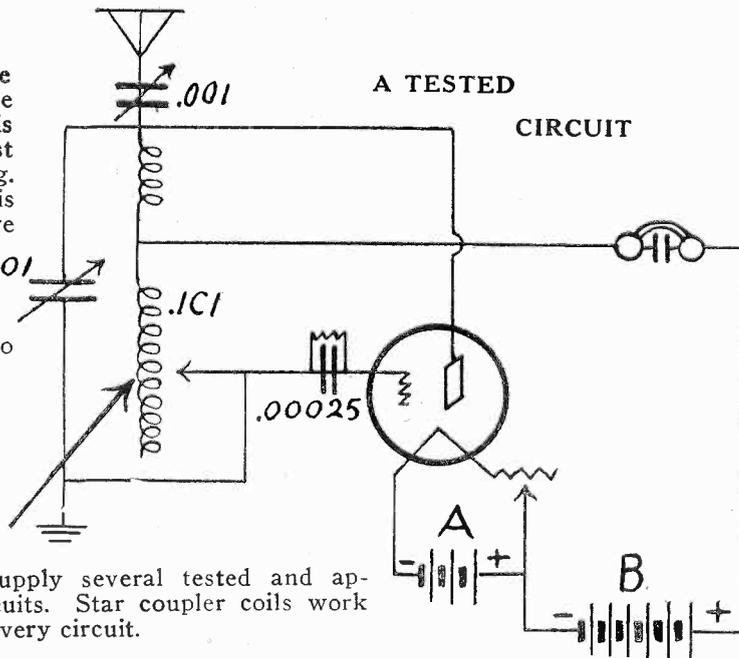

We can supply several tested and approved circuits. Star coupler coils work on nearly every circuit.

**MAILED COMPLETE WITH PRINTS
FOR TWO TESTED CIRCUITS FOR.. \$8.50**

— WE PAY POSTAGE AND INSURANCE —

THE STAR PRODUCTS GUARANTEE

All Star Radio products are guaranteed to give perfect satisfaction.
Guaranteed to be of the best material and workmanship obtainable.
Guaranteed to be easily attached without soldering.

DEALERS—WRITE OR WIRE FOR EXCLUSIVE TERRITORY.
DISTRIBUTORS—SAMPLES AND DESCRIPTION UPON REQUEST.

STAR RADIO

711 SO. DEARBORN



PRODUCTS CO.

CHICAGO, ILL.

**Federal Standard
Radio Products**

Standard of the Radio World, 130 separate units, each fully Guaranteed. Write for Catalog.

Federal Telephone and Telegraph Co.
BUFFALO, N. Y.



Ask for Newman's RADIO CONSTRUCTOR Plans and Books at your dealers. Blue prints showing full size templates, wiring connections and instructions, for building the most popular circuits.

S. NEWMAN, Publisher
74 Dey Street New York City

Workman Radio Service

"THE ACCENT IS ON SERVICE"

14-16 Vesey St. NEW YORK

VARIOCOUPERS	
\$3.50 Workrite 180° Silk Wound	\$2.95
3.50 Fisher, Large, 90°	2.75
2.75 Fisher, 180°	2.25
VARIOMETERS	
\$3.50 Workrite	\$2.95
5.00 Pathé Moulded	2.25
3.50 Fisher, Large	2.85
CONDENSERS	
\$2.00 R. C. 11 plate	\$1.05
2.35 R. C. 23 plate	1.35
2.75 R. C. 43 plate	1.65
VERNIER CONDENSERS	
\$4.00 R. C. 23 plate	\$2.25
5.00 R. C. 43 plate	2.95
PHONES	
\$18.00 DR. SEIBT IMPORTED "SUPER HEADSET"	\$5.90
\$12.00 N. & K., Imported	\$5.90

We specialize in the FAMOUS AMBASSADOR LONG DISTANCE CIRCUIT. Write for list of parts for this set. Either single or three tube set. Price of parts for single tube set... \$15.60. Price of parts for THREE TUBE SET... 28.90. Mail orders promptly attended to. All orders amounting to \$5.00 or more will be shipped prepaid. Will ship C. O. D. unless remittance accompanies order. The above items are just a few of our numerous attractive priced articles, which are contained in our BULLETIN OF RADIO PARTS. Gladly sent to you upon request.

**First Annual
RADIO SHOW**

under the auspices of

**The Radio
Merchants Association
of Washington, D. C.**

CONVENTION HALL

(60,000 Sq. Ft. Floor Space)

March 19th to 26th Inclusive


Featuring

Startling Government Exhibits.
The First Public Display of
Radio Photography by C.
Francis Jenkins, Inventor.
Many Other Late Developments.

See the Nation's Capital in the Grip of a Tremendous Epidemic of "Radioitis."

(Address all inquiries to Alfred L. Stern, Director, Washington Radio Show, Suite 333, Star Building, Washington, D. C.)

Kellogg Variocouplers

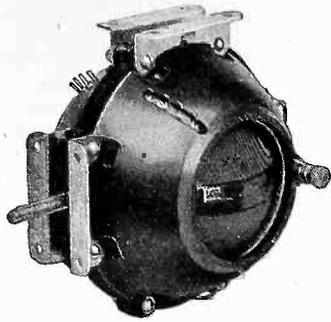

No. 501 Variocoupler

The Kellogg variocoupler furnishes coupling of the highest degree assuring maximum volume and clarity.

The shells are of Bakelite treated to prevent distributed capacity. There are eleven stator and two rotor taps. No sliding contacts; rotors are made with special flexible wire through hollow shaft to binding posts on stator shell. Can be used as a split-variometer. Large bearings warrant smooth operation and long life. Specify Kellogg and know you have the best.

If your dealer does not handle Kellogg, communicate direct with us.



USE—Is The Test

KELLOGG SWITCHBOARD & SUPPLY COMPANY

1066 WEST ADAMS STREET
CHICAGO, ILLINOIS

Kill the Squealers—RADIO WORLD has pledged itself to clear the air. Watch us do it!

Additional Programs Station WOO, Philadelphia, Pa.

509 Meters (590 Kcys.) E. S. T. Feb. 15—11:00 A. M.—Grand organ. 11:30 A. M.—Weather forecast. 11:55 P. M.—Naval Observatory time signal. 12:00 Noon—Luncheon music by the Tea Room Orchestra. 4:45 P. M.—Grand organ and trumpets. 5:00 P. M.—Sports results and police reports. 7:30 P. M.—Dinner music from Hotel Adelphi Concert Orchestra, A. Candelori, director. 8:00 P. M.—Dr. R. Tait McKenzie. "Keeping Physically Fit." 8:15 P. M.—Lewis James Howell, musical setting of Longfellow's "King Robert of Sicily"; Harriette G. Ridley, accompanist. 8:30 P. M.—Special musical program from Fox Theatre Studio. 9:15 P. M.—Grand organ recital, Miss Mary E. Vogt at the Console. 9:55 P. M.—Naval Observatory time signal. 10:02 P. M.—Weather forecast. 10:03 P. M.—The Kentucky Kernels Dance Orchestra from Hotel Adelphi.

Feb. 16.—11:00 A. M.—Grand organ. 11:30 A. M.—Weather forecast. 11:55 A. M.—Naval Observatory time signal. 12:00 Noon—Luncheon music by the Tea Room Orchestra. 4:45 P. M.—Grand organ and trumpets. 5:00 P. M.—Sports results and police reports. 9:55 P. M.—Naval Observatory time signal. 10:02 P. M.—Weather forecast.

Station WBAP, Fort Worth, Texas

476 Meters (620 Kcys.) C. S. T. Feb. 17—11 A. M.—12:15 P. M.—Complete services of the First Methodist Church; Rev. J. W. Bergin, pastor. 4:5 P. M.—Organ concert. 5-6 P. M.—Vesper concert. 11-12 P. M.—Concert by Fred Cahoon's WBAP Southern Serenaders Orchestra.

Feb. 18—7:30-8:30 P. M.—Concert by the John Tarleton Agricultural College, under the direction of Charles W. Froh. 9:30-10:45 P. M.—Concert by the band of Grandview, Texas, James E. King, director.

Feb. 19—7:30-8:30 P. M.—Concert by the D. G. Griffin Quartet. 9:30-10:45 P. M.—Concert by E. Clyde Whitlock's violin ensemble.


Feb. 20—7:30-8:30 P. M.—Monthly student recital arranged by Sam S. Losh, baritone and pianist. 9:30-10:45 P. M.—Concert by George Freeman's Sooner Serenaders, the Texas Hotel Orchestra.

Feb. 21—7:30-8:30 P. M.—Concert by the jubilee singers of the Dickson Colored Orphanage, Gilmer, Texas. 9:30-10:45 P. M.—Organ concert by Will Foster, organist of the First Methodist Church.

Feb. 22—7:30-8:30 P. M.—Concert by the Yeoman Orchestra, Owen Crockett, director. (E. L. O. announcing.) 9:30-10:45 P. M.—Concert by the Palo Pinto, Texas, Square Dance Orchestra. (The Hired Hand announcing.)

Feb. 23.—7:30 P. M.—Review of the interdenominational Sunday School lesson and Radio Bible Class presented by Mrs. W. F. Barnum.

Every Question ANSWERED for only \$1

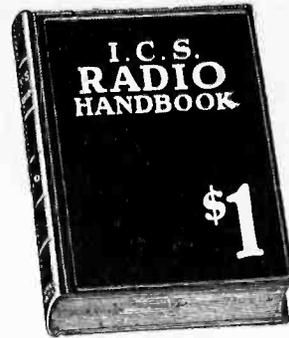

JUST OUT
514 PAGES

Compiled by
HARRY F. DART,
B.S.E.E.

Formerly with the
Western Electric Co.,
and U. S. Army In-
structor of Radio.

Technically edited by
F. H. Doane

NO MORE need you turn from book to book, hoping to find what you want. It is all here, in 514 pages crammed full of every possible radio detail. Written in plain language, by engineers for laymen. 20,000 sold.

IT EXPLAINS: Electrical terms and circuits, antennas, batteries, generators and motors, electron (vacuum) tubes, every receiving hook-up, radio and audio frequency amplification, broadcast and commercial transmitters and receivers, super-regeneration, codes, license rules. Many other features.

Send \$1 to-day and get this 514-page I. C. S. Radio Handbook—the biggest value in radio to-day.

International Correspondence Schools
Box 8792, Scranton, Penna.

I enclose One Dollar. Please send me—post-paid—the 514-page I. C. S. Radio Handbook. It is understood that if I am not entirely satisfied I may return this book within five days and you will refund my money.

Name.....

Address.....

Come on, Fellows! Let's all build that Super-dyne that appeared in RADIO WORLD for Dec. 15, 22 and 29. It's the best thing that the past year brought out. Start it now!

RADIO WORLD, the only radio paper that keeps right up to the minute on all radio news—it's NEWS when you see it in RADIO WORLD.

COMPLETE PARTS FOR THE original "C. White Power Amplifier"

with Como Duplex Transformers


This amplifier has been considered the best that can be made for
QUALITY AND VOLUME

Parts for one stage Como Push-pull amplifier as illustrated consisting of:—

- 1 Pr. Como Duplex Transformers
- 2 Tube Sockets
- 1 Rheostat
- 1 Mahogany Mounting Board, Wire, Screws and Terminals
- 1 Photographic Diagram.

Price \$16.00

Complete

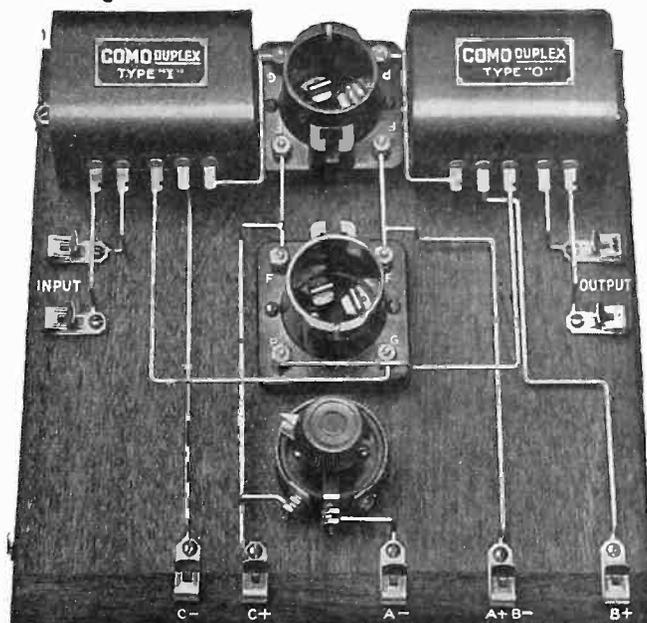

Parts for two stage Power Amplifier consisting of:—

- 1 Pr. Como Duplex Transformers
- 3 Tube Sockets
- 1 Rheostat
- 1 Audio Frequency Transformer
- 1 Mahogany Mounting Board, Wire, Screws and Terminals.
- 1 Photographic diagram

Price \$21.50

Complete

Above illustration shows the hook-up for one stage Como Duplex Push-Pull

These parts are complete and nothing else is required.

Results are absolutely guaranteed. For those who do not wish to assemble the parts we can furnish the board all wired with everything in place and ready to use at an additional cost of \$3.00 for one stage and \$4.00 for two stage; Radio tested in our laboratory.

POND RADIO LABORATORIES, 264 So. Huntington Ave., Boston, Mass.

CROSLEY
RADIO CATALOG FREE

Describes fully the complete line of radio frequency sets, regenerative sets (licensed under Armstrong U. S. Patent No. 1,113,149) and parts.

Write for Catalog Today

THE CROSLEY RADIO CORPORATION
POWEL CROSLEY Jr., President
2402 Alfred Street Cincinnati, Ohio

For best reception you need

The Goodman

The niftiest short wave tuner on the market. Great for present broadcasts, local and DX. Used in all parts of the world. Certificates of merit from testing laboratories. Pamphlet on request.

L. W. GOODMAN, Mfr., Drexel Hill, Pa.

ON ONE TUBE

Broadcasting from Atlantic Coast, Mexico, Hawaii, Canada and Cuba heard in California by users of CROSS COUNTRY CIRCUIT. Range due to simplicity of set and only one tuning control. Easily and cheaply built by any novice. Dry coil tubes may be used. All instructions, blueprint panel layout, assembly photo, etc. Postpaid 25c. Stamps accepted.

VESCO RADIO SHOP, BX RW-117, Oakland, Cal.

RADIO
BIG MONEY IN A BIG FIELD

Wanted — and wanted quick are men who can qualify for big pay positions in the enormous, fast growing Radio Industry. Once in a lifetime chance. Fast, easy to learn. No previous experience needed.

Be A Radio Expert
\$3,000 to \$10,000 a Year

Learn at home, by actual practice, to design, construct, install, operate, repair and sell Radio Equipment. Pleasant, fascinating, profitable. My methods are simple, clear and successful. Turn your spare time into cash.

FREE WONDERFUL 1000 MILE TUBE RECEIVING SET. Write today for Booklet "Radio Facts" FREE. L. S. Mohaupt, Radio Eng., American Radio Association 4513 Ravenswood Ave., Dept. 92, Chicago

FOR RELIABLE UP-TO-DATE
RADIO MAILING LISTS

Use Our Card Catalog Directory in use now with over 200 Radio Manufacturers and Jobbers

Your ENVELOPES ADDRESSED
At \$2.50 per 1,000

Write for Particulars

Sydell's Radio Trade Directory
410 W. 31st St., New York. Chickering 9840

THAT SUPERDYNE RECEIVER!

The receiver every fan has been looking for. The Four-Tube Receiver that is more powerful than a six-tube Naval Receiver. The Receiver which does not require a laboratory expert to build or operate. The Receiver that accomplishes anything any other will—and then more.

SEE RADIO WORLD

for Dec. 15, 22 and 29, and get all the details which will enable you to build this marvelous four-tube wonder. The 3 copies for 45c, or sent free if you send \$6.00 for yearly subscription. NOW!

BUILD a "S-U-P-E-R-D-Y-N-E"

RADIO WORLD, 1493 Broadway, N. Y. C.

Government Wants Radio Engineers

THE United States Civil Service Commission announces the following open competitive examination: Radio engineer, \$4,000 to \$5,000 a year; associate radio engineer, \$3,000 to \$4,000 a year; assistant radio engineer, \$2,000 to \$3,000 a year.

Receipt of applications will close March 11. The examinations are to fill vacancies in the Signal Service, McCook Field, Dayton, Ohio, and Camp Alfred Vail, N. J., at an entrance salary of \$2,000 a year, plus the increase of \$20 a month, and vacancies in the federal classified service throughout the United States at the salaries indicated above.

The duties of appointees are to conduct or superintend the development, design, construction, installation, standardization, and the writings of specifications for practical and special apparatus and methods of radio communication, such apparatus to include sets for land use for more or less permanent stations, also for portable land stations, and for airplane and ship sets; to carry out advanced technical work in radio research; to analyze the data accruing from observations of the operation of various radio apparatus and installations; to make recommendations as to policy, apparatus, or installation in accordance with inspections; to plan and execute experimental investigations; and to perform other related work.

Competitors will not be required to report for examination at any place, but will be rated on their education, experience, and fitness, and publications, reports, or thesis to be filed with the application. Full information and application blanks may be obtained from the United States Civil Service Commission, Washington, D. C., or the secretary of the board of U. S. civil-service examiners at the post office or customhouse in any city.

Steamship in Pacific Gets Detroit

EDITOR, RADIO WORLD: The oil tank steamer "Eurana," chartered by the Tidewater Oil Company, was in touch with Detroit (WWJ) and Los Angeles (KHJ) all the way from Baltimore to San Pedro, Cal., via Panama Canal. A DeForest honeycomb coil set with two stages of audio-frequency amplification was used but signals were perfectly clear on detector alone.

Truly yours,
R. W. WOODS,
Radio Operator.

1365 So. 2nd St., Plainfield, N. J.

IT'S A FRAME-UP
CAST ALUMINUM FRAMES

FOR YOUR RADIO SET
MAKE IT RIGID and STRONG

NO WARPING NO SHORT CIRCUITS
SPRINGING BROKEN WIRES

NO MORE CABINETS

JUST APPLY FLAT MAHOGANY OR PLATE
GLASS COVERS TO THE FRAMES

A SIZE FOR YOUR SET. PRICE **85c. Each**

QUINBY RADIO CONSTRUCTION CO.
Subway Bldg., 181st Street and St. Nicholas Avenue
New York City

NEUTRODYNE PARTS

Full set of Neutroformers, Variable Condensers with dials, and Neutrodons **\$13.25**

Above parts are guaranteed, and are made under Hazeltine patents.

Complete parts for three tube Neutrodyne tuner, (tubes, batteries, or phones not included), drilled panel, tube sockets, rheostats, fixed condensers, Jack, binding posts, wire, spaghetti, and blue prints.

COMPLETE FOR \$19.95

Postage additional on all shipments.
Ask for our price list.

Send no money, Order by postcard,
Pay the Postman

RADIO SURPLUS STORES
HELENA, MONTANA

Trade-**"THORIO"**-Mark
DETECTOR-AMPLIFIER

T. No. 1. Detector-Amplifier. 1 1/2 Volt Filament. 1/4 Ampere. Plate Voltage, 22 1/2-90.
T. No. 3. Detector-Amplifier. 5 Volt Filament. 1.25 Ampere. Plate Voltage, 22 1/2-90.
T. No. 5. Detector-Amplifier. 6 Volt Filament. 25 Ampere. Plate Voltage, 22 1/2-90.
T. No. 7. Detector. 6 Volt Filament. 1/4 Ampere. Plate Voltage, 16-22 1/2.

Filament licensed under Patent No. 1422019 July 4th, 1922.

THORIO TUBES GUARANTEED
Superior to any on the market for Volume, Clearness, Distance and lack of Tube Noise. Mailed Post Paid to any address in the United States at \$4.00 each.

HAYDEN SALES COMPANY
109 GRAND STREET JERSEY CITY, N. J.
Dealers' orders given prompt attention

Radio of Excellence
"PARAGON"

Type RB 2A, \$125.00

Parts for Acmedyne in Stock

BALLANTINE Tuned Radio Frequency Transformer \$9.60
LANGBEIN & KAUFMAN
Variometers and Variocouplers 7.00
AMPERITES 1.10
MYERS HI-MU Vacuum Tubes 4.35

Service That Is Certain

RADIO & MECHANICAL TRADING CORP.
23 Warren St. New York City

The Latest in
Circuit Designs

HENLEY'S
222
RADIO
CIRCUIT
DESIGNS

A Complete and Up-to-Date Collection of
Modern Receiving and Transmitting
Hook Ups

Written and Edited by a Staff of Radio Engineers of Wide Practical Experience and Thorough Theoretical Training.

Editor JOHN E. ANDERSON, A.B., M.A.
Formerly with the Western Electric Co.
ARTHUR C. C. MILLS, Radio Expert
ELMER H. LEWIS, Assoc. I.R.E., Radio Instructor
East Side Y. M. C. A., New York City—
Author of "A B C of Vacuum Tubes"

Price \$1.00

256 Pages.
284 Diagrams and Illustrations Specially made for this book.

AN ENTIRELY new and thoroughly practical book on radio circuit designs which will meet the needs of every radio enthusiast, whether novice or expert, amateur or professional. It is replete with correct and trustworthy radio information from which any one can successfully build and operate any of the circuits given. Contains the largest collection of radio circuits and Hook Ups ever published and includes all the standard types and latest developments.

This new book treats the subject in an entirely different and novel way, as it is the only book that illustrates the complete electrical design of the circuits, showing the electrical values of impedances, capacities and resistances, with the name of each element on the diagram of the circuit. It surpasses all other books in the scope of its subject matter, in the simplicity and novelty of presentation, and in thoroughness of detail.

THE COLUMBIA PRINT
1493 BROADWAY NEW YORK CITY

**Additional Programs
Station WDAF, Kansas City, Mo.**

411 Meters (730 Kcys.). C. S. T. Feb. 19.—3:30 to 4:30 P. M.—R. Davis "Radio" Orchestra. 6:00 to 7:00 P. M.—Piano tuning in number on the Duo-Art; marketgram, weather forecast, time signal and road report; address, speaker from the Kansas City Children's Bureau; the children's story and information period; music, Fritz Hanlein's Trianon Ensemble, Hotel Muehlebach. 8:00 to 9:15 P. M.—Classical program featuring prominent negro artists of the country. 11:45 P. M. to 1:00 A. M.—The "Merry Old Chief" and the Conn-Sanders Novelty Singing Orchestra, Plantation Grill, Hotel Muehlebach.

Feb. 16.—3:30 to 4:30 P. M.—The Riley-Ehrhart Orchestra. 6:00 to 7:00 P. M.—Piano tuning-in number on the Duo-Art; marketgram, weather forecast, time signal and road report; address, Edgar A. Linton, writer-lecturer; the children's story and information period; music, Fritz Hanlein's Trianon Ensemble, Hotel Muehlebach. 11:45 P. M. to 1:00 A. M.—(Nighthawk Frolic.) The "Merry Old Chief" and the Conn-Sanders Novelty Singing Orchestra, Plantation Grill, Hotel Muehlebach.

Station KSD, St. Louis, Mo.

546 Meters (550 Kcys.). C. S. T. Feb. 18.—3:30 P. M.—Vocal and instrumental specialties, orchestra and organ recital direct from Grand Central Theatre.

Feb. 19.—8:00 P. M.—Studio recital by Mrs. William H. Hopkins, soprano; Miss Mildred Freeze, accompanist. Address "Weeds Used in Medicine," by O. S. Ledman.

**VACUUM TUBES
REPAIRED**

WD-11, WD-12, UV-201A, UV-199
and others
for **\$3.00**

Quick service. All tubes repaired by us guaranteed to work as good as new. Send your dead tubes. We prepay parcel post to you. All you pay is \$3.00 to post-man.

THOMAS BROWN CO.
511-519 ORANGE ST. NEWARK, N. J.

**ARE YOU GOING TO
BUILD A SET?**

Our specialty is:—Making outfits of complete parts for the construction of all good sets.

Our sets contain only the best standard apparatus. No inferior material is used in order that we may reduce the cost of the set to us. Our prices are absolutely the lowest that it is possible to sell good reliable outfits at.

By selling the complete outfit we are enabled to give a lower price than what the parts would cost if bought separately.

The outfits are complete, with drilled panel, base, bus-wire, binding posts, best standard parts, and directions, all assembled, ready to wire, which takes but a few hours.

We pay transportation charges, and we guarantee satisfaction.

1. Autoplex. One tube. Operates a loud speaker. The simplest set that has yet been designed \$12.00
2. Flewelling. One tube. Equal to three tube sets for distance..... 10.50
3. Reflex. One tube. Operates a loud speaker. 2000 to 3000 miles with phones. No howling. No re-radiation. This set incorporates one stage of radio frequency amplification, detector, and one stage of audio frequency amplification with only one tube..... 15.00
4. Reflex. Two tube. 500 to 1000 mile loud speaker range 23.00
5. Reflex. Three tube. Up to 3000 mile loud speaker range 33.00
6. Neutrodyne. Five tube. Save \$105 by building your own Neutrodyne..... 45.00
7. Ultradyne 45.00
8. Superdyne. Four tube. The Wonder Set. The set just described in Radio World. Results equal those obtained on an eight tube super-heterodyne..... 38.00
9. Major Armstrong's Radio Flivver. Two tube. This set is the most powerful ever made. In actual tests, using only a loop, this set has given greater volume than a regenerative set, using an outdoor antenna, three stages of audio frequency amplification, and three stages of power amplification. Slightly harder to operate than an ordinary set at first, but it is well worth while 25.00

If you wish to make any set which is not listed here, write us. We make outfits of all kinds of sets, and use only the best of apparatus.

BILTMORE RADIO COMPANY
238 Lamartine St. Boston 30, Mass.

**ALL LINES OF
RADIO MERCHANDISE
ARE IN OUR STOCK**
New York Prices Direct to You
Just Tell Us What You Want
GLOBE RADIO SHOP
115 West 23rd Street New York

Ackerman
LOUD SPEAKER, \$9.50
Complete—Ready for Immediate Use
Delivered Anywhere in the U. S. A. A Marvelous
Speaker for the price of a headset.
Dealers and Jobbers Write for Discounts.
ACKERMAN BROS. CO., Inc.
301 W. 4th St. (Dept. "RW"), New York, N. Y.

**An Absolute Guarantee
with every instrument
made them famous!**

SHAMROCK
FOR SELECTIVE TUNING

180°

Vario-Coupler

list price,
\$3⁵⁰ each

**DOUBLE
DUTY
PIG-TAIL
Variometer**

SHAMROCK MFG. CO.
316 W. Market St. — Newark N. J.



The long-life tube!

Since their inception, radio vacuum tubes have been fragile. To knock or drop one incurred the expense of a new tube. But now there are


MYERS TUBES

Practically Unbreakable

—so protected by their unique design that they have been dropped on the floor without injury. But their sturdiness is only one feature. They are the most perfect detectors and amplifiers obtainable. Smaller capacity and no bunched leads mean less interference—more clarity and greater amplification. Actual tests, all over the world, have proved their supremacy. Two types—**Dry Battery** and **Universal** (for storage battery). At your dealer's—or send price and be supplied postpaid. Write for free circuit diagrams.

\$5 EACH Complete with clips ready to mount on your set; no sockets or extra equipment required.

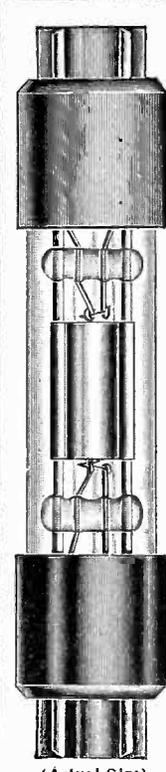F. B. Myers Co. Ltd.
Radio Vacuum Tubes
240 CRAIG ST. W.
MONTREAL CANADA



(Actual Size)

**FILL OUT AND MAIL NOW
SUBSCRIPTION BLANK
RADIO WORLD**

RADIO WORLD

1493 Broadway, New York City

Please send me RADIO WORLD for..... months, for which

please find enclosed \$.....

SUBSCRIPTION RATES:

- Three Months 1.50
- Single Copy \$ 1.15
- Six Months 3.00
- One Year, 52 Issues..... 6.00
- Add \$1.00 a Year to Foreign Postage; 50c for Canadian Postage.

LOUD SPEAKING CRYSTAL SET

Music heard all over room, and distant stations brought in on any type of crystal set with Steinmetz Amplifier. Get our complete Radio catalog. **STEINMETZ WIRELESS MFG. CO., 5752 Penn. Ave., Pittsburgh, Pa.**

CURE RE-RADIATION!

CLEAR THE AIR FOR RADIO

Why Raise Cain with Your Neighbor?

THE NEW


DK Radio Frequency Transformer
will do it—**BESIDES**

Increasing your Receiving Range tremendously—
Absolutely eliminating all Squeals and Howls—
Adding Selectivity, Clarity and Volume—
Enabling the use of a Loop.
The **DK RADIO FREQUENCY TRANSFORMER**
is small, compact and can be placed in any desired
position in your set. Anybody can add this indis-
pensable unit in a few moments.

PRICE \$4.50

If your dealer cannot supply you, send direct to
R. ROBINSON COMPANY

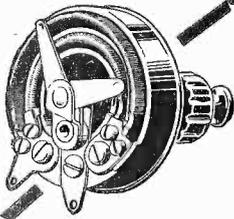83 Barclay St. (Tel. Barclay 7543), New York City
Dealers Write for Terms



**100%
EFFICIENCY**
From Your Tubes
with the
**PREMIER
"MICROSTAT"**
Trade-Mark
**SUPER-VERNIER
RHEOSTAT**

\$3.00
and worth it

There is no substitute for the Premier
"MICROSTAT"—no other instrument that gives
such perfect control of the current delivered to
the filament of radio tubes. New principle—two
windings in parallel; one 6 ohms, other 40 ohms.
Absolutely noiseless. Infinite control—handles any
tube. Capacity 3 amperes. Bakelite moulded—
silver etched dial. Do not install a rheostat until
you know all about the "MICROSTAT." Our
Bulletin No. 92 explains it in detail. Send for
it. It's FREE.

Ask for and Insist on "MICROSTAT" at your
dealer's.

Premier Electric Company

1805 Grace Street Chicago, Ill.

Back numbers of Radio World supplied
at regular price of 15c. a copy. Any 7
copies for \$1.00. Radio World, 1493
Broadway, New York.

WEAF Increases Its Power

WEAF'S development work in connection with the use of higher power has aroused the interest of radio listeners not only in the metropolitan area but throughout the eastern half of the United States, according to a statement issued by the American Telephone & Telegraph Co. It has long been realized by radio engineers who have studied the situation here that there can be no further improvement in broadcasting conditions, particularly as regards spark telegraph interference, unless it is possible to increase the power of New York broadcasting stations. Increased power results in greater volume; it reduces the ratio of telegraph and static interference as compared with the broadcast program. This improvement applies not only to expensive receiving sets but to the most modest equipment in operation. The owner of a crystal receiving set receives WEAF's program with much greater volume and is consequently much better able to enjoy the program. Those possessing vacuum tube sets with many stages of amplification are able to operate successfully with reduced amplification avoiding overloading of tubes and securing in consequence a much higher quality of reproduction. Sensitive receiving sets must, of course, be adapted by correct adjustments to receive properly under the new conditions. Audio-frequency amplifiers, if overloaded by signals of too great volume, do not reproduce as faithfully as they do when amplifying a current of normal volume.

Receiving sets located within a short distance of WEAF's transmitter or those not adapted to selective tuning may at first interfere with satisfactory reception of other local broadcasting stations. However, this is a condition which can certainly be corrected by simple adjustments of the receiving sets. It may be recalled that when two-channel broadcasting operation was first inaugurated last year on 360 and 400 meters, listeners were troubled by interference but by improvement of their sets now separate these two wave lengths without any difficulty. Similar difficulty was experienced when four-channel operation was undertaken in the metropolitan area.

An indication of the selectivity obtainable with suitable receiving apparatus is given by the fact that 600 meter watch is maintained
(Concluded on next page)

SLEEPER MONOTROL

Reg. U. S. Pat. Off.

Licensed under the Grimes Inverse Duplex Inventions. No aerial—no ground. Just one dial to turn. Perfect selectivity—no interference. The Monotrol will bring in more stations with better reception than any other set you have ever heard.

Booklet "W" on request.

SLEEPER RADIO CORPORATION
88 Park Place New York

Radios of the Better Class

Fada's Neutrodyne Sleeper's Monotrol
Complete Line
Parts Sets

LEDO RADIO CO.

5 Columbus Circle N. Y. City

1,000 MILES Guaranteed on Our New ONE TUBE RECEIVER

Complete with tube, phones, batteries, aerial, insulators, etc. Ready to work. Quantity limited. Send money order for shipment by return mail. Money back if you want it.

\$17.50

Send for Price List

NATIONAL RESERVE RADIO CO.
17-19 Bridge Street New York City

YOU SAVE 50% OF THE USUAL COST



WORLD RADIO

Batteries

Are Guaranteed
2 years in Writing
Will ship C. O. D.
subject to inspection,
or allow 5% discount
for cash with order.
Orders shipped same
day received. WRITE
TODAY.

World Battery Co.

Dept. 17

1218 So. Wabash Ave.

Chicago, Ill.

6 Volt, 100 Amps. \$12.50

6 Volt, 120 Amps. 14.50

6 Volt, 140 Amps. 16.00

2 VOLT STORAGE

BATTERY for

WD11 — WD12 \$5.00

6 V., 60 Amps. \$3.50

6 V., 80 Amps. 10.00

Before you forget it, send that check or money order for \$6.00 in to RADIO WORLD, 1493 Broadway, New York City, for your year's sub!

DO YOU WANT TO BUY, SELL OR EXCHANGE RADIO OR OTHER GOODS? TRY THIS
DEPARTMENT AT 5c A WORD

RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS

SHIELDED FORMICA PANELS six cents per square inch. Stops body capacity and howls. Write for prices on shielded cabinets. **KELLY RADIO NOISE ILLUMINATOR**, 5434 S Sawyer Ave., Chicago, Ill.

AN ORIGINAL TRANSCONTINENTAL HOOK-UP. A wonder for simplicity, cheapness and efficiency. One tube, one dry cell, one B battery. Send one dollar for blue print and detailed building instructions. Stillwater Radio Laboratory, Lock Box 13, Stillwater, N. Y.

"20TH CENTURY MIRACLE" 320-page Radio Instructor. Fully illustrated. \$1.25. Laine, 2428 Wilcox Street, Chicago, Ill.

EDISON ELEMENTS \$0.03 pair. New 6-volt batteries \$6.50. Magnet wire No. 20 \$0.35 pound. Radio Generator \$20.00. 824 North Fifth, Philadelphia, Pennsylvania.

USED BOOKS bought, sold and exchanged. List free. Ray McConnell, Ravenna, Nebraska.

IVORY RADIO PANEL: White pyralin ivory makes the most beautiful set of all. Guaranteed satisfactory. Any size 3/16 inch thick. Three cents per square inch. Sample sent. E. P. Haltom, 614 Main, Dept. W., Fort Worth, Texas.

INCREASE YOUR RANGE AND VOLUME by adding a Westinghouse 3-stage Radio Frequency Amplifier unit to your set. These units originally sold for \$80.00, but my special price is only \$43.00 while the supply lasts. All instruments are new and in original cartons. Can you afford to pass this up? N. E. Ristey, 251 West 95th Street, New York City.

LOWER PRICES on new tubes

Box 342, New Haven, Indiana.

EDISON ELEMENTS for building storage B batteries \$2.00 per hundred pairs. First grade elements only. Edison 300 ampere hour storage battery \$6.75. Cost \$40.00 new. All material F. O. B. Philadelphia. Mail orders filled. J. Zied, 530 Callowhill Street, Philadelphia, Pa.

RADIO FANS—Have some applause cards on your Radio Table, fill in the blank spaces as program comes in, and they are ready to mail: 12 for 25c, 28 for 50c, 60 for \$1.00. Sent prepaid, stamped, ready to mail. Satisfaction or money refunded. Address The Powell Radio Applause Card, Prescott, Ariz. Retail and wholesale.

VARIOCOUPLER AND VARIOMETERS silk wound including dial \$1.35; 3000 ohm headsets \$2.85; 3 plate condensers \$0.55; phone condensers \$0.10; contact points \$0.13 doz. Order from ad. Include postage. Everything guaranteed. Huth Radio Supply Co., 1280 Elm Street, Green Bay, Wisconsin.

SPECIAL—Two stage R. C. A audio amplifier \$20.00, original price \$45.00. This is an ideal instrument incorporating unusual features of design and workmanship. Includes special stabilizer control, eliminating distortion of speech and music. Supply is limited. N. E. Ristey, 251 West 95th Street, New York City.

DETECTIVES NEEDED EVERYWHERE. Excellent positions, cities, towns. Particulars free. **Captain Wagner**, 188 East 79th St., New York.

WANTED—Mail us your discarded jewelry, Gold Crowns and Bridges, Watches, Diamonds, Silver, Platinum, and Old magneto points. Money promptly mailed. Goods returned if offer refused. United States Smelting Works (The Old Reliable). Dent 55 Chicago

HOW TO RENEW DRY CELLS, 10 cents. Circulars mailed, 25 cents per 100; \$2.00 per 1,000. **UNIVERSAL MAILERS**, 650 Center, Waukegan, Ill.

BODY CAPACITY BOTHER YOU? The Stabulo circuit uses no shield. Gets distance, volume, tone. Result two years experimenting. Simple to make. Booklet, 50 cents cash. Charles R. Ladd, Bellows Falls, Vermont.

VACUUM TUBE RESULTS FROM A CRYSTAL SET! A "PT" Ultra-Sensitive Contact will increase the range and audibility of your crystal receiver. The most sensitive catwhisker in the world. It will not jar out. Thousands in use. Record, 1,000 miles on phone; 3,300 miles on spark. Price twenty-five cents in coin. "PT" CRYSTAL CONTACT COMPANY, Box 1641, Boston.

PATENTS—SEND DRAWING OR MODEL FOR EXAMINATION AND OPINION. Booklet free. Watson E. Coleman, Patent Lawyer, 644 G St., Washington, D. C.

AUDIO FREQUENCY TRANSFORMERS, REPUBLIC MAKE GUARANTEED. \$2.50 postpaid; circular on request. Flint Radio Co., 1766 Wilson Ave., Chicago, Ill.

PATENTS—Write for free Guide Books and Record of Invention Blank before disclosing inventions. Send model or sketch of your invention for our prompt Examination and Instructions. No charge for the above information. Radio, Electrical, Chemical, Mechanical and Trademark experts. Victor J. Evans & Co., 924 Ninth, Washington, D. C.

\$100.00 a week to agents. Box 732, New Britain,

WEAF Increases Power

(Concluded from preceding page)

within a few feet of WEAF's antenna. A short receiving antenna is employed which successfully eliminates WEAF so that reception of ship wave lengths is possible. If this can be done within 50' of the broadcasting station, the feat can be duplicated at greater distances.

One of the causes of difficulty which has frequently been noted is the use of antenna of too great lengths for local reception. A 100' outdoor antenna may be suitable for long distance reception while the local stations are not operating but it may be unsuitable for interference-free local reception.

PANELS

7x10...\$0.95	7x18...\$1.65	7x26...\$2.40
7x12... 1.10	7x21... 1.95	7x28... 2.60
7x14... 1.30	7x24... 2.25	7x30... 2.75
9x14... 1.75	9x18... 2.25	9x21... 2.50
12x14... 2.25	12x18... 3.00	12x21... 3.50

3/16" thick—BLACK—1/4" add 25%
Send money order or pay Postman.

UNION RADIO COMPANY

144 N. Union Street Akron, Ohio

RADIO BARGAINS

Pathe Moulded Variometers.....	\$1.98 each
Pathe Moulded Couplers.....	1.98 each
Air-Way Bakelite Couplers.....	89c each
Ajax Panel Type Combination Rheostat and Socket.....	1.49 each
Ace 23 plate Var. Condensers.....	79c each
Ace 43 plate Var. Condensers.....	89c each
C.O.D. Postage Extra.....	"Everything in Radio"

Write for new price list on REAL RADIO BARGAINS

ACE RADIO CO., 710-712 B'wy, Schenectady, N. Y.

SOME SUNBEAM SAVINGS

12 Years in the Same Spot.



From Wholesaler Direct to You.

SUNBEAM

Federal No. 65 Transformers.....	\$5.60
All-American Transformers.....	3.85
Cockaday Coils.....	1.85
Hercules 6 ohm Rheostats.....	.45
Music Master Loud Speaker.....	26.00
Brandes Table Talker.....	9.00
Federal Phones.....	4.95


FREE WITH EVERY ORDER. OUR HANDY RADIO RECORD BOOK

SUNBEAM ELECTRIC CO.

71 Third Avenue New York City

FAHNESTOCK'S


RADIO PRODUCTS

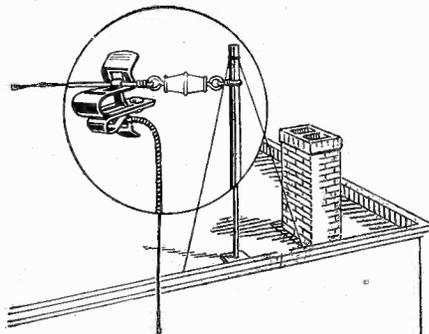

No. 31

The Antenna Connector

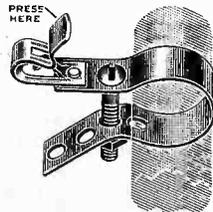Snap larger connector over Antenna Wire; insert Lead-in Wire into smaller clip and a perfect connection is the result.



Improved Ground Clamp

Equipped with Fahnestock Patent Wire Connectors. Easily Attached.

No Soldering—For Radio Use Only
Our name stamped on all products, none genuine without it.


At Your Dealers

FAHNESTOCK ELEC. CO.
LONG ISLAND CITY, NEW YORK

Marvelous New "Sun" Receiver Guaranteed Non-Regenerative


Most Important Development in Radio Reception in Three Years

(Patent Applied for)

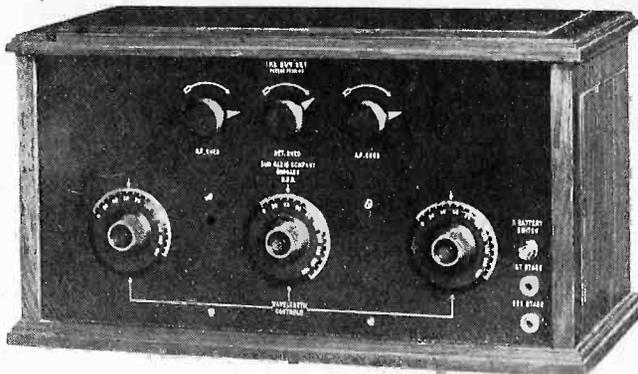

Phenomenally successful results through development of accurately balanced counter Electric Motive Force. Superior in range and selectivity to most 5 and 8 tube sets. Wonderful new principle brings in quality and volume of tone unequalled. Reproduces piano or the elusive notes of the soprano as faithfully as if the artist were in the room. Loud-speaker volume at long range surpasses local reception of other sets at any price. Entirely free from distortions, howls, squeals or hissing spill-overs common to other sets. There is no other set like the "Sun."

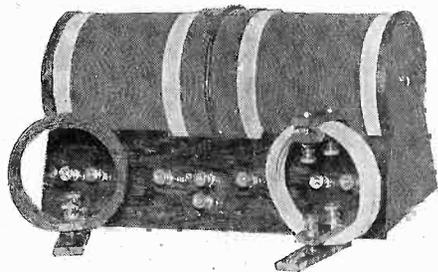With This "Sun" Tuner Unit and Standard Parts It Is Easy to Assemble a Genuine "Sun" Set.



Special "Sun" Tuner Unit, Including Sun Loading Coil and Sun R. F. Transformer,

Only \$24.00

We furnish complete list of parts required, easily understood wiring diagram and instructions for assembly so comprehensive that any one can understand and follow them. If you prefer to order a "Sun" Receiving Set, as illustrated, the price is \$150. Established dealers everywhere are prepared to furnish the "Sun" Tuner Unit at \$24.00, or completely assembled "Sun" Receiver Sets at \$150. (If your dealer cannot supply you, we will ship either complete "Sun" Receiver Set or "Sun" Tuner Unit direct on receipt of check or money order.)

SUN RADIO COMPANY

4884-90 North Clark Street

Chicago, U. S. A.



SUN
RADIO
COMPANY

DIALS
KNOBS
TUBING

MAHOGANITE
and BLACK
RADION PANELS

SOCKETS
MAHOGANITE
BINDING
POSTS

ALL STOCK SIZES, Also CUT TO ANY SPECIAL SIZE

HARD RUBBER PANELS (H-R. Grade) ALWAYS IN STOCK

WHOLESALE

Send for Our Complete Price List.

RETAIL

N. Y. HARD RUBBER TURNING CO.

212R CENTRE STREET

Telephone: Canal 8315

NEW YORK, N. Y.

NOW \$25 FOR \$10

BEL-CANTO LOUD SPEAKER
Delivered Direct from Factory to You on receipt of only \$10.

BEL-CANTO MFG. CO., INC.

Bensel-Bonis Co., Inc. Tel. Vanderbilt 8959
417 E. 34th ST. NEW YORK CITY

The Ultimate Radio Receiver

THE FLEX-O-DYNE CO.

1674 Broadway (At 52nd St.)
New York, N. Y.

Circle 4569

For Better Radio Reception

FRESHMAN PRODUCTS

GUARANTEED:—to be mechanically perfect, scientifically accurate and built for unusual durability. Used by discriminating manufacturers and amateurs all over the world, who realize that a radio set is only as good as each individual part.

The Standard Unit for Every Tube Set


FRESHMAN Variable Grid Leak and Condenser Combined



Permits you to adjust your circuit to any resistance you wish from zero to 10 megohms, in an unbroken range of 180 degrees. It takes the place of a grid condenser, grid leak mounting and grid leak, and, in addition permits an adjustment to the correct amount of resistance. It is the most compact, the most efficient, the most adaptable to all grid circuits, and the only one which is entirely sealed and always remains unaffected by any climatic conditions.

Base on Panel Type complete with
.00025 or .0005 Freshman Condenser. **\$1**
Either type without condenser, \$.75

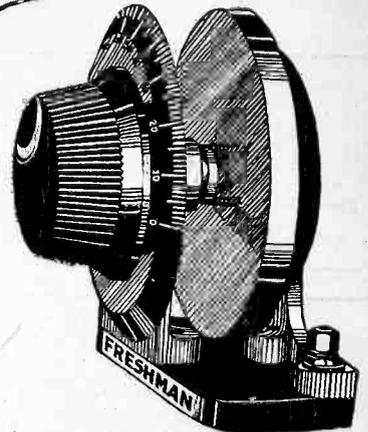"Freshman Selective" Mercury Variable Condenser for Transmission or Reception




It is the only variable condenser the plates of which vary in area—AN ENGINEERING FEAT NEVER ACCOMPLISHED BEFORE—making it most efficient for fine adjustment and selective tuning.

The "Freshman Selective" is attractively compact, quiet in operation and will withstand 5,000 volts without leakage or danger of short circuiting.

.0003 MF (Equiv. to 17 plate) **\$5**
.0005 MF (Equiv. to 23 plate) **EACH**
.0001 MF (Equiv. to 43 plate)

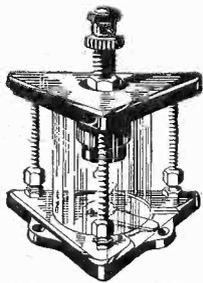All molded parts
and dial of finest
Bakelite.



Double Adjustable Freshman Crystal Detector

for base or panel mounting. When mounted on panel only the knob shows on the front. No more searching for the sensitive spot. Merely turn the knob as you would a dial thus adjusting the crystal instead of the cats-whisker. Best for both Reflex and Crystal sets.

Price
\$1.50

Guaranteed Capacities



Capacity	Each
.00005	\$.035
.0001	.35
.00015	.35
.0002	.35
.00025	.35

The Condenser Sensation of Modern Radio FRESHMAN Noiseless Tested Mica Condensers

Every Condenser is individually tested on high voltage for capacity, breakdown and leakage. Every piece of Mica embodied in the Condenser is individually tested and examined.

The new style No. 101 is equipped with Freshman Soldering Terminals which allow 3 distinct connections with a very small amount of solder.

Capacity	Each
.0003	\$.035
.00035	.35
.0005	.35
.0006	.40
.0008	.40

Capacity	Each
.001	\$.040
.0015	.40
.002	.40
.0025	.50
.003	.60

Capacity	Each
.0035	\$.070
.004	.75
.005	.75
.006	.75
.007	1.00



Capacity	Each
.008	\$.100
.009	1.00
.01	1.00
.015	1.50

FRESHMAN VERNIER DIAL



A Bakelite dial with Vernier adjustment. A small rubber tired wheel through the slot in the dial permits you to set the dial to the exact point and obtain the same dial setting every time. Just the thing for Neutrodyne and Heterodyne.

Price, 3 in. \$1.00
Price, 4 in. \$1.50

At your dealers, otherwise send purchase price and you will be supplied prepaid.

No Outside Wires Needed

ANTENELLA
attached to any lighting socket eliminates the inconveniences in radio, such as unsightly outdoor aerials, insulators, lightning arresters, lead-ins, etc.



ANTENELLA
It is not only a real distance getter, but also overcomes static annoyances. The complete and efficient aerial, **ANTENELLA**. Price only.....\$1.25



Freshman Fix-O A Fixed Grid Leak Combination 4 in 1

Freshman Condenser .00025
Leak Mounting
Freshman Grid Leak
Safe-T Handle } **65c**
Price Complete

Furnished in any value of resistance from 1/20 to 10 megohms.

Ask your dealer or write for our free diagrams of Neutrodyne, Tri-Flex, Kaufman and other circuits

Chas. Freshman Co. Inc. Radio Condenser Products

106 Seventh Avenue
New York City