

Sept. 12

1925

# SHOW NUMBER

15 Cents

# RADIO WORLD


Title Reg. U.S. Pat. Off

Vol. 7. No. 25. ILLUSTRATED Every Week

155-181

## THE 1926 DIAMOND

By HERMAN BERNARD

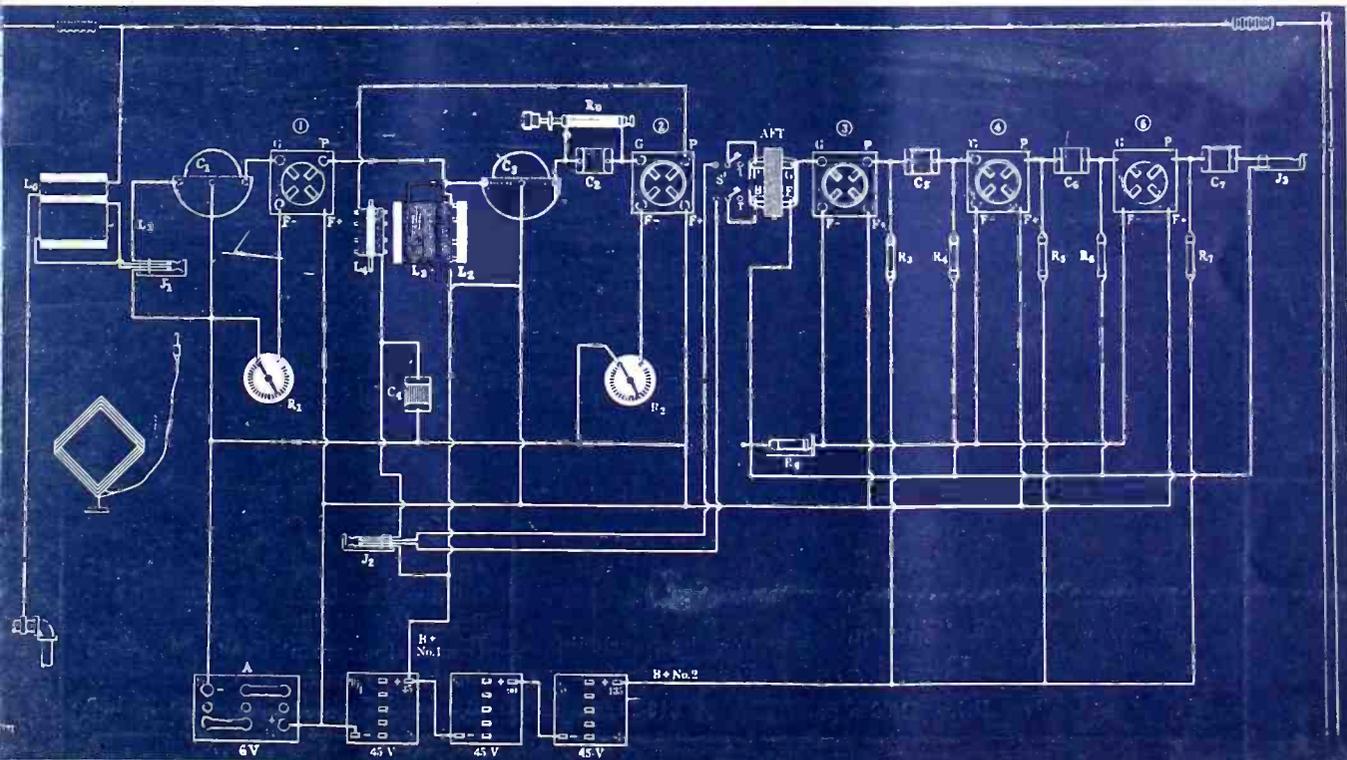

RADIO WORLD'S most popular circuit, The Diamond of the Air, shown in blueprint form. This is the 1926 model, embodying the Bernard audio amplifier. See page 5 for article on construction of this receiver.

Herman Bernard's  
Triumph



# The 1926 Model DIAMOND OF THE AIR

## WITH THE BERNARD AUDIO HOOKUP

We have just made a happy purchase of a large quantity of the VENUS STRAIGHT LINE FREQUENCY condensers and we are able to present them to our patrons at the remarkably low prices listed below.



Straight line frequency condensers will separate the lower wave stations and give the broadcast listeners the benefit of the lower wave programs.

.00025, \$1.95—.00035, \$2.10—.0005, \$2.25

This List of Parts is Indorsed and Certified by the Author

One Bruno No. 99 R.F. Transformer, L&L.  
One Bruno No. 99 3-circuit tuner, L&L.  
Two .0005 mfd. Bruno No. 16 variable condensers, C1, C3.  
Two Bruno 20 ohm rheostats, R1, R2.  
One Bretwood variable grid leak, R3.  
Two double-circuit jacks, J1, J2.  
One single-circuit jack, J3.  
One Federal No. 65 AFT.  
Fixed condensers: One .00025 mfd. grid condenser, without clips, C2; one .001 mfd., C4; three 0.25 mfd., C5, C6, C7.  
One 1/2-ampere ballast resistor, R4.  
One double-throw, double-pole switch, S1.  
One A battery switch, S2.  
Two Vebby leaks, R4, 1.0 meg; R4, 6.5 meg.  
Three 6.1 meg. Vebby resistors, R3, R5, R7.  
One Bruno 5-gang socket shell.  
Five sockets.  
One pair of Bruno brackets.  
Three vernier dials.  
One 7" x 24" drilled and engraved panel.  
One set of binding posts.

**\$39.50**

## The New R. C. A. UX Tubes in Stock

Listen-in on McMillan  
with  
Sidney E. Finkelstein's  
25-110 Meter  
Short Wave Receiver  
Construction fully described in  
this issue.



COMPLETE KIT CONSISTING OF  
One short-wave 3-circuit coupler, L1L2L3.  
One .00025 mfd. S.I.F. variable condenser, C1.  
One .00025 mfd. fixed condenser, C2.  
One .005 mfd. fixed condenser, C3.  
One 2-meg. grid leak, R1.  
One 20-ohm rheostat, R2.  
One 20-ohm rheostat, R3.  
One 6.1 meg. Vebby resistor, R3.  
One 1.0 meg. Vebby resistor (leak), R4.  
One push-pull switch, S.  
One single-circuit jack, J.  
Two sockets.  
One socket strip.  
One panel, 7" x 19", drilled.  
Two 3" dials.

**\$12.95**



Improve the  
Appearance of  
Your Set  
with  
"Bruno"  
Brackets  
Price, \$1.00 a pair

Bernard's  
Audio Hookup  
Kit

Complete, including  
Federal Transformer  
\$10.50

### Compare Our Specials

Amperites .....	\$0.95
Dubilier Duratran .....	2.25
Bruno Journal Filter Coils .....	2.25
General Instrument Cond .....	2.95
Amertran Transformers .....	3.85
Bretwood Variable Grid Leaks .....	1.50

# B-C-L RADIO SERVICE CO.

220 FULTON STREET  
NEW YORK

Write in for  
Free  
Catalogue

# new ULTRADYNE

## MODEL L-3



To protect the public, Mr. Lecault's personal monogram seal (R. E. L.) is placed on the assembly lock bolts of all genuine Ultradyne Model L-3 Receivers. All Ultradynes are guaranteed as long as their seals remain unbroken.



### No Dials-No Panel Built-in Loud Speaker

IF the Ultradyne Model L-3 were merely another new receiver, its influence in the industry would be little felt.

But it is in reality the first step in the general revision of radio receiver design which is bound to follow its advent.

For the new Ultradyne Model L-3, is an entirely new type of receiver—radically different in appearance and method of operation—gives finer results from finer engineering. Employs six tubes—is completely assembled and wired, ready for the tubes and batteries.

It has no dials—no panel—no needless controls. Two levers, an exclusive Ultradyne feature, give you control of the entire broadcast program. Its operation is practically automatic—simply slide the pointer to the station you want and adjust the volume control, soft or loud as you like it.

Loud Speaker and "B" Batteries self enclosed in a beautiful cabinet that is far from mechanical in design and is an ideal mahogany furniture piece for the most charming home.

This new Ultradyne Model L-3 gives you the best there is in radio—truer reproduction than you have ever known before.

**PHENIX RADIO CORPORATION** 116-F East 25th Street  
New York

Ask your dealer for a demonstration. The contrast between the Ultradyne and other receivers is so marked that the desire to own one will be bred there and then.

# \$135

Write for descriptive folder <sup>®</sup>





Five Tubes, Tuned Radio Frequency

**RELY UPON EXPERIENCE TO PRODUCE QUALITY AT LOW COST**

**Sleeper**  
1888

REG. U. S. PAT. OFF.

**RADIO RECEIVING SETS**

—are better built of better materials to the most exacting specifications by an organization that has engaged exclusively in the manufacture of fine radio equipment since 1919.

**Super  
RADIO  
Reception**

Only experience and "pride of product" could have built such a set as the Serenader at so low a cost. For this is a new kind of radio set. Not until now has a receiver combined such tonal quality with such volume, selectivity and sensitivity. Your first twenty minutes with the Serenader will give you a wholly new conception of radio reception.

**T**URN the switch and the softened glow of the concealed visored lights illuminate the tuning controls. Move the silver pointers to the designated wave length of your favorite station and you will hear it loud and clear, as distinctly and as naturally as though the artist were at your side—then, and only then, you will realize what Super Radio Reception means.

Other Sleeper models:

The Scout, \$75.00. The Monotrol, \$130.00.  
The Super-Symphonic, \$150.00.



Serenader with console table, \$135.00

The table has a compartment for "A" battery and one for charger with switch for instantaneous change to charger. A better, more convenient radio installation at a remarkably low price.

If the Authorized Sleeper Dealer in your community has not yet received his quota, write us for descriptive literature and catalogue "W."

**SLEEPER RADIO CORPORATION**

438 WASHINGTON AVENUE,

LONG ISLAND CITY, NEW YORK

# RADIO WORLD

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under the act of March 3, 1879]

A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawanna 6976 and 2063

Vol. VII. No. 25. Whole No. 181.

September 12, 1925

15c per copy, \$6.00 a year

## The 1926 Model Diamond

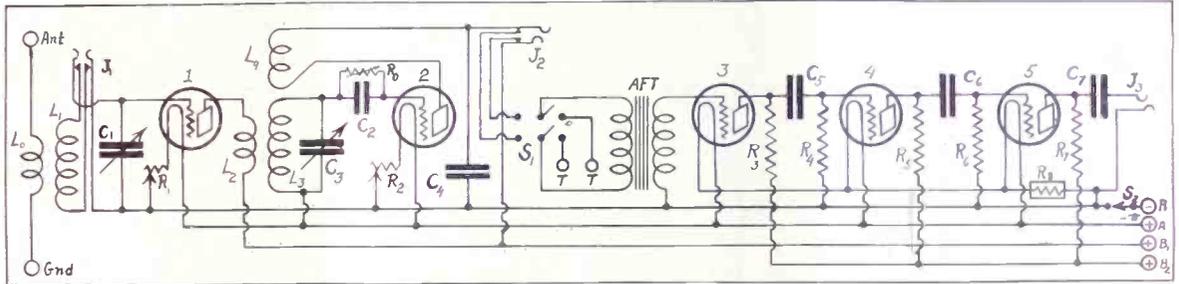


FIG. 1, the wiring diagram of the 1926 Model Diamond of the Air. The improvement is exclusively in the audio circuit and the greater possibilities of using it. The double-pole double-throw switch enables use of the audio hook-up in conjunction with any other set or detector test circuit. The AF consists of one transformer stage and two resistance steps. A novelty exists in the speaker connections, one speaker tip going to A—, the other to one side of a large condenser. This is a quality asset.

By Herman Bernard

Associate, Institute of Radio Engineers

PART I

IT is five months since The Diamond of the Air was first presented to the public. It represented the most that was obtainable from four tubes. The radio-frequency side included a stage of tuned RF and a regenerative detector using a tickler coil. There is nothing I can suggest that would improve the fundamental RF hookup, hence it is the same now as then. A bypass condenser is omitted, because after many tests it was found to be unnecessary. A separate rheostat is now included in the detector tube, instead of hooking up that filament with the audio stages, because the detector may be operated at a lower filament voltage, hence A battery saving is accomplished, but not much.

The improvement lies in the audio circuit, where instead of the two transformer-coupled steps previously used, there now appear one transformer and two resistance stages, with a special manner of connecting the speaker so that virtually no B battery current will flow in it. This accomplishes something worthwhile, provided the condenser C7 is large enough. The difference is particularly notable when the sensitive cone type of speaker is used.

The audio hookup also takes care of the question of grid bias, ignored in most resistance-coupled audio stages when they reach the final tube. If the same B battery voltage is applied to the battery side of the plate resistors, R3 and R5, as at the plate of the last tube, then the actual B battery voltage at the final plate may be twice as high as in the previous resistance steps. This would require a C bat-

tery for proper bias of the grid of the last tube to achieve the efficient and economical point, and also cut down distortion. The resistor R7, which is the same as the other plate resistors, serves to bring the same voltage to the final plate and dispenses with a biasing battery.

The quality of the received signal will be excellent indeed, even better than that obtainable from two stages where transformers of the very best make are used. Such transformers must necessarily have large windings and be otherwise than very cheap in price. The one transformer used, however, must be among the best, otherwise the attempt to approach perfection in audio amplification is in vain. Federal No. 65, General Radio No. 285, Rauland Lyric, Stromberg-Carlson or other good make should be embodied.


A novelty included in the circuit is a double-pole double-throw switch. As the set is to be made by radio experimenters, naturally they represent a class that is always dabbling in hookups, frequently making detector circuits that they would like an easy opportunity to hear on a speaker. If the audio hookup is so wired (Fig. 1) that a test set may be easily hooked up to it, so much the better. I was much disinclined to remove the plate connections of an audio hookup in a completed set just to make such test, hence had to go build an audio amplifier especially for that single experiment.

Many may desire to compare the audio hookup (Fig. 1) with some other they

have on hand or may construct. That may be done with ease by connecting the output of the test receiver to a plug, pushing this into the jack J2. The DPDT switch would be set to include, then to exclude, the AF of The Diamond. These comparisons I invite, for I have made them myself and I rest on the hookup as shown in Fig. 1.

The DPDT switch may be mounted on the baseboard or, if a socket shelf is used, may be placed thereon, to keep it off the panel. The lid of the cabinet would be lifted and the switch thrown to the desired position. As this would not be done often there is no necessity for placing the switch on the panel. Besides, it might not look like very much there.

There are three controls on the panel (Fig. 2), because they are necessary for maximum efficiency. Under no circumstances can the number of controls actually be reduced and yet provide better reception. All methods of control reduction, excepting possibly the double condenser method, if that is properly handled, seem to require some compensating device, either an extra little variable condenser, or some other part with an adjustable function. Then the number of controls really remains the same. The only change is that a major control is reduced to a minor one. If a double condenser is used, provided one of the stages is not required to tune too sharply, and the condenser is of excellent workmanship, real reduction of condenser-tuned controls

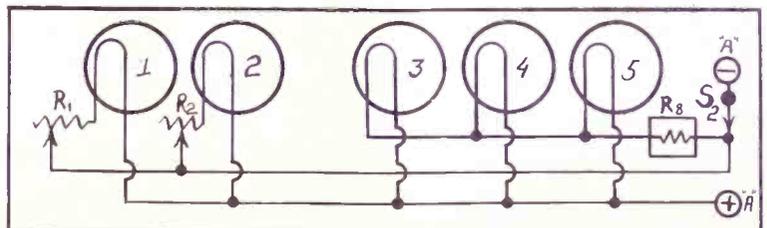

DETAIL of the filament wiring of the 1926 Model Diamond of the Air.



Five Tubes, Tuned Radio Frequency

RELY UPON EXPERIENCE TO PRODUCE QUALITY AT LOW COST

**Sleeper**

REG. U. S. PAT. OFF.

**RADIO RECEIVING SETS**

—are better built of better materials to the most exacting specifications by an organization that has engaged exclusively in the manufacture of fine radio equipment since 1919.

*Super*  
**RADIO**  
*Reception*

Only experience and "pride of product" could have built such a set as the Serenader at so low a cost. For this is a new kind of radio set. Not until now has a receiver combined such tonal quality with such volume, selectivity and sensitivity. Your first twenty minutes with the Serenader will give you a wholly new conception of radio reception.

**T**URN the switch and the softened glow of the concealed visored lights illuminate the tuning controls. Move the silver pointers to the designated wave length of your favorite station and you will hear it loud and clear, as distinctly and as naturally as though the artist were at your side—then, and only then, you will realize what Super Radio Reception means.

Other Sleeper models:

The Scout, \$75.00. The Monotrol, \$130.00.  
The Super-Symphonic, \$150.00.



Serenader with console table, \$135.00

The table has a compartment for "A" battery and one for charger with switch for instantaneous change to charger. A better, more convenient radio installation at a remarkably low price.

If the Authorized Sleeper Dealer in your community has not yet received his quota, write us for descriptive literature and catalogue "W."

**SLEEPER RADIO CORPORATION**

438 WASHINGTON AVENUE,

LONG ISLAND CITY, NEW YORK

# RADIO WORLD

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under the act of March 3, 1879]

A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawanna 6976 and 2063

Vol. VII. No. 25. Whole No. 181.

September 12, 1925

15c per copy, \$6.00 a year

## The 1926 Model Diamond

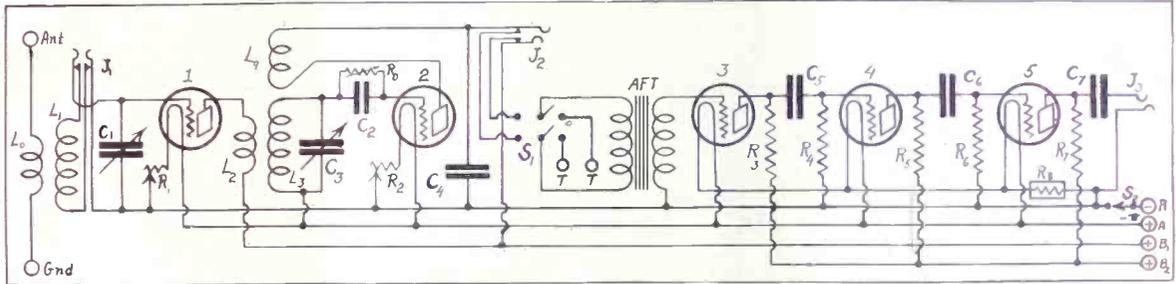


FIG. 1, the wiring diagram of the 1926 Model Diamond of the Air. The improvement is exclusively in the audio circuit and the greater possibilities of using it. The double-pole double-throw switch enables use of the audio hook-up in conjunction with any other set or detector test circuit. The AF consists of one transformer stage and two resistance steps. A novelty exists in the speaker connections, one speaker tip going to A—, the other to one side of a large condenser. This is a quality asset.

By Herman Bernard

Associate, Institute of Radio Engineers

PART I

IT is five months since The Diamond of the Air was first presented to the public. It represented the most that was obtainable from four tubes. The radio-frequency side included a stage of tuned RF and a regenerative detector using a tickler coil. There is nothing I can suggest that would improve the fundamental RF hookup, hence it is the same now as then. A bypass condenser is omitted, because after many tests it was found to be unnecessary. A separate rheostat is now included in the detector tube, instead of hooking up that filament with the audio stages, because the detector may be operated at a lower filament voltage, hence A battery saving is accomplished, but not much.

The improvement lies in the audio circuit, where instead of the two transformer-coupled steps previously used, there now appear one transformer and two resistance stages, with a special manner of connecting the speaker so that virtually no B battery current will flow in it. This accomplishes something worthwhile, provided the condenser C7 is large enough. The difference is particularly notable when the sensitive cone type of speaker is used.

The audio hookup also takes care of the question of grid bias, ignored in most resistance-coupled audio stages when they reach the final tube. If the same B battery voltage is applied to the battery side of the plate resistors, R3 and R5, as at the plate of the last tube, then the actual B battery voltage at the final plate may be twice as high as in the previous resistance steps. This would require a C bat-

tery for proper bias of the grid of the last tube to achieve the efficient and economical point, and also cut down distortion. The resistor R7, which is the same as the other plate resistors, serves to bring the same voltage to the final plate and dispenses with a biasing battery.

The quality of the received signal will be excellent indeed, even better than that obtainable from two stages where transformers of the very best make are used. Such transformers must necessarily have large windings and be otherwise than very cheap in price. The one transformer used, however, must be among the best, otherwise the attempt to approach perfection in audio amplification is in vain. Federal No. 65, General Radio No. 285, Rauland Lyric, Stromberg-Carlson or other good make should be embodied.

A novelty included in the circuit is a double-pole double-throw switch. As the set is to be made by radio experimenters, naturally they represent a class that is always dabbling in hookups, frequently making detector circuits that they would like an easy opportunity to hear on a speaker. If the audio hookup is so wired (Fig. 1) that a test set may be easily hooked up to it, so much the better. I was much disinclined to remove the plate connections of an audio hookup in a completed set just to make such test, hence had to go build an audio amplifier especially for that single experiment.

Many may desire to compare the audio hookup (Fig. 1) with some other they


have on hand or may construct. That may be done with ease by connecting the output of the test receiver to a plug, pushing this into the jack J2. The DPDT switch would be set to include, then to exclude, the AF of The Diamond. These comparisons I invite, for I have made them myself and I rest on the hookup as shown in Fig. 1.

The DPDT switch may be mounted on the baseboard or, if a socket shelf is used, may be placed thereon, to keep it off the panel. The lid of the cabinet would be lifted and the switch thrown to the desired position. As this would not be done often there is no necessity for placing the switch on the panel. Besides, it might not look like very much there.

There are three controls on the panel (Fig. 2), because they are necessary for maximum efficiency. Under no circumstances can the number of controls actually be reduced and yet provide better reception. All methods of control reduction, excepting possibly the double condenser method, if that is properly handled, seem to require some compensating device, either an extra little variable condenser, or some other part with an adjustable function. Then the number of controls really remains the same. The only change is that a major control is reduced to a minor one. If a double condenser is used, provided one of the stages is not required to tune too sharply, and the condenser is of excellent workmanship, real reduction of condenser-tuned controls



Herman Bernard

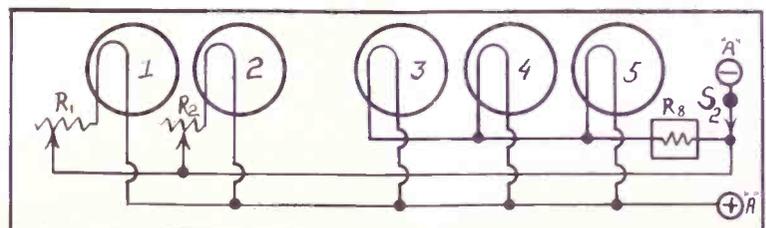

DETAIL of the filament wiring of the 1926 Model Diamond of the Air.



# A Low-Loss Skeleton Coil

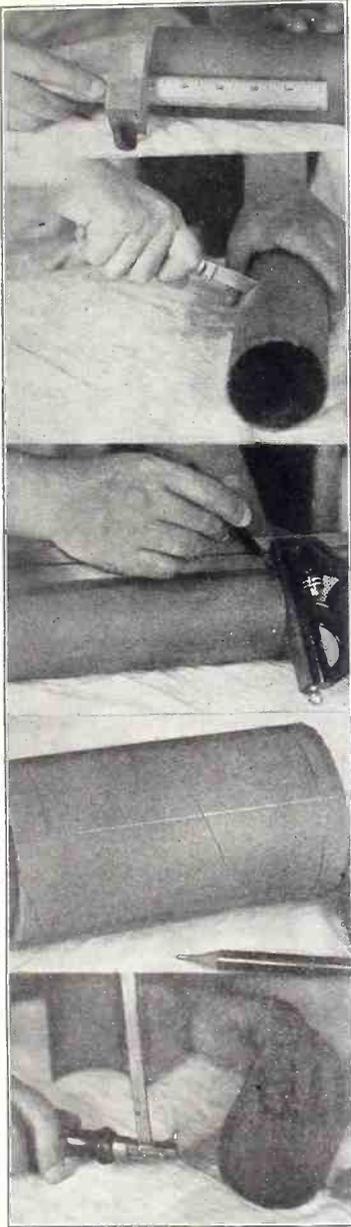


FIG. 1 (top), get a piece of cardboard tubing,  $3\frac{1}{2}$ " diameter, 6" long or so. Fig. 2 (third from top), a straight line is drawn down the tubing and another line diametrically opposite. Fig. 3. (third from top), two other lines are marked  $\frac{1}{2}$ " from the natural circumference and from the scratched one. Fig. 4 (second from top), cut the tubing at the drawn circumference 5" from the other one. Fig. 5 (bottom) shows how a scroll saw may be used rather than a knife. L.

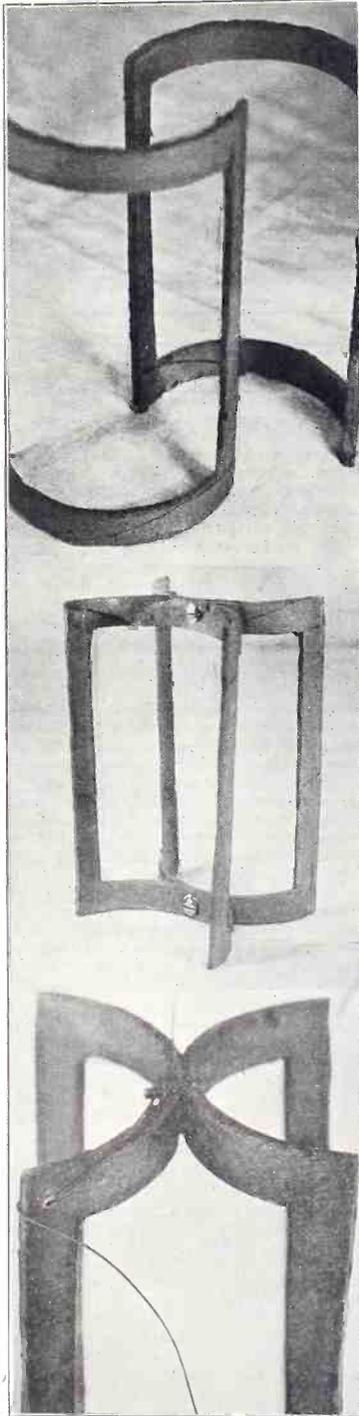


FIG. 6 (top), the two pieces after the tubing has been cut. Fig. 7, reverse the halves and fasten together. Fig. 8, secure the magnet wire (No. 22 DSC) as shown.

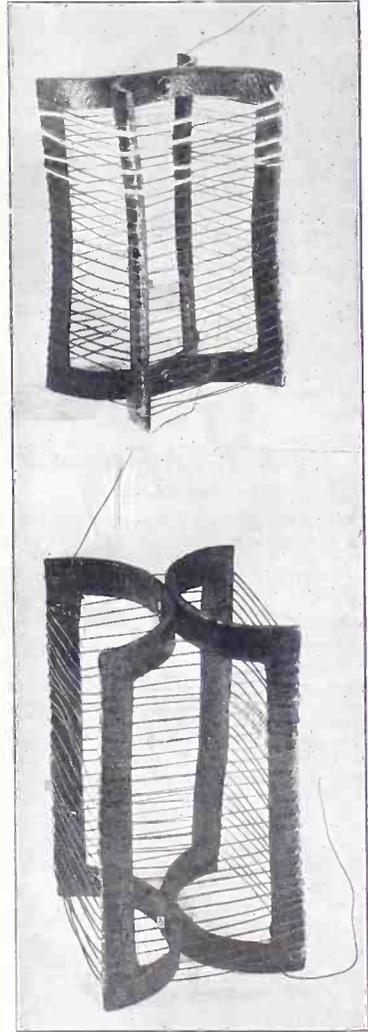


FIG. 9 (top) shows an RF transformer, 4 turns No. 18 DCC wire for primary, 25 turns No. 22 DSC wire for secondary. Fig. 10 is an impedance coil. (Hayden Photos)

smaller condensers use more turns. This type of coil is excellent where selectivity is desired and also helps a trifle to spread out the lower wave stations on the dial.

A LOW-LOSS coil, space wound for reduction of distributed capacity, may be made in skeleton style by cutting up a cardboard tubing as illustrated. The diameter used was  $3\frac{1}{2}$ ", but less may be employed, even to  $1\frac{1}{2}$ ", since the reversed method of securing the cut forms gives a much larger resulting diameter. If smaller diameters than  $3\frac{1}{2}$ " are used

originally, put on more wire. The coil may be a radio-frequency transformer (Fig. 9) or an impedance coil (Fig. 10). The impedance coil would do nicely to tune a plate circuit. The inductances as described, with 25-turn secondaries, require a .0005 mfd. tuning condenser. For

## One Thing We Don't Do

Service Is Our Motto





# Powertone Trouble-Shooting

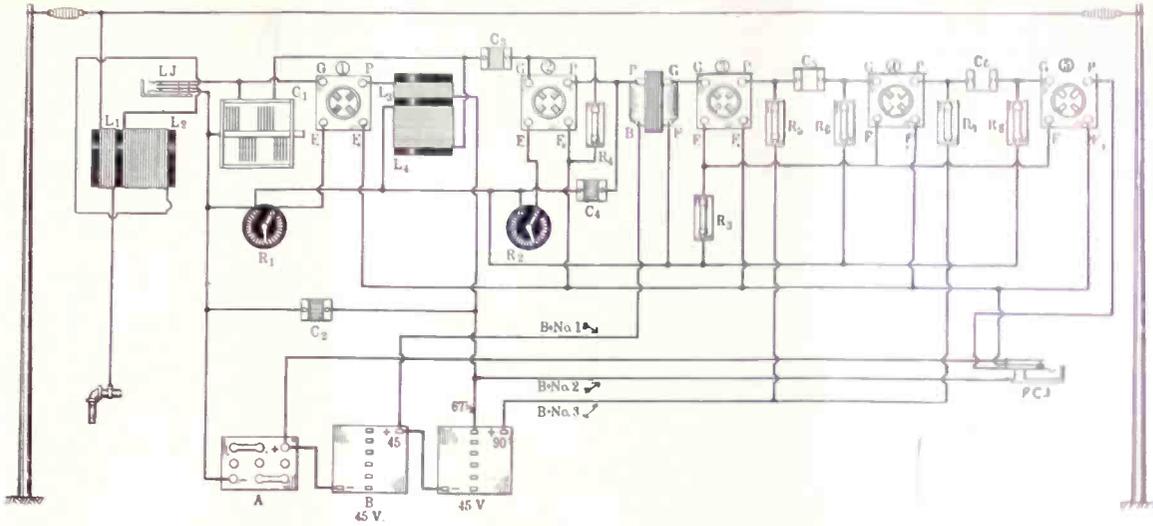


FIG. 1, the wiring diagram of The Powertone in picture form. The coils L1L2 and L3L4 are wound in the same direction. If a 2 3/4" diameter is used, with No. 24 silk covered cotton wire, then 10 turn primaries and 49-turn secondaries may be employed, with a double condenser of .0005 mfd. capacity in each section. The range covered is 180 to 555 meters. R1 and R2 are 20-ohm rheostats, R3 a 3/4-ampere ballast resistor. LJ is the loop jack, a double-circuit affair, while FCJ is the filament control jack. R4 is a grid leak, C3 a grid condenser. R5 and R7 are 100,000 ohms each, R6 is 1.0 meg. and R8 is 0.5 meg. B plus No. 1 is exclusively for the detector plate. B plus No. 2 is for the RF plate and the final audio plate, while B plus No. 3 goes to the first and second audio plates. More than 9 volts, even up to 180, could be used for the B plus No. 3 lead with a possibility of volume increase.

By Herbert E. Hayden

FOR proper functioning of a receiver that has only one stage of tuned radio-frequency amplification ahead of a non-regenerative tube detector it is necessary to have the RF tube very sensitive. Otherwise the desired selectivity may be lacking and volume as well. The achievement of the correct condition is simple. The only requirements are that you have a readily oscillating RF tube and that you use sufficient plate voltage thereon. It is assumed that the set is correctly wired and that coil terminals are connected with due respect to the advantages of proper polarities. These matters, too, I will discuss in this article.

From the trouble-shooting viewpoint it is surprising how great a difference in performance will result from the observance of the rules. As the set has only one control, C1, a double condenser which tunes both secondaries with one motion, the most likely sources of trouble would be:

- (1) Failure of synchronization on the dial setting.
  - (2) A slight failure of selectivity.
  - (3) Not quite enough volume.
- But when the set is working properly the volume will be great, the selectivity all that it need be, and the synchronization very good.

### The Plate Voltage

The more B battery voltage applied to the plate of the RF tube, the greater the oscillating tendency of the tube, until it reaches a saturation point, when the tube will take on a semblance of paralysis, due to excessive B voltage. This point affects both synchronization failure, selectivity and volume, since an inefficient RF stage makes one section of the condenser tune very broadly and puts almost the whole

selectivity burden on the section tuning the detector input.

Therefore the diagram, Fig. 1, is especially helpful, in that it shows how one B plus lead is common to the RF plate and to the final audio output. If greater B battery voltage than 67 1/2 is necessary to induce oscillation in the RF tube it may be obtained by tapping at a higher voltage post. Likewise, if there is over-oscillation less B voltage may be tried.

### The Oscillation Control

The rheostat R1 will control oscillations satisfactorily not only because of the variation in filament heating but also on account of the varied grid bias. There is about 1 volt maximum negative bias on the RF grid, due to the grid being connected to minus A, which is 6, and the negative filament being minus 5, 1 volt being dropped in the rheostat, energy dissipated in the form in heat. As all reckoning must be from minus filament, the difference is 1 volt, the maximum negative bias. This is obtained only when the full volt is dropped, which is true usually when the rheostat is turned up 1/4 of the way, a point that must be reached, anyway, to light the tube sufficiently.

The detector tube also plays a part in this oscillation control, under some conditions. The detector tube should be lighted only to a brilliancy that enables one to get oscillation on the higher waves. Usually the detector tube may be left that way and only the RF rheostat manipulated. However, once in a while it will be found that local stations come in with too great volume and rattle the speaker. One may turn the RF rheostat lower, but still some trace of a rattle may persist, that is, there is still excessive volume. The detector tube may not respond properly if turned lower, because only greater oscillation would be induced. The solution, obviously, is to turn the detector rheostat up, burning that tube more brightly. But when one returns to normal reception, embodying stations that do not come in with tremendous power, the detector rheostat should assume its previous condition. The example cited is

a rarity, of course, but the situation should be understood so that if the problem arises the solution is at hand.

The RF rheostat is also a volume control, since the proper tube condition, just below the saturation or over-oscillating point, governs volume as well as selectivity.

### The Synchronization Problem

There is one more reason that may defeat synchronization, which means the representation of the same wavelength or frequency by the same dial setting. If the coils are not properly matched, then one may expect that some stations will come in at two different dial settings, infrequently at the upper readings, but more particularly on the lower wavelengths. It is usually easy to determine which secondary is "off" because that point where the signal comes in louder will represent the interstage secondary, L4, since it is the detector input. Therefore suppose a station is heard at 15 on the dial and also at 17, the 17 setting being louder. The natural period of the L2C1 combination therefore is higher than that of L4C1. Whatever coil represents a higher dial reading has a lower inductance, let us say, because it requires greater capacity, i.e., higher dial setting, to reach the same wavelength. Hence if the detector requires 17 and the RF only 15, the higher setting indicates a deficiency in inductive value for L4. The system of reckoning is therefore reverse. If the number is too high the coil is too low.

The difficulty often may be solved even without touching the secondaries. Much depends on the separation between primary and secondary in the RF coil. If L1 and L2 are 1/4" apart, and it is found that the louder signal (detector) comes in at a lower reading than the other, then increase the separation. The closer L1 is to L2 the greater contribution of the aerial antenna system's capacity to the secondary L2. Very tight coupling has the effect of introducing much of the antenna capacity in parallel with L2, while L1 may be moved sufficiently far away to preserve independence of L2 in respect to the antenna capacity. But the separation



HERBERT E. HAYDEN

# Efficiency of Powertone Is Lauded by Hayden

must not be so great that instability will result or that volume will drop, due to insufficient transfer of energy from L1 to L2. The apparent resistance of the antenna system is helpful in introducing a stabilizing element, for it is theoretically possible to create feedback to such a marked degree that even a negative resistance results. A certain amount of resistance is necessary in every set and it is foolhardy to go below that practical minimum. The instability factor need not be expected to arise in this receiver. The separation may safely be varied from  $\frac{1}{4}$ " to 1", or even  $1\frac{1}{2}$ " under excellent antenna conditions.

Also, one may reduce turns on the coil that has too great a period, that is, the coil that shows up as requiring the lower dial setting. Remove half a turn at a time. Either of these two methods should work, and if not, use both methods.

Suppose that the trouble is not remedied even yet. The trouble then will lie in the tuning condenser. If it is a precision instrument the capacity variations will be varied in step with all-sufficient exactness. If you have a condenser defective in that there is a lead and lag as between respective sections, the remedy would be the connection of a midjet variable condenser, one side of that tiny instrument going to one of the stators and the other side to the remaining stator of the two-section tuning condenser C1. The setting of the midjet instrument would be varied until synchronization results. The midjet condenser method is a sheer makeshift to avoid purchasing another tuning condenser. If you bought wisely and well in the first instance the other methods would solve your problem.

## The Polarity Question

The discussion up to this point covers the three classifications: synchronization, selectivity and volume. It was assumed that the set was wired correctly, including polarity orthodoxy. Fig. 1 shows the correct coil terminal connections. Aerial goes to beginning of L1, ground to the end of L1, while the terminal of L2 that adjoins the ground side of L1 goes to the jack lead that joins to minus A, the remaining secondary connection being made to the jack spring that connects to the RF grid. Hence the potential sources or "high" sides of each coil (aerial and grid) are as far apart as possible, to avoid leakage loss, while the low potentials, ground and battery, are side by side. Batteries always are "low" potential. In this case the coils are all wound in the same direction and this refers also to L3L4. If the primary L1 were reversed would a different condition would exist, but the unidirectional method of winding, with connections making up for the resulting phase change, is simpler. The interstage coupler is connected with the beginning of L3 to plate, the end of L3 to B plus, the terminal of L4 adjoining the battery connection to L3 going to A minus and the remaining end of L4 to one side of the grid condenser. This method is in keeping with that employed in the case of L1L2. The low loss potentials, both batteries, are together, while the potential sources or "high" sides of the coils, plate and grid, are as far apart as possible. One may now recall with some understanding why experts long have been advising against running plate and grid wires in parallel or near to each other. The capacity effect that would result in the mere internal wiring of the set would also be present if the plate and grid connections to L4 were side by side. This is an obnoxious form of coupling and loss.

As the object is also to have the detec-

tor output in phase, to avoid losses due usually to voltage leading the amperage, the double reversal of phase in the coils, that is, one reversal in L1L2, another in L3L4, is made up by the reversal taking place in each tube. One complete turn reversal of 180 degrees takes place in any RF or detector tube, hence where two tubes are used on the RF side, as here, one balances the other, and the coils should be wound or connected accordingly. As for the audio circuit, it makes little or no difference.

## The Audio Plate Voltage

The same voltage should not be used on the final audio plate as on the other two audio plates, because the two others have 100,000-ohm resistors in the circuit, cutting down the voltage perhaps 70 per cent. (including the plate resistance of the tube, figured at 30,000 ohms for the 201A). The final audio plate resistance and the speaker resistance, combined, are less than 35,000 ohms, hence  $67\frac{1}{2}$  volts on the final audio plate is all-sufficient for audio purposes, although if the RF tube requires more it is all right to include extra voltage.


## An Efficient Set

The Powertone need not be expected to develop all the troubles I have outlined, for I made a set for the sole purpose of introducing as many points of misfortune as was possible, then analyzed each, on the assumption that only one trouble might develop in a few sets and I wanted to be sure that I had covered that one. In point of fact the Powertone is a very efficient receiver and its performance will astound many who up to a week or so ago assumed that, if no tickler were present in a set, at least two stages of RF would be necessary for proper sensitivity, selectivity and volume.

The Powertone is one of the most efficient 1-control sets that can be constructed. Whenever one desires to make a 1-dial set of course he must make some little sacrifice in favor of the attained simplification. The set will give great volume and bring in stations 1,000 miles or more away on the speaker, under favorable conditions, that much having been achieved even in mid-August, in the greatly congested area of New York City.

Even loop operation is successful, although not much DX need be expected on a loop. Moreover, the loop must be matched with L4, and that is most easily done with a semi-collapsible loop designed to be tuned with a .0005 mfd. variable condenser. Tune in a local station on the aerial. Plug in the loop at LJ. Maybe no signal will be heard. Then slowly press down the loop, so that it becomes more "squat," until the signal comes in loud. The inductance of such a loop is reduced when the frame is collapsed. The Werner loop embodies this plan.

[The construction of the Powertone was described in the August 29 and September 5 issues of RADIO WORLD].

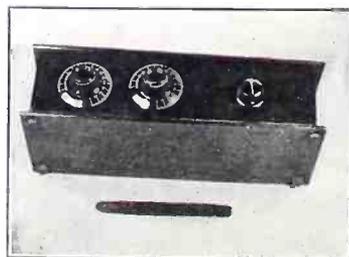

This 3-tube set is only twice as long as a cigar.

# Super-Power No Panacea

WASHINGTON.

Three important conclusions have been reached by the Bureau of Standards as the result of an analysis of higher or super-power broadcasting during this summer. In the order of their importance, they are:

Super-power will not prevent fading.  
Super-power will not cause excessive interference or blanketing of smaller stations.

While materially increasing the service range of a station, super-power will not overcome static on reception at great distances.

## Summer Tests

Throughout the summer a number of stations have increased their power to 5 kilowatts as a result of the recommendations of the last radio conference. Last week WGY used 50 kilowatts on three evenings for test purposes. After measurement of the signals, the following report is made by the Bureau of Standards: "The past summer has witnessed a 10-fold increase of power used in many of the broadcasting stations, as well as experiments on still higher powers, running up to 50 kilowatts. Measurements on the actual signals delivered by these stations have been made by the Bureau of Standards, Department of Commerce and co-operating laboratories. These measurements culminated in special observations on the alternating 50 and  $2\frac{1}{2}$  kilowatt transmission of WGY on August 22, 24, and 25. Some surprising conclusions can be announced.

## No Great Intensity

"The results are remarkable for some things that did not happen as well as for some that did. First and foremost, high power has not resulted in signals of overwhelming intensity. Even the 50-kilowatt transmissions reached many listeners with an intensity which was not noticeably greater than that of many other stations on moderate power. Excessive interference or blanketing of lower power stations is another element of the popular picture of 'superpower' which has failed to materialize. These results, from the viewpoint of scientific investigation, are regarded as important verification of the calculations of radio engineers, who have consistently maintained that the apprehensions of stifling effects of higher power were wholly unfounded.

"The most startling conclusions are in reference to fading, or signal fluctuation. At all distances greater than about 50 miles from a station, actual tests show that the received wave intensity is continually fluctuating, the variation from maximum to minimum being as great as 100 to 1. The ear is notoriously insensitive to intensity changes, otherwise the reception of distant broadcast programs would be quite unacceptable. Increasing the power was found to affect no improvement in the degree of fluctuation. It can therefore be definitely stated that high power is not the solution of the fading problem.

## Not a Great DX Boon

"For still another reason, the distance over which a broadcast station gives highly satisfactory, dependable service is quite limited. This is the omnipresent background of static and all sorts of electrical disturbance, which requires that the radio wave have more than a certain minimum intensity in order to assure reception free from interference."

# The Rush to the Dial's Rescue

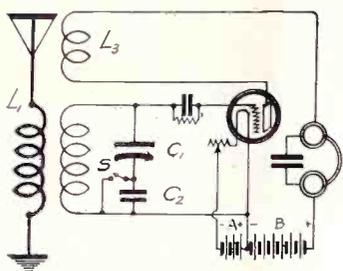


FIG. 1, a fixed condenser in series with C1, a switch S being used for cutting out this condenser by the short-circuiting method.

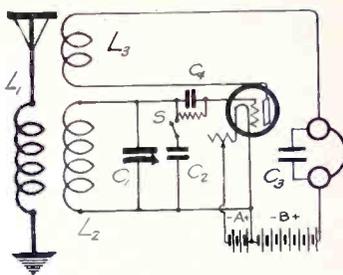


FIG. 2, a fixed condenser switched on for parallel connection with C1.

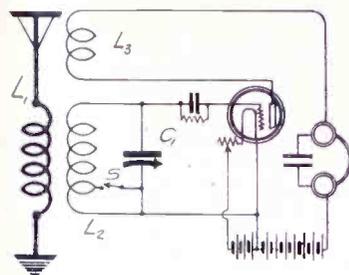


FIG. 4, a tapped secondary, with switch to short-circuit the otherwise dead end.

## Analysis of Methods of Uncrowding the Lower Capacity Settings, to Facilitate Tuning — Straight-line Frequency Dials the Newest Addition to the Ranks.

By Capt. P. V. O'Rourke

THE most practical present way of separating low-wave stations on the dial is by employing a straight-line frequency or a spiral condenser. We all know that when listening-in to low wavelength stations on a set which employs some other type of condenser that the stations are jammed together on the lower end. This is illustrated in daily practice.



CAPT. PETER V. O'ROURKE

If you use a straight-line wavelength condenser the stations still will be crowded a little, but at equal points, either on high waves or on low waves. This is because the stations may be only 6 meters apart, whether on high or low waves.

If you use an SL capacity condenser (circular plate), somewhat the same effect is obtainable as in the SL wavelength condenser type. The stations are more crowded at the lower end.

### Advantages of SLF Condenser

The SLF condenser solves the problem. Channels are separated by 10 kilocycles by the Department of Commerce. The higher the frequency, the lower the wavelength (1,000 kcy.=300 meters). The lower the frequency the higher the wavelength (500 kcy.=600 meters). As we reach the high wavelengths on the frequency condenser, the numbers get closer together, while on the lower wavelengths (upper end of dial), the numbers are spaced more. Frequency condensers should have dials that turn clockwise. I believe, that in the future, condensers will be made so that the low-wave stations will be separated even more than on the SLF type, and maybe the high wave stations brought still closer. The spiral condenser fulfills the first part of this idea.

Low waves are coming fast. Signals on low wavelengths are much better in volume and less power accomplishes more than on high waves. High power cannot

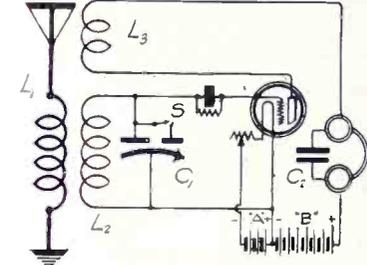


FIG. 3, how a double condenser is used, one stator being cut in by S in parallel with the other stator, or only one stator (at left) being used alone.

successfully be used on low wavelengths due to the low amount of capacity and inductance required for good transmission. A station having an output of 500 watts on a low wavelength can be heard twice as far as a station having 1,000 watts on a high wavelength. The recent Superpower tests tend to confirm this.

During this winter all these facts will be proved anew. High power will be used for retransmission work. Several broadcasters will be putting out programs on short waves or ultra-frequencies. Short waves must not be confused with low (broadcast band) waves.

### Condenser Law

When you connect condensers in series you have to apply the reciprocal law: the capacity of the condenser equals one over one over the condenser plus one over the other condenser.

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

Therefore when we connect condensers in series the total capacity is reduced and if the three components are of the same value the total capacity is one-third the capacity of any one.

Condensers in parallel add up the respective capacities. If two .001 mfd. condensers are connected in parallel, the total capacity is .002.

In Fig. 1 C2 is connected in shunt with C1. C1 is connected in shunt with the secondary. A condenser connected as is C1 increases the fundamental wavelength of the set. However, it is here used as a tuning element and not as a loading unit. By inserting C2 we decrease the wavelength of the set. This in turn allows us to listen to lower wavelengths. It spreads out the lower wavelengths and jams the high wavelengths on the dials or misses some of them. Let us say that C1 has a capacity of .0005 mfd. and C2 a capacity of .0005 mfd. also. The total capacity of this bank is .00025 mfd.

The second method is shown in Fig. 2. Here C2 is connected in shunt with C1 (i.e., in parallel). Condensers in parallel

are added. Let us say that C1 and C2 each has a capacity of .0005 mfd. The two will then total .001 mfd. With C2 in the circuit say we can listen to the low wavelength stations. There is not very much of a spread-out on the dials. The ratio of the spread-out with the condenser C2 in, compared with it out of the circuit, is about 2.5 to 1 between the wavelengths of 200 to 400 meters, while between 300 and 350 meters the ratio is 4 to 1. This is some improvement.

### Other Methods

The next method tried is shown in Fig. 3. We used a double condenser. The manner of connecting the condenser is the same as in Fig. 2. We do not have the peculiar spreading out of low wave stations, though. From 200 to 400 meters the separation between stations is a 4-to-1 ratio throughout. Thus far this is the best method, but a little expensive.

Fig. 4 shows another method. In this scheme the inductance was varied instead of the capacity. By decreasing the number of turns we could tune in the low-wave stations but with no ease. This was one of the worst of the methods tried. As a matter of fact the stations were more crowded than with just plain capacity tuning.

The next method and one which is one of the most difficult is illustrated in Fig. 5. We have a 2-tube receiver, one tuned radio-frequency amplifier and a regenerative detector. The secondaries of both coils are tuned by one condenser, C1. L0 and L2 were tapped at the 22nd turn (each turn had 44 turns). This tap was connected to the stator of C1. The tap was varied on both coils (10th turn on L0 and L2, 15th turn on L0 and L2, etc.) so as to bring in the low wavelength stations with a spread-out effect on the dial. This was not successful. Stations on the lower end were quite jammed (ratio about 1.5 to 1).

The last inductance method tried is given in Fig. 6. I never thought that a variometer ought to have a straight-line frequency effect, but it certainly needs one. I tried about nine-tenths of all the manufactured variometers on the market. The low wavelengths could be tuned in, but oh, what jamming! It was worse than the circular plate condenser. To get the high wavelengths six load coils were used. The high wavelength stations were spread out. In other words the present commercial variometers are impractical as easy tuning elements, especially as secondaries. There are a few exceptions.

Summarizing all these data we find that the method in Fig. 2 is the best makeshift. This method is very simple. A remarkably good effect obtained with this scheme.

They all point to the SLF or spiral condenser. All, I trust, are familiar with the SLF condensers, such as Amsco, Pacent, Karas, General Instrument and the like, at least as to the theory. The Amsco is accurate on frequency variation to 1/10 of

# Spreading Out the Lower Wave

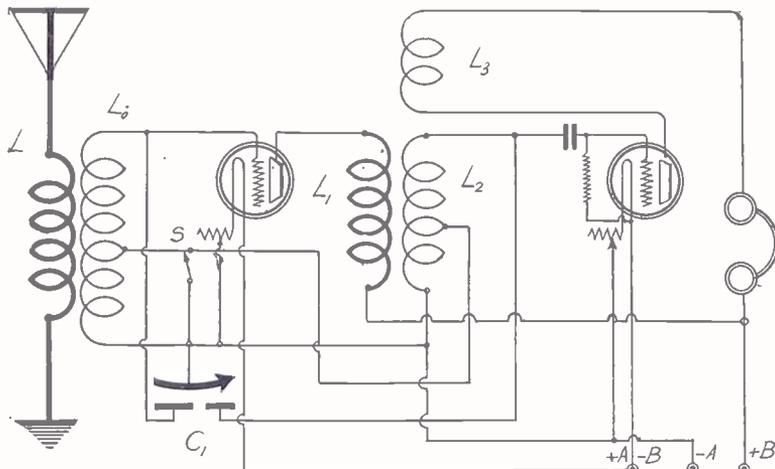


FIG. 5, a double condenser, C1, used to tune two stages at once, the switch S tapping each secondary at the same relative point.

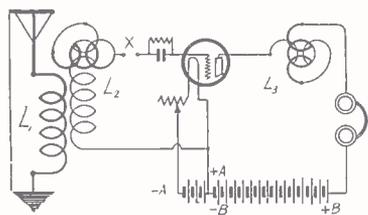


FIG. 6, a variometer used as a tuned secondary. The break at X is for a loading coil.

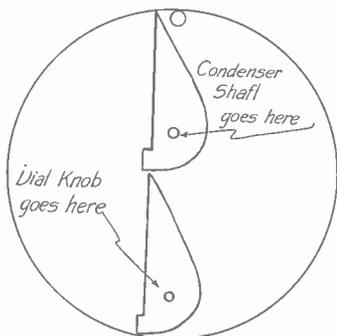


FIG. 7, the fundamental idea of a straight-line frequency dial.

1% and others are accurate, too. The special condenser is something new and rather startling. The rotor plates enter the stator field by a special or screw-line motion, without touching, of course! The effect is the same as if another type of condenser gradually engaged one plate at a time, instead of all at once. The spread-out is marvelous. For a .0005 mfd. type it is 540 divisions of a 100-division dial which is made to revolve at about 5-to-1 ratio. An indicator on the special dial shows up the revolution numbers, i.e., 1, 2, 3, etc. The dial divisions are 100 for 360 degrees, which in itself is a 2-to-1 ratio. On top of that the extremely slow motion of the engaging rotor more than doubles the spreadout, so that 0 to 270 covers from 200 to 400 meters with the proper inductance. The dial indicator reads "2" and the dial itself "70," i.e., 270. The condenser is known as the Kapaciton.

Then aside from coils and condensers a frequency effect dial was tried. The

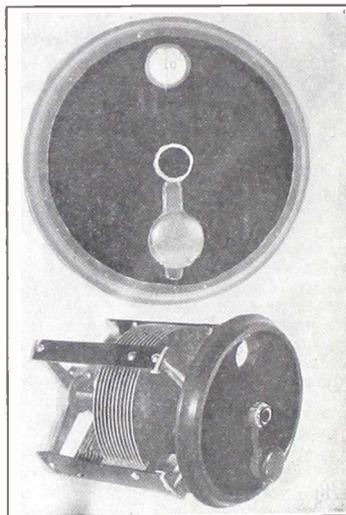


FIG. 9 (top), the front of the dial, with the dial reading visible through the window. The slot is in plain view, with the travelling dial knob in it. The center circle is a decorative knob behind which is a bushing with thread and screw for engaging the condenser shaft.

turning knob moved in a slot, actuating a cam, which moved another cam. The fundamental theory is exemplified in Fig. 7. The dial is moved by one cam (either one), and the condenser by the other. Thus by shaping the plates of the dial, i.e., the cams, a SLF effect is obtained, akin to that of the SLF condenser, although a round-plate (SLC) condenser was used. The Fig. 7 scheme is not practical for commercial production because both cams have to be large, and probably need gearing, traction being unable to induce motion of sufficient strength at all points. The dial would have to be 5" for any safety margin, even with gears.

A better plan is shown in Figs. 8 and 9. Here there is a circular cam for greater strength of motion, and a smaller shaped cam, the large one moving the dial, for the numbers are on the reverse side of the large cam. The other cam moves the condenser, so that slow motion (20-to-1 vernier) exists on the low waves, and gradually diminishes, until when the upper waves are reached it is almost only

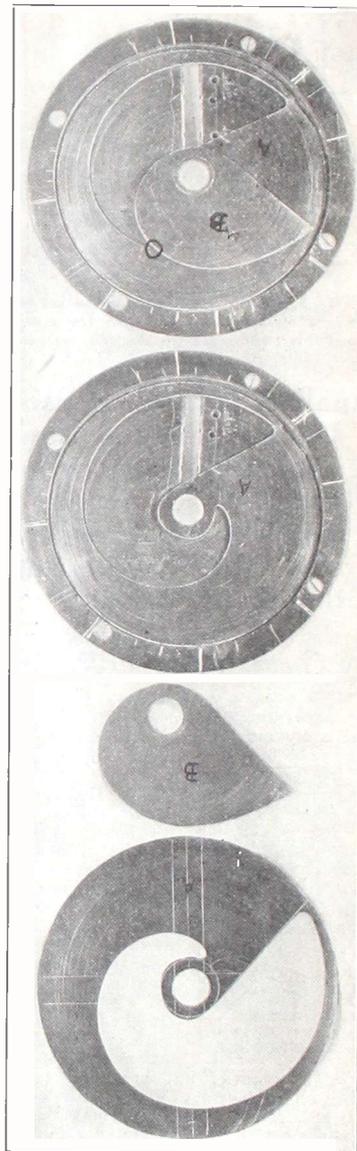


FIG. 8, the cams of an SLF dial. They are A and B. When B is superimposed on A an angle O is developed. In the slot (under shaft hole) a pinion moves up and down, depending on how you turn the dial knob attached to the pinion. The slot is toothed. If point O is brought down to the slot the pinion will move the circumference of A evenly, for dial readings, but, due to the shaped cam B, will introduce slow motion, or much slighter capacity change, on the lower waves.

1-to-1. For mechanical reasons even this may not produce exactly SLF motion, only something better than SLW. However, take an SLW condenser, use a frequency-type dial and you get as good a separation as with a SLF condenser. Use a dial like this on a SLF condenser and you almost overdo it! This type of dial will serve an excellent purpose in affording tuning ease for possessors of circular-plate condensers. Soon there will be several on the market: Radiall, Walbert, Bruno, Rathbun, etc. This type probably will lead the dial market, while SLF condensers will be sold much more than the other condensers before November.

# The Official List of Stations

## Corrected and Revised Up to September 2

Station	Owner and Location	Meters
KDKA	Westinghouse E. & M. Co., E. Pittsburgh, Pa.	309
DLR	Radio Elec. Co. Devils Lake, N. D.	211
KDPM	Westinghouse E. & M. Co., Cleveland, Ohio	250
KDYL	Newhouse Hotel, Salt Lake City, Utah	250
KDZB	F. E. Seifert, Bakersfield, Cal.	210
KFAB	Nebraska Buick Auto Co., Lincoln, Neb.	240
KFAD	McArthur Bros. Merc. Co., Phoenix, Ariz.	360
KFAE	State College, Pullman, Wash.	349
KFAF	Western Radio Corp., Denver, Colo.	278
KFAJ	University of Colorado, Boulder, Colo.	261
KFAN	University of Idaho, Moscow, Idaho	231
KFAU	Boise High School, Boise, Idaho	275
KFAW	Radio Den, Santa Ana, Cal.	214
KFBB	F. A. Buttrely Co., Havre, Mont.	275
KFBC	W. K. Azbill, San Diego, Cal.	278
KFBG	1st Presbyterian Church, Tacoma, Wash.	250
KFBK	Kimball Upson So., Sacramento, Cal.	248
KFBL	Leese Bros., Everett, Wash.	231
KFBS	School District No. 1, Trinidad, Colo.	270
KFBU	Bishop N. S. Thomas, Laramie, Wyo.	238
KFCB	Nielson Radio Co., Phoenix, Ariz.	238
KFCC	1st Congregational Church, Helena, Mont.	248
KFCF	F. A. Moore, Walla Walla, Wash.	256
KFCY	Western Union College, Lemars, Iowa	252
KFCZ	Central High School, Omaha, Neb.	258
KFD	St. Michael's Cathedral, Idaho	275
KFDH	University of Arizona, Tucson, Ariz.	268
KFDJ	Oregon Agricultural College, Corvallis, Ore.	254
KFDM	Magnolia Petroleum Co., Beaumont, Texas	316
KFDX	1st Baptist Church, Shreveport, La.	250
KFDZ	State College of Agriculture, Brookings, S. D.	271
KFEY	H. O. Iverson, Minneapolis, Minn.	231
KFEC	Meier & Frank Co., Portland, Ore.	248
KFEL	Winner Radio Corp., Denver, Colo.	254
KFEQ	J. L. Scroggin, Oak, Neb.	268
KFEY	Bunker Hill & Sullivan, Kellogg, Idaho	233
KFFP	1st Baptist Church, Moberly, Mo.	256
KFFV	Graceland College, Lamoni, Iowa	250
KFGC	Louisiana State University, Baton Rouge, La.	268
KFGD	College for Women, Chickasha, Okla.	252
KFGH	Leland Stanford Junior University, Stanford University, Cal.	270
KFGJ	Cray Co., Boone, Iowa	226
KFGK	1st Presbyterian Church, Orange, Texas	250
KFHA	Western State College, Gunnison, Colo.	252
KFHL	Penn College, Oskaloosa, Iowa	240
KFI	E. C. Anthony, Inc., Los Angeles, Cal.	469
KFIF	Benson Institute, Portland, Ore.	243
KFIO	North Central High School, Spokane, Wash.	265
KFIU	1st Methodist Church, Yakima, Wash.	256
KFIW	Alaska Elec. Co. Juneau, Alaska	276
KFIZ	Daily Commonwealth, Fond du Lac, Wis.	223
KFJB	Marshall Elec. Co., Marshalltown, Ia.	248
KFJC	R. B. Fegan, Junction City, Kan.	219
KFJD	National Radio Co., Oklahoma City, Okla.	261
KFJJ	Liberty Theatre, Astoria, Ore.	246
KFJM	University of N. D., Grand Forks, N. D.	278
KFJR	Ashley C. Dixon & Son, Portland, Ore.	263
KFJS	State Teachers College, Cedar Falls, Ia.	258
KFJT	Tunwall Radio Co., Ft. Dodge, Iowa	246
KFJZ	W. E. Branch, Ft. Worth, Tex.	254
KFKA	State Teachers College, Greeley, Colo.	273
KFKQ	Conway Radio Laboratory, Conway, Ark.	250
KFKU	University of Kansas, Lawrence, Kans.	275
KFKX	Westinghouse E. & M. Co., Hastings, Neb.	288
KFLP	Everette M. Foster, Cedar Rapids, Ia.	256
KFLR	University of N. M., Albuquerque, N. M.	254
KFLU	Rio Grande Radio Sup. Co., San Benito, Texas	236
KFLV	Swedish Evangelist Church, Rockford, Ill.	230
KFLX	George R. Clough, Galveston, Texas	240
KFLZ	Atlantic Auto Co., Atlantic, Iowa	273
KFMB	Christian Churches of Little Rock, Little Rock, Ark.	254
KFMO	University of Ark., Fayetteville, Ark.	300
KFMR	Morningside College, Sioux City, Iowa	261
KFMT	Dr. G. W. Young, Minneapolis, Minn.	265
KFMA	Carleton College, Northfield, Minn.	337
KFNF	Henry Field Seed Co., Shenandoah, Iowa	266
KFNG	Wooten Radio Shop, Coldwater, Miss.	254
KFNL	Union High School, Paso Robles, Cal.	240
KFNV	L. Drake, Santa Rosa, Cal.	277
KFOA	Rhodes Company, Seattle, Wash.	455
KFOL	L. M. Schafbuch, Marengo, Iowa	234
KFON	Echophone Radio Shop, Long Beach, Cal.	234
KFOO	Latter Day Saints University, Salt Lake City, Utah	261
KFOR	David City Tire & Elec. Co., David City, Neb.	226

Station	Owner and Location	Meters
KFOT	College Hill Radio Club, Wichita, Kan.	231
KFOF	Techart High School, Omaha, Neb.	243
KFOY	Beacon Radio Service, St. Paul, Minn.	252
KFPG	Oliver S. Garretson, Los Angeles, Cal.	238
KFPL	C. C. Baxter, Dublin, Texas	252
KFPM	New Furniture Co., Greenville, Texas	242
KFPF	Forestry Department, Los Angeles, Cal.	231
KFPW	St. John's Church, Cartersville, Mo.	268
KFPY	Symonds Investment Co., Spokane, Wash.	266
KFQA	The Principia, St. Louis, Mo.	261
KFQB	Searchlight Publishing Co., Ft. Worth, Texas	254
KFQC	Kidd Bros., Taft, Cal.	231
KFQD	Radio Service Co., Burlingame, Cal.	231
KFQE	G. S. Carson, Jr., Iowa City, Ia.	224
KFQF	National Guard, Denison, Tex.	252
KFQU	W. Riker, Holy City, Cal.	234
KFQW	F. C. Kriermer, North Bend, Wash.	216
KFQA	Farmers State Bank, Beiden, Neb.	273
KFQZ	Taft Radio Co., Hollywood, Cal.	226
KFRB	Hall Bros., Beeville, Texas	249
KFRD	Paris Dry Goods Co., San Francisco	268
KFRE	Men's Club, Grand Forks, N. D.	240
KFRU	Etherial Studio, Bristow, Okla.	395
KFRW	United Churches, Olympia, Wash.	220
KFRX	J. G. Klemgard, Pullman, Wash.	217
KFRY	College of Agriculture, State College, N. M.	256
KFRZ	College of Agriculture, State College, N. M.	266
KFRZ	The Electric Shop, Hartington, Neb.	222
KFSG	Echo Park Evangelistic Ass'n, Los Angeles, Cal.	278
KFSY	The Van Blaricom Co., Helena, Mont.	243
KFUJ	Hoppert P. and H. Co., Breckenridge, Minn.	242
KFUL	T. Goggan & Bro., Galveston, Tex.	258
KFUM	W. D. Corley, Colorado Springs, Colo.	242
KFUO	Concordia Theo. Seminary, St. Louis, Mo.	549
KFUP	Fitzsimmons General Hospital, Denver, Colo.	234
KFUR	H. W. Peery and R. Redfield, Ogden, Utah	224
KFUS	Louis L. Sherman, Oakland, Cal.	233
KFUT	University of Utah, Salt Lake City, Utah	261
KFUU	Colburn Radio Laboratories, San Leandro, Cal.	224
KFUV	G. P. Ward, Springfield, Mo.	252
KFUZ	M. C. A. Virginia, Minn.	248
KFVD	Chas. & W. J. McWhinnie, San Pedro, Cal.	205
KFVE	Film Corp., St. Louis, Mo.	240
KFVF	Clarence B. Juneau, Hollywood, Cal.	208
KFVG	1st Meth. Epis. Church, Independence, Kan.	236
KFVH	Herbert Whan, Manhattan, Kans.	219
KFVI	56th Cav. Brigade, Houston, Tex.	248
KFVO	F. M. Henry, Kirksville, Mo.	226
KFVW	Moonlight Ranch, Denver, Colo.	246
KFVS	Caps Girardeau, Battery Station, Cape Girardeau, Mo.	224
KFVU	The Radio Shop, Eureka, Cal.	210
KFVV	Airfan Radio Corp., San Diego, Cal.	246
KFVX	Radio Shop, Bentonville, Ark.	236
KFVY	Radio Supply Co., Albuquerque, N. M.	250
KFVZ	Glad Tidings Tabernacle, Inc., San Francisco, Cal.	234
KFWA	Browning Bros. Co., Ogden, Utah	214
KFWB	Warner Bros. Pictures, Inc., Hollywood, Cal.	252
KFWC	L. E. Wall & C. S. Myers, Upland, Cal.	211
KFWD	Ark Light Co., Arkadelphia, Ark.	266
KFWF	St. Louis Truth Center, St. Louis, Mo.	214
KFWH	F. Wellington Morse, Jr., Chico, Cal.	254
KFWO	Lawrence Mott, Avalon, Cal.	211
KFWP	Rio Grande Radio Supply House, Bronsville, Texas	214
KFWI	Radio Entertainers, Inc., South San Francisco, Cal.	220
KFWU	Louisiana College, Pineville, La.	238
KFVN	Carl E. Bagley, Welcome, Minn.	227
KGB	The Ledger, Tacoma, Wash.	250
KGO	General Electric Company, Oakland, Cal.	361
KGU	M. A. Mulrony, Honolulu, Hawaii	270
KGW	The Oregonian, Portland, Ore.	492
KGY	St. Martin's College, Lacey, Wash.	246
KHJ	The Times, Los Angeles, Cal.	405
KHO	Louis Wasmer, Seattle, Wash.	273
KJBS	J. Brunton & Sons Co., San Francisco, Cal.	236
KJR	Northwest Radio Co., Seattle, Wash.	484
KJS	Bible Institute, Los Angeles, Cal.	294
KLDS	Reorganized Church of Jesus Christ of Latter Day Saints, Independence, Mo.	441
KLS	Warner Bros. Radio Co., Oakland, Cal.	242
KLX	Tribune, Oakland, Cal.	508
KLZ	Reynolds Radio Co., Denver, Colo.	266
KMA	May Seed & Nursery Co., Shenandoah, Va.	252
KMJ	San Joaquin Corp., Fresno, Cal.	252
KMO	Love Elec. Co., Tacoma, Wash.	250
KNX	Express, Hollywood, Cal.	337
KOA	General Electric Co., Denver, Colo.	322
KOB	College of Agri., State College, N. M.	349

Station	Owner and Location	Meters
KOIL	Monarch Manufacturing Co., Council Bluffs, Ia.	278
KOP	Detroit Police Department, Detroit, Mich.	473
KPO	Hale Brothers, San Francisco, Cal.	229
KPPC	Pasadena Presbyterian Church, Pasadena, Cal.	229
KPRC	Houston Print Co., Houston, Tex.	297
KQP	Apple City Radio Club, Hood River, Ore.	270
KQV	Doubleday Hill Elec. Co., Pittsburgh, Pa.	275
KRE	Gazette, Berkeley, Cal.	258
KSAC	Kansas State Agricultural College, Manhattan, Kans.	341
KSD	Post Dispatch, St. Louis, Mo.	545
KSL	Radio Service Corp., Salt Lake City, Utah	308
KTAB	Tenth Ave. Baptist Church, Oakland, Cal.	216
KTCL	American Radio Tel. Co., Inc., Seattle, Wash.	306
KTHS	New Arlington Hotel, Hot Springs, Ark.	375
KTW	1st Presbyterian Church, Seattle, Wash.	454
KUB	Examiner, San Francisco, Cal.	246
KUOM	State University of Montana, Missoula, Mont.	245
KUPR	Union Pacific R. R. Co., Omaha, Neb.	270
KWG	Portable Wireless Tel. Co., Stockton, Cal.	298
KWVG	City of Brownsville, Brownsville, Tex.	278
KYW	Westinghouse E. & M. Co., Chicago, Ill.	535
KZKZ	Electric Supply Co., Manila, P. I.	270
KZM	Western Radio Inst., Oakland, Cal.	241
KZRQ	Far Eastern Radio, Inc., Manila, P. I.	222
WAAB	V. Jensen, New Orleans, La.	273
WAAC	Tulane University, New Orleans, La.	275
WAAD	Ohio Mech. Institute, Cincinnati, O.	250
WAAF	Drovers Journal, Chicago, Ill.	273
WAAM	I. R. Nelson Co., Newark, N. J.	363
WAAW	Omaha Grain Exchange, Omaha, Neb.	234
WABA	Lake Forest University, Lake Forest, Ill.	227
WABB	Harrisburg Sporting Goods Co., Harrisburg, Pa.	266
WABC	Asheville Battery Co., Inc., Asheville, N. C.	254
WABI	Bangor Ry. & Elec. Co., Bangor, Me.	240
WABL	Agricultural College, Storrs, Conn.	275
WABO	Lake Avenue Baptist Church, Rochester, N. Y.	273
WABQ	Haverford College Radio Club, Haverford, Pa.	261
WABR	Scott High School, Toledo, O.	263
WABW	College of Wooster, Wooster, O.	207
WABX	H. B. Joy, Mt. Clemens, Mich.	254
WABY	John Magaldi, Philadelphia, Pa.	242
WABZ	Coliseum Place Baptist Church, New Orleans, La.	275
WADC	Allen Theatre, Akron, Ohio.	258
WAFD	A. B. Parfet Co., Port Huron, Mich.	256
WAHG	A. H. Grebe Co., Richmond Hill, N. Y.	316
WAIT	A. H. Waite & Co., Taunton, Mass.	229
WAMD	Hubbard & Co., Minneapolis, Minn.	249
WARG	American Radio Res. Corp., Medford Hillside, Mass.	261
WBAA	Purdue University, West Lafayette, Ind.	276
WBAK	State Police, Harrisburg, Pa.	273
WBAO	James Millikia University, Decatur, Ill.	263
WBAP	Star Telegram, Fort Worth, Tex.	476
WBAY	Erner Hopkins Co., Columbus, O.	294
WBAX	J. H. Stenger, Jr., Wilkes-Barre, Pa.	256
WBBA	Plymouth Congregational Church, Newark, O.	236
WBBC	I. Vermilya, Mattapoisett, Mass.	240
WBBL	Grace Covenant Presbyterian Church, Richmond, Va.	229
WBMM	H. L. Atlas, Chicago, Ill.	226
WBPP	Petsky High School, Petoskey, Mich.	238
WBRR	Peoples Pulpit Ass'n., Rossville, N. Y.	273
WBSS	1st Baptist Church, New Orleans, La.	252
WBST	Jenks Motor Sales Co., Monmouth, Ill.	234
WBWW	Ruffner City High School, Norfolk, Va.	222
WBBY	Washington Light Infantry, Charleston, S. C.	268
WBNC	Southtown Economist, Chicago, Ill.	266
WBDC	Baxter Laundry Co., Grand Rapids, Mich.	256
WBES	Bliss Electrical School, Takoma Park, Md.	222
WBOQ	A. H. Grebe & Co., Richmond Hill, N. Y.	236
WBR	State Police, Butler, Pa.	203
WBRC	Edonald Radio Co. (portable), Joliet, Ill.	216
WBRE	Baltimore Radio Ex., Wilkes-Barre, Pa.	231
WBS	D. W. May, Inc., Newark, N. J.	252
WBT	Southern Radio Co., Charlotte, N. C.	275
WBZ	Westinghouse E. & M. Co., Springfield, Mass.	333

Station	Owner and Location	Meters	Station	Owner and Location	Meters	Station	Owner and Location	Meters
WCAD	St. Lawrence University, Canton, N. Y.	263	WFBG	W. F. Gable Co., Altoona, Pa.	278	WIBT	Orlando E. Miller Portable Station, N. Y.	211
WCAE	Kaufman & Baer, Pittsburgh, Pa.	461	WFBH	Concourse Radio Corp., New York, N. Y.	273	WIBU	The Electric Farm, Paynette, Wis.	222
WCAH	Entrenka Electric Co., Columbus, O.	266	WFBJ	Galvin Radio Supply Co., Camden, N. J.	236	WIBW	Dr. L. L. Dill, Logansport, Ind.	220
WCAJ	Nebraska Wesleyan University, University Place, Neb.	275	WFBK	St. Johns University, Collegeville, Minn.	236	WIBX	Grid-Leak, Inc., Utica, N. Y.	205
WCAL	St. Olaf College, Northfield, Minn.	337	WFBM	Onondaga Hotel, Syracuse, N. Y.	252	WIBZ	Powell Electric Co., Montgomery, Ala.	231
WCAO	Sanders & Stayman, Baltimore, Md.	275	WFBN	Merchants Lighting Co., Indianapolis, Ind.	268	WIBO	Benson Radio Co., St. Louis, Mo.	273
WCAP	C. & P. Tel. Co., Washington, D. C.	469	WFBQ	Wynne Radio Co., Raleigh, N. C.	252	WIPC	Gumbel Brothers, Philadelphia, Pa.	538
WCAR	Southern Radio Corp., San Antonio, Texas.	263	WFBW	Maryland National Guard, Baltimore, Md.	254	WJAD	Jackson's Radio Elec. Co., Waco, Tex.	353
WCAT	School of Mines, Rapids City, S. D.	240	WFBX	Signal Corps, Ft. Ben Harrison, Ind.	258	WJAG	Norfolk Daily News, Norfolk, Nebr.	270
WCAU	Durham & Co., Philadelphia, Pa.	278	WFBZ	Knox College, Galesburg, Ill.	234	WJAK	Rev. C. L. White Greentown, Ind.	254
WCAX	University of Vermont, Burlington, Vt.	250	WFC	Strawbridge & Clothier, Philadelphia, Pa.	395	WJAM	D. M. Perham, Cedar Rapids, Ia.	258
WCAZ	Carthage College, Carthage, Ill.	246	WFBK	Francis K. Bridgman, Chicago, Ill.	217	WJAR	The Outlet Co., Providence, R. I.	306
WCBA	Queen City Radio, Allentown, Pa.	254	WGC	Lancaster Elec. Supply Co., Lancaster, Pa.	248	WJAS	Pittsburgh Radio Supply House, Pittsburgh, Pa.	275
WCBC	University of Michigan, Ann Arbor, Mich.	229	WGAO	W. G. Patterson, Shreveport, La.	263	WJAZ	Zenith Radio Corp., Chicago, Ill.	267
WCBD	W. G. Voliva, Zion, Ill.	345	WGAZ	The Tribune, South Bend, Ind.	275	WJBA	D. H. Lentz, Jr., Joliet, Ill.	208
WCBE	Uhalt Radio Co., New Orleans, La.	263	WGBA	Jones Elec. & Radio Co., Baltimore, Md.	254	WJBB	L. W. McClung, St. Petersburg, Fla.	207
WCBF	H. S. Williams, Mayfield, Ky.	268	WGBB	H. H. Carman, Freeport, N. Y.	244	WJBC	Hummer Furniture Co., 2nd and Joliet Sts., La Salle, Ill.	234
WCBH	University of Mississippi, Oxford, Miss.	242	WGBE	1st Baptist Church, Memphis, Tenn.	266	WJBD	Ashland Broadcasting Committee, Ashland, Wis.	233
WCBM	Hote Chateau, Baltimore, Md.	242	WGBF	The Finke Furniture Co., Evansville, Ind.	217	WJBI	R. S. Johnson, Red Bank, N. J.	219
WCBQ	1st Baptist Church, Nashville, Tenn.	242	WGBG	Breitenbach's Radio Shop, Thirifton, Va.	226	WJBN	Dennison University, Granville, O.	217
WCBR	C. H. Messer (Portable), Providence, R. I.	205	WGBT	Frank S. Megargee, Scranton, Pa.	240	WJBU	Loyal Order of Moose, Mooseheart, Ill.	303
WCBU	Arnold Wireless Co., Arnold, Pa.	220	WGBL	L. W. Campbell, Johnstown, Pa.	248	WJBY	Radio Corp. of Ama, New York, N. Y.	405
WCBY	Forks Electrical Shop, Buck Hill Falls, Pa.	231	WGBM	Elyria Radio Assn., Elyria, Ohio.	227	WJZ	Radio Corp. of Ama, New York, N. Y.	455
WCBZ	Neutrowound Radio Mfg. Co., Chicago Heights, Ill.	217	WGBN	Hub Radio Shop, La Salle, Ill.	256	WKAA	H. F. Paar, Cedar Rapids, Iowa.	278
WCCO	Washburn Crosby Co., Minneapolis, Minn.	416	WGBQ	Dr. Roses Artisan, San Juan, P. R.	275	WKAF	WKAF Broadcasting Co., Milwaukee, Wis.	261
WCEE	C. E. Erbstein, Elgin, Ill.	275	WGBR	Stout Institute, Menomonie, Wis.	234	WKAP	D. W. Flint, Cranston, R. I.	234
WCK	Stix Baer & Fuller Co., St. Louis, Mo.	273	WGBS	Florida Cities Finance Co., Fulford By-the-Sea, Fla.	278	WKAQ	Radio Corp. of Porto Rico, San Juan, P. R.	341
WCLO	C. W. Whitmore, Camp Lake, Wis.	231	WGBT	Furman University, Greenville, S. C.	316	WKAR	Mich. Agricultural College, Lansing, Mich.	285
WCM	Texas Market Department, Austin, Texas	268	WGBU	Marshfield Broadcasting Association, Marshfield, Wis.	229	WKAV	Laconia Radio Club, Laconia, N. H.	210
WCNH	Henry P. Rines, Portland, Me.	256	WGBV	Gimbel Brothers, New York, N. Y.	316	WKBE	K. & B. Electric Co., Webster, Mass.	231
WCOS	Wittenberg College, Springfield, Ohio.	248	WGBW	Furman University, Greenville, S. C.	316	WKBG	C. L. Carrell, (Portable) Chicago, Ill.	216
WCST	C. T. Sherer Co., Worcester, Mass.	268	WGBX	University of Maine, Orono, Maine.	252	WKRC	Kodel Radio Corp., Cincinnati, O.	326
WCUW	Clark University, Worcester, Mass.	238	WGCN	The Tribune, Chicago, Ill.	370	WKY	WKY Radio Shop, Oklahoma City, Okla.	275
WCX	Detroit Free Press, Detroit, Mich.	517	WGMU	A. H. Grebe & Co., Inc., Richmond Hill, N. Y.	236	WLAL	1st Presbyterian Church, Tulsa, Okla.	250
WDAA	Tampa Daily News, Tampa, Fla.	273	WGNP	George H. Phelps, Inc., Detroit, Mich.	270	WLAP	W. V. Jordan, Louisville, Ky.	275
WDAB	Kansas City Star, Kansas City, Mo.	336	WGPC	Grand Central Palace, N. Y. City	273	WLAX	Greencastle Commun. Broad. Sta., Greencastle, Ind.	231
WDAC	J. Amarillo, Amarillo, Tex.	263	WGR	Federal Telephone Mfg. Co., Buffalo, N. Y.	319	WLB	University of Minneapolis, Minneapolis, Minn.	278
WDAY	Radio Equipment Corp., Fargo, N. D.	244	WGST	Ga. School of Tech., Atlanta, Ga.	270	WLBL	Wisconsin Department of Markets, Stevens Point, Wis.	278
WDBC	Kirk, Johnson & Co., Lancaster, Pa.	258	WGY	General Elec. Co., Schenectady, N. Y.	380	WLIT	Lit Brothers, Philadelphia, Pa.	395
WDBE	Gilham-Schoen Elec. Co., Atlanta, Ga.	278	WHA	University of Wisconsin, Madison, Wis.	525	WLS	Sears Roebuck Co., Chicago, Ill.	345
WDBF	R. G. Phillips, Youngstown, O.	222	WHAD	Marquette University, Milwaukee, Wis.	275	WLTS	Lane Technical High School, Chicago, Ill.	248
WDBJ	Richardson Wayland Elec. Co., Roanoke, Va.	229	WHAG	University of Cincinnati, Cincinnati, Ohio	233	WLW	Crosley Radio Corp., Cincinnati, O.	258
WDBK	M. F. Broz, Furn. Cleveland, O.	227	WHAM	University of Rochester, Rochester, N. Y.	278	WLWL	Missionary Society of St. Paul the Apostle, N. Y. City	288
WDBL	Department of Markets, Stevens Point, Wis.	278	WHAP	Wm. H. Taylor Finance Corp., Brooklyn, N. Y.	240	WMAC	C. B. Meredith, Cazenovia, N. Y.	275
WDBO	Rollins College, Winter Park, Fla.	240	WHAR	F. P. Cooks Sons, Atlantic City, N. J.	275	WMAF	Round Hills Radio Corp., Dartmouth, Mass.	360
WDBQ	Morton Radio Supply Co., Salem, N. J.	234	WHAS	The Courier Journal Times, Louisville, Ky.	400	WMAK	Norton Laboratory, Lockport, N. Y.	266
WDBR	Tremont Temple Baptist Church, Boston, Mass.	261	WHAV	Wilmington Elec. Spec. Co., Wilmington, Del.	266	WMAN	1st Baptist Church, Columbus, Ohio	278
WDBS	S. M. K. Radio Corp., Dayton, O.	275	WHAZ	Kensinger Polytechnic Institute, Troy, N. Y.	280	WMAP	Chicago Daily News, Chicago, Ill.	448
WDBX	Dyckman Radio Shop, New York, N. Y.	233	WHB	Sweeney School Co., Kansas City, Mo.	366	WMAY	Kings Highway Presbyterian Church, St. Louis, Mo.	248
WDBY	North Shore Congregational Church, Chicago, Ill.	258	WHBA	Shaffer Music House, Oil City, Pa.	250	WMAZ	Mercer University, Macon, Ga.	261
WDBZ	Boy Scouts of America, Kingston, N. Y.	233	WHBB	Hebal's Store, Stevens Point, Wis.	240	WMBB	Trionon Ball Room, Chicago, Ill.	250
WDD	Chattanooga Radio Co., Chattanooga, Tenn.	256	WHBC	Rev. E. P. Graham, Canton, Ohio.	254	WMBF	Fleetwood Hotel, Miami Beach, Fla.	384
WDR	Doolittle Radio Corp., New Haven, Conn.	268	WHBD	Charles W. Howard, Bellefontaine, Ohio	222	WMC	The Commercial Appeal, Memphis, Tenn.	500
WDF	Duttee Wilcox Flint, Inc., Cranston, R. I.	441	WHBF	Beardsley Specialty Co., Rock Island, Ill.	222	WMCA	Hotel McAlpin, N. Y. C.	341
WDFW	J. L. Bush, Tuscola, Ill.	278	WHBG	John S. Skane, Harrisburg, Pa.	231	WMAB	Shepard Stores, Boston, Mass.	250
WDZ	F. T. Fallain, Flint, Mich.	234	WHBH	Culver Military Academy, Culver, Ind.	222	WMAC	Shepard Stores, Boston, Mass.	280
WEA	A. T. & T. Co., New York, N. Y.	492	WHBI	Lover Auto Co., Ft. Wayne, Ind.	234	WMAD	Omaha of Okla., Norman, Okla.	254
WEAF	A. T. & T. Co., New York, N. Y.	492	WHBK	Franklin St. Garage, Ellsworth, Me.	231	WMAL	Omaha Central High School, Omaha, Neb.	258
WEAH	Wichita Board of Trade, Wichita, Kans.	268	WHBL	J. H. Slusser, Logansport, Ind.	220	WMAN	Wittenberg College, Springfield, O.	248
WEAI	Cornell University, Ithaca, N. Y.	254	WHBM	C. L. Carroll (Portable), Chicago, Ill.	233	WMAR	1st Christian Church, Butler, Mo.	231
WEAJ	University of South Dakota, Vermillion, S. D.	278	WHBN	1st Ave. Methodist Church, St. Petersburg, Fla.	258	WMAT	Lenning Bros. Co., Philadelphia, Pa.	250
WEAM	Borough of North Plainfield, N. Plainfield, N. J.	261	WHBO	Y. M. C. A., Providence, R. I.	231	WMAX	Dakota Radio App. Co., Yankton, S. D.	244
WEAN	Shepard Co., Providence, R. I.	270	WHBP	Johnstown Auto Co., Johnstown, Pa.	256	WMNJ	Radio Shop, Newark, N. J.	233
WEAO	Ohio State University, Columbus, O.	294	WHBQ	St. John's M. E. Church, Memphis, Tenn.	233	WMNO	Peoples Tel. & Tel. Co., Knoxville, Tenn.	268
WEAR	Goodyear T. and R. Co., Cleveland, O.	390	WHBR	Scientific E. & M. Co., Cincinnati, O.	216	WMNY	Municipal Station, New York, N. Y.	526
WEAU	Davidson Bros. Co., Sioux City, Ia.	275	WHBS	F. W. Ling, Mechanicsburg, Ohio.	238	WMOC	Page Organ Co., Lima, Ohio.	261
WEAY	Iris Theatre, Houston, Texas	270	WHBU	B. V. Boche's Sons, Anderson, Ind.	219	WMOI	South East Equipment Co., San Antonio, Texas	395
WEBA	The Electric Shop, Highland Park, N. J.	233	WHBW	D. R. Kienzle, Philadelphia, Pa.	216	WMON	Vaughan Con. of Music, Lawrenceburg, Tenn.	283
WEBC	W. C. Bridges, Superior, Wisc.	242	WHBY	St. Norbert's Coll., West DePere, Wis.	250	WMOW	Woodmen of the World, Omaha, Neb.	526
WEBD	Elec. Equipment & Service Co., Anderson, Ind.	246	WHDI	Wm. Hood Dunwoody Ind. Inst., Minneapolis, Minn.	278	WMOX	F. J. Wolf, Trenton, N. J.	240
WEBE	Roy W. Waller, Cambridge, Ohio.	234	WHDC	Hickson Elec. Co., Rochester, N. Y.	258	WMOC	Palmer School of Chiro, Davenport, Ia.	484
WEBH	Edgewater Beach Hotel, Chicago, Ill.	370	WHDK	Radiovox Company, Cleveland, Ohio.	273	WMOD	Odeia Radio, Paterson, N. J.	203
WEBJ	Third Avenue R. R. Co., New York, N. Y.	273	WHDL	George Schubel, New York, N. Y.	361	WMOL	Hotel Jamestown, Jamestown, N. Y.	275
WEBK	Grand Rapids Radio Co., Grand Rapids, Mich.	242	WHDM	Bankers Life Co., Des Moines, Ia.	526	WMOC	Triple Alliance Radio Station, Sycamore, Ill.	205
WEBL	Radio Corp. of Ama. (Portable)	226	WHDT	H. S. Miller, Philadelphia, Pa.	250	WMOI	Iowa State College, Ames, Iowa	270
WEBM	Radio Corp. of Ama., Portable Mobile Station	226	WHDU	Wm. Hood Dunwoody Ind. Inst., Minneapolis, Minn.	278	WMON	Neutrowound Radio Mfg. Co., Homewood, Ill.	217
WEBP	E. B. Peddicord, New Orleans, La.	280	WHEC	Hickson Elec. Co., Rochester, N. Y.	258	WMOP	John Wanamaker, Philadelphia, Pa.	508
WEBQ	Tate Radio Co., Harrisburg, Ill.	226	WHED	Radiovox Company, Cleveland, Ohio.	273	WMOQ	Unity School of Christianity, Kansas City, Mo.	278
WEBR	H. H. Howell, Buffalo, N. Y.	240	WHEF	George Schubel, New York, N. Y.	361	WMOR	L. Bamberger & Co., Newark, N. J.	405
WEBT	Dayton High School, Dayton, Ohio.	256	WHEG	Bankers Life Co., Des Moines, Ia.	526	WMOS	Peoples Pulpit Assn. Batavia, Ill.	275
WEBU	Beloit College, Beloit, Wisc.	268	WHFH	H. S. Miller, Philadelphia, Pa.	250	WMOT	Mo. State Marketing Bureau, Jefferson City, Mo.	254
WEBV	Savannah Radio Corp., Savannah, Ga.	234	WHFI	Capital Times, Madison, Wis.	236	WMOW	Main Auto Supply Co., Ft. Wayne, Ind.	227
WEBW	Edison Electric Illuminating Co., Boston, Mass.	476	WHFJ	L. M. Tate Post, V. F. W. St. Petersburg, Fla.	222	WPAK	N. D. Agricultural College, Agricultural College, N. D.	285
WEHS	Robert E. Hughes, Evanston, Ill.	205	WHFK	Elite Radio, New Bedford, Mass.	210	WPAZ	Dr. John R. Koch, Charleston, W. Va.	268
WEMC	Emm. Missionary College, Berrien Springs, Mich.	286	WHFL	Fredek B. Zittel, Flushing, N. Y.	219	WPFC	Municipality, Atlantic City, N. J.	300
WENR	All-Amer. Radio Corp., Chicago, Ill.	266	WHFM	C. L. Carrell, Chicago (portable)	216	WPSC	Penn State College, State College, Pa.	261
WEW	St. Louis University, St. Louis, Mo.	248	WHFN	Univ. of Toledo, Toledo, O.	205	WQAA	H. A. Beale, Jr., Parkersburg, Pa.	220
WEWA	Dallas News & Journal, Dallas, Texas	476	WHFO	Nelson Bros., Chicago, Ill.	226	WQAC	Gish Radio Service, Amarillo, Texas	234
WEWB	The Times, St. Cloud, Minn.	273	WHFP	Flite Radio Stores, New Bedford, Mass.	210	WQAE	Moore Radio News Station, Springfield, Vermont	246
WEWC	University of Nebr., Lincoln, Nebr.	275	WHFR	Billy Maine, Chicago, Ill.	216	WQAM	Electric Equipment Co., Miami, Fla.	268
WEWD	Eureka College, Eureka, Ill.	240	WHFS	First Presbyterian Church, Meridian, Miss.	210	WQAN	The Scranton Times, Scranton, Pa.	250
WEWE	1st Baptist Church, Knoxville, Tenn.	250	WHFT	F. M. Schmidt, Farina, Ill.	210	WQAO	Calvary Baptist Church, New York, N. Y.	360
WEWF	J. V. De Walle, Seymour, Ind.	226	WHFU	Thurman A. Owings, Weirton, W. Va.	246			
			WHGV	N. J. National Guard, Elizabethtown, N. J.	203			

# A 25-to-110-Meter Receiver

By **Sidney E. Finklestein**

Associate, Institute of Radio Engineers.  
**T**HE 3-circuit tuner, if the inductance used is small, will make a very satisfactory short-wave set. It will be possible



SIDNEY E. FINKELSTEIN

to tune from about 25 to 110 meters, using a .00025 mfd. variable condenser. It is advisable to employ the straight-line frequency type of variable condenser, as the tuning is made easier thereby.

The hookup is shown in Fig. 1. It is a regulation 3-circuit tuner, to which is added one stage of resistance-

(Cut this part out and paste it on page 14 for permanent record.)

Station	Owner and Location	Meters
WQJ	Calumet Rainbo Broadcasting Co., Chicago, Ill.	448
		224
WRAF	Radio Club, Inc., Laporte, Ind.	256
WRAM	Economy Light Co., Escanaba, Mich.	244
WRAM	Lombard College, Galesburg, Ill.	263
WRAW	Antioch College, Yellow Springs, O.	238
WRAW	Avenue Radio Shop, Reading, Pa.	268
WRAX	Flexon's Garage, Gloucester City, N. J.	268
WRBC	Immanuel Lutheran Church, Valparaiso, Ind.	278
WRC	Radio Corp. of America, Washington, D. C.	466
WREO	Reo Motor Co., Lansing, Mich.	289
WRHF	Radio Hospital Fund, Washington, D. C.	256
WRK	Doron Bros. Elec. Co., Hamilton, O.	270
WRNY	Experimenter Publishing Co., (Radio News) N. Y. City	258
WRM	University of Illinois, Urbana, Ill.	273
WRMU	A. H. Grebe & Co., Inc., Motor Yacht Club, N. Y. City	236
WRW	Tarrytown Research Laboratory, Tarrytown, N. Y.	273
WSAC	Clemson Agricultural College, Clemson College, S. C.	337
WSAL	U. S. Playing Card Co., Cincinnati, O.	326
WSAJ	Grove City College, Grove City, Pa.	229
WSAN	Allentown Call, Allentown, Pa.	229
WSAP	City Temple, New York, N. Y.	264
WSAR	Doughty & Welch Elec. Co., Fall River, Mass.	253
WSAU	Camp Marenefed, Cephem, N. H.	229
WSAV	C. W. Vick Radio Construction Co., Houston, Tex.	248
WSAZ	Chase Electric Shop, Pomeroy, Ohio	244
WSB	The Atlanta Journal, Atlanta, Ga.	428
WSBC	World Battery Co., Chicago, Ill.	200
WSKC	World's Star Knitting Co., Bay City, Mich.	261
WSMB	Saenger Amuse. Co., New Orleans, La.	319
WSOE	School of Engineering, Milwaukee, Wisc.	246
WSRF	Harden Sales & Service Co., Broadlands, Ill.	233
WSRO	Radio Co., Hamilton, Ohio	251
WSUL	State University of Iowa, Iowa City, Iowa	484
WSY	Alabama Polytechnic Institute, Auburn, Ala.	250
WTAB	Fall River Daily Herald, Fall River, Mass.	266
WTAC	Penna. Traffic Co., Johnstown, Pa.	268
WTAL	Toledo Radio & Elec. Co., Toledo, O.	252
WTAM	Willard Storage Battery Co., Cleveland, Ohio	389
WTAP	Cambridge Radio Elec. Co., Cambridge, Ill.	242
WTAQ	S. Van Gordon & Son, Osseo, Wis.	254
WTAR	Reliance Radio & Elec. Co., Norfolk, Va.	301
WTAS	Charles E. Erbstein, Elgin, Ill.	263
WTAT	Edison Elec. Ill. Co. (Portable), Boston, Mass.	244
WTAW	Agricultural Kas. Mech. College, College Station, Tex.	270
WTAX	Williams Hardware Mfg. Co., Streator, Ill.	231
WTAY	Oak Leaves Broadcasting Assn., Oak Park, Ill.	250
WTAZ	T. J. McGuire, Lambertville, N. J.	261
WTC	Kansas State Agricultural College, Manhattan, Kas.	273
WTIC	Travelers Insurance Co., Hartford, Conn.	347
WWAD	Wright & Wright, Inc., Philadelphia, Pa.	250
WWAE	Alama Ballroom, Joliet, Ill.	242
WWGL	Radio Engineering Corp., Richmond Hill, N. Y.	213
WWL	Ford Motor Co., Dearborn, Mich.	266
WWJ	Detroit News, Detroit, Mich.	517
WWL	Loyola University, New Orleans, La.	275

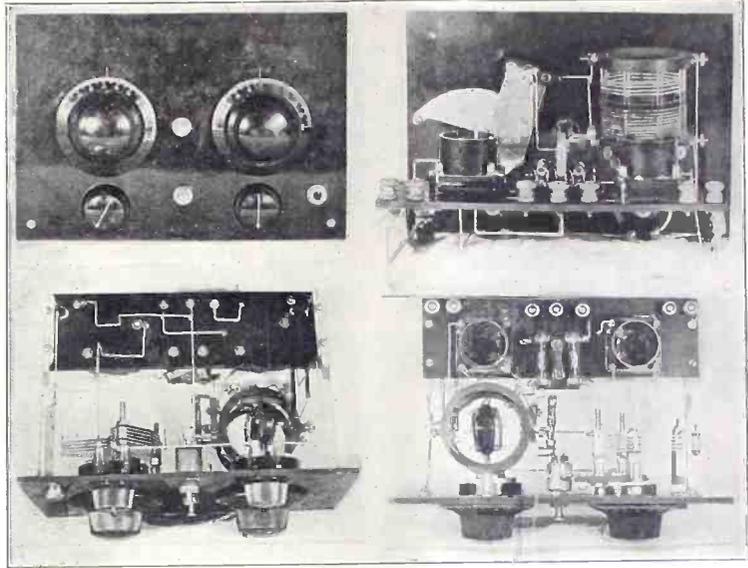


FIG. 2, top, left, the front view of the set. Fig. 3, bottom, left, the bottom view. Fig. 4 (top, right) rear view, and Fig. 5, the top view. (Hayden Photos.)

coupled audio-frequency amplification, so that the signals will be made louder. This to some extent increases the audible range. Transformer coupling AF is pretty good in such a set, too, but there is always a little danger of magnetic feedback and accentuated body capacity effects.

The form used had a stator 2" mean diameter, 2 1/2" high. Between two insulation rings were quartzite glass rods and on these rods the wire was wound. A commercial coupler was used, with 4 turns on the primary, L1, 1/4" space, and a secondary of 12 turns, the wire being flat aluminum for primary and flat copper for secondary. The tickler form is 1" diameter, 1" high and has 13 turns of No. 26 silk covered wire.

Flattened space-wound wire was used in making the coils shown in the photographs because of the lesser distributed capacity. No. 20 DCC wire may be used, but should be space-wound. The distributed capacity will be a trifle higher. Especially on short-wave work it is sometimes desirable to have this distributed coil capacity at the very minimum, because of its relative effect on tuning, as would be shown by a characteristic curve, and because of resistance losses. The SLF type condenser aids in overcoming the effect of this distributed capacity, so far as tuning is concerned, but the winding alone can account for avoiding excessive losses.

In either case the tickler would be the same. The finer wire used here makes little comparative difference in resistance, a mere fragment of the 30,000 ohms resistance in the plate of the tube (201A).

The tuning of the set under most conditions will have to be done by the beat note method. There is not much to object to when this is done on short waves.

In building a short-wave set it is most important to keep the grid and plate leads short and not run them parallel. In fact, all leads should be short. Then there will be less likelihood of uncontrollable whistles and body capacity effects.

The same B battery voltage is applied at the source, and this is quite proper. The voltage may be up to 135, but 90 will suffice. This does not mean putting 90 volts on the detector plate, because there is a large voltage drop, about 75 per cent., in the resistor R3 and the plate of the tube. Rating the applied gross voltage

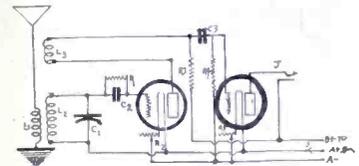


FIG. 1, the wiring diagram of the short-wave set.

at 96, if a 6-volt storage battery is used and B—connected to A+, then the actual net effective voltage at the plate is 24. The audio-tube has about 60 volts, when the voltage drop due to resistance in the plate is deducted.

The set will work well with other types of tubes, too, including the 199, but the 201A gave very satisfactory service.

### LIST OF PARTS

- One short-wave 3-circuit coupler, L1L2L3.
- One .00025 mfd. SLF variable condenser, C1.
- One .00025 mfd. fixed condenser, C2.
- One .006 mfd. fixed condenser, C3.
- One 2-meg. grid leak, R1.
- One 20-ohm rheostat, R2.
- One 20-ohm rheostat, R5.
- One 0.1 meg. resistor, R3.
- One 1.0 meg. resistor (leak), R4.
- One push-pull switch, S.
- One single-circuit jack, J.
- Two sockets.
- One socket strip with brackets, or base-board, 7x9".
- One panel, 7x10".
- Two 3" dials.

## JOIN THE A. B. C.

A. B. C. stands for American Broadcast Club, an organization of fans banded together to promote the welfare of radio. There are no dues, no obligations. Address A. B. C. Editor, RADIO WORLD, 1493 Broadway, New York City. The names and addresses of new members follow:

- Richard A. Doan, 463 Gunnison Ave., Grand Junction, Col.
- M. C. Bundel, 3731 Madison Ave., Kansas City, Mo.
- Edward Lembart, 2122 Park Ave., Chicago, Ill.
- Adolph Souček, Bladen, Neb.
- C. V. Slack, 747 17th St. Niagara Falls N. Y.

## A THOUGHT FOR THE WEEK

Official radio expositions may come and go, but there is a perennial radio show in every radio store for the pudgy-nosed, eager little chaps who stand more or less disconsolately on the outside looking in.

# RADIO WORLD

Radio World's Slogan: "A radio set for every home."

TELEPHONES: LACKAWANNA 6976 and 2063  
 PUBLISHED EVERY WEDNESDAY  
 (Dated Saturday of same week)  
 FROM PUBLICATION OFFICE  
 HENNESSY RADIO PUBLICATIONS CORPORATION  
 ROLAND BURKE HENNESSY, President  
 M. B. HENNESSY, Vice-President  
 FRED S. CLARK, Secretary and Manager  
 1493 BROADWAY, NEW YORK, N. Y.  
 (Putnam Bldg., Times Square and 43rd Street)  
 European Representatives: The International News Co.,  
 Breams Bldgs., Chancery Lane, London, Eng.  
 Paris, France, Brentano's, 38 Avenue de l'Opera,  
 San Francisco, Loyd B. Chappell, 656 O'Farrell St.

EDITOR, Roland Burke Hennessy  
 MANAGING EDITOR, Herman Bernard

## SUBSCRIPTION RATES

Fifteen cents a copy, \$6.00 a year, \$3.00 for six months, \$1.50 for three months, Add \$1.00 a year extra for foreign postage. Canada, 50 cents.  
 Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address also. State whether subscription is new or a renewal.

## ADVERTISING RATES

General Advertising  
 1 Page, 7 1/4" x 11" 462 lines.....\$300.00  
 1/2 Page, 7 1/4" x 5 1/2" 231 lines..... 150.00  
 1/4 Page, 4 1/2" x 7" 115 lines..... 75.00  
 1 Column, 2 1/4" x 11" 154 lines..... 100.00  
 1 Inch..... 10.00  
 Per Agate line..... .75  
 Times Discount  
 52 consecutive issues..... 20%  
 26 times consecutively or E. O. W. one year..... 15%  
 4 consecutive issues..... 10%  
 WEEKLY, dated each Saturday, published Wednesday.  
 Advertising forms close Tuesday, eleven days in advance of date of issue.

## CLASSIFIED ADVERTISEMENTS

Ten cents per word. Minimum, 10 words. Cash with order. Business Opportunities, 50 cents a line; minimum, \$1.00.

Entered as second-class matter, March 28, 1922, at the Post Office at New York, N. Y., under the act of March 3, 1879.

SEPTEMBER 12, 1925

## RESULTS

## RESULTS EDITOR:

I have just finished building Lewis Winner's 4-Tube Marconi Feedback set, described in the August 15 issue of RADIO WORLD, and it certainly works fine. I can sit about 65 feet from the set and hear the program from KTHS, Hot Springs, Arkansas, loud and clear. I have built most of your sets from "The One Dial Set That Gets DX" to the famous Diamond, but this is the best of them all by far.

My attention was recently called to the "sin and shame" letter, in which the 1-tube Rofpatkin Reflex (Nov. 21 issue) was criticized. Out of curiosity I built it and it worked so well that I built two more for friends. One of them liked it better than his Superdyne. I believe that if Mr. Hancock would have more patience he could make his set work well. I have been interested in radio for five years and have learned that patience is necessary if one desires a good set.—Frank Vebber, Jr., 694 Cramer St., Milwaukee, Wis.

A 1-CONTROL PORTABLE by Capt. P. V. O'Rourke; A Baby Super-Heterodyne, by J. E. Anderson; A More Powerful Diamond, Still only 4 tubes, by Herman Bernard. Other features in RADIO WORLD, dated July 11, 1925, 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

# Radio's Greatest Season

THE 1926 season is under way, auspiciously begun. It started earlier than in any previous year. First to feel this gratifying effect was the retail trade, with breath somewhat taken away. The commotion immediately spread to the jobbers, distributors, authorized agents and manufacturers. The effect was cumulative and reciprocal. Orders started to arrive in quantity nearly two weeks ago and a sudden upward trend even followed upon that gratifying start. Now come two great radio shows, the Fourth Annual, at Grand Central Palace, and the Radio World's Fair, at the 258th Field Artillery Armory, both in New York City.

Opinions vary as to the advisability of having two simultaneous shows. As was to be expected, much competition and some open hostility existed between the two groups. The radio trade and the public at large will await the result, to determine whether the two-at-a-time plan is a good thing for radio. It may be.

Exhibitors fell into a highly co-operative mood in respect to both shows, and there is no apparent reason why both should not be a success, even though the managers of one may cast glowering eyes on the managers of the other.

The outstanding features of the shows no doubt are enhanced simplicity of control in radio sets, particularly the single-dial idea, and the great advances in beautification. When one looks back upon the sets of yesteryear one feels that long strides indeed have been made upon the aesthetic path of radio. The prophesied revolution has not arrived and perhaps never will.

RADIO WORLD'S Survey Bureau has completed a canvass of manufacturing and sales conditions. On the basis of data that are decidedly weighty, both physically and intellectually, it is unquestionable that this will be by far and wide the greatest sales season in radio's history. Simply tremendous will be the success of the leaders in the respective fields, with sets showing a greater percentage of gain than the parts business, but with parts representing a larger total financial volume. Sales resistance is gone at this moment, the hot days happily over and brisk business actually a fact. Perhaps coming years will see the beginning of the radio season in early August, instead of near the close of that month, and radio tradefolk will be the happier for it. This Summer, all told, was no worse than others, and it is comforting to think of how lively will be the radio days from now until after the holidays.

The post-Yuletide slump may be offset somewhat next year because of the wise selection of the date for International Radio Week (January 24). Keen interest will be displayed in this all over the world.

What could be happier in radio than this great wealth of healthy activity and wisely proportioned action?

## World Will Enjoy His Scheme of Radio Movies, Says Collegian

IMAGINE tuning in your radio set and seeing a complete moving picture flashed on the screen! This is not a fairy tale, for according to reports from Madison, Wis., a young college student, Douglas W. F. Coffee, of that city, has invented such a machine. He has successfully transmitted moving pictures by radio over a distance of seven miles, he says, and claims it is the first time that any such feat has been accomplished.

Although complete data on the operation of the receiver and transmitter is not known, the following is a brief description of what happens. A small light is played upon a rotating movie film strip. It is then transferred into electrical vibrations. This is then sent by a specially devised radio transmitter, neither microphone or key being used. At the receiving end it is transferred into light waves

and then transferred on the screen. The receiver used is also especially made, and a 20-foot indoor antenna is used to pick up the energy.

It will not be very long before radio moving pictures, with the personages in the film talking instead of the captions being played upon the screen, will be an established and recognized fact, says coffee. At present, the invention is in its experimental stage.

## INTERFERENCE PROTECTION

The time is not far distant when we must determine just how much right to protection from inductive interference the user of an ultra-sensitive receiving set is entitled to. If, in any community, we succeed in lowering the interference level to a given point the users of sensitive receivers immediately increase the amount of amplification in use until the same interference level exists in his mind, as before, and the same problem arises again.

My experience in the radio communication field has led me to the conclusion that there is no other field where the need of co-operative effort directed towards the solution of common problems is greater.

—Prof. C. M. Jansky.



DOUGLAS W. F. COFFEE



# THE RADIO UNIVERSITY

A QUESTION and Answer Department conducted by RADIO WORLD for its Readers by its staff of Experts. Address Letters to The Radio University, RADIO WORLD, 1493 Broadway, New York City.

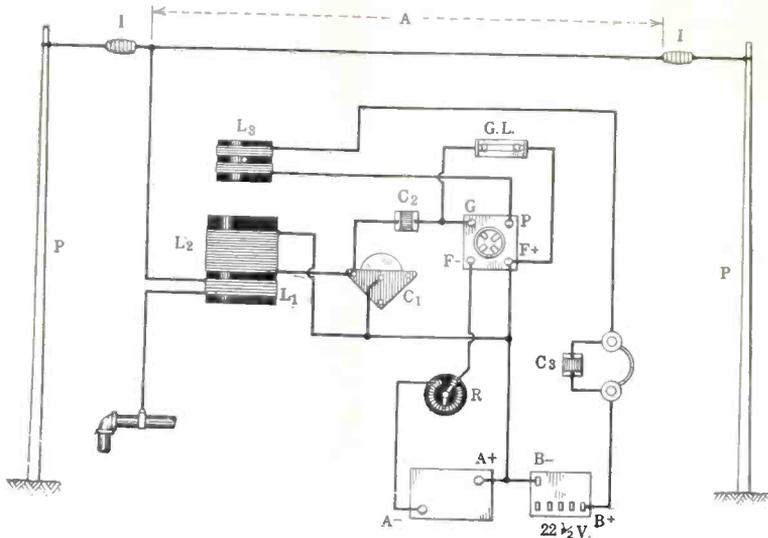


FIG. 199, showing a picture diagram of a 1-tube regenerative receiver. L1L2L3 is a 3-circuit tuner. L1 has 10 turns, wound on a tubing  $3\frac{1}{2}$ " in diameter, with No. 22 DCC wire. L2 has 45 turns and wound on the same tubing with same kind of wire. L3 has 35 turns, wound on a tubing 2" in diameter, 2" high, using same kind of wire as for L1L2. C1 is a .0005 mfd. variable air condenser. C2 is a .00025 mfd. grid condenser. GL is the grid leak having a resistance of 2 megohms. C3 is a .001 mfd. fixed condenser. R is a 10-ohm rheostat. A UV200 or UV201A tube may be used.

**WILL YOU** please give a picture diagram of a 1-tube Regenerative receiver?—T. B. Lock, Portsmouth, N. D.  
See Fig. 199.

**I HAVE** a 5-tube tuned radio-frequency set. When a local station is broadcasting, it can be heard practically all over the three dials. Disconnecting the antenna seems to make very little difference. This being true, can I hope, by the introduction of a wave-trap, to eliminate the undesired station?—F. M. Padelford, 126 June Street, Fall River, Mass.

Try disconnecting your ground. Leave your antenna connected. A wave-trap will help. The coil should have 50 turns and wound on a  $3\frac{1}{2}$ " tubing, with No. 22 DCC wire. Across this coil shunt a .005 mfd. variable condenser. Place the coil in inductive relation to the antenna lead-in.

**IN REGARD** to Tim Turkey's Silk Hat Circuit for Dress Occasions, published in the Jan. 3 issue of RADIO WORLD. (1) Is this circuit sensitive and clear and is it free from disturbing noises on DX stations? (2) To how low and how high a wavelength will this circuit tune?—Calvin Martin, 518 24th St., Oakland, Calif.

(1) Yes. If there is no static prevalent, the stations will all come in, without distortion. The set itself is a non-distorting one. (2) From 150 to 600 meters, using a 100-foot antenna (including lead-in) and a 10-foot ground (from ground to set). Watch A & B wiring carefully. Do not connect B+ with A— or B—.

**I HAVE** several 23-plate variable condensers rated at .0005 mfd. I want to make a .0004 mfd. variable. How many plates will I have to take out?—W. H. Johnson, Box 605, Hilo, Hawaii.

You cannot determine the capacity of a condenser by the number of plates. A condenser having 25 or 26 plates may have a capacity of .0005 mfd. The only

way to determine the actual capacity of a condenser is by calculating the area of the surface of the plates, the thickness of the material used, the spacing between the plates, and employ these data in a formula. This formula is found in the Bureau of Standards circular on Radio Instruments and Measurements, obtainable from the Superintendent of Documents, Washington, D. C., for \$60. A better way to reduce the capacity of your condenser is to put a condenser in series with the one you have. A .00075 mfd. will be just right.

**CAN YOU** kindly furnish information that will enable me to use the waveband of 200 to 600 meters on the following receiver set—Tuning unit of .0005 variable condenser, a commercial coil (3-circuit type), coil is on Bakelite form 3 in. by 3 in. primary, 15 turns, secondary, 45. Tickler is one  $2\frac{1}{2}$  in. by  $1\frac{1}{2}$  in., and has about 28 turns. Can get Pitts-

burgh Post station, which is on 463 meters, on phones, clear, but weak, with the condenser  $\frac{1}{2}$  engaged and tickler zero. When the tickler is opened, signals are shut out with whistles  $\frac{3}{4}$  way around. 2—Is the Diamond of the Air as shown in May 23rd issue of RADIO WORLD, as efficient as the circuit in Aug. 15. 3—Can I use Robert's 3-circuit tuner and R. F. T. (basket weave), in the Diamond of the Air? If so, how will I use the neutralizing coil that goes with the R. F. T. It has same number of turns as the R. F. T. primary.—J. C. Reid, 12 Powell Ave., Evansville, Ind.

(1)—Insert a .0005 mfd. variable condenser in series with aerial. Put a switch across this condenser, so that you may cut it in and out of the circuit. (2)—Yes. (3)—Yes., Disregard it.

**WILL THE** "3-Circuit Tuner You Can Log" get DX? (2)—What does Percy Warren mean when he says the B.C.L. may omit the coils L5, L6 in the Marconi Broadcast Receiver in the July 18 issue of RADIO WORLD? Will this set get DX stations?—Joseph Hacker, 1021 N. Castle St., Baltimore, Md.

(1)—Yes. (2)—They are not required for use by the Broadcast Listener. (3)—Yes.

**IN REGARD** to the home-made Toroidal coil as described by George Hostetter in August 22 issue of RADIO WORLD, how many turns of wire will I have to wind on or take off the coil so I can use it with a .0005 mfd. variable condenser.—Teddy Damm, Rolla, Mo.

Add on 20 turns.

**PLEASE GIVE** the electrical of a 3-tube set, using a 3-circuit tuner with 2 steps of AF amplification using transformers for coupling.—P. Long, Pittsfield, Mass.

See Fig. 200.

**MY ANTENNA** is strong between two trees, the height on one end is about 50 feet, the other end is about 75 or 80 feet. I have dropped back 3 feet from the lower end for my lead-in. Is this correct or should I have a continuous or center lead-in. I have insulated twice on each end. Antenna is 80 feet long. Used on a

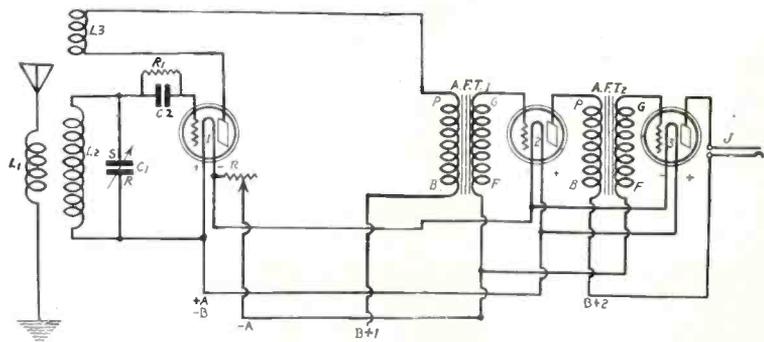


FIG. 200, showing the electrical diagram of a 3-tube set. The constants for the coil are the same as in the coil of Fig. 199. C1 is a .0005 mfd. variable condenser. C2 is the .00025 grid condenser. R1 is a 2 megohm grid leak resistance. A 6-ohm resistance is used to control the filaments of the UV201A tubes. The new UX tubes may be used here also. AFT 1 and 2 are both of the low ratio type.

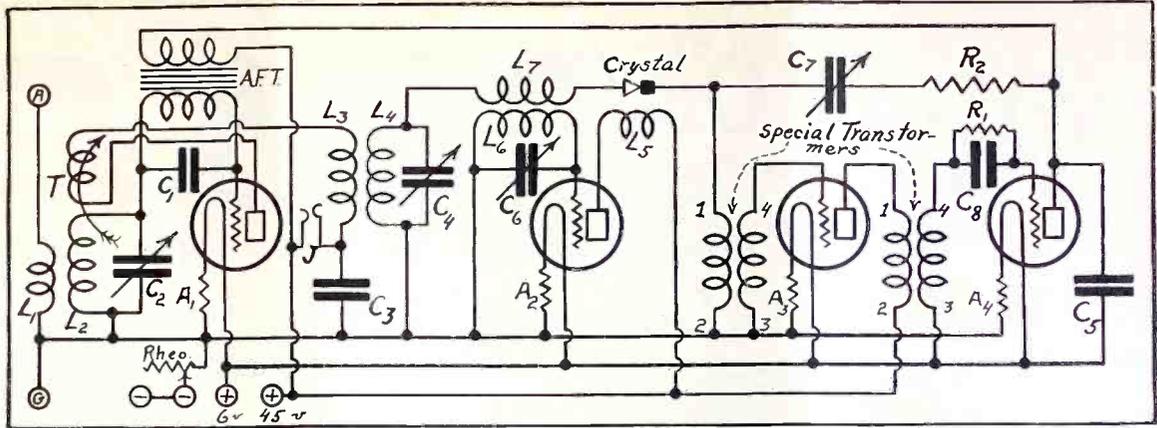


FIG. 201, showing the 4-Tube Super-Heterodyne. L1L2 is wound on tubing 3" in diameter with No. 22 DSC wire. Primary contains 10 turns and the secondary 43 turns. There is a separation of about 1/4" between the two windings. T is wound on a 2" tubing, 2" high, with 40 turns of No. 36 DCC wire. L3L4 is wound on a spool 1" in diameter and 1" long. Primary consists of 20 turns and is wound next to the core. Over the primary are two layers of heavy wrapping. Over this, wind the secondary. There are 93 turns here. C2 and C4 are a double condenser (common rotor) with a capacity of .0005 mfd. L6 is the oscillating coil, which contains 43 turns of No. 24 DSC wire wound on a 3" tubing. L5 is wound on the same form, with the same size wire, 35 turns being used. L7 is wound on tubing 1 1/2" in diameter with 50 turns of No. 36 DCC wire. The Inter-Frequency coils are wound on spools 1" long and 2" in diameter. The primary consists of 180 turns of No. 36 DCC wire. Over the primary are two layers of cloth. The secondary consists of 760 turns of same size wire as the primary. C6 is a .0005 mfd. variable condenser. C8 is a .00025 mfd. grid condenser. C1 is a .0005 mfd. condenser. C3 is a .001 mfd. condenser. C9 is a .0005 mfd. condenser. C7 is a midget variable condenser.

Crosley Super-Trirdyn.—Frank R. Thompson, Houston, Tex.

You should have a continuous lead-in.

\* \* \*

A DIAGRAM of a 4-Tube Super-Heterodyne is requested.—D. T. Larksons, Chico, Cal.

See Fig. 201.

\* \* \*

PLEASE answer these questions: (1)

What is the difference between a grid condenser and a grid leak condenser? Which one of these should be used in the "1-Tube DX Set for the Novice," described by Percy Warren in May 23 issue of RADIO WORLD? I am going to use a Bretwood variable grid leak. (2) If when I stop operating the set, shall I disconnect the headsets or leave them inserted? (3) What wavelength will this set tune in?—John Sporna, Box 24, Escatawpa, Ala.

(1) They are both the same article. The Bretwood is O. K. (2) No. (3) 150 to 600 meters.

\* \* \*

I AM about to build the Diamond of the Air, and intend using Bruno coils as I have two .005 low-loss condensers. (1) Can I use them with the above named coils, or will I have to change the coils to suit the condensers?—John M. Birmingham, 676 Myrtle Ave., Brooklyn, N. Y.

(1) It is advisable to change your condensers. They have too high a capacity.

\* \* \*

WILL YOU please publish size of wire, diameter of coil and number of turns for Toroidal coil to be tuned by a .0005 mfd. condenser.—C. S. Gilbert, Box 3, Hollywood, Florida.

Use No. 24 DCC wire. Wind on a 1 1/4" tubing, 9" long. There are 195 turns wound. See August 22 issue of RADIO WORLD for complete toroidal coil data.

\* \* \*

REFERENCE is made to "Byrt C. Caldwell's Reflex" wiring diagram of which was printed in June 14 issue of RADIO WORLD. (1) Can the following parts, as is, be used efficiently: Fodu variocoupler, two tri-coil RF transformers and three DV3 tubes. The coupler having 7 single and 7-10's taps? (2) Should a connection to A— be indicated between the secondary of the first AFT and the primary of the second RFT?

(3) Will the set operate with a loop by inserting an appropriate jack between the .005 condenser and secondary of the coupler? (4) Could this hook-up be built on a 13 1/2"x6" panel, 5" baseboard, and work efficiently as a portable set?—William H. Jenkins, 146 West Loudon St., Germantown, Philadelphia, Pa.

(1) Yes. (2) No. (3) Yes. (4) Yes.

\* \* \*

IN REFERENCE to the Diamond of the Air in the August 29 issue of RADIO WORLD, would you be kind enough to tell me the proper ohmage of the rheostat controlling the detector and the audio-frequency tubes? (2) What is the voltage of the 2 C batteries?—Robert A. Masson, 13 Meade St., West Orange, N. J.

(1) This rheostat has a resistance of 6 ohms. (2) 4.5 volts apiece.

\* \* \*

I AM contemplating the construction of Hayden's Handsome Portable as described in July 4 issue of RADIO WORLD. Without a doubt, condenser C1, is of .0005 capacity, but inasmuch as the Bruno condensers included in the kit for constructing the set have three capacities, I am uncertain of what capacity C2 should be.—Charles V. Ruden, Dallas, Texas.

C1 and C2 are both .0005 mfd. variable condensers.

IN THE August 29 issue of RADIO WORLD, there was published in the Radio University the "Freedom Reflex." The "Freedom Reflex," as was printed previous in the July 4 issue of RADIO WORLD, shows a .0001 mfd. capacity and the one in the University at .001 mfd capacity. Which is correct? (2) Can Freshman Master-piece radio frequency tuning units be used in this hook-up?—A. W. Gustafson, 1075 Jessie St., St. Paul, Minn.

(1) C4 being a .001 mfd. condenser is correct. (2) Yes.

\* \* \*

I AM going to build the Diamond. (1) How many feet and of what size wire should I use in constructing a loop for same? (2) Can I use an Amperite on the RF tube?—R. W. Deck, 406 Center St., Sandusky, O.

(1) 90 feet of No. 22 DCC wire. (2) Yes.

\* \* \*

IN THE August 22 issue of RADIO WORLD a circuit called the "Electrostatic Regenerator," by Percy Warren, was published. Wiring the set according to the diagram in Fig. 1, I get an open circuit hum, unless I connect the ground with the A+ and B— post, which connection is not shown on the diagram. Is this O. K.?—Milton M. Schuman, 575 N. Gay St., Baltimore, Md.

(1)—That is O. K.

## Join RADIO WORLD'S University Club

and we will enter your name on our subscription and University lists by special number. Put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it in your queries and the questions will be answered the same days as received.

And Get Free Question and Answer Service for the Coming 52 Weeks.

RADIO WORLD, 1493 Broadway, New York City:

Enclosed find 6.00 for RADIO WORLD for one year (52 Nos.) and also consider this an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year, and a number indicating my membership.

Name .....

Street .....

City and State .....

**"Bruno"**  
PATENT PENDING

**MAGIC**

Makes Any Circular-Plate Condenser Tuner

A New Member of the Bruno



THE BRUNO MAGIC DIAL—MOULDED BAKELITE

Again has the genius of William A. Bruno triumphed. The noted radio engineer has designed a dial that widely separates the low-wavelength stations, so exasperatingly crowded on other dials, while maintaining wide separation on the high waves.

Tuning is made really simple on any set if the Bruno Magic Dial is used. The circular-plate (straight-line capacity) condensers thus are magically endowed with all the virtues of the straight-line frequency condensers!

Instantly attachable to any condenser shaft — the lowest-price, highest quality and handsomest frequency type dial made!

**\$2.50**


Dealers, Write for Terms on Dial, Powertone Set, Boxed Powertone Kit, Etc.

The Bruno 1-Dial  
Licensed Under the



The Lowest-Price Quality  
5-Tube Set That Is Tuned  
by Only One Control!

*"It Has a Soul for Music"*

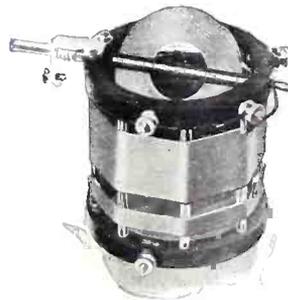

"77" Broadcast Tuner

This "Bruno" coil is wound on quartzite glass rods in the improved BRUNO method, as prescribed and used by the Bureau of Standards. When tuned with a 0005 condenser the coil gives a range of from 200 to 575 meters. The newly designed BRUNO pancake tickler allows regeneration to come on gradually without the usual howls and squeals. The BRUNO "77" mounts with a single screw and has a pleasing appearance, as the secondary winding is brilliant orange and the primary and tickler windings are deep green.....\$5.50



**Bruno** Short Wave

This coil is the latest word in tuners for short-wave reception. The method of winding the primary, copper and aluminum wire, which thus eliminates to a great extent capacity losses. When tuned with from 20 to 110 meters is obtained to receive the benefits of C.W. reception. A special feature, the tickler which enables the receiver to receive the benefits of the detector out any noticeable loss of the detector.

**BRUNO RADIO**  
Dept. 512 221 FULTON

# LOG DIAL



Reg. U. S. Patent Office


Like The Straight-Line Frequency Type  
Family of Precision Instruments

Powertone Set  
Hogan Patents



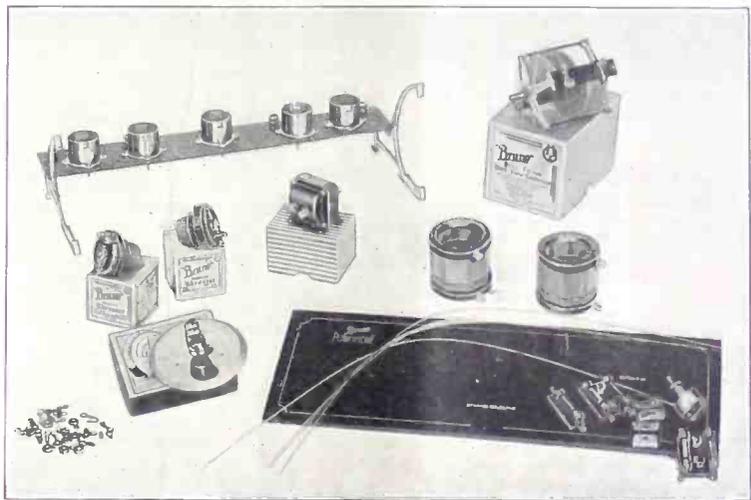**\$39.50**


The Kit for the 1-Dial Powertone  
Licensed Under the Hogan Patents



Two Bruno 99 RF transformers.  
One Bruno No. 21 Ultra-Varlo condenser.  
One 7x18" drilled and engraved panel.  
Two 20-ohm Bruno rheostats.  
One Vebly ballast resistor, 3/4 amp.  
Two 1 megohm Vebly resistors.  
Three Vebly grid leaks: 2 meg., 1 meg., 5 meg.


Five fixed condensers.  
One 4" vernier dial.  
One AF transformer.  
One filament-control jack.  
One 5-gang Bruno socket strip.  
Five sockets.  
One pair of Bruno brackets.  
Binding posts, lugs, bus bar.

**\$29.50**

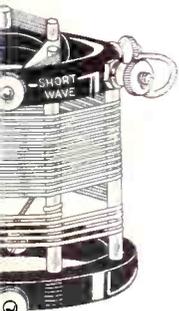

Coil

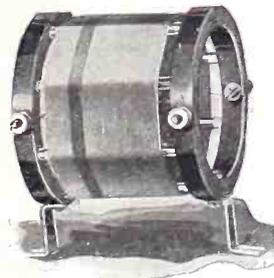Low-loss design of 3-circuit secondary with flat rolled spaced by a special method, detrimental distributed capacitance condenser a range of which will enable the high regular transmission and of this coil is the design of which will be controlled with wavelength.....\$5.50



"55" Radio Frequency Transformer

This coil is matched with the BRUNO "77" so as to synchronize with the dial settings, thus permitting use of a single condenser to tune the both secondaries. The BRUNO method of winding on quartzite glass rods is used in this transformer which can be mounted in any position desired due to the brackets that come with each one.....\$3.00



*Bruno* "99" Broadcast Tuner

This 3-circuit tuner is designed to cover the entire broadcast range of from 200 to 575 meters when tuned with a .0005 condenser but is smaller than the BRUNO "77" coil. This feature enables its use in portable sets and other receivers where the conservation of space is a necessary feature. The BRUNO quartzite glass method of winding is employed, which minimizes the losses. This tuner mounts with but one screw which is placed through the panel.....\$5.50

CORPORATION  
STREET NEW YORK CITY

Meet Us at Booth 83, Grand Central Palace,  
and Get a Cardboard Bruno Log Dial FREE!

# Fourth Annual Show Starts the 1926 Season



IRA GODING



J. C. JOHNSON

The Fourth Annual National Radio Exposition, Sept. 12 to 19, at Grand Central Palace, New York City, according to Harold Bolster, director of the exposition, opens the 1926 radio season. Mr. Bolster stated that the demand for tickets was nearly double that of last year.

All branches of the industry took great interest in the event. Thousands of retailers, manufacturers and radio fans will mingle to witness the great spectacle of radio progress spread before their eyes on three floors of the immense exposition building.

## A Proving Ground

The National Radio Exposition assumed added significance because of the public's great interest in the simplification of receiving sets and their operation. Manufacturers exhibit for the first time many new devices at the exposition, and the public's approval or disapproval will determine the policy of the manufacturer in offering new equipment. The exposition will be a proving ground for the manufacturer, where he will be able to determine with a fair degree of accuracy what types of sets and apparatus will prove popular during the coming season.

## Program of Features

Remarkable demonstrations of the use of radio will be made daily. On Sept. 12 (Saturday) the exposition will be opened by a message broadcast from London by the Duke of Sutherland, which will be picked up and made audible to the visitors at the exposition. The Duke of Sutherland is president of the Radio Association of Great Britain. If weather conditions are favorable the message will be picked up by fans in general.

Other novel demonstrations of the growing uses of radio will emphasize the great progress being made. A radio-controlled automobile will wind its way about the third floor; a radio-controlled airplane will hover over the exposition building; motion pictures that speak as well as move will be exhibited; the photograph of a prominent public official speaking in Washington will unfold itself upon a huge screen through the agency of radio as the words of the speaker are picked out of the air and made audible to the visitors at the exposition.

## Radio Fashion Show

An outstanding feature of the exposition will be the broadcasting of 1926 fashions that will be exhibited daily on the third floor an hour in the afternoon and an hour in the evening. Leading importers, as well as domestic style creators, are taking part in the affair. Beautiful mannequins, artists' models and film stars will appear in the style pageant. It is expected that thousands of women in the metropolitan and surrounding territory will tune in to hear the last word in style trends.

A large stage was constructed on the third floor of the exposition building in the form of a huge radio set, 60 feet long.

The models emerge from a huge speaker and walk upon the set.

## Women's Clubs to Participate

Miss Anne Morgan and Miss Robinson Smith, officers of the American Woman's Association, which is planning to construct a \$5,000,000 clubhouse, will broadcast on Thursday, Sept. 17, messages telling about the growing importance of radio in the home. Other prominent members of the woman's association will appear on Thursday, which will be known as Woman's Day. Marie Dressler, the comedienne, and Vaughn de Leath will be on the program.

Many other civic and social organizations are co-operating to furnish an elaborate program of entertainment at the exposition. The Boy Scouts will stage drills and other demonstrations and prominent stage and screen stars, as well as radio artists and announcers, will take part in entertainments.

## Educational Exhibits

In addition to the many exhibits of manufacturers displaying their latest designs and models educational exhibits will be placed on the third floor to acquaint the public with some of the mysteries of radio transmission. A complete sending station will be set up and the transmission of a radio program will be demonstrated to the public. The intricate control devices will be placed in full view, with an attendant in charge to explain their operation.

## Public Interest

The National Radio Exposition is a leading event in radio circles. With the approach of Fall, renewed interest in radio is springing up and because of the central location of Grand Central Palace, it is expected that the immense exposition building will be jammed throughout the eight days the exposition is in session.

Radio fans in New York are focusing their attention on amateur events to be staged at the exposition, to be held under the auspices of the Second District Executive Radio Council, which comprises in its membership the chief amateur clubs in the second broadcasting district. Hundreds of dollars in cash, silver cups and radio sets will be distributed to the participants in the contests.

## Industry's Support

The industry is co-operating to make the exposition a grand success. The leading New York newspapers and radio magazines, took booths and planned to run special radio sections during the exposition. Local broadcasting stations will send out the features of the program to thousands of listeners-in. Practically all the leading radio manufacturers have reserved space at the exposition.

The show is being run by the American Radio Exposition Co., Inc., J. C. Johnson, general manager, and Ira Goding, sales manager.

## DATE FOR CHEMICAL SHOW

The tenth exposition of Chemical Industries, with a special radio display, will be held in Grand Central Palace, New York City, September 28 to October 3. Risher & Amend, Third Avenue and 18th Street, New York City, will have a specially fine display.

## BATTERY MAKERS TO MEET

The September meeting of the National Battery Manufacturers' Association will be held on Friday and Saturday, September 18 and 19, at the Hotel Roosevelt, New York City.

# WHAT'S NEW THIS FALL IN PRODUCTS

By P. E. Edelman  
Electrical Engineer

What is new this Fall in radio? Not basically so much, perhaps, but there are many refinements. Touching some of the high spots after looking in at the laboratories and factories of some of the best-known factors in the industry, here is a summarized outline of improvements:

## Sets

This is expected to be a year of 6-tube sets. Some will run to eight tubes, because tubes are lower priced. Appearance is the main concern of many this Fall. There will be an absence of panels marred by machine screws and plenty of fancy panels with beautiful controls, including some with photo-engraved gold design and dial etchings. Cabinets run to handsome furniture, even in models ranging below \$100 list. Circuits are basically the same with improved stabilization control. Sets are on a production basis, with several models using stamped bus wiring, riveted fastenings, and press work products. The loft factory days of radio are passing. Price range is decidedly lower, some lists reading like jobbers' net cash prices 18 months ago. A few sets will have impedance audio amplification and some resistance amplification stages. Many sets will have straight-line frequency condensers exclusively. A few will have balancers to make up for variations in tubes.

## Tubes

Several new names will appear on the tube market and the big group will bring out a few new models. Increasing use of the new base will follow. The AC tube may be a factor, especially if improved. The greatest need of radio today is more uniform standardized tubes. Lists are expected to settle at \$2.50 per tube.

## Batteries

Chemical improvements increasing shelf life and improved discharge rate are noticed in dry cells. One maker is offering a battery assembled with flat type plates. Storage battery makers are bringing out small ampere hour sizes for use with low rate or trickle type chargers.

## Condensers

Straight-line types have the run this Fall. One novelty is a cam spiral control condenser using square plates. Condensers are made with balancer plate to assist matching radio stage tuning and make up for coil differences. Two and three gang types with single dial control are being made in quantities.

## Eliminators

There are numerous B eliminators offered, also a few A and B eliminators. These run somewhat high in list price. Eliminator kits are also offered for home assemblers. This is an eliminator year.

## Loops

Several refined loops appear, some with basket and banked windings.

## ZBINDEN WITH GLEASON CORP.

H. J. Zbinden has severed connections with the Barawik Co. to take charge of production for the Gleason Corp. 559 West Monroe St., Chicago, manufacturers of straight-line frequency and midget condensers.

# What the Show Will Reveal in Design and Style of Sets

By J. C. Johnson

General Manager Fourth Annual National Radio Exposition

The principle in radio development that has received major attention from radio engineers during the last twelve months is termed in engineering circles acoustic synchronization. The inflections of the human voice, it is explained, and the vibrations of the musical scale, occupy an acoustical frequency of from 16 to 10,000 vibrations per second. The transmission of speech or music from the broadcasting station, on the other hand, is within a frequency of 140 to 6,900 vibrations per second. The task of co-ordinating or synchronizing the acoustical elements at the transmitting and receiving ends of the radio circuit has been accomplished this year to a remarkable degree.

## Loudspeakers Up to \$250

The result of these developments is that leading radio manufacturers of the United States are bringing out loudspeaker units in some cases almost as elaborate as the sets themselves. One of the new loudspeakers to be shown at the exposition includes transformers, filters, chokes, rectifier tubes and amplifier tubes. When used in connection with a certain type of set it may be employed also to energize the grid, plate and filament circuits, thus constituting a complete AC operated set.

So amazing have been the results attained in acoustical synchronization that for the first time the feat will have been achieved this year of reproducing in the home an orchestra or a concert with the original volume and yet without the least distortion. Because of the extraordinary volume thus obtainable some of the loudspeakers will be furnished with long cords, of as much as fifty feet, so that the loudspeaker may be placed at this distance from the receiver.

## Vacuum Tubes

A new super-power amplifier tube, designed for AC lighting mains, will attract a large amount of technical and popular attention at the Fourth Annual National Radio Exposition. Intensive research, it is said, has developed the fact that the employment of a powerful amplifying tube in the last audio stage will result in revolutionary improvement in volume and in the quality of reproduction.

Other tubes, designed in some cases for storage battery operation and in other cases for dry battery use will result in a

remarkable improvement in reception this year, it is claimed.

## Sets Operate Off Main

Notwithstanding the progress made in meeting the problem of utilizing alternating house current in the operation of radio receivers there is no immediate sign that either storage or dry batteries are likely to be displaced to a very large extent. Some of the larger radio manufacturers who have been developing radio receivers which would require no batteries whatsoever will this year for the first time place sets on the market that will operate on AC current, and which, it is declared, will be free from all hum characteristic of house current. One set will include a glow lamp and a ballast lamp in its circuit which will automatically control filament and plate current and also the fluctuations of the AC lighting current. These sets are necessarily in the higher price ranges.

## Single Control Sets

Many leading manufacturers this year will place on the market uni-controlled sets. In most of these cases the tuning condensers in the first three radio frequency stages are operated by one control knob, thus enabling one station after another to be reproduced merely by moving the control throughout its scale. For extremely long distance reception there is an added regeneration control whereby the additional sensitivity and selectivity provided by regeneration is brought into play.

## Other Features

New and improved styles of battery eliminators designed to provide plate voltages for any type of radio receiver will be brought out this year. There is practically no unit in radio receiving sets that will not be represented by new designs at the exposition. Grid leaks have been made airtight so that they are free from the influence of moisture; a new special steel has been utilized in making condenser coils, and new design in battery construction will make them more efficient and of longer life.

## In the Home

The place that radio is expected to occupy in the home this year is reflected in the many beautiful cabinet designs that will be shown for the first time. A leading manufacturer of the Neutrodyne group will show a five-tube set in a cylindrical cabinet, little larger than a clock.

# NO DIALS ON THE NEW L-3 ULTRADYNE

By M. L. Muhleman



The L-3 Ultradyne.

R. E. Lacault, chief engineer of the Phenix Radio Corporation, has designed a set conspicuous for its absence of knobs and dials and prominent for its absence of mechanical appearance.

The photograph shows a front view of this new set, the Model L3 Ultradyne. The circular grill conceals the speaker horn, which is directly behind it, and serves as a scaling for the two station finders that run along its periphery.

These station finders, the only tuning controls, are levers with small handles at their ends. You cannot see the levers but the small handles are visible near the top of the grilling.

All one has to do to tune the set is to grasp these two handles and move them upwards or downwards until he hears the station he wants. The periphery is calibrated.

## Nature of Controls

There is a volume control, operated by a small knob, just to the right of the grill so that one can have his program rendered soft, medium or loud, as he may wish. When this knob is turned full to the left the A battery circuit is opened, thus the set is placed out of operation.

A small jack mounted to the left of the grill serves as a head phone connection and when a plug is inserted the loud speaker is automatically disconnected.

The cabinet is made of 5-ply mahogany veneer and is a rich brown color. It is 24 inches long, 14 inches high and 14 inches deep.

This set utilizes six vacuum tubes of the storage battery type. Three of them function as radio-frequency amplifiers, one as the detector and two as the audio-frequency amplifiers. The filaments of the tubes are controlled automatically.

Two of the radio-frequency stages are tuned and the third is fixed. A resist-ance system of tube stabilization is employed, which prevents these circuits from oscillating at resonance points.

## Use SLW Condensers

The "bunching" of stations of low wavelength within a small area on the scales, has been eliminated by the use of the Ultra Low-loss variable condensers which have a straight-line wavelength curve. The wavelengths are evenly distributed over the entire scale readings.

The speaker unit is specially designed to have the same impedance value as that of the audio-frequency stages. This electrical matching eliminates distortion and at the same time increases the output volume.

Either an indoor or an outdoor aerial can be used with the new Ultradyne, in fact a wire run around the moulding of a room is highly satisfactory for average purposes.



A SET manufacturer's plant these days is an imposing looking place, reflecting the enormity of the industry. The photo shows workers assembling condensers. Radio gives employment to many thousands of such workers. (Fotograms).

# Second Radio World's Fair Opens Monday With a Bang

The second great Radio World's Fair opens Monday, September 14, in the 258th Field Artillery Armory, New York City, the largest auditorium on earth.

The second Radio World's Fair pays testimony and tribute also to the interest now displayed by the women of the country, in fact, in all lands, in radio. They now look upon radio as an indispensable factor in their homes, for the entertainment and information that comes through the other end, as amply demonstrated by the competition to determine the Radio Diana, are experts in tuning in far distant stations and writing their impressions of what radio means to them and to mankind as a whole.

A contest to select the Radio Diana will be determined. This has proven the most popular ever conducted in connection with the new science and the winners of first, second and third prizes will win national and international honors. The winner will come to New York to be presented with a silver cup by Gov. Alfred E. Smith, who will open the exposition on the evening of Sept. 14, on behalf of the management and the radio fans of the United States.

Gov. Smith's address will deal with radio's contribution to the cause of good government and general enlightenment. It will be broadcast.

### Much Broadcasting

The second Radio World's Fair will be notable for the broadcasting of special features. The metropolitan stations will participate in this, the most elaborate program of its kind ever arranged by a radio show. The immense size of the armory permits each station to have a studio and reception room where well-known announcers and artists will meet their hitherto invisible friends.

In the center of the armory will be a glass enclosed broadcasting studio, in use at all hours, that everyone may see as well as hear the artists and speakers. J. Andrew White will be director of broadcasting.

The second Radio World's Fair is the official show of the Radio Manufacturers' Association, 300 members of which will participate in the conferences and discussions at the exhibition. They will meet nearly 5000 dealers and jobbers, who have accepted invitations to attend the fair. Some will come from west of the Mississippi.

### Industry Lends a Hand

Executives and employes of radio factories and salesmen from a thousand stores will also participate. One hundred large industrial concerns are distributing tickets among their employes.

The usual set-building contests for amateurs, code competitions for the "hams," and the other regular features of a radio show are on the program.

The amateur operator who heard the MacMillan Expedition most times will be presented with a silver cup on Sept. 18. Nightly communication will be maintained with MacMillan from the fair.

Probably on opening night Graham McNamee, popular announcer, will be awarded a gold cup emblematic of 1925 honors he won in a contest.

The 258th Field Artillery Armory is located at Kingsbridge Road and Jerome Avenue.

The big fair will be open to the general public from 1 to 11 P. M. daily and, as in 1924, the exclusive "jobbers and dealers' hours" will be from 11 A. M. to 1 P. M. daily.

The Army and the Navy will have

elaborate exhibits of apparatus, old and new.

Diplomatic and consular representatives of thirty nations will be guests, and many of them will take special pride in exhibits from their own countries. Stage and screen stars will be present at all sessions.

It is due to the far-seeing and painstaking efforts of U. J. Herrmann, managing director, and his associates in various capacities, that such a splendid opportunity is given to the public to see all that is new and much that made previous history in radio. Closely identified with Mr. Herrmann was an experienced show director, James F. Kerr, whose death last June stunned friends from one end of the country to the other. On August 1 Clay Irwin was appointed general manager to fill the vacancy. Mr. Irwin has become a partner of Mr. Herrmann in the management of the annual Radio World's Fair and the Chicago Radio Exposition, the fourth of which will be held in November.

## Clarostat and Clarotuner

When you've been in the radio game for quite a long time, and you've become pretty much hardened to "new" devices, and you suddenly run across a little instrument that makes you sit right up and take notice—well, that's worth a story. Hence this tale about the Clarostat and its cousin the Clarotuner, both products of the American Mechanical Laboratories of Brooklyn, N. Y.

The first stop on the tour through the factory was at a unique demonstration board. Meters are so rigged on this testing machine that the comparative functioning of a Clarostat and any other variable resistance is seen at a glance. A portion of this board is reserved for the same kind of visual test of the Clarotuner in competition with any other similar tuning device. It's all very simple after you get the hand of the thing.

To make a long story short, the Clarotuner brought the circuit right up to the oscillation point, right up to within a very shade of it, and held it there. No trouble at all—but just the same the other tuning units sort of put their tails between their legs and gave it up for a bad job. The Clarostat did its job like a man, too. The dials showed a remarkably gradual resistance change when the knob was turned. Other resistance devices were noticeably jerky.

The reason for the results just noted became obvious at the next stop, where a Clarostat had been opened up and its parts scattered about on a display board. The precision manufacture apparent in all the parts, from the main spindle to the smallest stamping, would do credit to a watch. It all just goes to show that, even in radio, it's worth doing things well.


Tested and Approved by RADIO WORLD Laboratories

### C. S. ANDERSON IN NEW POST

C. S. Anderson, managing editor of the first radio magazine in this country, "The Wireless Age," has accepted a similar position with the Waverly Co., 45 Rose Street, New York City, since the consolidation of "Wireless Age" with "Popular Radio." Mr. Anderson in his new field of activity manages a service intended to help publishers and advertisers in their publishing and printing requirements.

**BABY PORTABLE SET.** How to make it. See RADIO WORLD dated May 16, 1925 per copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, N. Y. C.

## Condenser Test

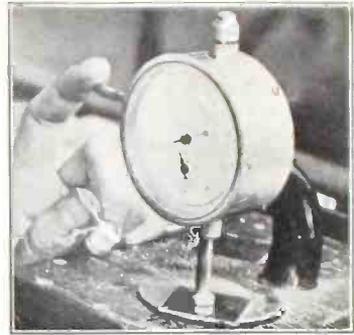

WHEN a mica fixed condenser is carefully made the thickness of the mica is measured with a meter and voltage is applied for electrical test. (International Newsreel)

# WORLD BATTERY STATION READY TO OPEN UP

Making its maiden bow and bid for popular favor is the 1000-watt broadcast transmitter sponsored by the World Battery Company of Chicago, operating under station call letters WSBC, on 210 meters, and constructed by the engineers of that concern. The World Battery Company Transmitter, as the new outfit is officially designated, is novel in many respects. The power for the operation is supplied entirely by storage batteries, made up of identically the same materials as are used in the standard, stock batteries supplied to radio users for the operation of receiving sets. The B or tube plate supply of 2,400 volts is furnished by the equivalent of over 400 ordinary receiving 6-volt A batteries made up of the same parts that are used in the unit familiar to all radio fans. By an ingenious switch arrangement these can be connected in straight series to operate the set or in series parallel for charging.

The C or biasing batteries as well as those used for the microphone circuits are made up of the parts used in the standard 24-volt units such as are used for the B supply in receiving sets.

The new station will be located on the roof garden of the New Southern Hotel, 13th Street and South Michigan Avenue, Chicago, and will be on the air every night beginning September 15.

## Business Opportunities Radio and Electrical

Rates: 50c. a line; Minimum, \$1.00

**RETAIL RADIO, ELECTRIC SUPPLY,** wants partner, experience, invest \$5,000 to \$10,000; stand thorough investigation; long lease; wish to expand. Box BB, RADIO WORLD.

**RADIO AND SPORTS GOOD STORE** in busy shopping section, near Penn station, subway, "L" and tubes, car and bus lines; rent \$5,000 year; will sell for cost of merchandise and fixtures plus \$2,000 for good will; owner engaged in other business. Box CC, RADIO WORLD.

**ELECTRICAL ENGINEER** has perfected entirely new radio loud-speaker; has no horn, operates like sounding board; extremely simple; cheap to manufacture; expert musicians say quality is perfect; appearance is especially pleasing; party with capital will find in this exceptional opportunity for quick returns; references and complete information gladly furnished. Box DD, RADIO WORLD.

# THE RADIO TRADE

## Exports More Than Double For the First Half of the Year

WASHINGTON.

Exports of radio equipment from the United States during January to June, 1925, inclusive, totalled \$4,068,442, an increase of \$2,242,196 over the total of \$1,826,246 for the same months of 1924, according to the Electrical Equipment Division of the Department of Commerce. The marked growth which is taking place in the exports of radio apparatus from the United States is further evidenced by a comparison of shipments of \$6,050,914 during the entire year of 1924 with those of the first six months of the current year which amounted to \$4,068,442. Thus radio exports for the first half of 1925 reached approximately 68 per cent of the 1924 total.

Although exports of radio apparatus for each of the first six months of 1925 have not always exceeded those of the preceding month, they have consistently been considerably in excess of the shipments made during the same month of 1924. The largest increase during the same months of 1924 and 1925 occurred in April, exports totalling \$229,903 and \$853,148 respectively. Average monthly exports for the first six months of 1925 are \$678,074, an increase of \$373,700 over the monthly average of \$304,374 for the corresponding period of 1924.

During the first six months of 1925, Europe and Canada maintained their position as the most important foreign markets for radio apparatus of American origin. Shipments to Europe during the first six months of the current year totalled \$674,571, an increase of \$429,038 over the corresponding period of 1924 and an increase of \$146,419 over the entire year of 1924.

Great Britain and Spain were the leading European markets during the first half of the current year, while for 1924, Great Britain ranked first and Sweden second. Exports of radio apparatus to Great Britain during the first six months of 1925 were almost twice those made during the entire year 1924, due largely to the lifting of the radio ban in that country on January 1, 1925. Shipments to Spain during the first half of 1925 were also almost twice those of the entire preceding year. This volume of business has been built up by American radio manufacturers and exporters through the sale of quality goods, and although European radio manufacturers have been competing in this market, the purchasers have consistently preferred sets and parts of American origin.

### NEW CORPORATIONS

- Mackenzie Radio Corp., N. Y. City, \$50,000; P. B. Klugh, I. C. Gaverick, M. E. Schafer (Atty.), Bash & Kulkin, 1,265 B'way, N. Y. City.)
- Walcome Radio Mfg. Co., N. Y. City, \$10,000; H. Weedenbaum, M. J. Kanin, G. Weiss, (Atty., G. F. Frankel, 19 West 44th St., N. Y. City.)
- Rexco Corp., radio, N. Y. City, 200 shares, \$10 each; 200 common, no par; I. F. Seigler, A. N. Feinberg, W. R. Lightfoot. (Atty., Jones & Weuberger, 115 B'way, N. Y. City.)
- Radio Grand Corp., N. Y. City, radio, \$10,000; B. J. Greenbaum, M. W. Weintraub, L. W. Graham. (Atty., M. Neufeld, 291 B'way, N. Y. City.)
- McPhibben Radio Corp., Jamaica, N. Y., 750 shares, \$11 each, to 1000 common, no par, and 700, \$100 each.

### Coming Events

- SEPT. 12 to 19—Fourth Annual National Radio Exposition, Grand Central Palace, N. Y. C. Write American Radio Exp. Co., 522 Fifth Ave., N. Y. C.
- SEPT. 14 to 19—Second Radio World's Fair, 258th Field Artillery Armory, Kingsbridge Road and Jerome Ave., N. Y. C. Write Radio World's Fair, Times Bldg., N. Y. C.
- SEPT. 14 to 19—Pittsburgh Radio Show, Motor Square Garden. Write J. A. Simpson, 420 Bessemer Bldg., Pittsburgh, Pa.
- SEPT. 14 to 18—Radio Show, Winnipeg, Can., Canadian Expos. Co.
- SEPT. 21 to 26—First Annual Radio Expos., Broadcast Listeners' Association, Cadle Tabernacle, Indianapolis, Ind. Write Claude S. Wallin, Hotel Severin.
- SEPT. 21 to 29—International Radio Exposition, Steel Pier, Atlantic City, N. J.
- SEPT. 28 to Oct. 3—National Radio Exposition, American Exp. Palace, Chicago. Write N. R. E., 440 S. Dearborn St., Chicago, Ill.
- SEPT. 28 to OCT. 3—Midwest Radio Week.
- OCT. 3 to 10—Radio Exposition, Arena, 46th and Market Streets, Philadelphia, Pa., G. B. Boden-hof, manager, auspices Philadelphia Public Ledger.
- OCT. 5 to 10—Second Annual Northwest Radio Exposition, Auditorium, St. Paul, Minn. Write 515 Tribune Annex.
- OCT. 5 to 10—Second Annual Radio Show, Convention Hall, Washington, D. C. Write Radio Merchants' Association, 233 Woodward Bldg.
- OCT. 10 to 16—National Radio Show, City Auditorium, Denver, Colo.
- OCT. 12 to 15—Radio exposition, Post-Dispatch (KPRC), Houston, Tex.
- OCT. 12 to 17—Boston Radio Show, Mechanics' Hall. Write to B. R. S., 209 Massachusetts Ave., Boston, Mass.
- OCT. 12 to 17—St. Louis Radio Show, Coliseum. Write Thos. P. Convey, manager, 737 Frisco Bldg., St. Louis, Mo.
- OCT. 12 to 17—Radio Show, Montreal, Can., Canadian Expos. Co.
- OCT. 17 to 24—Brooklyn Radio Show, 23d Regt. Armory. Write Jos. O'Malley, 1157 Atlantic Ave., Brooklyn, N. Y.
- OCT. 19 to 25—Second Annual Cincinnati Radio Exposition, Music Hall. Write to G. B. Boden-hof, care Cincinnati Enquirer.
- OCT. 26 to 31—First Annual Rochester Times-Union Radio Exposition, Convention Hall, Rochester, N. Y. Write Howard H. Smith, care Times-Union.
- NOV. 2 to 7—Radio Show, Toronto, Can., Canadian Expos. Co.
- NOV. 3 to 8—Radio Trade Association Exposition, Arena Gardens, Detroit. Write Robt. J. Kirschner, chairman.
- NOV. 19 to 25—Milwaukee Radio Exp., Civic Auditorium. Write Sidney Neu, of J. Andrae & Sons, Milwaukee, Wis.
- NOV. 17 to 22—4th Annual Chicago Radio Exp., Coliseum. Write Herrmann & Kerr, Cort Theatre Bldg., Chicago, Ill.

### Literature Wanted

THE names of readers of RADIO WORLD who desire literature from radio jobbers and dealers are published in RADIO WORLD on request of the reader. The blank below may be used, or a post card or letter will do instead.

Trade Service Editor,  
RADIO WORLD,  
1493 Broadway, New York City.

I desire to receive radio literature.

Name .....

City or town.....

State .....

Are you a dealer?.....

If not who is your dealer?

His Name .....

His Address .....

- S. W. Sullivan, Eric, Pa.
- W. M. Dodd, 74 N. 24th St., Portland, Ore.
- W. A. Schulze, 582 20th St., Milwaukee, Wis.
- Nelson Greer, Lake Wood Park, Lake View, Ia.
- Ralph N. Chambers, 619 5th St., Albion, Neb.
- J. D. Boyd, Fayetteville, N. C.
- Lavex Chemical Co., Kansas City, Mo. (Dealer).
- Edward A. Lambert, 2122 Park Ave., Chicago, Ill.
- John Hartl, 1910 South K St., Tacoma, Wash.
- R. F. Scheibeck, 244 Locust St., Chillicothe, O. (Dealer).
- Edwin J. Wall, 917 Gates Ave., Brooklyn, N. Y.
- H. Younger, Weseville, Pa.
- Frank Adams, 1830 Post St., Jacksonville, Fla.
- V. J. Stoltz, South Amboy, N. J.
- Thomas E. Jackson, 820 Harrison St., Indianapolis, Ind.
- H. A. Worden, 10 W. 3rd St., Tulsa, Okla.
- Adolph Souček, Bladen, Neb. (Dealer).

### A 1926 Show Planned

The International Radio Exposition, which is to be a brand new type of industrial exhibition, is scheduled to take place in New York City early next year under the management of Calvin Harris, who recently resigned as Publicity Director of the second Radio Chicago World's Fair and the fourth Annual Chicago Radio Show. The dates will be January 25 to 30, 1926, but the location has not yet been selected. If satisfactory arrangements can be made the show will take place in the Ringling-Rickard Garden now under construction.

The new enterprise primarily will be devoted to the interests of the general public. There will be twelve selected manufacturers' exhibits.

RECENT BACK NUMBERS of RADIO WORLD, 15 cents each, or any seven for \$1. Address Circulation Manager, RADIO WORLD, 1493 Broadway, New York City.

FILL OUT AND MAIL NOW  
SUBSCRIPTION BLANK

## RADIO WORLD

RADIO WORLD

1493 Broadway, New York City

Please send me RADIO WORLD for ..... months, for which

please find enclosed \$.....

SUBSCRIPTION RATES:

Single Copy.....\$ .15

Three Months..... 1.50

Six Months..... 3.00

One Year, 52 Issues..... 6.00

Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.

# THE KEY TO THE AIR

## KEY

Abbreviations: EST, Eastern Standard Time; CST, Central Standard Time; MST, Mountain Standard Time; PST, Pacific Standard Time; DS, Daylight Saving Time.

How to tune in a desired distant station at just the right time—Choose your station from the list published herewith. See what time division the station is under (EST, CST, etc.); then consult the table below. Add to or subtract, as directed from the time as given on the PROGRAM. The result will be the same BY YOUR CLOCK that you should tune in, unless daylight saving time interferences, as explained below.—The table:

If you are in	And want a station in	Subtract	Add
EST	CST	1 hr.	..
EST	MST	..	2 hrs.
EST	PST	..	3 hrs.
CST	EST	1 hr.	..
CST	MST	..	1 hr.
CST	PST	..	2 hrs.
MST	EST	2 hrs.	..
MST	CST	1 hr.	..
PST	EST	3 hrs.	1 hr.
PST	CST	2 hrs.	..
PST	DST	1 hr.	..

If you are under DST and the station you want is under that time, too, or if both are under ST, the above table will hold.

If you are under DST, and the station operates under ST, add one hour to the table result.

If the station uses DST, and you are under ST, subtract one hour from the table result.

## FRIDAY, SEPTEMBER 11

WAAM, Newark, N. J., 263 (ESTDS)—11 AM to 12  
 WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12 to 1:05 PM; 8 to 12 PM  
 WAMD, Minneapolis, Minn., 243.8 (SCT)—12 to 1 PM; 10 to 12  
 WBBM, Chicago, Ill., 226 (CST)—8 to 10 PM  
 WBBR, New York City, 272.6 (ESTDS)—8 PM to 10  
 WBOQ, Richmond Hill, N. Y., 236 (ESTDS)—7:30 PM to 11:30  
 WBZ, Springfield, Mass., 333.1 (ESTDS)—6 PM to 11  
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 to 4; 5:30 to 10  
 WCAE, Pittsburgh, Pa., 461.3 (ESTDS)—12:30 to 1:30 PM; 4:30 to 5:30; 6:30 to 11  
 WDAF, Kansas City, Kansas, 365.6 (CST)—3:30 to 7 M; 8 to 10; 11:45 to 1 AM  
 WFAF, New York City, 492 (ESTDS)—6:45 AM to 7:45; 11 to 12; 4 PM to 5; 6 to 12  
 WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 8 to 11  
 WEOA, Ohio State University, 293.9 (EST)—8 PM to 10  
 WEEI, Boston, Mass., 476 (ESTDS)—6:45 AM to 7:45; 2 PM to 3:15; 5:30 to 10  
 WEMC, Berrien Springs, Mich., 286 (CST)—9 PM to 11  
 WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30  
 WFBH, New York City, 272.6 (ESTDS)—2 PM to 6  
 WGBS, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 4; 6 to 11  
 WGPC, New York City, 252 (ESTDS)—2:30 PM to 5:15; 8 to 11  
 WGES, Chicago, Ill., 250 (CSTDS)—5 PM to 7; 10:30 to 1 AM  
 WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30  
 WGR, Buffalo, N. Y., 319 (ESTDS)—12 M to 12:45 PM; 7:30 to 10  
 WGY, Schenectady, N. Y., 379.5 (EST)—1 PM to 2; 5:30 to 10:30  
 WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8:30 to 10  
 WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9  
 WHN, New York City, 360 (ESTDS)—12:30 PM to 1; 2:15 to 5; 7 to 11; 12 to 12:30 AM  
 WHO, Des Moines, Iowa, 526 (CST)—7 PM to 9; 11 to 12; 12:30 to 1:30; 4:30 to 5:30; 6:30 to 9:30  
 WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 8:45 to 10:05; 10:30 to 1 AM  
 WIP, Philadelphia, Pa., 508.2 (ESTDS)—7 AM to 8; 1 PM to 2; 3 to 4:50; 6 to 7  
 WJY, New York City, 405 (ESTDS)—7:30 PM to 11:30  
 WJZ, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 6; 7 to 10:30  
 WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 12:30; 2 to 3; 4:30 to 6; 7:30 to 1 AM  
 WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15; 1:30 PM to 2:30  
 WMCA, New York City, 341 (ESTDS)—11 AM to 12M; 6:30 PM to 12  
 WNYC, New York City, 526 (ESTDS)—3:45 PM to 4:45; 6:20 to 11  
 WOAW, Omaha, Neb., 526 (CST)—12:30 PM to 1; 5:45 to 7:10; 9 to 11  
 WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 5:45 to 12  
 WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7  
 WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9  
 WPG, Atlantic City, N. J., 299.8 (ESTDS)—7 PM to 8:30; 10 to 12  
 WQO, Chicago, Ill., 448 (CST)—11 AM to 12 M; 8 PM to 4; 7 to 8 AM  
 WRC, Washington, D. C., 469 (EST)—4:30 PM to 5; 6:45 to 12

WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 11  
 WRNY, New York City, 258.5 (ESTDS)—11:59 to 2 PM; 7:59 to 9:45  
 WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12  
 WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 10; 12 PM to 1 AM  
 WWJ, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30; 3 to 4; 6 to 7; 8 to 10  
 KDKA, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:20 PM; 1:30 to 3:20; 3:30 to 11  
 KFAE, State College of Wash., 348.6 (PST)—7:30 PM to 9  
 KFDY, Brookings, S. D., 273 (MST)—8 PM to 9  
 KFI, Los Angeles, Cal., 467 (PST)—5 PM to 10  
 KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 9:30 to 12  
 KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10  
 KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 11  
 KGO, Oakland, Cal., 361.2 (PST)—11:10 AM to 1 PM; 1:30 to 3; 4 to 7  
 KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 12:30 PM; 5 to 11  
 KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:30 PM; 5:30 to 11:30  
 KJR, Seattle, Wash., 484.4 (PST)—10:30 AM to 11:30 AM; 1 PM to 6:30; 8:30 to 11  
 KNX, Hollywood, Cal., 337 (PST)—11:30 AM to 12:30 PM; 1 to 2; 4 to 5; 6:30 to 12  
 KOB, State College of New Mexico, 348.6 (MST)—11:55 AM to 12:30 PM; 7:30 to 8:30; 9:55 to 10:10  
 KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 8:45; 11 to 12 M  
 KPO, San Francisco, Cal., 429 (PST)—7:30 AM to 8; 10:30 to 12 M; 1 PM to 2; 4:30 to 11  
 KSD, St. Louis, Mo., 545.1 (CST)—4 PM to 5  
 KTHS, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:20 to 10  
 KYW, Chicago, Ill., 536 (CSTDS)—6:30 AM to 7:30; 10:55 to 1 PM; 2:25 to 3:30; 6:02 to 7:20; 9 to 1:30 AM  
 CNRA, Moncton, Canada, 313 (EST)—8:30 PM to 10:30  
 CNRE, Edmonton, Canada, 516.9 (MST)—8:30 PM to 10:30  
 CNRS, Saskatoon, Canada, 400 (MST)—2:30 PM to 3  
 CNRT, Toronto, Canada, 357 (EST)—6:30 PM to 11

## SATURDAY, SEPTEMBER 12

WAAM, Newark, N. J., 263 (EST)—7 PM to 11  
 WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12 to 2 AM  
 WAMD, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12  
 WBBM, Chicago, Ill., 226 (CST)—8 PM to 1 AM  
 WBBR, New York City, 272.6 (ESTDS)—8 PM to 9  
 WBOQ, Richmond Hill, N. Y., 236 (ESTDS)—3:30 PM to 6:30  
 WBZ, Springfield, Mass., 333.1 (ESTDS)—11 AM to 12:30 PM; 7 to 9  
 WCAE, Pittsburgh, Pa., 461.3 (ESTDS)—10:45 AM to 12M; 3 PM to 4; 6:30 to 7:30  
 WCBD, Zion, Ill., 344.6 (CST)—8 PM to 10  
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12:30 PM; 2:30 to 5; 6 to 10  
 WDAF, Kansas City, Kansas, 365.6 (CST)—6:45 AM to 7:45; 4 PM to 5; 6 to 12  
 WEEI, Boston, Mass., 476 (ESTDS)—6:45 AM to 7 AM  
 WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 7 to 8  
 WEMC, Berrien Springs, Mich., 286 (CST)—11 AM to 12:30 PM; 8:15 to 11  
 WFAA, Dallas, Texas, 475.9 (CST)—12:30 PM to 1; 6 to 7; 8:30 to 9:30; 11 to 12:30 AM  
 WFBH, New York City, 272.6 (ESTDS)—2 PM to 6  
 WGBS, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 3; 6 to 12  
 WGPC, New York City, 252 (ESTDS)—2:30 PM to 5:15  
 WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 3 to 5:57; 6 to 11:30  
 WGR, Buffalo, N. Y., 319 (ESTDS)—8:45 to 10:15 PM; U. S. Army Band  
 WGY, Schenectady, N. Y., 379.5 (EST)—7:30 PM to 10  
 WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:30 PM; 4 to 5; 6 to 7:30  
 WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9  
 WHN, New York City, 360 (ESTDS)—2:15 PM to 5; 7:30 to 10  
 WHO, Des Moines, Iowa, 526 (CST)—11 AM to 12:30 PM; 4 to 5:30; 7:30 to 8:30  
 WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 8:45 to 10:05; 10:30 to 1 AM  
 WIP, Philadelphia, Pa., 508.2 (ESTDS)—7 AM to 8; 1 PM to 2; 3 to 4; 6 to 11:30  
 WJY, New York City, 405 (ESTDS)—2:30 PM to 5; 8 to 10:30  
 WJZ, New York City, 455 (ESTDS)—9 AM to 12:30 PM; 2:30 to 4; 7 to 10  
 WKRC, Cincinnati, O., 326 (EST)—10 to 12 M; 12:30 PM; 7:30 to 10  
 WMAK, Lockport, N. Y., 265.5 (EST)—10:25 AM to 12:30 PM  
 WMCA, New York City, 341 (ESTDS)—3 to 5 PM; 6:30 to 2  
 WNYC, New York City, 526 (ESTDS)—1 to 3 PM; 7 to 11  
 WOAW, Omaha, Neb., 526 (CST)—10 AM to 1; 2:15 to 4; 9 to 11  
 WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 5:45 to 7:10; 9 to 12  
 WOO, Philadelphia, Pa., 508.2 (ESTDS)—11 AM to 1 PM; 4:40 to 5; 10:55 to 11:02

WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7:30; 8 to 11  
 WQJ, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 3 AM  
 WPG, Atlantic City, N. J., 299.8 (CST)—7 PM to 12  
 WRC, Washington, D. C., 469 (EST)—4:30 to 5:30 PM; 6:45 to 12  
 WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 12  
 WRNY, New York City, 258.5 (ESTDS)—11:59 to 2 PM; 7:59 to 9:30; 12 M to 1 AM  
 WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 3 to 4; 5 to 6; 10:45 to 12  
 WWJ, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10; 11:55 to 1:30 PM; 3 to 4  
 KDKA, Pittsburgh, Pa., 309 (EST)—10 AM to 12:30 PM; 1:30 to 6:30; 8:45 to 10  
 KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11  
 KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 9:30 to 12:30  
 KF.NF, Shenandoah, Iowa, 268 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10:30  
 KFOA, Seattle, Wash., 455 (PST)—Silent  
 KGO, Oakland, Cal., 361.2 (PST)—11 AM to 12:30 PM; 3:30 to 5:45; 7:30 to 9  
 KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11  
 KHJ, Los Angeles, Cal., 405.2 (ESTDS)—7 AM to 7:30; 10 to 1:30 PM; 2:30 to 3:30; 5:30 to 2 AM  
 KJR, Seattle, Wash., 484.4 (PST)—1 PM to 2:45; 6 to 6:30; 8:30 to 10  
 KNX, Hollywood, Cal., 337 (PST)—1 PM to 2; 6:30 to 2 AM  
 KOA, Denver, Colo., 322.4 (MST)—11:30 AM to 12:30 PM; 7 to 10  
 KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 9  
 KPO, San Francisco, Cal., 429 (PST)—8 AM to 12M; 2 PM to 3; 6 to 10  
 KSD, St. Louis, Mo., 545.1 (CST)—7 PM to 8:30  
 KTHS, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:30 to 10:30  
 KYW, Chicago, Ill., 536 (CSTDS)—11 AM to 12:30 PM; 4 to 5; 7 to 10  
 CKAC, Montreal, Canada, 411 (EST)—4:30 PM to 5:30  
 CNRO, Ottawa, Ontario, Canada, 435 (EST)—7:30 PM to 10  
 PWX, Havana, Cuba, 400 (EST)—8:30 PM to 11:30

## SUNDAY, SEPTEMBER 13

WBBM, Chicago, Ill., 226 (CST)—4 PM to 6; 8 to 10  
 WBBR, New York City, 272.6 (ESTDS)—10 AM to 12 M; 9 PM to 11  
 WCCO, St. Paul and Minneapolis, Minn., 416 (CST)—11 AM to 12:30 PM; 4:10 to 5:10; 7:30 to 9  
 WDAF, Kansas City, Kansas, 365.6 (CST)—4 PM to 5:30  
 WFAF, New York City, 492 (ESTDS)—3 PM to 5; 7:20 to 10:15  
 WEAR, Cleveland, O., 390 (EST)—3:30 PM to 8; 7 to 8; 9 to 10  
 WFBH, New York City, 272.6 (ESTDS)—5 PM to 8  
 WGBS, New York City, 316 (ESTDS)—3:30 PM to 4:30; 9:30 to 10:30  
 WGPC, New York City, 252 (ESTDS)—8 PM to 11  
 WGN, Chicago, Ill., 370 (CST)—11 AM to 12:46 PM; 2:30 to 5; 9 to 10  
 WGR, Buffalo, N. Y., 379.5 (EST)—9:30 AM; 7:15 to 8 PM  
 WGY, Schenectady, N. Y., 379.5 (EST)—9:30 AM to 12:30 PM; 2:35 to 3:45; 6:30 to 10:30  
 WHAD, Milwaukee, Wis., 275 (CST)—3:15 PM to 4:15  
 WHN, New York City, 360 (ESTDS)—1 PM to 1:30; 3 to 6; 10 to 12  
 WHT, Chicago, Ill., 238 (CSTDS)—9:30 AM to 1:15 PM; 5 to 9  
 WIP, Philadelphia, Pa., 508.2 (ESTDS)—10:45 AM to 12:30 PM; 4:15 to 5:30  
 WKRC, Cincinnati, O., 326 (EST)—6:45 PM to 11  
 WMCA, New York City, 341 (ESTDS)—11 AM to 12:15 PM; 7 to 7:30  
 WNYC, New York City, 526 (ESTDS)—9 PM to 11  
 WOCL, Jamestown, N. Y., 251.1 (EST)—9 PM to 11  
 WOO, Philadelphia, Pa., 508.2 (ESTDS)—10:45 AM to 12:30 PM; 2:30 to 4  
 WPG, Atlantic City, N. J., 299.8 (ESTDS)—3:15 PM to 5; 9 to 11  
 WQJ, Chicago, Ill., 448 (CST)—10:30 AM to 12:30 PM; 3 to 4; 8 to 10  
 WREO, Lansing, Michigan, 285.5 (EST)—10 AM to 11  
 WRNY, New York City, 258.5 (ESTDS)—3 PM to 5; 7:59 to 10  
 WSBF, St. Louis, Mo., 273 (CST)—9 to 11 PM  
 WWJ, Detroit, Mich., 352.7 (EST)—11 AM to 12:30 PM; 2 to 4; 6:20 to 9  
 KDKA, Pittsburgh, Pa., 309 (EST)—9:45 AM to 10:30; 11:55 to 12 M; 2:30 PM to 5:30; 7 to 11  
 KFNF, Shenandoah, Iowa, 266 (CST)—10:45 AM to 12:30 PM; 2:30 to 4:30; 6:30 to 10  
 KOA, Denver, Colo., 322.4 (MST)—10:55 AM to 1 PM; 4 PM to 5:30; 7:45 to 10  
 KOIL, Council Bluffs, Iowa, 278 (CST)—11 AM to 12:30 PM; 7:30 to 9  
 KGW, Portland, Oregon, 491.5 (PST)—10:30 AM to 12:30 PM; 6 to 9  
 KHJ, Los Angeles, Cal., 405.2 (ESTDS)—10 AM to 12:30 PM; 6 to 9  
 KJR, Seattle, Wash., 484.4 (PST)—11 AM to 12:30 PM; 3 to 4:30; 7:15 to 9  
 KTHS, Hot Springs, Ark., 374.8 (CST)—11 AM to 12:30 PM; 2:30 to 3:40; 8:40 to 11

## MONDAY, SEPTEMBER 14

WAAM, Newark, N. J., 263 (ESTDS)—11 AM to 12 M; 7 PM to 11

**WAHG**, Richmond Hill, N. Y., 316 (ESTDS)—12 PM to 1:05 PM; 8 to 2 AM.

**WAMB**, Minneapolis, Minn., 243.8 (CST)—10 PM to 12.

**WBMM**, Chicago, Ill., 226 (CST)—6 PM to 7.

**WBRR**, New York City, 272.6 (ESTDS)—8 PM to 9.

**WBZ**, Springfield, Mass., 333.1 (ESTDS)—6 PM 11:30.

**WCAE**, Pittsburgh, Pa., 461.3 (ESTDS)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 12.

**WCBD**, Zion, Ill., 344.6 (CST)—8 PM to 10.

**WCCO**, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 PM to 6:15.

**WDAF**, Kansas City, Kansas, 365.6 (CST)—3:30 PM to 7; 8 to 10; 11:45 to 1 AM.

**WEAF**, New York City, 492 (ESTDS)—6:45 AM to 7:45; 4 PM to 5; 6 to 11:30.

**WEAR**, Cleveland, O., 300 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 7 to 8.

**WEEL**, Boston, Mass., 476 (ESTDS)—6:45 AM to 8; 3 PM to 4; 5:30 to 10.

**WEMC**, Berrien Springs, Mich., 286 (CST)—8:15 PM to 11.

**WEAA**, Dallas, Texas, 475.9 (EST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30.

**WFBH**, New York City, 272.6 (ESTDS)—2 PM to 6:30.

**WGBS**, New York City, 316 (ESTDS)—10 AM to 11; 1:30 to 3:10; 6 to 7:30.

**WGES**, Chicago, Ill., 250 (CSTDS)—5 PM to 8.

**WGCF**, New York City, 252 (ESTDS)—2:30 PM to 5:18; 8 to 10:45.

**WGN**, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 5:57.

**WGR**, Buffalo, N. Y., 319 (ESTDS)—12 M to 12:30 PM; 2:30 to 4:30; 7:30 to 11.

**WGY**, Schenectady, N. Y., 379.5 (EST)—1 PM to 2; 5:30 to 8:30.

**WHAD**, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8 to 10.

**WHAS**, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.

**WHN**, New York City, 360 (ESTDS)—2:15 PM to 5; 6:30 to 12.

**WHO**, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 7:30 to 9; 11:15 to 12.

**WHT**, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.

**WIP**, Philadelphia, Pa., 508.2 (ESTDS)—7 AM to 8; 1 PM to 2; 3 to 8.

**WJZ**, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 5:30; 6 to 6:30; 7 to 11.

**WKRC**, Cincinnati, O., 326 (EST)—12:02 PM to 1; 2 to 3; 4:30 to 6; 7:30 to 11:30.

**WLW**, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15 PM; 1:30 to 2:30; 3 to 5; 6 to 10.

**WMAK**, Lockport, N. Y., 265.5 (EST)—8 PM to 12.

**WMCA**, New York City, 341 (ESTDS)—11 AM to 12 M; 6:30 PM to 12.

**WNYC**, New York City, 526 (ESTDS)—3:15 PM to 4:15; 6:20 to 11.

**WOAW**, Omaha, Neb., 526 (CST)—12:30 PM to 1:30; 5:45 to 10:30.

**WOC**, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 5:45 to 6.

**WOO**, Philadelphia, Pa., 508.2 (ESTDS)—11 AM to 1 PM; 4:40 to 6; 7:30 to 11.

**WOR**, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 to 4; 6:15 to 11:30.

**WPAK**, Fargo, N. D., 283 (CST)—7:30 PM to 9.

**WPG**, Atlantic City, N. J., 299.8 (ESTDS)—7 PM to 11.

**WQJ**, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4.

**WRC**, Washington, D. C., 469 (EST)—1 PM to 2; 4 to 6.

**WRPO**, Lansing, Michigan, 285.5 (EST)—10 PM to 11.

**WRNY**, New York City, 258.5 (ESTDS)—11:59 AM to 2 PM; 7:30 to 11.

**WSB**, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12.

**WSBF**, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 10:30; 12 to 1 AM.

**WWJ**, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 10.

**KDKA**, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:15 PM; 2:30 to 3:20; 5:30 to 10.

**KFAE**, State College of Wash., 348.6 (PST)—7:30 PM to 9.

**KFL**, Los Angeles, Cal., 467 (PST)—5 PM to 11.

**KFKX**, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30.

**KFNP**, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.

**KFOA**, Seattle, Wash., 455 (PST)—12:45 PM to 1:30; 4 to 5:15; 6 to 10.

**KGO**, Oakland, Cal., 361.2 (PST)—9 AM to 10:30; 11:30 AM to 1 PM; 1:30 to 6; 6:45 to 7; 8 to 1 AM.

**KGW**, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30; 5 to 8.

**KHJ**, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 1:30 PM; 5:30 to 10.

**KJR**, Seattle, Wash., 384.4 (PST)—1 PM to 2:45; 6 to 6:30; 7 to 11.

**KNX**, Hollywood, Cal., 337 (PST)—12 M to 1 PM; 4 to 5; 6:30 to 12.

**KOB**, State College of New Mexico, 348.6 (MST)—11:55 AM to 12:30 PM; 7:30 to 8:30; 9:55 to 10:10.

**KOIL**, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 10.

**KPO**, San Francisco, Cal., 429 (PST)—10:30 AM to 12 M; 1 PM to 2; 2:30 to 3:30; 4:30 to 10.

**KSD**, St. Louis, Mo., 545.1 (CST)—7:30 PM to 10.

**KTHS**, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:30 to 10.

With  
**IRVING HOFFMAN**  
at  
**WMCA**

Hotel McAlpin, New York, N. Y.



AV. LLUFRIO, CHIEF ANNOUNCER AND STUDIO DIRECTOR.



SNEDDEN WEIR, ANNOUNCER WAS FORMERLY WITH ROXY AND HIS GANG.



RALPH C. POWELL, CHIEF OPERATOR FORMERLY WROTE FOR RADIO WORLD.



MISS HELEN A. MORRIS, HOSTESS AND ACCOMPANIST, HAS A FINE SOPRANO VOICE.



JOSEPH WEBER, A SPLENDID SINGER AND ALL-AROUND PERFORMER.



MISS LINA LANZA, POSSESSOR OF A MOST BEAUTIFUL VOICE.



MARY MOODY, MISS LANZA'S TEACHER IS A MASTER OF PIANO TONE AND TECHNIQUE.

**WAHG**, Richmond Hill, N. Y., 316 (ESTDS)—12 PM to 1:05 AM.

**WAMB**, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12.

**WBMM**, Chicago, Ill., 226 (CST)—8 PM to 12.

**WBQO**, Richmond Hill, N. Y., 236 (ESTDS)—3:30 PM to 6:30.

**WBZ**, Springfield, Mass., 333.1 (ESTDS)—6 PM to 11.

**WCAE**, Pittsburgh, Pa., 461.3 (ESTDS)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 11.

**WCCO**, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 PM to 4; 5:30 to 10.

**WDAF**, Kansas City, Kansas, 365.6 (CST)—3:30 PM to 7; 11:45 to 1 AM.

**WEAF**, New York City, 492 (ESTDS)—6:45 AM to 7:45; 11 to 12 M; 4 PM to 5; 6 to 12.

**WEAR**, Cleveland, O., 300 (EST)—11:30 AM to 12:10 PM; 7 to 10; 10 to 11.

**WEEL**, Boston, Mass., 476 (ESTDS)—6:45 AM to 8; 1 PM to 2; 6:30 to 10.

**WFAA**, Dallas, Texas, 457.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30; 11 to 12.

**WFBH**, New York City, 272.6 (ESTDS)—2 PM to 6:30; 11:30 to 12:30 AM.

**WGBS**, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 3; 6 to 11:30.

**WGCF**, New York City, 252 (ESTDS)—2:30 PM to 5:15.

**WGN**, Chicago, Ill., 250 (CSTDS)—5 PM to 8; 10:30 to 1 AM.

**WGN**, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30.

**WGR**, Buffalo, N. Y., 319 (ESTDS)—11 AM to 12:45 PM; 7:30 to 11.

**WGY**, Schenectady, N. Y., 379.5 (EST)—11 PM to 2:30; 5:30 to 7:30; 9:15 to 11:30.

**WHAD**, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30.

**WHAS**, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.

**WHN**, New York City, 360 (ESTDS)—12:30 PM to 1; 2:15 to 3:15; 4 to 5:30; 7:30 to 10:45; 11:30 to 12:30 AM.

**WHO**, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 7:30 to 9; 11 to 12.

**WHT**, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.

**WIP**, Philadelphia, Pa., 508.2 (ESTDS)—7 AM to 8; 1 PM to 2; 3 to 4:30; 6 to 11.

**WJZ**, New York City, 455 (ESTDS)—7:30 PM to 1:30.

**WJZ**, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 6; 7 to 11.

**WKRC**, Cincinnati, O., 326 (EST)—6 PM to 12.

**WLIT**, Philadelphia, Pa., 395 (EST)—11 AM to 12:30 PM; 2 to 3; 4:30 to 7.

**WLW**, Cincinnati, O., 422.3 (EST)—10:45 AM to 1 PM; 1:30 to 2:30; 3 to 5; 6 to 11.

**WMAK**, Lockport, N. Y., 265.5 (EST)—11 AM to 12 M; 6:30 PM to 12.

**WNYC**, New York City, 526 (ESTDS)—3:45 PM to 5; 6:50 to 11.

**WOC**, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 5:45 to 10.

**WOO**, Philadelphia, Pa., 508.2 (ESTDS)—11 AM to 1 PM; 4:40 to 5; 10:55 to 11:02.

**WOR**, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7:30.

**WPG**, Atlantic City, N. J., 299.8 (ESTDS)—7 PM to 11.

**WQJ**, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 2 AM.

**WRC**, Washington, D. C., 469 (EST)—4:30 PM to 5:30; 6:45 to 11.

**WRPO**, Lansing, Michigan, 285.5 (EST)—8:15 PM to 11.

**WRNY**, New York City, 258.5 (ESTDS)—11:59 AM to 2 PM; 4:30 to 11.

**WSB**, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12.

**WSBF**, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 8 to 10; 11:30 to 1 AM.

**WWJ**, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 10.

**KDKA**, Pittsburgh, Pa., 309 (EST)—9:45 AM to 12:15 PM; 2:30 to 3:20; 5:30 to 10.

**KFAE**, State College of Wash., 348.6 (PST)—7:30 PM to 9.

**KFL**, Los Angeles, Cal., 467 (PST)—5 PM to 11.

**KFKX**, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30.

**KFNP**, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.

**KFOA**, Seattle, Wash., 455 (PST)—12:45 PM to 1:30; 4 to 5:15; 6 to 10.

**KGO**, Oakland, Cal., 361.2 (PST)—9 AM to 10:30; 11:30 AM to 1 PM; 1:30 to 6; 6:45 to 7; 8 to 1 AM.

**KGW**, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11.

**KHJ**, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:20 PM; 5:30 to 11.

**KJR**, Seattle, Wash., 384.4 (PST)—9 AM to 6:30 PM; 8:30 to 1 AM.

**KNX**, Hollywood, Cal., 337 (PST)—9 AM to 10; 1 PM to 2; 4 to 5; 6:30 to 12.

**KOIL**, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 9; 11 to 12 M.

**KPO**, San Francisco, Cal., 429 (PST)—7 AM to 7:45; 10 to 12 M; 1 PM to 2; 3:30 to 11.

**KSD**, St. Louis, Mo., 541.1 (CST)—6 PM to 7.

**KTHS**, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:30 to 10:30.

**KYW**, Chicago, Ill., 536 (CSTDS)—6:30 AM to 7:30; 10:55 to 1 PM; 2:15 to 3:30; 6:02 to 7.

**TUESDAY, SEPTEMBER 15**  
**WAAM**, Newark, N. J., 263 (ESTDS)—11 AM to 12 M; 7 PM to 11.

(Continued on page 29)

# Features of the Week

**FREE BOOKLET FOR INVENTORS**

IF YOUR INVENTION is new and useful it is patentable. Send me your sketch. Z. H. POLACHEK, 70 Wall St., New York.

Reg. Patent Attorney-Engineer



**\$3.25** RADIO Storage "B" Battery

Lasts Indefinitely—Pays for Itself

Economy and performance unheard of before. Recharged at a negligible cost. Approved and listed as Standard by leading Radio Authorities, including Pop. Radio Laboratories, Pop. Standard, Radio New Lab., Lefax, Inc., and other important institutions. Equipped with Solid Rubber Case, an insurance against acid and leakage. Extra heavy glass jars. Heavy, rugged plates. Order yours today!

SEND NO MONEY Just state number of batteries wanted and we will ship day order is received. Extra Offer: 4 batteries in series (66 volts), \$12.75. Pay expressman after examining batteries. 5 per cent discount for cash with order. Mail your order now!

**WORLD BATTERY COMPANY**  
1219 So. Wabash Ave., Dept. 82 Chicago, Ill.

Makers of the Famous World Radio "A" Storage Battery.  
Price: 6-cells, 100 Amp. \$11.25; 125 Amp. \$12.50; 140 Amp. \$14.00.  
All equipped with Solid Rubber Case.

**World STORAGE BATTERIES**

Set your Radio Dials at 210 meters for the new 1000 watt World Storage Battery Station, WBSB, Chicago. Watch for announcements.

WKA-WEAF-WGN-WJS-KHU-KGO-KFAX-WJW-KOP

**UNIVERSAL**  
A Universal precision instrument that meets ALL resistive needs.

WHEN reception is so indistinct that you must use imagination to get the sense, that's the time to install CLAROSTAT. CLAROSTAT across the transformer of your amplifier will clear up distortion. Installed in a moment and lasts a lifetime.

Ask about the new Clarostats American Mechanical Laboratories, Inc. 285 N. 6th St. Brooklyn, N. Y.

**CLAROSTAT**

\$2.25 LIST

**FRIDAY, SEPTEMBER 11**

WHT, Chicago, Ill., 238 (CSTDS)—8:45 to 10:15 PM, Elmer Kaiser's Review Park Ballroom orch.

WGBS, New York City, 315.6 (ESTDS)—7 PM to 7:10, Heiman Bernard, "Your Radio Problem."

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

WOO, Philadelphia, Pa., 508.2 (ESTDS)—7:30 PM to 8:30, dinner music by the Hotel Adelphia Roof Garden orch.

**SATURDAY, SEPTEMBER 12**

WEAF, New York City, 492 (ESTDS)—11 PM to 12 PM, Vincent Lopez orch.

KGW, Portland, Ore., 491.5 (PST)—10 PM to 12 PM, dance music from Portland Hotel by Jackie Souders' orch.

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

**SUNDAY, SEPTEMBER 13**

WBBM, Chicago, Ill., 206 (CST)—12 PM to 2 AM—Sunday, Midnight Nut Club Feature. Sanovar orch.

**MONDAY, SEPTEMBER 14**

WEAF, New York City, 492 (ESTDS)—9:15 PM to 10:15, Goldman Band concert; 11 to 12, Jack Alben and his Hotel Bossert orchestra.

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

WOO, Philadelphia, Pa., 508.2 (ESTDS)—7:30 PM to 8:30, dinner music by the Hotel Adelphia Roof Garden orch.

**TUESDAY, SEPTEMBER 15**

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

WEAF, New York City, 492 (ESTDS)—9 PM to 10: "Everyday Hour,"; 11 to 12 PM Vincent Lopez Pennsylvania orchestra.

WOO, Philadelphia, Pa., 508.2 (ESTDS)—7:30 PM to 8:30, dinner music by the Hotel Adelphia Roof Garden orch.

WEEL, Boston, Mass., 476 (ESTDS)—10 PM to 11—From New York, WEAF Grand Opera Company.

**WEDNESDAY, SEPTEMBER 16**

WHO, Des Moines, Ia., 526 (CST)—10 to 11:34 PM—The Barret-Philbreck Orch.

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

**THURSDAY, SEPTEMBER 17**

WEAF, New York City, 492 (ESTDS)—11 PM to 12 PM, Vincent Lopez Hotel Pennsylvania orch.

WGR, Buffalo, N. Y., 319 (ESTDS)—8 to 11 PM—Joint broadcasting with WEAF, N. Y. City, Atwater Kent Radio Artists, and Goodrich Silvertown Chord orch.

WIP, Philadelphia, Pa., 508.2 (ESTDS)—3 PM to 4: "Song of the Surf,"—surf sounds of Atlantic Ocean, picked up by special microphone, underneath the breakers of Steel Pier at Atlantic City, N. J.

WOO, Philadelphia, Pa., 508.2 (ESTDS)—7:30 PM to 8:30, dinner music by the Hotel Adelphia Roof Garden orch.

**Jones MULTI-PLUG**

THE STANDARD SET CONNECTOR

**HOWARD B. JONES**  
618 S. CANAL STREET CHICAGO

**WOUND WIRE AERIAL**

Sound theory, concerns the added capacity of the aerial wire itself. 43,000 turns to an aerial. It gets results. Radio owners write. Sample showing construction, 5 cents postpaid. Patent being solicited. Will sell interest to market big.

WOUND WIRE AERIAL COMPANY, Redville, Va.

**ANY RADIO MAP A MONTH OLD IS OUT OF DATE**

Unless it has a monthly supplemental service.

**The Air-Line Radio Map and Log**

With patented movable mile scale has this service. Lists stations by call letters, also by wave lengths.

**Unique Broadcasting Schedule Log**

Shows location; difference in time; power, meters and kilocycles. Spaces to list dial settings; time heard, distance, signal strength. Whether you use outdoor aerial or loop, direction of loop; phones or loud-speaker.

**An Individual Log for Every Station**

If you do not find this the most complete, serviceable RADIO MAP and LOG published, we will refund your money.

PRICE, 50 CENTS

At your dealers, or sent postpaid. Dealers and Jobbers, write at once.

**Multivider Co.** Askev and St. John Kansas City, Mo.

**A Satisfied Radio Dealer**

The Seal of

Satisfaction

**THE BOWER RADIO SHOP**  
READING, MICHIGAN

Gets quantity discounts, quick shipments, guaranteed products, reliable repairs, personal attention and real SERVICE. All of these things are represented by "THE SEAL OF SATISFACTION." Look for it! It appears on all radio supplies sold by us. It is your guarantee of satisfaction. Write us a card to-day. Just say I am interested in The Seal of Satisfaction, or send three two-cent stamps for our new Loose Leaf Catalog.

**GEM TUBE**

A Guaranteed Radio Tube Within Reach of All

Every tube guaranteed. A tube for a dollar of \$2 value. Trial order will convince you as it has thousands of others. Send your orders at once. Orders sent C.O.D. parcel post.

Type .201A  
Type .200  
Type .189  
Type .199A

(with standard base) EACH

Dealers. Write for Discounts

**GEM TUBE CO.**

Dept. W, 200 Broadway, N. Y. C.  
220 So. State St., Chicago, Ill.  
Lafayette Bldg., Detroit, Mich.

**Mailing Lists**

Will help you increase sales. Send for FREE catalog giving counts and prices on classified names of your best prospective customers—National, State, Local—Individuals, Professions, Business Firms.

99% Guaranteed 5c each by refund of 5c each

**ROSS-GOULD CO.** 10th St. St. Louis

**S. HAMMER RADIO CO.**  
303 Atkins Avenue, Brooklyn, N. Y.

Please send me FREE Your NEW RADIO CATALOG

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

FILL OUT AND MAIL

**At Last Your Reflex Trouble Is Over**

**Goucher's Micrometer Rectifier**

and Super-Sensitive Crystal is the most efficient rectifier known.

Your detector is just as important as the carburetor is on your automobile engine.

Send P. O. Money Order \$3.00 or we will send C. O. D.

**GUARANTEE:** Try it one week. Money back if this rectifier does not respond on your reflex circuit or crystal set beyond your expectation.

**JAMES L. GOUCHER & COMPANY**  
11 SPRINGFIELD AVENUE, NEWARK, N. J.

**1925 BACK NUMBERS OF RADIO WORLD WANTED**

Mail us copies of any of the following 1925 issues of RADIO WORLD, and we will send you a copy of a current issue for every copy sent us: January 10, February 7, March 21, 28; April 4, 11; May 30.

# THE KEY TO THE AIR

(Continued from page 27)

CNRR, Regina, Saskatchewan, Canada—8 PM to 11.

## WEDNESDAY, SEPTEMBER 16

WAAM, Newark, N. J., 263 (ESTDS)—11 AM to 12 M; 7 PM to 11.  
 WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12 M to 1:05 PM; 8 to 12.  
 WAMB, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12.  
 WBBM, Chicago, Ill., 226 (CST)—8 PM to 10.  
 WBZ, Springfield, Mass., 333.1 (ESTDS)—6 PM to 11.  
 WCAE, Pittsburgh, Pa., 461.3 (ESTDS)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 11.

WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 to 4; 5:30 to 11.  
 WDAF, Kansas City, Kansas, 365.6 (CST)—3:30 PM to 7; 8 to 9:15; 11:45 to 1 AM.  
 WEAJ, New York City, 492 (ESTDS)—6:45 AM to 7:45; 11 to 12 M; 4 PM to 5; 6 to 12.  
 WEOA, Ohio State University, 293.9 (EST)—8 PM to 10.  
 WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 6:45 to 7:45.  
 WEEL, Boston, Mass., 476 (ESTDS)—6:45 AM to 8; 3 PM to 4; 5:30 to 10.  
 WEMC, Berrien Springs, Mich., 266 (CST)—8:15 PM to 11.  
 WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1.  
 WFBH, New York City, 270.6 (ESTDS)—2 PM to 7:30; 12 M to 1 AM.  
 WGCP, New York City, 252 (ESTDS)—2:30 PM to 5:18; 8 to 10.  
 WGES, Chicago, Ill., 250 (CSTDS)—5 PM to 7; 10:30 to 1 AM.  
 WGBS, New York City, 316 (ESTDS)—10 AM to 11 PM; 1:30 to 4; 6 to 7.  
 WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30.  
 WGR, Buffalo, N. Y., 319 (ESTDS)—12 M to 12:45 PM; 2:30 to 4:30; 6:30 to 11.  
 WGY, Schenectady, N. Y., 379.5 (CST)—5:30 PM to 7:30.  
 WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8 to 10; 11:30 to 12:30 AM.  
 WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.  
 WHN, New York City, 368 (ESTDS)—2:15 PM to 5:30; 7:30 to 11; 11:30 to 12:30 AM.  
 WHO, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 6:30 to 12 M.  
 WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.

WIP, Philadelphia, Pa., 568 (ESTDS)—7 AM to 8; 10:20 to 11; 1 PM to 2; 3 to 4; 6 to 8.  
 WJZ, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 6; 6 to 11:30.  
 (Continued on next page)

# ACME

for amplification

## THE ROYAL

TYPE 201-A TUBE

5 Volts **98c**  
22 Amps

### DETECTOR, RADIO OR AUDIO AMPLIFIER

A Tube of Exceptional Quality  
FULLY GUARANTEED

Please Send Money Order—No Stamps

## MAGNITE LABORATORIES

P. O. Box 472 NEWARK, N. J.

OUR NEW CATALOGUE

Just completed—listing hundreds of BARGAINS, will be mailed to you upon receipt of name and address—

GET YOUR NAME ON OUR MAILING LIST

SIMPLEX RADIO SUPPLY CO.

1806 LAFAYETTE AVE. Dept. D ST. LOUIS, MO.

Developed for Those Who Demand the Best

### Apex Vernier Dials

are constructed on exhaustively tested and truly scientific principles and are engineered to meet the precise requirements of experts—consequently they more than meet the expectations of the average radio user. They bring in distant stations with alacrity and positiveness seldom encountered and provide control and accuracy essential to full radio enjoyment. They impart a degree of elegance that creates a marked improvement in the appearance of any set. Clockwise or counter clockwise.

Royal Brass Finish, 4in. \$2.00; 3 1/4 in. \$1.65  
 Satin Silver Finish, 4in. 2.50; 3 1/4 in. 1.90  
 DeLuxe Gold (24K) 4in. 3.00; 3 1/4 in. 2.50

### Apex Rheostat Dials

are little brothers to Apex Vernier Dials. Accurate, handsome—a necessity to satisfactory operation, beauty of appearance.

Royal Brass Finish ..... \$ .75  
 Satin Silver Finish ..... .85  
 DeLuxe Gold (24K) ..... 1.00

If your dealer is unable to supply you, order direct from us.

APEX ELECTRIC MFG. CO.

1410 W. 59th St., Dept. 23 : Chicago

# THE TODD "B" BATTERY

MOST ECONOMICAL **OUTFIT EVER BUILT**

The 100 Volt Unit

## TEN

# Facts!

- 1—TODD "B" BATTERY challenges any substitute battery to equal it in performance.
- 2—With a TODD "B" reception is the clearest obtainable.
- 3—TODD "B" has tens of thousands of satisfied users.
- 4—Most economical both in cost and up-keep.
- 5—Recharging cost—practically nil.
- 6—The ONLY Radio Product, since Radio achieved popularity, to "hold its own."
- 7—A product absolutely GUARANTEED against mechanical defects.
- 8—A battery O'Ked and recommended by Radio Authorities and the PRESS.
- 9—Accredited as being "the everlasting 'B' battery."
- 10—A product the Radio world is proud of.

Don't Fail to Own One

THE TODD ELECTRIC CO., Inc.

36 W. 20th Street  
(Tel. Watkins 9266)  
New York

# COMING!

## RADIO WORLD'S 4th Annual Fall Buyers' Number!

Dated October 3, 1925. Last form closes September 22

### EVERY READER A BUYER OF RADIO GOODS

Advertisers have found that Radio World's FALL BUYERS' NUMBER of former years were business-bringing issues. The 1925 FALL BUYERS' NUMBER will be much better than the former issues, as our regular editions now are improvements over those of former years.

Use space in this goods-selling issue and reach the thousands of purchasers of sets and parts who are contemplating buying radio goods for the first time, or are about to change their radio equipment.

Regular advertising rates in force for an enlarged edition and sale.

Advertising rates: \$300 a page, \$150 one-half page, \$75 one-quarter page, \$100 1 column, \$10 per inch.

If copy for page is received by September 21 it will be printed, on request, in an extra color without extra cost.

Get in your order and copy now for Radio World's 4TH ANNUAL FALL BUYERS' NUMBER, and cash in on its profit-making circulation.

(Continued from page 29)

WKRC, Cincinnati, Ohio, 326 (EST)—8 PM to 10.  
 WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 12:30; 2 to 3; 4:30 to 6; 7:30 to 9.  
 WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15 PM; 1:30 to 2:30; 3 to 5; 6 to 11.  
 WMCA, New York City, 341 (EST)—10:45 AM to 12 M; 6:30 PM to 12.  
 WNYC, New York City, 526 (ESTDS)—6:30 PM to 11.  
 WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 4 to 7:05; 9 to 11.  
 WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 12 M.

WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9.  
 WOJ, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 2 AM.  
 WRC, Washington, D. C., 469 (EST)—1 PM to 2; 4 to 6:30.  
 WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 11.  
 WRNY, New York City, 258.5 (ESTDS)—11:59 AM to 2 PM; 7:59 to 9:55.  
 WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 5:30; 5 to 6; 10:45 to 12.  
 WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 9.  
 WWJ, Detroit, Mich., 352.7 (EST)—6 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 7; 8 to 10.  
 KDKA, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:15 PM; 2:30 to 3:20; 5:30 to 11.  
 KFAE, State College of Wash., 348.6 (PST)—7:30 PM to 9.  
 KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11.  
 KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30 AM.  
 KFMQ, Fayetteville, Ark., 299.8 (CST)—7:30 PM to 9.  
 KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.  
 KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 10.  
 KGO, Oakland, Cal., 361.2 (PST)—11:30 AM to 1 PM; 1:30 to 2:30; 3 to 6:45.  
 KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 10.  
 KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 1:30 PM; 5:30 to 12.  
 KJR, Seattle, Wash., 484.4 (PST)—9 AM to 1 AM.  
 KNX, Hollywood, Cal., 337 (PST)—1 PM to 2; 7 to 12.  
 CNRO, Ottawa, Ontario, Canada, 435 (EST)—7 PM to 11.

**THURSDAY, SEPTEMBER 17**

WAAM, Newark, N. J., 263 (ESTDS)—11 AM to 12 M; 7 PM to 11.  
 WAHG, Richmond Hill, N. Y., 316 (EST)—12 PM to 1:05.  
 WAMB, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12 M.  
 WBBM, Chicago, Ill., 226 (CST)—8 PM to 10.  
 WBOQ, Richmond Hill, N. Y., 236 (ESTDS)—3:30 PM to 6:30.  
 WBZ, Springfield, Mass., 333.1 (ESTDS)—6 PM to 11:45.  
 WCAE, Pittsburgh, Pa., 461.3 (CSTDS)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 11.  
 WCBD, Zion, Ill., 344.6 (CST)—8 PM to 10.  
 WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 PM to 4; 5:50 to 10.  
 WEAF, New York City, 492 (ESTDS)—6:45 AM to 7:45; 11 to 12 M; 4 PM to 5; 6 to 12.  
 WEAR, Cleveland, O., 390 (EST)—10:30 AM to 12:10 PM; 3:30 to 4:15; 7 to 11.  
 WEEL, Boston, Mass., 467 (ESTDS)—6:45 AM to 7:45; 1 PM to 2; 2:30 to 10.  
 WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30; 11 to 1 AM.  
 WFBH, New York City, 226.6 (ESTDS)—2 PM to 7:30.  
 WGBS, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 4; 6 to 7:30.  
 WGCP, New York City, 252 (ESTDS)—2:30 PM to 5:15.  
 WGES, Chicago, Ill., 250 (CSTDS)—5 PM to 8; 10:30 to 1 AM.  
 WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30.  
 WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 11:30; 6 PM to 7:15; 8:30 to 11.  
 (Continued on next page)

**RADIO TUBES DIRECT**

**NO DEALER PROFIT**  
 Postage Prepaid—Satisfaction Guaranteed  
 ONE—"Goode" Two-o-one A Tube.....\$1.89  
 THREE—"Goode" Two-o-one A Tubes.....5.00  
 The above is a five volt, quarter-ampere tube for use on storage batteries and can be used either as a Detector or an Amplifier.  
**THE GOODE TUBE CORP., Inc.**  
 OWENSBORO (Dept. B), KENTUCKY

**RADIO MANUFACTURERS INVENTORS EXPERIMENTERS**

Mechanical Consultants. We develop your ideas, make models and manufacture.  
 (Mechanics assigned to work under customer's supervision if desired.)  
**MANUFACTURERS' & INVENTORS' ELECTRIC COMPANY**  
 228 West Broadway (Smith Bldg.) New York City

**CROSLEY**  
**RADIO CATALOG FREE**  
 Describes fully the complete line of radio frequency sets, regenerative sets (licensed under Armstrong U. S. Patent No. 1,118,149) and parts.  
 Write for Catalog Today.  
**THE CROSLEY RADIO CORPORATION**  
 POWEL CROSLEY, Jr., President  
 7408 Sassafras Street Cincinnati, Ohio

**The PERFECT RESISTANCE COUPLED AMPLIFIER**

**COMPLETELY ASSEMBLED EASY TO ATTACH**  
 3 Step Amplifier  
  
**TYPE 7 G PRICE \$11.00**  
 Amplifier Kits, 3 stage.....\$6.00  
 Amplifier Kits, 4 stage.....8.25  
 Paraffin sealed resistors, 500 ohms to 10 meg.  
**FREE hook-up, send for bulletin 67**  
 If your dealer cannot supply you, send direct to  
**GENERAL RESISTOR COMPANY**  
 153 WRIGHT STREET NEWARK, N. J.

**RADIO BOOKS You Want**

Add these books to your library and get good value from your radio. Any book sent postpaid on receipt of price.

Radio Telegraph and Telephone Receivers for Beginners.....\$0.75  
 Design Data for Radio Transmitters and Receivers—M. B. Sleeper......75  
 Wireless in the Home—De Forest......15  
 Commercial Type Radio Apparatus—M. B. Sleeper......75  
 A B C of Vacuum Tubes—Lewis.....1.00  
 Operation of Wireless Telegraph Apparatus......35  
 Lessons in Wireless Telegraphy......35  
 Radio Hookups—M. B. Sleeper......75  
 Construction of New Type Transatlantic Receiving Sets—M. B. Sleeper......75

Any book sent on receipt of price, postpaid. 20% discount on any two books of same title. The whole list of 9 books sent for

**\$5.25**

**THE COLUMBIA PRINT**  
1493 Broadway, New York City

**RADIO FANS**

**BUILD YOUR OWN**  
**"B" Battery Eliminator**  
 from Our Kit of Knock Down Parts  
 Can Be Assembled in One Hour

Large working blueprint furnished with each kit.  
 Operates from House Current

**COMPLETE LAYOUT**  
 Nothing Else to Buy **\$14.95**  
 Operates 100 Hours for 3 Cents

Please Send Money Order  
**MAGNITE LABORATORIES**  
 P. O. Box 472 Newark, N. J.

**8 DAY JEWELLED MOVEMENT**  
  
**Send Only 10¢**

**For This Latest Model Imported Jewelled Movement Watch**  
**Runs 8 Days with One Winding**  
 Only a down payment of 10c required and we make immediate shipment of this beautiful and serviceable watch.

**WE TRUST YOU**  
**Shipment Same Day**  
**No References Needed**

Elsewhere you would probably be required to pay upwards of \$16 for a full-jewelled open face 8 Day watch of this quality. Our price reduced to \$12 and you may pay it \$1 per week.  
 Make first payment only to postman when he delivers package.  
 Send name and address at once. Our money back and 20 year guarantee protect you.  
**E. O. Deelite Co., 530 B'way, New York**

**LESTRON**  
**THE REAL 110 VOLT TUBE**  
 Works Without Batteries  
**FOR A. C. or D. C. NO REWIRING**  
**LESTEIN CORPORATION**  
 2 BROADWAY N. Y. CITY

**Attention, Readers and Newsdealers!**

**READERS:** If you are going away on your vacation, and wish to have a complete file of RADIO WORLD, be sure to tell your newsdealer to put aside a copy of each issue until you return.

**NEWSDEALERS:** Your regular RADIO WORLD customers will undoubtedly want for file copies that they have missed while away on their vacations. The publisher suggests that each week you put aside copies of RADIO WORLD for these customers. They will consider this service.

Readers and newsdealers can get back numbers of any issue for the summer of 1925 at our regular price; or a subscription can be started with any back number published during the summer.

Circulation Manager, RADIO WORLD, 1493 Broadway, New York City.

# THE KEY TO THE AIR

(Continued from preceding page)

WGR, Buffalo, N. Y., 319 (ESTDS)—12 M to 12:45 PM; 2 to 4; 7:30 to 11.  
 WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8 to 10.  
 WHAS, Louisville, Ky., 399.6 (CST)—4 PM to 5; 7:30 to 9.  
 WHN, New York City, 360 (ESTDS)—2:15 PM to 5; 7:30 to 11; 11:30 to 12:30 AM.  
 WHO, Des Moines, Iowa, 526 (CST)—7:30 PM to 9; 11 to 12.  
 WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.  
 WIJ, New York City, 405 (ESTDS)—7:30 PM to 11:30.  
 WIJZ, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 6; 7 to 12 M.  
 WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 12:30; 2 to 3; 4:30 to 6; 8:30 to 9.  
 WLW, Cincinnati, O., 422.3 (EST)—10:40 AM to 12:15 PM; 1:30 to 5; 6 to 8; 10 to 11.  
 WMAK, Lockport, N. Y., 265.5 (EST)—11 PM to 1 AM.  
 WMCA, New York City, 341 (ESTDS)—11 AM to 12 M; 6:30 PM to 12.  
 WNYC, New York City, 526 (ESTDS)—3:15 PM to 4:15; 6:50 to 11.  
 WOAW, Omaha, Neb., 526 (CST)—12:30 PM to 1:30; 5:45 to 11.  
 WOC, Davenport, Iowa, 484 (CST)—12:57 AM to 2 PM; 3 to 3:30; 4 to 7:10; 8 to 9.  
 WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7.  
 WPG, Atlantic City, N. J., 299.8 (ESTDS)—7 PM to 11.  
 WQJ, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 2 AM.  
 WRC, Washington, D. C., 469 (EST)—1 PM to 2; 4 to 6:30.  
 WREO, Lansing, Michigan, 285.5 (EST)—8:15 PM to 9:45; 10 to 11.  
 WRNY, New York City, 258.5 (ESTDS)—11:59 AM to 2 PM; 7:39 to 10.  
 WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12.  
 WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 5 to 4; 8 to 9.  
 WWJ, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30; 3 to 4; 6 to 7; 8 to 9.  
 KDKA, Pittsburgh, Pa., 309 (EST)—9:45 AM to 12:15 PM; 2:30 to 3:30; 5:30 to 10:15.  
 KFAE, State College of Washington, 348.6 (PST)—7:30 PM to 9.  
 KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11.  
 KFXX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30.  
 KPNP, Shenandoah, Iowa, 266 (CST)—12:15 to 1:15 PM; 3 to 4; 6:30 to 10.

KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 7.  
 KGO, Oakland, Cal., 361.2 (PST)—11:30 AM to 1 PM; 1:30 to 3; 4 to 6:45; 7:15 to 10.  
 KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11.  
 KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:20; 5:30 to 11:30.  
 KJR, Seattle, Wash., 484.4 (PST)—9 AM to 1 AM.  
 KNX, Hollywood, Cal., 337 (PST)—11 AM to 12:05 PM; 4 to 5; 6 to 12.  
 KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 9.  
 KOB, State College of New Mexico, 348.6 (MST)

—11:55 AM to 12:30 PM; 7:30 to 8:30; 9:55 to 10:10.  
 KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 9.  
 KPO, San Francisco, Cal., 429 (PST)—7 AM to 8; 10:30 to 12 M; 1 PM to 2; 4:30 to 11.  
 KSD, St. Louis, Mo., 545.1 (CST)—7 PM to 10.  
 KTHS, Hot Springs, Ark., 374.8 (CST)—8:30 PM to 10.  
 KYW, Chicago, Ill., 536 (CSTDS)—6:30 AM to 7:30; 10:55 to 1 PM; 2:15 to 4; 6:02 to 11:30.  
 PWX, Havana, Cuba, 400 (EST)—8:30 PM to 11:30.  
 CNRA, Calgary, Alberta, Canada, 435.8 (MST)—9 PM to 11

# RADIO'S GREATEST

## 4th Annual National Radio Exposition

at Grand Central Palace, New York

September 12-19 inclusive

Over two miles of exhibits covering every phase and aspect of the radio industry


HAROLD BOLSTER, Director

J. C. JOHNSON, General Manager

Office, 522 Fifth Avenue, New York

### The Famous Bernard
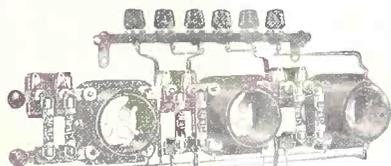
## "DIAMOND OF THE AIR"—with Resistance Coupled Amplification



The VEBY Completely Assembled Resistance Coupled Amplifier

Just as was to be expected, Mr. Herman Bernard, in deciding on the best resistors and mounts for amplifier of his famous "Diamond of the Air," chose the VEBY PRODUCTS in preference to all others. He found that the VEBY PRODUCTS measure up to the standard set for it—wonderful volume of that superior tone quality found only with the better Resistance Coupled Amplifiers.

### VEBY Products



The VEBY Resistance Coupler

are all laboratory tested. The Resistors are guaranteed moisture proof, noiseless and constant in value. They are to be depended upon when all others fail. The impregnated element perfectly sealed insures stability of resistance value under varying operating and atmospheric conditions.



The VEBY Resistor

- The VEBY 3-Stage Resistance Coupled Amplifier ..... \$10.00
- The VEBY Resistance Coupler ..... 1.25
- The VEBY Resistors 1 to 10 meg. .... .40
- The VEBY Resistors 12,000 to 75,000 Ohms .60
- The VEBY Resistors 5,000 to 10,000 Ohms .75

DISTRIBUTORS—we have territory open.

# VEBY RADIO CO.

47-51 MORRIS AVENUE

"Quality Resistors" NEWARK, N. J.



TUBES Especially Made for Resistance Coupled Amplifiers

A. F. 20 ..... \$3.00  
 A. F. 6 Power Tube 3.50

# How to Make the Coil Right for Anderson's Wavemeter

(Continued from page 8)

than in this case. Hence it is advisable to use about 61.5 turns on L2.

Now when the tuning condenser is connected across L1, the tickler, the dial setting for a given wavelength is about twice that when it is connected across L2, that is, the inductance of the tickler is one-half that of the secondary. Hence the range is about from 390 meters to 120 meters when tuning condenser is across L1. It would be desirable to reach lower

wavelengths, and this, of course, may be done by reducing the number of turns on the tickler. Two or three turns may be removed without affecting the efficiency of the set as an oscillator. The set has not yet been calibrated for the short-wave range, but for the broadcast range a point has been accurately located for nearly every broadcasting station now operating. Not all of these points are shown in Fig. 3 in the accompanying chart.

So that the calibration be definite it is necessary to use the oscillator in exactly the same way in which it was calibrated. For this reason the filament and plate batteries are always placed in the same position with respect to the set, and leads of fixed lengths are used. The same applies to the tuning condenser, in which case bus-bar leads of fixed length are always used. It is also important when the coil L3 is used for taking off the radio-frequency oscillations that no appreciable current flows in this coil which might alter the effective inductance of the tuning coil, or that the distributed capacity does not change appreciably. The set is remarkably consistent with respect to the calibration.

The grid condenser C1 has the usual value of 250 micro-microfarads (.00025 mfd.), but the grid leak R is lower than the usual value in a receiving circuit. It should not be greater than 0.5 megohm, or blocking might occur when the circuit is oscillating.

Two amperites A are used in the filament circuits to limit the heating current. Even with these in the circuit the set operates satisfactorily with only 3 volts across the terminals 7 and 9 and 22.5 volts on the plates. A couple of UV199 tubes are used.

The transformer T is a 3.5 to 1 ratio instrument. This was used because it was available, but if one is bought especially for the purpose it is better to get a lower ratio transformer. This is desirable because the higher ratio will cause the audio-frequency tube to oscillate too violently and may kill off the oscillations in the first tube. If this occurs there are several ways in which the amplitude of the audio-frequency oscillations may be reduced. The natural frequency of the oscillator may be reduced by increasing the value of condenser C2; the input to the audio tube may be reduced by connecting a resistance across the secondary terminals; or an external rheostat may be inserted between the terminals 11 and 12. In some cases the by-pass condenser C2

(Continued on next page)

**THOUSANDS OF BARGAINS**  
 FACTORY GUARANTEED MOSE, BY MAIL  
 Genuine New Radiotron or Cunningham Tubes  
 UV-199—200—201A—WD-11—12..... \$1.98  
 C299—300—301A—C11—12.....  
 Fresh Burgess or Eveready "B" Batteries  
 22½ Volt large size \$1.20—45 Volt large size \$2.80  
 Write for Free new Complete Catalog on  
 Sets and Parts  
**STONE ELECTRIC CO.,** 714 Pine St., St. Louis, Mo.  
 All Mfgs. F. D. B. St. Louis, Mo. Dept. W

For Maximum Amplification Without Distortion and Tube Noises use the well known  
**Como Duplex Transformer**  
 Push-Pull  
 Send for Literature  
**COMO APPARATUS COMPANY**  
 448 Tremont Street Boston, Mass.

**BATTERY LEAD TAGS**  
 PAT. PEND.  
  
 SET OF TEN TWO OF EACH SAFE & QUICK 15 PRICE CENTS  
 ASK YOUR DEALER  
**MFD. BY PAUL CLANZO**  
 203 LAFAYETTE ST. NEW YORK

**Men Wanted**  
 to build radio sets in spare time.  
**LEON LAMBERT**  
 562-H Kaufman Building  
 Wichita, Kansas

**Radio Parts Sets Kits at BIG SAVINGS**  
 Get our big FREE Catalog. Illustrates and describes most advanced hook-ups. Newest standard kits, and latest parts at prices far below others. Save money! Write for this book at once. No charge. No obligation.  
**BARAWIK CO.**  
 32-60 S. Clinton St., Chicago

Look for the name  
  
**WD-11 Radiotron**  
 REG. U. S. PAT. OFF.

**NEUTRODYNE KIT \$19.75**  
 Complete kit of licensed Neutrodyne parts, including panel, tube sockets, rheostats, jack, fixed condensers and grid leak. Neutroformers complete with variable condensers and neutrons. Every part included even to screws and wire. Easy read plans.  
 Send No Money Pay the Postman Order by Postcard  
**RADIO SURPLUS STORES**  
 HELENA MONTANA

**LOUD SPEAKER RECEPTION**  
 from either coast on three tubes.  
 Blueprint and instructions.....\$1.00  
 Necessary low loss coil.....\$2.50  
 Beautiful finished instrument.....\$35.00  
**S. A. TWITCHELL CO.**  
 1930 Western Avenue Minneapolis, Minn.



## How to Get LOUD-SPEAKER VOLUME

**EASY.** Inexpensive. Results guaranteed. Hook up a Daven Super-Amplifier. Adds three stages of audio amplification—Daven Resistance Coupled—no labor of assembly—positively no distortion—perfect reception. Daven precision-built unit with Bakelite base. Wonderful assembly. Compact, beautiful—\$15.00. Knock-down Kit (build your own)—\$9.00. For volume, use two Daven High Mu Tubes—\$4.00 each, and one Mu-6 (for last or output stage)—\$5.00.

Mail the coupon for complete information.  
*The Sine of Merit*  
**DAVEN RADIO CORPORATION**  
 Resistance Specialists  
 Reg. U. S. Pat. Off.  
 Newark New Jersey  
 DAVEN RADIO CORPORATION L-19-25  
 158 Summit Street, Newark, N. J.  
 Please send me the following:  
 ..... Resistor Manual. 30c is enclosed.  
 ..... Complete Catalogue (free).  
 Name.....  
 Address.....  
 Get the Handbook of Resistance Coupled Amplification. At Dealer's 25c. By mail 30c.  
 FOR DEALERS: Send your letter-head and we will have our nearest distributor communicate with you.  
**THE BIG LITTLE THINGS OF RADIO**

**BARBLEY'S**  
 Authorized and Official  
**BRUNO SERVICE**  
 Also Specialists on  
 All Radio World Circuits  
**Powertone, Diamond of the Air**  
**Superdyne, Pressley, Rasla-Reflex, etc.**  
 Parts and Sets Always in Stock  
 Sets Built to Order—Factory Workmanship  
 Write for Quotations  
 Bruno "77"..... \$5.50  
 Bruno "55"..... 3.00  
 Powertone Set in Beautiful Cabinet..... 39.50  
 Complete Diamond of the Air Kit..... 41.50  
 (Parts as Specified by Bernard)  
 Special Attention Given to Mail Orders  
 We Pay Postage if Remittance Accompanies Order  
**BARBLEY'S RADIO SERVICE**  
 135 Liberty St. (Dept. RW) New York City  
 "Barbley Is Dependable"

# Explanation of the Parts Used in the Oscillating Meter


(Continued from preceding page)

may not be necessary for radio-frequency oscillation in the first tube, but it is usually desirable in order to lower the frequency of the audio oscillations, as these are likely to be several octaves too high for pleasant listening.

All the apparatus that make up the circuit, exclusive of the tuning condenser, batteries, and phones, are mounted on a hard rubber panel 4.5x7", and enclosed in a box having inside dimensions 3 3/4" wide, 6 1/2" long and 3 5/16" deep. The binding posts on the panel are arranged as shown in Fig. 2. The mounting screws used for holding the parts are also used for binding posts where ever this is practicable, and this shortens the leads and makes the compact assembly possible. The tuning coils are supported by the binding posts 1 to 4, being held away from the panel by four pieces of stiff bus-bar wire. The two Amperites are supported by the two binding posts 5 and 6, which are also used for the terminals of the coupling coil L3. The radio-frequency tube is supported by 9 and 9a, and the audio-frequency tube by 12 and 12a. The tubes are mounted upside down. The transformer is supported by 7, 8, 8a, and 11. Only those marked (a) are not used for binding posts. The somewhat irregular arrangement of the battery binding posts, or course, is due to the double use of the mounting screws. The large binding posts are a small-sized Eby, and the small are merely 6-32 machine screws with knurled thumb nuts.

The jack required in this circuit is a three-spring jack which opens one contact as the plug is inserted. In the set constructed a Pacent 63 was used, which is a double circuit jack, but one of the springs was left dead.

## AT LAST— The Perfect Loud Speaker

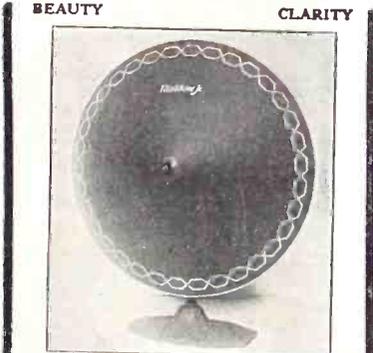

**VOLUME QUALITY**  
**VITALITONE**  
THE TRULY LIFE-LIKE TONE  
**RADIO REPRODUCER**

THE VITALITONE is not sold by argument, but by comparison, and after you've heard it, you will agree with us that there is no comparison.

**Suspended Diaphragm**

**No Horn**

**Large Model, Price . . . . \$30.00**

**Junior Model, Price . . . . 15.00**

ON DEMONSTRATION AT  
**ROSSITER & CO.**

SOLE SALES AGENTS

136 LIBERTY STREET NEW YORK

### CORDELL IN NEW POST

Peter C. Cordell, formerly manager of general assembly and production for the Erla Manufacturing Co., Chicago, has become associated with Aero Products, Inc., 1772 Wilson Ave., Chicago.

22 1/2  
VOLT  
\$2.95



It's OUT—Complete overlasting ready to run non-acid, non-sulphating 22 1/2-volt rechargeable "B" storage battery, \$2.95. Includes chemical. Does not lose its charge standing idle. Special 2-22 1/2 volts (45 volts) \$6.25; 90 volts, \$10.00. 112 1/2 volts \$12.50; 135 volts \$14.75; 157 1/2 volts \$16.80. Nearly 3 years sold on a non-red tape. 30-day trial offer, with complete refund if not thoroughly satisfied. Further guaranteed 2 years. Knockdown kits at still greater savings. Complete ready to run "B" battery charger \$2.75. Sample cell 35c. Order direct—send no money—simply pay expressman its cost on delivery, or write for my free literature, testimonials and guarantee. Same day shipments. My large 36-page radio goods catalogue 10c. B. L. Smith, 31 Washington Ave., Danbury, Conn.

### A RECHARGEABLE "B" WITH A STRONG GUARANTEE

The SEE-JAY BATTERY has met all tests and is endorsed and recommended by the Washington Information Service Bureau and more than 20,000 satisfied users. Genuine Alkaline connected elements; strictest Government test passed and recommended. No drilling or wiring. Connectors crimped under 1,000-pound pressure. Save time, temper and money. 100-volt unit, \$5.00; 140-volt, \$8.00. Why pay more? Complete assembled batteries, solution separate, shipped dry, 100-volt, \$12.00; 140, \$16.00. See-Jay unit sold on money-back guarantee. Write for literature and send 20c for improved sample cell. SEE-JAY Battery Co., Dept. W, 915 Brook Ave., New York. Mail order service.

WHOLESALE AND RETAIL

**PANELS and BASES**

**RADION BAKELITE AND HARD RUBBER**

Cut, Drilled and Engraved for your Specifications

**CORTLANDT PANEL ENGRAVING CO.**

81 CORTLANDT ST., N.Y.  
TEL-RECTOR 3268

*A guide to what is right and standard in Radio*

*Ward's sets are easy to install*

**MONTGOMERY WARD & CO.**

*Send for your free copy*

## Ward's New Radio Catalogue

The 52 fully illustrated pages of this new catalogue are simply invaluable to every one interested in Radio. And one copy is to be yours Free—merely for the asking!

It shows guaranteed Radio sets, one tube sets that give remarkable results, and sets of every variety up to Ward's new five-tube one-dial control. Think of tuning in one station after another by turning a single dial!

It shows guaranteed, tested parts, batteries, cabinets, contains a list of stations, a radio log for recording stations. It is a complete radio manual—sent entirely free!

### Ward's is Headquarters for Radio

And best of all, the catalogue offers you everything new in Radio at a big saving in price.

At Ward's, everything for Radio is sold without the usual "Radio Profits." Thousands of pleased customers write us of their constant delight with Ward's Radio products.

### Our 53 year old Policy

For 53 years we have sold our quality merchandise under a Golden Rule Policy. You can rely absolutely upon the quality of everything shown in this Radio Catalogue.

Be sure and ask for Radio Catalogue No. 42-R

# ESTABLISHED 1872 Montgomery Ward & Co.

The Oldest Mail Order House is Today the Most Progressive

Baltimore Chicago Kansas City St. Paul Portland, Ore. Oakland, Calif. Ft. Worth

# January 24 is Date Set for International Week

The Committee on Arrangements for International Radio Week held a joint luncheon meeting at the Commodore Hotel, New York City.

Leo Potter, of the Thermodyne Radio Corporation, who was responsible for the calling of this meeting is the Chairman of the Committee.

The following also were present: H. S. Fraine, "Radio Broadcast," secretary; Paul West, National Carbon Co.; C. C.

Hartzell, Hartzell Sales Co.; Lewis Winner, RADIO WORLD. Others on the committee are: C. P. Belden, Belden Mfg. Co.; L. M. Staunton, C. Brandes, Inc.; Heckert L. Parker, Pacific Coast Radio Trade Association; Chas. Porter, Radio Manufacturers' Association.

The important question discussed was the date for the International Radio Week. To create a greater export radio business by a change in the wavelengths of the European and other foreign receivers to those used by the United States stations was advocated.

The radio tests will be of no value unless our signals are receivable by European listeners, who can not "get" them with their present type of sets, as the wavelengths used by the broadcasting stations over there are very high as com-

pared with those used by the stations here.


An effort will be made to get Secretary Hoover to advocate a pact with European stations to change their wavelengths. The American stations will be asked to use high power during International Week. Receivers which employ any direct method of obtaining regeneration should not be used during these tests. Last year radiation was one of the main reasons for the failure of the International tests.

The date for International Radio Week was set for January 24. This week was selected because of the following reasons: (1) After the Christmas holidays there is a lull in the radio trade. A radio week will keep the public interest awake. (2) It takes three or four weeks fully to learn how to operate the receivers purchased during the holidays. Distant stations can only be tuned in by an operator who has had experience with his receiver. (3) Radio reception is very good during this time of the year. (4) Business conditions are not fully settled until this part of the year. That is, in order to obtain, the full interest in the week all other obstacles must be put out of the way.



CONDENSERS  
VERNIERS  
RHEOSTATS

AMSCO PRODUCTS, Inc. New York City

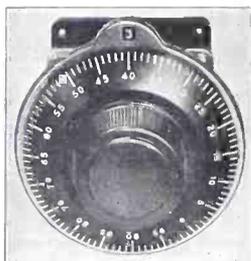

## Something Brilliantly New— The Helicon Variable Condenser! Far Better Than Straight-line Frequency!

This revolutionary condenser has spiral plates. The rotor gradually worms its way through the stator, giving the effect of one rotor plate entering the stator at a time. The 100-division dial reads from 0 to 540 in the .0005 type by a special indicating device used also in the other types. From 200 to 400 meters. The stations are spread over about 270 divisions! The oscillation point can be easily approached and stations heard that otherwise would be missed.

.0005, \$7— .00035, \$6.75— .00025, \$6.50

Prices include Dials

KAPACITON CO.

26 ELLIOTT PLACE JERSEY CITY, N. J.

Direct Factory Representatives: Utility Manufacturing Co., 54 Marlborough St., Springfield, Mass.

## The Weekly Rebus



**A Special Combination!—**  
**The Powertone**  
 Licensed Under Hogan Patent  
 with  
**Bretwood Variable Grid Leak**  
*In the Set*  
 The Great 5-Tube 1-Dial Receiver Equipped with the Sensational Leak.  
**RADIO DIVISION, COLUMBIA PRINT**  
 1493 BROADWAY New York City

\$41.00

**EVERY SET BUILDER NEEDS THIS**

**“Morsing Bus-Bar Union”**

Makes for quick assembling. Repairs can be made by using Morsing Bus-Bar Union without taking set apart.

Assemble round or square Bus-Bar and solder three wires at a time. Order No. 1 for No. 14, No. 2 for 12 wire. Send 25 cents for enough for building one set, or ten dozen for \$1.00.

Newark Watch Case Material Co.  
 15 Ward Street Newark, N. J.  
**DISTRIBUTORS WANTED**

# RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS.

10 CENTS A WORD. 10 WORDS MINIMUM

**AGENTS WANTED**  
**SELLS FOR \$9.75**—Prints ad on wrapping paper, envelopes, etc. \$4.00 commission. Send 10c for sample work. Automatic Ad-Stamp, Joclin, Mo.

**A LIFE TIME TROUBLE PROOF "B" BATTERY**/ Made from genuine largest size Edison elements. Complete parts for 48-volt unit; \$7.00 postpaid. Send 15c for sample cell, "dope" sheet, and price list. Chas. Snively, Woodburn, Ore.

**DISSATISFIED WITH YOUR SET?** A stage of tuned radio-frequency will improve it. No change of wiring. Write on panel. Good parts. Postpaid, complete with tube, \$6.50. Specify type tube. Albert Beybom, 452 E. 136 St., New York City.

**ANDERSON'S 6-TUBE SUPER-HETERODYNE**, by J. E. Anderson; the 3-Tube Marconi Broadcast receiver, by Percy Warren; How to Make a Good Battery Connector; other features in RADIO WORLD, July 18, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

**AGENTS WANTED TO SELL** standard radio apparatus. Write us at once if interested. Radio Development and Engineering Co., 180 Broadway, New York.

**NEW WONDERFUL SELLER.** Cost 10c, profit \$1.40, monogramming autos. Experience unnecessary. Free samples. Worcester Monograms, B132, Worcester, Mass.

**MAKE \$100 WEEKLY** in spare time. Sell what the public wants—long-distance radio receiving sets. Two sales weekly pays \$100 profit. No big investment, no canvassing. Sharpe of Colorado made \$955 in one month. Representatives wanted at once. This plan is sweeping the country—write today before your county is gone. Ozarka, Inc., 126 West Austin Ave., Chicago, Ill.

**DINING AND SLEEPING CAR CONDUCTORS** (White). Exp. unnecessary. We train you. Send for book of Rules and application. Supt. Railway Exchange, Sta. C, Los Angeles.

**RADIO PUBLICATIONS**—Send stamp for Bulletin E651. Smith, Box 1032, Rockford, Illinois.

**RADIO HOSPITAL**—Specialists in Neurodynes and Super-Heterodynes. Dept. 4, Abilene, Kansas.

**A 1-CONTROL PORTABLE** by Capt. P. V. O'Rourke; A Baby Super-Heterodyne, by J. E. Anderson; A More Powerful Diamond, Still only 4 Tubes, by Herman Bernard. Other features in RADIO WORLD, dated July 11, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

**\$12 AN HOUR** actually earned selling the new Double-Wear Work Shoe. \$5.00 value selling at only \$2.95. A world-beater. Liberal commission. Write quick. The Double-Wear Shoe Company, Dept. H, East Lake St., Minneapolis, Minn.

**PATENTS**—Write for free Guide Books and "Records of Invention Blank" before disclosing inventions. Send model or sketch of your invention for our inspection and instructions free. Terms reasonable. Radio, Chemical, Mechanical, Electrical and Trademark experts. Victor J. Evans & Co., 924 Niath, Washington, D. C.

**RADIUMART REMOVES** Warts, Moles, Superfluous Hair, Coal Powder and Tattoo Marks. Particulars sent free. Radiumart Co., 1416 Cadwallader St., Philadelphia, Pa.

**A DYNAMIC SET, Enormous Power on 3 Tubes**, by P. E. Edelman. An Anti-Radiation Toroid Set, by Capt. P. V. O'Rourke. Four Crystal Hook-ups, by Lewis Winner. Other features in RADIO WORLD dated July 25, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

**RECENT BACK NUMBERS** of Radio World, 15c each. RADIO WORLD, 1493 Broadway, New York City.

## "HOW TO MAKE"

The following illustrated constructional articles have appeared in recent issues of RADIO WORLD:

- Sept. 6, 1924—A simplified Neutrodyne with Grid-Biased Detector, by J. E. Anderson.
- Sept. 13—A Low-Loss Wave Trap, by Brewster Lee.
- Sept. 27—A 1-Tube No Crystal Reflex, by Nov. 15—A Sturdy Low-Loss Coil, by Lieut. P. V. O'Rourke.
- Oct. 1—A Ultra 2-Tube Receiver, by Byrt C. Caldwell.
- Dec. 13—The World's Simplest Tube Set, by Lieut. P. V. O'Rourke.
- Dec. 20—A 1-Tube DX Wonder, Rich in Tone, by Herman Bernard. An Interchangeable Detector, by Chas. M. White.
- Dec. 27—A 2-Tube Gelula's Super Flex, by P. V. O'Rourke.
- Jan. 3, 1925—A 3-Tube Portable That Needs No Outdoor Aerial, by Abner J. Gelula.
- Jan. 10—A Low-Loss DX Inductance, by Herbert E. Hayden.
- Jan. 17—A \$25 1-Tube DX Wonder, by Abner J. Gelula.
- Jan. 24—A Selective \$15 Crystal Set, by Brewster Lee. A Varionometer-Tuned Reflex, by Abner J. Gelula. An \$18 1-Tube DX Circuit for the Beginner, by Feodor Rafatkin.
- Jan. 31—A Regenerative Neutrodyne for More DX, by Abner J. Gelula. A Transcontinental 2-Tube Set, by H. E. Wright. An Experimental Reflex, by Abner J. Gelula.
- Feb. 14—A Super-Sensitive Receiver, by Chas. H. M. White. A Honeycomb RFT for DX, by Herbert E. Hayden.
- Feb. 21—A 1-Tube Reflex for the Novice, by Feodor Rafatkin. A Set for Professional Folk, by Lieut. P. V. O'Rourke. A Honeycomb Crystal Receiver, by Raymond B. Wallis.
- Feb. 28—A Set That Gets the Most Possible, With 6 Tubes, by Thomas W. Benson. Three Resistance Stages of AF on the 3-Circuit Tuner, by Albert Edwin Sonn.
- March 7—Storage Batteries, by Herbert E. Hayden. Benson's Super-Heterodyne. Ideal Coils for Best Circuits, by J. E. Anderson.
- March 14—The Reflexed 3-Circuit Tuner That You Can Log, by Herman Bernard. The Right Way to Put Coils and Condensers in a Set, by Byrt C. Caldwell.
- March 21—A Variable Leak, by Herbert E. Hayden. A 4-Tube, 3-Control Set That Gets the Most DX, by Lieut. P. V. O'Rourke.
- March 28—The Improved DX Dandy Set, by Herbert E. Hayden. A 3-Tube Reflex for the Novice, by Feodor Rafatkin.
- April 18—The Diamond of the Air (Part 3), by Herman Bernard. The 7-Tube Pressley Super-Heterodyne (Part 1), by Thomas W. Benson. An Easy 8-Tube Set, by Lewis Winner.
- April 25—A 3-Tube, 2-Control DX Reflex, by Brewster Lee. Trouble Shooting Article on Diamond of the Air, by Herman Bernard. Wiring the Pressley Set (Part 2), by Thomas W. Benson.
- May 2—The Twinplex, by J. E. Anderson.
- May 9—A Set to Cut Static, by Feodor Rafatkin. Toroid Circuit with Resistance AF, by E. I. Sidney. A Push-Pull AF Amplifier, by Lt. Peter V. O'Rourke.
- May 16—A 3-Tube Reflexed Neutrodyne, by Percy Warren. The Baby Portable, by Herbert E. Hayden. One Tube More for Quality, by Brewster Lee.
- June 6—The Smokestack Portable, by Neal Fitzgibbon. A and B Battery Eliminators, Using DC (Part 1), by P. E. Edelman. A Wave-meter, by Lewis Winner. Full List Broadcasting Stations.
- June 13—Simple Short-Wave Circuits, by Herbert E. Hayden. A Simple Push-Pull Rheostat, by A. C. G. Force. A and B Battery Eliminators, Using AC (Part 2), by P. E. Edelman. A Portable Super-Heterodyne, by Walnwright Astor.
- June 20—The Diamond as a Reflex, by Herman Bernard. A 2-Tube Portable Reflex, by Herbert E. Hayden. A Reflex for 99 Type Tubes, by L. R. Barbley.
- June 27—The Pocketbook Portable, by Burton Lindehm. The Power Tube Set, by John Merson. Lesson on Learning the Code.
- July 4—The Handsome Portable, by Herbert E. Hayden. The Freedom Reflex, by Capt. P. V. O'Rourke. 5-Tube Super-Heterodyne, by Almer J. Gelula.
- July 11—The Baby "Super," by J. E. Anderson. A 1-Dial Portable Receiver, by Capt. P. V. O'Rourke.
- July 18—Anderson's 6-Tube Super-Heterodyne. The 3-Tube Marconi Receiver, by Percy Warren. A Good Battery Connector, by Herbert E. Hayden.
- July 25—A Dynamic Radio Amplifier, by P. E. Edelman. An Anti-Radiation Toroid Set, by Capt. P. V. O'Rourke. Crystal Sets for Work Today, by Lewis Winner. Construction of the Diamond Described for the Novice, by Herman Bernard.
- Aug. 1—Enormous Volume on DX Stations, by Sidney E. Finkelstein. The Metropolitan Local Set, by J. E. Anderson. 4-Tube DX Divided Circuit, by Herbert E. Hayden. Series and Parallel Effects, by Herman Bernard.
- Aug. 8—The Evolution Reflex, by Capt. P. V. O'Rourke. The Midget—A 3-Tube Set in Sewing Machine Cabinet, by Herbert E. Hayden. How to Build Your First Set, by Herman Bernard. 2-Year-Old Wins DX Strike, by Lewis Winner.
- Aug. 15—A 2-Tube Speaker Reflex, by Brewster Lee. Capt. P. V. O'Rourke's Favorite Audio Amplifier. A Set That Taxes Ingenuity, by Lewis Winner. The Loop Jack in the Diamond, by Herman Bernard.
- Aug. 22—The 5-Tube Diamond, by Sidney E. Finkelstein. A Home-Made Todoidal Coil, by George B. Hestetter. The Electrostatic Regenerator, by Percy Warren. Crystal Sets That You Can Log, by Herman Bernard.
- Aug. 29—The 1-Dial Power-tone, by Herman Bernard. A Set of Baby Can Build, by Herbert E. Hayden. A Fine Meter Switchboard, by Lewis Winner. A Powerful 1-Tube Set, by Percy Warren.

Any copy, 15c. Any 7 copies, \$1.00. All these 88 copies for \$5.25, or start subscription with any issue. Radio World, 1493 Broadway, N. Y. City.

## Winner's Set

(Continued from page 17)

placed to the extreme right of the baseboard and near the two audio-frequency amplifying tubes.

### Rack Mounting

Now for the panel mounting the tap switch rack. Procure a rack 16" in length. One inch from both ends make angle turns (45 degrees) of the tubing itself. Now procure some stock brass tubing 16" in length. The diameter of all the brass tubing used is 3/16". Make 45-degree angle turns 1" from both ends on the tubing or the same as you did with the rack. With a steel drill bore a hole in the rack angle and in the shaft (tubing) angle. In order to perform this act with ease, put plenty of oil on the drill and take your time. It is not very simple to drill through metal. Before drilling the tubing it is a good idea to flatten the whole of the tubing from one end to the other with a hammer, so that you will have an even surface to drill through. It is easier to drill than the usual flat stretch of brass. Perform the same operation of drilling on the other end of the rack.

At any hardware store buy a pair of movable slot holders, 5" in length, with a slot 4" length and 1/2" high. These usually have angles on the ends with holes for mounting. Mount one of these at each end of the rack.

The tap switch holders should be 3" in circumference. Mount these on the panel, leaving a 1/8" separation between them. Get another piece of brass tubing, 1" in length. Insert in dial shaft hole. Pass through the panel. Mount the rack, by inserting set screws in the holes on the ends of panel, already provided for. Solder a pinion on the end of the brass dial tubing. This should fit snugly on the rack. On the shafts of all the individual tap holders solder on a pinion. These pinions should also fit snugly on the rack. Now move the rack back and forth using the dial. The arm of the tap switch should revolve smoothly on the taps, and all at the same time, viz., all arms hitting same tap at same time.

When performing all these mechanical acts, refer to the diagrams Fig. 2 and 5, at all times, otherwise you will be stuck,

## THE RAMBLER SIX A REAL PORTABLE

Volume, Clarity, Portability, Durability and Beauty Unequaled

Lightest in weight, 21 pounds.  
Smallest in size, 14x9 1/2 x 9 3/4 inches.

LIST PRICE..... \$80.00

If your dealer cannot make immediate delivery we will ship direct from factory same day your money order or check is received.

American Interstate Radio Service  
183 Greenwich Street, New York City  
Distributors, Jobbers, Dealers, write for special trade terms.

## MEGGIT RESISTOR



To build the most perfect Resistance Coupled Amplifier, it is essential to use Meggit Resistors and Grid Leaks—they are noiseless, moisture proof and accurate in resistance.

Send 10c for booklet on Resistance Coupled Amplification with circuit diagrams.

COLE RADIO MFG. CO.  
Bloomfield, N. J.

## HERCULES AERIAL MAST



20 Ft. Mast \$10  
40 Ft. Mast \$25  
60 Ft. Mast \$45

All steel construction, complete with guy wires and masthead pulley. We pay the freight.  
B. W. HULL & CO., Dept. E3  
2048 E. 79th St., Cleveland, O.

FREE  
Write for literature and Blueprint


### Clearness—Volume \$3.50

## FLINT AUDIO TRANSFORMERS

All Circuits—All Stages at Your Dealer or Direct.  
FLINT RADIO CO.  
1606 Wilson Ave., Chicago


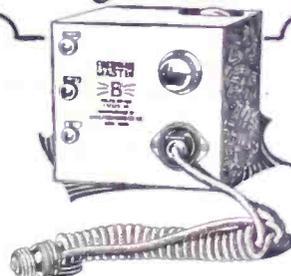
# YOU don't need "B" Batteries if you use the FRESHMAN MASTER "B" Battery Eliminator



Connects from any electric light socket right to your radio set;—that's all there is to it.

With the Freshman Master "B" Eliminator your set will always be supplied with constant and uniform power. Noiseless in operation; your reception will not be marred by the snap and crackle due to chemical action in "B" batteries.

A. C. Model \$20.00 for alternating current

Freshman Rectifying Tube is required for operation of the A. C. Model. Price..... \$2.50

D. C. Model \$17.50 for direct current

Costs less than one-tenth of a cent per hour to operate.

Sold by AUTHORIZED FRESHMAN DEALERS only

Chas. Freshman Co. Inc.  
Radio Receivers and Parts  
FRESHMAN BUILDING  
240-248 WEST 40TH ST.—NEW YORK, N.Y.  
CHICAGO OFFICE — 327 S. LA SALLE ST.

### HOOK-UPS

A lot of them, some of which are sure to suit your purpose, appeared in RADIO WORLD dated August 15. 15c a copy, or start your subscription with that number.  
RADIO WORLD, 1493 Broadway, New York City

(Continued from preceding page)  
as it is no cinch to make these devices operate successfully.

The concluding material that is to be mounted consists of the rheostats, the terminal strip, and the jack.

Bring the beginning of L1 to the antenna and the end to the ground. Bring the ground post to one terminal of C5 and to the arm of R1.

Bring the other end of C5 to the resistance wire (left hand side of P). The top of L2 (rotor winding) goes to the grid. The tap post T, goes to the end terminal of L2 (stator winding) and to the left off terminal of C5. This same connection also goes to the arm of the

potentiometer. Still the same connection goes to the tap arms T2 and T3. T2 is connected to end of L4 (stator winding). T3 is connected to end of L6 (stator winding). The stator plates of C1 goes to the top rotor winding of L2 and to the grid post of tube No. 1. The rotor plates go to the arm T1. The top of L3 goes to the plate post on tube No. 1, the end going to the end of L5 and to the B+ 67½ volts post. The stator of C2 goes to the beginning of the rotor winding and to the grid post on tube No. 2. The rotary plates go to tap arm T2. The top of L5 goes to the plate post on tube No. 2. The rotor (beginning) winding of L6 goes to the stator plates of C3, to one terminal of C4 and to one terminal of R4. The other terminals of R4 and C4 go to the grid post on tube No. 3. The rotor of C3 goes to T3.

Connect the taps from the stator winding of L2 to the tap switch. There are nine taps. The same is done with the taps of L4 and L6.

The resistance wire of R1 goes to F—post on tube No. 1. The arm of R1 goes to the resistance of P (same side as C5 goes). The other resistance side of P goes to the F+ on socket of tube No. 1. The other rheostats R2 and R3 are connected in like fashion to that of R1. The rheostat side of the resistance wire of P goes to the A minus post, while the other resistance wire side of P goes to A plus. The audio-frequency stages are connected up in standard fashion and I don't think there is any necessity of special detail being made. There is no C battery used in this set. This is due to negative grid bias on all the tubes, which comes from the action of the potentiometer (P).

*It isn't a genuine  
WD-11 unless it's  
a Radiotron*



**WD-11  
Radiotron**

**Oh boy!**  
**KESTER**  
*Rosin Core*  
**Radio SOLDER**  
Sure! is Safe and Simple  
APPROVED BY  
RADIO ENGINEERS  
A GENUINE SOLDER  
CHICAGO SOLDER COMPANY  
4242 Wightwood Ave., Chicago, U.S.A.  
Originators and World's Largest Manufacturers of Self Fluxing Solder  
YOUR DEALER CAN SUPPLY YOU

**RADIO DE LUXE  
THE CLEARFIELD 6 TUBE**  
Encased in plate glass cabinet. Tuned Radio Frequency with Resistance Coupled Amplification. True Tone Quality. List Price... \$115  
Write for Illustrated Booklet.  
**Sherman Radio Mfg. Corporation**  
112-114 Trinity Place New York, N. Y.  
Dealers write for our proposition.

**PANELS**  
RADIUM and HARD RUBBER  
RETAIL ANY SIZE WHOLESALE  
PRICE LIST MAILED ON REQUEST  
**HARD RUBBER  
SHEETS—RODS—TUBING**  
Special Hard Rubber Parts Made to Order.  
Send Sample or Sketch for Quotation.  
**NEW YORK HARD RUBBER TURNING CO.**  
212 CENTRE ST. NEW YORK

**FREE two unusual  
RADIO CATALOGS**

**FOR "FANS"** OUR new 64-page Radio Catalog including all the best and latest Kits, Parts and Accessories for broadcast receiving sets. Lowest prices in the country.

**FOR "HAMS"** NEW 32-page booklet of army and navy transmitting apparatus and miscellaneous specialties for "hams" such as W. E. Choke Coils, Generators, Resistance Boxes, etc.

More than 1,000,000 fans and hams make our store their headquarters—got these books and find out why.

Write for either or both

509 South State Street  
**CHICAGO SALVAGE STORES**  
Dept. R. W. 6 Chicago Ill.

**RADIO WORLD'S 2-For-Price-of-1 Subscription Offer**  
For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements  
—To offer a year's subscription FREE for any one of the following publications with one year's subscription for RADIO WORLD  
—RADIO NEWS or —RADIO DEALER or  
—RADIO JOURNAL or —RADIO (San Francisco) or  
—POPULAR RADIO or —THE EXPERIMENTER or  
—RADIO BROADCAST or —RADIO AGE  
—SCIENCE AND INVENTION or

This is the way to get two publications  
—for the price of one!  
—Send \$6.00 today for RADIO WORLD  
—for one year (regular price  
—for 52 numbers)  
—and select any one of the other  
—nine publications for twelve months.

—Add \$1.00 a year extra for  
—Canadian or Foreign Postage.  
—Present RADIO WORLD subscribers  
—can take advantage of this offer by  
—extending subscriptions one year  
—if they send renewals NOW.

**RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK**  
RADIO WORLD, 1493 Broadway, New York City.  
Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers), beginning \_\_\_\_\_ and also \_\_\_\_\_ without additional cost, Radio News, or Popular Radio, or Radio Broadcast, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or The Experimenter, or Radio Journal, or Radio Age (or \$10.00 for two yearly subscriptions).

Indicate if renewal.  
Offer Good Until  
October 1, 1925

Name \_\_\_\_\_  
Street Address \_\_\_\_\_  
City and State \_\_\_\_\_

The World Expected a Supreme Radio Set  
from **KELLOGG**

*and here it is!*



## A Separate Circuit for Each 45 Meter Wavelength Band!



**WAVE-MASTER**  
Standard Model  
\$125.00



**WAVE-MASTER**  
Brown Walnut Console  
with inbuilt horn  
\$275.00

*Kellogg* — for 28 years makers of precision telephone instruments and equipment — producers of quality parts since radio began — Kellogg has perfected a radio receiver worthy to bear the Kellogg name.

In the illustration we visualize this wonderful engineering achievement.

In the new **WAVE-MASTER** there are nine separate circuits — one for each 45 meter wavelength band. Each circuit gives that maximum efficiency heretofore found only in one short section of the dials of ordinary radio frequency sets. Each circuit brings within the range of the tuning dial a different group of stations.

How wonderfully simple tuning becomes! Merely set the pointer to the wave zone in which you are interested and bring in the desired station with the single Selector dial.

This remarkable tuning dial actu-

ally has a tuning range of 540 degrees — equal to 1½ times around a complete circle — over three times the station finding range of any other set.

All other radio frequency sets have variable capacity which must be tuned, usually with three different dials, to balance with their inductance coils.

The **WAVE-MASTER'S** inductance is not fixed but variable and is easily and quickly tuned, with the one Station Selector dial, to balance the fixed capacities.

Write for full description and complete technical explanation of the Wave Master circuit. Please mention your radio dealer's name.

Kellogg Switchboard & Supply Company  
1034 W. Adams St., Dept. I Chicago, Ill.

**KELLOGG**  
**WAVE MASTER**  
SWITCHBOARD & SUPPLY CO.

**Radio Dealers and Jobbers**

The **WAVE-MASTER** franchise, backed by Kellogg resources and our powerful advertising campaign, is most valuable. Open territory is being closed rapidly. Wire us, or get into Chicago, quick, and see us.

# Improve Your Set By Installing The "BRETWOOD"

*Pulls in  
inaudible  
stations*



*Eliminates  
tube  
noises*

Range 300,000 to 10,000,000 ohms

## Variable Grid Leak

Bretwood, Ltd., London, Eng., Sole Patentees and Owners.

Used in eighty per cent of all  
receiving sets in Great Britain

### It Functions Where Others Fail

The Bretwood Variable Grid Leak used in a detector tube circuit, strengthens weak signals, makes DX easier, eliminates tube noises and internal howling, due to incorrect leakage from the grid of the tube.

By simply turning the knob the carrier wave may be tuned from the silent point to maximum audibility.

The Bretwood is absolutely noiseless in operation and will hold any given setting indefinitely. It is a single-hole panel mount leak.

The Bretwood Variable Grid Leak, tested in the National Physical Laboratory (the official laboratory of Great Britain) and by RADIO WORLD'S Laboratory, proved to be a scientifically accurate instrument. The total range, 9,700,000 ohms, produced by 25 turns of the knob, make a minute adjustment very simple.

The Bretwood Variable Grid Leak is constructed on a different principle and produces better results than any other grid leak. In its specially-constructed barrel is a patented plastic, non-drying resistance material, in which there is a small movable plunger which again moves freely in an absorbent cartridge which gives the setting of the instrument great stability, making it far superior to the graphite, carbon or fibre, compressed or decompressed, resistance elements. It can be used in the most critical circuits with the greatest success.

### Sent You on a Money Back Absolute Satisfaction Guarantee

The Bretwood Variable Grid Leak will be immediately shipped on receipt of order to any address in the United States, prepaid for \$1.50. After 10 days' trial if it is not 100% better than any grid leak you have ever had and does not in every way substantiate all claims made for it, your money will be refunded without question.

## The North American Bretwood Company

*Sole Distributors for  
United States and Canada*

1505 BROADWAY, NEW YORK CITY

*Dealers and Jobbers Write for  
Special Trade Terms*

THE NORTH AMERICAN BRETWOOD CO.  
1505 Broadway, New York City  
Room 326

Gentlemen:

Enclosed find \$1.50 for which you will please send me one Bretwood Variable Grid Leak prepaid. Satisfaction guaranteed or my money back after trial within ten days of receipt by me.


NAME.....

STREET.....

CITY.....STATE.....

# DAVID Grimes

SUPER-SELECTIVE  
RADIO

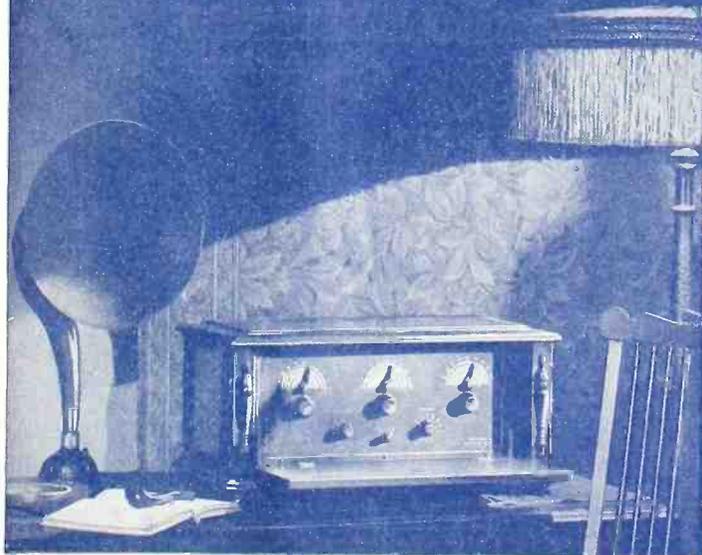

David Grimes  
Super-Tone  
**LOUD SPEAKER**  
with a mica diaphragm  
that eliminates  
distortion . . . **\$25**

**ITALIAN RENAISSANCE MODEL**  
Utilizing 4 tubes with the efficiency of 6  
tubes. Built in a Renaissance Cabinet of  
two-tone Mahogany and Wal-  
nut concealing all batteries. **\$125**  
(Without Accessories)

Ask a Grimes Dealer for Demonstration

## More Stations On the Air

**Y**OU'LL want to hear them all—  
but one at a time. The Grimes  
Circuit in the Grimes Inverse Du-  
plex receiver will give you the sharp  
tuning desired. Greater volume, dis-  
tance range and a tonal quality  
you've never heard before are also  
yours in this remarkable instrument.

Dual operation of the tubes, pro-  
viding two stages of radio frequency,  
vacuum tube detector and three stages  
of audio frequency amplification,  
gives you the energy of a six tube  
set with the economy of four tubes. A  
super power switch gives tremendous  
reserve power for distant stations.

A new form of inductance—the twin  
cylinder coils and straight line con-  
densers allows you to tune in the de-  
sired programs and shut out the rest.



**BABY GRAND Duplex Model**,  
using 3 tubes with the power of  
4 tubes. In two-tone mahogany  
cabinet, housing all batteries.  
(Without  
Accessories) **\$49.50**  
West of Mississippi \$60



**EMPIRE MODEL**, in reality a 6  
tube set operating on 4 tubes.  
Enclosed in 17th Century Solid  
Mahogany French Cabinet, hous-  
ing all batteries. **\$125**  
(Without Accessories)

Products of  
**David Grimes Radio  
& Cameo Record  
Corporation**  
1571 Broadway, New York, N.Y.

**EVEREADY HOUR  
EVERY TUESDAY AT 8 P. M.**  
*(Eastern Standard Time)*

For real radio enjoyment, tune in the "Eveready Group." Broadcast through

WEAF	New York	WSAI	Cincinnati
WJAR	Providence	WWJ	Detroit
WEEI	Boston	WCCO	Minneapolis
WFI	Philadelphia	WOC	St. Paul
WGR	Buffalo		Davenport
WCAE	Pittsburgh		

# PREFERRED

It is no accident that more Eveready Radio Batteries are purchased by the radio public than any other radio battery made.

Such complete and voluntary endorsement can lead to but one conclusion—for best reception and longest life, Eveready Radio Batteries lead the field.

You can prove this for yourself by hooking Eveready Radio Batteries to your set. You will find that they deliver a steady, vigorous stream of power that lasts longer. It is Eveready economy that has created such an overwhelming preference for Evereadys. For every radio use there is a correct, long-lasting Eveready Radio Battery. There is an Eveready dealer nearby.


*Manufactured and guaranteed by*

**NATIONAL CARBON COMPANY, INC.**  
New York San Francisco  
Canadian National Carbon Co., Limited, Toronto, Ontario

# EVEREADY Radio Batteries

*-they last longer*

Eveready  
Columbia  
Ignitor  
"A"  
Battery  
The  
proven  
dry cell  
for all  
radio  
dry cell  
tubes  
1½  
volts

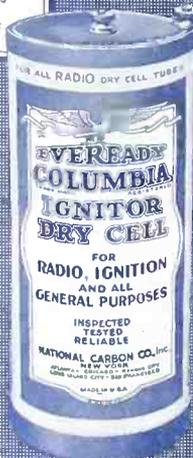

No. 772  
45-volt  
Large  
Vertical  
Price  
\$3.75



No. 767  
45-volt  
Large  
Horizontal  
Price  
\$3.75  
With  
variable  
taps