

RADIO WORLD

Title Reg. U.S. Pat. Off.

#183

Vol. 8. No. 1 ILLUSTRATED Every Week

USING A SECONDARY AS A LOOP

By J. E. Anderson


HOW TO WIRE UP THE 1926 DIAMOND

By Herman Bernard


William Bergstrom

THE 8-TUBE SUPER-HETERODYNE

By Sidney E. Finkelstein

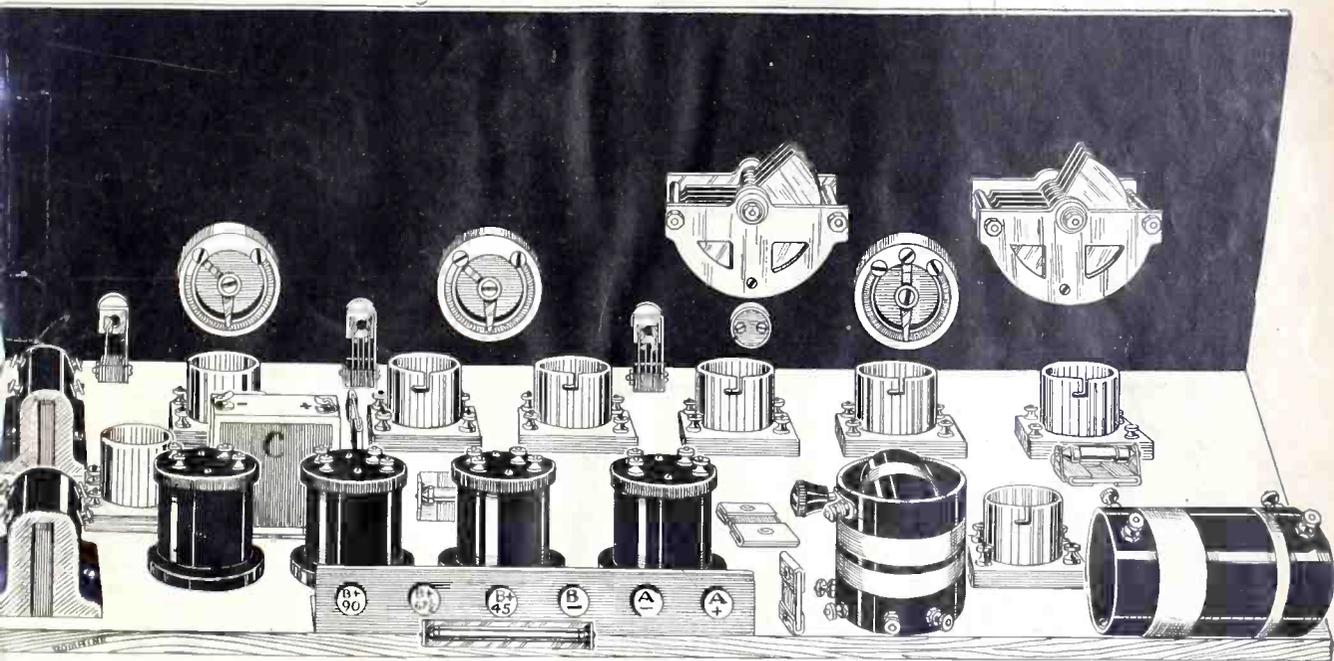

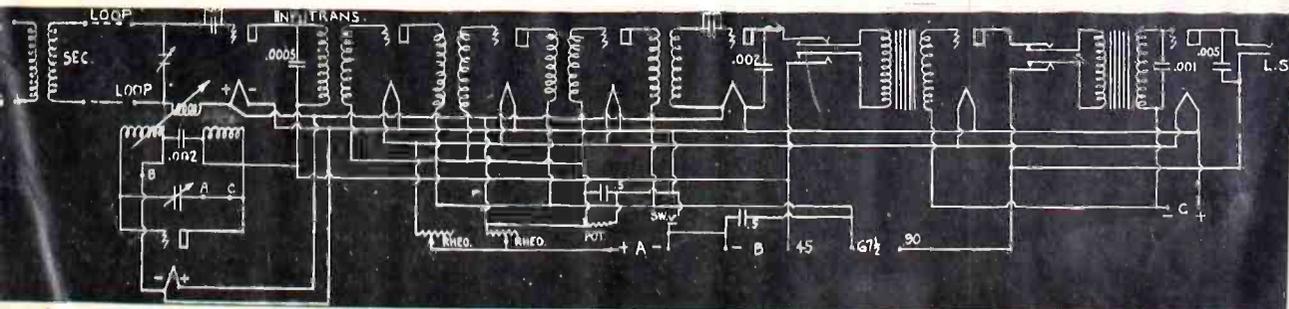REAR VIEW of the 8-Tube Standard Super-Heterodyne showing the placement of the parts. See article on page 8.



THE WIRING of the 8-Tube Super-Heterodyne


The World's Greatest Radio Values!



Model 5-F-6
The Perfect Combination

Genuine mahogany, loud speaker built as part of set itself, and plenty of room for all accessories in the table.

\$82⁵⁰

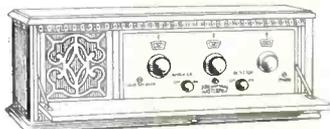

Receiving Set of the Franklin Console
Genuine mahogany with full-throated loud speaker built in.

\$75



\$115

The Franklin Console
Composed of two separate and distinct units. 5-ply genuine mahogany in a two tone effect of soft and alluring beauty.



Master "B" Eliminator

Connects from light socket right to your radio. Constant and uniform power all the time—free from noises caused by chemical action in "B" batteries.

A. C. Model **\$20** D. C. Model **\$17.50**

Freshman Rectifying Tube for use with A. C. Model.....\$2.50

New and Improved FRESHMAN MASTERPIECE


Five-Tube Tuned Radio Frequency Receiving Sets For Dry or Storage Battery Tubes

A complete line of the world's most beautiful radio receiving sets, ranging from the improved 5-Tube Tuned Radio Frequency Receiver listing at \$39.50 up to the handsome, genuine mahogany Franklin Console, of vigorous lines and fine proportions, at \$115.00.

Write for illustrated booklet (in seven colors) describing our entire line.

For Sale by Authorized Freshman Dealers Only

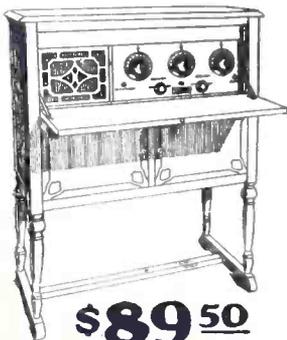Chas. Freshman Co. Inc.
Radio Receivers and Parts
FRESHMAN BUILDING
240-248 WEST 40TH ST.—NEW YORK, N.Y.
CHICAGO OFFICE — 327 S. LA SALLE ST.



\$89⁵⁰


Model 5-F-7

A ruggedly built piece of furniture of conservative and stately appearance. Built-in loud speaker.



Model 5-F-5
The Sensation of the Season.
Made of finest low loss materials with built-in loud speaker in a genuine mahogany cabinet.

\$60

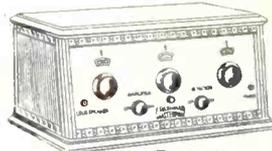

\$49⁵⁰

Model 5-F-4 The Perfect Radio
In the genuine mahogany cabinet it is the equal in appearance, as well as performance, of any set on the market, regardless of price.



\$39⁵⁰

Model 5-F-2
The Greatest Buy in Radio
In a massive cabinet of striking lines and pleasing appearance, with sloping panel. Distance—Selectivity and Clarity combined.



\$75

Concert Model
An exquisite article of furniture made of the finest mahogany, in a two-tone effect with a rich, subdued wax finish.

RADIO WORLD

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under the Act of March 3, 1879]

A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawanna 6976 and 2063

Vol. VIII. No. 1. Whole No. 183.

September 26, 1925

15c per copy, \$6.00 a year

How to Wire the Diamond Explicit Directions for the 1926 Model

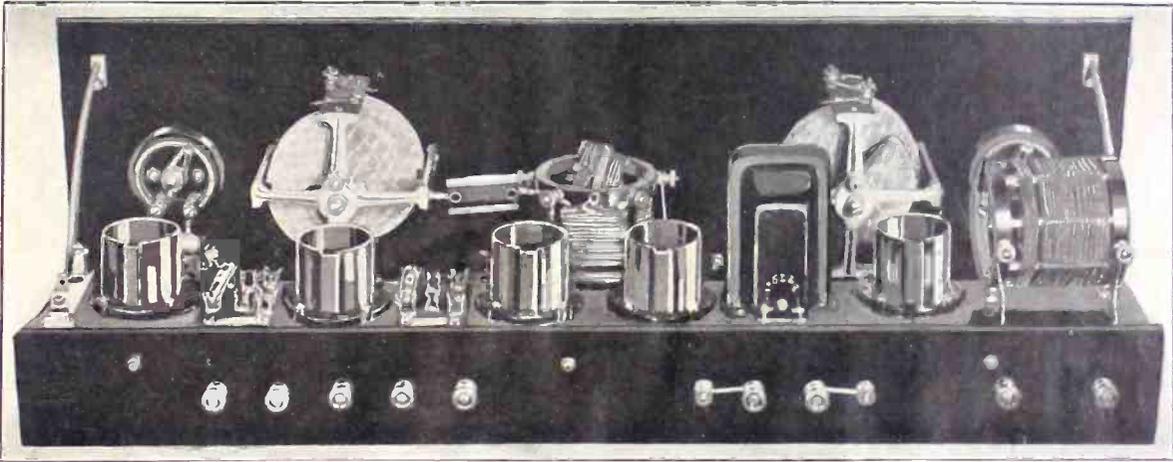


FIG. 7, rear view of the 1926 Model Diamond of the Air. The binding posts, right to left on the supporting strip, are (1) aerial; (2) ground; (3) detector plate; (4) P post of AFT; (5) B post of AFT; (6) B+ No. 1; (7) A minus; (8) A plus; (9) B minus; (10) B+ No. 1, and (11) B+ No. 2. Note (6) and (10) are the same lead. The two are interconnected behind the supporting strip that holds the binding posts, as (10) better accommodates the battery cable lead. Posts (4) and (5) are T and T in Fig. 8.

["How to Build Radio World's 1926 Model Diamond of the Air" is published in three parts, of which the following is the final one. Part I appeared September 12 (Radio Show Number), Part II was in the September 19 issue.

The 1926 model Diamond was exhibited at the two big radio shows held recently in New York City and evoked exclamations of appreciation of its expertness of design and handsome appearance. As for its performance, it is one of the most efficient receivers that the art has yet produced.—EDITOR.]

By Herman Bernard

Associate, Institute of Radio Engineers

PART III

THE panel template, Fig. 2, was published in the September 12 issue. The dimensions were given, and these will guide you or, if the same parts are used as in the original model, will be your unailing authority. The center shaft holes will apply universally so far as the two variable condensers, the 3-circuit tuning coil, the two rheostats and the Bretwood Variable Grid Leak are concerned. Other points of variation may arise if other parts than those prescribed are employed.

In Fig. 2 at extreme left are two holes, both countersunk, this fact being represented by the double ring effect in the diagram. Corresponding holes are at the right-hand side of the panel. These four holes

are for machine screws used in mounting the Bruno brackets to support the socket shelf. If other bracket devices are used, then drill accordingly and to that extent disregard Fig. 2. Note that a No. 29 drill is used. This might not apply to some other make of brackets.

There are five holes along the bottom. These are, left to right, as you look at the front of the panel: loop jack, J1; battery switch, S2; Bretwood Variable Grid Leak, Ro; detector double circuit jack, J2; and the speaker single circuit jack J3. S1 and J2 are interchangeable as to permanent position on the panel. S1TT is not represented on the panel, except only so far as its connections interlink with J2, which already is provided for. Of the five holes, four are drilled with a $\frac{3}{8}$ " drill, as jacks and switches normally are accommodated by such size of aperture, while the Bretwood Variable Grid Leak, which also is a single panel mount device, has a $\frac{1}{4}$ " shaft, hence a $\frac{5}{16}$ " drill should be used to achieve easy clearance.

The Rheostat Mounting

The two rheostat shaft holes are $2\frac{1}{2}$ " from left and right ends of the panel, respectively, and are on a central line, $3\frac{1}{2}$ " from top and bottom of the panel plane. Use a $\frac{5}{16}$ " drill for shafts. If other rheostats are used than those in the original model, drill the shaft holes according to Fig. 2 nevertheless, but the countersunk mounting holes may have to be different. These are always to be distinguished from the center shaft holes. By holding a rheostat onto the panel, with the back of the rheostat at front of the panel, the two mounting holes may be conveniently located if other rheostats are used. If you have a template for the rheostats that you will use, by all means follow that. As both rheostats are of the same value, provided

the same type of tubes is used, the two shaft holes apply interchangeably to R1 and R2.

Next locate the shaft holes for the two tuning condensers, C1 at left and C3 at right. These are respectively $6\frac{1}{2}$ " from left and right ends of the panel, but not on the central line. They are 4" up. For the Bruno condensers follow Fig. 2. For other condensers, drill holes to suit them, using a template, even if you have to make your own template from cardboard. As each condenser is a .0005 mfd. variable (500 micro-mfd.), these two locations interchangeably represent C1 and C3.

There remains only the 3-circuit tuning coil, L2, L3, L4. This is not mounted on the central line either, but is $4\frac{3}{16}$ " up. The panel appearance is made more attractive by this method and plenty of room reserved for the grid leak. The hole for the mounting screw is shown on Fig. 2 for the Bruno coil, but if another make of coil is used be sure to drill the proper mounting screw holes. The shaft hole is correct for virtually every type of 3-circuit coil made.

Cabinet Holes

That ends the panel drilling, except that, after the set is completed, and it is to be permanently installed in a cabinet, two small drill holes will be made at the left and right sides of the pane (four in all) and two at top and bottom of the panel (total, eight), so that wood screws may be used to secure the panel to the cabinet. Countersink these holes. If your cabinet has two grooves at the sides so that the panel may be slid in and held taut, then no drilling for cabinet fastening is necessary.

Note that the rheostat R1 and the loop jack are in perpendicular alignment with each other; so are the grid leak and the tickler shaft, likewise the speaker jack and



Herman Bernard

Panel Drilling Directions

For the 1926 Diamond of the Air

the rheostat R2. Thus the loop jack and the speaker jack, just like the rheostats, are $2\frac{1}{2}$ " from the panel sides.

The panel is 7×24 " and no smaller size should be considered. The panel may be of hard rubber or, if the extra difficulty in drilling is not objectionable, may be Bakelite.

As previously mentioned, no simplification of the panel layout was attempted that would involve the slightest sacrifice of efficiency, and it is well to have on the panel every item stated.

After the panel is marked, the drilling is done, but the foregoing order will not be followed. Now, because the drill that is in the brace will be used for making all the holes of that size, then another drill inserted and all the holes of the new size made. For checking up purposes the following data are given: there are four holes to be drilled with a $\frac{7}{8}$ " drill; five holes with a $5/16$ " drill; eight holes with a No. 29 drill, and five with a No. 26 drill. The rheostat and bracket mounting holes require No. 29, the tickler and condenser holes No. 26. The bracket holes may be located, by the way, by consulting the right-hand side of Fig. 2 and reading the same dimensions into the left-hand side.

Socket Shelf and Terminal Strip

The socket shelf is 3" wide x 23" long. This is mounted horizontally. The binding post strip is $2\frac{1}{2}$ " wide x 23" long and is mounted upright. The socket shelf is notched for $\frac{1}{2}$ " square at both ends, but on one side only, to allow room for the Bruno brackets. The binding posts in Fig. 7, right to left, are located on a central line ($1\frac{1}{4}$ " from top and bottom) as follows, measured from right: (1), $1\frac{1}{8}$ "; (2), $3\frac{1}{4}$ "; (3), 6"; (4), 7"; (5), $8\frac{1}{4}$ "; (6), $9\frac{7}{8}$ "; (7), 14"; (8), $15\frac{1}{4}$ "; (9), $16\frac{5}{8}$ "; (10), $17\frac{7}{8}$ "; (11), $19\frac{3}{8}$ ". The socket centers, right to left on the shelf are: 5", 10", $12\frac{3}{4}$ ", 17", 21". The transformer central point is $7\frac{1}{2}$ " from right.

In Fig. 7 the two double mounts for resistors R3R4, R5R6, are centered $14\frac{1}{2}$ " and $18\frac{1}{2}$ " from right, respectively. The resistor R7 is put on a single mount which runs at right angles to the length of the shelf and is at extreme left. Behind the last socket in Fig. 7 is the ballast resistor R8, also in a single mount, which is next to and at right angles to the R7 mount.

On the bottom of the socket shelf is most of the wiring, excepting the A minus battery lead. Turning the set up 90 degrees from the Fig. 7 position (the same order of reading) the condenser C7 is mounted with connecting lugs at right, while C5 and C6 are mounted with lugs pointing toward the binding posts. At right of C5 is the grid condenser. Socket terminals and various leads are the only other things on the bottom of the shelf.

The panel drilled, mount the parts. If you find that through some inadvertence one or more of the parts do not mount conveniently, for instance, rotor shafts bind, remove that part and drill the shaft hole oversized, if necessary, using an old pair of scissors to enlarge the hole. In that way even if mounting holes (for machine screws) do not coincide with the threaded holes in the instruments, you will likely make them do so by enlarging the shaft hole, thereby enabling you to move the instrument to proper position, which the $5/16$ " hole prevented. Under no circumstances, because of incorrect drilling, tolerate the use of only one mounting screw where two are called for. Do not trust to chance that things will turn out all right. Particularly must the grid leak, variable condenser, rheostat and tickler shaft enjoy easy motion,

Order of Marking Panel for the Set

The marking for drilling the panel for the 1926 Diamond may be done conveniently in the following order: **First, tickler; second and third, tuning condensers; fourth and fifth, rheostats; sixth, grid leak; seventh, A battery switch; eighth, double-circuit jack; ninth, loop jack; tenth, speaker jack; eleventh and twelfth, thirteenth and fourteenth, the bracket holes.**

otherwise the mounting will be awry, if not at first, then after the misfit instrument is used awhile. The rheostat arm may stick or the condenser plates touch, later on, due to poor mounting on the panel.

The Socket Shelf

Now mount the parts required on the (horizontal) socket shelf, these including the coil LoL1, the five sockets, the audio transformer, the two double mount resistor receptacles and the one single mount. The drill holes for these must be determined by the constructor, unless the commercial type is used, for they will vary considerably, depending on the make of instruments. But this drilling is very simple. Fig. 7 will be a great aid to anybody who meets any trouble at this point.

In mounting the RF coil, shown at right in Fig. 7, be sure to mount it as shown, and not perpendicularly. The reason is that for best efficiency you do not want this coil to function with a loop effect and independently pick up broadcast energy when you are using an outdoor aerial. Perpendicular position of mounting creates the loop effect, because the windings will then be in a direction quite suitable to energy pickup. As the two coils, LoL1 and L2 L3 L4 are mounted at right angles to minimize or prevent inductive feedback from detector to RF stage, the 3-circuit coil is in loop effect position, but at a point where it is ineffective for such, e.g., it is an interstage coupler.

In Fig. 7 the tubes are, right to left: RF, detector, first (transformer) radio and second and third (resistance) audio. The inverse order is due, of course, to the fact this is a rear view. At extreme left is the single mounting for the resistor in the plate circuit of the final tube (R7). Note that the coupling condensers, C5, C6 and C7, are not visible. They are mounted under the socket shelf. See Fig. 5 in last week's issue (September 19). The sub-mounting accounts for the vacant clips in the center of the double mountings.

Note in Fig. 7 where the by-pass condenser is placed, supported only by the busbar joining it with the condenser C3 and the coil L3.

Reconciliation

Before proceeding with wiring directions it is well to reconcile some diagrammatic discrepancies:

(1) The blueprint published September 12 proved such a poor engraving that some of the lines failed to register (e. g., from battery to R8) and also this made the diagram read as if both A leads were closed at F+ on the detector tube. Hence disregard the blueprint and follow the blackprint published this week, Fig. 8. This corresponds in all particulars with Fig. 1, the schematic diagram published in the September 12 issue.

(2) S2 is the A battery switch, as

shown in Fig. 1, September 12, and as shown in picture form, Fig. 8, this week. S1 is a special binding post switching device, with double-pole double-throw effect, and a DPDT switch may be used (Fig. 1, September 12) or just the binding posts (Fig. 8), and I think the posts should prevail, as they are cheaper and avoid overcrowding the socket shelf, as all the posts are on the broad, long terminal strip that also acts as a support on the shelf, by the aid of three $1\frac{1}{2}$ -inch brass right angles.

(3) The picture diagrams all show the RF coil mounted perpendicularly. Disregard the diagrams to this extent.

(4) The three resistors not in the photograph, Fig. 8, should be there.

Preparatory to wiring, securely mount the brackets in the rear of panel and mount the socket strip on the brackets. Drill for binding post holes on the socket strip, following Fig. 8 approximately. Of course there is leeway here—as elsewhere—but watch your step! J. E. Anderson, the noted radio engineer, was so struck with the 1926 Model Diamond of the Air that when I showed him the diagram in advance of publication he taxied back to his private laboratory and built the very set the photographs portray. In fact, Fig. 9 shows him pointing an approving finger at that part of the audio hookup where novelty exists. This is the set he now uses for broadcast reception.

The binding posts, right to left, as you look at the rear view, Fig. 8, are (1) aerial; (2) ground; (3) detector plate; (4) beginning of primary, P, of AFT; (5) end of primary, B, of AFT; (6) B plus No. 1, normally 45 volts; (7) A minus; (8) A plus; (9) B minus; (10), B plus No. 1 again, the common lead from 6 to 10 being carried under the socket shelf; (11) B plus No. 2, normally 90 to 135 volts, preferably 135.

The Wiring Directions

Begin wiring with the filament circuit. We will assume that the set is to be operated so that the A battery switch, S2, turns the set on or off as a unit (Fig. 1, September 1 issue, Fig. 8, this week's issue).

Connect A battery minus to one side of the switch, the other side of the switch to the post of R1 that makes contact with the movable arm of that rheostat (see special detail diagram, September 12). Carry this lead over to the same position on the other rheostat, R2, R1 is for the RF tube, R2 for the detector. Continue this lead to one side of the $\frac{3}{4}$ -amp. ballast resistor, R8. Now join the remaining open sides of R1, R2 and R8 to the proper binding posts on the sockets. R1 goes to F minus of the RF tube (1); R2 goes to the F minus post of the detector tube (2); R8 goes to the F minus post of all three audio tubes 3, 4 and 5). A plus is connected directly to the F plus posts of all five sockets.

The Aerial Transformer

All coils are wound in the same direction and only in that event do the following data apply to the polarity question. The aerial is connected to the extreme right-hand binding post in Fig. 7. That is the beginning of the primary, the same relative position as shown in the picture diagrams. Because the post is at right and nearer the end of Lo do not assume that the connection is made to the end of Lo, for the terminals of Lo are brought through the inside of the coil form to posts on the form itself, to secure the winding in place, this being done in the

The Full Wiring, Step by Step

Bernard Gives Directions In Masterly Detail

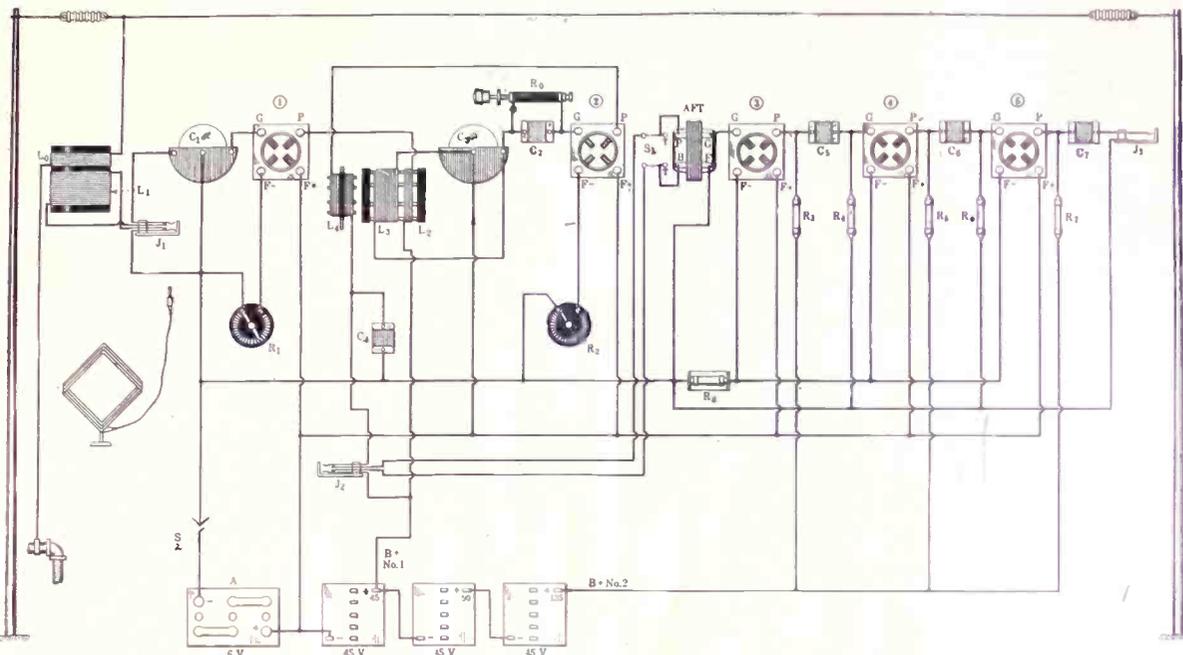


FIG. 8, the circuit diagram of the 1926 Diamond shown in picture form, with the A battery switch S2 used as a master switch, to turn the set on or off as a unit.

manufacture of the coil. Hence the connections actually are just as explained. The end of L_0 is joined to the binding post, which will accommodate the ground connection. That completes the wiring of the primary of the aerial circuit transformer, $LoL1$.

As for the secondary, also be careful to follow the directions precisely. The beginning of the secondary goes to the lower inside prong of the jack, that is, the spring third from top. The jack referred to is the double-circuit one, $J1$. The right angle of the jack, that is, the lower outside terminal, the one that makes contact with the beginning of $L1$, goes to A battery minus and to the rotor plates of $C1$. Do not make this connection to filament minus. The difference between the two is that A minus is the lead as it comes right from the battery, while F minus is the same lead after it has gone through the rheostat $R1$. If you connect to F minus (i. e., the socket post) instead of to A minus (battery post) you will destroy the bias effect possible from the actuation of the rheostat, and also possibly cause a tuning effect due to the inductance in the wire-wound rheostat being included as a part of the radio circuit. Follow directions and exclude it from the radio circuit. There is no radio in the A battery or filament wiring. Check up and notice whether the end of the primary L_0 goes to ground and the beginning of the secondary $L1$ goes to A minus. The beginning of the secondary adjoins the end of the primary. The remaining terminal of $L1$, end of secondary, goes to the other inside spring of $J1$, second from top, while the hooked spring, the uppermost jack lead and the only remaining unconnected one on $J1$, goes to the stator plates of $C1$, and to grid or G post of the RF tube, No. 1.

The stator plates are represented in the picture diagram by posts at the outside of the end plate, while the rotor is represented in the middle, where the con-

Bernard Audio Circuit an Original Hookup

The double-pole double-throw switch effect from binding posts (SITT) affords a novel advantage. In Fig. 7 the posts are shown third, fourth, fifth and sixth from right, on the terminal stub. Notice that two pieces of bus bar are used, each one joining the outside post to its neighbor. These pieces are called "straps." They are left just as shown when The Diamond of the Air is used as a unit. But should one desire to hookup some external detector circuit, to get speaker volume through the Diamond audio amplifier, this may be done very readily by pivoting the straps off the large binding posts, letting them hang from the smaller ones, and connecting the experimental detector circuit to the large posts, which represent the audio input (P and B in AFT). Also, with the straps in "off" position, as described, the smaller posts, representing the detector output of The Diamond, may be connected to an external audio-amplifier, to compare the results of The Diamond's audio hookup with those obtainable from some other kind of audio-amplifier. This connection to an external amplifier could be made through a plug inserted in $J2$. $J2$ is for earphone use when The Diamond is operated as a unit, to tune in a DX station perhaps. The idea of listening to programs on earphones is getting less popular year by year. But any one desiring to avail himself of this service may hookup the A battery switch according to Fig. 4, September 19 issue, or pull out the ballast resistor $R8$, of Figs. 1 or 8 is followed, to unlight the three AF tubes, or simply remove those three tubes from the sockets.

The audio hookup is a novelty at the final output, no B current flowing in the speaker, and no C battery being required, neither of these things being true of the so-called standard resistance hookup.

denser shaft would be, for it is this that moves. Both outside posts therefore represent exactly the same lead, since the end plate is only one piece of metal. The rotor is insulated from the stator and hence represents another lead. Do not be confused therefore by the seeming existence of two leads (one to grid end of the secondary, the other to grid), whereas in fact they are one lead and the condenser stator is used for omitting a few unnecessary inches of busbar.

You connected the stator of $C1$ also to the grid of the RF tube, marked G on the socket. If there are no identifying marks on the sockets, take the position of the bayonet hinge, i. e., slot of the socket, as your guide. Considering the slot as in the center, at rear, of the socket, the post at left front will be A minus, that at right front will be F plus, that at left rear will be grid and that at right rear will be plate. Standard sockets are being considered, not the 99 type, which are different.

The Interstage Coupler

Connect the plate (P post) of the RF tube socket (No. 1) to the beginning of $L2$, the small winding on the stator form of the 3-circuit tuning coil. The end of this coil goes to the B plus 45 volt binding post. This would be a marked B plus detector, since the same voltage will be used on the detector plate. Also connect this B plus lead to the third spring from top in the double-circuit jack $J2$, called the detector jack. The beginning of the secondary, $L3$, that terminal adjoining the end of the primary, goes to the rotor plates of $C3$ and to A plus. The other terminal of $L3$ goes to the stator plates of $C3$, to one side of the grid condenser $C2$ and to the connection or lug of the grid leak L_0 , which is almost against the panel. The remaining open end of the grid condenser goes to the G post of the detector tube socket and to the terminal of the grid leak, which is farther

Anderson Is "First Customer"

Noted Radio Engineer Picks 1926 Diamond

LIST OF PARTS

One RF transformer, L0L1.
 One 3-circuit tuner, L2L3L4.
 Two .0005 mfd. variable condensers, C1, C3.
 Two 20-ohm rheostats, R1, R2.
 One variable grid leak, R0.
 Two double-circuit jacks, J1, J2.
 One single-circuit jack, J3.
 One audio-frequency transformer.
 Fixed condensers: One .00025 mfd. grid condenser, without clips, C2; one .001 mfd., C4; three 0.25 mfd., C5, C6, C7.
 One $\frac{3}{4}$ -ampere ballast resistor, R8.
 One A battery switch, S2.
 Three 0.1 meg. resistors, R3, R5, R7.
 Fixed leaks, 1.0 meg., R4; 0.5 meg., R6.
 Five sockets.
 Three 4" vernier dials.
 One 7x24" panel.
 One socket shelf, 3x23".
 One pair of brackets.
 One terminal (binding post) strip, 2 $\frac{1}{2}$ x23".
 Eleven binding posts (includes provision for S1).

Three brass angles ($\frac{3}{8}$ to $1\frac{1}{2}$ " arms).
 Accessories: One 24" cabinet, 8" deep inside, as the set is 7" deep; 100 ft. aerial wire; 50 ft. No. 14 insulated leadin wire; One lightning arrester; one loop for .0005 mfd. condenser tuning; one speaker; two phone plugs, one for loop, one for speaker; six 6 32 nuts and $\frac{1}{2}$ " bolts for right angles; one 100-amp. hr. storage battery for 6-volt type tubes; three 45-volt B batteries.

The parts used in the original model: L0L1, 99 RF; L1L2L3, No. 99 3-circuit tuner; C1, C3, No. 21 condensers; R1, R2, 20-ohm rheostats, all these Bruno; J1, J2, Arco; J3, Arco; AFT, General Radio No. 285; C2, C4, C5, C6, C7, Dubilier; R3, R5, R7, R4, R6, R8, Weby resistors; Brooklyn Metal Stamping vernier dials; R0, Bretwood Variable grid leak; Bruno socket shelf, Bakelite sockets, Bruno brackets.

from panel. The P post of the detector tube socket (No. 2) goes to the end of L4, the tickler coil, while the beginning of L4 goes to the top spring (hooked leaf) of the detector jack J2. If confused as to the tickler connections, because the actual connections are hidden, due to pigtail leads, etc., hook up the tickler either way experimentally, determine which way works to your greater satisfaction, and make that gratifying connection permanent. C4, the .001 mfd. bypass condenser, should be connected from B plus 45 volts to A minus.

The Audio Hookup

It will be noticed that the inside springs of the jack J2 are still unconnected. The spring (second from top) that makes contact with the tickler coil L4 (by closing on the top hooked spring) goes to one of the smaller binding posts shown (4) in Fig. 7. The remaining unconnected inside spring, third from top, goes to the other small binding post. Of course all binding posts may be of the same size, but if so, be sure to identify them. Metal markers are purchasable for a few cents. Scratch the figure "1" for plate and "2" for B plus on the binding post stub. Connect the two detector output binding posts to the two larger ones that adjoin them, using bus bar as the straps (Fig. 7). The detector plate lead is connected to the P post of the audio transformer AFT, while the B plus 45 lead

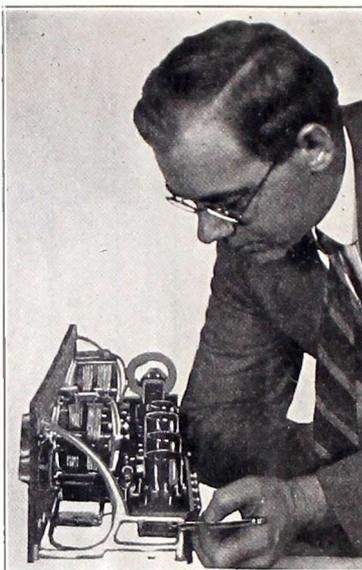


FIG. 9. J. E. Anderson, noted radio engineer, and the 1926 Model Diamond of the Air he built for his personal use.

goes to the B post. G on AFT goes to grid of the first audio tube (No. 3), while F of AFT is connected to A minus (not to F minus).

On some transformers the markings are different than P, B, G and F. The following covers all the systems used: P, P1 or 1, for the beginning of the primary, the connection made to plate; B, P2 or 2 for connection made to B plus; G, S1 or 3, for beginning of secondary, the connection made to grid; F, S2 or 4, the connection made to A minus.

The plate of the first audio tube (No. 3) is connected to one side of the 0.25 mfd. fixed condenser, C5, and also to one side of the 0.1 meg. resistor, R3. The other or remaining free side of that resistor goes to B plus, which may be 90 volts with good effect, but preferably should be 135 volts for greatest volume. This B lead is shown as B plus No. 2, while B plus No. 1 is 45 volts (for detector and RF). The open side of C5 goes to the grid post of the second audio tube (No. 4) and to one side of the resistor R4, which is 1.0 meg. (one megohm). That fixed resistor is a leak, not to be confused, however, with the variable grid leak. The other side of R4 goes to A minus (not to F minus).

The plate of the second audio tube (No. 4) goes to one side of the 0.25 mfd. fixed condenser, C6, and to one side of the resistor R5, which is 0.1 meg., as are all the plate resistors. The other side of R5 goes to B plus No. 2 (high voltage). The open side of C6 goes to one side of the leak R6, which is 0.5 meg. The other side of this leak goes to A minus (not F minus).

And now for the odd part of the audio hookup, which appears in this form in the 1926 Diamond for the first time anywhere, so far as I know.

The same coupling and isolating system is followed as in the resistance stages of audio. The plate of the last tube connects to one side of the 0.25 mfd. fixed condenser C7 and also to one side of the resistor, R7, which is 0.1 meg. The other side of R7 goes to B plus No.

2. The remaining unconnected side of C7 goes to the hooked spring of the final jack, J3, while the right angle of the jack, or only other terminal thereon, goes to A minus.

This completes the wiring of the set itself. The external connections remain to be made.

Up to this point connections have not been made to A minus, A plus, aerial, etc., as only the binding posts to which these leads will be joined have received the actual contact. Now physically connect A minus to its post and A plus to its post. Then five tubes in the set at once. See if they light when they should. See that the rheostats actually govern the brilliancy of the two tubes they control. Try the switch. See that it turns the set on and off as a whole. Assuming that all works well so far, or that if trouble is encountered, that it is checked up by the textual or diagrammatic directions and remedied, take all five tubes out of their sockets. Disconnect A minus from its binding post. Connect B minus (of a 45-volt battery) to A plus and connect B plus 45 to its post. Now insert one tube in one socket only. See if the tube lights. If it does, take it out as quickly as possible. There is a short circuit. Find it. Remedy it. Of course use an old tube for this particular test if you have one that at least lights. If a short circuit existed and is assumptively remedied, put the tube in the same socket again. If it does not light repeat the test for the four remaining sockets, with the same tube. Do not try all five tubes at once under this test. All being well, restore the A minus lead to its proper binding post, leave B minus connected to A plus, and connect the one or two remaining 45-volt B batteries, depending on whether you intend to use 90 or 135 volts. You need not be afraid that 90 volts will not work well, nor need you doubt that 135 volts will not give fuller tone. The A and B batteries are connected in series, i. e., A minus is the starting point, A plus connects to B minus, B plus 45 on that the already-connected B battery goes to B minus on the next succeeding B battery of 45 volts, B plus 45 on the second B battery goes to B minus on the third and B plus on the third goes to binding post for B plus No. 2 in the diagrams. As series connection adds the voltages, the highest voltage post on each of the three batteries is, in the order of sequence, 45, 90 and 135.

The actual voltage used is a little more, because the A battery is in series too, hence contributes additional voltage. It is not the full 6 volts, but 6 volts minus the voltage drop in the filament resistors, say 1 volt, hence the actual voltage posts may be taken to be 50, 95 and 140.

Now connect aerial and ground to posts, and speaker to J3 and tune in.

Loop or Outdoor Aerial

If a loop is to be used, attach the loop cords to a phone plug and plug in at the detector loop jack, J1. This lifts the springs connecting to L1 and hence Lo L1, which means the aerial and ground system, is out of the circuit and the loop alone supplies the pickup. Many fans reported receiving great distances on a loop with speaker volume, some of them asserting that they had coast to coast reception on the speaker. I frequently tune in Florida and Chicago stations on a loop from New York City, and I have scarcely been able to receive any station
 (Concluded on page 24)


A HOME-MADE NEUTRALIZING CONDENSER

By Herbert E. Hayden


HERE is how to make a precision neutralizing condenser: Mark off a square of 1" on a piece of
(Concluded on page 13)



TOP to bottom, Figs. 10, 11 and 12.

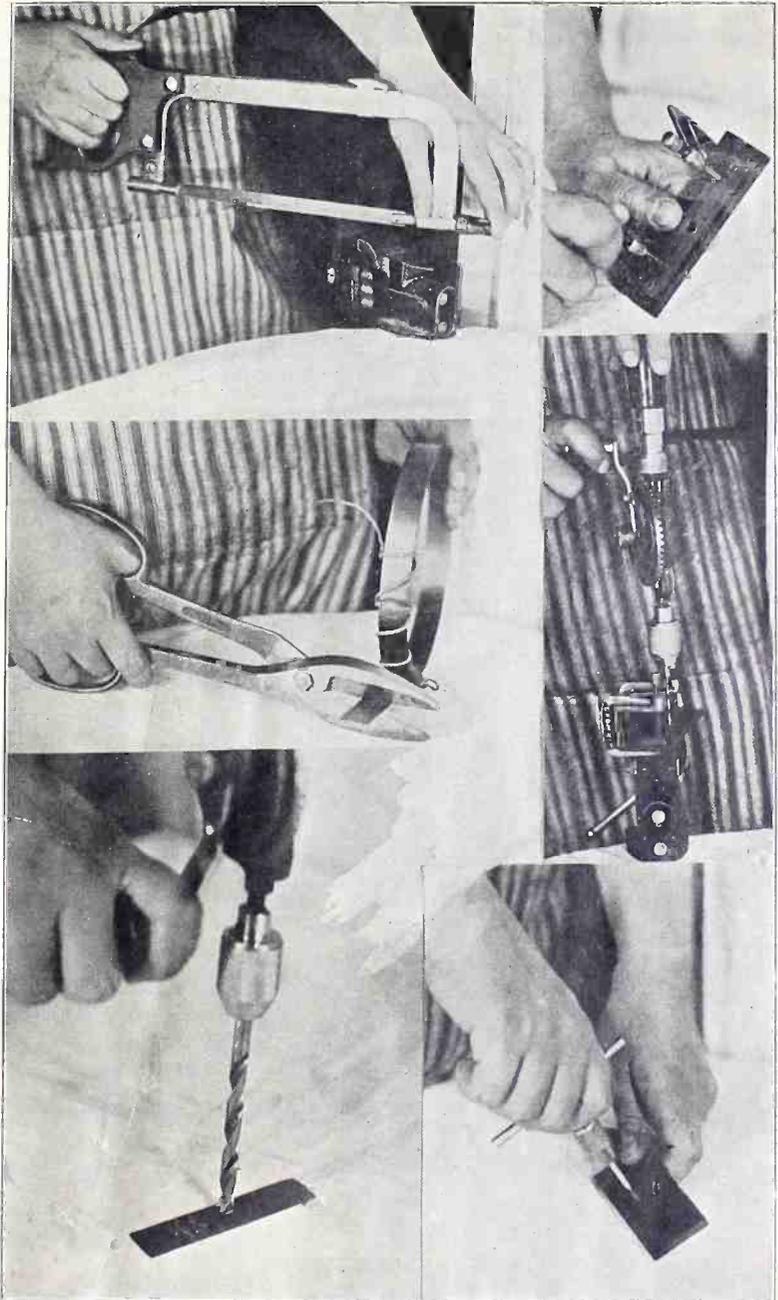

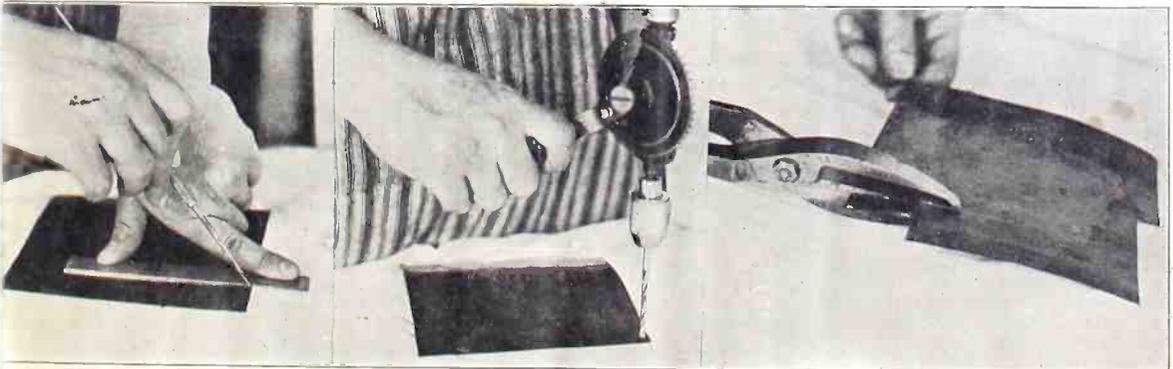LEFT, top to bottom, Figs. 4, 5 and 6. Right, top to bottom, Figs. 7, 8 and 9.



LEFT to right, Figs. 1, 2 and 3, showing cutting of phosphor bronze.

The 8-Tube Super-Hetrodyne

By **Sidney E. Finkelstein**

Associate, Institute of Radio Engineers

HERE is no receiver, disregarding the number of tubes employed, that can equal the Super-Heterodyne in every respect.



SIDNEY E. FINKELSTEIN

The only possible objection to this receiver was that there are eight tubes. This objection is now wiped aside, I believe, due to the low cost of tubes, and the small amount of current that the filaments consume. By properly biasing the grids of these tubes the B battery consumption can be cut in half.

There are only two major controls. One is the tuning condenser and the other the oscillator condenser. Both of these should be of a very good grade, as the most efficient working of this set depends much on these instruments.

The Welty coils are made for this receiver, also the intermediate transformers.

How to Make Coils

Procure a bakelite, hard-rubber or cardboard tubing with an inside diameter of 2". The height of this tubing should be about 3 3/4". The wire used for the winding of this coil is No. 24 DSC. These data are for the antenna coupler. Stand the form up. One half inch from the top, in any portion of the circumference, make a dot. One and one-half inches from this dot and in the same line as the other dot, make another dot. Now stand the coil on the other circumference. Draw a straight line from one dot to a point on this circumference. Draw another line from the other dot to the same end of the form as the other one was. You will now find that these two lines are parallel to each other and separated 1 1/2" at all points, in other words the lines are equi-distant. On this line drawn, but 1/2" from the top of the form, make a dot. On the other

line and in the same plane make another dot. Drill 1/8" holes at all these dots. On any end, 1 1/8" from the hole, start winding the primary. Pull the beginning of the winding through one loop. Wind 11 turns. Punch a small hole here. Run the end of the wire through this hole and thence to the hole opposite the one in which the beginning of this winding was brought. Leave 1 1/2" and punch a small hole. This hole should be in between the two drawn lines.

Leave 1 1/2" and in the same line as the other hole just punched, punch another. Run the wire through this punched hole and pull through the drilled hole that is directly opposite the hole containing the beginning of wire. Wind 68 turns, which constitutes the secondary. Run the end of the wire through the punched hole and thence to the only other drilled hole left. Now insert binding posts in these drilled holes. Mark the post carrying the beginning of the primary winding ant. and the binding post carrying the end of this winding Gnd. The post carrying the beginning of the secondary (68-turn portion) is marked F plus. The post carrying the end of the winding is marked G.

Winding the Oscillator

Lay this coil aside. The next coil to be wound is the oscillator. Procure a form 2 3/8" in diameter and 2 1/4" in length. Stand the coil up on one end. One-half inch from the top and 3/4" apart, make four dots. Drill four holes through these dots. Stand the coil on its other circumference. One-half inch from the top and in between the two holes drilled at the other end, make a dot. One-half inch from the top, and also in the center of the other two holes make another dot. Drill two holes where these dots were made. The diameter of these holes are 1/8". Three-quarters of an inch to the left of one of the two holes just drilled, and in the same line, drill another 1/8" hole. Three-quarters of an inch to the right of the other hole drilled, make the final hole, which is also 1/8" in diameter.

One-half inch from the center of the hole of the first binding post start winding the plate coil. Run the beginning of

the wire through the first hole and continue winding 35 turns. Punch hole at the end of the winding and run this end to the hole adjacent to the hole carrying the beginning of the plate winding. Leave 1/16" and punch a small hole about 2" away from the hole punched for the end of the plate winding. One-half inch from this hole and in the same line punch another hole. Run the beginning of the wire through this hole and through the third drilled hole adjacent to the last one carrying the end of the plate winding. There are 39 turns wound. This is the grid coil. The end is run through the last hole punched, and to the only remaining drilled hole on that side, or adjacent to the hole carrying the beginning of the grid winding.

Now procure a form 1 1/4" in diameter and 3/4" long. One-half inch from both edges, drill a hole 1/8" in diameter. Take a ruler and lay it over the top of the form (either circumference). Make as straight a line as possible. Make a scratch on the end of the circumferences that have no hole drilled. Now 1/2" from the top and the bottom of the form, and where the scratch is, drill a hole. A perfectly straight piece of wood or any object should be run through these two holes, without any trouble.

Leave 1/16" from the edge and wind 10 turns. Connect the beginning to a small nut on the shaft of the tubing. Connect the end to the beginning of the other 10-turn winding which is separated 1/2" from this winding. Connect the ending of this winding to the lock nut of the shaft at the other end. This shaft is not one piece. On each end insert a piece of brass shaft. This should go through the holes of the smaller tubing. The length of these pieces of shaft should be 1 1/8". In order to hold the end of the shaft on, a lock nut or a piece of solder is put on the outside of the tubing. At this end, before the shaft enters the small tubing and after it enters the tubing, drop a piece of solder or insert a locknut. On the other end the same is done, except that at the end, there is set on a binding post head. This head should be either screwed or soldered on. Place some solder after the head is placed on the shaft. In order to make contact, there is a piece of copper plate between the lock nuts of both ends of the shaft to the binding posts to be placed.

How to Wire the Set


Bring the rotor plates of the variable condenser to a loop binding post and also to one terminal of the tickler coil. The stator plates of this condenser goes to the other terminal of the loop post, and to one terminal of the grid condenser as well as the grid leak. The other terminal of the grid leak goes to the grid post of the first detector tube. The other lead of the tickler coil goes to the F plus lead of this same lead. Connect the beginning of the plate coil to the rotor plates of the variable condenser, and to the plate post of the oscillator tube.

The end of this winding goes to one terminal of the .002 mfd. condenser, to one terminal of the input .0005 mfd. condenser, to the B post of the filter coil, to the 45-volt B plus terminal post, and to the upper terminal contact of the detector jack. The beginning of the grid winding goes to the left-off terminal of the .002 mfd. condenser and to the F minus posts on all the tubes. This F minus connection also goes to one terminal of the A battery switch. The other terminal of the switch goes to the A minus and B minus post on the terminal strip.

The end of the grid winding goes to the stator plates of the oscillator condenser and to the grid post on the oscillator tube. The plate post of the first tube goes to

(Concluded on page 26)

Receiver Calibrates Wavemeter

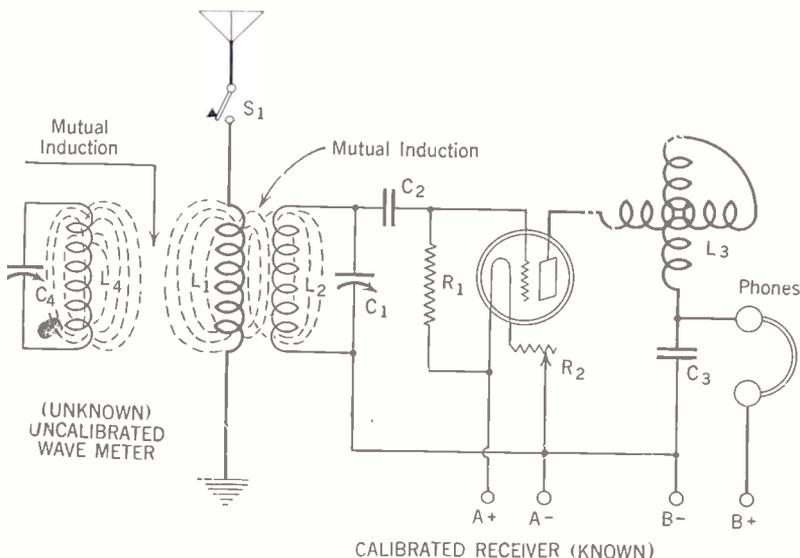

IF you know the dial readings of your regenerative receiver you may calibrate a wavemeter. C4 is a .0005 mfd. variable condenser. L4 is a 50-turn coil, wound on a tubing 3" in diameter with No. 22 DCC wire.

The 5-Tube Browning-Drake

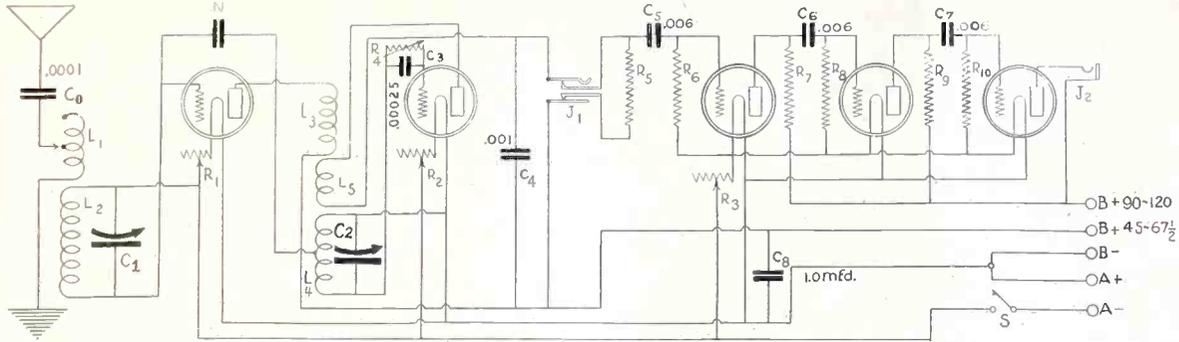


FIG. 1, wiring diagram of the 5-tube Browning-Drake receiver, including 3-stage resistance-coupled audio-amplifier.

By Capt. P. V. O'Rourke

ONE of the receivers that combines regeneration and tuned radio-frequency amplification that are very popular is the Browning-Drake, Fig. 1, shown as a 5-tube set. The circuit comprises one stage of RF, regenerative detector and three stages of resistance-coupled audio-frequency amplification. The RF tube is neutralized.

The primary of the aerial circuit transformer, L1, instead of being a plain winding and connected directly to aerial and ground, has an adjustable factor. The coil is not rotated for adjustment but a tap is taken on the primary. Instead of the aerial being connected directly to the primary it is joined to a .0001 mfd. fixed condenser, the other side of this condenser being connected to the movable arm of the tap switch. There should be two points on this tap switch and in addition two end stops.

The only other coil combination used in the tuned circuit is the 3-circuit inductance, L3L4L5. This is connected in standard fashion.

The diagram, Fig. 1, is so drawn that the correct manner of connecting the coil terminals is easily determined. For instance, the movable arm of the tap switch goes to one side of the aerial series condenser which is introduced at beginning of L1 or at the tap thereon. The ground goes to the end of L1 and a minus is connected to the beginning of the secondary and to the rotor plates of C1. This is actually shown in Fig. 1. The end of the secondary goes to the grid, to one side of the neutralizing condenser, N, and to the C1 stator plates.

With the 3-circuit tuning coil the same regard must be paid to polarities, and these are shown in Fig. 1 to be: plate to beginning of L3, B plus to end thereof; A plus to beginning of secondary (that terminal next to end of primary) and to the rotor plates of C2. The other secondary terminal goes to one side of the grid condenser to one side of the variable grid leak, and to the C2 stator plates. The tickler leads are so connected that the current flows in the tickler in the same direction as it does in the secondary, which is opposite to the direction in which current flows in the aperiodic primary, L3. Hence connect beginning of tickler to B plus and end to plate. This position is determined when the tickler and secondary windings are in the same direction.

In the audio circuit the hookup follows



CAPT. PETER V. O'ROURKE


that of the Daven unit, the Daven resistors being used. The coils for this set most commonly used are manufactured by the National Company, and this holds good of the variable condensers, too, which are .0005 mfd. each.

Coil Data



Those desiring to make their own coils may procure two 3 1/2" diameter forms, 4" high, and one form 2" diameter, 2" high. L1 may consist of 12 turns of No. 22 double cotton covered wire, tapped at the sixth turn, this tap being connected to the movable arm of the switch. It is a good plan to connect not only the tap to the movable arm of the switch but also to connect the beginning of the primary to the switch arm. This tends to minimize if not entirely prevent dead-end losses. The circuit as shown, however, is the one put forth by the sponsors of the circuit. Leave 1/4" space at end of the primary and wind 45 turns for the secondary. This completes L1L2 which are on one form. Next wind 12 turns for L3, leave 1/4" space, wind 12 turns of L4, take a tap (by looping the wire at this point and scraping insulation), then wind the additional 33 turns to constitute the full 45 for L4. The wire used in all these cases is the same kind and all windings are in the same direction.

The tickler consists of 38 turns of No. 26 SSC wire on the 2" diameter, room being allowed for the introduction of the rotor shaft of L5 (tickler). This shaft may penetrate the secondary L4 at the 1/4" space between L4 and L3. The tap on L4 goes to the open side of N.

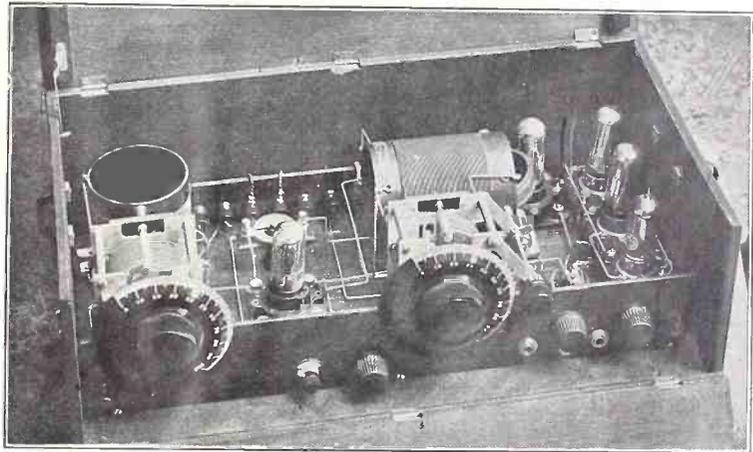The audio hookup has the following constants: R5, R7, R9, each 0.1 meg.; R6, 1.0 meg.; R8, 0.5 meg.; R10, 0.25 meg. The



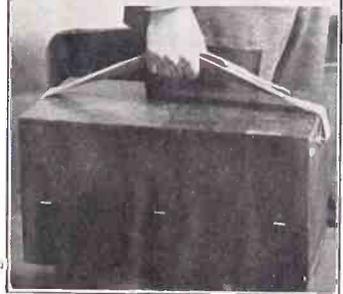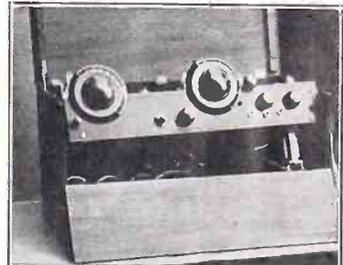A VIEW of the assembly of the portable set.




THE movable panel is shown above. The lower photo shows the set being carried in cabinet.

coupling-isolating condensers are .006 mfd. each.


The photographs show the set as built by R. E. Cox, a salesman of the W. L. Douglas Shoe Co., Brockton, Mass. He made it in portable form, so that he might have it with him in his travels, and when

(Continued on page 30)


Four Good Audio Hookups

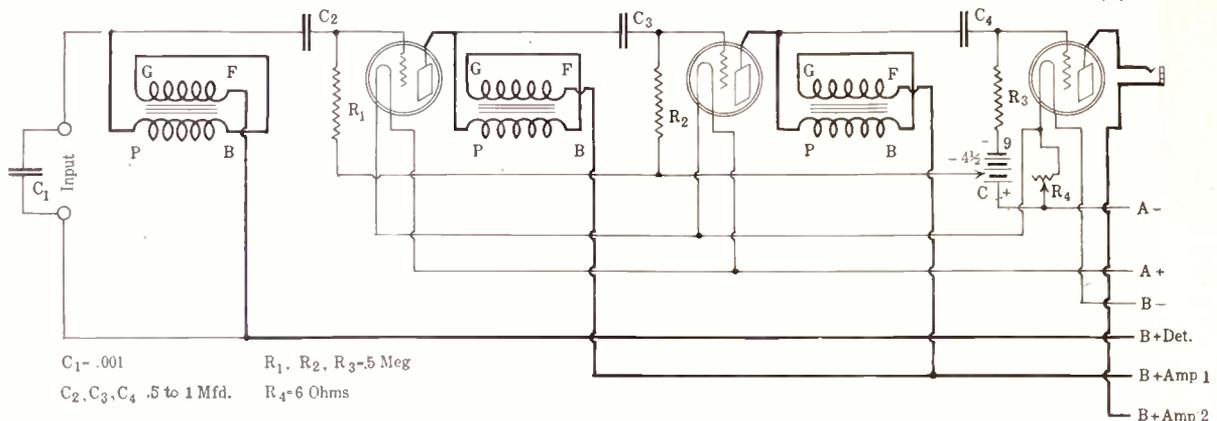

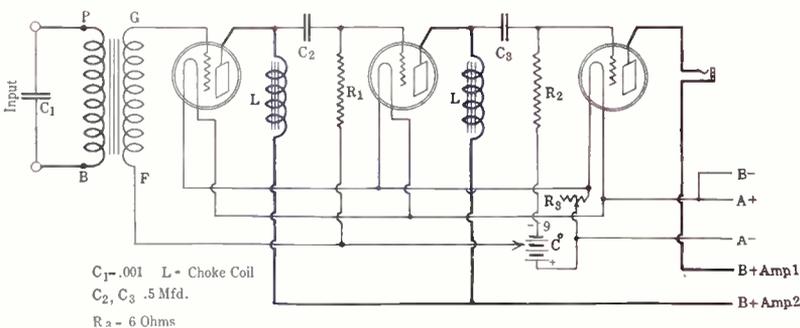
THREE stages of impedance-coupled AF amplification. Transformers are used as the choke coils, the primary and secondary of each being connected series-aiding. The markings are not correct for all types of transformers.



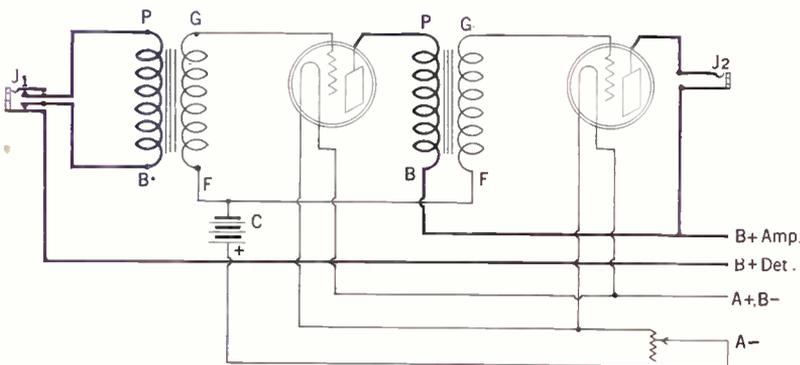
ONE transformer stage and two impedance steps. The choke coils L may be audio-transformers as in the hookup for three impedance-coupled stages. For C_2 and C_3 one may use .006 mfd., but .5 mfd. or even 1.0 mfd. would be better.



THE MOST POPULAR form of audio-amplification, consisting of two transformer-coupled stages. J_1 , a double-circuit jack, is connected with outer springs to plate of the detector tube (top leaf in diagram) and B+ detector voltage. The inner spring making contact with the outer plate spring goes to the P post of the first audio transformer, the remaining spring to the B post. A battery, about 4½ volts for 90 on the plate, is used for both stages. One rheostat actuates the filaments of the two tubes. J_2 is a single-circuit jack. No by-pass condensers are shown.

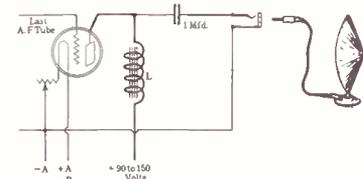

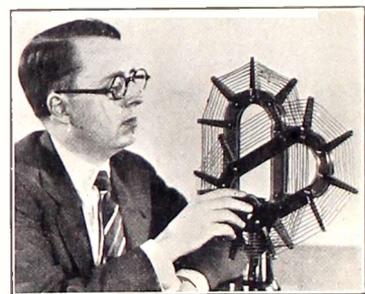HOW the final audio output may be connected from plate to filament. L is a choke coil.



STEWART C. WHITMAN demonstrating his new tuning loop aerial. It is the first loop of its type that tunes the incoming signals to the peak of the wave desired. Tuning is simplified, in that all dial readings may be Calibrated. A great directional effect is obtainable with this loop. (Kadel & Herbert.)

Prospective Stations to Plead for a Wave

WASHINGTON.

Several new broadcasting stations in course of erection throughout the country will not be able to get wavelengths unless there is a radical change in the situation. The class B band is already crowded to overflowing while practically all of the class A channels have been assigned.

It is reported that the owners of these new stations are preparing to attend the next national radio conference with the hope of being able to talk Secretary Hoover into giving them a wavelength. He has none.


Present plans are that there will be no reallocation of wavelengths this fall.

Some Recent Numbers

HOW TO BUILD THE POWERTONE, 1 dial, 5 tubes, described in RADIO WORLD, issues of Aug. 29 and Sept. 5. Powertone Trouble-shooting, Sept. 12. Send 15c for all three. Special diagrams and "blueprint in black" included among the many illustrations. RADIO WORLD, 1493 Broadway, New York.

A DYNAMIC SET. Enormous Power on 3 Tubes, by P. E. Edelman. An Anti-Radiation Toroid Set, by Capt. P. V. O'Rourke. Four Crystal Hook-ups, by Lewis Winner. Other features in RADIO WORLD dated July 25, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

The Weekly Rebus

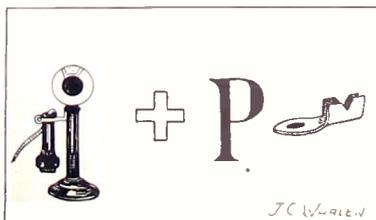

B Battery Eliminator Theory

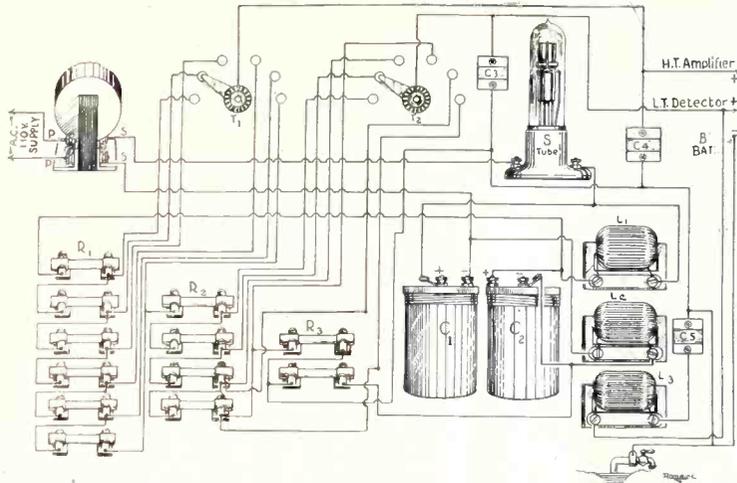


FIG. 1, showing the picture diagram of the tube B battery eliminator. Note that the last two resistances of the 4-125 ohm batch.

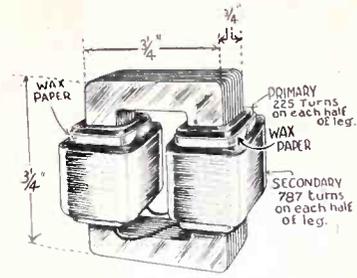


FIG. 2, showing how the AC transformer should be wound. Note the waxed paper separating the primary and the secondary windings. There is also waxed paper underneath the primary windings.

By Lewis Winner

Associate, Institute of Radio Engineers

[Part I of this article on how to build a B battery eliminator was published last week, issue of September 19. Part II, the conclusion, follows].

PART II

BY no means is this B battery eliminator perfect. It is, though, a step nearer the ultimate. It is the only one that can be made at home to come within most of the specifications of such an eliminator, which specifications are given later on in the text.



LEWIS WINNER

There is a hum, which cannot be noticed, however, except by the most discerning.

The operation of this eliminator is simple. All that is required for successful operation is to turn on the house juice and regulate the amount of voltage required for the specific tubes in your receiver. The voltage does not fluctuate at all. This can easily be tested with a voltmeter. The needle will not wiggle, that is, when each voltage is tried out, the reading of the voltage on the meter will be constant at all times, regardless of the length of time the meter is connected in series with the line.

No Worry

When working at these low voltages there is nothing to worry about insofar as flash overs or breakdowns are concerned. The instrument should work as soon as completed. Test your output leads and see if you are getting your rated voltage.

This instrument can be placed in a 7x18" cabinet. The cabinet can hide all unsightly wires as the insides of this article is by no means neat, especially if the step-up transformer was made at home. Use No. 12 rubber covered insulated wire for connecting up purposes.

Commercial Receivers With Eliminators

There are many radio receivers now being shown for the first time that incorporate an A and B battery eliminator. Some are wonderful receivers. The designers of these sets are to be congratulated. Some very ingenious engineering designs (so far as the B battery eliminator is concerned) are used.

What Requirements Should Be Fulfilled by a Good B Battery Eliminator

But the eliminators are not perfect. The DC ripple is still present after filtering. It is not noticeable by those who do not actually want to find it, but nevertheless it is present. The vocal, instrumental and oratorical student will have no difficulty in locating the hum, either on the extreme high or low frequencies. On the so-called middle notes (about 3,000 to 5,000 cycles), it is nearly perfect.

The main difficulty lies in compensating the capacity and the inductance of the line for the purpose of making the filter operate perfectly all the time, regardless of what happens to the line. There are a few manufacturers who have introduced such a method in the receiver, but the compensator does not seem to compensate somehow or other.

What would then constitute a perfect B battery eliminator?

A perfect B battery eliminator should have the following aspects:

- (1) No parts to be replaced.
- (2) No chemical cells employed. Chemical cells require attention, in that water and solution have to be added from time to time. They also wear out.
- (3) Very few of the present day eliminators, in fact I know of only two such instruments, are passed by the Underwriters' Laboratory. In order that your fire insurance policy shall be covered it is absolutely necessary either to get a certificate from the Underwriters' Laboratory or that there be some mark of their approval on the eliminator. Unless the eliminator is marked, "Approved by the Underwriters' Laboratory," a certificate of inspection should be obtained from the local inspection department of the Underwriters. The fire insurance company places a clause in the policy which covers all radio apparatus, provided a lightning arrestor is installed. Unless the current is generated by the insured, this clause covers all radio apparatus. The eliminator is not covered, according to the Fire Underwriters, unless specially so. I do not think that many users have given

this much notice, as I never have heard anyone ask, when purchasing a B battery eliminator, or any electrical device, if it was passed by the Fire Underwriters, or to say, "Wait till I consult my insurance company."

(4) A vacuum tube rectifier shall be incorporated in the eliminator. This tube should have no filament and emit no light or heat. By eliminating the filament a long tube life is obtained, approximately 3,000 hours.

(5) There should be some sort of a compensating device so that the filtering action will be perfect all the time.

(6) This compensating device should be automatic in operation. In last week's article it seemed as if I meant that the device should be controlled by hand, but that is not the case. One that has to be adjusted is almost as bad as none at all. You would have to keep adjusting it unless you own the house you live in and know that nobody is fiddling with the line.

(7) The eliminator if separate should weigh no more than five pounds. This allowance is made on account of the large physical windings of the step-up transformer.

(8) The voltage delivered should not fluctuate. If it does, the fluctuation should be within 1/10 of 1% of the rated output.

(9) The eliminator tubes should be properly fused, so that no injury may be done to the vacuum tubes in the set or to the house line.

(10) If the eliminator is placed within the set, it should be properly insulated to prevent accidental contact with the rest of the receiver.

The Hum

R4, the 5,000-ohm resistance unit, is connected in series with R3.

There might be some question in the minds as to the AC hum discussion. We really do not have an AC hum that is heard in the receiver, if the tube is rectifying properly. What we have is a DC ripple. Rectified AC is in reality pulsating DC. If a photograph were taken the pulsating DC would look like the big teeth of a saw. It is because of this irregularity that the filter system is employed. If we rectify AC and properly filter it, then it will be on a par with the DC which is obtained from a storage battery. Therefore when the filter system is destroyed, we hear the pulsating DC in the receiver and not the AC hum. The DC note is as annoying and is on the same basis as the raw AC. The AC hum is often referred to as being the real failure of eliminators, due to this peculiar action which is all right, as the effect is the same in both cases, except that one has a negative and positive alteration (AC) and the other one (DC) only has a steady positive
(Concluded on next page)

A 1-Control Regenerative Set

By Percy Warren

WE have had a great many 2-control, 1-tube receivers, but very few 1-tube, 1-control receivers. Fig. 1 shows the electrical wiring diagram of a 1-tube, 1-control regenerative receiver, good for volume on distant signals as well as on local reception.



PERCY WARREN

The plate and the grid we coupled by means of the coils L2 and L3. This receiver will squeal like the devil if the coils are not constructed and tuned with care.

The only control is the variable condenser, shunted across the secondary of L2.

The cost of this set is very small. Most folk will have all the apparatus at home. The only expensive article that will have to be purchased will be the condenser.

How to Wind the Coil

The coil is wound on one form, No. 22 DCC wire being used. A form 4" in diameter and 6" long will accommodate the windings. One-half inch from either edge anchor the beginning the wire and wind 10 turns. Anchor the end in the tubing, where a small hole should be punched. Leave $\frac{1}{4}$ " and begin winding the secondary L2. Anchor the begin-

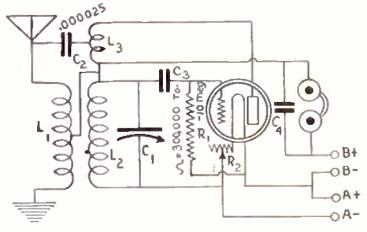


FIG. 1 showing the electrical wiring diagram of the receiver, described in the text.

ning of this winding in a small hole in the form. Wind 45 turns. Anchor the end. Leave $\frac{1}{4}$ ". Wind 35 turns (L3) and anchor. The primary coil L1 is tapped at the 5th turn from the end. The plate coil L3 is tapped at the 18th turn from the end (B plus side). If you wish to use a $3\frac{1}{2}$ " form, the following number of turns should be used. L1 has 12 turns and tapped at the 7th turn. L2 has 49 turns. L3 has 40 turns, tapped at the 21st turn. If you wish to use the 3" form, the following number of turns should be wound: L1 has 15 turns, tapped at the 8th turn. L2 has 56 turns. L3 has 50 turns and is tapped at the 26th turn. Number 24 DCC wire may be used without changing the number of turns.

Don't use any dope on the coils.

How to Place the Parts

Use a 7 x 10" panel, with a cabinet to fit. The baseboard should be 6" long and 4" wide. Three and one-half inches from both edges of the panel and $3\frac{1}{2}$ "

from the top and bottom drill a $3/16$ " hole. This is for the shaft of the variable condenser. Two inches from the left-hand edge and 2" from the bottom drill a $15/32$ " hole for the shaft of the rheostat, R2. R1, the variable grid leak, may be put on the outside of the panel or in the set proper. If you desire to place the leak on the panel it should be at the other end of the panel. This is 2" from the right-hand edge and 2" from bottom. The socket should be placed near the variable grid leak, and in case you place this one on the panel, the grid post of the socket should be placed near thereto. This means that the coil will have to be placed in the back of the baseboard, or about 1" from the edge of board. Directly in back of this coil, place the terminal strip. The grid condenser is placed on the grid binding post of the socket. C2, the special antenna capacity coupler should be placed near the antenna post on the terminal strip. C4, the by-pass condenser, should be placed near the B plus post on terminal strip.

How to Wire the Set

The beginning of L1 goes to one terminal of C2 and to the antenna post on the terminal strip. The end of L1 goes to the ground post. The left-off terminal goes to the tapped portion of L3. The beginning of L2 goes to the rotary plates of C1 and to the arm of the rheostat, which is also connected to the A minus post on the terminal strip. The end of L2 goes to the tapped portion of L1. It also goes to the end of L3, to the stator plates of C1 and to one terminal of C3. The other terminal of C3 goes to the grid post of the socket, and to one terminal of the grid leak. The left off terminal of R1 goes to the F plus side of the socket and to the A plus post on the terminal of the strip. This A plus post connects to the B minus post. The end of L3 winding goes to one phone binding post, in which one terminal of the phones is connected to. The other terminal is connected to the B plus post. The beginning of the L3 winding goes to the plate post on the socket. The resistance wire of the rheostat, R2, goes to the F minus post on the socket. The by-pass condenser C4 is connected across the phones.

Tuning the Set

There should be no difficulty in the operation of this receiver. As soon as the set is completely wired up, the phones inserted, the A and B batteries hooked up, the antenna and the ground attached, signals should be heard. If it is found that the signals are broad, reverse the leads of the secondary winding. If the oscillations are beyond control, reduce the number of turns on the plate coil. Also reverse the leads of this coil. If the signals are not loud, reverse the A battery leads. Use a UV201A tube, with 45 volts on the plate. Take out the by-pass condenser. Decrease the amount of resistance in the grid leak. I found that about 6 megohms was just right, but all tubes require different amounts of resistance in the grid circuit for successful operation. Try placing the grid leak across the condenser, for obtaining clearer reception. If you find that the set still oscillates too much, disconnect the lead from the end of L2 to the end of L3. Use a very short antenna (about 65 feet for best results). The rheostat will never have to be adjusted at all. Tuning is done with the condenser dial. If body capacity prevails, reverse the leads of the condenser, or ground the shaft of the condenser. Use No. 14 rubber covered wire for connecting up the set.

Various Uses for the "S" Tube

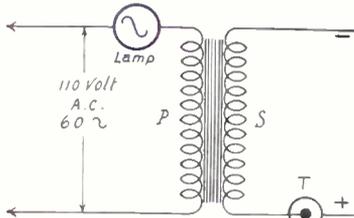


FIG. 3, showing how to hookup the "S" tube for charging purposes. T is the S tube.

(Concluded from preceding page)

flow. The other half of the cycle is not recited with this tube.

Other Uses of the S Tube

Those who have a storage B battery may use the S tube to a great advantage for charging purposes. In Fig. 1, we have the electrical diagram of the wiring of such a charger. Nothing in this device should be attempted to be made at home. The time involved in making the step-up transformer is too great. The operations are tedious. The cost is small, but the above two disadvantages outweigh the cost factor. This transformer should be able to deliver a voltage of from 450 to 11,000 AC. The current-carrying capacity should be about from $1/5$ to $1/2$ amperes.

The charging current is regulated by the lamp, which is connected in series with the primary side of the line. A resistance, which is equal in value to that of the lamp, may be used instead of the lamp. The lamp should be of the carbon or the tungsten type. No other should be employed. The rate of charging the B battery is stated on the cover of the battery by the manufacturer. The following table shows how, with different sizes of lamps, the charging

rate may be increased or decreased. The results given are within 10% correct:

Watts in Lamp	Charging Rate
100	.046 amperes
150	.068 amperes
200	.89 amperes
250	.995 amperes

In all these cases 550 volts secondary output were used on the S tube. The batteries that were charged had a rated output of from 20 to 100 volts. If you desire to charge a battery with a higher voltage insert a parallel lamp of a greater number of watts rating. For obtaining an intermediate number of amperes also place lamps in parallel, viz., 100-watt lamp in parallel with a 25-watt lamp gives you a charging rate of approximately .056 amperes. If you wish to charge a battery the rated amperage being .026, insert a 100-watt lamp in series with the original 100-watt lamp. It should take about 12 hours to charge a B battery. You cannot use this type of a circuit (in which the S tube is incorporated), to charge an A battery because the S tube delivers too small a current output.

There is a great deal of experimenting to be done in the B battery eliminator field. The road is tough. The telephone companies, who have had some of the greatest telephone and electrical engineers in the world working on this principle have not succeeded in finding a perfect eliminator. They use this current for the same purpose that the radio receiver uses it, that is, to supply the plates of the amplifier tubes. If there is one place where the current has to be constant it is here, as the least fluctuation in the line current will cause an annoying drone at the receiving end. They have eliminators but when they require perfect reception, as for line work, the storage type of battery is used.

Using the Secondary as a Loop

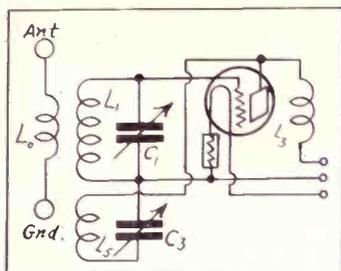


FIG. 1, the wiring diagram of the circuit that uses the secondary as a loop.

By J. E. Anderson
Consulting Engineer

MANY modern sensitive receivers, such as The Diamond of the Air, multitube radio-frequency sets, Super-Heterodynes, and some reflexes operate satisfactorily on a loop for local and even distant stations. But a loop is often inconvenient to use on account of the large space it requires if it is to be comparable to an outdoor antenna and capable of being turned through 360 degrees. For this reason it may be desirable to use a very small loop, one that may be built into the cabinet of the receiver. But such a small loop is not capable of picking up sufficient energy from distant stations to operate satisfactorily any except the most sensitive receivers. It will, however, work with entire satisfaction for local stations for the types of receivers enumerated above. Such a loop may simply be a low-loss tuning coil having a diameter as small as five inches; but, of course, it should be as large as the amount of available space in the cabinet will permit.



J. E. ANDERSON

If such a small loop is used a time may come when it may be desirable to employ an outside aerial in order that extremely distant stations may be received. The usual plug and jack arrangement for interchanging a loop and antenna is not particularly adaptable to the built-in loop, and it is not very desirable at any time if a simpler means may be found. The difficulty may be solved by a simple arrangement which the writer has designed for use in his 1926 model Super-Heterodyne. A description of this arrangement follows.

Divided Circuit Used

Fig. 1 shows the beginning of this Super-Heterodyne, or of any other radio-frequency circuit having tuned transformers. Regeneration is employed in the first tube, and due to the peculiar requirements of the loop, the Weagant method of obtaining it has been selected.

L1 is the tuning coil which is used as a loop. It is mounted with its axis horizontal in such a manner that it may be turned through an angle of 360 degrees. The fixed tickler L3 is mounted concentrically with the loop with rigid supports so that it turns with the loop. Regeneration is then varied by means of the condenser C3. Thus the regeneration is independent of the orientation of the loop coil.

Now if the coil is to be used as a loop for the reception of local stations nothing is connected to the terminals "Ant" and

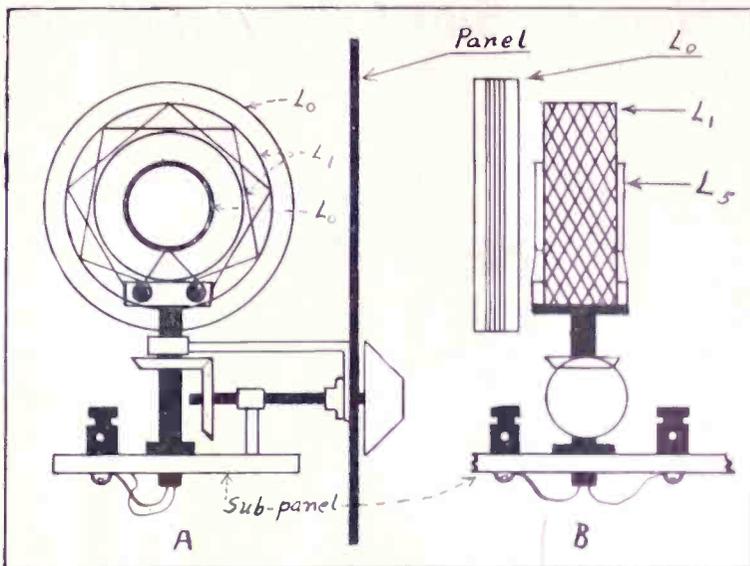


FIG. 2, the side and back views (A and B) of the coil as mounted.

"Gnd" of the coil L0. But if distant stations are to be received the antenna and ground leads are connected as marked. Now the coil L0 consists of a few turns of wire mounted in a fixed position on the wall of the cabinet or near the secondary coil L1. These turns of course constitute the primary, and any desired coupling between it and the secondary may be obtained by simply turning the loop. If very close coupling is desired the primary turns may be of larger diameter than the loop so that the loop may partly turn inside the primary, in which case the primary should be mounted away from the wall of the cabinet.

Since the loop must be capable of turning it will be necessary to use flexible

leads to both L1 and L3, or an arrangement may easily be devised in which stiff phosphor bronze springs complete the connections in wiping contacts. It is preferable, however, to use soldered pigtail connections, at least for the tuned circuit.

The rotation of the loop is controlled with a knob mounted on the panel. A long coupling rod connects the dial with a 45 degree bevelled gear which engages with a similar gear mounted on the loop shaft. The details of the mounting of the coils and the control gear are shown in Fig. 2, A and B. As much as possible of the supports, including the control gear, should be made of hard rubber or other low-loss insulating material.

THE NEUTRALIZER

(Concluded from page 7)

28 gauge phosphor bronze (Fig. 1). Use a scriber for this purpose or a sharp nail. A pencil will not suffice as the lines drawn are very hard to distinguish.

Before cutting this little square from the sheet of metal drill (Fig. 2) three holes in the positions as shown in Fig. 10. That is one near the bottom in the center, and two near the top, in each corner. The drilling should be done with a No. 27 drill. Now cut the 1" square of bronze from the big piece, using an old pair of shears, or a pair of metal snips if you happen to have them. (Fig. 3).

Saw a piece of Bakelite $1\frac{1}{4} \times 2\frac{1}{4} \times \frac{1}{4}$ " (Fig. 4).

Secure a piece of brass ribbon $\frac{1}{2}$ " wide and cut off a strip one and three-quarters wide. (Fig. 5).

In the center of this strip drill a $\frac{1}{4}$ " hole and near the ends drill two more holes with a No. 27 drill. (Fig. 6). This is shown also in Fig. 11.

After this has been done, place the brass strip on the piece of bakelite, and hold it down tight with two little clamps. Now place the whole thing in a vise. With the No. 27 drill make three holes through the ones previously drilled in the brass, and right on through the Bakelite. Do not drill a $\frac{1}{4}$ " hole through the Bakelite, just through the brass strip.

Next take a 6-32 tap and pass it through the holes drilled in the Bakelite (Fig. 9), to receive the machine screws, which will be described later.

Now place the small square of phosphor

bronze over the Bakelite with the center top hole over the center one in the Bakelite piece, and which has also been tapped with the 6-32 tap.

The two lower holes in this little square are also drilled through the Bakelite strip, and these two are to be used for holding one side of the bronze fast to the Bakelite. The machine screws are placed right through and cut off flush on the other side.

The brass strip is placed as shown in Fig. 11, just under the little square.

Now the large head 6-32 machine screw. If you cannot get a large head machine screw, solder

a washer just under the head of the screw.



HERBERT E. HAYDEN

Set Baby Can Build Brings in Great DX

RESULTS EDITOR:

I have just finished The Set A Baby Can Build, as described by Herbert E. Hayden in the August 29 issue. I added a two-step amplifier (3 tubes in all) and picked up stations WGY, WBZ, WLW and KDKA on the speaker. On the phones I picked up stations WCX, WWJ, KYW, CNRA, WEBH, WQJ, WORD, WOO, WEAF, WTAS and WSAI. I wish to thank Mr. Hayden for this circuit.—Willie Martin, 734 Clay Ave., Norfolk, Va.

Wiring the 1-Control Reflex

Oscillations Are Squelched by Inductances

LIST OF PARTS

Two straight-line frequency condensers, .0005 mfd.
 Two variocouplers.
 Four Amperites.
 Two audio-frequency transformers, 3½-to-1 ratio.
 Four sockets.
 One fixed crystal detector.
 Two .005 fixed condensers.
 One vernier dial.
 Two automatic filament-control jacks.
 One 7x21" panel.
 One 7x20" baseboard.
 Six binding posts.

the larger baseboard, because with the smaller size there would be no room left. The set can then be wired as shown in our wiring diagram.

A front view of the set would show only one knob and the turning of this knob will not only bring in the locals, but the DX (distant) stations as well, without any other control whatsoever. The phone jack for head-phones is at the left, while the jack for loud speaker is at the right. When through using the set, the listener pulls out the plug, which automatically disconnects all the vacuum tubes. There is no switch on this receiver.

Operation of the Set

This is a world in which you cannot hope to get anything for nothing. By this I mean that when you have reduced the usual six or seven controls in your set to a single one and still expect to get exactly the same results, if not better, than with the old controls, you must of necessity compensate for this. **And it is in the full compensation of this set that its success lies.** I recommend to the builder of this set that he try the carborundum detector as well as several others. As a matter of fact, it becomes necessary to have several fixed detectors, because it will be found that not all of them are suitable for this set. Not every detector will work, and I have found that the detector that is too sensitive will make the set howl and squeal, which is exactly what it is not supposed to do, and does not do if the detector is well chosen.

You will understand, of course, that the B battery minus goes to plus A. This saves one binding post in the set when you connect it.

Not One Rheostat

As will be seen, no rheostats are used in the set. These are supplanted by automatic resistances or Amperites, which work very nicely. If the set is completely wired as per instructions, and if the correct materials have been used, we are now ready to tune the set.

It will be found that on locals the set, if the connections are right, will work immediately, although it may squeal and howl. It now becomes necessary to adjust the tickler controls. **The whole secret of the set lies right in these tickler controls.** As I said before, in a world in which you cannot hope to get anything for nothing, it will be found that a little work must be put in to adjust these two coils in proper relation.

How to Tune In

Proceed as follows:

Tune in the lowest possible station, say around 210 or 220 meters. Adjust your tickler controls in such a way that the station comes in loudly without squealing.

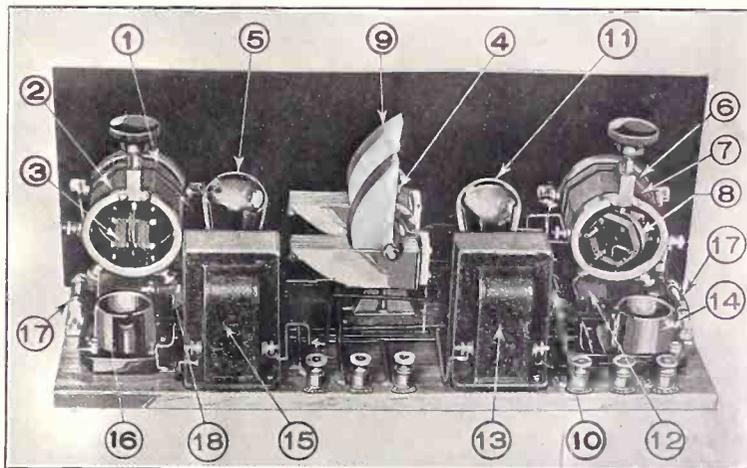


FIG. 2, rear view of the receiver. The numerals identify the parts correspond to those in Fig. 1.

By turning both tickler controls very slowly you will find a point which is just below the oscillation. That is the correct point. It will be found that, as you turn the condenser tuning control, the stations will snap in with a startling loudness without being accompanied by any squealing or howling throughout the entire range of 200 to 545 meters. If there should be howling or squealing at any of the higher stations, the ticklers are not adjusted correctly. It may be necessary to turn one tickler all the way around and try working it back the other way. Sounds should come in not only loudly, but without distortion of any kind. **If distortion exists, the ticklers are incorrectly adjusted.**

It will take you a little while to become familiar with this adjustment, but once you "get the hang of it," you will be astonished at the power and selectivity of the set.

If, despite everything, the set still howls, then the trouble lies in the coupling between the two condensers. In other words, the condensers do not balance the inductances. In that case the condenser sleeve, as shown in Fig. 5, should be loosened and one of the rotors of one of the condensers advanced or retarded ¼", more or less. This can best be determined by experiment. In the set which we see illustrated here it was found that for best operation the outside rotor was almost ¼" out of step with its mate. With a little experimenting you can find the correct point, after which the sleeve may be tightened. This should stop all squealing, and the set may now be said to be perfectly balanced.

There may be other reasons for squealing and before attempting to adjust the condensers, please bear the following important considerations in mind: No two tubes are alike. It will be found necessary in most cases to switch around the four tubes; this often remedies the trouble. Also, as stated before, the fixed crystal detector may be at fault. A detector that is too sensitive causes howls. You will also notice that as you insert a new detector into its holding brackets, you have to retune the set slightly.

The detector may work better if reversed. Try this and you will find that when it is operated in one position, reception is louder.

Of what good is the crystal detector?

It gives an amplification factor of about 10 to 20. This may not be so apparent on locals, but if you short-circuit the detector on distant stations, you will find that the signals are in all cases practically killed. Besides, the detector in the grid circuit makes for great clarity of signals.

Trouble Hints

Another important point is the detector voltage. With the set shown here, the particular voltage for best results was 21. This means that you should use a tapped B battery on the detector side. Forty-five volts on this particular set practically killed all signals, except powerful local stations.

Try reversing aerial and ground. Very often this makes a big difference. If your aerial is 100 feet or longer, it is quite necessary to place a .00025 fixed condenser in series with the antenna.

The set may be said to work normally when, by turning the tuning control, the stations snap in with a loud clucking sound at their full power. **There should be no howl or squeal through the entire broadcast range.** When the set is finally adjusted and works at its best, it may be noticed that during the month it develops a squeal. This is a sure sign that the batteries are running down. With a new battery the ticklers may need a slight retuning. If new tubes are used or tubes are switched around, retuning of the ticklers is, of course, necessary.

This particular set, on a 60-foot aerial, brings in KDKA at a dial setting of 50, and the volume is tremendous—stronger than some of the locals. This in midsummer, with lots of static prevailing and transmitting conditions notoriously poor. The locals, of course, come in with tremendous volume over the entire range. Distant stations that have been heard on a single evening are given in the list. This should by no means be considered a record, because receiving conditions in New York are poor. Besides, the log represents that of a sultry August night, with a great deal of static which made it impossible to get the calls of many more stations that otherwise could have been logged.

The receiver should be of particular
 (Concluded on page 30)

Radio University

A QUESTION and Answer Department conducted by RADIO WORLD for its Readers by its staff of Experts. Address Letters to The Radio University, RADIO WORLD, 1493 Broadway, New York City.

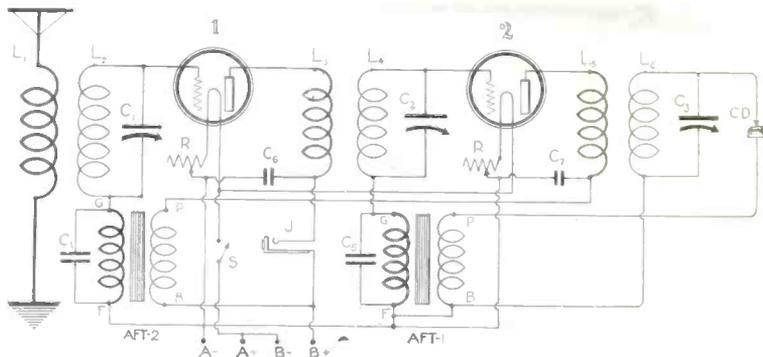


FIG. 202, a 2-tube Inverse Duplex. L1, the primary, has 10 turns wound on a 3 1/2" tubing 4" high, with No. 24 DSC wire. There is 1/4" space left and L2, the secondary, has 43 turns. L3 and L5 are the same as L1. L4 and L6 are the same as L2. C1, C2 and C3 are variable condensers having a capacity of .0005 mfd. C6 and C7 are .001 mfd. condensers. C4 and C5 are both .0001 mfd. condensers. The rheostats R have a resistance of 20 ohms. CD is the crystal detector.

A DIAGRAM of 2-tube Grimes Inverse Duplex is requested.—T. Larkins, Swithimpson, N. D.
See Fig. 202.

CAN I use a 3-circuit tuning coil in The Diamond? The primary is wound with Litz wire and has 10 turns, the secondary is wound with No. 22 SCC wire and has 34 turns. The tickler has 30 turns, and is wound with Litz wire. (2) Is it vital to use Litz wire rather than No. 22 SCC wire? (3) Can the RFT be wound with No. 22 DCC wire? There are 12 turns on the primary and 45 turns on the secondary.—A. F. Scheibeck, 244 Locust St., Chillicothe, O.

(1) Yes. (2) No; No. 22 DCC or SCC wire is usually used on account of the ease encountered in winding and also soldering connections. Litz has a high resistance at high frequencies. (3) Yes.

I INTEND to build The Diamond of The Air and would like to use .0003 mfd. condensers in the set. Would they give satisfactory results and range with the proper coils? If so, what would be the proper number of turns for the coils? (2) Can basket-weave coils be used with equal results? (3) Can a tuned plate coil be used with a .0003 or .00035 condenser in

place of the regenerative tickler? If so what would be the proper type coil to use?—F. L. Mills, 8121 Korman Ave., Cleveland, O.

(1) Yes. The primary of the RFT coil may be wound on a 3 1/2" diameter tubing and contain 15 turns. The secondary contains 57 turns and is wound on the same tubing, using No. 22 DCC wire. The primary and the secondary intermediate coil is the same as above. The tickler is wound on a 2 1/2" diameter tubing 2" high and contains 40 turns, wound with No. 24 SCC wire. (2) Yes. (3) A 40-turn coil wound on a 3 1/2" tubing, using No. 22 DCC wire.

I BUILT The Diamond and get very broad tuning. Is there any possible remedy?—J. Uher, 413 East 84th St., N. Y. City.

Reverse the tickler leads. Add more turns to the tickler coil. Reverse the secondary of the RFT. Use a short antenna. Check up your wiring. There is a mistake in it, otherwise the set would be selective.

WOULD a straight-line frequency .0005 mfd. condenser be better to use in H. E. Wright's Transcontinental 2-tube set that was described in Jan. 31 issue of RADIO WORLD than three of the other types? Could I separate the stations on the low

wavelengths with the kind mentioned above?—George Steidle, Jr., 941 Centre St., Mauch Chunk, Pa.

The efficiency depends on the make of condenser, and SLF has to do only with separating low wave stations easily. You may use the SLC condensers with SLF dials, with nearly same results.

WITH REFERENCE to the Very Loud 1-Tube DX Set published in the Sept. issue of RADIO WORLD. (1) I have one 11-plate condenser on hand and would very much like to use it in building this circuit. Kindly advise the number of turns of wire necessary to enable me to use this condenser. I have number 24 DCC wire on hand. (2) Will a C12 tube be O.K.?—H. Reuss, Philadelphia, Pa.
(1) There should be 75 turns wound on the same sized tubing as prescribed in the text of that issue, for shunting the secondary of L2. There are 65 turns wound for L3. (2) Yes.

I AM building The Diamond. (1) I would like to know if an Uncle Sam 3-circuit low-loss coil and an Ambassador antennae coil would work well? (2) Will a 6-ohm rheostat run three 201A tubes?—Kenneth Shipton, 3220 Emerald St., Philadelphia, Pa.

(1) Yes. (2) Yes, but the separate rheostats for the RF and detector should be used. The 6-ohm would do for the two or three AF.

WE HAVE an Autoplex receiver, to which we have added two stages of audio frequency amplification. (1) Would it be feasible to place a step of radio-frequency amplification ahead of this detector?—Donald P. Finch, 58 Firingston St., New Haven, Conn.

It is not advisable to add radio-frequency ahead of a receiver of this particular type, which is a super-regenerative.

I HAVE built The Diamond with the optional loop, but can get no results when I plug in the loop. The set works excellently otherwise.—W. Nimblett, 22 West 135th St., N. Y. City.

There is an open circuit in your jack or a short circuit in the loop. Look at the two interior jack springs and see if they are making contact with the upper one. A better way is put a pair of phones in series with a 1 1/2-volt dry cell contacts and test for a complete circuit.

IN BUILDING The Diamond I would like to use three rheostats, one for the RF tube, one for the detector tube, and one for the two AF tubes. Would it be advisable to use ballast resistances? I am using UV201A tubes.—E. J. Bower, Sioux Lookout, Ontario, Canada.

The rheostats for the radio-frequency and the detector tubes should have a resistance of 6 ohms, while a 3/4-amp. ballast resistor will do for three AF tubes, or a 1/2-amp. type for two AF tubes.

WHY ARE some coils wound with single, double cotton or silk covered wire? (2) What advantage has the single cotton covered over double cotton covered wire? (3) Is silk better than cotton? (4) Can stranded wire be used with advantage? (5) Is No. 18 stranded rubber covered wire good for loop winding? (6) What is the best type of wire to use in The Diamond, double cotton covered or silk covered wire? (7) I have a Ford Mica 3 1/2 and 5 to 1 AFT. Can they be used in The Diamond?—P. L. Lengthen, Randon, Cal.

(1) So that there will be more or less inductance present in the coil and, in some cases, e.g., DCC wire, less distributed capacity. When using single cotton

Join RADIO WORLD'S University Club

and we will enter your name on our subscription and University lists by special number. Put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it in your queries and the questions will be answered the same days as received.

And Get Free Question and Answer Service for the Coming 52 Weeks.

RADIO WORLD, 1493 Broadway, New York City:

Enclosed find \$6.00 for RADIO WORLD for one year (52 Nos.) and also consider this an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year, and a number indicating my membership.

Name
Street
City and State

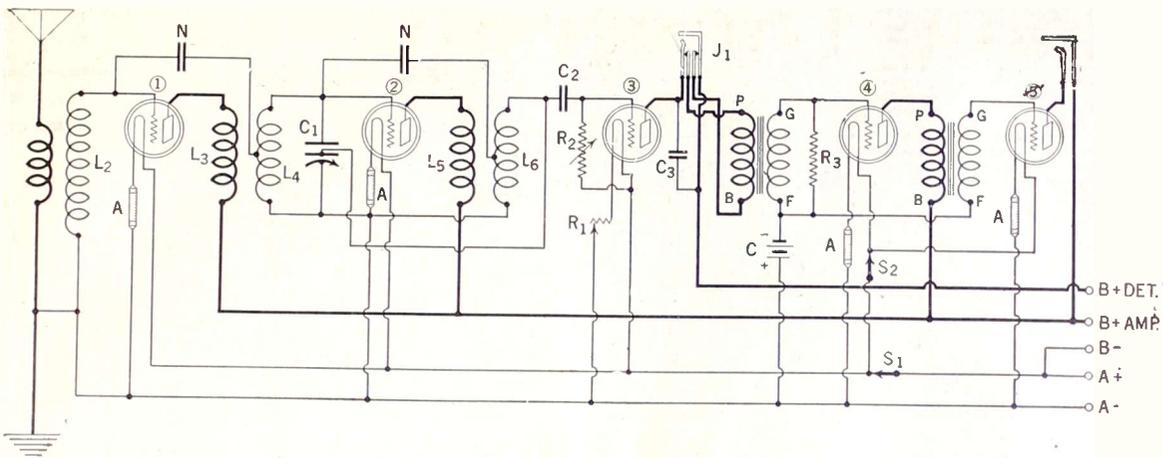


FIG. 203, showing a 5-Tube Neurodyne, using only one control. The coil constants are: LL2 is a standard commercial (fixed) RFT. L3L4 is wound on a form 3" in diameter and 4" long. There are 12 turns in the primary. Use No. 22 DCC wire, leave 1/8" and wind 12 turns; make a loop and wind 33 more turns, making a total of 45 turns on the secondary. The 12th turn tap is for connecting the neutralization condenser. L5L6 is wound on the same kind of tubing and same number of turns as L3L4. The double condenser (C1) has two separate stators and a common rotor. C2 is a .00025 mfd. grid condenser. R2 is a variable grid leak. N are the neutralizing (variable) condensers. R1 is a 6-ohm rheostat. R3 is a 100,000-ohm resistor. J1 is a double circuit jack. The jack is a single circuit jack. A are the amperites (type to be determined by kind of tubes used).

covered wire, there are fewer turns of wire needed than with DCC. (3) No. (4) Yes. (5) Yes. (6) Double cotton covered wire is considered the best. Usually the kind of wire makes little practical difference. (7) Yes.

PLEASE INSERT a diagram of a 1-dial 5-tube Neurodyne receiver. — T. D. Blankins, Longston, Tex.
See Fig. 203.

I WOULD like to use the UV199 tubes in the RFT and the AFT of The Diamond while a Sodian tube is used in the detector socket. Is this a good combination? (2) Can the loop be successfully used on this set? (3) I cannot make my set tune in step. One dial reads 45 for a certain station while the other one reads 65.—F. D. Love, Williamson County, Tex.

(1) This is a good combination. (2) Yes. (3) If you mean the condenser dials, remove turns from the coil whose condenser gives the higher reading.

WILL YOU please give me the winding of the RFT to work in connection with the Globe Low Loss Tuner?—Frank Bertoldo, Box 53, Coalgate, Okla.

There are 10 turns on the primary of a 3 1/2" tubing using No. 22 DCC wire. The secondary consists of 45 turns, employing the same wire, and immediately adjoins the primary.

COULD I use the UV199 tubes in The Diamond? (2) What is the resistance of the rheostat?—C. B. Arendt, 409 9th St., Valley Junction, Ia.

(1) Yes. (2) 50-ohms, when using a 6-volt storage A battery, 20 ohms when using the 4 1/2-volt A battery.

DOES television apparatus attach directly to the output of your receiver? (2) Will there be any drawbacks such as static and will static bother the pictures and in what way will it manifest itself? (3) How bright should the light in a rectifying bulb used in charging batteries be? Mine gets very hot while operating. Is this a sign that the transformer is not just right?—William R. Haaugsted, 606 9th St., Nevada, Ia.

(1) No, a special receiver is required.

There are no general data obtainable on this subject. It will be discussed a great deal at radio engineering societies. Keep in touch with these societies, as well as the Bureau of Standards Circulars. Little is generally known on the subject. (2) Static is one of the drawbacks. It distorts the picture. (3) The filament should give a bright light. It matters nothing if the tube gets hot.

THE DIAGRAM of the 3-tube Marconi Broadcast Receiver is requested.—S. Sanford, Long Island City, N. Y.
See Fig. 204.

WHAT SIZE tubing, wire and how many turns are required for a 3-circuit tuner, when a .0003 mfd. condenser is shunted across the secondary of this coil?

(2) Will this coil tune to the broadcast wavelengths?—C. V. R. Dehart, 348 West Side Ave., Haustown, Md.

There are 15 turns wound on a 3 1/2" tubing, using No. 22 DCC wire for the primary. The secondary is wound separately, next to this coil and contains 57 turns. (2) This coil tunes to all the wavelengths from 200 to 555 meters.

I BUILT the carborundum crystal set as was described by Lewis Winner in the July 25 issue of RADIO WORLD and find it is a wonder. I get clear reception on the speaker. However, it will not work when I connect the batteries in the circuit.—G. Claybrooke, 616 E 25th St., Los Angeles, Cal.

There must be a short circuit in the potentiometer or you have reversed the polarities of the A batteries.

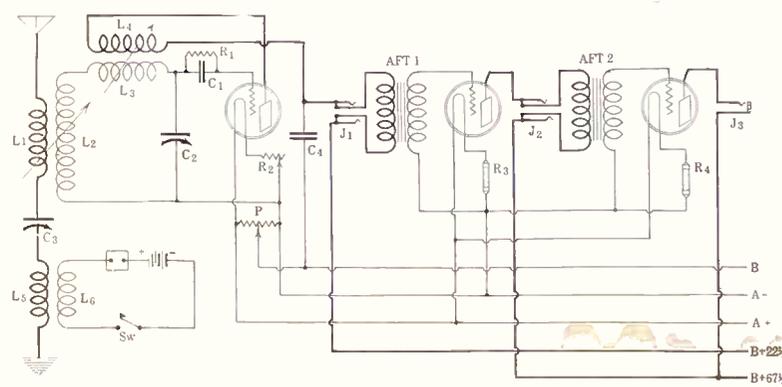


FIG. 204, showing the 3-tube Marconi Broadcast Receiver. L1 is wound on a 3" diameter tubing, 3" in height and has 9 turns. L2 (the rotor) is wound on a 2" form, 2 1/4" high, and has 36 turns. Use No. 22 DCC wire. L3 is wound on the same type of form as L1, except that it has 22 turns. L4 is wound on a 2" form, 2 1/4" in height and has 45 turns. This is the rotor. L1L2 is placed at right angles to L3L4 C3 is a .001 mfd. variable condenser, to be used in tuning in the shorter waves, in case the receiver does not respond so well. C2 is a .0005 mfd. variable condenser. R1 is a 2 megohm grid leak. C1 is a .00025 mfd. grid condenser. R2 is a 6-ohm rheostat. C4 is a .001 mfd. by-pass condenser. J1 and J2 are both double circuit jacks. J1 is a single circuit jack. AFT 1 and 2 are of the low ratio type. R3 and R4 are special ballast resistors, the resistance of which is determined by the tube. P is a 400-ohm potentiometer. The special test buzzer is not required and therefore no data will be given.

THE KEY TO THE AIR

KEY

Abbreviations: EST, Eastern Standard Time; CST, Central Standard Time; MST, Mountain Standard Time; PST, Pacific Standard Time; DST, Daylight Saving Time. How to tune in a desired distant station at just the right time—Choose your station from the list published herewith. See what time division the station is under (EST, CST, etc.); then consult the table below. Add to or subtract, as directed from the time as given on the PROGRAM. The result will be the same BY YOUR CLOCK that you should tune in, unless daylight-saving time intervenes, as explained below.—The table:

Table with columns: If you are in, And want a station in, Subtract, Add. Rows include EST, CST, MST, PST and DST for various time zones.

FRIDAY, SEPTEMBER 25

WAAM, Newark, N. J., 263 (ESTDS)—11 AM to 12:30 PM; 10:30. WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12:30 to 1:05 PM; 7:30 to 11:05 PM. WAMD, Minneapolis, Minn., 243.8 (CST)—12 to 1 PM; 10 to 12. WBBM, Chicago, Ill., 226 (CST)—8 to 10 PM. WBBR, New York City, 272.6 (ESTDS)—8 PM to 10. WBOQ, Richmond Hill, N. Y., 236 (ESTDS)—7:30 PM to 11. WBZ, Springfield, Mass., 333.1 (ESTDS)—6 PM to 11. WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 to 4; 5:30 to 10. WCAE, Pittsburgh, Pa., 461.3 (ESTDS)—12:30 to 1:30 PM; 4:30 to 5:30; 6:30 to 11. WDAF, Kansas City, Mo., 365.6 (CST)—3:30 to 7 PM; 8 to 10; 11:45 to 1 AM. WFAF, New York City, 492 (ESTDS)—6:45 AM to 7:45; 11 to 12; 4 PM to 5; 6 to 12. WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 8 to 11. WEOA, Ohio State University, 299.9 (EST)—8 PM to 10. WEEL, Boston, Mass., 476 (ESTDS)—6:45 AM to 7:45; 2 PM to 3:15; 5:30 to 10. WEMC, Berrien Springs, Mich., 286 (CST)—9 PM to 11. WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30. WFBH, New York City, 272.6 (ESTDS)—2 PM to 6. WGBS, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 4; 6 to 7:30. WGCP, New York City, 252 (ESTDS)—2:30 PM to 5:15; 8 to 11. WGES, Chicago, Ill., 250 (CSTDS)—7 to 9 PM; 11 to 1 AM. WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30. WGR, Buffalo, N. Y., 319 (ESTDS)—12 M to 12:45 PM; 7:30 to 11. WGY, Schenectady, N. Y., 379.5 (EST)—1 PM to 2; 5:30 to 10:30. WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8:30 to 10. WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9. WHN, New York City, 360 (ESTDS)—12:30 PM to 1; 2:15 to 5; 7 to 11; 12 to 12:30 AM. WHO, Des Moines, Iowa, 526 (CST)—7 PM to 9; 11 to 12; 12:30 to 1:30; 4:30 to 5:30; 6:30 to 9:30 PM. WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 4 to 8:30; 8:45 to 10:05; 10:30 to 1 AM. WIP, Philadelphia, Pa., 508.2 (ESTDS)—6:45 AM to 7:15; 10 to 11; 1 PM to 2; 3 to 5; 6 to 7. WJY, New York City, 405 (ESTDS)—7:30 PM to 11:30. WJZ, New York City, 455 (ESTDS)—10 AM to 11; 1 PM to 2; 4 to 6; 7 to 10:30. WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 12:30; 2 to 3; 4:30 to 6; 7:30 to 1 AM. WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15; 1:30 PM to 2:30. WMCA, New York City, 341 (ESTDS)—11 AM to 12 M; 6:30 PM to 12. WNYC, New York City, 526 (ESTDS)—3:45 PM to 4:45; 6:20 to 11. WOAW, Omaha, Neb., 526 (CST)—12:30 PM to 1; 5:45 to 7:10; 9 to 11. WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 5:45 to 7. WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7. WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9. WPG, Atlantic City, N. J., 299.8 (ESTDS)—7 PM to 8:30; 10 to 12. WOJ, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 12 M. WBC, Washington, D. C., 469 (EST)—9 AM to 10; 12 PM to 1; 5 to 7. WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 11. WRNY, New York City, 288.5 (ESTDS)—11:59 to 2 PM; 7:59 to 9:45. WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12. WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 10; 12 PM to 1 AM.

WWJ, Detroit, Mich., 352.7 (EST)—6 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30; 3 to 4; 7 to 7; 8 to 10. KDKA, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:30 PM; 1:30 to 3:30; 3:30 to 11. KPAB, State College of Wash., 348.6 (PST)—7:30 PM to 9. KFDY, Brookings, S. D., 273 (MST)—8 PM to 9. KFI, Los Angeles, Cal., 467 (PST)—5 PM to 10. KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 9:30 to 12. KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10. KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 11. KGO, Oakland, Cal., 361.2 (PST)—11:10 AM to 1 PM; 1:30 to 3; 4 to 7. KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11. KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:30 PM; 5:30 to 11:30. KJR, Seattle, Wash., 484.4 (PST)—10:30 AM to 11:30 AM; 1 PM to 6:30; 8:30 to 11. KKNY, Hollywood, Cal., 357 (PST)—11:30 AM to 12:30 PM; 1 to 2; 4 to 5; 6:30 to 12. KOA, Denver, Col., 322.4 (MST)—11:45 AM to 12:30 PM; 3:30 to 4:15; 6 to 10. KOB, State College of New Mexico, 348.6 (MST)—11:55 AM to 12:30 PM; 7:30 to 8:30; 9:55 to 10:10. KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 8:45; 11 to 12 M. KPO, San Francisco, Cal., 429 (PST)—7:30 AM to 8; 10:30 to 12 M; 1 PM to 2; 4:30 to 11. KSD, St. Louis, Mo., 545.1 (CST)—4 PM to 5. KTHS, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:20 to 10. KYW, Chicago, Ill., 536 (CSTDS)—6:30 AM to 7:30; 10:55 to 1 PM; 2:25 to 3:30; 6:02 to 7:20; 9 to 1:30 AM. CNRA, Moncton, Canada, 313 (EST)—8:30 PM to 10:30. CNRE, Edmonton, Canada, 516.9 (MST)—8:30 PM to 10:30. CNRS, Saskatoon, Canada, 400 (MST)—2:30 PM to 3. CNRT, Toronto, Canada, 357 (EST)—6:30 PM to 11.

SATURDAY, SEPTEMBER 26

WAAM, Newark, N. J., 263 (EST)—7 PM to 11. WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12:30 PM; 1:05 to 12 to 2 AM. WAMD, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12. WBBM, Chicago, Ill., 226 (CST)—8 PM to 1 AM. WBBR, New York City, 272.6 (ESTDS)—8 PM to 9. WBOQ, Richmond Hill, N. Y., 236 (ESTDS)—3:30 PM to 6:30. WBZ, Springfield, Mass., 333.1 (ESTDS)—11 AM to 12:30 PM; 7 to 9. WCAE, Pittsburgh, Pa., 461.3 (ESTDS)—10:45 AM to 12 M; 3 PM to 4; 6:30 to 7:30. WCBD, Zion, Ill., 344.6 (CST)—8 PM to 10. WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12:30 PM; 2:30 to 5; 6 to 10. WFAF, New York City, 492 (ESTDS)—6:45 AM to 7:45; 4 PM to 5; 6 to 12. WEEL, Boston, Mass., 476 (ESTDS)—6:45 AM to 7:45 AM. WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 7 to 8. WEMC, Berrien Springs, Mich., 286 (CST)—11 AM to 12:30 PM; 8:15 to 11. WFAA, Dallas, Texas, 475.9 (CST)—12:30 PM to 1; 6 to 7; 8:30 to 9:30; 11 to 12:30 AM. WFBH, New York City, 272.6 (ESTDS)—2 PM to 7:30; 11:30 to 12:30 AM. WGBS, New York City, 316 (ESTDS)—10 AM to 11; 1:30 PM to 3; 6 to 11. WGCP, New York City, 252 (ESTDS)—2:30 PM to 5:15. WGES, Chicago, Ill., 250 (CSTDS)—7 PM to 9; 11 to 1 AM. WGN, Chicago, Ill., 370 (CST)—9:31 AM to 2:30 PM; 3 to 5:57; 6 to 11:30. WGY, Schenectady, N. Y., 379.5 (EST)—7:30 PM to 10. WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:30 PM; 4 to 5; 6 to 7:30. WHAR, Atlantic City, N. J., 275 (ESTDS)—2 PM to 3; 7:30 to 9. WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9. WHN, New York City, 360 (ESTDS)—2:15 PM to 5; 7:30 to 10. WHO, Des Moines, Iowa, 526 (CST)—11 AM to 12:30 PM; 4 to 8:30; 7:30 to 10. WHT, Chicago, Ill., 400 (CSTDS)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM. WIP, Philadelphia, Pa., 508.2 (ESTDS)—7 AM to 8; 10:30 to 11; 1 PM to 2; 3 to 4; 6 to 11:30. WJY, New York City, 405 (ESTDS)—2:30 PM to 5; 8 to 10:30. WJZ, New York City, 455 (ESTDS)—9 AM to 12:30 PM; 2:30 to 4; 7 to 10. WKRC, Cincinnati, O., 326 (EST)—10 to 12 M. WLW, Cincinnati, O., 422.3 (EST)—9:30 AM to 12:30 PM; 7:30 to 10. WMAK, Lockport, N. Y., 265.5 (EST)—10:25 AM to 12:30 PM. WMCA, New York City, 341 (ESTDS)—3 to 5 PM; 6:30 to 2. WNYC, New York City, 526 (ESTDS)—1 to 3 PM; 7 to 11. WOAW, Omaha, Neb., 526 (CST)—10 AM to 1; 2:15 to 4; 9 to 11. WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 5:45 to 7:10; 9 to 12. WOO, Philadelphia, Pa., 508.2 (ESTDS)—11 AM to 1 PM; 4:40 to 5; 10:55 to 11:02. WOR, Newark, N. J., 405 (ESTDS)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 7:30; 8 to 11.

WOJ, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 3 AM. WPG, Atlantic City, N. J., 299.8 (CST)—7 PM to 12. WRC, Washington, D. C., 469 (EST)—1 PM to 2; 6:45 to 12. WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 12. WRNY, New York City, 288.5 (ESTDS)—11:59 to 2 PM; 7:59 to 9:30; 12 M to 1 AM. WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 3 to 4; 5 to 6; 10:45 to 12. WWJ, Detroit, Mich., 352.7 (EST)—6 AM to 8:30; 9:30 to 10; 11:55 to 1:30 PM; 3 to 4. KDKA, Pittsburgh, Pa., 309 (EST)—10 AM to 12:30 PM; 1:30 to 6:30; 8:45 to 10. KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11. KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 9:30 to 12:30. KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10:30. KFOA, Seattle, Wash., 455 (PST)—Silent. KGO, Oakland, Cal., 361.2 (PST)—11 AM to 12:30 PM; 3:30 to 5:45; 7:30 to 9. KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 6 to 7; 10 to 11. KHJ, Los Angeles, Cal., 405.2 (ESTDS)—7 AM to 7:30; 10 to 1:30 PM; 2:30 to 3:30; 5:30 to 2 AM. KJR, Seattle, Wash., 484.4 (PST)—1 PM to 2:45; 6 to 6:30; 8:30 to 10. KNX, Hollywood, Cal., 337 (PST)—1 PM to 2; 6:30 to 2 AM. KOA, Denver, Colo., 322.4 (MST)—11:30 AM to 1 PM; 7 to 10. KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 9. KPO, San Francisco, Cal., 429 (PST)—8 AM to 12 M; 2 PM to 3; 6 to 10. KSD, St. Louis, Mo., 545.1 (CST)—7 PM to 8:30. KTHS, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:30 to 10:30. KYW, Chicago, Ill., 536 (CSTDS)—11 AM to 12:30 PM; 4 to 5; 7 to 8. CKAC, Montreal, Canada, 411 (EST)—4:30 PM to 5:30. CNRO, Ottawa, Ontario, Canada, 435 (EST)—7:30 PM to 10. PWX, Havana, Cuba, 400 (EST)—8:30 PM to 11:30.

SUNDAY, SEPTEMBER 27

WBBM, Chicago, Ill., 226 (CST)—4 PM to 6; 8 to 10. WBBR, New York City, 272.6 (EST)—10 AM to 12 M; 9 PM to 11. WCCO, St. Paul and Minneapolis, Minn., 416 (CST)—11 AM to 12:30 PM; 4:10 to 5:10; 7:20 to 10. WDAF, Kansas City, Mo., 365.6 (CST)—4 PM to 5:30. WFAF, New York City, 492 (EST)—3 PM to 5; 7:20 to 10:15. WEAR, Cleveland, O., 390 (EST)—3:30 PM to 5; 7 to 8; 9 to 10. WFBH, New York City, 272.6 (EST)—5 PM to 7. WGBS, New York City, 316 (EST)—3:30 PM to 4:30; 8 to 10. WGCP, New York City, 252 (EST)—8 PM to 11. WGES, Chicago, Ill., 250 (CST)—5 PM to 7; 10:30 to 12 M. WGN, Chicago, Ill., 370 (CST)—11 AM to 12:45 PM; 2:30 to 5; 9 to 10. WGR, Buffalo, N. Y., 319.5 (EST)—9:30 AM; 7:15 to 8 PM. WGY, Schenectady, N. Y., 379.5 (EST)—9:30 AM to 12:30 PM; 2:35 to 3:45; 6:30 to 10:30. WHAD, Milwaukee, Wis., 275 (CST)—3:15 PM to 4:15. WHAR, Atlantic City, N. J., 275 (EST)—2:30 PM to 3:45; 7:50 to 10; 11:15 to 12. WHN, New York City, 360 (EST)—1 PM to 1:30; 3 to 6; 10 to 12. WHT, Chicago, Ill., 238 (CST)—9:30 AM to 1:15 PM; 5 to 9. WIP, Philadelphia, Pa., 508.2 (EST)—10:45 AM to 12:30 PM; 4:15 to 5:30. WJZ, New York City, 455 (EST)—9 AM to 12:30 PM; 2:30 to 4; 7 to 11. WKRC, Cincinnati, O., 326 (EST)—6:45 PM to 11. WMCA, New York City, 341 (EST)—11 AM to 12:15 PM; 7 to 7:30. WNYC, New York City, 526 (EST)—9 PM to 11. WOCL, Jamestown, N. Y., 275.1 (EST)—9 PM to 11. WOO, Philadelphia, Pa., 508.2 (EST)—10:45 AM to 12:30 PM; 2:30 to 4. WPG, Atlantic City, N. J., 299.8 (EST)—3:15 PM to 5; 9 to 11. WOJ, Chicago, Ill., 448 (CST)—10:30 AM to 12:30 PM; 3 PM to 4; 8 to 10. WREO, Lansing, Michigan, 285.5 (EST)—10 AM to 11. WRNY, New York City, 288.5 (EST)—3 PM to 5; 7:59 to 10. WSBF, St. Louis, Mo., 273 (CST)—9 to 11 PM. WWC, Detroit, Mich., 352.7 (EST)—11 AM to 12:30 PM; 2 to 4; 6:30 to 9. KDKA, Pittsburgh, Pa., 309 (EST)—9:45 AM to 10:30; 11:55 to 12 M; 2:30 PM to 5:30; 7 to 11. KFNF, Shenandoah, Iowa, 266 (CST)—10:45 AM to 12:30 PM; 2:30 to 4:30; 6:30 to 10. KOA, Denver, Col., 322.4 (MST)—10:55 AM to 1 PM; 4 PM to 5:30; 7:45 to 10. KOIL, Council Bluffs, Iowa, 278 (CST)—11 AM to 12:30 PM; 7:30 to 9. KGW, Portland, Oregon, 491.5 (PST)—10:30 AM to 12:30 PM; 6 to 9. KHJ, Los Angeles, Cal., 405.2 (EST)—10 AM to 12:30 PM; 6 to 9. KJR, Seattle, Wash., 484.4 (PST)—11 AM to 12:30 PM; 3 to 4:30; 7:15 to 9. KTHS, Hot Springs, Ark., 374.8 (CST)—11 AM to 12:30 PM; 2:30 to 3:40; 8:40 to 11.

MONDAY, SEPTEMBER 28

WAAM, Newark, N. J., 263 (EST)—11 AM to 12 M; 7 PM to 11.
WAHG, Richmond Hill, N. Y., 316 (ESTDS)—12:30 M to 1:05 PM; 7:30 to 12.
WAMB, Minneapolis, Minn., 243.8 (CST)—10 PM to 12.
WBMM, Chicago, Ill., 226 (CST)—6 PM to 7.
WBRR, New York City, 272.6 (ESTDS)—8 PM to 9.
WBZ, Springfield, Mass., 333.1 (EST)—6 PM to 11:30.
WCAE, Pittsburgh, Pa., 461.3 (EST)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 12.
WCCB, Zion, Ill., 344.6 (CST)—8 PM to 10.
WCCO, St. Paul and Minneapolis, Minn., 416 (CST)—9:30 AM to 12 M; 1:30 PM to 6:15.
WDAF, Kansas City, Mo., 365.6 (CST)—3:30 PM to 7; 8 to 10; 11:45 to 1 AM.
WEAF, New York City, 492 (EST)—6:45 AM to 7:45; 4 PM to 5; 6 to 11:30.
WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 7 to 8.
WEEL, Boston, Mass., 476 (EST)—6:45 AM to 8; 3 PM to 4; 5:30 to 10.
WEMC, Berrien Springs, Mich., 286 (CST)—8:15 PM to 11.
WFAA, Dallas, Texas, 475.9 (EST)—10:30 AM to 11:30; 2:30 PM to 4; 2:30 to 6; 6:45 to 7; 8:30 to 9:30.
WFBH, New York City, 272.6 (EST)—2 PM to 6:30.
WGCP, New York City, 252 (EST)—2:30 PM to 1:30; 3:10; 6 to 7:30.
WGES, Chicago, Ill., 250 (CST)—5 PM to 8.
WGCP, New York City, 252 (EST)—2:30 PM to 5:18; 8 to 10:45.
WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 3:30 to 5:57.
WGR, Buffalo, N. Y., 319 (EST)—12 M to 12:30 PM; 2:30 to 4:30; 7:30 to 11.
WGY, Schenectady, N. Y., 379.5 (EST)—1 PM to 2:50; 3 to 8:30.
WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8 to 10.
WHAR, Atlantic City, N. J., 275 (EST)—2 PM to 3; 7:30 to 9.
WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.
WHN, New York City, 360 (EST)—2:15 PM to 5; 6:30 to 12.
WHIO, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 7:30 to 9; 11:15 to 12.
WHT, Chicago, Ill., 400 (CST)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.
WIP, Philadelphia, Pa., 508.2 (EST)—7 AM to 8; 1 PM to 2; 3 to 8.
WJZ, New York City, 455 (EST)—10 AM to 11; 1 PM to 2; 4 to 5:30; 6 to 6:30; 7 to 11.
WKRC, Cincinnati, O., 326 (EST)—8 PM to 10.
WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 1; 2 to 3; 4:30 to 6; 7:30 to 11:30.
WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15 PM; 1:30 to 2:30; 3 to 5; 6 to 10.
WMAK, Lockport, N. Y., 265.5 (EST)—8 PM to 12.
WMCA, New York City, 341 (EST)—11 AM to 12 M; 6:30 PM to 12.
WNYC, New York City, 526 (EST)—3:15 PM to 4:15; 6:20 to 11.
WOAW, Omaha, Neb., 526 (CST)—12:30 PM to 1:30; 5:45 to 10:30.
WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 3 to 3:30; 5:45 to 6.
WOO, Philadelphia, Pa., 508.2 (EST)—11 AM to 1 PM; 4:40 to 6; 7:30 to 11.
WOR, Newark, N. J., 405 (EST)—6:45 AM to 7:45; 2:30 PM; 6:15 to 11:30.
WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9.
WPG, Atlantic City, N. J., 299.8 (EST)—7 PM to 11.
WQJ, Chicago, Ill., 488 (CST)—11 AM to 12 M; 3 PM to 4.
WRC, Washington, D. C., 469 (EST)—9 AM to 10; 12 M to 2; 6:15 PM to 6:30.
WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 11.
WRNY, New York City, 258.5 (EST)—11:59 AM to 2 PM; 7:30 to 11.
WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12.
WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 10:30; 12 to 1 AM.
WVJ, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 10.
KDKA, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:15 PM; 2:30 to 3:20; 5:30 to 10.
KFAE, State College of Wash., 348.6 (PST)—7:30 PM to 9.
KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11.
KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30.
KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.
KFOA, Seattle, Wash., 455 (PST)—12:45 PM to 1:30; 4 to 5:15; 6 to 10.
KGO, Oakland, Cal., 361.2 (PST)—9 AM to 10:30; 11:30 AM to 1 PM; 1:30 to 6; 6:45 to 7; 8 to 1 AM.
KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30; 5 to 8.
KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 1:30 PM; 5:30 to 10.
KJR, Seattle, Wash., 384.4 (PST)—1 PM to 2:45; 6 to 6:30; 7 to 11.
KNX, Hollywood, Cal., 337 (PST)—12 M to 1 PM; 4 to 5; 6:30 to 12.
KOB, State College of New Mexico, 348.6 (MST)—11:55 AM to 12:30 PM; 7:30 to 8:30; 9:55 to 10:10.
KOIL, Council Bluffs, Iowa, 278 (CST)—7:30 PM to 10.
KPO, San Francisco, Cal., 428 (PST)—10:30 AM to 12 M; 1 PM to 2; 2:30 to 3:30; 4:30 to 10.
KSD, St. Louis, Mo., 541.1 (CST)—7:30 PM to 10.
KTHS, Hot Springs, Ark., 374.8 (CST)—12:30 PM to 1; 8:30 to 10.

KYW, Chicago, Ill., 536 (CSTDS)—6:30 AM to 7:30; 10:55 to 1 PM; 2:15 to 3:30; 6:02 to 7.

TUESDAY, SEPTEMBER 29

WAAM, Newark, N. J., 263 (EST)—11 AM to 12 M; 7 PM to 11.
WAHG, Richmond Hill, N. Y., 316 (EST)—12 PM to 1:05 AM.
WAMB, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12.
WBMM, Chicago, Ill., 226 (CST)—8 PM to 12.
WBRR, New York City, 272.6 (EST)—3:30 PM to 6:30.
WBZ, Springfield, Mass., 333.1 (EST)—6 PM to 11.
WCAE, Pittsburgh, Pa., 461.3 (EST)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 11.
WCCO, St. Paul and Minneapolis, Minn., 416 (CST)—9:30 AM to 12 M; 1:30 PM to 4; 5:30 to 10.
WDAF, Kansas City, Mo., 365.6 (CST)—3:30 PM to 7; 7:15 to 11:45 to 1 AM.
WEAF, New York City, 492 (EST)—6:45 AM to 7:45; 11 to 12 M; 4 PM to 5; 6 to 12.
WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 7 to 10; 10 to 11.
WEEL, Boston, Mass., 476 (EST)—6:45 AM to 8; 1 PM to 2; 6:30 to 10.
WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1; 2:30 to 6; 6:45 to 7; 8:30 to 9:30; 11 to 12.
WFBH, New York City, 272.6 (EST)—2 PM to 6:30; 11:30 to 12:30 AM.
WGBS, New York City, 316 (EST)—10 AM to 11; 1:30 PM to 3; 6 to 11:30.
WGCP, New York City, 252 (EST)—2:30 PM to 5:15.
WGES, Chicago, Ill., 250 (CST)—7 PM to 9; 11 to 1 AM.
WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30.
WGR, Buffalo, N. Y., 319 (EST)—11 AM to 12:45 PM; 7:30 to 11.
WGY, Schenectady, N. Y., 379.5 (EST)—11 PM to 2:30; 5:30 to 7:30; 9:15 to 11:30.
WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30.
WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.
WHAR, Atlantic City, N. J., 275 (EST)—2 PM to 3; 7:30 to 9; 11:15 to 12.
WHN, New York City, 360 (EST)—12:30 PM to 1; 2:15 to 3:15; 4 to 5:30; 7:30 to 10:45; 11:30 to 12:30 AM.
WHO, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 7:30 to 9; 11:30 to 12.
WHT, Chicago, Ill., 400 (CST)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.
WIP, Philadelphia, Pa., 508.2 (EST)—7 AM to 8; 1 PM to 2; 3 to 8.
WJZ, New York City, 455 (EST)—10 AM to 11; 1 PM to 2; 4 to 5:30; 6 to 6:30; 7 to 11.
WKRC, Cincinnati, O., 326 (EST)—8 PM to 10.
WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 1; 2 to 3; 4:30 to 6; 7:30 to 11:30.
WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15 PM; 1:30 to 2:30; 3 to 5; 6 to 10.
WMAK, Lockport, N. Y., 265.5 (EST)—8 PM to 12.
WMCA, New York City, 341 (EST)—11 AM to 12 M; 6:30 PM to 12.
WNYC, New York City, 526 (EST)—3:15 PM to 4:15; 6:20 to 11.
WOAW, Omaha, Neb., 526 (CST)—12:30 PM to 1:30; 5:45 to 10:30.
WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 3 to 3:30; 5:45 to 6.
WOO, Philadelphia, Pa., 508.2 (EST)—11 AM to 1 PM; 4:40 to 6; 7:30 to 11.
WOR, Newark, N. J., 405 (EST)—6:45 AM to 7:45; 2:30 PM; 6:15 to 11:30.
WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9.
WPG, Atlantic City, N. J., 299.8 (EST)—7 PM to 11.
WQJ, Chicago, Ill., 488 (CST)—11 AM to 12 M; 3 PM to 4; 7 to 8; 10 to 2 AM.
WRC, Washington, D. C., 469 (EST)—9 AM to 10; 12 M to 2; 6:55 PM to 11.
WREO, Lansing, Michigan, 285.5 (EST)—8:15 PM to 11.
WRNY, New York City, 258.2 (EST)—11:59 AM to 2 PM; 4:30 to 5; 8 to 11.
WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 8 to 9; 10:45 to 12.
WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 10:30; 12 to 1 AM.
WVJ, Detroit, Mich., 352.7 (EST)—8 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 10.
KDKA, Pittsburgh, Pa., 309 (EST)—9:45 PM to 12.
KFAE, State College of Wash., 348.6 (PST)—7:30 PM to 9.
KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11.
KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30.
KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.
KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 10.
KGO, Oakland, Cal., 361.2 (PST)—11:30 AM to 1 PM; 1:30 to 2; 2:30 to 3:30; 4:30 to 10.
KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11.
KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:20 PM; 5:30 to 11.
KJR, Seattle, Wash., 384.4 (PST)—9 AM to 6:30 PM; 8:30 to 1 AM.
KNX, Hollywood, Cal., 337 (PST)—9 AM to 10; 1 PM to 2; 4 to 5; 6:30 to 12.

WEDNESDAY, SEPTEMBER 30

WAAM, Newark, N. J., 263 (EST)—12:30 PM to 1:05; 7:30 to 11:05.
WAHG, Richmond Hill, N. Y., 316 (EST)—12 M to 1:05 PM; 8 to 12.
WAMB, Minneapolis, Minn., 243.8 (CST)—12 M to 1 PM; 10 to 12.
WBMM, Chicago, Ill., 226 (CST)—8 PM to 10.
WBZ, Springfield, Mass., 333.1 (EST)—6 PM to 11.

WCAE, Pittsburgh, Pa., 461.3 (EST)—12:30 PM to 1:30; 4:30 to 5:30; 6:30 to 11.
WCCO, St. Paul and Minneapolis, Minn., 416.4 (CST)—9:30 AM to 12 M; 1:30 to 4; 5:30 to 12.
WDAF, Kansas City, Mo., 365.6 (CST)—3:30 PM to 7; 8 to 9:15; 11:45 to 1 AM.
WEAF, New York City, 492 (EST)—6:45 AM to 7:45; 11 to 12 M; 4 PM to 5; 6 to 12.
WEAO, Ohio State University, 293.9 (EST)—8 PM to 10.
WEAR, Cleveland, O., 390 (EST)—11:30 AM to 12:10 PM; 3:30 to 4:10; 6:45 to 7:45.
WEEL, Boston, Mass., 476 (EST)—6:45 AM to 8; 3 PM to 4; 5:30 to 10.
WEMC, Berrien Springs, Mich., 286 (CST)—8:15 PM to 11.
WFAA, Dallas, Texas, 475.9 (CST)—10:30 AM to 11:30; 12:30 PM to 1.
WFBH, New York City, 270.6 (EST)—2 PM to 7:30; 12 M to 1 AM.
WGCP, New York City, 252 (EST)—2:30 PM to 5:18; 8 to 10.
WGBS, New York City, 250 (CST)—7 PM to 9; 11 to 1 AM.
WGBS, New York City, 316 (EST)—10 AM to 11 PM; 1:30 to 4; 6 to 7.
WGN, Chicago, Ill., 370 (CST)—9:31 AM to 3:30 PM; 5:30 to 11:30.
WGR, Buffalo, N. Y., 319 (EST)—12 M to 12:45 PM; 7:30 to 4:30; 6:30 to 11.
WGY, Schenectady, N. Y., 379.5 (CST)—5:30 PM to 7:30.
WHAD, Milwaukee, Wis., 275 (CST)—11 AM to 12:15 PM; 4 to 5; 6 to 7:30; 8 to 10; 11:30 to 12:30 AM.
WHAS, Louisville, Ky., 399.8 (CST)—4 PM to 5; 7:30 to 9.
WHN, New York City, 368 (EST)—2:15 PM to 5:30; 7:30 to 11; 11:30 to 12:30 AM.
WHO, Des Moines, Iowa, 526 (CST)—12:15 PM to 1:30; 6:30 to 12 M.
WHT, Chicago, Ill., 400 (CST)—11 AM to 2 PM; 7 to 8:30; 10:30 to 1 AM.
WIP, Philadelphia, Pa., 508 (EST)—7 AM to 8; 10:20 to 11; 1 PM to 2; 3 to 4; 6 to 8.
WJZ, New York City, 455 (EST)—10 AM to 12; 12:45 PM to 2; 4 to 6; 6 to 11:30.
WKRC, Cincinnati, Ohio, 326 (EST)—8 PM to 10.
WLIT, Philadelphia, Pa., 395 (EST)—12:02 PM to 12:30; 2 to 3; 4:30 to 6; 7:30 to 9.
WLW, Cincinnati, O., 422.3 (EST)—10:45 AM to 12:15 PM; 1:30 to 2:30; 3 to 5; 6 to 11.
WMCA, New York City, 341 (EST)—10:45 AM to 12; 6:30 PM to 12.
WNYC, New York City, 526 (EST)—6:30 PM to 11.
WOC, Davenport, Iowa, 484 (CST)—12:57 PM to 2; 3 to 3:30; 4 to 7:05; 9 to 11.
WOR, Newark, N. J., 405 (EST)—6:45 AM to 7:45; 2:30 PM to 4; 6:15 to 12 M.
WPAK, Fargo, N. D., 283 (CST)—7:30 PM to 9.
WRC, Chicago, Ill., 448 (CST)—11 AM to 12 M; 3 PM to 7; 8 to 10; 12 to 2 AM.
WRC, Washington, D. C., 469 (EST)—9 AM to 10; 12 M to 2; 6:25 PM to 7.
WREO, Lansing, Michigan, 285.5 (EST)—10 PM to 11.
WRNY, New York City, 258.5 (EST)—11:59 AM to 2 PM; 7:59 to 9:55.
WSB, Atlanta, Ga., 428.3 (CST)—12 M to 1 PM; 2:30 to 3:30; 5 to 6; 10:45 to 12.
WSBF, St. Louis, Mo., 273 (CST)—12 M to 1 PM; 3 to 4; 7:30 to 9.
WWJ, Detroit, Mich., 352.7 (EST)—6 AM to 8:30; 9:30 to 10:30; 11:55 to 1:30 PM; 3 to 4; 6 to 7; 8 to 10.
KDKA, Pittsburgh, Pa., 309 (EST)—6 AM to 7; 9:45 to 12:15 PM; 2:30 to 3:20; 5:30 to 11.
KFAE, State College of Wash., 348.6 (PST)—7:30 PM to 9.
KFI, Los Angeles, Cal., 467 (PST)—5 PM to 11.
KFKX, Hastings, Neb., 288.3 (CST)—12:30 PM to 1:30; 5:15 to 6:15; 9:30 to 12:30 AM.
KFNF, Shenandoah, Iowa, 266 (CST)—12:15 PM to 1:15; 3 to 4; 6:30 to 10.
KFOA, Seattle, Wash., 455 (PST)—12:30 PM to 1:30; 4 to 5:15; 6 to 10.
KGO, Oakland, Cal., 361.2 (PST)—11:30 AM to 1 PM; 1:30 to 2; 2:30 to 3:30; 4:30 to 10.
KGW, Portland, Oregon, 491.5 (PST)—11:30 AM to 1:30 PM; 5 to 11.
KHJ, Los Angeles, Cal., 405.2 (PST)—7 AM to 7:15; 12 M to 3:20 PM; 5:30 to 11.
KJR, Seattle, Wash., 384.4 (PST)—9 AM to 6:30 PM; 8:30 to 1 AM.
KNX, Hollywood, Cal., 337 (PST)—9 AM to 10; 1 PM to 2; 4 to 5; 6:30 to 12.

CRYSTAL SETS FOR USE TODAY, by Lewis Winner, with diagrams, in RADIO WORLD, dated July 25, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

HAVE YOU ANYTHING TO SELL OR EXCHANGE? Use RADIO WORLD'S Classified Department and get great results. 10c a word. RADIO WORLD, 1493 Broadway, N. Y.

LISTEN IN every Friday at 7 P. M. and hear Herman Bernard, managing editor of RADIO WORLD discuss "Your Radio Problem" from WGBS, Gimbel Bros., New York City. 315.6 meters

A THOUGHT FOR THE WEEK

The man who said he would physically demonstrate the theory of perpetual motion was, Marconi is!

RADIO WORLD

Radio World's Slogan: "A radio set for every home."

TELEPHONES: LACKAWANNA 6976 and 2063
PUBLISHED EVERY WEDNESDAY
(Dated Saturday of same week)
FROM PUBLICATION OFFICE
HENNESSY RADIO PUBLICATIONS CORPORATION
ROLAND BURKE HENNESSY, President
M. B. HENNESSY, Vice-President
FRED S. CLARK, Secretary and Manager
1493 BROADWAY, NEW YORK, N. Y.
(Putnam Bldg., Times Square and 43rd Street)
European Representatives: The International News Co.
Brema's Bldg., Chancery Lane, London, Eng.
Paris, France, Brentano's, 38 Avenue de l'Opera.
San Francisco, Loyd B. Chappell, 656 O'Farrell St.

EDITOR, Roland Burke Hennessy
MANAGING EDITOR, Herman Bernard

SUBSCRIPTION RATES

Fifteen cents a copy, \$6.00 a year, \$3.00 for six months, \$1.50 for three months. Add \$1.00 a year extra for foreign postage, Canada, 50 cents.
Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address also. State whether subscription is new or a renewal.

ADVERTISING RATES

General Advertising		
1 Page, 7 1/2" x 11"	462 lines	\$300.00
1/2 Page, 7 1/2" x 5 1/2"	231 lines	150.00
1/4 Page, 4 1/2" x 11"	115 lines	75.00
1 Column, 2 1/2" x 11"	154 lines	100.00
1 Inch		10.00
Per Agate line		.75
Times Discount		
52 consecutive issues		20%
26 times consecutively or E. O. W. one year		15%
4 consecutive issues		10%


WEEKLY, dated each Saturday, published Wednesday.
Advertising forms close Tuesday, eleven days in advance of date of issue.

CLASSIFIED ADVERTISEMENTS

Ten cents per word, minimum, 10 words. Cash with order. Business Opportunities, 50 cents a line; minimum, \$1.00.

Entered as second-class matter, March 28, 1922, at the Post Office at New York, N. Y., under the act of March 3, 1879.

SEPTEMBER 26, 1925

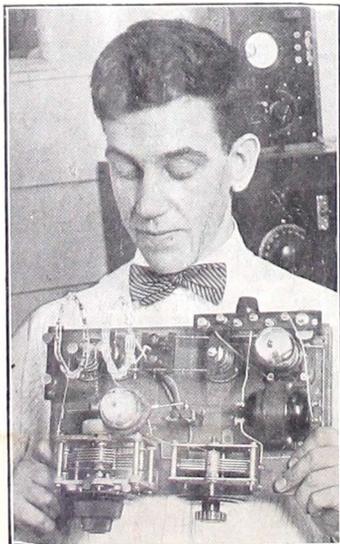

HERE IS the amateur's delight, a short wave low-loss receiver. The circuit is the standard regenerative type, with a tickler employed in the plate circuit and will tune from 20 to 110 meters. The base of the tube was taken off so that there would be no extra capacity to raise the wavelength of the set or make it hard to control. The coils are of the air wound type. Note the large porcelain insulators on the baseboard.

Super-Power Blanketing of Small Stations Only A Myth, Experts Find

By Thomas Stevenson

WASHINGTON.

Super-power will never supplant the local station. This is the outstanding conclusion of radio experts at Washington as a result of the recent 50-kilowatt experiments of WGY at Schenectady.

The test proved almost conclusively that regardless of the power used by any station, its service area will be too small to render absolutely dependable reception over wide areas.

Radio engineers estimate that the dependable service area of a 500-watt station does not exceed 25 miles. This does not mean that the station cannot be heard beyond that distance, but that fans more than 25 miles away cannot always depend on being able to get that particular station every time it is on the air with sufficient clarity to fully appreciate its programs. The crystal set service range of a 500-watt station is less than 25 miles.

Distance Results

Some laymen thought that when the power was increased from 500 to 50,000 watts that it would correspondingly increase the service range 100 times, or to 2,500 miles. But this is not true at all. Instead, it can safely be said that the service range of a 50-kilowatt station does not exceed 100 miles. As a matter of fact, fading was experienced on the signals of WGY during the test at much less than 100 miles. Of course, with the strength of the signals, the fading could be partially overcome. Also, the fading probably would not be experienced at all times.

There is no doubt that the subject will receive considerable attention at the next national radio conference. It is believed that the conclusion of the conference will

be that there is a definite place for both the higher-power and the local station, and that interconnection should be depended on for the broadcasting of national events rather than super-power stations.

Need 2,000 Stations!

With the present limitation to the service area of a broadcasting station, there has been much speculation as to the number of stations that would be required to give perfect reception to all parts of the country. Estimates now are that probably more than 2,000 stations would be required to give perfect reception to every citizen in the United States.

At the present time there are about 560 stations, many of which are 100 watts or less. Until some method is found to put stations closer together in the present broadcasting band, or else enlarge it, it is not believed the total number of stations will exceed 600.

(Copyright, 1925, by Stevenson Radio Syndicate)

STATIONS ARE PREPARING TO USE HIGHER POWER

Anticipating that the next National Radio conference will approve higher power, several stations throughout the country are now being equipped to go as high as 50 kilowatts, it has been learned.

It is believed that the subject will provoke quite a heated discussion when the conference assembles. Last year the increase to 5,000 watts was bitterly opposed until suggestion was made that the increase be placed on an experimental basis with the understanding that if interference or blanketing resulted, the stations would be forced to decrease their power.

The contention of those who oppose higher power is that it would result in blanketing of the smaller stations and thereby create a monopoly.

New Books

Dynamo Electric Machinery, a technical treatise on the construction and operation of Direct and Alternating Current Machines, by Erich Hausmann, E.E., Sc.D., Thomas Potts Professor of Physics and Electrical Communication at the Polytechnic Institute of Brooklyn, N. Y., published by D. Van Nostrand, N. Y. City.

This volume is intended for extensive classroom use. Due to the ingenious manner that this volume is presented, recitations, computations and occasional lectures supplemented by laboratory sessions can be obtained.

The first two chapters deal with the electric and magnetic circuits. Direct-current machinery is discussed in the following five chapters. Properties of alternating currents and their circuits are treated thoroughly in the next three chapters. Alternating current machines and transformers are discussed. The last chapter deals with conversion apparatus. All these data are given in accordance with modern practice and standardization. The beginner as well as the advanced will find a lot of interesting matter in this book.

* * *

Radio: Beam and Broadcast, an interesting book on the history of radio-telegraphy and telephony and its patents, by A. H. Morse, Associate, Institute of Electrical Engineers, Member, Institute of Radio Engineers. Published by D. Van Nostrand, N. Y. City.

In this book patents of the American and British inventors relating to radio are treated fully. It is the authors' object to

help to correct the perspective of newcomers in the patent field. This book is also intended to be of some assistance to the British and American agents and attorneys who are new to the art, and also to the inventors, experimenters and radio enthusiasts on both the American and British soil. The evolution of radio is traced through the patent office, therefore this volume is of historical value.

JOIN THE A. B. C.

A. B. C. stands for American Broadcast Club, an organization of fans banded together to promote the welfare of radio. There are no dues, no obligations. Address A. B. C. Editor, RADIO WORLD, 1493 Broadway, New York City. The names and addresses of new members follow:

Edwin L. Parrish, 216 W. 31st St., Norfolk, Va.
John H. Simon, 1747 N. Crosey St., Philadelphia, Pa.

Edward Hassel, 513 Superior St., Grove St., Pa.
William Haugsted, 606 9th St., Nevada, Ia.
Jerome L. Cheatham, 24 Hillside Ave., Montclair, N. J.

Clifford Corbett, 65 Whiting Ave., Tarrington, Conn.

Gaston Casanova, 7 Dr. Vadi St., Mayaguez, Porto Rico.

Alex Silva, 945 15th Ave., Milwaukee, Wis.
Roy Sadler, 2501 East 9th St., Kansas City, Mo.

Vialis F. Walz, Glen Haven, Wis.

William C. Peace, 126 Seaton Place, Washington, D. C.

J. F. Greenan, 228 Garden Ave., Toronto, Canada.
L. A. Tucker, R. I. Box 52, Azle, Tex.

LISTEN IN every Friday at 7 P. M. and hear Herman Bernard, managing editor of RADIO WORLD, discuss "Your Radio Problem," from WGBS, Gimbel Bros., New York City, 315.6 meters.

Both N. Y. Shows Succeed

Big Men at the Armory Event

Wound Wire Aerial

The Wound Wire Aerial Co. of Reedville, Va., submitted to Radio World's Laboratories a roll of their wound wire antenna wire. This was tested on a standard receiver and the results obtainable were excellent. The signals were louder than with the common type of antenna wire employed. Most of the ideals that make up the perfect antenna are incorporated in this antenna. The outer coating of wire is coiled, with about 6 turns of the wire to the inch. The wire used for this coiling is No. 18 enameled copper wire. Underneath this coil of wire is the antenna wire, which is No. 14 soft drawn enameled copper wire. This type is very good for use as an indoor antenna. The total area covered by this kind of winding is much greater than with any other type, which gives us a greater space for the collecting of electromagnetic energy. Enameled wire is much better for reception of signals than with plain copper hard drawn wire.

Coming Events

- SEPT. 21 to 26—First Annual Radio Expos., Broadcast Listeners' Association, Radio Tabernacle, Indianapolis, Ind. Write Claude S. Wallin, Hotel Severin.
- SEPT. 21 to 29—International Radio Exposition, Steel Pier, Atlantic City, N. J.
- SEPT. 23 to Oct. 3—National Radio Exposition, American Exp. Palace, Chicago. Write N. R. E., 440 S. Dearborn St., Chicago, Ill.
- SEPT. 28 to OCT. 3—Midwest Radio Week.
- OCT. 3 to 10—Radio Exposition, Arena, 46th and Market Streets, Philadelphia, Pa., G. B. Boden-hof, manager, auspices Philadelphia Public Ledger.
- OCT. 5 to 16—Second Annual Northwest Radio Exposition, Auditorium, St. Paul, Minn. Write 515 Tribune Annex.
- OCT. 5 to 11—Second Annual Radio Show, Convention Hall, Washington, D. C. Write Radio Merchants' Association, 233 Woodward Bldg.
- OCT. 10 to 16—National Radio Show, City Auditorium, Denver, Colo.
- OCT. 12 to 15—South Texas Radio Exposition, Post-Dispatch (KPRC), Houston, Tex.
- OCT. 12 to 17—Boston Radio Show, Mechanics' Hall. Write to B. R. S., 209 Massachusetts Ave., Boston, Mass.
- OCT. 12 to 17—St. Louis Radio Show, Coliseum. Write Thos. P. Convey, manager, 737 Frisco Bldg., St. Louis, Mo.
- OCT. 12 to 17—Radio Show, Montreal, Can., Canadian Expos. Co.
- OCT. 17 to 24—Brooklyn Radio Show, 23d Regt. Armory. Write Jos. O'Malley, 1157 Atlantic Ave., Brooklyn, N. Y.
- OCT. 19 to 25—Second Annual Cincinnati Radio Exposition, Music Hall. Write to G. B. Boden-hof, care Cincinnati Enquirer.
- OCT. 26 to 31—First Annual Rochester Times-Union Radio Exposition, Convention Hall, Rochester, N. Y. Write Howard H. Smith, care Times-Union.
- NOV. 2 to 7—Radio Show, Toronto, Can., Canadian Expos. Co.
- NOV. 3 to 8—Radio Trade Association Exposition, Arena Gardens, Detroit. Write Robt. J. Kirschner, chairman.
- NOV. 19 to 25—Milwaukee Radio Exp., Civic Auditorium. Write Sidney Neu, of J. Andrae & Sons, Milwaukee, Wis.
- NOV. 17 to 22—4th Annual Chicago Radio Exp., Coliseum. Write Herrmann & Kerr, Cort Theatre Bldg., Chicago, Ill.

Business Opportunities Radio and Electrical

Rates: 50c a line; Minimum, \$1.00

- RADIO ENGINEER, HIGH-GRADE, FOR** nationally known manufacturer; brilliant future capable man; state experience, religion and salary expected. P. O. Box 561, Newark, N. J.
- RADIO LOUD SPEAKER, HORNLESS,** New type, protected basic patents, fully demonstrated and approved by most eminent radio experts, revolutionizes sound production, needs capital for immediate marketing. Box 11, Radio World.
- RADIO—I HAVE INVENTED A "B" BATTERY** eliminator which was successfully tested for 8 months; patent was allowed; will either sell outright on royalty or have responsible party or parties finance the manufacture and sale; large profit assured. Box 12, Radio World.



THE Second Annual Radio World's Fair (Manufacturers' Association) at the 258th Field Artillery Armory, New York City.

Lessons from Two Shows

What a thing of beauty the real radio set of today has become was brought home very forcefully at the two recent radio shows in New York City. Next to enhanced beauty, in point of manufacturing development, came simplicity. There were more than seventy receivers operated of the single-control type. Much of what was new in point of appearance or design was not immediately purchasable. This brings up the prevalent merchandising plan of radio manufacturers—to start advertising, and even exhibiting samples of their products long before any deliveries can be made. This practice is not followed from sheer perversity. Some of the favorable factors are:

- (1) The trade and consumer response

may be roughly measured and the production plans formulated accordingly.

- (2) The shrinking of the gap between the previous production of the product and the subsequent demand for it.
- (3) The expediting of actual production due to the psychological effect of having to meet an already existing demand.


Therefore economical considerations impel many manufacturers to avoid, so far as possible, gross overproduction.

Contradicted in Other Lines

But the practice is against what is regarded as the better mode in most forms of business. Where it is considered not only wasteful to wage a publicity campaign

(Continued on next page)

Personages at Fourth Annual

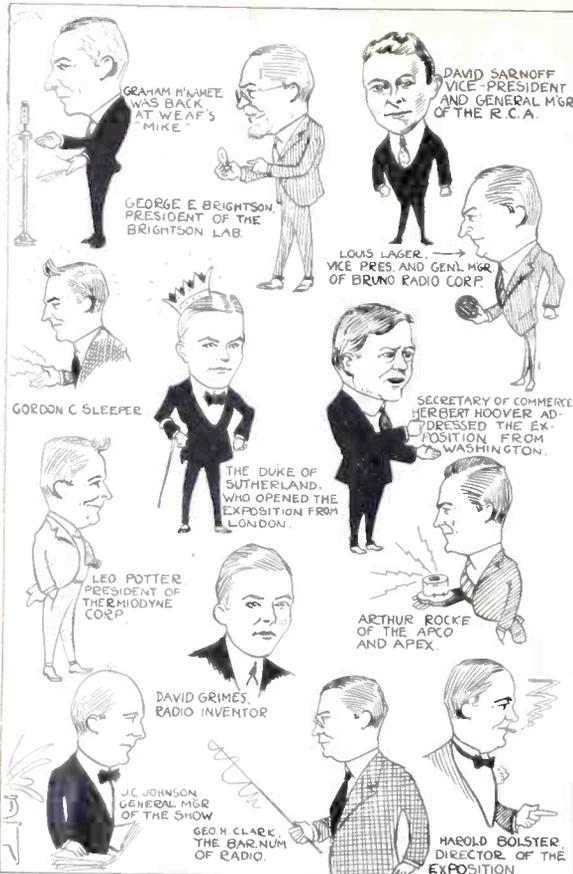

THE Fourth Annual Radio Exposition at Grand Central Palace, New York City.

(Continued from preceding page)

paid long before production can be expected, but to savor somewhat of trifling with the trade and the public.

In radio the trade takes no particular offense if informed that an advertised product that they order from distributor or manufacturer will not be ready for delivery for several weeks. Experience has calloused the trade to the practice. What the reaction of the consumer public is can only be guessed, but as yet no definite proof has been offered that the public, either, is greatly offended because the manufacturer is even more anxious than they to obtain his own product.

It is undeniable, however, that the public is being trifled with when pre-production campaigns are waged, and the measure of response used as a production gauge. The question remains unanswered whether this is good because of the margin of safety that it affords the manufacturer. Prosperity in the trade is a boon to the public, and failures of radio concerns hurt the public more considerably than most persons suppose. Products that skim the horizon today and sink tomorrow leave hordes of owners almost wholly unprotected as to repair service. It might seem that the public would soon learn to deal only with long-established firms, and if this is so it would be deleterious indeed, since keenness for new products, whether of new or old firms, is to be encouraged. The measure of public response should be on the basis of the value of the product, not on the seniority of the manufacturer, even though previous good service by a given concern is bound to be a cumulative asset.

A gap must exist somewhere between

production and popularity and the problem is where to locate that gap.

Take the popularity of the product for granted, regardless of the chronological point at which that trade and public esteem is established. No human being can so nicely balance the two considerations that the moment he is on a quantity production basis the trade and public are consuming his output at exceeding pace.

The factory is a place of many vexations and problems up to the point of quantity production, and meanwhile another branch of the business—the advertising department or agency—has its own great problems to meet. There must be perfect synchronization between the advertised description of the product, both as to appearance and operation, with the actuality. These days many tons of literature are circulated, among the trade particularly, in the honest expectation that every wash drawing shown thereon and every descriptive word written coincides exactly with what the finished product will be. But as the product can not be said to be finished until quantity production sets in, changes do occur. The problem is often solved by the discard of hundreds or thousands of dollars of such literature before insulation, because of a disparity, or the distribution of a new circular. Under either plan the wasteful expense is suffered.

The Schemers

If the advertising long precedes the time when a ready supply of the product can be furnished, then an anxious gap exists. The manufacturer is swamped with orders. He may get a false impression. Especially if some recognized company is producing a new article, dealers and

BEAUTIES graced the Fourth Annual Show, the models in a special fashion show draping themselves gracefully about the landscape. What it all had to do with radio not all fully understood, but the crowds flocked to where the beauties were. Bess Mitchell is shown in the bell of the speaker. (Acme.)



STATUESQUE indeed was this pretty miss, fashion show model, appearing at the Fourth Annual Radio Show. Wonder if the regular fashion shows ever have radio adjuncts? (Acme.)



jobbers will order promiscuously, on the theory that the orders will be filled on a percentage basis. Assuming that all orders could not be filled for weeks or months, the order-gushers assume that the 10,000 articles they cunningly ordered will entitle them, on say a 10 per cent. basis, to a shipment of 1,000. Even 500 would be fine. Indeed, 100 would be quite acceptable. Imagine ordering 10,000 of anything (with the usual cancellation privilege for any unfilled part), and being gratified to receive only a few hundred. Manufacturers know this trick, of course, and fill orders on the basis of the buyer's normal outlet and his credit standing, broad smiles now greeting the huge orders from the little schemers.

Both Methods Used

That situation exists when the gap, in chronological order, is between the demand and the ability to supply it. But if first, the product is ready, or almost (Concluded on next page)

(Concluded from preceding page)
 ready, and the demand is started then, a manufacturer may find that competitors, using the other method, have captured the field, because everybody has been talking about and asking for the other fellow's product. Hence maybe the existing practice has a material force or perhaps a happy medium may be struck, whereby the public and the manufacturer both share the gap. At least it is true that several very substantial concerns this year advertised their products only when ready to deliver.

Such an example is the Amsco Company, with its straight-line frequency condenser. A contrast with this method exists in the case of the Karas Company, which advertised its SLF condenser to

the public in July, the copy having been prepared probably in late May or early June, whereas some dealers found it impossible to obtain any of the Karas condensers until mid-September, and this condition may be assumed to have been general.

The psychological effect of having to meet a previously-created condition has its advantages, but is it too much to ask that manufacturers base their enthusiasm on their product for its own sake? After all, they are selling a radio article, not publicity. It is the radio article that they SELL, the publicity that they BUY.

Remembering that the radio business is a young one, and that the principles of merchandising that prevail in much older lines are at variance with the general practices in radio, it may be assumed that overdoing the publicity work before production, and underdoing it afterward, is an attribute of adolescence and will disappear when the youth reaches his majority.—H. B.

OUR NEW CATALOGUE
Just completed—listing hundreds of BARGAINS, will be mailed to you upon receipt of name and address—
 GET YOUR NAME ON OUR MAILING LIST
SIMPLEX RADIO SUPPLY CO.
 1806 LAFAYETTE AVE. Dept. D. ST. LOUIS, MO.



WOUND WIRE AERIAL
 ABSOLUTELY "DIFFERENT"
 NOTHING BEATS AN OUTSIDE AERIAL
 MAKE those stations that you ALMOST GET—COME IN.
 Don't buy a NEW set. GET THE BEST out of YOURS.
 WRITE TODAY—Price \$5.00. Shipped C.O.D.
 YOUR AERIAL IS IMPORTANT, WHY NOT HAVE THE BEST?
 Your money back if it does not beat any aerial that you have ever used.
THE WOUND WIRE AERIAL CO.
 REEDVILLE, VIRGINIA

FREE two unusual RADIO CATALOGS



FOR "FANS" Our new 64-page Radio Catalog including all the best and latest Kits, Parts and Accessories for broadcast receiving sets. Lowest prices in the country.
 More than 1,000,000 fans and hams make our store their headquarters—get these books and find out why.
 Write for either or both

FOR "HAMS" NEW 32-page booklet of army and navy transmitting apparatus and miscellaneous specials for "hams" such as W. E. Choke Coils, Generators, Resistance Boxes, etc.

509 South State Street
CHICAGO SALVAGE STORES
 Dept. R. W. 6 Chicago Ill.

A Special Combination!—
The Powertone
 Licensed Under Hogan Patent
 with
Bretwood Variable Grid Leak
 In the Set
The Great 5-Tube 1-Dial Receiver Equipped with the Sensational Leak.
RADIO DIVISION, COLUMBIA PRINT
 1493 BROADWAY New York City

\$41.00

Attention, Radio World Subscribers!
 Subscribers will note that the end of their subscriptions is indicated on the labels on wrappers. If your wrapper shows the date later than the current issue, you are behind in your subscription. Please send payment for renewal. Thank you!
 RADIO WORLD, 1493 Broadway, New York City.

NEW INCORPORATIONS

National Radio Service League, N. Y. City, \$100,000; J. L. Diamond, M. B. Moscovitz. (Atty., J. A. Byrne, 305 Broadway, N. Y. City.)
 Frevan Corporation, N. Y. City, radio equipment, 500 common, no par; C. Taylor, J. M. Clark, G. Tilson. (Atty., C. Ogburn, 120 Broadway, N. Y. City.)
 Rodgers Radio Co., Wilmington, Del., \$250,000. (Corporation Trust Company of America.)
 Slap Radio Corp., N. Y. City, \$10,000; N. Feinberg, A. Kiernan, A. Slap. (Atty., S. Ginsberg, 1 Madison Ave., N. Y. City.)
 Gumaer Corp., Jersey City, N. J., radio supplies, \$100,000 in preferred and 2,500 shares, no par common; John R. Turner, Basking Ridge, N. J.; J. E. Braud, Plainfield, N. J.; Alfred D. McCabe, Brooklyn, N. Y. (Atty., Corporation Trust Company, Jersey City, N. J.)
 White Radio Corp., Jersey City, N. J., builders, \$500,000. (Registrar and Transfer Company.)

THOUSANDS OF BARGAINS
FACTORY GUARANTEED MISER BY MAIL
 Genuine New Radiotron or Cunningham Tubes
 UV-189—200—201A—WD-11—12..... **\$1.98**
 C239—300—301A—C11—12.....
 Fresh Burgess or Eveready "B" Batteries
 22½ Volt large size \$1.30—4½ Volt large size \$2.80
 Write for Free new Complete Catalog on Sets and Parts
STONE ELECTRIC CO., 714 Pine St., St. Louis, Mo.
 All Mds. F.O.B. St. Louis, Mo. Dept. W

Literature Wanted
 THE names of readers of RADIO WORLD who desire literature from radio jobbers and dealers are published in RADIO WORLD on request of the reader. The blank below may be used, or a post card or letter will do instead.
 Trade Service Editor,
RADIO WORLD,
 1493 Broadway, New York City.
 I desire to receive radio literature.

Name

City or town.....

State

Are you a dealer?.....

If not who is your dealer?.....

His Name

His Address

Leonard B. Napora, 16 Concord St., Buffalo, N. Y.
 H. H. Donaldson, Tupper Lake, New York.
 W. H. Milne, 1216 Goodfellow Ave., St. Louis, Mo.
 D. G. Libbey, Box 13, U.S.S. Nevada, San Francisco, Cal.
 Robert Hitner, Webb City, Mo.
 Guy L. Howard, 6707 Fir Ave., Cleveland, O.
 Frank Jones, Wright, Kan.
 Jewell-Bradley Radio Shop, 84 Livingston Ave., Albany, N. Y. (Dealer.)
 Louis Keiman, 1013 Kirby E., Detroit, Mich.
 Edward Lack, Germantown, Philadelphia, Pa. (Dealer.)
 A. E. Browning, 4739 Vermont Ave., Detroit, Mich. (Dealer.)
 Cook Hardware Co., Dow City, Ia. (Dealer.)
 Joseph Siemietkoski, 134 Kenihorth, Philadelphia, Pa.
 Columbia Radio Co., 4 Roland Ave., Baltimore, Md.
 H. A. Geldert, Box 251, Groveland, Fla.
 John B. Jones, Ridgeway, Va.
 James H. L. Jewell, 84 Livingston St., Albany, N. Y.
 G. M. DeRose, Roseburg, Ore.

RADIO AGENTS WANTED
5 Tube Demonstrator FREE!
 Earn \$25 to \$100 a week, part or full time. Everyone a prospect. Complete line standard sets and accessories. \$5 to \$30. Write today for illustrated catalog and exclusive selling plan for live dealers and community agents.
20TH CENTURY RADIO CO., 1101 Coca Cola Bldg., Kansas City, Mo.

DAVEN

What is a L-E-A-K-A-N-D-E-N-S-E-R?



EVERY detector tube needs a grid leak of known and permanent value, and a grid condenser of fixed capacity.
 Daven has again blazed the trail by combining in a single unit a grid condenser without mica and without tin foil plates, that does not change its capacity, and does away with wide variations, plus a Daven Grid Leak, standard of accuracy the world over.
 The Leakandenser is simple, effective, sturdy, handsome. Precision-built, takes up less space, better looking, with new fastener clip—\$1.00.

Mail the coupon for complete information.

The Slave of Merit
DAVEN RADIO CORPORATION
 Resistor Specialists
 Reg. U. S. Pat. Off.

Newark New Jersey

DAVEN RADIO CORPORATION L-10-25
 168 Summit Street, Newark, N. J.
 Please send me the following:
 ...Resistor Manual. 50c is enclosed.
 ...Complete Catalogue (free).
 Name.....
 Address.....

Get the Handbook of Resistance Coupled Amplification. At 5c in r's 25c. By mail 30c.

FOR DEALERS: Send your letterhead and we will have our nearest distributor communicate with you.

THE BIG LITTLE THINGS OF RADIO

Diamond Finely Selective, Wonderful for DX Reception

(Concluded from page 6)

on my outdoor antenna (which is a good one, too) that I could not get on a loop. This supports my theory, which I have repeatedly stated: circuits to-day afford such great amplification at radio frequencies that the comparatively small amount of energy picked up by a loop is amply sufficient and enables clearer

and more distant reception than an outdoor antenna. The outside aerial is likely to cause an abnormally high static level for the reception of distant stations and also induce tube overloading, which affects quality. The directional qualities of the loop, moreover, put the Diamond on a loop in the same selectivity class as

the Super-Heterodyne, and enable the separation of low-wave stations that are only 10 kilocycles apart in their frequency assignment, yet very close at hand physically. If there is any set that a person can build at home that gets greater distance and affords finer quality of tone on outdoor aerial or loop, with great volume, I do not know what that set is.

The tuning is not difficult, except for reception of some distant stations, and for the general run of DX reception all receivers are a little difficult to tune. C1 and C3 are the wavelength controls and are at left and right on the panel, while the regeneration control is in the center. Local stations should be tuned in by the voice or music, with the tickler so positioned that it causes no whistle or squawk on any low wave, even before tuning in is attempted. Once a station is received the condenser settings should be noted for logging purposes. It is impossible to log an inductive feedback coil, such as this tickler, so the coupling is tightened until the desired volume is obtained. For reception of distant stations it is necessary to catch the whistle caused by the carrier wave and the oscillating receiver beating. Then the tickler-coupling is made less until the whistle disappeared and only the program is heard.

Many hundreds, if not thousands, built the 1925 Model Diamond, and not one reported serious difficulty. However, anybody who encounters any trouble whatsoever, or who desires information concerning parts or on any point I have not covered, is invited to send his questions to me at 1493 Broadway, New York City.

* * *

FROM CANADA HE GETS MIAMI BEACH ON DIAMOND

DIAMOND EDITOR:
I have just completed building The Diamond of the Air, and tuned in tonight for the first time, using a 115-foot aerial. The stations I listened to were: WBBR, Staten Island, N. Y.; WBZ, Springfield, Mass.; WGY, Schenectady, N. Y.; WPG, Atlantic City, N. J.; WEEL, Boston, Mass.; WHAR, Atlantic City, N. J.; WHT; WIBO; WBBM, Chicago; WOAT, San Antonio, Texas, and WMBF, Miami Beach, Fla.

Every one of the above was received on the speaker with sufficient volume to be enjoyed in the next room. In fact WBZ and WGY nearly blew my Amplion speaker to pieces. I built the J. E. Anderson low-loss Superdyne as described in RADIO WORLD, Nov. 22 and 29, 1924, and although I had remarkable results with it I think Herman Bernard with his Diamond has stolen a march on Mr. Anderson.

A. E. MEGARITY,

49 Cranston Ave., St. John, N. B., Canada.

A RECHARGEABLE "B" WITH A STRONG GUARANTEE

The SEE-JAY BATTERY has met all tests and is endorsed and recommended by the Washington Information Service Bureau and more than 20,000 satisfied users. Genuine Alkaline connected elements, strictest Government test passed and recommended. No drilling or wiring. Connectors crimped under 1,000 pound pressure. Save time temper and money 100 volt unit \$5.00-140 volt, \$8.00 Why buy more? Complete assembled batteries, solution separate, shipped dry, 100-volt, \$12.00; 140, \$18.00. See-Jay unit sold on money-back guarantee. Write for literature and send 20c for improved sample cell. SEE-JAY Battery Co., Dept. W, 315 Brook Ave., New York. Mail order service.

WHOLESALE AND RETAIL

KESTER Radio SOLDER

(Rosin-Core)

If your dealer cannot supply you
send us 25c in postage

CHICAGO SOLDER COMPANY
CHICAGO, U. S. A.

Free LOG also RADIO CATALOG



SAVE
on all the latest standard radio merchandise! No exceptions. Our 1926 Beautifully Illustrated Catalog

JUST OFF THE PRESS!!
Everything new in Radio Line AT SLASHED PRICES.
Write for it today, before you buy anything. Delay means losing exceptional chance to participate in this great bargain-sale. Rush your name and address at once and get also a

LOG BOOK FREE
ECONOMY RADIO SALES COMPANY
288 6th Ave., Dept. 10, New York
DEAL DIRECT AND SAVE REAL MONEY (No Dealers)

CROSLEY
RADIO CATALOG FREE
Describes fully the complete line of radio frequency sets, regenerative sets (licensed under Armstrong U. S. Patent No. 1,113,149) and parts.
Write for Catalog Today.
THE CROSLEY RADIO CORPORATION
POWEL CROSLEY, Jr., President
7408 Sasafraas Street
Cincinnati, Ohio

AMSCO RADIO PARTS

CONDENSERS
VERNERS
RHEOSTATS

AMSCO PRODUCTS, Inc. New York City

ACME
for amplification

HERCULES AERIAL MAST




20 Ft. Mast \$10
40 Ft. Mast \$25
60 Ft. Mast \$45

All steel construction, complete with guy wires and masthead pulley. We pay the freight.
S. W. HULL & CO., Dept. E3
2048 E. 79th St., Cleveland, O.

FREE
Write for literature and Blueprint

At Last Your Reflex Trouble Is Over

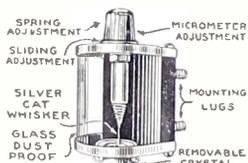

Goucher's Micrometer Rectifier

and Super-Sensitive Crystal is the most efficient rectifier known. Your detector is just as important as the carburetor is on your automobile engine.

Send P. O. Money Order **\$3.00**
or we will send C. O. D.

GUARANTEE: Try it one week. Money back if this rectifier does not respond on your reflex circuit or crystal set beyond your expectation.

JAMES L. GOUCHER & COMPANY
11 SPRINGFIELD AVENUE, NEWARK, N. J.

THE TODD "B" BATTERY

MOST ECONOMICAL The 100 Volt Unit OUTFIT EVER BUILT

Facts!

- 1-TODD "B" BATTERY challenges any substitute battery to equal it in performance.
- 2-With a TODD "B" reception is the clearest obtainable.
- 3-TODD "B" has tens of thousands of satisfied users.
- 4-Most economical both in cost and up-keep.
- 5-Recharging cost—practically nil.
- 6-The ONLY Radio Product, since Radio achieved popularity, to "hold its own."
- 7-A product absolutely GUARANTEED against mechanical defects.
- 8-A battery O'Ked and recommended by Radio Authorities and the PRESS.
- 9-Accredited as being "the everlasting 'B' battery."
- 10-A product the Radio world is proud of.

Don't Fail to Own One. Price \$21.00 with A. C. Charger.

THE TODD ELECTRIC CO., Inc.

36 W. 20th Street
(Tel. Watkins 9266)
New York

List Shows What Channels Are Used for Short Waves

WASHINGTON.

With winter and better radio reception approaching, officials of the Department of Commerce are beginning to worry again about the wavelength situation.

The subject will be taken up at the National Radio Conference which Secretary Hoover will call late in September or early in October. It is possible, although highly improbable, that the conference may be able to find some solution of the problem.

To give a clearer picture of the situation, the following table, showing the allocation of all wavelengths, is presented:

Meters	Meters
0 to 4.69	—Beam transmission.
4.69 to 5.35	—Amateur.
5.35 to 16.7	—Public service and mobile.
16.7 to 18.7	—Amateur.
18.7 to 21.4	—Public service and mobile.
21.4 to 26.3	—Public service.
26.3 to 27.3	—Relay broadcasting exclusive.
27.3 to 30.0	—Relay broadcasting.
30 to 33.3	—Relay broadcasting exclusive.
33.3 to 37.5	—Public service and mobile.
37.5 to 42.8	—Amateur and army mobile.
42.8 to 52.6	—Public service.
52.6 to 54.5	—Relay broadcasting exclusive.
54.5 to 60	—Public service.
60 to 66.6	—Relay broadcasting exclusive.
66.6 to 75	—Public service and mobile.
75 to 85.7	—Amateur and army mobile.
75.7 to 105	—Public service.
105 to 109	—Relay broadcasting exclusive.
109 to 120	—Mobile.
120 to 133	—Aircraft, exclusive.
133 to 150	—Point to point, non-exclusive.
150 to 200	—Amateurs.
200 to 545	—Broadcasting.
545 to 600	—Aircraft and fixed saving of life stations.
600 to 1,052	—Marine and coastal, including radio compass and beacons.
1,052 to 3,156	—Government, point to point, marine and experimental.

(Copyright 1925 by Stevenson Radio Syndicate.)

THE MOST WONDERFUL SOLDERING FLUID ON THE MARKET

SOLDER
the New Way With
Radio Soldering Fluid

A fluid that will make the amateur a professional. No Scraping. Solders any metal. No more paste. No corroding.
Just apply **FLUID** with any Solder

25c per bottle; 30c mailed
IMPETAL SOLDERING FLUID CO.
81 Cortlandt Street New York

GRAPH PAPER

for Drawing Curves for All Radio Purposes, including dial settings plotted against wavelength, frequency or capacity.

Size 7 x 5 1/2". Ten decimals wide (100 squares) and eight high (80 squares). Heavily ruled for divisions of tens and fives. This is the graph paper used by J. E. Anderson, Herman Bernard and others.

Special Price—40c a dozen. 12 dozen \$4.00. Check, P. O. Money Order, Stamps or Coin.

Radio Division, The Columbia Print
1493 Broadway New York City

Jones
MULTI-PLUG
THE STANDARD SET CONNECTOR

HOWARD B. JONES
818 S. CANAL STREET CHICAGO

EVEREADY
Radio Batteries
—they last longer

BATTERY LEAD TAGS
PAT. PEND.

SET OF 14 TWO OF EACH SAFE & QUICK 15 PRICE CENTS
ASK YOUR DEALER
MFD. BY PAUL CLAMZO
203 LAFAYETTE ST. NEW YORK

FREE BOOKLET FOR INVENTORS

IF YOUR INVENTION IS new and useful it is patentable. Send me your sketch. Z. H. POLACHEK, 70 Wall St., New York.
Reg. Patent Attorney-Engineer



\$3.25
RADIO Storage "B" Battery
Lasts Indefinitely—Pays for Itself

22 Cells 22 Volts
Economy and performance unheard of before. Recharged at a negligible cost. Approved and listed as Standard by leading Radio Authorities, including Pop. Radio Laboratories, Pop. Sell. Inst., Standards, Radio News Lab., Letz, Inc., and other important institutions. Equipped with Solid Rubber Case, an insurance against acid and leakage. Extra heavy glass jars. Heavy, rugged plates. Order yours today!

SEND NO MONEY Just state number of batteries wanted and we will ship day order is received. Extra Offer: 4 batteries in series (96 volts), \$12.75. Pay a grossman after examining batteries—6 per cent discount for cash with order. Mail your order now!

WORLD BATTERY COMPANY
1219 So. Wabash Ave., Dept. 62 Chicago, Ill.
Makers of the Famous World Radio "A" Storage Battery
Prices: 6-volt, 100 Amp. \$11.25; 150 Amp. \$15.25; 140 Amp. \$14.00.
All equipped with Solid Rubber Case.

World STORAGE BATTERIES
Set your Radio Dials at 210 meters for the new 1000 watt World Storage Battery Station, WJMC, Chicago. Watch for announcements.
KDKA-WEAF-WGN-WJS-KLU-KGO-KFAT-WJY-KOJ

ULTRA-VERNIER TUNING CONTROL

A VERNIER DIAL ON WHICH YOU CAN PENCIL RECORD THE STATIONS. GEARED 20 TO 1. SILVER FINISH \$2.50. GOLD FINISH \$3.50

PHENIX RADIO CORP., 116-F East 25 St., N.Y.C.

Mailing Lists

Will help you increase sales. Send for FREE catalog giving counts and prices on classified names of your best prospective customers—National, State, Local—Individuals, Professions, Business Firms. Guaranteed 99% by refund of 5c each

ROSS-Gould Co. SEN 100 St. St. Louis

A NEW SUPER-HET KIT \$17.50

With Perfectly Matched Transformers and Filter

This is a SUPERADIO Product—Your Guarantee of Satisfaction!

The most selective, the most powerful, longest ranged, finest toned 8 tube super over designed. Intermediate transformers matched to identical peaks and filter tuned to same peak. Kit includes Antenna Coupler, Oscillator Coupler, Special Variable Condenser, Tuned Input Transformer, 3 matched intermediate transformers and hardware. Complete with booklet, diagrams and full sized working drawings which positively assure perfect success. Order now. Only \$17.50.

SAVE MONEY ON THIS COMPLETE OUTFIT
Every Kit Made Up of Individually Tested Parts as Follows:

Superadio Inductance and Transformer Kit, 2 Heath Radiant Condensers, 2 Keystone Audio Transformers, 8 Benjamin Sockets, 2 Carter Rheostats, 1 potentiometer, all necessary fixed condensers, 2 "Megitts" Grid Leaks, 1	Mounted Blinding Post Board, 1 Base Board, 1 Drilled Panel, 2 "Dialog" Vernier Dials, 2 Truitt Rheostat Dials, 3 Carter Jacks, 1 Carter Filament Switch, Soldering Lugs, Bus Wire and wood screws, diagram and instructions.
---	--

\$73.50

5-TUBE MONARCH OF THE AIR
SUPER-SELECTIVE TUNED RF

With Dialog Vernier Dials and Other World's Finest Quality Parts

When assembled, this receiver will shade the performance of any other 5 tube set ever devised. New greater efficiency obtained through unique circuit and through use of only such parts as match laboratory standards. Never before has a kit of such high quality parts been made up for a 5 tube set. Each part in each kit individually tested. Uses either 5 tubes or 4 tubes and Welty's Crystatone— which kills static. Working drawings and full instructions. Order now. **\$52.50**

3 TUBE DX SPECIAL

A kit of high quality parts individually tested. Makes up into an amazingly selective, abundantly powered 3 tube regenerative receiver. Considering the quality of parts furnished this kit at \$38.50 is an exceptional value. Drawings and instructions included. **\$38.50**

Write for our free Radio Catalog of newest parts
William A. Welty Company, 36 So. State St., Dept. 604, Chicago

The Super-Heterodyne 8-Tube DX Receiver

DAVID GRIMES
Super-Selective RADIO

Baby Grand Duplex Model..... \$59.50
Empire Model..... 100.00
Italian Renaissance Model..... 100.00
David Grimes Super-Tone Loud Speaker.... 25.00

Ask a Grimes Dealer for Demonstration
David Grimes Radio & Cameo Record Corp.
1571 Broadway New York, N. Y.

PANELS
RADION and HARD RUBBER
RETAIL ANY SIZE WHOLESALE
PRICE LIST MAILED ON REQUEST

HARD RUBBER
SHEETS—RODS—TUBING
Special Hard Rubber Parts Made to Order.
Send Sample or Sketch for Quotation.
NEW YORK HARD RUBBER TURNING CO.
212 CENTRE ST. NEW YORK

THE RAMBLER SIX
A REAL PORTABLE

Volume, Clarity, Portability, Durability and
Beauty Unequaled

Lightest in weight. 21 pounds.
Smallest in size. 14x9½x9¾ inches.

LIST PRICE..... **\$80.00**

If your dealer cannot make immediate delivery we will ship direct from factory same day your money order or check is received.

American Interstate Radio Service
183 Greenwich Street, New York City
Distributors, Jobbers, Dealers, write for special trade terms.

(Concluded from page 8)

left off terminal of the .0005 mfd. condenser and to the P post on the filter RFT. Connect the F posts of the filter RFT and the other two RFT together. This common lead goes to the mid-section (arm) of the potentiometer and to one terminal of the .005 mfd. condenser. The other terminal of the .005 mfd. condenser goes to the outer terminal of the potentiometer (resistance wire), and to the F minus post of all the tubes. The left-out F post on the last RFT goes to the F plus post on the second detector and to the left off connection of the potentiometer, which also goes to the resistance wire of the detector rheostat. The arm portions of both rheostats are connected together and go to the A plus lead. The resistance wire of the last rheostat goes to the F plus posts on all the other tubes. The grids of the Filter, 1st and 2nd, RF all go to their respective grid posts on the sockets (Filter to the 1st tube of radio frequency, 1st RF to the grid of the second radio-frequency tube, etc.). The grid post of the last RFT goes to one terminal of the grid condenser and leak. The left off connection of the leak and the condenser go to the grid post of the 2nd detector tube. The plate posts on the 1st RF, 2nd RF and the 3rd RF go to their respective plate posts on the sockets, viz., plate post on 1st RFT to plate post of the 1st radio tube, etc. The B post of the 1st, 2nd and the 3rd RFT go to the B plus 67½-volt post. One terminal of a .1 mfd. condenser goes to the A minus post, and the other post goes to the B plus 67½ volts. The plate of the 2nd detector tube goes to the bottom terminal of the double circuit detector jack, and also to one terminal of the .002 mfd. condenser.

- LIST OF PARTS**
- One Welty antenna coupler.
 - One Welty oscillator coupler.
 - One Welty tuned input (filter) transformer.
 - Three Welty matched intermediate-frequency transformers.
 - Two Heath radiant .0005 mfd. variable condensers.
 - Two Keystone audio-frequency transformers.
 - One 7x24" panel.
 - Eight sockets.
 - 2 6-ohm rheostats.
 - One 400-ohm potentiometer.
 - Two .00025 mfd. grid condensers.
 - Two .002 mfd. fixed condensers.
 - Two .005 mfd. fixed condensers.
 - One .0005 mfd. fixed condenser.
 - One .001 mfd. fixed condenser.
 - One .1 mfd. fixed condenser.
 - Two "Megit" grid leaks, 1 megohm.
 - Two 4" vernier dials.
 - Three jacks, two single circuits and one single circuit.
 - One filament switch.
 - One 7x23" baseboard.
 - Two rheostat 2" dials.
 - Accessories: One small variable condenser (optional), soldering lugs, bus bar, wood screws, phones, loud speaker, A and B batteries, connecting wire etc.

The other terminal of this condenser goes to the F minus post on the sockets. The audio-frequency portion of the wiring is standard, and there is no need of going into detail of this wiring, as it has been repeated consistently. A C battery is used. The negative post of this battery goes to the F minus posts of both AFT. The plus post goes to the A minus post. Across the primary of the second AFT a .001 mfd. condenser is placed. Across the output post a .005 mfd. is connected. There are 90 volts used on the plates of the amplifier tubes.

For those who wish to use the outside antenna, the following data are given: The antenna post goes to the antenna and the ground post goes to the ground post. Connect the loop post which connects to the filament plus side, to the beginning of the secondary winding. Connect the end of this winding to the other loop post. Automatically, when this is done, the condenser is shunted across the secondary of the coil.

How to Obtain Success

This set is by no means an easy job to wire. All wiring is done with No. 14 rubber covered wire. All leads should be as short as possible. Where soldering can be avoided, do so, as the soldering most people do is a detriment to the set instead of a help. Make tight connections.

The special variable condenser should be used in place of the .0005 input fixed condenser. This condenser should be adjusted when the set is tuned to a distant station.

The transformers as shown in the diagram are somewhat different from those now supplied by the Welty people. When wiring connect to posts as lettered on top of new transformers, as the location of these posts has been changed over from the old transformers as shown in the diagram to facilitate wiring.

In the case signals are not loud enough, reverse the A battery leads. Use UV201A tubes throughout. UV199 tubes may be used. The new UX tube may be used in the last step of AF. The panel is 7x24". The baseboard is 6x22".

WASHINGTON JEWELRY CO., BOSTON, MASS.

75c plug FREE



"The SONGBIRD of Loud-speakers"

Songster LOUD SPEAKER

HORN The Horn is made of treated FIBRE that lends mellowness, softness, sweetness. It actually absorbs harsh, coarse sounds. It is NON-RESONATING, NON-VIBRATING. It AMPLIFIES and BEAUTIFIES and repeats FAITHFULLY and CLEARLY the high notes of the singer, the sweet tones of the violin, the stirring march of bands, the natural inflections of the orator—and delightful richness of concert music. To own the SONGBIRD is like having a SONGBIRD in your home.

UNIT The Unit is super-sensitive—with resilient Diaphragm, and special electro-magnets that amplify POWERFULLY. There is an adjuster in the bottom to regulate reception from faintest whisper to thunderous volume.

DESIGN The graceful lines of the SONGBIRD were designed by acoustic experts—and patterned after the shapely throats of the Oriole, the Nightingale and other song birds. This design of HORN is recommended by Radio Scientists. We have sold hundreds to delighted customers. Height, 28 inches. Solid CONVENTIONAL style Base with cords attached. Usually sells for \$20. We have just 792 of them. Our price (while they last) to gain Radio friends..... **\$13.85**

SENT ON 10-DAYS' FREE TRIAL!
YOU PAY ONLY \$1 NOW!

Yes, only \$1 NOW! We want you to use, to hear, to ENJOY it before paying more money. If pleased, you may pay at rate of

\$3 A MONTH \$12.65

or if you wish to pay cash, after 10 days, take \$1.20 discount and send check or money order for

ORDER NOW! ONLY 792 at this price, 10 DAYS' TRIAL! SEND ONLY \$1 TODAY!

Gentlemen: Please send me \$13.85 "SONGBIRD" Loudspeaker. I enclose \$1 first payment. If I am satisfied after 10 DAYS' TRIAL, I have the privilege of paying for it at the rate of \$3 monthly—or of deducting \$1.20 and sending \$12.65 in FULL SETTLEMENT. Otherwise, I shall return it, and my \$1 will be refunded.

NAME.....
ADDRESS.....

2 Generations of Honorable Dealings
WASHINGTON JEWELRY CO.

Importers and National Mail Order House
365 Washington Street, Boston, Mass.
For Prompt Attention Address Radio, Dept. 106

Please write PLAINLY! Tear this coupon out NOW! If you wish to tell us something about yourself it will be appreciated.
R.W. 9-26-25

SOLVED!

—THE "B" BATTERY PROBLEM

Throw away your "B" Batteries and install a Kellogg Trans-B-Farmer. It gives you "B" Battery current direct from your electro light socket at the trifling cost of one-fifth of a cent per hour. Gives better reception—no interferences. Write for details.

Trans-B-Farmer
Kellogg Switchboard & Supply Co.
1066 West Adams Street Chicago, Ill.

Stations Off Their Waves Cause Whistles In Sets

WASHINGTON.

The Department of Commerce is attempting to minimize heterodyne interference which has troubled so many fans, said Dr. C. B. Jolliffe, an engineer of the Bureau of Standards.

"At times, when tuning-in a broadcasting station," remarked Mr. Jolliffe, "there is heard in the receiving set a whistling sound whose pitch (frequency) cannot be changed no matter what is done to the controls of the set. As the tuning adjustments are changed, the whistle reaches greatest intensity at one point on the dials and dies away gradually as they are turned from this tuning point. The fact that the note remains the same pitch distinguishes it from the whistle of varying pitch ('birdies') produced by you own or some other person's generating (oscillating) receiving set.

"If the tuning controls are turned slowly while one listens carefully it will usually be found that there are two stations which can be heard very close together when the whistle is at its maximum loudness. These two transmitting stations are 'beating' and producing the whistle. Let us take, for example, two stations that are on frequencies of 800 and 801 kilocycles per second (wavelengths 375 and 374.5 meters).

"Signals from both of these stations enter the receiving set and in addition to giving up to the set the messages (music, etc.), which the radio-frequency currents produced by the carrier waves, combine and produce a note which has a frequency equal to the difference between the frequencies of the two received waves, in this case 1000 cycle (1 kilocycle) per second. This is a high-pitched whistle.

"Any two stations that are closer together than 3000 cycles will give a whistle which can be heard and which is very annoying. The frequency of the whistle is always the difference in the frequencies of the waves of the two beating stations.

"The assignment of frequencies (wavelengths) which is made by the Department of Commerce to the transmitting stations is such that two Class B stations oper-

ating simultaneously should be no closer in frequency than 10,000 cycles. Two stations having a difference in their frequencies of 10,000 cycles produce a beat note which is too high to be readily audible. So if all Class B broadcasting stations maintain accurately the frequency which they are legally entitled to use they would produce no beat interference. These Class B stations are the ones to which the large majority of the people listen.

LOUD SPEAKER RECEPTION

from either coast on three tubes.
Blueprint and instructions.....\$1.00
Necessary low loss coil.....\$2.50
Beautiful finished instrument.....\$35.00

S. A. TWITCHELL CO.

1930 Western Avenue Minneapolis, Minn.

NEUTRODYNE KIT \$19.75

Complete kit of Heened Neutrodyne parts, including panel, tube sockets, rheostats, jack, fixed condensers and grid leak. Neutroformers complete with variable condensers and neutrodynes. Every part included even to screws and wire. Easy read plans.

Send No Money Pay the Postman Order by Postcard

HELENA MONTANA RADIO SURPLUS STORES

HOOK-UPS!—A lot of them, some of which are sure to suit your purpose, appeared in RADIO WORLD dated Aug. 15. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.

SEEK PLACE ON AIR

Last winter, with stations crowded so closely together, thousands of complaints reached the Department of Commerce of interference. Unless there is a change, conditions will be no better this winter and as a result fans will be unable to get a lot of stations that they like to listen in on.

To make matters even worse, there are pending nearly 200 applications for licenses for new stations. The owners are very anxious to go on the air.

For Maximum Amplification Without Distortion and Tube Noises use the well known

Como Duplex Transformer

Push-Pull
Send for Literature
COMO APPARATUS COMPANY
448 Tremont Street Boston, Mass.

RADIO MANUFACTURERS INVENTORS EXPERIMENTERS

Mechanical Consultants. We develop your ideas, make models and manufacture.
(Mechanics assigned to work under customer's supervision if desired.)
MANUFACTURERS' & INVENTORS' ELECTRIC COMPANY
228 West Broadway (Smith Bldg.), New York City

DEALERS BIG DISCOUNTS

Radio's biggest season is here. Get our new catalog showing huge stocks of radio parts, sets, kits at lowest rock-bottom prices. Quick service. Wonderful special offer on best sets, tubes, batteries. Write for free copy.
W. C. Braun Co., 32- S. Clinton St., Chicago, U.S.A.

"LE CALLE" Six Tube Radio

\$98.50

NET

All complete, in console as shown.

\$200.00 list

Long distance receiver. Built-in loud speaker. Tubes, batteries, unit, aerial outfit. Everything complete. Simple to operate, fully guaranteed.

Two tone walnut finish cabinet.
Terms: 25% down, balance C.O.D.


Agents wanted. Catalog upon request.

RADIO BUYERS' SYNDICATE

1429 So. Michigan Ave. Dept. A Chicago



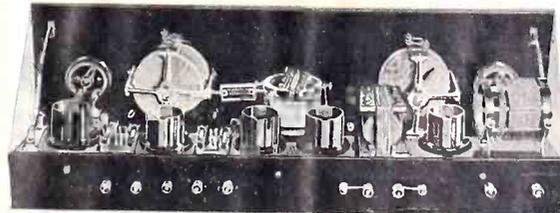FOR THE FINEST RESULTS BUILD HERMAN BERNARD'S 1926 DIAMOND OF THE AIR



Complete Kit of Certified Parts

\$39.50




"Bruno" "99" 3-circuit tuner wound on quartzite with specially designed tickler.

\$5.50



"Bruno" "99" matched Radio Frequency coil for use with the "99"

\$3.00

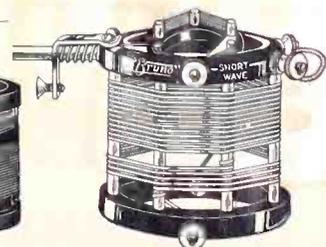

"Bruno" short wave coil tunes from 25-110 meters. Wound on glass, Quartzite minimizing losses.

\$5.50

For Short Waves Build Sidney E. Finkelstein's 2-Tube, 25-110 Meter Set. Complete Kit **\$12.95**

Venus Straight Line Frequency Condenser

.0025	\$1.95
.0035	\$2.10
.005	\$2.25

Write for Free Catalogue

B - C - L RADIO SERVICE CO.,
218 FULTON STREET, NEW YORK CITY

S. HAMMER RADIO CO.

303 Atkins Avenue, Brooklyn, N. Y.
Please send me FREE, Your NEW RADIO CATALOG

Name
Address
City State
FILL OUT AND MAIL


The PERFECT RESISTANCE COUPLED AMPLIFIER
COMPLETELY ASSEMBLED EASY TO ATTACH
 3 Step Amplifier



TYPE 7 G PRICE **\$11.00**

Amplifier Kits, 3 stage \$6.00
 Amplifier Kits, 4 stage 8.25
 Paraffin sealed resistors, 500 ohms to 10 meg.
FREE hook-up, send for bulletin 67
 If your dealer cannot supply you, send direct to
GENERAL RESISTOR COMPANY
 153 WRIGHT STREET NEWARK, N. J.

SLF Condenser Found Marvelously Accurate

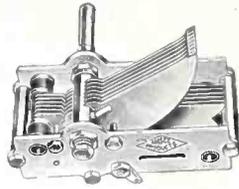

AMSCO .0003 mfd. SLF Condenser

When a straight-line frequency condenser is used, if the exact frequency variation is to be obtained, each division of a 100-division dial representing 10 kilocycles, the proper coil should be used. If there is even a relatively large deviation from the fundamental coil, the stations still will be spread out very well, but the scientific achievement of 10 kcy. separation between adjoining divisions will be only approximate. Reporting on the .0003 mfd. Amsco SLF condenser, one of the three different capacity condensers made by this company, Lester L. Jones, consulting engineer, 693 Broadway, New York City, says:

"The condenser plate is shaped for use with an inductance coil having an inductance of .275 millihenries and in a circuit having a total effective capacity across the condenser of .000029 mfd. In such a circuit the condenser will tune from 522 to 1,510 kilocycles (or a wavelength of from 575 to slightly under 200 meters). The variation in frequency between 6 and 100 degrees on the condenser is quite exactly 10 kilocycles per division (scale having 100 divisions). The variation from the straight-line frequency curve is less than 1%."

The .000029 mfd. capacity was made up of .000009 tube-socket capacity .000012 coil capacity, and .000008 lead capacity.

Two New Stations
 WASHINGTON.

Two new class A stations were licensed recently. They follow:

Station	Owner and Location	Mtrs.	Wts.
KFRM	First Field Artillery, Fort Sill, Okla.	242	50
WBBZ	C. L. Carrell, Portable Station Chicago, Ill.	215.7	50

Men Wanted

to build radio sets in spare time.

LEON LAMBERT
 562-H Kaufman Building
 Wichita, Kansas



Automatic Radio Log Chart

Radio's newest aid makes locating any station simple as A B C. Fill in the blank spaces on revolving disc with dial readings from your own set. Eastern, Western, Canadian and local stations provided for—180 of them. Station you want to "listen in" on can thus be turned to instantly. Mail \$1 with the coupon today.

Sent Postpaid to any address on Receipt of **\$1.00**

Agents Wanted

Pacific Radio Mfg. Co. BW
 8-10 Central Bank Bldg.
 Central, Wash.
 Gentlemen—Enclosed is \$1 for which send me Automatic Radio Log Chart.
 Name
 Street
 City State

GEM TUBE

A Guaranteed Radio Tube Within Reach of All

Every tube guaranteed. A tube for a dollar of \$2 value. A trial order will convince you as it has thousands of others. Send your orders at once. Orders sent C.O.D. parcel post.

- Type .201A
- Type .200
- Type .199
- Type .199A

\$1.00

(with standard base) EACH
 Dealers, Write for Discounts
GEM TUBE CO.

Dept. W, 200 Broadway, N. Y. C.
 220 So. State St., Chicago, Ill.
 Lafayette Bldg., Detroit, Mich.



EVERY SET BUILDER NEEDS THIS

"Morsing Bus-Bar Union"

Makes for quick assembling. Repairs can be made by using Morsing Bus-Bar Union without taking set apart.

Assemble round or square Bus-Bar and solder three wires at a time. Order No. 1 for No. 14, No. 2 for 12 wire. Send 25 cents for enough for building one set, or ten dozen for \$1.00.

Newark Watch Case Material Co.
 15 Ward Street Newark, N. J.
 DISTRIBUTORS WANTED

BARFIELD V

Marko Vernier Dials **\$50.00**
 No extra charge



Special Features

Straight line frequency condensers.
 Two Dial control.
 Cable Cord.
 Only 28 soldered connections.
 This five tube set brings in stations 1500 miles away with local volume and has the appearance and performance of sets selling for several times the price.

Jobbers, dealers and set builders write for our money making proposition.

BARFIELD RADIO COMPANY
 13 Tillary Street Dept. W.B. Brooklyn, N. Y.

COMING!

RADIO WORLD'S 4th Annual Fall Buyers' Number!

Dated October 17, 1925. Last form closes October 6

EVERY READER A BUYER OF RADIO GOODS

Advertisers have found that Radio World's FALL BUYERS' NUMBER of former years were business-bringing issues. The 1925 FALL BUYERS' NUMBER will be much better than the former issues, as our regular editions now are improvements over those of former years.

Use space in this goods-selling issue and reach the thousands of purchasers of sets and parts who are contemplating buying radio goods for the first time, or are about to change their radio equipment.

Regular advertising rates in force for an enlarged edition and sale.

Advertising rates: \$300 a page, \$150 one-half page, \$75 one-quarter page, \$100 1 column, \$10 per inch.

If copy for page is received by October 5, it will be printed, on request, in an extra color without extra cost.

Get in your order and copy now for Radio World's 4TH ANNUAL FALL BUYERS' NUMBER, and cash in on its profit-making circulation.

"Bruno"

Magic Dial




Makes any semi-circular plate condenser tune like the straight-line frequency type. No gears, no backlash.

\$250

BRUNO RADIO CORPORATION
Dept. 926 221 Fulton St. New York City

AT LAST— The Perfect Loud Speaker

BEAUTY CLARITY

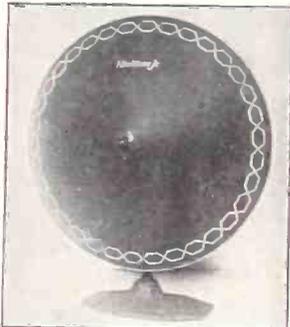

VOLUME QUALITY

VITALITONE

THE TRULY LIFE-LIKE TONE
RADIO REPRODUCER

THE VITALITONE is not sold by argument, but by comparison, and after you've heard it, you will agree with us that there is no comparison.

Suspended Diaphragm

No Horn

Large Model, Price.....\$30.00

Junior Model, Price..... 15.00

ON DEMONSTRATION AT

ROSSITER & CO.

SOLE SALES AGENTS

136 LIBERTY STREET NEW YORK

HOOK-UPS

A lot of them, some of which are sure to suit your purpose, appeared in RADIO WORLD dated August 15. 15c a copy, or start your subscription with that number.
RADIO WORLD, 1493 Broadway, New York City

RESULTS

1,200 Miles on Speaker Easy to Get on Powertone

RESULTS EDITOR:

I have just finished my first set from RADIO WORLD hookups and want to say that I surely am pleased. I constructed the Powertone 5-tube 1-control set. There are six local stations over here, of which three are over 1,000 watts power. I have just tuned in several Los Angeles stations and Portland, and now listening to Vancouver, B. C. (1,200 miles) and can hear it distinctly 30 feet from speaker. I never expected to get such good results from a 1-dial set. It is just as selective as 2- or 3-dial sets. What I like most about it, is the wonderful tone of the audio amplifier, using one transformer and two resistance-coupled stages. Thanks to the inventor of the Powertone for his articles. August 29, September 5 and 12 issues.—George Shoptaugh, 209 Ridgeway Avenue, Oakland, Cal.

"Wonderful Success," His Report on Powertone

RESULTS EDITORS

I want to tell you of my wonderful success with the Powertone by Herman Bernard in the August 29, September 5 and 12 issues.

I got better results than on my neighbor's 5-tube Freed-Eismann Neutrodyne. Your staff sure knows their "stuff." I have built at least one hookup every issue and I find them all good.—Ed. Harlan, Berkeley, Cal.

DIAMOND A DX-GETTER ON A LOOP, FAN FINDS

Diamond Editor:

Last night I completed The Diamond of the Air. From my home in Niles, O., I picked up the following stations with speaker volume, using a home-made loop: KDKA, WCAE, Pittsburgh; WEAR, WTAM, Cleveland; WSAI, WDW, Cincinnati; WCCO, Minneapolis-St. Paul; WEAJ, New York; CNRO, Ottawa, Canada; WBZ, Boston; WCX, WJR, Detroit; and KYW, Chicago.

This convinced me that The Diamond will "do its stuff" with a loop. It is a remarkable circuit. Tell Hancock to "give 'er another whirl!"—E. J. CARIS, 139 Sheridan avenue, Niles, Ohio.

EASY TO MAKE, HARD TO BEAT IS DETROITER'S ESTIMATE

DIAMOND EDITOR:

This is the answer that I have for your critic regarding your hook-ups.

I constructed The Diamond of the Air and at first had a little trouble in tuning, but after a little practice I found out that this is a circuit easy to make, easy to tune and mighty hard to beat.—Geo. D. Kelsey, 4178 Lenox, Detroit, Mich.

STATION FOR PARAGUAY

Paraguay is to have a broadcasting station. The Ministry of War and Marine has been authorized to purchase 60,000 Paraguayan paper pesos worth of material and tools for the radio stations which is to be erected at Fuerte Olimpo. As one Paraguayan paper peso is worth approximately two cents, it is not believed the station will be very powerful.

LESTRON

THE REAL 110 VOLT

TUBE

Works Without Batteries
FOR A. C. or D. C. NO REWINDING
LESTEIN CORPORATION
2 BROADWAY N. Y. CITY

Bruno POWERTONE



"It Has a Soul for Music."

Five Tubes
One Dial
No Trouble

Licensed Under
Hogan Patent
Set, in Handsome
Cabinet

\$39.50

Boxed Kit, \$29.50

Write for Trade Terms

Bruno Radio Corporation
221 Fulton St., N. Y. City

HOW TO BUILD THE POWERTONE, 1 dial, 5 tubes, described in RADIO WORLD, Issues of Aug. 29 and Sept. 5. Powertone Trouble-shooting, Sept. 12. Send 15c for all three. Special diagrams and "blueprint in black" included among the many illustrations. RADIO WORLD, 1493 Broadway, New York.

RADIO WORLD'S 2-For-Price-of-1 Subscription Offer

For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements

—To offer a year's subscription FREE for any one of the following publications with one year's subscription for RADIO WORLD

- RADIO NEWS or —RADIO DEALER or
- POPULAR RADIO or —RADIO JOURNAL or
- RADIO BROADCAST or —RADIO (San Francisco) or
- SCIENCE AND INVENTION or —THE EXPERIMENTER or
- RADIO AGE

This is the way to get two publications

- for the price of one
- Send \$8.00 today for RADIO WORLD
- for one year (regular price
- for 52 numbers)
- and select any one of the other
- nine publications for twelve months.
- Add \$1.00 a year extra for
- Canadian or Foreign Postage.
- Present RADIO WORLD subscribers
- can take advantage of this offer by
- extending subscriptions one year
- if they send renewals NOW.

RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK

RADIO WORLD, 1493 Broadway, New York City.

Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers), beginning _____ and also without additional cost, Radio News, or Popular Radio, or Radio Broadcast, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or The Experimenter, or Radio Journal, or Radio Age (for \$10.00 for two yearly subscriptions).

Indicate if renewal.

Offer Good Until

October 25, 1925

Name

Street Address

City and State

Constants for the 5-Tube Browning-Drake Set

(Concluded from page 9)

home would have a standard parlor receiver, too.

"I can use almost anything for an aerial," he said, "and clamp on to cold water pipes for a ground. I carry the set with me in my car."

The rheostats in the list of parts are for the 4½-volt dry-cell tubes. For the 6-volt type use two 20-ohm and one 15-ohm.

RADIO DE LUXE THE CLEARFIELD 6 TUBE

Encased in plate glass cabinet. Tuned Radio Frequency with Resistance Coupled Amplification. True Tone Quality. List Price... **\$115**

Write for Illustrated Booklet.
Sherman Radio Mfg. Corporation
112-114 Trinity Place New York, N. Y.
Dealers write for our proposition.

AERO COIL


The most **SELECTIVE**, most **POWERFUL** inductance ever designed.

3-CIRCUIT TUNER, \$2.
RADIO FREQUENCY REGENERATIVE KIT, \$11.
WAVE TRAP UNIT, \$4.
OSCILLATOR FOR SUPER-HETERODYNE, \$5.50
AERO PRODUCTS, Inc.
217 N. DESPLAINES ST. CHICAGO, ILL.

\$100.00 A Week Up

Experienced Radio Men wanted to operate factory branches. We guarantee big money and a wonderful future.

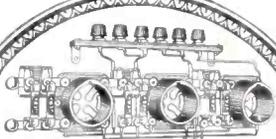Write giving full details to
BARFIELD RADIO COMPANY
13 Tillary St. Dept. W.R. Brooklyn, N. Y.



The VEBY Resistance Coupled Amplifier

Mr. Herinam Bernard. In his receiver, "The Diamond of the Air," used the VEBY method of Resistance Coupled Amplification to the exclusion of all others—he wanted the best—he got the best and maintained the supremacy of his receiver.

The VEBY Amplifier Illustrated; completely assembled; nothing else to buy. \$10.

VEBY RADIO COMPANY
"Quality Resistors"
47-51 Morris Ave.
Newark, N. J.

- LIST OF PARTS**
- One aerial transformers, L1L2.
 - One 3-circuit tuning coil, L3L4L5.
 - Two .0005 mfd. variable condensers, C1, C2.
 - One neutralizing condenser, N.
 - Two 30-ohm rheostats, R1, R2.
 - One 15-ohm rheostat, R3.
 - One double-circuit jack, J1.
 - One single-circuit jack, J2.
 - Fixed condensers: one .00025 mfd. grid condenser; one .001 mfd. by-pass; one 1.0 mfd. by-pass; one .0001 mfd.
 - One variable grid leak.
 - One A battery switch.
 - Five sockets.
 - One 7x21" panel.
 - One baseboard.
 - Three dials.
 - One tap switch.

GERNSBACK'S SET

(Concluded from page 15)

appeal to those who wish the simplest possible control of a radio set.

[The coils used by Mr. Gernsback were wound on a 2½" diameter stator tubing, No. 24 silk over cotton wire being used for the 10-turn primary and the 52-turn secondary. About ¼" separation exists between primary and secondary. The tubing is 3" high. The tickler has 40 turns of No. 28SSC wire on a 1½" diameter, 1¼" high. The secondary inductance in each case is shunted by a .0005 mfd. condenser.]

Mr. Gernsback by special arrangement has consented to answer queries on this circuit. Address Mr. Hugo Gernsback, care RADIO WORLD, 1493 Broadway, New York City, and your letter will be handed to him personally.]



MEGGIT RESISTOR

To build the most perfect Resistance Coupled Amplifier it is essential to use Meggit Resistors and Grid Leaks—they are noiseless, moisture proof and accurate in resistance.

Send 10c for booklet on Resistance Coupled Amplification with circuit diagrams.

COLE RADIO MFG. CO.
Bloomfield N. J.

CRYSTAL SETS FOR USE TODAY, by Lewis Winner with diagrams in RADIO WORLD, dated July 25, 1925. 15c a copy, or start your subscription with that number. RADIO WORLD, 1493 Broadway, New York.



PANELS and BASES RADION BAKELITE AND HARD RUBBER

Cut, Drilled and Engraved for your Specifications

CORTLANDT
PANEL ENGRAVING CO.
81 CORTLANDT ST. N.Y.
TEL.- RECTOR 3268

Developed for Those Who Demand the Best

Apex Vernier Dials

are constructed exhaustively tested and truly scientific principles and are engineered to meet the precise requirements of experts—consequently they more than meet the expectations of the average radio user. They bring in distant stations with accuracy and positiveness seldom encountered and provide control and accuracy essential to full radio enjoyment. They impart a degree of elegance that creates a marked improvement in the appearance of any set. Clockwise or counter clockwise.

Royal Brass Finish, 4 in. \$2.00; 3¼ in. \$1.65
Satin Silver Finish, 4 in. 2.50; 3¼ in. 1.90
DeLuxe Gold (24K) 4 in. 3.00; 3¼ in. 2.50

Apex Rheostat Dials

are little brothers to Apex Vernier Dials. Accurate, handsome—a necessity to satisfactory operation, beauty of appearance.

Royal Silver Finish \$.75
Satin Silver Finish85
DeLuxe Gold (24K) 1.00

If your dealer is unable to supply you, order direct from us.

APEX ELECTRIC MFG. CO.
1410 W. 59th St., Dept. Chicago



RECENT BACK NUMBERS of RADIO WORLD, 15 cents each, or any seven for \$1. Address Circulation Manager, RADIO WORLD, 1493 Broadway, New York City.

RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS.

10 CENTS A WORD. 10 WORDS MINIMUM

ATTENTION RADIO FANS! A 5-tube tuned RF long-distance set for \$16.85, fully guaranteed by manufacturers. J. S. Radio Co., 86 E. 4th Street, New York City.

ROLL FRONT CABINET. Mahogany or walnut finish. Will take panel from eight inches to including twenty-four inches long; seven inches high or less. Moulded top and bottom. Carved front. Is an ideal and beautiful piece of furniture to house your set. Write for circular. Agents wanted. J. A. Kelly Sales Company, Clinton, Iowa.

DINING AND SLEEPING CAR CONDUCTORS (White). Exp. unnecessary. We train you. Send for book of Rules and application. Supt. Railway Exchange, Sta. C, Los Angeles.

RADIO HOSPITAL—Specialists in Neutrodynes and Super-Heterodynes. Dept. 4, Abilene, Kansas.

AGENTS WANTED TO SELL standard radio apparatus. Write us at once if interested. Radio Development and Engineering Co., 180 Broadway, New York.


PATENTS—Write for free Guide Books and "Record of Invention Blank" before disclosing inventions. Send model or sketch of your invention for our Inspection and Instructions Free. Terms reasonable. Radio, Chemical, Mechanical, Electrical and Trademark experts. Victor J. Evans & Co., 924 Ninth, Washington, D. C.

HOOK-UPS

A lot of them, some of which are sure to suit your purpose, appeared in RADIO WORLD dated August 15. 15c a copy, or start your subscription with that number.
RADIO WORLD, 1493 Broadway, New York City



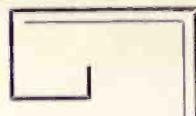EVERY LEAK is thoroughly tested by the audible beat method, with an Osglim tube (above), and again on a megometer. (Foto Topics.)



... if you're not elated.

The Bretwood is the officially prescribed leak for
RADIO WORLD'S 1926 Model Diamond of the
Air.



North American Bretwood Co., 1505 Broadway, New York City.—Enclosed find \$1.50. Send one Bretwood Variable Grid Leak, prepaid, on 10-day money-back guarantee.

*Dealers and Jobbers
Write for
Trade Terms*

Name

Street

City State

North American Bretwood Co.
1505 Broadway New York City

Telephone LACkawanna 2063

GOLD SEAL TUBES



her!

has
ularity

the peak
nsensus
wher-

under the
other

Everywhere
\$2.50
and
guaranteed



plant, Gold Seal s
send each tube out

If you use a tube reju
get longer tube life.

A no-argument guarantee goes with every Gold Seal Tube. Your dealer in giving you this guarantee knows it means what it says because he knows the resources of the Gold Seal organization.

Just say Gold Seal to your dealer. You'll get the tube you have waited for. If your dealer is not yet supplied, write us direct.

- 1— Gold Seal tubes are only as good as the organization behind them.
- 2— Gold Seal tubes are made on tested machinery.
- 3— Dealers stand behind them because we stand back of them.
- 4— Gold Seal's engineers are radio experts; the Gold Seal plant is a reality and a model of efficiency.
- 5— There were six months of exhaustive experiment before Gold Seal Engineers would permit a single tube to be offered to the public.

GOLD SEAL PRODUCTS CORPORATION

250 PARK AVENUE, NEW YORK