

Oct. 16
1926.

RADIO WORLD


Reg. U. S. Pat Off.

15 Cents


Vol. 10, No. 4

America's First and Only National Radio Weekly

Illustrated

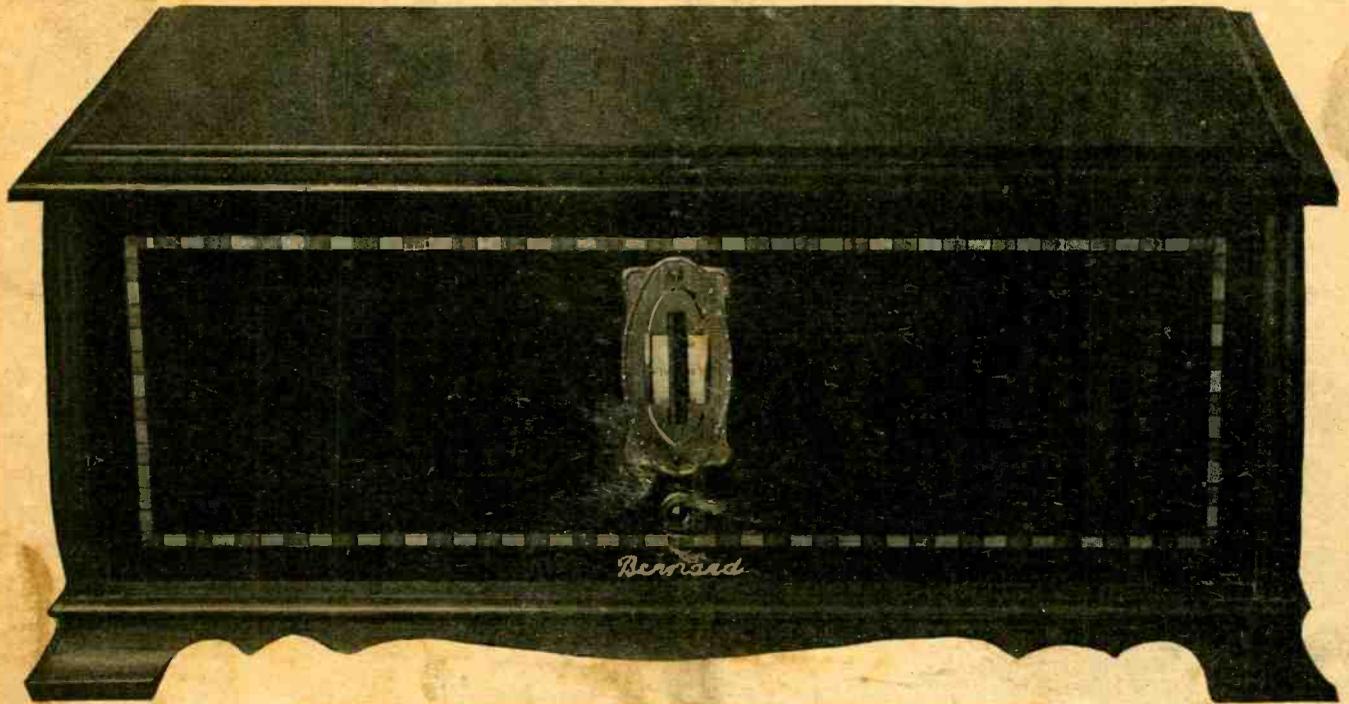


G S'HEEDY.

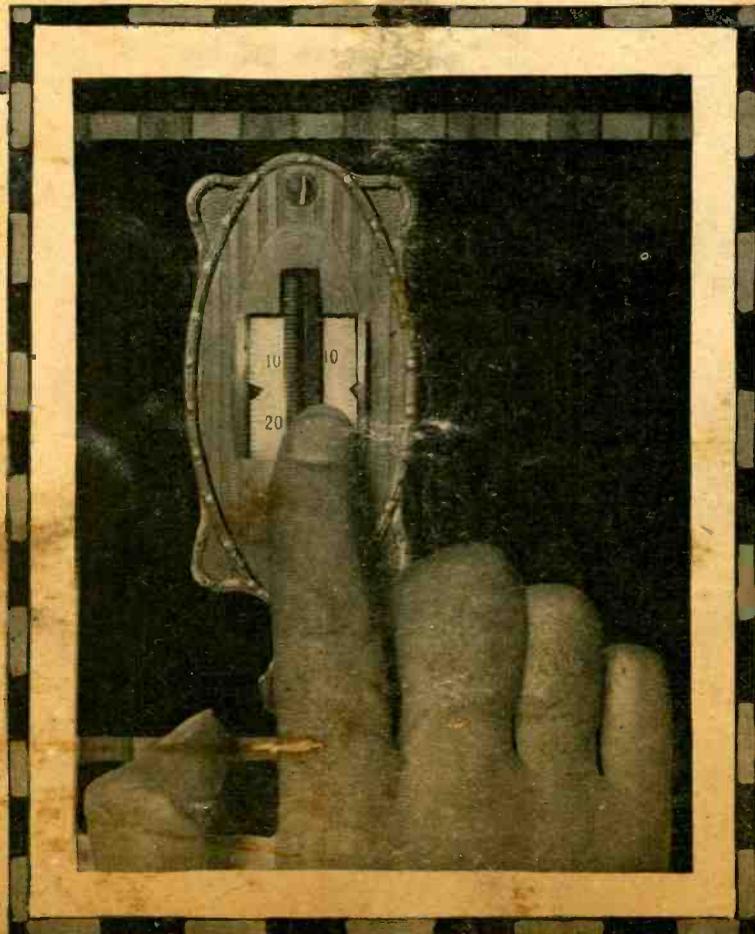

ONE FINGER TUNES BERNARD'S SET—See Page 3

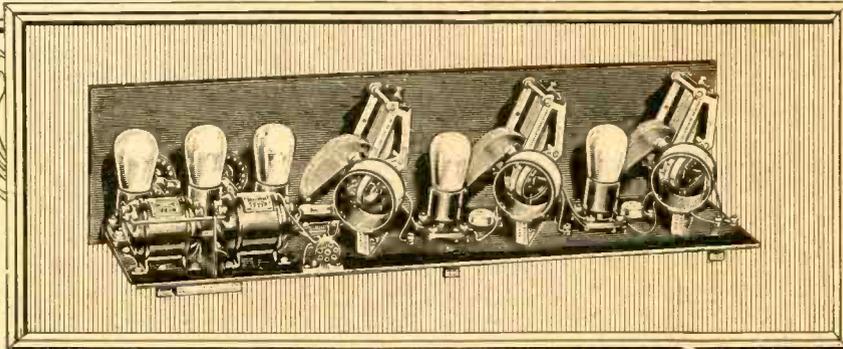Build this Powerful Sweet-tone Receiver. The Karas Equamatic Five Tube Sensation



A Radical Development in Tuned Radio Frequency

THE Karas Equamatic Five Tube Sensation makes it possible for the first time to take full advantage of the amplification factor of your tubes. You can turn the dials from one end of the scale to the other and all stations within range come in with FULL VOLUME. No forcing of tubes at high wave lengths. No troublesome oscillations on low wave lengths. There is no need to touch your rheostats when tuning from one station to another. These results are possible because in the Karas Equamatic System there is always a CONSTANT EQUAL TRANSFER of energy between primary and secondary coils at ALL WAVE LENGTHS from 200 to 600 meters.

How the Equamatic System Works

In the Karas Equamatic System the primary and secondary coils of the R. F. transformers are entirely separated from each other. Each primary is mounted by a special fitting to the extended shaft of the condenser so that it turns with the condenser dial. The secondary coils are attached to sliding standards, and are mounted on the subpanel so that they may be moved toward or away from the primaries. When all coils are properly placed and adjusted the coupling is AUTOMATICALLY varied as the set is tuned, at a rate which keeps the tubes operating CONSTANTLY just below their oscillation point.

A Clear, Powerful Signal on ALL Wave Lengths

The arrangement of coils and condensers and the perfect coupling at every wave length setting eliminates overlapping of electrostatic and electromagnetic fields, and as a result there are no harmful broadening and distorting effects in the Karas Equamatic System. The signals are pure



Karas Micrometric Dial

and clear as those from a crystal receiver. Volume is equal to the usual seven tube set. In addition, there is a sensitivity that rivals a regenerative circuit!

Because all parts work at their highest efficiency, the Karas Equamatic has SELECTIVE qualities not found in any other five tube receiver. Stations snap in and out with remarkable precision.

You Can Build This Set Easily and Quickly

You do not have to be a radio engineer to build the Karas Equamatic and get even better results than we claim. Though you have never built a set before you can build the Karas Equamatic Receiver with the fullest and most complete confidence that you will get the maximum results.

Packed with every set of Karas Equamatic Coils is a complete detailed manual of simple diagrams and instructions showing where to place every part and telling you exactly how to make each connection. In this manual the system is completely described and illustrated.

To build this receiver you will need the Karas parts listed on the coupon, plus other standard parts that you can easily secure.


Order from Your Dealer or Direct

Karas Equamatic parts are carried in stock by reliable dealers in most cities.

If your dealer happens to be out of stock, order direct from us by using the coupon at the right. **SEND NO MONEY.** Just pay the postman the price of the Karas parts, plus a few cents postage.

Karas Equamatic Is Licensed Under King Patents Pending

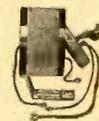
Essential Parts of the Karas Equamatic Sensation



KARAS EQUAMATIC INDUCTANCE COILS are packed three in a carton, and come to you with complete manual of simple diagrams and instructions, all necessary nuts, screws and binding posts, ready for mounting in your receiver.

Price, set of three coils, \$12.00.

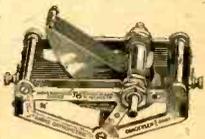KARAS SPECIAL 17 PLATE ORTHOMETRIC CONDENSERS, three of which are used in the Equamatic Receiver, have special extended shafts upon which to mount the primary coils of the Inductances.



Price, each \$7.00.

KARAS HARMONIK AUDIO FREQUENCY AMPLIFYING TRANSFORMERS

are essential to the tone quality success of the Equamatic receiver. Two of these are used for the two stages of Audio frequency amplification. Price, each \$7.00.

KARAS EQUAMATIC RETARD COILS, two of which are used, were designed especially for the Equamatic System. Price, each \$1.00.

KARAS EQUAMATIC SUB PANEL BRACKETS. To insure the necessary exact positions of primary and secondary coils these brackets are essential. Price, set of three, 70c.

KARAS MICROMETRIC DIAL. It has a 63 to 1 vernier and tunes to 1/1000 of an inch. Price, \$3.50.

KARAS ELECTRIC CO., 1147 Association Building, Chicago, Illinois. Please send me a set of 3 Equamatic Inductance Coils, \$12.00; 3 special Orthometric Condensers with extended shafts, \$7.00 each; 3 Micrometric Vernier Dials, \$3.50 each; 2 Harmonik Audio Transformers, \$7.00 each; 2 Equamatic Retard Coils, \$1.00 each; and 3 sub-panel brackets, 70c, for which I will pay postman \$60.20, plus postage, upon delivery. It is understood that I have the privilege of returning any of this apparatus for full refund any time within 30 days if it does not prove entirely satisfactory.

Name
Address
City State
(If cash accompanies order we will ship postpaid.)


KARAS ELECTRIC COMPANY

1147 Association Building
CHICAGO

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under Act of March 3, 1897]

BERNARD

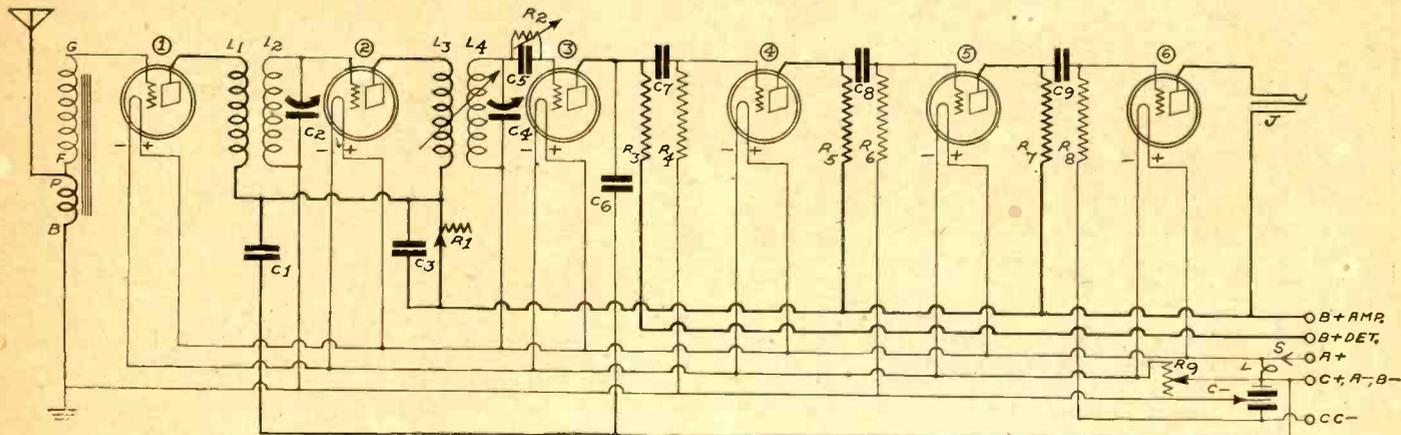A 6-TUBE CIRCUIT
BEAUTIFUL
TO EAR AND EYE



(Design Copyright 1926)

FIG. 1

The Bernard 6-tube receiver, shown in circuit network.

**Tone Quality of Set Excites Hearers to Frenzied Enchantment—
RF Channel Cleared of Distortion and Squealing by Six Points of
Balance, Principal Among Them High Negative Bias, Recom-
mended as Stabilizer for First Time—Drum Type Tuning
Control Used—Only Other Part on Panel is the Switch
—Audio Channel is Metallized Resistance Coupled**

[The complete article on how to construct the Bernard receiver is published herewith. The theory of the set is explained, as well as some points of quasi-construction, followed by full textual wiring directions that enable any one to build this set. No knowledge of radio is required, due to the picture diagram and the careful detail with which the subject-matter is presented by America's most lucid radio writer.]

By Herman Bernard

Associate, Institute of Radio Engineers

(Copyright 1926. All rights reserved)

THE kind of a radio receiver that everyone wants to have is one that not only gives delight to the owner even in his moments of solitude, but which excites visitors to frenzied enchantment and makes them inquire immediately where they can obtain such a set. This aim is easily reached where expense is not so important, but the problem of making available a splendid tone quality receiver within almost everybody's financial reach has not been wholly free of difficulty. Such an opportunity, however, is now presented to those whose hobby is to gather together parts so that with their own hands they can put together a set endowed with quality in every aspect.

Besides the fine, strong, evenly magnified tones that this set can feed to a speaker, an outstanding advantage in any set, and one only lately begun to be appreciated, the result is attained with manual simplicity. All the tuning is done with two drums that actuate the pair of tuning condensers. The device used is the Bruno Unitone, Model 2-CB.

Drum control became available to the

home constructor only this season, and the present receiver is one of the first of consequence to utilize this convenient method. Besides the drums and the ornamental face plate slotted for their manual rotation no part appears on the front panel except the light switch, thus adding a touch of beautiful simplicity to the front elevation. The whole trend in tuning is toward simplicity and this is achieved in the present receiver to a degree almost impossible to surpass without utilizing gang devices that are fraught with possibilities of trouble.

Faithful to the End

As the photographs show, the receiver is an ornament to any home, the beautiful appearance being due in no small degree to the inclusion of a special front panel, made of Lignole, done in walnut, with border of inlay, and matching a Corbett walnut cabinet.

As for electrical performance, the receiver is so faithful to tone values because of the complete balancing of the radio frequency amplifying channel by a method never before presented, so far as I am aware, and by the preservation of this faithfulness through the use of resistance-coupled audio frequency amplification.

Starting from the input, we find that aerial and ground are connected to the primary of a radio frequency transformer of the fixed or so-called untuned type. One primary post is joined to one secondary post, thus converting the coil into an auto-transformer, where PB is the primary and GB the secondary. (Fig. 1). This coil is an Acme R3, and it has an iron core. The transformer is peaked in such fashion that it favors amplification on higher wavelengths in the broadcast spectrum. This serves the triple purpose of flattening out the amplification curve, so that the RF magnification will be more nearly straight line frequency than would be possible otherwise, reducing the tendency of the set toward self-oscillation on the troublesome low waves, and removing the possibility of uneven dial readings or necessity for compensating subterfuges to make up for the uncertainties of capacity effects in the antenna-ground system.

The New Stability Method

It will be noticed that the grids of the two radio frequency amplifying tubes, 1 and 2, are returned to a common C minus lead, and that the B plus amplifier voltage is fed to the plates of these two tubes, except only for the voltage dropped in the variable resistance, R1. This negative grid bias, seldom employed in any receivers in the radio channel, is used as the principal method of stabilization.

It is well known that the grid of radio amplification tubes may be so biased, either negatively or positively, as to reduce the amplification, indeed, even cause the signal to disappear. The positive bias was resorted to a few years ago with

Bias Balances Receiver

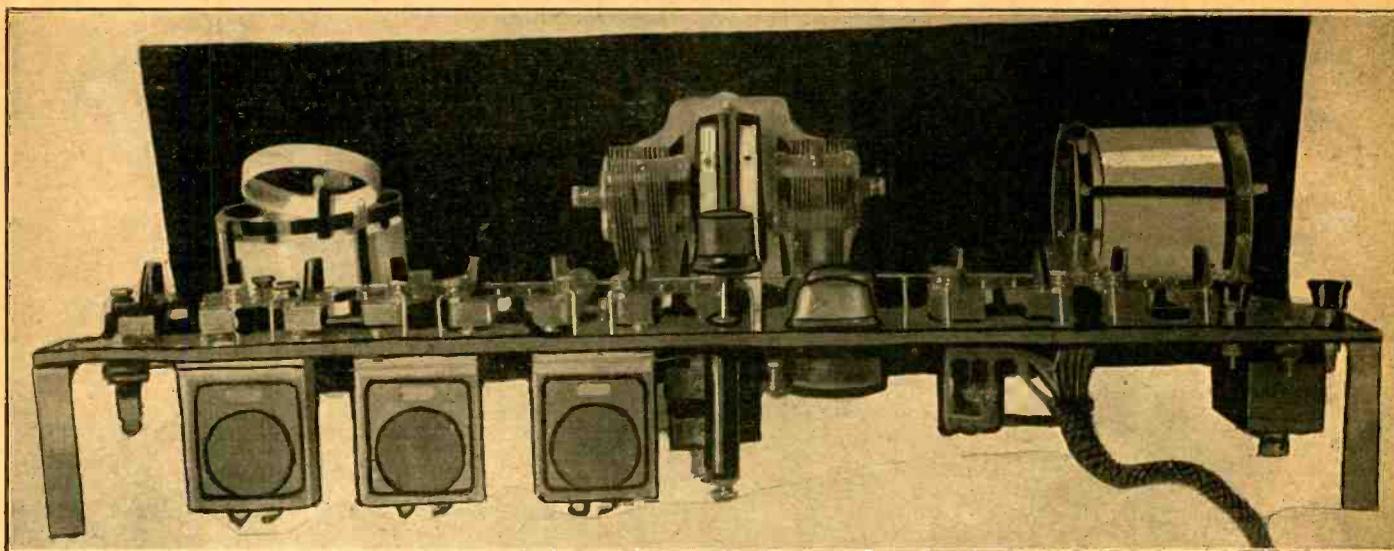


FIG. 2.

The rear view of the receiver shows how the three .25 mfd. condensers are mounted vertically, these being, right to left, C7, C8 and C9. The Bretwood Variable Grid leak with grid condenser is at center, in plain view. The variable resistor, R1, is in the foreground, to the right of the Bretwood, and behind R1 is the rheostat, R9. The battery cable leads are soldered directly to points in the receiver, without going through any terminal strip.

great fervor, a potentiometer being the instrumentality, and in its day it served its good purposes. But the potentiometer was nothing less than a control of regeneration requiring constant adjustment for different wavelengths or degrees of signal intensity. The present method uses a negative bias of a fixed or unvaried kind, and this is the new point.

Why the Extra Bias

The rheostat R9, controlling all six tubes, which are of the 5-volt type, is utilized to drop the one volt necessary from the 6-volt storage battery source. This instrument is not mounted on the front panel, as once it is set there is no need to tinker with it.

The negative bias on the grids of tubes 1 and 2, therefore, is slightly greater than what is theoretically considered most suitable. Tubes used as audio amplifiers will stand a greater negative bias than when the same tubes are used as radio amplifiers, since in radio amplification it is important to operate the tube on the steep part of the grid voltage-plate current chart or characteristic curve.

Now, the negative bias for radio amplifying purposes, and particularly for stabilizing the tube by making self-oscillation utterly impossible on any broadcast wavelength, is rather critical. Since no grid current (DC) is flowing, fine graduations by means of an adjustable series resistance are not possible, for if a rheostat in this lead affected the grid bias to any noticeable extent it would merely prove there was something wrong with the set, possibly the A battery leads were reversed. A potentiometer across a C battery, with grid return to the movable arm, is one workable scheme, but the attainment of exactly the right negative bias this way is delicate and the potentiometer soon drains the battery. The only reason for the variable resistance R1 (Electrad Type F), therefore, is to cut down the plate voltage applied to these two tubes, hence the plate current consumption so that this current exactly matches the 3 or $4\frac{1}{2}$ volts negative bias used for the two grids (the lead marked C— in Fig. 1). Hence nothing critical is encountered in the grid bias—you simply use 3 or $4\frac{1}{2}$ volts.

The greater the negative grid bias, for any given plate voltage, the smaller the

plate current. The drain may be reduced to zero, indeed this is the basis of one form of vacuum tube voltmeter. As we are faced with the practical necessity of choosing negative bias in steps of $1\frac{1}{2}$ volts, since C batteries are made thus, we choose 3 volts, or, if need be, $4\frac{1}{2}$ volts, and stop self-oscillation by turning the knob of R1 until the setting of greatest effectiveness is found. This is simple, for if the negative bias is too much as compared with the plate wattage, the signal strength will be low; if it is too little there will be squeals when one tunes in some stations, particularly on the lower wavelengths, while when it is just right full volume, quiet tuning and almost uniform amplification at radio frequencies will be obtained—without drop in volume on the higher waves, due to GFBP.

It will be noticed that the primary L3 of the coil system connecting the second RF tube to the detector is adjustable. This has some bearing on stabilization, too, but it is included principally as a means of obtaining such selectivity as one's location demands.

If one uses the receiver under such conditions of interference as are encountered in New York and Chicago, for instance, or lives near a powerful local, it will be necessary to move the primary L3 to a position of very loose coupling. This adjustment is finally completed in a few minutes, as the Aero coil primary in this case may be pushed one way or another. Set it as required and thereafter leave it alone. Thus is another control eliminated.

The closer the coupling between L3 and L4 the greater the tendency of tube 2 toward self-regeneration at the lower wavelengths. Hence smaller negative bias would be required in the case of loose coupling, and if tight coupling is preferred any experimental bias voltage may have to be increased. Remember, therefore, the tighter the coupling here, the greater the negative bias should be.

In closing the discussion of elements entering into stabilization one must mention the detector plate voltage and the Bretwood Variable Grid Leak, R2. The plate voltage applied to R6, in the detector circuit, may well be 45, due to the drop in the .1 megohm resistor before the voltage is actually useful on the plate, not to mention the resistance of the plate itself, some 12,000 ohms extra. If 90 volts

are applied here, tendency toward self-oscillation in the detector tube may be experienced.

The Bretwood Variable grid leak is mounted on the sub-panel and is turned to the point of greatest volume, then left alone. The more the plunger is inserted (knob turned to right), the less the resistance.

Points of Balance

Therefore the six points of balance are (1), state of lessened resonance in the first RF tube on the troublesome low wavelengths; (2) negative grid bias, with plate wattage adjustment for simplest achievement of the neutralized state; (3) setting of primary L3, primarily for selectivity as needed, but incidentally a self-oscillation suppresser; (4) setting of the variable grid leak, an over-oscillating detector tube being easily controlled in this way; (5) rheostat setting, this being incidental, as it is intended only to get the proper voltage of 5 on the filaments; (6) detector plate voltage.

Leaving the RF channel, in which the detector tube is included because its input is RF, we turn to the audio amplifier. The resistance-coupled stages are standard, the correct values of resistance being utilized, when the plate impedances are considered and the load on the grids of the respective tubes. The resistors must be of a type that will not materially change in value when the voltage is applied, even if the set is operated for hours and hours on end. That is why the Lynch metallized resistors were selected.

Special attention should be given to the negative bias (CC—) on the grid of the last tube, which should be a 5-volt power tube. It is inadvisable to pay much attention to grid bias formulas as published in the circulars enclosed in tube boxes, as these bias facts, while accurate mathematically, usually have to do with theory or the operation of the tube in a tester, rather than in an actual receiver. You may use the ear test, if you like, especially when you are told that with 135 volts on the plate of the last tube, the negative grid bias may be anything from $3\frac{1}{2}$ to 6 volts, with the chances strongly in favor of $4\frac{1}{2}$.

The Steady Needle

A milliammeter in series with the plate lead of the last tube serves an excellent

High Mu Tubes Add Pep

**Used in First and Second Audio Sockets, While a 5-Volt Power Tube Is Recommended for the First RF Stage and the Final Audio Position—
—Type A Tubes Used in the Other Sockets**

purpose in guiding you. Adjust the bias until the needle fluctuates least on loud signals. If the needle kicks up, reduce the bias. If the needle kicks down, increase the bias. You will find this bias a little bit critical, but select the most suitable post on the C battery.

The coupling-isolating condensers (that couple one audio tube to the next succeeding one, yet serve also to keep the preceding tubes' positive plate potential off the succeeding grid) should be of fairly large capacity in any resistance or impedance coupled audio circuit, and in this instance the Electrad 0.25 mfd. 200-volt bypass condensers were used.

Now, for the tubes. You may be surprised to learn that the tube favored for the first radio frequency stage is a power tube—the type usually marked “last audio stage only.” The reason is that for any given plate voltage the RF amplification is about twice as great as if the A type of 5-volt tube were used, hence you get both radio and audio amplification, since you can not increase the RF without increasing the AF. Higher amplitudes are higher amplitudes, wherever encountered. The effect in the present instance is about the same as if an extra stage of resistance coupling AF were added, and it is strongly recommended that the first socket house a power tube unless your location requires extraordinary selectivity.

Ce-Co Tubes Used

In the laboratory models of the Bernard receiver the tubes finally decided on, after many tests, were CeCo, and the types for the respective sockets follow: 1, type F power tube; 2, type A; 3, type A; 4, type G (high mu); 5, type G; 6, type F power tube. Those who intend to construct the receiver, using such other tubes they have, of the 5-volt variety, will employ a CX312 in the first and last sockets, or UV112, and in the other sockets CX301A or UV-201A or equivalents of these. The two high mu tubes in the audio channel, however, not only increase volume but stand a heavier load. It will be noted that tubes 4 and 5 (first and second AF) take whatever negative bias is made necessary by the balancing of the RF tubes, and this is good practice, since the negative bias is never to exceed $4\frac{1}{2}$.

It will occur to many that a tube that amplifies at radio frequencies much more effectively than some other tube also is likely to introduce over-oscillation trouble, and in receivers not balanced this is indeed a drawback, and makes such tubes great nuisances instead of valuable assets as radio amplifiers. But in our receiver we have a balancing means that spreads in six directions, and we know that we shall be able to operate the set with full volume from highest to lowest wavelength without so much as a squeal emerging from the speaker, an asset that not only commends itself to the unexperienced tuners in the family, but also facilitates

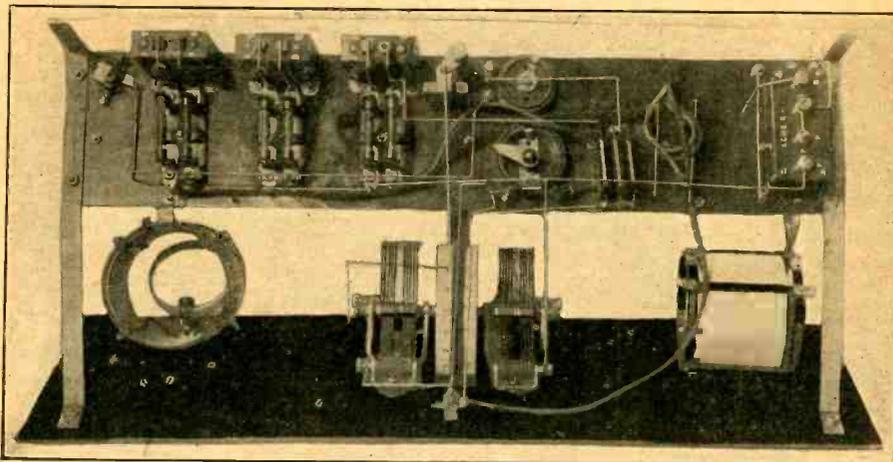


FIG. 3

View of the bottom. The fixed condensers, in the audio circuit, are at left, being, right to left, C7, C8 and C9. The first Aero coil, L1L2, is secured to the sub-panel or socket strip by twisting each of the two mounting brackets that are supplied by the coil manufacturer. Note the A plus battery lead coming direct to the Bruno light switch.

the reception of distant stations, as there is no need of getting rid of a whistle to be able to distinguish what is being said or played. And the orchestra from a far-distant station does not cause the reproduction of noises that sound like thump-thump on a cracked bass drum. Side-band cutting, worst cause of distortion on the radio side, is avoided, stations roll in without screeching the news of their anonymous arrival, and a distortionless audio channel permits real quality to be preserved.

By-Pass Condensers

A few items in the circuit diagram have not been discussed in detail or at all. The fixed condensers C1, C3 and C6 are inserted for by-pass purposes, and may be small because their resistance at any radio frequency will be less than the resistance of the possible sources of losses they tend to remedy—B batteries that have developed high resistance due to use after exhaustion, the damping effect of the high resistor R1, and the RF resistance of R3, in the detector plate circuit. Sometimes when a set loses its selectivity, especially in one stage and not in another, fans often wonder why, and rundown B batteries are likely to be the cause. Even so, if a receiver includes the by-pass condensers, connected from the B plus end of the coils themselves, to A minus or C minus, selectivity often will return, though the battery resistance is higher than it ought to be. Sometimes, too, this resistance is high when the battery has many weeks of useful service ahead of it.

By the way, B batteries, if properly chosen, will last six to eight months, so by marking on your batteries the date of purchase you will be able to judge about when it is time to replenish them, although batteries never should be discarded until actual operating conditions further attest the advisability of replenishment. Though not as convenient as B eliminators, they are more economical, when every item of expense—investment and upkeep—is considered.

S is a switch, lower right in Fig. 1, and L is the flashlight lamp that fits in the special socket on this switch is provided. The instrument is a Bruno light switch and has a red window that glows fascinatingly when the set is in operation. To turn on the switch, turn the window itself strongly all the way to the right and let go. To turn it off simply press against

the window with your finger. This releases a spring and the switch snaps off.

The other Bruno items in the list of parts are the collapsible brackets and the Unitune, Model 2CB. The two drums, two special Bruno .00035 mfd. variable condensers, mounted on a frame, and the embossed bronze panel plate, constitute the 2CB. The variable condensers are .00035 mfd., it will be noted, and not the .0005 mfd., ordinarily supplied with the Model 2-C.

The Bruno condensers are unlike any other on the market, in that the shaft is of special clear Bakelite and is the only means of insulating stator from rotor, the stator being built in the frame, hence rotor plates must go to grid and stator plates to A minus, a rule that applies only to Bruno condensers. The high insulation shaft prevents body capacity effects in receivers prone to produce them, but the present set fortunately is not one of them.

The .00035 capacity is required for the tuned coils in the Bernard, these being Aero radio frequency transformers. One of them, L1L2, has a fixed primary, wound inside the secondary, near the end of the secondary which should go to the C battery lead. This position gives maximum inductive coupling consistent with minimum capacity coupling between the respective windings. Besides, the primary is widely space wound, a most excellent precaution against capacity coupling. Besides, the Aero coils are wound on Bakelite strips, thus having minimum insulation on the form, and represent extreme electrical efficiency.

The output jack is an Electrad single circuit closed jack, for it is well to have such a type here, in case one ever wants to use a power pack in conjunction with the set. Such a pack usually consists of a B eliminator and a stage of power audio amplification. The type of jack shown (J in Fig. 1), enables plugging in just as if it were a double circuit open jack.

The Bernard works on a lamp socket antenna in nearly all instances, and affords fine volume with this convenient form of aerial. No greater volume will be required by most persons, although of course an outdoor antenna does give more volume.

If an outside aerial is used the total length, including lead-in, need not exceed 65 feet. It is advisable to have an outdoor antenna as high as possible.

How to Wire the Bernard

Textual Explanation of the Construction Sets Forth the Progressive Steps in Assembly and Connections — Rotors of the Bruno Condensers Go to Grid, Due to Special Construction

(Copyright 1926 by Herman Bernard)

THE layout of the parts in the Bernard receiver is very orderly, and anybody will find it an easy matter to perform the wiring, either by following the schematic diagram, Fig. 1, on page 3 of this issue, or the picture diagram of the wiring, Fig. 4, if he is a novice. Even an experienced set constructor may find some simplifying points in the picture diagram, since it shows the physical location of the wiring.

Let us take up some of the mounting points first. The front panel, if obtained as part of the official kit, will be completely drilled and engraved, and the bracket holes will be suitable for the new Bruno adjustable brackets. However, the picture diagram shows panel holes and other data for use in case you are trying to accommodate the set to brackets of your own manufacture, hence the 9/64 hole at upper right on the front panel is intended only as a guide to including improvised brackets. The design for home-made brackets is shown at center left in the picture diagram.

The slot for the drum may be drilled oblong, 1 1/4 x 2 3/4, without rounded corners. The official panel, however, has all this drilling already done.

The frame for holding the condensers C2 and C4 and the panel plate, which is bronzed, is mounted on the front panel by means of machine screws held by nuts in the panel rear. The plate holes are two 9/64 one of which is so marked, although both are shown.

The light switch is mounted in a 5/8 hole, which is centered 1 3/8" from the bottom of the panel, in the central line. In following Fig. 4 for panel drilling directions, necessary only in case you are drilling your own panel, remember that the panel is shown as upside down, as it were, this representing the view of the panel when it is folded back, so that you see the rear, with the real bottom seemingly at top.

The picture diagram shows the mounting of the parts that go on the bottom of the socket strip, this view being at top of Fig. 4, while just below are set forth the parts that go on the top of the socket strip. The top view is marked "top" and the bottom view is marked "bottom." Therefore if you follow the layout as given you cannot go wrong, as the dimensions were taken from the laboratory model of the receiver.

Assuming that the panel parts are mounted, as well as the socket strip parts, first wire the filaments.

Connect all F minus posts of all six sockets with one bus. This lead runs on top of the socket strip. All A plus posts of the sockets are joined together with one bus, and this too is atop the socket shelf, although a little farther from the socket posts.

Make the following connections next:

Join the Ant. binding post to the F post of the Acme R3 transformer, GFPB, and join the F and B posts. Connect the B post to ground. G of this transformer is connected to grid of the tube through a hole drilled in the socket strip near the grid post of the socket (1).

Next tackle the coil L1L2. This has its P post connected to plate of tube 1, its B post to one side of C1, its G post to G of socket 2, while F is unconnected for the moment.

Going to the input into the detector tube, the coil system L3 L4 is wired with P to plate, B one side of R1 and to one side of the fixed condenser C3. If only three posts are designated on the coils you can tell the missing one by deduction. G goes to one side of the grid condenser C5 and one side of the grid leak. With the condenser already mounted on the leak one connection takes care of both. The F post of L4 goes to F plus. The other side of the grid condenser-leak is leak soldered to the lug on the G post of the detector socket (3). The plate of detector tube is connected to C6, one of the three fixed condensers side by side on the bottom of the subpanel (Micamold .00025 mfd. each). The other side of C6 is left unconnected for a while.

The Lynch mountings for the audio resistors next are wired.

The nearest terminal to detector plate is connected thereto, while the opposite points on the two other plate resistor clips are jointed together. Each plate lead of each of the three sockets, detector (3) first audio (4) and second audio (5), is joined to one side of a fixed condenser of .25 mfd. capacity, all these being the Electrad 200-volt bypass of that valve. The open sides of the .25 mfd. condensers then are joined to nearest Lynch mounting clips for grid resistors and to the grid of the succeeding tube.

The Filaments Are Wired First, Then Radio and Audio Channels, and the Panel is Next Affixed So That the Variable Condensers and Light Switch May Be Connected

The single closed circuit jack is on the sub panel. The plus post (so marked on instrument) is joined to open side of the plate resistor clip for the second audio tube (5) and the corresponding clip of the previous tube (4), and this lead is carried to the movable arm of the Electrad Royalty type F and to the open side of C3, one of the three fixed condensers. If you can not easily distinguish the movable arm from the stationary post of the Royalty, R1, connect either way.

Now carry the closed sides of the grid resistor clips intended for service in the grids of tubes 5 and 4 to ground.

The front panel and the sub panel now may be joined and the top lead of the Bruno light switch connected to the plus bus wire of all sockets, at any one point. One side of the rheostat R9 is connected to the upper bottom switch point and the other side of R9 goes to the F minus lead of the six Air gap sockets. The free switch point goes to F plus.

Connect the variable condensers. The rotor of C2 goes to grid of tube 2 and stator to ground. The rotor of C4 goes to grid condenser C5 and stator goes to F plus (any socket.) For Bruno condensers rotor to grid is correct.

The open ends of C1 and C6 go to A minus.

Connect the cable leads. Red may be used for A plus and be connected to switch, the corresponding switch contact to the F plus bus of the sockets. The A minus, black, goes to the rheostat at post other than the one connected directly to F minus of tubes. B plus det. is soldered to the open terminal of the detector plate mount, while B plus amp. goes to the Electrad Royalty terminal other than the one connected to coils. CC minus is the lead to the last grid leak, R8, while C minus is the ground lead, connected by cable to any convenient point.

The top should be put on the cable leads at the forked terminals reserved for battery connections.

Connect the coil side of C1 to the corresponding side of C3.

LIST OF PARTS

- C2, C4—Two Bruno .00035 mfd. straight line frequency variable condensers, which, with two drums, mounting frame, bronze panel plate and screws constitute the Bruno Unitune, Model 2CB.
- L1, L2—One Aero fixed primary radio frequency transformer, stock No. WT-40.
- L3, L4—One Aero adjustable primary radio frequency transformer, stock No. AX-45.
- GFPB—One Acme R3 radio frequency transformer.
- R2, C5—One Bretwood Variable Grid Leak with attached grid condenser, .00025 mfd.
- R3, R5, R7—Three Lynch metallized fixed resistors, 0.1 meg. each.
- R4, R6, R8—Three Lynch metallized fixed resistors, respectively 1.0 meg., 0.5 meg. and 0.25 meg.
- 1, 2, 3, 4, 5, 6—Six Air Gap or Eby push type sockets.

- R1—One Electrad Royalty variable high resistance, Type F, range 0 to 2,000 ohms.
- C7, C8, C9—Three Electrad 0.25 mfd. fixed condensers.
- R9—One Electrad 2-ohm semi-power rheostat.
- J—One Electrad single closed circuit jack.
- C1, C3, C6—Three Micamold .00025 mfd. fixed condensers.
- One 7x21" Lignole inlaid walnut front panel, drilled and engraved.
- One Birnbach 6-lead battery cable, with forked terminals.
- Nine Glamco cable tags (one A plus, one A minus, one C plus, one B minus, three C minus, one B plus amp. and one B plus det.)
- Two C. A. L. binding posts (Ant. and Grd.)
- Three Lynch double mountings.
- One pair of Bruno adjustable brackets.
- Ten lengths of stiff Acme Celatsite (vari-colored).


ACCESSORIES

- One 7x21" Corbett cabinet, genuine walnut, with 2" slope for panel.
- One Electrad lamp socket antenna.

- One R. F. I. Balanced Oval cone speaker.
- Five CeCo tubes, consisting of two type

- Type F power tubes, two type A tubes and two type G tubes.
- One Centralab modulator plug.

Picture Diagram of Wiring

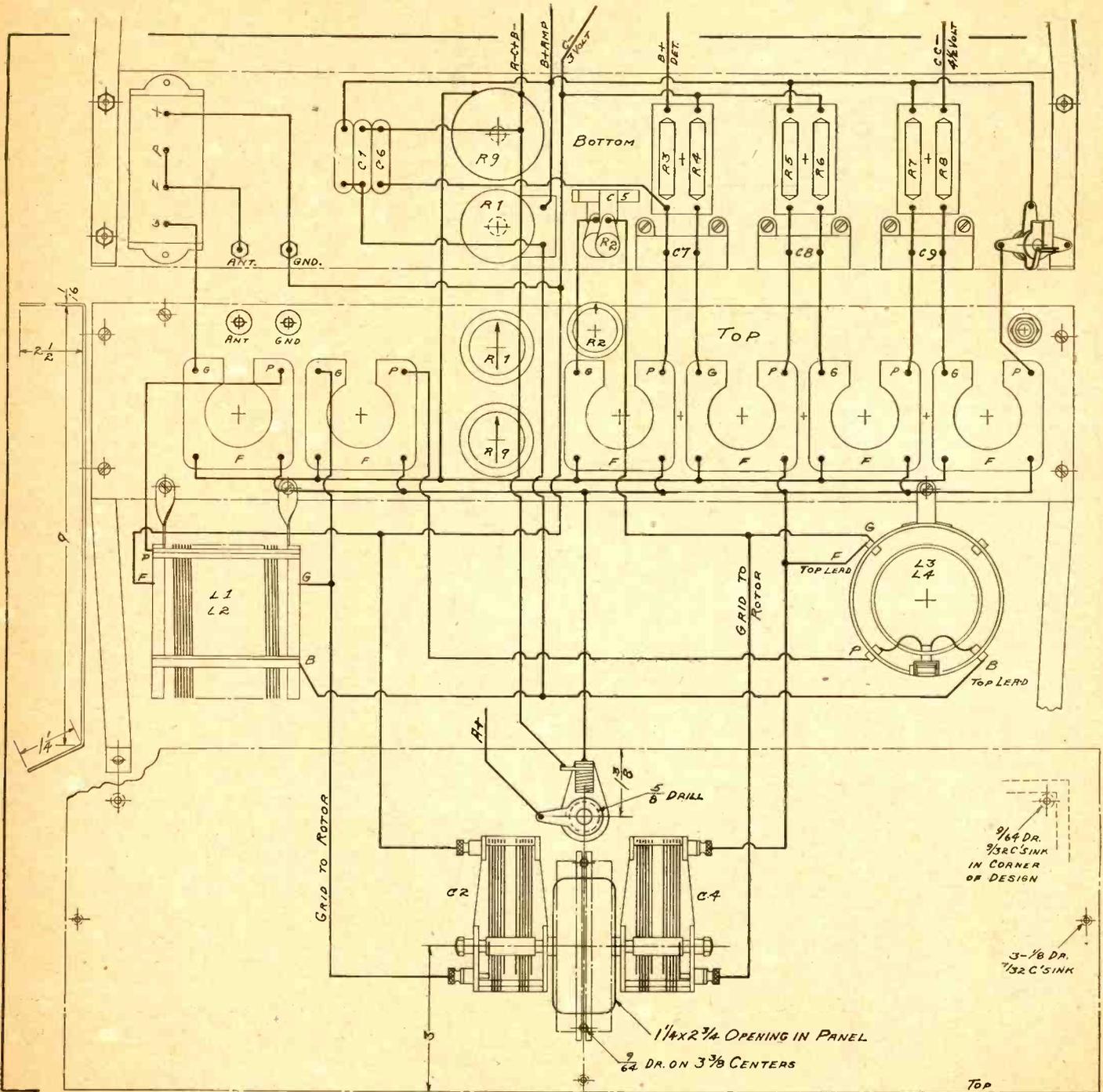

(Design Copyright 1926)

FIG. 4

The picture diagram of the wiring of the Bernard 6-tube set. The subpanel or socket strip is shown in top and bottom views. The panel is shown folded back, so to speak, to align with the upper diagram. The C3 fixed condenser, top left, is unmarked.

“A” Problem Solved By Trickle Charger

Bernard Receiver Draws 2 Amperes, But That Makes No Difference Where the Floating Charge System Is Used—Drain Is Conservative

The use of a 6-volt storage battery, with trickle charger, is very satisfactory in connection with the Bernard receiver.

Under these conditions the storage battery need not be one of high rating in ampere hours. With the periodic charging system

formerly so popular, a receiver like this, which, if a power tube is used in the first RF stage, and the other tubes as specified, draws 2 amperes, nothing less than a 120-ampere-hour storage A battery would be convenient. Otherwise recharging would have to be done too often.

But the trickle charger does away with the necessity of large capacity of the battery, because the trickle charging goes on (at a very, very slow rate) all the while the set is not in use, and does not take place while the receiver is being operated. Hence no wide range of drain is necessary.

If the longest stretch during which you use the set is 5 hours on end, then you would consume 10 amperes. Allowing a 50 per cent. safety margin, the A battery
(Continued on page 8)

Sets Called Best on Music

Background Noises Limit Field for Educational Lectures National in Scope, Says Gernsback, Adding Elimination of Parasitic Sounds Is Engineers' Greatest Task

By Hugo Gernsback

Editor, "Radio News"

IT is well known that, for the past few years, no revolutionary improvements in radio or revolutionary radio inventions have been created. Old, well-triedout, and reliable devices, which have been known to the art for many years, have been perfected gradually; and the development of radio receivers today may be said to follow very much along the same lines as that of the phonograph and the automobile.

It is this process of slow evolution that we may expect in the future, as well, and the old adage also holds true in radio: "Natura non facit saltum"—which, translated, says that Nature does not make jumps. In other words, all developments are part of a slow-moving plan of evolution. Even revolutionary inventions, when they do come along, will be found in the end to be not half as great a departure as they were thought to be at first.

When broadcasting was initiated, the prediction was freely made that radio would soon become a tremendous instrument for the purposes of education. It was foretold, on all sides, that every school would have radio outfits installed, by means of which the pupils would be instructed by lectures from a central place, where some men of great eminence would lecture, so that the classes all over the country would get the same information simultaneously.

Hard to Practice

While this idea is feasible in theory, so far it has not been put into practice; though the question is often asked by many people in all walks of life, "Why is there not more instruction and more education from our big stations?" Let us analyze the problem, and see what really is wrong. We find at once that very few stations today give any great number of lectures. If these are given, they are usually limited to fifteen minutes' duration, and very seldom run much longer. The broadcast directors seem to have acquired from experience the idea that a listener will not stand for longer talks than fifteen minutes; and many directors maintain that even this is too long.

On the other hand, the majority of listeners, when questioned, will tell you that they wish to be entertained, or that, if they do listen to lectures, they tire one too quickly. The latter statement is full of meaning for those who can read the signs aright.

Let us take a typical case. You sit in front of your loud-speaker and listen to a highly instructive, important lecture. Or, if you wish to observe scientifically, try it with one of your friends. Then watch his face carefully, and you will

NEW ADDITION



COLIN O'MORE

Major Edward Bowes, ever on the alert to provide the vast number of radio listeners with the best type of entertainment, has made an important addition to his Capitol Theatre Family in the person of Colin O'More, the popular American lyric tenor. Mr. O'More has done some distinguished work in the symphony and concert field, having appeared with such outstanding organizations as the San Carlo Opera Company, the Schola Cantorum, and several of the large symphony orchestras. The richness of his voice and the warmth of his personality have particularly contributed to his great success as an interpreter of Irish ballads.

Mr. O'More joins Major Bowes' Family in the broadcasting studio to contribute a group of songs of the type with which he has won favor throughout the country.

find that at no time during the lecture is he completely at ease.

Prefer Music

He has to strain to catch the words as they come from the loud-speaker, and very often an annoyed expression will come over his face. You can tell from his features that he is not being entertained. It is really hard work, nowadays, to listen to any lecture, throughout the greater part of the year. There are seasons when it is not quite so difficult; but we must be frank in admitting that during most of the time we would much rather listen to music, for we do not have to strain our attention to follow the motif, as we do when listening to a more or dry lecture.

What is the reason for this? Let us presume that the radio set is not at fault, or, at least, not greatly. Let us also presume that we have a first-class loud-speaker, which reproduces perfectly. Then, what is wrong?

The answer is simple. Turn on your radio set at any time during the evening,

Dispelling the "Mush" Level Will Be Brought About in Next Few Years, Says Noted Editor and Scientist—Cites Tube Noises as Determing Factor to Speech

and set it at a point on the dials where no station is audible. You will immediately notice a background of sound "mush," whose intensity depends greatly upon your location, the season, and many other conditions. If you are located in a great city, all the man-made static in the neighborhood will be collected on your aerial or loop, and will make itself heard in the loud-speaker. Every time some one lifts a telephone from its hook, every time some one rings a bell, runs an elevator, starts his automobile or tunes his radio, every time a trolley car passes by, and from many, many other similar electrical disturbances, a slight noise is produced in the loud-speaker.

Other Noises

Then, too, atmospheric electricity makes itself known by even louder noises in the loud-speaker. Of course, there is not always an abundance of static; but there is always some static electricity in the air, which, even during the best season, makes some impression upon the loud-speaker, loud enough to be heard.

The conglomeration of all these static noises comes out of the loud-speaker at the same time as the reproduced words; and in this fact the present deficiency of radio sets lies. We have no means as yet to stop this so-called static "mush," which blends with the transmitted voice, making it hard for us to understand perfectly the spoken word. The conditions are the same as if some one were speaking in a large room with every one else talking at low voice, making it almost impossible to understand the orator, or possible only with difficulty. At such a time, listening is no longer a pleasure, but becomes hard work.

In the modern radio set, furthermore, we have another producer of disturbing sounds, and that is the vacuum tube; marvelous instrument that it is, the tube is not perfect, for nothing in this world ever can be. The radio tube, due to its inherent sensitiveness, also gives rise to characteristic sounds commonly known as "tube noises." Even without the static "mush" background, there are always noises produced by the tubes themselves.

Tube Noises

Every time a metallic particle is thrown off from an incandescent filament inside the tube, a noise is caused in the loud-speaker. There are various other tube noises, such as those produced by the slight jarring of the building in which the radio set is located, by temperature changes, etc. All of these give rise to some little current impulses, which, being amplified, produce a "noise level" of their own in the loud-speaker.

As long as all of these disturbances prevail it will be impossible to put on lectures that can be enjoyed by a very great number of people. While the imagination has to work hard to supply the miss-

(Concluded on page 26)

Radio Divining Rod Tested

Hope Is Held Out for Successful Location of Hidden Metals in Earth's Bosom for Easy Location of Rich Deposits—Hunt for Gold Goes On As Early Experiments Are Called Satisfactory

By Thomas Stevenson

DISCOVERY of the mythical pot of gold at the end of the rainbow may be accomplished with the development of the radio cameraphone which seeks precious metal deposits below the earth's surface.

In recent years geologists and scientists have been searching feverishly for a method of locating hidden ore bodies. Their hunt has held out greater promise of reward than the search for pirate gold and sunken galleons. To the successful will go fabulous wealth, greater than all of Captain Kidd's treasure.

According to the American Mining Congress there has been a steady decline in the mineral output of several Western states, because known ore bodies are being exhausted more rapidly than new ones are being discovered. The old type of prospectors who roamed over the hills with their burros and dogs have covered the field pretty thoroughly and most of the ore bodies with a visible outcrop have been found.

Much Hidden Riches

Most of the large deposits of the country, however, have never been touched because they are beneath the surface and difficult to locate. No one can estimate the vast quantities of gold, silver and other precious metals awaiting the man who can penetrate the earth's surface and find them at will.

For a number of years the divining rod had a following as a means of locating oil and metals. But it was not long before all but the most credulous lost faith in it and efforts were turned in another direction for a way to seek out the earth's buried treasure.

Since 1924 William A. Sharpe of Denver, has been working on the radio cameraphone, which is his invention. He describes recent experiments as "satisfactory and convincing." The American Mining Congress believes Mr. Sharpe is following the right lead and has given him editorial endorsement.

Mr. Sharpe's cameraphone consists of three units—the radio broadcaster, the receiver and the motion picture camera. The transmitter sends radio waves into the earth, extending to regulated progressive depths, the length of the wave advancing one foot at a time. This radio wave is returned by a closed circuit to the receiver, where the tone pitch of the sound varies according to the mineral, metal or substance at the far terminal of the wave.

The Pitch Varies

Metallic substances produce a much higher tone pitch than any other mineral, and recognizable variations in tone are produced by different minerals. These tones might be described as radio echoes, although they are not so technically. This name, however, is very expressive of



WILLIAM A. SHARPE,
with radio cameraphone, searching for meteor in Northern Arizona and supposedly embedded.

the effect produced, each mineral giving forth its peculiar echo.

The photographic unit of the radio cameraphone is fitted with a vibratory illuminated thin metal foil about 1" square, suspended by a fine hair spring in contact with the diaphragm of the telephone mechanism in the radio receiver. The illumination of this foil is reflected in a magnifying mirror that intensifies it 30 or 40 times, so that the tiniest vibration is caught.

The reflected light of the foil in the magnifying mirror is thrown on a ground glass screen, the vibrations appearing as lights and shadows, and these are photographed by a regular motion picture camera which is automatically exposed. One picture is taken with each foot of advancement in the radio wave length and the photographic film developed from these exposures may then be thrown on a screen by a regular motion picture projecting machine.

Metals Almost Violent

The radio cameraphone has been perfected from a similar instrument designed to locate oil and gas pools. The detecting of different densities and compositions in rock beds, earths, fluids and gasses proved a delicate undertaking and innumerable tests were required to learn how each

mineral and compound reacted on the instrument.

Mr. Sharpe found that metallic substances behave in a positive and almost violent manner toward the instrument. A most illuminating demonstration was obtained when the radio camera photographed the steel beams of the seven floors of a Denver office building with great clearness.

One of the most interesting accomplishments of the radio cameraphone was the location of a mysterious meteor which buried itself in the earth centuries ago at Meteor Crater in Northern Arizona. Although many fragments of the shooting star were scattered for many miles around the crater, the large iron core that tore the hole had never been found.

Instrument Responds

Shaft sinking and drilling were fruitless but pictures taken by the radio cameraphone showed that the iron body of the meteor lay 100 feet south of the rim of the crater, and at a depth of 1,410 feet. This showed that the meteor had hit the earth at an angle.

Another important test was made in the Gold Dust section of the Las Animas mining district in southwestern New Mexico. The mineralization there con-

(Continued on page 27)

HAS GIANT RECEIVER



(Keystone View)

H. P. HAYES, extreme left, noted Boston radio engineer, is the designer of the the gigantic receiver shown above, which is valued at \$3,500. Eight months were spent in designing this receiver, while two months were spent in the construction. Five different tuning bands, from 35 to 20,000 meters, without the change of coils, are covered.

New Chain Effected; WGBS, WIP, WPG

Two Gimbel Bros. Stations Permanently Hooked Up With Atlantic City Broadcaster—May Add WCAE, Pittsburgh, to List

A PERMANENT hook-up has been inaugurated between the two Gimbel Brothers stations, WGBS in New York and WIP in Philadelphia. Later, WPG, Atlantic City, was added to them, forming the nucleus of a permanent chain broadcast.

Gimbel Brothers has been a pioneer in the development of radio. WIP, in Philadelphia, has been established for four years, during which time it has sent out on the air many events of importance, such as sporting events from Franklin Field, the University of Pennsylvania, etc. The station has recently been considerably enlarged, both as to staff and equipment.

A little less than two years ago WGBS began its operations in New York (although Gimbel Brothers had been broadcasting for two years before) leaping at once into the front rank of broadcasters with a stellar program which superseded any single program that had even gone out in the air prior to that time. Eddie Cantor, as master of ceremonies on that all-star night, made his radio debut at that time; other celebrities who participated included "Bugs" Baer, Harry Hershfield, Fannie Hurst, Louis John Bartels, Cliff Edwards, George Gershwin, Edythe Baker, Rudolph Friml, and others too numerous to list here.

Only several days after the gala pre-

miere, WGBS did the impossible—the broadcasting of "The Miracle" from the Century Theatre. This was hooked up with WIP, by the way. Experts had said the beauty of Morris Gest's spectacular production would be lost in an air presentation; the verdict of the thousands who heard it, however, was that it was one of the most beautiful things that had even been their privilege to listen to.

Later came the broadcasting of a specially devised entertainment staged on board the gigantic liner, S.S. Leviathan, the first time a program had been broadcast from a ship. This was done primarily for the purpose of experimenting in the radioing of programs to ships at sea and was extremely successful, for reports were received from many transatlantic boats far out in the ocean that the program was heard clearly.

Another unusual experiment was the broadcasting of a musical program from the Sikorsky airplane, which has figured in the news of late as the one that was to attempt to cross the ocean. Programs were picked up without difficulty by listeners in New York, Atlantic City, Baltimore and Washington as the airplane flew over those cities. Thus, WGBS was the first station to broadcast entertainment from the air.

While the antennas and operating plant were originally located atop the Gimbel

Brothers store at Broadway and 33rd street, New York, WGBS engineers conducted experiments over a period of six months to find the most suitable point for sending out the programs. An automobile with portable broadcasting set made a thorough tour of the Metropolitan area and selected a site in Astoria, Long Island, opposite 90th street, Manhattan, as the most desirable spot. The towers and power plant were moved there and now the programs are sent via landwire from the Gimbel studio at 33rd street to Astoria.

Plays have been given particular attention by the WGBS staff and Dailey Paskman, director of the station. Mr. Paskman, associated with the theatrical world before his entry into radio, has been responsible for the development of the radio drama. A highly successful prize play contest was held last year, in which plays were submitted from all parts of the country—plays written expressly for broadcasting in the air theatre.

Mr. Paskman has originated the particular type of radio play which is known as the music drama; he makes the musical setting or background an integral feature of the many plays broadcast from the Gimbel studio with professional players of wide repute, including Howard Kyle, Charlotte Walker and others. Likewise, he has dramatized the lives of many of the world's greatest composers—Beethoven and Mozart—presenting plays around these interesting figures with their own works played throughout the action.

All these features which are to be continued during the season, which will also probably see the introduction of many new and novel events on the air, are thus to be given a wider audience with the hook-up with WIP, increasing the area of listeners.

From Philadelphia will be heard many musical events, programs from the Metropolitan Opera House there, by the San Carlo Opera Company and other groups, symphony concerts, including the Philadelphia Symphony Orchestra and features from the Sesquicentennial, now in progress.


This hook-up does not merely mean that New York programs will be broadcast through a Philadelphia station, but that features of interest from other cities will be brought to the Metropolitan audience.

Gimbel Brothers have recently acquired the Kaufman and Baer Store in Pittsburgh, Pa. The Kaufman & Baer Store operates station WCAE. WCAE is another station belonging to the Gimbel Brothers' group, but at this time is not being included in the chain. However, these are three broadcasting stations that are controlled by Gimbel Brothers.


WGY Aids Many

WGY is proving a valuable training school for radio announcers. Occasionally listeners twisting the dials may discover a familiar WGY voice, coming from a wholly unexpected quarter and on wavelengths far removed from that of the Schenectady station. A few months George Markham, formerly in charge of the agricultural hour at WGY, left to become general manager of WDBO, at Winter Park, Florida.

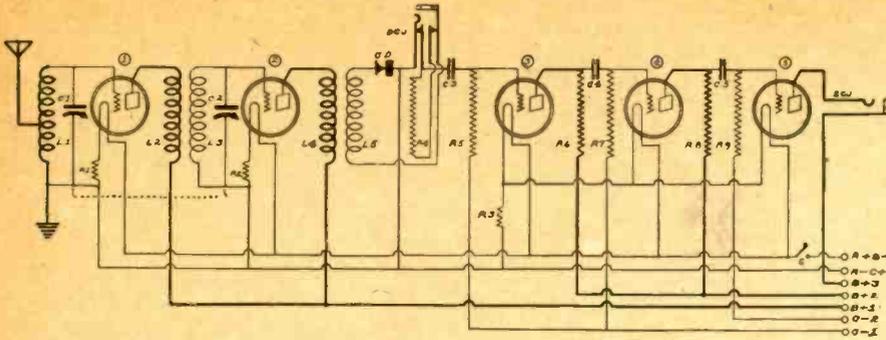
Now Witter T. Cook, a graduate of Massachusetts Institute of Technology, more recently an announcer of WGY and one of the WGY Players, has accepted a position with the air forces of WDAE, at Tampa, Florida. Cook has a voice that is chockful of inflections and he can make the reading of a market report a thing of beauty and delight to the ear.



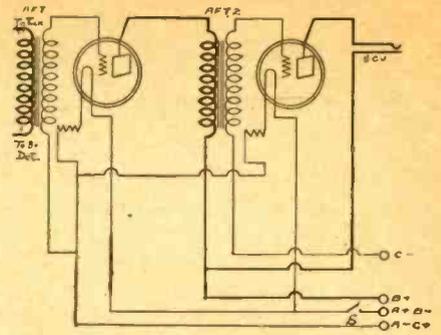
A 5-TUBE quality receiver, employing two stages of tuned radio frequency amplification, a crystal as a detector and three stages of resistance coupled audio frequency amplification. An untuned RFT is used to couple the RF output to the detector input. Ballast resistors are used throughout for filament control.



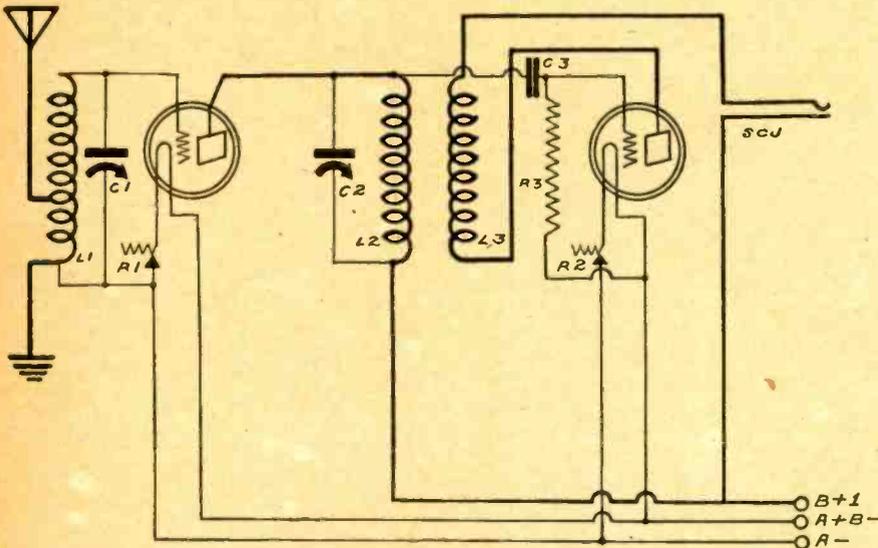
THE SCHEMATIC diagram of a 2-stage transformer coupled AF amplifier, with the proper connections for the installation of a power tube. The "To Tick" connection may go to the tickler post in detector plate circuit or to only the plate post of detector tube. Ballast resistors control the filaments of both AF tubes. Note the C battery connection.



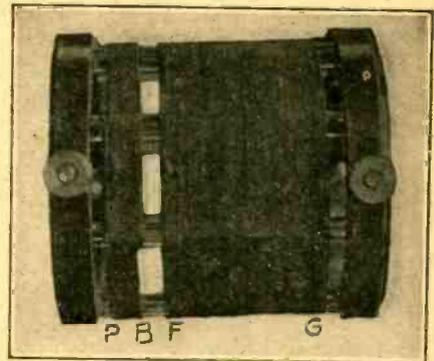
THE ELECTRICAL diagram of a 2-tube receiver, employing a regenerative RF and detector tube. This set is quite critical, but will give excellent results when properly controlled. Impedance coupling is used.



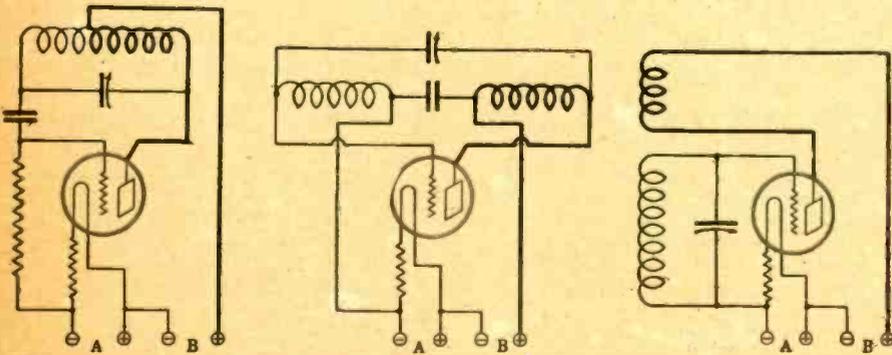
HOW TO wire up a standard tuned radio frequency coil is clearly outlined in the above photograph. P equals plate; B equals B plus; F equals A minus or plus and G equals grid. Note that B and F, the low potential points, are kept together.



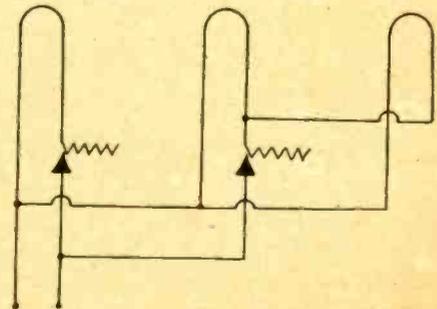THREE POPULAR oscillator systems, employed in Super-Heterodyne. The most stable of the three is the 3-circuit tuner, shown at the right.



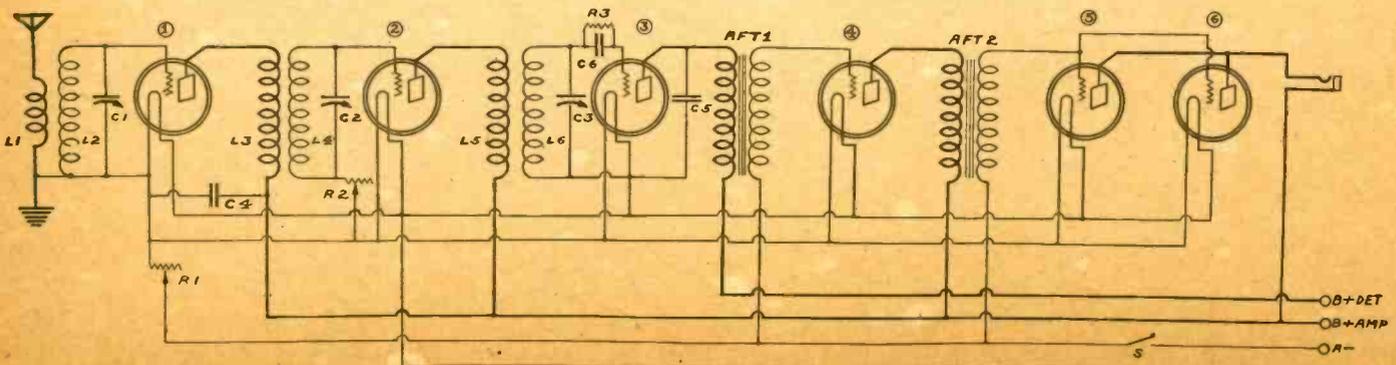THE ABOVE electrical diagram shows how to connect up one rheostat to control the filament of the detector tube and another rheostat in a 2-stage audio amplifier circuit, for filament control.



A 6-TUBE TRF receiver. Transformer AF coupling is used. Two tubes are used in the last AF stage, so that the output is balanced and free of distortion. A single rheostat is used to control the filaments of all the tubes.

Radio University

A FREE Question and Answer Department conducted by RADIO WORLD for its yearly subscribers only, by its staff of Experts. Address: Radio University, RADIO WORLD, 145 West 45th St., N. Y. City.

When writing for information give your Radio University subscription number.

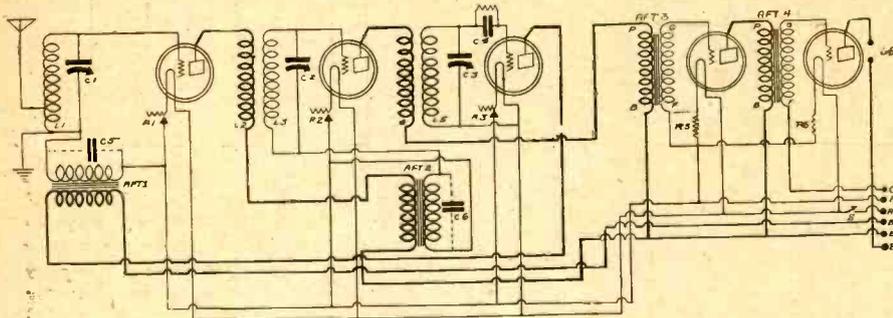


FIG. 443

The circuit diagram of the 5-tube reflex, from which results equal approximately to a 7-tube receiver are obtained. The broken plate lead in the det. circuit is not intended.

I HAVE one 6 to 1 ratio AFT and three 3 to 1 ratio AFT. Please give the circuit diagram of a 5-tube receiver using these parts and whatever else is necessary. I wish to use -01A tubes all through, except in the last stage of audio frequency amplification, where I would like to use a power tube (-112 type). I also have .0005 mfd. variable condensers, which I would like to use. The electrical data on all other parts would be appreciated.—Arthur Roberts, Glenn Cove, L. I., N. Y.

The circuit diagram of such a receiver is shown in Fig. 443. You will note that the first and second tubes act both as radio and audio frequency amplifiers. AFT1 is the 6 to 1 ratio audio frequency transformer. AFT2 is one of the 3 to 1 ratio audio frequency transformers. The other two 3 to 1 ratio audio frequency transformers are used in the regulation transformer stages. The antenna coil L1 consists of 65 turns, tapped at the 10th turn. This is wound on a 2 3/4" diameter tubing, using No. 24 double cotton covered wire. The primaries, L1 and L3, consist of 10 turns. The secondaries, L2, L4, consist of 55 turns. Each primary and secondary is wound on a separate tubing, which is 2 3/4" in diameter. No. 24 dcc wire is used in both cases. A 3/4" space is left between the two windings. The filaments of the RF-AF and detector tubes are controlled by 20 ohm rheostats. C1, C2 and C3 are the .0005 mfd. variable condensers. R5 is a 1/4 ampere ballast resistor. R6 is a 1/2 ampere ballast resistor for the power amplifier tube. C5 and C6 are .001 mfd. condensers and as indicated by the dotted lines are experimental. C4 is the .00025 mfd. grid condenser. The grid leak is of the 2 megohm type. The output connections are made via binding posts or phone tips, and indicated on the diagram by LS. The plate of the detector tube receives about 45 volts. The plates of the RF-AF tubes receive 90 volts. The voltage to be applied to the plate of the power tube should be noted on the carton. S is the filament switch. Place AFT1 and AFT2 at right angles so that there is no coupling between the two. The antenna coil should be placed horizontally, the first RF coil perpendicular and the last RF coil at an angle.

IS THE detector circuit of the reflex shown in Fig. 442, Radio University columns, Oct. 9 issue of RADIO WORLD, wired for the -00 or -00A type tube? I note that the grid return is to A minus.—Tom Rogers, Los Angeles, Cal.
Yes. If you wish to use the -01A tube, the grid return is to the A plus.

I HAVE some 2 3/4" diameter tubing and some No. 24 dcc wire. Please give the electrical data of the coils used in the 5-

tube receiver, shown on page 9 of the July 17 issue of RADIO WORLD, using these tubings and wire. What capacity condensers should I employ?—Frank Werner, Boston, Mass.

The primaries consist of 10 turns. The secondaries consist of 80 turns. This secondary is for the .0005 mfd. variable condensers. If you wish to use .00035 mfd. variable condensers, then the secondaries should consist of 95 turns.

I AM building a battery table and would like to get the approximate size of the cabinet portion. I wish to place an A battery (100 ampere type), A charger, and three large upright 45-volt B batteries inside.—Clark McDonough, Atlanta, Ga.

The cabinet portion of the table should be approximately 31" wide, 17" high and 15" deep. This will allow ample space for the articles you mention.

WHEN DID Prof. L. A. Hazeltine receive his patent on neutralization? (2) When were the first licenses issued to broadcasting stations? (3) In what year did constant radio communication between Japan and U. S. go into effect? (4) Where were the terminal stations located?—Larry Mason, Pittsfield, Mass.

(1) 1923. (2) Sept., 1921. (3) July, 1915. (4) The terminal stations were located at San Francisco, Cal., and Funabashi, near Tokio.

PLEASE GIVE the values of the rheostats to employ, when using from 1 to 8 -01A type tubes, on a 6-volt battery. (2) Please give the values of the rheostats to employ, when using from 1 to 4 -112 type tubes, from a 6 volt battery.—Dave Martens, Rocky Mount, Mo.

(1) For one tube, use a 20 ohm rheostat; for two tubes, use a 10 ohm rheostat; for three and four tubes use a 6-ohm rheostat; for five and six tubes, use a 3 ohm rheostat and for seven and eight tubes, use a 2 ohm rheostat. In each case the resistance wire must be heavy enough to pass the current, e.g., the 3 ohm rheostat should be able to pass 1 1/2 amperes, etc. (2) For one tube use a 10 ohm rheostat; for two tubes, use a 6 ohm rheostat; for three tubes, use a 3 ohm rheostat and for four tubes use a 2 ohm rheostat. Again the wire must be heavy enough to pass the proper current.

I HAVE a 50,000 ohm variable resistor. I would like to connect this up, so that it will control the volume output of my set. How can this be done?—Jack Barrett, Turner, Ia.

This can be connected at the speaker output terminals. That is, one terminal of the resistor should be connected to the

plate terminal of the last tube, while the other terminal should be connected to the B plus amp. post. Both these terminals are already connected to the speaker.

WHAT IS .0025 megohms equal to? (2) What is .05 megohms equal to? (3) What is 400,000 ohms equal to? (4) What is 6,000,000 ohms equal to? (5) What is 2.5 megohms equal to?—Walt Clifton, Jersey City, N. J.
(1) 2,500 ohms. (2) 50,000 ohms. (3) .4 megohms. (4) 6 megohms. (5) 2,500,000 ohms.

I HAVE three 50 turn honeycomb coils. Can these be used as L1, L2 and L3 in the 5-tube receiver shown on page 9 of the Sept. 4 issue of RADIO WORLD? (2) What capacity variable condensers should be employed?—Roy Namm, Hutton Valley, Mo.

(1) Yes. (2) Use .0005 mfd. variable condensers.

IN SOME circuit diagrams of single tube regenerative receivers using the tuned plate and tickler systems, the grid leak is run to the A plus, instead of across the condenser, as is usually done. Are the results any better, if this method is used?—Carol Kingle, Redford, N. Y.

The results will be the same.

I HAVE a double condenser, each section having a capacity of .0005 mfd. which I would like to use in the 7-tube receiver, described in the radio university columns of the Sept. 11 issue of RADIO WORLD. Instead of using three stages of tuned RF amplification, I would like to use two stages. Can this be done, using the double condenser? How?—Gerald Green, Conway Springs, Kans.

Yes. The double condenser should be connected in the second RF and detector circuits; stators going to the ends of the secondaries, while the common rotor goes to the beginnings of the secondaries. The single condenser is connected in the secondary circuit of the first RF circuit. The antenna, ground and rheostat connections are made in the same manner as per original diagram.

I HAVE two .00025 mfd. variable condensers. Please give the constants of the coils for the set shown in the Radio University columns, Fig. 418, Aug. 28 issue of RADIO WORLD.—Robert Hamrard, Adams City, Col.

Using a 3" diameter form, the secondaries consist of 65 turns. The primaries consist of 10 turns. Use No. 22 double covered wire. Allow a 3/4" separation between the windings.

I AM building the old type Harkness reflex, described in the May 15 issue of RADIO WORLD, Radio University columns. The text states that the coils should be mounted on the end plates of the variable condensers. I find that if the coils are placed in this manner, they would hit the tops of the tubes, this being due to the narrowness of the cabinet. Could these coils be placed directly on the baseboard at right angles to each other? The leads to the condensers will only be 3" distant.—Wilbert Donald, Havana, Cuba.

Yes, this can be done. Be sure that the coils are at right angles to each other, with the center of the secondary winding of one coil facing the circumference of the other coil.

I HAVE two tuned radio frequency transformers and a 3-circuit tuner. The primaries on each of the coils consist of 10 turns. The secondaries consist of 40 turns. Each primary and secondary is wound on 3 3/4" diameter tubing, using No. 22 dcc wire. The tickler consists of 30 turns of No. 26 SSC wire, wound on a

1 3/4" diameter tubing. Could these be used in the Crosley 5-38 receiver shown in an electrical diagram on page 11, July 31 issue of RADIO WORLD?—Henry Stone, West Point, N. Y.
 Yes. Use .0005 mfd. variable condensers.

I HAVE two 3 to 1 ratio audio frequency transformers. Can these be used in the 2-tube reflex, shown on page 15 of the Aug. 28 issue of RADIO WORLD.—Edward Marret, Clinton, N. Y.
 Yes.

I HAVE a piece of galena crystal. Can this be employed in the quality receiver shown in the Radio University columns of the May 29 issue of RADIO WORLD?—Harry Mertens, Los Angeles, Cal.

Yes. However, if the input signals are too strong, it will burn out. A fixed or synthetic crystal would give longer service. The strength of the signals with the latter at the output will not be as loud as with the galena, but you will be assured of more steady reception.

IN THE Sept. 18 issue of RADIO WORLD, page 13, there appeared a circuit diagram of a 3-tube reflex, using a non-regenerative detector. Would you please give me detailed information regarding the type of coils; capacity of the variable condensers; size of rheostats; capacity of condensers, C5 and C6; ratio of the two audio frequency transformers and the resistance of P. (2)—What is SCJ? (3)—Please state the respective markings or method of wiring up the radio frequency transformers.—F. J. Jones, Los Angeles, Cal.

(1)—L1 is a continuous winding antenna coil, consisting of 50 turns tapped at the 8th turn, wound on a tubing 3" diameter, using No. 22 dcc wire. L2 and L4, the primaries of the RFT, consist of 10 turns. L3 and L5, the secondaries, consist of 45 turns. These are wound on the same tubings as their respective primaries, on a 3" diameter tubing, using No. 22 dcc wire. Allow a 1/4" separation between the primary and secondary windings. R1, R2 and R3 are 20 ohm rheostats. Both audio transformers are of the 6 to 1 ratio type. P is a 400 ohm potentiometer. C1, C2 and C3 are .0005 mfd. variable condensers. C5 and C6 are of the .001 mfd. fixed type. C4 is a .00025 mfd. grid condenser. R4 is a 2 megohm grid leak. (2)—SCJ is a single circuit jack. (3)—The beginning of the antenna coil goes to the G post of tube 1. Tap goes to the antenna. End of coil goes to ground. Beginning of L2 goes to plate post of tube 1. End of winding goes to top spring on DCJ. Beginning of L3 goes to rotary plates of C2 and to G post on AFT2. End of winding goes to G post on tube 2 and stationary plates of C2. Beginning of L4 goes to plate post on tube 2. End goes to top spring of SCJ. Beginning of L5 goes to rotary plates of C3 and to A plus. End of winding goes to stationary plates of C3 and one terminal of C4 and R4.

I HAVE a fixed radio frequency transformer, marked 150 to 600 meters, which I would like to use in the Federal type 59 receiver shown in the Aug. 14 issue of RADIO WORLD, page 13. I also have a tuned RFT, having a 20 turn tapped primary and a 50 turn secondary, both of which are wound on a 3" diameter tubing. No. 22 dcc wire is used. Could these be used? (2) What capacity variable condensers should be employed? (3) What is the resistance of the potentiometer? (4) Will the -01A type tubes work successfully here? (5) What is the resistance of the rheostats? (6) What is the ratio of the AFT? (7) Are DCJ1 and DCJ2 double circuit jacks? (8) Is C3 a .00025 mfd. grid condenser? (9) What value is R5?—John Rand, Pittsburgh, Pa.
 (1) Yes. (2) C1 should have a capacity of .0005 mfd., while C2 should have a

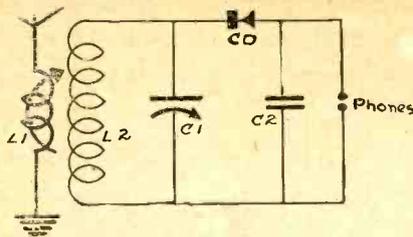


FIG. 444

The circuit diagram of an efficient crystal receiver.

capacity of .00004 mfd., (midget type). (3) 400 ohms. (4) Yes. (5) 20 ohms. (6) AFT1 is a 3 to 1, while AFT2 may be a 3 to 1 or higher ratio. (7) Yes. (8) Yes. (9) 2 megohms.

I HAVE an antenna coupled, with a variable primary. This consists of 20 turns, wound on a 2" diameter tubing. The secondary is wound on a 3" diameter tubing and consists of 65 turns. The wire seems to be No. 24 double cotton covered. The primary is placed inside of the secondary winding, at the end of the winding. I have a fixed crystal detector also. Could I have a circuit diagram of a crystal receiver, using these parts. What capacity variable condenser should I place across the secondary?—Manny Jules, Milwaukee, Wisconsin.

A receiver using these parts is diagrammed in Fig. 444. L1 is the variable primary, while L2 is the secondary. C1 is the variable condenser and is of the .00025 mfd. type. C2 is the .001 mfd. fixed condenser, while CD indicates the crystal detector. The phone connections are indicated at the word "phones." This receiver should give excellent results. The variable primary aids the receiver's selectiveness.

PLEASE SHOW how to connect a

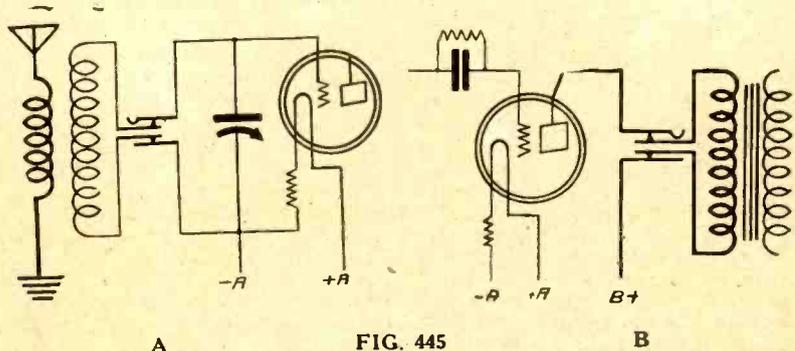


FIG. 445

The electrical diagrams illustrating the proper methods of hooking up double circuit jacks, for use in the antenna-loop circuit and in the detector output.

double circuit jack, so that a loop or an antenna may be used interchangeably. Explain method of connection, (2)—Please show how to connect a double circuit jack at the detector output. Explain connections.—Gilbert Stram, Tulsa, Okla.

(1 and 2)—Fig. 445 show both methods of connection. In A, we have the loop-antenna method illustrated, while in B we see the detector output method. As to the loop-antenna. The beginning of the secondary of the RFT is connected to the second spring from the frame. The end of this winding is brought to the third spring from the frame. The top spring is connected to the stationary plate terminal of the variable condenser and to the grid post of the socket. The frame terminal of the jack is brought to the rotary plate connection of the variable condenser and to the A minus battery post. Be sure that the coil connections are connected to the inner terminals of the jack, also that the proper potentials are kept. As to the detector output connections. The plate post of the detector tube is brought to the top terminal or fourth spring from the frame of the jack. The second spring from this terminal is connected to the P post on the AFT. The next spring is brought to the B post on the AFT, while the last terminal or frame is connected to the B plus detector voltage. It will be noted in both cases that the inner terminals of the jacks are connected to windings.

WILL AN indoor antenna about 60 feet in a straight line, give results equal to an antenna the same length out of doors, on a Super-Heterodyne?
 Yes, for local reception.

HOW MUCH filament current does the CX300A draw at 5 volts at the terminal?—Numan Rogers, Dillard, Ga.

This tube draws .25 ampere, the same as the -01A type.

Join RADIO WORLD'S University Club

And Get Free Question and Answer Service for the Coming 52 Weeks
 This Service for Yearly Subscribers ONLY

Have your name entered on our subscription and University lists by special number. Put this number on the outside of your forwarding envelope (not the accompanying return stamped envelope) and also put at the head of your queries. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University. NO OTHER PREMIUM GIVEN WITH THIS OFFER.

[In sending in your queries to the University Department please paragraph them so that the reply can be written under or alongside of each query. Write on one side of sheet only. Always give your University number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for RADIO WORLD for one year (52 Nos.) and also enter my name on the list of members of RADIO WORLD'S University Club, which gives me free information in your Radio University Department for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State

EXPERTS REFUTE EDISON

Noted Inventor's Statement That Radio Music is Distorted, and Not to Be Compared with Phonograph's, Answered by Goldsmith, Free, Lynch and Others

[Thomas A. Edison, the great inventor, said: "Music on the radio is very poor because it is distorted. The chief difference between the radio and the phonograph is in distortion." Herewith are published statements answering Mr. Edison's charge.]

By Arthur H. Lynch

Former Editor, "Radio Broadcast"; noted designer, author and parts manufacturer


It was with a great deal of surprise that radio engineers observed the statements made by Mr. Edison that the reproduction by radio is inferior to the reproduction of music by the phonograph. To make such a statement regarding either art without fully explaining the basis on which the statement is made hardly seems fair.

While it is perfectly true that a modern phonograph is capable of reproducing music with great volume and fidelity, it is also true that this same volume and same fidelity is possible by radio. In fact, nearly all of the more recent developments in phonograph engineering which have made the newer type of phonograph possible are the result of scientific investigation carried out in radio and other electrical laboratories. The modern phonograph is an entirely different sort of contrivance from the phonograph of yesterday. The best phonograph reproduction now comes from a film rather than from a record of the usual character. Without going into a long technical discussion of this subject we think it but fair to radio to call to Mr. Edison's attention the fact that once the recording has been finished, the fundamental system of amplification and reproduction in a modern phonograph are identical to those used in radio and most of these fundamentals have been adopted by the phonograph companies after their use has been proven satisfactory in radio laboratories.

From a scientific viewpoint there are many more obstacles to overcome in the development of a perfect phonograph than there are in a perfect radio receiver, and these problems have been mastered to a surprising degree by the technicians who work in both arts. It is very doubtful that the average person would be able to find any difference whatever between the reproduction of the latest type phonograph and the latest type radio receiver, and it is equally true that even scientific measurements of the difference in this reproduction would show discrepancies very little in favor of one over the other.

It is most unfortunate that Mr. Edison, enjoying the reputation and confidence he does should at the beginning of

SOME IRONY

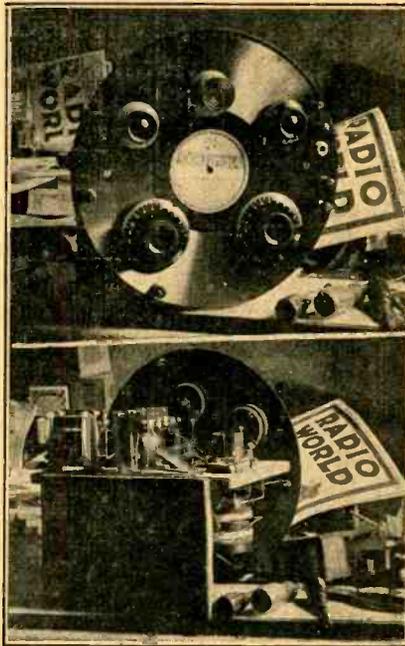

ANENT the phonograph-radio controversy, behold the radio set made on a phonograph record as a panel, by W. F. Innis, 1218 Belgrade Street, Philadelphia, to prove what he prefers. Mr. Edison's defense might be it was not an Edison record!

the radio season make such an unwarranted statement.

There is a real place in the modern home for both the latest type phonograph and the radio. Each offers a service which cannot be supplied by the other. In their present state of development, both are extremely satisfactory, and because of the recent developments which have been applied to both radio and the phonograph, the business done during this season by each of these branches of the acoustic industry should be particularly gratifying.

By Dr. A. N. Goldsmith

Chief Broadcast Engineer, Radio Corporation of America

Every one today respects and admires the sterling achievements of Mr. Edison in the electrical field. He was a pioneer in the early days of the industry and has given much to the perfection of phonographs, electricity and moving pictures. But, as much as we respect and admire him, we disagree with his opinion that radio is a failure as far as reproduction of music is concerned.

When orchestra leaders and critics find radio a necessary adjunct to their work, Edison's opinion in the matter is inconsequential. Engineers have instruments that can take the measurements of reproduction of music, both by radio and phonographs. If their findings were made known the results obtained by radio will be as good, if not better, than those received from a phonograph.

The final judgment comes from the

public. They are the ones who cast the deciding vote in the matter—and they are in favor of radio. Thousands of letters in broadcasting stations show the faith people have in radio as a dispenser of music. They, as final arbiters, are satisfied.

We are close to the point where, with a good receiving set, music from any part of the country can be heard and enjoyed by radio. Broadcast receivers today are being built to reproduce good music.

By Joseph D. R. Freed

Set Manufacturer

Thomas A. Edison is wrong in his conception of radio.

The most important distinction between the radio and the phonograph is that radio is alive in the sense that the imagination of the listener is stimulated by the fact that there is a real human being at the microphone.

I do not take the position that there is a waning field for the phonograph. The talking machines will, I believe, always remain a factor in the home. Its usefulness in the future will be limited to its specific capability, namely:—the reproduction of music which has heretofore been produced, whereas the field of radio is the reproduction of music which is actually at the moment being produced. The phonograph will always be valuable in preserving the voices of great singers who have passed away. The radio will give to millions the voices of those who are still with us.

It is my opinion that when Mr. Edison speaks the world should listen, but even greatness such as is his may be constrained to utter a dictum which is proven incorrect by the avalanche of public interest in the music delivered by modern radio. We wish Mr. Edison success with the new record he is out to place on the market.

By Dr. Sidney N. Baruch

Inventor and Broadcast Engineer

Those remarks by Mr. Edison are too puerile to deserve any discussion.

By Dr. E. E. Free

Consulting Engineer

Music from a first-class broadcasting station, in my judgment, is reproduced every bit as well by a radio set as the reproduction by a phonograph or any other electro-mechanical instrument. Of course there are some cheap old-model receivers on the market that cannot do this, but later models can.

Distortion is due to one of two things: either the set is not properly designed to handle music or the person tuning the set has no knowledge of what it is all about. When the latter is the case distortion invariably occurs.

I have a set at my home that I will match against any phonograph Edison has produced, and guarantee that the repro-

WHAT do you think of Edison's
RADIO V

EDISON'S SLUR ON RADIO

DELIGHTS FANS



(Photograms)

ANNA CASE, famous American soprano, who opened the Atwater Kent radio concert series for 1926-27 from WEA and a chain of stations throughout the country. Miss Case is known as the "Star Spangled Banner Lady," since she has sung this national anthem at more public functions than any singer.

all its own, which are apparent. The phonograph, which recently has been improved by radio devices, occupies an enviable position in bringing into the homes of the world the finest of music. Every great invention, records show, has found its place, and few have brought about revolutionary changes.

But Mr. Edison was further wrong in classing radio music as "tinny." The greatest improvement in radio has been along the lines of superior reproduction. Acoustical experts agree that the advance within the last year has been striking. At the Radio World's Fair the subject of finer tonal qualities was one of main discussion.

Through shielding of the radio and audio frequency stages of receivers, to eliminate damaging stray currents that tend to distort reception, through the use of finer tubes, capable of carrying highly amplified signals, and by reason of the excellent new speakers that have been put on the market, radio music is charming to the ear. We confess that a few years ago, loud speakers were not all they should have been, but even Mr. Edison should have no reason to complain of the present day results.

The great inventor, by his attack, centralized attention on the all-round merits of the radio, not the least of which is its worth as a factor in our sociological progress.

Attacks on radio are about on a par with casting a pebble to smash Gibraltar.

By Frank Reichmann

Set, Parts and Accessory Manufacturer

Thomas A. Edison, the well known inventor, recently announced that radio had

Priess Points to the Wizard's Defective Hearing, Freed, Palmer, Eisenmann and Reichmann Lift Voices to Disprove Allegations in Inventor's Statement

been a failure and did not compare with the phonograph industry as a business, or with the phonograph as a means of reproduction.

I am citing statistics recently announced by the Radio Manufacturers Association that definitely answer Mr. Edison's argument that the radio industry is not thriving.

As yet I have had no reply to my offer to supply Mr. Edison with a radio receiving set so that he may compare the quality of reproduction of the receiver with that of his own or other phonographs.

I am presenting these facts, believing it unfair for the young and thriving radio industry to be the victim of such an attack. The statistical reports follows:

The growth of the radio industry is shown in statistics recently prepared by J. B. Hawley, chairman of the statistical committee of the Radio Manufacturers Association.

From 37,000 radio receiving sets in operation in 1920 the industry has developed to the point where more than 5,000,000 homes are equipped with radio, according to the statistics prepared by Mr. Hawley.

The detailed figures follow:

Sales by Years

Year	Sets	Parts	Accessories	Total
1922	\$5,000,000	40,000,000	1,500,000	46,500,000
1923	15,000,000	75,000,000	30,000,000	120,000,000
1924	100,000,000	100,000,000	150,000,000	350,000,000
1925	175,000,000	74,000,000	200,000,000	449,000,000
1926	225,000,000	75,000,000	230,000,000	530,000,000

Sets in Use by Years

1920	37,000
1921	75,000
1922	150,000
1923	2,000,000
1924	3,000,000
1925	4,000,000
1926	5,000,000

By William H. Priess

Engineer and Set Manufacturer

Mr. Edison is quite deaf, and if the opinion voiced in the press was his, he should not be taken as a final judge in the matter.

The public never had faithful reproduction of music until the advent of radio. The old phonograph was a tin pan affair, and when radio became popular, due to its faithful electro-mechanical reproduction of music, it naturally hurt the phonograph business.

Today the phonograph is coming back, thanks to radio. Engineers of the various phonograph concerns are taking a page from the book of radio and trying to duplicate the tonal effect obtained with a good receiver.

Formerly an artist played into a horn in the recording studio, and when the record was played behind the music was a "scratchy" sound. Now the artists are playing into a microphone, thereby eliminating the "scratch" from the records. The same applies to the horn in a phonograph. What the phonograph engineers have learned regarding the acoustics from radio, they are applying to phonographs.

Phonographs are always given a formal artificial performance; not so with radio. When you tune in on a symphony orchestra many notes that are not heard on a record can be readily distinguished by radio. There is more life to a selection played by radio than there is to the same selection when played on a phonograph.

By Eric H. Palmer

Radio Publicity Expert

A recent attack upon radio has been turned into its greatest advertisement.

This was the criticism of radio music by Thomas A. Edison, which for his purpose, that of particularly emphasizing the merits of the phonograph, could not have been more ill-timed.

It came when the minds of 25,000,000 people were upon the magnificent program of the Annual Radio Industries Banquet, probably the finest entertainment ever put on the air, and also upon the eve of the broadcasting of the Dempsey-Tunney, which was listened to by an equal number of people in the United States and Canada, and even in far-off England and South Africa.

Complete and prompt answers to Mr. Edison's attack were made by representatives of the broadcast public, of which the Radio Queen of America, Mrs. Lotta Harrauff, was one; by the official organizations of the radio industry, and by the press in leading editorials.

There is no rivalry between the radio and the phonograph, no more than radio can take the place of the printed word. Each supplements the other for the benefit of the people. The radio has its peculiar advantages and a special fascination

remarks? Write your views to **WORLD**

WAVE QUIRK MAKES A SET SOUND ROUGH

Dr. Dellinger Explains Mysterious Effect as Not Due Either to Transmission or Reception, But to Some Strange Intervention—Dead Spots Investigated

WASHINGTON.

Radio dead spots are caused by the topography of the land or by the presence of peculiar kinds of obstacles, according to Dr. J. H. Dellinger, chief of the Radio Laboratory of the Bureau of Standards. Dr. Dellinger is planning to make a study of dead spots this winter with the hope of finding some way to counteract them.

"There are frequent complaints of the existence of dead spots," says Dr. Dellinger. "They are tied in with the fact that radio transmission is better in some directions from a station than others. These differences can usually be explained in terms of topography of the land or presence of particular kinds of obstacles.

"The radio waves travel better and are less absorbed over water than over land, and hence tend to follow rivers. They are impeded by mountains which, so to speak, cast a shadow or cause something of a dead spot in the region beyond them.

"In special cases where a mountain or large cluster of tall steel buildings is near the transmitting set, the shadows may be very marked indeed and may practically cut off all reception in regions beyond them. The largest cluster of tall buildings in New York creates dead areas in which reception from WEAf is very poor; these areas extend well into Connecticut and Long Island."

Roughening of the quality of received sounds sometimes may not be due to the transmitting or receiving apparatus, says Dr. Dellinger, but actually something in the wave transmission is responsible. The roughening quality is more likely to appear in the case of weak signals, he says.

Deaf and Dumb Girl Learns How to Talk

LOS ANGELES.

One of the more wonderful things that has been credited to radio is the teaching of a little deaf and dumb girl to learn how to talk. Eddie Albright, at KNX, has spent many months working with "Little Jean" and at the recent radio exposition held here showed the rapid strides that had been made in her education.

"Little Jean" has learned to tell how old she is, what color her hair is, who she loves best and such things during the time that Mr. Albright has worked with her. She is just four years old, and last year, before it was discovered that, through the aid of radio sound could be transmitted to her, she had never heard at all.

Now the remarkable thing about the work is that, after many months of diligent work, "Little Jean" can talk and hear sounds without earphones.

CAPITOL FAMILY PORTRAIT



THE CAPITOL Theatre Family. Left to right, seated, are Caroline Andrews, Major Edward Bowes and Celia Turrill. Standing from left to right, Martha Wilchinski, C. Barclay, Dr. Billy Axt, Sigurd Nilssen, Waldo Mayo and Yasha Bunchuk.

Inspectors Stop Fight on Noises

Interference from Power Lines, Static Machines, X-Rays and Wave Deviation Outside Their Legal Scope, Attorney-General's Opinion Holds

WASHINGTON.

Fans who suffer from interference this Winter need not look to radio supervisors for help. Chief Radio Supervisor W. D. Terrell has instructed supervisors throughout the country that they have not the authority to act in most cases of interference and they, therefore, cannot do anything about it.

According to the interpretation of the law by the Department of Justice, radio supervisors have the authority only to inspect ship and land stations. They have no jurisdiction whatever over the wavelength or power of stations nor can they act in cases of non-radio electrical interference.

A large percentage of interference is caused by stations themselves through deviation of wavelength or the use of too much power. The wave deviation causes the station to interfere with some other broadcaster, while too much power in a congested area results in a blanket of the immediate neighborhood.

Last winter inspectors attempted to minimize this type of interference. Also in cases of non-radio electrical interference investigations were made whenever possible.

Whenever it is possible, however, the radio supervisors will co-operate with fans, Mr. Tyrrell says.

"I believe the best bet," Mr. Terrell advises, "is for fans who suffer from interference caused by power lines, elevators, street cars, etc., to report the trouble to the companies themselves. These com-

panies are generally glad to do everything in their power to eliminate the interference.

"If the interference is caused by stations, I'm afraid there's nothing that can be done about it, unless the fans complain to the station that causes the interference."

Better Class Music Gains Popularity

LOS ANGELES.

Is the trend of the public mind turning with the constant use of radio? Are listeners in enjoying classical music more than they used to? These two questions have caused station managers to worry and grow gray.

Naylor Rogers, manager of KNX, believes that radio has served to bring about a desire on the part of the radio public for better quality and higher class numbers.

In the earlier days of broadcasting the so called "jazz" music was in demand. Everyone that phoned in wanted one of the popular airs played. The mails were crowded with requests of this kind. Now it is a different story; the phone calls are divided and so is the mail.

"It indicates very clearly to me," said Mr. Rogers, "that radio is doing a great deal in educating the public to better music."

AIR PIRATES FEEL EFFECT OF STRIKERS

**Chicago Headquarters Es-
tablished by Broadcast
Listeners' Association
that Opposes Wave
Jumping, Time Seizure
and Unauthorized
Power Increase**

CHICAGO.

A very short while ago, Chicago claimed the distinction of having the first broadcasting listeners' strike. At that time it was directed against stations which remained on the air during the desired Monday night of silence. Again the BCLs of Chicago come into prominence with a strike against those stations which have taken other than their assigned wave, increased their power or taken unassigned time, as a result of the recent Department of Commerce announcement stating that the 1912 radio laws gave the department no control over broadcasting. The Broadcast Listener's Association is again backing the strike.

The last strike made a decided impression on the broadcasters, for they soon abided by the "gentlemen's agreement" of the other silent stations and remained off the air. This was due to the empty mail basket the morning after and also the poor response via the telephone for requests, etc.

The association contends that new broadcast transmitters which may come on the air in its present crowded condition and those which select wave-lengths other than those to which they originally were assigned by the Department of Commerce are "unfair" and urges its members to pass them over when they are turning their dials.

In addition to affecting Chicago stations, the association has stated that its movement is nationwide and that listeners all over the country are joining in the effort to keep the air free of congestion. They are also taking upon itself the task of warning stations which stray about in the air, advising them that their listeners will decrease in number as a result.

Response to the strike has been large, the association officials said today, adding that the drive will be continued until more stable conditions prevail, or until Congress enacts a law governing the situation.

The newest feature is the established strike headquarters at the radio fair here.

Diskay Popular With Coast Fans

LOS ANGELES.

Joseph Diskay, Hungarian tenor, has established himself, through the aid of radio, as one of the outstanding tenor voices on the coast. KNX has used Mr. Diskay as an exclusive artist for many months and his following in the radio world is extremely large.

CAGE AERIAL OVER HEAD



GRACE ORRELL of Somerville, Mass., and Minnie Butler of Boston, Mass., left to right, with the new cage antenna headpiece, which was on exhibition at the Boston Radio Show.

WRNY Gets Along Without Announcer

A metropolitan newspaper radio critic recently came out with the opinion that stations could do very well without announcers.

WRNY was willing to try the recommendation, and on October 15 for the entire evening program had no announcers whatsoever. For the whole evening the station tried to get along and the public was asked to judge whether announcers are really needed. Not even the station's call letters were mentioned—there being no announcer to give them—but after every selection the Staccatone signal was used, which itself identifies WRNY.

The radio listeners expected quite a few surprises during the course of this announcerless evening. Just how the whole program would be managed was a little

secret of WRNY up to the last minute. On the very same evening, Friday night being novelty night, there was the usual novelty feature, at 10:15, also announcerless. The novelty consisted of a peek behind a broadcast station's scenes. The entire staff of WRNY was heard preparing the next week's program, interviewing artists and getting "samples" from the various performers. It was the first time that the public listened to what goes on behind the scenes in a modern broadcast station—not only from the program end but from the technical end as well.

THREE IRISH STATIONS WASHINGTON.

Three new broadcasting stations are to be established in the Irish Free State, according to a report to the Department of Commerce. The new stations will each be of 1,500 watts power and are designed to make programs available to owners of low power sets.



**VICTOREEN
Super Coils**

Send for Folder
Geo. W. Walker Co.
6528 Carnegie Ave.
Dept. B Cleveland, O.

Look for the Trade Mark



on the condensers you buy and make
sure they are for the proper voltage.

Tobe Deutschmann Co.
Cambridge, Mass.

NATIONAL

NATIONAL
in name
NATIONAL
in fact
NATIONAL

Radio Set Essentials
are known and appreciated
in every corner of this
great United States.

**NATIONAL
BROWNING - DRAKE**


Spacewound coils and radio-
frequency transformers.

**NATIONAL
VELVET - VERNIER**

DIALS—Type A and B and the

**NATIONAL
ILLUMINATED**

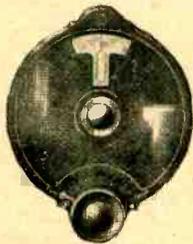Velvet-Vernier Dial Type C with its brilliantly
lighted scale and ease of attachment to any radio-set



**NATIONAL ILLUMINATED
VELVET-VERNIER DIAL TYPE C**

**NATIONAL
EQUICYCLE & EQUIMETER**

Variable Condensers are good and stay good.
They space out the crowded stations.

**NATIONAL
IMPEDAFORMERS**

are units for quality
impedance-coupled audio.

NATIONAL

Transmitting Condensers are
used by hams the world over.

NATIONAL

B-Eliminator Parts will
be ready soon.

**NATIONAL
COMPANY, INC.**

W. A. Ready, Pres.
110 Brookline
Street
Cambridge, Mass.

will gladly send you bulletins
on any or all of these items.
Mention Radio World

World to Celebrate Invention of Bulb


"Electric Night," marking the anniversary of the invention of the incandescent lamp by Thomas A. Edison and heretofore a national observance only, will become world-wide October 21, when fifty broadcasting stations scattered throughout the world will join in offering programs to mark the forty-seventh anniversary of Edison's epochal invention.

People in the Far East, South America, South Africa, the countries of Europe, Canada and the United States will listen to special anniversary programs initiated by leaders in the electrical industry.

Two years ago a few radio stations broadcast an "Electric Night" anniversary program and the following year the number of participating stations was increased so that the entire United States was literally covered. At least one station is within listening distance of everyone. This year the interest in "Electric

Night" is even greater in the United States where thirty-five stations will cooperate, while stations in many foreign lands will dedicate programs to Thomas A. Edison and the industry which has grown out of his invention.

Forty-seven years ago, October 21, after months of patient work, Edison carbonized a piece of cotton sewing thread bent into a loop. This he sealed in a glass globe from which the air had been exhausted. The lamp was put on an electric circuit and was lighted brightly to incandescence and burned steadily for over forty hours. That marked the birth of a practical incandescent lamp. From that lamp, with its sewing thread filament, has grown the electric light and power industry which in 1925 showed a gross revenue of \$1,470,000,000 with an estimated capitalization in 1926 of \$7,500,000,000.

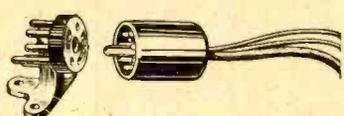

Follow Instructions

Equip your Karas Equamatic set with the famous Jones **MULTI-PLUG**. It is specified by the designers of this set because they want your Karas to be unrivalled in performance, operation and service. At your dealer or write direct.

HOWARD B. JONES
618 S. Canal St. Chicago, Ill.

**Jones
MULTI-PLUG**
THE STANDARD SET CONNECTOR

Trade Mark Registered U. S. Patent Office.

YAXLEY

**Gold Plated Parts
for the
Karas Equamatic System**

Your dealer will gladly secure Yaxley Approved Radio Products in the Gold Plated Finish for your hook-up. The parts are actually gold plated, not merely washed, and will retain their rich handsome appearance.

Prices Are for Gold

10 and 20 Ohm Rheostats.....	\$1.50
No. 1 Open Circuit Jack.....	.75
No. 4 Interstage Jack.....	1.05
No. 10 Midget Battery Switch.....	.75

All other parts also furnished in Gold

Cable Connector Plug

The No. 660 Cable Connector Plug for quickly and conveniently connecting and disconnecting battery wires will give you a new kind of satisfaction from cable plugs. Bakelite construction. Try it..... **\$3.50**

At your dealer's. If he cannot supply you, send his name with your order to

Yaxley Manufacturing Co.
Dept. W, 9 So. Clinton Street
CHICAGO ILLINOIS

FREE BOOKLET FOR INVENTORS

IF YOUR INVENTION is new and useful
it is patentable. Send me your sketch.
Z. H. POLACHEK, 70 Wall St., New York
Reg. Patent Attorney-Engineer



**Silent
"B" Power with
World Radio Storage "B" Battery**

**12 Cells
24
Volts**

Lasts Indefinitely — Pays for Itself

Dependable. Quiet "B" power, clear without "hum." Economy you have never before thought possible. Convenience. Outstanding performance. Recharged for almost nothing. Solid rubber case insures against leakage or acid. Extra heavy glass jars. Heavy rugged plates. Approved and listed as standard by Pop. Radio Laboratories, Pop. Sci. Inst. Standards, Radio News Lab., Lefax, Inc., and other Radio authorities.

Extra Offer: 4 Batteries in series (96 Volts) \$10.50.

SEND NO MONEY! just state number of batteries wanted and we will ship same day order is received. Pay expressman after examining batteries. 5 per cent discount for cash with order. Send your order today—NOW!


WORLD BATTERY COMPANY
1219 So. Wabash Ave. Dept. 82 Chicago, Ill.

Makers of the Famous World Radio "A" Storage Battery
Prices: 6-volt, 100 Amp. \$10.50; 150 Amp. \$12.50; 150 Amp. \$13.25.
All equipped with Solid Rubber Case.

**World
STORAGE BATTERIES**

Set your Radio Dials for the new 1000-watt World Storage Battery Station, WSB, Chicago. Always something interesting.

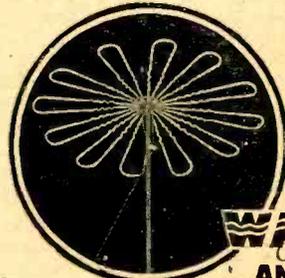KOKA - WEAF - WGN - WJS - KHJ - KGO - KFAF - WJY - KGO



**Bring in
Every
Station
on the
Air
With a
WAVE-X
Condensing
ANTENNA**

An aerial that can be erected on wall, chimney or roof, anywhere 5 foot square is available. Provides sharper tuning, increases selectivity and is non-directional. Twelve highly conductive feelers reaching out in all directions have the capacity of long single wire. Perfect insulation prevents losses. Erected and dismantled quickly. A single upright to erect, hammer and screw-driver the only tools needed. No. 2, 8 foot pole ready to install, full instructions, \$12.50. Get a Wave-X now.

**REDI-MAST
FOR AERIALS**

A strong hand turned rock maple pole 5 or 8 foot lengths. Fits any roof. Will carry heaviest sheet covered single or multiple wire antennas in strong wind. Complete, guy rods, nee irons, roof sockets, anchor pins and full instructions. 5 foot mast \$3.50 each, 8 foot \$4.25. Ask your dealer. Dealers—Wave-X and Redit-Mast are quick sellers. Write today for our dealer offer.

THE ZINKE CO.
1323 S. Michigan Ave., Chicago
THE PRESSED METAL MFG. CO.
Waukesha, Wis.

Church Exhibits At Chicago Show

For the first time in history a church exhibited at a radio exposition.

At the invitation of the Radio Manufacturers' Show Association, the Immanuel Lutheran Church of Valparaiso, Indiana, was represented at the Chicago Radio Show at the Coliseum.

A model of this church, with its famous radio station WRBC, was shown to 250,000 visitors.

"This is a happy illustration of the tremendous strides that radio is making towards our well-being," declared G. Clayton Irwin, Jr., general manager of the show. "We believe that radio has been of tremendous assistance to the church. We congratulate the Rev. Dr. George Schutes, pastor of Immanuel Lutheran, on his wonderful success in touching so many hearts with his sermons over the radio and increasing the number of his congregation, visible and invisible, each succeeding Sunday." Dr. Schutes quite

proudly recalls the fact that WRBC was one of the first stations established for church extension, but it also features lectures by the faculty of Valparaiso University, farm organization leaders, agricultural experts, and others.



UX POWER TUBES installed in any set without rewiring by Na-Ald Adapters and Connectorals. For full information write Alden Manufacturing Co., Dept. S-20, Springfield, Mass.

FREE

NEW RADIO CATALOG

Write Today to
Chicago Salvage Stock Store
509 S. State St., Dept. R.W., CHICAGO, U.S.A.

MORE THAN a score of new kits—all the latest and best—with specified parts to build them—at prices that mean big savings for you. And all the latest parts and accessories as advertised in current radio magazines. The largest, most complete and up-to-date radio stock in the world. Yours to choose from in this new catalog. Write for your copy.



LOOK UP DOWN

SUPERHETERODYNE SPECIALIST
Complete parts for Infra-dyne—Fenway Four, etc.
Handsome Leatherette Leg and Data Book.
FREE Send Ten Cents to Cover Mailing Cost
CHAS. W. DOWN, M. E.
2050 Broadway, N. Y. C., Phone: Trafalgar 5979

HARD RUBBER

SHEET—ROD—TUBING
Special Hard Rubber Parts Made to Order
RADION HARD RUBBER PANELS ANY SIZE

Send for Price List
WHOLESALE RETAIL
NEW YORK HARD RUBBER TURNING CO.
212 Centre Street New York

CARTER

Chosen for New Victoreen Circuit
No. 4 Jack Switch
Double Pole—Double Throw
—complete with knob and pointer\$1.60

"TIP" JACK Fits any standard cork tip 10c.
No. 2 Short Jack Makes good contact with all plugs. Closed circuit. 30c ea.

Any dealer can supply.
In Canada—Carter Radio Co., Limited, Toronto



BLUE PRINT FOR 1926

Diamond of the Air

A blue print for wiring the circuit that has swept the country may be obtained by sending 50c in stamps, money order, cash or check. This blue print is full size and is personally certified by Herman Bernard.

Guaranty Radio Goods Co.

145 West 45th Street New York City

SAVE ON RADIO

All Standard Merchandise

It will pay you to deal with us

We carry one of the largest lines of Radio in the East.

All standard makes of Sets, Loud Speakers, Batteries, Parts, etc., in stock for immediate delivery.

EVERY ITEM FULLY GUARANTEED

Write for our quotations today

ECONOMY RADIO SALES CO.

"Everything in Radio at a Saving"
288-6th Ave. Dept. E. New York



HEAVY DUTY Centralab Radiohm

with 5
New Advantages

Designed to control the output current of "B" Battery Eliminators, Centralab Heavy-Duty Radiohms are fully approved by the Raytheon Laboratories. Full resistance variation with a single turn of knob, allowing panel marking for proper setting to provide various voltages.

Good for the Life of Your Set

Resistance remains as adjusted. (No carbon particles or discs to compact after adjustment.) Bushing and shaft insulated to withstand 1500 volts. Will remain smooth and noiseless for the life of the eliminator. \$2.00 at your dealers or mailed direct.

CENTRAL RADIO LABORATORIES

13 Keefe Avenue Milwaukee, Wis.

Makers of a full line of variable resistances for 69 manufacturers of leading standard sets.



INSTALL THE BRETWOOD GRID LEAK and have absolute control of your volume. Sent on receipt of \$1.50. North American Bretwood Co., 145 W. 45th St., N. Y. C.

FILL OUT AND MAIL NOW

SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City
(Just East of Broadway)

Please send me RADIO WORLD for.....months, for which

please find enclosed

SUBSCRIPTION RATES:


Single Copy.....\$.15
Three Months..... 1.50
Six Months..... 3.00
One Year, \$2 Issues..... 6.00
Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.

Announcing the
**NEW BRETWOOD
 VARIABLE GRID LEAK
 WITH CONDENSER ATTACHED**

This Combination
 Instrument Used in

Bernard

The Handsome Set of
 Rich Tone Quality

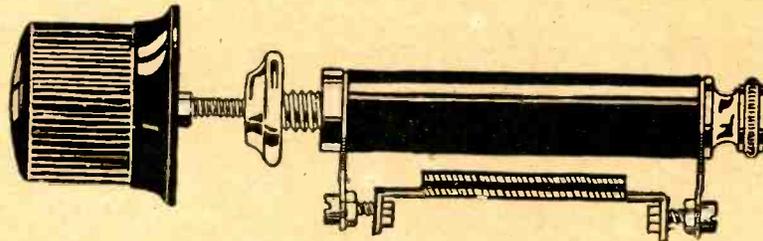

The New Bretwood Variable Grid Leak with Condenser Attached, Price \$2.00
Guaranteed Precision Range, $\frac{1}{4}$ to 10 megohms.

Let the Best Be None Too Good for You!

Connect a BRETWOOD Variable Grid Leak in the detector circuit of your set and turn the knob until the signals clear up beautifully.

Use a BRETWOOD Variable Grid Leak across your last stage audio transformer, or put one in place of the fixed leak in the final grid of impedance or resistance coupled audio. Turn the knob and note the amazing improvement in quality.

In any circuit where a grid leak has to be used its value in ohms is important. Conditions differ in individual circuits and with different equipment. Experts cannot specify definite values that are applicable to all cases. The variable leak takes the guesswork out of the grid circuit, and the BRETWOOD is the best for the purpose. "It Does the Trick!"

NORTH AMERICAN BRETWOOD CO.
 143 WEST 45th STREET
 NEW YORK CITY

NORTH AMERICAN BRETWOOD CO.,
 143 West 45th Street, N. Y. City

Enclosed find \$2.00, for which send me one BRETWOOD Variable Grid Leak with Grid Condenser attached (or \$1.50 without condenser) on five-day money-back guarantee.

NAME

STREET ADDRESS


CITY and STATE

(Inquiries Invited from the Trade)



For Best Reception Use a Bretwood

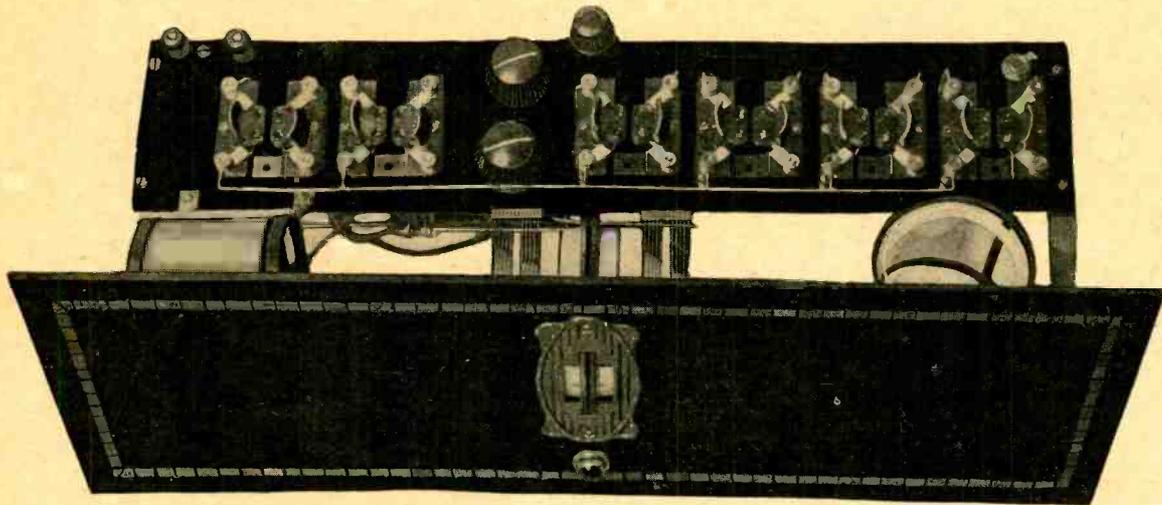A New Note of Beauty Has Struck! The *Bernard* 6-Tube Kit Makes the Handsomest Set



VIEW OF SET made from the official list of parts, as printed below. Note the Bruno Unitune, Model 2CB, constituting the Tuning Control.

OFFICIAL LIST OF PARTS

Exactly as Specified by Herman Bernard and Bearing His Personal Indorsement

C2, C4—Two Bruno .00035 mfd. straight line frequency variable condensers, which, with two drums, mounting frame, panel plate and screws constitute the Bruno Unitune, Model 2CB.
LS—One Bruno light switch, bronze type, special for this kit.
L1L2—One Aero fixed primary radio frequency transformer, stock No. WT-40.
L3L4—One Aero adjustable primary radio frequency transformer, stock No. AX-45.
GFPB—One Acme R3 radio frequency transformer.

C3, C1, C6—3 micamoid .00025.
R2, C5—One Bretwood Variable Grid Leak with grid condenser, .00025 mfd.
R3, R5, R7—Three Lynch metallized fixed resistors, 0.1 meg. each.
R4, R6, R8—Three Lynch metallized fixed resistors, respectively 1.0 meg., 0.5 meg. and 0.25 meg.
1, 2, 3, 4, 5, 6—Six Air Gap push type sockets.
R1—One Electrad Royalty variable high resistance, Type F, range 0 to 2,000 ohms.
C7, C8, C9—Three Electrad 0.25 mfd. fixed condensers.

RU—One Electrad 2-ohm semi-power rheostat.
J—One Electrad single closed circuit jack.
One pair Bruno adjust brackets.
One 7x21" Lignole inlaid walnut front panel, drilled and engraved.
One Birnbach 6-lead battery cable, with forked terminals.
Nine Glamco cable tags (one A plus, one A minus, one C plus, one B minus, three C minus, one B plus amp. and one B plus det.)
Two C. A. L. binding posts (Ant. and Grd.)
Three Lynch double mountings.
10 lengths stiff Acme Celatsite.

Official Blueprint of Wiring Free With Each Kit Order

Each Kit Boxed and Sealed

\$40

ONE FINGER TUNES THE SET!

The inclusion of the Bruno Unitune, Model 2CB, enables the tuning to be accomplished with one finger. The only other panel part is the Bruno light switch, which also illuminates the scale on the tuning drums. Beauty of appearance and tone combine with simplicity to make this kit the prime attraction of the season.

Order Your Kit NOW for
Immediate Delivery from

B-C-L Radio Service Corp.
Dept. RW, 221 Fulton St. N. Y. City

B-C-L RADIO SERVICE, INC.
221 Fulton St., New York.

Gentlemen: Enclosed please find (check) (money order) for \$40, for which please ship at once one complete boxed and sealed kit for the Bernard 6-tube set, as advertised by you in Radio World.

NAME

ADDRESS

CITY AND STATE

Authorized Agents for the Bernard Kit

- New York City**
B-C-L Radio Service Corp., 221 Fulton St.
Enter-City Radio, 223 Fulton St.
Try-Mo Radio, 9 West Broadway
Radio Kit Co., Suite 1202, at 1482 Broadway
Walthal Electric Co., Inc., 60 Cortlandt St., and 142 East 86th St.
Yorkville Radio Co., 86th St. and Lexington Ave.
Fannill Radio Co., Inc., 62 Cortlandt St.
Klein's Radio Stores, 30 Park Place, and 120 Fulton St.
Perfection, 58 Cortlandt St.
Jayuxon Laboratories, 57 Dey St.
Amco, 65 Cortlandt St.
Kenwood Radio Co., Inc., 63 Cortlandt St.
Oscar's Radio Shop, 172 Washington St., 178 Greenwich St.
43d St. Radio Shop, 100 West 43d St., and 407 Lexington Ave.
City Radio Stores, 110 W. 42nd St., and 79 Cortlandt St.
J. Mueller & Co., Vesey & Church Sts.
Otto Furman Radio Corp., 175 East 86th St.
Holland Radio Stores, 75 West 125th St.
S. & S., 305 West 125th St.
Elliott's Radio Dept., 59 Cortlandt St.
Spartan Electric Co., 350 W. 34th St.
Haynes-Griffin, 141 W. 43d St., and 10 Wall St.
Saul Bros., 111 Second Ave., and 407 Lexington Ave., and 12 W. 45th St., and 16 Ave. B. and 1366 Fifth Ave.
Davega's, 125 W. 125th St., and 831 Broadway, and 111 E. 42nd St., and 15 Cortlandt St.
- Brooklyn**
Walthal Electric Co., Inc., 118 Flatbush Ave., opp. L. I. R. H.
Rix Radio Supply House, Inc., 5595 Fourth Ave.
Brooklyn Radio Service Corp., 577 Myrtle Ave., and 1188 Fulton St., and Smith and Livingston Sts., and 20 Fourth Ave.
S. Hammer, 303 Atkins Ave.
- Chicago**
Barawik Co., 541 Monroe St.
New Eng. Mills Co.
Chicago Salvage, 509 S. State St.
Randolph Radio, 180 N. Union Ave.
- Elsewhere**
Radio Shop, 20 Worth St., Stamford, Conn.
Consumers Service, 261 42d St., Paterson, N. J.
Radio Guild, 243 Market St., Newark, N. J.
Standard Radio, 1410 Walnut St., Kansas City, Mo.
M. & H. Sporting Goods Co., 512 Market St., Philadelphia.


Great Atlantic Radio Co.

International Distributors to the Trade
223 Fulton Street New York City
Inquiries Invited from the Trade

Protect Your Set
BIRNBACH BATTERY CABLE
 SIMPLIFIES THE CONNECTING OF
RADIO BATTERIES
 SEPARATE COLORED WIRES
5 Conductor Cable with Soldered Terminals 50¢
 ALSO MADE IN 6-7-8-WIRE CABLES

Improve Your Reception
 BY PLACING YOUR LOUD SPEAKER ANY
 DISTANCE FROM YOUR RECEIVER
20ft Extension Cord with Connector \$1.00
 AND 30-40-50-100-FOOT UNITS
 SEND FOR FREE LITERATURE
BIRNBACH RADIO CO.
 370-SEVENTH AVE. ~ NEW YORK CITY

EBY
SOCKETS
 and
BINDING POSTS

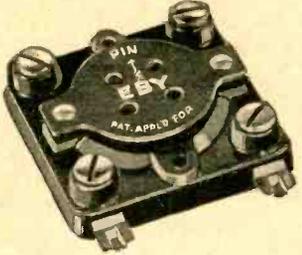

Specified for Victoreen and Lynch Lamp Socket Amplifier


Eby products are also recommended and specified in the Infradyne, Hammarlund-Roberts, Cockaday, L. C. 27, Browning-Drake, Madison-Moore and Varion Power Units and other popular circuits. They add to the performance and appearance of any receiver.

H. H. Eby Manufacturing Co.
 4710 Stenton Ave. Philadelphia

Herman Bernard
Uses and Recommends

CECO
TUBES

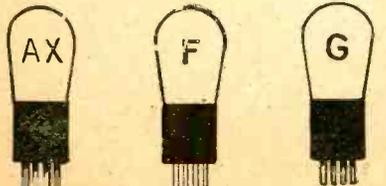Read his article on the
BERNARD SIX
 in this issue of Radio World



TYPE "A" Storage Battery General Purpose Price \$2.00
TYPE "F" Storage Battery Power Amplifier Price \$5.00
TYPE "G" High Mu for Resistance and Impedance Amplifiers Price \$2.50

Make a Good Receiver Better with CeCo Tubes

C. E. MFG. CO., Inc.
 PROVIDENCE, R. I., U. S. A.

Receiver Properly Located Cuts "Mush"

(Concluded from page 10)


ing words which the ear does not catch, studying by radio is too much of a task; and the public would much rather listen to music, when these disadvantages do not cause so much annoyance.

It seems to me that the greatest task of the radio engineer at the present time is the elimination of the extraneous, parasitic noises, which now issue from every loud-speaker over the whole world. Nor

is the task hopeless. It seems possible that it can be accomplished by the use of correct filter circuits, installed in the radio sets.

It would be welcome even to cut down the power of the set, if by so doing we could at the same time cut down the static and "mush" level. I have no doubt that this trouble will be dispelled during the next few years.

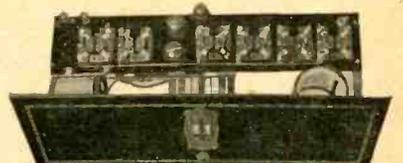Bernard
 Registered U. S. Patent Office
 The 6-Tube Receiver of Exquisite Tone



Complete boxed kit of parts, exactly as specified by Herman Bernard, and bearing his personal approval—Price (including wiring blueprint)..... **\$40**

LIST OF PARTS COMPRISING KIT

C2, C4—Two Bruno .00035 mfd. straight line frequency variable condensers, which, with two drums, mounting frame, panel plate and screws constitute the Bruno Unitune, Model 2CB.
 LS—One Bruno light switch, bronze type.
 L1L2—One Aero fixed primary radio frequency transformer, stock No. WT-40.
 L3L4—One Aero adjustable primary radio frequency transformer, stock No. AX-45.
 GPPB—One Acme R3 radio frequency transformer.
 R2, C5—One Bretwood Variable Grid Leak with attached grid condenser. .00025 mfd.
 R3, R5, R7—Three Lynch metallized fixed resistors, 0.1 meg. each.
 R4, R6, R8—Three Lynch metallized fixed resistors, respectively, 1.0 meg., 0.5 meg. and 0.25 meg.
 1, 2, 3, 4, 5, 6—Six Air Gap or Eby push type sockets.
 R1—One Electrad Royalty variable high resistance. Type F, range 0 to 2,000 ohms.
 C7, C8, C9—Three Electrad 0.25 mfd. fixed condensers.
 R9—One Electrad 2-ohm semi-power rheostat.
 J—One Electrad single closed circuit Jack.
 One 7x21" Lignole inlaid walnut front panel, drilled and engraved.

BERNARD—A Receiver of Rare Beauty

One Birnbach 6-lead battery cable, with forked terminals.
 Nine Glanzco cable tags (one A plus, one A minus, one C plus, one B minus, three C minus).
 Cl, C3, C3—Three micamold .00025 mfd. Ten lengths of stiff Acme Celatsite (varicolored).

ACCESSORIES (Extra)


R. F. I. Balanced Oval Cone Speaker..... \$25.00
 CeCo type F, \$5, Type A, \$2; Type G..... 2.50
 Genuine Walnut Corbett Cabinet for Bernard, 7x21"..... 15.00
 Electrad Lamp Socket Antenna..... 1.10
 Centralab Modulator Plug..... 2.50

SEPARATE ITEMS

Lignole drilled and eng. inlaid panel for Bernard..... \$7.50
 Bretwood Variable Grid Leak, \$1.50; with condenser..... 2.00
 [Note: We give careful and prompt service. When you deal with us you deal with a firm whose reliability you can trust to the utmost.]

RADIO KIT CO. (Suite 1202), 1482 Broadway, New York City

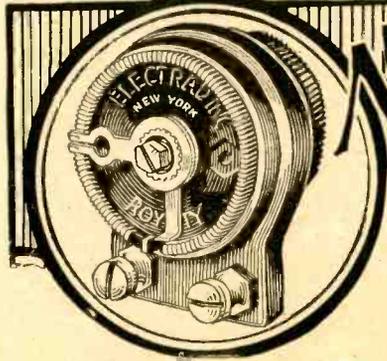New MODEL ELECTRAD
Royalty Variable High Resistances



Licensed by Technidyne Corporation, under U. S. Patent 1593685, July 27, 1926.

ELECTRAD Royalty, the original wire-wound high resistance, is the choice of engineers and technicians who demand dependable and accurate resistance in ranges exactly adapted to their requirements. The new ELECTRAD Royalty High Resistances embody important improvements. All ranges dissipate 3 watts. Select the range that fits your needs:

Type A—1/10 to 7 megohms.
 Type B—1500 to 100,000 ohms.
 Type C—500 to 50,000 ohms.
 Type D—10,000 to 7000,000 ohms. (Detector control for B eliminator).
 Type E—Compensator—500,000-ohm Potentiometer.
 Type F—0 to 2000 ohms.
 Type G—0 to 10,000 ohms.
 Type H—0 to 25,000 ohms.
 Type J—0 to 200,000 ohms.
 Type K—0 to 5000 ohms.
 Type L—0 to 500,000 ohms.
 Type E—\$2.00—All other types \$1.50.

Electrad Certified Radio Essentials are known to users and dealers everywhere for their dependable and consistent performance. Specify ELECTRAD and be sure of results.

ELECTRAD, INC.
 428 Broadway, New York

ELECTRAD

RICH ORE IS DETECTED

(Concluded from page 11)

sisted of complex ores, mainly those containing lead, iron and manganese at the top of the limestone and those containing gold, silver and copper deposited in single veins or shear zones in the andesite. The instrument responded very sensitively to the metallic enrichment in the veins and ore bodies, so that the lean and rich areas were readily detected.

In the tests made in the Las Animas district eighteen new veins were found, all of which have been prospected with good results.

The zone of the ore deposits is at a very considerable depth in the earth's crust, and when ores are exposed on the surface today it is because they have been laid bare by surface erosion. It is obvious that all of the ore bodies in the earth's crust which were formed by rock replacements or fissure fillings have not yet been exposed by the wearing off of the earth's crust, as has been shown by occasional discoveries at deep levels in mines. Ore bodies in many instances have been discovered whose highest point has never been reached by surface erosion.

So startling have been developments in other directions during the past few years that it is remarkable no one has hit upon an efficient method of locating hidden ore bodies until recently. It is believed the radio cameraphone may solve the problem of finding new deposits to replace the ones that are exhausted and place at the disposal of man the mineral wealth of the earth.

I GUARANTEE

to permanently stop squealing in any 5-tube radio frequency receiver for \$7.50, or any 6-tube RF set for \$10. Patent pending on device used. 24-hour service. Sets can be left at Enter City Radio, 223 Fulton St., N. Y., or sent to me at 40 Paynter Ave., L. I. City (phone Stillwell 5370).

JOHN F. RIDER

Contributing Editor, Radio World; author of Laboratory Scrap Book, N. Y. Sun.

Bernard BLUEPRINTS

Wiring Blueprint.....\$1.50
 Panel and Subpanel (both together)..... 1.00
 or send \$2 for the complete set of Bernard Blueprints

Special: Send \$6 for a full year's subscription to RADIO WORLD (52 numbers) and get the complete set of Bernard Blueprints FREE!
RADIO WORLD
 145 West 45th Street
 NEW YORK, N. Y.
 Nameplates Free to All!



Herman Bernard especially recommends the following:—

- Three .1 Meg.
- One .1 "
- One .5 "
- One .25 "
- Complete, \$3.75

METAL long has been recognized as the best of electrical conductors. The Lynch Metallized Resistor has received the unqualified endorsement of leading engineers, experimenters and test laboratories because it is absolutely silent in operation and remains permanently accurate.

Comprising a concentrated metallized deposit one-thousandth of an inch thick upon a glass core and sealed within a glass tube, each LYNCH METALLIZED FIXED RESISTOR wins in the exacting tests of time and service.

**Warranted—
 Absolutely Noiseless
 Permanently Accurate,
 Dependable!**

If your dealer cannot supply you, we will ship by return mail. You take no risk as Lynch products are sold on a money-back guarantee. Use the Convenience Coupon below.

PRICES	{	.25 to 10 Megohms... .50
		above .01 to .24 "75
		.001 to .01 " ... \$1.00
		Single Mounting35
		Double Mounting..... .50


ARTHUR H. LYNCH, Inc.
 Fisk Bldg., B'way and 57th St.
 New York, N. Y.



Dealers—
 Write us!

Send me the Lynch Assortment described above (6 Lynch Metallized Resistors) with the understanding that I am to receive my money back if not satisfied. I will pay postman on delivery \$3.75, plus postage.

(Name) _____
 (Address) _____

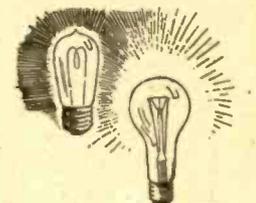

The old carbon lamp consumed more current to give less light. Tungsten, which is metal, proved more efficient, more dependable. The Lynch Metallized Resistor gives non-arcing, conductive resistance. It marks as great an advance as did the tungsten lamp.
 Arthur H. Lynch

Or send check or money order and save postage.

The RADIO SHOP *of* **STAMFORD**
20 Worth St., Stamford, Conn.
SERVICE FOR SET BUILDERS

KIT OF COMPLETE PARTS FOR

The Bernard Six

\$40.00 POSTPAID


THE BERNARD PORTABLE SUPER-HET-ERODYNE appeared in RADIO WORLD dated April 3, 10, 17 and 24. Sent on receipt of 60c. or start your subscription with April 3 issue RADIO WORLD. 145 West 45th St., N. Y. City

The CELATSITE
Wire specified for the 1927
BERNARD "6" is made only by
THE ACME WIRE CO., New Haven, Conn.
ACME WIRE

THE GREAT AID OF BY-PASS CONDENSERS, by John F. Rider, appeared in RADIO WORLD dated May 8. Sent on receipt of 15c. or start sub. with that number. RADIO WORLD. 145 W. 45th St., N. Y. C.

INSTALL THE BRETWOOD GRID LEAK and thus avoid scratchy signals. Send \$1.50 for this famous grid leak. North American Bretwood Co., 145 W. 45th St., N. Y. C.

Nonoise Variable Grid Leak

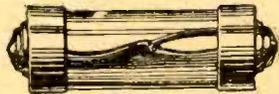

Pat'd June 16, 1925

Operates on a New Principle. Noiseless.

Range 1/2 to 7 megohms. Retains Adjustment.


Set Manufacturers who do not skimp on equipment use it in their sets.

If your dealer does not stock them send us 85c and we will send you one.

RADIO FOUNDATION, Inc.

25 WEST BROADWAY

NEW YORK, N. Y.

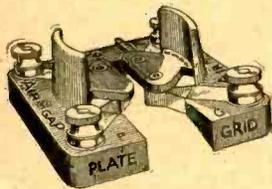

Type U.X. Universal
Price 60c

Herman Bernard specially recommends AirGap Sockets for the

Bernard

on account of its low grid and plate capacity, which makes the difference.

The AIRGAP SOCKET

"It gets that last mile"


AIRGAP SOCKETS will rid your set of those squawks, howls and frying noises due to socket capacity; they keep your grids negative, stabilizing your circuit, causing tube to go into oscillations more smoothly and not "spill over" until maximum results are attained.

AIRGAP PRODUCTS CO.

Sent direct Post-paid if your Dealer cannot supply you.

10 Campbell Street


Newark, N. J.

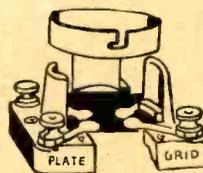

Type U.V. Standard
Price 75c

LIGNOLE Chosen by *Bernard* for His 6-Tube Set

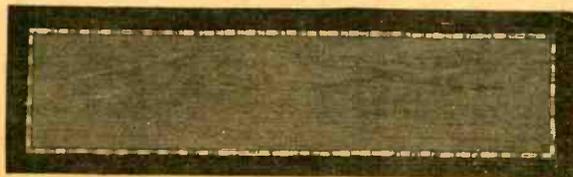After thoroughly canvassing the field for a front panel that combined the highest electrical efficiency with beauty unsurpassed, Herman Bernard selected inlaid walnut LIGNOLE for the Bernard set. The most discriminating radio engineers and designers regularly choose LIGNOLE, the new specially treated wood that meets all panel requirements.



LIGNOLE CORPORATION OF AMERICA

508 South Dearborn Street

CHICAGO, ILL.

Try-Mo Radio Company
9 West Broadway New York City
near Barclay Street Tel. Cortland 5079

Headquarters for
Bernard



Complete Boxed Kit of Parts for this beautiful receiver, exactly as specified by Herman Bernard:

C2, C4—Two Bruno .00035 straight line frequency variable condensers, which, with two drums, mounting frame, panel plate and screws constitute the Bruno Untune, Model 2CB.

LS—One Bruno light switch, bronze type.

L1L2—One Aero fixed primary radio frequency transformer, stock No. WT-40.

L3L4—One Aero adjustable primary var. radio frequency transformer, stock No. AX-45.

GFPP—One Acme R3 radio frequency transformer.

R2, C5—One Bretwood Variable Grid Leak with grid condenser, .00025 mfd.

R3, R5, R7—Three Lynch metallized fixed resistors, 0.1 meg. each.

R4, R6, R8—Three Lynch metallized fixed resistors, respectively, 1.0 meg., 0.5 meg. and 0.25 meg.

1, 2, 3, 4, 5, 6—Six Air Gap push type sockets.

R1—One Electrad Royalty variable high resistance, Type F.

C7, C8, C9—Three Electrad 0.25 mfd. fixed condensers.

R1, R3, R6—Three micamold .00025.

R9—One Electrad 2-ohm semi-power rheostat.

J—One Electrad single coiled circuit jack.

One 7x2 1/2" Lignole inlaid walnut front panel, drilled and engraved.

One Birnbach 6-lead battery cable, with forked terminals.

Nine Glanzco cable tags (one A plus, one A minus, one C plus, one B minus, three C minus, one B plus amp., one B plus det.)

Two C. A. L. binding posts (Ant. and Grd.).

Three Lynch double mountings.

Bruno adjust. brackets.

Official blueprint.

Acme Celatsite (stiff).

\$40

RADIO WORLD'S QUICK - ACTION CLASSIFIED ADS.

10 CENTS A WORD
10 WORDS MINIMUM.
CASH WITH ORDER.

SALESMAN WANTED
MAKE \$100 WEEKLY in spare time. Sell what the public wants—long distance radio receiving sets. Two sales weekly pays \$100 profit. No big investment, no canvassing. Sharpe of Colorado made \$955 in one month. Representatives wanted at once. This plan is sweeping the country—write today before your county is gone. OZARKA, INC., 431 N. La Salle Ave. R., Chicago, Ill.

PATENTS—Write for free Guide Books and "Record of Invention Blank" before disclosing inventions. Send model or sketch of your invention for our Inspection and Instructions Free. Terms reasonable. Radio, Chemical, Mechanical, Electrical and Trademark experts. Victor J. Evans Co., 924 Ninth, Washington, D. C.


OFFICIAL LIST OF STATIONS, giving call letters, owner, location, wavelength in meters, even unto decimal fractions, and the frequency in kilocycles, was published in the October 2 issue of RADIO WORLD. Send 15c for copy. RADIO WORLD, 145 West 45th St., N. Y. City.

PATENTS—Write for free Guide Books and "Record of Invention Blank" before disclosing inventions. Send model or sketch of your invention for our Inspection and Instructions Free. Terms reasonable. Radio, Chemical, Mechanical, Electrical and Trademark experts. Victor J. Evans Co., 924 Ninth, Washington, D. C.

SELL AND INSTALL RADIO SETS. With a \$25 capital we can put you in the radio business and show you how to earn a hundred or two a week. For full details write Guaranty Radio Goods Co., 145 West 45th Street, New York City.

THE 1927 MODEL VICTOREEN has been covered in the following issues of RADIO WORLD: Sept. 11, 18, 25, Oct. 2 and 9. Any copy sent on receipt of 15c., or the five issues for 75c., or start sub. with any one of these issues. RADIO WORLD, 145 W. 45th St., N. Y. C.

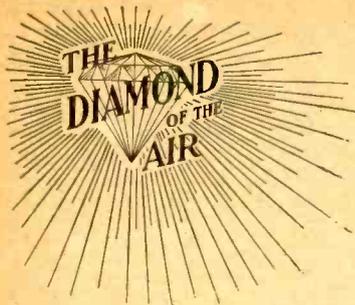THE BROWNING-DRAKE CIRCUIT—Text and illustrations covering this famous circuit starting with our issue of Aug. 14. The 3 numbers sent on receipt of 45c. RADIO WORLD, 145 W. 45th St., N. Y. C.



THE NEW IMPROVED DIAMOND OF THE AIR KIT

Manufactured by the CLAPP-EASTHAM CO., for BRUNO RADIO CORP.

The only licensed Kit that is fairly priced at \$37.50 (not \$97.50) and distributed by us direct to you to save you the difference. Every fan knows the DIAMOND OF THE AIR, created and introduced by HERMAN BERNARD one year ago. 100,000 fans have praised this wonderful Kit. All complete with blue print ready to wire—your pliers and screwdriver, all you need. ORDER YOURS NOW.

THE DIAMOND

GIVES YOU


CLARITY

QUALITY

SELECTIVITY

Direct to You

\$37.50

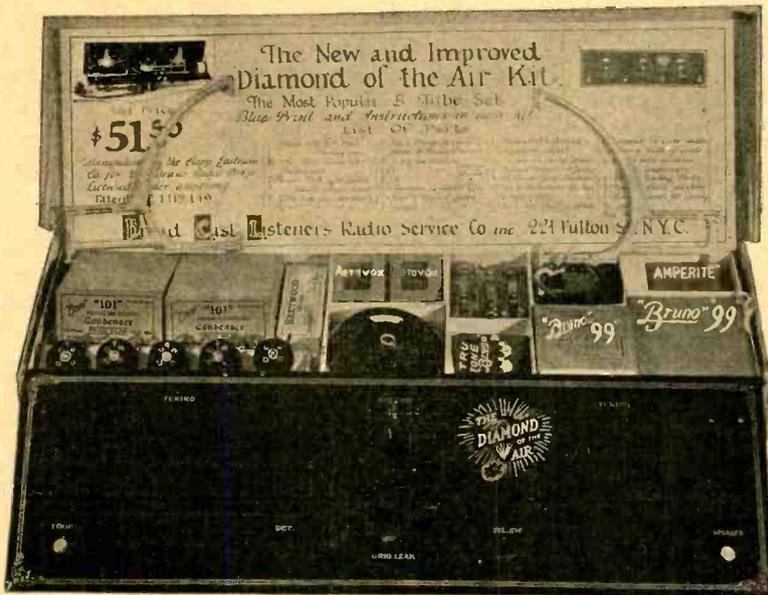

THE DIAMOND

WORKS ON A LOOP

Outside Aerial
Indoor Antenna

Direct to You

\$37.50

KIT VIEW OF THE DIAMOND OF THE AIR

Licensed Under ARMSTRONG PATENT No. 1,113,149, Exclusively for BRUNO RADIO CORPORATION
SEND FOR NEW BOOKLET MAIL ORDERS PROMPTLY FILLED

B. C. L. RADIO SERVICE CO., Inc., Dept. R. W., 221 Fulton St., NEW YORK CITY

AEROVOX

"Built Better"

Fixed Condensers and Resistors
Specified by Herman Bernard in the
**NEW, IMPROVED
"DIAMOND OF THE AIR"**

Aerovox Wireless Corp.
489-491-493 Broome St., New York City

PERFECT FILAMENT CONTROL

in the
"DIAMOND OF THE AIR"
Is Assured with AMPERITE

Eliminates hand rheostats. Simplifies set wiring. Accepted as the only perfect filament control in every popular construction set.

Radiall Company

Dept. R.W.-14, 50 Franklin St., N. Y. City



Write for
"RADIALL
BOOK"

AMPERITE

The "SELF-ADJUSTING" Rheostat

RADIO PANELS

In Quantities for Manufacturers
Century Panels Beautify the Diamond of the Air
Special Department for Individual Orders

CENTURY RADIO PANEL CO.

26-28 Barclay Street New York

HERMAN BERNARD, managing editor of RADIO WORLD, broadcasts every Friday at 7 p. m., from WGBS, Gimbel Bros., N. Y. City, 315.6 meters. He discusses "What's Your Radio Problem?" Listen in!

Bruno

TRUTONE TRANSFORMER

Specified by HERMAN BERNARD for the
"NEW IMPROVED DIAMOND of the AIR"



Bruno Trutone Transformer is designed for maximum uniform amplification over the major portion of harmonic scale, matches characteristics of all Vacuum Receiving Tubes of standard make.

Price, Ratio 3 1/2-1.....\$4.00

Write for Booklet of Complete Bruno Line

BRUNO RADIO CORPORATION

40 Paynter Avenue Long Island City, N. Y.

BLUE PRINT and Book, DIAMOND OF THE AIR sent on receipt of 50c. Guaranty Radio Goods Co., 145 West 46th Street, New York City.

General Resistor Products

Selected and Certified for the
NEW and IMPROVED

DIAMOND OF THE AIR

By RADIO WORLD Laboratories




General Resistor Co., Inc.

190 Emmett Street, Newark, N. J.

The Diamond of the Air Owes Some of Its Efficiency to This Leak

THE BRETWOOD

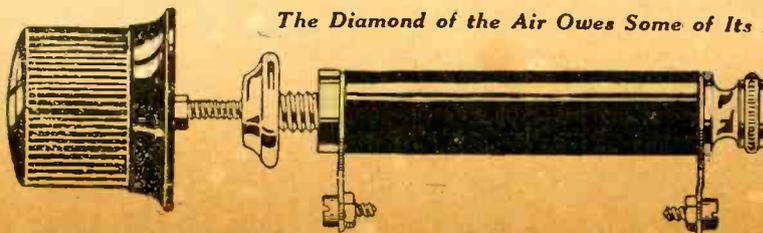Variable Grid Leak
Certified for
The Diamond



THE BRETWOOD

Improves Any Set!

Price, \$1.50

NORTH AMERICAN BRETWOOD CO., 145 West 45th Street, New York City

S. HAMMER RADIO CO.
 303 Atkins Avenue, Brooklyn, N. Y.
 Please send me FREE, Your NEW
RADIO CATALOG

Name
 Address
 City State
 FILL OUT AND MAIL

**WORLD'S FINEST
 LOUD-SPEAKER**



A three-foot cone speaker—unit developed by the inventor of the Tropadyne. Easily assembled, saving 80% of the cost. Complete Kit with blue prints sold on rigid money-back guarantee—shipped prepaid or C.O.D. \$10.

Engineers' Service Co.
 25 Church Street New York

"RAMBLER-SIX"

THE ONLY REAL PORTABLE **\$90** without tubes or batteries

Satisfaction Guaranteed
 WRITE FOR KIT PRICES
 Approved by Radio World Laboratories

American Interstate Radio Service
 183 Greenwich Street, New York City
 Distributors, Jobbers, Dealers, write for special trade terms

**Gem Tube Company
 In New Quarters**

The Gem Tube Company, pioneer tube manufacturers, and first to make and popularize a good dollar tube, have removed from 200 Broadway to much larger quarters at 16 Hudson street, New York City, one of the radio centers of the metropolis. The half floor they occupy in this large building is well laid out in the modern manner for the best service. First come the executive offices and the reception room for the trade, followed by the testing laboratories and the shipping rooms in that order. In the test room every tube receives a triple test before going on to the shipping room. In the laboratories proper their experts are continually experimenting towards the perfect tube.

The great growth of this concern in most part is due to the constant good values and satisfaction they have given the public. This is evidenced by their

TUN-A-LOOP
 THE LOOP SENSATION OF THE NEW SEASON
 AN ENGLISH-WHITMAN PRODUCT
 If your dealer cannot supply you, write for information.
 ENGLISH-WHITMAN PRODUCTS
 120 Broadway New York City

Free Mailing Lists
 Will help you increase sales
 Send for FREE catalog giving counts and prices on classified names of your best prospective customers—National, State, Local—Individuals, Professions, Business Firms.
 99% Guaranteed by refund of 5¢ each
ROSS-Gould Co. 515 N. 10th St. St. Louis

now motto, "Winning and holding good will," and the fact that they are working night and day to fill their orders. The old-timer, Lou Newman, has reached his Mecca, one also for which many are striving, and that is, the Gem tubes are now stocked in every good radio store in Greater New York and most of them all over the country. He is a hard man to see nowadays as he is so busy trying to keep the local trade supplied. Besides the New York office, this concern also has offices in Newark, Chicago, Detroit and Windsor, Canada. They will be pleased to send interesting tube facts to all who ask. Mention Radio World.

RESULTS

RESULTS EDITOR:

I have had the Diamond of the Air in my home for quite awhile and am very much satisfied with it. I have received Fort Worth, Clearwater and New York many times.

L. C. ZACHARIAS,
 Lansing, Mich.

* * *

RESULTS EDITOR:


Whenever my friends ask me which receiver is the best I always recommend the Diamond of the Air. They are all delighted with the results. These folk have made many receivers, but since building the Diamond they say that they have reached their goal.

J. WELSH,
 903 W. 8th St.,
 Cincinnati, O.

RADIO BARGAINS

FREE RADIO CATALOG & GUIDE of 1927 ideas. 164 pages of special book-ups with illustrations. Shows savings up to 50% on standard radio parts, sets, kits. Be sure to get this thrifty book before you buy. Also please send address of another radio fan. Write letter or postal NOW.
 BARAWIK CO., 560 Monroe St., CHICAGO, U. S. A.

Welty's RADIO PRODUCTS

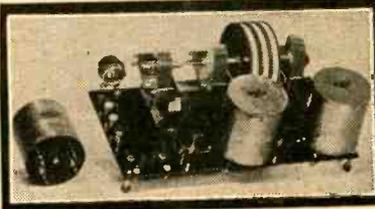

A new Welty unit. Two step tuned R. F., all wired and ready to install in any set. The condenser of NaAid made with localized tuning dials extending through the panel. All condensers may be operated simultaneously or separately. Equipped with either copper, shielded or unshielded R.F. coils of the plug in type. Absolutely dependable. Exceptional selectivity. Excellent tonal quality.

Price, with Shielded Coil.....\$32.50
 With Unshielded Coils.....\$28.50
 Separate Coils, Shielded.....\$12.50
 Separate Coils, Unshielded.....\$8.50

Ask for literature on other radio apparatus
WM. A. WELTY & CO., 36 South State St., Chicago

THE 1927 FENWAY for DX!

The something big in radio you have been waiting for is here. Published exclusively in
The Radio Man's Magazine
 249 WEST 53rd ST., NEW YORK, N. Y.
 Your Copy is Ready!
 Send us twenty-five cents.

SPECIAL PREMIUM SUBSCRIPTION OFFER
 For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements
 —To offer a year's subscription FREE for any one of the following publications with one year's subscription for RADIO WORLD

—RADIO NEWS or —BOYS' LIFE or
 —POPULAR RADIO or —RADIO DEALER or
 —SCIENCE AND INVENTION or —RADIO (San Francisco) or
 —RADIO AGE.

This is the way to get two publications
 —for the price of one:
 —Send \$6.00 today for RADIO WORLD
 —for one year (regular price)
 —for 52 numbers)
 —and select any one of the other
 —nine publications for twelve months.

—Add \$1.00 a year extra for
 —Canadian or Foreign Postage.
 —Present RADIO WORLD subscribers
 —can take advantage of this offer by
 —extending subscriptions one year
 —if they send renewals NOW!

RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK

RADIO WORLD, 145 West 45th Street, New York City.
 Enclosed find \$6.00 for which send me RADIO WORLD for twelve months (52 numbers, beginning.....
 and also without additional cost, Popular Radio, or Radio News, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or Radio Age, or Boys' Life (or \$10.00 for two yearly subscriptions). (No other premium with this offer.)


Indicate if renewal Offer Good Until October 30, 1926.

Name
 Street Address
 City and State


B S T-5 Gets Certificate of Merit

from
RADIO NEWS
and
RADIO WORLD


B—Beauty
S—Selectivity
T—Tone

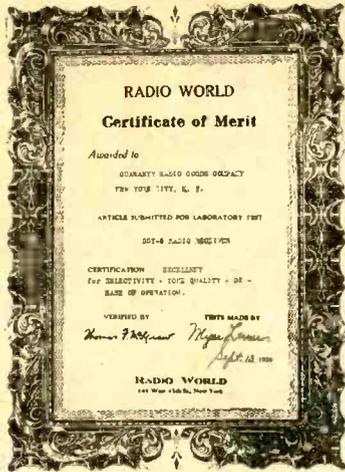

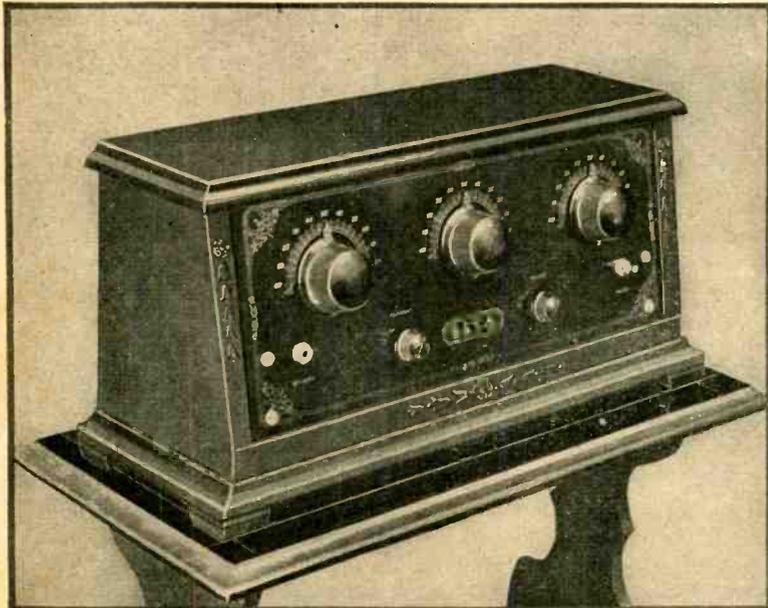1927 Model Shielded Radio Receiver
Powerful, Selective, Highly Sensitive
A \$75 Set Sold Direct From Factory at \$40



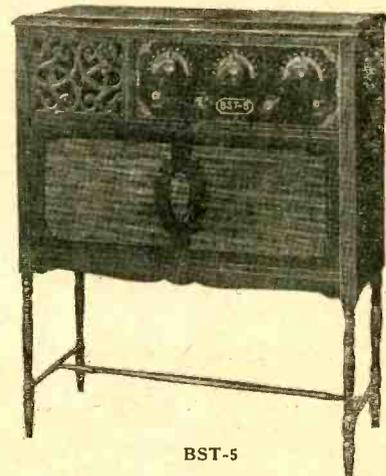New model cabinet, Du Pont Duco finish; base 21" long by 8" wide, height 9 1/2", top 21" by 6" Five-ply walnut veneer piano finish.



BST-5

RENAISSANCE MODEL CONSOLE

With built-in Utah Unit Loud Speaker and commodious compartment in which there is ample room for batteries, charger, eliminators, etc.

COMPLETE—
BST-5 RECEIVER, } **\$57.00**
Loud Speaker and Console

THIS highly sensitive, powerful and selective BST-5 radio receiver has all up-to-the-minute improvements. Heavy aluminum automobile type chassis, shielded against stray currents and distortion. Flexible grip, Universal type sockets, eliminating microphonic noises. Has provision for battery eliminator and any power tube. Fahnestock clips on sub-panel for adjusting C battery, has voltages for power tube. Efficient on either long or short aerial, including indoor aerial. This BST-5 sets a new standard for true tone values and selectivity. This BST-5 gives greater volume than many six-tube sets and consumes less current.

28 Stations in 3 1/2 Hours

Mr. E. H. Thiery, Tax Collector, New Hartford, Conn., writes: "I am well pleased with my BST. In three hours and a half last night I got the following stations: WTIC, WJZ, WGY, WBZ, WPG, WNAC, WMSG, WEEL, KDKA, WAAM, WEAN, WSAK, WJBI, WMAC, WLWL, WJAR, WAHG, WBNY, WEAF, WNJ, WCSH, WSAN, WHK, WMCA, WRVA, WHN, WHAR, WWJ."

GUARANTEE

Satisfaction or Money Back

Each receiver is tested and retested, boxed and inspected before leaving factory, and guaranteed to reach you direct in perfect condition.

Workmanship throughout guaranteed the best. Assembled by experts.

Immediate Delivery

\$40.00

BST-5 in Console - \$57.00

Send Check or P. O. Money Order

GUARANTY RADIO GOODS CO., 145 West 45th St., New York, N. Y.

RADIO WORLD Guarantees the Responsibility of This Advertiser

A BEAUTIFUL CONSOLE for YOUR HOME



New and Improved
**FRESHMAN
MASTERPIECE**

"THE ARISTOKRAT"

A one-piece Console
of finely selected

**Genuine
Mahogany**

One of the finest pieces of furniture in which
a radio receiving set has ever been installed. It
is truly an aristocrat with its distinctive, finely
proportioned lines and rich lustrous finish.

**Equipped with
the finest of
CONE SPEAKERS**

especially designed to bring forth the full merit
of the new construction of the Freshman Master-
piece circuit. Designed for the employment of
the new UX-112 Radiotron Power Tube and
the necessary "C" battery connection — all metal
SHIELDED front and sub-panel.

**Sold on easy terms by Authorized
Freshman Dealers, who also
install and service them**

**CHAS. FRESHMAN CO., INC.,
FRESHMAN BUILDING, NEW YORK**

\$99.50

GENUINE RCA RADIOTRONS

are shipped with Freshman Masterpiece Receivers — matched
and tested for each individual set. Price with this equip-
ment (one UX 112 Power Tube; one UX 200A
Detector Tube; three UX 201A Amplifying Tubes) **\$117**

Write for our beautiful new booklet illustrating
and describing our 1927 Receivers and Accessories

The World's Great Radio!