


VIRTUAL pH METER
For PC computers

PIC PROGRAMMER REVISITED
More features, easier to operate

WIN
Two Tickets
for the Air Tattoo
See Page 47

WALL OF SOUND

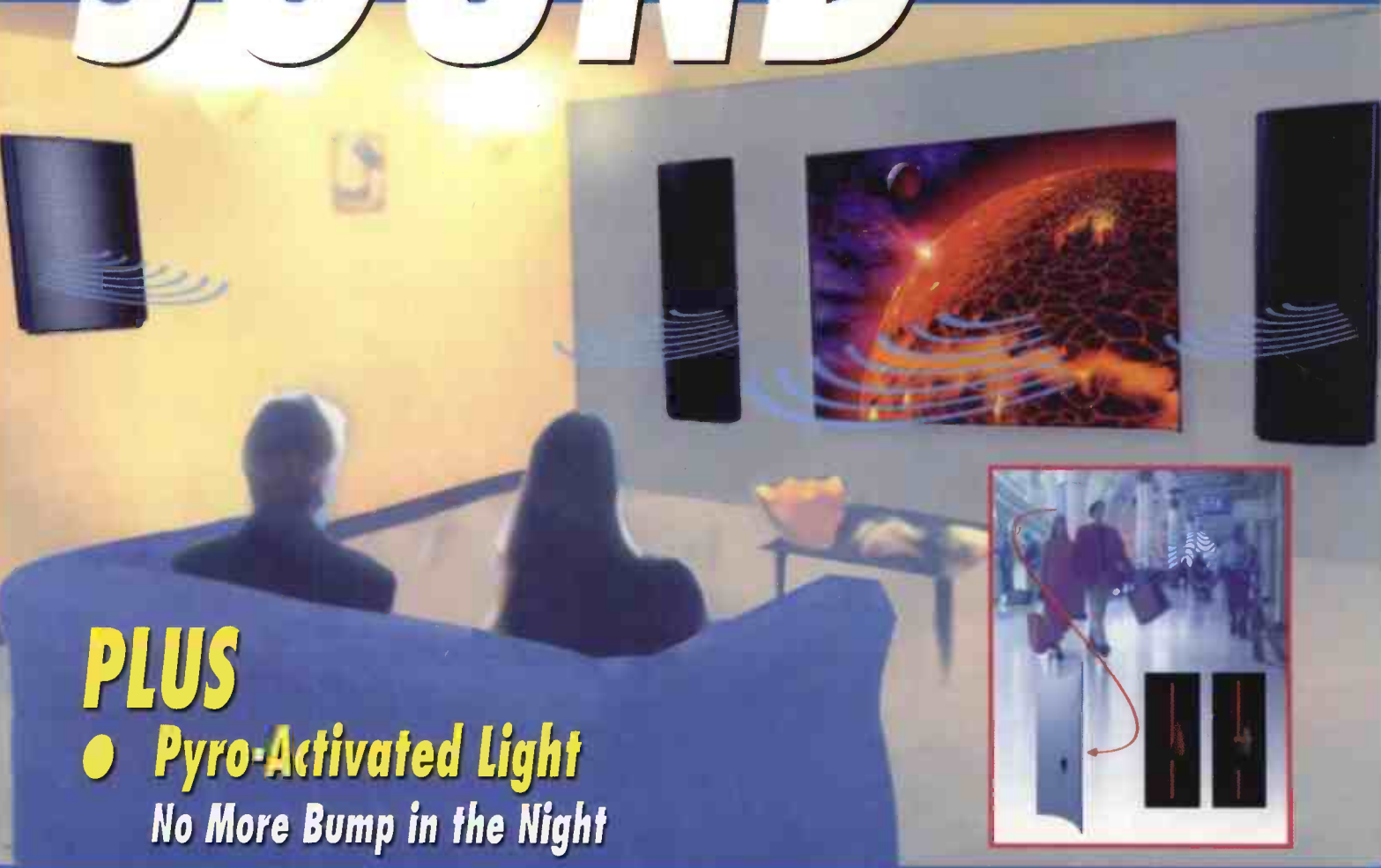**THE NEW LOUDSPEAKERS
WILL BE HEARD
AND NOT
SEEN**



PLUS

● **Pyro-Activated Light**
No More Bump in the Night

● **Light-powered
Continuity Quick-Tester**
● **Handy Moisture Meter**



"attractive to those seeking a less fraught introduction to pcb cad"

Electronics World Dec 96

For over 5 years, Quickroute has been a solution for those seeking easy to use Schematic & PCB design software. Users from all walks of life have found Quickroute's simple approach a refreshing alternative.

"probably the most intuitive of the integrated schematic-drawing and autorouter products"
Electronics World Dec 96

For example, because Quickroute integrates both schematic & PCB design into one package, you only have to learn how to use one set of tools!

"The drawing facility is logical, sequentially organised and really user-friendly"
Educational Computing & Technology Oct/Nov 96

Furthermore, with schematic capture available at the touch of a button, there is no need to mess with net-lists or files.


We haven't forgotten value for money either.

"extremely good value for money for such a comprehensive package"
Practical Wireless July 96

Quickroute 3.6 Designer costs just £149 and includes "one click" schematic capture to turn your circuit into a PCB rats-nest, auto-routing, design checking and support for drill & B.O.M files. For those seeking more power, we have Quickroute PRO+, together with a range of plug in modules and extended libraries. Phone us now or fill in the coupon for a free demonstration pack.

Tel 0161 476 0202
Fax 0161 476 0505

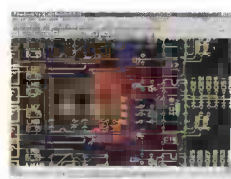WWW <http://www.quickroute.co.uk>
EMail info@quicksys.demon.co.uk



***FREE Demonstration Pack *FREE Technical Support**
***FULL Printed Documentation *Windows 3.1/95/NT Compatible**

All trademarks acknowledged & respected. Our Terms & Conditions are available on request.

Tell me more!

Quickroute Systems Ltd, Regent House, Heaton Lane, Stockport, SK4 1BS, U.K.

Name _____

Address _____

Phone/Fax _____




Contents

Volume 26 No.6

& Features Projects

Next Issue 20th June 1997

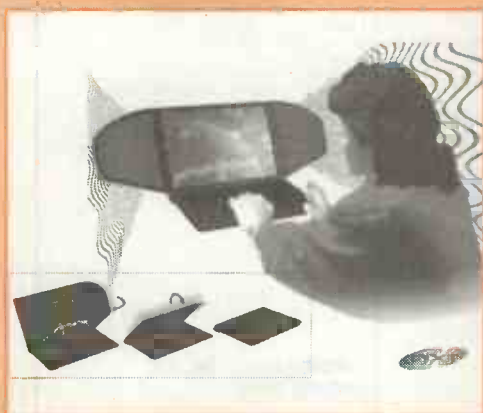

Regulars

News

PCB foils

Round the Corner

8, 9, 11

66, 68

74

Wall of Sound

13

In the future we will be able to hear our loudspeakers more clearly than ever before - even in difficult locations like railway stations and aircraft. But we may not be able to see them. Andrew Armstrong reports.

Project Designers Wanted

23

ETI is looking for new projects to publish - could one of them be yours?

Continuity Quick-Tester

25

Terry Balbirnie's continuity tester is battery-free - it works on light, even room lighting from an ordinary light bulb, and is handy for testing fuses and filament lamps, switch and relay contacts, wire or PCB continuity and faulty connections in plugs and sockets.

IR Activated Auto-Light

29

A pyro-sensor-activated safety light for indoor use, Robert Penfold's brainchild responds to movement nearby and, once switched on, remains on for a user-defined time after the last activation.

PIC Programmer Re-Visited

39

Robin Abbott's popular PIC Programmer has been updated - it now has a 40 pin multi-width ZIF socket which can take the 8-pin 12C50X, 18-pin 16C55X, 6x, 7x, 8X, F8X, and PIC14000 with an adaptor.

Win Two Tickets to the Royal International Air Tattoo

47

Use your skill to spot the difference - you may win tickets to one of Britain's fastest and most fascinating days out at the Air Tattoo.

Fast Fivers

49

The game of Put-and-Take has been popular since the Middle Ages and is still popular with modern humans of all ages. By Owen Bishop.

Virtual pH meter for use with the PC

51

Valentin Obec Roda and Ronaldo Bruno has developed the hardware and software for this scientific instrument that is easily transportable and connects to a PC.

Handy Moisture Meter

61

A simple device with two small prongs - no, not a pitchfork, but a pocket moisture-meter to put you on guard when hunting for a home, says Raymond Haigh.

ETI 1995 Index

71

All the projects and main features from ETI 1995 on a single-page index



**SUBSCRIPTIONS
& BACK ISSUES HOTLINES:**
01858 435344
ORDERS:
ENQUIRES:
01858 435322
Lines Open 9am - 6.30pm

Subscribe & Save

Phone the
hotline and take
advantage of
our special offer
detailed on
page 37

DIGITAL MULTIMETERS

CM2300 DIGITAL MULTIMETER



FEATURES:

- 3.5 LCD DISPLAY
- HEIGHT 12mm
- MAX READING 1999
- HV INDICATION FOR HIGH VOLTAGE
- SINGLE MANUAL ROTARY SWITCH FOR FUNCTION AND RANGE OPERATION
- ALL RANGES OVERLOAD PROTECTED
- 10A DC CURRENT TEST
- DC VOLTAGE 2V/20V/200V/500V
- AC VOLTAGE 200/500V
- DC CURRENT 200mA
- RESISTANCE 2K Ω /20K Ω /200K Ω /2M Ω
- SUPPLIED WITH TEST PROBES

ORDER CODE: CM2300
PRICE: 975p

CM2400T DIGITAL MULTIMETER WITH TEMP MEASUREMENT



FEATURES:

- 3.5 LCD DISPLAY
- HEIGHT 12mm
- MAXIMUM READING 1999
- 10A DC CURRENT TEST
- DC VOLTAGE 200mV/2V/20V/200V/1000V
- AC VOLTAGE 200/750V
- DC CURRENT 0.2mA/200mA/20mA/200mA/20A
- RESISTANCE 200 Ω /2K Ω /20K Ω /200K Ω /2M Ω
- SUPPLIED WITH TEST PROBES
- TEMPERATURE MEASUREMENT
- CONTINUITY TEST
- DIODE TEST & CONTINUITY CHECK
- ALL RANGES OVERLOAD PROTECTED

ORDER CODE: CM2400T
PRICE: 1450p

CM2900 PACKET DIGITAL MULTIMETER



FEATURES:

- 3.5 LCD DISPLAY
- COMPACT AND LIGHTWEIGHT POCKET SIZE
- MAXIMUM READING 1999
- DC CURRENT 7 RESISTANCE OVERLOAD PROTECTED
- SLIDE SWITCHES FOR FUNCTION AND RANGE OPERATION
- SUPPLIED IN WALLET WITH TEST PROBES
- DC VOLTAGE 2V/20V/200V/500V
- AC VOLTAGE 200V/500V
- DC CURRENT 200mA
- RESISTANCE 2K Ω /20K Ω /200K Ω /2M Ω

ORDER CODE: CM2900
PRICE: 1150p

CM3900A DIGITAL MULTIMETER



FEATURES:

- LARGE LCD DISPLAY
- HEIGHT 18mm
- MAXIMUM READING 1999 + UNIT
- SINGLE MANUAL ROTARY SWITCH FOR FUNCTION AND RANGE OPERATION
- AUTO POWER OFF (APPROX 15 min)
- DIODE TEST FUNCTION
- ALL RANGES OVERLOAD PROTECTED
- SUPPLIED WITH TEST PROBES
- DC VOLTAGE: 200mV/2V/20V/200V/700V ACCURACY $\pm 0.5\%$
- AC VOLTAGE: 200mV/2V/20V/200V/700V
- DC CURRENT A: 200 μ A/20mA/200mA/2A/20A
- AC CURRENT A: 200 μ A/20mA/200mA/2A/20A
- RESISTANCE: 200 Ω /2K Ω /20K Ω /200K Ω /2M Ω /20M Ω

ORDER CODE: CM3900A
PRICE: 2900p

CM3920 DIGITALMETER WITH TEMP MEASUREMENT



FEATURES:

- TEMPERATURE MEASUREMENT
- DIODE & TRANSISTOR HFE TEST
- LARGE LCD DISPLAY
- HEIGHT 18mm
- MAXIMUM READING 1999 + UNIT
- SINGLE MANUAL ROTARY SWITCH FOR FUNCTION AND RANGE OPERATION
- AUTO POWER OFF (APPROX 15 mins)
- DIODE TEST FUNCTION
- ALL RANGES OVERLOAD PROTECTED
- SUPPLIED WITH TEST PROBES
- DC VOLTAGE: 200mV/2V/20V/200V/1000V ACCURACY $\pm 0.5\%$
- AC VOLTAGE: 200mV/2V/20V/200V/700V
- DC CURRENT 2mA/20mA/200mA/20A
- AC CURRENT A: 200mA/20A
- RESISTANCE: 200 Ω /2K Ω /20K Ω /200K Ω /2M Ω /20M Ω
- CAPACITANCE: 2nF/20nF/200nF/2 μ F/20 μ F

ORDER CODE: CM3920
PRICE: 4100p

CM2700 AUTORANGING DIGITAL MULTIMETER



FEATURES:

- 3.75 LCD DISPLAY WITH DECIMAL POINT
- 33 SEGMENT BARGRAPH DISPLAY
- OVERRANGE INDICATION
- ROTARY SWITCH FOR FUNCTION SELECTION
- AUTO POWER OFF (APPROX 15 mins)
- AUTO POLARITY WITH INDICATION
- DIODE TEST & CONTINUITY TEST WITH BUZZER
- ALL RANGES OVERLOAD PROTECTED
- LOW BATTERY INDICATION
- SUPPLIED WITH TEST PROBES
- DC VOLTAGE: 320mV/3.2V/32V/320V/600V
- AC VOLTAGE: 320mV/3.2V/32V/320V/600V
- DC CURRENT A: 320 μ A/3200 μ A/32mA/320mA/10A
- AC CURRENT A: 320 μ A/3200 μ A/32mA/320mA/10A
- RESISTANCE: 320 Ω /3.2K Ω /32K Ω /320K Ω /3.2M Ω /32M Ω

ORDER CODE: CM2700
PRICE: 4050p

CM3230 DIGITAL CAPACITANCE METER



FEATURES:

- 3.5 LCD DISPLAY
- HEIGHT 18mm
- MAXIMUM READING 1999
- CAPACITANCE 9 RANGES FROM 200pF-20000 μ F
- MEASURING FROM 1pF - 20000 μ F
- SINGLE MANUAL ROTARY SWITCH FOR FUNCTION AND RANGE OPERATION
- ZERO ADJUST KNOB

ORDER CODE: CM3230
PRICE: 3950p

8 Way Preprogrammed Universal Remote Control



A single remote control to operate Television, Videos and Satellite Receivers. Plus Auxiliary Options!!

- Replaces up to 8 remotes with one
- Simple 4 digit setup routine
- Controls 1000's of models
- Teletext functions with Fastext
- Clear (large key) layout
- Code Search Facility
- Stylish and easy to operate
- Replace broken or lost remotes
- Original Remote note required

Order Code: 8 WAY
Price: 1450P + VAT

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,
SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB
Telephone: 0181-900 2329 Fax: 0181-903 6126
OPEN Monday to Saturday.
Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE
HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR
LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt, Colleges, etc.
Orders accepted. Please allow 7 days for delivery. Prices quoted are subject
to stock availability and may be changed without notice.

TV and video parts sold are replacement parts.

Access & Visa Card accepted
WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA
SERIES. PLEASE RING US FOR FURTHER INFORMATION.

SATELLITE POWER SUPPLY REPAIR KITS

ALBA	CODE	ECHOSTAR	CODE	MIMTEC	CODE
SAT660	SATPSU2	SR5500 EARLY PSU WITH ADJ 6500, SR7700, SR8700	SATPSU12 SATPSU13	SOPRENSEN TYPE PSU ONLY	SATPSU15
AMSTRAD	CODE	FIGURON	CODE	NETWORK	CODE
SRD510, SRD520, SRD540, SRD550	SATPSU3	SRD 5, SRD16	SATPSU1	9000, 9200	SATPSU2
SRDR45		SRV1	SATPSU2	NOKIA	CODE
SRD500	SATPSU4	SRDE4	SATPSU11	SAT1500	SATPSU2
SRX320, SRX340, SRX345, SRX350	SATPSU5	FINLUX	CODE	PAGE	CODE
SRX100	SATPSU6	SR5700	SATPSU12	PRD800, PRD900, PSR800, PSR900	SATPSU1
SRD600	SATPSU14	GOODMANS	CODE	MRD920, SS9000, SS9010, SS9200,	SATPSU2
SAT250, SR950, SRD700, SRD950,	SATPSU16	ST700	SATPSU1	SS9210, SS9220	
SRX1002, SRX2001, SRX301,				D100, D150,	SATPSU6
SRX501, SRX502				MSS100	SATPSU8
SRD2000	SATPSU18			APOLLO, MSS200, MSS300	SATPSU9
				MSS500, MSS1000	SATPSU10
BRITISH TELECOM	CODE	GRUNDIG	CODE	PHILIPS	CODE
SVS300	SATPSU17	STR1	SATPSU1	STU802/05M	SATPSU1
BUSH	CODE	GIRD200, FIRD3000	SATPSU2	STU801	SATPSU2
IRD150	SATPSU12	MANHATTAN	CODE	THOMSON	CODE
IRD155	SATPSU19	850, 950	SATPSU1	SRS4	SATPSU2
CHURCHILL	CODE	MASPRO	CODE	TOSHIBA	CODE
D3MAC DECODER	SATPSU7	SRE250S/1, SRE350S/1	SATPSU1	SAT99, TU-SDU200	SATPSU1
		SRE250S, SRE350S, SRE450S	SATPSU2		

CODE	PRICE	CODE	PRICE	CODE	PRICE	CODE	PRICE
SATPSU1	650p	SATPSU6	650p	SATPSU11	835p	SATPSU16	730p
SATPSU2	650p	SATPSU7	650p	SATPSU12	1735p	SATPSU17	850p
SATPSU3	650p	SATPSU8	730p	SATPSU13	3125p	SATPSU18	1175p
SATPSU4	650p	SATPSU9	900p	SATPSU14	3135p	SATPSU19	650p
SATPSU5	650p	SATPSU10	1230p	SATPSU15	77.5p		

PACE SATELLITE TUNERS

MODELS	CODE	PRICE
PRD800, MSS200 (2GHZ) (221-2077062)	TUNER01	1650p
PRD900, MSS500, MSS1000 (2Ghz) (221-2177012)	TUNER02	1650p

PACE SWITCH MODE TRANSFORMERS

MODELS	CODE	PRICE
PACE9000	PACE9000	800p
PACEPRD800, PRD900	PRD800	550p

SATMETER

THE SATMETER IS A PROFESSIONAL PORTABLE SATELLITE STRNTH METER DESIGNED FOR THE INSTALLATION AND MAINTENANCE OF SATELLITE TV SYSTEMS. THE SATMETER CAN BE USED AS STAND ALONE METER WITH POWERING THE LNB AS WELL AS IN LOOP. THROUGH OPERATION WITH SATELLITE RX POWERING THE LNB.

ACOUSTICAL SIGNAL: ON SIGNAL STRENGTH
INPUT IMPEDENENCE: 75 Ohm
MAX.INPUT SIGNAL: -10 DBM

LED INDICATOR: VERTICAL/HORIZONTAL
POWER AMPLIFIER: 18 DB

FREQUENCY RANGE: 900 TO 2050 MHZ
DETECTION RANGE: -60 TO -10 DBM

ORDER CODE: TOOL 22 PRICE: 8500p

SATELLITE LNB'S

MAKE & MODEL	ORDER CODE	PRICE	MAKE & MODEL	ORDER CODE	PRICE
Cambridge AE22/AE5 0.8dB standard 10.95-11.70 GHz Gold Range	LNB1	2160p	Cambridge AE7 Twin O/P H+V Both Enhanced	LNB7	4000p
Cambridge AE14 Universal LNB 10.7-11.7/11.7-12.75 GHz	LNB2	2500p	Cambridge AE2 Dual O/P H+V Separate Enhanced	LNB8	3550p
Cambridge AE21/AE5 Single O/P Switching LNB 1.0dB Standard	LNB3	2050p	Grundig Super Universal 'Anis' 10.7-12.75 GHz 0.8dB	LNB9	2600p
Cambridge AE19/AE6 Single O/P Switching LNB 1.0dB Enhanced	LNB4	2050p	Grundig Universal 'Anis' 10.7-12.75 GHz 1.0dB	LNB10	2250p
Cambridge AE23/AE12 0.8dB Enhanced 10.7-11.8GHz Gold Range	LNB5	2160p	Cambridge AE1 Twin O/P H+V Both Standard	LNB11	4000p
Cambridge AE8 Dual O/P H+V Separate Enhanced	LNB6	4000p			

FUSES

CURRENT RATING	TIME LAG (20MM)		QUICK BLOW (20MM)	
	ORDER CODE	PRICE	ORDER CODE	PRICE
100mA	FUSE36	75p	FUSE37	60p
160mA	FUSE01	75p	FUSE17	60p
250mA	FUSE02	75p	FUSE18	60p
315mA	FUSE03	75p	FUSE19	60p
400mA	FUSE04	75p	FUSE20	60p
500mA	FUSE05	75p	FUSE21	60p
630mA	FUSE06	75p	FUSE22	60p
800mA	FUSE07	60p	FUSE23	60p
1A	FUSE08	60p	FUSE24	60p
1.25A	FUSE09	60p	FUSE25	60p
1.6A	FUSE10	60p	FUSE26	60p
2A	FUSE11	50p	FUSE27	60p
2.5A	FUSE12	50p	FUSE28	60p
3.15A	FUSE13	55p	FUSE29	50p
4A	FUSE14	55p	FUSE30	50p
5A	FUSE15	60p	FUSE31	50p
6.3A	FUSE16	60p	FUSE32	50p

CERAMIC PLUG TOP

CURRENT RATING	ORDER CODE	PRICE
3A	FUSE33	100p
5A	FUSE34	100p
13A	FUSE35	100p

20mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
6.3A	FUSE38	100p
8A	FUSE39	100p
10A	FUSE40	100p
3.15A	FUSE41	85p
4A	FUSE42	85p
5A	FUSE43	85p

38mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
10A	FUSE48	815P

32mm CERAMIC SLOW BLOW

CURRENT RATING	ORDER CODE	PRICE
8A	FUSE44	185P
10A	FUSE45	185p
15A	FUSE46	185p
20A	FUSE47	210p

NB.

ALL FUSES ARE MADE IN THE UK AND FULLY MEET BS4265 & BS1362 SAFETY STANDARDS AND SHOULD NOT BE COMPARED WITH CHEAP IMPORTED TYPES.

****ALL THE ABOVE PRICES ARE FOR PACKS OF 10 FUSES****

TRANSISTORS

PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE
AC125	30P	BD647	50P	BU409	85P	BUX48A	150P	MPSA14	15P	2N3553	100P
AC126	30P	BD649	50P	BU412	175P	BUX55	180P	MPSA20	15P	2N3585	650P
AC127	30P	BD675	40P	BU413	175P	BUX80	160P	MPSA42	15P	2N3702	9P
AC128K	40P	BD676	40P	BU414B	250P	BUX81	160P	MPSA43	15P	2N3703	9P
AC141K	45P	BD677	38P	BU415A	170P	BUX84	50P	MPSA44	40P	2N3704	9P
AC176	22P	BD678	40P	BU426A	70P	BUX85	50P	MPSA55	12P	2N3705	9P
ACY18	48P	BD679	40P	BU433	120P	BUX86	50P	MPSA56	12P	2N3706	9P
ACY19	48P	BD680	40P	BU500	100P	BUX87	50P	MPSA70	15P	2N3707	9P
AD149	60P	BD681	45P	BU500D	225P	BUX88A	350P	MPSA92	20P	2N3710	12P
AF125	50P	BD682	45P	BU505	60P	BUY18S	150P	MPSA93	20P	2N3711	12P
AF139	8P	BD705	50P	BU505D	90P	BUY47	150P	MPSU10	200P	2N3717	85P
BC107	8P	BD707	50P	BU505DF	90P	BUY57	125P	MPSU45	550P	2N3722	90P
BC108	8P	BD709	50P	BU506	100P	BUY69A	200P	MPSU56	400P	2N3733	100P
BC109C	8P	BD711	50P	BU506D	70P	BUY71	250P	MPSU60	350P	2N3732	150P
BC140	10P	BD736	50P	BU506DF	120P	BUZ10	65P	MR510	35P	2N3739	18P
BC140	20P	BD826	50P	BU508A	70P	BUZ11	200P	MR556	36P	2N3819	29P
BC143	20P	BD828	50P	BU508AF	95P	BUZ11A	175P	OC28	350P	2N3820	70P
BC142	20P	BD839	55P	BU508APH	80P	BUZ14	550P	OC29	250P	2N3823	40P
BC149	8P	BD897	50P	BU508D	90P	BUZ20	225P	OC35	350P	2N3866	110P
BC149	8P	BD899	50P	BU508DF	115P	BUZ21	250P	OC36	250P	2N3903	11P
BC159	8P	BD977	50P	BU508DR	130P	BUZ24	350P	OC45	50P	2N3906	11P
BC160	30P	BDX33	60P	BU508V	110P	BUZ25	450P	OC200	180P	2N3958	375P
BC171	10P	BDX37	100P	BU508VF	100P	BUZ32	125P	R2008B	100P	2N3958	375P
BC172	10P	BDX44	100P	BU526	75P	BUZ36	800P	R2010B	100P	2N4031	25P
BC177	14P	BDX47	75P	BU536	100P	BUZ44A	525P	S2000AF	175P	2N4033	25P
BC178	14P	BDX54C	75P	BU546	125P	BUZ45A	800P	S2000AF	175P	2N4036	25P
BC179	14P	BDX62C	150P	BU603	125P	BUZ50B	500P	S2055A	175P	2N4220	175P
BC182	7P	BDX63C	175P	BU606D	225P	BU53A	800P	S2055AF	200P	2N4347	130P
BC182L	7P	BDX64C	175P	BU608D	120P	BUZ71	75P	S2530A	100P	2N4391	60P
BC183	7P	BDX65	175P	BU626	120P	BUZ71AF	100P	S2800M	72P	2N4392	50P
BC183L	7P	BDX66C	175P	BU705	130P	BUZ72A	100P	TIP29	15P	2N4393	55P
BC184	7P	BDX67C	275P	BU706DF	175P	BUZ72AF	100P	TIP29A	22P	2N4399	200P
BC184L	7P	BDX71	70P	BU706F	150P	BUZ73A	150P	TIP29C	25P	2N4401	12P
BC212	7P	BDX77	175P	BU724A	100P	BUZ76A	110P	TIP29E	25P	2N4403	12P
BC212L	7P	BDX87C	175P	BU801	70P	BUZ80	200P	TIP30	25P	2N4416	120P
BC213	7P	BDX88C	150P	BU806	70P	BUZ80AF	200P	TIP30C	25P	2N4420	75P
BC213L	7P	BDW24	55P	BU807	60P	BUZ83	200P	TIP31A	22P	2N4427	75P
BC214	7P	BDW93	50P	BU807F	75P	BUZ90A	180P	TIP31C	27P	2N4920	50P
BC214L	7P	BDW94	50P	BU808DF	300P	BUZ91A	400P	TIP32	24P	2N4922	30P
BC237	7P	BDY29	225P	BU810	110P	BY448	20P	TIP32A	21P	2N4923	30P
BC238	7P	BDY56	225P	BU824	120P	BYT11	25P	TIP32C	28P	2N5038	175P
BC239	7P	BDY58	500P	BU826	120P	C106D	28P	TIP33	50P	2N5061	20P
BC300	20P	BDY90	125P	BU826A	110P	COY80	40P	TIP33C	60P	2N5088	20P
BC301	20P	BDY92	100P	BU902	110P	IRF120	225P	TIP34	65P	2N5109	100P
BC302	20P	BF137	35P	BU903	110P	IRF130	475P	TIP34C	60P	2N5116	175P
BC303	20P	BF167	30P	BU910	80P	IRF140	550P	TIP35C	65P	2N5154	150P
BC304	25P	BF181	18P	BU912	100P	IRF230	550P	TIP36C	65P	2N5160	600P
BC327	7P	BF183	7P	BU920	100P	IRF240	425P	TIP42A	20P	2N5179	40P
BC328	7P	BF195	7P	BU922	110P	IRF250	75P	TIP41C	22P	2N5192	50P
BC337	7P	BF199	7P	BU930	100P	IRF330	600P	TIP42A	20P	2N5241	500P
BC338	7P	BF200	16P	BU932	175P	IRF340	325P	TIP42C	22P	2N5245	45P
BC441	28P	BF225	30P	BU941	250P	IRF350	750P	TIP47	40P	2N5294	30P
BC446	8P	BF240	16P	BU2508A	130P	IRF450	650P	TIP48	40P	2N5296	30P
BC477	18P	BF245	25P	BU2508AF	130P	IRF10	150P	TIP50	60P	2N5320	50P
BC516	22P	BF254	12P	BU2508D	130P	IRF520	150P	TIP51	80P	2N5322	55P
BC537	25P	BF255	15P	BU2508DF	225P	IRF530	150P	TIP52	80P	2N5401	10P
BC546	8P	BF256	18P	BU2520AF	225P	IRF540	200P	TIP54	85P	2N5416	40P
BC547	8P	BF257	18P	BU2520DF	225P	IRF610	150P	TIP102	70P	2N5448	12P
BC548	8P	BF259	18P	BU2525A	325P	IRF611	150P	TIP105	65P	2N5457	45P
BC549	8P	BF262	25P	BU2525AF	325P	IRF620	160P	TIP106	65P	2N5458	55P
BC550	8P	BF270	18P	BU2527AF	400P	IRF630	150P	TIP107	65P	2N5460	55P
BC556	8P	BF273	15P	BU2527AF	400P	IRF640	150P	TIP110	40P	2N5461	75P
BC557	7P	BF311	21P	BU405A	200P	IRF642	200P	TIP111	40P	2N5462	45P
BC558	8P	BF336	20P	BUH15D	250P	IRF650	200P	TIP112	35P	2N5484	55P
BC559	8P	BF337	20P	BUH15	200P	IRF710	150P	TIP112H	50P	2N5551	12P
BC560	8P	BF338	20P	BUH15D	250P	IRF720	150P	TIP115	30P	2N5671	350P
BC637	20P	BF362	30P	BUH157	275P	IRF730	150P	TIP116	30P	2N5672	400P
BC639	20P	BF367	13P	BUH157D	17P	IRF740	150P	TIP117	30P	2N5680	55P
BC640	20P	BF371	17P	BUH171	425P	IRF820	150P	TIP120	37P	2N5884	175P
BCY33	200P	BF421	18P	BUH93	375P	IRF830	160P	TIP121	35P	2N5886	325P
BCY34	200P	BF422	21P	BUK444	200P	IRF840	150P	TIP122	30P	2N6031	250P
BCY70	16P	BF423	25P	500B		IRF9140	1000P	TIP125	30P	2N6049	55P
BCY71	16P	BF455	12P	BUK444	200P	IRF9150	150P	TIP126	40P	2N6059	150P
BCY72	16P	BF458	19P	800B		IRF9151	150P	TIP127	35P	2N6088	50P
BD115	30P	BF462	50P	BUK445	200P	IRF920	150P	TIP130	30P	2N6089	45P
BD124P	25P	BF471	28P	600B		IRF930	400P	TIP131	30P	2N6107	40P
BD131	25P	BF472	28P	BUK446	400P	IRF933	200P	TIP132	30P	2N6109	40P
BD133	50P	BF479	30P	800B		IRF940	300P	TIP136	40P	2N6211	400P
BD135	20P	BF494	16P	BUK455	200P	IRF9541	200P	TIP137	65P	2N6248	150P
BD136	20P	BF495	16P	600B		IRF9510	150P	TIP162	110P	2N6284	250P
BD137	20P	BF595	16P	BUK456	200P	IRF9620	150P	TIP141	65P	2N6287	225P
BD138	20P	BF596	16P	BUW81A	150P	IRF9622	150P	TIP143	75P	2N6292	40P
BD139	20P	BF615	30P	BUW81	190P	IRF9630	325P	TIP145	50P	2N6385	120P
BD140	20P	BF617	30P	BUR52	190P	IRF9640	375P	TIP146	70P	2N6403	160P
BD144	90P	BF760	40P	BUS11A	100P	IRFD9220	100P	TIP147	80P	2N6427	25P
BD157	38P	BF763	40P	BUS12A	200P	IRFBC30	200P	TIP150	90P	2N6476	250P
BD166	30P	BF780	22P	BUS14A	500P	IRFBC40	400P	TIP151	60P	2N6488	90P
BD175	30P	BF871	22P	BUS23	225P	IRFP140	250P	TIP295S	50P	2N6491	90P
BD177	30P	BF960	35P	BUS48A	175P	IRFP150	300P	TIP305S	50P	2N6547	300P
BD179	32P	BF961	38P	BUT11A	55P	IRFP240	300P	TIP1760	100P	2N6609	375P
BD181	45P	BF964	38P	BUT11AF	55P	IRFP250	400P	TIP1762A	200P	2N6660	375P
BD182	60P	BFQ232	75P	BUT12	80P	IRFP350	325P	TIP1763A	200P	2N6675	175P
BD182	60P	BFQ252A	60P	BUT13	310P	IRFP450	400P	TIP1791A	80P	2N6678	225P
BD184	60P	BFQ90	85P	BUT18	80P	IRFP460	775P	TIS61	15P	4N35	50P
BD187	30P	BFQ91	99P	BUT18AF	1700P	IRFP9140	1450P	TIS90	15P		
BD201	38P	BFQ93	30P	BUT30V	100P	IRFP9240	500P	TIS93	20P	RECTIFIER DIODES	
BD202	38P	BFQ99	30P	BUT56A	600P	IRFPC50	600P	TXS107	11P		
BD203	42P	BFQ84	20P	BUT76A	80P	IRFRC20	250P	ZTX108	11P	BY127	8P
BD204	42P	BFQ85	20P	BUT90	1300P	IRFZ20	65P	ZTX109	12P	BY133	20P
BD222	31P	BFQ87	15P	BUT92	1200P	IRFZ44	275P	ZTX212	10P	BY164	40P
BD225	31P	BFQ88	15P	BUT18	650P	IRFZ44	275P	ZTX300	16P	BY179	35P
BD232	31P	BFQ89	15P	BUT20	650P	MJ900	200P	ZTX302	10P	BY184	32P
BD233	30P	BFQ90	14P	BUT21	400P	MJ10001	200P	ZTX303	20P	BY206	11P
BD234	32P	BFQ91	24P	BUT23	475P	MJ1001	200P	ZTX330	10P	BY207	19P
BD235	28P	BFQ92	14P	BUT25	350P	MJ2501	100P	ZTX340	20P	BY227	20P
BD236	30P	BFQ93	25P	BUT26	110P	MJ2955	55P	ZTX350	10P	BY228	19P
BD237	21P	BFQ94	25P	BUT27	150P	MJ3000	100P	ZTX502	10P	BY298	15P
BD238	24P	BFQ95	45P	BUT28	125P	MJ3001	100P	ZTX503	18P	BY299	18P
BD239	30P	BFQ96	85P	BUT28	110P	MJ4032					

TRANSISTORS

PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE
I.C. SOCKETS		1A/50V	18p	TIC116C	59p	8156	300p	4075	13p
8 PIN	4P	W01		8A/300V	240p	8224	240p	4076	42p
14 PIN	5P	1A/100V	19p	TIC116D	70p	8226	240p	4077	13p
18 PIN	6P	W02		8A/400V	75p	8250	75p	4078	13p
20 PIN	9P	1A/200V	21p	TIC126D	90p	8251	200p	4081	13p
22 PIN	10P	W04		12A/400V	28p	8253	160p	4082	13p
24 PIN	12P	LA/400V	23p	TIC126M	28p	8257	220p	4085	36p
28 PIN	13P	W06		12A/600V	37p	8271	340p	4086	30p
40 PIN	15P	LA/600V	28p	4A/400V	37p	8279	270p	4089	75p
ZENER DIODES		BR810	33p	BR103	28p	8283	400p	4093	18p
400m	WATT	2A/100V	33p	BR106	180p	8284	440p	4094	44p
2V7 TO 39V	5P	BR82D	33p	BT119	100p	8287	260p	4094	44p
1.3	WATT	2A/200V	37p	17088	200p	8288	650p	4098	50p
2V7 TO 39V	9P	BR84D	37p	17089	200p	82C206PLCC	500p	4099	42p
VOLTAGE REGULATORS		2A/400V	43p	17127	200p	8748	700p	4501	26p
7805	25P	BR86D	43p	15/80H	230p	8755	800p	4502	36p
7806	25P	2A/600V	43p	15/85R	230p	8726	95p	4504	35p
7808	25P	BR88D	43p	SG 264	800p	8728	110p	4505	80p
7812	25P	2A/800V	43p	SG613	1500p	CMOS IC's		4506	58p
7815	25P	BR32	43p	COMPUTER IC's		4507	30p	4507	50p
7818	25P	2A/200V	43p	Z80ACPU	1000p	4508	67p	4510	32p
7824	25P	BR34	43p	Z80ADMA	2000p	4511	30p	4511	30p
7905	25P	2A/400V	43p	Z80ACTC	140p	4512	38p	4512	38p
7906	25P	BR62	80p	Z80ASIO-1	210p	4514	65p	4514	65p
7908	25P	6A/200V	72p	Z80ASIO-2	210p	4515	36p	4515	36p
7912	25P	BR64	72p	75107	65p	4516	100p	4516	100p
7915	25P	6A/400V	150p	75110	13p	4517	36p	4517	36p
7918	25P	BR251	150p	75113	13p	4518	28p	4518	28p
7924	25P	25A/100V	165p	75122	110p	4519	28p	4519	28p
7924	25P	BR252	165p	75164	100p	4520	33p	4520	33p
7924	25P	2A/200V	185p	75162	700p	4521	36p	4521	36p
7924	25P	BR254	185p	75183	95p	4522	36p	4522	36p
7924	25P	25A/400V	200p	BR2155	200p	4523	13p	4523	13p
7924	25P	25A/600V	240p	2114	150p	4524	25p	4524	25p
7924	25P	BR258	240p	2532	200p	4525	13p	4525	13p
7924	25P	25A/800V	185p	26LS32	75p	4526	60p	4526	60p
7924	25P	BR351	200p	2716	100p	4527	30p	4527	30p
7924	25P	35V/100V	220p	2732	200p	4528	33p	4528	33p
7924	25P	35V/200V	220p	2732A	220p	4529	36p	4529	36p
7924	25P	BR354	220p	2764	200p	4530	17p	4530	17p
7924	25P	35V/400V	230p	27C64	200p	4531	52p	4531	52p
7924	25P	BR356	230p	27128	150p	4532	60p	4532	60p
7924	25P	35V/600V	260p	27258-25	150p	4533	38p	4533	38p
7924	25P	BR358	260p	27512	300p	4534	76p	4534	76p
7924	25P	35V/800V	40p	4116	40p	4535	42p	4535	42p
7924	25P	BY164	40p	4164-15	80p	4536	46p	4536	46p
7924	25P	1.5A/100V	40p	41256-15	80p	4537	30p	4537	30p
7924	25P	BY176	40p	41256-12	100p	4538	36p	4538	36p
7924	25P	1.5A/800V	40p	41256-10	110p	4539	72p	4539	72p
L.E.D.'s 3mm		TRIACS		41464-12	150p	4540	36p	4540	36p
RED	5p	TIC206D	60p	6116	80p	4541	36p	4541	36p
YELLOW	8p	4A/400V	69p	6264-10	210p	4542	30p	4542	30p
GREEN	8p	TIC225D	68p	62256-12	300p	4543	36p	4543	36p
5mm	5p	6A/400V	85p	6502A	360p	4544	36p	4544	36p
RED	8p	TIC226D	105p	65C02	930p	4545	26p	4545	26p
YELLOW	8p	8A/400V	105p	6522	280p	4546	18p	4546	18p
GREEN	8p	TIC235D	205p	6800	210p	4547	38p	4547	38p
RECTANGULAR LED's		12A/400V	105p	6802	220p	4548	35p	4548	35p
5mm x 2.5mm	5p	TIC246D	105p	6803	500p	4549	50p	4549	50p
RED	8p	16A/400V	190p	6808	500p	4550	52p	4550	52p
YELLOW	8p	TIC253D	190p	6810	150p	4551	40p	4551	40p
GREEN	8p	20A/400V	205p	6818	380p	4552	52p	4552	52p
BRIDGE RECTIFIER		TIC263D	205p	6821	130p	4553	20p	4553	20p
W005	16p	25A/400V	20p	6840	290p	4554	120p	4554	120p
THYRISTORS		2N5061	20p	6845	200p	4555	13p	4555	13p
THYRISTORS		0.8A/60V	20p	6850	90p	4556	13p	4556	13p
THYRISTORS				74F244	35p	4557	32p	4557	32p
THYRISTORS				8085A	300p	4558	20p	4558	20p
THYRISTORS				8086	500p	4559	25p	4559	25p
THYRISTORS				8088	480p	4560	15p	4560	15p

SERVICE AIDS

DESCRIPTION	VOLUME	CODE	PRICE	DESCRIPTION	VOLUME	CODE	PRICE
VIDEO HEAD CLEANER	75ML	SP01	180p	EXCEL POLISH 80	250ML	SP18	150p
VIDEO HEAD CLEANER	200ML	SP27	250p	ADHESIVE 120	400ML	SP19	190p
SWITCH CLEANER	176ML	SP02	180p	LABEL REMOVER 130	200ML	SP20	240p
SUPER 40	400ML	SP15	250p	REFURB 140	400ML	SP21	240p
SILICONE GREASE	200ML	SP03	210p	TUBE SILICON GREASE	50 GRAMMES	SP11	220p
FREEZE IT	170ML	SP04	320p	TUBE TUBE SILICON			
FREEZE IT	400ML	SP16	600p	SEALANT WHITE	75ML	SP22	280p
FOAM CLEANER	400ML	SP05	200p	TUBE SILICON SEALANT			
ANTI STATIC	200ML	SP06	190p	CLEAR	75ML	SP23	280p
AEROKLEANE	200ML	SP07	220p	TUBE HEAT SINK COMPUND	25 GRAMMES	SP12	150p
AERO DUSTER	150ML	SP08	310p	DRIVE CLEANER	200ML	SP24	150P
AERO DUSTER	400ML	SP17	550p	SCREEN CLEANER	200ML	SP25	150p
PLASTIC SEAL	200ML	SP09	250p	COMPUTER CARE KIT		SP26	2100p
GLASS CLEANER	250ML	SP10	160p	ANTI STATIC FOAM CLEANER	400ML	SP28	175p
COLDKLENE	250ML	SP13	230p	AIR DUSTER	400ML	SP29	450p

ALL THE ABOVE ITEMS ARE MANUFACTURED BY SERVISOL

IF YOU PURCHASE MORE THAN ONE SERVISOL PRODUCT POSTAGE & PACKING WILL BE CHARGED AS FOLLOWS:

300P FOR 5 CANS

450p FOR MORE THAN 5 CANS

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,
SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB

Telephone: 0181-900 2329 Fax: 0181-903 6126

OPEN Monday to Saturday.

Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE
HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR
LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt. Colleges, etc.
Orders accepted. Please allow 7 days for delivery. Prices quoted are subject
to stock availability and may be changed without notice.

TV and video parts sold are replacement parts.

Access & Visa Card accepted

WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA
SERIES. PLEASE RING US FOR FURTHER INFORMATION.



Young Electronics Designers of the Year Award

His Royal Highness the Duke of York, Patron of the Young Electronic Designer Awards, presented the Young Electronic Designer Awards for 1997 to the winners in front of 200 guests at a special presentation dinner at the Science Museum, London, on 26th March. Earlier in the evening, TV Personality Sally Grey announced the winners. The Awards which are sponsored by Mercury Communications and Texas Instruments in association with the Institution of Electrical Engineers, challenge young designers to invent and produce an innovative device or system based on electronics to meet an everyday need. The competition is open to students between the ages of 12 and 25 in secondary schools, colleges and universities.

The winner of the Duke of York's Award for the most imaginative concept is 18-year-old Michael Brown of Bancroft's School, Woodford Green, Essex for his "Gremlinator" circuit testing aid. The "Gremlinator" was also highly commended in the Senior overall category. The Mercury Communications Prize for the best

communications-based project went to 14-year-old Emily Collins of Ridley High School, Blyth, Northumberland, for her SAFE (Sensory Alert For Everyday), ingeniously combining flashes and vibration to give smoke, intruder, doorbell and telephone alarm warnings for the deaf, and designed to be worn on the wrist. Her project also received a Highly Commended award in the Junior-overall category. The Texas Instruments Prize for the most commercially viable project went to 17-year-old Simon Todd of Bolton School, Bolton, Lancs, for a domestic

iron safety device. Simon's project also came first in the Intermediate (15-17 years) overall category. The winner of the IEE Award for the best new entrant to YEDA is Mark Gould, 14, of Gryphon School, Sherborne, Dorset, for a detector to indicate whether electric fences

are turned on or off, which also took the second prize in the Junior overall category. The first prizewinner in the Senior (18-25 years) category is James Smith, 22, of Brunel University for his "Manta" through-water communication device for recreational scuba divers.

Other winners are Peter Smith, 23, of the Bangor University of Wales, second in the Senior category for an integrated low-cost noise badge dosimeter for people working in noisy environments; Leighton Spicer, 21, of the Bangor University, third in the Senior category for an electronic system to reduce the incidence of pressure sores in older or disabled people; David Marson, 16, of St Joseph's College, Trentvale, Stoke on Trent, second in the Intermediate category for an electronic hand-held pedestrian crossing sign; Susannah Baker, 15, and Elizabeth Humphreys, 14, of Bishop's Castle Community College, Shropshire, for their 'Braille Rail' talking electronic map of the London Underground; Edward Brocklebank, 14, of Radley College, Abingdon, Oxon, first in the Junior category (under 15 years) for a safety device for a bicycle providing enhanced visibility at night and including left/right turn indicators; Rachel Downing, 13, Kerry-Anne Devlin, 13, Anna Burke, 12, and Anne-Marie Gaillard, 12, of St Mary's Junior High School, Lurgan, Northern Ireland, third in the Junior category for an educational toy to enhance knowledge of the earth and solar system.

Also Highly Commended in the Senior category was Gwyn Jones, 22, of Bangor University for a pre-eclampsia monitoring system; in the Intermediate category Sumit Rai, 17, of Dulwich College, London, for an opto-electrical swipe entry card for a public gym; Jonathan Taylor, 15, of Bryanston School, Blandford, for the "Coxbox" device to give the rowing cox and steersmen a stroke rate readout; Andrew

Buckmaster, 16, of Radly College, Abingdon for a device for measuring and displaying the quantity of water used by showers and hose pipes (an increasingly topical subject these days); John Morton, 16, and Max Kendall, 16, for a bath temperature warning device in the form of a toy and Andrew Early, 16, of Ravens Wood School, Bromley, for a model rocket launch controller. Highly Commended in the Junior category were also Guy Kewish, 13, Philip Reid, 13, and Alasdair Lynch, 13, of Merchiston Castle School, Colinton, for BASICS (Babies and Safety in Car Seats) and Stephen Wyber, 13, of Bancroft's School, Woodford Green, for his kitchen weighing scales for the blind.

All the competition entrants had to exhibit awareness of the ease of use, commercial applicability and production engineering of their projects, as well as the basic electronics concepts. We congratulate them and wish them good progress in their chosen careers in the future...




Mercury-free batteries ready to change the market

The first mercury-free rechargeable batteries have been released in the UK. Allied Battery Technologies has announced the cells, known as RAM (tm) (Rechargeable Alkaline Manganese) cells, for use in all kinds of electronic and home equipment, including power toys, cameras, radios, audio equipment, remote controls and torches. As they are being marketed as "Pure Energy Rechargeable Alkaline", we can hope that the already thinly-stretched "RAM" acronym will not confuse buyers into thinking that these are specialist computer batteries.


The RAM cells are designed as long-life rechargeables and the company stresses that they are not to be confused with attempts to recharge conventional alkaline manganese batteries in "universal" chargers. The charge and recharge characteristics of the new batteries are such that the useful life is 10 to 50 times that of a conventional alkaline battery, or more. The simple purpose-designed RAM charger, which fits into a normal 13 amp wall socket, hold batteries ready for use. The cells can be recharged from 10 to over 50 times, and have a shelf life of five years. They come charged, and so do not have to be charged up before first use.



Photo flash comparison

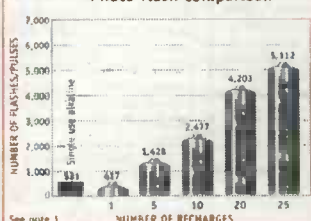

Personal cassette player comparison

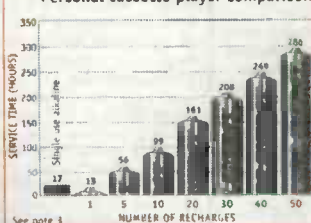

RAM cells have the major "green" advantage that they contain no toxic chemicals such as mercury or cadmium, used in most other types of dry cell. They have a similar application pattern to NiCads, but without the threat of pollution. The company found that the new technology captured 53% of the NiCad rechargeable market within six months.

Initially, AA cells will be available in the UK with AAA cells to follow later this year. The RAM cells are based on patented technology developed by Professor Karl Kordesch, the inventor of the single-use disposable alkaline battery so well known today. They represent to performance characteristics of disposable alkaline batteries and the economic benefits of rechargeability, along with the environmental advantage of low toxicity. The Pure Energy branded RAM calls are completely interchangeable with conventional, non-rechargeable alkaline batteries, and also suitable in many cases as an alternative to rechargeable NiCads. They can also be used in equipment labelled "unsuitable for rechargeable nickel cadmium batteries", because they do not deliver "overcurrent" that is potentially damaging to some consumer electronics. There is, in addition, no "memory effect" as occurs with NiCads - RAM cells perform best when "topped up" in their charger when not in use. The Ram cell is a 1V5 cell rather than a 1V2 cell, and therefore more efficient in 3V and 6V applications.

Chargers

Two chargers will be available for the new batteries: the MegaCharger is a table-top charger which will take up to eight AA or AAA cells for high-volume use, fully charging eight batteries in six hours. The EnviroCharger is a compact unit that will take up to four AA or AAA cells, and plugs into a 13A wall socket. It will charge four batteries overnight from a fully discharged state, and will recharge partially discharged batteries much sooner.

The Pure Energy RAM cells are described as being rechargeable from 10 times up to 25 times or more. In a high-discharge application such as a child's toy or other motor drives, the RAM cell can be recharged giving it a total life of more than 17 times a single-use alkaline battery. Tests under low-current drain conditions simulating the use of a personal cassette player in stop/start mode showed a total life more than 50 times longer than a conventional alkaline manganese battery.

The batteries will be on retail sale. Further enquires to Allied Battery Technologies, 14 Bates Industrial Estate, Wycombe Road, Stokenchurch, Bucks HP14 3RJ.

Low-profile meter needs no soldering

First in a new family of low-profile, DIN-cased digital panel meters, Lascar Electronics' DPM 390 is housed in a snap-in DIN case and features 200 mV full scale reading, auto-polarity, auto-zero and 14.2 mm digit height. Designed to be used without the need for soldering, the DPM 390 contains internal DIP switches for selection of input mode and decimal points. Connection is made via an optional T/blk-1 screw terminal blockboard. Lascar are recommend the DPM 390 for high and low volume applications.

For more information tel. 01794 884567.



DIFFERENTIAL THERMOSTAT KIT Perfect for heat recovery, solar systems, boiler efficiency etc. Two sensors will operate a relay when a temperature difference (adjustable) is detected. All components and pcb. £29 ref F/LT93

MAGNETIC RUBBER TAPE Selfadhesive 10 metre reel, 8mm wide perfect for all sorts of applications! £15 ref LOT87

MAINS POWER SAVER UK made plug in unit, fitted in seconds, can reduce your energy consumption by 15%. Works with fridges, soldering irons, conventional bulbs etc. Max 2A rating. £9 each ref LOT71, pack of 10 £69 ref LOT72

YUASA SEALED LEAD ACID Batteries, ex equipment but ok bargain price just £5.99 each ref YA1. 100 or more £3.50 each.

DC TO DC CONVERTERS

DRM58 input 10-40vdc output 5v 8A £15 DRM128 input 17-40vdc output 12v 8A £18 DRM158 input 20-40vdc output 15v 8A £18 DRM248 input 29-40vdc output 24v 8A £12 DRS123 input 17-40vdc output 12v 3A £10 DRS153 input 20-40vdc output 15v 3A £20 DRS243 input 29-40vdc output 24v 3A £8

HITACHI LM225X LCD SCREENS 270x150mm, standard 12 way connector, 640x200 dots, tec spec sheet. £15 each ref LM2

VARIABLE CAPACITORS Dual gang, 60x33x45mm, reduction gearing, unknown capacity but probably good quality (military spec) general purpose radio tuner. £9 ref VC1

ELECTRONIC FLASH PCB Small pcb fitted with components including a flash tube. Just connect 12vdc and it flashes, variable speed potentiometer. £6 ref FLS1

THIEF PROOF PEN! Amazing new ball point pen fitted with a combination lock on the end that only you know! £2.49 ref TP2

JUMBO BI COLOUR LEDS PCB with 15 fitted also 5 giant seven segment displays (55mm) £8 ref JUM1

HOME DECK CLEARANCE These units must be cleared! leads, a n infra red remote qwerty keyboard and receiver, a standard UHF modulator, a standard 1200/75 BT approved modern and loads of chips, capacitors, diodes, resistors etc all for just £10 ref BAR33.

6.8MW HELIUM NEON LASERS New units, £65 ref LOT33

COIN SLOT TOKENS You may have a use for these? mixed bag of 100 tokens £5 ref LOT20.

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £65 ref F/XP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £45 ref F/TKE1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15 ref F/EH2

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock sheepskin out of simple materials and without any visible means- cause it to levitate. £10 ref F/GR1.

WORLDS SMALLEST TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, 'Plasma in a jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5 ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10 ref F/ICV1.

VOICE SCRAMBLER PLANS Miniature solid state system tunes speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6 ref F/VSS.

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCREET ADVISED. £8 ref F/TJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development etc. Excellent security device or very interesting science project. £8 ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc £12 ref F/LC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £6 ref F/ANT1K.

FRUIT POWERED CLOCK Just add a fresh orange, tomato, banana or any other fruit plug in the probes and the clock works! £9.95 ref SC154

DYNAMO FLASHLIGHT Interesting concept, no batteries needed just squeeze the trigger for instant light apparently even works under water in an emergency although we haven't tried it yet! £6.99 ref SC152

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £6 ref F/ULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/ SOUND

AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £6 ref F/HGA7

WOLVERHAMPTON ELECTRONICS STORE NOW OPEN IN WORCESTER ST TEL 01902 22039

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate £6 ref F/DOG2

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £12 ref F/LUST1

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 ref F/LLS1

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £6 ref F/PPS4

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5 ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance-requires adult supervision £5 ref F/EML2

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £5 ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8 ref F/PM5

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 ref F/HV/M7/ TCL4.

MEGA LED DISPLAYS PCB fitted with 5 seven segment displays each measuring 55 x 38mm. £5 ref LED5.

MOD TRANSMITTING VALVES 6J180E £80 ref LOT112 SWITCHED MODE PSU's 244 watt, +5.32A, +12.6A, -5.0.2A, -12.0.2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC inlet Suitable for PC use (6 d/drive connectors 1 m/board). £15 ref LOT135

HYDROGEN FUEL CELL PLANS There is a lot of interest in using Hydrogen as the fuel of the future, Hydrogen is easy to produce using chemicals and surplus solar generated electricity. It is also easy to store with little or no loss. Hydrogen fuel cells are designed to store hydrogen and weight for weight will hold twice as much energy as a full petrol tank. Our plans give you loads of information on Hydrogen production, storage and practical plans to build your own Hydrogen fuel cell! you will need access to a well equipped workshop for this but full construction details and drawings are included. Full cell plans £9 ref HY1

VIDEO PROCESSOR UNITS 76v 10AH BATT/24V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2 x 6v 10AH sealed lead acid batts, pcb's and a BA7 24v toroidal transformer (mains in). sold as seen, may have one or two broken knobs etc due to poor storage. £15.99 ref VP2

RETRON NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw infrared laser included. £325 ref RETRON.

MAKE YOUR OWN CHEWING GUM KIT Everything you need to make real chewing gum, even the bowl and tree sap from the Sapodilla tree. £7.99 ref SC190

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 MHz but easily changed to cover 63-130 MHz. Works with a common 9v (PP3) battery. 0.2W RF. £9 ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £15 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, i/c speaker. £18 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w

power handling, microphone included. £17 ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3RF stages, microphone and audio preamp included. £24 ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 hz (a lot faster than conventional strobes). Mains operated. £17 ref 1037.

COMBINATION LOCK KIT 9 key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £13 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £9 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 ref 1131

TELEPHONE BUG KIT Small bug powered by the 'phone line, starts transmitting as soon as the phone is picked up! £12 ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction control supplied with 12 LEDs (you can fit triacs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 ref 1069.

HELPING HANDS Perfect for those fiddly jobs that need six hands. 6 ball and socket joints, magnifier. £7.99 ref YO57A

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recordings etc, adjustable sensitivity. £10 ref 1073.

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls, 18vdc, Input sens 100mA £15 ref 1052

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

15 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yagi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9v dc design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref G/R20

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £45 ref NIK39.

Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12VDC adjustable from 0-30 secs. £4.99 HY1260M, 12VDC adjustable from 0-60 mins. £4.99 HY2405S, 240v adjustable from 0-5 secs. £4.99 HY24060M, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and o/p leads 17V DC 900mA output. Bargain price £5.99 ref MAG6P9

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £12.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 285x135x60mm, 4 drive connectors 1 mother board connector, 150Watt, 12v fan, i/c inlet and on/off switch. £12 ref EF6.

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34.

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA Bargain price just £5.99 ea REF MAG6P12

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together! belived to cause rain! £3 a pair ref EF29.

3' by 1' AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 watts, aluminium frame, screw terminals, £55 ref MAG45

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £9 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £9 ref 7P36.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £8.99 ref R/9.

COMPAQ POWER SUPPLIES WITH 12V DC FANS Ex equipment psu's, some ok some not but worth it for the fan alone probably about 300 watt PC unit with IEC input. £3.50 each ref CQ1

BALLON MANUFACTURING KIT British made, small blob blows into a large, longlasting balloon, hours of fun! £3.99 ref G/E99R

9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

SOLID STATE RELAYS

CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50
SMT20000/3 3-24vdc operation, 28-280vac 3A £4.50

**FREE COLOUR CATALOGUE
WITH EVERY ORDER**

**WE BUY SURPLUS STOCK
FOR CASH
SURPLUS STOCK LINE 0802 660335**

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3.50 P&P PLUS VAT.

24 HOUR SERVICE £4.50 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50

(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

phone orders : 01273 203500

FAX 01273 323077


E-mail bull@pavilion.co.uk

Multi-tasking kernel assists embedded systems

Arcom Control Systems has ported an efficient multi-tasking kernel from US Software onto its new range of low-cost 16- and 32-bit embedded controllers. The software will assist in upgrading embedded control systems to much higher levels of computing performance to meet the need for greater control flexibility, connectivity and user ergonomics, while keeping down costs, timescales and the difficulties of migration.

In conjunction with Arcom's PC-based development tool, the software provides the same kind of simplicity and speed as developing a PC-based target, but without the overheads needed by a PC running Windows. This can save significant costs in hardware and software licensing for each control system installed. The Arcom controller range is based on the latest 25 MHz 188EB and 33MHz 386EX embedded processors from Intel, giving high computing performance and large memory-addressing ranges at price levels designed to attract designers currently using microcontroller chips.

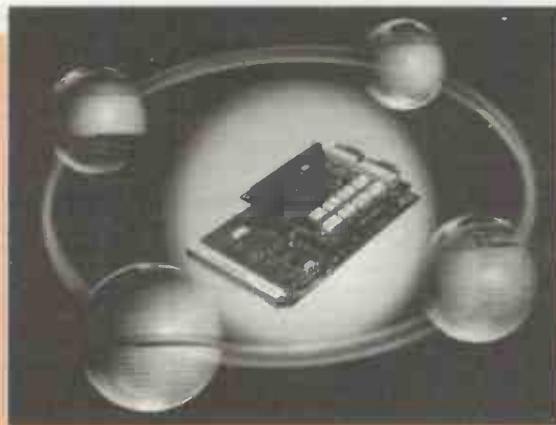For example, compared with popular 8-bit devices like the 8051, these new processors offer very considerably higher performance. The CPUs are packaged on single Eurocards with a range of real-time-oriented hardware, as well as PC/104 and (optionally) STEbus expansion interfaces.



The multi-tasking kernel, SuperTask!, allows designers to divide application programs into structured tasks which interface with a real-time database, such as control algorithms, communications, and human interface routines. The kernel ensures that each routine is serviced regularly according to user-defined priority criteria. The use of the kernel can greatly reduce the complexity of programming for advanced control systems. Benchmarks for the 396EX board show that task switching occurs in 20 microseconds, for example, with interrupt latency of less than 80 us, giving designers true determinism for critical segments of code - apparently debugged code segments can occasionally give unpredictable results due to interrupt timing; the low latency in this system addresses this problem.

Run time licenses are just £16 for medium-volume applications.

For further details contact Arcom Control Systems Ltd., Clifton Road, Cambridge CB1 4WH, UK. Tel 01223 411200 email sales@arcom.co.uk Web www.ussw.com

Government plugs new information programmes

The UK Government (as we write) is promoting a potentially wide-ranging package of programmes under the aegis of the ISI (Information Society Initiative) "to help the UK take its place as a leading nation in the development of the Information Society ... it is an initiative which will continue until the end of the decade".

Among other things, the Government will "a new Information and Communications Technology fund which will enrich our lives ... but no money from the new fund will be available until 2001 at the earliest," reported Minister Ian Taylor.

The main ISI activities include: Programme for Business: a partnership with business to encourage development of new technologies and applications; IT for All: access opportunities for citizens to help overcome technology barriers; Education Department Superhighways Initiative: raising awareness of computer networks in education (computer networks in schools); and government.direct (electronic delivery of government services to homes and businesses). (Information from the Cabinet Office).

The Government is supporting the IT Industry Training Organisation in developing "rigorous standards" of competence at all levels of IT skill. According to the Government, this has already been done with regard to the National Curriculum. The UK is one of the few countries in the world in which IT must be used in all curriculum subjects. UK Education Departments will be publishing purchasing and good practice guidance later this year. A working knowledge of IT "to at least Level 8 in the National Curriculum for Pupils" will be integrated into teacher training qualifications. Industrial sponsors are sought for the DTI's Schools OnLine project.

Other areas to be addressed are the extension of the UK's telecommunications capabilities through investment by cable and telecomms companies. BT is investing around £2M a year to upgrade its network to fibre-optic cable to street-cabinet level. Fixed price ISDN packages are in the meantime available from telephone providers. Much of a record amount of direct foreign investment in the UK has been in information and communications technology (such as Siemens, Fujitsu, Morotola, Nortel, Samsung and LG).

A forum is to be established for industry, academia and other bodies to work together to maximise the UK's research, development and learning capabilities, "with a goal of creating a positive balance of trade in IT-related intellectual property rights by 2005. The DTI has made efforts to improve the protection of intellectual property rights (although participants still find that the situation is far from clear in many cases, the last major redraft being the Copyright, Designs and Patents Act of 1988, before many Internet services went on-line).

The ISI Programme for Business Publicity Centre Tel 0171 828 1593

OVERSEAS READERS

To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.

MODSMODSMODSMODSMODSMODS

In the **Freezer Alarm** (Vol 26 issue 4), a wire link is missing in figure 3 (the component layout). This runs from pin 8 of IC3 to the power rail on track 12 and is clearly shown on the far right of the photograph on page 26 of the article. The link can be inserted to the right of R9 without moving the resistor.

In **The Little Mule** (Vol 26 issue 3). The "missing" IC1 is a 4093 nand Schmitt trigger, available from Maplin and other suppliers.

THERE IS ONE DANGER YOU CAN'T SEE, HEAR, SMELL OR FEEL- ITS RADIATION. THERE ARE OVER 10,000 SHIPMENTS OF RADIOACTIVE MATERIAL IN THE UK EVERY YEAR BY ROAD AND RAIL! WOULD ANYBODY TELL YOU OF A RADIATION LEAK?

NEW GEIGER COUNTER IN STOCK Hand held unit with LCD screen, autoranging, low battery alarm, audible 'click' output. New and guaranteed. £129 ref GE1

RUSSIAN BORDER GUARD BINOCULARS £1799

Probably the best binoculars in the world right for colour brochure.

RUSSIAN MULTIBAND WORLD COMMUNICATIONS RECEIVER Exceptional coverage of 9 wave bands, (5 short, 1 LW, 1FM, 1MW) internal ferrite and external telescopic aerials, mains/ battery. £45 ref VEGA

NEW LASER POINTERS 4.5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) 670nm. £29 ref DEC49

HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES Comprehensive 270 page book covers all aspects of spirit production from everyday materials. Includes construction details of simple stills etc. £12 ref MS3

NEW HIGH POWER MINI BUG With a range of up to 800 metres and a 3 days use from a PP3 this is our top selling bug! less than 1" square and a 10m voice pickup range. £28 ref LOT102.

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators and propellers. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

PC KEYBOARDS PS2 connector, top quality suitable for all 286/ 386/486 etc £10 ref PCKB. 10 for £85.

NEW LOW COST VEHICLE TRACKING TRANSMITTER KIT £29 range 1.5-5 miles, 5,000 hours on AA batteries, transmits info on car direction, left and right turns, start and stop information. Works with any good FM radio. £29 ref LOT101a

HIGH SECURITY ELECTRIC DOOR LOCKS Complete brand new Italian lock and latch assembly with both Yale type lock (keys inc) and 12v operated deadlock. £10 ref LOT99

***NEW HIGH POWER WIRELESS VIDEO AND AUDIO BUG KIT 1/2 MILE RANGE** Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! Supplied with telescopic aerial. £169

CCTV PAN AND TILT KIT Motorize your CCTV camera with this simple 12vdc kit. 2 hermetically sealed DC linear servo motors 5mm threaded output 5 secs stop to stop, can be stopped anywhere, 10mm travel, powerful. £12 ref LOT125

GPS SATELLITE NAVIGATION SYSTEM Made by Garmin, the GPS38 is hand held, pocket sized, 255g, position, altitude, graphic compass, map builder, nitro filled. Bargain price just £179 ref GPS1.

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA. auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera, enables the camera to be used in total darkness! £8 ref EF138

INFRA RED POWERBEAM Handheld battery powered lamp, 4 inch reflector, gives out powerful pure infrared light! perfect for CCTV use, night sights etc. £29 ref PB1.

SUPER WIDEBAND RADAR DETECTOR Detects both radar and laser, X K and KA bands, speed cameras, and all known speed detection systems. 360 degree coverage, front & rear waveguides, 1.1"x2.7"x4.6" fits on sun visor or dash £149 ref

CHIEFTAN TANK DOUBLE LASERS 9 WATT+3 WATT+LASER OPTICS

Could be adapted for laser listener, long range communications etc. Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, no circuit diagrams due to MOD, new price £50,000? us? £199. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. £199 for one. Ref LOT4.

EASY DIY/PROFESSIONAL TWO WAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) includes full instructions. £12 ref TW1.

NEW LOW PRICED COMPUTER/WORKSHOP/HI-FI RCB UNITS Complete protection from faulty equipment for everybody! inline unit fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £8.99 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!

TWO CHANNEL FULL FUNCTION B GRADE RADIO CONTROLLED CARS From World famous manufacturer these are returns so they will need attention (usually physical damage) cheap way of buying TX and RX plus servos etc for new projects etc. £12 each sold as seen ref LOT2.

MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL £9.95 Cased with fileleads, designed to read standard credit cards! complete with control electronics PCB and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

RUSSIAN 900X MAGNIFICATION ZOOM MICROSCOPE metal construction, built in light, mirror etc. Russian shipmtr faml, group viewing screen, lots of accessories. £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34

RUSSIAN NIGHTSIGHTS Model TZ54 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range. 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices,

16 character 2 line, 99x24mm £2.99 ref SM1623A

20 character 2 line, 83x19mm £3.99 ref SM2024A

16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1, 110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical 'scope, everything you need for some serious star gazing! up to 165x magnification. Send or fax for further information. 20kg, 885x800x1650mm ref TAL-1, £249

YOUR HOME COULD BE SELF SUFFICIENT IN ELECTRICITY Comprehensive plans with loads of info on designing systems, panels, control electronics etc £7 ref PV1

COLOUR CCTV VIDEO CAMERAS, BRAND NEW AND, CASED, FROM £99.

**PERFECT FOR SURVEILLANCE,
INTERNET, VIDEOCONFERENCING,
SECURITY, DOMESTIC VIDEO**

**Works with most modern video's, TV's,
Composite monitors, video grabber cards etc**
Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8,
500x582, 12vdc, mounting bracket, auto shutter,
100x50x180mm, 3 months warranty, 1 off price £119
ref XEF150, 10 or more £99 ea 100+ £89

MICRO RADIO It's tiny, just 3/8" thick, auto tuning, complete with headphones. FM £9.99 ref EP35

25 SQUARE FOOT SOLAR ENERGY BANK KIT 100 6"x6" 6v Amorphous 100mA panels, 100 diodes, connection details etc to build a 25 square foot solar cell for just £99 ref EF112.

CONVERT YOUR TV INTO A VGA MONITOR FOR £25!
Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. **SALE PRICE £25 REF SA34**

***15 WATT FM TRANSMITTER** Already assembled but some RF knowledge will be useful for setting up. Preamplifier, 4 stage 80-108mhz, 12-18vdc, can use ground plane, yagi or dipole £69 ref 1021

***4 WATT FM TRANSMITTER KIT** Small but powerful FM transmitter kit. 3 RF stages, mic & audio preamp included £24 ref 1028

YUASHA SEALED LEAD ACID BATTERIES 12v 15AH at £18 ref LOT8 and below spec 6v 10AH at £5 a pair

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc **SALE PRICE JUST £4.99 REF SA28**

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £12.99 REF AUG10P3.

SOLAR POWER LAB SPECIAL You get 2 6"x6" 6v 130mA cells, 4 LEDs, wire, buzzer, switch + 1 relay or motor. £7.99 REF SA27

12V DC MOTOR SPEED CONTROL KIT Complete with PCB etc. Up to 30A. A heat sink may be required. £19.00 REF: MAG17

SOLAR NICAD CHARGERS 4 x AA size £9.99 ref 6P476, 2 x C size £9.99 ref 6P477

MEGA POWER BINOCULARS Made by Helios, 20 x magnification, precision ground fully coated optics, 60mm objectives, shock resistant cased prisms, case and neck strap. £89 ref HPH1

GIANT HOT AIR BALLOON KIT Build a 4.5m circumference, fully functioning balloon, can be launched with home made burner etc. Reusable (until you loose it!) £12.50 ref HA1

AIR RIFLES 22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 ref EF78. 500 pellets £4.50 ref EF80

***NEW MEGA POWER VIDEO AND AUDIO SENDER UNIT.** Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 500m range! (tune TV to channel 31) 12v DC

op. Price is £65 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies

with a range up to 2 km in open country. Units measure 22x52x155mm. Including cases and earpieces. 2xPP3 req'd. £37.00 pr. REF: MAG30

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever! why pay £700? or price is £18 REF: EF62 (kit) Transmits to any FM radio. Built and tested version now available of the above unit at £45 ref EXM34

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £14.95 Ref EF82B extra pellets (500) £4.50 ref EF80.

HEAT PUMPS These are mains operated air to air units that consist of a aluminium plate (cooling side) and a radiator (warming side) connected together with a compressor. The plate if inserted into water will freeze it. Probably about 3-400 watts so could produce 1kw in ideal conditions. £30 ref HP1

3 FOOT SOLAR PANEL Amorphous silicon, 3' x 1' housed in an aluminium frame, 13v 700mA output. £55 ref MAG45

SOLAR/WIND REGULATOR Prevents batteries from over charging. On reaching capacity the regulator diverts excess power into heat avoiding damage. Max power is 60 watts. £27.99 ref S/CA11-05

FANCY A FLUTTER? SEEN OUR NEW PUBLICATION? Covers all aspects of horse and dog betting, systems etc and gives you a betting system that should make your betting far more profitable! £6 a copy ref BET1

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £24.95 ref R/7.

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £6 ref EP70

NICAD CHARGERS AND BATTERIES Standard universal mains operated charger, takes 4 batts + 1 PP3, £10 ref PO11D. Nicads- AA size (4 pack) £4 ref 4P44, C size (2 pack) £4 ref 4P73, D size (4 pack) £9 ref 9P12.

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! LED system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £89 ref EP3.

3" DISCS As used on older Amstrad machines, Spectrum plus 3's etc £3 each ref BAR400.

STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue.

SECOND GENERATION NIGHT SIGHTS FROM £748

RETRO Russian night sight, 1.8x, infra red lamp, 10m-inf, standard M42 lens, 1.1kg. £349 ref RET1

LOW COST CORDLESS MIC 500' range, 90 - 105mhz, 115g, 193 x 26 x 39mm, 9v PP3 battery required. £17 ref MAG15P1

HI POWER SURVEILLANCE TELESCOPE Continuous zoom control from 20 times to an amazing 60 times magnification, 60mm fully coated objective lens for maximum light transmission, complete with tripod featuring micro elevation control. £75 ref ZT1

JUMBO LED PACK 15 10mm bicolor leds, plus 5 giant (55mm) seven segment displays all on a pcb £8 ref JUM1. Pack of 30 55mm seven seg displays on pcbs is £19 ref LED4, pack of 50 £31 ref LED50

12VDC 40MM FANS MADE BY PANAFLO, NEW. £4. REF FAN12

HELP WANTED WITH MOTORS We have thousands to clear at rock bottom prices! bumper pack of 20 motors (our choice) is just £19.95! Some of these will be 5" or maybe larger!

HELP WANTED WITH MULTI RAIL POWER SUPPLIES Again we have thousands available, most with fans, mostly cased, sold as seen, condition may vary, some working some not. Pack of 10 is £19.95

HELP WANTED WITH TELEPHONE COIN BOXES Need we say, thousands available! these are units designed to convert an ordinary phone into a coinbox phone. They have damaged cases but the electronics and coin slots are ok. Speech chip on the board talks to you as you program it! Pack of 10 is £19.95

HELP WANTED WITH EXTERNAL MICRO TAPE STREAMERS 10,000 in stock, space needed! brand new cased units with loads of interesting bits (motor, tape heads, PCB etc etc. Very smart plastic case useful for projects etc. Pack of 20 is £19.95 ref MD2

HELP WANTED WITH YUASHA 12V 6.5AH SEALED LEAD ACID BATTERIES About 10 pallets full just inside warehouse no 21 pack of 5 for just £19.95 also some below spec 6v 10Ah at £19.95 for a pack of 8

Check out our WEB SITE

**full colour interactive
1997 catalogue**

<http://www.pavilion.co.uk/bull-electrical>

**FREE COLOUR CATALOGUE
WITH EVERY ORDER**

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

**WE BUY SURPLUS STOCK
FOR CASH
SURPLUS STOCK LINE 0802 660335**

**FREE 10%
DISCOUNT VOUCHER**
CUT OUT AND INCLUDE THIS
CORNER WITH YOUR ORDER
AND DEDUCT 10%
FROM ALL THE ITEMS IN THIS
ADVERT!

ETI

BULL ELECTRICAL
250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).
MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3.50 P&P PLUS VAT.
24 HOUR SERVICE £4.50 PLUS VAT.
OVERSEAS ORDERS AT COST PLUS £3.50
'phone orders: 01273 203500
(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)
FAX 01273 323077
E-mail bull@pavilion.co.uk



Wall of Sound



The loudspeakers of the future are thin, flat and could be built into your wall. The first ones are more likely to be built into your laptop.

They disobey the wave equation. They are the first serious competition for traditional loudspeaker design. Andrew Armstrong reports.

It appears that the days of the conventional loudspeaker may be numbered, and that for the most part flat panel loudspeakers will be used in the future. If you remember our editorial challenge to make a real improvement in loudspeaker performance - well, the NXT design looks like the most serious contender to provide the answer. This is an account of a visit to the labs where the loudspeakers were developed.

I went to see and hear the new loudspeakers as a sceptic, open minded enough to ask for a demonstration of this new type of technology, but not suspecting the far reaching consequences of the new developments.

V Labs at Huntingdon is a shared R&D facility for several well respected hi-fi brands including Mission, Quad, and Roksan. This in itself inspires some confidence in the quality of the work to be expected.

The working conditions are ones which would delight most designers: the computer equipment is upgraded regularly, and the "old" equipment is passed on to less critical areas of the company. I was particularly taken with the mechanical design section, in which the casework is designed with CAD software able to display any stage of the assembly and which can also show the finished equipment displayed with other hi-fi items to see if the styling is compatible with other respected models on the market, as hi-fi products are frequently "mixed and matched" by discerning users. The CAD can also provide an animated display of the casework being assembled.

This is not simply about style and marketing, however. When sample mechanical parts are needed, laser stereo lithography is used. The process uses numerical data to control laser beams directed into a tank of a plastic material which is polymerises at the crossing point of the laser beams. Thus, the lasers can draw a mechanical shape required in 3D, and this shape forms in the tank. The data

to control the laser beams is generated straight from the design in the computer, and a physical drawing is not needed. Assuming that the part produced by stereo lithography is correct, data from the same CAD file is used to control the CNC machines which manufacture the final parts (or which manufacture the moulds for plastic parts). This level of simulation cuts down the stages of development.

Many people will be relieved to hear, however, that the actual electronics prototyping is carried out in traditional manner with prototype assemblies.

The start of the project

Before the project first began in 1994, a scientist from the Defence Research Agency (DRA) noticed that panels intended for sound deadening in airframes were acting as loudspeakers. He developed this effect into a working loudspeaker which functioned by principles not properly understood, and which were not good enough for serious use. It was only able to work over a limited frequency range, and then not very smoothly. He asked Mission if they could develop it far enough to become useful. The engineers examined it and concluded that it was too far from being useful to be worth pursuing. However, Henry Azima, the Chairman of V-labs, was not satisfied with this answer. Clearly, something worked in a way which could not be explained and he wanted to know more about it before rejecting it.

He set two mathematicians who were experts in the field of finite element analysis to see what they could find out. After two months of work, they developed a finite

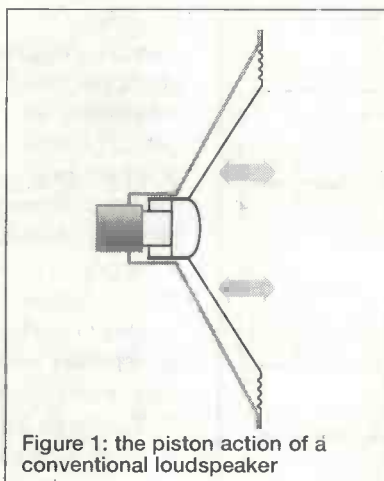


Figure 1: the piston action of a conventional loudspeaker

element analysis program which analysed the vibrational modes of the panel. It was then seen to be possible to use a different but related vibrational principle to make a loudspeaker good enough to be of use.

V-labs still licenses the original patent from DRA, and has a total of 22 patents and 450 claims on their own new technology going forward to date.

Pistons and other vibrations

An ordinary loudspeaker works as a piston, pushing backwards and forwards a volume of air. This principle is illustrated in figure 1. Virtually all loudspeakers have worked on this principle, and a modern loudspeakers of this type would be largely familiar to a sound engineer as far back as 70 years ago. Refinements such as new cone materials, more compliant suspension, and ferro-fluid, are incremental advances which would seem very logical to the sound engineer of the past.

The NXT flat panel loudspeakers do not work anything like this. Instead of the whole panel acting like a piston and moving a mass of air, it vibrates in an apparently incoherent fashion. The analysis of this is very complicated and can probably only be understood by a few mathematicians. The computer program which is used to help design loudspeakers to this principle is said to take many hours to run even on the fastest currently available Pentium.

Figure 2 illustrates the vibration pattern of a conventional stretched panel, and figure 3 shows that of an NXT flat panel

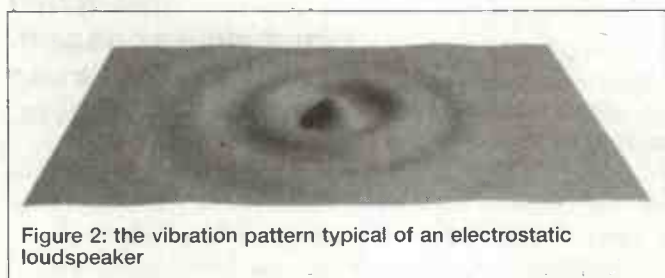


Figure 2: the vibration pattern typical of an electrostatic loudspeaker

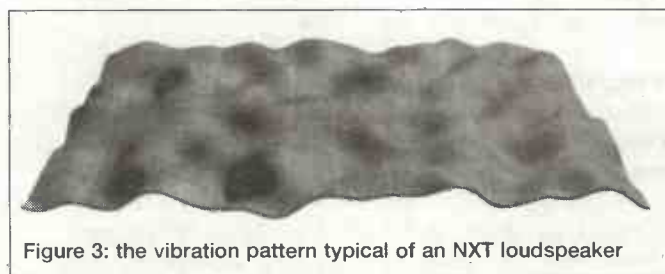


Figure 3: the vibration pattern typical of an NXT loudspeaker

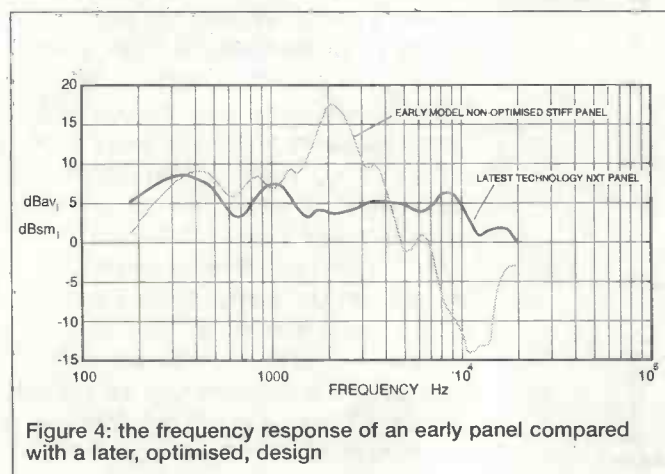


Figure 4: the frequency response of an early panel compared with a later, optimised, design

loudspeaker. The conventional stretched panel has an easily comprehensible pattern, very much like the pattern of ripples caused when a stone is dropped in a pond. Radiation from the back face is out of phase with that from the front, and therefore tends to cancel.

The NXT loudspeaker, on the other hand, has an apparently incoherent vibrational pattern, which is not the same front and back. This apparently chaotic pattern adds at a distance rather in the way that white lights add, while the addition of conventional loudspeakers is more like that of phase coherent laser beams.

Acoustic characteristics

The acoustic characteristics of an NXT flat panel loudspeaker depend very much upon how well it is designed and built. As far as NXT are prepared to tell us how the technology works, the design is done so that the vibrational modes at different frequencies, though they may appear very different when shown as a vibrational pattern, transfer power to the air with similar efficiency.

Factors which have to be correct in order to make the transducer work efficiently and with an even frequency response include:

- the shape of the panel
- the position of the driver
- the bending stiffness
- the surface density
- the sheer modulus of the core
- the damping factor
- the method by which the panel is suspended

Inevitably, the discontinuity represented by the edge of the panel gives rise to the possibility of resonance, and so adds to the complexity of the equations that must be solved to design the panel. Equally, some parts of the panel vibrate at a higher amplitude, and any damping at these points would impair the performance. It is vital that suspension points are chosen so that they affect the vibrational pattern of the panel as little as possible or in a predictable fashion which is taken account of at the initial design stage.

If the design parameters are slightly wrong, the performance is considerably reduced. Figure 4 compares the performance of an earlier design in which some of the parameters were not optimum, with a later design which is much nearer to optimum. The earlier design has a very uneven frequency response, for instance, a resonance in the middle region and a steep falling off of response at the treble end - around 15dB at 10kHz (triangles and cymbals lose sharpness). The subsequent design has a much more even frequency response. Although DSP frequency response correction could have made the earlier design sound reasonable, as a general rule using frequency correction to get rid of large peaks and troughs in the frequency response of a loudspeaker results in poorer performance than if the loudspeaker response is nearer to flat in the first place, because an unsuitably configured transducer is being forced to respond in a way that is unnatural to it and will add distortion of its own in the process.

One of the valuable characteristics of the flat panel loudspeaker is that it is not highly directional even at high frequencies. Figure 5 shows the radiation pattern from an NXT panel at a range of frequencies from 250 Hz to 16kHz showing a reasonably even pattern at all these frequencies.

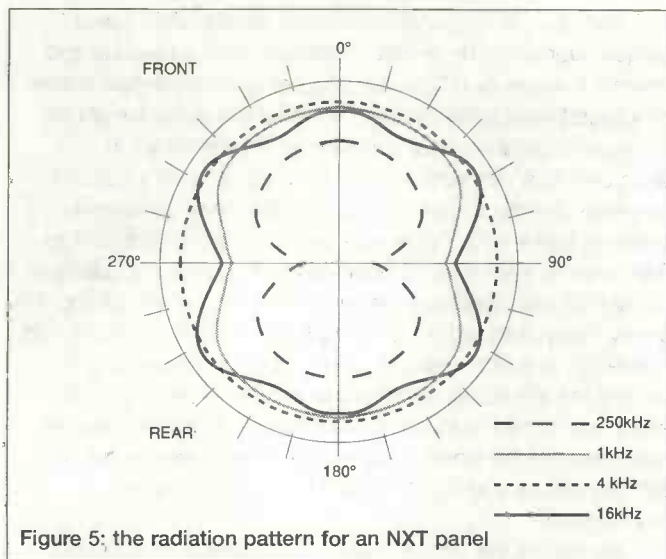


Figure 5: the radiation pattern for an NXT panel

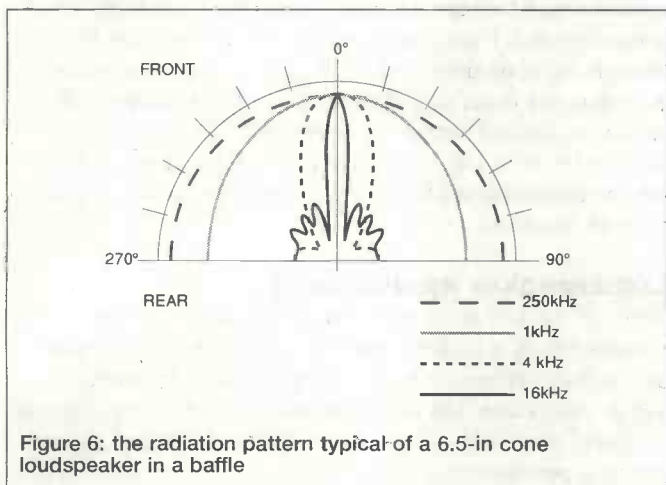


Figure 6: the radiation pattern typical of a 6.5-in cone loudspeaker in a baffle

In contrast, figure 6 shows the radiation pattern typical of a 6.5in diameter cone loudspeaker in a baffle. Even at 4 kHz, this shows a very directional pattern while at 16kHz you would be very lucky to be able to locate the optimum position to hear that frequency.

What is also noticeable from these diagrams as well as from the frequency response in figure 4 is that the one drawback the NXT panel displays is a limited low-frequency response. A very big panel can provide a tolerable low frequency response, but the people at verity labs say that at around 80 to 100 Hz the panel is working more as a piston rather than using the complex vibrational 'distributed mode' characteristic of NXT. On this evidence it is likely that conventional cone loudspeakers will retain their popularity at sub-woofers.

Power drop with distance

With conventional loudspeakers the aim has been to approximate the effect of a point source transducer. A point source would suffer from a halving of sound level with each doubling of distance, the well-known "inverse square law". The NXT however approaches a linear law over a limited range, as is illustrated by the comparative curves in figure 7.

The effect of this linear law is that people near to the loudspeaker are not deafened, while people who are farther away can still hear clearly. Public address systems will benefit greatly, and the area of the living room in which you get good stereo sound will expand. In an ideal world, it may even be that you will be able to get the TV loud enough to hear clearly without disturbing the neighbours.

While meaningful accurate comparative measurements are not at present available, it is clear that less amplifier power is required to give sufficient sound level over a listening area than would be required with conventional loudspeakers.

Another fundamental difference between NXT and conventional loudspeakers is that while the sound radiation from a conventional loudspeaker is focused and, in the technical sense, coherent, the radiation from an NXT panel is diffuse. While this might appear to be a drawback, what it means in reality is that interference to sound quality caused by room boundaries is much reduced. This effect minimises the peaks and troughs normally associated with sound reflecting from the walls of the room.

This also means that hanging one of these flat panel loudspeakers on the wall like a picture will not cause unpleasant resonances, although it will cause a reduction in sound level of about 3dB, due to the loss of radiation from the rear of the panel. And hanging the panels on the wall will be a reality, as the panels can be as thin as 2mm and any area from 25 square metres to 100 square metres.

Listening tests

In the listening room, varied program material was played including some CDs I brought along myself. As I sat in the normal listening position that one would pick for hifi loudspeakers I could not immediately hear any difference between the NXT flat panel speakers being demonstrated and any true hifi standard loudspeaker system. At that stage the most impressive thing was that there were no big bulky boxes in evidence.

On more careful consideration, I reckoned that the clarity and sense of openness in the sound was better than I would normally expect even from a good set of loudspeakers. I suspect that this is a characteristic of the NXT panels, but I cannot say for sure until I hear a set in a room which is less acoustically good than the demonstration room.

I was encouraged to walk around the room to hear how the sound intensity changes as you move up closer to the loudspeakers. In fact, it changes very little, so that with the four channel home theatre demonstration, you could hear all four channels over most of the room. The loudspeaker you were standing next to did not drown out the sound from the other channels. This sounds absurd, but the reason, at least in part, is that as you get close to a large flat-panel loudspeaker, a lot of the sound being radiated from it goes


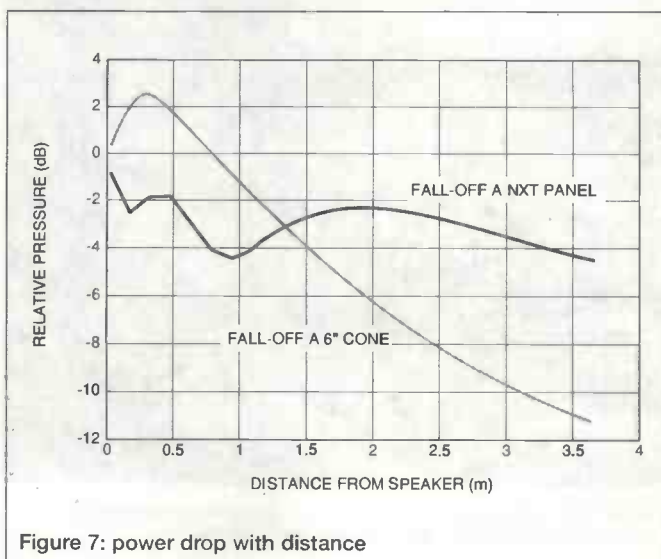



Figure 7: power drop with distance

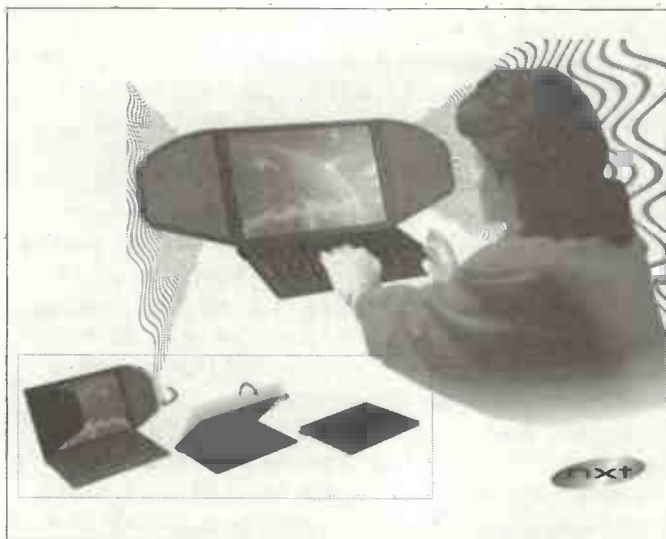

I don't believe your ears! Design for a fold-out laptop with thin panel speakers.

past you and does not reach your ears. It is also partly a function of the very complex vibrational mode.

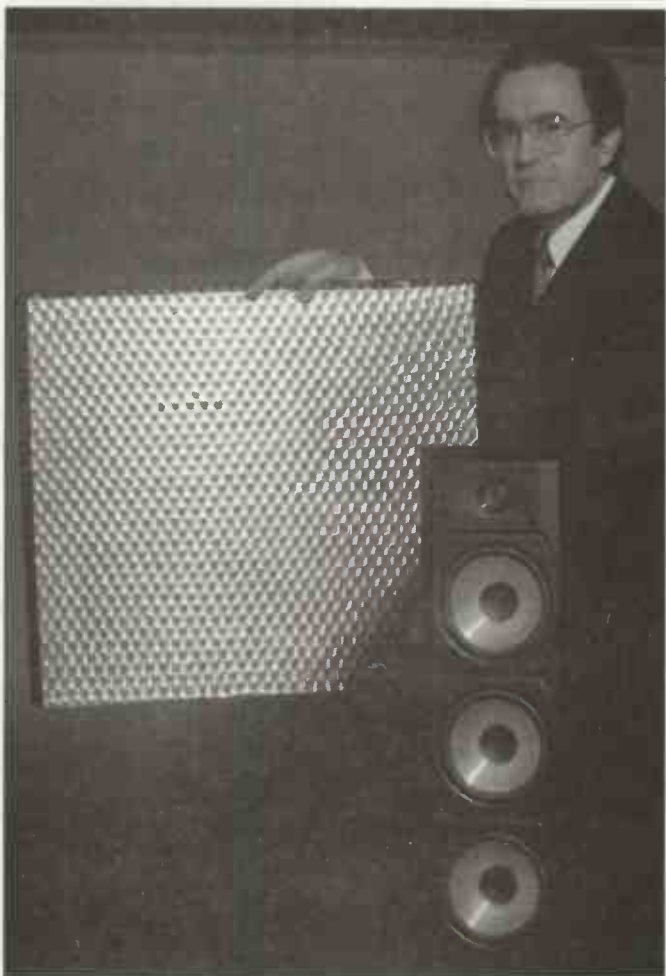One of the many effects of this is that if you are using NXT flat panel speakers as part of a public address system, the microphone can get close to the loudspeakers before feedback occurs, because the sound intensity at a point does not rise in the same way that it does when you approach a small area piston-type loudspeaker. Other implications of this effect are discussed below.



Chief Executive Farad Azima with an improbable-looking but remarkable-sounding NXT flat speaker panel.

I was given a flat panel speaker to handle while it was actually working. The model I handled was rectangular and roughly 1 metre by 0.5 metre, and being made almost entirely of a secret composite material of about the same weight as corrugated cardboard (and indeed appeared similar in structure) was very light, and as I turned it round I noticed very little change in sound level or quality until it was almost edge-on to my ears. There was very little sound vibration to feel, even at a reasonable listening level, though the quality of the sound was affected by where I held the panel. Holding it in a way that would disturb its complex vibrational pattern could noticeably impair the sound quality. The transducer which excites the vibrations in this panel was only noticeable as a slight ripple in the surface. Unsurprisingly, given the extreme complexity of the vibrational mode, it was off-centre rather than central as you would expect with a piston-type loudspeaker.

One part of the demonstration which made an impression upon me was the use of a mock ceiling tile in the foyer for an announcement. I first heard it while I was in the listening room, through the open door, and for something that was plainly audible under these circumstances it was not exceptionally loud when I stood right underneath the NXT tile. This really brought home to me the point about how much the very even volume dispersion will be able to improve the quality of public address systems.

Loudspeaker applications

Although the first application which may come to many peoples minds is for flat panel hifi loudspeakers for domestic use, a likely application to come first is that of multimedia laptop computers. The loudspeakers in laptop computers are inevitably small, with an inevitably shrill tone. The picture here shows a possible application, with flat panel loudspeakers as pull out ears from the sides of the display.

In fact, it may turn out to be possible to make displays with the right mechanical characteristics to work as the loudspeakers. Yes, the plural was deliberate. If two drivers are used, one to each side of the screen, then although the whole panel will radiate the sound from each driver, the sound straight from the driver will reach the ear before that which has travelled across the panel before being radiated. This timing information has been shown to give the ear directional cues, hence stereo.


Obviously, public address or, more correctly, sound reinforcement with little tendency towards feedback will be a great boon, the other aspect of the acoustic characteristic, that of less reduction of sound intensity with distance, is equally valuable. What it means is that fewer loudspeakers are needed to give audible sound over a wide area. A particular plus point from many peoples point of view is that there is not a specially loud area just under a roof loudspeaker.

Recently we ended up leaving a bar in which the only unoccupied tables were those directly under loudspeakers, but the bar staff would not turn the sound any lower otherwise some people couldn't hear it. NXT loudspeakers, in place of the occasional ceiling tile, would have gone a long way towards solving this problem. A ceiling tile as a sound source will likely be welcomed in airport waiting rooms and the like, ensuring that all can hear the announcements without the need to deafen those near the loudspeakers.

Of course, if unobtrusive loudspeakers can look like ceiling tiles, then so can microphones. Bugging in plain sight might be the next fashion in international espionage

OMP MOS-FET POWER AMPLIFIERS
HIGH POWER. TWO CHANNEL 19 INCH RACK

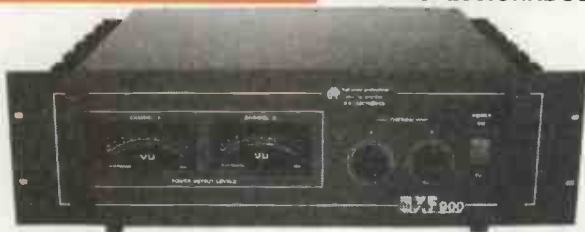THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3½" (2U)xD11"
MXF400 W19"xH5¼" (3U)xD12"
MXF600 W19"xH5¼" (3U)xD13"
MXF900 W19"xH5¼" (3U)xD14½"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE

★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3½" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2"x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2"x6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3½" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
IBI FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features: ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts
R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P

OMP/MF 1000 Mos-Fet Output power 1000 watts
R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:
STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz.
PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE

8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. PRICE £36.67 + £3.50 P&P
RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB.
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
RES. FREQ. 58Hz, FREQ. RESP. TO 8KHz, SENS 98dB.
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5½" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6½" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE. RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHERNO-ON-SEA,

ESSEX. SS2 6TR

Tel. 01702 - 527572 Fax: 01702-420243

The Japanese intend to go a large step better. In overcrowded Japan, space is at a premium, and a company which makes pre-formed bathrooms - the whole thing, washbasin, floor and all - is now planning to make pre-formed wall panels which will be NXT type loudspeakers. Then the stereo speakers will not occupy any room space - just connect the hifi system to the wall and listen in comfort. Of course, sound will also be radiated from the other side of the panel, into the adjoining room, but I do not doubt that when the time comes there will be an answer to this - perhaps a second panel to cancel the sound from the first in one direction only.

This brings me to another application. With the drive for quieter machinery, it is likely that active sound deadening will be incorporated, within the next few years into a number of products. The less directional response at high frequencies will make the NXT panel more effective as an active sound cancellation source. While it is unlikely that the distribution pattern of the NXT loudspeaker will exactly match the source of noise, it is likely to do so reasonably over a wider angle and thus be more effective than an ordinary loudspeaker.

Electrical characteristics

The energy transfer from the loudspeaker to the air is complex and fairly efficient. It is also similar over a wide range of frequencies. The effect of this is that there are no mechanical effects of the sort which make the graph of the impedance of an ordinary loudspeaker far from smooth. The curves supplied look like simple resistance plus the inductance of the moving coil transducer.

This means, of course, that it is very likely that fancy loudspeaker cables will be less relevant, and that amplifier distortion will be lower because the impedance being driven is so much nearer to a plain resistance.

Why should loudspeaker cables matter less? Well there has for some time been controversy as to whether loudspeaker cables do have a significant effect on sound, but it is increasingly accepted that some difference between cables does exist, and it seems plausible that the differences are caused by resistance, inductance, and capacitance reducing the ability of the amplifier to damp resonances of the loudspeaker. A loudspeaker which has a resistive impedance and little in the way of resonances is less likely to be affected by a little extra impedance between it and the amplifier.

There are two ways to excite the NXT panel using moving coil drivers, and these are illustrated in figures 8 and 9. The first is an inertial magnet driver in which the mass of the magnet must be sufficient that the majority of the vibration is transferred to the panel and not to the magnet, while the other sort of driver is a clamped driver which bends the panel. This has a much higher mechanical impedance. It would also be possible to drive an NXT panel with a piezo-electric transducer, but this would not match well with ordinary hifi amplifiers.

In any event, the magnitude of vibration of a panel is typically a few microns over the middle frequency range, well within the elastic limit of the material. Thus, the panel itself adds negligible distortion to the signal. Also, the magnet and coil move very little relative to each other, so that distortion caused by any unavoidable non-uniformity of magnetic field is minimised.

Figure 10 shows second and third harmonic from a typical conventional loudspeaker compared with that from a typical NXT.

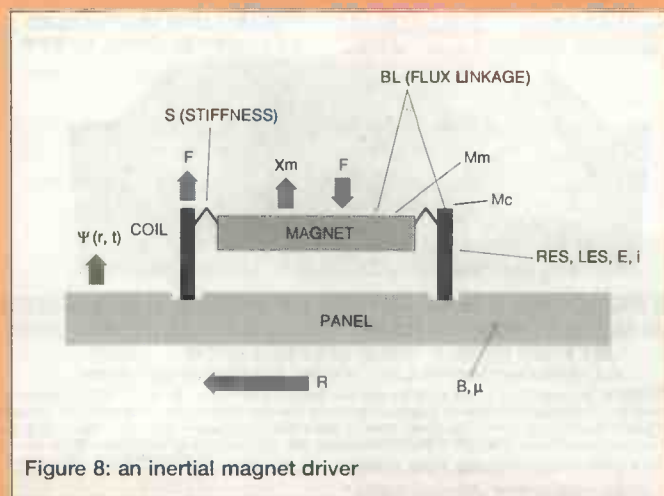


Figure 8: an inertial magnet driver

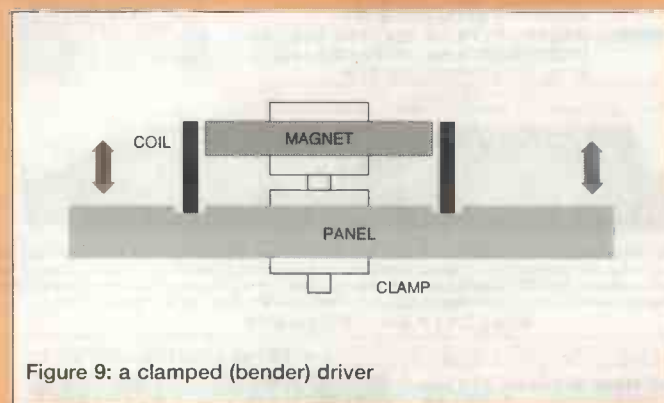


Figure 9: a clamped (bender) driver

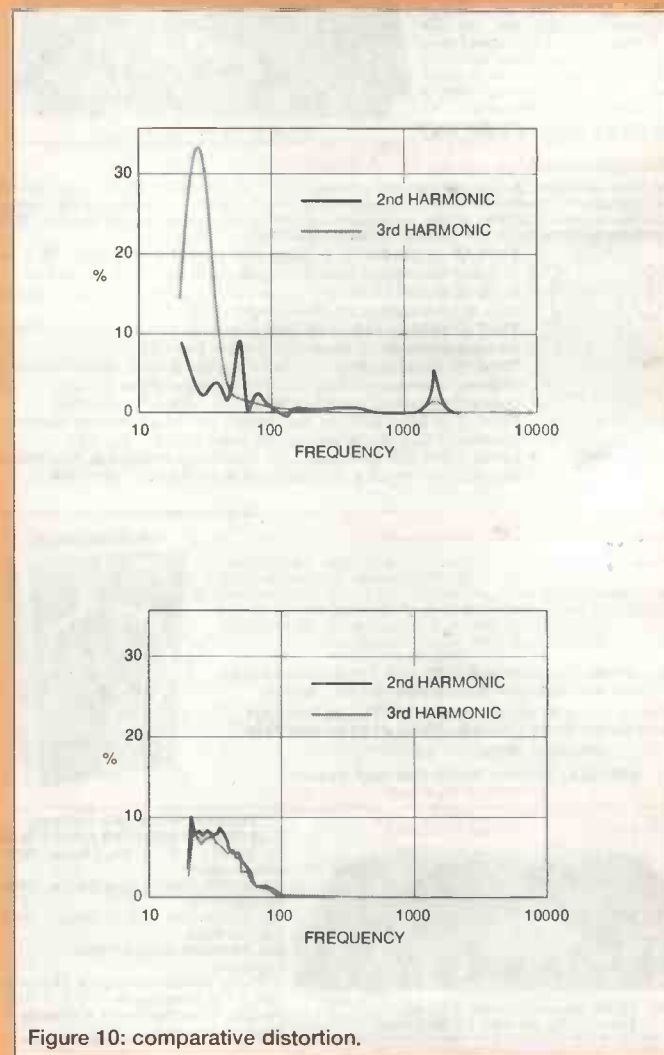


Figure 10: comparative distortion.

Surplus always
wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

Order as HIGRADE 286 **ONLY £129.00 (E)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered	£22.50
NE2000 Ethernet (thick, thin or twisted) network card	£29.00

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard sima connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable.

Many other options available - call for details. **Only £399.00 (E)**

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95 (B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95 (B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£18.95 (B)
5 1/4" Teac FD-55GFR 1.2 Meg. (for IBM pc's) RFE	£18.95 (B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE	£29.95 (B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95 (B)
Table top case with integral PSU for HH 5 1/4" Floppy or HD	£29.95 (B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00 (E)
8" Shugart 810 8" SS HH Brand New	£195.00 (E)
8" Shugart 851 8" double sided refurbished & tested	£250.00 (E)
Mitsubishi M2894-63 8" double sided NEW	£275.00 (E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00 (E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00 (E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

3 1/2" FUJI FK-309-26 20mb MFH I/F RFE	£59.95 (C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE	£59.95 (C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE	£69.00 (C)
3 1/2" RODIME R030575 45mb SCSI I/F (Mac & Acorn)	£69.00 (C)
3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00 (C)
5 1/4" MINISCRIIBE 3425 20mb MFH I/F (or equiv.) RFE	£49.95 (C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95 (C)
5 1/4" CDC 94205-51 40mb HH MFH I/F RFE tested	£69.95 (C)
5 1/4" HP 9754A 850 Mb SCSI RFE tested	£89.00 (C)
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00 (C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00 (E)
Hard disc controllers for MFH, IDE, SCSI, RLL etc. from	£16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£36.95
TELEBOX STL as ST but fitted with integral speaker	£39.50
TELEBOX MB Multi-band VHF/UHF/Cable/Hyperband tuner	£69.95

For overseas PAL versions state 5.5 or 6 mHz sound specification.

*For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Telebox's is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock. Call for info / list.

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition.

TIR & Swivel Base £4.75

VGA cable for IBM PC included.

External cables for other types of computers CALL

As New - Used on film set for 1 week only!!

15" 0.28 SVGA 1024 x 768 res. colour monitors. Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitor's. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed fan controls, VCR correction button etc. Good used condition - fully tested - guaranteed

Dimensions: W14" x H12 3/4" x 15 1/2" D. **Only £95 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. **Only £79.00 (D)**

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition. **Only £125 (E)**

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

MITS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400Kw - 400 Hz 3 phase power sources - ex stock	£245
IBM 8230 Type 1, Token ring base unit driver	£950
IBM 53F5501 Token Ring ICS 20 port lobe modules	£750
IBM MAU Token ring distribution panel 8228-23-5050N	£95
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE	£550
Trend DSA 274 Data Analyser with G703(2M) 64 I/O	£8500
Marconi 6310 Programmable 2 to 22 GHz sweep generator	£3750
HP1650B Logic Analyser	£950
HP3781A Pattern generator & HP3782A Error Detector	£1800
HP APOLLO RX700 system units	£175
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£675
HP3081A Industrial workstation clw Barcode swipe reader	£675
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£675
HP54121A DC to 22 GHz four channel test set	£1850
HP7580A A1 8 pen HPGL high speed drum plotter	£650
EG-G Brookdeek 95035C Precision lock in amp	£1425
Ving Eng. Mod 1200 computerised inspection system	£1425
Ling Dynamics 2Kw programmable vibration test system	£3750
Computer controlled 1056 x 560 mm X Y table & controller	£9500
Kelthley 590 CV capacitor / voltage analyser	£2200
Racal ICR40 dual 40 channel voice recorder system	£1200
Fiskers 45KVA 3 ph On line UPS - New batts Dec.1995	£1150
ICI R5030UV34 Cleanline ultrasonic cleaning system	£1450
Mann Tally MT645 High speed line printer	£1450
Intel SBC 486/133SE Multibus 486 system, 8Mb Ram	£1450
Zeta 3220-05 A0 4 pen HPGL fast drum plotters	£1450
Nikon HFX-11 (Ephiphot) exposure control unit	£1450
Motorola VME Bus Boards & Components List. SAE / CALL	£1450
Trilo 0-18 vdc linear, metered 30 amp bench PSU. New	£550
Fujitsu M3041R 600 LPM band printer	£1950
Fujitsu M3041D 600 LPM printer with network interface	£1250
Perkin Elmer 2998 Infrared spectrophotometer	£3750
VG Electronics 1035 TELETEXT Decoding Margin Meter	£950
Andrews LARGE 3.1 m Satellite Dish & mount (For Voyager)	£1995
Sekonic SD 150H 18 channel digital Hybrid chart recorder	£750
TAYLOR HOBSON Tallysur amplifier / recorder	£485
System Video 1152 PAL waveform monitor	£300
Test Lab - 2 mtr square quietised acoustic test cabinets	£850
Kenwood 9601 PAL Vectorscope - NEW	£850

Please call for further details on the above items

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays.

Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels.	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W)

Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)

Over 1000 racks - 19" 22" & 24" wide
3 to 44 U high. Available from stock !!

Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse !! (a driver is indeed available!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)**

Full MICROTOUCH software support pack and manuals for IBM compatible PC's. £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied, RFE. Fully tested and guaranteed. Windows compatible. **£59.95 (A1)**

Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640K DOS limit. Complete with data.

Order as: XT RAM Exp. 256k. £34.95 or 512k £39.95 (A1)

SIMM SPECIALS

1 MB x 9 SIMM 9 chip 120ns	Only £16.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£19.50 or 70ns £22.95 (A1)
1 MB x 9 SIMM 9 chip 80 ns	£21.50 or 70ns £23.75 (A1)
4 MB 70 ns 72 pin SIMM - with parity	Only £95.00 (A1)
INTEL 486-DX3 CPU £55.00	INTEL 486-DX66 CPU £69.00 (A1)

FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST

FANS & BLOWERS

EPSON D0412 40x40x20 mm 12V DC	£7.95 10 / £65
PAPST TYPE 612 60x60x25 mm 12V DC	£8.95 10 / £75
MITSUBISHI MMF-D6D12DL 60x60x25 mm 12V DC	£4.95 10 / £42
MITSUBISHI MMF-08C12DM 80x80x25 mm 12V DC	£5.25 10 / £49
MITSUBISHI MMF-09B12DH 92x92x25 mm 12V DC	£5.95 10 / £53
PANCAKE 12-35 92x92x18 mm 12V DC	£7.95 10 / £69
EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 V. £6.95. 80 x 80 x 38 mm - specify 110 or 240 V. £5.95	
IMHOFF B26 1900 rack mnt 3U x 19" Blower 110/240V NEW	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

DISPLAY
-ELECTRONICS-

ALL MAIL & OFFICES

Open Mon-Fri 9.00-5.30
Dept ET. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP

Open Mon - Sat 9.00 - 5.30
215 Whitehouse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL©

The Original
FREE On line Database
Info on 20,000 + stock items!
RETURNING SOON!

ALL ENQUIRIES

0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.00, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=£21.00. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O E. 06/6

Commercialisation

NXT have licensed their sister companies Mission and Wharfedale to make loudspeakers with this technology, but they are also licensing other, unrelated, companies worldwide, such as NEC and the pre-formed wall panel manufacturers mentioned above. They have recently licensed Samsung. A cross-licensing agreement has also been signed with United States company Noise Cancellation Technologies (NCT), with NCT, which has developed its own piezo-electric Flat Panel Transducer technology, sublicensing the joint intellectual property in the automotive and transportation sectors allied to noise cancellation issues, while NXT expands its sub-licensing activities in all other fields. Each company will be able to include the other's technology in its own sub-licences

What the licensee gets is design software, and the right to use the technology in a particular product area. Without the software it would be effectively impossible to design an NXT type loudspeaker, and even with the software it may be difficult first time round. The NXT team have been able to advise licensees on how to get the results they need on their introduction to the new technology.

They have also suggested a machining technique. It is necessary for the correct functioning of the loudspeakers that the edge is free to vibrate normally. Cutting methods which cause irregularities on the edge, or which melt the edge of the material to form a stiffer rim around the cut, interfere with the correct functioning of the panel. NXT has found that cutting with high pressure water jets is most effective.

The folks at NXT reckoned that products incorporating the next flat panel technology might be available as early as July 1997, perhaps in the USA. The first application on the market is quite likely to be - yes - a multimedia laptop PC. The first hifi applications may be available by the end of 1997.

The design and the tuning of the manufacturing process to produce loudspeakers that work well may be much more difficult than for conventional loudspeakers, but it is also likely that the unit costs in volume production will be much less than for conventional speakers, at least for the higher quality applications. Maybe this will not initially translate to lower prices, but rather to higher ones due to the novelty value. In the long run, however, I expect top quality loudspeakers which I can place on the wall, or in the wall, or even *instead of* the wall, to be available prices comparably lower than the traditional loudspeaker technology.



NXT speakers with their lightweight nature and superior sound quality, are a natural match for all multimedia computing applications, in particular notebooks and PDAs.



NXT speakers integrated with rear parcel shelf of a car, acting as a structural member. The nature of NXT sound provides uniform sound distribution in the car environment without any hot spots.

Below: NXT's table of applications for the first products expected on the market

Application	Response	Sensitivity	Characteristics
SonTile™	100Hz-12kHz	87db	Unique voice intelligibility; concealed speaker mounting; lightweight; exceptional sound distribution; very low installation cost.
Multimedia and laptops	200Hz-12kHz	84dB	Much superior to conventional speakers computers fitted to laptops and mm computers
Stereo audio (.6msq)	100Hz-18kHz	88dB	High quality stereo sound, slimline, matched to decor
SoundField™	120Hz-18kHz	87dB	Exceptional ambient sound field creation, most suitable for rear channel AV; cinema and domestic
SoundVu™	60Hz-18kHz	88dB	Unique performance and combination of diffuse soundfield loudspeaker with video screen; large audience coverage.

Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger .. for as little as £49.00

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

Hardware and software are supplied together as a package - no more worries about incompatibility and no programming required.

Pico Technology specialises only in the development of PC based data acquisition instrumentation. We have the product range and experience to help solve your test and measurement problem.

Call for your guide on 'Virtual Instrumentation'.
We are here to help you.



The ADC-10 supplied with PicoScope gives your computer a single channel of analog input.

ADC-10 £49
with PicoLog £59

Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog data logging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199 TC-08 £224 with cal. Cert.
complete with serial cable & adaptor. Thermocouple probes available.



Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible input ranges ($\pm 50\text{mV}$ to $\pm 20\text{V}$) make the unit ideal for audio, automotive and education use.


ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50\text{mV}$ to $\pm 20\text{V}$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00
ADC 200-50 £499.00

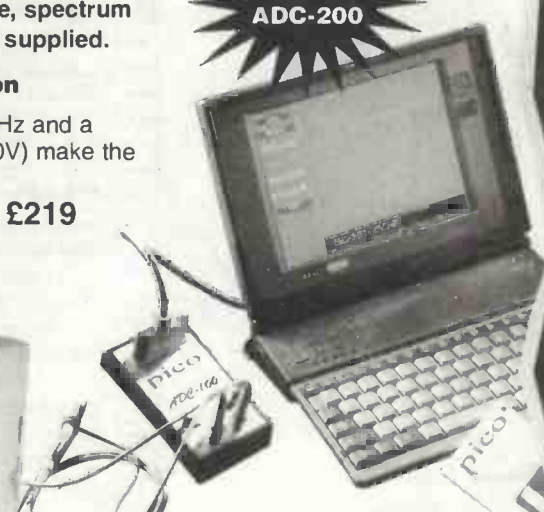Both units are supplied with cables, power supply and manuals.



Call for free demo disk and product range catalogue

Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: + 44 (0)1954 211716 Fax: + 44 (0)1954 211880
E-mail: post@picotech.co.uk Web site: <http://www.picotech.co.uk/>

Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

releasing PC potential


releasing PC potential

Pico Technology Limited

EASY-PC Professional XM

Schematic and PCB CAD

From Super Schematics

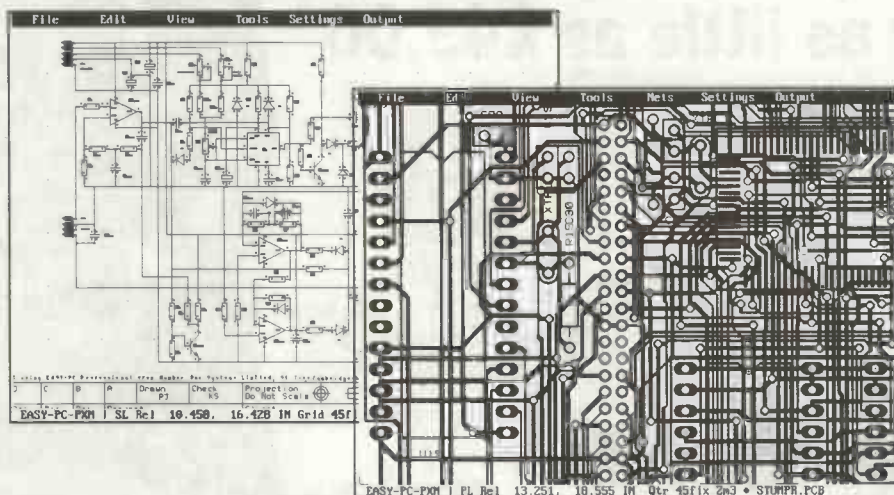


To Perfect PCB's

Prices from £75

- Runs on:- PC/ 386/ 486 with VGA display
- Links to PULSAR (logic), ANALYSER III (analogue) & LAYAN (electromagnetic) simulators.
- Design:- Single sided, Double sided and Multi-layer boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Optional, powerful, 32 bit Multi-pass, Shape based, Shove Aside, Rip-up and Re-try Autorouter.

Simulation can even include the parasitic effects introduced by the Board Layout

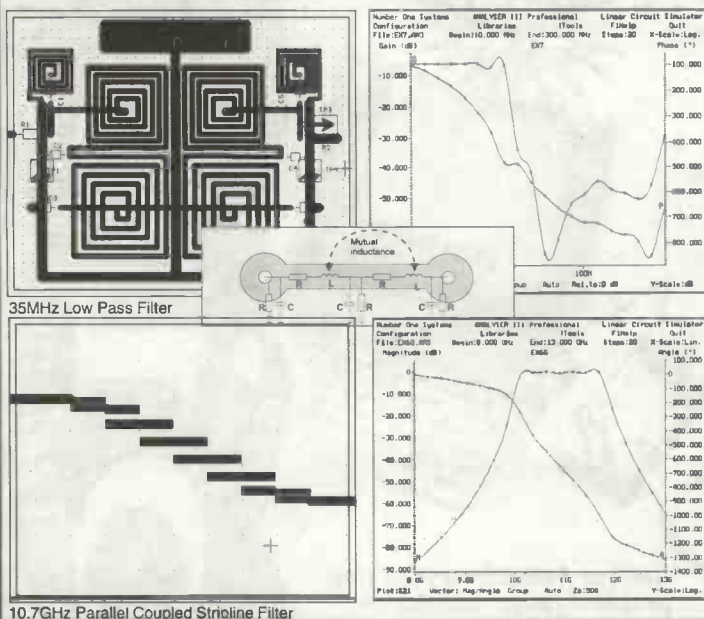LAYAN - Electro-magnetic Simulation ONLY £495



Affordable Electronics CAD

EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	From \$245	£145
MultiRouter: 32bit Multi-pass Autorouter	\$475	£295
LAYAN: Electro-Magnetic PCB Layout Simulator. Include the board parasitics in your Analogue simulations. Links with and requires EASY-PC Professional XM and ANALYSER III Professional	\$950	£495
PULSAR: Digital Circuit Simulator	From \$175	£98
ANALYSER III: Analogue Linear Circuit Simulator	From \$175	£98
FILTECH: Active and Passive Filter Design program	From \$245	£145
STOCKIT: New comprehensive Stock control program for the small or medium sized business	From \$245	£145
EASY-PC: Entry level PCB and Schematic CAD.	\$135	£75
Z-MATCH: Windows based Smith-Chart program for RF Engineers.	From \$245	£145

*We operate a no penalty upgrade policy.
US\$ prices include Post and Packing
Sterling Prices exclude P&P and VAT.*

For full information and demo disk, please write, phone, fax or email:-

Number One Systems

UK/EEC: Ref. ETI, Harding Way, St.Ives, Cambridgeshire., ENGLAND, PE17 4WR.

Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042

USA: Ref. ETI, 126 Smith Creek Drive, Los Gatos, CA 95030

Telephone/Fax: (415) 968-9306

e-mail: sales@numberone.com

International +44 1480 461778

<http://www.numberone.com>



ada4prla

Construction Authors

If you have designed and built any kind of electronics gadget for yourself, your home, your friends or your business, it may be suitable for publication in ETI. You may be a private hobbyist, an engineer of advanced standing, or a student. You may be yourself and a soldering iron, a club or a business.

Read on!

You may have a one-off project you would like to share; you may be a regular constructor with a new design you are especially pleased with, or you may be a pro designer trying out ideas and looking for feedback.

Your ideas may be simple or complex, analogue or digital, computer-related or rooted in tradition; elaborately cased or (in some cases) not cased at all.


ETI is looking for original project design for publication. "Original" simply means that you have designed the project for a particular purpose or to a general specification, and have worked out how you want to do it for yourself. You can be applying well-known and established techniques, or using the latest components in new applications, as long as the final result is your own design.

For further details of authors' fees and how to write up a project for publication, please write to ETI for our Potted Project Production information sheet. A self-addressed envelope

WRITE FOR ETI!

Much as we like all mod cons, project authors do not have to produce CAD output, professionally drafted plans or Shakespearean prose. ETI's mission is to publish projects and "how to" articles. ETI does not buy news items or short feature articles from outside contributors. ETI commissions a small number of full length feature articles from experienced independent contributors only.

Stock Control Software

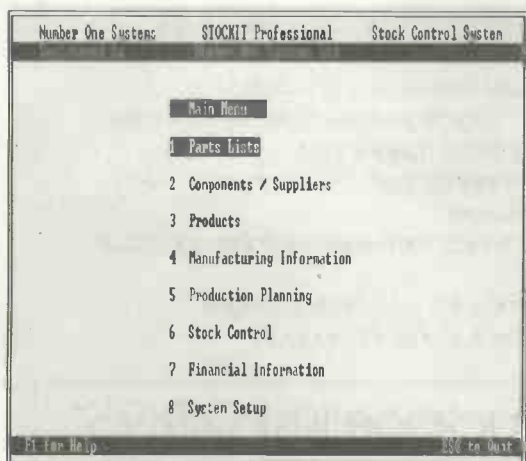

- STOCKIT Professional Provides Comprehensive Capability and Features.
- Includes Full Financial Information, Assigns Stock To Production, Provides Stores Picking Lists, Bin Locations, Trial Kitting, Minimum Pack Quantities, Sub-assemblies, etc.
- Print Requests for Quotations and Orders on plain paper - allowing customisation.
- Allows Scheduled and Random Orders, Nested Products, Automatic re-ordering
- Low cost - High Performance
- Runs on Low Cost 386sx 4MB ram PC
- Price only £395 for STOCKIT Professional

Prices exclude VAT& P&P

Number One Systems

Write, fax, phone or e-mail for full information.

UK/EEC: Ref: ETI, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR. e-mail: sales@numberone.com

Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042

International +44 1480 461778/494042

USA: Ref: ETI, 126 Smith Creek Drive, Los Gatos, CA 95030

Telephone/Fax: (408) 395-0249

<http://www.numberone.com>




adhistk

Electronics Principles 3.0

For Windows 3.1, '95 & NT.

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Electronics Principles 3.0 now contains fifty-eight Windows and an extended range of nearly 300 fully interactive analogue and digital electronics topics. Currently used in hundreds of UK and overseas schools & colleges to support GCSE, A-level, BTEC, City & Guilds and university foundation courses. Also NVQ's and GNVQ's where students are required to have an understanding of electronics principles.

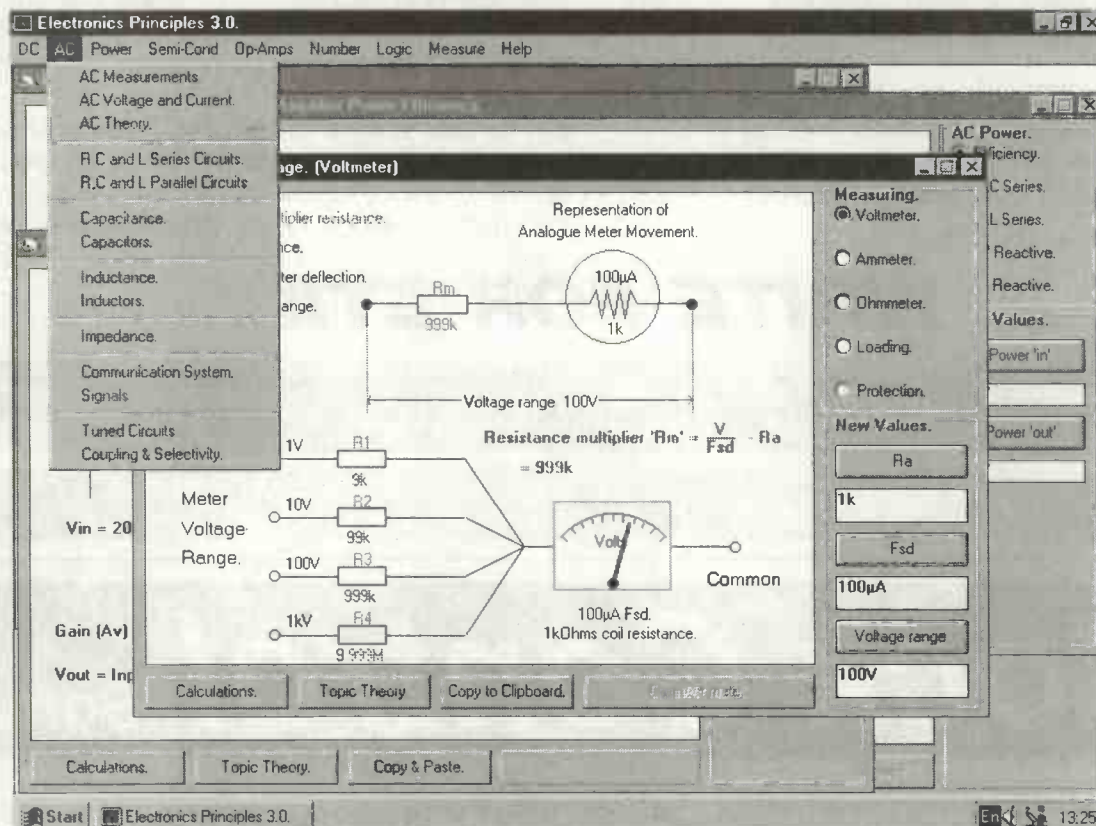

Other titles available.

Electronics Toolbox 3.0 £19.95*

Presents commonly used electronics formulae and routines in a way that makes calculations easy. Just select the topic, 'pop' in your values and find the result.

Mathematics Principles 3.0 £49.95*

Study or revise mathematics in what we believe is an interesting and enjoyable way. Nearly two hundred topics, including the GCSE syllabus with interactive, full colour graphics to enable 'learning through doing'.

Electronics Principles 4.0 £99.95*

Contains all of the extended version 3 and many more digital and analogue topics. Plus: Microprocessor & microcomputer operation, registers, arithmetic and logic unit, ROM, RAM etc. Addressing modes and full instruction set can be executed on the screen.

Inputs & outputs use electronics symbols.

Scientific notation avoided where possible to make numbers & calculations meaningful.

Experiment with standard textbook examples, even check your homework!

Hundreds of electronics formulae available for circuit investigation.

Multi-user site licence for schools & colleges.

Produce OHP slides & student handouts.

Complete Package just £49.95*

For more information, upgrades or software by return.

Telephone (01376) 514008.

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ. Tel/Fax: 01376 514008.

E-Mail sales@eptsoft.demon.co.uk Web pages <http://www.octacon.co.uk/ext/ept/software.htm>

* UK Please Add £2 per order for post & packing + VAT. Make cheques payable to EPT Educational Software.

Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date.


OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.

Low power, light-powered

By Terry Balbirnie

Continuity Quick-Tester

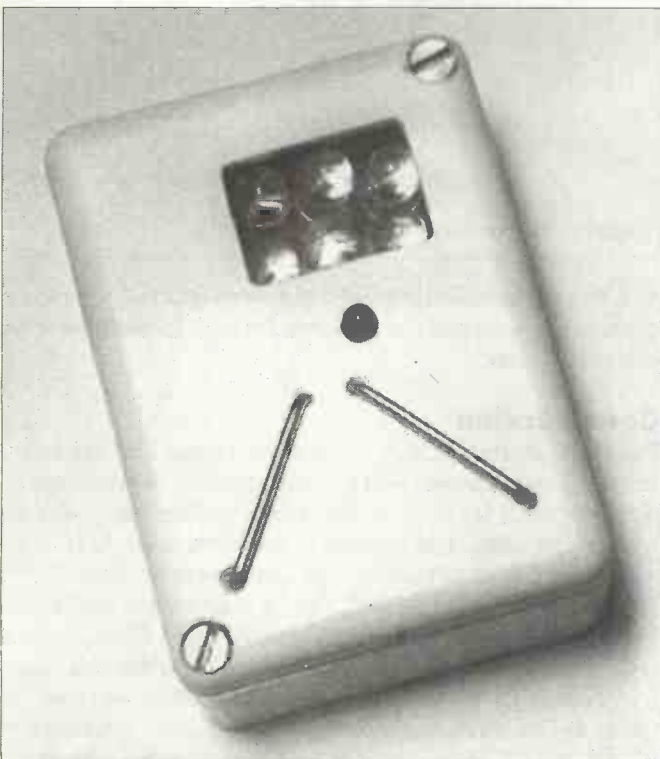**Hold it up to a light
- and presto!
Needs no batteries.**




A continuity tester is a device that indicates a low resistance path. It would be useful having one in the home or workshop for testing fuses and filament lamps, to identify switch and relay contacts, to look for breaks in pieces of wire or PCB tracks and to find faulty connections in plugs and sockets. You could also use one to check situations where there should not be continuity - for example, where a blob of solder has bridged adjacent PCB tracks.

Using a meter

Of course, if you have a multi-tester you could set this to a low resistance range and use it for the purpose. A low reading would indicate continuity. Using a meter would be fine if it was always to hand and if it was to be used by an experienced person. However, someone who did not have the necessary knowledge would not be able to set the range correctly and they might have difficulty interpreting the reading. To have an instrument specially made for the job is definitely a good idea. The traditional type has the disadvantage of being battery-operated - as it will probably be used only occasionally, the battery is likely to be found missing just when you need to make a test (having been "borrowed" for something else), or gone flat from being left on or just from old age.

Testing - with a difference

This continuity tester is different because it does not use batteries and has no on/off switch. This is because it uses light as an energy source! Even artificial room lighting will be sufficient to make it work. Normally, the tester will be left in a position where light can reach it, such as on a window sill, and it will then be available for instant use. If it has been kept in the dark - in a drawer, for example, it will be ready to operate in a minute or two. This circuit is principally a one-shot device intended to give one test at a time. This is because, after providing a positive result, there is a delay before it will respond again. This "dead" time will depend on the brightness of the ambient light - in normal room lighting it will be about one or two minutes but in bright daylight it may only be a second or two. There is a trick which enables several tests to be made in quick succession and this will be explained at the end.

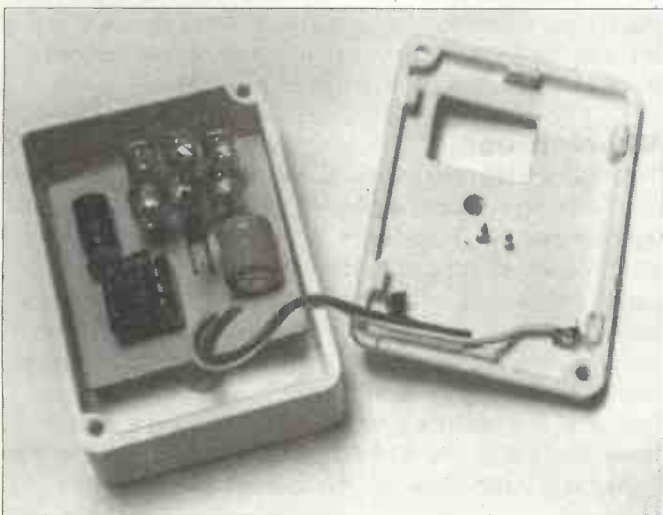

The circuit will respond to resistances from zero to about 200 ohms. This makes it suitable for checking lamp filaments (whose cold resistance will be a few ohms or tens of ohms), many transformer windings, chokes and relay coils in addition to "straight" continuity tests. It will even identify a good diode (because this will show continuity when connected one way but not the other). The Continuity Quick-Check is very versatile and, no doubt, readers will find other uses for it.

The object to be tested is used to bridge a pair of wire rails arranged in the form of an inverted "V" on top of the box. A red LED will then flash to show continuity. Most fuses, switch tags, bulbs and connectors will bridge the rails quite easily. Where this is not possible, a pair of extension leads may be made, as described at the end.

How it works

The circuit for the Continuity Quick-Check is shown in figure 1. The components labelled D1 - 6 are silicon photodiodes (LEDs). However, in this circuit they are used as photovoltaic cells. When light shines on them, they develop a small voltage between their ends. This voltage will be some 0.2V to 0.4V over a wide range of light levels. The ability of this type of device to deliver current is very limited and will depend on the brightness of the light reaching it. In sunlight, for example, it may reach 1mA or more. In room lighting it will fall to 2mA or less. Photovoltaic cells make a convenient and compact power source when only a small current is needed. @B:Conventional solar cells appear to be available only in larger sizes and since several of them would be needed, the finished device would be rather large. Also, they do not respond as well as the specified devices in room lighting. Note that not all photodiodes will work in this circuit, and it is essential to use the type shown in the parts list unless you are prepared to experiment.

The photodiodes are connected in series. Thus, the voltage across the set will be six times greater than that across one. With an average value of 0.3V, this will provide a nominal 1.8V. This charges capacitor C1, which is then used to power the rest of the circuit. If the LEDs are shaded so that light can no longer reach them, the charge stored in C1 cannot easily drain back through the diodes. This might appear to be possible because they are forward biased (see figure 1). However, each one needs about 0V6 across it to conduct (that is, 3V6 for the set of six) but the maximum voltage across the capacitor is only 2V4 (with 0V4 across one photodiode) or thereabouts. The photodiodes can therefore "pump" charge into the capacitor but, once there, it can only escape by leakage or, of course, by being used. In the prototype unit, the capacitor self-discharges in 30 minutes approximately. After having charged up, the tester will therefore be capable of working for some time even in darkness.

When the rails are bridged by a low resistance, the positive end of C1 will be connected to IC1 input, pin 5, and establishes a supply to it. This component is an LED flasher/oscillator and C2 is the capacitor needed to make the circuit oscillate (provide pulses). There is also a voltage-doubling effect whereby the pulses applied to light-emitting diode, LED1, are of double supply voltage (nominally 3V6). Note that no series resistor is necessary here because current limiting takes place on the chip. LED1 will continue to flash until C1 has discharged to about 1V. Below this, the ic stops working and also (taking into account the voltage doubling effect) there will be insufficient to operate the LED. Normally, the charge arriving will be much less

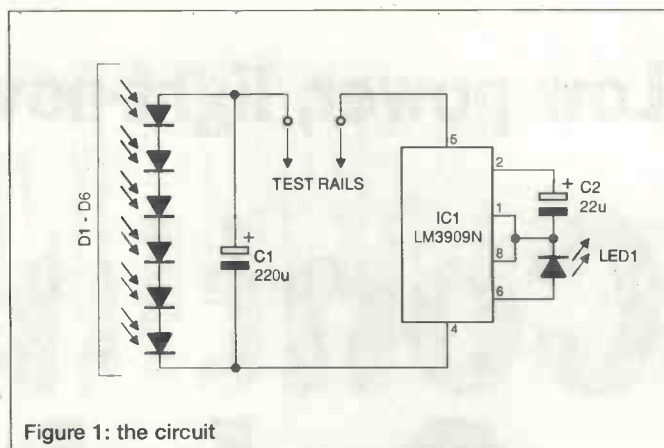


Figure 1: the circuit

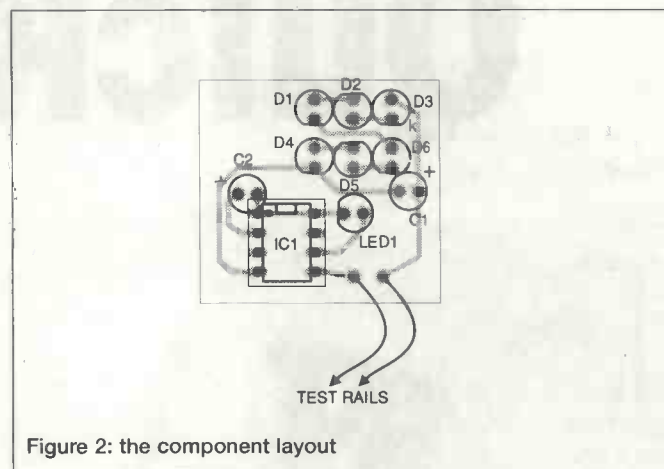


Figure 2: the component layout

than that being drawn so that C1 will be substantially discharged during each test - hence the need for recovery time referred to earlier.

Construction

The PCB component layout is shown in figure 2. Begin by mounting the ic socket and photodiodes D1 - 6 (these are simply labelled "1" to "6" in the diagram). Take care, because it is easy to solder one or more of them the wrong way round and this would prevent the circuit from working. The cathode (negative) of each ("k" in the diagrams) is identified by a slightly shorter lead and by a "flat" on the body. Add the LED, again, taking care over the polarity. Note that, although a standard LED will work, a high-brightness type will give better results. Both capacitors are electrolytics - check the polarity. Solder short pieces of light-duty stranded wire to the pads labelled "test rails". Insert the ic into its socket with the correct orientation. Since this is a CMOS device, it can be static sensitive - it is wise to touch something earthed (such as a water tap) before handling the pins.

Check it out

The PCB should now be checked before it is mounted in the box. Keeping the wires separated, place it on a table so that light reaches the photodiodes. Allow about two minutes for the capacitor to charge sufficiently for a test to be made. Touch the wires together. The LED should flash a few times showing that there is a low-resistance path between them. If this test does not work, allow more time for the capacitor to charge or use brighter light.

If all is well, the box may be prepared. Begin by measuring the positions of the photodiodes and LED on the PCB. Mark these places on the lid and make holes to



correspond. The two wire rails should now be cut out. In the prototype, pieces of paper clip were used with their ends bent through right-angles. Small holes are drilled in the lid so that, when the ends of the wires are passed through, they form an inverted "V". Leave a small space between each rail and the lid of the box. The wires from the PCB should now be soldered to one end of each rail on the inside. Paper clip material is not the easiest to solder to, and care must be taken to use sufficient heat to make good electrical connections without melting the plastic. If necessary, the ends may be locked in position using a little quick-setting epoxy-resin adhesive or they may be carefully bent over. The PCB may be secured inside the box using an adhesive fixing pad and raised as necessary so that the LED protrudes slightly through its hole.


Short pieces of wire with a small crocodile clip on one end and a test probe on the other will be useful for checking items where it would be difficult bringing them into direct contact with the test rails. The crocodile clips are simply clipped on to the rails. This method will be useful when checking the continuity of PCB tracks.

Multiple tests

There may be times when several tests need to be made in quick succession. This may be done by holding the unit within 1ft (30cm) of an ordinary, say 60W, light bulb for two or three seconds each time. This will make the unit ready for use again almost instantly. Note that when using the tester, the best sources of light are daylight and tungsten filament bulbs. Fluorescent light is rather poor for the purpose.

All components for the Continuity Quick-Check were obtained from Maplin.

Calling all Radio enthusiasts

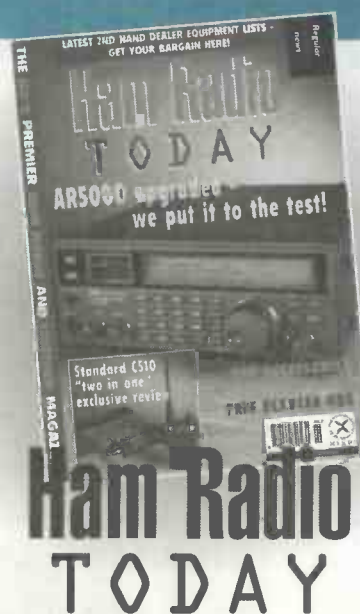

The magazine for amateur radio

New equipment, scanners, packet radio, construction, club news, views and much more.

This month in HRT:

Exclusive Review

The new Standard C510 "two in one" handheld with Power Booster unit.

Aerial Matching Unit (Part 2)

Coil winding, construction and operation of last month's Raymond Haigh project.

Upgrade Review

AOP AR5000 receiver upgraded - we put it to the test.

New! Trade-in Market Place
Second-hand dealer equipment lists.

QRP Accessories

Dick Pascoe G0BPS with two easy "Oner" low power accessory projects.

New! Net Communication

Jeremy Boot G4NJH with amateur radio topics on the Internet.

"Ranging the Box"

Brian Kendal G3GDU shows how to measure the distance from a repeater.

PLUS

Radio Today, Scanners for listeners, free radio Software Offers, free reader's ad's, band reports and more.

OUT NOW!

All contents are currently planned, but may alter.

PARTS LIST

Capacitors

- C1 220u 10V radial electrolytic
- C2 22u 10V radial electrolytic

Semiconductors

- IC1 LM3909N
- D1 - 6 SFH2030 silicon photodiodes, Maplin order code CY90X
- LED1 3mm high-brightness red LED


Miscellaneous

PCB materials, 8-pin dip socket, plastic box.

See Next / Last Months Ad. for
 COMPONENT ACCESSORIES

4000 Series	74HC Series	74LS Series	74ALS Series	74S Series	74V Series	74V Series	74V Series	74V Series
-------------	-------------	-------------	--------------	------------	------------	------------	------------	------------

Infra-red Activated Auto Light

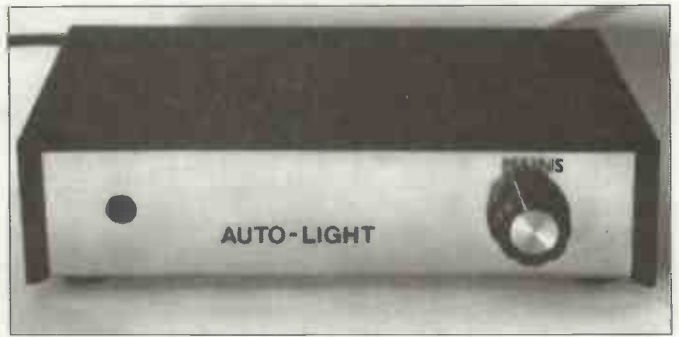

Robert Penfold's auto light switch is driven by a low-sensitivity, low-power pyro detector to provide movement-sensitive indoor lighting for night-time wanderers.

This project will be of interest to anyone who has got up in the middle of the night and stumbled around looking for the light switch. It is essentially the same as an outside security light, but it has much lower sensitivity as it is only intended for indoor use. Simply moving around near the sensor results in the controlled light being switched on. You can climb the stairs with your Once switched on, the light remains on for about one minute after the last activation of the sensor. This delay is sufficient to ensure that the light does not get a bout of the "flickers", but it is short enough to prevent the light from staying on for long periods of time when no one is present. The delay time is easily altered to suit individual requirements.

Like security lights, this unit uses a passive infra-red detector, but as only a limited range is required it does not use any form of lens system. Even so, a range of a few metres can be achieved. One disadvantage of using a lens-free detector is that the angle of view is not very large. However, this will not normally be of any great significance, and good results should still be obtained provided the unit is installed in a suitable place. Of course, a lens system can be used if either high

sensitivity or a wide angle of view are essential, but a lens should not normally be required. This type of sensor is activated by the body-heat of someone moving within its area of coverage. An advantage of this type of sensor is that it is not easily "fooled", and false alarms are rare occurrences. Something like a moth flying around the room will not activate the light!

The pyro-sensor

The infra-red sensor, or "pyro" sensor, as this type of component is normally called, is a ceramic device. It is in some respects similar to a Piezo-electric component such as a crystal microphone, and consists of a slice of ceramic material with an electrode on each surface. However, rather than the twisting of the ceramic material producing a voltage across the electrodes, it is heat that produces an output signal. Normal semiconductor infra-red detectors are sensitive to wavelengths of around 900nm, which is close to the visible red part of the spectrum. Pyro sensors operate at much longer wavelengths of around 1 to 20 micrometres. In other words, pyro sensors carry on where ordinary infra-red devices leave off.

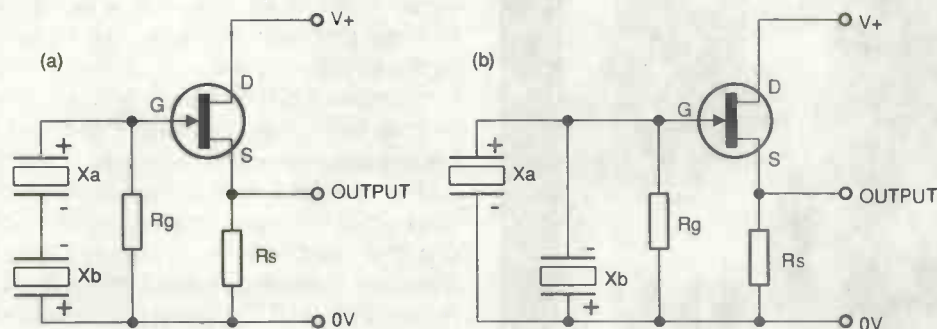


Figure 1: two-element pyro-sensors use anti-phase sensing elements to reduce sensitivity to background infra-red


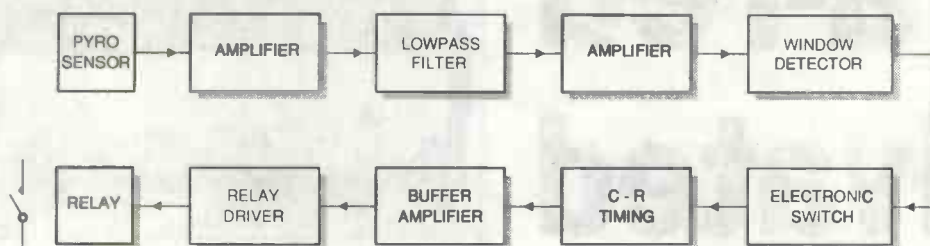


Figure 2: the block diagram for the auto-light

Most pyro sensors have two sensing element connected out-of-phase. Some data sheets show the two elements connected in series (figure 1a), while others show them connected in parallel (figure 1b). In either case the effect is much the same, with the output from one element tending to cancel out the signal from the other element. This may seem to be of little practical value, but you have to bear in mind that the purpose of a pyro sensor is not to detect a steady level of infra-red. It is designed to detect a moving infra-red "target", and in normal use the infra-red "light" is swept across the sensor as the detected person moves across the field of view. The infra-red signal is therefore detected by one element and then the other. This gives a positive signal from the first element followed by a negative signal from the second element, or vice versa.

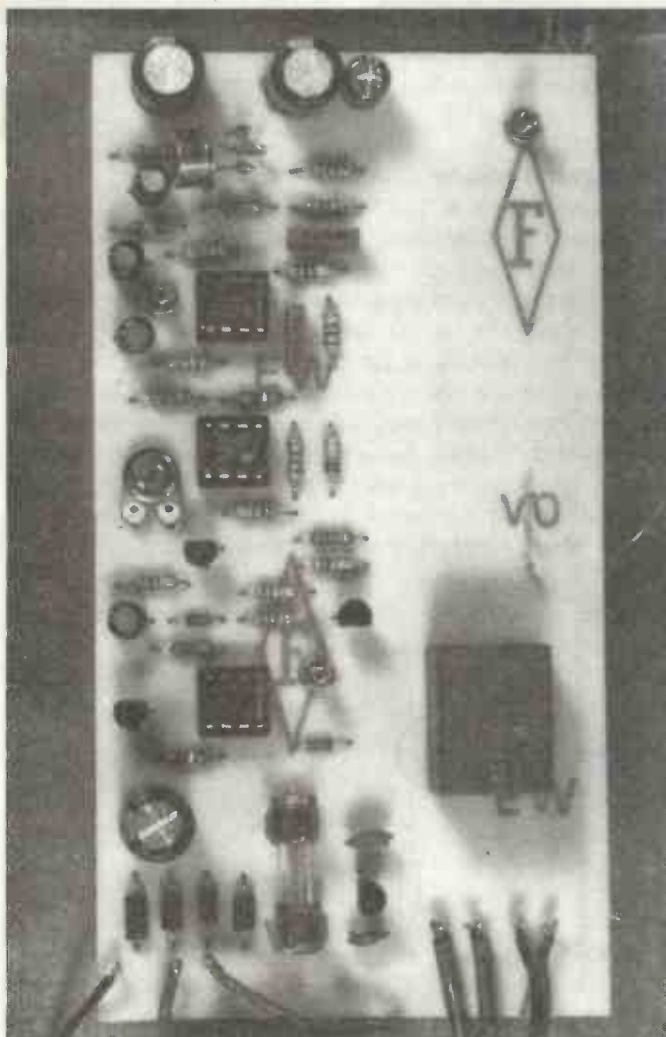

In either event, the result is a strong output signal from the sensor. The point of using two sensing elements is that it provides a cancelling effect on any changes in the background infra-red level, which will affect both elements simultaneously, it but provides good sensitivity to anyone crossing the field of view. As a result, it is possible to achieve high sensitivity with only very infrequent spurious triggering.

Practical pyro sensors invariably include a jfet buffer amplifier, which provides a relatively low output impedance despite the high output impedance of the sensing elements. The load resistor for this amplifier is sometimes included in the sensor, but in most cases it is a discrete component. The gate bias resistor is invariably built into the sensor. A pyro sensor has a strictly limited frequency response which typically extends from about 0.3 hertz to around 3 hertz. The low frequency response is limited by the value of the bias resistor in the buffer amplifier.

The high frequency response is limited by the time it takes for the sensing elements to heat up and cool down. The slices of ceramic material are made very thin in order to maximise the high frequency capabilities, but an upper limit of a few hertz is the best that can be achieved. In practice this very limited response is adequate, and is actually well matched to the frequency of the signals generated in this application.

System operation

Figure 2 is the block diagram for the automatic light. The output level from the pyro sensor will usually be extremely small, and may sometimes be under one millivolt peak to peak. A large amount of amplification is therefore needed in order to provide reliable operation of the main circuit. The output signal from the sensor is therefore boosted by two high gain amplifiers. These provide an output level of a few volts peak to peak even if the output signal from the pyro sensor is very weak. With such a high level of gain there can be major problems with noise. This noise is in part generated by the amplifiers, but it is to a large extent produced by the pyro sensor. It can be greatly reduced by lowpass filtering, and the filter cut-off frequency can be set very low due to the low signal frequencies involved in this application.

This enables a large amount of attenuation to be obtained at the mains frequency of 50 hertz. Direct pick-up of mains "hum" from mains powered lighting seems to be absolutely minimal, but it is difficult to avoid a small amount of stray pick-up in the wiring. The lowpass filtering avoids problems with spurious triggering due to stray pick-up of "hum" and noise spikes in the input wiring.

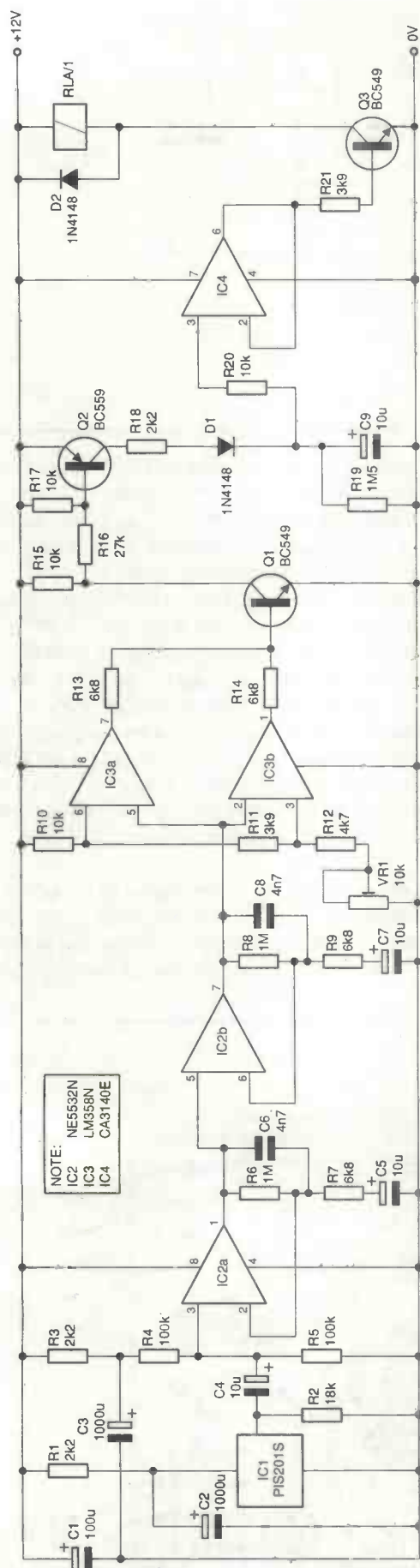


Figure 3: the main circuit diagram for the auto-light

The output potential from the second amplifier is normally about half the supply voltage, but it varies around this level when the unit is activated. A window discriminator detects when the voltage potential of the amplifier strays by about one volt or more from its quiescent level. It then turns on an electronic switch which in turn drives a C-R timing circuit. This circuit has a fast attack time so that the light is switched on almost at once when the unit is activated. Its decay time is very much longer so that once the light is switched on it does not switch off again for about half a minute. If the unit is activated before the voltage on the timing capacitor has decayed, the charge voltage will be boosted to its maximum level again. In this way the time that the light is switched on is controlled by a combination of the timing circuit and whether or not the unit continues to be activated.

The timer stage feeds into a buffer amplifier which ensures that loading on the timing capacitor does not significantly affect the circuit's decay time. The output of the amplifier controls the relay via a simple driver stage. A normally open relay contact connects power through to the controlled lamp while the relay is switched on.

Circuit operation

Figure 3 shows the main circuit diagram for the auto-light. The circuit for the mains power supply unit and the other mains wiring is shown separately in figure 4. Taking figure 4 first, IC1 is the pyro sensor, and it is a type which requires a discrete load resistor (R2). The circuit should work well with any similar pyro detector, but R2 should obviously be omitted if a sensor having an integral load resistor is used. C4 couples the output from IC1 to a two stage non-inverting mode amplifier based on IC2. The two sections of IC2 are used in identical amplifiers which each provide a voltage gain of about 150. The lowpass filtering is provided by C6 and C8, which provide increased feedback and reduced gain at frequencies of more than a few hertz. Biasing for these direct coupled stages is provided by R4 and R5. With such high gain there is a risk of feedback through the supply lines causing low frequency oscillation. Both IC1 and the bias circuit for IC2 are fed from the positive supply line via a decoupling network which has a long time-constant, and this avoids problems with low frequency instability.

IC3 is used in a conventional window discriminator which has R10, R11, R12, and VR1 to produce the two reference voltages. VR1 enables the reference voltages to be adjusted to suit the exact output voltage of IC1 under standby conditions. The output of IC3a goes high if the upper reference level is exceeded, and the output of IC3b goes high if output of IC2b drops below low lower reference potential. In either instance, Q1 is switched on, and it in turn switches on Q2. C9 is then rapidly charged via R18 and D1, but when Q2 switches off again D1 ensures that no current can flow back into Q1 and Q2. The only significant discharge path for C9 is through the high value of R19. The voltage on C9 is used to control switching transistor Q3 via a simple voltage follower (IC4). Q3 drives the relay coil, and the relay remains switched on while the voltage on C9 remains at more than about 0.6 volts. It takes roughly one minute for the charge on C9 to decay from its maximum level to the point where the relay switches off, but this time is easily changed as it is proportional to the value of R19. For example, changing the value of R19 to 750k gives a hold-on time of about 30 seconds.

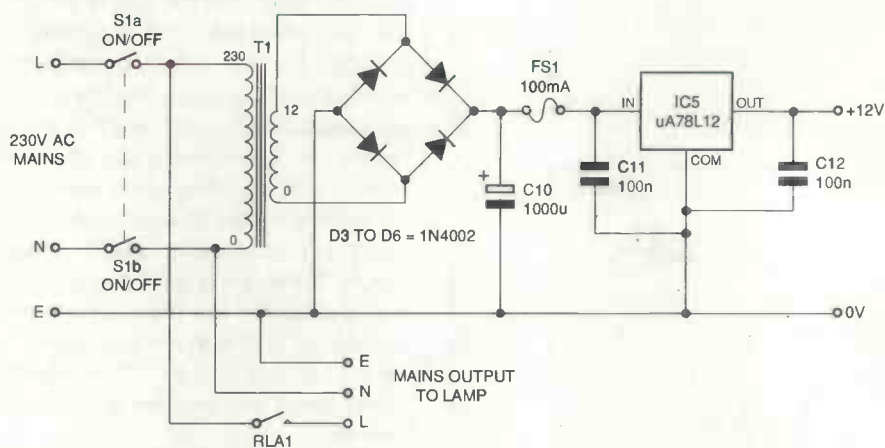


Figure 4: the circuit diagram of the mains power supply

The mains power supply unit (figure 4) has T1 to provide isolation from the mains and a voltage step-down. D3 to D6 form a bridge rectifier which full-wave rectifies the output from T1. Smoothing is provided by C10, and IC5 then provides regulation and electronic smoothing of the output. IC5 incorporates current limiting which protects the supply in the event of an overload, and further protection is provided by fuse FS1. The current consumption of the main circuit is only a few milliamps under standby conditions, but it rises to around 45 milliamps when the relay is switched on.

Construction

The component overlay for the printed circuit board appears in figure 5. This board is reasonably simple to construct, but there are one or two points that require some amplification. As far as the electrical characteristics are concerned, any relay that has a coil resistance of about 300 ohms or more and a 12 volt coil is suitable for use in this circuit. The only other proviso is that it must have at least one normally open contact having adequate ratings for this application. This

means a contact rating of at least 230 volts AC and one amp. On the other hand, only the specified relay on an exact equivalent will fit this printed circuit design properly. This makes it extremely difficult to use an alternative relay, and I would strongly advise against doing so.

The CA3140E used for IC4 has a PMOS input stage, and consequently requires the normal anti-static handling precautions. The most important of these is to fit the device in a holder, and it is not a bad idea to use holders for the other DIL integrated circuits even though they are not static-sensitive. The CA3140E should be supplied in some form of anti-static packaging, and it should be left in this until it is time for it to be fitted into its holder. Try not to handle the pins any more than is really necessary when fitting this device, and avoid any obvious sources of static charges.

One way of arranging the general layout of the unit is with the circuit board mounted on the rear panel of the case and the pyro sensor "looking" through a window cut in the front panel. If this approach is used the pyro sensor can be

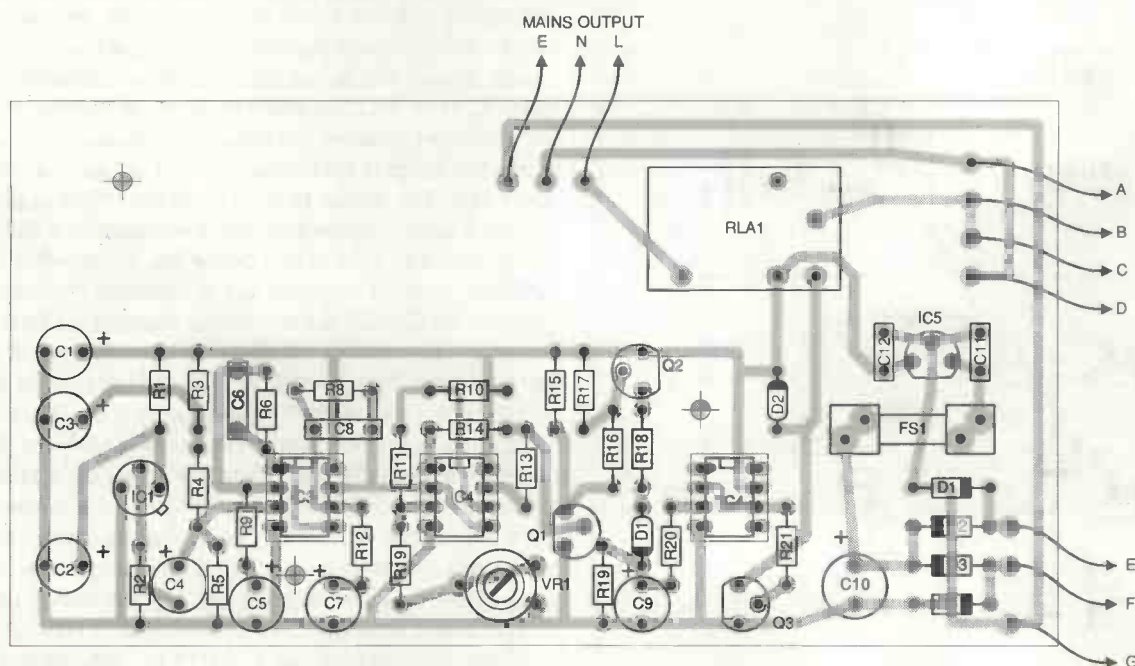


Figure 5: the component layout for the auto-switcher



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual Channel	£150
Cossor 3102 - 60MHz Dual Channel	£250
Gould 1602 - 20 MHz D.S.O. with printer (cursors)	£1150
Gould OS 245A/250/255/300/3000/3351/4000	from £125
Hameg 203/203-5 - 20MHz - Dual Channel	from £150
Hewlett Packard 180A/180C/181A/182C	from £200
Hewlett Packard 1740A, 1741A, 17744A, 100MHz dual ch	from £350
Hewlett Packard 54100D - 1GHz Digitizing	£2995
Hewlett Packard 54501A - 100MHz - Digitizing 4 channel	£1750
Hewlett Packard 54602A - 150MHz - 4 channel	£1750
Hitachi V650F - 60 MHz Dual Channel	£350
Hitachi VC6265 - 100 MHz Digital Storage (AS NEW) GPIB	£2250
Hitachi V152F/V302B/V302F/V353F/V550B/V650F	from £125
Intron 2020 - 20 MHz Digital Storage (NEW)	£650
Iwatsu SS 5710/SS 5702 - 20MHz	from £125
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace	£475
Kikusui 5100 - 100MHz - Dual Channel	£350
Meguro - MSO 1270A - 20 MHz Digital Storage (NEW)	£550
National VP5703A - 100MHz - Digital Storage	£750
Nicolet 310 - L.F. D.S.O. with twin Disc Drive	£550
Nicolet 3091 - L.F. D.S.O.	£900
Panasonic VP5741A - 100 MHz D.S.O. with Digital readout - waveform analysis - TV Signal Analysis Function - G.P.I.B.	£1995
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3243/PM 3244/PM 3261/PM 3262/PM 3263/PM 3540	from £125
Philips PM 3295A - 400MHz Dual Channel	£1750
Scopex 14D-15 - 15MHz - Dual Channel	£100
Tektronix 434 - 25MHz - 2 Channel. Analogue Storage	£250
Tektronix 454 - 150MHz - 2 Channel	£400
Tektronix 468 - 100MHz - D.S.O.	£750
Tektronix 2213 - 60MHz Dual Channel	£425
Tektronix 2215 60MHz dual trace	£450
Tektronix 2235 - 100MHz Dual trace	£800
Tektronix 2236 - 100MHz Dual Channel with Counter/Timer	£995
Tektronix 2335 Dual trace 100MHz (portable)	£750
Tektronix 2445 150 MHz - 4 Channel	£1250
Tektronix 2445A - 150MHz - 4 Channel	£1650
Tektronix 2465 - 350MHz - 4 channels	£2500
Tektronix 2225 - 50MHz dual ch	£450
Tektronix 455 - 50MHz Dual Channel	£350
Tektronix 464/466 - 100MHz An storage	from £350
Tektronix 465/465B - 100MHz dual ch	from £350
Tektronix 475/475A - 200MHz/250MHz Dual Channel	from £475
Tektronix 485 - 350MHz - 2 channel	£900
Tektronix 5403 - 60MHz - 2 or 4 Channel	from £250
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7904 - 500MHz	from £850
Tektronix 7934 500MHz with storage	from £1000
Trio CS-1022 - 20MHz - Dual Channel	£125

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20 MHz DUAL TRACE	£180
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY	£200

SPECTRUM ANALYSERS

Advantest 4131 - 10KHz - 3.5GHz (G.P.I.B)	£5000
Ando AC8211 - Spectrum Analyser 1.7GHz	£3000
Easton/Ailtech 757 - 10KHz - 22 GHz	£2750
Hewlett Packard 3580A - 5Hz-50KHz	£995
Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (As New)	£5750
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000
Hewlett Packard 3585A - 40MHz Spectrum Analyser	£5000
Hewlett Packard 141T + 8552B + 8555A - (10MHz - 18GHz)	£1600
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£7500
Hewlett Packard 8505A - Network Analyser 500KHz - 1300MHz	£3500
Hewlett Packard 853A + 8558B - 0.1 to 1500MHz	£3250
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz	£2750
Hewlett Packard 8565A - 0.01-22GHz	£3750
Hewlett Packard 8754A - Network Analyser 4-1300MHz	£2500
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30KHz - 200MHz	£1250
Meguro MSA 4901 - 1-300 GHz (AS NEW)	£1995
Meguro MSA 4912 - 1-1 GHz (AS NEW)	£3000
Polarad 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£2500
Takeda Riken 4132 - 1.0GHz Spectrum Analyser	£2750
Tektronix 7L18 with 7603 mainframe (1.5-60GHz with external mixers)	£2000

MISCELLANEOUS

Adret 740A - 100KHz-1120MHz Synthesised Signal Generator	£2000
ANRITSU ME 462B DF3 Transmission Analyser	£3000
Denbridge JP30A - 30KV Insulation Tester	£1500
Anritsu MG642A Pulse Pattern Generator	£1500
Dranzet 626 - AC/DC - Multifunction Analyser	£850
EIP 331 - Frequency counter 18GHz	£700
Farnell AP70-30 Power Supply (0-70V/30A) Auto Ranging	£750
Farnell TSV 70 Mkl Power Supply (70V-5A or 35V-10A)	£200
Farnell DSG-1 - Synthesised Signal Generator	£125
Flure 5100A - Calibrator	£2500
Flure 5101B - Calibrator with Tape Deck	£4000
Flure 5100B - Calibrator	£3500
Guilidine 9152 - T12 Battery Standard Cell	£550
Helden 1107 - 30V-10A Programmable Power Supply (IEEE)	£650
Hewlett Packard 331A - Distortion Analyser	£300
Hewlett Packard 333A - Distortion Analyser	£300
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz-21MHz)	£1000
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3456A Digital voltmeter	£850
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£2250
Hewlett Packard 3775A - PCM Terminal Test Set	£900
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	£650
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 339A - Distortion Measuring Set	£1500
Hewlett Packard 3455A 61/2 Digit M/Meter (Autocal)	£750
Hewlett Packard 3478A - Multimeter (5 1/2 Digit) + HP-1B	£550
Hewlett Packard 3776A - PCM Terminal Test Set	£P.O.A.
Hewlett Packard 3779A/3779C - Primary Mux Analyser	from £800
Hewlett Packard 436A + Sensor	from £1000
Hewlett Packard 4375A - LCR Meter (Multi Frequency)	£3950
Hewlett Packard 4338A - Millinometer (As New)	£2000


Hewlett Packard 4342A - 'Q' Meter	£995
Hewlett Packard 4952A - Protocol Analyser (with interfaces)	£2500
Hewlett Packard 4953A - Protocol Analyser	£2750
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4271B - L.C.R. Meter (Digital)	£900
Hewlett Packard 4279A - 1MHz, C-V Meter	£6500
Hewlett Packard 4948A - (TIMS) Transmission Impairment M/Set	£2000
Hewlett Packard 4972A - Lan Protocol Analyser	£2000
Hewlett Packard 5420A Digital Signal Analyser	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	£600
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5183 - Waveform Recorder	£2250
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter	£450
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005	£995
Hewlett Packard 6034 - 60V-10A System Power Supply	£1500
Hewlett Packard 6253A Power Supply 20V-3A Twin	£200
Hewlett Packard 6181C D.C. current source	£150
Hewlett Packard 6255A Power Supply 40V - 1.5A Twin	£200
Hewlett Packard 6266B Power Supply 40V-5A	£220
Hewlett Packard 6271B Power Supply 60V-3A	£225
Hewlett Packard 6034A - 0-60V-10A System P.S.U.	£1500
Hewlett Packard 7475A - 6 Pen Plotter	£250
Hewlett Packard 7550A - 8 Pen Plotter A3/A4	£450

HEWLETT PACKARD 6261B

Power Supply 20v-50A £450 Discount for Quantities

Hewlett Packard 8349B - Microwave Broad Band Amplifier	£3500
Hewlett Packard 83555A - Millimeter - Wave Source Module 33-50GHz	£4250
Hewlett Packard 8015A - 50MHz Pulse Generator	£750
Hewlett Packard 8403A - Modulator	£500
Hewlett Packard 8405A - Vector Voltmeter	£500
Hewlett Packard 8165A - 50 MHz Programmable Signal Source	£1650
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various Plug-Ins available) extra	£2650
Hewlett Packard 8152A - Optical Average Power Meter	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£650
Hewlett Packard 83554A - Wave Source Module 25.5 in 40 GHz	£3500
Hewlett Packard 8620C Sweep oscillator mainframe	£400
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen	£2750
Hewlett Packard 8620C Sweep oscillator mainframe	from £250
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz)	£2600
Hewlett Packard 8958A - Cellular Radio Interface	£4000
Hewlett Packard 8901A - Modulation Analyser	£3400
Hewlett Packard P382A Variable Attenuator	£250
Hewlett Packard 1630D - Logic Analyser (43 Channels)	£650
Hewlett Packard 16500A - Fitted with 16510A/16515A/16530A/16531A - Logic Analyser	£4000
Hewlett Packard 11729B - Carrier Noise Test Set	£2000
Krohn-Hite 2200 Lin/Log Sweep Generator	£995
Krohn-Hite 4024A Oscillator	£250
Krohn-Hite 5200 Sweep, Function Generator	£350
Krohn-Hite 6500 Phase Meter	£250
Marconi 2019 - 80KHz-1040MHz Synthesised Sig. Gen	£1850
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£1950
Marconi 2022A - 10KHz-10GHz AM/FM Signal Generator	£2000
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2610 - True RMS Voltmeter	£500
Marconi 2871 Data Comms Analyser	£2000
Philips PM 5167 10MHz function gen	£400
Philips 5190 L.F. Synthesiser (G.P.I.B.)	£800
Philips PM5519 - TV Pattern Generator	£350
Philips PM5667 - Vectorscope	£500
Philips PM6652 - 1.5GHz Programmable High Resolution Timer/Counter	£900
Philips PM6670 - 120MHz High Resolution Universal Counter	£350
Philips PM6673 - 120MHz High Resolution Universal Counter	£350
Prima 4000 - 6 1/2 Digit Multimeter (NEW)	£450
Racal 1392 - 1.3GHz Frequency Counter	£800
Racal Dana 9081/9082 Synth. sig. gen. 520MHz	from £500
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9303 R/F Level Meter & Head	£650
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9302A R/F millivoltmeter (new version)	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz)	£500
Racal 9085 Low Distortion Oscillator	£POA
Racal 9301A - True RMS R/F Millivoltmeter	£300
Racal 9921 - 3GHz Frequency Counter	£450
Rohde & Schwarz AMF 2 - TV Demodulator	£1100
Rohde & Schwarz LFM 2 - 60 MHz Group Delay Sweep Gen	£1600
Rohde & Schwarz SMFP2 - 1GHz Radio Comms T/Set	£2500
Rohde & Schwarz UPSF 2 - Video Noise Meter	£1400
Rohde & Schwarz URE - RMS Voltmeter (10Hz-25MHz)	£500
Rohde & Schwarz - Scud Radio Code Test Set	£300
Rohde & Schwarz SUF 2 Noise Generator	£300
Rohde & Schwarz UPGS - Psophometer	£150
Rohde & Schwarz SMDU - 15Hz to 525MHz Signal Gen (FM & AM)	£500
Schaffner NSG 203A Line Voltage Variation Simulator	£950
Schaffner NSG 222A Interference Generator	£850
Schaffner NSG 223 Interference Generator	£850
Schaffner WSG 431 Electrostatic Discharge Simulator	£1250
Schlumberger 4923 Radio Code Test Set	£950
Schlumberger 4031 - 1GHz Radio Comms Test Set	£7000
Schlumberger 2720 1250 MHz Frequency Counter	£500
Schlumberger 70607/065/7075 Multimeters	from £350
Solartron 1250 - Freq. Response Analyser	£2500
Stanford Research DS 340 - 15 MHz Synthesised Function (NEW) and arbitrary waveform generator	£1200
Syston Donner 6030 - Microwave Frequency Counter (26.5 GHz)	£2500
Teletest CT71 Curve Tracer	£250
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen	£1750
Tektronix 1240 Logic Analyser	£750
Tektronix DAS9100 - Series Logic Analyser	£500
Tektronix - Plug-Ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more	£POA
Tektronix 577 Curve Tracer	£1150
Tektronix AM503 + T501 + PG502 - Current Probe Amplifier	£995
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope Calibrator	£1995
Tektronix AA5001 + TM 5006 M/F - Programmable Distortion Analyser	£2500
Tektronix 577 - Curve Tracer	£1150
Time 9811 Programmable Resistance	£600
Time 9814 Voltage Calibrator	£750
Toelner7720 - Programmable 10 MHz Function Gen (AS NEW)	£700
Valhalla Scientific - 2724 Programmable Resistance Standard	£P.O.A.
Wayne Kerr 3245 - Precision Inductance Analyser	£3250
Wayne Kerr 4210 - LCR Meter	£500
Wayne Kerr 4225 - LCR Bridge	£500
Wayne Kerr 6425 - Precision Component Analyser	£275
Wayne Kerr 8905 - Precision LCR Meter	£850
Wavetek 171 - Synthesised Function Generator	£250
Wavetek 172B Programmable Sig Source (0.0001Hz-13MHz)	£P.O.A.
Wavetek 184 - Sweep Generator - 5MHz	£250
Wavetek 3010 - 1 - 1GHz Signal Generator	£1250
Wiltron 6620S - Programmable Sweep Generator (3.6 - 6.5GMZ)	£650

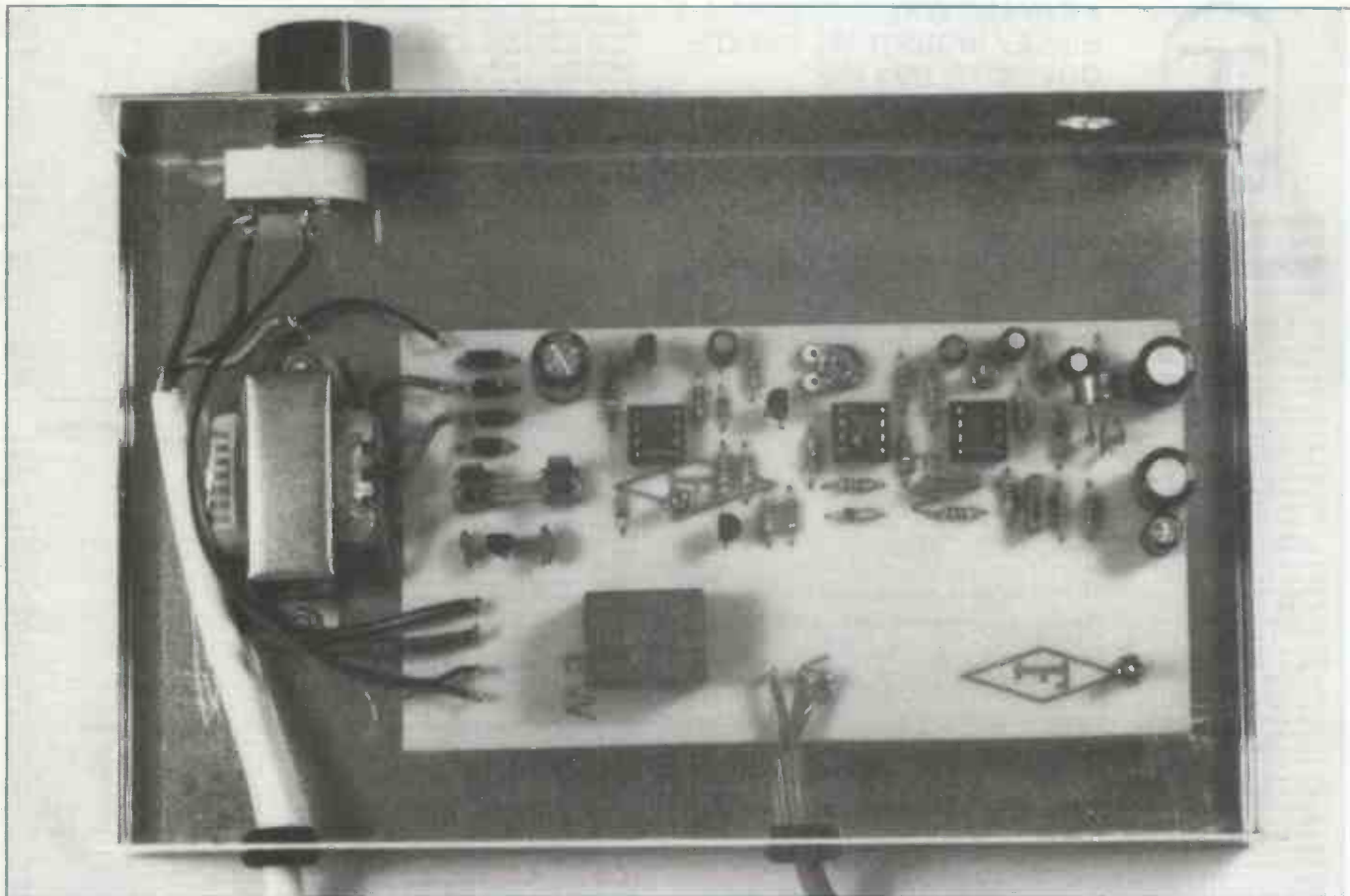**MANY MORE ITEMS AVAILABLE -
SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE
ORDERING - CARRIAGE & VAT TO BE ADDED
TO ALL GOODS**



mounted on the circuit board in the usual fashion. For optimum result it should be twisted slightly so that its window is precisely horizontal. The alternative approach is to have the printed circuit board mounted on the base panel of the case. The pyro sensor still "looks" through a window cut in the front panel of the case, but the sensor will obviously have to be mounted on perpendicular to the circuit board. Probably the easiest way of doing this is to first fit three solder pins to the board in place of the sensor. It should then be easy to fit the sensor on to the pins so that it is perpendicular to the board. Avoid touching the pyro sensor's window as this could reduce its sensitivity. If you should accidentally touch the window use a soft cloth to clean away any finger marks.

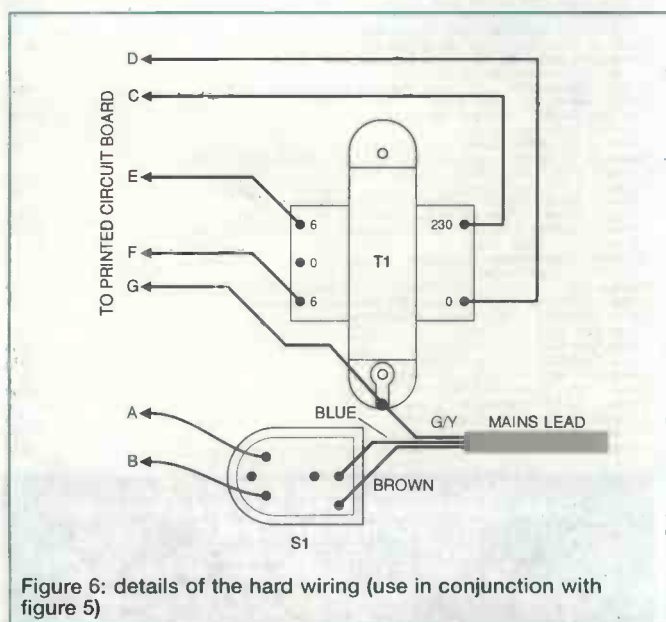


Figure 6: details of the hard wiring (use in conjunction with figure 5)

The fuse is mounted on the board via a pair of fuse-clips. The clips must be the type that has two pins, and not the single pin variety. C5 and C7 must be good quality electrolytic capacitors, or the biasing of the amplifier may be well off centre. Tantalum capacitors are ideal, but good quality electrolytic capacitors should suffice. In other respects construction of the printed circuit board is perfectly straightforward, but be careful to fit the diodes and rectifiers the right way round as mistakes here could cause damage to some of the components. Fit single sided solder-pins to the board at the points where connections will be made to the mains transformer, etc.

As this project connects to the dangerous mains supply it is essential that it is housed in a metal case that is reliably earthed to the mains earth lead. The case must also be a type which has a screw fitting lid or cover, and not one that has a clip-on lid that provides easy access to the mains wiring. Although it is not particularly complex, this project is definitely not suitable for beginners and it should only be undertaken by those who have the necessary experience. The general layout used is not overly important, but it is advisable to have on/off switch S1 and mains transformer T1 situated as far away from the pyro sensor as possible. A solder-tag fitted on one of the mains transformer's mounting bolts provides a chassis connection point. As some tracks of the printed circuit board carry the mains supply it is essential that the board is mounted securely. It is also essential that it is held about 10 millimetres or more clear of the case. Plastic stand-offs can be used, but I prefer 6BA or metric M3 screws plus spacers for boards that carry the mains supply.

The size of the window for the pyro sensor is not critical, but in theory a small hole gives longer operating range, and a larger hole produces shorter range with a wider angle of

From the Microcontroller Professionals:

Program PIC Microcontrollers:

We now have 3 programmers for PIC's !

Original - This is our original programmer for 16C5X, 16C55X, 16C6X, 16C7x, 16C8x, 16F8X devices.

Price : £40 for the kit, or £50 ready built.

Serial - This programmer programs the newest PIC devices in a single 40 pin multi-width ZIF socket. Will program: 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14000. Also In-Circuit programming.

Price : £40 for the kit, or £50 ready built.

Introductory - This programmer is intended for the smaller user, or newcomer to PIC's. Will program 8 pin and 18 pin devices : 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508, and 12C509.

Price £22 for the kit (not available ready built).

Note : All our programmers operate on a PC, using a standard RS232 serial interface (COM1, 2, 3, or 4). No hard to handle parallel cable swapping ! All programmers are supplied with full instructions, Windows programming software, MPASM, MPSIM and PICDE - the Windows based PIC assembler environment. (offers all features of PICDESIM below without the simulator).



Forest Electronic Developments

10 Holmhurst Avenue, Christchurch,
Dorset, BH23 5PQ. <http://www.ibmpcug.uk/~gmwarner/fed.htm>
01425-270191 (Voice/Fax)

PIC BASIC

FED's PIC BASIC products - straightforward, capable, powerful, rapid development.

In a Windows Development Environment our modules need no assembler or UV eraser to program your PIC's, and operate from a serial link to your PC.

The 16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I²C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external ram and all the standard 16C74 features.

Compiler - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and program your PIC chips directly.

16C57 Module Kit (8k EEPROM, 4MHz) £27.00, Pre-built £33.00
16C57 Module Kit (8k EEPROM, 10MHz) £31.00, Pre-built £37.00
16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00
16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00
16C84 chip programmed with BASIC - £25.00
Compiler - £60.00, or £50.00 when ordered with a module

Prices are inclusive, please add £3.00 for P&P and handling to each order.

Cheques/POs payable to Forest Electronic Developments, or phone with credit card details. Serial Cables - £7.50.



Windows Based PIC Development: PICDESIM - the Windows based development environment.

PICDESIM allows you to develop your PIC projects in one Windows program.

Incorporate multiple files, view help file information directly from the code, edit within the project, build, and track errors directly in the source, then simulate.

Simulator allows addressed, conditional and timed breakpoints, follow your code in the source editor window, set a breakpoint directly in the code. Run your program, or single step, or step over subroutines. Track variable values and trace them for display on the Trace Analyser. Input stimuli include clocks, direct values and asynchronous serial data. Profile your program - examine frequently called routines which are timed and use the information to optimise out bottle necks.

Trace Analyser allows any register or port value to be examined in analogue (graphical), waveform, or numeric values, check your program directly against your predicted waveforms.

Runs up to 50 times faster than MPSIM !

NEW ! - 32 bit version allows full use of Windows '95 and Windows NT 4.0 facilities.

Cost £30.00, or £25.00 for existing and new purchasers of any of our programmers. Please specify Windows 3.1, or Windows '95 (32 bit) versions of PICDESIM.

PIC's

PIC16C74/JW Erasable 20MHz	£24.00	PIC16C556 (14 bit versn 16C56)	£4.50
PIC16C74-04POTP 4MHz	£8.00	PIC16C74-20P OTP 20MHz	£11.00
PIC16C57-04POTP 4MHz	£5.00	PIC16C57-10P OTP 10MHz	£6.00
PIC16C84-04P 4MHz	£6.00	PIC16C84-10P 10MHz	£8.00
PIC16F84-04P 4MHz	£7.00	PIC12C508-04P OTP 4MHz	£2.20
PIC14000-04P OTP 4MHz	£10.00	PIC14000/JW Erasable	£23.00
PIC12C508-04P OTP 4MHz	£2.70	Ask about other chips!	

PIC Training

Our new training course introduces PIC's painlessly with a practical emphasis.

Our training package includes

- Full introductory manual to the PIC series including use of assembler, peripherals and interrupts for the 12 bit and 14 bit controllers.
- Video introducing the PIC, and showing use of PICDESIM
- Development board with PIC16F84, and all components required to develop 3 practical projects, including LED driving, handling delays and serial communications to a PC.
- PICDESIM - the Windows based Simulator (see left)
- Microchip MPSIM and MPASM programs

Training Course £80.00

Training Course with pre-built Introductory PIC programmer £99.00

Development Boards

Development boards allow simple prototyping of projects.

Our 18 pin development board includes a simple serial interface to a PC, 18 pin socket for any 18 pin device, 4MHz resonator and power regulator components. All instructions components, and circuits supplied. Includes a 16F84 - 10MHz version of 16C84 with an additional 32 bytes of RAM for programs.

Development board with all components for serial interface, power supply, oscillator and 16F84 device £20.00.

Coming soon...

Look out over the next few months as we expand our PIC BASIC range and extend our microcontroller support to another major manufacturer.

view. In practice small windows seem to give poor results, and it seems to be better to use a hole having a diameter of around 10 to 20 millimetres. Of course, if the sensor is mounted very close to the front panel, a much smaller hole will be required. It might be worthwhile making a large cut-out in the front panel, and pieces of card having apertures of various sizes can then be tried over the cut-out to determine the aperture which provides the best results in your particular set-up. Ideally some transparent material should be used to "glaze" the cut-out, but material that is transparent to visible light might not be transparent to long wavelength infra-red. It might be necessary to experiment a little in order to find a suitable window material. The lamp can be hard wired to the circuit board or connected to the unit via a mains socket mounted on the case. This depends on whether the lamp will always be used

with this unit or if it will sometimes be used on its own. The hard wiring method is used on the prototype and this is the more simple method to implement. It simply requires a hole for the mains output lead to the drilled in the rear panel of the case. A hole is also needed for the mains input lead. Both holes should be fitted with grommets to protect the leads.

Fitting a mains socket on the case is slightly awkward as a large and irregular cut-out is required. The shape of the cut-out must be determined by taking measurements from the socket itself. The cut-out can be produced using a miniature round file, Abrafile, fretsaw, etc. With this type of thing it is always advisable to cut just inside the perimeter of the required cut-out, and then enlarge the hole to precisely the required size and shape using a file. The fixing screws supplied with the sockets are unlikely to be of much use in this case and should be replaced with M3 bolts about 12 to 25 millimetres long. Together with a couple of M3 nuts these should enable the socket to be firmly fixed to the front panel. Details of the hard wiring are provided in figure 5, which should be used in conjunction with figure 4. This wiring is very simple indeed, but as the mains supply is involved it is essential to proceed with due care. Thoroughly checked the finished wiring for errors. A mains transformer having a single 12 volt secondary winding is required, but most modern mains transformers either have twin secondary windings or a centre-tapped winding. Probably the best choice is a transformer having a 6-0-6 volt secondary winding, with the centre-tap being left unused. The wiring diagram assumes that this type of transformer will be used.

It is possible for the mains transformer to heat up the air within the case, causing turbulence which will give spurious triggering. The easiest solution to this problem is to use some tissue paper or other wadding inside the case, between T1 and IC1, so that they are largely sealed off from one another. Make sure that the wadding does not block IC1's view.

Mains voltage is potentially dangerous. Constructors who are not experienced in fitting mains circuitry should seek the assistance of an experienced mains constructor.

Adjustment and use

The easiest way of giving VR1 a suitable setting is with the aid of a multimeter. First cover the sensor with (say) some Bostik Blue-Tack so that you can make measurements and adjust VR1 without activating the unit. After the circuit has had several seconds to settle down, measure the output voltage at pin 7 of IC2. Next monitor the voltage at pin 6 of IC3, and adjust VR1 to set it one volt higher than the voltage at pin 7 of IC2. If you do not have access to a multimeter, temporarily connect a resistor of about 27k in value across R19. This will shorten the hold-on time to only about one second. Trial and error can then be used to find a setting for VR1 that gives good freedom from spurious triggering.

When installing the unit, bear in mind that it is most sensitive to someone crossing the field of view, and least sensitive to someone moving directly towards or away from the unit. It is a matter of installing the unit where it will work effectively, and not simply mounting it on any wall or shelf that happens to be handy. There seems to be no major problem with optical feedback, but it would not be a good idea to have the unit aimed at the light it is controlling.

PARTS LIST for the IR Auto Light

Resistors (All 0.25 watt 5% carbon film)

R1,3,18	2k2 (3 off)
R2	18k
R4,5	100k (2 off)
R6,8	1M (2 off)
R7,9,13,14	6k8 (4 off)
R10,15,17,20	10k (4 off)
R11,21	3k9 (2 off)
R12	4k7
R16	27k
R19	1M5
VR1	10k min hor preset

Capacitors

C1	100u 16V radial elect
C2,3	1000u 16V radial elect
C4,5,7,9	10u 25V radial elect
C6,8	4n7 polyester, 7.5mm lead spacing
C10	1000u 25V radial elect
C11,12	100n ceramic

Semiconductors

IC1	PIS201S or similar pyro sensor
IC2	NE5532N
IC3	LM358N
IC4	CA3140E
IC5	uA78L12 12V 100mA positive regulator
Q1,3	BC549 (2 off)
Q2	BC559
D1,2	1N4148 (2 off)
D3,4,5,6	1N4002 (4 off)

Miscellaneous

RLA1	12 volt 300R or more coil resistance, single changeover contact rated at 230V ac and 1A or more (Maplin YX97F recommended)
FS1	20mm 100mA "quick-blow" fuse
T1	Standard mains primary, 12 volt 100mA secondary (or 6V - 0 - 6V 100mA secondary with centre-tap ignored)
S1	Rotary DPST mains on/off switch
Metal case about 203 x 127 x 51mm, printed circuit board, mains lead and plug fitted with 2A fuse, pair of 20mm fuse-clips, 8-pin DIL holder (3 off), control knob, wire, solder, etc.	

OSTIMAN ORK

ACORN ARCHIMEDES WORLD

13 issues

UK: WAS £48.75. NOW

£39.75. YOU SAVE £9.

Europe: £60.50, Overseas:

£62.50, USA: \$100.00



HAM RADIO TODAY

13 issues

UK: WAS £32.50. NOW

£29.00, YOU SAVE £3.50.

Europe: £39.50, Overseas:

£41.50, USA: \$66.00



E.L.

13 issues

UK: WAS £30.55. NOW

£27.00, YOU SAVE £3.55.

Europe: £40.00. Overseas:

£41.80, USA: \$64.00

Now this just has to be a good deal! Not only will you save a considerable amount of money, but your postman will also deliver the next 13 issues of your favourite electronics magazine directly to your door- with no fuss, no hassle, and no future price increases.

So go on, subscribe now, save your shoe leather, and up to 70p per issue.

Here's why YOU should subscribe to either ETI, Ham Radio Today or Acorn Archimedes World:

- ◆ FREE home delivery in the UK.
- ◆ A saving of up to £9 a year.
- ◆ Price protection- you won't pay any more if the cover price goes up.
- ◆ Guarantee receiving every issue.

This is one deal where you really can't lose.

REMEMBER, it's always cheaper to subscribe!

All savings are based upon buying the same number of issues from your newsagent. UK only.

SUBSCRIPTION ORDER FORM

YES, I would like to subscribe to (please tick):

☐ Acorn Archimedes World☐ Ham Radio Today☐ E.T.I.

for the next 13 issues (all subscriptions will start with the next available issue, unless extending).

The total value of my order is £.....I enclose a cheque/PO payable to 'Nexus Special Interests', or please debit my Access/Visa/Mastercard/AMEX account:

Card No: _____

Expiry...../.....

Signature.....

Your Details:

Name: Mr/Mrs/Miss Initial:.....Surname:.....

Address:

Post Code:

Tel no:.....

Please return, together with your payment, to: Nexus Subscriptions, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leics LE16 9EF

Offer closes: 31/7/97 Code: 0210

TO ORDER BY PHONE. PLEASE CALL OUR CREDIT CARD HOTLINE ON 01858-435344 (Mon to Fri, 9am - 5.30pm)

☐ Please tick this box if you do not wish to receive information from other companies

38 35

PIC Programmer *Re-Visited*

Robin Abbott has developed a more powerful and updated version of the popular ETI PIC programmer

In the June 1995 issue of Electronics Today International, I presented a PIC programmer which at the time was highly successful. It used a single PIC16C57 and a handful of other components to implement a programmer capable of programming all 12 and 14 bit core PICs in standard DIP packages which were available at the time. @B:Several hundred of these programmers have been built, either in the original form, or in kit form from Forest Electronics. The programmer was designed at the time to be as cheap as possible, and consequently it lacked certain advantages that might be available in a more sophisticated model. For instance:

18pin, 28pin and 40pin devices were all programmed in their own individual sockets, therefore a constructor requiring to use all 3 types of device would require 3 relatively expensive ZIF sockets for large scale programming. Although In-Circuit Programming (also known as In Service Programming (ISP)) was supported, PIC16C84 devices could not be erased in circuit as at the time Microchip had not published the serial programming specification for these devices.

At the time the programmer was designed to be expandable, and in fact many PIC devices released since the programmer was designed are able to be programmed, changing only the initialisation file used in the PC. However the newer 8 pin devices - the 12C508 and 12C509 cannot be programmed by the original programmer as they use a different algorithm from other devices in the series.

To overcome these disadvantages, and to bring the programmer up to date I have redesigned the original programmer to produce a new version with the following features:

- The programmer is now fitted with a single 40 pin multi-width ZIF socket which can accommodate the following PIC device types: 12C50X (8 pin), 16C55X (18 pin), 16C6x, 16C7x, 16C8X, 16F8X, and PIC14000 (with an adapter), in fact, all the current serially programmed 12 and 14 bit core PIC devices in packages with 40 pins or less.

- The programmer supports in-circuit programming of all serially programmed devices, including in-circuit erasure of the 16C8X series.

- The programmer is on a board approximately 2/3 the size of the original programmer.

- The new version is based itself around a PIC, either the 16C84, 16C56, 16C58, 15C556, or 16C558 PIC's may be used.



- The programmer operates on a serial link to a PC running either Windows 3.1 or Windows '95. I particularly dislike programmers (or indeed any peripherals) which use the parallel port, most PC's are only fitted with one parallel port and therefore need either a printer switch or an additional parallel card, parallel cables are also considerably more expensive, and are physically inflexible.

- The programmer supports standard HEX files produced by the Microchip MPASM assembler, or other assembler environments such as the FED PICDESIM assembler/simulator.

- The new programmer also switches Vdd to the chip being programmed (the original programmer always maintained Vdd).

- The programmer supports reading and programming of the eeprom data areas in those PICs which have an eeprom data area.

- The programmer supports Program Readable Identities (PRIDs). This allows the programmer to write a serial number to the program store in the PIC in the form of RETLW instructions which may be read by the application program. The serial number may be unique for each chip programmed with each application, or may be defined as the code checksum, or as a random number.

The only feature offered by the original programmer which is not provided in this version is support for programming in parallel mode. This mode is only used with the 16C5X series devices which are now becoming more expensive than more capable serially programmed devices, thus the 16C556 can be used as replacement for the 16C56 (with some minor code modifications), but has 4 times as much RAM as the 16C56, and is about 10% cheaper (at current UK distributor prices).




The instruction memory of the PIC is totally separate from the RAM area, and it is this that gives the PIC its tremendous speed in instruction execution. The next instruction may be fetched from the instruction memory at the same time as the current instruction is being executed, and all instructions (barring program jumps) are performed in 4 cycles of the external clock. This results in very fast code for which timed loop and real time software is extremely easy to program. The only disadvantage of the PIC architecture is that since the program area cannot be written from within the program then in-circuit emulators

The clock and data lines are used to serially address the chip. Commands are 6 bits and to perform any action the command is clocked into the chip, optionally followed by a

Table 1: PIC devices programmed

↑ SEE ETT AUG
VOL 25 NO 7 1997
P9

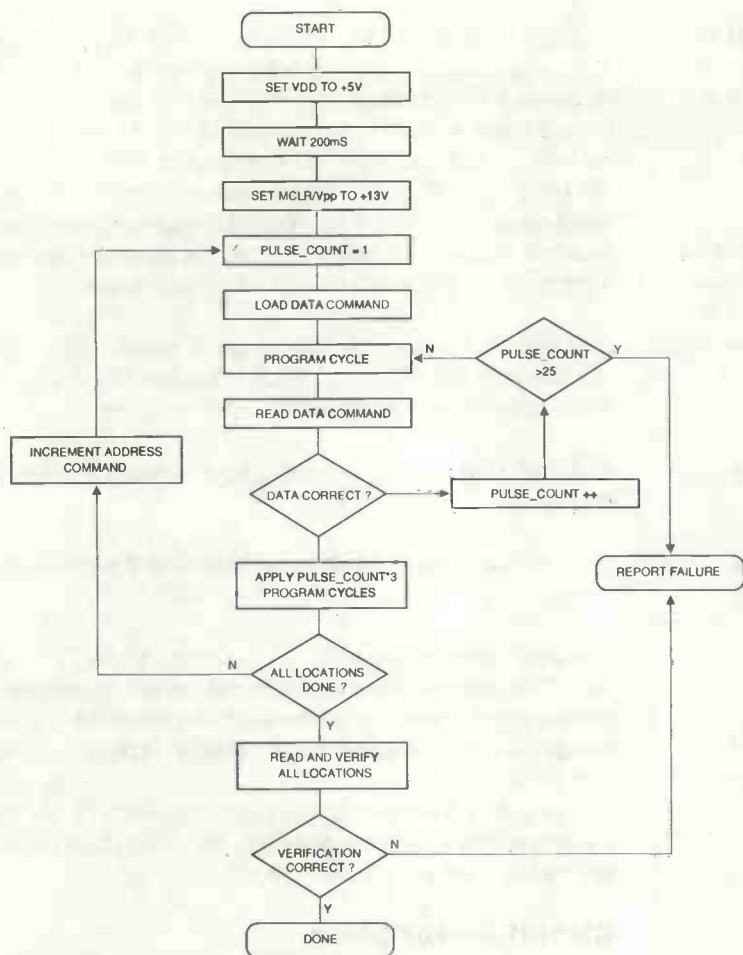

further 16 clocks which are used to clock data into or out of the chip to the 14 bit wide program store (The first and last clocks are unused). For example figure 1 shows the signals applied to a PIC to read the contents of location 0 in the program store.

There are 6 commands used to program the PIC. When Vpp is raised the address pointer is positioned to location 0. The load Data and Read Data input or read data for the current programming address respectively. Increment address moves the address location to the next address. The Begin and End programming commands start and end a programming pulse. Finally the load configuration command positions the address pointer at the configuration area (described below). The eeprom devices have additional commands to erase the eeprom device, and to program and read the eeprom data area.

The programming algorithm used is a fast program/verify/overprogram method, similar to fast algorithms used for standard eproms. Each location is programmed with a short pulse, and read to verify it. If the location fails then it is programmed again. When the location is correctly verified, then the location is programmed again with three times as many pulses as that required to program it in the first place. The algorithm is shown in figure 2.

Please note that the Microchip programming specification requires that the programming

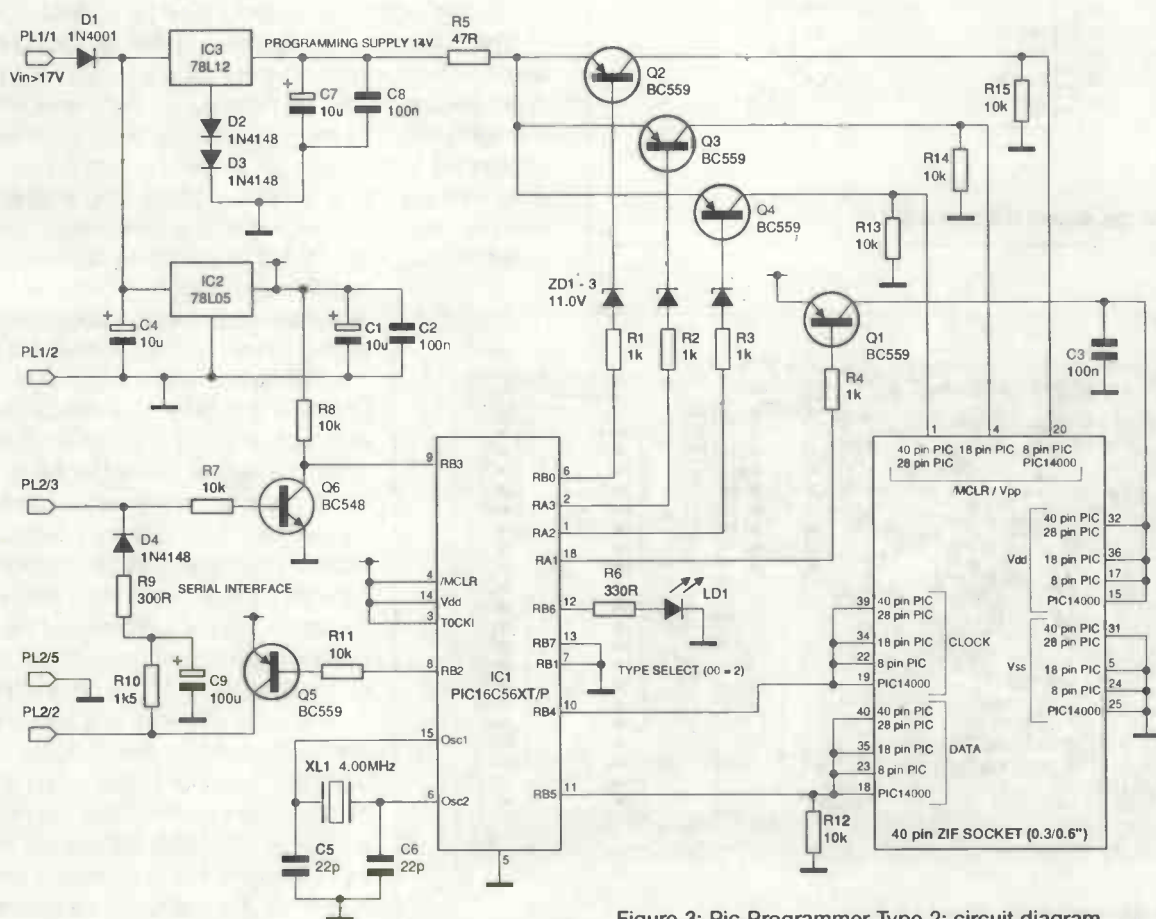


Figure 3: Pic Programmer Type 2: circuit diagram

should be performed at Vdd=5V, and verified at both 4V and 6V to ensure that the device has programmed correctly. This programmer only verifies at Vdd=5V, and therefore is classified by Microchip definition as a development programmer.

Configuration fuses

Each PIC device has a configuration fuse which defines its operation in the application circuit. Any PIC programmer must allow the configuration fuse values to be set. The configuration fuses allow the following device features to be set:

- 1. Oscillator type, as one of the following items:
LP - Low power crystal oscillator, for instance 32768 kHz
XT - Crystal Oscillator
RC - Resistor/capacitor based oscillator
HS - High speed crystal oscillator (more than 4MHz)

2. Code Protect (CP) bit. When set the CP bit forces the PIC, when read, to return a scrambled version of the code to prevent unauthorised copying. The PIC cannot be programmed in this state, however EEPROM versions may be erased. User words may be written or read when the CP bit is set. CAUTION - some devices (particularly the most recent PICs) have non-erasable code protect fuses, thus the expensive /JW variant may be rendered useless for further development once the CP fuse is set.

3. Brown Out Enable Bit. This is set to enable the brown out circuit in the PIC. This circuit holds the PIC in reset if the supply voltage drops below a pre-set level.

4. Watch Dog Enable. This bit is set to enable the watch dog timer.

5. Power up timer. This bit is set to enable the power up timer.

The user words may be set to any value as specified by the user. They may be used to define the version of software, or to provide a serial count for each individual chip. User words cannot be read by the application program running in the PIC.

The user words and configuration fuse may be set by the programmer PC host software, the dialog box used to set these is shown in screen shot 1.

Circuit Description

The circuit diagram is shown in figure 3.

The programming algorithm is implemented in IC1 - a PIC16C56, 16C556, or 16C84. This device also includes the serial interface software, and drives an LED which is illuminated when the subject PIC is being read or written.

The power supply requires a stable 5V supply for Vdd, and 13V for the programming supply Vpp. The 13V supply is obtained by a 78L12, boosted by two signal diodes in the earth return of the regulator (the output voltage is referenced to the earth pin of the regulator). The programming supply is applied to the chip through a 47R resistor - R5, and switched to any of 3 pins of the ZIF socket by Q2, Q3 or Q4. The switching of these transistors

is achieved through 11 V zener diodes - when the output of the controller PIC is high (+5V) the voltage differential between the PIC output and the transistor base is insufficient to bias the zener diode into conduction and the transistor is turned off, when the output is low the zener diode conducts and the transistor conducts. This type of circuit is necessary because the PIC outputs have static protection diodes forward conducting to Vdd, and without the zener the transistor would be permanently turned on by these diodes. Q1 switches +5V to the programmed PIC.

The serial interface is a cheap and simple 2 transistor circuit based around Q5 and Q6. The input of the circuit is driven by the output of the PC which in the idle state is at -12V. D4, R9 and C9 filter the input from the PC to provide a negative supply for the output of the interface which

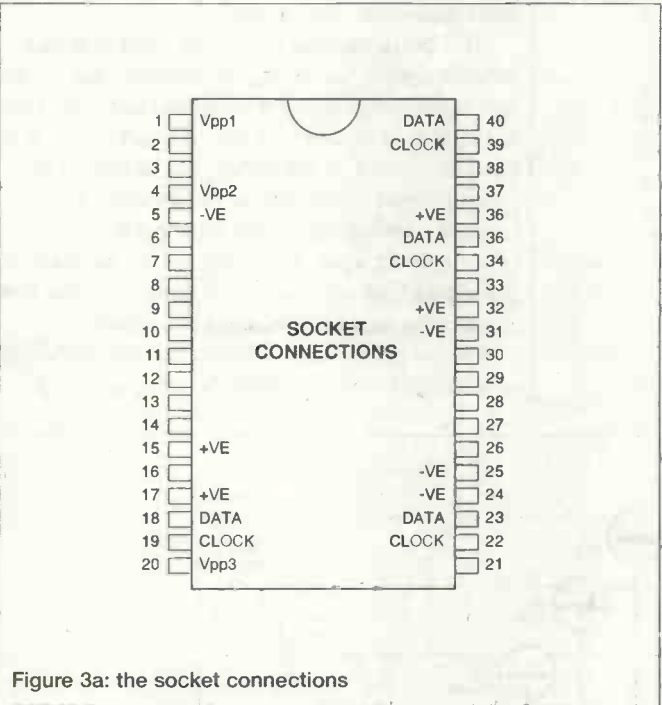


Figure 3a: the socket connections

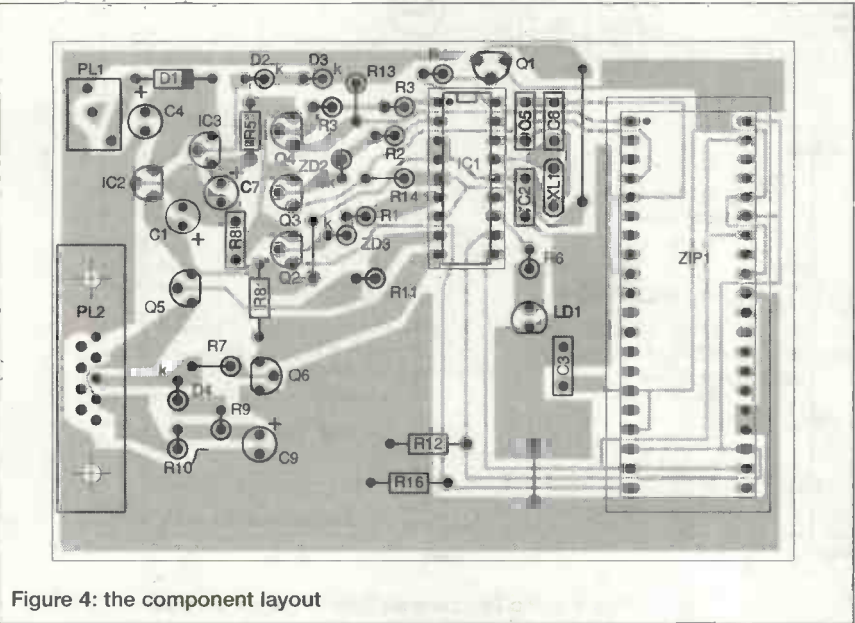


Figure 4: the component layout

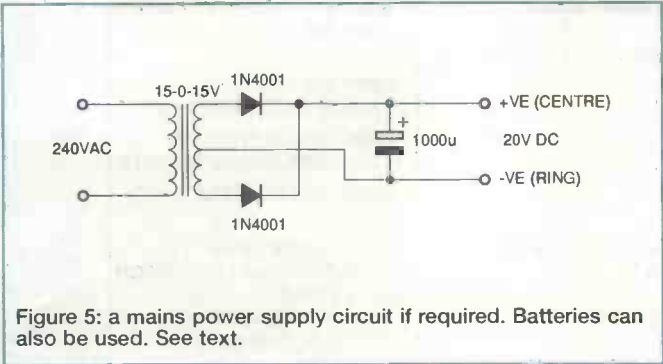


Figure 5: a mains power supply circuit if required. Batteries can also be used. See text.

PROGRAMMER	PC CONNECTOR TYPE:			
PL1	9 - WAY FEMALE	9 - WAY MALE	25 - WAY FEMALE	25 - WAY MALE
2	3	2	2	3
3	2	3	3	2
5	5	5	7	7

Figure 6: serial cable connections from the programmer to the host PC

is required to swing between -1V and +1V for the input of the PC. This circuit has proved to operate very well in practice, however on a very small number of PC's the input impedance is too low, and R10 may be reduced to 1k, or lower.

There are five different PIC pin-outs driven by this circuit. 18 pin devices, 28 pin devices and 40 pin devices are all programmed in the top of the ZIF socket. 8 pin devices and the PIC14000 are programmed in the bottom of the socket (The PIC14000 requires an adapter - see later section). Figure 3a shows the socket positions for the various devices programmed.

The two pins RB6 and RB7 are connected to ground to indicate to the controller PIC the type of programmer that is in use, this is because the same software load is actually used for a number of different programmer types.

Construction and test

Figure 4 shows the PCB overlay. Construction is straightforward, there being no special components or assembly required.

There are three links which should be fitted to the board first. Follow with the horizontally mounted resistors, D1, and then the IC sockets. The 40 pin ZIF socket should be fitted into an IC socket. Mount (in order) the vertical resistors, diodes, and capacitors, and finally the sockets and other components.

Once construction is complete the board may be tested. Do not fit IC1 at this stage.

The power supply required is 17V or greater. In practice power consumption of the programmer is so low that two 9V batteries may be used as a supply, or a 12V battery eliminator (they usually have an off load voltage in excess of 20).

Figure 5 shows the circuit diagram of a suitable mains power supply. If using a mains power supply, inexperienced mains constructors should ask for assistance from someone with mains experience.

Connect power to the circuit and check that the power supply on pins 5 and 14 of the socket for IC1 is +5V. Check that the power supply on the emitter of TR2 is about 13V, finally check that there is no significant voltage on any pin of the ZIF socket. Disconnect power and insert IC1, reconnect power, and the LED should flash five times which is a power up check implemented in the PIC.

The cable connection between the programmer and the PC is three-wire. Figure 6 shows the cable connections required for a self built cable, however any standard PC cable may be purchased. The programmer software will operate on any of the serial ports on a standard PC.

If you have a terminal emulator then set up your terminal emulator to the correct port which you are using for the programmer. Set the emulator to run 9600bps, no parity, no flow control, 8 bits, one stop bit. In Windows terminal this is the menu option under Settings / I Communications. Enter a capital D, the programmer should respond with 'L' which is the 'OK' report from the programmer. Enter an 'F' character and LD1 should illuminate. Enter 'K' and LD1 will go out. Finally check that all the pins on the ZIF socket are close to 0V.

Now install and run the host software to check the programmer with some real devices. Initial programming for all device types should be performed with erasable devices in case of problems with the construction.

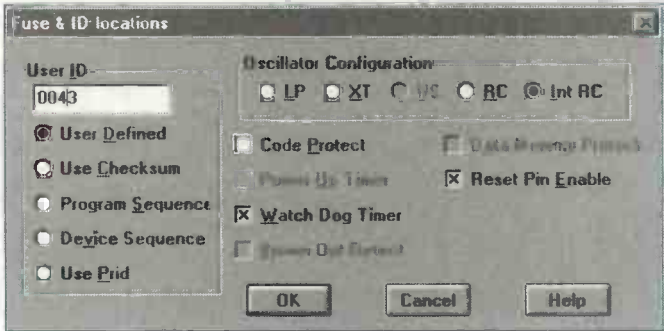


Figure 7: screen shot sample from the software

PC host software

The host software is installed by from Windows 3.1 or Windows '95 by running the program "INSTALL.EXE" on the supplied disk. This is achieved from Windows Program Manager by selecting the File, Run menu option, and then typing A:\INSTALL.EXE in the command line edit box. In Windows '95 use the start button then the run option and type A:\INSTALL.EXE in to the box. The software may be installed in any directory on your hard disk, but defaults to installation in a directory called "C:\PICPROG". Once installed then double click the icon called PICPROG to start the program. Figure 7 shows a screen shot of the PC program when running.

Once running the Options I Communications menu option may be used to connect to the programmer. The programmer software is supplied with a guide to its use, and with help files.

Programmer interface specification

For those users who wish to produce their own host software for the programmer this section defines the protocol used for the serial interface to the programmer.

COMMAND LETTER	FUNCTION	INPUT DATA	RETURNED DATA
A	SET MODE	SINGLE BYTE MODE DATA - SEE TEXT	ACKNOWLEDGEMENT BYTE
B	READ ENTIRE PIC	NONE	SIZE* WORDS + ACKNOWLEDGEMENT BYTE
C	READ CONFIGURATION WORD	NONE	CONFIGURATION WORD + ACKNOWLEDGEMENT BYTE
D	CHECK PROGRAMMER	NONE	ACKNOWLEDGEMENT BYTE - 'L'
E	PROGRAM 4 WORDS AT THE CURRENT LOCATION, MOVE THE CURRENT LOCATION ONWARD 4 WORDS	4 WORDS + SINGLE BYTE CHECKSUM	SINGLE BYTE COUNT OF OVERPROGRAM PULSES FOR ALL 8 WORDS + ACKNOWLEDGEMENT BYTE 'F' IF PROGRAM FAILED
F	ENTER PROGRAMMING MODE, SET CURRENT LOCATION TO 0	NONE	ACKNOWLEDGEMENT BYTE
G	PROGRAM USER WORDS	4 WORDS + SINGLE BYTE CHECKSUM	ACKNOWLEDGEMENT BYTE
H	CHECKSUM ENTIRE PIC AND CONFIGURATION WORD, EXCLUDES USER WORDS	NONE	16 BIT CHECKSUM IN LOW-HIGH FORMAT +ACKNOWLEDGEMENT BYTE
I	SET PIC PROGRAM OR EEPROM DATA SIZE	SIZE OF PROGRAM AREA IN LOW-HIGH FORMAT. LOW BYTE MUST ALWAYS BE ZERO EXCEPT FOR EEPROM DATA AREA WHEN LOW AND HIGH BYTES MUST BE IDENTICAL AND SET TO THE 8 BIT SIZE OF THE EEPROM	ACKNOWLEDGEMENT BYTE
J	READ USER WORDS	NONE	4 USER WORDS + ACKNOWLEDGEMENT BYTE
K	LEAVE PROGRAMMING MODE	NONE	ACKNOWLEDGEMENT BYTE
L	PROGRAM CONFIGURATION FUSES	SINGLE CONFIGURATION WORD + SINGLE BYTE CHECKSUM	ACKNOWLEDGEMENT BYTE
M	INCREMENT PROGRAM LOCATION (ONLY NEEDED TO STEP PAST CONFIGURATION IN PARALLEL DEVICES WHEN PROGRAMMING DATA - SEE TEXT)	NONE	ACKNOWLEDGEMENT BYTE
N	BLANK CHECK PIC	NONE	RETURN 'L' IF THE PIC IS BLANK, 'F' IF IT IS NOT BLANK
O	BULK ERASE EEPROM DEVICE PROGRAM AND DATA	NONE	ACKNOWLEDGEMENT BYTE
P	READ EEPROM DATA	NONE	SIZE* WORDS + ACKNOWLEDGEMENT BYTE
Q	PROGRAM 4 BYTES AT THE CURRENT EEPROM DATA LOCATION, MOVE THE CURRENT LOCATION ONWARD 8 BYTES	4 BYTES SENT AS WORDS IN PIC PARALLEL FORMAT, FOLLOWED BY A SINGLE BYTE CHECKSUM	ACKNOWLEDGEMENT BYTE

* SIZE IS PROGRAMMED BY THE SETSIZE COMMAND ('I')

Figure 8: table of commands and responses used by the programmer

Please note that the interface for this programmer is different to the original project, the programmers may be differentiated in host software by sending a D character to the programmer, the original programmer will respond with a 'K', this programmer will respond with an 'L'.

Communication to the programmer relies on a command/acknowledgement protocol driven by the host machine. Commands are given as a letter from 'A' to 'Q', and any bytes required by the command follow the command letter. The programmer responds with any bytes to be sent as a result of the command followed by an acknowledgement byte. The acknowledgement byte is either an 'L' or an 'F'. 'L' indicates the command was successfully obeyed, 'F' indicates that an error occurred such as a checksum failure on data sent to the programmer. Commands may take up to 100ms before the acknowledgement byte is returned, and if this time expires

then an error may assume to have occurred, the time-out in the prototype was set to 1s.

To initialise the programmer from any state then this sequence should be followed: Send 'D' 18 times, wait 1S and discard any bytes returned from the programmer. Send 'K' and wait for the acknowledgement - 'L', the programmer is now guaranteed to be in a waiting state. This sequence needs to be followed only at the beginning of an application program.

Figure 8 shows the list of commands which can be sent to the programmer, and the expected responses. The following paragraphs describe commands in more detail.

The Set mode command ('A') and the Size command ('I') should be sent before any other command is sent to the programmer. These set the type of PIC and the size of the program area. The Set mode command ('A') is followed by a single byte. The bits of this byte are as follows:

- Bit 0 - Set if the configuration register is being programmed
- Bit 1 - Set for an eepromdevice (10ms program pulses)
- Bit 2 - Set if Vpp is to be applied to pin 1 of the ZIF socket
- Bit 3 - Set if Vpp is to be applied to pin 4 of the ZIF socket
- Bit 4 - Set if Vpp is to be applied to pin 20 of the ZIF socket
- Bit 5 - Set if the device contains a 12 bit core

For example the PIC16C84 has the mode command definition value 10 decimal, the PIC16C74 has the value 4, and the PIC12C508 has the value 48 decimal.

All data words written to the programmer for programming (commands 'E', 'G', and 'L') are in PIC parallel format sent as the low byte followed by the high byte. This format has the upper 8 bits of the word in the upper byte, and the lower bits in the lower byte which should be padded with 0s. Thus the hex word "1EC7" for a 14 bit device is written to the programmer as the byte "07" followed by the byte "7B". Regardless of the number of words written to the programmer they are always followed by a single byte checksum which is the 8 bit sum of the data words. If the checksum fails then the programmer will return 'F'. 12 bit core devices are written in the same 14 bit format, however the two most significant bits are always set to 0.

All data read from the programmer in response to the 'B', 'C' or 'J' commands is in the PIC parallel format as for data written, but there is no checksum. All other 8 bit data is returned as a single byte. 16 bit data is returned in the normal low byte followed by high byte format.

To program data locations the Enter Program command ('F') is given. This sets the program counter to address 0. Now 4 words can be programmed at a time using the Program Data command ('E'). Each command returns the overprogram count (a single byte) followed by the acknowledgement. The overprogram count is the total number of pulses required to initially program the 4 words. Thus if the first three words all required one pulse to initially program the word, and the fourth word required 2 initial pulses, then the overprogram count returned will be 5. After each word is programmed the internal counter is incremented ready to write the next 4 words. After the entire program area is written then the End Programming command ('K') is given. Note that for 12 bit core devices the first word after the Enter Program command is the configuration fuse.

In similar fashion the user words may be programmed by sending the Enter Program ('F') command followed by the Program ID locations command ('G'), followed by the End Programming command ('K').

The user words are programmed by sending the Enter Program ('F') command followed by increment address commands to take the program counter to the correct address (2007 Hex) and then the Program configuration fuse command ('L'), followed by the End Programming command ('K'). Note if the Code Protect fuse is set to 0 (entering protect mode) then the program command may fail due to the inability to read back the correctly programmed value. Fuses must always be programmed after the program and user words.

The User configuration fuses are programmed by sending the Enter Program ('F') command followed by (7) increment address commands ('M') to take the program counter to the correct address (2007 Hex) and then the Program configuration fuse command ('L'), followed by the End Programming command ('K'). Note if the Code Protect fuse is set to 0 (entering protect mode) then the program command may fail due to the inability to read back the correctly programmed value. Fuses must always be programmed after the program and user words.

Data eeprom is written in the same way as program eeprom, using the F, Q and K commands. Note that data sent for data eeprom is still be sent and received as 8 words in PIC parallel format even though only 8 bit bytes are being sent. Thus the byte "FF" is sent as the byte "3F" followed by the byte "03". Note for reading and programming data eeprom the size command must be used to send the size of the eeprom data area, and not the program area. Also there is no check of eeprom data after it has been written - use the read command to verify it.

In-service programming

The in service programming facility requires a header to be constructed to connect the programmer to the device in the circuit. Figure 3 should be consulted to determine the connections from the ZIF socket to be used for each PIC type. For example to program the 16C84 in circuit, requires pins 4,5 and 35 to 37 of the ZIF socket to be wired to pins 4,5,13,14 and 15 of the 16C84 in the application circuit respectively. Use the shortest wires possible.

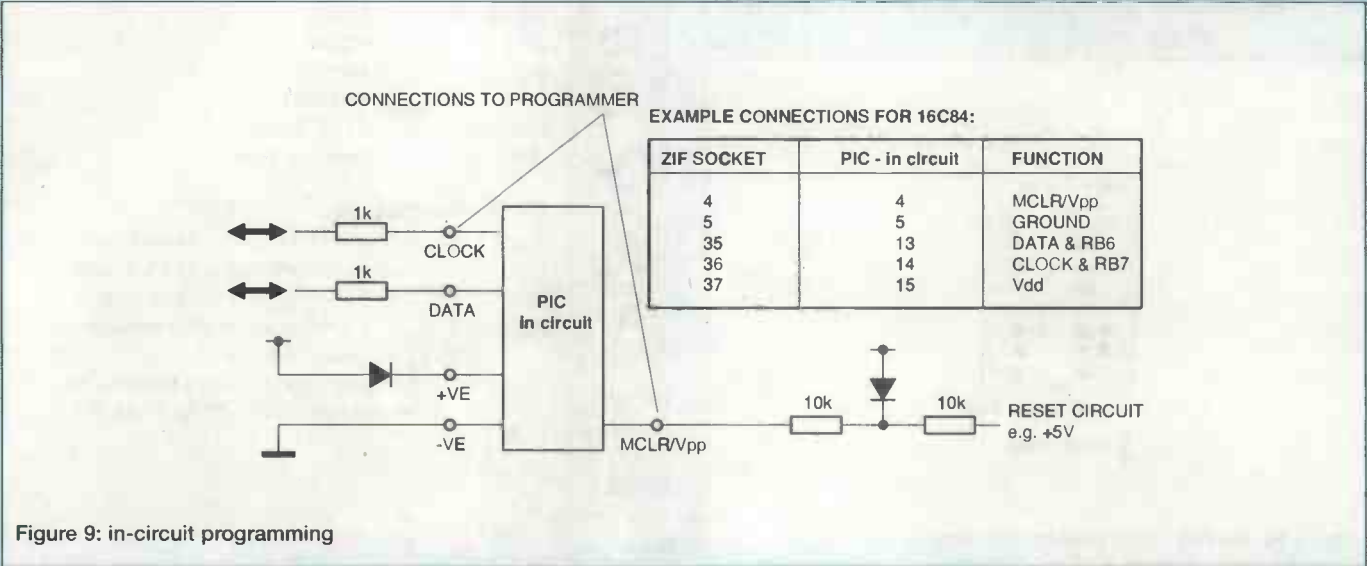


Figure 9 shows the wiring of the chip in circuit and the connections to the programmer. The clock and data pins of the PIC (which are usually port pins on the PIC) should be decoupled from the application circuit by 1k or greater resistors, if they can be left unused in the application so much the better. The power supply to the PIC in circuit is shown as an isolated supply by a diode, however if the application circuit can be powered then this connection is not required, however care is required in this case to check that no side effects will be generated by the PIC being programmed (all I/O pins in high impedance state, and programming waveforms on the clock and data pins). The MCLR/Vpp connection must be carefully handled to avoid the programming voltage being applied to other points in the application circuit.

PIC 14000

A special adapter is required for the PIC14000, this can be constructed on a small piece of Vero board. This is shown in figure 10. The adapter uses a 14 pin DIL socket, and 5 wire wrap pins. The adapter is inserted in the very bottom of the ZIF socket, and the PIC14000 inserted in the DIL socket so that pin 1 of the 14000 is towards pin 1 of the ZIF socket, only pins 8 to 21 of the PIC14000 are inserted in the DIL socket.

Finding out about PICs

The PIC data book is available from Maplin, or information may be downloaded from the internet at the Microchip Web Site: see <http://www.microchip2.com/products/micros> which allows all the datasheets to be downloaded. There are a number of good introductory texts on the PIC, for example "A beginner's guide to the Microchip PIC" from Maplin - Code AD31.

PIC-based Basic control systems including compilers are available from Parallax, or from Forest Electronics. This type of system allows rapid prototyping in BASIC, and then the program may be compiled, or re-written in assembler.

Obtaining components

The ZIF socket is available from Farnell on 0113-263-6311, their order code is 178-238. Farnell are quite prepared to sell to individuals for home or work use.

The author is prepared to supply programmed PICs for the project as well as to supply host software. The software supplied includes the Microchip assembler and simulator, the Windows based development environment PICDE, and

a data sheet for the 16C84 in Acrobat format is also supplied. The host software is supplied on 3.5in High Density floppy disk suitable for use with Microsoft Windows version 3.1 or 3.11 and Windows '95. To receive the programmed PIC and the software send an SAE and a cheque for £20.00 to **Robin Abbott, 37 Plantation Drive, Christchurch, Dorset, BH23 5SG**. The author is also happy to answer any queries on the use of the programmer, but please put them in writing.

A complete kit of parts including PCB, PIC and ZIF socket is available from Forest Electronics for £40.00+£3.00 P&P, 10 Holmhurst Avenue, Christchurch, Dorset. BH23 5PQ. 01425-270191. Please DO NOT direct any technical queries regarding this article to Forest Electronics, but to the author directly.

Note: **Farnell Electronic Components:** Farnell E C have a minimum order charge of £10 for cash orders before VAT. If the 40-pin ZIF socket, which is not otherwise widely available, is combined with XL1, this should meet Farnell's minimum order requirements. XL1 is also available elsewhere. For Sales, phone 0113 263 6311 and say that you are a cash order (cheque or credit card), not an account.

There is no postal charge for normal delivery.

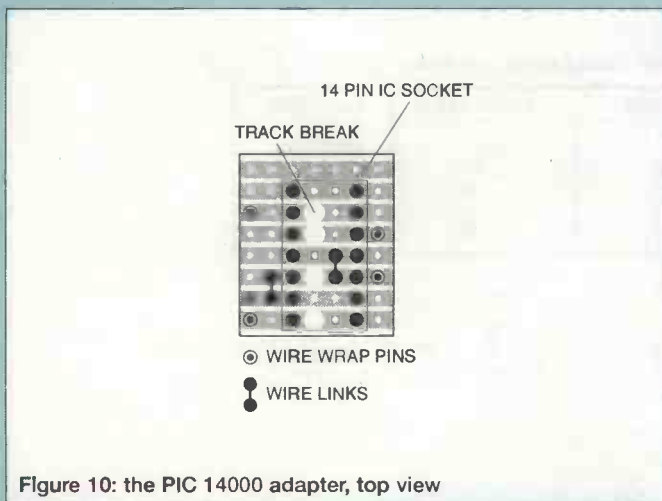


Figure 10: the PIC 14000 adapter, top view

PARTS LIST for the PIC Programmer		Resistors	
		All 1% 0.25 W	
		R1-4	1k
		R5	47R
		R6	330R
		R7,8,11-15	10k
		R9	300R
		R10	1k5
		Capacitors	
		C1,4,7	10uF 25V electrolytic radial
		C2,3,8	100nF disc ceramic
		C5,6	22pF disc ceramic
		Semiconductors	
		IC1	See Text
		IC2	78L05
		IC3	78L12
		TR1-5	BC559
		TR6	BC548
		D1	1N4001
		D2-4	1N4148
		ZD1-3	11.0V Zener
		LD1	Red led, 5mm
		Miscellaneous	
		XL1	4MHz resonator Farnell part number 170-230 £1.20 ex VAT
		PL1	Power socket PCB mounted
		PL2	9 pin D-socket PCB mounted IC socket DIL, 18 pin
		ZIF socket	40 pin multi-width Farnell part number 178-238 £9.87 ex VAT.
		PCB	
		Rubber feet for PCB	

The Royal International Air Tattoo 1997

WIN TICKETS!

... to the big family spectacle.

Nothing compares to the fast-paced action of The Royal International Air Tattoo as over 400 aircraft from 35 nations fly in to take part. Vintage aeroplanes and modern jets, breathtaking aerial routines, a two mile static park.

Use your skill and judgement to win two tickets to the 1997 show.

RIAT 1997 takes place at RAF Fairford, Gloucestershire on the 19th and 20th July 1997. The gates to RAF Fairford open at 6.30 am - up with the larks - and the flying programme runs from 10.30 am to 6.15 pm.

The might of the United States Air Force is in the spotlight for Britain's official 50th anniversary tribute at RIAT 97. The Spirit of the Eagle will be captured in a unique flying display tracing landmark USAF operations from the early Cold War years to recent campaigns like Operation Desert Storm.

In a show-stopping finale the RAF Red Arrows fly with the USAF to wish the world's biggest air force a very happy birthday.

You will need your walking shoes to see all the aircraft in the two-mile static line-up and to take in the 500 or more attractions at RIAT 97 - the action-packed arena, roadshows, virtual reality rides, marching bands, craft fair, motor show, exhibitions, street entertainers and strolling players. There will be a Sunset Festival to release up to 40 hot air balloons. And there will be food villages, beer tents, lots of ice cream vendors, picnic areas and a creche for 2 to 10 year olds, running special shows for children.

ETI and RIAT 97 are giving away 15 pairs of adult tickets to the first 15 readers of ETI who can correctly identify the 10 differences between the two action-filled cartoons on this page.

For enquires about RIAT 97, contact the RIAT Hot News Line on 0891 122999 or multiple-choice switchboard at 01285 713268. (Calls on 0891 numbers are charged at 50p per minute of which 15p per minute is donated to the RAF Benevolent Fund Enterprises, PO Box 1940, Gloucester GL7 4NA.) If you don't fancy your luck at spot-the-difference, want to make sure of getting to Fairford, or want to take the whole family, adult advance tickets are £16 each (£20 on the day), accompanied children (aged 15 and under) get in free. The RIAT 97 ticket hotline is 0891 122997 (credit card sales), or drop into your local Waitrose or Victoria Wine branch (who are selling advance tickets).

Competition rules: Entries must arrive at Nexus House on or before 12th June 1997. Winners will be notified by post following the judging. The judges' decision is final and no communication will be entered into concerning the results. Employees of Nexus Special Interest Ltd. and Swift Design Ltd., associated companies and family members are not eligible to enter. Multiple entries will not be accepted. The prize is two complimentary adult tickets to the Royal International Air Tattoo, RAF Fairford, Gloucester 19th & 20th July 1997, to be sent by post to the winners. No other goods, services or expenses will be supplied in connection with the competition. For further information about the RIAT 97 please contact the RIAT Hot News Line 0891 122999. Calls on 0891 numbers are charged at 50p per minute of which 15p per minute is donated to the RAF Benevolent Fund Enterprises, PO Box 1940, Fairford, Glos GL7 4NA. No communications can be entered into regarding the competition.

Look carefully at the two pictures. In the bottom one you will see that the artist has omitted a few details. Clearly ring the area where you think the details have been missed out on the lower picture, cut it out (or send a clear photocopy of both pictures) and send it to us to reach the ETI office at the address below **no later than Thursday 12th June 1997**. The first 15 entries to reach us that clearly identify all 10 differences correctly will receive two complimentary adult tickets to the show. So get flying!

Good luck!

Send your entries to RIAT Competition,
ETI, Nexus House, Boundary Way,
Hemel Hempstead, Herts HP2 7ST
by 12th June at the latest. Please clearly
mark your envelope **RIAT COMPETITION**.




PCB Designer

For Windows 3.1, '95 or NT



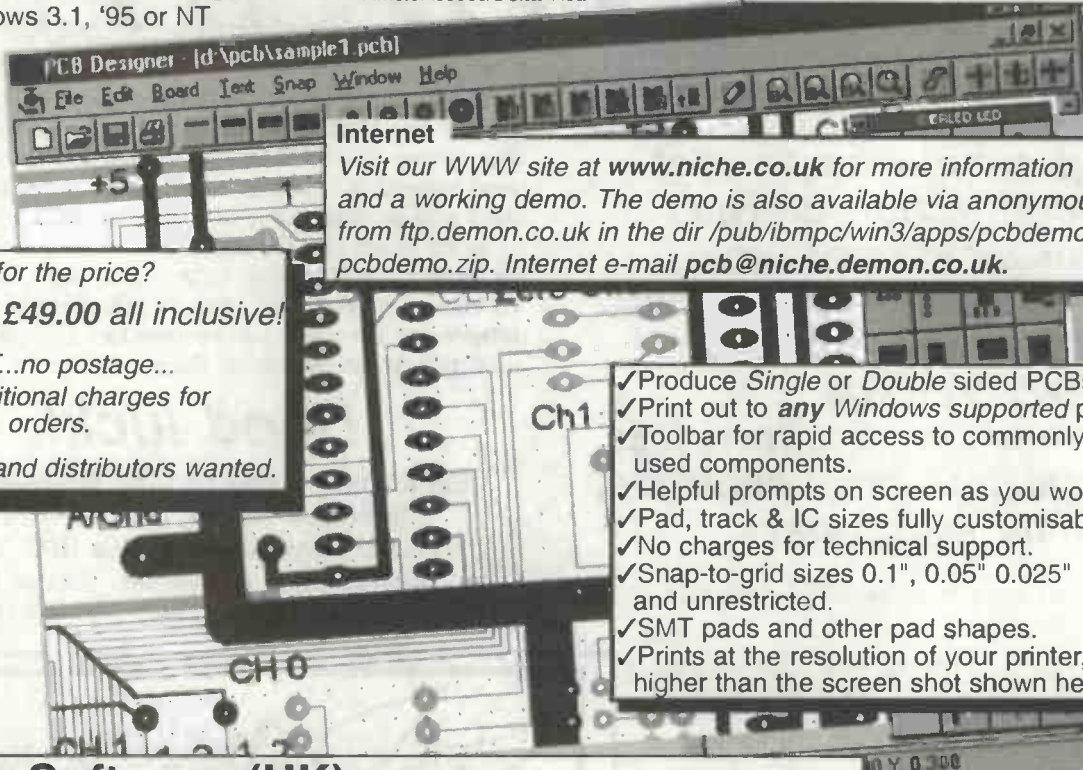Runs on any PC running Windows 3.1, Windows 95 or Windows NT with a minimum 2MB RAM
Will work with any Windows supported printer and monitor



Looking for the price?

It's just £49.00 all inclusive!

...no VAT...no postage...

...no additional charges for overseas orders.

Dealers and distributors wanted.

Internet

Visit our WWW site at www.niche.co.uk for more information and a working demo. The demo is also available via anonymous FTP from <ftp:demon.co.uk> in the dir /pub/ibmpc/win3/apps/pcbdemo/ as pcbdemo.zip. Internet e-mail pcb@niche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to *any* Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to-grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer, much higher than the screen shot shown here.

Niche Software (UK)

12 Short Hedges Close, Northleach, Cheltenham GL54 3PD Phone (01432) 355 414

Available in South Africa from JANCA Enterprises, PO Box 32131, 9317 Fichardtspark at R299,00



GREENWELD

Greenweld has been established for 23 years specialising in buying and selling surplus job lots of Electronic Components and Finished Goods. We also keep a wide range of new stock regular lines. Why not request our 1997 Catalogue and latest Supplement - both absolutely FREE!

BECOME A BARGAIN LIST SUBSCRIBER TO SEE WHAT'S ON OFFER BEFORE IT'S ADVERTISED GENERALLY

Standard Bargain List Subscription

For just £6.00 a year UK/BFPO (£10.00 overseas), we'll send you **The Greenweld Guardian** every month. With this newsletter comes our latest **Bargain List** giving details of new surplus products available and details of new lines being stocked. Each issue is supplied with a personalised **Order Form** and details of exclusive offers available to Subscribers only.

Gold Bargain List Subscription

For just £12.00 a year (£20.00 overseas) the **GOLD** Subscriber category offers the following advantages:

- ☐ **The Greenweld Guardian** and latest **Bargain List** every month, together with any brochures or fliers from our suppliers
- ☐ **A REDUCED POSTAGE RATE** of £1.50 (normally £3.00) for all orders (UK only) and a reply paid envelope
- ☐ **5% DISCOUNT** on all regular Catalogue and Bargain List items on orders over £20.00

So Don't Miss Out - Subscribe Today!

27E Park Road · Southampton · SO15 3UQ

TELEPHONE: 01703 236363 FAX: 01703 236307

INTERNET: <http://www.herald.co.uk/clients/G/Greenweld/greenweld.html>

Our stores (over 10,000 sq. ft.) have enormous stocks. We are open 8.00 am - 5.30 pm Monday to Saturday. Come and see us!



Fast Fivers

Adaptable, affordable - handy circuits for around £5. By Owen Bishop
3. Electronic Put-and-Take

Put-and-Take originated in medieval Germany and has been popular in one form or another ever since. The playing piece is a four-sided top, the dreidel, which has markings on each side. Players spin the dreidel in turn and then play according to which side is uppermost when it stops. In this electronic version there is a 7-segment LED which displays one of four characters:

- | | |
|---|---------------------------|
| 0 | Do nothing |
| 1 | Put one chip in the kitty |
| H | Take half the kitty |
| A | Take all the kitty |

Players (two or more) draw lots or spin the dreidel to decide who is to play first. They each contribute two chips to the kitty, then play begins. The chosen player spins the dreidel (more about that later) and 'puts' or 'takes' each time until the spin gives a '0', when the turn passes to the next player. Players contribute another two chips to the kitty every time it becomes empty.

How it works

The circuit consists of an oscillator (figure 1, IC1), a counter (IC2), a decoder (IC3) and the LED display. IC1 is actually an ic for building a phase-locked loop but there is no PLL in this circuit. We are using only one of the several useful items on this chip, the voltage controlled oscillator. The central frequency of this oscillator is determined by the values of C2 and R2, according to the equation:

$$f = 1/(C2.R2)$$

It is not just that the rate falls slowly because C1 and R1 are high-valued. The rate of fall at any instant is proportional to the charge on C1. The rate falls rapidly when S1 is first released, but falls more and more slowly as C1 discharges. We describe the rate of fall as exponential. This may sound like a dull mathematical relationship, but its effect is to add a substantial element of nail-biting suspense to the game, as we shall see later.

The stream of pulses coming from IC1 is counted by IC2, which is a 14-stage binary counter. Once again, we do not use everything that is on the chip. We need the output from two consecutive stages and, as the outputs from stages 2 and 3 are not available at the pins, we use stages 4 (pin 7) and 5 (pin 5). Given that a high voltage (close to 6V) is '1' and a low voltage (close to 0V) is '0', these outputs run through the four binary numbers 00, 01, 10 and 11, repeating until the oscillator stops. The outputs spend equal times in each state and are equally likely to stop in any one state. In this way the circuit appears to behave in a random way, just like the spinning dreidel.

The four characters have been chosen to make decoding easy. Segments b and c (figure 2) are to be switched on for all characters, so can be connected directly to the positive rail through a resistor R4. We need to decode only for segments a and c to g. This truth table shows the logic:

Inputs from IC2				Segment (logic equation in brackets)			
B (pin 5)	A (pin 7)	a (= A)	d (= A+B)	e (= A+B)	f (= A+B)	g (=B)	Character
0	0	0	0	0	0	0	1
0	1	1	1	1	1	0	0
1	0	0	0	1	1	1	H
1	1	1	0	1	1	1	A

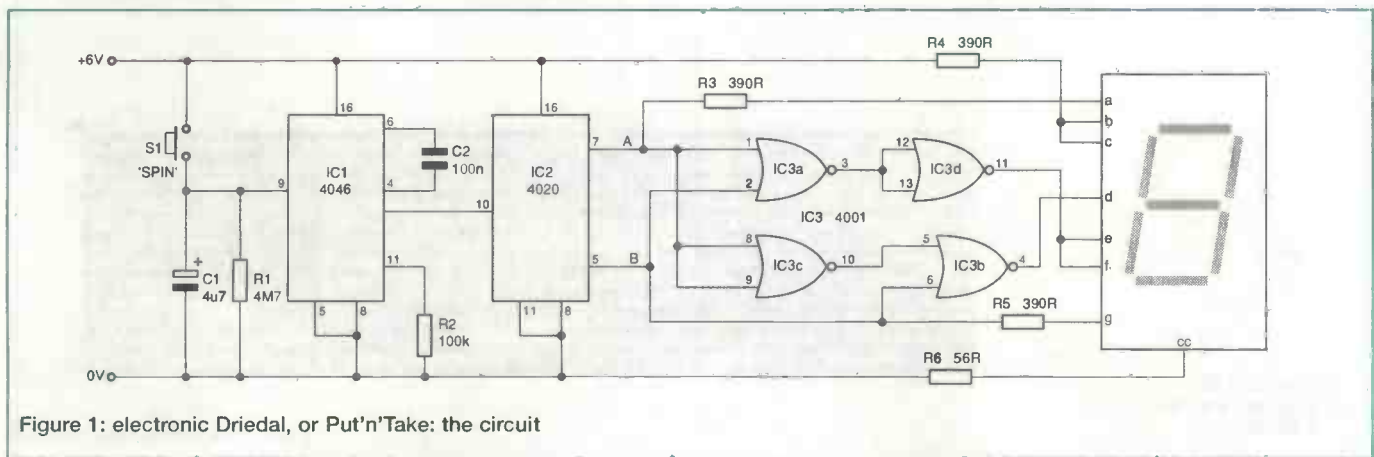


Figure 1: electronic Dreidel, or Put'n'Take: the circuit

The '+' sign represents the OR operation, while a bar over a letter or pair of letters means NOT (invert). To get 'e' and 'f' we simply NOR A with B. To get 'd' we invert A with gate 3, then NOR it with B in gate 2.

Summing up what happens during a spin, pressing S1 starts the oscillator at 100Hz but, because we dividing the rate at stages 1 to 3 before taking the outputs from stages 4 and 5, the display cycles through the set of characters just over 3 times per second (if you want it faster, decrease the value of R2). At first the display is changing a little too fast to distinguish the characters but after a few seconds we can begin to pick out the characters. Towards the end, each character remains displayed for several seconds each time. They remain longer and longer and longer ... Eventually one (but which one?) remains permanently displayed, and the payout (or in!) begins.

Construction

Figure 3 shows the stripboard layout. The connections to the LED display follow the pattern of commonly-available types, but check this with the component catalogue, since there are other ways in which the pins are designated. Note that is essential for the display to be of the common cathode type; the common anode type does not work in this circuit. The strips are cut beneath the board as indicated by crosses on Fig 3, but note that there are NO cuts at E31, G31, F35 and H35, since we are making use of the strips for two inter-pin connections and two connections to the display. Solder blobs between adjacent strips are used to connect: B14 to C14, B24 to C24, B33 to C33, C33 to D33, D43 to E43, H33 to H33, K11 to L11 and K21 to L21. The board has connections to a 6V battery, which may be a battery box for four 1.5V cells, if preferred. S1 is connected to the 0V supply and to the pin at E1.

PARTS LIST for the Put,n,Take

Resistors

(all 5% tolerance, 0.25W)

R1	4.7 megohm
R2	100 kilohm
R3, R4, R5	390 ohm (3 off)
R6	56 ohm

Capacitors

C1	4.7µF, electrolytic
C2	100nF, polyester

Semiconductors

IC1	4046 CMOS phase-locked loop
IC2	4020 CMOS 14-stage binary counter/divider
IC3	4001 CMOS quadruple 2-input NOR gate

Miscellaneous

S1	Push-to-make push-button
	7-segment LED display, common cathode, 0.3-in (7.62mm), preferably low-current; 2.5 mm stripboard, 119mm \times 30mm (46 holes \times 12 strips); 1mm terminal pins (3 off); 14-pin di IC socket; 16-pin di IC sockets (2 off); battery clip or 6V battery box.

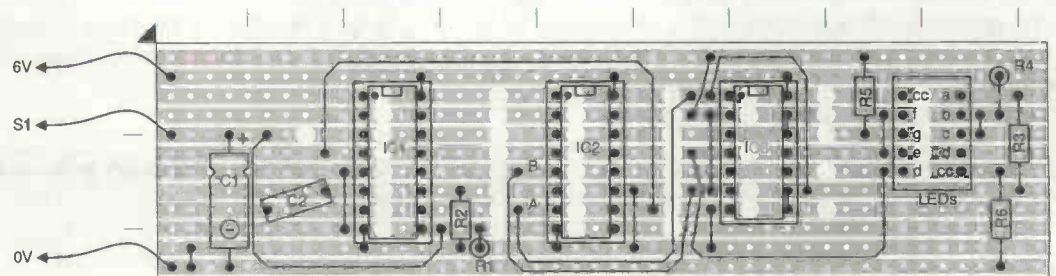
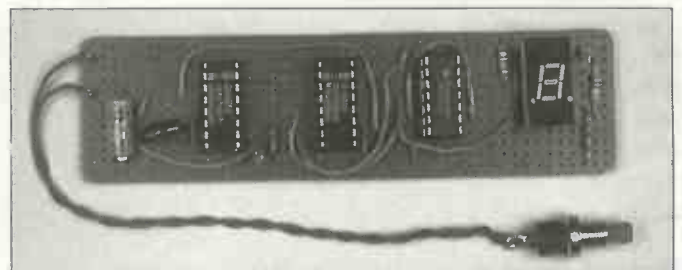


Figure 2: the segments of the LED display

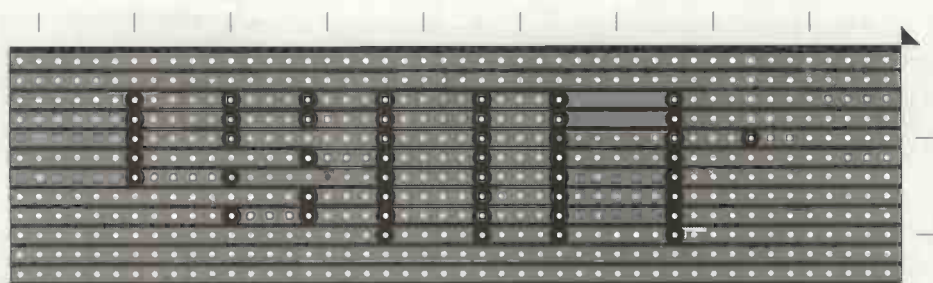


Figure 3: the stripboard layout

Virtual pH METER for PCs

Following the trend to PC-controlled scientific instruments, this design uses a low powered circuit operated via the serial port of the PC

**By Ronaldo Bruno and Valentin Obac Roda
Institute of Physics of Sao Carlos/University of Sao Paulo, Brazil**

The increasing use of personal computers in the most diverse areas of activity has radically changed the face of electronic instruments. Many instruments that were self contained a few years ago, such as oscilloscopes, voltmeters, spectrum analysers and so on can these days be bought as boards to be plugged in personal computers. The display, keyboard and mouse of the PC perform the control and data visualisation of the instruments. This new trend in instrumentation is known as 'Virtual instrumentation'.

One of the drawbacks of using dedicated instrumentation boards inside the computer is the lack of portability. To move the instrument from one place to another it is necessary to move the computer or to take the board and use it in another computer. There is also a restriction in the use of laptop computers, because most instrumentation boards do not fit inside them. In this article we present a virtual instrument connected to the computer via the serial port of the PC. To increase the portability we used a low power consumption circuit fed by the serial port of the PC. The instrument that we developed is a pH and temperature meter widely used for chemical analysis, the food industry, geochemistry, water treatment, biomedical and industrial applications.

pH is a measure of the acidity or alkalinity of solutions. The pH scale ranges from 0 to 14. Seven is the neutral point, and solutions that have pH less than seven are acid solutions. The glass electrode is the most common sensor used to measure pH. In the pH range, the pH glass electrode develops a voltage proportional to the pH of the solution. The glass electrode is used in conjunction with a reference electrode. There are electrodes available, known as combination electrodes, that combine the glass electrode and the reference electrode.

The electrical response of the electrode is linear and follows the equation:

$$E = E_0 + 2,3026 \frac{RT}{F}$$

known as the Nernst equation, where: E is the response of the electrode in V/pH and E₀ is the asymmetry potential, characteristic of the electrode and varying with its age. T is the temperature in absolute degrees. F is the Faraday Constant and R is the gas constant. Figure 1 shows the response of the electrode.

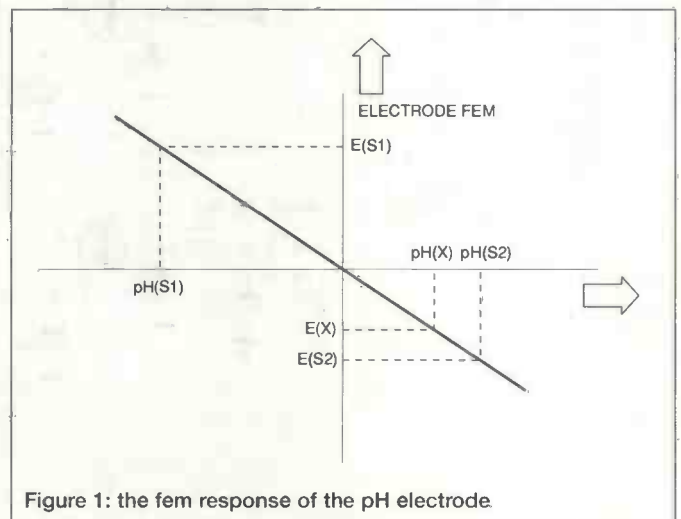


Figure 1: the fem response of the pH electrode

The internal resistance of the pH electrode is very high, around hundreds of megohms, and it is very sensitive to variations of temperature. pH meters should use a very high impedance input circuit. Before the pH measurements, the pH meter is calibrated according to the response of the electrode. This procedure is known as standardisation of the instrument. The pH meter requires the use of one or two of these standard calibration solutions according to the precision required (one- or two- point standardisation).

The Virtual pH meter that we developed has hardware controlled by a PIC microcontroller and software that runs under windows to control the instrument and visualise the data. The PC software was written in Visual Basic.

Hardware

Figure 2 shows the schematic diagram for the circuit of the pH meter. The input circuit of the pH meter is a high impedance, low consumption operational amplifier (LF442A). A LM35 integrated sensor is the temperature sensor. An analogue switch (CD4066) creates two analogue channels, one for the pH and another for the temperature. The circuits of the power supplies and the RS232 hardware implementation were built with discrete components.

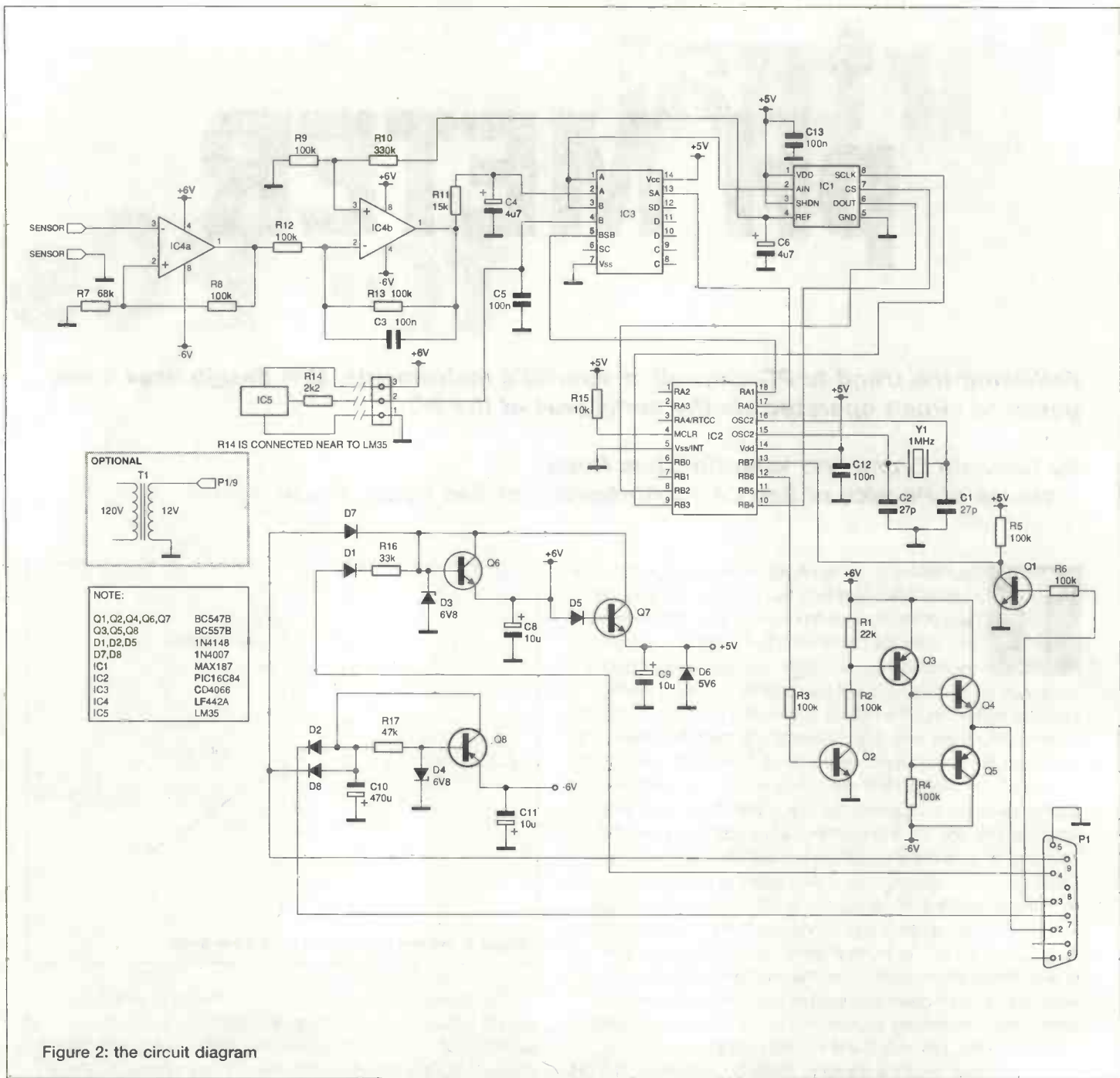


Figure 2: the circuit diagram

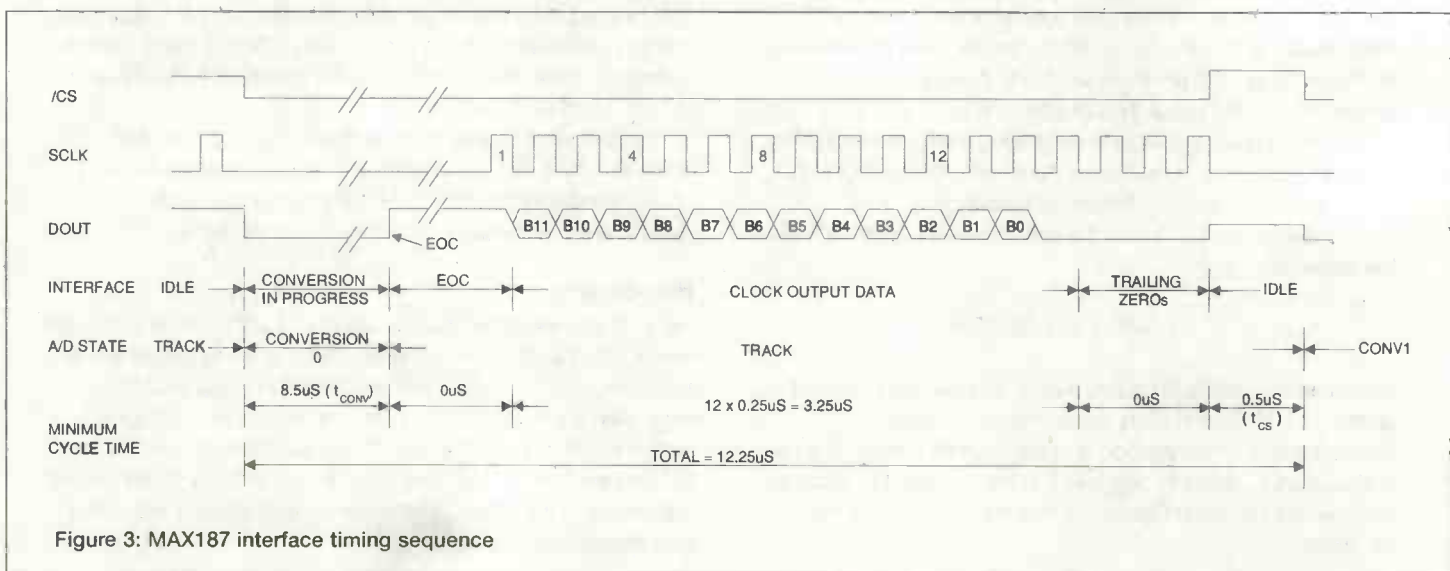


Figure 3: MAX187 interface timing sequence

The MAX187 12-bit A/D converter has a serial output, internal reference of 4.096V (available externally) and sampling rate of 75000 samplings/sec. There are no gain and offset adjustments in the A/D converter. The conversions are performed for voltages in the range 0 to 4.096V. The MAX187 has three control pins, CS, SCLK and DOUT. Figure 3 shows the converter communications protocol.

A P1C16C84 8-bit RISC microcontroller with internal eeprom controls the instrument, including the A/D converter, the analogue switches and the RS232 communication interface. The P1C16C84 has internally a ram, a real time clock counter, a watchdog timer and 13 I/O pins. The watchdog timer resets automatically the system on the occurrence of an internal program lock.

In the input circuit there are two operational amplifiers to amplify the pH sensor output to the A/D converter input. The first operational amplifier is a high input impedance, 2.5x gain, voltage follower. The output voltage of the first op amp goes, in the pH sensor range, from -1.5 V to + 1.5 V. The second op amp adds 2 V to the first op amp output, resulting in a single-polarity converted pH signal in the range of 0 to 3.5 V. An LF442 double op amp operational amplifier was used to implement the pH input circuit. The LF442 has a high input impedance of 1 terra-ohm (10 to the power of 12 ohms) and a low current consumption of 400 kA.

The transistor Q1 and the resistors R5 and R6 convert the level of the R232 input signal (-12V to + 12V) to the 0 to 5 V range. Although the RS232 is specified to work in the -12V to + 12 V range, it can work in the -6V to + 6V range. Q2, Q3, Q4, Q5, R1, R2, R3 and R4 convert the level of the RS232 output signal from TTL (0 to 5 V) level to the -6V to + 6V range.

Finally, we have the power supply circuit, supplying the -6V, +6V and +5V voltages. The MAX187 ic works with voltages from 4.75 to 5.25V and the PIC16C84 works with voltages from 2 to 6V. For the LF442A -6V and + 6V were used, considering that it has to have outputs going up to 3.5V.

The power supply was fed from the hand shaking signals of the RS232 DTRenable and RTSenable. When the instrument is initialised, RTSenable is set to -12V and DTRenable is set to +12V. The current capacity of DTRenable and RTSenable is low, about 8mA. When the current consumption grows the available voltage drops. For this reason the circuit was conceived to minimise the power consumption. The current for the P1C16C84 working on 1MHz is 600A The MAX187 consumes 1.8 mA and the LF442 consumes 400uA. The other parts of the circuit, including the regulators and level converters consume 1 mA more. The total current consumed by the circuit is only 3.8 mA which makes the voltage on the DTRenable drop to about 9V.

Optionally, you can feed the circuit with an AC 120/12V - 100mA transformer as shown in figure 2. This can be useful if the pH meter is going to work with a dedicated system, instead of a standard PC, that has the RS232 protocol communication but doesn't have the handshaking signals.

Seek assistance from a knowledgeable person when working the mains circuits if you not an experienced mains constructor.

Software

The software of the P1C16C84 implements basically the communications protocols of the MAX187 ND converter and of the RS232 serial interface. The serial communication is at 2400 baud, without parity, 8 data bits and one stop bit.

During the initialisation, the program waits a communication from the PC which sends the number 1 as a code to the microcontroller. During the wait loop the port pin of the PIC connected to the RS232 receive line is read continuously until data is received. When the PIC reads the number 1 it communicates with the MAX187 asking for two conversions (pH and temperature). The conversion time of the MAX187 is 8.5 us. Because we did not need to work at full conversion speed we waited a fixed time, longer than the conversion time of the MAX187, instead of waiting for its end-of-conversion signal. The 12-bit converted information is packed in two bytes. An XOR operation of the two conversion bytes generates a third byte used to detect possible communication errors. The pH and temperature values are transmitted to the PC, using six bytes of information according to the protocol shown in figure 4.

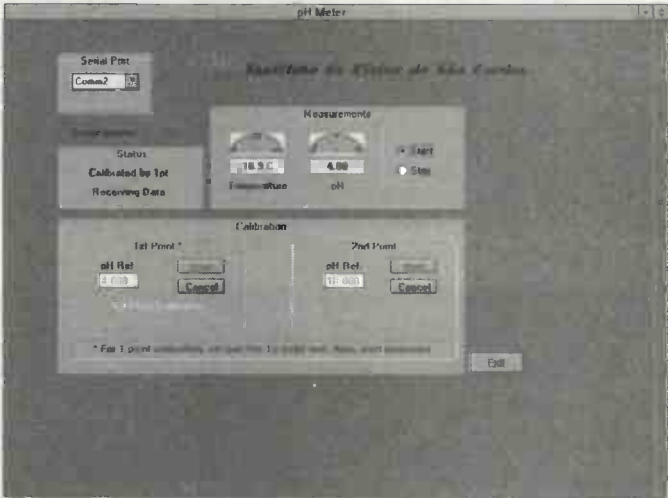


Figure 5: the virtual panel of the pH meter

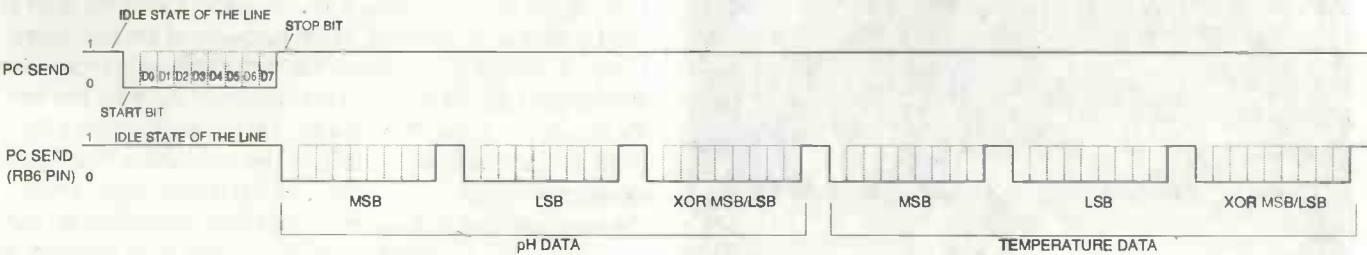


Figure 4: PC to PIC communication protocol

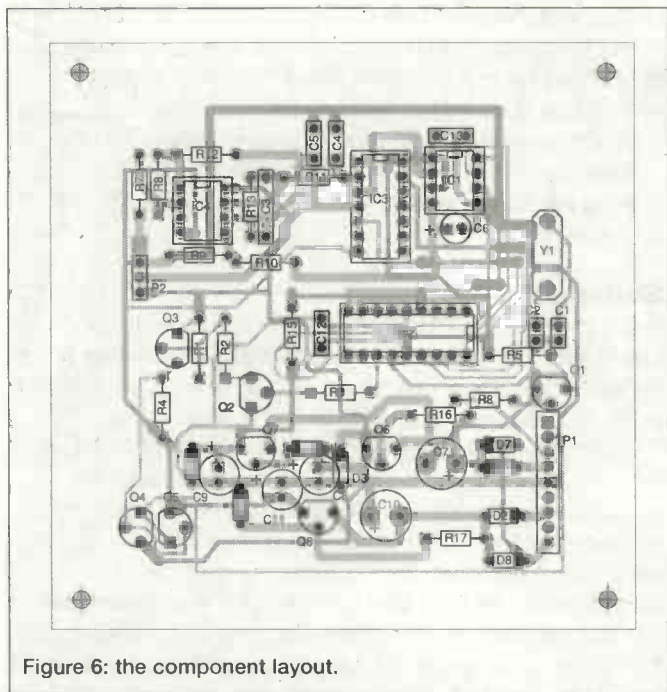


Figure 6: the component layout.


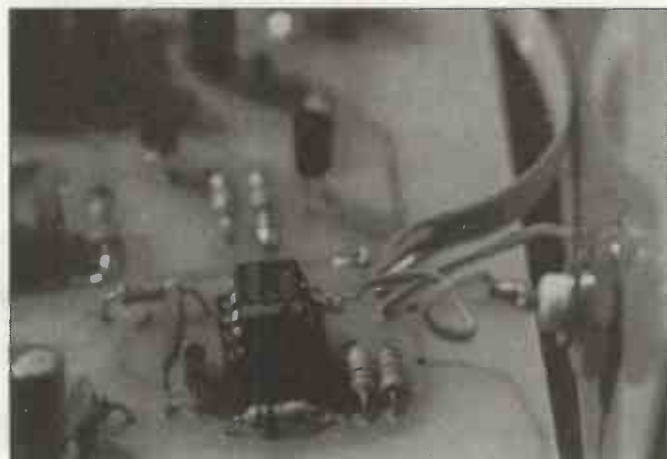


Figure 7: Above construction detail of the pH input

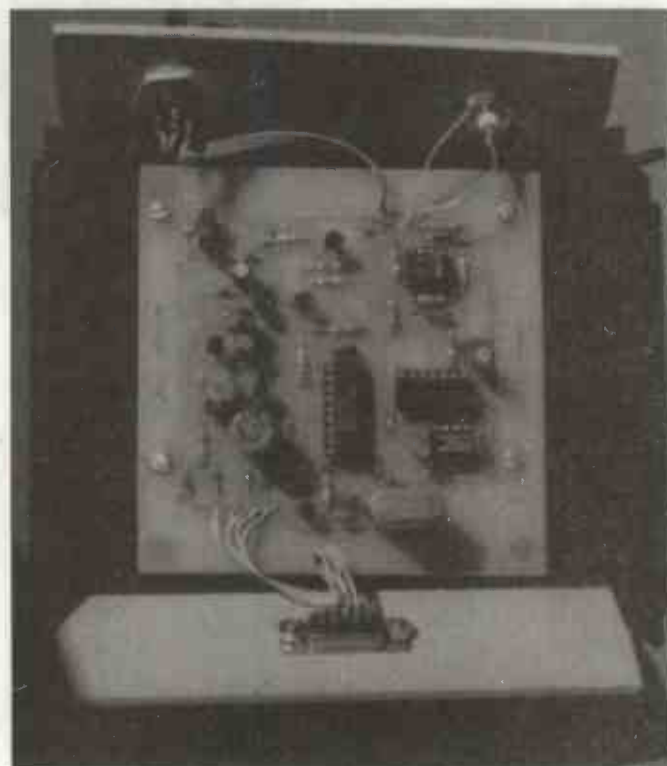

After sending the six bytes of information to the PC, the program returns to the initial wait loop. To avoid deadlocks, the program uses the watchdog timer of the PIC that is basically a counter driven by an internal RC oscillator. When the counter overflows, it resets the PIC, restarting the program. During the program execution on the PIC the watchdog timer counter is constantly reset. When the program enters in a deadlock, the watchdog timer counter is not set to zero and the PIC is then reset.

The software for the PC was developed in Visual Basic 3.0. The program includes routines for calibration, data visualisation and control of the instrument. Figure 5 shows a view of the screen of the instrument. Error treatment routines were included, user errors are trapped and helpful error messages are supplied. Also, when a communication fault is detected it is pointed on the screen. The program recovers automatically when the communication fault is corrected.

Construction details

For the construction of the pH meter, a double sided PCB was used. Figure 6 shows the layout of the printed circuit boards including the component layout. To keep the input for the pH sensor high avoiding current leakage through the printed circuit, pin 3 of the LF442 operational amplifier was directly connected to the BNC connector (pH connector), as shown in figure 7. A photo of the hardware of the instrument is shown in figure 8.

To connect the pH meter to the PC, it is necessary to have a RS232 cable. You can build one connecting a DB25 female to a DB9 female following table 1, which shows the pins for each connector.

Table 1 - RS232 Cable

DB25	DB9
2	3
3	2
4	7
20	4
7	5

Operating instructions

After installing the software, the user should choose an available serial port on the PC and connect the hardware of the instrument to the port. Avoid using COM1/COM2 or COM2/COM4 simultaneously, as this can cause conflicts. For example, if you have a mouse connected to COM1, choose COM2 for the pH meter. If you have the mouse at COM1 and a modem at COM2, choose COM4 for the pH meter and do not use the modem while using the pH meter. When the hardware setup is ready, install the PC software routines and start running the program by clicking the pH meter icon.

As shown in figure 5, we can see four distinct regions: Serial Port, Status, Measurements and Calibration. Initially we have to set the serial port according to the hardware of the instrument. The second step is to calibrate the instrument using one or two standard pH solutions. Before the calibration we have to insert the pH and temperature sensors in the standard solution. To measure the temperature standard click the button "Start" in the measurement region. After this, click the button "Stop" in the measurement region and enter in the Calibration reference first point, the pH of the standard solution. At this point you have to press "start" in the calibration region and wait until the calibration is ready, that is, when the message "1st Point Calibrated" appears on the screen.

The time necessary for the calibration varies according to the pH sensor. In general, it takes less than 30 seconds. If the instrument is calibrated with only one pH solution, the "Start" button in the Measurement region should be pressed. If a two-point calibration method is used, repeat the above calibration procedure for the second pH solution.

In the "Status" region there is available information about the operation of the system. There is a small circle that blinks, changing its colour between red and green, when the serial port is working. If the communication between the instrument and the PC fails, the Comm Monitor stops blinking until the communication problem is corrected.

The LF 442 op amp can be replaced by other dual low power high input resistance op-amps. The TL062 (Texas Instruments), RS/Electromail 638-908, Farnell TL062CN, and the MAX407 (Maxim), RS/Electromail 248-191 have the same pin configurations.

Agents for the **MAX187** 12-bit serial A/D converter (8-pin dil package) are:

2001 Electronic Components tel 01438 74 2001

HB Electronic tel 01204 525544

Both agents will take cash orders if the device is in stock. The list price is £10.48 ex VAT, post and packing and any credit card charges if applicable. At time of writing, HB have slightly lower charges, but 2001 have larger stocks and order more frequently.

Farnell Electronic Components Tel 0113 263 6311 have a minimum order charge of £10 for cash orders (cheque/credit card) before VAT. There is no postal charge for normal delivery.

The INSTALL software for the PC is available at the following WEB site:

<http://www.ifqsc.sc.usp.br/virtph>

or by anonymous FTP at the following address:

www.ifqsc.sc.usp.br/pub/valentin/virtph_directory/pub/valentin/virtph


Or contact the authors at the following address. The authors can also send by mail additional information about the instrument, including a 3 5-in disk with the programs.

Prof. Valentin Obac Roda
Departamento de Fisica e Informatica/IFSC/USP
Caixa Postal 369
13560-970 - 55o Carlos (SP) - Brazil
Fax +55 16 271 3616

or by email at:

VALENTIN @ IFQSC.SC.USP.BR

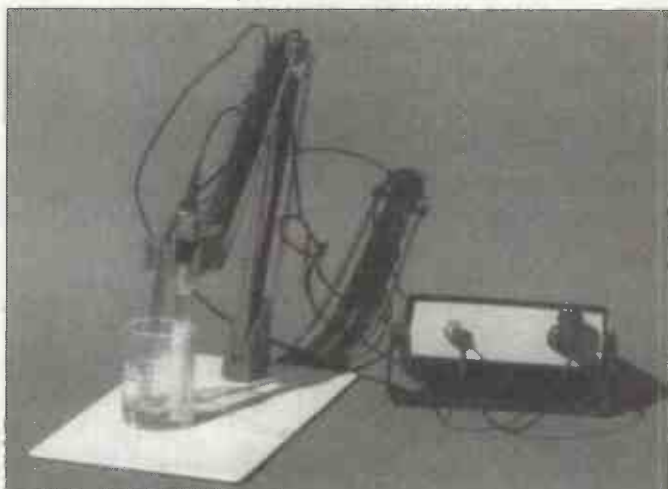Acknowledgements. The authors are grateful to the IFSC-USP, CNPq and PADCT, Brazil for the support for developing the present work and to MAXIM for the samples of the A/D converter.



PARTS LIST for the pH Meter

Resistors

All resistors are 1/8 - watt, 5%.

R1	22K
R2 to R6	100k
R7	68K
R8,R9, R12,R13	100k
R10	330k
R11	15k
R14	2k2
R15	10k
R16	33k
R17	47k

Capacitors

C1, C2	27pF, 25 volts, ceramic disk
C3, C5, C12, C13	100nF, 25 volts, ceramic disk
C4, C6	4.7uF, 16V, radial electrolytic
C7, C10	470uF, 16V, radial electrolytic
C8, C9, C11	10uF, 16V, radial electrolytic

Semiconductors

Q1, Q2, Q4, Q6, Q7	BC547B NPN transistor
Q3, Q5, Q8	BC557B PNP transistor
D1, D2, D5	1N4148 signal diode
D3, D4	Zener 6V8, 400mW
D6	Zener 5V6, 400mW
D7, D8	1N4007 rectifier diode
IC1	MAX187 12-bit ND converter
IC2	PIC16C84 microcontroller RS/Electromail 831-501; Farnell PIC16C84-04P
IC3	CD4066 analog switch RS/Electromail 640-908; Farnell 385-451
IC4	LF442A low power, high input impedance operational amplifier Farnell LF442CN (see below for alternatives)
IC5	LM35 integrated temperature sensor RS/Electromail 317-960 Farnell LM35DZ

Miscellaneous

X1	1MHz Crystal RS/Electromail 307-761 Farnell 170-859
P1	DB9 Panel Male Connector
P2	Three-pin Cannon Male connector
	BNC connector for pH input
	RS-232 Cable DB25 (female) to DB9 (female) - See text.
	5 x 5-in box

```

Listing: Picsoft.obj
#pragma object MPASM V01.21 6-Dec-
1996
"C:\USERS\RONALDO\PICSOFT.ASM"
#pragma interface
P 16C84
#pragma object
0 LINK101
10 START
11 LINK704 0180 0X0B
13 LINK703 3000 0X8E
14 LINK704 0080 0X81
16 LINK703 3000 0X87
17 LINK714 0060 0X6
19 LINK710 1000 0X6,3
20 LINK710 1400 0X6,4
21 LINK710 1000 0X6,6
23 LINK703 3000 0X0
24 LINK714 0060 0X5
26 LINK703 3000 0XFF
27 LINK704 0080 0X5
39 L3
39 LINK703 3000 0X2
40 LINK704 0080 0X15
42 LINK705 0800 0X15,1
43 LINK711 2000 P_ANALG
45 LINK704 0080 0X5
47 LINK703 3000 0X8E
48 LINK704 0080 0X81
50 L7
50 LINK711 2000 RXPIC
52 LINK705 0800 0X20,0
53 LINK702 3C00 0X1
55 LINK710 1800 0X3,2
56 LINK711 2800 L1
58 LINK711 2800 L7
61 L1
61 LINK711 2000 LECONV
63 LINK705 0300 0X15,1
64 LINK705 0800 0X15,0
66 LINK711 2000 P_ANALG
68 LINK704 0080 0X5
72 LINK705 0800 0X13,0
73 LINK704 0080 0X20
74 LINK711 2000 TXPIC
76 LINK705 0800 0X12,0
77 LINK704 0080 0X20
78 LINK711 2000 TXPIC
80 LINK705 0800 0X13,0
81 LINK705 0600 0X12,0
82 LINK704 0080 0X20
83 LINK711 2000 TXPIC
85 LINK705 0800 0X15,0
86 LINK710 1C00 0X3,2

```

```

87 LINK711 2800 L1
89 LINK711 2800 L3
96 P_ANALG
97 LINK705 0700 2,1
98 LINK702 3400 0X1E
99 LINK702 3400 0X1D
100 LINK702 3400 0X1E
108 RXPIC
109 C1
109 LINK710 1C00 0X6,7
111 LINK711 2800 C2
113 LINK701 0064
114 LINK703 3000 0X8E
115 LINK704 0080 0X81
117 LINK711 2800 C1
120 C2
120 LINK711 2000 DELAY2
122 LINK711 2000 DELAY1
124 LINK703 3000 0X8
125 LINK704 0080 0X14
127 C7
127 LINK710 1C00 0X6,7
128 LINK711 2800 C4
129 LINK710 1400 0X3,0
130 LINK711 2800 C5
131 C4
131 LINK710 1000 0X3,0
133 C5
133 LINK705 0C00 0X20,1
135 LINK711 2000 DELAY2
137 LINK705 0B00 0X14,1
139 LINK711 2800 C7
141 C8
141 LINK710 1C00 0X6,7
142 LINK711 2800 C8
144 LINK701 0008
152 TXPIC
153 LINK710 1400 0X6,6
155 LINK711 2000 DELAY2
157 LINK703 3000 0X8
158 LINK704 0080 0X14
160 B5
160 LINK705 0C00 0X20,1
163 LINK710 1C00 0X3,0
164 LINK711 2800 B2
165 LINK710 1000 0X6,6
166 LINK711 2800 B3
167 B2
167 LINK710 1400 0X6,6
169 B3
169 LINK711 2000 DELAY2
171 LINK705 0B00 0X14,1
173 LINK711 2800 B5
175 LINK710 1000 0X6,6

```

```

177 LINK711 2000 DELAY2
179 LINK701 0008
195 LECONV
196 LINK710 1000 0X6,4
198 LINK711 2000 DELAY3
201 LINK711 2000 RECDADO
202 LINK705 0800 0X0F,0
204 LINK704 0080 0X13
207 LINK711 2000 RECDADO
208 LINK705 0800 0X0F,0
210 LINK704 0080 0X12
212 LINK710 1400 0X6,4
213 LINK701 0008
220 RECDADO
221 LINK703 3000 0X8
222 LINK704 0080 0X14
224 E1
225 LINK705 0D00 0X0F,1
227 LINK710 1400 0X0F,0
229 LINK710 1C00 0X6,2
231 LINK710 1000 0X0F,0
234 LINK710 1400 0X6,3
236 LINK701 0000
237 LINK701 0000
238 LINK701 0000
239 LINK701 0000
240 LINK701 0000
241 LINK701 0000
243 LINK710 1000 0X6,3
246 LINK705 0B00 0X14,1
247 LINK711 2800 E1
248 LINK701 0008
255 DELAY1
256 LINK703 3000 0X0F
257 LINK704 0080 0X21
258 G1
258 LINK705 0B00 0X21,1
259 LINK711 2800 G1
260 LINK701 0008
262 DELAY2
263 LINK703 3000 0X1F
264 LINK704 0080 0X21
265 G2
265 LINK705 0B00 0X21,1
266 LINK711 2800 G2
267 LINK701 0008
269 DELAY3
270 LINK703 3000 0X02
271 LINK704 0080 0X21
272 G3
272 LINK705 0B00 0X21,1
273 LINK711 2800 G1
274 LINK701 0008

```



```

;#####
; Software for The pH Meter
; MAX187 e PIC16C84 CLK=1MHz
;#####
; Initialisation routine
;#####

```

START

```

CLRf      0x0B      ;Desable
                  Interruptions

MOVLW     0x8E      ;Programs
                  WatchDogTimer =1seg.

MOVWF     0x81

MOVLW     0x87      ;Programs Port B
TRIS      0x6

BCF        0x6,3    ;Initial level of the
                  SCLK signal
BSF        0x6,4    ;Initial level of the
                  CS signal
BCF        0x6,6    ;Initial level of
                  serial port

MOVLW     0x0       ;Programs Port A
TRIS      0x5

MOVLW     0xFF      ;Desable all analog
                  inputs
MOVWF     0x5

```

```

;#####
; Main routine: receives serial data sent by host.
; Starts 2 conversions, sending 3 bytes each
; conversion. 2 bytes (16-bit data word) and
; 1 verification byte based in a XOR of the 2 data
bytes
; Send protocol: MSB, LSB and verification Byte.
; It sends input AN0 and then AN1 (pH and Temp)
;#####

```

```

L3  MOVLW     0x2      ;Starts analog inputs
                  counter (F15H)
    MOVWF     0x15

    MOVF      0x15,1
    CALL      P_ANALG  ;Converts counter in
                  bits from 0 to 1 at
                  port A (analog input
                  selection)
    MOVWF     0x5      ;Sends selection to
                  port A

    MOVLW     0x8E      ;Refresh OPTION
                  register
    MOVWF     0x81

L7  CALL      RXPIC    ;Waits for the Host
                  (PC) communication

    MOVF      0x20,0    ;Verifies if received
                  byte = 01h
    SUBLW     0x1      ;If positive, starts
                  conversion routines

    BTFSC     0x3,2
    GOTO      L1

    GOTO      L7      ;If received byte
                  isn't = 01h waits for
                  new communication

L1  CALL      LECONV    ;Converts counter in
                  bits from 0 to 1 at
                  port A (analog input

```

```

selection)
;Sends selection to
port A

MOVWF     0x5

MOVF      0x13,0
MOVWF     0x20
CALL      TXPIC      ;Sends MSB byte

MOVF      0x12,0
MOVWF     0x20
CALL      TXPIC      ;Sends LSB byte

MOVF      0x13,0      ;Creates verification
byte
XORWF     0x12,0      ;verification byte =
f13 XOR f12

MOVWF     0x20
CALL      TXPIC      ;Sends verification
byte

MOVF      0x15,0
BTFSS     0x3,2      ;Tests analog input
counter ending.

GOTO      L1

GOTO      L3      ;restarts the main
routine

```

```

;#####
;Routine to convert the analog input counter in
bits of port A
;#####

```

P_ANALG

```

ADDWF     2,1
RETLW     0x1E
RETLW     0x1D
RETLW     0x1E

```

```

;#####
;Routine to implement the RS232 serial receiv
ing at 2400 baud
;Byte received is stored in F20h
;#####

```

RXPIC

```

C1  BTFSS     0x6,7    ;Waits for "Start
                  Bit"

    GOTO      C2

    CLRWDt    ;Clears WatchDogtimer
    MOVLW     0x8E      ;Refresh OPTION
                  register
    MOVWF     0x81

    GOTO      C1

C2  CALL      DELAY2    ;Inserts a 416us
                  delay

    CALL      DELAY1    ;Inserts a "1/2"
                  delay (208us)

    MOVLW     0x8
    MOVWF     0x14      ;Loads counter (f14H)

C7  BTFSS     0x6,7    ;Reads bit at RB7
    GOTO      C4
    BSF        0x3,0    ;Places "1" in Carry
    GOTO      C5
C4  BCF        0x3,0    ;Places "0" in Carry

C5  RRF        ;Locates read bit

    CALL      DELAY2    ;Inserts a 416us
                  delay

```

```

      DECFSZ      0X14,1      ;Checks counting
                           ending (1-8)

      GOTO        C7

C8      BTFSS     0X6,7      ;Verifies "Stop Bit"
      GOTO        C8

      RETURN

;#####
;Routine to implement the RS232 serial
;sending at 2400 baud
;It reads a byte in F20h and then sends it
;#####

TXPIC
      BSF         0X6,6      ;Sends "Start Bit"

      CALL        DELAY2     ;Inserts a 416us
                           delay

      MOVLW       0X8        ;Loads counter (f14H)
      MOVWF       0X14

B5      RRF        0X20      ;Locates , in Carry,
                           the bit that is going
                           to be read

      BTFSS       0X3,0      ;Reads bit through
                           Carry

      GOTO        B2
      BCF         0X6,6      ;Sends "1" at serial
                           port

      GOTO        B3
      BSF         0X6,6      ;Sends "0" at serial
                           port

B2      CALL       DELAY2     ;Inserts a 416us
                           delay

      DECFSZ      0X14,1      ;Checks for counting
                           ending (1-8)

      GOTO        B5

      BCF         0X6,6      ;Sends "Stop Bit"

      CALL        DELAY2     ;Inserts a 416us
                           delay

      RETURN

;#####
;Routine that controls MAX187
;The MAX187 12-bit converter works with 16-bit
;words made up of 2 bytes
;Data word: F13h (MSB) and F12h (LSB)
;The words are received serially (from MAX187)
;at the port RB2
;The LECONV routine place the data read in the
;registers F13h e F12h
;The conversion starts when CS signal goes
;to low level
;(CS=0)
;#####

LECONV
      BCF         0X6,4      ;Sends CS=0

      CALL        DELAY3     ;Waits about 50us for
                           conversion (Tc=8.5us)

      CALL        RECDADO    ;Receives the 1st
      MOVF        0X0F,0     data byte and stores
                           it in f13h

      MOVWF       0X13

```

```

      CALL        RECDADO    ;Receives the 2nd
      MOVF        0X0F,0     data byte and stores
                           it in f12h

      MOVWF       0X12

      BSF         0X6,4      ;Sends CS=1
      RETURN

;#####
;Routine that reads one data byte from MAX187 and
;stores in f05h
;#####

RECDADO
      MOVLW       0X8        ;Counter (1 byte)
                           f14h

      MOVWF       0X14

E1      RLF        0X0F,1     ;Rotates 13h register
                           (locates bit0 for
                           write)

      BSF         0X0F,0      ;Sets bit0=1. If bit
                           at DOUT=0 then the
                           next BFC do the
                           change

      BTFSS       0X6,2      ;Reads data at RB2
                           port (converter DOUT)

      BCF         0X0F,0      ;Locates bit read at
                           register f13h bit=0
                           position

      BSF         0X6,3      ;Sends SCLK=1

      NOP
                           ;The following NOPs
                           ;are inserted to make
                           ;the SCLK signal a
                           ;50% duty cycle signal

      NOP
      NOP
      NOP
      NOP
      BCF         0X6,3      ;Sends SCLK=0

      DECFSZ      0X14,1      ;Decrements counter e
                           jumps if reg=0

      GOTO        E1
      RETURN

;#####
;Delay Routines
;#####

DELAY1
      MOVLW       0X0F      ;Inserts "1/2" delay
                           (208us)

      MOVWF       0X21

G1      DECFSZ     0X21,1
      GOTO        G1
      RETURN

DELAY2
      MOVLW       0X1F      ;Inserts a 416us
                           delay

      MOVWF       0X21

G2      DECFSZ     0X21,1
      GOTO        G2
      RETURN

DELAY3
      MOVLW       0X02      ;Inserts a 50us delay
                           approx.

      MOVWF       0X21

G3      DECFSZ     0X21,1
      GOTO        G1
      RETURN

      END

```


SUMMERTIME IS OUTSIDE BROADCAST TIME



**For broadcasting
over any standard
telephone network**

£199 + £399 Prices to suit your pocket



PARTRIDGE ELECTRONICS




Suppliers of approved equipment for use on P.S.N.
or private circuits

56 Fleet Road, Benfleet ESSEX, SS7 5JN
Phone: 01268 793256 Fax: 01268 565759

osziFOX

£80

A universal 20 MHz
storage oscilloscope

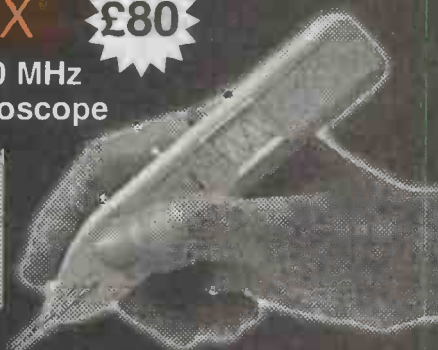

A slimline storage oscilloscope and digital
voltmeter with a sampling rate of up to 20 MHz.
Inclusive software enables the recorded signals to
be displayed simultaneously on a PC screen.

Sample Rates: From 50 ns to 1 ms.

Input Voltage: 1 V, 10 V, 100 V.

Trigger: \pm Internal, \pm External, Auto.

Voltmeter: AC and DC.

Supply Voltage: 9 V to 13 V DC, 13 mA, external.

Trigger, ground, power & serial cables included.

Purveyors of Quality

Electronic Things at

Very Friendly Prices

*No
Nuts
Limited*

2 Chase Cottages,

New Road, Aldham,

Essex CO6 3QT Tel. & Fax 01206 213322

Also Available;

3 mW Laser Pointers £26

CCD Camera Modules from £60

Pinhole camera in wall clock £80

Colour CCD modules from £170

Please add £2 p&p to all orders.

The Low Cost Controller That's Easy To Use

Features

The K-307 Module provides the features
required for most embedded applications

- Analogue** • 4 Channels in 1 Channel out
- Digital** • 36 Digital in or out & Timers
- Serial** • RS-232 or RS-485 plus I2C
- Display** • LCD both text and graphics
- Keyboard** • Upto 8 x 8 matrix keyboard
- Memory** • > 2Mbytes available on board
- Low Power** • Many modes to choose from

Development

The PC Starter Pack provides the quickest method
to get your application up & running

- Operating System** • Real Time Multi Tasking
- Languages** • 'C', Modula-2 and Assembler
- Expansion** • Easy to expand to a wide range
of peripheral cards

Other Features


Real Time Calendar Clock, Battery Back Up,
Watch Dog, Power Fail Detect, STE I/O Bus,
8051 interface, 68000 and PC Interface

**Cambridge Microprocessor
Systems Limited**

CMS

Units 17 - 18 Zone 'D'
Chelmsford Road Ind Est
Great Dunmow Essex CM6 1XG
E-mail cms@dial.pipex.com

Phone 01 371 875 644

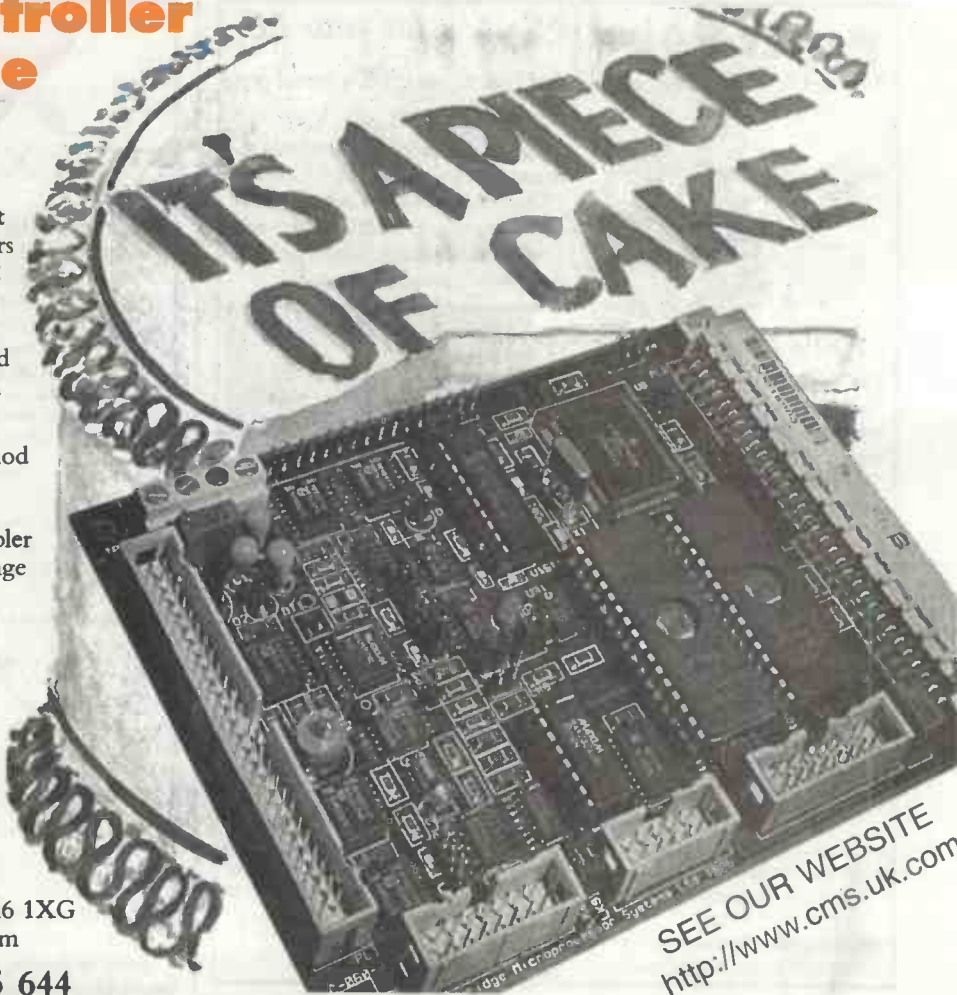

SEE OUR WEBSITE
<http://www.cms.uk.com>

NEW & HARDLY USED TEST EQUIPMENT




DUAL TRACE 20MHZ OSCILLOSCOPE MODEL HC3502
5MV - 20V/DIV, 0.2µ Secs to 0.5Sec/Div;
X - Y; X5 Magnifier; TV Sync etc
Used £180 Un-used £220



KENWOOD FL180A WOW/FLUTTER METER
0.003% - 10%; Frequency 3KHz/3.15KHz;
RMS/AVERAGE/PEAK; Weighted Filters; Digital Display
of rpm; 4 digit Frequency Counter (0.01KHz-9.999KHz-
55KHz)
Used £400 Un-used £500



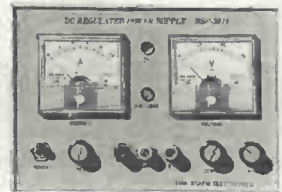PANASONIC VP8177A FM/AM SIGNAL GENERATOR
100KHz-110MHz; Output -19dB to 99dB;
FM 0-100KHz; AM 0-60%; 32 PreSet Memory; Digital
Display Frequency & Output
Used £450 Un-used £750



POWER SUPPLY MODEL HSP3010
0-30 Volts; 0-10Amps; Current Limiting; 2 metres
Used £235 Un-used £275



PANASONIC VP7637A STEREO SIGNAL GENERATOR
Generates Broadcast FM - RDS/ARI PreSet Memory; GPIB
Used £400 Un-used £700



GOODWILL GFC 8010G
FREQUENCY COUNTER
Range 1Hz-120MHz; 8
Digit Display;
15mVrms Sensitivity
Un-used £95



ANALOGUE
MULTIMETER Model
HC260TR
AC/DC Volts; DC Current
10 Amps; 17 Ranges;
Continuity Buzzer;
Transistor Tester
Un-used £15



GOODWILL GYT 427
DUAL CHANNEL AC
MILLIVOLTMETER
10µV - 300V in 12
ranges; Frequency 10Hz-
1MHz
Used £100 Un-used £125



GOODWILL GAG 8086
AUDIO GENERATOR
Sine/Square 10Hz-1MHz
in 5 ranges; 0.1% Low
Distortion; 5 steps Output
Attenuator
Used £60 Un-used £80



STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Tel: 01734 268041 Fax: 01734 351696 Callers Welcome 9am - 5.30pm MON-FRI

OMNI ELECTRONICS

174 Dalkeith Road,
EDINBURGH EH16 5DX

The following items are available until stocks are finished.

MISCELLANEOUS

Microswitch Omron V4 1A button 30p/each
RF screened ABS box 150x80x50mm £1.50/each
PCB switches red, yellow, green & blue 10p/each
Please state colour mix required. £1/pk 16
£5/pk 100



CAPACITORS

Ceramic	1n	F50Vdc	6mm	50p/pk 10
Ceramic	2n2	50Vdc	5mm	80p/pk 20
Mono Ceramic	100nf	50Vdc	all	£1/pk 20
Polyester	470nF	63Vdc	7.5mm	£1/pk 10
Polyester	680nF	100Vdc	15mm	50p/pk 10
Polyester	330nF	250Vdc	15mm	50p/pk 5
Bipolar (Rad)	6.8uF	100Vdc	7.5mm	30p/each
Axial Elec.	470uF	25Vdc	32mm	£1/pk 5
Axial Elec.	220uF	35Vdc	22mm	£1/pk 5
Radial Elec.	47uF	10Vdc	2.5mm	30p/pk 10
Radial Elec.	100uF	10Vdc	2.5mm	40p/pk 10
Radial Elec.	220uF	10Vdc	2.5mm	50p/pk 10
Radial Elec.	100uF	25Vdc	5mm	£1.25/pk 10
Radial Elec.	47uF	63Vdc	5mm	£1/pk 10
Radial Elec.	105°C		150mm solder tails	
	1,000uF	16Vdc	5mm	25p/each
Can Elec.	4,700uF	16Vdc	63x25mm	50p/each
Can Elec.	3,300uF	25Vdc	83x25mm	50p/each

Prices VAT inclusive. Add £1.25 P&P

Payment by cheque, PO, Switch, Amex, Visa, Mastercard
We stock a wide range of electronic components. Catalogue £2.00

Tel. 0131-667-2611 Fax. 0131-662-4063

Power Robotics . . . for your PC

A series of high-powered kits that link to your PC's serial port



Robotic Arm

This 5 axis arm delivers fast, accurate and repeatable movement. The kit includes all hardware, structural components, 6 Hitec servos, a Mini Serial Servo Controller kit, software, sample programs and a detailed assembly manual.



Mobile Arm

The mobile version adds to the excitement. The kit includes everything mentioned in the standard arm kit with the addition of wheels and 2 Hitec servos. This makes a great foundation to add sensors to create a fully featured robot.

Hexapod Walker



Micro Mouse



All prices exclude 17.5% V.A.T.
and £4.50 carriage charge.

technologyindex@btinternet.com
http://www.technologyindex.com

Technology Education Index
40 Wellington Road
Orpington
Kent BR5 4AQ
Tel: (01689) 876880



NEXUS

NEWS FROM THE NEXUS PHOTOSTAT SERVICE.

The Nexus Photocopying Service can provide you with all those interesting features and valuable projects that have been published in your favourite

magazine. The new costs of our photocopying service are as follows:-

First article: £2.75 inc of VAT. Please note that projects published over several issues must be ordered as a series of individual articles, each for £2.00.

A £2.75 search fee is required if full information is not supplied. Please note delivery could be up to 28 working days.

Please supply photo-copies of the following articles from
(Complete in BLOCK CAPITALS)

Month Year Page (if known)

TITLE

Month Year Page (if known)

TITLE

Month Year Page (if known)

TITLE

I enclose a cheque/postal order made out to Nexus Special Interests to the value of:

£ P&P £1.00 (UK only) 20% Overseas

Total remittance £

Name:

Address:

Post Code:

Send the completed form and remittance to:
Photocopy Service, Nexus Special Interests, Nexus House, Boundary Way,
Hemel Hempstead, Hertfordshire. HP2 7ST

Handy Moisture Meter

Going house-hunting? Raymond Haigh's inexpensive, easy-to-construct device could help you to avoid making the mistake of a lifetime.

Dampness in buildings is usually costly to eradicate. Equally important, it can create conditions which promote the establishment and growth of wood rotting fungi, and this can have serious structural consequences. Levels of dampness too low to be detected by touch or sight or smell can be sufficient to cause problems of this kind, and surveyors use a moisture meter when inspecting premises. Experience and judgement are needed to interpret the significance of the readings in a given situation, but the presence of dampness is always a warning sign. Even in inexperienced hands, therefore, a simple moisture meter may alert the user to potential problems.

If you think the property you're looking over could be the house of your dreams, but you suspect that there may be "damp spots", at least you'll be made aware of the need to call in a surveyor to check it out before you buy what could become a costly nightmare.

The instrument described here is inexpensive and easy to construct: indeed, most readers will already have suitable components in their spares boxes. Calibration couldn't be simpler, and guidance is given later on how to use it. The unit will detect low levels of moisture in common building materials. It will also give a clear indication of the relative moisture content, and this feature is often invaluable in establishing the source or cause of the dampness.

Principle of operation

Most porous, non-metallic building materials such as wood, brick, plaster and stone have a high electrical resistance when dry. As their moisture content increases, their electrical resistance reduces. This phenomenon is exploited by almost all of the moisture meters used by surveyors in order to



provide a rapid and non-destructive means of measuring dampness in buildings.

The resistances involved are quite high, above 10 megohms at very low moisture levels, and early instruments of this kind used a sensitive moving coil meter and a high voltage battery (75 - 90V) in order to obtain a reading. By connecting a transistor in a simple circuit it is possible to eliminate the need for the high voltage battery, and a more compact unit can be constructed and operated at modest cost.

The circuit.

The circuit of the unit is given in figure1.

The resistance of the wood or other material across the probe tips, in combination with R1 and R2, fixes the voltage on the base of Q1 and determines the current flowing through the base-emitter junction. This small current initiates a larger current flow through the collector circuit which is read on the meter placed in series with the power supply.

Pre-set resistor R2 enables the instrument to be calibrated; and pre-set R4 acts as a variable shunt across the meter so that the pointer can be set to full-scale when the probe tips are shorted together (that is, zero resistance). R5 limits the action of R4 and ensures that the pre-set is easy to adjust. The emitter resistor, R3, makes the circuit relatively immune to spreads in transistor characteristics.

The action of the circuit is extremely simple. The lower the resistance across the test probes, the greater the voltage on the base of Q1. This increases the current flowing through the transistor and the reading on the meter. The lower the resistance the higher the moisture content of the material under examination, and so the meter scale reads conventionally, from left to right.

Very little current flows when the probe tips are open circuit, (a tiny fraction of a micro-amp) and an on/off switch is not required.

Components.

The components are widely available and non-critical, and no difficulty should be encountered in obtaining them. Almost any low- frequency, small-signal, NPN silicon transistor should be suitable for Q1. If the specified BC171 is not to hand, try a BC107, 108 or 109.

Any moving coil meter with a FSD within the range 50 to 500uA will be suitable. A Maplin

60 x 45mm pan type meter with a 100uA movement is fitted in the prototype instrument, and the values of R4 and R5 have been chosen to suit its current range and 3750 ohms internal resistance. If a more sensitive unit is fitted, R5 may have to be shorted out in order to reduce the shunt resistance. Conversely, if a less sensitive meter is used, pre-set, R4, may need increasing to 2 or even 4K7 ohms in order to secure full scale deflection with the probe tips shorted. Constructors who do not wish to modify the meter scale would be wise to install an instrument with a scale calibrated 0 - 100, as this will make it easier to interpret the readings.

The probe tips have to be sharply pointed and hard enough to resist blunting when pressed into timber, plaster or the mortar joints in brickwork. Hardened steel picture hanging pins are used for this purpose in the prototype instrument. These pins have brass heads and this makes it easy to solder them to the probe leads.

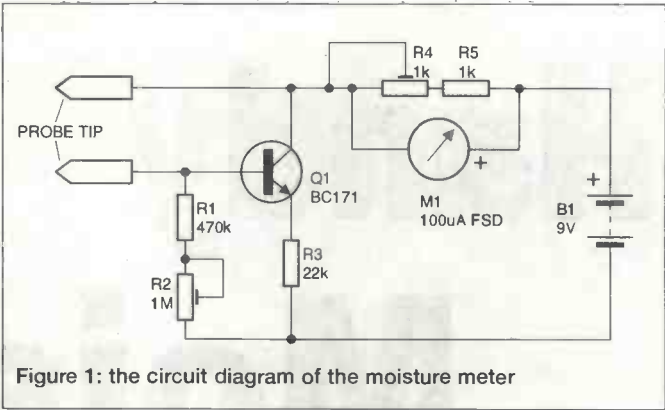


Figure 1: the circuit diagram of the moisture meter

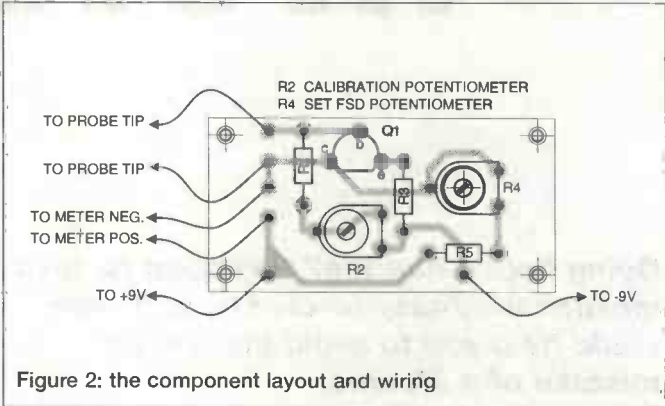


Figure 2: the component layout and wiring

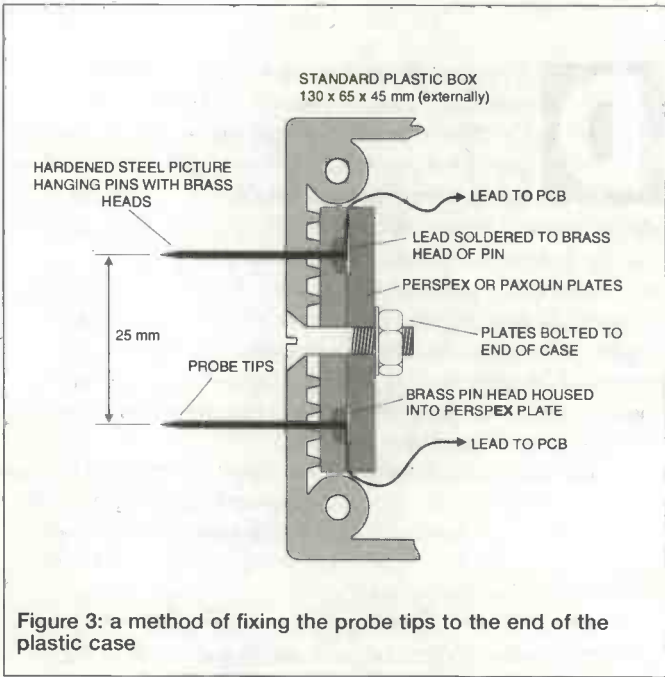


Figure 3: a method of fixing the probe tips to the end of the plastic case

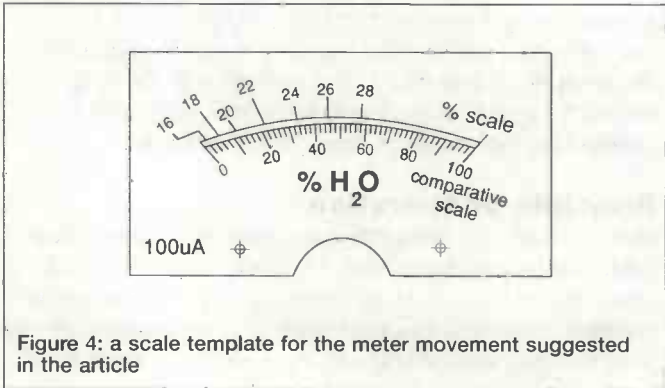


Figure 4: a scale template for the meter movement suggested in the article



Construction.

The components are mounted on a small PCB. The component side of the board is illustrated in figure2, and the foil side in figure3. Vero pins inserted at the lead-out points ease the task of off-board wiring.

Meter, battery and PCB should be housed in a small plastic box. The arrangement adopted for the prototype is shown in a photograph. The PCB and meter are mounted on the lid, and the battery is held in place by a Paxoline partition across one end of the box. A fretsaw or coping saw can be used to form the hole for the meter.

Attach the PCB to shallow stand-offs by means of short, self-tapping screws, then Superglue the stand-offs to the lid of the box, taking care to align the holes which access the adjustment slot of R4.

The probe tips project through the end of the box, and the method of securing them is illustrated in figure 4. The probe has to be pressed fairly hard into the material under examination, and the pin fixings must be able to resist this. If the pins are a tight fit into the piece of Perspex or Paxoline, it may be possible to hold them securely in place with cyanoacrylate adhesive (Superglue) and dispense with the nut, bolt and second piece of Perspex.

Setting up

Check the PCB for poor soldered joints or bridged tracks, and check the orientation of Q1. If all is in order, connect the meter, rotate the pre-sets to minimum resistance and connect a fresh 9V battery. The meter pointer should remain at zero.

Short the probe tips together and rotate R4 to increase the amount of resistance in circuit until the pointer is at full-scale.

Connect a 2M2 resistor across the probe tips and adjust R2 to set the meter pointer at 20 on the comparative (0-100) scale.

Check again for full-scale deflection with the probe tips shorted, and refine the adjustment of R5, if necessary. Check again for a scale reading of 20 with the 2M2 resistor across the probe.

The setting-up process is now complete and the sensitivity of the instrument has been fixed in the critical 20 - 22% moisture content region. A 620k resistor connected across the probes should now bring the pointer to 50 on the comparative scale (centre scale). This final test is desirable in order to check that the unit is functioning correctly.

If a 500uA meter, or a transistor with a low hFE, has been used, and full-scale-deflection cannot be obtained even with

R5 shorted out, try reducing the value of R3 to 10k.

Battery life is its shelf-life, but falling voltage affects the sensitivity of the unit. Check, from time-to-time, that full-scale deflection is obtained with the probe tips shorted, and adjust R4, as necessary, to ensure this.

Calibration

With the instrument constructed and set up as described, the moisture content percentages, at various points on the 0-100 meter scale, are as tabulated below:

Moisture content percentage						
16	18	20	22	24	26	28
Reading on 0-100 scale						
2	6	12	22	34	46	58

Readers can use the above information to re-calibrate any suitable meter. Alternatively, if the data is pasted onto the case of the unit, it should be reasonably easy to operate it without re-calibration provided the meter has an 0-100 scale.

The calibrated scale of the meter fitted in the prototype unit is reproduced in figure5. If the specified meter is used, a photostat could be stuck to the rear of the existing aluminium scale plate with a smear of Durofix adhesive.

Gently prise off the clear acrylic meter cover, remove the two self-tapping screws which secure the aluminium plate and slide it from beneath the pointer. There is generous clearance between the pointer and the surface of the plate, and the extra thickness of the new scale will not cause problems. Sticking the new scale to the reverse of the existing enables the original meter function to be restored, without difficulty, should this be desired. Before the plate is re fixed, colour the central band of the new scale bright red, from 20 percent to maximum, as a visual reminder of the danger zone.

Moving coil meters are very delicate things and the above operation should be carried out with the utmost care so as not to damage the pointer or the bearings of the movement.

For reasons which are explained later, the calibration of the unit is inevitably approximate, as, indeed, is the calibration of all moisture-measuring instruments of this kind.

Using the Moisture Meter

In order to check for dampness, simply press the probe tips into the timber or plaster and note the reading on the meter scale. When checking moisture levels in brickwork, press the probe into a mortar joint. If the material is too hard to permit penetration, press the probe tips firmly against the surface.

Try the unit out at home before boldly going forth to check moisture levels in someone else's property. If your house is free from dampness, the meter pointer will not shift from zero and you will have to try exterior woodwork or timber left lying around outside in order to experience a visible reading. (Pressing a finger across the probe tips should drive the pointer across the scale.) The testing procedure will, of course, leave tiny marks on surface decorations, and it is courteous and wise to obtain the approval of the house owner before using the moisture meter.

The following notes should help you to make some sense of readings you might obtain (and give you a few technical terms to help build up your 'street-cred' when talking to the experts).

(1) If the material is acceptably dry, there will be no deflection of the meter pointer. Any noticeable deflection, no matter how slight, is, therefore, an indication of dampness.

(2) The meter indicates the approximate moisture content of timbers commonly used for building purposes. Moisture content is the weight of absorbed water divided by the dry weight of the wood.

(3) The critical moisture level is 20% (12 on the 0-100 comparative scale). Above 20%, dry rot (*Serpula lacrymans*) can establish itself. Once established, it can survive with moisture contents as low as 14-15% (a slight deflection of the meter pointer).

(4) Wet rot (usually *Coniophora puteana*) requires a moisture content in excess of 40% (moving towards full-scale deflection of the meter pointer) before it can become established and develop.

(5) Timber joists and beams are built into walls. Readings on plaster or brickwork will, therefore, reveal the possibility that hidden timbers may be exposed to excessively damp conditions.

(6) The moisture meter indicates relative dampness levels in plaster, brick, concrete and stone, and this makes it a useful diagnostic tool. Rising dampness in a wall is indicated by readings close to full-scale at ground floor level petering out to near zero about one metre up.


(7) Condensation may be the culprit if fairly similar readings are obtained over the entire surface of a wall.

Limitations

Timber moisture content for a given resistance between the probe tips varies from species to species and, to a lesser extent, from tree to tree and within a single board or plank. The temperature of the wood, surface contamination, and impregnation with preservatives, also affect the readings obtained, and all of these factors combine to impose limitations on the accuracy of instruments of this kind. Resistance measuring moisture meters do, however, permit the rapid and non-destructive assessment of dampness levels, and they are standard items of equipment for surveyors who carry out detailed inspections of property.

Knowledge, skill and experience are needed to correctly interpret the significance of the readings in a given situation. In the case of a house you're only marginally interested in, however, discovering dampness could be the clincher that makes you decide not to proceed any further. If you find dampness in a property you've fallen in love with, call in an independent expert to carry out an inspection and prepare a report before you make an offer.

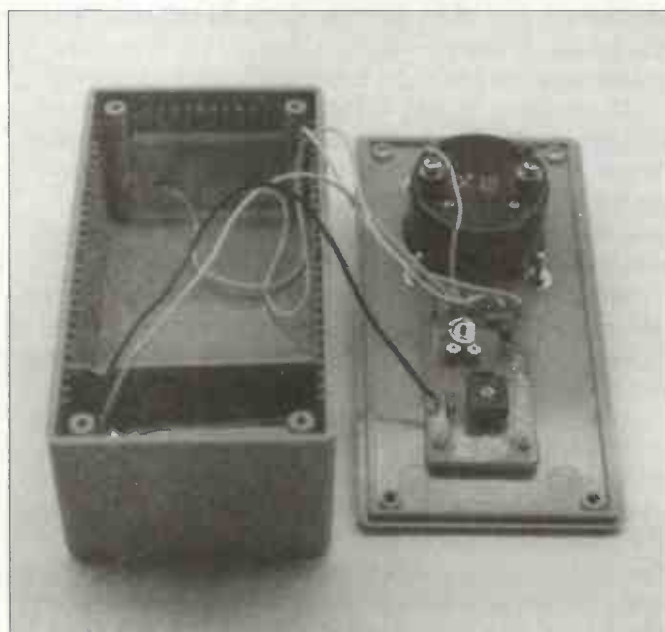Provided you bear in mind the limitations of the instrument (and, perhaps, your own limitations, too) an evening spent with a soldering iron could help you to avoid making the mistake of a lifetime.



PARTS LIST

Resistors

All 0.25 Watt, 5% tolerance unless otherwise stated.

R1	470k
R2	1M pre-set potentiometer.
R3	22k
R4	1k pre-set potentiometer.
R5	1k
R6	2M2 1% for calibration purposes.
R7	620k 1% for calibration purposes.

Semiconductors.

Q1	BC171
----	-------

Meter

M1	Moving coil type, 50 - 500uA FSD. See text.
----	--

Sundry items.

PCB making materials, Vero pins and hook-up wire. PP3 battery and connector. Plastic box. Brass-headed picture-hanging pins. Small pieces of Perspex or Paxoline. Small self-tapping screws and stand-offs. Cyanoacrylate adhesive (Superglue).

NEW SPECIAL OFFERS

New mini waterproof TV camera 40x40x15mm requires 10 to 20 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 380 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v In and video out).

£93.57 + VAT = £109.95 or 10+ £89.32 + VAT = £104.95.

High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software.

Kit £67.00 ready built £99.00

Software support and 4 digital inputs kit £27.00

power interface 4A kit £36.00

power interface 8A kit £46.00

Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit £23.00

Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty £33.45

LEDs 3mm or 5mm red or green 7p each

yellow cable leads 1p each £5.95 per 1000

£49.50 per 100,000

Rechargeable Batteries

AA (HP7) 500 mA £0.99

AA 500mAh with solder tags £1.55

AA 700 mA £1.75

C (HP 11) 1.2AH £2.20

C 2AH with solder tags £3.60

D (HP2) 1.2AH £2.60

D 4AH with solder tags £4.95

PP3 8.4V 110mAh £4.95

12AA with solder tags £1.55

Sub C with solder tags £1.75

AAA (HP16) 180mAh £1.75

1/3 AA with tags (philips CTV) £1.95

Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95

High power charger as above but charges the Cs and Ds in 5 hours AAAs Cs and Ds must be charged in 2s or 4s £10.95

Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) £3.75

Special offers please check for availability

stick of 4 42 x 16mm nicad batteries 171mmx16mm dia with red & black leads 4.8v £5.95

5 button cell 6V 280mAh battery with wires (Varta 5x250KD) £2.45

Shaded pole motor 240Vac 5mm x 20mm shaft 50 x 60 x 55mm excluding the shaft £4.95 each

115v ac 80v dc motor 4mm x 22mm shaft 50mm dia x 60 long body (excluding the shaft) it has replaceable thermal fuse and brushes £4.95 each £3.95 100+

7 segment common anode led display 12mm £0.45

LM337K TO3 case variable regulator £1.44 100+

GaAs FET low leakage current S8873 £12.95 each £9.95 10+ £7.95 100+

BS250 P channel mosfet £0.45, BC559 transistor £3.95 per 100

BC107 transistor 20 for £1.00

74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50

SL952 UHF Limiting amplifier LC 16 surface mounting

package with data sheet £1.95

DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output Isolation with data £4.95 each or pack of 10 £39.50

Hour counter used 7 digit 240v ac 50Hz £1.45

QWERTY keyboard 58 key good quality switches new for a box of 30 £6.00

Airpax A82903-C large stepping motor 14v 7.5 step 27cm 88mm dia body 6.3mm shaft £8.95 or £200.00

Polyester capacitors box type 22.5mm lead pitch 0.9uF 250vdc 18p each 14p 100+ 9p 1000+ 1uF 250vdc 20p each, 15p 100+, 10p 1000+ 1uF 50v bipolar electrolytic axial leads 15p each, 7.5p 100+ 0.22uF 250v polyester axial leads 15p each, 7.5p 100+ Polypropylene 1uF 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case 75p each 60p 100+

Philips 123 series solid aluminium axial leads 33uF 10v & 2.2uF 40p each, 25p 100+

Philips 108 series long life 22uF 63v axial 30p each 15p 1000+

Multilayer AVX ceramic capacitors all 5mm pitch 100v 100pF, 150pF, 220pF, 10,000pF (10n) 10p each, 5p 100+, 3.5p 1000+

500pF compression trimmer 60p

40 uF 370vdc motor start capacitor (dielectric type containing no PCBs) £5.95 or £49.50 for 10

Solid carbon resistors very low inductance ideal for RF circuits

270hm 2W, 680hm 2W 25p each 15p each 100+ we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list

P.C. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for lower case) dimes 212x49x143mm excluding switch £26.00 each

£138.00 for 6

MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test

AMD 27256-3 Eproms £2.00 each, £1.25 100+

DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+

Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £49.50 for 10

Hand held ultrasonic remote control £3.95

CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100

Varbatim R300NH Streamer tape commonly used on nc machines and printing presses etc. it looks like a normal cassette with a slot cut out of the top £4.95 each (£3.75 100+)

Heatsink compound tube 95p

HV3-2405-E5 5-24v 50mA regulator ic 18-264vac input 8 pin DIL package £3.49 each (100+ £2.25)

LM 555 timer ic 16p, 8 pin DIL socket 6p

All products advertised as new and unused unless otherwise stated. Wide range of CMOS TTL 74HC, 74F Linear Transistors kits, rechargeable batteries capacitors tools etc. always in stock.

Please add £1.95 towards P&P, vat inc. in all prices

JPG ELECTRONICS

ETI 276-278 Chatsworth Road,
Cheshamfield S40 2BH
Access Visa Orders (01246) 211202 fax 550959
Callers Welcome 9.30am-5.30pm Monday-Saturday

Visible Sound Limited

The following features apply to all our PC control cards:

Standard 8 bit ISA, base address fully selectable via dip switches, Installation instructions, application notes, circuit schematic and software examples in 'C', BASIC and assembler (on 3.5" floppy disk). All connections to the cards made via a standard 25 way female D-type connector on the end plate.

£29 H134A 24 Digital I/O's

Fully programmable TTL level digital I/O's based around the 8255. Kit K134A £27

£35 H130A 8 Channel Relay

Completely isolated programmable relay output card. 3 contacts available per channel, NO, NC and C. Contacts rated 1A @ 30v DC. (Readback feature). Kit £32

£35 Isolated I/O

For ultimate protection this virtually indestructible card offers 8 opto isolated inputs and 4 relay outputs. 5v H131A, 12v H132A, 24v H133A. Kits 5v K131A, 12v K132A, 24v K133A £32

A057A M/M 25 way cable

A058A M/F 25Way cable

£6 each

ALL Prices INCLUSIVE of vat and delivery (UK Only) Same day despatch.

151-s, The Exchange Building, Mount Stuart Square, Cardiff, CF1 6EB.
Tel (01222) 458417 Fax (01222) 625797 http://www.vsltec.demon.co.uk

Voice Command Module H138A

Based on the Sensory Devices RSC neural network recognition processor. Simply train this stand alone module with up to 40 words, giving you 99% speaker dependant recognition. 20 individual digital word ID outputs or IDC header. Automatic gain control on microphone jack input. Runs off 9-12vdc dc supply via 2.1mm plug

£55

H136A £33 Stepper motor

driver: Directly controls two 4 phase stepper motors whilst providing 8 optically isolated general purpose inputs. Ideal for implementing 2 channel positional control loops. Suitable motors and connector cables available. Kit K136A £30

H137A Pic Program-£25 mer: Programs

PIC16C17, PIC16C84 and the new 8 pin PIC12C508 and PIC12C509. Connects to parallel port. Kit K137A £24

PC compatible software F.O.C. when supplied with programmer.

12C508/JW £13.50, 12C508-04/P £2.30

12C509/JW £15, 12C509-04/P £2.70

16C71/JW £25, 16C17-04/P £6.99


16C84-04/P £6



CHELMEYER VALVE COMPANY

If you need Valves/Tubes or RF Power Transistors etc. ...then try us!

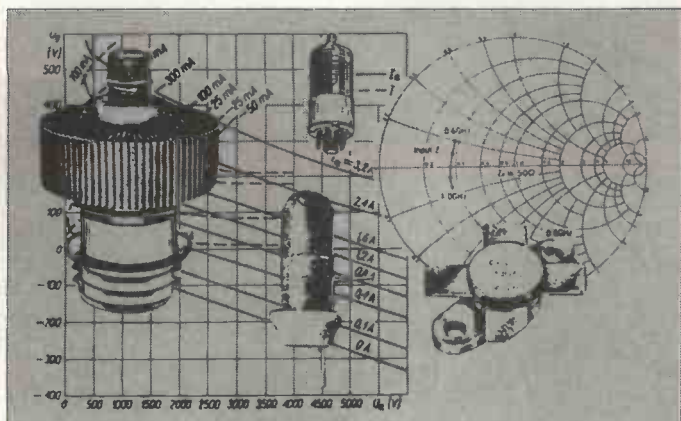We have vast stocks, widespread sources and 35 years specialist experience in meeting our customers requirements.



Tuned to the needs of the Radio Amateur

Chelmer Valve Company, 130 New London Road,
Chelmsford, Essex CM2 0RG, England.

Tel: 44-01245-355296/265865

Fax: 44-01245-490064

LASERS

Argon ion / Helium Neon / Diode / Carbon Dioxide

Colours include red, yellow, green, turquoise, blue and infra-red. Output powers range from 0.2mW to over 20 Watts. Applications include research, light shows, image projection, medical or industrial. New and Second hand. Pictured here is a 50mW cyan/blue argon ion air cooled laser head and a miniature 1mW red HeNe laser tube only 147mm long. Second hand blue (488nm) argon ion lasers start from only £100 + VAT.



LASERTECH

Mill Road, Great Barton, Bury St. Edmunds, Suffolk, IP31 2RU
Telephone 01284 788108 Fax 01284 788135



Major Lab Clearance, so Quality Test Equipment by HP, TEK, Marconi, Gould, etc. Lots of Scopes, PSU's, Logic Analysers, Micro Development Sytem, 50-75GHz Sig Gen, Microwave Items. Good prices, eg HP1740 100MHz scope for £330.

Also Bargain list of special interest items, eg Valve PSU, Valve 'Scope with Spectrum Analyser, AVO, etc.

Write or Phone for Lists : 0116 2717516

1 Brocks Hill, Close, Oadby, Leicester, LE2 5 RB.


PS VAT FREE ZONE. !

ETI


ELECTRONICS
TODAY INTERNATIONAL

TOMORROW'S TECHNOLOGY TODAY

FOILS FOR THIS ISSUE

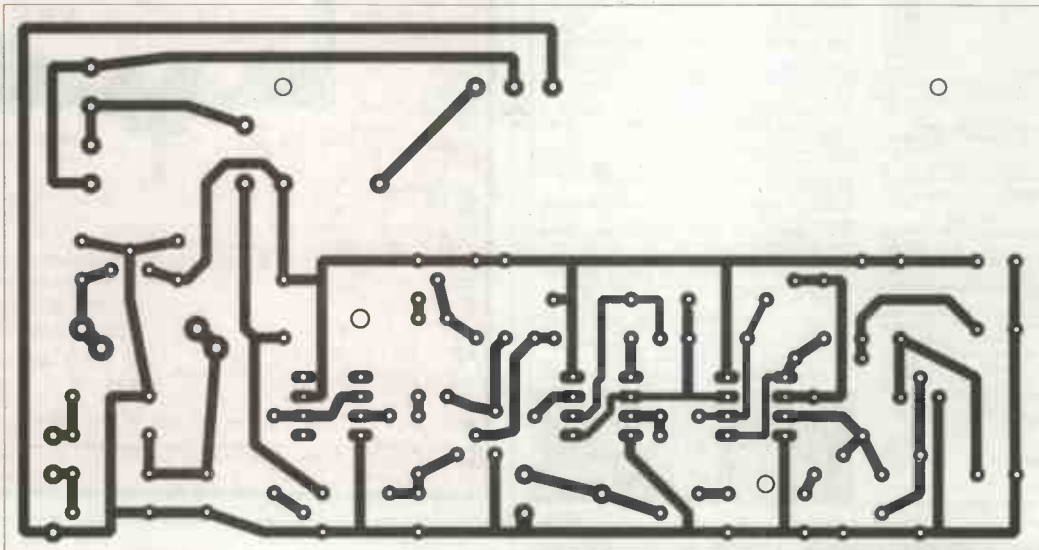


PYRO ACTIVATED LIGHT SWITCHER

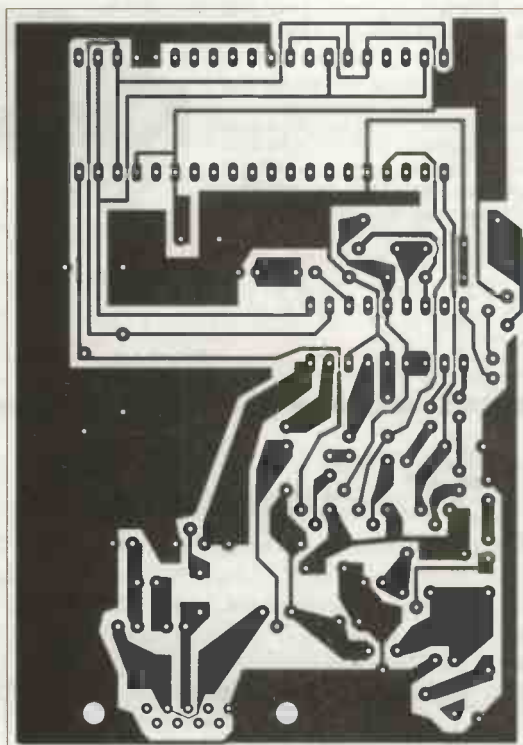

ETI PIC PROGRAMMER



MOISTURE METER

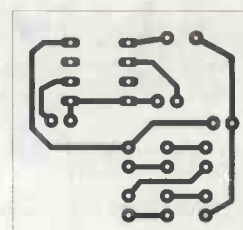

CONTINUITY QUICK-TESTER

T.I.S.

2 John Street, Larkhall, Lanarks, ML9 1HE
Tel: 01698 883334 / 884585 Fax: 884825
Send a S.A.E. for your **FREE** Catalogue & Quote.

T.I.S.

Unconditional replacement or refund on any item if not as requested

TOP SELLING BOOKS

Pract' TV or VCR Repairs-£16.95 (Both £30)
Buy/Sell/Serv/Repair Used Equipment :-
CD, TV or VCR - £10.95 each (All 3 £27)
6 Giant IC Ref' Manuals - £12.95 each
Data Ref' Guide - Identifies/ prices/ cross-refs
data for most models - £9.95 (3.5" Disk £5)
Microwave Energy & Ovens - £9.95
3.5" Disk Drives - £9.50
The Giant Fault-Finding Guides:-
CTV's £16.95/ VCR's £16.95



SERVICE MANUALS



DESIGNER COLLECTIONS

Comprehensive Circuits Collections of any make of CTV
as requested, prices from £8 to £49 (IE. Alba/Bush £20) Full
list in Free Catalogue.

Amateur Kit: 10 Service Manuals (as needed), Data Ref',
Pract' TV & VCR Repairs, Radio Repairs, Thorn Serv' Set &
any 3 CTV Circ Collections. **£199**

Professional Kit: As above + 10 Serv' Man's, Microwave
E&O, Buy/Sell/Serv' Collection & 2 More CTV Circ's. **£370**

3 UNIQUE SERVICE MANUAL OFFERS GUARANTEED SAVINGS TO YOU **NOW!!**

*LIBRARY Joining fee £65.00

You receive any Service Manuals, no matter
how expensive, for £10 each, and you get a £5
credit for any you return.

*PRE-PAY MANUALS

You get 20 Service Manuals, as and when you
need them; as many or few at a time as you
want, for a one-off payment of £185.

*SERVICE MANUAL EXCHANGE

If you have a Service Manual we don't have
and need another manual (ie. TV for TV, VCR
for VCR), we will exchange it for FREE.

Please add £2.50 to all orders to cover Postage & Handling

WORLD'S LARGEST SERVICE MANUAL COLLECTION

Normal Prices Given (Some Manuals may be Cheaper or more Expensive)



VCR/VIDCAM - FULL MANUALS £16.50 - CIRCUITS £8.00 COMPLETE
CTV's / CD's - FULL MANUALS £12.50 - CIRCUITS £6.00 COMPLETE



AUDIO, CD, COMPUTERS, MONITORS, DOMESTIC / TEST EQUIP', ETC.. FROM £4.00

SEETRAX CAE RANGER PCB DESIGN WITH COOPER & CHYAN AUTOROUTER

RANGER2 + SPECCTRA £400.00

RANGER & SPECCTRA AUTOROUTER
Together giving the most cost effective
PCB design system on the market TODAY!
SEETRAX'S ease of use combined with
COOPER & CHYAN'S renowned gridless
autorouter, at an outstanding price.

R2 Outputs: 8/9 & 24 pin printers, HP
Desk & Laser Jet, Cannon Bubble Jet,
HP-GL, Gerber,
NC Drill, AutoCAD DXF
Demo Disk available at £5.00 +VAT

RANGER2 £150

Up to 8 pages of schematic linked to artwork
Gate & pin swapping - automatic back annotation
Copper flood fill, Power planes, Track necking,
Curved tracks, Clearance checking,
Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)
Gerber-in viewer, AutoCAD DXF in & out



UPGRADE YOUR PCB PACKAGE TO RANGER2 £60

TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG
Call 01705 591037 or Fax 01705 599036 + VAT & P.P

All Trademarks Acknowledged

FOILS FOR THIS ISSUE

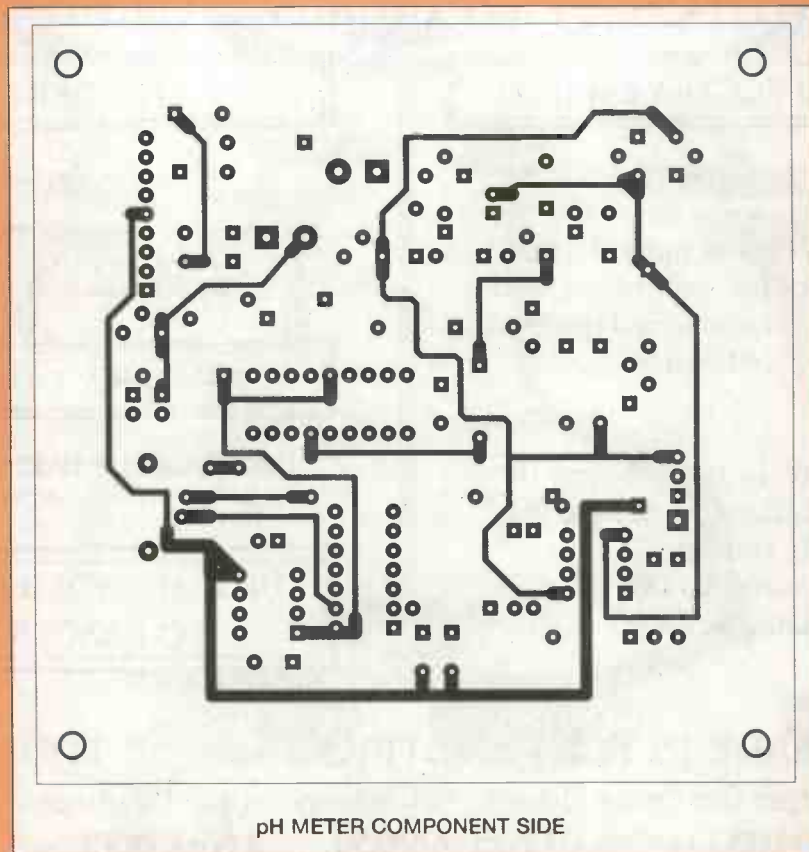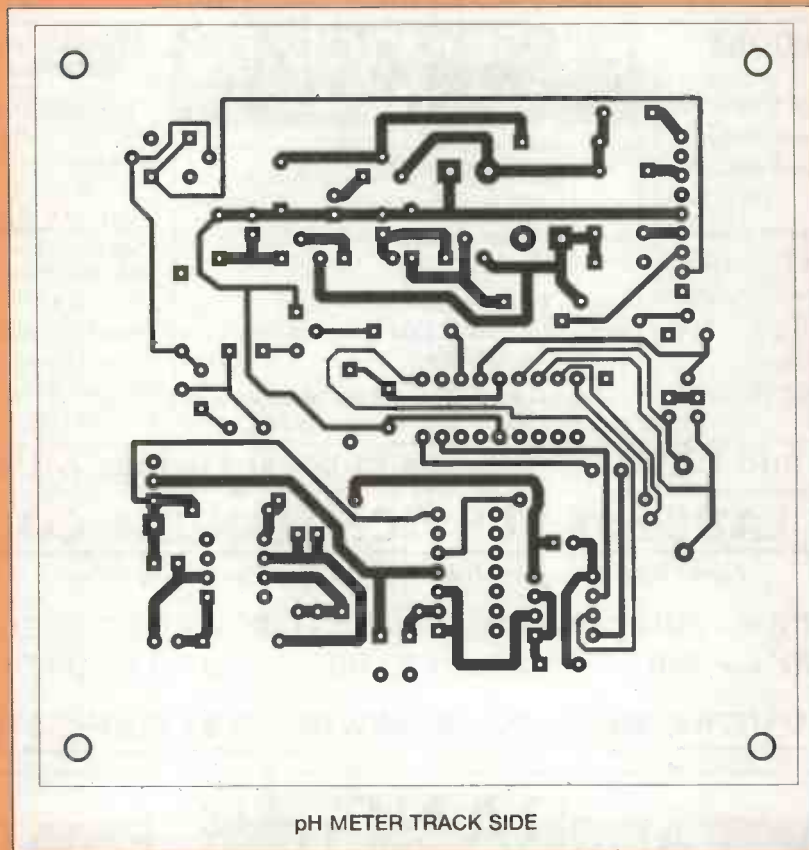

Robotica Ltd



Robotic Arm Kits

TOYBOT - EDUBOT

5 Axis open Kinematic Robotic arm kits with superb precision

CNC machined parts, PC controlled with

WINDOWS Software and fully programmable.

Can be interfaced with four external devices or other robots.

PIC Servo Controller

Controls up to 8 Servo

Fully Addressable

features two in and out ports

for interfacing

with up to 4 external devices

or other controllers

Phone for a brochure and price list



Robotica
Ltd

3 PARK GATE, GLASGOW, G3 6DL

TELEPHONE: +44 141 353 2261

FAX: +44 141 353 2614

SERVICE MANUALS & Technical Books

Available for most equipment, any make, age or model.

Return the coupon for your FREE catalogue

MAURITRON TECHNICAL SERVICES (ETI)

8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY,

Tel: -01844-351694, Fax: 01844 352554 email: - mauritron @ dial.pipex.com

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps, or £4.11 inc. vat for the complete Service Manuals Index on PC Disc plus catalogue.

NAME _____


ADDRESS _____

POSTCODE _____

Photocopy this coupon if you do not wish to cut the magazine

ROBOTICS!

NEW!
from the USA

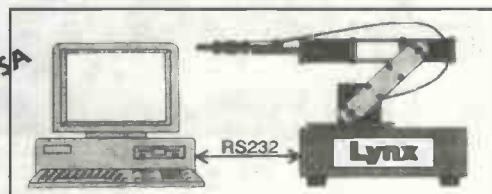


LYNX ARM

ROBOTIC ARM Kit, five axis motion with gripper. Control from any serial port. Uses R/C servos for good repeatability and accuracy. Kit includes pre-cut arm components, electronics controller board, PC software (inc source listing) and detailed construction manual. 40x30x20cm.

STAMP BUG

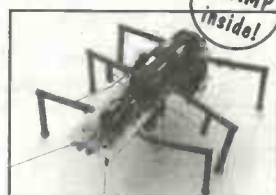"STAMP" based insect kit illustrates basic walking mechanisms. Twin feelers detect objects causing back-up and turn. Pre-programmed but with the option to re-programme (needs Stamp programming pack). Powerful 3 servo construction carries payloads up to 250gms and up to 3 hours motion from the on-board NiCads. 20x15x5cm



MUSCLE WIRES

Fascinating wires that **CONTRACT WHEN ELECTRICALLY HEATED** producing a useful amount of force (Up to 0.9kgf for 250µm wire). Require 0.3 V/cm and currents from 100ma to 1Amp. Choose from four gauges of wire (50,100,150 and 250 µm dia) Detailed Data and Project Book (128 pages) also available separately and with Delux Wire kit suitable for 13 projects

SERVO - IR - LCD CONTROLLERS

A range of low cost controller kits: **R/C servos** (up to 8 servos per board- simple RS232 commands from your PC hold servo in position until updated etc). **LCD display drivers** (All standard Hitachi controller types up to 4x20 characters- RS232 input) **IR programmable receivers** (7 output channels - accept any TV/HiFi controller- up to 25mA output per channel- programmable toggle/momentary switching action)

Please call to receive further details on any of the above products

MILFORD INSTRUMENTS

Creative Products for Enquiring Minds
01977 683665, Fax 01977 681465

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your choice.

Electrical Contracting & Installation
Electrical Engineering
C&G/ICS Basic Electronic Engineering
C&G/ICS Basic Mechanical Engineering
TV and Video Servicing
Radio and Hi-Fi Servicing
Refrigeration Heating & Air Conditioning
Motorcycle Maintenance

FREEPHONE 0500 75 73 75

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydesway Skypark, Glasgow, G3 8BR. Tel. 0500 75 73 75 or Tel/Fax: Ireland 01 285 2533.


Please send me my Free Information on your Electronics Courses.

Mr/Mrs/Ms/Miss (BLOCK CAPITALS PLEASE)	Date of Birth / /
Address	
Postcode	
Occupation	Tel. No.

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box ☐ Dept. ZETH230597



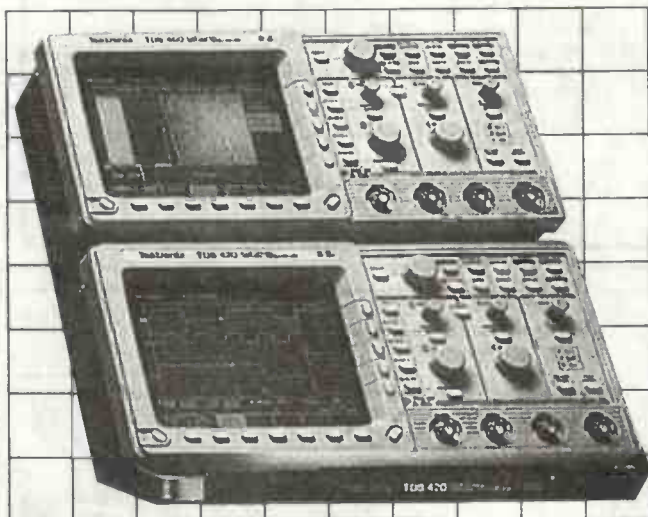SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0HD U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CATALOGUE AVAILABLE



OPERATING & SERVICE MANUALS



CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0HD U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CATALOGUE NOW ALSO AVAILABLE ON DISK



STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the
Electronics Industry

Do you have a requirement for any of the following services:

PCB Assembly (Conventional and
Surface Mount)
Wave & Hand Soldering
Complete Equipment
Manufacture
Device Programming from hand
written shts or PC 3 1/2" disc
Cable Harness Assembly/loom
Manufacture
Card Cage and Module Wiring
Full Inspection

Product Design/Consultation
Full Procurement Service
PCB Test & "Burn in" Facilities
Enclosure Design & Manufacture
PCB Artwork Manufacture
Circuits Drawn Professionally
Kit Procurement & Supply
Component Sales
Refurbishment a speciality
Top Quality Work at Reasonable
Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us
on (01438) 352742

EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

Printed Circuits in Minutes Direct From LaserPrint!

8 1/2" x 11"

* Or Photocopy

**Use standard

household iron

or P-n-P Press.



1. LaserPrint*

2. Press On**

3. Peel Off

4. Etch

Use Standard Copper Clad Board

5 Sheets £12.50, 10 Sheets £25.00 + VAT. Add £2.50 postage
Complete kits to manufacture your own PCB's from £40.00, or individual
items of material, chemicals, etchant etc.

PRESS-N-PEEL ETCHING SUPPLIES

18 Stapleton Road • Orton • Southgate
Peterborough PE2 6TD • Tel: 01733 233043

ADVERTISERS INDEX

ARRAN TECHNOLOGY	65	NO1 SYSTEMS	22
BK ELECTRONICS	17	NO NUTS	59
BULL ELECTRICAL	10, 12	OLSON	IBC
CMS	59	OMNI ELECTRONICS	60
CHELMER VALVE	65	PDSL	72
COOKE INTERNATIONAL	70	P H HAGAR	73
COLES HARDING AND CO	72	PARTRIDGE ELECTRONICS	59
DISPLAY ELECTRONICS	19	PLANCENTRE PUBLICATIONS	72
EPT EDUCATIONAL SOFTWARE	24	PICO TECHNOLOGY	21
ELECTROMAIL	38	PRESS AND PEEL	70
EQT	70	QUICK ROUTE SYSTEMS (POWERWARE)	IFC
ESR COMPONENTS	28	ROBINSON MARSHALL	IBC
F.K. ELECTRONICS	72	ROBOTICA	69
FOREST ELECTRONICS	35	SCIENTIFIC WIRE COMPANY	72
GRANDATA	4, 5, 6, 7	SEETRAX	67
GREENWELD ELECTRONICS	48	SERVICE TRADING CO	72
ICS	69	STEWART OF READING	60
JJ COMPONENTS	38	TECHNICAL EDUCATION INDEX	60
JPG	65	TECHNICAL INFORMATION	67
J+N FACTORS	72	TELNET	33
LASERTECH	38, 65	VAN DRAPER	38
MAURITRON	69	VARIABLE VOLTAGE TECHNOLOGY	72
MILFORD INSTRUMENTS	69	VERONICA FM	72
NICHE SOFTWARE	48	VISIBLE SOUND	65
		WILSON VALVES	73

ETI Contents Index - 1995

This index is divided into two sections: Technical and Construction, which features all articles on a constructional project or containing construction-related information, and Features, which contains our leading topic features and shorter features.

Technical and Construction

16-channel MIDI mixer	Oct 1995
80188 SBC - 4 channel touch switch interface	Jun 1995
80188 SBC - serial ADC for virtual instrumentation (Part 1)	Jul 1995
80188 SBC - serial ADC for virtual instrumentation (Part 2)	Aug 1995
80188 single board computer (Part 2)	Feb 1995
80188 single board computer (Part 3)	Mar 1995
80188 single-board computer (Part 1)	Jan 1995
8088 interrupt-based single board computer - single-stepping	Nov 1995
8088 interrupt-based single board computer	Sep 1995
8088 interrupt-based single-board computer	Aug 1995
Active Guitar Electronics	Feb 1995
Alarming Ideas - a collection of devices mainly for PC security	Feb 1995
Analogue shutter timer for cameras	Aug 1995
Bar-code reader for the PC	Dec 1995
Basic microcontroller (Part 1)	Oct 1995
Basic microcontroller (Part 2)	Nov 1995
Basic microcontroller (Part 3)	Dec 1995
Basic microcontroller (Part 4)	Jan 1996
Basic microcontroller (Part 5)	Feb 1996
Basic microcontroller (intro)	Sep 1995
Bat simulator and sound detector	May 1995
Bicycle loop alarm	Jun 1995
Child's night light (low power)	Oct 1995
Computer controlled SMART mains control system	Feb 1995
Computer controlled SMART mains control system	Mar 1995
Computerised radio control	Nov 1995
Computing without clocks	Jul 1995
Designing a PIC micro-based project (Part 1) with alarm clock	Jul 1995
Designing a PIC micro-based project (Part 2) with alarm clock	Aug 1995
Designing a PIC micro-based project (Part 3) with alarm clock	Sep 1995
Designing a PIC micro-based project (Part 4) with alarm clock	Oct 1995
Designing a PIC micro-based project (Part 5) with alarm clock	Nov 1995
Designing a PIC micro-based project (Part 6) with alarm clock	Dec 1995
Dry battery tester	Sep 1995
Electronic cycle alarm	Dec 1995
Eprom programmer, portable	Apr 1995
Fibre optic MIDI link	Sep 1995
Fibre optic transceiver for computers and peripherals	Jul 1995
Garden shed alarm (Part 1)	Mar 1995
Garden shed alarm (Part 2)	Apr 1995
General Purpose RS232 Card with 24 lines I/O (Part 1)	Dec 1994
General Purpose RS232 Card with 24 lines I/O (Part 2)	Jan 1995
Laser Tag game - Large scale displays (last part)	Jul 1995
Laser Tag game - light gun base (Part 2)	Apr 1995
Laser Tag game - light gun control	Jun 1995
Laser Tag game - light gun control (Part 3)	May 1995
Laser Tag game - the Gunman	Mar 1995
Laser Tag game (Part 1)	Mar 1995
Message Pad "Hello Mum"	Sep 1995
Metal effects unit	Jan 1995
Mobile robot	Apr 1995
Multi-checker for home and car	Aug 1995
Multi-core cable tester	Aug 1995
NiCad battery charger	Apr 1995
Noise masker	Dec 1995
Opto-compressor gain control for public address systems	Feb 1995

Parallax Basic Stamp - making servos work for you	May 1995
Parallax Basic Stamp - applications for the pulse command	Jul 1995
Parallax Stamp - building a serial relay controller for PC	Sep 1995
Parallax Stamp - LCD based mini terminal	Apr 1995
Parallax Stamp - signal processing	Jun 1995
PCW I/O port	Mar 1995
PIC programmer	Jul 1995
PIC programmer	Jun 1995
Programmable packer timer 3-digit, using a PIC	May 1995
Solid state darkroom safelight	Jan 1995
Switch regulators (Part 1)	Jun 1995
Switch regulators (part 2)	Jul 1995
The Parabender (Part 1) parametric EQ	Dec 1994
The Parabender (Part 2) stereo EQ	Jan 1995
The Raydor (Part 1)	Feb 1995
The Raydor (Part 2)	Mar 1995
Timed mains isolating switcher	Dec 1995
Touch test continuity tester	May 1995
Twinkling star	Jan 1995
Using eproms (Part 1) : proms vs logic	Dec 1994
Using eproms (Part 2)	Jan 1995
Using PIC micros on the Arizona Microsystems PIC controller	Feb 1995
Using the PC Parallel Port	Jun 1995
Versatile bench power supply (Part 1)	Oct 1995
Versatile bench power supply (Part 2)	Nov 1995

Features

Analysing light (feature)	Apr 1995
DC and electronically commutated electric motors	Aug 1995
Driving into the Future	Nov 1995
Electron Microscopy	Oct 1995
Electronics and the Internet	Jan 1995
Electronics in Medicine	Feb 1995
Interactive digital TV	Aug 1995
Movie Technology	Apr 1995
Nickel Metal Hydride Batteries	May 1995
Parallax Stamp review - small, low-cost control computer	Apr 1995
PC Clinic - installing sound cards	Apr 1995
PC Clinic - maintaining personal computers	Jan 1995
PC Clinic - sound boards and CD rom drives	Feb 1995
PC Clinic	Mar 1995
Shape Changing Robots	Dec 1995
Shape Memory Alloys	Jun 1995
Solar Panels ("Something for Nothing?")	Oct 1995
TEC 200 on trial - PCB-making kit/method	Jul 1995
The Ariane 5	Sep 1995
The Virtual World	May 1995
Uncovering Saturn's Secrets	Jun 1995
Walking insect robots	Mar 1995

Back issues and copy articles

Recent backissues of ETI can be obtained from Back Issues, Readers' Services Department, Nexus Special Interest, Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST £3.05 per issue.

Send enquiries about copies of articles from older issues, with details of the title, month and year of the article, to the Photocopying Service, Readers Services Department, Nexus Special Interest, Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST, priced £3.50 for the first article or part article, £3.00 per article thereafter. Postage and handling in the UK £1.00. Overseas plus 30 per cent, £1.50 minimum carriage. A search fee of £3.50 will be applicable where all details of name and location of the article are not included. Please contact the Nexus Readers Services Department if you need help.

ETI Classified



Andy Forder
01442 66551

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 75p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£10.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

Price P&P
PANEL MOUNTING

0.5KVA 2.5 amp max	£33.00	£6.00 (£45.83 inc VAT)
1KVA 5 amp max	£45.25	£7.00 (£61.39 inc VAT)
SHROUDED		
0.5KVA 2.5 amp max	£34.00	£6.00 (£47.00 inc VAT)
1KVA 5 amp max	£46.25	£7.00 (£62.57 inc VAT)
2KVA 10 amp max	£65.00	£8.50 (£86.36 inc VAT)
3KVA 15 amp max	£86.50	£3.50 (£111.63 inc VAT)
5KVA 25 amp max	£150.00	Plus Carriage & VAT
10KVA 45 amp max	£300.00	Plus Carriage & VAT
6KVA 3 PHASE Star	£205.00	Plus Carriage & VAT

Buy direct from the Importers. **KEENE'S** prices in the country
COMPREHENSIVE RANGE OF
TRANSFORMERS-LT-ISOLATION & AUTO
(110-240V Auto transfer either cased with American socket and
mains lead of open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt £14.00 (callers only)	£16.45 inc VAT
2ft 20 watt £9.00 (callers only)	£10.50 inc VAT
12in 8 watt £4.80 + 75p p&p	£5.52 inc VAT
9in 8 watt £3.96 + 50p p&p	£5.24 inc VAT
6in 4 watt £3.96 + 50p p&p	£5.24 inc VAT

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.05 + £1.40
p&p (£8.75 inc VAT)
The above Tubes are 3500/4000 angstrom (350-
400nm) ideal for detecting security markings, effects
lighting & Chemical applications.
Other Wave Lengths of U.V. TUBE available for
Germicidal & Photo Sensitive applications.
Please telephone your enquiries.

400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use
with a 400W P.F. Ballast
Only £38.00 + £4.00 p&p (£49.35 inc VAT)



12V D.C. BILGE PUMPS

500 GPH 15ft head 3 amp £15.98
1750 GPH 15ft head 3 amp £34.55
Also now available 24V D.C. 1750 GPH 15ft head
5 amp £35.55. All designed to be used
submerged. PRICES INCLUDE P&P & VAT

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses etc.
Approx 16 joules. Adjustable speed £50.00 + £3.00 p&p
(£2.28 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)
SAE for further details including Hy-Light and
Industrial Strobe Kits.



SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
TEL 0181-995 1560 FAX 0181-995 0549
ACCOUNT CUSTOMERS MIN. ORDER £10



Ample
Parking Space

SOFTWARE

PC ELECTRONIC, TECHNICAL AND SCIENTIFIC PROGRAMS LOW COST SPECIALIST LIBRARY

DESCRIPTIVE CATALOGUE AVAILABLE
PRICED AT £2.50. COMES WITH £2.00 OFF
MONEY VOUCHER TO PLACE AGAINST
YOUR FIRST ORDER.

PHONE/FAX FOR YOUR CATALOGUE FROM
PDSL, WINSOMBE HOUSE, BEACON ROAD,
CROWBOURGH, SUSSEX TN6 1UL
TEL 01892 663298 FAX 01892 667473

PLANS

ELECTRONIC PLANS, laser
designs, solar and wind
generators, high voltage teslas,
surveillance devices, pyrotechnics
and com-puter graphics tablet. 150
projects. For catalogue, SAE to
Plancentre Publications, Unit 7,
Old Wharf Industrial Estate,
Dymock Road, Ledbury,
Herefordshire, HR8 2HS.

5KVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise
Suppression, Ultra Isolation Transformer with terminal
covers and Knock-out cable entries. Primary 120/240V
Secondary 120/240V 50/60 Hz. .005 pF Capacitance.
Size L 37 x W 19 x H 16cm Weight 42 Kilos. PRICE
£120.00 + VAT
ex-warehouse. Carriage on request.

24V DC SIEMENS CONTACTOR

Type 3TH8022 DB 2 x NO and 2 x NC 230V AC 10A
contacts Screw or Din Rail fixing. Size H 120 x W 45 x
0.75mm. Brand New Price £7.63 incl. P&P and VAT.

240V AC WESTOOL SOLENOIDS

TT2 Mod 1 flat. 1 MAX stroke 1/4 in. Base mounting 1/2in.
stroke 5lbs pull approx. TT6 Mod 1 Rat. 2 Max stroke 1/8
in. Front mounting 1/2in. Front mounting 1/2 in. stroke
15lbs pull approx. Price incl. p&p & VAT. TT2 £5.88, TT6
£8.81. SERIES 400 £7.64.

AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low
Noise fan. Price £7.29 incl. P&P and VAT. Other voltages
and sizes available from stock. Please telephone your
enquiries.

INSTRUMENT CASE

Brand new Manuf. by Imhof L31 x H18 x 19cm deep.
Removable front and rear panel for easy assembly of
components. Grey finish complete with case feet.
PRICE £16.45 INCL. P&P & VAT 2 off £28.20 Inclusive.

SEWING MACHINE MOTOR

Brand new 220/240V AC/DC SEW-TRIC 2 lead Brush
Motor. Size L. 100mm x H. 70mm x W.55mm. Spindle,
1/4in. dia x 1in. long. £14.10 incl. P&P & VAT

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC Input
Including capacitor and transformer for 240V AC
operation.
Price Inc VAT & p&p £27.73

SOLID STATE EMT UNIT

Input 230/240V AC, Output approx 15KV. Producing 0.8mm
spark. Built-in 10 sec timer. Easily modified for 20sec, 30
sec to continuous. Designed for boiler ignition. Dozens of
uses in the field of physics and electronics, eg supplying
neon or argon tubes etc. Price less case
£8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the
price of a made-up unit kit of parts less case includes 12in
8 watt 2537 Angstrom Tube Ballast unit, pair of bi-pin leads,
neon indicator, on/off switch, safety microswitch and
circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP

Brand new 240V AC, fan cooled. Can be used for a variety
of purposes. Inlet 1 1/2in. outlet 1 in. dia. Price includes p&p
& VAT. £11.20 each or 2 for £20.50 inclusive.

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE
TINNED WIRE SILVER
PLATED COPPER WIRE
SOLDER EUREKA WIRE
NICKEL CHROME WIRE
BRASS WIRE LI TZ WIRE
BIFILAR WIRE MANGANIN
WIRE TEUFEL WIRE NICKEL
SAE BRINGS LIST 18 RAVEN
RD LONDON E18 1HW
FAX 0181 559 1114

£50 BT INSTRUMENT FOR ONLY £7.50

We refer to the BT insulation tester and multi-meter with which
you can read insulation directly in megohms, AC volts up to 230,
4 ranges of DC volts up to 500, 3 ranges of milliamperes and one
SA range and 3 ranges of resistance. These are in perfect
condition, have had very little use, if any, tested and fully
guaranteed. Complete with leads and prods £7.50, Order Ref
7.5P4. Carrying case which will take small tools as well. £2 extra.
Postage £3 unless your order is £25 and over.

J & N Factors

Dept ETI, Pilgrim Works, Stairbridge Lane, Bolney,
Sussex, RH17 5PA
Telephone: (01444) 881965



88-108MHz FM TRANSMITTERS

Professional PLL transmitter, Stereo Coder, and
Compressor/Limiter kits licensable in the U.K.
Also very stable VFO transmitter kits. Prices
from under £10 and a 'Ready Built' service is
available. Contact us for a free brochure
including prices and more detailed information.

18 Victoria St, Queensbury, BRADFORD, BD13 1AR
Tel 01274 816200 Email veronica@legend.co.uk



TELEPHONE BUGGING?

"STOP IT NOW!!" WITH THE NEW BUG X TERMINATOR.

Blocks all phone taps &
telecoders, keeps phone
calls and fax's private.
For details send a S.A.E. or
Tel/Fax: Write for details with
S.A.E. to: F.K.Electronics
services, Northgate house, St.
Marys Place, Newcastle Upon
Tyne, NE1 7PN.
Tel: 0191 4601706
Fax: 0191 4601707.

TRANSFORMERS

Variable Voltage
Technology Ltd

TRANSFORMERS

For valve and transistor circuits
HT Filament chokes high & low voltage
Standard and custom design
large and small quantities
Unit 24E, Samuel Whites Estate, Medina
Road, Cowes, Isle of Wight PO31 7LP
Tel 01983 280592 Fax 01983 280593

**Call Our Friendly
Sales Team on
01442 66551
& ask for details**

TURN YOUR SURPLUS
TRANSISTORS, ICS ETC INTO
CASH immediate settlement.

We also welcome the opportunity to quote
for complete factory clearance

Contact:

COLES-HARDING & CO

Unit 58, Queens Road, Wisbech,
Cambs PE13 7PO
BUYERS OF SURPLUS INVENTORY
ESTABLISHED OVER 20 YEARS
Tel: 01945 584188 Fax: 01945 475216

Professional AUDIO TRANSFORMERS

FREE 16 PAGE CATALOG AVAILABLE
Fax Toll-Free 0800-96-7106

SESCOM, INC. sescom@amv.net
2100 WARD DR., HENDERSON, NV 89015
Tech Line 702-565-3993 (weekdays 8 am - 4 pm PST)
Office 702-565-3400 Fax 702-565-4828

**FAX
your advert
to us on
01442 66998**

ELECTRONIC VALVES

KITS


PRINTED CIRCUIT BOARDS



WILSON VALVES

(PROP JIM FISH G4MH)

Over 50,000 valves stocked,
2000 different types,
vintage, military, audio, etc.
Fast service. Send SAE for list
VALVES WANTED FOR CASH
28 Banks Avenue, Golcar, Huddersfield,
West Yorks HD7 4LZ
Tel: 01484 654650
Fax: 01484 655699

SMARTCARD READER/WRITER KIT

Connects to PC serial port.
Full kit of parts £30, including instructions,
extensive application software & UK postage.
Many other kits available, please send for details
to:- P. Clark, PO Box 197, Portsmouth,
Hampshire, PO2 7YX,
or e-mail p.clark@bigfoot.com

PRINTED CIRCUIT BOARDS

Designed & Manufactured

- Prototype or Production Quantities
 - Fast turnaround available
- PCBs Designed from circuit diagrams
 - Almost all computer files accepted

Easy PC / Arles / VtuTrax / Cadstar Gerber / HPGL / iDraw and many others.

- Fast International service
- Contract Assembly & Test available

TELEPHONE 01432 473533
INTERNATIONAL +44 1232 473533

 **agar** **FAX - 01232 473533**
Circuits **Email - agar@argonet.co.uk**

36 WOODCOT AVENUE, BELFAST BT5 5JA

Try Me!

For PCB's,
One offs and low quantities.
High quality at low cost.
For details send SAE to:
33 Lennox Gardens,
Linlithgow, West Lothian.
EH49 7PZ.

**TO ADVERTISE WRITE TO OUR
CLASSIFIED DEPARTMENT AT
NEXUS SPECIAL INTERESTS,
NEXUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD, HERTS HP2 7ST.
OR TELEPHONE 01442 66551
OR FAX US ON 01442 66998**



**ELECTRONICS TODAY INTERNATIONAL,
CLASSIFIED ADVERTISEMENT DEPARTMENT,
NEXUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

All adverts must be prepaid.
Cheques payable to:
Nexus Special Interests Ltd.

Name

Address

Daytime Tel. No:.....

Signature

Date

PLEASE DEBIT MY ACCESS/BARCLAYCARD No.

[illegible]

Expiry Date

FOR SALE COMPONENTS PLANS OTHER – PLEASE STATE

Please ring the required heading.

£25.85
inc vat

£19.97
inc vat

£39.95
inc vat

£30.55
inc vat

Around the Corner



This issue reports the results of the Young Electronic Designer of the Year Awards. YEDA is for full time students, mainly from the electronics disciplines, and it lays

some fairly strict criteria for entrants: originality; technical competence and reliability; sound construction (and presentation); usefulness; and commercial feasibility. The young designers must consider who is going to use their design, and how practical it will be to operate. They must think about the cost of construction, where the parts are to come from, and how best to package and promote it to the eventual user. People from age 12 to 25 are encouraged to work in teams or as individuals to look at all aspects of electronics design and come up with something of their own. It is a fine and encouraging effort and a credit to the students and the sponsors, Mercury Communications, Texas Instruments and the Institution of Electrical Engineers.

In a nutshell, most of the criteria that apply to design in the wider world are the same criteria that apply to designing and publishing a project for constructors who want to build their own devices, equipment and machinery at home.

We have a slightly easier task, in fact, because most constructors are not upset if they have to do some calibration, or if the design does not include a mega-matt machine moulded heat-sealed non-reflective front panel, or even if they have to look a bit further for a specialised part (as long as we warn them, and tell them where to start looking).

But they, too, want something that works and something that will be useful or entertaining

or just intriguing. In our fraternity there is more room for the personal design, the useful widget that sits in a corner of the bench/car/attic and does something that no-one else really needs doing (but have you asked them?) in a way that is slightly different from the commercial norm. But once you have put your efforts into making your design useful, safe, reliable and maybe (but not necessarily) even attractive - not only have you met many of the criteria that determine the winners of design awards, but you may have something that others would like to build for themselves.

(There was quite a rumpus in a nearby household when the time came to replace the insulating jacket on the hot tank and the designer-in-chief suggested chucking out the widget he had built in a tobacco tin 10 years ago to monitor the hot water level. The household had come to rely on it to avoid squabbles about the hot water running out - but no-one had told him.)

If you do, we are always pleased to hear from people who have built an original-project and are thinking of writing it up. For more information, see the small ad. on page 23, or write to the editor for our Potted Project Production sheet.

Two pieces of news: author Bob Noyes reminds us that the LM3911 replacement board published last month for the Shake'n'Etch has been designed so that it can replace the discontinued LM3911 in any normal application with minimal tweaking.

The other piece of news is that negotiations for a new ETI PCB Service are far advanced, and the new service currently looks set to begin next month.

The Challenge - Things that electronics hasn't fixed yet

I wonder if it would be possible to convert electricity to light with integrated circuits, by having a very high frequency oscillator and a microscopic antenna, and generating the light in the same way as conventional radio frequency. The laser and the LED provided part of the answer, but if you could make a nano-size transmitter and receiver for light, then an array which responded to phase and frequency suitable could, for example, function as a camera without the need for a lens. Or it could be the ultimate flat screen display, with 3D capability inherent in its functioning. But how?

Next Month...

Volume 26 no. 7 of *Electronics Today International* will be in your newsagent on 20th June 1997 ... Robin Abbott will be describing the new Universal Serial Bus PC serial standard that can address up to 127 devices and is the contender to replace RS232 in the next few years. ... A new EEPROM programmer with personality modules for different devices from Keith Wardill ... our cryptic car-alarm look-alike ... a switched sine- and square-wave generator from Robert Penfold ... another Spiced Circuit ... the results of our EdWin competition ... and more ... *Contents are in preparation but are subject to space and availability.*



Published by
Nexus Special Interests Limited
Nexus House, Boundary Way,
Hemel Hempstead, Herts HP2 7ST
Tel: 01442 66551
Fax: 01442 66998

EDITORIAL

Editor
Helen Armstrong
Administration Assistant
Lynn Bugden
Consultant
Andrew Armstrong

PRODUCTION

Designer
Dan Sturges
Technical Illustrator
John Puczynski
Production Executive (Copy control)
Marie Quilter
Printed By
Wiltshire Ltd., Bristol
Origination by
Ebony, Liskeard

SALES

Group Sales Manager
Jason Wollington
Advertisement Manager
Andrew Forder

MANAGEMENT

Divisional Managing Director
John Bridges
Business Manager
Stuart Cooke
Circulation Manager
William Pearson
Marketing Manager
Jason Doran
Copy Sales Manager
David Pagendam

SUBSCRIPTIONS

UK: Orders 01858 435344
Enquiries 01858 435322
USA: Wise Owl Worldwide Publications, 4314
West 238th Street, Torrance, CA 90505-45009
USA: For VISA/Mastercard orders phone: (310)
375 6258. Fax: (310) 375 0548. Pacific Time: 9am -
9pm weekdays 10am - 6pm weekends

READERS SERVICES

Back issues (last 12 months) £3.05 per issue if available. Older issues: photocopies of whole articles often available. Write to The Photocopy Service, Readers Services Department, at Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST.
Binders for ETI: £7.50 each including UK post and packing. Overseas please add £1.50. Cheques to Spexus Special Interest at Nexus House, or phone VISA/Mastercard orders to Readers Services Department 01442 66551




© Nexus Special Interests Limited 1997
All rights reserved
ISSN 0142-7229

The Publisher's written consent must be obtained before any part of this publication may be reproduced in any form whatsoever, including photocopies, and information retrieval systems. While reasonable care is taken in preparation of magazine contents, the publishers, editors and their agents cannot be held legally responsible for loss howsoever arising from errors or other published material.

Mix it up with Electronics Workbench®

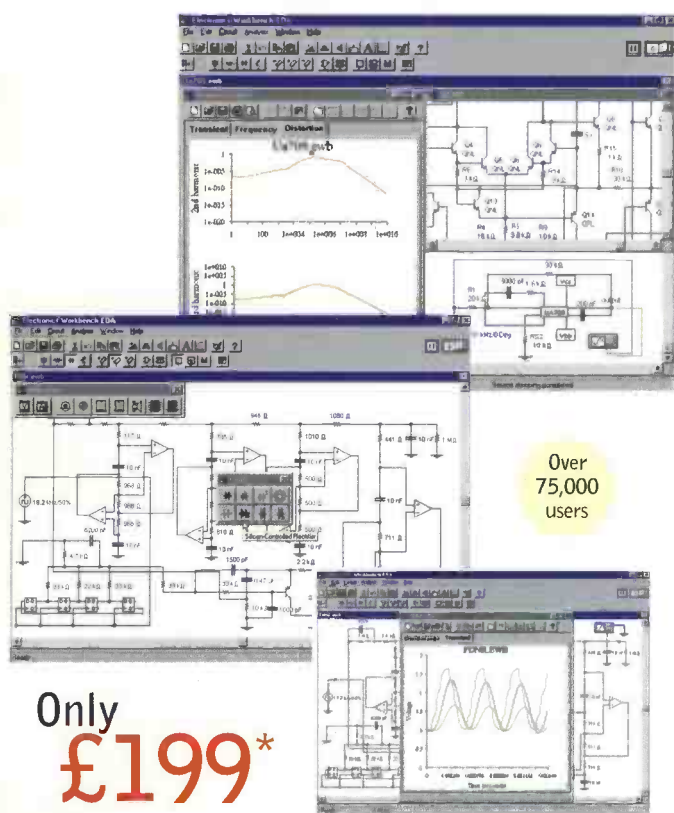The analog, digital and mixed-mode circuit simulator that really moves!



NEW! Electronics Workbench Version 5 with analog, digital and mixed A/D SPICE simulation, a full suite of analyses and over 4,000 devices. Still the standard for power and ease of use. Now ten times faster. Still the same low price.

Join over 75,000 customers and find out why more engineers and hobbyists buy Electronics Workbench than any other SPICE simulator. You'll be working productively in 20 minutes, and creating better designs faster. We guarantee it!

High-End Features

True Mixed Analog/Digital	Yes
Fully Interactive Simulation	Yes
Analog Engine	Spice 3F5, 32-bit
Digital Engine	Native, 32-bit
Temperature Control	Yes
Pro Schematic Editor	Yes
Hierarchical Circuits	Yes
Virtual Instruments	Yes
On-Screen Graphs	Yes
Analog Components	Over 100
Digital Components	Over 200
Device Models	Over 4,000
Money-Back Guarantee	30-day
Technical Support	Free

Powerful Analyses

DC Operating Point	Yes
AC Frequency	Yes
Transient	Yes
Fourier	Yes
Noise	Yes
Distortion	Yes



Turn on the power to your designs...
CALL +44 (0) 1203 233216 today!

No-risk 30-day money-back for first time buyers!

Runs on Windows 95/NT/3.1

*Special upgrade prices are available. All prices are exclusive of VAT and £7.99 p+p.



Robinson Marshall (Europe) Plc.

Leofric Business Park, Progress Close, Coventry CV3 2TF

Phone: +44 (0) 1203 233216 Fax: +44 (0) 1203 233210 E-mail: sales@rme.co.uk www.rme.co.uk

Shipping Charges UK £7.99. All prices are plus VAT. Electronics Workbench is a trademark of Interactive Image Technologies Ltd, Toronto, Canada. All other trademarks are the property of their respective owners




Australia • Belgium • Brazil • Canada • Chile • Colombia • Cyprus • Czech Republic • Denmark • Finland • France • Germany • Greece • Hong Kong • Hungary • India • Indonesia • Israel • Italy • Japan • Malaysia • Mexico • Netherlands • New Zealand • Norway • Philippines • Portugal • Romania • Singapore • Slovenia • South Africa • South Korea • Spain • Sweden • Switzerland • Taiwan • Thailand • Turkey • United Arab Emirates • United Kingdom

Trademarks are the property of their respective holders.

0497



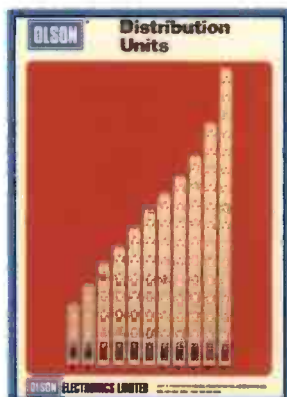**For all your Power
Distribution
Olson offer a varied
choice**



ELECTRONICS LIMITED

FOUNTAYNE HOUSE, FOUNTAYNE RD., LONDON N15 4QL
TEL: 0181-885 2884 FAX: 0181-885 2496

30% discount - 1GHz frequency meter

ELECTRONICS WORLD

Denmark DKr. 65.00
Germany DM 15.00
Greece Dra. 760
Holland Dfl. 14
Italy L. 7300
IR £3.30
Spain Pts. 780
Singapore S\$ 12.60
USA \$4.94

A REED BUSINESS PUBLICATION
SOR DISTRIBUTION

+ WIRELESS WORLD

May 1995

£2.10

FREE CAD disk

For the first 1000 replies

Migrating to C++


Single-chip fm receiver

Oscillators for uhf

Capturing transients

CAD software for Maths modelling

Bipolars or fets for audio?

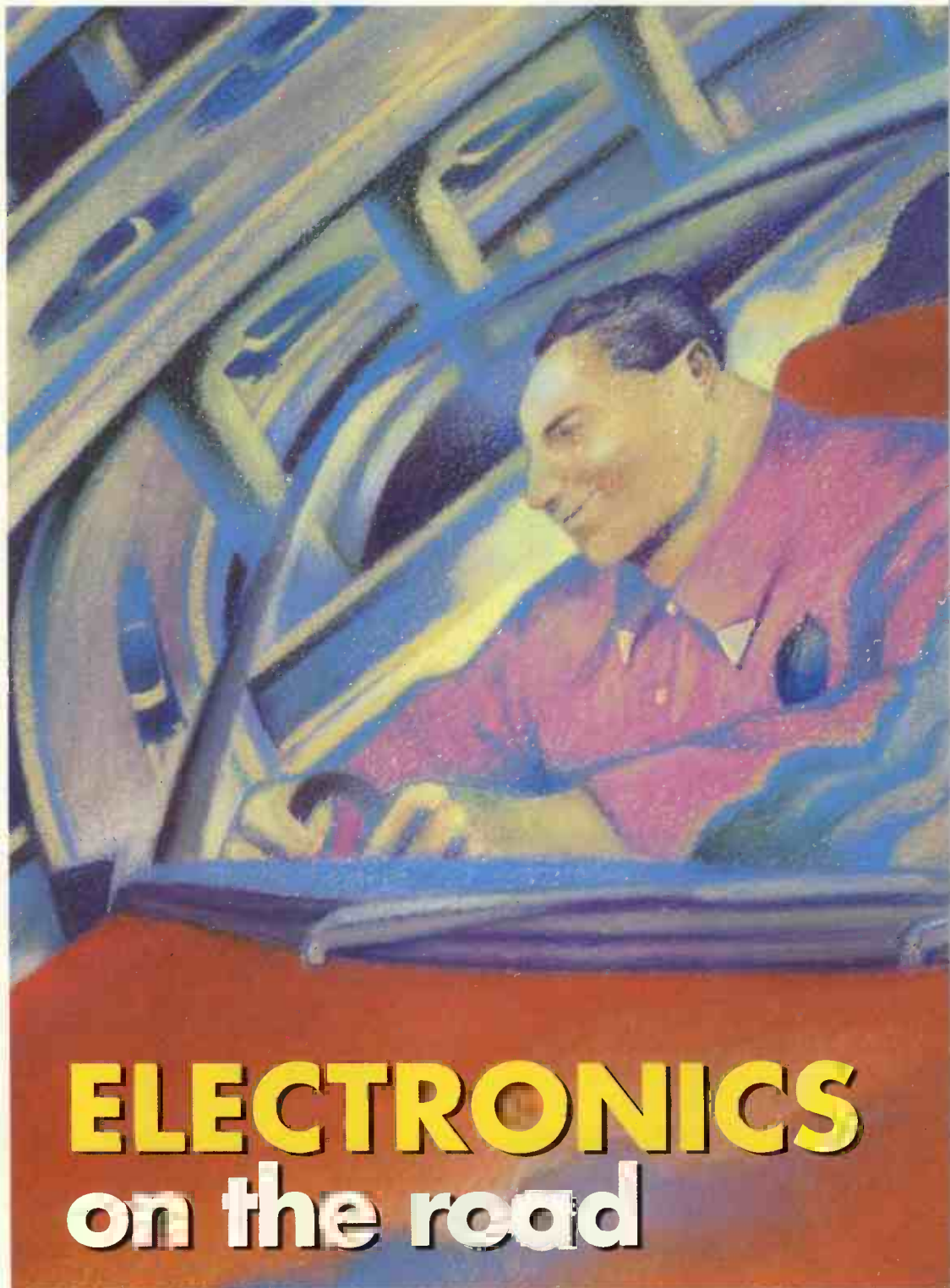

ELECTRONICS on the road



9 770959 833011


NEW!

FROM THE MAKERS OF THE WORLDS BEST SELLING UNIVERSAL PROGRAMMING AND TESTING SYSTEM

- * Ability to program 3 volt devices.
- * Calibration software to comply with ISO9000.
- * Batch software for production programming.
- * High quality 42 pin Textool zero insertion force sockets.
- * Rugged metal housing and heavy duty screened cable.
- * Ground control circuitry using relay switching.
- * Protection circuitry to protect against wrong insertion of devices.
- * Speed optimised range of programming algorithms.
- * Supplied with MICROTEC disassemblers for Z8, 8085, 8048, 8051, 6809 & 68HC11.

- * Programs PIC16 series without adaptor.
- * Software supplied to write own test vectors for custom ICs and ASICs etc.
- * One model covers the widest range of devices, at the lowest cost.
- * Over 2000 different devices (including several hundred MPU's) supported.
- * Tests and or identifies a wide range of logic devices.
- * High speed PC interface card designed for use with all types of PC.
- * No need to tie up a slow parallel port.
- * More Sunshine programmers sold world-wide than any other of its type.
- * UK users include BT, IBM, MOD, THORN EMI, MOTOROLA, SANYO, RACAL.
- * Two year free software update.
- * Free demo disk with device list available.

NOW ONLY £469

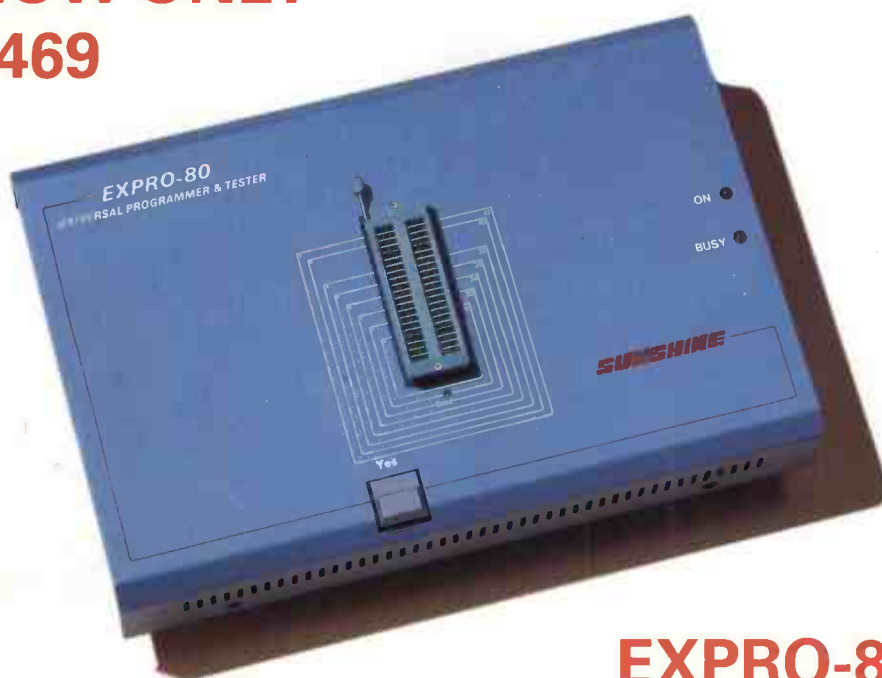

EXPRO-80

ORDERING INFORMATION

Expro-80 complete with interface card, cable, software and manual

only **£469**

Please add £8 carriage (by overnight courier) for UK orders, £30 for export orders and VAT where applicable.

ACCESS, MASTERCARD, VISA or CWO. Official orders are welcome from Government bodies and local authorities.



CITADEL PRODUCTS LTD
DEPT. WW, 50 HIGH ST.,
EDGWARE, MIDDX. HA8 7EP.

Phone now on: 0181 951 1848/9



Our stocked range of own manufactured and imported Sunshine products include:

- * Super fast EPROM Erasers.
- * 8Mbit EPROM Programmers:
 - ie: 1 gang £149
 - 4 gang £229
 - 8 gang £399
- * Battery operated portable EPROM programmers.
- * "In circuit" Emulators.
- * Handy pocket IC testers.



The Sunshine Expro-80 Universal Programmer and Tester is the 42 pin version of the immensely popular Expro-60/PC-82. Following that success, the Expro-80 is a PC-based development tool designed to program and test more than 2000 ICs. The culmination of over 8 years production experience has resulted in perfecting this rugged, classically designed programmers' programmer.

Volume production has now enabled us to offer this powerful programmer at a very competitive price for a product of such high quality. The Expro-80 has undergone extensive testing and inspection by various major IC manufacturers and has won their professional approval and support. Many do in fact use the Expro-80 for their own use!

The Expro-80 can program E/EPROM, Serial PROM, BPROM, DSP, PLD, EPLD, PEEL, GAL, FPL, MACH, MAX and MPU. It comes with a 42 pin DIP/SDIP socket capable of programming devices with 8 to 42 pins. It even supports EPROMs to 16Mbit, the PIC16 series of MPUs and many many more without the need of an adaptor. Adding special adaptors, the Expro-80 can program devices up to 84 pins in DIP, PLCC, LCC, QFP, SOP and PGA packages.

The unit can also test digital ICs such as the TTL 74/54 series, CMOS 40/45 series, DRAM (even SIMM/SIP modules) and SRAM. Furthermore it can perform functional vector testing of PLDs using the JEDEC standard test vectors created by PLD compilers such as PALASM, OPALjr, ABLE, CUPL etc. or by the user. The Expro-80 can even check and identify unmarked devices.

The Expro-80's hardware circuits are composed of 42 set pin-driver circuits each with control of TTL I/O and "active pull up", D/A voltage output, ground, noise filter circuit and OSC crystal frequency.

New features include negative programming voltages, 3 volt programming ability, protective circuitry for ICs incorrectly inserted, calibration software to comply with ISO9000, new six layer PCB and voltage clamping to banish noise and spikes.

A dedicated plug in card with rugged connecting cable ensures fast transfer of data to the programmer without tying up a standard parallel or serial port. Will work in all types of PC. In addition, there is now the Link-P1 enabling the programmer to be driven through the printer port. Ideal for portables and PC's without expansion capability.

The pull-down menus of the software makes the Expro-80 one of the easiest and most user-friendly programmers available. A full library of file conversion utilities is supplied as standard.

Sunshine's team of over 20 engineers are continually developing the software, enabling the customer to immediately program newly released ICs.

Citadel, a 33 year old company are the UK agents and service centre for the Sunshine range of programmers, testers and in circuit emulators and have a team of engineers trained to give local support in Europe.



Electronic systems keep this car going in a straight line on ice at 50km/h – page 372.



Cover Illustration Hashim Akib

CONTENTS

372 ELECTRONICS ON THE ROAD

Eric Russel looks at electronic systems that automotive manufacturers are planning for tomorrow's cars.

379 MODEL SOFTWARE FOR PROBLEM SOLVING

Maple V is the latest version of a modelling package capable of solving equations analytically, and much more, explains Alan Brown.

387 FETS VERSUS BJTS

How would bipolar transistors have been perceived by audio designers had they been invented after power mosfets asks Douglas Self?

391 DELAYED AUDIO SIGNALS

Ben Duncan argues that too few designers consider delays throughout the entire audio reproduction chain when they debate system performance.

396 MIGRATING TO C++

C++ is much more than an extension of C, but Gerard Maloney warns that getting the best from it involves more than simply buying new software.

402 TRANSIENT STORAGE FOR ANALOGUE SCOPES

Capturing transients in digital form and displaying them on an analogue oscilloscope is much cheaper than buying a digital storage.

410 LOW POWER SINGLE CHIP FM RECEIVER

Ed Baker describes an fm receiver based on a chip that saves power by automatically disconnecting the audio amp when not in use.

415 FREE DISC OFFER

Details of Smash – a mixed analogue/digital circuit design package free to the first 1000 readers.

418 OSCILLATING AT UHF

Ian Hickman discusses the often conflicting requirements of oscillators for uhf.

430 CIRCUIT ROUND UP

Eight circuit ideas, among them a crystal oven controller and a fast peak rectifier.

REGULARS

363 COMMENT

A sad foresight saga

364 NEWS

Polymer transistors and silicon coils.

368 RESEARCH NOTES

Lighter batteries, new life for sea cable.

424 CIRCUIT IDEAS

Mains fault monitor, 1.3GHz prescaler.

434 LETTERS


UK mains changes, audio debate.

439 NEW PRODUCTS

Pick of the month – classified for convenience.



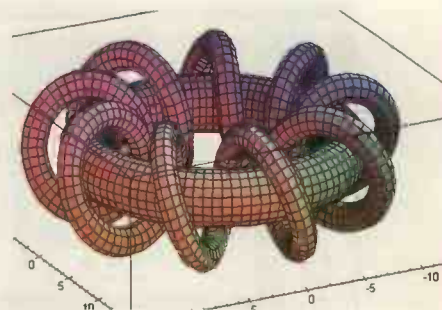Solar winds cause electricity supply problems, but new research could help make them more predictable – page 370.



Mathematical modelling software Maple V even produces animation, which can help provide an insight into temporal behaviour. – page 379.

Next month:

Douglas Self presents a completely new amplifier concept, Steve Webb describes a low-cost video digitiser, Cyril Bateman explains Internet and Jeff Macaulay describes the microreflex loudspeaker that we were unable to publish last month.

JUNE ISSUE – ON SALE 25 May

MIXED-MODE SIMULATION. THE POWER OF VERSION 4.

**New
Version 4**

Analog, Digital & Mixed Circuits


Electronics Workbench® Version 4 is a fully integrated schematic capture, simulator and graphical waveform generator. It is simple to mix analog and digital parts in any combination.

Design and Verify Circuits... Fast!

Electronics Workbench's simple, direct interface helps you build circuits in a fraction of the time. Try 'what if' scenarios and fine tune your designs painlessly.

Electronics Workbench®

The electronics lab in a computer™

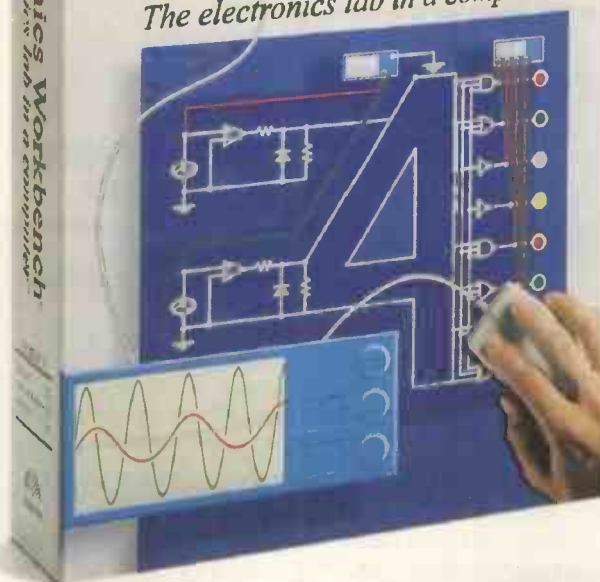

More Power

Simulate bigger and more complex circuits. Faster. On average, Electronics Workbench Version 4 is more than 5 times faster than Version 3.

More Parts

Multiple parts bins contain over twice the components of Version 3.


More Models

Over 350 real world analog and digital models are included free with Electronics Workbench. And, if you need more, an additional 2,000 models are available.

Incredibly Powerful. Incredibly Affordable.

If you need mixed-mode power at a price you can afford, take a look at this simulator and graphical waveform generator that mixes analog and digital with ease.

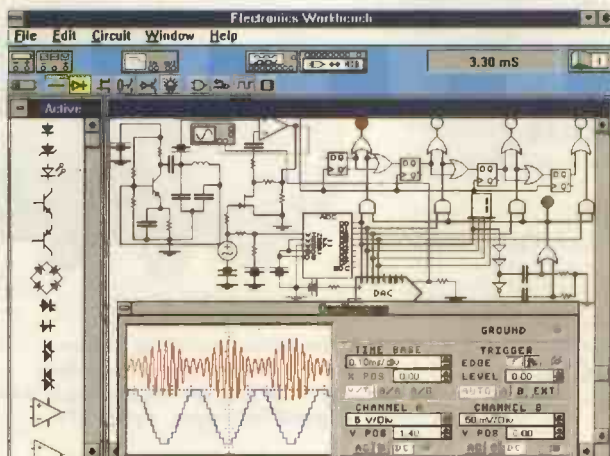With over 20,000 users world-wide, Electronics Workbench has already been tried, tested and accepted as an invaluable tool to design and verify analog and digital circuits. With Version 4 true mixed-mode simulation is now a reality with incredible simplicity.



True mixed-mode simulation: Simultaneous AM transmission, digitization and pulse-code modulation of a signal.

Electronics Workbench™

The electronics lab in a computer™

Order Now! Just £199*

44-(0)1203-233-216

RM Robinson Marshall (Europe) Plc

Nadella Building, Progress Close,
Leofric Business Park,
Coventry, Warwickshire CV3 2TF
Fax: 44 (0)1203 233-210

E-mail: rme@cityscape.co.uk

Shipping charges UK £5.99. All prices are plus VAT.
All trade marks are the property of their respective owners.
Electronics Workbench is a trademark of Interactive Image Technologies Ltd., Toronto, Canada.
* 30 Day money-back guarantee.



Australia: 2-519-3933 • Brazil: 11-453-5588 • Cyprus: 2-62-1068 • Denmark: 33-25-0017 • Finland: 0-297-5033 • France: 14-908-9000 • Germany: 711-62-7740 • Greece: 1-524-9981
Hungary: 1-215-0082 • India: 11-544-1343 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 3-774-2189 • Mexico: 5-396-3075 • Netherlands: 18031-7666
New Zealand: 9-267-1756 • Norway: 22-16-7045 • Portugal: 1-814-6609 • Singapore: 462-0006 • Slovenia: 61-317-830 • South Africa: 331-68309 • South Korea: 2-222-3431
Spain: 1-553-3234 • Sri Lanka: 1-86-5970 • Sweden: 8-740-5500 • Thailand: 66-2-398-6952 • United Kingdom: 203-23-3216

CIRCLE NO. 104 ON REPLY CARD

EDITOR

Martin Eccles
0181-652 3128

CONSULTANTS

Jonathan Campbell
Philip Darrington
Frank Ogden

DESIGN & PRODUCTION

Alan Kerr

EDITORIAL ADMINISTRATION

Jackie Lowe
0181-652 3614

E-MAIL ORDERS

jackie.lowe@rbp.co.uk

E-MAIL ENQUIRIES

martin.eccles@rbp.co.uk

ADVERTISEMENT MANAGER

Richard Napier
0181-652 3620

DISPLAY SALES EXECUTIVE

Malcolm Wells
0181-652 3620

ADVERTISING PRODUCTION

Christina Budd
0181-652 8355

PUBLISHER

Mick Elliott

EDITORIAL FAX

0181-652 8956

CLASSIFIED FAX

0181-652 8956

SUBSCRIPTION HOTLINE

01622 721666
Quote ref INJ

SUBSCRIPTION QUERIES

01444 445566

NEWSTRADE DISTRIBUTION

Martin Parr
0181 652 8171

BACK ISSUES

Available at £2.50

ISSN 0959-8332



A sorry foresight saga

Academic scientists have always had a disproportionate influence on the UK government's attitude to technology. That could be one reason why we have such a tiny microelectronics industry in the UK.

Earlier this month, the ITEC (Information Technology and Electronics) panel of the Government's Foresight programme looking at the UK's technological future, decided to write off the UK semiconductor industry.

As with the Alvey catch-up technology programme of the 1980s, the ITEC panel was dominated by academic scientists. Of the 25 man panel, 11 are working academics at universities, others are of an academic bent working on the boundaries of academia, and industry and not one of the 25 is a career semiconductor man.

The panel's principal microelectronics recommendation – that the UK needs a microelectronics R&D centre on the lines of the IMEC microelectronics research centre at the University of Leuven – will leave those people in the UK who struggle to make a living out of semiconductors, gasping for breath at its irrelevance.

The misdirection of government aid for the microelectronics industry has resulted in the UK having a chip industry made up mostly of design houses. These companies have world-class design skills – but they have nowhere in the UK to go to get leading-edge manufacturing services to turn their world-class designs into world-class products.

At a conference organised by the Federation of the Electronic Industry a couple of years back, delegates bemoaned the fact that there was no accessible, sympathetic British foundry facility where they could go for leading edge silicon – except for GEC Plessey Semiconductors (GPS). But now GPS has adopted a strategy of staying a year or two behind the leading technological edge, not even that exists.

But ITEC does not even purport to be aiming its microelectronics centre at helping the UK semiconductor industry – it is

intending it as a support facility for inwardly investing foreign semiconductor companies. In effect, ITEC does not see the UK semiconductor industry as worth support and does not regard an indigenous capability to manufacture first-class silicon as being of any importance.

Instead, the scientists of ITEC are directing the Government's thinking to other spheres – how to use the rapidly accelerating power of computers and the Information Superhighway to deliver the UK's undoubted strength in media products to Britain and to the world.

This is proper work for scientists! Conceptual, theoretical, intellectual stuff on which papers can be written, conferences attended and jobs for more scientists created.

But will it deliver any useful, practical technology to help the many entrepreneurial UK design houses or encourage the start-up of new high tech businesses? As with Alvey and with all previous scientist-driven initiatives, one doubts it.

David Manners



Electronics World + Wireless World is published monthly. By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Tlx:892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group.

Newstrade: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108. Subscriptions: Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year (normal rate) £30 UK and £43 outside UK.

USA: \$52.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Tlx 23827.

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

Printed by BPCC Magazines (Carlisle) Ltd, Newtown Trading Estate, Carlisle, Cumbria, CA2 7NR. Typeset by Wace Publication Imaging 2-4 Powerscroft Road, Sidcup, Kent DA14 5DT

©Reed Business Publishing Ltd 1995 ISSN 0959 8332

Focus on polymer transistors

With an all-polymer fet, it is easiest to begin with the insulating layer. This needs to have high homogeneity and good dielectric properties. Such fets could prove very useful for flat-panel display and smart-card type applications.

At least five major electronics firms are developing products based on all-polymer transistors, amid claims that the technology could eclipse amorphous silicon in applications such as flat panel displays and smart cards by the end of the century.

Japanese giants Matsushita and Mitsubishi, US-based Motorola and IBM and European firm Philips are

working on all-polymer transistor systems. Matsushita and Mitsubishi have already published research papers on the subject, and Mitsubishi is rumoured to be very close to producing the world's first all-polymer-transistor based flat panel display type for laptops.

Flexible polymer transistors have been pioneered by a team of researchers at the CNRS centre in France, led by Francis Garnier. The team has been working on the devices for the last five years, but now the technology is being taken up by electronics giants worldwide.

The main advantage of polymer transistors over silicon ones is their flexibility, which may allow complete bending or rolling without affecting their electrical properties. They should also be cheap to make in volume, and the devices can be made transparent, suitable for windshield applications in planes and cars. "Organic semiconductors will be available at lower cost", insisted Garnier. "They can be applied with web printing techniques and this will open the field for cheap, flexible electronics".

At present, polymer transistors are slower, larger and have lower output current than silicon transistors but these characteristics are expected to be improved with further development. Garnier

expects the first commercial products, probably in the form of displays for domestic appliances, as soon as 1996/7 and for these low-end applications to open the way for large-area, low-cost polymer electronics systems.


Unlike earlier work, where only the substrate was made of polymer, the latest transistors also have polymer-based electrodes made from graphite-based ink.

Svetlana Josifovska
Electronics Weekly

Video on the radio

Engineers at Racal Radio have developed a video compression technique said to be efficient and robust enough to transmit pictures reliably over a radio link. The technique, designed for immediate application in military surveillance systems, can transmit a real-time video stream over a 25kHz 16kbit/s radio link.

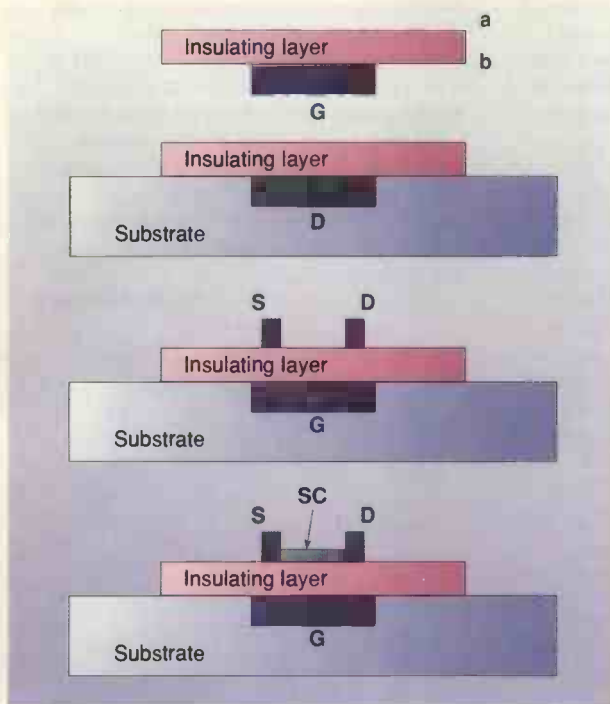The compression algorithm used is a Racal-developed version of the lapped orthogonal transform, coupled to an error resistant entropy code. The combination is said to be able to recover from 20 percent data loss. For worse losses, rather than an image failure, there is a gradual degradation of the received image quality as the channel error rate increases.



Low cost route to silicon modelling

As feature sizes continue to shrink and devices become more complicated, chip designers may have to resort to virtual reality techniques in which they can literally immerse themselves in a 3D simulation of a chip, according to a top researcher.

Interactions between electrons and the edge of devices have become more important in determining chip performance. These require complex equations to model the effects, which is why the key to 3D simulations will be the development of very fast, cheap parallel computers capable of

processing millions of equations.

Stanford University researchers, working with scientists at IBM, claim they have developed special algorithms that boost the performance of low cost parallel computer systems without the need to build specialised parallel computer systems costing tens of millions of dollars. The researchers have demonstrated the ability to solve 1.5 million equations at a speed of 9.5Gflops using an IBM Powerparallel SP-2 computer.

Robert Dutton, professor of electrical engineering and chief scientist at Stanford University's

Center for Integrated Systems says that, "At these rates, 3D will take about the same time to run as current two-dimensional simulations".

The new algorithm has been incorporated into Pisces - a commercial program that simulates the behaviour of microscopic electronic elements in complex semiconductors.

Dutton said the algorithm could be ported to desktop workstations where it can speed up 2D chip modelling tasks. Stanford has said it will license its technology to other companies.


Philips/Sony fight back on high density CD

The chances of Philips and Sony conceding victory to Toshiba in the battle of high-density cd systems seem remote. Philips has been mounting a major information offensive in support of its system with demonstrations at CeBIT, the Audio Engineering Society convention in Paris and its home base, Philips Research Laboratories in Redhill.


Players using the single-sided dual-layer system will be on sale next year, Philips promises, whether the film industry supports it or not. Increasingly Philips/Sony are looking to the professional computer market – a potentially much larger user base – to back the system. "We do not believe this is a technology which is a mass market proposition that's just around the corner," said John Hawkins, world head of Philips Media Distribution, at Redhill.

The demonstrations revealed some aspects of capability, such as the dual-layer system which was first used on Laserdiscs as far back as 1977, but also showed the complexity of the agenda which Philips is now grappling with. Although it needs to counter the Toshiba double-sided system, Philips also wants to create some space for the development of CDi, assisted by existing MPEG 1 CD Video. Hence its insistence on the high initial cost of high-density which, it contends, will preclude mass sales to begin with.

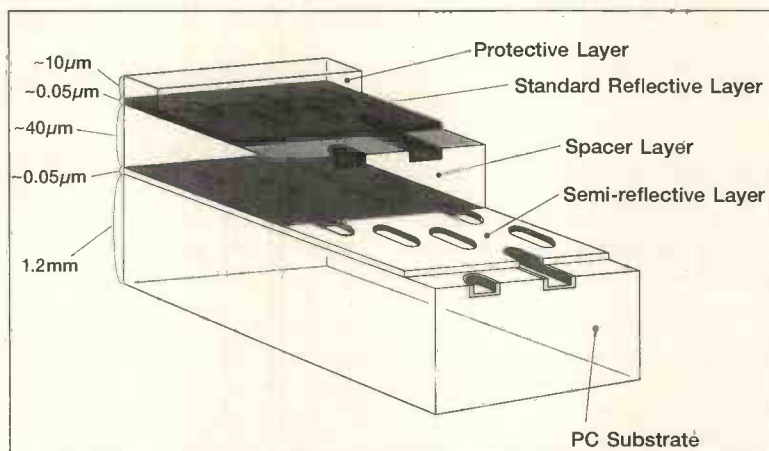MPEG 2 will require four times as much memory as MPEG 1, and far greater processing complexity, to say nothing of the HD drive and new laser and optics. All of these combined will push the price of



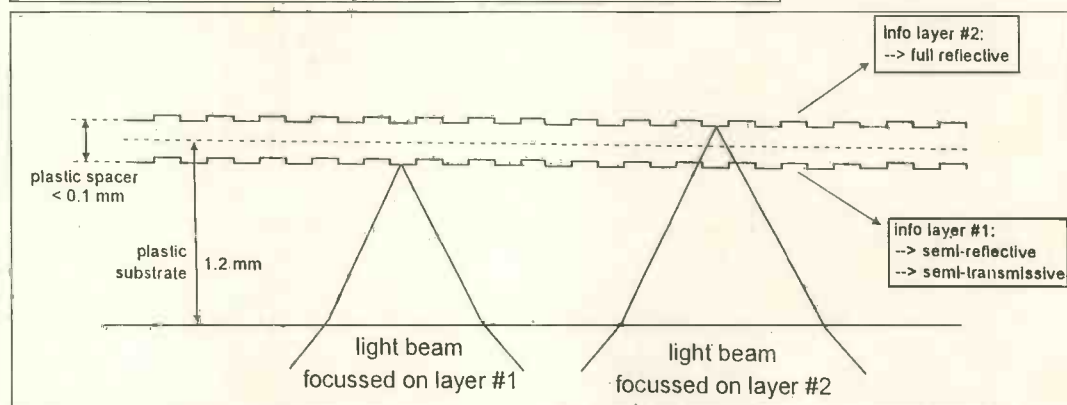Dual layer construction of Philips high-density CD system, whose complexity indicates initial take-up by the computer, not consumer, industry. Light beams will need to be focused separately on the two layers; each layer offers different read-out characteristics.



hardware up into the no-go area, well above £400.

Thus, initial uptake of high density technology is likely to be by the computer, rather than consumer, community, where increased storage capacity is always in demand. Only after start-up costs have been amortised in that market, so the Philips argument runs, will high-density become affordable enough to go mass-market.

Both proposed high-density standards can carry more than ten

times the current 650Mbyte capacity of CD-Rom. Philips/Sony will hold 7.4Gbyte in two layers; Toshiba, 10Gbyte, split between two sides. Both will use red laser technology with a wavelength of 635nm. Philips/Sony now promise backwards compatibility with existing formats. Apart from additional costs involved in accessing two sides of a disc, Toshiba has yet to work out where the label could be accommodated.

Peter Willis

Silicon coils for even smarter cards

While smart cards may give the impression of being easy to use, they can give rise to problems, usually associated with the way they are made. The rigidity of the antenna coil, which is wrapped on a chip fixed on a flexible fixture like a plastic card, means that it is possible to break some of the connecting wires within the chip if the smart card is flexed.

Micro Sensys, a German-based radio identification specialist, has come up with a simple, low-cost way of building coils onto chips by growing them onto the silicon wafer, which avoids the traditional bonding processes. The monolithic

microstructure employed is used in rf chips for contactless smart cards and other identification and access control applications. It integrates completely all of the analogue functions, a high-frequency rectifier, antenna coil and an EEPROM on a single chip.

In a conventional contactless smart card chip, the transceiver coil is applied using cmos metal layer technology. This method produces structures 1µm thick and below. These very thin layers introduce high surface resistance, inconsistent quality and inhibit the placement of active circuit elements (the logic gates, EEPROM and

the transmitter) in the coil area. These drawbacks can be rectified by using thicker structures (around 100µm), produced by X-ray lithography, which although technically feasible is expensive.

Instead, Micro Sensys uses a modified straight wall bumping process. This process is normally used in tape-automated bonding for chips with many contacts (between 200 and 300). A single metal layer is applied to the silicon substrate in the form of 'bumps', leaving structures that look like tower-blocks behind. This is achieved by raising the metal layer higher than the silicon substrate; passivation-layer channels still run in between. The metal layer forms the coil between the bumps.

1Gbit DRAMs nearing production stage

Sony has combined two leading edge chip fabrication devices – one a quadrupole light source and the other a phase shift mask, to stretch optical lithography towards 0.18 μ m feature fabrication. This is the feature size that will be needed to make the first generation of 1Gbit DRAMs in production quantities.

The surface of a wafer is not flat, but deviates up to 1 μ m. The image of the production mask must be in focus for all 'altitudes' on the wafer surface, so the projection optics must have a minimum depth of field (DOF) of 1 μ m.

The size of image that can be clearly focused onto the surface of the wafer is proportional to the wavelength of light used. For 0.35 μ m lithography (current state-of-the-art for production), specially-developed krypton fluoride (KrF) excimer lasers are used that emit

ultraviolet light at 248nm. For a given optical system, both the minimum image size and the depth of field are proportional to wavelength. These limitations restrict KrF lasers to feature sizes of 0.35 μ m.

Beyond the DOF, a circular spot projected on the wafer becomes a larger and larger circular blur. Sony has used a trick to reduce the effect of this problem by altering the characteristics of the laser beam.

Sony's modified optics split the laser beam in four, diverge the sub-beams using a prism array, then recombine them, creating a quadrupole light source. This replaces the normal circular light source with four smaller overlapping image ones. In sharp focus, the image looks like four spots but outside the DOF the blurred image has more energy in the centre and looks much more like a 'normal' focused spot.

This technique raises the effective DOF more than two times, allowing the optics to be changed and trading the increased DOF for smaller feature size.

If a feature size of 0.28 μ m is required, conventional illumination only gives a DOF of 0.77 μ m. The

new source gives a 1.1 μ m DOF, suitable for production techniques of the near future.

The second feature Sony has incorporated is a phase shift mask. A normal mask has transmissive and non-transmissive regions. The sharp transitions between these regions result in diffraction patterns over the wafer surface around the image. Diffraction effects can be reduced by deliberately phase-shifting light by different amounts at different points in the mask.

There are some limitations to phase shift masks: not all image shapes can be made and there can be a strong secondary image net to the primary one. On their own, phase shift masks can improve image resolution, but the quadrupole light source can be optimised to suppress most of the secondary image. The new light source and mask together allow 0.22 μ m features with a 1 μ m depth of field.

Sony has demonstrated that its combination technology can produce 0.22 μ m features and claims it can be developed to make first generation 0.18 μ m chips using optical lithography.

Steve Bush
Electronics Weekly


PCs fuel demand for electronic components

Industry analyst BIS Strategic Decisions reports that demand for electronic components continues to be fuelled by the booming markets for PCs, monitors and printers.

The BIS report, European Computer and Office Automation Equipment Production, expects the European computer market to be worth \$13.5 billion this year, up \$3.3 billion since 1993. In 1993, \$7.4 billion (around 72 percent) was accounted for by components in desktop and portable computers.

1995 European market for computer and office automation equipment.

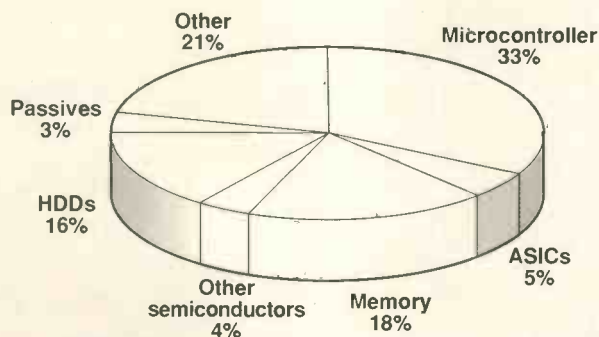1995 European Component Market in Computer/OA Equipment



Total European Market in 1995 = US\$13.5 billion

Source: BIS Strategic Decisions

Low cost single-chip demodulator

A single chip digital tv demodulator based on the 64/256 QAM systems used in North America's Grand Alliance HDTV trials has been introduced by VLSI Technology. The quadrature amplitude modulation (QAM) system, which could also be the basis of European terrestrial digital tv transmissions, was developed by Californian developer Applied Signal Technology and integrated by VLSI Technology into its library of functional system blocks.

The quadrature down converter equaliser demodulator (QED) would be used in QAM cable tv set-top box receivers. It sits between the cable and the MPEG compression functions and extracts the digital video and audio data streams from the 64/256 QAM modulated signal on the cable tv network.

Operating at an IF of 43.75MHz, it supports symbol rates up to 5.4Mbaud and implements the Reed-Solomon forward error correction

algorithm. The QAM protocol combines traditional amplitude modulation and quadrature phase shift keying (QPSK) to put the digitally coded tv signal on the carrier frequency.

An advantage of QAM is the relatively large number of phase and amplitude states, 64 and 256, used to represent the digital tv signal. As a result, QAM supports a high capacity data channel, equivalent to 40Mbit/s, by assigning 64 and 256 phase and amplitude states to represent the digital signal at 8 bits per symbol. The 40Mbit/s 256QAM digital channel can support up to five 8MHz PAL analogue tv signals or seven 6MHz US NTSC analogue television signals.

The QAM device is one of a number of chips VLSI is offering for low cost set-top box receiver designs. It is developing a separate QPSK demodulator with ComAtlas of France, and an MPEG-2 codec with US specialist, Mediamatics. ■

Surplus always
wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

SPECIAL BUY AT 286

40Mb HD + 3Mb Ram




LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & Integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

ONLY £149.00 (E)
CALL FOR QTY DISCOUNTS

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£24.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

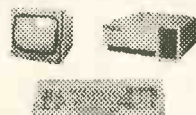PC SCOOP COMPLETE COLOUR SYSTEM ONLY £99.00



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go!! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.

Order as PC99COL	£99.00 (E)
Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95
Above prices for PC99 offer ONLY.	

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have

ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £335.00 (G)
OPT Rack 2 Rack, Less side panels £225.00 (G)

32U - High Quality - All steel cabinet

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features full slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions 64" H x 25" D x 23 1/2" W.



Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)

Over 1000 racks in all sizes 19" 22" & 24"
3 to 44 U. Available from stock !!
Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to a PCB with on board sophisticated electronics. From the board comes a standard serial RS232 or TTL output. The output continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the screen size !! So, no position, however small fails detection. A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc etc Imagine using your finger in 'Windows' instead of a mouse !! (a driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Supplied as a complete system including Controller, Power Supply and Data at an incredible price of only:

£145.00 (E)
RFE Full Software Support Available - Fully Guaranteed

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disk supplied. In good used condition fully tested and guaranteed.
Windows compatible. Order as: ABOVE CARD £59.95 (A1)
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.
Order as: XT RAM Upgrade £256k £32.95 or 512k £38.95 (A1)

SIMM OFFERS

1 MB x 9 SIMM 9 chip 120ns only	£19.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£23.50 70ns
1 MB x 9 SIMM 9 chip 80 ns	£22.50 70ns
1 MB x 9 SIMM 9 chip 80 ns	£22.50 70ns
4 MB 70ns 72 pin SIMM module only	£125.00 (A1)
SPECIAL INTELL 486-DX33 CPU	£79.99 (A1)

NO BREAK UNINTERRUPTIBLE PSU'S

EMERSON ACCUCARD UPS, brand new 8 Bit half length PC compatible card for all IBM XT/AT compatibles. Card provides DC power to all internal system components in the event of power supply failure. The Accusaver software provided uses only 6k of base RAM and automatically copies all system, expanded and video memory to the hard disk in the event of loss of power. When power is returned the machine is returned to the exact status when the power failed !! The unit features full self diagnostics on boot and is supplied brand new, with full, easy fitting instructions and manual. Normally £189.00 NOW! £69.00 or 2 for £120 (E)

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" from £22.95 - 3 1/2" from £24.95

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent	£24.95 (B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only *	£36.95 (B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£29.95 (B)
5 1/4" Teac FD-55GFR 1.2 Meg	£29.95 (B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95 (B)
* Data cable included in price.	
Shugart 800/801 8" SS refurbished & tested	£195.00 (E)
Shugart 851 8" double sided refurbished & tested	£250.00 (E)
Mitsubishi M2894-63 8" double sided NEW	£275.00 (E)
Mitsubishi M2894-63-02U 8" DS slimline NEW	£285.00 (E)
Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drives!	£499.00 (F)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full industry standard SMD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model. Complete with manual. Only

3 1/2" FUJITSU FK-309-26 20mb MFH I/F RFE	£59.95 (C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£69.95 (C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£89.00 (C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£99.00 (C)
5 1/4" MINISCRIBE 3425 20mb MFH I/F (or equiv) RFE	£49.95 (C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95 (C)
5 1/4" CD 94205-51 40mb HH MFH I/F RFE tested	£69.95 (C)
8" FUJITSU M2322K 160mb SMD I/F RFE tested	£195.00 (E)
Hard disc controllers for MFH, IDE, SCSI, RLL etc. from	£16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND
& VIDEO
TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£34.95
TELEBOX STL as ST but with integral speaker	£37.50
TELEBOX MB Multiband VHF-UHF-Cable - Hyperband tuner	£69.95
For overseas PAL versions state 5.5 or 6mhz sound specification.	
*For cable / hyperband reception Telebox MB should be connected to cable type service. Shipping code on all Teleboxes is (B)	

FANS & BLOWERS

MITSUBISHI MMF-D6B12DL 60 x 25 mm 12v DC	£4.95 10 / £42
MITSUBISHI MMF-09B12DH 92 x 25 mm 12v DC	£5.95 10 / £53
PANCAKE 12-3.5 92 x 18 mm 12v DC	£7.95 10 / £69
EX-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 v	£6.95
EX-EQUIP 80 x 38mm AC fans - tested specify 110 or 240 v	£5.95
VERO rack mount 1U x 19" fan tray specify 110 or 240v	£45.95 (E)
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240v NEW	£79.95
Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL	

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

5,000,000 items EX STOCK

For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

DISPLAY
-ELECTRONICS-

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept WW. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

DISTEL © The Original
FREE On line Database
Info on 1000's of items
V21, V22, V22 BIS
0181 679 1888

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Cash on delivery £100. (A)=£3.00, (B)=£4.00, (C)=£5.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1995. E & O.E. 4/5

CIRCLE NO. 105 ON REPLY CARD

RESEARCH NOTES

Jonathan Campbell

Thin film cell packs a punch

Weight is so often a limiting factor in design of rechargeable batteries. But researchers at Tokyo University and Matsushita Electrical Industrial have announced development of a low cost solid state rechargeable battery that can store 50% more electrochemical energy in its electrodes than the best conventional technology available.

Key to performance of the new battery is an organic thin-film cathode. Organic materials have been proving particularly attractive to battery designers because they offer large theoretical energy storage capacity, combined with low weight and high strength.

The Tokyo cell is made up of a Dimercaptan (DMcT) and polyaniline (PAn) cathode with a lithium anode – compounds already known to have had a complementary effect on performance, though the precise chemistry of the reaction is not yet definitively agreed. However, cells fabricated along these lines have been reported before.

The advance made by the Japanese team has been to prepare a solution containing the electrode materials which can be printed or painted by conventional techniques. Not only does that make for easy manufacturing, but, importantly, it allows excellent molecular-level mixing of the DMcT and PAn, leading to much higher efficiencies than have been achieved before.

Gravimetric energy density of the composite cathode is reported to be >600Wh/kg cathode (Dimercaptan-polyaniline composite electrodes for lithium batteries with high energy density, N Oyama *et al* (*Nature*, 373, pp.598-600). This compares to a figure of 400Wh/kg for the cathode in one of best commercial lithium-ion cells. So energy density of the DMcT-PAn cathode is 1.5 times better.

No deterioration in capacity was observed in 30 cycles for the test

cell, with the cathode charged at 4.5V and discharged at 0.1mA/cm² down to 2.25V. That compares with a loss of 15% in capacity by previous designs of this type of cathode.

At present the maximum useful current density looks to be 0.1mA/cm² – which is undeniably

small. But because the cathode is a film, a large electrode area can easily be obtained without weight penalty.


Expected applications will be in areas where weight rather than volume is the crucial factor, as high gravimetric density is offset by low physical density.

Deep conversations

Confidence in ultra-long-haul optical cable systems using cascaded erbium-doped fibre amplifiers has been boosted with news that Japanese workers have successfully made 5.3Gbit/s transmissions across 11,300km of installed submarine cable. This is the longest distance yet achieved using the technology. T Otyani *et al* (5.3Gbit/s 11,300km data transmission using actual submarine cables and repeaters, *Electronics Letters*, Vol 31, No 5, pp.380-381) from KDD Submarine Cable

Systems, made use of two fibre pairs in a real cable 2850km long that had 48 repeaters and a repeater spacing of 60km. By joining the fibres together at their ends with optical attenuators, the researchers were able to create a 11,300km transmission line.

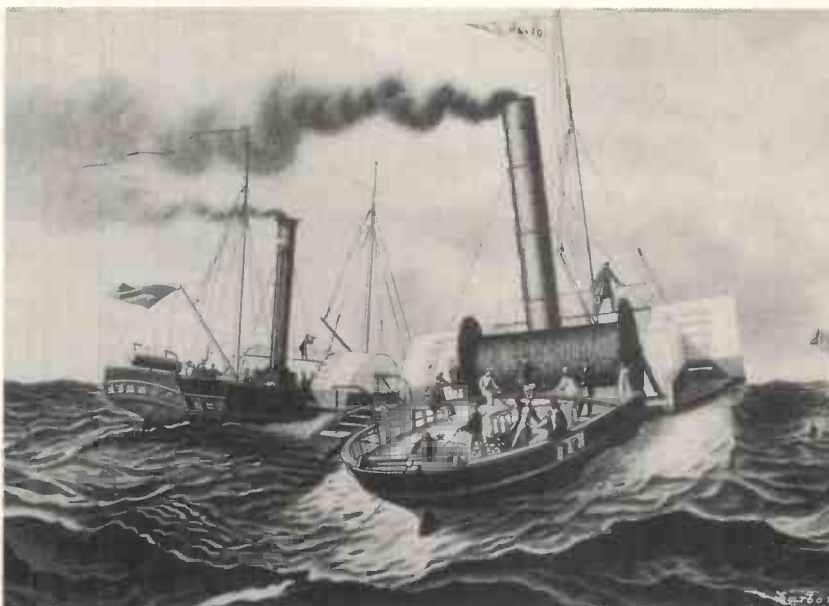The long distance success of using a cable made up of dispersion-shifted optical fibres and erbium-doped amplifiers – designed to operate under the sea for at least 25 years – clearly demonstrates that the low-cost and high reliabilities of such a system



Exploiting the full potential of submarine cables already laid will be vital to the development of optical fibre comms.

Ultrasonics open up memory capacity

Development of a simple and convenient ultrasonic method for manufacturing very small cobalt particles – magnetic nanocluster – could have an immediate effect on high-density recording media.

The process, developed by Charles Gibson and Kathy Putzer at the University of Wisconsin (Syntheses and characterisation of anisometric cobalt nanoclusters, *Science*, 267, pp1338-1340) produces single magnetic domain

particles with considerable shape- and magnetocrystalline anisotropy so that a preferred magnetic field orientation is adopted in the final product.

Relatively inexpensive reagents are used in the procedure and flocs of the suspended particles are stable for several days, so easing manufacturing flexibility.

The basis for the process is reduction of Co^{2+} with hydrazine. Low temperature reaction has been attempted before, but

despite looking thermodynamically possible, the reduction has not previously been successful.

Now Gibson's and Putzer's use of ultrasound to initiate the chemistry has made the reaction practical – and economical.

The result is the birth of a simple technique that could have immense importance for the manufacture of magnetic recording media and permanent magnets.



could be exploited in practice.

Other work currently going on is also helping to test the limits of undersea cables. For example, AT&T recently announced it had transmitted 10Gbit/s over a 2000km commercially installed undersea fibre-optic cable in the US. Normal operating limit for the cable was 2.5Gbit/s. AT&T achieved the increase through wavelength division multiplexing – the transmission of information on more than one wavelength of light on each fibre.

10Gbit+ transmission speeds greatly increase the capacity of

undersea cable and AT&T says the test gives it the potential to upgrade installed fibre-optic communications systems without making adjustments to cable already sitting on the sea floor.

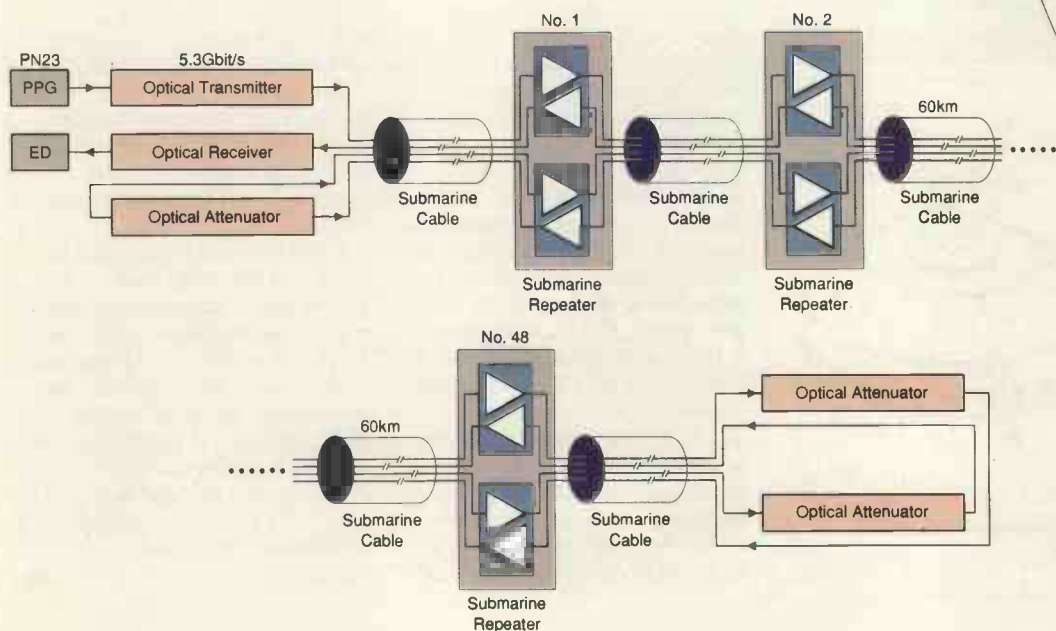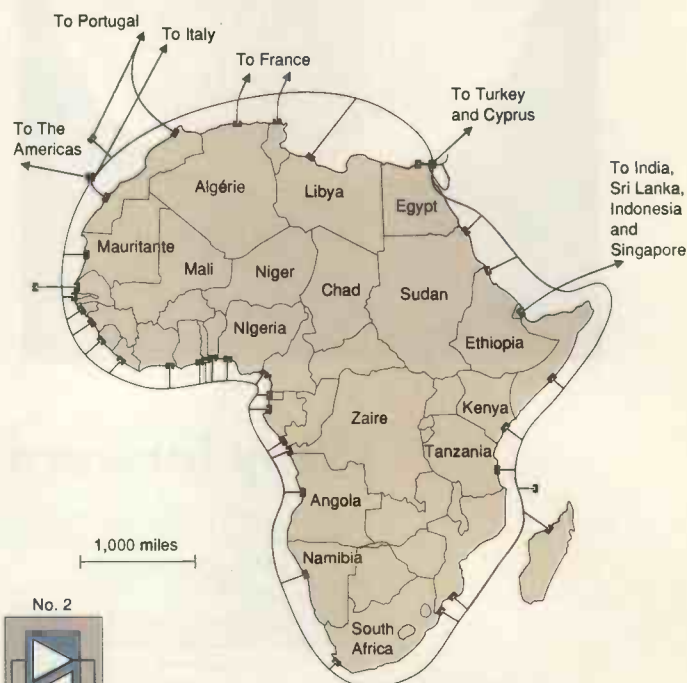AT&T has already announced a proposal to build a 32,000km optical fibre ring around Africa, linking 40 countries. Practical architectures for such a project are still being considered though AT&T researchers say that experiment is demonstrating that such a large-scale all-optical network having many high speed channels is certainly possible.




Continental drift: fibre optic technology is moving to make such projects as the 32,000km ring around Africa a reality.

11,300km is the longest distance yet for data transmission through commercial optical cable.

Getting the measure of solar wind

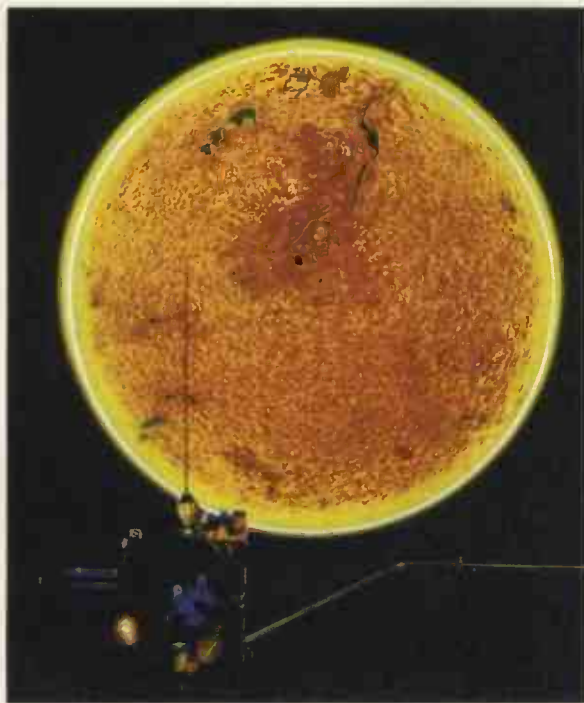Ulysses on its mission to explore the heliosphere – the region of space dominated by the outward flowing solar wind. (Picture courtesy European Space Agency).



Quite apart from giving rise to the haunting northern lights, the million-mile-per-hour charged particles that make up the solar wind can degrade communications, disrupt power transmission grids, and damage satellites. Yet scientists are still unable to predict with any certainty when such activity is going

to hit the earth. But data currently being processed from satellites belonging to the ISTP (International Solar Terrestrial Physics) programme could help change that.

ISTP involves coordinating experimentation aboard a number of space platforms, with different initiatives exploring key areas of geospace where the dynamics are controlled by Earth's magnetic field and its interaction with the solar wind.

For example Japan has been processing data from a satellite sitting in the magnetospheric tail formed by the solar wind as it rushes past the earth. Similarly, solar wind experiments (swe) aboard the 'Wind' satellite will measure properties of the solar stream before it reaches the Earth. Researchers are hopeful that Wind's location between the Earth and Sun could eventually give warning of magnetic storms.

Overall goal of the swe programme is to monitor how changes in the wind affect the environment around Earth, according to Alan J Lazarus, a senior research scientist in physics and head of the swe MIT team.

Since November, MIT's instruments have begun collecting samples of the charged particles that

make up the solar wind, and measuring their speed, density, and other properties. Scientists from Nasa, the University of New Hampshire, and Boston University are cooperating on the swe project and six more experiments on the satellite are focusing on other phenomena associated with the solar wind.


"There are efforts to return data in real time from this spacecraft, so we can report solar wind conditions to people who could be affected," says John T Steinberg, a research scientist at the Center for Space Research and also a member of the MIT team.

Ultimately, Wind will go into an orbit between the Earth and the Sun that will allow it to make continuous readings of the solar wind an hour before it reaches Earth.

The result would be that sensitive electronics on the spacecraft – which might otherwise be damaged – could be switched off. Varying magnetic fields can also have a serious effect on power grids, and have in the past caused massive power outages. One such incident occurred in Canada in 1989. With advance warning, power companies could make proper preparations for possible disruptions of their systems.

Way forward (or sideways) for robots?

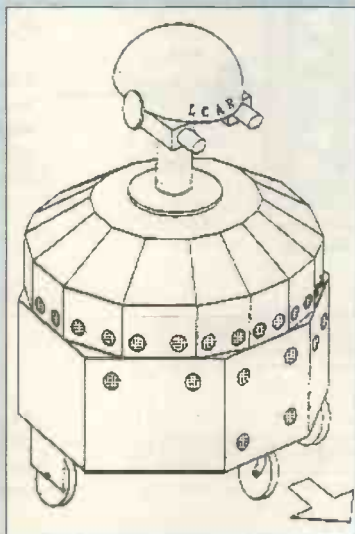Successfully negotiating our way around rooms full of furniture is a skill we learn as babies. For robots, the task is one some of them will never learn. But



Kaist's Lcar robot can switch between goal seeking behaviour and obstacle avoidance behaviour to negotiate obstacles in real time

researchers at the Korea Advanced Institute of Science and Technology (Kaist) hope their work could lead to fewer bruised robot shins in the future.

A robot's navigational problem is that whenever it moves in an uncertain environment towards a goal, avoidance behaviour and goal-seeking behaviour always conflict. Avoidance behaviour is used to seek the goal position, until obstacles loom, when avoidance takes precedence, and goal-seeking behaviour is used to seek the goal irrespective of obstacle location.

Hee Rak Beom and Hyung Suck Cho at Kaist have been using fuzzy logic to describe both behaviours and have been working to develop a robot control system that switches to the best strategy based on the robot's local environment (A sensor-based navigation for a mobile robot using fuzzy logic and

reinforcement learning, *IEEE Trans on systems, man and cybernetics*, 25, 3, pp.464-477).

Their Lcar robot has 26 ultrasonic sensors, stereo camera and sensors for dead reckoning.

Fuzzy logic is used to represent the mapping between the sensor input space and the mobile robot action space, with the correct mapping found by reinforcement learning.





So far the robot is managing to move around a 10 by 10m room packed full of obstacles towards its goal and is demonstrating an ability to adapt to unknown environments.

Importantly the small fuzzy-rule-base needed allows the method to be implemented in real time, while the reinforcement learning dispenses with the need to construct and tune the rule bases depending on the expert's knowledge. ■



®

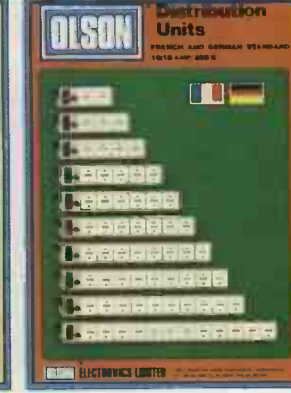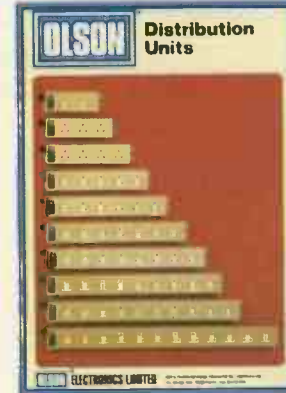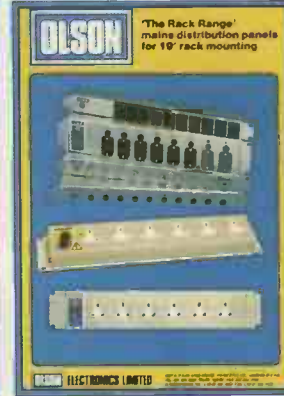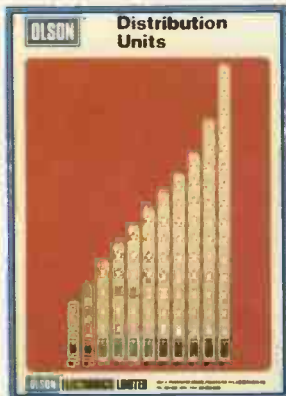*For all your Power
Distribution
Olson offer a varied
choice*



ELECTRONICS LIMITED

FOUNTAYNE HOUSE, FOUNTAYNE RD., LONDON N15 4QL
TEL: 0181-885 2884 FAX: 0181-885 2496

CIRCLE NO. 106 ON REPLY CARD



ELECTRONICS *on the road*

More vehicles come onto the roads each year and manufacturers are doing more and more to make them safer. The accent is moving away from mechanical developments towards electronic detection and control, with anti-collision radars, anti-skid systems and better anti-lock braking.

Aerospace technology has come down to road level, but the new technology is driving itself. More devices mean more wiring, which leads to intelligent harnesses, in turn resulting in more electronics. The automotive designer has to drive hard to keep up.

Driving on black ice

To be in full control while driving fast on black ice must be the ultimate motoring experience and it is promised for UK drivers this year by Mercedes-Benz.

Electronics is the key to this and other recent advances in automotive design in a trend which will shortly see more electronics than mechanics on the family saloon.

Eric Russell looks at innovations in electronic systems that automotive manufacturers are planning for the cars of tomorrow.

Mercedes-Benz calls its system Electronic Stability Program. It brings together traction control, intelligent brakes and aerospace technology to detect a car's direction of travel. ESP prevents skidding by braking individual wheels to maintain the car's balance. Control signals to the brakes derive from a computer which compares steering wheel position with the car's direction of travel.

When under- or over-steer is detected, the appropriate brakes are momentarily applied and engine torque is reduced. This brings the car back on line. The driver may not notice the system operating but a dashboard indicator illuminates, providing a warning.

Key to the system is a yaw detector. Housed under the rear seat of a car it gives an output signal proportional to the rate of rotation about a vertical axis.

Fig. 1. A car travelling on ice at 45mile/h is kept steerable and stable by the new Electronic Stability Program from Mercedes-Benz.



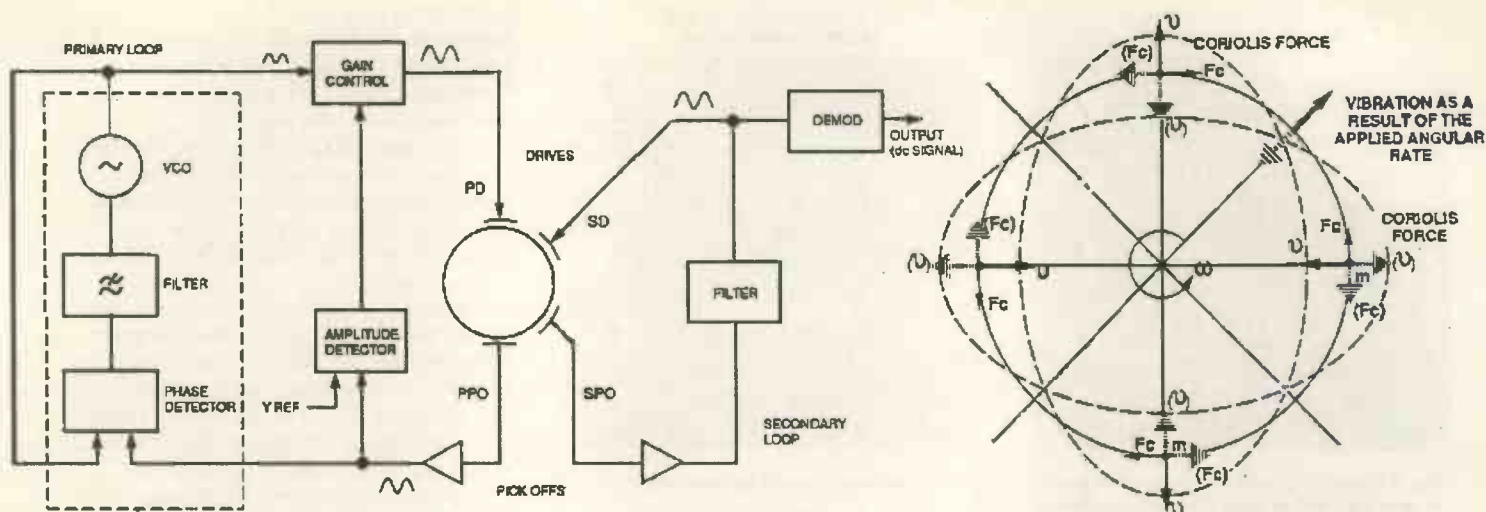


Fig. 2. Such a vibrating-structure gyroscope may be being used for yaw detection in Mercedes' electronic vehicle stabiliser. Output of the gyroscope is dc and proportional to the rate of rotation.

This data, together with steering wheel angle, individual wheel speeds, brake pressure and sideways acceleration are compared in a computer with a database which contains all the parameters for optimum stability.

The ESP control unit is linked to engine, automatic transmission, brakes, accelerator and sensors through a Controller Area Network data bus. The accelerator is electronically linked to the engine management system, bringing the new Mercedes close to drive-by-wire. A variable resistor is rotated as the accelerator is depressed to give a much finer control than with mechanical linkage.

ESP was recently demonstrated on a frozen lake in Sweden, Fig. 1. While a standard car was virtually uncontrollable at 30mile/h, the ESP car was steerable and stable at 45mile/h. Mercedes points out that such systems cannot beat the laws of physics and in unintended confirmation, a test driver promptly ploughed his vehicle into a snow bank.

The system was scheduled to become standard equipment in Germany in March on the S600 coupe. The first cars for Britain are promised in the autumn – in time for our own snow. Details of the ESP system are not available, "Because the system is not yet in production," says a spokesman. But the key component, the yaw detector, could be similar to a unit produced by British Aerospace (Systems and Equipment) Ltd.

This is a solid state gyroscope using the piezo-electric principle and the coriolis effect. The sensing element is a cylinder of man-made ceramic, a lead zirconate titanate composite, which is electronically vibrated.

The coriolis effect refers to the distortion of an object's trajectory by the earth's rotation. The effect of the force can be seen when a person sits on a typist's chair holding a spinning bicycle wheel by the axle ends. If the person lifts their right hand, tilting the wheel, the chair will rotate towards the right.

A similar force can be generated when a vibrating object is rotated. In British Aerospace's Vibrating Structure Gyroscope

the piezo-electric block is excited in one axis and electric output is taken from another axis. Output is dc and proportional to the rate of rotation, Fig. 2.

The solid state construction makes the VSG more robust than conventional mechanical gyroscopes with no maintenance requirement and minimal start-up time, which can be as low as 300ms. It can operate off a standard car power rail, Fig. 3.

At Lotus Engineering, the Active Technology Group uses vibrating-structure gyroscopes in active suspension designs. The company's system measures the load at the tyre contact patch once a millisecond and reacts to changes so a constant load is maintained. The VSG indicates when a road wheel is about to drop into a depression or rise over a bump and a hydraulic actuator is extended or retracted to keep the car body level.

This system is used in Arnold Schwarzenegger's Hummer, High Mobility Modular Wheeled Vehicle, but the price precludes its use in more popular cars. The servo valve on the actuator is an aerospace type, with an appropriate price tag, but if this could

Is ABS effective?

Research has shown that ABS is not often used in practice. Few drivers press the brake pedal hard enough to lock the wheels. In accident situations which demand hard braking drivers react in two stages: firstly a slightly harder than normal press of the pedal; then a heavier press when the situation is fully realised. Research also showed that if drivers reacted half a second earlier half of collisions would be avoided.

be manufactured in volume then active suspension would be seen on more vehicles.

Advances in car control system

It is a development of ABS that forms part of Mercedes' ESP. A brake booster is activated when brakes need to be applied by the system and ABS prevents wheels locking up. When ABS is activated, brake fluid is taken out of the system, so reducing pressure on the brake

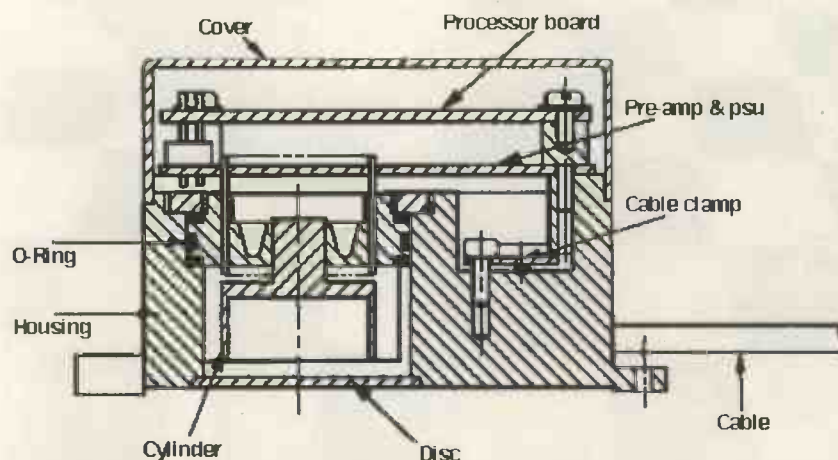


Fig. 3. Solid state construction makes the vibrating-structure gyroscope more robust than conventional mechanical types.

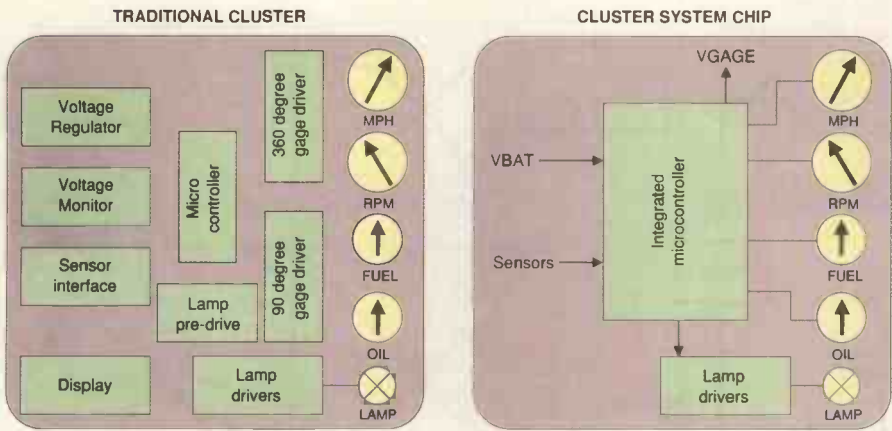


Fig. 4. Increasing microprocessor integration makes car electronics more reliable while improving compactness and maintainability.

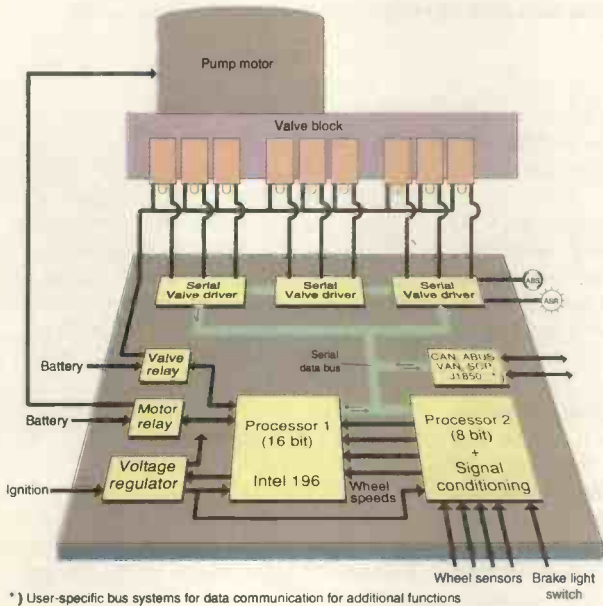


Fig. 5. In ITT's Teves Mk 20 ABS module, two processors – one of them 16 bits – work together, monitoring each other to eliminate the chance of a total loss of braking.

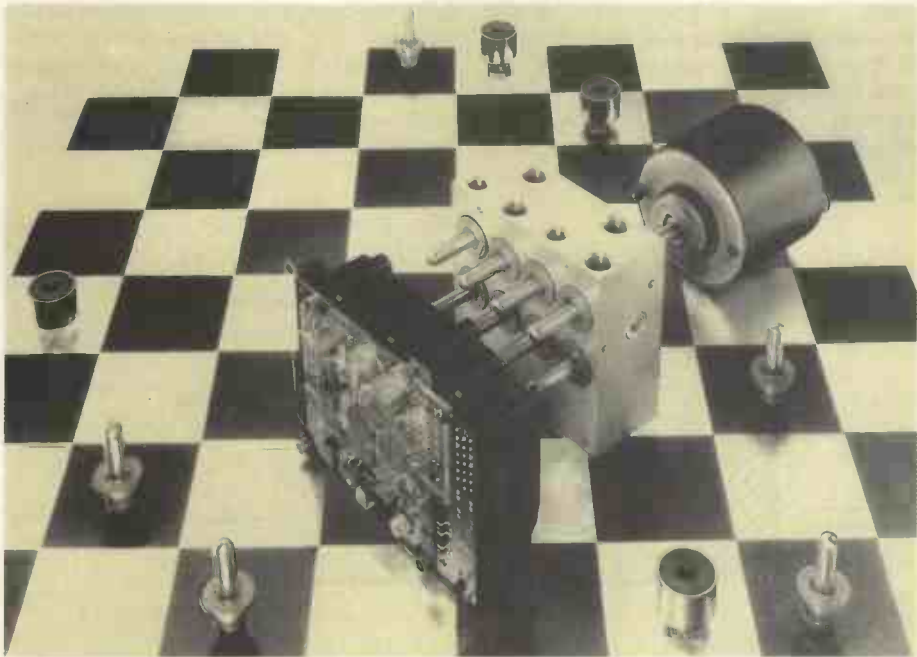


Fig. 6. ABS pump, electric motor, valves and a pcb containing two processors are all housed in a 16 by 10 by 10cm module – the Teves Mk 20 ABS system.

mechanism, be it disc or drum type. In an open system the brake fluid is returned into the master cylinder. In a closed system the fluid stays local to the wheel.

By the year 2000 ABS will be standard equipment on passenger cars according to a prediction from the Economist's Intelligence Unit. With 30% of cars fitted now, a compound growth for the technology of 22% per year is expected.

Against this background Texas Instruments recently announced a new customised microcontroller chip, the *cMCU370*. It will start to appear in a new design of ABS module from ITT subsidiary Alfred Teves, which is using some half dozen electronic subcontractors worldwide to assemble the modules.

TI has developed the microcontroller from the *TMS370* range of ICs. Sghaier Noury, TI's European Microcontroller Department Manager says: "It is part of a full product road map which includes many generations to come." The *cMCU370* has been designed under TI's Prism design methodology which evolved from a successful relationship with Delco Electronics. The principle of Prism is to steadily increase the number of functions that a chip can perform and to increase the different signal types it can handle, while using technology that has already been developed and proven, Fig. 4.

The *cMCU370* is an eight-bit device with a 16 bit version due next year and 32-bit architecture under development. At the launch of the new chip in Nice, TI also announced an agreement to supply ITT Automotive of Frankfurt with the product. The two companies have been co-operating for some six years using TI's knowledge of silicon and ITT's system experience. The *cMCU370* will be built into ITT's latest ABS module, the *Teves Mk 20*.

Under the agreement TI is expected to ship more than eight million microcontroller systems annually by 1997 rising to ten million by the year 2000. The first vehicles equipped with ABS using the new microcontrollers will be unveiled in 1996.

Teves' Mk 20 ABS module houses the electric motor, ABS pump, valves and pcb in a compact 16 by 10 by 10cm housing, Figs 5, 6. The system incorporates anti-skid control and electronic brake force proportioning. At the core of the hydraulic/electronic system is a lightweight aluminium block integrating the motor, pump and valves. Magnetic coils actuate the valves so there is no direct connection between controller and valve.

The pump conveys the brake fluid bled off by the ABS valves back to the master reservoir so the integration into one block saves installation time for the vehicle manufacturer.

Two microprocessor chips are carried on the pcb, a 16-bit Intel 196 and the Texas *cMCU370* 8-bit processor. These work together in 'asymmetrical redundancy' and monitor each other. This provides a high level of safety and protects against a failure which would open all the ABS valves, leaving the vehicle with no brakes.

Intel's chip processes the wheel speed and control algorithms. Complex mathematical formulae are written into the software, enabling the chip to calculate the best action to take from a given set of inputs. The TI chip simulates the calculations and then instructs the valve drivers. These are power semiconductors which replace the mechanical relays of previous designs and control current to the magnetic coils.

Within the pcb, the chips communicate via a serial data bus. This needs only three lines between each integrated circuit. The bits that make up each computer word are sent one after the other at a speed of two million bits per second. This communication system will link neatly into a vehicle's multiplexing harness whether the vehicle manufacturer has opted for CAN, ABUS, VAN, SCP or J1850 as the operating system.

Although both TI and ITT agree that multiplexing technology is both available and affordable, it awaits a change in outlook from the car manufacturers before being used regularly. There is also the consideration of higher after-care costs as a result of more complex systems.

The module could be a nucleus for the next project, a vehicle stability system. ITT Automotive anticipates its system arriving in the second half of the nineties.

More intelligence for ABS

Sensing the rotation of road wheels is a basic requirement of an ABS system and Siemens offers two sensor types – inductive and active. A toothed wheel is central to both systems. In the inductive version a magnet is fixed close to the wheel so as each tooth passes, the magnetic field is disturbed. These variations induce a current in a coil round the magnet

Fig. 7. Active speed sensor contains a highly sensitive inductive sensor combined with differential Hall IC to measure speeds almost down to zero. Output can be used for traction control, ABS and for driver information such as speed indication.

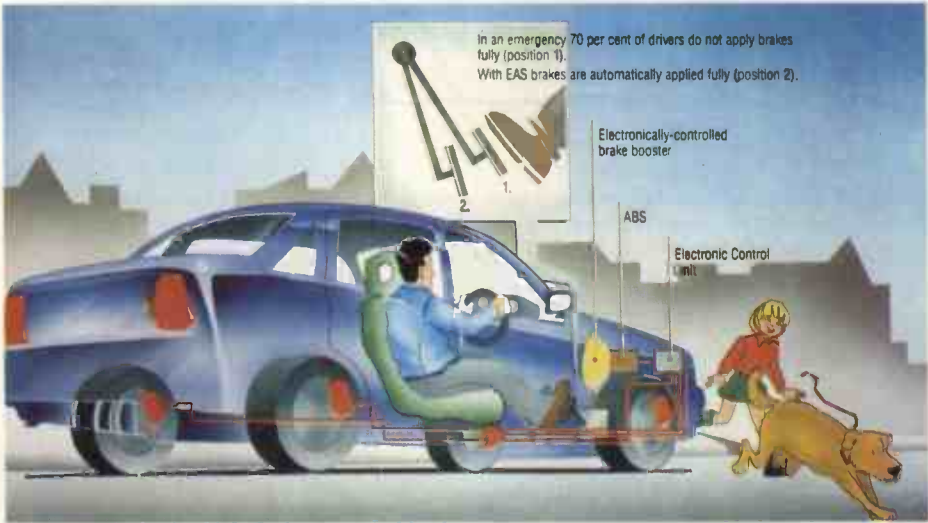
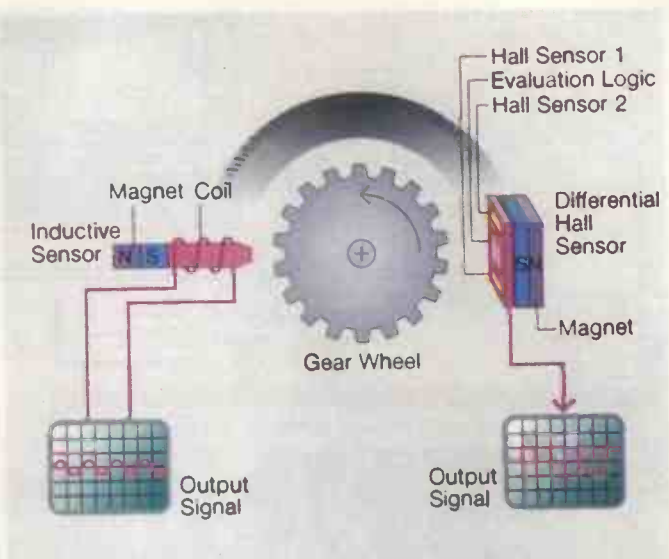


Fig. 8. One of the problems with ABS is that often, drivers only press the brake pedal hard enough to invoke ABS when it's too late. Lucas' new brake assistance system senses when the brake is pressed more rapidly than usual, and applies the brakes harder than would be the case if the pedal were depressed normally.

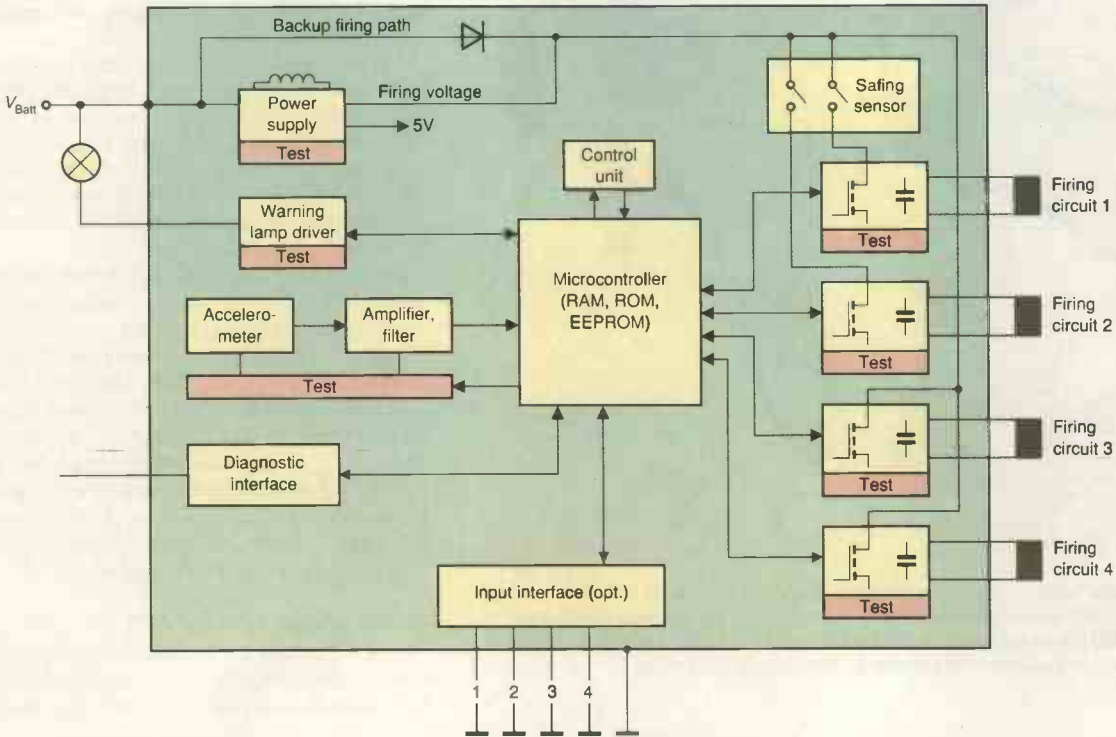


Fig. 9. Elements of a single-point sensing airbag electronic unit, courtesy Siemens. The system needs its own power supply in case the battery becomes disconnected due to the impact and there are multiple firing loops to cover for partial faults.

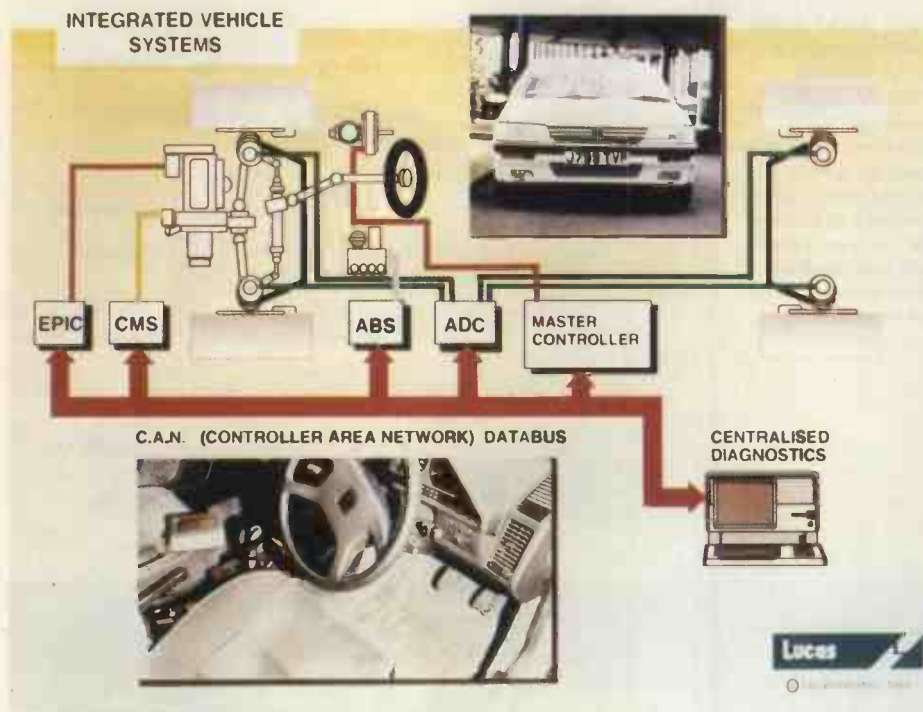


Fig. 10. Lucas's Advanced Prototype Vehicle, a Peugeot 605 turbo diesel, has completely integrated systems, controlled from a central processor via CANbus. EPIC is electronically programmed injection control and CMS is the clutch-management system.

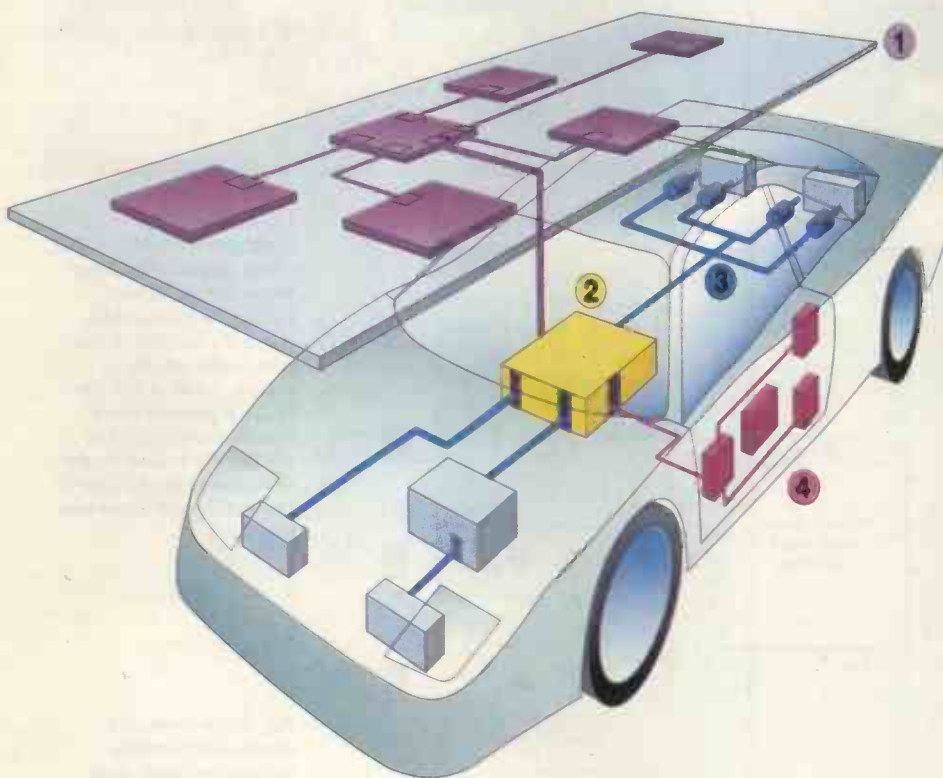


Fig. 11. With CANbus, cable harness requirements are greatly reduced since many switching and control signals can be multiplexed down one low-power bus. Conventional cabling for automatic windows, speakers, locking and mirror positioning means a lot of cabling between car and door, so this is one area where multiplexing is particularly attractive.

giving a sine wave output with each positive peak corresponding to a tooth on the wheel.

The active version, Fig. 7, uses a differential Hall sensor comprising two Hall switches and evaluation logic to provide a square wave output. In both systems the ABS computer counts the pulses and compares the result with time to provide an indication of road speed for the dashboard speedo and an indication of wheel lock to the ABS system.

Wheel bearing manufacturers are now producing intelligent bearings with on-board sensors and signal conditioning which reduces the effects of interference on the signal before it reaches the computer.

Grau's ABS system does not operate below 10km/h. This means that a stationary vehicle being held on a slope by the foot brake does not creep forward because the ABS system has detected an apparent wheel lock situation and reduces brake pressure.

To provide this extra margin needed to get round the drawbacks outlined in the ABS panel, Lucas is developing intelligent brakes. In an emergency, while the pedal may not be fully depressed, it is moved more quickly than normal. This can be detected and the signal used to operate an electronically controlled brake booster to apply the maximum servo force, Fig. 8. The controller compares pedal movements with the previous pattern of driver behaviour to assess an emergency situation. Operating the brake booster to its maximum invokes ABS, bringing the car to rest in the shortest possible distance.

This system could also work in conjunction with anti-collision radar, where microwaves or infra-red transmissions detect objects in front of a vehicle. The intelligence calculates when the distance is unsafe and, when intelligent cruise control is activated, reduces engine speed. Alternatively, the system can simply apply the brakes.

These electronic aids help when cars are well loaded with passengers or goods. The driver takes time to appreciate that longer braking is required in any given situation and may not have the space to stop in time. Intelligent brakes have an input from load sensors and the calculation includes the amount of load being carried.

Once all these functions are combined with a central computer, the brake holding system could also end hill start traumas.

Lucas's system has been developed within the Prometheus project. This concluded last year with a major demonstration of many new technologies at the Transport Research Laboratory. Prometheus – Programme for a European Traffic with Highest Efficiency and Unprecedented Safety – was a five year European initiative to develop automotive technology to a near-production state.

When it's too late for ABS

All these systems use electronics to help prevent accidents. When one does occur, the current spotlight is on airbags to protect the occu-

pants. Basically, an accelerometer triggers the airbag inflation valve during abnormal deceleration. While a crash takes several seconds to complete, airbags react in milliseconds. Practically there are many considerations which demand that airbag systems are computer controlled, Fig. 9.

The system needs its own power supply in case the car battery becomes disconnected. This amounts to energy storage for a matter of seconds but the storage system needs topping up, measuring and checking.

The whole system must be self-checking on start-up with an output to warning lamps for system failure. Multiple firing loops provide redundancy in case of a single failure. A safing sensor disarms the system during safe situations, so while the accelerometer looks for crash signals, the safing sensor looks for non-crash signals. Seat belt status and passenger presence may be monitored and there could be a communications interface for external diagnostic testing.

Besides the physical considerations, the software has to be rugged. Like ABS, airbags are safety critical – causing danger when they fail or operate unexpectedly. Software has to reflect this. In conjunction with the British Standards Institute and others, the Society of Motor Manufacturers and Traders has just issued guidelines for the software that will be used increasingly on vehicles.

Linking it all together

Connecting all these systems is the car wiring harness. On a Mondeo there's 1.5km of wiring. It takes two people to lift the harness on some American models. In addition, harnesses can be a problem when many switches are mounted in doors and arm rests.

The simple version of dedicated point-to-point wiring is a two-wire ring main carrying serial information and a ring main carrying power. Operating an instrument switch sends an address followed by an instruction. All devices on the network listen to the address and the unit which recognises an address as its own will then act on the next set of pulses and operate as required.

The traditional way of providing a device with an address is a bit switch. The device compares the address pulses with the bit switch setting and enables the device when the two coincide.

A specification called Controller Area Network, CANbus, has been developed by Bosch for networking in automotive applications and this has been recognised by the International Standards Organisation. CAN protocol uses a multi-master, contention based bus configuration for transferring communication objects between nodes on the network. Multiple access raises the problem of collisions of data on the network. This is resolved in CAN by sensing a carrier denoting the network is carrying traffic.

A communication object consists of an identifier plus control data segments. The control

segment contains all the information needed to transfer the message while the data segment contains up to eight bytes. Devices on the vehicle will only respond if their acceptance filter decides to receive a message. At each node the message identifier will have been set up in that controller's ram, Fig. 10.

The protocol can distinguish between permanent hardware failure and occasional soft errors. Defective nodes are switched off the bus, implementing a fail-safe procedure. To ensure robustness CAN uses non-return-to-zero bit coding. Ones and zeroes are indicated by a change in state, not the state itself. This produces fewer electromagnetic emissions at higher transfer rates than pulse width modulation or Manchester coding, which combine data and clock pulses.

One company manufacturing CAN control chips is NEC. Its μ PD72005 is a 52-pin flat package offering bi-directional two wire serial comms and two eight-bit i/o ports. Message memory space is 160 bytes and maximum data length is eight bytes – all of which highlights the relatively simple nature of car electronics compared with PCs.

Maximum transmission speed is 1Mbit/s. There are comprehensive error checking options including cyclic redundancy checking with a 15-bit crc generation polynomial, Fig. 11. The chip has been designed to fit into a large number of different networking configurations and the data book on it runs to some 96 pages.

Intel's CAN controller is the 44-pin 82527 fabricated in CHMOS III technology. Indicative of the harsh automotive environment, the 82527 copes with an ambient temperature range of -40 to +125°C.

In Russelsheim, Germany, Vauxhall says its car fitted with ISOTEC – Intelligent Safety and Orientation Technology – is currently being tested for reliability and suitability, before production sign-off. ISOTEC is a new research vehicle based on the recently launched Omega. On-board equipment includes distance radar, fog sensing, a night driving camera, and the latest navigation and guidance systems. Vauxhall says these are near-production electronic systems.

Distance measuring radar is connected to brakes, throttle and automatic transmission. The radar head is located behind the front bumper and detects other vehicles up to 140 metres ahead. Drivers can preselect a speed at which to travel and the distance radar will modify that according to the proximity of other vehicles. The required speed is selected on the indicator lever and a lamp in the speedometer indicates that speed.

When the Omega is too close to the vehicle in front, the distance controller first closes the throttle then applies the brakes. If the car reaches maximum automatic deceleration, an audible warning alerts the driver. Once the situation is stabilised the Omega automatically accelerates up to the preselected speed under guidance of the cruise control system.

Sensing obstacles by temperature

Infra-red is the technology used in the fog sensor. A beam of IR light from a black box mounted on top of the dashboard is reflected back by moisture droplets in the fog. The unit estimates the range of visibility, calculates a recommended speed and displays the figure on an led display once visibility falls below 200m. The fog sensor could be connected to the car's cruise control adjusting speed to visibility automatically.


An infra-red camera, located in the radiator grille of the Omega, records images of objects emitting heat. This applies to virtually all objects and the image is built up by making the screen brighter where more heat is being emitted. Should two objects be at the same temperature they will merge in the same way that similar tones merge in a conventional photograph, particularly when the scene is not well lit.

With infra-red systems it is possible to overlay the infra-red image with another taken by a conventional camera with light amplification. Combining the two technologies means that merged objects on one system will be separated on the other system. General Motors is assessing infra-red cameras in several high-way patrol police cars in America at the moment.


Infra-red is also used on the ISOTEC to receive route navigation information. A sensor positioned behind the rear-view mirror picks up infra-red light from beacons at the side of the road. Vauxhall is using the Euro-Scout system. The driver programmes in the destination and direction symbols appear on the special dashboard information display during the journey.

In the case of collision avoidance, the computer in the distance measuring radar will have a choice of reducing speed by closing the throttle, operating the brake or selecting another ratio in the automatic gearbox. Its chosen course of action will depend on road speed and closing speed as the vehicles approach each other. This means a continuous set of calculations to cause least disturbance to the car's occupants and to keep the car stable.

Electronics are pervading cars in other areas that are near to production: automatic gearboxes and clutches, automatic lane keeping, speed limiters, side impact detection for airbag systems, blind spot detection systems, electronic deadlocks, solid state tachographs and electronic dashboard displays. This is in addition to navigation systems, route guidance, traffic warning systems, electronic tolling, satellite telephones and road side displays. Plus the electronics in 'red-light' cameras and automatic number-plate reading. Not forgetting in-car entertainment with a serial link between the cd holder and player in the boot and the dashboard radio. And the smart cards in your wallet, and the black box 'flight recorder' available from Mannesmann Kienzle. No wonder we need electronic pace-makers. ■

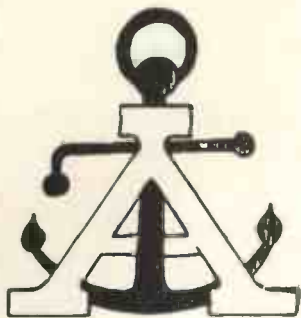

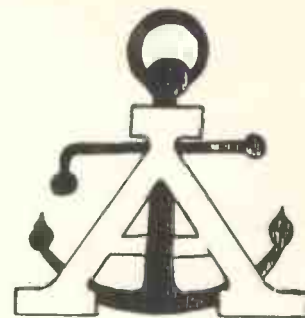ANCHOR SURPLUS LTD
THE CATTLE MARKET
NOTTINGHAM NG2 3GY
TEL: +44 (0115) 9864902/9864041
FAX: +44 (0115) 9864667



**OSCILLOSCOPE and
DIGITAL COUNTER SPECIAL OFFERS**

Iwatsu SS5416A "Synchroscope" 40MHz, 2 Trace, 2 Time Base £245
Gould OS4000 10MHz Digital Storage Scope, 2 Trace £325

HP1741A 100MHz Storage Scopes, 2 Trace, 2 Time Base Only £299

DIGITAL COUNTERS 25% OFF THESE PRICES FOR MAY '95 ONLY

Racal Dana 9904 Universal Counter Timer, 30MHz, 7 Digit LED £75
Racal Dana 9835 Universal Counter Timer, 30MHz, 6 Digit £50
Racal Dana 9838 Universal Counter Timer, 45MHz, 6 Digit £60
Racal Dana 9900 Universal Counter Timer, 30MHz, 6 Digit, Auto Range £75
Racal Dana 9913 200MHz, 8 Digit LED £95
Sabtronics 8000 100MHz, 8 Digit LED £95
Fluke 7620A Universal Counter Timer, 125MHz, 8 Digit LED £85
Racal Dana 9914 200MHz, 8 Digit LED £125
Racal Dana 9915 600MHz, 8 Digit LED £150
Racal Dana 9916 600MHz, 8 Digit LED £195
Syston Donner 6244A 512MHz, 8 Digit LED £150
Racal Dana 9015/11A Micro Computing Counter, 100MHz, 9 Digit + LED £250
HP 5334A Micro Computing Counter, 100MHz, 9 Digit + Math £275
Syston Donner 6054B 20MHz-24GHz, opt 13+18, 11 Digit LED £1050

A SELECTION OF OTHER INSTRUMENTS ON SPECIAL OFFER THIS MONTH ONLY

Marconi TF2603 RF Millivoltmeters, 1.5GHz, incl. Probe, Only £75
Solartron 7060 Systems Voltmeter, 6.5 Digit, IEEE, Only £195

**HP8660C + 86632A + 86603A 1Hz-2600MHz Signal Generator, AM/FM,
Excellent Condition, One Only £2250**

Marconi TF2300B, AM/FM Mod. Meters, 1200MHz £95
Marconi TF2120 Waveform Gens 0.001Hz-100KHz, Sine-Sq-Tri £195
Marconi TF893B Audio Power Meters £50
Racal Dana 9056/9058 Selective RF Analysers, 100MHz, Only £60

**Tritec Fase III Fusion Splicer + HSO II Heat Shrink Oven Optical Fibre Splice Kit
incl ALL accessories £1325**

IRD Mechanalysis 350M, Complete Set £145
IRD Mechanalysis 308, Complete Set £95

NOW OPEN SEVEN DAYS A WEEK

Monday to Friday: 9.00 am to 6.00 pm Saturday: 8.00 am to 4.00 pm
SUNDAY: 10.00 am to 4.00 pm

All prices are ex VAT & carriage.



**ALL ITEMS ARE TESTED WITH VERIFIED CALIBRATION AND COME
WITH OUR UNIQUE 30 DAY DAY UNCONDITIONAL WARRANTY**



Model software for *problem solving*

Allen Brown has been assessing the latest upgrade of a powerful modelling package capable – among other things – of solving equations analytically.

The low cost of powerful pcs hosting 486 or Pentium microprocessors, combined with highly visual graphics facilities, makes them very attractive tools for modelling applications. To match the performance of the pc, the engineer now has a variety of software modelling packages to choose from and one that merits consideration is *Maple V* from MathSoft of Massachusetts.

Now issued as Release 3, *Maple V* has over 2500 predefined operations and library functions, evokable as commands from the keyboard. These include such options as polynomial factorisation, equation solving, indefinite integrations and matrix manipulations. The package is capable of performing symbolic, numerical and graphical processing. In fact the 3D plotting is spectacular, and fast. *Maple* will work within dos or Windows although to access the full graphing features of the product a super-vga monitor, preferably with a graphics accelerator, is needed.

Maple V comprises three components: the kernel, the library and the interface. The kernel is the mathematical engine behind *Maple V*'s calculations. This is a compact, highly optimised set of routines written and compiled in the C programming language, and performs the large part of the basic computations done by the system.

Most of *Maple V*'s built-in procedures are written in the product's own programming language. Code written in *Maple V* is not compiled, but interpreted as it is read or entered, allowing users to create their own *Maple V* procedures interactively within the program. The interface is *Maple V*'s eyes to the world and defines, to a large extent, how the user interacts with the commands and procedures. In effect *Maple V* makes the whole discipline of mathematics more accessible for general usage such as engineering applications.

The method of entering instructions is by means of direct keying in commands. These commands form part of the native extensive command language. For example, to construct a sine function ranging from $-\pi$ to $+\pi$, you would enter on the prompt symbol (>),

```
> f(x) := (sin(2*Pi*x), x=-Pi..Pi);
```

Maple would respond by writing,

```
> f(x) := (sin(2πx), x=-π..πi);
```

All further operations on this function would refer direct-

```
> readlib(laplace);

proc(expr, t, s) ... end

> dif1 := L11*diff(i1(t), t$1) + L12*diff(i2(t), t$1) + R11*i1(t) = E, L22*diff(i2(t), t$1)
> ) + L12*diff(i1(t), t$1) + R22*i2(t) = 0 : fns := { i1(t), i2(t) };

fns := { i2(t), i1(t) }
```

```
> dsolve( {dif1, i1(0) = 0, i2(0) = 0}, fns );
```

$$i2(t) = \frac{\%2 e^{L12} e^{\left(\frac{1/2 - \%3 t}{L12^2 - L11 L22}\right)}}{\%4} + \frac{\%2 e^{L12} e^{\left(\frac{1/2 - \%2 t}{L12^2 - L11 L22}\right)}}{\%4}$$

$$i1(t) = -4 R22 \left(e^{L12^2} - e^{L11 L22} - \left(2 R11 R22 L12^2 + \frac{1}{2} L11^2 R22^2 - \frac{1}{2} \sqrt{\%1} R22 L11 + \frac{1}{2} \sqrt{\%1} R11 L22 - L11 R22 R11 L22 + \frac{1}{2} R11^2 L22^2 \right) \%2 e^{L11 L22} e^{\left(\frac{1/2 - \%3 t}{L12^2 - L11 L22}\right)} / (\%4 \sqrt{\%1}) - \left(-2 R11 R22 L12^2 - \frac{1}{2} L11^2 R22^2 + \frac{1}{2} \sqrt{\%1} R22 L11 - \frac{1}{2} \sqrt{\%1} R11 L22 + L11 R22 R11 L22 - \frac{1}{2} R11^2 L22^2 \right) \%2 e^{L12^2} e^{\left(\frac{1/2 - \%3 t}{L12^2 - L11 L22}\right)} / (\%4 \sqrt{\%1}) + \%2 e^{L12^2} R22 \sqrt{\%1} - R11 L22^2 \sqrt{\%1} + L11 R22 L22 \sqrt{\%1} + 4 R11 R22 L12^2 L22 - 2 L11 R22 R11 L22^2 + L11^2 R22^2 L22 + R11^2 L22^3 \right) e^{\left(\frac{1/2 - \%2 t}{L12^2 - L11 L22}\right)} L11 R11 L22 \sqrt{\%4^2} - \%2 e^{L12^2} (-2 L12^2 R22 \sqrt{\%1} - R11 L22^2 \sqrt{\%1} + L11 R22 L22 \sqrt{\%1} + 4 R11 R22 L12^2 L22 - 2 L11 R22 R11 L22^2 + L11^2 R22^2 L22 + R11^2 L22^3) e^{\left(\frac{1/2 - \%2 t}{L12^2 - L11 L22}\right)} R11 / \%4^2 \right) / (\%3 \%2)$$

```
%1 := 4 R11 R22 L12^2 - 2 L11 R22 R11 L22 + L11^2 R22^2 + R11^2 L22^2
```

```
%2 := L11 R22 + R11 L22 - \sqrt{\%1}
```

```
%3 := L11 R22 + R11 L22 + \sqrt{\%1}
```

```
%4 := -\sqrt{\%1} R22 L11 - \sqrt{\%1} R11 L22 + R11^2 L22^2 + 4 R11 R22 L12^2 - 2 L11 R22 R11 L22 + L11^2 R22^2
```

Listing 1. *Maple also produces analytical solutions to differential equations. This example shows the solution from a model of a simple transformer.*

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,
SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB

Telephone: 0181-900 2329 Fax: 0181-903 6126

OPEN Monday to Saturday.

Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE
HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR
LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt, Colleges, etc.
Orders accepted. Please allow 7 days for delivery. Prices quoted
are subject to stock availability and may be changed without notice.
TV and video parts sold as replacement parts.

Access & Visa Card accepted

WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND
TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.

TRANSISTORS

Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price	Part	Price
AAV32	9p	B0265	45p	BFY90	45p	MJ2501	100p	2N2102	50p	7815	25p	TIC236D	85p	AN315	210p
AC107	40p	B0267	45p	BLV48	85p	MJ2955	55p	2N2218A	24p	7818	25p	12A/400V	105p	AN316	350p
AC125	30p	B0269	45p	BR100	14p	MJ3000	100p	2N2219	24p	7824	25p	TIC246D	105p	AN360	100p
AC126	30p	B0278	50p	BR103	37p	MJ3001	100p	2N2221	23p	7905	25p	16A/400V	105p	AN362	140p
AC127	30p	B0311	100p	BR303	85p	MJE29A	30p	2N2222	23p	7906	25p	TIC253D	190p	AN366	150p
AC128K	30p	B0314	100p	BS574	14p	MJE30A	24p	2N2269	15p	7908	30p	10A/400V	160p	AN368	150p
AC141K	45p	B0315	150p	BSX20	15p	MJE340	25p	2N2484	15p	7912	30p	TIC263D	205p	AN3312	350p
AC176	22p	B0317	150p	BT100A	70p	MJE350	25p	2N2646	40p	7915	30p	25A/400V	205p	AN3821K	600p
ACV18	48p	B0331	40p	BT106	180p	MJE520	30p	2N2904	20p	7918	30p			AN3822K	600p
ACV19	48p	B0332	40p	BT109	90p	MP8112	45p	2N2905	20p	7924	30p			AN3900K	300p
AD149	60p	B0361	60p	BT119	100p	MPSA05	45p	2N2906	18p	7810S	24p			AN3991K	400p
AF125AD	30p	B0362	60p	BT146	90p	MPSA06	15p	2N2907	12p	78108	24p			AN5025	250p
AF139	30p	B0370	60p	BT179	140p	MPSA13	15p	2N3019	28p	7812	24p			AN5033	400p
AF239	30p	B0371	30p	BU105	80p	MPSA20	15p	2N3053	18p	7815	24p			AN5132	250p
BB105B	18p	B0410	30p	BU108	100p	MPSA42	15p	2N3054	18p	7818	24p			AN5150	400p
BB205B	24p	B0433	28p	BU109	80p	MPSA43	15p	2N3055	38p	78124	24p			AN5151	600p
BB207	8p	B0434	31p	BU110	90p	MPSA70	15p	2N3055H	50p	7910S	24p			AN5215	100p
BC109	8p	B0435	31p	BU111	100p	MPSA92	20p	2N3442	85p	79108	35p			AN5256	150p
BC182	8p	B0436	30p	BU124	60p	MPSA93	20p	2N3702	9p	7912	38p			AN5262	175p
BC109C	10p	B0437	28p	BU126	65p	MR510	30p	2N3703	9p	7915	35p			AN5265	80p
BC140	20p	B0438	36p	BU180	100p	MR856	36p	2N3704	9p	LM309K	100p			AN5352	600p
BC142	20p	B0439	36p	BU184	100p	OC28	350p	2N3705	9p	LM317T	100p			AN5411	450p
BC143	20p	B0440	40p	BU204	65p	OC29	250p	2N3706	9p	LM323K	350p			AN5421	150p
BC147	8p	B0441	40p	BU205	70p	OC31	350p	2N3707	9p	78H08KC	800p			AN5429	420p
BC149	8p	B0533	50p	BU206	70p	OC33	100p	2N3710	12p	79H12KC	700p			AN5512	100p
BC159	8p	B0534	38p	BU208	70p	OC45	50p	2N3711	12p	79HGKC	800p			AN5515	160p
BC160	30p	B0535	38p	BU208A	75p	OC200	180p	2N3771	85p					AN5520	550p
BC171	10p	B0536	38p	BU208AT	200p	R2008B	100p	2N3772	90p					AN5521	100p
BC172	10p	B0537	40p	BU208D	130p	R2010B	100p	2N3773	100p					AN5521	200p
BC177	14p	B0538	40p	BU209	90p	S2000A3	175p	2N3779	18p					AN5613	200p
BC178	14p	B0543	40p	BU225	120p	S2000AF	175p	2N3819	25p					CA3230K	150p
BC179	14p	B0545	50p	BU226	120p	S2055A	175p	2N3903	11p					CA3250	280p
BC182	7p	B0647	50p	BU312	90p	S2055AF	200p	2N3906	11p					CA3140E	38p
BC182L	7p	B0649	50p	BU325	55p	S2530A	100p	2N4031	25p					CA3160	85p
BC183	7p	B0675	40p	BU326A	75p	S2800M	72p	2N4401	12p					CA3189E	200p
BC183L	8p	B0676	40p	BU406	60p	TI29	15p	2N4403	12p					CA3193E	230p
BC184	8p	B0677	38p	BU406D	60p	TI23A	22p	2N4406	20p					CA3260E	170p
BC184L	8p	B0678	40p	BU407	55p	TI29C	25p	2N5088	20p					CA3260E	170p
BC212	7p	B0679	40p	BU407D	75p	TI29E	40p	2N5192	50p					CA3260E	170p
BC212L	7p	B0680	40p	BU408	60p	TI30	25p	2N5241	50p					CA3260E	170p
BC213	7p	B0681	40p	BU408D	75p	TI30C	25p	2N5245	45p					CA3260E	170p
BC213L	7p	B0682	45p	BU409	85p	TI31A	22p	2N5294	30p					CA3260E	170p
BC214	7p	B0705	40p	BU426A	70p	TI31C	27p	2N5296	30p					CA3260E	170p
BC214L	7p	B0707	50p	BU500	100p	TI32	22p	2N5448	12p					CA3260E	170p
BC237	7p	B0709	50p	BU505	90p	TI32A	21p	2N6107	40p					CA3260E	170p
BC238	7p	B0711	50p	BU505D	90p	TI32C	28p	2N6292	40p					CA3260E	170p
BC239	7p	B0736	50p	BU505DF	90p	TI33	50p	2N6385	120p					CA3260E	170p
BC300	20p	B0826	50p	BU506	100p	TI33C	60p	2N6403	160p					CA3260E	170p
BC301	20p	B0828	50p	BU506D	100p	TI33C	60p							CA3260E	170p
BC302	20p	B0839	55p	BU506DF	120p	TI34C	65p							CA3260E	170p
BC303	20p	B0897	50p	BU508A	90p	TI36C	65p							CA3260E	170p
BC304	25p	B0899	50p	BU508AF	95p	TI36C	65p							CA3260E	170p
BC327	7p	B0977	50p	BU508D	75p	TI41A	22p							CA3260E	170p
BC328	7p	B0978	50p	BU508DF	115p	TI41C	22p							CA3260E	170p
BC337	7p	B0985	60p	BU508V	110p	TI42A	22p							CA3260E	170p
BC338	7p	B0986	60p	BU508VDF	110p	TI42C	22p							CA3260E	170p
BC441	28p	B0993	50p	BU526	75p	TI47	40p							CA3260E	170p
BC446	8p	B0994	50p	BU536	100p	TI48	40p							CA3260E	170p
BC477	18p	B0992	100p	BU546	125p	TI50	60p							CA3260E	170p
BC516	25p	B1337	35p	BU608	120p	TI51	60p							CA3260E	170p
BC537	25p	B1617	30p	BU626	120p	TI52	60p							CA3260E	170p
BC546	25p	B1618	30p	BU705	130p	TI54	85p							CA3260E	170p
BC547	25p	B1619	30p	BU706DF	175p	TI505	65p							CA3260E	170p
BC548	25p	B199	80p	BU706F	150p	TI506	65p							CA3260E	170p
BC549	8p	B199	80p	BU801	70p	TI507	65p							CA3260E	170p
BC550	8p	B199	80p	BU806	70p	TI510	40p							CA3260E	170p
BC556	8p	B225	160p	BU807	60p	TI511	40p							CA3260E	170p
BC557	8p	B240	160p	BU808	60p	TI512	35p							CA3260E	170p
BC558	8p	B245	160p	BU809	60p	TI512H	50p							CA3260E	170p
BC559	8p	B254	160p	BU810	60p	TI515	30p							CA3260E	170p
BC560	8p	B255	12p	BU922	110p	TI516	30p							CA3260E	170p
BC567	20p	B256	18p	BU930	130p	TI517	30p							CA3260E	170p
BC639	20p	B257	18p	BU2508A	130p	TI520	37p							CA3260E	170p
BC640	20p	B259	18p	BU2508AF	130p	TI521	35p							CA3260E	170p
BC641	20p	B260	18p	BU2508D	130p	TI522	30p							CA3260E	170p
BC642	20p	B261	18p	BU2508DF	150p	TI525	30p							CA3260E	170p
BC643	20p	B262	18p	BU2520AF	225p	TI526	30p							CA3260E	170p
BC644	20p	B263	18p	BU2520DF	225p	TI527	35p							CA3260E	170p
BC645	20p	B264	18p	BU2525AF	325p	TI530	30p							CA3260E	170p
BC646	20p	B265	18p	BU2525DF	325p	TI531	30p							CA3260E	170p
BC647	20p	B266	18p	BU2525DF	325p	TI532	30p							CA3260E	170p
BC648	20p	B267	18p	BU2525DF	325p	TI533									

ly to $f(x)$. For example if a plot was required then you would enter,

```
> plot( f(x) );
```

The software responds by creating a 2D plot, autoscaled from $-\pi$ to $+\pi$. Alternatively by ending each line with a colon (:), you can effectively cascade a list of operations which are executed once the end semicolon (;) is reached.

All operations and functions are accessed in this way. However I must stress that the learning curve is quite steep. Owing to the low-level nature of *Maple V*'s command language, it is unforgiving and will require a fair amount of time and patience to master its rigid syntax.

Symbolic processing

It has often been said how useful it would be if computers could solve equations analytically, performing differentiations and integrations. Well, this software is able to perform just that. No matter how complex the equation, *Maple V* will find a solution – of sorts. It is very effective at expanding expressions, Fig. 1, and generating series terms, or for that matter factorising expressions.

With a package like this, one wonders why it is necessary to learn integration and differentiation techniques when the pc can find the answer in a fraction of the time. No more looking up tables to perform Laplace transforms and their inverse; *Maple V* performs these operations quite comfortably. However on occasions the answers do not agree with tabulated versions and it is difficult to know if there is an error or just an ambiguity. As expected, *Maple V* also performs numerical evaluations of equations and is particularly strong on the numerical evaluation of integrals and series.

Procedures

Maple V allows procedures to be created. These comprise a sequence of instructions. Like any other programming language, *Maple V*'s procedures incorporate conditionals, loops and exit loop conditions. The syntax is not too dissimilar to that of programming language Pascal.

An example of *Maple V* procedure is shown in Fig. 2. It calculates the transfer functions of different order low pass Chebychev filters. The iterative procedure shown for calculating the Chebychev coefficients from the recurrence relation is,


$$T_{n+1}(x) = 2xT_n(x) - T_{n-1}(x)$$

with starting conditions $T_0(0) = 1$ and $T_1(x) = x$. Although the procedures can be quite powerful they do have quite a steep learning curve associated with them and the syntax is very precise. However there are thousands of functions in the *Maple V* libraries which can be used within the procedure framework.

Solving differential equations

Maple V is quite effective for solving differential equations of any order. It will also solve coupled differential equations analytically, however the answer may appear to be somewhat unwieldy as illustrated in Fig. 3 which is a printout of the solution of circuit with mutual conductance – whoever said that transformer design was simple?

In line 2 *diff1* defines the coupled equations and line 3 performs the evaluation with the boundary conditions (no initial current in either the primary or secondary). Although not an immediately useful solution it does illustrate the analytical capability of *Maple V*. However by attaching numbers to the L, R and E values, numerical solutions will be produced. *Maple V* does not like nonlinear coupled differential equations to solve, in fact in several instances it refuses to do any

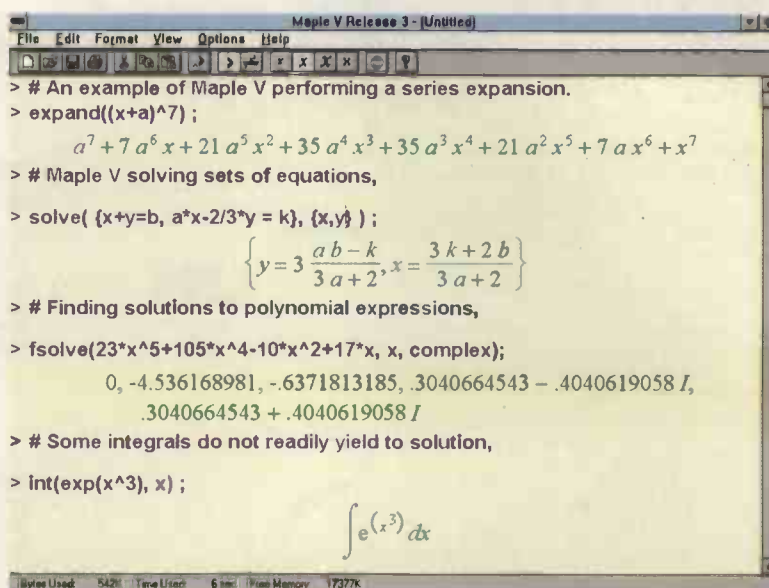

processing on them.

Old hacks at differential equations will know that there are several ways of solving them and *Maple V* offers the user the choice of a solution method. Electronics engineers would probably opt for using the Laplace Transform method for finding a solution and this is requested by augmenting the *dsolve* instruction by,

```
dsolve( diff_eq, y(x), method=laplace );
```


Although *Maple V* seems to tackle linear differential equations quite well, like a number of other maths software packages, nonlinear maths usually proves to be a little too testing and solutions are not always provided.

2D graphics

An essential aspect of any mathematical modelling package is its ability to generate graphs. These days such a task is no big deal as most numerical software can generate 2D graphs. An example of the 2D output from *Maple V* is shown in Fig. 2, displaying the Chebychev filter transfer functions with their characteristic ripples in the pass band. It is relatively easy to overlay several plots on the same graph and the scaling is performed automatically.

Fig. 1. Maple V is very effective at expanding expressions and generating series. In fact it performs many of the operations that an engineering student toils for hours over.

Fig. 2. Modelling performance of a Chebychev analogue filter is easy with Maple V. As seen in this example, increasing the number of poles improves the roll-off of the filter.

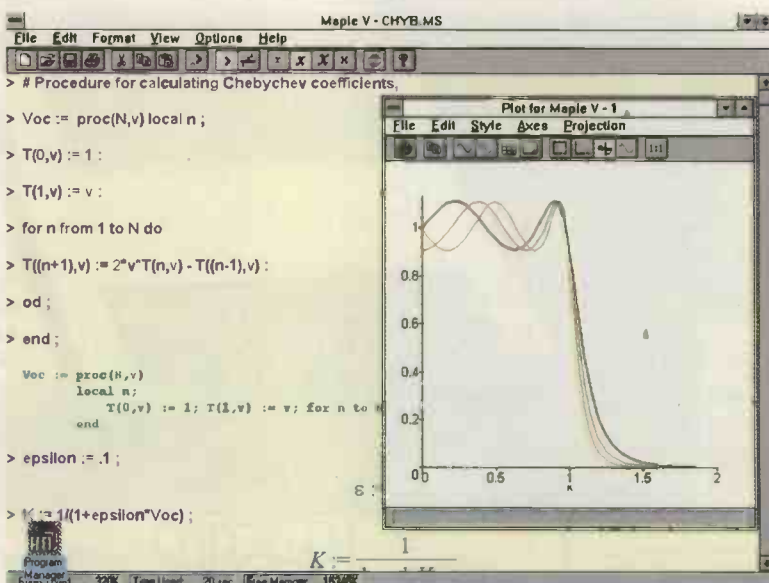


Finally an upgradeable PCB CAD system to suit any budget ...

Board Capture

BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

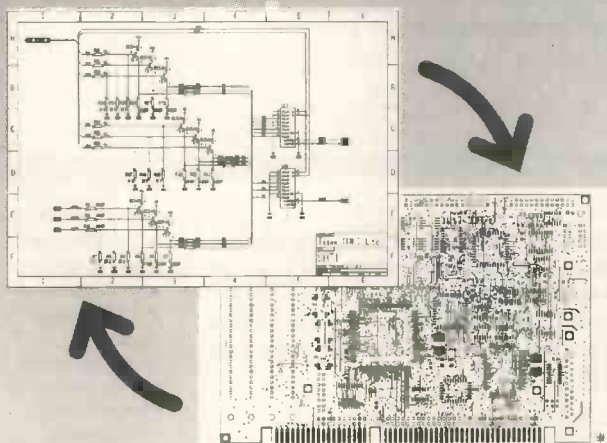

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCad, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

£395

BoardRouter

BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Contact Tsien for further information on
Tel 01354 695959
Fax 01354 695957



tsien

Tsien (UK) Ltd Aylesby House Wenny Road Chatteris Cambridge PE16 6UT

CIRCLE NO. 109 ON REPLY CARD

DEVELOPMENT AND PRODUCTION SOLUTIONS

- Gang Programmers
- Development Programmers
- Universal Cross Assembler
- Package Converters
- Development Tools
- Emulator Pods + Adapters



IRELAND 1-2800395
GERMANY 089/4602071
NORWAY 0702-17890
ITALY 02 92 10 35 54
FRANCE 1 69 30 13 79
SWEDEN 08 590 32185
Also from ELECTROSPED UK



mqp ELECTRONICS Ltd
Park Road Centre, Malmesbury, Wiltshire SN16 0BX UK
Tel: 01 666 825146 Fax: 01 666 825141
e/mail 100447.1124@compuserve.com

Ask for Free
Information Pack
and Demonstration
Discs

CIRCLE NO. 110 ON REPLY CARD

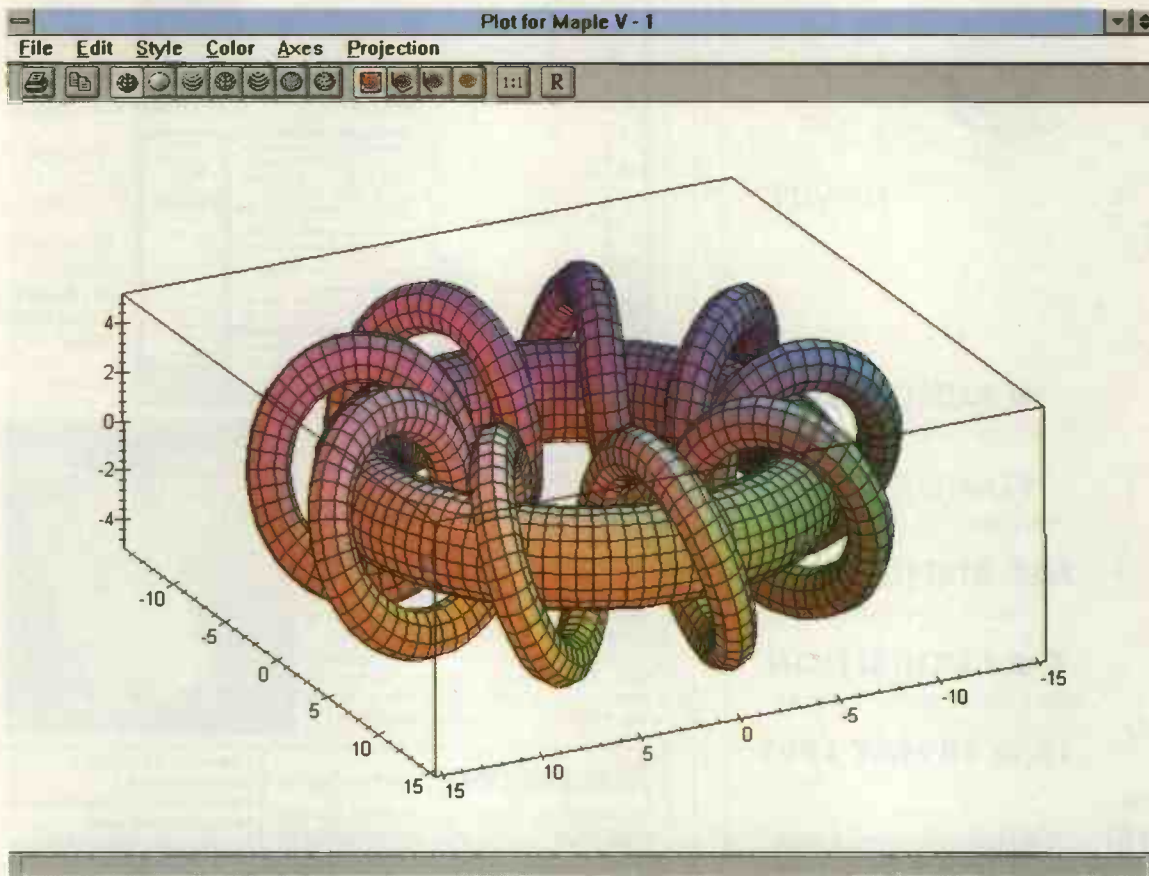


Fig. 4. 3D plot generation with *Maple V* can produce some fascinating solid modelling. Animation can also be added to the modelling to give an insight into temporal behaviour.

Provisions are available for plotting in cylindrical coordinates and performing contour plots. It would however be helpful if more control could be exercised on the plotting features, axis definition and labelling for example as it is likely that you will require a printing of 2D plots.

3D graphics

Features for performing the now commonplace function of 3D plotting are available in *Maple V*. But one of the extraordinary features of *Maple V* is its ability to plot in a variety of coordinate systems – spherical coordinates for example. This allows true solid modelling to be realised. For example, the complex mode structures in graded index optical fibres can be represented pictorially. They involve a lot of unfriendly

Bessel functions, however with *Maple V* they can become somewhat more accessible and easier to work with.

There is an impressive range of 3D plotting features but it does require a push of the imagination to realise their usage. The 3D surfaces also have a variety of colour shading as can be seen from the example given in Fig. 4; although pretty to look at, it is not terribly useful.

However if there was a need to model the 200MHz pulse propagation along pcb tracking, then *Maple V* could be used to determine the 3D impedance profiles along the length of the tracking (including reflections). Being able to visualise solutions such as these must be one of the main benefits of using modelling packages like *Maple V*.

Conclusion

There are very few areas of engineering where *Maple V* would not prove useful. Although the package is very powerful and undoubtedly applicable to a variety of modelling purposes a word of caution must be expressed.

New users must be prepared to spend a lot of time learning how to use the package proficiently. It will probably be several hours before they will be in a position to apply *Maple V*. A number of manuals are provided to help the learning process, including the Reference Manual and a Tutorial Introduction.

The Tutorial presents many examples, which are necessary for a package with such rigid syntax rules. Working through these manuals is an absolute must. There is also a well-designed screen-based tutorial which should prove helpful to the new user. Also available for *Maple V* are a number of text books written by third parties. It is certainly pleasing to know that if you have a pc on which you want to perform complex mathematical operations, *Maple V* will certainly put it through its paces and uses all of its memory and calculating power. ■

System requirements

A realistic minimum is,
33MHz 486-pc
SVGA monitor
Graphics accelerator, 256 colours
8Mbyte ram
10Mbyte hard disc space, excluding virtual memory
Laser printer
Windows 3.1

Source

Adept Scientific Micro Systems Ltd
6 Business Centre West
Avenue One
Letchworth.
Telephone: 0462-480055
Fax: 0462-480213
Cost £660 offer ex vat & carriage.

SEE THIS £50*

Interactive development,


EMBEDDED

easy to learn with

CONTROL

ready-made libraries.

COMPUTER

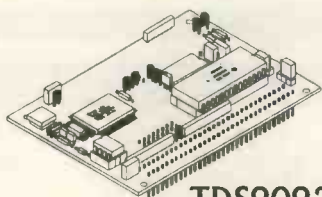

TDS9092

IN ACTION ON

Graphics display and keypad

STAND E33 AT

interfaces, 35 parallel and

NEC BIRMINGHAM

2 serial input/outputs,

C & I EXHIBITION

non-volatile memory etc. etc.

16 to 18 MAY 1995



**Triangle Digital
Services Ltd**

Tel 0181-539 0285

Fax 0181-558 8110

*100+ price. Starter Pack £150.

CIRCLE NO. 111 ON REPLY CARD

MicroTuner[®]


High quality
software FM

**Tuner
with
RDS
decoder**

£295

includes:

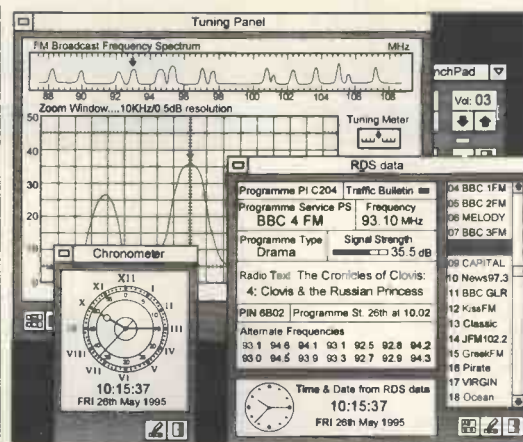MicroTuner
Software
DC supply
Serial cable
Aerial



Microsoft Windows compatible. Connects to PC via serial port. RISC microcontroller design, with full RDS decoding of PI, PS, PTY, TP, TA, AF, EON, RT and CT.

Indirect synchronisation of the PC to the Rugby MSF time standard.

Synthesised tuning in 10 KHz steps. Low noise dual gate MOSFET front end, with triple 10.7MHz ceramic filters. Signal strength with resolution 0.5dB. Frequency spectrum of 87.6 to 108.8 MHz can be printed out as hard copy.

Class AB output stage, to drive Line, Sound Card or Loudspeakers. Requires minimum of 386/25MHz (rec. 486/33MHz) with 4 Mbytes ram, 1Mbyte hard disk, running Windows 3.1



Microgen ELECTRONICS

43 Salisbury Road, Carshalton, Surrey
SM5 3HA Tel/Fax 0181 647 8238

Please add £4.50 p&p

Zero rated for VAT

Please make cheques payable to:

Microgen Electronics


Full specification available on request.

CIRCLE NO. 112 ON REPLY CARD

Premier
EDA Solutions

Desktop EDA for Windows

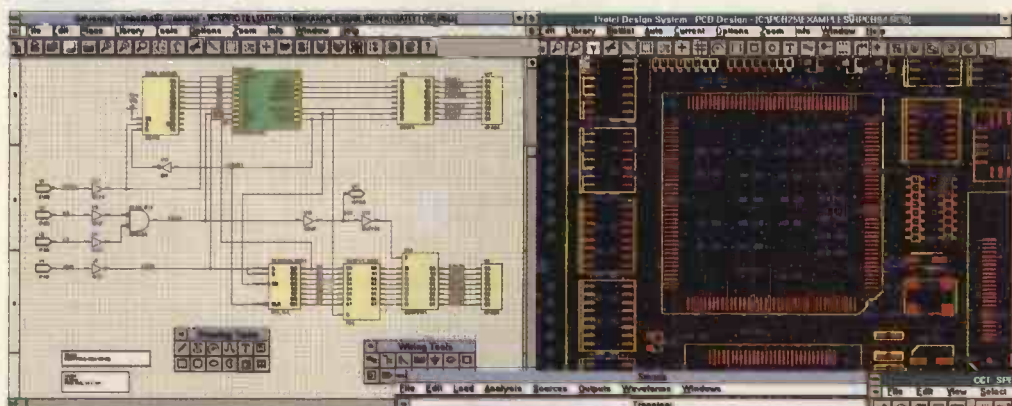First class solutions for electronic design automation



▲ Protel Technology, Advanced Schematic.

A complete design entry tool for Windows that gives you all the power you need. The 30+ different netlist outputs allow you to work with a variety of systems for PLD/FPGA programming, simulation, analysis & PCB layout. It will even directly read OrCAD schematics & libraries.

Dolphin Integration, SMASH.

A multi-level, mixed signal simulator. Allows simulation of analogue, digital and mixed signal circuits at a user-selectable level of abstraction - from simple SPICE libraries to full behavioural modelling.

◀ Protel Technology, Advanced PCB.

A full-featured, intuitive PCB design system, with support for all common PCB technologies from simple single-sided to complex multi-layer SMT designs. Advanced PCB also allows loading of PADS, PCAD, DXF & Gerber data.

Cooper & Chyan Technology, SPECCTRA.

Utilising powerful shape based algorithms, SPECCTRA's innovative rules-driven approach allows precise control. With optional modules allowing design for manufacture, fast circuit and interactive trace shove. SPECCTRA is leading the field of PCB autorouting. ▼

Premier EDA Solutions Ltd. 133 Cardiff Road, Reading, Berkshire. RG1 8ES.

Telephone: 01734 574 444. Facsimile: 01734 599 519.

Or see Protel in the CAD/CAM/CAE forum on CompuServe.

CIRCLE NO. 113 ON REPLY CARD

Why Wait for Windows EDA?

Best rf article '95

Following the success of 1994's Writers Award, **Electronics World** and **Hewlett-Packard** are launching a new scheme to run from January to December 1995.

Only articles which have an element of rf design will be eligible for consideration by the judging panel. It is hoped that this year's award will focus writer interest on rf engineering in line with the growing importance of radio frequency systems to an increasingly cordless world.

The aim of the award scheme is to locate freelance authors who can bring applied electronics design alive for other people.

Qualifying topics might include direct digital synthesis, microstrip design, application engineering for commercially available rf ICs and modules, receiver design, PLL, frequency generation and rf measurement, wideband circuit design, spread spectrum systems, microstrip and planar aerials... The list will hopefully be endless.

All articles accepted for publication will be paid for – in the region of several hundred pounds for a typical design feature.

Win a £4000
programmable signal
generator from
Hewlett-Packard



The prize for the coming year's award is a £4000 Hewlett-Packard HP8647A 1GHz programmable signal generator. It features HPIB interface, solid state programmable attenuator and built in AM-FM modulation capability.

For further details about our quest for the best, call or write to:
Martin Eccles, Editor, Electronics World,
Quadrant House, The Quadrant, Sutton,
Surrey, SM2 5AS
Tel 081-652 3128

It will be...PRECISELY!

It's common knowledge that the average PC Clock is not the most accurate time-keeping device. Until the DC-76 Atomic Controlled Clock!

Now your PC can be accurate to \pm one second in a million years. Synchronised to the atomic clock at Frankfurt Germany within a radius of 2,500 Km. Choose between serial/game-port versions. Software for Windows and DOS is standard. Drivers for Novel, OS/2, Warp, LAN Server, LINUX and SCO UNIX are optional. Installation is as easy as connecting a new mouse!



£79.00
+ Carr
& VAT


The DC-76 is complete, consisting of, receiver, connecting cable with software and user manual.

It's only available from ON-TIME SYSTEMS and fully supported right here in the UK! Call now to place your order! VISA and MasterCard accepted.

**ON-TIME SYSTEMS – Unit C5, Worth Corner,
Turners Hill Road, Pound Hill, West Sussex RH10 7SL**
Tel: 01293 886820 Fax: 01293 886821
Barnes Elliott Limited, Trading as ON-TIME SYSTEMS

CIRCLE NO. 114 ON REPLY CARD

COMPONENTS & SYSTEMS FROM IOSIS

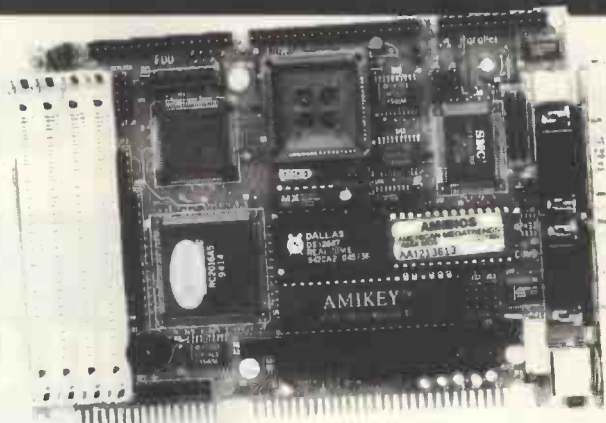

INDUSTRIAL SPEC COMPONENTS AND SYSTEMS
386SX-40 All-in-one CPU Board on PC half card from £215. Requires only display adapter and RAM to complete the core of a PC-compatible system. PC/104 or ISA bus expansion. PC/104 display adapter from £135. Desktop LCD mono VGA monitor with display adapter and passive back-plane from £499. Please enquire for complete systems. Prices exclude VAT and carriage.

2c Chandos Road, Redland, Bristol BS6 6PE, UK
Tel: 0117 973 0435 Fax: 0117 923 7295

CIRCLE NO. 115 ON REPLY CARD

PIC 16/17Cxx DEVELOPMENT TOOLS

High Specification PIC Tools from PARALLAX

ClearView In-Circuit Emulators




20-MHz in-circuit debugging for PIC 16C5x/64/71/84/..
Set breakpoints, step through code, modify registers.
Friendly DOS and Windows software.

From **£399** (separate units for "5x" and "xx" PICs)

PIC Programmer Pack

Programmer for PIC16C5x/64/71/84/..
Documentation on disk.
User supplied cables and power supply.


Just £89

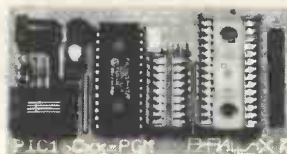

	Programmer Emulator	Assembler	Software Simulator	16C5x	16C64	16C71	16C84	17C42	Execution speed (MHz)	Programming Adaptors
PIC 16Cxx Programmer	•	•	•	•	•	•	•	•		ZIF, SOIC, SSOP
BackDraft 17	•	•	•	•	•	•	•	•		PLCC
ClearView '5x'	•	•	•	•	•	•	•	•	20	
ClearView 'xx'	•	•	•	•	•	•	•	•	20	

NEW BASIC STAMPS

Stamp-sized Computer Modules Run BASIC

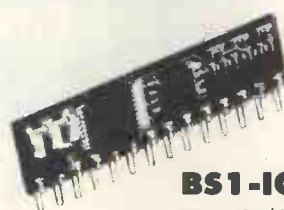


BS1-IC

8 I/O

100 line capacity: 4-MHz Clock

£29

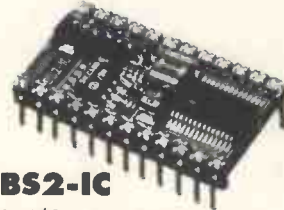


BS2-IC

16 I/O

600 line capacity: 20-MHz Clock

£49

Two **NEW** BASIC Stamp Controllers offering even more flexibility to Industry, Education and the Hobbyist. Both run Parallax "PBASIC" with familiar BASIC commands plus serial I/O, pulse measurement and button debounce. The BS2-IC includes additional support for LCDs, keypad, DTMF encoding/decoding, X-10 transmit and external time clocks. The BASIC Stamp programming package at £66 contains editor software, cables, manual and extensive application notes; everything you need to program Stamps using your PC.

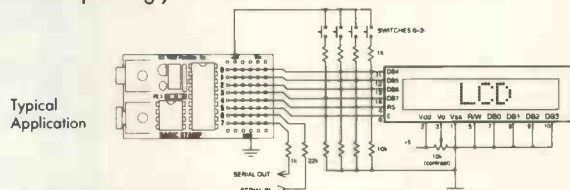

All prices exclude VAT and £3 shipping per order.
For further details on any of these products please phone for our new colour catalogue.

Milford House, 120 High Street,
SOUTH MILFORD, Leeds LS25 5AQ
Telephone 01977-683665 (24 hour) 01977-681465 (Fax)

CIRCLE NO. 116 ON REPLY CARD

MILFORD INSTRUMENTS

Fets versus bjts

the linearity competition

"Had bipolar transistors been invented before power mosfets, they would have been heralded as a major step forward in components for power amplification," suggests Douglas Self.

There has been much debate recently as to whether power fets or bipolar junction transistors (bjts) are superior in power amplifier output stages. Reference 1 is a good example. It has often been asserted that power fets are more linear than bjts, usually in tones that suggest that only the truly benighted are unaware of this.

In audio electronics it is a good rule of thumb that if an apparent fact is repeated times without number, but also without any supporting data, it needs to be looked at very carefully indeed. I therefore present my own view of the situation here, in the hope that the resulting heat may generate some light.

I suggest that it is now well-established that power fets, when used in conventional Class-B output stages, are a good deal less linear than bjts.² Gain deviations around the crossover region are far more severe for fets than the relatively modest wobbles of correctly biased bjts, and the shape of the fet gain-plot is inherently jagged, due to the way in which two square-law devices overlap.

The incremental gain range of a simple fet output stage is 0.84 to 0.79, range 0.05, and this is actually much greater than for the bipolar stages in Reference 2; the emitter-follower stage gives 0.965 to 0.972 into 8Ω , with a range of 0.007, and the complementary feedback pair gives 0.967 to 0.970 with a range of 0.003. The smaller ranges of gain-variation are reflected in the much lower thd figures when

PSpice data is subjected to Fourier analysis.

However, the most important difference may be that the bipolar gain variations are gentle wobbles, while all fet plots seem to have abrupt changes. These are much harder to linearise with negative feedback that must decline with rising frequency. The basically exponential I_C/V_{be} characteristics of two bjts approach much more closely the ideal of conjugate mathematical functions, — ie always adding up to 1. This is the root cause of the much lower crossover distortion.

Close-up examination of the way in which the two types of device begin conducting as their input voltages increase shows that fets move abruptly into the square-law part of their characteristic, while the exponential behaviour of bipolar devices actually gives a much slower and smoother start to conduction.

Similarly, recent work* shows that less conventional approaches, such as the common-collector/common-emitter configuration of Bengt Olsson, also suffer from the non-conjugate nature of fets. They also show sharp changes in gain. Gevel³ shows that this holds for both versions of the stage proposed by Olsson, using both N and P-channel drivers. There are always sharp gain-changes.

Class A stage

It occurred to me that the idea that fets are more linear was based not on Class-B power-amplifier applications, but on the behaviour of a single device in Class-A. You might argue that the roughly square-law nature of a fet's I_d/V_{gs} law is intuitively more 'linear' than the exponential I_C/V_{be} law of a bjt, but it is difficult to know quite how to define 'linear' in this context. Certainly a square-law device will generate predominantly low-order harmonics, but this says nothing about the relative amounts produced.

In truth the bjt/fet contest is a comparison between apples and aardvarks, the main problem being is that the raw transconductance (g_m) of a bjt is far higher than for any power fet. Figure 1 illustrates the conceptual test circuit; both a TO3 bjt *MJ802* and an *IRF240*

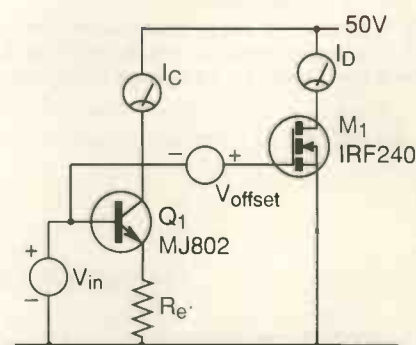


Fig. 1. Linearity test circuit. Voltage V_{offset} adds 3V to the dc level applied to the fet gate, purely to keep the current curves helpfully adjacent on a graph.

power fet have an increasing dc voltage, V_{in} , applied to their base/gate, and the resulting collector and drain currents from PSpice simulation are plotted in Fig. 2.

Voltage V_{offset} is used to increase the voltage applied to fet M_1 by 3.0V because nothing much happens below a V_{gs} of 4V, and it is helpful to have the curves on roughly the same axis. Curve A, for the bjt, goes almost vertically skywards, as a result of its far higher g_m . To make the comparison meaningful, a small amount of local negative feedback is added to Q_1 by R_e . As this emitter degeneration is increased from 0.01 to 0.1 Ω , the I_C curves become closer in slope to the I_d curve.

Because of the curved nature of the fet I_d plot, it is not possible to pick an R_e value that allows very close g_m equivalence; a value of 0.1 Ω was chosen for R_e , this being a reasonable approximation; see Curve B. However, the important point is that I think no-one could argue that the fet I_d characteristic is more linear than Curve B.

This is made clearer by Fig. 3, which directly plots transconductance against input voltage. There is no question that fet transconductance increases in a beautifully linear

* The subject of an article by Douglas to be published in *EW+WW* in the near future — Ed.

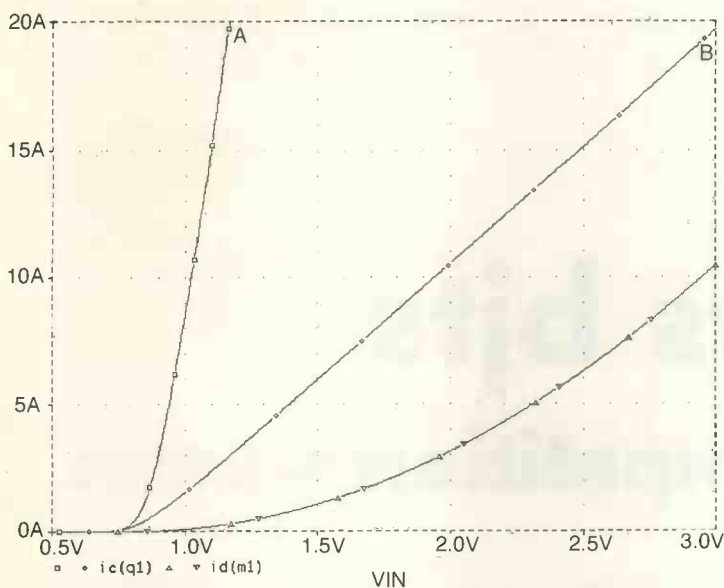


Fig. 2. Graph of I_c and I_d for the bjt and the FET. Curve A shows I_c for the bjt alone, while Curve B is the result for $R_e=100m\Omega$. The curved line is the I_d result for a power fet without any degeneration.



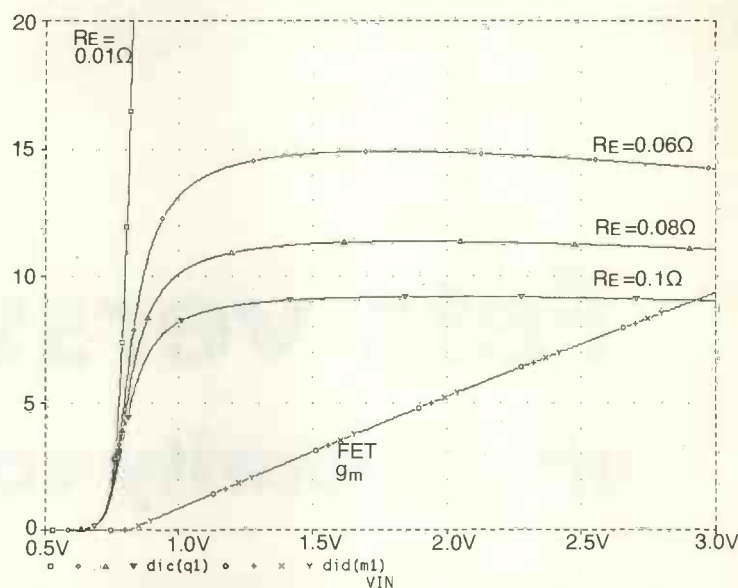


Fig. 3. Graph of transconductance versus input voltage for bjt and fet. The near-horizontal lines are bjt g_m for various R_e values.

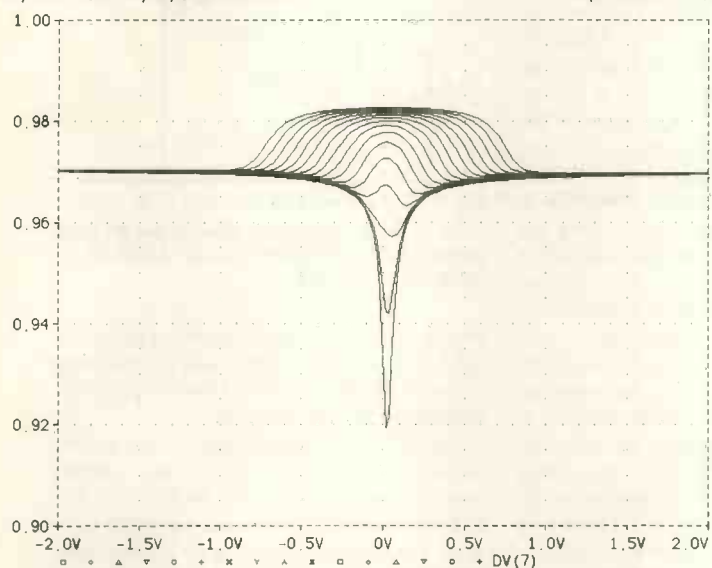OUTPUT4C.CIR CFP O/P, MPSA42/92, MJ802/4502, $R_e=0R22$, $V_{bias}= 18/6/93$
Date/Time run: 08/04/93 23:42:02 Temperature: 25.0



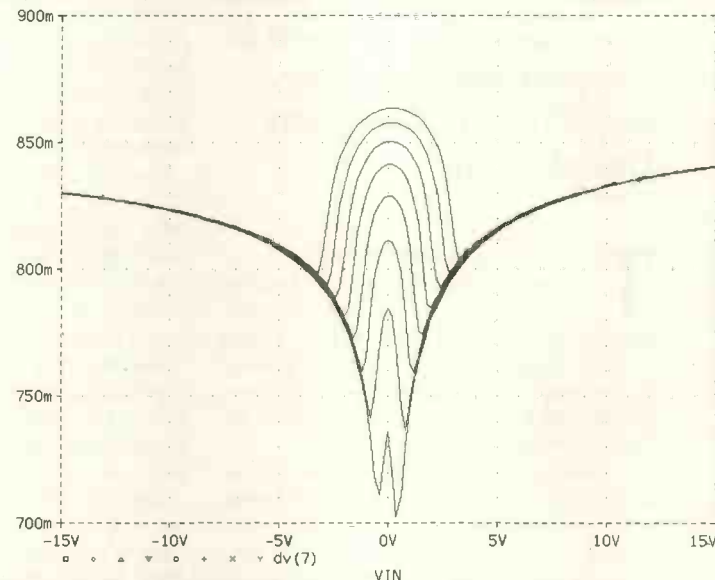OUTFET.CIR FET O/P stage, voltage drive; 2SK135/2SJ50, 14/6/93
Date/Time run: 08/05/93 21:32:19 Temperature: 25.0



Left are curves for a bipolar complementary feedback pair, crossover region $\pm 2V$, V_{bias} as a parameter. Fourth curve up provides good optimal setting – compare with curves on the right, for a fet source follower crossover region with $\pm 15V$ range.

manner- but this 'linearity' is what results in a square-law I_d increase. The near-constant g_m lines for the bjt are a much more promising basis for the design of a linear amplifier.

To forestall any objections that this comparison is nonsense because a bjt is a current-operated device, I add here a small reminder that this is untrue. The bjt is a voltage operated device, and the base current that flows is merely an inconvenient side-effect of the collector current induced by said base voltage. This is why beta varies more than most bjt parameters; the base current is an unavoidable error rather than the basis of transistor operation.

The PSpice simulation shown was checked against manufacturers' curves for the devices,

and the agreement was very good – almost unnervingly so. It therefore seems reasonable to rely on simulator output for these kind of studies; it is certainly infinitely quicker than doing the real measurements. In addition, the comprehensive power-fet component libraries that are part of PSpice allow the testing to be generalised over a huge number of component types without you needing to buy them.

To conclude, I think it is probably irrelevant to simply compare a naked bjt with a naked fet. Perhaps the vital point is that a bipolar device has much more raw transconductance gain to begin with, and this can be handily converted into better linearity by local feedback, ie adding a little emitter degeneration.

If the transconductance is thus brought down roughly to fet levels, the bipolar has far superior large-signal linearity. I must admit to a sneaking feeling that if practical power bjts had come along after fets, they would have been seized upon with glee as a major step forward in power amplification. ■

References

1. Hawtin, V., Letters, *EW+WW* Dec 1994, p.1037.
2. Self D., 'Distortion In Power Amplifiers', Part 4, *EW+WW*, Nov 1993, pp 932-934.
3. Gevel M., Private Communication, Jan 1995.

TOROIDAL TRANSFORMERS

High Quality Low Prices

In addition to our standard range we will be pleased to quote for your special requirements.

PRICE LIST

VA	Mail Order	Quantity Price Excluding VAT & Carriage				
		2+	10+	25+	50+	100+
15	14.59	10.21	7.69	5.69	5.52	5.35
30	16.04	11.23	8.45	6.25	6.06	5.89
50	17.83	12.48	9.40	6.95	6.74	6.53
60	18.02	12.61	9.49	7.02	6.82	6.61
80	17.98	12.60	9.49	7.02	6.81	6.60
100	21.07	14.74	11.11	8.21	7.96	7.72
120	21.54	15.08	11.35	8.39	8.15	7.89
150	25.98	18.19	13.70	10.12	9.82	9.53
160	23.83	16.68	12.56	9.28	9.00	8.73
225	30.10	21.07	15.87	11.73	11.39	11.04
300	34.32	24.02	18.09	13.38	12.98	12.58
400	46.19	32.32	24.35	17.99	17.47	16.94
500	50.48	35.34	26.61	19.67	19.09	18.51
625	53.09	41.36	31.14	23.02	21.24	20.57
750	58.39	44.23	33.30	24.62	23.89	23.17
1000	78.80	55.16	41.54	30.70	29.80	28.89
1200	82.45	57.72	43.46	32.12	31.17	30.23
1500	105.10	73.63	55.40	40.94	39.74	38.53
2000	114.45	96.13	72.39	53.51	51.93	50.36
2500	163.04	114.13	85.94	63.51	61.64	59.79

These prices are for 240volt primary and two equal secondaries with 8" colour coded fly leads. Each transformer is supplied with a mounting kit (steel dish washer pads, nut and bolt) Mail order prices include vat and postage. Please do not hesitate to telephone or write with your particular requirements.



Airlink Sales Co

16 Knight Street, Sawbridgeworth, Herts CM21 9AT

Tel: 01279 600139 Fax: 01279 726379

CIRCLE NO. 117 ON REPLY CARD


HEWLETT PACKARD HP71B

As easy to use as a calculator but as powerful as a computer

BARCODE READER

Smart wand

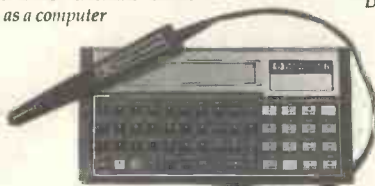Automatically recognises and decodes all major bar-code standards.



- A powerful set of basic functions, statements and operators - over 230 in all - many larger computers don't have a set of basic instructions in this complete.
- Advanced statistics functions enabling computations on up to 15 independent variables.
- Recursive subprograms and user defined functions.
- An advanced internal file system for storing programs and data - the HP71B has continuous memory - when you turn the computer off it retains programs and data.
- A keyboard that can be easily customised for your specific application.
- HP-IL Interface pre-installed to create a system that can print, plot, store, retrieve and display information. Control or read instruments or speak to other computers, 5000 bytes/sec. Built in ROM includes 46 separate commands. Interface to HP-IL, HP-IB, RS232C, GPIO or series 80. Includes connection cables.

These are second user systems ex DHSS are fully tested and working but have no programming (THAT IS UP TO YOU)

HP71B	£29.95
Bar-code Reader	£12.95
AC Power Supply	£4.95
(Works from batteries normally)	
Keyboard Overlay	£1.00
(Limited quantities)	
Unknown Program - Memory	
Modules (2 different types)	£3.00
(Limited quantities)	
Complete kit of HP71B, Bar-code Reader and power supply	£39.50

(Prices include VAT - delivery £3.00)
(Currently selling in USA for US\$500)
Allow 7 days for delivery

SPECIAL OFFER

Buy 2 Kits For £59.00

Other products at give-away prices

Numeric keypad for 'AT' computer

£5 + £2 Carriage (Carriage FREE if ordered with above).

INTERCONNECTIONS LTD

Unit 41, InShops, Wellington Centre, Aldershot, Hants GU11 5DB

Tel: (01252) 341900 Fax: (01293) 822786

CIRCLE NO. 118 ON REPLY CARD

"moving from schematic to layout could not be easier"

Electronics World & Wireless World Jan 1995

NEW
Extended
Library
Pack Just
£39.00!

quickroute 3.0

Integrated Schematic and PCB Design for Windows 3.1

DESIGNER £99


*Schematic & PCB Drawing *1/2 layer auto-router *Supports Windows printers/plotters *Full set of libraries *Clipboard support *Designer Special (manual on disk) also available.

PRO £199


*Schematic & PCB Design *Schematic Capture *Integrated Rats-Nest Generation *1-8 layer Auto-router (faster than Designer) *Net-List Export *Supports Windows printers/plotters *CAD-CAM outputs.

PRO+ £299

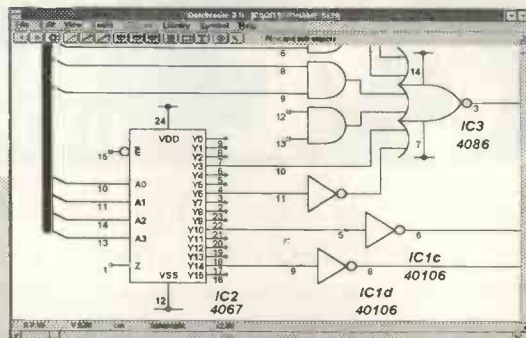As the PRO but also includes *Advanced Schematic Capture (Busses, Power rails, etc) *Larger Schematic & PCB Designs *Gerber file IMPORT for File Exchange *Extended libraries including Surface Mount, CMOS, etc.



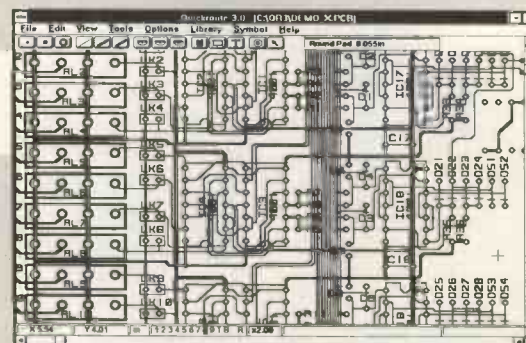Busses & power rails handled using Global Nets on PRO+



Integrated Schematic & PCB Design.

POWERware, 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, U.K.

Tel/Fax 0161 449 7101


CIRCLE NO. 119 ON REPLY CARD

*Prices exclude P+P and V.A.T. *VISA/MasterCard Accepted *Network versions available.

FREE
Demo
Pack
Available.

Electronic Designs Right First Time?

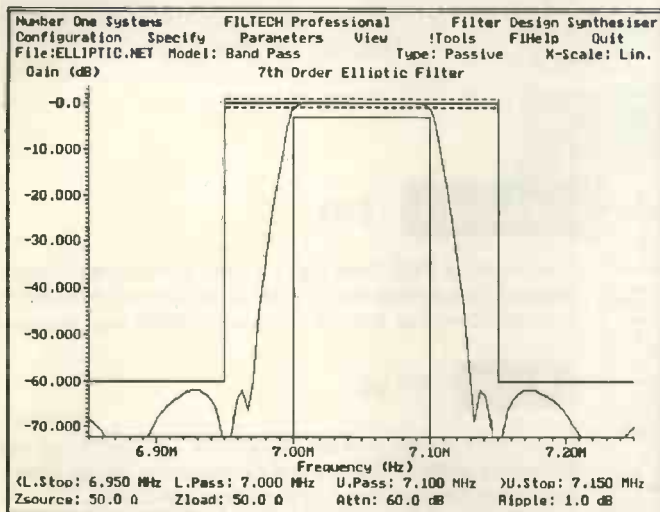Active and Passive Filter Design - FILTECH -



From only £145!

Visa, Delta, Switch, MasterCard
and American Express welcome

Affordable Electronics CAD

LAYAN: Electromagnetic Layout Simulator. Links to EASY-PC Pro' XM and ANALYSER III Pro'.	£495.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links to ANALYSER III and PULSAR.	From £195.00
PULSAR: Digital Circuit Simulator	From £98.00
ANALYSER III: Linear Analogue Circuit Simulator	From £98.00
Z-MATCH for Windows: Smith Chart based problem solving program for R.F. Engineers	£245.00
FILTECH: Active and Passive Filter design	£145.00
FILTECH Professional: Enhanced Filter Design Program including Elliptic Filters (up to 12th order)	£245.00
EASY-PC: Entry level PCB and Schematic CAD	£98.00

Technical Support FREE for life! Prices exclude P&P and VAT.

Special discount schemes for education

Number One Systems

Ref: WW, Harding Way, St. Ives,
Huntingdon, Cambs. PE17 4WR, UK.

For Full Information Please Write, Phone or Fax

Tel: +44 (0) 1480 461778

Fax: +44 (0) 1480 494042


CIRCLE NO. 120 ON REPLY CARD



**CHELMER
VALVE
COMPANY**

*If you need Valves/Tubes or RF Power
Transistors e.t.c. ... then try us!*

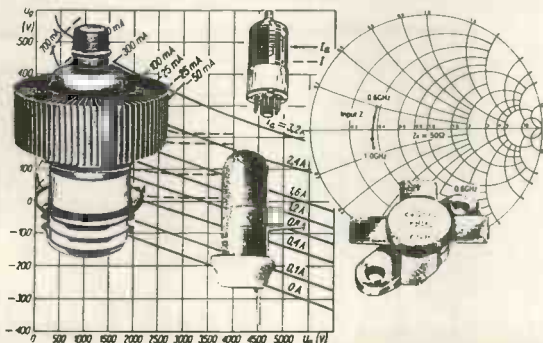We have vast stocks, widespread sources and
33 years specialist experience in meeting our
customers requirements.



Tuned to the needs of the Professional User

Chelmer Valve Company, 130 New London Road,
Chelmsford, Essex CM2 0RG, England

44-01245-355296/265865

Fax: 44-01245-490064

CIRCLE NO. 121 ON REPLY CARD

the new

CRICKLEWOOD Electronics
Very Interesting CATALOGUE

**ASTRONOMICAL RANGE AT
DOWN TO EARTH PRICES**

- TRANSISTORS+ICs+SEMICONDUCTORS
 - RESISTORS+CAPACITORS+INDUCTORS
 - SURVEILLANCE+SECURITY+SECURITY
 - PLUGS+SOCKETS+LEADS+CONNECTS
 - TV & VIDEO SPARES (inc Video Heads)
 - HIFI+DISCO+HIFI GADGETS+SPEAKERS
 - AUDIOPHILE COMPONENTS (inc Capacitors)
 - IN CAR AUDIO+SPEAKERS (inc Bass tubes)
 - COMPUTER ACCESSORIES+BOARDS
 - TOOLS+TEST EQUIPMENT+BENCHWARE
- & much much much more (over 10,000 lines).*

SEND TODAY FOR *THE VERY INTERESTING CATALOGUE*
Pay by PO, Cheque, Credit Card or tape Coins to Paper

Please send mecopies of the 1995 Cricklewood Catalogue.

I enclose £2.50 per copy (UK & Europe). £5.00 overseas

Name.....

Address.....

.....

.....

.....

Please Charge my Credit Card no.....

Expiry Date.....Tel no..... WW

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway
London NW2 3ET Tel 0181 450 0995 Fax 0181 208 1441

CIRCLE NO. 122 ON REPLY CARD

Delayed audio signals

*Too many audio designs are deeply flawed in the bass, says **Ben Duncan**, recalling recent work of Douglas Self and Edward Cherry. Here Duncan uses simulation to explain the reasons and ramifications for the entire audio chain.*



Dependence of the quality of reproduced sound on the number of components through which it is passed still seems to be doubted by some commentators¹. But how many have actually bothered to examine exactly what happens to a given signal between the mic terminals – via multitrack recording process and recording media – and its emergence from a domestic power amplifier?

A realistic record-to-reproduction path could include six gain stages with dc blocking in input and feedback paths; three high pass (–12 and –18dB/octave) filters; and 52 other dc blocking capacitors, Fig. 1. In a typical consumer grade path, capacitor values for assorted random f_{3Ls} ($\omega_{low}/2\pi$) will be centered around 4-6Hz, and up to 16Hz. In fact this is a specification that is becoming increasingly prevalent even in supposedly professional equipment.

Analysing the frequency responses of 50 of these paths, Fig. 2, at different points shows the gain stages, high pass filters and buffers to range from –3dB, at from below 3Hz, up to 63Hz in the worst case. Uncorrected response at the end of the chain is –3dB at 45-200Hz.

This doesn't mean that bass is absent by so much: it is

Fig. 1. Over 70 cascaded RC high-pass elements model a complete (electronic portion of an) audio record-to-reproduction path. Capacitor tolerances are engaged to simulate random equipment combinations, as well as tolerance, temperature and drift variables.

compensated for during the recording production process. But compensatory equalisation means the real path experiences even more phase corruption.

The figures nonetheless suggest the kind of roll-off commensurate with the delay and waveform distortion existing.

Delay problems can be appreciated by examining the contribution of a solo gain stage, Fig. 3. Just this one type of stage clearly exhibits more delay than the 52 buffers (otherwise the sum would exceed the upper plots in Fig. 3).

The effect of this aurally significant delay is mistiming of

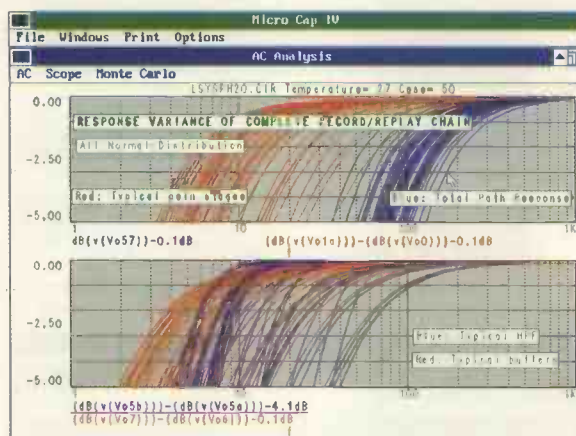


Fig. 2. Unequalised frequency responses of a possible complete consumer-grade audio reproduction path (upper panel, blue plots). Upper panel red plots, and blue and red lower panel plots, show typical responses of constituent gain stages, high-pass filters and buffers. Each Monte Carlo run represents myriad design differences, as nearly all audio chains are made from effectively random equipment assemblies. There are no standards for f_{3L} . Y axis is decibels.

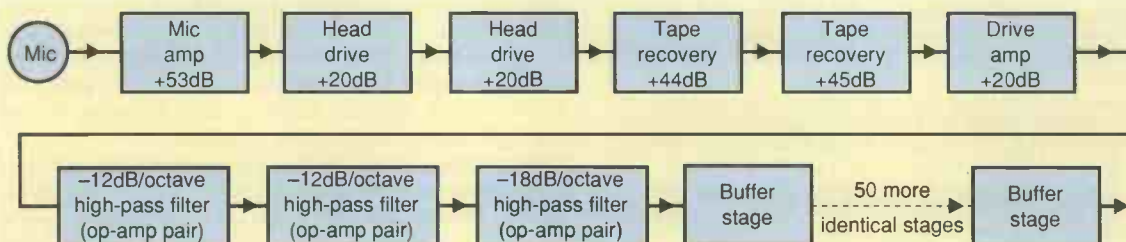


Fig. 3. Group delay vs frequency, individual and total, for a complete, consumer-grade reproduction path. Note the convergence on linearity only at extreme frequencies. Y-axis is milliseconds of delay.

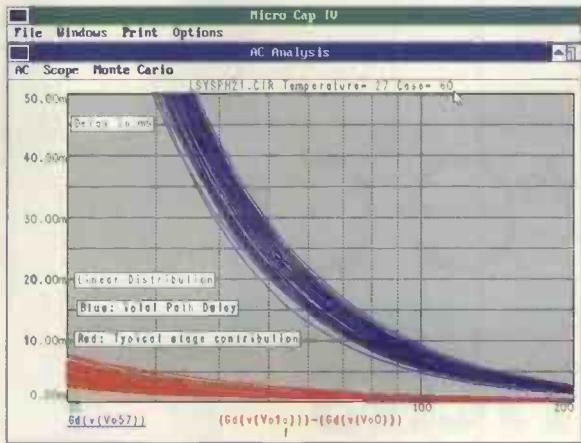


Fig. 4. The BDR method: like Fig. 2, but with 100 times less signal delay. Note Y-axis scale change.

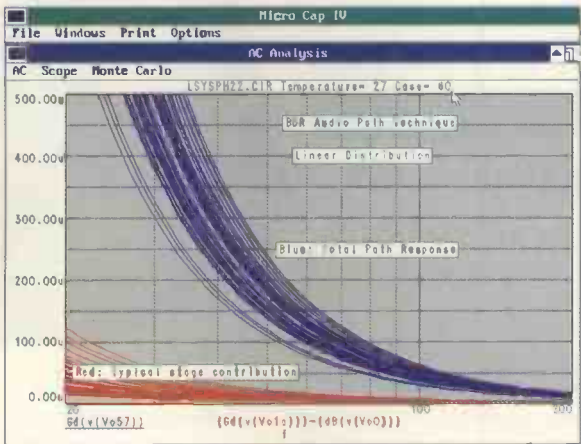


Fig. 5. Complete consumer path again. A pulse goes down the chain, with just five Monte Carlo runs for clarity. The emerging wave should not seem 'suitable for its intended purpose'. Fortunately, music productions only occasionally comprise such waveforms and 'data corruption' to the ears may be less fundamental than it appears to the eyes. Y-axis is volts.

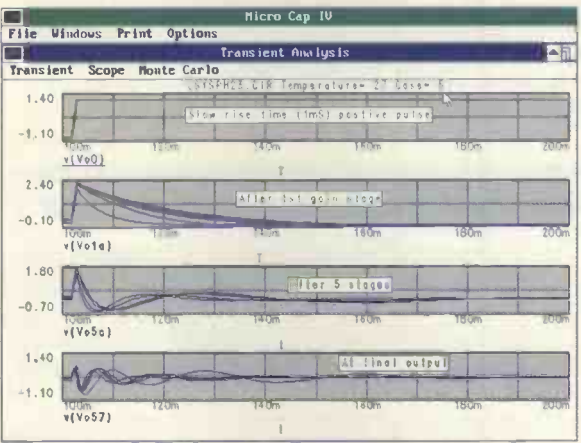


Fig. 6. Keeping the pulse. How bdr handles a pulse – something that looks very like the input pulse emerges at the output (lowermost).

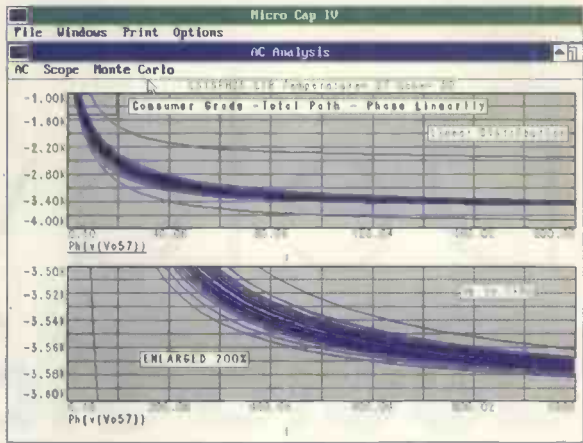
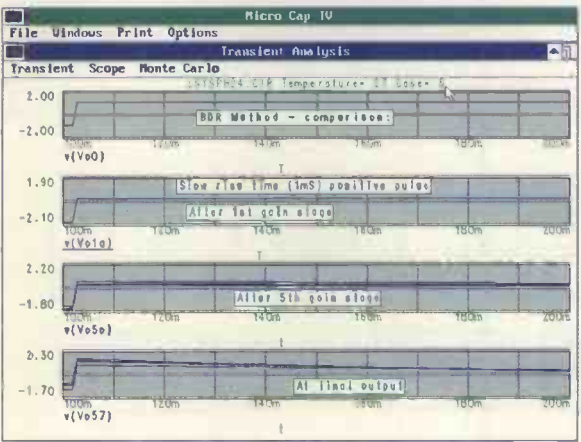


Fig. 7. Phase disaster at path output. With consumer values, the phase response of the whole path is truly non-linear, and the rate of phase shift changes at hundreds of degrees every few Hz around 40Hz. In the lower panel, the phase change rate (enlarged x30) isn't even linear by 1kHz. Note also the wild singleton – a disparate of excess phase. Y-axis is degrees.

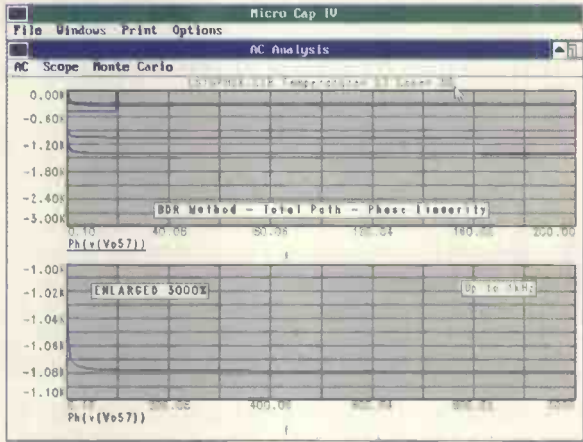


Fig. 8. Attaining global phase linearity. With bdr, the rate of change of phase is far, far less at the end of a full audio reproduction chain. In the lower panel, even x30 enlargement fails to reveal any visible curvature above 100Hz.

the music – here as much as 43ms at 40Hz – while the higher harmonics of a note at this frequency can have periods many times shorter than this.

Clearly, the music is playing out of step with itself, and any RC components that add hp filtration will compound this delay. The real test of a design is to measure delay after passing a signal through seventy (of Douglas Self's 'blameless') power amplifiers – with appropriate interstage attenuation.

Distortion suffered by wideband audio waveforms (10Hz to 20-100kHz, Fig. 3) resulting from this delay is horrific: 'smeared' is a fair description.

Phase compensation suggested by Cherry² ought to help, but will it? Compensation must be in use in not just one stage, but throughout a fair fraction of – if not all – the audio chain. Plainly this would prove unworkable as each stage's inevitable xdB of subsonic gain would accumulate, soon eating up headroom. Also, any compensatory equalisation circuit would require further critically-toleranced RC parts, and its own phase relations and tolerance deviations would destroy Cherry's compensation's benefits.

The problems of the consumer approach are self-inflicted. To demonstrate what would happen if the bdr (see panel, BDR vs Cherry and Self) approach were used throughout the audio path, the capacitor values can simply be increased by x167.

Effect on group delay is to make it 100 times smaller, Fig. 4 and contribution of the solo gain stage also ranges higher.

So what would be the fate of a simple positive pulse as it passes through the chain, Fig. 5? After the 57th high-pass function, the edge reduces to something like a damped oscillation. But using the bdr method, Fig. 6, although the final output may be a little tilted, at least it's recognisable and quite faithful.

Similarly, phase linearity for the consumer path is a disaster at all frequencies below 1kHz, Fig. 7, with the rate of change of phase per hertz accelerating. This can be compared with the bdr method, Fig. 8, which demonstrates an almost text book model of phase linearity. No significant curvature is visible above 100Hz.

Ironically, without the expense of hundreds of volts of If headroom extension, Cherry's phase compensation scheme

can in practice only be used once or twice. It is only in this almost phase-linear environment that it would have significant objective effect. Yet, in ordinary signal chains the effect would readily be heard as an improvement. But the same phase correction of just one stage in 60+ would be nearly invisible in any objective measurement of the whole chain due to phase jitter.

References

1. D Self, "Unacceptable Terms", *Letters, EW + WW*, Feb 1995.
2. E Cherry, "Ironing out distortion", *EW + WW*, Jan '95.
3. B Duncan, "Spirit of Bass", *EW + WW*, Feb '94.
4. D Self, "High speed audio power", *EW + WW*, Sept '94.
5. D Jensen, "High Frequency phase response specifications – useful or misleading?", 81st AES convention, Nov '86, reprinted with corrections by Jensen transformers, 1988.

Ben vs Self and Cherry: simulated contest

Ben Duncan wonders if he's the only designer left who really cares about the effects of phase and group delay on bass response.

Simulation of the Ben Duncan Research (bdr) simple and low-compromise approach to low frequency reproduction accuracy³ can quickly provide a straightforward picture of phase and group delay, audio aspects of which are evidently still only foggily understood by some. Simulation also allows the design to be compared with those of Douglas Self⁴ and Edward Cherry².

First step is to enter the three circuits into *MicroCap IV* to compare different approaches to low frequency reproduction (Fig. 1). In the bdr approach, topology is minimal and f_{3L} (alias $\omega_{low}/2\pi$) is made extremely low, typically <0.1Hz.

The "consumer grade" version of the same topology, has lean *hp* capacitors to save pennies (eg Self⁴, though to be fair, far worse examples are extant) and f_{3L} is typically 3-10Hz. In this and the bdr circuit, the main resistive arm values have been scaled to be identical to those specified by Cherry so like is being compared with like.

In practice, I would use a 1000 μ F – not 3300 μ F – lower arm capacitor, and scale the associated *R* values by a factor of three. In Cherry's circuit, extra parts have been introduced, apparently to compensate for having used too lean a principal elcap value in the first place. One practical problem

with Cherry's method is that an exact ratio of three between electrolytics requires some messy paralleling when only E3 series values (10, 22, 47, 100 μ F etc) are available, as is often the case.

Plotting If frequency response and phase using conventional log frequency scale (Fig. 11, upper panel) for the three circuits does not give meaningfully view of phase behaviour for reproduction errors. In *MicroCap*, while simultaneously plotting by frequency, the scale for the phase data can be set to linear with 0Hz ('dc') as the origin, Fig. 11. This will remove the delay⁵ independent of frequency,

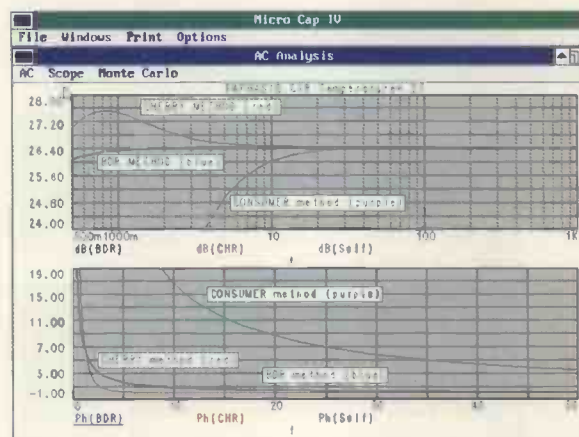


Fig. 11. Frequency responses (upper panel) of the three contrasted circuits all provide negligible roll-off in the audio band >20Hz, but with true, frequency-dependent phase shift visible for a change (lower panel), the consumer/Self circuitry commits phase crime well within the ear's most sensitive domain.

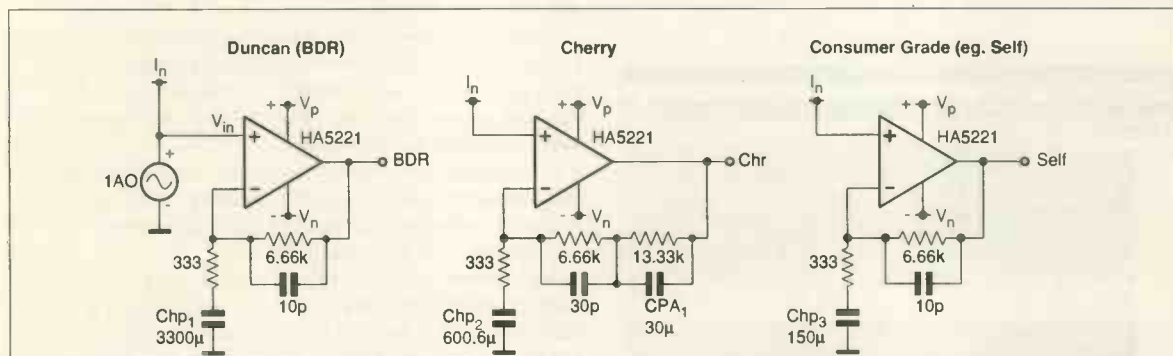


Fig. 1. Three bass response approaches compared. Centre is Prof Cherry's "phase compensation" scheme. Note ac test source (left) drives all three. Measurements are referred to node labels; nodal numbering in *MicroCap* is automatic and transparent. Left and right circuits vary only in their elcap size. The Harris HA5221 IC model parameters are Level 1 for speed, and have been over tweaked but these factors have no appreciable effect on simulation accuracy or validity in our strictly If arena.

Fig. III. MicroCap's ac analysis prolog screen. Note the frequency range origin is set at 1mHz, not quite dc but near enough, to speed up plotting. Also, the the decibel and phase plots are set logarithmically and linearly, respectively. Y-axis is milliseconds of delay.

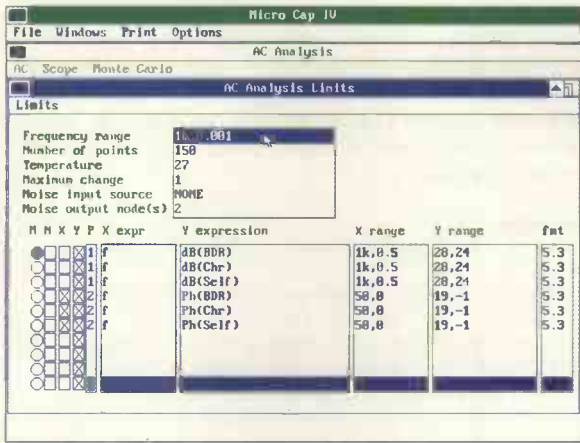


Fig. IV. Square wave responses compared. Upper panel shows all three. Lower panel magnifies the positive pedestal and abstracts it in time too, to clarify the differences between the Cherry (convex) and bdr (near-linear) methods. Y-axis is volts.

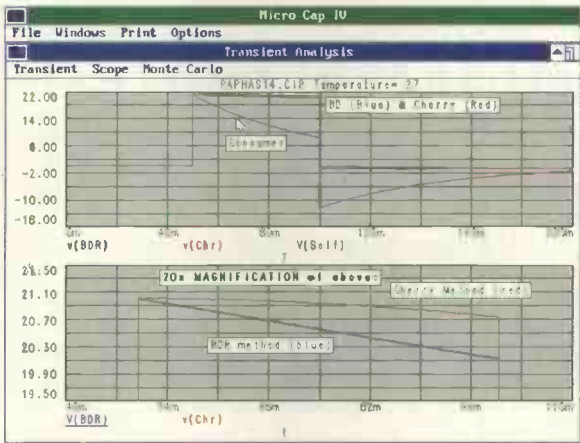


Fig. V. Mass frequency responses. Upper graph covers half the amplitude of the lower. The Monte Carlo linear run shows what could occur in a real population. Y-axis is decibels.

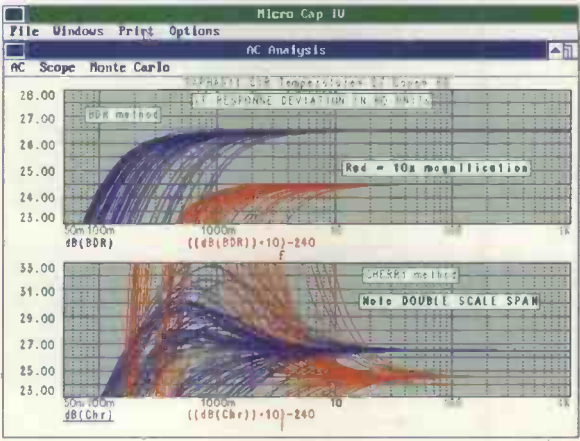


Fig. VI. Cherry's phase disaster: A Monte Carlo run showing true phase response after Jensen, in a production population. Note linear frequency scale. The vertical step just discernible in the origin of the upper plot is because frequency was set to begin at 0.1Hz rather than 0Hz. This speeds the run. Y-axis is degrees.

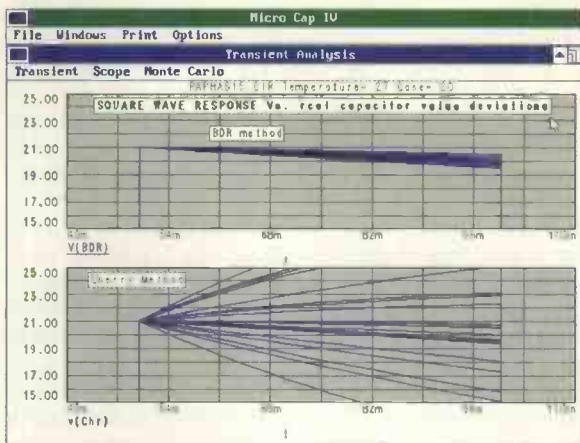
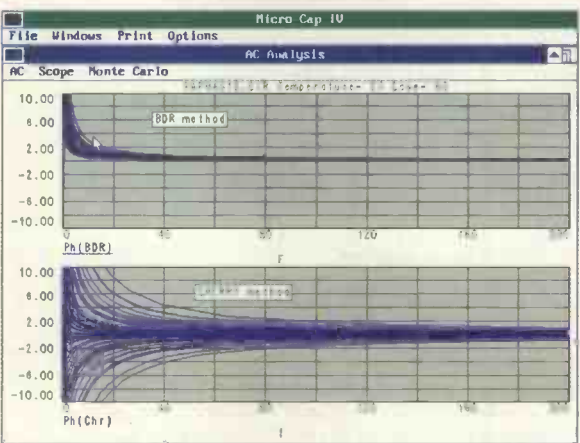


Fig. VII. Effect on the two square waves shown in the lower panel of Fig. IV when capacitor values are stepped over real world tolerances. The lower set of plots shows how – with most variations – Cherry's method fails to achieve the flat top that is its goal. The bdr method is clearly much less sensitive to part tolerance, though with more than 20 plots (a limit imposed for visual clarity) a few 'wild' plots will occur. Y-axis is volts.

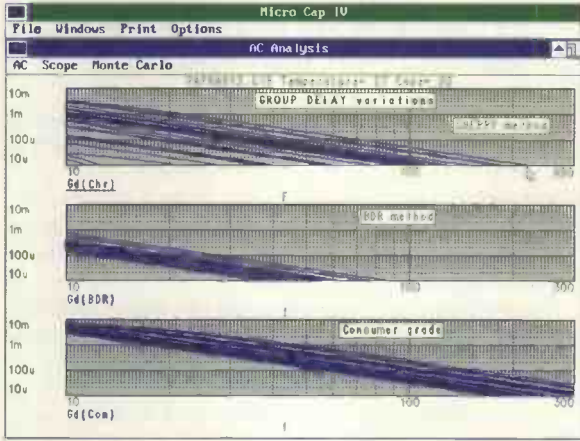


Fig. VIII. Three signal delay patterns. Group delay is plotted with the 'Gd' operator. For clarity with the three, smaller, scales and because smooth Gd plotting demands slower runs than phase or amplitude, the number of Monte Carlo runs has been reduced from 60 to 30.

revealing true phase linearity so that a straight line on this linear scale, whether sloping or level, indicates absence of waveform distortion. Anything bending is slurring the signal with respect to frequency.

Using this technique, both the Cherry and bdr methods can be seen to have (Fig. II, lower panel) audio band, to 20Hz, true phase linearity well within 1°. But the consumer approach shows almost 4.5° of tilt at 42Hz – the lowest fundamental from a bass guitar.

Cherry is certainly more linear at sub-sonic frequencies than bdr, and that would improve the accuracy of say, an earthquake or explosion (for hi-fi video entertainment). But we must ask: "Is it really worth it?"

Square-wave responses, Fig. IV, show a major tilt in the consumer approach, while a 20 times magnification is needed to see that the BDR method tilts more than Cherry's and the slope is almost linear. A sign of Cherry's phase compensation can be seen in the slightly convex curvature, whereas the consumer tilt is concave.

The lower arm dc blocking capacitor is inevitably electrolytic – Douglas Self agrees¹ – even if for sonic reasons a far smaller valued polypropylene capacitor is shunted

across. Scaling R up and C down is just not practical on grounds of noise, microphony and increased electrostatic/EMI sensitivity³.

Electrolytic tolerances may have improved greatly over the years, but they are still commonly as poor as $\pm 30\%$ and most are $\pm 20\%$ at best. Electrolytics also have the poorest temperature coefficients of any capacitor type. Typically the value will change from that at switch on by at least $+10\%$, and possibly to over 50% , after the unit's internal temperature has risen by 35°C . Equally, faradic value could drift by 25% with time.

Taking the midpoints of these, we have $25\% + 30\% + 25\%$. So in real use the two elcap values on which Cherry's scheme depends may realistically and independently vary by $\pm 80\%$ (ie from $\times 0.2$ to $\times 1.8$). To reflect this, all capacitors definition statements for the simulation (Fig. 1) have been appended with $\text{LOT}=80\%$. For clarity, resistor values are assumed to be invariant.

Re-running the simulations with Monte Carlo analysis, using linear distribution, shows the effect of real world capacitive value variation.

Amplitude response variation across 60 units for bdr (Fig. V) shows no peak, nor any aberration above 0.1dB in the audio band.

But Cherry's scheme shows that the response and damping (Q) varies all over (so badly that the scale is halved to see just a bit of it) and the variation infects frequencies considerably above 20Hz .

In the worst-case true phase error at 20Hz , Fig. VI, bdr varies just 1.8° between $+0.2$ and $+2^\circ$. Yet Cherry's scheme varies over 16° from at least $+8^\circ$ to -8° . Worse, the phase error varies by more than $\pm 0.75^\circ$ at 200Hz , a far more critical and phase-sensitive midrange frequency.

Looking again at the square wave response, even with only 20 Monte Carlo runs, Fig. VII, bdr shows only mild changes while Cherry already varies wildly. In fact Cherry's response – completely different from the slight tilt intended – makes it most dubious where anything but individually-selected oven-mounted electrolytics, measured and calibrated monthly, are available.

Finally, we should consider group delay. Plotted against logarithmic frequency, this displays frequency-dependent signal delay directly.

At first sight, delay varies almost linearly with frequency using all three schemes, Fig. VIII. However, both Cherry and the consumer method exhibit plots that are non-monotonic: try a ruler against them.

What matters most though, is the excess absolute delay. The consumer scheme is worst, with the largest delay (in only 30 random production units remember) being nearly $400\mu\text{s}$. With Cherry, the worst delay at 80Hz is below a quarter of this, $70\mu\text{s}$. Again, bdr is best, with barely $10\mu\text{s}$. For an 80Hz partial to be lagging 70 or $300\mu\text{s}$ behind the mid-range may not sound much, and even those with critical ears will not easily hear this difference. But, clearly, few audio designers have ever thought through the entire-path ramifications. ■

LOW COST DEVELOPMENT SYSTEM

ECAL comprises a versatile relocatable assembler with integral editor which runs about ten times faster than typical assemblers. Support includes 4, 8, 16 & 32 bit processor families including 75X, 6502, 6809, 68HC05/11, 8031/51, H8-300, 78K, PICs, ST6 & Z80/180, 68000, 80C196, H8-500 & Z280.

ECAL is either available for a single processor family or all families.

Single processor version £295
Multiprocessor version.... £395

**Overseas
distributors
required**

OEMA Ltd.,

**7 & 7A Brook Lane,
Warsash,
Southampton SO31 9FH
Tel: 01489 571300
Fax: 01489 885853**

The PC based ECAL hardware emulator is fully integrated with the assembler. Connection is made to the target through the eprom socket so a **single** pod can support **all** processors. Facilities include windows for the inspection or change of registers or memory. You can even watch your program executing at source level!


Download time is about two seconds!

Pods can be daisy-chained for 16/32 bit systems.

Applications include software development, hardware debug, test and, finally, teaching about micro-controllers in education.

ECAL emulator £475

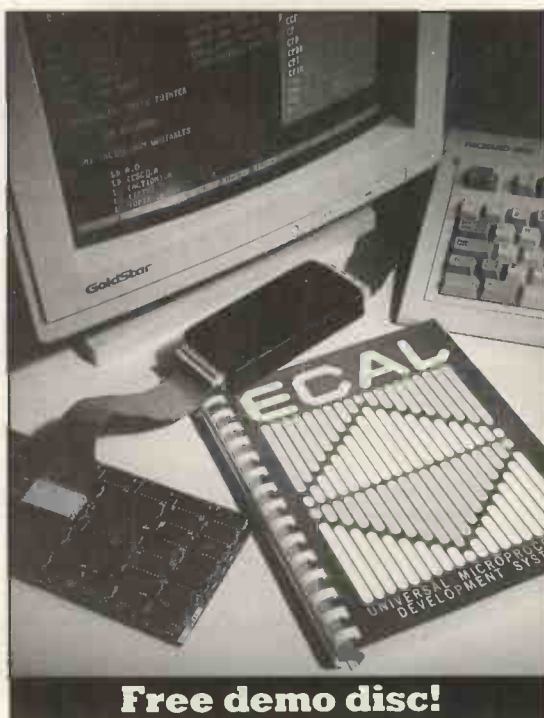Quantity discounts of up to 50% make ECAL software ideal for education.



Free demo disc!

CIRCLE NO. 123 ON REPLY CARD

C Migrating to

Object-oriented design has been heralded as offering radical benefits in the software development cycle. However, without adequate appreciation and management of the process, the gains expected may materialise, as Gerard Maloney explains.

In theory if not in practice, software development has traditionally been based on 'structured' design methods, which emphasise the procedures by which a solution is achieved. But the ever increasing size and complexity of software systems, not to mention the demands in areas such as graphical interfaces, cad/cam, artificial intelligence and distributed systems, has increasingly highlighted the inadequacies of this approach. As a result, alternative design methods are coming increasingly to the fore.

Of these alternative methods the 'object oriented' approach is the one currently gaining ground across a wide diversity of applications. Here, we will outline the underlying philosophy of object-oriented programming, looking in particular at what has become the dominant programming language for implementing such designs – C++.

Programming with objects in mind

Object oriented design has as its basis a key shift in emphasis away from concentrating on how a task is achieved to identifying the key abstractions within an application. It also takes into account how these abstractions interact with one another.

From this basis it is hoped to model a more effective and intuitive solution to the task at hand. Coupled with this shift in emphasis is a movement away from the 'top-down' approach to the development cycle, to an approach whereby the development cycle is seen as an iterative process. Each phase in the cycle is reviewed, as the design evolves to fulfil its final requirement.

Figures 1 & 2 outline the change in emphasis. For a great number of engineers Fig. 2 only sets out precisely how they currently approach their development work. Within an organisation however, the change from a structured to an object oriented approach requires a review of the overall management

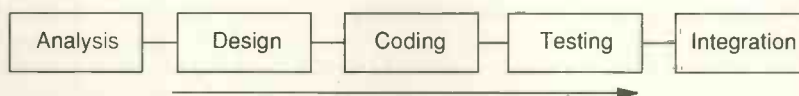


Fig. 1. In the traditional structured design cycle, progress is linear.

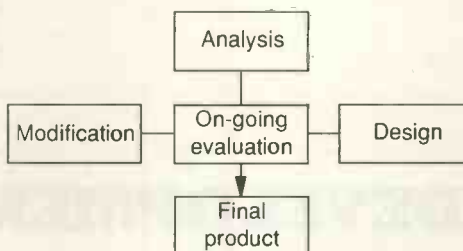


Fig. 2. Object oriented design cycle involves an iterative approach throughout the design cycle.

of technical projects in order to implement the changeover effectively.

The use of object-oriented design has gathered apace over the past ten years, to the point where it now looks set to become the dominant design methodology within the software industry. This has no doubt been aided immeasurably by the emergence of C++ as a commercially available and mature language. Although not the 'purest' of object oriented languages, C++ has evolved to directly support the paradigm, while maintaining its roots in C.

Of itself, object oriented design is not a panacea for bad design. Likewise its adoption will not be effective unless project team structures and management practices change to

enable its correct implementation.

The language requires a more fluid and evolutionary approach to design, and the extent to which its introduction benefits companies is largely dependent upon the recognition of this fact. Used correctly, object oriented techniques implemented in an appropriate language, will result in designs that map directly onto the applications domain, enabling increased software re-use, ease of maintenance and an evolutionary approach to future development.

Object oriented design – key concepts

To be effective any design methodology requires tools that support it directly. In this case these are the 'object oriented programming languages', a wide range of which are available. However, in order to be able to model and organise abstractions effectively, which concepts and mechanisms ought these languages support?

In his book 'Object Oriented Design with Applications', Grady Booch outlines the concepts which are fundamental to what he terms 'the object model'. These are direct support for abstraction, encapsulation, hierarchy and modularity. To these ought to be added support for parameterised types, which have the potential of adding significantly to software

Applications Domain:

Waveforms:
Sine, Square, Triangle, Ramp

Processes:
Acquisition, Filtering, Output

Software Implementation:

A range of waveform types.

Arrays, filter types, output drivers.

Fig. 3. Mapping abstractions. Object-oriented design allows 'types' to be created. These map directly into the application's domain.

re-use. Secondary properties which he outlines as desirable are strong 'typing', and support for concurrency and object persistence. A brief outline of each of these concepts is given below.

(i) **Abstraction:** in order to support abstraction a language must allow for the creation of user defined types which map directly onto concepts within the application domain. In a signal-processing application you might need to create waveform and filter types; in a graphics library, matrix and transformation types. Figure 3 illustrates the concept.

(ii) **Encapsulation:** any abstraction can be said to have two major attributes: its structure and its behaviour. Within software this translates to a representation and an associated set of functions (procedures/methods). Generally, the functionality is of interest; the representation/implementation should not be accessible except through a strictly defined set of functions implementing the interface to the user.

In effect the representation should be 'encapsulated'. Figure 4 illustrates how encapsulation might be achieved for a type representing a sinewave.

(iii) **Hierarchy:** within object oriented software, creating hierarchies of user types is of prime importance. The base of the hierarchy provides generalisation with further specialisation provided by the lower layers. Support for hierarchical types allows for designs that are highly intuitive and efficient, and provides a basis for further evolution. Figure 5 is an example of a partial hierarchy for geometric transformations.

(iv) **Modularity:** any complex system needs to be modular. Within object-oriented systems, modularity exists to keep related abstractions together.

Modularity exists at a number of levels; libraries provide re-usable collections of domain specific abstractions, source files provide modularity at the application level while encapsulation provides modularity at the abstraction level.

(v) **Parameterised types:** often, structures and functions are required that can be used across a range of types. As an example, consider matrices. The structure of a matrix and its operations have a generality across a range of algebraic structures. The ability to capture this type of generality is a powerful aid to extended re-use.

(vi) **Typing:** static type checking can ensure errors are caught at compile time, and it can introduce a strong discipline into programming. Not all object oriented languages support static typing, but in most instances the benefits far outweigh the perceived loss in flexibility.

(vii) **Concurrency and persistence:** support for concurrent processes is not inherent with-

in object oriented languages. However a process itself can be viewed as an abstraction and therefore concurrency can be implemented. Likewise the need for objects which exist over extensive periods of time – as in database and distributed systems – can easily be supported at the abstraction level.

Having outlined these concepts I will now look specifically at language support for these within C++.

Objects and C++

C++ was developed as a general purpose programming language which would directly support object-oriented programming in an efficient and straightforward manner. By guaranteeing that C++ would maintain C's inherent low-level strength and by maintaining a high level of compatibility with C, C++ has been in a unique position as developers looked to adopt object oriented methods.

In his work 'The Design and Evolution of C++', Bjarne Stroustrup says that in his view, C had successfully addressed the 'computational' aspects of a language. In developing C++, one criteria was to maintain this, while dealing effectively with the 'organisational' aspects.

A further criteria was to remove the necessity for the unsafe practices used widely in C, such as casts and the proliferation of pre-processor directives and global data.

Object oriented development support Within C++, there are various structures, included to aid object-oriented development.

(i) **Classes:** Within C++, a 'class' is the fundamental mechanism by which user defined types are implemented and they receive almost identical support within the language as the built in types such as 'int', 'char' etc.

Classes not only represent the abstractions within the application, but within the class 'encapsulation' is enforced. A class defines a scope, and is the fundamental organisational component in C++. Below is a simple sinewave class showing the separation of the representation from the interface to it.

```
class sinewave{
    //the representation
    float frequency;
    float amplitude;
public:
    //the interface to the representation.
    sinewave(float x, float y){frequency=x;amplitude=y;}
    ~sinewave();
    //other appropriate functionality.
};
```

C++ allows for different levels of access to be defined and very efficient and intuitive interfaces can be built, given features which allow for in-line code and the defining of operators on a class specific basis.

A user of a sinewave class requires only the interface to use the class, and application specific class libraries are the toolsets to be used by application developers.

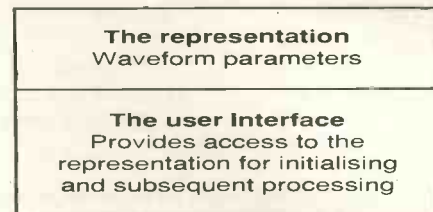


Fig. 4. Example of encapsulation. The representation and the interface parallel two major attributes of an abstraction – its structure and its behaviour.

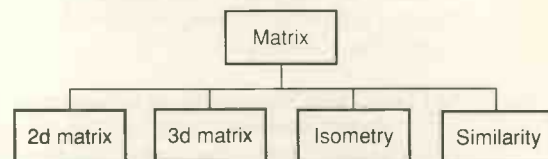


Fig. 5. A matrix hierarchy supporting geometric transformations. The root matrix provides generic behaviour while the derived classes provide for specific functionality.

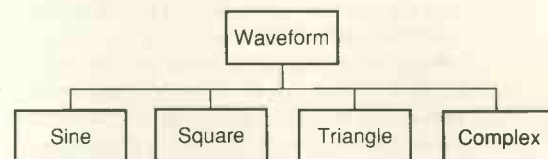


Fig. 6. Example of simple hierarchy structure for waveform generation.

(ii) **Derived classes:** Given an application, generally hierarchies of related types exist. Below is a hierarchy of waveform types, with the 'base' of the hierarchy being the 'waveform' class and the 'derived' classes being 'sine', 'square' etc, Fig. 6.

Hierarchies allow related types to share common functionality and to be viewed in many instances as objects of their common base class. Below the sinewave class has been derived from a waveform class allowing a large measure of its functionality to be expressed in terms of its base class.

```
class sinewave : public waveform{
    //representation in base class.
    //common to all wavetypes.
public:
    sinewave(float x, float y):waveform(x,y,){
        //only need sinewave specific functions.
        //otherwise view as a generic waveform.
    };
```

Whatever their type, waveforms share a great deal in common and are thus able to use a great deal of generic code. With an appropriate class library, C++ enables the following to be written:

```
complexwave1=sine1+square3+ramp5+sine7;
complexwave2=(mybandpass)(complexwave1);
```

Not only is this semantically clear but it is as

Requirements:	Solution:
general lists of	
employees	a list type that can
accounts	hold any type for which
waveforms in	a list makes sense
a complex wave	

Fig. 7. Parameterised types allow for the creation of generic classes and functions.

efficient if not more so than code written in C.

Hierarchies, therefore have a crucial role to play in organisational terms and introduce a high degree of code re-use.

(iii) **Templates:** Whereas hierarchy supports re-use through derivation, templates support re-use through parameterised types. Thus you define a class or function to provide services across a range of types which may not necessarily be related to one another. **Figure 7** illustrates the general requirement and solution.

Initially, they arose from the requirement to provide a library of container classes which is a fundamental requirement within most development environments. Assume we need lists; but lists of what exactly? How is it possible to provide for the lists that may be needed in the future? Templates fulfil this requirement, below we look at the outline of a matrix template:

```
template <class T> class matrix{
    int col;
    int row;
public:
    matrix(int x,int y){col=x;row=y;}
    ~matrix();
    //other matrix stuff
};
```

A developer can now declare matrices of any type;

```
matrix <int> intmatrix(2,2);
matrix <complex> complexmatrice(5,3);
```

and given that those types are available matrix algebra can be applied to them. Likewise at a future date matrix algebra could be applied to as yet unspecified types.

Used together with derivation the potential for re-use and the impact on program organisation are enormous. Taking as a case in point, in our matrix example we can derive from matrix and apply templates to a specific type of matrix. I may perhaps wish to optimise for geometric transformations which are derived from a matrix and are able to take a variety of types as their parameters.

Together, classes, the related subjects of hierarchies, and templates, form the basis of support for object oriented techniques within C++. Also incorporated within the class concept are features to encourage semantically meaningful syntax, the efficient creation and deletion of objects and the minimisation of global data and pre-processor directives. In addition, there is the introduction of static typing, which is equally applicable to stand-alone functions. Static typing enforces compile-time

checking of arguments, and can go a long way to eliminating run-time errors. It is to be recommended in almost all cases.

Finally, modularity is supported in C++ by the use of libraries and separate source and header files. Organisation is in terms of abstractions, related abstractions reside in the same files and are interfaced through their header files, **Fig. 8**.

Application specific libraries can then be generated from these files and made available for general use. With a good library of classes that map well onto the application's domain it should not generally be necessary to access the source code in order to use or add further speciality.

In summary

Without a doubt C++ is rapidly becoming the language of choice in many areas, and given its excellent support for object oriented programming coupled with its association with C it looks set to be a major development language in all spheres.

What is often overlooked, however, is that C++ also addresses those areas in which C is deficient. Features such as static typing, class specific dynamic memory allocation, static class members, exception handling are radical improvements when viewed from a software engineering perspective.

C++ also supports mixed-language development with a simple linkage model, allowing previous software investment to be fully used. Given these advantages there is a strong case both commercially and technically for companies to considering C++ seriously as the basis for their future software development.

However, while the benefits to be gained by adopting an object oriented approach to development – whether C++ based or otherwise – can be enormous; unfortunately without an adequate understanding of the issues involved, these benefits may not be achieved.

With no informed strategy for the adoption of C++, the net result within organisations will be disenchantment amongst development staff, and a discrediting of the whole process. Such a strategy should deal directly with the change in emphasis that the philosophy requires. It should set out a program in which object oriented design methods and programming are introduced over a period of time at both a project and individual level. Given such a strategy the resultant impact on design and implementation are indeed significant. ■

Fig. 8. Organisation using header files.

```
//App.cpp
#include "waveform.h"
//two header files for accessing
    waveform and processing stuff
#include "process.h"
//the application accesses required
    functions via header files
sine sine1(1000,1.125);
```

Further reading

Grady Booch, 'Object Oriented Design with Applications', Benjamin Cummings.
Bjarne Stroustrup, 'The Design and Evolution of C++', Addison Wesley.
The C++ Programming Language, Addison Wesley.

SAVE £15

**For this month
only, save
£15.00 when
ordering the
Interfacing with C
software disk.
Simply mention
'C – special offer'
when you send
your order.**

INTERFACING WITH C




HOWARD HUTCHINGS

If you have followed our series on the use of the C programming language, then you will recognise its value to the practising engineer.

The book is a storehouse of information that will be of lasting value to anyone involved in the design of filters, A-to-D conversion, convolution, fourier and many other applications, with not a soldering iron in sight.

To complement the published series, Howard Hutchings has written additional chapters on D-to-A and A-to-D conversion, waveform synthesis and audio special effects, including echo and reverberation. An appendix provides a 'getting started' introduction to the running of the many programs scattered throughout the book.

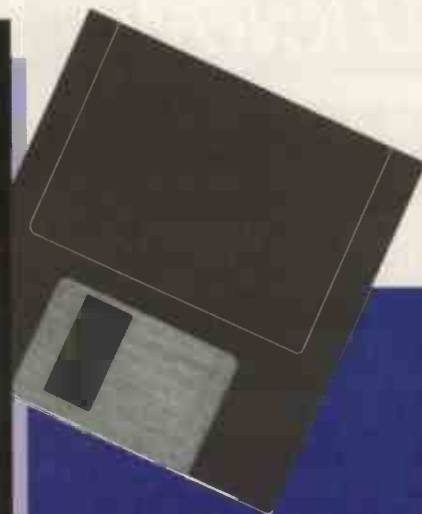This is a practical guide to real-time programming. The programs having been tested and proved. It is a distillation of the teaching of computer-assisted engineering at Humberside Polytechnic, at which Dr Hutchings is a senior lecturer.



A disk containing all the example listings used in this book is available, Please specify size required

Please supply _____ copies of

INTERFACING WITH C

Price £14.95

Please supply _____ copies of

Disk containing all the example listings £29.96

Remittance enclosed £ _____

**Interfacing with C can be obtained from
Jackie Lowe, Room L333, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS**

Cheques should be made payable to
Reed Business Publishing Group Ltd

Please debit my credit card as follows:

Access/Master Barclay/Visa Amex Diners

Credit Card No. _____

Exp date _____

NAME (Please print) _____

ADDRESS _____

POST CODE _____

DATE _____ TELE _____

SIGNATURE _____

VAT NO. _____

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

**Credit card orders
accepted by phone.
Call 0181 652 3614.**

ELECTRONICS WORLD+WIRELESS WORLD May 1995

SOFT INDEX ON DISK



A computerised index of *Electronics World+Wireless World* magazine is now available. It covers the five years 1990 to 1994 – volumes 96 to 100 – and contains over 1400 references to feature articles, circuit ideas and applications, with a synopsis for each. The software is easy to use and very quick. It runs on any IBM or compatible PC with 512K ram and a hard disk. Each disk is scanned before shipping with the current version of Dr Solomon's Anti-Virus Toolkit.

For the UK, the five year index is priced at £20. Please specify 5¹/₄ or 3¹/₂in format. This price includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders.

Photo copies from back issues of *EW+WW* are available at 50p per page plus VAT (in EC) and a flat postage charge of 50p (UK), £1 (rest of EC), and £2 (rest of world). For enquiries about photo copies send an sae to Video Interface Products.

Please allow up to 28 days for delivery. Cheques should be made payable to **Video Interface Products**, not *EW&WW* or Reed Business Publishing.

Please post your request to **Video Interface Products Ltd, 1 Vineries Close, Cheltenham GL53 0NU, UK.**

Unique *EW+WW* reader offer

30% discount on TTI's PFM1300 1.3GHz frequency meter

5Hz to 1.3GHz hand-held frequency/period meter for just £85.76, fully inclusive – almost a third lower than the normal price of £134.55.

With a resolution of 0.0001mHz, the professional PFM1300 hand-held frequency meter from Thurlby Thandar measures from 5Hz to 1.3GHz with very high sensitivity at all frequencies.

This battery-powered instrument also features a reciprocal counting technique providing superior accuracy, and a push-to-measure function with auto power down. Readings to eight digits are shown on a large eight-digit display and the meter incorporates a full range of annunciators.

Measurement – range A

Frequency range	5-25MHz
Resolution	10 ⁻⁷ Hz to 10Hz
Accuracy	±1 digit + timebase error

Measurement – range B

Frequency range	20MHz-1.3GHz
Resolution	1Hz to 1kHz
Accuracy	±1 digit + timebase error

Period

Frequency range	5-25MHz
Resolution	10 ⁻⁷ ns to 1µs
Accuracy	±1 digit + timebase error

Note: resolution depends on measurement time and input frequency.

Input A, 5Hz-25MHz

Impedance	1MΩ/25pF
Sensitivity	sine, 15mV rms, 10Hz to 20MHz

Input B, 20MHz-1.3GHz

Impedance	50Ω
Sensitivity	10mV rms, 20MHz to 700MHz, 50mV rms to 1.3GHz

Input A/B limits

Abs. maximum i/p voltage	250V dc, 250V rms
	50Hz to 400Hz i/ps A,B,
	1V rms >1MHz i/p A, 1V rms 20MHz to 1.3GHz for i/p B.

Detailed specifications available – send s.a.e. marked

Meter Details to

EW+WW, Room L330 Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.



The PFM1300 – the hand-held frequency meter with bench-top performance.

Fully-inclusive price UK £85.76 Europe £90.44 Rest of world* £97.46 Cheques payable to Reed Business Publishing Group Ltd please, and posted to address above

Name _____		Total _____
Card Holders Address _____		


Credit Card name, no _____		
Expiry date _____	Tel: _____	
Signed _____	Date _____	

*We regret that this offer is not open to readers in North America.

Rather than tie up an expensive dso looking for infrequent transients, Ken Deevy, Dan Sheehan and Mike Byrne* show how to use a low-cost, dedicated transient recorder with an ordinary analogue oscilloscope or XY plotter.

To capture fast events accurately, you need a high-speed a-to-d converter and a wide-bandwidth track/hold amplifier. For example, an eight-bit a-to-d converter having a 1 μ s conversion time can capture 1 μ s transients only when not preceded by a track/hold amplifier. With a 100kHz track/hold amplifier, the converter can recover 6 μ s-wide 5V transients.

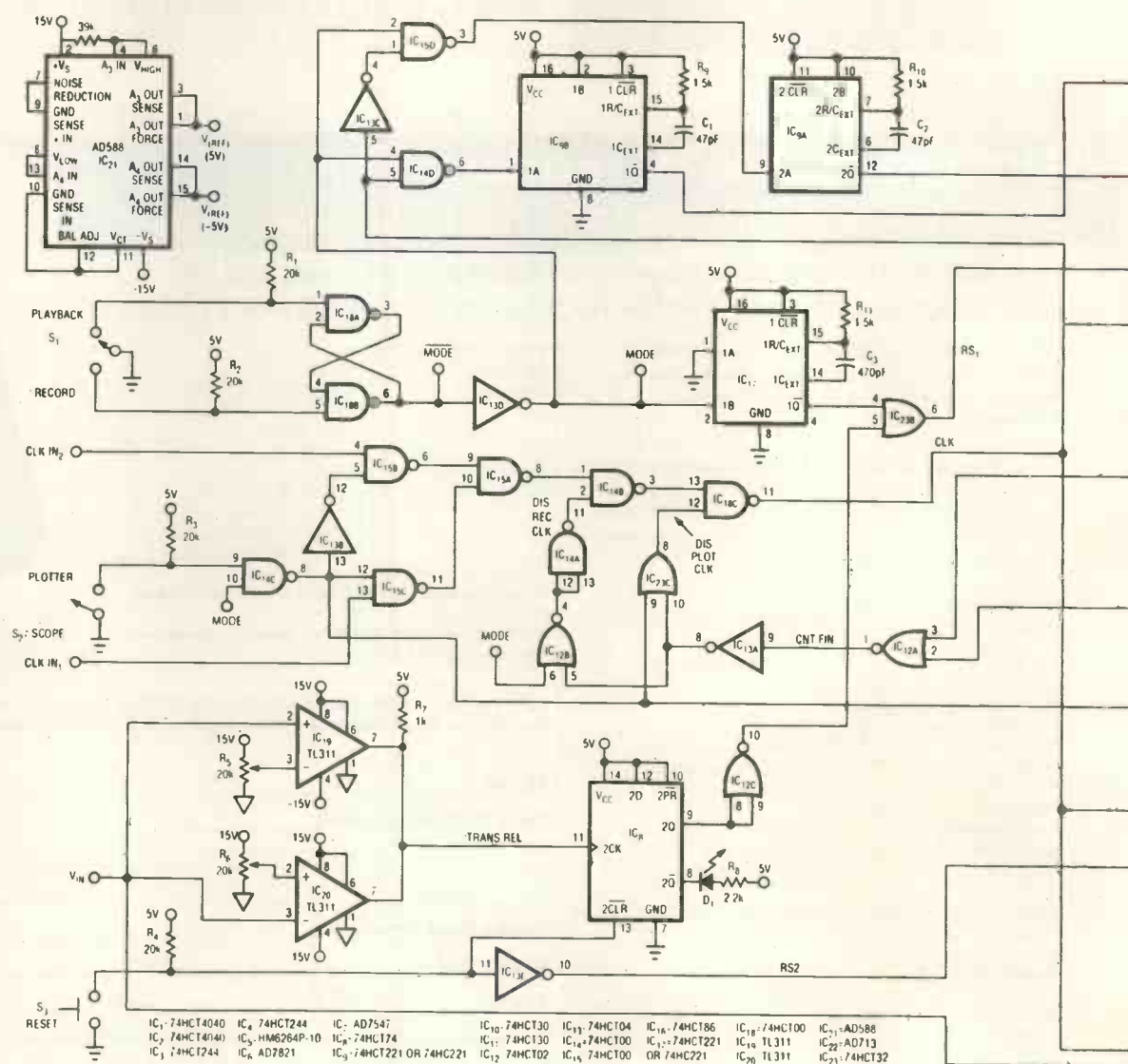Another important criterion is cost. There is little point in replacing one expensive instrument with another. Figure 1 shows that two counters, IC_1 and IC_2 , determine where the circuit stores pre-transient and transient data, also clocking out data to the oscilloscope or X-Y plotter. You can use the



*Ken Deevy, Dan Sheehan and Mike Byrne are with Analog Devices Inc. This article first appeared in *EDN*.

fast clock input, CLK IN₁, for the clock source in record mode or when displaying stored data on an oscilloscope. A slower clock input, CLK IN₂, is for use when printing data on an X-Y plotter.

Switch *S*₁ selects the two basic modes: record and playback, IC_{18a} and IC_{18b} providing debouncing. With the MODE output of IC_{13d} low, one input of both IC_{15d} and IC_{14d} is low, so the clock inputs of IC_{9a} and IC_{9b} are disabled, ensuring that the 1Q_N and 2Q_N outputs of IC_{9a} and IC_{9b} are high. Besides disabling the chip-select inputs of the d-to-a converter, CSA_N and CSB_N, the circuit disables the output enable signals of IC₃, IC₄ and IC₅, the HM6264 memory chip, ensuring that the playback portion of the transient recorder is turned off.

Input CLK IN₁ serves as the clock source for the counters via IC_{18c}, IC_{14b}, IC_{15a} and IC_{15c}. While the MODE signal is low, CLK is the clock input for both counters and provides the RD_N (convert) signal for the AD7821 a-to-d converter, IC₆. At the same time, IC₆'s CS_N input is active, ensuring that the device is selected. After a reset from *S*₃ initialises the circuit, counter 2 begins counting. Monostable IC₁₇ and IC_{23b} hold the reset (CLR) input of counter 1 high from power-up, keeping it in reset until the circuit detects a transient.

Connecting pin 7 of the AD7821, labelled Mode, to ground, sets the operating sequence in which, when the CLK signal toggles its RD_N input, the a-to-d converter executes continuous conversions of the input signal, *V*_{in}. (This Mode pin is in no way connected with the mode signal in the circuit dia-

gram.) Counter 2 provides the memory addresses for the a-to-d conversion results. Data transfers from the digital outputs of IC₆ to IC₅ employ the INT_N output of IC₆ to drive the WE_N input of IC₅.

The circuit automatically loads the first conversion result after reset into location 0 of memory and the second into location 1. After transferring the result of the 4096th conversion to memory location 4095, the counter resets and stores the next conversion result in location 0. Memory always, therefore, contains the most recent 4096 samples of the input waveform.

Fast transients

Input signal *V*_{in} goes directly to two TL311 comparators and the analogue input of the a-to-d converter. Comparator IC₁₉ detects positive transients and IC₂₀ negative ones, threshold levels being adjusted by *R*₅ and *R*₆. Wiring the outputs of the comparators together ensures that they produce a rising edge to the clock input of IC₈ when either a negative or a positive transient occurs.

Once the circuit detects a rising edge at pin 11 of IC₈, it illuminates a led, *D*₁. At the same time, it releases counter 1 from its reset condition by taking RS₁ low and both counters clock as a-to-d conversions continue, counter 2 counting up from the value it held before the transient was detected. Memory locations determined by the output of counter 2 store the transient data while overwriting the oldest 2048 samples of pre-transient data already stored in memory.

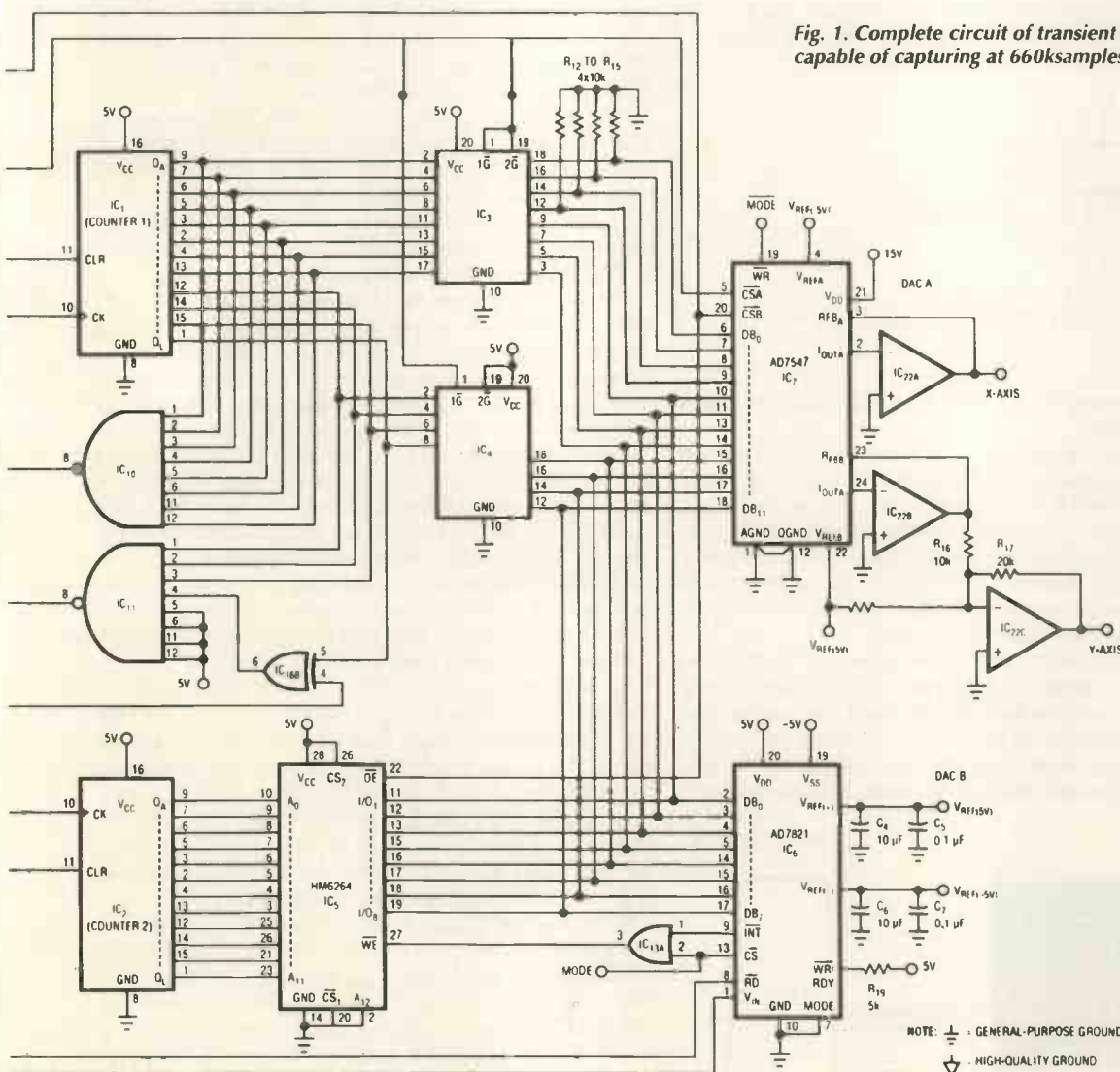


Fig. 1. Complete circuit of transient recorder capable of capturing at 660ksamples/s.

Transient recording


A transient recorder or burst-mode event sampler consists of a high-speed a-to-d converter, a wide-band track/hold amplifier, and an antialiasing filter. The a-to-d converter needs a sampling rate of at least twice the bandwidth to satisfy the Nyquist criterion, although at this rate the filter needs an infinite roll-off rate to avoid aliasing effects. With three times oversampling, the roll-off requirement drops to 50dB/octave in an eight-bit system and oversampling at a ratio of 10:1 requires a filter roll-off of only about 16dB/octave.

High-speed, sampling a-to-d converter chips often include track/hold amplifiers on the same chip; the AD7821 is an example of this trend, combining a 100kHz track/hold amplifier with a 1Msamples/s, eight-bit a-to-d converter. Because the a-to-d conversion rate is ten times the input bandwidth, there is no need for a complex antialiasing filter; indeed, if the input signal exhibits only a low-power spectral content at and above 500kHz, no filter is needed at all.

The AD7821 uses a half-flash conversion technique to perform an eight-bit conversion in 660ns which, with the requirement of a 350ns signal-acquisition period between conversions, results in a maximum acquisition rate of 1Msamples/s. It accepts either single or dual supplies for unipolar or bipolar inputs.

Figure A1 is a block diagram of a transient recorder, showing the minimum hardware needed to build a high-speed transient recorder with playback. For simplicity, the design uses a clock with an even mark/space ratio, which limits the acquisition rate to 660ksamples/s rather than the a-to-d converter's 1Msamples/s maximum rate, the oversampling ratio now being 6.6:1. A memory chip stores the digitised data for later playback on an X-Y plotter or oscilloscope, via a dual, 12-bit d-to-a converter and a quad op-amp. Half the samples are pre-transient information and the other half transient data.

Fig. A1. Block diagram of the transient recorder – mainly digital, but with data converters at each end.

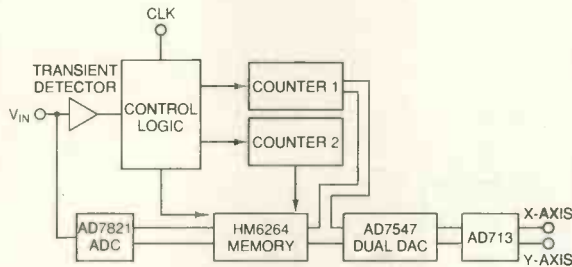


Counter 1 counts off the 2048 clock states that correspond with the samples.

Because the output of IC_{16b} is always high in the record mode, when counter 1 reaches 2047, all inputs to IC_{10} and IC_{11} are high and the outputs of both ics go low. As a result, the output of IC_{12a} goes high, causing the output of IC_{14a} to go low via IC_{13a} and IC_{12b} , this DIS REC CLK signal gating off CLK IN₁ from the rest of the circuit in IC_{14b} . The output of IC_{18c} ensures that the CLK signal is held low, stopping both counters and the a-to-d converter.

At the end of the transient-record cycle, the memory will contain 4096 samples of the input waveform. Half of these samples are transient data, the other half representing pre-transient information. Whatever value is in counter 2 will be the last memory location for the transient data and the next memory location will hold the first of the 2048 words of pre-

Fig. 2. Recorder presents results on either an analogue oscilloscope (a) or on a plotter, as at (b). Pre-transient information occupies the first half of the trace, the second half being the data after the trigger.

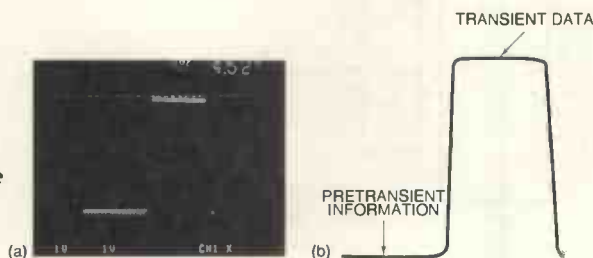

transient data; when playback mode starts, the first output from the counter will correspond to the memory location of the first pre-transient sample. To alter the ratio of transient to pre-transient samples, simply alter the connections from counter 1 to IC_{10} and IC_{11} .

To convert the input waveform to stored data accurately, you must pay close attention to the circuit. Use a precision reference, IC_{21} , to generate 5V and -5V references for the V_{ref+} and V_{ref-} inputs of the a-to-d converter. Make sure that these reference voltages are properly decoupled, along with the V_{DD} and V_{SS} lines of the a-to-d converter. Connect the GND pin of IC_6 to the star ground of the system, ie the point in the circuit at which you connect the analogue and digital grounds. Make sure that the conductor between the a-to-d converter and the star ground is as wide as circuit board layout constraints allow. Further, ensure that the WR/RDY line is pulled high via R_{19} to avoid noise pickup on this pin.

Playing back captured signals

Information is retained as long the power remains on or until you depress the reset button. Select play-back mode with S_1 . This takes the MODE\ signal low, activates the WR\ input to IC_7 , and deselects IC_6 by taking its CS\ high. Display the transient on either an analogue oscilloscope or an X-Y plotter, depending on the position of S_2 . Make sure to select the oscilloscope or the plotter before starting playback.

For the oscilloscope display, the clock source for the circuit is the same as in the record mode. If you use a plotter for playback, the clock frequency is much lower and is applied via the CLK IN₂ input. CLK, from either CLK IN₁ or CLK IN₂, passes through gates IC_{15d} and IC_{14d} because the MODE signal is high. IC_{9a} and IC_{9b} generate the CSA\ and CSB\ pulses for IC_7 from this CLK signal.

Monostable IC_{9a} drives the CSA\ input of IC_7 as well as providing the enable signals for IC_3 and IC_4 . In playback mode, counter 1 resets and starts counting from 0 to 4095, its output being the digital input code to DAC A of IC_7 , which drives the X axis of either the oscilloscope or the plotter. d-to-a converter A produces a unipolar output range from 0 to 5 V, with a resolution of 4096 steps.

Output of IC_{9b} drives the CSB\ input of IC_7 and also sets the logic level on the output-enable line of IC_5 , OE, to latch the data from memory into DAC B, which drives the Y axis of the oscilloscope or plotter. Use of dual supplies allows DAC B to be set for a bipolar output range to reconstruct both positive and negative transients.

Counter 2 starts its count from the point at which it stopped at the end of the record mode; the first memory output word to IC_7 is the oldest sample in memory. Scanning then proceeds through the 2048 samples of pre-transient information and the 2048 samples of transient information. Output of each sample from memory to the Y axis, via DAC B, corresponds to the output of a count value from counter 1 to the X axis via DAC A. In this way, the circuit reconstructs the pre-transient and transient waveforms.

For oscilloscope display of waveforms, place S_2 in the 'oscilloscope' position. Doing so locks out CLK IN₂ from the rest of the circuit but allows CLK IN₁ to operate as clock signal for the circuit. Unlike the operation of plotter display, where counter 1 runs through once and then stops, CLK runs continuously. CNT FIN does go high when counter 1 reaches a count of 4095 but, because the output of IC_{14c} is high, the DIS PLOT CLK signal does not go low. Figure 2(a) shows a typical oscilloscope waveform display.

Switching S_2 to 'plotter' locks out the CLK IN₁ input from the rest of the circuit and permits CLK IN₂ to generate the clock signal for the circuit. IC_{16b} , IC_{10} , IC_{11} and IC_{12a} generate a high CNT FIN signal function, as in record mode, but this time IC_{10} and IC_{11} go low when counter 1 reaches a count of 4095. IC_{13a} goes low and, because the output of

IC_{14c} is already low, the DIS PLOT CLK signal goes low, turning off CLK IN₂ at IC_{18c} and holding the CLK signal high. Figure 2(b) shows a captured transient displayed using a plotter as the display method.

Record-mode timing and clock waveforms

Figure 3 shows the logic relationships for the record mode, when MODE (not shown) is low and the DIS REC CLK signal is high. Signal RS₂ goes high when the recorder receives a reset command via S₃, resetting counter 2. The next falling edge of the CLK signal clocks out an address for IC_5 from counter 2 and initiates a conversion. Within 700ns, the INT_N signal of IC_6 goes low, activating the WE_N input of IC_5 . The rising edge of CLK resets the INT_N line 50ns later.

When the circuit detects a transient, TRANS REC goes high, causing the RS₁ line to go low and releasing counter 1 from its reset state, the next falling edge of CLK clocking out the contents of counter 1. When the output from counter 1 reaches 2047, CNT FIN goes high and causes the DIS REC CLK signal to go low, shutting off the CLK signal.

Since, in record mode, the a-to-d converter needs a CLK-low time of 750ns to convert and latch the data into IC_5 , the 50:50 mark/space ratio of the clock signal limits clock frequency to 660kHz. However, the CLK-high time can be as short as 350ns, the time required between conversions by the AD7821. Therefore, if the input to CLK IN₁ has a low time of 750ns and a high time of 350ns, the circuit can make one conversion every 1100ns – equivalent to approximately 900ksamples/s.

Record-mode timings

Figure 4 shows waveform timing during playback to an oscilloscope. MODE, the WE_N input of IC_5 , and the DIS REC CLK signal are high and, with S₁ in the playback mode, RS₁ goes high, resetting counter 1. CLK generates a CSA_N signal for IC_7 on its rising edge and a CSB_N signal on its falling edge. Data from counter 1 is clocked out on the falling edge of the CLK signal and the rising edge of CSA_N updates the X axis; the falling edge of OE_N outputs stored data from memory and the rising edge of CSB_N updates the Y axis. CLK runs continuously when the circuit is in oscilloscope play-back mode.

Figure 4(b) shows circuit operation for play-back on a plotter. Once again, MODE, the WE_N input of IC_5 , and the DIS REC CLK signals are high. The circuit generates CSA_N and CSB_N to update the X and Y axes. Compared with oscilloscope play-back, the difference in the circuit's operation is that when the output count from counter 1 reaches 4095 and the CNT FIN signal goes high, the DIS PLOT CLK signal goes low, forcing the CLK signal into a high state.

Sampling in burst-mode

Burst-mode event sampling places requirements on an a-to-d converter similar to those for transient recording. In burst-mode sampling, the recorder looks at the input waveform infrequently, but when it does, it must acquire a large number of samples in a short time. With slower microprocessors or microcontrollers, timing constraints impose a much lower throughput than the a-to-d converter can deliver.

Timing limitations in a burst-mode sampler are reduced by using a direct-memory-access, dma, controller to initiate a-to-d conversions and transfer conversion data to memory, allowing the a-to-d converter to run at or near its maximum sample rate and permitting high oversampling ratios and the acquisition of short transients.

Building a burst-mode sampler is relatively easy with the popular 8052 microcontroller, shown in the circuit diagram of Fig. 5. Although the 8052 does not support hardware dma, it does support what is termed 'fake dma'. However, the response time to dma requests is much slower than is possi-

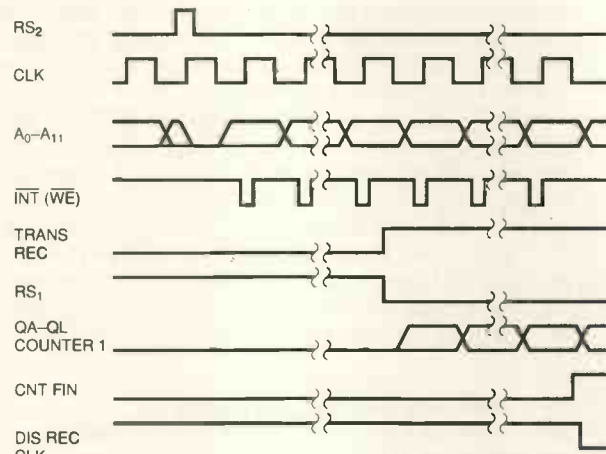


Fig. 3. Record-mode timing waveforms, the process beginning at the first falling edge after RS₂ goes high.

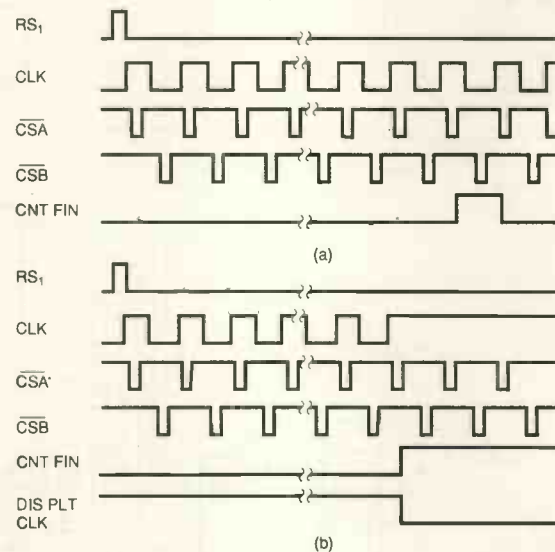


Fig. 4. Waveforms in play-back configuration, which runs once in plotter mode (b) and continuously for oscilloscope play-back (a).

ble with microcontrollers that support genuine dma.

Memory chip IC_3 , an HM6264P, stores the control program for IC_1 , of which the first part is the initialisation routine. This routine, Listing 1, sets up the sense of the DACKO line of the 8237 dma controller, IC_2 , to be active high and loads the starting data address into it for the first conversion results. Microcontroller IC_1 initialises the counting register to control the number of conversions before IC_2 returns control to IC_1 . The program must also set up IC_1 for 'fake dma'.

After running the initialisation program, IC_2 is ready to take control when requested to do so. Although IC_2 has four

Listing 1. Initialisation routine for the burst-mode sampler.

```

10  XBY(8008R) = 80H      :SETS DACK SENSE ACTIVE HIGH
20  XBY(800FH) = 0EH      :CLEARS DREQ0 MASK REGISTER
30  XBY(800BH) = 94H      :SETS MODE REGISTER
40  XBY(800CH) = 00H      :CLEARS FIRST/LAST FLIP-FLOP
                          : (ONLY NEEDED IF 8237 IS
                          : NOT RESET BETWEEN DMA REQUESTS)
50  XBY(8000H) = 00H      :LOADS LOWER BYTE OF STARTING DATA
                          : ADDRESS TO BASE AND CURRENT ADDRESS
60  XBY(8000H) = 08H      :LOADS HIGHER BYTE OF STARTING DATA
                          : ADDRESS TO BASE AND CURRENT ADDRESS
70  X8Y(8001H) = 00H      :LOADS LOWER BYTE OF COUNTING NUMBER
                          : TO COUNT REGISTER
80  XBY(8001H) = 02H      :LOADS HIGHER BYTE OF COUNTING NUMBER
                          : TO COUNT REGISTER
90  DBY(38) = DBY(38) .OR.02H
100 IE = IE.OR.81H
110 GOTO 10

```

interrupt-request lines, this circuit uses only one, DREQ0. An external command signal drives this interrupt line high, telling IC₂ to take control of the circuit and start the a-to-d converter sampling the input waveform.

When IC₂ receives the DREQ0 request, its HRQ line goes high and IC_{14c} output, which drives the INTO line of IC₁ low, which takes the INTO line of IC₁ low, its P1.6 line low and the output of IC_{14a} high, selecting inputs of IC₇, IC₈, IC₉ and IC₁₀. When the output of IC_{14a} goes high, it shuts off IC₁'s address and data lines from the rest of the circuit and deselects the output's address decoder, IC₁₃. The inverted P1.6 line also feeds the HLDA input of IC₂, acknowledging IC₂'s request for control, IC₂ then taking control of the

address and data bus and sampling of the input waveform.

To reduce pin count, IC₂ multiplexes the eight higher-order address bits on the data lines, an external device being needed to latch these address bits. Address strobe signal, ADSTB, takes AEN high to switch the OC line of IC₆ low; ADSTB drives the C input of IC₆ to latch the higher address lines to the outputs of IC₆. The inverted AEN line also drives one input of IC_{16d}, the other input of this gate being fed by the decoded output of IC₁₃, Y0. Therefore, because both IC₂ and IC₁ must be able to access IC₃, either a high on AEN or a low on the decoder output selects it.

Acknowledge line DACK0 goes high at about the same time that ADSTB latches the address and drives one input of

Fig. 5. Burst-mode sampling using an 8052 microcontroller and dma controller allows the a-to-d converter to run at its maximum sampling rate to give higher levels of oversampling.


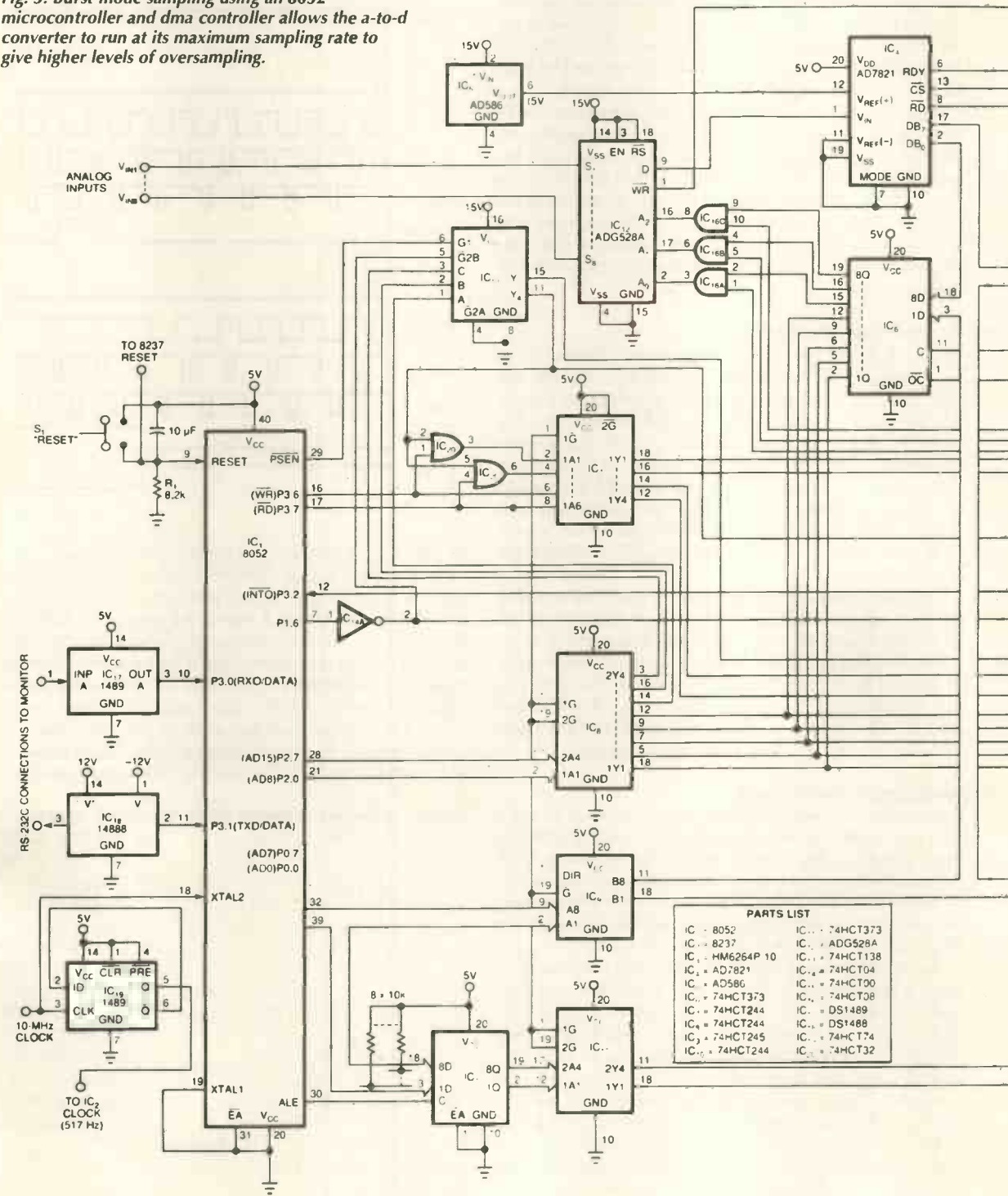


Fig. 7. Requirements of an antialiasing filter depend on the degree of oversampling. Since 10 times oversampling allows three octaves for roll-off, and since an 8-bit a-to-d converter needs 48dB of attenuation, a three-pole filter giving 18dB/octave will suffice.

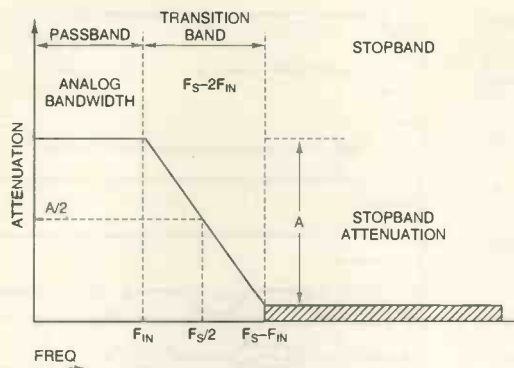

and write data to memory.

The microcontroller uses a 10MHz input-clock frequency, a 74HCT74 counter (IC_1) dividing this frequency to form the clock input to IC_2 . As the standard 8237 operates from a 3MHz maximum clock frequency, you can divide the 10MHz clock by four to give an acquisition rate of 608ksample/s. A faster version of the 8237, the 8237-5, operates from a 5MHz input clock, allowing you to divide the clock frequency by two and enabling the circuit to take 812ksample/s. If IC_1 were used on its own to control the sampling of the input waveform, the best acquisition rate would be approximately 100ksample/s.

The entire circuit operates from 15V and 5V supplies. If there is no 5V supply in your system, add a regulator to generate 5V. In addition, use a precision 5V reference (IC_5) for the a-to-d converter, allowing an input range of 0-5V. To obtain accurate conversion results, obey the usual guide lines regarding decoupling and grounding in both the circuits described.

Slow and medium speed microprocessors that support direct memory access requests can be used in this circuit to provide a much faster dma response than that of the 8052's 'fake dma'. Because microprocessors that support genuine dma will tri-state their address and data lines during a dma transfer, you can eliminate the tri-state driver chips.

Oversampling and antialiasing

In the spectrum of a periodically sampled waveform, the spectrum of the (unsampled) input signal repeats around harmonics of the sampling frequency. Any frequency contained in the input signal is repeated above and below each harmonic of the sampling frequency. Therefore, in the spectrum of the sampled signal, the band between 0 and f_{in} (the input spectrum) appears, among other places, between $f_s - f_{in}$ and f_s , where f_s is the sampling frequency.

Although you may be under the impression that the input-signal bandwidth is 100kHz, if the sampling frequency is 1Msample/s, a signal at 991kHz in the input spectrum would

appear as a 9kHz alias component in the spectrum of the sampled signal.

An antialiasing filter removes or at least attenuates any noise or spurious signals that could be aliased back into the bandwidth of interest. Figure 7 shows the frequency response of such a filter for a generalised a-to-d converter. Determine the filter roll-off by drawing a straight line between the highest signal frequency of interest, f_{in} , and the stop-band attenuation frequency, $f_s - f_{in}$. As the ratio of f_s to f_{in} increases (that is, as the oversampling ratio increases) the slope of the line decreases.

In an eight-bit system, an ideal a-to-d converter's signal-to-noise ratio (s/n) is slightly greater than 256:1 or 48dB. To prevent noise limiting the system performance, the ratio of the input signal-to-noise ratio should exceed the approximate 48dB limit imposed by the converter. Here, the signal is the peak-to-peak value of the signal within the band of interest, and the noise is the square root of the sum of the squares of the amplitudes of all the frequency components outside that band.

Attenuation required for signals outside the band of interest depends on the application and the expected magnitude of the out-of-band signals. In most cases, the magnitude of these signals is much lower than that of the desired signal.

Usually, eight-bit systems require 50dB of attenuation for signals that can be aliased into the band of interest. Even if 50dB is not the desired number, the following calculations show the kind of reduction in antialiasing filter requirements brought about by oversampling. With $2\times$ oversampling, i.e. with $f = 2f_{in}$, f_s and f_{in} are at the same point and the filter has to have infinite roll-off to attenuate signals at $f_s - f_{in}$. With $f_s = 3f_{in}$, ($3\times$ oversampling), the filter's attenuation must drop from 0dB at f_{in} to 50dB at $2f_{in}$. In other words, the slope of the attenuation vs frequency curve must be 50dB/octave; the filter (if it has a Butterworth characteristic) must have more than eight poles.

With $10\times$ oversampling, there are three octaves for the attenuation to drop from 0 to 50dB; the required slope is a little more than 16dB/octave and a three-pole Butterworth filter will do the job.

This analysis of the antialiasing filter holds true regardless of the type of a-to-d converter that follows the filter. No matter what the conversion technique, oversampling reduces the antialiasing filter requirements. Oversampling also reduces the converter noise within the signal bandwidth because it spreads the quantisation noise over a wider bandwidth. Oversampling has recently gained considerable popularity in connection with sigma-delta a-to-d converters. In the case of these converters, the advantages of oversampling are much greater than with successive-approximation or flash converters because noise shaping produces dramatic improvements in noise performance as the oversampling ratio increases.

However, the relationship between antialiasing-filter performance and oversampling is exactly the same for an oversampled sigma-delta modulator as for half-flash or successive-approximation alternatives; sigma-delta and half-flash a-to-d converters with the same oversampling ratio place the same demands on the antialiasing filter.

Pipelining or averaging inherent in sigma-delta converters is a disadvantage of the sigma-delta process for transient recording. Because of the pipelining, a step change requires a significant time (the settling time of the converter's digital filter) to ripple through to the output. Therefore, there is a delay before a sigma-delta converter produces an output that represents an input change. Between the time the input changes and the sigma-delta converter's output reflects the change, the a-to-d converter's output does not accurately represent the converter's input. Such performance is not appropriate for transient recorders of the type discussed here. ■

EDN
DESIGNER'S COMPANION


Series for Design Engineers

- Digital Techniques
- Analog Technology
- A/D Conversion
- Test and Measurement
- Standards
- Oscillators
- Generators
- Power Sources
- Motor Control
- Clocks

EDITED BY
IAN HICKMAN & BILL FRANKS

EDN Designer's Companion is available by postal application to room L333 EW+WW, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS. Please make cheques out to Reed Business Publishing Group Ltd. Credit card orders accepted by 'phone on 0181 652 3614. 254pp hardback ISBN 0 7506 1721 7 Price £25.00+£2.50 UK postage, £5 Europe, £8 worldwide.

Programming Solutions

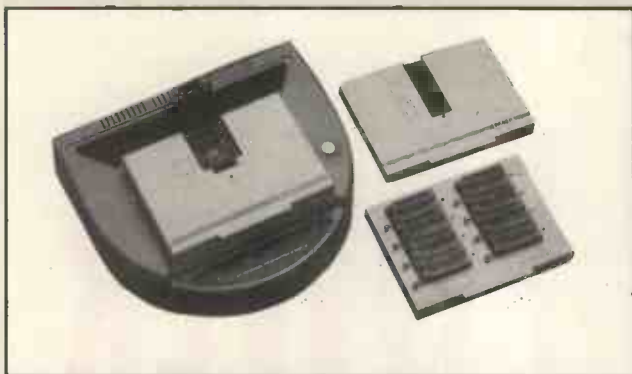

Multi-Device Programmer

- ◆ EPROMs, E²PROMs, Flash EPROMs, Serial E²PROMs, PLDs, GALs, PEELs, EPLDs, MACHs & WSI PSDs
- ◆ Micros – Intel, Microchip, Motorola, Zilog
- ◆ Fast programming algorithms.
- ◆ Connects direct to pc printer port.
- ◆ Simple full colour software.
- ◆ No expensive adapters.

ONLY
£325

Universal Programmer

- ◆ Uses standard pc printer port works with notebook and handbook pc's
- ◆ Pin driver expansion can drive up to 256 pins.
- ◆ Supports over 2000 IC's – 3 and 5 volt devices. EPROMs, E²PROMs, Bipolars, Flash, Serial EPROMs over 150 microcontrollers, WSI/Philips PSDs, PLDs, EPLDs, PEELs, PALs, GALs, FPGAs including MACH, MAX, MAPL & Xilinx parts
- ◆ Universal DIL (up to 48 pins), PLCC and gang PACs
- ◆ Powerful full colour menu driven software.
- ◆ Approved by AMD, TI, NatSemi, etc...
- ◆ Tests TTL, CMOS and SRAM devices (including SIMMS)

ONLY
£595

Eprom Programmer

EPROMs, E²PROMs, Flash and 8748/51 micros.
Fast programming algorithms. Simple colour menu operation.

ONLY
£139

EMULATORS • SIMULATORS • COMPILERS • ASSEMBLERS
PROGRAMMERS • 8051 8085 Z8 68020 77C82 80C552
320C25 68HC11 6301 6502 87C751 65816 Z80 6809
PIC 7720 MIPS etc.

SMART
COMMUNICATIONS

2 Field End • Arkley • Barnet • Herts • EN5 3EZ • England
Telephone +44 (0)181 441 3890 Fax +44 (0)181 441 1843

CIRCLE NO. 127 ON REPLY CARD



LANGREX SUPPLIES LTD


PHONE 0181 684 1166 FAX 0181 684 3056
DISTRIBUTORS OF ELECTRONIC VALVES
TUBES, SEMICONDUCTORS AND I.C.S.
1 MAYO ROAD • CROYDON • SURREY CR0 2QP
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

E.P.	EL86	2.75	PY500A	4.00	68A7	5.00	68K7	3.00
AZ31	EL91	3.00	PY800	1.50	68E6	1.50	68L7GT	4.50
CB131	EL95	2.00	PY801	1.50	68H6	2.50	68N7GT	4.50
CL33	EL360	18.50	QV02-6	12.00	68J6	2.25	68S7	3.00
DY86/7	EL509	12.00	QV03-10	5.00	68N6	2.00	68U8A	1.50
E88CC Mull	EM34	15.00	QV03-20A	15.00	68Q7A	3.50	68VGT	4.25
E180F	EM81	4.00	QV06-40A	17.50	68R7	6.00	68X	3.00
E810F	EM84	4.00	QV03-12	10.00	68R8A	4.00	68XGT	2.50
E8BC80	EM87	4.00	U19	10.00	68S7	6.00	12AT7	3.00
EB91	EN91 Mull	7.50	UABC8Q	1.50	68W6	4.50	12AU7	3.00
EBF80	EY51	2.50	UBC41	4.00	68W7	1.50	12AX7	3.50
EBF89	EY85	1.75	UBF89	£1.50	68Z6	2.50	12AX7A GE	7.00
ERL31	EY88	1.75	UCH42	4.00	6C4	2.00	12BA6	2.50
ECC33	EZ80	3.50	UCH81	2.50	6C6	5.00	12BE6	2.50
ECC35	EZ81	3.50	UCL82	2.00	6C85A	3.00	12BH7A GE	6.50
ECC81	GY501	3.00	UCL83	3.00	6C06GA	5.00	12BY7A GE	7.00
ECC82	GZ32 Mull	8.50	UF89	4.00	6CL6	3.75	12E1	15.00
ECC83	GZ33	8.00	U41	12.00	6CC7	7.50	12HG1/2GN7	6.50
ECC85	GZ34 GE	7.50	U84	3.50	6CH6	8.00	30FL1/2	1.50
ECC88 Mull	GZ37	6.00	UY41	4.00	6CW4	8.00	30P19	2.50
ECC91	KT61	10.00	UY85	2.25	6D6	5.00	300B(PR)	110.00
ECF80	KT66	10.00	VR105/30	2.50	6D05 GE	17.50	572B	70.00
ECF85	KT88	15.00	VR150/30	2.50	6D06B	12.50	805	50.00
ECH42	N78	9.00	2759	25.00	6E88	3.50	807	3.75
ECH81	OA2	2.70	2803U	25.00	6E85	1.85	811A	18.50
ECL80	OB2	2.70	2021	3.50	6F6	3.50	812A	65.00
ECL82	OC3	2.50	3B2B	15.00	6F07	£7.50	813	27.50
ECL83	OD3	2.50	4CK250B STC	55.00	6GK6	4.00	833A	85.00
ECL86 Mull	PCF80	2.00	5R4GY	6.00	6H6	3.00	865A	25.00
ECL880	PCF82	1.50	5U4G	5.25	6H56	4.95	872A	20.00
EF37A	PCF86	2.50	5V4G	4.00	6J5	3.00	931A	25.00
EF39	PCF801	2.50	5Y3GT	2.50	6J6	3.00	2050A GE	10.00
EF40	PCF802	2.50	5Z3	4.00	6J7	4.00	5751	6.00
EF41	PCLB2	2.00	5Z4GT	2.50	6J86A GE	19.00	5763	3.00
EF42	PCLB3	3.00	6AH6	4.50	6J86C	20.00	5814A	5.00
EF80	PCLB4	2.00	6AK5	4.50	6J86C GE	17.50	5842	12.00
EF85	PCLB5	2.50	6AL5	1.00	6KSGT	3.00	6080	7.50
EF86	PCLB6	2.50	6AM6	2.00	6K7	4.00	6146B GE	15.00
EF91	PCLB05	2.50	6AN5	5.00	6K8	4.00	6550A GE	20.00
EF92	PD500	6.00	6AN8A	4.50	6L6G	8.50	68B3B GE	16.00
EF183	PL36	2.50	6A05	3.25	6L6GCSYL	12.50	7025 GE	7.00
EF184	PL81	1.75	6AR5	25.00	6L6G Siemens	7.50	7027A GE	17.50
EL32	PL82	2.00	6AS6	3.50	6L6G GE	12.50	7199	10.00
EL33	PL83	2.50	6AS7G	9.50	6L7	1.50	7360	25.00
EL34 Siemens	PL84	2.00	6AT6	2.00	6L06	20.00	7586	15.00
EL36	PL504	2.50	6AUSGT	5.00	607	4.00	7587	23.00
EL41	PL508	5.50	6AU6	2.50	6RHH8/GN8B	12.00	7868	12.00
ELL80	PL509/PL519	6.00	6AW8A	4.00	6SA7	3.00	8417 GE	17.50
EL81	PL802	6.00	6B7	4.00	6SC7	3.00		
EL84	PY81	1.50	6B8	4.00	6SG7	2.50		
EL84 Mull	PY88	2.00	6BA6	1.50	6SJ7	3.00		

OPEN TO CALLERS MON-FRI 9AM-4PM, CLOSED SATURDAY.
OVER 6,000 TYPES AVAILABLE FROM STOCK. OBSOLETE ITEMS
A SPECIALITY. QUOTATIONS FOR ANY TYPES NOT LISTED.
TERMS: CWO/VISA/ACCESS. POST & PACKING: 1-3 VALVES £2.00,
4-6 VALVES £3.00. ADD 17.5% VAT TO TOTAL INC. P&P.

CIRCLE NO. 128 ON REPLY CARD

CROSSWARE

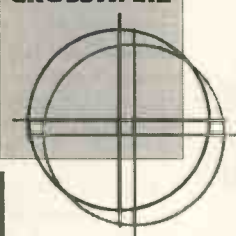

CROSS DEVELOPMENT
SOFTWARE TOOLS FOR THE PC

8051 C • ASSEMBLY

• SIMULATION

FULLY SUPPORTED
QUALITY SOFTWARE

8051 C Compiler (DOS)

An optimising C compiler with full support for floating point arithmetic, interrupts, embedded assembler, linking and relocation, IEEE695 debug output. Includes a complete relocatable cross assembler. Price: £349.00

8051 Cross Assembler (DOS)

Available in two variants: absolute and relocatable. The relocatable assembler allows you to flexibly link and locate your program into 8051 address space and generates IEEE695 debug output for symbolic information (ideal for use with our simulator). The absolute assembler is easy to use and creates final 8051 code from a single assembler source file.

Prices: Relocatable £169.00, Absolute £99.00

8051 Simulator (Microsoft Windows)

Watch your program run on your PC. Set breakpoints, single step, trace, watch and modify memory and SFR's. Generate interrupts, run the timers, serial port and parallel ports. All without a single piece of 8051 hardware. Works with any 8051 assembler or compiler that generates Intel hex, OMF51, IEEE695 or binary output. Uses debug information in OMF51 and IEEE695 files to create a symbolic disassembly of your program. Price: still only £99.00!

Data sheets and demo discs from:

(prices exclude VAT and delivery)

CROSSWARE PRODUCTS

St John's Innovation Centre, Cowley Road, Cambridge, CB4 4WS, UK
Tel: +44 (0) 1223 421263, Fax: +44 (0) 1223 421006
BBS: +44 (0) 1223 421207 (8-N-1), Internet: sales@crossware.com

CIRCLE NO. 129 ON REPLY CARD

LOW POWER

single-chip fm receiver

With fm receivers designed for battery-powered equipment, disconnecting the audio amplifier from the supply when it is not in use saves power and eliminates unnecessary audio hiss. Ed Baker describes an fm receiver ic designed to disconnect its own audio power stage.

This article describes how to apply the *ULN3883A*, a low-power, narrowband fm receiver ic providing the second converter, second IF demodulator and audio amplifier circuitry for communications and scanning receivers.

The device offers a number of advantages over other types of narrowband frequency-modulated receiver circuits, particularly for cordless telephones and other battery-operated receivers. Most such units operate in a mode in which the receiver is muted by removal of the audio input to the amplifier driving the loudspeaker, while still leaving this amplifier drawing a considerable current. This current can often be many times greater than that drawn by the rest of the receiver.

A more sensible way to mute the receiver is to disconnect the audio amplifier from its power supply so that it draws little or no current. This not only improves battery life (or intervals between charging), but also removes what can be a very annoying hiss from the loudspeaker.

This is exactly what is achieved in the *ULN3883A*. During normal operation, with no input present, the ic draws up to 15mA. Once the mute is operated, this drops to typically 3mA, drawn by the rest of the circuit: i.e. the

mixer, IF amplifier, detector and filter amplifier. This current reduction extends battery life considerably, depending on the operate-standby ratio of the equipment. In an extreme case, where a receiver spends 95% of its life in standby mode, battery life would be increased by a factor of ten.


Functional description

The device, which contains a number of distinct on-chip functions, Fig. 1, was originally designed for use as the second IF stage of a dual-conversion superheterodyne receiver with a first IF of 10.7MHz and a second IF of 455kHz. The high performance of the input circuitry, which exceeded its designer's expectations, also allows it to be used as a single conversion receiver for frequencies up to the low end of the vhf band. A typical application of the device in this role is the cordless telephone receiver shown in Fig. 2. Functions included in the *ULN3883A* are as follows:

Double balanced mixer. The active mixer, because of its nature, has an extremely high rejection of both input and oscillator frequency feedthrough, as well as reduced local-oscillator re-radiation. The circuit also exhibits a very wide dynamic range; in excess of 80dB.

Since the input circuitry is internally biased,

Fig.1. Schematic of the *ULN3883A* fm receiver ic shows the three subsections — converter, If demodulator and audio amplifier.

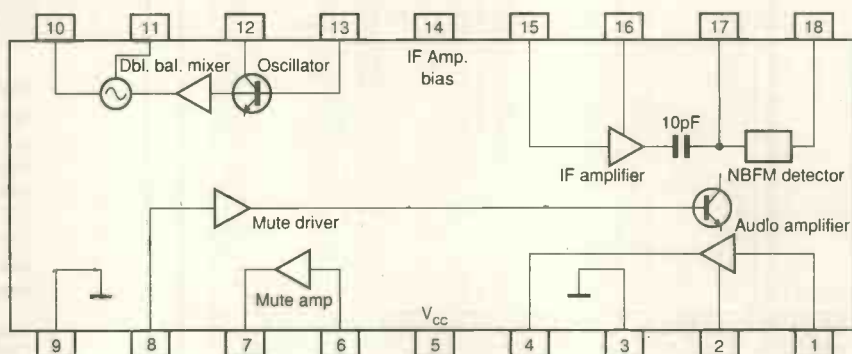

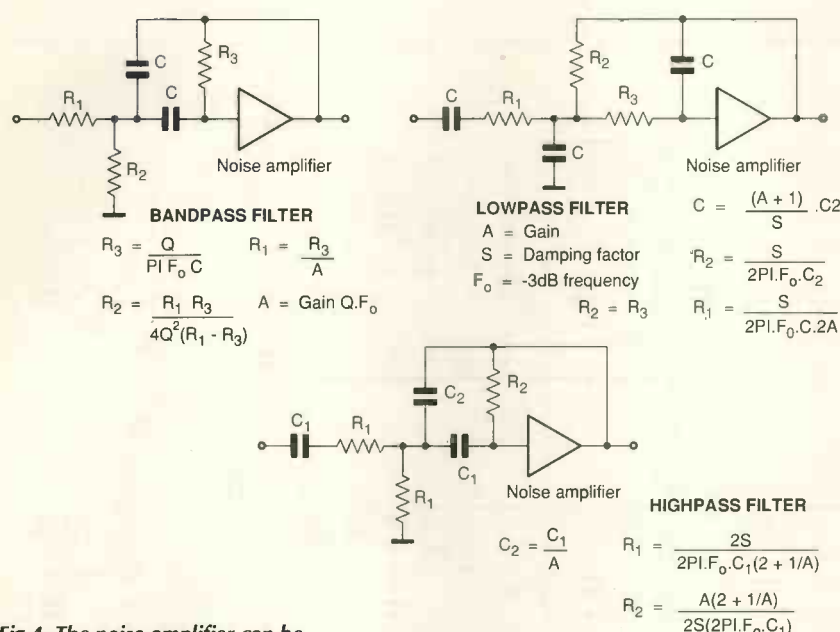


Fig.4. The noise-amplifier can be configured in a number of ways, the most common being the highpass filter.

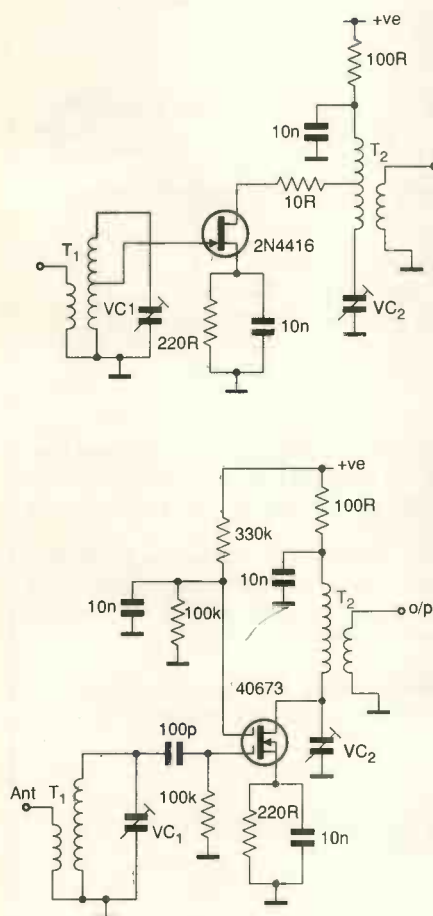


Fig.5,6. Improvements on noise factor and sensitivity of the receiver can be achieved using a jfet or a double gated mosfet in the rf input stage.

is fed into the detector output via an on-chip 10pF capacitor. This is brought out to pin 17, and connected to an external tuned circuit which is tuned to the IF frequency. The signal level on this pin should have a minimum level of 100mV rms for correct detector operation. The component connected to this pin is determined as follows:

$$V_{17} = V_1 Q_1 [10pF / (10pF + C)]$$

$$R_1 = Q_0 C [Q_1 / 9Q_0 - Q_1]$$

where
 $V_1 = 140mV$ rms
 $C =$ detector tuning capacitance
 $Q_1 =$ loaded Q of detector coil
 $Q_0 =$ unloaded Q of detector coil
 $R_1 =$ damping resistor across tuned circuit.

The output circuit of the detector is an emitter of 400Ω output impedance. Since some of the IF signal is still present, care needs to be taken with the circuit layout so that the circuitry connected to pin 18 does not associate with the components connected to pin 16.

Audio amplifier. The stage gain of the power amplifier is typically 35dB, and is designed to drive either a 4Ω or an 8Ω loudspeaker. With a supply voltage of 5V, it is capable of an output of 260mW at a third-harmonic distortion of 10%.

The output-circuit coupling capacitor should be selected to give the desired IF response and to reduce power consumption caused by unwanted IF drive to the loudspeaker. To ensure optimum stability, the ground side of the speaker return should be connected as close as possible to pin 3: the amplifier (and main) ground connection.

Noise amplifier. This is an inverting amplifier with an open-loop gain of 53dB at 4kHz, and requires a feedback resistor between the

input and output (pins 6 and 7) to reduce the gain to a more practical level.

The amplifier can be configured as a low-pass filter, a bandpass filter or a highpass filter, the last being the most commonly used in applications of this type (Fig. 4). All capacitors used should be of a high-Q variety such as polystyrene or polycarbonate; if ceramics are used, the filter will not perform to the required specifications.

Muting switch. The input circuit is a 22kΩ resistor in series with the base of a transistor whose emitter is connected to ground. As expected, the threshold is the same as the forward bias point of a transistor (around 600mV). Since all muting functions are on the chip, this stage has no output pin.

Applications

The application shown in Fig. 2 is by no means definitive. Improvements in this design can be made by changing the rf input stage to a jfet (Fig. 5), a dual-gate mosfet (Fig. 6) or even a gaAsfet. Since receiver sensitivity is determined by the selection of this stage, a device must be chosen to give a noise factor and gain which presents sufficient input to give full limiting (8μV) and enough sensitivity for a reasonable signal to noise ratio with the signal being received. The market abounds with suitable alternatives to those given (e.g. U310, BF800, BF981, 3SK51, 3N200, 3N140 etc.). Depending on which is chosen, the component values will have to be modified to suit the transistor selected.

The ceramic filter connected to L_4 determines the degree of rejection of image signals and so should have a good out-of-band rejection characteristic, while the filter connected to IFT_1 determines the overall receiver bandwidth and adjacent channel rejection. The first filter could be replaced by a saw filter, and the second by a crystal filter, if improved performance is required.

The circuit shown in Fig. 2 has an audio filter which tailors the audio for speech reception in series with the af amplifier. If this is not required for reasons of cost or fidelity, it can be omitted, and a simpler circuit using a 50kΩ volume control can be used.

As shown in Fig. 2, the ULN3883A is used with (a) a crystal oscillator using the onboard circuitry; (b) a tuned LC oscillator, again using the onboard circuitry; or (c) either of the above using an external oscillator or a synthesiser. If option (c) is required, a signal with an amplitude of 500mV is required at pin 13 of the ULN3883A.

The device is, of course, not limited to acting as a single superheterodyne receiver. As indicated, it can also act as the second mixer/oscillator and IF amplifier in either a fixed capacity or as a tuneable If with a broadband front-end circuit. This practice is very common in vhf and uhf receivers where it is difficult and expensive to manufacture stable oscillators or synthesisers.

NEW LOW PRICE - NEW COLOUR HP141T SPECTRUM ANALYSERS TESTED

HP141T + 8552A or B IF - 8553B RF - 1kHz - 110Mc/s - A IF £600 or B IF - £700.
HP141T + 8552A or B IF - 8554B RF - 100kHz - 1250Mc/s - A IF £800 or B IF - £900.
HP141T + 8552A or B IF - 8555A RF - 10Mc/s - 18GHz - A IF £1400 or B IF - £1600. The mixer in this unit costs £1000, we test every one for correct gain before despatch.
HP141T + 8552A or B IF - 8556A RF - 20Hz - 300kHz - A IF £600 or B IF - £700.

HP ANZ UNITS AVAILABLE SEPARATELY NEW COLOUR - TESTED

HP141T Mainframe - £350 - 8552A IF - £200 - 8552B IF - £300 - 8553B RF - 1kHz - 110Mc/s - £200 - 8554B RF - 100kHz - 1250Mc/s - £400. 8555A RF - 10Mc/s - 18GHz - £1000. 8556A RF - 20Hz - 300kHz - £250.
HP8443A Tracking Generator Counter - 100kHz - 110Mc/s - £300 - £400.
HP8445B Tracking Pre-selector DC - 18GHz - £400 - £600 or HP8445A - £250.
HP8444A Tracking Generator - £750 - 1300Mc/s.
HP8444A Opt 059 Tracking Generator - £1000 - 1500Mc/s.

SPECIAL OFFER - 14 ONLY HP140T (NON-STORAGE)

Mainframe Plus 8552A IF Plug-In Plus 8556A RF Plug-In 20Hz - 300kHz Plus 8553B RF Plug-In 1kHz - 110Mc/s. Tested with instructions - £700.

Marconi TF2008 - AM-FM signal generator - also sweeper - 10Kc/s - 510Mc/s - from £250 - tested to £400 as new with manual - probe kit in wooden carrying box.
 HP Frequency comb generator type 8406 - £400.
 HP Vector Voltmeter type 8405A - £400 to £600 - old or new colour.
 HP Sweep Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18.40GHz. P.O.R..
 HP Network Analyzer type 8407A + 8412A + 8501A - 100Kc/s - 110Mc/s - £500 - £1000.
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447F. 1-1300Mc/s £400.
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.
 HP 8410 - A - B - C Network Analyzer 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411a - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000.
 Racal/Dana 9301A - 9302 RF Millivoltmeter - 1.5-2GHz - £250-£400.
 Racal/Dana Counters 9915M - 9916 - 9917 - 9921 - £150 to £450. Fitted FX standards.
 Racal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.
 Marconi RCL Bridge type TF2700 - £150.
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055A - 6059A - 6057A - 6056 - £250-£350. 400Mc/s to 18GHz.
 Marconi TF1245 Circuit Magnification meter + 1246 & 1247 Oscillators - £100-£300.
 Marconi microwave 6600A sweep osc., mainframe with 6650 PI - 18-26.5GHz or 6651 PI - 26.5-40GHz - £1000 or PI only £600. MF only £250.
 Marconi distortion meter type TF2331 - £150. TF2331A - 200.
 Tektronix Plug-Ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - 7B80 + 85-7B92A
 Gould J3B test oscillator + manual - £200.
 Tektronix Mainframes - 7603 - 7623A - 7613 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904 - 7834 - 7104 - 7623 - 7633.
 Altech 757 Spectrum Analyser - 001 22GHz - Digital storage + readout - £2000.
 Marconi 6155A Signal Source - 1 to 2GHz - LED readout - £400.
 Barr & Stroud Variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2163S attenuator - 1GHz. £200.
 Farnell power unit H60/50 - £400 tested. H60/25 - £250.
 Racal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A or N.A Interface.
 Marconi TF2330 - or TF2330A wave analysers - £100-£150.
 Racal/Dana signal generator 9082 - 1.5-520Mc/s - £500.
 Racal/Dana signal generator 9082H - 1.5-520Mc/s - £600.
 Tektronix - 7S14 - 7T11 - 7S11 - 7S12 - S1 - S2 - S39 - S47 - S51 - S52 - S53 - 7M11.
 Marconi mod meters type TF2304 - £250.
 HP 5065A rubidium vapour FX standard - £2.5k.
 Systron Donner counter type 6054B - 20Mc/s - 24GHz - LED readout - £1k.
 Racal/Dana 9083 signal source - two tone - £250.
 Systron Donner - signal generator 1702 - synthesized to 1GHz - AM/FM - £600.
 Tektronix TM515 mainframe + TM5006 mainframe - £450 - £850.
 Rhodes & Schwartz power signal generator SLRD-280 - 2750Mc/s - £250-£600.
 Ball Efratom rubidium standard PT256B-FRKL - £1000.
 Farnell electronic load type RB1030-35 - £350.
 Racal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards.
 HP4815A RF vector impedance meter c/w probe - £500-£600.
 Marconi TF2092 noise receiver. A, B or C plus filters - £100-£350.

Marconi TF2091 noise generator. A, B or C plus filters - £100-£350.
 HP180TR, HP182T mainframes £300-£500.
 Fluke 8506A thermal RMS digital multimeter. £400.
 Philips panoramic receiver type PM7900 - 1 to 20GHz - £400.
 Marconi 6700A sweep oscillator + 6730A - 1 to 2GHz - £500.
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.
 Racal/Dana VLF frequency standard equipment. Tracer receiver type 900A + difference meter type 527E + rubidium standard type 9475 - £2750.
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz.
 HP 432A - 435A or B - 436A - power meters + powerheads - Mc/s - 40GHz - £200-£1000.
 Bradley oscilloscope calibrator type 192 - £600.
 Barr & Stroud variable filter EF3 0.1Hz - 100Kc/s + high pass + low pass - £150.
 Marconi TF2370 spectrum ANZ - 110Mc/s - £900.
 Marconi TF2370 spectrum ANZ + TK2375 FX extender 1250Mc/s + 1st gen - £1.5k.
 HP8614A signal generator 800Mc/s - 2.4GHz, new colour £400.
 HP8616A signal gen 1.8GHz - 4.5GHz, new colour £400.
 HP 3325A syn function gen 20Mc/s - £1500.
 HP 3336A or B syn level generator - £500-£600.
 HP 3586B or C selective level meter - £750-£1000.
 HP 3575A gain phase meter 1Hz - 13Mc/s - £400.
 HP 8671A syn microwave 2 - 6.2GHz - £2k.
 HP 8683D S/G microwave 2.3 - 13GHz - opt 001 - 003 - £4.5k.
 HP 8660 A-B-C syn S/G. AM + FM + 10Kc/s to 110Mc/s PI - 1Mc/s to 1300Mc/s - 1Mc/s to 2500Mc/s - £750-£2800.
 HP 8640B S/G AM-FM 512Mc/s or 1024Mc/s. Opt 001 or 002 or 003 - £800-£1250.
 HP 8656A S/G AM-FM 0.1 - 990Mc/s - £1500.
 HP 8622B Sweep PI - 01 - 2.4GHz + ATT - £1750.
 HP 8629A Sweep PI - 2 - 18GHz - £1000.
 HP 86290B Sweep PI - 2 - 18GHz - £1250.
 HP 86 Series PI's in stock - splitband from 10Mc/s - 18.6GHz - £250-£1k.
 HP 8620C Mainframe - £250. IEEE - £500.
 HP 8615A Programmable signal source - 1MHz - 50Mc/s - opt 002 - £1k.
 HP 8601A Sweep generator. 1 - 110Mc/s - £300.
 HP 4261A LCR meter + 16038A test leads - £400.
 HP 4271B LCR meter 1MHz digital meter + 16063A test adaptor - £850.
 HP 4342A Q meter 22kHz - 70Mc/s 16462A + qty of 10 Inductors - £850.
 HP 3488A HP - IB switch control unit - £500 + control modules various - £175 each.
 HP 3561A Dynamic signal ANZ - £3k.
 HP 8160A 50Mc/s programmable pulse generator - £1400.
 HP 853A MF ANZ + 8558B - 0.1 - 1500Mc/s - £2500.
 HP 8349A Microwave Amp 2 - 20GHz Solid state - £1500
 HP 3585A Analyser 20Hz - 40Mc/s - £4k.
 HP 8569B Analyser .01 - 22GHz - £5k.
 HP 3580A Analyser 5Hz - 50kHz - £1k.
 HP 1980B Oscilloscope measurement system - £600.
 HP 3455A Digital voltmeter - £500.
 HP 3437A System voltmeter - £300.
 HP 3581C Selective voltmeter - £500.
 HP 5370A Universal time interval counter - £450.
 HP 5335A Universal counter - 200Mc/s - £500.
 HP 5328A Universal counter - 500Mc/s - £250.
 HP 6034A System power supply - 0 - 60V - 0 - 10 amps - £500.
 HP 3960A 3964A Instrumentation tape recorders - £300-£500.
 HP 5150A Thermal printer - £250.
 HP 1645A Data error analyser - £150.
 HP 4437A Attenuator - £150.
 HP 3717A 70Mc/s modulator - £400.
 HP 3710A - 3715A - 3716A - 3702B - 3703B - 3705A - 3711A - 3791B - 3712A - 3793B microwave link analyser - P.O.R.
 HP 3730A + B RF down converter - P.O.R.
 HP 3552A Transmission test set - £400.
 HP 3763A Error detector - £500.
 HP 3764A Digital transmission analyser - £600.
 HP 3770A Amp delay distortion analyser - £400.
 HP 3780A Pattern generator detector - £400.
 HP 3781A Pattern generator - £400.
 HP 3781B Pattern generator (bell) - £300.
 HP 3782A Error detector - £400.
 HP 3782B Error detector (bell) - £300.
 HP 3785A Jitter generator + receiver - £750-£1k.
 HP 8006A Word generator - £100-£150.
 HP 8016A Word generator - £250.
 HP 8170A Logic pattern generator - £500.
 HP 59401A Bus system analyser - £350.
 HP 59500A Multiprogrammer HP - IB - £300.
 Philips PM5390 RF syn - 0.1 - 1GHz - AM + FM - £1250.
 Philips PM5519 Colour T.V. pattern generator - £250.
 S.A. Spectral Dynamics SD345 spectroscopy 111 - LF ANZ - £2500.
 Tektronix R7912 Transient waveform digitizer - programmable - £400.
 Tektronix 496 Analyzer 1kHz - 1.8GHz - £3.5k.
 Tektronix TR503 + TM503 tracking generator 0.1 - 1.8GHz - £1k - or TR502.
 Tektronix 576 Curve tracer + adaptors - £900.
 Tektronix 577 Curve tracer + adaptors - £900.
 Tektronix 1502/1503 TDR cable test set - £1000.
 Tektronix 7L5 LF analyser - 0 - 5Mc/s - £800. OPT 25 - £1000.
 Tektronix AM503 Current probe + TM501 m/frame - £1000.
 Tektronix SC501 - SC502 - SC503 - SC504 oscilloscopes - £75-£350.
 Tektronix 465 - 465B - 475 - 2213A - 2215 - 2225 - 2235 - 2245 - £250-£1000.
 Kikusui 100Mc/s Oscilloscope COS6100M - £350.
 Farnell PSG520 Signal generator - £400.
 Nicolet 3091 LF oscilloscope - £1000.
 Racal 1991 - 1992 - 1988 - 1300Mc/s counters - £500-£900.
 Tek 2445 150Mc/s oscilloscope - £1400.
 Fluke 80K-40 High voltage probe in case - BN - £100.
 Racal Recorders - Store 4 - 4D - 7 - 14 channels in stock - £250 - £500.
 Racal Store Horse Recorder & control - £400-£750 Tested.
 EIP 545 microwave 18GHz counter - £1200.
 Fluke 510A AC ref standard - 400Hz - £200.
 Fluke 355A DC voltage standard - £300.
 Schlumberger 5229 Oscilloscope - 500Mc/s - £500.
 Solartron 1170 FX response ANZ - LED display - £280.
 Wiltron 610D Sweep Generator + 6124C PI - 4 - 8GHz - £400.
 Wiltron 610D Sweep Generator + 61084D PI - 1Mc/s - 1500Mc/s - £500.
 Time Electronics 9814 Voltage calibrator - £750.
 Time Electronics 9811 Programmable resistance - £600.
 Time Electronics 2004 D.C. voltage standard - £1000.
 HP 8699B Sweep PI YIG oscillator .01 - 4GHz - £300. 8690B MF - £250. Both £500.
 Schlumberger 1250 Frequency response ANZ - £2500.
 Dummy Loads & power att up to 2.5 kilowatts FX up to 18GHz - microwave parts new and ex equip - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors, etc.
 B&K Items in stock - ask for list.
 W&G Items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Racal etc. Ask for list.


ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS, AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA
 ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCHROS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No: (01274) 684007. Fax: 651160

CIRCLE NO. 130 ON REPLY CARD

PROFESSIONAL SCHEMATIC CAPTURE AND PCB SOFTWARE FOR WINDOWS *NEW!*

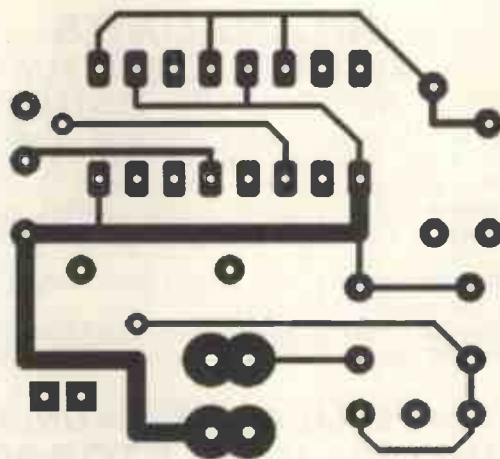At last, professional schematic and PCB design software for Microsoft Windows is available at prices that won't break the bank. CADPAK for Windows offers entry level schematic and PCB drafting whilst PROPAK for Windows adds netlist integration, multi-sheet schematics, highly effective autorouting, power plane generation and much more.



ISIS Illustrators

ISIS Illustrators was the first schematic drawing package for Windows and it's still the best. Illustrators's editing features will enable you to create circuit diagrams as attractive as the ones in the magazines.

- Runs under Windows 3.1.
- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Automatic wire routing and dot placement.
- Fully automatic annotator.
- Comes complete with component libraries; edit your own parts directly on the drawing.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Exports diagrams to other applications via the clipboard.

ARES for Windows

ARES for Windows provides all the functionality you need to create top quality PCB layouts under Microsoft's GUI. Combining the best of our DOS based PCB layout technology with the best of Windows, this package is our most powerful and easy to use PCB design tool to date.

- True 32 bit application under Windows 3.1.
- Advanced route editing allows modification or deletion of any section of a track.
- Unlimited number of named pad/track styles.
- Comprehensive package library for both through hole and SMT parts.
- Full imperial & metric support including all dialogue forms.
- Gerber, Excellon and DXF outputs as well as output via Windows drivers. Also includes Gerber viewer.
- Multi-strategy autorouter gives high completion rates; power plane generator creates ground planes with ease.

LOW PRICES!

CADPAK for Windows	£149
CADPAK for DOS	£79
PROPAK for Windows	£495
PROPAK for DOS	£395

Labcenter
Electronics

Prices exclude postage (£5 for UK) and VAT. All manufacturers trademarks acknowledged.

Call us today on 01756 753440 or else fax 01756 752857 for a demo pack - please state DOS or Windows as these products are available for both platforms.

CIRCLE NO. 131 ON REPLY CARD

53-55 Main St. Grassington, N. Yorks. BD23 5AA

Smash – simulation via Windows

*Smash – the subject of this month's **free disk offer** – is a multi-level, mixed-mode simulator running under Windows and featuring true behavioural modelling.*

The simple example, starting on the right, demonstrates the possible analyses in *Smash*. As it may be the first example you will try, it is kept simple, being purely analogue and using only primitives. However, it demonstrates features like parameter sweeping and Monte Carlo analysis. It is a simple RC network, the demonstration files for which are on the evaluation disk. The disk is a fully-working version of *Smash*, limited only to 25 analogue and 50 digital nodes.

Notes on behavioural modelling

Behavioural modelling is a term you have probably heard a number of times. The fact is that most often, people talk about behavioural modelling as soon as the model is not a low-level primitive – a transistor or gate.

This is particularly true where analogue simulation is concerned. Some people even consider, or want you to believe, that a G device (i.e. Spice-device) is a behavioural model. But genuine behavioural modelling goes far beyond this.


The designation behavioural has long been reserved for a design method that describes parts of your system via a high-level programming language. Behavioural means that you describe the way a component works, without presuming the way it is actually implemented. The purpose of the method can be to make an architectural study of a system at early stages of the design, before implementation has been fully decided. Or you can use it simply to increase the speed of a simulation – a few lines of code can easily replace thousands of transistors or gates.

There is nothing wrong with using a different term (behavioural) for differentiating things which do not readily map to anything physical, like a G-device, a Laplace-defined block, or a non-linear equation. But you should be aware that behavioural modelling may have more than one meaning.


In *Smash*, you can use Laplace-defined blocks and non-linear conditional equations. But the true power of the software comes from its capacity to mix genuine behavioural models – both analogue and digital – with primitives. As the *Smash* HDL is based on the popular C language, you can use variables, complex control structures – loops, etc – and all the features available in a

high-level programming language.

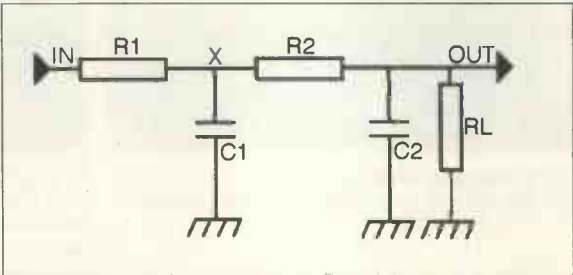Since these models are compiled, not interpreted, they are highly efficient and you can simulate complete systems, ics and/or pcbs, that you would not be able to simulate with any other tool.



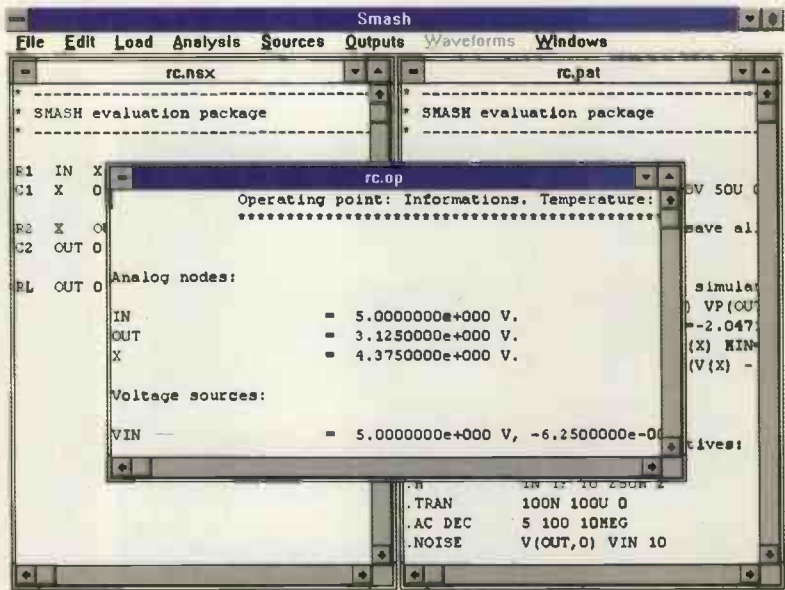*A: This is a simple RC circuit used to demonstrate some of *Smash*'s features.*



B: These three windows are the netlist, pattern and operating point files for the simple RC circuit. These files are contained on the evaluation disk in the 'eval' folder (example continued over)...


Free CAD software offer

The full version of the Smash multi-level, mixed-mode simulator costs £1500. The first 1000 EW+WW readers sending in the coupon opposite this page can obtain a size-limited but otherwise fully functional evaluation version of Smash free of charge.


Smash and schematic entry

There is no proprietary schematic entry in *Smash*. Instead it interfaces at the netlist level with commercial schematic entry packages. Basically any schematic entry program with a Spice netlist output can be used with *Smash*.

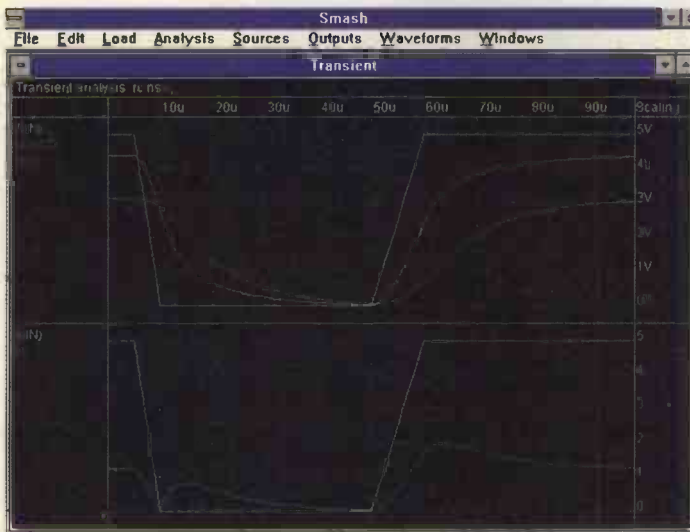
Some packages are tightly integrated with *Smash*, with libraries available etc. Among these are *DesignWorks* from Capilano Computing, *ECS/Synario* from Data I/O, and *Opus 4.2.2* from Cadence. The *DesignWorks* and *ECS/Synario* libraries for *Smash* are contained on the evaluation floppy. ■



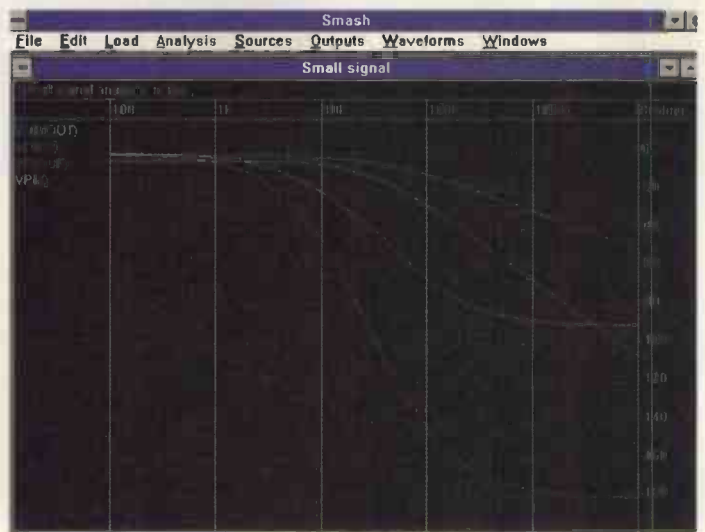
C: Analysing the circuit for transients is simply a matter of selecting the transient parameters under the Analysis menu and running the routine.



D: Small-signal analysis is equally simple. Note that running this analysis does not result in the previous transient analysis window being lost. Waveform processing – zooming, measuring etc – is available, even when a simulation is running, through the commands under the Waveforms menu. You may add new signals in the window with the Add analogue signals item. A dialog box displays a list of available signals. Simply double-click the name of the signals you want to view.

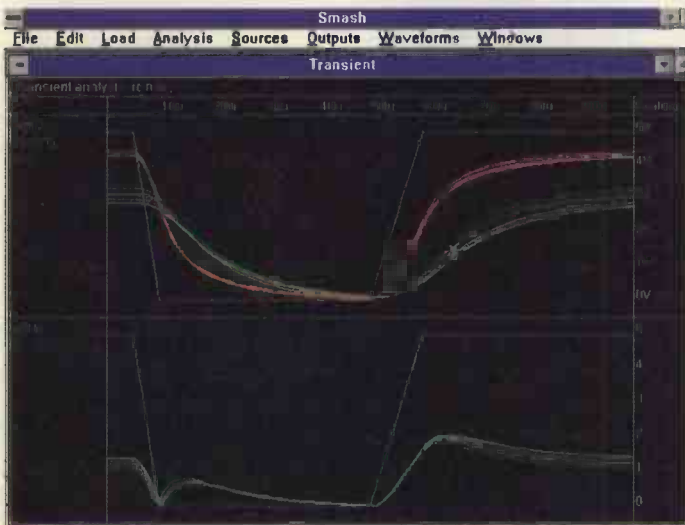

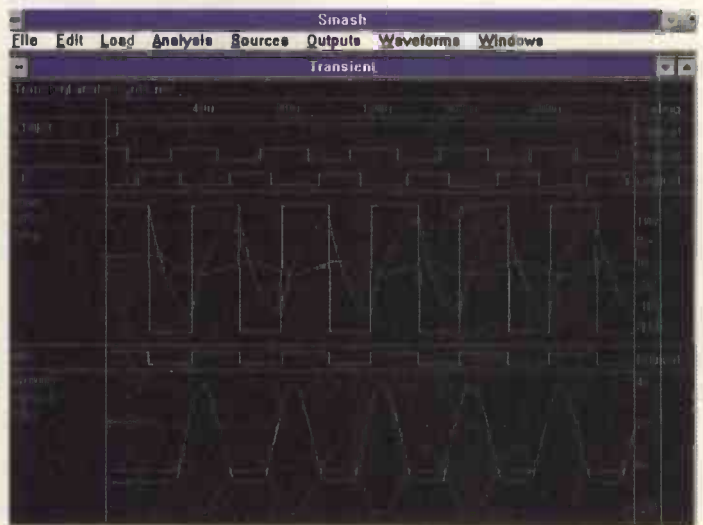E: In Monte Carlo analyses component values are varied at random, according to specified statistical distributions and tolerances. Also, the analyses are re-run a number of times. In this way, you can simulate how off-the-shelf component tolerances affect the circuit's response.



F: An example of running the transient analysis routine for a mixed analogue and digital circuit. In this case, *Smash* has to deal with both analogue voltages and logic levels. Whenever a node connects to both analogue and digital components, it becomes an interface node.

KENWOOD

TEST & MEASURING INSTRUMENTS
A SUPERB RANGE OF OVER 100
QUALITY INSTRUMENTS.

Available from
B.K. ELECTRONICS



- FM-AM Signal Generators ★ Colour Pattern Generators ★ Video Signal Analyser ★ Video Timing Analyser ★ Video Noise Meter ★ Distortion Meter ★ Waveform Monitors ★ Vectorscopes ★ Audio Generators ★ Wow and Flutter Meters ★ Electronic Voltmeters ★ Digital Multimeters ★ Function Generators ★ Frequency Counters ★ Bus Analyser ★ Resistance Attenuator ★ Oscilloscopes ★ Fully Programmable Digital Storage Oscilloscopes ★ Regulated D.C. Power Supplies

A free, 50 page colour brochure, including price list, is available on request. Please make your request on company headed notepaper, by post or by fax, to:

B.K. ELECTRONICS
Unit 1 Comet Way,
SOUTHEND-ON-SEA,
Essex, SS2 6TR.
Tel: 01702-527572
Fax: 01702-420243



CIRCLE NO. 132 ON REPLY CARD

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200. PLUG-INS SOLD SEPARATELY

TEKTRONIX 2465, 4 Ch, 300MHz Delay Sweep Cursors	£1750
TEKTRONIX 2245A, 4 Channel 100MHz Cursors/Polymeter etc	£1250
TEKTRONIX 2245A, 4 Channel 100MHz Cursors etc	£1000
TEKTRONIX 485 Dual Trace 350MHz Delay Sweep	£750
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£500
TEKTRONIX 465 Dual Trace 150MHz Delay Sweep	£400
TEKTRONIX SC504 Dual Trace 60MHz in TM5036 As new	£500
IMATSU SS5711C 4 Channel 100MHz Delay Sweep with DMM	£500
TRIO CS2019 4 Channel 70MHz Delay Sweep	£450
TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep	£450
TEKTRONIX 2213 Dual Trace 60MHz	£350
HITACHI VS509 Dual Trace 60MHz Delay Sweep	£350
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400
GOULD OS1100 Dual Trace 30MHz with Delay	£240
HITACHI 412 Dual Trace 20MHz Trng to 40MHz Delay	£225
TEKTRONIX T922 Dual Trace 150MHz	£700
GOULD OS2508 Dual Trace 150MHz	£125
BECKMAN 9020 Dual Trace 20MHz Delay Sweep	£240
IMATSU SS5702 Dual Trace 20MHz	£200
TRIO CS3555A Dual Trace 20MHz	£700
PHILIPS PM3207 Dual Trace 15MHz TV Trng	£200
HITACHI VC5045 Dual Trace 100MHz 40MS/S Cursors Digital Storage	£1100
PHILIPS PM3305 Dual Trace 15MHz Digital Storage	£650
H.P. 1741A Dual Trace 100MHz Analogue Storage	£350
GOULD OS4000 Dual Trace 100MHz Digital Storage	£200

THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE

HEWLETT PACKARD 1740A Oscilloscopes 100MHz Dual Trace Delay Sweep	only £350
---	-----------

EATON/ALTECH 380K11 Syn Gen 1-2000MHz with PM3602 AM/FM Phase Mod.

H.P. 8656A Syn Sig Gen 100kHz - 990MHz	£1900
MARCONI 2010 Syn AM/FM Sig Gen 50kHz - 1040MHz	£1800
MARCONI 2022 AM/FM Sig Gen 10kHz - 1000MHz	£1250
MARCONI 2018 Synthesized AM/FM Sig Gen 60kHz - 520MHz	£700
H.P. 8620C Sweep Oscillator with 86245A S.S. - 12.4GHz	£400
SYSTEM DUNMER 1702 Syn AM/FM Sig Gen 10kHz - 1GHz	£500
RACAL 9081 Synthesized AM/FM Sig Gen 5 - 520MHz	£500
FARNELL SS5520 Synthesized AM/FM Sig Gen 10 - 520MHz	£400
MARCONI TF2015 AM/FM Sig Gen 10 - 520MHz	£200
MARCONI TF2015 with Synchronizer TF2171 (Lock box)	£350
MARCONI TF2016 AM/FM Sig Gen 10kHz - 120MHz	£250
MARCONI TF2016 with Synchronizer TF2173 (Lock box)	£375
H.P. SMITH ANTENNA type 12-602-A	£200
RACAL INSTRUMENTATION RECORDER type Slore 4DN	£500
MARCONI TF2337 Automatic Distortion Meter	£700
RADFORD 100A Low Distortion Oscillator	£300
RADFORD LDM52 Low Distortion Measuring Set	£100

SPECTRUM ANALYSERS

H.P. 8565A 0.01 - 220Hz	£5000
POLARAD 641-1 10kHz - 18GHz	£1500
ANDO AC8281 with AC8211 1700MHz	£1500
H.P. 182 with 8558B 100kHz - 1500MHz	£1500
H.P. 141T with 8554B & 8552B 500kHz - 1250MHz	£1200
H.P. 141T with 8553B & 8552A 1kHz - 110MHz	£800
MARCONI TF2370 30Hz - 110MHz	£1000
H.P. 141T Main Frames only, Good Tubes	£275
TEKTRONIX 7L12 10kHz - 1800MHz Complete with Main Frame	£1200
TEKTRONIX 7L5 20Hz - 5MHz Complete with Main Frame	£1000

MARCONI 2440 Microwave Counter 10GHz - 20GHz MPB	£1250
H.P. 3456A DVM 6 1/2 digit DC/Time RMS AC/Ris HPB	£600
H.P. 3341A Frequency Counter 50MHz - 1.5GHz LED	£300
MARCONI 2435 Digital Frequency Meter ZGH	£400
RACAL 1956 Frequency Counter 1.30Hz (Options GPIB & High Stab)	£300
RACAL/DANA 1991 Universal Counter/Timer 150MHz 9 digit	£800
MARCONI 2437 Universal Counter/Timer DC - 100MHz 8 digit	£175
MARCONI 2431A Frequency Counter 10Hz - 200MHz 8 digit	£150
MARCONI 2430A Frequency Counter 10Hz - 50MHz 8 digit	£175
RACAL 9918 Frequency Counter 10Hz - 520MHz 9 digit	£200
RACAL 9906A Universal Counter Timer 200MHz	£250
RACAL 9916 Frequency Counter 10Hz - 50MHz 8 digit	£175
DATRON 1014 6 1/2 digit Automatic Multimeter True RMS AC/Current	£150
H.P. 3435A 3 1/2 digit Multimeter AC/DC/Ohms/Current LED	£100
PHILIPS PM2534 Multi Function DMM 3 1/2 - 6 1/2 digit GPIB/IEEE	£450
SOLARTRON 7150 6 1/2 - 3 1/2 digit DMM with IEEE	£400
SOLARTRON 7045 4 1/2 digit Multimeter Vrms/Amps/Ohms	£80
MARCONI TF2700 Universal Bridge Battery Operated	from £150
MARCONI TF1313A Universal LCR Bridge 0.1Hz	£175
WAYNE KERR 8424 Digital Component Meter LCR	£200
BRADLEY 192 Oscilloscope Calibrator	£600
WILTRON 560 Scalar Network Analyser with Detectors	£1000
FARNELL 1030 100 - 30 Volts 0 - 100 Amps Metered	£800
FARNELL TYS70 Mx2 70 Volts 5 Amps/35 Volts 10 Amps Metered	£200
FARNELL 830 10 30 Volts 10 Amps Variable	£200
FARNELL 3302 0 - 30 Volts 0 - 5 Amps Metered	£175
THURLBY PL320MD 30V 2A Twice Digital	£250
THURLBY PL320 30V 2A Digital	£120
H.P. 8516A 0 - 30V 0 - 5mA Metered	£150
BRANDENBURG Model 4728 4 - 28V Metered	£200
FEEDBACK FG600 Sine Sq Trn 0.01Hz - 100kHz	£60
BLACK STAR Meter 100 - 100MHz - Frequency Counter	£70
FARNELL PS101 Pulse Gen 100ns 10kHz (1 Sec. Hold)	£125
LINDOS LA1 Mx2B Audio Analyser	£500
UNOAHM BP501 Audio Analyser	£350
PHILIPS PM5518 Colour TV Pattern Generator	£1000
H.P. 4275A Multi Freq LCR Component Meter	£3500
TNANOR TG501 Fun Gen 0.005Hz-5MHz Sine/Sq Trn/Ramp/Pulse etc	£200
MARCONI TF2331 Distortion Factor Meter 20MHz-200kHz 0.05%	£150
MARCONI TF2163 Attenuator DC - 28V Metered	£200
MARCONI TF633B Audio Power Meter Sine	£250
H.P. 16300 Logic Analyser 43 Chn	£750
H.P. 8405A Vector Voltmeter 1-1000MHz	from £300
RACAL 910A RF Power Meter 1MHz - 1GHz 10mW-300W	£400
RACAL 9100 Absorption Wattmeter 1.5MHz-520MHz 300mW	£100
H.P. 5005A Signature Multimeter	£250
CALIFORNIA Inst AC POWER SOURCE 971XP	P.B.A.

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1015 Triple Trace 130MHz Delay Timebase	£847
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep	£653
HAMEG OSCILLOSCOPE HM203.7 Dual Trace 20MHz Component Tester	£362
HAMEG OSCILLOSCOPE HM205.3 Dual Trace 20MHz Digital Storage	£653

All other models available - all oscilloscopes supplied with 2 probes

BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10-100MHz Counter Timer Ratio/Period/Time interval etc	£234
APOLLO 100-100MHz (As above with more functions)	£332
METER 100 FREQUENCY COUNTER 600MHz	£119
METER 600 FREQUENCY COUNTER 100MHz	£119
METER 1000 FREQUENCY COUNTER 1GHz	£189
JUPITOR 500 FUNCTION GEN 0.1Hz-50kHz Sine/Sq Trn	£275
ORION COLOUR BAR GENERATOR Pal/TV/Video	£243

All other Black Star Equipment available

OSCILLOSCOPE PROBES Switchable x1 x10 (PAP £3) £12

Used Equipment - GUARANTEED. Manuals supplied if possible.

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (01734) 268041. Fax: (01734) 351696
Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)




CIRCLE NO. 133 ON REPLY CARD

SEETRAX CAE - RANGER - PCB DESIGN

Ranger1 £100

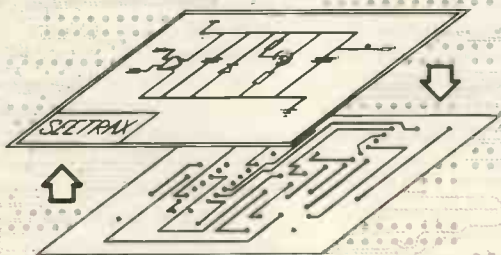- ★ Schematic capture linked to PCB
- ★ Parts and wiring list entry
- ★ Outline (footprint) library editor
- ★ Manual board layout
- ★ Full design rule checker
- ★ Back annotation (linked to schematic)
- ★ Power, memory and signal autorouter - £50



All systems upward compatible. Trade-in deals available.

Call **Seetrax CAE** for further information/demo packs.
Tel 01705 591037 Fax 01705 599036

Seetrax CAE, Hinton Daubnay House, Broadway Lane,
Lovedean, Hampshire, PO8 0SG

All trademarks acknowledged

Ranger2 £599

- ★ All the features of Ranger1 plus
- ★ Gate & pin swapping (linked to schematic)
- ★ Track highlighting
- ★ Auto track necking
- ★ Copper flood fill
- ★ Power planes (heat-relief & anti-pads)
- ★ Rip-up & retry autorouter

Ranger3 £3500

- ★ All the features of Ranger2 plus
- ★ UNIX or DOS versions
- ★ 1 Micron resolution and angles to 1/10th degree
- ★ Hierarchical or flat schematic
- ★ Unlimited design size
- ★ Any-shaped pad
- ★ Split power planes
- ★ Optional on-line DRC
- ★ 100% rip-up & retry, push & shove autorouter

Outputs to:

- ★ 8/9 and 24 pin dot-matrix printers
- ★ HP Desk/Laser Jet, Canon BJet, Postscript (R3 only)
- ★ HP-GL Houston Instruments plotters
- ★ Gerber photoplotters
- ★ NC Drill Excellon, Sieb & Meyer
- ★ AutoCAD DXF

CIRCLE NO. 134 ON REPLY CARD

Oscillating AT Uhf

Two basic circuit configurations are responsible for most oscillator designs working at frequencies up to the uhf range.

Ian Hickman describes the often conflicting requirements of uhf oscillators – including a disadvantage of the emitter-follower now put to good use.

Oscillators for frequencies to uhf and beyond have been built using all sorts of active devices, from valves onwards. Most of them use three terminal active devices, often connected to a simple tuned circuit in one of two basic ways, which were enumerated for my benefit as a student by an older colleague of many years experience with the aid of a sketch which I call *O'Connor's Universal Oscillator Circuit*, Fig. 1. It is drawn in an unconventional way to emphasise the following points.

For the circuit to function as an oscillator, Z_2 and Z_3 must be reactances of the same sign – both inductances or both capacitances – while Z_1 must be of the opposite sign. With this proviso, the diagram shows that, relative to the cathode (emitter, source), the voltages at the other two electrodes are in antiphase.

No earth connection is shown, since in principle the circuit could be provided with the necessary power supplies via ideal rf chokes of infinite reactance at the operating frequency, and a , g or k earthed as convenient, or the whole circuit left floating.

If Z_1 is an inductor with capacitors at Z_2 , Z_3 , the circuit is a Colpitts oscillator, whilst if a tapped inductor forms Z_2 and Z_3 with Z_1 being a capacitor then the circuit is a Hartley oscillator. One way or another, all three electrodes

of the active device must be connected to the tuned circuit.

Many other circuit arrangements are possible, some using more than one active device, a variety being shown in Fig. 2. However, at uhf a circuit using a single device, connected as in Fig. 1, often proves best because additional phase shifts associated with a second active device or parasitics associated with coupled windings introduce additional complexities into the design process, effects that would be smaller or negligible at vhf or hf.

Colpitts oscillator

As a basis of a signal generator, an oscillator with a wide tuning range is required. While at one time this would have been tuned by a precision mechanical variable capacitor, in a more modern application varactor tuning will usually be employed, permitting accurate frequency control by means of a phase-lock loop. With a possible application in view, I experimented with what might be regarded as a Colpitts oscillator, if you draw in the transistor's internal base/emitter capacitance to go with the 3.3pF external collector/emitter capacitance as Z_2 and Z_3 , Fig. 3(a).

In a wide-range oscillator, one needs to be able to vary its frequency over a wide range at will, but then instantly have its frequency as stable as a rock once one has set it to a particular desired frequency. To start with, it pays at the outset to design the oscillator circuit to have very stable dc conditions, ensured in Fig. 3(a) by the supply regulator, and by the base bias chain with its low source resistance at dc, which is moreover well decoupled at rf. As first constructed, the oscillator covered from under 400MHz to over 600MHz, but was modified as shown for the intended purpose to cover well over 200MHz centred on 400MHz.

This is shown in Fig. 3(b). The oscillator was tuned back and forth across its range during the six-second exposure required by the

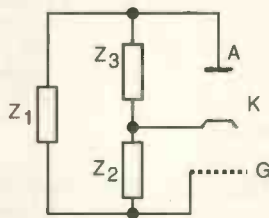


Fig. 1. O'Connor's universal oscillator circuit. Z_1 is a reactance of one sign while Z_2 and Z_3 are both of the other. For 'valve' read n-p-n bipolar, n-channel fet, hemt etc, as appropriate.

home-made oscilloscope camera, which does duty also for my spectrum analyser. There is a general slope in level of several decibels across the tuning range. But the superimposed ripples are due to the connection to the spectrum analyser. This effect was demonstrated by doubling the length of coaxial cable used for the connection, which gave twice as many ripples. Clearly, the analyser's input impedance isn't exactly 50Ω on the most sensitive range used; switching in 10dB at the input attenuator largely removed the ripples.

Base-current phase shift

It is a convenient fiction that, in common-cathode, emitter or source mode, an active device is an inverting amplifier, i.e. that the voltages at the other two electrodes are in antiphase. This is true in the case of valves up to fairly high frequencies, since the velocity of electrons *in vacuo* is a good deal faster than minority carriers in silicon. But in a transistor, phase shifts start to show up even in high-frequency devices at a much lower frequency, as is illustrated in Fig. 4.

Figure 4(a) shows the relation between the currents in the three electrodes of a transistor at dc, and recaps on the relation between the current gains α and β . The latter is often also called α' or h_{FE} . Figure 4(b) shows how even a small phase shift in the collector current can result in a phase shift in the base current which is much larger, and moreover in the opposite direction.

In the simplified treatment given here, any phase shifts suffered by the base or collector currents after they part company, due to 'transmission line delay' in different regions of the bulk of the semiconductor, are assumed to be negligible.

The higher the dc value of β , i.e. the more nearly the magnitude of the collector current equals that of the emitter, the smaller the phase shift in the collector current needed to give a 45° advance to the base current. For an audio-frequency transistor such as the BC109 with its typical β of 300 and f_T of 300MHz, this occurs at around 1MHz. At higher frequencies, the base current can lead the emitter current by not far off 90°.

An emitter follower is an extremely useful and widely used circuit, acting as a buffer and permitting a high-impedance source to drive a lower-impedance load. But the circuit has an unfortunate tendency to oscillate, particularly if the load is a bit capacitive. The phase advance suffered by the base current is the culprit.


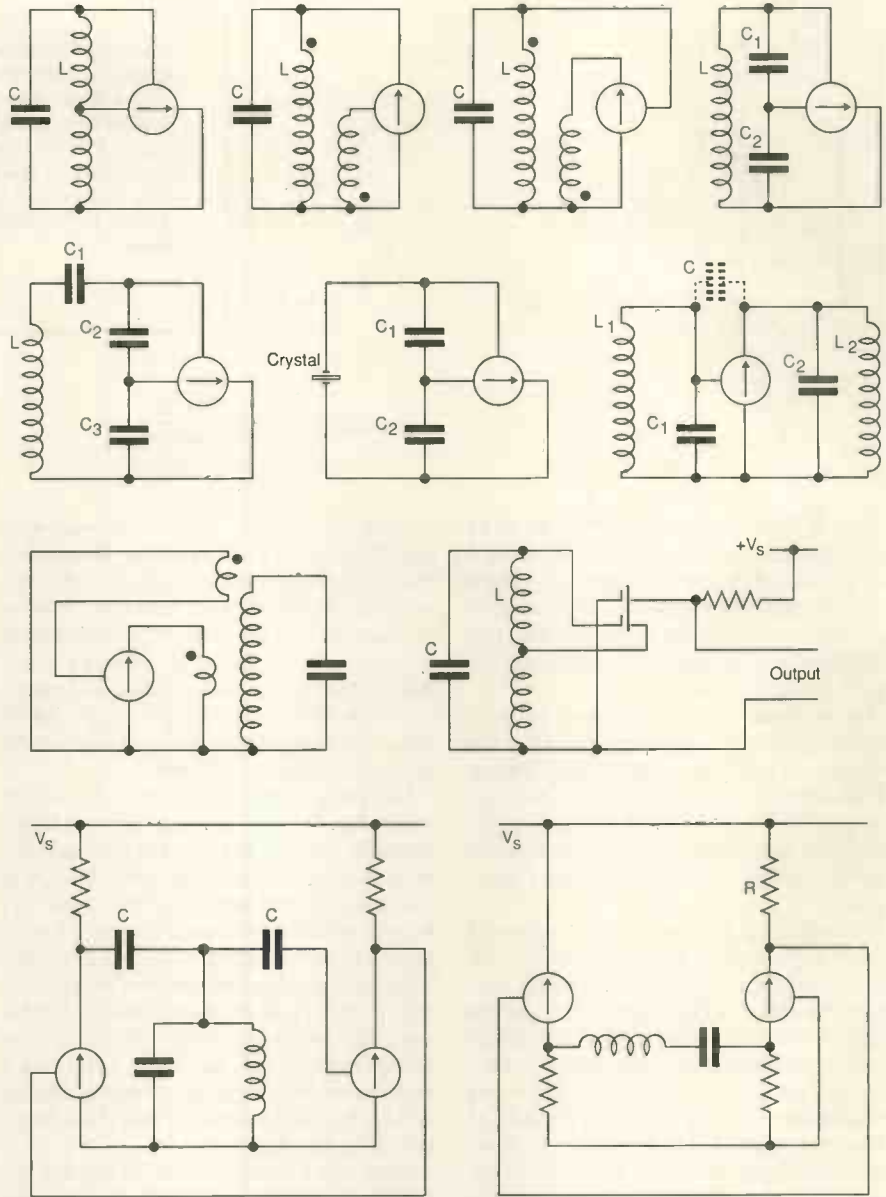


Fig. 2. A variety of oscillator circuits, some more suited to lower frequencies, reproduced from Newnes Practical RF Handbook published by Butterworth Heinemann.

Fig. 3. Wide-range, uhf, varicap-tuned oscillator circuit at (a) offers the tuning range shown at (b), covering from below 300MHz to over 500MHz. Span 0-1000MHz, 10dB/div vertical.

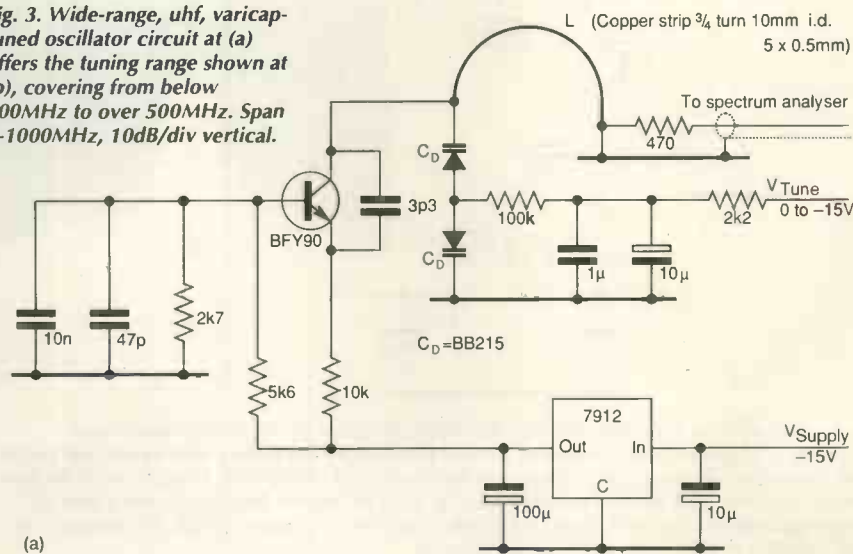

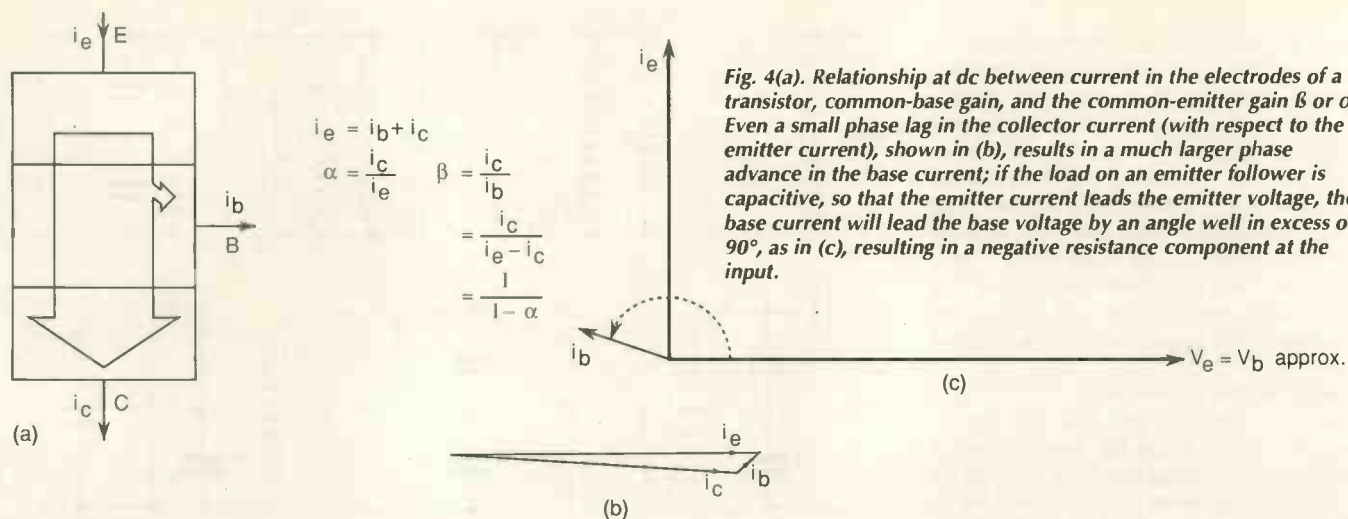


Fig. 4(a). Relationship at dc between current in the electrodes of a transistor, common-base gain, and the common-emitter gain β or α . Even a small phase lag in the collector current (with respect to the emitter current), shown in (b), results in a much larger phase advance in the base current; if the load on an emitter follower is capacitive, so that the emitter current leads the emitter voltage, the base current will lead the base voltage by an angle well in excess of 90° , as in (c), resulting in a negative resistance component at the input.

This is illustrated in Fig. 4(c). Here an important assumption is made: the mutual conductance of the device is high (its output impedance low compared to the impedance of the load connected to the emitter) so that, to a first approximation, the voltage at the emitter equals that at the base.

As the emitter current is leading the base voltage by up to 90° , with a purely capacitive load, and the base current substantially leading the emitter current, it follows that the base current leads the base voltage by well over 90° . The input impedance consists of a negative resistive component in parallel with a capacitive.

This effect has been used as the basis of a microwave oscillator design producing over 100mW output at 2GHz¹. It can equally well be used at uhf, and Fig. 5 shows just such an application. The reactance of 18pF at 345MHz is 25 Ω , doubtless effectively reduced somewhat by the inductance of the leads even though these were kept as short as possible, so the emitter circuit load is almost purely capacitive. The capacitance tuning the inductor consisted only of the capacitive component of device input impedance, and device and circuit strays.

If the circuit of Fig. 5(a) is compared with that of Fig. 3, it will be seen to be almost identical. In both cases, the collector is connected to the opposite end of the tuned circuit from the base, while a capacitor is connected from the emitter to the collector end of the tuned circuit. Thus in fact most oscillators operating at vhf or above and using a single active device are likely to be found on analysis to be negative resistance oscillators.

Depending on the Q of the tuned circuit (and that in Fig. 5(a) was certainly not very high), the noise performance or short term stability of such an oscillator can be good, though of course the medium and long term stability will be poor unless the oscillator is used as a voltage-controlled oscillator in a phase-lock loop.

Figure 5(b) shows the output of the Fig. 5(a) circuit, the centre frequency being 345MHz and the horizontal scale 5kHz/division. Analyser bandwidth was set to 1kHz and a great many sweeps occurred during the six second exposure needed to record the background and graticule.

Some noise modulation is evident but the overall shape is not so very different from that of the analyser's 1kHz filter. However, towards the end of the exposure the oscillator

took it into its head to start wandering up in frequency; a stability of 1kHz in an open-loop uhf oscillator could be achieved, but only with a more sophisticated circuit, using a high- Q cavity resonator for example.

Line stabilisation

Another arrangement providing improved frequency stability without resorting to a phase-locked loop is the line-stabilised oscillator. Using a line consisting of 150cm of 50 Ω miniature coaxial cable, believed to have a velocity ratio of around 0.66, with its far end shorted, the Fig. 5(a) was modified to work in this mode. A tuning capacitor was added to enable the tank circuit to be tuned to a frequency at which the emitter load looked capacitive. It oscillated at 235MHz, at which frequency the length of the line would be just over one and three quarter wavelengths, i.e. capacitive.

Clearly there are other frequencies, both higher and lower, at which the line looked capacitive, for example where the line length is $5/4\lambda$, $9/4\lambda$, $11/4\lambda$ etc, and the tuned circuit is used to pick out one of these as the operating frequency. If the tank circuit Q is high and the regeneration only just sufficient to ensure oscillation, then only one of these modes can be sustained. If the tank Q is lower and the negative resistance much lower than necessary to sustain oscillation, the circuit can oscillate in several modes at once.

This was the case when the collector supply was the same as in Fig. 5(a). Reducing collector voltage until it equalled the base voltage, as shown in Fig. 6(a), prevented oscillation in several modes simultaneously. With a constant tail current generator or rf choke/resistor combination in place of the 10k Ω resistor to -12V, the oscillator circuit would work happily on a supply of a volt or two.

Output from the loosely coupled winding was as in Fig. 6(b), where the span is 0-1000MHz and the fundamental at 235MHz is visible, together with the second, third and fourth harmonics. Figure 6(c) zooms in on the fundamental, at 5kHz per division horizontal. At the selected video filter bandwidth, a single sweep took six seconds and at 60dB down, the

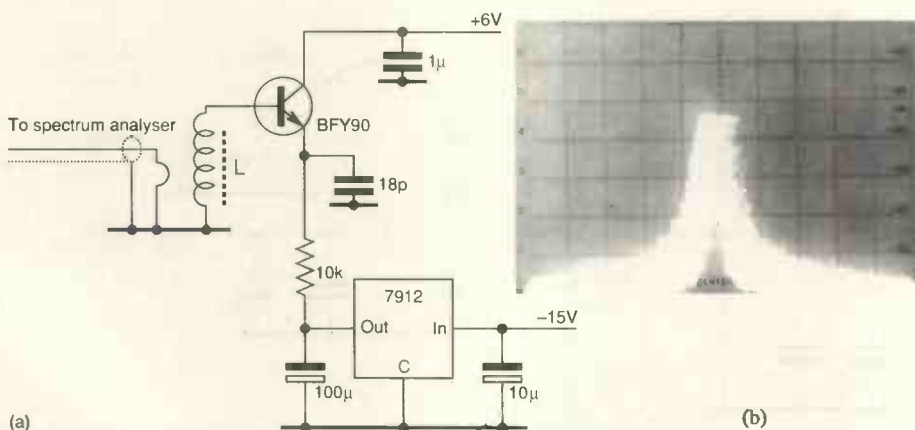


Fig. 5. Uhf oscillator at (a) uses the negative input resistance effect, tuning capacitance consisting of the capacitive component of base circuit input impedance plus device and circuit strays. Inductor L is three turns (spaced one wire width) of 16swg tinned-copper wire, on 5mm internal diameter with a 3.75mm ferrite slug. At (b) is the output from the loosely coupled, single-turn winding, centre frequency 345MHz, 5kHz/div. horizontal, 10dB/div. vertical, ref. level -10dBm, 1F bandwidth 1kHz, video filter off.

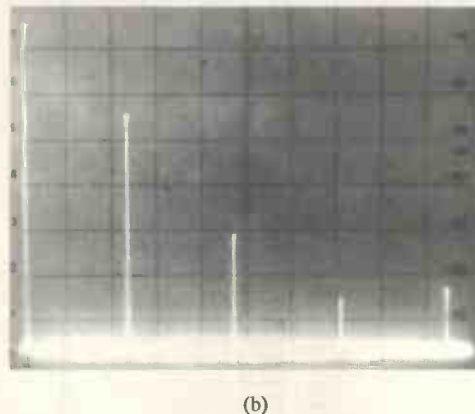
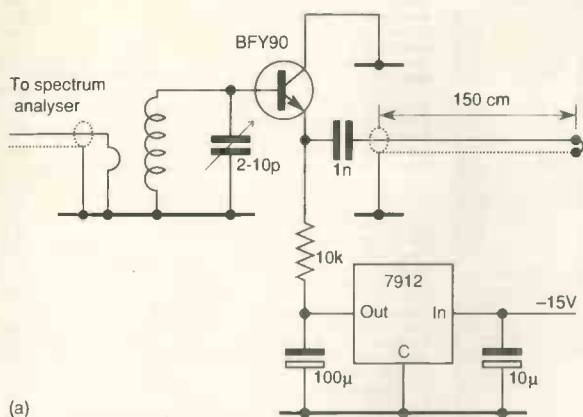


Fig. 6. Simple and fairly crude line-stabilised oscillator (a) gives output at (b); span 0-1000MHz, 10dB/div vertical, ref. level (top of screen) -10dBm. Fundamental component of (b) shown in (c), with centre frequency 235MHz and horizontal scale 5kHz/div, IF bandwidth 1kHz, video filter at max. (giving a post-detector bandwidth of 1.5Hz), 10dB/div. vertical, ref. level -30dBm.

response is 15kHz wide, which is more or less identical to the analyser's 1kHz filter specification.


Of course, a length of coaxial cable does not make for a very convenient line stabilised oscillator. Even if semi-rigid, solid-outer coaxial were used, the stability of the oscillator with temperature would not be wonderful. But line stabilisation is now very attractive and competitive, in the form of surface acoustic wave resonators.

Owing to the extremely slow propagation speed of acoustic waves in lithium niobate – slow at least compared with the speed of light – a compact package can contain a line length of many wavelengths. Such devices are used at uhf in lieu of crystals, where tight frequency control is required. An example is the range

of 418MHz telemetry modules featured in Ref. 2.

Connecting a negative resistance across a tuned circuit results in an oscillator, and the negative resistance need not imply a three terminal device. Many years ago a two terminal device – the tunnel diode – was a popular means of making uhf oscillators. This was at a time when transistors with adequate performance were not available, or at best very expensive.

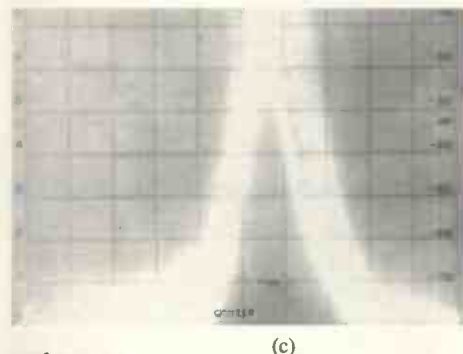Now that transistors with more than adequate performance are common and cheap, the tunnel diode uhf oscillator has taken a back seat. But negative resistance two terminal oscillator circuits are still used at microwave frequencies, in the form of the Gunn diode oscillator.



References
1. Partha and Krishnakumar. Oscillator design employs common-collector bipolars. *Microwaves and RF*, October, 1994 pp. 88-92.
2. Hickman I. Low power radio links, *EW+WW*, February 1993, pp. 140-144.

ADD VALUE AND CREDIBILITY WITH REPRINTS

Multiple copies of your articles and advertisements published in this magazine make ideal promotional material for sales literature, exhibition handouts, direct mail, new product launches, distributor promotions, Public Relations etc.

You can add your own artwork and copy, utilise the front cover of this magazine, include your list of distributors, and/or your latest advertisement/s. Reasonably priced reprints can be tailor-made to your own specific requirements or simply reprinted in their original form. (Minimum order number 250)

For a FREE quotation please telephone Jan Crowther now on: 0181-652 8229 or fax: 0181-652 3978

Reprint Services, Reed Business Publishing,
Room 1006, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, England



OSCILLOSCOPES	
Gould OS4000, OS4200, OS4100, OS1000B	from £125
Gould OS3000 - 40MHz dual ch	£250
Gould 4035 - 20MHz digital storage	£600
Gould 4050 - 35MHz digital storage	£750
Gould 5110 - 100MHz intelligent oscilloscope	£950
Hewlett Packard 1707A, 1707B - 75MHz dual ch	from £275

Gould OS4000, OS4200, OS4100, OS1000B	from £1250
Gould OS3000 - 40MHz dual ch.	£250
Gould 4035 - 20MHz digital storage	£600
Gould 4050 - 35MHz digital storage	£750
Gould 5110 - 10MHz Intelligent oscilloscope	£350
Hewlett Packard 174A, 1707B - 75MHz	from £350
Hewlett Packard 1740, 1741, 1744A - 100MHz dual ch	£1750
Hewlett Packard 54201A - 300MHz digitizing	£1750
Hewlett Packard 5450A - 400MHz digitizing (As new)	£3500
Hitachi V-212 - 20MHz dual trace	£175
Hitachi V-422 - 40MHz dual ch.	£300
Nicolet 3091 - Low freq D.S.O.	£1100
Philips 3315 - 60MHz D.S.O.	£750
Tektronix 468 - 100MHz dual ch.	£800
Tektronix 2213 - 60MHz dual ch.	£425
Tektronix 2215 - 60MHz dual ch.	£400
Tektronix 2220 - 60MHz digital storage	£995
Tektronix 2225 - 50MHz dual trace	£450
Tektronix 2235 - 100MHz dual ch. (portable)	£800
Tektronix 2335 - 100MHz dual ch. (portable)	£750
Tektronix 2465A - 300MHz 4 ch.	£2950
Tektronix 464A - 100MHz digital storage	from £350
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 713, 7603, 7613, 7623, 7633, 100MHz 4 ch.	from £300
Tektronix 7704 - 250MHz 4 ch.	from £650
Tektronix 7834 with 7842, 78B0, 78B5 - Plug-ins (Storage 400MHz)	£1500
Tektronix 7904 - 50MHz	from £850
Telequipment D68 - 50MHz dual ch.	£200
Philips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2 ch.)	from £125 to £350
Philips PM3295A - 400MHz dual channel	£1950
Philips PM3296 - 350MHz dual channel	£1800

Hewlett Packard 358A - 5Hz - 50KHz	£395
Hewlett Packard 3582A - 25KHz analyser, dual channel	£2500
Hewlett Packard 1827 with 8559A (10MHz - 21GHz)	£3750
Marconi 2370 - 110MHz	£395
Marconi 2371 - 30Hz-200MHz	£1250
Rohde & Schwarz - SWOB5 Polyskop 0.1 - 1300MHz	£2750
Schlumberger 1250 - Frequency response analyser	£2500
Alltech 727 - 22.4GHz	
Alltech 7077 - Tracking Generator for 727 (10KHz- 12.4GHz)	£2000
Tecscan AL51A - GHz	£995
Tektronik 7L14 with 7603 - Mainframe (1.8GHz)	£1500
Tektronik 7L12 with 7603 mainframe (1.8GHz)	£1500
Tektronik 7L18 with 7603 mainframe (18GHz)	2950
Polrad 641-1 10MHz - 18GHz	£1500
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000

Anritsu MG642A Pulse pattern generator.....	£1500
Ballantine 323 True RMS voltmeter.....	£350

Datatab DL 1080 – Programmable Transient Recorder	£350
Dynaport TP220 – Intellipace tape peel tester, immaculate condition	£195
Data I/O MODEL 29B (with 12 fixtures) + logic pack	£995
E.I.P. 331 18kHz frequency counter	£850
Farnell 2081 R/F Power meter	£385
Farnell TS770 MkII – Power supply (70V–5A or 35V–10A)	£220
Ferrogirth RS72 Audio test set with ATU1	£250
Fuke 5101A – Calibrator AC/DC	£1,500
Fuke 5101B – Calibrator AC/DC	£650
Fuke 5220A – Transconductance Amplifier (20A)	£3,000
Fuke 720A – Kelvin – Varley Voltage Divider	£450
Fuke 750A – Reference Divider	£450
Heiden 1107 – 30V–10A Programmable power supply (IEEE)	£650
Gould K100D – 100MHz Logic Analyser with PODS	£635
Hewlett Packard 436A Power meter + 8481A sensor	£1,500
Hewlett Packard 3325A – 21MHz synthesiser/functiogen	£1,500
Hewlett Packard 3400A DC system voltmeter	£1,500
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3490A Digital multimeter	£295
Hewlett Packard 3586A – Selective level meter	£1,750
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	

Hewlett Packard 3711A/3712A/3791B/3793B Microwave link analyzer		\$3500
Hewlett Packard 3760/3761 Data gen + error detector	each	\$300
Hewlett Packard 3762/3763 Data gen + error detector	each	\$350
Hewlett Packard 3764A Opt.002 - Digital Trans. Analyzer		\$250
Hewlett Packard 3777A Channel selector		\$250
Hewlett Packard 3775A - 379C Primary mult. analyzer		\$600
Hewlett Packard 3776A Primary mult. analyzer		\$500
Hewlett Packard 5316A - Universal counter HP1B		\$1000
Hewlett Packard 5316B - Universal counter HP1B		\$750
Hewlett Packard 5385A - Frequency counter 1 GHz (HP1B) with Opts		\$1500
001/003/004/005		\$995
Hewlett Packard 59501B HP1B interface O/A power supply programmer		\$1000

Hewlett Packard 6261B Power supply 20V-50A	£500
<i>DISCOUNT FOR QUANTITIES</i>	

Hewlett Packard 6453A – Power supply 15V–200A.....	£1250
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins.....	£300
Hewlett Packard 8005B Pulse generator.....	£500
Hewlett Packard 8011A Pulse gen. 0.1Hz – 20MHz.....	£250
Hewlett Packard 8152A – optical average power meter.....	£1250
Hewlett Packard 8155B – optical attenuator with opt's 002 + 001.....	£1700
Hewlett Packard 8443A Tracking gen./counter with IEEE.....	£300 / £400
Hewlett Packard 8620C Sweep oscillator mainframe.....	£300
Hewlett Packard 8750A Storage normaliser.....	£475
Hewlett Packard 8657B – Synthesised Sig. Gen. (2600MHz).....	£725
Hewlett Packard 3456A Digital voltmeter.....	£750
Hewlett Packard 3456A Digital voltmeter control unit.....	£750
Hewlett Packard 6864A – 5–4GHz to 12.5GHz Sig. Gen.....	£1300
Hewlett Packard 3785A – I-ter Generator + Receiver.....	£300
Hewlett Packard 6632A – System Power Supply (HPiB).....	£850
Hewlett Packard 8640B – AM/FM Signal Gen. (512MHz).....	£500
Hewlett Packard 8640B – AM/FM Frequency Counter.....	£500
Hewlett Packard 3356A – 19GHz Frequency Converter Head.....	£4500
Hewlett Packard 432A – Power meter (with 478A Sensor).....	£275
Hewlett Packard 4343A or B – Att. meter (with 8481A/8484A).....	£750
International Light – IL 1700 series radiometer with Erythral sensor and lead.....	
head LCR745G – LCR Meter.....	£1150

Marconi PG73N/P/55/PGBZ/P/G Pulse generator	from £225
Marconi 2019 - AM/FM sig. gen. 1040MHz	£1800
Marconi 2306 Programmable Interface	£400
Marconi 2337A Automatic dist. meter	£150
Marconi 2356 20MHz level oscillator	£300
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2830 Multiplex tester	£1000
Marconi 2831 Channel access switch	£400
Marconi 893B A/F power meter	£325
Multicore "Vapourtec" bench top vapour phase SMD soldering machine (new and unused) (£1100 + new)	£650
Philips PM 5170 100MHz function generator	£400
Philips PM 5190 FLF synthesizer with GPIB	£1200
Philips 5390 1GHz signal gen.	£1250
Philips PM 5716 Pulse generator high freq. mos.	£600
Phoenix 5500A - telecommms analyser with various interface options	£3750
Racal 9301A True RMS R/F millivoltmeter	£300
Racal Dana 1992 - 1300MHz frequency counter opts 4B + 55	£800
Racal Dana 3100 40 - 130MHz synthesiser	£750
Racal Dana 5002 Wideband level meter	£650
Racal Dana 5003 Digital level meter	£150
Racal Dana 9000 Microprocessing timer/count. 52MHz	£250
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 9301A/9302 R/F Millivolt meter	from £300
Racal Dana 9303 True RMS/R/F level meter	£650
Racal Dana 9341 LCR databridge	£250
Racal Dana 9800 Universal timer/counter 100MHz	£200
Racal Dana 9921 3GHz frequency counter	£450
Rohde & Schwarz BN36711 Digital Q meter	£400
Rohde & Schwarz LFMD Sweep generator 0.02 - 60MHz	£1500
Rohde & Schwarz SCF2 Radio code test set.	£1500
Rotek 3980 A - AC/DC Precision Calibrator with Rotek 350A High Current Adaptor	£POA
Schlumberger SI 4040 - Stablock, high accuracy 1GHz radio test set	£7000
Schlumberger 4923 - Radio Code Test Set	£1750
Schlumberger 7728 - 1250MHz Freq. Counter	£600
System Vitec 1258 Waveform analyser + 1255 vector monitor + 140 differential phase & gain module + 1270 remote control panel	£2250
Syston Donner 6054R or D - 18GHz or 24GHz Freq. Counter	from £800
Tektronix DA59100 Series Logic Analyser	£500
Tektronix 577 Curve Tracer with Fixtures	£800
Tektronix - Plug-ins - Many available such as PG508, FG504, SC504, SW503, SG 502 etc.	£300
Time 9811 Programmable resistance	£300
Time 9814 Voltage calibrator	£750
Watanabe WTP211 3 pen plotter	£250
Weller D90 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350
Wiltron 560 SCA Network analyser	£800

**MANY MORE ITEMS AVAILABLE - SEND
LARGE S.A.E. FOR LIST OF EQUIPMENT ALL
EQUIPMENT IS USED - WITH 30 DAYS
GUARANTEE. PLEASE CHECK FOR AVAILABILITY
BEFORE ORDERING - CARRIAGE
& VAT TO BE ADDED TO ALL GOODS**

CIRCLE NO. 136 ON REPLY CARD

The modifications include four additional circuit boards providing

- *Rechargeable memory and clock back-up
- *Balanced Audio line output
- *Reduced AM distortion
- *Buffered IF output for monitoring transmitted modulation envelope on an oscilloscope
- *Mains safety improvements.

*Advanced Active Aerial 4kHz-30MHz *PPM10 in-vision PPM and chart recorder *Twin Twin PPM Rack and Box Units
*Stabilizers and Fixed Shift Circuit Boards for howl reduction
*10 Outlet Distribution Amplifier 4 *Stereo Variable Emphasis Limiter 3 *Stereo Disc Amplifiers *Peak Deviation Meter
*PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements *Broadcast Stereo Coders.

**The Forge, Lucks Green, Cranleigh
Surrey GU6 7BG
Telephone: 01483 275997 Fax: 276477**

High quality stepper motors, kits all including stepping motors) Computers: input/output of 2 stepping motors by PC (Via the parallel port) with 2 motors and software Kit £67.00	SL952 U1F Limiting amplifier LG 16 surface mounting package with data sheet £5.00
Ready built £99.00	CM27503 £1.25 each (90p 100+) x 100 (100+ (6p 100+))
Software support and 4 digital inputs kit £27.00	AD4007UB 100 (100+ (6p 100+))
	Sinclair light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50Hz

Power interface BA kit \$46.00
Stepper kit #4 (manual control) includes 200 step stepping motor and control circuit..... \$23.00

We are now stocking a range of stepping motors and kits to drive them, please ask for the stepping motor data sheet for full information.

Inverter toroidal transformers 225VA 10.5-0-10.5 primary @ 260-280V secondary..... £29.95

LEDs 3mm or 5mm red or green7p each
Yellow11p each

Cable ties, 1p each, £5.95 per 1000. £49.50 per 10,000.
High quality photo resist copper clad epoxy glass boards

Dimensions	single sided	double sided
3x1 inches	\$1.09	\$1.23
4x4 inches	\$2.70	\$2.99
6x12 inches	\$6.20	
12x12 inches	\$12.25	

Rechargeable Batteries

AA (1P)	300mAh	with solder
\$0.99		\$1.35
AA 700mAh	£1.75	(CH1P1) 1.8Ah
C 2AH 1 with solder tags	£3.60	DH2P1 2.1Ah
D 1AH with solder tags	£1.95	PPS 6 AV 10mAh
1/2AA with solder tags	£2.50	Sub C with solder tags
AA (HP16) 180mAh	£1.55	I/2 AA with tags (Philips GTV).....

Standard charge rates 4 x AA cells in 5 hours or 1C
or Cs in 12-14 hours + XSPPS (1, 2, 3 or 4 cells may be charged at a time) £5.95

High power charger as above but charges the Cs and Ds in 5 hours. AAs, Cs and Ds must be charged in 2's or 3's £5.95

Nickel Metal Hydride AA cells high capacity with no memory. 1000mAh £3.50

1200mAh AA £3.75

Special prices check for availability.

Stick of 4 x32G16m Nicad batteries 171x16mm dia with red & black leads 4.8v £5.95

Computer grade capacitors with screw terminals

5700uf 60v	£1.95
115V AC 470uf 250v 50mm dia	£1.95

cold thermal body (excluding the shaft) it has a replaceable forming face and brushes

segment common metal lead display 12mm	40.45
L1M357K TOS case variable resistor	£1.95

GaAs FET low leakage current S8873 £12.95 ex VAT
(£9.95 10+. £7.95 100+)

BS290 P channel mosfet £0.45
BC550N NPN transistor £2.95 ex VAT
74LS09 hex inverter £10.00 per lot

Use 8718 Microcontroller £3.50

DC-DC converter Reliability model V12P3 12v in vs 200ma out 300V input to output isolation with over temp protection 100% duty cycle 100000 hrs MTBF Hour counter used 7 digit 210V AT501U £1.15

QUERY! Keyboard 58 key good quality switches new £6.10

Aimaps AS290X3 Large steel strong unit 11v 1.7 3 slot 2200168mm dia hole 6.3mm shell £8.95

@ £20.00 for a box of 30

Polyester capacitors box type 22.5um lead pitch 0.95mm 100V 100pF 100k+ 20p each
EUF 25kVdc 20p each
13p...100+ 10p...1000+

3.3uf 100Vdc 50p each 20p...100+ 15p...1000+

EUF 50v bipolar electrolytic axial leads 7.5p 1000+

0.22uf 250v polyester axial leads 15p each

Polypropylene 1uf 100Vdc (Wima MKP type) 27mm pitch 32x25x17mm case 7.5p each

Philips 125 series solid aluminium axial leads - 35uf 100V 22uf 60V 25p 100+

Philips 108 series long life 22uf 65V 30p each

Multilayer AVX ceramic capacitors all 15p 1000+ 100K 100Vf, 150pf, 220pf, 10.000pf(10n) 15p each

400pf compression trimmer 60p

40p of 700v 1000uf capacitor (dielectric type containing no pcbs) £3.95 or £19.50 for 10

Solid carbon resistors very low inductance ideal for RF circuits - 27ohm 2W, 68ohm 2W 25p each

We have a range of 0.25w 0.3w 1w and 2w solid carbon resistors, please send SA for list

P.C. 400V PSU (Intel part 201035-001) with standard 4 pin ATX connector, 2 pin disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for tower case dim) 212x149x149mm excluding switch £26.00 each

X-M180 Digital multimeter 17 ranges 1000Vdc 750vac 2Mohm 200mA transisor 1Hfe 9v and 1.5v battery test £12.95

ATX 255 5 pin connector 2.00 each £1.95

DIP switch 3PCD 12 pin (ERG SDC-3-023) 60p each

40p...100+

Disk drive boxes for 3.5in disk with room for a power supply, light grey plastic, 67x268x147mm 100000 hrs MTBF 75c or £430.50 for 10

Hand held ultrasonic remote control £3.95

CVC2486 gate relay, 30x10mm dia with 3 wire terminals, will also work as a neon light 20p each

£7.50 per lot


All products advertised are new and unused unless otherwise stated.
Wide range of CMOS TTL 74HC 74F Linear Transistors kits. Rechargeable batteries, capacitors, tools etc
always in stock. Please add £1.95 towards p&p. VAT included in all prices.

JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH
Access/Visa **(01246) 211202 Fax: 550959** Callers welcome

CIRCLE NO. 138 ON REPLY CARD

Reference books to buy

For Audio Engineers

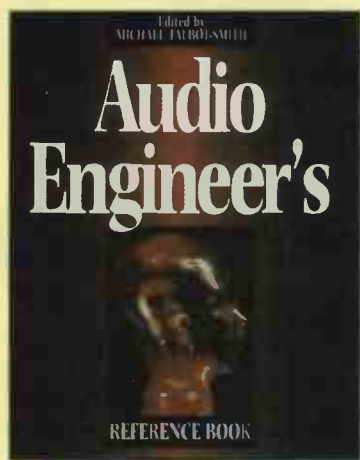


Subjects include

Recording, microphones
and loudspeakers
Digital audio techniques
Basic audio principles
Acoustics and
psychoacoustics
Audio and television
studios and their facilities
Radio and telephony

- Comprehensive – over 600 pages
- Written by leading authorities from the audio world
- Easy to read, compiled for maximum accessibility
- Concise and authoritative
- Covers topics from noise measurement to studio installation

Invaluable reference work for anyone involved with audio – from broadcast consultant to serious enthusiast. *Audio Engineer's Reference Book* is written by an international team of experts and edited by Michael Talbot-Smith – previously a trainer of audio engineers at BBC Wood Norton and now a freelance audio consultant and technical writer.

For TV & Video Engineers

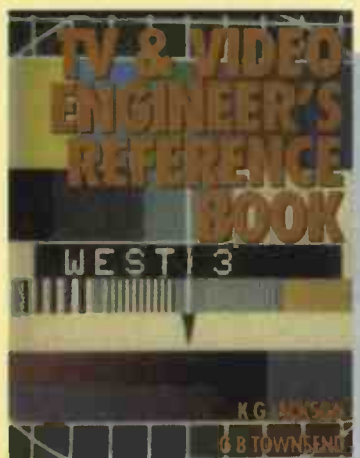

Subjects include

Fundamentals of colour TV
TV studios
High definition TV
Satellite broadcasting
Distribution of broadband signals
TV receiver servicing
Video and audio recording and playback
Teletext

- Over sixty chapters on the latest techniques in video and television
- Up to date reference on EMC requirements, DBS and HDTV
- Easy-to-use reference, eminently suitable for students
- Topics range from materials and construction to medical and defence applications of television.

The *TV & Video Engineer's Reference Book* will be of immense value to anyone involved with modern tv & video techniques – in particular broadcast engineers. The new format makes it an excellent reference for students. Edited by KG Jackson and GB Townsend from contributions written by acknowledged international experts.

Please supply me _____ copies of the
Audio Engineer's Reference Book,

(ISBN 0 7506 0386 0)

Fully-inclusive price – UK £62.50, Europe £68, Worldwide £78. Please add vat at local rate where applicable.

Please supply me _____ copies of the
TV & Video Engineer's Reference Book,

(ISBN 0 7506 1953 8)

Fully-inclusive price – UK £42.50, Europe £48.00, Worldwide £58.00, Please add vat at local rate where applicable.

Remittance enclosed £ _____

Cheques should be made payable to Reed Business Publishing Group Ltd

Please return to: Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please debit my credit card as follows:

Access/Master Barclay/Visa Amex Diners

Credit Card No. _____

Exp date _____

NAME (Please print) _____

ADDRESS _____

POST CODE _____

DATE _____ TEL _____

SIGNATURE _____

VAT RATES

6% Belgium, 25% Denmark, 5.5% France, 7% Germany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain.
FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)

VAT NO. _____

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change.

Please delete as appropriate. I do/do not wish to receive further details about books, journals and information services.

Business purchase: Please send me the book listed with an invoice. I will arrange for my company to pay the accompanying invoice within 30 days. I will attach my business card/letterhead and have signed the form below. Guarantee: If you are not completely satisfied, books may be returned within 30 days in a resalable condition for a full refund.

Credit card orders accepted by 'phone. Call 0181 652 3614

Do you have an original circuit idea for publication? We are giving £100 cash for the month's top design. Additional authors will receive £25 cash for each circuit idea published. We are looking for ingenuity in the use of modern components.

All-in-one mains monitor

All the components of this monitor will work separately or form a complete indicator of the health of a mains supply, showing the presence of spikes, over/under voltage or voltage fluctuations and containing a mains noise filter.

Filter. Removes the 50Hz waveform to reveal the presence of noise and harmonics, heard on a speaker, and spikes indicated by a bicolour led, which shows by its predominant colour whether the spikes are positive or negative. Adjust the 22k Ω pot. in the filter for least light from the led.

Spike detector. Spikes on the rectified filter output trigger the SCR and sound the buzzer for just under 1s, until current is established through the SCR. Triggering occurs when household appliances switch on and off and the 2.2k Ω pot. should be adjusted so that the circuit does not trigger when the monitor is switched on. Do not use a sensitive SCR.

Over/under voltage. Normally, the led flashes at around 6Hz, this frequency doubling for a +10% mains voltage change and stopping for a -10% variation. Choose


the correct zener for the relevant mains voltage.

Mains fluctuations. Significant variations in mains voltage modulate the red led heavily, from full on to off, independently of average mains voltage.

Bear in mind that the circuit is connected to the mains and that the large capacitors will probably stay charged for some time.

D Di Mario
Milan
Italy

100 WINNER

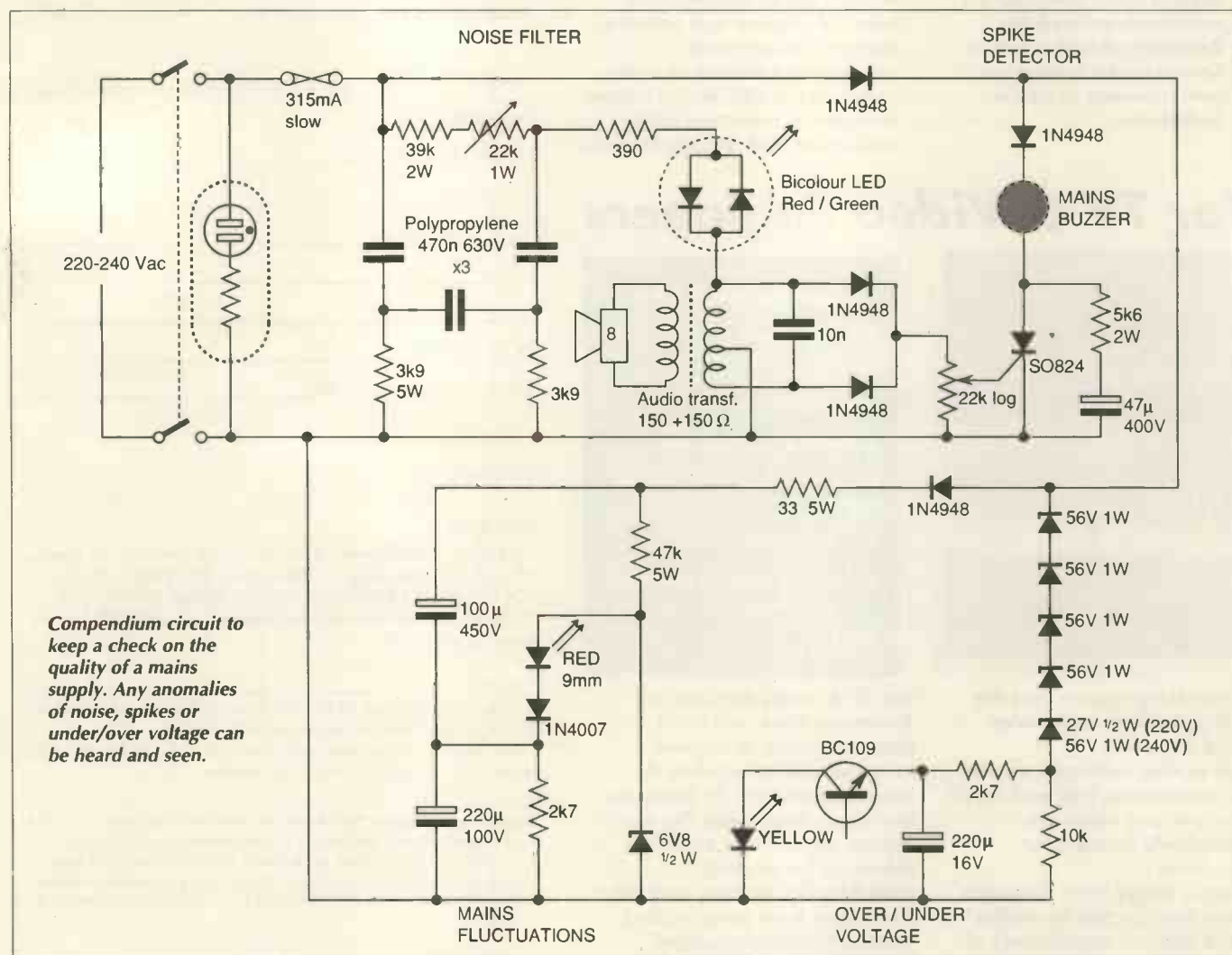

YOU COULD BE USING A 1GHz SPECTRUM ANALYSER ADAPTOR!

Got a good idea? Then this Thurlby-Thandar Instruments TSA1000 spectrum analyser adaptor could be yours.

Covering the frequency range 400kHz to over 1GHz with a logarithmic display range of 70dB \pm 1.5dB, it turns a basic oscilloscope into a precision spectrum analyser with digital readout calibration.

Recognising the importance of good design, TTI will be giving away one of these excellent instruments every six months to the best circuit idea published in the preceding period until further notice. This incentive will be in addition to our £100 monthly star author's fee, together with £25 for all other ideas published.

Our judging criteria are ingenuity and originality in the use of modern components – with simplicity particularly valued.



Thermally stable current source

This thermally stable current source features very high dynamic impedance, high output voltage swing and wide bandwidth.

In the connection shown, the op-amps maintain the same voltage drop across R_{ref} as across the reference diode, so that the output current is precisely determined. Op-amp OP_2 sinks bias current, which has therefore almost no effect on I_{ref} .

Highest instantaneous output voltage is given by the highest value of R_{bias} consistent with there being enough bias current to operate the diode, while the lowest R_{bias} value is determined by the maximum power from OP_2 . Output current


and reference voltage determine the value of R_{ref} .

With values given, a 24V supply and 1mA output, a 2.2k Ω R_{bias} gives 50mW of power in OP_2 ; R_{ref} gives the 1mA output when used with a Plessey ZN458B reference diode and the minimum diode current gives a 17V output swing.

Since both op-amps act as buffers, it is unnecessary to use high-performance types, although improvements would be seen. As it is, the circuit works well over the audio range with any op-amp and diode.

Andrea Scozzari

Livorno
Italy

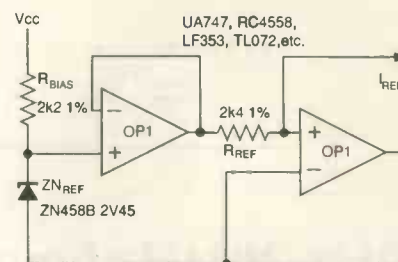

Current source provides very high thermal stability. Output current is determined by value of R_{ref} and diode voltage.


Positive start for 555 oscillator

Using a 555 as an astable oscillator in a digital delay circuit entails holding the reset pin low until the oscillator is required to start. Normally, this causes the timing capacitor to discharge completely via the timing resistor, so that the first charge is longer than succeeding ones at $1.1(R_a + R_b)C$ instead of $0.69(R_a + R_b)C$.

To avoid the effect, the capacitor must be held at $V_{cc}/3$ when the oscillator is stopped, by means of the p-n-p transistor controlled by the run/stop signal, R_c being $2R_b$.

Mike Aldington
Gillingham
Kent

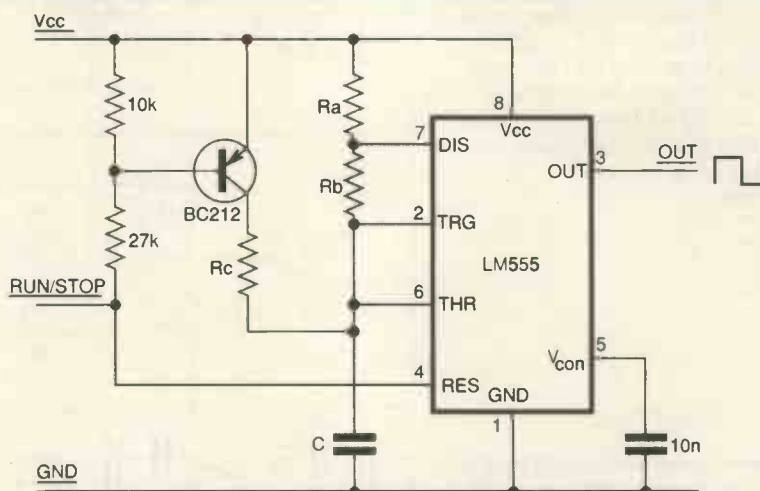Circuit prevents total discharge of timing capacitor in 555 astable oscillator when oscillator stops, ensuring time of first mark period same as subsequent cycles.



Prescaler functions to 1.3GHz

Using two ICs, a 74LS90 and a TFK U665B two-modulus (960/1024) divider, the circuit divides frequencies up to 1.3GHz by 1000.

A logic level on the 665B's mod input, pin 6, determines which modulus is used – logic zero gives 1024 and one, 960. Pulses from the QA output of the 74LS90


decade divider form the sequence 00000111 to give 5 at 1024 and 3 at 960 ($5 \times 1024 + 3 \times 960 = 8000$ input pulses for eight output pulses, or $8000/8 = 1000$).

Bi-quinary connection of the 74LS90 allows forced resetting to 9, when its natural output is 7, by the connection of its reset-9 inputs to QA and QB. One's

first thought, that a shift register might perform the function, is not valid, since glitches and noise have a tendency to cause errors.

For connection to a long output lead, use the prescaled output on pin 7.

Stefano Pigozzo
Belluno
Italy

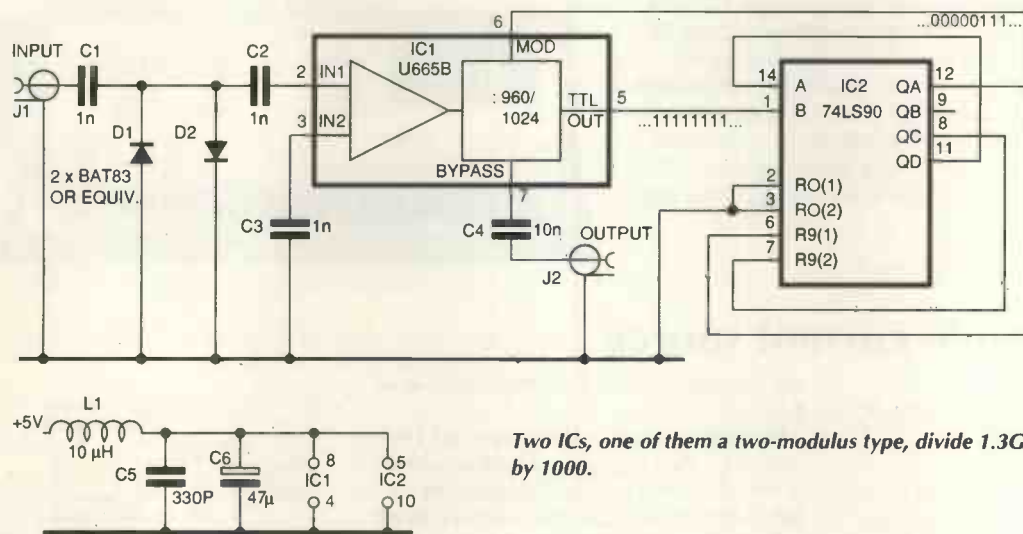

Two ICs, one of them a two-modulus type, divide 1.3GHz by 1000.


20Hz-20MHz function generator with duty-cycle adjust

Giving a 2V pk-pk output, the Maxim MAX038 is a 20Hz-20MHz function generator providing sine, square and triangle waveforms with an adjustable duty cycle on squares and triangles of 15%-85%.

Logic levels on A₀ and A₁ pins select the output waveform; position 1 of Sw₁ gives sine, 2 square and 3 triangle. Output frequency depends on current into I_{in}, set by R_{4,6} and the 2.5V reference voltage output, and the values of C₁₋₆ on the C_{osc} pin, selected by Sw₂ to give six 10:1 ranges.

Varying the voltage on the DADJ pin between -2.3V and +2.3V by R₂ varies duty cycle from 15% to 85% when square and triangle waves are in operation.

Yongping Xia
Torrance
California
USA

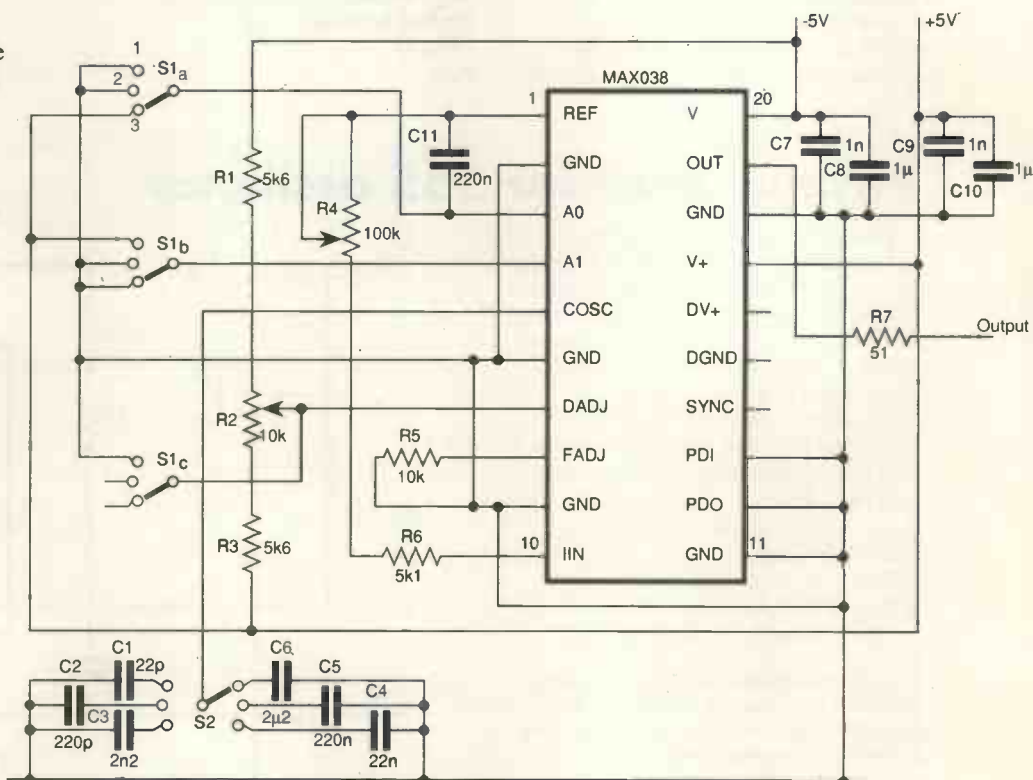

Flexible function generator uses MAX038 to provide sine, square or triangle waveforms over a very wide frequency range and with adjustable duty cycle.

SMART CARD READER/PROGRAMMER

On board ISO 7816 Card Reader Socket (Videocrypt etc). Software runs on IBM/PC enabling the user to read & write to card. Board also contains a PIC16C84 programmer. Ideal smart card development tool £59.95
Requires external power 15-20v AC or DC @250 ma. (optional extra £6.50)

MICRO-ENGINE MCS80C31/51 Development board.

Tiny 72mm x 42mm PCB contains socketed 44 pin CPU, turned pin rom socket, 12 MHz xtal and ports 1, 3 output on IDC connector. Ideal for stand alone projects or development work. Supplied with CIRCUIT & MCS8051/52 development software £49.95

PIC ICE II* In Circuit Emulator for PIC16C54-55-56-57-71-84.

Replaces all 18 or 28 pin PICs. All ports Bi-directional, OSC2 output, RTCC input. On board A/D converter for PIC167C1. Supplied with PICDEV54 and PICDEV71 software, manual, connecting leads & headers, ASM examples, and hardware circuit projects. £159.95

PIC ICE STD In-Circuit Emulator for 18 pin PICs only no A/D.

Plugs into the printer port, appears to the target system as a normal Pic device including OSC2 and RTCC in/out. Runs in real time from the IBM PC changes made to File registers reflected on target. Supplied with Development software PicDev 54-57 and PicDev 71/84 £69.95

PIC PROGRAMMER* Programs Pic16C54-55-56-57-71-84. Centronics port interface. Powerful editing software to read, write & copy Pic devices including data memory in Pic16C84. Top quality components used throughout including production ZIF socket. Now includes a Text Editor/Assembler for all above PICs. £79.95
Requires external power 15-20v AC or DC @250ma. (optional extra £6.50).

MEGAPROM programmer, EPROMS, E2PROMS, and FLASH memories from 2k (2716) to 8 Meg (27C080). Runs on IBM/PC via the centronics port using standard printer cable. Works on all PC compatibles, laptops, and notebooks. No special port requirements. Top quality components used throughout including production ZIF socket £99.95
Requires external power supply 18-25v AC or DC @250ma. (optional extra £6.50).

EPROM EMULATOR Works on ANY computer with centronics printer port. Data sent to the printer appears in the target board Eprom socket. Emulates from 1k to 23k Byte (27C256) roms, board switchable. Very fast download. Works with or without our Development software. £59.95

DEVELOPMENT SOFTWARE.

Develop software on your IBM/PC for other Microprocessors, Controllers, Pic's etc. Software has fully integrated Text Editor, Assembler, Disassembler, and Simulator. Code can be downloaded directly to our EPROM Emulator. All software supplied with sample ASM files, and user documentation manual.

Available for the following:-

MCS8051/52/55 £19.95 each
PIC16C54/56/71 PIC16C71/84 R6502
MCS8048/49 HD63/6809

All hardware carries a 12 months parts and labour Guarantee. No Vat payable. Please add £1.50 for Carriage.

Starred items also available from FARNELL (Leeds).

CREDIT CARD ORDERS SAME DAY DESPATCH

JOHN MORRISON DEPT WW

4 REIN GARDENS, TINGLEY,


WEST YORKSHIRE WF3 1JR

TEL (or FAX) 01132 537507



CIRCLE NO. 139 ON REPLY CARD

THE clock for your computer

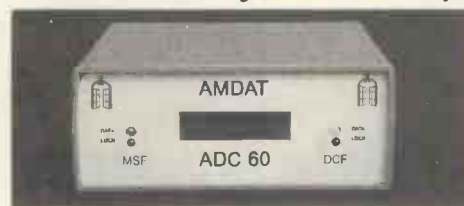

The ADC-60 brings the accuracy of a time standard to your computer. It provides a data source which can be used by any system which has a serial port such as a PC, MAC or mainframe. The ADC-60 offers improved reliability by using both the British MSF and German DCF time standards. If one of the signals cannot be received the other source will automatically be used.

Other ADC-60 Features include:

- LCD display showing current time and date together with the lock status of the unit.
- Provides GMT or Local time outputs together with the date
- Serial output in ASCII or BCD format
- Includes 2 software packages, the first is a TSR which runs under DOS, the second runs as a minimised window in Microsoft Windows

Contact us today for further information on this superb product

AMDAT

4 Northville Road, Northville

Bristol BS7 0RG

Tel: 01179 699352 Fax: 01179 872228

CIRCLE NO. 140 ON REPLY CARD


The new schematic capture program *Geswin* (GESECA for Windows™) adds more than a pretty face to *SpiceAge*. Upgrade for £100+ VAT*

- *Geswin* DDE links with *SpiceAge* to provide instant circuit editing. Because this link enables *SpiceAge* to retain all its simulation settings, the schematic (produced by *Geswin*) is uncluttered so that you can create clean drawings that may be clipboarded into your other Windows applications.
- You can clipboard sections of your netlist from *SpiceAge* back into *Geswin*'s attribute Inspector if you wish to use patches of existing circuits.
- *Geswin* has inherited *GESECA*'s speed and ease of use. You will find it's best-loved "bucket of bits" components' store waiting for your instant use from a special self-replenishing window.
- The *SpiceAge* component library has been expanded and re-drawn into "stubbies". The new symbols allow more components to fit within a given screen area without compromising clarity.
- Multiple windows allow you to scratch pad your designs (simulating as you work) and clipboard them into a fair copy window.
- File compatible with *GESECA*: schematics and components from *GESECA* may be read.
- Comprehensive HELP provides reference material; tutorial style manual reassures you of your own intuition.
- *Geswin* automatically invokes (or switches to) *SpiceAge*; you can also invoke *Geswin* from *SpiceAge*.

Please contact Those Engineers Ltd, 31 Birkbeck Road,
LONDON NW7 4BP.

Tel 0181-906 0155, FAX 0181-906 0969.

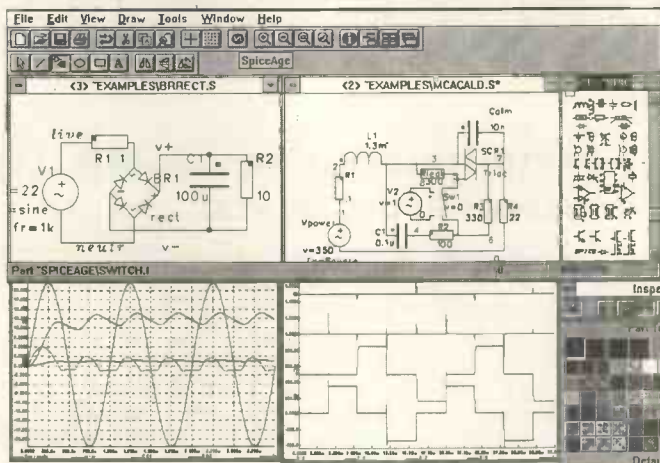*upgrade price from *GESECA*; £295 + VAT new



**Those
Engineers Ltd**



CIRCLE NO. 141 ON REPLY CARD

Bistable switch


Providing a bistable output that reverses after a set time in each state, this switch continues in the same state after a loss of power.

Digitally controlled potentiometer IC₁ – a Xicor X9C103P, for example – and comparator IC_{2a} are the basic elements, IC₁ wiper moving its complete travel when 100

pulses are applied; the values of the potentiometer and R_{11,12} determine the full-scale output voltage. As the hundredth pulse arrives, the potentiometer output voltage to the comparator exceeds the reference voltage from the zener, the output changes state and the potentiometer changes the direction of travel.

To ensure that the chip-select line of the potentiometer is low after the power supply has settled and high before it falls below the 4.5V lowest working voltage of IC₁, IC_{2b} controls this input to the potentiometer.

A J Stephenson
Seaford
East Sussex

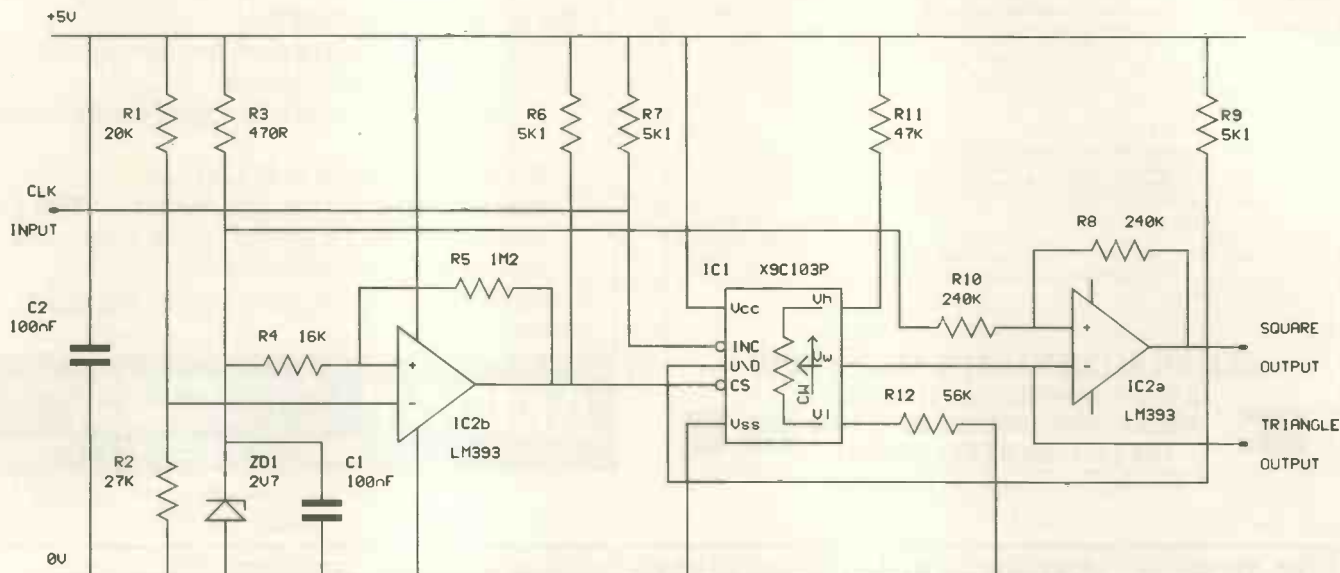


Bistable circuit changes output state after a given number of pulses are applied to the input, retaining its setting after power is removed.

Simultaneous sawtooth, square and triangle waves from a vco

A voltage-controlled oscillator producing square and triangular waves was described by Horowitz and Hill in *The Art of Electronics*, published by Cambridge University Press. CA3160E op-amps IC_{1,2} form the oscillator, supplied from a 5-12V rail and generating triangular and square waves at A and B respectively.

A third CA3160E operates as either a follower or as an inverter, depending on whether the mosfet conducts or is cut off. If the input to IC₃ is taken from the triangle wave and the mosfet drive comes from the square wave output, output C is a replica of the rising ramp of the sawtooth, followed by an inverted version of the falling ramp, the result being a sawtooth. Input voltage V_{control} should conform to $0 \leq V_{\text{control}} \leq 2(V^+ - 1.5V)$, so that $f = 150V_{\text{control}}/V^+$.

L Szymanski
Stamford
Lincolnshire

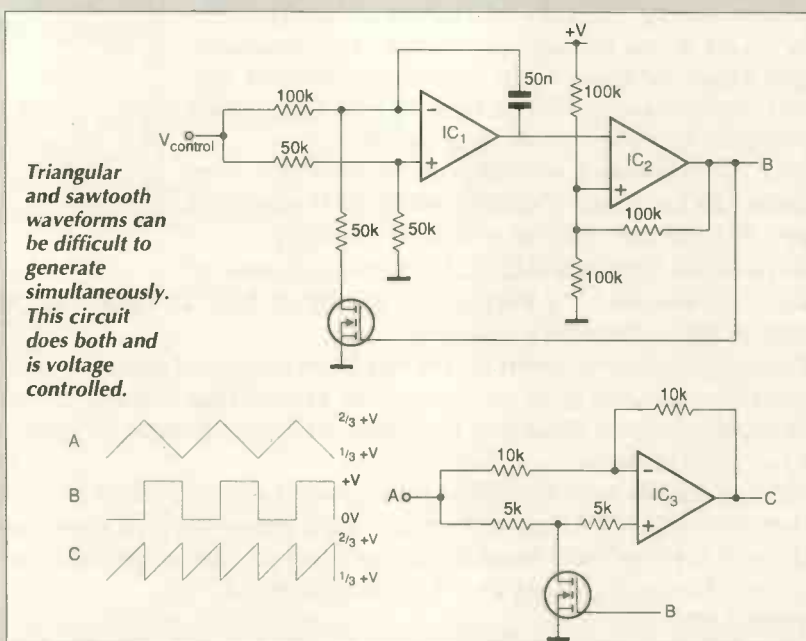

MONO VGA MONITORS

Some with slight screen burns but OK at £19.95 Ref EF40 and some without burns at £29.95 Ref EF39.

A4 DTP MONITORS Brand new, 300 DPI. Complete with diagram but no interface details (so you will have to work it out!) Bargain at just £12.99 each!!!!

OPD MONITORS 9" mono monitor, fully cased complete with rasterboard, switched mode psu etc. CGATTL input (15way D), IEC mains. £15.99 ref DEC23. Price including kit to convert to composite monitor for CCTV use etc is £21.99 ref DEC24

PC CONTROLLED 4 CHANNEL TIMER Control (on/off times etc) up to 4 items (8A 240v each) with this kit. Complete with Software, relays, PCB etc. £25.99 Ref 95/26

COMPLETE PC 300 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. **SALE PRICE** just £119.00.

RACAL MODEM BONANZA! 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

HOW LOW ARE YOUR FLOPPIES? 3.5" (1.44) unbranded. We have sold 100,000+ so ok! Pack of 50 £24.99 ref DEC16

BRITISH TELECOM MULTIMETERS SA9083 These are 'retains' so they may have faults but look ok. Complete with new leads and leather case. Price for two meters & 1 case is £10 ref DEC89.

6mw LASER POINTER. Supplied in kit form, complete with power adjuster, 1.5mw, and beam divergence adjuster. Runs on 2AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. Cheapest in the UK! just £39.95 ref DEC49

SHOP WOBBLERS! Small assemblies designed to take D size batteries and 'wobble' cardboard model signs about in shop windows! £3.99 Ref SEP42.

RADIO PAGERS Brand new, UK made pocket pagers clearance price is just £4.99 each 100x40x15mm packed with blits! Ref SEP5.

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 Ref TEN/1

COMPUTER RS232 TERMINALS. (LIBERTY) Excellent quality modem units, (like wise 50, s) 2xRS232, 20 function keys, 50 thro to 38,400 baud, menu driven port, screen, cursor, and keyboard setup menus (18 menu's). £29 Ref NOV4.

OMRON TEMPERATURE CONTROLLERS (E6C2). Brand new controllers, adjustable from -50 deg C to +1,200 deg C using graduated dial, 2% accuracy, thermocouple input, long life relay output 3A 240v ac contacts. Perfect for exactly controlling a temperature. Normal trade £50+, ours £15. Ref EF5C2.

ELECTRIC MOTOR BONANZA! 110x60mm. Brand new precision, cap start (or spin to start), virtually silent and features a moving outer case that acts as a fly wheel. Because of their unusual design we think that 2 of these in a tube with some homemade fan blades could form the basis for a wind tunnel etc. Clearance price is just £4.99 FOR A PAIR! (note-these will have to be wired in series for 240v operation Ref NOV1.

MOTOR NO 2 BARGAIN 110x90mm. Similar to the above motor but more suitable for mounting vertically (ie turntable etc). Again you will have to wire in 2 in series for 240v use. Bargain price is just £4.99 FOR A PAIR! Ref NOV3.

OMRON ELECTRONIC INTERVAL TIMERS.

Minute adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12VDC adjustable from 0-30 secs. £9.99
HY1210M, 12VDC adjustable from 0-10 mins. £9.99
HY1260M, 12VDC adjustable from 0-60 mins. £9.99
HY2460M, 24VAC adjustable from 0-60 mins. £5.99
HY241S, 24VAC adjustable from 0-1 secs. £5.99
HY2460S, 24VAC adjustable from 0-60 secs. £5.99
HY243H, 24VAC adjustable from 0-3 hours. £8.99
HY2401S, 240v adjustable from 0-1 secs. £9.99
HY2405S, 240v adjustable from 0-5 secs. £9.99
HY24060M, 240v adjustable from 0-60 mins. £12.99
PC PAL VGA to TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. £49.95. Ideal for laptops or a cheap upgrade. We also can supply this in kit form for home assembly at £34.95 ref EF54.

KIRKING BIRD Remember these? hook onto wine glass (supplied) and they drink, standup, drink, standup ETC! £4 each Ref EF1

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P1.

GUIDED MISSILE WIRE. 4,200 metre reel of ultra thin 4 core insulated cable, 28lbs breaking strain, less than 1mm thick! Ideal alarms, intercoms, fishing, dolls house's etc. £14.99 ref MAG15P5

300v PANEL METER 70X60X50MM, AC, 90 degree scale. Good quality meter. £5.99 ref MAG6P14. Ideal for monitoring mains etc.

ASTEC SWITCHED MODE PSU BM41012 Gves +5 at 3.75A, +12 at 1.5A, -12 at 4A. 230/110, cased, BM41012 £5.99 ref AUG6P3.

TORRODIAL TX 30-0-30 480VA, Perfect for Mosfet amplifiers etc. 120mm dia 55mm thick £18.99 ref APR19.

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a dgpr plug. 12v 2watt. £9.99 ea ref AUG10P3.

FLOPPY DISCS DSDD Top quality 5.25" discs, these have been written to once and are unused. Pack of 20 is £4 ref AUG4P1.

ECLATRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. £9.99 ref APR10P5.

24v AC 96WATT Cased power supply. New. £13.99 ref APR14.

MILITARY SPEC GEIGER COUNTERS Unused antistat from Her majesty's forces. £50 ref MAG 50P3.

STETHOSCOPE Fully functioning stethoscope, ideal for listening to hearts, pipes, motors etc. £8 ref MAR6P6.

OUTDOOR SOLAR PATH LIGHT Captures sunlight during

the day and automatically switches on a built in lamp at dusk. Complete with sealed lead acid battery etc. £19.99 ref MAR20P1.

ALARM VERSION Of above unit comes with built in alarm and pir to deter intruders. Good value at just £24.99 ref MAR25P4.

CARETAKER VOLUMETRIC Alarm. Will cover the whole of the ground floor against forced entry. Includes mains power supply and integral battery backup. Powerful internal siren, will take external bell if req'd. Retail £150+, ours? £49.99 ref MAR50P1.

TELEPHONE CABLE White 6 core 100m reel complete with a pack of 100 dips. Ideal 'phone extns etc. £7.99 ref MAR8P3.

MICRODRIVE STRIPPER Small cased tape drives Ideal for stripping, lots of useful goodies including a smart case, and lots of components. £2 each ref JUN2P3.

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26V DC 57x43x21mm with terminal screws £3.99 REF MAG4P10

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea, Ours? just four for £9.99 REF MAG10P2.

RGB/CGA/EGA/ATL COLOUR MONITORS 12" in good condition. Back anodised metal case. £79 each REF JUN79

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF MAG18P1. PSU £5 ref MAG5P12

SWITCHED MODE PSU ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

PLUG IN PSU 9v 200mA DC £2.99 each REF MAG3P9

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC 200mA output. Bargain price £5.99 ref MAG6P9

ACORN ARCHIMEDES PSU +5v @ 4.4A, on/off sw uncased, selectable mains input, 145x100x45mm REF MAG7P2

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. Now only £19 REF AUG19.

9v DC POWER SUPPLY Standard plug in type 150mA 9v DC with lead and DC power plug, price for two is £2.99 ref AUG3P4

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm. £3 a pack. REF MAG3P11

13.8V 1.9A psu cased with leads. Just £9.99 REF MAG10P3

PPC-MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

200 WATT INVERTER Converts 10-15v DC into either 110v or 240v AC. Fully cased 115x36x156mm, complete with heavy duty power lead, cigar plug, AC outlet socket. Auto overload shutdown, auto short circuit shut down, auto input over voltage shutdown, auto input under voltage shut down (with audible alarm), auto temp control, unit shuts down if overheated and sounds audible alarm. Fused reversed polarity protected. output frequency within 2%, voltage within 10%. A extremely well built unit at an excellent price. Just £64.99 ref AUG65.

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

MAINS-CABLE Precut black 2 core 2 metre lengths ideal for repairs, projects etc. 50 metres for £1.99 ref AUG2P7.

COMPUTER COMMUNICATIONS PACK kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 Interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance. Complete kit £8.99.

MINI CYCLOPS PIR 52x62x40mm runs on PP3 battery complete with shrill sounder. Cheap protection at only £5.99 ref MAR6P4.

ELECTRIC MOTOR KIT Comprehensive educational kit includes all you need to build an electric motor. £9.99 ref MAR10P4.

VIEWDATA SYSTEMS made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. £18 each Ref EF88.

BOOMERANG High tech, patented polypropylene, 34cm wing span. Get out and get some exercise for £4.99 ref EF83

AIR RIFLES. 22As used by the Chinese army for training purposes, so there is a lot about £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

PEANUT TREE Complete kit to grow your own peanuts! full instructions supplied. £3 Ref EF45.

PLUG IN POWER SUPPLYS Plugs in to 13A socket with output lead, three types available, 9vdc 150mA £2 ref EF58, 9vdc 200mA £2.50 ref EF59, 6.5vdc 500mA £3 ref EF61.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***TERRA RADIO TRANSCEIVERS** A pair of walkie talkies

***SOME OF OUR PRODUCTS MAY BE UNLICESABLE IN THE UK**

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***TERRA RADIO TRANSCEIVERS** A pair of walkie talkies

***SOME OF OUR PRODUCTS MAY BE UNLICESABLE IN THE UK**

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***TERRA RADIO TRANSCEIVERS** A pair of walkie talkies

***SOME OF OUR PRODUCTS MAY BE UNLICESABLE IN THE UK**

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***TERRA RADIO TRANSCEIVERS** A pair of walkie talkies

***SOME OF OUR PRODUCTS MAY BE UNLICESABLE IN THE UK**

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

with a range of up to 2km in open country. Units measure 22x52x155mm. Including cases and ear/pes. 2xPP3 req'd. £30.00 pr. REF: MAG30

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc in fact everything bar the case and electronics, a good stripper £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

LED PACK of 100 standard red 5m leds £5 REF MAG5P4

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

GYROSCOPE About 3" high and an excellent educational toy for all ages! Price with instruction booklet £6 Ref EF15.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec Inlet and on/off switch. £12 Ref EF6.

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34.

PC POWER SUPPLIES (returns) These are 140x150x90mm, o/ps are +12, -12, +5 and -5v. Built In 12v fan. These are returns so they may well need reparing! £3.50 each ref EF42.

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever! why pay £700? or price is £15 REF: EF62 Transmits to any FM radio. (this is in kit form with full instructions.)

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

AT KEYBOARDS Made by Apicort these quality keyboards need just a small mod to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

HEADPHONES Ex Virgin Atlantic. 8 pairs for £2 REF: MAG2P8

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

GAS HOBS Brand new made by Optimus, basic three burner suitable for small flat etc bargain price just £29.95 ref EF73.

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82 extra pellets (500) £4.50 ref EF80.

CHRISTMAS TREE KIT Start growing it now! £3 ref EF53.

DOS PACK Microsoft version 5 Original software but no manuals hence only £5.99. 3.5" only.

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

MOBILE CAR PHONE £5.99 Well almost complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG6P11

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 Ideal for experiments! 30m for £12.99 ref MAG13P1

HEATSINKS (finned) TO220, designed to mount vertically on a pcb 50x40x25mm you can have a pack of 4 for £1 ref JUN1P11.

STROBE LIGHT KIT Adjustable from 1 hz right up to 60hz! (electronic assembly kit with full instructions) £16 ref EF28.

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together! belived to cause rain! £3 a pair Ref EF29.

NEW HIGH POWER LASERS

15mW, Helium neon, 3 switchable wavelengths. 63um, 1.15um, 3.39um (2 of them are Infrared) 500:1 polarizer built in so good for holography. Supplied complete with mains power supply. 790x65mm. Use with EXTREME CAUTION AND QUALIFIED GUIDANCE. £349+Vat.

WE BUY SURPLUS STOCK FOR CASH

FREE CATALOGUE

1995 100 PAGE CATALOGUE NOW AVAILABLE, 45P STAMP OR FREE WITH ORDER.

PORTABLE RADIATION DETECTOR

WITH NEW COMPUTER INTERFACE.

£59.00

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook. Ref. NOV18.

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX

BN3 5QT (ESTABLISHED 50 YEARS)

MAIL ORDER TERMS: CASH PO OR CHEQUE

WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 01273 203500

FAX: 01273 323077

CIRCLE NO. 142 ON REPLY CARD

Circuit round-up

Contributed by designer John Burnill, this collection of circuit ideas covers a variety of applications.

Meter response equaliser

Pointer movement of dc milliammeters exhibits a second order response to changing current. This can be equalised by the circuit shown, speeding up the response typically by a factor of ten. Response time is limited by the low-pass filter on the input, which is there to prevent the subsequent circuitry clipping on full scale steps in amplitude.

Values shown are for a typical 200µA/1kΩ 'VU' meter. Resistor R_3 adjusts the Q. This is independent of R_1 which adjusts the corner frequency.

These equations give the corner frequency and the Q. Resistor R_4 is assumed equal to R_5 .

$$f = \frac{1}{2\pi C \sqrt{R_1 R_2}}$$



$$Q = \frac{R_3}{2\pi f R_1 R_2}$$

Fast full-wave peak rectifier

This full wave peak rectifier is fast due to the fact that none of the op-amps saturate. The circuit is accurate to 1dB to 300kHz using TL081s. Attack time is limited by the limited output current of the op-amps. Decay time is set by the 4.7MΩ resistor. Taking this resistor to the negative supply rail gives approximately linear decay against time.

Video-signal processing

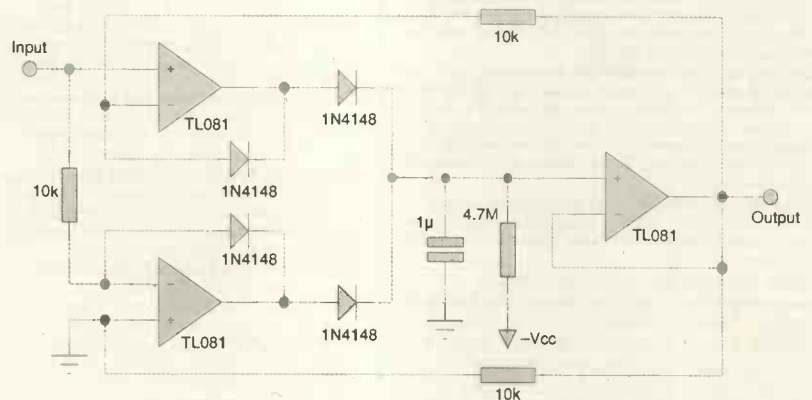
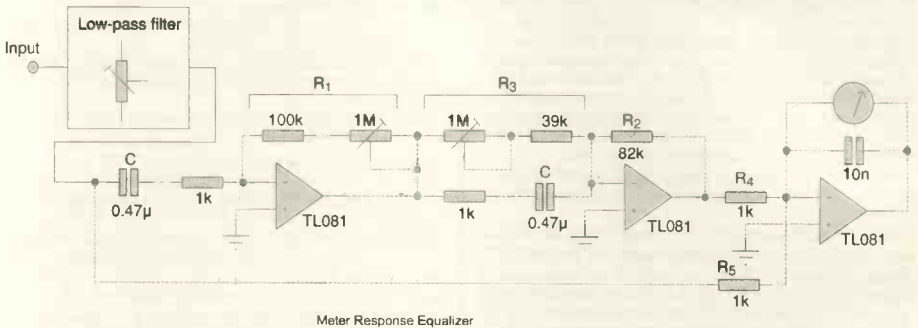
Two ideas related to each other in that they concern the processing of video signals. First is a precision dc restorer. Basic circuits using a diode can mangle the sync enough to cause loss of frame sync on some receivers. The circuit shown here solves the



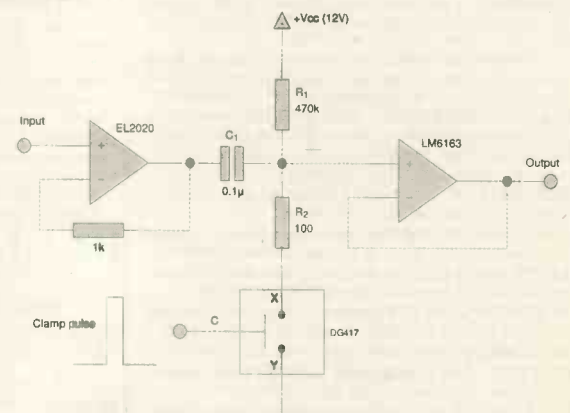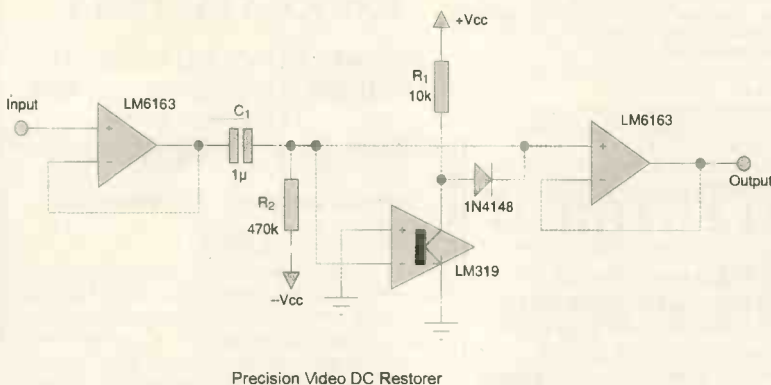problem. Resistor R_1 controls the 'attack' time and R_2 the tilt.

The second circuit is a very simple clamp with more than adequate performance. Clamping time is determined by the time constant R_2/C_1 . Resistor R_1 is to offset the


input current of the output op-amp to minimise drift on the clamped wave form. The input amplifier is a EL2020 because when the clamp is switched on it must drive a 100Ω load.



Oven for crystal stabilisation

A circuit to use as a heater for temperature stabilisation of a crystal. Base emitter junction voltage of the heater transistor is sampled as a measure of device temperature while collector current is held constant. Resistor R_1 provides reference current. The op-amp is the sample-and-hold and loop error amplifier. A reference voltage is applied to the non-inverting input to set the temperature.

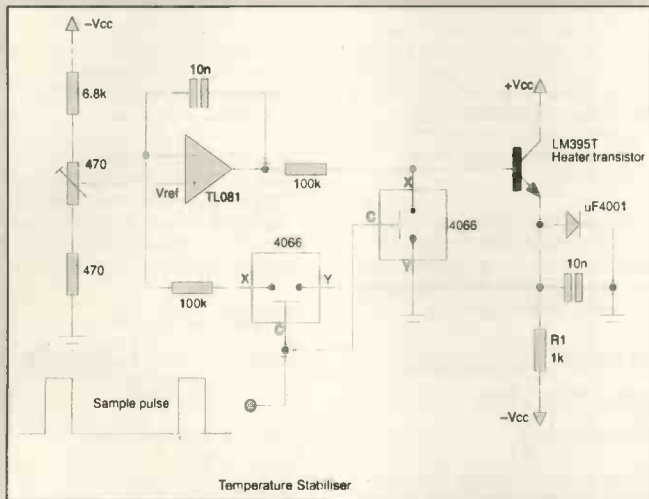The heater transistor used is a **LM395**. This device is overload and overtemperature protected, making temperature adjustment idiot proof. For best performance the crystal to transistor thermal resistance should be minimised and the thermal resistances from the two to ambient maximised. Power supplies are $\pm 8V$. Sample timing is not critical. A 1ms period and 0.2ms sample width are fine.




Narrow and wide-range voltage-controlled oscillators

Two more related ideas. A voltage controlled crystal oscillator designed to maximise the pulling range of a parallel crystal. The two diodes decrease the rf voltage across the varicap.


Capacitor C_1 sets the centre frequency. This is done using the final layout to compensate for circuit strays. There is no need for a trimmer if all the crystals are cut to the same load capacitance. Pulling range is about $\pm 50Hz$ for a typical 2MHz crystal.

A simple wide-range vco is shown in the second diagram. The diodes decrease the rf voltage across the varicap and have the added benefit of making the output waveform symmetrical.

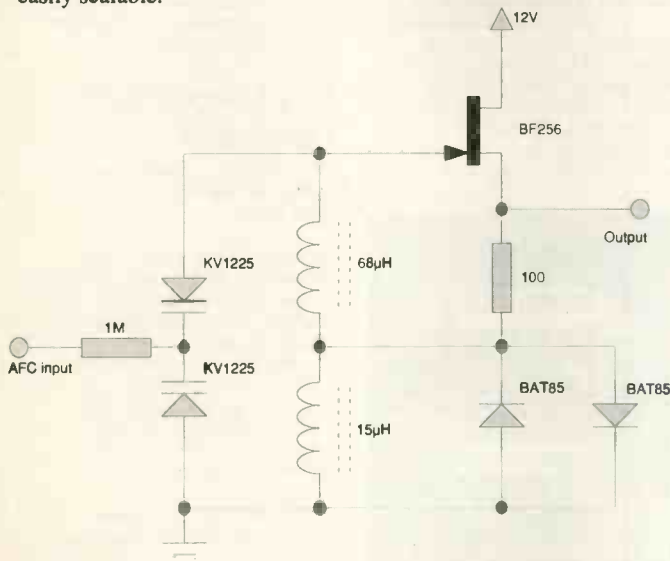Output is low impedance. Range for this circuit is 1MHz-3.5MHz for a voltage swing of 1-29V on the varicap. The arrangement is easily scalable.



IBM PC compatible


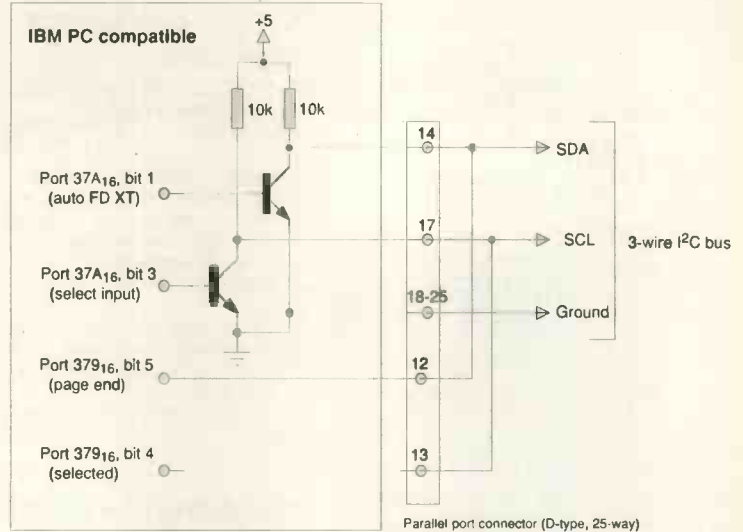



Simple I²C interface for pcs

This is a way of interfacing an IBM pc compatible to the I²C bus. The software is too lengthy to be given here. Port 379₁₆ is used to read data in. The relevant output must be off (port 37A₁₆ set low). Port 37A₁₆ is for outputting data. Note there is polarity inversion.

Both SDA and SCL lines need 1kΩ pull up resistors at the receive end if the bus is to be used at full speed over reasonable length connections.

Integrator with no signal inversion

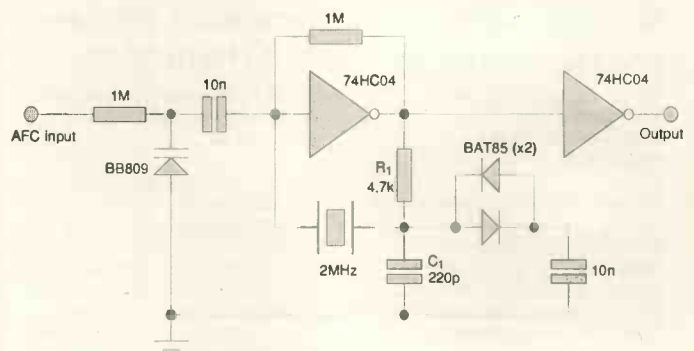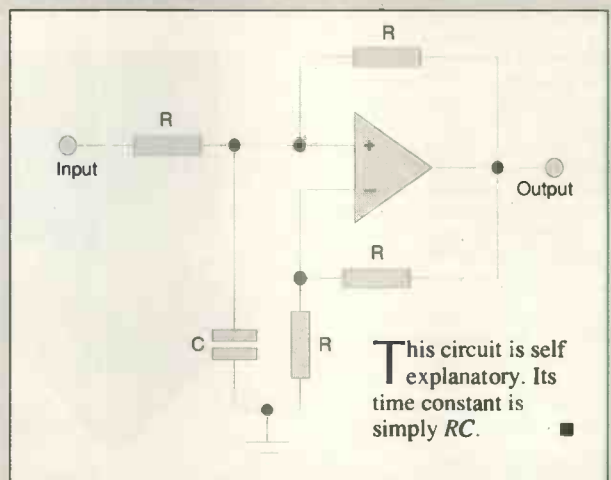

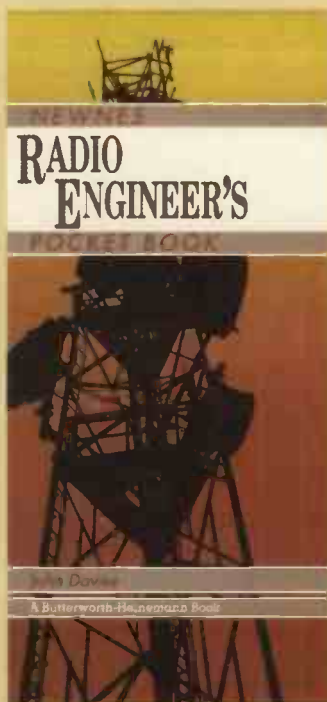

Radio Engineer's Pocket Book

by John Davies, 240pp, hardback
Order – ISBN 0 7506 1738 1
Price £12.99

Contains: Propagation; decibel scale; transmission lines; antennas; resonant circuits; oscillators; piezo-electric devices; bandwidth requirements and modulation; frequency planning; radio equipment; Microwave comms; information privacy and encryption; multiplexing; speech digitisation and synthesis; vhf and uhf mobile communication; signalling; channel occupancy, trunking; mobile systems; base station management; instruments; batteries; satellite comms; connectors and interfaces; broadcasting; abbreviations and symbols; tables and data; glossary.

Covers all aspects of radio and communications engineering from very low frequencies to microwaves, with particular emphasis on mobile communications. Wave principles and the decibel scale, instrumentation and power supplies, equipment types and encryption methods, connectors and interfaces, are all included in this book.

Audio Recording and Reproduction

Michael Talbot-Smith, 204pp, paperback
Order – 0 7506 1917 1
Price £12.99

Contains: Physics of sound waves; hearing; basic acoustics; microphones; loudspeakers; public address; stereo; simple mixing equipment; recorders; introduction to digital audio; music and sound effects; miscellaneous data.

This book gives a simple and straightforward approach to audio techniques, detailing technical and practical information for those with no specific training in the subject.

Circuit Designer's Companion

by T Williams, 320pp, paperback
Order – 0 7506 1756 X
Price £15.99

Contains: grounding and wiring; printed circuits; passive components; active components; linear integrated circuits; digital circuits; power supplies; electromagnetic compatibility.


Valued by linear and digital designers alike, this guide explains and outlines solutions that take into account the imperfect behaviour of real components, interconnections and circuits.

Servicing Personal Computers

by Michael Tooley, 304pp, hardback
Order – ISBN 0 7506 1757 8
Price £25.00

Contains: Microcomputer systems; test equipment; fault diagnosis; tape and disk drives; printers and monitors; servicing IBM pc compatibles and 68000-based computers.

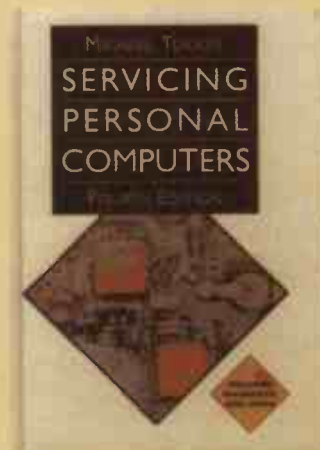This completely rewritten fourth edition still covers the whole range of microcomputer equipment but now also includes a guide to developments and trends such as the new generation of diagnostic software – code included – and applications such as serial communication, and memory and hard disk management.



Newnes Audio and Hi-Fi Handbook

by Ian Sinclair, 656pp, hardback
Order – ISBN 0 7506 0932 X
Price £40.00

Contains: Sound waves and acoustics; studio acoustics; microphones; sound synthesis; introduction to digital principles; compact disc technology; other digital systems – DAT, NICAM, DCC, MD – analogue tape recording; noise reduction systems; LP records; disc reproduction; tuners and radio receivers; preamps and inputs; voltage amplifiers/controls; loudspeakers and enclosures; Headphones; public address; in-car audio; Interconnections; the future.

Covers a wide perspective of high-quality sound reproduction, including reproduction under adverse circumstances, from less conventional sources and with regard to the whole technology from studio to ear.

TV & Video Engineer's Reference Book

by Boris Townsend, 876pp, paperback
Order – ISBN 0 7506 1953 8
Price £40.00

Contains: Materials; components and construction; colour tv fundamentals; broadcast transmission; distributing broadband; DBS; tv studios; mobile and portable equipment; tv sound; tv receivers; servicing tvs; video recorders; teletext etc; HDTV; other applications of tv; performance measurements.

Covers information on every aspect of modern broadcast technology. Of value to all practicing engineers and managers involved with broadcast, cable and satellite services.

Masts, Antennas and Service Planning

by Geoff Wiskin, 256pp, hardback
Order – ISBN 0 240 51336 3
Price £49.50

Contains: Antennas; antenna support structures; service planning.

Covers all aspects of Information conveyance via radio-wave transmission. Invaluable to anyone planning for broadcast and mobile-radio coverage, or designing, installing and maintaining antenna systems.

Operational Amplifiers

by Jiri Dostal, 400pp, hardback
Order – 0 7506 9317 7
Price £40.00

Contents: The operational amplifier; basic concepts; operational amplifier parameters; operational amplifier properties; the operational circuit; the ideal operational circuit; analysis of the real operational circuit; static and dynamic errors in the frequency domain; dynamic errors in the time domain; input and output impedances;

offset; noise; stability; good laboratory practices.

Presents an extensive treatment of applications and a practically oriented, unified theory of operational circuits. Provides the reader with practical knowledge necessary to select and use operational amplifier devices.

Servicing Video Cassette Recorders

by Steve Beeching, 250pp, hardback
Order – ISBN 0 7506 0935 4
Price £25.00

Contains: Vcr systems; azimuth tilt; Frequency modulation; servo mechanisms; colour systems; systems control; long play; VHS-C & camcorders; a-v sockets.

Written for students and people involved with vcr servicing, this book is an invaluable guide and reference covering all aspects of modern vcrrs. Contains new material on basic magnetic theory to C&G 224

Principles of Transistor Circuits

by S W Amos, 384pp, paperback
Order – 0 7506 1999 6
Price £17.99

Contains: Semiconductors and junction diodes; basic principles of transistors; common-base and common-gate amplifiers; common-emitter and common-source amplifiers; common-collector and common-drain amplifiers; bias and dc stabilisation; small-signal af amplifiers; large-signal af amplifiers; dc and pulse amplifiers; rf and if amplifiers; sinusoidal oscillators; modulators, demodulators, mixers and receivers; pulse generators; sawtooth generators; digital circuits; further applications of transistors and other semiconductor devices.

This seminal work has now been presented in a clear new format and completely updated to include the latest equipment such as laser diodes, Trapatt diodes, optocouplers and GaAs transistors, and the most recent line output stages and switch-mode power supplies.

Logic Designer's Handbook

by Andrew Parr, 488pp, paperback
Order – 0 7506 0535 9
Price £30.00

Contains: Simplified data on a comparative basis of ttl and cmos ics; storage devices; logic circuits; timers; counters; drivers; interface circuits; logic gates; definitions of ic characteristics; event driven logic; communication and highways; analogue interfacing; practical considerations; summaries by function of all relevant circuits; Individual pin-out diagrams.

Easy-to-read, but nonetheless thorough, this book on digital circuits is for use by students and engineers, and is a readily accessible source of data on devices in the ttl and cmos families.



The Art of Digital Audio

John Watkinson, 490pp, hardback
 Order – 0 240 51320 7
 Price £49.50

Contains: Why digital?; conversion; AES/EBU; digital audio coding and processing; digital compact cassette (DCC); advanced digital audio processing; digital audio interconnects; digital recording and channel coding; error correction; rotary head recorders; stationary head recorders; NAGRA and data reduction; Digital Audio Broadcasting (DAB); the compact disc/mini disc.

New edition, completely updated to include all the latest developments, including DCC, the mini disc and digital audio broadcasting.

Microphone Engineering Handbook

by Michael Gayford, 384pp, hardback
 Order – 0 7506 1199 5
 Price £65.00

Contains: Microphone techniques; precision microphones; optical microphones; high quality rf microphones and systems; radio microphones and ir systems; microphone testing; ribbon microphones; microphone preamplifiers; stereo microphones; microphone standards.

Comprehensive and authoritative book for engineers, technicians, students and anyone else concerned with the design and use of microphones.

MIDI Systems and Control

by Francis Rumsey, 256pp, paperback
 Order – 0 240 51370 3
 Price 19.95

Contains: Introduction to principles and terminology; synchronisation and external machine control; common implementations; systems control sequences and operating systems; implementation of midi with peripheral devices; practical systems designs.

Second edition is updated and enlarged to take MIDI evolution into account. More examples of real implementations, more diagrams and the whole book has been rewritten to include a far greater practical element, to complement its existing technical strengths. Several completely new sections and complete chapters have been added including a new opening chapter as an introduction to principles and terminology; MIDI timecode; librarians and editors.

Loudspeaker and Headphone Handbook

by John Borwick, 224pp, hardback
 Order – 0 240 51371 1
 Price £35.00

Contains: This book brings together in a single volume every aspect of loudspeaker and headphone theory and practice in sufficient depth to equip students and practitioners alike with a solid working knowledge of the subject. A comprehensive technical reference on the theory and practice of loudspeaker and headphone performance, design and operation.

The Art of Linear Electronics

by John L Hood, 400pp, paperback
 Order – 0 7506 0868 4
 Price £16.99

Contains: Electronic component symbols and circuit drawings; passive components; active components based on thermionic emission; active components based on semi-conductors; practical semi-conductor components; dc and low frequency amplifiers; feedback negative and positive; frequency response; modifying circuits and filters; audio amplifiers; low frequency oscillators and waveform generators; tuned circuits; high frequency amplifiers/oscillators; radio receiver circuitry; power supplies; noise and hum; test instruments and measurements.

This practical handbook gives a complete working knowledge of the basics and technology of linear electronics – with application examples in such fields as audio, radio, instrumentation and television.

Servicing Audio and Hi-Fi Equipment

by Nick Beer, 304pp, hardback
 Order – 0 7506 2117 6
 Price £25 .00


Contains: Introduction; tools and test equipment; radio receivers; amplifiers; power supply circuits; portable audio; cassette deck mechanics; cassette electronics; turntables; system control; motors and servo circuits; compact disc; mini disc; digital audio tape; digital compact cassette; speakers, headphones and microphones; repair, addresses.

As a bench-side companion and guide, this work has no equal. Its purpose is to ease and speed up the processes of fault diagnosis, repair and testing of all classes of home audio equipment: receivers, amplifiers, recorders and playback machines.

EMC for Product Designers

by Tim Williams, 304pp, hardback
 Order – ISBN 0 7506 1264 9
 Price £25.00

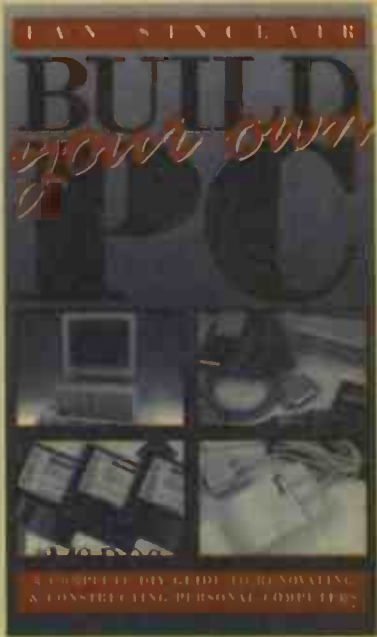Contains: What is EMC? standards; EMC measurements; interference coupling mechanisms; circuits; layout and grounding; interfaces; filtering and shielding.



'This book is likely to become essential reading for those designing electronic products for the European market,' according to *New Electronics*. Widely regarded as the standard text on EMC, providing all the information needed to meet requirements of the EMC Directive.

Build Your Own PC

by Ian Sinclair, 256pp, paperback
 Order – ISBN 0 7506 2006 4
 Price 16.95

Contains: Assembly from scratch – mainly for masochists; fundamentals and buying guide; case, motherboard and keyboard; disk-drive details; improvers and modifiers for graphics and i/o; DOS operation and hints; Windows; connecting printers; glossary.

Covers Building your own pc from scratch or from modules. Written at a level suitable for beginners and those with experience of computers or electronics. In addition, this work provides a useful guide for anyone wanting to save money by upgrading their pc themselves.

Return to Jackie Lowe, Room L333, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following titles:

Qty	Title or ISBN	Price

Please add £2.50 UK Postage, £5.00 Europe £7.50 Rest of World

Total _____

Name _____

Address _____

Post code _____ Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Publishing

Credit card no _____

Card expiry date _____ Signed _____

LETTERS

Letters to "Electronics World + Wireless World" Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

UK mains change – any effects?

Kettles, toasters, electric ovens and any piece of domestic electrical equipment with an ac motor – even if it has a power stabiliser for its dc electronics – all have reduced power following the normalisation of Britain with the European Union's electrical standards body Cenelec, based in Brussels.

Electricity boards can take advantage of the new rules to supply more consumers from a single generator. This, rather than any change in hardware, reduces average supply from 240V to 230V.

The 8.2 per cent associated average decrease in power was too subtle to be obvious to everyone, but hundreds of complaints have been reported.

On the individual scale, last minute rushers have found themselves missing buses and trains in the morning after a slightly delayed breakfast.

These complaints may soon be forgotten as people adjust to get up a few minutes earlier, but the attempted cover-up was quite a remarkable piece of work. A Sunday tabloid editor was successfully fobbed off by

an electricity board public relations spokesperson.

Only when a sackful of irate letters arrived at the tabloid's London office after the paper's editor wrote about his search for 'loose wires' or 'crumbs' in his kettle and toaster, were experts consulted as the media began to wonder whether January's regulations change could really be to blame.

Confusion has arisen over the difference in the changes in volts and power. Power is simply volts squared and divided by resistance. The latter varies with temperature, but this is usually negligible over the 4.2 per cent reduction in volts. Thus, the mains electric power has been reduced by around 8 per cent.

Concerns over hospital life-support systems, word processors and computers, and video recorders slowing down are mainly unfounded. All use regulated dc power from an in-built mains ac converter.

Old fashioned electric clocks are of course unaffected, because the alternating frequency of the generators, still 50 hertz, keeps them on time. Mains electronic clocks using crystal oscillators again have a power regulator which compensates easily for the reduction.

We may also be able to turn the oven up easily, but we can hardly take some windings off the coils of our electric motors, or reduce the electrical resistance of our kettles.


So vacuuming, boiling for tea or coffee, toasting, and lawn mowing will just have to take longer. At least, until manufacturers reduce the resistance of their products by 8.2 per cent, so that they deliver the same average power and speed of work as their specifications state, and until consumers buy the new appliances.

Nigel Cook
Addlestone
Surrey

Learning while earning

Andrew Ainger's leader 'Training Dinosaurs' in EW+WW March '95 expressed an interesting idea, but can he offer any clues as to how the idea of learning on the job might be work in practice?

H. Martinson
Newcastle

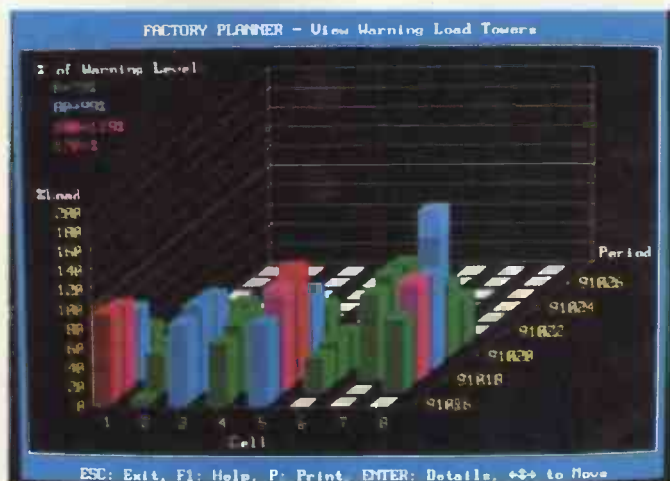

Cell-based factory: horizontal axis indicates manufacturing cells while the vertical axis gives overall load on the cells. 'Depth' axis is the time.

Andrew replies:

An example of human-centred technology – technology that enables staff to learn while they earn – is as follows.

Consider a very common industrial problem, that of planning what each machine has to do within a manufacturing organisation. For a manufacturer to remain competitive it has to remain profitable. To remain profitable the business has to maximise use of factory resources.

In the past this Manufacturing Resource Planning (MRP) was achieved by what has been termed MRPII computer systems. These systems attempted to plan out what each machine in the factory does, and when and how it does it. In theory, this approach works. In practice it may work well in companies where the products are relatively simple, but in the vast majority of cases, MRPII schedules are unrealistic, unreliable and – as many a manufacturing manager knows – often a work of fiction.

This is not really surprising as it only takes one small deviation from the plan to upset the rest of the downstream factory. It is rather like planning your car journey from Lands End to John O'Groats and telling your aunt, who lives in Birmingham, when she should put the kettle on for your cup of tea.

In modern manufacturing organisations there is now a move towards Cell-Based manufacture. This is rather like splitting the Lands

End to John O'Groats journey into sections. In many ways this can be regarded as a way of remedying the planning problem via an organisational solution. There can be no doubt that cell-based manufacturing, with its added flexibility, has proved to be an extremely effective and profitable way of manufacturing products.

Traditional IT planning systems are trying to catch up and match this flexibility. However it is not only the IT systems that have to be flexible but also – and more importantly – the people.

For people to remain flexible they have to welcome change; in order to welcome change they have to gain new knowledge. Human Centred Systems appear to be the only solution to this problem.

Rather than presenting data to the manufacturing personnel, the human-centred way is to provide them with information.

The diagram depicts a cell-based factory: the horizontal axis indicates manufacturing cells while the vertical axis gives the overall load on the cells. The 'depth' axis gives the time, divided into periods, which may be shifts, days or weeks for example. Using this diagram and the information it embraces, three learning opportunities emerge:

● First and most obviously, this view (map) of the factory enables the state of the factory to be judged at a glance, production hot spots

IEE 'nonsense'

Many people working in the field of bioelectromagnetics research have been shocked and angered at the review published last year by the UK Institution of Electrical Engineers. The organisation published a similar study in 1991, I believe, which no-one took very seriously.

The latest conclusions are that there are no effects, either hazardous or beneficial, from weak elf em fields. This is not only an absolute nonsense but contradicts many thousands of cellular live animals and epidemiological studies. In my view it is simply propagandist material masquerading as science.

The IEE refuses to disclose the references on which it claims to rely. A look at the composition of its working committees shows that they are heavily weighted with power-utility-related personnel.

Roger Coghill
Gwent

identified and appropriate action initiated.

● Trends can be identified extremely quickly. For example, depending upon the work load and the factory's capacity, 'waves of colour' can be seen to ripple over the surface of the factory. These trends can alert the system operator to situations that have been hitherto undetected in traditional print-outs.

● Output of this particular planning system enables the 'sensitivity' of the factory to certain orders to be 'felt', just as the driver of a car can feel the difference when driving over different road surfaces. Over time the sensitivity to certain orders and the 'feel' of the factory can give advanced warning to the human-centred IT system operators when a particularly awkward product mix is being contemplated.

This type of diagram adds credence to the saying that 'a picture is worth a thousand words'. It is these types of IT systems that enable users to assimilate and build knowledge while they work – a true learning earning environment. It is not easy to design IT systems that can be used in this human-centred way, but it is possible. The mindset of the design engineers concerned has to be woken up to this new design philosophy.

Bear in mind that although you cannot design human-centred technology you can design the opposite. Although the logic of this statement is initially surprising, it becomes quite straightforward when you consider that we cannot design a perfectly safe car but we can certainly design an unsafe one.

It is only by designing technology that can be used in a human-centred way – as will a true Human Centred System – that continued incremental learning can take place. By this I mean that the car may be designed with safety in mind, but it is the way it is driven that is most important.

The challenge is to design IT systems that can be used in a human-centred way, enabling people to learn while they earn. It is only through continued learning that organisations can continue to change, flex and survive. Engineers should take note. A new and powerful design philosophy has emerged, and if we fail to embrace it the 'future' may fail to embrace us.
Andrew Ainger
Human Centred Systems
Windsor

Beyond TV Sat 2

Reg Williamson's complaint (Letters, March '95) of arbitrary cessation of TV Sat and its 16-station service might cause a perceptive person to ask what are German listeners doing about it?

The answer must be that they, like

me, are retuning to the lower powered Kopernicus transmission and receiving the same service – albeit with the odd flip if anything other than a very large dish is used. At my latitude, one metre is recommended, but an 80cm dish combined with an Inb made for the telecom band, is acceptable for my purpose, which is recording the audio on digital tape.

When the Kopernicus service ends, we will have to pay for digital audio satellite transmissions. But it will still be cheaper than buying cds, and preferable to Classic FM and its relentless commercials – not to mention Radio 3 fm, which varies from grand ole opry to children's hour, with cricket in the summer to induce total somnolence.

Hugh Haines
Sunderland

Roadside oxide

In a recent photovoltaics installation used for a display by the environmental group Common Ground, some components such as leds corroded and broke down after being exposed to the elements for a period of five weeks.

Can any of you say whether this is normal, or caused by adverse conditions such as acid rain? The installation was near a busy London road and quite a lot of rain fell during the five weeks.

Since we are planning a similar installation to coincide with the end of 1995, we would like to learn from this, especially if it involves a mistake on our part.

Nicolas Holliman
London

Cheap talk

I saw an article in Computing and Control Engineering Journal October 1994 about a development that could lead to entirely free electronic mail – once the equipment has been bought.

The problem with Internet is that it requires the use of the telephone system, which can never be free. However most broadcasting is free. Although some countries like the UK charge a licence fee, this is only to pay for the government station, in our case the BBC. The commercial channels are all free, as are foreign stations receivable here.

Although it sounds far-fetched, this freedom of broadcasting can be transferred to two way communication.

The secret is that every node is a transmitter and receiver of very low range, and the system relies on each node being able to send its message to the next node and so on. In addition, the message contains directional information, so nodes that are in the wrong direction can refuse it.

Unknown rectifier materials

I know of no electrolytic rectifiers using the electrode combinations mentioned by 'unsigned' (Letters, February) being used as radio detectors. However, electrolytic rectifiers using similar electrodes were used with accumulator chargers and were described in 1920s radio books. So far, I have been unable to discover whether they evolved before or after Fessenden discovered the barretter, or the evolution of the crystal detector.

In 1935, when a schoolboy experimenter, I employed four electrolytic rectifiers in a bridge circuit to trickle charge 6V accumulators. Unfortunately I have long since lost my records but I seem to remember experimenting with aluminium/lead and aluminium/iron electrodes. Large jam jars served as cells and the electrolyte was ammonium phosphate.

'Unsigned' explains that with iron/zinc alloy electrodes, an insulating film develops on the alloy electrodes but this disappears when current flows from iron to alloy. Presumably the same applies to my electrolytic rectifiers.

On the other hand, rectification with the barretter seems to depend more on the movement of ions.

Nonetheless, I would like to experiment with the electrode combinations mentioned by 'Unsigned' and would be most grateful for any further information.

George Pickworth
Kettering

Hisses and glows from the past

George Pickworth's recent articles, *Detection before the diode*, and the unsigned letter from Middlesex in the February 1995 issue brought back memories of some seventy years ago.

In the very early days of domestic radio I had gradually acquired enough 12V lead-acid accumulator blocks to give me 120V ht. We lived out of town and I used to carry these on my bicycle to my grandmother's cellar where 220V dc was available.

Later on, electricity reached our house – ac of course – so I was able to recharge them at home when I'd made a rectifier. This was a chain of ten or twelve tiny sample jam jars with electrodes of aluminium strip and carbon rods from exhausted 4.5V batteries, in a solution of ammonium phosphate.

One could buy ammonium phosphate, sold as fertiliser, from the seed shop. These cells made a peculiar hissing noise and in the dark you could see a pulsating glow on the aluminium strips. I don't know what the reverse current was but it may have been good for the health of the battery. All this information must have come from *Wireless World* – happy days.

I was given a coherer some years ago and it still works. Put in series with a 1V cell and an AVO on the 3V range there was no visible deflection. Flicking 230V ac mains across a 4µF capacitor at a distance of 15cm gave an immediate deflection of several milliamps. A very light tap to the coherer and it immediately returned to its non-conducting state ready for the next burst of rf energy.

Ralph Wesr
Villereal, France

The system will not work in areas of low population density, but as humanity is fairly well concentrated in small areas of the planet most people should have access.

The article describes a wireless local area network. That is to say the network is limited to a particular business or other grouping of computers. However there is no reason why such networks shouldn't communicate with each other using a radio version of the Internet. The article also says that wireless lans would meet type approval so as to be licence free, as they are low power transmissions.

Initially the existing telephone-based Internet would be used to connect wireless lans that were out

of range of each other, but as more and more are installed they would be able to communicate with each other directly and the use of the telephone Internet would fall.

John de Rivaz
Truro

What conspiracy?

In a letter to WW, Nov. '81, JL Linsley Hood writes that "censorship has been effective throughout my own professional career...". He lists nine authors who could not have been published anywhere but in *Wireless World*.

As Pete Davis (EW+WW Dec. '94) asserts, there is usually no conspiracy to suppress heretical

views. There is no need of one, except in some specific instances, because as Charles McCutcheon wrote in the *New Scientist* (itself a notorious suppressor, but not as bad as *Nature*) on 29 April 1976, p225, "An evolved conspiracy" suffices. For example, I ran into a discussion in the interval at the Royal Institution seminar to celebrate the centenary of the Michaelson-Morley experiment. An American who was setting up an international conference on relativity discussed with one of the lecturers whether ether buffs should be suppressed at that conference. He

also asked the lecturer how Harold Aspden should be dealt with. They concluded that if Ether believers kept to Establishment mathematics, they should be allowed to put their case.

The American told me he regarded heresy in science much as he regarded heresy in religion. More generally, suppression in science results from fear that a new idea will disrupt the normal, calm progression of academic career progress and research funding.

Suppression is the norm rather than the exception. Even Maddox, editor of *Nature*, now says he is worried!

With his track record, that is mind-blowing. Scientists have successfully resorted to false authorship and false addresses to get into *Nature*.

The most interesting and most destructive aspect is the pandemic suppression of advances relating to the AIDS epidemic. Other experts, whose names I can supply, specialise in the allied subject of fraud in science. Stewart and Feder lead this field.

My first publication on suppression in science was 'The Rise and Fall of Bodies of Knowledge', published in *The Information Scientist* No 12 (4)

Dec. 1978, pp. 137-144, where I discuss some of the cases of suppression which litter science. My article was re-published in my book 'Electromagnetic Theory vol 1', 1979, p. 117. All of the content of that book is suppressed, including the point that I raised at the Michaelson-Morley centenary seminar, asking about the apparent paradox in their experiment that although Michaelson-Morley pre-date wave/particle dualism, both wave and particle have to be assumed at different stages in the experiment to suppress anomalies.

Sine waves – another turn

I see from the March issue of *EW+WW*, p. 215, that Ian Hickman has kindly accepted my challenge for an explanation of how sinewaves appear across an *LC* circuit from an applied step function of voltage.

In his case he prefers to use a very short and theoretically extremely high pulse of voltage from a generator with an extremely high internal resistance. He then proceeds with some high powered computer analysis and calculations which I do not understand at all. In fact, Ian admits that he may well be "simply solving the differential equations by stealth".

I agree, of course, that the terminal voltage across an inductor is proportional to the rate of change of magnetic flux linkage, and therefore current, within it. I also agree that the current through a capacitor is proportional to the rate of change of electric flux, ϕ_C , within it. This is in turn proportional to the rate of change of charge, q_C , across it. We may need to know, though, more about the Ether before we can fully explain these fluxes.

In the meantime however we can simply write the following equations. Voltage across inductor *L* is:

$$V_L = L \frac{d\phi_L}{dt} = L \frac{di_L}{dt}$$

where ϕ_L is flux in the inductor, i_L is inductor current, d/dt is rate of change. Voltage across capacitor *C* is:

$$V_C = \frac{q_C}{C}$$

so,

$$\frac{dq_C}{dt} = C \frac{dV_C}{dt} + C \frac{d\phi_C}{dt} = i_C$$

where ϕ_C is electric flux within the capacitor, and is proportional to the amount of charge, q_C , on it.

From these equations you can produce a second order differential equation whose solution is a sine function. I have discovered though that at the initiation of the oscillation, the rising voltage across the capacitance is non-linear since a small proportion of the initial voltage step appears across the capacitor before the sine oscillation gets underway. This seems to suggest that the capacitor also must contain some inductance which initiates the sine oscillation, then proceeding by the fall of voltage across the inductor which produces back emf to charge the capacitor.

Textbooks such as 'An Introduction to Electronics' by Dennis F Shaw, p 18, say though that initial voltage across the capacitor is zero, but I have found this not to be the case.

I conclude that simple mathematical analysis as outlined above gives the only explanation we can have at present for the waveforms produced. The exception is the initiation waveform across the capacitor, which is non-linear, containing a discontinuity.

Peter Dawe
Oxford

Ian replies:

On Mr Dawe's own analysis, there cannot be an instantaneous voltage step across an ideal capacitor, unless, that is, an infinite current flows – which was precisely the case with the delta function in Ref. 1. If Mr Dawe really seems to see an 'instantaneous' voltage step across the capacitor in his circuit, there is a limited number of possible explanations: i) the capacitor possesses significant series loss (possible, but unlikely, ii) The capacitor possesses significant inductance (as Mr Dawe himself suggests, was it a capacitor rated for pulse operation?), iii) The rise in voltage was not really instantaneous or, iv) There is a measurement error (it was not


clear how Mr Dawe was measuring the voltage across the capacitor, which – from the diagrams – had neither end grounded.)

Analysis of the operation of his circuit is complicated by the fact that his 'step function' recurred, with alternating polarity, every 5ms; i.e. it was actually a 100Hz squarewave, while the resonant frequency of the tuned circuit to which it was applied was observed to be only some thirty times higher (approximately), with an unspecified *Q*. Furthermore, far from being instantaneous, the rise time of the 'step function' from zero to +4V was 50µs – around one sixth of the period of the tuned circuit's natural frequency.

A solution of the circuit's response to the given stimulation is straightforward, but could not be undertaken without exact values for the complex impedances of the components used. For example, the iron cored inductor doubtless had significant iron and copper loss in addition to its self capacitance. (The values of *L* and *C* – 0.0016µF and 5H – which Mr Dawe gives do not tally even approximately with his observed natural frequency of around 3kHz). The observed voltage step across the capacitor is probably due to the division of the applied step between the said 0.0016µF capacitor and the self capacitance of the inductor.

As the stimulus is a simple recurrent waveform, the circuit could be analysed in either the time or frequency domain though of course both analyses could give the same result. However, one important point is perhaps made clear more easily by consideration in the frequency domain. The squarewave drive signal will have significant harmonics up to the resonant frequency of the tuned circuit. If the tuned circuit has a high *Q* and resonates exactly at one of these harmonics, there will be no phase changes in the damped oscillatory response, only magnitude changes. However, slight mistuning either side of the harmonic can result in dramatic changes in the response, as was illustrated with actual measurements in Ref. 2. If, on the other hand, the circuit *Q* is so low that the response to one edge of the squarewave dies away completely before arrival of the next, then analysis of the effect of an isolated quasi-step function with a finite rise-time would give the complete solution. Either way, there is no need to invoke unknown effects of the Ether to explain the observed results.

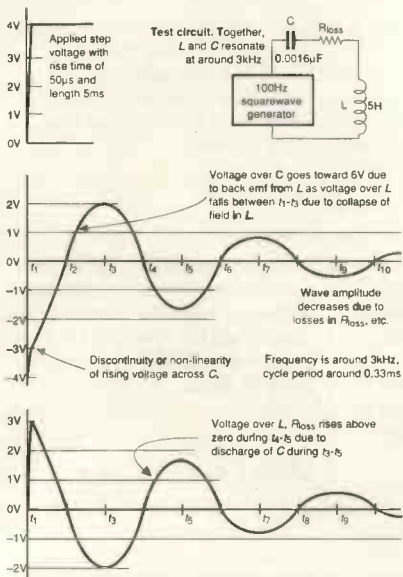1. Hickman, I, Sinewaves step by step, *EW+WW* March 1995, p. 215.
2. Hickman, I, Integrated creativity, *EW+WW* Jan. 1992, pp. 40-42.



"Apart from the initiation waveform, which is non-linear and has a discontinuity, this waveform is explained by the mathematical analysis shown."

It appears to me that for the experiment to have any value, the light must act as particles during its travel, because parallel waves would interfere with each other and ruin the experiment; but it has to act as waves on arrival in order to determine transit time difference by interference fringes. In the Michaelson-Morley centenary seminar, speaker Professor Kilminster said, "That has never been mentioned before". It has never been mentioned since – being suppressed for good reason.

To raise such questions, and there are many, is cheating, like making your pawn move as a combination of knight and bishop in a chess match. Science today is the manipulation of pre-agreed axioms and old knowledge; nothing more. Further, the request for more detailed statements of the axioms, as in my case with Michaelson-Morley, is resisted to the death. Today's science resembles the religious service, which should not be interrupted by the raising of theological questions.

My work on wafer-scale integration, described in *Wireless World* July 1981, was always rejected for publication by all learned journals, even though it attracted £16m of funding – including government funding – and became a widely praised product in the field. Of course, its suppression reduced the threat that it would upset the research funding being received in their universities by journal referees for their own approaches to WSI. In spite of my track record, my new WSI invention, *EW+WW* March 1989, for which I have worldwide patents, cannot be published in any learned journal.

In a letter in *Wireless World*, January 1983, I wrote that during 25 years of work, I have never succeeded in publishing any of my work on e-m theory in any British learned journal. This ban now extends to 35 years. However, Davis should particularly think about the refusal of the Establishment, when approached, to clarify the classical theory they are defending. Professor M Pepper FRS and his boss Professor A Howie FRS, head of Cavendish Laboratories, disagree with each other² as to where the negative charge comes from in the Catt Anomaly, *EW+WW* Sep '87. They refuse either to discuss it with us or with each other, or to say that the matter is of no importance.

Not only are new theories ignored and suppressed. We also find that the Establishment is nonchalant about its contradictory versions of old theory. See also the co existing, hopelessly contradictory, versions of a TEM wave pointed out in 'The Heaviside Theory', *WW* July '79, which has been totally ignored.

Ivor Catt
St Albans

1 Maddox says that suppression is increasing. "The epoch making paper by Francis Crick and James Watson outlining the structure of DNA, which appeared in *Nature* in 1953, which 'probably not be publishable today', Mr Maddox laments..." – *Daily Telegraph*, 1 May '89, p. 18.

2 Howie says it comes from the west. Pepper says that (since electrons would have to travel at the speed of light) it cannot come from the west, and must come from the south. Until this is resolved, we do not have a classical theory. Before it can exist, a theory has to be stated

Lend a golden ear

I followed Doug Self's series – and the debate that followed – with interest. As some of the statements expressed by readers that do not share Mr. Self's approach to amplifier design appeared to me at best biased, it is not surprising that Mr Self has lost his patience in the Feb. '95 letters column. True, the subjectivists' arguments have been around long enough, without much concrete progress, but could it be that engineers and the 'golden eared' are simply not speaking the same language?

To illustrate, one of my grammar school colleagues, who later became a professional musician, was able to detect signal level differences of a fraction of a decibel consistently, even if the changed level was presented to him after several minutes of silence. His ability was discovered accidentally. One of my stereo amplifiers had a 20.9k Ω resistor on one input and a 22.3k Ω on the other while the preamp output impedance was 1k Ω , and he noticed a difference in output levels between channels. No need to mention, he was able to detect absolute pitch, too.

Six years ago I owned an Alfa Romeo Sprint Veloce which developed a rattling sound in its engine. It turned out to be a loose screw on the air filter cover, but the mechanic noticed a hissing above 3000rev/min. Two days later I returned to him with a broken main bearing.

We are able to identify a familiar voice on the 'phone almost immediately, in spite of the badly distorted and band-limited signal, even if we have not heard the voice for many years.

Most of us will readily accept these impressive examples of performance of the ear-brain combination as a normal every-day experience. But when it comes to hi-fi equipment, our opinions change.

When discussing amplifier and speaker performance with musicians, I have often experienced that when I was talking of amplifier bandwidth, I had in mind the standard half-power

definition, while they were referring to the frequency at which the phase is shifted by no more than a few degrees. When they were talking of clarity and presence, they were referring to being able to pin-point a sound source on the stereo image, while I was suspecting excessive 3 to 5kHz lift. When we were discussing transient performance, I was referring to the rise-time and overshoot of the response to a square-wave input, while they were referring to the attacking part of the complex waveform envelope which in most cases implied many waveform periods.

I'm certainly not advocating that audio engineers should rely on their ears only. But we should try to adopt the attribute of lawyers and doctors and listen carefully to what other people are saying before making a judgement. Indeed, we know the limitations of our instrumentation and we struggle hard to eliminate systematic errors when making sensitive measurements, so why not treat other people as sensitive instruments – albeit somewhat strange, sometimes unreliable ones?

Of course, the 'golden eared' must willingly accept being treated like instruments if they continue to seek credibility.

Erik Margan
Ljubljana
Slovenia

Supplies for audio power

I read with great interest the article 'Distortion off the rails' by D. Self in the March issue. While certainly not questioning Douglas' undoubted skills in audio amplifier design, may I draw attention to Douglas' statement, "I assume that any rail filtering arrangements will work with constant or increasing effectiveness as frequency increases; this is clearly true for resistor-capacitor filtering."

Taking as a base for availability the Famell catalogue, data from Philips' 1994 Data Handbook, and assuming an axial capacitor of 100 μ F at 40V or more, as in Douglas' Figs 2&3, then the Philips 021 and 031 styles will have a self inductance of 40–50nH and an esr of some 0.55 to 1.2 Ω at 10kHz, depending on exact choice. Also 47 μ F at 63V, depending on case size, can exhibit inductance up to 85nH.

Similar values of radial styles have less inductance, say 25nH. From Philips' data curves, these types have a self resonant frequency of around 20–50kHz. Above this they become totally inductive. Also at 100Hz, a typical esr of 1.25–2.5 Ω must be expected.

As Douglas states, the amplifier internal loop gains will be reducing at frequencies when the capacitor starts to become inductive.

My two questions for Douglas are: what effect would a capacitor having 100 μ F, 50nH, 1 Ω , as a series LCR, have on amplifier performance at 10kHz and above with regard to the simulation curves of Figs 2 & 3? Secondly, what effect would an esr of 2.5 Ω , as a series CR, have on modelling or measurements at 100Hz?

Cyril Bateman
Acle
Norfolk

Douglas replies:

Mr Bateman is of course completely correct in pointing out that capacitors have parasitic inductance and esr, and that this is ignored in my article, which used only pure capacitance in the simulations. However, a technical article is not a legal document; you cannot enumerate all the ifs and buts, and exceptions and caveats, without the prose becoming as uninformative as it would be unreadable. In this case, some of the concepts involved are not wholly straightforward (eg the change of reference in the voltage amplifier), and adding a further layer of complication simply to make the components more realistic would not have been a good idea.

The other point is that parasitic inductance, esr, etc, seem to make no difference in practice; ordinary electrolytics do the job very well. Ripple and signal voltages on the rails do not reach up into the rf regions, and even if they did, the series inductance of the supply conductors combined with the hf rail decoupling would reduce it. The only credible source of rf is commutation spikes in the bridge rectifier, and these need to be dealt with at source by the usual snubbing network.

Reflection on deflection

With reference to the piece 'Cathode-ray conundrum' in the April issue letters column, the proposition goes against provable laws of physics.

The effect described is of very small magnitude in relation to the others occurring at the same time – a potent source of error.

The flaw in Lerwill's proposition is that an electron beam which has been deflected off the precise axis of the acceleration system will have an effect in one or both of the orthogonal axes. There will be an electrostatic or electromagnetic interaction with the acceleration system, amounting exactly to the reaction which seems to have escaped – just too small to measure.

NPE Wheeler
Sutton,
Surrey

'OFF-AIR' FREQUENCY STANDARD



- Provides 10MHz, 5MHz & 1MHz
- Use it for calibrating equipment that relies on quartz crystals, TCXOs, VXCOS, oven crystals
- Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP — French eq to NPL)
- British designed and British manufactured
- Options available include enhanced receiver, sine wave outputs and 13MHz output for GSM. Prices on application.

Variants from
£195+VAT

Output frequencies –
10MHz, 5MHz, 1MHz
Short term stability – better
than 1×10^{-8} (1 sec)
Typical – 4×10^{-9} (1 sec)
Long term – tends to
 2×10^{-12} (1000 sec)

Call for 'Off-Air' Standard list

TEST EQUIPMENT

We are well known for our quality, new and used Test Equipment. Our list is extensive, the following will give some idea of our range and prices:

TIME 404S Precision mV source	£95	PHILIPS 5716 pulse generator	£495
TIME 2003N DCV Pot/Cat, 0-10V, null, etc	£249	FEEDBACK DPM609 10Hz-100Hz phase meter	£125
TIME 2004 DC Volt standard 0.005%	£945	FEEDBACK SSO603 1MHz sine/square oscillator	£125
HP134CA X-Y displays	£95	TEKTRONIC 2465 300MHz 4 trace, dual delay T/B	£1950
E.V. EV4020A NTSC V/scope	£395	TEKTRONIC 2215 60MHz dual trace, dual delay T/B	£450
LEADER LG398 NTSC pattern generator	£395	MARCONI TF2370 100MHz spectrum analyser	£995
PHILIPS 5509 PAL pattern generator	£195	DRAKE MN2700 ATU/PSU	£980
PHILIPS 5519 PAL pattern generator	£295	ADRETT 740A 0.1MHz-1.2GHz sig. gen. AM/FM/PM	£1450
PHILIPS PM5134 function generator	£1495		

Call for Equipment list

ONE ONLY OFFER

One only, mint condition VIDEO/COMPUTER PROJECTOR as used in AV theatres, and similar large screen or wall projection applications. Can be ceiling or bench mounted. This is a very high quality instrument, new price upwards of £10k, serious offers only.

HALCYON ELECTRONICS
423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 0181-542 6383. FAX 0181-542 0340

CIRCLE NO. 143 ON REPLY CARD

KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
27C64-15	2.00	1.45	628128LP-80	8.30	7.20
27C128-15	2.40	1.80	62256LP10	3.00	2.20
27C256-15	2.20	1.65	6264LP-10	2.10	1.40
27C512-15	2.20	1.65	MM58274CN	4.90	3.75
27C010-15	3.60	2.20	ULN2003A	0.43	0.25
27C020-15	6.00	3.99	LM555	0.30	0.18
27C040-15	8.60	6.45	MAX232	1.35	0.88
80C31-12	2.10	1.65	7406	0.35	0.23
80C32	3.00	2.40	7407	0.35	0.23
80C85ARS	2.90	2.30	74HCT244	0.35	0.27
8255AC-2	2.00	1.50	74HCT245	0.35	0.27
D8748H	4.30	3.35	74HCT373	0.35	0.26
D8749H	4.40	3.45	74HCT374	0.32	0.26

74LS, 74HC, 74HCT Series available

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

178 Brighton Road,
Purley, Surrey CR8 4HA
Tel: 0181-668 7522. Fax: 0181-668 4190.

CIRCLE NO. 144 ON REPLY CARD

TELFORD ELECTRONICS

HP 8750A Storage Normalizer	£350	Marconi TF2438 5.0MHz Universal counter/timer	£250	Racal HF Receiver RA219B consisting of RA2170 receiver and MA323 FSK loudspeaker terminating unit. Frequency range 1-30MHz. All mode reception	£275
HP 8553B Spectrum Analyzer plug-in 110MHz	£200	Marconi TF2016 AM FM 10Hz-110MHz Sig. generator	£170	Harris automatic antenna coupler 1.6-30MHz	£500
HP 8556A Spectrum Analyzer plug-in 300MHz	£200	Racal 9301A RF Millivoltmeter 10kHz-5110MHz	£225	Bird 43 Thru-line watt meter	£100
HP 59313A A/D converter	£250	Racal MA1720 Drive unit	£500	Rhode & Schwarz Q-2000MHz UHF attenuator 50ohm 0-140dB	£125
HP 11683A Range Calibrator	£250	Racal 9082 synthesized signal generator 1.5-520MHz	£480	Tektronix 454 150MHz Dual trace scope	£950
HP 8709B Synthesizer	£200	Racal Dana 9932 instrument interface	£120	Tektronix 453 100MHz Dual trace scope	£150
HP 3406A Broadband sampling voltmeter	£150	Racal Dana 9915M frequency meter 10Hz-520MHz (fitted FX Standard)	£125	Tektronix 475 200MHz Delay sweep/dual trace	£450
HP 5150A Thermal printer	£150	Racal Dana 9904 universal counter/timer 50MHz	£100	Tektronix 465 100MHz Delay sweep/dual trace	£375
HP 3400A RMS Voltmeter 10MHz	£115	Racal Dana 9300 RMS voltmeter	£250	Tektronix 2215A 60MHz delay sweep/dual trace	£375
HP 483A Microwave amplifier 1-2GHz	£275	Racal Dana 5001 digital multimeter	£300	Tektronix 7854 c/w 7511 plug-in/7111 fitted with S1 sampling heads - 1GHz	£1600
HP 491C Microwave amplifier 2-4GHz	£275	Racal Dana 5002 logic state analyzer	£300	Tektronix 492 spectrum analyser 50MHz-18GHz	£4500
HP 4204A Oscillator 10Hz-1MHz	£150	Racal Dana 205 logic state analyzer	£300	Tektronix curve tracer 577	£750
HP 8443A Tracking Generator/counter	£400	Racal Dana 4800 Digital voltmeter	£50	Crotech 3131 15MHz Dual trace scope	£125
HP 8755 Sweep amplitude analyzer c/w heads	£750	Racal Dana 9904M 50MHz counter/timer	£100	Gould DS250A 15MHz Dual trace scope	£120
HP Spectrum analyzer 1821 main frame c/w 8558B plug-in 100kHz-1.5GHz c/w HP 8750A Storage normalizer	£2,000	Racal Dana 9914 VHF Frequency counter 10Hz-200MHz (fitted FX standard)	£125	Gould DS255 15MHz Dual trace scope	£120
HP1740A 100MHz Dual trace storage scope	£325	Racal Dana 1992 Universal counter 1.3GHz	£700	Gould DS300 20MHz Dual trace scope	£175
HP1741A 100MHz Dual trace storage scope	£340	Racal 9104 RF power meter	£125	Gould DS3500 60MHz Dual trace scope	£200
HP1742A 100MHz Dual trace storage scope	£350	Racal instrument recorder store 7DS	£500	Gould DS3600 100MHz Dual trace scope	£275
HP1804 100MHz Dual trace scope	£175	Philips PM7632 SWR meter	£175	Gould 13B 10Hz-100kHz LF Oscillator	£150
HP1201B 500kHz Dual trace scope	£125	Philips PM 7841 power meter	£125	SE LABS 111 18MHz Dual trace scope	£85
HP5004A Signature Analyser	£200	Philips PM5132 function generator 0.1Hz-2MHz NEW	£350	Telegquipment D1011R 10MHz Dual trace scope	£75
HP3707B Telephone line analyser	£400	Philips PM3055 50MHz Dual trace scope	£600	Telegquipment DM63 50MHz 4 trace storage scope	£150
HP8405A Vector voltmeter 1MHz-1000MHz	£250	Philips PM3262 100MHz Dual trace scope	£250	Telegquipment DM64 10MHz Dual trace scope	£75
HP419C DC null voltmeter	£150	Philips PM5715 Pulse Generator 1Hz-50MHz	£750	Tylo CS1566A 20MHz Dual trace scope	£150
HP435A power meter c/w HP8481A	£750	Philips PM5508 Colour TV pattern generator	£450	CDU150 35MHz delay timebase scope	£95
HP432A power meter c/w HP478A	£280	Philips SWR meter PM782	£400	Kemo phase meter DP1	£95
HP432A c/w HP485 26.5-400Hz waveguide	£500	Farnell P.S.U. TSV70 Mk11 0-35V/0-10A +70V/0-5A	£250	Siemens 7X84303 Wattmeter	£300
HP8290B DC PSU 0-320V/0-0.1A	£75	Wayne Kerr auto balance universal B642	£200	Radiometer AFM3B mod. meter	£300
HP6291A CD PSU 0-40V/0.5A	£100	Wayne Kerr universal bridge B224	£200	Aval 8559 500V variable frequency converter	£800
HP6111A CD PSU 0-20V/0.1A	£70	Wayne Kerr component meter B424/N resistance/capacitance/inductance	£195	Avo RM215-F/T insulation resistance and breakdown tester	£250
HP2911A Selective voltmeter	£125	Norma precision wattmeter D4155	£350	Pegelmesser 200Hz-620kHz model D2155	£500
HP3568B Selective level meter	£800	Norma multi function meter D4135A	£300	Fluke 8000A Digital multimeter	£45
HP342A Microwave frequency counter 18GHz	£1400	Norma Model D5155 AC power analyser	£800	Time CD Millivolt pot source Model 404N c/w DC current source Model 505	£1200
HP5308A 75MHz Time counter	£100	EIP S75 source locking microwave counter opt. 02.04 10Hz-18GHz	£1,850	Nagra T instrumentation tape recorder	£700
HP5305A 1100MHz counter	£275	Syston Donner 6054B microwave counter 20Hz-18GHz	£250	Datron 1061A Autocal digital multi meter True RMS AC/Current	£700
HP8654B signal generator 10MHz-520MHz	£400	Thandar TA2160 20MHz logic state analyser	£250	Datron 1051 Multifunction meter	£65
HP8654A signal generator 10kHz-520MHz	£350	Schlumberger 7055 microprocessor volt meter	£50	Datron 1055 DC Voltmeter	£65
Marconi TF21635 UHF attenuator DC 1GHz	£100	Schlumberger 4200 Digital voltmeter	£50	Datron 1030A RMS Voltmeter	£65
Marconi TF2162 Step attenuator DC-1MHz	£60	Schlumberger 4220 Digital voltmeter	£50	Datron 1030 RMS Voltmeter	£65
Marconi TF2015 AM/FM signal generator 10MHz-520MHz	£165	Schlumberger 7055 Microprocessor voltmeter	£250	Leader LCR Bridge LCR resistance/capacitance/inductance D, Q measuring range: 9V operation	£150
Marconi TF2016 AM/FM signal generator 10kHz-120MHz	£165	Wavelek 20MHz sweep modulation/generator type 193	£300	Haven temperature calibrator DTB5 oil/water bath	£500
Marconi TF2700 Universal Bridge (Battery op.)	£125	Wavelek 3000 Sig. generator 1-520MHz	£300	Haven thermal i.s. thermocouple simulator/calibrator	£60
Marconi TF2008 AM/FM signal generator 10kHz-520MHz	£300	Wavelek Sweep generator Model 164 30MHz	£500	Avo 8 Mk 5 + 6 c/w case, leads, prods etc. (c/w cal cert. NPL)	From £85
Marconi TF2370 Spectrum analyser 30Hz-110MHz	£890	Rediffon synthesized R1001 15kHz-30MHz all modes	£750	Avo CT160 valve tester c/w valve data book	£75
Marconi signal source 6058A 12-18MHz c/w levelling amp. 6587	£215	Rediffon R500 Band New (back ltr) HF	£750		
Marconi signal source 6058B 8-12.5GHz c/w levelling amp. 6587	£215	Rediffon VLF/AF (in current use with Royal Navy Submarines)	£750		
Marconi TF2303 FM/AM Mod. meter	£225				
Marconi TF2604 Electronic voltmeter	£45				
Marconi TF2431 200MHz Digital frequency meter	£150				

AN EXTENSIVE RANGE OF TEST EQUIPMENT IS AVAILABLE. PLEASE SEND FOR OUR NEW CATALOGUE
Postage and packing must be added. Please phone for price. VAT @ 17½% to be added to all orders. Please send large SAE for details.

Telford Electronics, Old Officers Mess, Hoo Farm, Humbers Lane, Horton, Telford TF6 6DJ
Tel: 01952 605451 Fax: 01952 677978

CIRCLE NO. 145 ON REPLY CARD

NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

ACTIVE

Discrete active devices

Little mosfets. Meant for use on PCMCIA cards, Micrel's *MIC94030/1 TinyFETs* boast the lowest on resistance for their size, at 1 Ω and 3.3V, and are contained in SOT-143 packages, being only a quarter of the size of current 8-pin SOIC mosfets. *MIC94030* is a basic 4-lead p-channel device, while the *MIC94031* has an internal gate pull-up resistor to turn the device off when driven by tri-state or open-drain logic. Solid State Supplies Ltd. Tel., 01892 836836; fax, 01892 837837.

Digital signal processors

NEC's *μ PD7701X* family of general-purpose dsp chips has a new member with larger memory, the 3V

μ PD77018, which handles up to 250 million operations per second. Memory is 256 by 32 bit instruction ram and 24K by 32 bit rom, data memory consisting of two blocks of 3K by 16 bit ram and two blocks of 12K by 16 bit rom. The device has a 30ns instruction cycle time, a three-stage pipeline architecture and its instruction set enables eight operations to be performed in parallel. Development tools available operate through a workbench under Windows. NEC Electronics (UK) Ltd. Tel., 01908 691133; fax, 01908 670290.

Floating-point DSP. TI's latest digital processor, the *TMS320C32*, allows the use of floating-point techniques used for research and development in commercial products to eliminate the usual switch to fixed-point working for commercial use. It is available in 40MHz, 50MHz and 60MHz versions and uses new memory management and data packing features to allow the flexible use of 8-bit, 16-bit and 3-bit memory architecture. There is also a two-channel dma co-processor for data movement. SR Communications (Texas Instruments). Tel., 0181 692 7575; fax, 0181 692 8057.

Logic

3.3V logic devices. Quality Semiconductor announces seven 3.3V, 8bit logic elements, the *FCT3244* buffer/line driver, *FCT3245* transceiver, *FCT3373* buffered latch, *CT3240* inverting buffer, *FCT3540* flow-through inverting buffer, *FCT3541* flow-through buffer and *FCT3573* flow-through latch. They are all function and pin compatible with existing 5V devices and will accept 5V inputs while the outputs are at 3.3V. Speed is compatible with Bicmos and power consumption with cmos. Quality Semiconductor, Inc. Tel., 01420 563333; fax, 01420 561142

Memory chips

Low-voltage serial eeprom. New from Holtek of Taiwan, via Hero Electronics, is the *HT93LC46* 1Kbit serial eeprom, to which one can write to at 2.7V and read from at 2V. Operating current is 2mA and maximum standby 2 μ A. Data is retained for ten years. Hero Electronics Ltd. Tel., 01525 405015; fax, 01525 402383.

Mixed-signal ICs

Energy measurement. A range of five ICs from the South African firm of

SAMES are for single and three phase ac power or energy measurement over a 60dB range, meeting the requirements of IEC 521/1036 for Class 1 ac watt-hour meters. They are protected against overvoltage and use shunt resistors or current transformers for current sensing, a voltage reference being built in. Output is either digital or analogue in form. Ginsbury (UK) Ltd. Tel., 01634 290903; fax, 01634 290904.

Optical devices

Laser measurement. Matsushita's *LM200* analogue laser is immune to surface irregularities and colour changes. This is because of its use of light feedback and triangulation range measurement to minimise analogue output error. An aspherical glass lens provides good linearity combined with low temperature drift. The measurement range is ± 3 mm or ± 6 mm while resolution is 1 μ m. Matsushita Automation Controls Ltd. Tel., 01908 231555; fax, 01908 231599.

Fibre pigtailed laser diodes. A series of diode laser assemblies designed to couple laser radiation into single and multi mode fibres is available from Melles Griot. Both visible and infrared diodes are used, the >700 nm infra-red types being over 55% efficient and the <700 nm visible diodes better than 30% efficient. Powers from 0.5mW to 30mW are offered. The housing is stainless steel and has a 1m length of fibre with a cleaved end, ST, FC and SC connectors being used. Melles Griot Ltd. Tel., 01223 420071; fax, 01223 425310.

Programmable logic arrays

Fast 128-cell device. AMD has brought out what it claims to be the fastest 128-macrocell complex programmable logic device, the *MACH231*. This is one of the new *Performance Plus* family of 7.5ns complex plds. The addition of power-down macrocells means that each macrocell can be configured into a low-power mode. Additionally, input/outputs and inputs have a latching facility to avoid the long pull-up times associated with resistors. Advanced Micro Devices (UK) Ltd. Tel., 01483 740440; fax, 01483 756196.



Oscillators

3.3V crystal oscillator. Q-Tech has a range of military-grade crystal clock oscillators, believed to be the first 3.3V types to operate over a -55°C to 125°C temperature range while preserving ± 100 ppm stability. Output is at logic level into 15pF with transient times of 3ns. Many package styles are available. Wavelength Electronics Ltd. Tel., 01843 602869; fax, 01843 862276.

PASSIVE

Passive components

Low-voltage tantalum. Low-voltage *Series* surface-mounted tantalum capacitors by AVX are rated at 2-10V and are meant for use in products needing 1.5-5V supplies. Packaging is of 1.2mm profile. AVX Ltd. Tel., 01252 770000; fax, 01252 770001.

Audio products

Audio codec. Crystal Semiconductor announces the *CS4225*, a multi-channel audio codec for automotive and surround-sound application, which replaces three stereo data

NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

converters, three volume-control ICs, an input multiplexer, a 12-bit a-to-d converter and numerous passive components, not to mention affording a reduction size over conventional equipment of around 90%. An on-board phase-locked loop generates clock pulses to reduce EMI. Crystal Semiconductor Corporation. Tel., (USA) 00 512 442 7555; fax, 00 512 445 7581.

Connectors and cabling

Board/board connector. Wieland pluggable board-to-board connector with 2-16 ways on a 5.08mm pitch is rated at 250V to VDE 0110 GR C and 10A. The female socket can be

mounted vertically or at right angles to provide connection for daughter boards. Wieland Electric Ltd. Tel., 01483 31213; fax, 01483 505029.

PCMCIA SM connectors. Methode MCFK Types I, II and III surface-mounting connector frame kits snap together without the assistance of glue or any other fixative. The connectors have stainless-steel covering, UL94V0 rating and electrical grounding via spring tabs. Surtech Interconnection Ltd. Tel., 01256 51221; fax, 01256 471180.


Bendy coax. From Belden comes *Conformable Coax*, an alternative to semi-rigid coaxial cable that can be hand manipulated into curves with radii down to 3.18mm, retaining its shape when formed. There are two types of microwave cable, 1671A RG-405 type of 0.085in outside diameter and 1673A (RG-402) of 0.138in od, both with 50Ω impedance. Type 1672A is for video at 75Ω, having an od of 0.087in. Cables can be flexed many times without damage. Belden UK Ltd. Tel., 01483 726818; fax, 01483 771569.

IDC connector.

Insulation-displacement connector blocks used by *Mod-Tap* in voice and data equipment are now available to network users. The blocks are designed for pcb mounting and can be used in wall sockets or patch panels. Termination tools are offered, but standard tools can be used. Blocks take two-pair and four-pair combinations and are in blue/orange, green/brown or in custom colour codes. MOD-TAP Ltd. Tel., 01703 701919; fax, 01703 704063.

Displays

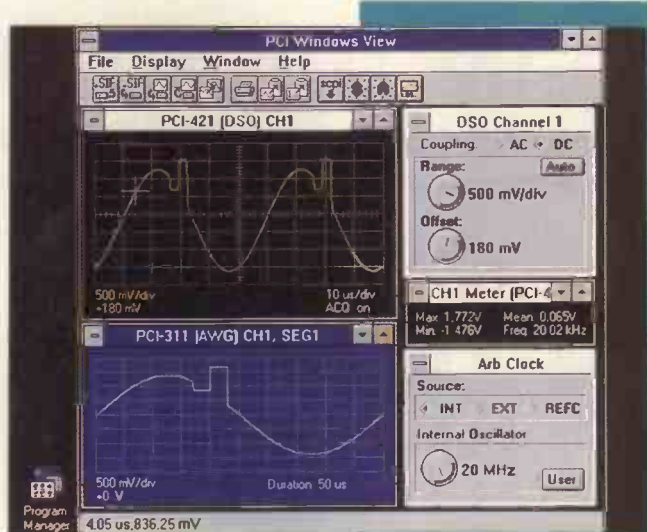Tft colour lcs. Ginsbury's *GE10* and *GE14* 10in and 14in thin-film transistor colour lc displays are said to give a stable image with no flicker. They may be driven by a dedicated graphics card for best quality or by an internal analogue card to emulate crt monitors. As an option, a capacitive touch screen can be fitted, RS232



and Windows mouse emulation is standard. A robust polystyrene enclosure suits industrial use and can be fully IP65 sealed on request. Ginsbury (UK) Ltd. Tel., 01634 290903; fax, 01634 290904

Filters

Programmable video filter.

Raytheon's *RC6601* is an integrated continuous-time filter, fully programmable for video filtering, antialiasing, comms filtering and hdtv use. In addition, it costs about half as much as analogue filter alternatives. Cut-off frequency is voltage-variable in the 1 to 10MHz range and the device is phase-corrected to 0.2°; differential gain is 0.25%. It meets CCIR601 for NTSC and Pal signals, providing ±0.25dB pass-band ripple to 5.5MHz, with a -40dB pass-band starting at 8MHz. Ambar Components Ltd. Tel., 01844 261144; fax, 01844 261789.

Rf filters. Filters in the *BTF* range from BLP Components are for use in the protection of telephone networks, being flexible to accommodate future requirements, conforming to MIL-STD-220A and usable in all Tempest-rated networks as well as low-current control circuitry and audio lines. Configurations include two, four and ten line stand-alone forms and ten-line modules to fit 50, 100 and 200 line cabinets. They are in steel cases and are provided with idc connectors. BLP Components Ltd. Tel., 01638 665161; fax, 01638 660718.

Hardware

Control knobs. Attractive knobs in Sifam's *Trio* range are made using a technique whereby three shots of material are injected into the mould, providing a more versatile design and the opportunity for more detailed colour-coding. Material is nylon, with a matt body and contrasting gloss pointer. Two 11mm-diameter versions are made, with and without a nut cover, taking shafts up to 6mm diameter. The three-shot facility is


also offered to customers needing custom-designed knobs, for which designs can be accepted in electronic form. Sifam Ltd. Tel., 01803 613822; fax, 01803 613926.

Waveform generator. Taking the form of a pc expansion board, the Scensys *PCI-311/2* occupy one slot and perform the functions of a stand-alone generator but rather more conveniently. Output from each channel is 12Vpk-pk into 50Ω from 12bit a-to-d converters with update rates to 50Msample/s to 0.01% frequency tolerance. A 99-segment waveform memory, each segment of which holding one waveform, allows the creation of irregular shapes such as video test patterns and encoded communications signals using *BenchTop* or *BenchCom* software, importing them from maths programs or from an oscilloscope card. Scensys Scientific & Engineering Systems Ltd. Tel., 01296 397676; fax, 01296 397878.

also offered to customers needing custom-designed knobs, for which designs can be accepted in electronic form. Sifam Ltd. Tel., 01803 613822; fax, 01803 613926.

Instrumentation

Function generators. First members of Vann Draper's *H6000* series of function generators are the *H6000* and *H6001*, which produce sine, square, triangle, pulse and sawtooth outputs in the frequency ranges 0.1Hz-10MHz (*H6000*) and 0.2Hz-20MHz, prices being £149/199. Both allow external frequency control for modulation, sweep and pulse modulation. Outputs are tti and 50Ω, with 600Ω as an option, controlled by switched attenuator and a continuous control. Thd is under 1% and triangular wave linearity better than 99%. Vann Draper Electronics Ltd. Tel., 0116 2813091; fax, 0116 2570893

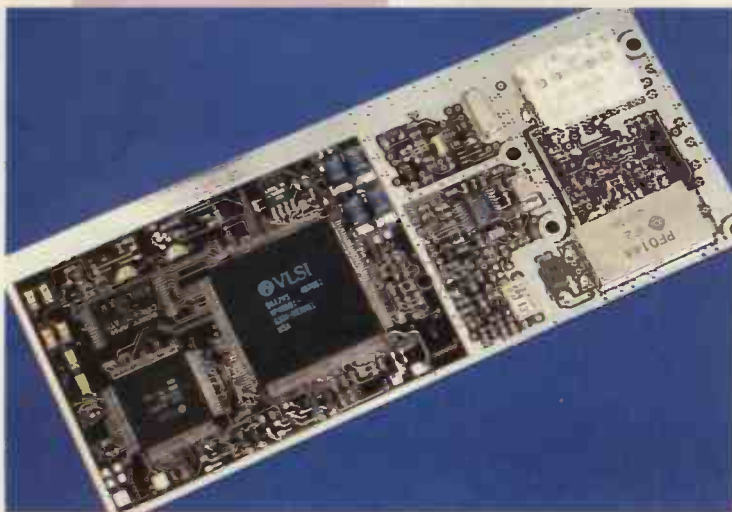

Please quote "Electronics World + Wireless World" when seeking further information

CPC – components. A new circa 1600-page catalogue from CPC – a company said to be UK's leading specialist spares distributor – is now available. Products carried include batteries, cables, capacitors, connectors, power supplies and semiconductors. This A4 publication also features industrial and office equipment, and, of course, a multitude of spares for consumer, office and industrial electronic equipment. CPC plc, Tel., 01772 654455, fax 01772 654466.



ELECTRONIC COMPONENTS CATALOGUE

Digital video analyser. Rohde & Schwarz's *Video Component Analyser* is a video analyser and waveform monitor in one case, and said to be the first wholly digital instrument of its kind. Measurement of analogue television waveform monitors is combined with new functions to allow monitoring of digital encoding and signal transmission, detecting errors in transmission, showing bit errors and checking sync frame. Features include the numeric dump function to allow video signals to be shown at bit level. Rohde & Schwarz UK Ltd. Tel., 01252 811377; fax, 01252 811447.

MIDI-Scope. Artistic Licence has the *MIDI-Scope*, a hand-held analyser for the Musical Instrument Digital Interface. When used as a receiver, the lcd screen shows data either in hex or as command icons, while received data can be stored for later analysis or re-transmission. The transmitter is used to regenerate received data or to transmit up to eight programmable messages. Other functions include cable testing, oscilloscope triggering and an RS485 output boost to drive long cables. Artistic Licence (UK) Ltd. Tel. and fax, 0181 863 4515.

Cable simulator. Designed to simulate the effect of up to 500m of coaxial cable on serial digital signals, Faraday's *Cable Clone* is a hand-held unit, requiring no other equipment, that is simply connected in the cable.


By means of eight switches, the effective cable length is increased in 5m steps until the signal deteriorates to an unacceptable point. The length of cable inserted indicates the margin. *Cable Clones* simulate amplitude and differential group delay of coax. with the SMPTE 267 360Mbit/s serial signal from 5MHz to 360MHz. Faraday Technology Ltd. Tel., 01782 661501; fax, 01782 630101.

Comms test set. H-P's *HP 8920B* communications test set has more than 22 functions to measure the performance of radio telephone equipment, including signal generator, modulation analyser, power meter, audio sources, digital oscilloscope, sinad meter, frequency meter and, as an option, a spectrum analyser with tracking generator. Measurement programmes are stored on a PCMCIA card. Hewlett-Packard Ltd. Tel., 01344 366666; fax, 01344 362269.

Nanovolt/micro-ohm meter. *HP 34420A* by Hewlett-Packard is a low-noise nanovolt-microohmmeter offering 7.5-digit resolution, 2ppm, 24-hour dc voltage accuracy and selectable filtering. There is a two-channel programmable scanner for ratio and difference measurement, and built-in conversion routines to display thermocouple, thermistor and rtd readings directly in degrees, resolved to 0.001°C. Features include scaling and statistics functions, 1024-reading memory, chart recorder analogue input, RS-232 and HP-IB interfaces and both SCPI and Keithley 181 programming languages. Hewlett-Packard Ltd. Tel., 01344 366666; fax, 01344 362269.

Direct recording oscilloscope. Gould's *DataSYS 765* dr oscilloscope

Conductive greases. Two types of grease from *Planned Products* of Santa Cruz not only lubricate and protect against moisture, but provide electrical and thermal conduction to drain away static and provide grounding and to dissipate heat. *Circuit Works Conductive Grease 7100* for low-to-medium loads and speeds is a silicone grease containing silver for greatest conductivity, giving a typical resistivity of <0.01Ωcm and high thermal conductivity. It is stable over the -57 to 252°C temperature range. Unworked and worked penetrations are 210 and 250, with steel-on-steel wear of 1.5mm. The *7200 Carbon Conductive Grease* has <30Ωcm resistivity, with penetrations of 335 and 338, wear measuring 2mm. Both types are chemically inert, thermally stable and non-flammable. Intertronics Ltd. Tel., 01865 842842; fax, 01865 842172.

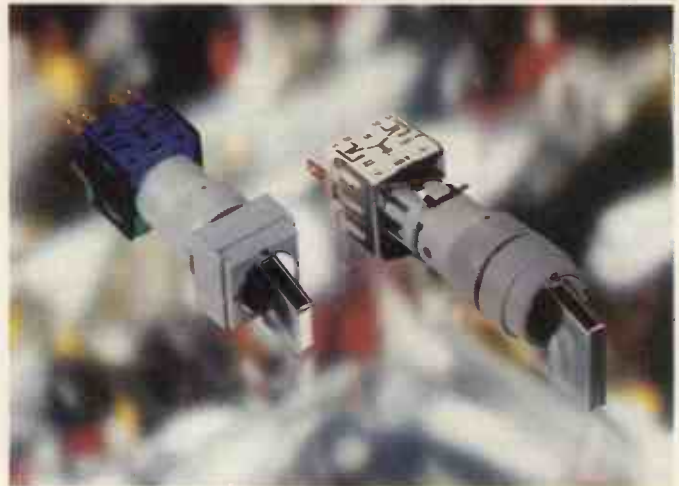

has a 500Mbyte hard-disk drive and handles direct data recording to disk at up to 250Kbyte/s with no dead time. Recordings can also be made to paper or recalled from disk to paper. As a 150MHz digital storage oscilloscope, the instrument offers 100Msample/s single-shot acquisition on four channels. Although the 765 captures glitches down to 10ns, the storage provided allows recording for a period of 230 days, recordings being displayed as though on a paper roll, but with more control. Gould Instrument Systems Ltd. Tel., 0181 500 1000; fax, 0181 501 0116.

Literature

SM oscillators. Surface-mounted crystals and oscillators by *M-tron* are now obtainable in the UK and are described in a new 40-page catalogue containing details of, among many other devices, crystals for use in extreme environments and oscillators for use as clock generators and in military application. Semi-Dice (UK) Ltd. Tel., 01494 488353; fax, 01494 771396.

RS Components. In its new catalogue, RS Components introduces over 200 new potentiometers from makers including Bourns, Meggit Piher and Spectrol. From Bourns, a 6mm, 0.5W pot. for machine adjustment and with a multi-wire wiper; by Meggit Piher, a series of 10mm, 150mW and 12mm, 200mW units with plug-in spindles and top or side adjusted edge wheels as options; and 12mm cermet pots by Spectrol rated at 1W and offering ±100ppm/°C temperature coefficient. RS Components Ltd. Tel., 01536 201234; fax, 01536 405678.

Batteries. Batteries by Univercell are described in a new loose-leaf brochure. The company, formed by a group of managers from Ever Ready, manufactures layer cell zinc-carbon types, NiCd, special packs using various types of cell and memory-protection NiCd batteries. It also undertakes packaging to order. Univercell Battery Company Ltd. Tel., 01952 580505; fax, 01952 680075.

Loughborough Sound Images. In

Modular switches. Lever switches in the Swiss *SwissTac* range of modular types are now obtainable in the UK. Virtually all elements of the switches are interchangeable, contacts at the rear remaining in the same plane when switches are block mounted. Since contacts can be removed from the switch, it is possible to carry out the wiring as a separate process. Switches are available in five sizes from 18mm diameter to 24mm square, in grey or black, the actuators being black or chromed. EAO-Highland Electronics Ltd. Tel., 01444 236600; fax, 01444 236641.

132 pages, LSI provides details of a comprehensive range of digital signal-processing hardware and software support for VMEbus, PCbus and SBus, and a product guide to equipment for industrial image processing and video multimedia. Loughborough Sound Images Ltd. Tel., 01509 634300; fax, 01509 634333.

Blue Micro. Blue Micro is IBM's representative company, dealing only in IBM products. On offer is the company's 20-page publication giving brief details of, for example, the *Blue Lightning 486* 32-bit microprocessor, the *Power PC* 64-bit and 32-bit risc processors and the *403GA* 32-bit risc embedded controller. Also covered are peripheral chips and sets, MPEG-2 decoding, memory and PCMCIA products. Free from Blue Micro Electronics. Tel., 01604 603310; fax, 01604 603320.

Materials

Insulation for semiconductors. *Thermalflex* tube by Warth is in a flexible plastic material designed to fit round semiconductor packages to allow them to meet higher flash test requirements while retaining good thermal performance. A 0.5mm wall takes most standard packages and grips the device for assembly. Tubes come in two sizes: 25mm long by

Please quote "Electronics World + Wireless World" when seeking further information

10mm wide for TO-220 packages and 30mm long by 13mm wide for TO-218/3P/247 and SOT-93. Catalogues and samples available. Warth International Ltd. Tel., 01342 315044; fax, 01342 312969.


Power supplies

Power-factor correction. XP has provided power-factor correction on its *ZX series* 350/550W power supplies to meet the requirements of EN61000-3-2 and EN55022 without increasing unit size, so that they can replace uncorrected supplies with no mechanical redesign. The psus are universal-input types covering the 2V-60V range of outputs. XP plc. Tel., 01734 845515; fax, 01734 843423.

Radio communications products

Vhf transmitter/exciter. *SU 125* from Rohde and Schwarz is said to be the first true vhf transmitter/exciter, as opposed to those that are simply modulators, with driver stages and add-ons. This contains in one case the stereo coder, modulator, rf amplifier, deviation meter, transmitter control and monitor, the latter two facilities allowing the unit to be combined with any fm amplifier. The microprocessor would then monitor, protect and control the amplifiers and exciter. Inputs include af and auxiliaries such as RDS and interfaces for remote control. It is usable as a stand-alone 20W transmitter or can be used with an R&S 600W vhf amplifier. Rohde & Schwarz UK Ltd. Tel., 01252 811377; fax, 01252 811447.

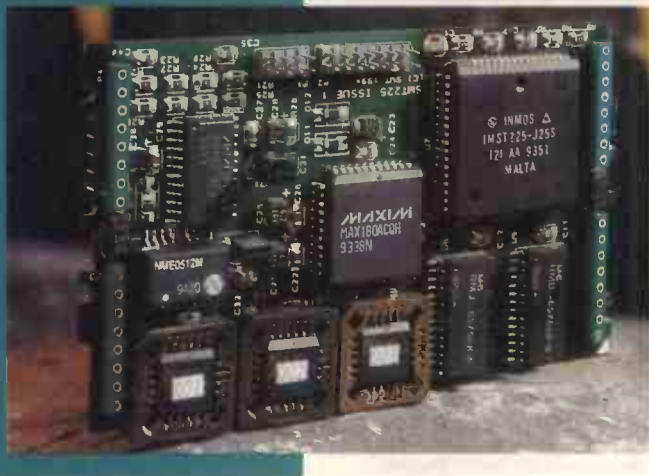Data converter interface. *SMT225* is a size 2 TRAM board (TRANputer Module in parallel processing systems) by Sundance that combines 12-bit d-to-a and a-to-d converters with a 25MHz transputer to provide a versatile interface for control. It is half the size of alternatives and about one-third the price. Sundance Multiprocessor Technology Ltd. Tel., 01494 431203; fax, 01494 726363.



Protection devices

3V transient protection. Protek's *SOT/SMDB* series of silicon avalanche transient voltage suppressors are expressly designed for 3V/3.3V use at up to 500W, protecting one or four unidirectional lines, being packaged in SOT-23 or SO-8 respectively. Theoretical response times are 8µs and 20µs. Hunter Electronic Components. Tel., 01628 75911; fax, 01628 75611.

Switches and relays

Power reed relays. *S series* vacuum reed relays made by Kilovac Corp. are high-voltage, high-power types for use at rf and with a mechanical life of 50 million operations. Voltage ratings are up to 10kV at 5A continuous, and the contacts switch 500W loads. Standard coils are 5V, 12V and 24V. LRE Relays + Electronics Ltd. Tel., 01962 734433; fax, 01962 734685.

Slow relay. With turn-on and turn-off times of 8.5ms and 4.1ms, Matsushita's *Soft-on/off PhotoMos* solid-state relay reduces the transients that occur when switching reactive or incandescent filament loads, thereby protecting itself and associated components; no other forms of transient protection are needed. Contacts handle 4A at 80V. Matsushita Automation Controls Ltd. Tel., 01908 231555; fax, 01908 231599.

Hf relays. *AK* and *RG* relays by Matsushita exhibit an insertion loss of 0.3dB at 900MHz and use only 200mW, or less when the optional latched type is driven by pulses. Contacts are single or double changeover and the footprint is 20.2mm by 11.2mm. Matsushita Automation Controls Ltd. Tel., 01908 231555; fax, 01908 231599.

Transducers and sensors

Low-pressure sensor. Higher sensitivity than is common, 100mV for 1lb/in² compared with around 50mV, is offered by IC Sensors' new board-mounted, temperature-compensated device in TO-8 or HIT packaging. Two ranges cover 0-0.03lb/in² and 0-1lb/in². Linearity (best fit straight line) is around 0.01% of span. Eurosens. Tel., 0171 405 6060; fax, 0171 405 2040.

COMPUTER

Vision systems

PCI-bus image capture. Image Technologies has the *IC-PCI* high-speed board offering 'plug-and-play' facility for image acquisition on the PCibus, direct-memory access being provided. Transfer rate is up to 80Mbyte/s directly to a PCI VGA card and acquisition rate to local memory up to 40Mbyte/s. DataCell. Tel., 01628 415415; fax, 01628 415400.

Computer board-level products

Single-board computer. Motorola's *68360* processor with on-board Ethernet and the *68060* make Syntel's *SYN-SBC5* single-board computer suited to both communications and control applications. It has a processing speed of 60Mips and possesses up to 32Mbyte of dram, 16Mbyte of flash eeprom and 2Mbyte of sram. There is a PCMCIA interface, a SCSI interface and an on-board 32-bit graphics controller supporting lcds, electroluminescent and crt displays. Syntel Microsystems. Tel., 01484 535101/2/3; fax, 01484 519363.

PC instrument control. National Instruments offers the *PC/104-GPIB*, an IEEE488 interface board for embedded pcs with *PC/104* expansion. It is compatible with NI's *AT-GPIB/TNT* plug-in interface and uses the *HS488* mode for GPIB transfers to 1.6Mbyte/s, enabling an embedded pc with the *PC/104-GPIB* to control, monitor and communicate with GPIB-based instruments. National Instruments UK. Tel., 01635 523545; fax, 01635 523154.

Computer systems

Single-chip PC core logic. NEC and Future Technology Devices collaborated to produce the *FTD 82C4591*, a single-chip device containing the core logic of a *386/486* pc-compatible embedded control system with bus speeds to 66MHz. It has ISA and VL-bus interfaces with programmable speed and only needs standard buffers for the ISA address lines. The device connects directly to an sram-based, direct mapped, bank interleaved cache, supporting write-back and through modes. Sunrise Electronics Ltd. Tel., 01908 263999; fax, 01908 263003.

PC-AT-compatible board. Arcom has a new PC-compatible single-board computer, the *VSCIM486DX*, using the 100MHz 486DX4 processor. A full VMEbus interface is complemented by ports to the SCIM mezzanine local expansion bus, the *Signal Conditioning Scheme* (SCIM), STBus and two memory expansion buses. It can be provided with 68Mbyte of dram, 256Kbyte of cache sram, 128Kbyte of battery-backed ram dual-ported to STBus and an accelerated SVGA graphics controller with 1Mbyte of ram; the chip incorporates a 32-bit maths

co-processor. Since the board runs dos and windows, software such as *LabView* is accessible. Arcom Control Systems Ltd. Tel., 01223 411200; fax, 01223 410457.

Industrial workstations. H-P's *HP9000* workstations are based on the company's *PA-RISC* processors running at up to 100MHz and supporting H-P's version of UNIX, HP-UX. Models *745i/50* and *745i/100* are the basic types with four EISA slots and 50MHz or 100MHz *PA-RISC* processors, while *747i/50* and *747i/100* have six VME slots and two EISA slots. XP plc. Tel., 01734 845515; fax, 01734 843423.

Data communications

Digital packet radio. *PackNet-2* by the Swedish company Radius is a vhf/uhf packet radio for remote control telemetry and data transfer, providing a link between the components of computer networks and control systems. Radio transceiver, microprocessor control and modem are combined in one box and a built-in repeater or external repeaters allow for extension of a network. *PackNet-2* offers both serial and parallel connection, a full RS-232-C interface being provided. Radius Telecommunications (UK) Ltd. Tel., 01256 469460; fax 01256 842362.

Multimedia

Installation diagnostics. Developed to assist those installing or upgrading pcs with multimedia hardware, Eurosoft's *CD-Check Diagnostic Disk* tests the installation and operation of cd drives, memory, sound cards and

Media accelerators. *BtV MediaStream* by Brooktree is first in a family of products combining hardware and software to allow a pc to take full advantage of the facilities offered by multimedia offerings. It is a three-chip set enabling dos games-compatible audio or digital sound, 1280 by 1024 graphics and 30frame/s, television-quality, full-motion video windows. *BtV MediaStream* is intended for use with add-on cards, 486 VL local-bus systems and the new PCI-based *Pentium* pcs, either on cards or on the motherboard. An important feature is the provision to output all-digital audio directly to consumer equipment with digital ports, such as DAT and cd players. The system produces high-quality graphics even when multiple windows run and good video lip-sync. at 30frame/s. It also supports standards such as the Microsoft MCI and DCI extensions under Windows and Microsoft's Plug-and-Play. Brooktree Ltd. Tel., 01252 811358; fax, 01252 811505

display, supplying a report on the results. It checks all system components to the Multimedia PC Council (MPC) standards. Eurosoft (UK) Ltd. Tel., 01202 297315; fax, 01202 558280.

Programming hardware

In-circuit programmer. In-circuit, board-level programming becomes necessary in military or other critical applications when ICs must be programmed after assembly, to ensure nothing happens to the data during soldering. Stag has produced the *ICP 9000* board-level programming system which reduces the need for extensive mechanical work in interfacing to the board and for complicated software where the board contains ICs other than eproms. With the *ICP 9000*, the only interface needed is a removable interface adaptor and the software can be written much more easily, by a technician, using a purpose-designed high-level language, so that boards not designed to accept ICP are able to benefit. A library of definition files further reduces the programming needed and facilitates the wrtling of programs for future requirements. The time taken for the process is said to be reduced from weeks to hours. Stag Programmers Ltd. Tel., 01707 332148; fax, 01707 371503.

Software

Interconnection analysis. *IPA 510 Interconnect Parameter Analyser* by Tektronix is an expansion of the earlier *IPA 310*. In essence, it models and verifies the interconnections of semiconductor devices on boards and even from the chip to the pins of packages. The system consists of a time-domain reflectometry oscilloscope and associated software. *IPA 510* will extract and verify Spice models, perform tdr and td transmission and execute network analysis, presenting true impedance diagrams of purely passive interconnections from zero to 12.5GHz and modelling energy through dissipation or coupling to effects on adjacent traces on the board. Interfaces for *Contec-Spice* and *P-Spice* are available and, since the system links measurement and Spice simulation, Spice models can be developed by extracting models from overlay of time-domain results. The oscilloscope used is an *11801B* and the software runs under Windows. Tektronix UK Ltd. Tel., 01628 486000; fax, 01628 474799.

Development tools. *TNT Embedded ToolSuite* by Phar Lap is a set of tools, running under dos or Windows, for the development of 32-bit embedded systems based on the Intel *386/486* family. It supports 32-bit C and C++ compilers from Borland, Microsoft and MetaWare. Facilities include the *TNT* embedded kernel, *Visual System*

Builder, a 32-bit linker/locator, embedded cross-debugging, C and C++ run-time libraries and a floating-point emulation library. Phar Lap Software Inc. Tel., 00 617 876-2972; fax, 00 617 661 1510.

Ice debugger for Windows. Nohau has introduced a Windows-based in-circuit emulator debugger for the *8051* emulator. The debugger uses an unlimited number of windows instead of the common single one, displaying data in up to 12 different forms simultaneously. In this way, the user can view at the same time C source code, disassembled code, data, assembler with comments and more. The debugger comes either as a package with the emulator or as a software update for existing users. Nohau UK Ltd. Tel., 01962 733140; fax, 01962 735408.

Fm noise analysis. The fm noise simulation package by Phasor Design includes the facility to determine bit error rate in digital communications systems from carrier-to-noise ratio and the ssb phase noise of oscillators, fm deviation, emphasis and noise weighting being included. It carries out numerical integration in the frequency domain to obtain s:n ratio, numerical summation of the amplitude distribution giving error probability to one bit. The package runs on a pc with a gui, and data files of system characteristics such as phase noise

and de-emphasis are included or can be written by the user. Phasor Design. Tel., 01858 432148; fax, 01858 432109.

Instrument-to-program translator. *SoftwareWedge* takes serial input data from measuring instruments fitted with RS-232, parses it and filters it to suit any application program running on a pc, as though the data were being typed in. In the other direction, keyboard and program instructions to the remote instruments are also translated into the correct form. Dos and Windows versions are available, the Windows version also supporting OS/2, NT and DDE. Kyle Data Service Ltd. Tel., 01292 311169; fax, 10292 318005.

Bare-board tester. *FIXpert* is a windows-based package to make drill patterns and test programs for the testing of unpopulated printed-circuit boards to design data. Since the 'known good board' approach is not used, the possibility of a fault being perpetuated is avoided. Drill files and their test programs are automatically produced and the whole process of creating the test routine from input to production of files and test program takes under an hour. Dense boards are 100% tested in two passes and double-sided boards are tested for side-to-side connectivity. Circuitest Ltd. Tel., 01903 218086; fax, 01903 218689.

FREE TO SUBSCRIBERS

Electronics World offers you the chance to advertise ABSOLUTELY FREE OF CHARGE!

Simply write your ad in the form below, using one word per box, up to a maximum of twenty words (remember to include your telephone number as one word). You must include your latest mailing label with your form, as this **free** offer applies to private subscribers only. Your ad will be placed in the first available issue.

This offer applies to private sales of electrical and electronic equipment only. Trade advertisers should call **Malcolm Wells on 0181-652 3620**

All adverts will be placed as soon as possible. However, we are unable to guarantee insertion dates. We regret that we are unable to enter into correspondence with readers using this service, we also reserve the right to reject adverts which do not fulfil the terms of this offer.

Please send your completed forms to: Free Classified Offer: Electronics World, L329, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

ELECTRONICS WORLD+WIRELESS WORLD May 1995

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

RECRUITMENT

ADVERTISEMENT AGENT REQUIRED

THE RADIO SOCIETY OF GREAT BRITAIN seeks to appoint an independent advertisement agent to handle the advertising space in its publications, principally the magazine *Radio Communication*.

Radio Communication is the UK's leading title targeting the licensed radio amateur. Published monthly and circulated to 31,000 members, it is a 100-page, A4 colour production carrying on average 30% of content as display and classified advertising pages.

Applications are sought solely from prospective agents with relevant experience and capability. It will be a significant advantage to be the holder of a current amateur radio licence or to have a practical knowledge of electronics terminology. This is not an opportunity to learn on the job!

The agency responsibilities will include:

- 1 Marketing of the space to the trade and agencies.
- 2 Production work, technical copy writing, layout and typography for trade setting or with own DTP system.
- 3 Page make-up, proofing, classifieds and setting-house liaison.
- 4 Administration of orders, schedules, charging out (via RSGB).
- 5 Provision of professional advice to the Society and an impartial complaints service to members and advertisers.

The agent will act independently on all routine matters but will be contracted as an agent in law. Remuneration will be by commission only. Applications will be considered from established professionals and those with the experience who may choose to take this opportunity to open a new and suitably financed venture.

Applications should be made in writing with an outline of relevant professional experience and supporting facilities. Total confidentiality will be observed. Marking your letter 'CONFIDENTIAL' please write to the General Manager at:



Radio Society of Great Britain

Lambda House, Cranborne Road, Potters Bar, Herts EN6 3JE

ARTICLES WANTED

WE WANT TO BUY !!

**IN VIEW OF THE EXTREMELY
RAPID CHANGE TAKING PLACE
IN THE ELECTRONICS
INDUSTRY, LARGE QUANTITIES
OF COMPONENTS BECOME
REDUNDANT. WE ARE CASH
PURCHASERS OF SUCH
MATERIALS AND WOULD
APPRECIATE A TELEPHONE
CALL OR A LIST IF AVAILABLE.
WE PAY TOP PRICES AND
COLLECT.**

R.HENSON LTD.

**21 Lodge Lane, N.Finchley,
London N12 8JG.**

5 Mins, from Tally Ho Corner.

TELEPHONE

081-445-2713/0749

FAX 081-445-5702.

VALVES

ELECTRONICS VALVES & SEMICONDUCTORS

Phone for a most
courteous quotation

We are one of the largest
stockists of valves etc,
in the U.K.

COLOMOR ELECTRONICS LTD

**170 Goldhawk Road,
London W12 8HJ
England.**

Tel: 0181 743 0899

Fax: 0181 749 3934

DISTRIBUTORS WANTED

DISTRIBUTOR INQUIRIES INVITED

Small, expanding manufacturer of
PC-based test and measuring
instrumentation wants aggressive
distributors in UK and Germany.

**Allison Technology
Corporation**

**8343 Carvel, Houston,
TX 77036 U.S.A.
Tel: 713-777 0401
Fax: 713-777-4746**

SERVICES

DESIGN SERVICES

Software Design: High and Low Level.
Hardware Design: Analogue, Digital,
Micro and Embedded.
PCB, Schematic and Production Drawings.
Prototyping and Feasibility services.

Archimedes Custom

Equipment: Tel 0974 282670

WANTED

High-end Test Equipment, only
brand names as Hewlett-Packard,
Tektronix, Rhode & Schwarz,
Marconi etc. Top prices paid.
Please send or fax your offer to:

HTB ELEKTRONIK

**Alter Apeler Weg 5,
27619 Schiffdorf, West Germany**

TEL: 01049 4706 7044

FAX: 01049 4706 7049

BBC COMPUTERS and/or software
needed by Nanhurst School and chil-
dren's hospital. Please donate
unwanted kit. Ring Douglas Hainline
on 0483 275121

WANTED

High-end Test, Communication &
Computer Equipment. **Top prices paid.**

Please send or fax your offer to:

**Steigerwald GmbH
Neusserstrasse 9, 80807 Munich
South Germany
Tel: 01049 89 3615833
Fax: 01049 89 3615899**

WANTED

Test equipment, receivers, valves,
transmitters, components, cable
and electronic scrap and quantity.
Prompt service and cash.

**M & B RADIO
86 Bishopgate Street,
Leeds LS1 4BB
Tel: 0532 435649
Fax: 0532 426881**

9956

PURCHASE FOR CASH

SURPLUS - OBSOLETE - REDUNDANT - EXCESS stocks of
electronic, electrical components/accessories, part processed and/or
finished products. Please submit preliminary information or lists for
immediate response to:

**K.B. COMPONENTS, 21 Playle Chase, Gt Totham,
Maldon, Essex CM9 8UT
Telephone 0621-893204. Facsimile 0621-893180.**

CLASSIFIED

TEL 0181 652 3620

FAX 0181 652 8956

ARTICLES FOR SALE



Cooke International SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS,
VOLTMETERS, GENERATORS, OSCILLOSCOPES,
POWER METERS, ETC. **ALWAYS AVAILABLE**

ORIGINAL SERVICE MANUALS FOR SALE
COPIES ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME,
SEND LARGE "A3" S.A.E. + 50P POSTAGE FOR LISTS
OF EQUIPMENT AND MANUALS.

ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY-FRIDAY 9AM-5PM

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0EB

Tel: (+44) 01243 545111/2

Fax: (+44) 01243 542457

EQUIPMENT & ACCESSORIES PURCHASED

CIRCLE NO. 147 ON REPLY CARD

TURN YOUR SURPLUS TRANSISTORS, ICS ETC, INTO CASH

Immediate settlement.

We also welcome the opportunity to
quote for complete factory clearance.

Contact:

COLES-HARDING & CO, Unit 58,
Queens Road, Wisbech, Cambs. PE13 2PQ
ESTABLISHED OVER 15 YEARS

Buyers of Surplus Inventory

Tel: 01945 584188 Fax: 01945 475216

**TO ADVERTISE
HERE PLEASE CALL
MALCOLM WELLS
ON
0181 652 3620**

FREE CLASSIFIED

WANTED: SOUJET-Russian "spy"
radio. Clandestine sets, all eras. Offer,
swap or cash. 028RO R. Otterstad,
Hoskerkovej 10, DK-3460 Birkerød.
E-mail: Danmec Q INET.UNI-C. DK.

MAINS POWER conditioner, 1250w
type RS208-361, unused, mint, £200
ono. Buyer collects or carrier. Phone
Rasik 0438 748711, evenings only.

WANTED: PRE-WAR TELEVISION.
Jac Janssen, Hogeham 117D, NL-5104
JD Dongen, Netherlands. Tel: 01031
1623 18158; Fax (office): 01031 13
624664.

WANTED: User books and commercial
software for the Osborne 01 computer,
will also consider buying a second
machine. Andrew Emmerson, 71 Fal-
cutt, Way, Northampton NN2 8PH.
Tel: 01604-844130.

SALE OR SWOP for 486PC,
HP8405A, 1MH-1GHz vector volt-
meter complete with 11570A kit.
Offers Pericom Graphics Terminal £50
ono. Tel: 0767 680268.

SUPERMAG, patented magnetic
antenna equipped with 2.5m mini-low-
loss cable for best electrical and me-
chanical performance. Carant AntennAB,
Sweden. Tel: +46 87680365 Fax: +46
87920677.

PCB ASSEMBLY frames (radio
spares), small £20, large £25. Please
telephone 01705 818034 (Portsmouth).

WANTED Operating manual for Boon-
ton Radio 260A QMeter. Debraban-
dere Ommegangstr 14, 9690 Kluis-
bergen, Belgium 00-32-55-388968.

WANTED: 178 Tektronix plug-in for
577 tracer and IC test fixtures manuals.
Sagnard, 47 Rue de la Procession,
75015, Paris. Tel/fax: 33 14056 30 24.

**COLLECTION OF "WIRELESS
WORLD"** 1936-1979. Interested?
Please contact: 0181-946-9449.

1.5KW HARMER SIMMONS switch-
mode power supply. 198V-264V A.C.
I/P 52-58V 28A O/P, with manual. As
new £60. J. Jeffery 0171-873-2735.

WANTED. WWII R1155. Any condi-
tion or any parts. Could collect, reason-
able price as retired. Search attics,
cellars. Lawdham, London 0171 352
4174.

INDEX TO ADVERTISERS

	PAGE		PAGE
Airlink Sales Co.	389	Kestral Electronic Components	438
Amdat	427	Keytronics	444
AMI	400	Lab Center	414
Anchor Surplus Ltd	378	Langrex Supplies Ltd	409
Barnes Elliott Ltd	386	M & B Radio (Leeds)	400
BK Electronics	417	Microgen Electronics	384
Bull Electrical	429	Millford Instruments	386
Chelmer Valve Co.	390	MQP Electronics	382
Citadel Products Ltd	IFC	Number One Systems	390
Cricklewood Electronics	390	OEMA	396
Crossware Products	409	Olson Electronics Ltd	371
Dataman	BC	Powerware	389
Display Electronics Ltd	367	Premier EDA Solutions	384
Field Electric Ltd	400	Ralfe Electronics	448
Grandata Ltd	380	Robinson Marshall (Europe) Ltd	362
Halcyon Electronics	438	Seetrax Ltd	417
Interconnections	389	Smart Communications	409
IOSIS	386	Stewart of Reading	417
John Morrison (MICROS)	427	Surrey Electronics	422
Johns Radio	413	Telford Electronics	438
JPG Electronics	422	Telnet	422
		Those Engineers Ltd	427
		Triangle Digital Services	384
		Tsien Ltd	382
		Ultimate Technology Ltd	IBC

CONTRACT VACANCIES

RF Design	Microstrip antenna techniques	Oxon	BCO524
ATE Engineer	Design/development	Berkshire	BCO476
Senior RF Eng	FM modulation, CCT to 3GHz	Hants	SCO389
RF Engineer	Mobile comms	Hants	BCO401
RF Design	Mobile comms	Cambs	BCO478
RF Design	To 500MHz	Berks	BCO534
Antenna Technician	Ideally Royal Signals trained	Hants	BCO534
Test Engineer	458MHz, SMT dense	Hants	BCO541
RF Design	Amps to 1GHz	Cambs	BCO535
Approvals Test	UHF private mobile radio	Wilts	SCO405
Software Engineer	C, mobile comms	Surrey	BCO527

ALL CONTRACTORS PAID WEEKLY BY BACS

PERMANENT VACANCIES

RF Design Engineer	Circuit des (1GHz), telecomms	£30k	Various	BP0251
Microwave Engineer	MICs/RF antennas	£27k	M4 corridor	BPO307
Test Engineer	RF PCB fault-find mobile comms	£17k	Hants	BP0224
System Test Engineer	GSM/DCS systems	£neg	M4 corridor	BP0287
Snr Design Engineer	HF/EHF	£neg	M4 corridor	BP0204
Digital VLSI Design	GSM, PCN, VHDL, ASICS	£neg	Wilts	SP0268
RF IC Design	Filters, low noise/IF amps	£neg	Wilts	SP0268
Analogue IF Design	High level modelling, BICMOS	£neg	Wilts	SP0268
Product Systems Des	Hardware systems design, GSM	£neg	Hants	SP0281

CALL TO DISCUSS OTHER PERMANENT OPPORTUNITIES


Latest Vacancies on Internet; <http://www.cityscape.co.uk/users/cl87/index.html>.

92 Broadway
Bracknell
Berks RG12 1AR
Tel: 01344 489489
Fax: 01344 489505
E.Mail: cl87@cityscape.co.uk

161 Bitterne Road West
Southampton
Hants SO18 1BH
Tel: 01703 229094
Fax: 01703 220326

**Offices in London, Brussels, Manchester, Birmingham,
Bracknell, Stevenage, Southampton, Crawley**

CLIVEDEN
Technical Recruitment
Cliveden Consultancy Services plc

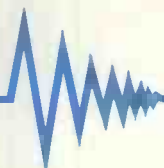

Established 1977.

FRES MEMBER.

Managing Director: Roger Howard C. Eng. M.I.E.E.

SPECTRUM ANALYSERS



IFR MODEL A-7550 1GHz portable with built tracking gen & IEEE ops £5000
 HP141T 18GHz system (8552B, 8555A) £2000
 HP3580A 5Hz - 50KHz audio frequency spectrum analyser £1500
 HP3582A audio frequency f/t analyser dual-channel £2500
 HP8559A 21GHz spec an in 853A digital mainframe HPIB £4500
 HP8568A high-specification 1.5GHz spectrum analyser £7500
 HP8566B (genuine "B") top-of-the-range in laboratory analysers.
 Price... don't ask
 HP8593A portable spectrum analyser to 22GHz IEEE £10000
 TEKTRONIX 492 21GHz spectrum analyser £5000

MARCONI INSTRUMENTS




2019 synthesized AM/FM signal generator 80KHz - 1040MHz £2000
 2305 modulation analyser 50KHz - 2.3GHz £3750
 2828A/2829 digital simulator/analyser £1000
 2955 mobile radio test set ALL SOLD
 2955R as above with sensitive receiver inbuilt
 605X-series signal sources, all in range
 6460/6421 power meter & sensor 10MHz 12.4GHz
 6500 amplitude analyser c/w 2c 6514 waveguide detectors
 OA2805A pom regenerator test set
 TF2910/4 non-linear distortion (video) test set
 TF2910 TV interval timer

RALFE · ELECTRONICS

36 EASTCOTE LANE, S. HARROW, MIDDLESEX HA2 8DB
 TEL: 0181-422 3593. FAX: 0181-423 4009

NOW
 IN
 40th
 YEAR

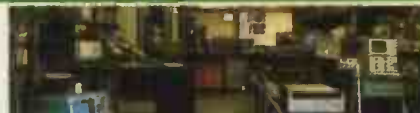

DISTRIBUZIONE E ASSISTENZA, ITALY: TLC RADIO, ROMA (06) 871 90254

TEST EQUIPMENT

ANRISU ME518A portable error rate test set £2000
 BRUEL & KJAER 2511 vibration meter (file set 1621 filter) £2000
 BRUEL & KJAER 2317 portable level recorder £1500
 BRUEL & KJAER 2635 charge amplifier £950
 BRUEL & KJAER 2318 graphics printer £750
 BRUEL & KJAER 2308 analogue X-Y pen recorder £750
 DATRON 1065 digital multimeter £500
 FARNELL 2081/100 RF power meter to 100W & 1GHz £250
 FLUKE PM97 scopemeter £500
 FOTEK M200 fibre optic lsd power meter & test source £250
 GOULD 1604/104 20MHz - 20MS/s digital oscilloscope w inbuilt plotter IEEE £1500
 HITACHI VS09 50MHz portable battery powered oscilloscope (includes batts) £550

• ralfe electronics • exclusively a professional T&M

★ TELECOM & DATACOM TEST ★
HP37721A DIGITAL TRANSMISSION ANALYSERS
 Some basic, some with options 001/003 £3250/£3500

★ IMPORTANT NOTICE TO ALL EXISTING CUSTOMERS ★
 Due to the high-quality of the equipment sold by us over the past few years, we would be extremely interested in buying any of it back for stock should it happen to be in a situation now where it is no longer required, or is not being fully utilised. Please do not hesitate to call us.

PLEASE REQUEST OUR LATEST UPDATED STOCK LISTS.
 FULL EXPORT SERVICE AVAILABLE. WE FAX LISTS & SHIP
 FULLY GUARANTEED INSTRUMENTS WORLDWIDE

KIKUSUI 8520 frequency response analyser 20Hz-200KHz £750
 RACAL-DANA 1992 frequency counter 1.3GHz IEEE option £600
 SCHLUMBERGER 1250 frequency response analyser £3000
 SCHLUMBERGER 4040 communications test set, many options included £5000
 SYSTRON-DONNER 6054B frequency counter 20Hz-24GHz GPIB £1250
 TEKTRONIX P6303 scope probes NEW 250MHz X1X10 with readout pin £500ea
 TEKTRONIX transistor curve tracer type 576 & 577 ea £1500
 TEKTRONIX PG502 250MHz pulse generator (requires TM-series mainframe) £750
 UHER report 4200 portable tape recorder £250
 WAYNE KERR SR268 source & detector £350

HEWLETT PACKARD



1640B serial data analyser £500
 334A distortion meter £300
 3325A function generator £1600
 3400A voltmeter, analogue 10Hz-10MHz £250
 3456A digital multimeter £750
 3552A transmission test set £750
 3581C selective voltmeter £1250
 3586A selective level meter £2000
 3762A/3763A data generator/error detector, pair £1000
 4140B pA meter, DC voltage source £3250
 415E swr meter £200
 4275A multi-frequency lcr meter £4000
 432A/R486A uWave power meter waveguide 26-40GHz £500
 436A microwave power meter c/w 8481A detector HPIB opt £1000
 5335A 200MHz frequency counter w ops 20 & 40 £2000
 5370B universal time-interval counter £2000
 6012A power supply 0-60V 0-50A 1000W £650
 6033A system power supply 0-20V 0-30A £1250
 6038A system power supply 0-60V 0-10A £1250
 6253A dual power supply 0-20V 0-1A twice £250
 6443B power supply 0-120V 0-2.5A £400
 6825A bipolar power supply/amplifier -20V to +20V, 0-1A £350
 8011A pulse generator 0.1Hz-20MHz £500
 8116A 50MHz pulse generator £1500
 816A slotted line 1.8-18GHz with carriage 809C and 447B £500
 8444A tracking generator with option 059 £1500
 8505A 500KHz-1.3GHz RF network analyser £4500
 8671A synthesized signal generator 2-6-2GHz £2500
 8672A synthesized signal generator 2-18GHz £6000

URGENTLY REQUIRED - HIGHEST CASH PRICES PAID FOR 8566A/B/C, Spectrum/network analysers. 8590/1/2/3 portable analysers. Please call us if you have high-end capital equipment being under-utilised.

PLEASE NOTE: ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT LABORATORY

We would be pleased to handle all grades of calibration or NAMAS certification by same laboratory at cost price. All items covered by our 90-day parts and labour guarantee and 7-day "Right to Refuse" (money back) warranty.

ALL PRICES SUBJECT TO ADDITIONAL VAT AND CARRIAGE

CIRCLE NO. 148 ON REPLY CARD

ELECTRONIC UPDATE

Contact Malcolm Wells on
 0181-652 3620

A regular advertising feature enabling
 readers to obtain more information
 on companies' products or services.

mqp

Models S2200 and S2400



Gang and Set Programmers for
 24, 28 & 32 pin EPROMs, EEPROMs,
 FLASH Emulators and OTPs up to 8M bit.

The system 2000 is an ideal programmer for the production environment. Fast programming results in high throughput and rigorous verification leads to improved quality control. Single key functions and checks against misoperation facilitates its use by unskilled staff.

MQP ELECTRONICS LTD.
 Tel: 0666 825146
 Fax: 0666 825141

CIRCLE NO. 149 ON REPLY CARD

NATIONAL INSTRUMENTS 1995 CATALOGUE

The 1995 National Instruments catalogue describes more than 900 software and hardware products. Engineers and scientists can use these to develop integrated instrumentation systems for test and measurement process monitoring and control, using industry-standard personal computers and workstations.

**NATIONAL INSTRUMENTS
 FOR FURTHER
 INFORMATION CALL
 01635 523545**

CIRCLE NO. 150 ON REPLY CARD



1995 MASTER PRODUCT CATALOGUE



BRAIN BOXES

1995 MASTER PRODUCT CATALOGUE NOW OUT!


Test and Instrument control solutions.
 48 pages of full description and technical data on our own range of solutions to your PC and PS2 interfacing problems; IEEE488 (GPIB) * DIO * Timer/Counters * RS232 * RS422/485 * A/D * D/A * plus Opto Isolated versions. New Parallel/Serial RS232, Opto Dual RS232, Motion Control, Converter and Repeater for 1995!
 ISO 9001 Quality guarantee ✓
 UK design and manufacture ✓
 36 month no-quibble warranty ✓
 Telephone hotline support ✓
 Competitive pricing on the page ✓
 Intelligent solutions - friendly service ✓

BRAIN BOXES
 Unit 3f Wavertree Boulevard South
 Wavertree Technology Park
 Liverpool L7 9PF

CIRCLE NO. 151 ON REPLY CARD

OLSON

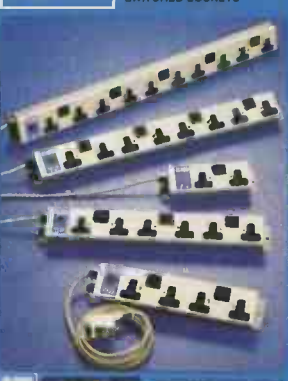FUSED SUPER SLIM
 MAINS DISTRIBUTION PANELS
 WITH DOUBLE POLE
 SWITCHED SOCKETS




OLSON ELECTRONICS LIMITED is a leading manufacturer in the field of mains distribution panels of every shape and size to suit a variety of needs. For use in Broadcasting, Computing, Data Communications, Defence, Education, Finance, Health etc. All panels are manufactured to BS5733. BRITISH AMERICAN, FRENCH, GERMAN CEE22/IEC and many other sockets. Most countries catered for.

All panels are available ex-stock and can be bought direct from OLSON.

Olson Electronics Limited
 Tel: 081 885 2884
 Fax: 081 885 2496

CIRCLE NO. 152 ON REPLY CARD


FROM CONCEPT TO ARTWORK IN 1 DAY

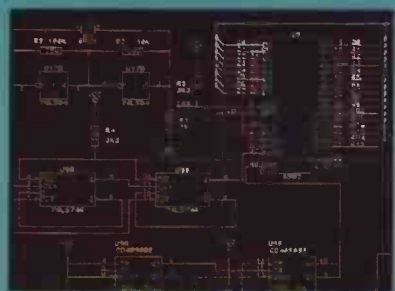


Your design ideas are quickly captured using the ULTicap schematic design Tool. ULTicap uses REAL-TIME checks to prevent logic errors. Schematic editing is painless; simply click your start and end points and ULTicap automatically wires them for you. ULTicap's auto snap to pin and auto junction features ensure your netlist is complete, thereby relieving you of tedious netlist checking.




ULTishell, the integrated user interface, makes sure all your design information is transferred correctly from ULTicap to ULTiboard. Good manual placement tools are vital to the progress of your design, therefore ULTiboard gives you a powerful suite of REAL-TIME functions such as, FORCE VECTORS, RATS NEST RECONNECT and DENSITY HISTOGRAMS. Pin and gate swapping allows you to further optimise your layout

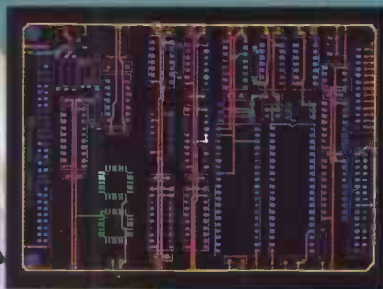

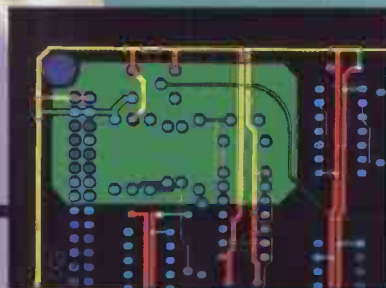
Now you can quickly route your critical tracks. ULTiboard's REAL-TIME DESIGN RULE CHECK will not allow you to make illegal connections or violate your design rules. ULTiboard's powerful TRACE SHOVE, and REROUTE-WHILE-MOVE algorithms guarantee that any manual track editing is flawless. Blind and buried vias and surface mount designs are fully supported.



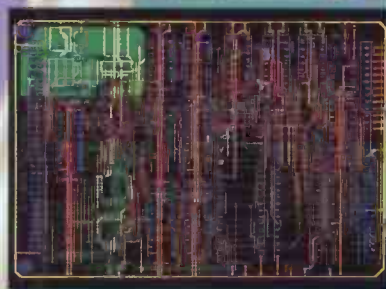If you need partial ground planes, then with the Dos extended board systems you can automatically create copper polygons simply by drawing the outline. The polygon is then filled with copper of the desired net, all correct pins are connected to the polygon with thermal relief connections and user defined gaps are respected around all other pads and tracks.



ULTiboard's autorouter allows you to control which parts of your board are autorouted, either selected nets, or a component, or a window of the board, or the whole board. ULTiboard's intelligent router uses copper sharing techniques to minimise route lengths. Automatic via minimisation reduces the number of vias to decrease production costs. The autorouter will handle up to 32 layers, as well as single sided routing.

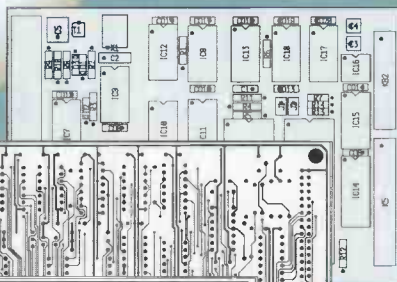

ULTiboard's backannotation automatically updates your ULTicap schematic with any pin and gate swaps or component renumbering. Finally, your design is post processed to generate pen / photo plots, dot matrix/laser or postscript prints and custom drill files.

CIRCLE NO. 102 ON REPLY CARD

NEW


ULTiboard/ULTicap evaluation system:

- all features of the bigger versions
- full set of manuals
- design capacity 500 pins

Price incl. S & H, excl. VAT:

£95

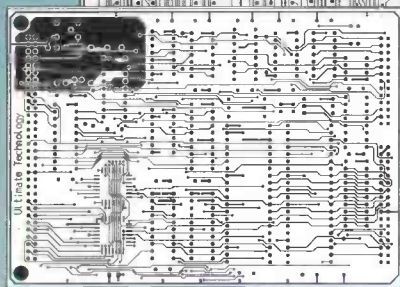Purchase price is 100% credited when upgrading to a bigger version. • Also suitable for study & hobby



ULTiboard PCB Design/ULTicap Schematic Design Systems are available in low-cost DOS versions, fully compatible with and upgradable to the 16 and 32 bit DOS-extended and UNIX versions, featuring unlimited design capacity.

The European quality alternative

ULTICAP + ULTIBOARD = MAXIMUM PRODUCTIVITY

ULTimate Technology UK Ltd. • 2 Bacchus House, Calleva Park, Aldermaston Berkshire RG7 4QW • Fax: 0734 - 815323 • Phone: 0734 - 812030

S4 The best by design!

Credit card holders call now for special bundle deals

S4'S VITAL STATISTICS:

- **Totally handheld programmer/emulator**
- **Fast approved programming algorithms;**
eg. program and verify:
National 27C512 in 16 seconds
AMD 29F010 in only 90 seconds
- **EPROMs to 8Mbit, 5v, 12v and BOOT-BLOCK FLASH, EEPROMs and PEROMs**
- **Three year parts and labour guarantee**
- **Free next day delivery (UK only)**
- **30 day trial available (UK only)**
- **Full 24 byte on-screen editor**
- **Continuous programming whilst charging (nonstop operation)**
- **Moulded designer case - feels as good as it looks**
- **Rubberised colour-coded full travel keypad**
- **Big, easy-view 80 character supertwist LCD**
- **Optional modules available to program PICs, 8751, 16-bit EPROMs, Toshiba 4-bit, Hitachi H8**
- **Optional sockets for programming and emulating PLCC devices**


S4's 32 pin ZIF socket programs a huge library of 8 & 16bit EPROMs, EEPROMs, FLASH, PICs and other popular microcontrollers using manufacturers approved algorithms. Our free and easily updatable device library enables users to always have the latest software installed. During our sixteen years of designing and selling innovative and fast programming solutions to industry, Dataman has *never* charged for software updates or technical support.

Built in emulation enables you to see your code running before committing yourself to an EPROM. Load your program from an EPROM or download

code from your PC into S4's memory. Plug S4's emulation lead into the target system, press the emulation key and run the system. Changes can be made using S4's powerful editor, and you can re-run the code to test and confirm changes. When the code is proved to be working, it can then be programmed to a fresh ROM.

The S4 package comes complete with mains charger, emulation leads, organiser-style instruction manual, PC software and a three year guarantee.

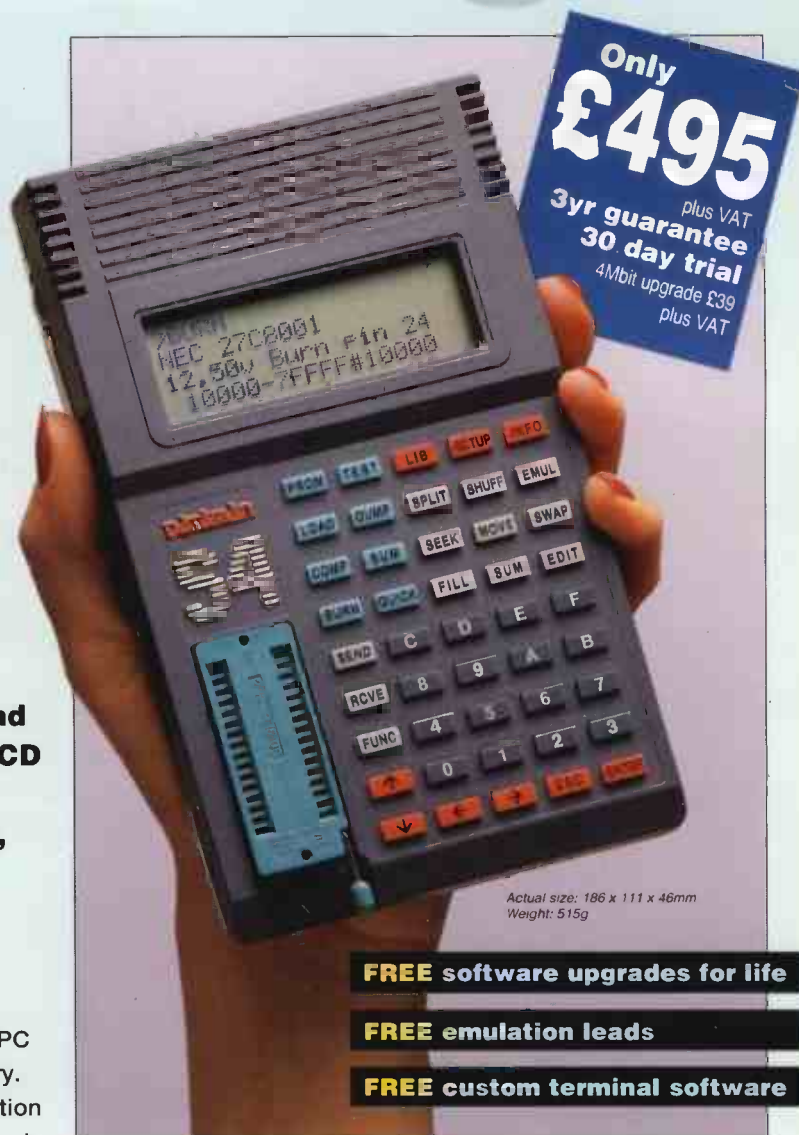S4 is always available off the shelf and we ship worldwide on a daily basis. Call now for delivery tomorrow!



Actual size: 186 x 111 x 46mm
Weight: 515g

FREE software upgrades for life

FREE emulation leads

FREE custom terminal software

Bona-fide UK customers can try S4 for thirty days without risk. 18,000 satisfied users worldwide can't be wrong!

Dataman
Dataman Programmers Ltd

Station Road, Malden Newton
Dorset, DT2 0AE, UK.

Tel: 01300 320719 Fax: 01300 321012
Telex: 418442 BBS: 01300 321095
Modem: V.34/V.FC/V.32bis

22 Lake Beauty Drive, Suite 101
Orlando, FL 32806, USA
Tel: (407) 649-3335 Fax: (407) 649-3310
BBS: (407) 649-3159 24hr
Modem V32bis/16.8K HST

CREDIT CARD HOTLINE 01300 320719 for same-day dispatch



CIRCLE NO. 103 ON REPLY CARD