

PRACTICAL

# ELECTRONICS


MARCH 1981

65p

**LISTEN IN**  
WITH OUR  
**27/28MHz**  
**Converter**

**FREE!**  
INSIDE ■  
**DIODE IDENTICHART**

*Also* Simple Microphone Mixer

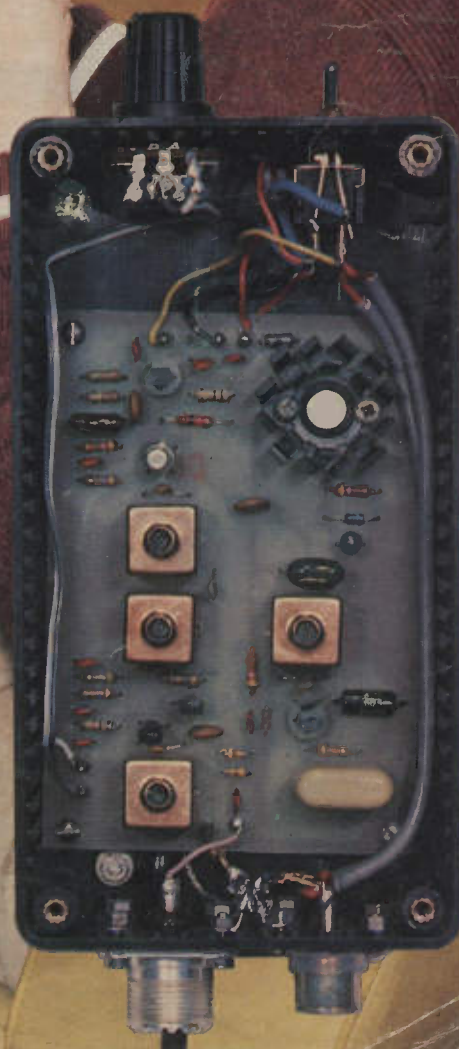



## COMP POCKET COMPUTER GREATEST BREAKTHROUGH YET



**£99.90**  
+ VAT

COMPUTER  
POWER THAT  
ONCE FILLED A ROOM  
CAN NOW BE CARRIED IN YOUR POCKET!

• Programs in BASIC • "QWERTY" Alphabetic Keyboard • 1.9K Random Access Memory • Long Battery Life.

Computer power that once filled a room can now be carried in your pocket! It's easy to load with ready-to-run software from cassette tape (interface and recorder optional) or program it yourself in easy-to-learn BASIC. 24-character liquid crystal readout displays one line at a time. Special feature is advanced non-volatile memory allows you to power on and off without losing the contents of memory. Note: Memory must be transferred to tape before changing batteries. Automatic statement compaction squeezes every ounce of memory space. Features power-off retention of programs and data. Powerful resident BASIC language includes multiple statements, math functions, editing, strings, arrays and much more. Multiple program loading capability subject to RAM availability. Carrying case and batteries included.

Program	Each	Program	Each
Real Estate	£13.95	Games 1	£8.95
Civil Engineering	£13.95	Business Statistics	£10.95
Aviation	£13.95	Business Financial	£10.95
Math Drill	£8.95	Personal Financial	£10.95



only **£325** + VAT

### TRS80 LEVEL 2 16K

Fully converted to UK T.V. Standard. Comes complete with easy to follow manuals. UK Power Supply - Cassette Leads - Sample tapes. Special box to enable you to plug into your own TV. Recommended for first-time buyers. Simply plug in and go. Full Range of Software Available

Interface to Centronics Parallel for TRS80 **£75.00** + VAT

only **£295** + VAT

Expand your TRS80 by 32K  
32K Memory on board  
Centronics parallel port  
Disk controller card Real time clock. Requires Level II Basic. Interface for 2 cassette decks. complete with power supply

### 32K TRS80 EXPANSION INTERFACE



### NASCOM 2 GAMES TAPE

featuring Space Invaders and Android Nim, Re-numbering program and other goodies!

**£7.50** + VAT

COMING  
SOON

THE 1981

COMP SHOP CATALOGUE

## THE ATARI VIDEO COMPUTER GAMES SYSTEM

Atari's Video Computer System now offers more than 1300 different game variations and options in twenty Game Program™ cartridges!

Most Cartridges only **£13.90** + VAT  
Prices may vary with special editions Basic Maths, Airsea Battle, Black Jack, Breakout, Surround, Spacewar, Video Olympics, Outlaw, Basketball, Hunt & Score, Space War, Sky Diver, Air Sea Battle, Codebreaker, Miniature Golf.

Extra Paddle Controllers - **£14.90** + VAT  
\*Keyboard Controllers - **£16.90** + VAT

**SPACE INVADERS NOW IN STOCK £25**



## EUROPE'S FASTEST SELLING ONE BOARD COMPUTER COMPUKIT UK101

★ 6502 based system - best value for money on the market. ★ Powerful 8K Basic - Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed - Plug-in and go. ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Disassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

40 pin Expansion Jumper Cable for CompuKit expansion **£8.50** + VAT

Build, Understand and Program your own Computer for only a small outlay.

KIT ONLY **£179** + VAT  
NO EXTRAS NEEDED

Available ready assembled, tested & ready to go **£228** + VAT

### NEW MONITOR FOR COMPUKIT UK101

• In 2K Eprom 2716 • Allows screen editing • Saves data on tape • Flashing cursor • Text scrolls down **£22.00** + VAT

### FOR THE COMPUKIT

Assembler/Editor	<b>£14.90</b>
Screen Editor Tape	<b>£5.90</b>

All Prices exclusive VAT

### Game Packs

1. Four Games	<b>£5.00</b>
2. Four Games	<b>£5.00</b>
3. Three Games 8K only	<b>£5.00</b>

Super Space Invaders (8K)	<b>£8.50</b>
Space Invaders	<b>£5.00</b>
Chequers	<b>£3.00</b>
Real Time Clock	<b>£3.00</b>
Case for CompuKit	<b>£29.50</b>

## NEW REDUCED PRICES

8K **£399**

16K **£499**

32K **£599**

RRP £795 for 32K

### The PEDIGREE PETS

Very popular for home & business use. 8K Microsoft Basic in ROM. 8K Pet 32K & 16K with new improved keyboard. All with green screen.

Cassette Deck **£55** extra. Full range of software available.

Interface PET IEEE - Centronics Parallel  
Decoded **£77.00** + VAT

We give a full one year's warranty on all our products.

## SPECIAL SCOOP GET YOURSELF A PRINTER FOR YOUR PET AND SAVE A FORTUNE

only **£299** + VAT

Interface Cards **£49**

Full Pet Graphics including cables. Ready to go. **EX-STOCK.**

Interfaces with APPLE, PET, EXIDY, TRS80, COMPUKIT and NASCOM.

## THE VIDEO GENIE SYSTEM EG3000 Series

16K **£299** + VAT  
WITH 16K user RAM

plus extended 12K Microsoft BASIC in ROM • Fully TRS-80 Level II software compatible • Huge range of software already available • Self contained, PSU, UHF modulator, and cassette • Simply plugs into video monitor or UHF TV • Full expansion to disks and printer • Absolutely complete - just fit into mains plug.

## HITACHI PROFESSIONAL MONITORS

9" - **£129** **£99.95**  
12" - **£199** **£149**

• Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability. • 500 lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved in picture center. • Stable picture Even played back pictures of VTR can be displayed without jittering. • Looping video input Video input can be looped through with built-in termination switch. • External sync operation (available as option for U and C types) • Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

## WE ARE NOW STOCKING THE APPLE II EUROPLUS AT REDUCED PRICES

16K **£599**  
32K **£649**  
48K **£659** + VAT

Getting Started APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:

• BASIC - The Language that Makes Programming Fun.  
• High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays.  
• Sound Capability that Brings Programs to Life.  
• Hand Controls for Games and Other Human-Input Applications.  
• Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM: for Big-System Performance in a Small Package.  
• Eight Accessory Expansion Slots to let the System Grow With Your Needs.

You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

Delivery is added at cost. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS** number.

CREDIT FACILITIES ARRANGED - send S.A.E. for application form.

### MAIL ORDER AND SHOP:

14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station - Moorgate Line).  
Telephone: 01-441 2922 (Sales) 01-449 6596 Telex: 298755 TELCOM G

### NEW WEST END SHOWROOM:

311 Edgware Road, London W2. Telephone: 01-262 0387

OPEN - 10am - 7pm - Monday to Saturday

• IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933

• COMP SHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705.  
Telephone: 0101 714 5472526



"Europe's Largest Discount  
Personal Computer Stores"



**COMP** COMPUTER  
COMPONENTS

(Part of the Compshop Ltd. Group)





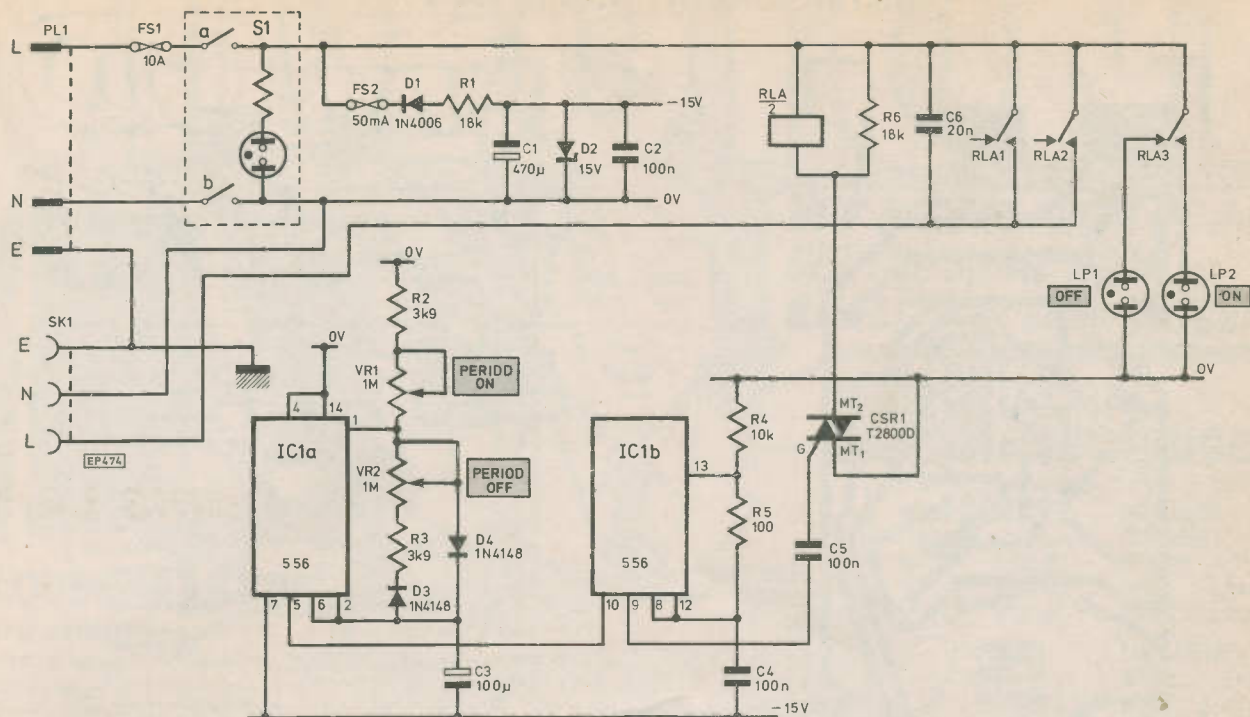


Fig. 1. Circuit of Tester

#### Resistors

R1, R6	18k 2W (2 off)
R2, R3	3k9 (2 off)
R4	10k
R5	100

All  $\frac{1}{4}$ W carbon unless otherwise stated

#### Capacitors

C1	470µ 25V elect
C2	100n polyester Mullard C280
C3	100µ 25V elect
C4, C5	100n (2 off)
C6	20n

#### Potentiometers

VR1, VR2	1M linear (plastic shafts)
----------	----------------------------

#### Semiconductors

D1	1N4006
D2	15V 400mW Zener
D3, D4	1N4148 (2 off)
IC1	ICM 7556
CSR1	T2800D triac


#### Relay

RLA	240V coil with 10A contacts (RS 349-563)
-----	---



#### Miscellaneous

LP1, LP2 mains neons, S1—illuminated double pole mains, FS1-10A  $1\frac{1}{4}$  in quick blow fuse with panel fuseholder, cable grommet, cable, knobs, box—ABS 190 x 110 x 60 mm PL1, SK1—13A plug and flush socket. FS2-50mA with p.c.b. mounting.

## COMPONENTS . . .

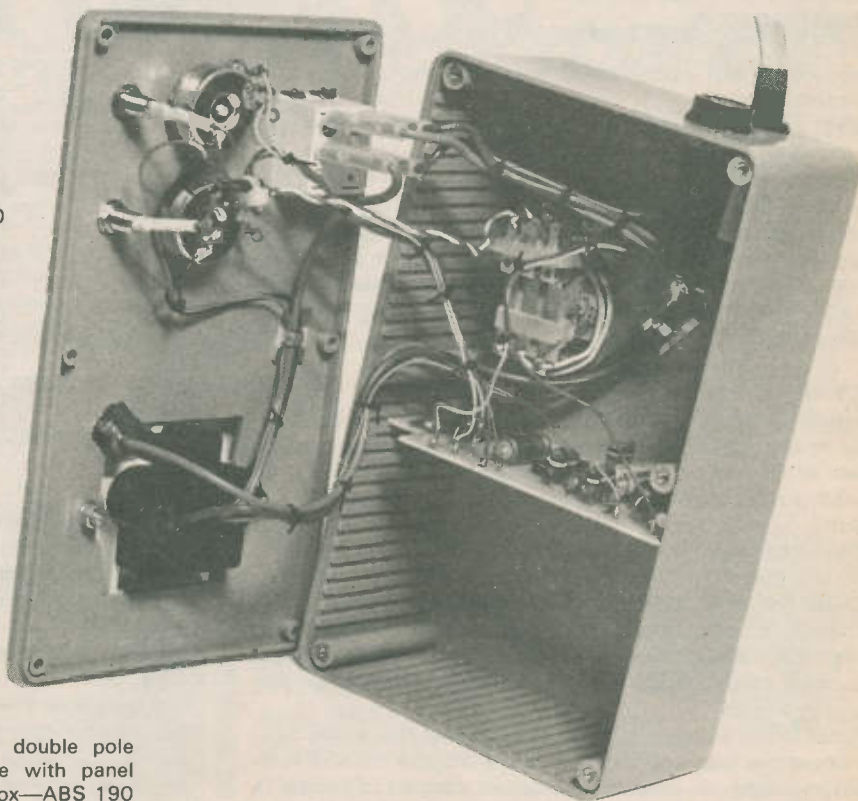

## PRINTED CIRCUIT BOARD AND . . .

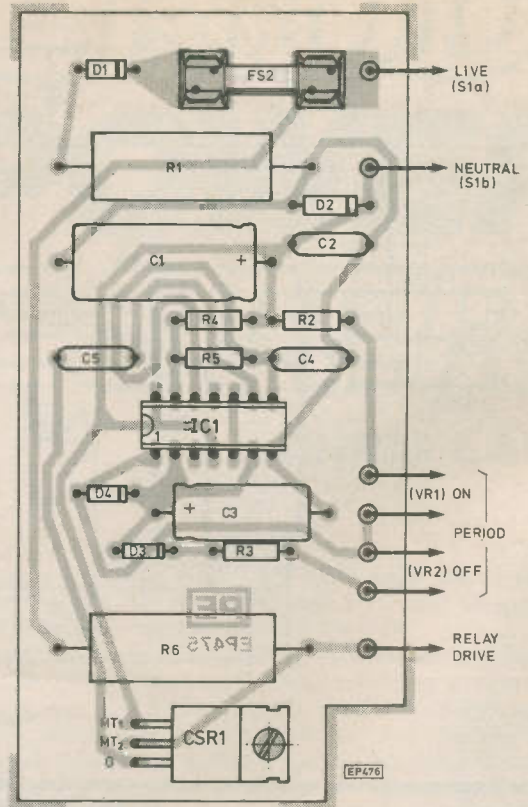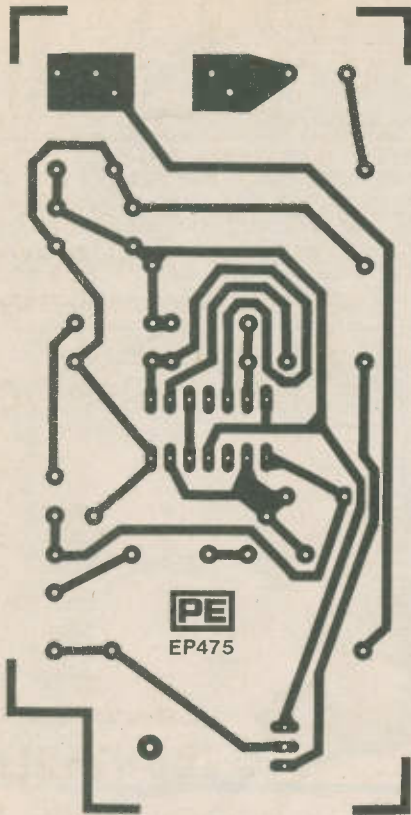

### CONSTRUCTION

The prototype board is of the printed circuit variety. Veroboard is not recommended due to the presence of live mains.

Wire up the board and relay as shown, except for the mains connections. The front panel must be earthed if metal, as must the potentiometer cases. The latter should have plastic shafts.

Ensure the unit is well fused; the prototype has a  $1\frac{1}{4}$  in fuseholder loaded with a 10 amp fuse in circuit as well as the 50 milliamp p.c.b. fuse. The whole was built into an ABS box with p.c.b. mounting slots and so no mounting holes are available on the board design.

### TESTING


Before commencing testing remember that this unit employs mains electricity directly, and as such is potentially lethal. Initial testing should be completed with an external 12 volt power supply connected across C1, observing the polarity.

Do not use a 15 volt supply because the Zener diode will fail.

Check that the output of the first 555 oscillates slowly, and if an oscilloscope is available check the pulse output of the second. If no scope is available measure the voltage output with a meter set to a sensitive range; some deflection should be noted.

Remove the external supply, and connect the mains supply. Cover the fuse and live end of the dropper resistor with insulating tape to prevent accidental contact. Connect a meter across C1, set to 15 volt f.s.d. Stand back and switch on. The voltage across C1 should rise slowly (about 5 seconds) to 15 volts. If it continues past 15 volts switch off

### . . . RELAY WIRING

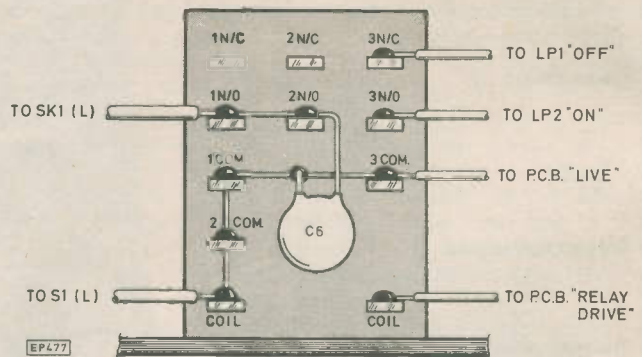

quickly and check the state of the Zener diode. On no account let the supply exceed 18 volts, at which point the i.c. will fail. If all seems well complete the assembly, and test properly, paying particular attention to earth continuity to the socket.

### IN USE

Remember that this unit presents a very severe test to any equipment and it would be short sighted to expect an average amplifier to stand up to a 15 second cycle time while running at full power. Remember, if the equipment does fail a reason exists, so changing the faulty component will not always effect a cure if the cause is still present.





# VIDEOTONE

**BUY DIRECT FROM US AND  
GET THE SAME HIGH  
QUALITY AT LOW PRICES!**

DISCOUNT  
SELLING PRICE  
**£50.00**

## LOUDSPEAKERS

The complete fully reviewed range of Videotone Speakers which dominate within their class. NOW AT LOWEST EVER PRICES.

D100	£38.00
Minimax 11	£44.00
GB3	£50.00
GB2	£60.00
GBS	£207.00
D 93	£40.00

## AMPS-TUNER-CASSETTE

30 watt amp MC input SA4 130	£75.00
Stereo Tuner ST 4120	£68.00
Cassette full features SC 4200	£95.00
50 watt amplifier WA7700	£77.00
20 watt amplifier LA2020	£58.00


This new range of Electronics from Videotone redefines the words quality and value for money to a new high.

DISCOUNT  
SELLING PRICE  
**£68.00**

DISCOUNT  
SELLING PRICE  
**£75.00**

## MICROPHONES

MU 105-22	£29.30
MU 105-12	£22.25
MU 25 C	£17.39

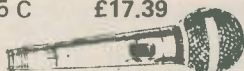

## HEADPHONES

Superbly made with top flight performance	
HP90	£12.65
HP80	£9.69



## CORAL CARTRIDGES

Fast becoming one of the top names

MOVING COIL	MOVING MAGNET
UK's No. 1 Cartridge	
MC 81 £48.87	555SX £7.28
777EX £35.00	555E £14.22
777E £25.00	666E £32.48

HEAD AMP	HEADSHELLS
S100 £6.00	
H300 £51.75	S101 £7.00
T100 £24.75	S200 £4.00

## TURNTABLES

Sansui SR222 Mk2	£69.00
Sansui P50S	£69.00


### \* A MESSAGE FROM VIDEOTONE \*

Dear Customer

You will find that the products advertised on this page are the best possible value for money. They are only low in price because we have eliminated large amounts of selling costs that other brands have to suffer. These savings are passed directly onto you. We have full brochures on any specific item you may be interested in and a competent realistic staff of engineers at our London Showrooms to help you in your choice. Our consumer protection packages are comprehensive and we offer every form of financing you may require. We carry out our own servicing and are dedicated to giving Value for Money. We are confident our products are unbeatable. You may purchase with confidence because our Engineers have specially selected them from competitive sources throughout the world and we import them directly ourselves. Remember, you have 21 days trial period on all products. That is the measure of our confidence.

*Cliff Hardcastle*

Cliff Hardcastle, Managing Director.

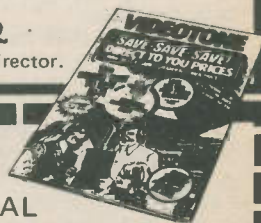

Quality plus value ~ always

# VIDEOTONE

ALL  
PRICES  
INCLUDE  
VAT

ALL PRODUCTS  
ON DISPLAY &  
CONTINUOUS  
DEMONSTRATIONS

98 CROFTON  
PARK ROAD  
LONDON SE4  
TEL: 01-690 8511/2

SEND FOR OUR LATEST  
FREE BROCHURE  
AND DETAIL LIST OF LOCAL  
SALES OUTLETS IN THE U.K.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

PE



# Readout...

## A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

### CB and the Law

The following correspondence should help to clarify certain aspects of the law about which readers may be unsure.

To Press and PR Office,  
Home Office.

Dear Sirs, We are investigating some of the legal aspects of 27MHz CB which is being operated in this country. Would you please supply the following information as soon as possible?

1. Is it illegal to listen to 27MHz CB transmissions?
2. Is it illegal to purchase or to supply a receiver capable of receiving 27MHz CB?
3. I understand that it is illegal to import 27MHz CB transceivers, is it illegal to import a 27MHz receiver?
4. Are CB converters capable of being purchased and used legally in this country?

Finally, are the Home Office proposing any new laws that may affect the answers to the above questions?

Mike Kenward,  
Practical Electronics.

Dear Mr. Kenward—Thank you for your letter regarding the law and CB radio. The answers to your questions are as follows:

1. Under the Wireless Telegraphy Act 1949 it is an offence to listen to CB transmissions without a licence. Penalty for contravention is £200 maximum fine.
2. It is not an offence to purchase a receiver but it could be a common law offence to supply.
3. It is not illegal to import a receiver if it does not possess the capability to transmit. The importation of transmitters is controlled by the Radio Telephonic Transmitters (Control of Manufacture and Importation) Order 1968. Penalties under the Customs and Management Act 1979 attract on summary conviction, a fine three times the value of the goods or £1,000, whichever is the greater, or 2 years. On indictment, an unlimited fine or 6 months maximum.
4. CB converters are capable of purchase, but their use is illegal.

During the first nine months of this year (1980), 325 persons were convicted for unlicensed installation and/or use of 27MHz citizens band radios.

You may be interested to know that the Home Office will be seeking powers to prohibit the sale, hire or advertising for sale or hire of 27MHz band equipment as soon as Parliamentary time permits.

I hope this information is of some assistance.

M. J. Palau (Miss),  
Public Relations Branch,  
Home Office.

*It is also interesting to note that the CBA recently sent the following letter to all MPs.*

Sir—The Citizens' Band Association has just sent the Home Office a response to the Discussion Document "Open Channel". This response was, I am afraid, critical of their proposals. The CBA is well aware of the amount of paper an MP receives, so we have not sent you a copy of our response—if you would like one, however, do please let us know and we shall send you one at once.

We should also like to offer you the loan of a Citizens' Band receiver. You may not appreciate just how commonplace the use of CB radio has become in the UK, even though such use is still illegal. If you would like to listen to CB transmissions for yourself we should be happy to lend you a receiver so that you may do so. We cannot lend you a transmitter, however, as their possession is illegal.

James M. Bryant,  
President, CBA.

### Counter Proposals

*The following is an extract from the rather lengthy CBA response to the discussion document. The following is part of the CBA counter proposals.*

The Citizens' Band Association therefore calls on the Home Office to announce a VHF FM system of Citizens' Band Radio during December 1980. The system should come into operation no later than February 1st 1981, and preferably on New Year's Day. Suitable frequencies are 41 or 230 MHz and a power output of at least 2 watts and preferably 5 watts should be permitted.

If this proves impossible the Home Office should reverse its former position and legalise 27MHz CB AT ONCE. The present disregard of the law cannot be allowed to continue but it would be wrong to mount a draconian campaign against an activity which is shortly to be made legal. The CBA has fought for VHF CB and against 27MHz for five years but continued procrastination by the Home Office has brought the UK to a position where within weeks it will be impossible to do anything but legalise a "fait accompli". It may, indeed, be too late already.

If 27MHz is legalised the American 40 channel a.m. system should be adopted unchanged. The vast majority of sets in this country and the world are to this standard and the European CB Federation has called for its adoption as a common pan-European standard. Although there is a European CEPT specification for 27MHz CB the equipment is

more expensive than equipment to the FCC specification, even though the performance is poorer. As a result the majority of European CB users buy and use the cheaper, but higher performance, American sets, even though their use is not legal. If we adopt 27MHz CB we should avoid the problem by allowing the equipment which the majority of people will actually use.

The CBA feels that in the, hopefully brief, period between the end of the discussion period and an announcement, the Home Office should meet with the CBA and other interested parties to discuss the proposed announcement in time for the Home Office to modify its proposals in the light of any valid comments from these parties.

### CB: Social Uses

Sir—The Yorkshire Ripper is just another example in which CB (Citizens' Band) radio could help society. The continuing unwillingness of the GPO to license 27MHz amateur radio and the efforts applied by the police to detection and prosecution of users is astonishing. It is evidence of some Establishment fear about free use of this medium. This is in spite of overwhelming evidence from overseas that in case of fire, flood or natural disaster of any kind, road accidents or merely traffic congestion, CB can be used to warn, avert further disaster, summon help and keep all relevant authorities informed. The important point is that with CB, it all happens simultaneously: no need to find a 'phone box (probably vandalised anyway); no need to know the number to dial; no need to dial a series of numbers and repeat the same message: just press a button and say "help" or tell what's happened. Watered-down proposals using UHF will never be effective: sets will simply be too dear. Arguments that CB on 27MHz is already overcrowded are not substantiated by US experience; limit transmitter power to 100mW and effective radius is very small. Join a Euro 27MHz union and curb the power of Italian sets. Manhattan Island, with free 27MHz CB, is an extreme example of a densely-populated area, yet CB is a tremendous social asset. Approaching Manhattan from New Jersey by road, ask into any of 40 CB channels "Which bridge is free of traffic?" and within seconds several helpful strangers will all tell you traffic conditions on the different bridges. Your day is made easier by strangers: CB is an antidote to big-city ills; you help, others help you, but there is no threat to your privacy; you can always switch off!

An immediately relevant application is in combating rapists, muggers, wage snatchers etc. A simple 27MHz bleeper which when pressed shouted a radio "Mayday" would alert and enable rapid location by police or others willing to help. In the early seventies, the only effective safeguard against child-snatching was based on radio: it was not used because of the official veto on the free use of radio by ordinary people. Please let us sweep aside this bureaucratic nonsense to allow the use of radio by citizens, not just by the government.

Alan Vincent,  
Dorset.



# P.E. INVENTORS COMPETITION RESULTS

**R**ESULTS of a competition from June '78? We did announce the prizewinners of our Inventors Competition in December '78 but one proposal which did not receive a prize, because no prototype was available, was considered by one of the organisers to merit further investigation. The results of that investigation and of nearly two years intensive development and field testing is a flue-gas analysis test unit that sets a new standard for the modern combustion engineer. The unit is called the Anagas and is now being produced by Colwick Instruments Ltd.

## THE INNOVATION

When setting up the combustion in boilers, heaters, etc., to the optimum, it is necessary to carry out analysis of flue gas remarking, in the case of oil fired equipment, percentage oxygen or carbon dioxide, flue gas temperature and smoke density, and in the case of gas fired equipment, carbon dioxide, flue gas temperature, and an indication of the presence of toxic, and combustible gases (ie carbon monoxide). From the above information, the correctness of the combustion, and the overall efficiency of the heating equipment may be calculated.

Until now, test equipment has taken the form of chemical analysis apparatus produced by several companies, the best known of which is named "Fyrite". The kit used comprises a set of separate instruments to analyse respectively, carbon dioxide, smoke density, flue gas temperature and carbon monoxide, using reagents to absorb or change colour. The reagents are short lived and somewhat messy, and in the case of the tests for carbon monoxide involve the use of a glass phial containing crystals (after the manner of the breathalyser). The glass phial is non-reusable and costs around £1 per test!

Some four years ago, being aware that all the gas characteristics required could be measured electrically or electronically, Mr. B. Drake decided to attempt to design a portable test apparatus which would automatically measure CO<sub>2</sub> and flue gas temperature, and give an indication of the presence of carbon monoxide and smoke. At that time, it was not envisaged that the instrument would be manufactured in quantity, but was merely entered into as a project which may have practical applications within Mr. Drake's own boiler servicing company.

After a considerable amount of spare time research, the means to carry out each measurement, together with a block scheme of the in-

strument was produced; it was then found that the time involved in development would be more than could be worthwhile unless a marketable product could result from this work. The opportunity for further work on the project came in May 1978 with the announcement of the Inventors Competition in *P.E.* An entry was made up and submitted by Mr. Drake with a note to the effect that the project was as yet undeveloped, but was based on tried and tested technology.

Mr. Derek Buckley, one of the organisers, contacted Mr. Drake and further development took place with the aid of Mr. Drake's associate Mr. Cameron. The analyser was completed and bench tested in early June 1979 and has since been on trial in the field by Mr. Drake's employees. Frequent reports as to its behaviour have been received since that time and the general performance in measurement of CO<sub>2</sub>, flue gas temperature and carbon monoxide is as good or better than anticipated. More important, verbal reports from the field indicate that the service engineers actually like to use the instrument, and find a considerable time saving in its operation.

## THE UNIT

As mentioned above, the Anagas unit is an instrument for analysing flue gases from a boiler or heater, and measuring the temperature within the flue. It uses one sampling probe for its three functions, which in order are: measurement of net flue gas temperature (temperature within the flue minus ambient temperature), measurement of the percentage of carbon dioxide in the sample, and detection of any combustible gases such as carbon monoxide which would be indicative of incomplete combustion.

The analyser consists of an executive case accommodating all the electronic components including a charging circuit to enable the built-in rechargeable batteries to be kept powered. Samples of flue gas are drawn, by means of an electrically operated pump, into the analyser. From the probe they pass first into a condensation trap and into the gas analysing cells, one of which responds to carbon dioxide and the other to carbon monoxide. Signals from the gas cells are amplified and diverted via a three position switch on the front panel of the analyser, to the meter. Zero adjustments are provided on the front panel to enable the user accurately to set the CO<sub>2</sub> and temperature range.

Although all these three measurements are continuously available within the instrument, the switch enables the quantity to be measured to be selected individually by the user. The use of a single probe enables the user to monitor all three indications while at the same time making adjustments to the combustion equipment. This is to be compared with the present method which involves the use of each of three separate measuring instruments each time an adjustment is carried out, ie. chemical equipment.

The system offered has several other clear advantages over conventional equipment, one of which is the ability to measure nett flue gas temperature ( $\Delta t$ ) directly, whereas conventional equipment needs to have ambient temperature deducted from the thermometer reading. Another advantage is its lighter weight and inherent portability. The Anagas costs less than £450 inclusive and is available from Colwick Instruments Ltd., 9 New Vale Road, Colwick, Nottingham. Tel 0602 249947.

We believe that the Anagas has a bright future and that this application of electronics will be of great assistance to combustion engineers everywhere. We are pleased that *P.E.* has been able to play a small part in the development of this unusual product.





# Strictly Instrumental

by K. Lenton-Smith

WHEN does an electronic organ cease to be an organ? Judging by the range of organs currently available, the answer to this question is any time now.

Musically, the organ's character is changing rapidly. Its voice is no longer simply a handful of flute pitches modulated by a doppler speaker—a most pleasant sound, whose source is instantly identifiable—or conventional organ tone colours. The modern instrument will also incorporate a very convincing string chorus and synthesised solo voices which are already close to perfection.

The oboe, jazz flute, piano and accordion sound much like their orchestral counterparts and synthesised brass is now better than ever. Thus a skilled player is able to make an appropriate organ sound like an orchestra: the listener may be deceived until the use of 'organ sound' (as we used to know it) gives the game away.

## ORCHESTRA

Practically all of the manufacturers are following this trend towards the orchestral organ. A good example is the *Riha* 'Orchestra', played by Brian Sharp on cassette tape VCA049 (VFM Records and Tapes), where the instrument certainly lives up to its name. Indeed, synthesised voices are so similar between one make of organ and another that one could be forgiven for thinking that they all used the same circuitry!

Less expensive instruments still tend to be based on a simple divider generator system with top octave synthesiser, conventional waveform filters and a modest rhythm unit. Bearing inflation in mind, the majority of organs still represent very good value for money. Despite advances in circuitry and the addition of new features in recent years, much of the hand-wiring has been eliminated and modern p.c.b.s. require less labour-intensive treatment.

Paying upwards of £1000 will see the instrument fitted with orchestral features. These will include a string synthesiser and either or both monophonic and polyphonic synthesiser sections. An 'ensemble' tab is not unusual, which gives the effect of a chorus of voices from a single stop: based on string synthesiser techniques. Other uses for 'bucket brigade' devices include reverberation and 'electronic Doppler' effects.

Not so very long ago the synthesiser was a separate, bulky instrument and the polyphonic type uncommon. Circuit condensation by means of LSI has allowed the manufacturer to fit all these extras into a small console and still leave room for more.

## COMPUTER

The *Allen* computer organ has been in existence for several years now and the microprocessor is being used increasingly in organs of all makes. Its applications include advanced rhythm units which are often programmable and far less monotonous than their predecessors. It can also be used to provide memory facilities and the easy-play features which help to inspire raw beginners at the keyboards.

Classical organs are, of course, exceptions where automation is concerned. It is interesting to note that the fine classical range from *Johannus* still uses diode keying and a special form of divider generators to obtain chorus effect. This company's Model 130, a large 3-manual instrument with drawstops, sounds impressive and is a good recommendation for established methods of keying and tone generation.

Free phase generators are unusual in commercial organs today, although *Conn* still use this method. In this case, an individual, tuneable oscillator is employed for each note of the compass: the tiny tuning discrepancies and lack of any phase relationship provide results akin to a pipe organ.

The majority of commercial instruments use a single master oscillator which operates at about 2MHz. This feeds a TOS (Top Octave Synthesiser) which provides the 12 chromatic frequencies of the top octave. Each of these top notes has its own divider string and these may incorporate divider-keyer i.c.s similar in principle to the TDA 1008 described in the *September 1978* edition. Some organs use clock-keying and multiplexing methods to eliminate key-click. Even so, a number of instruments are fitted with a 'Key-Click' tab—to restore the very feature that was probably responsible for making the pre-war *Hammond* organ so popular with rhythmic players of the day. Digital systems of generation are also becoming common as in the new 'D' series of organs from *Wurlitzer*.

## CONTROLS

Touch switches are a feature of the 'Equinox' organs from *Gulbransen*, providing a clinical appearance to the consoles. From the player's point of view, however, there is often not enough time to touch precisely the correct part of the control panel: I think I would rather have a tab or button to manipulate. These and other organs are capable of automatic introductions and breaks, where harmony is dependent solely on the pedal part.

Arpeggiators are more or less standard on all new organs. This facility gives automatic runs of notes up and down the keyboard, their harmony being controlled by the accompaniment chord being played and their speed by the rhythm pattern in use. There are options on how the arpeggios are played—down, up and up, down, for example—and the effect can be overlaid on the lower manual part in a quite different registration.

Easy-play features are what sell organs to the customer, so these are fitted to even the most expensive models. To many prospective purchasers, 'one-finger chords' is an essential facility. With the appropriate tab in operation, touching a single note on the lower manual will give a major chord—gated according to the rhythm pattern in use. By pressing another single note, major chords can be turned into minor chords: in some cases, conversion is by means of a switch on the swell pedal and there may be methods of producing dominant and diminished chords automatically.

The number of different chords encountered in sheet music is well beyond the scope of the 'one-finger chord' facility, but it may well help to get the beginner off the ground with the conviction that progress is being made. When more experienced or when reading from a three stave score, this feature can be switched off.

The *Elka 30* ranks high on my list for the best easy-play organ on the market. This organ's music stand is provided with several rows of l.e.d.s over which specially punched music is placed. A cartridge containing programmes of several tunes is placed in a slot in the console, then the organ will do everything except play the single line melody. The player has the music to guide him and an l.e.d. lights at the beginning of each bar to help him to keep in step with his automatic instrument.

*National/Technics* have been back to the drawing board and produced their new 'U' series of organs, all but one of which have a programmable chord computer. A sequence of chords is captured by playing each singly, followed by a capture key: the sequence can then be played back in chosen tempo and rhythm pattern, leaving the player to use both hands for the melody and its block chords.

The 'Vocalist' synthesiser from *Logan* sings in four voices, or a choir of these, electronically and without recourse to microphones. Playing a single note produces the Soprano, whilst playing chords adds the Alto, Tenor and Bass voices. The player can alter the timbre of the voices to suit his taste.



## ULTIMATE

The last word in automation is the *Lowrey MX1*. In a rather different price bracket, it is described by the manufacturer as 'the ultimate in micro-electronic computer logic'. Having heard this extraordinary instrument, I can believe the claim! The automatic accompaniment is fully orchestrated and the mode—Big Band or Blue Grass, for example—can be selected. Other *Lowrey* features such as Magic Genie and A.O.C. (Automatic Organ Computer)

are also present. In 'Big Band' mode, the brass and soli saxophone section sounds very much like the real thing: once set in motion, the automatic accompaniment will find its own harmonies and instrumental sections long after the organist has walked off to lunch! It is good to know that the organist is still in full control—and not vice versa—and can even play the *MX1* as a 'straight' organ if he wishes.

The new flagship of the *Hammond* range is the *Elegante*, a development of the

*Colánnade*. This has all the refinements the enthusiast could wish for. There are two 5-octave manuals with reverse colour preset keys and 25-note pedalboard. Its Auto-Vari 64 rhythm unit uses 16 rhythms, each with four programmable variations, and is very effective. The usual cluster of easy-play features have not been forgotten.

It would certainly seem that organs are becoming strictly instrumental. Possibly the choice of title for this series, made almost ten years ago, was far seeing?

# Countdown

**Microsystems** (exhibition and conference) March 11–13. Wembley Conf. Centre, London. **ZI**  
**INSPEX** March 16–20. NEC, Birmingham. **ZI**  
**Seminex** (seminars only) March 23–27. Imperial College, London. **HI**  
**BEX** (Business Equipment) March 25–26. Metropole, Brighton. **K**  
**The Northern Electronic Test & Measurement Exhibition** March 31–April 2. Wythenshawe Forum, Manchester. **T**  
**Laboratory** April 1–2. Glasgow. **I**  
**BEX** April 8–9. Centre Hotel, Liverpool. **K**  
**Laboratory** April 8–9. Manchester. **I**  
**All Electronics Show** April 22–24. Grosvenor House, Park Lane, London. **FI**  
**Computer Graphics** April 28–30. The Barbican Centre, London. **O**  
**BEX** April 29–30. Dragonara Hotel, Leeds. **K**  
**Entertainment** May 9–17 (weekday mornings trade only). NEC, Birmingham. **B2**  
**The European Consumer Electronics Show** May 10–13. Nuremberg, West Germany. **I**  
**The European Consumer Electronics Show** May 10–13. Nuremberg Fair Centre, W. Germany. (Trade) **I**  
**BEX Train** May 11–22. Calling at: Cambridge, Norwich, Leicester, Sheffield, Newcastle, Middlesbrough, Hull, Nottingham, Reading and Portsmouth. **K**  
**Defence Components Expo** May 12–14. Brighton Metropole. **I**  
**East Suffolk Wireless Revival** May 24. Sports ground of Ipswich Civil Service Sports Association, Straight Road, Ipswich. **VI**  
**Scotalex** June 2–4. Royal Highland Exhibition Hall, Ingliston, Edinburgh. **AI**  
**Semlab** June 2–5. Grand Hall, Olympia, London. The international scientific, educational, medical and industrial laboratory equipment exhibition. (Trade). **I**  
**Transducer Tempcon** June 9–11. Wembley Conf. Centre, London. **T**  
**Components** (Electronics Components Industry Fair) June 9–12. Earls Court, London. **I**  
**International Word Processing Exhibition & Conf.** June 23–26. Wembley Conf. Centre, London. **Z**  
**Solar Energy Exhibition** Aug. 23–28, Brighton. **M**  
**Laboratory** Sept 8–10. Grosvenor House, Park Lane, London. **I**

- I** Industrial Trade Fairs. ☎ 021-705 6707  
**K** Douglas Temple Studios, 1046 Old Christchurch Road, Bournemouth  
**M** Montbuild. ☎ 01-486 1951  
**O** Online Conference. ☎ 0895 39262  
**T** Trident International Exhibitions. ☎ 0822 4671  
**AI** Institute of Electronics. ☎ 0706 43661  
**VI** Jack Tootill, Ipswich. ☎ 0473 44047  
**ZI** IPC Exhibitions Ltd., 40 Bowling Green Lane, London EC1R 0NE. ☎ 01-837 3636  
**B2** Brintex Exhibitions Ltd., 178–202 Great Portland Street, London WIN 6NH. ☎ 01-637 2400

# News Briefs

## FUEL CELL BREATHROUGH


**A** NEW compact fuel cell with a generating capacity of 12 Volts at 4 Amperes has been developed by Hitachi. Described as the world's first compact portable methanol fuel cell, it is intended for use in home appliances, and agricultural and engineering equipment.

The new fuel cell weighs only half that of an automobile type lead-acid battery of the same size, and has been made possible by the development of a new type of electrode, yielding a three-fold increase in power output compared to the conventional methanol fuel cell. Hitachi's platinum ruthenium catalyst, in place of the platinum single catalyst, overcomes the low electric current density and low electrode voltage problems which have retarded the fuel cell's exploitation in industry.

Furthermore, a development of a new battery structure using ion exchange film as an electrolyte has made the 12V 4A fuel cell an eventual reality.


The day may yet arrive when such things as methanol powered electric lawn mowers appear on the market!

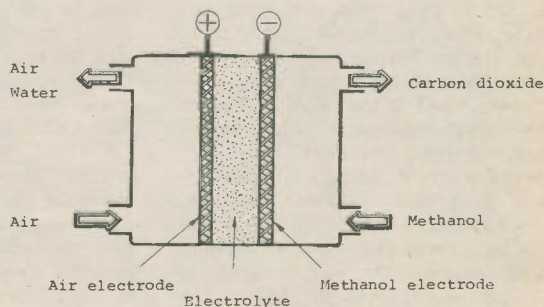**Hitachi's experimental model portable methanol fuel cell**



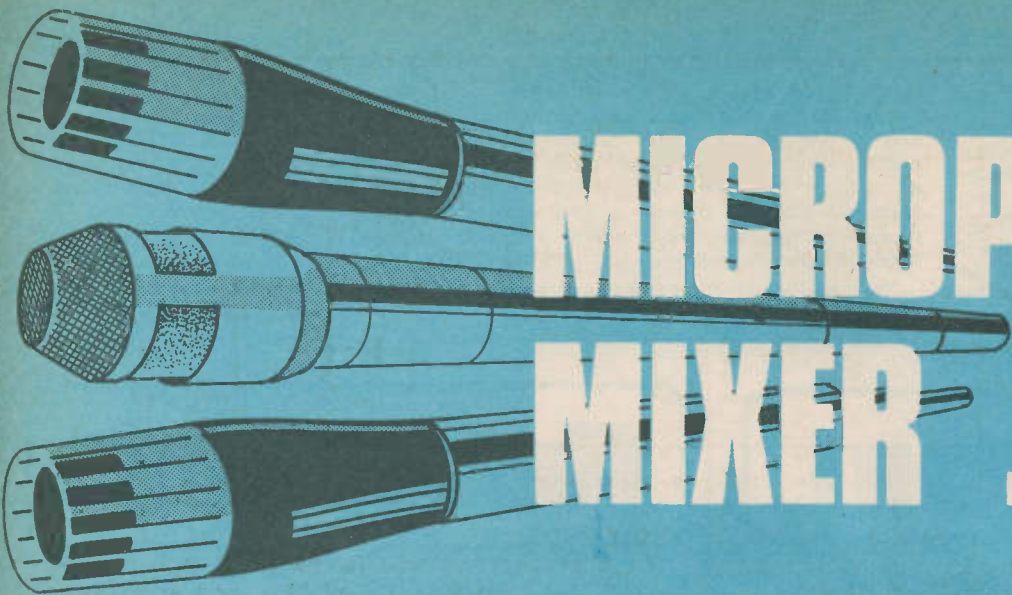**Fuel cells directly convert fuel (in this case Methanol alcohol) into electricity through the reaction of an oxidising agent**





# MICROPHONE MIXER

R.A. PENFOLD

A POPULAR method of making simple "live" stereo recordings is to use two microphones; one being positioned each side of the sound stage. However, even if the microphones are of the correct type and are positioned properly, this method does not always give very good results because it is prone to the so called "hole in the middle" effect where the centre of the sound stage is lacking when the recording is played back.

This problem is easily overcome by using three microphones, these being positioned at the left, right, and centre of the sound stage. Signals from the centre microphone are mixed equally into the left and right channels, and are reproduced at equal volume by both speakers during playback. Provided the two channels have the proper in-phase relationship which is necessary for good stereo imaging, a very vivid centre sound stage should then be produced.

The simple mixer which forms the subject of this article is designed to give the necessary form of mixing for this recording method, and in practice seems to give excellent results for such a simple arrangement. The unit is primarily designed for use with high impedance (50k) microphones, but seems to work satisfactorily with 600 ohm types.

## CIRCUIT DESCRIPTION

The circuit is based on two low noise operational amplifier i.c.s, and these are both used in the standard operational amplifier style mixer configuration. The circuit actually con-

sists of two identical sections; one to mix the centre and left hand channels, and the other to mix the centre and right hand channels, with one i.c. being utilized in each section.


As can be seen from the circuit diagram in Fig. 1, the two mixer stages are basically standard inverting amplifier circuits. If we consider IC1, the non-inverting input is biased to about half the supply potential by R2 and R3. At d.c. there is 100 per cent negative feedback through R4, and so under quiescent conditions the output and inverting input also assume half the supply voltage.

The input from the left hand channel microphone is coupled to the inverting input of IC1 via d.c. blocking capacitor C2, and series resistor R1. If there is an input potential of (say) 1mV positive, then this will unbalance the input potentials of IC1, and the polarity of the signal across the inputs is such that the output is sent negative. Although a voltage difference of less than a millivolt at the inputs of an operational amplifier is sufficient to send the output fully positive or negative due to the high innate ("open loop") voltage gain, the output will in fact only go 1.5mV negative. This is due to the feedback through R4, and the fact that with the output 1.5mV negative and the input 1mV positive, the potential divider action across R1 and R4 balances the input potentials and prevents the output from going further negative. The voltage gain of the amplifier (known as the "closed loop" gain) is controlled by the ratio of R1 to R4, and is equal to R4 divided by R1, or 1.5 times in this case.

The signal from the central microphone is coupled to the





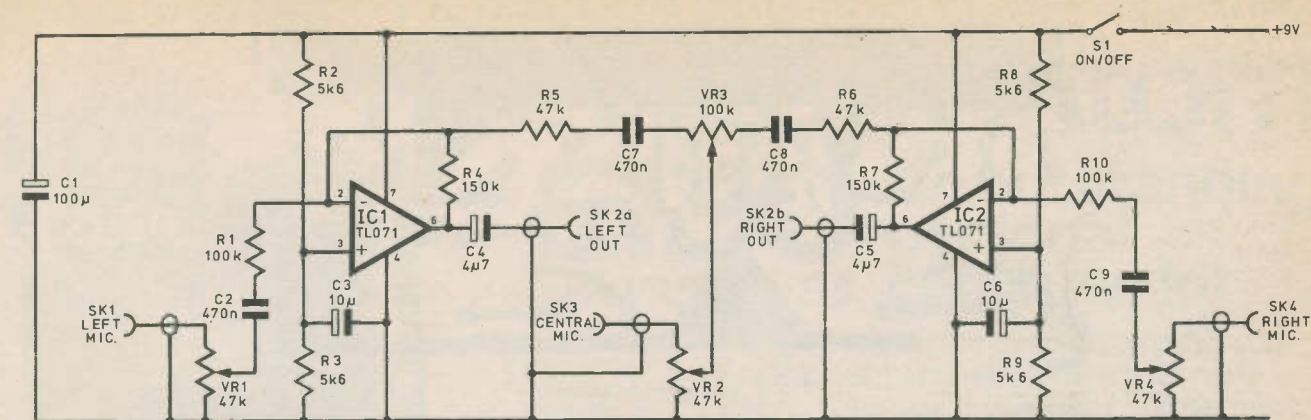


EG 502

Fig. 1. Circuit diagram of the Mixer.

inverting input of IC1 by way of a part of VR3's track, d.c. blocking capacitor C7, and R5. If the slider of VR3 is at the centre of its track, VR3 and R5 combine to effectively form a 97k input resistor. This gives a voltage gain from the central input to the output of approximately 1.5 times, as was the case for the left hand channel. With input signals applied at both these inputs, the output will obviously be 1.5 times the sum of the two inputs, and the required mixing action is obtained. Moving the slider of VR3 to the left increases the gain from the central input to the left hand output, but reduces the gain from the central input to the right hand output (where it provides increased rather than decreased-input resistor value). Moving the slider of VR3 to the right has the opposite effect. Thus it is possible to balance the level of the central signal in the two stereo channels by adjusting VR3.

VR1, VR2, and VR4 are the level controls for the left, central, and right hand channels respectively, and enable a correct overall signal balance to be achieved. On/off switching is provided by S1, and the circuit has a current consumption of approximately 4mA. Capacitors C3 and C6 are used to decouple any stray pick up that might otherwise occur at the non-inverting inputs of IC1 and IC2.

Although there might appear to be a signal path through R5, C7, VR3, C8 and R6 that could severely degrade the channel separation of the unit, no significant cross coupling occurs here. This is because the negative feedback action of the circuit maintains the inverting inputs at a virtually constant voltage (producing what is termed a "virtual earth"), and this effectively isolates the left and right channel inputs.

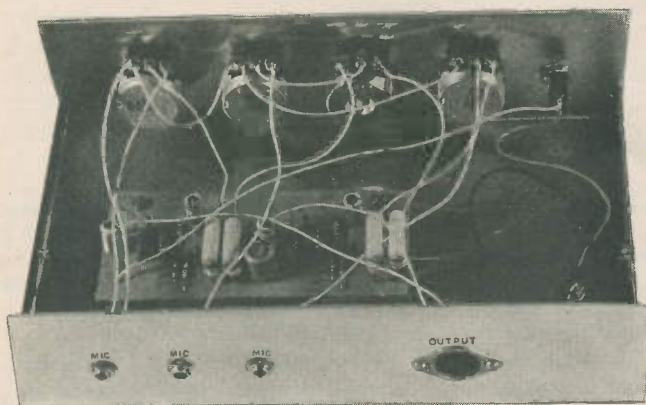

Internal view of the Microphone Mixer

## NOISE

It is obviously essential for the circuit to have an extremely low noise level as it will be processing signals that are likely to have maximum amplitudes of only a few millivolts r.m.s. at most. A suitably low noise level is obtained by the use of Texas bifet operational amplifiers which are designed for optimum noise performance, and give good results in practice. The use of substitute devices is not recommended.

Although the circuit has good supply ripple rejection, the unit would need to be powered from a well smoothed mains power supply in order to obtain a low enough hum level at the output. Great care would also need to be taken to avoid introducing hum due to stray pick up. The prototype is powered from a 9 volt (PP3 size) battery, and this is probably the most practical power source.

## COMPONENTS . . .

### Resistors

R1, R10	100k (2 off)
R2, R3, R8, R9	5k6 (4 off)
R4, R7	150k (2 off)
R5, R6	47k (2 off)
All resistors $\frac{1}{4}$ W 5% carbon	

### Potentiometers

VR1, VR2, VR4	47k log. carbon (3 off)
VR3	100k lin. carbon

### Capacitors

C1	100µ 10V electrolytic
C2, C7, C8, C9	470n type C280 (4 off)
C3, C6	10µ 10V electrolytic (2 off)
C4, C5	4µ 7 10V electrolytic (2 off)

### Semiconductors

IC1, IC2	TL071CP (2 off)
----------	-----------------

### Switch

S1	Sub-miniature toggle type s.p.s.t.
----	------------------------------------

### Miscellaneous

Printed circuit board.  
Input and output sockets (see text).  
Metal case about 200x130x50mm.  
Four control knobs.  
PP3 battery and connector to suit.  
Wire, solder, i.c. sockets.



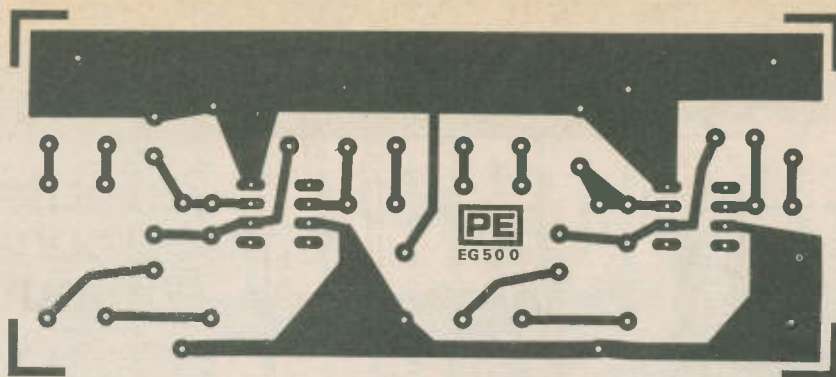


Fig. 2. Design for the p.c.b.

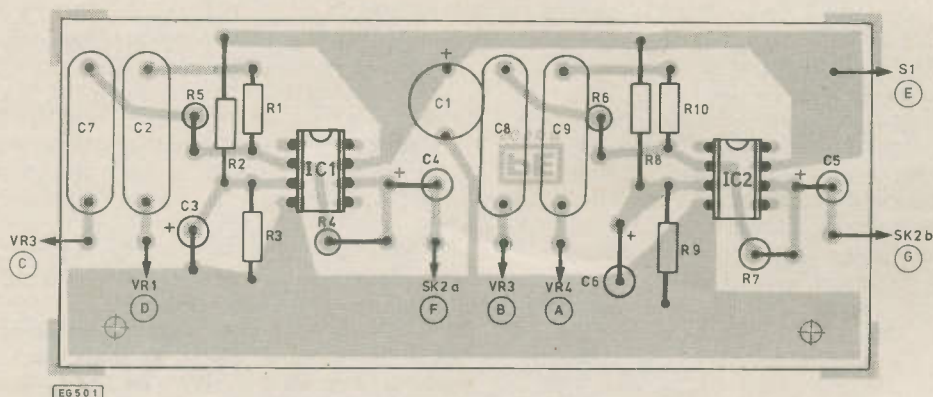


Fig. 3. Component layout for the p.c.b.

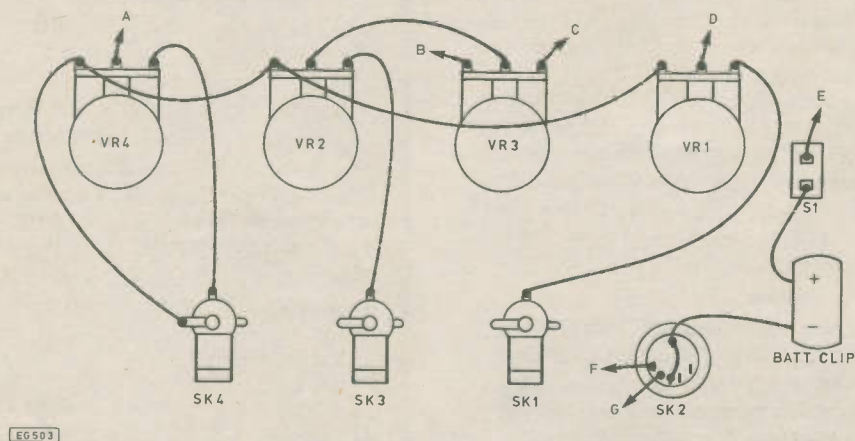


Fig. 4. Wiring diagram.

## CONSTRUCTION

It is advisable to house the unit in a case of all-metal construction that will screen the circuitry from sources of electrical interference. The prototype was built into a metal instrument case measuring about 200×130×50mm, and the four potentiometers used were all rotary types. The input and output sockets are mounted on the rear of the case. 3.5mm jacks were used for the microphone sockets and a 5 way DIN type socket for the output, but these should be types that suit the equipment with which the mixer will be employed.

The printed circuit design for the circuit is shown in Fig. 2, with the component layout shown in Fig. 3. Note that the two i.c.s are JFET types and not MOSFET devices, and therefore they do not require any special handling precautions to protect them from static charges.

A wiring diagram for the unit is shown in Fig. 4. Screened cable should be used to couple the output of the mixer to the microphone inputs of the recorder so that there is no significant noise or r.f. pick up. The output is at a fairly low impedance, and so a long connecting cable can be used without causing any significant loss of performance. ★



Unique in concept - the home computer that grows as you do!

**NEW!**  
Colour Encoder  
for full colour  
graphics  
**£21.50**

# -The Acorn Atom

**£120** An outstanding  
personal  
computer kit  
plus VAT and p&p.




Also available  
ready-built  
**£150**  
plus VAT and p&p

The ATOM - a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now - tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!

\*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

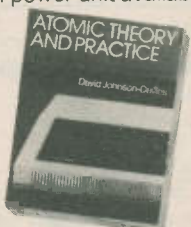**The standard ATOM kit includes:**

- Full sized QWERTY keyboard
  - Rugged polystyrene case
  - Fibreglass PCB
  - 2K RAM
  - 8K ROM
  - 23 integrated circuits
  - Full assembly instructions including tests for fault-finding. (Once built, connect it to any domestic TV and power source)
  - Power requirement: 8V at 800 M.A. ATOM power unit available.
- See coupon. PLUS FREE MANUAL written in two sections - teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



**The ATOM concept**

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMs may be linked to each other - or to a master system with mass storage/


hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally. So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

**The ATOM hardware includes:**

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions)
- 6502 processor
- Video Display allows high resolution (256 x 192) graphics and red, green and blue output
- Cassette Interface - CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output
- Bus output includes internal connections for Acorn Eurocard.

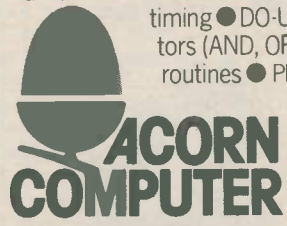**The ATOM software includes:**

- 32-bit arithmetic ( $\pm 2,000,000,000$ )
- High speed execution
- 43 standard/extended BASIC commands
- Variable length strings (up to 256 characters)
- String manipulation functions
- 27 32-bit integer variables
- 27 additional arrays
- random number function
- PUT and GET byte
- WAIT command for timing
- DO-UNTIL construction
- Logical operators (AND, OR, EX-OR)
- LINK to machine-code routines
- PLOT DRAW and MOVE.



**4a Market Hill,  
CAMBRIDGE CB2 3NJ**

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Quantity	Item	Item price inc. VAT + p&p	TOTALS
	ATOM KIT - 8K ROM + 2K RAM (MIN)	@ £140.00	
	ATOM ASSEMBLED - 8K ROM + 2K RAM (MIN)	@ £174.50	
	ATOM KIT - 12K ROM + 12K RAM (MAX)	@ £255.00	
	ATOM ASSEMBLED - 12K ROM + 12K RAM (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM (inc. in 12K Version)	@ £23.30	
	PRINTER DRIVE	@ £10.35	
	6522 VIA	@ £3.17	
	(inc. in 12K version) LS244 Buffer	@ £21.50	
	COLOUR ENCODER	@ £10.20	
	MAINS POWER SUPPLY (1.3 amps)		
	TOTAL		

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £

Please debit my Access/Barclaycard No.

Signature



Name (Please print)

Address

Telephone No.

Registered No: 1403810. VAT No: 215 400 220

PE/3/81



## PROJECT PACKS

Clap switch (79026) Responds from a hand clap to switch on an electrical appliance	£6.60
Pools predictor (79053) An analogue computer that may win you a fortune	£8.15
Talk Funny (80052) A ring modulator circuit that produces very strange results when fed with a human voice	£9.60
Pest Pester (80130) An electronic insect repellent.	£2.35
Steam train sound effects (80019) Simulates the sound of steam and whistle.	£6.50
Electronic Nuisance (80016) Makes an annoying noise, but only in the dark!	£3.85
Cackling Egg timer (9985) An egg timer with a difference, it clucks like a hen.	£3.85
Chorosynth (80060) A cheap mini synthesizer. Send for details.	£57.90
Elektor Vocoder (80060) The first Vocoder designed to be built in kit form. 10 Channel modular construction.	£162.50
Analogue Reverberation Unit (9973) Uses a SAD 1024 which can produce a delay up to 100mS.	£27.70
Guitar Preamp (77020) With three tone controls.	£6.50
Transistor Curve Tracer (80128) Interface with your scope to display Ic./Vce characteristics on the screen.	£2.40
Linear Thermometer (80127) Simple but effective meter reading thermometer using a diode as sensor.	£13.45
Precision Power Unit (80514) Produces accurate reference voltages at presettable current limits up to 2 Amps.	£48.65
Top-preamp (80031) Mini, all IC preamplifier for use with most power amplifiers.	£34.40
Programmable Slide Fader (81002) Mixes audio signals on tape with operation of two slide projectors.	£46.50
Stereo dynamic Preamp (80532) A low noise high quality disc preamplifier.	£5.20
STAMP (80543) Super tiny amplifier with up to 1 Watt output.	£3.75
Transistor Ignition (80082) The most significant advantages of other systems combined in one.	£20.45
Dipstick Probe (80102) Direct warning of high oil temperature. State long or short dipstick required.	£11.25
Intelligent Wiper Delay (80086) Can be set to produce delayed wipes at any predetermined interval.	£15.85
Fuel Economiser (81013) Audible guide to cheaper driving.	£8.05
Simple fuel consumption meter (81043) MPG display for your car.	POA
Disco Projects.	

Send for details

Our Project Packs include the electronic components, the PCB, sockets and solder together with assembly instructions. Cases, knobs etc can be supplied as extra items if required. This is only part of our wide range of projects. See our catalogue for details of other projects that we can supply. You can also ring our number between 12.30 p.m. and 1.30 p.m. any weekday for a recorded announcement of any new items we have available.

To order: send cheque or postal order + 40p P&P to DORAM ELECTRONICS LTD All prices include VAT.  
a de boer company TELEPHONE: (0760) 21627 TELEX: 817912



## The SENSATIONAL CROFTON Offer



Sony colour camera type 2010P only £375.00 total including VAT and P & P. 12v operation IV composite video out. adapter box and modulator available for £25.00 total when purchased with camera. Normally £69.50.

9" metal cased monitors at the lowest price ever — £48.50 plus VAT and P & P. P4 phosphor standard. P31 and P39 available at an extra £11.50 total.



Ask for Crofton Mail Order Catalogue.



All major credit cards accepted.

All items subject to availability. The above prices include VAT. Carriage will be charged at cost.

Phone or write to

**CROFTON ELECTRONICS LIMITED**  
35 Grosvenor Road, Twickenham, Middx TW1 4AD.  
Tel: 01-891 1923/1513



## Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX • AUDIOMASTER • BAKER • BOWER & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EAGLE • ELAC • EMI • FANE • GAUSS • GOODMAN'S • HARBETH • ISOPHON • I.M.F. • JORDAN • JORDAN WATTS • KEF • LOWTHER • MCKENZIE • MISSION • MONITOR AUDIO • MOTOROLA • PEERLESS • RADFORD • RAM • ROGERS • RICHARD ALLAN • SEAS • SHACKMAN • STAG • TANNOY • VIDEOTONE • WHARFEDALE

**WILMSLOW AUDIO (Dept. P.E.)**  
35/39 CHURCH STREET, WILMSLOW, CHESHIRE

Tel: 0625 529599  
FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.  
Tel: 0625 526213  
(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS





## AFTER THE PASS

Voyager 1 has now passed to its future which lies outside the Solar system. Once again all those directly or indirectly involved with the project have the same breathless words on their lips, 'We have learned more about Saturn and the Saturn system in a week than in the whole span of recorded History!' This statement and the statements made previously about other missions seem to have an increasing excitement. It must be hoped that the new knowledge will be used well.

Some of the more significant highlights will be covered in this issue of Spacewatch and then space must be given to other matters. There will of course be frequent updating as details become available and perhaps old theories shaken, discarded or modified. Some things have been confirmed, some things are entirely new but much of the early astronomers' thinking has proved right. One particular item stands out and that is the varied nature of the rings. A few years ago there was an intense radar observation carried out to determine exactly what were the differences in size of the particles. Part of this survey led to the conclusion that there were boulders up to a metre in diameter or perhaps more exactly, size. When the first pictures were returned from the spacecraft it appeared to indicate that there were no large particles. However it has now been established that in fact rocks up to a metre are present.

On December 19 the cameras were shut down concluding the pass of Saturn. Up to that time the spacecraft had returned some 18,000 photographs and recorded 560 pre-programmed images, flew within 2,500 miles of Titan to pass downward through the rings. At the time of the closest encounter with the planet the speed was 56,000 miles per hour. The spacecraft emerged finally through the slit in the ring structure caused by the satellite Dione. One of the advantages of seeing both sides of the ring system structure was that the forward and back scattering of the sunlight

could be observed. The advantages that accrued were threefold. The extent of the ring, designated G, was determined at a radius of 93,000 miles. Estimates place this ring just inside the orbits of the co-orbital satellites S-10 and S-11.

A second benefit was that it was clear that the range of particle size was from fine dust to boulders of metre extent. Highly detailed structure of the rings was observed and it may be that up to a thousand ringlets will finally be known at the end of the count.

Thirdly it enabled the faint D-ring inside the C-ring. Speculation is that this ring is from material that has leaked past the C-ring where the edge seems to form a barrier.

The thin braided ring designated the F-ring may be intertwined with a third ring element, which initially was seen as a diffuse ring component outside the braided structure. Perhaps the fact that the F-ring, which is outside the primary ring structure, has greater contrast when the spacecraft imaging system observes the forward scattering of sunlight from the ring and indicates that there are a large number of particles involved.

Still another discovery was that the satellite Titan, thought to be the largest moon in the solar system, was found to be smaller than the satellite of Jupiter called Ganymede. Titan's atmosphere has an abundance of nitrogen and it is possible that there are lakes of liquid nitrogen.

The atmosphere of Saturn has winds which flow at 900 miles per hour and in contrast to those of Jupiter seem to be continuously in one direction at the equator. There is a very high magnetic field on the planet possibly one hundred times that of the Earth. This would indicate a field of the order of 50 gauss. Nothing like this had been expected. With such a high level it is expected that there could be considerable electrostatic effects. This might suggest a solution to the problem of the rings. The small particles would respond to static charging rather than to gravity and could account for the behaviour of the scattering effects. Some of these problems may be solved when Voyager 2 reaches the area next August. It may well be that the main attention then is concentrated on the rings.

Titan's atmosphere has been subject to a good measure of analysis though there is much yet to be done. Some of the findings are very surprising. At a point in the satellite's atmosphere the pressure is about 1.5 times that of the Earth. This suggests that the pressure at Titan's surface is three times that of the Earth. Also at the point of measurement this indicates that the satellite is less than 3,200 miles in diameter. The preliminary findings show that the satellite may be warmer at the surface than was supposed. The temperature at 1.5 atmospheres was  $-294^{\circ}\text{F}$ . The theoretical model of the atmosphere postulated that the main constituent would be methane rich. This was not found to be the case. There is about 1 per cent methane. The atmosphere is dense, with nitrogen the abundant ingredient. It is certainly an alien body. According to the imaging member of the team, Tobias Owen, who said 'It is not like Mars, the Moon or even Venus. If you landed on Titan, you won't be looking at rocks or impact craters; all such features will be hidden under aerosols. If the layer of aerosols is as deep as it seems, liquid

ammonia rather than liquid water will be flowing across the surface. The poles might well be liquid nitrogen.' Earth observations have already shown the presence of acetylene and ethane. Titan is the most accessible object in the solar system which because of its temperature and environment accumulated these important ices, in particular the ammonia and methane. A step toward discovering the early history of this moon would be to put a lander on the surface to more accurately determine the abundance of complex organic molecules.

Despite the haze that lay over the cloud tops of Saturn the pictures after enhancement were able to indicate meteorological conditions. There were major differences between Jupiter and Saturn. Long lived jet streams flow on Saturn at 400 metres per second, compared with 100 metres per second on Jupiter. During the next months the temperature gradient between the equator and the poles will be intensely studied to determine how they will be affected. The northern hemisphere of the planet seems to be darker markings suggesting warmer temperature and the wider and lighter areas were colder.

Radioastronomy measurements showed very large bursts of radio emission from the vicinity of the planet. These covered a very wide spectrum. Some may have emanated from the rings.

The haze layers seem to be in three levels. One is at about 150km above the clouds, another at 300km above and a third at 500km. The haze is made of polymers and other hydrocarbon chemicals formed by the action of the Sun on methane. The temperature of the haze varies from  $175^{\circ}\text{K}$  at the top to  $65^{\circ}\text{K}$  at the cloud tops.

Other items of particular interest are: The side of Titan facing Saturn radiates noise in the radio spectrum. The rings of Saturn emit radio noise caused by electric fields and collisions between particles. Radio emissions come only from the northern hemisphere, possibly due to an anomaly in the magnetic field.

## THE SECRET OF VENUS

The rapid rotation of the atmosphere of Venus has been a puzzle for some time. Now the Ames Research Centre at Moffet field have an answer to the problem. They have found that the ratio of Argon to Krypton in the atmosphere of Venus is higher than in the Earth's atmosphere. They have also found that the greenhouse effect derives from three sets of chemicals.

The team monitored the movement of the atmosphere by tracing the dark markings. Analysis of two years photography shows that the atmosphere rotates at the same speed for all latitudes. It rotates from East to West. The rate is very high, something of the order of 100 metres a second. This is a complete circulation of the planet in four days. This rotation seems to be due to the pressure differences in the cloud layers. The differences in temperature between day and night is as much as  $20^{\circ}\text{C}$  in the daytime and  $-173^{\circ}\text{C}$  at night. Differences in day and night temperatures below the cloud layers is not more than  $5^{\circ}\text{C}$ .



# Interfacing COMPUKIT

## Part 3 D.E.Graham

**T**HIS month we shall be looking at the output of data from CompuKit in digital form through the 6821 PIA and through sets of latches, to control devices from relays to 7-segment displays; and will cover applications such as a 7400 series i.c. tester, and full interfacing for the *P.E. Speech Synthesis Unit*.

### DIGITAL OUTPUT

The Decoding Module described in parts 1 and 2 of the series allows the CompuKit to output up to 16 parallel bits of data through the MC6821 PIA. The Module also provides a number of address-decoded Write Enable lines which may be used to activate sets of latches, to provide an alternative data output. These may be connected to CompuKit's data bus via SK5 or 6 of the Decoding Module; and when enabled will store data appearing instantaneously on the bus, and make it available for use at the latch outputs. This output will be maintained until the latch Enable is retriggered by the appropriate address-decoded Write line from the Module.

From the range of t.t.l. latches available for this purpose, we have selected the commonly used 74LS75 quad latch. It is somewhat less convenient to use than more complex devices such as the 74116, which provides reset facilities and allows for active-low Enable, but has the advantage of relatively low cost, and is readily available in LS. Fig. 3.1 shows a pair of 74LS75s wired to provide an 8-bit port that connects directly to the Decoding Module. Note that only the Module's active-high Enable lines are suitable for connection to this latch, such as for example, W12, 13, 14 or 15 at pins 19, 9, 18 or 10 of SK5.

Note also, that if latches etc. are to be powered as well as enabled by the Decoding Module, then more than one earth connection should be made to it.

### SEVEN-SEGMENT L.E.D.S

Either port of the PIA, or a 74LS75 port may be used to control 7-segment l.e.d.s using an intermediary as decoder-driver such as the 7447.

The circuit of Fig. 3.2 is for a two-digit Display Unit that plugs directly into SK5 of the Decoding Module to provide CompuKit with digital readout, whilst leaving the PIA completely free for other uses.

The circuit uses a pair of 74LS75s to drive a pair of 74LS47 decoders which in turn drive a pair of FND 507 low cost common anode displays. These plug into a single 24-pin d.i.l. socket mounted on the board. The 7475s are both connected to the lowest four bits of the data bus, and are activated by two *separate* Enable lines from the Module. This

procedure makes software control easier than it would have been had both l.e.d.s been run from the full 8-bits at a single address.

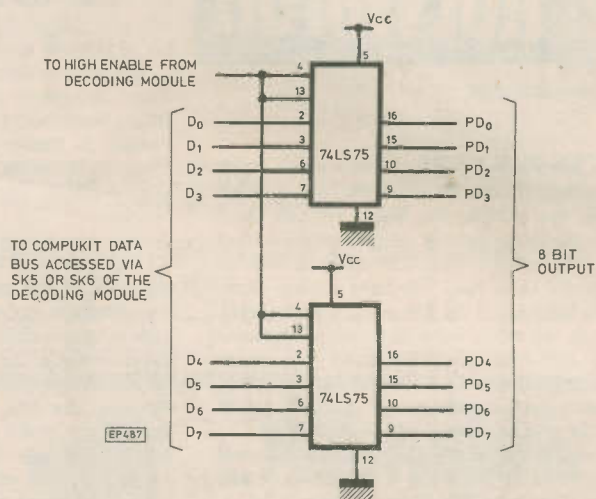


Fig. 3.1. 74LS75 8-bit Port


Figs. 3.3 and 3.4 give p.c.b. artwork and component overlay for the Display Unit. All connections to the board are via a single 16 pin d.i.l. socket which connects to SK5 on the Decoding Module, providing data bus, Write Enables and 5 volt supply. See Table 3.1 for pin connections.

The unit should not draw more than 200mA when displaying "88" so that it should be possible to run a pair of these boards from the Decoding Module power supply, to give a four digit readout (in which case pins 15 and 14 of SK1 on the second display board should be connected to pins 18 and 10 of SK5 on the Decoding Module). If two Display Units are used however, the Decoding Module power supply will not be able to support the next add-on board of the series, to be introduced next month.


Using the Display Board is extremely simple. The command POKE 61324, X: POKE 61325, Y will display the number YX on the display (where Y and X are integers between 0 and 9).

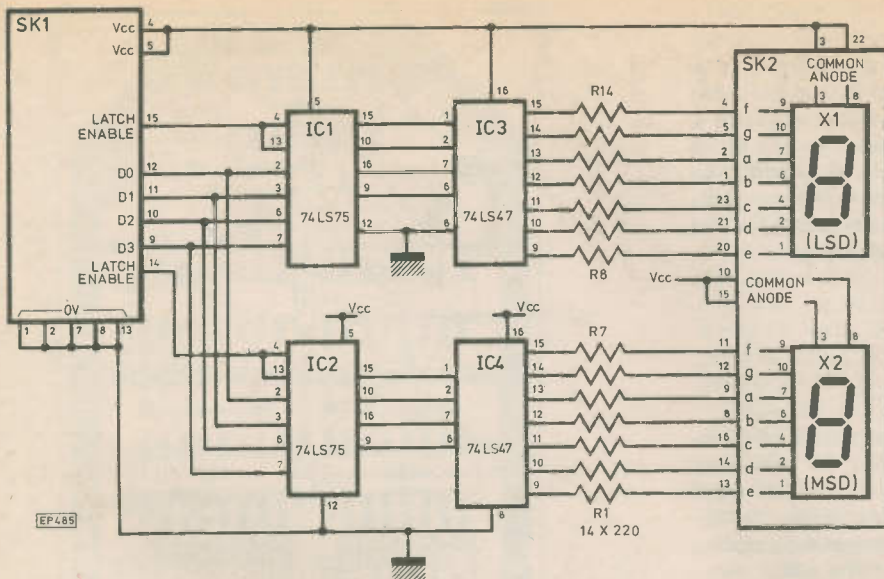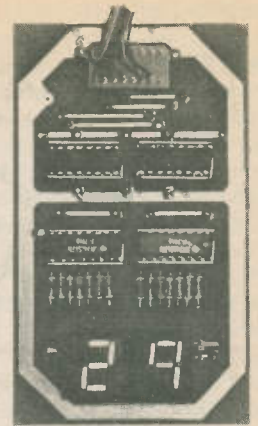Table 3.2 gives a program that will count seconds from 0 to 99 in decimal on the l.e.d. display located at 61324 and 5. Note how the two count digits are separated out in lines 130 and 140, and POKEd to the two separate addresses. It should be possible to achieve timing accuracies of up to about 0.1 per cent with this program by adjusting the length of the waiting loop on line 160.

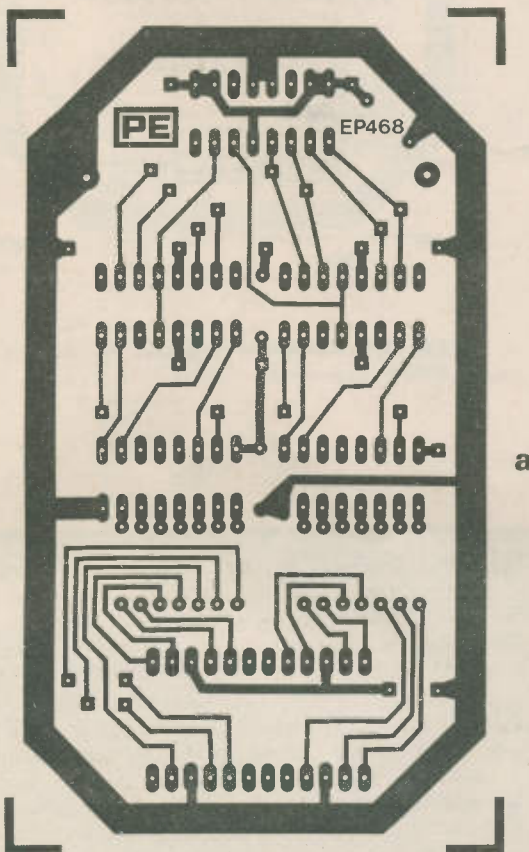





**Fig. 3.2.**  
7-segment  
display  
circuit



**Fig. 3.3. (Below), p.c.b. for Display Unit (actual size). (a) Copper side (b) Component side**



a

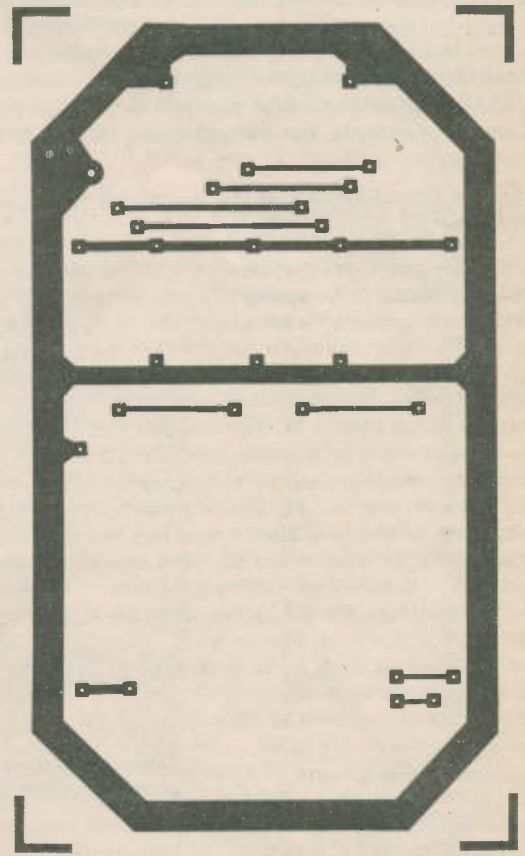

b

Incidentally, although the count is only taken up to 9 on each digit in this program, the 7447 will in fact decode for the hex values A-F using the symbols shown in Table 3.3, so that it would be possible to display values up to FF hex (or 255) with the Display Board, albeit at some loss in ease of readout.

By employing similar techniques, it is possible to add a routine to the joystick screen writing program given last month so as to provide a digital readout of the screen ad-

dress of the cursor. This is a useful facility in setting up graphics work, and the use of l.e.d.s for outputting the data is particularly convenient in that it leaves the full screen clear for graphics development. The full program is given in Table 3.4. As may be seen, the bulk of the work is carried out in a routine starting at line 400. This causes the two-digit display to show a sequence consisting of the first, second and third pairs of digits of the 6-digit screen address currently occupied by the cursor. The display then goes blank before repeating the sequence.



## AUDIO OUTPUT

There are many ways in which Compukit can be interfaced for the production of sound. About the simplest is to connect a single bit of an output port directly to an audio amplifier, and then generate a series of pulses in software. Fig. 3.5 gives a circuit that can be connected to one bit of either port of the 6821 or to a 74LS75 latch. When used with the following program it will produce a square wave output at about 140Hz with a mark to space ratio of about 1:3 on all bits of Part A on the PIA.

100 P=61340

110 POKE P+1,0 : POKE P,255

120 POKE P+1,255

130 POKE P,255

140 POKE P,0

150 GOTO 130

The output frequency is limited by the speed of Compukit's BASIC interpreter, though this may be enhanced somewhat by using variables (eg X and Y) in place of the 0 and 255 of lines 130 and 140, and giving these the appropriate values at the start of the program; and by adding the contents of lines 140 and 150 to that of line 130.

If higher frequencies are required, it is necessary to resort to programming in 6502 machine code, which can then be accessed from BASIC using the USR(X) call. Table 3.5 gives an assembler listing of such a program. It was assembled on the UK101 Assembler/Editor. Column 1 of the listing gives dummy line numbers; the second gives the actual hex ad-

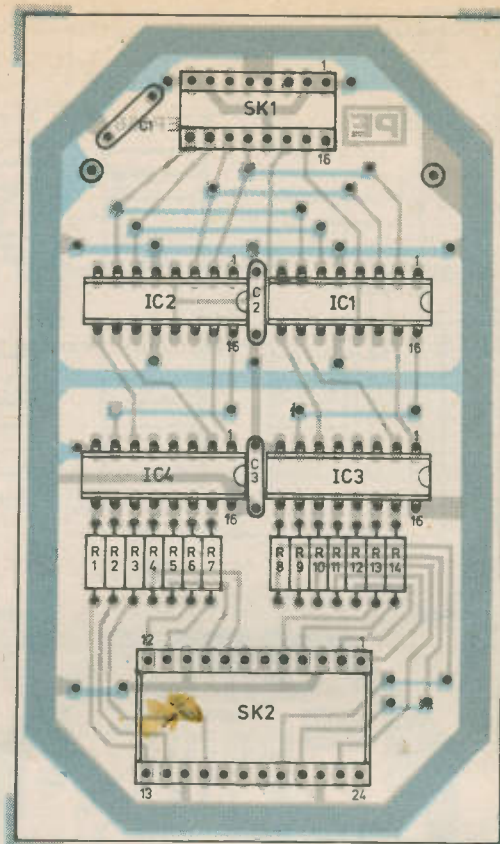


Fig. 3.4. Component layout for Display Unit

Table 3.1 Connections of Display Board to Decoding Module

SK1 on Display Board	To SK5 on Decoding Module	Function
1	1	GND } Not connected if
2	2	GND } 10-strand ribbon
3	/	n/c } cable is used
4	11	Vcc
5	12	Vcc
6	/	n/c
7	15	GND
8	16	GND
9	20	D3
1/ 0	7	D2
11	21	D1
12	6	D0
13	/	GND
14	9	Write Enable (MSD)
15	19	Write Enable (LSD)
16	/	n/c


```

80 REM INTERFACING UK101 PROGRAM 4
90 REM 0-99 COUNTER ON61324/5
100 P=61324
120 FORA=0TO99
130 A1=INT(A/10)
140 A2=A-10*A1
150 POKEP,A2
155 POKEP+1,A1
160 PORT=IT01100:NEXT
170 NEXT
180 GOTO120

```

Table 3.2. Seconds counting program

Table 3.3. 7447 symbols

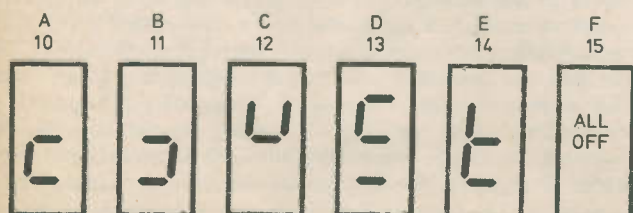

## COMPONENTS . . .

### DISPLAY MODULE

#### Resistors

R1-R14 220  $\frac{1}{4}$ W (14 off)

#### Capacitors

C1-C3 100n low voltage disc. cer. decoupling (3 off)

#### Semiconductors

IC1, IC2 74LS75 (2 off)  
IC3, IC4 74LS47 (2 off)  
X1, X2 FND 507 (2 off)

#### Miscellaneous

SK1 16 pin d.i.l.  
SK2 24 pin d.i.l. (for displays)  
16 pin d.i.l. sockets (4 off)  
Printed circuit board  
16-pin d.i.l. header  
10-strand ribbon cable

### Constructors' Note

A complete kit of parts is available from Technomatic Ltd., 17 Burnley Rd., London NW10.



```

80 PEM INTERFACING UK101 PROGRAM 5
90 REM JOYSTICK DRAWING ROUTINE
95 REM WITH LED SCREEN POSN READOUT
96 REM POKED TO 61324/5
100 FOR I=0 TO 15:PRINT:NEXT
110 V=53260
120 X=23:Y=8
125 VP=V+X+64*Y
126 VE=VP:V1=0:V2=0
130 P=61340
140 C=161
145 J=5
150 POKEP+1,0:POKEP,0
160 POKEP+1,255
165 R=61324:REM LED ADDRESS *****
170 Q=PEEK(P)
180 IF(QAND64)=0 THEN 200
184 C=C+1:IF C=191 THEN C=128
186 POKEVP,C
188 FOR I=0 TO 300: NEXT
210 IF(QAND2)=0 AND Y=0 THEN Y=Y+1
220 IF(QAND4)=0 AND X=0 THEN X=X+1
230 IF(QAND8)=0 AND X<47 THEN X=X+1
240 IF(QAND128)=0 THEN 100
250 VP=V+X+64*Y
260 C1=PEEK(VP)
265 POKEVP,35
270 B=B+1:IF B=5 THEN B=0:GOTO400
275 FOR T=0 TO 100: NEXT
277 POKEVP,C
280 IF(QAND16)=0 THEN 170
290 IF(QAND32)=0 THEN POKEVP,32:GOTO170
300 POKEVP,C1
310 GOTO170
400 IF I<1 THEN POKEP,255:POKEP+1,255:J=5:VE=VP:V2=0:GOTO500
410 VE=VE-V2*10T(J+1)
420 V1=INT(VE/(10TJ))
430 VE=VE-V1*10TJ
440 V2=INT(VE/(10T(J-1)))
450 POKEP,V2:POKEP+1,V1
460 J=J-2
500 GOTO277

```

**Table 3.4. Screen Writer program with readout**

```

5 0000 ;ASSEMBLY LISTING OF SQUARE WAVE GEN
6 0000 ;AUDIO OUTPUT ON PORT A OF PIA AT 61340
7 0000 ;RELOCATABLE PROGRAM BASED AT 0230 HEX
10 0000 START=$0230
20 0230 *=START
30 0230 ME1=START-3
40 0230 ME2=START-2
50 0230 ME3=START-1
60 0230 A900 LDA #00
70 0232 8D9DEF STA 61341
80 0235 A9FF LDA #255
90 0237 8D9DEF STA 61340
100 023A 8D9DEF STA 61341
110 023D AC2E02 STT LDY ME2
120 0240 AE2D02 STU LDX ME1
130 0243 CA A1 DEX
140 0244 D0FD BNE A1
150 0246 88 DEY
160 0247 D0F7 BNE STU
170 0249 8D9DEF STA 61340
180 024C E901 SBC #1
190 024E D0ED BNE STT
200 0250 CE2F02 DEC ME3
210 0253 D0E8 BNE STT
220 0255 60 RTS

```

**Table 3.5. Assembler Listing for Audio output**

```



60 REM INTERFACING UK101 PROGRAM 6
70 REM SQUARE WAVE GENERATOR
75 REM USES USR ROUTINE TO PIA AT 61340
77 REM REQUIRES ACCOMPANYING 6502 CODE PROGRAM
80 PRINT:PRINT:PRINT
90 PRINT,"SQUARE WAVE GENERATOR"
95 PRINT:PRINT
100 POKE11,48
110 POKE12,2
120 PRINT" FREQ 1-255 (255 = LF)"
130 INPUT
135 POKE557,A:POKE558,A
137 PRINT" DURATION 1-255 (0 OR 255 = LONG)"
140 INPUT
145 POKE559,B
200 X=USR(X)
210 GOTO80

```

**Table 3.6. Basic control program for above**

**Fig. 3.6. Relay operation**

**Fig. 3.5. Transistor amplifier for audio output**

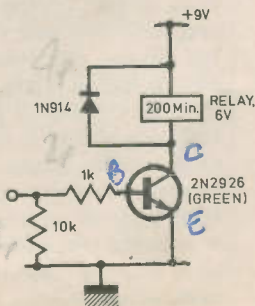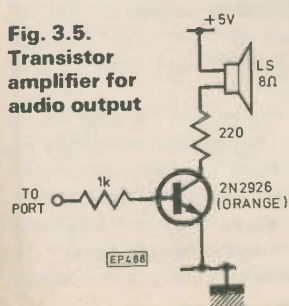

dress in memory; the third, the instruction sequence in 6502 code; and the right hand column gives the assembly language listing, with standard 6502 mnemonics. STT, STU and A1 are dummy labels used during assembly.

The program uses data stored in 022D and 022E hex to determine the time period of its output, and the contents of 022F to determine the duration of sound output. It then outputs a square wave on all 8 bits of port A of the PIA, each bit differing by one octave from the next.

To enter the program, column 3 of the listing could be input manually via Compukit's monitor, placing A9 at 0230 hex, and so on, up to 60 at 0255 hex. Alternatively this string of data could be POKEd into the appropriate addresses using a program in BASIC, though addresses and data would first have to be decimalised.

Once the values are in, the short BASIC program in Table 3.6 may be run to access the machine code program via the USR(X) call. Using this set-up the output frequency as measured at bit 0 of the PIA may be controlled from about 2Hz to 20KHz. At bit 7 it is 1/128 of this.


Because the machine code program is located at an unused space before 0300 hex (the start of Compukit's BASIC file space), it is safe from any attempts to erase it (except by switching off). Even a Cold Start will not shift it.

There is of course one obvious limitation to this method of sound production: it ties up the CPU for the whole duration of sound output. We shall examine more economical means of sound production next month.


## OTHER OUTPUTS

The PIA and any 7475 port may also conveniently be used for control purposes, with each of the eight bits controlling a separate device. Power handling is easily achieved in such applications through the use of relays. Fig. 3.6 gives a circuit for relay operation from a single bit of such a port. It should be noted that if this circuit is used with port A of the PIA, the relay contacts will be closed even when the PIA is set to input (as it is on Reset), since port A output buffers are not tristate; this is not the case with port B. An alternative way of driving relays from either of the ports is to use a driver i.c. such as the 7416 hex inverting driver, or the 7417, its non-inverting equivalent. These devices will sink up to 40mA per bit, and their open collector outputs may be used with supply voltages up to 15V; although the chip supply on pin 14 must not exceed 5 volts. These i.c.s are also ideal for driving i.e.d. indicators (see Fig. 3.7) and opto-isolators from the PIA.

Software for this type of application is easily written even if all 8 bits of a port are simultaneously in use. One approach to this is to use a function such as  $A1 \times 1 + A2 \times 2 + A3 \times 4 + A4 \times 8 + A5 \times 32 + A6 \times 64 + A7 \times 128$ , where A1 to A8 are variables which take the value of zero for low output on the appropriate bit (relay off), and 1 for high output (relay on)—or the reverse if a non-inverting driver is used as in Fig. 3.7. All that is then required of the control program is to allocate ones or zeros to the 8 variables as desired, and then to POKE this function to the appropriate port.

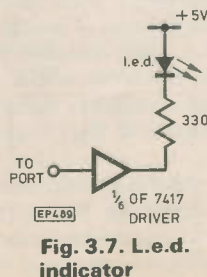


**Fig. 3.7. I.e.d. indicator**

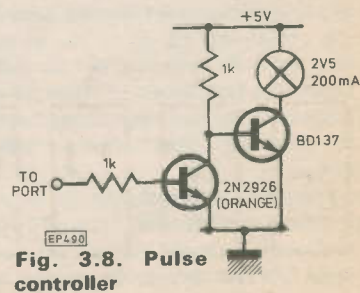

**Fig. 3.8. Pulse controller**

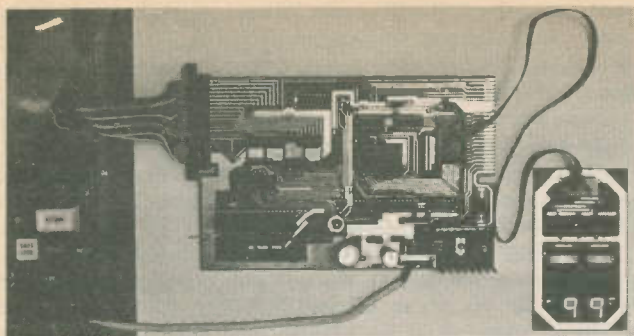



It is also possible to use each bit of a port to achieve a degree of analogue control by using pulse techniques. This involves generating variable duty cycle pulses in software, and POKEing these to a given bit of an output port which is connected to a current amplifier. In order to illustrate this method Fig. 3.8 gives a circuit for controlling the brightness of a 2.5 volt 200mA torch bulb. A short test program to drive this from any bit of port A of the PIA is given below:

#### 50 REM DUTY CYCLE LAMP CONTROL

90 P=61340

100 POKE P+1,0: POKE P,255

110 POKE P+1,255

120 INPUT "BRIGHTNESS 0 (BRIGHT) TO 10 (OFF); X

130 POKE P,0

140 FOR A=1 TO 10: NEXT

150 POKE P,255: FOR A=1 TO 10\*X: NEXT

160 GOTO 130

The program requests a number from 0 to 10, and controls the brightness of the lamp accordingly; decimal numbers in the range 0 to 1 giving greatest illumination. This means of control suffers somewhat from the relatively low pulse frequency obtainable in interpreted BASIC, and from the fact that it monopolises the CPU during power output. In many respects a more satisfactory means of achieving analogue power control is to use D/A conversion techniques, details of which will be given next month.


#### 7400 SERIES IC TESTER

The ability of the PIA to configure any of its 16 bits for either input or output allows it to be used as the basis for a t.t.l. i.c. tester. To show how this may be achieved, we give details of a tester suitable for most 14 pin i.c.s of the 7400 series. It will in fact work with all those using pins 7 and 14 for power supply connection, and whose gates are configured symmetrically across the middle, as are those of the 7400 and 7420, for example, but not the 7415, whose third gate has 2 inputs on the LH side and one input and its output on the RH side. The principles used may be extended to cover most 7400 devices with 14, 16 or 18 pins, though removing the symmetry condition will increase data and software complexity.

For the 14 pin tester, a 14 pin d.i.l. socket is wired to a pair of 16 pin headers as shown in Fig. 3.9 which plug directly into SK3 and 4 of the Decoding Module. Pins 7 and 14 of the test socket are taken to ground and Vcc respectively, and the remaining 12 go to the lowest 6 bits of ports A and B. The six 4.7k resistors act as pull-up resistors on the port B inputs, so that when confronted with a high impedance state (as would be the case when testing a 74125 tristate buffer for example), the tester consistently detects a high logic state.

To perform a test, the i.c. is plugged into the socket, and the program listed in Table 3.7 is run on CompuKit. This first requests the user for the i.c. number, and checks program lines 5000 onwards to see if it has data on the device. If it

Fig. 3.9. I.c. tester connections

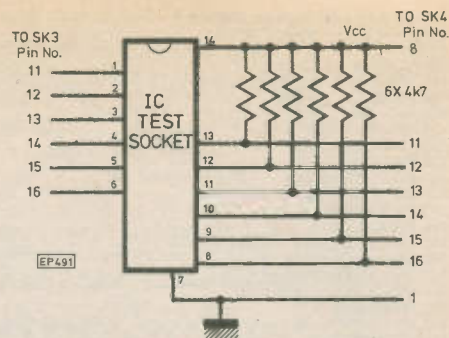

```

2 REM INTERFACING UK101 PROGRAM 7
5 REM UK 101 IC TESTER
10 FOR I=1 TO 16: PRINT: NEXT
15 PRINT, "UK101 7400 SERIES IC TESTER"
20 RESTORE
70 P=61340
80 F=0
90 PRINT: PRINT: PRINT
100 PRINT "ENTER NUMBER OF DEVICE"
110 PRINT "OR ZERO, IF NOT KNOWN"
120 INPUT D
130 IF D=0 THEN 280
140 IF D<7400 OR D>74999 THEN 170
150 IF D>7499 AND D<74000 THEN 170
160 GOTO 200
170 PRINT: PRINT
180 PRINT "ONLY 7400 SERIES PLEASE"
190 GOTO 20
200 READ D1
210 IF D1<1 THEN 240
220 PRINT: PRINT "NO DATA AVAILABLE ON THIS DEVICE"
230 GOTO 20
240 IF D1<>0 THEN 200
250 PRINT: PRINT: PRINT "DATA AVAILABLE ON "; D1
260 PRINT
270 GOTO 300
280 READ D1
285 IF D1<0 THEN 950
290 IF D1<7400 THEN 280
300 REM
320 READ R
340 POKE P+1,0
350 POKE P,63-R
360 POKE P+1,255
370 POKE P,0
380 POKE P+2,63-R
390 POKE P,3,255
400 READ S
410 IF S>255 OR S<0 THEN 770
420 READ T
430 F=F+1
440 POKE P,S
450 POKE P+2,S
460 IF (PEEK(P) AND R)<>T THEN 870
470 IF (PEEK(P+2) AND R)<>T THEN 870
480 GOTO 400
490 IF T<>0 THEN 800
780 PRINT: PRINT "DEVICE RECOGNISED AS "; D1
790 GOTO 830
800 PRINT
810 PRINT "F: TESTS COMPLETED ON "; D1
820 PRINT "DEVICE OK"
830 FOR I=1 TO 5000: NEXT
840 GOTO 20
870 IF D<>0 THEN 280
900 PRINT "*****"
910 PRINT "D1: FAILS ON TEST "; F
920 GOTO 20
950 PRINT: PRINT "*****"
960 PRINT "DEVICE NOT RECOGNISED"
970 GOTO 20
5000 DATA 7400,9,54,0,36,9,18,9,0,9
5010 DATA 7402,36,0,36,18,0,9,0,27,0
5020 DATA 7404,21,42,0,0,21
5030 DATA 7408,9,54,9,36,0,18,0,0,0
5040 DATA 7420,1,62,0,60,1,58,1,46,1,30,1,0,1
5060 DATA 7432,9,54,9,36,9,18,9,0,0
5070 DATA 74125,9,54,9,36,9,18,9,0,0
10000 DATA -1

```

Table 3.7. I.c. tester program

does, it sets up the ports for input and output on the appropriate pins and then performs a series of logic tests on the device, checking responses against data held for that device. It then prints out the results.

If the number of the i.c. is not known by the user (or he lacks the energy to enter it), a zero may be entered when the chip number is requested. This causes the program to perform its complete repertoire of tests in sequence until the i.c. is recognised; whereupon the device number is printed out. Successful recognition can of course only be achieved if the i.c. is fully operational, and if it is one whose data is included in the program.




As the program stands it will test the i.c.s 7400, 02, 04, 08, 20, 32 and 125; though since data for each device is handled in a single data line, it is a relatively easy matter to add data for further similar devices. When using the i.c. identification routine, it should be remembered that a number of devices in the 7400 series are logically similar (such as the 7404, 5, 6 and 16 for example). In such cases the program will simply print out the type number of the first device that it comes across whose data correctly matches the i.c. under test.

In order to facilitate additions to the program enabling it to test further devices, we will examine the derivation of the data used for testing the 7400. All the relevant data for this is stored in line 5000 of the program:

**5000 DATA 7400, 9, 54, 0, 36, 9, 18, 9, 0, 9**

The first number after the device code is used for setting up the PIA so as to input data from those pins of the i.c. which carry output, and to output data to those which carry input. The program is also so arranged that one only has to consider the LH side of the i.c. in setting up the data—ie pins 1–6: the RH side is automatically catered for providing that the i.c. has the required symmetry.

Fig. 3.10 gives a pinout of the 7400, with the port connections made by the test socket. From this it may be seen that pins 1, 2, 4 and 5 are inputs, and 3 and 6 are outputs. From the way in which the PIA ports are configured, ones are used to denote PIA outputs, and zeros input. The code used for configuring the ports in this program follows this, so that for the 7400 this is 9 (ie  $(0 \times 32) + (0 \times 16) + (1 \times 8) + (0 \times 4) + (0 \times 2) + (1 \times 1)$ ).

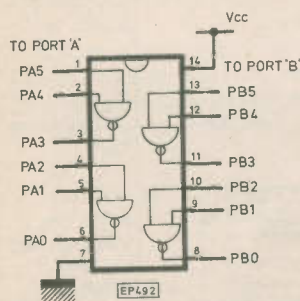

**Fig. 3.10. 7400 pin-out for tester**

**Table 3.8 Truth Table for 7400 IC Tests**

PIA Bit Decimal Bit Value	=	PA5	PA4	PA3	PA2	PA1	PA0	Code
	=	32	16	8	4	2	1	
First Test	input	1	1	X	1	1	X	54
	output	X	X	0	X	X	0	0
Second Test	input	1	0	X	1	0	X	36
	output	X	X	1	X	X	1	9
Third Test	input	0	1	X	0	1	X	18
	output	X	X	1	X	X	1	9
Fourth Test	input	0	0	X	0	0	X	0
	output	X	X	1	X	X	1	9
Key:	↑ = High 0 = Low X = Ignored							

The numbers which follow the port code in the data line are arranged in pairs; two for each test. The first of each specifies the test parameters, and the second the required result. Four sets of tests are used on the 7400 (see Table 3.8). The first test takes each input high, and looks for a low output. Since ones are used to denote high PIA output on any given bit, the code for the first test is 54 (ie  $(1 \times 32) + (1 \times 16) + (1 \times 4) + (1 \times 2)$ ). The result of the test should be zeros on bits 8 and 1. The code for this is  $(0 \times 8) + (0 \times 1)$ , or zero. Had the required result been high outputs from the i.c. on these two pins, as it is in the remaining tests, the result code would have been  $(1 \times 8) + (1 \times 1)$ , or 9.

The remaining test codes are constructed in a similar way, as may be seen from Table 3.8, and the program stops testing a device when, as it looks for the next test code it confronts a new device number. When performing the whole repertoire of tests, or when searching for a particular device number, it uses the -1 in line 10000 as an end indicator.

## USING THE PIA TO CONTROL SPEECH OUTPUT

In the December 1980 issue of *P.E.* Dr Berk described a Speech Synthesis Unit which can be used to provide a microcomputer system with a vocabulary of 24 or 64 spoken words. This unit cannot be easily interfaced to Compukit because Compukit possesses no user port; and even when the unit is interfaced via the 2114 memory sockets, word timing problems are encountered because such an arrangement provides no way of monitoring the Busy signal from the Speech Unit.

The PIA on the Decoding Module provides a simple way of fully interfacing the Speech Synthesis Unit to Compukit, and at the same time gives us an opportunity to examine the use of the peripheral control facilities provided by the 6821. These will be used in the present instance to monitor the state of the Synthesis Unit, and inform Compukit when the unit is busy outputting a word, and when it is ready for the next. But first we will look at the simpler question of how to interface the Speech Unit to the PIA without monitoring the Busy signal.

## PIA INTERFACE

The Speech Unit requires six parallel data lines to specify the word to be output. These may be connected to the lowest six bits of either port of the PIA. Apart from the Busy line, which we shall ignore for the moment, there are two other lines to consider: Latch and Start. The former requires a positive-going edge to cause the 74174 data latches on the Speech Interface Board to capture data on its bus. The requirement for the Start line is that it be taken low to trigger the output of a word, and left in that state until the word is completed.

These requirements may be met using the remaining two bits of the chosen port of the PIA. Bit 6 of the port should be connected directly to the Latch Enable, and bit 7 to the Start line. Software can then be used to control their status.

To output the word "four" for example, the following commands would be executed after initialising the PIA for output on all 8 bits of a port:

**POKE A, 128 + 4**

**POKE A, 64 + 4**

A is 61340 for port A of the PIA (or 61342 for port B). The first command takes the Start line high, the Latch low, and places the number 4 on the bottom 6 data lines. The second command triggers the latch by taking bit 6 high, and initiates speech output by taking bit 7 low, while maintaining the data on the lowest 6 lines. Technically the Start signal should come marginally later than the Latch, but the above



arrangement appears to work well at both ports of the PIA.

The program below will output the full 24 word vocabulary of the Speech Unit using the techniques described above:

```
100 A=61340
110 POKE A+1,0
120 POKE A,255
130 POKE A+1,255
140 FOR B=0 TO 23
150 POKE A,128+B
160 POKE A,64+B
170 FOR C=1 TO 1500: NEXT
180 NEXT
```

As Dr Berk has suggested, if the Busy line cannot be monitored, a timing loop, such as that given in program line 170, must be used to allow one word to finish before the next begins. One difficulty with this approach is that since the words are of differing length, spaces between them will also be variable. In the present program there are considerable pauses after the 10 digits in order that much longer expressions such as "times minus" may be spoken without interruption. This problem may be overcome by using one of the PIA's peripheral control lines.

### PERIPHERAL CONTROL WITH THE PIA

Each port of the 6821 PIA has two so-called peripheral control lines: CA1 and CA2 on port A, and CB1 and CB2 on port B. These have been taken out to pins 2 and 3 of SK3 and 4 respectively, of the Decoding Module.

CA1 and CB1 are input only lines, and may be programmed to set a flag, and optionally cause an interrupt when transitions occur on them.

CA2 and CB2 may be programmed as either inputs or outputs. In the discussions which follow we shall be using the CA1 (or CB1) line, and if the reader requires data on the slightly more complex CA2 and CB2 lines he is referred to the Motorola data sheet on the 6821.

The key to understanding the 6821's peripheral control facilities lies in its two control registers CRA and CRB, mentioned briefly last month. One of these registers is dedicated to each port, and both have a similar structure. Table 3.9 gives their format. As may be seen, bits 1 and 0 determine the mode of operation of control lines CA1 and CB1, whilst bit 7 is the flag which monitors the status of the relevant control line.

Table 3.10 gives the four possible states of the lowest two bits of the control register, and their effect on CA1 (or CB1). It will be seen that bit 1 determines whether the flag is set on a high or a low transition of the control line, while bit 0 determines whether the interrupt line  $\overline{\text{IRQ}}$  (connected directly to Compukit's  $\overline{\text{IRQ}}$  pin via the Decoding Module) will be activated (taken low) when the flag is set or not. In the discussions which follow we shall not be employing the interrupt facility (which requires handling-routines in 6502 code). The use of interrupts will be treated in a later issue in connection with the 6522 VIA.

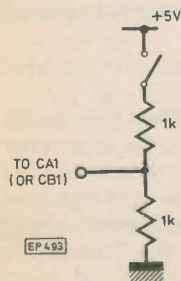


Fig. 3.11. Resistor chain to test flag

Table 3.9 Structure of PIA Peripheral Control Registers

Bit	7	6	5 4 3	2	1 0
Control Register A (CRA) at 61341	$\overline{\text{IRQ}}$ (CA1)	$\overline{\text{IRQ}}$ (CA2)	CA2 Control	DDRA Access	CA1 Control
Control Register B (CRB) at 61343	$\overline{\text{IRQ}}$ (CB1)	$\overline{\text{IRQ}}$ (CB2)	CB2 Control	DDRB Access	CA2 Control

Note: DDRA — The Data Direction and Peripheral Register Access through bit 2 of the control Register was treated last month.

Table 3.10 CONTROL OF INTERRUPT INPUTS CA1 AND CB1

CRA-1 (CRB-1)	CRA-0 (CRB-0)	Interrupt input CA1 (CB1)	Interrupt Flag CRA-7 (CRB-7)	MPU Interrupt Request $\overline{\text{IRQA}}$ ( $\overline{\text{IRQB}}$ )
0	0	↓ Active	Set high on ↓ of CA1 (CB1)	Disabled— $\overline{\text{IRQ}}$ remains high
0	1	↓ Active	Set high on ↓ of CA1 (CB1)	Goes low when the interrupt flag bit CRA-7 (CRB-7) goes high
1	0	↑ Active	Set high on ↑ of CA1 (CB1)	Disabled— $\overline{\text{IRQ}}$ remains high
1	1	↑ Active	Set high on ↑ of CA1 (CB1)	Goes low when the interrupt flag bit CRA-7 (CRB-7) goes high

Notes: 1) ↑ indicates positive transition (low to high)  
 2) ↓ indicates negative transition (high to low)  
 3) The interrupt flag bit CRA-7 is cleared by an MPU Read of the A Data Register, and CRB-7 is cleared by an MPU Read of the B Data Register.  
 4) Of CRA-0 (CRB-0) is low when an interrupt occurs (interrupt disabled) and is later brought high,  $\overline{\text{IRQA}}$  ( $\overline{\text{IRQB}}$ ) occurs after CRA-0 (CRB-0) is written to a "one".

### TESTING THE PERIPHERAL CONTROL FLAG

We can now proceed to test the operation of the control line CA1. To do this, first connect the resistor network of Fig. 3.11 to pin 2 of SK3 of the Decoding Module. Then reset the PIA using the Reset push button on the Decoding Module, and run the following program:

```
100 A=61340
120 POKE A+1,0
130 POKE A,255
140 POKE A+1,254
200 PRINT (PEEK (A+1) AND 128)
220 FOR Z=1 TO 100: NEXT
300 GOTO 200
```



This initialises port A for output as usual, but in line 140, it places 254 into control register A. It may be recalled from last month (see Table 2.1) that the control registers for ports A and B may be directly accessed, and are located at 61341 and 61343 respectively. With 254 in CRA, bit 1 of the register will be high, and bit 0, zero. This sets up the conditions shown in the third row of Table 3.10: ie the interrupt is disabled, and the flag will be set high on a positive going transition of CA1.

The program then monitors the contents of bit 7 of the control register. It should print out a string of zeros, indicating that the flag is not set. Closing the switch in the circuit of Fig. 3.11 will set the flag, and cause the program to print out a series of 128s.


The flag will remain set (and the 128s will continue to register) even when the switch is reopened, in order that the CPU can monitor the flag when it wishes without a risk of missing the control line signal. To clear the flag, one must read (or write to) the associated data register of the PIA. Thus if we insert the line:

**210 X=PEEK (A)**

into the above program, the screen will register only one 128 after any switch closure, subsequently registering zeros, and indicating that the flag has been reset.

### PERIPHERAL CONTROL OF SPEECH OUTPUT

We are now in a position to use control line CA1 (or CB1 which functions similarly) with the Speech Board to inform Compukit when speech output is complete. The Speech Board Busy signal goes low when speech begins, returning high when a word is completed. The Busy line may thus be connected directly to CA1, and the data 1 placed in bit 1 of CRA, and 0 in bit 0. This will cause the flag at bit 7 to go high at the end of each word output, and the program can simply inspect this bit, and enter a waiting loop until it returns high, before outputting the next word. The full connections for the interface are given in Fig. 3.12.

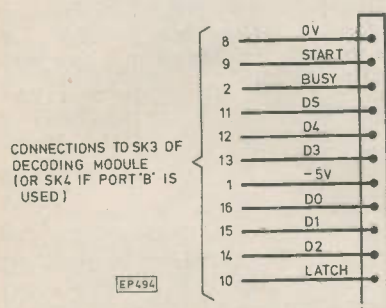

**Fig. 3.12. Connections of speech board to SK3**

### SPEECH PROGRAM

These principles have been put into practice in the program listed in Table 3.11. It performs four different functions according to a menu printed out at the start. "1" gives the full 24 word vocabulary of the board. "2" counts to any predetermined number. "3" speaks a string of figures entered via the keyboard; and "4" initiates a dice routine in which a random number from 1 to 6 is spoken at each press of the Return key.

Incidentally, this last routine uses an apparently unpublished facility of the RND function on Compukit. Calling RND(X) will give a random number *independent* of the value of X for all positive integers. But if X is negative then this has the effect of "seeding" the random number generator to a position *dependent* on the value of X, and can thus be used to start off the generator at a new point.

All four of the routines described make use of one or more of the digit and speech handling routines at lines 1000 and

```

70 REM INTERFACING UK101 PROGRAM 8
80 REM SPEECH ROUTINES
100 A=61340
120 POKEA+1,0
130 POKEA,255
140 POKEA+1,254
200 FORA1=1TO16:PRINT:NEXT
210 PRINT,"1. VOCABULARY"
220 PRINT,"2. COUNTING"
230 PRINT,"3. READOUT"
240 PRINT,"4. DICE"
250 PRINT:PRINT:PRINT
260 INPUTA
270 ONARGOTO300,450,600,750
280 GOTO200
300 PRINT:PRINT,"VOCABULARY"
320 FORM=0TO23
330 GOSUB2000
340 NEXT
350 GOTO200
450 PRINT:PRINT
460 INPUT" COUNT TOTAL";AD
470 FORA=0TOAD
480 GOSUB1000
490 FORA=-1TO1000:NEXT
500 NEXT
510 GOTO200
600 PRINT:PRINT:PRINT
610 PRINT,"INPUT NUMBER STRING"
620 INPUTWS
625 WS="0"+WS
630 GOSUB1070
640 GOTO200
750 REM DICE
760 PRINT:PRINT:PRINT
770 PRINT,"DICE ROUTINE"
780 PRINT,"ENTER RANDOM NUMBER"
790 INPUTA6
800 A7=RND(-A6)
810 PRINT:PRINT" PRESS RETURN FOR EACH THROW"
820 PRINT," PRESS T TO EXIT"
830 POKE530,1
840 POKE57088,223
850 A8=PEEK(57088)
860 IFA8=239THENPOKE530,0:GOTO200
870 IFA8<>247THEN840
880 WN=INT(1+6*RND(8))
890 GOSUB2000
900 GOTO840
910 REM
920 REM
1000 REM
1050 WS=STR$(W)
1060 PRINTWS
1070 FORW1=2TOLEN(WS)
1080 WWS=MIDS(WS,W1,1)
1085 WN=VAL(WWS)
1090 GOSUB2000
1100 NEXT
1200 RETURN
1900 REM
1910 REM
1920 REM
2000 REM SPEECH POKE
2050 POKEA,128+WN
2060 POKEA,64+WN
2070 A1=PEEK(A+1)
2090 A3=AAND128
2100 IFA3=0THEN2070
2110 FORA4=1TO100:NEXT
2120 RETURN
OK

```

**Table 3.11. Speech handling program**

2000. The first splits up a variable W into a sequence of digits WW (or if entered at 1070 does the same for a string of characters W\$). These are then output sequentially by the speech handling routine at line 2000, which simply "speaks" the digit WW, waiting until speech output is complete before a Return is executed either to the first subroutine or to the main body of the program. This is achieved in lines 2070-2100 by examining bit 7 of the PIA control register for a 1.

These two routines should be found useful in other applications of the Speech Board.

**NEXT MONTH** we will introduce an Analogue Board which plugs directly into the Decoding Module to provide Compukit with an AY-3-8910 Programmable Sound Generator, a D/A converter, an 8 channel A/D converter, and a 6522 Versatile Interface Adaptor, allowing counting and timing operations, as well as providing a second 16 bit input/output port.



# PATENTS REVIEW....

Copies of Patents can be obtained from:  
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1.45 each.

## 3-D VIEWING

Two recent patent applications protect different approaches to the transmission and display of stereoscopic or 3-dimensional TV pictures.

To obtain a realistic 3-D image it is necessary to present each eye with an image of different perspective. It is well known to project cinema films with the left and right eye images separated either by colour or optical polarisation. The audience then wears either coloured or polarised spectacles. If red or green images are superimposed on the screen then the audience wears spectacles which place a red filter over one eye and a green filter over the other. If the two superimposed images on screen are projected by differently polarised light, then the spectacles must have differently polarised filters for each eye. In new British patent application 2 040 134, filed by the Marconi Company of Chelmsford, Essex, the polarisation technique is adapted for TV use. Figure 1 shows a camera with two lenses 4 spaced apart by the natural separation distance of human eyes. Mirrors 5 and 6 and a lens 8 register the resultant two images together on a camera tube 7. Cross-polarised filters 9 and 10 optically separate the beams e.g. the polariser 9 is vertically orientated and polariser 10 horizontally orientated. Both the beams then pass through a liquid crystal cell 11 and a further polariser 12. The cell has electrodes connected to an electrical supply which changes polarity at the TV camera frame rate. This change of

electrode polarity switches the liquid crystal filter so that it either rotates the plane of polarisation by  $90^\circ$  or leaves it unchanged. The polariser 12 is of fixed character so as the filter 11 switches between its two optical states, the camera tube 7 alternatively receives images from the two halves of the optical system 2,3.

At the receiver (Figure 2) frame rate signals are extracted from the incoming video signals and used to switch the polarising behaviour of another liquid crystal cell 19. This is sandwiched against a fixed polariser 18 and a TV display tube 16. The viewer wears spectacles with cross polarised filters 21,22. As the filter 19 switches its polarisation effect in synchronism with the filter 11 in the camera, the viewer's left and right eyes respectively see only the images produced by the left and right halves of the camera optical system. This produces a 3-D effect. But as each eye sees only alternate frames there will be noticeable flicker unless the overall frame rate is artificially increased.

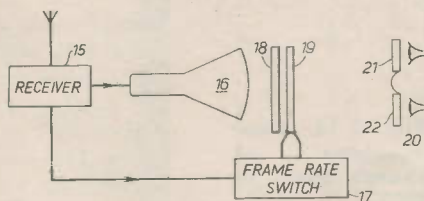


Fig. 2

At the Tokyo Electronics Show in October, 1980, Matsushita (National Panasonic) showed an apparently quite similar system in operation. Members of the public could peer through a fixed pair of "binoculars" at a TV display tube hidden inside a large decorative sphere. Switched filters in the binocular optics chopped the image to produce an impressive, but rather flickery, 3-D effect. Although Matsushita and National Panasonic have not made available any details of the system demonstrated in Tokyo it seems likely that it closely resembles that now being patented by Marconi. It thus remains to be seen who has the earliest patent priority date, Marconi, Matsushita or others working along similar lines. The Marconi date is November 1978.

The second 3-D TV system for which patents have recently been applied works on a quite different principle. William Etra of Oakland, California claims, in International

PCT patent application WO 80/01447, to have devised a technique for processing ordinary 2-D video signals so that they create a 3-dimensional effect. But the processed signals remain compatible with existing TV receivers. In other words the Etra system is claimed to offer 3-D from 3-D tv receivers and 2-D from conventional receivers.

It is already known that a pseudo-3-D effect can be produced by artificially colour-fringing out-of-focus objects with magenta and cyan. When viewed through coloured glasses the colour-fringing creates an illusion of depth but for viewers without glasses the blurs are barely noticeable. But it is expensive to modify TV cameras to produce the necessary colour fringing. Etra claims that a similar effect can be obtained, much more cheaply, by taking advantage of the change in position, from TV field to TV field, which occurs when an object is moving across the TV screen. In Europe 25 TV pictures are displayed every second, but each separate picture or frame is built up from two interlaced fields. If an object is moving fast it will be "seen" at a different position by each field and thus reproduced as a blur when the two fields are interlaced to form a full TV picture frame. The patented idea is to use this blur as a basis for colour-fringing.

Fig. 3

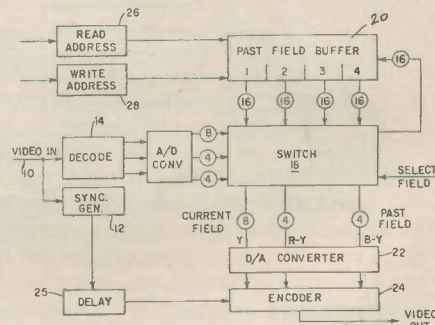


Figure 3 shows an encoder for connection after a TV camera or video recorder. The incoming video signals 10 are separated at 14 into luminance (Y) and chrominance (R - Y and B - Y) components. The components are then converted into digital code for processing to produce the required colour-fringing.

Figure 4A represents a first TV field of a picture frame with a square moving towards a circle. Figure 4B represents the


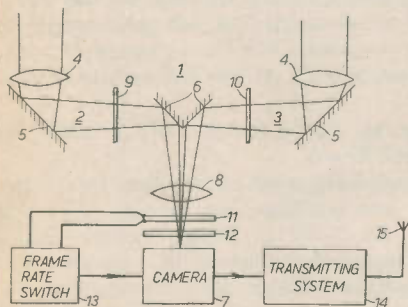


Fig. 1

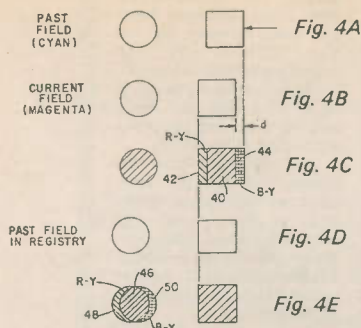



next TV field of the same frame. By now the square has moved the distance  $d$ . If the two fields are encoded in complementary

colours (e.g. cyan and magenta) then by combining the two fields a colour-fringing effect is achieved. Figure 4C shows a combination of the two fields. The stationary circle includes exactly matching cyan and magenta images without any fringing, while the moving square is depicted by mis-registered cyan and magenta squares. The mis-register shows up as cyan fringing to one side and magenta fringing to the other. According to the inventor if the composite image of Figure 4C is viewed through terest in the TV picture should consist of achieved. It is advantageous however, to take the invention a step further. In practice it is preferable that the major objects of interest in the tv picture should consist of perfectly registered colour components. Usually the major object of interest will be

moving—eg. a sportsman running, so Figure 4D and 4E shows how the fringe effect is transferred to the stationary object (the circle) to leave the moving object (the square) free from fringing. The digital signals corresponding to the last four fields are routed by write address 28 to a buffer circuit 20 for temporary storage.


Either manual or computer controls are then used to track a selected moving object and so keep it free from fringing. Selected past and present TV fields are brought into registration by advancing or retarding the starting address of a read circuit 26 for the buffer 20. The technique can of course provide only "psychophysiological" or pseudo-3-D, i.e. the 3-D effect is artificial rather than a true representation of the perspectives seen by a spaced lens camera.

## POINTS ARISING

### TELETEXT (August 1980–November 1980)

Five problems have come to light with the Teletext project:

1. The supplied VDM on the tuner board should have an internal wire link to bring the video output signal to pin 12. The necessary link is shown in Fig. 1.

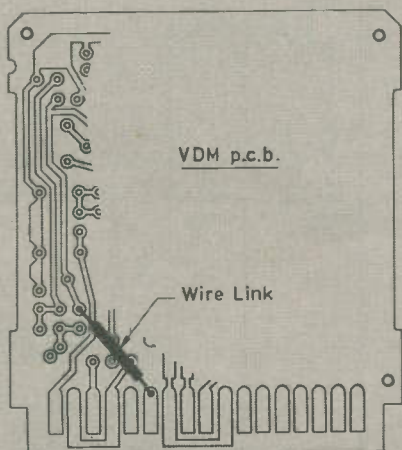

**Fig. 1. VDM p.c.b. showing the wire link required to bring the video output signal out to pin 12**

2. If the PE1X is used on the Video Summer Board then pins 17 and 10 on the daughter board (Fig. 2.9) should be linked, to bring the blanking signal out to plug 3.
3. The 5V supply for the buffer modification (Fig. 4.3) should be obtained from IC14 pin 18 and the earth connection from IC10 pin 8.
4. The p.c.b. design for the Tuner Board shown in Fig. 4.4 should have pin 11 of IC3 connected to earth and not pin 12.
5. To ensure reliable operation of the blanking signal a pull-up resistor should be used (5k6). This should be connected from pin 10 IC19 to the 12V supply on the Video Summer Board.

## News Briefs

JVC'S VIDEO Information Centre is planning a course for the general public on "Camera Operation and Home Video Techniques", and is designed to help users to get the most from their video equipment.

The course will start this year and probably consist of two days of instruction. After the demand for such a course has been assessed, it will be introduced on a weekday basis or as a weekend course.

The Video Information Centre offers professional services to the domestic user — as well as being a showroom for the full range of JVC video equipment, VIC has a fully equipped small studio, editing and dubbing facilities and a tele cine conversion unit among its many facilities. Expert advice is on hand to help users and enquirers with any problem concerning video.


The new course is an additional part of JVC's educational role in video. VIC already runs two courses for dealers, and a third will soon be introduced.



The Video Information Centre is open from 10.00 am–5.00 pm on weekdays and 9.30 am–12.30 pm on Saturdays.

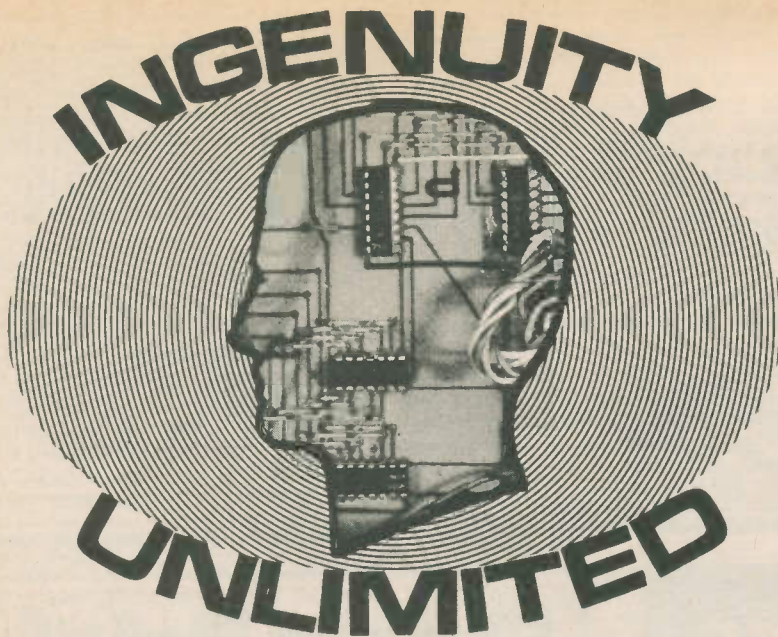Any member of the public who may be interested in the new course should contact Mike Whyman at the JVC Video Information Centre at 82 Piccadilly, London W1 (01-450 2621).





A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit your idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere.

## PIP GENERATOR

**T**HIS is an improved version of a circuit that was built for use in a stage play, wherein a player took the role of the telephone "speaking clock", and the circuit generated the "pips".

One push-button activates the circuit (after switch on) after which it cycles through a count of three pips before resetting itself ready for the next push-button operation.


IC1c is configured as a free-running astable multivibrator, with a mark-space ratio of 1:2 and a frequency of approximately 1Hz. Its output provides both clock pulses for IC2, and gate pulses for IC1d, which oscillates at audio frequency.

D1, D2, R8, R9, R10 and TR2, form a two input NOR gate, which gates the audio signal to the amplifier (TR3), and the speaker, depending on the condition of the Q0 output of IC2 (pin 3). This pin is held "high" when IC2 is in its reset state, and goes low on the first clock pulse after the reset is removed.

IC1a and IC1b form a conventional flip flop which is "set" by S1 being momentarily closed, and "reset" when TR1 is switched off by a "high" output from IC2, Q4 (pin 10). Pin 10 goes "high" on the rising edge of the fourth clock pulse from IC1c after the circuit has been activated.

The circuit has always been found to assume its reset state after switch 2 was closed and therefore no initialising circuitry was included.

John D. Ritchie,  
Cranwell,  
Lincs.

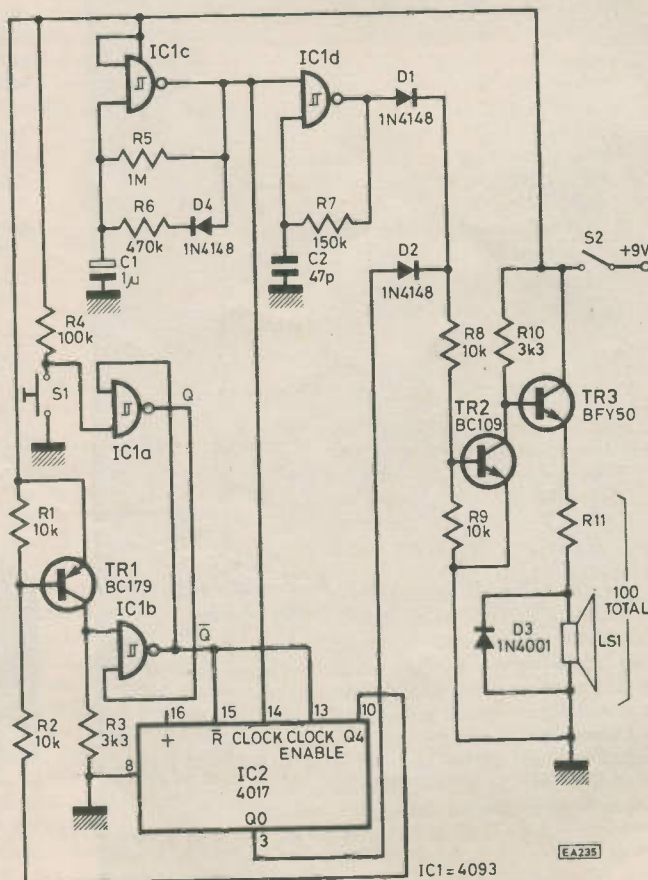



## GRAPH DISPLAY UNIT



**T**HIS is a device which will display a graph on a cathode ray oscilloscope or converted TV. The graph may be in block form, or a point to point configuration. It will give a simulated computer display with applications in the sales office or classroom and may be expanded to give more entries.

IC1 functions as a continuous clock feeding into IC2 decade binary adder. The four outputs are decoded by IC3 which now operates as a sequential switch with open collectors.

At the decode state 0, C1 is grounded for the duration of one clock pulse, but subsequently begins to charge up via VR1. This potentiometer must be adjusted so that it grounds in the next cycle, before the upper part of the exponential curve is reached. This sawtooth waveform is fed into the X input of the scope. The outputs 1-9 each go to variable resistors which set up wave amplitude. These join a common load R1 where the Y signal is generated. A capacitor C2 of about 200nF will angle off the leading edges of the square waves to produce a simulated point to point graph.

One may be tempted to omit the X generator but during adjustment severe sync problems arise. Rather than calibrate the potentiometers, a simple acetate sheet graticule will permit easy setting up. The perimeter can include a central zero line and minus figures can be entered by simple manipulations.

B. Darnton,  
Romsey,  
Hants.

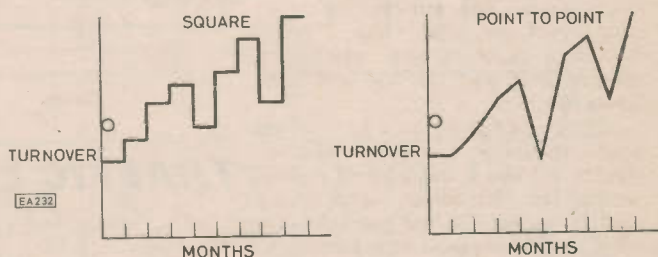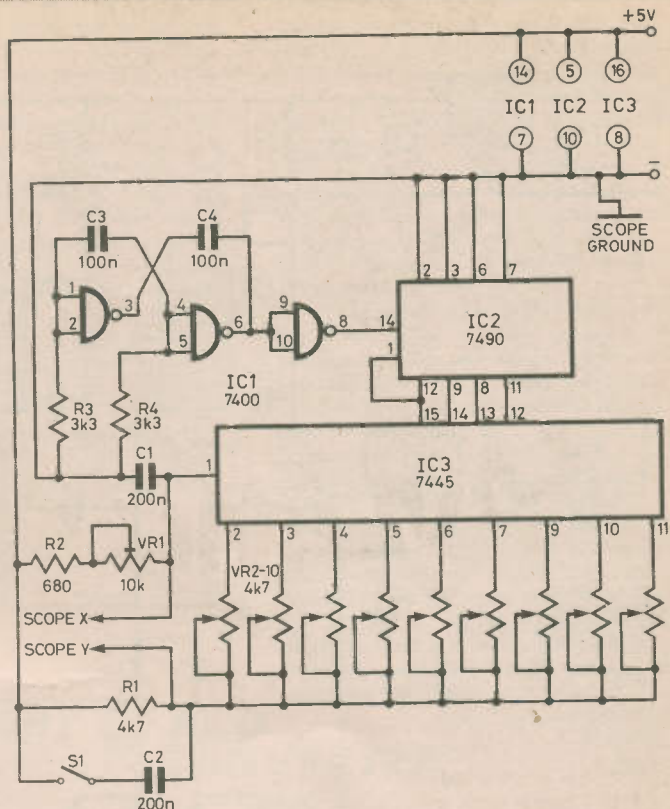


**E**VER wanted to know how far a thunderstorm is from you? One old method was to count the interval between the lightning and the thunder, giving an answer in miles. But as sound travels at 330m or 1090 feet/second this method is highly inaccurate.


To measure this more accurately a device is needed which counts at approximately 1 count per 3 seconds (sound travelling approximately 1km in 3 seconds). The circuit consists of a 555 timer oscillating at 3.33Hz driving a two digit counter. Display X1 shows  $\times 0.1$ km and X2  $\times 1$ km. To operate the unit S1 is set to the stop position and S2 pressed to reset the counters. When a lightning flash is seen S1 is set to the start position and returned to the stop position when the thunder is heard. The distance is then read.

R. Jonasar  
Aylesbury  
Bucks

## STORM DISTANCE ESTIMATOR

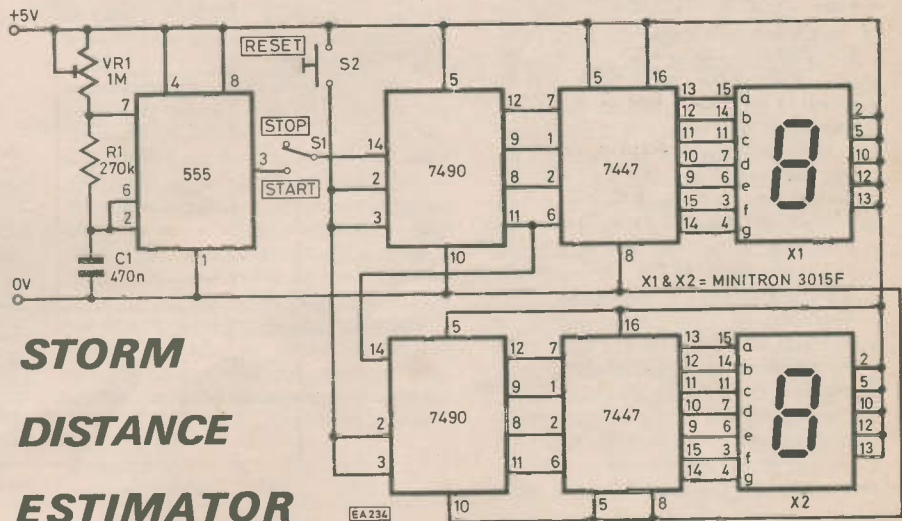



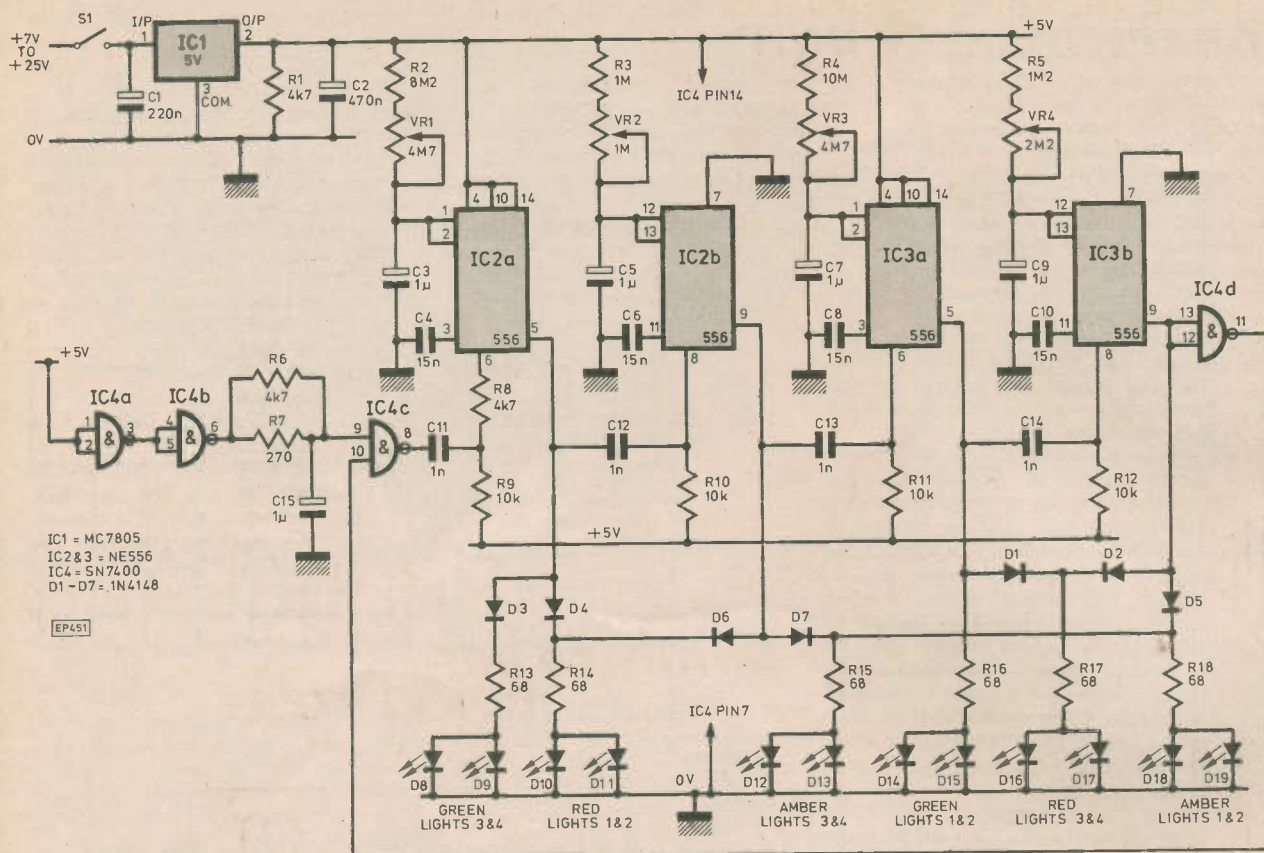

## TRAFFIC LIGHTS

THE circuit is basically two 556 i.c. timers used in a sequential mode to action the sequencing of two sets of traffic lights. The traffic lights being 0.2in diameter. I.e.s coloured red, green and yellow. Each half of the 556 is responsible for the respective times generated for the colour sequence, commencing with red eight seconds, red/yellow one and half seconds, green fifteen seconds and amber two seconds, these times may be adjusted by altering values of R/C connected to pins 1 and 2/12 and 13, respectively.


The timers are connected in a monostable mode, the first half of the timer being triggered by negative going pulse through pin 6, output 5 goes positive causing the appropriate colour to be displayed through the respective blocking diode. As the timing period elapses output 5 falls to zero transmitting a negative going pulse

through a coupling capacitor to pin 8, triggering the second timing period and a new colour display.

These operations are in turn repeated on the second 556 also further displaying colour sequences, where upon final negative going edge from pin 9 is fed to a SN7400 gate ready to repeat the whole sequence again. The 4.7 kilohm resistor in series with initial trigger will ensure reliable triggering. The SN7400 gates with delay is included only to overcome any spurious triggering at initial switch on.

The colour sequence discussed is for the first set of directly opposite traffic lights note the other pair have exactly the opposite colour sequence of green, amber, red, red and amber.

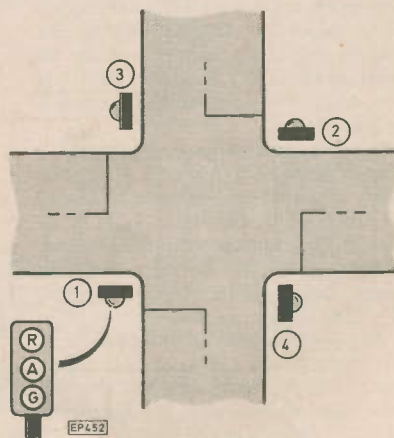R. J. Jones,  
Keighley,  
West Yorkshire.






Here the input data is latched by a set of 7475 i.c.s. This data is then compared with the output of a binary counter which counts from zero upwards. The comparator is formed by a set of

When the latched input data and the outputs of the binary counters become equal, the comparator inhibits the clock. At this instant the data in the BCD counters are transferred to the output by another set of 7475 i.c.s.

The clock is built around a 7400 and the frequency is set by C1 at 10 MHz. It can be changed, if necessary, by changing C1

The circuit as shown is for 8 bit binary input, but it can be easily expanded or reduced by using appropriate numbers of counting i.c.s both in the input and the output side. The input and output latches can be eliminated if they are found redundant in a particular application. This circuit can act as a universal converter if the counting i.c.s are changed according to the need. For example, if 7490s i.c.s are used in the input side and 78493s i.c.s at the output, the circuit will behave as a BCD to binary converter. The maximum conversion time (T) is given by the formula:  $T = 2^n / f$  seconds, where n is the number of bits in the input word. Here  $f = 10^7$  and  $n = 8$  and hence  $T = 25 \mu s$ .

Kunal Sen,  
Calcutta,  
India.

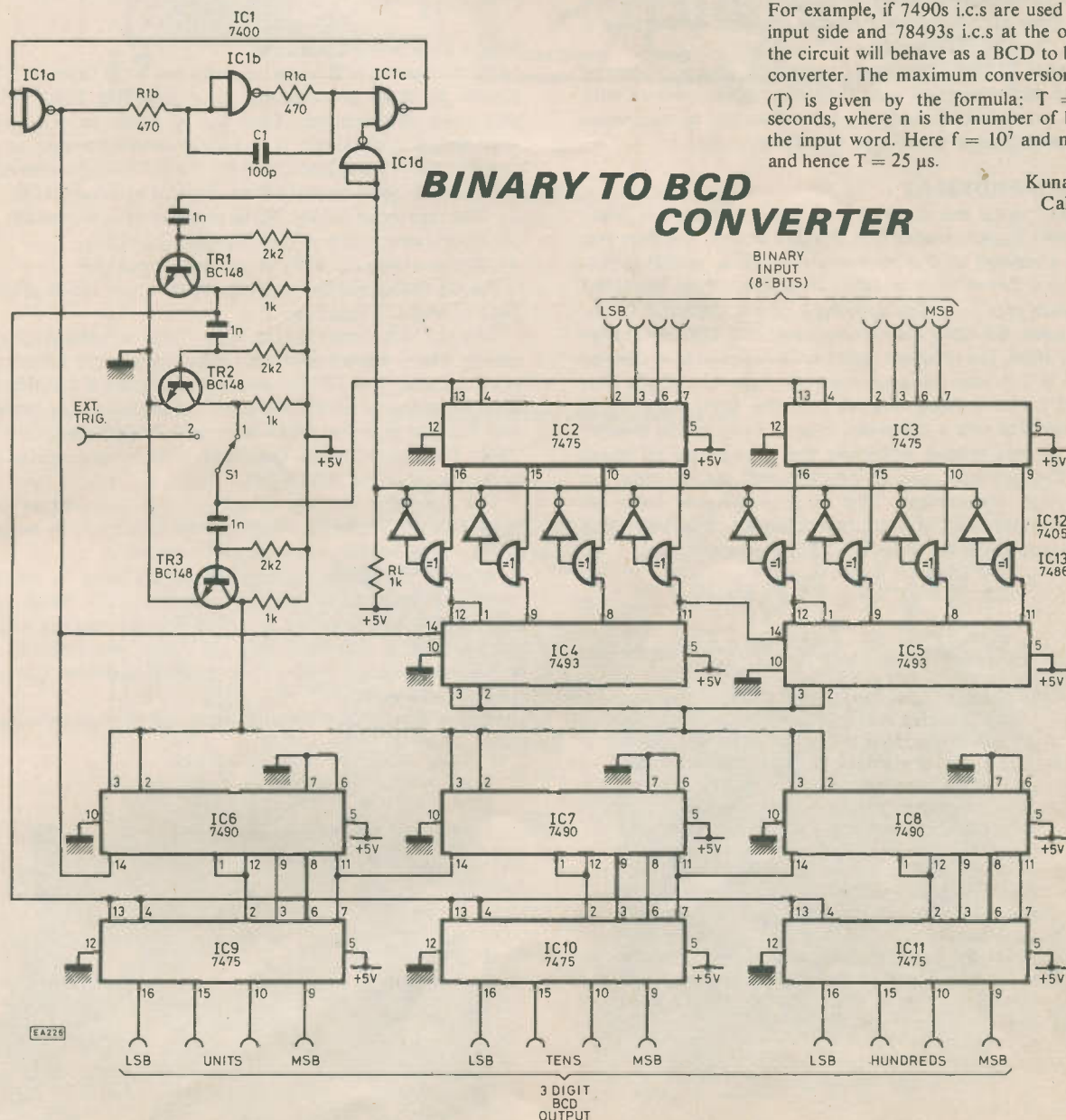



# Digital COUNTER/TIMER

PART 2

Dr. MARK SAWIKI and ALEX KOWALEWSKI B.Sc.

**C**ONSTRUCTION of the Universal Counter-Timer is straightforward using the component layout as shown in Fig. 2. (components side).

The only components which are soldered on the copper side are two capacitors i.e.  $33\mu\text{F}/10\text{V}$ —tantalum type and a small ceramic  $100\text{n}$ . The reason for the above pair of capacitors being soldered into the copper side (main Board) is simple; they should be as close as possible to the pins 8 and 18 on the ICL 7216A chip.

The Intersil 7216A Universal Counter i.c. is manufactured using a low voltage metal gate C-MOS process, and as with all CMOS products, should not be subjected to excessive levels of static charge in storage, handling or use.

## GENERAL HARDWARE

All the electronics are planned into three p.c.b.s, i.e. Main Board, Power Supply Board and Display Board. The first two should be screwed to the aluminium chassis, which is formed out of a 2mm thick aluminium sheet, using insulated plastic screws and nuts. The prototype of the Universal Counter/Timer uses standard instrument case (RS 509-901) also obtainable from many other electronic suppliers. A display "window" is cut into the enclosure front panel and the display board p.c.b. is fixed directly into the front panel. It is recommended to use a polarised filter in front of the display segments as this greatly improves the contrast of all visual displays. The authors used a red coloured display filter on the prototype instrument. The l.e.d. segments may be soldered directly into the p.c.b., however, the use of a suitable segment socket (RS 401-730) is possible.

All front panel slide and rotary controls are absolutely standard, obtainable from practically everywhere, one suggestion, however seems to be worth noting; after a few months of using the instrument, the possibility of replacing the HOLD and RESET subminiature rocker switches with subminiature pushbuttons, but obviously this is quite non-critical, merely an operational preference.

## SOCKETS AND CABLES

Both channel A/B input sockets are a 75 Ohms BNC type similar to most professional counters. The BNC socket is also used on the output from the oscillator (mounted at the rear of the enclosure). It is highly recommended to use a proper quality screened cable for the following connections:

- 1) Channel input socket (A) to channel attenuator (A)
- 2) Channel input socket (B) to channel attenuator (B)
- 3) Attenuator output (A) to pre-amp input (A)
- 4) Attenuator output (B) to pre-amp input (B)



As on many similar occasions, all input leads should be kept as short as feasible.

The 7216A Intersil chip is a really excellent one from nearly every aspect and no problems should occur during construction. The 7216A counter chip uses a 10MHz quartz crystal timebase which in this prototype was supplied by RS., and housed in a metal can with wire ended leads (RS. 307-799). The above crystal should be used in conjunction with a crystal socket (RS. 401-936).

For convenience and simplicity, 20 way ribbon colour-coded cables are used, which can be split into any number of ways by tearing between the conductors.

A word about the voltage regulators used in the instrument's power supply unit. Both the TO3 fixed voltage (LM309K) regulators are soldered directly into the p.c.b. and no heatsink is required. The LM309Ks are rated at about 1.2A each (Ref.  $5 \pm 0.2\text{V}$ ) and the instrument uses about 150mA at 5V per rail.

The Power ON/OFF control is a red neon illuminated rec-

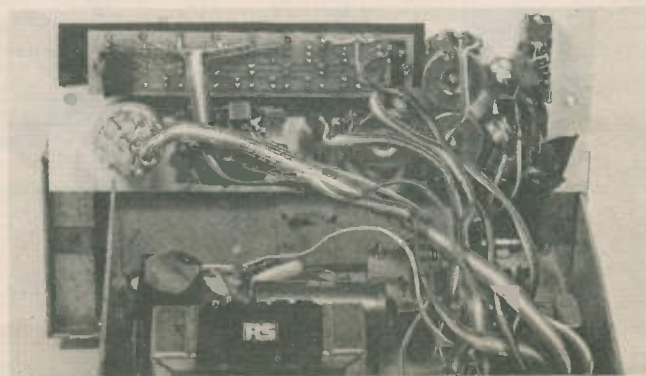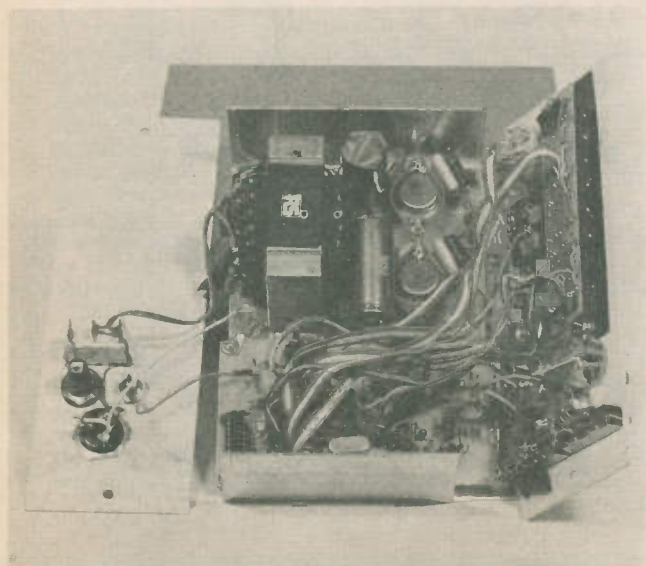




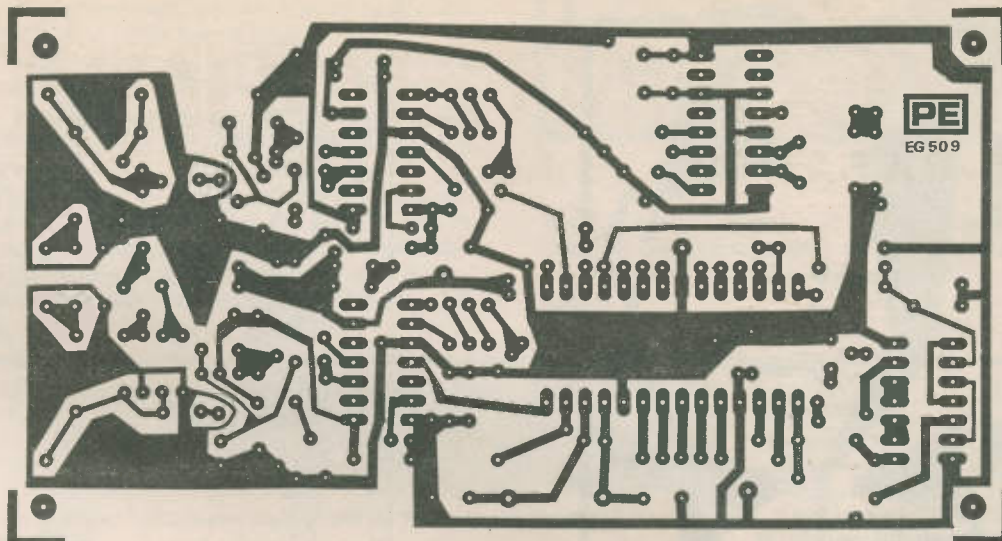


Fig. 2.1. Main Board p.c.b. (actual size)

Fig. 2.2. Main Board component layout

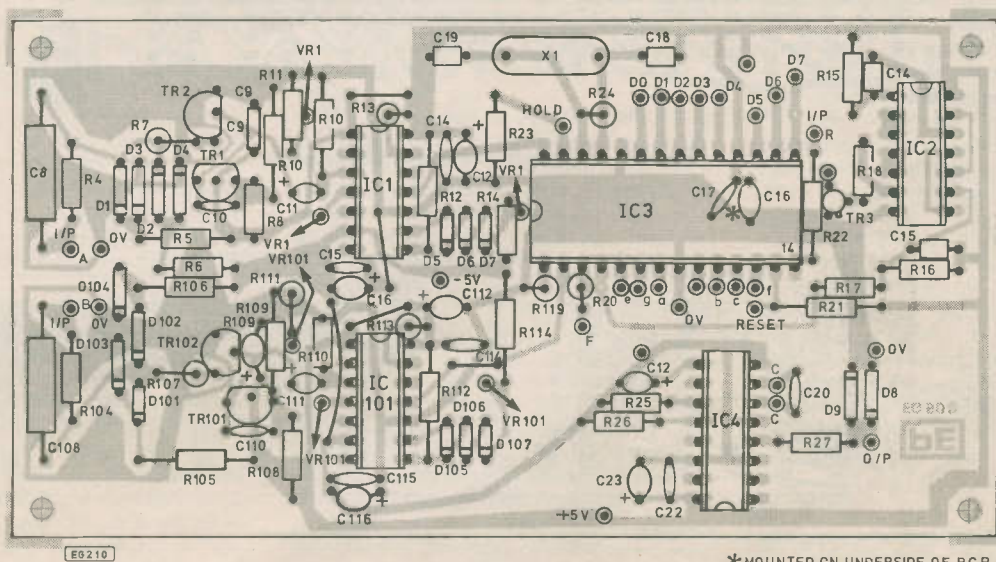



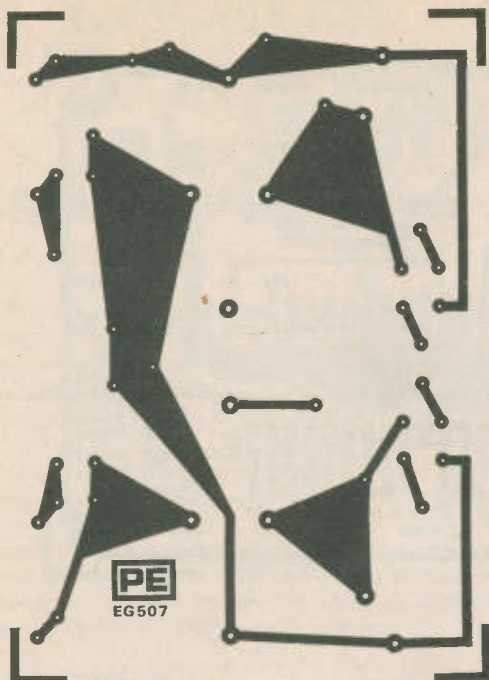


Fig. 2.3. PSU printed circuit (actual size)

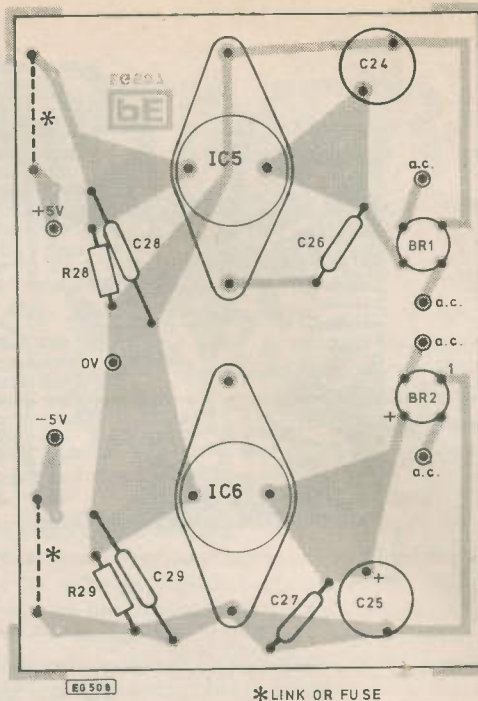


Fig. 2.4. PSU component overlay

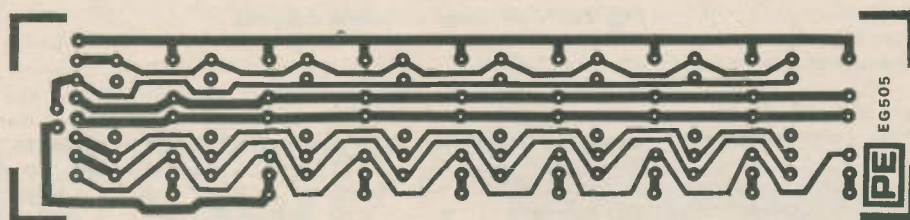


Fig. 2.5. Display Board p.c.b. (actual size)

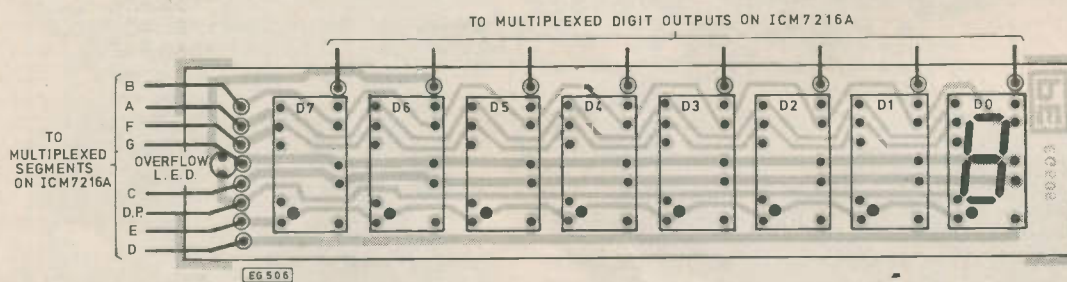


Fig. 2.6. Display Board component overlay




tangular I.E.C. switch mounted on the rear side of the instrument, and a safe 3-pin earthed type mains "Euroconnector" type socket is used.

The supply protection is 500mA/240V "Fast-Blo" 20mm glass type fuse, housed in the appropriate type of fuseholder and mounted directly next to the mains socket.

After completing the assembly of all the components and sub-systems, no alignment or tuning is required and the instrument should work from go. Because of the nature of the ICM 7216 chip, the frequency will be displayed in KHz, and time is displayed in  $\mu$ Sec.

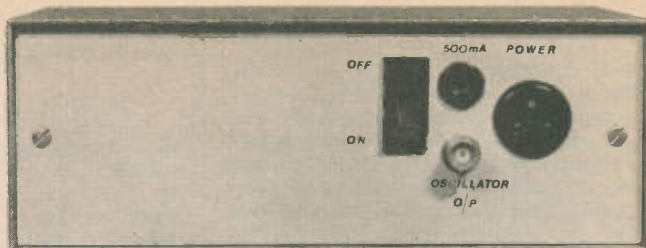The display is multiplexed at 500Hz with about 12.5 per cent duty cycle for the individual digit. The ICM 7216A is designed for common anode display and a typical peak segment current consumption is approximately 25mA. An interesting point is that Intersil claim that in the "Display Off"



mode both digit drivers and segment drivers are turned off, enabling the above display to be used for other functions should the instrument be incorporated into a multi-function system. ★

## MICRO PROMPT.

The hardware and software exchange point for PE computer projects

### OF TELETYPE AND BAUD

Sir—As yet another satisfied compukit UK101 owner I have had particularly great pleasure from the many notes and updates in relation to this system. In this connection I have made a couple of observations that might interest other readers, as well. First, I have found that the hardware modification described by Dr. A. A. Berk in his 'compukit update' of March 1980 can be simplified somewhat.

However, there is no need for his point (3). Leaving pin 11 of IC63 connected with pin 11 of IC57 instead of moving it to pin 12 will still give the 'divide-by-nine' effect that is the aim of the rearrangement. The main difference will be that of the duration of the pulse fed from IC57 to IC63. But since it only functions as a clock pulse for IC63, its duration is not critical.

I quite agree that it may be worth while to make the modification switchable, and this will be much easier by leaving pin 11 of IC63 tied to pin 11 of IC57. The remaining changes, including the shift from 'C3' to 'C5' of IC60 for the clock pulses to be fed into IC57, can then be completely taken care of using any ordinary type of double pole, double throw switch. I have found this to work perfectly!

On the other hand, in his 'compukit update' of June 1980, Dr. Berk also refers to a soft BAUD rate modification suggested by Mr. C. S. K. Clapp. It works through the modification of the 6850 ACIA routine, by POKEing 82 into its address of 61440, in combination with the modifications shown in his Fig. 2. As can be seen, the resetting of the counter IC57 after modifying is obtained—not by 'clear'ing, as originally—but by loading a binary number into its data inputs a, b, c and d on reaching its twelfth count. After the modification one of these data inputs is tied to the 'RTS'-output of the ACIA. If this output is at a logical 'low', IC57 will then receive zero to its data inputs (all the others remaining permanently

grounded). During initialization through the compukit monitor routine, the 'RTS'-output will be set to a logical 'low' level, corresponding to just this case. Consequently, the counter will then go through a 'divide-by-thirteen' cycle, resulting in 300 BAUD, exactly as in the unmodified case.

By POKEing 82 into the ACIA address, one of the changes produced will be the setting of 'RTS' to a logical 'high' level. This, then, results in presetting the IC57 counter to a non-zero number, with the overall consequence of reducing the counting cycle. However, by connecting 'RTS' with pin 4 (data input b) of IC57 the effect of preloading with binary 0010 (decimal 2) will result, giving a net 'divide-by-eleven' cycle. This is clearly wrong. 'RTS', from pin 5 of IC14 should instead be tied to pin 5 of IC57! This gives preloading with binary 0100 (decimal 4), resulting in a 'divide-by-nine' cycle.

The other effect of 'POKE 61440,82' is to change the internal division ratio of the 6850 ACIA from 1:16 to 1:64 (while maintaining the output format of 1 start bit +8 bits +2 stop bits, with no parity, also used in the default case). Thus, the resulting BAUD rate can readily be calculated from the 125 kilohertz pulse train that IC57 receives from 'C3' of the master counting chain:

$$125000/(9 \times 2 \times 64) = 108.5$$

This is, of course, exactly the same BAUD rate as that obtained by the hardware modifications described earlier, and it is definitely close enough to the ideal 110 BAUD for problem-free operation with an ordinary teletype printer. I have, as a matter of interest, made it a point here to support this claim by choosing to write these lines on my compukit and have them printed just on such a printer, hooked onto my 108.5 BAUD converted interface through a 20 milliamps current loop. For convenience, I chose the hardware version, myself (although I also tested out the soft BAUD

modification). I now can select to my heart's delight from tele-type 110 BAUD, cassette 300 or 600 BAUD, and finally processor frequencies of 1 or 2 megahertz! All works very reliably.

I have nothing but praise for the potential of the compukit system, considering its reasonable price class. And I hope, among other things, to see a great many more write-ups relating to it, in future issues of your interesting magazine.

Gisle K. Dyvik  
Norway

### UNCRASH

Sir—During my thirteen months use of my Ohio Superboard, I have discovered a few most interesting and original short cuts for anyone using the machine. One I am submitting for publication here. The routine below can be used for any Ohio machine, and the UK101. Its purpose is to get back into BASIC with the user's program intact. During use of the machine, page zero can be disrupted due to a careless POKE, programming error, etc. This is where my routine comes in. With page zero in disarray, it is impossible to get back into BASIC and/or save your program or in any way avoid the loss associated with a crash. However, by doing the following, if the RAM storing the program has not been disrupted, the user may continue programming in the usual way as though nothing had happened.

- 1) **PRESS BREAK, C, BREAK, M**
- 2) **TYPE: /4C, 74, A2, 4C, C3, A8, 05. AE**
- 3) **PRESS BREAK, W**
- 4) A warm start should now occur. You may now carry on in the usual way.
- 5) **NOTE:** If locations 11 and 12 have been changed, they will now be restored to their original value. They may be changed back to your values by POKE-ing them in the usual way.

R. Wells,  
Margate.

### MAPPING, GET IT RIGHT!

Sir—In your September issue Mr. M. C. Mannering pointed out an error in the address decoding of the UK101. However a second fault also exists in the decoding. The keyboard address decoding only uses address lines A15-A10 for generating the



keyboard enable signals  $\overline{RKB}$  and  $WKB$ . This results in the keyboard occupying a 1K block of memory from DC00-DFFF (Hex), instead of just one location as suggested in the manual.

As Mr. Mannering found these faults only show up when experimenting with memory mapped peripherals. Thus anyone contemplating adding an expansion should have a clear idea of what areas of memory are available. With this in mind before expanding my Compukit, I made out two useful charts.

The first is a hardware memory map which is intended to show exactly where devices are found in memory and where free blocks occur. The second chart indicates what address decoding is available on-board, and the range of addresses which they cover.

These charts show the two faults, but also indicate the existence of useful empty blocks of memory and spare decode lines available. Two separate 1K blocks with Read and Write Enables are available and would be perhaps suited to an expansion to the video RAM or anything else requiring separate Read, Write Enables. IC17 provides effectively 7 spare decode lines for blocks of 256 Bytes from F100-F7FF. This is achieved by using A10 as another "Enable" line. This way two expansion's may share a common output provided A10 activates one when high and another when low. Spare "Enable" lines suitable for 8K RAM cards are also available.

I think these charts would be very useful for any of your readers wishing to expand their Compukit, as it helps avoid mistakes like placing a programmable sound generator in the ACIA memory block (or didn't you notice that slip?).

David McDonnell,  
Eire

Hmmph... Yes, we did notice... afterwards! See "PSG Bug", Micro Prompt, November 1980—Ed.

## XY VIDEO

Sir—I would like to put forward a much more simple way to 'POKE' information onto the screen. The statement is:

```
LET P=53196 + X + (Y*64)
POKE P,N
```

where X is the x-coordinate  
Y is the y-coordinate

X must be > 0 and < the end of the line  
Y must be > 0 and < 17

eg. If X=24 and Y=7 and N=161, then a white block will be placed at location 53668.

Gerhart Ellett,  
Gt. Yarmouth.

## ALWAYS A SIMPLER WAY

Sir—In response to Mr. J. Plews's letter, the INT function in BASIC always rounds down. If one wishes to round to the nearest integer you have to add .5 (ie. ?INT (10/(2↑1) + .5) this returns to the value 5.

I'm sure you could have found something better to publish in place of "Just A Little Something". This three line program does

## UK101 HARDWARE MEMORY MAP

Fig. 1

Location		Memory		COMMENTS
Hex.	Decimal	Type		
0000	0	RAM		PAGE ZERO; SCRATCH PAD RAM
T0				
00FF	255			
0100	256	RAM		PAGE ONE; STACK
T0				
0221	545			
0222	546	RAM		UNUSED—USING NEW MONITOR EPROM This region seems to exist between 0223 and 02FA
T0				
02FA	762			
0301	769	RAM		PAGE THREE; BEGINNING OF BASIC WORKSPACE
				END OF FIRST BLOCK OF 1K RAM
03FF	1023	RAM		END OF 2K OF RAM
07FF	2047	RAM		END OF 3K OF RAM
0BFF	3071	RAM		END OF 4K OF RAM
0FFF	4095	RAM		END OF 5K OF RAM
13FF	5119	RAM		END OF 6K OF RAM
17FF	6143	RAM		END OF 7K OF RAM
1BFF	7167	RAM		END OF 8K OF RAM
1FFF	8121	RAM		END OF ON-BOARD USER RAM
				END OF 16K OF RAM
3FFF	16,383			END OF 24K OF RAM
5FFF	24,575			END OF 32K OF RAM
7FFF	32,767			END OF 40K OF RAM
9FFF	40,959			HIGHEST ADDRESS TO WHICH USER MEMORY MAY BE CONTINUOUSLY EXPANDED
A000	40,960	ROM		BEGINNING OF 8K BASIC INTERPRETER
T0				
BFFF	49,151	ROM		END OF BASIC INTERPRETER FREE; TOTAL = 4K
C000	49,152			
T0				
CFFF	53,247			
D000	53,248	RAM		VIDEO REFRESH MEMORY TOTAL = 1K
T0				
03FF	54,271			
0400	54,272			FREE; TOTAL = 2K
T0				
0BFF	56,319			
D000	56,320	PERIPHERAL		KEYBOARD OCCUPIES THIS BLOCK TOTAL = 1k
T0				
DFFF	57,343			
E000	57,344			FREE; TOTAL = 4K
T0				
EFFF	64,439			
F000	61,440	PERIPHERAL		ACIA; TOTAL = 256 BYTES
T0				
F0FF	61,695			
F100	61,696			FREE; TOTAL = 1791 BYTES
T0				
F7FF	63,487			
F800	63,488	ROM/EPROM		OPERATING MONITOR
T0				
FFFF	65,535			END OF DIRECTLY ADDRESSABLE MEMORY

the same thing, but for any base less than ten.

```
10 INPUT "NUMBER, BASE"; BS, A
20 FOR B = 1 TO LEN (BS):
  T = T + VAL (MID$(BS, B, 1)) *
  A ↑ (LEN(BS) - B): NEXT
30 PRINT BS; "=", A: RUN
```

R. Armstrong,  
Kilmacollm.  
Renfrewshire.

## NULL RETURN RECTIFIER

Sir—In the July 1980 Micro Prompt, David Swash pointed out that for the UK101, if Return is pressed in response to an INPUT, then there is a return to command mode, but the program can be restarted using Cont. Although this is true, it is not always very useful, for example if the VDU display is a combination of direct mapping and PRINT statements.

The problem can sometimes be avoided by keyboard polling, or by PEEK (531), this



## UK101 ADDRESS DECODING

**Fig. 2**

NOTE: all outputs are active low

Range (Hex)	IC	Pin	In	
Low	High	No.	No.	Use
0000	1FFF	23	15	8K BLOCK; ENABLES IC22
0000	03FF	22	7	RS0: 1K RAM ENABLE
0400	07FF	22	9	RS1: 1K RAM ENABLE
0800	0BFF	22	10	RS2: 1K RAM ENABLE
0000	0FFF	22	11	RS3: 1K RAM ENABLE
1000	13FF	22	12	RS4: 1K RAM ENABLE
1400	17FF	22	13	RS5: 1K RAM ENABLE
1800	1BFF	22	14	RS6: 1K RAM ENABLE
1C00	1FFF	22	15	RS7: 1K RAM ENABLE
2000	3FFF	23	14	8K BLOCK; UNUSED
4000	5FFF	23	13	8K BLOCK; UNUSED
6000	7FFF	23	12	8K BLOCK; UNUSED
8000	9FFF	23	11	8K BLOCK; UNUSED
A000	BFFF	23	10	8K BLOCK; ENABLES IC17 DECODER No. 1
A000	BFFF	15d	13	BS BASIC SELECT FOR 8K ROM
A000	A7FF	17	7	BS0; BASIC ROM SELECT
A800	AFFF	17	6	BS1; BASIC ROM SELECT
B000	B7FF	17	5	BS2; BASIC ROM SELECT
B800	BFFF	17	4	BS3; BASIC ROM SELECT
C000	DFFF	23	9	8K BLOCK; ENABLES IC20 $\bar{V}$ LINE ALSO DECODES THIS BLOCK
D000	D3FF	20	12	1K BLOCK; DECODES VIDEO RAM ON READ PORTION OF R/W CYCLE
D000	D3FF	20	7	1K BLOCK; DECODES VIDEO RAM ON WRITE PORTION OF R/W CYCLE
D400	D7FF	20	13	1K BLOCK; ENABLED ON READ PORTION
D400	D7FF	20	9	1K BLOCK; ENABLED ON WRITE PORTION
D800	DBFF	20	14	1K BLOCK; ENABLED ON READ PORTION
D800	DBFF	20	10	1K BLOCK; ENABLED ON WRITE PORTION
DC00	DFFF	20	15	1K BLOCK; ENABLES KEYBOARD ON READ
DC00	DFFF	20	11	1K BLOCK; ENABLES KEYBOARD ON WRITE
E000	FFFF	23	7	8K BLOCK; ENABLES ACIA AND MONITOR ROM DECODING
F000	F0FF	17	12	256 BYTES; ACS—ENABLES ACIA ASSUMING A11, A10 = 0
F100	F1FF	17	11	256 BYTES; ASSUMING A11, A10 = 0
F200	F2FF	17	10	256 BYTES; ASSUMING A11, A10 = 0
F300	F3FF	17	9	256 BYTES; ASSUMING A11, A10 = 0
F400	F4FF	17	12	256 BYTES; ASSUMING A11 = 0, A10 = 1
F500	F5FF	17	11	256 BYTES; ASSUMING A11 = 0, A10 = 1
F600	F6FF	17	10	256 BYTES; ASSUMING A11 = 0, A10 = 1
F700	F7FF	17	9	256 BYTES; ASSUMING A11 = 0, A10 = 1
F800	FFFF	19	6	2K; MCS—ENABLES MONITOR ROM

### COMMENTS

space. For numeric inputs this will produce a REDO error, and should be replaced by 30H. Pressing Return will then INPUT zero.

A slight modification to this subroutine enables a program to demand a password, and for the password to be entered without printing to the screen. The modification is that the accumulator is not pushed to stack, and the pull is replaced by a load accumulator instruction. Whatever is loaded will be printed instead of the typed characters.

This modified routine should be called only for the password INPUT, as in the following example:

05 POKE1,0:POKE2,0:POKE 530,1

10 DATA..... } To  
POKE  
subroutine

20

30

50 PRINT CHR\$(12)

60 PRINT "PASSWORD?";

70 POKE538,48 : POKE539,2

80 INPUT PS

90 POKE538,212 : POKE539,251

100 IF PS="UK101" THEN 150

110 T = T + 1:IF T = 2 THEN PRINT  
"PROG. ABORTED AND  
ERASED":NEW

120 GOTO 60

150 PRINT "ACCEPTED"

160 REM BODY OF PROGRAM

This gives you two chances to give the password—in this case UK101—and if you fail erases the program. It prevents the use of Return and then LIST to discover the password, Reset, (W)arm Start, LIST is jammed by line 05, as is Control C. It still allows entry to the Monitor, but protecting against this is probably excessive for most programs likely to run on the UK101.

Bob Potter,  
Oxford.

makes string input difficult. The method I prefer is a very simple subroutine which prevents the Basic Interpreter from returning to command mode on a null INPUT.

The input buffer is in zero page, 13H to 59H, and is terminated by 00H. If Return is pressed in response to INPUT then 00H is stored in 13H. This is the flag for return to command mode in the INPUT routines. Most of the INPUT subroutines are within ROM, and not directly modifiable. However there is a vectored jump to output the characters to the VDU. The routine is corruptible at this point.

The subroutine, for the new Monitor ROM, is:

```
0230      48      PHA
0231      A5 13    LDAZ $13
0233      D0 06    BNE $023B
0235      85 14    STAZ $14
```

```
0237      A9 60    LDAIM $60
0239      85 13    STAZ $13
023B      68      PLA
023C      4C D4 FB JMP $FBD4
```

This can either be entered directly using the Monitor, or POKEd by a BASIC routine at the beginning of the program. It is protected from Reset, and does not need memory sizing.

To be initialised, the output vector in 021AH,021BH needs to be changed from FBD4H to 0230H. Again this can be using Monitor, or POKE538,48:POKE539,2 Reset restores the usual vector so POKE is preferable.

The 60H in 0238 is the character INPUT by pressing Return in response to an INPUT statement. In my UK101 character set ASCII 60H prints a space but can be distinguished from 20H, the usual ASCII

## DEVELOPMENT TOOL?

Sir—In the July issue of Practical Electronics you published two programs, a variable save and a screen editor program, although it is possible to load both these programs into memory it is not possible to run them both at the same time. This is an obvious disadvantage as they are both essential aids to program development, and one without the other is a bit of a hindrance to program development. I, having only just started to unravel the mysteries of machine code and not knowing an awful lot about it, was wondering if it is possible to link these two programs together to produce a very useful program development tool. I am hence writing to you to request your help, or that of your readers, to enable the two programs to be executed as one.

Johann ckh Riedel,  
Solihull.



A compulsive game has been submitted by *Mr. J. Semple* of *Jesus College, Oxford*. We are told that 60 is a good score, and 89 is the highest so far. We added sound just for fun, and this is underlined for those who have no sound board. Just leave out the indicated instructions for silent suffering. Note that the sound unit is assumed to be located at 61808 and 61809 decimal (**R1** & **R2** in Line 10). Only line 10 need be changed to re-vector for the Sound Board if located elsewhere.

## TRACE

*Sir—When your UK101 BASIC program starts doing things you didn't intend—or vice versa—then the program "Trace" will help to keep an eye on it. When activated,*

The program is small enough to fit into the free RAM at 546 decimal but equally well it can be loaded at the top of memory in the space protected by the "MEMORY SIZE?" request (its size is 87 decimal bytes).

To load Trace simply run the following BASIC program which can be deleted from memory after use if required. It will ask you where to load Trace and your answer will probably be 546 (free RAM), 4008 (top of 4K) or 8104 (top of 8K). It then prints out two bits of information. The first is a command line which will activate Trace when typed in immediate mode (eg: POKE 11,34:POKE 12,2:X=USR(X)) and the second is a location which can be POKED at any time in immediate mode with a delay count (1 to 255) allowing the running speed of your program being "traced" to be controlled. This location is set to 3 by default but setting it larger will slow your program down and allow you to keep track of the statement numbers on the screen more easily.

```

62999 REM ** TRACE LOADER. P.BECKETT NOV 80 **
63000 DATA169,0,141,28,2,169,0,141,29,2,96
63001 DATA165,136,201,255,208,3,76,155,255,133
63002 DATA167,166,135,134,174,162,144,56,32
63003 DATA232,183,169,91,141,16,208,169,93,141
63004 DATA22,208,32,110,185,162,0,189,1,1,240
63005 DATA10,157,17,208,232,224,5,240,12,208
63006 DATA241,169,32,157,17,208,232,224,5,208
63007 DATA248,162,0,240,3,32,128,254,232,224
63008 DATA3,208,167,165,155,255
63009 INPUT"Type load address";A
63010 FORI=ATOA+86:READX:POKEI,X:NEXT
63011 S=A+1
63012 S1=INT(S/256)
63013 S2=S-S1*256
63014 POKEA+1,S2:POKEA+6,S1
63015 PRINT"For TRACE startup:"
63016 A1=INT(A/256):A2=A-A1*256
63017 PRINT"POKEI1","A2";"POKEI2","A1";"X=USR(X)"
63018 PRINT"TRACE delay count="A;A+81

```

*Incidentally, the Trace feature is deactivated every time a warmstart is executed. The top of the VDU was used for the printout rather than the bottom so that line-feeds which may be produced by your program don't cause the screen to be obliterated by a column of numbers.*

Trace uses routines in the BASIC ROMs as well as the cassette input routine at FE80 as a delay. It was written for the standard UK101 but using the assembler listing (top right), modifications can easily be made if required.

Mr. P. Beckett,  
Blackpool.

	LDA	#\$2D	A9	2D		
	STA	\$021C	8D	1C	02	
	LDA	#\$02	A9	02		
	STA	\$021D	8D	1D	02	
	RTS		60			
	LDA	\$88	A5	88		
	CMP	#\$FF	C9	FF		
	BNE	A	D0	03		
	JMP	\$FF9B	4C	9B	FF	
A	STA	\$AD	85	AD		
	LDX	\$87	A6	87		
	STX	\$AE	86	AE		
	LDX	#\$90	A2	90		
	SEC		38			
	JSR	\$B7E8	20	E8	B7	
	LDA	#\$5B	A9	5B		
	STA	\$D010	8D	10	D0	
	LDA	#\$5D	A9	5D		
	STA	\$D016	8D	16	D0	
	JSR	\$B96E	20	6E	B9	
	LDX	#\$00	A2	00		
B	LDA	\$0101,X	BD	01	01	
	BEQ	C	F0	0A		
	STA	\$D011,X	9D	11	D0	
	INX		E8			
	CPX	#\$05	E0	05		
	BEQ	E	F0	0C		
	BNE	B	D0	F1		
C	LDA	#\$20	A9	20		
D	STA	\$D011,X	9D	11	D0	
	INX		E8			
	CMP	#\$05	E0	05		
	BNE	D	D0	F8		
	LDX	#\$00	A2	00		
	BEQ	E	F0	03		
F	JSR	\$FE80	20	80	FE	
E	INX		E8			
	CPX	#\$03	E0	03		
	BNE	F	D0	F8		
	JMP	\$FF9B	4C	9B	FF	



# The Art of Electronics

P. HOROWITZ and W. HILL

This is a text/reference book that emphasises electronic circuit design techniques and scientific measurements. It begins at a level suitable for those with no previous exposure to electronics and takes the reader through to a reasonable level of design proficiency, emphasising the techniques used daily by circuit designers. The overall approach is one of simplicity and practicality, and there are numerous design examples, with particular emphasis on the choice of circuit configurations and components.

Hardcovers £35.00 net  
Paperback £12.50 net

**CAMBRIDGE  
UNIVERSITY PRESS**

## HI-FI YEAR BOOK — and home entertainment —

1981	price: £4.00
<b>DESIGN OF PHASE/LOCKED LOOP CIRCUITS</b>	
by M. Berlin	price: £6.50
<b>ELECTRONIC MUSIC SYNTHESIZERS</b>	
by D. T. Horn	price: £4.00
<b>POWER SUPPLY PROJECTS</b>	
by R. A. Penfold	price: £2.00
<b>99 PRACTICAL ELECTRONIC projects</b>	
by H. Friedman	price: £3.60
<b>1001 THINGS TO DO WITH YOUR PERSONAL COMPUTER</b>	
by M. Sawusch	price: £5.75
<b>LC CIRCUITS</b>	
by R. P. Turner	price: £4.15
<b>DESIGN OF TRANSISTOR CIRCUITS WITH EXPERIMENTS</b>	
by Dr. K. A. Pullen, Jr.	price: £9.40
<b>THE MASTER IC COOKBOOK</b>	
by C. L. Hallmark	price: £7.00
<b>HOW TO USE I/C LOGIC ELEMENTS</b>	
by J. W. Streaker	price: £4.50

★ ALL PRICES INCLUDE POSTAGE ★

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

## INDEX TO ADVERTISERS

Acorn	49
Aitken Bros	12
Alcon	75
Ambit	88
Audio Electronics	73, 79
Barrie Electronics	85
B.I.E.T.	12
Bi-Pak	13
Bi-Pre-Pak	75
Bolster Instruments Co.	82
British National Radio & Electronics School	5
Cambridge Kits	81
Cambridge Learning	79
Cambridge University Press	87
Chromasonic Electronics	10-11
Clef Products	11
Codespeed	74
Commodore	25
Computer Components (Teleplay)	Cover II
C.R. Supply Co.	80
Crofton Electronics	50
C.U.A.	85
Doram	50
Dziubas	28
Electrovalve	82
Feltglow	28
G.M.T.	8
Hall, Adam (P.E. Supplies)	81
Heathkit	28
Hiykon Limited	81
Home Radio	84
I.C.S. Intertext	83, 81
I.L.P. Electronics	76-77, 86
Industrial Supplies	82
Jayen Developments	78
Keelmoor	15
L & B Electronics	83
London Electronics College	80

MacIn-Zand	3
Maplin Electronics	Cover IV
Marshall, A.	84
Micro Circuits	9
Microsystems '81	78
Modern Book Co.	87
Mutek	20
N.I.C.	20
Northern Radio	12
Pan Electronics	80
Parndon	20
Phononics	14-15
PKG Electronics	82
Progressive Radio	82
Proto Design	82
Radio Component Specialists	87
Radio & T.V. Components	16
Rapid Electronics	78
Saxon Entertainments	4, 85
Science of Cambridge	6-7
Scientific Wire Co.	82
Sentinel Supply	74
Solid State Security	82
Swanley Electronics	4
Technomatic	Cover III
Tempus	8
Titan	4
T.K. Electronics	88
TUAC	74
U.K. User Group	80
Vero	20
Videotone	41
Watford Electronics	2-3
Williamson Amplification	82
William-Stuart Systems (Video music)	82
William-Stuart Systems (Big Ears)	81
Wilmslow Audio	50
Yale Products	84

## BAKER 50 WATT AMPLIFIER £69



Post £2  
Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass. Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). White wording on black cabinet.

## BAKER 150 Watt AMPLIFIER 4 Inputs £89

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Printed Circuit. £3

## DELUXE MODEL Ready Built. 800 watts £4

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be banged to make multi-way stereo mixers. £2-95

## R.C.S. SOUND TO LIGHT CONTROL KIT

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4.50. Post 50p

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4. or 12 for £7.50.

## MAINS TRANSFORMERS Primary 240V A.C. ALL POST 99p

250-0-250V 70mA, 6-5V, 2A	£4.50
250-0-250V 80mA, 6-3V, 3A, 6-3V, 1A	£5.00
350-0-350V 250mA, 6-3V, 4A C.T. 5V/6-3V 2A	£12.50
300-0-300V 120mA, 2x6-3V 2A C.T. 5V 2A	£16.00
220V 45mA, 6-3V 2A	£2.50

## GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available	
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£6.00
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£9.50
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£16.00
6V, 500mA	£2.00
12V, 100mA	£1.30
12V, 750mA	£2.00
10-0-10V 2 amp	£3.00
30V, 5 amp and 17V, 0-17V	£2.00
2 amp	£4.00
0-5, 8, 10, 16V, 1 amp	£2.50
9V, 3 amp	£3.50
15-0-15V 2 amp	£3.75
30V, 2 amp	£3.50
30V, 1 amp	£3.30
6-0-6V, 100mA	£1.50
20V, 40V, 60V, 1 amp	£4.00
12V, 3 amp	£3.50
30V, 40V, 2 amp	£3.50
12V, 2 amp	£3.25
20V, 1 amp	£3.00
20-0-20V, 1 amp	£3.50
30V, 0-30V, 2 amp	£8.00
2 of 18V, 6 amp, each	£11.00
12-0-12V, 2 amp	£3.50
9V, 1 amp	£1.50

## AUTO TRANSFORMERS 115V to 240V 500W £12.00

## CHARGER TRANSFORMERS - METER RECTIFIERS

5 amp	£2
6-12V 3a	£4.00
6-12V 4a	£6.50
6-12V 2a	£1.00
6-12V 4a	£2.00

## R.C.S. LOUDSPEAKER BARGAINS

3 ohm, 4in, 5in, 7x4in, £1.50; 6in, 8x5in, £3; 8in, £3.50.
8 ohm, 2in, 2 1/2in, 3in, 3 1/2in, 5in, £1.50; 8in, £4.50; 10in, £5; 12in, £6.
15 ohm, 3in, 5x3in, 6x4in, 7x4in, £1.50.
25 ohm, 3in, 5x3in, 7x4in, £1.50; 120 ohm, 3 1/2in, dia, £1.50.

## R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS 90-100 mA Post 50p £2-95

All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7.5 or 9 or 12V d.c. up to 100mA. State voltage.

## PP BATTERY ELIMINATOR, BRITISH MADE £4-50

Mains power pack 9 volt 400 ma stabilised, Post 50p  
with overload cutout. Plastic case size 5 x 5 1/2 x 2 1/2. Suitable Radio/Cassettes. DELUXE Switched Model 3-6-7 9V, 400ma £7-50.

## THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes, and all sizes of tape reels.  
A.C. mains 200/240V.

Leaflet S.A.E. £8 Post 50p

## HEAD DEMAGNETISER PROBE £5-00

A.C. ELECTRIC MOTORS POST 50p	
2 Pole, 240V, 2 Amp Spindle 1-43	
0-212in. £1.75, 2 pole, 240V, 15 Amp	
Double spindle - 1.75 x 0-16in. Each	
£1.50, 2 Pole, 120V, .5 Amp, Spindle -	
0-75 x 0-2in. Two in series - 240V, 75p	
each. Brush Motor. From a Food Mixer	
240V, 3 Amp. High Speed and	
Powerful. Spindle - 0-5 x 0-25in. £2-95	

## ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted

corners: 6 x 4 x 2 1/2in. £1.20; 8 x 6 x 2 1/2in. £1.50; 10 x 7 x 2 1/2in. £1.90; 14 x 9 x 2 1/2in. £2.50; 16 x 6 x 2 1/2in. £2.40; 12 x 3 x 2 1/2in. £1.50; 12 x 8 x 2 1/2in. £2.20; 16 x 10 x 2 1/2in. £2.70.

## ALI ANGLE BRACKET 6 x 1/2 x 1/2in. 25p

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.30; 14 x 9in. £1.20; 6 x 4in. 36p; 12 x 8in. 90p; 10 x 7in. 80p; 8 x 6in. 60p; 14 x 3in. 60p; 12 x 5in. 60p; 16 x 10in. £1.40; 16 x 6in. 90p.

## ALUMINIUM BOXES. MANY SIZES IN STOCK

4 x 2 x 2in. £1.00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1.30; 8 x 6 x 3in. £2.10; 12 x 5 x 3in. £2.30; 6 x 4 x 3in. £1.60; 10 x 7 x 3in. £2.50.

## HIGH VOLTAGE ELECTROLYTICS

8/800V	£1.20	50/500V	£1.20	50+50/500V	£1-80
16/500V	75p	220/450V	95p	40+80/500V	£2
32/500V	75p	8+16/450	75p	16+32+32/500V	£2

## DE LUXE BSR HI-FI AUTOCHANGER

Stereo Ceramic Cartridge

Plays 12in., 10in., or 7in records

Auto or Manual. A high quality unit

240V A.C.

Size 13 1/2 x 11 1/2in.

Above motor board 3 1/2in.

Below motor board 2 1/2in.

Deluxe Plinth hinged lift up cover £10-50 post £2

BSR Single Player P207 cueing device, ceramic cartridge. £15

Garrard Single Player 6-200 metal turntable, cueing device, aluminium arm. Stereo cartridge. £22

BSR, C172. Slim arm. Metal Turntable Ceramic Head. Cueing Device Auto Stop. £20

B.S.R. Auto Changer. 11in. Turntable. Budget price. £17-50

Stereo ceramic, reliable unit, 3 speed

R.C.S. Disco Deck 3 speed stereo £9-95 or £18 pair

Rapid Mail Order 50p minimum postage. Callers Welcome.

Access - Visa. Lists 20p. Closed Wed.

## Radio Components Specialists

337, WHITEHORSE ROAD

CROYDON, SURREY, U.K. TEL: 01-684 1665.



## THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the TD300K, which made knob-controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW, TK have designed a touch dimmer kit with an Infra Red Remote Control, enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDEK extension kit). As with all our kits, these units come complete with all components, including RF1 suppression, frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal pads to touch, ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.



We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

In two years' time everyone will be selling remote control dimmers but you can have your TDRK300K kit NOW for only £14.30 for the dimmer unit and £4.20 for the transmitter. For the more athletic of you, the TD300K is still available at £6.50 and the TDE/K at £2.00.

DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.

## NEW REMOTE CONTROL KITS

- MK6 - Simple Infra Red Transmitter - A pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. £4.20
- MK7 - Infra Red Receiver - Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, can be modified for use with 5-15V dc supplies and transistor or relay outputs. £9.00
- \*Special Price\* MK6 and MK7 together. Order as RC500K £12.50
- MK8 - Coded Infra Red Transmitter - Based on the SL490, the kit includes two IR LEDs, measures only 8x2x1.3 cms. Requires a 9V (PP3) battery. £5.90
- MK9 - 4 Way Keyboard - for use with the MK8 kit, to make a 4-channel remote control transmitter. £1.90
- MK10 - 16 Way Keyboard - for use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML928 receiver (MK12 kit). £5.40
- MK12 - 16 Channel IR Receiver - for use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary depending on whether the ML928 or ML928 is specified. Includes its own mains supply. Size 9x4x2 cms, excluding transformer. £11.95

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 50p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT. Send s.a.e. with all enquiries



**TK Electronics**  
(P.E.), 11 Boston Road, London  
W7 3SJ. TEL. 01-579 9794



The CT4000 has been designed to preset the state (on or off) of four outputs at four times per day for up to 7 days in advance, enabling the unit to control tape recorders, appliances, central heating, lights, etc. The times are set on a 0.1" high red LED display by means of a keyboard and the output states are displayed on four LEDs. Each output can switch up to 20mA at 9V. For mains loads use our Solid State Relay Kit (MK2). The kit includes a PCB, keyswitches, I.C., 4 digit LED display, transformer, plus all other components and a screen printed and drilled box which can also accommodate up to 4 Solid State Relay Kits.

**£25.25**

Size: 10x12x4.5 cms.  
Colour: Black.



## D.V.M. THERMOMETER KIT

Based on the ICL 7106. This Kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply. (PP3 battery)

**£19.50**

## INTEGRATED CIRCUITS

- 555 Timer 21p
  - 741 Op. Amp. 19p
  - AY-5-1230/2 Clock/Timer £2.60
  - AY-5-1224 Clock £4.50
  - AY-3-1270 Thermometer £8.20
  - ICM7555 CMOS555 Timer £7.00
  - LM377 Dual 2W Amp. 79p
  - LM3795 Dual 6W Amp. £1.45
  - LM380 2W Audio Amp. £3.50
  - LM382 Dual low noise Preamp 80p
  - LM386 250mW low voltage Amp. £1.00
  - LM1830 Fluid Level Detector 75p
  - LM2817 F-v Converter (14 pin) £1.50
  - LM3909 LED Flasher/Oscillator £1.60
  - LM3911 Thermometer 60p
  - LM3914 Dot/Bar Driver LIN. £1.20
  - LM3915 Dot/Bar Driver LOG. £2.20
  - MM74C911 4 digit display controller £6.50
  - MM74C915 7 segment-BCD converter 96p
  - MM74C926 4 digit counter with 7 seg. o/p £4.50
  - S5668 Touchdimmer £2.50
  - SL440 AC Power Controller £1.75
  - SN76477 Complex Sound Generator £2.52
  - TBA800 5W Audio Amp. 68p
  - TBA810AS 7W Audio Amp. £1.00
  - TDA1024 Zero Voltage Switch £1.20
  - TDA2020 20W Audio Amp. £2.85
  - ZN1034E Timer £1.80
- All ICs supplied with data sheets.  
Data Sheets only, 10p each device.

## DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

### DL1000K

This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60

### DL21000K

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00

Optional Opto Input DLA1 60p

## 24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit £14.90

CT1000KB with white box (56/131x71mm) £17.40

Ready Built £22.50

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome

CATALOGUES 60p ea., all three for £1.60  
POST/PACKAGE CHARGE NOW 35p

**ambit**  
INTERNATIONAL

**200 North Service Road, Brentwood, Essex**  
TELEPHONE (STO 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

CWO PLEASE: Commercial MA terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.


CATALOGUES 2 & 3...60p ea  
4...75p  
(4 inc. rev. of part 1)

ALL PARTS: £1.75.....

SSB transceiver module - based on G4CLF designs

- \* High level mixer
- \* 8 pole filter

- \* 1 W AF on the PCB

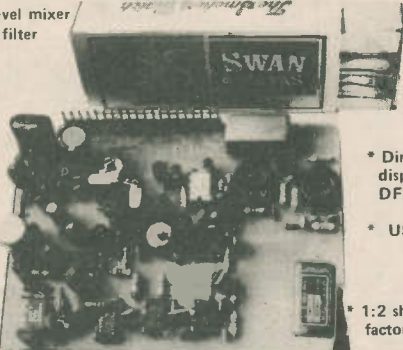

- \* Direct freq. display with DFM7

- \* USB/LSB

- \* 1:2 shape factor

Add an LO and the RF selectivity, and you have a very simple yet high performance signal processing 'heart' of an SSB transceiver in the range 100kHz to 1000MHz (with the correct LO/RF stages). The Ambit 91600 costs just £44 +vat, and includes an 8 pole SSB crystal filter, SL1600 signal processing circuitry, double balanced schottky diode mixer and full USB/LSB electronic switching.


The use of 10.7MHz, instead of 9MHz (as in the original unit) now enable direct connection to an AMBIT D77 for 1kHz frequency readout with far greater ease and accuracy than can be achieved with mechanical dial systems. Buy them both and save 15%...DFM7+91600= £69.46 inc.

**The AMBIT catalogue - now with the new Part 4 for 1981**  
The most complete range of specialist radio component kits in Europe.

- \* VHF tunerheads

- \* Stereo decoders
- \* Frequency synthesis
- \* Block LPFs
- \* keyswitches
- \* DC audio control ICs
- \* Ultimate HiFi

## communication radio

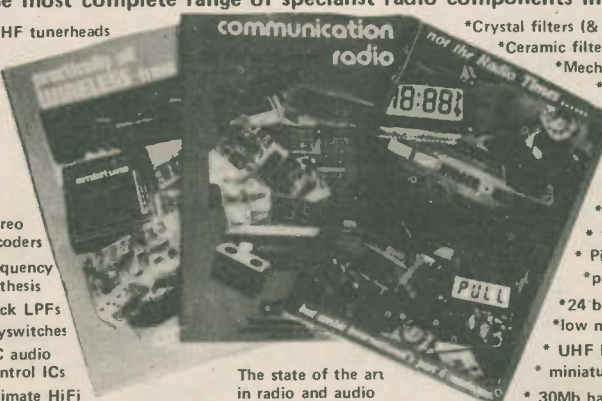

The state of the art in radio and audio

- \* Crystal filters (& theory)
- \* Ceramic filters for AM/FM
- \* Mechanical filters
- \* Fixed chokes
- \* MC meters
- \* CMOS/TTL
- \* NB/FM IFs
- \* WB/FM IFs
- \* flat top LEDs
- \* Variable chokes
- \* Piezo sounders
- \* potentiometers
- \* 24 bit NC plotters
- \* low noise RIAA ICs
- \* UHF Helical filters
- \* miniature electrolytics
- \* 30Mb hard disks

You need all three sections for a complete picture. Each section is revised on a triennial cycle - so this year the part 4 contains the revised remnants of the original part 1 - plus all the many new items for 1981. £1.75 for the lot, or 60p each for parts 2 & 3, and £0.75p for the bumper part four section. (prices include postage).

Special Offers... each catalogue is supplied with a 'special offer' order form that will enable you to save the cost of the catalogues with your first few purchases.

**New for 1981 -- The RX80 modular HF SSB dual conversion receiver, as featured in this edition. Send large S.A.E for full details of component kits, hardware, and accessories being supplied exclusively by Ambit for this excellent home construction project.**

Published approximately on the 15th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/Sia) Ltd; South Africa - Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £10.60 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. Practical Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



<b>TTL by TEXAS</b>		74180	93p	4000 SERIES	93 SERIES	160p	VEROBOARD	TRANSISTORS	•BF880	25p	TIP33A	90p	•2N3706/9	14p
7400	11p	74181	16p	4000	9301	160p	0.1	AC126	25p	TIP33B	115p	•2N3708/9	12p	
7401	11p	74182	90p	4000	9302	175p	(open clamp)	AC127	25p	TIP33C	115p	•2N3773	30p	
7402	12p	74183	150p	4000	9308	316p	21 x 3	AC176	25p	TIP33D	115p	•2N3819	25p	
7403	12p	74184	150p	4000	9310	275p	21 x 5	AC177/8	25p	TIP33E	225p	•2N3820	50p	
7404	14p	74185	500p	4006	9311	275p	31 x 3	AF116/7	50p	TIP33F	290p	•2N3823	70p	
7405	14p	74186	500p	4007	9312	275p	31 x 5	AD149	70p	TIP33G	270p	•2N3866	90p	
7406	18p	74187	90p	4008	9313	180p	31 x 7	BF549	45p	TIP33H	140p	•2N3903A	18p	
7407	36p	74188	90p	4009	9314	180p	31 x 17	AU107	250p	TIP33I	90p	•2N3905/6	20p	
7408	17p	74189	90p	4010	9315	225p	31 x 17	BC107/8	11p	TIP33J	70p	•2N4037	65p	
7409	19p	74190	90p	4011	9321	225p	Plot of 100 pins	BC109	11p	TIP33K	70p	•2N4058/9	12p	
7410	19p	74191	90p	4012	9322	180p	Spot face cutter	BC117/8	20p	TIP33L	82p	•2N4060	12p	
7411	24p	74192	90p	4013	9323	180p	Pin insertion	BC119	20p	TIP33M	82p	•2N4061/2	18p	
7412	24p	74193	90p	4014	9334	340p	tool	BC149	19p	TIP33N	70p	•2N4077	90p	
7413	20p	74194	90p	4015	LINEAR I.C.s			BC157/8	11p	TIP33O	70p	•2N4126/8	27p	
7414	40p	74195	90p	4016	•AY1-0212	600p		BC159	11p	TIP33P	150p	•2N4401/3	27p	
7415	40p	74196	90p	4017	•AY1-1313	250p		BC169C	12p	TIP33Q	150p	•2N4421	90p	
7416	27p	74197	80p	4018	•AY1-1320	320p		BC172	12p	TIP33R	150p	•2N4507	27p	
7417	27p	74198	150p	4019	•AY1-5050	850p		BC177/8	17p	TIP33S	150p	•2N4517	27p	
7418	27p	74199	150p	4020	AY3-1270	850p		BC179	18p	TIP33T	150p	•2N4519	90p	
7419	27p	74200	150p	4021	AY3-8912	650p		BC182/3	11p	TIP33U	150p	•2N4574	50p	
7420	17p	74201	90p	4022	AY3-1224A	650p		BC184	11p	TIP33V	150p	•2N4578	50p	
7421	40p	74202	110p	4023	•AY5-1315	600p		BC187	30p	TIP33W	150p	•2N4585	44p	
7422	22p	74203	110p	4024	•AY5-1317A	775p		BC189	30p	TIP33X	150p	•2N4589	44p	
7423	34p	74204	110p	4025	•CA3019	80p		BC192/3	11p	TIP33Y	150p	•2N4627	90p	
7424	34p	74205	110p	4026	•CA3028A	90p		BC195	12p	TIP33Z	150p	•2N4637	90p	
7425	34p	74206	110p	4027	•CA3046	70p		BC197	12p	TIP33A	150p	•2N4638	90p	
7426	34p	74207	110p	4028	•CA3048	70p		BC199	12p	TIP33B	150p	•2N4639	90p	
7427	34p	74208	110p	4029	•CA3080E	225p		BC201	12p	TIP33C	150p	•2N4640	90p	
7428	36p	74209	150p	4030	•CA3080E	225p		BC203	12p	TIP33D	150p	•2N4641	90p	
7429	36p	74210	150p	4031	•CA3080E	225p		BC205	12p	TIP33E	150p	•2N4642	90p	
7430	17p	74211	150p	4032	•CA3080E	225p		BC207	12p	TIP33F	150p	•2N4643	90p	
7431	17p	74212	150p	4033	•CA3080E	225p		BC209	12p	TIP33G	150p	•2N4644	90p	
7432	30p	74213	150p	4034	•CA3080E	225p		BC211	12p	TIP33H	150p	•2N4645	90p	
7433	30p	74214	150p	4035	•CA3080E	225p		BC213	12p	TIP33I	150p	•2N4646	90p	
7434	30p	74215	150p	4036	•CA3080E	225p		BC215	12p	TIP33J	150p	•2N4647	90p	
7435	30p	74216	150p	4037	•CA3080E	225p		BC217	12p	TIP33K	150p	•2N4648	90p	
7436	30p	74217	150p	4038	•CA3080E	225p		BC219	12p	TIP33L	150p	•2N4649	90p	
7437	30p	74218	150p	4039	•CA3080E	225p		BC221	12p	TIP33M	150p	•2N4650	90p	
7438	35p	74219	150p	4040	•CA3080E	225p		BC223	12p	TIP33N	150p	•2N4651	90p	
7439	35p	74220	150p	4041	•CA3080E	225p		BC225	12p	TIP33O	150p	•2N4652	90p	
7440	17p	74221	150p	4042	•CA3080E	225p		BC227	12p	TIP33P	150p	•2N4653	90p	
7441	70p	74222	150p	4043	•CA3080E	225p		BC229	12p	TIP33Q	150p	•2N4654	90p	
7442	70p	74223	150p	4044	•CA3080E	225p		BC231	12p	TIP33R	150p	•2N4655	90p	
7443	112p	74224	150p	4045	•CA3080E	225p		BC233	12p	TIP33S	150p	•2N4656	90p	
7444	112p	74225	150p	4046	•CA3080E	225p		BC235	12p	TIP33T	150p	•2N4657	90p	
7445	100p	74226	150p	4047	•CA3080E	225p		BC237	12p	TIP33U	150p	•2N4658	90p	
7446	93p	74227	150p	4048	•CA3080E	225p		BC239	12p	TIP33V	150p	•2N4659	90p	
7447	93p	74228	150p	4049	•CA3080E	225p		BC241	12p	TIP33W	150p	•2N4660	90p	
7448	80p	74229	150p	4050	•CA3080E	225p		BC243	12p	TIP33X	150p	•2N4661	90p	
7449	80p	74230	150p	4051	•CA3080E	225p		BC245	12p	TIP33Y	150p	•2N4662	90p	
7450	80p	74231	150p	4052	•CA3080E	225p		BC247	12p	TIP33Z	150p	•2N4663	90p	
7451	17p	74232	150p	4053	•CA3080E	225p		BC249	12p	TIP33A	150p	•2N4664	90p	
7452	17p	74233	150p	4054	•CA3080E	225p		BC251	12p	TIP33B	150p	•2N4665	90p	
7453	17p	74234	150p	4055	•CA3080E	225p		BC253	12p	TIP33C	150p	•2N4666	90p	
7454	17p	74235	150p	4056	•CA3080E	225p		BC255	12p	TIP33D	150p	•2N4667	90p	
7455	17p	74236	150p	4057	•CA3080E	225p		BC257	12p	TIP33E	150p	•2N4668	90p	
7456	17p	74237	150p	4058	•CA3080E	225p		BC259	12p	TIP33F	150p	•2N4669	90p	
7457	17p	74238	150p	4059	•CA3080E	225p		BC261	12p	TIP33G	150p	•2N4670	90p	
7458	17p	74239	150p	4060	•CA3080E	225p		BC263	12p	TIP33H	150p	•2N4671	90p	
7459	17p	74240	150p	4061	•CA3080E	225p		BC265	12p	TIP33I	150p	•2N4672	90p	
7460	17p	74241	150p	4062	•CA3080E	225p		BC267	12p	TIP33J	150p	•2N4673	90p	
7461	17p	74242	150p	4063	•CA3080E	225p		BC269	12p	TIP33K	150p	•2N4674	90p	
7462	17p	74243	150p	4064	•CA3080E	225p		BC271	12p	TIP33L	150p	•2N4675	90p	
7463	17p	74244	150p	4065	•CA3080E	225p		BC273	12p	TIP33M	150p	•2N4676	90p	
7464	17p	74245	150p	4066	•CA3080E	225p		BC275	12p	TIP33N	150p	•2N4677	90p	
7465	17p	74246	150p	4067	•CA3080E	225p		BC277	12p	TIP33O	150p	•2N4678	90p	
7466	17p	74247	150p	4068	•CA3080E	225p		BC279	12p	TIP33P	150p	•2N4679	90p	
7467	17p	74248	150p	4069	•CA3080E	225p		BC281	12p	TIP33Q	150p	•2N4680	90p	
7468	17p	74249	150p	4070	•CA3080E	225p		BC283	12p	TIP33R	150p	•2N4681	90p	
7469	17p	74250	150p	4071	•CA3080E	225p		BC285	12p	TIP33S	150p	•2N4682	90p	
7470	17p	74251	150p	4072	•CA3080E	225p		BC287	12p	TIP33T	150p	•2N4683	90p	
7471	17p	74252	150p	4073	•CA3080E	225p		BC289	12p	TIP33U	150p	•2N4684	90p	
7472	17p	74253	150p	4074	•CA3080E	225p		BC291	12p	TIP33V	150p	•2N4685	90p	
7473	17p	74254	150p	4075	•CA3080E	225p		BC293	12p	TIP33W	150p	•2N4686	90p	
7474	17p	74255	150p	4076	•CA3080E	225p		BC295	12p	TIP33X	150p	•2N4687	90p	
7475	17p	74256	150p	4077	•CA3080E	225p		BC297	12p	TIP33Y	150p	•2N4688	90p	
7476	17p	74257	150p	4078	•CA3080E	225p		BC299	12p	TIP33Z	150p	•2N4689	90p	
7477	17p	74258	150p	4079	•CA3080E	225p		BC301	12p	TIP33A	150p	•2N4690	90p	
7478	17p	74259	150p	4080	•CA3080E	225p		BC303	12p	TIP33B	150p	•2N4691	90p	
7479	17p	74260	150p	4081	•CA3080E	225p		BC305	12p	TIP33C	150p	•2N4692	90p	
7480	17p	74261	150p	4082	•CA3080E	225p		BC307	12p	TIP33D	150p	•2N4693	90p	
7481	100p	74262	150p	4083	•CA3080E	225p		BC309	12p	TIP33E	150p	•2N4694	90p	
7482	84p	74263	150p	4084	•CA3080E	225p		BC311	12p	TIP33F	150p	•2N4695	90p	
7483	84p	74264	150p	4085	•CA3080E	225p		BC313	12p	TIP33G	150p	•2N4696	90p	
7484	100p	74265	150p	4086	•CA3080E	225p		BC315	12p	TIP33H	150p	•2N4697	90p	
7485	100p	74266	150p	4087	•CA3080E	225p		BC317	12p	TIP33I	150p	•2N4698	90p	
7486	30p	74267	150p	4088	•CA3080E	225p		BC319	12p	TIP33J	150p	•2N4699	90p	
7487	30p	74268	150p	4089	•CA3080E	225p		BC321	12p	TIP33K	150p	•2N4700	90p	
7488	30p	74269	150p	4090	•CA3080E	225p		BC323	12p	TIP33L	150p	•2N4701	90p	
7489	210p	74270	150p	4091	•CA3080E	225p		BC325	12p	TIP33M	150p	•2N4702	90p	
7490	210p	74271	150p	4092	•CA3080E	225p		BC327	12p	TIP33N	150p	•2N4703	90p	
7491	80p	74272	150p	4093	•CA3080E	225p		BC329	12p	TIP33O	150p	•2N4704	90p	
7492	80p	74273	150p	4094	•CA3080E	225p		BC331	12p	TIP33P	150p			



# Make it for a Song!



## The New Maplin in Matinée

**Amazing Value  
For Only**

**£299.95** + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard.

Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique counter melody line with each rhythm. Truly amazing value for money. Full construction details start in the March issue of Electronics & Music Maker on sale Feb. 14th.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.



Post this coupon now for your copy of our 1981 catalogue price £1.  
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.  
I enclose £1.25.

Name

Address

PE381

## MAPLIN

Maplin Electronic Supplies Ltd.  
All mail to P.O. Box 3, Rayleigh, Essex SS6 8LR  
Telephone Southend (0702) 554155. Sales (0702) 552911.

Shops:  
159-161 King Street, Hammersmith, London W6 Telephone: (01) 748 0926  
284 London Road, Westcliff-on-Sea, Essex Telephone: Southend (0702) 554000.  
Both shops closed Mondays

Catalogue now on sale in all branches of WHSMITH  Price £1.00



# PRACTICAL ELECTRONICS

VOLUME 17

No. 3

MARCH 1981

## CONSTRUCTIONAL PROJECTS

<b>27/28MHz CONVERTER</b> by M. Tooley BA .. .. .	30
Modifies your radio for 27/28MHz listening	
<b>PERIOD POWER TESTER</b> by Chris Lare .. .. .	38
Variable switching for surge testing equipment	
<b>MICROPHONE MIXER</b> by R. A. Penfold .. .. .	46
Three microphone stereo mixer	
<b>INTERFACING COMPUKIT</b> Part 3 by D. E. Graham .. .. .	52
Display Board	
<b>DIGITAL COUNTER TIMER</b> Part 2 by Dr Mark Sawicki and Alex Kowalewski BSc .. .. .	66
Construction and p.c.b.s (conclusion)	

## GENERAL FEATURES

<b>AUDIO LINES</b> by Ben Duncan .. .. .	22
Dealing with problems associated with audio transmissions	
<b>CEGMON</b> Reviewed by Mike Abbott .. .. .	26
An updated monitor	
<b>SEMICONDUCTOR UPDATE</b> by R. W. Coles .. .. .	36
SG1547 TDC1023J INS8073	
<b>STRICTLY INSTRUMENTAL</b> by K. Lenton Smith .. .. .	44
When is an organ not an organ?	
<b>INGENUITY UNLIMITED</b> .. .. .	62
Pip Generator—Graph Display Unit—Storm Distance Estimator—Binary to BCD Converter—Traffic Lights	
<b>MICROPROMPT</b> .. .. .	69
Hardware geometry, plus software for pleasure and debugging	

## NEWS AND COMMENT

<b>EDITORIAL</b> .. .. .	17
<b>MARKET PLACE</b> .. .. .	18
New products	
<b>INDUSTRY NOTEBOOK</b> by Nexus .. .. .	21
The Electronics Industry stays on top	
<b>NEWS BRIEFS</b> .. .. .	24, 45, 61
<b>SPECIAL OFFER—TELEQUIPMENT S61 OSCILLOSCOPE</b> .. .. .	37
<b>READOUT</b> .. .. .	42
Some feedback on the sensitive subject of CB	
<b>PE INVENTORS COMPETITION RESULTS</b> .. .. .	43
An intriguing follow-up	
<b>COUNTDOWN</b> .. .. .	45
What to see; where and when to see it	
<b>SPACEWATCH</b> by Frank W. Hyde .. .. .	51
After the pass—The Secret of Venus	
<b>PATENTS REVIEW</b> .. .. .	60
3-D Viewing	
<b>POINTS ARISING</b> .. .. .	61
PE Teletext	

**OUR APRIL ISSUE WILL BE ON SALE FRIDAY, 13 MARCH 1981**  
(for details of contents see page 29)

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



# Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

by  
**David  
Shortland**

## LOW PRICED VIDEO

With a recommended retail price of just £399, Hitachi are launching possibly the cheapest colour video camera available today and one which they claim will appeal to both a newcomer to video filming as well as the ardent enthusiast.

The camera, model VKC 750, has a built in double image optical viewfinder which is linked to a 2.8:1 zoom lens with a focal length of 13.5mm to 37.5mm. Perfectly focussed pictures are obtained every time by lining up the images in the viewfinder and being an optical viewfinder, the user sees exactly what the camera sees.



A single pick up tube and the wide use of i.c.s enable the weight and size of the camera to be kept to a minimum. No bigger than a normal 8mm cine camera, it weighs only 4lbs.

Fitted to the camera is a colour temperature control button which operates in conjunction with a balance meter to ensure the correct colour reproduction under varying light conditions. Also on the camera, to get the best possible pictures under dim lighting conditions, there is a high-low sensitivity switch

which can be altered when filming in the early evening or under indoor lighting conditions.

A built-in non directional electret microphone of hi-fi sensitivity is fitted to the camera but provision is also made for the connection of an external microphone. Other features include a detachable pistol grip and an on/off button to stop and start the tape.

## THANDAR PRESCALER

Designed to provide high sensitivity (better than 10mV r.m.s.) the TP600 from Thandar will extend the upper frequency limit of most frequency meters by a factor of X10 up to a maximum of 600MHz.



The TP600 can be used with the Thandar PFM200 hand-held frequency meter or the Thandar TF200 l.c.d. frequency meter, to extend their frequency range to cover a wide range of specialised applications, including transmitter/receiver test for mobile and ham radio.

The TP600 (pictured here with the TF200 frequency meter) is priced at £37.50 plus VAT. Further information is available from Sinclair Electronics Ltd, London Road, St Ives, Huntingdon, Cambs. PE17 4HJ. (0480 64646)

## MINI PRINTER

Digitronix Ltd, of Milton Keynes, have launched the Mini-Printer, a compact 32-column printer which they claim to be the lowest-priced universal printer available.

The Mini-Printer accepts conventional ASCII Serial inputs at RS232, TTL and 20 mA current loop levels, at seven baud rates from 110 to 4800, and can therefore interface with almost any microprocessor-based machine. In addition to these user-selectable options, it also accepts data on a parallel port.

The printing unit is of the electrosensitive type, and prints the 64 character ASCII font at 64 characters/sec. on to aluminised paper rolls 59 mm wide. The unit is quiet in operation and has many special features, including double-width characters, and back spacing. On automatic test mode, it will print out a sample set of characters.



The unit is made for the professional market, constructed to a high standard throughout and housed in a rugged steel case size 277 x 138 x 70 mm. Likewise, the electronics are manufactured to provide the highest standard of reliability, especially necessary in remote operation applications for which the Mini-Printer is very suitable.

Mains power is used, but there is provision for low voltage d.c. input, primarily for applications where other Digitronix equipment is interfaced.

Digitronix say that the Mini-Printer is extremely versatile, mainly through the incorporation of a microprocessor based architecture which facilitates reprogramming for special applications. The print font can be changed and, in addition to alphanumeric fonts, the output can be converted to create graphic dot patterns, representing, for example, analogue expressions of measured parameters.

The Mini-Printer is available direct from Digitronix at £195 plus VAT. They can also supply leads, paper etc. For further information contact: Digitronix Ltd., 10 Burners Lane, Kiln Farm Industrial Estate, Milton Keynes (0908 566888)

## REMOTE CONTROL KITS


TK Electronics, who specialise in Electronic Kits for the hobbyist, have now extended their range of Mini Kits (which include timers and temperature controllers) by introducing a range of remote control kits.

The Mini Kit range consists of units designed to perform certain functions, eg. temperature control, while still retaining full flexibility to enable the user to incorporate them into his own systems if required or alter such parameters as power output or supply voltage.




The new kits include the MK6 Simple Infra Red Transmitter, the MK7 Infra Red Receiver, the MK8 Coded Infra Red Transmitter and the MK12 16-Channel Receiver.

The MK6 and MK7 consists of a small hand held transmitter which requires a 9V battery (PP3) and a small mains powered receiver with a triac output cable of switching a mains load of up to 500W. The receiver may be wired for toggle (push on, push off) action or a momentary action, the load being switched off after a preset time, and may be easily modified for operation from d.c. supplies in the 9 to 15 volt range.

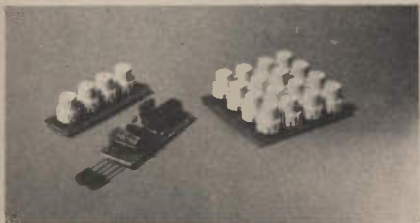

The MK8 is an encoded Infra Red Transmitter which also runs from a 9V PP3 battery and measures only 60 x 20 x 13 mm. It can transmit up to 32 different commands depending on the keyboard used. At present the MK9 Four-way and MK10 16-way keypad kits are available for use with this kit, to provide remote switching of up to 4 or up to 16 outputs on the MK12 receiver kit.

The MK12 Receiver is a mains powered unit with 16 CMOS outputs (0 to 15V) which may be interfaced with logic, or used to drive relays or triacs for power switching. A 15V 30mA rail is also available for powering external circuitry if required. The unit may be ordered in the momentary or latched output versions depending upon the application. In the first case, one of the 16 outputs goes high only while a code is being received while the second version latches the output pertaining to the last code received. When assembled, the receiver measures only 60 x 40 x 20 mm. (excluding transformer) and requires only the adjustment of a preset to set up.

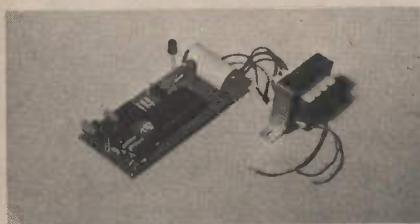

By changing the value of one resistor in the MK8 kit and adjusting the preset on the MK12, simultaneous operation of two or more receivers in the same area can be achieved.

Prices for the kits are as follows; MK6—£4.20, MK7—£9.00, MK8—£5.90, MK9—£1.90, MK10—£5.40, MK12—£11.95. Add 15% VAT and 40p postage.

TK Electronics, 11 Boston Road, London, W7 3SJ.

## CUT PRICE CASES

West Hyde Developments have announced significant price reductions on their range of Bocon cases. The reductions have been made



possible by the "Strong Pound", as the cases are manufactured in West Germany.


In particular, West Hyde have reduced prices of the two-tone grey cases in the Bocon range by over 25 per cent. Further details are available from:

West Hyde Developments Ltd., Unit 9, Park Street Industrial Estate, Aylesbury, Bucks. HP20 1ET (0296 20441)
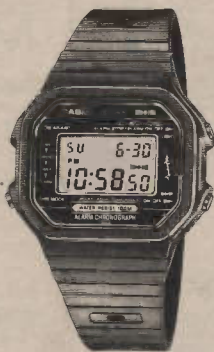
## CASIO

The Casio W-100 series of watches, which are able to function underwater to a depth of 100 metres, feature a 12-digit l.c.d. capable of displaying hours, minutes, seconds, am/pm, day, month and year.

Even when operating secondary functions, countdown alarm and stopwatch, and showing appropriate figures in those modes, the W-100's capacity is sufficient to continue dis-



playing the current time in hours and minutes, albeit in an offset position.

Further capabilities include daily alarm function, and half-hourly time signal function.

Casio W series is a range of watches offering a choice of case and bracelet styles. The W-100 itself has resin case and strap at RRP £22.95. W-150C features stainless steel with black resin strap at RRP £27.95. Top of the 'waterproof' range is W-150 with full stainless steel case and bracelet, at RRP £32.50.

## HI-FI SOLUTIONS

Two new products that are claimed to give improved sound quality for records and tapes have been introduced by Kanus Chemicals.

"Hi-Degree" solution is simply applied with a soft cloth onto the record surface and penetrates deep into the track to clean away accumulated dust. Static is removed and after one application the record remains permanently anti-static.

Only a microscopic layer which never hardens, softens, thins or gels, is deposited on to the record, providing continuous protection to the track and stylus, reducing wear and main-

taining the original sound quality.

It is suitable for all records and eliminates surface 'rustle', reduces scratch noises and improves the quality and clarity of old records.

The second product is 'Eclat' a specially formulated chemical solution designed specifically for magnetic tapes. Applied sparingly with the dropper supplied, Eclat cleans both tape and sound head, removing static and preventing moisture absorption.

Reproduction is enhanced and one of the features is the improved spooling of the tape, preventing binding, breaking and damage when subjected to stopping, shock and uneven tension.

The use of 'Eclat' also eliminates static from the tape and static build up caused by the winding wheels running on the plastic face of the cassette case.

Sixty millilitres of "High Degree" which is sufficient for 100 l.p.s is priced at £2.85 and ten millilitres of "Eclat" which is sufficient for 50 cassettes is priced at £1.80. Both prices include VAT and p&p.

Kanus Chemicals Limited, 56 The Boulevard, Crawley, Sussex, RH10 1XH (0293 25113)

## MULTI COMBI

Anyone who has accidentally drilled or nailed through an electric cable or pipe will be interested in the new combined metal detector and voltage probe known as the Multi Combi.



This hand held unit will detect metal objects up to 200 mm and live cables up to 100 mm. There is a sensitivity control for both functions and indication is via a red or yellow l.e.d. the Multi Combi which is powered by a PP3 battery also has a neon test probe for mains checks. When not in use the voltage probe retracts into the body and the search head folds down, automatically switching off the unit.

The Multi Combi is priced at £11.95 inclusive of VAT and p&p.

A Marshall's (London Ltd.), Kingsgate House, Kingsgate Place, NW6 4TA (01-624 8582)

## VIDEO GUIDE

With UK sales of video recorders forecast to pass the 300,000 mark by the end of the year, Sony has recognised the need to assist existing owners in utilising their equipment to its best advantage.

The company has produced a 48 page full colour handbook containing comprehensive details not only of the best ways to exploit all facilities of video recorders.

The handbook, entitled 'How To Video', uses simple non-technical language and is available either from Sony's London showroom price 60p or by post (30p extra).

Sony London Showroom, 134 Regent Street, London, W1.



# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER. CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND INDUSTRIAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & ADD 40P TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

## VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.  
We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

### POLYESTER CAPACITORS:

400V: 1nF, 1.5n, 2.2n, 3.3n, 4.7n, 6.8n 11p; 10n, 15n, 18n, 22 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 68p; 2µF 85p.  
160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1µF 42p; 1µF 45p; 2µF 48p; 4µF 58p.  
1000V: 1nF 17p; 10nF 30p; 15µ 40p; 22n 36p; 33n 42p; 47n, 100n 50p; 470n 99p.

### POLYESTER RADIAL LEAD CAPACITORS: 250V;

10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µ 23p; 1µ5 40p; 2µ 46p.

### ULTRASONIC

TRANSDUCERS  
40KHz 350p pr.

### ELECTROLYTIC CAPACITORS (Values in µF):

500V: 10 52p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p; 4.7, 9p; 6.8, 10, 15, 22 12p; 33 15p; 47 12p; 100 19p; 1000 70p; 50V: 47 12p; 68 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 15, 22, 33p; 330 90p; 470 120p; 25V: 1.5, 6.8, 10, 22, 33p; 33p; 47p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 100 30p; 2200 50p; 3300 76p; 4700 92p; 16V: 40, 47, 100 9p; 125 12p; 330 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 33p; 3300 74p; 4700 79p.

TAG-END TYPE: 450V: 100µF 65p; 70V: 470 245p; 64V: 3300 198p; 2200 139p; 50V: 3300 154p; 2200 110p; 40V: 4700 160p; 25V: 10000 320p; 15000 345p.

### TANTALUM BEAD CAPACITORS:

35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8, 10, 20 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8, 10 19p; 15 36p; 22 30p; 33, 47, 100 25p; 100V: 1.5, 2.2 26p; 33, 47, 100 35p; 100 55p.

### MYLAR FILM CAPACITORS:

100V: 1nF, 2n, 4n, 4n7, 10 6p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 470n/50V: 12p.

### CERAMIC CAPACITORS: (50V)

Range: 0.5pF to 10nF 4p  
15nF, 22nF, 33nF, 47nF 5p  
100nF/30V 7p; 220nF/6V 8p

### POLYSTYRENE CAPACITORS:

10pF to 1nF 8p 1 5nF to 12nF 10p.

### SILVER MICA (pF)

2, 3, 4, 7, 6.8, 10, 12, 18, 22, 27, 33, 39, 47, 56, 68, 75, 82, 85, 100, 120, 150, 180

### TRIMMERS miniature

2-6pF, 2-10pF 22p  
2-25pF, 5-56pF 30p  
10-85pF 35p

### COMPRESSION

3.40pF, 10-80pF 20p  
20-250pF 28p  
100-580pF 39p  
400-1250pF 48p

### RESISTORS - ERIE make 5% carbon

Miniature High Stability. Low Noise.  
RANGE, Value 1-99 100+  
0.25W 202-4 M7 E24 2p 1p  
0.5W 202-4 M7 E12 2p 1p  
1W 202-10M E12 5p 3p  
2% Metal Film 10Q-1M 6p 4p  
1% 0.5W 51Q-1M24 8p 6p  
100+ price applies to Resistors of each type not mixed values.

### COMPUTER IC's


74S138 240 7448 75 74156 75 74LS13 35  
2114-450n 175 74S158 240 7450 20 74159 165 74LS00 13  
2114-300n 245 74S188 210 7451 20 74159 165 74LS01 13  
2708 350 74S189 158 7453 20 74160 99 74LS02 15  
2716-5V 450 74S194 150 7454 20 74161 99 74LS03 15  
4116 295 74S241 540 7460 20 74162 99 74LS04 16  
6520 325 74S287 825 7472 30 74163 99 74LS05 23  
6520 325 74S287 825 7472 30 74163 99 74LS06 22  
6520 325 74S287 825 7472 30 74163 99 74LS07 22  
6520 325 74S287 825 7472 30 74163 99 74LS08 22  
6520 325 74S287 825 7472 30 74163 99 74LS09 22  
6520 325 74S287 825 7472 30 74163 99 74LS10 22  
6520 325 74S287 825 7472 30 74163 99 74LS11 22  
6520 325 74S287 825 7472 30 74163 99 74LS12 22  
6520 325 74S287 825 7472 30 74163 99 74LS13 35  
6520 325 74S287 825 7472 30 74163 99 74LS14 35  
6520 325 74S287 825 7472 30 74163 99 74LS15 35  
6520 325 74S287 825 7472 30 74163 99 74LS187 35  
6520 325 74



# ARE YOU INTERESTED IN ELECTRONICS?
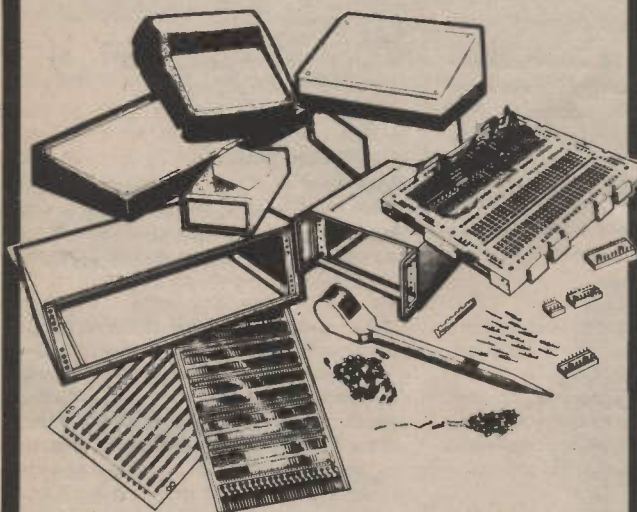
## THEN YOU SHOULD KNOW ABOUT VERO.

We manufacture a wide range of products for the electronics industry and can make available to you a selection suitable for project work. We offer you a large choice of Veroboard and circuit board accessories, including the latest solderless breadboard — VEROBLOC, which enables you to use those valuable components time and time again. Use a piece of Veroboard to save a successfully completed circuit and choose a box or instrument case from our vast range to give your project that professional touch.



For further details and a copy of the brochure please fill in the coupon below.

Vero Electronics Ltd.  
Retail Department.  
Industrial Estate,  
Chandler's Ford.  
Hampshire. SO5 3ZR.  
Tel. (042 15) 62829

**vero**  
**vero**  
**vero**

### Vero Hobbyist Brochure.

I enclose 40p. for package and postage

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Firmware from Mutek

## CEGMON

The new monitor PROM for UK101 and Ohio Scientific systems, with the right range of features!

**Twin-cursor screen editor**

**Improved keyboard routine**

**New programmable screen handler**  
defined scrolling area, protected 'windows'  
screen and 'window' clear, cursor controls

**New expanded machine-code monitor**  
vastly simplifies machine-code programming

**Disc bootstrap loader, and much more**

Complete with full manual and reference card for

**£29.50+VAT**

## BASIC 1 and 3

Replacement PROMs to allow direct entry of graphics and to fix the string-array handling bug respectively in the OSI/UK101 BASIC-in-ROM.

**£15.00+VAT for the pair**

**MUTEK**

Quarry Hill Box, Wilts  
Tel: Bath (0225) 743289

### PARNDON ELECTRONICS LTD.

Dept. No. 21 44 Paddock Mead, Harlow, Essex, CM18 7RR. Tel: 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range  $\pm 5\%$  tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.

**£1.00** per hundred mixed (Min 10 per value)

**£8.50** per thousand mixed (Min 50 per value)

Special stock pack. 60 values. 10 off each **£5.50**

**DIODES:** IN4148 3p each. Min order quantity — 15 items.  
**£1.60** per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed base — solve those programming problems.  
4 Way **86p** each. 6 Way **£1.00** each. 8 Way **£1.20** each.

**DIL SOCKETS:** High quality, low profile sockets.  
8 pin — **10p**. 14 pin — **13p**. 16 pin — **15p**. 18 pin — **19p**. 20 pin — **25p**.  
22 pin — **29p**. 24 pin — **35p**. 28 pin — **39p**. 40 pin — **57p**.

**ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS**  
MIN ORDER — U.K. £1.00. OVERSEAS £5 — CASH WITH ORDER PLEASE

## 27/28 MHZ CONVERTER

AS FEATURED IN THIS ISSUE

**KIT OF PARTS AVAILABLE**

Price on application

**CB ACCESSORIES, AERIALS ETC**

**ALSO AVAILABLE**

**COMPUTERS GAMES BOOKS**

**PLEASE SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES.**



**N.I.C.**

UNIT 9, 61 BROAD LANE, LONDON N15 4QJ  
Day 01-808 0377; Eve 01-889 9736



(PE)





# INDUSTRY NOTEBOOK

*By Nexus*



## Sparkle

The optimistic sentiment of Industry Notebook throughout 1980 inevitably attracted criticism in a period when British industry in general was being universally portrayed as in a critical state, if not actually wounded beyond recovery. My confidence, of course, was confined to the electronics industry and year-end results proved that confidence was well-founded.

It was a dank December day when GEC, Plessey and Ferranti all brought a touch of sunshine and warmth with their latest trading results. Even in good times the performance of all three would have been creditable. Set against the prevailing gloom they positively sparkled. GEC profits were up from £155 million to £190 million. Plessey first-half profits soared from £19.4 million to £38.6 million. Ferranti was equally impressive with a leap from £3.5 million to £6.4 million. And all three have substantial order books to keep them busy through to 1982 and beyond.

Such results are all the more remarkable when one recalls that quite recently, before major surgery, Plessey's performance was mediocre and Ferranti suffered the humiliation of a 'rescue'. GEC, a conservative plodder rather than a sparkler, proved once again that good products and a diverse market backed by sound management is not only a recipe for survival but also for improvement in bad times as well as good.

## Aye, Aye, Sir!

The Racal Group, historically the brightest sparkler of all, is currently maintaining a low profile, financially speaking, while attempting to re-invigorate Decca. Nobody doubts Racal's ability in this respect. Only the length of time needed to effect the transformation.

Chairman Ernie Harrison had no sooner received the Group's 10th Queen's Award than another honour came along. That of Captain of Industry awarded to Harrison by the Livingstone Industrial and Commercial

Organisation. Whether the Captain tag will stick is open to question but in the nautical sense it should because Harrison runs one of the tightest and fleetest ships in the business, not to mention new-acquisition Decca with its close association with merchant fleets and navies and his own war-time call-up when he trained as a Fleet Air Arm pilot.

'Captain' Harrison is navigating towards a landfall of £500 million turnover in the current financial year. He will probably make it but with little more, if any, than last year's £61 million pre-tax profits. Racal-Decca is bound to be a drag until its bottom is cleared of branches and that may take a lot longer than a year.

But overall the Group is as lively as ever. On the Racal-Decca trip the new ARPA (Automatic Radar Plotting Aids) radar was well-received. This is the type which is to be a mandatory fit on all large vessels this decade. Racal-Decca hopes to achieve one third of the sales to some 10,000 ships to be fitted and although deliveries will not start until the autumn some 50 sets have already been sold or are in negotiation. R & D cost £2 million and selling price per set is in the £27,000 upwards bracket with a potential sale of £100 million worth over the next ten years.

Elsewhere in the Group a co-operative agreement has been reached with US General Electric in mobile radio which has resulted in the formation of Racal Messenger Ltd headed up by Gerry Whent, a Racal live-wire who says he will be addressing a market worth £500 million a year. Another important agreement is with General Instrument Micro-electronics in which the two companies will co-operate in production of oxide isolated silicon gate CMOS circuits.

Less publicised was another Anglo-USA tie, this time between Decca and Wilcox Electric which has now come to fruition in Racal's emergence as a principal supplier of ILS systems with the first of 37 for the Ministry of Defence already installed at RAF Abingdon. Watch out, too, for Racal penetration of the offshore oil industry spearheaded by Racal-Decca Survey.

## De-manning

Although of little consolation to our own unemployed it is worth drawing attention to the difficulties of others resulting not so much by trade recession as of technology change. The flourishing Thomson Group in France, for example, is to axe 5,000 employees by 1983, 4,000 of them in telecommunications because of change in the type of systems being made. This is a parallel of our own switch from electro-mechanical to electronic exchanges. Unskilled labour, according to Thomson will need to be cut by half while qualified engineers employed will increase by one third.

We tend to imagine that drastic changes of this nature are an entirely new phenomenon of the last quarter of the twentieth century. In fact it is only the latest phase of an historical progression. Nobody today would dream of employing a

hundred navvies with picks and shovels on motorway construction when a bulldozer manned by a single driver will perform the task quicker, better and more economically.

The silicon chip in its numerous applications is no different in principle, only the newest of a long line of innovative tools invented for a better if not the ultimate 'good' life.

The Association of Professional, Executive, Clerical and Computer Staff (APEX) is complaining bitterly that companies are using the world trade recession as an excuse for shedding staff so that they can introduce new technology 'through the back door'. I don't doubt it, if only because APEX and other like-minded organisations stop it coming through the front door, or let it in only to impose penalties on operation which largely neutralise any planned gains. The Unions, in their view, are performing the function for which they were created but rigid rejection of new practices or excessive demands for compensation can result in total closure as, for example, the Times newspaper group.

According to John Yeomans of Urwick Nexos Ltd, in most Western countries office workers now account for over 50 per cent of the working population and the proportion is still increasing. This area is fertile ground for innovation and the present decade will see enormous expansion in the capital-intensive electronic office. Good news for the supplying electronics industry—bad news for office workers displaced by the electronic revolution.

Continued de-manning or, to put it another way, continuous increase in worker productivity, is here to stay and it seems likely that a level of 10 per cent unemployment will have to be accepted as normal, whatever the pious hopes of politicians.

## Captain

Another Captain, unrelated to Captain Ernie Harrison (see above), is Character And Pattern Telephone Access Information Network. This ingenious English-language acronym is remarkable for being purely Japanese in origin and is in fact the name for a Japanese relation of Prestel. Another unusual feature is that the experimental trials proudly started on Christmas Day back in 1979 as if Captain were a special treat, although Japan is a decidedly non-Christian country.

Captain now has over 1,000 terminals operating in the Tokyo area and like Prestel relies on frames of information supplied by nearly 200 organisations such as press agencies, department stores and travel firms. Where Captain differs from other videotext systems is that it will handle hand-drawn pictures and Chinese and Japanese ideographs and syllabaries of extremely complex shape. I often wonder whether the intricacies of Japanese texts and the mental effort to communicate in a far-from-simple script is one reason why the Japanese are so sharp and hard working. Or is our 'simple' 26-character alphabet and formation of words and sentences just as baffling to them as theirs is to us?



# AUDIO LINES

BEN DUNCAN

THIS article attempts to answer many of the more perplexing queries associated with audio transmissions in professional and domestic audio applications.

## AUDIO MATCHING

Almost without exception, the outputs of audio circuits are treated as voltage sources, and audio equipment interfaces are arranged to cause a negligible voltage loss. There is no intrinsic merit in this approach. Current matching can be equally valid for some systems. But a by-product of transistor audio circuits exhibiting very high open loop gain and using abundant negative feedback (for the sake of good linearity) is a chance to choose the values of input and output impedances. Since audio transducers tend to prefer (or are designed to prefer) voltage matching, audio circuit input and output impedances throughout a system are chosen to accord with this arbitrary matching scheme.

In theory, this boils down to making the input impedance ( $R_{in}$ ) of a stage at least ten times greater than the output source impedance ( $R_s$ ) of the preceding stage. In practice, the ratio  $R_{in}/R_s = 10$  is often too low and distortion can result in the preceding stage, particularly when the output voltage approaches the supply rails. A 741 op-amp, for instance, with near 100 per cent negative feedback may have an output impedance of a fraction of an ohm at audio frequencies. But it would not look favourably upon an  $R_L$  ten times greater, say 5 ohms, owing to the internal current limit, necessary to prevent excessive dissipation in the i.c.'s output stage.

A 741 will happily feed a 10k load with an output of several volts, however, with  $R_L < 2k$ , current limiting greatly reduces the output voltage, and the loading decreases the loop gain. The net effect is serious distortion, particularly at high frequencies.

The behaviour of the 741 is typical of the majority of small signal amplifiers, whether discrete or integrated; a good rule of the thumb for these is to make  $R_{in}$  no less than 10k. However, the temptation to go to town with ultra-high input impedances is just as partisan as expecting a 741 to drive 600 ohms at  $\pm 20\text{dBm}$ . Input impedances in excess of 100k are quite harmless while they are tied down to a low source impedance, but in the case of an unused channel or input (excepting those which can be shorted when redundant),

thermal noise, microphony, RFI and capacitively induced hum are foibles to beware of.

In general, input impedances between 10k and 100k are satisfactory. Opt for the 100k region when low cost, domestic audio equipment is being interfaced, and around 10k in PA applications. If you have 300 feet of cable plugged into a 500 watt amplifier, and the plug falls out at the wrong end, or the cable's screen connection breaks, and the amplifier has a 10k input impedance, it will probably do no more than arouse the interest of the sound engineer! On the other hand, an amplifier with a 1M input impedance under the same circumstances is likely to pick up enough RFI, hash, and hum to destroy itself, and an expensive loudspeaker.

## BALANCED LINES AND LINE DRIVERS

In professional audio applications, it is often desirable to be able to connect equipment in any combination without worrying about earth loops. Another requirement, being a particularly stringent one in recording studios, is that audio lines must not pick up any interference or stray signals whatsoever.

The balanced line shown in Fig. 1 can meet these requirements. The purpose of the input transformer is to make the signal appear in opposite phases across the lines (B, C). T2, at the input of the following stage, recombines these out of phase signals paying no attention to signals which appear in phase across the lines. The phase of any interfering electromagnetic waves or electric fields acting on the wires will be identical; this assumes that the wavelength of the interference is much greater than the distance between the conductors, which is true up to UHF frequencies, and the induced interference, being in phase, is cancelled out at T2. In addition, the isolating action of the transformer prevents earth loops; the only common earth connections are between the equipment chassis and these earth connections normally have no effect on the signal. Finally, interference picked up and drained to earth via the screen cannot intermingle with the return signal currents, as in a normal screened cable.

The stage feeding the line is appropriately termed a 'line driver' and here is a special case where a small signal stage is required to drive an impedance  $\ll 10k$ , typically at levels of

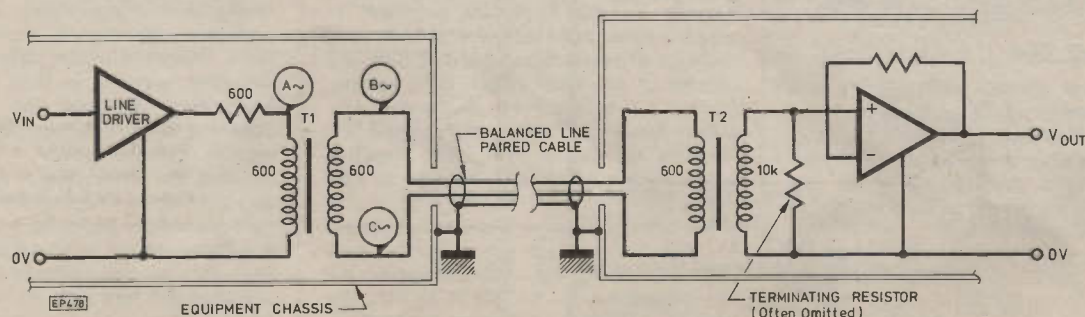


Fig. 1. A balanced line



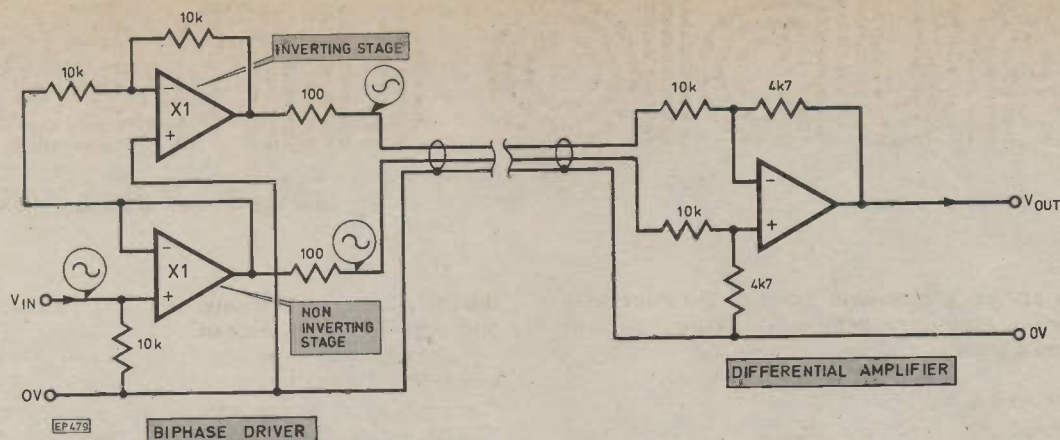


Fig. 2. Op-amp may be used in place of transformers to balance a line

1–10V r.m.s. High performance op-amps are capable of driving 8V r.m.s. or so into 600 ohms, but higher voltages are often required, and here, a discrete stage may be 'tacked onto' the output of an i.c. op-amp. Such a stage usually takes the form of a low-power class AB amplifier. As its name suggests, the line distribution amplifier is similar but designed to be capable of driving several 600 ohm lines simultaneously. This type of amplifier is used primarily by broadcasting organisations for programme distribution, and an essential requirement is that if several of the lines are short circuited, the line distribution amplifier carries on regardless.

The interference rejection properties of a balanced line system depend greatly on the qualities of the transformers. Although transformers can be cheap and elegant problem solvers when correctly applied, they have imperfections and if these are not heeded, transformers can create as many problems as they are intended to solve. Reputable transformer manufacturers will offer numerous models and copious data for this reason; they will also frequently custom-design a transformer for your application. This is by far the best course. Transformers are sometimes disregarded altogether, ostensibly on the basis of cost, and a line is balanced 'electronically'—which is a clumsy way of saying that a pair of op-amps are used to provide the out-of-phase signals. Fig. 2 shows this arrangement, which is cheaper than using a transformer at high levels (1V); the performance, however, is not necessarily any better, particularly at high frequencies, where interference rejection can fail miserably.

#### QUASI-BALANCED LINES

Balanced lines using transformers are most successful in recording studios and radio stations, where the environment

is well ordered, or when used for entertainment in small venues, where cable lengths are short and conditions are not especially arduous. Large rock concert PA systems, on the other hand, often seem to attract the epitome of all that is taboo in a high-quality audio system—RF pick-up, instability, earth loops, plus resonances and response irregularities in the audio band. With the feeling that balanced lines between the mixing desk and the amplifiers cause more problems than they solve, or at best give a false sense of security, some of Britain's more innovative hire companies have broken with tradition and returned to using unbalanced lines—just standard, screened wires.

Another arrangement which breaks with tradition is quasi balancing (Fig. 3). The important point is that the cable screen carries no signal current—as in the balanced line—its purpose is solely to provide electrostatic shielding and to drain interference currents to ground, via the equipment chassis. Note that the screen is connected at one end only.

The long cable coupled to the output of the line driver in Fig. 3 presents an essentially capacitive load at low frequencies. This parallel capacitance introduces a phase lag and can precipitate instability, particularly in op-amp line drivers. One solution is to add a series resistor, as in Fig. 4a. Regrettably, this increases the source impedance of the line, causing a slight loss of headroom at the very least. By placing the series resistor in the feedback loop, low output impedance is restored, but now RFI picked up along the line can easily enter the line driver's input via the feedback loop (Fig. 4b). A series choke can be added in series outside the loop to circumvent this effect; or the choke can simply be used in place of the series resistance in Fig. 4a. In this case, it not only buffers the line capacitance, but acts to reject RFI.

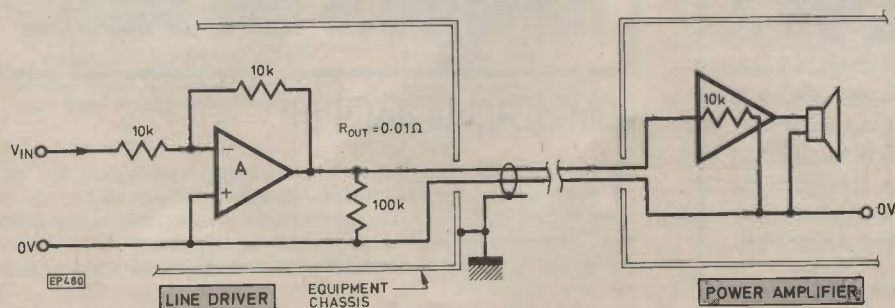


Fig. 3. A quasi-balanced audio line. The cable screen carries no signal current as in the balanced line it being connected at one end only



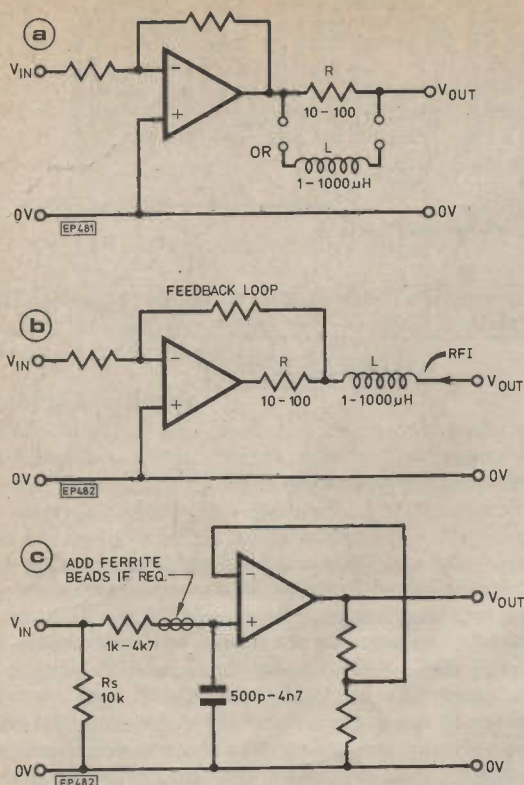


Fig. 4. (a) Overcoming instability caused through a long cable; (b) Preventing RFI entering a line driver; (c) Attenuating RFI at a line input

RFI rejection is equally important at the input of the stage following the line: a simple RC network will usually suffice here (Fig. 4c) but in exceptional cases, ferrite beads may be added at point 'A'.

#### EARTHING

Earth loops in both unbalanced and quasi-balanced systems are avoided by simply earthing the OV rails to the mains earth at one point only in the system. This is usually at the mixing desk to provide the tightest ground for the low-level signals from microphones. OV rails and chassis earths are kept separate throughout the system; the latter are always connected to mains earth for safety. Equipment other than the mixer may have OV rails connected to the chassis

via a resistor to prevent annoying buzzes due to an open circuit OV along the line. These resistors appear in parallel, and to prevent the tiny earth loop currents growing to produce an audible hum, a minimum total value of 22-100 ohms is usually advisable. The resistor values will therefore be in the region of 100-4k7 when a lot of equipment is involved. A parallel capacitor may be used to tie the OV rails to chassis at radio frequencies, though this may aggravate RFI in certain cases.

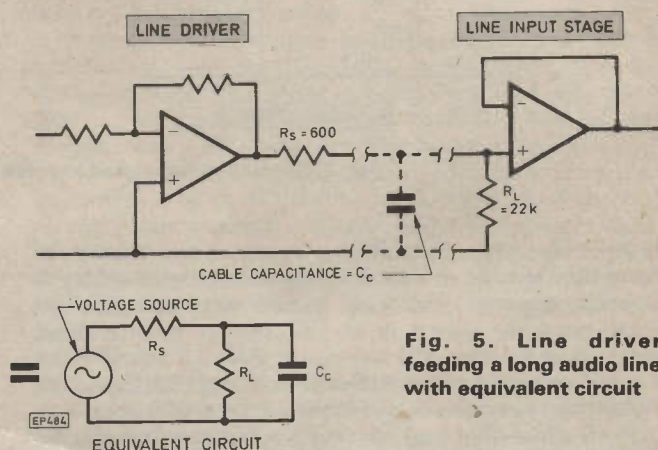


Fig. 5. Line driver feeding a long audio line with equivalent circuit

Finally, long audio lines can exhibit enough capacitance to cause premature high frequency roll off. Looking at Fig. 5, it's obvious that the source impedance ( $R_s$ ) should be as low as possible to keep the -3dB breakpoint well above the audio band. In the example given, the -3dB point occurs at a paltry 14kHz. However, in balanced line systems, power matching ( $R_s = R_L$ ) is common; usually the impedance is 600 ohms. Power matching provides a 50 per cent voltage loss, but in this example, making  $R_L$  600 ohms instead of 22k will raise the -3dB point to a fairly acceptable 28kHz. However, a voltage matched system using an op-amp or line driver with  $R_s$  typically  $\ll 1$  ohm is clearly a far better arrangement. The moral, then, is to avoid traditional 600 ohm balanced line systems unless you can be sure their limitations aren't going to be balanced by very real advantages. ★

## ON SALE NOW!

Our new book *PE Popular Projects* containing a selection of popular recent projects is now on sale at newsagents and components stores. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid or £1.80, overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

## News Briefs

### COMMERCIAL BACK-UP

THE originator of the UK101 User Group, Adrian Waters, has formed a company in conjunction with Mr. K. Stale, called 'Computer User Aids'. This full-time situation is expected to enable the organisers to cope more easily with the overwhelming response and demands of the group, and should provide such back-up as various properly marketed kits.

The address of Computer User Aids is: 9 Moss Lane, Romford, Essex, RM1 2QB.



# Outstanding value. Superb support.



Commodore produce Britain's number one microcomputer. But we don't stop there. We also insist on providing comprehensive support throughout our national dealer network.

Our dealers can examine your needs and demonstrate which hardware and software will suit you best. Their trained engineers are always at hand and a 24-hour field maintenance service is available.

Ask your local dealer to tell you more about the following Commodore Services.

**The Commodore PET**  
The Commodore PET computer range covers everything from the self-contained unit at under £500 to complete business systems at under £2,500.

**Commodore Business Software and Petpacks**  
Our software range covers hundreds of applications. Business software includes Sales and Purchase Ledgers, Accounting, Stock Control, Payroll, Word Processing and more. In addition over 50 Petpacks are available covering such titles as Strathclyde Basic Tutorial, Assembler Development System, Statistics, plus our Treasure Trove and Arcade series of games.

**Commodore Approved Products**  
Compatible products of other manufacturers with Commodore's mark of approval are also available.

**Commodore Courses**  
Commodore offer a range of residential training courses and one day seminars. An excellent start. And when you have installed your system the PET User's Club Newsletter can keep you informed of new ideas and latest developments.

## LONDON AREA

Advanced Management Systems, EC2. 01-638 9319  
Centralex - London Ltd, SE13. 01-318 4213  
Computer Sales & Software Centre Ltd, ILFORD, 01-554 3344  
Cream Microcomputer Shop, HARROW, 01-863 0833  
Da Vinci Computer Shop, EDGWARE, 01-952 0526  
Henderson Bennett, SE25. 01-654 5609  
Home and Business Computers, E12. 01-472 5107  
L & J Computers, NW9. 01-204 7525  
Logic Box Ltd, SW1. 01-222 1122  
Merchant Systems Limited, EC4. 01-353 1464  
Micro Computer Centre, SW14. 01-878 3206  
Sumlock Bondain Ltd, EC1. 01-250 0505  
Sumlock Bondain Ltd, EC4. 01-626 0487

## HOME COUNTIES

Millhouse Designs Ltd, ALTON, 84517  
HSV Microcomputers, BASINGSTOKE, 62444  
MMS Ltd, BEDFORD, 40601  
Amplicon Micro Systems Ltd, BRIGHTON, 562163  
T & V Johnson (Microcomputers Etc) Ltd, CAMBERLEY, 20446  
Wego Computers Ltd, CATERHAM, 49235  
Dataview Ltd, COLCHESTER, 78811  
Amplicon Micro Systems Ltd, CRAWLEY, 26493  
S.M.G. Microcomputers, GRAVESEND, 55813  
South East Computers Ltd, HASTINGS, 426844  
Bromwall Data Services Ltd, HATFIELD, 60980  
Alpha Business Systems, HERTFORD, 57423  
Commonsense Business Systems Ltd, HIGH WYCOMBE, 40116  
Kingsley Computers Ltd, HIGH WYCOMBE, 27342  
Brent Computer Systems, KINGS LANGLEY, 65056  
Computopia Ltd, LEIGHTON BUZZARD, 376600  
South East Computers Ltd, MAIDSTONE, 681263  
J.R. Ward Computers Ltd, MILTON KEYNES, 562850  
Sumlock Bondain (East Anglia) Ltd, NORWICH, 26259  
T & V Johnson (Microcomputers Etc) Ltd, OXFORD, 721461  
C.S.E. (Computers), READING, 61492  
Slough Microshop, SLOUGH, 72470

Business Electronics, SOUTHAMPTON, 738348  
H.S.V. Microcomputers, SOUTHAMPTON, 22131  
Super-Vision, SOUTHAMPTON, 774023  
Symtex Systems Ltd, SOUTHAMPTON, 38868  
Stuart R Dean Ltd, SOUTHEAST-ON-SEA, 62707  
The Computer Room, TUNBRIDGE WELLS, 41645  
Orchard Computer Services, WALLINGFORD, 35529  
Photo Acoustics Ltd, WATFORD, 40698  
Microchips, WINCHESTER, 68055  
P.P.M. Ltd, WOKING, (04867) 80111  
Oxford Computer Systems, WOODSTOCK, 812838

## MIDLANDS & S. HUMBERSIDE

C.B.S. Consultants, BIRMINGHAM, 772 8181  
Marchant Business Systems Ltd, BIRMINGHAM, 706 8232  
Micro Associates, BIRMINGHAM, 328 4574  
Peach Data Services Ltd, BURTON-ON-TRENT, 44968  
Jondane Associates Ltd, COVENTRY, 664400  
Davidson-Richards Ltd, DERBY, 366803  
Allen Computers, GRIMSBY, 405 68  
Caddis Computer Systems Ltd, HINCKLEY, 613544  
Machsize Ltd, LEAMINGTON SPA, 312542  
Arden Data Processing, LEICESTER, 22255  
Roger Clark Business Systems Ltd, LEICESTER, 20455  
Lowe Electronics, MATLOCK, 2817  
A.J.R. Office Equipment Services Ltd, NOTTINGHAM, 206647  
Betos (Systems) Ltd, NOTTINGHAM, 48108

PEG Associates (Computer Systems) Ltd, RUGBY, 65756  
Walters Computer Systems Ltd, STOURBRIDGE, 70811  
Systems Micros, TELFORD, 460214

## YORK & N. HUMBERSIDE

Microprocessor Services, HULL, 23146  
Holdene Ltd, LEEDS, 459459  
South Midlands Communications Ltd, LEEDS, 782326  
Yorkshire Electronics Services Ltd, MORLEY, 522181  
Computer Centre (Sheffield) Ltd, SHEFFIELD, 53519  
Hallam Computer Systems Ltd, SHEFFIELD, 663125  
Holbrook Business Systems, SHEFFIELD, 484466

## NORTH EAST

Dyson Instruments, DURHAM, 66937  
Currie & Maughan, GATESHEAD, 774540  
Elfton Ltd, HARTLEPOOL, 61770  
Fiddes Marketing Ltd, NEWCASTLE, 815157  
Intex Datalog Ltd, STOCKTON-ON-TEES, 781193

## S. WALES & W. COUNTRY

Radan Computational Ltd, BATH, 318483  
C.S.S. (Bristol) Ltd, BRISTOL, 779452  
T & V Johnson (Microcomputers Etc) Ltd, BRISTOL, 422061  
Sigma Systems, CARDIFF, 34869  
Reeves Computers Ltd, CARMARTHEN, 32441  
A.C. Systems, EXETER, 71718

Milequip Ltd, GLOUCESTER, 411010  
Micro Media Systems, NEWPORT, 59276  
J.M. Computer Services Ltd, NEWQUAY, 2863  
A.C. Systems, PLYMOUTH, 260861  
J.A.D. Integrated Services, PLYMOUTH, 62616  
Business Electronics, SOUTHAMPTON, 738248  
Computer Supplies (Swansea), SWANSEA, 290047

## N. WEST & N. WALES

B+B (Computers) Ltd, BOLTON, 26644  
Tharstern Ltd, BURNLEY, 38481  
Megapalm Ltd, CARNFORTH, 3801  
Catlands Information Systems Ltd, CHESTER, 46377  
Catlands Information Systems Ltd, WILMSLOW, 527166

## LIVERPOOL

Aughton Microsystems Ltd, LIVERPOOL, 548 7788  
Stack Computer Services Ltd, LIVERPOOL, 933 5511

## MANCHESTER AREA

Byte Shop Computerland, MANCHESTER, 236 4737  
Cytek (U.K.) Ltd, MANCHESTER, 872 4682  
Professional Computer Services Ltd, OLDHAM, 061-624 4065

## SCOTLAND

Gate Microsystems Ltd, DUNDEE, 28194  
Holdene Microsystems Ltd, EDINBURGH, 668 2727  
Gate Microsystems Ltd, GLASGOW, 221 9372  
Robox Ltd, Glasgow, 221 5401

To: Commodore Information Centre,  
360 Euston Road, London W1 3BL. 01-388 5702  
Please send me further information about the Commodore PET.

Name \_\_\_\_\_

Position \_\_\_\_\_

Address \_\_\_\_\_

Intended application \_\_\_\_\_

Do you own a PET? YES ☐ NO ☐

**commodore**

01PE1

This list covers dealers participating in our advertising.





# CEGMON

*What can it do for your* **UK101?**

**C**EGMON is to some extent a "clear up" campaign by Ohio Scientifics, in which a 2516/2716 EPROM replaces the original SYNMOM ROM to give the system the benefit of a full 2K monitor and all the facilities that this allows. Ohio's original monitor was all things to all machines, such that the 2K in your Superboard monitor would have only a small part of it dedicated to your particular machine, the rest being there to make the same package compatible with other systems in Ohio's range. This philosophy is a hangover from the days of more expensive memory, and the situation is the same for MONUK101 on the Compukit, which of course, is the son of Superboard!

Now, for the sake of two or three very simple wiring alterations to accommodate the 2716's Enable and supply lines, you can plug in the CEGMON chip and be ready to go; immediately having the following additional power to your programming elbow:

## ASCII KEYBOARD

The polled keyboard is decoded in conventional ASCII format, such that with Shift-Lock released it is rather more conventional. The two Shift keys are decoded identically; Carriage-Return, Line-Feed, Rubout and Escape (not UK101) are all accessible regardless of the state of Shifts or Shift-Lock. Control returns the same value from alphabetical keys regardless of Shift or Shift-Lock, whereas Shift-Lock does work with Control for *non-alphabet* keys, to access otherwise inaccessible characters. For the same reason, Shift and Shift-Lock pressed together with alphabetic keys will still produce a range of unrelated characters, in order to allow Shift-K to -O to access the up-arrow (and others in the range 91-95).

## A SCREEN HANDLER

Cegmon's screen control system allows a protected area and a scrolling window. All output to the screen is via a window whose position, height and width are user-definable, and software controllable. Four cursor-position commands, a window-clear command, and full screen-clear, are available, see Table 1. The display starts at the *top* of the screen, and printing is very fast until scrolling is necessary.

**Table 1. Cursor Controls**

CTRL-J	CHR\$(10)	cursor down (Line-Feed)
CTRL-K	CHR\$(11)	cursor right
CTRL-L	CHR\$(12)	cursor home (to top left of window)
CTRL-M	CHR\$(13)	cursor left to start of line (Carriage Return)
CTRL-Z	CHR\$(26)	clear screen
CTRL-SHIFT-N	CHR\$(30)	clear window

Window-clear is called by CTRL-"up-arrow" or CHR\$(30), which clears and homes but does not print the cursor. Total screen clear is implemented by CTRL-Z, or CHR\$(26).

Programming with multiple windows is possible, and parameters of the current window are held in five memory locations, from 546-550, see Table 2. SWIDTH needs to be one less than the number of characters to be printed per line.

**Table 2. Store Names and Contents**

SWIDTH	column width (-1)
SLTOP	low byte of TOP
SHTOP	high byte of TOP
SLBASE	low byte of BASE
SHBASE	high byte of BASE
LTEXT	555 low byte of text-line start
HTEXT	556 high byte of text-line start

Scrolling and clearing operate from the window TOP and BASE inclusive, such that, for example, one section of screen may be scrolled relative to another *static* part of the screen. A danger, however, is that no check is made to ensure that TOP and BASE are within the screen memory! But this does allow any memory-mapped device to be accessed and PRINTed to by defining a window. Ideal for PRINTing colour values or PRINTing to an additional display. This does give the expansionist enormous flexibility.

## IN THE MONITOR

Cegmon is not as comprehensive as OSI's Extended Monitor (ExMon), but it may be co-resident with both BASIC and Assembler, and is immediately available on switch-on, of course. It would be useful for developing short m/c routines or for debugging larger routines being developed with an Assembler.

On start-up via M, the monitor's prompt > appears after a clear-screen. The commands then available are:

/ jump to data mode, leaving current address unchanged  
 . "do nothing"—loop back to get address  
 L sets load flag—calls for input from the BASIC load vector at \$FFEB  
 S save machine code  
 M do memory block move  
 T do tabular dump/display of memory contents  
 Z set a breakpoint  
 R restart from a breakpoint  
 U jump to user routine



In the data mode loop the following commands are available:

- return to address mode
- / re-open current address, to correct a mis-type
- G** start execution at the current address
- enter text entry loop
- increment current address
- LF** (Line-Feed)—increment current address, do CR/LF, display new current address and contents on next line
- CR** (Carriage Return)—as for LF, but do CR only; display by overwriting on same line
- (up-arrow, SHIFT-N)—as for LF, but decrement current address

In Command/address mode the following key strokes apply:

- / jump to data mode
- On start-up, the current address is set to zero; thereafter it is not changed on a restart.

#### **L load**

The m/c load flag is set and the system restarts at the beginning of the data mode loop. It then expects input via the ACIA, either from tape or RS-232 serial interface. Load can run up to 4800 Baud (1MHz machine).

#### **S save**

The Syntax is: .Saaaa,bbbb cccc where cccc is the restart address, either to the beginning of the routine for auto-start, or back to the monitor. Code is saved from aaaa to bbbb. Save waits until Return is pressed to give you time to start your recorder. The "start" and "go" addresses and hex codes are displayed. It should be noted that the CR which separates each byte is directed to the ACIA, and as a result, this routine cannot vector a user-defined output, i.e. it can only be used through the ACIA for the cassette port and RS-232 interface.

#### **M memory block move**

This Syntax is: .Maaaa,bbbb cccc where aaaa is the start of the code to be copied, bbbb is the end, and cccc is the new start location.

#### **T tabular display**

Syntax: .Taaaa,bbbb where the code displayed is aaaa—bbbb. The memory contents are displayed as a table of eight-byte blocks.

#### **Z zero—set breakpoint**

Syntax: .Zaaaa where aaaa is the address at which the breakpoint is to be inserted. The original content of the chosen address is stored at BRKVAL.

#### **R restart**

Restart from a breakpoint.

#### **U jump to user routine**

Causes a jump-indirect to a routine whose start address is held in \$0233-34. This is useful for calls to regularly-used locations like the Assembler restart.

In Data Mode: the following keystrokes apply:

- exit to command/address mode
  - / re-open current address
- Used if the value just typed was incorrect.

#### **G go**

Sets all registers to \$00, and starts execution at the current address.

#### **start text mode**

The text mode expects ASCII text rather than hex digits. Control characters such as cursor controls, and graphics characters, can also be typed direct into memory. No editing is possible without exiting back to the data mode.

A second ' exits back to the data mode on the same line.

#### **increment current address**

Used to space succeeding entries into memory. The contents of the missed addresses are left unaltered.

#### **LF line-feed—increment current address, display on next line**

#### **CR carriage-return—increment current address, display on current line**

#### **Up-arrow (SHIFT-N)—decrement current address, display on next line**

Identical to LF, except that the current address is decremented rather than incremented.

#### **EDITOR**

The Editor works in much the same way as that which we published for Compukit in the November 1980 issue of PE, except that it is a full page editor (i.e. the line to be altered need not be listed separately).

The Edit cursor is generated, or eliminated, by CTRL-E, and may be moved around the screen according to the rules shown in Table 3. CTRL-Q copies forward to reproduce on the Edit line at the foot of the screen, and of course, extra characters can be interjected via normal keystrokes, whilst characters can also be "dropped" through the use of CTRL-D.

An editor such as this is the basic next step for anyone wishing to upgrade their system firmware from the standard of the UK101.

**Table 3. Edit Cursor Controls**

CTRL-E	Generate or remove edit cursor
CTRL-D	Move forward (does not copy)
CTRL-Q	Copy forward (copies characters over which it passes)
CTRL-A	Move backwards
CTRL-F	Move down
CTRL-S	Move up

#### **THE MANUAL**

The documentation accompanying CEGMON is well presented and generous in its information, and although most references are intended for the OSI camp, there is very little which does not also apply to the UK101.

Editing, error handling and break-point handling are explained, and much of the philosophy behind CEGMON is revealed too, which is helpful.

A Trace routine, Graph Plotter and other useful software is included in the manual to help the user to make the best use of the facilities available. Perhaps most importantly, a listing of routine entry points, data storage locations, and what each of these does is found at the end of the booklet.

Some of the niggling points of the UK101 remain after fitting CEGMON, like the unnecessary error message on that first attempt at a Command Mode instruction. For instance, after a CTRL-Z (clear screen), the machine will come back with an error message the first time you try to do anything. However, this is familiar behaviour, and the exciting additional facilities which CEGMON provides would, for many users, make it worth the added investment of £29.50 + VAT.

#### **NOTE**

The price of these monitors is, in our view, rather high in comparison to the hardware used (2716's are available for under £5.00 retail). However, we understand that another UK101 monitor is being developed by an independent source and this one will sell at less than £20.00. We hope to review it as soon as it is available.



# We're giving away this soldering iron worth over £10.



Choose any of 10 selected kits from the Heathkit catalogue as your first order, and we'll give you a superb soldering iron worth over £10. Plus a 10% discount!

These kits have been specially designed with first-time kit builders in mind. So even if you've never built an electronic kit before you won't find it difficult. In fact, the simple to follow step-by-step instructions make it easy to build any Heathkit kit.

And with your special offer discount you can afford to see just how easy it is.

Full details of this FREE offer are available in the Heathkit 48 page catalogue. So send the coupon for your copy now.

To: Heath Electronics (UK) Limited, Dept. (PE3), Bristol Road, Gloucester, GL2 6EE.


Please send me a copy of the Heathkit catalogue. I enclose 25p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

NB: If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

# HEATHKIT



4 1/2 in x 3 1/2 in **METER.** 30µA, 50µA or 100µA, **£5.10.** 50p P. & P.

**MICROPHONES FOR TAPE RECORDERS**  
DM228R 200 ohm with 3-5 and 2-5mm Jack Plugs **£1.70**  
DM229R 50K with 3-5 and 2-5mm Jack Plugs **£2.25**  
DM18D 200 ohm with 5 and 3 pin Din Plugs **£1.99**  
Postage on above microphones 17p



### CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. **£8.02.** 50p P. & P.

2in x 2in meters 500µA, **£4.14** 17p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, **£4.00.** 26p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

### MULTI-METER

7 N 360TR  
20,000 ohm/volt  
RESISTANCE  
RANGES  
X1, X10, X1K,  
X10K  
**£13.30**  
P. & P. 75p



### LP30 LOW PASS FILTER

Cut off frequency 30MHz  
**£3.50** post 75p

### SWR9-SWR & FS METER

**£10.20** Post 75p

### CX3 CO-AX SWITCH

For one transceiver to 3 aerials or 3 aerials to one transceiver. 150 watt **£5.65** Post 75p

PL259 Plug **33p**; Socket **33p**; PL259/SO239 Angled Connector **70p**; 1 watt dummy lead **95p**; 2m Rubber Neck Aerial with PL259 Plug **£3.30.** POST ON ABOVE ITEMS 14p.

All above prices include V.A.T. Send 40p for new 1980 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

## M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

## P.E. STAR SPINNER

A FULL KIT OF PARTS AND ALSO INDIVIDUAL ITEMS ARE AVAILABLE AS FOLLOWS FROM  
**FELTGLOW LTD, 105B LONDON ROAD, BEXHILL, E. SUSSEX**

### DESIGNER APPROVED PARTS FOR THIS EXCITING PROJECT

P.C.B. Drilled & Tinned	<b>£6.45</b>
MM2708 Ready Programmed	<b>£11.85</b>
Mains Transformer	<b>£11.75</b>
Set 20 TRIACS	<b>£28.50</b>
Set 20 Darlington Opto's	<b>£19.40</b>
Complete set of I.C.'s (other than above) & Holders	<b>£9.80</b>
Set of Resistors, Caps, etc.	<b>£4.80</b>
Set of Fuse Holders/Fuses/ Switches/LEDs	<b>£10.65</b>
Complete Set of Metalwork comprising: Printed Front Panel Printed Chassis Lid & Heatsinks & Grommets Chrome Front Screws & Internal Fixings	<b>£14.75</b>
Set of DIN Rail Terminals & Rail	<b>£8.60</b>

If Purchased Separately **£126.55**

**SPECIAL OFFER  
FULL KIT  
PRICE OF  
£109.95**

**SAVING £16.60  
OVER INDIVIDUAL  
PRICES.**

**COMPLETE KIT  
INCLUDES FULL  
CONSTRUCTIONAL  
DETAILS**

**PRICES INCLUDE VAT - ADD POST & PACKING 60p  
ON INDIVIDUAL ITEMS - COMPLETE KIT P&P FREE**

Send Cheque or Crossed P.O.'s or Write/Phone your Card No.



**FELTGLOW LTD.**  
105B LONDON ROAD,  
BEXHILL, E. SUSSEX.  
(0424) 221686.





# NEXT MONTH...

## PE DIGISOUNDER



The PE Digisounder depth gauge features an l.c.d. readout and a presettable depth alarm. The system can be calibrated to show the depth in any desired unit—feet, metres, fathoms and will replace the Seafarer type used in many boats, as it utilises the same ultrasonic transducer.



## SPEECH PROCESSOR

Increases the intelligibility of a voice signal by increasing the level of input and reducing noise and harmonic distortion. May be readily inserted in the signal path of PA amplifiers, tape recorders, transmitters and transceivers.

## ULTRASONIC INTRUDER ALARM

Protect your home with our updated ultrasonic alarm system. Modifications to the original design include the use of a sensitivity control, single unit construction and a steady alarm output.

PRACTICAL

# ELECTRONICS

OUR APRIL ISSUE WILL BE ON SALE FRIDAY 13 MARCH 1981



A black and white photograph of a man with glasses driving a car. He is wearing a dark jacket over a light-colored shirt. His hands are on the steering wheel. In the foreground, the car's dashboard is visible, featuring a custom-built electronic device with various knobs, switches, and a small display screen. The device is identified by the text as a 27/28 MHz converter. The background shows the car's interior and a glimpse of the road through the windshield.

# LISTEN IN WITH OUR 27/28 MHz CONVERTER

M. TOOLEY B.A.

THERE is a considerable and rapidly growing interest in listening to radio transmissions in the 10 and 11 metre bands. This is, in no small way, due to the upsurge in 'CB' activity around 27MHz which, although legal in many European countries, is outlawed in the UK. The amateur 28 to 29.7MHz band is adjacent to the band used for 'CB'. This is also an exciting and somewhat surprising band for listeners, lying as it does on the borders between HF and VHF. How, then, does one begin to listen? Very few domestic receivers have a short wave band which extends above 20MHz and the purchase of a specialist "communications" receiver involves a very considerable outlay. What better than to utilise an existing medium wave receiver in conjunction with a purpose built converter. This is a low cost means of starting and yet it is capable of producing excellent results which will satisfy all but the most discerning. Furthermore, the method is ideally suited to mobile applications where a converter may be readily inserted in the connecting lead between a car aerial and receiver.

The circuit described is a converter for use between 26 and 30MHz, the precise frequency coverage being a matter for the individual constructor's preference. It should, however, be emphasised at the outset that this is a high performance unit which should not be confused with inferior "mixers".



The converter offers the following features:

- low noise high gain cascode front-end;
- dual gate f.e.t. mixer for high conversion gain and excellent strong signal handling performance;
- variable r.f. gain for local/DX listening;
- crystal controlled oscillator to ensure accuracy and eliminate drift;
- regulator to cope with large variations in supply voltage;
- normal operation of the medium wave receiver may be restored at the flick of a switch;
- receiver requires no internal modification whatsoever, converter simply connects in the aerial lead.

Low cost, readily available components are used throughout and the circuit may readily be built and aligned by the complete newcomer to r.f. constructional practice. The inductors, in particular, have been designed with ease of construction in mind however the faint hearted will be pleased to note that the coils are also available ready wound.

## FREQUENCY CONVERSION

Frequency conversion is achieved when an incoming signal is combined with a locally generated signal in a device called a mixer. The mixer has a non-linear characteristic so that the oscillator signal is effectively modulated by the incoming signal and additional sum and difference frequency components are present in the output. The basic arrangement of a mixer is shown in Fig. 1. Assuming that the input is at

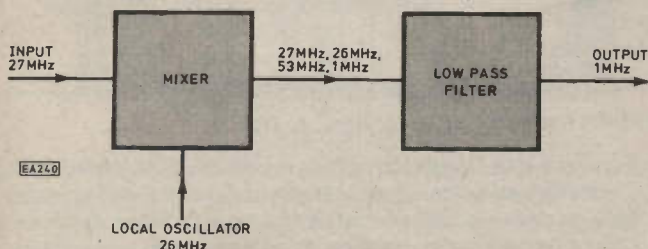


Fig. 1. Frequency conversion process in a mixer

27 MHz and that the local oscillator is at 26 MHz, the output will contain components at 27 MHz, 26 MHz (27-26) MHz, and (27 + 26) MHz. Of these only one, the difference, is required. A simple low pass filter may be used to reject the unwanted signals and allow the 1 MHz component to pass through. The 1 MHz signal will, of course, contain exactly the same modulated information as the 27 MHz input signal.

## DESIGN CONSIDERATIONS

### Local oscillator

A block diagram of the Converter is shown in Fig. 2. The majority of medium wave receivers cover the range 0.6 to 1.6 MHz (500 to 188 metres respectively). Thus the converter should produce output signals over this range. The oscillator frequency must therefore be approximately 1 MHz below (or above) the centre of the desired input signal range. It will then be possible to tune over a 1 MHz wide segment of the 27/28 MHz band and the required oscillator frequency may readily be ascertained from the relationship:  $f_{osc} = f_{sig} \pm f_{out}$ . To ensure a high degree of accuracy and stability the local oscillator should be crystal controlled. This also simplifies the alignment procedure since the crystal guarantees that the oscillator frequency is correct.

### Mixer

The mixer must provide an adequate level of isolation between the input signal and local oscillator. This reduces an

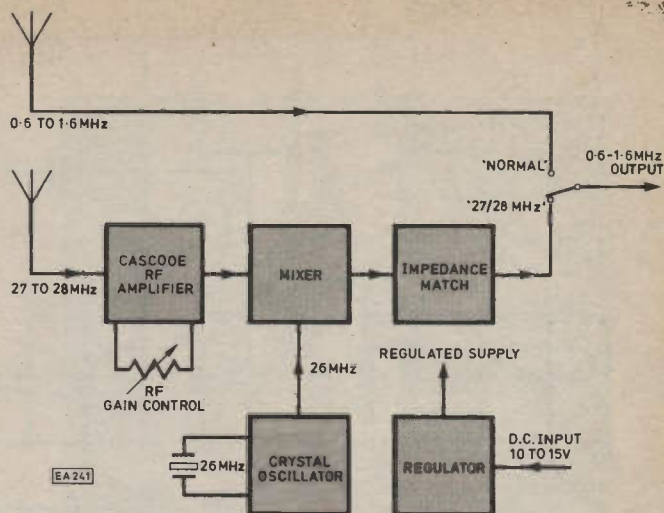


Fig. 2. Block schematic of the Converter

effect known as "pulling" in which the local oscillator frequency changes when a strong input signal is present. This, fortunately, is not normally a problem where the local oscillator is crystal controlled. The mixer must be capable of handling strong signals without cross-modulation or blocking. The dynamic range must therefore be as large as possible but, at the same time, the mixer should exhibit a high value of conversion efficiency. These two requirements are somewhat contradictory since high gain devices can be prone to severe degradation in performance when strong input signals are present. In this respect the dual gate f.e.t. provides a reasonable compromise whilst offering a high degree of isolation and excellent square law characteristics.

### RF stage

An r.f. stage is essential in order to provide rejection of the 1 MHz signal (which would otherwise appear as an interfering signal going "straight through" the mixer) and to reduce interference from unwanted signals on the image channel at around 25 MHz. The r.f. stage also provides some additional gain which can be useful when the input signal level is very small. Selectivity is achieved by the incorporation of several tuned circuits within the r.f. amplifier stage. These can also have the dual function of providing coupling and impedance matching between stages. The active devices in the r.f. amplifier should have a reasonably low noise figure since any noise generated in this stage is given the maximum benefit of amplification in the rest of the receiver.


### Voltage regulation

Most constructors will want to incorporate the converter in a vehicle where the supply will be derived from a nominal 12V battery. Under charging conditions, however, the voltage can rise to around 14V and, when the vehicle is stationary with the engine off, the voltage can fall to around 11.5V. Hence a regulator must be fitted so that this somewhat excessive variation is not passed on to the converter where it may cause variations in both gain and operating frequency. Furthermore, since the internal combustion engine and its associated electrical system is a very effective wideband noise generator (in the form of ignition pulses, dynamo "hash" etc.) the supply rail must be adequately filtered over a wide range of frequencies.
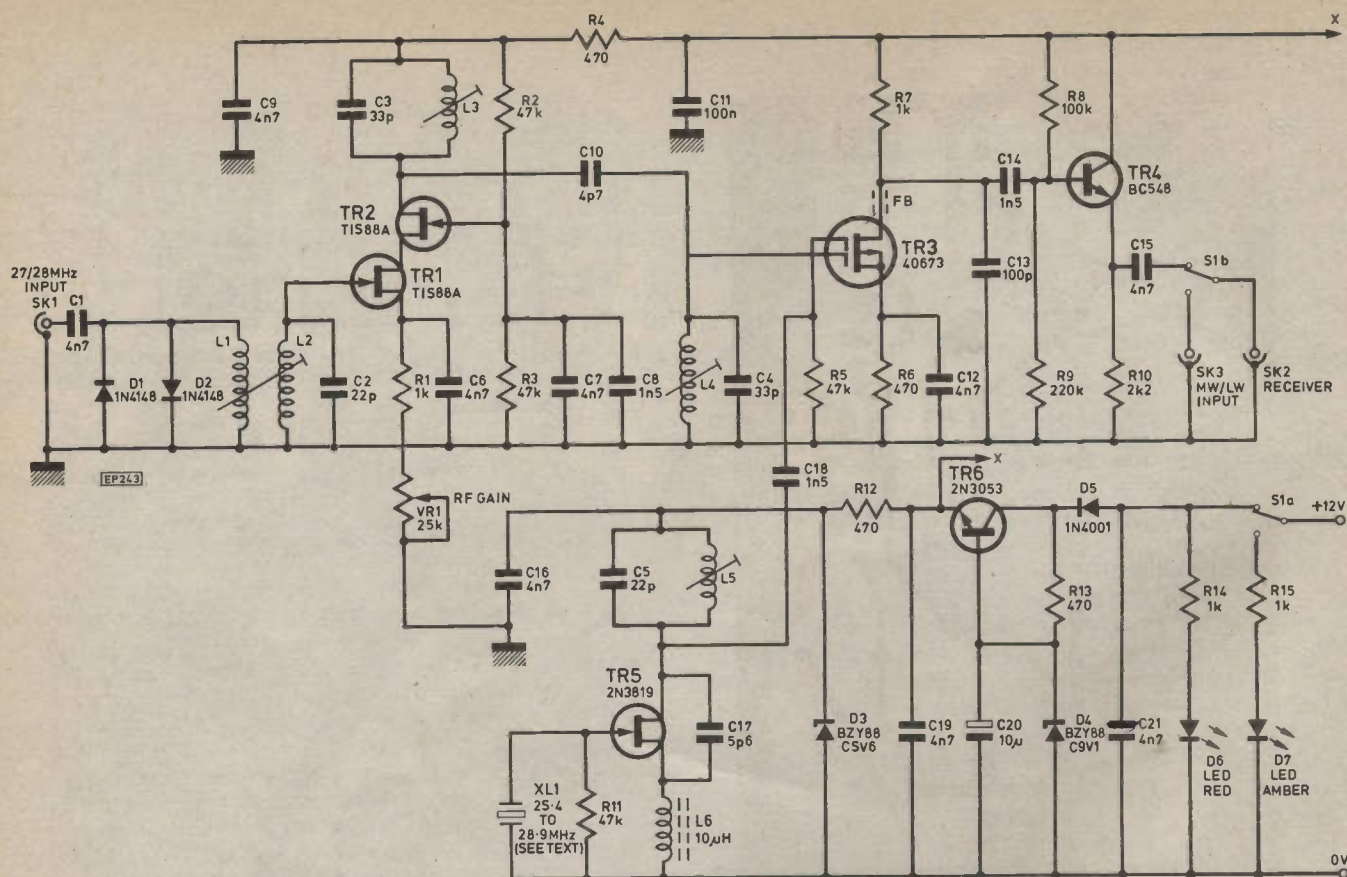
## CIRCUIT DESCRIPTION

The complete circuit diagram of the Converter is shown in Fig. 3. Diodes D1 and D2 provide input protection and con-






duct whenever the input voltage exceeds 1.2V pk-pk. TR1 and TR2 form a cascode r.f. amplifier stage which provides some 26dB of gain with a noise figure of around 2dB. The output of this stage is coupled to the mixer, TR3, via a capacitively coupled bandpass filter formed by C3/L3 and C4/L4. TR5 forms a crystal controlled overtone oscillator, the supply for which is regulated by D3. Oscillator injection is applied to gate 2 of TR3 and the mixer output is developed across R7. The ferrite bead in conjunction with C13 forms a simple low-pass filter and TR4 acts as an impedance matching stage between the mixer and output. The supply rail is regulated at 8.5V by means of TR6 and its associated components. D5 protects against inadvertent reverse polarity connection of the supply and D6 and D7 provide visual indication of the operating status which is either 'normal medium wave' or '27/28MHz'.

## CONSTRUCTION

The majority of the components are mounted on a single sided p.c.b., the foil layout of which is shown in Fig. 4. Whilst the component layout is shown in Fig. 5. No other form of construction should be attempted since this may result in severe instability. It is recommended that the components be assembled in the following sequence; resistors, capacitors, diodes, inductors, transistors, crystal. TR6 should be mounted on an adequate heatsink since, in mobile applications, its dissipation can approach 250mW. Care should be exercised when soldering the crystal to the p.c.b. The minimum soldering temperature should be used and excessive contact with the soldering iron should be avoided. Note that the p.c.b. will accommodate any crystals of the following types: HC25/U, HC6/U, HC18/U and HC33/U. The two latter types are wire ended and are preferred for solder-

ing to a p.c.b. To ensure optimum performance and to avoid instability adequate de-coupling is essential. For this reason only modern type disc or miniature ceramic plate capacitors should be used, other types may be very much less efficient. The inductors are wound according to the data given in Fig. 6. Care should be taken to ensure the correct orientation of the former base relative to the p.c.b. Each former should be fitted with a ferrite dust core and the winding secured by means of a drop of "Denfix" or similar polystyrene solution. (Do not use varnish, lacquer or anything containing a solvent which may attack the enamel coating of the wire). When complete the inductors may be soldered to the p.c.b. and the screening cans should be fitted. Constructors who are lucky enough to possess a grid-dip meter may wish to roughly check the resonant frequency of each tuned circuit before soldering the cans in place.

When the p.c.b. is complete carefully check the board for any errors. The board should then be mounted on four short stand-off pillars and wired according to the layout of Fig. 8. All interconnecting leads should be as short and direct as possible and those from SK2 and SK3 should use short lengths of r.f. co-ax cable. The earth connections of SK1,

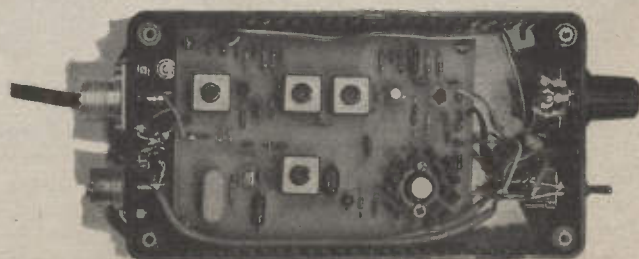




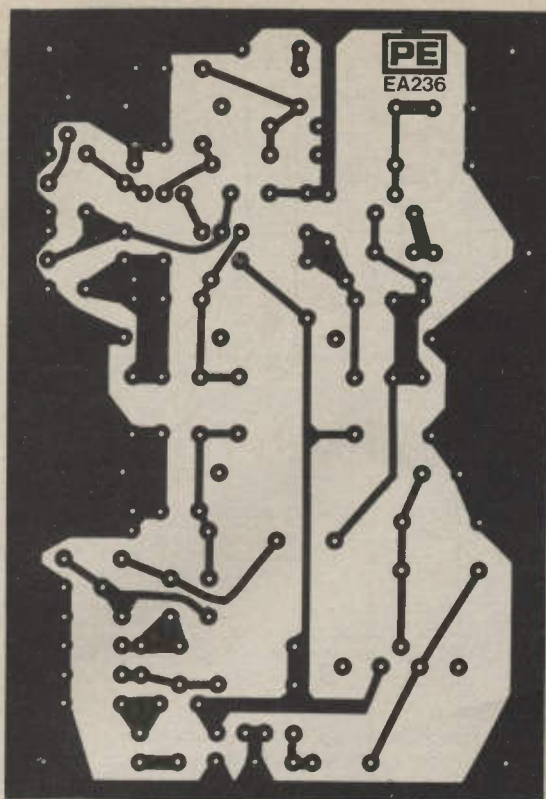


Fig. 4. P.c.b. layout

SK2 and SK3 should be linked by copper braid. The input supply lead should preferably also be screened with the outer (screening) returned directly to the common earth connection of the input and output sockets—this helps to reduce ignition interference. Carefully check the wiring before carrying out the initial checks and alignment procedure which follows.

If the unit is to be fitted in a car a diecast metal case should be used to house the components; for other use a plastic box is suitable.

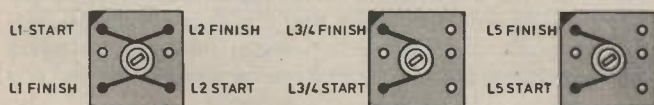

EA239

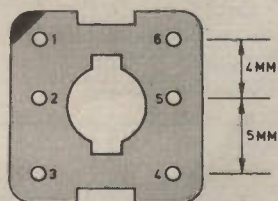


Fig. 6. Coil winding details

### INITIAL CHECKS AND ALIGNMENT

Connect the converter as shown in the interconnection diagram of Fig. 7. When the installation is in a car it is recommended that the aerial lead be cut as close as possible to the receiver and the two cut ends of the cable terminated with standard Belling-Lee co-ax plugs which will mate with

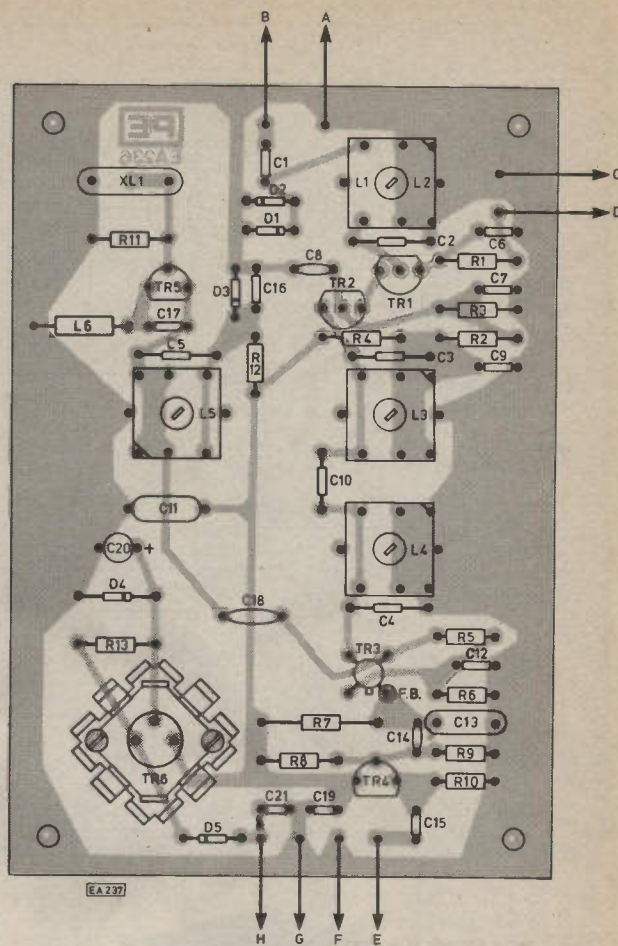


Fig. 5. Component layout

the sockets on the converter. Should the converter later be removed from the car a standard back-to-back socket connector can be used to rejoin the cut length of cable. The 27/28MHz antenna should be mounted as far away from the engine as possible and in as favourable a position as

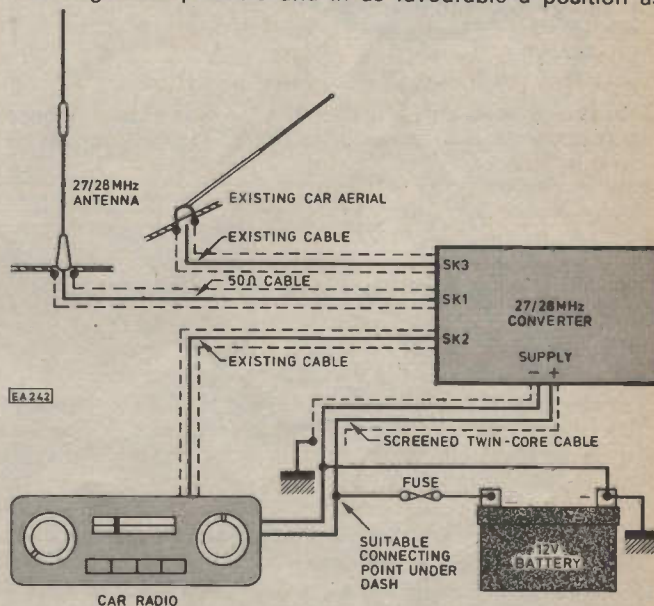


Fig. 7. Interconnection diagram for the Converter. If constructors wish to use only their existing car aerial then SK1 and SK3 should be linked together



## COMPONENTS . . .

### Resistors

R1, R7	1k (2 off)
R2, R3, R5, R11	47k (4 off)
R4, R6, R12, R13	470 (4 off)
R8	100k
R9	220k
R10	2k2
R14, R15	1k $\frac{1}{2}$ W 5% (2 off)

### Potentiometers

VR1	25k lin
-----	---------

### Capacitors

C1, C6, C7, C9, C12, C15, C16, C19, C21	4n7 (9 off)
C2, C5	22p (2 off)
C3, C4	33p (2 off)
C8, C14, C18	1n5 (3 off)
C10	4p7
C11	100n polyester
C13	100p
C17	5p6
C20	10 $\mu$ tant

All capacitors should be ceramic plate or disc except where otherwise stated.

### Semiconductors

D1, D2	1N4148 (2 off)
--------	----------------


D3	BZY 88 C5V6
D4	BZY 88 C9V1
D5	1N4001
D6	Red l.e.d.
D7	Yellow l.e.d.
TR1, TR2	TIS 88A (2 off)
TR3	40673
TR4	BC548
TR5	2N3819
TR6	2N3053

### Miscellaneous

S1	D.p.d.t. miniature toggle switch
SK1	"UHF"/SO239 co-ax socket
SK2	Standard Belling Lee co-ax socket
SK3	Standard Belling Lee co-ax socket
L6	10 $\mu$ H r.f. choke
Ferrite bead	
Crystal: 26MHz overtone type; HC6/U, HC33/U, HC18/U or HC25/U (see text and crystal frequency chart)	
Diecast or plastic case	
150 x 80 x 50mm (see text)	
Knob. Four stand-off pillars, Grommet, p.c.b.	
4 coil formers (type 722/1) fitted with ferrite dust cores, bases and screening cans	
26 and 30 s.w.g. enamelled copper wire	
Heatsink T05 17°C/W or better	
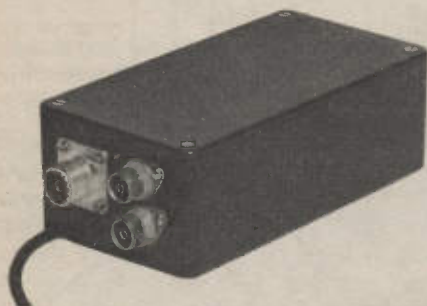
### Constructor's Note

The p.c.b. and all components for this project are available from **Howard Associates, 59 Outlands Avenue, Weybridge, Surrey KT13 9SU**. Inductors can, if required, be supplied ready wound. Please send s.a.e. for details.



possible. Roof mounting is ideal but the rear quarter or boot lid may be preferable. Alternatively a magnetic mount or

gutter clip accessory may be purchased. This allows the aerial to be removed when it is not in use.

Insert a milliammeter to measure the supply current. Check that this is in the range 25 to 35mA and that one of the two l.e.d.'s is alight. If this is not the case carefully re-check the wiring. Tune the medium wave receiver to approximately 1MHz (300 metres), set the function switch to "27/28MHz" and the r.f. gain control to "maximum" (fully clockwise). Using a proper trimming tool (not a metal screwdriver which may easily damage the ferrite cores) set the cores in all inductors so that they are in line with the tops of the cans. Tune the medium wave receiver around 1MHz until a signal is obtained, check that this is at 27/28MHz. Adjust L5 for maximum signal. If, however, no signals are heard turn the core of L5 five turns clockwise (into the former) and

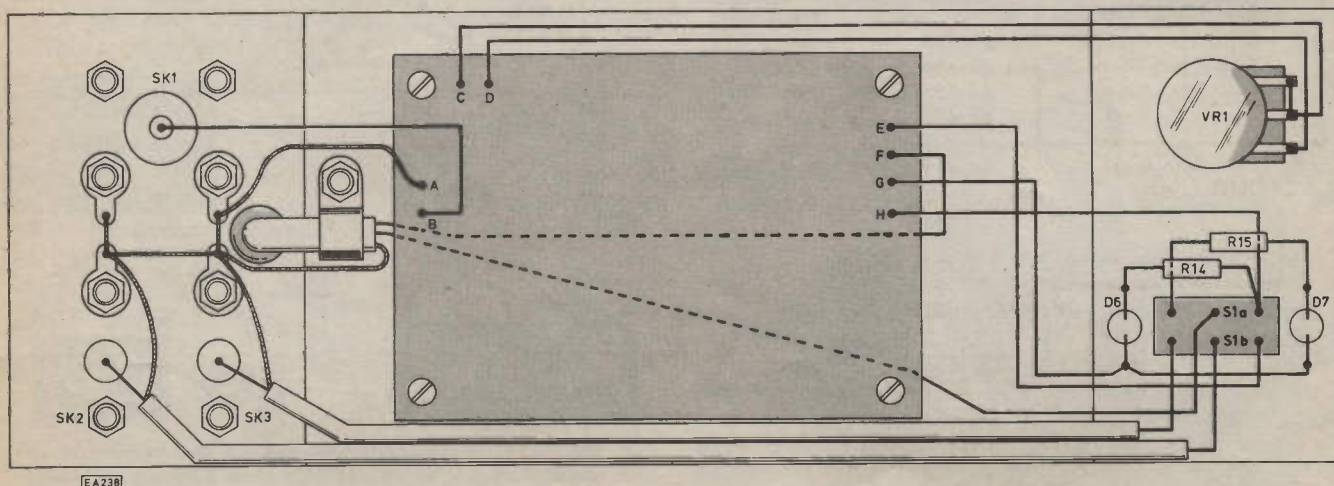


Fig. 8. Internal layout and wiring diagram

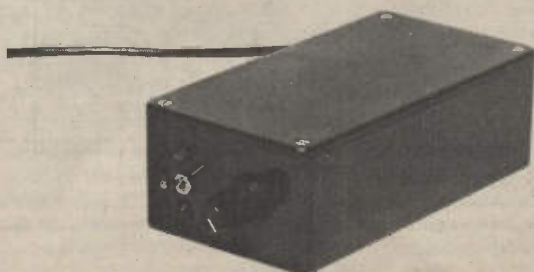


TABLE OF PRINCIPAL 'CB' CHANNEL FREQUENCIES		
'CB' channel number	Frequency (MHz)	Medium wave receiver (kHz)
1	26.965	965
2	26.975	975
3	26.985	985
4	27.005	1005
5	27.015	1015
6	27.025	1025
7	27.035	1035
8	27.055	1055
9	27.065	1065
10	27.075	1075
11	27.085	1085
12	27.105	1105
13	27.115	1115
14	27.125	1125
15	27.135	1135
16	27.155	1155
17	27.165	1165
18	27.175	1175
19	27.185	1185
20	27.205	1205
21	27.215	1215
22	27.225	1225
23	27.255	1255
24	27.235	1235
25	27.245	1245
26	27.265	1265
27	27.275	1275
28	27.285	1285
29	27.295	1295
30	27.305	1305
31	27.315	1315
32	27.325	1325
33	27.335	1335
34	27.345	1345
35	27.355	1355
36	27.365	1365
37	27.375	1375
38	27.385	1385
39	27.395	1395
40	27.405	1405

(Note: Medium wave receiver frequencies are quoted for a 26.0MHz crystal).

TABLE OF MODEL CONTROL FREQUENCIES			
Channel number	Colour code	Frequency (MHz)	Medium wave (kHz)
1	Brown	26.995	995
2	Red	27.045	1045
3	Orange	27.095	1095
4	Yellow	27.145	1145
5	Green	27.195	1195
6	Blue	27.245	1245

(Note: Medium wave receiver frequencies are quoted for a 26.0MHz crystal).



VOLTAGE TABLE		
TR1	source	1.0
	gate	0
	drain	5.4
TR2	source	5.4
	gate	4.0
	drain	7.9
TR3	source	0.7
	gate 1	0
	gate 2	0
TR4	drain	7.0
	emitter	4.8
	base	5.4
TR5	collector	8.4
	source	0
	gate	0
TR6	drain	5.4
	emitter	8.4
	base	9.1
TR6	collector	11.3

The above voltages were measured using a d.c. voltmeter having an input resistance of 10MΩ. The incoming supply voltage was 12V.

CRYSTAL FREQUENCY TABLE		
Tuning Range (MHz)	Crystal Frequency (MHz)	Notes
26.0-27.0	25.4	Preferred crystal for 'CB'
26.5-27.5	25.9	
26.6-27.6	26.0	
27.0-28.0	26.4	
27.5-28.5	26.9	
27.6-28.6	27.0	Preferred crystals for 10m amateur band
28.0-29.0	27.4	
28.5-29.5	27.9	
28.6-29.6	28.0	
29.0-30.0	28.4	
29.5-30.5	28.9	

again tune the receiver to locate a signal. Once a signal has been obtained adjust the inductors in the following sequence: L3, L4, L1/L2 for maximum. Repeat this procedure several times (there may be some slight interaction between L3 and L4) peaking, if possible, on progressively weaker signals. Signals with heavy fading present should not, of course, be used during the alignment process. The procedure can be considerably simplified if the receiver has a signal strength meter (a somewhat unusual feature in a car radio!) alternatively the alignment can be carried out in the "base station" with the aid of such a receiver and then the converter can be fitted in the vehicle. A slight re-adjustment to L1/L2 will normally be necessary in order to cope with a change of aerial. Where test equipment, such as a calibrated r.f. signal generator, is available the alignment is extremely simple. An attenuated locally generated 27/28MHz signal being substituted for the "off-air" signal provided by the aerial. In this case it is recommended that the tuning of L3 and L4 be staggered to peak at 27.3MHz and 26.9MHz respectively whilst L1/L2 is adjusted for maximum at 27.1MHz (or equivalent frequencies for a 10 metre amateur band version). ★

#### IMPORTANT NOTE

The Wireless Telegraphy Act only permits the reception of authorised transmissions. In the UK, 'CB' transmissions on 27MHz are, as has been stated before, unauthorised.

See Readout page 42.



# Semiconductor UPDATE...

FEATURING

SG1547 TDC1023J INS8073

R.W. Coles

## POWER MONITOR

Building the power supplies for a project has never been easier, and to some of us, this is the cause of great sadness. There used to be a great deal of satisfaction to be gained from the design of a neat and capable power unit, and it was one of the few areas in electronics where the results of one's design calculations could be readily checked out with little more than a multimeter. Voltage regulators, with their OC29 series pass transistors, Zener diodes, and long-tailed pair amplifier stages were a source of delight (when they worked!) and the addition of ingenious current limiting circuits and overvoltage protection has occupied many a happy hour. Alas, those days are gone, and in today's project a single TO3 can often contain all that is necessary to provide a frustratingly well regulated and protected power supply at a price which makes the do-it-yourself approach completely obsolete.

I came to terms with the "no-thought" power supply design like everyone else, but I have retained an interest in power supplies in general, and because of this I was attracted to a new device from Silicon General, the SG 1547 Power Supervisor. Add one of these to your multi-rail power supply and you can stop worrying about component failures and other disasters inflicting damage on the rest of the system, because the SG 1547 contains all the necessary circuitry to check up to three output voltages and the mains input for correct operation.

Inside the new device there are under and over voltage comparator circuits which compare the outputs from the associated supply with a fixed reference level generated on the chip. If any of the supply rails go over or under their tolerance limit the SG. 1547 produces an output to warn of the fact, and will provide automatic correction if required. Supply tolerance can be adjusted between plus and minus 0% and plus and minus 25% by means of a single external resistor, and the voltages monitored can include one negative rail, thanks to an inverting stage provided on the chip.

A "line-sense" input allows the monitoring of the a.c. mains feeding the power supply, and the SG 1547 provides a TTL level clock at the mains frequency as well as a "mains-failure" indication after a delay set by an external capacitor. Delays can also be incorporated on the under and over voltage outputs by means of capacitors

attached to the appropriate package pins, and this is particularly relevant on the over voltage output which is latched and would normally be used to activate a thyristor "crowbar" protection circuit. A particularly novel feature of the chip design is the use of "analogue—OR" gating to save on voltage comparators. The two OR gates, pass, respectively, the most positive and the least positive of the input rails to, respectively, the over voltage and the under voltage comparator circuits, making only two comparators necessary rather than six.

The SG 1547 is housed in a sixteen pin d.i.p. and can be used with a wide range of d.c. supply inputs. Each comparator output is capable of sinking 50 milliamps to drive l.e.d.s. or can fan out to five standard TTL loads.

## SEE YOU LATER CORRELATOR

Correlation is a technique for measuring the similarity between two signals, the measure of similarity being expressed as a "correlation coefficient". The more closely a signal resembles another signal with which it is being compared, the higher the correlation coefficient becomes, and this is a very useful property which can be exploited in the processing of digital information, particularly when searching for a desired signal in the presence of noise.

One simple application is the measurement of the distance between a deep space probe, such as Voyager, and planet Earth. A long binary pattern in the form of a "Pseudo Random Binary Sequence" is generated by shift register feedback and transmitted in serial form to the space-craft which receives it and sends it back to Earth. When it is received back at the sending point it will invariably be corrupted by noise, but this is overcome by correlating the received signal with a delayed version of the transmitted sequence. The delay is adjusted until a peak in the correlation coefficient is obtained and the range of the spacecraft can then be directly calculated from the delay setting, despite the presence of signal corruption. The trick here is that when the two signals are shifted by even one bit position, the correlation is negligible, but when they are in step the correlation is good, even though many bits have been corrupted by noise. The same principle can be exploited to send digital data to and from the spacecraft, and can be used in other fields such as medical research and pattern recognition.

Now you may be saying "So What?" and that would have been a perfectly respectable response until today, because the techniques of digital correlation required such expensive bits of hardware that any hobby interest was quite out of the question. From now on, however, digital correlation is an idea whose time has come, and soon no self respecting robot will be without a correlator in its optical system, thanks to the TDC 1023J from TRW LSI Products.

The new chip is a complete 64 bit digital correlator in a 24 pin package, and it consists of four 64 bit serial shift registers, a 64 bit digital summer and a seven bit threshold comparator and register. In operation the serial signal is shifted into the data register at a rate of up to 40MHz and then compared with the data in the reference latches. The two other 64 bit registers are the reference register which accepts new reference words entered in serial before transfer to the reference latches, and the mask register which allows any of the 64 bits to be excluded from the correlation process. The result of a correlation is a seven bit "correlation coefficient" which can be read in parallel form for computer processing. A threshold flag output is also provided to show whether the correlation coefficient exceeds the threshold value loaded into the threshold register.

The TDC 1023J is still a bit expensive for the average domestic robot, but this is only the beginning, correlation is a technique which cannot be ignored!

## BASIC MICRO

It had to happen one day, and now it has. New from National Semiconductor comes a microprocessor which can be programmed directly in the BASIC language.

The new chip, coded INS8073, and a relative of the famous SC/MP microprocessor, contains a 2.5K Tiny Basic interpreter with useful features such as branch ON interrupt and LINK to assembly language routines, in addition to the more traditional Basic statements such as IF/THEN DO/UNTIL and FOR/NEXT.

The processor is housed in a 40 pin package, runs from a single 5 Volt supply and has an on board 64 byte RAM array in addition to the usual SC/MP registers. On power up, the INS8073 searches for the external RAM location and size, and will automatically execute any valid BASIC program it finds there.



# SPECIAL OFFER!

## TELEQUIPMENT S61 OSCILLOSCOPE

# £114

**PLUS  
V.A.T.  
AND  
POSTAGE**

**Total price including £10 packing and dispatch, and VAT £142.60**

ONE of the most useful items of test equipment for the hobbyist is an Oscilloscope, so when we saw the chance of PE Special Offer on a lightweight scope from this renowned manufacturer we jumped at it.

PE has arranged this offer exclusively for readers, we believe it represents excellent value for money. Since there is only a limited supply of available units orders will be processed on a first come, first served basis, if we run out your money will be refunded.

### TELEQUIPMENT S61 SINGLE TRACE 5MHz OSCILLOSCOPE

Large 5 inch c.r.t., fully calibrated to manufacturer's specification, covered by the Carston 90 day guarantee which covers both parts and labour. Supplied with full handbook giving all details including circuit diagrams and p.c.b. layouts.

#### VERTICAL SYSTEM

**Bandwidth** DC-5MHz (-3dB) approx.

**Risetime** 70ns (approx.)

**Sensitivity** 5mV/div. to 20 V/div. in 12 positions.

**Input Coupling** Switched a.c. or d.c. or ground reference.

**Input Impedance** 1M $\Omega$ /35pF.

**Operating Modes** Single Channel Y/t or external X.

#### HORIZONTAL SYSTEM

**Sweep Speeds** 1 $\mu$ s/div. to 500 ms/div. in 18 ranges. Variable control provides overlap between ranges. Accuracy  $\pm$ 5%.

#### TRIGGER

**Trigger Sources** Internal, external, line.

**Trigger Level** Level control with integral  $\pm$  operation. Bright line auto in absence of a signal.



**Offer limited to UK mainland addresses only.**  
To: Carston Electronics Ltd., Shirley House, 27 Camden Rd., London NW1 9NR. Tel. 01-267 5311/2

Please complete both parts of the coupon in BLOCK CAPITALS

Please send me .....Telequipment S61 at £142.60 each

I enclose P.O./Cheque No. .... Value .....

Make cheques payable to Carston Electronics Ltd.

Please charge my Barclaycard/Access account

No. ....

Signature .....

Name .....

Address .....

.....

.....

.....

.....

.....

Name .....

Address .....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

Please allow 21 days for delivery  
**OFFER CLOSING FRIDAY 27th MARCH 1981**

From: Carston Electronics Ltd., Shirley House, 27 Camden Rd., London NW1 9NR. Tel. 01-267 5311/2.

**Please note:** Although Carston Electronics specialize in supplying second user equipment the Telequipment S61s are brand new and supplied in the manufacturer's packing—probes are not provided, but are available as an extra from Carston.





# PERIOD POWER TESTER

**CHRIS LARE**

## Variable interval switching for surge testing amplifiers etc.

**T**HERE is little need for stringent tests to be performed on electronic equipment designed or built for home use, since any faults that might occur can be quickly rectified by the person concerned. However, if the equipment is intended for use where the designer or builder will not always be available or where a failure can be very embarrassing (e.g. equipment used for public demonstrations or performances) exhaustive tests are required during the commissioning of the equipment.

The tests should be designed to stress every component of the equipment, thus causing premature failure of any dubious devices. Naturally, the tests must be carefully chosen so that no good components fail. Such tests usually include the "soak" where the equipment is left on for many hours at full power, shake and drop tests, overload tests and any others particular to that type of equipment.

These tests all overlook the fact that most equipment fails when it is switched on or off, due to the sudden surge currents and spikes which occur during the stabilisation period. The only way to induce these effects is to keep switching the equipment on and off at short intervals. The design described here is for a simple unit to do just that, with presettable on and off periods.

### DESIGN OBJECTIVES

The tester was designed with PA amplifiers and lighting units particularly in mind. A 250 watt amplifier has a massive switch on surge current initially, even though the standing current is very low. Because of this surge it is not really appropriate to use an electronic switch such as a triac,

since even a 25 amp version will stand a real chance of failing. Accordingly this design employs a 10 amp relay with a pair of contacts in parallel to switch the load.

If this relay was a low voltage version, many milliamps would be required to drive it, thus requiring a conventional power supply and transformer. Instead this design uses a triac to switch a mains relay, and by firing the triac with pulses the continuous current drawn by the circuit is about 3 milliamps well within the bounds of a simple dropper resistor supply.

### THE CIRCUIT

The circuit is centred around two 555 timers, and in the interests of low power consumption one of the fairly recently introduced CMOS 556 timers is used. In Fig. 1 the first timer is connected in astable mode, with variable on and off times, both selected from front panel potentiometers. The diodes in series with the timing resistors determine which resistors are used for charge and discharge, so the functions are completely independent. The second 555 is also connected as a astable, but with a very narrow pulse output of 1.6 kHz. This pulse train only appears when the output of the first 555 is high, by virtue of the connection to the reset line of the second 555. The pulses are then fed directly to the gate of the triac via a 100nF capacitor which serves as a d.c. current block when the pulses are not present.

The pulse train is required because the holding current of the triac is very close to that consumed by the relay, and thus there is no guarantee that the triac will remain fired. To drive the triac continuously would be in order, but would require very much more power. The triac is further helped by the 18 kilohm resistor which increases the current.

The power supply follows the usual pattern for mains dropper derived supplies. The excess voltage is dropped by the 18 kilohm resistor, and rectified by the series diode. The resultant voltage is smoothed by C1, and clamped at 15 volts by the Zener diode. Note that the negative d.c. supply is 15 volts below mains neutral, this is to allow the triac to be directly fired.

Two neons were connected across the third set of relay contacts to provide a form of status indication. A 20nF ceramic capacitor is required across the switching contacts to help prevent arcing when inductive loads (as are most loads) are being tested.