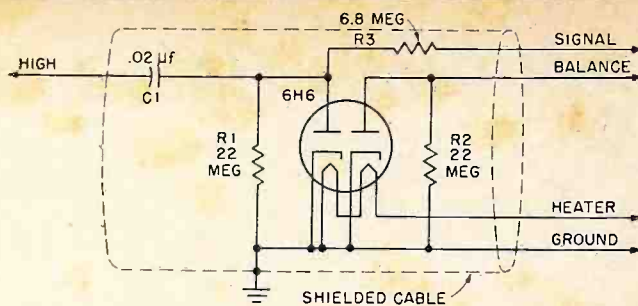


JANUARY, 1951

Fig. 1. The schematic of a typical probe used for the measurement of r-f voltages is shown here. One section of the 6H6 balances the contact potential of the other section.



RADIO FREQUENCY PROBES USED WITH VACUUM-TUBE VOLTMETERS

By JOHN F. RIDER

A probe is a device or circuit added to the input of an electronic voltmeter to facilitate the measurement of radio, intermediate, or video frequencies, and/or high voltages. There are various types of probes, each designed for a specific purpose. In general, probes are designed either to increase the input resistance or to decrease the input capacitance of the voltmeter.

Since a probe permits the use of very short connecting leads, its widest application is with high-frequency voltmeters. The development and improvement of such probes has been going on for over twenty years. Since early vacuum-tube voltmeters were single tube affairs in which rectification and d-c amplification or meter coupling were accomplished in a single tube, and since early tubes were large and awkward, early probes were more or less cumbersome affairs. The gradual development in the art has evolved smaller and smaller probes mounted on more and more flexible cables.

At frequencies above a few hundred kilocycles, long connecting leads to voltmeters or other measuring apparatus introduce errors and increase the circuit loading. At frequencies of the order of 100 megacycles, it is desirable to do away with connecting leads entirely, even to the extent of soldering the probe or rectifier terminals directly to the circuits under test.

The probe schematic shown in Fig. 1 is typical of most r-f probes used today. An equivalent circuit showing the four major components of the input impedance is shown in Fig. 2. These four components are R_E , which is equal to the parallel combination of

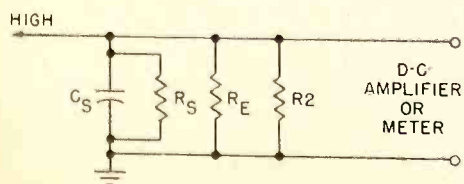


Fig. 2. Equivalent circuit for the r-f probe shown in Fig. 1.

R_1 and R_3 in Fig. 1 (R_3 goes to ground through a coupling capacitor in the voltmeter proper), the diode shunt resistor R_2 , the equivalent shunt capacitance C_s , and the equivalent shunt resistance R_s .

The effective input capacitance C_s consists of all the shunting capacitances of the probe. This includes the capacitance of the "high" terminal, the input coupling capacitor, the diode plate capacitance, as well as the capacitance of the diode socket (if one is used), the connecting leads, the high side of the shunt and filter resistors, and all other parts. The equivalent shunt resistance R_s represents the shunt resistance component of the capacitor dielectric. At audio and low radio frequencies, R_s is usually large compared to R_E and R_2 , so that the input impedance essentially consists of C_s shunted by R_E and R_2 . With the values given in Fig. 1 for R_1 and R_3 , we find that R_E is equal to:

$$R_E = \frac{6.8 \times 22}{6.8 + 22} = 5.2 \text{ megohms.}$$

The total input resistance, R_T , at low frequencies is, therefore, equal to:

$$R_T = \frac{R_E \times R_2}{R_E + R_2} = \frac{5.2 \times 22}{5.2 + 22} = 4.2 \text{ megohms.}$$

The capacitive shunt resistance decreases linearly in value as the frequency increases. In the typical probe, this resistance becomes equal in value to the combination of R_E and R_2 at about 1 megacycle. At higher frequencies, R_s rapidly becomes the predominant factor, so that at frequencies above 1 megacycle, the input impedance of the probe is almost entirely that of C_s shunted by the R_s .

A probe having an input capacitance of $5 \mu\text{f}$ will have a capacitive reactance of 3,185 ohms at 10 megacycles. (The reactance of

a capacitor is equal to $1/2\pi fC$, where f is the frequency in cycles, and C is the capacitance in farads.) The shunt resistance component of this capacitor will be about 1 megohm at this frequency (Q times the reactance value). As the frequency increases, the capacitive reactance decreases and the shunt resistance assumes more and more importance.

When making voltage measurements across a tuned circuit, an estimate of the error caused by the voltmeter probe may be obtained by comparing the equivalent resistance of the probe to the tuned impedance of the circuit. The impedance of a parallel tuned circuit at resonance, Z_r , is purely resistive and is equal to:

$$Z_r = Q_r^2 R$$

where Q_r is the Q value of the circuit at resonance, and R is the equivalent series resistance of the circuit.

Since by definition, the Q of a series circuit is the ratio of its reactance to its resistance, we have:

$$Q_r = \frac{W_r L}{R}$$

or

$$R = \frac{W_r L}{Q_r}$$

where W_r is equal to 2π times the resonant frequency.

(Continued on page 14)

Editor's Note: This article is an abridgement of the section on r-f probes appearing in chapter 9, entitled "Probes for D.C. and R.F.," from the new and complete text **VACUUM-TUBE VOLTMETERS**, a book to be published soon by John F. Rider Publisher, Inc. This book is a revision of the former book **VACUUM-TUBE VOLTMETERS** by John F. Rider.

Television Changes

Wilcox-Gay G306, G402, G403, G404, G426, G427, G624, G914

Wilcox-Gay Model G306 is similar to Majestic Model 12T6. Model G402 is similar to Majestic 12C4. Model G403 is similar to Majestic 14T2. Model G404 is similar to Majestic 14C4. Model G426 is similar to Majestic 16C4, and Model G427 is similar to Majestic 16C6. Except for cabinet designs or picture tube size, Majestic Models 12T6 and 14T2 are the same as Majestic Model 12T2. Majestic Model 14C4 is the same as Majestic Model 12C4, and Majestic Model 16C6 is the same as 16C4.

Wilcox-Gay Model G624 is similar to Majestic Model 1674, and Model G914 is similar to Majestic Model 1974.

Mars Dartmouth, Hampton, Oriental, Versailles, Ch. K-2

The chassis layout for the K-2 chassis is shown in the accompanying figure. 6CB6 tubes can be substituted for the 6AG5 tubes shown marked with asterisks, and a 6W4GT can be substituted for the 5V4G reaction scanning tube. The rear chassis controls are shown at the bottom of the illustration.


Crosley 10-414MU, 10-416MU, 10-416MIU, 10-429MU

On later sets resistor R151, 150,000 ohm, 10%, 1/2 w (part No. 39374-51) was changed to 220,000 ohm, 10%, 1/2 w (part No. 39374-53). This change was made to increase the horizontal hold control range.

Associated Merchants 12T1, 12T2, 12T3, 120C1, 120C2, 120C3, 160C1, 160C2, 160C3

The service data for these models are the same as those for Bendix Models 2025, 3033, and 6002 except for the changes in the parts list that are shown below. For all service data and change notices see Bendix 2025, 3033, and 6002.

Stock No.	Description
FP0P07	Frame, paper, decorative (12 1/2" table and console models)
FP0P08	Frame, paper, 12 1/2" picture tube
FW0P05	Frame, wood, 16" picture tube
HP0M08	Plate, metal, decorative (12 1/2" and 16" console models)
KC0B26	Knob, control, contrast
KC0B27	Knob, control, Off-On-Volume
ZW1T06	Cabinet, table model, mahogany
ZE1V08	Cabinet, console model, mahogany (12 1/2")
ZW1V09	Cabinet, console model, mahogany (16")

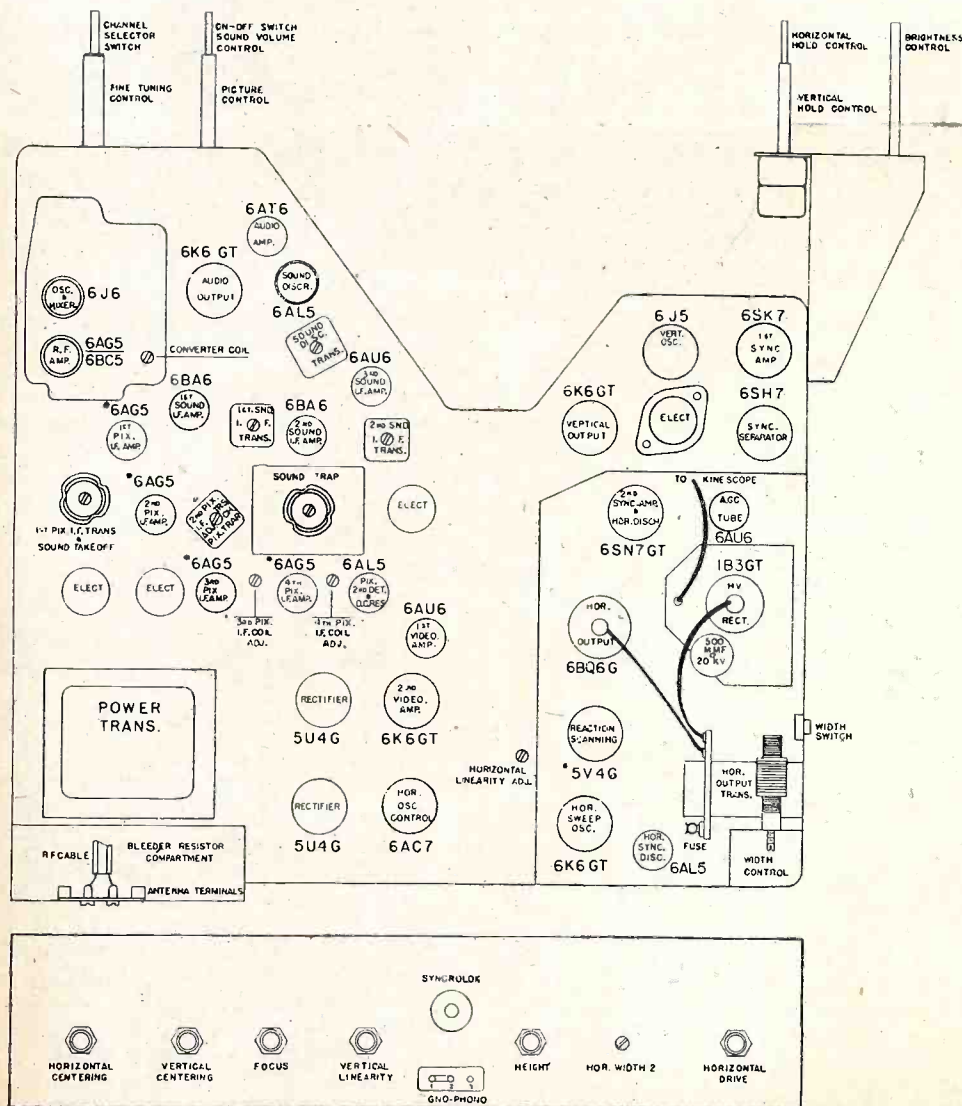

Chassis layout and rear chassis controls for Mars K-2.

Majestic 14CT4, 16CT5, 19C6, 19C7, 1671, 1672, 1673, 1674, 1675, 1900, 1974, 1975, 97 & 98 Series

Model 14CT4 is a consolette with a mahogany finish and employs a 14" rectangular picture tube. Model 1671 has a table cabinet with a mahogany finish and employs a 16" rectangular tube. Models 16CT4 and 16CT5 are consolettes using 16" round tubes. Model 16CT4 has a mahogany finish, while Model 16CT5 has a bleached finish. Model 1900 is also a consolette with a mahogany finish, although it employs a 19" round tube. A total of 20 tubes including the picture tube is used in these receivers.

The service data for these models in the 97 and 98 Series are the same as the data for the 94 and 97 Series except for the differences and additions mentioned in the following paragraphs.

Under the section titled "Picture Tube Installation in 16" Receivers," add:

For receiver Models 1672 or 1673, remove the two screws which hold the front mask assembly. These pass through the two corner blocks on the inside of the cabinet at the top. When these screws are removed, the front panel may be lifted out. For receiver Models 1671, 1674, or 1675, remove the four decorative screws which hold the front panel and mask assembly. These pass through the four corners of the picture frame. Carefully lift out the front panel and mask assembly. For Model 1671, loosen the two screws which fasten the metal picture-tube retaining band sufficiently so that the picture tube may be slipped through the opening. The high-voltage connector should be located on the right side of the chassis, as viewed from the front. Secure the metal band over the top of the tube by tightening the two screws alternately and evenly, so that the rectangular picture tube is not forced to rotate or twist in its mounting.

The picture tube installation in 19" receivers is as follows:

The bulblike glass separation between the neck of the picture tube and its metal cone is treated with an anti-corona coating to reduce high-voltage leakage under humid atmospheric conditions. Avoid touching this treated area since perspiration may reduce its effectiveness. If handled accidentally, wash with water or mild soap and water. Remove all traces of soap. Use no chemical solvents or abrasives for cleaning.

1. Remove the slotted head P.K. screws retaining the back and release with the interlocked line cord.



2. Remove the bag containing the beam bender, the hardware for deflection and focus coil assembly, and the front plug buttons, if used.

3. Remove the deflection and focus coil assembly which is fastened to a shelf for shipping purposes. Remove retaining wires that are wrapped around focus coil adjustment screws.

4. Carefully slide the deflection yoke and focus coil assembly over the neck of the picture tube, so that the deflection yoke adjustment thumb screw faces the top of the cabinet.

5. Assemble the deflection yoke and focus coil assembly to the support bracket using the

(Continued on page 6)

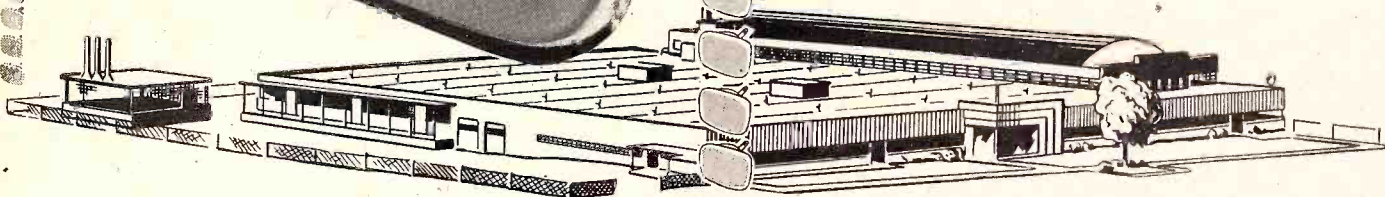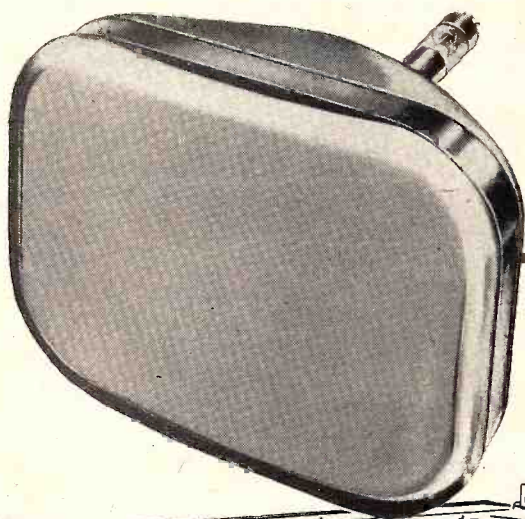

uniform

Yes, UNIFORM! There's no such thing as a "better tube" or a "poorer tube" when you insist on Du Mont Teletrons. Advanced engineering, precise mechanization second to none, and the most rigid quality control account for uniformly dependable performance that has made the Du Mont label symbolic of the finest in TV tubes. Best of all, with a productive capacity in excess of one million BIG picture tubes a year, the giant Du Mont Allwood plant meets quantity as well as quality requirements. Literature on request.

DU MONT

*Teletrons**

*TRADE-MARK

FIRST WITH THE FINEST IN TV
ALLEN B. DU MONT LABORATORIES, INC.
Cathode-ray Tube Division, Clifton, N. J.

Please mention Successful Servicing when answering advertising.

Because
**They're Free of
 Contamination...**



MALLORY CAPACITORS


Give Long, Continuous Service!

One reason why Mallory Capacitors deliver full rated capacity throughout their long life is the unusual care taken in production to prevent contamination, which is the source of corrosion and shortens the life of capacitors.

Even at high temperatures, Mallory Capacitors operate perfectly over extremely long periods of time. Tests consistently show dependable performance for more than 2000 hours at temperatures up to 185°F (85°C). Special design and meticulous production methods make such records possible.

Mallory Capacitors have set new long-life standards for the industry, yet cost no more. You will find it pays to rely on the complete Mallory Capacitor line . . . electrolytic, plastic tubular, paper, mica and ceramic.

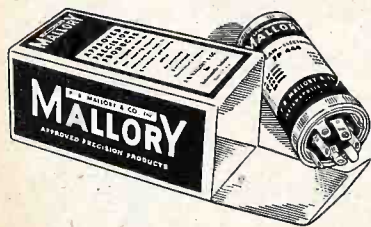See your Distributor for Mallory Precision Quality Parts at Regular Prices.



MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
 • RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

JANUARY, 1951

No. 3

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
E. H. BEAUMONT, Associate Editor

Copyright 1950 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher

WOrth 4-8340
WOrth 4-8341



CURTAIN TIME

Five Billion Dollar Electronic Equipment Procurement

Defense orders to be placed for electronic equipment during 1951 will approximate 5 billion dollars. If this is the case, it is inevitable that some time during 1951 there will occur complete stoppage in the manufacture of electronic equipment for home use. It is reported that the first quarter of 1951 will still see a reasonable output of television and radio receivers because many manufacturers have the necessary components on hand, but it is our feeling that the second quarter will see remaining inventories directed to the production of defense equipment.

In view of the above, the servicing history of World War II will repeat itself—servicing will increase tremendously. Whether or not the public demand will be satisfied is still another question. From the way things look now, both manpower and components are destined to be in short supply. It is said that the curtailment of set production may make more parts available for the servicing industry. We hope so, but we aren't banking on it. Common sense dictates that it will be determined by how rapidly the defense pro-

gram is put into effect and by the size of the orders sent to the manufacturers.

Inasmuch as home electronic equipment (radio and television receivers) must be maintained for public morale and for direct communication so that instantaneous contact between the government and the people of the nation is possible, the depletion of servicing personnel by the demands of the Armed Forces and industry deserves serious consideration. Every effort will have to be made to replenish the ranks of service technicians as they dwindle. Commercial schools, high schools, vocational schools, and even colleges, may be called upon to train personnel for duties in this activity as well as for industry and the Armed Forces. The Boards of Education in different parts of the country might well pay greater heed to the needs of the vocational schools. Perhaps electronics may soon become a subject in high schools. In view of the needs, it could well replace the conventional shop course. It might be well if the different educational boards in the nation inaugurated night classes to teach radio and television servicing. It would not create problems for the commercial schools because it is inevitable that the student strength in

these institutions will increase in order to satisfy the needs of the various branches of the Armed Forces.

It is not beyond the realm of possibility that youngsters and oldsters who may gather a limited amount of electronic background from attendance at municipal schools may prove useful in local service shops, where they can work under the supervision of more competent personnel.

The curtailment of new set production will make the present-day TV set installer a prospect for servicing education. The manner of operation of the contract houses will no doubt be changed—they'll have to drop the contract idea completely and do cash and carry servicing. This will demand an increase in servicing personnel as compared to installation personnel. It may mean that each contractor will have to set up his own training program or maybe enroll his men at his own expense in some home study course. We might comment that this is being done right now by a very big service contract organization with advantage to the public, the men, and the company.




Rider's TV 6 AND TV 7

The impending curtailment of TV receiver production some time in 1951, as well as the very grave paper shortage, pose a problem for us in connection with the forthcoming Rider TV Manuals Volumes 6 and 7. Rider TV Manual Volume 6 will contain 2,300 pages (8½" x 11") of TV data. Accordingly, it is our plan to release Rider TV Manual 6 in March 1951 and TV Manual 7 soon thereafter. Each will be a full-size manual, if not an over-sized manual. In that way we can get into the hands of the servicing industry all of the information which is vital to its operation.

Things have reached such a pass, relative to paper and printing, that stocks must be accumulated in order to accomplish a printing. These two volumes will require approximately 200,000 pounds of paper. We have been successful in exacting promises for this amount in time for the printings. If you are in the TV servicing business, you will need these volumes. Contact your source of

(Continued on page 15)

RESOLVED IN 1951—

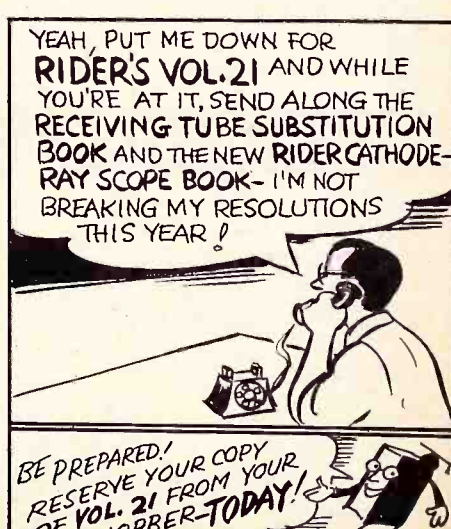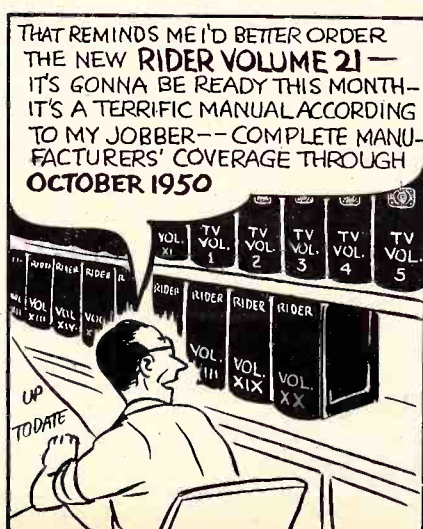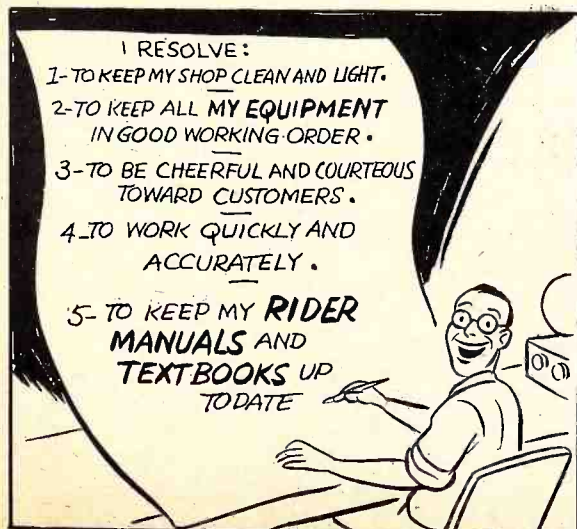


Beat the Tube Shortage!

This Sensational New RIDER Book Shows You HOW to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

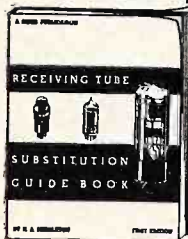For AM-FM-TV Receivers and Allied Equipment!



URGENT! Receiving tubes are very scarce... and will get scarcer. There is a wide scramble for every type of tube, and you can't always get what you need. What can you do when you can't find a tube replacement? How can you get a set working again? How can you substitute one tube for another?

HERE!

HERE Are The Answers To All Tube Problems!

- 2500 Radio And TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

Here the serviceman will find 2500 radio and TV tube types systematically listed in numerical sequence with accompanying wiring instructions for making the substitutions. There are views of original and substitute tube sockets, and clear explanations for whatever changes may be necessary. In this, one of the most important servicing books ever published, and certainly a most timely one right now, the serviceman will find the way to turn out jobs that would otherwise remain on the shelf because of lack of proper tubes.

EXTRA! EXTRA! In addition to tube information... this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, and Converting Farin Radio for Electrified Operation.

224 Pages in Heavy Durable Paper Cover. 8 1/2 x 11 inches. Only **\$2.40**

ORDER YOUR COPY TODAY!
It will work for you every day!
It will help solve your tube problems every day! It will make money for you every day!

Rush This Coupon Today

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street, New York 13, N.Y.

Please send me.....copies of "RECEIVING TUBE SUBSTITUTION GUIDE BOOK" at \$2.40 per copy. I am enclosing check ☐ money-order ☐ in the amount of \$..... If, within 10 days, I am not satisfied—I will return the book(s) in good condition, for refund.

Name.....

Address.....

City.....Zone.....State.....

1-51

Majestic 97 and 98 Series

(Continued from page 2)

hardware provided. See Fig. 1 for proper hardware assembly and mounting procedure.

6. Remove the 6-32 grounding screw from the yoke frame (see Fig. 1 for location). Attach the ground lug on the brown wire coming from the chassis, and replace the screw.

7. Slide the beam bender over the neck of the picture tube.

8. Connect the picture tube socket to the tube base.

9. Connect the male octal plug from the deflection yoke and focus coil assembly to the female octal socket from the chassis.

The rear panel adjustments that are illustrated for Models 1672, 1673, 1674, 1675, 19C6, 19C7, 1974, and 1975 apply to the other models mentioned in this article. The location of the front panel controls are shown for Models 1974 and 1975 in Fig. 2, and for the rest of the models in Fig. 3.

The circuit description for these models is the same as that for the 94 Series, except that in the section titled "Vertical Deflection Circuit (Block H)," the generated sawtooth voltage is amplified by the 6K6 output tube (V20), rather than the "other half of the 6SN7 duo-triode (V14)."

The Alignment Procedure, Video I-F and Sound Alignment, and the R-F and Oscillator Alignment for the 97 and 98 Series is the same as that found for the 94 Series. The Voltage Chart for all models except 14CT4, 1674, and 1900, is the same as that shown on page 5-13. The voltage readings for Model 1900 are the same as those shown on page 5-13, except for the following changes: Picture tube (V1)—pin 2 is 2 v, pin 10 is 230 v. Audio output (V4, 6V6)—pin 1 is N.C., pins 5 and 6 are -6 v. Ratio detector driver (V6, 6AU6)—pin 1 is 4.5 v, pin 7 is 5 v. The voltages on pins 5 and 6 of the 1st, 2nd, and 3rd video i-f tubes (V7 6AU6, V8 6AG5, V9 6AG5) are 115 v. Video amplifier (V11, 6AC7)—pins 3 and 5 are 0.2 v, pin 4 is -2 v, pin 6 is 145 v, and pin 8 is 115 v. D-c restorer-clipper-separator-amplifier (V12, 12AU7)—pin 1 is 90 v, pins 2 and 6 are 24 v, and pin 3 is 25 v. Vertical sweep oscillator (V14, 6C4)—no voltage on pin 1, pin 5 is 100 v, and pin 6 is -25 v. Horizontal sweep output (V16, 6BQ6-GT)—pins 3 and 4 are 155 v, pins 5 and 6 are -26 v, and pin 8 is 7 v. High-voltage rectifier (V17, 1B3)—pins 2, 6, and 7 are 11.5 kv. Horizontal damper (V18, 6W4)—pins 2 and 4 are N.C., pin 3

is 370 v, pins 5 and 6 are 210 v, pin 7 is 6.3 vac, and pin 8 is 0 v. Power rectifier (V19, 5U4G)—pins 2 and 8 are 380 v, and pins 4 and 6 are 365 vac. Vertical output (V20, 6K6)—pin 1 is 0 v.

The voltage readings for Models 14CT4 and 1674 are the same as those on page 5-13 except for the following changes: Picture tube (V1)—pin 2 is 4.3 v, pin 10 is 245 v, and pin 11 is 17-v. Oscillator-converter (V3, 6J6)—pin 1 is -0.7 v, pin 2 is 0 v. Audio output (V4, 6V6)—pin 1 is -138 v, pin 3 is 195 v, pin 4 is 210 v, and pins 5 and 6


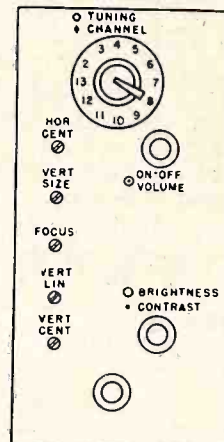


Fig. 2. Front panel layout for Models 1974 and 1975.

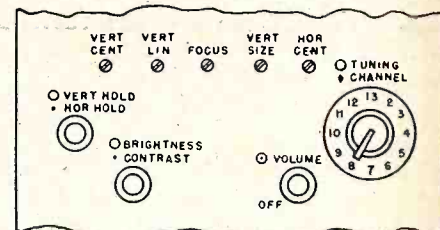are -9 v. Ratio detector-audio amplifier (V5, 6T8)—pin 6 is -0.5 v, pin 9 is 115 v. Ratio detector driver (V6, 6AU6)—pin 1 is 8 v, pin 2 is 8.5 v, pin 5 is 220 v, pin 6 is 105 v, and pin 7 is 9 v. Third video i.f. (V9, 6AG5/6BC5)—pin 7 is 1.2 v. D-c restorer-clipper-separator-amplifier (V12, 12AU7)—pins 2 and 6 are 160 v, pin 3 is 162 v. Horizontal



tal phase detector (V13, 6AL5)—pin 1 is 6 v, pin 2 is -6 v. Horizontal sweep oscillator (V15, 6SN7)—pin 5 is 100 v. Horizontal sweep output (V16, 6BQ6-GT)—pins 3 and 4 are 210 v, pin 5 is 48 v, no voltage on pin 6, and pin 8 is 72 v. High-voltage rectifier (V17, 1B3)—pins 2, 6, and 7 are 10.1 kv. (Continued on page 10)

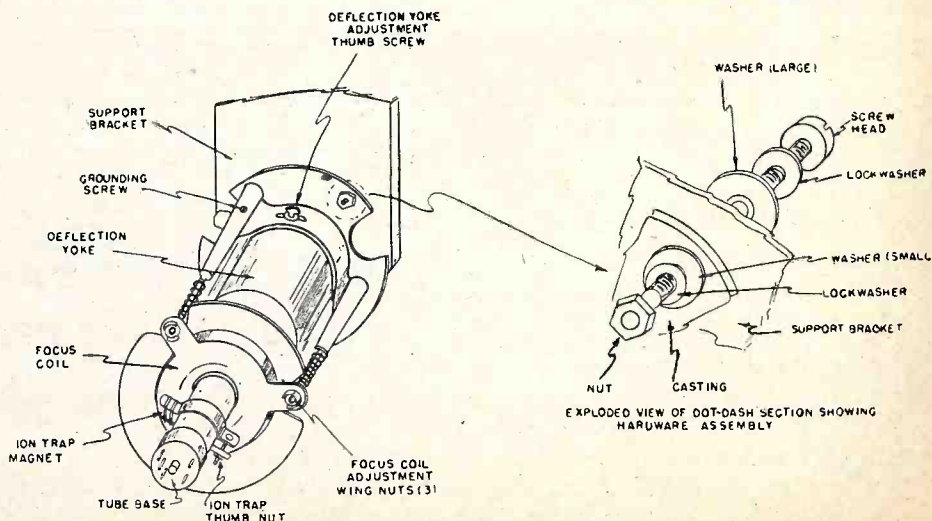


Fig. 1. Deflection yoke and focus coil assembly.


THE NEW PRECISION CR-30 CATHODE RAY TUBE TESTER

TESTS ALL TV PICTURE TUBES

(MAGNETIC AND ELECTROSTATIC)

'SCOPE TUBES AND INDUSTRIAL CR TYPES

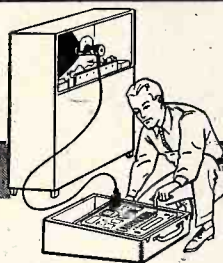for True Beam Current (Proportionate Picture Brightness)
Tests ALL CR Tube Elements—Not Just a Limited Few



IN FIELD OR SHOP
Tests CR Picture Tubes
Without Removal from
TV Set or Carton!

The new Precision CR-30 fills an obvious gap in the test equipment facilities employed by TV service and installation technicians.

Because of the absence of a reliable cathode ray tube tester, up to 50% of so-called "rejected tubes" are found to be fully serviceable and should rightfully never have been "pulled out."

Proven product of extended development, the CR-30 has been

specifically engineered to answer the question, "Is It the TV Set or is it the Picture Tube?"


The Precision CR-30, a complete and self-contained Electronic Instrument, incorporates a TRUE BEAM CURRENT Test Circuit. The CR-30 checks overall electron-gun performance for proportionate picture brightness as well as additional direct testing facilities for accelerating anodes and deflection plate elements.

The Precision CR-30 should not be confused with mere adapters connecting to ordinary receiving tube testers which were never designed to meet the very specialized needs of CR tube checking. Similarly, it is not to be confused with neon-lamp units or similar devices of limited technical merit and which do not check all CR tubes or all tube elements.

GENERAL AND TECHNICAL SPECIFICATIONS

- ★ Tests All Modern Cathode Ray Tubes:—Magnetic and Electrostatic, 'Scope Tubes and Industrial Types.
- ★ Tests All CR Tube Elements:—Not just a limited few.
- ★ Absolute Free-Point 14 Lever Element Selection System, independent of multiple base pin and floating element terminations, for Short-Check, Leakage Testing and Quality Tests. Affords maximum anti-obsolescence insurance.
- ★ True Beam Current Test Circuit checks all CR Tubes with Electron-gun in operation. It is the Electron Beam (and NOT total cathode emission) which traces the pictures or pattern on the face of the CR tube.

Total cathode emission can be very high and yet Beam Current (and picture brightness) unacceptably low. The CR-30 will reject such tubes because it is a true Beam Current tester. Conversely, total cathode emission can be low and yet Beam Current (and picture brightness) perfectly acceptable. The CR-30 will properly pass such tubes because it is a true Beam Current tester. The significance of the above rests in the fact that Beam Current (and picture brightness) is primarily associated with the condition of the center of the cathode surface and not the overall cathode area. (See illustration below)

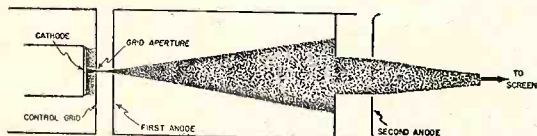

- ★ Voltage Regulated, Bridge Type VTVM provides the heart of the super-sensitive tube quality test circuit. Such high sensitivity is also required for positive check of very low current anodes and deflection plates.
- ★ Micro-Line Voltage Adjustment
Meter-monitored at filament supply.
- ★ Accuracy of test circuits closely maintained by use of factory adjusted internal calibrating controls; plastic insulated, telephone type cabled wiring; highest quality, conservatively rated components.
- ★ Built In, High Speed, Roller Tube Chart.
- ★ Test Circuits Transformer Isolated from Power Line.
- ★ 4½" Full Vision Meter with scale-plate especially designed for CR tube testing requirements.
- ★ Heavy Gauge Aluminum Panel etched and anodized.
- ★ PLUS many other "PRECISION" details and features.

SERIES CR-30—In hardwood, tapered portable case, with hinged removable cover. Extra-Wide Tool and Test Cable Compartment. Overall Dimensions 17¼ x 13¾ x 6¾". Complete with standard picture tube cable, universal CR Tube Test Cable and detailed Instruction Manual.

Shipping Weight:—22 lbs. Code: Daisy
NET PRICE:—\$99.75

See the new CR-30 on display at leading electronic equipment distributors. Place your orders now to assure earliest possible delivery.




PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York

Export Division: 458 Broadway, New York, U.S.A. Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

Please mention Successful Servicing when answering advertising.

**WITH
'SCOPES**

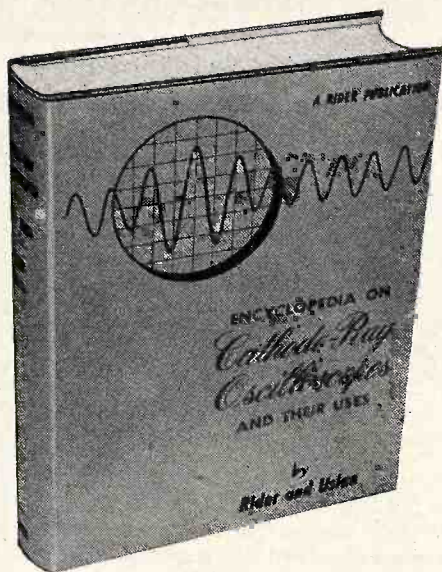

Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses

By JOHN F. RIDER and SEYMOUR D. USLAN

**Fully and clearly describes the oscilloscope
... its construction ... its capabilities ...**

... its applications in servicing, engineering, research ... with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described — with specifications and wiring diagrams.

Planning to buy a scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's *usefulness* and, naturally, its *value* to you!

We GUARANTEE that it will SAVE and EARN many, many times its cost for you!

992 Pages

3,000 Illustrations

22 Chapters

Easy to Read

Half a million words

8½" x 11" Size

Completely Indexed

Cloth-bound

Only \$9.00

BECOME

This **FIRST** and **ONLY** book of its kind tells you everything that you should know about an Oscilloscope!

WHAT it is what it can **DO** and **HOW** to use it properly!

HERE IS A TYPICAL CHAPTER BREAKDOWN

CHAPTER 10 — THE BASIC OSCILLOSCOPE AND ITS MODIFICATIONS.

THE BASIC OSCILLOSCOPE

Sections of the Basic Oscilloscope
The Cathode-Ray Tube
The Beam-Positioning System
The Vertical-Deflection Amplifier
The Horizontal-Deflection Amplifier
The Time-Base System
The Synchronizing System
The Intensity-Modulation System
The Power Supply
Panel Organization of the Controls
Nomenclature of the Controls
Horizontal-Amplifier Control Nomenclature

FUNCTIONAL ORGANIZATION OF THE BASIC OSCILLOSCOPE

Direct Connection to Deflection Plates
The Cathode-Ray Tube with Amplifiers
Vertical Deflection Only
Frequency Comparison
Horizontal Deflection Only

WAVEFORM PRESENTATION

Relationship Between Sweep and Signal Frequencies
Integral and Fractional Sweep-Signal Frequency Ratios
Keeping the Pattern Stationary (The Synchronizing Control)
Variables in Waveform Display
Vertical Amplitude Variations
Insufficient and Excessive Synchronization
Sweep Frequency Higher Than Signal Frequency
Distortion of Complex Wave Input
Sweep Frequency for Complex Waves
External Synchronization of Sawtooth Oscillator
60-cps or Line Synchronization of Sawtooth Oscillator
Distortion Due to Nonlinear Sweep
Summary of Waveform Display
Sine-Wave Time Base Presentation

FACTORS CONTROLLING APPLICATION OF THE BASIC OSCILLOSCOPE

Frequency as a Controlling Factor
Importance of Deflection-Plate System
Low-Frequency Response of Cathode-Ray Tube
Operation Features of Vertical Amplifiers
Required Amplifier Gain
Frequency Requirements of Vertical Amplifiers
Importance of Harmonics
Pulse Duration and Rise Time
Bandwidth in Television Oscilloscopes
Composition of a Sawtooth Wave
Frequency Bandwidth for Sawtooth Waves
Phase or Time Delay in Amplifiers
The Behavior of Vertical-Amplifier Attenuators

Frequency-Response Curves
Limits of Bandwidth
Basis of Wide-Band Response
Frequency-Compensation Methods
The Advantage of Wide-Bandwidth Amplifiers

CIRCUIT FEATURES OF VERTICAL AMPLIFIERS

A-C and D-C Amplifiers
The Direct-Coupled (D-C) Amplifier
Practical D-C Amplifiers
D-C Coupling and Square Wave Amplification
Phase Inverters and Push-Pull Systems
Advantages of Push-Pull Amplification
Phase Relationship Between Input and Output Signals
Cathode-Follower Input System Circuits
Input Probes and Attenuating Cables

CIRCUIT FEATURES OF THE HORIZONTAL AMPLIFIER

Horizontal Amplifier Bandwidth
Horizontal Amplifier Input Impedance
X vs. Y Amplifier Circuits
The Horizontal Gain Control and Sweep Amplitude

THE TIME-BASE GENERATOR (REPETITIVE SWEEP)

Visibility of the Retrace
Blanking of the Retrace
Markers by Intensity Modulation
Triggered Sweeps
The Delay Circuit
Sweep Speed
Sweep Calibrator
Vertical Amplitude Calibrators

POWER-SUPPLY CIRCUITS AND OTHER CONSIDERATIONS

Power-Supply Frequency
Power-Supply Input Voltage
Power-Supply Circuit Arrangements
Component Parts of Power Supplies
The Half-Wave Rectifier
The Full-Wave Rectifier
Filter Systems
The Voltage Divider
Voltage Regulators
Multibeam Oscilloscopes

FREQUENCY COMPENSATION

Low-Frequency Compensation
High-Frequency Compensation
Shunt Peaking
Series Peaking
Shunt-Series Peaking
The Compensated Amplifier

Each and every chapter receives the same detailed treatment. All phases of the cathode-ray tube and oscilloscope are thoroughly discussed. Here's the complete listing of chapter headings. Note how complete and up-to-date the coverage is. In addition you are always guaranteed that a Rider text is *authentic, accurate, and authoritative*. Practical as well as theoretical applications to all fields assures you a working tool that will serve you continually in your daily work.

CHAPTER HEADINGS

Chapter 1 — Introduction
Chapter 2 — Principles of Electrostatic Deflection and Focusing
Chapter 3 — Principles of Electromagnetic Deflection and Focusing
Chapter 4 — Mechanical Characteristics
Chapter 5 — The Electron Gun
Chapter 6 — Deflection Systems
Chapter 7 — Screens
Chapter 8 — Spot Displacement
Chapter 9 — Linear Time Bases (Sweep Circuit)
Chapter 10 — The Basic Oscilloscope and Its Modifications
Chapter 11 — Synchronization
Chapter 12 — Phase and Frequency Measurements
Chapter 13 — Nonlinear Time Bases

Chapter 14 — Auxiliary Equipment
Chapter 15 — Testing Audio Frequency Circuits
Chapter 16 — Visual Alignment of AM, FM, and TV Receivers
Chapter 17 — Waveform Observation in Television Receivers
Chapter 18 — AM, FM, and TV Transmitter Testing
Chapter 19 — Electrical Measurements and Scientific and Engineering Applications
Chapter 20 — Complex Waveform Patterns
Chapter 21 — Special Purpose Cathode-Ray Tubes
Chapter 22 — Commercial Oscilloscopes and Related Equipment
Appendix I — Characteristics of Cathode-Ray Tubes
Appendix II — Cathode-Ray Tube Basing
Appendix III — Photography Extensive Bibliography: Index

EXPERT

**WITH
ANTENNAS**

The complete story of receiving antenna knowledge! Supplies all of the answers to **WHICH** type is best **HOW** to use it and **WHAT** each type can do!

TWO TYPICAL CHAPTER BREAKDOWNS

CHAPTER 6 — THE THEORY OF SIGNAL INTERCEPTION

HOW THE ANTENNA INTERCEPTS A SIGNAL

THE CURRENT TREATMENT

Quarter-Wave Rod
Resonance
Half-Wave Rod
Broadside Pickup
Short-Cut Method
Current Loops

VOLTAGE PHASE AT FEED POINTS OF ANTENNA ROD

POWER EXTRACTION OF HALF-WAVE DIPOLE

Maximum Power Transfer
Standing Waves in Space
Near Field and Far Field
Effective Height
Received Signal Power
Effective Capture Area

DIRECTIVITY DIAGRAMS

Vertical Rotation
Horizontal Rotation
Three-Dimensional Directivity Diagrams
Standard Antenna

PHYSICAL LENGTH OF HALF-WAVE ANTENNAS

POWER DELIVERING ABILITY OF ANTENNAS

Internal Resistance
Radiation Resistance
Optimum Load Resistance
Mismatch
Systems Operated Off Resonance

RESONATING AN ANTENNA BY ADDING EXTRA COMPONENTS

PRACTICAL EFFECTS OF OPERATING ANTENNAS OFF RESONANCE

FREQUENCY CHANGES VS. LENGTH CHANGES

FEEDING THE HALF-WAVE ROD

USE OF ANTENNA SYSTEMS AND GROUND PLANES

Antennas Placed over Large Reflecting Surfaces
Modification of Free-Space Pattern
Antennas Very Close to Reflecting Surfaces

DIRECTIVITY OF RECEIVING ANTENNAS OVER A FREQUENCY BAND

Higher-Order Resonances
Variation of Broadside Signal

SIMPLE ZERO-GAIN ANTENNAS

Choice of Impedance

CHAPTER 7 — THE CENTER-FED ZERO-DB HALF-WAVE ANTENNA

Effective Capture Area

CONTROLLING FACTORS OF ANTENNA UTILITY

Configuration

Uniform Cross Section
Effect of Configuration on Resistance of Uniform Cross Section Antennas
Effect of Configuration on Directional Response of Uniform Cross Section Antennas
Half-Wave Antennas with Non-Uniform Cross Section
Configuration of the Folded Dipole
Configuration of Coaxial Antennas
Shunt-Connected Center-Fed Antennas
Unbalanced Types
Summary

Physical Dimensions of Zero-db Antennas

Physical Dimensions of Center-Fed Half-Wave Antennas
Relationship Between Circular, Square, and Strip Conductors

Power Transfer Capabilities of a Zero-db Antenna

Heat Loss of Antenna
Losses Due to Mismatch of Resistance
Standing-Wave Ratio
Equivalent Antenna Action Off Resonance

Antenna Matching over a Frequency Band

Resistance of Center-Fed Half-Wave Antenna With Uniform Cross Section
Surge Impedance of Center-Fed Antennas
 R_A and Q_A of Center-Fed Antenna Over a Wide Frequency Band
Nonharmonic Relationship Between Resonant Frequencies of Antennas
Summation of Band Width Characteristics for Center-Fed Antennas

QUALITY OF SIGNAL POWER DELIVERED TO THE LOAD

Effect of Highly Frequency-Selective Antenna
Safe Limits of Antenna Sharpness
Echoes Created in the Antenna System
Echoes Created by Antenna-To-Load Mismatches
Echoes in Other Parts of the System
Summary


Directional Response of Center-Fed Half-Wave Antenna

Directional Response of Tiny Segment
Response of Complete Antenna
Noise-Rejection Capabilities
Broadside Response Over a Frequency Band
Appearance of New Lobes
Response Variations With Frequency
Summary

TABLE OF CONTENTS

Chapter 1 — Review of Definitions and Terminology
Chapter 2 — The Television Signal and Its Bandwidth
Chapter 3 — Problems of Television Reception
Chapter 4 — The Electromagnetic Wave
Chapter 5 — The Radio Path
Chapter 6 — The Theory of Signal Interception
Chapter 7 — The Center-Fed Zero-db Half-Wave Antenna
Chapter 8 — Comparison of Zero-db Half-Wave Antennas

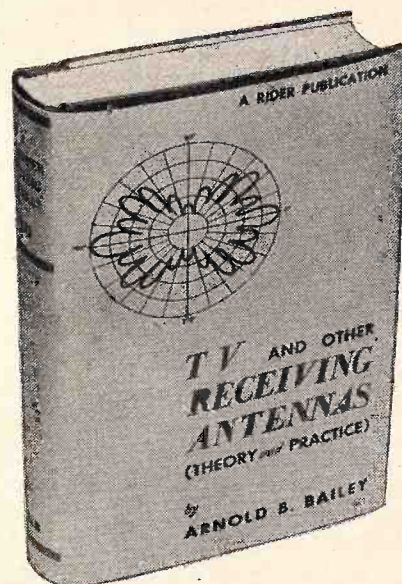Chapter 9 — Parasitic-Element Antennas
Chapter 10 — Horizontally Polarized Antennas
Chapter 11 — Vertically Polarized Antennas
Chapter 12 — Practical Aspects of TV and Other Receiving Antennas
Review Questions
Index
Chapter-end Bibliographies



TV and Other Receiving Antennas (Theory and Practice)

By ARNOLD B. BAILEY

If you have any questions about receiving antennas — you'll find the answers in this book . . .

Teacher, engineer, student, service technician — all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable — because mathematics has been translated in tables, charts, and graphs.

The analysis and preselection of antennas are aided by merely referring to the data pages on approximately 50 different basic types. The advantages and disadvantages of each type are discussed, and suggestions are given as to what antennas are required in the various reception areas.

Everything you hoped for . . . and asked for

606 Pages
Cloth-bound

310 Illustrations
5 7/8" x 8 3/8"


Economically priced . . . **\$6.00**

Majestic 97 and 98 Series (Continued from page 6)

Horizontal damper (V18, 6W4)—pin is —85 v, pins 5 and 6 are 225 v.

Model 1671 uses a single 5" p-m speaker. Models 16CT4 and 16CT5 use a single 10" p-m speaker. The schematic for Series 97 and 98 is the same as that which appears on page 5-14 except for the following changes in the ratio detector driver stage. A 100-ohm resistor, R10, is inserted from the junction of R28 and C49 to pin 1 of V6, the 6AU6 ratio detector driver. Capacitor C55, the 0.02- μ f capacitor connected from pin C of ratio detector transformer T6 to ground, has been relocated and now goes from pin C to pin 7 of V6, the ratio detector driver. The value of C55 has been changed to 5000 μ f. A 5000- μ f capacitor C32 has been added from pin 7 to pin 2 of V6. An 82-ohm resistor R26 has been inserted from pin 7 to R27, the 1,000-ohm grid resistor.

The schematic for models 14CT4 and 1674 is the same as that described above for Series 97 and 98 except for a change in the sweep circuit. Resistor R18, 390,000 ohms now goes from the junction of R83, 100,000 ohms, and C79, 13 μ f, 2 kv, to the junction of R48 (the 250-ohm resistor going from ground to pin 8 of the horizontal sweep output tube V16) and R80 (mentioned below), instead of from R83 and C79 to ground. Resistor R80, that was connected from ground to capacitor C92 (connected to pin 8 of V16), was relocated and now goes from the junction of R18 and R84 to R85 (mentioned below), and the value of R80 has been changed from 47 ohms to 470 ohms, 7 watts. Resistor R85, the 30,000-

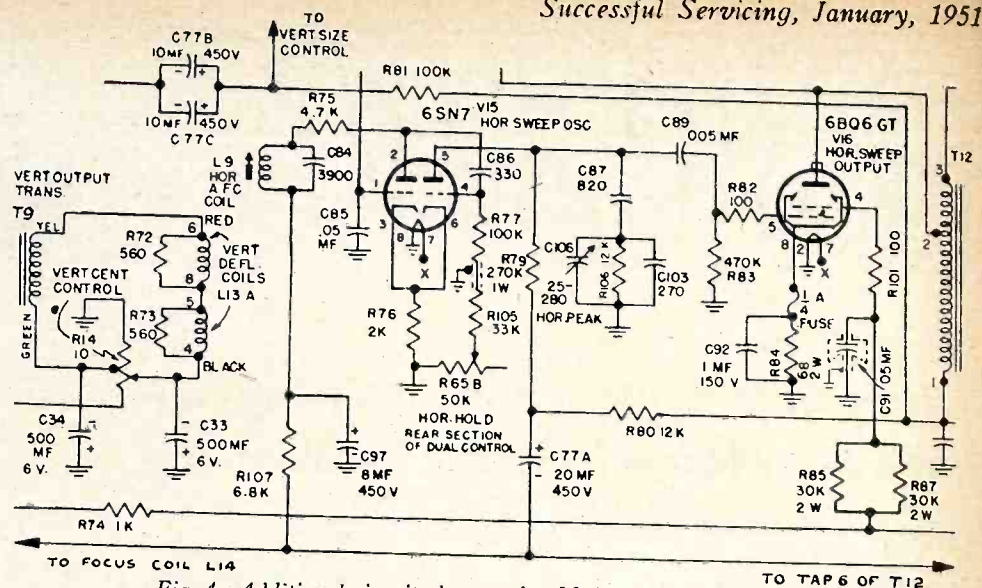

NEW! REVISED AND ENLARGED! RADIO OPERATOR'S LICENSE Q & A MANUAL

by Milton Kaufman

UP-TO-DATE as of Sept. 1950 FCC supplements, systematically listed here are the questions and answers to past FCC exams, plus a FOLLOW THROUGH discussion . . . a simplified explanation of the answer, so necessary for a complete understanding of the technical question.

CONTENTS

Element I—Basic Radio Laws, Rules, and Regulations; Element II—(New) Radiotelephone Operating Practice; Element III—Basic Theory and Practice, Radiotelephone, and (New) Basic Radiotelephone; Element IV—Advanced Radiotelephone; Element V—(New) Radiotelegraph Operating Practice; Element VI—Radiotelegraph and Advanced Radiotelegraphy; Element VII—Aircraft Radiotelegraph for Flight Radio Operator; Amateur Radio Questions and Answers; Rules Governing Amateur Radio Service; Classes B and C Amateur Radio License Examination Questions and Answers; Class A Radio License Examination Questions and Answers; Appendix I—Part 13—Rules Governing Commercial Radio Operators; Appendix II—Extracts from Radio Laws; Appendix III—Conventional Abbreviations; International Morse Code; Appendix IV—Small Vessel Direction Finders; Appendix V—Automatic Alarm; Index of Subjects.

766 Pages

240 Illustrations

5 1/2" x 8 1/2"

Only \$6.60

Garod 12T6, 14C4, 14T2, 14T6, 16C6, Series 94

Except for cabinet designs or picture tube size, Models 12T6, 14T2, and 14T6 are the same as Model 12T2, Model 14C4 is the same as Model 12C4, and Model 16C6 is the same as 16C4.

Bendix 2025, 3033, 6002

These models use tuner assemblies AROTO4 (type 1), AROTO5 (type 2) and AROTO3 (type 3) as mentioned in the parts lists for the models. The schematic for AROTO4 and alignment notes are given in the service data for Models 2025, 3033, and 6002. The schematic and alignment notes for tuners AROTO3 and AROTO5 are given in the service data for Models 2051, 3051, 6001, 6003, and 6100.

Capehart-Farnsworth CX-33

Where vertical instability occurs, check capacitor C-230 from the cathode of the 12AU7 pre-sync separator. The lead may have been broken in shipment. Check the value of R-256 grid resistor of the 6SN7 sync-clipper to ground, and if it is higher than 3.9 megohms, replace. Check R-269, the 38,000-ohm temperature compensating resistor in series with the vertical hold control. Its normal value (at 25° C) is 38,000 ohms, plus or minus 20%. As the chassis operating temperature rises, its value will decrease to a minimum of 18,500 ohms, plus or minus 20% (at 65° C). Replace this resistor if it is out of these limits, and especially if it increases in value.

Emerson 66B, 86B; 611, Ch. 87B

In the Oscillator Alignment Chart, under the column headed VTVM, the VTVM goes to the junction of R41, C28 and C29 for Chassis 66B, only. For Chassis 86B and 87B, the VTVM should go to point C.

Associated Merchants 114C, 114T, 116C, 116CD, 16RCT

The service data for these models are the same as those for Bendix Models 2051, 3051, 6001, 6003, and 6100 except for the parts listed below:

Stock No.	Description
BZ0D50	Baffle, wood & grille cloth (16" console w/o doors)
BZ0D51	Baffle, wood & grille cloth (16" console w, w/o doors)
FW0P02	Frame, wood, 16" picture (16" console w, w/o doors)
FW0P03	Frame, wood, 16" picture (16" console comb.)
FW0P05	Frame, wood, 14" picture (14" table model)
FW0P07	Frame, wood, 14" picture (14" console)
HK0R21	Knob, door pull (16" console comb.)
HZ0H21	Handle, door (16" console w doors)
KB0B06	Knob, control channel indicator (all models)
KC0B24	Knob, control, fine tuning (all models except 16" console comb.)
KC0B24	Knob, control, fine tuning, radio tuning (16" console comb.)
KC0B25	Knob, control, hor. hold (all models except 16" console comb.)
KC0B25	Knob, control, hor. hold, TV Vol Radio Vol (16" console comb.)
KC0B26	Knob, control, contrast (all models except 16" console comb.)
KC0B26	Knob, control, TV contrast, radio tone, Radio-Off-TV (16" console comb.)
KC0B27	Knob, control, Off-On-Volume (all models except 16" console comb.)
KC0B29	Knob, control, radio bandswitch (16" console comb.)
S00D15	Socket, dial light (16" console comb.)
ZW1T09	Cabinet (14" table model)
ZW1V10	Cabinet (16" console model w/o doors)
ZW1V11	Cabinet (16" console model w doors)
ZW1V13	Cabinet (16" console comb.)
ZW1V17	Cabinet (14" console model).



Music—sweet music to his ears!

And why not? A satisfied customer has telephoned—yes, actually telephoned—to thank this service-dealer for the swell repair job on his TV sets.

Your customers may not take the trouble very often to do this, but you can bet your last dime that a dissatisfied customer will lose no time in telling you what he thinks. This means call-backs on which you lose time, money, and reputation.

The trick, of course, is to eliminate call-backs. Unfortunately, you can't eliminate them *all*. But, you can keep them to a minimum by using only parts on which you can stake your reputation.

Look at any tube marked TUNG-SOL. There is the same tube—the same performance standards—the same dependability

which eight out of ten leading set manufacturers use for initial equipment. All TUNG-SOL tubes are made to meet their requirements. So, when you make replacements with TUNG-SOL tubes, you're putting back into the set the same high quality with which it left the factory.

This TUNG-SOL "one standard" policy safeguards your service work, your prestige and your profit.

Tell your distributor's salesman you'd rather have TUNG-SOL tubes.

TUNG-SOLLAMPWORKS INC., NEWARK 4, N. J.
Sales Offices: Atlanta, Chicago, Dallas, Denver, Detroit, Los Angeles, Newark



TUNG-SOL
RADIO AND TV TUBES

ONE STANDARD—The best that can be made—

For Initial Equipment and Replacement

Please mention Successful Servicing when answering advertising.

The Most Powerful RADIO Advertising

**BIG
NATIONAL
ADS**



See these big-space ads! They're appearing in the *Saturday Evening Post*, *Life*, *Look*, and *Collier's Magazine*. Each is loaded with stop-appeal and sales-appeal. Each one features an endorsement of your service by a famous star such as Paulette Goddard, Marie Wilson, Diana Lynn, or Patrice Munsel.

Marie Wilson Says:

"I think it's perfectly wonderful about the Sylvania Service man. He keeps my radio and television sets in such perfectly wonderful condition."

RADIO TELEVISION SERVICE
Sylvania Tubes
Radio and Television Picture Tubes

Diana Lynn Says:

"I'm not the superstitious type, but there's one sign I do believe in... that's the Sylvania sign. The finest radio and television service."

RADIO TELEVISION SERVICE
Sylvania Tubes
Radio and Television Picture Tubes

Paulette Goddard Says:

"Let me emphatically emphasize about the quality of my radio and television reception. That's why I call the Sylvania service sign. Let's see your service sign replace in top form."

RADIO TELEVISION SERVICE
Sylvania Tubes
Radio and Television Picture Tubes

Patrice Munsel Says:

"I'm keen about the fine and pure quality of my television set... my radio, too. Most sound just right. That's why when it comes to service I call on expert... the dealer who displays the Sylvania sign."

RADIO TELEVISION SERVICE
Sylvania Tubes
Radio and Television Picture Tubes



SYLVANIA

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT

TV SERVICE Campaign ever launched!

HERE'S the hardest hitting . . . and the most complete advertising campaign ever planned, to bring service business to every dealer who displays the Sylvania emblem.

All during 1951, your prospects are certain to SEE, HEAR, and READ about your expert service in magazines, on television, and through window displays.

**POPULAR
WEEKLY
TV SHOW**



The great Nation-wide TV show, "Beat the Clock," featuring Bud Collyer over CBS-TV, will go to bat for your service and the Sylvania products which you sell. Clever animated cartoon commercials on the CBS-TV station in your area will inform prospects of your expert workmanship and prompt service.

Tying everything together is the greatest and most colorful dealer tie-in program you have ever seen!

You get **FREE** giant, full-color displays of the featured stars. You get counter cards . . . bright window streamers . . . spot radio announcements . . . mailing pieces . . . all designed to identify you as the Sylvania Service Dealer advertised on television and in the national magazines.

Ask your jobber for full information about the bigger-than-ever 1951 Service Dealer Advertising Program. If he can't give you all the facts, mail the coupon now!

**DEALER
TIE-IN
PROGRAM**

"Service business is booming . . . tie-in with Sylvania's national advertising and get a bigger share!"



Be sure to display this emblem. Put up these Sylvania decals right now! This seal is the target of the whole Sylvania Service Dealer campaign. Put them on your windows and on your trucks. Made in 8-inch and 12-inch sizes. Order a supply from your jobber **TODAY!** They're free!

ELECTRIC

NEON TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

Sylvania Electric Products Inc.
Dept. R-2701, Emporium, Pa.
Please send me full details about the greatest in the history of the industry.

Name _____
Street _____
City _____ Zone _____ State _____

RADIO FREQUENCY PROBES

(Continued from page 1)

Substituting this into the equation above:

$$Z_r = \frac{Q_r^2 W_r L}{Q_r}$$

or

$$Z_r = Q_r W_r L$$

Let us, for example, compute the resonant impedance of a tuned circuit having an inductance of 5 microhenrys, a Q of 200, and a resonant frequency of 10 megacycles. Using the equation above,

$$Z_r = 200 \times 2\pi \times 10^7 \times 5 \times 10^{-6}$$

or

$$Z_r = 62,800 \text{ ohms.}$$

Using the impedance just obtained and comparing it to that of the probe analyzed above, we find that the tuned-circuit impedance will be reduced by approximately 5 per cent when the probe is connected across it. The gain and selectivity of the circuit will be similarly affected.

Coil and capacitor circuits of conventional design have maximum Q values of from 200 to 300, so that a good 5- μ f input-capacitance probe is usable up to 100 megacycles or so. At still higher frequencies, circuits having very high Q values are encountered. A resonant line is an example of a circuit capable of building up a very high impedance at frequencies above 100 megacycles. Some newly developed high frequency diodes are available and accomplish significant reductions in the input capacitance. Some of these with their characteristics are listed in Table 1.

There are two additional considerations in

mately one-half the resonant frequency. The error gradually increases until, at resonance, the reading on the meter is 200 to 300 per cent higher than the actual voltage. After resonance, the error decreases rapidly and finally becomes a negative one. It should be emphasized that the resonant frequency of the whole probe is considerably below the resonant frequency of the tube alone. For instance, a tube may have a resonant frequency of 1,000 megacycles, yet the probe it is used in, even when of the best design, will resonate at 500 megacycles or less.

Other causes for error in the meter reading near resonance are the increased loading effect accompanying resonance and the transit-time effect of the diode. The transit time is the period it takes for an electron to move from the cathode to the plate of the tube. At high frequencies, the movement of electrons between the tube elements is not simultaneous with the change in grid voltage. Because of this, the relation between the plate current and the applied signal voltage is subject to error; the higher the frequency, the larger the error.

Large connecting clips and long leads may increase regeneration in circuits under test due to their inherent inductances and capacitances. At 10 megacycles, leads of No. 18 wire, or larger, and two or three inches long do not seriously disturb most circuits. At 50 to 100 megacycles, the shortest possible leads should be used as well as the smallest clips or, better still, the leads should be soldered directly to the circuit. Above 100 megacycles, even more stringent precautions should be taken such as extensive shielding of all components. Some probes have removable tips, etc., to improve their operation at very high frequencies.

TABLE I
HIGH FREQUENCY DIODES USED IN R-F PROBES

Tube Name	Heater Voltage (volts)	Heater Current (amperes)	Input Capacitance (micromicrofarads)	Resonant Frequency (megacycles)	Tube Type
6AL5	6.3	0.3	3.2	700	Miniature
1247	0.7	0.065	0.6		Sub-Miniature
9004	6.3	0.15	1.6	850	Acorn
9005	3.6	0.165	1.0	1500	Acorn
9006	6.3	0.15	1.6	700	Miniature
2-01C	5.0	0.34	0.7	2800	Eimac


the application of diodes to high-frequency measurements. In the above analysis, the effective series inductance of the probe input circuit has been neglected. Also, no mention was made of transit-time effects. Both of these limit the frequency range of a diode rectifier.

Neglecting resistance effects, a probe looks like a capacitance to the circuit across which it is connected, at all frequencies up to about several hundred megacycles, above that it looks like an inductance. This is due to the fact that, in addition to the above discussed shunt capacitance, there is always series inductance in the internal circuits of the probe. This inductance, composed of the inductance of the series leads, the series inductance of the input coupling capacitor, and the inductance of the leads inside the tube, usually varies from 0.01 to 0.1 microhenry.

As the frequency at which measurements are made is increased, the probe resonance (the frequency at which the capacitive reactance equals the inductive reactance) is approached, reached, and passed. The effect of resonance starts to show up as an increase in the reading of the voltmeter above approxi-

Successful Servicing, January, 1951

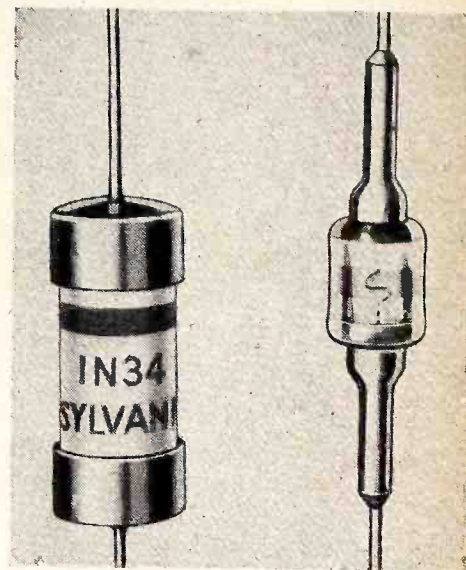frequency response of the crystal due to inadequate general probe design. This is unfortunate, since most of the real advantages of crystal probes are found only at the very high frequencies (50 megacycles and higher).



Courtesy Sylvania Electric Products Inc.

Fig. 3. Two crystal diodes of the type used in r-f probes. On the left is shown the ceramic type where the crystal is enclosed in a ceramic cartridge with metal caps. The one on the right consists of a crystal contained in a hermetically sealed glass container.

For frequencies less than 50 megacycles, the crystal probe is at best, equal to the vacuum-tube probe, and as the frequency is decreased, it becomes definitely inferior in several respects.

At low frequencies, the back resistance (the resistance at negative voltages), becomes an important characteristic. In most tube diodes it is at least high enough so that it can be neglected in comparison with the usual shunt resistance and other shunts in the circuit. That is to say, it is negligible compared to resistances of the order of 5 megohms. However, almost all germanium crystals have back resistances ranging from a few thousand ohms to a few megohms, and these must be taken into consideration at low radio and at audio frequencies. Since the back resistance is effectively in parallel with the probe input, it may seriously limit the input impedance of the probe at low radio frequencies and at audio frequencies.

It should be noted that there may be considerable variation in back resistance among crystals of the same type, even those made by the same manufacturer. The back resistance is also, generally, a function of applied voltage. A crystal which shows a relatively high back resistance on small signals may show a considerably smaller resistance on large signals. Therefore, crystals for voltmeter use should be tested carefully for back resistance and voltage tolerance.

One characteristic of crystal probes which make their use more convenient is that they have no contact potential. Thus, they may be used to feed directly into a single-ended d-c voltmeter without requiring special balancing provisions in the amplifier. They are, therefore, useful as a means for converting a d-c voltmeter of the electronic type having a

Crystal Probes

Germanium crystals are coming into considerable use for high-frequency probes. They have advantages of simplicity, freedom from contact potential, extended high-frequency response, low input capacitance, and small physical size. However, they have several serious disadvantages in that they are relatively unstable, show large variations in current due to temperature changes, are limited in voltage acceptance, and show wide variations in loss factor. The technique of manufacture as well as the general characteristics of germanium crystal diodes is being constantly improved. The best types available today are many times better than those which were available a few years ago.

Germanium crystal diodes are being made in increasingly smaller sizes. Some of the latest types are only about 1/2-inch in length and less than 1/4-inch in diameter as shown in Fig. 3. The series inductance and shunt capacitance of these elements are correspondingly small, and the frequency response is uniform to hundreds and even thousands of megacycles. Many commercially available crystal probes do not approach the inherent

high-impedance input into an a-c and r-f meter without circuit changes. Since crystal diodes are usually used as peak rectifiers, a special calibration may be necessary. For readings above a few volts, approximately correct rms voltages will be indicated by the d-c meter if a dropping resistor equal to 40 per cent of the d-c voltmeter input resistance is placed in series with the crystal probe. This resistor also functions effectively as a filter resistor to reduce the effects of a.c. or r.f. on the d-c voltmeter circuits.

Figure 4A is an illustration of a typical crystal probe, and Fig. 4B is the circuit. The probe shown here has an input capacitance of 3.5 μf , and an input resistance of approximately 0.25 megohms at 500 kc, and 25,000


pedance peak response circuits such as is found in a crystal-diode probe. Because the efficiency of rectification changes with the temperature of the crystal, the calibration of voltmeters using crystal probes is unreliable where relatively large changes of temperature are experienced.

In addition to the characteristics of crystals noted above, two others should be mentioned. Crystal rectifiers have a tendency to drift under an applied voltage. Accompanying this drift there is usually a considerable change in back resistance. Also, crystals are limited in the voltage that can be safely applied to them. Some older types are permanently injured by the application of 20 to 30 volts of or more and will recover after momentary



(A)

Fig. 4. In (A) is shown a breakdown photograph of a typical crystal diode probe used for r-f measurements. The input coupling capacitor is located in the head of the probe and is only partly seen. (B) is the circuit of the probe shown in (A).

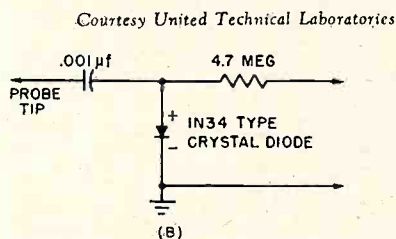

ohms at 100 Mc, so that it will give accurate readings up to about 200 Mc. The probe is designed to withstand loads of 400 volts d.c. A short ground lead and prod is shown in the illustration; in most cases the ground lead ends in an alligator clip. It is important to note that when measuring high-frequency voltages, the ground lead should always be connected to a point as close to the point being measured as possible to make certain that there is an adequate return path.

The input capacitance of a crystal probe may be kept down to 1 or 2 μf , so that in this respect they are inherently superior to vacuum-tube probes. Since the crystals have relatively low back resistances, no shunt load is required. This aids in keeping down the shunt capacitance and prevents detuning when they have a relatively large temperature co-measuring tuned circuits.

A serious disadvantage of crystals is that efficient of rectification efficiency. Although this affects their operation when the load resistance is low, it also shows up in high-im-

overload. Welded contracts appear to be ad-signal; some newer types will take 100 volts vantageous in helping a crystal to recover after overload.

The major considerations in the selection of a probe for any job or meter are the frequency range in which the probe will be used and the voltage the probe will be subjected to. Whereas crystal probes are useful in the upper frequencies (up to about 200 Mc), their voltage measuring range is limited to about 20-volts rms. Where it is expected that the r-f voltage to be measured exceeds this amount, it is necessary to use a probe with a conventional diode tube. In selecting a probe the features to look for are a ground lead with an alligator clip or some similar method for thoroughly fastening the ground lead to the chassis or ground, a body design which is thin and long enough to keep the hand away from high-voltage spots in the equipment being measured, accessibility of the probe to servicing, ruggedness of design, and durability.

Curtain Time

(Continued from page 5)

supply at once and place your order, because, judging by our experiences during the past three months, we cannot guarantee an adequate stock to every jobber.

We might mention to those men who have had some difficulty in securing their copy of our RECEIVING TUBE SUBSTITUTION GUIDE BOOK, that the first printing of 25,000 copies was completely sold out 21 days after publication. By the time this house-organ appears, the second printing will have reached our jobbers, but, as you can see, it was impossible to avoid the back-ordering situation and the delay between the first and second printings.

We might remark that if you need any Rider Manuals, get them as soon as you can. Also bear in mind that when you work with Rider Manuals, you are using the same information which the manufacturer is using in his servicing operations, and, that with the exception of the set manufacturer himself, no other source of service data can equal Rider Manuals in authenticity, accuracy, and completeness of coverage. Rider Manuals have been proven *Best by Test* over 21 years of Test.

JOHN F. RIDER

Erratum

In Rider's TV Manual Volume 4, Crosley pages 4-13 through 4-22 are corner carded 9-403, M3LD. These pages should read 9-409, M3LD.



An Indispensable
EMERGENCY
Tool for Every TV and
Electronic Technician!

QUIK-SHOT

Reg. U.S. Pat. Off.

SOLDERING IRON

• 250 Watts • Maintains Soldering Temperature for 6 to 8 Minutes • No Electricity • No Flame • No Blowtorch
Pull the Trigger and the Iron Heats Itself
In Less Than 10 Seconds!



QUIK-SHOT is a "must" for every emergency when line power is not available nor convenient. Heat is generated internally through the QUIK-SHOT cartridge which is inserted into the iron. UNCONDITIONALLY GUARANTEED! Absolutely safe. Accepts $\frac{1}{8}$ ", $\frac{1}{4}$ " and 1" tips.

Model QS 38 ($\frac{1}{8}$ " Pyramid or Chisel Tip) \$7.50
Model QS 58 ($\frac{1}{4}$ " Pyramid or Chisel Tip) \$7.50
Model QS 100 (1" Chisel Tip Only) \$8.25

All standard models complete with 4 QUIK-SHOT Cartridges and Pyramid Tip.

QUIK-SHOT Cartridges (12 in carton) \$1.92

SEPARATE TIPS

$\frac{1}{8}$ " or $\frac{1}{4}$ " Pyramid or Chisel \$2.25

1" Chisel Only \$3.00

Ask Your Jobber or Write Direct


JOHN F. RIDER LABORATORIES, Inc.

480 Canal Street • New York 13, N. Y.

FREE!

NEW SHURE

Cartridge Replacement GUIDE

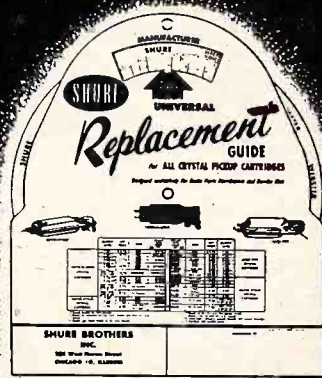

A TURN OF THE DIAL GIVES THE CORRECT REPLACEMENT MODEL OF ALL SHURE CARTRIDGES AND MOST OTHER MAKES

Ask your Shure Distributor for a "Guide" —or write direct, giving us his name.

SHURE BROTHERS, INC.

Microphones and Acoustic Devices

225 West Huron Street • Chicago 10, Illinois

Please mention Successful Servicing when answering advertising.

Radio Changes

Farnsworth P71, P72, P73; Capehart-Farnsworth P77, P777

The failure of the changer to shut off after playing the last record may be caused by dust or foreign particles collecting between the inner tube (No. 11379) and the outer tube (No. 55334) or by corrosion on the two parts, making their movement sluggish. This may be checked easily. The weight of a 10" record on the single speed changer and a 7" record on the dual and triple speed changer should hold the spindle down. When the record is dropped to the turntable, the unloaded spindle should raise up approximately 1/16". If the spindle does not raise freely, it should be disassembled and cleaned. If corrosion is discovered after disassembly of the spindle, it may be removed from the compression rod (part of No. 13674) and from the outer surface of No. 11379 by polishing with crocus cloth. The best way to remove corrosion from the inner wall of part No. 11379 is to use a pipe cleaner, rouge and a rust solvent. After cleaning thoroughly in this manner, an unused pipe cleaner should be inserted in order to remove any remaining rouge and rust solvent before re-assembly of the parts. *Do not use any lubricant.* The same will apply to the inner wall of the outer tube No. 55334. When re-assembling, be sure that the small washer, No. 55345, between the spring collets and the rubber is installed cup side down. If installed with the cup side up, two or more records will drop. As a final note on this point, spindle corrosion has nothing whatsoever to do with failure to drop records properly, unless, of course, the spindle parts are completely "frozen."


Failure of the changer to drop records properly may be caused by a spring collet, or by improper adjustments. In checking for proper adjustment, there are three dimensions which must be observed closely. Adjusting nut No. 37344 on the bottom of No. 13674 spindle must be set so that rubber washer,

part No. 62152, when fully compressed does not exceed 0.337 inches in diameter. Original engineering specifications on this part were 0.312 to 0.325. In order to operate more satisfactorily on older records, this was later increased to 0.335 to 0.337, although the original specifications should be entirely satisfactory on new records which are in good condition. If necessary to change adjusting nut No. 37344, be sure locknut No. 2015-002 is tightened securely.

Capehart-Farnsworth P-777

The rubber belt may run off the 78-rpm drive, due to the motor mounting frame being bent slightly, causing misalignment of the shafts. This should not be difficult to check, and if bent, to correct. If, for some reason, it proves impossible to effect permanent correction, then the only solution would obviously be replacement of the motor assembly.

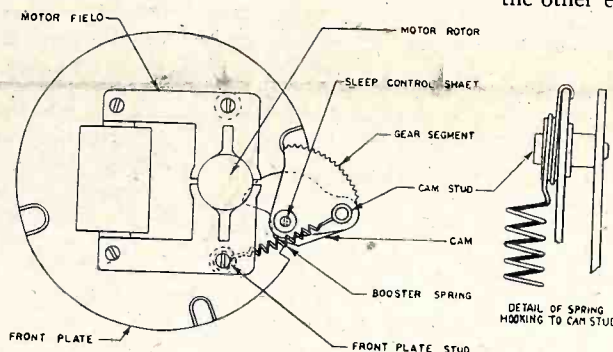Also check for excessive friction in the 45-rpm bearing. This pulley may be removed, and, if there is any tendency to excess friction, ream it out slightly, apply lubricant, wipe off the excess lubricant and replace. This may also be the correction for one of those hard to locate sources of "wow" or speed variation, noticeable especially on 33- and 45-rpm records.



Rear view of clock mechanism in General Electric Models 64 and 65, showing position of booster spring.

Successful Servicing, January, 1951

RCA Ch. RC-1065C, RC-1065D

The value of capacitor C3 in these chassis is 9.1-113.8 μ f. C3 is located across oscillator coil L2.

General Electric 64, 65

Late production receivers incorporate a helical spring in the clock mechanism which provides a more positive trip action to the switch contact assembly when operating the sleep control. Failure of switch contacts to open may be due to the incomplete travel of the sleep control gear segment and cam assembly after its release by the segment gear's drive pinion. Normally, the spring action of the switch contacts through the sleep control switch lever should be sufficient to allow sleep control cam and gear segment to spring outward completely after it becomes disengaged from its pinion drive gear. However, if binding or position of control parts results in failure of segment gear and cam to swing completely outward properly releasing switch control lever and contacts, the addition of the booster spring (catalogue no. RMS-203) will provide the additional tension to correct segment gear and cam operation.

To install the booster spring, remove the case and draw the clock mechanism forward from the front of the radio cabinet, just far enough to permit installation of the booster spring. The accompanying illustration shows the position of the booster spring as viewed from the rear of the clock mechanism. One end of the spring is fastened to the cam stud, the other end to the brass front plate stud.

All you want to know about master television antenna systems is in

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf

This is the only book on the subject, and it covers the subject completely. What is your master TV antenna problem . . . installation, sales, maintenance, use? TV MASTER ANTENNA SYSTEMS has the answer, thorough in technical detail, explained in a manner comprehensible to those not trained technically. Each problem and its solution is extensively covered from beginning to end. The authors have been able to give such complete coverage because they have worked with every phase of them. Ira Kamen has personally worked with each of the TV systems discussed

in this book, either designing or directing installation, including the following amplified master antenna systems that are covered in Chapter IV: The RCA Antennaplex System, The Intra-Video System, The Lynmar System, The Transvision System, The Brach Mul-Tel System, The RMS System, The TACO System, The Multitenna System, The TEC System, The Jerrold Mul-TV System.

A glance at the Table of Contents will show you how completely TV MASTER ANTENNA SYSTEMS covers the subject:

TABLE OF CONTENTS

1—Basic Television Antenna Systems; 2—The Need for Master Antenna Systems; 3—Non-amplified Master Antenna Systems; 4—Amplified Master Antenna Systems; 5—Installing Master Antenna Systems; 6—Video Distributing Systems; 7—Merchandising Master Antenna Systems; Appendix A—Temporary Landlord Agreement; Appendix B—Sample Electrical Specifications; Appendix C—Survey Report, Landlord Agreement, and Tenant Letters; Appendix D—Cautions; Index

AVAILABLE NOW

234 Illustrations

368 Pages

5 1/2" x 8 1/2" \$5.00

THE BIG 4

JFD

AIR COOLED TELEVISION BALLASTS



Choice of Manufacturers for ORIGINAL Equipment

Cash in on the growing TV ballast replacement market. You can't go wrong when you use the EXACT TV Ballast ORIGINALLY Used by the Manufacturers themselves. Models for EMERSON, MOTOROLA, TELE-TONE, BELMONT, STEWART-WARNER, PILOT, and others.

**LIST
\$2.25
Each**

FROM JFD

WORLD'S LARGEST SINGLE SOURCE
OF TV ANTENNAS and ACCESSORIES



TV Voltage Regulators

FOR REALLY STEADY TV PICTURES

Produces steadier TV pictures despite line voltage changes. Male and female connections. Operates on either 110v AC or DC. Plugs in between the TV set line cord and outlet. Recommended for use with all leading makes of TV sets: RCA, DUMONT, PHILCO, ADMIRAL, EMERSON, ZENITH, etc.


Model 93-7, 300 watts. List price, each **\$2.85**
Model 93-8, 375 watts. List price, each

JFD

DETENT SWITCH CONTROLS

- ★ DURABLE BRASS SPRING
- ★ BRASS and PHENOLIC SHAFTS

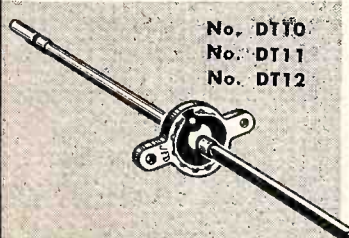JFD has the most complete line of Detent Switches on the market . . . exact replacements for RCA, Emerson, Admiral, Teletone and other TV sets. Designed for RCA Tuners used in 630, 700 and 721 type chassis. Available with or without locating plates. Write for FREE Replacement Reference Chart No. 60R.



No. DT10
No. DT11
No. DT12

No. DT10 . . . Short shaft, complete with locating plate. (Replaces RCA part No. 71463.)
No. DT20, without locating plate.
No. DT11 . . . Long shaft, complete with locating plates. (Replaces RCA part No. 72743.)
No. DT12 . . . Extra long shaft, complete with locating plate. (Replaces Admiral part No. 76B14 used in entire Model Series No. 30A and 8C.)
No. DT22, without locating plate.

(Designed for use with RCA TV Tuner part No. 71531—Replacement Type 201E1.)



No. DT13

No. DT13 . . . All phenolic shaft, complete with locating plate. (Replaces RCA part No. 73440.) Designed for use with RCA Tuner Replacement Types No. 74941, 73435, 74571.



No. DT14

No. DT14 . . . All phenolic shaft, complete with locating plate, for new RCA TV sets. (Replaces RCA part No. 75162.)

Write for FREE
Replacement Reference Chart #60R

Write for Complete Catalogue of JFD Television
Antennas and Accessories, No. 58G


JFD

"Clear Beam" WAVE TRAPS


"YOU CAN SEE
THE DIFFERENCE!"

JFD "Clear Beam" Wave Traps filter out FM image and amateur harmonic interference easily and effectively. Simply attach universal mounting bracket to television cabinet or chassis, then attach lugs to antenna input terminals. Result: clear, bright pictures with sustained signal strength. List,

\$2.75

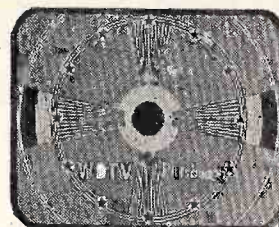

Without JFD Wave Trap

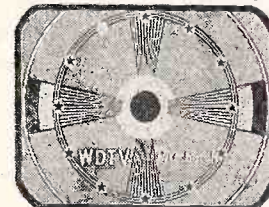

With JFD Wave Trap

- BR 106-10-30 Traps out amateur Harmonic Interference from 14 and 28 mc bands.
- BR 106-80-110 Traps out FM Image Interference.
- BR 106-30-60 Traps out 30-60 mc amateur Harmonic Interference.
- BR 106-60 90 Traps out 60-90 mc. Diathermy Interference.

JFD

MANUFACTURING CO., Inc.

6119A 16th Ave., Brooklyn 4, New York
FIRST in Television Antennas & Accessories

Television Changes

Philco 10", 12", 16" Models

To greatly facilitate service bench work, cathode-ray-tube and deflection-yoke extension cables may be prefabricated from the following accessory parts:

1. Deflection plug and cable assembly, Part No. 41-3860-6 Octal Socket and Cable, Part No. 41-3777.
2. Cathode-ray-tube cable and socket assembly, Part No. 41-3772 CRT plug, Part No. 54-4571-1.

This cable is approximately 28" long.

Capehart-Farnsworth CX-33

Sometimes a "whistle" occurs in the sound and/or lines (similar to a Barkhausen effect) appear in the picture, although both symptoms do not always appear. The cause in most cases is due to the fact that C-242D (electrolytic, between -90-volt point and chassis ground) has a higher than normal impedance at the horizontal oscillator frequency. To improve by-passing at this frequency, a 0.1- μ f, 200-volt capacitor is connected from the -90-volt point (junction of R-291 and R-290 near the 6BG6 tube) and chassis ground. This capacitor will be added in production.

If difficulty is encountered in accurately aligning the primary of transformer T-204, to the 4.5 Mc, it is possible that the tuning range has deviated, due to variations in material. A 5- μ f capacitor connected from terminals 3 and 4 of T-204 should correct this condition.

If the picture focus lacks sharpness, it may possibly be improved by connecting a 2,200-ohm 2-watt resistor in parallel with R-297 (focus control) and R-296B. This connection can be made at the terminals of the filter capacitors C-243C and C-264B. This change should be tried only after carefully making normal adjustment to obtain proper focus.

**Automatic P-490, TV-707, TV-709,
TV-710, TV-712, TVX313, TVX404**

These models all use Chassis AR-TV-709. A final oscillator adjustment for each channel

should be made on the receiver at the time of installation and whenever the 6J6 oscillator tube is changed. This oscillator adjustment can be made for each channel without removing the receiver from the cabinet. The following procedure should be followed in setting the oscillator frequency for each channel:

1. Turn channel selector to the required channel.
2. Remove channel selector knob.
3. Remove two wood screws securing channel selector indicating plate.

4. Locate oscillator coil to be adjusted by noting channel number on chassis around switch.

5. Insert fiber or bakelite-type screw driver carefully in slotted brass slug in oscillator coil.


6. Adjust for best compromise between picture and sound.

(Caution: Do not apply excessive pressure while adjusting!)

7. Turn Channel Selector switch to other channels and repeat above procedure.

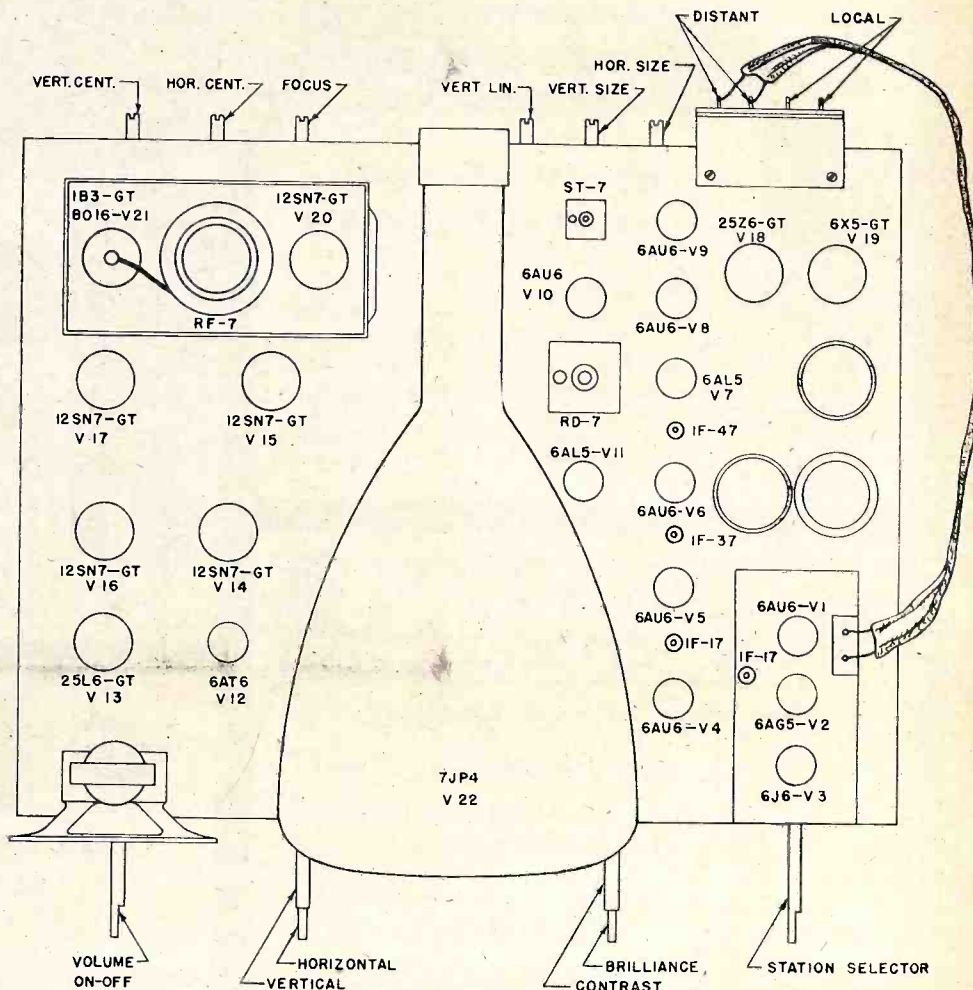8. Replace selector plate and knob.

The accompanying figure shows the tube layout.



Tube layout for Automatic Chassis AR-TV-709.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall

A clear, concise, easy-to-follow treatment of the practical details pertaining to all of the mechanical and electrical problems arising in TV installations. This is the only text which furnishes all the data pertaining to the mechanical considerations of TV antennas; ice loading, wind surface, and mounting requirements — whether for short chimney-attached mast or for an 80 ft. tower, including foundation. It also contains receiver adjustments in the home . . .

336 Pages 270 Illustrations

municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the United States.

A most practical "how-to-do-it" treatment of the subject, approved by TV receiver manufacturers, which every student will carry with him into his commercial work. To simplify instruction, summary and questions follow each chapter.

CONTENTS

Chapter 1 — Nature of Television:

5 5/8" x 8 5/8"


Chapter 2—Radio Propagation; Chapter 3—Antennas; Chapter 4—Transmission Lines and Special Antenna Systems; Chapter 5—Materials and Methods Used in Installations; Chapter 6—High Masts and Tower Installations; Chapter 7—Problems Arising in Television Installations; Chapter 8—Receiver Adjustment and Service in the Home; Chapter 9—Municipal Regulations; Appendix; Index; Review Questions.

A Phenomenal buy for Only \$3.60




WIDE RANGE 5-INCH OSCILLOSCOPE

MODEL 3440

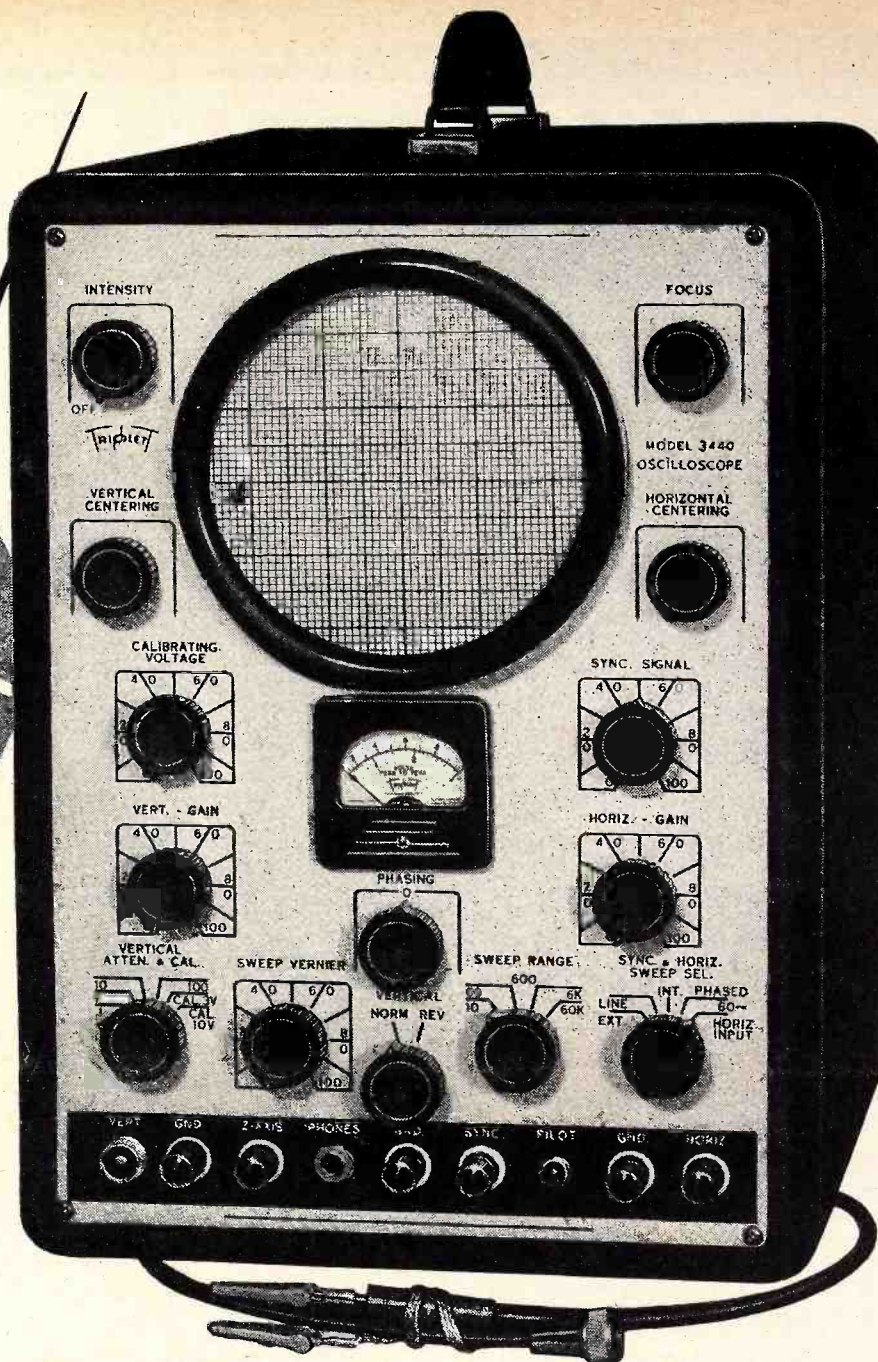

- * ● Provision for changing polarity—wave form shows in conventional manner.
- * ● Calibration Meter—to measure voltage of complex wave forms in TV receivers.
- * ● Vertical deflection sensitivity—.009 RMS volts/inch.
- Wide frequency range—20 cycles to 1 MC on Vertical—Services both TV & FM.
- Return trace eliminator.
- Internal phase controlled horizontal sweep.
- Internal sweep oscillator—10 to 60 MC/second linear.
- Z-axis input for intensity modulation.

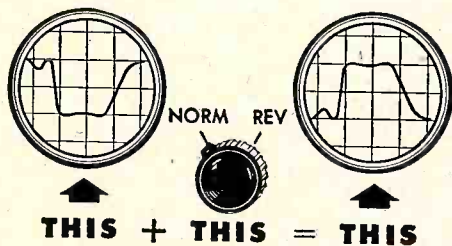

The first oscilloscope which permits changing polarity, thus keeping wave form showing in a conventional manner.

ONLY \$189.50 AT YOUR DISTRIBUTORS

- Copper plated feet for improved grounding.
- * EXCLUSIVE AT THIS PRICE LEVEL

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplett

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.

Please mention Successful Servicing when answering advertising.

63,500

There are 63,500 references to pertinent electronic and allied engineering articles published from 1925 through 1949 in the five editions of the

ELECTRONIC ENGINEERING MASTER INDEX

These indexes are invaluable to

- Librarians
- Engineers
- Management
- Government Officials
- Patent Attorneys
- Instructors
- Students
- Authors

The bibliographical listings, which have been compiled from foreign and domestic magazines, journals, proceedings, government reports, technical house organs, texts, and U. S. Patents, etc., give a complete source of information pertaining to electronic and allied fields.

THE ELECTRONIC ENGINEERING MASTER INDEX

1925-1945 edition—
(15,000 entries).....\$17.50

1935-1945 edition—
(10,000 entries).....\$10.00

1946 edition—
(7,500 entries).....\$14.50

1947-1948 edition—
(18,500 entries).....\$19.50

1949 edition—
(12,500 entries).....\$17.50

Electronics Research Publishing Company, Inc.
Dept. 55 480 Canal St., New York 13, N. Y.

Television Changes

Gamble-Skogmo 05TV1-43-8940B, 05TV1-43-9002B

These models are similar to Model 94TV1-43-8940A and Model 05TV1-43-9002A except for the following changes. Models 8940B and 9002B are 12½-inch television receivers, and the 9002B employs a 10-inch p-m speaker. A chassis identification number is assigned to each receiver in production. After identification number (group number) 14,200, a wiring change was made to improve the vertical sync, reduce "snow" in the picture, and to remove the tendency toward horizontal wavering. This wiring change was accompanied by a model number series change from A to B in both the 8940 and 9002 receivers.

The models 8940B and 9002B are identical to the 8940A and 9002A with the exception of the tuner input wiring and the changes listed for Model 94TV1-43-8940A. The changes in the parts lists are as follows:

Ref. No.	Part No.	Description
R4	C-9B1-74	10,000 ohms, ½ watt, 10%
	A-7M-15511-1	Trimmer plate
	A-2H-12337	Tube shield base
	A-7M-15510-1	Coil alignment strip
	A-2J-16310	Sliding contact
	A-5F-16311	Contact holder
	B-200-17086	Switch lever assembly
	C-2E-15486-1	Cover
	A-49A-15993	Take-up spring
	A-49A-15988	Tuner shaft spring
	A-55C-15496	Steel ball
	A-2C-16446	Retainer plate
	B-3B-18554	Vernier bushing
	N-23M-18571	Drive screw
	A-3C-18551	Vernier stud
	A-2M-18557	Vernier spring
	N-211-17078-1	Tuner assembly
	C-8F-18569	22 μ f
C63		.01 μ f
C85		.005 μ f
C90	C-8D-17608	.05 μ f, 400 volts
C93	C-8D-14461	.02 μ f
C95	C-8D-17607	.005 μ f, 200 volts
C105	C-8D-17785	22 μ f, 500 volts, ceramic
C110	C-8G-11892	820 μ f
C111	C-8F6-124	2 μ f (coil form)
C116	A-5D-18507	7 μ f, ceramic
C120	C-8G-11790	120 ohms, ½ watt, 10%
R28-56	C-9B1-51	Dual control, and switch
R32-61	A-10B-18441	10K ohms, ½ watt, 10%
R35	C-9B1-74	3300 ohms, 2 watts, 10%
R38	C-9B2-68	220K ohms, ½ watt, 10%
R45-82, 92	C-9B1-90	68K ohms, ½ watt, 10%
R73	C-9B1-84	2200 ohms, ½ watt, 10%
R50-81	C-9B1-66	680 ohms, 1 watt, 10%
R63	C-9B2-60	1.5 megohms, ½ watt, 10%
R72	C-9B1-100	1000 ohms, ½ watt, 20%
R79	C-9B1-13	680K ohms, ½ watt, 10%
R87	C-9B1-96	220 ohms, ½ watt, 10%
R110	C-9B1-54	5600 ohms, 2 watt, 10%
R103, R107, R108	C-9B4-71	
R109	C-9B1-77	18K ohms, ½ watt, 10%
R112	C-9B1-102	2.2 ohms, ½ watt, 10%
T6	C-12M-18689-1	Horizontal deflection transformer
T7	C-12A-18839	Power transformer
	B-15B-14274	Yoke socket
	A-19A-14275	Yoke plug
	A-15C-18735	1X2 tube socket
	A-5M-18733	Standoff insulator
	A-62D-18734	H-v ring
	B-201-16153	H-v cable assembly
	C-2B-18056	Shield can
	R-24D-18709	Cabinet (9002)
	C-18A-18157	10" PM speaker (9002)
	C-23J-18722	Back cover (9002)

National TV-1601, TV-1602, TV-1625, TV-1627

Models TV-1602 and TV-1627 are similar to Models TV-1601 and TV-1625. The following changes have been made in these National models.

In the audio output circuit (V-22), capacitor C-101, that went from pin 8 to the junction R-106, R-107 and R-108, has been relocated and is now inserted in the lead from pin 8 to R-109. The value of C-101 has been changed from 0.05 μ f to 10 μ f. R-106 has been removed from its position (from the junction

Successful Servicing, January, 1951

of C-101, R-108, and R-107, to socket X-1 pin 6) and relocated in parallel with C-101. The value of R-106 has been changed from 330,000 ohms to 270 ohms. Resistor R-107, 180,000 ohms, has been removed. In the audio amplifier circuit, R-104, 470,000 ohms, connected from pin 8 of V-21B to R-105, 470,000 ohms, has been removed from the circuit. The value of resistor R-99 connected to pin E of transformer T-5, has been changed from 220 ohms to 120 ohms.


In the ratio-detector driver circuit resistor, R-96, that went from pin 7 of V20 to R-97, 1000 ohms, has been relocated and now is connected in parallel with capacitor C-89, 0.005 μ f, from pin 6 to R-97. The value of R-96 has been changed from 68 ohms to 18,000 ohms. Capacitor C-88, 0.005 μ f from pin 7 to R-97 has been removed from the circuit and pin 7 is tied directly to R-97.

The value of resistor R-13, connected to the junction of pin 6 of V-3 the first video i.f. and L-8, has been changed from 100 ohms to 220 ohms. The value of resistor R-31, connected to pin 4 of V-8 the video amplifier, has been changed from 120 ohms to 100 ohms. A centering control, R-41, 8200 ohms, has been added from L-18 to socket X-2, pins 2-10. Tap 6 of transformer T-4 is connected to pin 7 instead of to pin 5 of socket X-2. The pins for the X-2 P-2 connections (in the lead that goes to the horizontal deflection coil), are designated 2-10.

Resistor R-48, 470 ohms, has been removed from across the focus control. Capacitor C-58, 20 μ f, connected to the vertical size control tap now goes to pin 7 of socket X-2, instead of to ground. A 47- μ f capacitor, C-44, has been added from pin 4 of the horizontal sweep oscillator to ground. Resistor R-62, 22,000 ohms, is now connected to pin 7 of socket X-2 instead of to fuse F-2. The value of R-64 connected to pin 5 of the horizontal sweep oscillator has been changed from 220,000 ohms to 150,000 ohms. The value of resistor R-68, connected to pin 8 of the horizontal sweep output, has been changed from 1500 ohms to 5600 ohms.

The 1000- μ f capacitor C-49, going from tap 5 to tap 8 of T-4, the horizontal output transformer, has been replaced by a direct connection. The value of R-73, connected to pin 2 of the horizontal phase detector, has been changed from 4700 ohms to 10,000 ohms.

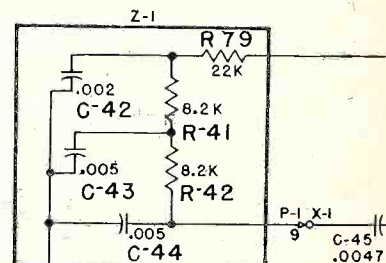The 22,000-ohm resistor, R-79, connected from pin 3 of the sync amplifier-splitter to pin 9 of socket X-1 is now included in Z-1 which is shown in the accompanying diagram.



Circuit changes in National Models.

Connection P-1 X-1 is now located as shown in the accompanying diagram, and pin of the sync amplifier-splitter is connected directly to the 22,000-ohm resistor of Z-1. The value of C-43 has been changed from 0.002 μ f to 0.005 μ f.

Crosley 1951 Models

To reduce hum or buzz, make certain that electrolytic capacitor C120 has a good ground connection by soldering a wire from the chassis to one of the ground lugs on the capacitor. This should be done on all sets contacted in the field to prevent trouble developing as the set ages. Later production sets have the capacitor grounded in this manner. Make certain that the sections of this electrolytic capacitor are properly connected as shown by the schematic. If the shield in back of the contrast control has been removed, be sure to replace it. On sets equipped with a resistor-capacitor unit (Part No. W-149881), dress the coupling capacitor C122 as far as possible away from the resistor-capacitor unit. If necessary, remove resistor R141. Adjust the ratio-detector transformer (T102) secondary for minimum hum or buzz, while the set is tuned to the station. Only a slight adjustment is required. If the screw is turned too far, the result may be weak or distorted audio output. Check over-all alignment.

To retard the accumulation of dust collecting on the glass area behind the metal bell of 16" and 19" (metal picture) tubes, this area was sprayed with silicon lacquer. In some cases this lacquer was hygroscopic, permitting moisture to be absorbed which resulted in corona on the glass portion of the tube, or arcing. When this condition is experienced, thoroughly clean all the silicon lacquer from the tube with acetone.

Motorola Ch. TS-67A

The TS-67A differs from the TS-67 in several tube types and tube functions. A 6AG5 sync segregator was added to replace the sync clipper V-6B (1/2 6AL5). The latter became the first of a new two-stage agc circuit. The second stage is a 6AU6 which replaces the 12AX7 of the TS-67. In addition, a sensitivity control was added to the agc circuit. The control, located on the top of the chassis, permits the agc to be pre-set at the desired level. The function of V-15A (1/2 6SN7GT) was changed from a squelch diode to a pulse shaper. The chassis contains 24 tubes plus a 19" picture tube.

Information on the TS-67 apply to television chassis TS-67A with the following addition:

Sensitivity Control

The sensitivity control determines the level of the agc curve and is adjusted as follows:

1. Turn receiver to channel on which the strongest signal is received.

2. Turn sensitivity control until the video amplifier overloads (picture starts to tear), and then back off until the picture is stable. The sensitivity control is located on approximately top center of chassis.

3. The audio should also be checked during this adjustment. Although there may be no evidence of tearing in the picture after step 2, the signal may still be strong enough to cause sync buzz. If this is the case, back off the sensitivity control until sync buzz disappears.

Alignment

The alignment procedure for chassis TS-67A is the same as that for TS-67, with the following exceptions:

4.5 Mc Trap Alignment

In step 1. Connect the signal generator to

the grid, pin 2 or 5, of the 2nd video amplifier tube V-8 (6AS5).

In step 2. Remove the agc tube V-10 (6AU6).

In step 3. Connect 3 volts of battery bias between the plate, pin 5, of the agc tube V-10 (6AU6) and ground. The positive terminal of the battery is on the plate.

In step 8. Connect an oscilloscope between chassis and the plate, pin 5, of the 1st video amplifier V-7 (6BA6).

The following parts should be added to the parts list. For components not mentioned here, refer to TS-67 Replacement Parts List.

Ref. No.	Part No.	Description
C-6	21R2748	Mica, 220 μ f, 300v
C-14	20A18355	Trimmer, mica, 1.3-15 μ f
C-31	21K700671	Ceramic, 1.5 μ f, 500v (temp comp)
C-36, 68, 69, 72	21K77373	Ceramic, 47 μ f 500v
C-38	21K470329	Ceramic, 30 μ f 500v
C-65, 71	21R6642	Mica, 68 μ f 500v
C-107	23A790904	Electrolytic, 50 μ f 25v
C-129, 130	8R9854	Paper, 0.1 μ f 200v
C-132	23K700624	Electrolytic, 1 section; 140 μ f, 150v
C-133	8R9856	Paper, 0.25 μ f 200v
C-134, 140	8R9874	Paper, 0.1 μ f 600v
C-135	21K792438	Ceramic, 100 μ f 3000v
C-136	8R9867	Paper, 0.002 μ f 600v
C-137	8R9834	Paper, 0.01 μ f 600v
C-138	8R9870	Paper, 0.01 μ f 600v
C-139	8R9867	Paper, 0.002 μ f 600v
C-141	21R6554	Mica, 100 μ f
R-2	6R3949	470, 20%, 1/2w
R-13	6R2013	27,000, 10%, 2w
R-18	6R6117	5600, 10%, 1/2w
R-35	6R6432	270, 10%, 1/2w
R-52	6R5660	180, 10%, 1/2w
R-97	6R2004	8200, 10%, 1/2w
R-100	6R6969	2200, 10%, 1/2w
R-101	6R6229	1000, 10%, 1/2w
R-104	6R6487	39,000, 10%, 1/2w
R-105	6R5697	560,000, 10%, 1/2w
R-111	6R5621	10, 10%, 1/2w
R-115	6R6299	10,000, 10%, 2w
R-120, 121	6R6004	1 megohm, 20%, 1/2w
100,000, 20%, 1/2w		
	R-122	6R6075

R-123	6R6056	47,000, 20%, 1/2w
R-124	6R2029	3300, 10%, 2w
R-125, 135	6R5631	120,000, 10%, 1/2w
R-126	18K700626	Sensitivity control, 2000 ohms
R-127	6R2098	22,000, 10%, 2w
R-128	6R6032	470,000, 20%, 1/2w
R-129	17K700623	Wire wound, 10,000, 10%, 5w
R-130	6R6080	4700, 10%, 1/2w
R-131	6R6320	10,000, 10%, 1/2w
R-132	6R6407	220,000, 10%, 1/2w
R-133	6R6429	820,000, 10%, 1/2w
R-134	6R6497	3.3 megohm, 10%, 1/2w
T-9	25C792563	Power Transformer (optional to 25K792564)

Part No.	Description
35A792756	Cushion, focus coil
14K700013	Insulator, high-voltage: small (on high voltage compartment shield)
13D792141	Mask, picture tube: rubber (for 19AP4 only)
13K700678	Mask, picture tube: rubber (for 19AP4A only)
2S7048	Nut, hex: 10-32 x 5/16 stl; cad pl (25K792564 power transformer mtg)
2S7003	Nut, hex: 8-32 x 5/16 stl; cad pl (25C792563 power transformer mtg)
5S7720	Rivet: .088 x 1/8 stl; pol nkl (sensitivity control mounting)
9K700041	Socket, picture tube: 5-pin; with leads
9A780011	Socket, tube: miniature 7-prong (V-10 and V-25)
31A791402	Strip, terminal: 6 ins, #4 gnd; 3/8" spacing
31K4573	Strip, terminal: 3 ins, #3 gnd; 1/2" spacing
31K31217	Strip, terminal: 1 ins, #2 gnd; 3/8" spacing
9K484579	Wafer, electrolytic mtg: cad pl
4K74579	Washer, fibre (R-91 mtg)
1X792530	Lead, phono: with plugs
1X600118	Lead, phono motor: with receptacle and plug
28K71775	Plug, 1-pin: insulated; 3/8" (short plug on phono lead)
28K22183	Plug, 1-pin: insulated; 15/16" (long plug on phono lead)
28K30736	Plug, 3-pin: 9/16" pins (on phono motor lead)
9A600040	Receptacle, plug: 0.640 diameter, 5/16" contacts (phono motor receptacle)
15K74443	Shell, receptacle: with insulator (on phono motor lead)
15A690616	Shell, receptacle: 3/8" diameter; with insulator on phono motor leads)

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED . . . AT YOUR SUGGESTION


Here is the custom-built AM-FM chassis that means BIGGER PROFITS for you!

The NEW ESPEY model 511-B FEATURES

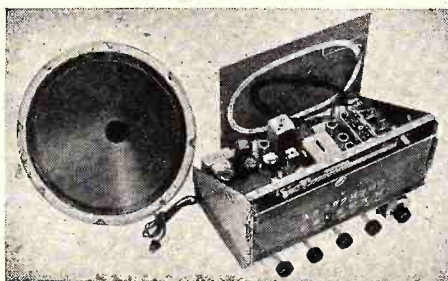1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY
TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.



SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

RIDER MANUALS

NEW ENGLAND TELEVISION CO.

ELECTRONIC RESEARCH LABORATORIES

544 SIXTH STREET • NEW YORK 9, N. Y.

November 21, 1950

Mr. Schlenger
John F. Rider, Publisher Inc.
480 Canal Street
New York 13, N.Y.

Dear Mr. Schlenger:

We have just completely overhauled and repaired approximately 200 old television sets of various manufacturer's in record time with excellent results. As these television sets were all "trade-ins" on late model sets and several years old, a large number of them had component's with wrong value's (obviously due to previous repairs) or had parts completely missing.

I wish to state that everyone of these television sets were put in working order with the aid of Rider's Television Manuals, furthermore, as a Television engineer, I cannot help but admire the fact that regardless of what chassis we picked up next we had but to look in Rider's Manuals to find the proper schematic.

It may be a bit early for holiday greetings but we sincerely wish you and everyone connected with John F. Rider "A MERRY CHRISTMAS AND A HAPPY NEW YEAR."

Very truly yours,

NEW ENGLAND TELEVISION CO.

Joseph Fromer

Joseph Fromer

jf:mf

Proven BEST by TEST

and here are the reasons **WHY!**

Because when you work with **RIDER TV MANUALS . . .**

➔ You possess the same information which the original receiver manufacturer uses. This means **accuracy, authenticity, and completeness of detail**. NOBODY — BUT NOBODY ELSE — can make this statement!

➔ You have at your fingertips descriptions of the circuit action. The five Rider TV Manuals contain **731 pages of such extremely valuable instructional information**. It is like a teacher telling you how the circuit functions. NOBODY — BUT NOBODY ELSE — furnishes this much of this kind of data necessary for successful and profitable TV servicing!

➔ You have at your fingertips **337 pages of official, accurate, unpacking and installation data**. NOBODY — BUT NOBODY ELSE — gives this much of this kind of time-saving, money-making TV servicing data.

➔ You have at your fingertips **293 pages of signal waveforms** — so vital to rapid trouble diagnosis of picture i.f., sound i.f., video, sync and sweep circuits. NOBODY — BUT NOBODY ELSE — even remotely approaches this much of this kind of time-saving and money-making TV servicing information!

➔ You have at your fingertips the most **complete coverage** of the TV receiver manufacturers' output — the pilot models and all the changes — from the very beginning. NOBODY — BUT NOBODY ELSE — who sells service data can make this statement!

➔ Compare the completeness of Rider TV Manuals with any other service and you will see why they are the **Best by Test** — why they are the most economical to buy in the long run and, most popular with all competent TV servicemen. Make your Rider TV Manual Library complete! Get the missing copies today.

In TELEVISION
5 RIDER TV MANUALS
 ★ **10,544 Pages***
 ★ **1,849 Models**

* Equivalent of 8½ x 11 ins. size

RIDER P.A. MANUAL
 ★ **2,024 Pages**
 ★ **1,285 Models**

In AM-FM-Auto Radio-Phono
21 RIDER MANUALS
 ★ **31,382 Pages**
 ★ **28,341 Models**

Complete your Rider Manual Library today... Get them from your Jobber

RIDER MANUAL VOLUME XXI (21) — Out this Month
RIDER TV MANUAL VOL. 6 — Out in March — TV7 Soon After

TV ANTENNA "TRIO"

We now have available a TV Antenna Trio—3 textbooks pertaining to television antennas, namely, TV AND OTHER RECEIVING ANTENNAS, TV INSTALLATION TECHNIQUES, and TV MASTER ANTENNA SYSTEMS—a "trio" relating to TV receiving antennas and offering to the industry a complete story on the subject. Bailey's TV AND OTHER RECEIVING ANTENNAS presents the theory; Marshall's TV INSTALLATION TECHNIQUES takes care of the problems of installation, both electrical and mechanical; and the Kamen-Dorf TV MASTER ANTENNA SYSTEMS furnishes the necessary information on this rapidly expanding phase of TV installation. An interesting side light on all of these books is that all of the authors have had an intimate association with the subject matter they treat: Bailey has designed antennas for 21 years, Marshall has taught TV installations courses and has done installation work, and Kamen and Dorf actually installed every one of the master antenna systems which they describe, which, incidentally, embraces all those available on the market.

Majestic 12T6, 14C4, 14T2, 14T6, 16C6, Series 94

Except for cabinet designs or picture tube size, Models 12T6, 14T2, and 14T6 are the same as Model 12T2, Model 14C4 is the same as Model 12C4, and Model 16C6 is the same as 16C4.

Crosley 1950 Models

To reduce carrier hum at high contrast, on some sets C122 was changed from 100 μ f, 500 v (Part No. C-137727-108), to 47 μ f, 500 v (Part No. 137727-112. R134 was changed from 220,000 ohms $\frac{1}{2}$ w (Part No. 39373-80), to 47,000 ohms, $\frac{1}{2}$ w (Part No. 39373-67). R138 was changed from 56,000 ohms, 10%, 1 w (Part No. 39374-134) to 27,000 ohms, 10%, 1 w (Part No. 39374-130).

This change will not show any great effect if the transmitting station is at fault, or the receiver is improperly aligned, or when receiver is operated at normal setting of the contrast control.

INDEX OF CHANGES

Model	Page Number
Successful Servicing	Rider Manual†
	From To

TELEVISION CHANGES

Associated Merchants
12T1, 12T2, 12T3,
120C1, 120C2,

120C3, 160C1, 160C2, 160C3, Bendix 2025, 3033, 6002	2	4-1	4-8
Associated Merchants 114C, 114T, 116C, 116CD, 16RCT Bendix 2051, 3051, 6001, 6003, 6100	11	5-1	5-11
Automatic P-490, TV-707, TV-709, TV-710, TV-712, TVX313, TVX404, Ch. AR- TV-709 Ch. AR-TV-709	18	2-1 *2-1, 2, 3 3-1	—
Bendix 2025, 3033, 6002 2051, 3051, 6001, 6003, 6100	11	4-1	4-8
Capehart-Farnsworth CX-33	11, 18	5-1	5-11
Crosley 10-414MU, 10-416MU, 10- 416MU, 10-429MU	2	5-37	5-41
Crosley 1950 Models	24		
Crosley 1951 Models	21		
Emerson 66B, 86B; 611, Ch. 87B	11	2-2 *2-4	—
Gamble-Skogmo 05TV1- 43-8940B, 05TV1- 43-9002B 94TV1-43-8940A 05TV1-43-9002A	20	4-21 Page 2 of Aug. issue of Successful Servicing	4-25
Garod 12T6, 14C4, 14T2, 14T6, 16C6, Series 94 12T2, 12C4, 16C4	11	5-1	5-14
Majestic 12T6, 14C4, 14T2, 14T6, 16C6, Series 94 12T2, 12C4, 16C4, Series 94	24	5-1	5-11
Majestic 14CT4, 16CT5, 19C6, 19C7, 16T1, 16T2, 16T3, 16T4, 16T5, 1900, 1974, 1975, 97 & 98 Series 2, 6, 10 94 & 97 Series	5-1	5-14	
Mars Dartmouth, Hampton, Oriental, Versailles, Ch. K-2	2	2-1 *2-1 5-2	2-4 *2-7, 8 —
Motorola Ch. TS-67A National TV-1601, TV-1602, TV-1625, TV-1627 TV-1601, TV-1625	21 20	5-22	5-33, 34
Philco 10", 12", 16" Models	18	5-3	5-12
Wilcox-Gay G306, G402, G403, G404, G426, G427, G624, G914 Majestic 12T2, 12C4, 16C4 Majestic 1674, 1974	2 5-1 5-12	5-11 5-14	

RADIO CHANGES

Capehart-Farnsworth P777	16	Rcd. Ch. 20-16	20-19
Farnsworth P71, P72, P73; Capehart-Farnsworth P77, P777	16	Rcd. Ch. 19-1 Rcd. Ch. 18-1	19-10 18-9
Farnsworth P71 Farnsworth P72, P73 Capehart-Farnsworth P77, P777	16	Rcd. Ch. 20-16	20-19
General Electric 64, 65	16	20-3	20-8
RCA Ch. RC-1065C, RC-1065D	16	18-45 C21-8	18-46 —

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

BOOKS FOR THE SERVICEMAN

TV Master Antenna Systems. 368 pages	\$5.00
Receiving Tube Substitution Guide Book. 224 pages	\$2.40
Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses. 992 pages	\$9.00
TV and Other Receiving Antennas (Theory and Practice). 606 pages	\$6.00
TV Installation Techniques 336 pages	\$3.60
Radio Operator's License Q & A Manual. 608 pages	\$6.00
The Business Helper 134 pages	\$2.00
FM Transmission and Reception 416 pages	\$3.60
TV Picture Projection and Enlargement. 190 pages	\$3.30
Broadcast Operators Handbook 278 pages	\$3.30
Understanding Vectors and Phase 158 pages	Cloth Cover \$1.89 Paper Cover \$0.99
Inside the Vacuum Tube 420 pages	\$4.50
Understanding Microwaves 396 pages	\$6.00
Servicing by Signal Tracing 370 pages	\$4.00
The Meter at Work 160 pages	\$2.00
Installation and Servicing of Low Power Public Address Systems 208 pages	\$1.89
A-C Calculation Charts 148 nomographs in 3 colors 168 pages	\$7.50
High Frequency Measuring Tech- niques Using Transmission Lines. 62 pages	\$1.50
The Oscillator at Work 254 pages	\$2.50
Automatic Frequency Control Systems. 154 Pages	\$1.75
Radar — What It Is 80 pages	\$1.00
Radio Amateur's Beam Pointer Guide. 32 pages	\$1.00
Master Index-Volume I to XV	\$1.50

Order Your Copy Now


JOHN F. RIDER PUBLISHER, Inc.

DOUGLASSON, L. I., NEW YORK
5310 OVERBROOK ST.
A. J. S. CERINO

PERMIT NO. 9427
NEW YORK, N. Y.
PAID
U. S. POSTAGE
Sec. 34.66, P. L. & R.

Return Postage Guaranteed
480 CANAL ST., NEW YORK 13, N. Y.
JOHN F. RIDER PUBLISHER, Inc.
From

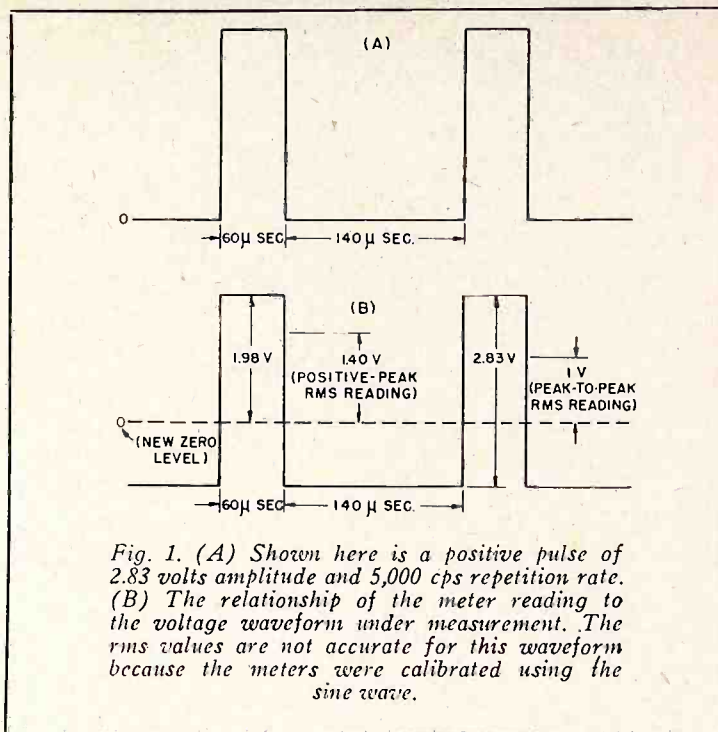PULSE MEASUREMENT WITH VACUUM-TUBE VOLTMETERS



THE use of pulse signals for synchronization in television reception, in microwave and radar applications, and in industrial and scientific analysis calls for new techniques in voltage measurement. Vacuum-tube voltmeters are admirably suited for this work because of their fast response and freedom from lag, high input impedance, range flexibility, and low loss characteristics. The application of VTVM's for pulse measurements will be discussed here. The use of the slide-back v-t voltmeter for pulse measurements was covered in Chapter 7.

The most useful v-t voltmeters for pulse measurements are those having peak-to-peak response. Although the dials of these meters are generally calibrated to give rms values (for sine waves), they can be converted to give the peak values of the pulse being measured with relative ease. For example, to find the value of the pulse signal shown in

Fig. 1A, which is a positive pulse of 2.83 volts with a repetition rate of 5,000 cycles per second, we need to remember that a positive-peak-response meter, calibrated to read in rms volts, gives the positive peak divided by 1.414. Similarly, the peak-to-peak-response meter calibrated for rms readings gives the peak-to-peak reading divided by 2.83. However, because the input to v-t voltmeters is capacitance coupled, the d-c component is removed, leading to a displacement of the zero level as shown in Fig. 1B. This does not affect the reading of the peak-to-peak voltmeter since it responds to the difference between the positive and negative peaks and not between the zero level and the positive peak as does the positive-peak-response meter.

To obtain the total amplitude of the pulse therefore, using the peak-to-peak voltmeter, it is only necessary to multiply the rms reading on the meter by 2.83. For the positive-peak

meter however, we must consider the displacement of the zero level. To obtain the total amplitude of the pulse on such a meter, we must first find the positive pulse amplitude, then the negative pulse amplitude, and, finally, the sum of the two. For the example given (60 μsec pulse with 140 μsec interval between pulses), and by referring to Fig. 1B, we find that the positive amplitude is:

$$1.40 \times 1.44 = 1.98 \text{ volts.}$$

To find the negative peak we use the simple proportion: the pulse duration divided by the interval between pulses (both in similar time units) is equal to the negative peak value (unknown) divided by the positive peak value. For example:

$$\frac{60 \mu\text{sec}}{140 \mu\text{sec}} = \frac{\text{Negative Peak Value}}{1.98 \text{ volts}}$$

with the result that:

$$\text{Negative Peak Value} = \frac{60 \mu\text{sec}}{140 \mu\text{sec}} \times 1.98 \text{ v}$$


$$\text{Negative Peak Value} = 0.85 \text{ volt.}$$

Therefore, the total amplitude of the pulse is:

$$1.98 + 0.85 = 2.83 \text{ volts.}$$

Similarly, when measuring negative pulses allowance must be made for the rms calibration of the meter as well as for the characteristics of the meter itself. By this we mean the response of the meter, whether peak-to-peak or positive peak, and the capacitance-coupling effect. For example, in measuring the negative pulse shown in Fig. 2A, a positive-peak-response meter gives 0.5 volt, which is the positive-peak amplitude divided by 1.414.

(Continued on page 10)

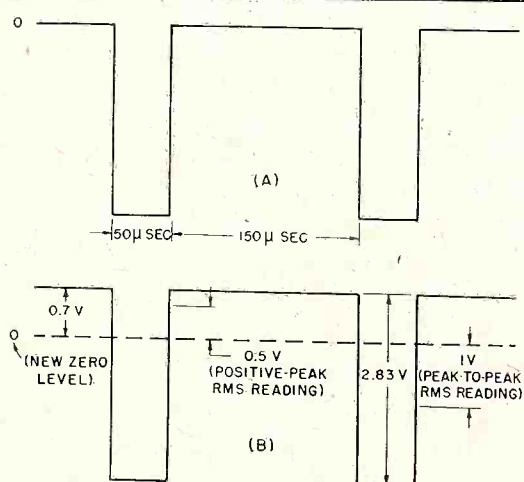

Editor's Note: This article is an abridgement of the section on pulse measurements appearing in chapter 12, entitled "Applications of Vacuum Tube Voltmeters," from VACUUM-TUBE VOLTMETERS, a book to be published soon by John F. Rider Publisher, Inc. This book is a revision of the former book VACUUM-TUBE VOLTMETERS by John F. Rider.

Television Changes

DuMont Savoy, Winthrop, Ch. RA-103C; Wellington, Ch. RA-104A

The Winthrop model uses chassis RA-103C and is identical to the Savoy except for the cabinet. The a-m tuners used in these models are similar to that which is used with RA-103 except for the differences mentioned below. The accompanying diagram shows bottom view of the Wellington tuner, Chassis RA-104-A3.

Capacitor C419, has been deleted and a 0.005- μ f capacitor C423 has been added in its place. The following table gives the resistance measurements (all readings to ground). An RCA Model 195-A VoltOhmyst was used.

Tube	V401	V402	V403	V404	V405	V406
1	2M	20K	1.5M	0	0	Nc
2	0	0.5	0	10M	0	Inf
3	0	0	0	0	Inf	Inf
4	.05	.05	.05	600K	Inf	109
5	Inf	Inf	Inf	600K	470K	Inf
6	Inf	Inf	Inf	Inf	Nc	116
7	0	1.5M	0	.05	.05	Nc
8				0	220	Inf

All readings in ohms, K = thousand, M = million.


The resistance readings of the coils are as follows. All readings are in ohms and were taken with coils disconnected.

Ref. No.	Resistance	
	Pri.	Sec.
L401	8.0	
L402	40.0	9.0
L403	.5	5.0
Z401	13.0	12.5
Z402	13.0	12.5
T401	5.5	200.0

The parts list is the same as that for the tuner in the RA-103 except for the following changes:

A-m Tuner RA-104-A3 Wellington

Ref. No.	Part No.	Description
C401	03018551	Capacitor, variable, 3 sections
C403	03012730	Capacitor, ceramic, 47 μ f, 10%, 500 v
C416, C417	03018570	Capacitor, fixed, paper, 0.02 μ f, 20%, 600 v
C419	Delete	
C423	03001570	Capacitor, paper, 0.005 μ f, 25%, 600 v
J403	09015921	Connector Asy
P402	09006472	Connector Asy
R422	01007070	Resistor, variable, 1 megohm, 20%, 1/4 w
S401	05003821	Switch a-m tuner.

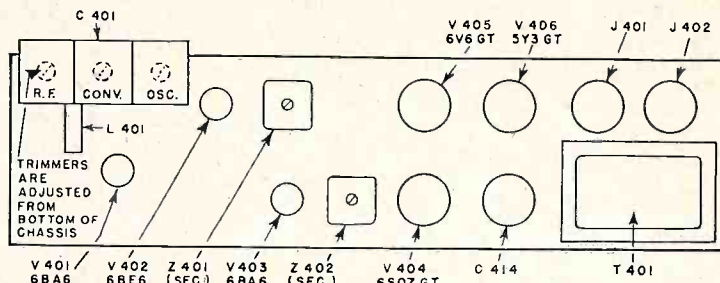

Bottom view of the DuMont Wellington tuner, Chassis RA-104-A3.

The parts list for the Savoy and Winthrop tuners are the same as for the Wellington except for the following:

A-M Tuner RA-103A

Ref. No.	Part No.	Description
C401	3C-12714	Capacitor, variable, 3 section
C419	3-1439	Capacitor, fixed, ceramic, 330 μ f, 20%, 350 v
J403	9-486	Connector, asy., female, 2 contact
P402	9-501	Cable asy., male, 2 contact
S401	5C-12914	Switch.

A-M Tuner RA-103C

Ref. No.	Part No.	Description
C401	3C-12714	Capacitor, variable, 3 section
J403	9A-13516	Connector asy
P402	9B-13514	Connector asy
S401	05003251	Switch.

Meck Service Hints

Failure of the 1X2 high-voltage rectifier is directly due to a variation of current demand of individual cathode-ray tubes. The operating potential of the 1X2 tube can be lowered by grounding the high-voltage filter capacitor. At the time of replacing a 1X2 with an open filament, remove the black lead from pin 5 (plate) of the 6W4 socket. This lead which ties to the base of the high-voltage capacitor should then be grounded on the 6W4 socket.

The TT-10006 tuner depends upon a variable inductance for its correct operation. This variable inductance unit consists of the carriage, mounted on top of the tuner, the stator coil assembly, and the rotor plate assembly. The carriage is the "U" shaped bracket which holds the copper rotor plate assembly and the rotor shaft. The stator coil assembly consists of six printed coils which are molded on linen bakelite strips. The center of each printed coil is terminated in a tinned eyelet which extends through the linen bakelite.

The tuner manufacturer used tinned dipped eyelets for this coil center; however, a small quantity of electro-tinned eyelets were inadvertently used in one production run of the tuners. Higher temperatures are required to flow solder on electro-tinned eyelets than on the dipped tinned eyelets.

Tuners in which this bond between the coil center and the eyelet is intermittent, can be

repaired with a small soldering iron with the tip turned down and filed into the shape of a small screw-driver blade. Run one-quarter inch of solder, a type that has a very small diameter, down the screw-driver blade to the eyelet. This operation should be done with the rotor blades turned out as far as possible, and should be necessary only for the oscillator and mixer coils. It is unnecessary to remove the tuner from the television chassis to carry out this soldering operation; however, with the round tube models, it may be necessary to bend the point of the iron at a right angle in order to place the tip of the iron in the correct position.

If, after soldering, arcing occurs between the rotor plates, spring the rotor plates slightly away from the coil. Springing of this rotor plate slightly will not alter the operation of the tuner unit.

The above operation should be used only in those tuners exhibiting intermittent qualities or those tuners exhibiting insensitivity of either high or low bands.

A defective receiving tube in this tuner unit can also account for this intermittent condition.

DuMont RA-105, RA-106


To reduce flicker the following changes have been made in the RA-105, RA-106 main chassis. The flicker referred to results from periodic line voltage fluctuations such as are produced by reciprocating pumps and like devices. This change is sometimes referred to as an "anti-flicker circuit."

Pins 6 and 7 on V206-B, the d-c restorer tube, are removed from ground. Pins 6 and 7 on V206-B are connected together and a lead is run from pin 6 of V206-B to pin 8 of V207, thus returning the d-c restorer to the cathode of the third video amplifier instead of to ground. Capacitor C224 is changed from 0.1 μ f, 200 volts, $\pm 25\%$, to 0.5 μ f, 400 volts, $\pm 25\%$. The part number of the new capacitor is 03014260. Capacitor C224 is connected between pin 11 of the cathode-ray tube and the junction of R235 and C220A. Resistor R347, 470 ohms, 1 watt, 10% (part number 02034730) is connected in series between R232 and R321.

Erratum


The following corrections should be made on page 57 of the RECEIVING TUBE SUBSTITUTION GUIDE BOOK under the section dealing with the 6A7 tube: Under the column headed Substitution, the 7J8 should be changed to read 7J7. Under the column headed Circuit Changes Necessary, cap to 6 should be added. The schematic of the original tube socket should have a grip cap.

LESS TENSION

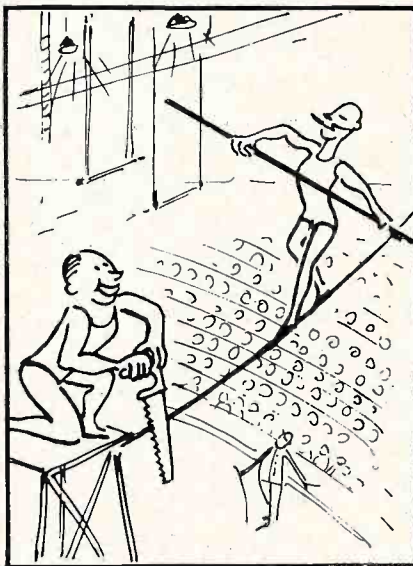

Metal or mental tension — servicemen relieve both by using Ersin MULTICORE Solder — the original 3-core solder and the only solder in the world made with non-corrosive, extra-active Ersin Flux. Wets metals faster! Melts rapidly! Works on difficult metals and on oxidized parts! Saves your time and secures your reputation. Write for FREE SAMPLE — Multicore Sales Corp., Dep't S., 164 Duane St., New York 13, N. Y.

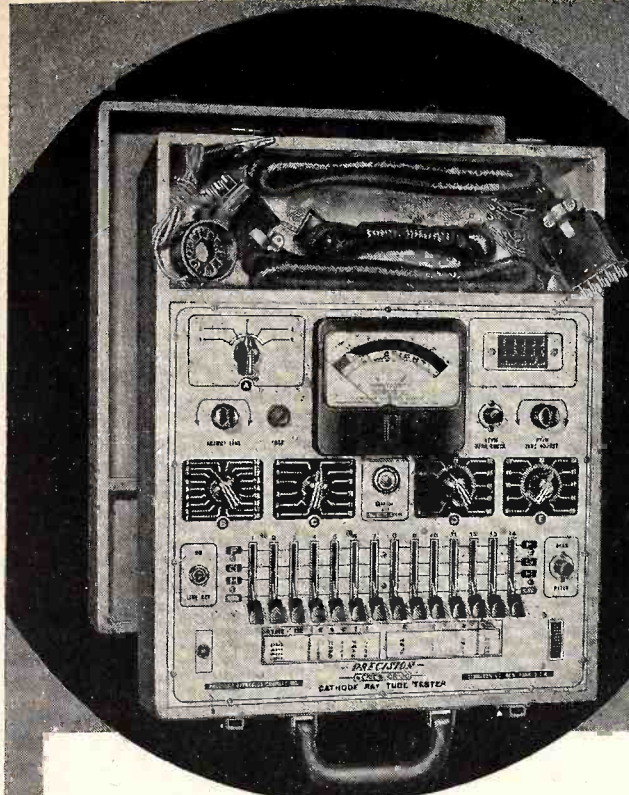Please mention Successful Servicing when answering advertising.



THE NEW PRECISION CR-30 CATHODE RAY TUBE TESTER

TESTS ALL TV PICTURE TUBES
(MAGNETIC AND ELECTROSTATIC)
'SCOPE TUBES AND INDUSTRIAL CR TYPES
for True Beam Current (Proportionate Picture Brightness)
Tests ALL CR Tube Elements—Not Just a Limited Few



IN FIELD OR SHOP
Tests CR Picture Tubes
Without Removal from
TV Set or Carton!

The new Precision CR-30 fills an obvious gap in the test equipment facilities employed by TV service and installation technicians.

Because of the absence of a reliable cathode ray tube tester, up to 50% of so-called "rejected tubes" are found to be fully serviceable and should rightfully never have been "pulled out."

Proven product of extended development, the CR-30 has been

specifically engineered to answer the question, "Is It the TV Set or is it the Picture Tube?"

The Precision CR-30, a complete and self-contained Electronic Instrument, incorporates a TRUE BEAM CURRENT Test Circuit. The CR-30 checks overall electron-gun performance for proportionate picture brightness as well as additional direct testing facilities for accelerating anodes and deflection plate elements.

The Precision CR-30 should not be confused with mere adapters connecting to ordinary receiving tube testers which were never designed to meet the very specialized needs of CR tube checking. Similarly, it is not to be confused with neon-lamp units or similar devices of limited technical merit and which do not check all CR tubes or all tube elements.

GENERAL AND TECHNICAL SPECIFICATIONS

- ★ Tests All Modern Cathode Ray Tubes—Magnetic and Electrostatic, 'Scope Tubes and Industrial Types.
- ★ Tests All CR Tube Elements—Not just a limited few.
- ★ Absolute Free-Point 14 Lever Element Selection System, independent of multiple base pin and floating element terminations, for Short-Check, Leakage Testing and Quality Tests. Affords maximum anti-obsolescence insurance.
- ★ True Beam Current Test Circuit checks all CR Tubes with Electron-gun in operation. It is the Electron Beam (and NOT total cathode emission) which traces the pictures or pattern on the face of the CR tube.

Total cathode emission can be very high and yet Beam Current (and picture brightness) unacceptably low. The CR-30 will reject such tubes because it is a true Beam Current tester. Conversely, total cathode emission can be low and yet Beam Current (and picture brightness) perfectly acceptable. The CR-30 will properly pass such tubes because it is a true Beam Current tester. The significance of the above rests in the fact that Beam Current (and picture brightness) is primarily associated with the condition of the center of the cathode surface and not the overall cathode area. (See illustration below)



- ★ Voltage Regulated, Bridge Type VTVM provides the heart of the super-sensitive tube quality test circuit. Such high sensitivity is also required for positive check of very low current anodes and deflection plates.
- ★ Micro-Line Voltage Adjustment
Meter-monitored at filament supply.
- ★ Accuracy of test circuits closely maintained by use of factory adjusted internal calibrating controls; plastic insulated, telephone type cabled wiring; highest quality, conservatively rated components.
- ★ Built In, High Speed, Roller Tube Chart.
- ★ Test Circuits Transformer Isolated from Power Line.
- ★ 4 5/8" Full Vision Meter with scale-plate especially designed for CR tube testing requirements.
- ★ Heavy Gauge Aluminum Panel etched and anodized.
- ★ PLUS many other "PRECISION" details and features.

SERIES CR-30—In hardwood, tapered portable case, with hinged removable cover. Extra-Wide Tool and Test Cable Compartment. Overall Dimensions 17 1/4 x 13 3/4 x 6 3/4". Complete with standard picture tube cable, universal CR Tube Test Cable and detailed Instruction Manual.

Shipping Weight:—22 lbs. Code: Daisy
NET PRICE:—\$99.75

See the new CR-30 on display at leading electronic equipment distributors. Place your orders now to assure earliest possible delivery.



PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York
Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

You wouldn't buy a business blindfolded!

Of course not. But a survey of hundreds of servicemen found that 57% order capacitors simply by rating, without specifying a brand. Don't forget you are staking your business reputation on the performance of the parts you use!



Make Sure! Make it Mallory!

Better performance, longer life, fewer comebacks. That is what you want in a capacitor. That is why so many servicemen swear by Mallory.

Mallory produced the first dry electrolytic capacitors—has led the way in major developments, resulting in longer life, reduced sizes, standardized mounting, and resistance to heat. *Every* Mallory FP is designed for trouble-free service at 185°F.

MALLORY PLASCAP




The plastic tubular specifically designed to meet your field service problems. Available in a complete range of ratings.

Mallory scored another first with the Plascap* plastic tubular capacitor. It is ruggedly molded and securely sealed to prevent leakage and shorting . . . has permanently fastened leads, clearly identified . . . stands up under high temperatures.

Don't just order capacitors. Order Mallory! Don't be satisfied with less than the best. It costs you no more to get the quality and performance that have made Mallory the first choice of leading equipment manufacturers.

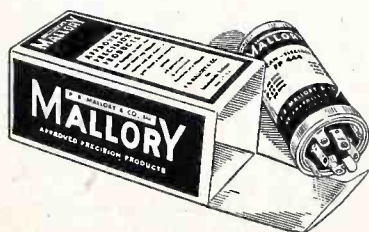Depend on your Mallory Distributor for precision quality at competitive prices.



*Trade Mark

P. R. MALLORY & CO. Inc. MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

FEBRUARY, 1951

No. 4

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
E. H. BEAUMONT, Associate Editor

WOrth 4-8340
WOrth 4-8341



Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher

CURTAIN TIME

TV Color

It is almost a certainty that the issue of color TV for the public is dead for the duration. As we see it, this means for quite a few years, although it is reasonable to suppose that some research will be carried on in connection with color television for Armed Forces activities. At the same time it makes sense to assume that rotating wheels will not be viewed with favor in Military or Naval installations where space and weight always are premium items.

As we have said once before, we are not concerned with who develops the final color system or whether it is the product of many brains from many different laboratories, but it is a certainty that when it does appear it is going to be all-electronic. If the technological advances made during the last war, are an indication, advances which gave birth to an acceptable television system in 1946 as demonstrated by the public's reaction during the four years which followed, it is safe to say that advance in research in connection with defense needs during the next few years will more than likely result in a completely finished color system for public use when these hectic days come to an end.

As far as the public is concerned, it is quite fickle. Their interest in color was strong

when the discussion was rampant, but now that shortages of all kinds are developing, the draft is being stepped up, and the defense effort is advancing rapidly, these latter items have absorbed their interest and color television is secondary in their minds. Let it be that way—"Requiescat in Pace."

Civilian Defense

This does not bear any relation to the technical phases of the radio and television industry. Much is being said about the apathetic response to civilian defense recruiting. It seems to us that a very good advertising medium is going to waste. We are referring to the test patterns which appear on TV screens. As a rule these show a station pattern, and occasionally a product advertisement on a station pattern; and when station breaks are made they similarly display the station letters and sometimes feature a forthcoming program.

It seems to us that reference to civilian defense might well become the theme of all television station break picture, test patterns, and the like. A statement as "join your local civilian defense effort" would easily fit on all patterns or station call letter announcements. Since the time devoted to these kinds of images

is not being timed except perhaps for what program advertising it may have, substituting a civilian defense pattern for a forthcoming program announcement could well prove fruitful to the civilian defense authorities in all communities located in TV areas. It would cost the station nothing to do so.

TV facilities exist in the majority of industrial areas; and it is reasonable to suppose that these regions form prime target areas, therefore civilian defense efforts in such places are extremely important. Since the population of these areas devote most of the TV hours to television viewing, television as a medium of recruiting personnel for civilian defense efforts in the industrial areas of the nation seems like a more expedient medium than radio.

Television Servicing Licensing in New York City

A new licensing bill covering television servicing in New York City has been introduced to the City Council. It arrived at our desk just as this issue was being closed. Inasmuch as the analysis of such a bill justifies more than a casual reading, we shall reserve our comments concerning it until the next issue. In a way it resembles a bill which was originally introduced in Detroit, Michigan, but never was passed because of an understanding which was reached by the television servicing industry and the City Fathers of that city. Let us hope that a similar situation will eventually develop in New York City.

JOHN F. RIDER

AS EXHIBITED AT THE-

Radio Engineering Show
Grand Central Palace

New York City

John F. Rider Publisher, Inc.
BOOTH 243

March 19-22 1951

RIDER MANUALS—NOW MORE THAN EVER!

AND SO IT SURE LOOKS AS THOUGH WE'LL ALL HAVE TO MAKE OUR OLD RADIO AND TV SETS LAST LONGER BECAUSE OF THE CURTAILMENT IN PRODUCTION!

THAT MEANS A HECK OF A LOT MORE SERVICE JOBS FOR ME - I'LL PROBABLY BE BURNING THE MIDNIGHT OIL!

I'M NOT GETTING CAUGHT SHORT - THE FIRST THING IN THE MORNING I'M CALLING MY JOBBER AND FILLING IN ON ALL MY TV - AM-FM-PA RIDER MANUALS - THEY'RE SURE TIME-SAVERS - THEY'LL BE WORTH THEIR WEIGHT IN GOLD!

WHILE SET PRODUCTION WILL BE CURTAILED DON'T CURTAIL YOUR EARNING POWER - COMPLETE YOUR SET OF RIDER MANUALS NOW! YOUR JOBBER HAS THE NEW VOLUME 21 AND ALL THE REST - RESERVE YOUR COPY OF RIDER'S TV 6 DUE IN MARCH!

It has always been the policy of John F. Rider Publisher, Inc., to keep the prices of our manuals and textbooks as low as possible and still give our customers the soundest texts with greatest coverage of the subject. We depend upon volume to make up for the low list prices.

Since January 1946, we have tried to hold the line in prices as much as possible and we have had relatively few increases in the list prices of our publications. During the year 1950, especially

since the start of the Korean situation, we have faced many serious price increases in production and labor costs. We have absorbed all of these but, since Korea especially, they have become very bad, so much so that we are forced to raise the list prices of our TV Manuals 1, 2, 3, 4, and 5. We are trying to hold the line on the regular AM and FM Rider Manuals. As much as we regret that the increase in prices is necessary— it is unavoidable and, beginning with February 1, 1951, Rider TV Man-

uals 2, 3, 4, and 5 are priced at \$24.00. TV 6, which will appear in March 1951, is priced at \$24.00. Rider TV 1 is priced at \$19.80.

We do not know how long we will be able to maintain our regular prices on the AM-FM Manuals. There are no price changes scheduled at the moment on Rider textbooks, but if the price of production continues increasing as it has for the past year, a change in those prices is imminent.


Farnsworth, Capehart 462P12, Ch.
C-267

Model 462P12 is a television console receiver using a chassis which is essentially the same as the U-12 television chassis as used in Farnsworth Model 461P with exception that a 6K6 power output tube has been added to the main chassis. Pin 5 of the 6K6 is connected to capacitor C24, the 0.005- μ f capacitor connected to the plate of V7, the 6T8 tube. A 270,000-ohm resistor is connected from pin 5 to the junction of ground and pin 8 and a 10- μ f capacitor is connected from the same junction to pin 4. Pin 4 of the 6K6 goes to terminal 1 of the speaker socket. A 0.003- μ f capacitor is connected from the plate of the 6K6 ground. Pin 3, the plate of the 6K6 also goes to terminals 2 and 3 of the speaker socket.

In addition to this change, the only other ways that this chassis differs from that of the 461P is that the a-c input to the audio amplifier A-13 and A-13 have been deleted, and a 4,700-ohm resistor has been added in parallel across R89, the 1,800-ohm cathode resistor for V22 (6V6 vertical output tube).

The cabinet used in this model is essentially the same as the 461P, with exception of the new "truncated circle" mask. The picture-tube aperture on these cabinets has been revised to accommodate the new mask. Another cabinet variation from the 461P is that the speaker panel is not hinged, since the new location of the h-v chassis (near the rear of the cabinet) permits adjustment of the secondary controls (on the h-v chassis) from the rear of the cabinet. The picture tube used in this model is the Farnsworth type "125" (12½ inch).

In current production of this model, the h-v supply chassis C-271 will be used. The C-271 chassis is electrically the same as the h-v supply C-263, used in the 461P. The only variation is that the power cable, deflection cable and the anode connector cable have all been shortened. This was brought about by the new mounting position of the h-v chassis in the cabinet. The chassis is located near the rear of the cabinet (looking at the cabinet back) in the lower right hand corner. Later production of this model will replace the

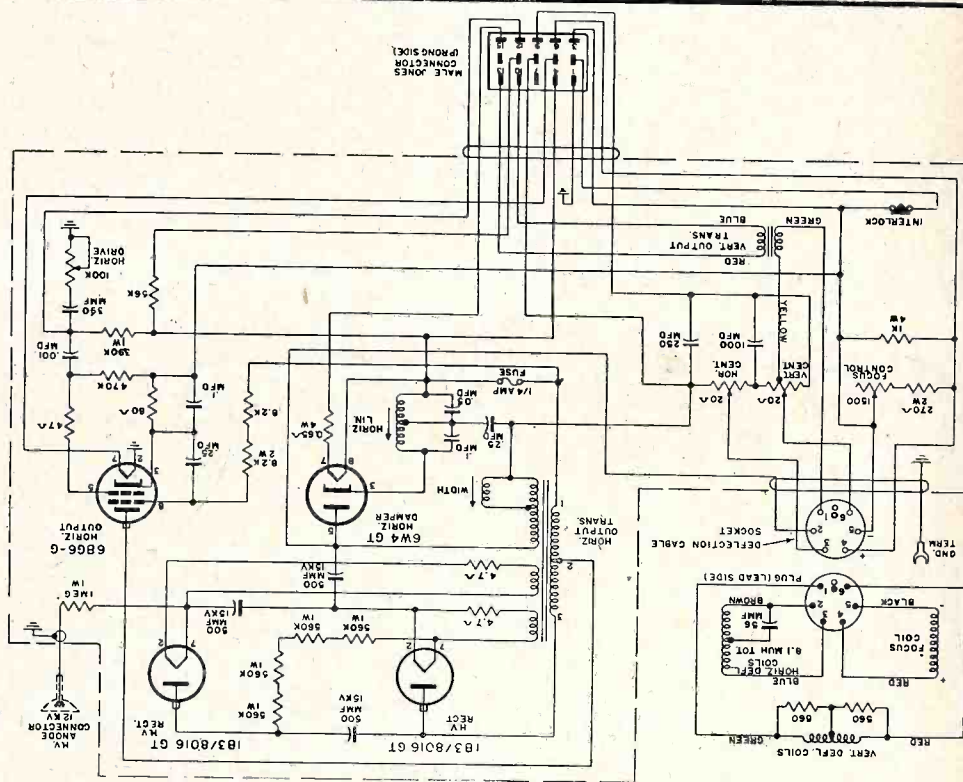

High-voltage Chassis C-266 used in Capehart-Farnsworth Model 462P12.

C-271 h-v chassis with the new h-v chassis C-266, which is shown in Fig. 1.

The focus coil used in the 462P12 is a combination p-m and electromagnetic coil (part No. 650001A-2) in which the p-m section has been partially demagnetized. These coils will be stamped in red with the letter "D" to identify them as demagnetized. Other new parts in the 462P12 are:

Part No.	Description
850044B	Plastic truncated aperture mask
750059B	Safety escutcheon glass.

**Wilcox-Gay G-414, G-614, G-624,
G-914, Series 97 & 98**

Wilcox-Gay Models G-414 and G-614 are the same as Majestic Models 14CT4 and 16CT4, respectively. Wilcox-Gay Models G-624 and G-914 are the same as Majestic Models 1674 and 1974, respectively. All data and change notices on the above mentioned Majestic Models also apply to the Wilcox-Gay Models.

Capehart-Farnsworth CX-33

The following component changes have been made in current production of these chassis:

1. C-253 has been changed from 0.0047 μ f to 0.001 μ f, and R-282 has been changed from 560,000 ohms to 100,000 ohms. This change was made to improve phasing in the horizontal afc circuit.
2. R-268 has been changed from 100,000 ohms to 47,000 ohms to improve the operation of the vertical hold control.
3. C-261, the h-v filter capacitor, incorrectly shown on the schematics as being connected to pin 2 of the 1B3GT/8016 h-v rectifier, should be shown connected to pin 7 of this tube.
4. C-257 has been changed from 0.001 μ f to 0.0047 μ f.
5. R-272 has been changed from 470,000 ohms to 560,000 ohms.

31,475



There are 31,475 models covered completely in RIDER TV-AM-FM-PA MANUALS.

And you may be called upon to service any one of these models... today... tomorrow...

...next week. Make sure you have the BEST servicing information—when you need it. Complete your RIDER MANUAL Library now. RIDER MANUALS—PROVEN BEST BY 21 YEARS OF TEST.

In TELEVISION
5 RIDER TV MANUALS
★ 10,544 Pages
★ 1,849 Models
 *Equivalent of 8 1/2 x 11 ins. size

RIDER P.A. MANUAL
★ 2,024 Pages
★ 1,285 Models

In AM-FM-Auto Radio-Phono
21 RIDER MANUALS
★ 31,382 Pages
★ 28,341 Models

These comprise the world's greatest compilation of ACCURATE — AUTHENTIC — RELIABLE Servicing Information... as furnished by the Service Departments of the Manufacturers themselves. And all of it is yours... at the astonishingly low cost of LESS THAN 1c PER PAGE!

Plus an **EXTRA** feature that is exclusive with **RIDER TV MANUALS**

CIRCUIT ANALYSIS... descriptions of important functions within the receiver... pertinent data originating from the manufacturers and presented by RIDER in a manner which makes this added information a valuable aid to the servicing technician—as well as a practical education in the actual design of television receivers.

John F. Rider Publisher, Inc.
 480 Canal Street New York 13, N. Y.

See Your Jobber For **RIDER MANUALS** PROVEN BEST BY 21 YEARS OF TEST

ELECTRIC CITY APPLIANCE CO., INC.
 All Major and Small Electrical Appliances
 67-19 FRESH POND ROAD
 RIDGEWOOD, N. Y.

April 5, 1950

J. F. Rider, Publisher, Inc.,
 480 Canal St.,
 New York, N. Y.

Gentlemen:

I would like to express our appreciation for the great help that your manuals have been to us.

We have found many short cuts repairing and servicing radio and television receivers with the information you have furnished.

Keep up the good work you are doing for the servicing industry.

Electric City Appl. Co. Inc.
 Service Dept.
 John Adams
 John Adams
 Service Mgr.

ja/ef

CONLAN ELECTRIC CORPORATION
 Electrical Engineers and Contractors
 Branch Office Main Office
 117 South Street 1042 Atlantic Avenue
 Baltimore 2, Md. Brooklyn 16, N. Y.

March 23, 1950

John F. Rider, Incorporated
 480 Canal Street
 New York, N. Y.

Dear Mr. Rider:

The results of a recent survey of our branches in the Bronx, Brooklyn, Roosevelt and Baltimore, to determine the technical reference requirements, developed conclusive evidence that the relative use, or your manuals as compared to all our other reference data, is the most outstanding of its overall reliability and concise, useful detail per set.

The above results prompt our commendations to you for your television manual which is fast proving itself as a most worthy contribution to the potentials of success in the servicing aspect of the television industry.

Yours very truly,
CONLAN ELECTRIC CORPORATION
 Television Division
 Gunnar Nelson
 Gunnar Nelson,
 Regional Service Director

GN:eoc

MARCUS H. MOSES, B.S. (E.E.)
 Electronical Technician
 35 Hamilton Place, New York 31, N. Y.

January 18, 1951

John F. Rider, Publisher, Inc.,
 480 Canal Street,
 New York 13, N. Y.

Gentlemen:

I am the proud owner of a complete set of Riders Perpetual Trouble Shooters Manuals to and including Volume 20 on Radio, Volumes 1 to 5 inclusive on Television and Volume 1 on Public Address Systems, as well as more than twenty of your textbooks including the very comprehensive Encyclopedia on Cathode-Ray Oscilloscopes and the indispensable Receiving Tube Substitution Guide Book.

The day of the man who owns a long nose pliers, side cutters, screwdriver and tube checker calling himself a radio service man is certainly gone along with hoop skirts and horse cars. With A.V.C., A.F.C., A.G.C., delayed action circuits, noise squelching circuits and the many other innovations being introduced into A.M., F.M. and T.V. receivers, the man without authentic service information is like a mariner at sea without a compass. I would not part with my Rider library for many times its cost unless I could replace it.

Yours,
 Marcus H. Moses

SERVICEMEN ARE SOLD

Yes, SOLD on RIDER MANUALS! And for good reason, too! Check for yourself... RIDER MANUALS give you ALL the information you need! COMPLETE coverage of the manufacturers' ENTIRE receiver output! ALL production runs (not just pilot models)... with ALL of the changes!

Yes, and ALL of the data is ACCURATE, AUTHENTIC, FACTORY-AUTHORIZED! ALL of it comes direct from the service departments of the receiver manufacturers themselves, and is compiled by RIDER into these indispensable television servicing manuals... giving you, in this ONE course, ALL of the priceless information that you MUST have

...and you can see WHY

For In the **FIRST FIVE RIDER TV MANUALS**, containing 10,544 pages:

731 pages are devoted to understandable descriptions of circuit action... telling you HOW the circuit functions. NOBODY, but RIDER furnishes you with so much of this necessary information!

293 pages are on signal waveforms... so vital to any rapid trouble diagnosis in picture i.f., sound i.f., video, sync and sweep circuits. Nobody, but RIDER, offers anywhere near this amount of important data!

337 pages have factory-issued unpacking and installation instructions. Nobody, but RIDER, brings you as many of these helpful, time-saving notes!

ONLY IN RIDER TV MANUALS

NOWHERE else can you get as much... in such easy-to-find format... so very easy-to-understand... so accurate... so thorough... so complete... so efficient...

★ ★ ★ ★ ★

RESERVE YOUR COPY OF TV MANUAL No. 6

Despite severe production difficulties, this new "BIG" TV Manual is being scheduled for delivery in March. However, due to paper shortages, we can print only a limited quantity. And since the contemplated curtailment of television receiver production makes the information contained in this volume absolutely essential to servicing technicians, we suggest that you order your copy IMMEDIATELY.

NOW AVAILABLE! RIDER MANUAL Vol. XXI

Factory-authorized servicing material from 61 manufacturers... AM-FM, auto radios, record changers, disc and tape recorders... Coverage from December 1949 to October, 1950. 1648 pages plus Cumulative Index Volumes XVI through XXI..... **\$18.00**

John F. Rider Publisher, Inc.
 480 Canal Street New York 13, N. Y.

Complete your Rider Manual Library! If any volumes are missing, order a replacement today!

Television Changes

Bendix 2060, 2070, 7001

These models are similar to Models 2051, 3051, 6001, 6003 and 6100, with the exception of the changes to follow. A 0.01- μ f capacitor C51 has been added from pin 2 of the 6AS5 audio output tube (V8) to the junction of R28 and pin 9 of V7. A resistor R78 (in some sets this is a 1.2-megohm resistor) has been added from pin 2 of V8 to R28. The value of R78 in some cases is 1.5 megohms. By changing R78 the grid bias to the 6AS5 tube is increased, causing a decrease in the plate current. This decrease in plate current decreases the cathode voltage. The cathode is connected directly to the B+ bus for the plates of the i-f stages, thereby maintaining B+ at approximately the correct value of 150 volts.

In some models a 6SQ7 is incorporated as a first audio stage. This change requires a slight physical modification to the main chassis, but no change in components. It is possible that some sets may use a 6AG5 as the sync limiter stage (V10), and a 6AG5 or 6BC5 as the second i-f amplifier stage (V4).

In code G and subsequent chassis, the 6T8 ratio detector (V7) is replaced by a 6AL5 and either a 6AQ6, 6AV6, or 6AT6 (1st audio amplifier). The circuit modifications that have been made for this change are shown in Fig. 1.

On a limited number of sets the 19T8 is to be used as a ratio detector and first audio stage. This will necessitate using a special power transformer with a 19-volt filament winding. The part number for this trans-

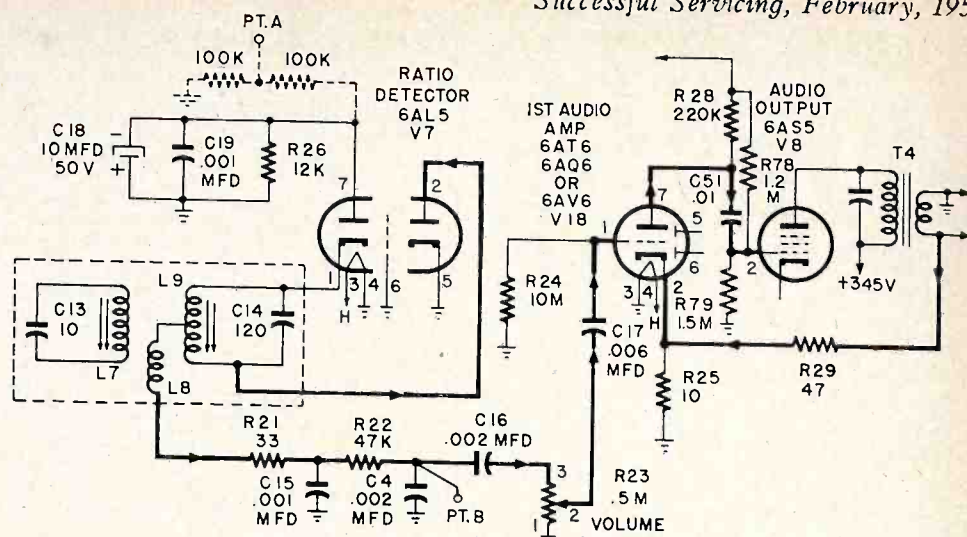


Fig. 1. Circuit modifications made in Bendix Models 2060, 2070, and 7001.

former is NH265085-1. On the upper end bell of the transformer this number will be stenciled.

The i-f frequencies should be as follows: L452 should be 25.1 Mc, T1 should be 23.6 Mc.

The diagram for the adaptation of the color plug to these receivers is shown in Fig. 2. The contrast control must be at *minimum* when the converter is used.

The parts list for Models 2070 and 7001 is the same as that for Models 2051, 3051, 6001, 6003, and 6100 except for the parts listed below:

Ref. No.	Part No.	Description
C21	CE1T11	Capacitor, electrolytic, 2 μ f, 50v
C34	CC6A30	Capacitor, ceramic, 47 μ f, 500v


C51	CP3S31	Capacitor, paper, 0.01 μ f, 400v
R5	RC22A101M	Resistor, comp, 100 ohms, $\frac{1}{4}$ w
R6	RC22A103K	Resistor, comp, 10,000 ohms, $\frac{1}{4}$ w, $\pm 10\%$
R8	RC22A155M	Resistor, comp, 1.5 megohms, $\frac{1}{4}$ w
R28	RC22A224M	Resistor, comp, 220,000 ohms, $\frac{1}{4}$ w, $\pm 20\%$
R63	RC22A124K	Resistor, comp, 120,000 ohms, $\frac{1}{4}$ w, $\pm 10\%$
R78	RC22A125M	Resistor, comp, 1.2 megohms, $\frac{1}{2}$ w
R79	RC22A155M	Resistor, comp, 1.5 megohms, $\frac{1}{4}$ w
T2	T10D28	Transformer, i-f output detector
L12	LCOF06	Coil, focus

Part No.	Description
BZOB33	Back, cabinet cover (7001)
BZOB40	Back, cabinet cover (2070)
BZOD48	Baffle, wood (7001)
BZOD52	Baffle, wood and grille cloth (2070)
DSOS01	Dial, scale, channel selector
FWOP10	Frame, wood, 17" picture (7001)
GZOS05	Glass, safety (7001)
GZOS08	Glass, safety (2070)
HCOM15	Cup, metal, back cover
HCOS92	Clip, spring, dial retainer
HWOS05	Washer, spur
HZOC12	Catch, bullet (7001)
HZOG01	Glide, metal (7001)
HZOH04	Hinge, door (7001)
HZOH22	Handle, door (7001)
JP2007	Jack, plug 2 contact
JP2011	Jack, plug 2 contact w/cable
KBOB07	Knob, control, channel selector
KCOB30	Knob, control, Off-On-Volume
KCOB31	Knob, control, contrast
KCOB32	Knob, control, hor. hold
KCOB35	Knob, control, fine tuning
SP4003	Speaker, 4 x 6 PM oval (2070)
SPOR02	Speaker, 10" PM round (7001)
ZW1V19	Cabinet, console with doors (7001)
ZW1T12	Cabinet, table model (2070)

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

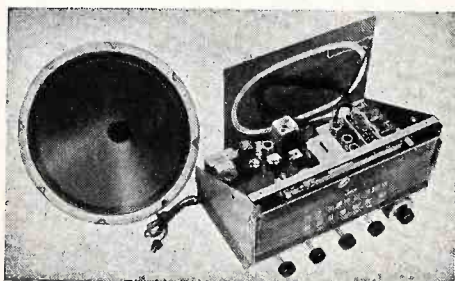Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!



SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 $\frac{1}{2}$ " wide x 8 $\frac{1}{2}$ " high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 $\frac{1}{2}$ x 10 $\frac{3}{4}$ inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12 AND NAME OF NEAREST DISTRIBUTOR.

The NEW ESPEY model 511-B FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RCA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.

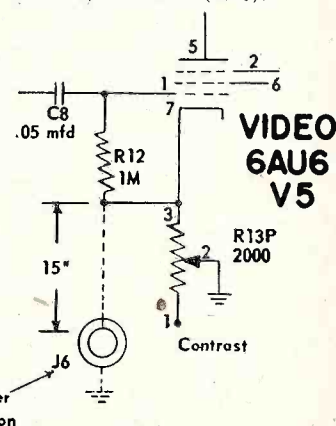


Fig. 2. Color converter connection for Models 2060, 2070, and 7001.

Westinghouse H-305C8, H-306C8, Ch. V-2137-4


The first two items in the parts list for these models should be changed to read as follows:

Part No.	Description
V-5982-2	Antenna assembly, a-m loop
V-598604	Antenna assembly, f-m loop.




Hands You Another TV Profit-Maker! NEW "Little Giant" TWIN LEAD LIGHTNING ARRESTER

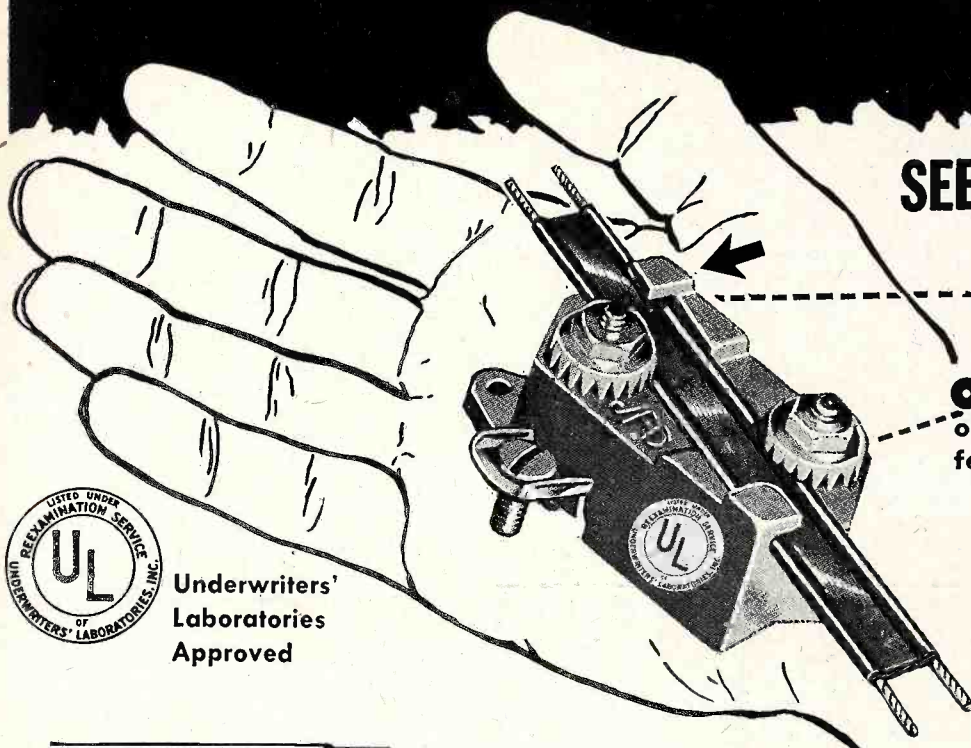PROTECTS Television Receivers Against Lightning and Static Charges!



SEEING IS BELIEVING!

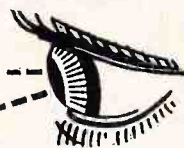

ONLY JFD Lightning Arresters offer you these exclusive patented features...

- 1 Note the exclusive patented strain-relief **Re-
taining Lip** which prevents pulling or straining against contact points.
- 2 You actually see positive contact made with lead-in wire.
- 3 Lead-in contact remains fully visible at all times.
- 4 No Guesswork!
- 5 No Arrestor Cover to Hide Poor Contacts!



Underwriters'
Laboratories
Approved



For Regular Twin Lead



For Oval Jumbo Twin Lead

STYLED FOR SALES

No. AT105 \$1.25
List

Individually Boxed with
Hardware for Mounting

SPECIAL, HIGH-DIELECTRIC FLAME-RETARDING PLASTIC

ASSURES maximum signal transfer...no varying of line impedance. INSTANT and EASY mounting anywhere, inside or out. NO WIRE STRIPPING or spreading of line necessary. CARRY one with you on every service call and make the EXTRA Profit!

MORE IMPORTANT THAN EVER!

With TV production curtailed...with component shortages developing...it is more important than ever to protect a TV receiver...and this JFD "Little Giant" will do the job!

Attractive 3 color Self-Selling Counter Display
available Free of Charge!



Order From Your Distributor or
Write Direct for Data Sheet No. 71R

MANUFACTURING CO., Inc.
6119B 16th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories

PULSE MEASUREMENT WITH VACUUM-TUBE VOLTMETERS

(Continued from page 1)

This is not the rms value of the pulse since the pulse is of square wave form, whereas the rms values were calibrated according to the meter's response to a sine wave. The peak-to-peak amplitude of the negative pulse may be obtained from the reading on the positive-peak-response meter by first finding the positive peak as follows:

$$\text{Positive Peak} = 0.5 \times 1.44 = 0.707 \text{ volt.}$$

Then the negative-peak value is obtained by equating the interval between pulses divided

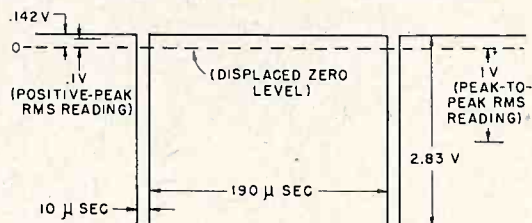


Fig. 3. A 5,000-cps negative pulse of 10 microseconds pulse duration. Note how close the positive-peak-response rms-calibrated reading is to the zero level.

by the pulse duration to the negative peak value divided by the positive peak value. Using the values for these quantities from the above example, we get the equation:

$$\frac{150 \mu\text{sec}}{50 \mu\text{sec}} = \frac{\text{Negative Peak Value}}{0.707 \text{ volt}}$$

or:

$$\text{Negative Peak Value} = \frac{150 \mu\text{sec}}{50 \mu\text{sec}} \times 0.707 \text{ v.}$$

$$\text{Negative Peak Value} = 2.12 \text{ volts.}$$

The peak-to-peak value equals the sum of the positive peak and the negative peak:

Amplitude of Negative Pulse =

$$2.12 \times 0.707 = 2.827 \text{ or } 2.83 \text{ volts.}$$

If a peak-to-peak-response meter is used, the total amplitude of the negative pulse is found by multiplying the rms meter reading by 2.83 as in the case for the positive pulse.

It should be obvious from the above discussion that the peak-to-peak-response meter is preferable to the positive-peak-response meter not only because of the simplicity of calculation of peak-to-peak pulse amplitude associated with the former, but also because measurement with the positive-peak meter becomes inaccurate as the pulse duration time is decreased. This may be seen by comparing the rms readings of the positive-peak-response meters in Fig. 2B and Fig. 3. With the values

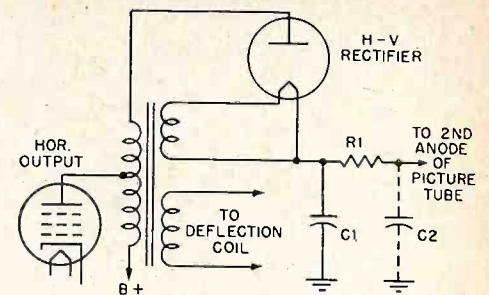


Fig. 4. Simplified schematic of a high-voltage power supply of the "kickback" type used in television receivers.

to the second anode of the picture tube. C2 may be an actual capacitor but is more likely to be the capacitance between the second anode and the external coating on the tube, which is grounded.

From the circuit it can be seen that the high-voltage pulse, shown in Fig. 5, will appear at the plate of the high-voltage rectifier and also at the plate of the horizontal output tube. The frequency of this pulse is 15,750 cycles per second and its amplitude is in the neighborhood of 5,000 volts. This type voltage is one that can be measured with a great degree of accuracy by a v-t voltmeter of the peak-to-peak type using a multiplier.

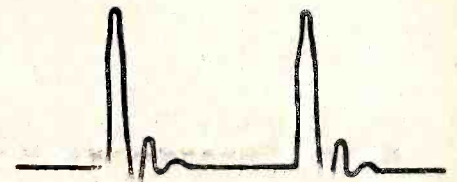


Fig. 5. High-voltage pulse obtained at the plate of the horizontal output tube and the plate of the high-voltage rectifier shown in Fig. 4.

Are you interested in the WHICH — WHY — HOW — WHEN of vacuum-tube voltmeters?
Get a copy of

VACUUM-TUBE VOLTMETERS

by John F. Rider

Completely revised and rewritten so that it is up-to-the-minute on all types of these very important devices. This is the only book devoted exclusively to this subject—the only book which gives you all of the information on the instrument you now use or own. The theory and application of all types of vacuum-tube voltmeters are described and discussed—completely—including schematics, parts lists, and maintenance instructions.

Examine the Table of Contents. Every-

thing for every VTVM use! Student, service technician, engineer, laboratory, instructor—all can use it to good advantage.

TABLE OF CONTENTS

1 — Fundamentals of Vacuum-Tube Voltmeters; 2 — Diode Vacuum-Tube Voltmeters; 3 — Triode Vacuum-Tube Voltmeters; 4 — Rectifier-Amplifier Vacuum-Tube Voltmeters; 5 — Tuned Vacuum-Tube Voltmeters; 6 — Amplifier-Rectifier Vacuum-Tube Voltmeters;

7 — Slide-Back Vacuum-Tube Voltmeters; 8 — Vacuum-Tube Voltmeters for D-C Voltage, Current, and Resistance Measurements; 9 — Probes for DC and RF; 10 — Design and Construction of Vacuum-Tube Voltmeters; 11 — Calibration and Testing of Vacuum-Tube Voltmeters; 12 — Applications of Vacuum-Tube Voltmeters; 13 — Commercial Vacuum-Tube Voltmeters; 14 — Maintenance and Repair of Vacuum-Tube Voltmeters; Bibliography; Index

NOW ON THE PRESS — OUT IN APRIL 1951


Profusely Illustrated

ORDER YOUR COPY TODAY! NOW!

JOHN F. RIDER PUBLISHER, INC., 480 Canal Street, New York 13, N. Y.

384 Pages

\$4.50

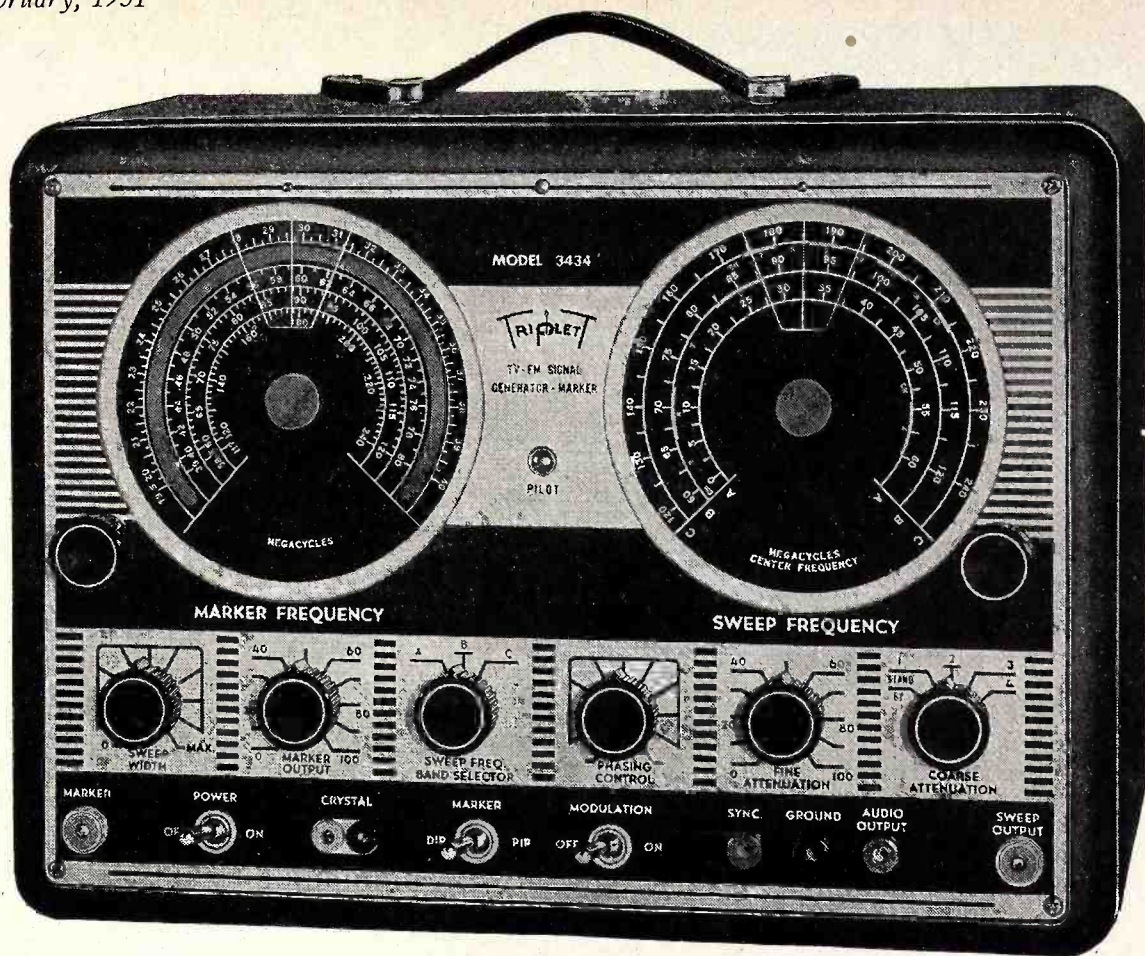


TV Sweep Generator with MIRROR-SCALE MARKER

MODEL 3434 for quick checks in all stages

Large Marker dial has a mirror scale for easier reading and reset accuracy. Straight line frequency tuning condensers provide linear scale markings. No "SKIPS" in frequency—continuously variable Sweep width control. Triplett-engineered shielding—all critical circuits enclosed. Copper plated steel construction. All these features (see Tech. Data) combined with the two built-in markers for simultaneous use set Model 3434 apart as one of the fundamental contributions to the rapid, accurate and profitable Servicing of Television.

TECH DATA	
Frequency Coverage:	
• SWEEP CENTER FREQUENCY Range 1— 0-60 MC Range 2— 60-120 MC Range 3—120-240 MC	• CRYSTAL FREQUENCIES To 20 MC on Fundamentals. Harmonics up to 216 MC. (Crystals Not Furnished)
• SWEEP WIDTH: 0-12 MC (Continuously Variable)	• MODULATION 400 Cycle on both Crystal and Marker Frequencies
• MARKER FREQUENCY 19.5 to 40 MC (fundamental). 39 MC to 240 MC (harmonic)	• AUDIO: 400 cycles

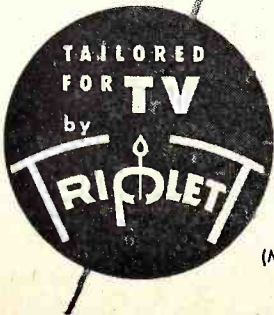The steel case is finished in black suede baked enamel, size 15 11/32"x11 1/32"x8 1/4". Leather handle. Panel is black, white and red etched on aluminum. Copper plated feet for grounding.



ONLY \$189.50 AT YOUR DISTRIBUTOR
(MODEL 3435 WITHOUT BUILT-IN MARKER, \$99.50 NET)



Please mention Successful Servicing when answering advertising.



**"BY GOLLY,
THERE GOES ANOTHER
CONDENSER, AND YOU CAN
BET YOUR SWEET LIFE
IT ISN'T A SPRAGUE!"**

Use dependable Sprague capacitors in every repair job.
The best costs no more!

Sprague Television Replacement Capacitors are designed to stand up in sweltering 185°F. chassis heat and give you the flexibility of small physical size. They can take it in any TV set!

Get your Catalog C-607-55 for the full listings of the complete Sprague line of Atom and Twist-Lok 'Lytics, Telecap Molded Tubulars, and tiny disc Cera-mites. Write today!

SPRAGUE

PIONEERS IN

ELECTRIC AND ELECTRONIC DEVELOPMENT

SPRAGUE PRODUCTS COMPANY

(Distributors' Division of Sprague Electric Co.)

NORTH ADAMS, MASSACHUSETTS

ATOM, TWIST-LOK, TELECAP, AND CERA-MITE ARE SPRAGUE TRADEMARKS

Belmont Service Hints

In the case of intermittent tuner trouble in 6J6 or early 12AT7 tuners, it has been found that the eyelet shown in Fig. 1 is not making a good electrical connection with the ground bracket at high frequencies and causes an intermittent condition. If the tuner is suspected

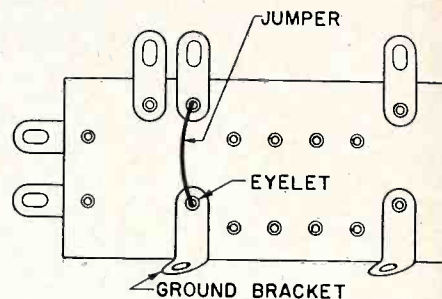


Fig. 1. Inside view of tuner terminal board.

to be causing an intermittent condition, it is suggested that the steps listed below be followed to eliminate the possibility of a poor ground connection:

1. Remove the tuner cover.
2. Place a hot soldering iron at the point shown in Fig. 2.

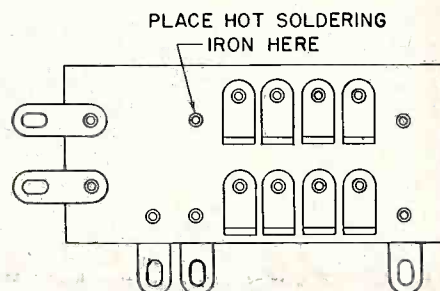


Fig. 2. Front view of tuner terminal board.

3. Allow sufficient time for heating.
4. Run solder between eyelet and ground bracket shown in Fig. 1.

An intermittent condition can also be caused by defective contacts and open or high resistance ground or coil solder connections.

Bendix 2070, 7001, T170

Model T170 is similar to Models 2070 and 7001. The following changes have been made in these models. A 0.02- μ f capacitor (C52, Part No. CP4T34) has been added from the junction of pin 7 of V5 (6AU6 video) and R12 the 1-megohm resistor (going to pin 1 of V5) to the color converter jack J6. The value of R79, from ground to pin 2 of the audio output tube V8 (6AS5), has been changed from 1.5 megohms to 1.2 megohms.

The Parts List for Model T170 is the same as that for Models 2070 and 7001 except for the changes listed below:

Stock No.	Description
BZOB41	Back, cabinet cover
BZOD49	Baffle, wood and grille cloth
DSOS01	Dial, scale, channel selector
FPOP09	Frame, plastic, 17" picture
GZOS09	Glass, safety
HCOM15	Cup, metal, back cover
HCOS92	Clip, spring, dial retainer
HVOS05	Washer, spur
HZOG01	Glide, metal
JP2007	Jack, plug 2 contact
JP2011	Jack, plug 2 contact w/cable
KBOB07	Knob, channel selector control
KCOB30	Knob, off-on-volume control
KCOB31	Knob, contrast control
KCOB32	Knob, hor. hold control
KCOB35	Knob, fine tuning control
SP4003	Speaker, 4 x 6 p-m oval
ZWIT14	Cabinet, table model
JR1S00	Jack, receptacle & contact, color converter (J6).

WE GUARANTEE that RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is . . . what it can DO . . . and HOW to use it properly!



ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usan

The **FIRST** and **ONLY** book that so fully and clearly describes the 'scope . . . its construction . . . its capabilities . . . its applications in communications, engineering, research . . . with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you . . . WHAT each type can do . . . HOW to use it . . . and WHICH is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians — all can use

this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages . . . 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home . . . municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY** and **IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth BoundAnd only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Usan



The entire system of frequency modulation is explained thoroughly . . . all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

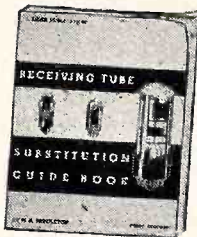

For AM-FM-TV Receivers and Allied Equipment!

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

EXTRA! In addition to tube information . . . this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc. . .

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New . . . Revised . . . Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman



All the **QUESTIONS** and **ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH** . . . a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer. It also lists "extras" not ordinarily found in a volume of this type . . . including Useful Appendices which take in Small Vessel Direction Finders and Automatic Alarm.

766 Pages, Hundreds of Explanatory Diagrams..\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc. . . in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed, how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth boundOnly \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.

Radio Changes

Westinghouse H-316C7, H-317C7,
H-326C7, Ch. V-2136-1, V-2136-1A

Model H-317C7 is the same as Models H-316C7 and H-326C7 except that an additional by-pass capacitor of 0.003 μf , 0.004 μf , or 0.007 μf , is connected across the output section of the filter capacitor C36 in some chassis. This additional capacitor is used in cases where the output section of C36 has excessively high impedance at radio frequencies. The chassis parts are listed in the H-316C7 service data. The cabinet and miscellaneous parts are the same as those for Model H-316C7 except for the parts listed below:

Part No.	Description
V-5982-4	Antenna assembly, a-m loop
V-6120	Background, dial
V-1223-2	Cabinet (blond)
V-9075-2	Clip, spring (ball head strike)
V-8568	Doors (matched pairs)
V-8569	Drawer, record changer (complete less hardware)
V-9832-2	Grille assembly, panel
V-9091-3	Hinge, L.H.
V-9091-4	Hinge, R.H.
V-10122-1	Pull, door
V-3246	Socket, octal wafer
V-9076-2	Strike, ball head.

In later production of the V-2136-1 chassis, the following changes were incorporated:

1. The oscillator injection capacitor (C24), which is connected between the top of the f-m oscillator coil and the top of the f-m—r-f coil, is changed in value to 0.68 μf (Part No. V-5658-4). This change improves the mixer efficiency and increases the sensitivity.


2. A 0.05- μf , 200-volt capacitor C44 (Part No. RCP10W2503M) is inserted in the line

Successful Servicing, February, 1951

that extends between point "Y" on the schematic diagram and the selector switch SW2. In addition, R34 (Part No. RC20AE224M), a 220,000-ohm $\frac{1}{2}$ -watt resistor, is inserted between the selector switch side of C44 and ground. These changes improve the tuning characteristics of the f-m band.

Some chassis used in later production of the subject models are designated V-2136-1A. These chassis are the same as the V-2136-1 except for the differences mentioned in the following paragraphs. These chassis use a 19T8 tube in place of the 12AL5 and 12AV6 tubes used in the V-2136-1 chassis. Tap 1 of ratio detector-transformer T3, that was connected to pin 1 of the 12AL5, is now connected to pin 3 of the 19T8; and tap 4 of T3 is connected to pin 1 of the 19T8. A 33,000-ohm resistor R35 (R5, 22,000 ohms which was in this position has been removed), is connected from pin 2 to pin 7 of the f-m detector 19T8. C30 is connected across R35, and the two 100,000-ohm resistors used for alignment purposes only are still connected to the junction of C30 and R35. R24, the 220,000-ohm resistor that was connected to C30 and the junction of R25 (4.7 megohms) and R2 (470,000 ohms), and the lead from R24 to SW2 have been deleted. Pin 6 of the 19T8 is connected to tap 1 of T6, the 2nd i-f—a-m transformer. Pin 7 is grounded; pin 9 goes to the junction of R31 and C19C and D; and pin 8 goes to the junction of R10 and C19A. R25, that was connected from R3 to the junction pin 6 of the 12AV6 and R24 and R2, has been deleted. R2, 470,000 ohms, is now connected from ground to the junction of R19 (the 2.2-megohm resistor going to tap 4 of 1st i-f—a-m transformer) and R6 (the 47,000-ohm resistor going to tap 2 of T6). C13, the 0.05- μf capacitor that went from terminal lug 4 of the antenna terminal board, is now located from tap 4 of T5 to ground, in place of C16, the 0.01- μf capacitor which has been removed. The positions of C31 and C19B have been reversed. Capacitor C31, 150- μf , is now located from ground to tap 2 of T6, and capacitor C19B, 220 μf , is now located from ground to the junction of R2, R6, and R19. A 470,000-ohm resistor R33 (Part No. RC20-AE484K) and a 100- μf capacitor C43 (Part No. RCM20B101K) have been added in parallel from tap 3 of T2 to ground.

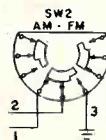The accompanying diagram shows switch SW2. Only the middle wafer contains changes that have been made in the V-2136-1A chassis.



Switch SW2 used in
Chassis V-2136-1A.

The first and last wafers are wired as shown in the schematic for V-2136-1. (The numbers in the illustration were added for reference only.) Contact 1 goes directly to B and A of C33, and thence to L10. Contact 2 goes directly to R20, 47 ohms, and thence to pin 7 of 12BE6. The 47,000-ohm resistor R26 and the 0.001- μf capacitor C2 connected to R20 have been deleted from the circuit, and contact 3 is grounded.

In the 50L6/GT output circuit capacitor C4, 0.005 μf , is connected to pin 8 rather than to pin 4. The 3.3-megohm resistor R27, that is connected from terminal lug 4 to SW2 in the V-2136-1 chassis, has been deleted in the V-2136-1A chassis.



Music—sweet music to his ears!

And why not? A satisfied customer has telephoned—yes, actually telephoned—to thank this service-dealer for the swell repair job on his TV sets.

Your customers may not take the trouble very often to do this, but you can bet your last dime that a *dissatisfied* customer will lose no time in telling you what he thinks. This means call-backs on which you lose time, money, and reputation.

The trick, of course, is to eliminate call-backs. Unfortunately, you can't eliminate them *all*. But, you can keep them to a minimum by using only parts on which you can stake your reputation.

Look at any tube marked TUNG-SOL. There is the same tube—the same performance standards—the same dependability

which eight out of ten leading set manufacturers use for initial equipment. All TUNG-SOL tubes are made to meet their requirements. So, when you make replacements with TUNG-SOL tubes, you're putting back into the set the same high quality with which it left the factory.

This TUNG-SOL "one standard" policy safeguards your service work, your prestige and your profit.

Tell your distributor's salesman you'd rather have TUNG-SOL tubes.

TUNG-SOL LAMP WORKS INC., NEWARK 4, N.J.
Sales Offices: Atlanta, Chicago, Dallas, Denver,
Detroit, Los Angeles, Newark



ONE STANDARD—The best that can be made—

For Initial Equipment and Replacement

Please mention Successful Servicing when answering advertising.



the Du Mont type 20_{CP4}

For the set that follows the "seventeen" in rectangular pictures, Du Mont supplies the "twenty" all-glass rectangular Type 20CP4.

Another in the series of Big-Picture Teletrons employing the NEW Bent-Gun for edge-to-edge sharpness that makes the difference in picture tubes of this size. The gray filter face plate improves contrast.

The first picture tube designed with the industry "standard" neck length of 7 $\frac{1}{2}$ ".


Our Commercial Engineering Department invites all design inquiries.

Allen B. Du Mont Laboratories, Inc., Cathode-Ray Tube Division, Clifton, N. J.

DU MONT
*Teletrons**

*Trademark

Please mention *Successful Servicing* when answering advertising.

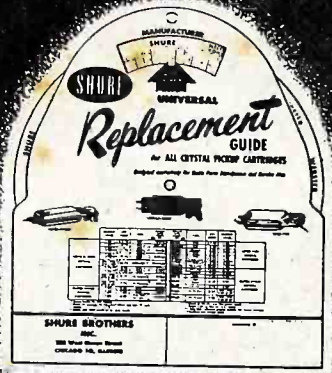FREE!**NEW SHURE****Cartridge Replacement GUIDE**

A TURN OF THE DIAL GIVES THE CORRECT REPLACEMENT MODEL OF ALL SHURE CARTRIDGES AND MOST OTHER MAKES

Ask your Shure Distributor for a "Guide" — or write direct, giving us his name.

SHURE BROTHERS, INC.

Microphones and Acoustic Devices

225 West Huron Street • Chicago 10, Illinois

Please mention Successful Servicing when answering advertising.

Sparton 130, 132, 135, 139, Ch. 5A10

Inability to procure type 12AV6 tubes in production quantities for the above models using radio chassis type 5A10 made it necessary to make the following production substitution. In the future, these models will use a 12AT6 tube in the 2nd detector and avc circuit in place of the original 12AV6 as shown in the schematic diagram. As these tubes are interchangeable, a change in other components of the circuit is not necessary.

Sparton 1080, 1081, Ch. 9L8A

Model 1080 in mahogany and Model 1081 in blond are radio-phonograph combinations using radio chassis type 9L8A. This nine tube-superheterodyne radio receiver incorporates f-m and a-m broadcast bands. Chassis 9L8A is used with television Model 4900TV and complete service data for this radio chassis were issued with the service data for the 4900TV.

INDEX OF CHANGES

Model Page Number
Successful Rider Manual†
Servicing From To

TELEVISION CHANGES

Belmont Service Hints	12		
Bendix 2060, 2070, 7001	8		
2051, 3051, 6001, 6003, 6100		5-1	5-11
Bendix 2070, 7001, T170	12		
2070, 7001	8		
Capehart-Farnsworth CX-33	6	5-1	5-12
DuMont RA-105, RA-106	2		
RA-105		2-5	2-33
		*2-5	*2-55, 56
RA-106		2-34	—
		*2-57	*2-58
DuMont Savoy, Winthrop, Ch. RA-103C; Wellington, Ch. RA-104A	2		
Savoy, RA-103; Wellington, Ch. RA-104A		*1-58	*1-80
		3-1, 2	3-3, 4
		4-1	4-4
Farnsworth, Capehart 462P12, Ch. C-267	6		
Farnsworth, Capehart 461P		Page 2, Dec. issue of Successful Servicing	
Farnsworth Ch. U-12		2-9, 10	2-15
		*2-1	*2-9, 10
		C4-2	—
Meck Service Hints	2		
Wilcox-Gay G-414, G-614, G-624, G-914, Series 97 & 98	6		
Majestic 14CT4, 16CT4, 1674, 1974		Page 2, Jan. issue of Successful Servicing	
Series 94 & 97		5-1	5-14

RADIO CHANGES

Sparton 130, 132, 135, Ch. 5A10	10	20-10	20-13
Sparton 1080, 1081, Ch. 9L8A	10		
4900TV, Radio Ch. 9L8		TV3-21	3-25
Westinghouse H-305C8, H-306C8, Ch. V-2137-4	8	21-1	21-4
Westinghouse H-316C7, H-317C7, H-326C7, Ch. V-2136-1, V-2136-1A	14		
H-316C7, H-326C7, Ch. V-2136-1		21-18	21-21

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

BOOKS FOR THE SERVICEMAN

TV Master Antenna Systems	368 pages	\$5.00
Receiving Tube Substitution Guide	Book. 224 pages	\$2.40
Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses.	992 pages	\$9.00
TV and Other Receiving Antennas (Theory and Practice). 606 pages		\$6.00
TV Installation Techniques	336 pages	\$3.60
Radio Operator's License Q & A Manual, 2nd Edition. 766 pages		\$6.60
The Business Helper	134 pages	\$2.00
FM Transmission and Reception	460 pages	\$3.60
TV Picture Projection and Enlargement. 192 pages		\$3.30
Broadcast Operators Handbook	288 pages	\$3.30
Understanding Vectors and Phase	160 pages	Cloth Cover \$1.89 Paper Cover \$0.99
Inside the Vacuum Tube	424 pages	\$4.50
Understanding Microwaves	385 pages	\$6.00
Servicing by Signal Tracing	360 pages	\$4.00
The Meter at Work	152 pages	\$2.00
Installation and Servicing of Low Power Public Address Systems	208 pages	\$1.89
A-C Calculation Charts	148 nomographs in 3 colors	\$7.50
High Frequency Measuring Techniques Using Transmission Lines. 64 pages		\$1.50
The Oscillator at Work	256 pages	\$2.50
Automatic Frequency Control Systems. 144 Pages		\$1.75
Radar — What It Is	72 pages	\$1.00
Radio Amateur's Beam Pointer Guide. 32 pages		\$1.00
Master Index-Volume I to XV		1.50

Order Your Copy Now**JOHN F. RIDER PUBLISHER, Inc.**

Return Postage Guaranteed

JOHN F. RIDER PUBLISHER, Inc.
480 CANAL ST., NEW YORK 13, N. Y.

From

A. J. S. CERINO
5310 OVERBROOK ST.
DOUGLASSON, L. I., NEW YORK

Sec. 34.66, P. L. & R.
U. S. POSTAGE
PAID
NEW YORK, N. Y.
PERMIT NO. 9427

FREQUENCY REQUIREMENTS OF OSCILLOSCOPE VERTICAL AMPLIFIERS

by John F. Rider

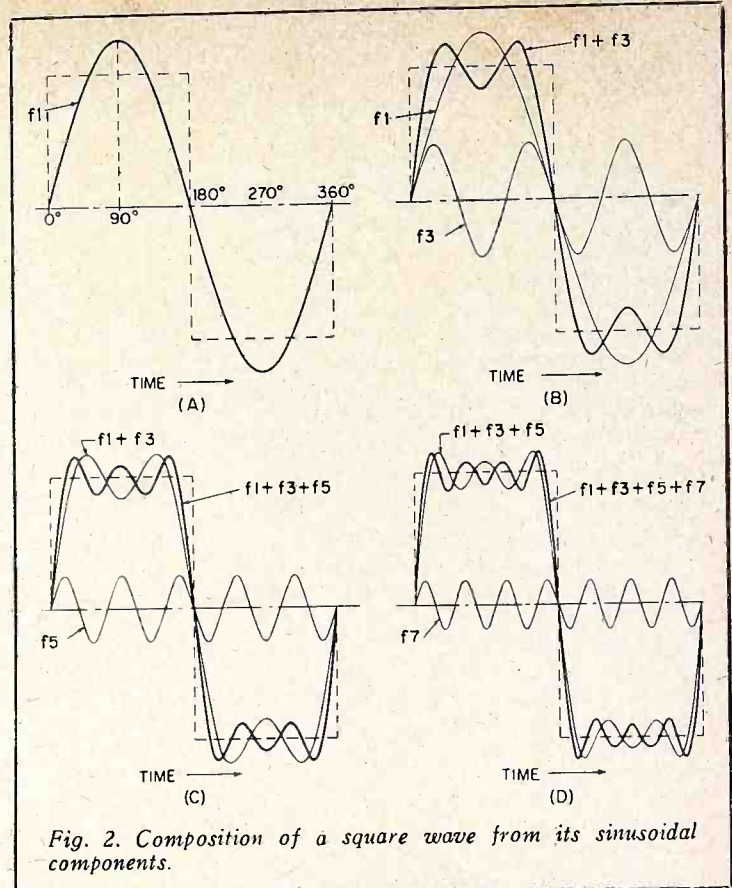


Fig. 2. Composition of a square wave from its sinusoidal components.

AN IMPORTANT capability of the vertical amplifier is the frequency over which the amplifier will operate. Although not generally identified as such, every amplifier is, in a way, a filter system, because it will neither pass all frequencies, nor will it amplify equally those frequencies which it will pass. The pass-band of the vertical amplifier in an oscilloscope has a great bearing on the utility of the device. This is true, regardless of voltage waveshapes which will be fed into the amplifier, but most significantly relative to nonsinusoidal waves, the investigation of which is today one of the paramount fields of utility of the oscilloscope.

Equipment cost is very closely tied to bandwidth; the higher the bandwidth, usually the greater will be the cost of the device. One of the very significant changes which has taken place in the design of cathode-ray oscilloscopes during the past fifteen years has been a gradual increase in the bandwidth of the amplifiers in the device, especially the vertical amplifier. The need for this improvement originates in the waveforms which have become standard in many kinds of equipment. We are speaking about square, sawtooth, triangular waves, etc.,

or combinations thereof. Many modern devices and systems make use of such waveforms for operation or testing.

Importance of Harmonics

The amplification of a sine wave involves only one frequency at a time, and the frequency limits of an amplifier are dictated simply by the range of individual frequencies which are to be raised in level. It is not so when working with nonsinusoidal waves. The relationship between the fundamental frequency of a square wave (as indicated in Fig. 1), for example, and the frequency range of an amplifier is of some importance; of much greater import, however, is the frequency range of the harmonics of that fundamental and the pass-band of the amplifier. For example, in Fig. 2 note the makeup of the sine-wave harmonics used to approach the reproduction of a square wave. In other words, an amplifier capable of amplifying all frequencies between, for example, 10 cps and 1.0 Mc within 3 db, could be used for the amplification of sine waves substantially beyond this frequency band, but it would not be suitable for the amplification of square waves having fundamental frequencies above about 100,000 cps.

The importance of the frequency response in the amplification of nonsinusoidal waves lies in the ability of the amplifier to uniformly amplify the harmonics as well as the fundamental, in that way affording good fidelity of signal reproduction. Then, for oscilloscope amplifiers, what shall be considered the required frequency range? Unfortunately, the answer is not as simple as the question. We know that the ideal condition never can be satisfied, because the ideal square wave, tri-

angular wave, or sawtooth wave requires the presence of an infinite number of harmonics. This is not attainable because it would require an amplifier with infinite bandwidth. So a compromise is forced on everyone, and it then becomes either a matter of individual preference, or the fulfillment of accepted specific standards, as to what shall be considered good quality of reproduction.

Different applications or measurements dictate different conditions. An order of quality acceptable for one application is not necessarily equally acceptable in another case. This is why it is possible to generalize, but not to set definite minimum requirements. There is no agreement among engineers as to the requirements, although there is general concurrence concerning a range of the minimum number of harmonics which should be present for a reasonable quality of reproduction of a nonsinusoidal wave. The absence of sufficient harmonics, nonuniform amplification of the harmonics, or a radical shift in relative phase of the frequency components of a wave during amplification can produce a very badly distorted reproduction of the input signal. This may be sufficient to destroy the utility of the device as a tool for study and comparison.

(Continued on page 12)

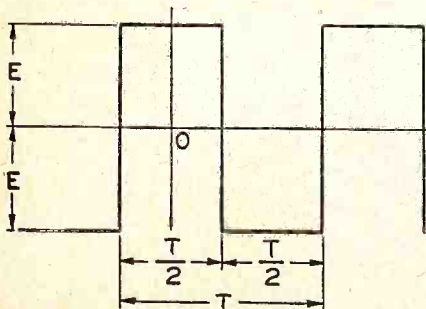


Fig. 1. Conventional square wave.

Editor's Note: This article is an abridged excerpt of the section on factors controlling the application of the basic oscilloscope appearing in Chapter 10, entitled "The Basic Oscilloscope and its Modifications," from **ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES** by Rider and Uslan, published by John F. Rider Publishers, Inc.

Television Changes

Westinghouse H-196A, H-207A, Ch. V-2130-1

The V-2130-1 chassis used in Models H-196A and H-207A is basically the same as the V-2130 chassis used in Models H-196 and H-207. Several changes have been made in the V-2130-1 chassis, however, and the revised circuits are discussed below. The alignment procedure remains unchanged.

The reference numbers applied to the components in this chassis, V-2130-1, differ from those found in the V-2130. A list is given below, comparing the reference numbers for Chassis V-2130 with the new numbers for V-2130-1. All changes for Chassis V-2130-1 etc. will be written up using the new numbering system unless indicated otherwise.

SYNC SEPARATOR AND AMPLIFIER CIRCUITS (See Fig. 1)—The necessity for using a phase inverter (1st sync amplifier in the V-2130) is eliminated in the V-2130-1 by taking the sync voltage from the plate circuit of the 1st video amplifier. At this point the polarity is correct for separating the sync from the blanking pedestal and video signal.

Interaction between the vertical and horizontal components is reduced by using individual coupling networks and separator tubes. The upper network (R429, C412, and R414) is designed to favor the low-frequency vertical sync pulses, while the lower network (C402 and R415) favors the high-frequency horizontal pulses.


R436 (27,000 ohms) and R419 (10,000 ohms) form a voltage-divider network which drops the voltage on plate 1 of the sync separator to approximately 8 volts. R446 (68,000 ohms) and R422 (10,000 ohms) perform the same function for plate 6 of the same tube, dropping the voltage to approximately 30 volts. C403 (270 μ F) by-passes any video that might get by the separator tube.

C413 (0.05 μ F) and R421 (100,000 ohms) form the coupling network for the vertical section of the 12AT7 horizontal-vertical sync amp, and C410 (0.01 μ F) together with R434 (4.7M) form the coupling for the horizontal section. Bias for the separator and amplifier tubes is developed by the time constant network in each grid circuit.

D-C RESTORER (See Fig. 2)—The d-c restorer circuit used in the V-2130-1 is much simpler than the one used in the V-2130 chassis. This circuit functions as a simple clamper and operates as follows:

When the negative sync and blanking pulse is impressed on the grid of the cathode-ray tube, the cathode of the 12AU7 becomes negative with respect to the plate, and the diode (grid and plate are connected together) con-

ducts. This effectively shorts out R324 (1M) which results in a short time constant. After the sync and blanking pulse passes, the diode becomes an open circuit, resulting in a much longer time constant. Thus, during the sync and blanking period, C337 (0.05 μ F) can charge very rapidly due to the short time constant, but during the interval between the sync and blanking pulses, it cannot discharge very rapidly due to the much longer time constant. In this manner a constant charge is kept on the capacitor which will be approximately equal

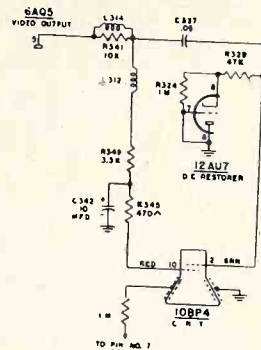

SERVICEMEN ARE SOLD

Yes, SOLD on RIDER MANUALS! And for good reason, tool Check for yourself... RIDER MANUALS give you ALL the information you need! COMPLETE coverage of the manufacturers' ENTIRE receiver output! ALL production runs (not just pilot models)... with ALL of the changes!

Yes, and ALL of the data is ACCURATE, AUTHENTIC, FACTORY-AUTHORIZED! ALL of it comes direct from the service departments of the receiver manufacturers themselves, and is compiled by RIDER into these indispensable television servicing manuals... giving you, in this ONE course, ALL of the priceless information that you MUST have

...and you can see WHY

For in the FIRST FIVE RIDER TV MANUALS, containing 10,544 pages:

731 pages are devoted to understandable descriptions of circuit action... telling you HOW the circuit functions. NOBODY, but RIDER furnishes you with so much of this necessary information!

293 pages are on signal waveforms... so vital to any rapid trouble diagnosis in picture I.F., sound I.F., video, sync and sweep circuits. Nobody, but RIDER, offers anywhere near this amount of important data!

337 pages have factory-issued unpacking and installation instructions. Nobody, but RIDER, brings you as many of these helpful, time-saving notes!

ONLY IN RIDER TV MANUALS

NOWHERE else can you get as much... in such easy-to-find format... so very easy-to-understand... so accurate... so thorough... so complete... so efficient...

★ ★ ★ ★ ★

TV MANUAL No. 6

Despite severe production difficulties, this new "BIG" TV Manual is being scheduled for delivery in March. However, due to paper shortages, we can print only a limited quantity. And since the contemplated curtailment of television receiver production makes the information contained in this volume absolutely essential to servicing technicians, we suggest that you order your copy IMMEDIATELY.

NOW AVAILABLE! RIDER MANUAL Vol. XXI

Factory-authorized servicing material from 61 manufacturers... AM-FM, auto radios, record changers, disc and tape recorders... Coverage from December 1949 to October, 1950. 1648 pages plus Cumulative Index Volumes XVI through XXI. \$21.00

John F. Rider Publisher, Inc.
480 Canal Street New York 13, N. Y.

Complete your Rider Manual Library! If any volumes are missing, order a replacement today!

STANLEY'S RADIO SERVICE

3033 16th Street
San Francisco 3, Calif.

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Dear Mr. Rider:

In all the years that I have been established as a radio and TV serviceman, my Rider manuals have never let me down.

Whenever a set is brought into my shop to be serviced, my Rider manual always has the servicing data available for me. I wouldn't know what to do if I didn't have all of Rider's on hand.

I will go along with you in your expression,
HAVE IT WHEN YOU NEED IT!

Keep up the good work.

Sincerely,

STANLEY'S RADIO SERVICE
Stanley Michelsen

TOWN RADIO CO.

501 Sutter Avenue
Brooklyn 7, N. Y.

John F. Rider
480 Canal Street
New York, N. Y.

Gentlemen:

We have been using Rider Manuals for twenty-one years, since Volume I was published. In our opinion, we cannot see how any service shop can operate without a complete set.

B. A. Shofler

AYOOB BROS. RADIO

2726 San Bruno Avenue
San Francisco, Calif.

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Gentlemen:

I have all of your Rider Manuals, AM, FM, TV, and PA, in my service shop.

I like the way they are presented, with factory-authorized data, so that each set that comes into my shop to be serviced, is the way it was designed by the factory engineer. Not only do your manuals cover data on the pilot runs but most all production runs, so I am assured that whatever set comes into my shop, I have the servicing data for it.

I also receive your SUCCESSFUL SERVICING which keeps me advised of new developments in the electronics field, and I look forward to reading this each month. Your Radio and TV changes that appear in SUCCESSFUL SERVICING, help keep my Rider Manuals up to the minute.

You are to be complimented on the way you keep the servicing industry up to date.

Sincerely,

AYOOB BROS. RADIO
Thomas W. Ayoub
Thomas W. Ayoub

22 YEARS and 28 Manuals TELL THIS STORY

Most servicemen inform us that they prefer RIDER MANUALS for their absolute reliability. Daily, they depend upon our Factory-Authorized, Factory-Accurate servicing information (from the service departments of the receiver manufacturers themselves) to speed repairs... remove all guesswork... and assure the satisfactory completion of repair jobs, whatever their nature.

Others favor the completeness of RIDER MANUALS... and the fact that, from this SINGLE SOURCE, they can get everything they need... original production runs, subsequent production runs—with all the changes.

And still others say it's the ease with which they are able to locate the exact data they want... and the ease with which they can make full use of this information.

Whatever their individual reasons may be, they all agree

Rider Manuals ARE BEST

The Latest in Television!

Rider TV Manual Vol. 6



Despite severe production difficulties, this new "BIG" TV Manual is ready for you. However, due to extreme paper shortages, we were unable to produce as many as we feel will be required. So make sure of your copy... order it from your jobber TODAY! This is another

LARGE SIZE manual, with the equivalent of 2320 of our former 8 1/2 x 11" page size, all filed in place.

\$24.00

The Latest in Radio!

Rider Manual Vol. XXI



FACTORY-AUTHORIZED servicing material from 61 manufacturers... AM-FM-Auto Radios-Record Changers-Disc and Tape Recorders. Coverage from Dec. 1949 through Oct. 1950. 1648 Pages PLUS Cumulative Index Volumes XVI through XXI. \$21.00

Make sure that your Working Library of RIDER MANUALS is complete... with ALL of these indispensable volumes on hand.

Television Manual Volume 6 (Plus Index)	\$24.00
Television Manual Volume 5 (Plus Index)	24.00
Television Manual Volume 4 (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 3 (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 2—In new, larger page size, 12" x 13". (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 1 (Plus "How It Works" Book and Index)	19.80
Volume XXI	21.00
Volume XX	21.00
Volume XIX	22.50
Volume XVIII	22.50
Volume XVII	19.80
Volume XVI	9.90
Volume XV	22.50
Volume XIV to VII (each volume)	19.80
Volume VI	15.00
Abridged Manuals I to V (one volume)	19.80
Master Index, Covering Manuals Vol. I to XV	1.50
PA Equipment Manual, Volume I	18.00

JOHN F. RIDER PUBLISHER, INC.
480 Canal St. New York 13, N. Y.



Don't Take Unnecessary Chances

An overwhelming majority of servicemen say that *performance* is what they want most in a capacitor. If you agree, and if you don't want to take chances, your best bet is . . .

Make Sure! Make it Mallory!

Performance is the one big reason why more than half of the hundreds of servicemen interviewed in a recent survey use Mallory Capacitors.

Despite excessive operating temperatures and higher ripple currents, Mallory Capacitors have taken the rugged service of TV operation

in stride. The far superior heat dissipating characteristic for which Mallory FP Capacitors have long been known is the reason for this trouble-free performance. And Mallory Plascap* plastic tubulars are suited for the same 185° F. (85° C.) operation.

When you are looking for performance, don't take a chance on just any capacitor. Make it Mallory . . . and make sure! It costs you no more to play safe.


MALLORY PLASCAP



The plastic tubular specifically designed to meet your field service problems. Available in a complete range of ratings.

Depend on your Mallory Distributor for precision quality at competitive prices.

*Trade Mark

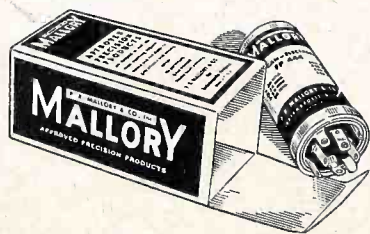

P. R. MALLORY & CO. Inc. MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

MARCH, 1951

No. 5

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

480 Canal Street
New York 13, N. Y.

Published by
JOHN F. RIDER PUBLISHER, INC.

JOHN F. RIDER, Editor
E. H. BEAUMONT, Associate Editor

Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher

Worth 4-8340
Worth 4-8341



CURTAIN TIME

About the Industry

Reports indicate that the income of CBS during 1950 from a-m radio exceeded 1949. If it's true with this chain, then the probability is that the other chains did not suffer too badly, if at all. In all probability they, too, have made money. In view of the dire forecasts made about a-m radio when TV first appeared, it is very heartening to note that a-m broadcasting is far from being eliminated by TV. Some time ago, we commented that TV faces one problem, namely, that the viewer must be stationary in order to watch the picture, whereas in a-m radio, a number of receivers in a home enables the listener to hear the program and still carry on other necessary duties. This is a very, very important point. Moreover, the cost of air time on TV has already exceeded radio time for equal periods with fewer TV outlets than a-m radio outlets. So, for perhaps the sixth or eighth time we say that a-m radio is far from dead. About 60,000,000 a-m radio units have been produced during the past five years.

Just Thinking

This has nothing to do with the radio and television industry. It stems from exposure

to security measures and classified documents during the last fracas. Just recently we read about the development of small A-bomb heads on projectiles. Orienting thinking on the part of the enemy in that direction may not be too grave a matter, but why disclose the use of the reflector as the means of accomplishing the solution to a problem of long standing. Was it necessary for public peace of mind?

Apparently it was a development of great importance, at least it was presented in that manner. If that is true, why save the enemy much time and effort? Why not let him go through the trials and tribulations of expensive and fruitless experimentation? Must we pinpoint the answer. Sure it's news, but what goal is achieved by stating those facts to the populace of the nation. The only purpose we can see, and we are not sure about this, is that it might tend to impress our might upon those who may eventually become embroiled in a war with us. Fine, but couldn't the same have been done without disclosing the answer to the problem of making small A bombs . . . By simply stating that small A heads have been developed for shells . . . Isn't the desire for news sort of jeopardizing our security?

Municipal Activity in TV Training

Of interest is the fact that the Service Committee of the Radio and Television Manufacturers Association (of which we are a member) is embarked upon a project of preparing a television technician's course outline for transmittal to vocational and other interested schools. The industry recognizes that shortages in trained electronics personnel are imminent. It is not expected that the course will be used as is, but it is hoped that the liaison which will be attempted by the Service Committee will be productive in creating interest among educators to develop such men as will meet the needs of the television servicing industry.

National Association


Recently, the National Electronic and Service Dealers Associations was formed in Washington. In the main, or rather at the moment, it is represented by television service personnel locally organized in Washington, D. C., throughout the states of Pennsylvania, New Jersey and New York. It is understood that representatives from local associations in other parts of the country also were present at the meeting.

We have had the good fortune to become familiar with the activities of the Federation of Radio Servicemen of Pennsylvania and the Empire State Federation of Electronic Technicians Association in New York State. They have done a great deal towards improving the welfare of their members, and, while it cannot be said that they have solved all of their problems, the fact remains that their existence has done a great deal for the betterment of the industry as a whole in those states.

The aims of this national organization are declared to be the following: 1) The furtherance and improvement of the electronic servicing industry; 2) To promote the welfare of servicing dealers and technicians; 3) To promote a better understanding between electronic service industry and the electronic industry; 4) To promote and secure better relations with the public; 5) To provide educational facilities for its members; 6) To

(Continued on page 16)

THERE IS A REASON!

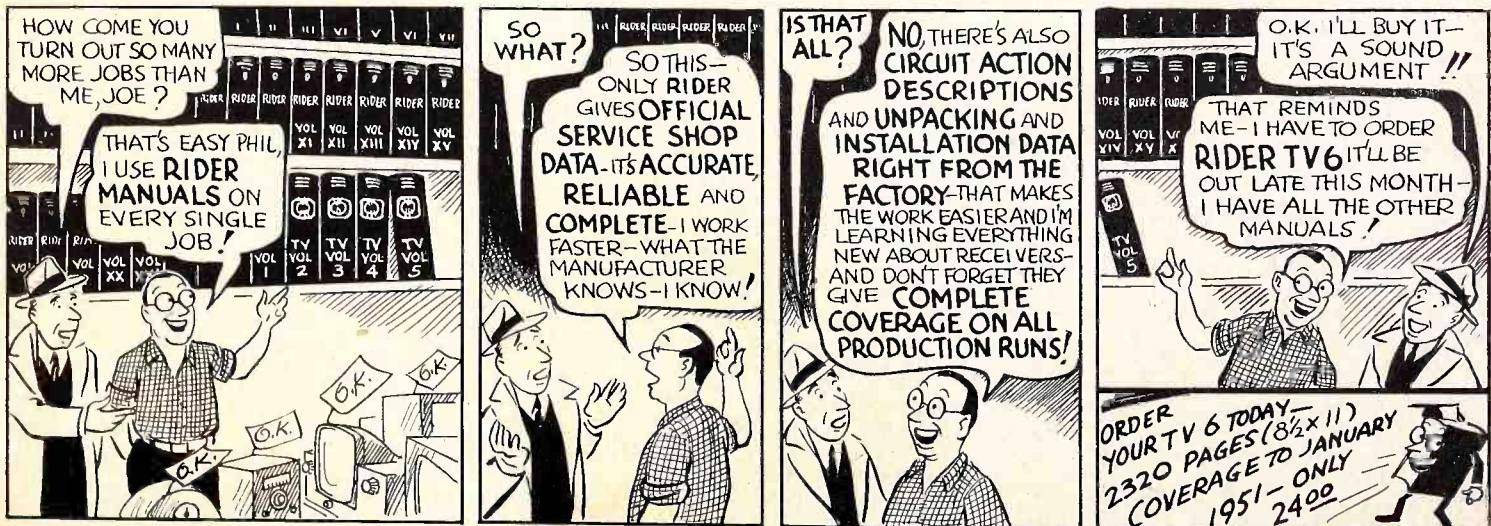

BUYERS

of RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

Say:

"Exceptional, no comparison to anything in the market today."

J's Radio Service Station, Medford, Mass.

"'Worth its weight in gold' to any serviceman faced with the present tube shortages."

G.M.A., Ewing, Nebr.

"Nothing like it, not only in Radio servicing, it just can't be beat in TV servicing."

F.L.D., Carrollton, Ohio

"... A must for every serviceman's bench. The most practical book on this subject I've ever seen. Would not hesitate to recommend it."

C.C.H., Philadelphia, Pa.

"... is the answer to my six months search through supply houses for just the tube manual to simplify tube substitution... It already seems as handy as my soldering iron. Thank you for the best technical book of these times."

A.A.P., Denison, Tex.

"This guide is a must for every serviceman. Simplifies tube problems."

W.H.McG., Leicester, N. Y.

"Indispensable to any Radio Technician regardless of his ability."

G.E.W., Birmingham, Ala.

"... gives clear detail, explanation of the subject, and how to do it. On this subject what more can a serviceman ask?"

L.J.B., Baltimore, Md.

"It is the best book I ever worked with. It saves many tedious hours of going through Tube Manuals."

F.J.S., Jr., Wyandotte, Mich.

"Just typical of everything else John F. Rider publishes — NOTHING BUT THE BEST—And I think it is worth at least three or more times what you charge for it. I have read it thoroughly and don't see how any service shop could be without it even when tube shortage does not exist. RIDER IS AGAIN FIRSTEST WITH THE BESTEST. THANKS A MILLION."

J.R.A., Jr., Millen, Ga.

- 2500 Radio And TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

Including material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors — Capacitors — Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, and Converting Farm Radio for Electrified Operation.

224 Pages in Heavy Durable Paper Cover. 8 1/2 x 11 inches. Only **\$2.40**

Do you have your copy?

GET IT TODAY!

Your favorite electronic parts jobber can supply you, or get it from us.

MAIL THIS COUPON NOW

JOHN F. RIDER PUBLISHER, INC.

480 Canal St., New York 13, N. Y.

Please send me.....copies of "RECEIVING TUBE SUBSTITUTION GUIDE BOOK" at \$2.40 per copy. I am enclosing check ☐ money-order ☐ in the amount of \$..... If, within 10 days, I am not satisfied—I will return the book(s) in good condition, for refund.

NAME.....

ADDRESS.....

CITY.....

ZONE.....

STATE.....

3-51

Westinghouse H-196A. H-207A

(Continued from page 2)

Chassis	Chassis	Chassis	Chassis
V-2130-1	V-2130	V-2130-1	V-2130
C328	C139	R440	R85
C329	C135	R441	R99
C330	C50	R443	R102
C331	C60	R445	R24
C332	C68	R447	R115
C333	C67	R448	R111
C334	C75	R449	R116
C335	C74	R450	R119
C336	C76	R452	R117
C337	C77	R453	R118
C338	C91	R454	R122
C339	C135	R455	R126
C340	C83	R456	R127
C342	C100	R457	R130
C343	C101	R458	R131
C344	C113	R459	R132
C345	C7	R460	R133
L301	L11	C401	C33
L302	L12	C405	C52
L303	L13	C406	C53
L304	L14	C407	C54
L305	L15	C408	C55
L306	L16	C409	C61
L307	L17	C411	C71
L308	L18	C414	C79
L309	L19	C415	C80
L310	L20	C416	C116
L311	L21	C417	C117
L312	L22	C418	C81
L313	L23	C419	C84
L314	L24	C420	C85
L316	L8	C421	C86
L318	L10	C422	C87
L320	—	C423	C82
Section 4—Sweep		C424	C89
R401	R3	C425	C88
R402	R4	C426	C90
R403	R5	C427	C92
R404	R6	C428	C93
R405	R7	C429	C94
R406	R8	C430	C96
R407	R9	C431	C97
R408	R10	C432	C104
R409	R29	C433	C105
R410	R30	C434	C106
R411	R35	C435	C109
R412	R36	C436	C110
R413	R37	L401	L30
R416	R47	L402	L27
R417	R87	L403	L28
R418	R48	L404	L35
R419	R30	L405	L33
R420	R55	L406	L34
R422	R56	L407	L31
R423	R62	L408	L32
R424	R63	L409	L25
R425	R64	L410	L26
R426	R68	Section 5—Power	
R427	R130	R501	R50
R428	R72	C501	C35
R430	R78	C502	C36
R431	—	C503	C37
R432	R79	C504	C98
R433	R81	C505	C102
R435	R84	C506	C103
R437	R88	C507	C107
R438	R76	C508	C108
R439	R77	L501	L29


The parts list for Chassis V-2130-1 is the same as that for Chassis V-2130 except for the following changes (the reference numbers are those for Chassis V-2130-1):

Ref. No.	Part No.	Description
R113	V-5911	Tuner assembly, r-f
C109	—	Resistor, 1,000 ohms
R210	RC20AE103M	Capacitor, 680 μ f
C206	RCM20C271K	Resistor, 10,000 ohms, 1/2 w
R215	R5CC21ZY471M	Capacitor, 270 μ f
C210	RC20AE103M	Capacitor, 470 μ f
C348	R2CC30CK050D	Resistor, 680,000 ohms, 1/2 w
L320	V-5902-2	Capacitor, 5 μ f
R408	RC20AE101K	Coil assembly, video peak-ing
R342	V-6304	Resistor, 100 ohms, 1/2 w
R417	RC20AE105M	Control, vertical hold, 2 megohms
R431	RC20AE561K	Resistor, 1 megohm, 1/2 w
R458	V-5963	Resistor, 560 ohms, 1/2 w
		Resistor, horizontal damp-ing, 7,800 ohms.

**RIDER TV VOL. 6 IS ON THE WAY
ORDER YOUR COPY NOW**

Philco 49-1002, 49-1040 Code 121

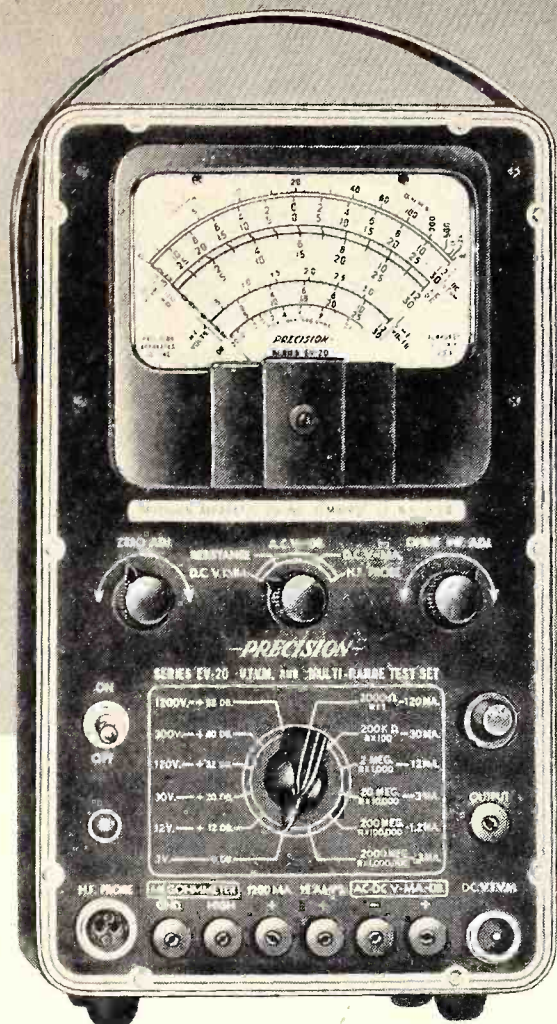The connection from the screen grid pin 8 of the 6BG6G horizontal output tube through R536 should be connected to the 320-volt bus that is the junction of R538 and C521, instead of to the point now shown, which is pin 6 of J501, R504, and R103.



A Compact, Versatile, Portable
Circuit-Testing Laboratory for
TV — FM — AM
The New
PRECISION
SERIES EV-20
VTVM and Multi-Range Test Set

Net Selling Price ... **\$68²⁵**

A Modern, Portable VTVM—Megohmmeter.
TRUE ZERO-CENTER on ALL VTVM ranges
PLUS Direct Reading High Frequency Scales
ALSO, complete, standard 1000 ohms per volt functions
48 RANGES TO
1200 Volts*, 2000 Megohms, 12 Amperes, +63DB

* D.C.-VTVM ranges to 12,000 and 30,000 Volts when
used with Series TV Super-High Voltage Test Probe.

Range Specifications

- ★ SIX ALL-ZERO CENTER VTVM RANGES: —13½ Megs. Constant Input Resistance. ±3, ±12, ±30, ±120, ±300, ±1200 volts. Direct Reading to ±12 KV and ±30 KV with Series TV Super-High Voltage Test Probe
- ★ SIX SELF-CONTAINED OHMMETER-MEGOHM-METER RANGES: 0-2000 - 200,000 ohms.
0-2-20-200-2000 Megohms.
- ★ FOUR DIRECT READING HIGH FREQUENCY VTVM RANGES: 0-3-12-30-120 volts. (When used with RF-10A High Frequency Vacuum Tube Probe, Net Price \$14.40. No crystal rectifiers employed.)
- ★ SIX AC-DC AND OUTPUT VOLTAGE RANGES at 1000 ohms/volt. 0-3-12-30-120-300-1200 volts.
- ★ EIGHT D.C. CURRENT RANGES: 0-300 microamps. 0-1-2-3-12-30-120-1200 milliamperes. 0-12 Amperes.
- ★ SIX DECIBEL RANGES from —20 to +63DB. Calibrated for 600 ohm, 1 mw., zero DB reference level.

IMPORTANT FEATURES

- ★ VOLTAGE REGULATED—BRIDGE CIRCUIT.
- ★ DIRECT READING. ALL ZERO-CENTER VTVM —indicates BOTH Polarity and Magnitude without switching or test lead reversal.
- ★ MASTER RANGE AND FUNCTION SELECTORS eliminate frequent and inefficient shifting of test leads.
- ★ SHIELDED CONNECTORS for both D.C.—VTVM and RF—VTVM. Permits simultaneous and non-interfering connection of both Circuit Isolating Test Probe and optional H.F. Vacuum Tube Probe Series RF—10A.
- ★ HIGH FREQ. VOLTAGE SCALES—Direct Reading.
- ★ DUAL-BALANCED ELECTRONIC BRIDGE OHMMETER—MEGOHMMETER uses two 1.5 volt flashlight cells easily replaced at rear of cabinet.
- ★ 1000 OHMS/VOLT MULTI-RANGE FUNCTIONS permit simple AC-DC voltage, DB and current measurements free of power line requirement.
- ★ 4½" RECTANGULAR METER—200 microamperes, ± 2%. Double-Sapphired, D'Arsonval construction.
- ★ 1% Film type. Metallized and Wire-Wound resistors for all shunts and multipliers.
- ★ Heavy gauge, round-cornered, louvred steel case with plastic handle. Etched, anodized, aluminum panel.


NET SELLING PRICE \$68²⁵

Complete with coaxial Circuit Isolating Test Probe, Shielded Ohmmeter Test Cable, Standard #227 Super-Flex Test Leads, Ohmmeter battery and full operating instructions.

Case dimensions—10½" x 6¼" x 5"

Shipping Weight: 11 pounds.

CODE:—Party

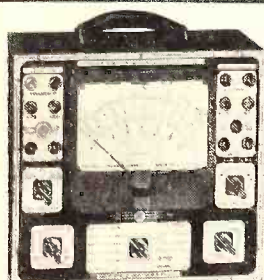

Also ask to see the "Precision" Series EV-10, DeLuxe VTVM—Megohmmeter with extra-large 7" meter. 59 self-contained ranges to 6000 volts and 70 DB.

Series EV-10, affords to the discriminating instrument purchaser, and equipment-conscious service-laboratory, the ultimate in visibility and performance.

EV-10-P
(Closed portable)—\$97.25
EV-10-MCP (Illustrated)
(Open Lab. Type)—\$94.50.

See complete EV-10 specifications on page 4 of latest Precision catalog, available at leading radio equipment distributors or write directly to factory for full details.



PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York
Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex

Television Changes

Sentinel 412, 413, 414, 415, 421, 422, 1U412, 1U413, 1U414, 1U415, 1U421, 1U422

Models 421, 422, 1U412, 1U413, 1U414, 1U415, 1U421, and 1U422 are similar to Models 412, 413, 414, and 415, except for the changes noted in the following paragraphs. The service notes for Models 412, 413, 414, 415, Series YA, YB, YC, and YD, also apply to the above models. The changes written up for the YG Series are changes that were made starting with Series YG.

L-7 and R-24, the video load choke assembly, Part No. 20E363-7, is used in Models 412, 413, 414, 415, Series YA, YB, and YC only. Starting with Series YD, in all models, Part No. 20E363-10 is used. R-24 is 10 megohms. R-29, connected from ground to pin 2 of the 1st i-f amplifier, is not used in Models 421 and 422.

The following changes have been incorporated in the above models starting with Series YE. R-106, from pin 6 of the video amplifier to ground, was 6000 ohms in Series YA through YD; the value is now 5000 ohms (Part No. 27E1016-4). The value of R-36 has been changed from 180 ohms to 270 ohms (Part No. 27E271-2). The value of R-103 the horizontal centering control has been changed from 30 ohms to 60 ohms (Part No. 28E54). The value of C-82, the dry electrolytic capacitor connected to R-103, has been changed from 500 μ f to 1000 μ f, 5 volts (Part

No. 25E52). The B+ take-off point for the audio section has been moved to the variable tap on the horizontal centering control. A 1500-ohm, 2-watt carbon resistor (Part No. 27E104-5) has been added in series with the output side of the focus coil L-17. The focus control has been rewired across focus coil L-17 and R-114. The value of resistor R-102, connected to the junction of R-101 and R-114, has been changed from 2000 ohms to 1000 ohms 3-watts, carbon (Part No. 27E1016-7), with a 10,000-ohm, 10-watt bleeder resistor connected across the 250-volt line. The 10,000-ohm bleeder resistor was not used starting with Series YF.

The following changes have been made starting with Series YF. The value of the focus coil L-17 has been changed from 1300 ohms to 3000 ohms (Part No. 2E104). The value of R-114 has been changed to 3000 ohms, 3 watts (Part No. 27E1816-8).

In Models 412, 413, 414, 415, starting with Series YD, and Models 421 and 422, starting with Series YA, a 6CB6 or 6AG5 or 6BC5 is used in the r-f amplifier and modulator tube sockets. Always use the same type tube for replacement. Intermixing these tubes may result in loss in sensitivity caused by the differences in tube capacities detuning the circuits and making it necessary to realign the r-f amplifier and modulator stages by spreading or squeezing turns on the coils. The 6CB6 cannot be used in the video i-f amplifier stage. The alignment tables for these models are the same as those given for Models 412, 413, 415 (Series YA, YB, YC), and the changes on video alignment that were noted for Series YD, except that Step Nos. 1 and 2 for Discriminator and Sound I-F Alignment, under Connect Signal Generator should read: In series with .01 μ f to junction of L-4 and C-19 on pin 5 of the 6AU6 video amplifier tube. An r-f choke L-18, Part Number 2E29, has been added from pin 7 of the video amplifier to the junction of the plus terminal of C-31 and R-23. A 0.05- μ f, 200-volt (Part No. 23E216) capacitor C-87 has been added from ground to the 140-volt bus. The 47,000-ohm resistor R-110, connected from fuse F-1 to the junction of C-64 and R-61, has been replaced by two 100,000-ohm, 2-watt resistors, R-110 and R-115 (Part No. 27E104-5). Resistor R-71, the 680,000-ohm resistor that was connected from pin 4 of the 1X2 h-v rectifier to R-57, has been deleted from the circuit and replaced with a direct connection. The value of R-57 has been changed from 470,000 ohms to 1.2 megohms, Part Number 27E1009-5. The 4700-ohm resistor R-97 across the horizontal linearity coil L-17 has been deleted from the circuit. R-53, connected to pin 2 of the 6SN7GT vertical oscillator, is no longer connected to the junction of R-88, R-102, and R-47, but now goes to the junction of R-98, C-81, and the vertical size control R-77.

The following changes apply to Models 421 and 422 starting with Series A. R-106, mentioned previously, has been removed from ground and is now connected to pin 2 of the 12AU7. Resistor R-118, 150 ohms, $\frac{1}{2}$ watt, carbon (Part No. 27E151-2), has been added from the junction of R-106 and pin 2 to ground. Resistor R-89, that was connected from the junction of pin 8 of the 12AU7 and C-62 to ground, is now connected from that

junction to the junction of R-118, R-106, and pin 2.


The parts for Model 414 are given in the change notice for that model, the remainder of the Model 414 cabinet parts are the same as those mentioned for Model 413. The parts for the other models are the same as those appearing in the Parts List for Models 412, 413, and 415, except for the Miscellaneous and Cabinet Parts List for Models 421 and 422 given below:

Part No.	Description
20E580	Pulley assembly for contrast control
20E253-28	Drive cord for contrast control
65E2	Spring, tension for drive cord
20E585	Pulley assembly on channel switch shaft
65E39	Spring "C" type locks pulley assembly on channel switch shaft
20E546-8	Cabinet back assembly with line cord (Model 421)
20E546-9	Cabinet back assembly with line cord (Model 422)
9E25-3	Safety glass (Model 421)
9E40	Safety glass (Model 422)
36E56-3	Mask, picture tube (Model 421)
36E56-4	Mask, picture tube (Model 422)
33E85	Gasket, rubber, for mask-35 in.
20E544-3	Knob assembly, channel switch
20E545-3	Knob assembly, off-on-vol.
37E59	Knob, channel switch, less metal plate
37E59-5	Knob, off-on-vol., less metal plate
37E67	Knob, contrast
37E67-2	Knob, brightness
36E57-2	Metal plate for channel switch knob
36E58-2	Metal plate, for off-on-vol. knob
7E250	Cabinet table, mahogany (Model 421)
7E251	Cabinet console, mahogany (Model 422)
20E550	Built-in antenna assembly (Model 421)
30E154	Trimmer and shaft assembly, for 20E550 antenna, consists of 9" shaft assembled to trimmer capacitor
20E550-4	Built-in antenna assembly (Model 422)
30E154-4	Trimmer and shaft assembly, for 20E550-4 antenna, consists of 12 $\frac{3}{8}$ " shaft assembled to trimmer capacitor
37E61	Knob, antenna tuning (Model 422)
37E62	Knob, antenna tuning (Model 421).

**RIDER TV VOL. 6 IS ON THE WAY
ORDER YOUR COPY NOW**

DuMont RA-105

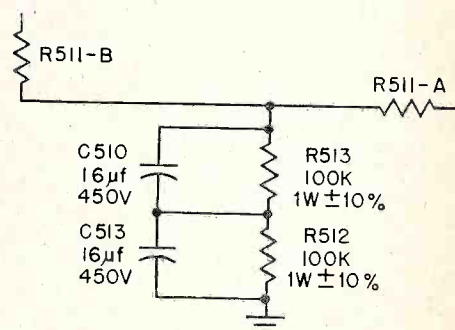Capacitor C510 in the a-m tuner has been changed from 8 μ f, 450 volts, to 16 μ f, 450 volts. In addition, the filter has been changed, as shown in the accompanying figure, by the



Filter used in DuMont RA-105.

addition of C513, R513, and R512. The following parts have been added to the parts list.

Ref. No.	Part No.	Description
C510, C513	03002050	Capacitor, electrolytic, 16 μ f, 450 v
R512, R513	02045010	Resistor, fixed, 100,000 ohms, 10%, 1 w.

In the Video I-F Alignment Table, for step #9, in the column headed "Connect Generator Leads Across," add an asterisk as shown below:

Pin 1 (grid)*
V102 and chassis

In step #3 of the Sound I-F Alignment Table in the column headed "Connect Generator Leads Across" delete the asterisk.

"Little Giant" TWIN LEAD LIGHTNING ARRESTER

Protects TV Sets Against Lightning and Static Charges

NO. AT105
\$7.25
List

For Regular Twin Lead

SEFING IS BELIEVING!

ONLY JFD Lightning Arresters offer you these exclusive patented features...

1. Patented strain-relief Retaining Lip which prevents pulling or straining against contact points.
2. You actually see positive contact made with lead-in wire.
3. Lead-in contact remains fully visible at all times.
4. No wire stripping. No Arrester Cover to Hide Poor Contacts!

At Your Jobber or Write Direct


JFD MANUFACTURING CO., Inc.
6119C 18th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories

Please mention Successful Servicing when answering advertising.

SERVICEMEN: *don't miss this*
fast-growing PROFIT opportunity

20,000,000

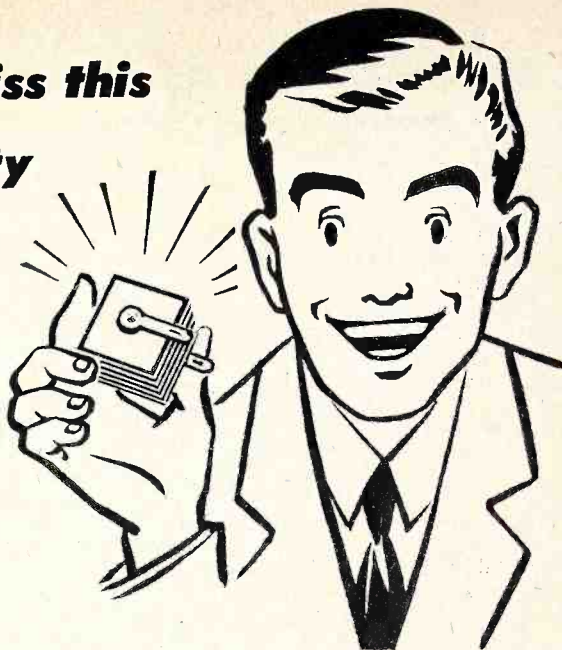**Selenium Rectifiers now used
in TV and Radio Receivers—a
gain of 10,000,000 in a year...!**



**GET YOUR SHARE OF THIS CONTINUING REPLACEMENT
MARKET** *with Federal* **"The Original Miniature
Selenium Rectifier"**

REPLACEMENT ITEMS are of top importance today ... as a source of *steady, extra* income. And one item to keep your eye on is the Miniature Selenium Rectifier ... now at the 20-million mark and growing by millions yearly.

Every time you tap this zooming market, be sure to tap it with a *Federal*—the *original* Miniature Selenium Rectifier. Federal is the leader in quality, for it was Federal that introduced the Selenium Rectifier to U. S. industry ... *pioneered* the miniature for AC-DC, portable, table and console radios ... TV receivers ... plus many other applications.

Get the facts today about Federal—the line with a miniature to meet every replacement requirement—the line that pays you a good profit—pays set owners in A-1 performance!

**Only 8 popular-type FEDERAL
Selenium Rectifiers handle the
majority of today's replacements:**


**THESE 4 HANDLE
80% OF TELEVISION REPLACEMENTS**



1090



1010

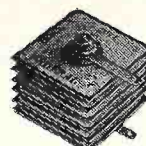

1021



1130

**THESE 4 HANDLE
95% OF RADIO SET REPLACEMENTS**



1002



1003



1004



1005

America's Oldest and Largest Manufacturer of Selenium Rectifiers



Federal Telephone and Radio Corporation



SELENIUM-INTELIN DIVISION

100 KINGSLAND ROAD, CLIFTON, NEW JERSEY

**In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.**

Please mention Successful Advertising when answering advertising.

Television Changes

Montgomery Ward 84HA-3010A,
84HA-3010B, 84HA-3010C

The following production changes have been made on these chassis:

1. Install a 47- μ f ceramic capacitor between pins 2 and 4 of V13, the 6SN7 horizontal oscillator tube.

2. Change R-83 in the horizontal oscillator circuit from 5600 ohms, $\frac{1}{2}$ watt, to 6800 ohms, 1 watt.

Greater White-to-Black Ratio

1. Install 2,200-ohm, $\frac{1}{2}$ -watt decoupling resistor in the 2nd video amplifier (V10) circuit from the junction of R-66 and L-29 to the junction of C-56 and R-67. Change R-67 from 4700 ohms to 2,200.

Improved Horizontal Linearity

1. Install a 20,000- to 30,000-ohm, 10-watt resistor between pins 4 (or 6) and 8 of V21, the 5U4 rectifier tube, if a non-correctable bulge appears on left hand side of test pattern.

Improved Definitions and Focus

1. Some sets do not have C-92, a 470- μ f mica capacitor connected in parallel with R-64, the cathode resistor for V-10 the 2nd video amplifier. Install this capacitor if it is not in the set.

2. Improved range of the focus control, R-103 in the power supply chassis, may be secured by removing R-116, an 1800-ohm, 2-watt resistor.

Increased Sensitivity

1. Increased sensitivity on the high-band channels may be secured by removing the


grounding leads from socket terminal 4 of V-1 and socket terminal 7 of V-2 and grounding these leads directly to the chassis.

2. Capacitors C-9 and C-11 in the tuner assembly should also be removed when the above (1) change is made.

Reduction of 4.5 Mc Hash in Picture

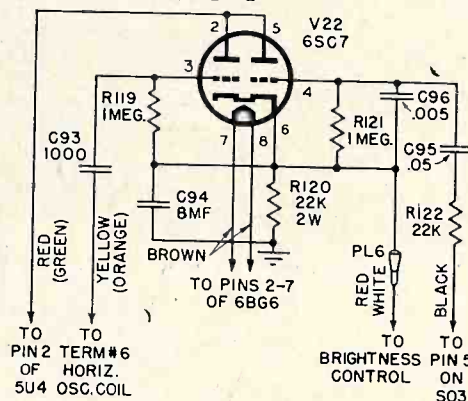1. 4.5-Mc signal hash in the picture may be reduced by installing a $1\frac{1}{2}$ " x 4" metal shield between the discriminator transformer and the tuner chassis. The discriminator coil slug also should be grounded.

After these sets reached the field, a picture tube protective circuit kit was made available for installation on these sets. The purpose of this circuit is to cut off the intense electron beam in the picture tube, in event of failure in either the horizontal or vertical sweep circuits. This prevents burning a line into the face of the picture tube and rendering the tube useless. Components in this circuit are assembled on a small sub-chassis that becomes a part of the power supply unit. The wiring diagram for the protective circuit is shown in the accompanying figure.



Protective circuit for Montgomery Ward 84HA-3010A, 84HA-3010B, 84HA-3010C.

In addition to the components added to the power supply chassis, the following alterations were made in the receiver chassis.

1. Resistor R-29, in series with the brightness control, was changed from 47,000 ohms to 150,000 ohms.

2. Resistor R-120, in the protective circuit, replaced R-30 in the receiver chassis. Therefore, R-30 is no longer used.

Following is a list of the additional parts used in this modification:

Ref. No.	Part No.	Description
C-93	CM20A102K	1,000 μ f, 500 v, mica
C-94	45A103	8 μ f, 475 v, electrolytic
C-95	46AY503J	0.05 μ f, 600 v, tubular
C-96	46AZ502J	0.005 μ f, 600 v, tubular
R-119, R-121	RC20AE105M	1 megohm, $\frac{1}{2}$ w, carbon
R-120	RC40AE223M	22,000 ohm, 2 w, carbon
R-122	RC20AE223K	22,000 ohm, $\frac{1}{2}$ w, carbon
PL-6	10A287	Connector.

RIDER TV VOL. 6 IS ON THE WAY
ORDER YOUR COPY NOW

Stromberg-Carlson TC-19

In the R152 position, the 1000-ohm, 10-watt resistor (Part No. 149216) is being changed to a 1000-ohm, 20-watt value (Part No. 149369) to accommodate the required dissipation.

Successful Servicing, March, 1951

A greater "in-focus" picture area can be obtained if the focus coil assembly is separated by approximately three-quarters of an inch ($\frac{3}{4}$ ") from the deflection yoke on the picture-tube neck. The separation distance is best determined by observing the picture while adjusting the focus coil position.

Loss of the anode high voltage to the kinescope tube often occurs because of poor contact at the junction of the male-female high-voltage connectors. These connectors should be firmly pressed together to assure positive contact. In addition, this connector lead should be dressed away from any miniature tubes to prevent heat deterioration of the connector-lead insulation, which could result in shorting of the high voltage. This high-voltage connector lead should be dressed on the side of the multi-lead cable away from the 12AU7 tubes. (This multi-lead cable is the one that plugs into the top of the main chassis.)

Early production of these receivers were subject to failure of the C231 and C232 (500 μ f, 15,000 volt, Part No. 110595) capacitors in the high-voltage supply, and short circuiting in the L3 deflection coil assembly (Part No. 114672) when internally developed heat deteriorated the insulation between windings. The subject capacitors have been replaced in production by a new type capacitor with smooth sides, a 500- μ f, 20,000-volt unit (Part No. 110680). When replacing capacitors in the field, this new part is being recommended.

A new deflection coil assembly (yoke) is now being used with better insulation properties as well as an open-type casing for better ventilation. The new yokes bear the same part number but are recognizable by the well-ventilated yoke body. When replacing yokes in the field, this ventilated yoke is recommended. In addition, it is recommended that the protective plastic funnel sleeve between the yoke and cathode-ray tube neck be removed entirely for better ventilation.

Because of current capacity requirements, the No. 22 conductor in the wiring of the primary circuit is being changed to No. 16 and the lead length is being shortened.

The following changes should be made on the schematic diagrams:

1. The connector pins labelled 4C, between the brightness control and the kinescope cathode should read 14C.

2. The connector pins labelled 8S, at the bottom end of the vertical deflection coil, should read 7S.

3. There should not be a connecting line from female 1P to the male 1P connector pin, in the X heater supply lead.

4. Pin 2 of V9, the 6AL5 second detector, is used in the chassis as a tie point for R240 and C240 of the agc line. This half of the tube has no circuit function.

5. The midpoint of R157 and R156 should be shown tied to the midpoint of C150 and C151, in the B plus power supply. Likewise, the midpoint of R151 and R159 ties to the midpoint of C152 and C153, in the same supply.

6. On the Trimmer Chart, the adjustment labelled L28, adjacent to the 6AU6 tube (V27), should read L30.


7. Schematic diagram connections around the V28, 6AU6 tube, should be corrected as follows:

- Connect pin 2 to pin 3
- Delete tie between pin 4 and pin 7
- Connect pin 3 to ground end of R280 and remove ground connection.

FREE!

NEW SHURE

Cartridge Replacement GUIDE

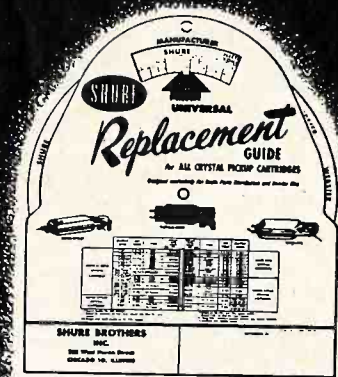

A TURN OF THE DIAL GIVES THE CORRECT REPLACEMENT MODEL OF ALL SHURE CARTRIDGES AND MOST OTHER MAKES

Ask your Shure Distributor for a "Guide"
—or write direct, giving us his name.

SHURE BROTHERS, INC.

Microphones and Acoustic Devices
225 West Huron Street • Chicago 10, Illinois

Please mention Successful Servicing when answering advertising.

Unit switch construction houses precision resistors in insulated recesses.

Easy-to-change standard batteries. Double spiral springs give permanent connection.

Direct connections—no harness cabling—no shorts.

Molded selector switch fully enclosed. Spiral spring index control—over 150,000 cycles without breaking.

Here's why top engineers and technicians use Model 630

Features like those shown above are what make this popular V.O.M. so outstandingly dependable in the field. The enclosed switch, for instance, keeps the silvered contacts permanently clean. That's rugged construction that means stronger performance, longer life. And tests show that the spiral spring index control, after more than 150,000 cycles of switch rotation, has no disruption or appreciable wear! Investigate this history-making Volt-Ohm-Mil-Ammeter today: 33 ranges, large 5½" meter.

ONLY
\$39.50
AT YOUR DISTRIBUTOR



FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplet

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.

Frequency Requirements of Oscilloscope Vertical Amplifiers

(Continued from page 1)

It would do no harm at this time to devote some attention to the composition of the varieties of nonsinusoidal waves previously mentioned. These are but a few of the many which can be illustrated, but they will serve their purpose because they will convey the impression so necessary for the understanding of what will follow.

Composition of a Square Wave

In Fig. 1 is shown a conventional square wave with like positive and negative alternations. The letter E designates the amplitude of the wave. The wave shown is ideal, which means that the rise from zero to the maximum amplitude takes place in zero time. Practically speaking, this is impossible. In such a wave,

the corners are perfectly square and the constant amplitude of the positive alternation and the negative alternation is shown by a perfectly straight line. Whatever the value of E , the voltage rises instantaneously to maximum, remains there for a while, and then falls in a straight line through zero to the maximum amplitude in the negative direction. This may be restated as saying that both the *rise time* and *decay time* are zero.

The period in which a cycle of amplitude change takes place is T , expressed in seconds; the reciprocal of this time, or $1/T$ corresponds to the *fundamental* frequency of the wave in cycles. If, for example, T is 0.0001 second, the fundamental frequency of this wave is $1/0.0001$ or 10,000 cps.

The means of developing a square wave are numerous. It may be the simple expedient of controlling a d-c source, it may be the clipped output of a multivibrator, or it may be the process of successively amplifying and clipping a simple sine wave. While the fundamental frequency of such waves may be obvious because of the apparent association with time, the frequency requirements for proper reproduction are more obscure. The fact that a square wave, or any nonsinusoidal wave, may be resolved into a number of harmonically related sine waves, each of a certain amplitude and relative phase to form a square wave or some other nonsinusoidal wave, is a mathematical approach. This is the Fourier analysis whereby a wave is broken down into its components.

Let us select as our example a sine wave f_1 of 1,000 cps, shown in Fig. 2A. The choice of frequency is arbitrary; what will be said and shown applies to any frequency one may choose. We shall assume that the amplitude of this wave, which is the fundamental frequency, is unity. The starting point of the wave is at the time axis and it advances in the positive direction. We mention this because there is another starting point which is used in the usual mathematical equation for a square wave. This point is 90° later, at the point indicated by the projection from the time base.

We will now add a third harmonic f_3 in phase with the fundamental f_1 and with an amplitude equal to one-third of the fundamental. This is shown in Fig. 2B; the fundamental and the third harmonic are illustrated by the light lines, and the resultant by the heavy line. The ideal square wave is shown by the dotted lines. Several pertinent details warrant mention. A comparison of the sides of the resultant wave, composed of f_1 and f_3 and the fundamental, f_1 , discloses that adding the third harmonic very materially steepens the sides of the wave. A second effect is a modification of the top of the wave on the positive and the negative alternations. The area included by each alternation has been increased and the period representing maximum amplitude has been lengthened.

Let us add the fifth harmonic f_5 to the resultant of the fundamental and the third harmonic. This is done in Fig. 2C; the added

harmonic has an amplitude equal to one-fifth of, and is in phase with, the fundamental. The result is shown by the heavy-line curve and a comparison with the dotted-line square wave illustrates the closer approach to the desired ideal: the sides of the wave have been made steeper; and, while the number of ripples on top have been increased, the area included by each alternation also has been increased; the maximum amplitude condition prevails for a longer time; and the top is flatter than before.

The addition of the seventh harmonic f_7 , equal to one-seventh the amplitude of, and in phase with, the fundamental is shown in Fig. 2D. An improved wave with steeper sides and flatter top is the result. We need not picture any more harmonics because what we have shown is ample to develop the proper line of thought. It is clearly evident that just as the addition of three consecutive odd harmonics to the fundamental transformed the simple sine wave into an approximation of a square wave, the further addition of a sufficient number of odd harmonics would cause very steep sides and a flat top.

Note that as the number of harmonics added to the fundamental increases, the magnitude of the amplitude variations at the top of the wave decreases. With a sufficient number of odd harmonics present, the ripples would approach an infinite number, thus forming a straight line. Two other very significant details can be seen from Fig. 2, namely, that as the wave contains more harmonics, the junction of the sides and the imaginary axis approaches a right angle; also that as the harmonics in the wave are increased in number, the curvature of the sides of the wave at top becomes smaller, ultimately forming a right angle when the number of harmonics contained in the wave is infinite. From the practical viewpoint, these ideal conditions are reached much sooner; that is, as far as the eye can see and equipment can perform, a good square wave is reached with relatively few harmonics.

Two other details deserve attention. One of these is the phase relation between the component frequencies; the other is the fixed amplitude relationship. Although the square wave of Fig. 2D is only an approach to a square wave, it nevertheless enables us to reach some conclusions. The phase is a fixed quantity based upon the mathematical analysis of such a wave. In the example chosen, we used in-phase sine-wave voltages. Exactly the same result will be obtained by the use of cosine waves, the point of origin of each component being 90° later. If you examine Fig. 2B, C, and D, and assume the starting point of each component as being located at 90° , as illustrated in Fig. 2A, it will be evident that the harmonics will alternately start in phase and 180° out of phase with the fundamental.

These references to phase lead to a very important conclusion. In our example, we showed the component phase conditions for the development of a square wave. In practice we are interested in the reproduction of a

(Continued on page 14)

PRICE CHANGES

Rider AM-FM Manual prices have been held in check since the middle of 1948. Many price increases have taken place in our costs. Since June 1950 they have become so great that we are forced to increase the prices of these manuals. We regret that it had to be done — but there was no way out. The following prices now prevail on Rider TV and AM-FM Manuals.


Rider TV Manuals

TV6	\$24.00
TV5	\$24.00
TV4	\$24.00
TV3	\$24.00
TV2	\$24.00
TV1	\$19.80

Rider AM-FM Manuals

XXI (21)	\$21.00
XX (20)	\$21.00
XIX (19)	\$22.50
XVIII (18)	\$22.50
XVII (17)	\$19.80
XVI (16)	\$ 9.90
XV (15)	\$22.50
VII, VIII, IX, X, XI, XII, XIII, XIV each	\$19.80
VI	\$15.00

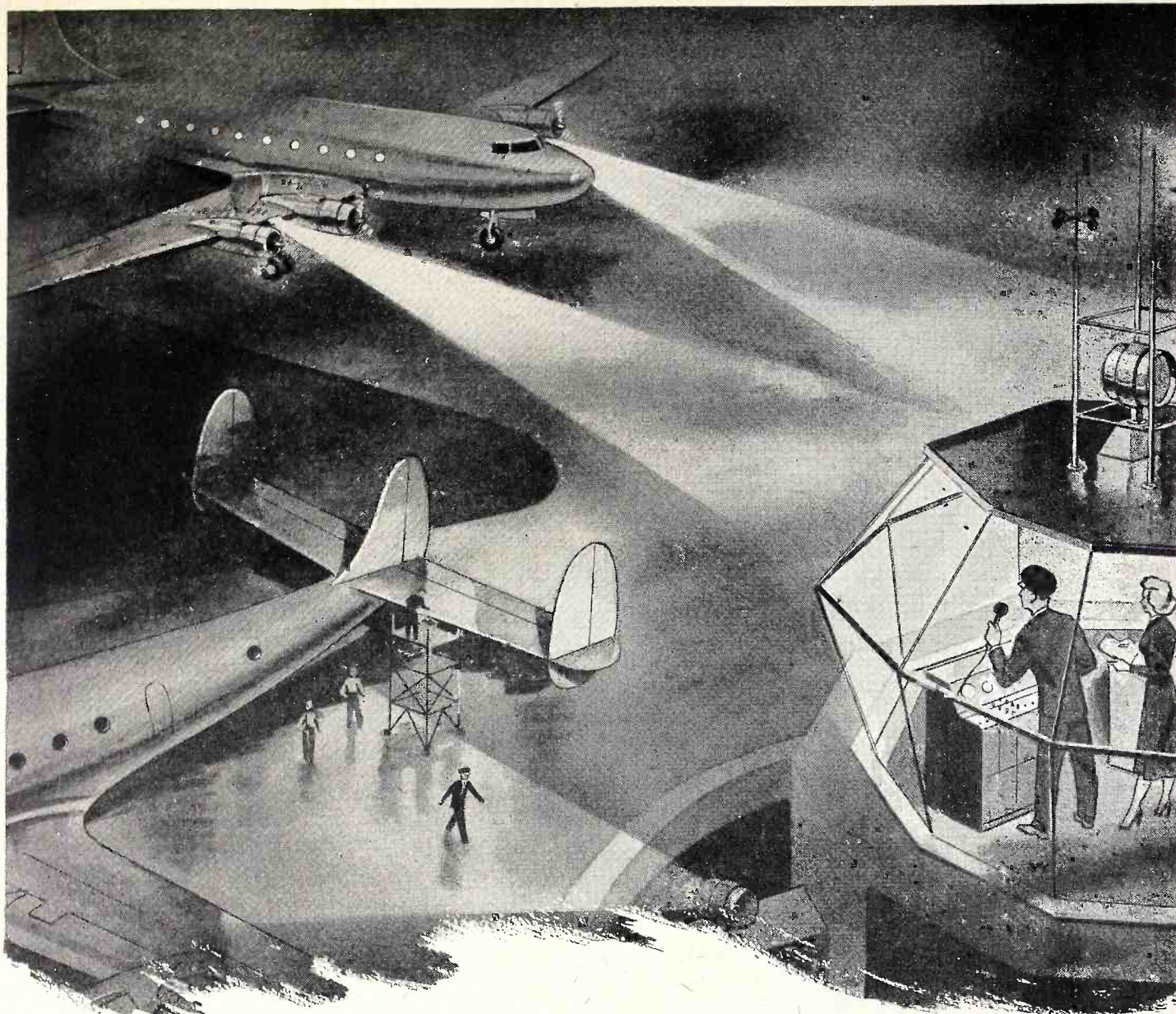There are no price changes scheduled at the moment on Rider textbooks, but if the price of production continues increasing as it has for the past year, a change in those prices is imminent.



No Margin for Error Here...

★ a drifting fog has no heart... it cares nothing of life it holds in the balance. Yet man has conquered its insidious threat in many ingenious methods. One progressive step is radio communication. An important part of every good receiver is the vibrator. Every time it is used may not be a crisis... but it must answer each call with peak performance.

NO MARGIN FOR ERROR HERE... that is why RADIART is specified. Reputation built up over the years for dependable performance has stemmed from superiority in engineering design and controlled manufacture. This same skill of design and manufacture is basic in every RADIART automotive vibrator — it pays to put this skill to work for you.



SUBSIDIARY OF



When It's Needed the Most... RADIART Quality Meets the Challenge

THE RADIART CORPORATION CLEVELAND 2, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES

Please mention Successful Servicing when answering advertising.

Frequency Requirements

(Continued from page 12)

square wave which is fed into a circuit. Since a certain phase condition between the components is assumed to exist in the input voltage, it is imperative for proper reproduction that the same phase condition between components exist in the output voltage. This is the responsibility of the amplifier which is a part of the reproduction system; while it is amplifying the components of the wave, it must retain the phase relationship as well. A change in phase of a component or a group of components will very materially change the output waveshape. This is a matter of amplifier design, and also a matter of evaluating the constants of the amplifier which is used to amplify such waves.


United Motors 984570, Pontiac

A 7Q7 may be used as the oscillator modulator tube in place of the 6SA7. 7C5's may be used as output tubes in place of 6V6GT's. These substitutions do not require any circuit changes.

Capehart-Farnsworth 3001-B, 3001-M, 3002-B, 3002-M, Ch. C-272, Ch. CX-30, Early Version, Series A, A-2, A-3, A-4; 3007-B, 3007-M, Ch. C-276, Ch. CX-30, Early, Series A, A-2

Model 3007-B is similar to Model 3007-M. The control panel for Models 3007-B and 3007-M is given in Fig. 1.

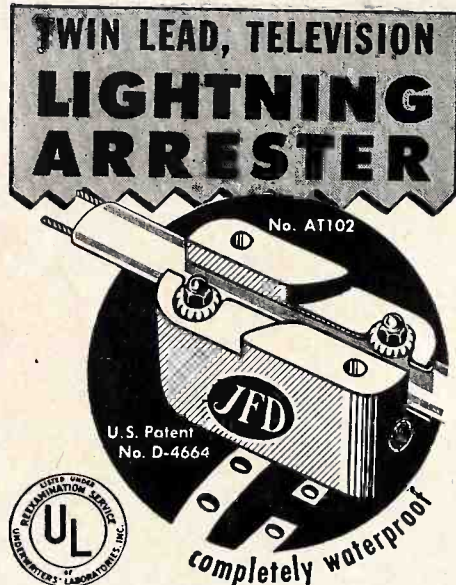The following information is presented as an aid in identifying production runs:



APPROVED for OUTDOOR-INDOOR Use \$2.25
Protects Television Sets
Against Lightning and Static
Charges

Twin Lead
JFD SAFE TV GUARD

Simple to install everywhere and anywhere
...no stripping, cutting or spreading of
wires. More than 300,000 in use today!

SEE YOUR JOBBER OR WRITE TO

JFD MANUFACTURING CO., Inc.
6119C 15th Avenue, Brooklyn 4, N. Y.
First in Television Antennas & Accessories

Please mention Successful Servicing when answering
advertising.

Chassis No. C-272 (12½" crt) used in Models 3001 and 3002:


1st production run referred to as "Early Version."

2nd production run referred to as "A" Series.

3rd production run referred to as "A-2" Series.

4th production run referred to as "A-3" Series.

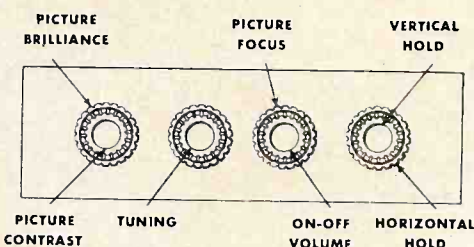5th production run referred to as "A-4" Series.



Control panel for Models 3007-B and 3007-M.

Chassis No. C-276 (16" crt) used in Model 3007:

1st production run referred to as "Early 3007" (equivalent to A-2 above).

2nd production run referred to as "A" Series (equivalent to A-3 above).

3rd production run referred to as "A-2" Series (equivalent to A-4 above).

Early Version CX-30 chassis had no electrical centering controls and no 6H6 tube. The 12SN7 sync stage was used for d-c restoration and sync clipping.

The "A" series chassis may be identified by the letter "A" stamped on the rear chassis apron preceding the serial number. This chassis employs an improved video amplifier circuit, electrical horizontal centering control, a modified focus control circuit, a change in grid loading of the third and fourth pix i-f stages, a modification in the horizontal scanning circuits including the feedback loop which is a part of the afc circuit, and some changes in the high-voltage supply section.

The "A-2" series chassis has the letter "A" preceding the serial number and "-2" following the serial number (i.e. A666666-2). This chassis is the first to use the 6H6 tube for d-c restoration and sync clipping. The 12SN7 sync amplifier and clipper was modified to provide improved sync pulse amplification and shaping.

The "A-3" series chassis (i.e. A000000-3) is very similar to the A-2 series. The only changes were the addition of an electrical vertical centering control and a further modification of the focus control circuit.

The "A-4" series is the final version of the CX-30 chassis. The 6H6 d-c restorer has been modified to provide a pre-sync clipping action with sync being taken off at this tube rather than the video amplifier load circuit. Also, the 12SN7 sync amplifier and clipper has again been modified by some small changes in component values. The feedback loop from the horizontal output transformer back to the horizontal oscillator has been removed. An additional 80-μf filter capacitor has been added at the input of the filter, and the heater returns for V11 and V12, 6AU6 driver and 6T8 ratio detector—first audio, have been made directly to B minus.

The first 16" models were similar to the 12½" "A-2" models except for picture tube

Successful Servicing, March, 1951

mounting, the arrangement of front panel controls, the negative power supply for the horizontal amplifier and the addition of the 6J5 tube in parallel with the output section of the vertical multivibrator tube. The "A" series 16" chassis is comparable to the A-3 series 12½" chassis on which the vertical electrical centering control was added.

The "A-2" series 16" chassis is the final production run and is comparable to the A-4 series 12½" chassis except for those differences noted above which adapt the chassis for 16" tube operation.

The schematic for Series A-3, Models 3001-M, 3002-B, and 3002-M, is the same as that for the A-2 Series.

The following parts should be added to the parts list:

Part No.	Description
Models 3007-M & 3007-B	
850067A-1	Speaker (12" e-m)
450540B-1	Brilliance, horiz. hold and focus knobs (3 required)
450541A-1	TV channel indicator knob
450542A-1	TV tuning knob (3007-M)
450542A-2	TV tuning knob (3007-B)
450543A-1	Vertical hold, volume & contrast knobs for 3007-M (3 required)
450543A-2	Vertical hold, volume & contrast knobs for 3007-B (3 required)
450836A-1	"Built-In" antenna phasing control knob (3007-M)
450836A-2	"Built-In" antenna phasing control knob (3007-B)
850062A-1	Safety glass escutcheon
450868A-1	Mounting strap for escutcheon
850060A-1	Plastic mask
750130A-G2	"Polatenna" assembly.

General Electric 509, 530

Catalogue items RWL-009 and RWL-106 should be deleted from the Parts List and replaced by the following items: RWL-025, Cord, power cord and plug (brown, heavy duty type) for Model 530; RWL-024, Cord, power cord and plug (white, heavy duty type) for Model 509.

TV AND OTHER RECEIVING ANTENNAS

The following review of Arnold B. Bailey's TV AND OTHER RECEIVING ANTENNAS appeared in the March 1951 issue of *Radio & Television News*:

"This book is a happy combination of both theoretical and practical material on the subject of receiving antennas, with special attention being given to the television antenna.

"Designed for television engineers, television technicians, antenna design engineers, students, teachers, hams, and broadcast station personnel, this text is a logical development of the subject matter. Treatment is straightforward and generally non-mathematical.

"The author has divided his subject matter into twelve main topics covering a review of definitions and antenna terminology, the television signal and its bandwidth, problems in television reception, the electromagnetic wave, the radio path, the theory of signal interception, the center-fed zero-db. half-wave antenna, a comparison of zero-db. half-wave antennas, parasitic-element antennas, horizontally-polarized antennas, vertically-polarized antennas and special types, and the practical aspects of TV receiving antennas.

"The author's tremendous grasp of his subject has not caused him to lose sight of the immediate problem of imparting this knowledge in an understandable fashion. The book should find wide audience among both beginning and advanced students of the subject."

**REACH OUT FARTHER...
AND BRING 'EM IN STRONGER!**



JFD

"Long Ranger"

YAGI TV ANTENNA ARRAYS

with High Impedance
Driven Element for
Direct Match to 300
Ohm Lead-in.

Five-element beam, custom-cut to exact wavelength of channel, delivers more powerful forward gain with high front-to-back ratio rejecting co-channel interference.

FAST and EASY installation

JFD YAGI antennas are completely pre-assembled at the factory. Just swing the "Quik-Rig" elements into position and tighten the wing nuts.

These all-aluminum JFD "Long Ranger" YAGI antennas are something to shout about... because even the really remote stations are now being pulled in with satisfactory viewing results. And JFD advanced design plus sturdy construction assure durability and long-lasting, trouble-free performance. Let these superior JFD YAGI installations help you e-x-p-a-n-d your television market.



**Especially recommended
for fringe and remote
areas!**



5-Element YAGIS

LOW BAND

No. 5Y2 (Channel 2)
No. 5Y3 (Channel 3)
No. 5Y4 (Channel 4)
No. 5Y5 (Channel 5)
No. 5Y6 (Channel 6)
No. 5Y7 (Channel 7)

HIGH BAND

No. 5Y8 (Channel 8)
No. 5Y9 (Channel 9)
No. 5Y10 (Channel 10)
No. 5Y11 (Channel 11)
No. 5Y12 (Channel 12)
No. 5Y13 (Channel 13)

"Long Ranger" YAGI antennas for all of the above channels are also available in stacked arrays.



MANUFACTURING CO., Inc.

6119C 16th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories

Write for FREE Technical Data Sheet No. 59

Curtain Time

(Continued from page 5)

raise the standards of the electronic servicing profession; 7) To cooperate with federal, state, and municipal agencies.

Temporary elected officers are: President—Max Leibowitz (N. Y. C.), Vice-President—Norman R. Selinger (Wash., D. C.), Corresponding Secretary—Richard R. Devaney (Phila., Pa.), Recording Secretary—Roger K. Haines (Haddenfield, N. J.), Treasurer—Vance E. Beachley (Harrisburg, Pa.). Samuel L. Marshall (N. Y. C.) was appointed chairman of the Inter-relations and Publicity Committees; James L. Burns (Wash., D. C.) chairman of the Membership Committee; and Frederick J. Schmidt (Steelton, Pa.) chairman of the Steering Committee.

The address of this new association is Dorchester House, 1625 Kalorama Road, N.W., Washington, D. C.

Our Pet Peeve

Too many commercials on TV programs! Plays lend to commercials between acts but variety shows do not. Most certainly motion picture presentations cannot accommodate intermission periods and commercials.

A Reminder

"Is not he imprudent, who, seeing the tide making haste towards him apace, will sleep till the sea overwhelms him?"—*Tillotson* . . . Why wait to buy your Rider Manuals; for on each occasion when you need them, and you do not have them, you lose an unnecessary

amount of time. A service facility sells time and knowledge. Anything which saves time, reduces costs and increases income. Time is money. Examine your Rider library. If you are shy a volume, buy it today. Have It When You Need It. Remember that it will work for you for years to come. Think back. How many years have your Rider Manuals been working for you?


JOHN F. RIDER

Successful Servicing, March, 1951

for this amplifier with the volume control is shown in the accompanying illustration.

The CT254A uses type "S" tuner, #700320-8, which is the same as is used in Chassis CT224, except that a 6AB4 or a 6C4 may be used as the V3 oscillator. A 1000-ohm resistor, R15, has been added from the junction of C5 and R8 to pin 7.

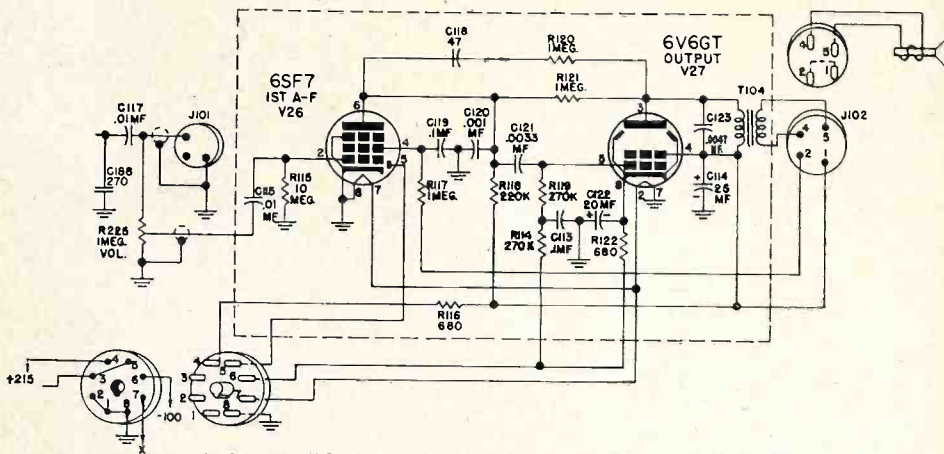Chassis CT254B uses type "R" tuner, #700317-2, which is the same as that used in Chassis CT235, except that a 680- μ f capaci-



Audio amplifier used in Magnavox CT254A and CT254B.

Magnavox CT254A, CT254B

These chassis are similar to Chassis CT224 and CT235. All of the data applicable to the CT224 and CT235 are applicable to the CT254A and CT254B except as noted below.

Chassis CT254A and CT254B are designed for use in models which feature television only. A #123B audio amplifier and a #220076 volume control have been added. The schematic

tor, C19, has been added from ground to the junction of L79 and the terminal pin, and resistor R14, 1000 ohms, connected to the converter transformer now goes to terminal pin 6.

The 6T5 AGC delay has been deleted. Terminal pin 3 goes to the X filament leads, and the connection from pin 6 that went to the 6T5 now goes to pin 3 of the socket shown in Fig. 1. A 0.0015- μ f capacitor has been added from pin 3 of the 6AG5 4th video i.f. (V11) to ground. A 1000-ohm, 2-watt resistor has been added in parallel with the focus coil.

The parts list for the audio amplifier is as follows:

Ref. No.	Part No.	Description
R114, 119	230104-91	Resistor, carbon, 270,000 ohms, 1/2 w
R115	230104-110	Resistor, carbon, 10 meg-ohms, 1/2 w
R116, 122	230105-60	Resistor, carbon, 680 ohms, 1 w
R117, 120, 121	230104-98	Resistor, carbon, 1 meg-ohm, 1/2 w
R118	230104-90	Resistor, carbon, 220,000 ohms, 1/2 w
C113, 119	250201-13	Capacitor, paper, 0.1 μ f, 600 v
C115	250201-7	Capacitor, paper, 0.01 μ f, 600 v
C118	250159-96	Capacitor, mica, 47 μ f, 500 v
C120	250201-1	Capacitor, paper, 0.001 μ f, 600 v
C121	250201-4	Capacitor, paper, 0.0033 μ f, 600 v
C123	250201-5	Capacitor, paper, 0.0047 μ f, 600 v
C114	270023-10	Capacitor, electrolytic, 25 μ f, 600 v
C122	270027-8	Capacitor, electrolytic, 20 μ f
T104	320027-4	Output transformer
J102	180382-8	Speaker cable socket.

**RIDER TV VOL. 6 IS ON THE WAY
ORDER YOUR COPY NOW**

General Electric 505, 506, 507, 508

Catalogue items RWL-009 and RWL-016 should be deleted from the Parts List and replaced by the following items: RWL-025, Cord, power cord and plug (brown, heavy duty type) for Models 505, 507, 508; RWL-026, Cord, power cord and plug (ivory, heavy duty type) for Model 506.

WHAT REVIEWERS SAY ABOUT OUR BOOKS!

The following review of TELEVISION INSTALLATION TECHNIQUES by Samuel L. Marshall, appeared in the February, 1951, issue of *Proceedings of the I. R. E.*

"This outstanding book was written as a reference and handbook, primarily for the television service man, but it is of great interest to the experimenter, the engineer, and the service manager.

"The first four chapters of the book present a well-balanced discussion of the nature of television, radio propagation antenna and transmission lines, and transmission and special antenna systems, supported by a clear-cut discussion of the essential theory, and supplemented by specific design methods and practical design information to meet almost any installation requirement.

"The next two chapters entitled, 'Materials and Methods used in Installations' and 'High Mast and Tower Installations,' cover the installation of antennas in primary service areas, with particular regard to safety and best installation practices. In the case of the high mast and tower installations, the principles of construction design formulas and data to take care of wind and ice loadings, and special design considerations are discussed in detail for most types of masts and towers.

"Two chapters are devoted to problems arising from television installations and receiver

adjustments in the home. Problems in connection with reflections, multiple installations, fringe area operations, television interference, TV filters, and the adjustment and servicing of sets in the home are covered in a most factual and satisfactory manner.

"The last chapter, 'Municipal Regulations,' covers safety precautions in general, and the National Board of Fire Underwriters Bulletin 275, the municipal codes and television ordinances of many of the cities of the United States.

"The Appendix includes a great deal of useful information in its ten tables and three charts pertaining to vhf TV stations on the air: Data on coaxial cables and transmission lines, data relative to the safe loads of anchors, bolts and guy cables, tape sizes, and a list of the various sizes and characteristics of cathode-ray picture tubes.

"This book includes authoritative information describing the best field practices in the installation of antennas to meet practical field problems and the installation and servicing of receivers to give maximum satisfaction to the customer, and points out the importance of attention to details in installations, both in the interest of the customer and of safety."

LEWIS M. CLEMENT
Crosley Division
Avco Manufacturing Corporation
Cincinnati, Ohio

"Sure we can fill many Shoes"



See how versatile SYLVANIA tubes help you solve shortage problems

Yes, radio tubes are still in short supply. But, Sylvania is doing its utmost to serve all its loyal customers.

Production facilities are being increased, and all Sylvania Distributors are being taken care of on the fairest possible allocation basis.

But, there's *no shortage* in ingenuity at Sylvania! Now this company offers you service dealers a great new tube substitution manual.

Here's a complete classified listing to assist service technicians and engineers in making substitutions for tube types not immediately available. This booklet includes circuit modifications and substitution directions for battery types, 150 ma. and 300 ma. types, as well as for Transformer and Auto Tube types . . . Television Tubes and Picture Tubes, too.

40 pages of valuable, up-to-the-minute information . . . FREE from Sylvania. Get your copy from your Sylvania Distributor NOW, or mail the coupon below.



This book is being given away FREE by Sylvania as a service to its good friends, the country's radio-television service dealers.



SYLVANIA ELECTRIC

Sylvania Electric Products Inc.
Dept. R-2703, Emporium, Pa.

Please send me new booklet "Sylvania Tube Substitution Manual."

Name _____

Street _____

City _____ Zone _____ State _____

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS
Please mention Successful Servicing when answering advertising.

Midwest KC-16

The mixer coil plate should be grounded to the front apron of the chassis with tinned copper braid to reduce f-m—r-f regeneration.

RCA T100, Ch. KCS38; T120, Ch. KCS34C

Current production of 10" and 12" television receivers are employing two different types of deflection yokes. One yoke is the older type, which had an iron wire wrap core. The new type yoke has a powdered iron core. The two yokes are easily identified in that the older iron wire wrap yoke has a cardboard outer housing, while the new powdered iron yoke has a molded bakelite housing.


The two yokes are not directly interchangeable, for while the iron wire wrap yoke will work in the circuit designed for the powdered iron core yoke, the powdered iron yoke would not be employed in the circuit designed for the iron wire yoke unless suitable circuit modifications are made.

In receivers employing the "electronic magnifier" deflection circuit, R191 was 470,000 ohms for the iron wire wrap yokes. This value has been changed to 220,000 ohms as a compromise value for both types of yokes.

Early T100 and T120 receivers with straight deflection systems employed a 1-megohm resistor for R181 when the iron wire wrap yoke was used. Later, some were built using a 150,000-ohm resistor which gave

more width and high voltage with the wire wrap yoke. When the powdered iron yoke is employed, R181 should not be less than 470,000 ohms (which gives greatest width), nor higher than 1 megohm (which gives the best linearity). A 470,000-ohm resistor is now being used in production as a compromise which is suitable for either type yoke.

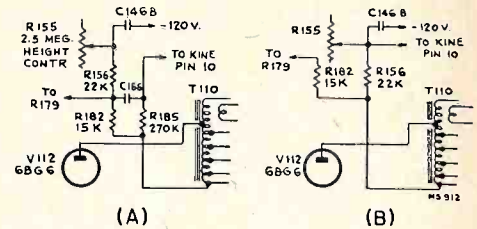Vertical Non-Linearity: T120 receivers employing the powdered iron core yokes have another modification necessary to prevent poor vertical linearity, this showed up as cramping at the bottom of the picture. The non-linearity was corrected by raising the vertical oscillator plate voltage by changes in the B boost filter as shown in the accompanying figure.



Filter connections (A) for iron wire wrap yoke, (B) for powdered iron yoke.


This change also prevents the formation of an extremely bright spot on the screen immediately after the set is turned off. If C146B develops excessive leakage it will cause the picture to be cramped at the bottom.

Raster Ringing: In most cases, the iron wire wrap yoke, type 201D3, will be supplied under stock numbers 71420 and 74262. In the 201D3 yoke, the 56- μ f capacitor across a portion of the horizontal deflection coil is connected across yoke terminals 1 and 2. Before installing the yoke, check the schematic of the receiver in which the yoke is to be installed. Some models require that the capacitor be between terminals 1 and 2, and other models specify between terminals 2 and 3. In the latter case, the capacitor must be reconnected. Failure to connect the capacitor properly will result in bad raster ringing. Except for the connection of the capacitor, the type 201D3 is an exact duplicate of the iron wire wrap yokes used in production.


If excessive raster ringing occurs on the left side of the picture of current 10" and 12" receivers, and the yoke capacitor is correctly connected, and the circuit appears normal, then remove the yoke red lead from terminal 4 of T110 and reconnect it to terminal 5. This reduces the ring at the possible slight expense of linearity. This modification is applicable to regular and electronic magnifier deflection systems.

If raster ringing occurs near the center or right side of the raster, it may be caused by misadjustment of the linearity control coil. Proper coil adjustment is best made by turning the core counter-clockwise all the way and then clockwise until the ring just moves off the right side of the picture. Normally the core stud is just about flush with the outside of the chassis. This adjustment is applicable to both the regular deflection system and to the electronic magnifier system.

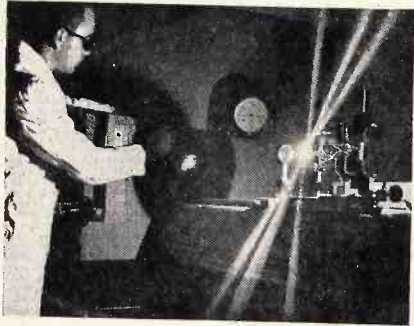On receivers with electronic magnifier deflection system, if the raster rings on the left side with the picture in the normal size, it may help to change the R-C network (C178, R188) in parallel with the series width coil from 10,000 ohms and 330 μ f to 5,000 ohms and 470 μ f.



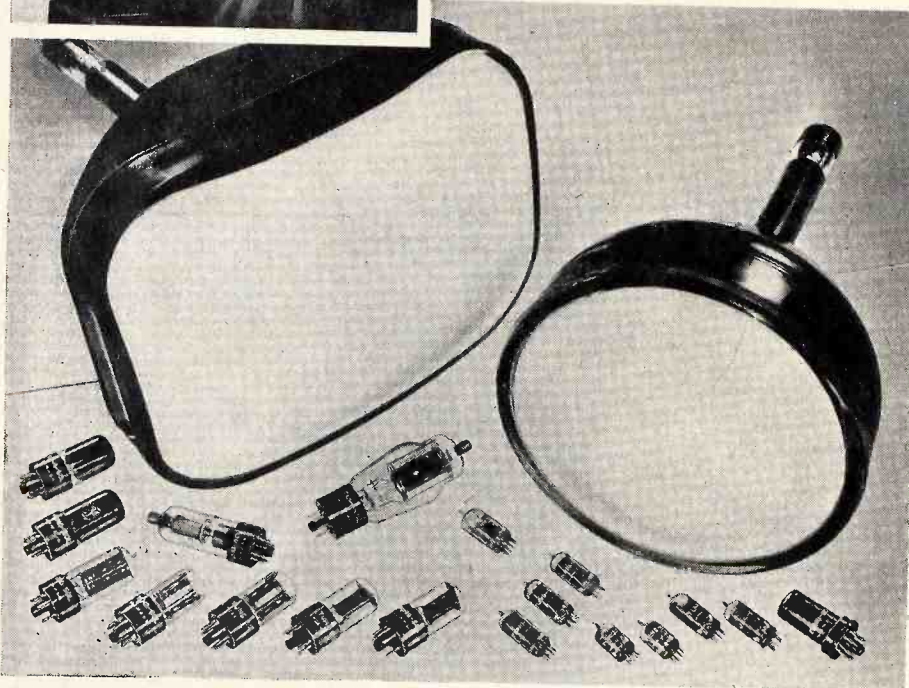Quality is built-in not "tested-in." Nevertheless, the guarantee of built-in quality is unlimited testing. Here is one of TUNG-SOL'S numerous and exacting quality control tests—the chemicals used in the screen of the TUNG-SOL picture tube are analyzed in the spectrograph to determine purity.



ENGINEERED to keep pace with the growth of the electronic industry.

MANUFACTURED to quality standards which meet fully the performance requirements of every leading radio and television set manufacturer.

*You can't buy
a better tube than*

TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

TUNG-SOL LAMP WORKS INC., Newark 4, N. J. • Sales Offices: Atlanta
Chicago • Dallas • Denver • Detroit • Los Angeles • Newark
Please mention *Successful Servicing* when answering advertising.

WE GUARANTEE that RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is... what it can DO... and HOW to use it properly!

ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usan

The FIRST and ONLY book that so fully and clearly describes the 'scope... its construction... its capabilities... its applications in communications, engineering, research... with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you... **WHAT** each type can do...
HOW to use it... and **WHICH** is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians—all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages... 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home... municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY** and **IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth BoundAnd only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Usan



The entire system of frequency modulation is explained thoroughly... all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

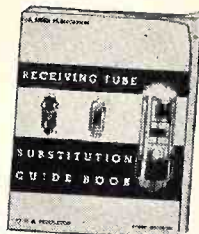

For AM-FM-TV Receivers and Allied Equipment!

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

EXTRA! In addition to tube information... this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc....

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New... Revised... Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman



All the **QUESTIONS** and **ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH**... a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer. It also lists "extras" not ordinarily found in a volume of this type... including Useful Appendices which take in Small Vessel Direction Finders and Automatic Alarm.

766 Pages, Hundreds of Explanatory Diagrams...\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc.... in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed, how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth boundOnly \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.

Radio Changes

Emerson 672B, Ch. 120097-B

The 672B is similar to Model 634B in that both models use a 120097-B chassis. The service data and Parts List for 672B, Ch. 120097-B, are the same as those for the 634B except for the cabinet parts listed below:

Part No.	Description
140396	Cabinet
470092	Lid support
620145	Chassis mounting board
580138	Shielded lead wire (25")
450099S	Knob
450099	Knob
587011	Spring insert
700053	Loop antenna
410807-1	Dial back plate
530002	Drive cord (37")
525022-1	Pointer.

Crosley 11-100U, 11-101U, 11-102U, 11-103U, 11-104U, 11-105U, Ch. 330

Chassis 330 is similar to Chassis 301, which is also used with the above models, except that the 330 uses a 12SQ7GT (V3) in the detector—avc 1st a-f amplifier stage, whereas the 301 uses a 12AV6. The 12SQ7GT is connected in the following way: pin 1 goes to the shield; pin 2 goes to the junction of R5 and C8B; pin 3 goes to the junction of ground, pin 4, and C8A; pin 5 goes to tap 2 of the 2nd i-f transformer T2, pin 6 goes to the junction of R8, C8C, and C8D; pin 7 goes to pin 3 of V1, and pin 8 is grounded. The voltage readings are as follows: pins 1, 3, 4, and 8 are 0 volts; pin 2 is -0.8 volt; pin 5 is -0.6 volt; pin 6 is 52 volts; pin 7 is 12 volts a.c.

The following part should be added to the parts list: TS2, Part No. W-46447-1, Shield, tube (V3).

United Motors 980899, Buick

The value of the 7259128 (Illustration No. 35) electrolytic capacitor has been changed so that all sections are now 20 μ f. Thus, the cathode bypass capacitance on the output tube has been raised from 10 μ f to 20, and the schematic should be altered to comply with this change.

The 470-ohm resistor (Illustration No. 63) in the cathode string of the 6R8 bucking diode circuit has been eliminated after Serial No. 94295.

General Electric 402

R2, shown connected to B+, should cross over the vertical B+ lead to pin 6 of V2, and a dot connection should be drawn at the vertical B- lead to pin 2.

Sparton 1080A, 1081A, Ch. 8L10

Model 1080A in mahogany and Model 1081A in blond are radio-phonograph combinations using radio chassis type 8L10. All of the information on Chassis 8L10 is contained in the service notes for this chassis.

Philco 50-621

This model completed production without change and appears as Run #1 only. The following corrections and additions have been made to the Parts List:

Part No.	Description
34-8003-1	Selenium rectifier, 100 ma, CR1
10761-3	Cabinet, brown
10761-4	Cabinet, beige
10761-5	Cabinet, green
54-4712-3	Back, brown
54-4712-4	Back, beige
54-4712-5	Back, green
Delete	Front
Delete	Shield base.

Successful Servicing, March, 1951

RCA RP-168 Series

The RP-168 Record Changer Series is used in the following instrument models:

Record Player Attachments 9JY, CP-5203, 45J, QJY

Record Players (without radio) 9EY3, 9EY31, 9EY32, 9EY35, 9EY36, 45EY, QEY3

Radio-Phonograph Combinations 9QV5, 9W51, 9W78, 9W101, 9W102, 9W103, 9W105, 9W106, 9Y7, 9Y51, A55, A78, A106.

Radio-Phonograph-Television Combinations 9TW309, 9TW333, 9TW390, TA128, TA129, TR126, S1000

Detailed drawings (see Fig. 1) and descriptions for the pickup arm assemblies are given below:

SUB-BASE ASSEMBLIES

Type I—Sub-base Stock No. 74070. Has staked studs for spring anchors and one-piece reject lever. Stamped or labelled RP168-1 or RP168-3.

Type II—Same as Type I, except it uses a two-piece reject lever. Use Stock No. 74743 Sub-base (Type III) for replacement.

Type III—Sub-base Stock No. 74743. Same as Type II, except that it has pickup-arm rest on sub-base (when motor-board rest is used, the sub-base rest is to be deformed).

Type IV—Sub-base Stock No. 74468. It uses an a-c input connector and audio output jack mounted on a separate bracket. Labelled RP168-2 and used only with Model CP-5203.

Type V—Sub-base Stock No. 74856. Has turned up lances for spring anchors. Idler wheel mounting plate (45B, Stock No. 74814) is removable. It is labelled RP168-1, RP168B-1, etc. It has pickup-arm rest on sub-base (when motorboard rest is used, the sub-base rest is to be deformed).

NOTE—Two different main levers (director lever) are used, depending upon which turntable assembly is used. Lever (41), Stock No. 74076 has a long end (41C) and is used with Turntables Types I and II. Lever (41), Stock No. 74857 has a short end and is used with Turntable Type III.

Type VI—Stock No. 74803. Similar to Type V, but it does not bear any "RP168" identification. It has pickup-arm rest on sub-base. Idler wheel mounting plate (45B) is secured to the sub-base with a shoulder rivet.

Type VII—Same as Type VI, except it does not have pickup-arm rest on sub-base. Use Stock No. 74803 (Type VI) for replacement (the pickup-arm rest is to be deformed).

NOTE: Type VI and VII—Late production of these types have the idler wheel mounting stud (22) staked to its mounting plate. The idler wheel retainer (horeshoe washer) is Stock No. 75081.

PICKUP-ARM ASSEMBLIES (LESS PICKUP)

Type I—Arm Stock No. 74041. Stamped 970488. Pickup-arm stud (9A) is full diameter for entire length (do not use where pickup-arm rest is on sub-base). Lead counterbalance is riveted to arm. Arm Stock No. 74443. For Model CP-5203 only. Black finish, otherwise similar to No. 74041.

Type II—Arm Stock No. 74824. Same as No. 74041 except that stud (9A) has a flat on one side at bottom end. Can be used with either type of pickup rest. Arm Stock No.

(Continued on page 22)



Opportunity
knocks
...for
you!

BUSINESS OPPORTUNITIES

WANTED—Radio, Music, and Appliance dealers and service stores. Earn substantial extra income. Sell and install high fidelity customers, local merchants, church, town hall, etc. Negligible investment, use present facilities. No special equipment required, only imagination and initiative.

MODEL 6201 COAXIAL SPEAKER

You'll find no compromise in the model 6201—a TRUE coaxial system, completely self-contained, with LC network and attenuator, at a sensible price. Full range response 45 to 15,000 cps, power capacity 25 watts. Highest quality construction throughout—separate Alnico V tweeter driver, exclusive UNIVERSITY "W" shape Alnico V "woofer" magnet, special cone edge treatment for longer life, minimum distortion; and even the famous UNIVERSITY wide angle "cobra" tweeter horn for uniform dispersion of the "highs." Variable attenuator adjusts "balance" to personal preference.

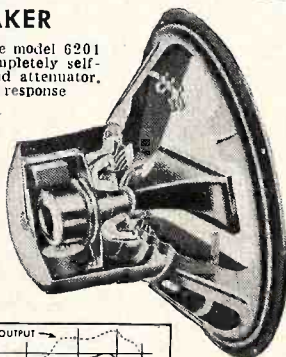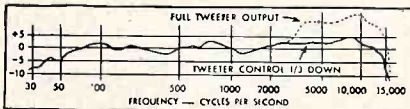

Address
Inquiries to
Desk 33

Write for
new free
TECHNILOG

A comprehensive UNIVERSITY handbook on sound casting technique and equipment. Shows all you need to know about selection and installation of University loudspeaker equipment.



UNIVERSITY LOUDSPEAKERS • INC

80 SO. KENSICO AVE., WHITE PLAINS, NEW YORK


Please mention Successful Servicing when answering advertising.

Here's the **BOOSTER** that says
"YES" to all your demands...



the New AUTOBOOSTER

THE *FULLY AUTOMATIC* TV-FM BOOSTER

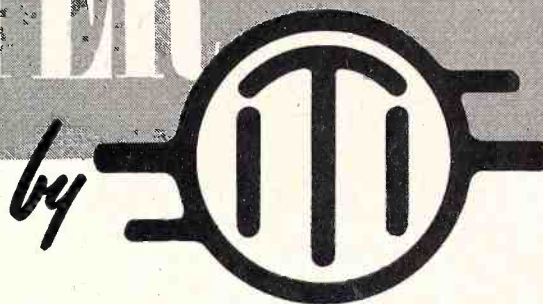

Here at last is a TV Booster that gives you gain up to nine times, full band width for undistorted video and audio on all channels, plus — the newest development in booster design — completely automatic operation.

The ITI AUTOBOOSTER turns itself on and off and is automatically tuned by the normal operation of the TV receiver. No confusing array of knobs — no unsightly mess of wires — You can install the ITI AUTOBOOSTER in the back of the receiver, out of sight. You get all the improved performance, all the fine picture quality that this precision-engineered booster can give you with none of the trouble of tuning, none of the exposed wiring usually involved in booster operation.

Customer acceptance is assured, too, because no customer instruction is needed. After it's installed, all you can see is the improved picture.

- ✓ **AUTOMATIC ON-OFF**
- ✓ **AUTOMATIC TUNING**
- ✓ **CONCEALED INSTALLATION**
- ✓ **SINGLE OR DUAL INPUT**
- ✓ **HIGH UNIFORM GAIN**

**BUY THE BOOSTER
 THAT SAYS "YES"
 to all your PROBLEMS**

WRITE FOR SPECIFICATION SHEET
 ORDER AUTOBOOSTER FROM
 YOUR JOBBER TODAY!



LIST
\$44.95
 F. O. B.
 CLIFTON, N. J.

BOOSTER CHECK LIST						
AUTOBOOSTER	A	B	C	D	E	F
Automatic On-Off	YES	YES	NO	NO	NO	NO
Automatic Tuning	YES	NO	NO	NO	NO	NO
Concealed Installation	YES	NO	NO	NO	YES	NO
Full Bandwidth (All Channels)	YES	NO	YES	YES	NO	NO
Amplifies FM Band	YES	YES	NO	NO	NO	NO
Single or Dual Input	YES	NO	NO	NO	NO	YES
Gain 19db on Low Channels 2 - 6 FM	YES	NO	NO	NO	NO	YES
Gain 14 db on High Channels 7 - 13	YES	NO	NO	NO	NO	NO
Made by a TV Receiver Manufacturer	YES	NO	NO	NO	NO	NO

THE ONLY TV BOOSTER
 DESIGNED AND MADE BY A
 TV RECEIVER MANUFACTURER



INDUSTRIAL TELEVISION, INC.

359 LEXINGTON AVE. - CLIFTON, N. J. - GREGORY 3-0900

RCA RP-168 Series (Continued from page 20)

75058. For Model 45EY only. Two-tone finish, otherwise same as No. 74824.

Type III—Arm Stock No. 75073. Stamped 3R1. Similar to No. 74824 except that a different pivot (9B) is used and the lead counter-balance is fastened to the arm with a screw. Stud (9A) is of smaller diameter at bottom end. Can be used with either type of pickup rest. Use only with No. 74059 pivot arm.

Type IV—Same as Type III except that stud (9A) is of full diameter for entire length. Use No. 75073 for replacement.

Type V—Arm Stock No. 74796. Stamped 3R1. Similar to Type III except that a different pivot (9B) is used and the lead counter-balance spring is not used. A $\frac{5}{8}$ " o.d. counter-balance spring is used. Can be used with either type of pickup rest. Use only with No. 74799 pivot arm.

Type VI—Same as Type V except that stud (9A) is of full diameter for entire length. **REPLACEMENT OF STYLUS**

Use No. 74796 for replacement.

When replacing a stylus, never bend the stylus support wire with crystal pickups (Stock Nos. 74067 and 74625) remove the two screws holding sapphire guard in place and remove the guard. Remove the small nut and washer on the threaded shaft of the sapphire holder and gently push the shaft through the hole in the armature shaft until the sapphire holder assembly comes free. Extreme care should be used when loosening the nut so that the twisting motion does not break the crystal. Take hold of the lower end of

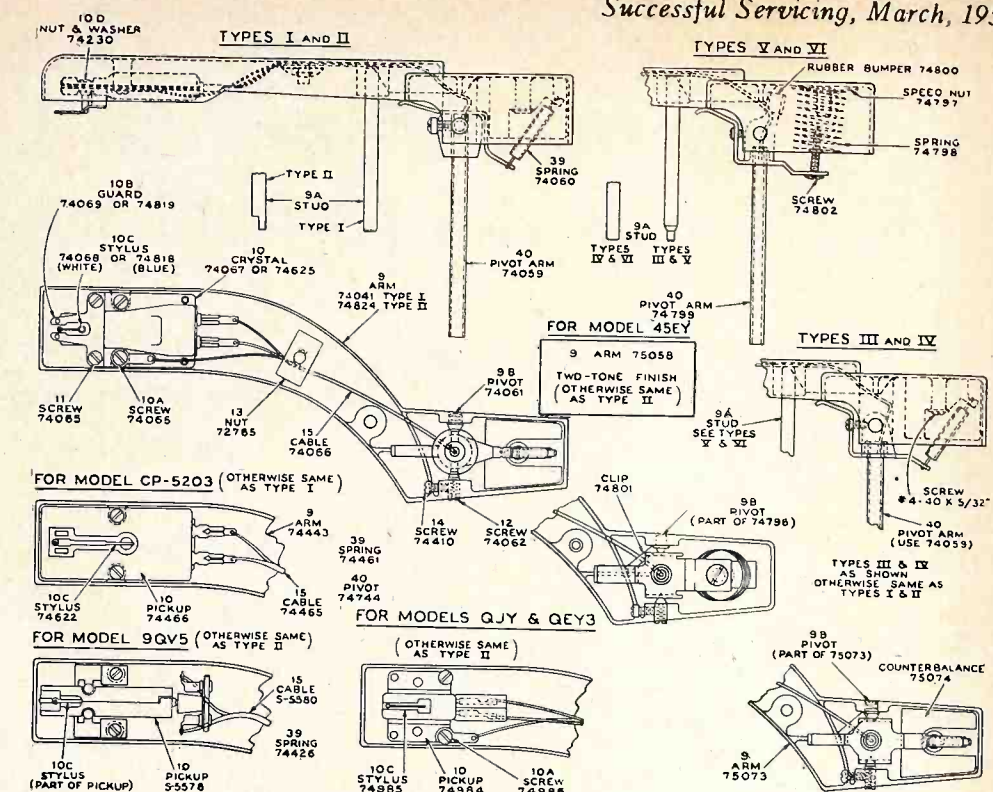


Fig. 1. Pickup arm assemblies for RCA RP-168 Series.

the shaft with a pair of pliers while loosening or tightening the nut, being very careful so as not to strip the threads or break the crystal. Insert threaded shaft of replacement sapphire holder through armature shaft and replace the washer and nut. Make sure that the sapphire is in the correct position. Replace

the sapphire guard, positioning it by means of the oversize screw slots. Make certain that the sapphire and its supporting wire are centered in the guard. Tighten the guard screws. Before using, check to see that the sapphire projects far enough beyond the guard so that the guard will not touch the record. If necessary, bend the guard a little.

When using a variable reluctance pickup (Stock No. 74466) to remove the stylus assembly, insert a bent paper clip or equivalent tool into the stylus stud pin socket (see Fig. 2). Press the assembly out from the

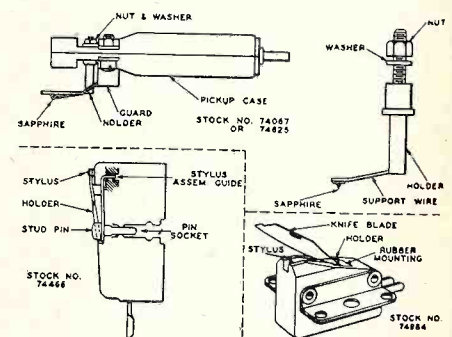


Fig. 2. Stylus replacement.


cartridge with the tool as shown by the arrow in the illustration. To replace the stylus assembly, insert the stud pin into the recess, with the locating tab positioned above the locating slot between the two pole pieces. Press assembly in firmly by applying pressure upon the stud pin with a blunt tool. Care must be taken to press assembly only at this point so as not to damage or distort the stylus arm.

When using a ceramic pickup (Stock No. 74984) to remove the stylus insert the point of a knife blade between the stylus wire and the case. The stylus may be pried out of its rubber mounting with a twisting motion of the knife blade. To replace stylus, push end of stylus wire down into its rubber mounting. Be certain that the stylus is centered in the groove of the pickup case.

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

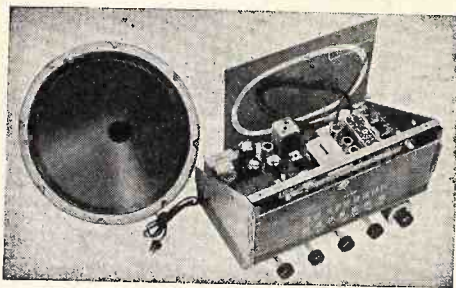Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!



SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

The NEW ESPEY model 511-B FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.

TEL. TrAfalgar 9-7000



the Du Mont type 20_{CP4}

For the set that follows the "seventeen" in rectangular pictures, Du Mont supplies the "twenty" all-glass rectangular Type 20CP4.

Another in the series of Big-Picture Teletrons employing the NEW Bent-Gun for edge-to-edge sharpness that makes the difference in picture tubes of this size. The gray filter face plate improves contrast.

The first picture tube designed with the industry "standard" neck length of 7 $\frac{1}{2}$ ".

Our Commercial Engineering Department invites all design inquiries.

DU MONT
*Teletrons**

Allen B. Du Mont Laboratories, Inc., Cathode-Ray Tube Division, Clifton, N. J.

*Trademark

Please mention Successful Servicing when answering advertising.

63,500

There are 63,500 references to pertinent electronic and allied engineering articles published from 1925 through 1949 in the five editions of the

ELECTRONIC ENGINEERING MASTER INDEX

1925-1945 edition— (15,000 entries).....	\$17.50
1935-1945 edition— (10,000 entries).....	\$10.00
1946 edition— (7,500 entries).....	\$14.50
1947-1948 edition— (18,500 entries).....	\$19.50
1949 edition— (12,500 entries).....	\$17.50

Electronics Research Publishing Company, Inc.
Dept. 55 480 Canal St., New York 13, N. Y.

General Electric 752

A 47- μ f, silver mica capacitor, C3, was added to the circuit of later receivers to prevent parasitic oscillation. C3 has been added from ground to the junction of R6 and the f-m terminal of S1E. In the Visual Alignment Chart, Step 5 of FM-IF Alignment, change adjustment "Core of T4" to read "Core of T9."

Westinghouse H-210, H-211, Ch. V-2144, V-2144-1

For convenience in later production, capacitor C11 that is connected between the common negative line and the chassis is changed to 0.15 μ f, 200 volts, part no. V-6066-2154M.

INDEX OF CHANGES

Model	Page Number
	Successful Servicing From To

TELEVISION CHANGES

Capehart-Farnsworth 3001-B,
3001-M, 3002-B, 3002-M,
Ch. C-272, Ch. CX-30,
Early version, Series A.

A-2, A-3 A-4; 3007-B,
3007-M, Ch. C-276,
Ch. CX-30, Early,
Series A, A-2
3001-B, 3001-M, 3002-B,
3002-M, Ch. C-272, Ch.
CX-30; 3007-M, Ch. C-276,
Ch. CX-30

DuMont RA-105	8	2-5 *2-5	2-33 *2-55, 56
Magnavox CT254A, CT254B CT224, CT235	16	4-1	4-13
Montgomery Ward 84HA-3010A, 84HA-3010B, 84HA-3010C	10	5-1	5-9
Philco 49-1002, 49-1040 Code 121 49-1002	6	2-70 *2-141 4-1 3-1	2-97 *2-196 4-2 3-3
49-1040, Code 121			
RCA T100, Ch. KCS38; T120, Ch. KCS34C T100, Ch. KCS38 T120, Ch. KCS34C	18	5-65 5-80	5-79 5-94
Sentinel 412, 413, 414, 415, 421, 422, 1U412, 1U413, 1U414, 1U415, 1U421, 1U422	8	4-10 C5-3	4-19 —
412, 413, 414, 415			
Stromberg-Carlson TC-19	10	5-1	5-7
Westinghouse H-196A, H-207A, Ch. V-2130-1 Ch. V-2130	2,6	3-1	3-18

RADIO CHANGES

Crosley 11-100U, 11-101U, 11-102U, 11-103U, 11-104U, 11-105U, Ch. 330 Ch. 301	20	21-10 21-1	21-13 21-3
Emerson 672B, Ch. 120097-B	20	21-15	21-18
General Electric 402	20	21-15	21-18
General Electric 505, 506, 507, 508	16	21-32	21-37
General Electric 509, 530	14	21-38	21-42
General Electric 752	24	21-69	21-74
Midwest KC-16	18	21-1	21-5
Philco 50-621	20	20-169	20-172
RCA RP-168 Series	20,22	Rcd. Ch. 19-1 C21-7	19-8 —
Sparton 1080A, 1081A, Ch. 8L10 Ch. 8L10	20	21-1	21-9
United Motors 980899, Buick	20	21-37	21-42
United Motors 984570, Pontiac	14	20-42	20-47
Westinghouse H-210, H-211, Ch. V-2144, V-2144-1	24	19-33	19-35

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

BOOKS FOR THE SERVICEMAN

TV Master Antenna Systems 368 pages	\$5.00
Receiving Tube Substitution Guide Book. 224 pages.....	\$2.40
Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses. 992 pages	\$9.00
TV and Other Receiving Antennas (Theory and Practice). 606 pages.....	\$6.00
TV Installation Techniques 336 pages	\$3.60
Radio Operator's License Q & A Manual, 2nd Edition. 766 pages	\$6.60
The Business Helper 134 pages	\$2.00
FM Transmission and Reception 460 pages	\$3.60
TV Picture Projection and Enlargement. 192 pages.....	\$3.30
Broadcast Operators Handbook 288 pages	\$3.30
Understanding Vectors and Phase 160 pages	Cloth Cover \$1.89 Paper Cover \$0.99
Inside the Vacuum Tube 424 pages	\$4.50
Understanding Microwaves 385 pages	\$6.00
Servicing by Signal Tracing 360 pages	\$4.00
The Meter at Work 152 pages	\$2.00
Installation and Servicing of Low Power Public Address Systems 208 pages	\$1.89
A-C Calculation Charts 148 nomographs in 3 colors 160 pages	\$7.50
High Frequency Measuring Tech- niques Using Transmission Lines. 64 pages	\$1.50
The Oscillator at Work 256 pages	\$2.50
Automatic Frequency Control Systems. 144 Pages.....	\$1.75
Radar — What It Is 72 pages	\$1.00
Radio Amateur's Beam Pointer Guide. 32 pages	\$1.00
Master Index-Volume I to XV.....	1.50

Order Your Copy Now

JOHN F. RIDER PUBLISHER, Inc.

PERMIT NO. 9427
NEW YORK, N. Y.

PAID
U. S. POSTAGE
Sec. 3466, P. L. & R.

LANCASTER, PENN.
437 NEVIN ST.
JOHN L. GIGL

Return Postage Guaranteed
480 CANAL ST., NEW YORK 13, N. Y.
JOHN F. RIDER PUBLISHER, Inc.
From

APRIL, 1951

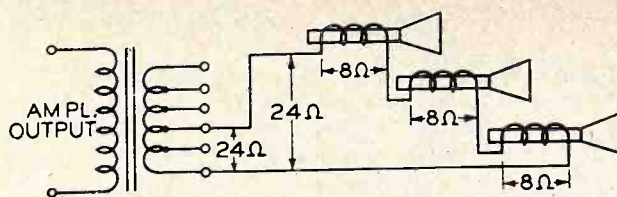


Fig. 1. When three 8-ohm loudspeakers are connected in series, the total impedance will match that of a 24-ohm tap.

LOUDSPEAKER MATCHING

by JOHN F. RIDER

Editor's Note: This article on Loudspeaker Matching is an excerpt from Chapter 3, entitled "Impedance Matching," of *INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS* by John F. Rider, published by John F. Rider Publisher, Inc. The May issue of *SUCCESSFUL SERVICING* will contain another article on the subject of impedance matching.

The matching of one component to another in a p-a system is very important. A bad match between a good amplifier and a loudspeaker will give poor results in terms of power output and fidelity.

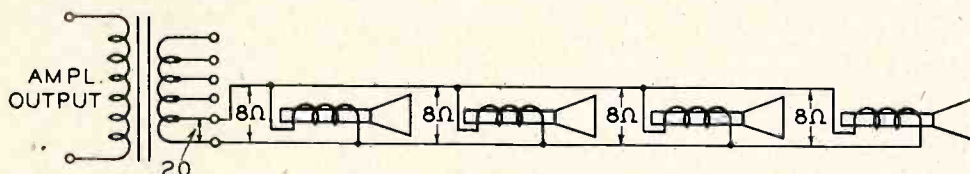


Fig. 2. Four 8-ohm loudspeakers connected in parallel will match the impedance of a 2-ohm tap.

Given an output tube having a stated plate circuit impedance, it is necessary that the loudspeaker voice-coil impedance match the impedance of the plate circuit. For the best possible fidelity, the source and load impedances should match within about 10 percent.

The impedance of a loudspeaker is the impedance of the voice coil and is always included in loudspeaker specifications. This impedance, which is equal to the voltage across the moving coil divided by the current through it, is given at a particular frequency, usually 400 cycles. Voice-coil impedances generally range from 2 to 16 ohms, with most between 6 and 8 ohms, however, in special loudspeakers it may be as much as 50 ohms. When loud-

speakers are directly connected in various types of series, parallel, or series-parallel combinations, the impedance offered by the total load may be anywhere from 0.1 ohm to 500 ohms in commercial practice.

Generally when the distance between the amplifier output transformer and the loudspeaker is about 200 feet or less, the line can be run at the impedance of the voice coil. The term "line impedance" as used here does not refer to any characteristic which the line itself has but means that the conductors are connected to a load of that type impedance. Thus a low-impedance line means that the wires are connected to a low-impedance load. Any combination of loudspeakers can be connected by a low-impedance line.

Matching of Loudspeakers on Low-Impedance Lines

The total load impedance offered by two or more loudspeakers connected in series is

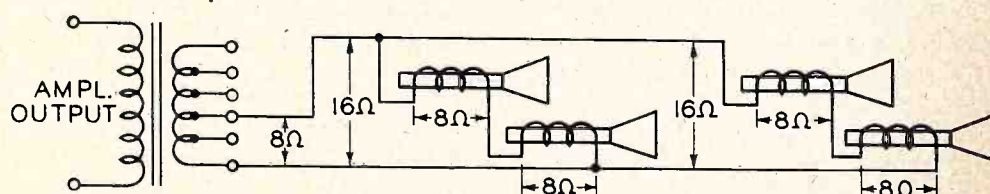


Fig. 3. When four 8-ohm loudspeakers are connected in two parallel branches of two series-connected loudspeakers each, the total load impedance will be 8 ohms.

the sum of their individual impedances. This total load can match the amplifier output by connecting it across the same value of tap

impedances. Thus, if three 8-ohm loudspeakers are series-connected, matching is secured by connecting the entire load across a 24-ohm tap on the output transformer as shown in Fig. 1.

The total load impedance offered by two or more loudspeakers connected in parallel, when all have the same voice-coil impedance, is equal to the impedance of any one loudspeaker divided by the number of loudspeakers. Thus, if four 8-ohm loudspeakers are connected in parallel, the total load impedance $Z_r = 8/4 = 2$ ohms. For proper matching, the loudspeakers should be parallel-connected to a 2-ohm tap on the output transformer as shown in Fig. 2.

The total load offered by four or more loudspeakers connected in series-parallel, when all have the same voice-coil impedance, is equal to the impedance of any series branch line, divided by the number of such series lines that are in parallel. If four 8-ohm loudspeakers are series-parallel connected so that there are two loudspeakers connected in series in each branch and two branches in parallel, then the effective load is $16/2 = 8$ ohms. This load should be connected to an 8-ohm tap for proper matching, as shown in Fig. 3.

Matching on High-Impedance Lines

Where several loudspeakers are situated at some distance from the amplifier and from

each other, then each loudspeaker (or group of loudspeakers) can be matched to a 500-ohm

(Continued on page 10)

Television Changes

Sarkes Tarzian TT3

The following revisions have been made in the TT3: The 6AG5 has been changed to a 6CB6 with no change in the wiring; a 680- μ f capacitor has been added from ground to the junction of R1 and the age lead.

Motorola 9L1

Model 9L1 incorporates a Chassis TS-18 or TS-18A and is electrically identical to the chassis published. The only difference is in the size of the picture tube and the hardware used with 9L1.

Affiliated Retailers AR-16CD,

AR-16CD-3CR, AR-163CR, AR-216,

AR-316, AR-316-3CM, AR-816-3CM

These models are similar to Models AR-16CX and AR-16-3CR, and employ 16-inch round picture tubes.

Muntz M159

Sets below Serial No. 22,000 did not contain a high-voltage filter capacitor as the coating on the outside of the picture tube had a capacitance effect and the capacitor was not necessary. Since picture tubes now leaving the factory do not have an aquadag coating upon the outer surface of the tube, it will be necessary to add the high-voltage filter capacitor Part No. CC-0070, 500 μ f., 20,000 volts d.c. (as shown in the schematic for Model M169), if a new picture tube is installed in chassis below 22,000.


Crosley 10-401, 10-414MU, 10-416MU

It has been found that on some receivers the horizontal oscillator exhibits a tendency to drift causing the receiver to fall out of horizontal sync after operating several hours, or, if the horizontal sync adjustment was made after the receiver has been operating for some time, the picture will not fall in sync when the receiver is cold. This trouble may be attributed to the 0.01- μ f capacitor, C160. This capacitor, if it is of the molded type (Type 487), may change capacitance with temperature change sufficiently to cause the receiver to fall out of horizontal sync. To make correction, replace the 0.01- μ f molded capacitor C160 with a 0.01- μ f, 600-v, paper-type capacitor (Part No. 39001-13).

If trouble is experienced with the above models in centering the picture and reducing the neck shadow, it may be caused by reversed polarity of the focus coil. If this is suspected, the polarity can be changed by reversing the current through the coil. To do this, interchange the leads to the focus coil at the points where they are soldered under the chassis. Try centering the picture again. If the centering action is easier and the neck shadow diminished, and if the angle the focus coil makes with the neck of the picture tube is almost a right angle, the connection is correct. The reason for difficulty in centering, when the focus coil polarity is incorrect, lies in the fact that the magnetic field from the focus coil interacts unfavorably with the field from the ion trap. When the coil is connected correctly, the current flow will pro-

duce a "North Pole" on that face of the coil nearest to the tube socket.

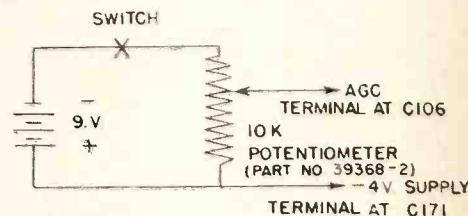Picture and sound separation can be caused by a narrow bandpass of the i-f stages, narrow bandpass of the r-f tuner, or a combination of both. Check the i-f bandpass with a sweep generator, marker, and scope. The response curve should appear as shown for Model 10-401. Check the r-f tuner by substituting it with a unit that is known to be in good alignment.



Battery pack arrangement used as bias for age circuit.

In some cases, when using test equipment to align the above models, or when the gain of the receiver may be affected by another section of the receiver such as improper functioning of the horizontal deflection circuits, it is advisable to substitute a bias for the age circuit which can be adjusted manually to any desired setting. It is suggested that the battery pack arrangement shown in the accompanying diagram be used for this purpose by clipping the two external leads into the chassis wiring at the points indicated. No wiring changes are necessary. A spst switch is employed to break the circuit when the battery pack arrangement is not in use. In order to prevent a run down battery, due to the switch being left turned on, it is suggested that a micro-switch be incorporated in one side of the unit. When the unit is placed on the chassis with the switch down the switch contact will close. When the unit is removed from the chassis the switch will open automatically.

Westinghouse H-605T12, Ch. V-2150-101

In some deflection yokes used in this model, the nut for the deflection yoke adjustment wing-screw may bind with the metal channel in which it rides. The binding makes it difficult to position the yoke snugly against the bell of the cathode-ray tube. If the yoke is not fitted snugly against the bell, shadows may appear around the edge of the crt face. To correct this condition, loosen the deflection yoke adjustment wing-screw and carefully force the deflection yoke forward as required. In extreme cases, it may be necessary to remove the deflection yoke and pry the nut toward the rear of the yoke using a screwdriver.

**ORDER YOUR COPY NOW
RIDER TV VOLUME 6**

Tele King MST14, 14TR, 17CA, 17RO, 114A, 117, 117C, 117CA, 117LO, 162, 173, 516A

These models are similar to Models 116 and 516. Models MST14, 14TR, and 114A employ 14-inch picture tubes. Models 162 and 516A employ 16-inch rectangular picture tubes. Models 17CA, 17RO, 117, 117C, 117CA, 117LO, and 173 employ 17-inch rectangular picture tubes.

VACUUM-TUBE VOLTMETERS

(Revised and Enlarged)

by John F. Rider

The 1951 revision brings the text up to date in its coverage of all types of voltmeters—diode, triode, rectifier-amplifier, tuned, amplifier-rectifier, and slide-back. This is the *only* book that deals exclusively with vacuum-tube voltmeters. The theory and application of the various types are described and presented in completed form—including schematics, parts lists, and maintenance instructions. Examine the Table of Contents. Everything for every VTVM use! Student, service technician, engineer, laboratory, instructor—all can use it to good advantage.

TABLE OF CONTENTS

1—Fundamentals of Vacuum-Tube Voltmeters; 2—Diode Vacuum-Tube Voltmeters; 3—Triode Vacuum-Tube Voltmeters; 4—Rectifier-Amplifier Vacuum-Tube Voltmeters; 5—Tuned Vacuum-Tube Voltmeters; 6—Amplifier-Rectifier Vacuum-Tube Voltmeters; 7—Slide-Back Vacuum-Tube Voltmeters; 8—Vacuum-Tube Voltmeters for D-C Voltage, Current, and Resistance Measurements; 9—Probes for DC and RF; 10—Design and Construction of Vacuum-Tube Voltmeters; 11—Calibration and Testing of Vacuum-Tube Voltmeters; 12—Applications of Vacuum-Tube Voltmeters; 13—Commercial Vacuum-Tube Voltmeters; 14—Maintenance of Vacuum-Tube Voltmeters; Bibliography; Index.

Published April, 1951

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.


213 illustrations
400 pages
5 1/2" x 8 1/2" \$4.50

★ Build Your Service-Sales Future on a Firm Foundation With.....

PRECISION
TEST EQUIPMENT
Standard of Accuracy...

These 5 "Precision" Instruments Provide a Complete, Modern Service Lab...for TV-FM-AM...at only moderate cost.

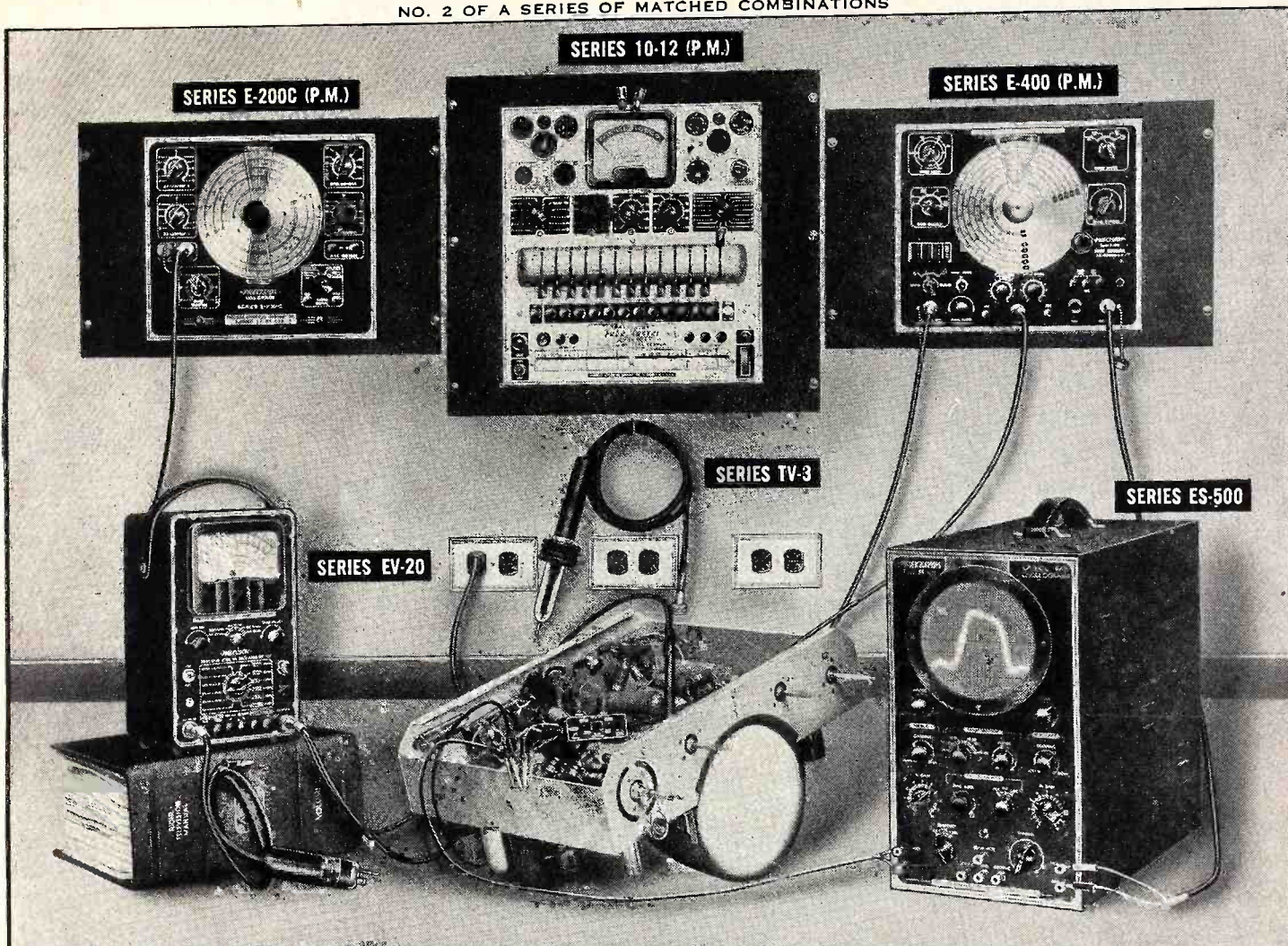NO. 2 OF A SERIES OF MATCHED COMBINATIONS



**SERIES E-200C (P.M.)
SIGNAL AND MARKER
GENERATOR**

Exceptional Accuracy and Stability • Direct reading • 88 KC to 120 MC. • 1000 pt. vernier calibrating scale • 0-100% Modulation • A.V.C. • A.G.C. Substitution network • Complete with output cable and technical manual. In standard panel 19" x 12 1/4".
Net Price: \$71.25

**SERIES E-400 (P.M.)
SWEEP SIGNAL
GENERATOR**

Narrow and Wide Band Sweep for F.M. and TV • Direct Freq. reading 2 to 480 MC. • Multiple Crystal Marker • 8 tubes including V.R. and rectifier • RG/62U Coaxial Terminated Output • Complete with 2 crystals. In standard panel 19" x 12 1/4".
Net Price: \$140.00

**SERIES ES-500
5" OSCILLOSCOPE
Wide Range
High Sensitivity**

V. Amp. Response to 1 MC. • Low C, High R input Step Attenuator • Z axis modulation terminals • 9 tubes incl. V.R. and 2 rectifiers • Complete with light shield and mask • Heavy gauge steel case. 8 1/4" x 14 1/2" x 18".
Net Price: \$159.50

**SERIES EV-20
True Zero Center VTVM
& Multi-range Test Set**

48 ranges to 1200 V., 2000 meg., 63 DB, 12 amps. • Voltage Regulated Bridge Type Circuit • 13 1/3 Megs. D.C. Input resistance • Direct reading high freq. scales • Optional RF-10-A High Freq. Probe • Heavy gauge steel case 6 1/4" x 5" x 10 1/2".
Net Price: \$68.25

**SERIES 10-12 (P.M.)
Electronamic*
TUBE MASTER**

Employs famous "PRECISION" Electronamic tube performance testing circuit plus dynamic Battery Tester • 12 element, anti-obsolete-cent-free-point lever system • Roller-chart • Dual short-check • Noise tests • In standard panel 19" x 17 1/2".
Net Price: \$106.50

SERIES TV-3 SUPER HIGH VOLTAGE SAFETY TEST PROBE. Extends range of Series EV-20 to 30 KV direct reading. Series TV probes available to match most VTVM's and 20,000 ohms per volt test sets. (NOTE: For deluxe Series EV-10 VTVM, with extra-large 7" meter, order Series TV-1 probe.) Net Price: \$14.75

*Reg. U.S. Pat. Off.

BUY PERFORMANCE—NOT SPECIFICATIONS!—BUY "PRECISION"

"PRECISION" PERFORMANCE, ACCURACY, WORKMANSHIP and VALUE have been setting a standard of comparison for over 15 years. DO NOT BE MISLED...It is not "PRECISION" test equipment unless it is manufactured by Precision Apparatus Co., Inc., Elmhurst, L.I., N.Y.

OTHER MATCHED COMBINATIONS

The instruments shown above illustrate one of many possible MATCHED COMBINATIONS of diversified "PRECISION" Test Equipment for TV-FM-AM. Each combination provides a selected and basic, modern, efficient Laboratory at moderate cost.

"Precision" Instruments are on display at leading radio equipment distributors.



PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York

Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

Convenient Purchase Terms can be arranged with your favorite Precision Distributor.

AM • FM • TV •

Please mention Successful Servicing when answering advertising.

New Round Shaft Mallory Midgetrol*

Saves Valuable Installation Time


Single Section Mallory Midgetrol

Now the *time-proved* Mallory Midgetrol offers two important new time-saving features.

This sturdy $\frac{15}{16}$ " control is supplied with a *permanently fixed, tubular brass shaft* that can be adapted for split-knurl or flatted type knobs in a few seconds by inserting one of the two steel shaft-ends packaged

with every Mallory Midgetrol. It gives you utmost convenience—without sacrificing a stable, permanently secured shaft.

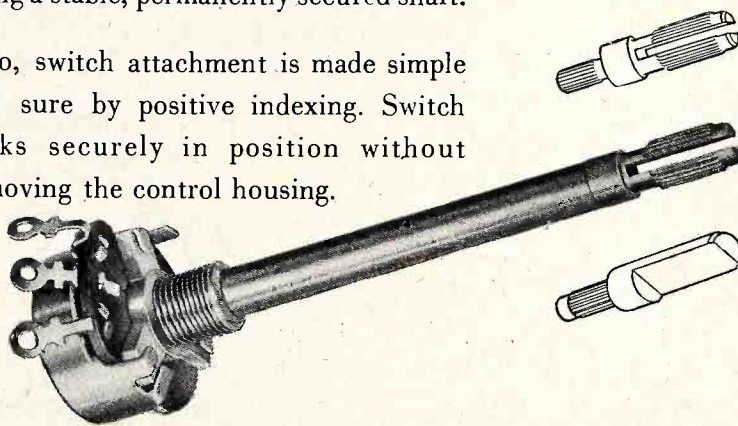Also, switch attachment is made simple and sure by positive indexing. Switch locks securely in position without removing the control housing.




Dual Concentric Mallory Midgetrol

This revolutionary new control can be assembled in five easy steps, in less than five minutes—permits you to match a wide range of combinations immediately from convenient distributor stocks, and without high "time" costs.

The "exploded" view below illustrates the parts and assembled control sections

supplied. Extremely simple instructions show you how to assemble them quickly and surely—without soldering—with only the simplest of tools.

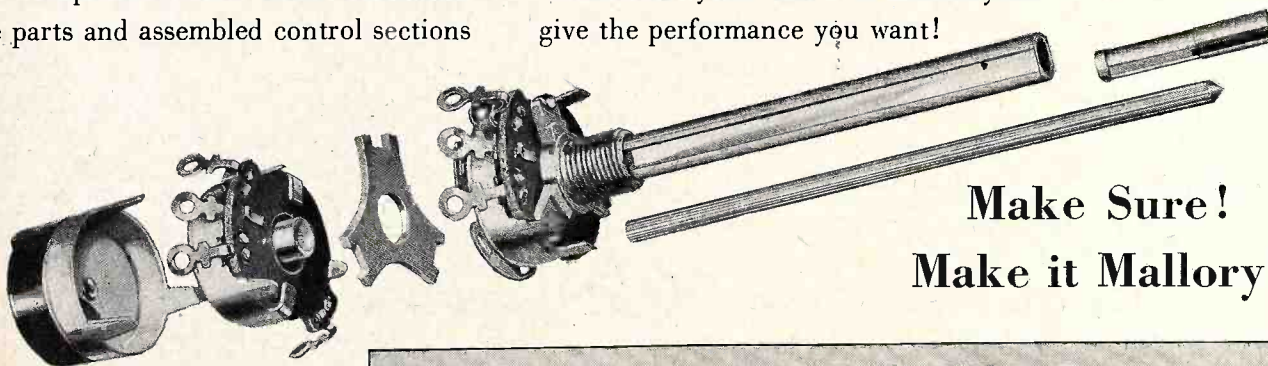Both front and rear sections are *factory-assembled and carefully inspected*. You can be sure that your final dual assembly will give the performance you want!



**Make Sure!
Make it Mallory!**

The Mallory Midgetrol gives you fast, sure, simple installation—with precision-controlled carbon element, smooth taper, quiet operation, accurate resistance value and less drift in TV sets.

*Trade Mark

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

APRIL, 1951

No. 6

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

Worth 4-8340
Worth 4-8341

JOHN F. RIDER, Editor
E. H. BEAUMONT, Associate Editor

Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.



CURTAIN TIME

Time is of the essence in the servicing industry! It is a certainty that it will become even more important as the days and months pass. One of the gripes that is being voiced by many service technicians is the time required to untwine leads wound around a connecting point as a part of the unsoldering operation. The loss of time, however, is not the only source of aggravation. An equally important sore spot is the frequent need for changing the lead dress of adjacent wires and circuit components in order to unwind the connection. Sometimes this is voluntary and, quite frequently, involuntary.

Considering the importance of correct lead dress in TV receivers, and for that matter in r-f, oscillator, and i-f systems of all receivers, it is only natural that the service technician be anxious to keep all unnecessary changes in wiring and component location to a minimum. To be forced to deliberately alter component conditions and then be certain that they are returned to their original locations so that resonance conditions and feedback conditions be normal, is a problem. Of that there is no doubt. We have had the experience ourselves.

Admittedly, a simple expedient when a connection is to be interchanged or a defective part is to be removed, is to clip a connecting wire at the junction point or soldering lug. This is quick, but it is messy and, strangely enough, is viewed with disfavor by meticulous service technicians. Isn't it possible to adapt a standard procedure of hooking the wire through a hole in the soldering lug or around the connecting point and then soldering? This would make the unsoldering operation very much simpler than having to untwist several turns. Quite frequently the solder cools and hardens before the untwisting job is completed, and it becomes necessary to re-heat the junction. If the soldering is done properly during the manufacturing stage, it makes for an equally good connection and a perfectly safe mechanical joint. Above all, it will be a boon to the servicing industry.

Changes

Quite a few of the changes relating to radio and television receivers contained in Rider Manuals and published in *SUCCESSFUL SERVICING* make direct reference to servicing problems being solved by the circuit change. This is very important information, and we

seriously recommend that if time does not permit a complete reading of each circuit change, the change should be glanced at prior to filing. The trouble being eliminated will be remembered even though the exact procedure may not always be retained in the mind. Quite a few of these troubles are obscure and, while tied specifically to one receiver in the reference, may be duplicated in some other receiver. The remedy as given may not be applied "in toto," but at least some direction of approach will be indicated.

The Self-Made Man

Many of the practicing servicemen of America are self-made men. By this we mean that their technical background has been gained by exposure to literature, by continued reading of theory, and, finally, by daily work at the bench. Expanding the storehouse of knowledge in this manner is nothing to be ashamed of for, after all, it is the practice of all people who have had a formal education and must keep up to date with the changing technology. A formal education can do nothing more than lay the foundation upon which more and more knowledge may be piled. As far as the servicing industry is concerned, the circuit descriptions which are contained in Rider Manuals, especially the TV Manuals, are vital sources of technical information. They comprise an education because they explain what happens in the TV receivers which are sold to the public. It is wrong for the serviceman to feel that he does not have time to read circuit descriptions. He *must* find time. The servicing industry is not a static industry. It is continually on the move, and the technical background of every TV technician must expand with it.

JOHN F. RIDER

Sarkes Tarzian TT2

The following revisions have been made in the TT2: L213 is now .180 (was .173); L313 is now .155 (was .160); and L401 is now .165 (was .170).

Tele King 16C03CR, 16CX, 162, 216, 316, 416CAF, 916, 916C, 916CAF, 3163CM

These models are similar to Models 416 and 716 and employ 16-inch round picture tubes.

RIDER MANUALS HELP BREAK RECORDS!



Television Changes

DeWald DT-160

The focus coil has been deleted from the circuit. This information was omitted inadvertently from the change notice on this model that appeared in the February 1950 issue of *SUCCESSFUL SERVICING*.


Affiliated Retailers AR-MST14, AR-MST16, AR-16ATR, AR-114A

Models AR-MST14 and AR-114A are similar to Model AR-14TR and employ 14-inch picture tubes. Models AR-MST16 and AR-16ATR are similar to Model AR-16TR and employ 16-inch rectangular picture tubes.


RCA 8T241 Series

Check to see that the receiver antenna transformer T115 is connected properly and that no windings are open. Remove 8T241 r-f unit and change R11 to 10,000 ohms.

If the receiver is to work in weak signal areas and never to receive a strong signal, then maximum r-f gain can be obtained by installing a small bleeder just to supply —0.5 volts for the r-f amplifier grid. R12 should be disconnected from its present position and reconnected to this —0.5-volt point. Check oscillator injection into mixer. This should read at least —2.5 volts on all channels when measured by a VoltOhmyst at test connection R13. If this is not achieved, adjust the link between L2 and L3 until such injection is obtained.

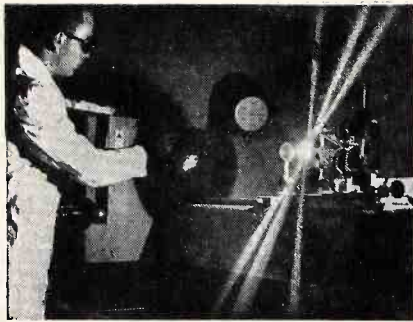

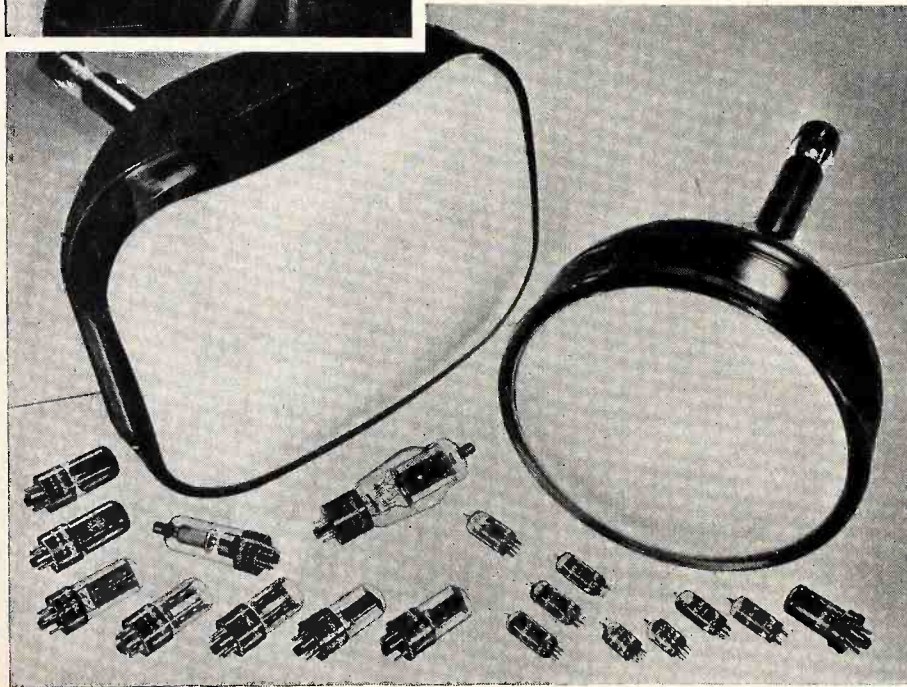Quality is built-in not "tested-in." Nevertheless, the guarantee of built-in quality is unlimited testing. Here is one of TUNG-SOL'S numerous and exacting quality control tests—the chemicals used in the screen of the TUNG-SOL picture tube are analyzed in the spectrograph to determine purity.



ENGINEERED to keep pace with the growth of the electronic industry.

MANUFACTURED to quality standards which meet fully the performance requirements of every leading radio and television set manufacturer.

*You can't buy
a better tube than*

TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

TUNG-SOL LAMP WORKS INC., Newark 4, N. J. • Sales Offices: Atlanta
Chicago • Dallas • Denver • Detroit • Los Angeles • Newark

Please mention *Successful Servicing* when answering advertising.

Successful Servicing, April, 1951

Realign r-f unit for peak performance on the channels to be received.

Change R102 to 68 ohms. Realign the picture i-f making sure that the high frequency slope of the response curve is broad as specified in the service data. If receiver is to be operated in a very weak signal area, place the picture carrier at 60%, or even 80% on the slope. Check to see that the receiver retains proper response at low signal input levels, and —1.0-volt i-f bias. Some change in response is normal, but the picture carrier should remain high on the curve. This alignment causes the picture to be smeared on strong signals but produces the best pictures on signals of less than 100 microvolts.

Make sure that the a-c line feeding the receiver is at least 115 volts at all times, as this radically effects the kinescope anode voltage. If the horizontal deflection system is operating improperly or is incorrectly adjusted, there may be insufficient high voltage on the kinescope. When a "snow flake" occurs, this causes the tube to bloom, making the snow more pronounced. Make sure that all +B voltages are normal, especially the 6BG6 screen. Change R181 to 150,000 ohms. Adjust the drive trimmer as far counter-clockwise as possible. It should be possible to have at least 9000 volts on the kinescope at this point.

Adjust the focus coil carefully so as to obtain best focus in white areas of the picture. Modify the video amplifier to saturate on whites, thus reducing the prominence of the "snow." Disconnect R124 from —120 volt bus and return it to ground. This causes adjustment of the picture control to affect brightness, however, once set, these adjustments can be left alone.

Adjust the agc threshold control counter-clockwise from the normal position to provide the best signal to noise (snow) condition. Unfortunately, this makes the sync more susceptible to impulse type interference such as ignition, etc.

Cut the antenna transmission line length to provide maximum signal. This effect is most noticeable on the high channels.

In general, use the highest gain antenna array that can be had, place it as high in the air as possible and above all surrounding obstacles, especially power lines. In some cases, however, if the electric field is distorted, a simple antenna may produce more signal than an elaborate array, and the height may become critical. In selecting an antenna for gain, make sure that high gain occurs on the channel or channels to be received. Some antennas, in order to reduce size, cut off badly on channel 2, and on some, the response is slightly down even on channel 3. In general, the best antenna or array for any particular channel is one cut for that channel.

Unless bothered with an extremely high noise level (ignition, etc.) the antenna transmission line should be the 300-ohm open type. Coaxial and twinex have higher losses than the open line, which in weak signal areas cannot be tolerated. In time, however, open wire line may foul up and have to be replaced. This fouling shows up as a loss of signal in wet weather.

The above modifications make these receivers so "hot," that a booster is not likely to be of help in the receiving of weak signals.

Tele King MST12, 312

These models are similar to Model 812 and employ 12½-inch picture tubes.

SERVICEMEN ARE SOLD

Yes, SOLD on RIDER MANUALS! And for good reason, too! Check for yourself... RIDER MANUALS give you ALL the information you need! COMPLETE coverage of the manufacturers' ENTIRE receiver output! ALL production runs (not just pilot models)... with ALL of the changes!

Yes, and ALL of the data is ACCURATE, AUTHENTIC, FACTORY-AUTHORIZED! ALL of it comes direct from the service departments of the receiver manufacturers themselves, and is compiled by RIDER into these indispensable television servicing manuals... giving you, in this ONE course, ALL of the priceless information that you MUST have

...and you can see WHY

For in the **FIRST FIVE RIDER TV MANUALS**, containing 10,544 pages:

731 pages are devoted to understandable descriptions of circuit action... telling you HOW the circuit functions. NOBODY, but RIDER furnishes you with so much of this necessary information!

293 pages are on signal waveforms... so vital to any rapid trouble diagnosis in picture i.f., sound i.f., video, sync and sweep circuits. Nobody, but RIDER, offers anywhere near this amount of important data!

337 pages have factory-issued unpacking and installation instructions. Nobody, but RIDER, brings you as many of these helpful, time-saving notes!

ONLY IN RIDER TV MANUALS

NOWHERE else can you get as much... in such easy-to-find format... so very easy-to-understand... so accurate... so thorough... so complete... so efficient...

★ ★ ★ ★ ★

Make sure that your Working Library of RIDER MANUALS is complete... with ALL of these indispensable volumes on hand.

Television Manual Volume 6 (Plus Index).....	\$24.00
Television Manual Volume 5 (Plus Index).....	24.00
Television Manual Volume 4 (Plus "How It Works" Book and Index).....	24.00
Television Manual Volume 3 (Plus "How It Works" Book and Index).....	24.00
Television Manual Volume 2—In new, larger page size, 12" x 15". (Plus "How It Works" Book and Index).....	24.00
Television Manual Volume 1 (Plus "How It Works" Book and Index).....	19.80
Volume XXI.....	21.00
Volume XX.....	21.00
Volume XIX.....	22.50
Volume XVIII.....	22.50
Volume XVII.....	19.80
Volume XVI.....	9.90
Volume XV.....	22.50
Volume XIV to VII (each volume).....	19.80
Volume VI.....	15.00
Abridged Manuals I to V (one volume).....	19.80
Master Index, Covering Manuals Vol. I to XV.....	1.50
PA Equipment Manual, Volume I.....	18.00

John F. Rider Publisher, Inc.
480 Canal Street New York 13, N. Y.

Complete your Rider Manual Library! If any volumes are missing, order a replacement today!

MIDWOOD RADIO AND TELEVISION SERVICE 1328 Coney Island Avenue Brooklyn 30, N. Y.

John F. Rider Publisher, Inc.,
480 Canal Street
New York 13, N. Y.

Gentlemen:

I use Rider TV Manuals in my service work. I have found the information covered more exact, and you can rely on the schematics because they are direct from the manufacturer. I can be sure that working with Rider's Manuals I have the complete servicing information to do an accurate and rapid job.

Keep up the swell work you are doing for the servicing industry.

Sincerely,
Herman Davis

RADIO REPAIR & SALES

273 Central Avenue
Newark 4, N. J.

John F. Rider Publisher, Inc.
480 Canal Street
New York, N. Y.

Gentlemen:

We have been in business for 18 years and have always used Rider Manuals. We have found them to be invaluable in our work. I can truthfully say that we couldn't possibly have gotten along without them. We have also found the information contained in Rider's Manuals clear and complete. We look forward to each new manual when it comes out.

Best wishes for your continued success.

Sincerely,
Frank A. Morrocco

TOWN RADIO & TELEVISION CO.

72-06 Main Street
Flushing, New York

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Gentlemen:

In the many years we have been operating as Radio and Television servicemen we were under the impression that we could operate successfully without Rider Manuals.

In the past few months we have been called upon to service many AM-FM and Television receivers for which we have needed all important service notes. So we went out and purchased a complete set of Rider's Manuals from our favorite parts jobber.

It is our contention that no service shop can operate successfully without a complete set of Rider Manuals, Radio and Television. We now know that for any receiver Television or AM that is brought into our shop to be serviced we have the factory authorized data. It is a satisfaction to know that we have the data on hand when we need it.

Keep up the splendid work.

Very truly yours,
TOWN RADIO & TELEVISION
Samuel Freeman
SAMUEL FREEMAN

You need it! Get it...Now!

New Rider TV Manual... VOLUME 6



at your nearby Jobbers' today! Hurry in for your copy before the present supply is exhausted!

EXCLUSIVE FEATURES

- All TV Production Runs and Changes from August, 1950 Through January, 1951.
- Circuit Function Descriptions.
- Unpacking and Installation Data.
- Signal Waveforms for Trouble Shooting.
- COMPLETE Alignment Data.
- COMPLETE Parts List.
- Circuit Changes.

RIDER TV MANUAL...Vol. 6

ACCURATE... AUTHENTIC... FACTORY-AUTHORIZED TV servicing information direct from 66 manufacturers. BIG 12"x 15" page size, and all pages filed in proper place. Large, easy-to-read diagrams. Equivalent of 2320 pages, (8½" x 11") plus Cumulative Index Volumes 1 through 6.....\$24.00

With all 6 RIDER TV MANUALS on your shelves you will have the world's greatest compilation of TV servicing information—right at your fingertips. This information will save you time, save you trouble, help you do a better servicing job, and help increase your profits. SEE YOUR JOBBER TODAY!

Now Available!

RIDER Manual...Vol. XXI



Here's another RIDER volume that you must have on your shelves...another time-saver...another money-maker for you! Factory-authorized servicing information from 61 manufacturers... AM-FM,

Auto Radios, Record Changers, Disc Recorders, Tape Recorders. Coverage from December, 1949 through October, 1950. 1648 pages plus Cumulative Index Volumes XVI through XXI.....\$21.00

Every Day, More and More Servicemen Buy RIDER MANUALS For PLUS Profits!

JOHN F. RIDER PUBLISHER, Inc.
480 Canal Street • New York 13, N. Y.

Television Changes

General Electric 12T3, 12T4, 12T7, 12C107, 12C108 and 12C109

Late production receivers incorporated the following change to increase the horizontal sweep width: Add a 220- μ f, 1500-volt capacitor (Stock RCU-295) between terminals #6 and #8 of the horizontal sweep output transformer, T351. Either two 390- μ f capacitors (Stock UCU-1042) in series or two 470- μ f capacitors (Stock UCU-1044) in series may be substituted for the 220- μ f capacitor.

Early production receivers made use of a 41.25-Mc trap coupled to the 2nd video i-f coil. This caused "buzz" in audio on some

receivers when the receiver was properly tuned for best picture detail at low contrast setting or when operating on a rather weak signal. This trap was removed on all late production receivers and was made less effective on receivers in process of fabrication, by shunting the trap by a 5100-ohm, $\frac{1}{2}$ -watt resistor by connecting it across the trap trimmer C281. If this change is desired in the field, the shunting of C281 by the resistor does not require a realignment of the video i-f.

To improve the "pull-in" range of the horizontal synchronizing circuit in the above receivers, a late production change was made which changes the value of R379 from 180,000 ohms, to 270,000 ohms, $\frac{1}{2}$ watt. This resistor is in the circuit which supplies bias to the afc control tube. In some receivers, a 220,000-

Successful Servicing, April, 1951

ohm resistor was substituted until an adequate supply of the recommended value was obtainable.

Westinghouse H-242, Ch. V-2150-31

The schematic diagram of the service notes for this chassis shows a capacitor, C336, and a resistor, R339, in the cathode circuit of the 6AH6 video output tube. These components were not incorporated in some of the early production chassis. In early chassis that do not contain C336 and R339, a sharper picture can be obtained in strong signal areas by adding the two components as shown on the schematic. It should be noted, however, that insertion of the two components will reduce the gain of the stage somewhat, and in weak signal areas the reduced gain may overbalance the improvement in sharpness.

Steps 5 to 7 of the "High-Voltage Oscillator Adjustment Procedure" should be changed to read as follows:

5. Turn off the receiver, disconnect the 13 megohms of resistance, and connect the high-voltage lead to the crt.

6. Connect the kilovoltmeter between the h-v lead and the chassis.

7. Turn on the receiver and adjust R466, which controls the d-c supply voltage to the h-v oscillator, so that the voltage indicated on the kilovoltmeter is 10.5 kilovolts, plus or minus 0.5 kv.

The frequencies specified in steps 5 to 8 of the alignment procedure should be changed to read as follows:

Step 5—22.6 Mc; Step 6—25.9 Mc; Step 7—25.6 Mc; Step 8—23.8 Mc.

ORDER YOUR COPY NOW RIDER TV VOLUME 6

Westinghouse H-603C12, H-608C12, Ch. V-2152-01

The schematic diagram of the V-2152-01 chassis (Figure 14 in the service notes) should be changed to include later production changes as follows:

1. The value of C408, which is connected from pins 5 and 7 of the 6AL5 horizontal afc tube to ground, has been changed from 0.0033 μ f to 0.002 μ f. This change is made to improve the horizontal hold.

2. Add a 0.0- μ f capacitor C439 from the junction of R441 and R433, located in the pin 7 grid circuit of the 12AU7 horizontal multivibrator, to ground. This change is made to improve the horizontal hold.

3. Change the resistance of R456 in the cathode circuit of the 6BQ6/GT horizontal output tubes from 33 ohms to 150 ohms.

4. Change the resistance of R431, located in the pin 6 plate circuit of the 12AU7 horizontal multivibrator, from 10,000 ohms to 33,000 ohms. This change stabilizes the operation of the multivibrator.

5. Add a 0.01- μ f capacitor C511 and a 100-ohm resistor R506 connected in series from the junction of L501 and R501 to ground. These components suppress arcing at the selector switch contacts.

The following changes and additions should be made to the Parts List:

Ref. No.	Part No.	Description
C408	V-6023-6202M	Capacitor, 0.002 μ f
C439	V-6023-4104M	Capacitor, 0.1 μ f, 440 v
R431	RC30AE333K	Resistor, 33,000 ohms, 1 w
C511	V-6023-4223K	Capacitor, 0.01 μ f, 400 v
R506	RC20AE101K	Resistor, 100 ohms, $\frac{1}{2}$ w.

Dependability is the word for

CORNELL-DUBILIER VIBRATORS

CORNELL-DUBILIER...the name that stands for quality — assures you of the finest in vibrators. A type for every replacement need...engineered for dependable peak performance under even the most adverse conditions. And they are QUIETER...affording the maximum in vibrator value...yet at no extra cost.

CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
SOUTH PLAINFIELD, NEW JERSEY

• CAPACITORS

• ANTENNAS

• ROTATORS

• VIBRATORS

• CONVERTERS

Please mention Successful Servicing when answering advertising.




Here's the **BOOSTER** that says
"YES" to all your demands...



the New
AUTOBOOSTER

THE *Fully Automatic* TV-FM BOOSTER

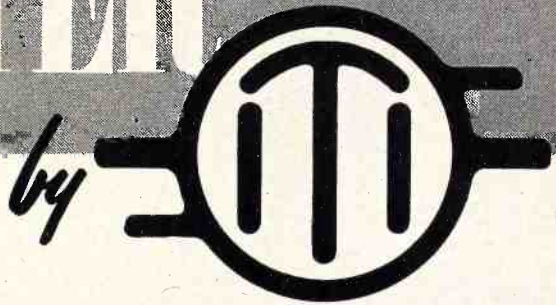

Here at last is a TV Booster that gives you gain up to nine times, full band width for undistorted video and audio on all channels, plus — the newest development in booster design — completely automatic operation.

The ITI AUTOBOOSTER turns itself on and off and is automatically tuned by the normal operation of the TV receiver. No confusing array of knobs — no unsightly mess of wires — You can install the ITI AUTOBOOSTER in the back of the receiver, out of sight. You get all the improved performance, all the fine picture quality that this precision-engineered booster can give you with none of the trouble of tuning, none of the exposed wiring usually involved in booster operation.

Customer acceptance is assured, too, because no customer instruction is needed. After it's installed, all you can see is the improved picture.

- ✓ **AUTOMATIC ON-OFF**
- ✓ **AUTOMATIC TUNING**
- ✓ **CONCEALED INSTALLATION**
- ✓ **SINGLE OR DUAL INPUT**
- ✓ **HIGH UNIFORM GAIN**

**BUY THE BOOSTER
THAT SAYS "YES"
to all your PROBLEMS**

WRITE FOR SPECIFICATION SHEET
ORDER AUTOBOOSTER FROM
YOUR JOBBER TODAY!



LIST
\$44.95
F.O.B.
CLIFTON, N. J.

BOOSTER CHECK LIST		OTHER BOOSTERS TESTED					
AUTOBOOSTER	A	B	C	D	E	F	
Automatic On-Off	YES	YES	YES	NO	NO	NO	NO
Automatic Tuning	YES	NO	NO	NO	NO	NO	NO
Concealed Installation	YES	NO	NO	NO	NO	NO	NO
Full Bandwidth (All Channels)	YES	NO	YES	YES	NO	YES	NO
Amplifies FM Band	YES	YES	NO	NO	YES	NO	NO
Single or Dual Input	YES	NO	NO	NO	NO	NO	YES
Gain 19db on Low Channels 2 - 6 FM	YES	NO	NO	NO	NO	NO	YES
Gain 14 db on High Channels 7 - 13	YES	NO	NO	NO	NO	NO	NO
Made by a TV Receiver Manufacturer	YES	NO	NO	NO	NO	NO	NO

THE ONLY TV BOOSTER
DESIGNED AND MADE BY A
TV RECEIVER MANUFACTURER




INDUSTRIAL TELEVISION, INC.

359 LEXINGTON AVE. - CLIFTON, N. J. - GRGregory 4-0900

"Little Giant" TWIN LEAD LIGHTNING ARRESTER

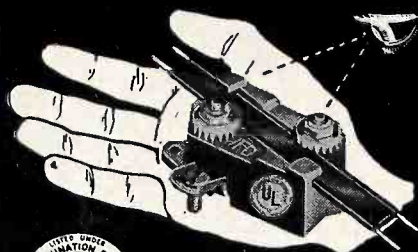Protects TV Sets Against
Lightning and Static Charges



SEEKING IS BELIEVING!

ONLY JFD Lightning Arresters offer you these exclusive patented features...

1. Patented strain-relief Retaining Lip which prevents pulling or straining against contact points.
2. You actually see positive contact made with lead-in wire
3. Lead-in contact remains fully visible at all times.
4. No wire stripping. No Arrester Cover to Hide Poor Contacts!

No. AT105
\$1.25
List

For Regular Twin Lead

At Your Jobber or Write Direct



MANUFACTURING CO., Inc.
6119D 16th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories

GREATER COVERAGE PER POUND



Perfect joints in less time with less solder — when you use Ersin MULTICORE Solder, the original 3-core solder and the only solder in the world made with non-corrosive, extra-active Ersin Flux! Eliminates "dry" joints! Bonds difficult metals! See for yourself! Send for FREE SAMPLE — Multicore Sales Corp., Dep't S., 164 Duane St., New York 13, N. Y.

Please mention Successful Servicing when answering advertising.

LOUDSPEAKER MATCHING

(Continued from page 1)

line (or other high impedance) by means of an individual transformer having a primary impedance such that in combination with the other individual transformer primary impedances the total load is 500 ohms (or equal to the amplifier tap impedance used). Four loudspeakers in series-parallel using two matching

transformers, or nine loudspeakers in three series-parallel groups using three matching transformers, can each be connected so as to offer an impedance equal to that of the line. Fig. 4 illustrates line matching of the above-mentioned series-parallel connected loudspeakers. It will be noticed that the matching transformer secondary impedance equals the load connected across it.

(More next issue)

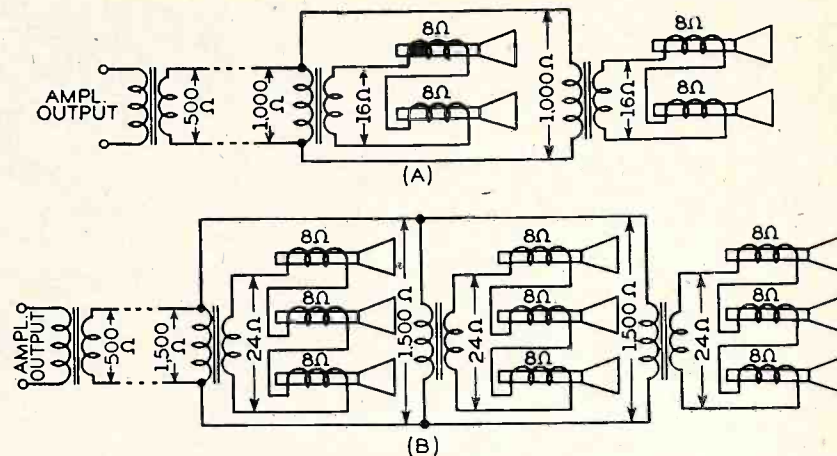


Fig. 4. Low-impedance loudspeakers can be connected to a high-impedance amplifier in many ways using line matching transformers. Parts (A) and (B) illustrate two such possible configurations.

Belmont C-1602 Series C

Model C-1602 Series C is similar to Model C-1602 Code 8 except for the differences mentioned below:

Resistor R3, the 470,000-ohm resistor connected from lug 2 (antenna input) to ground has been deleted. Lug 2 is connected directly to lug 4, 1 and 3 are connected to the antenna input terminals. The value of resistor R4, going to pin 1 of the 6AG5 r-f amplifier, has been changed from 100,000 ohms to 10,000 ohms. Resistors R2, R5, R8 and R10, that were tied to lug 10 of the tuner, are now grounded. Capacitor C33, 1000 μ f, that went from R10 to ground, has been deleted. Capacitor C32, the 200- μ f capacitor going from ground to the junction of pin 4 of 6AG5 r-f amplifier and tuner lug 6, has been deleted. Capacitor C31, the 220- μ f capacitor going from ground to the junction of pin 3 of the 6J6 converter and tuner lug 7, has been deleted. Capacitor C30, the 220- μ f capacitor that was connected from pin 4 of the 6J6 converter and tuner lug 8 to ground, now is connected from pin 3 of the converter to ground. Pin 3 of the 6AG5 and pin 3 of the 6J6 are tied directly to lug 8, which goes to the heater, pins 4 of both tubes are grounded. R4, mentioned above, now goes from pin 1 to lug 9, instead of to ground, and lug 9 is connected to agc at the junction of the low side of capacitor C55 (5 μ f, 50 volts) and the 2200-ohm resistor R53. The value of resistor R54 has been changed from 220,000 ohms to 68,000 ohms, and R54 is now inserted in the line going to tuner lug 9, instead of going from ground to tap 7 of T8. A 33,000-ohm resistor R110 has been added from ground to the junction of lug 9 and R54. The 0.2- μ f capacitor connected from ground to tap 7 of T8 has been deleted from the circuit.

In the tuner chassis, the 0.5- μ f capacitor C10, connected in parallel with C11, 1.5 μ f, has been deleted. The 51- μ f capacitor C28, connected from L9 to C29 has been deleted.

The 7- μ f capacitor C27, connected in parallel with L9, has been deleted from the circuit, and capacitor C24, the 7- μ f capacitor connected in parallel with C26, has been substituted in place of C27. The 51- μ f capacitor, C25, connected from the junction of C24 and C26 to pin 5 of the 6J6 converter, has been deleted from the circuit.

Gamble-Skogmo 94RA33-43-8135

The 94RA33-43-8135 is the same as Models 94RA33-43-8130C and 94RA33-43-8131C except for the differences mentioned below. The physical difference is the cabinet, larger drum on the tuning gang, speaker bracket, dial glass, dial bracket and power-cord strain relief. The parts list for Model 94RA33-43-8135 is the same as that for the 8130C and 8131C except for the following parts.

Part No.	Description
E81650-2	Tuning gang
E81645-S2	Speaker
M1607-2	Dial bracket
P1602-2	Dial glass
SR-2P	Strain relief
P1601A-2	Cabinet, walnut
M1605-2	Chassis

Crosley 11-100U, 11-101U, 11-102U, 11-103U, 11-104U, 11-105U

The following procedure should be used when installing an idler spring (part no. 151085) on the drive shaft:

1. Remove cotter from end of shaft under chassis.
2. Pull drive shaft straight out from chassis being careful to keep drive cord on shaft and pulley.
3. Remove spring washer from shaft.
4. Place idler spring on shaft and then hook one end of the spring under the chassis. The other end of the spring hooks around the portion of drive cord that is between the drive shaft and the tuning capacitor pulley.
5. Place spring washer on the drive shaft, insert drive shaft in chassis, and insert cotter on end of shaft.

WE GUARANTEE RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is . . . what it can DO . . . and HOW to use it properly!



ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usan

The **FIRST** and **ONLY** book that so fully and clearly describes the 'scope . . . its construction . . . its capabilities . . . its applications in communications, engineering, research . . . with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you . . . WHAT each type can do . . . HOW to use it . . . and WHICH is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians — all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages . . . 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home . . . municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY** and **IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth BoundAnd only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Usan



The entire system of frequency modulation is explained thoroughly . . . all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

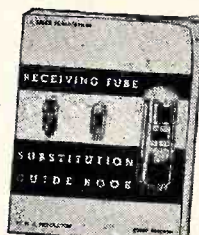

For AM-FM-TV Receivers and Allied Equipment!

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!


EXTRA! In addition to tube information . . . this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc. . .

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New . . . Revised . . . Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman

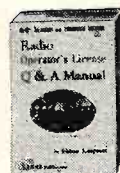

All the **QUESTIONS** and **ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH** . . . a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer. It also lists "extras" not ordinarily found in a volume of this type . . . including Useful Appendices which take in Small Vessel Direction Finders and Automatic Alarm.

766 Pages, Hundreds of Explanatory Diagrams..\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc. . . in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed, how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth boundOnly \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.



**DON'T LET THIS
HAPPEN TO YOU!**

AVOID COSTLY SERVICE CALLBACKS

When you replace a defective capacitor with a Sprague, it stays replaced!

Why risk your reputation and customers' goodwill when the best costs no more?

Sprague capacitors are the dependable capacitors.

P.S. Do you have the latest Sprague Catalog C-607-55 on your bench?

SPRAGUE
PIONEERS IN

SPRAGUE PRODUCTS COMPANY
(Distributors' Division of Sprague Electric Co.)
NORTH ADAMS, MASSACHUSETTS

ELECTRIC AND ELECTRONIC DEVELOPMENT

Please mention Successful Servicing when answering advertising.

Radio Changes

General Electric P15

To further clarify the identity of the three spindles for the record speeds for which they are to be used, the following descriptions have been added to the Parts List for record changer P15: RMU-060 Spindle, offset spindle for 7 inch, 33-1/3 rpm records; RMX-162 Spindle, for 10 or 12 inch, 33-1/3 or 78 rpm records; RMX-163 Spindle, for 7 inch, 45 rpm records.

Admiral 6RT41, 6RT42, 6RT43, Ch. 5B1-PH

Models 6RT41, 6RT42, and 6RT43 use radio chassis 5B1-PH. The 6RT41 is a plastic table combination using record changer RC160 or RC160A. The 6RT42 and the 6RT43 are wood table combinations using radio chassis 5B1-PH and record changers RC160 or RC160A. In addition to the RC160 and RC160A, the 6RT42 may use an RC150 record changer.

Admiral 6C71-71A, Ch. 10A1; 7C62-62A, Ch. 6M1; 7C63-63A, Ch. 7C1

Model 6C71-71A is a console combination using radio chassis 10A1 and record changer RC200. Model 7C62A-62A, Ch. 6M1, and Model 7C63A-63A, Ch. 7C1, are console combinations and use either record changer RC170 or RC170A.

Gamble-Skogmo 94RA4-43-8129A, 94RA4-43-8130A, 94RA4-43-8130B, 94RA4-43-8131A, 94RA4-43-8131B, 94RA4-43-8132A

Model 94RA4-43-8129A is the same as Model 43-8129A. Models 94RA4-43-8130A and 94RA4-43-8130B are the same as Models 43-8130A and 43-8130B, respectively. Model 94RA4-43-8131A is the same as Model 43-8131A. Model 94RA4-43-8131B is the same as Model 43-8131B. Model 94RA4-43-8132A is the same as Model 94RA4-43-8131A except that it employs a maroon cabinet.

ORDER YOUR COPY NOW RIDER TV VOLUME 6

Motorola BKO A, CT8A, GM9TA, GMOT, HNO, ILOT C, KR9A, OEO, PCO, PC9A, SR9A, Ch. 10A

The above models all use Chassis 10A. Model BKO A is used in 1950 Buick Special, Super and Roadmaster cars. It will also accommodate 1949 Buick Super and Roadmaster; also the 50-70 Series 1948, '47, '46, and '42 Buick cars. Model CT8A is used in 1948 Chevrolet. It will also accommodate 1947, '46, '42, and '41 Chevrolet cars. Model GM9TA is used in 1949 and 1948 GMC and Chevrolet trucks. Model GMOT is used in 1950, '49, and '48 GMC and Chevrolet trucks. Model HNO is used in 1950 Hudson (Pacemaker, Super, and Commodore). Model ILOT C is used in International L-Line trucks. Model KR9A is used in 1949 Kaiser and Frazer. Model OEO is used in 1950 Series 76 and 88, all 1949 and 1948 Futuramic Oldsmobile cars. Model PCO is used in 1950 and 1949 Pontiac cars. Model PC9A is used in 1949 Pontiac cars. Model SR9A is used in 1949 Studebaker cars.


BETTER { LOOKING! ENGINEERING! PERFORMANCE!

JFD

Panorama INDOOR TV ANTENNA

ABSOLUTELY TIP-PROOF!

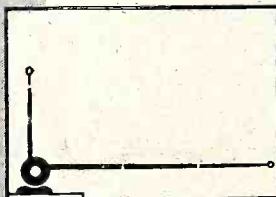Hundreds of thousands now in use with over 3,000 BEING SHIPPED DAILY! And every satisfied user helps you to sell another! No other indoor antenna has so many impressive sales features!



ABSOLUTELY TIP-PROOF!

Properly balanced and weighted, solid metal base prevents tipping of the antenna . . . regardless of the length or the angle at which the dipoles are set. Soft felt pad prevents scratching or marring of furniture.



MINIMIZE "GHOSTS"—REDUCES INTERFERENCE!


3-section, triple-chrome plated metal telescopic dipoles can be oriented for each individual channel. Gets all 12 TV plus FM.



MAXIMUM SIGNAL STRENGTH

. . . giving clearer, more stable pictures . . . with less "snow"!

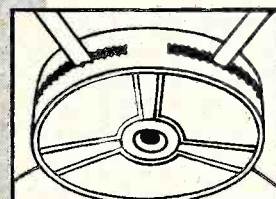Dipoles are easily adjustable from 15 to 41 inches . . . can be lengthened or shortened to the correct frequency for each channel.



SURE GRIP—SURE HOLD!

The ratchet contour inside the molded bakelite housing assures a firm grip and sure hold at whatever angle or length the dipoles are set.

No. TA135

. . . complete with 300 ohm twin lead.
List Price \$6.95



1½ lb. Weighted Base

"Made by JFD, the World's Largest Manufacturer of TV Antennas!"

Immediate Delivery From Your Jobber

JFD

MANUFACTURING CO., Inc.

6119D 16th AVENUE, BROOKLYN 4, N. Y.

FIRST In Television Antennas and Accessories

Radio Changes

Admiral 6T06, 6T07, Ch. 4A1

Models 6T06 and 6T07, Ch. 4A1, are wood table models using a farm battery.

Admiral 6T01, 6T05, Ch. 6A1

Model 6T01 is a plastic table model using chassis 6A1. Model 6T05 is a wood table model using chassis 6A1.

RCA 8X541, Ch. RC-1065L; 8X542, 8X547, Ch. RC-1065M

These instruments are almost identical to the previous production of these instruments which used Chassis RC-1065J and RC-1065K.

**ORDER YOUR COPY NOW
RIDER TV VOLUME 6**

Admiral 6T02, 6T04, Ch. 5B1

Models 6T02 and 6T04 are table models using chassis 5B1. Model 6T02 has a plastic cabinet, while Model 6T04 has a wood cabinet.

RCA A-82, Ch. RC-1094; A-91, Ch. RC-1095; A-108, Ch. RC-1096; 45-W-9, Ch. RC-1095A

The original carriage in all of the above models used a pull-out handle on the top front, the carriage now in use has a handle under the lower front edge. The same plastic frame may be used for all models. A plug button (supplied with each plastic frame) is used to cover a center hole which is unused on all models except A-108.

Frame—Stock No. 76161 is used as a replacement for frame Stock No. 75549 or 75571 (maroon).

Frame—Stock No. 76162 is used as a replacement for frame Stock No. 75683 or 75684 (light brown).

The new type of pull-out handle (lower front) is available as Stock No. 76125. If the original pull-out handle (top front) is desired it will be necessary to drill two holes in the frame. The holes are .203" diameter and are located .625" each side of the center line and 13/64" down from the top.

In Models A-91 and A-108 the color of wire used in the connecting cable has been changed. A black-white wire has been used as a substitute for the black wire (pin 1 to speaker) and a brown-white wire has been used as a substitute for the brown wire (pin 8 to speaker). A brown wire goes from pin 2 to the jewel lamp and a black wire goes from pin 3 to the jewel lamp.


In Model A-82 a substitute speaker (stamped 92569-9B) has been used in some instruments. It requires a different speaker cone than the one listed in the A-82 Parts List. Speaker 92569-9B uses Stock No. 75875 cone. Speaker 92569-9W uses Stock No. 74901 cone.

Admiral 6RT41A, 6RT42A, 6RT43A, Ch. 5B1A

Model 6RT41A is a plastic table combination using radio chassis 5B1A and record changers RC160 or RC160A. Models 6RT42A and 6RT43A are wood table combinations using radio chassis 5B1A and record changer RC160 or RC160A.

Successful Servicing, April, 1951

TWIN LEAD, TELEVISION LIGHTNING ARRESTER

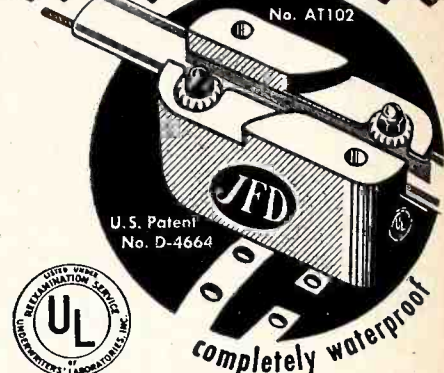

APPROVED for OUTDOOR-INDOOR Use \$2.25
Protects Television Sets
Against Lightning and Static
Charges

JFD SAFE TV GUARD

Simple to install everywhere and anywhere
...no stripping, cutting or spreading of
wires. More than 300,000 in use today!

SEE YOUR JOBBER OR WRITE TO

JFD MANUFACTURING CO., Inc.
6119D 16th Avenue, Brooklyn 4, N. Y.
First in Television Antennas & Accessories

Please mention Successful Servicing when answering advertising.

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED
RADIOS IN YOUR "BACK YARD" JUST WAITING
TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis
that means **BIGGER PROFITS** for you!



SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

The NEW ESPEY model 511-B FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly Illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.
TEL. TRafalgar 9-7000

Gamble-Skogmo 43-8101, 165, 197, 197U

Model 165 is the same as Model 94RA31-43-8115A. Model 197 is the same as Model 94RA31-43-8115B. Model 197U is the same as Model 94RA31-43-8116A. Model 43-8101 is electrically the same as Models 94RA31-43-8115A, -8115B, and -8116A.

Gamble-Skogmo 43-7661, 43-7852

Model 43-7661 is the same as Model 43-7660 except that the 7661 uses a blond cabinet. Model 43-7852 is the same as Model 43-7851 except that it uses a blond cabinet.

Westinghouse H-312P4, H-312P4U, H-313P4, H-313P4U, H-314P4, H-314P4U, H-315P4, H-315P4U, Ch. V-2153-1

The following part should be added to the parts list for these models: R13 (Part No. RC30AE332K), 3300 ohms, 1 watt.

United Motors 982421, Oldsmobile

Capacitance drift of the 0.0012- μ f mica capacitor used in the oscillator tank circuit (Illustration No. 20) sometimes occurs. This appears as intermittent oscillator frequency drift which seems to be the result of high temperature which may be caused by high input voltage or other extreme conditions. It may be necessary to cover the set or run at a high input voltage when bench testing in order to have the intermittent condition reappear. Since a fixed mica capacitor is usually considered a very stable unit, this condition is not a common occurrence. However, when oscillator frequency drift is encountered this capacitor should be considered as a possible source.

215

SQUARE INCHES OF FINEST
PICTORIAL REPRODUCTION...

*new Bent-Gun for
edge-to-edge sharpness,
gray filter face plate,
"Standard" neck length of 7 $\frac{3}{16}$ "*




*trade-mark

***Our commercial
engineering department
invites all design inquiries***

ALLEN B. DU MONT LABORATORIES INC., TUBE DIVISION, CLIFTON, N. J.

Please mention Successful Servicing when answering advertising.

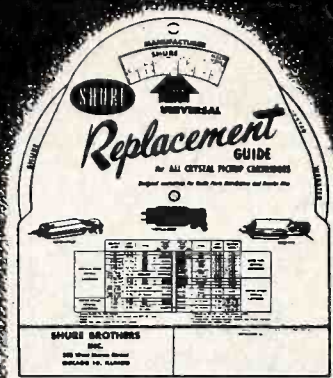FREE!**NEW SHURE****Cartridge Replacement GUIDE**

A TURN OF THE DIAL GIVES THE CORRECT REPLACEMENT MODEL OF ALL SHURE CARTRIDGES AND MOST OTHER MAKES

Ask your Shure Distributor for a "Guide" — or write direct, giving us his name.

SHURE BROTHERS, INC.

Microphones and Acoustic Devices

225 West Huron Street • Chicago 10, Illinois

Please mention Successful Servicing when answering advertising.

Westinghouse H-217, H-217A, Ch. V-2146-11DX; H-217B, Ch. V-2146-35DX

In the schematic diagram of the V-2146-11DX chassis (Fig. 6 of the service notes), the high-frequency oscillator tube should be a 6C4 rather than a 6AB4. In the schematic diagram of the V-2146-35DX chassis (Fig. 7 of the service notes) the 0.05- μ f capacitor C338 in the d-c restorer circuit should connect to the top (cathode) of the 1N34 rather than to the bottom (anode).

In later production of Model H-217B, a built-in TV antenna is incorporated. Replacement parts for the antenna are as follows:

Part No.	Description
V-9358-2	Antenna assembly, TV
V-5574	Bearing, shaft (TV antenna)
V-6146-5	Knob, TV antenna
V-9323-1	Pulley and shaft assembly (short shaft)
V-9324-3	Pulley and shaft assembly (long shaft)
V-9328-1	Sleeve, rubber (TV antenna)
V-4057	Spring, TV antenna drive
V-3752S	Washer, felt (TV antenna knob)

INDEX OF CHANGES

Model	Page Number	Successful Servicing	Rider Manuals†
		From	To

TELEVISION CHANGES

Affiliated Retailers AR-MST14, AR-MST16, AR-16ATR, AR114A AR-14TR, AR-16TR	6	6-1	6-9
Affiliated Retailers AR-16CD, AR-16CD-3CR, AR-163CR, AR-216, AR-316, AR-316-3CM, AR-816-3CM AR-16CX, AR-816-3CR	2	5-1	5-8
Crosley 10-401, 10-414MU, 10-416MU 10-401 10-414MU, 10-416MU	2	5-25 5-37	5-36 5-41
Belmont C-1602 Series C C-1602, Code 8	10	5-21	5-29
DeWald DT-160	6	3-2 C4-2	3-5 —
General Electric 12T3, 12T4, 12T7, 12C107, 12C108, 12C109 12T3, 12T4, 12C107, 12C108, 12C109 12T7	8	5-35 6-1	5-47 6-11
Motorola 9L1 TS-18, TS-18A	2	4-11, 12	4-18
Muntz M159	2	4-1	—
RCA 8T241 Series	6	3-1	3-14
Sarkes Tarzian TT2	5	4-1	4-2
Sarkes Tarzian TT3	2	4-3	4-4
Tele King MST12, 312 812	6	3-1 5-11	3-8 —
Tele King MST14, 14TR, 17CA, 17RO, 114A, 117, 117C, 117CA, 117LO, 162, 173, 516A 116, 516	2	5-12	5-20
Tele King 16C03CR, 16CX, 162, 216, 316, 416CAF, 916, 916C, 916CAF, 3163CM	5	5-1 5-1	5-10 5-8
Westinghouse H-217, H-217A, Ch. V-2146- 11DX; H-217B, Ch. V-2146-35DX	16	5-11	5-25
Westinghouse H-242, Ch. V-2150-31	8	4-1	4-8
Westinghouse H-603C12, H-608C12, Ch. V-2152-01	8	5-46	5-54
Westinghouse H-605T12, Ch. V-2150-101	2	5-55	5-63

RADIO CHANGES

Admiral 6C71-71A, Ch. 10A1; 7C62-62A, Ch. 6M1; 7C63-63A, Ch. 7C1	12	15-27	15-31
Ch. 10A1 RC200	RCD. CH.	17-8	17-13
Ch. 6M1		16-1	16-2
Ch. 7C1		16-11	—
Ch. 7C1 RC170, RC170A	RCD. CH.	16-3	16-6
		16-1	16-7

Admiral 6RT41, 6RT42, 6RT43, Ch. 5B1-PH Ch. 5B1-PH	12	15-9 15-12	— —
RC150, RC160, RC160A	RCD. CH.	15-1	15-17
Admiral 6RT41A, 6RT42A, 6RT43A, Ch. 5B1A Ch. 5B1 RC-160, RC-160A	14	15-11 15-11	15-12 15-17
Admiral 6T01, 6T05, Ch. 6A1 Ch. 6A1	14	15-12 15-15	— —
Admiral 6T02, 6T04, Ch. 5B1 Ch. 5B1	14	15-10 15-12	— —
Admiral 6T06, 6T07, Ch. 4A1 Ch. 4A1	14	15-4	15-5
Crosley 11-100U, 11-101U, 11-102U, 11-103U, 11-104U, 11-105U	10	21-10	21-13
Gamble-Skogmo 43-8101, 165, 197, 197U 94RA31-43-8115A, -8115B, -8116A	14	20-45	20-47
Gamble-Skogmo 43-7661, 43-7852 43-7660 43-7851	14	18-8 19-30	18-14 19-35
Gamble-Skogmo 94RA4-43- 8129A, -8130A, -8130B, -8131A, -8131B, -8132A 43-8129A, -8130A, -8130B, -8131A, -8131B	12	19-36	19-37
Gamble-Skogmo 94RA33-43- 8135 94RA33-43-8130C, 94RA33-43-8131C	10	20-52	20-53
General Electric P15 RCD. CH.	12	21-13	21-18
Motorola BK0A, CT8A, GM9TA, GMOT, HNO, ILOTC, KR9A, OEO, PCO, PC9A, SR9A, Ch. 10A Ch. 10A	12	21-1	21-4
RCA A-82, Ch. RC-1094; A-91, Ch. RC-1095; A-108, Ch. RC-1096; 45-W-9, Ch. RC-1095A A-82, Ch. RC-1094 A-91, Ch. RC-1095 A-108, Ch. RC-1096 45-W-9, Ch. RC-1095A	14	21-13 21-63 21-71 21-81	21-16 21-70 21-80 21-88
RCA8X541, Ch. RC- 1065L; 8X542, 8X547, Ch. RC-1065M 8X541, 8X542, 8X547, Ch. RC-1065J, Ch. RC-1065K	14	18-45 C21-8	18-46 —
United Motors 982421, Oldsmobile	14	19-44	19-49
Westinghouse H-312P4, H-312P4U, H-313P4, H-313P4U, H-314P4, H-314P4U, H-315P4, H-315P4U, Ch. V-2153-1	14	21-15	21-17

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

PERMIT NO. 9427
NEW YORK, N. Y.
PAID
U. S. POSTAGE
Sec. 34.66, P. L. 8 & R.

DOUGLASSON, L. I., NEW YORK
5310 OVERBROOK ST.
A. J. S. CERINO

Return Postage Guaranteed
480 CANAL ST., NEW YORK 13, N. Y.
JOHN F. RIDER PUBLISHER, Inc.
From

MAY, 1951

LOUDSPEAKER MATCHING

by JOHN F. RIDER

Unequal Power Distribution— Low-Impedance Lines

Proper matching of several loudspeakers connected across the same output transformer requires that the output or secondary impedance of the transformer equal the combined impedance of the loudspeakers. Assume that an amplifier with an output of 40 watts has a single output impedance of 6 ohms. It is desired to connect two loudspeakers, one rated at 15 watts and the other at 25 watts, in parallel across the output. What should each voice coil impedance be? The following equation will help solve this problem:

$$Z_{sec} = (\% P_T) Z_L \quad (1)$$

That is, the impedance of the secondary winding is equal to the percentage of the total power taken by one parallel load ($\% P_T$) times the impedance of that load (Z_L). Thus, in the example cited, for the 15-watt loudspeaker, $6 = 40\%$ (approx.) Z_L ; for the 25-watt loudspeaker, $6 = 60\%$ (approx.) Z_L . The respective voice-coil impedances are 15 ohms for the 15-watt loudspeaker and 10 ohms for the 25-watt loudspeaker.

The portion of power delivered to a single loudspeaker connected in parallel with other loudspeakers, expressed as a percentage of the total power in the network, is the ratio of the line impedance (total parallel impedance, Z_T) to the loudspeaker impedance (Z_{vc}), times one hundred. That is:

$$(\% P_T)_{vc} = \frac{Z_T}{Z_{vc}} \times 100. \quad (2)$$

The loudspeaker impedance is, of course, the voice-coil impedance, while the parallel-line impedance is given by the equation for parallel impedances:

$$Z_T = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} \quad (3)$$

If, for example, four loudspeakers which have voice-coil (vc) impedances of 2, 4, 8, and 16 ohms are in parallel, the parallel line impedance is then 1.07 ohms. When this parallel network is connected to a 1-ohm tap on the output transformer, the percentage of power delivered to each loudspeaker, using equation (2) is:

$$(\% P)_{2 \text{ ohms}} = \frac{1.07}{2} \times 100 = 53.4 \text{ percent}$$

$$(\% P)_{4 \text{ ohms}} = \frac{1.07}{4} \times 100 = 26.7 \text{ percent}$$

$$(\% P)_{8 \text{ ohms}} = \frac{1.07}{8} \times 100 = 13.3 \text{ percent}$$

$$(\% P)_{16 \text{ ohms}} = \frac{1.07}{16} \times 100 = 6.6 \text{ percent.}$$

The slight mismatch (1.07-ohm line to 1-ohm tap) does not affect the relative power distribution and does not have to be considered in making these calculations.

In a series-connected loudspeaker system, the percentage of the total power which one loudspeaker receives is the ratio of its voice-coil impedance (Z_{vc}) to the series-line impedance (Z_T) times 100. That is:

$$(\% P)_{vc} = \frac{Z_{vc}}{Z_T} \times 100. \quad (4)$$

If four loudspeakers having voice-coil impedances of 2, 4, 8, and 16 ohms are connected in series, the series-line impedance is the sum of the series impedances, or 30 ohms. The percentages of power delivered to each loudspeaker when the network is connected across a 30-ohm transformer tap, are approximately as follows:

$$(\% P)_{2 \text{ ohms}} = \frac{2}{30} \times 100 = 6.7 \text{ percent}$$

$$(\% P)_{4 \text{ ohms}} = \frac{4}{30} \times 100 = 13.3 \text{ percent}$$

$$(\% P)_{8 \text{ ohms}} = \frac{8}{30} \times 100 = 26.6 \text{ percent}$$

$$(\% P)_{16 \text{ ohms}} = \frac{16}{30} \times 100 = 53.4 \text{ percent.}$$

The percentage of the total power delivered to a loudspeaker connected in a series-parallel network of loudspeakers is a product of two ratios: the ratio of the loudspeaker impedance (Z_{vc}) to the series branch line impedance (Z_s) and the ratio of the total series-parallel impedance (Z_{sp}) to the series branch line impedance (Z_s), that is:

$$(\% P)_{vc} = \frac{Z_{vc}}{Z_s} \times \frac{Z_{sp}}{Z_s} \times 100. \quad (5)$$

Each series branch line impedance is considered as a single impedance connected in parallel with other impedances (each of which may be a series of loudspeaker impedances). If four loudspeakers having voice-coil impedances of 2, 4, 8 and 16 ohms are connected so that the 2- and 4-ohm loudspeakers are in series and the 8- and 16-ohm loudspeakers are in parallel across a transformer, then the series branch line impedances are 6 ohms and 24 ohms, and the total series-parallel impedance is 4.8 ohms. The power percentages delivered to the loudspeakers when the network

is connected to a 5-ohm transformer tap are as follows:

$$(\% P)_{2 \text{ ohms}} = \frac{2}{6} \times \frac{4.8}{6} \times 100 = 26.6\%$$

$$(\% P)_{4 \text{ ohms}} = \frac{4}{6} \times \frac{4.8}{6} \times 100 = 53.4\%$$

$$(\% P)_{8 \text{ ohms}} = \frac{8}{24} \times \frac{4.8}{24} \times 100 = 6.7\%$$

$$(\% P)_{16 \text{ ohms}} = \frac{16}{24} \times \frac{4.8}{24} \times 100 = 13.3\%.$$

If, on the other hand, the same loudspeakers were connected so that the two series branches consisted of the 2- and 8-ohm loudspeakers and the 4- and 16-ohm loudspeakers, then the power would be distributed as follows: 2-ohm loudspeaker—13.3 percent; 8-ohm loudspeaker—53.4 percent; 4-ohm loudspeaker—6.7 percent; and 16-ohm loudspeaker—26.6 percent. If the loudspeakers were connected so that the two branch lines consisted of the 2- and 16-ohm loudspeakers and the 4- and 8-ohm loudspeakers, then the power distribution would be as follows: 2-ohm loudspeaker—4.4 percent; 16-ohm loudspeaker—35.6 percent; 4-ohm loudspeaker—20 percent; and 8-ohm loudspeaker—40 percent.

(Continued on page 8)

Editor's Note: This is the second of two articles on Loudspeaker Matching and is taken from INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS by John F. Rider, published by John F. Rider Publisher, Inc. The first article, which appeared in the April issue of SUCCESSFUL SERVICING, discussed the matching of loudspeakers on low and high impedance lines. Loudspeaker matching is only one of the many topics pertaining to low power public address systems covered in the book, INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS. Other topics include fundamentals of sound, microphones, phonograph pickups, amplifier specifications, loudspeakers, installation (covering indoor and outdoor installations), and the servicing of public address systems.

Television Changes

Freed 54, 55, 56, 68, Ch. 1620B

The following service hints apply to these models:

Short sweep:

1. Check pins of deflection plug for partial shorts or carbonization. Leakage paths will absorb sweep energy and shorten the sweep.

2. Increase the value of C229 (across width coil) with about a 500- μ f, 1000-volt capacitor.

High-voltage fuse continually blows:

1. Check pins of deflection plug for shorts or carbonization.

2. Yoke shorted.

Small or trapezoidal picture:

1. Shorted turns in yoke.

Fine tuning very critical—sound bars:

1. Modify agc circuit as follows: Move tuner agc lead R137 and C134 from the intersection of R135 and R136 and connect these items to the plate (pin 9) of the 6T8 agc tube. Wiggle in the vertical wedges of the test pattern:

1. Install attenuator pad between antenna and receiver.

2. Replace 6T8 agc amplifier and 6AL5 agc detector.

3. Make agc change as noted under Fine Tuning Very Critical—sound bars.

4. Place a 4- μ f capacitor from agc bus to ground.

5. Connect R171 (vertical linearity control) to ground instead of to minus 120 volts. Also connect R230 (vertical output grid resistor) to ground instead of to minus 120 volts.

Picture linearity changes with setting of brightness or contrast control:

1. Incorrect setting of the horizontal linearity control may cause this. Screw horizontal linearity control all the way out (counterclockwise), then turn this slug in until first linear picture is obtained.

Noisy or intermittent tuner:

1. Clean tuner contact points with carbon tetrachloride or other suitable cleaning fluid.

2. Replace tuner tubes (6AG5, 6J6).

3. Install tuner bearing support (Freed-Eisemann Part #AA-308).

4. Replace tuner.

Sound bars in picture at high volume: (Compression and expansion of raster sweep lines)

1. Replace microphonic vertical output tube 6S4 (V122).

Square picture or bad vertical linearity:

1. Replace 6S4 vertical output tube (V122).


RCA 9TW390, Ch. KCS31-1

Model 9TW390 uses radio Chassis RC617A. A 0.05- μ f capacitor designated C389 has been added between terminal 8 of S304 (front) and tuning capacitors C303 and C304 in Chassis RC617A. Early production models of this receiver will not have this capacitor in the radio chassis.


When the radio function switch is in the TV position, the filament voltage is present on the high side of the tuning capacitors (C303 and C304) due to the function switch design. Any shorting of the tuning capacitors to ground causes L314 to burn out. The insertion of the capacitor removes filament voltage from the tuning capacitor without affecting its operation.

Interstate Stores (Plymouth) 250, 350, 750

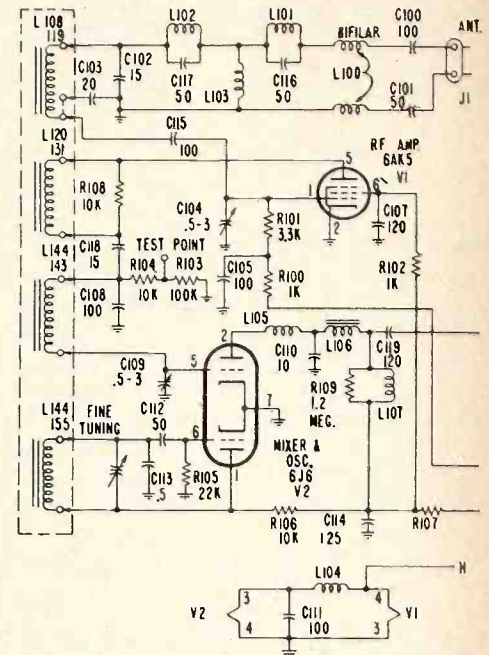The schematic for AROT03 tuner, type 3, is shown in the accompanying illustration. The alignment notes for the above models using



SHOUT - FROM THE ROOFTOPS!

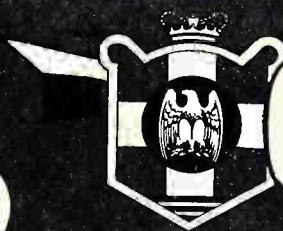

Ranger


COMMANDAIR

CONICAL ANTENNAS


Still the Lowest-Priced, Highest-Value Conicals on the Market Today!

**NEW!
IMPROVED!**

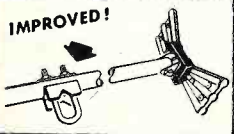
Better-Than-Ever Electrically and Structurally!



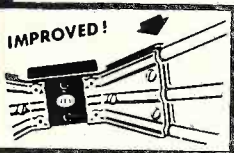
- ★ All-aluminum reinforced crossarm and heavy-duty U-bolt for longer lasting strength.



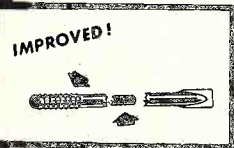
- ★ All-aluminum heavy gauge brackets with 3 full-length channels for secure anchoring of elements.



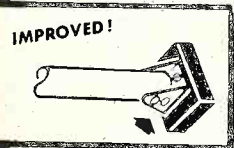- ★ All-aluminum elements with hardwood dowels for extra rigidity. Serrated surfaces for tight, non-slip grip.



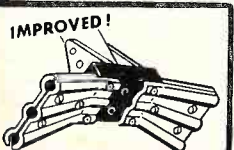- ★ All-aluminum "take-off" support, with double solid rivets, anchors crossarm to element bracket.



- ★ All-aluminum bracket of unique design takes any combination of element arrangements to best suit location.

See us at Booth No. 313 and Display Room No. 534 at the Chicago Parts Show.

JFD

MANUFACTURING CO., Inc.

6119E 16th AVENUE, BROOKLYN 4, N.Y.

FIRST in Television Antennas and Accessories

JFD "PLUS-FEATURE"

No. C660-C691 "Commandair" elements are reinforced with sturdy wood dowels and pressure-sealed ends. No. SR660 and SR661 "Commandair" arrays use 61ST6 1/4" od solid aluminum elements.

No. C660 (illustrated)

Engineered to Outperform! Priced to Outsell!


Dealers, Installers and Distributors everywhere acclaim JFD "Commandair" Conicals. They know from experience that feature for feature, dollar for dollar, JFD "Commandairs" are today's greatest conical antenna buy. Electrically superior, structurally stronger, they represent JFD's supreme achievement of years of pioneering in antenna design and manufacture. Add up the many extras you get with JFD "Commandair" Conicals and you'll see why it's the "sell-out" line for '51.

FREE! Brochure describing entire line of JFD "Ranger COMMANDAIRS" now available. Write for Form No. 87 today.

*All aluminum features are subject to future government restrictions.

In Volume Controls, too... fast, sure fit is important

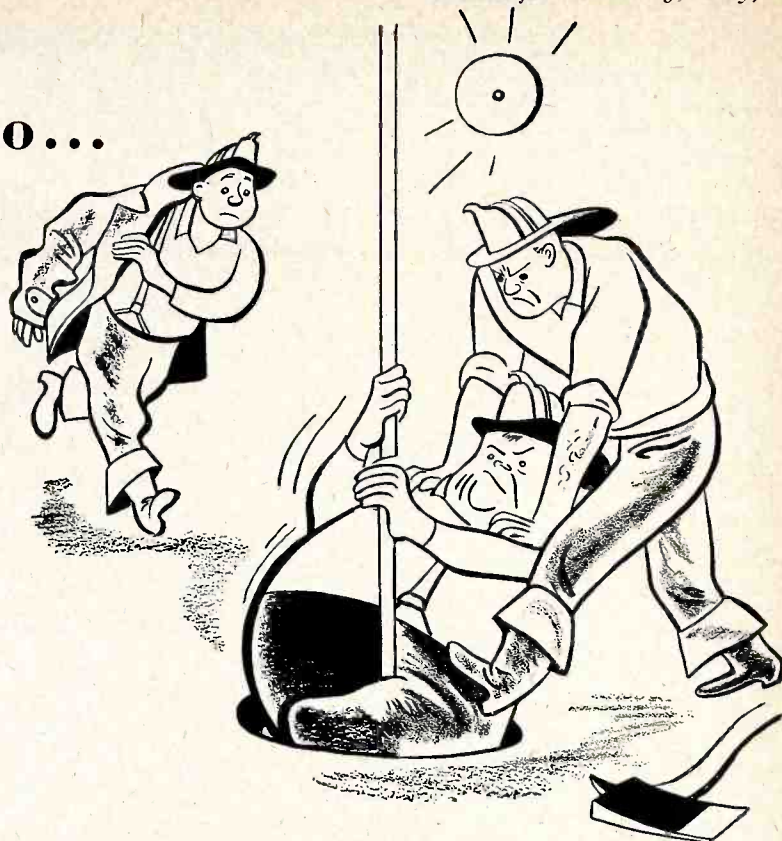In a survey of hundreds of servicemen, the importance of fast, sure installation was emphasized time after time in connection with volume controls. If you want a control that lets you do the job fast . . . and do it right . . .



Make Sure! Make it Mallory!

When you use the Mallory Midgetrol*, you get a combination of features that can't be matched.

First, you get a *permanently fixed, tubular brass shaft* that can be adapted for split-knurl or flatted type knobs in a few seconds by inserting one of the steel shaft ends supplied in every package. This means utmost convenience without sacrificing the stability of permanent, two-point shaft suspension.


Second, you get the convenience of AC switch design that permits secure attachment, *without*

removing the control housing. Positive indexing assures proper position.

Third, you get exceptionally accurate resistance values and taper curves.

Fourth, you can be sure of years of quiet, satisfactory service life through extremes of humidity and temperature.

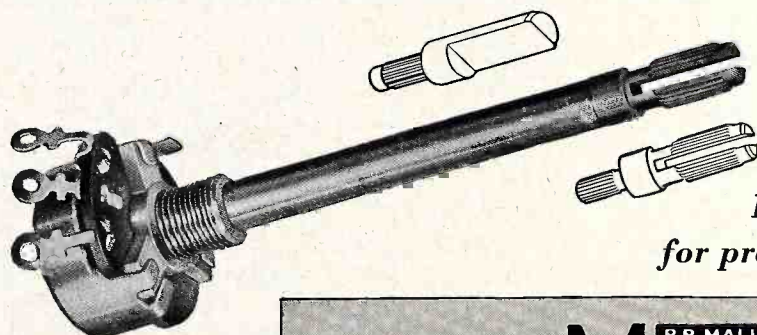Make it Mallory and make sure! Ask your distributor to show you the time-proved Mallory Midgetrol with the new features that make installation faster and simpler than ever.



Dual concentric Mallory Midgetrols can be made up easily by combining factory-assembled front and rear sections of desired resistance values. Ask your Mallory Distributor for details!

*Depend on your Mallory Distributor
for precision quality at competitive prices*

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

*Reg. U. S. Pat. Off.

Please mention Successful Servicing when answering advertising.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

MAY, 1951

No. 7

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
E. H. BEAUMONT, Associate Editor

Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.

Worth 4-8340
Worth 4-8341



CURTAIN TIME

We recall reading about the shortage of cobalt in the U. S., resulting in limited p-m speaker production and all things magnetic for civilian needs. How come a recent solicitation from an outfit in Pa. offering unlimited quantities of p-m speakers made in France? 'Tis said (in a copy of a cable) that the supply of cobalt in France is *unlimited*. Hm!

Every so often a service association attempts to secure parts directly from manufacturers, thus by-passing the electronic parts jobber. This is nothing new. Its been tried for years, and unsuccessfully at that. Virtually all parts manufacturers deal through electronic parts jobbers and there is little doubt that the practice will continue. The parts jobber has been a reliable source of supply to the servicing industry and also a good source of credit. Why bite the hand...

Is it true that W. U. is going in for TV installations? How come? What next? What's the connection between being a communication facility and selling TV installation and service?

We have a new distributor sales manager. It's going to give us more time for research and writing—we have big plans for some real

hot books and some good papers for several magazines. We're happy about the whole set-up.

Everybody complains about the TV serviceman. All right, here are a few incidents to ponder. A car repair shop is commissioned to change the oil in a new car. They remove the old oil but forget to put in new oil. Result—a new bearing job. Another auto service shop is asked to reline the brakes, so they simply tighten them and charge for new brakes. A tailor presses a suit and tears a button off the coat. A cleaner dry-cleans a dress and shrinks it three sizes so that it cannot be worn at all.

Politics is not our forte, but somehow or other we just can't develop that feeling of complacency which is besetting many people we know. Television receivers and many other items are in plentiful supply. So, immediately everyone asks where are the shortages—and applies the question to everything and for all time.

As we see things Russia is committed to a program. Nothing which has come to light indicates a departure from the road they elected to walk. The pattern is set—its just

a matter of time. What we are going through now is a respite—a relatively short one—a confusing one. Don't permit yourself to develop a false sense of security.

JOHN F. RIDER

General Electric 521, 522

Delete items RDK-217, RDS-090 and RWL-009 from the Parts List, and add the following items: RDK-237, Knob, tuning dial wheel with scale embossed; RWL-025, Cord, power cord and plug (brown, heavy duty type).

Firestone 4-A-86, 4-A-95, Westmoreland



Chassis 4-A-95 is the same as Chassis 4-A-86, except that the former has a white oak cabinet and the latter has a mahogany cabinet. In later production models, two 6AB4's (as r-f amplifier and mixer) have been substituted for the 12AT7. The only changes that have been made circuit-wise are the following:

Resistor R2, going from the junction of C4 and pin 6 of the 6BE6 to the junction of C5 and terminal 4 of T3, has been changed from 1000 ohms to 5600 ohms. The value of capacitor C24, connected from terminal 3 to terminal 2 of T7, has been changed from 20 μ f to 10 μ f. The value of C33, connected from ground to the junction of tone control R23 and R20, has been changed to 0.01 μ f. The 6AB4 r-f amplifier is connected as follows: pin 1 goes to the junction of C32A and choke L4; pins 2 and 3 go to ground; pin 4 goes to H; pin 7 goes to the junction of choke L3 and C30; pin 6 goes to the junction of C27 and R16 (R19, 470,000 ohms, that was connected from ground to this junction, has been deleted). The 6AB4 mixer is connected as follows: pin 1 goes to L2; pins 2 and 3 go to ground, pin 4 goes to H; pin 6 goes to the junction of C32B and R18; pin 7 goes to the junction of R18 and C39.


The following changes have been made in the Parts List:

Ref. No.	Part No.	Description
C24	47X523	10 μ f, ceramic
C33	B66103	0.01 μ f, 200 v, tubular
R2	B85562	5600 ohms, 0.5 watts, carbon
T6	9A2161	Discriminator transformer
T10	9A2209	Dipole antenna
T11	53X322	Power transformer
	10A765	Knob (white oak).

DON'T BORROW—OWN RIDER MANUALS

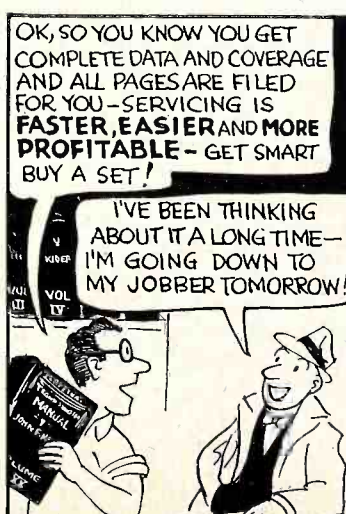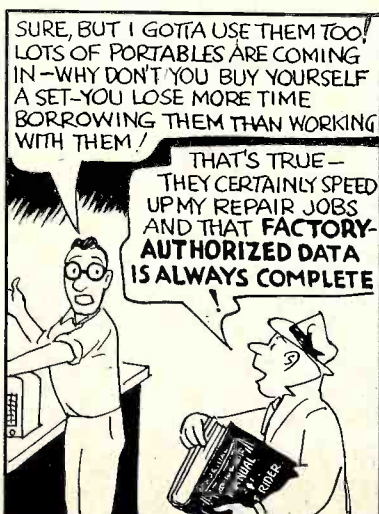

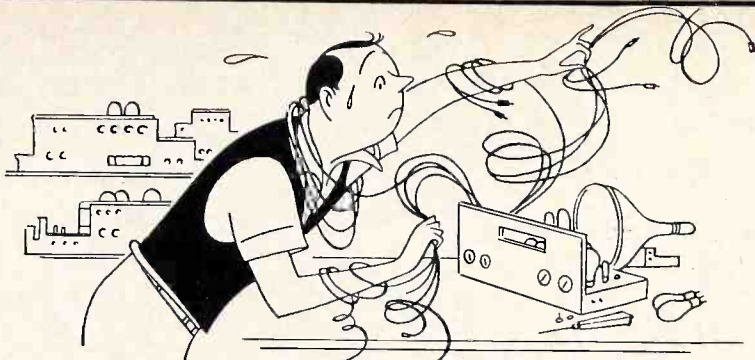RIDER MANUALS
FOR FASTER, EASIER
MORE PROFITABLE
SERVICING!



HELP! HELP! HELP!

Let John F. Rider help you untangle your servicing problems. **RIDER MANUALS AND BOOKS** have guided tens of thousands of servicemen on to better servicing and greater profits. They can be your "good right hand," too! Order from your Jobber today!

RIDER MANUALS

Now, more than ever, it is urgent that you have at your fingertips the priceless servicing data that can be found **ONLY** in **RIDER MANUALS**.

Rider TV Manual Vol. 6



ACCURATE... AUTHENTIC... FACTORY-AUTHORIZED TV servicing information DIRECT from 66 MANUFACTURERS. Big 12" x 15" page size, and all pages filed in place. Large, easy-to-read diagrams. Everything you need to speed servicing and satisfy your customers.

Exclusive Features:

- ALL TV production runs and changes from August, 1950 through January, 1951.
- Circuit action descriptions.
- Unpacking and installation material.
- Signal waveforms for troubleshooting.
- COMPLETE alignment data.
- COMPLETE parts list.
- Circuit changes.

Equivalent of 2320 pages (8 1/2" x 11") plus Cumulative Index Volumes 1 through 6... \$24.00. With all 6 **RIDER MANUALS** you will own the world's greatest compilation of TV servicing information. **SEE YOUR JOBBER TODAY!**

Now Available!

RIDER MANUAL Vol. XXI



FACTORY-AUTHORIZED servicing material from 61 manufacturers... AM—FM—Auto Radios—Record Changers—Disc and Tape Recorders. Coverage from December, 1949 through October, 1950. 1,648 pages PLUS Cumulative Index Volumes XVI through XXI... **\$21.00**

Television Manual Volume 6 (Plus Index)	\$24.00
Television Manual Volume 5 (Plus Index)	24.00
Television Manual Volume 4 (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 3 (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 2—In new, larger page size 12" x 15". (Plus "How It Works" Book and Index)	24.00
Television Manual Volume 1 (Plus "How It Works" Book and Index)	19.80
Volume XXI	21.00
Volume XX	21.00
Volume XIX	22.50
Volume XVIII	22.50
Volume XVII	19.80
Volume XVI	9.90
Volume XV	22.50
Volume XIV to VII (each volume)	19.80
Volume VI	15.00
Abridged Manuals I to V (one volume)	19.80
Master Index, Covering Manuals Vol. I to XV	1.50
PA Equipment Manual, Volume I	18.00

RIDER BOOKS

Practical books, written by men with actual firing line experience... help you increase your knowledge... save you time and money.

BEAT THE TUBE SHORTAGE



RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton
For TV-AM-FM Receivers
and Allied Equipment

This amazing book shows you how to keep radio and TV sets working even though exact tube replacements are unavailable. 2500 radio and television tube substitutions listed, TV receiver filament wiring; heater substitution wiring instructions; tube types classified by functions... plus other important data you must have in order to keep receivers going. 224 pages, 8 1/2" x 11" durable paper cover... **Only \$2.40**

ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usfan



This is the **ONLY** book that so fully describes the oscilloscope... its application in servicing, engineering, research. It contains thousands of time-saving and work-saving references, charts, waveforms, etc. More than 70 different models are described with specifications and wiring diagrams. 992 pages, 8 1/2" x 11", 3000 illustrations. 22 chapters, completely indexed... **Only \$9.00**

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



Here are facts you should know about wind surfaces, mounting requirements, etc. Here is accurate data on receiver adjustment in the home. Here are municipal regulations in all major TV areas. Here is complete information on mechanical and electrical considerations. 330 pages, 5 1/2" x 8 1/2", 270 illustrations. Cloth bound... **Only \$3.60**

OTHER BOOKS FOR THE SERVICEMAN

TV Master Antenna Systems	\$5.00
TV and Other Receiving Antennas	\$6.00
Radio Operator's License Q & A Manual, 2nd Edition	\$6.60
The Business Helper	\$2.00
FM Transmission and Reception	\$3.60
TV Picture Projection & Enlargement	\$3.30
Broadcast Operator's Handbook	\$3.30
Understanding Vectors and Phase	Cloth Cover \$1.89 Paper Cover \$0.99
Inside the Vacuum Tube	\$4.50
Understanding Microwaves	\$6.00
Servicing by Signal Tracing	\$4.00
Installation and Servicing of Law Power	
Public Address Systems	\$1.89
Vacuum Tube Voltmeters (Revised)	\$4.50
Automatic Frequency Control Systems	\$1.75

JOHN F. RIDER PUBLISHER, Inc. • 480 Canal St., New York 13, N. Y.

RADEX CO.

1722 Massachusetts Ave., Cambridge, Mass.

April 11, 1951

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Gentlemen:

If you want the accurate factory authorized service data you can find it only in Rider Manuals. I have been using Riders for the past twenty years and I don't know what I could do without them. I am sure that any set, AM-FM or TV, that I am called upon to service can be found in Rider Manuals. All pages filed in their proper places, properly indexed, make it easier to locate the model numbers in a jiffy.

Thanks for the excellent service.

Very truly yours,
RADEX CO.
Charles R. Rice
Ralph A. Panetta

RADIOLAND

108 Bedford Street, Fall River, Mass.

April 20, 1951

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Gentlemen:

As a researcher in Electronic devices for the U. S. Navy during the last war, I have found out that nothing compares with Rider Manuals for trouble shooting radio and television receivers. I have a complete set of the streamlined Rider Manuals. When a difficult service problem arises, with Rider Manuals at my fingertips, nothing is too hard. Due to our efficient service work with the aid of Rider Manuals, I have been appointed as the service organization for the most exclusive set manufacturers.

Very truly yours,
RADIOLAND
Alfred A. Fysel

STEWART-WARNER ELECTRIC

DIV. OF STEWART-WARNER CORPORATION

1826 Diversey Parkway, Chicago 14, Ill.

March 29, 1951

John F. Rider Publisher, Inc.
480 Canal Street
New York 13, N. Y.

Attention: Mr. S. B. Schlenger

Dear Mr. Schlenger:

Thanks very much for the complimentary copy of Volume 21 of your Perpetual Trouble Shooters Manual. I have personally checked its contents, giving particular attention to the service literature applicable to our products, and as usual I have found it to be complete in every respect.

I am sure that the thousands of radio and television service men who rely on Rider publications for their technical data will find their investment in this manual to be as profitable as their past investments in Rider literature have been.

Congratulations on another outstanding job.

Very truly yours,
STEWART-WARNER ELECTRIC
R. W. Felber
R. W. FELBER
Service Manager


RWF:br

★ Build Your Service-Sales Future on a Firm Foundation With.....

PRECISION
TEST EQUIPMENT
Standard of Accuracy...

These 5 "Precision" Instruments Provide a Complete, Modern Service Lab... for TV-FM-AM ...at only moderate cost.

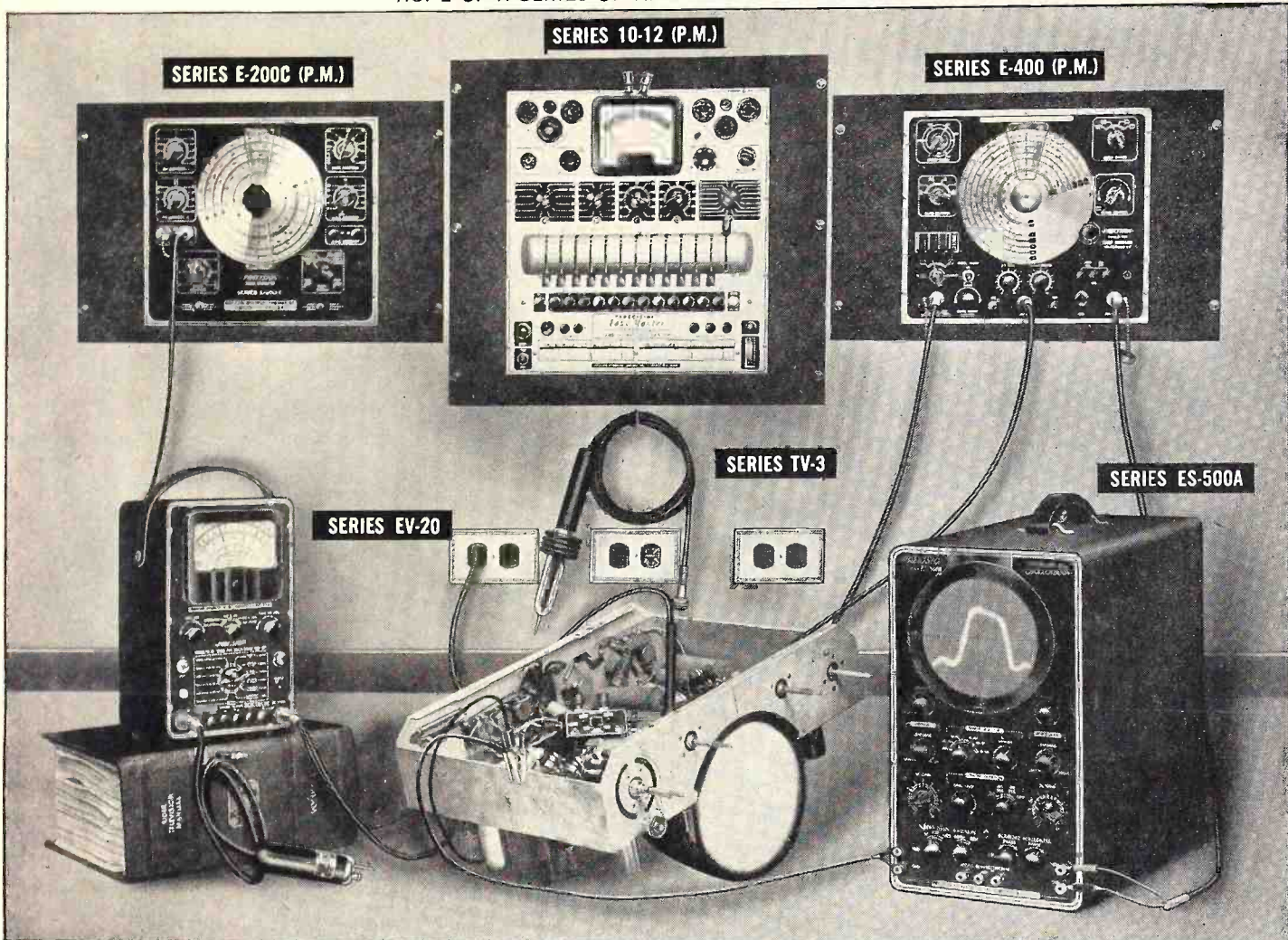NO. 2 OF A SERIES OF MATCHED COMBINATIONS



**SERIES E-200C (P.M.)
SIGNAL AND MARKER
GENERATOR**

Exceptional Accuracy and Stability • Direct reading • 88 KC to 120 MC. • 1000 pt. vernier calibrating scale • 0-100% Modulation • A.V.C. • A.G.C. Substitution network • Complete with output cable and technical manual. In standard panel 19 x 12 1/4".
Net Price: \$76.75

**SERIES E-400 (P.M.)
SWEEP SIGNAL
GENERATOR**

Narrow and Wide Band Sweep for F.M. and TV • Direct Freq. reading 2 to 480 MC. • Multiple Crystal Marker • 8 tubes including V.R. and rectifier • RG/62U Coaxial Terminated Output • Complete with 2 crystals. In standard panel 19 x 12 1/4".
Net Price: \$140.00

**SERIES ES-500A
5" OSCILLOSCOPE
Wide Range
High Sensitivity**

Push-Pull V and H Amplifiers • Response to 1 M.C. • High impedance, compensated V input Step Attenuator • Z axis modulation • 12 tubes incl. V.R. and 2 rect. • Detachable light shield and mask • Heavy gauge steel case. 8 1/4 x 14 1/2 x 18".
Net Price: \$169.50

**SERIES EV-20
True Zero Center VTVM
& Multi-range Test Set**

48 ranges to 1200 V., 2000 meg., 63 DB, 12 amps. • Voltage Regulated Bridge Type Circuit • 13 1/3 Megs. D.C. Input resistance • Direct reading high freq. scales • Optional RF-10-A High Freq. Probe • Heavy gauge steel case 6 1/4 x 5 x 10 1/2".
Net Price: \$68.25

**SERIES 10-12 (P.M.)
Electronamic*
TUBE MASTER**

Employs famous "PRECISION" Electronamic tube performance testing circuit plus dynamic Battery Tester • 12 element, anti-obsolescent-free-point lever system • Roller-chart • Dual short-check • Noise tests • In standard panel 19" x 17 1/2".
Net Price: \$106.50

SERIES TV-3 SUPER HIGH VOLTAGE SAFETY TEST PROBE. Extends range of Series EV-20 to 30 KV direct reading. Series TV probes available to match most VTVM's and 20,000 ohms per volt test sets. (NOTE: For deluxe Series EV-10 VTVM, with extra-large 7" meter, order Series TV-1 probe.)
Net Price: \$14.75

*Reg. U.S. Pat. Off.

BUY PERFORMANCE—NOT SPECIFICATIONS!—BUY "PRECISION"

"PRECISION" PERFORMANCE, ACCURACY, WORKMANSHIP and VALUE have been setting a standard of comparison for over 15 years. DO NOT BE MISLED... It is not "PRECISION" test equipment unless it is manufactured by Precision Apparatus Co., Inc., Elmhurst, L.I., N.Y.

OTHER MATCHED COMBINATIONS

The instruments shown above illustrate one of many possible MATCHED COMBINATIONS of diversified "PRECISION" Test Equipment for TV-FM-AM. Each combination provides a selected and basic, modern, efficient Laboratory at moderate cost.

"Precision" Instruments are on display at leading radio equipment distributors.

• TV • FM • AM



PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York

Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

Convenient Purchase Terms can be arranged with your favorite Precision Distributor.

AM • FM • TV •

Please mention Successful Servicing when answering advertising.

LOUDSPEAKER MATCHING

(Continued from page 1)

Thus, by properly connecting loudspeakers in series, parallel, or series-parallel circuits, not only can proper impedance matching be secured, but also the proper division of power may be obtained to provide the required sound level at each loudspeaker location.

Special Distribution Problems

Power distribution problems can often be solved by the insertion of a resistor of the proper ohmic and wattage values. To give a very simple example, assume that an installation requires three loudspeakers of equal output. Assume that the loudspeaker voice coils have impedances of 8 ohms each, and it is necessary to use the amplifier 8-ohm tap.

These requirements can be met by a setup such as shown in Fig. 1. The dummy load

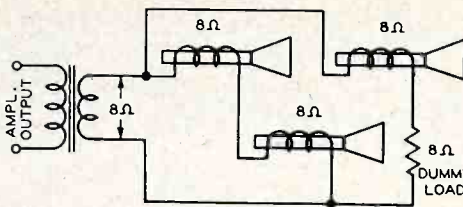


Fig. 1. Setup using an 8-ohm dummy resistor. absorbs the same power as the other loudspeakers and permits proper and uniform output.

Of course this is only one example of meeting power distribution and impedance matching problems between loudspeakers and the

output of some amplifier system. Other types of examples and methods regarding these problems are discussed further in INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS.

Belmont Console C-1104B, Suburban M-1105B, Rover M-1106, Belmont M-1107, Ch. 12AX27

A new RMA date code numbering system is now being used to number the chassis used in the above models. This new code system, consisting of six numbers and starting with 124023, will be stamped on the rear flange of the chassis. The first three numbers designate the manufacturer, the fourth number is the year, and the last two numbers represent the week number of the year.

The following changes apply to all chassis stamped with the RMA date code number 124023 and above. The video amplifier tube (12AU7) was changed to a 12AT7. Due to this change the video amplifier stage has been redesigned, although with the exceptions listed below, the wiring has remained the same. Coil L30, 410 μ hy, is now located from pin 7 of the 12AT7 to R37. The value of R37 has been changed from 8200 ohms to 3900 ohms. The value of resistor R35, connected to pin 6 of the 12AT7, has been changed from 6800 ohms to 4700 ohms, and the value of capacitor C60 connected in parallel across R35, has been changed from 68 μ mf to 100 μ mf. Resistor R38, connected from the junction of C60, R35, and C62, to C94-A and R123, has been changed in value from 3300 ohms to 1500 ohms. The 5600-ohm resistor R122, connected from the junction of R38, C94-A, and R123, to the 155-volt bus has been deleted, and the line is no longer connected to the 155-volt bus. Resistor R123 is now connected to the junction of R101, R102, and R39, instead of to ground. Peaking coil L20, 165 μ hy, is now located from pin 1 of the 12AT7 to the junction of L21 and C64.

Capacitor C24, 7 μ mf, has been removed from its position in parallel with C26 (connected to pin 5 of the 6J6 oscillator) and is now located in parallel with L9 and capacitor C29. The value of R82, connected from C99 in the afc circuit to pin 5 of the age amplifier and tap 6 of transformer T6, has been changed from 220,000 ohms to 470,000 ohms.

The parts list shown below lists the component changes that apply to these models.

Ref. No.	Part No.	Description
Tube 8	12AT7	Video amplifier
L-19	A-201-19363	Video trap and coil assembly
L-20	A-16A-19366	Peaking coil
L-21	A-16A-19367	Peaking coil
L-30	A-16A-19365	Peaking coil
C-60	C-8F1-113	100 μ mf x 300 volts
R-35	C-9B1-70	4700 ohms, 1/2 w, 10%
R-37	C-9B1-69	3900 ohms, 1/2 w, 10%
R-38	C-9B2-64	1500 ohms, 1 w, 10%


MEET "BILL" SLAWSON

On April 23, 1951, William "Bill" Slawson joined John F. Rider Publisher, Inc., as general sales manager. Formerly distributor sales manager of Federal Telephone and Radio Corporation, Bill came to us with an excellent sales background and a thorough familiarity with the electronics parts industry. He will direct the advertising and selling programs of Rider Manuals and texts.

ONE STANDARD - The best that can be made - For Initial Equipment and Replacement



TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

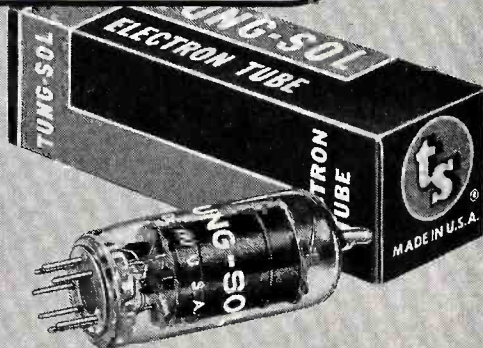

Optical comparator is used to check mica disc specifications to thousandth-inch accuracy.

TUNG-SOL LAMP WORKS INC., Newark 4, N. J.

Sales Offices: Atlanta · Chicago · Dallas · Denver · Detroit · Los Angeles · Newark

WE GUARANTEE that RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is... what it can DO... and HOW to use it properly!



ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usan

The **FIRST and ONLY** book that so fully and clearly describes the 'scope... its construction... its capabilities... its applications in communications, engineering, research... with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you... **WHAT** each type can do... **HOW** to use it... and **WHICH** is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians—all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages... 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home... municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY** and **IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth Bound.....And only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Usan



The entire system of frequency modulation is explained thoroughly... all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

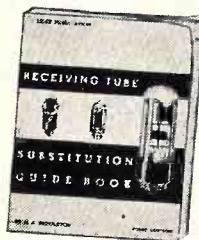

For AM-FM-TV Receivers and Allied Equipment!

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

EXTRA! In addition to tube information... this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc....

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New... Revised... Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman



All the **QUESTIONS** and **ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH**... a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer. It also lists "extras" not ordinarily found in a volume of this type... including Useful Appendices which take in Small Vessel Direction Finders and Automatic Alarm.

766 Pages, Hundreds of Explanatory Diagrams..\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc.... in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed,

how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth bound.....Only \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.

Television Changes

Westinghouse H-600T16, Ch. V-2150-61; H-601K12, H-602K12, Ch. V-2150-41; H-604T10, H-604T10A, Ch. V-2150-91A, Ch. V-2150-94, Ch. V-2150-94A

When these models are operated in weak signal areas, an improvement in the vertical hold characteristic may be desirable. An improvement can be obtained at the expense of increased susceptibility to noise pulses by changing the value of the resistor that is shunted across the integrating network input. This resistor is designated R419 in Models H-600T16, H-601K12, and H-602K12, and R416 in Models H-604T10 and H-604T10A. This resistor is normally 1000 ohms. To obtain the effects noted above, the resistor should be changed to 1800 ohms.

A 33-ohm resistor and a 0.033- μ f capacitor in the cathode circuit of the 6AH6 video output tube provide a sharper picture in these models. However, the sharper picture is obtained at the expense of video gain, and it may be desirable in weak signal areas to sacrifice the sharpness in favor of increased gain. The gain of the video amplifier can be increased by connecting a wire between pin 7 of the 6AH6 video output tube and the high side of the contrast control so as to short across the resistor and capacitor described above. A further increase in gain can be obtained at the expense of picture definition by changing the value of the plate load resistor for the 6AH6 video output tube. This resistor, which is normally 3600 ohms, can be replaced by a 3900-ohm, 1-watt resistor.

Capehart-Farnsworth, Ch. CX-33, CX-33A, CX-33F, CX-33K, CX-33L, CX-33LH, CX-33M, CX-33N, CX-33P, CX-33R, CX-33S

The following list shows the models that use the CX-33 series chassis:

Chassis No.	Size CRT	Used in Models	Prod. Runs
CX-33 (C-281)	16" Rect.	3011-M & B, 321-M & B, 322-M & B, 325-F	1, 2, 3, 4 & 5
CX-33F (C-286)	16" RD.	323-M, 332-M & B, 334-M	2, 3, 4 & 5
CX-33L (C-289)	17" Rect.	320-M & B, 321-AM & AB, 322-RAM & RAB, 324-M & B, 325-AF, 326-M	3, 4 & 5
CX-33LH (C-304)	17" Rect.	333-M & B	3, 4 & 5
CX-33N (C-298)	17" Rect.	320-M & B, 321-AM & AB, 322-RAM & RAB, 324-M & B, 325-AF, 326-M	5
CX-33S (C-303)	20" Rect.	335-M & B	5
CX-33A (C-285)	16" Rect.	327-M	3, 4 & 5
CX-33M (C-290)	17" Rect.	328-M, B, AB	3, 4 & 5
CX-33P (C-299)	17" Rect.	328-AM	5
CX-33K (C-292)	19" Rd.	337-M & RM	4 & 5
CX-33R (C-302)	20" Rect.	337-RAM	5

Chassis CX-33, CX-33F, CX-33L, CX-33LH, CX-33N and CX-33S are used in "TV only" instruments. Chassis CX-33A, CX-33M, CX-33P, CX-33K and CX-33R are used in "combination" instruments.

Production run No. 1 (the original CX-33 production) chassis were not coded, and the run was confined to sets using a 16" rectangular picture tube. Therefore, uncoded chassis employing a 16" rectangular crt can be considered as run No. 1. Production runs Nos. 1 and 2 were confined to sets using a 16"

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means BIGGER PROFITS for you!


The NEW ESPEY model 511-B

FEATURES

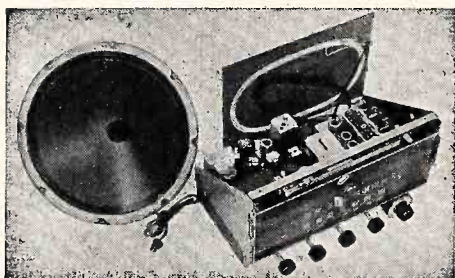1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY
TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.


Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

rectangular or 16" round picture tube. Production Runs Nos. 1 and 2 employed the Sarkes-Tarzan r-f unit, while runs Nos. 3, 4, and 5 employ the Standard Coil r-f unit. Chassis used in combination instruments (less audio section) do not employ V-209 and V-210, the 1st audio amplifier and power output tubes, respectively, and their circuits.


The schematic diagram for Production Runs Nos. 4 and 5 is similar to that for Run No. 3 except for the following changes. A printed circuit vertical integrator PC-201 is used in some chassis replacing R261, R260, C239 and C238. The printed circuit is shown in the accompanying illustration, showing the change in value of R259 and C237. B is connected to C240, A is connected to the -90-volt line, and C is connected to the cathode pin 3 of the 6SN7GT sync clipper.

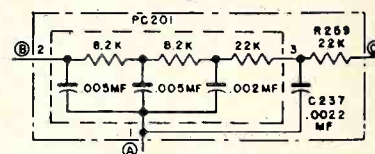

Printed circuit vertical integrator PC-201.

V203, the 3rd i-f stage has been changed from a 6AG5 to a 6CB6 tube. The socket wiring has been changed so that pin 7 (suppressor grid) is grounded. A 6AG5 tube cannot be used as a replacement in this socket unless the ground is removed from pin 7 and tied to pin 2 as shown on the schematic for Run No. 3. In connection with this tube change, R210, the grid resistor for V203, has been changed from 5600 ohms to 8200 ohms. A revised focus coil (Part No. 750249B-3) is incorporated in run No. 5 chassis. The construction of this coil has been revised to prevent breakdown. In the revised focus-coil-assembly mounting arrangement, the centering lever has been removed and the focus coil bracket has been provided with a wing screw


(Continued on page 12)

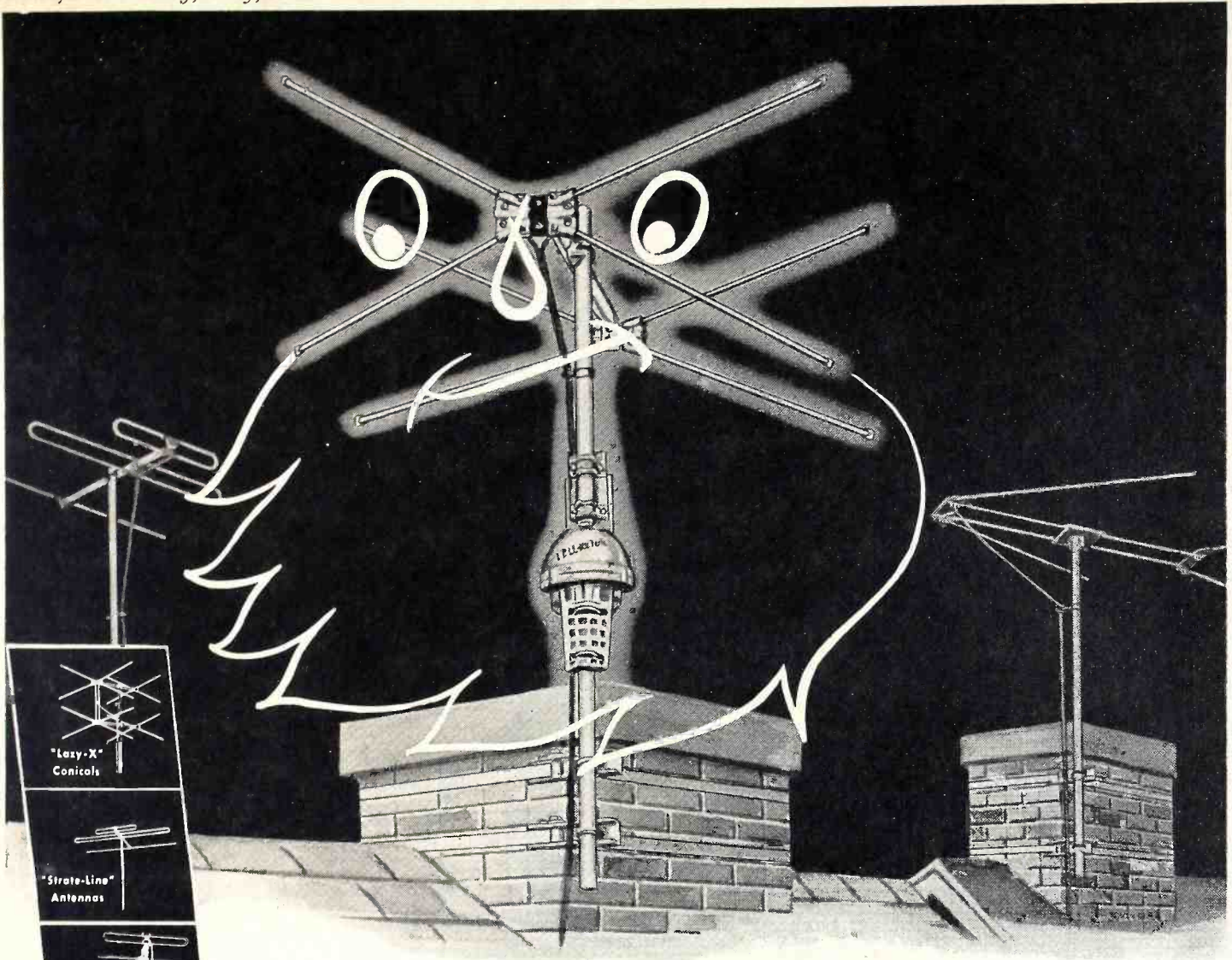

When It's Needed the Most...

RADIART Quality Meets the Challenge

IF it were possible for antennas, like men, to grow beards, RADIART ANTENNAS would have them. Because they're designed to last and last, in fact, to grow "old enough to shave". This length of service is one of the invisible features of RADIART design and construction that have helped establish leadership in the antenna field. When an installation of a RADIART antenna is completed, the serviceman and his customer KNOW that *that* antenna is up to stay and will perform in the manner of a true champion. No shorting out . . . no bending or twisting in wind, rain or snow . . . no rusting away of the elements — they're built to last. When it comes to durability, too . . . again, RADIART quality meets the challenge.

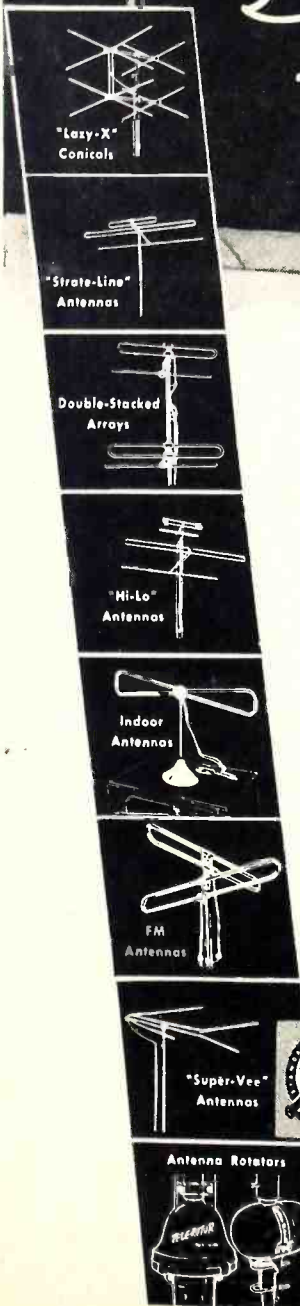

SUBSIDIARY OF



THE RADIART CORPORATION CLEVELAND 2, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES
Please mention Successful Servicing when answering advertising.

Capehart-Farnsworth Ch. CX-33 Series

(Continued from page 10)

at the side and also at the bottom. By loosening these two screws, the focus coil can be tilted in both the horizontal and vertical plane, thus providing picture centering. When the picture is properly centered, the wing screws can be tightened so that proper centering will be maintained.

The 10,000-ohm resistor R316, connected from the junction of focus control R297 and the plus side of capacitor C243C to the minus side of C243C, has been removed from the circuit. Capacitor C242B, connected to the junction of R298A and R298B, has been relocated and is now connected in the picture tube circuit (described below). A 20- μ f capacitor C285 is now connected from the junction of R298A and R298B to ground. A 0.1- μ f, 200-volt capacitor C286 has been added from the plus side of C242D to the -90-volt line. The value of R252, connected from the junction of the +235-volt line, R201 and C282 to the junction of R302 and R250, has been changed from 2.4 megohms to 2 megohms.

In the picture tube circuit the following changes have been made. A 100,000-ohm resistor R317 and a 0.1- μ f capacitor C284, connected in parallel, have been added from the junction of L207 and R232 to pin 11 of the picture tube, replacing a direct connection. R307, connected to pin 6 of the video amplifier, is no longer connected to +135-volt line, but is connected directly to the junction of C229 and R236 (connected to the shading control R235). The connection from C229 and R236

to the +135-volt line also has been removed. The value of R236 has been changed from 27,000 to 68,000 ohms. R306, the 5000-ohm resistor that was connected to the +235-volt line, is no longer connected to this line but now connected directly to the junction of C229, R236 and R307. A 5000-ohm resistor is connected from this junction to the +235-volt line. The minus side of C242B (mentioned previously) is connected to shading control R235 and the -90-volt line and the plus side is connected to the junction of R306 and R318. The value of R235 has been changed from 50,000 ohms to 200,000 ohms.

The value of C257, connected from pin 5 of V218 to the junction of R289 and R290, has been changed from 0.001 μ f to 0.0047 μ f. The 500- μ f, 20-kv capacitor C261 that was connected from ground to pin 2 of the h-v rectifier is now connected from ground to pin 7 of the same tube. The value of R268, connected to pin 4 of V214B, has been changed from 100,000 ohms to 470,000 ohms. R315, part of the deflection yoke L216, is used only in RCA, Sickles & Joyner yokes which have a coil resistance of 3.3 ohms. R308, connected to pins 3 and 4 of the 6K6GT tube V215 is 56,000 ohms on Chassis CX-33S. C270, the 270- μ f capacitor in the deflection yoke is omitted on the CX-33S Chassis.

The following parts should be added or changed in the Parts List for Chassis CX-33 series and are specifically for Production Run Nos. 4 and 5:

Ref. No.	Part No.	Description
R317	3229A-104	100,000 ohms, $\frac{1}{2}$ w, 10%, ins. carb.
R318	650101A-8	5000 ohms, 7 w, 10%, ww

FREE TEACHING AID FOR TV INSTALLATION INSTRUCTORS!

Instructors: You are invited to send for a *free* Term Plan for your television installation courses. Prepared by Samuel L. Marshall, this Term Plan centers around 75 theory lessons, and includes 19 shop projects for the lessons. The theory lessons tell the student *why* things are done; the shop lessons show him *how*.

Both the shop and the theory lessons refer you on each point to specific sections in Mr. Marshall's text, TV INSTALLATION TECHNIQUES. The plan is flexible and may be adjusted to a course of any length.

The Term Plan is available, at absolutely no cost, to *instructors only* for use in their television installation courses. Write on your school stationery to:

School Division

John F. Rider Publisher, Inc.
480 Canal St., New York 13, N. Y.

C284	2246A-1040	0.1 μ f, 200 v, paper
C285	650228A-2	20 μ f, 450 v, electrolytic
PC-201	452265A-1	Printed circuit
R210	3229A-822	8200 ohms, $\frac{1}{2}$ w, 10%, ins. carb.
R259	3229A-223	22,000 ohms, $\frac{1}{2}$ w, 10%, ins. carb.
R252	3228A-205	2 megohms, $\frac{1}{2}$ w, 5%, ins. carb.
R235	452226A-1	200,000 ohms, shading pot.
R236	3229A-683	68,000 ohms, $\frac{1}{2}$ w, ins. carb.
C237	2248A-2220	0.0022 μ f, 600 v, MOPT
L215	750149B-3	Focus coil, revised.

ORDER YOUR COPY NOW
RIDER TV VOLUME 6

Stromberg-Carlson TC19LX

The schematic diagram and service data for Model TC19LX is the same as for the TC19 Revised. The general assembly parts list for Model TC19LX is given below.

Part No.	Description
108147	Cabinet assembly, mahogany
108148	Cabinet assembly, avodire
155129	Speaker
1382029	Lens
134081	Knob (tone and volume)
134081	Knob (focus and brightness)
134081	Knob (vertical and horizontal)
134083	Knob (contrast)
134108	Knob (tuning)
134084	Knob (range selector)
101122	Back panel assembly
29956	Pilot lamp
801401	Lamp cap, red
801400	Lamp cap, white
101123	Tube mounting shelf
113065	Kinescope clamp assembly
105214	Focus coil support assembly
105110	Deflection yoke bracket
133074	Tube ring (plastic)
174010	Mask
165016	Anode connector, male
165017	Anode connector, female
143013	Plug assembly, 8 prong male
133075	Kinescope insulating sleeve, plastic
133078	Focus coil gasket (rubber)
133079	Kinescope clamp insulation
133080	Kinescope mounting block insulation
125046	Escutcheon assembly
125045	Escutcheon, front panel
105211	Bracket, flexible shaft (front panel)
150061	Flexible control shaft (contrast)
150062	Flexible control shaft (range)
150063	Flexible control shaft (tuning)
129023	Gear assembly (tuning)
150059	Shaft assembly (tuning)
122038	Dial assembly (tuning)
142105	Plate, flexible shaft mounting
142108	Plate, potentiometer mounting
150064	Flexible control shaft (focus)
152065	Pilot lamp socket assembly
29956	Pilot lamp $\frac{1}{4}$ amp
151108	Shield, focus potentiometer.

HIGH FIDELITY WIDE ANGLE DISPERSION and HANDSOME APPEARANCE

University LOUDSPEAKERS

Whether for the home or for use in a sound re-inforcement installation, specify UNIVERSITY—high fidelity reproducers with a tradition for quality and performance. UNIVERSITY "progressive engineering" assures you exclusive pace-setting design features, reliable factory ratings, and the advantage of specialized manufacturing know-how that brings you top quality products at sensible cost. Investigate, and be convinced that installing UNIVERSITY means installing the best.

Available Now! The TECHNILOG

New and informative, a technical catalog with valuable hints on sound-casting techniques and installation suggestions. Write today to Desk 51.

UNIVERSITY LOUDSPEAKERS • INC



80 SO. KENSICO AVE., WHITE PLAINS, NEW YORK

Please mention Successful Servicing when answering advertising.



MODEL 6200 WIDERANGE SPEAKER

Indisputably
today's best
buy in a
top quality,
high fidelity
12" reproducer

Specially shaped one-piece moulded cone provides wide angle dispersion. Cone edge treated for long life, also reduces distorting standing waves. Three inch dural dome at cone apex reinforces "highs," minimizes cone "break-up." Exclusive "W" shape Alnico 5 magnet, shockproof assembly result in unusual conversion efficiency—requires less amplifier power, assures low distortion output. 4" overall depth perfect for P.A. or home wall and ceiling mounting. Response 45 to over 10,000 cps, 8 ohms, 30 watts power capacity.



**"HURRY, HURRY, HURRY!
DON'T MISS THIS NEW,
SIMPLIFIED SERVICING BOOK!"**

FREE!

**only until May 31st...
with the purchase of one
Sylvania Picture Tube!**

Don't let this offer expire without your getting a copy of this splendid, fact-packed servicing manual. Filled with time-saving shortcuts and valuable servicing hints.

Now it's yours absolutely FREE from your Sylvania Distributor with the purchase of just one Sylvania Picture Tube, of any type. But the offer expires May 31st. So, act NOW! Write or call your distributor TODAY!

**SAVES TIME! SAVES MONEY! SOLVES
SCORES OF SERVICING PROBLEMS!**



This book contains 48 pages of pictures, diagrams, and easy-to-follow instructions covering:

Radio Servicing . . . Signal Tracing, Alignment, AVC and AFC Checking, Measurement of Voltages, Signal Levels, Power Output, Band Width and much more.

TV Servicing . . . Signal Tracing, Bandwidth Measurements, Wavetrap Checking, Sound Channel Tests and Alignment, Low and High Voltage Checks, Signal and Deflection Voltage Measurements, and numerous other subjects.

Audio Amplifier Servicing . . . DC, AC, and Signal Level Measurements; Tone Control, Fidelity, Gain Tests, Distortion, Power Output, and Noise Level Measurements; Signal Tracing, and Speaker Matching.

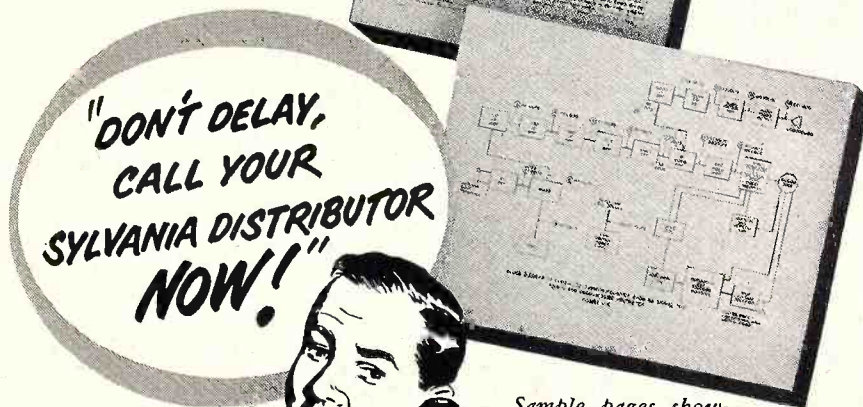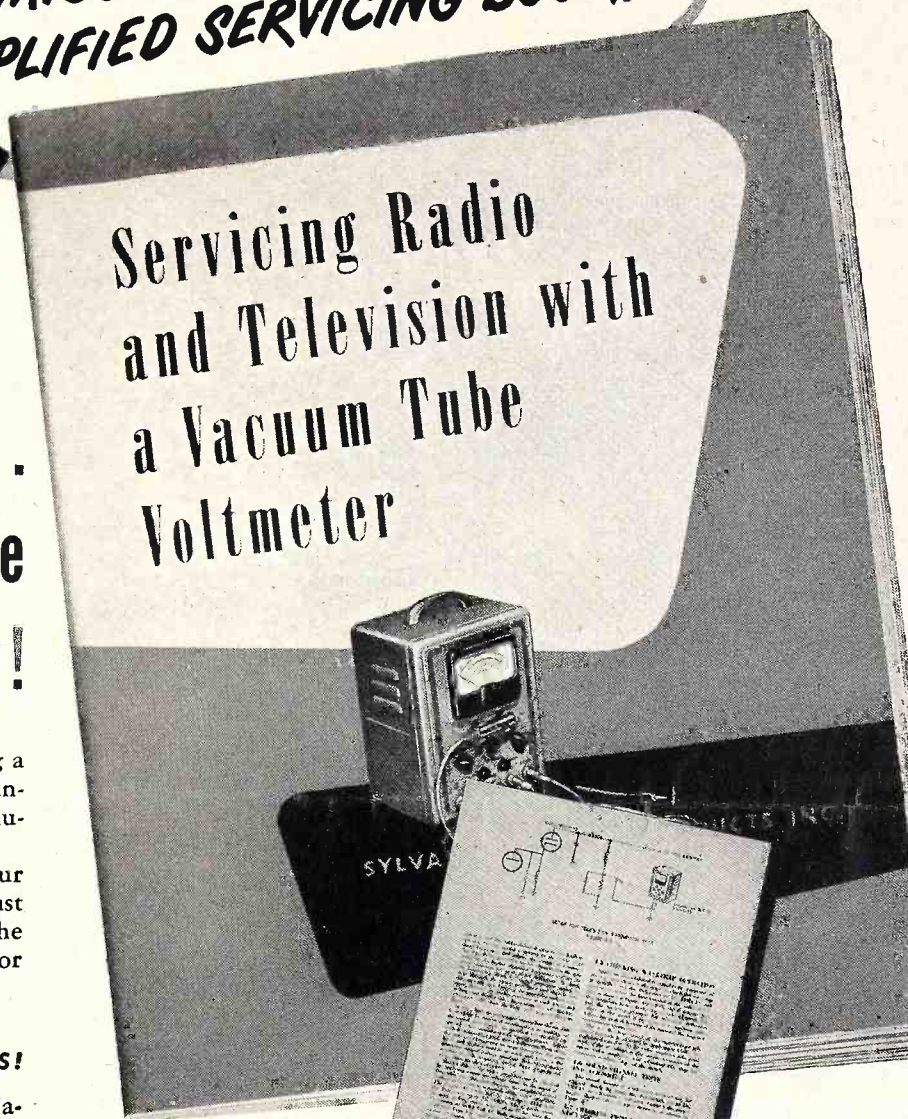Miscellaneous Applications . . . 19 different applications of VTVM including Detecting Gassy Tubes, Checking Capacitors, Q Measurement, Turns Radio Measurement, Impedance Checking.



**"DON'T DELAY,
CALL YOUR
SYLVANIA DISTRIBUTOR
NOW!"**



Sample pages showing detailed, easy-to-read diagrams.



SYLVANIA ELECTRIC


RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

Please mention Successful Servicing when answering advertising.

Radio Changes

Sparton 141XX, 142XX, 1040XX,
1041XX, 1085, 1086, 1090, 1091,
Ch. 8W10

Chassis 8W10 is similar to Chassis 8M10, and the service notes for the 8M10 apply also to the 8W10. The schematic diagram for the 8W10 is the same as that for the 8M10 except that a 68-ohm resistor, R38, has been added from the junction of C1B and C2B to pin 7 (a.m.) of switch S1-R. Models 141XX in mahogany and 142XX in blond are straight table model radio receivers. A new dial, front panel, and control knobs distinguish these models from Models 141X and 142X. Models 141XX and 142XX are equipped with a 6" x 9" p-m oval speaker.

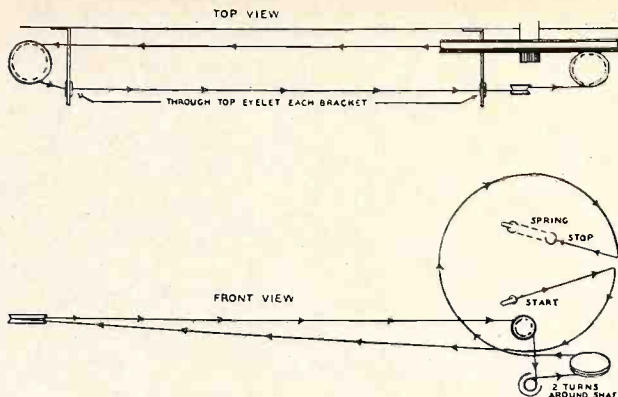

Models 1040XX in mahogany and 1041XX in blond are radio-phonograph combinations. The models also have new dials, front panels,

Dial stringing for
Sparton Chassis 8W10.

and control knobs and are equipped with a three-speed record changer. The cabinet styling is the same as Models 1040X and 1041X. The receiver chassis is mounted to the tilting front panel in the right-hand cabinet compartment. A 10-inch p-m speaker is standard equipment.

Models 1085 in mahogany and 1086 in blond are radio-phonograph combinations. The receiver chassis is mounted in the top center compartment with the record changer directly below. A compartment either side of the units has been reserved for record album storage. The record changer is stationary mounted. These models employ a 10-inch p-m speaker.

The accompanying illustration shows the dial stringing for these models.

The Chassis Parts List for these models is the same as the Parts List for the 8M10 Chassis. The following parts apply to Chassis 8W10 and the models which use this chassis:

Part No.	Description
PA5654	Knob, maroon, 4 req'd (1085 only)
PA5625-1	Knob, black, 4 req'd (1086 only)
PA5654-1	Knob, volume (all other models)
PA5654-2	Knob, tone, on-off
PA5654-3	Knob, f-m, a-m, ph.
PA5654-4	Knob, tuning
PB30017	Dial scale
PB40150	Escutcheon, black (1086 only)
PB40150-1	Escutcheon, maroon (1085 only)
PD93012-1	Escutcheon, maroon and gold (141XX, 1040XX, 1090)
PD93012-2	Escutcheon, gold (142XX, 1041XX, 1091)
PC63000-12	Speaker, 10" round p-m (all consoles)
PC63000-19	Speaker, 6" x 9" oval p-m (table models)

Emerson 559, Ch. 120059A

The schematic diagram for Chassis 120059A shows two resistors marked R15. The one going to pin 6 of the 117Z3 should be marked R10.

General Electric 218, 218H

Stock No. RLI-088 has been deleted from the Parts List and Stock No. RLI-084, Coil, f-m antenna choke, L2, added in its place.

**ORDER YOUR COPY NOW
RIDER TV VOLUME 6**

Jewel 920A

The Alignment Procedure and Parts List for Model 920A is the same as that for Models 921, 935, 936.

RCA X551, Ch. RC-1089B; X552, Ch. RC-1089C

R4, the 3.3-megohm avc filter resistor previously connected to the junction of R12, 47,000 ohms, and the phono jack J1, is now connected to the junction of R12 and terminal 2 of the 2nd i-f transformer T2.



C-D's Champion PUP

—from a long line of winners!

Just introduced—already rated "best in its class"! It's C-D's PUP, the new and advanced metallized capacitor. *Saves space*—half the size of conventional paper tubulars. *Saves trouble calls*—unique self-healing feature means extra long service life.



Write for Bulletin N142, Dept. R51
Cornell-Dubilier Electric Corp.
South Plainfield, N. J.

CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
CAPACITORS

Plants in South Plainfield, N. J., New Bedford, Worcester and Cambridge, Mass.; Providence, R. I.; Indianapolis, Indiana; Fuquay Springs, North Carolina, and subsidiary, The Radiart Corporation, Cleveland, Ohio.
Please mention Successful Servicing when answering advertising.

215

SQUARE INCHES OF FINEST
PICTORIAL REPRODUCTION...

*new Bent-Gun for
edge-to-edge sharpness,
gray filter face plate,
"Standard" neck length of 7 $\frac{3}{16}$ "*



***Our commercial
engineering department
invites all design inquiries***

ALLEN B. DU MONT LABORATORIES INC., TUBE DIVISION, CLIFTON, N. J.

Please mention Successful Servicing when answering advertising.

63,500

There are 63,500 references to pertinent electronic and allied engineering articles published from 1925 through 1949 in the five editions of the

ELECTRONIC ENGINEERING MASTER INDEX

1925-1945 edition— (15,000 entries).....	\$17.50
1935-1945 edition— (10,000 entries).....	\$10.00
1946 edition— (7,500 entries).....	\$14.50
1947-1948 edition— (18,500 entries).....	\$19.50
1949 edition— (12,500 entries).....	\$17.50

Electronics Research Publishing Company, Inc.
Dept. 55, 480 Canal St., New York 13, N. Y.

Affiliated Retailers AR-MST12

Model AR-MST12 is similar to AR-TV-12X and employs a 12½-inch picture tube.

United Motors 980980, Buick

The 1951 Buick Model 980980 is identical to the 1950 Model 980899 except that the antenna trimmer compensation is for antennas between 0.000061 and 0.000088 μ f. The parts list is identical to that for the 980899 except for the following service parts. The service part numbers are the same as the production part numbers except where the service part number is shown in parenthesis.

Illus. No.	Production Part No.	Description
63	1219487	470 ohms, ½ w, insulated (removed)
85	1211118 (A104)	100,000 ohms, ½ w, insulated (removed)
119	7260856	Transformer, output
128	7260454	Escutcheon assy
129	7260455	Dial
130	7260422	Dial backplate
133	7260456	Pointer backplate
134	1219847	Pointer tip pkg.
	1219846	Station selector bar pkg.
139	7260709	Station selector bar.

TROUBLE SHOOTING

The serviceman, radio or TV, is most frequently called upon to act as a trouble shooter—to repair a radio or television set. In order to service any set efficiently and profitably, he must have a thorough knowledge of symptoms, causes, and remedies so that he can analyze, localize and correct the trouble as rapidly as possible. Because of the thousands of radio and television sets in existence today (there are 28,341 Models and 14,966 Chassis covered in Rider's AM-FM Manuals, and 2,486 Models and 1,227 Chassis covered in Rider's 6 TV Manuals), it is impossible to become completely familiar with each individual set. However, it is possible to continually increase ones working knowledge by reading the circuit analyses and service hints (which are compiled from the analyses of service reports from the field) that manufacturers, and, consequently, Rider Manuals, offer to the servicemen.

Considerable experience has been gained through the years in recognition of the symptoms and causes of, and remedies for, receiver failures. By careful reading of *all* service hints, the serviceman can first apply the material to the specific set, and then, by correlating the various service hints, can use the general information when trouble shooting other sets.

Trouble shooting hints given in this issue, for example, are found on page 2 for Freed Models 54, 55, 56 and 68, and for RCA Model 9TW390; on page 10 for Westinghouse Models H-600T16, H-601K12, H-602K12, H-604T10, and H-604T10A; and the Westinghouse notice on this page. Read these and all service hints and remember that circuit analyses and service hints are published in Rider Manuals and **SUCCESSFUL SERVICING** so that *you*, the serviceman, can profit from the manufacturer's experience!

Admiral 6P32, Ch. 6E1; 7P35, Ch. 5H1

Model 6P32 uses chassis 6E1 and Model 7P35 uses chassis 5H1. These models are leatherette portables using an a-c—d-c battery.

Westinghouse H-217, H-217A, Ch. V-2146-1 Ch. V-2146-11DX; H-226 Ch. V-2146-21DX, V-2146-25DX

With early production versions of the models listed above, it may be desirable to increase the picture width. Check the voltage divider (R501, R502, R503, R504) in the voltage doubler circuit of the high-voltage supply. In original production, the plate of the 1B3GT doubler tube was connected to the junction of R501 and R502. To increase the picture width, move the plate connection down to the junction of R502 and R503. This has been done in later production.

INDEX OF CHANGES

Model Page Number
Successful Servicing Rider Manual†
From To

TELEVISION CHANGES

Affiliated Retailers AR-MST12 AR-TV-12X	16	3-1	3-7
Belmont Console C-1104B, Suburban M-1105B, Rover M-1106, Belmont M-1107, Ch. 12AX27	8	5-1	5-8
Capehart-Farnsworth Ch. CX-33 Series	10, 12	5-1 6-1 C6-2	5-12 6-20 —
Freed 54, 55, 56, 68, Ch. 1620B	2	3-1 C4-6	3-13 —
Interstate Stores (Plymouth) 250, 350, 750	2	5-1	5-11
RCA 9TW390, Ch. KCS31-1 Radio Ch. RC617A	2	5-32 5-39	5-47 5-40
Westinghouse H-217, H-217A, Ch. V-2146-1, Ch. V-2146-11DX; H-226, Ch. V-2146- 21DX, Ch. V-2146- 25DX	16	5-11 5-26	5-25 5-34
H-217, H-217A, Ch. V-2146-1, Ch. V-2146- 11DX			
H-226, Ch. V-2146- 21DX, Ch. V-2146-25DX			
Westinghouse H-600T16, Ch. V-2150-61; H-601K12, H-602K12, Ch. V-2150-41; H-604T10, H-604T10A, Ch. V-2150-91A, Ch. V-2150-94, Ch. V-2150- 94A	10	4-17 4-25 4-33	4-24 4-32 4-40

RADIO CHANGES

Admiral 6P32, Ch. 6E1; 7P35, Ch. 5H1 Ch. 5H1 Ch. 6E1	16	16-9 15-16	16-10 15-17
Emerson 559, Ch. 120059A	14	18-12	—
Firestone 4-A-86, 4-A-95, Westmoreland	5	21-13	21-16
General Electric 218, 218H 218 218H	14	21-4 21-10	21-9 21-11
General Electric 521, 522	5	21-52	21-56
Jewel 920A 921, 935, 936	14	20-2 20-3	— 20-4
RCA X551, Ch. RC- 1089B; X552, Ch. RC-1089C	14	21-39	21-40
Spartan 141XX, 142XX, 1040XX, 1041XX, 1085, 1086, 1090, 1091, Ch. 8W10 Ch. 8M10	14	21-11	21-14
United Motors 980980, Buick 980899, Buick	16	21-37	21-42

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

PERMIT NO. 9427
NEW YORK, N. Y.
PAID
U. S. POSTAGE
Sec. 3456, P. L. & R.

DOUGLASSON, L. I., NEW YORK
5310 OVERBROOK ST.
A. J. S. CERINO

Return Postage Guaranteed
480 CANAL ST., NEW YORK 13, N. Y.
JOHN F. RIDER PUBLISHER, Inc.
From

JUNE, 1951

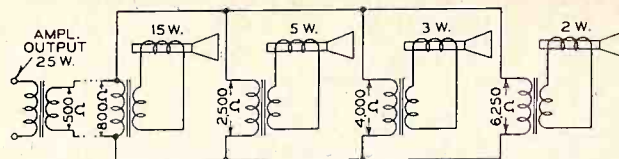


Fig. 1. A possible configuration for connecting loudspeakers requiring unequal power distribution. The individual matching transformer primaries must be so chosen that the correct power distribution is made to the various speakers.

LOUDSPEAKER MATCHING

by JOHN F. RIDER

Unequal Power Distribution— High-Impedance Lines

Although most loudspeakers have equal power distribution, there are many cases, such as in churches, schools, hospitals, factories, etc., where each loudspeaker must handle a different amount of power. The individual matching transformer primaries must then be of such impedance as to distribute the available power correctly among the various loads.

Assume that a 25-watt amplifier feeds four loudspeakers, rated at 15, 5, 3 and 2 watts, through a 500-ohm line. The primary impedance of the loudspeaker matching transformers may then be computed from the following formula: loudspeaker matching transformer primary impedance (Z_P) equals the line impedance (Z_{line}) times the ratio of amplifier power output (P_T) over rated loudspeaker power P_L ,

$$\text{or } Z_P = Z_{line} \times \frac{P_T}{P_L}$$

Thus the matching transformer primary impedance for the 15-watt loudspeaker is

$$Z_P = 500 \times \frac{25}{15} = 833 \text{ ohms}$$

The primary impedances for the other loudspeakers may be similarly found and are respectively 2,500 ohms, 4,170 ohms, and 6,250 ohms. Figure 1 illustrates how a close approximation to the desired power distribution is obtained. The impedances of the matching transformer primaries are in parallel so that the total load impedance approximately matches the line impedance. In actual practice, line or output transformers are used whose primary impedances are as close as possible to the calculated values.

In computing the primary impedances needed to secure power distribution, if any of the matching transformer primary impedances come to a value of 20,000 or more ohms, then the combination of loudspeakers must be changed or a lower line impedance used, since transformers having such high primary impedances do not have secondary impedances in the voice-coil impedance range. It will be necessary then to recompute the entire impedance problem using a lower impedance tap on the amplifier output transformer or by connecting the loudspeakers in different combinations. If the transformer primary impedance for the loudspeaker requiring the lowest power is computed first, it can then be determined whether or not this impedance is too great before proceeding with the rest of the computations.

An example of a more elaborate installation requiring unequal power distribution is given below. Ten 3-watt loudspeakers, three 5-watt loudspeakers, and one 15-watt loudspeaker are to be fed by a 60-watt amplifier in a school or factory sound system. The use of a high-impedance line is necessary since most of the loudspeakers will be located at some distance from the amplifier. All the loudspeakers are connected in parallel with their individual

matching transformers across a 500-ohm line fed by the 500-ohm tap of the amplifier output transformer. The primary impedances of the matching transformers can be determined by using the equation where Z_L is the effective load impedance:

$$Z_L = \frac{Z_{tap}}{\% P}$$

Substituting the known factors, we obtain three different loads for the three different powers required:

$$Z_L \text{ (for the 3-watt loudspeakers)} = \frac{500}{.50} = 1,000 \text{ ohms}$$

$$Z_L \text{ (for the 5-watt loudspeakers)} = \frac{500}{.25} = 2,000 \text{ ohms}$$

$$Z_L \text{ (for the 15-watt loudspeaker)} = \frac{500}{.25} = 2,000 \text{ ohms}$$

Since there are ten 3-watt loudspeakers in parallel and their effective load is to be 1,000 ohms, then each 3-watt loudspeaker requires a 10,000-ohm primary impedance-matching transformer. Since there are three 5-watt loudspeakers in parallel and their effective load is to be 2,000 ohms, then each 5-watt loudspeaker requires a matching transformer having a 6,000-ohm primary impedance. The single 15-watt unit requires a 2,000-ohm matching transformer.

To check that the total loudspeaker distribution system matches the 500-ohm tap, use the equation for parallel impedances. Since the impedances of the three types of loudspeakers are 1,000 ohms, 2,000 ohms and 2,000 ohms, then:

$$Z_T = \frac{1}{\frac{1}{1000} + \frac{1}{2000} + \frac{1}{2000}} = 500 \text{ ohms}$$

The voice coil impedances need not enter into any of the computations because most line or output transformers have secondary taps to match the more common voice-coil impedances.

(Continued on page 14)

Editor's Note: This is the last of three articles on Loudspeaker Matching, and is taken from INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS by John F. Rider, published by John F. Rider Publisher, Inc. Previous articles, which appeared in the April and May issues of SUCCESSFUL SERVICING, discussed the matching of loudspeakers on low and high impedance lines and unequal power distribution on low impedance lines. Loudspeaker matching is only one of the many topics pertaining to low power public address systems covered in the book, INSTALLATION AND SERVICING OF LOW POWER PUBLIC ADDRESS SYSTEMS. Other topics include fundamentals of sound, microphones, phonograph pickups, amplifier specifications, loudspeakers, installation (covering indoor and outdoor installations), and the servicing of public address systems.

Television Changes

Belmont Ch. 12AX27

If a squegging condition (parasitic oscillation) is noticed, the following wiring changes should be made. This change has been incorporated in group numbers above 7100.

Reroute the black a-c leads from the a-c input socket to the switch on the dual contrast and volume control. Disconnect the two black a-c leads at the switch terminals. Pull out the a-c leads from the side of the chassis and reroute them along the tuner side and bring them down to the switch. Cut off four inches from the longest lead and add eighteen inches to the shortest lead. Reconnect the leads to the switch terminals, making sure that they do not short to the chassis and will not tangle with the tuner or cam. It is suggested that a cable clamp be soldered to the tuner side of the chassis to hold the a-c leads in place.

If additional width is required in early code chassis, do not replace the horizontal deflection transformer, but replace the 6BG6 pulse amplifier tube.

Andrea CVK19 Normandy, Ch. VK-19

The following changes have been made in Chassis CVK19: Coil L1, that was connected to the junction of C2 and the antenna terminal board, is now connected from the junction of the antenna terminal board (the lug going to the shield) and the shield. The value of resistor R1, that was connected from ground to pin 7 of the 6J6 V1, has been changed from 220 ohms (GRC-218) to 68 ohms (GRC-214). R1 is no longer connected to pin 7 but to the junction of L2 and C3 (L2 is connected to pin 7). In early chassis, R2, 100 ohms (GRC-216), was connected from the junction of pins 5 and 6 of V1 to ground. In later chassis R2 has been removed from this position and pins 5 and 6 are grounded. The value of R2 has been changed to 10 ohms, $\pm 5\%$ (GRC-253), and R2 now goes from pin 1 to pin 2 of V1. Capacitor C4, that was also connected from the junction of pins 5 and 6 to ground, has been removed from the circuit. The value of resistor R3, that is connected from the junction of pin 1 of V1, R2 and C6 to the junction of C5, C16 and R101, has been changed from 10,000 ohms (GRC-263) to 6800 ohms, 2 watts (GRC-257). Resistor R4 has been relocated and now goes from the junction of C5, C16 and R101 to R3, and the value has been changed from 12,000 ohms to 3300 ohms, 1 watt. R4 formerly went from the junction of C6, C7 and L5 to ground. Resistor R5, which in early models went from the junction of C9, C10 and L8 to ground, is now located from the junction of C6, C7 and L5. No change was made in its value. The resistor in late models going from the junction of C9, C10 and L8 to ground is now designated R8, and its value is 12,000 ohms (GRC-272).

V3, the 6AG5 modulator, has been changed to a 6AK5. No wiring changes have been made. The 100,000-ohm resistor that goes from pin 1 of V3 to R65, and was designated R8, is now designated R9, with no change in value. Pin 7 of V3 is grounded. In the early chassis, a resistor designated R9, 47 ohms (GRC-211), went from pin 2 of V3 to ground. In later sets this resistor has been removed (the reference number 9 was given

to another resistor as mentioned previously) and pin 2 is now grounded. In early sets capacitor C24 went from pin 6 of V5, the 6AG5 2nd video i-f, to pin 2 of the same tube. In later sets C24 is no longer connected to pin 2 but goes directly to ground. Capacitor C133, 0.005 μf (HCC-1926), has been added from ground and the shield of T4 to the junction of R24 (22,000 ohms) and R23 (47,000 ohms). The value of resistor R26, which is connected in parallel with C32, has been changed from 100 ohms (GRC-216) to 560 ohms (GRC-250). The value of R40, connected from pin 7 of V11 to ground, has been changed from 220,000 ohms (GRC-270) to 330,000 ohms (GRC-301).

The value of R7, connected from C14 to pin 1 of V2, the 6J6 oscillator, has been changed from 10,000 ohms (GRC-267) to 22,000 ohms, 2 watts (GRC-238). The value of C12, connected from pin 6 of V2 to the junction of C11, L10 and L19, has been changed from 5.5 to 3.5 μf . The value of C46, going to pin 1 of V12A, has been changed from 0.1 to 300 μf . The 3300-ohm resistor R64, connected from the junction of C56 and ground to contrast control R63, has been deleted from the circuit, and R63 is now connected directly to ground. The 100,000-ohm resistor that is connected from the center tap of R63 to C56, has been deleted from the circuit, and C56 is connected directly to the center tap of R63.

DuMont RA-105, RA-106

In certain areas where television signals are received on two adjacent channels (such as halfway between two cities having television stations) adjacent channel video interference may occur. When tuned to the lower frequency of two such adjacent channels, interference is experienced from the higher frequency channel. This interference is usually seen as horizontal sync running back and forth through the desired signal.

This may be corrected by the addition of a series-parallel resonant trap in the third video i-f amplifier as illustrated in Fig. 1. The latest RA-105 and RA-106 chassis include this trap.

The trap will be tuned to 20.4 Mc. This 20.4 Mc is obtained when the local oscillator beats with the video carrier of the channel above the desired channel. Consider a loca-

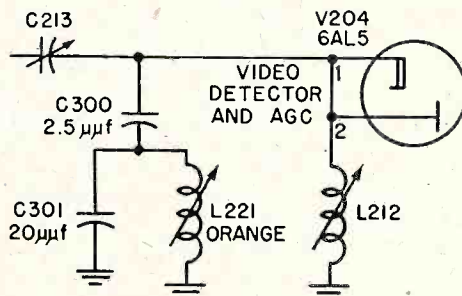


Fig. 1. Series-parallel resonant trap.

tion where both Channel 5 and Channel 6 can be received. With the set tuned to Channel 5, 76-82 Mc, the local oscillator is tuned to 77.25 Mc (video carrier of Channel 5) plus 26.4 Mc or 103.65 Mc. The local oscillator signal also beats with the video carrier

of Channel 6 (83.25 Mc) and produces a frequency equal to the difference between 103.65 Mc and 83.25 Mc which is 20.4 Mc.

The parts used are as follows:

Ref. No.	Part No.	Description
C300	03002720	Capacitor, ceramic, 2.5 μf , $\pm 0.5 \mu\text{f}$, 500 v
C301	03013800	Capacitor, ceramic, 20 μf , $\pm 5\%$, 500 v
L221	21003971	Variable inductance

Connect the 2.5- μf capacitor to the lug to which the end of the winding closest to the lug is soldered, leaving $\frac{1}{2}$ " of wire between the body of the capacitor and the lug. Connect a $2\frac{1}{2}$ " length of #18 bare-tinned copper wire to the other lug of the inductor. Connect the 20- μf capacitor across both of the lugs of the inductor, as shown in Fig. 2.

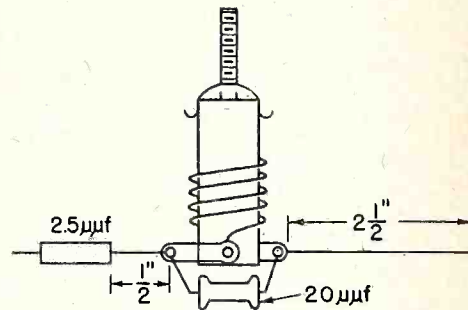


Fig. 2. Capacitor connection for series-parallel resonant trap.

Carefully enlarge the "keyhole," to 13/32 diameter, in the video i-f amplifier shield plate, using a Parker-Kalon metal punch XX. (See Fig. 3.) Use extreme caution when punching this hole so that alignment will not be disturbed. Insert the trap assembly in the hole so that the lugs are parallel to the main chassis and with the bare wire away from the main chassis. Solder the bare-tinned wire to the ground lug directly beneath the main chassis. Solder the free end of the 2.5- μf capacitor to the junction of L212, C213, and pins 1 and 2 of V204.

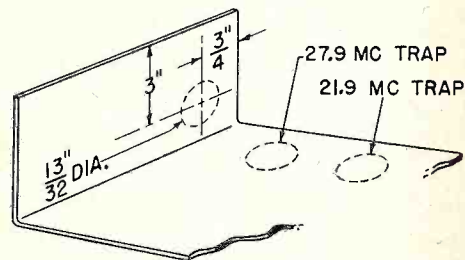


Fig. 3. Mechanical layout for series-parallel resonant trap.

The trap may be tuned, using a signal generator or by utilizing the interfering station.

1. Setting the trap by signal generator: Turn the contrast control to the extreme right. Connect a signal generator, 30% modulated at a carrier frequency of 20.4 Mc, to pin 1 (grid) of V201 and chassis. Connect an oscilloscope between pin 4 (grid) of V205 and ground. Adjust coil for minimum deflection of the oscilloscope.

2. Setting trap, using two adjacent stations: Tune receiver to sound of lower channel. Adjust contrast and watch for the interference. Tune trap from maximum inductance toward minimum inductance until the interference disappears. Rock trap tuning back and forth to be certain that the trap is correctly set.

Emerson 629D, 651D, 658B, Ch. 120124-B

The voltage and resistance measurements listed below are for chassis 120124-B stamped with triangle code 1A. Voltages may vary slightly from tables shown here if chassis is not coded as shown above. The conditions for taking voltage and resistance readings are listed below:

1. Antenna disconnected and antenna terminals shorted.

TABLE I
VOLTAGE READINGS

SYMBOL	TUBE PIN NO.								
	PIN 1	PIN 2	PIN 3	PIN 4	PIN 5	PIN 6	PIN 7	PIN 8	PIN 9
V1	-1	0	0	6.3 A.C.	96	96	0.3		
V2	-1	0	0	6.3 A.C.	96	96	0.3		
V3	0	0	0	6.3 A.C.	120	97	1.2		
V4	0	0	0	6.3 A.C.	130	97	1.2		
V5	0	-0.3	0	6.3 A.C.	0	0	-0.7		
V6	-170	-170	-170	-170	0	0	-170		
V7	-170	-170	-170	-170	-2.5	-130	-170		
V8	-0.8	-0.8	0	0	0	-1	0	-1.0	56
V9	N.C.	-170	38	48	-160	-170	-170	-160	
V10	-140	-170	-170	-170	-170	N.C.	N.C.	N.C.	-170
V11	100	-160	-165	-170	-170	110	-0.3	0	-170
V12	-210	-58	-170	-170	-67	-170	-170	-170	
V13	N.C.	-170	175	175	-160	170	-170	-130	
V14	N.C.	N.C.	400	N.C.	75	N.C.	390	390	
V15	HIGH VOLTAGE -- DO NOT MEASURE								
V16	N.C.	-175	-165	-185	-185	N.C.	-170	66	
V17	-180	3	-185	-260	6.3	-175	-175	-175	
V18	-92	-175	-175	-175	-175	-43	-190	-175	-175
V19	N.C.	200	N.C.	360 A.C.	N.C.	360 A.C.	N.C.	200	

2. Line voltage 117 volts.

3. All controls in position for normal picture.

4. All measurements taken with a vacuum tube voltmeter and ohmmeter.

5. All readings taken between points and chassis.

6. Resistance readings are given in ohms unless otherwise noted.

7. N.C. denotes no connection.

TABLE II
RESISTANCE READINGS

SYMBOL	PIN NUMBER								
	PIN 1	PIN 2	PIN 3	PIN 4	PIN 5	PIN 6	PIN 7	PIN 8	PIN 9
V1	1.2M	0	0	0	10K	10K	56		
V2	1.2M	0	0	0	10K	10K	56		
V3	0.8	0	0	0	13K	9K	180		
V4	0	0	0	0	9K	9K	170		
V5	28K	5.6K	0	0	0.3	0	95K		
V6	4.4K	4.4K	4.4K	4.4K	0.8	0	4.4K		
V7	60K	4K	4.4K	4.4K	1.2K	10K	4.4K		
V8	110K	110K	220K	0	0	1.2M	0	11M	0.5M
V9	N.C.	4K	10K	11K	0.5M	4.4K	4.4K	4.6K	
V10	23K	3.4M	4.4K	4.4K	4.4K	N.C.	N.C.	N.C.	4.4K
V11	15K	1M	5K	4.4K	4.4K	11K	6K	0	4.4K
V12	1M	1.6M	6.5K	70K	158K	6.5K	4.4K	4.4K	
V13	N.C.	4.4K	10K	10K	4M	240K	4.4K	7K	
V14	N.C.	N.C.	0.5M	N.C.	9K	N.C.	0.4M	0.4M	
V15	PLATE 0.4M, FILAMENT INFINITY								
V16	N.C.	4.4K	4.4K	0.8M	0.8M	N.C.	4.4K	20K	
V17	1.4M	70K	0.5M	0.5M	110K	4.4K	4.4K	4.4K	
V18	12K	0.5M	4.4K	4.4K	4.4K	3.5K	1.2M	6K	4.4K
V19	N.C.	9K	N.C.	4.4K	N.C.	4.4K	N.C.	9K	

The voltage readings for V20 are as follows: pin 1 is -170, pin 2 is -160, pin 10 is 180, pin 11 is -135, and pin 12 is -170 volts. The resistance readings for V20 are as follows: pin 1 is 4.4K, pin 2 is 1.2K, pin 10 is 9K, pin 11 is 55K, and pin 12 is 4.4K.

A low capacity probe must be used in order to faithfully reproduce high-frequency wave-shapes (15 kc and higher) and to prevent loading of the circuit under observation. Such a probe (see Fig. 1) can be readily con-


structed with parts on hand. Mount parts on a small sheet of bakelite, preferably inside a paper or mica tube. A shielded cable must be used because it prevents stray pickup. The length of this cable is very important since its capacitance is used in the design of the probe. The high capacitance of this cable (140 μf) and R-2 (100,000 ohms, $\pm 5\%$) minimizes the effect of different input impedances in various oscilloscopes. C_a is actually 4 feet of cable with 35 μf per foot capacitance. C-1, 15 μf , should have a tolerance of $\pm 10\%$. C-3 is 0.1 μf , 600 volts, and R1 is 1.2 megohms, $\pm 5\%$. With 10% tolerance in the cable and in C-1, the peak-to-peak voltages at 15 kc can be measured with 10% accuracy, provided the oscilloscope is calibrated on a 60-cycle sine wave. Due to the construction of the probe, the signal at the oscilloscope terminals is approximately 1/12 of its actual value. This means that a scope with at least 0.05 rms volts-per-inch vertical sensitivity is required. The average scope will meet these requirements. Since the scope is calibrated on a 60-cycle sine wave through the probe, the attenuation of the probe will not effect the accuracy of the peak-to-peak voltage readings. In trouble-shooting, it is of great value to know the peak-to-peak voltages of the various wave shapes. The oscilloscope can be easily calibrated to read these voltages. For information on calibrating the oscilloscope, see items listed below.

For taking wave shapes proceed as follows:

1. Observe the signal under test on the oscilloscope and set the gain control so that the whole signal is well within the screen limits.

2. Observe different 60-cycle voltages (12v, 25v, 117v, 350v a.c., etc.) on the oscilloscope with the same gain setting as before until one is found that is of the same peak-to-peak value, or less than the formerly observed signal. By measuring the 60-cycle voltage with a common a-c meter, and then comparing the two signals on the oscilloscope, a good estimation can be made as to the peak-to-peak voltage of the signal.

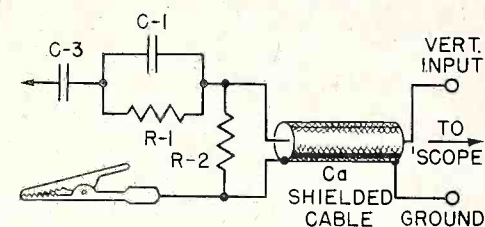3. An a-c voltmeter is calibrated to read the rms value of one-half a sine wave and not



Probe used with Emerson Ch. 120124-B.


the peak value. To convert from an rms value to a peak value, use the correction factor 1.4. The peak-to-peak value will therefore have a correction factor of 1.4×2 , or 2.8.

4. With a squared celluloid face mask on the screen, it is very easy to obtain accurate measurements.

For example: Take the 6.3-volt filament voltage, set the vertical gain control on the oscilloscope so that the wave covers 17.6 (6.3×2.8) boxes vertically from peak to peak. If the gain control is not moved, the oscilloscope will read 1 volt peak-to-peak per box on any signal. For a very weak signal, the calibration on a 6.3-volt a-c wave can be made with the vertical distance from peak to peak to 176 boxes instead of 17.6 boxes. The oscilloscope will then read 0.1 volt peak-to-peak per box instead of 1 volt peak-to-peak per box. If a stronger signal is encountered, the 117v a-c line can be used. The peak-to-peak value of this voltage is $117v \times 2.8 = 328$ volts.

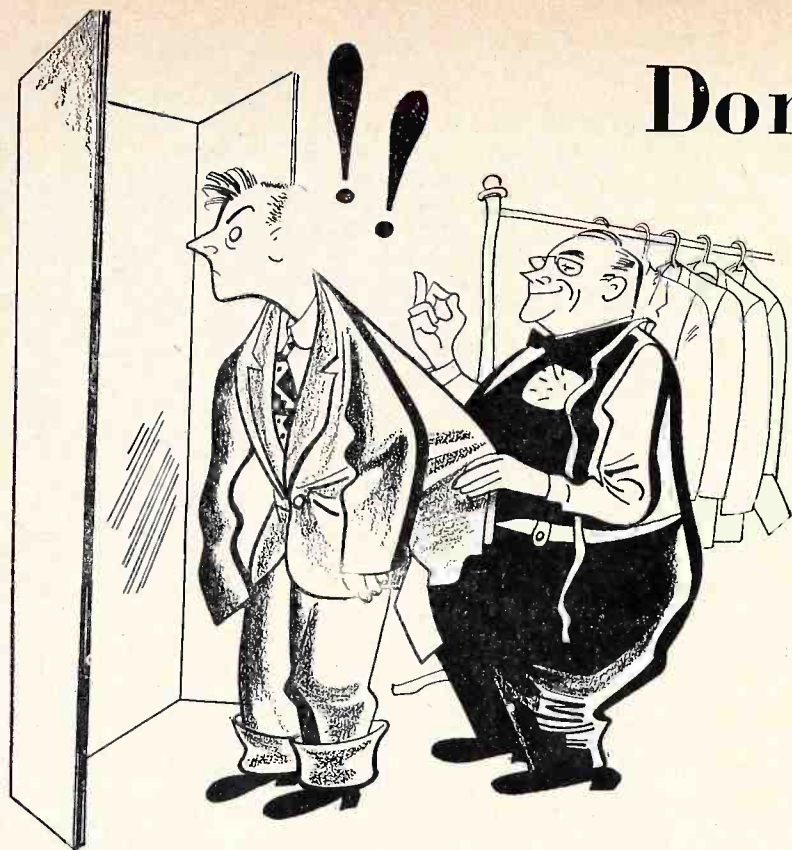G. E. 818

The following replacement part has been added to the Parts List: RDE-055, Overlay, metal overlay for picture tube masking.



Don't take chances with misfits!

In a field survey of servicemen on the subject of desirable volume control features, by far the most comments concerned easy adaptability and installation. If you want a control that is tailored for the job... and one that will deliver thousands of hours of smooth, quiet performance...

Make Sure! Make it Mallory!

When you use the Mallory Midgetrol* you are using a control designed to make your job easier and at the same time give your customer outstanding performance. Here is the unbeatable combination of Midgetrol features:


First, you get a permanently fixed, tubular brass shaft that can be adapted for split-knurl or flatted type knobs in a few seconds by inserting one of the steel shaft ends supplied in every package. This means utmost convenience without sacrificing the stability

of permanent, two-point shaft suspension.

Second, you get the convenience of AC switch design that permits secure attachment, without removing the control housing. Positive indexing assures proper position.

Third, you get exceptionally accurate resistance values and taper curves.

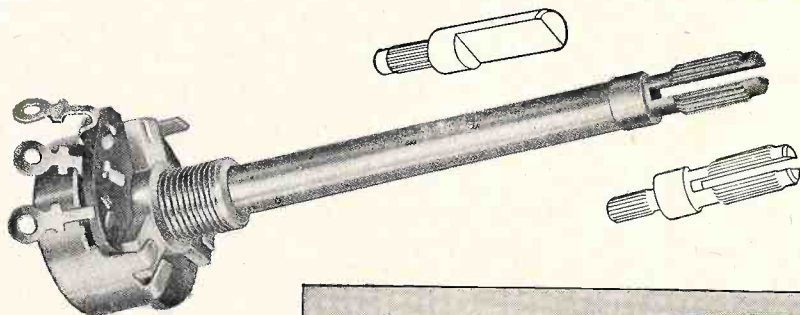Fourth, you can be sure of years of quiet, satisfactory service life through extremes of humidity and temperature.



Make it Mallory and make sure! Ask your distributor to show you the time-proved Mallory Midgetrol with the new features that make installation faster and simpler than ever.

In addition to single controls, dual concentric Mallory Midgetrols can be made up easily by combining factory-assembled front and rear sections of desired resistance values. Ask your Mallory Distributor for details!

P. R. MALLORY CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

*Reg. U.S. Pat. Off.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

JUNE, 1951

No. 8

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor

Worth 4-8340
Worth 4-8341



Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.

CURTAIN TIME

This is a hurried editorial. We are in the midst of reviewing the TV service situation in different sections of the country and hoped that it would be ready for this issue of SUCCESSFUL SERVICING. One condition bothers us greatly. It is the practice of some TV servicemen to charge for parts replacements which they *do not make*. Regardless of what the circumstances may be, this practice is inexcusable. It is downright larceny and it must stop if TV servicing is to survive.

There are no situations which warrant such malpractice! Unwillingness on the part of the public to pay a rightful price for good TV service does not warrant out-and-out theft. Numerous problems surround the relationship between the public and the servicing industry. They make the life of the service technician very difficult. The public is nontechnical and does not appreciate a fair and just price. This limits the earning capabilities of the honest servicemen. However, it is no excuse for outright stealing. Charging for replacements which are not made is just that, and the serviceman who does it is subject to arrest.

Some servicemen—fortunately only a relatively few by comparison—feel that any means to an end is justified. These same groups would be the first to yell to high heaven if a jobber charged for a dozen tubes and delivered only ten, or if the garage mechanic charged for new brake linings and did not install them.

Joe Blow, the serviceman who charges for a horizontal output transformer replacement which he does not make must be put out of the TV servicing business. He doesn't belong in society any more than the pickpocket who takes money out of your pocket.

On the other hand, the fact that dishonest people operate in the TV and radio service business should not indict the entire industry. There are more honest servicemen than dishonest servicemen. It is unfair for a newspaper to publish sensational copy by exposing the TV gyp without also devoting an equal amount of space to the honest operators in the area. It may not be equally lurid copy, but if newspapers are interested in the welfare of Mr. and Mrs. John Q. Public, it is their duty to advise TV owners where to go and the kind of organization to patronize in order that they may obtain the most for their money. We're not naive about this. Rackets deserve to be exposed—but editors should not hang everybody indiscriminately. Give the honest man a break. Make him known to the public. If an honest TV service association exists in the community, call it to the attention of the public. Give them a little publicity. They deserve it. Help them grow and they will overwhelm the racketeer—they'll put the gyp out of business by honest effort.

More next month.

JOHN F. RIDER

Olympic 752, 752U, 753, 753U, 755, 755U, 764, 764U, 766, 766U, 767, 769

If erratic horizontal hold, distortion, or picture tearing in strong signal areas occur, remove resistor R26, the 330,000-ohm $\frac{1}{2}$ -watt resistor located on peaking coil terminal strip adjacent to V11. Removal of this resistor provides higher agc voltage for the picture i-f tubes. Weak or gassy picture i-f tubes (V8, V9, or V10) will cause similar trouble.

If the picture is dark or shaded on the left side of the screen, change the value of R57 from 100,000 ohms to 47,000 ohms, $\frac{1}{2}$ watt. This resistor is located between 2 lugs on the horizontal linearity control L18. Make certain that the red lead to pin 10 on the kinescope socket is free and clear of the other leads to the socket.

The following change applies only to Models 752U, 753U, 755U, 764U, and 769, schematic drawing #DG-2346-2. If there is poor vertical linearity, that is stretching of the picture in the center and compression of the top of the picture, the following changes should be made:


1. C47 (4 μ f/450 v electrolytic) connected to the red lead of the vertical output transformer should be changed to a 20- μ f, 450-v, electrolytic capacitor. If 20 μ f is not available, use a 50- μ f electrolytic.
2. R55 (3300 ohms, 2 w) connected to the red lead of the vertical output transformer should be changed to 1000 ohms, 1 watt, $\pm 20\%$.
3. R54 (3300 ohms) and C46 (0.05 μ f, 600 v) peaking network. Disconnect ground side of the network and connect pin 6 of the 6SN7 (V14).
4. Check the 6SN7 (V15).

It is important that if one of the four changes mentioned above is made, all changes must be made. These changes are effective on chassis with serial numbers R584500 or S612800 and above.

General Electric 16C110, 16C111, 16C115, 16T1, 16T2

Capacitor C378, connected across the horizontal deflection coil D351, was changed from 56 μ f to 47 μ f. This change was made to reduce the possibility of vertical light bars appearing on the left side of the raster. On the Parts List, remove Stock RCU-297 and add Stock RCN-037, capacitor, 47 μ f, 1500 v, mica.

SAVE YOUR TIME AND TEMPER

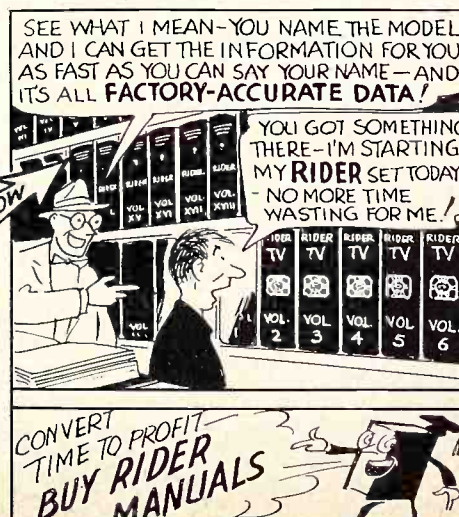

CONVERT
TIME TO PROFIT
BUY RIDER
MANUALS

Another Rider EXCLUSIVE!

VACUUM-TUBE VOLTMETERS

Second Edition, 1951

BY JOHN F. RIDER

ALL THE FACTS on all types of vacuum-tube voltmeters are at your finger tips. Learn about their design, construction, calibration, testing, applications, and maintenance. Know which type to select for your special needs; more than 40 commercial VTVM's with accompanying schematics and parts values, plus handy operating characteristics chart, help you do your selecting. This completely revised edition contains a valuable chapter on D-C and R-F probes. This is the only book that deals exclusively with VTVM's. **EXTRA! Chapter-end review questions.**

CONTENTS: 1. Fundamentals of Vacuum-Tube Voltmeters; 2. Diode Vacuum-Tube Voltmeters; 3. Triode Vacuum-Tube Voltmeters; 4. Rectifier-Amplifier Vacuum-Tube Voltmeters; 5. Tuned Vacuum-Tube Voltmeters; 6. Amplifier-Rectifier Vacuum-Tube Voltmeters; 7. Slide-Back Vacuum-Tube Voltmeters; 8. Vacuum-Tube Voltmeters for D-C Voltage, Current, and Resistance Measurements; 9. Probes for D-C and R-F; 10. Design and Construction of Vacuum-Tube Voltmeters; 11. Calibration and Testing of Vacuum-Tube Voltmeters; 12. Applications of Vacuum-Tube Voltmeters; 13. Commercial Vacuum-Tube Voltmeters; 14. Maintenance of Vacuum-Tube Voltmeters. Bibliography. Index. 422 pp. 215 illus. 5 1/2 x 8 1/2" \$4.50

Have You Seen These Recent Rider Books?

ENCYCLOPEDIA ON CATHODE-RAY OSCILLO- SCOPES & THEIR USES

by Rider & Usan

992 pp. 3,000 illus. Easy to read
Half a million words 8 1/2 x 11" \$9.00

FM TRANSMISSION & RECEPTION, Second Edition

by Rider & Usan

460 pp. Illustrated \$3.60

RECEIVING TUBE SUBSTI- TUTION GUIDE BOOK

by H. A. Middleton

224 pp. 8 1/2 x 11" \$2.40

JOHN F. RIDER PUBLISHER, Inc.
480 Canal St., N. Y. 13, N. Y.

Television Changes

Zenith Ch. 22H20Z

The 22H20Z chassis is identical in all respects to the 22H20, with the exception that a 12LP4B glass picture tube is used in place of the 12UP4B metal tube, resulting in the small differences in mounting outlined below.

Part No.	Description
	OMIT
19-207	Cathode-ray tube mtg. clip
80-838	Cathode-ray tube retaining spring
S-17409	Insulator strip & terminal
S-13428	Anode lead & eyelet assy.
12UP4B	Picture tube.
	ADD
19-177	Anode clip
22-4	0.004 μ f, ceramic disc (or 22-1706), 500 v
57-1692	Strap clamping plate (2 used)
80-841	Ground spring
82-27	Cathode-ray tube retaining strap
83-1879	Rubber strip (crt)
114-201	#8 x 5/16 hex hd. s.t. (2 used on each 57-1692)
S-17447	Anode clip & wire assy.
S-17773	Strip & gasket assy.
12LP4B	Picture tube.

Belmont C-1602 Series C, Ch. 16AX29

For the tuner replacement parts list of the continuous tuner used in Model C-1602 Series C, refer to the tuner parts list given with Chassis 12AX27. Only 16AP4 metal tubes are used in the C-1602 Series C receiver.

Trav-ler 14B50, 14C50, 16R60, 16R70

Model 16R60 is the same as 16R70. The alignment procedure and service information given for Models 16G50, 16G50A, 16R50, 16R50A, 16T50, and 16T50A also applies to Models 14B50, 14C50, 16R60, and 16R70.

Capehart-Farnsworth 335B, 335M, Ch. CX-33S, C-303

When installing a Model 335M television receiver the following revisions to the Installation and Set-Up Instructions for Chassis CX-33 must be taken into consideration.

The procedure for removal of the escutcheon is as stated for CX-33 except that Model 335M employs brass pressure clips to secure the wood mounting strip instead of screws. To remove these clips, insert a screwdriver beneath the head and pry out. Wrap a cloth around the screwdriver to prevent scratching the cabinet. To replace the clips, merely press in.

Model 335M does not employ the red shipping bracket mentioned to secure the focus coil. Instead, the focus coil is demounted from the crt and fastened to the rear of the cabinet chassis shelf for shipment. Upon installation the coil assembly will have to be properly mounted. To do this, first remove the ion trap from the neck of the crt and then remove the large bolt which secures the focus coil assembly to the cabinet. Slide the coil assembly over the neck of the crt (the proper direction of the coil is with the side of the coil with the four mounting ears facing toward the bell of the crt) and fasten it to the mounting bracket on the chassis using the hardware furnished. The lock washer fits next to the bolt head, then a flat washer goes between the lock washer and the coil bracket. On the underside of the mounting bracket, place the flat washer on first and then the remaining lock washer, followed by the wing nut. Slide the coil forward until it is approximately 3/8" from the deflection yoke and tighten the wing nut. Place the ion trap

magnet on the neck of the crt (in case of double magnet traps with the arrow pointing toward the bell of the crt) and connect the crt socket. Turn the receiver on and adjust the ion trap magnet until a raster is seen. If a raster is not obtained, adjust the shading and agc set controls. Upon obtaining a raster, adjust the magnet (by sliding back and forth and rotating about the neck of the crt) to obtain maximum brightness. With just the raster present (no picture), adjust the focus control for good focus and check to see if focus is good over entire tube; if it is not, adjust the focus coil assembly. To do this, loosen the wing nut which fastens the coil assembly to the mounting bracket and slide the coil back and forth until optimum focus is obtained, as evidenced by clear separation of the raster lines across the entire picture. The focus control must be readjusted each time the coil is moved. Readjust the ion trap magnet to insure maximum brightness.

Model 335M employs a focus coil assembly which does not include the adjustment handle. Therefore, to center the picture in the crt mask, loosen the wing screw at the left side of the focus coil assembly and also the wing nut which fastens the coil assembly to the mounting bracket. The coil can then be tilted in both the vertical and horizontal planes to provide horizontal and vertical centering. After the picture is properly centered, secure the coil assembly in place by tightening the wing screw and nut. After any adjustment of the focus coil, always readjust the ion trap magnet to insure maximum brightness and prevent damage to the crt.

The list of cabinet parts for Models 335B and 335M is given below:

Part No.	Description
850082A-1	Speaker assembly, 12" pm
850162A-1	Safety glass escutcheon
950118A-1	Picture tube mask
650345A-1	Balance knob
650345A-2	Shading knob
650342A-1	Channel knob
650344A-1	Sound knob.

Garod 14CT4, 16CT4, 16CT5, 19C6, 19C7, 1671, 1672, 1673, 1674, 1675, 1900, 1974, 1975, Series 97 and 98.


Model 14CT4 is a console with a mahogany finish and employs a 14" rectangular picture tube. Models 16CT4 and 16CT5 are console sets using 16" round tubes. Model 16CT4 has a mahogany finish, while Model 16CT5 has a bleached finish. Model 1900 is also a console with a mahogany finish, although it employs a 19" round tube. A total of 20 tubes including the picture tube is used in these receivers.

The service data for these models in the 97 and 98 Series are the same as the data for the 94 and 97 Series except for the differences and additions mentioned in the following paragraphs.

Under the section titled "Picture Tube Installation in 16" Receivers," add:


For receiver Models 1672 or 1673, remove the two screws which hold the front mask assembly. These pass through the two corner blocks on the inside of the cabinet at the top. When these screws are removed, the front panel may be lifted out. For receiver Models

(Continued on page 8)

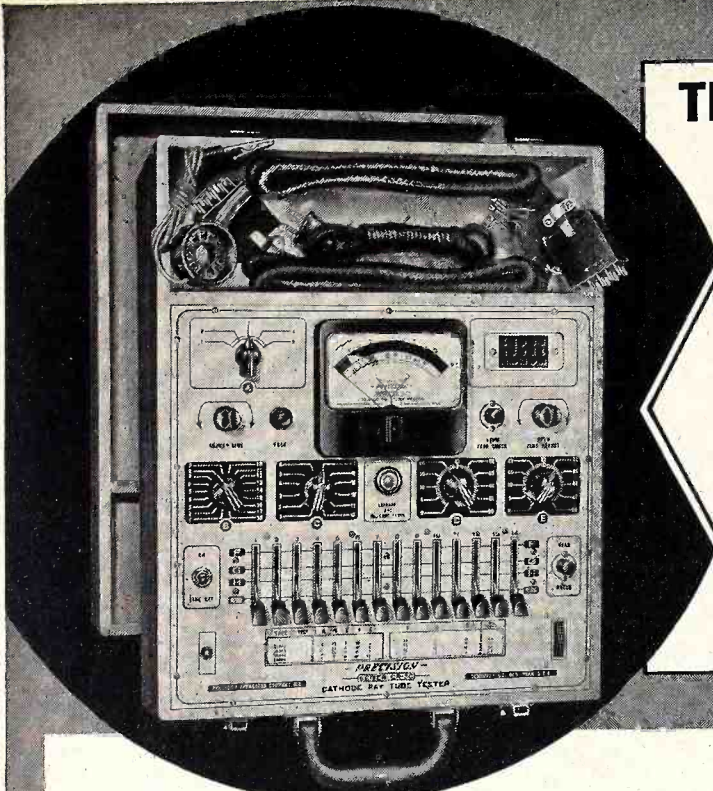

THE NEW PRECISION CR-30 CATHODE RAY TUBE TESTER

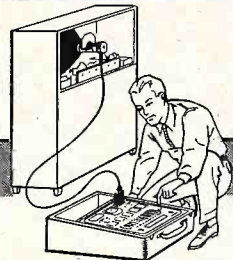TESTS ALL TV PICTURE TUBES
(MAGNETIC AND ELECTROSTATIC)
'SCOPE TUBES AND INDUSTRIAL CR TYPES
for True Beam Current (Proportionate Picture Brightness)
Tests ALL CR Tube Elements—Not Just a Limited Few



IN FIELD OR SHOP
Tests CR Picture Tubes
Without Removal from
TV Set or Carton!

The new Precision CR-30 fills an obvious gap in the test equipment facilities employed by TV service and installation technicians.

Because of the absence of a reliable cathode ray tube tester, up to 50% of so-called "rejected tubes" are found to be fully serviceable and should rightfully never have been "pulled out."

Proven product of extended development, the CR-30 has been

specifically engineered to answer the question, "Is It the TV Set or is it the Picture Tube?"


The Precision CR-30, a complete and self-contained Electronic Instrument, incorporates a TRUE BEAM CURRENT Test Circuit. The CR-30 checks overall electron-gun performance for proportionate picture brightness as well as additional direct testing facilities for accelerating anodes and deflection plate elements.

The Precision CR-30 should not be confused with mere adapters connecting to ordinary receiving tube testers which were never designed to meet the very specialized needs of CR tube checking. Similarly, it is not to be confused with neon-lamp units or similar devices of limited technical merit and which do not check all CR tubes or all tube elements.

GENERAL AND TECHNICAL SPECIFICATIONS

- ★ Tests All Modern Cathode Ray Tubes:—Magnetic and Electrostatic, 'Scope Tubes and Industrial Types.
- ★ Tests All CR Tube Elements:—Not just a limited few.
- ★ Absolute Free-Point 14 Lever Element Selection System, independent of multiple base pin and floating element terminations, for Short-Check, Leakage Testing and Quality Tests. Affords maximum anti-obsolescence insurance.
- ★ True Beam Current Test Circuit checks all CR Tubes with Electron-gun in operation. It is the Electron Beam (and NOT total cathode emission) which traces the pictures or pattern on the face of the CR tube.

Total cathode emission can be very high and yet Beam Current (and picture brightness) unacceptably low. The CR-30 will reject such tubes because it is a true Beam Current tester. Conversely, total cathode emission can be low and yet Beam Current (and picture brightness) perfectly acceptable. The CR-30 will properly pass such tubes because it is a true Beam Current tester. The significance of the above rests in the fact that Beam Current (and picture brightness) is primarily associated with the condition of the center of the cathode surface and not the overall cathode area. (See illustration below)

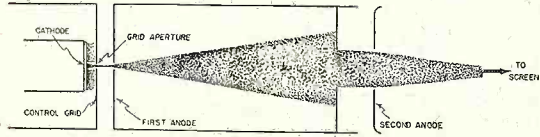

- ★ Voltage Regulated, Bridge Type VTVM provides the heart of the super-sensitive tube quality test circuit. Such high sensitivity is also required for positive check of very low current anodes and deflection plates.
- ★ Micro-Line Voltage Adjustment
Meter-monitored at filament supply.
- ★ Accuracy of test circuits closely maintained by use of factory adjusted internal calibrating controls; plastic insulated, telephone type cabled wiring; highest quality, conservatively rated components.
- ★ Built In, High Speed, Roller Tube Chart.
- ★ Test Circuits Transformer Isolated from Power Line.
- ★ 4 1/2" Full Vision Meter with scale-plate especially designed for CR tube testing requirements.
- ★ Heavy Gauge Aluminum Panel etched and anodized.
- ★ PLUS many other "PRECISION" details and features.

SERIES CR-30—In hardwood, tapered portable case, with hinged removable cover. Extra-Wide Tool and Test Cable Compartment. Overall Dimensions 17 1/4 x 13 3/4 x 6 3/4". Complete with standard picture tube cable, universal CR Tube Test Cable and detailed Instruction Manual.

Shipping Weight:—22 lbs. Code: Daisy
NET PRICE:—\$99.75

See the new CR-30 on display at leading electronic equipment distributors. Place your orders now to assure earliest possible delivery.



PRECISION APPARATUS CO., INC.
92-27 Horace Harding Boulevard, Elmhurst 14, New York
Export Division: 458 Broadway, New York, U.S.A. Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

Please mention Successful Servicing when answering advertising.

Garod Series 97 and 98 (Continued from page 6)

1671, 1674, or 1675, remove the four decorative screws which hold the front panel and mask assembly. These pass through the four corners of the picture frame. Carefully lift out the front panel and mask assembly. For Model 1671, loosen the two screws which fasten the metal picture-tube retaining band

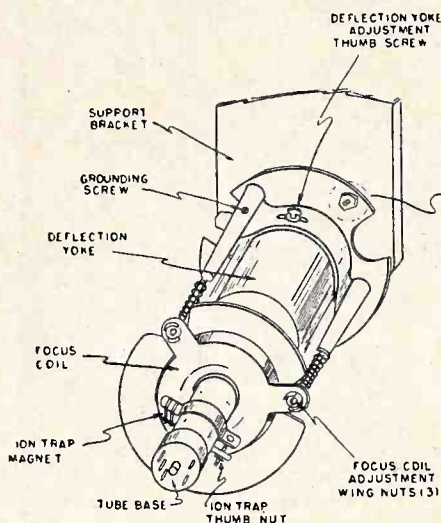



Fig. 1. Deflection yoke and focus coil assembly.

sufficiently so that the picture tube may be slipped through the opening. The high-voltage connector should be located on the right side of the chassis, as viewed from the front. Secure the metal band over the top of the tube by tightening the two screws alternately

and evenly, so that the rectangular picture tube is not forced to rotate or twist in its mounting.

The picture tube installation in 19" receivers is as follows:

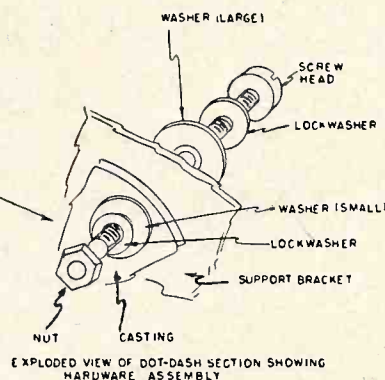The bulblike glass separation between the neck of the picture tube and its metal cone is treated with an anti-corona coating to reduce high-voltage leakage under humid at-



mospheric conditions. Avoid touching this treated area since perspiration may reduce its effectiveness. If handled accidentally, wash with water or mild soap and water. Remove all traces of soap. Use no chemical solvents or abrasives for cleaning.

1. Remove the slotted head P.K. screws retaining the back and release with the interlocked line cord.

2. Remove the bag containing the beam bender, the hardware for deflection and focus coil assembly, and the front plug buttons, if used.

3. Remove the deflection and focus coil assembly which is fastened to a shelf for shipping purposes. Remove retaining wires that are wrapped around focus coil adjustment screws.

4. Carefully slide the deflection yoke and focus coil assembly over the neck of the picture tube, so that the deflection yoke adjustment thumb screw faces the top of the cabinet.

5. Assemble the deflection yoke and focus coil assembly to the support bracket using the hardware provided. See Fig. 1 for proper hardware assembly and mounting procedure.

6. Remove the 6-32 grounding screw from the yoke frame (see Fig. 1 for location). Attach the ground lug on the brown wire coming from the chassis, and replace the screw.

7. Slide the beam bender over the neck of the picture tube.

8. Connect the picture tube socket to the tube base.

9. Connect the male octal plug from the deflection yoke and focus coil assembly to the female octal socket from the chassis.

The rear panel adjustments that are illustrated for Models 1672, 1673, 1674, 1675, 19C6, 19C7, 1974, and 1975 apply to the other models mentioned in this article. The location of the front panel controls are shown for Models 1974 and 1975 in Fig. 2, and for the rest of the models in Fig. 3.

The circuit description for these models is the same as that for the 94 Series, except that

in the section titled "Vertical Deflection Circuit (Block H)," the generated sawtooth voltage is amplified by the 6K6 output tube (V20), rather than the "other half of the 6SN7 duo-triode (V14)."

The Alignment Procedure, Video I-F and Sound Alignment, and the R-F and Oscillator Alignment for the 97 and 98 Series is the same as that found for the 94 Series.

The Voltage Chart for all models except 14CT4, 1674, and 1900, is the same as that shown on page 5-19. The voltage readings for Model 1900 are the same as those shown on page 5-19 except for the following changes. Picture tube: pin 2 is 2, pin 10 is 230 v, pin 11 is 10 v. Audio output (6V6): pin 1 is N.C. Video amplifier (6AC7): pins 3 and 5 are 0.2 v, pin 8 is 115 v. Vertical sweep oscillator (6C4): no reading for pin 1, pin 5 is 100 v.

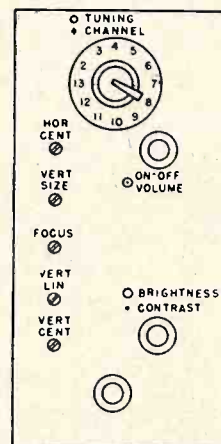


Fig. 2. Front panel layout for Models 1974 and 1975.

Horizontal sweep oscillator (6SN7): no reading for pin 8. Horizontal sweep output (6BQ6-GT): no reading for pin 1, pins 3 and 4 are 155 v, pins 5 and 6 are -26 v, pin 8 is 7 v. High-voltage rectifier (1B3): pins 2, 6 and 7 are 11.5 kv. Horizontal damper (6W4): pin 2 is N.C., pins 5 and 6 are 210 v. Power rectifier (5U4G): pins 2 and 8 are 380 v, pins 4 and 6 are 365 vac. Vertical output (6K6): pin 1 is 0 v. 6AG5's only are used as r-f amplifier, and 2nd and 3rd video i.f.


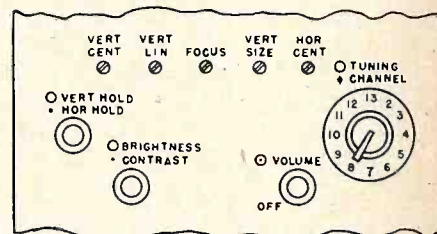


Fig. 3. Front panel layout for Series 97 and 98.

The voltage readings for Models 14CT4 and 1674 are the same as those shown on page 5-19 except for the following changes. Picture tube: pin 10 is 245 v. Oscillator-converter (6J6) pin 1 is -0.7 v, pin 2 is 0 v. Ratio detector-audio amplifier (6T8): pin 6 is -0.5 v, pin 8 is -1.5 v. Ratio detector driver (6AU6): pin 1 is 8 v, pin 2 is 8.5 v, pin 5 is 220 v, pin 6 is 105 v, pin 7 is 9 v. D-c rest.-clip.-sep.-amp. (12AU7): pins 2 and 6 are 160 v, pin 3 is 162 v. Horizontal sweep oscillator (6SN7): pins 3 and 6 are 12.5 v, pin 4 is -4.7 v, pin 5 is 100 v. Horizontal sweep output (6BQ6-GT): pins 3 and 4 are 210 v, pin 5 is 48 v, pin 8 is 72 v. High-voltage rectifier (1B3): pins 2, 6 and 7 are 10.1 kv. Horizontal damper (6W4): pin 2 is -85 v, pins 5 and 6 are 225 v.

(Continued on page 10)

ADEQUATE PROTECTION

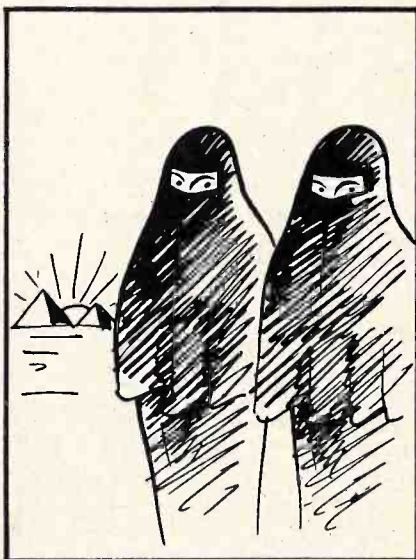

Ersin MULTICORE — the original 3-core solder and the only solder made with non-corrosive, extra-active Ersin Flux — protects your reputation! Melts rapidly! Wets metals faster! Prevents "dry" joints that cause customer complaints. Works rapidly and reliably on difficult metals and on oxidized parts! Write for FREE SAMPLE today! Multicore Sales Corp., Dep't S., 164 Duane St., New York 13, N. Y.

Please mention Successful Servicing when answering advertising.

**REACH OUT FARTHER...
AND BRING 'EM IN STRONGER!**



JFD

"Long Ranger"

YAGI TV ANTENNA ARRAYS

with High Impedance
Driven Element for
Direct Match to 300
Ohm Lead-in.

Five-element beam, custom-cut to exact
wavelength of channel, delivers more
powerful forward gain with high front-
to-back ratio rejecting co-channel inter-
ference.

FAST and EASY installation

JFD YAGI antennas are **completely pre-assembled** at the factory. Just swing the
"Quik-Rig" elements into position and
tighten the wing nuts.

These all-aluminum JFD "Long Ranger" YAGI
antennas are something to shout about... be-
cause even the really **remote** stations are
now being pulled in with satisfactory viewing
results. And JFD advanced design plus sturdy
construction assure durability and long-
lasting, trouble-free performance. Let these
superior JFD YAGI installations help you
e-x-p-a-n-d your television market.



SWING ELEMENTS INTO POSITION



5-ELEMENT YAGIS

LOW BAND

No. 5Y2 (Channel 2)
No. 5Y3 (Channel 3)
No. 5Y4 (Channel 4)
No. 5Y5 (Channel 5)
No. 5Y6 (Channel 6)

HIGH BAND

No. 5Y7 (Channel 7)
No. 5Y8 (Channel 8)
No. 5Y9 (Channel 9)
No. 5Y10 (Channel 10)
No. 5Y11 (Channel 11)
No. 5Y12 (Channel 12)
No. 5Y13 (Channel 13)

"Long Ranger" YAGI antennas for all of the high
band channels are also available in stacked array.
Jumper bars for stacking of low band "YAGIS" are
also available.



MANUFACTURING CO., Inc.

6119F 16th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories


Write for **FREE Technical Data Sheet No. 59**

Garrod Series 97 and 98

(Continued from page 8)

Model 1671 uses a single 5" p-m speaker. Models 16CT4 and 16CT5 use a single 10" p-m speaker. The schematic for Series 97 and 98 is the same as that which appears on page 5-20 except for the following changes in the ratio detector driver stage. A 100-ohm resistor, R10, is inserted from the junction of R28 and C49, to pin 1 of V6, the 6AU6 ratio detector driver. Capacitor C55, the 0.02 μ f capacitor connected from pin C of ratio detector transformer T6 to ground, has been relocated and now goes from pin C to pin 7 of V6, the ratio detector driver. The value of C55 has been changed to 5000 μ f. A 5000- μ f capacitor C32 has been added from pin 7 to pin 2 of V6. An 82-ohm resistor R26 has been inserted from pin 7 to R27, the 1,000-ohm grid resistor.

The schematic for Models 14CT4 and 1674 is the same as that described above for Series 97 and 98 except for a change in the sweep circuit. Resistor R118, 390,000 ohms, now goes from the junction of R83, 100,000 ohms, and C79, 13 μ f, 2 kv, to the junction of R84 (the 250-ohm resistor going from ground to pin 8 of the horizontal sweep output tube V16) and R80 (mentioned below), instead of from R83 and C79 to ground. Resistor R80, that was connected from ground to capacitor C92 (connected to pin 8 of V16), was relocated and now goes from ground to the junction of R18 and R84 to R85 (mentioned below), and the value of R80 has been changed from 47 ohms to 470 ohms, 7 watts. Resistor R85, the 30,000-ohm resistor that was connected in

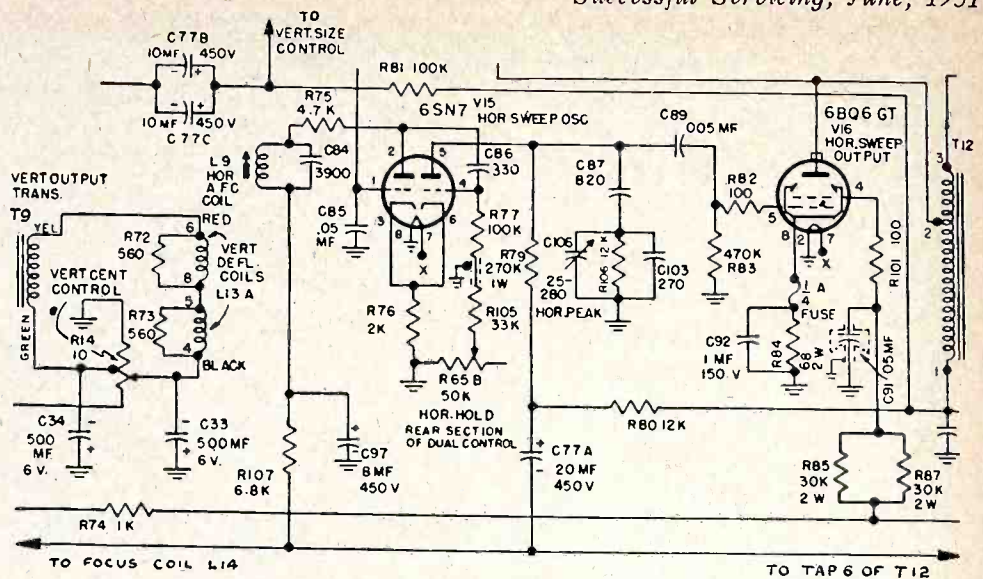

WE GUARANTEE that RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is... what it can DO... and HOW to use it properly!



ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Usan

The **FIRST and ONLY** book that so fully and clearly describes the 'scope... its construction... its capabilities... its applications in communications, engineering, research... with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you... **WHAT** each type can do... **HOW** to use it... and **WHICH** is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians—all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages... 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home... municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY** and **IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth Bound.....And only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Usan



The entire system of frequency modulation is explained thoroughly... all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

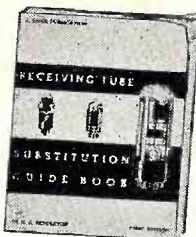

For **AM-FM-TV Receivers and Allied Equipment!**

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

EXTRA! In addition to tube information... this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc. ...

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New... Revised... Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman



All the **QUESTIONS** and **ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH**... a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer.

ELEMENT VIII: SHIP RADAR TECHNIQUES, is now available in a separately-bound booklet. Uses the same question-answer-discussion treatment as the text.

32 pages... heavy, durable cover.....78¢
766 Pages, Hundreds of Explanatory Diagrams..\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc. ... in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed, how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth bound.....Only \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.

Television Changes

Industrial 248, 348, Ch. IT-35R,
Ch. IT-48R

The IT-48R sweep chassis is used in Models 248 (16") and 348 (19"). The general description of the circuit is as follows:

Video
The video signal from the control unit is brought into the picture unit chassis through pins 1 and 8 of the octal socket J1. R1 serves to terminate the interconnecting cable at its characteristic impedance of 75 ohms. R2 (omitted in home receivers) is the auxiliary contrast control, which should be adjusted at the time of installation to equalize picture contrast between multiple viewer installations. V1 and V2, a 6AG5-6AQ5 combination, form a two-stage direct-coupled video am-

plifier, with a bandwidth of approximately 4.5 Mc, and a gain of about 100, with an output of 75 volts peak-to-peak. The amplified video signal is applied to the grid of the picture tube V4. A portion of the video signal is also applied to the d-c restorer and sync clipper (one-half of V3, a 12AU7) which separates the sync pulses from the composite signal, and which derives, from the composite video, a d-c potential which provides a constant black-level reference for the video signal.

Sync

The clipped sync pulses from the sync separator are fed to the grid of the sync amplifier (the other half of V3) which amplifies and further clips the sync, and also serves as a phase inverter to provide positive and negative sync pulses to the horizontal phase detector V5. A portion of the sync signal is picked off the cathode of the sync amplifier

and integrated to provide sync pulses for the vertical. These vertical sync pulses are further amplified by the first half of V11 (12AU7) before being applied to the vertical BTO.

Horizontal

The horizontal oscillator (V6) is a 12AU7 in a Potter type circuit, which is essentially a cathode-coupled multivibrator with a ringing coil L4 in one plate circuit. The other plate circuit has appropriate R-C networks to generate a peaked-sawtooth waveform suitable to drive the 6BG6 horizontal output amplifier, V7, that is coupled to the yoke through the output transformer T1. The 6W4, V10, serves to damp out any ringing or undesired transients in the yoke circuits. High voltage is obtained by rectifying the boosted primary pulse in a voltage doubler circuit using two 1B3's (V8 and V9) which provide about 14 kv of accelerating potential for the picture tube. A portion of the output pulse is picked off the secondary of T1, shaped, and fed back to the 6AL5 phase detector, V5, where it is compared with the incoming sync pulses, generating a proportional d-c potential that is applied to the grid of the horizontal oscillator, V6, to synchronize its frequency with that of the transmitter.

Vertical

The integrated and amplified vertical sync pulse is applied to the grid of the vertical BTO, the other half of V11, and locks it in sync with the transmitter. The plate supply circuit of the BTO has an integrating network which derives a saw from the BTO pulse to drive the 12AU7 vertical output amplifier V12, coupled to the vertical windings of the yoke through the vertical output transformer T3.

Audio Amplifier

The audio amplifier is a two-stage push-pull resistance-coupled amplifier, using a 12AU7 as voltage amplifier and phase inverter (V13) and two 6AQ5's (V14 and V15) as push-pull output amplifiers. V14 and V15 are also used as a voltage divider and regulator to provide a 200-volt supply for the sync clipper, amplifier, and horizontal oscillator circuits.

Power Supply

The power supply is relay controlled by the control unit, and provides 400 volts d.c. at 200 ma, and also the necessary heater power to operate the chassis. It is fused at 5 amps, and interlocked with the speaker plug to protect the input filter capacitor from excessive surge voltages.

The adjustments are as follows:

Auxiliary Contrast Control (not provided in Models 248 or 348).


This control, located on the chassis apron next to the octal input socket, should be left at maximum except when the installation includes more than one viewer on a single control unit. If two or more viewers are used with a single control, one of the viewers may require slightly reduced contrast to equalize the pictures to their individual locations. For instance, a viewer in a darker location may need less contrast for a perfect picture than one in a location with high ambient light on the tube face.

Brightness Control

This control, located on the chassis apron next to the contrast control mounting hole, serves to adjust the background or average picture brightness. This control should be



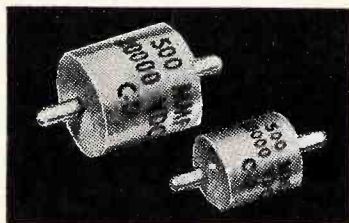The famous ceramic body made by C-D with an original engineering job inside and out! More dependable, longer lasting than any previous TV high-voltage ceramic capacitor! Can be used at full rated voltage, because it's conservatively rated for DC flash test up to 2x rated working voltage!



Send for Bulletin 2-614
Department R61
Cornell-Dubilier Electric Corp.
South Plainfield, N. J.



CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
CAPACITORS

Plants in South Plainfield, N. J.; New Bedford, Worcester, and Cambridge, Mass.; Providence, R. I.; Indianapolis, Ind.; Fuquay Springs, N. C.; and subsidiary, The Radiart Corp., Cleveland, Ohio
Please mention Successful Servicing when answering advertising.

Successful Servicing, June, 1951

adjusted so that with no picture the raster just disappears, and it should be rechecked with the picture to make sure that the retrace lines do not appear on any station.

Vertical Size

Located on the chassis apron next to the brightness control, the vertical size control serves to adjust the vertical height of the picture. It should be used in conjunction with the vertical linearity to adjust the picture to fill the frame with good vertical linearity.

Vertical Hold

This control, situated next to the vertical size control on the chassis apron, serves to adjust the vertical oscillator frequency so that it may be locked into synchronization with the incoming video signal. The picture will remain locked-in over a considerable range of this control, however, the control should be set at the middle of the locked-in range.

Vertical Linearity

On the chassis apron next to the vertical hold control is the vertical linearity control, which varies the relationship of the size of the top half of the picture with respect to the bottom half. This control should be adjusted in conjunction with the vertical size control as outlined above.

Horizontal Hold

This control, located on the chassis apron next to the vertical linearity control, acts in conjunction with the horizontal frequency adjustment L4 to set the frequency of the horizontal oscillator to synchronization with the incoming video signal. It is interdependent with the horizontal drive control, so that it is necessary to readjust the hold if the drive is changed. The hold should be set so that the picture is locked in, and so that adjustment of the control will expand the picture both ways. If this cannot be done, or if there is a "pull" or curvature in the vertical wedges of the test pattern, the horizontal frequency control should be reset to correct this condition. Several interrelated changes of these two controls may be necessary to properly adjust the horizontal setting.

Horizontal Drive

This control varies the amount of sawtooth voltage applied to the grid of the horizontal output amplifier, and is located on the apron of the chassis next to the horizontal hold control. Its purpose is to set the horizontal width of the picture to fill the mask. As mentioned under horizontal hold, adjustment of this control usually necessitates resetting of the hold control.

Horizontal Positioning

The next control after the horizontal drive is the horizontal positioning control. This control moves the entire picture to the left or right so that it may be centered in the mask opening.

Vertical Positioning

This control, the next to last control on the chassis apron, serves to vertically center the picture in the mask area.

Focus

The focus control, the last control on the apron, controls the magnetic field of the focus coil, thereby focusing the electron beam of the picture onto the screen. It should be adjusted for the maximum over-all picture sharpness, especially at the center of the picture.

Video Amplifier Bias

This control is located on top of the chassis close to the octal input socket, and is provided to adjust the bias on the second video

amplifier V2 to the proper operating point. This control need be used only if V1 or V2 is replaced, in which case, it would be adjusted so that the grid-cathode potential of V2 is 6.0 volts measured between pins 1 and 2 of its socket.

Cathode-ray-tube Drive

This control provides adjustment of the cutoff potential of the picture tube. It should need adjustment only if the picture tube is replaced. With no picture and the Brightness control set so that the grid-cathode bias of the picture is 45 volts, it should be set so that the raster just disappears.

Horizontal Frequency (L4)

This is a screw adjustment located on top of the chassis between the 6BG6 horizontal output amplifier, V7, and the chassis apron. (For use see horizontal hold above.)

Horizontal Linearity

This adjustment provides a variation of the horizontal sweep linearity near the center of the picture. It should never need adjustment in the field.

General Electric 12C107, 12C108, 12C109, 12T3, 12T4

In the above receivers using a type 6AB4 tube as the 1st r-f amplifier, the Stock No. RLA-035 input transformer is no longer available. The Stock No. RLA-036 is a direct substitution for it and is now being furnished with these receivers.


On late production receivers, the value of resistor R379, which goes from V12B to pin 7 of V11, has been changed from 180,000 ohms to 270,000 ohms. On the Parts List, remove R379 from Stock No. URD-103, and add URD-107, 270,000 ohms, 1/2 w, carbon, R379.

ONE STANDARD - The best that can be made - For Initial Equipment and Replacement



TUNG-SOL

RADIO, TV TUBES, DIAL LAMPS

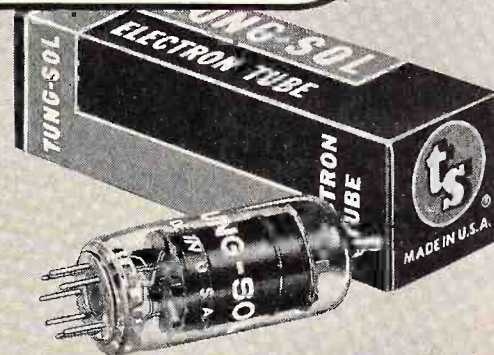

Optical comparator is used to check mica disc specifications to thousandth-inch accuracy.

TUNG-SOL LAMP WORKS INC., Newark 4, N. J.

Sales Offices: Atlanta • Chicago • Dallas • Denver • Detroit • Los Angeles • Newark

Please mention Successful Servicing when answering advertising.

LOUDSPEAKER MATCHING

(Continued from page 1)

Simultaneous Use of Several Taps—High-Impedance Lines

Assume that an installation requires very unequal distribution of power to several different groups of loudspeakers. To connect them through matching transformers in such a manner that their total load equals one of the high impedance taps available at the amplifier output may be impossible. To connect the low-powered loudspeakers directly across a tap on the output transformer is not usually possible, since the tap impedance required will be so low as not to be available. The simplest solution to this problem is to connect the various loads through the proper individual matching transformers to several taps on the output transformer so that power distribution is as desired and the amplifier is properly matched to the total loudspeaker distribution system.

A detailed example will clarify the above. The calculations required to design a p-a system for a church will be explained in detail. Figure 2 is a schematic of the loudspeaker distribution system.

The church uses a 75-watt amplifier having output tap impedances of 4, 8, 125, 250 and 500 ohms. Four 8-ohm, 15-watt loudspeakers are series-parallel connected to provide 60 watts to the belfry. One 8-ohm loudspeaker receiving 2 watts is used for the choir. Two 8-ohm loudspeakers receiving 4 watts each, are placed on the walls flanking the altar, facing the congregation. The power required is thus 70 watts, leaving 5 watts reserve power. An additional 8-ohm, 5-watt loudspeaker

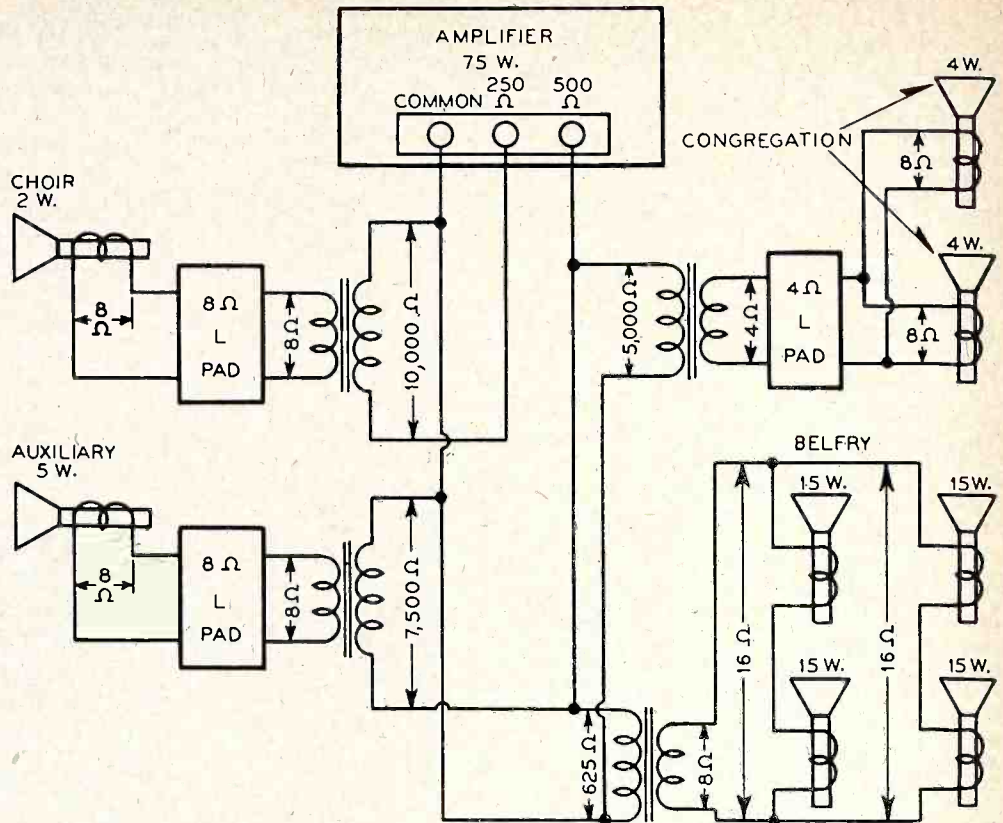


Fig. 2. Schematic representation of a church loudspeaker system. A 75-watt amplifier is used to feed all the loudspeakers.

located in the recreation room, for example, can take this 5 watts reserve power.

Since the belfry and congregation loudspeakers are at some distance from the am-

plifier, the loudspeaker lines feeding them will be run at high impedance and thus matching transformers are required. The choir and auxiliary loudspeakers must also use matching transformers because less than 1-ohm impedance would be necessary to get the required power if these loudspeakers were connected directly across part of the output transformer impedance. An impedance this low is not available, so these loudspeakers cannot be connected directly to the output transformer but must use matching transformers. The belfry and congregation loudspeakers use a 500-ohm line since they are some distance from the amplifier. To compute the values of the matching transformer primary impedances (the secondaries are 4 ohms in one and 8 ohms in the other), the equation given previously can be used.

$$Z_L = \frac{Z_{tap}}{(\% P)}$$

Since the belfry loudspeakers take 80 percent of the amplifier power applying the above equation we get

$$Z_L = \frac{500}{.8} = 625 \text{ ohms.}$$

Thus the impedance of the primary winding of the matching transformer for the belfry loudspeaker is 625 ohms.

Similarly the congregation loudspeakers use 10.6 percent of the total power and the primary impedance required for the matching transformer is

$$Z_L = \frac{500}{.106} = 4,710 \text{ ohms.}$$

Since this value is not available in commercial matching transformers, a primary impedance of 5,000 ohms may be used.

$$\text{Mismatching} = \left(\frac{\text{Actual load impedance}}{\text{Required load impedance}} \times 100 \right) - 100.$$


therefore,

$$\text{Mismatching} = \frac{5,000}{4,710} \times 100 - 100 = 106 - 100 = 6\%.$$

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

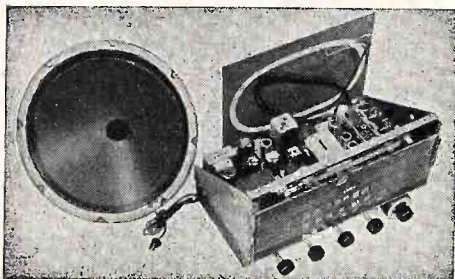Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

The NEW ESPEY model 511-B

FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

Makers of fine radios since 1928.

ESPEY

TEL. TRafalgar 9-7000

MANUFACTURING COMPANY, INC.

528 EAST 72nd STREET, NEW YORK 21, N. Y.

This will result in about 6 percent mismatching which probably would not be noticed.

Since the two primary windings (625 ohms and 5,000 ohms) are in parallel, then their effective impedance is 555 ohms.

$$\begin{aligned} Z_T &= \frac{1}{\frac{1}{Z_2} + \frac{1}{Z_1}} \\ &= \frac{Z_1 Z_2}{Z_1 + Z_2} \\ &= \frac{625 \times 5,000}{625 + 5,000} \\ &= 555 \text{ ohms.} \end{aligned}$$

This will give a mismatch of 11 percent. The installation will work satisfactorily with the above computed values, but if the 5-watt auxiliary loudspeaker were also connected by means of a matching transformer across the 500-ohm tap this would result in an even closer match. Thus, with the auxiliary loudspeaker taking 6.67 percent of the available power, the primary impedance of its matching transformer is

$$Z_L = \frac{500}{.0667} = 7,500 \text{ ohms.}$$

A matching transformer having a primary impedance of 7,500 ohms can be used.

Since the three matching transformers are in parallel, their effective load is 517 ohms which closely matches the 500-ohm output transformer tap. Of course, the auxiliary loudspeaker could be connected to any other tap if the primary impedance of the matching transformer used is calculated to provide overall matching. The table below indicates this.

TABLE I

Output Transformer Tap Impedance	Primary Impedance of Matching Transformer
4	60
8	120
125	1,875
250	3,750

The best over-all match is obtained when this auxiliary loudspeaker is connected across the highest impedance tap (500 ohms), but if a 7,500-ohm matching transformer is not available then the other choices are available.

The primary impedance of the matching transformer for the 2-watt choir loudspeaker can be similarly found. This loudspeaker utilizes 2.67 percent of the total power so that

$$Z_L = \frac{250}{.0267} = 9,360 \text{ ohms.}$$

A matching transformer with a 10,000-ohm primary can be used. A separate line and tap are used for this loudspeaker because, if fed from the 500-ohm line, the matching transformer would require a primary impedance of 20,000 ohms which is not available.

Since the matching transformer for each loudspeaker or group of loudspeakers has been calculated, the question arises, "Will the set-up as illustrated in Fig. 2 match the output impedance of the amplifier?" The proper value of the reflected load impedance at the primary of the output transformer is usually unknown. The recommended plate load impedance as given in tube manuals is rarely used without some change due to various

(Continued on page 16)

Look to **RIDER** the leader

ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider &
Seymour D. Usan

The only book of its kind that tells you all you should know about an oscilloscope. We guarantee it will save and earn you many times its cost!

PARTIAL LIST OF CHAPTER HEADINGS: Principles of Electromagnetic Deflection and Focusing; The Electron Gun; Screens; The Basic Oscilloscope and Its Modifications; Phase and Frequency Measurements; Nonlinear Time Bases; Waveform Observation in Television Receivers; Complex Waveform Patterns; Special Purpose Cathode-Ray Tubes; Commercial Oscilloscopes and Related Equipment.

992 pp. 3,000 illus. 8 1/2 x 11"
Bibliography Index \$9.00

FM TRANSMISSION AND RECEPTION

2nd Edition, 1950
by John F. Rider &
Seymour D. Usan

Answers all your questions about new developments in f.m. The latest functions and applications of f.m. are thoroughly and clearly discussed. Radio servicemen, radio amateurs, engineers, and students will find this an indispensable reference volume combining theory and practice.

CONTENTS: Part I: 1. Fundamental Considerations; 2. Frequency Modulation; 3. Essentials of F-M Transmitters; 4. Transmitters of Today; 5. The Transmission of F-M Signals. Part II: 6. Receiving Antennas; 7. The F-M Receiver; 8. Alignment of F-M Receivers; 9. Servicing F-M Receivers; 10. F.M. in Television Receivers. Appendix. Bibliography. Index.

460 pp. Illus. 5 1/2 x 8 1/2" \$3.60

Up-to-the-minute TV information

TV AND OTHER RECEIVING ANTENNAS (Theory and Practice) by Arnold B. Bailey

Information and suggestions on practical design considerations on more than 80 of the latest types of receiving antennas are given here. Some of this data has never before been published anywhere! Covers practically all types of VHF and UHF antennas.

606 pp. 5 1/2 x 8 1/2" 310 illustrations \$6.00

TV INSTALLATION TECHNIQUES by Samuel L. Marshall

This practical book is designed to help you make the best possible installation and eliminate return calls. You get complete information on all the mechanical and electrical considerations of TV installation.

336 pp. 5 1/2 x 8 1/2" 270 illustrations \$3.60

TV MASTER ANTENNA SYSTEMS by Ira Kamen and Richard H. Dorf

Installation, maintenance, usage and merchandising of TV master antenna systems—and the problems involved—are completely discussed. Covers virtually all amplified and nonamplified systems. This is the only available source book of its kind!

368 pp. 5 1/2 x 8 1/2" 234 illustrations \$5.00

published by

JOHN F. RIDER PUBLISHER, INC.
480 Canal St., New York 13, N. Y.

LOUDSPEAKER MATCHING

(Continued from page 15)

practical design considerations. It is unnecessary to know the value of the reflected load impedance, but is important that the proper value be obtained.

When the reflected impedance is unknown, the following formula may be used to determine if the desired reflected impedance has been obtained:

$$1 = \frac{Z_{tap1}}{Z_{load1}} + \frac{Z_{tap2}}{Z_{load2}}$$

Thus in the installation cited:

$$1 = \frac{250}{10,000} + \frac{500}{517} = .025 + .968 = .993$$

The two sides of the equation balance very closely so that the computed values will give correct matching.

Where it is desired to feed two different loads at the same time with equal power, the two loads should be connected to taps having half the impedance of the connected load. Thus, if the amplifier power is to be divided equally between a 250-ohm line and a 16-ohm loudspeaker, the 250-ohm line is connected to a 125-ohm tap and the 16-ohm load to an 8-ohm tap as shown in Fig. 3.

Checking this to see if the correct loading on the amplifier tubes is obtained, we get:

$$1 = \frac{125}{250} + \frac{8}{16}$$

so that matching is maintained.

Similarly three taps can be used to obtain equal division of power output if each tap load is connected to a tap impedance equal to one-third the load impedance. For example,

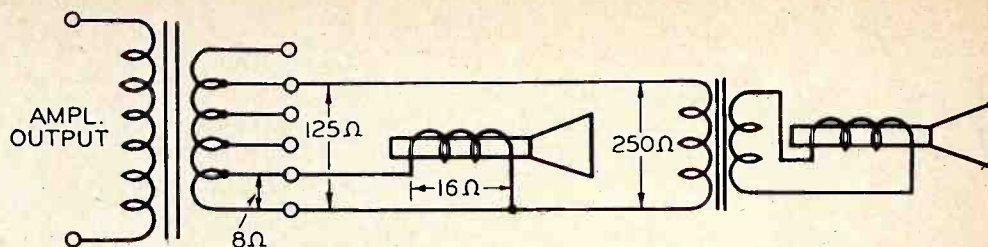


Fig. 3: If the amplifier power is to be divided equally between two different impedance loads, these loads should be connected to taps having half the impedance of the connected load, as shown.

a 600-ohm load, an 18-ohm loudspeaker, and a 6-ohm loudspeaker can be connected across taps whose values are 200 ohms, 6 ohms and 2 ohms, respectively.

A simple but common use of two taps is when it is desired to connect most of the output across one load (say a 500-ohm line) and a small part of the output across another load (15-ohm voice coil) such as a monitor loudspeaker. In this case the 500-ohm line is connected to its matching impedance, the 500-ohm tap, while the 15-ohm load is connected across a tap whose impedance is 20 percent or less of the impedance of the load. This will be 3 ohms or less, so the 15-ohm monitor can be connected to a 2.5-ohm tap.

Matching With Available Transformers

There are occasions when the exact type of line transformer required is not available. In many of these cases it will be possible to use a line transformer with different ratings and still obtain a match. When a transformer is rated as having a certain primary and secondary impedance, that transformer will properly match those impedances, but it does not mean that it can not be used for matching other impedances.

For example, let us assume that an 8-ohm loudspeaker has to be matched to a 250-ohm tap on the amplifier output and that the only line transformer available is rated as having a 500-ohm primary and multiple secondary taps. This rating indicates that when a load is connected to the proper tap on the secondary (as an 8-ohm loudspeaker connected to the 8-ohm tap), the primary of the transformer will present a 500-ohm load to the amplifier. By connecting the 8-ohm loudspeaker to a tap other than the 8-ohm tap, it may be possible to have the transformer present a 250-ohm load to the amplifier, which is desired in this particular case. To determine the tap to which the loudspeaker is connected, this equation can be used:

$$\frac{Z_{P1}}{Z_{P2}} = \frac{Z_{S1}}{Z_{S2}}$$

where: Z_{P1} = rated primary impedance.

Z_{P2} = desired primary impedance.

Z_{S1} = rated secondary impedance, or tap.

Z_{S2} = desired secondary impedance.

Since the secondary tap is desired, the equation can be rearranged by solving for Z_{S1} , giving:

$$Z_{S1} = \frac{Z_{P1}Z_{S2}}{Z_{P2}}$$

Substituting the known values we have:

$$Z_{S1} = \frac{500 \times 8}{250} = 16$$

Therefore, when the 8-ohm loudspeaker is connected to the 16-ohm tap on the secondary of the line transformer, the primary of the transformer will present a load of 250 ohms

to the amplifier and a proper match will be obtained. This method of matching is shown in Fig. 4.

Multi-Secondary Output Transformers

Transformers having two separate secondary windings may be used to feed different loudspeakers through frequency-discriminating circuits. This is one means of obtaining high- and low-frequency outputs from different loudspeakers. Sometimes three secondary windings can be obtained so that a middle-frequency output can also be obtained. Not all multi-secondary output transformers, however, are designed for simultaneous loading on all the secondaries. In many cases several windings are offered instead of a winding with several taps, to avoid any problems that might arise from unused taps. In such a case correct loading on any one winding will give the correct reflected impedance. Unless properly compensated for, the use of several windings where design does not permit, will result in improper loading in the output stage of the amplifier.

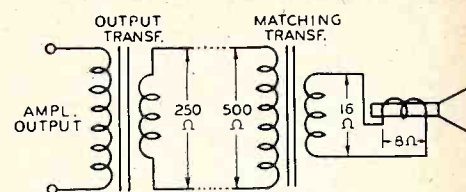


Fig. 4. A method for impedance matching when the proper line-matching transformer is not available.

Matching of Volume Controls and Pads

Ordinary volume controls such as potentiometers and rheostats cannot be used to control the level at loudspeakers, as any variation in the setting of the potentiometer will cause the load on the amplifier to change. The amplifier then will be properly matched at only one setting of the control. In order to keep the amplifier matched to the load at all settings of the control, a constant-impedance type of volume control, such as the L- or T-pad is necessary.

Pads, being resistive networks, will dissipate some power when in the circuit. This power is wasted, as it merely heats the pad and does not produce any sound. When an L- or T-pad is set for full volume output from the loudspeaker, there is no power loss in the control, but when it is at zero volume all the power is dissipated in the control. For settings between zero and full volume, the power supplied by the amplifier is split up between the pad and the loudspeaker. In other words, the full power must appear across the line at all times whether or not it is present at the loudspeaker.

(Continued on page 18)

63,500

There are 63,500 references to pertinent electronic and allied engineering articles published from 1925 through 1949 in the five editions of the

ELECTRONIC ENGINEERING MASTER INDEX

1925-1945 edition— (15,000 entries).....	\$17.50
1935-1945 edition— (10,000 entries).....	\$10.00
1946 edition— (7,500 entries).....	\$14.50
1947-1948 edition— (18,500 entries).....	\$19.50
1949 edition— (12,500 entries).....	\$17.50

Electronics Research Publishing Company, Inc.
Dept. 55 480 Canal St., New York 13, N. Y.

Please mention Successful Servicing when answering advertising.

*Actual reflected load
Desired reflected load = 1

HERE'S REAL NEWS FOR SERVICEMEN:

Federal's
**PREFERRED
TYPES
OF MINIATURE
SELENIUM
RECTIFIERS**
**HANDLE 90% OF TODAY'S
TV-RADIO REPLACEMENTS**

- ➔ **Save critical materials**
- ➔ **Assure continuous supply**
- ➔ **Reduce rectifier inventory**

HERE is important news for distributors, jobbers, dealers, servicemen—all who play a part in providing replacements for the more than 20,000,000 selenium rectifiers already installed in the nation's television and radio receivers!


Federal takes the lead in assuring an ample supply of these vital power conversion units by concentrating its materials on the *preferred types*—the miniature selenium rectifiers that are designed to handle approximately 9 out of 10 of all replacement demands.

Keep your profit finger on the selenium rectifier replacement market by sticking with Federal!

**America's Oldest and Largest Manufacturer of Selenium Rectifiers
and Originator of the Miniature Selenium Rectifier**




Federal Telephone and Radio Corporation

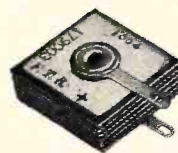


**FTR
1004**

USED FOR
REPLACING
50-100 MA, 130 V.

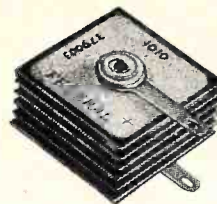


**FTR
1010**

USED FOR
REPLACING
150-250 MA, 130 V.

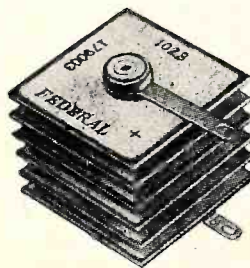

**FTR
1023**

USED FOR
REPLACING
300-350 MA, 130 V.

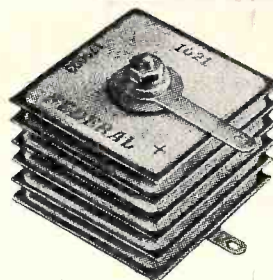

**FTR
1021**

450 MA
130 V.

THINK OF IT—

With the *Federal Preferred Types* illustrated above you can satisfy the great majority of replacement orders—and give customers the quality, efficiency and dependability that keeps Federal the leader in selenium rectifier design, engineering and production.

SELENIUM-INTELIN DIVISION

100 KINGSLAND ROAD, CLIFTON, NEW JERSEY

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

Please mention Successful Servicing when answering advertising.

• NOW AVAILABLE •

Element VIII Ship Radar Techniques

Available in a separately bound booklet, Element VIII brings RADIO OPERATOR'S LICENSE Q AND A MANUAL completely up to date. Same question, answer, discussion treatment as used in the text.

RADIO OPERATOR'S LICENSE Q AND A MANUAL

Second Edition, 1950

by Milton Kaufman

SYSTEMATICALLY LISTED are the questions and answers to past FCC exams plus a FOLLOW-THROUGH discussion of the answers, so necessary for complete understanding of technical questions. Abundant illustrations make difficult questions picture-clear.

Not simply an optional text, but an indispensable reference volume for student, operator, and radio amateur, it is up-to-date in all respects as of the publication date. Based on the Government Study Guide and supplementary FCC releases, the volume offers valuable appendices never before available in a book of this type. You will find yourself constantly referring to this complete, comprehensive handbook for a thorough review of essential theory, as well as for a refresher for advancement.

CONTENTS: Element I: Basic Radio Laws, Rules, and Regulations; Element II: (New) Radiotelephone Operating Practice; Element III: Basic Theory and Practice, Radiotelephone, and (New) Basic Radiotelephone; Element IV: Advanced Radiotelephone; Element V: (New) Radiotelegraph Operating Practice; Element VI: Radiotelegraph and Advanced Radiotelegraphy; Element VII: Aircraft Radiotelegraph for Flight Radio Operator; Element VIII: Ship Radar Techniques (separately bound) Amateur Radio Questions and Answers; Rules Governing Amateur Radio Service; Classes B and C Amateur Radio License Examination Questions and Answers; Class A Radio License Examination Questions and Answers. Appendices: Part 13—Rules Governing Commercial Radio Operators; Extracts from Radio Laws; Conventional Abbreviations; International Morse Code; Small Vessel Direction Finders; Automatic Alarm; Index.

766 pp. 5 1/2 x 8 1/2" 240 illus. \$6.60
Element VIII: 32 pp. 5 1/2 x 8 1/2" 78¢

JOHN F. RIDER PUBLISHER, Inc.
480 Canal St., N. Y. 13, N. Y.

LOUDSPEAKER MATCHING

(Continued on page 16)

From the point of view of impedance matching, however, the pad is the best type of individual (or group) loudspeaker level control, since it presents a constant impedance to the power source. Pads are available in many of the more common voice coil and line impedance values. In the design of a distribution system where a pad matching a voice coil or line is used, the computations can be made on the basis of the voice coil or line impedance and the presence of the pad can be ignored. An example of the use of L-pads is shown in the p-a system illustrated in Fig. 2.

Fixed pads can be inserted before loudspeakers to introduce a constant loss in signal level. This may be done to limit the maximum output of a particular loudspeaker or group of loudspeakers. Another use of fixed pads can be to obtain proper power distribution where particular taps or matching transformers are not available. This method is rather inefficient because of the loss in the pads and should not be used in high-power p-a systems.

Checking Load Impedance

After a distribution system has been designed and the loudspeakers and associated transformers connected, a check may be made on the impedance of the entire load. This is done by measuring the impedance of a voice coil, except that in this case the voice coil is replaced by the loudspeaker line which is disconnected from the amplifier.

The variable resistance should have a large enough range to cover the load impedance of the loudspeaker system. When the load impedance has been measured, this value can be used to check the computations that have been made, and in determining to which tap on the amplifier output the load should be connected.

Westinghouse H-251, Ch. V-2150-81, V-2150-82, V-2150-84

The -81 chassis utilizes a V-6771-2 tuner assembly. If the 6C4 h-f oscillator tube is replaced in this tuner, the different inter-electrode capacitance of the new tube may change the oscillator frequency enough to necessitate re-alignment of the oscillator. The oscillator adjusting screws are located on the front of the tuner assembly, and this procedure should be followed for their adjustment:

1. Remove the channel selector and fine tuning knobs. Remove the selector escutcheon plate and escutcheon mounting plate by removing the Phillips head screws securing them to the cabinet. The adjustments are accessible through the hole in the cabinet.
2. Set the fine tuning control to the middle of its range, and leave it in this position during the following adjustments.
3. Set the channel selector switch to the highest of the low band (Channels 2 through 6) stations operating in your locality.
4. Peak the appropriate oscillator slug for the best picture detail.
5. Repeat step 4 for each progressively lower channel on which a station transmits in your area.
6. Set the channel selector switch to the highest of the high band (Channels 7 through 13) stations operating in your locality.
7. Peak the appropriate oscillator slug for the best picture detail.

8. Repeat step 7 for each progressively lower channel in the high band on which a nearby station transmits.

9. Check the previously made low-band adjustments, and if the tuning has changed repeat steps 3 through 8.

The -82 chassis uses a V-6850 tuner assembly. In this tuner no adjustments are provided. Therefore, when a tube replacement is being made, different tubes should be tried until one is found that matches the characteristics of the original tube and provides normal operation.

The V-6238 tuner assembly used in the -84 chassis has several screw-adjusted slugs and trimmers located on the top and rear of the tuner. These adjustments affect the r-f bandpass of the tuner and are provided for production purposes only. They should not be used by the service technician. The h-f oscillator slugs are accessible through the front of the tuner and are the only adjustments that should be used when servicing the tuner. Replacement of the 6C4 h-f oscillator tube may, in some instances, necessitate readjustment of the h-f oscillator slugs. All of the channels should be checked, and if the stations cannot be tuned-in correctly within the range of the fine tuning control, the oscillator slugs on the front of the tuner assembly should be adjusted as follows:


1. Remove the channel selector and fine tuning knobs. Remove the selector escutcheon plate and escutcheon mounting plate by removing the Phillips head screws that secure them to the cabinet. The adjustments are then accessible through the hole in the cabinet.
2. Set the fine tuning control to the middle of its range, and leave it in this position during the following adjustments.
3. Set the channel selector switch to the highest channel on which a station transmits in your area.
4. If in the preceding step the channel selector was set to a high band (Channels 7 through 13) station, adjust the slug marked "13" for best picture detail. Note: If stations in your locality transmit on more than one of the high-band channels, a compromise setting of slug "13" must be made that will allow all high-band stations to be tuned-in using the fine tuning control. Slug "13" is the only adjustment for high-band stations. If in the preceding step the channel selector was set to a low band (Channels 2 through 6) station, adjust the appropriate (3, 4, 5, or 6) slug for best picture detail.
5. Set the channel selector to the next lower channel on which a station transmits in your area, and adjust the appropriate oscillator slug for best picture detail. Note: Since there is no adjustment labeled "2", a compromise setting of slug "3" must be made to allow Channels 2 and 3 to be tuned-in using the fine tuning control.
6. Repeat step 5 for each progressively lower channel used in your area.
7. Check back at the highest channel and then each progressively lower channel to make certain that the slugs are still correctly adjusted. There is some interaction between coils, and "touch-up" adjustments may be required during the checking procedure.

Replacement of the 6AG5 r-f amplifier tube may change the characteristics of the tuner. To compensate for this, different tubes should be tried until one that matches the characteristics of the original tube and functions normally is found.



No Margin for Error Here!

★ Thick, black smoke blots out the sky as the sickening hiss and crackle of scorching flames race man in the fight against destruction. Every ounce of skill and strength trained men can muster is pitted against the scourge of destructive fire. The equipment used in this never-ending battle is the finest known. Two-way radio, now standard equipment on all modern fire-fighting apparatus, must stand alert and ready for each critical assignment. The vibrator, although small, is a tremendously important factor in fire-fighting communication. It has helped save lives . . . and dollars, too. It must answer each call with peak performance. **NO MARGIN FOR ERROR HERE . . .** that is why RADIART is specified. Reputation built up over the years for dependable performance has stemmed from superiority in engineering design and controlled manufacture. This same skill of design and manufacture is basic in every RADIART automotive vibrator — it pays to put this skill to work for you.

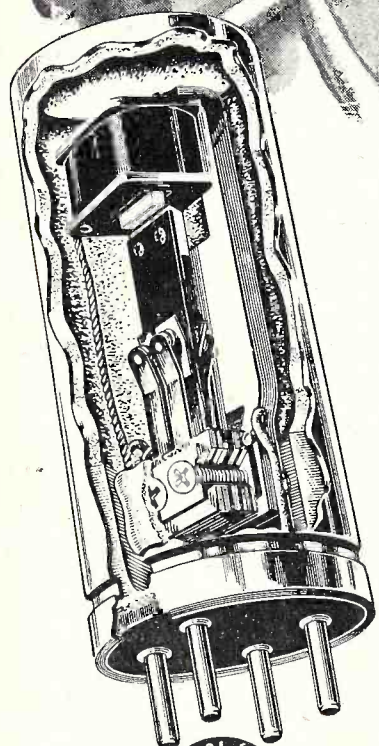


When It's Needed the Most . . . RADIART Quality Meets the Challenge

THE RADIART CORPORATION CLEVELAND 2, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES

Please mention Successful Servicing when answering advertising.

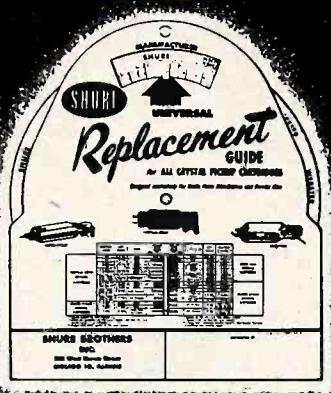FREE!**NEW SHURE****Cartridge Replacement GUIDE**

A TURN OF THE DIAL GIVES THE CORRECT REPLACEMENT MODEL OF ALL SHURE CARTRIDGES AND MOST OTHER MAKES

Ask your Shure Distributor for a "Guide"—or write direct, giving us his name.

SHURE BROTHERS, INC.

Microphones and Acoustic Devices

225 West Huron Street • Chicago 10, Illinois

Please mention Successful Servicing when answering advertising.

Crosley 9-409M3-LD, 9-419M1-LD, 9-422M-LD

The LD models on the '49 series receivers such as the above were designed especially for fringe area reception. In some cases when these sets are operated in areas where the signals from one or more stations are exceptionally strong, the strong signals may cause the contrast control to operate very critical, the sound output may be weak, picture fading may occur, or there may be critical vertical sync. Since these sets were built, other factors may have caused stronger signals: some local stations may have gone into operation, the earlier stations may have increased their power, or the receiver may have been moved into a strong signal area producing this condition. This strong signal condition can be corrected without the receiver losing sensitivity by adding a variable bias to the 3rd picture i-f stage, in the following manner:

1. Disconnect the 3rd i-f grid coil (L205 in Model 9-422M-LD, L206 in Models 9-409M3-LD and 9-419M1-LD) from ground.
2. Connect a 1000- μ f capacitor (Part No. 160034) between the low side of the 3rd i-f grid coil and ground.
3. Connect a 1-megohm resistor (Part No. 39374-61) between the low side of the 3rd i-f grid coil and the center tap of the contrast control.

If picture brightness fluctuation is still encountered due to line voltage changes, disconnect the 470,000-ohm picture tube grid resistor from the cathode of the d-c restorer tube (6AL5) and connect to chassis.

Radio Changes**United Motors 980979, Buick**

Model 980979 is used in all 1951 Buick cars, and is identical to the 1950 Model 980863 Buick except for the parts listed below. The antenna trimmer compensation is for antennas between 0.000061 and 0.000088 μ f. In the Parts List given below, the service part number is identical to the production part number except where the service part number is given in parenthesis.

Illus. No.	Production No.	Description
4	7260499	Oscillator coil
13	7258221 (G390)	Capacitor 0.000039 μ f molded
49	7234563	Resistor 360 ohms, 1w, ww
62	7259502	Speaker, 8", round p.m.
64	7260855	Transformer, output
81	7260421	Backplate pointer
90	7260420	Pointer assembly
	1219845	Pointer tip pkg.
92	7260416	Escutcheon Assy.
93	7260423	Dial
94	7260422	Dial backplate
98	1219840	Push button and slide assy "B"
99	1219841	Push button and slide assy "U"
101	1219842	Push button and slide assy "I"
102	1219843	Push button and slide assy "C"
103	1219844	Push button and slide assy "K"
104	7260414	Worm gear and bracket assy.

General Electric 600, 601, 603, 604

The description "maroon for Models 600 and 601" should be added to Stock items RAB-096, RAU-308, RHY-010, and RHB-006. The following additional replacement parts have been added to the Parts List for Models 600, 601, 603, and 604.

Part No.	Description
RAB-125	Back, cabinet back, tan, less hinges (603)
RAB-126	Back, cabinet back, green, less hinges (604)
RAU-327	Cabinet, cabinet body, tan (less back, handle and hardware) (603)
RAU-328	Cabinet, cabinet body, green (less back, handle and hardware) (604)
RDK-204	Knob, volume or tuning, green (604)
RDK-205	Knob, volume or tuning, tan (603)
RHB-014	Button, plug button, tan, in cabinet over alignment trimmers (603)
RHB-015	Button, plug button, green, in cabinet over alignment trimmers (604)
RHM-052	Clip, for rim-mounting speaker
RHM-062	Clip, for hole-mounting speakers
RHW-024	Cup washer, retaining washer for item RMS-217, handle shock spring
RHY-016	Handle, cabinet handle, tan (603)
RHY-017	Handle, cabinet handle, green (604)
RJP-028	Plug, battery connecting plug P1
RMS-216	Guide spring, used with item RMC-040
RMS-217	Spring, shock spring for cabinet handle
UCG-022	Capacitor, 56 μ f, mica, C15.

Chevrolet 986067

Model 986067 is designed expressly for 1947, '48, '49, and '50 Chevrolet trucks. In checking voltages of the 986067, it will be necessary to remove the rear cover of receiver and remove radio chassis from the case. Hook up radio on the service bench to a 6-volt power unit or a fully charged battery. The master selector switch of the volt-ohm-milliammeter should be set to the 12 position and the voltage selector switch to D.C. 1K/v position. Place test leads in jacks marked "test leads," ground the negative lead to the radio chassis for ground, with the red lead check all tube pins marked "H" which show a reading on voltage chart. Now set the Master selector switch to the 600 position and the voltage selector switch to A.C. 1K/v position. With red lead check the two terminals marked "P" on the OZ4 tube, both should read 270 to 280 volts a.c. each. If incorrect or no voltage check the following:

1. Check or replace capacitors (Illus. Nos. 31 and 32).
2. Check or replace resistor (Illus. No. 47).
3. Check or replace power transformer.
4. Check or replace vibrator.
5. Check or replace OZ4 tube socket.

Now change the Master selector switch to the 300 position and the voltage selector switch to D.C. 1K/v position. Pin "K" on OZ4 should read 245 to 255 volts d.c. If incorrect or no voltage, check or replace OZ4 tube.

Pin "P" on the 6V6GT tube should read 235 to 245 volts d.c. If incorrect or no voltage, check the following:

1. Check or replace electrolytic capacitor (Illus. No. 24B).

2. Check or replace resistors (Illus. Nos. 48 and 49).

Pin "S" on the 6V6GT tube should read 200 to 210 volts d.c. If incorrect or no voltage, check the following:

1. Check or replace electrolytic capacitor (Illus. No. 24C).

2. Check or replace resistors (Illus. Nos. 48 and 49).

Pin "K" on the 6V6GT tube should read 10 to 14 volts. If incorrect or no voltage check the following:

1. Check or replace electrolytic capacitor (Illus. No. 25A).

2. Check or replace resistor (Illus. No. 45).

Pin "P" on 6SQ7 tube should read 65 to 75 volts d.c. If incorrect or no voltage check the following:

1. Check or replace capacitors (Illus. Nos. 25, 26, and 32).

2. Check or replace resistor (Illus. No. 43).

Pin "P" on 6SK7 intermediate frequency amplifier tube should read 200 to 210 volts d.c. If incorrect or no voltage, check or replace the intermediate frequency transformer.

Pin "S" on 6SK7 i-f amplifier tube should read 60 to 70 volts d.c. If incorrect or no voltage, check the following:

1. Check or replace resistor (Illus. No. 38).

2. Check or replace capacitor (Illus. No. 17).

Pin "P" on the 6SA7 tube should read 200 to 210 volts d.c. If incorrect or no voltage, check or replace intermediate frequency transformer.

Pin "S" on the 6SA7 tube, should read 60 to 70 volts d.c. If incorrect or no voltage check the following:

1. Check or replace capacitor (Illus. No. 17).

2. Check or replace resistor (Illus. No. 38).

Pin "P" on the radio frequency amplifier 6SK7 tube should read 155 to 165 volts d.c. If incorrect or no voltage check the following:

1. Check or replace capacitor (Illus. No. 18).

2. Check or replace resistor (Illus. No. 39).

Pin "S" on r-f amplifier 6SK7 tube should read 60 to 70 volts d.c. If incorrect or no voltage check the following:

1. Check or replace resistor (Illus. No. 38).

2. Check or replace capacitor (Illus. No. 17).

If the tubes, vibrator, and voltages are correct and radio does not play, the trouble will


(Continued on page 22)

TRIPL ETT

Load-Chek

introduces
**Servicing
by
Power
Consumption**

MODEL 660

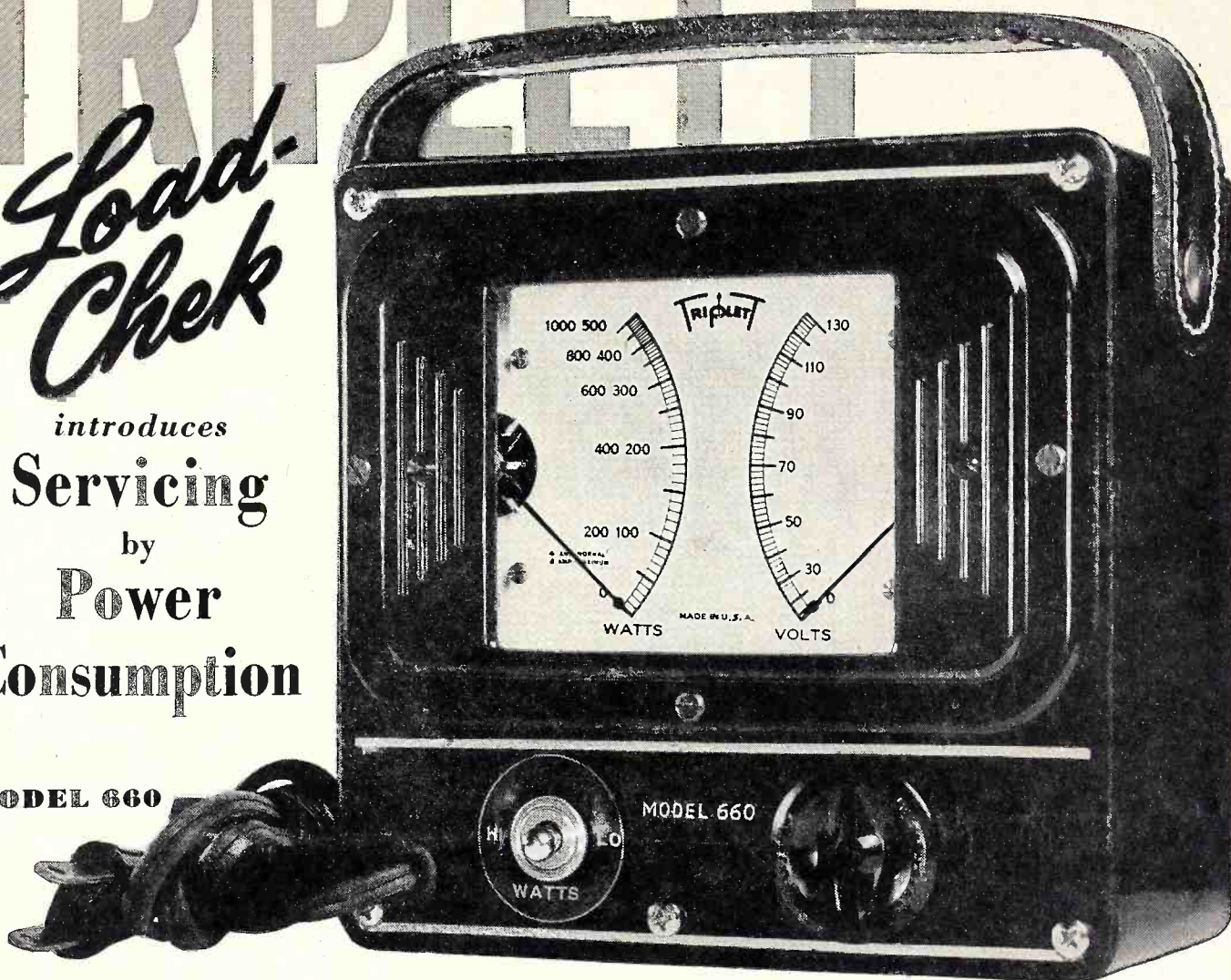

LOAD-CHEK for the first time makes it possible for every technician to utilize what is perhaps the simplest and quickest of all service methods—Servicing by Power Consumption Measurements.

Power consumption measurement has long been proved by auto-radio servicemen as a rapid method of localizing troubles in auto radios. But Triplet's new **LOAD-CHEK** is the *first* Wattmeter to be produced at moderate cost, and with the proper ranges, to bring this short-cut method within the reach of every radio and TV service man.

Basis of the **LOAD-CHEK** method is the tag or label on every radio and TV chassis which shows the normal power consumption. The following examples are only two of many time-saving uses of this new instrument.

LOCATING A SHORT—The chassis tag may show a normal consumption of 225 Watts. Simply plug the power cord of the chassis into **LOAD-CHEK** (there are no loose ends to connect or be in the way). Note the reading—which should be possibly 350 Watts. By removing the

rectifier tube you can determine at once which side of the tube the short is on. With a soldering iron and long-nosed pliers you can check through the chassis, locate and correct the trouble without having to lay down tools or to check with lead wires!

REPLACING BURNED OUT RESISTORS—With the chassis to be repaired plugged into a **LOAD-CHEK MODEL 660**, note the wattage reading with the burned out resistor circuit open. Now replace the resistor. Should the increase in watts be greater than that of the resistor rating being installed, it indicates that an extra load has caused the trouble which has not been cleared.

LOAD-CHEK is made-to-order for the busy service man and can help stop costly "come back" repair jobs. It's a profit-maker because it's a Time-Saver. And at its moderate cost **LOAD-CHEK** can be standard equipment on every service bench. By all means, inspect this versatile instrument at your distributor and place your order, for under present conditions we must fill all orders on a basis of "First Come, First Served."

SEE MODEL 660 **LOAD-CHEK** AT YOUR DISTRIBUTOR'S

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplet

TRIPL ETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.

Please mention Successful Servicing when answering advertising.



ANY SERVICEMAN CAN DO IT...

More jobs in Less time = Greater Profit!

With a COMPLETE Library of RIDER AM-FM-TV MANUALS you have all the information you need for a quick, efficient, profitable servicing job. Have at your fingertips these...

EXCLUSIVE RIDER MANUAL FEATURES:

- CIRCUIT ACTION DESCRIPTIONS
- COMPLETE ALIGNMENT DATA
- SIGNAL WAVEFORMS FOR TROUBLE SHOOTING
- LARGE, EASY-TO-READ DIAGRAMS
- COMPLETE PARTS LISTS AND VALUES
- UNPACKING AND INSTALLATION DATA
- FACTORY AUTHORIZED DATA

RIDER TV MANUAL Vol. 6



All TV production runs and changes from August, 1950, through January, 1951. ACCURATE...FACTORY-AUTHORIZED servicing material direct from 66 manufacturers. Convenient 12" x 15" page size, all pages filed in place. Equivalent of 2320 pages (8 1/2 x 11) plus Cumulative Index Volumes 1 through 6. Only \$24.00

RIDER MANUAL Vol. XXI



Don't let any job get away from you. Complete your RIDER MANUAL Library with this important volume. FACTORY-AUTHORIZED servicing information from 61 manufacturers. AM-FM-Auto Radios...Record Changers...Disc and Tape Recorders. Coverage from December 1949, through October 1950. 1648 pages plus Cumulative Index Volumes XVI through XXI. Only \$21.00

MAKE MONEY WITH RIDER BOOKS, TOO!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton



For TV-AM-FM receivers and allied equipment. 2500 radio and TV tube substitutions listed... tube types classified by functions... plus other important data you must have in order to keep receivers going. 224 pages, 8 1/2" x 11" Only \$2.40

VACUUM-TUBE VOLTMETERS (REVISED EDITION)

by John F. Rider



Up-to-the-minute in its coverage of all types of vacuum-type voltmeters. Discusses design, construction, maintenance and applications. Review questions at the end of each chapter. 432 pages, 5 1/4" x 8 1/2", 215 illustrations. Only \$4.50

ORDER RIDER FROM YOUR JOBBER TODAY!

JOHN F. RIDER PUBLISHER, Inc. • 480 Canal St., New York 13, N. Y.

Chevrolet 986067
(Continued from page 20)

be in the grid circuit of the radio. To continue, it will be necessary to check the grid circuit by means of signal tracing.

Turn on signal generator on and off switch, place the modulation switch in the modulated position, set signal generator tone control to 0.5 and place shielded lead assembly in jack marked "audio." Ground the black lead to the radio chassis. Turn on radio receiver with volume to maximum position.

With red lead touch pin marked "P" on the 6V6GT tube. If you have no signal, check the following:

1. Check or replace speaker.
2. Check or replace audio transformer.

Touch pin "G" on 6V6GT tube. If no signal check or replace 6V6GT tube.

Touch pin "P" on the 6SQ7 tube. If no signal check the following:

1. Check or replace capacitors (Illus. Nos. 25, 26, 27, and 28).
2. Check or replace tone control.

Touch pin "G" on 6SQ7 tube. If no signal, check or replace 6SQ7 tube.

Touch the two pins marked "DP" on 6SQ7 tube. A signal should be heard on each one. If no signal check or replace 6SQ7 tube.

Change the signal generator shielded lead to the intermediate frequency "I.F." jack. Tune signal generator to exactly 262 and set band switch in "A" position. Turn the signal generator volume control about one-third open and touch pin "P" on intermediate frequency 6SK7 amplifier tube. If no signal, check the following:

1. Check or replace intermediate frequency transformer.
2. Check or replace volume control.
3. Check or replace capacitor (Illus. No. 23).
4. Check or replace resistor (Illus. No. 44).

Touch pin "G" on i-f 6SK7 amplifier tube. If no signal check or replace 6SK7 tube.

Touch pin "P" on 6SA7 tube. If no signal check the following:

1. Check or replace intermediate frequency transformer.
 2. Check or replace sensitivity control.
- Touch pin marked "G" on 6SA7 tube. If no signal check or replace 6SA7 tube.

Change the signal-generator shielded lead to the radio frequency "R.F." jack, tune signal generator to exactly 1000 kc and set band switch to "B" position. Tune radio to 1000 kc. Touch pin "P" on 6SK7 amplifier tube. If no signal check the following:

1. Check or replace radio frequency coil (Illus. No. 3).
2. Check or replace oscillator coil (Illus. No. 4).
3. Check or replace capacitors (Illus. Nos. 18, 19A, 19B, 20 and 21).

Touch pin "G" on r-f 6SK7 tube. If no signal check or replace 6SK7 tube.

Place a 0.000075- μ f capacitor on the end of red lead and plug in antenna socket. If no signal check the following:

1. Check or replace antenna coil (Illus. No. 1).
2. Check or replace choke coils (Illus. No. 2).
3. Check or replace antenna trimmer (Illus. No. 16).
4. Check or replace resistors (Illus. Nos. 37 and 42).



the Du Mont type 20_{CP4}

For the set that follows the "seventeen" in rectangular pictures, Du Mont supplies the "twenty" all-glass rectangular Type 20CP4.

Another in the series of Big-Picture Teletrons employing the NEW Bent-Gun for edge-to-edge sharpness that makes the difference in picture tubes of this size. The gray filter face plate improves contrast.

The first picture tube designed with the industry "standard" neck length of 7 $\frac{3}{8}$ ".

Our Commercial Engineering Department invites all design inquiries.

Allen B. Du Mont Laboratories, Inc., Cathode-Ray Tube Division, Clifton, N. J.

DUMONT
*Teletrons**

*Trademark

VACATION TIME

The office of John F. Rider Publisher, Inc. will be closed for vacations from July 21 through August 5. Please try and anticipate your needs and send your orders and requests for schematics in to us before July 21 or after August 5. We'll be back all sunburned and rested on August 6, ready to serve you again.

Jewel 349, 949

Model 349 is the same as Model 949. The Alignment Procedure for these models is the same as that for Models 921, 935 and 936, except that "Reduce input as needed to keep output near 1.28 volts (0.5 watt)" should read "to keep output near 0.4 volt (0.5 watt)," and in the third column, 12BE6 grid (mentioned twice) should read 1R5 grid. The Parts List for Models 349 and 949 is given below:

Ref. No.	Part No.	Description
C1	30-17A	Variable capacitor, 2 gang, 420 & 162 μ f
C2, 3, 11	32-4	Tubular paper capacitor, 0.05 μ f, 200 v
C4, 6	32-29	Tubular paper capacitor, 0.01 μ f, 200 v
C5, 7	32-17	Tubular paper capacitor, 0.002 μ f, 200 v
C8	32-20	Tubular paper capacitor, 0.005 μ f, 200 v
C9	32-5	Tubular paper capacitor, 0.05 μ f, 400 v
C10	32-32	Tubular paper capacitor, 0.2 μ f, 200 v
C12, 13	35-4	Mica capacitor, 100 μ f, 500 v
C14	31-16A	Electrolytic capacitor, 50 x 30 μ f, 150 v
C15	31-17	Electrolytic capacitor, 200 μ f, 15 v
R1	20-49	100K, $\frac{1}{4}$ w, 20%
R2	20-46	3.3M, $\frac{1}{2}$ w, 20%
R3	20-6	2.2K, $\frac{1}{2}$ w, 20%
R4	20-42	8K, $\frac{1}{2}$ w, 20%
R5	20-57	4K, $\frac{1}{4}$ w, 20%
R6	20-53	4.7M, $\frac{1}{4}$ w, 20%
R7	20-74	220K, $\frac{1}{4}$ w, 20%
R8	20-14	1M, $\frac{1}{2}$ w, 20%
R9	20-31	47 ohms, 1 w, 10%
R10	20-143	2.5K, 8 w, 5% ww
R11	20-134	2.7K, 1 w, 10%
R12	20-109	1.5K, $\frac{1}{2}$ w, 10%
R13, 14	20-67	1K, $\frac{1}{2}$ w, 10%
R15	50-17	Volume control, 1 megohm, DPST switch (S2)
T1	61-12	Input i-f transformer
T2	61-13	Output i-f transformer
L1	62-16	Loop
L2	60-10	Oscillator coil
S1	65-4	Manual slide switch, DPDT
	73-3	Selenium rectifier, 65 ma
	80-15	4" p.m. speaker with output transformer
	120-28	Leatherette cabinet
	120-29	Front panel and baffle board
	W122-24	Volume knob
	W122-19	Selector knob
	123-9	Plastic dial

INDEX OF CHANGES

Model Page Number
Successful Rider Manuals
Servicing From To

TELEVISION CHANGES

Admiral Ch. 20Z1	24	—	—
Andrea CVK 19 Normandy Ch. VK-19	2	2-8 *2-9, 10 3-1 5-1,2	2-22 *2-37 3-3, 4 —
Belmont C1602 Series C, Ch. 16AX29 Ch. 12AX27	6 2	5-1 Page 8, May issue of Successful Servicing	5-8
Capehart Farnsworth 335B, 335M, Ch. CX-33S, C-303	6	Page 10-12, May issue of Successful Servicing	5-1 5-12 6-1 6-20
CX-33	—	—	—
Crosley 9-409M3-LD, 9-419M1-LD, 9-422M-LD	20	—	—
DuMont RA-105, RA-106	2	2-5 *2-5 C3-1 C4-2 2-34 *2-57 5-27 C6-2	2-33 *2-55, 56 — — — *2-58 5-31 —
Emerson Ch. 120124-B	3	—	—
621, 628, Ch. 120098B; 622, Ch. 120098P; 630, Ch. 120099B	24	—	—
Garod 14CT4, 16CT4, 16CT5, 19C6, 19C7, 1671, 1672, 1673, 1674, 1675, 1900, 1974, 1975, Series 97 and 98	6, 8, 10	5-1 5-18 5-15 4-24 C6-4	5-14 5-20 5-17 4-33 —
General Electric 818	3	—	—
12C107, 12C108, 12C109, 12T3, 12T4 16C110, 16C111, 16C115, 16T1, 16T2	43 5	5-35 6-35	5-44 6-44
Industrial 248, 348, Ch. IT-35R, Ch. IT-48R 12, 13	13	3-1 C4-4 C5-2 5-1	3-8 — — —
Olympic 752, 752U, 753, 753U, 755, 755U, 764, 764U, 766, 766U, 767, 769	5	6-1 6-1	6-11, 12 6-15
Trad TT-63-SH	24	—	—
Travler 14B50, 14C50, 16R60, 16R70	6	6-1 6-3	6-2 6-4
16G50, 16G50A, 16R50, 16R50A, 16T50, 16T50A	5-1	—	5-10
Westinghouse H-251, Ch. V-2150-81, V-2150-82, V-2150-84	18	4-9	4-16
Zenith Ch. 22H20Z Ch. 22H20	6	6-1	6-20

RADIO CHANGES

Chevrolet 986067	20, 22	16-1	16-4
General Electric 600, 601, 603, 604	20	21-57	21-60

Jewel 349, 949 921, 935, 936	24	20-5 20-3	— 20-4
United Motors 980979, Buick 980868	20	18-20 20-26	18-21 20-31

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

Admiral Ch. 20Z1

Microphonics in television tuner 94C21-2 can be due to vibration of loose wires or loose components. In some instances, the ceramic stator plate M118 (tuning stator) has been a source of microphonics since the rivets which fasten this part to the tuner chassis may be loose. This can be remedied by soldering the plate mounting bracket to the tuner chassis. To solder the plate mounting bracket to the tuner chassis, remove the bakelite tuner shaft bearing plate at the front of the chassis and also the grounded tuning stator plate M107, and move the tuner shaft M104 forward.

Intermittent or noisy operation noticeable when the channel selector knob is "rocked" is commonly due to a broken coil section, or dirty or loose coil contacts (see information for 20X1, 20Y1 chassis). In some instances it has been found that the turret retainer springs M125, holding the turret in the housing, do not have sufficient pressure on the turret shaft to hold the turret firmly enough to insure good contact. A heavier spring made from .057 stock was used in later tuners. The old spring was made from .049 stock. All replacement springs are made of the heavier stock, although the part number remains the same, 98A45-85.

Trad TT-63-SH

The following changes have been made in Model TT-63-SH. Resistor R181, the 1200-ohm resistor going to the red lead of T109, is now connected to the +290-volt line, instead of to the +270-volt line. The value of resistor R203, connected from pin 8 of V123 to the +270-volt line, has been changed from 1800 ohms to 3000 ohms. A connection to the +290-volt line has been added at the junction of C160A, C158A and L120.

Emerson 621, 628, Ch. 120098B; 622, Ch. 120098P; 630, Ch. 120099B

The 1500-ohm cathode resistor R91 should go from pin 3 of V20 to the B— line, and not to the junction of R90 (horizontal hold control) and R92 as shown on the schematic for Ch. 120098B.

PERMIT NO. 9427
NEW YORK, N. Y.
PAID
U. S. POSTAGE
Sec. 34.66, P. L. & R.

A. J. S. CERINO
5310 OVERBROOK ST.
DOUGLASSON, L. I., NEW YORK

Return Postage Guaranteed
JOHN F. RIDER PUBLISHER, Inc.
480 CANAL ST., NEW YORK 13, N. Y.

JULY, 1951

Successful SERVICING

IT'S

KNOW-HOW THAT COUNTS

BY JOHN F. RIDER



The Public Howls

In our travels around the nation, we hear more and more about licensing the television servicing industry. Two issues are involved. One of these is safeguarding the people's funds when they pay in advance for service to be delivered in the future. The second is technical competency. If one is to judge by lurid tales which appear almost daily in different newspapers throughout the nation, it is safe to forecast that regulation of television servicing is inevitable in several major television centers before the end of 1951. How far the program will spread is indefinite, but the patterns set by large cities can well become the basis for state-wide regulation.

But this is not the story of television licensing or regulation, although what we have to say is related to it. We are interested in the question of technical competency in TV servicing. Most certainly it is an important subject. While we have the utmost confidence in the survival of AM radio, if not FM, it is pretty certain that the financial future of the servicing industry lies in television.

Technical Competency — How?

How does one achieve technical competency? Not by any one thing alone. Rather, it is a combination of a number of things, a result of complete understanding of the entire activity. It would be so much pleasanter and simpler for all, if the development of television receivers were at a static level so that everyday servicing operations would be conducted on receivers which contained similar circuitry. In other words, if nothing but experience were necessary to increase compe-

tency. Such is not the case, however, and in that respect television servicing is not comparable to any other kind of service activity.



Television receiver circuit design is in a state of flux and will more than likely remain that way for quite a while. Competition demands that costs be reduced and the market enlarged; that the effective range of television receivers be increased, thereby creating more viewers for a station; that the number of controls be reduced to make operation easier; that receivers be made more stable, more sensitive. All of this forces never-ceasing research for new tubes, new component designs, and new combinations of circuits to achieve these ends. The differences in end product resulting from research may not be too evident when things function properly, but the moment a television technician is called upon to probe the innards of a receiver, he is face-to-face with the many artifices of communication equipment engineering.

Research Never Ceases

Many servicemen state that it would not be half so bad if the new designs were known beforehand. One can understand, however,

that this is impossible, for then a manufacturer who has spent much time and money in research would be orienting the thinking of his competitors, defeating his own efforts. Of course, in many cases, coming events cast their shadows before, as in the contents of numerous research papers which appear in the different engineering publications. But even these do not always disclose the commercial end product, the specific circuit which eventually appears in the receiver. Frequently, this circuit may not see the light of day until perhaps two or three years after the preliminary disclosure.

Training Must Go On

Under such circumstances how does one achieve technical competency in television servicing? Is it just schooling? Obviously the answer is in the negative, for, after all, even the finest school is limited in the length of its course and the scope of its training. The school lays the foundation; it is then up to the graduate to perform the labors necessary to build on that foundation. No school course can be so broad in its coverage as to

(Continued on page 7)



Television Changes

Montgomery Ward 94WG-3022A,
94WG-3026A, 94WG-3029A

The following information supplements the Picture I-F and Trap Adjustment Alignment Table and replaces the Retouching of Picture I-F adjustments and Response curves sections. **Checking Picture I-F Adjustments**—The response curve, secured after completing steps 5 through 12 may be observed by connecting the sweep generator to the TEST POINT (as shown in Fig. 1) which is the junction of R-6 and R-7, and by connecting the oscilloscope to the junction of L-8 and R-51. The marker signal generator should be loosely coupled to the sweep generator output leads.

With the Contrast control set at -3 volts (Step 5) the response curve should be approximately flat topped as shown in Fig. 2. A 25.75-Mc (picture carrier) marker signal should appear approximately 45% down, and a 23.0-Mc marker approximately 10% down. A 21.25-Mc signal (sound carrier) and a 27.25-Mc signal (adjacent sound carrier) should have zero response. Some final adjustment of T-1 (bottom), L-5, T-10 (top), and L-7 may be required to secure an ideal response curve. The portions of the curve affected by these adjustments are shown in Fig. 2. Do not change trap adjustments T-1 (top), T-5 or T-10 (bottom) after they have been set according to steps 6, 7 and 8.

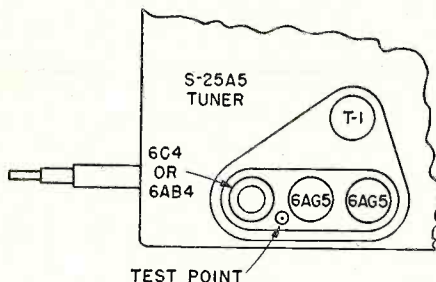


Fig. 1. Test point for Montgomery Ward Models 94WG-3022A, 94WG-3026A, 94WG-3029A.

In areas of low signal strength it may be desirable to increase the i-f sensitivity by aligning the i-f with a -1 volt setting of the contrast control. If this is done the response curve will be approximately as shown in Fig. 3. The marker signals should have the same relative positions as for -3 volt alignment.

R-F Response Curves—The response curves shown in Figure 18 for the "A" Series may be observed by connecting the sweep generator and the marker signal generator (loosely coupled) to the antenna input and by connecting the oscilloscope to the TEST POINT (junction of R-6 and R-7) on the tuner as shown in Fig. 1.

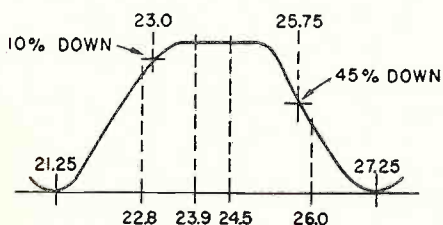


Fig. 2. I-f response for -3 volts on contrast control.

The response curves obtained in this check indicate the accuracy of adjustment of the r-f and converter coils. Any appreciable variation from the curves shown in Figure 18 indicate coil misalignment. If such a condition is found the entire tuner unit should be returned to the factory for repair. To check for correct oscillator coil adjustment on each channel connect the sweep generator and the marker signal generator (loosely coupled) to the antenna input. Connect the oscillator to the junction of L-8 and R-51. The response

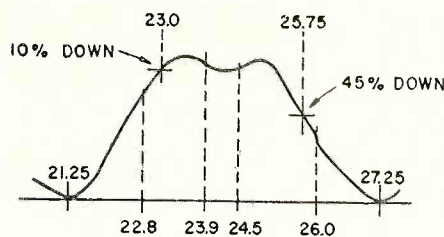


Fig. 3. I-f response for -1 volt on contrast control.

curve should be approximately the same as for the i-f response check. The picture carrier marker should be approximately 45% down and the sound carrier at zero level. To adjust each oscillator coil, set the Fine Tuning control in the center of its range and adjust each coil screw to properly position the markers.

The following miscellaneous parts have been added. Most of these parts are required because of the addition of brown and white cabinets.

Ref. No.	Description
RAB-093	Cover, back cover (white)
RAB-094	Cover, back cover (brown)
RAC-063	Cover, loop cover (maroon) substitute for RAC-057
RAC-069	Cabinet, main body (brown) includes hinge
RAC-070	Cabinet, main body (white) includes hinge
RAC-071	Cover, front cover (white) includes hinge
RAC-072	Cover, front cover (brown) includes hinge
RAC-075	Cover, loop cover (white)
RAC-076	Cover, loop cover (brown)
RAI-007	Stop, cover stop
RDK-173	Knob, brown control knob
RHR-004	Rivet, tube socket rivet
RHY-009	Handle, cabinet handle
RSW-070	Switch, power, operates in conjunction with lid.

Belmont C-1602, M-1601, Ch. 16AX23, 16AX25, 16AX26

In early production of the above chassis, the 6V6 plate supply voltage was connected through the fuse. If the fuse happened to blow, the 6V6 plate supply voltage (350 volts) would be cut off leaving the screen at 240 volts, a condition which will cause damage to the tube. It is suggested that whenever a 16-inch set is received for repair the following change be made: Disconnect the red lead of the vertical output transformer from the B+ point and reconnect to pin 5 of the power jumper socket. If the fuse blows after the change is made, the plate will remain at 350 volts and the 6V6 tube will not be damaged by excessive screen current.

The following modification has been made on all chassis starting with group numbers 7500 and up, and it is suggested that it be made on all chassis with group numbers below

7500. The modification will limit the 1X2 filament voltage and prevent tube failures. A 10-ohm, 1/2-watt, 10% resistor (Part No. C-9B1-38) is added in parallel with each of the two 1X2 tube filaments. The resistor should be connected from pin 1 to pin 5.

Admiral Ch. 20T1, 20V1

A circuit change has been made in these chassis as follows: Resistor R314 (680,000 ohms) is no longer connected to pin 7 of V304, the 6AL5 video detector and agc, but now goes from pin 1 of V304 to the junction of R317 (4700 ohms) and L303. Remove the tuner agc lead (white) from the agc lug and ground the wire to the chassis.

A new p-m focus assembly is being used in some of the 20T1 and 20V1 chassis. The following information is a supplement to the "Installation and Service" notes for these chassis and is to be used only for those chassis employing the p-m focusing assembly. This assembly consists of a mounting bracket, a picture positioning lever, and a permanent magnet focusing control. Three alternate types of p-m focus assemblies are used. These assemblies (Part Nos. 94C33-1, 94C33-2, 94C33-3) are electrically and physically interchangeable. However, they differ slightly in location of adjustments and methods of adjusting. Part No. 94C33-1 has the picture centering lever mounted between the focus assembly mounting plate and the focus magnet, and has the focus control shaft located below the picture tube socket. Part Nos. 94C33-2 and 94C33-3 have the picture centering lever extending from the back of the focus magnet, and have the focus control shaft located above the picture tube socket. The parts eliminated from the B+ (filter) circuit when the p-m focus control is used are focus coil L404, focus control R445, and resistor R444. Electrically these parts have been replaced with resistor R505 (200 ohms, 10 w, Part No. 61A7-20). Resistor R505 is connected between filter capacitor C409B and C409C. The screen R438 (6800 ohms, 2 w) formerly connected to the junction of fuse M401 and C430 (0.1 μ f) is now connected to the opposite side of C430 (junction of white lead from deflection yoke T403B and C430).

Focus adjustment can be made without removing the cabinet back from the receiver. Set the picture control for normal picture and the brightness control at slightly above average brightness. Insert a screwdriver through the hole near the center of the cabinet back. When the screwdriver blade engages the slot at the end of the focus control shaft, rotate the control to the right or to the left until the picture is in sharp focus. Slight rotation in either direction generally should bring the picture into focus.

If the picture is off center, it can be centered by using the picture positioning lever, and, when necessary, repositioning the p-m focus assembly around the picture tube neck. Follow the instructions given below:

To center the picture: (1) Adjust ion trap as instructed in the "Installation and Service Notes." (2) Center the picture by adjusting the picture positioning lever. Note that the picture positioning lever can be moved sideways, and up and down. It may be necessary to reduce picture height and width to determine correct centering unless a test pattern is used. (3) Readjust the ion trap.

For difficulty in centering the picture: (1)

Adjust the ion trap as above. (2) Slightly loosen the two screws which mount the p-m focus assembly to the yoke bracket. Facing the back of the chassis, move the p-m focus assembly fully to the left while rotating it counterclockwise (to the left as far as possible). Then tighten the two mounting screws. (3) Center the picture with the picture positioning lever. If the picture cannot be centered with the lever, it may be necessary to repeat Step 2, resetting the focus assembly slightly off center in another direction and then centering the picture with the picture positioning lever. (4) Readjust the ion trap.

ORDER YOUR COPY NOW RIDER TV VOLUME 6

Admiral 32X15, 32X16, 32X26, 32X27, 32X27A, 32X35, 32X35A, 32X36, 32X36A, Ch. 20Z1

Models 32X27A, 32X35A and 32X36A are the same as Models 32X27, 32X35 and 32X36 in that they use a 94C21-2 tuner, a 5B2 radio chassis, a 2PA1 power supply, and a 20Z1 television chassis. They differ, however, in that the locations of the radio-phonograph unit and the television receiver are reversed. Models 32X27A, 32X35 and 32X36 have the tv compartment on the right side of the cabinet, and Models 32X27, 32X35A and 32X36A have the tv compartment on the left side of the cabinet facing the front of the set. Consequently, with the exception of the cabinet parts listed below, the Parts List for Models 32X27A, 35A and 36A are identical to those given for Models 32X27, 35 and 36, and Chassis 20Z1 and 5B2. The following parts should be added to the Cabinet Parts List for Models 32X15, 32X16, 32X26, 32X27, 32X35 and 32X36.

Description	Part No.
Back, cabinet (for radio-phonograph and album compartment)	
32X15, 32X16	43C 128-1
32X26, 32X27, 32X35, 32X36	43C 128-2
32X27A, 32X35A, 32X36A	43C 129-1
Back, cabinet (for television compartment)	
32X27A, 32X35A, 32X36A	A3225
Base, cabinet	
Blond (32X27A)	35E 123-55
Walnut (32X35A)	35E 124-57
Mahogany (32X36A)	35E 124-58
Cabinet, wood	
Blond (32X27A)	35E 123-6
Walnut (32X35A)	35E 124-4
Mahogany (32X36A)	35E 124-5
Walnut (32X35)	35E 115-1
Mahogany (32X36)	35E 115-2
Carton and fillers	
32X35A, 32X36A	44B 172
32X27A	44B 173
Decal, cabinet refinishing (consists of 2 panel decals and 7 decal strips)	
32X35, 32X35A (walnut)	35E 116-63
32X36, 32X36A (mahogany)	35E 116-64
Door catch and strike plate	
Walnut (32X35A), mahogany (32X36A)	35E 124-56
Blond (32X27A)	35E 123-59
Door, record compartment complete	
Blond (32X27A), 16" x 14"	35E 123-53
Walnut (32X35A), 14 3/4" x 14"	35E 124-53
Mahogany (32X36A), 14 1/4" x 14"	35E 124-54
Doors, tv and radio-phonograph compartment (matched pair)	
Blond (32X27A) tv door: 18" x 16 3/4", radio door 16" x 15 3/4"	35E 123-51
Walnut (32X35A) tv door 18" x 16 3/4", radio door 15" x 15 3/4"	35E 124-50
Mahogany (32X36A) tv door 18" x 16 3/4", radio door 15" x 15 3/4"	35E 124-51
Gasket, sponge rubber (for back of picture window, includes cardboard backing)	
32X26, 32X27, 32X27A, 32X35, 32X35A, 32X36, 32X36A	98A 61-7
Hinge, knife door (pair)	
32X27A (blond)	35E 123-57
32X35A (walnut), 32X36A (mahogany)	35E 124-55
Socket, pilot light (with 50" lead)	82A 11-60
Socket, cable and plug, pilot light	A3192.

Westinghouse H-216A, Ch. V-2146-45DX

The chassis used in this model incorporates provisions for phono operation which are not indicated on the schematic diagram. A DPDT switch is inserted between point "D" on the schematic and the 0.01- μ f capacitor C213. The switch is connected so that in one position, the output of the ratio detector (point "D") is connected to C213 as shown on the schematic for this chassis, while in the other position point "D" is grounded and C213 connects instead to a phono connector on the chassis. Parts for this circuit are as follows: V-3254S Connector, phono; V-5406 Switch, TV-phono.

Westinghouse H-242, Ch. V-2150-31A

In later production of Model H-242, a V-2150-31A chassis is used. The differences between this chassis and the original V-2150-31 chassis are in the high-voltage power supply. As shown in Fig. 1, a 6Y6G high-voltage oscillator tube is used instead of a 6V6/GT, and the high-voltage power supply circuit is different. The physical appearance of R463, which is connected in series with the focus control, is different in later production chassis. The new resistor is covered with asbestos, and the assembly of resistor and asbestos is designated part No. V-8214. The electrical ratings of the old and new resistors are identical. The red wire that runs from the tie point for the old resistor to the tie point for the new resistor should be clipped from the circuit when the new resistor is installed.

It may be noted that the 3rd i-f amplifier screen dropping resistor R348 is designated 100,000 ohms in the service notes. This is the correct value for the resistor. However,

in early chassis a 47,000-ohm resistor is used. In chassis containing the 47,000-ohm resistor, it may be possible to reduce noise at the cathode-ray tube grid by increasing the value of R348 to 100,000 ohms.

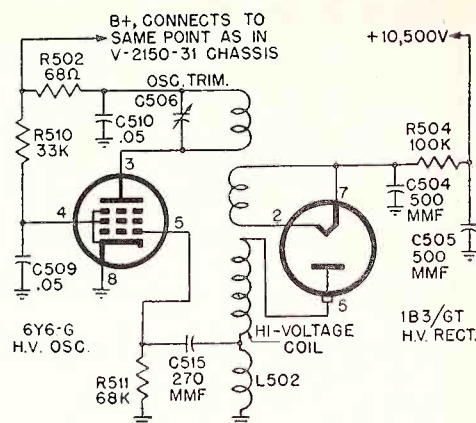


Fig. 1. High-voltage power supply Westinghouse Ch. V-2150-31A.

The parts list for Chassis V-2150-31A is the same as that for Chassis V-2150-31 except for the following changes and additions. Change the part numbers of C204 to C212, inclusive, to read "V-6023-" rather than "V-6203-." Change R463 to read as follows: R463, V-8214, Resistor assembly, 110 ohms, 3 w, Focus coil shunt.

Ref. No.	Part No.	Description
C515	RCM20B271K	Capacitor, grid coupling, 270 μ f
R510	RC40AE333K	Resistor, screen dropping, 33,000 ohms, 2 w
R511	RC20AE683K	Resistor, grid bias, 68,000 ohms, 1/2 w
L502	V-9279-1	Coil, r-f choke (V-2150-31A chassis)
—	V-9278	Coil, hi-voltage (V-2150-31A chassis).

What Reviewers Say About

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf

Proceedings Of The I.R.E.

"This book was designed to be a working manual for many kinds of organizations and people concerned with master-television systems. The authors have succeeded to a remarkable degree in satisfying technical completeness and yet insuring the layman's comprehension by treating problems and their solutions.

Although primarily presented for those whose interests are in manufacture, sales, installation, maintenance, and use, this is also a tutorial work of interest to radio engineers.

The information is clearly presented in an easily readable manner. The book also covers video distribution systems, and provides an appendix with landlord agreement, survey report, and tenant letter forms."

Radio News

"A thoroughly practical 'how-to-do-it' text which covers all phases of the installation, maintenance, operation, construction, and merchandising of master antenna systems for television reception.

The book is clearly written and both technical and non-technical personnel should experience no difficulty in grasping the material."

Industrial Arts And Vocational Education

"Its seven chapters cover the information about basic television antenna systems, the need for master antenna systems, nonamplified and amplified antenna systems, how to install master systems, the video distribution systems, and merchandising these systems.

... The book contains clear explanations, illustrations and wiring diagrams."

a RIDER publication

WE GUARANTEE that RIDER BOOKS will show you how to do BETTER and MORE PROFITABLE servicing jobs...

This practical book tells you everything you should know about an oscilloscope! WHAT it is . . . what it can DO . . . and HOW to use it properly!



ENCYCLOPEDIA ON CATHODE-RAY OSCILLOSCOPES AND THEIR USES

by John F. Rider and Seymour D. Uslan

The **FIRST and ONLY** book that so fully and clearly describes the 'scope . . . its construction . . . its capabilities . . . its applications in communications, engineering, research . . . with thousands of time-saving and labor-saving references, charts, waveforms, etc.

All oscilloscopes produced during the past ten years, a total of more than 70 different models, are accurately described—with specifications and wiring diagrams.

Planning to buy or build a 'scope? This book will help you select the type best suited to your needs! If you already own one, the book will show you how to increase your instrument's usefulness in a thousand and one ways.

992 Pages • 500,000 Words • 3,000 Illustrations
8½ x 11" Size • 22 Chapters • Completely Indexed
Easy to Read • Cloth Bound.....And only \$9.00

TV and OTHER RECEIVING ANTENNAS

(Theory and Practice)
 by Arnold B. Bailey



Tells you . . . WHAT each type can do . . . HOW to use it . . . and WHICH is best!

This is a text book on all types of receiving antennas. If you have any questions—you'll find the answers in this book! Manufacturer, engineer, student, teacher, service technicians — all can use this text. **WE GUARANTEE IT!** Antenna data never before published anywhere will be found in it. And it's readable—because mathematics has been translated into charts and graphs.

606 Pages . . . 310 Illustrations.....And only \$6.00

Order this RIDER book, the **ONLY** text that gives you complete information on all the mechanical and electrical considerations.

TV INSTALLATION TECHNIQUES

by Samuel L. Marshall



KNOW the absolute facts about such things as ice loading, wind surface, and mounting requirements—whether for short chimney-attached mast or an 80 ft. tower, including foundation.

HAVE at your fingertips, accurate data on receiver adjustments in the home . . . municipal regulations governing the installation of TV antennas and masts in all of the major television areas in the U.S.

SURE to help you wherever and whenever any part of the installation requires "doping out"! A **TIMELY and IMPORTANT** book!

336 Pages • 270 Illustrations • 5½ x 8½ Size
Cloth BoundAnd only \$3.60

FM TRANSMISSION AND RECEPTION

by John F. Rider and Seymour D. Uslan



The entire system of frequency modulation is explained thoroughly . . . all types employed in amateur radio, television, broadcast, railroad, aviation, marine, police, point-to-point and mobile receivers. Basic theory, transmission, reception, circuit design and servicing are covered, with mathematics kept to a minimum. Almost all of the presently used FM commercial transmitters are described in detail.


460 Pages, Profusely Illustrated.....\$3.60

Beat the Tube Shortage!

This Sensational New RIDER Book Shows You **HOW** to Do It!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton

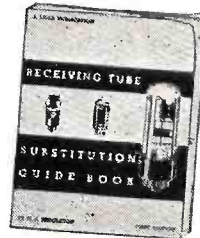

For AM-FM-TV Receivers and Allied Equipment!

- 2500 Radio and TV Tube Substitutions Are Listed!
- TV Receiver Filament Wiring!
- Heater Substitution Wiring Instructions!
- Tube Types Classified By Functions!
- And A Wealth Of Other Priceless Data!

EXTRA! In addition to tube information . . . this sensational book contains material on Cathode-Ray Tube Characteristics, Complete Tube Characteristics Chart, Ballast Tube Data, Pilot Light Information, Resistors—Capacitors—Transformer Color Codes, Transformer Substitution, Fixed Condenser Substitution, etc. . .

224 Pages in Heavy Durable Paper Cover. 8½ x 11"
Only.....\$2.40

New . . . Revised . . . Enlarged

RADIO OPERATOR'S LICENSE Q and A MANUAL

by Milton Kaufman



All the **QUESTIONS and ANSWERS** for the FCC examinations. New Elements 2, 5 and 7 have been included—and Elements 3 and 6 have been revised as of the September, 1950, FCC Supplements. However, the outstanding feature of this book is a **THOROUGH FOLLOW-THROUGH . . .** a carefully prepared discussion of the answer to the technical question, so necessary for an absolute understanding of the answer.

ELEMENT VIII: SHIP RADAR TECHNIQUES, is now available in a separately-bound booklet. Uses the same question-answer-discussion treatment as the text.

32 pages . . . heavy, durable cover.....78¢
766 Pages, Hundreds of Explanatory Diagrams..\$6.60

TV MASTER ANTENNA SYSTEMS

by Ira Kamen and Richard H. Dorf



50 million dollars will be spent in 1951 for TV Master Antenna Systems installed in apartment buildings, hotels, hospitals, etc. . . in both new and old buildings. In **TV MASTER ANTENNA SYSTEMS**, the authors provide a practical working manual which deals with installation, maintenance, usage, etc. This book shows how the Master Antenna is installed, how it works, and how you can capitalize on this fast-growing field.

368 pages • 234 explanatory illustrations.
Cloth boundOnly \$5.00



WE GUARANTEE your satisfaction! Make these books **PROVE** their value to you. Examine them at your favorite jobber. If he does not have them, send your order to us.

JOHN F. RIDER,

JOHN F. RIDER PUBLISHER, Inc.
 480 Canal Street, New York 13, N. Y.

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

JULY, 1951

No. 9

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
H. YUSEM, Associate Editor

Worth 4-8340
Worth 4-8341



Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.

CURTAIN TIME

The TV Factory Service Manager

No one can deny that much is to be desired in TV servicing. The public is not yet receiving the satisfaction it deserves in connection with maintenance. This cannot be placed in the lap of servicemen only. Some of the responsibility rests on the shoulders of other groups in the TV industry. Many TV servicemen have voiced opinions concerning TV servicing which warrant a great deal of attention among those who produce the nation's receivers. Granted that a TV receiver manufacturer tries hard to produce a good receiver and to make his parts available, the fact remains that there is still much to be done at the manufacturing level.

For instance, some TV receiver manufacturers provide very convenient test points at different places on the chassis. Others do not. These test points are very important to the individual who ultimately services the receiver. It speeds up the operation, reducing the cost to both the serviceman and the public. The presence or absence of test points is most probably decided by those who engineer the receiver. It is understandable that every penny saved in the construction of a TV receiver is important, but it seems to us that

giving recognition to the servicing phase during the design of the equipment is equally important. Frankly, we believe that the service managers of the different TV receiver manufacturers should have a greater say in the output of the nation's TV factories. Their suggestions may add slightly to the cost of a TV receiver but what they will save the public and the servicemen will in the long run more than repay the added cost. We'll hazard the statement that all factory service managers will recommend test points in TV receivers.

Sales as well as engineering management in TV manufacturing organizations must realize that word-of-mouth advertising by the TV servicemen of the nation can be favorable or unfavorable. It can defeat or aid the magazine, newspaper, radio and TV sales efforts of the receiver manufacturers. The relationship between the TV set owner and the servicing group is very close—much more tightly linked than in the case of radio. This is so because the public generally has only one TV receiver and does not wish to part with it for even a day. The public lends a willing ear to all statements about a receiver, especially when the device has developed a failing which is difficult to remedy.

The service managers of the manufacturing companies are the ones who receive the comments of the trade and the public. Their shoulders are broad and we know from personal contact that they are capable of carrying the load. But that is not the answer. The practice of some TV manufacturer should be the practice of all—approval of the receiver design by the service manager prior to production. Then and only then will TV receiver manufacturers save themselves many headaches and servicing problems. The suggestion is not extraordinary. It is being done today! Unfortunately, however, it is not being done by enough manufacturers.



There are good reasons why a TV receiver should be designed in such a way that the physical layout lends itself most effectively to future service operations. To provide adequately for service is not a reflection upon the engineering capabilities of the organization. On the contrary, it denotes a complete understanding of the numerous conditions which surround the operating life of the receiver. The more easily a TV receiver can be repaired, the greater is the return received by a customer on his investment, for the receiver will then be out of use for the least possible amount of time.

In this respect the service manager can be of utmost aid. He knows what is happening in the field. He knows what is needed service-wise. He is the one who hears the gripes and is able to give valuable counsel about their elimination. Exposing the engineering department to the thinking of the service department cannot help but prove beneficial. The engineer has a choice of many designs for one receiver—the one which is most effective for future servicing is the one which should be chosen.


There is no conflict between service and engineering. It is simply a meeting of the minds with the same goal in view—most rapid service with maximum satisfaction to the public. Mr. Manufacturer—give your service manager a greater voice in your TV receiver design and production, and be happier in the long run!

JOHN F. RIDER

OLD SETS — NEW SALES

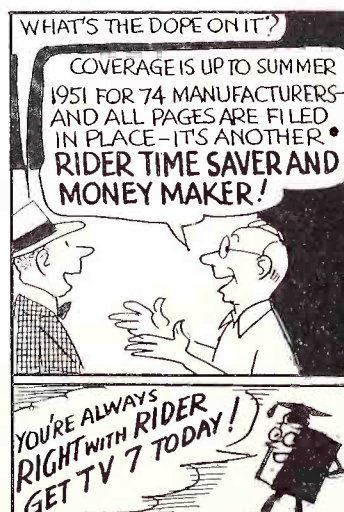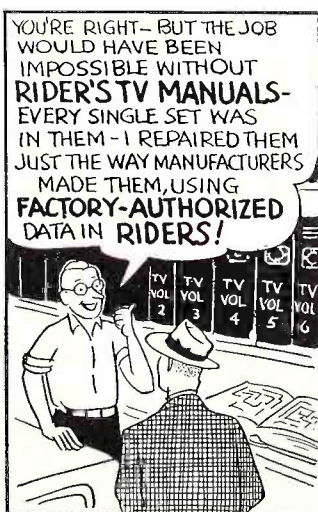

WITH RIDER TV MANUALS

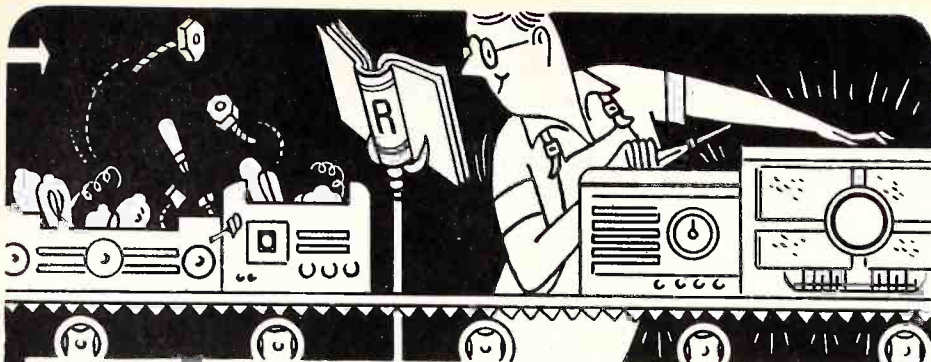

ANY SERVICEMAN CAN DO IT...

More jobs in Less time = Greater Profit!

With a COMPLETE Library of RIDER AM-FM-TV MANUALS you have all the information you need for a quick, efficient, profitable servicing job. Have at your fingertips these...

EXCLUSIVE RIDER MANUAL FEATURES:

- CIRCUIT ACTION DESCRIPTIONS
- COMPLETE ALIGNMENT DATA
- SIGNAL WAVEFORMS FOR TROUBLE SHOOTING
- LARGE, EASY-TO-READ DIAGRAMS
- COMPLETE PARTS LISTS AND VALUES
- UNPACKING AND INSTALLATION DATA
- FACTORY AUTHORIZED DATA

RIDER TV MANUAL Vol. 6



All TV production runs and changes from August, 1950, through January, 1951. ACCURATE...FACTORY-AUTHORIZED servicing material direct from 66 manufacturers. Convenient 12" x 15" page size, all pages filed in place. Equivalent of 2320 pages (8 1/2 x 11) plus Cumulative Index Volumes 1 through 6. Only \$24.00

RIDER MANUAL Vol. XXI



Don't let any job get away from you. Complete your RIDER MANUAL Library with this important volume. FACTORY-AUTHORIZED servicing information from 61 manufacturers. AM-FM-Auto Radios...Record Changers...Disc and Tape Recorders. Coverage from December 1949, through October 1950. 1648 pages plus Cumulative Index Volumes XVI through XXI. Only \$21.00

MAKE MONEY WITH RIDER BOOKS, TOO!

RECEIVING TUBE SUBSTITUTION GUIDE BOOK

by H. A. Middleton



For TV-AM-FM receivers and allied equipment. 2500 radio and TV tube substitutions listed... tube types classified by functions... plus other important data you must have in order to keep receivers going. 224 pages, 8 1/2" x 11" Only \$2.40

VACUUM-TUBE VOLTMETERS (REVISED EDITION)

by John F. Rider



Up-to-the-minute in its coverage of all types of vacuum-type voltmeters. Discusses design, construction, maintenance and applications. Review questions at the end of each chapter. 432 pages, 5 1/4" x 8 1/2", 215 illustrations. Only \$4.50

ORDER RIDER FROM YOUR JOBBER TODAY!

JOHN F. RIDER PUBLISHER, Inc. • 480 Canal St., New York 13, N. Y.

Radio Changes

General Electric 140

The rectifier assembly, REX-004, is no longer stocked riveted to a mounting bracket. The new rectifier may be screw mounted to the original rectifier bracket as follows: remove wires at the connecting lugs of the old rectifier; using screwdriver blade between plates of rectifier to be removed, pry plates off from rectifier mounting bracket; assemble new rectifier to bracket, using a #6-32 x 1 inch long screw through rectifier and bracket hole and fasten using lock washer and nut; replace wire connections to new rectifier.

General Electric 505, 506, 507, 508, 509, 530

Change Step 1 (column 2) of the Alignment Chart to read "12BA6 grid pin (1)," and Step 2 (column 2) to read "12SA7 grid pin (8)." Change the tube type numbers of the I-F Stage Gains to read: 12SA7 grid to 12BA6 grid—50 at 455 kc; 12BA6 grid to 12SQ7 diode plate—50 at 455 kc.

Jewel 955

The Alignment Procedure for Model 955 is the same as that given for Model 964. Model 955 also uses 12SA7, 12SQ7, 50L6, and 35Z5. The Parts List is as follows:

Ref. No.	Part No.	Description
C1, 3	32-17	Tubular paper capacitor, 0.002 μ f, 200 v
C2	32-4	Tubular paper capacitor, 0.05 μ f, 200 v
C4, 5	32-29	Tubular paper capacitor, 0.01 μ f, 200 v
C6	32-5	Tubular paper capacitor, 0.05 μ f, 400 v
C7	35-4	Mica capacitor, 100 μ f, 500 v
C8	31-20	Electrolytic capacitor 50 x 30 μ f, 150 v
C9	30-18	Variable capacitor, 420 & 162 μ f
R1	20-3	22K, 1/2 w, 20%
R2	20-7	4.7M, 1/2 w, 20%
R3	20-8	10M, 1/2 w, 20%
R4	20-19	470K, 1/2 w, 20%
R5	20-14	330K, 1/2 w, 20%
R6	20-73	1.5K, 1 w, 20%
R7	20-93	22 ohms, 1/2 w, 20%
R8	20-96	22 ohms, 1 w, 20%
R9	50-11B	Volume control, 2 megohms, SPST switch
	60-12	Oscillator coil, with spring clip
61-5 or	61-14	I-f transformer, with solder tabs
	62-17	Antenna coil
	47-3	Antenna hank, 15'
	80-17	4" p.m. speaker with output transformer
	120-30A	Cabinet (specify color)
	122-15	Knob (2) (specify color).


ORDER YOUR COPY NOW RIDER TV VOLUME 6

Jewel 964

In later Model 964 receivers, pin 5 of the 12AT6 is connected to the junction of the i-f transformer and pin 6, instead of to the junction of the antenna coil and the 4.7-megohm resistor (going to the i-f transformer). The Alignment Procedure is the same as that given for Models 921, 935, and 936, except that 1500 kc, under Coupling Capacitor, should read 50 μ f; under Connection to Receiver should be Antenna (Disconnect antenna hank by unsoldering), and under Ground Connection should be B—. The seven markings on the dial represent 550 kc, 650 kc, 750 kc, 900 kc, 1100 kc, 1400 kc, and 1600 kc, respectively.

**United Motors 982582, 982583,
Oldsmobile**

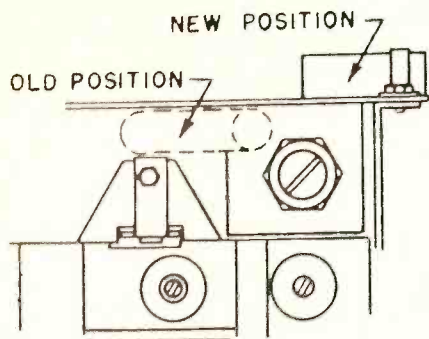The tuner solenoid capacitor (Illustration No. 43) has been moved to a new position and is now secured by a circular mounting bracket. The new location is directly above the solenoid on the top of the tuner frame, as shown in the accompanying diagram, and eliminates any tendency for the rear cover to bind on this capacitor when located on the rear of the tuner.



New position of tuner solenoid capacitor on United Motors Models 982582, 982583.

The clamp fastens around the capacitor approximately $\frac{1}{2}$ -inch from the ground end and this lead is soldered to the clamp for grounding. A self tapping screw secures the clamp to the liner frame. The hot lead to the capacitor is insulated by a heavy sleaving to the tuner return switch.

The value of the 7259128 electrolytic capacitor (Illustration No. 35) has been changed so that all sections are now 20 μ f. Thus, the cathode bypass capacitance on the output tubes has been raised from 10 μ f to 20 μ f and the schematic should be altered to comply with this increase.

The oscillator coil is now the same as that which is used on both the Cadillac and Buick signal seeking tuner type radios. The part number for this coil is now 7259184.

**RCA BX55, Ch. RC-1088; BX57,
Ch. RC-1088A**

Capacitor C11, 0.047 μ f, must be dressed away from the metal chassis and in such position that inserting the chassis into the case will not change its position. The side of C11 which may short to chassis is the side which connects directly to the selenium rectifier. If this side contacts the chassis it will place the chassis at power line potential.

The 2600-ohm, 6-watt resistor R13 now being used in Model BX57 is of improved design. The original resistor was a ceramic type and the type now being used is a flat armored type. When the new type is used to replace the original type, it is necessary to drill a .120" diameter hole in the front apron of the chassis to accommodate a self-tapping screw for mounting purposes.

General Electric 515, 516, 517, 518

Catalogue items RWL-009 and RWL-016 should be deleted from the Parts List and replaced by the following items: RWL-025, Cord, power cord and plug (brown, heavy duty type) for Models 515, 517, 518; RWL-026, Cord, power cord and plug (ivory, heavy duty type) for Model 516.

IT'S KNOW-HOW THAT COUNTS

(Continued from page 1)

encompass all of the practical circuit realities which issue from the manufacturing plants of the various companies.

Every Repair Job Must Teach

Unhappy though the situation may be, the practicing TV service technician is forced to expose himself daily to the many technical ideas which underlie operations in the field. Since there is no compromise with competency, there can be no compromise with the steps which must be taken to attain it. If the correction of a defect in a television receiver is accomplished as a mechanical act without regard to what can be learned from it, it is a fruitless effort. Every repair job is capable of teaching something. It may involve a new phenomenon or a repetition of an old and known one, but, whatever it is, it can teach. It may be that an old defect manifests itself in a new fashion; if so, a new symptom has been learned for future recognition. Or it may be an old symptom but one that stems from a malfunctioning new circuit. The demands of the television servicing business are such that more than just pay must be realized from every repair job.

Reading, Studying — Ad Infinitum

Reading and studying is the lot of the television serviceman. It simply cannot be avoided. Many men feel that they are so preoccupied with the actual labor of effecting the diagnosis and then the repair, that not

a minute is left for other duties. Possibly this is true in some cases, but even then we wonder if there isn't a way out. Our experience of over twenty-five years shows that there is a means of improving the situation. Technical competency is nourished by experience, but it grows much more rapidly when the food is ever-increasing knowledge. The more one learns about what is inside a television receiver, the more rapidly will a defect be diagnosed. In light of the varieties to be found in the different production runs of the same model, and then in the end product, knowing how the circuits of a receiver function will save a tremendous amount of time. As a matter of fact, it is one of the most effective ways of becoming familiar with new circuit designs, and becoming more competent as a service technician.

Know Your Circuits

The reading of technical articles that appear in the different journals circulating in the servicing industry is important, but it is even more important to read the circuit description or circuit analysis found in receiver service data. When we say this, we have Rider Manuals in mind, and we can not stress too strongly that every owner of these publications could well profit by devoting time to such reading.

The suggestion that circuit descriptions contained in service data be read, does not

(Continued on page 8)

WE NEED YOUR HELP!

We want to make **SUCCESSFUL SERVICING** of greater value to all its readers. We plan to reorganize the contents to best suit your requirements. We need your help!

In order to plan a magazine that is most useful to you, we need to know how many of our readers own **RIDER TV MANUALS**. Please indicate on the coupon below *whether or not* you own **RIDER TV MANUALS**. Just paste the coupon on a penny postcard and return it to us. Regardless of how you fill it in, you will continue to receive **SUCCESSFUL SERVICING**.

This is *your* magazine. Help us make it most useful to *you*. Our sincere thanks for your cooperation.

MAIL THIS COUPON NOW

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street — Dept. SS
New York 13, N. Y.

Gentlemen:

I have the following **RIDER TV MANUALS** in my servicing library (please circle those you own)

RIDER TV MANUAL 1 2 3 4 5 6

I do not own **RIDER TV MANUALS** ☐

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

VACATION TIME

The office of John F. Rider Publisher, Inc. will be closed for vacations from July 21 through August 5. Please try and anticipate your needs and send your orders and requests for schematics in to us before July 21 or after August 5. We'll be back all sunburned and rested on August 6, ready to serve you again.

INDEX OF CHANGES

Model	Page Number		
	Successful Servicing	Rider Manuals From	To
TELEVISION CHANGES			
Admiral Ch. 20T1, 20V1 32X15, 32X16, 32X26, 32X27, 32X27A, 32X35, 32X35A, 32X36, 32X36A, Ch. 20Z1	2	6-14	6-20
Belmont C-1602, M-1601, Ch. 16AX23, 16AX25, 16AX26	2	5-21	5-29
Montgomery Ward 94WG- 3022A, 94WG-3026A, 94WG-3029A	2	4-38	4-46
Westinghouse H216A, Ch. V-2146-45DX H-242, Ch. V-2150-31A	3	5-1	5-10
	3	4-1	4-8
RADIO CHANGES			
General Electric 140	6	17-21	17-23
505, 506, 507, 508, 509, 530	6	21-32	21-37
515, 516, 517, 518	7	21-47	21-51
Jewel 955	6	20-6	—
964	6	20-7	—
RCA BX55, Ch. RC-1088; BX57, Ch. RC-1088A	7	21-31	21-34
		21-35	21-38
United Motors 982582, 982583	7	21-55	21-60

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

● **KNOWLEDGE IS OF TWO KINDS: WE KNOW A SUBJECT OURSELVES, OR WE KNOW WHERE WE CAN FIND INFORMATION UPON IT.**

Samuel Johnson

IT'S KNOW-HOW THAT COUNTS

(Continued from page 7)

imply that each and every service operation must be preceded by a reading session. Far from it. We know only too well that a program of that kind is impractical. We do, however, recommend, and seriously so, that an hour each day be devoted to reading and studying, and if more time than that is available, it can well be spent in that way. It is the road to increased technical competency.

What is technical competency in television servicing? It is the ability to "read" the trace which appears on the picture tube of the receiver and a proper understanding of the contribution made by each section of the television receiver to the end product that appears upon the picture tube. This leads to a rapid diagnosis. If one listens to complaints of the public concerning technical incompetency, the story is always the same. The service technician did not completely repair the defect. This may or may not be so, but in many cases one defect may mask the other and improper interpretation leads to incomplete diagnosis.

Service Notes Help

The explanation of circuit functioning contained in service data is a deliberate attempt on the part of the receiver manufacturer to *teach* in the service notes—to expose each and every television technician, no matter how extensive or meagre his background, to explanations of circuit operations. Reading these explanations may be viewed as non-profitable time. That is farthest from the truth. One of the most progressive steps towards achieving technical competency is to follow up one's tentative diagnosis of a receiver by reading the appropriate circuit description. Quite frequently, it will be found that tremendously valuable facts are gleaned during the two or three minutes required to read such data. Equally frequently, the solution to the problem at hand becomes evident or measurement short cuts are indicated—to say the least, the time is not wasted. Every time even a small fraction of what is read is retained, more and more is learned, and little by little, diagnosis becomes easier and familiarity with television circuit design becomes broader.

It's A Tough Road

The road to technical competency is paved with work and demands perseverance and constancy of purpose. There are many who look at service information as simply reference

information. It is more than just a means to an end. Complete service information such as that which issues from receiver manufacturers and Rider Manuals has tremendous educational value, as well as reference value. Wave forms are not just pictures which are presented for comparison purposes. Each tells a story of what is happening in a portion of the circuit. Each carries a message, especially when the test oscilloscope shows something other than what is correct.

Every service technician is interested in saving time. That is the function of test equipment and service data, but the saving of time stems basically from recognition of the fault indicated by an incorrect trace or an improper reading on a test device. A sign of technical competency is knowing where to look for the fault and instantly recognizing circuit reorganization when examining a schematic. This does not come easily. It takes time, patience and the desire to learn. It is not an easy road, but it is a worthwhile one. Even today, a really competent television serviceman can name his own price. Even with all the criticism being heaped on the television industry, the public shows signs of recognizing ability. However, it has every right to expect those who service television receivers to really know what they are doing.

For Easier Servicing

RCA'S NEW FINGERTIP WRENCH SET solves the problem of holding, placing, and adjusting nuts in hard-to-reach corners of radio and television sets. These wrenches are worn on the finger, as shown, and are used to steady the nut or bolt as the screw is driven in place. Each set consists of five wrenches for the most commonly used nut and bolt sizes—3/16", 1/4", 5/16", 11/32", and 3/8".



PERMIT NO. 9427
NEW YORK, N. Y.
PAID
U. S. POSTAGE
Sec. 34.66, P. L. & R.

JOHN L. GIGL
437 NEVIN ST.
LANCASTER, PENN.

JOHN F. RIDER PUBLISHER, Inc.
480 CANAL ST., NEW YORK 13, N. Y.
Return Postage Guaranteed

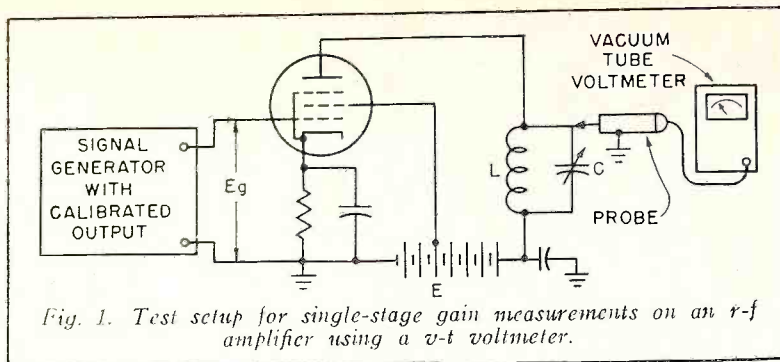


Fig. 1. Test setup for single-stage gain measurements on an r-f amplifier using a v-t voltmeter.

Using the VTVM

for

Amplifier

Stage

Measurements

by John F. Rider

GENERAL PRECAUTIONS IN USE OF VTVM

Before using a vacuum-tube voltmeter, it is important to check several things.

1. Is the frequency of the voltage to be measured within the range of the instrument? If the frequency is near or beyond the primary range limits, a correction may be required.

2. What is the effect of the voltage being measured on the voltmeter reading? Sine-wave voltage is assumed in most voltmeter calibrations; an input with a waveform other than sine-wave will cause varying errors. An oscilloscope is useful in such cases for interpreting the voltmeter reading.

3. What is the effect of the voltmeter input impedance upon the circuit under test? If detuning and loading is to be kept to a minimum in making measurements on tuned and other high impedance circuits, the highest possible input impedance meter must be chosen.

4. Is the voltmeter range switch set for the highest voltage? The ranges are then progressively reduced until there is a sufficient deflection of the pointer to allow a convenient reading. It is conceivable that two settings of the voltage range switch may result in two different voltage readings. If the error on either range exceeds the rated accuracy of the instrument, it indicates a defect in the instrument on one of the two ranges. It must be remembered that the rated accuracy applies to full scale readings.

The higher the frequency of operation the greater the possibility of errors in excess of the manufacturer's rating. Generally speaking, accuracy ratings are a compromise. No device is absolutely flat in its

response over a wide frequency range; as the outlying portions of the frequency range are approached the greater will be the possible departure from the rated accuracy.

5. Has the position of the probe ground been altered while making r-f measurements on two voltage ranges? If so, changes in readings may be expected, first, because the difference of potential between the probe tip location and the ground point may be different due to standing waves; second, because resonance conditions are subject to change along a ground bus at high frequencies; and third, because the new "ground" may be ineffective as a ground. Signal voltages are often present at "grounded" points decreasing the effectiveness of the point as a ground. In the final analysis, the importance of such variations depends upon the criticalness of the measurement. Whenever possible, the high side of the voltmeter input system should be joined to the exact point where the voltage is to be measured, particularly at high frequencies. A very substantial difference in indication results if the input tip makes contact with the plates or the control grid of a tube rather than with the high side of the tuned circuit located in these systems. This is a very important precautionary note because many systems contain circuit elements between the tube electrodes and the tuned circuits, so that the signal voltage at the tuned circuit is not the same as will be found at the tube electrodes. When the aforementioned circuit elements are absent, it is quite satisfactory to measure at the tube electrode terminals.

One of the most important measurements for which the vacuum-tube voltmeter is particularly suitable is the r-f stage-gain measurement. The object is to find the voltage gain of an r-f amplifier stage under various conditions. Stage gain measurements may be made on a stage by itself, as in design, or with the stage as part of a circuit. The gain of a given stage may be considerably modified in an actual complete circuit by over-all regenerative or degenerative effects.

Figure 1 shows a typical setup for single-stage gain measurements. The gain is a function of the tube characteristics, operating voltages, and resonance conditions (tuned impedance) of the plate circuit. If the signal generator has a known output (calibrated in microvolts) the value of the grid voltage E_g is known and it is only necessary to measure the signal voltage across the tuned circuit by means of the VTVM. The stage gain is then the voltage across the tuned circuit as read on the v-t voltmeter divided by the grid voltage as shown on the signal generator output attenuator dial.

To explain the significance of the stage gain in terms of the circuit components, refer to the equivalent circuit of the single stage shown in Fig. 2. The grid voltage E_g is effectively multiplied by μ , the amplification factor of the tube, and this amplified signal voltage appears in series with the dynamic plate re-

Editor's Note: The above precautions and the accompanying article are abridged from chapter 12, entitled "Applications of Vacuum-Tube Voltmeters," from VACUUM-TUBE VOLTMETERS, 2nd Edition, recently published by John F. Rider Publisher, Inc. This book is a revision of the former book VACUUM-TUBE VOLTMETERS by John F. Rider.


(Continued on page 5)

Television Changes

Tele King MST14, 14TR, 17CA, 17RO, 114A, 116, 117, 117C, 117LO, 162, 516A, 516

The tuner used in these revised models is shown in the accompanying diagram. The lead from terminal 1 goes to the junction of pin 1 of V4, the 6AU6 1st video i-f, and R201. Terminal 2 goes to pin 2 of the 6AQ5 audio output tube V1.

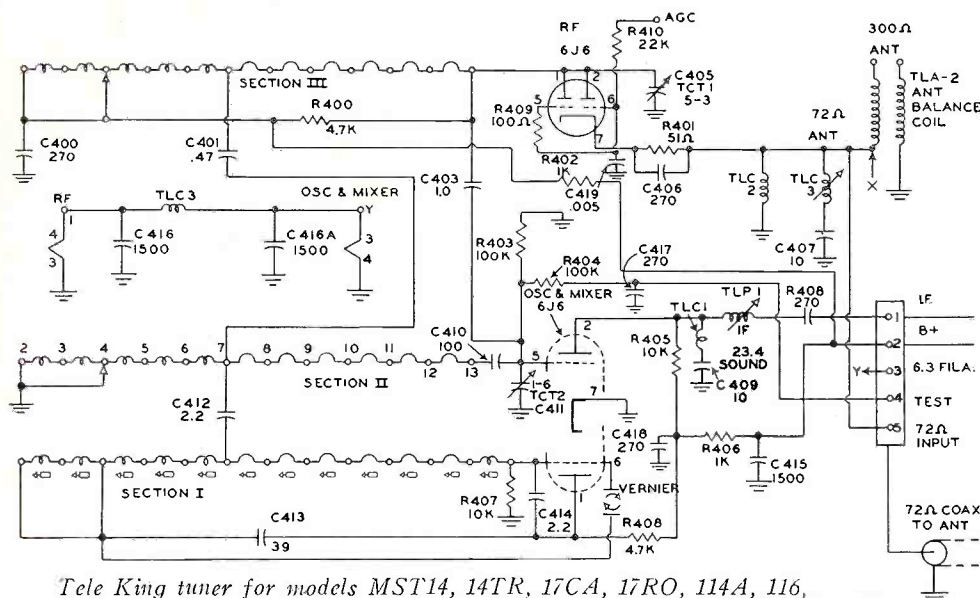has been added from ground to the junction of pin 6 of V6, L11 and R231. The 100- μ f capacitor C215 that was connected from the junction of pin 5 of V6 and L11 to the junction of L11 and pin 2 of V7 has been deleted and replaced by a direct connection. A 22,000-ohm resistor R232 has been added from the junction of pin 2 of V7 and L11 to the junction of C225 and L11. The value of C225 has been



Tele King tuner for models MST14, 14TR, 17CA, 17RO, 114A, 116, 117, 117C, 117LO, 162, 516A, 516.

The revised models contain the changes given in the following paragraphs.

The value of R201 has been changed from 10,000 ohms to 8200 ohms. In the filament circuit of V4, L5 has been deleted. R204, the 100-ohm resistor that goes from the junction (of the tuner used in early sets), has been of pin 6 of V4, L6, and R208, to terminal 3 deleted. The value of C203 has been changed from 0.002 μ f to 0.001 μ f. C205, the 0.002- μ f capacitor that went from ground to the junction of R201, R205, and terminal 1 (of the tuner used in early sets) has been deleted.

The 2nd and 3rd video i-f tubes, V5 and V6, have been changed from type 6AU6 to type 6CB6. The cathode of the 6CB6 tube is pin 2. Pin 7 of the 6CB6 is grounded. Except for these changes in pin numbers, V5 and V6 are connected as in early models. The value of resistor R207, connected to the cathode of V5, has been changed from 82 ohms to 47 ohms. Resistor R230, 330 ohms, has been inserted from the junction of pin 6 of V5, L8, and C209, to the junction of R208 and R211, replacing a direct connection between these two points. The value of resistor R209 going to pin 1 of V6 has been changed from 8200 ohms to 6800 ohms. The value of R210, the resistor connected to the cathode (pin 2) of V6 has been changed from 82 ohms to 180 ohms. The value of C211, connected in parallel with R210, has been changed from 0.002 μ f to 0.005 μ f. A 330-ohm resistor R231 has been inserted from the junction of pin 6 of V6 and L11 to the junction of R211, C213 and R214, replacing the direct connection between these two points. A 0.001- μ f capacitor C227

changed from 0.002 μ f to 0.001 μ f. The value of C213 (mentioned previously) has been changed from 0.002 μ f to 0.001 μ f.

The value of R341, connected from the focus control to the junction of the focus coil L17 and filter choke L16 has been changed from 100 ohms to 750 ohms. The 1200-ohm, 2-watt resistor R342 that was connected in parallel with focus coil L17 has been removed from the circuit. The value of C310, connected from pin 1 of V13 to T3, has been changed from 0.005 μ f to 4700 μ f, 800 v. A 0.1- μ f capacitor C342 has been added in parallel with the vertical deflection yoke L19. The primary of the width coil now goes from tap 5 (red) to tap 4 of T5 (black) instead of from tap 8 to tap 5.

DuMont RA-105, RA-106

The procedure for eliminating vertical jitter or bounce in these chassis is identical to the method suggested for Chassis RA-101B, RA-102, and RA-103, except that the last step (#9) should read "Remove resistor R340 (12,000 ohms) for Chassis RA-105 and RA-106."

It has been found desirable to use impregnated vertical blocking oscillator transformers to prevent failure of this transformer usually caused by very humid weather. The opening of the primary results in loss of vertical sync. The impregnated transformers, identified by a black wax coating on the outside, should be used whenever it becomes necessary to make a replacement.

Sylvania 5150M, Ch. 1-274; 7150M, 7160B, Ch. 1-357

The following changes have been incorporated in the 1-274 and 1-357 chassis under change codes as listed below:

	1-274	1-357
C146 from 0.1 μ f to 0.005 μ f	CO3	CO2
C147 from 0.05 μ f to 0.005 μ f	CO3	CO2
R169 from 47 ohms to 180 ohms	CO3	CO2
V13, V18 from 12AU7 to 6SN7GT	CO4	CO4
(12AU7's not available)		

Revised wiring (improves sync circuit)

CO3

Picture contrast control R168 (formerly connected to R169) is now connected directly to the -135-volt line. R169 has been re-located and is now connected from the -135-volt line to R164. The connection from C195 goes to the junction of R169 and R164.

The revised wiring changes include a direct connection from C146 to the junction of C147 and ground. C146 formerly went to the -135-volt line. A direct connection has been made from pin 2 of V8 (the 6BF5 video amplifier) to the junction of R145, R146 and C145. Pin 2 formerly was connected to the -135-volt line.

The pin connections for the 6SN7GT V13 are as follows: pin 1 goes to the junction of C170, C172 and R186; pin 2 goes to the junction of R187 and R188; pin 3 is connected as before; pin 4 goes to the agc control; pin 5 goes to the junction of R176 and C168; and pin 6 goes to the junction of R163 and R164. The connections of the 6SN7GT V18 are as follows: pin 1 goes to the junction of C200 and R223; pin 2 goes to the junction of R224, R226 and C203; R3 goes to R223 and the -135-volt line; pin 4 goes to the junction of R221 and C196; pin 5 goes to the junction of R222, C200 and L63; and pin 6 goes to T62.

In code CO1 for Chassis 1-357, the value of R192 (going to the vertical hold control) was changed from 1.5 megohms to 1 megohm. The value of the vertical hold control R193 is now 1.5 megohms instead of 1 megohm.

The change in Parts List is as follows:

Ref. No.	Part No.	Description
C146, C147	166-5000D	Capacitor, ceramic, 0.005 μ f, 450 v
R169	181-01815	Resistor, 180 ohms, 1/2 w
V13, V18	622-0005G	Tube, 6SN7GT.

Belmont Ch. 12AX26, 14AX21

Microphonic i-f amplifier tubes may cause sound bar shadings of the picture when the volume control is advanced past the normal listening level. To determine which tube is microphonic, gently tap each of the first three i-f amplifier tubes while viewing the picture. If this condition is noticed, interchange the sound i-f amplifier, agc amplifier and fourth i-f amplifier tubes with the first three i-f amplifier tubes (interchange tubes 6, 10, 11 with tubes 3, 4, 5).

Emerson 629D, 651D, 658B, Ch. 120124-B

The Emerson low capacity probe as outlined in the June issue of SUCCESSFUL SERVICING is not adaptable for use with different oscilloscopes since it cannot be calibrated.

To revise this probe, change C1 from a fixed capacitor to a trimmer capacitor which is variable from 4 μ f to 30 μ f. The value of R1 must be changed from 1.2 megohms to 1.5 megohms, 5%. The method of calibrating the revised Emerson probe can be found in service notes for Ch. 120133-B.

Radio Changes

Sears 8260, Ch. 101.823 series

The loop antenna lead wires in the front cover of the above portable have continued to break despite careful assembly and inspection at the source. An analysis of a large number of these radios on life test showed that variations in the spring tension which takes up the slack in the leads is the greatest contributing factor in these failures.

It is recommended that this spring be disconnected on every model 8260 in store stock prior to sale and delivery to the customer. The only purpose of the spring is to hold the wires taut for better appearance. The slightly different appearance of slack wires is more desirable than the potential complaint due to broken leads.

Open the back cover and find the lug in the outer case (in line with the loop leads) to which the small spring is attached. With a small screwdriver or knife bend the lug out enough to slip off the spring loop. Use a paper clip bent to form a hook, if necessary. It is not essential to remove the spring, but merely to disconnect one end as described. When this spring is disconnected the possibility of broken loop leads is reduced to a minimum.

General Electric 218, 218H

A 15,000-ohm, 1/2-watt resistor R33 has been added between the high side of the volume control and the arm of the band switch S1D. This improves receiver stability. The following changes should be made in the Parts Lists for these models:

Delete Stock No. RLI-084; Add RLI-088, Choke, f-m antenna (L2), used in 218 only; Add URD-077, Resistor, 15,000 ohms, 1/2 w, carbon.

General Electric 60, 62, 64, 65, 66, 67

The stock item RAB-054, Cabinet back and loop, is no longer available and Stock No. RAB-097, Cabinet back and loop, is substituted in its place. For those receivers produced, employing RAB-054 with connections made to the primary antenna winding, the black wire to chassis ground is removed when RAB-097 is substituted for replacement.

Sears 220, Ch. 528.173

A quantity of model 220 portable radios was shipped on which a corner boss in the cabinet body became broken. Breakage of either or both bosses released the spring (Littlefuse) clip preventing the secure latching of the back in the closed position. When this condition is found a new case (cabinetless back) should be used. Follow instructions below to prevent repetition of the same trouble.

Remove the handle from the case. Save all parts. Discard the case with the broken bosses, the support brackets and the screws that held the Littlefuse clips in place. Retain the Littlefuse clips and screws, flat washers and grommets that secured the brackets at the bottom to the rear apron of the chassis.

Replace the items that were discarded with the following new items. Order from source number 528.

Part No.	Description	Amount Required
T42-467	Case	1
T97-147	Screw - No. 4-24 x 1/2 thread cutting	2
T11-420	Bracket - chassis support	2
T47-118	Grommet - 5/16 pure gum rubber	2
T86-74	Washer - flat 3/8" O.D.	2

The new support bracket has a larger diameter hole at the top for the new grommet. The mounting screw is longer and a flat washer has been added.

Reassemble the brackets on the chassis as before, using the hardware saved from the original mounting. Place the new grommets

in the holes at the top of the brackets. When the chassis is in place, place the new screws through the holes in the Littlefuse clips saved from original installation; then place the new washer on the screw and secure the top of the bracket to the boss in the upper corner of the cabinet.

Arvin 540T, Ch. RE-278

Model 540T is the same as model 440T, chassis RE-278, except for the part numbers listed below.

Ref. No.	Part No.	Description
R3	C23068	Resistor, Volume Control, 2 meg.
C2A, C2B	A20375	Condenser, I. F. Trans. Trimmers
T2	C22878-1	Output Transformer
T1	C22863-1	I. F. Transformer
L1	C22864-1	Antenna Coil
L2	C22865-1	Oscillator Coil
—	E24328-1	Cabinet with grille cloth, Ivory
—	C24096-1	Ivory cabinet, rear cover
—	E24328-1	Cabinet with grille cloth, citron
—	C24096-8	Citron cabinet, rear cover
—	E24328-7	Cabinet with grille cloth, flame
—	C24096-7	Flame cabinet, rear cover
—	E24328-9	Cabinet with grille cloth, cherry
—	C24096-9	Cherry cabinet, rear cover
—	E24328-10	Cabinet with grille cloth, Avocado, green
—	C24096-10	Cabinet rear cover, Avocado, green
—	E24328-11	Cabinet with grille cloth, Pebble
—	C24096-11	Cabinet, rear cover, Pebble
—	A24372-1	Arvin Name—on cabinet
—	A24084	Couplate
—	A24330-1	Knob, volume
—	C24331-1	Knob, dial
—	A18136	Antenna hank

General Electric 123, 124, 125

A self-tapping screw, #4 x 1/4 inch, Cat. No. RHS-044, Shakerproof type 25, has been added to the Parts List for the above models. Cabinets of later production receivers were tapped for these screws to mount the loudspeaker in lieu of the Tinnerman clip, RHM-061, used in earlier speaker mountings.

Gamble-Skogmo 43-9841A

Model 43-9841A is the same as Model 94RA31-43-9841A.

Regal 7151

Model 7151 is electrically the same as Model 205.

RIDER TV 7


Off The Press!

Factory-authorized service data!

All production runs and changes to Summer 1951!

Equivalent of 2,352 pages (8 1/2" x 11")


Cumulative index TV Volumes 1 through 7

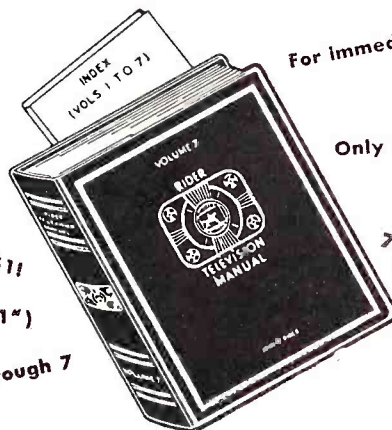

For immediate bench use

Only \$24.00

74 manufacturers represented

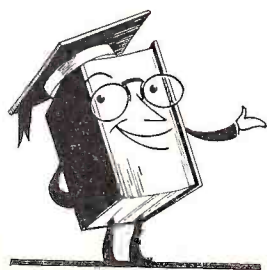

Rider Manuals
mean
Successful Servicing

Nobody but Rider gives you

Complete manufacturers' parts lists
Complete manufacturers' alignment data
Circuit action descriptions
Signal waveforms for trouble shooting

RIDER BOOKS

The Standard of the Industry

Accurate, — Authoritative, the first guide to better servicing . . . higher profits.

Receiving Tube Substitution Guide Book

by H. A. Middleton

For AM-FM-TV Receivers and Allied Equipment

2500 Tube Substitutions . . . TV Rec. filament wiring . . . Heater Sub. wiring instructions . . . Tube types classified by functions . . . Cathode-Ray Tube Characteristics; Ballast Tube data; Resistors . . . Capacitors . . . Transformer . . . Color codes; and a wealth of other vital data. 224 pp. Heavy paper cover 8½ x 11. \$2.40

Broadcast Operator's Handbook

by Harold E. Ennes

The co-ordinated facts . . . Result in a general set of rules that serve as standards of good operating practice. 288 pp. 5½ x 8½ illustrated. \$3.30

TV, Master Antenna Systems

by Ira Kamen and Richard H. Dorf

Explains the workings of the fast-growing master antenna field . . . Provides the practical knowledge for installation, maintenance and usage for apartment buildings . . . hotels . . . hospitals, etc. . . 368 pp. 234 ill. Cloth Bound. . . . \$5.00

TV Installation Techniques

by Samuel L. Marshall

A "must" for difficult installations . . . Know ice loading, wind surface, mounting requirements . . . plus accurate data on receiver adjustments in the home; municipal regulations governing antenna installations . . . 336 pp. 270 ill. 5¾ x 8¾. Cloth Bound. . . . \$3.60

Encyclopedia on Cathode-Ray Oscilloscopes and their uses:

by John F. Rider and Seymour D. Usan

Everything you should know about the scope . . . What it is; What it can do; How to use it, Told practically and informally . . . Over 70 models described . . . complete with specifications and wiring diagrams . . . 992 pp. 3,000 ill. 8½ x 11 completely indexed. Cloth Bound. . . . \$9.00

TV and Other Receiving Antennas Theory and practice

by Arnold B. Bailey






Tells you the function of each type; How to use it; which is best . . . The best Antenna Authority in the field . . . Easy to read because mathematics are translated into charts and graphs. 606 pp. 310 ill. . . . \$6.00

Vacuum — Tube Voltmeters

by John F. Rider

New, Revised 1951 Edition

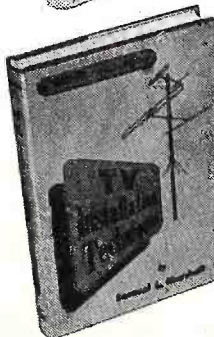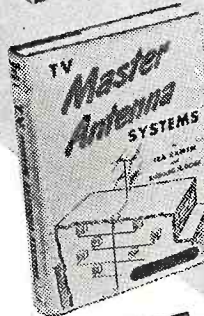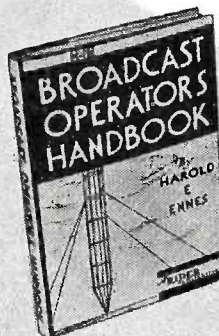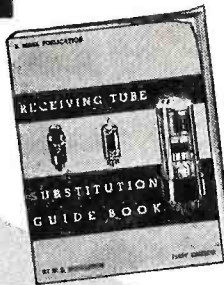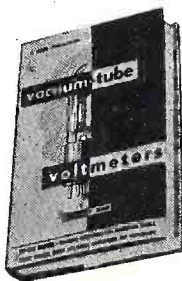Covers all types of voltmeters . . . diode, triode, rectifier-amplifier, tuned, amplifier-rectifier, and slide-back . . . Bibliography of more than 200 listings and comparative tabulations of operating characteristics are included . . . Written for practice with emphasis on field conditions . . . Review questions each chapter . . . 432 pp. 5½ x 8½. 215 ill. \$4.50



SEND FOR COMPLETE CATALOG ON ALL RIDER BOOKS



JOHN F. RIDER PUBLISHER, INC.

480 Canal Street

New York 13, New York

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

AUGUST, 1951

No. 10

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
H. YUSEM, Associate Editor

Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.

Worth 4-8340
Worth 4-8341



AMPLIFIER STAGE MEASUREMENTS

(Continued from page 1)

sistance, R_p , and the tuned circuit L-C. At resonance, the plate load L-C is equivalent to a resistance having a value of $2\pi QLf$, and the signal current, I , around the loop will be μE_g divided by $R_p + 2\pi QLf$. The signal voltage across the tuned circuit at resonance will be $2\pi QLf \times I$ (the signal current times the load of the tuned impedance), and the stage gain will be this output signal voltage divided by E_g , the input signal voltage:

$$\text{Stage Gain} = \frac{2\pi QLfI}{E_g} = \frac{2\pi QLf\mu}{R_p + 2\pi QLf}$$



Fig. 2. Equivalent circuit of a single r-f amplifier stage.

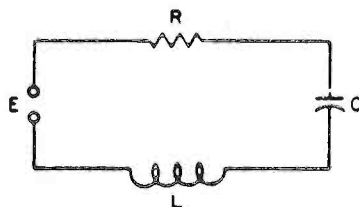


Fig. 3. Series-tuned circuit with R , C and L components. At resonance, the total impedance equals R .

While the stage gain is always taken at resonance, that is, with L-C tuned to the frequency of the signal generator output, the off-resonance gain may also be measured. A resonance curve will give both the resonance and off-resonance gain.

The gain of a stage is a function of the Q values of each of the tuned circuits in the stage. To understand the resonance curve it is necessary at this point to discuss the factors upon which the Q of a tuned circuit depend.

For series-tuned circuits of the type shown

CURTAIN TIME

Since Mr. Rider is on vacation, his customary editorial, "Curtain Time," does not appear this month.

in Fig. 3, when resonance is reached, X_L , the inductance reactance, equals X_C , the capacitive reactance, so that the impedance of the circuit is R . At this value the current in the circuit is greatest, for as the frequency changes, the balance between X_L and X_C is destroyed and the total impedance consists of R plus some value of reactance as is seen from the following equation for the impedance of a series circuit:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

where Z is the total impedance of the circuit.

Since the current at resonance is largest, the voltage drop across L and C will be largest. (The total effect of the voltage drops is zero since they are 180° out of phase, so that only the voltage across R , equal to the applied voltage, is effective.)

Q is defined as the ratio of reactance to resistance in a series circuit at resonance. The reactance is equal to:

$$X_L = \frac{E_L}{i_{res}}$$

where X_L is equal to the inductive reactance at resonance.

E_L is equal to the voltage across the inductance at resonance.

i_{res} is the current flowing in the circuit at resonance.

The resistance is:

$$R = \frac{E_R}{i_{res}} = \frac{E}{i_{res}}$$

where E_R is the voltage across R at resonance and is equal to the applied voltage E .

Q , therefore, may be found from the following equations:

$$Q = \frac{X_L}{R}$$

(Continued on page 6)

GOOD NEWS FOR SERVICING BLUES

RIDER'S TV 7

IT'S A GOOD THING WE HAVE RIDER TV MANUALS FOR THIS JOB—IT'S THE MANUFACTURER'S 3rd PRODUCTION ON THE CHASSIS AND RIDER HAS THE MODIFIED SCHEMATIC AND ALL THE DATA!

YEAH, NOW WE DON'T HAVE TO WASTE TIME DOPING IT OUT OURSELVES—THE MANUFACTURER MADE A HEAP OF CHANGES ON THIS PRODUCTION RUN AND RIDER TV MANUALS IS THE ONLY SOURCE THAT PUBLISHES IT!

THERE'S NO GETTING AWAY FROM IT—IF YOU WANT COMPLETE SERVICE DATA, THE PILOT MODEL SCHEMATIC AND ALL THE CHANGES, NOBODY BUT RIDER GIVES IT TO YOU!

THAT'S SO—RIDER TV MANUALS IS THE ONLY SOURCE OF SERVICING DATA SO SPECIALIZED TO HELP YOU DO FASTER—EASIER—MORE PROFITABLE TV SERVICING—COMPARE RIDER'S WITH ANY OTHER SERVICE DATA AND PROVE IT YOURSELF!

RIDER TV MANUALS—BEST BY TEST—GET TV 7 NOW!

AMPLIFIER STAGE MEASUREMENTS

(Continued from page 5)

$$Q = \frac{\frac{E_L}{i_{res}}}{\frac{E}{i_{res}}} = \frac{E_L}{E}$$

Since X_L is equal to $2\pi fL$ we get from the last equation:

$$E_L = EQ = E \frac{2\pi fL}{R}$$

From these equations we see that the Q of a tuned circuit increases as the resistance of the tuned circuit decreases. Also, if the applied voltage is held constant, and the frequency is varied, the voltage across the inductance will vary as shown in Fig. 4. This is a resonance curve for the L - C circuit. Note how sharply the voltage rises for a small difference in frequency about the resonance frequency. The higher the Q value of the circuit, the sharper is this rise.

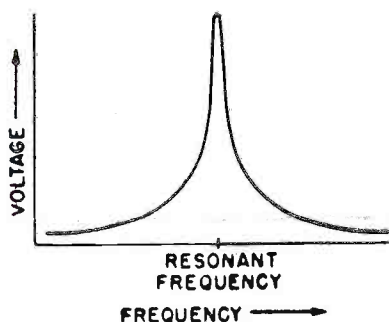


Fig. 4. Graph showing the variation of voltage across L in Fig. 3 with the frequency of the input voltage.

For parallel circuits of the type shown in Fig. 5, the current flow is smallest at resonance. (This is so because at resonance $X_L = X_C$ so that the only branch drawing current is R .) This may be expressed in another way by saying that the impedance of the circuit is greatest at resonance. Actually, if we plotted the impedance of the circuit vs. the frequency, we would obtain an impedance curve of the kind shown in Fig. 6. Any parallel L - C circuit, with or without a resistance branch will give the same type results as those described for the circuit of Fig. 5. To actually plot an impedance curve, we measure the voltage across the circuit and the current in

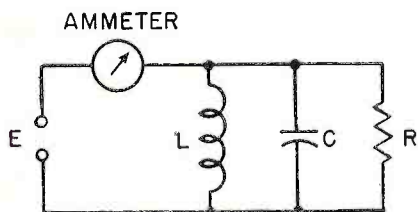


Fig. 5. Parallel-tuned circuit. At resonance only R draws appreciable current while the L - C combination offers maximum impedance.

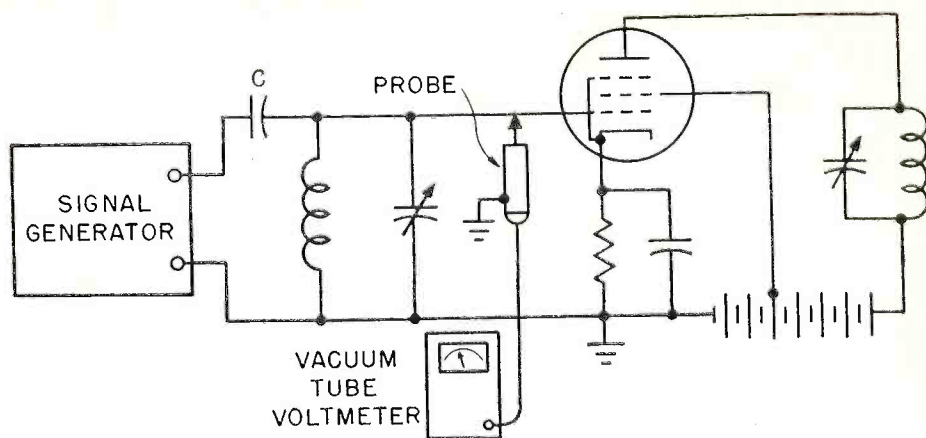


Fig. 7. Test setup for measuring the regenerative rise of an r-f amplifier. This effect is one of the causes of oscillation in amplifiers.

the circuit for various values of frequency. For parallel circuits, the higher the Q value, the sharper the impedance curve.

Since for both types of circuits, the gain is a function of the Q value, we see that the selectivity curves (which are plots of the gain of a stage versus the frequency of the signal output), will be roughly similar to the resonant impedance curves of the tuned circuits of the stage.

The selectivity of the single stage is obtained by measuring the gain for several frequencies as the generator frequency is varied above and below resonance. The effect of the cathode, screen and plate voltages on the stage gain may be found by varying these voltages independently.

In making these measurements, the probe is usually connected from the high side of the plate load circuit to ground as shown in Figs. 1 and 7. This places a considerable d-c voltage across the probe. If therefore, the probe input coupling capacitor has leakage, an initial reading will be observed on the voltmeter with no signal present. If the reading is small, it may be corrected by resetting the voltmeter zero adjust. If it is large, a low leakage capacitor should be placed in series with the probe input, or the probe capacitor should be changed.

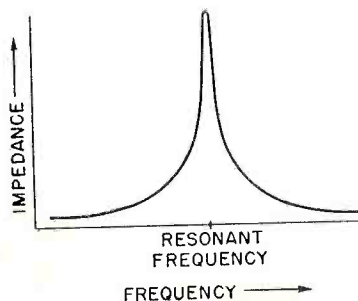


Fig. 6. An impedance vs. frequency curve for the circuit in Fig. 5. The steepness of the curve about the resonant frequency depends on the Q of the circuit.

In making stage gain and selectivity measurements, care should be taken not to over-

load the tube. This may be especially important when a calibrated signal generator is not available and gain is obtained by measuring E_g and L - C voltages with a voltmeter. A good rule to follow is never to allow the peak of the signal voltage on the grid to exceed the cathode or grid steady-bias voltage.

The above technique applies as well to gain measurements in a mixer or converter stage, except that a second r-f signal is required in the case of the mixer to represent the local oscillator voltage.

Another important design factor which may be measured by means of the stage gain setup is called "regenerative rise." When both plate and grid circuits of an amplifier stage are tuned to the same frequency there may be feedback which causes the gain to increase above that normally expected in the stage. It is more useful to look at this as an increase in grid signal voltage due to tuning the plate circuit. The ratio of this voltage increase to the initial signal voltage on the grid is then the regenerative rise. If the rise voltage is greater than the initial signal voltage, that is, if the ratio is greater than 1, the stage will oscillate. A conservative design, for example, might dictate that the regenerative rise be not more than 20 per cent (or 1:5).

Figure 7 shows the circuit for measuring regenerative rise. Tuned circuits are placed in series with both the plate and the grid. The signal generator is loosely coupled to the grid circuit through a small capacitor C (of the order of $2\mu\text{f}$). The VTVM is placed across the signal-grid tuned circuit which is tuned to the frequency of the signal generator. The signal voltage at the grid is noted. Then the plate circuit is tuned to resonance and the increase in signal voltage at the grid is observed. This increase divided by the amplitude of the original signal is the regenerative rise.

The measurements outlined above as well as others may be made in actual circuits utilizing r-f amplifier stages as in radio and television receivers. Care should be taken when making such measurements that short leads are used to connect the v-t voltmeter probe to the

circuit under test, and that the voltmeter input connecting lead does not increase regenerative coupling effects in the circuit. For accurate measurements, the circuit across which the probe is connected should be tuned with the probe connected, and returned after the probe is removed.

A typical outline for the measurement of stage-by-stage gain for an a-m receiver follows:

1. Connect an unmodulated signal generator to the antenna terminals of the set.

2. Adjust the signal generator for maximum voltage output. A generator output of at least 0.1 volt is desired for satisfactorily determining the gain of the first r-f stage.

3. Tune the receiver to the signal generator. Short out the receiver avc.

4. Set the v-t voltmeter range switch to the most sensitive scale in the a-c range, the selector switch to "A-C Volts."

5. With the probe shell grounded, measure the voltage at the plate of the r-f tube. Similarly, measure the grid voltage of the r-f tube. The ratio of the voltages gives the gain of the r-f stage, as previously stated.

6. Reduce signal generator to zero output and check receiver oscillator voltage at oscillator grid and plate, and at converter tube injector grid.

7. Restore signal generator to output level which gives readable signal level at r-f tube plate. Measure the signal generator output voltage and voltage at converter tube plate. The ratio of these voltages is the conversion gain of converter tube.

8. Measure voltage at the plate of first i-f tube. This voltage is divided by the voltage at the plate of the converter tube for the stage gain.

9. Repeat for succeeding stages, reducing signal generator output to keep from overloading stages under test or adjacent stages, since avc is not operating.

10. Restore avc voltage.

As an example of what may be expected in the r-f portion of a small ac-dc receiver, the following figures are given. With 0.1 volt of rf fed to the receiver thru a standard IRE dummy antenna, the avc on the control grid of the 12SA7 tube was 5.8 volts dc. Rf appeared on the various tubes as follows:

12SA7 converter grid	0.13 volts rf
12SA7 converter plate	0.7 volts rf
12SK7 i-f grid	0.2 volts rf
12SK7 i-f plate	6.4 volts rf
12SQ7 diode plate	3.6 volts rf

These figures will, of course, vary with different receivers and circuits, but in general, a minimum of 3 volts should always be found at the diode plate of the second detector.

For triode-detector circuits, the gain may be found from the following equation:

Gain =

$$\frac{\text{Audio Output Voltage across Detector Load}}{\text{Input Carrier Voltage} \times \% \text{ Modulation}}$$

(Continued on page 8)

Service Hints

Belmont

Improper dressing of the 1X2 filament leads may cause frequent 1X2 tube failures or poor high-voltage regulation (blooming, picture expansion as brightness or contrast is increased). The 1X2 filament leads should be dressed as far away from the coil as possible. The leads should overlap and be tight against the terminal board. Coil dope should be used to secure the leads in place. The coil leads to terminals 1, 2, 4, and 6 should be dressed as far away from the filament leads as possible.

Video buzz can be eliminated by simply following the instructions listed below:

1. Dress the white leads from the volume control switch as close to the chassis as possible.

2. Dress the green lead from the center tap of the volume control as far away from the switch as possible.

3. Adjust the sound pick-off coil for maximum gain.

4. Adjust the ratio detector coil, both primary and secondary for maximum sound and minimum buzz.

5. Adjust the video trap coil L19 for minimum buzz and smooth continuous horizontal scanning lines. This coil when misadjusted will cause video buzz and "sand" in the picture.

6. Video buzz may also be caused by a defective audio detector tube or capacitor C-83.

If the sound and picture do not come in simultaneously, adjust i-f transformer T-1 manually until both the sound and picture come in together.

If resistor R97 is open or partially opened,

a squegging condition may occur. If the 0.002- μ f capacitor (C105) is open, the effects will be a shaky or saw-tooth pattern. Low high voltage and a narrow raster can be caused by either an open 0.25- μ f capacitor (C114) or an open mica capacitor across terminals 1 and 3 of the horizontal deflection transformer in the 14AX21 chassis. If the agc windings are reversed or defective the symptoms will be either poor or no horizontal sync.

Belmont

The following adjustments listed below are suggested for the improvement of reception for those sets to be used in the fringe area. The adjustments are to be made only on the 16 and 17 inch sets which will be used in the fringe area. If this adjustment is made in the local signal area a definite decrease in picture quality will be noticed.

1. A-13A-19514 sound pick-off coil (T-8) must be in set. If not, change.

2. Turn 2nd (L-12) and 4th (L-14) i-f coil cores $\frac{1}{4}$ turn into coil.

3. If the above step does not produce enough improvement follow steps 5, 6 and 7.

4. If the sound pick-off coil was removed and the A-13A-19514 coil was added, follow steps 5, 6 and 7.

5. Peak the sound pick-off coil (T-8) for maximum sound.

6. Adjust the ratio detector (T-2) primary (bottom of coil) for maximum sound.

7. Adjust the ratio detector (T-2) secondary (top of coil) for best noise rejection.

The above adjustments are *not* to be used on the 20 inch sets.

WE STILL NEED YOUR HELP!

We want to make **SUCCESSFUL SERVICING** of greater value to all its readers. We plan to reorganize the contents to best suit your requirements. We need your help!

In order to plan a magazine that is most useful to you, we need to know how many of our readers own **RIDER TV MANUALS**. If you have not already done so, please indicate on the coupon below *whether or not* you own **RIDER TV MANUALS**. Just paste the coupon on a penny postcard and return it to us. Regardless of how you fill it in, you will continue to receive **SUCCESSFUL SERVICING**.

This is *your* magazine. Help us make it most useful to *you*. Our sincere thanks for your cooperation.

MAIL THIS COUPON NOW

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street — Dept. 55
New York 13, N. Y.

Gentlemen:

I have the following **RIDER TV MANUALS** in my servicing library (please circle those you own)

RIDER TV MANUAL 1 2 3 4 5 6 7

I do not own **RIDER TV MANUALS** ☐

own shop ☐

full-time employee ☐

other ☐

NAME _____

ADDRESS _____

CITY _____

ZONE _____ STATE _____

AMPLIFIER STAGE MEASUREMENTS


(Continued from page 7)

Stage-by-stage gain measurements for f-m receivers are made in the same way as those described above for a-m receivers, since the sets are similar up to the limiter and discriminator. F-m i-f circuits will probably be found to be less sensitive to detuning caused by the application of the r-f probe.

For each measurement be sure that the shell of the r-f probe makes contact with the receiver chassis, or that it is connected to the

chassis by an alligator clip, or short lead.

It is not always appreciated that while the vacuum-tube voltmeter is a high impedance device, its input capacity should not in many cases be neglected. As an illustration, a probe having an input capacitance of $5 \mu\text{f}$ was placed across a tuned circuit with a $200\text{-}\mu\text{f}$ capacitor, a Q of 160, and a resonant frequency of 600 kc. The probe caused a drop in voltage due to detuning of 73 per cent. When the circuit was returned, however, with the probe as part of the circuit, the error introduced was of a minor magnitude.

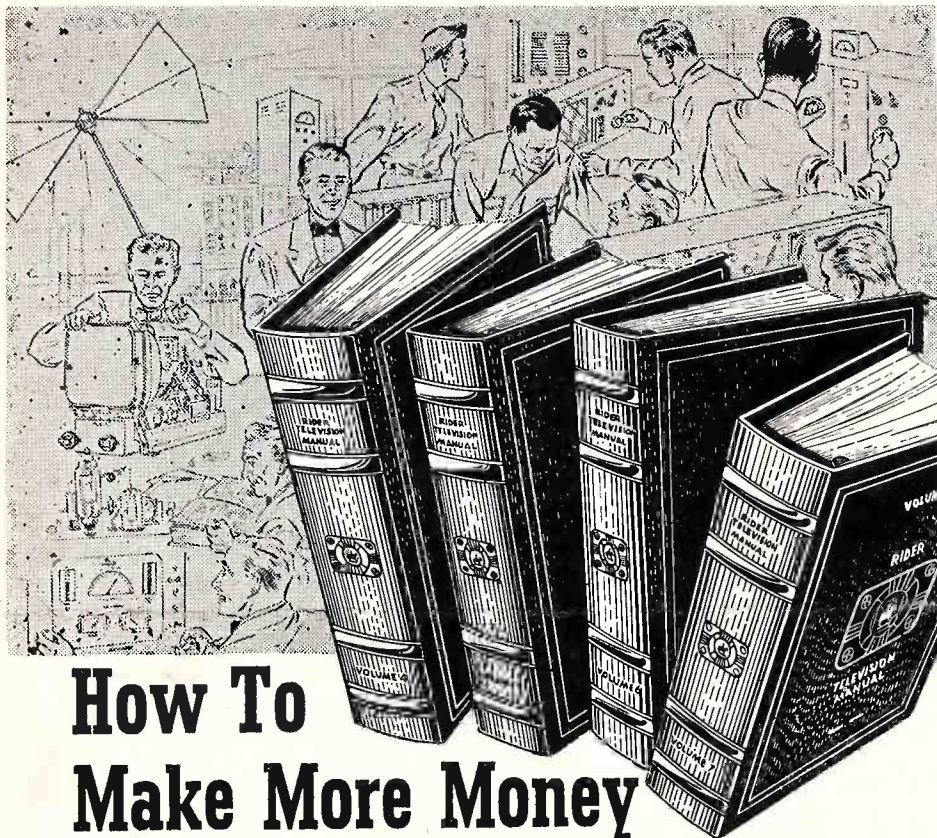

How To Make More Money

Take less time per call...do a better job. The secret is knowing the complete, accurate, factory-approved answers to every Television and Radio problem. There's only one source for this staggering amount of information...Rider TV Manuals. The only complete television and radio manuals in the world. You'll find that dollar-for-dollar, page-for-page the Rider manual is far less expensive than any other source... and far more valuable for you. Ask your jobber for TV 7



JOHN F. RIDER Publisher, Inc.
480 Canal Street, New York 13, N. Y.

Successful Servicing, August, 1951

INDEX OF CHANGES

Model	Page Number		
	Successful Servicing	Rider Manual† From	To
TELEVISION CHANGES			
Belmont 12AX26, 14AX21 Service Hints	2 7	5-9	5-20
DuMont RA-105, RA-106 RA-105	2	2-5 *2-5 C3-1 C4-2 C7-2	2-33 *2-55, 56 — — —
RA-106		2-34 *2-57 C3-1 C4-2 C5-1 C7-2	*2-58 — — — —
RA-101B		2-1 *2-1, 2 C6-2	2-4 *2-3, 4 —
RA-102		*1-34 C6-2 *1-58	*1-57 — 1-80
RA-103		C3-1 C6-2 C7-1	— — C7-2
Emerson 629D, 651D, 658B	2	5-27 C6-2	5-31 —
Sylvania 5150M, Ch. 1-274; 7150M, 7160B, Ch. 1-357	2	6-18	6-36
Tele King MST14, 14TR, 17CA, 17RO, 114A, 116, 117, 117C, 117LO, 162, 516A, 516	2	5-12 C7-3	5-20 —

RADIO CHANGES

Arvin 540T, Ch. RE-278	3	21-3	21-5
Gamble-Skogmo 43-9841A	3	20-48	20-51
General Electric 218, 218H	3	21-4 21-10 Page 14, May issue of Successful Servicing	21-9 21-11 20-15
123, 124, 125	3	20-13 C21-2 C21-3	20-15 — —
60, 62, 64, 65, 66, 67	3	17-16 20-3 20-9 C21-2	17-18 20-8 20-12 —
Regal 7151 205	3	19-7	—
Sears 8260, Ch. 101.823 series	3	16-6	16-8
220, Ch. 528.173	3	21-12	21-14

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the $8\frac{1}{2}$ " by 11" page size Manual only.


The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

Sec. 34.66, P. L. & R.
U. S. POSTAGE
PAID
NEW YORK, N. Y.
PERMIT No. 9427

H. W. HOOPS, 3RD
3 HALSTED ST.
VERONA, NEW JERSEY

From
JOHN F. RIDER PUBLISHER, Inc.
480 CANAL ST., NEW YORK 13, N. Y.
Forwarding and
Return Postage Guaranteed

SEPTEMBER, 1951

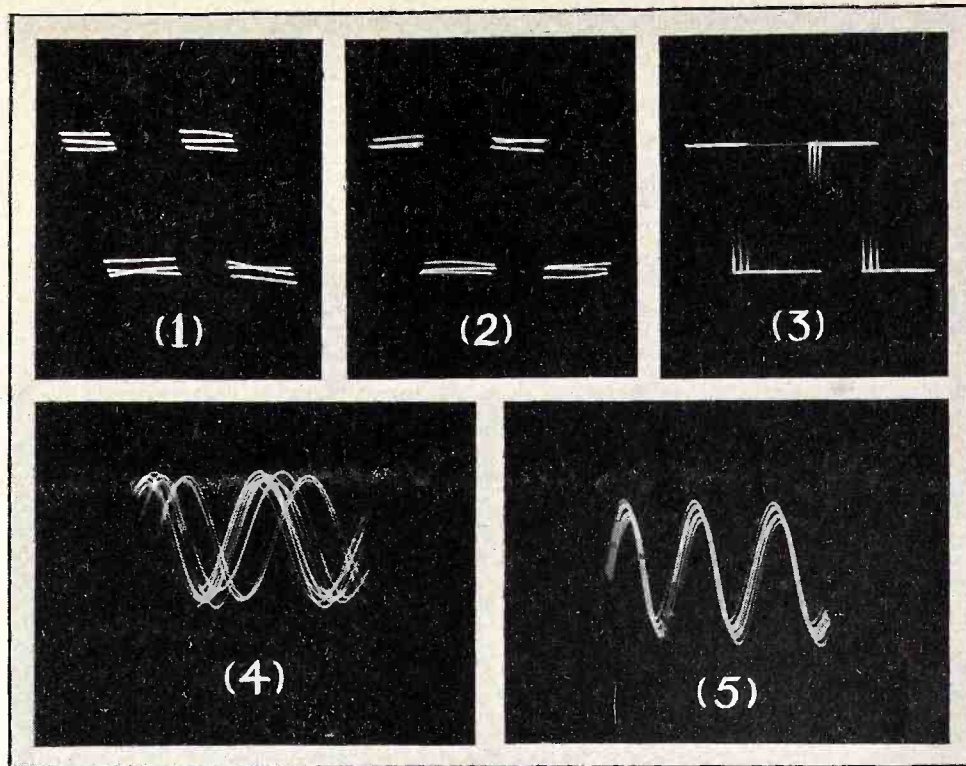

DISTORTION OF SCOPE TRACES

BY JOHN F. RIDER

Every so often conditions of operation result in distorted test oscilloscope traces, interfering with the application of the scope and proper interpretation of the pattern.

When this happens, it is not necessarily because anything is wrong with the equipment being checked, or with the test oscilloscope; quite often the difficulty lies in the physical arrangement of the test setup and the behaviour of some of the equipment.

It therefore becomes necessary to recognize the possible origin of the distortion by proper interpretation of the trace. Included here are several scope patterns extant under certain conditions of test. In each instance the remedy is simple, but unless the cause is known, the cure cannot be effected.

All scopes are contained inside metal cabinets. The cathode-ray tube is usually mounted within a high permeability metal shield to protect the electron beam from external fields. This arrangement is effective, but at times not sufficiently so to keep the trace free from external influences.

It is quite natural for current-carrying transformers to be in the proximity of a test setup. These may vary from small to large voltage regulating units, and can cause surprisingly strong fields which will materially effect the electron beam inside the scope.

Patterns 1, 2 and 3 show the effects of a transformer carrying several amperes of current which was located near a cathode-ray scope while tests were being made on square


waves. Pattern 1 shows the effect of the external field when the transformer was located on top of the scope cabinet. Pattern 2 shows the effect when the transformer was located adjacent to the scope cabinet, all other conditions remaining the same. (Both of these locations for auxiliary equipment are commonplace when bench space is not too plentiful.) When the transformer in the latter instance was rotated by 90° the trace shown in pattern 3 resulted.

The a-c field issuing from the transformer resulted in the multiple traces of patterns 1 and 2, with evident vertical displacement. In addition, the sinusoidal nature of the current responsible for the field caused the curvature in the flat portions of these traces. In the case of pattern 3 a multiple trace also occurred, but was not very obvious because in this instance the displacement was horizontal. The horizontal traces overlap each other and therefore can only be detected by careful observation of the retraces of the square wave in this pattern. (The traces appearing in pattern 3 have been made more obvious by retouching.)

Similar effects displayed on a sine wave trace are shown in patterns 4 and 5. In the former the displacement is in the horizontal direction, in the latter, in vertical.

Pattern 6 is a reference pattern for a square

(Continued on page 24)

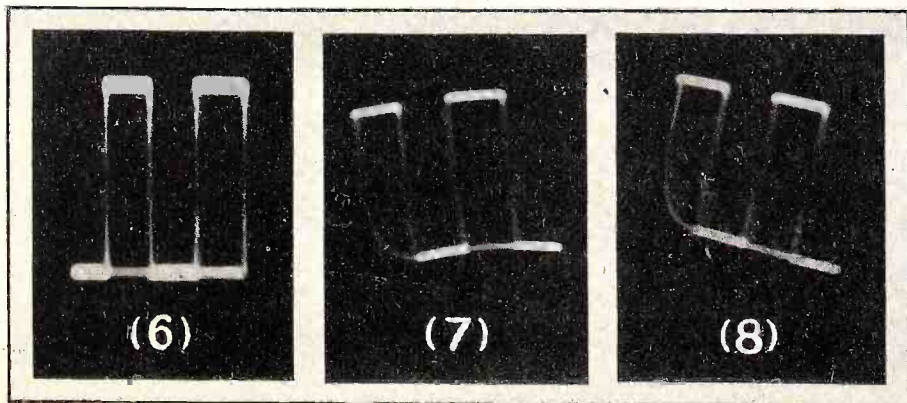

INTERCARRIER RECEIVER NOISE:

CAUSES AND CURES

by Bob Middleton

Buzz May Be Caused by Faulty Station Transmission

In a few cases, intercarrier TV receivers produce buzz in the sound because of technical difficulties at the transmitter. To check this possibility, tune in another channel to see if the buzz persists. If the buzz disappears, the trouble may be due to faulty transmission. But it may also be caused by receiver overloading on the first channel, as explained below.

Check the Latest Service Data for the Receiver

Receiver manufacturers frequently issue supplementary service data which includes minor design changes for eliminating or minimizing buzz. For example, instructions may have been issued for the addition of a large electrolytic capacitor between the screen of the audio output tube and ground; insertion of a series resistance capacitance network between the output of the AGC tube and ground; a high-frequency decoupling network in the filament circuit to the r-f tuner; change of grounding points; reversal of capacitor

connections to reverse the outer foil; or a change in capacitor values.

These design changes are representative and they emphasize the absolute necessity of checking the latest factory service data before work is started.

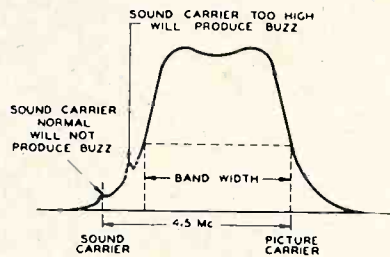


Fig. 2. Picture and sound carrier positions.

Is the Receiver Overloading?

Buzzes are generated in intercarrier receivers when the input signal is excessive. Make sure that the AGC system is working, and that all capacitors and resistors in the AGC circuit are O.K. Some receivers have an attenuator pad at the antenna terminals, and the antenna should be connected to the attenuator if the signal level is high. (See attenuating pad in upper left corner of figure 5 at end of article.)


Investigate the Operation of the Volume Control

Buzz may or may not change in intensity, when the volume control is turned. This test is valuable in localizing the injection point of the buzz. If the buzz does not change in level, it is evidently getting into the audio section at a point following the volume control.


Most Buzz Is Tunable

Observe whether the buzz or hum persists when the TV station is not tuned in. If so, the problem is greatly simplified because the buzz must then originate in the vertical sweep circuit, power supply, or heater string. Vary the vertical-hold control to see whether the buzz changes in pitch; if so, the vertical-deflection circuits are the source of buzz; if not, the filter sections and the heater circuits must be investigated.

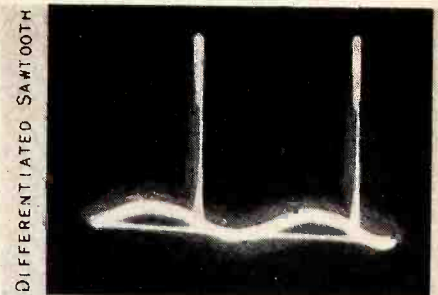However, if the buzz is tunable, the source can be in the tuned circuits, such as the r-f tuner, i-f amplifier, or the 4.5-Mc sound amplifier. The source can also be in the video amplifier or in the sync circuits. Accordingly, tunable buzz is much more difficult to localize than untunable buzz.



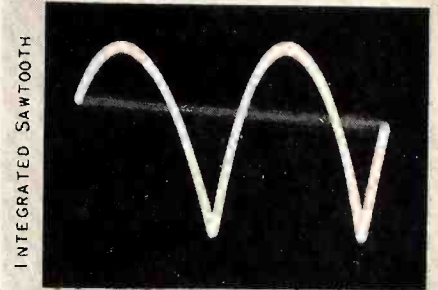TYPICAL BUZZ AND HUM WAVEFORM. PRODUCES HARSH RASP IN SOUND



TYPICAL BUZZ AND HUM WAVEFORM. PRODUCES LESS HARSHNESS IN TONE

Fig. 3. Typical buzz waveforms.

Discriminator, Ratio Detector, or Gated-Beam Detector

First tune in a weak signal, and tune for maximum volume. Then tune in a strong signal, and tune for minimum buzz. The primary of the discriminator and ratio-detector transformers controls the volume, while the secondary controls the buzz. Note that in the case of gated-beam detectors, the bias (or buzz) control should be set for minimum buzz during alignment. The buzz control is a part of the limiting system, which clips the 4.5-Mc signal to eliminate amplitude modulation.


In the case of a discriminator circuit, limiting is accomplished by a separate limiter stage; check the dc voltages of this stage, as incorrect electrode potentials will cause faulty limiting.

Ratio detectors accomplish limiting by virtue of the large electrolytic capacitor connected across the ratio-detector load resistors. Check this capacitor.


Any of these limiting circuits can be tested for a.m. rejection by applying a modulated 4.5-Mc signal to the sound-takeoff point of the receiver, and listening to the output from the speaker with the volume control set to maximum.

If a.m. rejection is found throughout the sound i-f band, the limiter section can be dismissed. On the other hand, if rejection is not complete throughout the band, it is well to check the electrode potentials of the limiter tube against the manufacturer's service data.

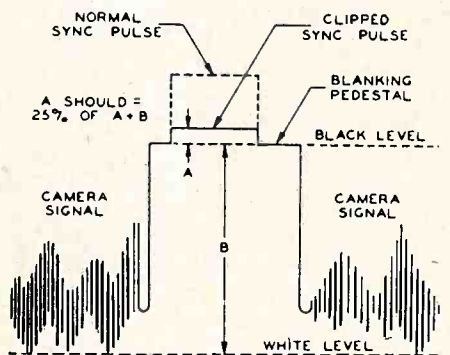The operation of the limiter can be more closely checked with the use of a vacuum-tube voltmeter and diode probe. With this



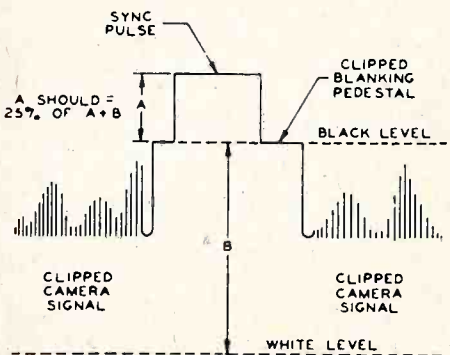A. TYPICAL WAVEFORM CAUSED BY SYNC PULSE LIMITING IN EITHER VIDEO-IF OR VIDEO AMP.



B. TYPICAL WAVEFORM CAUSED BY CAMERA SIGNAL LIMITING IN VIDEO AMP.

Fig. 1. Typical waveforms caused by limiting action.

tool, the output of the limiter tube can be measured as the r.f. input from the generator is varied.

Clipping or Limiting in the Video and Video-i-f Amplifiers

It should be understood that the i-f amplifier can cause buzz when unwanted clipping or limiting occurs. All intercarrier type receivers are provided with AGC circuits to avoid this possibility.

The best way to check for limiting is to observe the composite video signal at the sound-takeoff point with a good oscilloscope. Watch the waveform for evidence of clipping, as shown in Figs. 1A and 1B.

Common causes for sync pulse limiting (Fig. 1A) are:

1. Overloading due to excessive antenna signal.
2. Overloading due to faulty AGC circuit.
3. Overloading due to inadequate plate or screen voltages on i-f tubes.

Common causes for camera signal limiting (Fig. 1B) are:

1. Excessive output from picture detector.
2. Incorrect bias on video-amplifier tubes.
3. Incorrect plate and screen voltages on video-amplifier tubes.

Note: Limiting is required in the 4.5-Mc sound section to remove amplitude modulation. *But*, limiting must be avoided in the picture i-f amplifier, or in the video amplifier, to minimize introduction of buzz modulation.

I.f. or L.f.-R.f. Alignment Difficulties

Buzz can be caused by a misaligned i.f. or i.f.-r.f. system, causing the sound carrier to ride too high on the response curve. If this

cause is suspected, use a sweep-signal generator, marker generator, and scope to check

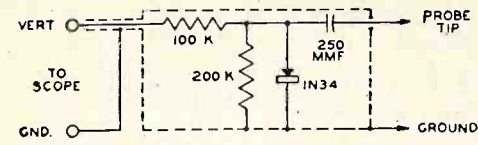


Fig. 4. High-frequency signal tracing probe.

the response curve. A response of the form shown in Fig. 2 will not produce buzz. However, the local oscillator must operate at the correct frequency to beat-in the carriers at the proper points. Touch up the local-oscillator trimmer, as required. In rare cases, the r-f tuner distorts the over-all response curve sufficiently to produce buzz; in such cases, realign r-f coils as required.

Remove Tubes Progressively for Further Clues

To localize the source of the buzz from a different angle, remove the vertical-oscillator tube, and observe whether the buzz disappears. Then replace the tube, and remove the video output tube, observing whether the buzz disappears. If tube removal cures the trouble, study the circuit diagram to see why.

Note: In the case of receivers utilizing series filament strings, you will have to maintain filament continuity by using dummy tubes having all but filament pins clipped off.

Analyze the Waveshape of the Buzz with a Scope

A scope is very useful, not only to trace the buzz through the circuits, and sometimes to localize the source by this means, but also to display the waveshape of the buzz. This waveshape is frequently important, because

New to SS Readers

These trouble shooting data are abridged from a forthcoming TV Troubleshooting Guide Book which we shall announce in the October issue of *SUCCESSFUL SERVICING*. This is a brand new type of book relating to television servicing. Nothing like it has ever been written before!

JOHN F. RIDER PUBLISHER, INC.

the shape is a clue to the kind of circuits the buzz is traveling through.

Fig. 3 shows the result of stray coupling effects such as that which occurs between volume control leads and vertical sweep leads. Various values of resistance and capacitance in the TV circuits produce varying degrees of wave shaping.

How to Check the 4.5-Mc Amplifier

The envelope of the 4.5-Mc signal should be fairly uniform, without any sudden large pulses or dips. To check whether the buzz is entering with the 4.5-Mc signal, an oscilloscope is most useful. However, most service scopes will not respond to an input frequency of 4.5-Mc, and therefore a detector probe must be used to make this test. Probe details are shown in Fig. 4.

To get the "feel" of this device, observe the waveform in the 4.5-Mc amplifier of a receiver in normal operating condition. Then compare the waveform in the 4.5-Mc amplifier of the receiver which has buzz in the sound. The high-frequency signal-tracing probe will show immediately whether the buzz voltage is present in the 4.5-Mc amplifier.

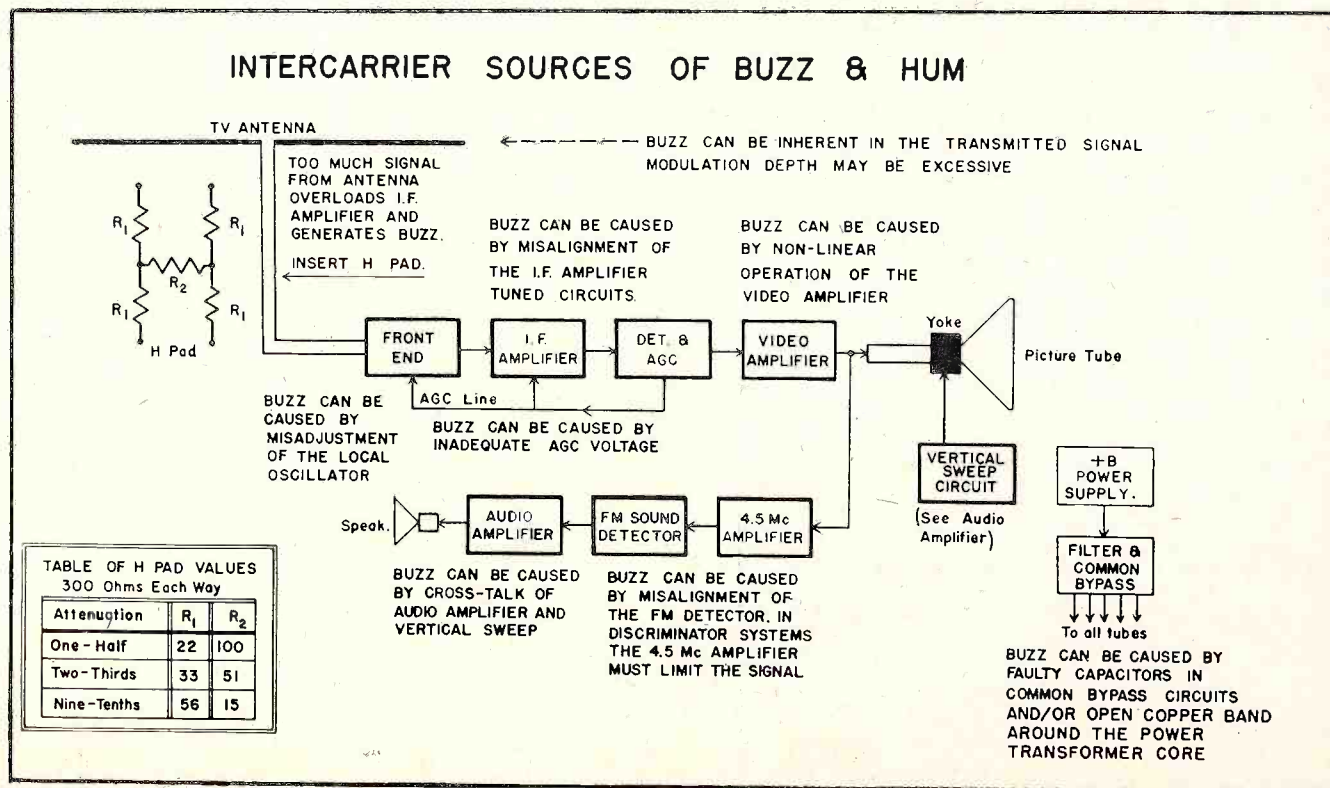


Fig. 5. Sources of intercarrier receiver noise.

another important first from du mont:

the tube that is always in focus

automatically

...the tube that needs no

focusing circuits or components

...the tube that replaces either

electromagnetic- or electrostatic-focusing tubes

...the tube the whole industry has

wished for...the...

DUMONT

Complete Technical Information

on Request:

CATHODE-RAY TUBE DIVISION,

ALLEN B. DU MONT LABORATORIES, INC.,

CLIFTON, N. J.



*Trade-mark

Successful SERVICING

REG. U.S. PAT. OFF.

Vol. 12

SEPTEMBER, 1951

No. 11

Dedicated to the financial and technical advancement of the
Electronic Maintenance Personnel

Published by
JOHN F. RIDER PUBLISHER, INC.

480 Canal Street
New York 13, N. Y.

JOHN F. RIDER, Editor
H. YUSEM, Associate Editor

Worth 4-8340
Worth 4-8341



Copyright 1951 by John F. Rider
No portion of this publication may be reproduced
without the written permission of the publisher.

CURTAIN TIME

New SS

Effective with this issue, several changes are under way in **SUCCESSFUL SERVICING**. They are aimed at producing a better publication—one which will afford the utmost benefit to the reader. More articles, solicited from outside authors, will be published in each issue. To do this requires a change in presentation. Text will be terse and to the point, using a maximum of illustrations whenever possible. Advertising is no longer restricted to not more than two manufacturers of similar products per issue. Several monthly features deemed of interest to radio, television, and allied maintenance activities will be added. The fundamental theme throughout will be maintenance of electronic equipment. We are sure that you will like SS even more in the future than you have in the past.

About Sports

Maybe we're all wet in our belief, but somehow or other we are gradually arriving at the conclusion that maybe sport telecasts are not as important any more as they were at one time. What we're leading up to is that theater television for the purpose of showing sporting events may not, in the long run, prove as significant as the present hullabaloo indicates. If you're looking for a reason for the above, it is simple—women represent the buying power in radio and they represent the

major audience and buying power in television too. They're not too partial to sports telecasts—if partial at all.

A Word to City Fathers

We don't like licensing. We're certain that the majority of the servicing industry feels the same way. But you, City Fathers the nation over, are adamant on the point and licensing will be with us. So, when the bills come up for decision, please consider the following:

a. Don't set up an inspection bureaucracy. It can prove very bad.

b. Don't place the whole financial responsibility in the lap of the company who accomplishes the service contract. Make certain, if you can, that the vendor of the contract, the guy who gets his kickback or commission, is responsible also. Then he will see to it that the service contractor he selects is reliable.

c. Don't place the full authority of control over the licensee in the hands of only one individual. Set up a board of competent advisors representing all facets of the television industry and the municipal authorities. Make the License Commissioner work with this board and take its advice before revoking licenses. Make the Commissioner state in writing why he refuses to accept their advice, if that does happen.

d. Don't make the technical requirements of the license too stringent without giving the

men now practicing an opportunity to bone up on technical details. If you do, your city's population will be without servicing facilities. The bill before the New York City Council calls for permits for all, at present, and licenses 2 years hence, after qualification examinations. It makes much sense.

e. Don't burden the TV service facilities with high financial costs. Your public pays in the long run.

f. Don't form the impression that licensing will make a man more honest or more competent. Examine the operations of those facilities which you already have licensed.

Mr. City Fathers, pay some heed to these don'ts. If you do, your licensing bill will be more beneficial to your population and to the TV servicing industry.

Mr. TV Serviceman, see to it that your local city administrators know about some of these don'ts. If you need extra copies to send to them—ask us; we'll send them to you as long as they are available. If we run out, you can photostat this editorial.

JOHN F. RIDER

Air King Service Hint

For a short while, Air King placed the chassis identification plates on the back apron of the chassis rather than on the dog house, where they were originally placed. When used on the back apron, the mounting screws may short out the B plus causing the rectifier tube and resistor to burn up. If any models are found with the chassis identification plate on the back apron they should be changed to this previously used position on the dog house cover.

Belmont 16- and 17-inch Chassis

A production change was incorporated in Raytheon 16 and 17 inch television receivers to prevent the possibility of the picture tube sliding forward or shifting in shipment.

The rubber sponge pad was cemented only to the front mounting brackets in the past. At the present time the rubber sponge pads are being cemented both to the brackets and the glass of the cathode-ray tube.

If removal of the cathode-ray tube is necessary, use care to loosen the tube from the pad before removing the tube from the chassis. In most cases a slight amount of pressure between the chassis and the tube will release the adhesion.

The serviceman is cautioned: Do not force removal of the tube as an implosion may result.

ATTENTION AUTHORS:

We are soliciting articles concerning radio, television, and allied electronic maintenance. All aspects are of interest. Articles of 1,000 to 2,000 words are desired. Preference is given to subject matter which reflects practical work rather than theory. The presentation should be direct, to the point, and amply illustrated. Finished art work will be prepared by us from the roughs submitted. Photographs are welcome. The rate of payment is on a word basis—and, needless to say, good writing rates good pay!

Submit all articles and inquiries to Editor, *Successful Servicing*.

JOHN F. RIDER PUBLISHER, Inc.
480 CANAL STREET
New York 13, N. Y.

MOST COMPLETE BOOK OF ITS KIND

—a "Must" for TV-Radio Servicemen!



**Simplifies and Speeds
the Replacement of**

SELENIUM RECTIFIERS

In TV and Radio Sets

**COVERS OVER 20,000,000
UNITS ALREADY INSTALLED**

Millions more being added yearly!

A VALUABLE GUIDE PLUS HANDBOOK

—packed with authoritative, up-to-the-minute data on how to service the growing, profitable Selenium Rectifier Replacement Market!

Important sections in this new book include:

- ★ TV replacement part numbers and corresponding Federal numbers
- ★ Radio replacement part numbers and corresponding Federal numbers
- ★ Operating characteristics of Federal selenium rectifiers
- ★ Fundamental circuits using Federal selenium rectifiers
- ★ How to replace a 35Z5 with a Federal 100 Ma selenium rectifier
- ★ "Packaged Power" for engineering your own AC to DC power conversion

Order one or more copies now—from your Federal Distributor

**America's Oldest and Largest Manufacturer
of Selenium Rectifiers**

Federal
Telephone and Radio Corporation

SELENIUM-INTELIN DIVISION • 100 Kingsland Road, Clifton, N. J.

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P.Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

Please mention Successful Servicing when answering advertising.

FEDERAL'S Selenium Rectifier Replacement Guide is a book the servicing industry has been waiting for. A copy should be on *every* TV-radio workbench!

Since 1946, when Federal pioneered and introduced the miniature selenium rectifier, the use of this versatile component by leading set makers has grown tremendously . . . a huge replacement market potential has been created. Now this fact-filled book tells how to service it quickly, easily, effectively and profitably.

Get your copy without delay, Mr. Serviceman. You'll be ready to tell at a glance the *right* selenium rectifier to use for *any* job. And remember: It pays to replace with the best . . . to insist on *Federal* . . . the *original* miniature selenium rectifier. Use the handy coupon below:

MAIL To Your FEDERAL Distributor

To My FEDERAL Distributor: F-610

Name _____

I am enclosing \$_____ to cover the cost of _____ copies (at 50¢ per copy) of the Federal Selenium Rectifier Replacement Guide.

Name _____

Company _____

Address _____

City _____ Zone _____ State _____

Television Changes

DuMont RA-103

The following production changes have been made on the RA-103. A 6AL7-GT tube has been substituted for the 6U5/6G5 tuning indicator tube, V225, and connected as shown in Fig. 1. A 1-megohm resistor has been added from pin 4 of this tube to pin 4 of J201. Capacitor C288, 1.6 μ f, has been inserted in place of C214 and L211, which have been deleted from the video i-f circuit. Capacitor C289, 2 μ f, has been inserted in the video i-f circuit in place of C205 and L205, which have been deleted. Capacitor C90, 0.005 μ f, is inserted in parallel across R209 which is connected to pin 7 of the 2nd video i-f tube V202. Capacitor C291, 2.5 μ f, has been added from pin 7 of V209, the 6AL5 sound detector to ground. Resistor R270, 6800 ohms, has

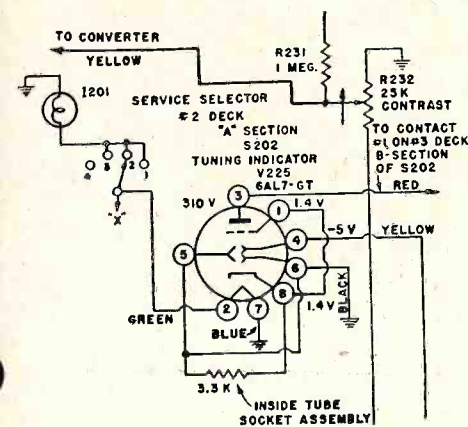


Fig. 1. New tuning indicator tube, DuMont RA-103.

been deleted from pin 6 of V216-A, the vertical buffer. Resistor R277, the vertical size control from R276 to the red lead of T202, has been changed in value from 2 megohms to 4 megohms. The value of resistor R278 which went to pins 3 and 6 of V217, the 6SN7-GT vertical deflection amplifier, has been changed from 3900 ohms to 4700 ohms. Two resistors R326, 1800 ohms, and R327, 3300 ohms, have been connected in series from R278 to pins 3 and 6 of the above mentioned tube V217. The value of resistor R304, from tap 4 of T204 to


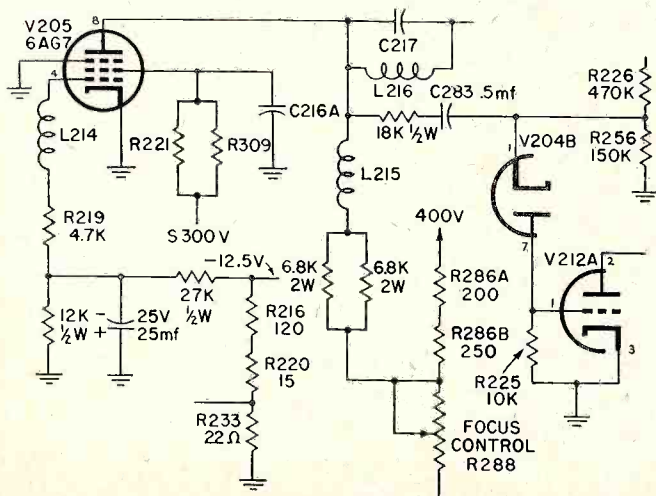


Fig. 2. Vertical sync modifications, DuMont RA-103.

Fig. 3. Horizontal sync modifications, DuMont RA-103.

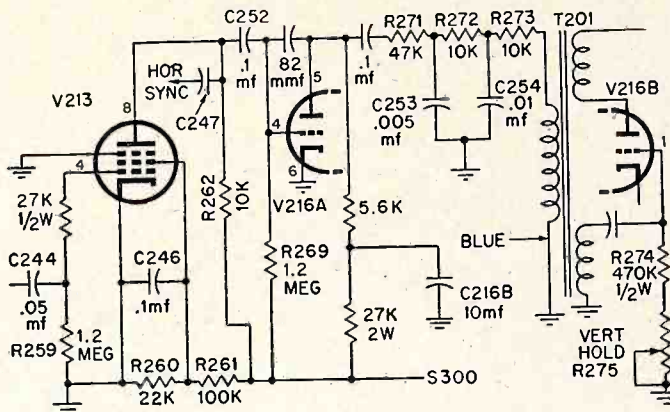

pin 8 of tube V223, has been changed from 6000 ohms to 8500 ohms. The position of the contacts have been relocated so that they now go from pin 8 of V219, and 5U4 rectifier, to the junction of L217 and R316. Resistor R205, connected to pin 6 of the 1st video i-f, has been changed to 6800 ohms.

The vertical sync circuit modifications given below are recommended for use in areas where noise causes loss in vertical sync.

1. Replace V205, the 6AC7 video amplifier, with a type 6AG7 tube as shown in Fig. 2.

2. Disconnect the low side of R219, the 4700-ohm resistor in the grid circuit of V205, from the junction of R216, 120 ohms, and R220, 15 ohms.

3. Connect a 12,000-ohm, 1/2-watt resistor from the low side of R219 (just disconnected) to ground. Place a 25- μ f, 25-volt capacitor in parallel with this resistor. Be sure to connect the positive side of the capacitor to ground.

4. Add a 27,000-ohm, 1/2-watt resistor between the junction of R219 and the 25- μ f, capacitor and 12,000-ohm resistor added in step 3 and the junction of the -12.5-volt line and R216.

5. Remove R223 (3.6 ohms), the plate load resistor of the video amplifier, and replace with the two 6800-ohm 2-watt resistors connected in parallel. Connect one end of this combination to the low end of L215 and run a lead from the other end of this combination

to the junction of R288, the focus control, and R286B, the candohm strip resistor.

6. Remove R222, 3300 ohms connected to C216B.

7. Add an 1800-ohm, 1/2-watt resistor from the junction of L215, C217, and L216, to capacitor C283.


8. Remove capacitor C282, connected from pin 7 of V204B to ground. Remove capacitor C219, located between pin 7 of V204B and pin 1 of V212A, and replace with a short lead, using pin 7 terminal lug to which C219 was connected.

(Continued on page 9)

QUICK ACTION



Save time — and at the same time do a better job! Use quick-acting Ersin MULTICORE, the original 3-core solder and the only solder made with non-corrosive, extra-active Ersin Flux. The slight difference in price more than pays for itself by eliminating "dry" joints and insuring your customer's good will. Try it! Send for your FREE SAMPLE today! Multicore Sales Corp., Dep't S., 164 Duane St., New York 13, N. Y.

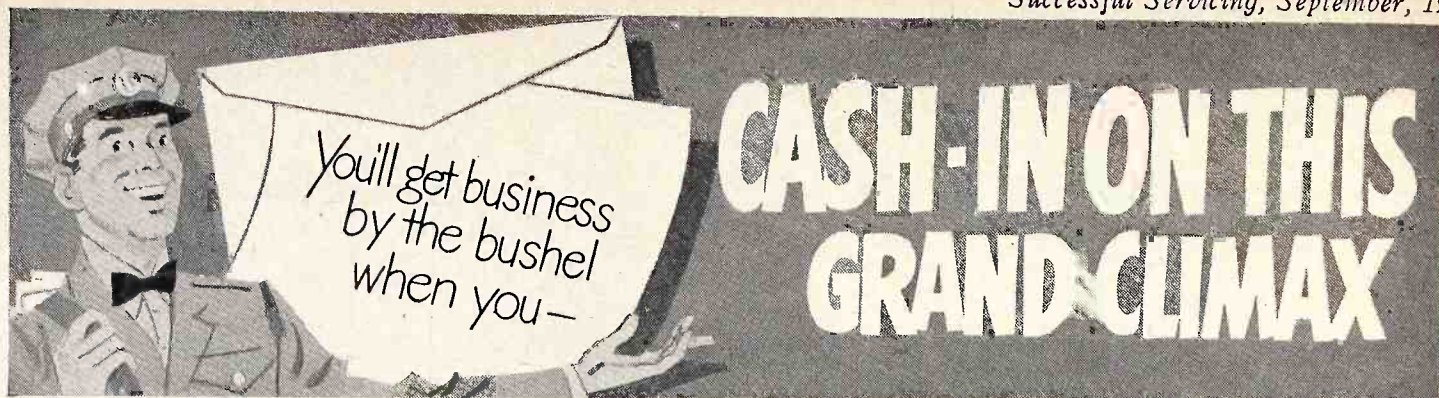

CASH-IN ON THIS GRAND CLIMAX



of Sylvania's big brilliant campaign for Service Dealers

Now begins the second half of Sylvania's greatest and most appealing ad campaign ever offered to Service Dealers.

Featuring 2 famous celebrities, Paulette Goddard and Patrice Munsel, this campaign ties in with big ads soon to appear in the Saturday Evening Post, Look, Life, and Collier's magazine, and is backed by the nation-wide weekly TV show, "Beat the Clock."

Everything included

Here's everything you need for a record harvest of fall service business. You get big, smashing life-like displays of the famous stars. You get counter cards, streamers, direct-mail pieces . . . even radio spot announcements.

Remember, you pay only one cent each for the mailing pieces. All the rest is FREE! So don't let another minute go by without calling your nearest Sylvania distributor . . . or mail the coupon NOW.



SYLVANIA

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS



Sylvania Electric Products Inc.
Dept. R-2709, Emporium, Pa.

Please send me full details about Sylvania's great Fall 1951 Service Dealer Campaign.

Name _____

Street _____

City _____ Zone _____ State _____

DuMont RA-103

(Continued from page 7)

9. Remove resistor R224, located between pin 1 of V212A and ground.
- For the following steps refer to Fig. 3.
10. Add a 27,000-ohm, $\frac{1}{2}$ -watt resistor from the junction of C244 and R259 to pin 4 of V213.
11. Change the value of capacitor C252 (from pin 8 of V213 to pin 4 of V216A) to 0.1 μ f.
12. Disconnect the ground side of R269, in the grid circuit of V216A. This will be connected in step 17.
13. Connect an 82- μ f capacitor between pins 4 and 5 of V216A.
14. Disconnect R271, 10,000 ohms, from pin 5 of V216A. This resistor will be replaced in step 18.
15. Connect a 5600-ohm, $\frac{1}{2}$ -watt resistor to pin 5 of V216A.
16. Connect the other end of the 5600-ohm resistor just added to a 27,000-ohm, 2-watt resistor. Run a lead from the junction of these two resistors to C216B.
17. The other end of the 27,000-ohm resistor is to be connected to the junction of R262 and R261 and to the low side of R269 (the 1.2-megohm resistor in the grid circuit of V216A).
18. Replace R271 with a 47,000-ohm, $\frac{1}{2}$ -watt resistor.
19. Connect a 0.1- μ f capacitor between pin 5 of V216A and 47,000-ohm resistor just added.
20. Disconnect the blue lead of the primary of T201 from the +175-volt line and run directly to ground.


**ORDER YOUR COPY NOW
RIDER TV VOLUME 7**

DuMont RA-104A, RA-108A, RA-110A

To eliminate the condition in RA-104A and RA-110A chassis, known as Barkhausen Oscillation (the indication of this trouble is one or more vertical black lines on the left-hand side of the raster) the following procedures should be observed.

Use only coax transmission lines (RG-11/U in the fringe areas and RG-59/U in strong signal areas). Make sure that the shield of the coax is properly grounded to the antenna connector shield. Keep the coax transmission line away from the power supply chassis. Place a metal plate (preferably copper) under the power supply chassis and main chassis. This plate need only be large enough to act as a bond between the two chassis. If the above suggestions do not cure the condition, replace the 6BG6 and ascertain that the drive control is properly adjusted.

"Thumping" sometimes occurs in RA-108A and RA-110A chassis using the 19AP4 metal picture tube. This condition may be described as an "electrostatic pendulum," the pendulum consists of a swinging back and forth in a definite rhythm of the tag tied to the high-voltage lead. This warning tag makes a resounding "thump" each time it strikes the metal. To prevent this condition, change the position of the tag.

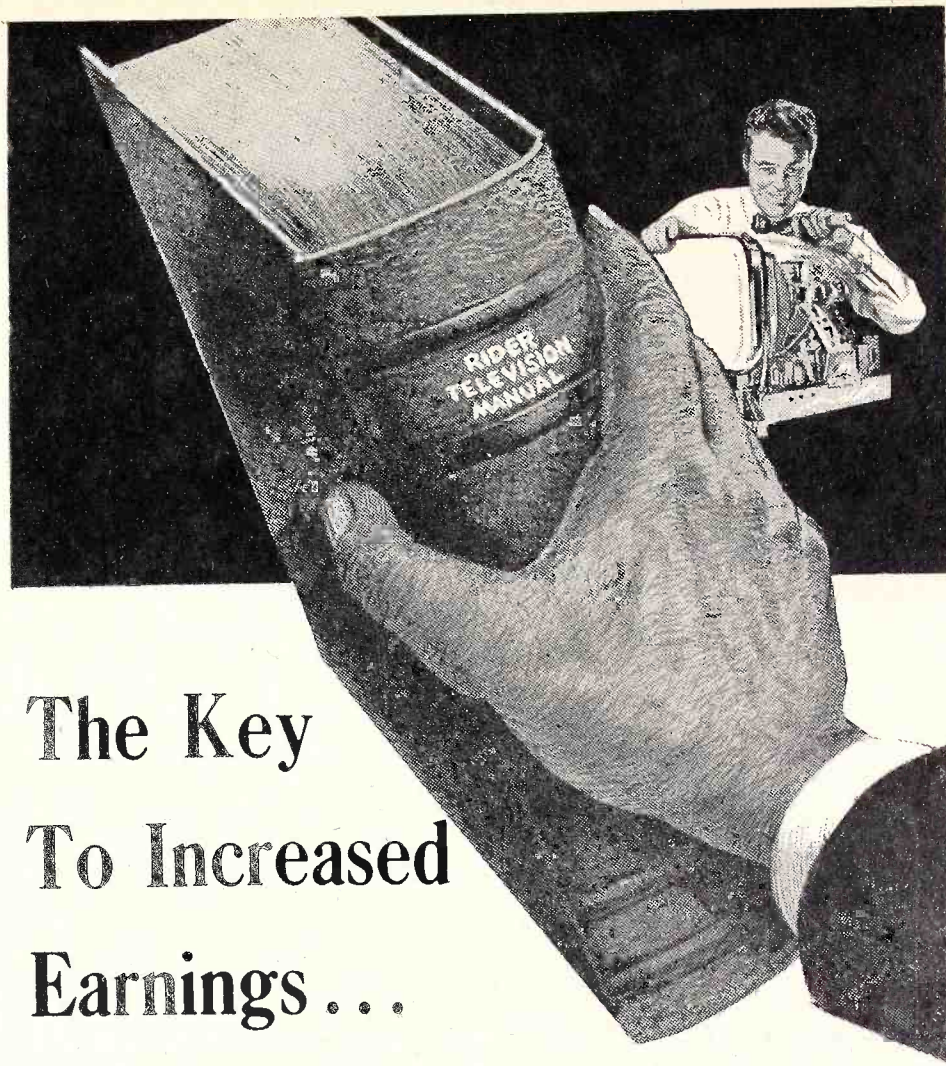

The Key To Increased Earnings ... Is At Your Fingertips

Now, more than ever before, your knowledge of every phase ... every detail ... of servicing each set in the manufacturer's line really pays off. And there's only one source that gives you *all* you must know. It's Rider Radio & TV Manuals. The only complete, authoritative service data on television and radio in the world!

Here you'll find the answers to all your servicing questions. From complete unpacking and installation data to complete factory parts lists. With Rider's accurate, factory-authorized information at your fingertips you'll spend less time per call ... and do a better job! The result is greater profits. Ask your jobber to show you the latest Rider Manual — today!



JOHN F. RIDER Publisher, Inc.
480 Canal Street, New York 13, N. Y.


Competence

is the word for Model 3432

Take it at face value, and you can't be wrong! The big, BIG no-glare illuminated dial, the fine control Output Attenuator, the wide frequency range, improved shielding to control radiation, and other performance features—all proved for action and accuracy. Give it the bench test—you'll find more competence packed in its handsome metal case than any test oscillator you ever used. It's double-copper shielded and individually calibrated against precise crystal standards. It is competent every step of the way.

Extra-Large Dial

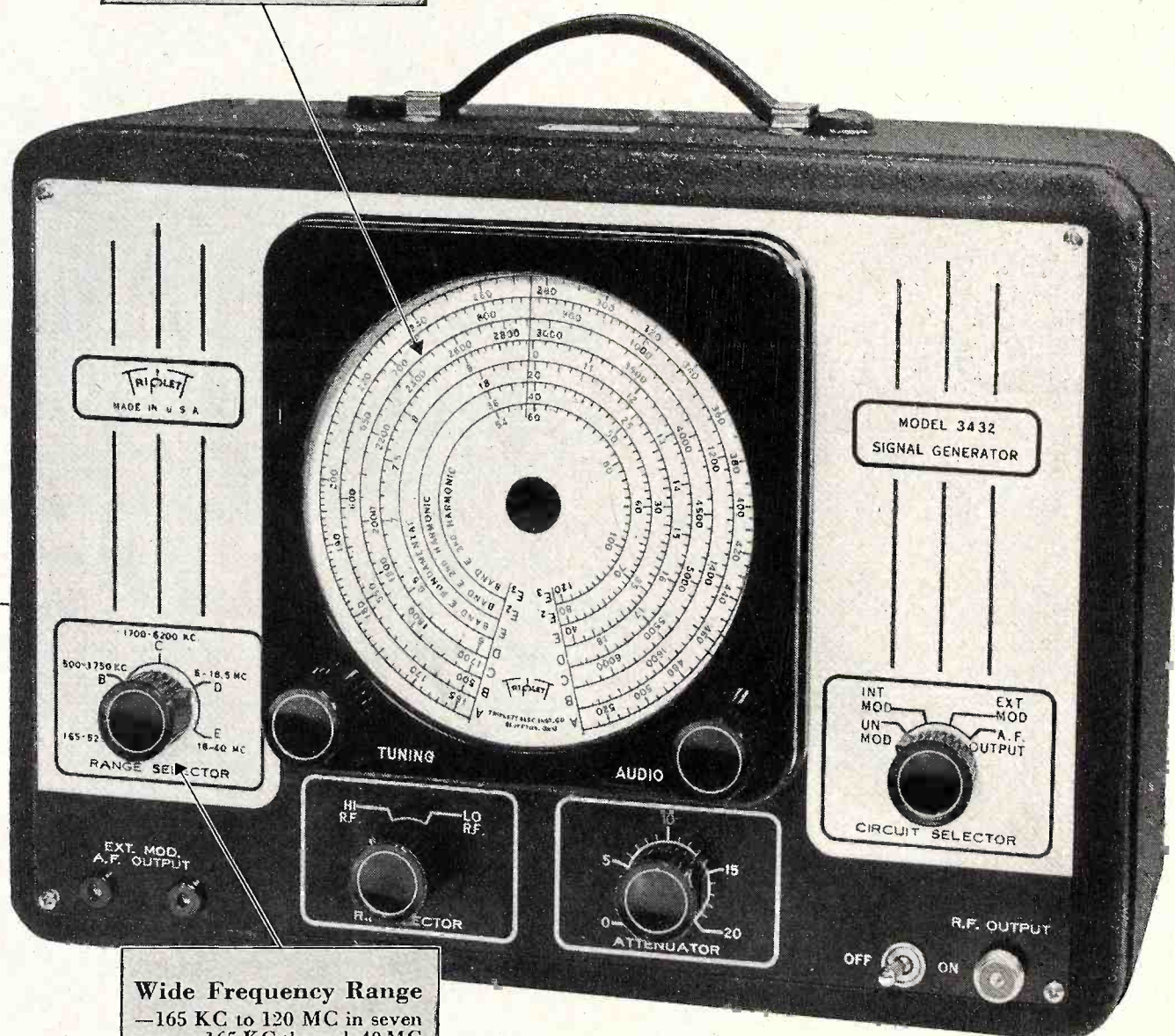Seven long 330° scales for easy reading at any spot on the dial. All Illuminated—no glare. Top scale is 16" long. Dial has 10 to 1 ratio vernier tuning.



Wide Frequency Range

—165 KC to 120 MC in seven ranges. 165 KC through 40 MC fundamentals; through 120 MC by strong harmonics.

ONLY \$79.50 at your Distributor
(Price subject to change)

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplet

TRIPLETT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO, U. S. A.

Please mention Successful Servicing when answering advertising.

Television Changes

Gamble-Skogmo 94TV1-43-8940A

As changes were made in the production of Model 94TV1-43-8940A, code numbers were assigned to distinguish the differences in the sets. The differences between the different code numbers are explained below:

Code 1. Code 1 chassis are wired as shown in the schematic diagram in Volume 4, except for the tuner chassis filament wiring. Only terminals 6 and 7 should be connected to H. Terminals 5, 8, and 10 should be grounded. There should be no direct connection between C32 and C31, as indicated in Volume 4. C32 should go directly to terminal 6, and C31 should go directly to terminal 7.

Code 2. A 1,000- μ f capacitor is used in place of C111. The value of resistor R92 is changed from 270,000 ohms to 220,000 ohms, and the lead from R92 now goes to the +350-volt line instead of to the +250-volt line. The value of R63 is changed from 560 ohms to 680 ohms, 1 watt.

Code 3. This is similar to Code 2 except that capacitor C109, 47 μ f has been deleted from pin 1 tube 16 to ground.

Code 4. This is similar to Code 3 except that C117 is no longer connected to terminal 1 of T6. It is now grounded.

Code 5. C111, 680 μ f, and C109, 80-480 (A-8E-18508) are now connected in parallel from the junction of C110 and R95 to ground.

Code 6. C116, 0.2 μ f (coil form, A5D 18507) has been added from pin 3 to tube 9-B, the 6SL7 agc amplifier, to pin 5 of tube 18, the 6W4.

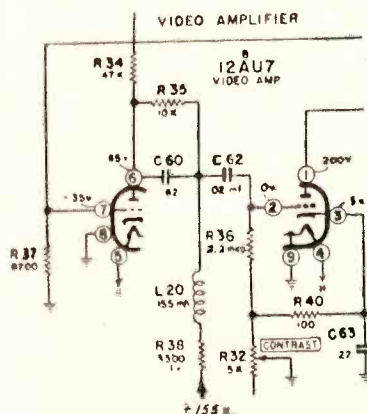


Fig. 1. Changes in the video amplifier circuit of the Gamble-Skogmo 94TV1-43-8940A.

Code 7. R48 is no longer connected to the +350-volt line, instead it now goes directly to tap 3 of T6.

Code 8. R98 now goes to the +350-volt line, instead of to tap 3 of T6. C113 is grounded instead of going to the junction of C114 and the +350-volt line. Capacitor C119, 1,000 μ f, has been added from ground to the junction of C118-A and the lead from C114 that goes to tap 3 of T6.

Code 9. The value of R73 is changed from 100,000 ohms to 68,000 ohms.

The following additions have been made to the parts list in Codes 1 through 9:

Parts No.	Description
B-15P-18282	Focus magnet
A-19A-14275	Yoke plug
B-15B-14274	Yoke socket
C-2B-18056	Power-supply shield can
A-1B-18446-74	Knob (5 used)
A-6M-18412	Indicator plate.

The deflection-yoke socket is now numbered in the following way: pin 1 is now designated as pin 4, 2 is now 5, 3 is now 1, 4 is now 2.

Code 10. The value of R47 is changed to 68,000 ohms (C-9B1-84), and a switch-on volume-contrast control has been added from R47 to the +250-volt line. R73 is changed to 18,000 ohms (C-9B1-77). R76 is changed to 560,000 ohms (C-9B1-95). R100 has been removed from its position at pin 6 of tube 19 and is now located from the junction of pin 11 of tube 10 and C67 to the tap of R46, brightness control. The value of R100 is 100,000 ohms. R103 is changed to 5,600 ohms, 2 watts (C-9B4-74). R108, 5,600 ohms, 2 watts (C-9B4-74), has been added from C61-D to the +350-volt line. R105 and F-1 have been deleted from the circuit. C118-A is now located from pin 1 of the power-jumper plug to ground; C119 goes from ground to pin 1 of the jumper plug and C114. A 1/4-amp fuse has been inserted from pin 6 to pin 1 of the jumper plug.

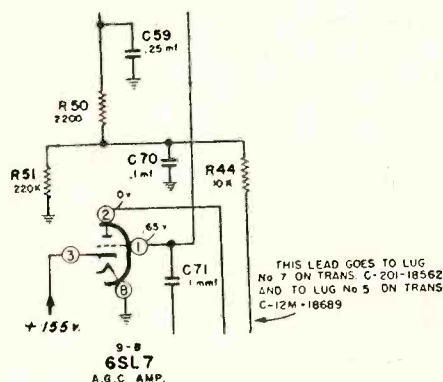


Fig. 2. Changes in the agc circuit of the Gamble-Skogmo 94TV1-43-8940A.

Code 11. Resistor R107, 3,900 ohms, 2 watts (C-9B4-69) is added from pin 3 of tube 18, the 6W4, to the minus side of C115. The horizontal-deflection transformer T6 has been changed from C-12M-18285 to C-201-18530.

Code 12. Capacitor C120, 7 μ f (ceramic, C-8G-11790) has been added in parallel across coil L10.

Code 13. Capacitor C56 has been deleted. R32, contrast control, and R34 are now located as shown in Fig. 1. Additional changes in component location in this circuit are also shown in Fig. 1. The lead from R34 goes to pin 1 of tube 9-B, the agc amplifier. The lead from R37 goes to L16. The lead from pin 1 goes to the junction of C64 and L21. R37 has been relocated, as shown in Fig. 1, and its value is changed from 1,000 ohms to 8,200 ohms. C61-A has been deleted. R35 and C60 have been added. R32, R38, R40, and C63 are changed to 5,000 ohms, 3,300 ohms, 100 ohms, and 22 μ f, respectively. Since the contrast control was moved to a new location after Code 12, the output connection of an oscilloscope or meter will not be connected across the contrast control, but now across resistor R37 (pin 7 of tube 7 to ground).

R53 has been deleted and C59 has been added. Additional changes in component location are shown in Fig. 2. The lead from R50 and C59 goes to the agc line. The lead from C71 goes to C116, and the other side of C116 goes to pin 4 of tube 9-A, the 6SL7 sync amplifier. The lead from pin 2 goes to tap 6 (an additional winding which is de-

(Continued on page 13)

Make Every Workbench an Assembly Line with

RIDER MANUELS

A complete chronological history of FACTORY-AUTHORIZED American circuits and data on radio receiver design and operation.

VOLUME XXII, 1520 pages.....	\$18.00
VOLUME XXI, 1648 pages.....	\$21.00
VOLUME XX, 1776 pages.....	21.00
VOLUME XIX, 2122 pages.....	22.50
VOLUME XVIII, 2036 pages.....	22.50
VOLUME XVII, 1648 pages.....	19.80
VOLUME XVI, 768 pages.....	9.90
VOLUME XV, 2000 pages.....	22.50
VOLUME XIV, 1376 pages.....	19.80
VOLUME XIII, 1672 pages.....	19.80
VOLUME XII, 1648 pages.....	19.80
VOLUME XI, 1652 pages.....	19.80
VOLUME X, 1664 pages.....	19.80
VOLUME IX, 1672 pages.....	19.80
VOLUME VIII, 1650 pages.....	19.80
VOLUME VII, 1600 pages.....	19.80
VOLUME VI, 1240 pages.....	15.00
VOLS. I-V ABRIDGED, 2000 pages.....	19.80

TELEVISION VOLUME 7 Equivalent of 2352 pages (8 1/2 x 11).....

24.00

TELEVISION VOLUME 6
Equivalent of 2320 pages (8 1/2 x 11).....

24.00

TELEVISION VOLUME 5
Equivalent of 2320 pages (8 1/2 x 11).....

24.00

TELEVISION VOLUME 4
Equivalent of 2296 pages (8 1/2 x 11).....

24.00

TELEVISION VOLUME 3
Equivalent of 2032 pages (8 1/2 x 11).....

24.00

TELEVISION VOLUME 2
Equivalent of 1896 pages (8 1/2 x 11).....


24.00

TELEVISION VOLUME 1
Equivalent of 2000 pages (8 1/2 x 11).....

19.80

PA EQUIPMENT VOLUME 1
2024 pages.....

18.00

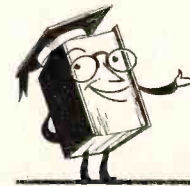

"The World's
Greatest Compilation
of
AM-FM-TV-PA
Servicing Data."

SHURE

2

New phono pickup cartridges to help simplify cartridge replacement



Model W22AB-T

TURNOVER CARTRIDGE

WHAT IT IS:

A high quality extended range "Vertical Drive" Cartridge complete with positive turnover mechanism. Has sapphire tipped fine-groove and osmium tipped standard-groove needle.

WHAT IT DOES:

Offers greatly improved performance when used as replacement for single-needle all purpose cartridge. Also recommended for replacement of other types of turnover and dual-needle cartridges. Replaces not only cartridge but turnover mechanism as well.

SPECIAL FEATURES:

1. Extended frequency response to 10,000 c. p. s.
2. Tracks at low needle point pressure — only 8 grams.
3. Sturdy construction guarantees long life of turnover mechanism.
4. Standard $\frac{1}{2}$ " bracket mount has elongated holes for versatility and quick easy installation.

MODEL W22AB-T — CODE: RUVUR
LIST PRICE \$10.00



Model W42BH

"DUAL-VOLTAGE CARTRIDGE"

WHAT IT IS:

A low cost "Lever Type" Cartridge for 78 RPM records. Equipped with unique "slip on" condenser-harness for dual-voltage output. 1.5 volts or 3.75 volts obtainable in one cartridge.

WHAT IT DOES:

Gives servicemen an ideal replacement for old style 78 RPM cartridges. A "leader" value — it modernizes the equipment at an extremely low price — only \$4.95 list. It guarantees improved reproduction. Minimizes inventory problem. One cartridge with choice of two output voltages covers bulk of requirements.

SPECIAL FEATURES:

1. "Lever Type" construction assures improved tracking.
2. Specially designed needle guard which protects crystal from breakage.
3. Equipped with pin jacks and pin terminals.
4. If used for high output, the condenser may be used separately by the serviceman for other purposes.

MODEL W42BH — CODE: RUVUS
LIST PRICE \$4.95



At Your Shure Distributor

FREE! THE WONDERFUL NEW CARTRIDGE Replacement Manual No. 66

Contains over 1500 Phonographs—Radio-TV Phono Combinations equipped with or which can effectively use Shure crystal or ceramic cartridges. These sets are made by 123 manufacturers and date from 1938 to 1951.

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE

SHURE BROTHERS, Inc.
225 W. Huron St., Chicago 10, Illinois



MANUFACTURERS of
MICROPHONES and ACOUSTIC DEVICES
Cable Address: SHUREMICRO

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 11)

scribed below), of T6. C71 is now 1 μ f, and R50 is 2,200 ohms.

R54, which went from R17 to pick-off coil T8, has been deleted. C72 has also been deleted. R99, to tap 5 of T6, has been deleted. T6 has been changed (see parts-list changes listed below), and now has an additional winding which is located between the winding for the filaments on the 1X2 and the winding going to the plate of the 1X2.

The value of R82 is changed from 1 megohm to 220,000 ohms, and the lead goes to tap 6 of T6, instead of to tap 5. C98 is changed from 75 μ f to 82 μ f. R87 is changed from 1.5 megohms to 680,000 ohms. C110 has been relocated and now goes from R87 to the junction of C112, R96, and R97. The value of C110 is changed from 220 μ f to 22 μ f, 500 volts. R95 has been deleted and the value of C111 is changed from 680 ohms to 820 ohms. Pin 8 of tube 17, the 6BQ6 pulse amplifier, is now tied to pin 2 of the same tube.

The change in parts list is as follows:

Ref. No.	Part No.	Description
C60	C-8F3-112	82 μ f, mica
C63	C-8F-18569	22 μ f, mica
C70	B-8D-18491	0.1 μ f, paper
C71	A-8G-12495-2	1 μ f, ceramic
C98	C-8F3-112	82 μ f, mica
C110	C-8G-11892	22 μ f, 500 volts, ceramic
C111	C-8F6-124	820 μ f, mica
R34	C-9B1-82	47,000 ohms, $\frac{1}{2}$ watt
R35	C-9B1-74	10,000 ohms, $\frac{1}{2}$ watt
R37	C-9B1-73	8,200 ohms, $\frac{1}{2}$ watt
R38	C-9B2-68	3,300 ohms, 1 watt
R40	C-9B1-74	100 ohms, $\frac{1}{2}$ watt
R50	C-9B1-66	2,200 ohms, $\frac{1}{2}$ watt
R82	C-9B1-90	220,000 ohms, $\frac{1}{2}$ watt
R87	C-9B1-96	680,000 ohms, $\frac{1}{2}$ watt

Code 14. R44 is changed from 3.3 megohms to 10,000 ohms, $\frac{1}{2}$ watt (C-9B1-74).

Code 15. The value of R56 is changed from 68 ohms to 120 ohms, $\frac{1}{2}$ watt (C-9B1-51).

Ref. No.	Part No.	Description
C61	A-8C-18487	30-30 μ f x 450 volts, 125 μ f x 25 volts
	B-5B-18552-85	Tuning knob (vernier)
	B-2M-18553	Vernier disk
	B-55P-18638	Focus magnet
	A-51A-15713	Iron core, for L4, 8, 9
	A-10B-18794	Vertical size control (screwdriver shaft)
	A-10B-18795	Linearity size control (screwdriver shaft)

In later production, group numbers (chassis identification numbers) were assigned to each set. The production changes made are explained below:

Code 16 or Group Numbers 6,700 to 8,999. Video trap coil L19 was relocated and connected to pin 7 of the 12AU7 video amplifier, tube 8, and L16. Peaking coil L21 (A-16A-17961) was replaced with A-16A-18685 (white dot). The high-voltage capacitor and socket assembly (N-201-18161) was removed and replaced with a wafer tube socket (A-15C-18735), high-voltage ring (A-62C-18734), two insulators (A-5M-18733), and mounting hardware. A 2.2-ohm, $\frac{1}{2}$ -watt, wire-bound resistor (C-9C1-1067) or a filament choke (A-16A-18785) was added in series with the 1X2 filament lead as shown in Fig. 3.

Code 17 or Group Numbers 9,000 to 12,399. To reduce capacitor failures, capacitor C64 is replaced with a 0.01- μ f, 600-volt capacitor (C-8D-11128).

Code 18 or Group Numbers 12,400 to 14,199. To reduce horizontal size, the white and black leads to the horizontal-deflection transformer T6, lugs 2 and 3, respectively, were interchanged, black to lug 2 and white to lug 3.

Code 19 or Group Numbers 14,200 and above.

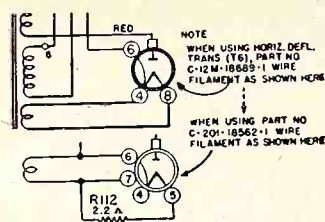


Fig. 3. Wiring for the 1X2 filament lead of the Gamble-Skogmo 94TV1-43-8940A.

Both the C-12M-18689 and C-201-18562 horizontal-deflection transformers were removed and replaced with new transformers. The part numbers are the same with the addition of a dash one (-1). The black and white horizontal-deflection-transformer leads are connected as in Code 17. Resistor R4 is changed to 10,000 ohms. Resistors R8 and R10 are grounded, C33 has been deleted, and the tuner chassis filament wiring has been changed. Pin 4 of the 6AG5 is grounded, pin 3 of the same tube and pin 3 of the 6J6 are tied to tuner terminal 8 and go to H. Pin 4 of the 6J6 is grounded. C30, C31, and C32 have been deleted. C25, C27 and C28 have been deleted. The value of R45 is changed to 220,000 ohms (C-9B1-90), and a resistor R110, 220,000 ohms, $\frac{1}{2}$ watt (C-9B1-90) has been added from pin 5 of the 6SL7 sync amplifier, tube 9-A, to ground. R28 is changed to 120 ohms.

Resistor R109 has been added across transformer T1, from pin 5 to pin 6 of the 6AU6 3rd i.f. The value of resistor R107 (see Code 11) has been changed from 3900 ohms to 5600 ohms. To eliminate vertical jitters, R73 is changed to 68,000 ohms (C-9B1-84). R72

is changed to 1.5 megohms (C-9B1-100). C95 is changed to 0.02 μ f (C-8D-17607). C106 is changed to 0.1 μ f (C-8D-10771). Capacitor C91 is deleted. C90 has been relocated to between R77 and C95, and its value has been changed to 0.005 μ f (C-8D-17608). A dual control and switch (A-10A-18441) has been added to the parts list. Resistor R3 has been deleted from lug 2 (antenna input). Lug 2 is now connected directly to lug 4, 1 and 3 are connected to the antenna input terminals.

Five different horizontal deflection transformers T6 have been used on the various production runs.

1. Chassis Coded 1 through 12. These chassis use part number C-12M-18285 transformer. This is a laminated iron core transformer with a 5-lug terminal board. This transformer should be used for replacement. The C-12M-18689 transformer can be used for replacement if the agc leads are removed from lugs 5 and 6 (left hanging free) and a 1-megohm, 1-watt resistor is added from lug 5 to the blue 6BQ6 plate lead terminal. If horizontal non-linearity (left-hand bulge) is noticed on any of these chassis, it may be corrected by reversing the leads connected to terminals 2 and 3.

2. Chassis Coded 13 through 15 and Group Numbers to 14,200. These chassis use either part number C-12M-18689 or part number C-201-18562 transformers. The C-12M-18689 is a laminated iron core transformer with a 6-lug terminal board, and the C-201-18562 is a molded iron core transformer (racetrack shape) with 5 lugs on one side of the terminal

(Continued on page 15)

ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

The NEW ESPEY model 511-B

FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly Illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-50 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

Makers of fine radios since 1928.

ESPEY TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.


Competence

is the word for Model 3432

Take it at face value, and you can't be wrong! The big, BIG no-glare illuminated dial, the fine control Output Attenuator, the wide frequency range, improved shielding to control radiation, and other performance features—all proved for action and accuracy. Give it the bench test—you'll find more competence packed in its handsome metal case than any test oscillator you ever used. It's double-copper shielded and individually calibrated against precise crystal standards. It is competent every step of the way.

Extra-Large Dial

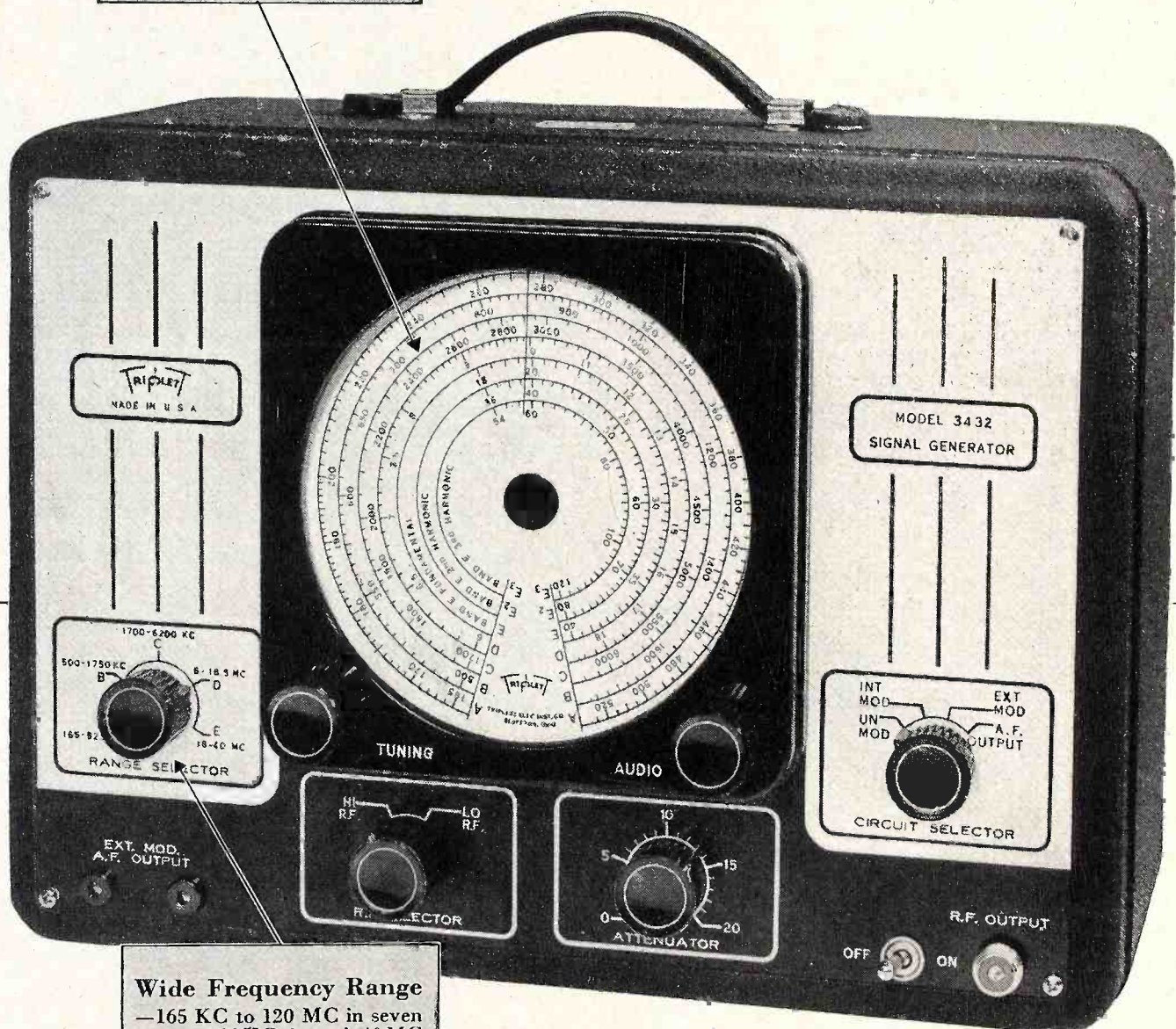Seven long 330° scales for easy reading at any spot on the dial. All Illuminated—no glare. Top scale is 16" long. Dial has 10 to 1 ratio vernier tuning.



Wide Frequency Range

—165 KC to 120 MC in seven ranges. 165 KC through 40 MC fundamentals; through 120 MC by strong harmonics.

ONLY \$79.50 at your Distributor
(Price subject to change)

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplet

TRIPLITT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO, U. S. A.

Please mention Successful Servicing when answering advertising.

Television Changes

Gamble-Skogmo 94TV1-43-8940A

As changes were made in the production of Model 94TV1-43-8940A, code numbers were assigned to distinguish the differences in the sets. The differences between the different code numbers are explained below:

Code 1. Code 1 chassis are wired as shown in the schematic diagram in Volume 4, except for the tuner chassis filament wiring. Only terminals 6 and 7 should be connected to H. Terminals 5, 8, and 10 should be grounded. There should be no direct connection between C32 and C31, as indicated in Volume 4. C32 should go directly to terminal 6, and C31 should go directly to terminal 7.

Code 2. A 1,000- μ f capacitor is used in place of C111. The value of resistor R92 is changed from 270,000 ohms to 220,000 ohms, and the lead from R92 now goes to the +350-volt line instead of to the +250-volt line. The value of R63 is changed from 560 ohms to 680 ohms, 1 watt.

Code 3. This is similar to Code 2 except that capacitor C109, 47 μ f has been deleted from pin 1 tube 16 to ground.

Code 4. This is similar to Code 3 except that C117 is no longer connected to terminal 1 of T6. It is now grounded.

Code 5. C111, 680 μ f, and C109, 80-480 (A-8E-18508) are now connected in parallel from the junction of C110 and R95 to ground.

Code 6. C116, 0.2 μ f (coil form, A5D-18507) has been added from pin 3 to tube 9-B, the 6SL7 agc amplifier, to pin 5 of tube 18, the 6W4.

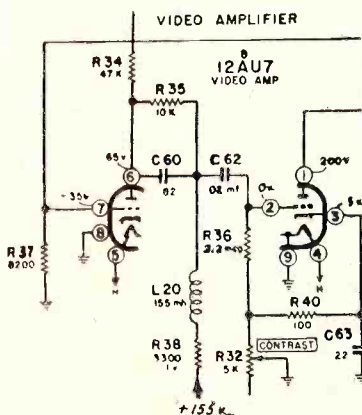


Fig. 1. Changes in the video amplifier circuit of the Gamble-Skogmo 94TV1-43-8940A.

Code 7. R48 is no longer connected to the +350-volt line, instead it now goes directly to tap 3 of T6.

Code 8. R98 now goes to the +350-volt line, instead of to tap 3 of T6. C113 is grounded instead of going to the junction of C114 and the +350-volt line. Capacitor C119, 1,000 μ f, has been added from ground to the junction of C118-A and the lead from C114 that goes to tap 3 of T6.

Code 9. The value of R73 is changed from 100,000 ohms to 68,000 ohms.

The following additions have been made to the parts list in Codes 1 through 9:

Parts No.	Description
B-55P-18282	Focus magnet
A-19A-14275	Yoke plug
B-15B-14274	Yoke socket
C-2B-18056	Power-supply shield can
A-5B-18446-74	Knob (5 used)
A-6M-18412	Indicator plate.

The deflection-yoke socket is now numbered in the following way: pin 1 is now designated as pin 4, 2 is now 5, 3 is now 1, 4 is now 2.

Code 10. The value of R47 is changed to 68,000 ohms (C-9B1-84), and a switch-on volume-contrast control has been added from R47 to the +250-volt line. R73 is changed to 18,000 ohms (C-9B1-77). R76 is changed to 560,000 ohms (C-9B1-95). R100 has been removed from its position at pin 6 of tube 19 and is now located from the junction of pin 11 of tube 10 and C67 to the tap of R46, brightness control. The value of R100 is 100,000 ohms. R103 is changed to 5,600 ohms, 2 watts (C-9B4-74). R108, 5,600 ohms, 2 watts (C-9B4-74), has been added from C61-D to the +350-volt line. R105 and F-1 have been deleted from the circuit. C118-A is now located from pin 1 of the power-jumper plug to ground; C119 goes from ground to pin 1 of the jumper plug and C114. A $\frac{1}{4}$ -amp fuse has been inserted from pin 6 to pin 1 of the jumper plug.

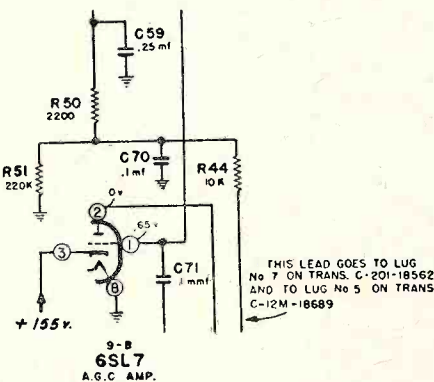


Fig. 2. Changes in the agc circuit of the Gamble-Skogmo 94TV1-43-8940A.

Code 11. Resistor R107, 3,900 ohms, 2 watts (C-9B4-69) is added from pin 3 of tube 18, the 6W4, to the minus side of C115. The horizontal-deflection transformer T6 has been changed from C-12M-18285 to C-201-18530.

Code 12. Capacitor C120, 7 μ f (ceramic, C-8G-11790) has been added in parallel across coil L10.

Code 13. Capacitor C56 has been deleted. R32, contrast control, and R34 are now located as shown in Fig. 1. Additional changes in component location in this circuit are also shown in Fig. 1. The lead from R34 goes to pin 1 of tube 9-B, the agc amplifier. The lead from R37 goes to L16. The lead from pin 1 goes to the junction of C64 and L21. R37 has been relocated, as shown in Fig. 1, and its value is changed from 1,000 ohms to 8,200 ohms. C61-A has been deleted. R35 and C60 have been added. R32, R38, R40, and C63 are changed to 5,000 ohms, 3,300 ohms, 100 ohms, and 22 μ f, respectively. Since the contrast control was moved to a new location after Code 12, the output connection of an oscilloscope or meter will not be connected across the contrast control, but now across resistor R37 (pin 7 of tube 7 to ground).

R53 has been deleted and C59 has been added. Additional changes in component location are shown in Fig. 2. The lead from R50 and C59 goes to the agc line. The lead from C71 goes to C116, and the other side of C116 goes to pin 4 of tube 9-A, the 6SL7 sync amplifier. The lead from pin 2 goes to tap 6 (an additional winding which is de-

(Continued on page 13)

Make Every Workbench an Assembly Line with RIDER MANUELS

A complete chronological history of FACTORY-AUTHORIZED American circuits and data on radio receiver design and operation.

VOLUME XXII, 1520 pages.....	\$18.00
VOLUME XXI, 1648 pages.....	\$21.00
VOLUME XX, 1776 pages.....	21.00
VOLUME XIX, 2122 pages.....	22.50
VOLUME XVIII, 2036 pages.....	22.50
VOLUME XVII, 1648 pages.....	19.80
VOLUME XVI, 768 pages.....	9.90
VOLUME XV, 2000 pages.....	22.50
VOLUME XIV, 1376 pages.....	19.80
VOLUME XIII, 1672 pages.....	19.80
VOLUME XII, 1648 pages.....	19.80
VOLUME XI, 1652 pages.....	19.80
VOLUME X, 1664 pages.....	19.80
VOLUME IX, 1672 pages.....	19.80
VOLUME VIII, 1650 pages.....	19.80
VOLUME VII, 1600 pages.....	19.80
VOLUME VI, 1240 pages.....	15.00
VOLS. I-V ABRIDGED, 2000 pages.....	19.80

TELEVISION VOLUME 7

Equivalent of 2352 pages
(8½x11) 24.00

TELEVISION VOLUME 6

Equivalent of 2320 pages (8½x11)..... 24.00

TELEVISION VOLUME 5

Equivalent of 2320 pages (8½x11)..... 24.00

TELEVISION VOLUME 4

Equivalent of 2296 pages (8½x11)..... 24.00

TELEVISION VOLUME 3

Equivalent of 2032 pages (8½x11)..... 24.00

TELEVISION VOLUME 2

Equivalent of 1896 pages (8½x11)..... 24.00

TELEVISION VOLUME 1

Equivalent of 2000 pages (8½x11)..... 19.80

PA EQUIPMENT VOLUME 1

2024 pages 18.00



"The World's
Greatest Compilation
of
AM-FM-TV-PA
Servicing Data."

SHURE

2

New phono pickup cartridges to help simplify cartridge replacement



Model W22AB-T
TURNOVER CARTRIDGE

WHAT IT IS:

A high quality extended range "Vertical Drive" Cartridge complete with positive turnover mechanism. Has sapphire tipped fine-groove and osmium tipped standard-groove needle.

WHAT IT DOES:

Offers greatly improved performance when used as replacement for single-needle all purpose cartridge. Also recommended for replacement of other types of turnover and dual-needle cartridges. Replaces not only cartridge but turnover mechanism as well.

SPECIAL FEATURES:

1. Extended frequency response to 10,000 c. p. s.
2. Tracks at low needle point pressure—only 8 grams.
3. Sturdy construction guarantees long life of turnover mechanism.
4. Standard $\frac{1}{2}$ " bracket mount has elongated holes for versatility and quick easy installation.

MODEL W22AB-T — CODE: RUVUR
LIST PRICE \$10.00



Model W42BH
"DUAL-VOLTAGE CARTRIDGE"

WHAT IT IS:

A low cost "Lever Type" Cartridge for 78 RPM records. Equipped with unique "slip on" condenser-harness for dual-voltage output. 1.5 volts or 3.75 volts obtainable in one cartridge.

WHAT IT DOES:

Gives servicemen an ideal replacement for old style 78 RPM cartridges. A "leader" value—it modernizes the equipment at an extremely low price—only \$4.95 list. It guarantees improved reproduction. Minimizes inventory problem. One cartridge with choice of two output voltages covers bulk of requirements.

SPECIAL FEATURES:

1. "Lever Type" construction assures improved tracking.
2. Specially designed needle guard which protects crystal from breakage.
3. Equipped with pin jacks and pin terminals.
4. If used for high output, the condenser may be used separately by the serviceman for other purposes.

MODEL W42BH — CODE: RUVUS
LIST PRICE \$4.95



At Your Shure Distributor

FREE! THE WONDERFUL NEW CARTRIDGE Replacement Manual No. 66

Contains over 1500 Phonographs—Radio-TV Phono Combinations equipped with or which can effectively use Shure crystal or ceramic cartridges. These sets are made by 123 manufacturers and date from 1938 to 1951.

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE

SHURE BROTHERS, Inc.
225 W. Huron St., Chicago 10, Illinois



MANUFACTURERS of
MICROPHONES and ACOUSTIC DEVICES
Cable Address: SHUREMICRO

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 11)

scribed below), of T6. C71 is now 1 μ f, and R50 is 2,200 ohms.

R54, which went from R17 to pick-off coil T8, has been deleted. C72 has also been deleted. R99, to tap 5 of T6, has been deleted. T6 has been changed (see parts-list changes listed below), and now has an additional winding which is located between the winding for the filaments on the 1X2 and the winding going to the plate of the 1X2.

The value of R82 is changed from 1 megohm to 220,000 ohms, and the lead goes to tap 6 of T6, instead of to tap 5. C98 is changed from 75 μ f to 82 μ f. R87 is changed from 1.5 megohms to 680,000 ohms. C110 has been relocated and now goes from R87 to the junction of C112, R96, and R97. The value of C110 is changed from 220 μ f to 22 μ f, 500 volts. R95 has been deleted and the value of C111 is changed from 680 ohms to 820 ohms. Pin 8 of tube 17, the 6BQ6 pulse amplifier, is now tied to pin 2 of the same tube.

The change in parts list is as follows:

Ref. No.	Part No.	Description
C60	C-8F3-112	82 μ f, mica
C63	C-8F-18569	22 μ f, mica
C70	B-8D-18491	0.1 μ f, paper
C71	A-8G-12495-2	1 μ f, ceramic
C98	C-8F3-112	82 μ f, mica
C110	C-8G-11892	22 μ f, 500 volts, ceramic
C111	C-8F6-124	820 μ f, mica
R34	C-9B1-82	47,000 ohms, 1/2 watt
R35	C-9B1-74	10,000 ohms, 1/2 watt
R37	C-9B1-73	8,200 ohms, 1/2 watt
R38	C-9B2-68	3,300 ohms, 1 watt
R40	C-9B1-74	100 ohms, 1/2 watt
R50	C-9B1-66	2,200 ohms, 1/2 watt
R82	C-9B1-90	220,000 ohms, 1/2 watt
R87	C-9B1-96	680,000 ohms, 1/2 watt

Code 14. R44 is changed from 3 1/2 megohms to 10,000 ohms, 1/2 watt (C-9B1-74).

Code 15. The value of R56 is changed from 68 ohms to 120 ohms, 1/2 watt (C-9B1-51).

Ref. No.	Part No.	Description
C61	A-8C-18487	30-30 μ f x 450 volts, 125 μ f x 25 volts
	B-5B-18552-85	Tuning knob (vernier)
	B-2M-18553	Vernier disk
	B-55P-18638	Focus magnet
	A-51A-15713	Iron core, for L4, 8, 9
	A-10B-18794	Vertical size control (screwdriver shaft)
	A-10B-18795	Linearity size control (screwdriver shaft)

In later production, group numbers (chassis identification numbers) were assigned to each set. The production changes made are explained below:

Code 16 or Group Numbers 6,700 to 8,999. Video trap coil L19 was relocated and connected to pin 7 of the 12AU7 video amplifier, tube 8, and L16. Peaking coil L21 (A-16A-17961) was replaced with A-16A-18685 (white dot). The high-voltage capacitor and socket assembly (N-201-18161) was removed and replaced with a water tube socket (A-15C-18735), high-voltage ring (A-62C-18734), two insulators (A-5M-18733), and mounting hardware. A 2.2-ohm, 1/2-watt, wire-bound resistor (C-9C1-1067) or a filament choke (A-16A-18785) was added in series with the 1X2 filament lead as shown in Fig. 3.

Code 17 or Group Numbers 9,000 to 12,399. To reduce capacitor failures, capacitor C64 is replaced with a 0.01- μ f, 600-volt capacitor (C-8D-11128).

Code 18 or Group Numbers 12,400 to 14,199. To reduce horizontal size, the white and black leads to the horizontal-deflection transformer T6, lugs 2 and 3, respectively, were interchanged, black to lug 2 and white to lug 3.

Code 19 or Group Numbers 14,200 and above.

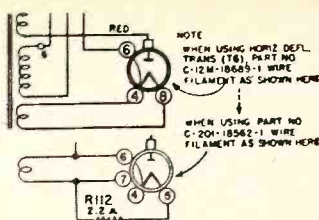


Fig. 3. Wiring for the 1X2 filament lead of the Gamble-Skogmo 94TV1-43-8940A.

Both the C-12M-18689 and C-201-18562 horizontal-deflection transformers were removed and replaced with new transformers. The part numbers are the same with the addition of a dash one (-1). The black and white horizontal-deflection-transformer leads are connected as in Code 17. Resistor R4 is changed to 10,000 ohms. Resistors R8 and R10 are grounded, C33 has been deleted, and the tuner chassis filament wiring has been changed. Pin 4 of the 6AG5 is grounded, pin 3 of the same tube and pin 3 of the 6J6 are tied to tuner terminal 8 and go to H. Pin 4 of the 6J6 is grounded. C30, C31, and C32 have been deleted. C25, C27 and C28 have been deleted. The value of R45 is changed to 220,000 ohms (C-9B1-90), and a resistor R110, 220,000 ohms, 1/2 watt (C-9B1-90) has been added from pin 5 of the 6SL7 sync amplifier, tube 9-A, to ground. R28 is changed to 120 ohms.

Resistor R109 has been added across transformer T1, from pin 5 to pin 6 of the 6AU6 3rd i.f. The value of resistor R107 (see Code 11) has been changed from 3900 ohms to 5600 ohms. To eliminate vertical jitters, R73 is changed to 68,000 ohms (C-9B1-84). R72

is changed to 1.5 megohms (C-9B1-100). C95 is changed to 0.02 μ f (C-8D-17607). C106 is changed to 0.1 μ f (C-8D-10771). Capacitor C91 is deleted. C90 has been relocated to between R77 and C95, and its value has been changed to 0.005 μ f (C-8D-17608). A dual control and switch (A-10A-18441) has been added to the parts list. Resistor R3 has been deleted from lug 2 (antenna input). Lug 2 is now connected directly to lug 4, 1 and 3 are connected to the antenna input terminals.

Five different horizontal deflection transformers T6 have been used on the various production runs.

1. Chassis Coded 1 through 12. These chassis use part number C-12M-18285 transformer. This is a laminated iron core transformer with a 5-lug terminal board. This transformer should be used for replacement. The C-12M-18689 transformer can be used for replacement if the agc leads are removed from lugs 5 and 6 (left hanging free) and a 1-megohm, 1-watt resistor is added from lug 5 to the blue 6BQ6 plate lead terminal. If horizontal non-linearity (left-hand bulge) is noticed on any of these chassis, it may be corrected by reversing the leads connected to terminals 2 and 3.

2. Chassis Coded 13 through 15 and Group Numbers to 14,200. These chassis use either part number C-12M-18689 or part number C-201-18562 transformers. The C-12M-18689 is a laminated iron core transformer with a 6-lug terminal board, and the C-201-18562 is a molded iron core transformer (racetrack shape) with 5 lugs on one side of the terminal (Continued on page 15)


ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

The NEW ESPEY model 511-B FEATURES

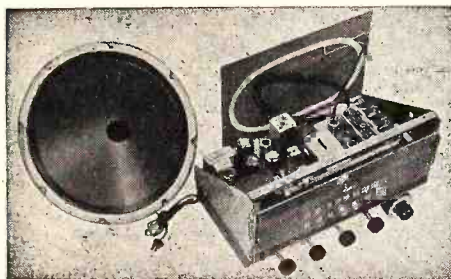1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

Makers of fine radios since 1928.

ESPEY TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.

SHURE

2

New phono pickup cartridges to help simplify cartridge replacement



Model W22AB-T
TURNOVER CARTRIDGE

WHAT IT IS:

A high quality extended range "Vertical Drive" Cartridge complete with positive turnover mechanism. Has sapphire tipped fine-groove and osmium tipped standard-groove needle.

WHAT IT DOES:

Offers greatly improved performance when used as replacement for single-needle all purpose cartridge. Also recommended for replacement of other types of turnover and dual-needle cartridges. Replaces not only cartridge but turnover mechanism as well.

SPECIAL FEATURES:

1. Extended frequency response to 10,000 c. p. s.
2. Tracks at low needle point pressure—only 8 grams.
3. Sturdy construction guarantees long life of turnover mechanism.
4. Standard $\frac{1}{2}$ " bracket mount has elongated holes for versatility and quick easy installation.

MODEL W22AB-T — CODE: RUVUR
LIST PRICE \$10.00



Model W42BH
"DUAL-VOLTAGE CARTRIDGE"

WHAT IT IS:

A low cost "Lever Type" Cartridge for 78 RPM records. Equipped with unique "slip on" condenser-harness for dual-voltage output. 1.5 volts or 3.75 volts obtainable in one cartridge.

WHAT IT DOES:

Gives servicemen an ideal replacement for old style 78 RPM cartridges. A "leader" value—it modernizes the equipment at an extremely low price—only \$4.95 list. It guarantees improved reproduction. Minimizes inventory problem. One cartridge with choice of two output voltages covers bulk of requirements.

SPECIAL FEATURES:

1. "Lever Type" construction assures improved tracking.
2. Specially designed needle guard which protects crystal from breakage.
3. Equipped with pin jacks and pin terminals.
4. If used for high output, the condenser may be used separately by the serviceman for other purposes.

MODEL W42BH — CODE: RUVUS
LIST PRICE \$4.95



At Your Shure Distributor

FREE!

THE WONDERFUL NEW CARTRIDGE Replacement Manual No. 66

Contains over 1500 Phonographs—Radio-TV Phono Combinations equipped with or which can effectively use Shure crystal or ceramic cartridges. These sets are made by 123 manufacturers and date from 1938 to 1951.

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE BROTHERS, Inc.
225 W. Huron St., Chicago 10, Illinois



MANUFACTURERS of
MICROPHONES and ACOUSTIC DEVICES
Cable Address: SHUREMICRO

Please mention Successful Servicing when answering advertising.

SHURE

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 11)

scribed below), of T6. C71 is now 1 μ f, and R50 is 2,200 ohms.

R54, which went from R17 to pick-off coil T8, has been deleted. C72 has also been deleted. R99, to tap 5 of T6, has been deleted. T6 has been changed (see parts-list changes listed below), and now has an additional winding which is located between the winding for the filaments on the 1X2 and the winding going to the plate of the 1X2.

The value of R82 is changed from 1 megohm to 220,000 ohms, and the lead goes to tap 6 of T6, instead of to tap 5. C98 is changed from 75 μ f to 82 μ f. R87 is changed from 1.5 megohms to 680,000 ohms. C110 has been relocated and now goes from R87 to the junction of C112, R96, and R97. The value of C110 is changed from 220 μ f to 22 μ f, 500 volts. R95 has been deleted and the value of C111 is changed from 680 ohms to 820 ohms. Pin 8 of tube 17, the 6BQ6 pulse amplifier, is now tied to pin 2 of the same tube.

The change in parts list is as follows:

Ref. No.	Part No.	Description
C60	C-8F3-112	82 μ f, mica
C63	C-8P-18569	22 μ f, mica
C70	B-8D-18491	0.1 μ f, paper
C71	A-8G-12495-2	1 μ f, ceramic
C98	C-8F3-112	82 μ f, mica
C110	C-8G-11892	22 μ f, 500 volts, ceramic
C111	C-8F6-124	820 μ f, mica
R34	C-9B1-82	47,000 ohms, 1/2 watt
R35	C-9B1-74	10,000 ohms, 1/2 watt
R37	C-9B1-73	8,200 ohms, 1/2 watt
R38	C-9B2-68	3,300 ohms, 1 watt
R40	C-9B1-74	100 ohms, 1/2 watt
R50	C-9B1-66	2,200 ohms, 1/2 watt
R82	C-9B1-90	220,000 ohms, 1/2 watt
R87	C-9B1-96	680,000 ohms, 1/2 watt

Code 14. R44 is changed from 3.3 megohms to 10,000 ohms, 1/2 watt (C-9B1-74).

Code 15. The value of R56 is changed from 68 ohms to 120 ohms, 1/2 watt (C-9B1-51).

Ref. No.	Part No.	Description
C61	A-8C-18487	30-30 μ f x 450 volts, 125 μ f x 25 volts
	B-5B-18552-85	Tuning knob (vernier)
	B-2M-18553	Vernier disk
	B-55P-18638	Focus magnet
	A-51A-15713	Iron core, for L4, 8, 9
	A-10B-18794	Vertical size control (screwdriver shaft)
	A-10B-18795	Linearity size control (screwdriver shaft)

In later production, group numbers (chassis identification numbers) were assigned to each set. The production changes made are explained below:

Code 16 or Group Numbers 6,700 to 8,999. Video trap coil L19 was relocated and connected to pin 7 of the 12AU7 video amplifier, tube 8, and L16. Peaking coil L21 (A-16A-17961) was replaced with A-16A-18685 (white dot). The high-voltage capacitor and socket assembly (N-201-18161) was removed and replaced with a wafer tube socket (A-15C-18735), high-voltage ring (A-62C-18734), two insulators (A-5M-18733), and mounting hardware. A 2.2-ohm, 1/2-watt, wire-bound resistor (C-9C1-1067) or a filament choke (A-16A-18785) was added in series with the 1X2 filament lead as shown in Fig. 3.

Code 17 or Group Numbers 9,000 to 12,399. To reduce capacitor failures, capacitor C64 is replaced with a 0.01- μ f, 600-volt capacitor (C-8D-11128).

Code 18 or Group Numbers 12,400 to 14,199. To reduce horizontal size, the white and black leads to the horizontal-deflection transformer T6, lugs 2 and 3, respectively, were interchanged, black to lug 2 and white to lug 3.

Code 19 or Group Numbers 14,200 and above.

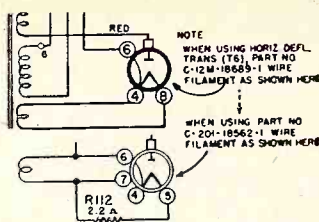


Fig. 3. Wiring for the 1X2 filament lead of the Gamble-Skogmo 94TV1-43-8940A.

Both the C-12M-18689 and C-201-18562 horizontal-deflection transformers were removed and replaced with new transformers. The part numbers are the same with the addition of a dash one (-1). The black and white horizontal-deflection-transformer leads are connected as in Code 17. Resistor R4 is changed to 10,000 ohms. Resistors R8 and R10 are grounded, C33 has been deleted, and the tuner chassis filament wiring has been changed. Pin 4 of the 6AG5 is grounded, pin 3 of the same tube and pin 3 of the 6J6 are tied to tuner terminal 8 and go to H. Pin 4 of the 6J6 is grounded. C30, C31, and C32 have been deleted. C25, C27 and C28 have been deleted. The value of R45 is changed to 220,000 ohms (C-9B1-90), and a resistor R110, 220,000 ohms, 1/2 watt (C-9B1-90) has been added from pin 5 of the 6SL7 sync amplifier, tube 9-A, to ground. R28 is changed to 120 ohms.

Resistor R109 has been added across transformer T1, from pin 5 to pin 6 of the 6AU6 3rd i.f. The value of resistor R107 (see Code 11) has been changed from 3900 ohms to 5600 ohms. To eliminate vertical jitters, R73 is changed to 68,000 ohms (C-9B1-84). R72

is changed to 1.5 megohms (C-9B1-100). C95 is changed to 0.02 μ f (C-8D-17607). C106 is changed to 0.1 μ f (C-8D-10771). Capacitor C91 is deleted. C90 has been relocated to between R77 and C95, and its value has been changed to 0.005 μ f (C-8D-17608). A dual control and switch (A-10A-18441) has been added to the parts list. Resistor R3 has been deleted from lug 2 (antenna input). Lug 2 is now connected directly to lug 4, 1 and 3 are connected to the antenna input terminals.

Five different horizontal deflection transformers T6 have been used on the various production runs.

1. Chassis Coded 1 through 12. These chassis use part number C-12M-18285 transformer. This is a laminated iron core transformer with a 5-lug terminal board. This transformer should be used for replacement. The C-12M-18689 transformer can be used for replacement if the agc leads are removed from lugs 5 and 6 (left hanging free) and a 1-megohm, 1-watt resistor is added from lug 5 to the blue 6BQ6 plate lead terminal. If horizontal non-linearity (left-hand bulge) is noticed on any of these chassis, it may be corrected by reversing the leads connected to terminals 2 and 3.

2. Chassis Coded 13 through 15 and Group Numbers to 14,200. These chassis use either part number C-12M-18689 or part number C-201-18562 transformers. The C-12M-18689 is a laminated iron core transformer with a 6-lug terminal board, and the C-201-18562 is a molded iron core transformer (racetrack shape) with 5 lugs on one side of the terminal (Continued on page 15)


ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

The NEW ESPEY model 511-B FEATURES

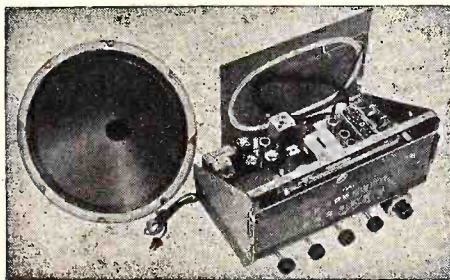1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

Makers of fine radios since 1928.

ESPEY TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.

SHURE

2

New phono pickup cartridges to help simplify cartridge replacement



Model W22AB-T
TURNOVER CARTRIDGE

WHAT IT IS:

A high quality extended range "Vertical Drive" Cartridge complete with positive turnover mechanism. Has sapphire tipped fine-groove and osmium tipped standard-groove needle.

WHAT IT DOES:

Offers greatly improved performance when used as replacement for single-needle all purpose cartridge. Also recommended for replacement of other types of turnover and dual-needle cartridges. Replaces not only cartridge but turnover mechanism as well.

SPECIAL FEATURES:

1. Extended frequency response to 10,000 c. p. s.
2. Tracks at low needle point pressure—only 8 grams.
3. Sturdy construction guarantees long life of turnover mechanism.
4. Standard 1/2" bracket mount has elongated holes for versatility and quick easy installation.

MODEL W22AB-T — CODE: RUVUR
LIST PRICE \$10.00



Model W42BH
"DUAL-VOLTAGE CARTRIDGE"

WHAT IT IS:

A low cost "Lever Type" Cartridge for 78 RPM records. Equipped with unique "slip on" condenser-harness for dual-voltage output. 1.5 volts or 3.75 volts obtainable in one cartridge.

WHAT IT DOES:

Gives servicemen an ideal replacement for old style 78 RPM cartridges. A "leader" value—it modernizes the equipment at an extremely low price—only \$4.95 list. It guarantees improved reproduction. Minimizes inventory problem. One cartridge with choice of two output voltages covers bulk of requirements.

SPECIAL FEATURES:

1. "Lever Type" construction assures improved tracking.
2. Specially designed needle guard which protects crystal from breakage.
3. Equipped with pin jacks and pin terminals.
4. If used for high output, the condenser may be used separately by the serviceman for other purposes.

MODEL W42BH — CODE: RUVUS
LIST PRICE \$4.95



At Your Shure Distributor

FREE!

THE WONDERFUL NEW CARTRIDGE Replacement Manual No. 66

Contains over 1500 Phonographs—Radio-TV Phono Combinations equipped with or which can effectively use Shure crystal or ceramic cartridges. These sets are made by 123 manufacturers and date from 1938 to 1951.

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE BROTHERS, Inc.
225 W. Huron St., Chicago 10, Illinois



MANUFACTURERS of
MICROPHONES and ACOUSTIC DEVICES
Cable Address: SHUREMICRO

Please mention Successful Servicing when answering advertising.

SHURE

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 11)

scribed below), of T6. C71 is now 1 μ f, and R50 is 2,200 ohms.

R54, which went from R17 to pick-off of T8, has been deleted. C72 has also been deleted. R99, to tap 5 of T6, has been deleted. T6 has been changed (see parts-list changes listed below), and now has an additional winding which is located between the winding for the filaments on the 1X2 and the winding going to the plate of the 1X2.

The value of R82 is changed from 1 megohm to 220,000 ohms, and the lead goes to tap 6 of T6, instead of to tap 5. C98 is changed from 75 μ f to 82 μ f. R87 is changed from 1.5 megohms to 680,000 ohms. C110 is being relocated and now goes from R87 to the junction of C112, R96, and R97. The value

C110 is changed from 220 μ f to 22 μ f. R95 has been deleted and the value of C111 is changed from 680 ohms to 10 ohms. Pin 8 of tube 17, the 6BQ6 pulse amplifier, is now tied to pin 2 of the same tube.

The change in parts list is as follows:

Ref. No.	Part No.	Description
	C-8F3-112	82 μ f, mica
	C-8F-18569	22 μ f, mica
	B-8D-18491	0.1 μ f, paper
	A-8G-12495-2	1 μ f, ceramic
C98	C-8F3-112	82 μ f, mica
C110	C-8G-11892	22 μ f, 500 volts, ceram
C111	C-8F6-124	820 μ f, mica
R34	C-9B1-82	47,000 ohms, 1/2 watt
R35	C-9B1-74	10,000 ohms, 1/2 watt
R37	C-9B1-73	8,200 ohms, 1/2 watt
R38	C-9B2-68	3,300 ohms, 1 watt
	C-9B1-74	100 ohms, 1/2 watt
	C-9B1-66	2,200 ohms, 1/2 watt
	C-9B1-90	220,000 ohms, 1/2 watt
	C-9B1-96	680,000 ohms, 1/2 watt

Code 14. R44 is changed from 3.3 megohms to 10,000 ohms, 1/2 watt (C-9B1-74).

Code 15. The value of R56 is changed from 68 ohms to 120 ohms, 1/2 watt (C-9B1-51).

Ref. No.	Part No.	Description
C61	A-8C-18487	30-30 μ f x 450 volts, 35 μ f x 25 volts
	B-5B-18552-85	Tuning knob (vernier)
	B-2M-18553	Vernier disk
	B-5SP-18638	Focus magnet
	A-51A-15713	Iron core, for L4, 8, 9
	A-10B-18794	Vertical size control (screwdriver shaft)
	A-10B-18795	Linearity size control (screwdriver shaft)

In later production, group numbers (chassis identification numbers) were assigned to each set. The production changes made are explained below:

Code 16 or Group Numbers 6,700 to 8,799.

The trap coil L19 was relocated and connected to pin 7 of the 12AU7 video amplifier, tube 8, and L16. Peaking coil L21 (A-1A-17961) was replaced with A-16A-1835 (white dot). The high-voltage capacitor in the socket assembly (N-201-18161) was removed and replaced with a wafer tube socket (A-1A-18735), high-voltage ring (A-6C-18734), two insulators (A-5M-18733), and mounting hardware. A 2.2-ohm, 1/2-watt, wire-bound resistor (C-9C1-1067) or a filament choke (A-16A-18785) was added in series with the 1X2 filament lead as shown in Fig. 3.

Code 17 or Group Numbers 9,000 to 12,999. To reduce capacitor failures, capacitor 54 is replaced with a 0.01- μ f, 600-volt capacitor (C-8D-11128).

Code 18 or Group Numbers 12,400 to 14,999. To reduce horizontal size, the white and black leads to the horizontal-deflection transformer T6, lugs 2 and 3, respectively, were interchanged, black to lug 2 and white to lug 3.

Code 19 or Group Numbers 14,200 and above.

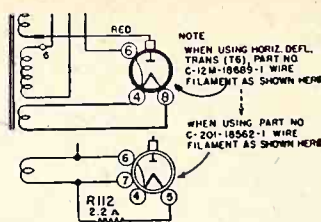


Fig. 3. Wiring for the 1X2 filament lead of the Gamble-Skogmo 94TV1-43-8940A.

Both the C-12M-18689 and C-201-18562 horizontal-deflection transformers were removed and replaced with new transformers. The part numbers are the same with the addition of a dash one (-1). The black and white horizontal-deflection-transformer leads are connected as in Code 17. Resistor R4 is changed to 10,000 ohms. Resistors R8 and R10 are grounded, C33 has been deleted, and the tuner chassis filament wiring has been changed. Pin 4 of the 6AG5 is grounded, pin 3 of the same tube and pin 3 of the 6J6 are tied to tuner terminal 8 and go to H. Pin 4 of the 6J6 is grounded. C30, C31, and C32 have been deleted. C25, C27 and C28 have been deleted. The value of R45 is changed to 220,000 ohms (C-9B1-90), and a resistor R110, 220,000 ohms, 1/2 watt (C-9B1-90) has been added from pin 5 of the 6SL7 sync amplifier, tube 9-A, to ground. R28 is changed to 120 ohms.

Resistor R109 has been added across transformer T1, from pin 5 to pin 6 of the 6AU6 3rd i.f. The value of resistor R107 (see Code 11) has been changed from 3900 ohms to 5600 ohms. To eliminate vertical jitters, R73 is changed to 68,000 ohms (C-9B1-84). R72

is changed to 1.5 megohms (C-9B1-100). C95 is changed to 0.02 μ f (C-8D-17607). C106 is changed to 0.1 μ f (C-8D-10771). Capacitor C91 is deleted. C90 has been relocated to between R77 and C95, and its value has been changed to 0.005 μ f (C-8D-17608). A dual control and switch (A-10A-18441) has been added to the parts list. Resistor R3 has been deleted from lug 2 (antenna input). Lug 2 is now connected directly to lug 4, 1 and 3 are connected to the antenna input terminals.

Five different horizontal deflection transformers T6 have been used on the various production runs.

1. Chassis Coded 1 through 12. These chassis use part number C-12M-18285 transformer. This is a laminated iron core transformer with a 5-lug terminal board. This transformer should be used for replacement. The C-12M-18689 transformer can be used for replacement if the age leads are removed from lugs 5 and 6 (left hanging free) and a 1-megohm, 1-watt resistor is added from lug 5 to the blue 6BQ6 plate lead terminal. If horizontal non-linearity (left-hand bulge) is noticed on any of these chassis, it may be corrected by reversing the leads connected to terminals 2 and 3.

2. Chassis Coded 13 through 15 and Group Numbers to 14,200. These chassis use either part number C-12M-18689 or part number C-201-18562 transformers. The C-12M-18689 is a laminated iron core transformer with a 6-lug terminal board, and the C-201-18562 is a molded iron core transformer (racetrack shape) with 5 lugs on one side of the terminal (Continued on page 15)


ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

The NEW ESPEY model 511-B FEATURES

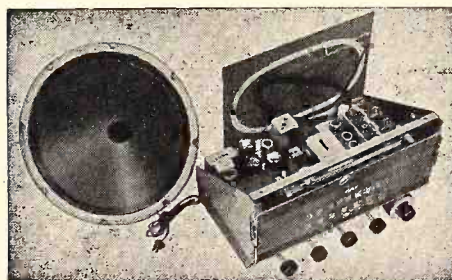1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Tuning.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with or without crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered under symbol #174.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

Made in U.S.A. since 1928.





You wouldn't want a car that drives only in circles!

Of course not. What you want is a car that will go where you want it to go. And so it is with volume controls, too... a survey of hundreds of servicemen revealed the importance you place on adaptability to the job at hand. Naturally, you want a control that is easily tailored to *any* job.

Make Sure! Make it Mallory!


Using the Mallory Midgetrol* helps you make sure that the installation is exactly as you want it... easier for you and insuring complete customer satisfaction.

There are three big reasons why the Midgetrol $\frac{15}{16}$ " control does a better job... because the *permanently fixed tubular brass shaft* can be adapted for any popular knob in a few seconds... because AC switch attachment is simple and positive... because the precision-controlled carbon element gives

smoother taper, quieter operation, more accurate resistance value and less drift in TV sets.

These same advantages are available in the Dual Concentric Midgetrol, tailor-made on the job to match each specific requirement. It is assembled in five easy steps, in less than five minutes, using complete, *factory-inspected* control sections. You can make over 10,000 different combinations from sub-assemblies available in distributor stocks.

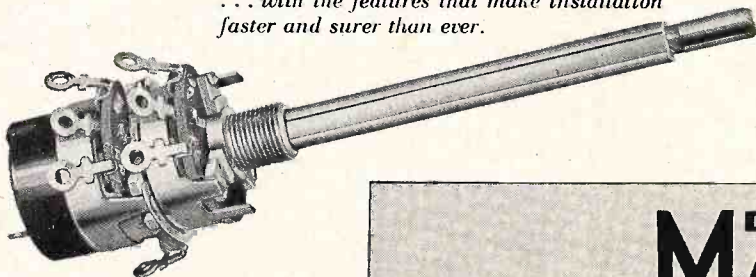Make it Mallory and make sure! Ask your distributor to show you the Mallory Midgetrol... with the features that make installation faster and surer than ever.



Complete Dual Concentric Midgetrol illustrated. Single section control available in complete line of resistance values.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 13)

board and two on the other. These transformers are interchangeable except for resistor R-107 (3900 ohms, 2 watts). Resistor R-107 is used only with the C-201-18562 transformer. If horizontal non-linearity is noticed on any of these chassis, reverse the leads connected to terminals 2 and 3 or add a 2900-ohm resistor. If the C-12M-18689 transformer is used, the 3900-ohm, 2-watt resistor should be added, and if the C-201-18562 transformer is used, another 3900-ohm, 2-watt resistor should be used in parallel with the one wired in the chassis. These changes have been made in receivers that were converted. Converted receivers can be identified by a dot behind the Model No. on the decal or chassis.

3. Chassis with Group Numbers 14,200 and up. These chassis use either part number C-12M-18689-1 or a C-201-18562-1 transformer. The dash one transformers are identical, except they have fewer turns on the output section. These transformers are interchangeable.

Crosley 11-442MU, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472BU, 11-474BU, 11-483BU, Ch. 331, 331-1, 331-2; 11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2


Chassis 331-1 and 331-2 are similar to Chassis 331 except for the changes noted below. Chassis 323-1 and 323-2 are similar to Chassis 323 except for the changes noted below.

Chassis 323-1 and 331-1 are equipped with a 6T8 tube (V110A, V110B) mounted on a plate and socket assembly (Part No. AB-150226). A 0.005- μ f, 500-volt ceramic disc capacitor (Part No. 144675-2) is connected from lug 2 of the socket to ground. All other parts and connections to the socket for Chassis 323-1 and 331-1 are identical to those shown in the schematic wiring diagrams for Chassis 323 and 331, respectively.

Chassis 323-2 and 331-2 are equipped with a 6AL5 tube (V110A) and a 6AV6 tube (V110B), which have their sockets mounted on a socket and plate assembly (Part No. AB-150227). This assembly consists of the parts and wiring shown in the accompanying illustration. Capacitor C183 is a 0.005- μ f, 500-volt, ceramic disk capacitor (Part No. C-144675-2). Resistor R147 is a 3.9-megohm, 10%, 1/2-watt resistor (Part No. 39374-75). The Part No. of the socket is 146966.

The following changes apply to Chassis 331, 331-1, and 331-2, only. The main chassis Parts List for Chassis 331 should include an audio output transformer T103, Part No. 149460. It is used on models equipped with the 5 1/4", 50-ohm, e-m speaker SP101 (Part No. AD-149502). The audio output transformer T110 (Part No. 149654) is used on all models equipped with 10 p-m speakers. The Part No. of the fuse F101 should be W-150431 instead of W-150065. The Part No. of the power cable and plug assembly CA102, used on Models 11-444MU and 11-474BU, should be AW-149652 instead of C-132300-6. The C-132300-6 cable is used on the models that are not equipped with radio and record changer. The Part No. of the springs used on the control access doors is W-149095.

SOMETHING TO REMEMBER

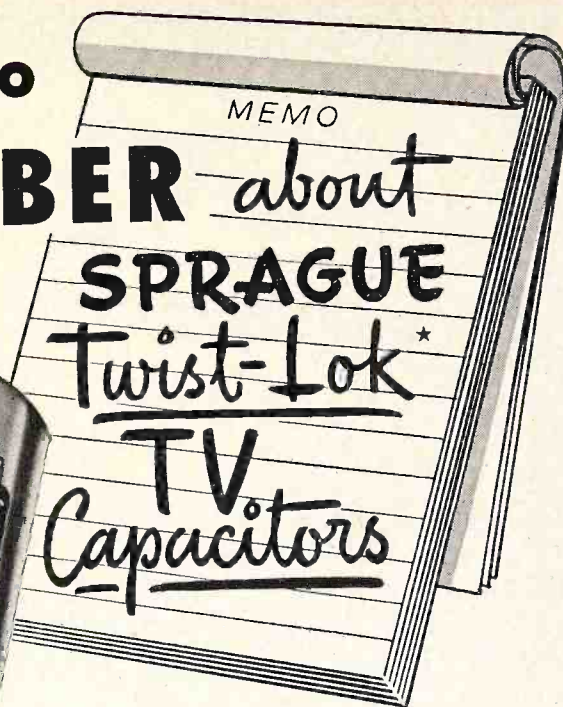

More twist-prong electrolytic capacitors are made by Sprague than by any other manufacturer... And Sprague naturally lists the largest, most complete line for exact TV replacement applications.

And when you use a Sprague Twist-Lok TV Capacitor, you can be sure it's dependable. No costly callbacks will jeopardize your profit or your reputation. Your business judgment will tell you to *accept no substitutes*.

GET YOUR NEW SPRAGUE TV CAPACITOR REPLACEMENT MANUAL TODAY!

Besides making the largest TV capacitor line, Sprague makes it easy for you to pick the correct replacement for practically any television receiver! Just off press, this NEW 3rd edition of the famous Sprague Manual is jam-packed with up-to-the-minute replacement recommendations for critical capacitors in 964 TV sets of more than 60 brand names. FREE from your Sprague parts distributor or send 10c directly to Sprague to cover handling and mailing costs.



★Trademark



PRODUCTS COMPANY

55 Marshall St.
NORTH ADAMS, MASSACHUSETTS
(Distributors' Division of the Sprague Electric Company)

PIONEERS IN ELECTRIC AND ELECTRONIC DEVELOPMENT

Please mention Successful Servicing when answering advertising.

SHURE

2

New phono pickup cartridges to help simplify cartridge replacement



Model W22AB-T
TURNOVER CARTRIDGE

WHAT IT IS:

A high quality extended range "Vertical Drive" Cartridge complete with positive turnover mechanism. Has sapphire tipped fine-groove and osmium tipped standard-groove needle.

WHAT IT DOES:

Offers greatly improved performance when used as replacement for single-needle all purpose cartridge. Also recommended for replacement of other types of turnover and dual-needle cartridges. Replaces not only cartridge but turnover mechanism as well.

SPECIAL FEATURES:

1. Extended frequency response to 10,000 c. p. s.
2. Tracks at low needle point pressure — only 8 grams.
3. Sturdy construction guarantees long life of turnover mechanism.
4. Standard 1/2" bracket mount has elongated holes for versatility and quick easy installation.

MODEL W22AB-T — CODE: RUVUR
LIST PRICE \$10.00



Model W42BH
"DUAL-VOLTAGE CARTRIDGE"

WHAT IT IS:

A low cost "Lever Type" Cartridge for 78 RPM records. Equipped with unique "slip on" condenser-harness for dual-voltage output. 1.5 volts or 3.75 volts obtainable in one cartridge.

WHAT IT DOES:

Gives servicemen an ideal replacement for old style 78 RPM cartridges. A "leader" value — it modernizes the equipment at an extremely low price — only \$4.95 list. It guarantees improved reproduction. Minimizes inventory problem. One cartridge with choice of two output voltages covers bulk of requirements.

SPECIAL FEATURES:

1. "Lever Type" construction assures improved tracking.
2. Specially designed needle guard which protects crystal from breakage.
3. Equipped with pin jacks and pin terminals.
4. If used for high output, the condenser may be used separately by the serviceman for other purposes.

MODEL W42BH — CODE: RUVUS
LIST PRICE \$4.95



At Your Shure Distributor

FREE! THE WONDERFUL NEW CARTRIDGE Replacement Manual No. 66

Contains over 1500 Phonographs—Radio-TV Phono Combinations equipped with or which can effectively use Shure crystal or ceramic cartridges. These sets are made by 123 manufacturers and date from 1938 to 1951.

Patented by Shure Brothers and licensed under the Patents of the Brush Development Company

SHURE BROTHERS, Inc.
225 W. Huron St., Chicago 10, Illinois



MANUFACTURERS of
MICROPHONES and ACOUSTIC DEVICES
Cable Address: SHUREMICRO

Please mention Successful Servicing when answering advertising.

SHURE

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 11)

scribed below), of T6. C71 is now 1 μ f, and R50 is 2,200 ohms.

R54, which went from R17 to pick-off coil T8, has been deleted. C72 has also been deleted. R99, to tap 5 of T6, has been deleted. T6 has been changed (see parts-list changes listed below), and now has an additional winding which is located between the winding for the filaments on the 1X2 and the winding going to the plate of the 1X2.

The value of R82 is changed from 1 megohm to 220,000 ohms, and the lead goes to tap 6 of T6, instead of to tap 5. C98 is changed from 75 μ f to 82 μ f. R87 is changed from 1.5 megohms to 680,000 ohms. C110 has been relocated and now goes from R87 to the junction of C112, R96, and R97. The value of C110 is changed from 220 μ f to 22 μ f, 500 volts. R95 has been deleted and the value of C111 is changed from 680 ohms to 820 ohms. Pin 8 of tube 17, the 6BQ6 pulse amplifier, is now tied to pin 2 of the same tube.

The change in parts list is as follows:

Ref. No.	Part No.	Description
C60	C-8F3-112	82 μ f, mica
C63	C-8F-18569	22 μ f, mica
C70	B-8D-18491	0.1 μ f, paper
C71	A-8G-12495-2	1 μ f, ceramic
C98	C-8F3-112	82 μ f, mica
C110	C-8G-11892	22 μ f, 500 volts, ceramic
C111	C-8F6-124	820 μ f, mica
R34	C-9B1-82	47,000 ohms, 1/2 watt
R35	C-9B1-74	10,000 ohms, 1/2 watt
R37	C-9B1-73	8,200 ohms, 1/2 watt
R38	C-9B2-68	3,300 ohms, 1 watt
R40	C-9B1-74	100 ohms, 1/2 watt
R50	C-9B1-66	2,200 ohms, 1/2 watt
R82	C-9B1-90	220,000 ohms, 1/2 watt
R87	C-9B1-96	680,000 ohms, 1/2 watt

Code 14. R44 is changed from 3.3 megohms to 10,000 ohms, 1/2 watt (C-9B1-74).

Code 15. The value of R56 is changed from 68 ohms to 120 ohms, 1/2 watt (C-9B1-51).

Ref. No.	Part No.	Description
C61	A-8C-18487	30-30 μ f x 450 volts, 125 μ f x 25 volts
	B-5B-18552-85	Tuning knob (vernier)
	B-2M-18553	Vernier disk
	B-55P-18638	Focus magnet
	A-51A-15713	Iron core for L4, 8, 9
	A-10B-18794	Vertical size control (screwdriver shaft)
	A-10B-18795	Linearity size control (screwdriver shaft)

In later production, group numbers (chassis identification numbers) were assigned to each set. The production changes made are explained below:

Code 16 or Group Numbers 6,700 to 8,999. Video trap coil L19 was relocated and connected to pin 7 of the 12AU7 video amplifier, tube 8, and L16. Peaking coil L21 (A-16A-17961) was replaced with A-16A-18685 (white dot). The high-voltage capacitor and socket assembly (N-201-18161) was removed and replaced with a wafer tube socket (A-15C-18735), high-voltage ring (A-62C-18734), two insulators (A-5M-18733), and mounting hardware. A 2.2-ohm, 1/2-watt, wire-bound resistor (C-9C1-1067) or a filament choke (A-16A-18785) was added in series with the 1X2 filament lead as shown in Fig. 3.

Code 17 or Group Numbers 9,000 to 12,399. To reduce capacitor failures, capacitor C64 is replaced with a 0.01- μ f, 600-volt capacitor (C-8D-11128).

Code 18 or Group Numbers 12,400 to 14,199. To reduce horizontal size, the white and black leads to the horizontal-deflection transformer T6, lugs 2 and 3, respectively, were interchanged, black to lug 2 and white to lug 3.

Code 19 or Group Numbers 14,200 and above.

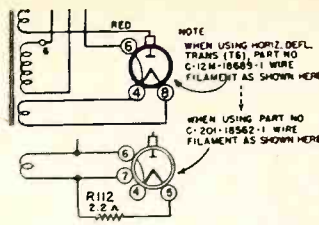


Fig. 3. Wiring for the 1X2 filament lead of the Gamble-Skogmo 94TV1-43-8940A.

Both the C-12M-18689 and C-201-18562 horizontal-deflection transformers were removed and replaced with new transformers. The part numbers are the same with the addition of a dash one (-1). The black and white horizontal-deflection-transformer leads are connected as in Code 17. Resistor R4 is changed to 10,000 ohms. Resistors R8 and R10 are grounded, C33 has been deleted, and the tuner chassis filament wiring has been changed. Pin 4 of the 6AG5 is grounded, pin 3 of the same tube and pin 3 of the 6J6 are tied to tuner terminal 8 and go to H. Pin 4 of the 6J6 is grounded. C30, C31, and C32 have been deleted. C25, C27 and C28 have been deleted. The value of R45 is changed to 220,000 ohms (C-9B1-90), and a resistor R110, 220,000 ohms, 1/2 watt (C-9B1-90) has been added from pin 5 of the 6SL7 sync amplifier, tube 9-A, to ground. R28 is changed to 120 ohms.

Resistor R109 has been added across transformer T1, from pin 5 to pin 6 of the 6AU6 3rd i.f. The value of resistor R107 (see Code 11) has been changed from 3900 ohms to 5600 ohms. To eliminate vertical jitters, R73 is changed to 68,000 ohms (C-9B1-84). R72

is changed to 1.5 megohms (C-9B1-100). C95 is changed to 0.02 μ f (C-8D-17607). C106 is changed to 0.1 μ f (C-8D-10771). Capacitor C91 is deleted. C90 has been relocated to between R77 and C95, and its value has been changed to 0.005 μ f (C-8D-17608). A dual control and switch (A-10A-18441) has been added to the parts list. Resistor R3 has been deleted from lug 2 (antenna input). Lug 2 is now connected directly to lug 4, 1 and 3 are connected to the antenna input terminals.

Five different horizontal deflection transformers T6 have been used on the various production runs.

1. Chassis Coded 1 through 12. These chassis use part number C-12M-18285 transformer. This is a laminated iron core transformer with a 5-lug terminal board. This transformer should be used for replacement. The C-12M-18689 transformer can be used for replacement if the agc leads are removed from lugs 5 and 6 (left hanging free) and a 1-megohm, 1-watt resistor is added from lug 5 to the blue 6BQ6 plate lead terminal. If horizontal non-linearity (left-hand bulge) is noticed on any of these chassis, it may be corrected by reversing the leads connected to terminals 2 and 3.

2. Chassis Coded 13 through 15 and Group Numbers to 14,200. These chassis use either part number C-12M-18689 or part number C-201-18562 transformers. The C-12M-18689 is a laminated iron core transformer with a 6-lug terminal board, and the C-201-18562 is a molded iron core transformer (racetrack shape) with 5 lugs on one side of the terminal (Continued on page 15)


ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED... AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

The NEW ESPEY model 511-B FEATURES

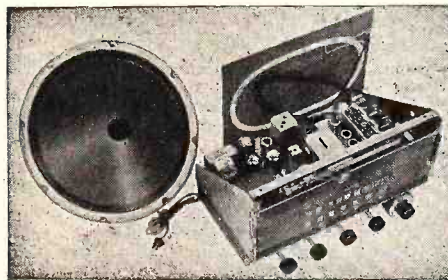1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 Tubes plus rectifier and Pre-Amp Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.
6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 10 watts (max.) Push-Pull Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.



SPECIFICATIONS

Supplies ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.

Chassis Dimensions: 13 1/2" wide x 8 1/2" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 3/4 inches.

Net Weight: 17 pounds each.

Sold through your favorite parts distributor.

WRITE FOR CATALOGUE KD12
AND NAME OF NEAREST DISTRIBUTOR.

Makers of fine radios since 1928.

ESPEY TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.



You wouldn't want a car that drives only in circles!

Of course not. What you want is a car that will go where you want it to go. And so it is with volume controls, too... a survey of hundreds of servicemen revealed the importance you place on adaptability to the job at hand. Naturally, you want a control that is easily tailored to *any* job.

Make Sure! Make it Mallory!


Using the Mallory Midgetrol* helps you make sure that the installation is exactly as you want it... easier for you and insuring complete customer satisfaction.

There are three big reasons why the Midgetrol $15\frac{1}{16}$ " control does a better job... because the *permanently fixed tubular brass shaft* can be adapted for any popular knob in a few seconds... because AC switch attachment is simple and positive... because the precision-controlled carbon element gives

smoother taper, quieter operation, more accurate resistance value and less drift in TV sets.

These same advantages are available in the Dual Concentric Midgetrol, tailor-made on the job to match each specific requirement. It is assembled in five easy steps, in less than five minutes, using complete, *factory-inspected* control sections. You can make over 10,000 different combinations from sub-assemblies available in distributor stocks.

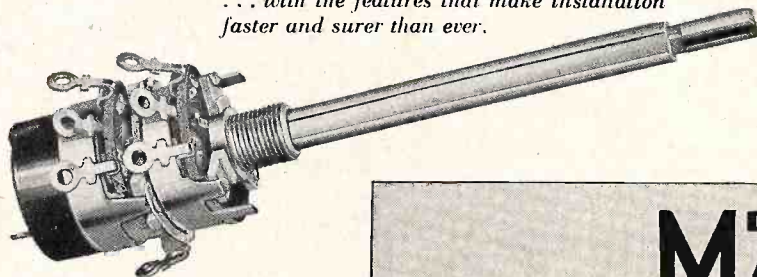Make it Mallory and make sure! Ask your distributor to show you the Mallory Midgetrol... with the features that make installation faster and surer than ever.



Complete Dual Concentric Midgetrol illustrated. Single section control available in complete line of resistance values.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 13)

board and two on the other. These transformers are interchangeable except for resistor R-107 (3900 ohms, 2 watts). Resistor R-107 is used only with the C-201-18562 transformer. If horizontal non-linearity is noticed on any of these chassis, reverse the leads connected to terminals 2 and 3 or add a 2900-ohm resistor. If the C-12M-18689 transformer is used, the 3900-ohm, 2-watt resistor should be added, and if the C-201-18562 transformer is used, another 3900-ohm, 2-watt resistor should be used in parallel with the one wired in the chassis. These changes have been made in receivers that were converted. Converted receivers can be identified by a dot behind the Model No. on the decal or chassis.

3. Chassis with Group Numbers 14,200 and up. These chassis use either part number C-12M-18689-1 or a C-201-18562-1 transformer. The dash one transformers are identical, except they have fewer turns on the output section. These transformers are interchangeable.

Crosley 11-442M1U, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472B1U, 11-474BU, 11-483BU, Ch. 331, 331-1, 331-2; 11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2


Chassis 331-1 and 331-2 are similar to Chassis 331 except for the changes noted below. Chassis 323-1 and 323-2 are similar to Chassis 323 except for the changes noted below.

Chassis 323-1 and 331-1 are equipped with a 6T8 tube (V110A, V110B) mounted on a plate and socket assembly (Part No. AB-150226). A 0.005- μ f, 500-volt ceramic disc capacitor (Part No. 144675-2) is connected from lug 2 of the socket to ground. All other parts and connections to the socket for Chassis 323-1 and 331-1 are identical to those shown in the schematic wiring diagrams for Chassis 323 and 331, respectively.

Chassis 323-2 and 331-2 are equipped with a 6AL5 tube (V110A) and a 6AV6 tube (V110B), which have their sockets mounted on a socket and plate assembly (Part No. AB-150227). This assembly consists of the parts and wiring shown in the accompanying illustration. Capacitor C183 is a 0.005- μ f, 500-volt, ceramic disk capacitor (Part No. C-144675-2). Resistor R147 is a 3.9-megohm, 10%, 1/2-watt resistor (Part No. 39374-75). The Part No. of the socket is 146966.

The following changes apply to Chassis 331, 331-1, and 331-2, only. The main chassis Parts List for Chassis 331 should include an audio output transformer T103, Part No. 149460. It is used on models equipped with the 5 1/4", 50-ohm, e-m speaker SP101 (Part No. AD-149502). The audio output transformer T110 (Part No. 149654) is used on all models equipped with 10 p-m speakers. The Part No. of the fuse F101 should be W-150431 instead of W-150065. The Part No. of the power cable and plug assembly CA102, used on Models 11-444MU and 11-474BU, should be AW-149652 instead of C-132300-6. The C-132300-6 cable is used on the models that are not equipped with radio and record changer. The Part No. of the springs used on the control access doors is W-149095.

SOMETHING TO REMEMBER

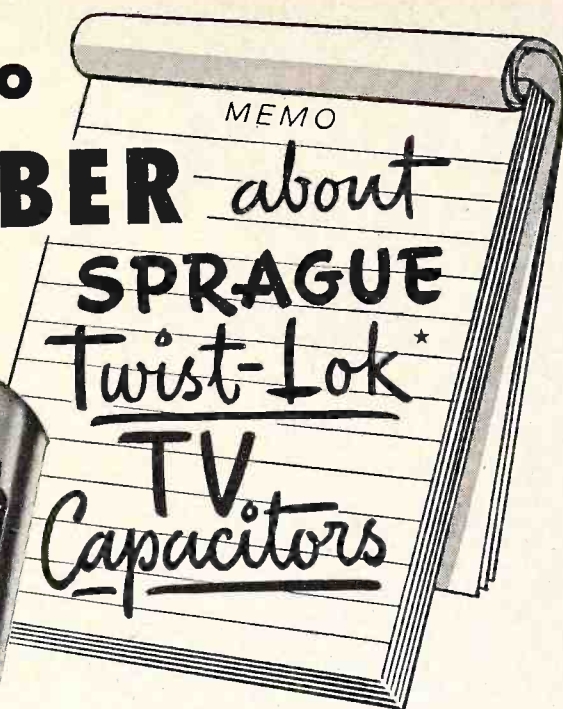

● More twist-prong electrolytic capacitors are made by Sprague than by any other manufacturer... And Sprague naturally lists the largest, most complete line for exact TV replacement applications.

● And when you use a Sprague Twist-Lok TV Capacitor, you can be sure it's dependable. No costly callbacks will jeopardize your profit or your reputation. Your business judgment will tell you to *accept no substitutes*.

GET YOUR NEW SPRAGUE TV CAPACITOR REPLACEMENT MANUAL TODAY!

Besides making the largest TV capacitor line, Sprague makes it easy for you to pick the correct replacement for practically any television receiver! Just off press, this NEW 3rd edition of the famous Sprague Manual is jam-packed with up-to-the-minute replacement recommendations for critical capacitors in 964 TV sets of more than 60 brand names.

FREE from your Sprague parts distributor or send 10c directly to Sprague to cover handling and mailing costs.



★Trademark



PRODUCTS COMPANY

55 Marshall St.

NORTH ADAMS, MASSACHUSETTS

(Distributors' Division of the Sprague Electric Company)

PIONEERS IN ELECTRIC AND ELECTRONIC DEVELOPMENT

Please mention Successful Servicing when answering advertising.



You wouldn't want a car that drives only in circles!

Of course not. What you want is a car that will go where you want it to go. And so it is with volume controls, too... a survey of hundreds of servicemen revealed the importance you place on adaptability to the job at hand. Naturally, you want a control that is easily tailored to *any* job.

Make Sure! Make it Mallory!


Using the Mallory Midgetrol* helps you make sure that the installation is exactly as you want it... easier for you and insuring complete customer satisfaction.

There are three big reasons why the Midgetrol $1\frac{5}{16}$ " control does a better job... because the *permanently fixed tubular brass shaft* can be adapted for any popular knob in a few seconds... because AC switch attachment is simple and positive... because the precision-controlled carbon element gives

smoother taper, quieter operation, more accurate resistance value and less drift in TV sets.

These same advantages are available in the Dual Concentric Midgetrol, tailor-made on the job to match each specific requirement. It is assembled in five easy steps, in less than five minutes, using complete, *factory-inspected* control sections. You can make over 10,000 different combinations from sub-assemblies available in distributor stocks.

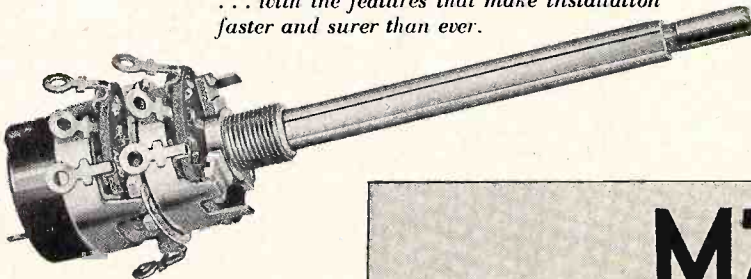Make it Mallory and make sure! Ask your distributor to show you the Mallory Midgetrol... with the features that make installation faster and surer than ever.



Complete Dual Concentric Midgetrol illustrated. Single section control available in complete line of resistance values.

PR MALLORY CO Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 13)

board and two on the other. These transformers are interchangeable except for resistor R-107 (3900 ohms, 2 watts). Resistor R-107 is used only with the C-201-18562 transformer. If horizontal non-linearity is noticed on any of these chassis, reverse the leads connected to terminals 2 and 3 or add a 2900-ohm resistor. If the C-12M-18689 transformer is used, the 3900-ohm, 2-watt resistor should be added, and if the C-201-18562 transformer is used, another 3900-ohm, 2-watt resistor should be used in parallel with the one wired in the chassis. These changes have been made in receivers that were converted. Converted receivers can be identified by a dot behind the Model No. on the decal or chassis.

3. Chassis with Group Numbers 14,200 and up. These chassis use either part number C-12M-18689-1 or a C-201-18562-1 transformer. The dash one transformers are identical, except they have fewer turns on the output section. These transformers are interchangeable.

Crosley 11-442M1U, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472B1U, 11-474BU, 11-483BU, Ch. 331, 331-1, 331-2; 11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2


Chassis 331-1 and 331-2 are similar to Chassis 331 except for the changes noted below. Chassis 323-1 and 323-2 are similar to Chassis 323 except for the changes noted below.

Chassis 323-1 and 331-1 are equipped with a 6T8 tube (V110A, V110B) mounted on a plate and socket assembly (Part No. AB-150226). A 0.005- μ f, 500-volt ceramic disc capacitor (Part No. 144675-2) is connected from lug 2 of the socket to ground. All other parts and connections to the socket for Chassis 323-1 and 331-1 are identical to those shown in the schematic wiring diagrams for Chassis 323 and 331, respectively.

Chassis 323-2 and 331-2 are equipped with a 6AL5 tube (V110A) and a 6AV6 tube (V110B), which have their sockets mounted on a socket and plate assembly (Part No. AB-150227). This assembly consists of the parts and wiring shown in the accompanying illustration. Capacitor C183 is a 0.005- μ f, 500-volt, ceramic disk capacitor (Part No. C-144675-2). Resistor R147 is a 3.9-megohm, 10%, $\frac{1}{2}$ -watt resistor (Part No. 39374-75). The Part No. of the socket is 146966.

The following changes apply to Chassis 331, 331-1, and 331-2, only. The main chassis Parts List for Chassis 331 should include an audio output transformer T103, Part No. 149460. It is used on models equipped with the $5\frac{1}{4}$ " 50-ohm, e-m speaker SP101 (Part No. AD-149502). The audio output transformer T110 (Part No. 149654) is used on all models equipped with 10 p-m speakers. The Part No. of the fuse F101 should be W-150431 instead of W-150065. The Part No. of the power cable and plug assembly CA102, used on Models 11-444MU and 11-474BU, should be AW-149652 instead of C-132300-6. The C-132300-6 cable is used on the models that are not equipped with radio and record changer. The Part No. of the springs used on the control access doors is W-149095.

SOMETHING TO REMEMBER

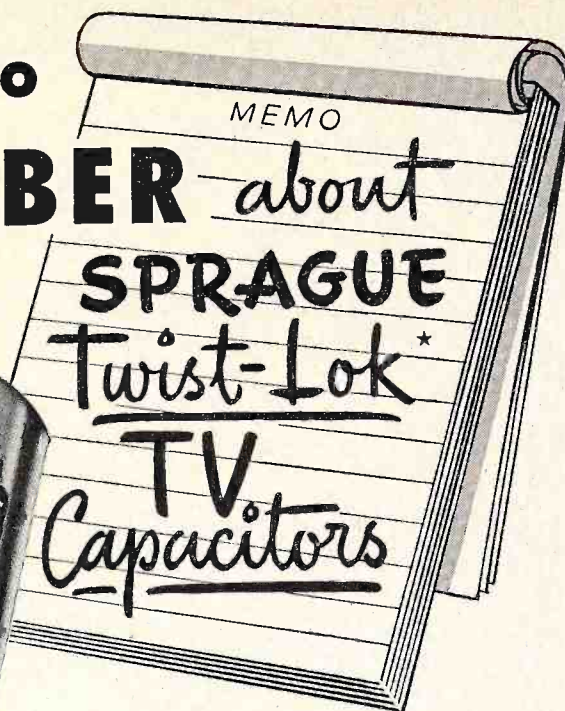

More twist-prong electrolytic capacitors are made by Sprague than by any other manufacturer... And Sprague naturally lists the largest, most complete line for exact TV replacement applications.

And when you use a Sprague Twist-Lok TV Capacitor, you can be sure it's dependable. No costly callbacks will jeopardize your profit or your reputation. Your business judgment will tell you to *accept no substitutes*.

GET YOUR NEW SPRAGUE TV CAPACITOR REPLACEMENT MANUAL TODAY!

Besides making the largest TV capacitor line, Sprague makes it easy for you to pick the correct replacement for practically any television receiver! Just off press, this NEW 3rd edition of the famous Sprague Manual is jam-packed with up-to-the-minute replacement recommendations for critical capacitors in 964 TV sets of more than 60 brand names. FREE from your Sprague parts distributor or send 10c directly to Sprague to cover handling and mailing costs.



★Trademark



PRODUCTS COMPANY

55 Marshall St.
NORTH ADAMS, MASSACHUSETTS
(Distributors' Division of the Sprague Electric Company)

PIONEERS IN ELECTRIC AND ELECTRONIC DEVELOPMENT

Please mention Successful Servicing when answering advertising.



You wouldn't want a car that drives only in circles!

Of course not. What you want is a car that will go where you want it to go. And so it is with volume controls, too... a survey of hundreds of servicemen revealed the importance you place on adaptability to the job at hand. Naturally, you want a control that is easily tailored to *any* job.

Make Sure! Make it Mallory!


Using the Mallory Midgetrol* helps you make sure that the installation is exactly as you want it... easier for you and insuring complete customer satisfaction.

There are three big reasons why the Midgetrol $1\frac{5}{16}$ " control does a better job... because the *permanently fixed tubular brass shaft* can be adapted for any popular knob in a few seconds... because AC switch attachment is simple and positive... because the precision-controlled carbon element gives

smoother taper, quieter operation, more accurate resistance value and less drift in TV sets.

These same advantages are available in the Dual Concentric Midgetrol, tailor-made on the job to match each specific requirement. It is assembled in five easy steps, in less than five minutes, using complete, *factory-inspected* control sections. You can make over 10,000 different combinations from sub-assemblies available in distributor stocks.

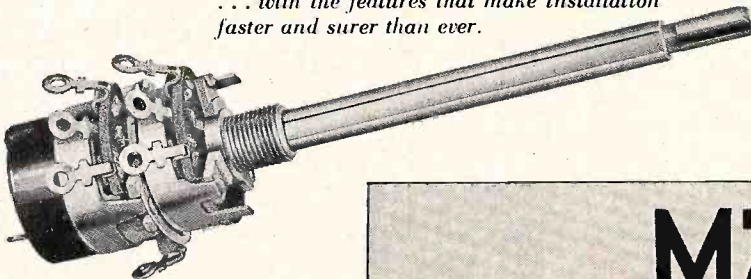Make it Mallory and make sure! Ask your distributor to show you the Mallory Midgetrol... with the features that make installation faster and surer than ever.



Complete Dual Concentric Midgetrol illustrated. Single section control available in complete line of resistance values.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Please mention Successful Servicing when answering advertising.

Gamble-Skogmo 94TV1-43-8940A

(Continued from page 13)

board and two on the other. These transformers are interchangeable except for resistor R-107 (3900 ohms, 2 watts). Resistor R-107 is used only with the C-201-18562 transformer. If horizontal non-linearity is noticed on any of these chassis, reverse the leads connected to terminals 2 and 3 or add a 2900-ohm resistor. If the C-12M-18689 transformer is used, the 3900-ohm, 2-watt resistor should be added, and if the C-201-18562 transformer is used, another 3900-ohm, 2-watt resistor should be used in parallel with the one wired in the chassis. These changes have been made in receivers that were converted. Converted receivers can be identified by a dot behind the Model No. on the decal or chassis.

3. Chassis with Group Numbers 14,200 and up. These chassis use either part number C-12M-18689-1 or a C-201-18562-1 transformer. The dash one transformers are identical, except they have fewer turns on the output section. These transformers are interchangeable.

Crosley 11-442M1U, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472B1U, 11-474BU, 11-483BU, Ch. 331, 331-1, 331-2; 11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2

Chassis 331-1 and 331-2 are similar to Chassis 331 except for the changes noted below. Chassis 323-1 and 323-2 are similar to Chassis 323 except for the changes noted below.

Chassis 323-1 and 331-1 are equipped with a 6T8 tube (V110A, V110B) mounted on a plate and socket assembly (Part No. AB-150226). A 0.005- μ f, 500-volt ceramic disc capacitor (Part No. 144675-2) is connected from lug 2 of the socket to ground. All other parts and connections to the socket for Chassis 323-1 and 331-1 are identical to those shown in the schematic wiring diagrams for Chassis 323 and 331, respectively.

Chassis 323-2 and 331-2 are equipped with a 6AL5 tube (V110A) and a 6AV6 tube (V110B), which have their sockets mounted on a socket and plate assembly (Part No. AB-150227). This assembly consists of the parts and wiring shown in the accompanying illustration. Capacitor C183 is a 0.005- μ f, 500-volt, ceramic disk capacitor (Part No. C-144675-2). Resistor R147 is a 3.9-megohm, 10%, 1/2-watt resistor (Part No. 39374-75). The Part No. of the socket is 146966.

The following changes apply to Chassis 331, 331-1, and 331-2, only. The main chassis Parts List for Chassis 331 should include an audio output transformer T103, Part No. 149460. It is used on models equipped with the 5 1/4", 50-ohm, e-m speaker SP101 (Part No. AD-149502). The audio output transformer T110 (Part No. 149654) is used on all models equipped with 10 p-m speakers. The Part No. of the fuse F101 should be W-150431 instead of W-150065. The Part No. of the power cable and plug assembly CA102, used on Models 11-444MU and 11-474BU, should be AW-149652 instead of C-132300-6. The C-132300-6 cable is used on the models that are not equipped with radio and record changer. The Part No. of the springs used on the control access doors is W-149095.

SOMETHING TO

REMEMBER

MEMO

about
SPRAGUE
Twist-Lok^{*}
TV
Capacitors



● More twist-prong electrolytic capacitors are made by Sprague than by any other manufacturer... And Sprague

naturally lists the largest, most complete line for exact TV replacement applications.

● And when you use a Sprague Twist-Lok TV Capacitor, you can be sure it's dependable. No costly callbacks will jeopardize your profit or your reputation. Your business judgment will tell you to *accept no substitutes*.

GET YOUR NEW SPRAGUE TV CAPACITOR REPLACEMENT MANUAL TODAY!

Besides making the largest TV capacitor line, Sprague makes it easy for you to pick the correct replacement for practically any television receiver! Just off press, this NEW 3rd edition of the famous Sprague Manual is jam-packed with up-to-the-minute replacement recommendations for critical capacitors in 964 TV sets of more than 60 brand names. FREE from your Sprague parts distributor or send 10c directly to Sprague to cover handling and mailing costs.



★Trademark



PRODUCTS COMPANY

55 Marshall St.
NORTH ADAMS, MASSACHUSETTS
(Distributors' Division of the Sprague Electric Company)


PIONEERS IN ELECTRIC AND ELECTRONIC DEVELOPMENT

Please mention Successful Servicing when answering advertising.


the First **VEE** with **GOOD** Low Band Performance

RADIART SUPER VEE


This antenna design is recognized as the top "high-band" performer compared with any other all-channel array. High forward gain, sharp directivity and excellent rejection from back and sides on channels 7 to 13, combine to deliver the best picture possible! NOW . . . THE RADIART DOUBLE STACK VV2, features full 1/2 wave spacing between bays and extra "Q" bar length giving you more total gain and OUTSTANDING LOW BAND PERFORMANCE. An exclusive RADIART development!

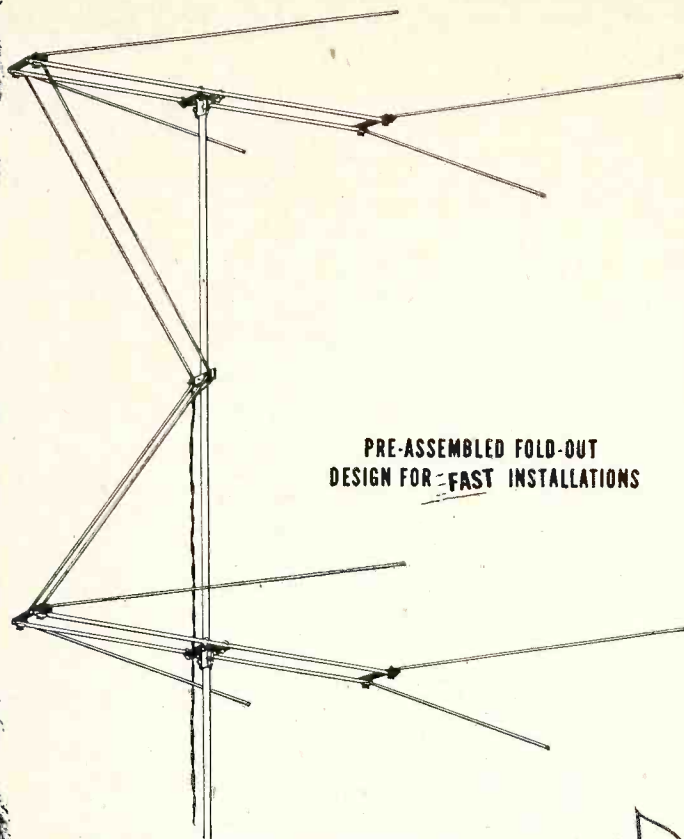

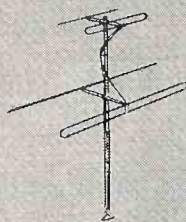
PRE-ASSEMBLED FOLD-OUT
DESIGN FOR ~~FAST~~ INSTALLATIONS




HI-LO ANTENNAS

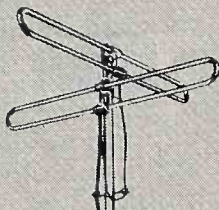

FM ANTENNAS

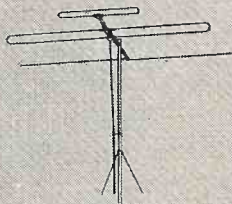


STRATE-LINE ANTENNAS

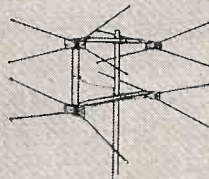

LAZY-X CONICALS



INDOOR ANTENNAS

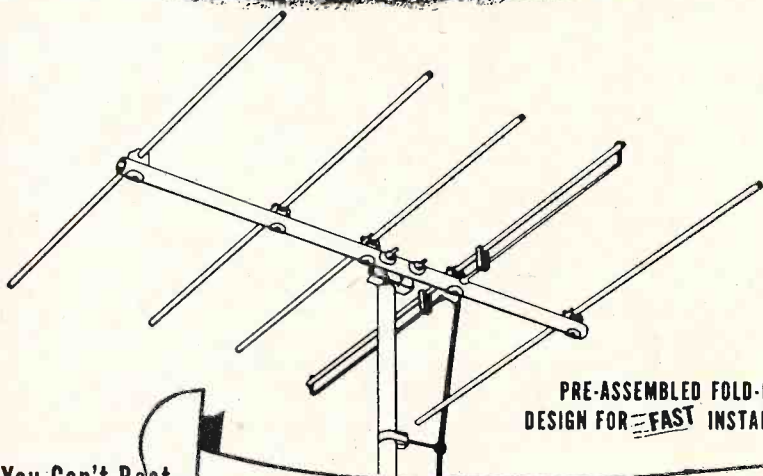

PRE-ASSEMBLED FOLD-OUT
DESIGN FOR ~~FAST~~ INSTALLATIONS



RADIART YAGI

The perfect answer to the need for maximum signal pick-up in "fringe" areas. Each YAGI is cut for a specific TV channel and may be used singly or doubly stacked. Features include low standing wave ratio . . . over 8 db. forward gain . . . and narrow beam width that develops high signal-to-noise ratio.

You Can't Beat
a RADIART
Antenna on a
TELE-ROTOR
...IT'S TOPS!



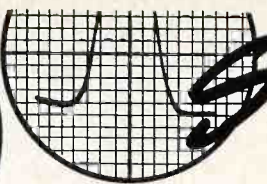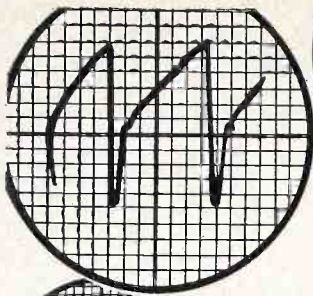THE **RADIART** CORPORATION CLEVELAND 2, OHIO
VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES



See YOUR ANSWER

WITH THE


PRECISION ES-500A

HIGH SENSITIVITY—WIDE RANGE

5" OSCILLOSCOPE

PUSH-PULL VERTICAL AND HORIZONTAL AMPLIFIERS

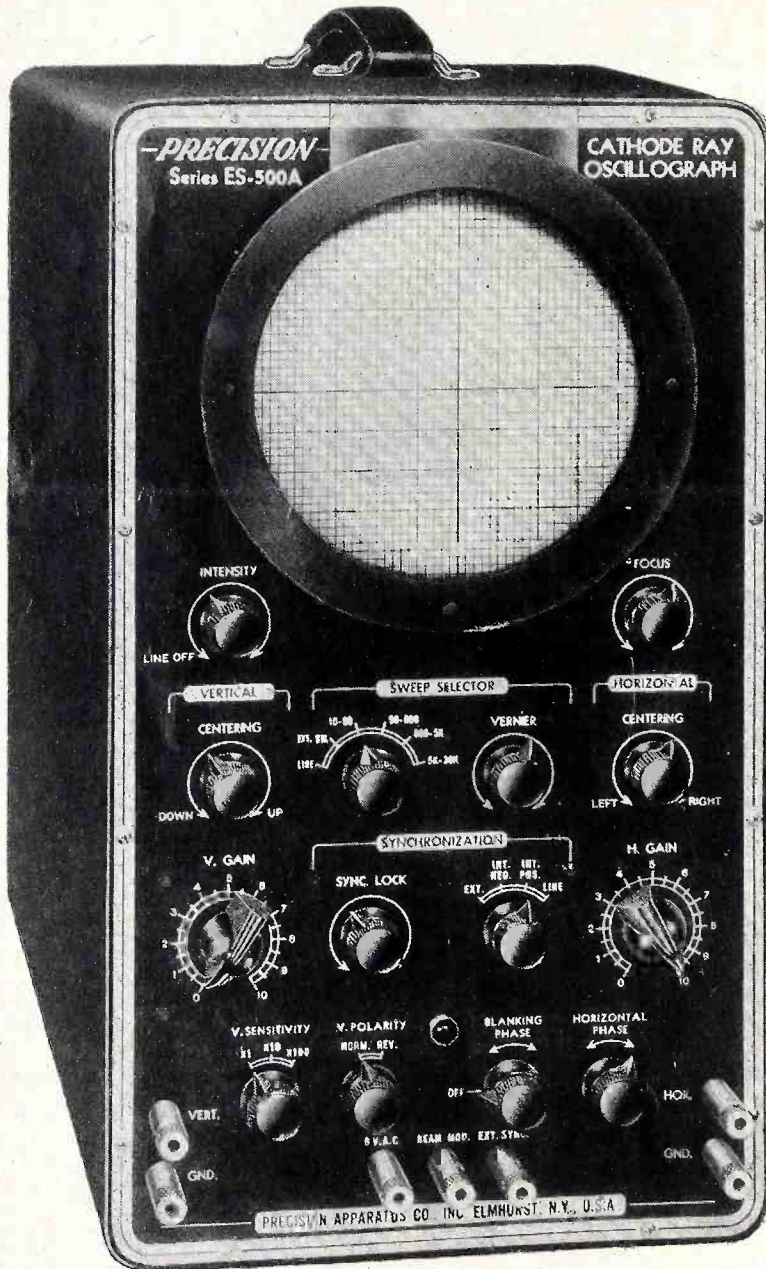20 MV PER INCH "V" SENSITIVITY—150 MV PER INCH "H" SENSITIVITY



SERIES ES500A affords the ultimate in performance, visibility and operational flexibility at moderate cost. "Precision" engineers have incorporated every necessary basic feature which they have found to be required to meet the needs of the rapidly advancing art of electronics, A.M., F.M., and TV.

The new Series ES-500A provides an unparalleled combination of high sensitivity, extended frequency range and other essential operating features specifically desired for experimental and commercial visual circuit analysis.

SUMMARY OF IMPORTANT FEATURES

- * **High Sensitivity, Extended Range, Voltage Regulated Push-Pull Vertical Amplifier**—20 MV (.02 V) per inch deflection sensitivity. 10 cycles to 1 MC response. 2 megohms input resistance. Approx. 22 mmfd. input capacity.
- * **Frequency Compensated Vertical Input Step Attenuator**—X1, X10, X100 plus continuous variable gain control in cathode follower input stage.
- * **Vertical Phase-Reversing Switch** permits inversion of all patterns at will. Non-frequency discriminating.
- * **Extended Range, High Sensitivity Push-Pull Horizontal Amplifier**—150 MV (.15 V) per inch high deflection sensitivity adequate for most all "H" drive purposes. 10 cycles to 1 MC response at full gain. 1/2 megohm input resistance. Approx. 20 mmfd. input capacity.
- * **Linear Multi-Vibrator Sweep Circuit**—10 cycles to 30 KC plus line and external sweep.
- * **Amplitude Controlled, 4-Way Synch. Selection**—Internal Positive, Internal Negative, External and Line.
- * **"Z" Axis Modulation** input facility for blanking, timing, etc.
- * **Internal, Phasable 60 cycle Beam Blanking** for elimination of alignment retrace; clean display of synch. pulses etc.
- * **Sweep Phasing Control** for sinusoidal line sweep usage. Wide angle bridge circuit.
- * **Direct H and V Plate Connections** and Audio Monitoring phone jacks at rear. All four plates accessible.
- * **High Intensity CR Patterns** through use of adequate high voltage power supply with 2X2 rectifier.
- * **The Circuit and Tube Complement**—6C4 Vertical input cathode follower. 6CB6 first "V" amplifier. 6C4 "V" phase inverter. Push-Pull 6AU6's vertical CR driver. 7N7 first "H" amplifier and phase inverter. Push-Pull 6AU6's horizontal CR driver. 7N7 Multi-vibrator internal linear sweep oscillator. 5Y3 low voltage rectifier. 2X2 high potential rectifier. VR-150 voltage regulator. 5CP1/A CR Tube.
- * **7 Four-Way Lab. Type Input Terminals**—Take banana plugs, phone tips, bare wire or spade lugs.
- * **Light Shield and Mask** removable and rotatable.
- * **Extra Heavy-Duty Construction** and components to assure "Precision" performance.
- * **Heavy Gauge, Etched-Anodized, No-Glare, Aluminum Panel.**
- * **Fully Licensed** under Western Electric Co. patents.

* **Series ES-500A** In louvred, black ripple, heavy gauge steel case. Size 8 1/4" x 14 1/2" x 18". Complete with light shield, calibrating mask and instruction manual.

NET PRICE \$169.50

See the new ES-500A Oscilloscope on display and available at leading Radio Parts & Equipment Distributors.

AM • FM • TV



PRECISION APPARATUS CO., INC.

92-27 Horace Harding Boulevard, Elmhurst 14, New York

Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., Toronto, Ontario

Convenient "PRECISION" Purchase Terms can be arranged with your local favorite authorized "PRECISION" Distributor.

AM • FM • TV

Farnsworth 100P Series, 400P Series, Capehart; RCD. Ch. 41E-MP

(Continued from page 17)

the entire frequency response of the pickup is allowed to pass on to the preamplifier without any compensation other than that presented by the low-frequency "rumble filter." The "rumble filter" is a circuit designed to eliminate the undesirable effects of low-frequency resonance. The circuit is designed so that its resonant frequency is within the range of frequencies causing the undesirable rumble. In this case, the resonant frequency is approximately 19 cps. Positions 2, 3, and 4, shunt the pickup with parallel *R* and *C* combinations.

General Electric Model P15

To convert the model P15 record changer, RBH-015 motor, to 110, 50-cycle operation motor, the following steps are advised:

Connect a 70-ohm resistor (RRW-005) in series with the motor leads to reduce the voltage to approximately 95 volts to prevent the motor from over-heating. Replace the 60-cycle bushing on the rotor shaft, with a 50-cycle bushing (RMS-231).

The following items should be added to the replacement parts list:

RRW-005 Resistor-70 ohms, 25 watt
RMS-230 Bushing 60 cycle spring type bushing
RMS-231 Bushing-50 cycle spring type bushing.

Add to the Index Remedy: A few early P15 changers may occasionally index the tone arm for 10" records while playing 7" records. To remedy this, bend the small half-round tab on the discriminator lever (item 160, ER-S-P15) about 30° so that it will limit the downward travel of the lever.

General Electric Models 752, 753

To reduce "radio talk" when models are operated on phono, late production models have the following changes incorporated:

1. C59 which was originally grounded on the rear apron of the chassis should now be grounded to the same ground as C60. This ground point can be found near the end of the terminal board.
2. C42 should be dressed towards the end of the chassis and away from V5 as far as the leads will permit.
3. Dress the blue lead from pin 5 and green lead from pin 6 of V8 (phono preamp), in front of the terminal board instead of in back.

General Electric Models 14T2, 14T3, 14C102, 14C103, 16T1, 16T2, 16C110, 16C111 and 16C115

The following items should be added to the replacement parts list: Spacer part RHJ-006; Capacitor C227, 800 μ f; 350v (stock RCW-3037).


Place metal spacer sleeve over deflection yoke clamp screws. To reduce Channel #4 smear (4.5 Mc harmonic interference) and Channel #6 oscillations, connect C227, 800 μ f, 350 v, (stock RCW-3037) across the isolating gap between receiver chassis and

rear edge of head-end chassis. Using as short leads as possible, solder one end of C227 to the soldered head-end chassis connection of C206 mounting clip. The other lead may be soldered to a lug fastened securely at the punched receiver chassis hole adjacent to tube socket V21. Change C227 on the schematic from a head-end chassis ground symbol to a main-chassis ground symbol.

Admiral RC550 record changer

Production changes in the RC550 record changer are listed below, coded RUN 1, RUN 2, etc. Run number stamped on model label indicates this changer has had the change(s) incorporated which are explained under that particular run number below, as well as all changes (lower run numbers) made prior to

(Continued on page 21)

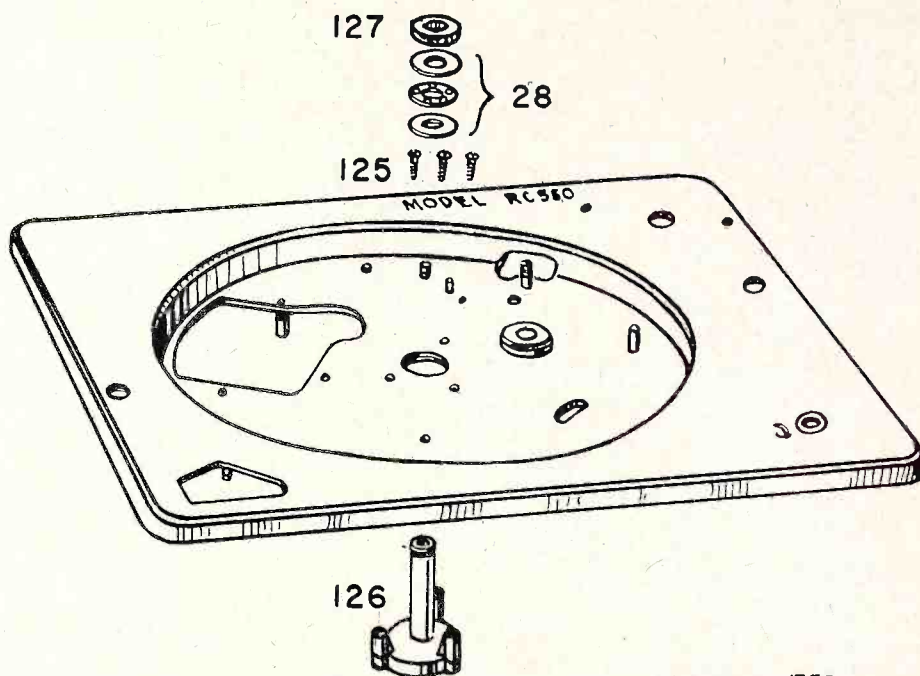

-here's what you call **RUGGED**

University
Model SA-30
UTILITY
HEAVY DUTY
DRIVER UNIT

90-10000 CPS
EXTENDED
RESPONSE

30 WATTS
CONTINUOUS
DUTY

MATCHES ANY
SYSTEM OR
AMPLIFIER

SELF-ALIGNING
RIM-CENTERED
ASSEMBLY

RUGGED DIE-CAST
ALUMINUM
HOUSING

Additional exclusive features include Bakelite Screw Type Terminal Strip, Gland Nut Type Cable Entrance, Special 45 ohm Transformer Tap, and Equalized Palate Type Breakdown Proof Diaphragm Assembly—write Desk 68

An Engineering Achievement of **UNIVERSITY LOUDSPEAKERS INC.**
80 So. Kensico Ave., White Plains, New York

Please mention Successful Servicing when answering advertising.

RIDER BOOKS

The Standard of the Industry

Accurate, — Authoritative, the first guide to better servicing . . . higher profits.

Receiving Tube Substitution Guide Book

by H. A. Middleton

For AM-FM-TV Receivers and Allied Equipment

2500 Tube Substitutions . . . TV Rec. filament wiring . . . Heater Sub. wiring instructions . . . Tube types classified by functions . . . Cathode-Ray Tube Characteristics; Ballast Tube data; Resistors . . . Capacitors . . . Transformer . . . Color codes; and a wealth of other vital data. 224 pp. Heavy paper cover 8½ x 11. \$2.40

Broadcast Operator's Handbook

by Harold E. Ennes

The co-ordinated facts . . . Result in a general set of rules that serve as standards of good operating practice. 288 pp. 5½ x 8½ illustrated. \$3.30

TV Master Antenna Systems

by Ira Kamen and Richard H. Dorf

Explains the workings of the fast-growing master antenna field . . . Provides the practical knowledge for installation, maintenance and usage for apartment buildings . . . hotels . . . hospitals, etc. . . 368 pp. 234 ill. Cloth Bound . . . \$5.00

TV Installation Techniques

by Samuel L. Marshall

A "must" for difficult installations . . . Know ice loading, wind surface, mounting requirements . . . plus accurate data on receiver adjustments in the home; municipal regulations governing antenna installations . . . 336 pp. 270 ill. 5½ x 8½. Cloth Bound . . . \$3.60

Encyclopedia on Cathode-Ray Oscilloscopes and their uses.

by John F. Rider and Seymour D. Uslan

Everything you should know about the scope . . . What it is; What it can do; How to use it, Told practically and informally . . . Over 70 models described . . . complete with specifications and wiring diagrams . . . 992 pp. 3,000 ill. 8½ x 11 completely indexed. Cloth Bound . . . \$9.00

TV and Other Receiving Antennas Theory and practice

by Arnold B. Bailey




Tells you the function of each type; How to use it; which is best . . . The best Antenna Authority in the field . . . Easy to read because mathematics are translated into charts and graphs. 606 pp. 310 ill. . . . \$6.00

Vacuum - Tube Voltmeters

by John F. Rider

New, Revised 1951 Edition

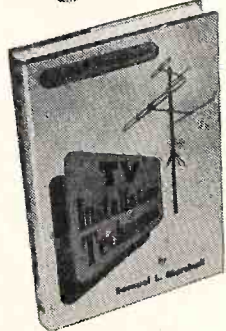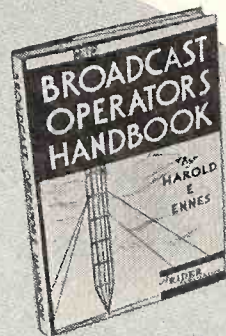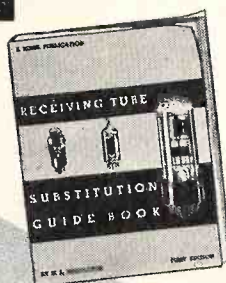Covers all types of voltmeters . . . diode, triode, rectifier-amplifier, tuned, amplifier-rectifier, and slide-back . . . Bibliography of more than 200 listings and comparative tabulations of operating characteristics are included . . . Written for practice with emphasis on field conditions . . . Review questions each chapter . . . 432 pp. 5½ x 8½. 215 ill. \$4.50



SEND FOR COMPLETE CATALOG ON ALL RIDER BOOKS

JOHN F. RIDER PUBLISHER, INC.

480 Canal Street

New York 13, New York

(Continued from page 19)

that time. At the start of production, chassis were stamped RUN 1.

RUN 1—Change in Push-Off Link and Stud Assembly (86). In early changers, push-off link and stud assembly (86) is made from .060" stock; washer (94) used with it is 1/16" thick. (Previous parts list erroneously gives the washer (94) thickness as 1/6".) In later changers the link (86) was made from .074" stock, and the washer (94) used is 1/32" thick. The .074" stock was used to reduce the possibility of bending of the push-off link with resulting push-off and/or trip failure. All service replacements are made from the .074" stock. Be sure to use correct washer (94).

RUN 2—The Selector Cam (89) was modified slightly; cams are directly interchangeable, however.

RUN 3—Change in Turntable Support Hub (126). The turntable support hub (126), which was staked to the changer pan in earlier production, is now mounted to the underside of the changer pan with three drive screws. See accompanying diagram. This part is now replaceable and has part number 404A35. The screw has part number 402A68. A spacer washer (127), part number 401A364, is also added. Note that this washer was omitted when the later turntable and thrust bearing were used; see Run 4 below.

RUN 4—Change in Turntables. The original turntable, part number G400B507, has been replaced with a slightly different turntable, part number G400B585. Part number G400B585 turntable has a longer hub, and consequently a "thinner" thrust bearing, part number 415A29, is used with this turntable. The turntable support hub (126), mentioned in Run 3 above, must be used with this new turntable. *It is not necessary to stock the new turntable, since the G400B507 turntable can always be used if suitable washers are used with either thrust bearing (28) to provide proper turntable clearance.*

The parts listed below are additions and corrections to the original parts list.

Ref. No.	Part No.	Description
28	415A11	Thrust Bearing (early type; total thickness 9/32")
28	415A29	Thrust Bearing (late type; total thickness 3/16") (415A29 can be used in place of 415A11 if a 3/32" spacer washer is used.) See RUN 1 in production changes.
52	G400B507	Turntable (early type: 3/4" hub): Use with 415A11 (28)
52	G400B585	Turntable (late type: 1" hub): Use with 415A29 (28) See RUN 4 in production changes. G400B507 can always be used for replacement if suitable washer(s) are used with either thrust bearing (28) to provide proper turntable clearance.
94	4B1-78-47	Washer (early type) .196" ID x 3/8" OD x 1/16" thick.
94	4B1-68-47	Washer (late type) .196" ID x 3/8" OD x 1/32" thick. See RUN 1 in production changes.
125	402A268	Drive Screw, #6 x 3/8"
126	404A35	Turntable Support Hub. See RUN 3 in production changes.
127	401A364	Spacer Washer, 13/16" OD x 29/64" ID x 5/32" thick. See RUN 3 in production changes.

The following service hints are offered:

1. Record Slipping — 45 RPM. (a) The adaptor nibs may be deformed, may not fit tight enough in the record, or may be cocked. Be sure that the records are not warped. A new type of plastic adaptor will be available soon; this new adaptor will fit in the record better and will have sharper nibs. (b) Needle force may be too great for this type of record. Try removing a tone arm weight (121), part

number 414A45. Two of these weights were used with the Electro-Voice cartridge, 409A13-1, and one weight was used with the Shure cartridge, 409A13.

2. Groove Skipping. Anything that may cause a drag on the tone arm will contribute to groove-skipping. For example, a worn needle will tend to skip grooves. Another possibility is that the Lubriplate (lubricant) between the gear engagement pawl (33) and the trip motion arm (32) may become excessively tacky after the changer has been in use for some time. The Lubriplate is applied between these two parts, strictly as a safety measure, to insure a friction load if the friction

washer becomes loose. If the trip friction washer (34) has the correct tension, the changer will function properly with the Lubriplate removed. Therefore, we suggest that you remove all of the Lubriplate from between these two parts and leave them dry. It may be necessary to bend the washer (34) to get proper friction, but don't add too much tension. Do **NOT** remove lubricant from any other place in the changer.

3. Erratic Trip Action. This may be caused by failure of the trip slider return spring (102B) to return the trip slider (36) to proper position as the changer goes through its cycle.



C-D's Metapup

Best by Field Test!

Chassis space at a premium? Dependability a "must"? Then the job calls for METAPUP, C-D's new and advanced metallized paper tubular capacitor. Metal-encased, hermetically-sealed, self-healing, ultra-compact... every inch a champion!



Send for Bulletin NB 144. R-91
Cornell-Dubilier Electric Corp.
South Plainfield, N. J.

CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
CAPACITORS

Plants in South Plainfield, N. J., New Bedford, Worcester and Cambridge, Mass.; Providence, R. I.; Indianapolis, Indiana; Fuquay Springs, North Carolina, and subsidiary, The Radiart Corporation, Cleveland, Ohio.

Please mention Successful Servicing when answering advertising.

It's Tung-Sol for radio and tv



Quality -that keeps pace with the growth of the electronic industry
 -that meets fully the performance requirements of all
 radio and tv set manufacturers
 -that safeguards dealer service work

TUNG-SOL
 RADIO, TV TUBES, DIAL LAMPS

TUNG-SOL LAMP WORKS INC., Newark 4, N. J. — Sales Offices: Atlanta • Chicago • Dallas • Denver • Detroit • Los Angeles • Newark

Please mention Successful Servicing when answering advertising.



Whether you BUY or SELL, these REPORTS will help in your purchasing and inventory problems. Obsolete items on your shelves cut into your profits. Keep your inventory up to date by following these monthly REPORTS.

← New to SS Readers

Beginning with this issue, SUCCESSFUL SERVICING will offer its readers a monthly summary of product developments including price changes, new and discontinued items, as supplied by RADIO'S MASTER, published by United Catalog Publishers, Inc., New York City.

Antennas and accessories—TV, FM, AM

ALPRODCO: Model S-12R, rotating standoff TV Tower has been discontinued. Model TV Tower AT-6 has been replaced by model AT-6W. In addition two new Towers and six accessories have been added to their line.

EASY-UP TOWER: TV Tower with accessories (model 400) has been discontinued.

HI-LO ANTENNA: The dealer discount schedule has been revised to include a 25 to 49 quantity.

PHOENIX ELECTRONICS: The 10' coil and 100' coil of perforated steel strap has been discontinued. One new antenna, model PAR-6, has been added to the line.

TECHNICAL APPLIANCE: The Taco TV Master Antenna Distribution System has been revised to incorporate additional units. Also, two additional antennas have been added to the Taco line, models Super 980 and 981. Both are 5 element twin driven antennas. The former is two bay, while the latter is single bay.

TELREX: The Metro or Universal Series of conical antennas has been discontinued, while the Vanguard and Telrex "Yagi" Antennas were introduced.

Miscellaneous radio, TV, and electronic parts

BELDEN: The popular HF Formvar and Cotenamel Magnet Wire are now on 1 lb. spools.

DRAKE, R. L.: A new model High Pass TV Receiver Filter has been added to the Drake line of TV filters. Model number, TV-300-54HP.

DUOTONE: Prices for the Kolor-Vision Screen, sizes 7" to 20", decreased.

EBY SALES: Prices of two screw terminals, numbers 56-7 and 56-9 have been revised downward, while two others, numbers 56-6 and 56-8 increased.

GON-SET: A new converter, 1.6-6.0 has been introduced to the Gon-Set line at \$46.00 net.

INDUSTRIAL TELEVISION: Announced production of new Cascade Autobooter, Model IT-90A. Retains all the features of IT-75A Autobooter plus higher gain and improved signal to noise factor. Made especially for sub-fringe applications and community antenna systems.

INTERNATIONAL RESISTANCE: A Precision Type Resistor (WW10) and the new LC1 type Loudness Control and Base Elements have been added to their Resistor line. Type BT2 insulated composition 2 watt resistor and assortments 10 and 11 cabinets have been discontinued.

J-B-T: Prices on an adjustable stop molded switch, model MAS-14-6 and a molded switch MS-14-6 were decreased.

MERIT TRANSFORMER: Three new transformers, models HVO-8, MDF-30 and P-3046 have been added to the company's line of transformers.

NATIONAL CARBON: Prices increased on the Eveready Air Cell "A" Batteries for 2 Volt Receivers and type A-1300 for 1.4 Volt Receivers.

RADIART: Model 5YG Antenna and Wire types ATX-9 and 10A have been added to the company's lines. Prices on No. AK-85 TV Accessory and Wire types ATX-8 and 10 have been decreased and increased respectively.

RADIO RECEPTOR: Type F1B1S1B, F2B1S1B, WF6B1S1B and WFB1S1B industrial type Selenium Rectifiers have been discontinued, while types W1B1S1B, W2B1S1B, WW6B1S1B and WW7B1S1B were added.

RCA: Type VS016C Battery has been added to the Portable "B" series at \$2.28 net.

SANGAMO: Prices on 20 items in their Type 30 Molded Tubular Paper Capacitors line have been reduced.

SPRAGUE: Printed circuits types 100C1 and 101C1 have been added to their line. Also, the Ceramic capacitors are now being listed under their new numbers, series 5GA, 5HK, STCC and STCU.

STANDARD TRANSFORMER: Stancor now producing the following components for the Williamson Amplifier: output transformer A-8054, power transformer PC 8412 and filter choke C-1411. Bulletin 382 available describes construction of amplifier with drawings and parts list.

STANWYCK: Two new G. E. type coils, numbers 980 linearity coil, and 981 width coil were introduced.

TRIPLETT: Type 3434 TV-FM Sweep Signal Generator with built-in markers, has been discontinued and replaced by model 3434A. DC Microammeters, models 521, 524, 626 and 726, in 0-20 range have been discontinued. Price adjustments have been

made on the DC Ammeter Switchboard Shunts, 1000 and 2000 amps., and model 325 DC Voltmeter in 1000 ohms, ranges 0-100 and 0-150.

Recording equipment, microphones, speakers, turntables, cartridges, etc.

ALTEC-LANSING: Model 820A Corner Speaker System Complete, 821A Cabinet, A-333A Amplifier and A-433A Pre-Amplifier have been added to the Altec-Lansing line of equipment.

ASTATIC: Five mikes have been added and one Switch Connector, model SC-12.

AUDIO-DEVICES: The line of Audiotape has been expanded to include two smaller reels of 150' and 300' which will be ready about the first of September.

BEL: Numerous additions and deletions to the company product line were made effective July 2, 1951. Nevertheless, a small quantity of inter-office communication systems, models 350, 351-M and B-23, is still on hand. Also Public Address Systems, models PA-3715-A, PA-3725-A and PA-3750-A are now listed less microphones, which are to be ordered separately as in the case of Stands and other accessories.

GENERAL ELECTRIC: Model RPX-009 is now available as model RKP-009, as a replacement parts kit for Triple Play Cartridge at \$15 net, less stylus assemblies.

JENSEN MFG.: Stock number ST-768, blonde mahogany finish Cabinet with 15" speaker, has been dropped and replaced with ST-838. ST-788, cordovan mahogany with 15" speaker has been changed to stock number ST-858. Also two Cabinets have been added, stock number ST-863 consisting of cordovan leg assembly and number ST-843 with a blonde leg assembly. In addition, Viking Loudspeakers, 10J12 with overall dimensions of 10 1/2", depth 3 11/16", and 12J12 (overall 12 3/16", depth 4 7/16") have been discontinued. However, the 10J11 alternate design may be substituted for the 10J12 and the 12J11 alternate design may be substituted for the 12J12.

LOWELL MFG.: Models RS8-A and RS12-A, Recessed Wall Type Directional Speaker Baffles decreased in price.

MINNESOTA MINING: Have added to their line of Scotch Brand Recording Tape (both paper and plastic) a new size, 1/4" tape x 300 feet.

RECOTON: Number 450, Replacement Phonedee Kit and 36 other Recoton Replacement Needles have been added to the company's line.

STEPHENS MFG.: Prices of speakers, models 52-N (natural) and 52-S (Silver) were adjusted upward to a list of \$79.00.

Test equipment

HICKOK: Two new Oscilloscopes, models 640 HA with UP-11 high actinic type CR tube and 640 LP with SUP-7 long persistence CR tube; and model CRT Adapter for tube testers to test CR Tubes (at \$9.90 net) have been added.

NATIONAL UNION: Portable picture tube checker now available at \$28.75 dealer net. Can be used either in shop, customer's home or can even test the tube while in shipping carton.

Tools and hardware

KESTER SOLDER: Prices of Kester Solder were revised downward to conform with their lower tin cost.

MULTICORE: Prices of Ersin Multicore Solder were decreased.

Tubes—TV, receiving, special purpose, etc.

EUREKA TV and TUBE: Prices decreased on Picture Tubes ranging in size from 14" to 20".

GENERAL ELECTRIC: Three new types of 12" and 16" Picture Tubes have been added to the GE TV tube line.

HYTRON: Reduced prices on 6 TV picture tubes, sizes 16", 17" and 20".

RAULAND: Added to their TV Picture Tube line a new 10", 20", 21" and 24" tubes. Also reduced prices on several of their 16", 17" and 20" tubes.

RCA: Kinescope types 20CP4 and 21AP4 decreased in price to \$59.00 and \$61.00 respectively.

SHELDON: Prices for Sheldon TV Tubes have been revised to show prices under a 12 month warranty and a differential under a 7 month warranty.

RADIO OPERATOR'S LICENSE Q AND A MANUAL

by Milton Kaufman,
Instructor, RCA Institutes

Third Edition



Includes Element VIII:
Ship Radar Techniques.
Includes new elements 2, 5, and 7,
revised elements 3 and 6.

Contents

ELEMENTS:

- I. Basic Radio Laws, Rules, and Regulations
- II. Radiotelephone Operating Practice
- III. Basic Theory and Practice: Radiotelephone, Basic Radiotelephone
- IV. Advanced Radiotelephone
- V. Radiotelegraph Operating Practice
- VI. Radiotelegraph; Advanced Radiotelegraphy
- VII. Aircraft Radiotelegraph for Flight Radio Operator
- VIII. Ship Radar Techniques

APPENDICES:

1. Part 13—Rules Governing Commercial Radio Operators
2. Extracts from Radio Laws
3. Conventional Abbreviations; International Morse Code
4. Small Vessel Direction Finders
5. Automatic Alarm

INDEX

734 pages 243 illus. \$6.60

Element VIII (separately bound)
32 pp. illus. 5 1/2 x 8 1/2" 78c

JOHN F. RIDER PUBLISHER, Inc.
480 CANAL STREET
NEW YORK 13, N. Y.

INDEX OF CHANGES

Model	Page Number	Successful Servicing	Rider Manual† From	To
TELEVISION CHANGES				
Air King Service Hint	5			
Belmont 16- and 17-inch chassis	5			
Crosley 11-442MIU, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472BIU, 11-474BU, 11-483BU, Ch. 331, 331-2, 11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2	15			
11-442MIU, 11-444MU, 11-453MU, 11-460MU, 11-470BU, 11-472BIU, 11-474BU, 11-483BU, Ch. 331, 331-1, 331-2	6-27			6-34
11-443MU, 11-454MU, 11-458MU, 11-473BU, 11-484BU, Ch. 323, 323-1, 323-2	6-35			6-40
Du Mont RA-103	7			
DuMont RA-103 Chatham, RA-103 and Savay, RA-103	7	C6-2, *1-58, C3-1, C6-6, C7-1, *1-58, C3-1, C6-2, C7-1		*1-80, —, —, —, *1-80, —, —, C7-2
Winthrop, RA-103				
Du Mont RA-104A	9			
DuMont RA-104A Hastings, RA-104A	9	3-1, 2, 4-1, 3-1, 2, 4-1, C7-1		3-3, 4, 4-4, 3-3, 4, 4-4, C7-2
Wellington RA-104A				
Du Mont RA-108A	9			
DuMont RA-108A Bradford, Mansfield RA-108A	9	4-5		4-14
Du Mont RA-110A	9			
DuMont RA-110A Fairfield, Westwood, RA-110A	9	3-1, 2, 4-1		3-3, 4, 4-4
Gamble-Skogmo 94TV-1-43-8940A	11	4-21, C6-3		4-25, —
RADIO CHANGES				
Admiral RC550 RDC. CH.	19			
21-9				21-16
Farnsworth 100P, 400P Series Capehart; RDC. CH. 41E-MP 406N, 410N, 413N, 414N	17			
18-16				18-44
General Electric Co. RDC. CH.	19			
21-13				21-18
General Electric Models 752, 753	19			
21-69				21-74

† The Rider Manual Page Numbers given under Television Changes are for Rider TV Manuals. The volume number is the number preceding the dash. Volume numbers preceded by an asterisk (*) apply to the 8½" by 11" page size Manual only.

The Rider Manual Page Numbers given under Radio Changes are for Rider AM-FM Manuals. The volume number is the number preceding the dash.

TV AND ELECTRONICS
AS A CAREER

To the many young men and women who have asked, time and again, "How can I get into the TV and electronics industry?", John F. Rider is proud to be the first to offer definitive answers in a forthcoming publication, **TV AND ELECTRONICS AS A CAREER**. By Kamen and Dorf.

Both the newcomer embarking on a career and the electronics "oldtimer" who wishes to change his specialty will now be able to learn first-hand just what the electronics industry has to offer and what they must offer it in return.

Roughly speaking, the electronics industry is composed of seven branches of activity: engineering, broadcasting, manufacturing, servicing, parts and receiver distributing, sales representation, and retailing. Each of these special fields is discussed in the text by an acknowledged authority currently active in the field.

The men who have collaborated to make this book a valuable guide to the individual seeking employment in the electronics industry are J. R. Poppele, vice-president, WOR-TV, R. W. Peterson, assistant manager, Electronics Division, Admiral Corporation; W. H. Bohlke, manager, custom service operation section, RCA Service Corporation; Ira Kamen, director of TV development, Brach Manufacturing Corporation; and R. H. Dorf, television consultant.

In addition to the eight chapters covering the various phases of activity in the electronics industry, useful appendices include typical salaries for operating personnel in small and large radio stations, the curriculum of electrical engineering courses at Illinois Institute of Technology, and a listing of public and private schools teaching radio and TV courses.

The authentic, behind-the-scenes stories of such men as Benjamin Abrams, Allen B. Dumont, David Sarnoff, Ross Siragusa, Russell Sprague, Vladimir Zworykin, etc., reveal the qualities that lead to success in the industry.


TV AND ELECTRONICS AS A CAREER will contain 130 illustrations of the industry at work and approximately 325 pages. It is priced at \$4.95.

Watch for this new "Rider first" to roll off the press!

DISTORTION OF SCOPE TRACES

(Continued from page 1)

wave. (Excessive exposure thickened the trace.) Pattern 7 shows distortion in this trace when subjected to a very strong, steady magnetic field issuing from a powerful, permanent magnet (that of a magnetron assembly) which happened to be in front of the tube screen. Pattern 8 is the effect of the same magnet moved to one side of the cabinet housing. The extent of the tilt in patterns 7 and 8, and the direction of the tilt, is a function of the intensity of the external interfering field and its direction.

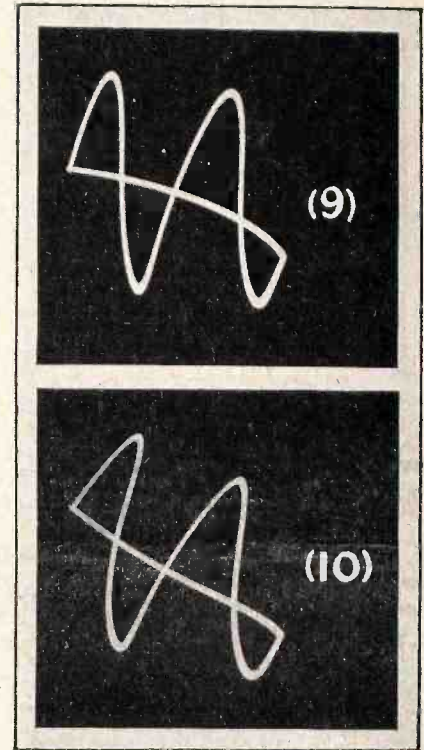

The effects of similar interfering field conditions on a sine wave trace are shown in patterns 9 and 10.

The solution in each case is simple: removal of the source of the interfering field. Sometimes the interference of the external field can be minimized by reorientation, but this merely shifts the plane in which the displacement of the electron beam occurs. The best remedy is increasing the distance between the scope and the device creating the field. Grounding has no effect.

More traces will be shown next month.

Sec. 34.66, P. L. & R.
PAID
U. S. POSTAGE
NEW YORK, N. Y.
PERMIT NO. 9427

H. W. HOOPS, 3RD
3 HALSTED ST.
VERONA, NEW JERSEY

From
JOHN F. RIDER PUBLISHER, Inc.
480 CANAL ST., NEW YORK 13, N. Y.
Forwarding and
Return Postage Guaranteed