



THEO. AUDEL & CO., PUBLISHERS 49 W. 23rd St., New York AUDELS WIRING DIAGRAMS FOR LIGHT AND POWER

COPYRIGHT 1937, 1939, 1948, 1957, 1959, 1962 BY THEO. AUDEL & CO. New York

All Rights Reserved

,

Printed in the United States

Foreword-

THE importance of wiring diagrams of electrical machinery and associated relays and instruments are well known to all electrical workers and students of electricity.

In this book an attempt has been made to bring together a time-saving, well organized, ready reference group of popular connection diagrams, and while it is impossible to cover all possible power system arrangements and operating conditions, attention has been given to the conditions most often encountered in average practice.

Numerous illustrative diagram examples are given, especially in the parts dealing with power transformers and synchronizing connection of alternating current generators, due to the importance of this subject, whenever electric energy is generated and transmitted.

Because other symbols and methods of wiring may be possible in electrically equivalent circuits, great care should be observed when connecting electrical apparatus. The diagrams furnished by the manufacturer of equipment to be installed, should be followed in each individual case.

THE AUTHOR.

The successful operation of power systems depends upon knowledge of the concerted effects of many interconnected machines.

LIST OF SECTIONS

Note.-Each section consists of a related group of diagrams

		rages
Wiring Symbols		I-X
House Wiring Bells and Annunciator Circuits		1- 38
Meters and Connections		39- 52
Relays and Instrument Connections		53- 72
Ground Detector and Connections	•	73- 76
Switchboard and Wiring Diagrams		77- 96
Circuit Breaker Arrangement and Diagrams		97-108
A.C. and D.C. Generator and Motor Diagrams		109-136
Fractional Horsepower Motor Diagrams		137-150
Synchronism Indicator and Wiring Diagrams		151-158
Transformer Connections		159-184
Industrial Control Wiring of D.C. Motors		185-198
Industrial Control Wiring of A.C. Motors		199-246
Miscellaneous Wiring Diagrams		247-271

WIRING SYMBOLS

I

WIRING SYMBOLS



2

WIRING SYMBOLS (Continued)



3

WRH

WIRING SYMBOLS (Continued)



4

WOH

WIRING SYMBOLS (Continued)



WIRING SYMBOLS



6

HOUSE WIRING BELLS AND ANNUNCIATOR CIRCUITS

VARIOUS LAMP CONTROL SCHEMES



In the lamp control diagrams represented above, fig. A illustrates the connection when one single pole snap switch is used.

FIG. B shows how two lights (or two group of lights) can be controlled individually from a set of two single pole switches.

FIGS. C to F illustrate a series of special types of lamp control used in, for example, test circuits, or in any location where particular control schemes are desirable.



A convenient and often used method for control of a lamp or a group of lamps from two points by means of 3-way switches is shown in the diagrams. The lamps may be extinguished or lighted from either switch regardless of the position of the other. When both switches are in the positions shown in fig. A, the lamps are extinguished, and can be illuminated by the operation of switch No. 1 or 2. If as shown in diagram, No. 2 switch is operated the lamps will be illuminated, and can now be extinguished from either switch. A typical sequence of operation is shown diagramatically in figs. A to E.

LAMP CONTROL FROM 2-LOCATIONS



This connection provides an economical means of lamp control from two locations. Although not permissible under the National Electric Code it is shown only as an electrically possible circuit. As in the previous connections shown, both switches are in off position in fig. A, the lamps extinguished, and can be lit by operating either switch. If switch No. 2, fig. B. is operated to position "S" the lamps will be illuminated, and can be extinguished again from any one of the two switches. Figs. A to E inclusive shows the lamps lighted or extinguished, depending on position of switch No. 1, relative to the position of switch No. 2.



Large fixtures or electroliers are often wired so that lights can be controlled in two or more independent groups. As shown in the diagram the two groups of lamps are extinguished in the first position of the switch. When operating the switch to second position, group No. 2, will be illuminated. In the third position the maximum amount of brightness is obtained as both groups of lamps are illuminated, and finally in the fourth position, group No. 1 only is lit. This switch may not be considered as standard, it is only one of several arrangements.

11



A 3-circuit electrolier switch from which three groups of lamps are controlled is shown above. The sequence of operation is depicted diagramatically and is principally the same as shown in the previous 2-circuit switch. In the 4th position maximum illumination is obtained, with all lamps lighted. The switch shown is typical only among a great variety of switches manufactured for electrolier or dome lamp control. The current carrying capacity of the switch as well as potential of the source to be connected should be considered for each individual application.



The series of connection diagrams shown in figs. A to D, illustrate the conventional methods of lamp control when using 3- and 4-way switches. With reference to fig. A, it is obvious that for any additional point of control desired a 4-way switch connected the same as the middle switch must be used. See figs. B to D.

STAIR-WAY LAMP CONTROL WIRING



As shown in circuit diagram the switches used in this type of light control consist of two double pole switches, inter-connected on the first and last floor, and one 3-way switch for each floor. The sequence of operation is as follows: Closing switch on the first floor lights lamp on first and second floor. Turning the switch on the second floor extinguishes the light on the first floor and lights the lamp on the third floor, etc. This operation is continued until the top floor is reached, in other words the switch on each floor should be turned in passing. It can be readily seen that this light control arrangement lends itself to operation of lamps irrespective of number of floors encountered.



Schematic Diagram of Typical Fluorescent Lamp Circuit. The necessary auxiliaries for any fluorescent lamp installation is (1) the ballast, and (2) the starter.

The ballast for operating lamps on 60 cycle A.C. consists of a small choke coil (reactor) wound on an iron core The ballast serves three important functions, namely:

1. It preheats the electrode to make available a large supply of free electrons.

C/L

- 2. It provides a surge of relatively large potential to start the arc between the electrodes.
- 3. It prevents the arc current to increase beyond the limit set for each size of lamp.

Ballasts. These may be designed for operation of a single lamp or as is more common, for two lamps mounted

in a single fixture. Certain practical advantages are obtained from the choice of an electrical circuit which combines under one cover the equipment for the control of two lamps.

Chief among the advantages are improved power factor, decreased stroboscopic effect and reduced auxiliary losses. Each iamp is operated through a separate choke coil. A condenser is connected in series with one lamp and its choke coil to give a leading current. The leading and lagging current will combine with a resulting line power factor of very nearly 100%.

When connecting lamps, ballast and starter into an electric circuit, it is of the utmost importance to observe the manufacturers' diagram usually labeled on the ballast. This diagram should be followed in each instance for proper operation of the lamp or lamps. Also it should be clearly understood that each lamp size must have a ballast designed for its particular wattage, potential and frequency.



Wiring Diagram of Single Fluorescent Lamp. In the glow type starter A, represents glass bulb filled with inert gas; B, fixed electrode; C, bi-metal strip.

Starters. The starter is designed to act as a time delay switch which will connect the two filament type electrodes in each end of the lamp in series with the ballast during the short pre-heating period when the lamp is first turned on and then open the circuit to establish the arc. This pre-heating causes the emission of electrons from the cathodes and thus makes it possible for the arc to strike without the use of excessively high voltage.

OPERATION. The switch is enclosed in a small glass bulb and consists of two electrodes, one of which is made from a bi-metal strip in an inert gas such as neon or argon. These electrodes are separtaed under normal conditions but

when closed form part of a series circuit through the lamp electrodes and the choke coil (ballast).

When voltage is applied a small current flows as a result of the glow discharge between two electrodes of the switch. Heating of the electrodes results, which by the expansion of the bi-metallic element, causes the electrodes to touch. This short circuiting of the switch stops the glow discharge but allows a substantial flow of current to pre-heat the lamp electrodes. There is enough residual heat in the switch to keep it closed for a short period of time for the electrode pre-heating. The glow being quenched, the bi-metal cools, the switch opens and the resultant high voltage surge starts normal lamp operation. If the lamp arc fails to strike, the cycle is repeated.



STARTER

Wiring Diagram of Single Fluorescent Lamp with Capacitor for Improvement of Power Factor. For operation of the 13, 30, 40 and 100 watt lamps on 110-125

Power Factor. For operation of the 13, 30, 40 and 100 watt lamps on 110-125 volt circuits, the ballast must include a transformer for stepping up the voltage.



Wiring Diagram of Single Fluorescent Lamp with Power Factor Corrected Ballast and Auto-Transformer for Stepping Up the Voltage.

17



Wiring Diagram of Two-Lamp Ballast with Built in Starting Compensator and Auto-Transformer.



Wiring Diagram of Two-Lamp Ballast with Built-In Starting Compensator.



TWO-LAMP BALLAST

Wiring Diagram of Two-Lamp Ballast with Auto-Transformer and a Four-Contact Starter Socket for Each Lamp.



A.C. LINE

Wiring Diagram for Operating Two 14 Watt Fluorescent Lamps in Series with a Special Incandescent Ballast Lamp.

19



Wiring Diagram of Fluorescent Lamp for Operation on Direct Current. While the fluorescent lamp is basically an alternating current lamp, it is also used on direct current where alternating current is not available. Due to the lack of voltage peaks, where direct current is used, lamp starting is generally more difficult than on alternating current and special starting devices must be used. The thermal and manual starting switches in addition to a starting inductance is generally employed.

With fluorescent lamps, one end of the tube may become dim after operating a few hours on direct current. This is due to the bombardment of electrons in one direction only. By reversing the direction of current flow at certain intervals (once a day or more frequently if desired) by means of a special reversing switch, this end dimming may be eliminated.



Wiring Arrangement for Ballast Test Board. By means of a circuit of this type 40 watts two lamp ballasts for use on standard voltage may easily be tested.

This is simply a two-lamp circuit with binding posts left at the point where the ballast must be connected in order that quick connections may be made. By providing socket spacing necessary to receive lamps of other sizes, such a test board can be used to check ballasts of any size, provided care is taken to make the connections through the proper binding posts.



Wiring Diagram Illustrating a Simple Testing Board for Fluorescent Lamps. A test board of this type may be used for checking of 40 watt lamps, for example, with the lamp holders spaced to receive lamps of the proper size, and are provided with a starter socket and manual starter switch, properly connected to a suitable ballast. A filament continuity checker can also be included if desired. This consists of a fluorescent lamp socket, in series with an incandescent lamp of the 25 watt size or smaller.

A testing board of this type has been found helpful for checking of flourescent lamps and starters to see that they operate satisfactorily.

Lamp boards of this general type may also be made to check lamps of several different sizes by providing the necessary ballasts and lampholders properly spaced to receive the lamps, or one lamp socket mounted stationary and the other provided with pins so that it can be plugged into jacks located at the proper distance for taking lamps of various lengths.



Wiring Diagram of Portable Test Kit for Checking Fluorescent Lamps and Starters.

By means of a circuit arrangement of this type various size lamps and starters may be tested directly on the job. All that is required is that the kit be large enough to hold the required ballasts, as connection to one end of the lamp is made by means of a lamp holder on the end of an extension cord. A selector switch must be included for making connections to the proper ballast.

VARIOUS METHODS OF INSTALLING SERVICE DROPS





TYPICAL METHOD OF GROUNDING FOR HOUSE WIRING SERVICE



24

WRH



(1)

WIRING DIAGRAM OF THREE WIRE METER AND SERVICE BOXES



SERVICE CONNECTION FOR A THREE WIRE SYSTEM



Installation Notes. It is important that all wiring be installed to conform with the requirements of the National Electric Code or any local requirements for safe electrical installation.

The first requirement for any installation is to determine the type and size of load (number of lamps, motors, heating elements, etc. required). When this is done it is a comparatively easy matter to compute the maximum wattage requirements, from which data the current is obtained from Ohm's law.

When the current load for each circuit is known, the size of fuses and wire for the main and branch circuits is determined from wiring tables. In most branch circuits where the maximum load does not exceed 15 amperes, No. 14 wire is used, although in some localities the branch circuit load is limited to 1200 watts (at 110 volts) and no branch circuit may include more than twelve outlets. Generally circuits supplying oil burners, washing machines, refrigerators, electric ranges, and any heating appliance exceeding 1000 watts, are wired on independent circuits, separate from the light circuits. In three wire systems it is required that the load be balanced or evenly distributed between the ground and the outside wires.

WR

SWITCH BOX AND METHOD OF INSTALLATION



WIRING DIAGRAM OF VARIOUS BRANCH CIRCUIT FUSE BOXES



CONNECTION DIAGRAM OF A COMBINATION METER AND CONTROL PANELBOARD FOR APARTMENT-HOTEL



30

.
CONNECTION OF WATTHOUR-METERS (FRONT VIEWS)



EXTERNAL CONNECTION DIAGRAMS OF WATTHOUR-METERS



ANNUNCIATOR WIRING DIAGRAM



Gravity Drop Annunciator. When the circuit is completed by the operation of the push button, the current flows from B_1 of the battery through the coil of the electromagnet marked (M) in the detail sketch and energizes its core, and the latter attracts the armature A, pivoted at B. When the armature is moved to the position C, the claw D, is thrown to the position D₁ thereby releasing the shutter S, pivoted at T, allowing it to drop by gravity to position O, thus displaying the number marked upon its face.

Needle Drop Annunciator. In sending a current through the coil of the electromagnet, the armature E, turns on its pivot toward the magnet core A, thereby releasing the arm D, which in falling rotates the arrow to the position shown in the dotted lines. The arrow is reset by pressing a button, which raises the rod F, carrying the arm G.

INTERNAL CONNECTION OF BELLS



SINGLE STROKE BELL

STROKE BELL

Operation of Series Vibrating Bell. When the push button is operated, the current energizes the magnet and attracts the armature causing the hammer to strike the bell, but before it reaches the end of the stroke, the contact breaker breaks the circuit and the hammer, influenced by the tension of the armature spring rapidly moves back to its initial position, thus completing the cycle.

Operation of Single Stroke Bell. When the push button is operated the current energizes the magnet and attracts the armature causing the hammer to strike the bell. The armature remains in the attracted position so long as the current flows through the magnet. When connection with the battery is broken, the hammer spring pulls the armature back against M. A stop S, averts the motion of the armature, momentum springing the lever and causing the hammer to strike the bell.

INTERNAL CONNECTION OF BELLS



Operation of Combination Vibrating and Single Stroke Bell. This bell is essentially a vibrating bell with the addition of a third terminal and a stop to prevent continued contact of the hammer with the bell when working single stroke.

Operation of Shunt-vibrating and Single Stroke Bell. This is simply an ordinary shunt bell with a switch arranged so that the short circuit through the contact maker, armature and lever may be cut out, thus restricting the current to the magnet winding.

Operation of Differentially-wound Vibrating Bell. When the battery circuit is closed, current flows through the magnetizing winding and energizes the magnets which in turn attract the armature. The contact maker closes the circuit through the demagnetizing coils, which demagnetize the magnets. The armature spring pulls the armature back against the stop, while the contact maker breaks the circuit through the demagnetizing coils.

Operation of Differential and Alternate Bell. When the battery circuit is closed by means of the push button, current flows through the magnetizing winding M and energizes F, which attracts end A of the armature. The contact maker closes circuit through magnetizing coil, and the single coil S, of magnet G. After which the demagnetizing coil demagnetizes F, and as a result, magnet G attracts end of C, of the armature after which contact maker breaks the circuit through demagnetizing coil D, and single coil S, of magnet G, completing the operation cycle.

VARIOUS BELL CIRCUITS



WIRING DIAGRAM FOR BELLS IN APART-MENT BUILDING



OPERATION. When for example, push button to apartment on 4th floor is operated, a circuit is completed from battery B_1 through bell #4 and to battery B_2 causing the bell to ring. Similarly when door opener push button on 4th floor is pressed, a circuit is formed from battery B_2 energizing the release coil, which opens the door. The auxiliary push buttons from the service entrance functions in a similar manner, notifying tenant by means of buzzer, the presence of service

ELECTRIC METER READING

How to Read an Electric Meter. A consumer of electricity is billed for the amount of electrical energy in kilowatt-hours registered by the meter located on the premises at certain intervals of time—usually once a month. In order ta facilitate the reading of meters, the front of the meter is usually equipped with four equally divided dials as shown in the figures below. It should be observed that each division on the first right hand dial represents one kilowatt-hour or unit. (One kilowatt-hour equals 1,000 watt-hours). Beginning with this dial read each dial to the left in succession, placing the figures in the same order as passed. If uncertain if the dial finger has actually passed a certain figure or not, note whether the next dial has passed its zero (0), remembering that no dial finger has completed a division until the dial finger next to the right has made a complete revolution.



The relation between the speeds of all dial fingers is ten to one, i.e. one complete revolution of one dial hand indicates one division on the next dial to the left. If the above precautions be observed, it is a simple matter to read any meter. For example, the meter shown in example No. 1, indicated 0.1 (onetenth) on the dial at the extreme right, the two next following indicate one sach and finally the last dial also indicates one, making the total register reading 1111.1 or a registration of 1111.1 kilowatt hours.

The reading example represented by Meter No. 2 in a similar manner, indicates 0.9 (nine-tenths) on the dial at the extreme right; the second dial finger rests on 0, but since the first rests only on 0.9 and has not as yet completed its revolution, it follows that the second dial finger also indicates 9. This 9 placed before 0.9 already obtained gives 9.9. The same is true about the thira dial. The second dial finger at 9 has not as yet completed its revolution so the third has not completed its division; hence another 9 is obtained making 99.9. The same is true about dial four, thereby making the total registration 999.9 kilowatt-hours. The number of kilowatt-hours registered on meters Nos. 3 and 4 will similarly be obtained, being 1001 and 9994 respectively.

METERS AND CONNECTIONS









WR





POWER IS THE SUM OF THE TWO READINGS. BELOW 50% POWER FACTOR, IT IS NECESSARY TO REVERSE THE READING OF ONE WATTMETER (BY REVERSING ITS CURRENT LEADS) AND THEN TAKE THE DIFFERENCE BETWEEN THE READINGS OF THE TWO METERS.



WRH



A watt-hour meter is used for measurement of electric energy. Principally it consists of an electric motor with associated windings so arranged that the mechanical torque produced indicates the electrical power.

One winding of the meter is usually connected in series with the load and the other across the circuit. The torque of such a motor will be proportional to the power and the total revolutions of the motor will be a measure of energy consumed by the load.

In addition a watt-hour meter is equipped with a register which records the revolutions of the meter shaft and a magnetic brake whose function it is to retard the revolutions of the motor.

Due to the inability of most meters to record the energy consumption correctly over a period of time, periodic test schedules are usually followed where each meter in service is compared with a **portable standard** meter, that is a meter in which the error has been reduced to a minimum.



festing Circuit for a Two-Wire Meter, Using a Resistance Load.

The size of error permitted may vary in different parts of the Country but is usually around ± 3 per cent of its rated load.

When setting up a meter for test the current coils of the two meters, that is, the Portable Standard and the meter under test are connected in series, whereas their potential coils are connected in parallel.

During the test period, the revolutions of the **standard** are compared with the meter under test for the same interval of time, allowance being made in the calculations for the disc constant of the two meters.

In cases where the load be unknown it may be determined by timing the standard with a stop watch and comparing the value of the watts from the expression,

$$True watts = \frac{3,600 \times Revolutions \times Watt-hour Constant}{Time in seconds}$$
(1)

With reference to the test circuits the rotating standard is operated by a potential switch, which stops and starts the standard, a reading of the standard is taken at the beginning and at the end of the test and the difference between these two readings gives the number of revolutions of the standard.

If no correction is to be applied to the rotating standard, the per cent accuracy of the watt-hour meter under test is obtained from equation,

Per cent accuracy =
$$\frac{k_h \times r}{K_h \times R}$$
 (2)

Where

r = revolutions of meter under test.

R = revolutions of rotating standard.

kh = watt-hour constant of meter under test.

 K_h = watt-hour constant of rotating standard.

The method shown may be facilitated by introducing an additional symbol, volues for which may be given to the tester in tabular form. Thus, if R_o = the number of revolutions the rotating standard should make when the tested meter is correct, the number of revolutions of two watt-hour meters for a given load vary inversely as their disc constants, then

$$\frac{R_o}{r} = \frac{k_h}{K_h} \text{ or } R_o = \frac{k_h \times r}{K_h}$$
(3)

Subsituting R_0 in the equation for per cent accuracy, we obtain

% accuracy = $\frac{R_o \times 100}{r}$

Example. In a certain test the rotating standard has a constant K_h =0.05 and the watt-hour meter under test has a constant k_h =0.5. If the number of revolutions of the meter under test, r=2, determine the number ot revolutions of the rotating standard.

Solution. Substituting values in formula (3) we obtain

$$R_o = \frac{k_h \times r}{K_h} = \frac{0.5 \times 2}{0.05} = 20.$$
 Ans.

That is, for 2 revolutions of the meter under test, the standard should make 20 revolutions.

49

WRH

Example. Assume the rotating standard in the previous example actually made 20.24 revolutions, what is the accuracy of the watt-hour meter under test?

Solution.

Per cent accuracy =
$$\frac{R_o \times 100}{r} = \frac{20 \times 100}{20.24} = 98.8\%$$
. Ans

This actually means that the meter is 1.2% slow and should be speeded up slightly.

Example. In a test of a D.C. 15 amperes watt hour meter, the corrected average volt and ampere readings are 220 and 14.75, respectively. During the test interval 38 revolutions are counted in 53.5 seconds and the meter constant is 1.25. What is the percent accuracy of the meter at this load?

Solution. Average standard watts

$$W_1 = 14.75 \times 220 = 3,245$$

Inserting our values in equation (1) we obtain the average meter watts as

$$W = \frac{3,600 \times 38 \times 1.25}{53.5} = 3,196$$

Meter accuracy =
$$\frac{W}{W_1} = \frac{3,196}{3,245} = 0,985$$
 or 98.5%. Ans.

Other well known methods used in testing of watt-hour meters are: (1) the indicating instrument method and (2) the stroboscopic method. In the former, load is applied to the meter and watt-hours are measured by means of indicating instruments and timing devices such as stop watches or cronographs.

The ratio between the indicated or meter watt-hours and true watt-hours represent the accuracy of the meter under test, and is usually expressed in per cent.

The stroboscopic method involves the comparison of the speed of two similar discs, and utilizes a light source, a lens system, a photo-electric cell and amplifying equipment. This method of meter testing finds application in meter shops having a large number of meters to be tested. It is not limited to type of meter to be tested except that marking or slotting of the disc is necessary in order to obtain pulsating light.

50

WR)



Testing Circuit for a Two-Wire Meter, Using a Loading Transformer. NOTE: Line side of meter may be left connected to service and potential jumper omitted. With such connections secondary of loading transformer and current coil of rotating standard will be at line potential.



Testing Circuit for a Three-Wire, Single Phase Meter, Using a Resistance Load on Line to Line Voltage.

51

WR

POWER MEASUREMENT IN POLYPHASE SYSTEMS

Power Measurements with Two Watt-Meters: With reference to connection diagram, the current coils of the meters should be in two of the lines and each potential coil connected from that line in which its current coil is placed, to the third line. The algebraic sum of the connected watt-meter readings gives the total wattage. That is, if the power factor of the load be unity, each watt-meter will read one half the total power. If the power factor is 50%, one watt-meter will read zero and the other will read the total power. If the power factor is somewhere between 50% and 100%, one watt-meter will read more than the other, in which case the total power is found by adding the two watt-meter readings. If the power factor is below 50% one watt-meter will indicate backwards. The connection of the current or voltage coil of this meter should be reversed in order that a reading may be obtained. In this case the power taken by the circuit is determined by subtracting the reading of the watt-meter that reversed from the other watt-meter reading.



METHOD OF CONNECTING TWO WATTMETERS TO A POLYPHASE CIRCUIT

Power Factor Measurement. In a balanced **three phase** circuit, the power factor may be obtained from the readings of the two watt-meters, without measuring the voltage or the amount of current of any of the circuits, by applying the following formula.

 $\tan \varphi = \frac{W_1 - W_2}{W_1 + W_2} \sqrt{\frac{1}{W_1 + W_2}}$

Where Ø = angle of lag; W₁ = reading on watt-meter indicating the larger amount of power; W₂ = reading on watt-meter indicating the smaller amount of power



METHOD OF CONNECTING THREE WATTMETERS TO A POLYPHASE CIRCUIT

To measure the power in a three phase four wire system, three watt-meters should be used and connected as shown. The current coils should be connected in the three lines and each potential coil should be connected from the line in which the current coil is placed to the neutral line. In this case watt-meter (W_1) measures the power taken by phase 1 watt-meter (W_2) the power taken by phase 2, etc. and the total power is equal to the sum of the readings of the three meters.

RELAYS AND INSTRUMENT CONNECTIONS



METHODS OF OVERLOAD PROTECTION WITH INDUCTION TYPE OVERLOAD RELAYS



DIAGRAM OF CONNECTION FOR DIFFERENTIAL PROTECTION OF POWER TRANSFORMERS



OPERATION. Differential protective equipment is used with power transformers most frequently when two or more are operated in parallel. Thus, when this system of protection is utilized both automatic and simultaneous tripping of the high- and low-voltage breaker is obtained in case of internal breakdown in the transformers.

It is important that current transformers be selected of proper ratios to give equal secondary currents on the high- and low-voltage side. However, most frequently the ratio of transformation is such that this is difficult to obtain, in which case toos are resorted to, which may be changed from time to time. (For operation of relays see following page.)

CONNECTIONS FOR DIFFERENTIAL PROTECTION OF TRANSFORMER-BANK WITH A TERTIARY WINDING USING INDUCTION TYPE OVER CURRENT RELAYS



OPERATION. When due to internal faults in transformer windings the current through the overcurrent relays exceeds that for which the relays are set to operate, the relays close their contacts, in turn energizing the auxiliary relay coil resulting in a simultaneous tripping of the three circuit breakers.



PLUNGER TYPE OVERLOAD RELAY

Operation Principles. When due to certain conditions in the circuit to be protected, the current exceeds the value at which the relay is set to operate, the plunger raises and carries up with it the movable cone contact, or it strikes against the center of the toggle mechanisms (depending upon the type of contacts in the relay) thus causing the contacts to function.

Generally, when a relay functions to open its contacts it is referred to as a **zircuit-opening** type, and when it functions to close its contacts, it is referred to as the **circuit-closing** type. In this manner the function of the contacts of a relay is nost frequently used as a means of identification, a relay being **circuit-closing** or **zircuit-opening** and **circuit-closing**.

Timing Features. In regard to speed of operation a relay may be referred to as instantaneous or **time** delay. The word **instantaneous** conveying a general gualifying term applied to any relay indicating that no delayed action has been purposely introduced.

The time relays are similar in construction to the instantaneous type, except for he addition of an air bellows which limits the rate of travel of the relay plunger, and in this way introduces an interval of time to the opening or closing of the relay contacts.

This time delay may be regulated to suit the special service desired, which is accomplished by means of a needle valve located in the head of the bellows as shown on page 58. This valve controls the rate of air flow from the bellows under various operating conditions.

METHODS OF OVERLOAD PROTECTION WITH PLUNGER TYPE CIRCUIT CLOSING RELAYS



5.1

OVERLOAD PROTECTION WITH PLUNGER TYPE CIRCUIT OPENING RELAYS



OPERATION. In this circuit overload protection is accomplished by means of a set of current transformers, with its associated relays and trip coils. The relay contacts are normally closed. When the overload through the trip coils exceeds that for which the relays are set to operate, the contacts open, placing the trip coils in series with the relay coils, causing the trip coils to trip the oil circuit breaker.

OVERLOAD PROTECTION WITH PLUNGER TYPE CIRCUIT CLOSING RELAYS



OPERATION. When tripping reactors are used as in over-current and other lypes of relays, instrument and meters should be connected from an extra set of current transformers.

Tripping reactors are frequently employed when a direct current or reliable alternating current is not available as a tripping source for the relays.

Normally the trip coil circuit is open and the reactor forms the closed circuit of the current transformer secondary. When the overload is of a sufficiently high value to cause operation of the relay, it closes the trip coil circuit in shunt with the reactor causing sufficient current to be passed through the coils to trip the breaker.

TRIPPING OF TWO OIL CIRCUIT BREAKERS USING TRIPPING REACTORS AND CIRCUIT CLOSING RELAYS



Note. Auxiliary switch "a" is open when cil circuit breaker is open, and auxiliary switch "b" is closed when the oil circuit breaker is open.

APPLICATION OF LOCKING RELAYS TO FEEDER CIRCUITS



OPERATION. In this system each feeder is equipped with a complement of time overload relays adjusted to trip the feeder breaker on simple over-current, and a set of instantaneous locking relays with high current coil setting, adjusted not to function as long as the primary current does not exceed the capacity of the feeder breaker, but to function instantaneously in case the current exceed this value.

The operation of the locking relays opens the tripping circuit of the feeder breaker, thus locking the feeder breaker closed, and closes the tripping circuit of the heavy duty group circuit breaker.

APPLICATION OF LOCKING RELAYS TO FEEDER CIRCUITS



OPERATION. In this, as in the system shown on the previous page, the locking relays operate only upon excessive over-current in which case the locking relays close the feeder breaker and open the group breaker.

An additional relay equipped with a direct current coil is arranged to close instantaneously and reset itself (open) in a definite time, is used as an auxiliary relay to work in conjunction with a circuit closing auxiliary switch on the group breaker to open the feeder breaker after the group breaker has been opened.

δ5




Overload protection on typical A.C. feeder circuit. <u>OPERATION</u>: When current exceeds the setting of the relays, the relays will close their contacts energizing the trip coil, which trips the oil circuit breaker.

The test links shown are optional but will, if used, facilitate the testing and calibration of instruments.

The current in each phase is measured by means of ammeter and three way switch.



Overload protection on typical A.C. feeder. <u>OPERATION</u>: When current exceeds the setting of the relays, the relays will close their contacts, energizing the trip coil which trips the oil circuit breaker.

The test links are optional but will, if used, facilitate testing or calibration of instruments.

The current in each phase is measured by individual ammeters.



Overload protection on typical A.C.feeder. <u>OPERATION</u>: When current exceed the setting of the relays, the relays will close their contacts, energizing the trip coil which trips out the oil circuit breaker. The energy is measured by means of a watt-hour

meter, and the current in each phase by ammeter and three way switch.

Test links shown are optional but will, if used, facilitate the testing of relays and instruments.



Overload protection on A.C. feeder. <u>OPERATION</u>: When the current exceeds the setting of the relays, the relays will close their contacts, energizing the trip coil which trips out the breaker.

The energy is measured by means of a watt-hour meter, and the current in each phase by individual ammeters. Test links are optional but will, if used, facilitate the testing or calibration of relays and instruments.





using temperature relays.

<u>OPERATION</u>: When the overcurrent exceed the rating at which the relays is set to operate, the heating effect of the current passing through the relays will cause the relay contacts to close and energize the trip coils which trips the oil circuit breaker. The relays operating charactaristics is usually inverse-time, in that the time to operate the relay varies inversely with the overcurrent applied.

GROUND DETECTOR AND CONNECTIONS

GROUND DETECTOR



GROUND DETECTOR

On underground systems, A.C. as well as D.C., it is necessary to install some kind of equipment for detection or reading leakage to ground, in accord with the N.E.C.S. rules.

For low voltage two wire systems, the simplest method is to connect two lamps of the system voltage in series across the two wires, with the connection between the two lamps grounded.

Ground on one side will obviously short circuit and dorken the lamps on that side.

Above 300 volts, static or glover type of ground detectors are generally used; a typical instrument for ground detection is shown above, and standard connection for same are shown on the following pages as well as ground detection by voltmeter or lamp method.

Before connecting ground detection instrument, compare operating voltage with that given on the meter, and in each case follow the manufacturers recommendation.

For example of ground detection diagrom, See the following pages.





SWITCHBOARD AND WIRING DIAGRAMS



This type Switchboards are used primarily where the vertical board cannot be used on account of its limited space to mounting a required number of devices within a certain optical and operating range. The Oil Circuit Breakers when using this type of switchboard ore usually located and operated remotely from the switchboard ore usually located and operated remotely from the switchboard

The OII Circuit Breakers when using this type of switchboard are usually located and operated remotely from the switchboard itself; and all secondary wiring is loid in conduits leading to oil circuit breaker solenoids, current and potential transformers Etc.

 $\begin{array}{l} a = Neter \\ b = Ponei \ support \ and \ wire \ conduit. \\ c = Synchronous \ indicator. \\ d = Control \ swift.h. \\ e = Wire \ grille. \end{array}$

BENCH TYPE SWITCHBOARD

SWITCHBOARD ARRANGEMENT Ammeter -BUSSS Swinging Bracket BUS Supports current transformer Rheostal ____ Connection Bar oil circuit-Breaker lever - Cable terminal Mechanism Watt-Hour-Oil Orcuit Breaker Oil Crouit Breaker Support Floor fitting Switchboord pipe Supports

TYPICAL BACK-OF-BOARD CONNECTIONS

This switchboard shows a typical back of board arrangement with busses supported on pipes attached to the switchboard mounting pipes.

The bus supporting pipes also serve as wall Braces to support the switchboard proper.

The rheastats are controlled from front of board by meons of concentric handles as shown.







Connection of a shunt wound direct current generator. The connections art largely self-explanatory, the voltmeter being connected across the main leads at the generator side of the double-pole knife switch. This will enable the operator to read the voltage of the machine at all times, regardless of the position of the main switches. The current indicator (ammeter) is connected in series with the positive lead connecting the machine to the load. The purpose of the over-load coil on the circuit breaker is to prevent the current from reaching dangerous proportions, that is, when the current exceeds the calibrated settings of the coil. the breaker trips, disconnecting the generator from its load.





Detail connection diagram for parallel operation of two shunt-wound generators. It is customary to employ only one voltmeter with the addition of receptacles and a plug as shown. Sometimes a rotary switch arrangement employed, in which case the receptacles and plug be omitted. The voltmeter may in either

employed, in which case the receptacies and plug be onlitted. The voltated may one of two or more case be connected at will, to read the voltage across the terminals of any one of two or more generators. Occasionally voltage readings across the bus-bars (load) may be included in the voltmeter-switch arrangement. The method for operating the two generators in parallel are as follows: Assume that generator B, by means of its prime mover has been brought up to normal speed and is already connected to the bus-bars. Then with the switch and circuit breaker of A open, start the prime mover of A, and bring it up to speed. Now adjust the field rheostat of A, and note the voltmeter reading on this machine. Finally close the circuit breaker, and switch of generator A.





Connection for Parallel Operation of Two

D. C. COMPOUND GENERATOR Detail of connections for two compound generators in parallel. When two overcompounded generators are to be operated in parallel, it is necessary for a satisfactory division of loads, to parallel their respective series field. This is accomplished by connecting their negatives together as indicated, and this common connector is usually referred to as the equalizer. The instruments and switches shown are connected in the usual manner, which are

equatizer. The instruments and extra the second sec





Direct Current Three-Wire Generator

D. C. GENERATOR

The three-wire generator with external balance coil is often resorted to when it is desired to obtain a three-wire system with a minimum of rotating machinery. The third wire (sometimes misleadingly called *neutral*) is obtained as follows: To an ordinary genarator designed to give a terminal voltage equal to that between the two main wires, are added two slip rings as shown; from these slip rings two leads are brought out and connected to armature points located 180 electrical degrees apart (this connection is not shown in the diagram). Collectors from the slip rings are connected from the two ends of the balance coil wound on an iron core, and the middle point of this coil is finally connected to the third wire. It should be observed that in a system of this kind it is necessary to balance the load between the two main wires and the wire leading from the balance coil as closely as possible. The mount of unbalance allowed for a properly designed system (usually specified by the manufacturers) should not exceed 10% approximately of the total current.







Connection for D.C. Operated Solenoid Used for Control of D.C. Oil Circuit Breaker



Typical connection diagram for a remote controlled oil circuit breaker. In this method of operation, it is necessary, however, that an unfailing supply of direct current be available. The operation of the breaker is accomplished as follows: Assume the breaker is open and the condition for its closing has been established. When the main breaker is open, auxiliary switch marked (b) is closed, and the green lamp on the instrument board is lighted. When the closing switch is operated, the coil of the control relay. Whose contacts are normally open, becomes energized and closes its contact which in turn actuates the closing coil (which is mechanically connected with the breaker contacts) closing the breaker. This closing of the breaker simultaneously reverses the position of the auxiliary switches, opening the previouslyclosed switch marked (b) and closes switch marked (a), which in turn extinguishes the green lamp and lights the red. The breaker may be opened in a similar manner by operating the lower of the two switches on the control board.

91

WRH

Electrolytic Generator with Polarity-Directional Protection



Polarity directional protection such as that which may be used, where protection against sparks is of the utmost importance, for example, where hydrogen or other high explosive materials are manufactured. In such cases it is of the utmost importance that the polarity be not inverted, as the explosion resulting from such a condition might endanger both life and property. The polarity-directional relay consists essentially of a pair of stationary permanent magnets, a rotable soft iron armature pivoted within a stationary coil and a double throw set of contacts. The winding of the coil is of such direction that when potential is applied, connected with the proper polarity, the armature tends to rotate in a direction to keep the contacts closed to one side. A spring, in tension, tends to pull the armature back, open the closed contacts and close the contacts on the other side. When an invertion of the polarity occurs, the spring overcomes the action of the magnet which opens the circuit breaker,



Direct Current Generators in Three-Wire Service-



D. C. GENERATORS

Common method of obtaining three-wire service by means of a small motor-generator of identical size, usually identified as a balancer set. The additional wire or the so-called *neutral* is obtained and brought out from the common lead in the balancer set connecting the positive of one machine with the regative of the other. By the employment of a system of this kind, it is possible to establish better economy, in that the higher potential between the main generators, positive and negative leads can be utilized for power service. The amount of this saving in copper may best be understood by the fact that the weight of the conductors (and therefore the cost) required to transmit a given amount of power at a given efficiency is inversely proportional to the square of the line voltage. When establishing such a system, however, it is necessary to employ some protective scheme to guard against the unbalance of voltage in case the balancer set should become disconnected. The voltage differential relay shown, will protect against unbalanced voltage, and as this relay is practically instantaneous in action, and to protect against false operation, therefore, upon transitory disturbances, definite time Vint relays are utilized in the contact circuits





The voltage differential relay functions principally as follows: The relay consists essentially of a pair of solenoids of equal characteristics, and each with a plunger core connected to a balanced lever which actuates the contacts. One winding is connected across on: circuit and the other winding across the other circuit of the two circuits to be differentially protected. As long as the voltages are equal, the balance lever is in equilibrium and the contacts remains open. When for any reason the voltage becomes unequal, the unequal pull of the two solenoids tends to close the contacts and when this difference in voltage reaches the value at which the relay is calibrated, the contacts close instantaneously energizing the definite time limit and auxiliary relays which in turn shorts the coil of undervoltage device on the circuit breakers, tripping the breakers and disconnects the generators from the buses.



TYPICAL SWITCHBOARD RESISTANCE UNIT FOR BACK OF BOARD CONNECTIONS.

CIRCUIT BREAKER ARRANGEMENT AND DIAGRAMS





OIL CIRCUIT BREAKER



└─Oil Circuit Breaker METHOD OF MOUNTING OIL CIRCUIT BREAKERS

There are four standard methods of mounting Oil Circuit Breakers: (1) On back of panel. (2) On panel frame. (3) On framework remote from panel. (4) In cells.

 Back of panel mounting are used for small plant switchboard for circuits up to and including 2500 volts and up to 800 kmp. in capacity.
On panel frome up to and including 2500 volts and for any breakers alone 800 amperes in capacity, but is not recommended when the greater humber of breakers is 800 kmp. as prabove in capacity.

3. On framework remote from panel for circuits above 2500 volts and up to 6600 volts, and for double-throw breakers except in occasional cases where connections can be made satisfactorily on back of panel, or on panel frame. For large tank type breakers up to and including 13000 volts.

A. In cells for circuits above 6600 volts. For various methods of oil circuit Breaker mounting, see the following pages.






104 OIT NESSET REMOVED (GENERALE (REGINE MAG.) SINGLE POLE OIL CIRCUIT BREAKER UNIT WITH MONOBIE BLODE כסטןסכן צייטלבנא pursofs buissofunay-צוטלבר ן סעווטסויסטו כוסשטועם גוסיה pos buijojosuj-6014 -sng buryojnsug. ניוטם דים סכבפור נמנה סלב-JONOS HILL وروندانه أحد المعموم budging alloss stigo cuito polis tor anyor star Contact stud Harvey and זוננן רסטייסרי נסק BREAKER UNIT SINGLE POLE OIL CIRCUIT

102 P = עראוויסגא זאוגרץ סלפט מעיבו אבעעבג וז כנסזבק.
NOTE: O = עראוויסגא זאוגרץ סלפט מעיבו אבטעבע וז כנסזבק. MARDAID DNIRIW SOLENOID OPERATED OIL C.B. קטקוכסויטל דמחוף SOG JAHUOZ-- nottud 1109 --אנרגלסטורסן נטקורסנים Uoffag Ing-412215 Tray dwoy buijosipuj. sasaj juj xy2. Breaker paz סון כונבחוק 204 piouzog. Anna Rock AND LING hojay 12Ugd 1900 bulffld blisay > indensodid diaj OIL CIRCUIT BREAKER SOLENOID OPERATED

CRAILE. MOTOR MECHANISM FOR OIL CIRCUIT BREAKER Bufferspring Crank and weight Auxiliary Switches Trip Mechanism Revolving Weight Shaf Crosshead Terminal Board Motor A.C. control Pesistor Fuses Red Lomp MOTOR MECHANISM Control Switch OIL CIRCUIT BREAKER Green **OPERATION WITH WIRING** = Resistor Board DIAGRAM. Closed when breaker is open Res. OPERATION -The breaker is closed by means of a pull button switch which completes the circuit of the control relay. The control relay in turn energizes the motor of the mechanism, and seals itself to insure complete closing operation. ЛЛ As the motor of the mechanism increases in speed the flyreights move outward, away from the driving shaft, and pull away from the driving shaft, and pull downward the taggle mechanism to close the breaker. This action raises the counterweight, which returns to its normal position after the breaker opens and reset the taggle mechanism for the next closing Operation. Aux. Su open Myen oll cire. Br. 13 open Trip coi/s Control Relay The circuit breaker at all times trips ree from the mechanism, and is normal-ly tripped by overload trip coils. Res MOTOR



WRH

OIL CIRCUIT BREAKERS AND CONTROL ARRANGEMENT FOR LARGE SYNCHRONOUS MOTOR



A.C. AND D.C. GENERATOR AND MOTOR DIAGRAMS

TERMINAL MARKINGS AND CONNECTIONS FOR DIRECT CURRENT MOTORS AND GENERATORS

Marking of Terminals. The purpose of applying markings to the terminals of electric power apparatus according to a standard is to aid in making up connections to other parts of the electric power system, and to avoid improper connection that may result in unsatisfactory operation or damage.

Location of Markings. The markings are placed on or directly adjacent to terminals to which connections must be made from outside circuits, or from auxiliary devices which must be disconnected in order to facilitate shipments from manufacturer.

Precautions. Although the system of terminal markings with letters and subscript numbers gives information, facilitating the connections of electrical machinery, there is the possibility of finding the terminals marked without system or according to some system other than standard (especially on old machinery or machinery of foreign manufacture). There is a further possibility that internal connections having been changed or that errors be made in markings. It is therefore advisable, before connection of apparatus to power supply systems, to make a check test for phase rotation, phase relation, polarity and equality of potential.

Subscript Numerals on Direct-Current Machinery Terminals. As applied to the terminals of direct-current windings of generators, motors and synchronous converters, the subscript numerals indicate the direction of current-flow in the windings. Thus, with standard direction of rotation and polarity, the current in all windings will be flowing from 1 to 2, or from a lower to a higher subnumber

Direction of Rotation for D.C. Motors. Connections shown on the following pages will give the standard counter-clockwise rotation facing the end opposite the drive. To obtain the opposite direction, or clockwise 'rotation, the armature or main field leads must be reversed.

Direction of Rotation for D.C. Generators. The standard direction of rotation for D.C. generators is **clockwise** when facing the end of machine opposite drive, usually the commutator end of the machine. Direct current generators with connections properly made up for standard rotation (clockwise) will not func tion if driven counter-clockwise, as any small current delivered ,by the armature tends to demagnetize the fields and thus prevents the armature from delivering current. If conditions call for reversed rotation, connections should be made ur with either the armature leads transposed or the field leads transposed.

TERMINAL MARKINGS AND CONNECTIONS FOR DIRECT CURRENT MOTORS AND GENERATORS —continued

Motor Generators. Any direct current machine can be used either as a generator or as a motor. For desired direction of rotation, connection changes may be necessary and should be accomplished as previously described. The conventions for current flow in combination with the standardization of opposite directions of rotation for direct current generators, and direct current motors works out so that any direct current machine can be termed generator or motor without change in terminal markings. A direct-current motor or a direct current generator, by direct coupling constitutes a motor generator. With such coupling, direction of rotation of motor and generator are necessarily reversed when each is from the end opposite the drive. The standard clockwise rotation for direct current motors meets such coupling requirements withcut change in standard connections or rotation for either direct current machine.

Coupling of A.C. and D.C. Motors and Generators. In the same manner as that already described for direct current motors and generators, a direct current motor may be coupled to an alternating current generator without changing from the standard in either individual machine. When, however, the coupling of an alternating current motor to a direct current generator becomes necessary, this coupling cannot be made without rotation other than standard for one of the two machines. Since the rotation of the alternating current motor generator with clockwise rotation viewed from the generator end.

Example on How to Change Direction of Rotation in a D.C. Motor. When brushes are set for standard counter-clockwise rotation, it will be necessary to change assembly of brush holders for trailing operation. With reference to page 114 showing diagram and connections of a typical motor, proceed as follows: 1. Change connection as shown for clockwise rotation, 2. To change assembly of brush holders for trailing operation, first lock the armature in position of one brush on the commutator surface. Mark the brush holder stud of this brush X and studs of the opposite polarity Y. Raise all brushes in the holders, remove holders from the study and reassemble them on the same study in the reverse direction. Lower brush holders until the distance between the bodies and commutator surface is 3/2 in. then shift brush holder yoke until the nearest brush from either stud Y exactly fits over the space previously occupied by the brush X. The leads rom the brush holder studs, one from the commutating fields and the other from he terminal board (lead A1), should be interchanged in the studs. Erase paint nark on bearing housing and make a new mark to line up with the mark on the orush yoke.

TERMINAL MARKINGS AND CONNECTIONS FOR D.C. SHUNT-WOUND MOTOR



The above drawings represent a typical shunt-wound motor, with terminal connections for either the standard counter-clockwise rotation or clockwise rotation, which sometimes is utilized to facilitate the proper functioning of machinery to be operated.

All motor and control wiring should be carefully installed in accordance with the NATIONAL ELECTRIC CODE and any local requirements, and should be of ample capacity based on a maximum line voltage drop of 2 per cent at full load current.

Before operation, make sure that voltage on motor and control nameplates correspond with that of power supply.

TERMINAL MARKINGS AND CONNECTIONS FOR D.C. COMPOUND-WOUND MOTOR



STANDARD DIRECTION OF ROTATION COUNTER-CLOCKWISE WHEN FACING COMMUTATOR END OF MOTOR.



DIAGRAM OF CONNECTIONS

TYPICAL CONNECTION DIAGRAM FOR COMPOUND-WOUND MOTOR

<u>OPERATION OF MOTORS</u>: Before placing the motor in service for the first time the following precautions should be observed:

Dry out all moisture. If the motor has been exposed to moist atmosphere for a long time while in transit or storage (or has been idle for a long period after installation in moist atmosphere) it should always be dried out thoroughly before being placed in service. If possible, place the motor in an oven and bake at a temperature not exceeding 85°c.

Fair results can be obtained by enclosing the motor with canvas or other covering inserting some heating units or incandescent lamps to raise the temperature and leaving a hole at the top of the enclosure to permit the escape of moisture. The motor may also be dried out by passing a current at low voltage (motor at rest) through the field windings that will raise the temperature not over 85°c. The heat should be raised gradually until the whole winding is of this uniform temperature.

TERMINAL MARKINGS AND CONNECTIONS FOR STANDARD AND CLOCKWISE ROTATION



STARTING RHEOSTAT AND CONNECTION DIA-GRAM FOR D.C. COMPOUND-WOUND MOTOR



STARTING RHEOSTAT AND CONNECTION DIA-GRAM FOR D.C. SERIES-WOUND MOTOR



failure of source, the NoVoLTAGE release coil will automatically release the moveable arm, which by action of its spring (not shown in diagram) returns to its "OFF" or starting position.

STARTING RHEOSTAT AND CONNECTION DIA-GRAM FOR D.C. SHUNT-WOUND MOTOR



DECATION: When voltage tails or shunt field be interrupted the NoVoLTAGE release coil will automatically release the moveable arm, which is returned to its starting position by action of holding spring (not shown in diagram). This method of starting will prevent accidental application of a heavy current thru the motor armature, causing fuses to blow, or serious damage to motor.

STARTING RHEOSTAT AND CONNECTION DIA-GRAM FOR D.C. COMPOUND-WOUND MOTOR



CONNECTION DIAGRAMS FOR D.C. SERIES-WOUND MOTORS



CONNECTION DIAGRAMS FOR D.C. SHUNT-WOUND MOTORS



CONNECTION DIAGRAMS FOR D.C. COMPOUND-WOUND MOTORS



121

CONNECTION DIAGRAMS FOR UNIVERSAL TYPE MOTORS (A.C. OR D.C.)



CONNECTION DIAGRAMS FOR D.C. GENERATORS (TWO-WIRE)



Ŵ

CONNECTION DIAGRAMS FOR D.C. GENERATORS (TWO-WIRE)



CONNECTION DIAGRAMS FOR D.C. GENERATORS (THREE-WIRE)



CONNECTION DIAGRAMS FOR SYNCHRONOUS CONVERTERS (TWO-WIRE)



Standard Direction of Rotation Clockwise When Facing the Direct Current or Commutator End of Converter

The above (standard) direction of rotation is obtained only if the terminal subnumerals 1, 2, 3 applied to the collector rings M_1 , M_2 , M_3 are connected to alter nating current generator leads marked T_1 , T_2 and T_3 respectively. Due to the great variety of **shunt field** connections, these diagrams are shown separately from the other connection diagrams. In some cases a shunt field connection diagram may be used with only one machine diagram, whereas in other cases a machine diagram may be used in combination with any of several shunt field diagrams.





CONNECTION DIAGRAMS FOR SYNCHRONOUS CONVERTERS (TWO-WIRE)



127

WR

CONNECTION DIAGRAMS FOR SYNCHRONOUS CONVERTERS (TWO-WIRE)



SHUNT FIELD CONNECTIONS FOR SYNCHRONOUS CONVERTERS



SYNCHRONOUS CONVERTER WIRING DIAGRAM



TRANSFORMER CONNECTIONS AND VECTOR DIAGRAMS FOR SYNCHRONOUS CONVERTERS





WR

TRANSFORMER CONNECTIONS AND VECTOR DIAGRAMS FOR SYNCHRONOUS CONVERTERS



TRANSFORMER CONNECTIONS AND VECTOR DIAGRAMS FOR SYNCHRONOUS CONVERTERS



133

WRH







FREQUENCY CONVERTER-SET AND RESISTANCE STARTER FOR WOUND-ROTOR INDUCTION MOTOR



FRACTIONAL HORSEPOWER MOTOR DIAGRAMS

FRACTIONAL HORSEPOWER MOTORS



The Split-Phase Induction Motor. This motor type is commonly manufactured in fractional horsepower sizes. It is equipped with a squirrel-cage rotor for constant speed operation and has a starting winding of high resistance (commonly termed auxiliary winding), which is physically displaced in the stator from the main winding. This displacement produced by the relative electrical reistance values in the two windings, creates starting ability similar to that of a ployphase motor.

In series with the auxiliary winding is a starting switch (usually centrifugally operated) which opens the circuit when the motor has attained approximately 75 to 80 percent of synchronous speed.

The function of the starting switch is to prevent the motor from drawing excessive current from the line and also to protect the starting winding from damage due to heating. The motor may be started in either direction by reversing eithe the main or auxiliary winding.

Single-phase, split-phase motors are suitable for oil burners, blowers, busines machines, buffing machines, grinders, etc.


The Split-Phase, Permanently Connected Capacitor Motor. This type of splitshase motor, is commonly manufactured in fractional horsepower sizes.

In common with other types of split-phase motors, it is equipped with a squirretcage rotor and a main and auxiliary winding. A capacitor is permanently connected in series with the auxiliary winding, thus a motor of this type starts and uns with a fixed value of capacitance in series with the auxiliary winding.

The motor obtains its starting torque from a rotating magnetic field produced by the two stator windings physically displaced. The main winding is connected lirectly across the line, while the auxiliary or starting winding is connected to he line through the capacitor, giving an electrical phase displacement.

A motor of the permanent split-phase capacitor type is suitable for direct onnected drives requiring low starting torque, such as fans, blowers, certain ypes of centrifugal pumps, etc.

139

WR



The Split-Phase, Capacitor-Start Motor. This fractional horsepower motor marbe defined as a form of split-phase motor having a capacitor connected in serie with the auxiliary winding.

The auxiliary circuit is opened by means of a centrifugally operated switch when the motor has attained a predetermined speed (usually approximately 70 to 80 per cent of synchronous speed).

A motor of this type is sometimes termed a capacitor-start, induction-run moto in contrast to the straight capacitor run type which is termed a capacitor-start capacitor-run motor.

The rotor is of the squirrel cage type as in other split-phase motors. The main winding is connected directly across the line, while the auxiliary or starting winding is connected through a capacitor which may be connected into the circuit through a transformer with suitable designed windings and capacitor c such values that the two windings will be approximately 90 degrees apart.

This type of motor is particularly suited for such applications as air conditioning domestic and commercial refrigeration, belt driven fans, etc.





The Split-Phase, Capacitor-Run Motor. This type of motor, also termed twovalue capacitor-motor has a running capacitor permanently connected in series with the auxiliary winding, the starting capacitor being in parallel with the running capacitor only during the starting period.

In operation the motor starts with the starting switch closed. After the motor has attained a speed of approximately 70 to 80 per cent of synchronous, the starting switch opens, thus disconnecting the starting capacitor.

The running capacitor is usually of the paper-spaced oil filled type, normally rated at 330 volt A.C. for continuous operation. They usually range from 3 to 16 micro-farads, depending upon the size of the motor.

The starting capacitor is generally of the electrolytic type and may range in sizes of from 80 to 300 micro-farads approximately, for 110 volt, 60 cycle motors.

This type of motor is designed for applications requiring high starting torque, such as compressors, loaded conveyors, reciprocating pumps, refrigeration compressors, stokers, etc.



The Split-Phase Capacitor-Run Motor. Another type of two-value capacitor motor is using a capacitor transformer unit. The motor is of the split-phase squirrel cage type with the main and auxiliary winding physically displaced in the stator.

This type of motor employes a **transfer switch** which is equivalent to a single pole double throw switch, by means of which a high voltage is impressed across the capacitor during the starting period.

After the motor has attained a speed of 70 to 80 per cent of synchronous, the transfer switch operates to change the voltage taps on the transformer. The voltage impressed upon the capacitor by means of the transformer will be of a value of from 600 to 800 volts during the starting period and approximately 350 volts for continuous operation.

This type of motor is designed for applications requiring high starting torque such as compressors, loaded conveyors, reciprocating pumps, refrigeration compressors, stokers, etc.

WRH



The Split-Phase, Capacitor-Run, Induction Motor (Reversible type). In applications where it is necessary to employ a reversible high-torque intermittently rated capacitor type, a motor connected as shown has found employment.

When the reversing switch is in the B position, the auxiliary winding becomes the main winding, and the main winding becomes the auxiliary winding. With the switch in the A position, both windings functions as shown in the diagram.

Since the direction of rotation in split-phase motors is always from the auxiliary winding toward the main winding, it follows that an interchange of the winding will also reverse the direction of rotation.

From the foregoing it follows that with motor connections arranged in this manner, the main and auxiliary windings in the motor must be identical both as to size of wire and number of effective turns.



The Reactor-Start, Split-Phase, Induction Motor. This type in common with other types of split-phase motors is equipped with an auxiliary winding, displaced in magnetic position from, and connected in parallel with the main winding.

The function of the reactor is to reduce the starting current and increase the current lag in the main winding. At approximately 75 per cent of synchronous speed the starting switch operates to shunt out the reactor, disconnecting the auxiliary winding from the circuit.

The starting switch must be of such construction so as to be equal to a single pole double throw switch.

This is a constant speed motor and lends itself best for such applications as light running machines such as fans, small blowers, business machines, grinders, etc.



The Split-Phase, Single Value Capacitor Motor (Dual-Voltage Type). A motor of this type differs from the conventional type of capacitor motor in that it has two identical main windings arranged for either series or parallel connections.

With the main windings connected in parallel the line voltage is usually 220 volts, whereas when the main windings are connected in series a line voltage of 110 volts is usually employed.

The starting switch and operating characteristics of the motor do not differ from single-value capacitor-start motors previously described.

In common with other types of split phase motors, the auxiliary winding is a separate winding displaced in space from the main winding 90 degrees. Also in series with the auxiliary winding is the usual centrifugal switch and starting capacitor.

A winding arrangement of this type gives only half as much starting torque on 110 volts as on a 220 volts winding.



The Repulsion Motor. By definition a repulsion motor is a single phase motor which has a stator winding arranged for connection to the source of power and a rotor winding connected to a commutator. Brushes and commutators are shortcircuited and are so placed that the magnetic axis of the rotor winding is inclined to the magnetic axis of the stator winding.

It has a varying speed characteristic, a high starting torque and moderate starting current.

Due to its low power factor except at high speeds, it is often modified into the **compensated repulsion motor**, which has another set of brushes placed midway between the short-circuited set and this added set is connected in series with the stator winding.

The Repulsion-Start Induction Motor. By definition a repulsion-start induction motor is a single phase motor having the same windings as a repulsion motor, but at a predetermined speed the rotor winding is short- circuited or otherwise connected to give the equivalent of a squirrel cage winding. This type of motor starts as a repulsion motor, but operates as an induction motor with constant-speed characteristics.



It has a single-phase distributed field winding with the axis of the brushes dis placed from the axis of the field winding. The armature has an insulated winding.

The current induced in the armature is carried by the brushes and commutator resulting in high starting torque. When nearly synchronous speed is attained the commutator is short-circuited so that the armature is then similar in its functions to a squirrel cage armature.



The Repulsion-Start, Induction Motor (Reversible Type). In certain applicaions, it is necessary to reverse the direction of rotation. A motor of this type has wo stator windings displaced as indicated. Reversal of the motor can be accomplished by interchanging the field winding connections.

Thus, for example, with the switch in the upper position, the motor will rotate n a counter-clockwise direction, whereas if the switch be in the lower position he motor will run in the opposite direction, or clock-wise.

The Shaded-Pole Motor. By definition a shaded-pole motor is a single phase nduction motor provided with an auxiliary short-circuited winding or windings displaced in magnetic position from the main winding.



Although there are a number of different construction methods employed principally the motor operates as follows: The shading coil (from which the motor has derived its name) consists of low resistance copper links embedded in one side of each stator pole, and are used to provide the necessary starting torque. When the current increases in the main coils a current is induced in the shading coils that opposes the magnetic field building up in part of the pole pieces they surround.

When the main coil current decreases, that in the shading coil also decreases until the pole pieces are uniformly magnetized. As the main coil current and the pole piece magnetic flux continue to decrease, current in the shading coils re verses and tends to maintain the flux in part of the pole pieces.

When the main coil current drops to zero, current still flows in the shading coil to give the magnetic effect which causes the coils to produce a rotating mag netic field which makes the motor self starting.

This motor is used largely where the power requirements are small, such as in electric clocks, instruments, toys, hair dryers, small fans, etc. It is simple in con struction and low in cost and is in addition very rugged and reliable.

The Shaded-Pole Motor (Skeleton Type). This type of motor is built for ap plications where the power requirements are very small. The field circuit with



its winding, is built around the conventional squirrel cage rotor and consists or punchings that are stacked alternately to form overlapping joints, in the same manner that small transformer cores are assembled.

Motors of this class will operate only on alternating current; they are simple in construction, low in cost and extremely rugged and reliable. Their principal limitations are, however, low efficiency and a low starting and running torque.

A shaded pole motor is not reversible, unless shading coils are provided on each side of the pole, and means for opening one and closing the other coil are provided.

The inherently high slip of a shaded pole motor makes it convenient to obtain speed variation on a fan load, for example, by reducing the impressed voltage.

The Universal Type Motor. The universal motor is designed for operation on either alternating or direct current. It is of the series-wound type, that is, it is provided with a field winding on the stator which is connected in series with a commutating winding on the rotor.

Universal motors are commonly manufactured in fractional horse-power sizes and are because of their use on either A.C. or D.C. currents, preferred, particularly in areas where power companies supply both types of current.



Full-load speeds generally range from 5,000 to 10,000 r.p.m. with no-load speeds from 12,000 to 18,000 r.p.m. Typical applications are portable tools, office appliances, electric cleaners, kitchen appliances, sewing machines, etc.

The speed of universal motors can be adjusted by connecting a resistance of proper value in series with the motor. Advantages of this speed control method is obvious, in such applications as motor operated sewing machines, where it is necessary to operate the motor over a large range of speed.

In such applications adjustable resistances are used and the speed varied at will of the operator. Universal motors may be either compensated or uncompensated, the latter type being used for the higher speeds and lower ratings only.

Universal Motor Connection Method. As previously noted, speed regulation is commonly accomplished by means of a variable resistance in series with the motor. Speed reversal in a universal type motor is usually obtained by an interchange of the brush-holder leads, having the armature connected off neutral. In the split-series, three-wire reversible type universal motor, one stator coil is used to obtain one direction and the other stator coil to obtain the other direction of rotation, only one stator coil being in the circuit at a time. The only requirement being that the armature connections be on neutral in order to obtain satisfactory operation in both directions of rotation.

SYNCHRONISM INDICATOR AND WIRING DIAGRAMS

- SYNCHRONISM INDICATOR -

PARALLEL OPERATION OF SYNCHRONOUS GENERATORS Before Generator Z can be connected in parallel with Generator 7, the following conditions must be obtained:

(1) Both machines must have the some frequency and wave form. (2) Their terminal voltages must be equal.

GENERAL METHOD OF SYNCHRONIZING

(3) Their sequence of Maximum potential values must be the same. Whan synchronizing proceed as follows: 1. LAMP SYNCHRONIZING: Machine*I is running and supplying the load and

LAMP SYNCHRONIZING : Machine *1 is running and supplying the load and its ail circuit breaker is closed, the running plug is inserted. Bring machine 2 upto voltage by Slowly increasing the speed of its prime mover, as the speed of mach.*2 increases insert the starting plug, when now the machines are running at nearly the same speed, the synchronizing lamps light up then go out, light up again etc. If the machines are in steps with lamps out or lamps in, (Depending on if light or dark lamp connections are used) wait until they go out for a few seconds then close the oil circuit breaker on machine*2 and the machines are now in parallel.

Proceed same as before: The rotary motion of the pointer on the indicator indicates whether the Generator to be synchronized is running to slow or to fast. When the pointer remains stationary in the vertical position the two machines are in synchronism and the oil circuit breaker can be closed.

After paralleling the two machines adjust the mechanical power input and the generated e.m.f. until each machine supplies its share of the total load, and the power factor of each machine is the same and equal to that of the total load.













TRANSFORMER CONNECTIONS

CIRCUIT CONNECTIONS & DEFINITIONS OF VOLTAGE AND CURRENTS IN THREE-PHASE SYSTEMS.

In a three-phase system, (Transformer-circuit or apparatus) there are two voltages between which a sharp distinction must be made: The voltage



Fig.1

between the phase conductors, and the voltage from phase conductor to neutral (or ground where the neutral is at ground potential).

In the usual diagrammatic representation as in fig.1, these voltages are denoted as the delta-voltage and the star-voltage.

If then, I, 2 and 3 are the three phase conductors of a three-phase circuit, 0 the neutral, (regardless of whether it actually exists as conductor or not) the DELTA-VOLTAGES I-2, 2-3, 3-1 are variously called the, Line Voltage, Voltage Between Lines, Voltage Between Conductors, or simply the Three-phase Voltage or the voltage of the system; The STAR-VOLTAGES 0-1, 0-2, 0-3 are similarly called the Voltage To Ground, Voltage To Neutral, or Neutral Voltage, etc. Delta-voltage = 1.73 times Star-voltage. Star-voltage = <u>Delta-voltage</u> 1.73

Thus the delta-voltage is the higher one, the starvoltage being a part only of the delta-voltage. Similarly a distinction is made between the deltacurrent and the star-current in a three phase system. The DELTA-CURRENT is the current which flows from phase to phase: From 1to2, from 2 to 3, from 3 to1.

The STAR-CURRENT is often simply denoted as the Current, Current Per Phase, Line Current is the Current flowing in the phase conductors in 1, or 2, or 3 and may be supposed to flow towards the neutral O.

Star-current = 1.73 times delta-current Delta-current = <u>Star-current</u> 1.73

When speaking of the Voltage and the Current or LineVoltage and Line Current of a three-phase system, without further qualifications, the Delta Voltage and the Star Current are understood.

In the conventional denotations, voltage and current in the three-phase system thus do not correspond to each other; and therefore are not in phase with each other on noninductive load, but show a phase displacement of 30 degrees: the angle 0-1-2 in fig.1.

TRANSFORMERS & CONNECTIONS A transformer is defined as a form of stationary induction apparatus in which the primary and secondary windings are ordinarily insulated one from another. A transformer does not generate power, but merely changes the power from one voltage to another.

The three-phase transformer consists of three primary and three secondary windings, (see fig. 1) usually connected in star or delta respectively.

Single-phase transformers (see fig. 2), connected in star or delta are often preferable to three-phase transformers because of the fact that single-phase reverse units are less expensive; and also because damage to one single-phase transformer may be repaired, while another identical spare-transformer is inter-connected in the three-phase unit without loss of service.



Fig.1

When two sets of transformers are connected in parallel to the primary and secondary circuits of a threephase system, any combination of delta and star may be used in each set except that, with one set of transformers connected in delta-star or star-delta, the other set may not be connected delta-delta or star-star.

For example of transformer connections, See the following pages.



O TEST FOR POLARITY: WITH PRIMARY AND SECONDARY IN SERIES (ONE PRIMARY LEAD BEING ONNECTED TO THE ADJACENT SECONDARY LEAD) THE TRANSFORMER IS EXCITED FROM AN .C SOURCE ON EITHER SIDE AND THE VOLTAGES ACROSS THE HIGH-VOLTAGE WINDING AND LSO BETWEEN THE FREE PRIMARY AND SECONDARY TERMINALS ARE MEASURED. IF THE ATTER VOLTAGE IS FOUND TO BE LESS THAN THAT ACROSS THE HIGH-VOLTAGE WINDING, HE POLARITY IS SUBTRACTIVE, IF MORE IT IS ADDITIVE. IN TESTING FOR POLARITY A TRACTION OF THE RATED VOLTAGE IS SUFFICIENT. VECTOR AND WIRING DIAGRAM OF CONNECTIONS FOR INDICATING WATTMETER CONNECTED ACROSS A STAR-DELTA GROUP OF POWER TRANSFORMERS.



DIAGRAM SHOWING CONNECTIONS FOR STAR-STAR POWER TRANSFORMER GROUP TO OBTAIN ADDITIVE OR SUBTRACTIVE LINE POLARITY.



DIAGRAM SHOWING CONNECTIONS FOR DELTA-DELTA POWER TRANSFORMER GROUP TO OBTAIN ADDITIVE OR SUBTRACTIVE LINE POLARITY.



VECTOR AND WIRING DIAGRAM SHOWING CONNECTIONS FOR OBTAINING ADDITIVE LINE POLARITY WITH TRANSFORMER UNITS OF EITHER ADDITIVE OR SUBTRACTIVE POLARITY IN STAR-STAR GROUPS.



VECTOR AND WIRING DIAGRAM SHOWING CONNECTIONS FOR OBTAINING ADDITIVE LINE POLARITY WITH TRANSFORMER UNITS OF EITHER ADDITIVE OR SUBTRACTIVE POLARITY IN DELTA-DELTA GROUPS.



VECTOR AND WIRING DIAGRAM SHOWING CONNECTIONS FOR OBTAINING SUBTRACTIVE LINE POLARITY WITH TRANSFORMER UNITS OF EITHER ADDITIVE OR SUBTRACTIVE POLARITY IN DELTA-DELTA GROUPS.



DIAGRAM OF CONNECTIONS FOR TYPICAL POWER FACTOR INDICATOR CONNECTED ACROSS A STAR-DELTA TRANSFORMER BANK.



VECTOR AND WIRING DIAGRAM OF CONNECTIONS FOR INDICATING WATTMETER CONNECTED ACROSS A STAR-DELTA GROUP OF POWER TRANSFORMERS.



171

CONNECTIONS OF STAR-DELTA TRANSFORMER BANK, WITH ADDITIVE POLARITY UNITS.



CONNECTIONS OF DELTA-DELTA TRANSFORMER BANK , WITH ADDITIVE POLARITY UNITS.



CONNECTIONS OF STAR-STAR TRANSFORMER BANK, WITH SUBTRACTIVE POLARITY UNITS.





VECTOR AND WIRING DIAGRAM SHOWING SYNCHRONIZING CONNECTIONS ACROSS A DELTA-DIAMETRICAL BANK OF TRANSFORMERS CONSISTING OF SUBTRACTIVE POLARITY UNITS.



VECTOR AND WIRING DIAGRAM SHOWING THREE PHASE VOLTAGES CARRIED ACROSS VARIOUS TRANSFORMER GROUP FORMS RESULTING IN IN-PHASE VOLTAGES ON THE QUARTER PHASE SYSTEM.



VECTOR AND WIRING DIAGRAM SHOWING CONNECTIONS FOR DIFFERENTIAL PROTECTION AND SYNCHRONIZING ACROSS A STAR-DELTA TRANSFORMER BANK.


VECTOR DIAGRAM REPRESENTING CURRENT RELATIONS AT A GIVEN INSTANT IN CURRENT TRANSFORMERS ARRANGED FOR DIFFERENTIAL PROTECTION WITH POWER TRANSFORMERS CONNECTED IN STAR - DELTA. See opposite page.



VECTOR AND WIRING DIAGRAM SHOWING TYPICAL CONNECTIONS FOR DIFFERENTIAL PROTECTION AND SYNCHRONIZING ACROSS & DELTA-STAR TRANSFORMER BANK.



PRIMARIES AND SECONDARIES OF CURRENT TRANSFORMERS ON HIGH VOLTAGE SIDE



PHASE POSITION AND DIRECTION OF CURRENTS IN SECONDARIES ON HIGH VOLTAGE SIDE. (5.00 AMPERES)



PRIMARIES AND SECONDARIES OF CURRENT TRANSFORMERS ON LOW VOLTAGE SIDE. PHASE POSITION AND DIRECTION OF CURRENTS IN SECONDARIES ON LOW VOLTAGE SIDE. (8.66 AMPERES)

VECTOR DIAGRAM REPRESENTING CURRENT RELATIONS AT A GIVEN INSTANT IN CURRENT TRANSFORMERS ARRANGED FOR DIFFERENTIAL PROTECTION WITH POWER TRANSFORMERS CONNECTED IN DELTA-STAR. See opposite page.



VECTOR AND WIRING DIAGRAM SHOWING LOW DIFFERENTIAL RELAY MAY BE CONNECTED ACROSS A STAR-DELTA OR DELTA-STAR GROUP OF POWER TRANSFORMERS.



VECTOR AND WIRING DIAGRAM CONNECTIONS FOR DIFFERENTIAL PROTECTION AND SYNCHRONIZING ACROSS A SCOTT-CONNECTED BANK OF ADDITIVE POLARITY TRANSFORMERS.



VECTOR AND WIRING DIAGRAM OF CONNECTIONS FOR DIFFERENTIAL PROTECTION AND SYNCHRONIZING ACROSS A SCOTT-CONNECTED BANK OF SUBTRACTIVE POLARITY TRANSFORMERS.



VECTOR AND WIRING DIAGRAM SHOWING SYNCHRONIZING CONNECTIONS ACROSS A STAR-DIAMETRICAL BANK OF TRANSFORMERS CONSISTING OF ADDITIVE POLARITY UNITS.



BANK OF TRANSFORMERS CONSISTING OF SUBTRACTIVE POLARITY UNITS.



VECTOR AND WIRING DIAGRAM SHOWING SYNCHRONIZING CONNECTIONS ACROSS A STAR-DOUBLE DELTA BANK OF TRANSFORMERS CONSISTING OF SUBTRACTIVE POLARITY UNITS.



INDUSTRIAL CONTROL WIRING OF D.C. MOTORS

D.C. MOTOR STARTER WITH MAGNETIC CONTACTOR AND THREE CONTROL STATIONS



Motor Control by Means of Magnetic Contactor. The above diagram will facilitate the understanding of the advantage connected with the usage of a magnetic contactor, especially when it is desired to operate the motor from any one of several places, as for example in operation of a conveyor. The line magnetic contactors have a large following for the following reasons: (a) If the motor is to be operated at frequent intervals, less physical effort will be exerted to operate the push button than that required to close a heavy breaker; (b) A number of control stations may be arranged to operate the motor from several locations, thus saving time and providing for a more economical operation, especially since the control wiring consists of small inexpensive wire.

OPERATION. When the starting button is operated a circuit is formed through the operating coil causing the contactor to close its contact. The magnetic contactor does not open after the finger is removed from the starting button, because a new circuit is accomplished through auxiliary switch "A" by means of which the operating coil is energized. To stop the motor the trip button is operated. This action de-energizes the operating coil causing the contactor to open and disconnects the motor from its source.

D.C. MOTOR STARTER WITH MAGNETIC CONTACTOR AND OVERLOAD RELAY



OPERATION. When the starting button is operated a circuit is formed through the operating coil causing the contactor to close its contact. The magnetic contactor does not open after the finger is removed from the starting button, because a new circuit is accomplished through auxiliary switch "A" by means of which the operating coil is energized.

To stop the motor the trip button is operated. This action de-energizes the operating coil causing the contactor to open and disconnects the motor from its cource. The overload relay is set to operate at a certain overload depending upon the particular operating conditions but should in no case be caused to operate on the motor starting current.

D.C. COUNTER E.M.F. STARTER WITH TWO CONTACTORS



OPERATION. With reference to the diagram, this starter functions as follows: When the starting button is pressed the operating coil is energized through a resistance closing the magnetic contactor. After the finger has been removed from the starting button the lower section of the accelerating contactor is placed in series with the magnetic contactor operating coil. This reduces the power re quired to hold the magnetic contactor closed and the magnetizing action of the lower accelerating contactor coil aids the upper section of the coil closing thi contactor when the armature voltage has reached a predetermined value. The motor is disconnected from its course by means of operation of the trip butto which de-energizes the operating coil causing the magnetic contactor to oper

D.C. MOTOR STARTER WITH SERIES LOCKOUT CONTACTORS



OPERATION. Closing the starting button the magnetic contactor closes, connecting the motor to the line through all the series resistances. Contactor #2 closes its contacts as soon as the current has reached the value at which the contactor is set to operate. This shunts out R_2 and cuts in coil of contactor #1 in the circuit. As the accelerating process of the motor continues the current decreases and contactor #1 closes connecting the motor directly across the line.

D.C. MOTOR STARTING BY MEANS OF SERIES CONTACTORS



OPERATION. After the magnetic switch is closed and the starting button is released, R_{11} and R_{22} is connected in series with the closing coil. At the closing of the magnetic contactor, the shunt field is connected directly across the line and current passes from L₁ through the series field, armature, the whole starting resistance and the coil of contactor #1 to L₂. Contactor #1 will close when the current reaches a value corresponding to its setting. With the closing of this contactor R_1 is shunted out and the current flows through the series field, armature, R_2 , R_2 and the coils of contactors #2 and #1 to L₂. The decrease in current due to the closing of contactor will cause contactor #2 to be locked out. Contactor #2 closes as soon as the current has reached a value to which it is set. This action again shunts out R_2 and coil of contactor #3 is brought into the circuit. Contactor #3 closes when its current setting has been reached, shunting out R_3 , finally connecting the motor across its supply source. In this starting method, contactors #1 and #2 drop out while contactor #3 is held closed by the holding coil shown at the top of the contactor.

D.C. MOTOR STARTER EMPLOYING SERIES RELAYS



OPERATION. In this method of motor starting, an interlock type of relay is provided for each step of starting resistance. The relay contacts are normally held closed by gravity, although the magnetic force produced by the coil holds it open until the current has reached a set value. The starting method is as follows: The magnetic switch is closed in the usual manner causing the current to flow from L₁ through relay coil A, resistances R₁, R₂, motor armature to L₂. When the starting current reaches the value for which relay A is set, its contacts closes, which in turn causes contactor #1 to close. This action shunts out relay A and R₁ and provides a path for the current through R₂, relay coil B, and contactor #1. This operation is repeated until all the contactors are closed at which time the relay coils are shunted out and the motor is connected directly across the line.

D.C. STARTER WITH CURRENT LIMITING CONTACTORS



OPERATION. When the starting button is closed energizing the operating coil the magnetic contactor closes. The starting current flows from L₁ through the series field, armature, starting resistance, contactor coils C₁ and C₁₁ to L₁. The shunt field is connected directly across the line. After the current through contactor #1 has reached the contactors setting value, this contactor closes its contact, shunting out coils C₁, C₁₁ and R₁. This operation provides a current path through C₁₂₂, C₂ via contactor #1 and its coil C₁. After the current through contactor #2 has reached the contactors setting value, this contactor closes, and so the process is repeated until all the contactors are being closed, at which time the motor is connected directly across the line.

D.C. COMPOUND-WOUND MOTOR WITH SERIES RESISTANCE STARTER



OPERATION. When the starting button is pressed, contactor #1 closes, connecting the entire starting resistance in series with the motor. After a predetermined interval of time, contactor #2 is engaged shunting out resistance R. In a similar manner each one of the contactors will serve to cut out the resistance preceding it until the entire resistance has been shunted out and the motor is connected across the line at normal voltage. The overload relay serves to protect the motor against over-current and may be set to operate to suit individual operating conditions. When the over-current exceeds the setting value of the relay the relay contacts opens, de-energizing the solenoid coil which trips the contactors, disconnecting the motor from its supply source.



OPERATION. Direct current motors for motor-driven reversing mills, are used only on low voltage circuits usually not exceeding 250 volts, consequently remote control is easily secured and contactors can be used with entire satisfaction for closing, opening and reversing the armature circuit and for cutting out resistance. In addition to the disconnecting switches shown, a combined shunt field and control switch is supplied which renders it impossible to open the shunt field without at the same time disconnecting the armature from the line. An overload relay and shunt field relay afford protection respectively in case of overloads or accidental opening of the shunt field. Current limit relays insure uniform acceleration, while no-voltage protection is secured automatically since the contactors are actuated by line potential.

WIRING LIAGRAM AND FRONT VIEW OF TYPICAL FACE PLATE CONTROLLER



CPERATION. As shown in the illustrations the segments are installed in a circle on the face of the controller. Connections from these segments to the collector plates (designated A and A₁) are established by means of two arms which by a movement in either direction changes the resistance in the circuit to be operated, as indicated in the wiring diagram. Thus when the handle is moved in a forward direction sections of the starting resistance are cut out in steps, causing the armature to increase its speed.

When on the other hand the arm is moved in a reversed direction, the current becomes reversed in the armature (only) which causes the motor to rotate in the opposite direction. Finally when the arm is in the off position, the arm rests on two insulating plates in which case the operating handle is the vertical position.

WIRING DIAGRAM AND INSIDE VIEW OF TYPICAL DRUM CONTROLLER



Operation of Controller. The drum controller consists generally of a drum cylinder insulated from its central shaft to which the operating handle is attached. To facilitate the operation, copper segments are attached to the drum. These segments are connected to and insulated from one another as shown in the digaram of connections. A series of stationary fingers are arranged to contact with the segments. These fingers are insulated from one another but interconnected to the starting resistance and the motor circuit. The drum assembly has a notched wheel keyed to the central shaft, the function of which is to indicate to the operator when complete contacts are made. With reference to the diagram, when the controller is moved forward one notch, the fingers are in position 1. The current then flows from L_1 through all the series resistance to L_2 , and the motor starts rotating. When the handle is moved further the resistance is aradually being cut out of the armature circuit and inserted in the field circuit. Finally, when the handle is turned to notch 4, all the resistance has been transferred from the armature to the field circuit, and the motor is running at ful! speed.

REVERSING CONTROLLER FOR D.C. MOTOR



197

OPERATION. In some industrial processes a combination of dynamic breaking and reversing is required. A common type of switch for this requirement is shown, together with a sequence in which the contacts are made. With reference to diagrams, L1 and L1 are connected to the positive and negative terminals. When the handle is in the reverse position, H and A1 are positive, while F and F1 are negative, If the handle be turned to forward position F, F1 and H, A1 exchange polarities. Suppose that the motor armature be connected between A1 and F1, the current through it and hence the direction of rotation will be reversed as the handle is turned from reverse to forward. Therefore this switch is fundamentally a reversing switch and may hence be utilized in connection with any starter.



REVERSING CONTROL SWITCH WITH DYNAMIC BRAKE



WIRING DIAGRAM OF REVERSING AND DYNAMIC BREAKING CONTROLLER FOR D.C. MOTOR



OPERATION. As indicated in the diagram the shunt field is connected directly across the line through the rheostat when the switch is in a closed position. With reference to the diagram of the drum controller wiring, with the main switch in the **forward** position the line circuit is from L_1 to F_1 , through all the starting resistance, motor armature to the negative terminal and L_2 . Contractors #1, #2 and #3 close their contacts in sequence as the armature current decreases, which connects the motor directly across its supply source.

Dynamic Breaking. This is effected by turning the handle of the control switch from the **forward** to the **off** position. Segments in the control switch connects A_1 and B together, placing sections R_2 and R_3 of the starting resistance across the armature. This circuit provides dynamic breaking action causing the motor to slow down rapidly. As the motor slows down the generation voltage diminishes and the current through the resistance decreases as a consequence, tending to reduce the breaking torque.

INDUSTRIAL CONTROL WIRING OF A.C. MOTORS

The Functions of Motor Control. The elementary functions of any motor control are starting, stopping and reversing the motor. These functions however, are only a few of the many contributions which the control renders to efficient operation of modern electric drives. Among the common functions of motor control required in motor installations are:

- Motor Starting. This includes the basic function of starting and stopping the motor, including protection from overload and under-voltage when required
- Motor Starting and Reversing. This includes the basic function of starting the motor where the direction of rotation of the motor is changed at will of the operator.
- Motor Starting and Speed Regulation. Basic function of starting and stopping the motor involving speed regulation or adjustment of motor speed as by rheostat control.
- Motor Starting Reversing and Speed Regulation. Basic function of starting, stopping or reversing the motor involving speed regulation as by rheostat control.
- Motor Starting and Speed Selection. Basic functions of starting and stopping the motor, involving selection of one of several basic speeds as by pole changing.
- Motor Starting, Reversing and Speed Selection. Basic functions of starting, stopping and reversing, including selection of one of several basic speeds.

With respect to the general construction and method of starting and control required in motor installations as:

- Across the Line Starter. This consists of a line switch (with protection as may be required) for connecting the motor directly across the supply line. This method of starting is also referred to as "full voltage starting".
- 8. Starting Rheostat. Also referred to as the face-panel type. This is a type of rheostat whose stationary contacts are mounted upon the face of an insulating panel whose surface is a plane, the contacts being arranged in the form of an arc (or arcs) of a circle and the moveable contact (or contacts) being mounted upon a pivoted switch arm (or arms).
- 9. Primary Resistor Starter. A starter which provides reduced voltage to the primary of the motor by inserting resistance in the primary circuit during acceleration. The device includes the necessary switching mechanism, which may be manually or magnetically operated.
- Secondary Resistor Starter. A starter which reduces the primary starting current by inserting resistance in the secondary circuit usually the rotor of a wound rotor motor during acceleration. The device includes the

necessary switching mechanism, which may be manually or magnetically operated.

- 11. Compensator or Autotransformer Starter. A starter which provides for reduced voltage starting by means of a compensator or auto-transformer from which a predetermined fractional part of the winding is tapped off to produce voltage reduction to suit the particular starting load. The device includes the necessary switching mechanism to switch from the tap to full voltage and also to open the circuit of the compensator winding.
- 12. Star-Delta Starter. A star-delta starter is one which is applicable for starting of motors which have their windings arranged for full rated operation, with windings connected in delta, and arranged for starting at reduced voltage with windings connected in star.
- 13. Magnetic Controller. One wherein the main circuits are made and broken by magnetically operated switches controlled by a master switch located either within the controller or at any desired distance from the main controller.

With respect to the operation of the control circuit, magnetic controllers may be sub-divided as follows:

- 14. Non-Automatic. Where the operator is responsible for all control functions of starting, stopping and accelerating the motor.
- 15. Semi-Automatic. Where the rate of acceleration after starting by the operato ', is dependent upon accelerating contactors, which are adjusted to function under pre-determined conditions of currents, voltages and time.
- 16. Full-Automatic. Where all basic functions including starting or stopping of the motor, are performed without the necessity of manual direction in any degree after being initially energized.

With respect to their type for operating magnetic controllers, the sub-classification of master switches may be made as follows:

- 17. Drum Switch. In general for non-automatic types of controllers.
- 18. Push Button. In general for semi-automatic types of controllers.
- 19. Automatic Switch. Operated by float, pressure, etc., for full automatic controllers.
- 20. Emergency Run Feature. Provides a means for temporarily rendering the overload device inoperative during an emergency.

With respect to the proximity of the master switch, magnetic controllers may be sub-classified as follows:

21. Distant Motor Control. Where the master switch is mounted apart from, the main control panel.

22. Local Motor Control. Where the master switch may be combined with the main control panel.

The service classification of control resistors with reference to the duty period are:

- 23. Continuous Rating. Where the load is required to be carried for an unlimited period.
- 24. Periodic Rating. Where the load can be carried for alternate periods of load and rest.
- 25. Standard Periodic Rating. Where the starting and intermittent duty may be standardized as light, heavy, or extra heavy starting, or intermittent duty classifications.

The kind of protection to be provided where required may be termed as:

- 26. Low or Under-Voltage Protection. Operates to cause and maintain the interruption of the main power or reduction or failure of voltage.
- Low or Under-Voltage Release. Operates to cause the interruption of power upon reduction or failure of voltage, but not to maintain the interruption of power upon return of voltage.
- 28. Overload Protection. Operates to protect against escessive current to cause and maintain the interruption of current not in excess of six times the rated motor current.
- 29. Short-circuit Protection. Where the overload protection does not provide for short-circuit protection such short-circuit protection shall be provided as by fuses.
- 30. Single-Phase Protection or Indication. Where required, shall indicate and protect the personnel and equipment upon the failure of any part of the circuit which would cause an open phase.

MOTOR PROTECTIVE DEVICES

The function of motor protective devices are to protect the motor against certain abnormal conditions, such as:

- 1. Overloads.
- 2. Short-circuits.
- 3. Under-voltage, etc.

This includes devices which functions on the basis of temperature, voltage, frequency or time and causes the switching mechanism to operate when a predetermined set of conditions exist.

Overload Relays. These devices are of two general types, namely:

- 1. Thermal overload relay, and
- 2. Dash-pot overload relay.

Thermal and dash-pot overload relays are again divided into two types as:

- 1. Hand reset, and
- 2. Automatic reset.

As the name denotes, hand reset relays must be reset by hand after having tripped (usually by pressing a button projecting through the enclosing case) whereas the automatic reset type resets themselves automatically.

Thermal Overload Relay. The thermal overload relay consists of a heater coil which is connected directly to the line of the motor, and which heats up directly in the proportion of current flowing through it. Mounted adjacent to the neater is a strip of thermostatic metal anchored at one end, the other end being tree to move. As the thermostatic metal is made up of two metals rolled together (each metal having a different expansion constant) the thermostatic strip will bend or warp when heated.



Illustrating a Two-Pole Temperature Overload Relay with Detachable Heater and Thermal Unit. NOTE: Heater removed from right hand unit to show thermostatic metal strip. (Courtesy General Electric Co.)

Because one end is solidly anchored, all of the movement occurs at the free end. When the metal is cold, its end position prevents a trigger (on which control :ircuit contacts are mounted) from tripping.

A relay of this type is quite accurate and its operating characteristics is well defined. It is possible to design a heater that will raise the temperature of the thermostatic strip at the same rate as the temperature in the motor with which it is being used, and so adjust the relay that it will trip the control contacts when the temperature of the motor has reached the allowable maximum.

Because some time is required to transmit the heat from the heater coil to the thermostatic strip, it is not affected by monentary current increases. This makes it possible to start the motor with an inrush of six to ten times normal current without tripping the relay.

Dash-pot Overload Relay. The dash-pot overload relay uses the mechanical retardation principle of a dashpot to retard the movement of a core in a magnetic field, produced by a solenoid coil in series with the motor leads. Such an arrangement is affected by the quality of the mechanical clearance between piston and cylinder wall, changes in viscosity of the dash-pot oil caused by temperature variations and other extraneous conditions tending to upset its accuracy.



Illustrating Typical Dash-Pot, Two-Element Magnetic Type Overload Relay with Oil Dash-Pots to Give Inverse Time Tripping Characteristics. (Courtes) General Electric Co.)

It is mainly because of its inaccuracy that this relay is at present being replace by relays operating on the thermal principle.

Under-Voltage Protection. Under-voltage or low-voltage protection as it is sometimes called is defined as: The effect of a device operative on the reduction or failure of voltage, to cause and maintain the interruption of power to the main circuit.

With reference to the diagram page 206, under-voltage protection is provided for in the following manner: Contactor \mathbf{M} , handles the motor circuit. It contains a normally open contactor holding interlock \mathbf{B} , which closes when the contactor is closed.

The two-button, push-button station consists of a normally open start contact C and a normally closed stop contact D. When contact is made momentarily at C, by pressing the start button, the contactor coil M, is energized and contactor M closes, which in turn closes the interlock circuit B. It will be noted that the interlock B parallels the start contact C. The contactor is, therefore, held in through the interlock circuit B, even after the start contact C, opens up when the finger is removed from the button.

In the case of voltage failure, coil **M**, is de-energized and contactor **M** opens which in turn opens interlock circuit **B**. When voltage returns, the contactor will not close until the circuit is again established at **C**, by pushing the start button.

Under-Voltage Release. Under-voltage or low-voltage release is defined as: The effect of a device operative on reduction or failure of voltage to cause the interruption of power to the main circuit, but not to prevent re-establishment of the main circuit on return of voltage.

With reference to the diagram page 207, under-voltage release is provided for in the following manner: The control consists of a contactor **M**, for handling the motor circuit, and a maintained contact control switch **B**. Switch **B**, can be a knife switch, a float switch, a pressure switch or a maintained contact pushbutton station whose contacts close and remain closed regardless of the voltage on them.

To start the motor, the control switch **B**, is closed. This energizes the contactor coil **M**; the contactor **M**, closes and the motor is connected to the line. Now if voltage fails, the coil **M**, is de-energized and contactor **M**, opens. Nothing happens to contact **B**, as a result of the failure.

When this type of control is used on certain machines, such as saws, millers, etc. there is always danger if an operator returns to his machine and attempts to remove the saw or milling head, not realizing that the machine has stopped because of the momentary voltage failure. By providing under-voltage protection this hazard is eliminated, because the motor cannot restart when the power returns after a voltage failure, until the operator presses the start button.



Fundamental Wiring Diagram of Under-Voltage Protection as Employed on a Manually Operated Squirrel-Cage Induction Motor. It should be noted that any combination of control sequence for under-voltage protection can be obtained by applying these two fundamental rules: (1) Wire all stop buttons in series with the holding coil, with each other and with the electrical interlock. (2) Wire all start buttons in parallel with each other and with the interlock.



Fundamental Wiring Diagram Showing Method of Wiring to Obtain Under-Voltage Release. Under-voltage release allows the control to drop out if for any reason the power source voltage is inadequate, but when the voltage again reaches sufficient value the control will function automatically to connect the apparatus to the line through the proper starting sequence.

Control Methods of Squirrel Cage Motors. Polyphase induction motors of the squirrel cage type may be started and controlled by several methods. They are:

- 1. Directly across the line.
- 2. By means of autotransformers.
- 3. By means of resistors or reactors in series with the stator winding.
- 4. By means of the star-delta method.

Starting Current-Torque Relationship. Before discussing the various methods which are available for reducing starting current and improving line-voltage conditions, it is important to have a thorough knowledge of the effects of reduced voltage starting on the motor, as well as on the power system.

Any method which reduces the starting current to the motor is accomplished by a reduction in starting torque. Therefore, it is essential to know something about the load torque characteristics in determining if a given current limitation can be met. In other words, there are boundary conditions in which the permissible current to be taken from the line would not provide the needed output torque at the motor shaft, necessary for the successful acceleration of its connected load. With all starting methods, the torque of a squirrel cage motor varies is the square of the applied voltage at the motor terminals.

Across the Line Method of Starting. This is generally the most economical method of starting, but is on account of the large starting current required, usually limited to motors up to 5 horse power. With this method of starting the motor is connected direct to full line voltage by means of a manually operated switch or a magnetic contactor.

Starting by Means of Autotransformer. In the case of the autotransformer type of starting the current taken from the line varies as the square of the voltage applied to the motor terminals, and it is convenient to remember that the torque and line currents are reduced at the same rate. Thus, an autotransformer starter, designed to apply 80% of the line voltage to the motor terminals, will produce 64% of the torque that would have been developed if the motor had beer started on full voltage, and will, at the same time, draw 64% as much of the current from the line as would have been required for full-voltage starting.

Starting by Means of Resistors or Reactors. With resistor or reactor starting the starting current varies directly with the voltage at the motor terminals, because the resistor or reactor is in series with each line to the motor and mus carry the same current that flows in each motor terminal.

It is evident therefore, that the resistor and reactor type of reduced voltage starting requires more line current in amperes per unit of torque in foot-pounds than does the autotransformer type.

Thus, if a motor connected to a loaded centrifugal pump, for example, is started with 80% top on the autotransformer the initial torque is 64%. If, on the other hand, the motor were started with a primary resistor, limiting the starting voltage to 65% of line voltage, the initial torque would only be 42.25%.

On some power systems, it is necessary to meet a restriction on the rate of current increase in starting. The rate of increase of current is determined to meet the conditions as they exist at that particular point on the system where the motor is started.

Starting By Means of the Star-Delta Method. Three phase induction motors of the squirrel cage type may occasionally be started by the star-delta method. This starting method is associated only with motors designed for their full power with the delta connected three phase winding. There must also be provided additional leads from the motor which when regrouped will result in a star arrangement of the three phase winding.

There will be six main leads required from the motor to accomplish the switch from start across the line (star-connection) to run across the line (delta-connection). The starting connection is always star, since the voltage is $1/\sqrt{3}$ or 57.8% of the delta or line voltage.

From the foregoing it follows that this type of reduced voltage starter (which is limited to 57.8% of line voltage at starting) can be employed only where the motor has a light starting load. In all other applications higher starting voltages are obtained with the resistor, reactors or autotransformers as previously outlined.



Illustrating Typical Connection Diagram when Star-Delta Method of Starting is Used for Squirrel-Cage Induction Motor. In the case of large motors that is motors rated above 5 h.p. a special oil switch controller is most commonly employed.


Fundamental Wiring Diagram of Typical Across the Line Non-Reversible, Single-Speed, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Non-Reversible, Single Speed, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Across the Line, Non-Reversible, Single Speed, Magnetically Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Non-Reversible, Single Speed, Magnetically Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Across the Line, Reversible, Single Speed, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Reversible, Single Speed, Manually Operated Squirrel-Cage Induction Motor



Jamental Wiring Diagram of Typical Reduced Voltage, Non-Reversible, le Speed, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Two-Speed t Reversible, Manually Operated Squirrel-Cage Induction Motor.



damental Wiring Diagram of Typical Across the Line, Two Speed, Nonersible, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Two-Speed, N Reversible, Manually Operated Squirrel-Cage Induction Motor.



undamental Wiring Diagram of Typical Across the Line, Two-Speed, Nonleversible, Magnetically Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Two-Speed, Nor Reversible, Magnetically Operated Squirrel-Cage Induction Motor.



^cundamental Wiring Diagram of Typical Across the Line, Two-Speed, Reversible, Manually Operated Squirrel-Cage Induction Motor.



Fundamental Wiring Diagram of Typical Reduced Voltage, Two-Speed, R versible, Manually Operated Squirrel-Cage Induction Motor.



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel-Cage Induction Motor. The push button circuit consists of two control stations, each with two momentary contacts, one closed and one open. The circuit provides under-voltage protection. The operating duty is: Start-stop, start-stop.



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel-Cage Induction Motor. The push button circuit consists of two control stations with only three wires between the stations. The circuit provides under-voltage protection. The operating duty is: Start-stop, start-stop.



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel-Cage Induction Motor. The push button circuit consists of one control station, with two momentary-contact buttons and one selector switch. The circuit provides under-voltage protection plus inching. The operation duty is: Start-run, inch-stop.





Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel-Cage Induction Motor. The push button circuit consists of one push button station, with three momentary contacts and an inching relay. The circuit provides under-voltage protection plus fool-proof inching. The operating duty is: Startinch-stop.



Viring Diagram of Typical Remotely Controlled Magnetically Operated Squirrelage Induction Motor. The push button circuit consists of one control station vith two momentary-control buttons, one open and one closed with safety latch. he circuit provides under-voltage protection. The operating duty is: Start-stop on inch for latch).



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel Cage Induction Motor. The push button circuit consists of one-control station with three momentary contact buttons of which two are open and one closed The circuit provides under-voltage protection plus inching by holding dowr stop button. The operating duty is: Start-inch-stop.



Viring Diagram of Typical Remotely Controlled Magnetically Operated Rersible Squirrel-Cage Induction Motor. The push button circuit consists of one antrol station, with three momentary contact buttons, two open and one closed. The circuit provides under-voltage protection, interlocked through push buttons. The operating duty is: Forward-reverse-stop.

231



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Reversible Squirrel-Cage Induction Motor. The push button circuit consists of or control station, with three momentary contact buttons, two open and one close. The circuit provides under-voltage protection with electrical interlocks. The operating duty is: Forward-reverse-stop.



Wiring Diagram of Typical Remotely Controlled Magnetically Operated Squirrel-Cage Induction Motor. The push button circuit consists of one control station with two momentary control buttons, one open and one closed, plus an indicating ight showing operating position of contactor. The circuit provides under-voltage protection. The operation duty is: Start-stop.

233



Wiring Diagram of Typical Across the Line, Single Speed, Non-Reversible, Magnetically Operated Squirrel-Cage Induction Motor.



Wiring Diagram of Typical Reduced Voltage, Single Speed, Non-Reversible, Magnetically Operated Squirrel-Cage Induction Motor. In the Diagram T.C. is a Time Closing Contact.

ACROSS THE LINE A.C. MOTOR STARTING ARRANGEMENT



MANUAL COMPENSATOR WITH MAGNETIC OVERLOAD RELAYS



OPERATION. The motor is disconnected from the line when the contactor operating handle is in the **off position**. In starting, the handle is thrown to the **start position** which closes the starting contacts forming connections through the Yconnected auto-transformers which reduces the impressed voltage of the motor during the **starting period**. After normal speed is reached, the operating handle s thrown to the **run position**, which opens the starting, and closes the **running** contacts, connecting the motor directly across the line.

237

MANUAL COMPENSATOR WITH THERMAL OVERLOAD RELAY



OPERATION. The starting of the motor is accomplished as follows: With the motor disconnected from the line the operating handle is in **off position**. **First step**. Throw the operating handle to the start position. The motor is now connected to the line at reduced voltage through the taps of the auto-transformer.

Second step. After the motor has reached normal speed operate the handle to **run position**; at this time the starting contacts are automatically disengaged, and the motor is connected across the line at full voltage.

STARTING AND REVERSING CONTROL ARRANGEMENT FOR A THREE PHASE INDUCTION MOTOR



OPERATION. In some industrial processes it is necessary to run the motor alternately at forward and reverse direction.

This is accomplished by a control arrangement which interchanges the connection of two of the three supply lines to the motor.

In following through the wiring method it will be observed that when the forward button is operated the forward contactor coil will be enorgized closing the contactor, connecting the motor to the line. If it be desired to reverse the motor, it is necessary merely to press the reverse button, which opens the circuit of the forward contactor coil and closes the reverse contactor at the same time interchanging two of the line wires. The motor is now

running in the reverse direction. This operating method is not common where large motors are employed due to the fact that a heavy starting current will cause undesirable voltage fluctuation in the power line system.

A.C. MOTOR

239

RESISTANCE STARTING FOR A.C. MOTOR



is maintained through the time interlock on the dash-pot timer, whose contact close after a definite time has elapsed. This in turn completes the circuit throug the coil of contactor #2, which closes its contacts, shunting out the starting resist ance and connects the motor at full voltage directly across the line.

AUTOMATIC STARTING CONTACTOR FOR **REMOTE CONTROL OPERATION**



OPERATION. This type of contactor operates as follows: when the starting button is operated the starting contactor coils become energized closing the starting contacts of the contactor, which connects the motor to the line through a suitable tap of the auto-transformer. A circuit which operates the timing relay is also completed closing the contacts which connect terminals 1 and 2 and thus A.C. MOTOR completes the holding circuit for the relay coil.



Finally after a definite time depending upon the relay setting the escapement releases and allows the contact arm to break the contact at 6 and make contact at 4 causing the starting contact to open and the running contacts to close connecting the motor directly across the line.

DIAGRAM OF INDUCTION MOTOR CONTROL FOR STEEL MILL, MAIN ROLL DRIVE



OPERATION. The essential parts of the control for a large induction motor are relatively few and simple, though sometimes the interlocking devices when carried to an unnecessary extent become exceedingly complex. This diagram shows a typical arrangement of control for such a motor where only occasional partial speed operations or reversal is required. The incoming line passes through disconnecting switches by means of which the motor and control can be completely isolated from the line during adjustments or repairs. For high voltage motors a double-throw hand-operated reversing oil switch with inverse time limit overload and no-voltage release is employed in addition. A push button located conveniently in the mill short circuits the no-voltage release, thus tripping out the oil switch and stopping the motor in emergency. (Text continued)

INDUCTION MOTOR CONTROL FOR STEEL MILL, MAIN ROLL DRIVE

Ihe motor panel should be provided with a voltmeter, ammeter and indicating wattmeter. Integrating and curve drawing wattmeters are often desirable. The secondary circuit consists of a three-phase resistance permanently connected to the slip rings. Shunt contactors of the double-pole type (where sizes permit) are used to short circuit successive portions of the resistance as the motor accelerates. The energizing current is obtained from a potential transformer in the primary circuit between the oil switch and the motor. Current limit relays govern the rate of acceleration. In case the primary oil switch is opened intentionally, or by means of the no-voltage release, the secondary circuit so that, even with the master controller still in the running position, the motor will receive no harm when the voltage is again thrown on the line. This automatic action of the secondary contactors also affords protection against reversing with the resistance all cut out, since the contactors drop out as the oil switch is opened and notch again as it is thrown to the reverse position.

CONTROLLERS FOR A.C. MOTOR OPERATING AT TWO SPEEDS



OPERATION. Generally the purpose of controllers for motors having more than one speed is to interconnect the stator terminals in a desirable manner and also to connect them to the line as required for each speed. In the system of control under consideration, the schematic diagram shows the basic principles. Here for the sake of clarity the high speed and low speed contacts are labeled "H" and "L" respectively.

With reference to the complete diagram, one button is utilized for each speed. If it be desired to change the speed from low to high for example, the operation of the high speed button will automatically cause the motor to change over to that speed.

CONTROLLERS FOR A.C. MULTI-SPEED MOTOR



Note. For operating data see following page.

215

CONNECTION DATA FOR MULTI-SPEED A.C. MOTOR

SPEEDS	OMIT JUMPERS	CONNECT TERMINALS AS FOLLOWS
600/900	a and c	$\begin{array}{c} T_1 - T_{37}, \ T_2 - T_{40}, \ T_3 - T_{41}, \\ T_4 - T_{30}, \ T_5 - T_{31}, \ T_6 - T_{32}, \\ T_7 - T_{42}, \ T_{11} - T_{36}, \ T_{12} - T_{38}, \\ T_{14} - T_{33}, \ T_{15} - T_{34}, \ T_{16} - T_{35}, \\ T_{17} - T_{43} \end{array}$
600/1200	b and c	$\begin{array}{c} {}^{T_1-T_{33}-T_{37},\ T_2-T_{34}-T_{40},}\\ {}^{T_3-T_{35}-T_{41},\ T_4-T_{30},}\\ {}^{T_5-T_{51},\ T_6-T_{32},\ T_7-T_{36}-T_{42}} \end{array}$
600/1800	b and c	T_1-T_37 , T_2-T_{40} , T_3-T_{41} , T_4-T_{30} , T_5-T_{31} , T_6-T_{32} , T_7-T_{42} , $T_{11}-T_{32}$, $T_{12}-T_{34}$, $T_{13}-T_{35}$, $T_{17}-T_{36}$
900/1200	b and c	$T_{1}-T_{33}$, $T_{2}-T_{34}$, $T_{3}-T_{35}$, $T_{12}-T_{40}$, $T_{13}-T_{41}$, $T_{14}-T_{30}$, $T_{15}-T_{31}$, $T_{16}-T_{32}$, $T_{17}-T_{42}$
900/1800	b and c	$T_{11}-T_{33}-T_{37}$, $T_{12}-T_{34}-T_{40}$, $T_{13}-T_{35}-T_{40}$, $T_{14}-T_{30}$ $T_{15}-T_{31}$, $T_{16}-T_{32}$, $T_{17}-T_{36}-T_{42}$
1200/1800	b and d	$T_{1}-T_{30}, T_{2}-T_{31}, T_{3}-T_{32}, T_{7}-T_{37}, T_{11}-T_{33}, T_{12}-T_{34}, T_{13}-T_{35}, T_{17}-T_{37}$

OPERATION. In the connection diagram shown on the previous page, the 4-speed motor is connected for two speeds, that is when the low speed button is operated three of the contacts connect the winding parallel-star and the three connect the winding to the line.

This gives eight poles or a synchronous speed of $\frac{120 \times 60}{9}$ or 900 r.p.m.

Again when the high speed button is operated the low speed contacts opens and the delta connection is completed connecting the winding to the line through six poles which gives a synchronous speed of $\frac{120 \times 60}{6}$ or 1200 r.p.m.

Method of connection to obtain 4 speeds is shown in the accompanying table.

246

WRH
MISCELLANEOUS WIRING DIAGRAMS

















EMERGENCY SWITCHING METHODS



REMOTE CONTROL WIRING FOR OIL CIRCUIT BREAKER (SOLENOID OPERATED TYPE)



[umu]

VARIOUS SWITCHING METHODS



WRH

MOTOR DISCONNECTING AND CONTROL METHODS



POWER DISTRIBUTION AND WIRING METHODS



The above diagrams suggest three methods of motor wiring. However, due to individual operating conditions the type of wiring adopted should be carefully analyzed for the particular case involved. Certain applications for example by their very nature will prove themselves better suited for one scheme than the other. The "National Electric Code" as well as any local requirements should be strictly adhered to and the wire should be of ample capacity to prevent excessive voltage drops.

REMOTE CONTROL WIRING FOR SMALL MOTORS



Note. All motors and control wiring should be carefully installed in accordance with the "National Electric Code" and any local requirement. The wire should be of ample capacity based on a maximum drop of 2 per cent of line voltage at full load current.

HEATING ELEMENTS ON THREE-PHASE SYSTEMS



DIAGRAM OF CONNECTION FOR ELECTRIC RANGE



In a standard type of electric range such as that shown, the various heating elements are connected in such a manner that a nearly balanced load is established under all conditions of usage.

As each heating element is rated at less than 30 amp. each no fuses are required to protect the elements and their connecting wires except in the receptacle circuit, where an exterior appliance may be connected.

The wiring should be of an approved and sufficient size to supply the range at its rated wattage without overheating. Generally for a range rated at 7500 watts #8 wire is required.

SWITCHING PANELS AND FEEDER DISTRIBUTION METHODS





MOTOR CONTROL METHODS





Schematic wiring diagram showing typical feeder layout and watthour meter connections for a single phase three wire 115/230 volt a.c. system.

Automatic Electric Water Heaters



Wiring diagram for limited demand service on a single unit water heater. In a circuit of this type, the single throw, single pole thermostat functions to close and open the circuit to the heating unit, at specified temperatures according to its setting. The time controlled switch will determine the hours of the day when the circuit will be opened or closed, thus preventing unlimited use of hot water during the hours of greatest power load.

.

Automatic Electric Water Heaters



Wiring diagram for limited demand service on double-unit water heater. In a wiring method of this type the upper heating unit is controlled by a double throw single pole thermostatic switch. This switch has two sets of contacts, one of which controls the flow of current to the upper heating unit and the other controls the flow of current to the lower thermostat. The lower heating unit is controlled by a single throw, single pole thermostatic switch. This switch has only one set of contacts and opens and closes in response to the temperature of the water in the lower tank. The function of the time switch is to prevent unlimited use of hot water during a predetermined time (or times) usually during that period of the day when the general demand for power is the greatest.



Typical wiring diagram showing connection of a compound-wound motor to its face plate starter. For shunt-wound motors the series field coil is omitted. This starter is used for *starting duty only*.



Typical wiring diagram showing connection of a compound-wound motor to its face plate starter. For shunt-wound motors the series field coil is omitted. This starter is used for starting and speed regulating duty by field control only.



Typical wiring diagram showing connection of a compound-wound motor to its face plate starter. For shunt-wound motors the series field coil is omitted. This starter is for speed regulating duty-50% speed reduction by armature control.



Typical wiring diagran, showing connection of a compound wound motor to its face plate starter. For shunt-wound motors the series field coil is omitted. This starter is used for speed regulating duty—50% speed reduction by armature control and 25% increase by field control.

READ AUDELS MECHANICS GUIDES A BRIEF SUMMARY OF CONTENTS

AUDELS PAINTING & D'CORATING MANUAL 54

JUST OFF THE PRESS. A RELIABLE GUIDE FOR PAINTERS, JOURNEYMEN, APPRENTICES, CONTRACTORS. HOME OWNERS, AND ALL PAINT USERS.

The hook is divided into two sections. Section I, contains information on: basic tools and equip-ment; selection of proper paint; guide to color; techniques of applying paint with brush, roller and spray gun; wood and floor finishings. Section II, provides information about cost estimate; glossary of painting terms; paint chemistry; a review of the necessary mathematics and information about running a painting business.

585 pages; profusely illustrated.

5/1 AUDELS GAS ENGINE MANUAL

An up-to-date practical book covering the construction, operation and repairs on all types of modern gas engines. Part I, covers gas engine principles; two and four-stroke cycle engines; engine parts; auxiliaries; timing methods; ignition systems. Part II, covers trouble shooting; servicing and repairs. 467 pages; fully illustrated.

Audels REFRIGERATION & Air Conditioning Guide \$6

4 Books in One; covering basic principles, servicing, operation, repair of :---1. Household Refrigeration. 2. Special Refrigeration Units. 3. Commercial and Industrial Refrigeration. 4. Air Conditioning Systems. A gold mine of essential important facts for Engineers, Servicemen and Users.

gold mine or essential more and facts to Engineers, service and out of a complete Library in ONE VOLUME, A Good Book is a Good Friendl Here you have at your fingers' ends a Complete Library in ONE VOLUME, the necessary data you have been looking for on: MODERN UNITS, SYSTEMS & MACHINES, REFRIGER-the necessary data you have been looking for on: MODERN UNITS, SYSTEMS & MACHINES, REFRIGER-

ANTS including Freen, Quick Freezing, Lockers, Water Coolers & Air Conditioning Systems. 1360 Pages, 46 Chapters all Fully Illustrated & Indexed for Ready Reference with Answers to Your Questions.

AUDELS WATER SUPPLY & SEWAGE DISPOSAL GUIDE \$4

Just off the Press. A practical fully illustrated book giving detailed data on every phase of rural water supply, septic tank and sewage systems. A MUST BOOK for plumbers, well drillers, home owners and farmers located outside of Municipal water and sanitary service areas. CONTAINS PRACTICAL INFORMATION ON: How to locate and build wells-water pumps and pumping systems pump controls pressure tanks-hydraulic rams water treatment methods how to calculate pumping systems sewage disposal methodsseptic tank layouts drainage systems-drainage pumps water heaters, gas and electric-installation methods-plumbing system essential, 436 PAGES.

AUDELS GUIDE TO CREATIVE PHOTOGRAPHY . \$3.95

Practical from first page to the last, written in simple, concise, easy-to-understand language. All technical terms are clearly defined and profusely illustrated. Its vast scope-from simple picture-taking techniques to elementary developing and printing, from lens optics to photo chemi try, from principles of photo composition to techniques of working with color-an Informative volume for all interested in photography. 416 pages.

A new practical, concise treatise explaining in detail both domestic & industrial oil burners, including electrical hook ups and wiring diagrams.

416 pages, 320 illustrations & diagrams. Pocket size.

Fully covering the Theory, Construction, Installation, Operation, Testing, Servicing & Repair of all oil burner equipment. Fully indexed for ready reference.

AUDELS AUTO MECHANICS GUIDE

PRACTICAL READY REFERENCE FOR AUTO MECHANICS, SERVICE MEN, TRAINEES & OWNERS Explains theory, construction and servicing of modern motor cars, trucks, buses, and auto type Diesel engines, 1132 pages, fully illustrated, 73 chapters, Indexed,

FEATURES: All parts of an automobile-physics-gas engines-pistons-rings-connecting rods-crank shafts-valves-valve gear-cams-timing-cooling systems-fuel feed systems-mixture-carburetorsautomatic choke—superchargers—transmissions—clutches—universals, propeller shafts—differentials—rear axles—running gear—brakes—wheel alignment—knee action—steering gear—tires—lubrication—ignition systems-spark plugs-ignition coils-distributors-automatic spark control-ignition timing-generators --starters-lighting systems-storage batteries. Fluid & Hydramatic Drives Fully Explained A STANDARD BOOK FOR AUTO MECHANICS AND OPERATORS

AUDELS TRUCK & TRACTOR GUIDE

A Shop Companion for Truck Mechanics & Drivers-Shop Foremen-Garagemen-Maintenance Men-Helpers-Owners-Trouble Shooters-Fleet Maintenance Men-Bus Mechanics & Drivers-Farm Tractor Operators & Mechanics-Covering Gas & Diesel Motor Principles-Construction-Operation-Maintenance -Repair-Service Operations-Trouble Shooting-Engine Tune Up-Carburetor Adjusting-Ignition Tuning-Brakes-Service of all Parts-1376 Pages. 78 PRACTICAL FULLY ILLUSTRATED CHAPTERS-INDEXED-1001 FACTS AT YOUR FINGER ENDS.

AUDELS DIESEL ENGINE MANUAL

A PRACTICAL, CONCISE TREATISE WITH QUESTIONS AND ANSWERS ON THE THEORY, PRAC-TICAL OPERATION AND MAINTENANCE OF MODERN DIESEL ENGINES.

640 pages, fully illustrated. Explains Diesel principles-starting-starting valves-fuel spray valves-valves -timing-fuel pumps-fuel injection compressors-starting air compressors-scavenging air compressors -pistons and piston rings-cylinders-lubrication-cooling systems-fuel oil-engine indicator-governors -engine reversing-semi-Dieset engines-high speed Diesel engines-answers on operation-calculations. including two-cycle Diesel engines.

THIS BOOK IS OF EXTREME VALUE TO ENGINEERS, OPERATORS, STUDENTS,

AUDELS WELDERS GUIDE

A CONCISE, PRACTICAL TEXT ON OPERATION AND MAINTENANCE OF ALL WELDING MACHINES, FOR ALL MECHANICS,

608 pages, fully illustrated 5 x $6\frac{1}{2}$ x 2. Covers Electric, Oxy-acetylene, Thermit, Unionmelt Welding for sheet metal, spot and pipe welds, pressure vessels and aluminum, copper, brass, bronze and other metals, airplane work, surface hardening and hard facing, cutting, brazing-eye protection, EVERY WELDER SHOULD OWN THIS GUIDE,

AUDELS ANSWERS ON BLUE PRINT READING \$3

COVERS ALL TYPES OF BLUE PRINT READING FOR MECHANICS AND BUILDERS. 448 pages, very fully illustrated, service bound, pocket size.

How to read scales-the standard symbols-detail and assembly prints-the different kinds of working drawings; orthographic, pictorial, descriptive-development by parallel and radial lines, conventional lines, triangulation. Warped and other surfaces-specifications-how to sketch-how to make working drawingshow to make blue prints—short cuts—helps—hints and suggestions. "The blue print of to-day is the machine of to-morrow." The man who can read blue prints is in line for a

better job. This book gives you this secret language, step by step in easy stages. NO OTHER TRADE BOOK LIKE IT.

AUDELS NEW MECHANICAL DICTIONARY \$6.95

The authoritative word book for Mechanics, Technicians and Students. With the revolutionary progress being made today in all mechanical fields, new words and phrases come into use. Any mechanic who wants to be up to date must know this new trade language. Audels New Mechanical Dictionary gives you these new words and also the old. Every mechanic will find his job made easier if he knows the exact meaning and use of technical words that come up every day at work. It is an engineer's shop companion and a student's guide. DEFINES 17,000 WORDS-TERMS, PHRASES-RULES AND FORMULAS, 712 PAGES.

AUDELS DO-IT-YOURSELF ENCYCLOPEDIA 2 Vols. \$8.95

Over 1,000 pages, packed with step-by-step plans, thousands of photos, helpful charts. Fully indexed and alphabetized, A really authentic, truly monumental, home repair and home project guide.

EVERYTHING YOU NEED TO KNOW

INSIDE THE HOUSE ... OUTSIDE THE HOUSE ... AROUND THE HOUSE

Air conditioning Aluminum Anatomy for building Asphalt tiles Attics Basements **Book rack** Breakfast nook **Built-ins** Bunk beds Ceilings Cement Ceramic Closet Concrete Concrete patching and repair Conner tubing Cork, floors and walls Cornice, window Doors.

A PARTIAL LIST OF CONTENTS

Dormer Dry rot Electrical bazards Electric wiring Finishing wood floors Fire hazards Firebrick Fireplaces Flagstone tiles Floor repairs Foundation drainage Furniture finishing renairs Garden concrete blocks Glass cutting Glazing windows Guide to painting **High Fidelity** House, structural parts Insulation lalousie

Kitchen lavouts contemporary appliances modernizing ideas storage cabinets Lacquer finish Lawn grass guide Lawn mower Lighting flytures Locks Lumber Magnetic circuit breaker Marble tile Masonry Miter joint Mortar Paint Painting Pickled pine finish Pines Plastic tile Plumbing

Plywood Polishing buffs and compounds Pools Radiator covers Boom dividers Safety checklist Sanding old floors Screens Shellac finish Spray painting Stain finishes Stairs Sticking drawers Storm door Termite Upholstering Varnish finish Wallnapering Wood floors Work bench

AND THOUSANDS OF OTHER IMPORTANT SUBJECTS

AUDFUS HOME APPLIANCE SERVICE GUIDE -\$6

864 Pages-500 Illustrations • 1001 Facts. A PRACTICAL "HOW TO DO IT" BOOK.

For Practical Electric & Gas Servicemen, Mechanics & Dealers, Covers Principles, Servicing & Repairing of Home Appliances, Tells How to Locate Troubles, Make Repairs, Reassemble & Connect, Wiring Diagrams & Testing Methods. Easy to Read. How to fix Electric Refrigerators, Washers, Rangers, Toasters, Ironers. Broilers, Dryers, Vacuums, Fans, also many other Gas & Electric Appliances. Lawn Mowers.

AUDELS POWER PLANT ENGINEERS GUIDE 55

A COMPLETE STEAM ENGINEERS LIBRARY IN ONE BOOK WITH QUESTIONS & ANSWERS. 1568 Pages, over 1700 clear, expertly drawn Illustrations, Graphs and Charts. 1001 FACTS & FIGURES AT YOUR FINGER ENDS. For all Engineers, Firemen, Water Tenders, Oilers, Operators, Repairmen and Applicants for Engineers' License Examinations.

SPECIAL FEATURES INCLUDE: Boilers, all types; Boiler and Engine room Physics; Fireman's Guide: Boiler Examination Questions; Boiler Operation; Pulverized Coal Systems; Instant Steam; Boiler Fixtures: Boiler Renairs and Calculations: Boiler Accessories; Feed Pumps; Feed Water Heaters; Economizers; Feed Water Treatment and Deaeration; Indectors; Safety Valve Calculations; Mechanical Stokers; Oil Burners; Condensers; Air Pumps and Air Ejectors; Evaporators; Steam and Hot Water Heating; Pipe Fitting. Steam Engines; Valve gears; Turbines; Compressors; Hoists; Gas and Diesel Engines; Lubricants and Lubrication.

65 Instructive, Interesting Illustrated Chapters-ALL FULLY INDEXED FOR READY REFERENCE.

AUDELS QUESTIONS & ANSWERS FOR ENGINEERS AND FIREMANS EXAMINATIONS . \$2.50

An aid for Stationary, Marine, Diesel & Hoisting Engineers' Examinations for all grades of Licenses. A new concise review explaining in detail the Principles, Facts & Figures of Practical Engineering, 544 Pages & 435 Ilustrations of Questions & Answers, fully indexed for ready reference. Pocket size.

AUDELS SHEET METAL PATTERN LAYOUTS ... \$7.50

10 Sections, 1152 pages, 350 layouts, 1600 illustrations,

A PRACTICAL ILLUSTRATED ENCYCLOPEDIA COVERING ALL PHASES OF SHEET METAL WORK INCLUDING PATTERN CUTTING, PATTERN DEVELOPMENT AND SHOP PROCEDURE. 10 Big Sections Covering: Heating & Air Conditioning Duct Patterns-Special Sheet Metal Layouts-Lay-

outs for various sheet metal shapes-Conductors, Leaders and Leader Head Layouts-Gutters and Roof Outer Layouts-Sheet Metal Boat Patterns - Geometrical Problems, Mensuration and Sheet Metal Boat Patterns Developed by experts for Sheet Metal Workers—Layout mon—Mechanics and Artisans, Apprentices and Students. A MASTER BOOK FOR ALL THE SHEET METAL TRADES.

AUDELS SHEET METAL WORKERS HANDY BOOK \$2.50

Containing practical inside information, essential and important facts and figures. Easy to understand, Fundamentals of sheet metal layout work. Clearly written in everyday language covering: Aircraft sheet metal work, principles of pattern cutting, sheet metal work layout, development of air conditioning ducts, sheet metal machines, welding sheet metal, boiler plate work, practical drawing, how to read plans, geometrical problems, mensuration. FULLY ILLUSTRATED. READY REFERENCE INDEX. 448 PAGES-HANDY SIZE,

GUETHS MECHANICAL DRAWING \$2.50

A CONCISE DRAWING COURSE, 192 pages, 50 plates, size 6 x 9.

A complete instructor and reference work on: Drawing tools and their use, drafting room and shop practice. laying out sheets and lettering, important rules for working drawings, three views and isometric simple models, joints and carpentry work, machine drawing, projections, sections, intersections, warped surfaces, method of plan of elevation, method of vanishing point, shades and shadows, points, lines and planes, prisms and syramids, spheres, screw surfaces, shadow perspective. How to use the slide rule,

52

ROGERS DRAWING AND DESIGN

MECHANICAL DRAWING SELF TAUGHT.

410 pages, 600 illustrations (many full page drawings), flat-opening.

A standard work, with all details so clearly explained that this valuable training is easily obtained without an instructor. Covers terms and definitions, how to use drawing board-instruments, T square, triangles, how to do lettering, shade and section lining, geometrical drawing, development of surfaces and isometric, cabinet and orthographic projections, working drawings, explains how to do tracing and make blue prints, how to read prints, machine design. How to use the slide rule. A STANDARD STUDY TEXT FOR DRAFTING ROOM AND SHOP.

AUDELS MILLWRIGHTS & MECHANICS GUIDE . . . \$5

PRACTICAL INFORMATION ON PLANT INSTALLATION, OPERATION & MAINTENANCE. 1248 pages, completely illustrated, 5 x 61/2 x 2, flexible covers, fully indexed. 1000 facts at your fingertips. For millwrights, mechanics, erecting maintenance men, riggers, shopmen, service men, foremen, inspectors, superintendents.

Section 1: Mechanical power transmission-2: millwrights and mechanics tools and their use-3: building and construction work-4: plant operation and maintenance-5: installation and maintenance of electrical machinery-6: practical calculation and technical data-how to read blue prints,

AUDELS PUMPS, HYDRAULICS COMPRESSORS 56

A COMPREHENSIVE GUIDE FOR ENGINEERS, OPERATORS, MECHANICS, STUDENTS, WITH QUESTIONS AND ANSWERS.

UDESTICING AND ANSWERS. 1248 Pages—Books in one—fully illustrated. Practical information covering: PUMPS: Centrifugal—Rotary—Reciprocating Pumps—Air and Vacuum Chambers—Power & Air Pumps —Jet Condensers—Surface Condensers—calculations. Cooling Ponds—Cooling Towers—Water Supply— Hydraulic Rams—Special Service Pumps—Automotive Fire Pumps—Dredges.

HYDRAULICS: Physics-Drives-Machine Tool Power-Accumulators-Elevators-Airplane Control-Automobile Brakes-Shock Absorbers-Presses-Turbines. AIR COMPRESSION: Compression-Work-Compressor Classification-Parts, Types-Inter and After

Coolers-Regulating Devices-Installation-Lubrication-Operation-Maintenance-Blowers-Superchargers -Pneumatic Hand Tools-A Ready Reference.

□ AUDELS MATHEMATICS & CALCULATIONS FOR MECHANICS

MATHEMATICS FOR HOME STUDY OR REFERENCE. 672 pages, 550 illustrations, pocket size. This work has been arranged as a progressive study, starting with the first principles of arithmetic and advancing step by step, through the various phases of mathematics, including the many necessary rules and calculations, for figuring mechanical and electrical engineering problems. Thousands of mathematical calculations and tables, fully indexed for quick use.

\$2

Practical mathematics from the beginning. How to figure correctly. New, easy, correct methods covering a complete review of practical arithmetic. Illu trated with examples. Includes mensuration-plane and solid geometry-trigonometry-algebra calculus electrical and mechanical shop calculation-practical testsreference tables and data. How to use the slide rule. A REAL HELP TO ALL MECHANICS.

AUDELS MACHINIST & TOOL MAKERS HANDY BOOK

COVERS MODERN MACHINE SHOP PRACTICE IN ALL BRANCHES, 5 PRACTICAL BOOKS IN ONE Tells how to set up and operate lathes, screw and milling machines, shapers, drill presses and all other machine tools.

1250 pages, fully illustrated, 5 x 612 x 2. Indexed. Easy to read and understand.

A complete instructor and reference book for every machinist, tool maker, engineer, machine operator, mechan-Ical draftsman, metal worker, mechanic and student, covering lathes, screw and milling machines, shapers, drill presses, etc.

A SHOP COMPANION THAT ANSWERS YOUR OUESTIONS.

AUDELS CARPENTERS & BUILDERS GUIDES

A PRACTICAL ILLUSTRATED TRADE ASSISTANT ON MODERN CONSTRUCTION FOR CARPEN-TERS, JOINERS, BUILDERS, MECHANICS AND ALL WOODWORKERS.

Explaining in practical, concise language and by illustrations, diagrams, charts, graphs and pictures, principles, advances, short cuts, based on modern practice. How to figure and calculate various jobs.

Vol. 1-Tools, steel square, saw filing, Joinery, furniture-431 pages.

Vol. 2-Builders mathematics, drawing plans, specifications, estimates-455 pages,

Vol. 3-House and roof framing, laying out, foundations-255 pages.

Vol. 4—Doors, windows, stair building, millwork, painting—448 pages. 4 VOL. 1600 PAGES, 3700 ILLUSTRATIONS. \$9.00, EACH VOLUME POCKET SIZE, SOLD SEPARATELY \$2.50 A VOL.

AUDELS PLUMBERS & STEAMFITTERS GUIDES

A PRACTICAL ILLUSTRATED TRADE ASSISTANT AND READY REFERENCE FOR MASTER PLUMBERS, JOURNEYMEN AND APPRENTICE STEAM FITTERS, GAS FITTERS AND HELPERS. SHEET METAL WORKERS AND DRAUGHTSMEN, MASTER BUILDERS AND ENGINEERS. Explaining in plain language and by clear illustrations, diagrams, charts, graphs and pictures the principles

of modern plumbing practice.

Vol. 1-Mathematics, physics, materials, tools, lead work-374 pages.

Vol. 2-Water supply, drainage, rough work, tests-496 pages.

Vol. 3-Pipe fitting, ventilation, gas, steam 400 pages.

Vol. 4—Sheet metal work, smithing, brazing, motors. 4 VOLS.—1670 PAGES. 3642 DIAGRAMS, \$9.00. EACH VOL. POCKET SIZE. SOLD SEPARATELY \$2.50 A VOL.

AUDELS MASONS & BUILDERS GUIDES

A PRACTICAL ILLUSTRATED TRADE ASSISTANT ON MODERN CONSTRUCTION FOR BRICK-LAYERS STONE MASONS CEMENT WORKERS—PLASTERERS AND TILE SETTERS.

Explaining in clear language and by well-done illustrations, diagrams, charts, graphs and pictures, principles, advances, short cuts, based on modern practice-including how to figure and calculate various jobs.

Vol. 1-Brick work, bricklaying, bonding, designs-266 pages.

Vol. 2-Brick foundations, arches, tile setting, estimating 245 pages.

Vol. 3 Concrete mixing, placing forms, reinforced stucco-259 pages.

Vol. 4-Plastering, stone masonry, steel construction, blue prints-344 pages.

4 VOLS .- 1100 PAGES-2067 ILLUSTRATIONS-COMPLETE SET, \$9.00. EACH VOL. (POCKET SIZE) \$2.50 A VOL.

AUDFLS HOUSE HEATING GUIDE

For Heating, Ventilating and Air Conditioning Engineers, Plumbers, Maintenance Men. Contractors, Building Superintendents and Mechanics seeking practical, authentic information on Heating, Ventilating, Air Conditioning, 966 Pages-910 Illustrations-57 Chapters explaining the working principles of all Modern House Heating, Ventilation and Air Conditioning systems. Fully illustrated and Indexed. This up-to-date book of reference gives answers to 1001 questions.

AUDELS ELECTRIC MOTOR GUIDE

Covers the construction, hook-ups, control, maintenance and trouble shooting of all types of motors including armature winding. Explains entire subject in every detail. A Handy Guide for Electricians and all Electrical Workers.

Over 1000 Pages of Information-31 Instructive, Interesting Chapters-617 Diagrams, hook-ups and drawings. All types of motors fully illustrated and indexed for ready reference.

AUDELS NEW RADIOMANS GUIDE

A KEY TO THE PRACTICAL UNDERSTANDING OF RADIO, FOR RADIO ENGINEERS, SERVICE-MEN, AMATEURS.

1088 pages. 400 illustrations and diagrams. Size 5 x 61/2.

Features: Radio fundamentals and Ohm's Law-physics of sound as related to radio science-electrical measuring instruments-power supply units-resistors, indicators and condensers-radio transformers and examples on their designs-broadcasting stations-principles of radio telephony-vacuum tubesradio receivers-radio circuit diagrams-receiver construction-radio control systems-loud speakersantenna systems-antenna systems (automobile)-phonograph pickups-public address systems-aircraft radio-marine radio equipment-the radio compass and principle of operation-radio beacons-automatic radio alarms-short wave radio-coil calculations-radio testing-cathode ray oscillographs-static elimination and radio trouble pointers-underwriter's standards-units and tables.

AUTHENTIC CLEAR CONCISE.



AUDELS TELEVISION SERVICE MANUAL

Gives practical information in Installing, Trouble-Shooting & Repairing, This greatly needed fact-finding manual is easy to understand, 480 pages, more than 225 illustrations & diagrams covering operating principles of modern television receivers.

Covers T.V. information at your finger ends. Shows good receiver adjustment and How to get Sharp, Clear Pictures. How to Install Aerials-Avoid Blurs, Smears and How to test. Explains color systems and methods of conversion, 1001 FACTS-18 CHAPTERS.

AUDELS HANDY BOOK OF PRACTICAL ELECTRICITY \$5

FOR MAINTENANCE ENGINEERS, ELECTRICIANS AND ALL ELECTRICAL WORKERS, 1052 pages, 1300 illustrations.

A guick, simplified, ready reference book, giving complete instruction and practical information on the rules and laws of electricity-maintenance of electrical machinery- A.C. and D.C. motors-wiring diagramshouse lighting-power wiring-meter and instrument connections-bells and signal wiring-motor wiring -transformer connections-fractional horsepower motors-circuit breakers-relay protection-switchgears nower stations-automatic substations.

THE KEY TO A PRACTICAL UNDERSTANDING OF ELECTRICITY.

AUDELS WIRING DIAGRAMS FOR

Electricians, wiremen, linemen, plant superintendents, construction engineers, electrical contractors and students will find these diagrams a valuable source of practical help.

This book gives the practical man the facts on wiring of electrical apparatus. It explains clearly in simple language how to wire apparatus for practically all fields of electricity. Each diagram is complete and self-explaining—304 pages, illustrated. A PRACTICAL, HANDY BOOK OF HOOK-UPS.

AUDELS ELECTRONIC DEVICES 57

TELLS WHAT YOU WANT TO KNOW ABOUT THE ELECTRIC EYE.

Covering photo-electric cells and their applications. Includes easily understood explanations of the workings of the electric eye, amplifiers, anodes, candlepower, color temperature, illumination, frequencies, photo tubes, grid basis, voltage, photo-electric tubes, photocell, vacuum tubes, the oscillator, electron tubes, electrons versus atoms, Ohm's Law, wiring diagrams. 304 pages.

A PRACTICAL BOOK ON ELECTRONICS.

AUDELS NEW ELECTRIC LIBRARY \$2.50 a vol.

FOR ENGINEERS, ELECTRICIANS, ALL ELECTRICAL WORKERS, MECHANICS AND STUDENTS. Presenting in simplest, concise form the fundamental principles, rules and applications of applied electricity, Fully illustrated with diagrams & sketches, also calculations & tables for ready reference. Helpful questions and answers. Trial tests for practice, study and review. Design, construction, operation and maintenance of modern electrical machines and appliances. Based on the best knowledge and experience of applied electricity.

- Vol. 1-Principles and rules of electricity, magnetism, armature winding, repairs-700 illustrations-480 pages.
- Vol. 2-Dynamos, D.C. motors, construction, installation, maintenance, trouble shooting-573 illustrations 418 nages.
- Vol. 3-Electrical testing instruments and tests, storage battery construction and repairs-631 illustrations -472 pages.
- Vol. 4-Alternating current principles and diagrams, power factor, alternators, transformers-801 illustrations-484 pages.
- Vol. 5-A.C. motors, windings, reconnecting, maintenance, converters, switches, fuses, circuit breakers-1489 illustrations—498 pages.
- Vol. 6-Relays, condensers, regulators, rectifiers, meters, switchboards, power station practice-689 illustrations-548 pages.
- Vol. 7-Wiring-house, light and power, circuits, high tension transmission, plans, calculations, code, marine wiring practice-1218 illustrations-728 pages.
- Vol. 8-Railways, signals, elevators, -1078 illustrations-
- Vol. 9-Radio, telephone, telegraph, television, motion pictures-793 illustrations-576 pages.
- Vol. 10-Refrigeration, illumination, welding, x-ray, modern electrical appliances, index-1084 illustrations -674 pages.

COMPLETE SET \$22.50

AUDELS ELECTRICAL POWER CALCULATIONS \$3

275 TYPICAL PROBLEMS FULLY WORKED OUT.

Gives and explains the mathematical formulae and the fundamental electrical laws for all the everyday, practical problems in electricity-Ohm's and Kirchhoff's laws for Direct Current-the generation and application of alternating current-problems in series and parallel circuits-transformers-transmission lineselectrical machinery. Valuable notes on Radio Circuit Calculation.

With 289 Diagrams, and Tables on Conversion, Wire Gauges and Capacities, etc. Other Data; Symbols, Formulae. 480 pages, fully diagrammed. Two parts (A.C.-D.C.). Indexed.

EVERY ELECTRICAL WORKER & STUDENT NEEDS THIS MODERN "MATHEMATICAL TOOL."

AUDELS NEW ELECTRIC DICTIONARY \$3

FOR EVERY WORKER WHO HAS TO DO WITH ELECTRICITY.

The language of your profession in convenient, alphabetical order so you can instantly locate any word, phrase or term. To be an expert in any line you must "talk the language." Audel's New Electric Dictionary enables you to understand and explain electrical problems so your hearer will thoroughly understand you. Defines more than 9000 words, terms and phrases in plain and unmistakable language, compiled with the

same accuracy and thoroughness that has characterized Audel books for 82 years.

Valuable as an Encyclopedia of Electricity and as a Dictionary. AN ABSOLUTE NECESSITY TO EVERY ELECTRICAL WORKER AND STUDENT.

AUDELS QUESTIONS & ANSWERS FOR **ELECTRICIANS EXAMINATIONS**

A PRACTICAL BOOK TO HELP YOU PREPARE FOR ALL GRADES OF ELECTRICIANS LICENSE EXAMINATIONS. A helpful Review of all the fundamental principles underlying each question and answer needed to prepare you to solve any new or similar problem, which while being asked differently still calls for the same answer and knowledge.

\$2 50

Covering the National Electrical Code, Questions and Answers for License Tests; Ohm's Law; with applied Examples; Hook-ups for Motors; Lighting and Instruments; 272 Pages. Fully Indexed and Illustrated. Pocket Size. A COMPLETE REVIEW FOR ALL ELECTRICAL WORKERS.



Check

You Can Look Over Any Guide In Your Own Home

Start the Easy Payments If Satisfied RECOMMENDED BY

MAIL HIS ODAY

MAIL ORDER THEO.AUDEL&CO., 49W.23 St., New York 10, N.Y.

Please mail me for 7 days' free examination the books marked (X) below. I agree to mail \$2 in 7 days on each book or set ordered, and to further mail \$2 a month on each book or set ordered until I have paid purchase price plus shipping charges. If I am not satisfied with Guides I will return them.

GAS ENGINE MANUAL 4. 4. 4. 4. 4. 01L BURNER GUIDE, 416 Pages 52.50. 4. GUIDE TO CREATIVE PHOTOGRAPHY, 416 Pages 3.95 CREFRIGERATION & Air Cunditioning, 1360 Pages. 6. 4. 4. 4. 4. 4. 4. 4. 4. 4. 4. 4. 4. 4.
OIL BURNER GUIDE, 416 Pages \$2.50 Water Supply & Sewage Disposal Guide, 436 Pages 4 GUIDE TO CREATIVE PHOTOGRAPHY, 116 Pages 3.95 REFRIGERATION & Air Cunditioning, 1360 Pages 6 AUTOMOBILE MECHANICS GUIDE, 1132 Pages 6 TRUCK & TRACTOR GUIDE, 1376 Pages 3 DIESEL ENGINE MANUAL, 640 Pages 3 WELDERS GUIDE, 608 Pages 3 BLUE PRINT READING, 448 Pages 3 MELDERS GUIDE, 608 Pages 3 MELDERS GUIDE, 608 Pages 3 DIESEL ENGINE MANUAL, 640 Pages 3 BLUE PRINT READING, 448 Pages 3 MECHANICAL DICTIONARY, 712 Pages 6.95 DO-IT YOURSELF ENCYCLOPEDIA, 2 Vols. 8.95 HOME APPLIANCE SERVICE GUIDE, 864 Pages 6 POWER PLANT ENGINEERS GUIDE, 1568 Pages 5 BHEET METAL PATTERN LAYOUTS, 1152 Pages 7.50 SHEET METAL DRAWING & DESIGN, 410 Pages 3 MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages 3 MILLWRIGHTS & MECHANICS GUIDES (4 Book Set) 3 MATHEMATICS & CALCULATIONS, 672 Pages 3 MACHANICAL DRAWING GUIDES (4 Book Set) 9 <td< td=""></td<>
Water Supply & Sewage Disposal Guide, 436 Pages 4 GUIDE TO CREATIVE PHOTOGRAPHY, 416 Pages 3.95 REFRIGERATION & AIR C.Jnditioning, 1360 Pages 6 AUTOMOBILE MECHANICS GUIDE, 1132 Pages 6 DIESEL ENGINE MANUAL, 640 Pages 3 WELDERS GUIDE, 608 Pages 3 BUESEL ENGINE MANUAL, 640 Pages 3 WELDERS GUIDE, 608 Pages 3 MECHANICAL DICTIONARY, 712 Pages 6.95 DO-IT YOURSELF ENCYCLOPEDIA, 2 Vols 8.95 BOO-IT YOURSELF ENCYCLOPEDIA, 2 Vols 8.95 BENGINEERS & FIREMANS EXAMS, 544 Pages 6 POWER PLANT ENGINEERS GUIDE, 1568 Pages 6 SHEET METAL PATTERN LAYOUTS, 1152 Pages 7.50 SHEET METAL DRAWING GUIDE, 192 Pages 2.50 MECHANICAL DRAWING GUIDE, 192 Pages 3 MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages 5 PUMPS, Hydraulics & Air Compressors, 1248 Pages 6 MATHEMATICS & CALCULATIONS, 672 Pages 3 MACHINISTS HANDY BOOK, 1250 Pages 6 MATHEMATICS & Steamlitters GuiDES (4 Book Set) 9 PLUMBERS & Steamlitters Guides (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book S
GUIDE TO ČREATIVĚ PHOTOGRAPHÝ, 416 Pages 3.95 GREFRIGERATION & Air Conditioning, 1360 Pages 6 AUTOMOBILE MECHANICS GUIDE, 1132 Pages 6 TRUCK & TRACTOR GUIDE, 1376 Pages
REFRIGERATION & Air Cunditioning, 1360 Pages 6 Cautomobile Mechanics Guide, 1132 Pages 6 TRUCK & TRACTOR GUIDE, 1376 Pages
AUTOMOBILE MECHANICS GUIDE, 1132 Pages
TRUCK & TRACTOR GUIDE, 1376 Pages
DIESEL ENGINE MANUAL, 640 Pages
WELDERS GUIDE, 608 Pages 3 BLUE PRINT READING, 448 Pages 3 MECHANICAL DICTIONARY, 712 Pages 6.95 DO-IT YOURSELF ENCYCLOPEDIA, 2 Vois. 8.95 HOME APPLIANCE SERVICE GUIDE, 864 Pages 6 POWER PLANT ENGINEERS GUIDE, 1568 Pages 6 SHEET METAL PATTERN LAYOUTS, 1152 Pages 7.50 SHEET METAL WORKERS HANDY BOOK, 448 Pages 2.50 MECHANICAL DRAWING GUIDE, 192 Pages 7.50 SHEET METAL WORKERS HANDY BOOK, 448 Pages 2.50 MECHANICAL DRAWING & DESIGN, 410 Pages 3 MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages 5 PUMPS, Hydraulics & Air Compressors, 1248 Pages 6 MATHEMATICS & CALCULATIONS, 672 Pages 6 CARPENTERS & BUILDERS GUIDES (4 Book Set) 9 PLUMBERS & Steamfitters Guides (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book Set) 9
BLUE PRINT READING, 448 Pages
Image: Construction of the system of the
DO-IT YOURSELF ENCYCLOPEDIA, 2 Vois
HOME APPLIANCE SERVICE GUIDE, 804 Pages 6 POWER PLANT ENGINEERS GUIDE, 1568 Pages 5 ENGINEERS & FIREMANS EXAMS, 544 Pages 2.50 SHEET METAL PATTERN LAYOUTS, 1152 Pages 2.50 SHEET METAL WORKERS HANDY BOOK, 448 Pages. 2.50 MECHANICAL DRAWING GUIDE, 192 Pages 2.50 MECHANICAL DRAWING & DESIGN, 410 Pages 3 MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages. 5 PUMPS, Hydraulics & Air Compressors, 1248 Pages. 6 MATHEMATICS & CALCULATIONS, 672 Pages
POWER PLANT ENGINEERS GUIDE, 1968 Pages ENGINEERS & FIREMANS EXAMS, 544 Pages
HIGHNERS & FIRLMANS EXAMS, 344 Pages
SHEET METAL PATTERN LAYOUTS, 1132 Pages
MECHANICAL DRAWING GUIDE, 192 Pages
Image: Chanical Drawing & Does 192 Pages 2.30 Image: Chanical Drawing & Design, 410 Pages 3 Image: Chanical Drawing & Design, 410 Pages 3 Image: Chanical Drawing & Design, 410 Pages 5 Image: Chanical Drawing & Design, 410 Pages 5 Image: Chanical Drawing & Design, 410 Pages 5 Image: Chanical Drawing & Design, 410 Pages 6 Image: Chanical Drawing & Calculations, 672 Pages 6 Image: Chanical Drawing & Dook, 1250 Pages 7 Image: Chanical Drawing & Dook, 1250 Pages 7 Image: Chanical Drawing & D
MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages. 5 MILLWRIGHTS & MECHANICS GUIDE, 1248 Pages. 5 MATHEMATICS & CALCULATIONS, 672 Pages
Implementation Imple
Imathematics & calculations, 672 Pages 3 Imathematics & calculations, 672 Pages 3 Imachinists Handy BOOK, 1250 Pages 6 Imachinists Handy BOOK, 1250 Pages 9
MACHINISTS HANDY BOOK, 1250 Pages
CARPENTERS & BUILDERS GUIDES (4 Book Set) 9 PLUMBERS & Steamlitters Guides (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book Set) 9 HOUSE HEATING GUIDE, 966 Pages
CONTRACTOR S & Steamfitters Guides (4 Book Set) 9 MASONS AND BUILDERS GUIDES (4 Book Set) 9 OHOUSE HEATING GUIDE, 966 Pages
MASONS AND BUILDERS GUIDES (4 Book Set) 9 HOUSE HEATING GUIDE, 966 Pages
HOUSE HEATING GUIDE, 966 Pages
TELECTRIC MOTOR GUIDE, 1056 Pages 5
DRADIOMANS GUIDE, 1088 Pages 5
TELEVISION SERVICE MANUAL, 480 Pages 3
THANDY BOOK OF ELECTRICITY, 1052 Pages 5
WIRING DIAGRAMS (Light & Power), 304 Pages 2.50
LIELECTRIC LIBRARY, 6000 Pages (10 Book Set) 22.50
ELECTRIC LIBRARY, 6000 Pages (10 Book Set) 22.50
LECTRIC LIBRARY, 6000 Pages (10 Book Set) 22.50 ELECTRIC POWER CALCULATIONS, 480 Pages 3 ELECTRIC DICTIONARY, 9000 Terms

