Rudolf F. Graf William Sheets

COMPLATIVE IMPER

Encyclopedia of ELECTRONIC CIRCUITS

Volume 6



Encyclopedia of

ELECTRONIC CIRCUITS

Volume 6

To Russell May you always be as self-confident as you are today.

Patent notice

Purchasers and other users of this book are advised that several projects described herein could be proprietary devices covered by letters patent owned or applied for. Their inclusion in this book does not, by implication or otherwise, grant any license under such patents or patent rights for commercial use. No one participating in the preparation or publication of this book assumes responsibility for any liability resulting from unlicensed use of information contained herein.

•

Encyclopedia of

ELECTRONIC CIRCUITS

Volume 6

Rudolf F. Graf & William Sheets

McGraw-Hill

New York San Francisco Washington, D.C. Auckland Bogotá Caracas Lisbon London Madrid Mexico City Milan Montreal New Delhi San Juan Singapore Sydney Tokyo Toronto

McGraw-Hill



A Division of The McGraw-Hill Companies

©1996 by **Rudolf F. Graf & William Sheets**. Published by The McGraw-Hill Companies, Inc.

Printed in the United States of America. All rights reserved. The publisher and the authors take no responsibility for the use of any of the materials or methods described in this book, nor for the products thereof.

pbk 1234567890FGR/FGR 9009876 hc 1234567890FGR/FGR 9009876

Product or brand names used in this book may be trade names or trademarks. Where we believe that there may be proprietary claims to such trade names or trademarks, the name has been used with an initial capital or it has been capitalized in the style used by the name claimant. Regardless of the capitalization used, all such names have been used in an editorial manner without any intent to convey endorsement of or other affiliation with the name claimant. Neither the author nor the publisher intends to express any judgment as to the validity or legal status of any such proprietary claims.

Library of Congress Cataloging-in-Publication Data (Revised for vol. 6)

Graf, Rudolf F.

The encyclopedia of electronics circuits

Authors for v. 6-: Ruldolf F. Graf & William Sheets. Includes bibliographical references and indexes. 1. Electronic circuits-Encyclopedias. I. Sheets, William. II. Title TK7867G66 .1985 621.3815 84-26772 ISBN 0-8306-0938-5 (v. 1) ISBN 0-8306-1938-0 (pbk.: v. 1) ISBN 0-8306-3138-0 (pbk. : v 2) ISBN 0-8306-3138-0 (v. 2) ISBN 0-8306-3348-0 (pbk. : v 3) ISBN 0-8306-7348-2 (v. 3) ISBN 0-8306-3895-4 (pbk, : v 4) ISBN 0-8306-3896-2 (v. 4) ISBN 0-07-011077-8 (pbk, : v 5) ISBN 0-07-011076-X (v. 5) ISBN 0-07-011275-4 (v. 6) ISBN 0-07-011276-2 (pbk. : v 6)

McGraw-Hill books are available at special quantity discounts to use as premiums and sales promotions, or for use in corporate training programs. For more information, please write to the Director of Special Sales, McGraw-Hill, 11 West 19th Street, New York, NY 10011. Or contact your local bookstore.

Acquisitions editor: Roland S. Phelps Editorial team: Lori Flaherty, Executive Editor Andrew Yoder, Book Editor Joann Woy, Indexer Production team: Katherine G. Brown, Director Rose McFarland, Desktop Operator Nancy Mickley, Proofreading Design team: Jaclyn J. Boone, Designer Katherine Lukaszewicz, Associate Designer 0112762

Contents

	Introduction	ix
1	AGC and ALC Circuits	1
2	Air-Flow Circuits	4
3	Alarm and Security Circuits	7
4	Amateur Circuits	17
5	Amateur Television (ATV) Circuits	33
6	Amplifier Circuits	46
7	A/D Converter Circuits	58
8	Antenna Circuits	61
9	Attenuator Circuits	68
10	Audio Signal Amplifier Circuits	71
11	Audio Power Amplifier Circuits	83
12	Automotive Circuits	94
13	Battery Charger Circuits	105
14	Battery Monitor Circuits	114
15	Bridge Circuits	121
16	Buffer Circuits	124
17	Clock Circuits	129

18	Computer-Related Circuits	132
19	Continuity Circuits	142
20	Converter Circuits	146
21	Crystal Oscillator Circuits	156
22	Current Source and Sink Circuits	161
23	dc/dc Converter Circuits	164
24	Decoder Circuits	168
25	Delay Circuits	172
26	Detector Circuits	174
27	Differential Amplifier Circuits	185
28	Display Circuits	188
29	Driver Circuits	196
30	Electronic Lock Circuits	203
31	Fiber-Optics Circuits	206
32	Filter Circuits	208
33	Flasher Circuits and Blinkers	223
34	Flip-Flop Circuits	228
35	Frequency-to-Voltage Converter Circuits	231
36	Function Generator Circuits	234
37	Game Circuits	244
38	Humidity Sensor Circuits	255
39	Indicator Circuits	258
40	Infrared Circuits	261
41	Instrumentation Amplifier Circuits	272
42	Integrator Circuits	278
43	Interface Circuits	280
44	Inverter Circuits	282
45	Ion Circuits	286
46	Laser Circuits	289
47	Light-Controlled Circuits	297

48	Logic Circuits	313
49	Mathematical Circuits	317
50	Measuring and Test Circuits	327
51	Metronome Circuits	364
52	Miscellaneous Treasures	367
53	Mixer Circuits	392
54	Model and Hobby Circuits	-394
55	Modulator Circuits	397
56	Morse-Code Circuits	404
57	Motor-Control Circuits	410
58	Multivibrator Circuits	417
59	Noise Circuits	420
60	Operational Amplifier Circuits	425
61	Oscillators (Audio)	432
62	Oscillators (Miscellaneous)	441
63	Oscillators (RF)	448
64	Oscilloscope Circuits	460
65	Photography-Related Circuits	465
66	Piezo Circuits	469
67	Power Line Circuits	471
68	Power Supply Circuits	476
69	Power Supply Circuits (High Voltage)	499
70	Power Supply Circuits (Multiple Output)	506
71	Power Supply Circuits (Variable Output)	514
72	Probe Circuits	520
73	Protection Circuits	525
74	Radar Detector Circuits	527
75	Radiation Detector Circuits	530
76	Receiving Circuits	534
77	Reference Circuits	559

78	Regulator Circuits	561
7 9	Relay Circuits	568
80	Sample-and-Hold Circuits	573
81	Sawtooth Generator Circuits	575
82	Scanner Circuits	578
83	Siren, Warbler and Wailer Circuits	581
84	Sound-Effects Circuits	585
85	Square-Wave Generator Circuits	<i>593</i>
86	Staircase Generator Circuits	595
87	Stepper Motor Circuits	600
88	Switching Circuits	603
89	Sync Circuits	615
90	Telephone-Related Circuits	619
91	Temperature-Related Circuits	629
92	Timer Circuits	648
93	Tone Control Circuits	651
94	Touch/Proximity Control Circuits	654
95	Tracer Circuits	658
96	Transmitter and Transceiver Circuits	660
97	Ultrasonic Circuits	666
98	Video Circuits	671
99	Voltage-Controlled Amplifier Circuits	684
100	Voltage-Controlled Oscillator Circuits	686
101	Voltage-Measuring Circuits	688
102	Waveform Generator Circuits	696
103	Waveguide Circuits	703
104	White-Noise Generator Circuits	705
	Sources	707
	Index	736
	About the Authors	789

•

Introduction

The enthusiastic reception of the first five volumes of *The Encyclopedia of Electronic Circuits* prompted the authors to produce this volume—the sixth in the popular series.

Taken together, the six volumes contain approximately 6000 circuits—by far the largest and broadest collection of practical electronic circuits available anywhere.

As in the other volumes, the 1000+ circuits presented here are arranged alphabetically, by category. All circuits in this volume, as well as those from the previous five volumes, are included in the index, which now has approximately 6000 entries.

We express sincere appreciation to the many electronic industry sources and publishers who graciously allowed us to utilize some of their materials. Their cooperation is gratefully acknowledged.

Once again, it gives us great pleasure to extend our sincerest thanks to Loretta Gonsalves-Battiste, a fine lady whose skill at the computer and willingness to work long and hard made on-time delivery of the manuscript for this book possible.

> Rudolf F. Graf & William Sheets September 1995


1

AGC and ALC Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

AGC Audio Preamp 3-MHz Low-Noise AGC System IF AGC Network Audio Leveler

AGC AUDIO PREAMP

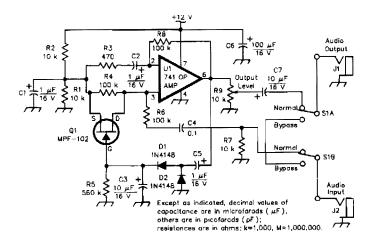


QST

Fig. 1-1

The circuit uses an easily obtained 741 op amp set for an internal gain of about 200. A portion of the op amp's output signal is rectified by the 1N4148 diodes, then filtered and fed to the gate of the FET input shunting circuit. As the output rises, more and more input shunting takes place. That is, more of the input signal is bypassed, effectively keeping the output level constant.

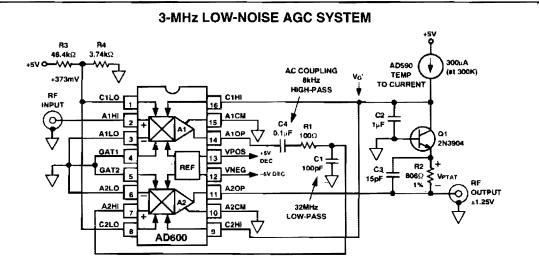The circuit offers a 100:1 limiting action. The input level can change over a 100:1 ratio with little or no effect on the output level. The output level itself can be set from less than unity all the way up to nearly the gain of the amplifier, making the circuit usable in other applications as well.




ANALOG DIALOG

Fig. 1-2

The AD600 dual voltage-controlled amplifier in this circuit provides a 3-MHz AGC system with 80-dB range.


IF AGC NETWORK

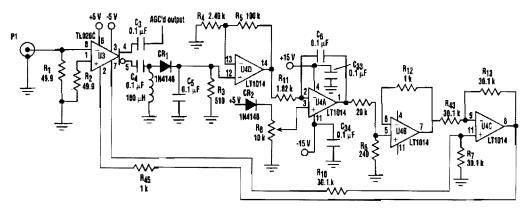

ELECTRONIC DESIGN

Fig. 1-3

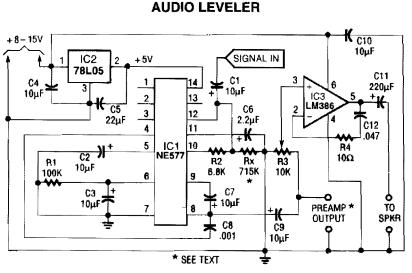A simple IF AGC circuit that features wide dynamic range and excellent linearity can be achieved with two chips: TI's TL026C voltage-controlled amplifier IC and Linear Technology's LT1014 (or any other similar basic quad op amp).



1994 EXPERIMENTERS HANDBOOK

Fig. 1-4

A low power programmable compandor chip, the Signetics NE577 IC is used. Incoming audio is compressed, rectified and conditioned so that the input signal level always remains about the noise level. The compressor is an ALC circuit that outputs a constant level and the expander part of the IC is not used.


2

Air-Flow Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Hot-Wire Anemometer Electronic Anemometer Air Flow Detector

HOT-WIRE ANEMOMETER

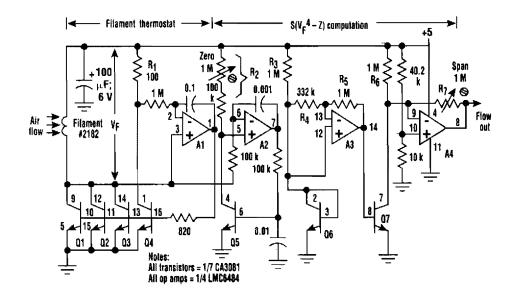


ELECTRONIC DESIGN

Fig. 2-1

An anemometer can be realized by utilizing the inherent transconductance match of transistors in the array, instead of passive series resistances, to control filament current. As a result, as A1 serves the collector current of Q4 and thereby the voltage across R1, it simultaneously adjusts the filament (a 2182-type incandescent lamp denuded of its glass envelope) voltage, $V_{\rm f}$. The ratio of the filament to R1 current is stably maintained by the identical temperature and operating points of Q1 through Q4. The net result is that A1 drives the filament temperature to the value that causes filament resistance to equal $R1/3 = 33 \Omega$. This is about double the cold resistance of the filament and therefore, assuming tungsten wire with a 0.0045/degree coefficient of resistance, represents a filament operating temperature of around 230°C. This is hot enough that moderate changes in ambient temperature are unimportant factors in filament power demand, but not so hot as to cause the filament to burn.

Rail-to-rail input amplifier A2 continuously serves the collector current of Q5 to $V_{\rm f}/R_2$, making the $V_{\rm bc}$ of LQ5 a logarithmic function of $V_{\rm f}$. A3 multiplies this log by 4 and applies the product of Q7. Q7 does the antilog function so that its collector current is proportional to the fourth power of $V_{\rm f}$. Thus, by King's law, it's proportional to air speed in the vicinity of the filament. This current is offset and scaled by A4 to produce a voltage output that, thanks to the rail-to-rail output capability of the LMC6484, can range from 0.01 to 4.99 V. Full-scale air speed can be adjusted, using R7, to any value in the range of 1 to 10 meters/s.


ELECTRONIC ANEMOMETER

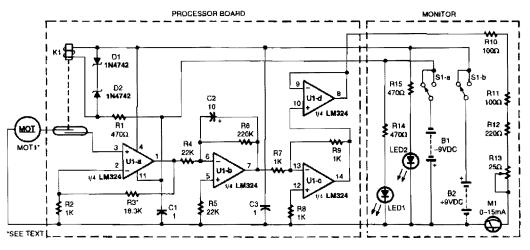

POPULAR ELECTRONICS

Fig. 2-2

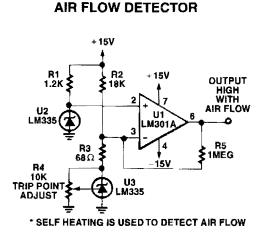A motor used as a generator is used as a transducer to generate a dc voltage that is proportional to wind speed. K1 prevents the transducer voltages from being applied to the circuit if no dc power is present. U1A through U1D is a dc amplifier, integrator, and buffer. This circuit drives the meter M1. The processor board is mounted in a housing along with the generator M1.



POPULAR ELECTRONICS

Fig. 2-3

The self heating of a semiconductor that is cooled by airflow is used as a sensing method.


3

Alarm and Security Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

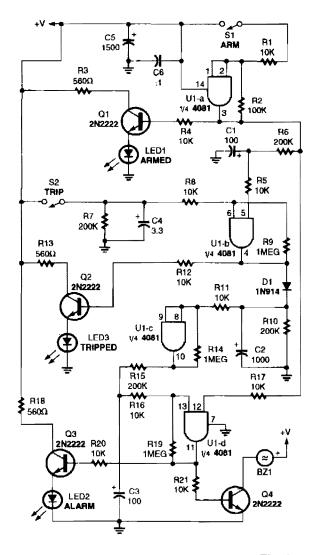Burglar Alarm Circuit Auto Security System Transmitter Home Security System Auto Security System Receiver Flashing Brake Light for Motorcycles Car Alarm Decoy Motorcycle Alarm Simple Bike Horn Door Ajar Indicator Motorcycle Burglar Alarm Horn Circuit for Motorcycle Use





POPULAR ELECTRONICS

Fig. 3-1

This alarm circuit is built around a single 4081 (CMOS) quad AND gate. It offers an exit and entry delay (around automatically reset two minutes after tripping, provided that the trip input is not left high).


The arming switch must go high to arm or low to disarm. After arming, U1-a begins to charge C1 via R6. Around 20 seconds later (after the exit delay), C1 has a sufficient charge to produce a high at the pin-5 input of U1-b. Also, when the circuit is armed, Q1 is turned on to indicate arming, and one input of U1-d is brought high.

After the exit delay times out, if the trip input opens, it causes an output on gate U1-b. Transistor Q1 is turned on, lighting the trip indicator (LED3), C2 instantly charges, and the output of U1-c goes high. At that point, C3 begins charging to provide the entry delay.

After 20 seconds, C3 has sufficient charge to produce a high at pin 13 of U1-d. That forces U1-d's output high, tuning Q3 and Q4 on, which activates the alarm indicator (LED2) and sounder (BZ1), respectively. If disarmed after a trip pulse, but before the 20-second, entry delay time out, pin 12 of U1-d goes low, so the gate's output does not go high and the alarm does not sound.

Components C2 and R10 hold U1-c on for around 2 minutes and 20 seconds to provide the two-minute alarm. After C2's charge drops below half of the supply voltage, U1-c's output goes low, awaiting another trip pulse to set it off again.

AUTO SECURITY SYSTEM TRANSMITTER

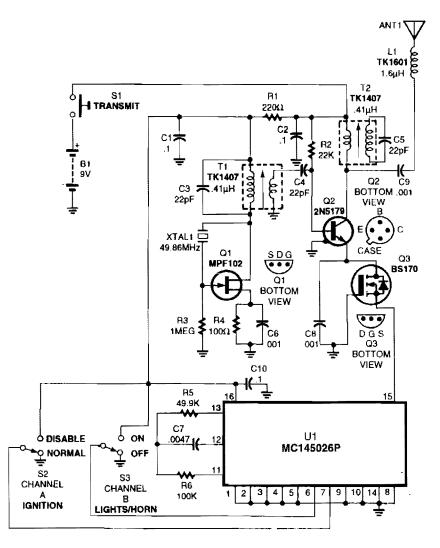


POPULAR ELECTRONICS

Fig. 3-2


This transmitter operates at 49 MHz and uses an M145026 programmable digital encoder to generate a unique digital code, depending on the positions of S2 and S3, to control ignition and lights or horn. Q1 is the oscillator, Q2 the power amplifier. The antenna is a 36-inch whip or wire antenna.

HOME SECURITY SYSTEM

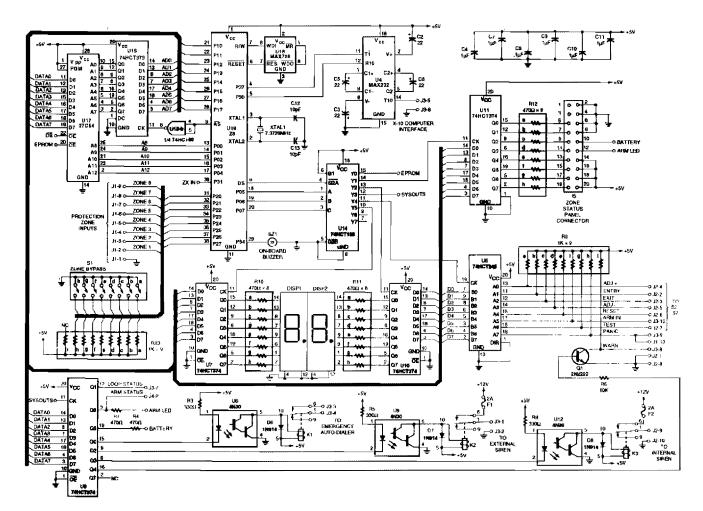

.

10

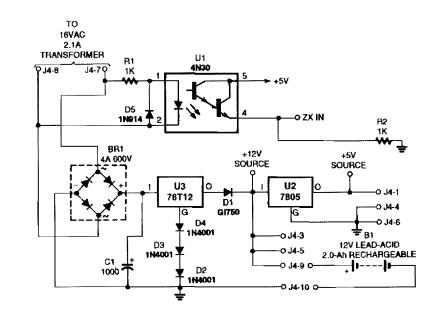


POPULAR ELECTRONICS

Fig. 3-3

At the heart of the main-control unit is U16, Zilog's Z8-8-bit microcontroller, which receives its program instruction from U17, a 27C64 8K x 8 EPROM. The home security system in its most basic form, features eight individual protection zones, adjustable entry and exit delays, a panic switch (for emergency situations), automatic system reset, support for an auto-dialer (which, in case of emergency, dials pre-programmed telephone numbers), it's X-10 compatible (allowing it to control house lights and appliances), has a backup battery (to keep the system on-line during a power failure), and there is also an optional zone-status panel that is used to individually show the condition of each protection zone.

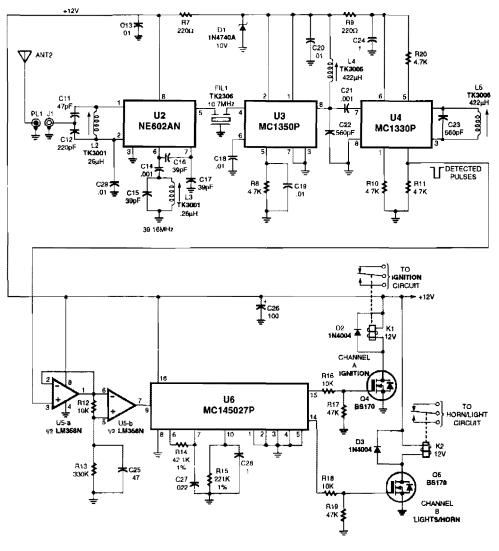This system's power supply provides 12 Vdc for the sirens and digital keypad, and 5 Vdc for the on-board electronics, while also providing a constant 12-V output that's used to charge the backup-battery.




AUTO SECURITY SYSTEM RECEIVER

POPULAR ELECTRONICS

Fig. 3-4

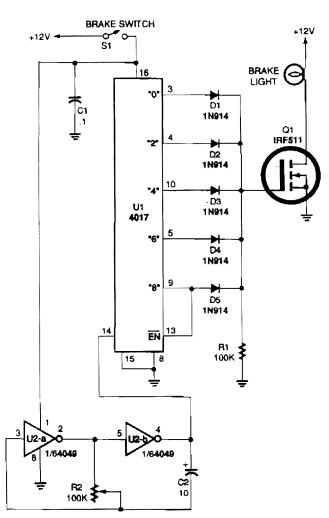This receiver is a superheterodyne type tuned to 49 MHz. U2 is a mixer, followed by a 10.7-MHz filter and two-stage IF (U3, U4) and detector. The encoded received RF pulse signal from the antenna produces detected pulse from the MC1330P. These pulses are amplified by U5 and fed to decoder IC U6, and MC1450278. Two channels are available at the-output, which drives K1 and K2.




FLASHING BRAKE LIGHT FOR MOTORCYCLES

POPULAR ELECTRONICS

Fig. 3-5

When brake-light switch S1 is closed, power is applied to U1 and U2. Two inverters of U2, a 4049 hex inverting buffer, are connected in a low-frequency oscillator circuit that feeds clock pulses into U1, a 4017 decade counter/divider. Outputs 0, 2, 4, 6, and 8 of U1 are coupled to the gate of Q1 through a 1N914 diode. As the 4017 counts down, it turns the brake light on and off four times and then leaves it on until the brake switch is released. The on/off rate can be set by potentiometer R2; for best results, the on/off rate should be set so that it is rapid.


CAR ALARM DECOY

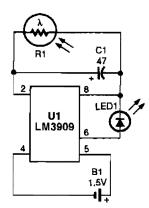

The device will simulate the presence of a burglar alarm in automobiles or homes. Mount R1 where daylight can fall on it. During darkness, LED1 flashes, making potential intruders think an alarm system is installed.

POPULAR ELECTRONICS

Fig. 3-6

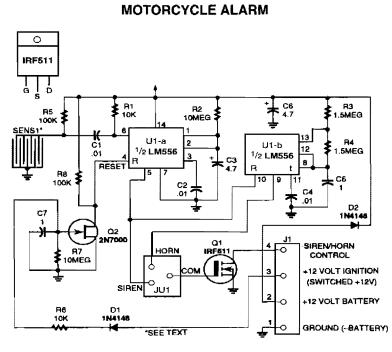


POPULAR ELECTRONICS

Fig. 3-7

A dual timer is used to generate a long pulse, which gates a second timer, producing a square wave (nonsymmetrical) and controls the on/off time of the horn. Siren operation can be selected with a jumper. In this case, the output of Q1 will be continuously on and not cycled. Sensor S1 is a row of adjacent circuit board traces with a stainless steel ball bearing laying on them. Any movement causes momentary shorting and opening of the circuit, triggering U1-a.

SIMPLE BIKE HORN

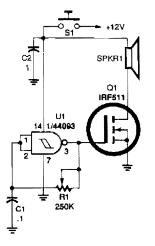


The horn circuit uses only one gate of a 4093 quad 2-input NAND Schmitt trigger, U1, connected in a simple, low-frequency, square-wave oscillator circuit. The oscillator's output, at pin 3, drives the gate of Q1. The drain of that FET drives a small horn speaker.

Potentiometer R1 can be adjusted to set the horn's output frequency. Some horn speakers are frequency sensitive, so play with the oscillator's frequency control for the best or loudest sound.



Fig. 3-8

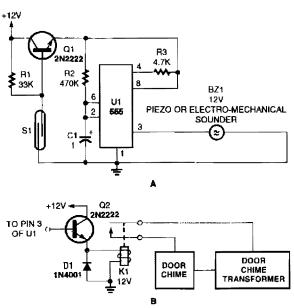


POPULAR ELECTRONICS

Fig. 3-9

This simple sounder (A) makes a good door annunciator. If the buzzer is replaced with the circuit in B, the annunciator can be made more pleasant to the ear.

DOOR AJAR INDICATOR

MOTORCYCLE BURGLAR ALARM

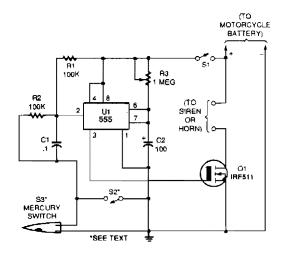


A 555 IC is connected in a one-shot timer circuit that turns on a FET transistor and either a siren or the bike's horn for a preset time period. Switch S1 is used as an on/off switch.

Closing either of two switches, S2 and S3, will trigger the IC. When either switch closes, pin 2 of U1 goes low. That triggers the IC to produce a positive output at pin 3 and sounds the alarm for the time period set by R3. The mercury switch, S3, is the switch that activates the alarm should anyone move your bike. Switch S2 can be used as a panic switch.

POPULAR ELECTRONICS

Fig. 3-10

HORN CIRCUIT FOR MOTORCYCLE USE

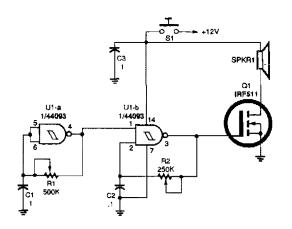

Gates U1-a and U1-b of the 4093 quad 2input NAND Schnitt trigger are connected in variable, low-frequency, square-wave oscillator circuits. The output of gate U1-a is connected to one of the inputs of gate U1-b. The square-wave output of gate U1-a modulates oscillator U1-b, producing a two-tone output. A really interesting sound can be produced by carefully adjusting potentiometers R1 and R2.

POPULAR ELECTRONICS




4

Amateur Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

1.2-kW 144-MHz Amplifier Power Supply 1.2-kW 144-MHz Amplifier Control Circuitry 1.2-kW 144-MHz Linear Amplifier Four-Stage 75-Meter SSB Superhet Receiver Improved CW Transmitter Keying Circuit **One-Chip AFSK Generator** Programmable CW Identifier Audible SWR Detector Adapter Audio Breakout Box One-Watt CW Transmitter PTT Control from Receiver Audio Transceiver Memory Backup 80-Meter SSB Receiver CW Audio Filter RF Line Sampler/Coupler Battery Pack and Reverse Polarity Protection Simple Identifier Transmit Keyer Interface Circuits Mobile Radio On-Alarm Timer


1.2-kW 144-MHz AMPLIFIER POWER SUPPLY

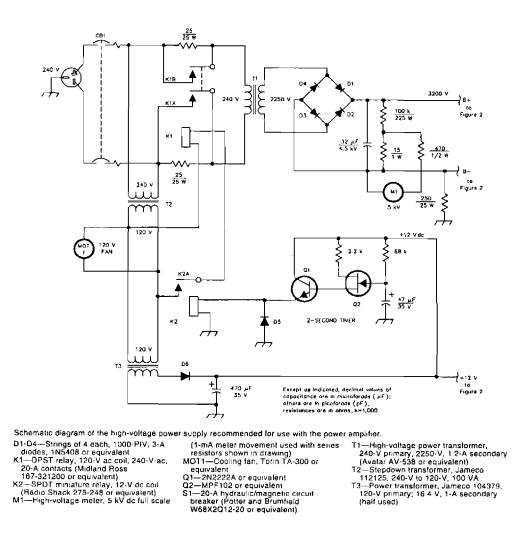

QST

Fig. 4-1

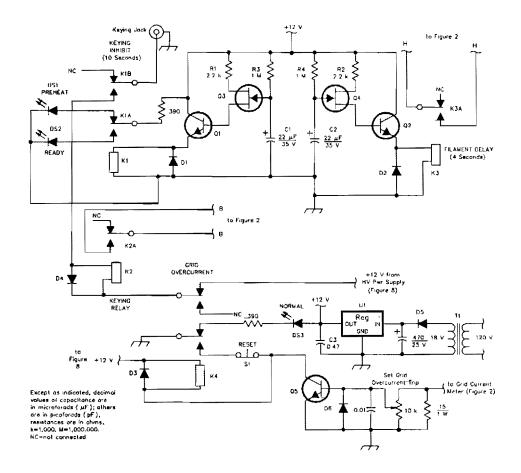A schematic diagram of the high-voltage power supply recommended for use with the power transformer. This power supply can also be used for other equipment with similar requirements. CAUTION: hazardous high voltages.




1.2-kW 144-MHz AMPLIFIER CONTROL CIRCUITRY

QST


Flg. 4-2

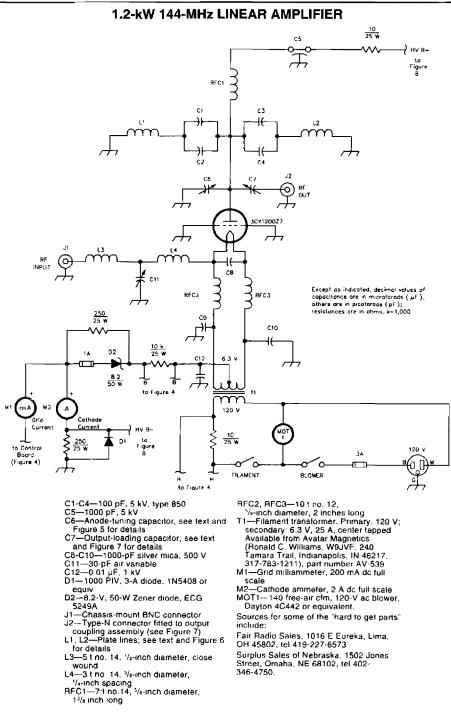Schematic diagram of the amplifier-control circuits.



Schematic diagram of the 2-meter amplifier.

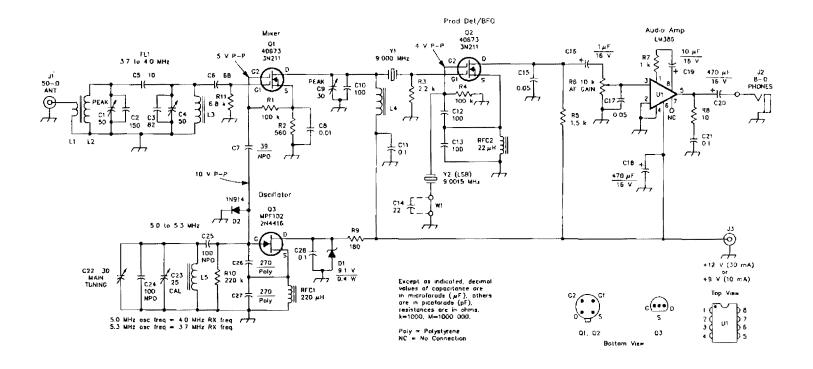FOUR-STAGE 75-METER SSB SUPERHET RECEIVER




OST

Fig. 4-4

A simple superhet receiver for SSB reception in the 75-meter amateur band is shown. Y1 acts as a crystal filter.

IMPROVED CW TRANSMITTER KEYING CIRCUIT

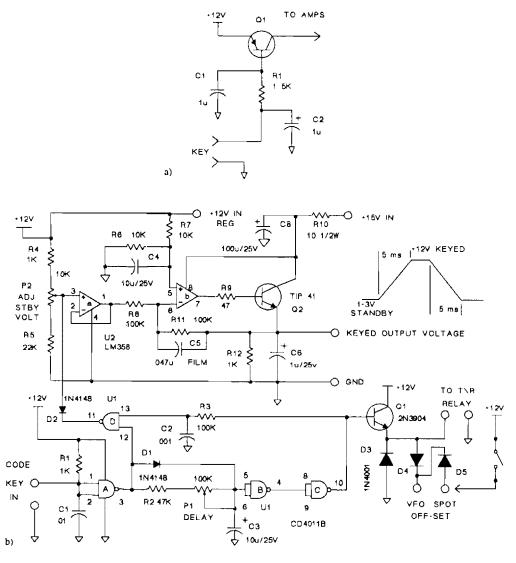

73 AMATEUR RADIO TODAY

Flg. 4-5

Typical (A) QRP keying circuit; (B) Improved QRP keying circuit with CMOS T/R keying control. Op amp U2b is a basic inverting amplifier with a gain of one. The capacitor C5 across the feedback resistor R11 makes it an integrator. The RC time constant of R11 and C5 determine the ramp time. The values shown will produce a 5-ms ramp. Use a good-quality capacitor for C5, such as a mylar or polypropylene type. A power transistor is placed inside the feedback loop so that the circuit can supply several hundred milliamperes of current. Control P2 sets the stand-by output voltage as seen at


IMPROVED CW TRANSMITTER KEYING CIRCUIT (Cont.)

the emitter of Q1. U2a buffers the voltage from P2. This isolates the pot from the input of the integrator. With the key up, adjust the pot until you just start to see an output from your transmitter, then back it off a little. Typically, this will be between 2 and 4 V. Your output signal will now have the proper 5-ms leading and falling edges and there will be no delay between key closure and the start of the output signal.

You must supply the op amp and collector of Q2 with at least 15 V to produce a full 12-V output on the emitter.

Parts list			
R1, R4, R12	1 kΩ ¼ W	C1	0.01 μF disk
R2	47 kΩ ¼ W	C2	0.001 µF disk
R3, R8, R11	100 k Ω	C3, C4	10 µF, 25 V electrolytic
R6, R7	22 kΩ	C5	$0.047 \mu F$ poly-film type
R9	47Ω	C6	1 µF, 25 V electrolytic
R10	10 Ω	$\mathbf{C7}$	Skipped
$\mathbf{P1}$	100 k Ω or 500 k Ω trimpot	C8	100 μF, 26 V electrolytic
P2	$10 \text{ k} \Omega$ trimpot	D1, D2	1N4148 diode
		D3, D4, D5	1N4001 1-A diode
$\mathbf{Q1}$	2N3904 NPN		
$\mathbf{Q}2$	Tip 41-to-220 NPN		
U1	4011B CMOS NAND gates		
U2	LM358 dual op amp		


ONE-CHIP AFSK GENERATOR

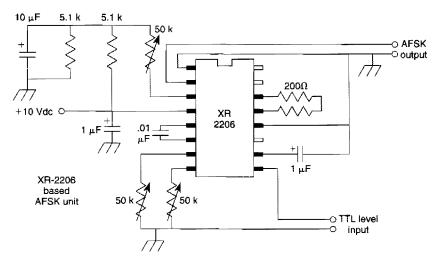

73 AMATEUR RADIO TODAY

Fig. 4-6

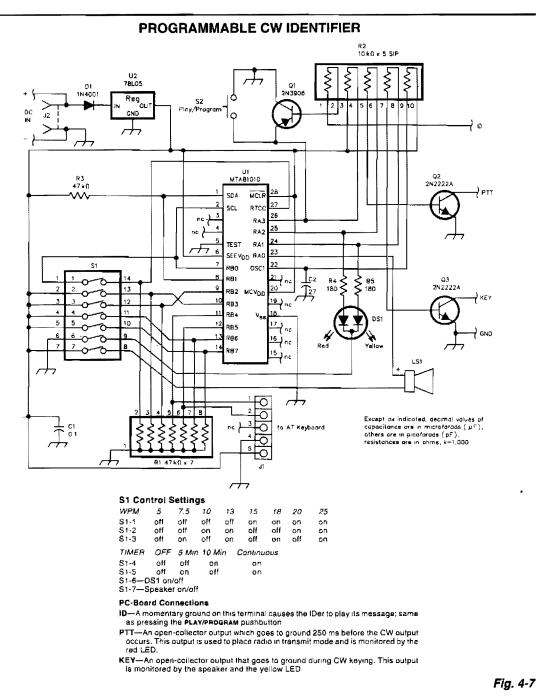Built around an XR2206 IC, this circuit will generate AFSK signals in the 1000- to 3000-Hz range.



QST

The identifier uses an MTA81010 microchip, containing a 1024-bit serial EEPROM and a microcontroller. It runs from a 9-V battery. A standard AT-type keyboard is used to program the desired message. Speed varies from 5 to 25 wpm.

AUDIBLE SWR DETECTOR ADAPTER


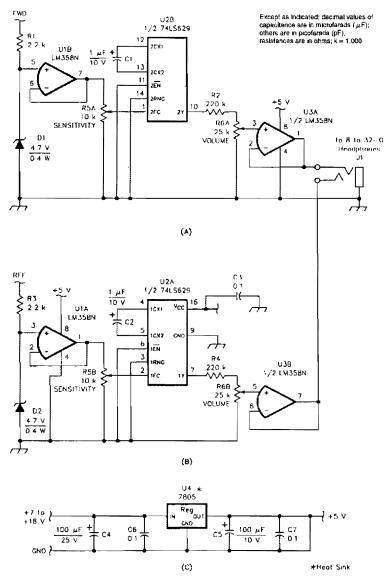


Fig. 4-8

ast

This SWR detector audio adapter is designed specifically for blind or vision-impaired amateurs, but anyone can use it. Instead of using a meter (or meters) to indicate antenna system forward and reflected voltages, this adapter generates two tones with frequencies that are proportional to the respective voltages. The tones are fed to a pair of stereo headphones (the miniature types are ideal) so that one ear hears the forward-voltage tone and the other ear hears the reflected-voltage tone. Thus, tuning up a transmitter is simply a matter of tuning for the highest-pitched tone in the left ear and the lowest-pitched tone in the right ear.

AUDIO BREAKOUT BOX

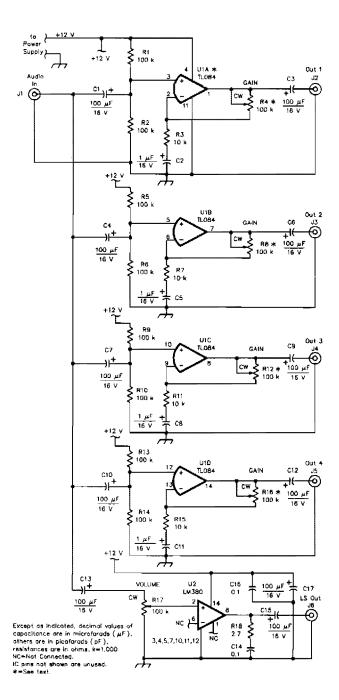


Flg. 4-9

.

AUDIO BREAKOUT BOX (Cont.)

In many radio shacks, one receiver audio-output line feeds a multitude of add-ons, such as one or more TNXs, SSTV modems, PC plug-in boards, and, perhaps, speakers. Having to manually plug the audio source from one accessory to another is inconvenient, if not frustrating as well. Overload-ing the sources by connecting the loads in parallel isn't satisfactory, either.

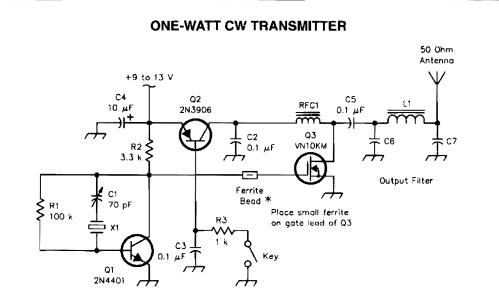The audio breakout box takes the audio output from a receiver (or other audio source) and applies it to the inputs of four identical, independent, low-level AF buffer/amplifiers and one high-level (1-W output) AF channel. Each low-level output channel can provide up to 20 dB of gain that's independently adjustable.



OST


C6,C7

820 pF disc ceramic (160 meters) 470 pF disc ceramic (80 meters) 220 pF disc ceramic (40 meters) 150 pF disc ceramic (30 meters) 100 pF disc ceramic (20 meters) 82 pF disc ceramic (17 meters)

L1

33 turns, #30, T37-2 (160 meters) 23 turns, #30, T37-2 (80 meters) 17 turns, #26, T37-2 (40 meters) 14 turns, #26, T37-2 (30 meters) 12 turns, #26, T37-2 (20 meters) 10 turns, #26, T37-2 (17 meters) Fig. 4-10


PTT CONTROL FROM RECEIVER AUDIO

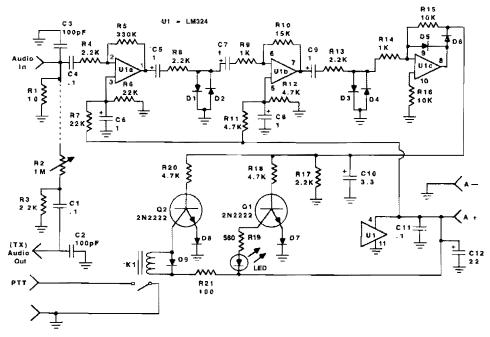

73 AMATEUR RADIO TODAY


Fig. 4-11

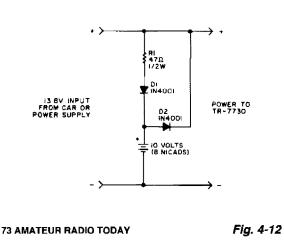This system will key a transmitter or other device that can be keyed by a relay closure. Audio is amplified, limited, and is rectified and drives relay driver Q2 and LED indicator. The transmitter audio output was used to feed a keyed transmitter and can be deleted or ignored where this feature is unnecessary.



TRANSCEIVER MEMORY BACKUP


Although designed for a Kenwood TR7730, this idea might be adapted to other transceivers. This circuit will retain the frequencies in memory while moving the rig from car to house and vice versa. When connected to an external power source, battery B1 is charged through R1 and D1. D1 prevents B1 from discharging when connected to an external supply that is turned off. When external power is removed, D2 provides a current path to the TR-7730 to retain the memory's contents. However, the TR-7730 power switch should be turned off before external power is removed because B1 will not provide power for normal operation.

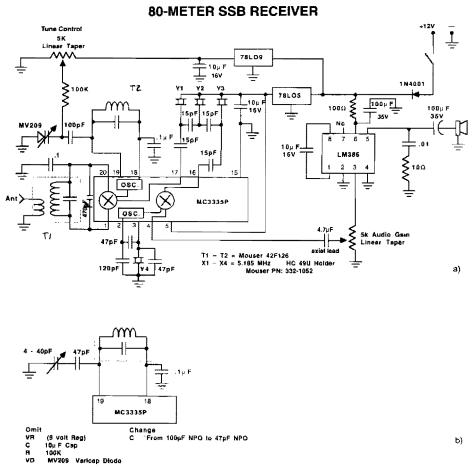

73 AMATEUR RADIO TODAY


Fig. 4-13

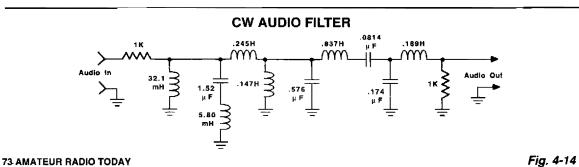This circuit uses an MC3335P IF chip and features a 3-pole crystal filter made from microprocessor crystals. Tuning is done either with a varactor diode or air-variable capacitor, as shown. Values are for 80 meters.



A high-performance passive filter. The center frequency is 700 Hz; -3-dB bandwidth is 200 Hz.

RF LINE SAMPLER/COUPLER

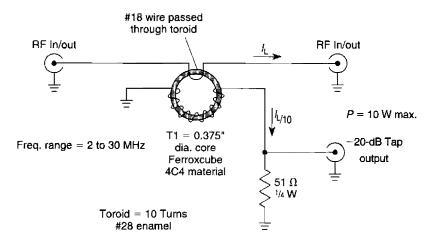

WILLIAM SHEETS

Fig. 4-15

Suitable for RF line sampling, this coupler is useful where an indirect measurement of line current is needed. A 10:1 turn ratio yields a secondary current about $\frac{1}{20}$ (ideally) of the line current. A 51- Ω resistor terminates the secondary. Insertion loss in the main line is negligible, < 0.1 dB. For higher power levels, use proportionately larger core for T1.

BATTERY PACK AND REVERSE POLARITY PROTECTION

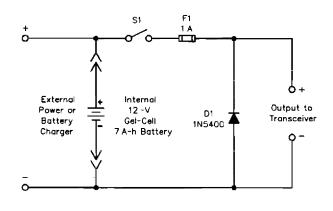


Fig. 4-16

OST

Schematic diagram and parts list for the reverse-polarity protection circuit (optional).

- D1 1N5400 silicon diode
- F1 1-A fast-acting fuse
- S1 SPST rocker switch

SIMPLE IDENTIFIER


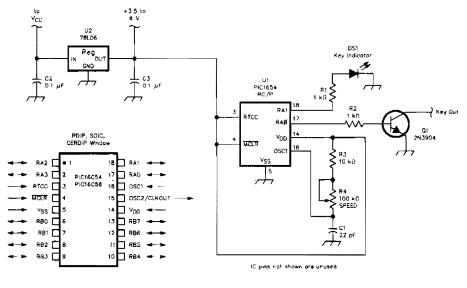


Fig. 4-17

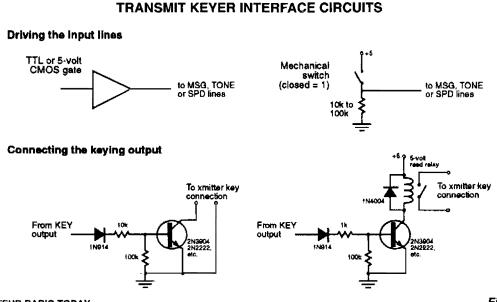This identifier uses a PIC 16C54 microcontroller which must be programmed for your desired identifier.




73 AMATEUR RADIO TODAY

QST

Fig. 4-18

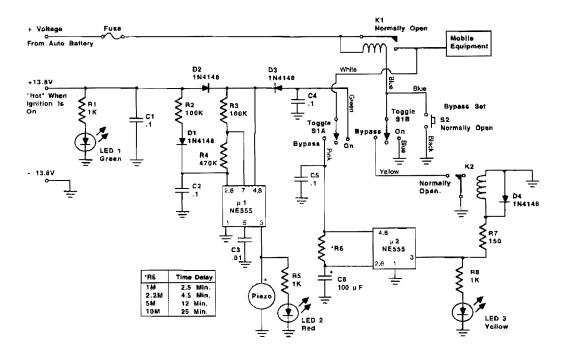These circuits are for use with Morse keyers and identifiers. They can be used to interface various devices with the identifier circuitry.



MOBILE RADIO ON-ALARM TIMER

73 AMATEUR RADIO TODAY

Fig. 4-19


This system will prevent you from accidentally leaving your mobile radio on, draining the battery. LED1 will light when the vehicle's ignition is on, or while the car is running. Switch S1 in the ON position will close relay K1, completing the power circuit to the equipment. If the ignition switch is shut off, and switch S1 is still in the ON position, an alarm (piezo) will begin to beep and LED2 will flash. Returning S1 to the center position will shut everything off. If equipment operation is desired after shutting off the vehicle, you can place switch S1 in the AUTO position and momentarily press S2, a normally open push-button switch. Depressing this switch begins a timing cycle. The length of time that the Mobile-ON alarm/timer operates before shutting everything off can be "programmed" by selecting R6. The approximate time delays are provided in the chart with the schematic. Or, you could change the value of C6. These components control the holding time of relay K1. LED3 will light while the circuit is in AUTO status. Incidentally, you can also cancel the time delay at any time during the delay period by simply switching it off.

5

Amateur Television (ATV) Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

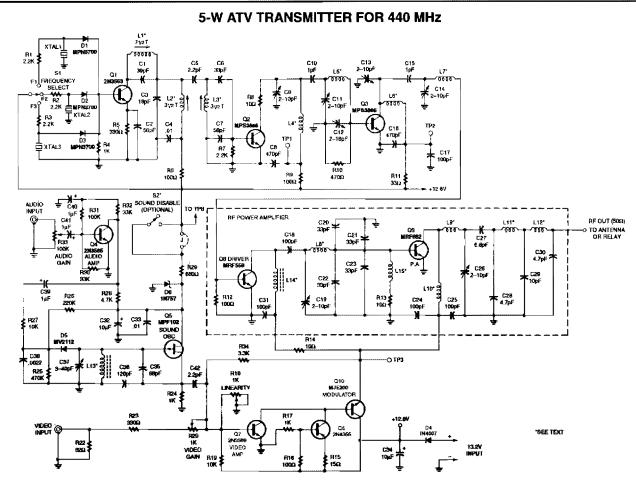5-W ATV Transmitter for 440 MHz 5-W ATV Transceiver Mini ATV Transmitter Dummy Load and Video Detector for Transmitter Tests Mast-Mounted ATV Preamp Three-Channel 902- to 928-MHz ATV Transmitter ATV Downconverter for 902 to 928 MHz Three-Channel 420- to 450-MHz ATV Transmitter ATV Downconverter for 420 to 450 MHz




ELECTRONICS NOW

Fig. 5-1

The circuit will produce typically 6 W RF output on synch tips. A crystal oscillator drives a doubler to produce a 220-MHz output. Another doubler produces 440 MHz to drive the power amplifier. A high-level series modulator provides the video modulation capability. A sound subcarrier is generated using a VCO circuit and combined with the video information. A complete kit of parts, including the PC board, is available from North Country Radio, P.O.Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.

5-W ATV TRANSCEIVER

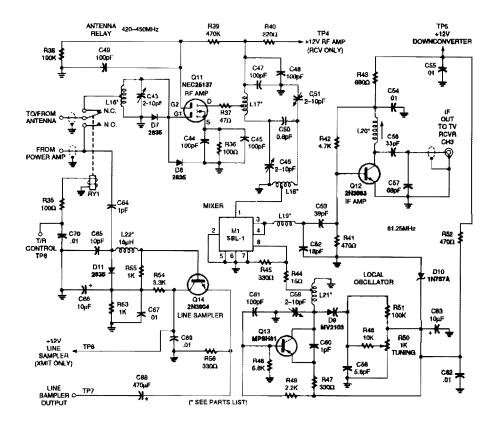


ELECTRONICS NOW

Flg. 5-2

For the transmitter schematic (part of this transceiver), see entry entitled "5-W ATV Transmitter for 440 MHz, Fig. 5-1." The downconverter portion is shown here.

This transmitter contains both a video and sound section. Five to six watts PEP on synch tips of NTSC video are produced. Three channels are available. Channel switching is via PIN diodes. Power supply voltage is 12 to 14 Vdc. The receiver function is provided with a downconverter circuit and is tunable. A relay is used for T-R switching. A complete kit of parts, including PC board, is available from North Country Radio, P.O.Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.



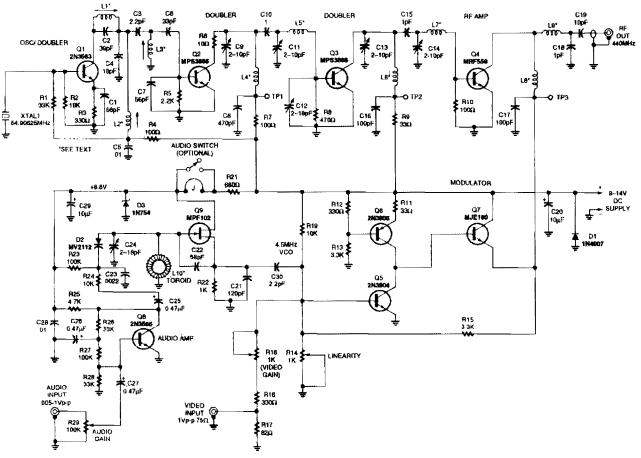


ELECTRONICS NOW

Fig. 5-3

This low-power NTSC video and sound transmitter is useful for amateur radio, video handie-talkie, R/C and surveillance purposes. A crystal oscillator-multiplier RF power amplifier. Video modulation is via a three-transistor series modulator. The sound subcarrier is generated with a VCO circuit and is combined with the video information. The output is 0.4 to 1.2 W with supply voltages of 9 to 14 volts. A complete kit of parts, including PC board, is available from North Country Radio, P.O. Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.

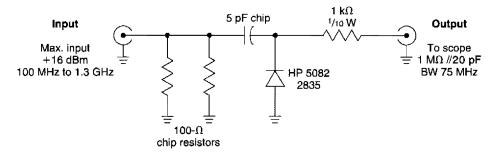DUMMY LOAD AND VIDEO DETECTOR FOR TRANSMITTER TESTS




WILLIAM SHEETS

Fig. 5-4

This circuit is useful as a video modulation monitor for testing low-power video transmitters. For higher power inputs, use a suitable attenuator between the detector and the source. The detector should be connected to scope with as short a cable as possible to preserve video bandwidth.


MAST-MOUNTED ATV PREAMP

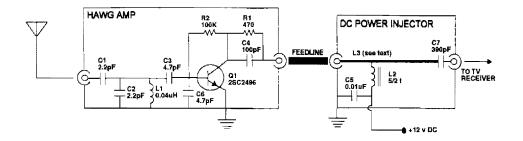

73 AMATEUR RADIO TODAY

Fig. 5-5

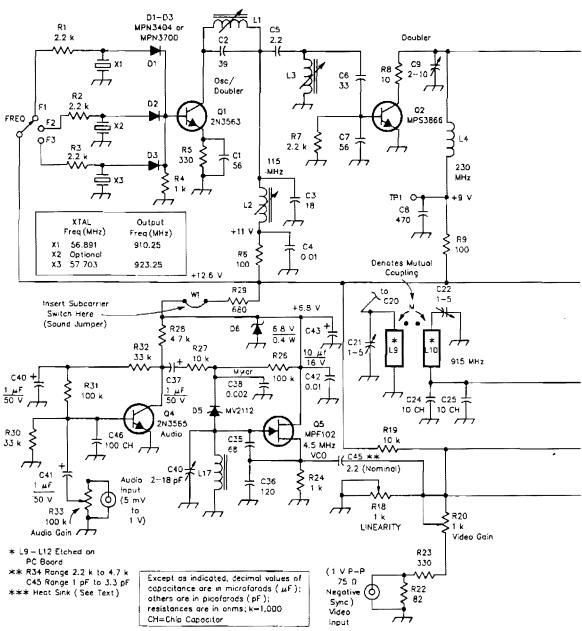This simple ATV preamp covers the 427- to 439-MHz ATV frequencies and can be mast mounted and dc powered through the feedline.



THREE-CHANNEL 902- TO 928-MHz ATV TRANSMITTER

OST

This transmitter is for ATV applications in the 902- to 928-MHz band. It has three crystal-controlled channels, and will accept standard NTSC video input. It also has a 4.5-MHz sound subcarrier. Because this is an AM transmitter, audio can be transmitted as AM on the RF carrier. Simply use the


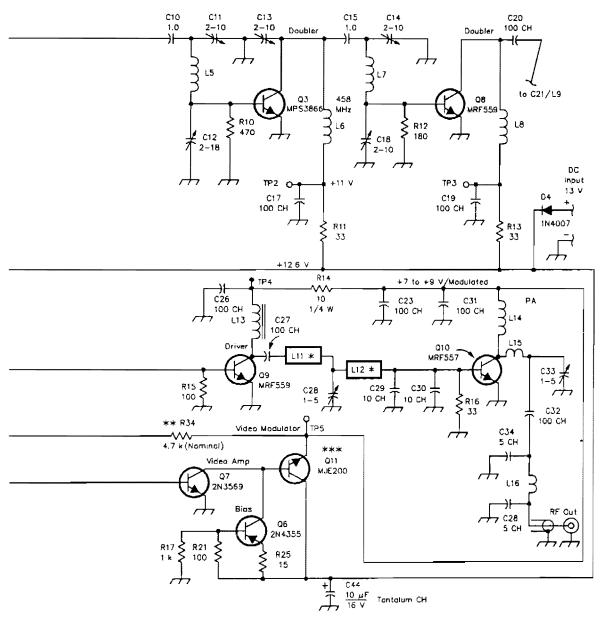


Fig. 5-6

video input. Bandwidth of audio can be restricted to 20.kHz by placing a capacitor with a value of about 0.002 μ F across R34. The output is 1.5 to 2 watts PEP into a 50- Ω load. A complete kit of parts including PC board, is available from North Country Radio, P.O. Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.

ATV DOWNCONVERTER FOR 902 TO 928 MHz

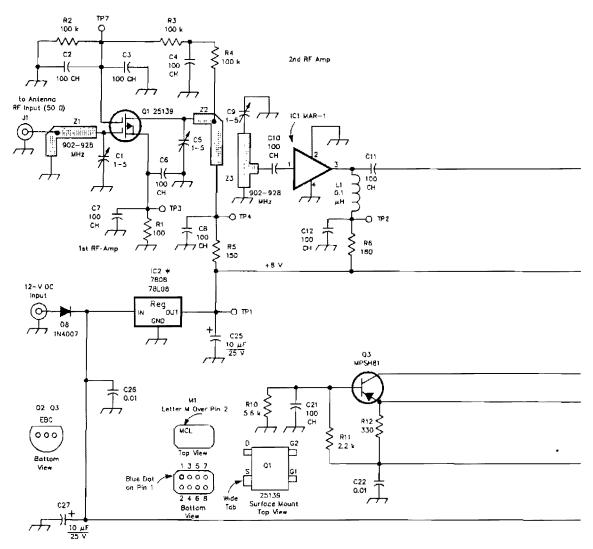

QST

This downconverter converts ATV signals in the 902- to 928-MHz range to a 61.25- or 67.25-MHz IF output frequency (CH 3 or CH 4) to enable reception of these signals on a standard VHF TV receiver or monitor. It features a low-noise RF amp feeding a Schottky diode double-balanced mixer, a tunable LO and one IF preamp stage. The RF amplifier is a low-noise dual-gate GASFET that is followed by a second RF stage using an MMIC. Five tuned circuits are used in the RF amplifier. This feeds a packaged Schottky diode mixer assembly for better dynamic range and reduced susceptibility to intermodulation and strong signal areas. The on-board local oscillator (LO) is voltage tuned and if desired can be set up for remote tuning. All necessary circuitry for remote tuning is on board for coax dc and IF feed. This en-


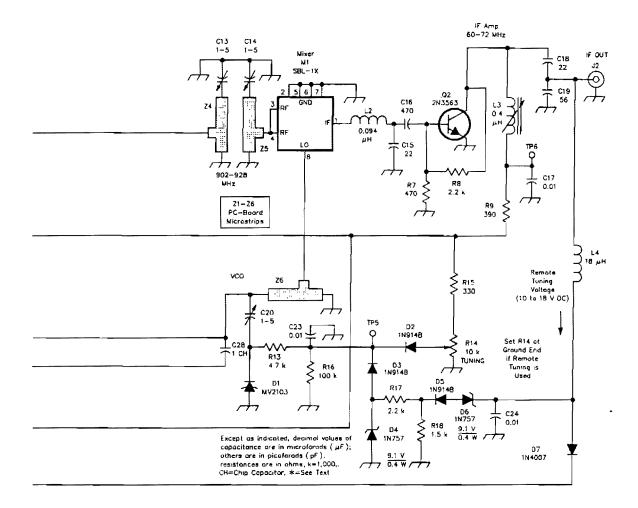


Fig. 5-7


ables the downconverter to be mast mounted to get around feedline losses generally associated with this frequency range. No separate dc feed is necessary because the coax (RG59/U recommended) carries dc power, tuning voltage, and IF signal. A dc block is used at the receiver for the purpose of separating dc voltage supply and the tuning voltage. This allows a cable run of several hundred feet, if needed.

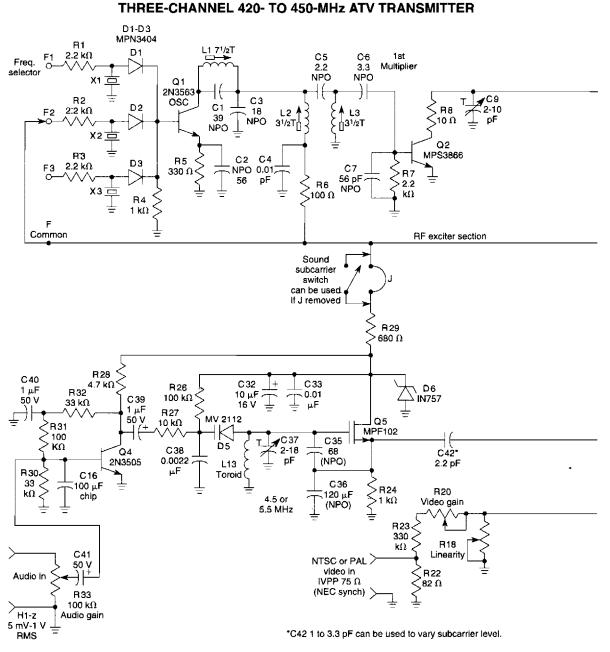By using this downconverter and transmitter, a physically small 915-MHz ATV station or even a video HT can be constructed because both units are each 2.50×4.00 inches $\times 1.00$ high, and can be stacked together. A complete kit of parts, including PC board is available from North Country Radio, P.O. Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.



RUDOLF F. GRAF AND WILLIAM SHEETS


This transmitter is a 2-watt PEP output device for 420- to 450-MHz amateur TV operation. It has three crystal-controlled channels and will accept standard NTSC video input. It also has a 4.5-MHz sound subcarrier capability. Because this transmitter has AM modulation, audio can be transmitted in

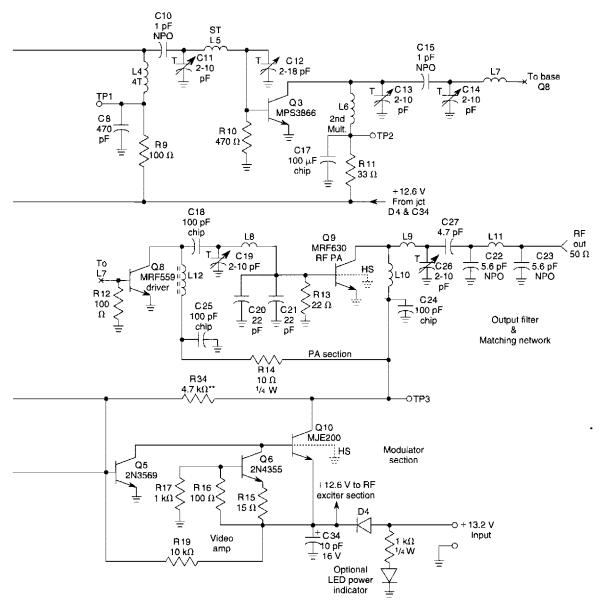

Flg. 5-8

AM form on the RF earrier by applying audio to the video input. Bandwidth of audio can be restricted to 20 kHz by placing a 0.002- μ F capacitor across R34. A complete kit of parts, including PC board is available from North Country Radio, P.O. Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.

ATV DOWNCONVERTER FOR 420 TO 450 MHz

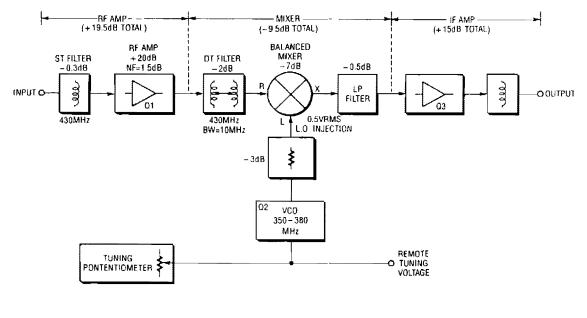


RADIO-ELECTRONICS

Fig. 5-9

This ATV downconverter converts the 420- to 450-MHz ATV band, which is several channels below the lower limit of the UHF band, to channel 3 or 4 for viewing on virtually any TV. The downconverter has a low-noise preamplifier stage and a double-balanced passive mixer for good performance and a wide dynamic range. That is necessary with today's crowded UHF bands. The converter draws about 27 milliamperes from a 13.2-volt dc source, so it can be used in portable and mobile applications. An extra IF stage gives an overall gain of about 25 dB. A block diagram of the downconverter is also shown. A complete kit of parts, including PC board, is available from North Country Radio, P.O. Box 53, Wykagyl Station, New Rochelle, NY 10804-0053A.

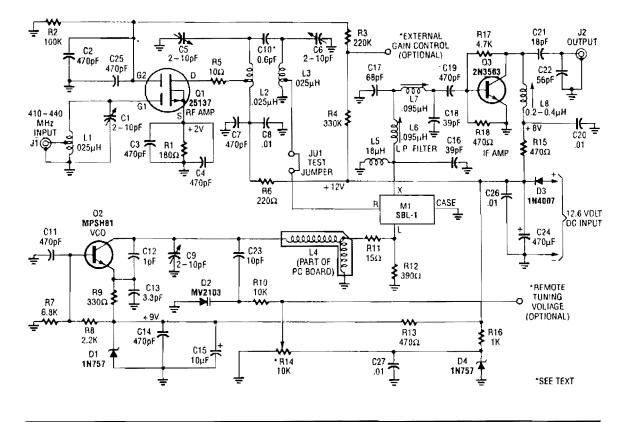ATV DOWNCONVERTER FOR 420 TO 450 MHz (Cont.)




6

Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Operational Transconductance Amplifier with Booster VCR Head Amplifier Tester Lowpass Amplifier **Highpass Amplifier** ISD 1000A Record/Playback Circuit **R**emote Amplifier Programmable Gain Amplifier Programmable Input Amplifier **Remotely Powered Sensor Amplifier Tuned Amplifier** Difference Amplifier with Wide Input Common-Mode Range **Bandpass** Amplifier High-Side Current-Sensing Amplifier High-Input Impedance ac Amplifier **MOSFET** Push-Pull Amplifier Low-Voltage Microphone Preamp Basic Logarithmic Amplifier Using Op Amp **Crystal Tuned Amplifier**

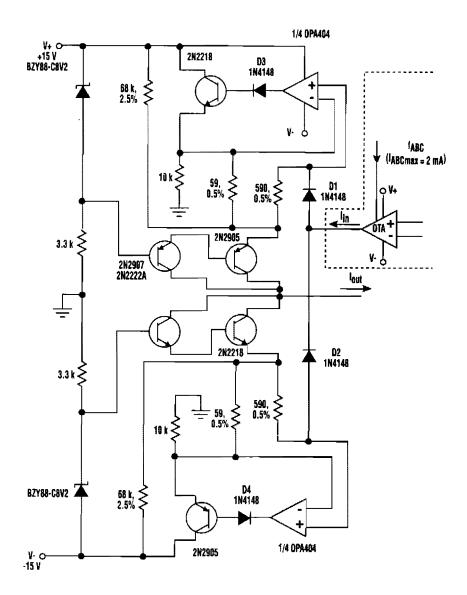


ELECTRONIC DESIGN


Fig. 6-1

Implementing a bidirectional precision current amplifier in an operational transconductance amplifier (OTA) can boost the OTA's output current. To accomplish this task, two diodes and a complementary stage are added to this otherwise simple design.

VCR HEAD AMPLIFIER TESTER

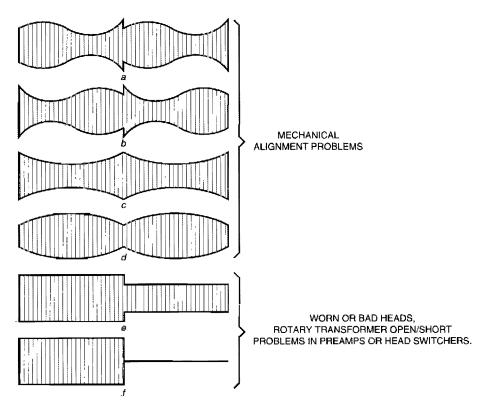

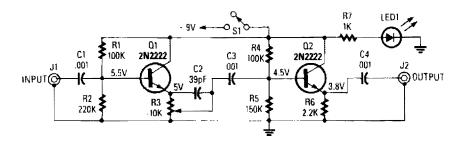IMPROPER WAVEFORMS. Waveforms a-d are caused by mechanical misalignment of the tape guides. The waveforms in e and f indicate proper alignment, but show that there's a problem with either the video heads, pre-amps, or head switcher.





R-E EXPERIMENTERS HANDBOOK

Fig. 6-2

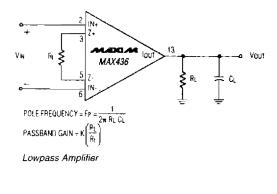This amplifier enables you to use a signal from a working VCR to test the head amplifiers of a suspected defective VCR. The circuit is basically a video amplifier.






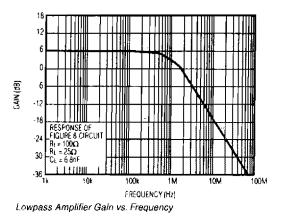


MAXIM

Fig. 6-3

HIGHPASS AMPLIFIER

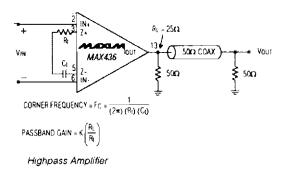

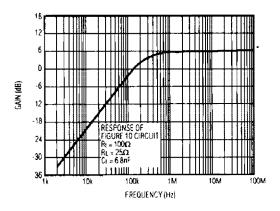


Highpess Amplifier Gain vs. Frequency

MAXIM

Fig. 6-4


ISD 1000A RECORD/PLAYBACK CIRCUIT

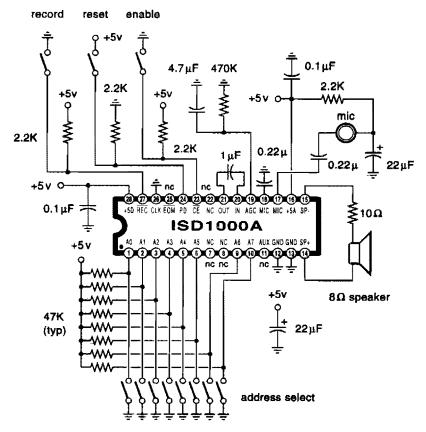

ELECTRONICS NOW

Fig. 6-5

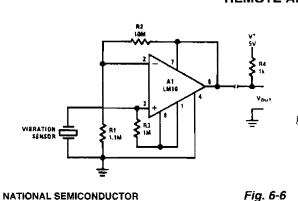
This circuit uses the Information Storage Devices ISD1000A chip (Radio Shack P/N 276-1325).



REMOTE AMPLIFIER

Useful for transducers and such where a single two-wire pair are the only leads available.

PROGRAMMABLE GAIN AMPLIFIER

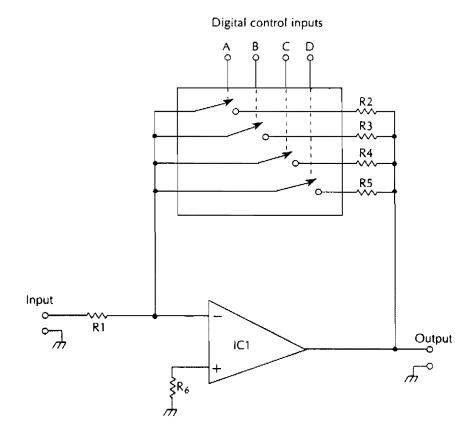


AMPLIFIERS, WAVEFORM GENERATORS & OTHER LOW-COST IC PROJECTS

Fig. 6-7

The gain of this amplifier is $-R_f/R_1$ where $R_f =$ effective value of resistance selected by the digital R1 inputs.

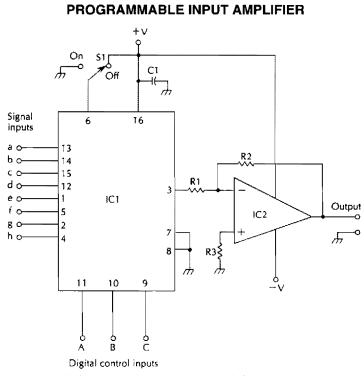- IC1 op amp
- IC2 CD4066 quad bilateral switch
- R1 $1-k\Omega$, $\frac{1}{4}-W$ 5% resistor
- R2 10-k Ω , ¼-W 5% resistor
- R3 4.7-k Ω , ¼-W 5% resistor
- R4 2.2-kΩ, ¼-W 5% resistor
- R5 $1-k\Omega$, $\frac{1}{4}-W$ 5% resistor
- R6 2.2-k Ω , ¼-W 5% resistor




AMPLIFIERS, WAVEFORM GENERATORS & OTHER LOW-COST IC PROJECTS

Fig. 6-8

This amplifier has eight inputs selectable digitally.

IC1	CD4051 SP8T bilateral switch	R1	10-kΩ, ¼-W 5% resistor
IC2	op amp to suit application	R2	22-k Ω , ¼-W 5% resistor
C1	0.1-µF capacitor	$\mathbf{R3}$	18-kΩ, ¼-W 5% resistor
S1	SPST switch		

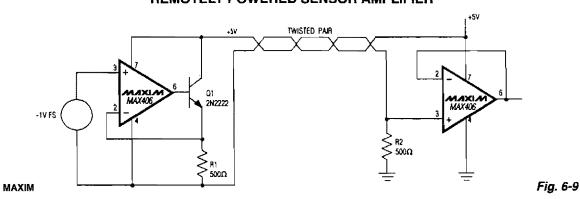

REMOTELY POWERED SENSOR AMPLIFIER

For remote sensor applications, this circuit enables use of a single twisted pair.

TUNED AMPLIFIER

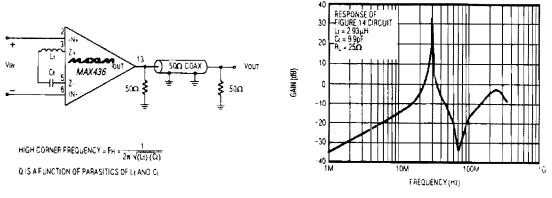


Figure A Tuned Amplifier

Figure B Tuned Amplifier Gain vs. Frequency

MAXIM


Fig. 6-10

This circuit is a tuned amplifier circuit, tuned to the resonant frequency of the LC transconductance network:

$$F_{\rm c} = \frac{1}{2\pi \sqrt{L_{\rm t} C_{\rm t}}}$$

The impedance of the transconductance network is a minimum at the resonant frequency, providing maximum amplifier gain at that frequency. The Q of the amplifier is a function of the parasitic components associated with the LC network. The graph is the frequency response of the circuit, with $L_t = 2.93 \,\mu\text{H}$ and $C_t = 9.9 \,\mu\text{F}$.

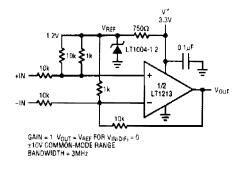
DIFFERENCE AMPLIFIER WITH WIDE INPUT COMMON-MODE RANGE



LINEAR TECHNOLOGY

Fig. 6-11

BANDPASS AMPLIFIER

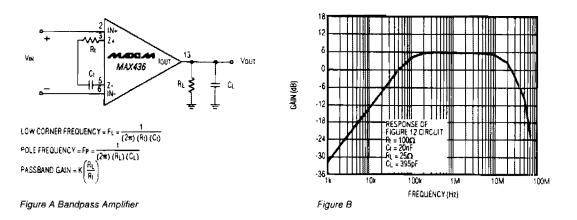


MAXIM

Fig. 6-12

The circuit A is a bandpass amplifier, with the low corner frequency set by the impedance of the transconductance network. The high corner frequency is set by the impedance of the RC network at the amplifier output. The passband gain is $(k) \ge (R_1/R_t)$. Figure B is a plot of the circuit in Figure A, with $R_t = 100 \ \Omega$, $C_t = 20 \ \text{nF}$, $R_1 = 25 \ \Omega$, and $C_1 = 395 \ \text{pF}$.


HIGH-SIDE CURRENT-SENSING AMPLIFIER

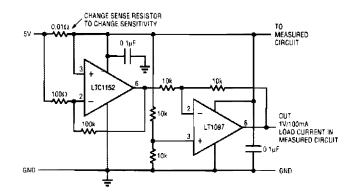

LINEAR TECHNOLOGY

Fig. 6-13


HIGH INPUT IMPEDANCE ac AMPLIFIER

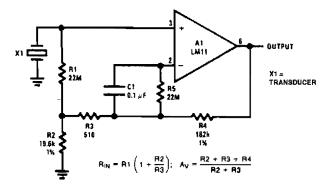

NATIONAL SEMICONDUCTOR

This figure shows an op amp used as an ac amplifier. It is unusual in that dc bootstrapping is used to obtain high input resistance without requiring high-value resistors. In theory, this increases the output offset because the op amp offset voltage is multiplied by the resistance boost.

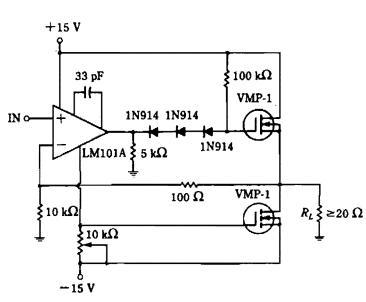But when conventional resistor values are used, it is practical to include R5 to eliminate biascurrent error. This gives less output offset than if a single, large resistor were used. C1 is included to reduce noise.




MOSFET PUSH-PULL AMPLIFIER

MCGRAW-HILL

Fig. 6-15

This amplifier can be used for audio or as a driver for inverter service.

LOW-VOLTAGE MICROPHONE PREAMP

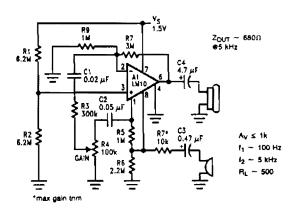


A microphone amplifier is shown. The reference, with a 500-kHz unity-gain bandwidth, is used as a preamplifier with a gain of 100. Its output is fed through a gain-control potentiometer to the op amp, which is connected for a gain of 10. The combination gives a 60-dB gain with a 10-kHz bandwidth, unloaded, and 5 kHz loaded at 500 Ω . Input impedance is 10 k Ω .

Potentially, using the reference as a preamplifier in this fashion can cause excess noise. However, because the reference voltage is low, the noise contribution, which adds root-mean-square, is likewise low. The input noise voltage in this connection is 440-500 nV Hz, about equal to that of the op amp.

NATIONAL SEMICONDUCTOR

Fig. 6-16

BASIC LOGARITHMIC AMPLIFIER USING OP AMP

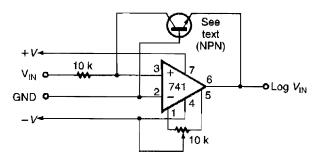


ELECTRONICS NOW!

This logarithmic amplifier uses a single op amp. The current in the feedback loop of the op amp is equal to the current flow at the input of the op amp.


-Fig. 6-17

CRYSTAL TUNED AMPLIFIER

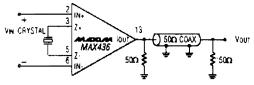

CENTER FREQUENCY = FC = CRYSTAL FREQUENCY

Crystal Tuned Amplifier

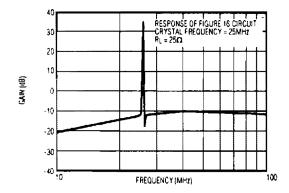

Crystal Tuned Amplifier Gain vs. Frequency

MAXIM

Fig. 6-18


7

A/D Converter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

High-Speed A/D Converter System A/D Converter for PCs

HIGH-SPEED A/D CONVERTER SYSTEM

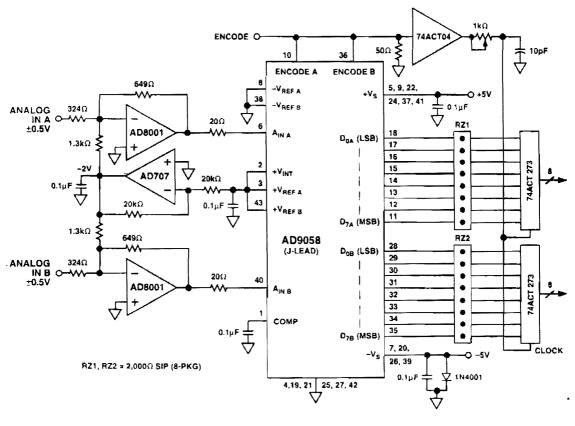


ANALOG DEVICES

Fig. 7-1

The AD8001 is well suited for driving high-speed analog-to-digital converters, such as the AD9058. The AD9058 is a dual 8-bit 50 Msps ADC. In the circuit shown, there are two AD8001s driving the inputs of the AD905f8 which are configured for 0- to +2-V ranges. Bipolar input signals are buffered, amplified (-2×), and offset (by +1.0 V) into the proper input range of the ADC. Using the AD9058's internal +2-V reference connected to both ADCs (as shown) reduces the number of external components required to create a complete data acquisition system. The 20- Ω resistors in series with ADC input are used to help the AD8001 drive the 10-pF ADC input capacitance. The two AD8001s only add 100 mW to the power consumption while not limiting the performance of the circuit.

A/D CONVERTER FOR PCs

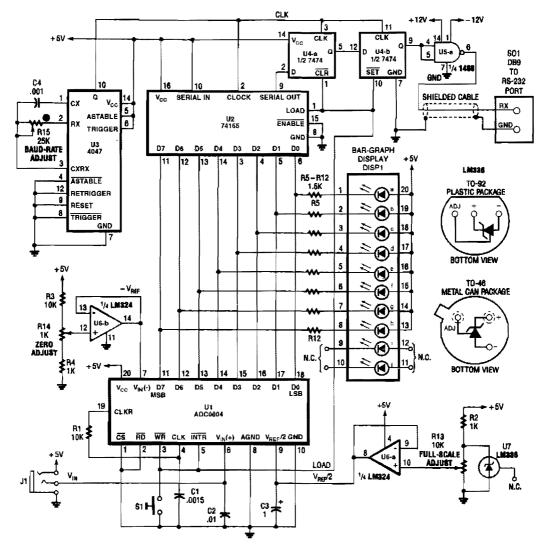

POPULAR ELECTRONICS

Fig. 7-2

An ADC0804 A/D converter converts analog data to digital. This is fed to a 74165 8-bit shift register and converted to serial data. U3 provides a baud-rate clock. U4A and U4B are used to generate start and stop bits needed at beginning and end of each data word.


8

Antenna Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Remote Tuned Active HF Antenna Miniature Broadband Antenna (3 to 30 MHz) FM Auto Radio Diversity Antenna Tunable FM Antenna Booster Matchbox Antenna Tuner Antenna Tuner Active Antenna for UHF Scanners

REMOTE TUNED ACTIVE HF ANTENNA

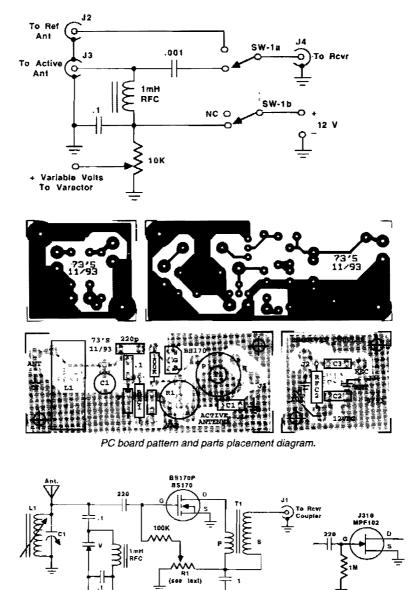

73 AMATEUR RADIO TODAY

Fig. 8-1

An MV1662/S varactor diode tunes this active antenna/preamplifier. R1 varies gate bias on the BS170 FET. T1 is a 3:1 toroidal winding suitable for the frequencies of interest.

Ć

Variabi Volta -


SGD 85170

DGS

BS170P

690

MPF102 J310

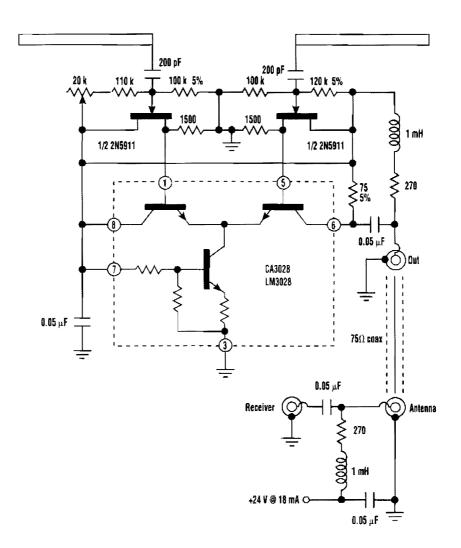


MINIATURE BROADBAND ANTENNA (3 TO 30 MHz)

ELECTRONIC DESIGN

Fig. 8-2

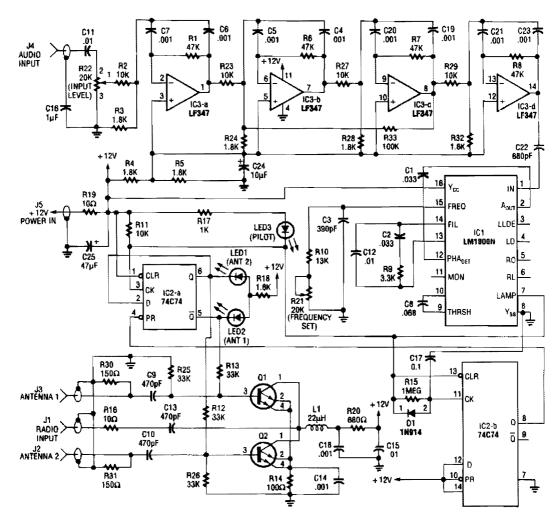A short dipole antenna and impedance converter combined together can be rotated to null out an interfering signal. The converter supplies a tremendous current gain so that the voltage appearing at the dipole's output eventually drives a $75-\Omega$ load.



FM AUTO RADIO DIVERSITY ANTENNA

ELECTRONICS NOW

Fig. 8-3

A second antenna, installed on your vehicle as far away from the original equipment antenna as practical, provides the second FM signal. The figure is a simplified block diagram of the diversity system.


The cables from both antennas are connected to the electronic antenna switch. The 19-kHz pilot signal from the receiver's audio output is passed through a high-gain bandpass active filter, which attenuates audio programming that is much stronger than the pilot signal. After amplification, the pilot subcarrier becomes the reference frequency for a phase-locked loop (PLL) circuit. The output of the PLL locks to the 19-kHz pilot signal and functions as a subcarrier detector. When the reference frequency becomes noisy, the PLL will lose "lock" and trigger the flip-flop, whose output switches the

FM AUTO RADIO DIVERSITY ANTENNA (Cont.)

state of the electronic antenna switch. This action switches the alternate antenna into the system while disabling the original antenna.

If that second antenna is positioned for better reception, the received signal will clear, and the PLL will again lock to the subcarrier and hold the switch in that state until the pilot signal drops out again. If the second antenna does not restore the pilot signal reception after a 0.1-second delay, the primary antenna is switched back on.

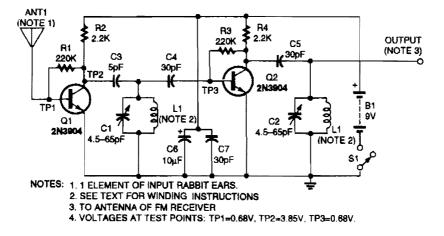When the radio is receiving AM, the absence of the 19-kHz subcarrier will also reactivate the primary antenna that is tuned to the receiver for the best AM reception.




TUNABLE FM ANTENNA BOOSTER

ELECTRONICS NOW

Fig. 8-4

This two-transistor amplifier circuit with tunable tank circuits boosts the distant FM signals. Coils L1 and L2 are $1\frac{1}{2}$ turns #20 AWG bail tinned wire wound around a $\frac{3}{2}$ diameter mandrel.

MATCHBOX ANTENNA TUNER

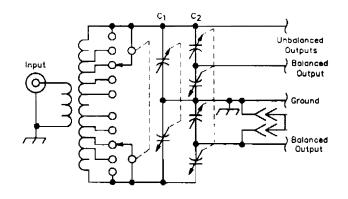


QST

Fig. 8-5

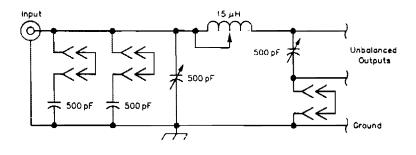C1 is a split stator capacitor and C2 is a dual differential capacitor. The top unbalanced output connection is used for high-impedance unbalanced loads, and the other is used for low-impedance unbalanced loads. In the latter case, the unused balanced load connection is grounded.






QST

Flg. 8-6

This is a circuit diagram of the Collins Model 180S-1 antenna tuner. Three unbalanced configurations are available, two of which form an L-network and the other is a π -network. The tuning range is impressive.

ACTIVE ANTENNA FOR UHF SCANNERS

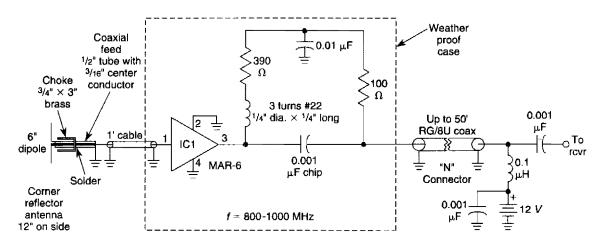

WILLIAM SHEETS

Flg. 8-7

This active antenna is a $\frac{1}{2}$ -wave dipole mounted in a $12^{\circ} \times 12^{\circ} \times 12^{\circ}$ goor corner reflector. A builtin active preamp IC1, fed dc through the RF coaxial line, provides 15 dB gain at 900 MHz to offset cable losses. This provides superior reception for scanners covering the 800- to 1000-MHz range.


9

Attenuator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Switchable Power Attenuator Variable Voltage Attenuator

SWITCHABLE POWER ATTENUATOR

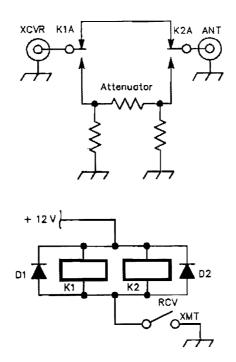

QST

Fig. 9-1

Schematic diagram of a switchable power attenuator that can be used to reduce the power output of transmitters that don't have ALC lines.


Values for 10 and 20 dB:

10 dB: $R_1 = R_3 = 91 \ \Omega$ $R_2 = 75 \ \Omega$ nearest standard values

20 dB: $R_1 = R_3 = 62 \ \Omega$ $R_2 = 240 \ \Omega$ nearest standard values

Note: R1 must handle the largest share of the input power, and R2 somewhat less. This depends on attenuation selected.

VARIABLE VOLTAGE ATTENUATOR

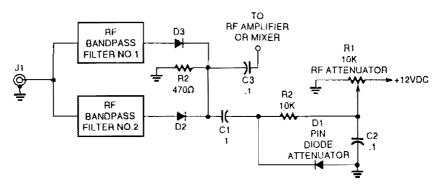

POPULAR ELECTRONICS

Fig. 9-2

The front-end of this circuit is a bank of selectable bandpass filters. The output of the filter banks are shunted to ground via capacitor (C1) and PIN diode (D1). The PIN diode acts like an electronically variable resistor. The resistance across the diode's terminals is a function of the applied bias voltage. This voltage, hence the degree of attenuation of the RF signal, is proportional to the setting of potentiometer R1. The series resistor (R2) is used to limit the current when the diode is forward biased. This step is necessary because the diode has a very low resistance when a certain rather low potential is exceeded.


10

Audio Signal Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Vacuum Tube Audio Amplifier Micropower Linear Amplifier NB FM Audio Amplifier Two-Transistor Audio Amplifier Personal Stereo Audio Amp Transistor RIAA Preamp for Magnetic Phone Cartridges Dynamic Microphone Preamp **Balanced Microphone Preamplifier RIAA** Line Amplifier/Driver Single-Ended HI-Z Microphone Preamp Low-Level Audio Amplifier Simple 20-dB Gain Audio Amplifier High-Gain Dynamic Microphone Preamplifier FET Phono Cartridge Preamp Simple High-Gain Audio Amplifier **RIAA** Preamplifier Basic Complementary Class-AB Single-Supply Amplifier High-Impedance Microphone Input Circuit Electronic-Ear Low-Noise Audio Amplifier (for Parabolic Dish Mikes)

VACUUM TUBE AUDIO AMPLIFIER

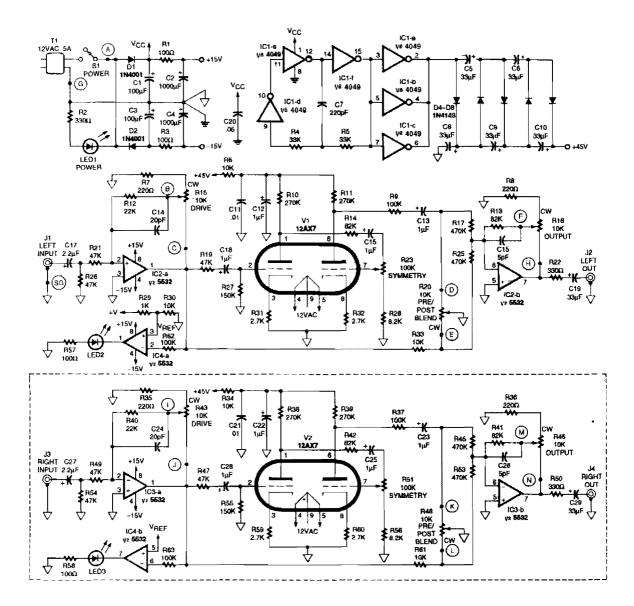


ELECTRONICS NOW

Fig. 10-1

VACUUM TUBE AUDIO AMPLIFIER (Cont.)

This schematic is for a tubehead amplifier. The output from transformer T1 is positive half-wave ac rectified by D1 and filtered by C1, C2, and R1 for a +15-V supply. A -15-V supply is available from D2, C3, C4, and R3. The plate supply for the 12AX7 tubes is produced by a voltage multiplier.

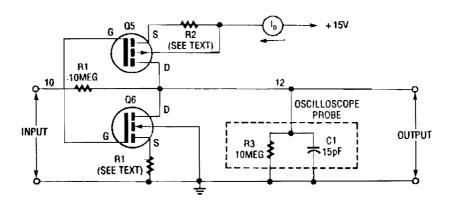Some listeners prefer the sound of a vacuum tube audio system. Although this is rather subjective and a personal preference, this circuit can be used to simulate the "tube sound" preferred by these listeners.




MICROPOWER LINEAR AMPLIFIER

ELECTRONICS NOW

Fig. 10-2

This circuit, based on the inverter in the CD4007UB CMOS linear amplifier, shows a method for reducing drain current.

NB FM AUDIO AMPLIFIER

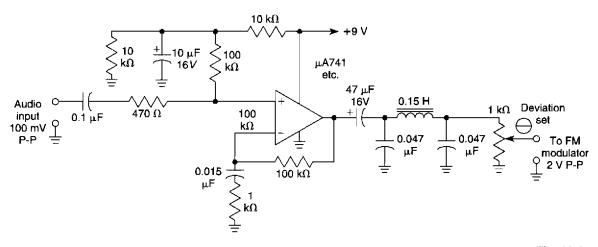


WILLIAM SHEETS

Fig. 10-3

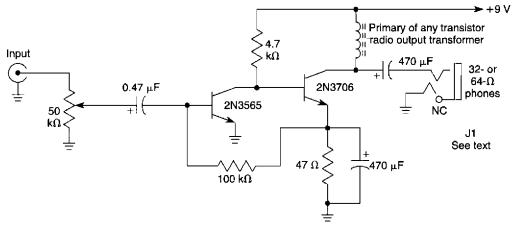This audio system amplifies, limits, and filters an audio voice signal for use with an FM modulator or VCO. It has pre-emphasis of 6-dB/octave 300–3000 Hz. Almost any suitable op amp can be used.






WILLIAM SHEETS

Fig. 10-4

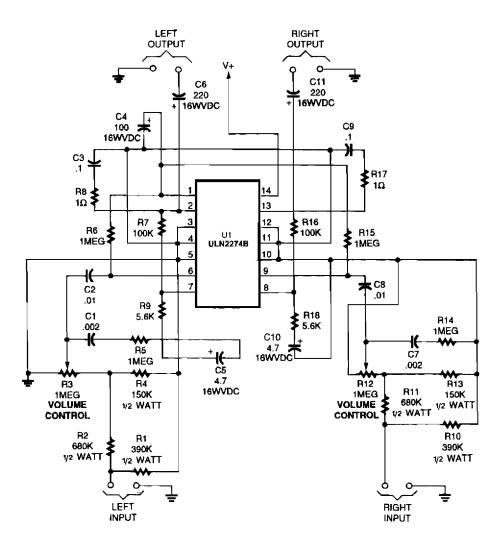This is a general-purpose audio amplifier for driving a pair of stereo earphones in monaural mode. Two can be used for stereo. In this case, ground the center top of the earphone (sleeve of J1).




PERSONAL STEREO AUDIO AMP

POPULAR ELECTRONICS

Fig. 10-5


You can make your personal stereo do double duty as a small room stereo by adding this 2-watt amplifier.

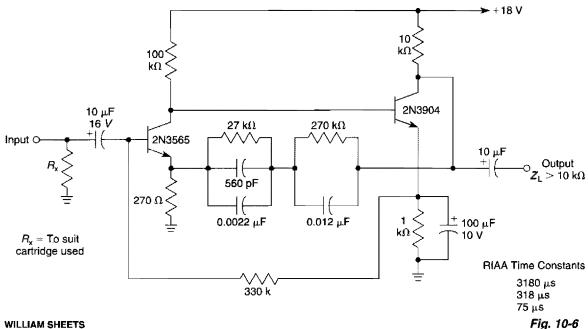TRANSISTOR RIAA PREAMP FOR MAGNETIC PHONE CARTRIDGES



This two-transistor circuit has around 40 dB (midband) gain at 1 kHz. A magnetic cartridge is used as a source.


DYNAMIC MICROPHONE PREAMP

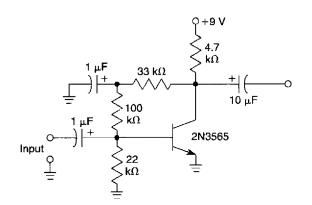

WILLIAM SHEETS

Fig. 10-7

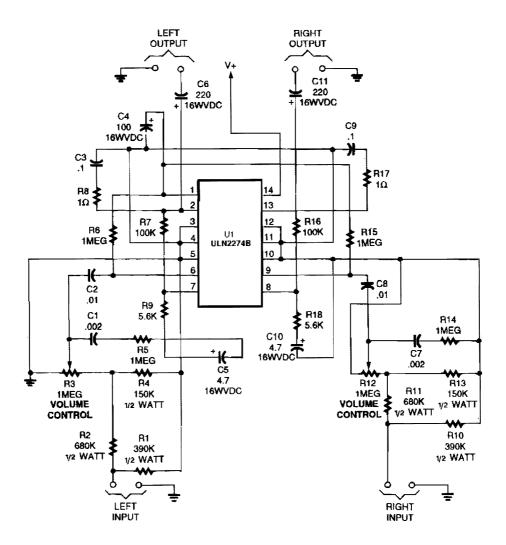This preamplifier provides 40- to 43-dB gain when used with a low-impedance (<1 k Ω) dynamic microphone.




PERSONAL STEREO AUDIO AMP

POPULAR ELECTRONICS

Fig. 10-5

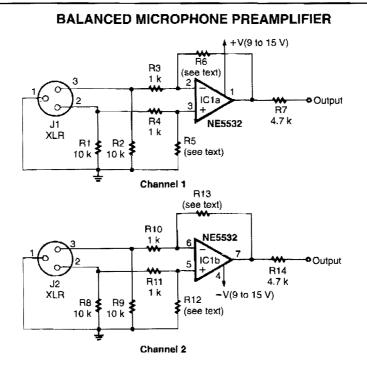You can make your personal stereo do double duty as a small room stereo by adding this 2-watt amplifier.




ELECTRONICS NOW

Fig. 10-8

A balanced input for microphones can solve hum and noise pickup problems. R6 and R13 should equal R5 and R12, respectively. Typical values would be 10 k Ω to 22 k Ω .

RIAA LINE AMPLIFIER/DRIVER

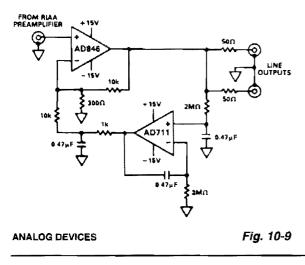

Two op amps by Analog Devices are used in this audio line amplifier, which is suitable for interfacing with an RIAA preamplifier.


P7, 64.9kO w /₅ = +5V VBIAS C5 100µF R1 25 Ċ4 R8 22.1kΩ C2 10µF 49.9kΩ 44 100µF 25V R3 22.1kΩ 470 VOUT 1% th DYNAMIC OR CRYSTAL 100µ F 1**00**Ω MICROPHONE 25V **≦**^{82a} U1 = 1/2 SSM2135. 221Ω M AD822, AD820 $GAIN = 1 + \frac{R1}{R2}$ CI Ş 47kΩ 100µF 25V Z ≥ 600Ω R20 -vs R4 2.5kΩ REV LOG -ŏ 22.1kQ


SINGLE-ENDED HI-Z MICROPHONE PREAMP

ANALOG DEVICES

Fig. 10-10

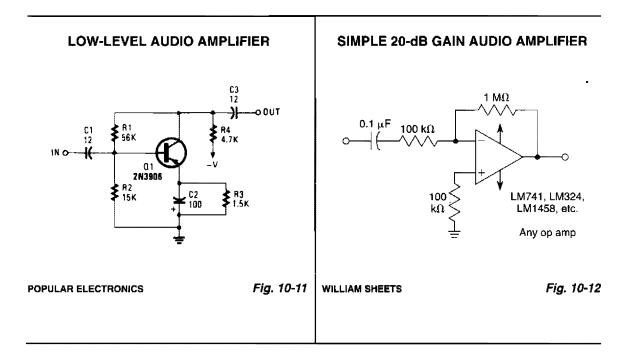This low noise circuit works on a +5-V supply. Gain range is 20 to 40 dB and bandwidth is 20 kHz with the AD820. THD is 0.05% with 1 V RMS into a 2-k Ω load. Noise output with the input shorted is less than 200 μ V.



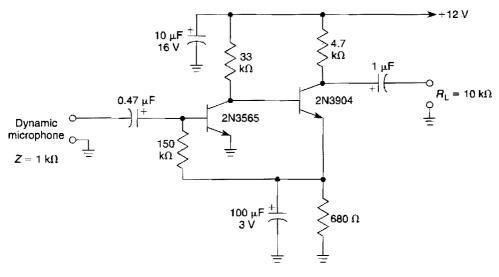


HIGH-GAIN DYNAMIC MICROPHONE PREAMPLIFIER

WILLIAM SHEETS

Fig. 10-13

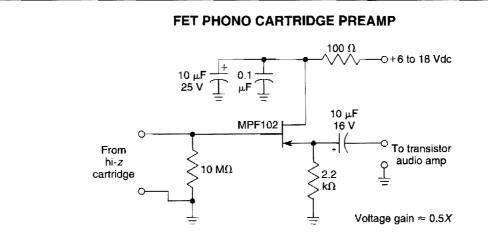This microphone preamplifier is capable of about 70 dB or more gain at audio frequencies. Its gain is approximately equal to the product of the $h_{\rm fe}$ of both transistors times the ratio of the load resistance to the input resistance of the preamp. As an approximation, these resistances are usually similar in value (≈ 2 to 5 k Ω) for most applications, so this ratio can be taken as unity.




WILLIAM SHEETS

A high-Z phono cartridge can be matched to a low-Z amplifier with this circuit. The FET provides a current gain of over 1000× and a voltage gain of about 0.5×.

Fig. 10-14

SIMPLE HIGH-GAIN AUDIO AMPLIFIER

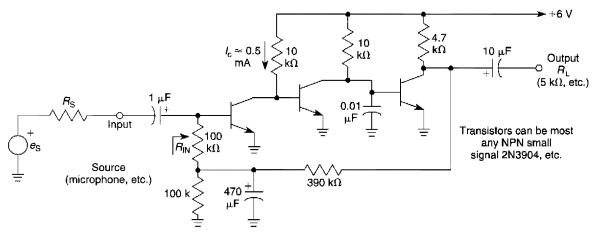


WILLIAM SHEETS

Flg. 10-15

This amplifier has a very high gain in the audio range and is approximately the product of the current gains of the three transistors multiplied by the ratio of $R_{\rm L}$ to $(R_{\rm IN} + R_{\rm S})$. $R_{\rm IN}$ is approximately to:
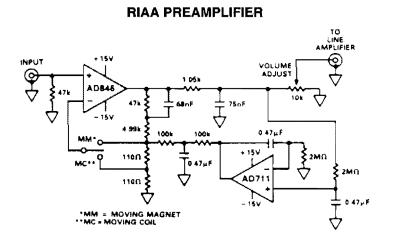
$$(\beta_{Q1} + 1) (26) \overline{I_{EQ1}}$$




ANALOG DEVICES


Fig. 10-16

This preamp for RIAA phone use uses two op amps by Analog Devices. A switch selects compensation for moving magnet or moving coil pickups.

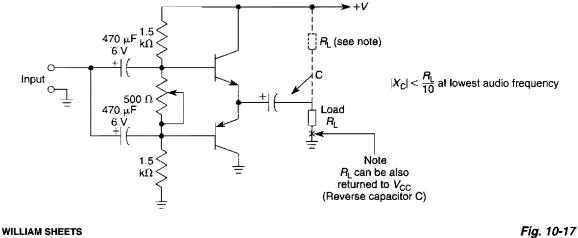BASIC COMPLEMENTARY CLASS-AB SINGLE-SUPPLY AMPLIFIER




HIGH-IMPEDANCE MICROPHONE INPUT CIRCUIT

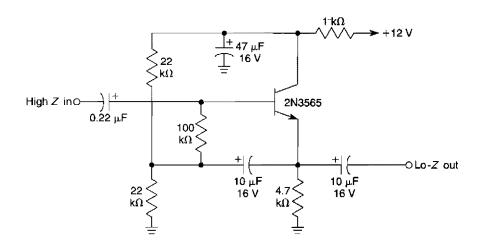

WILLIAM SHEETS

This input circuit will enable use of a high-impedance microphone where a low-impedance microphone would be needed.

Fig. 10-18

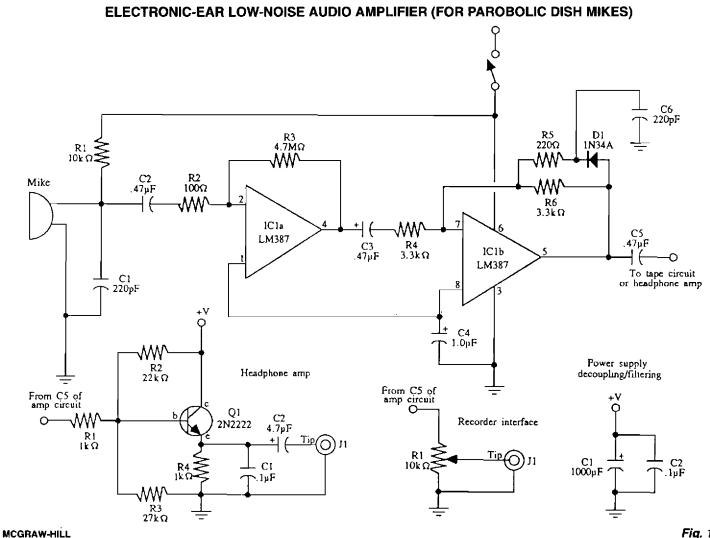

Use this circuit with a parabolic reflector microphone for eavesdropping on distant sounds.

Fig. 10-19


11

Audio Power Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Audio Power Amplifier, 1.5 W, 12 V Parallel Power Op Amps 10-Watt Audio Amplifier Power Bridge Amplifier with Single-Ended Output Line-Operated Audio Amplifier Basic Complementary Class-AB Power Amplifier Simple Vacuum Tube Amplifier Power Supply for Vacuum Tube Amplifier 16-W Bridge Amplifier **RFI-Proof** Audio Power Amplifier Basic Quasi-Complementary Power Amplifier with Split Power Supplies **RIAA Phono Amplifier** Basic Quasi-Complementary Power Amplifier Circuit Phone Amp 80-Watt IC Audio Amplifier **Basic Complementary Power Amplifier Circuit** General-Purpose AF Amplifier Bridge Connection of Two Power Op Amps 90-V 10-A High-Power Amplifier Mini-Megaphone

AUDIO POWER AMPLIFIER, 1.5 W, 12 V

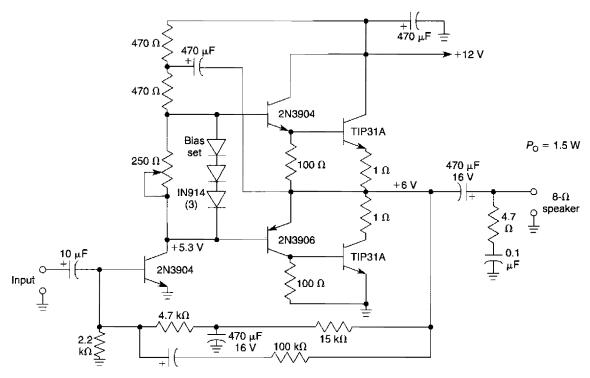

WILLIAM SHEETS

Fig. 11-1


The power amplifiers, A2 and A3, are wired

as followers and connected in parallel with the

outputs coupled through equalization resistors.


Although ICs have largely replaced circuits such as this, this circuit still finds use where the flexibility of a discrete device design is desirable. Parts are easy to obtain and the problem of IC obsolescence is eliminated. The TIP31A can be heatsinked to a small metal heatsink, if desired.

PARALLEL POWER OP AMPS

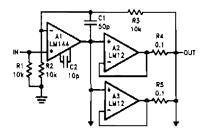

NATIONAL SEMICONDUCTOR



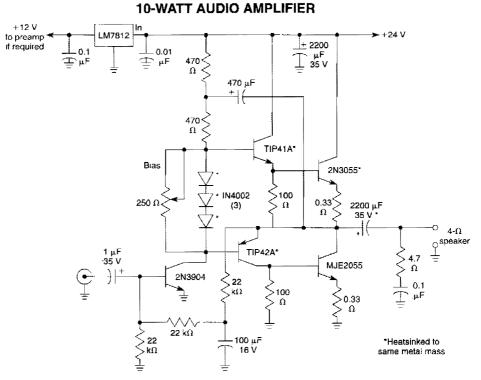


WILLIAM SHEETS

Fig. 11-3


This circuit is a general-purpose 10-W audio amplifier for moderate-power PA or modulator use in an AM transmitter. With higher voltages and a change in bias resistors, up to 30 W can be obtained.

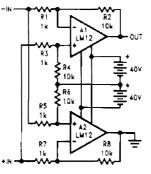POWER BRIDGE AMPLIFIER WITH SINGLE-ENDED OUTPUT



Bridge amplifier with a single-ended output uses floating supply. Either input can be grounded.

LINE-OPERATED AUDIO AMPLIFIER

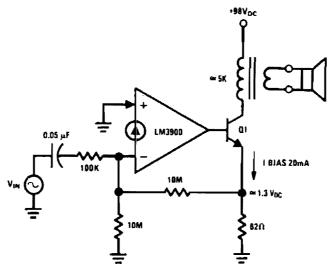


NATIONAL SEMICONDUCTOR

Fig. 11-5


An audio amplifier which operates off a +98-Vdc power supply (the rectified line voltage) is often used in consumer products. The external high-voltage transistor, Q1, is biased and controlled by the LM3900. The magnitude of the dc biasing voltage, which appears across the emitter resistor of Q1 is controlled by the resistor. The resistor is placed from the (-) input to ground.

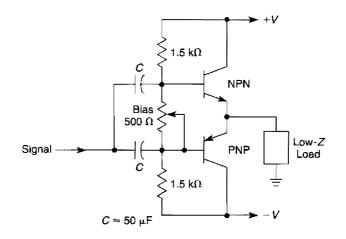BASIC COMPLEMENTARY CLASS-AB POWER AMPLIFIER



WILLIAM SHEETS


SIMPLE VACUUM TUBE AMPLIFIER

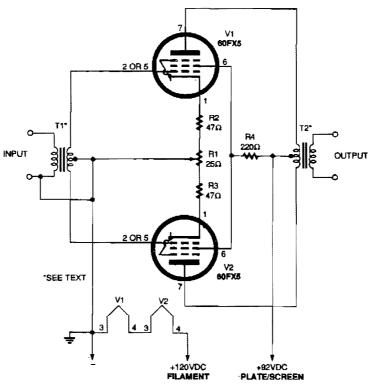


POPULAR ELECTRONICS

Fig. 11-7

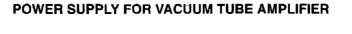Using a pair of 60 FX5 tubes, direct operation from 120 Vac is possible. However, the use of a power supply with an isolation transformer is recommended. R1 is adjusted for equal voltages at pin 1 of V1 and V2. The power output is about 2 to 3 watts.



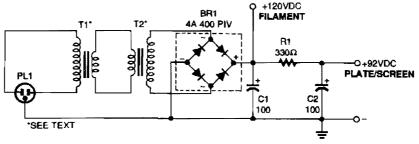


POPULAR ELECTRONICS

Fig. 11-8


The power supply for the amplifier uses two low-voltage transformers connected back-to-back. The full-wave bridge rectifier, BR1 provides dc for the filaments, plates, and screens.

16-W BRIDGE AMPLIFIER

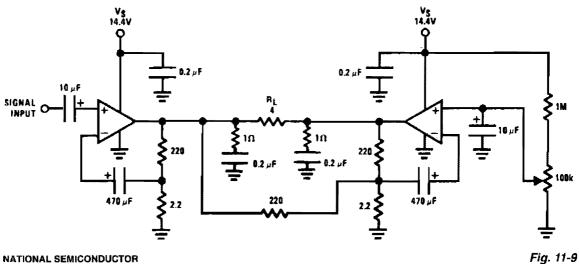

NATIONAL SEMICONDUCTOR

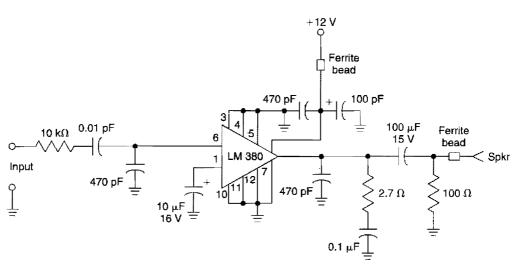This circuit delivers 16 W RMS audio into a 4- Ω load (R_1). The ICs are LM383s.




RFI-PROOF AUDIO POWER AMPLIFIER

WILLIAM SHEETS

This 1-watt audio amplifier was used in an FM repeater and proved to be immune to strong RF signal pickup. It functioned well in very strong RF fields.

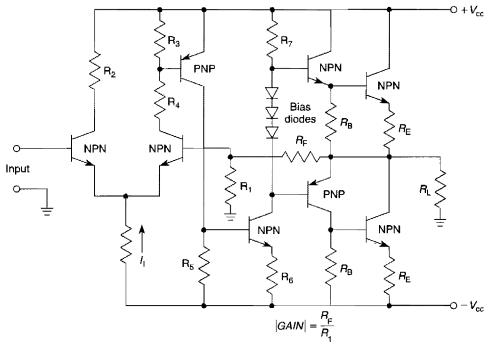
BASIC QUASI-COMPLEMENTARY POWER AMPLIFIER WITH SPLIT POWER SUPPLIES



WILLIAM SHEETS

Fig. 11-11

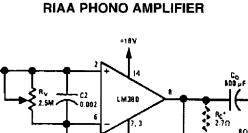This is the basic circuit used in many audio power output stages where split supplies are used. This amplifier is inherently dc coupled and has high open loop gain and good dc stability if the feedback network is properly designed.



NATIONAL SEMICONDUCTOR

 $\textit{Mid-band gain} = \frac{R_1 + 150 \text{ k}\Omega}{150 \text{ k}\Omega}$

C1 220 pf R, = 1.5M



C1 .05 µF

2

 $V_S = 18V$

LM380

7.3

С₀* 0.1 µF

500 ul


Rc 2.70



-F1 75k


R_v 25K 25K TONE CONTROL

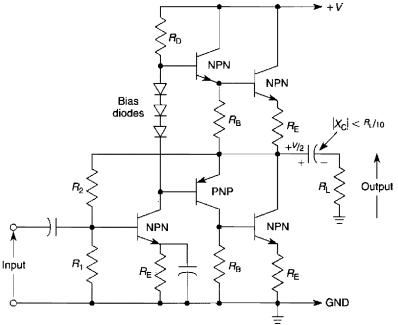The figure shows the LM380 with a voltage-divider volume control and high-frequency roll-off tone control.



WILLIAM SHEETS


Fig. 11-13

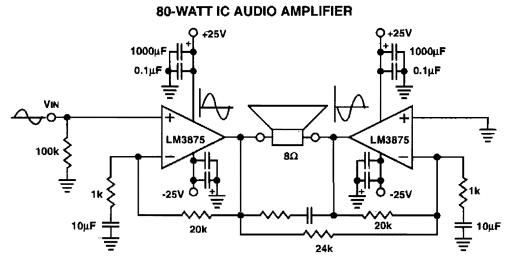


NATIONAL SEMICONDUCTOR

Fig. 11-15

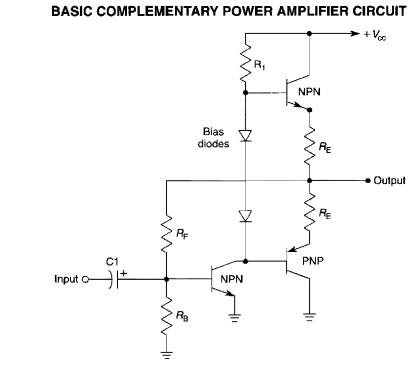This audio power amp will deliver 80 W of audio into an 8- Ω load. The LM3875 IC devices should be suitably heatsinked. Note that the amplifier is a bridged circuit, with both speaker leads "hot."




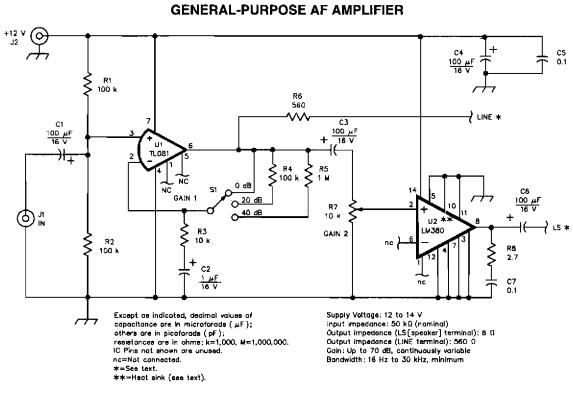


QST

Fig. 11-17

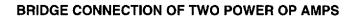Schematic of the general-purpose AF amplifier. All resistors are ¼-W, 5%-tolerance carbon-composition or metal-film units. Equivalent parts can be substituted. General-purpose IC replacements are shown in parentheses.



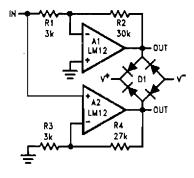


NATIONAL SEMICONDUCTOR

Fig. 11-18

These bridge connections provide differential outputs that approach twice the total supply voltage. Diode bridge clamps output to the supplies.


90-V 10-A HIGH-POWER AMPLIFIER

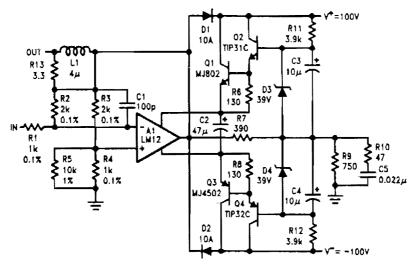

NATIONAL SEMICONDUCTOR

```
-Fig. 11-19
```

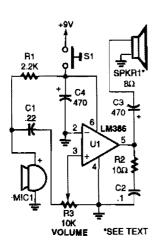This amplifier can drive ± 90 V at 10 A, more than twice the output swing of the LM12. The IC provides current and power limiting for the discrete transistors.



MINI-MEGAPHONE

The Mini-Megaphone is comprised of an electret microphone (MIC1), and LM386 low-voltage audio-power amplifier (U1), a horn speaker (SPKR1), and a few other components.

POPULAR ELECTRONICS


12

Automotive Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Electronic Auto Stethoscope Automotive Electrical Monitor Car Alternator Monitor (Idiot Light) Cigarette Lighter 9-V Adapter Motorcycle Turn-Signal System Tachometer Signal-Conditioning Circuit Smart Turn Signal for Autos and Motorcycles Turn-Signal Alarm High-Power Audio Amp for Automotive Installation High-Power 12-V IC Auto Amplifier Capacitor Discharge Ignition System Car Audio Power Supply Motorcycle Headlight Monitor Headlight-Off Indicator Auto Battery Isolator Circuit Automotive HI-Z Test Light

ELECTRONIC AUTO STETHOSCOPE

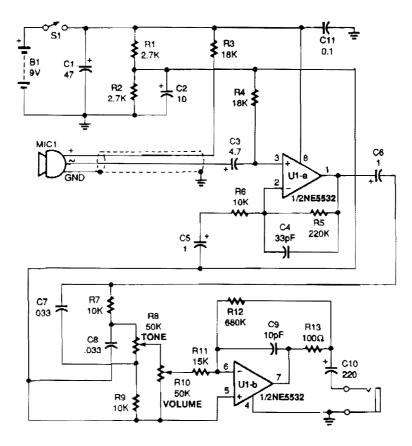

POPULAR ELECTRONICS


Fig. 12-1

The heart of the Stothoscope is the NE5532 audio op amp, U1. That component directly drives low impedances and allows the use of headphones without adding another amplifier.

AUTOMOTIVE ELECTRICAL MONITOR

Condition	Normal Voltage	Possible Fault
Vehicle at rest	12.6 volts	<12.4 volts: bad cell or severely undercharged battery
Cranking	>9 volts	<9 volts: Weak battery
Idling	>12 8 volts	<12.8 volts: Not charging; bad alternator or wiring
Running minimum load	>13.4 volts	<13.4 volts: defective alternato or voltage regulator
Running minimum load	<15.2 volts	>15.2 volts: Overcharging; defective regulator
Running maximum load	>13.4 volts	<13.4 volts: alternator defective or belt slipping




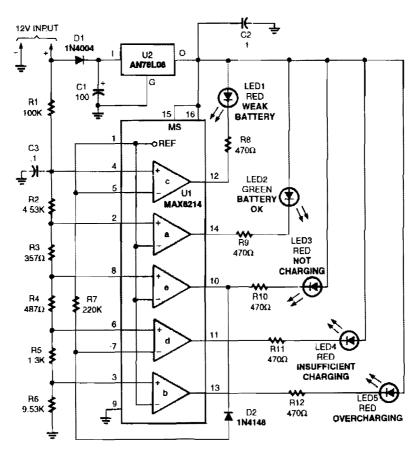

POPULAR ELECTRONICS

Fig. 12-2

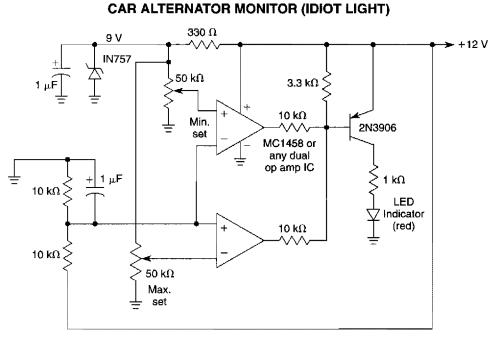The automotive electrical diagnostic system is built around a Maxim MAX8214ACPE five-stage voltage comparator, which contains a built-in 1.25-volt precision reference, and on-board logic that allows the outputs of two of the comparators to be inverted.




WILLIAM SHEETS

Fig. 12-3

A window comparator is used to detect a too-low or a too-high system voltage. The minimum and maximum settings are set with two 50-k Ω pots, as desired.

CIGARETTE LIGHTER 9-V ADAPTER

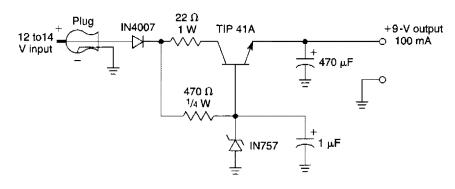


WILLIAM SHEETS

A simple way to provide +9 V at 100 mA from a 12-V auto source. Applications include small radios, cassettes, etc.

97

Fig. 12-4

MOTORCYCLE TURN-SIGNAL SYSTEM

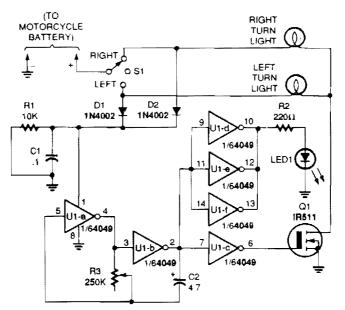


POPULAR ELECTRONICS

Fig. 12-5

Tired of making hand signals? Build this simple turn-signal system and keep your hands on the handlebars.

TACHOMETER SIGNAL-CONDITIONING CIRCUIT

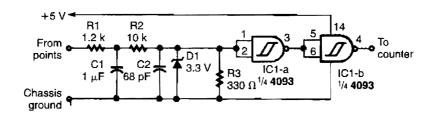


ELECTRONICS NOW

Fig. 12-6

This circuit, for use with auto tachometers, cleans up the ragged distribution waveform before it is sent to pulse counter circuits.

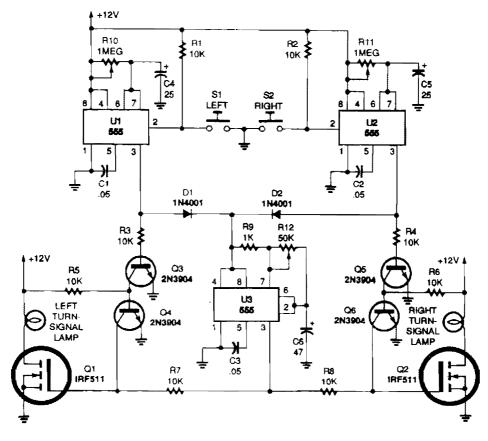SMART TURN SIGNAL FOR AUTOS AND MOTORCYCLES




POPULAR ELECTRONICS



Momentarily pressing S1 starts the left on-time timer and produces a positive output at pin 3 of U1. Power for the on/off signal timer, U3, is supplied through D1.

Also, a positive bias is supplied from U1's output to the base of Q3, turning it on and turning Q4 off. Unclamped Q1 turns the left turn-signal lamp on and off at that same low-frequency rate. Because U2 is not activated, its output at pin 3 is low, keeping Q5 off. With Q5 turned off, Q6 is on, clamping the gate of Q2 to ground and keeping it from responding and supplying an output for the right turn-signal lamp. The left turn signal continues to operate until the U1 timer circuit times out; the right turn signal operates in a similar manner, with U2 setting its operating time.

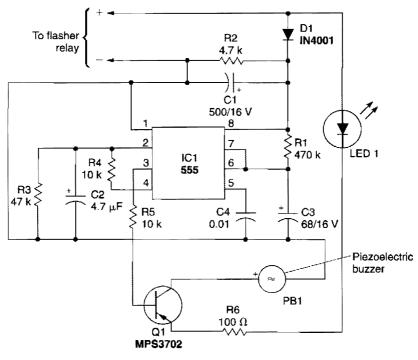Potentiometer R10 sets the running time for the left turn signal and R11 sets that for the right turn signal.



TURN SIGNAL ALARM


RADIO-ELECTRONICS

Fig. 12-8

This circuit can be used to tell the driver of a vehicle when his or her turn signal has been left on for too long. The circuit consists of IC1, a 555 timer; transistor Q1, and MPS3702 PNP preamp/driver; PB1, a piezoelectric buzzer; along with an assortment of resistors, capacitors, and diodes. The 555 is connected in the monostable mode, requiring only a momentary negative pulse at pin 2 to trigger the timing cycle.

Power for the circuit is picked off the flasher relay and applied to IC1, pin 8, provided by an initially discharged capacitor, C2. After the initial triggering, the voltage across C2 rises as it becomes charged through R4, a 10-k Ω resistor. This prevents subsequent interference with the delay function caused by false triggering.

Capacitor C3 and resistor R1 determine the delay. With the component values shown, a delay of about one minute will be provided before the intermittent tweet sound generated by the circuit begins. If higher values are used for C2 and R1, a longer delay time will result. The light-emitting diode, LED1, provides a voltage drop to assure complete transistor blocking during the off periods of the flasher. Alternatively, two diodes in series can be used.

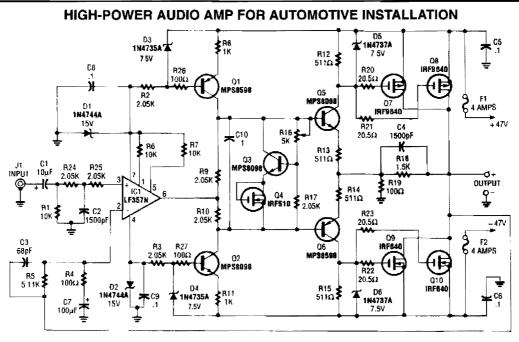

RADIO-ELECTRONICS

Fig. 12-9

Two of these audio amplifiers can be used to make a stereo amplifier 200 W per channel. IRF640 and IRF9640 power MOSFETs are used to drive the output load, which might be 4 or 8 Ω . Response is 12 Hz to 45 kHz (-3 dB), THD <0.1%. Power is supplied by a switching-type power supply, which is external to the amplifier (±47 V). About 600 W total power (peak) is needed.


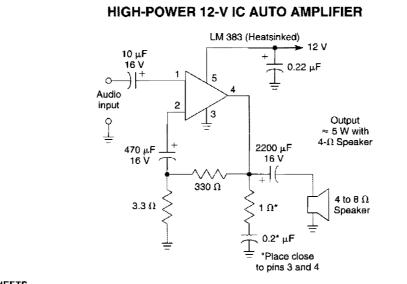


Fig. 12-10

CAPACITOR DISCHARGE IGNITION SYSTEM

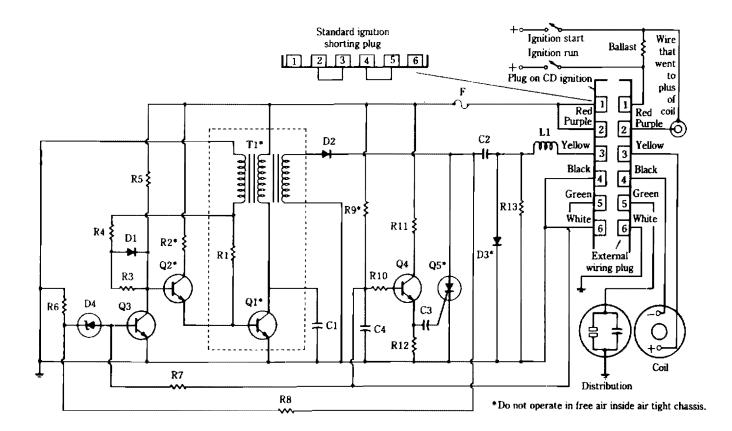

MCGRAW-HILL


Fig. 12-11

This ignition system charges a capacitor (C2) to 350 V and discharges it through the ignition coil.


CAPACITOR DISCHARGE IGNITION SYSTEM (Cont.)

A Parts list

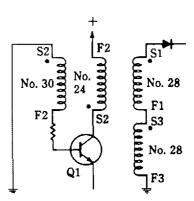Q1-2N3055 Q2-2N3053 Q3-2N3241 Q4-2N3241 Q5-RCA 40657 D1-1N3193 D2-1N3195 D3-1N1763A D4-12 V, 1/4 W C1-0.25 µF, 200 V C2-1 µF, 400 ∨ C3-1 µF, 25 V C4-0.25 µF, 25 V F-5A L1-10 µH, 100 Turns of No. 28 Wire Wound on a 2-W Resistar (100 Ohms or More) R1-1000 ohms, 1/2 W R2-35 ohms, 5 W R3-22,000 ohms, 1/2 W R4-1000 ohms, 1/2 W R5-18,000 ohms, 1/2 W R6-15,000 ohms, 1/2 W R7-8200 ohms, 1/2 W R8-0.39 megohm, 1/2 W R9-220 ohms, 1 W R10-1000 ohms, 1/2 W R11~68 ohms, 1/2 W R12-4700 ohms, 1/2 W R13-27,000 ohms, 1/2 W



Details of inverter transformer

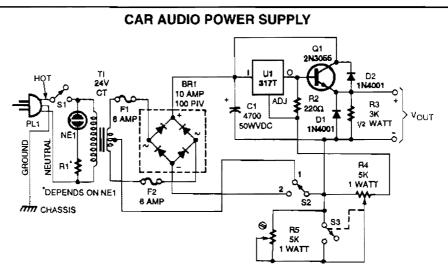

POPULAR ELECTRONICS

Fig. 12-12

This supply has a variable output voltage feature and a dual voltage switch, S2. Q1 should be adequately heatsinked.

MOTORCYCLE HEADLIGHT MONITOR **HEADLIGHT-OFF INDICATOR** (TO MOTORCYCLE 170 MOTORCYCLE BATTERY) HEADLIGHT BATTERY R1 470Ω ** HEADLIGHT HEADLIGHT SWITCH SWITCH HEADLIGHT R1 R2 4 7K 0 LED. 100K C١ q 8 10 U1 POPULAR ELECTRONICS Fig. 12-13 655 The headlight on most newer bikes is keyed LED 83 on with the ignition switch to guarantee that you 330 M are never underway without your headlight bc-BZ1 ing on. However, many older bikes have a fac-~ tory headlight switch, and a growing number of **POPULAR ELECTRONICS** Fig. 12-14 the newer bikes are owner-modified in the same wav. Increasing the value of R_2 or C_1 will lower the oscillator's frequency and decreasing one of those A simple headlight monitor circuit consists of just an LED and a current-limiting resistor values will increase the frequency. The IC's output wired across the headlight switch, as shown. at pin 3 drives the LED through R3 and sends When the ignition is on and the headlight switch power to the piezo sounder. Use a bright LED so is off, the LED will glow. that you will be able to see it in the daytime. **AUTO BATTERY ISOLATOR CIRCUIT** AUTOMOTIVE HI-Z TEST LIGHT CASE 3V BULD To main From electrical alternator **B**1 system Τo 1.57 (starter, etc) accessories R2 \circ 1.5V PROBE Main Aux **R**2 battery battery 10MEC VN2221 81 2MEG OR 89170 **POPULAR ELECTRONICS** Fig. 12-16 Fig. 12-15 ELECTRONICS NOW The diodes ensure that current can flow in This test light has a high-input impedance both batteries from the alternator, but the main and draws only 1 mA at 12 V. Q1 switches dc to a battery can't feed the accessory system, nor vice battery and lamp circuit. versa.


13

Battery Charger Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Smart Battery Charger Rechargeable LED Flashlight Battery Charger Controller Single-Cell Lithium Battery Charger Battery-Charging Current Limiter Three-Cell Lithium Charger NiCad Battery Charger Backup Battery Monitor/Charger/Alarm NiCad Charger/Zapper 2- to 5-Cell Lithium Battery Charger Lead-Acid Trickle Charger NiCad Battery Charger


SMART BATTERY CHARGER

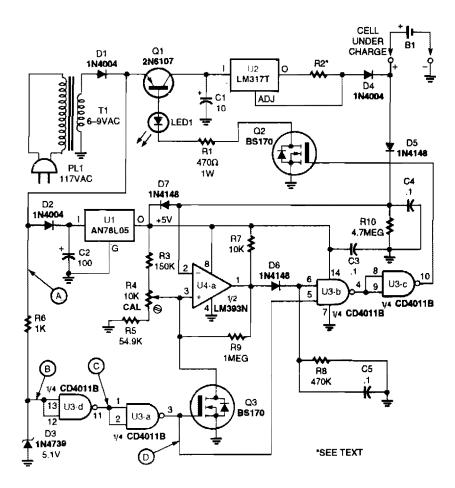

ELECTRONICS NOW

Flg. 13-1


This charger will work with NiCad or the new rechargeable alkaline batteries. The Smartcharger is comprised mainly of four chips—an AN78L05 5-V, 100-mA regulator (U1), an LM317T 1-A adjustable-voltage regulator (U2), a CD4011BE quad 2-input NAND gate (U3), and an LN393N dual-voltage comparator (U4). The value and rating of R2 is selected as described in the text. R2 is selected for a 1.2-V drop across it at the charging current (3 Ω for 400 mA, 6 Ω for 200 mA).

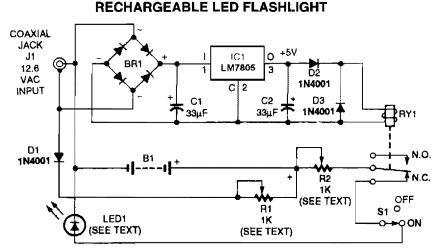

ELECTRONICS NOW

Fig. 13-2


This flashlight is useful for applications where night vision and/or darkness adaptation must be maintained. It uses an HLMP8150 T4 LED with a wavelength of 637 nm. This schematic is for the flashlight module. When the battery pack consisting of the four NiCad cells is fully charged (and there is no voltage at J1), 4.8 Vdc flows through trimmer potentiometer R2, the normally closed contact of relay RY1, and push-on/push-off power switch A1. Trimmer R2 limits the current flowing through LED1. Switch S1 can turn LED1 on and off when the battery is not being charged.

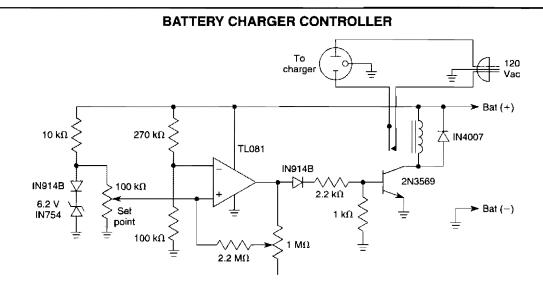

WILLIAM SHEETS

Fig. 13-3

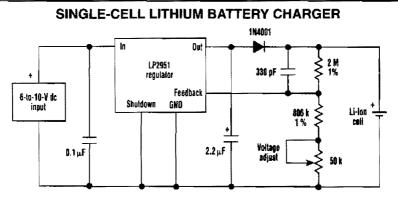When the battery voltage is low, the TL081 comparator produces a high output, turning on the 2N3569 relay driver. As the battery voltage approaches the set point, the relay driver is cut off, opening the 120-Vac supply.




ELECTRONIC DESIGN

Fig. 13-4

An LP2951 regulator was chosen for this single lithium cell-charging circuit for its built-in current-limiting capability. In addition, the regulator's output voltage is extremely stable, which is a prerequisite for lithium battery charging. This figure details an example circuit designed to recharge a single cell. The required output set voltage was specified as 4.200 V (± 0.025 V) with a maximum charging current of about 150 mA.

An LP2951 regulator was selected for two reasons. One is that its built-in current limiter holds the maximum current to 160 mA (typical). The other is because the output voltage can be very accurately set to 4.200 V, thanks to the regulator's stable internal bandgap reference.


The 1.23-V reference appears between the feedback pin and ground, which causes a precise current to flow in the output resistive-divider string. The amount of current flowing in these resistors determines (sets) the charger output voltage that appears across the battery terminals. Large-value resistors keep the battery drain below 2 μ A when the dc input is removed (a customer requirement). A trimming potentiometer sets the output to 4.200 V. It must be adjusted when the battery isn't connected to the charger output. A blocking diode is required at the LP2951's output to prevent current from flowing out of the battery and back into the output when the dc-input source is removed. Because the diode is in series with the output, the minimum input-output voltage differential required for this circuit to operate is about 1.5 V.

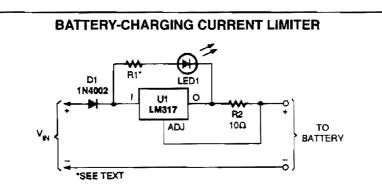

POPULAR ELECTRONICS

Fig. 13-5

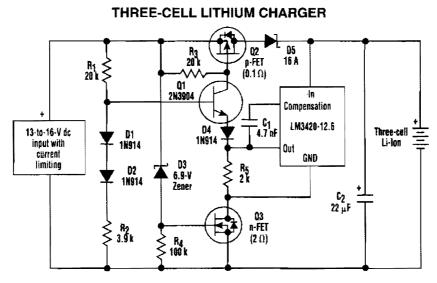
This circuit uses an LM317 as a current regulator to limit charging current to a lead-acid battery. R2 should produce a 1.2-V drop at the desired limiting value of charging current.



ELECTRONIC DESIGN

Fig. 13-6

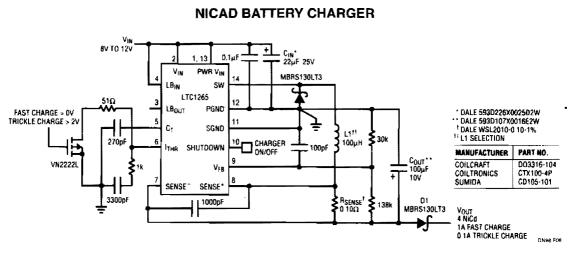This 3-A, three-cell charging circuit for lithium batteries includes a built-in on/off switch made up of Q3, R4, and D3. When a dc input is present, D3 turns on Q3, which allows current to flow through the LM3411 and Q1. If dc voltage is removed, Q3 turns off, cutting battery drain to zero.




LINEAR TECHNOLOGY

The LTC1265 is configured as a battery charger for a four-NiCad stack. It has the capability of performing a fast charge of 1 A, a trickle charge of 100 mA, or the charger can be shut off. In shut-off, diode D1 serves two purposes. First, it prevents the LTC1265 circuitry from drawing battery current and second, it eliminates "back powering" the LTC1265, which avoids a potential latch condition at power up.

Fig. 13-7

BACKUP BATTERY MONITOR/CHARGER/ALARM

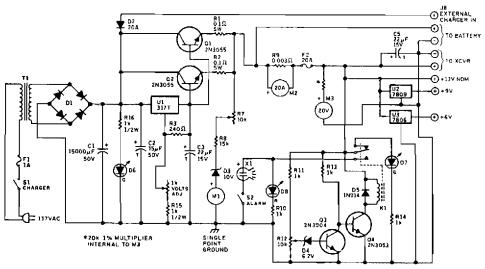

73 AMATEUR RADIO TODAY

Battery Condition Meter Calibration Fig. 13-8

Lead-Acid Battery		Lead Calcium Battery	
Color	Voltage	Color	Voltage
Red	11.6 and below	Red	11.6 and below
Yellow	11.6 to 12.0	Yellow	11.6 to 12.0
Green	12.0 to 13.8	Green	12.0 to 13.5
Red	13.8 and higher	Red	13.5 and higher

Charging voltage is constant at the normal full-charge level, so the charging current drops as full charge is approached, and full charge is maintained with a trickle current. The charging voltage can be adjusted between approximately 10 and 15 Vdc to accommodate lead-acid (13.8 V) or lead-calcium (13.2 V, 13.5 V maximum) deep-cycle storage batteries.

A separate connection is provided so that an external charger can be used when greater than 3 A is needed to charge a partially discharged battery. Internal circuitry will maintain the charging voltage to the battery at the nominal full-charge voltage level, regardless of the voltage supplied by the external charger, which will be 2 V or more greater than that applied by the regulator to the storage battery. Warning: do not fast-charge deep-cycle storage batteries!


A pair of meters calibrated to indicate 20 Vdc and 20 Adc full-scale monitor voltage and current when battery power is used.

A separate, suppressed zero, expanded-scale meter calibrated over the range of about 10 to 15 Vdc allows immediate and constant indication of the state of charge of the station's backup battery. This meter scale is calibrated in bands of red, yellow, and green, as explained in the table. The narrow yellow segment is based on the assumption that solid-state transceivers might not operate properly below +12 Vdc. The internal power supply is used to calibrate this meter. A DMM should be used for greatest accuracy.

BACKUP BATTERY MONITOR/CHARGER/ALARM (Cont.)

An alarm circuit is included to indicate when the battery has been discharged by 60 percent to the 11.6-Vdc level. When battery voltage is above 11.6 V, the green LED will be illuminated; when voltage fails to 11.6 V, the green LED goes out and the red LED lights. A piezo audible alarm sounds at this low-voltage level unless silenced by the toggle switch controlling it.

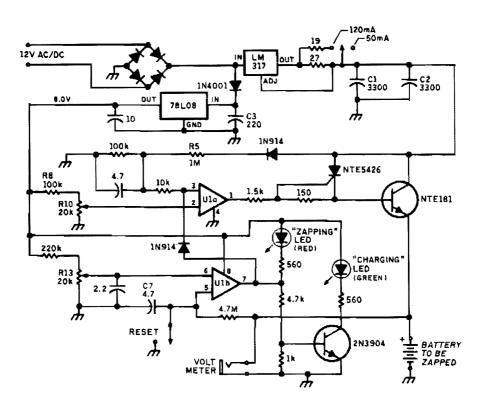A pair of fixed three-terminal regulators are included to provide +9 and +6 Vdc.




NICAD CHARGER/ZAPPER

73 AMATEUR RADIO TODAY

Flg. 13-9

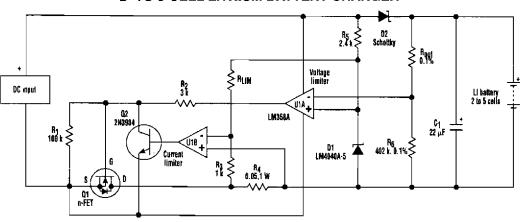The NiCad charger/zapper has a built-in charger and zapper circuit to clear shorted NiCads. This circuit delivers a high-current pulse to trim out internal shorts.




2- TO 5-CELL LITHIUM BATTERY CHARGER

ELECTRONIC DESIGN

Fig. 13-10

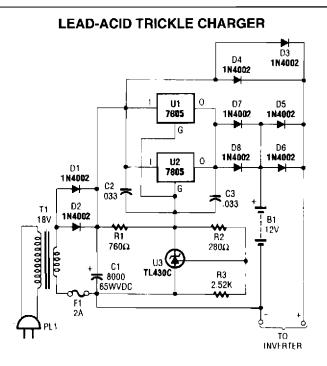A more generally applicable circuit-design concept for recharging lithium batteries could easily accommodate different cell types and various numbers of cells. That's because both the charger output-voltage set point and current limit, or maximum charging current, can be adjusted by simply changing a resistor.




POPULAR ELECTRONICS

Fig. 13-11

This lead-acid battery trickle charger can be used as a stand-alone circuit (for alarm systems and such) or combined with the circuit in the figure to create an emergency lighting system.

NICAD BATTERY CHARGER

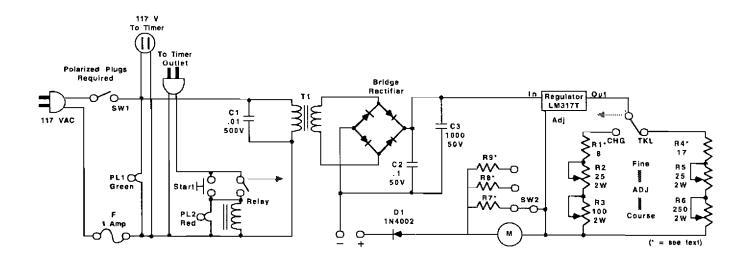

73 AMATEUR RADIO TODAY

Fig. 13-12

This circuit has a current regulator and uses an external timer to control the charging rate.

.


14

Battery Monitor Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Battery Monitor Battery Butler Undervoltage Indicator for Single Cell Battery Charger Probe Low-Battery Circuit Battery Charge Indicator Battery Status Indicator Lithium Memory Backup Replacement Battery-Condition Indicator for 12-V Batteries

BATTERY MONITOR

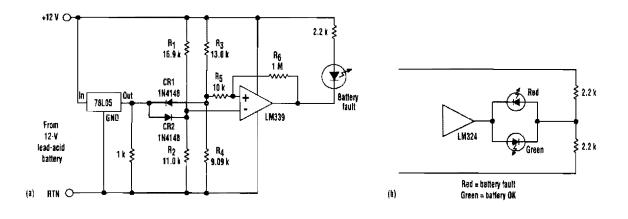

ELECTRONIC DESIGN

Fig. 14-1


One typical application for the detector involves monitoring a lead-acid battery. It indicates a fault when the battery voltage is outside an 11- to 14-V window. Because the circuit is powered by the battery, the input and reference were switched to keep the comparator inputs within its common-mode range.

The circuit's reference is 5.0 V. The resistor values in divider, R1/R2 were selected to produce 5.5 V at the inverting input when the battery voltage is 14.0 V. Divider R3/R4 is set to produce 4.5 V at the noninverting input when the battery voltage is equal to 11.0 V.

When the battery voltage is within the window, the noninverting input is more positive than the inverting input which is clamped at 4.5 V by CR2, the noninverting input continues below that, the comparator's output goes low, and the LED turns on. When the battery voltage rises above 14 V, the noninverting input is clamped at 5.5 V by CR1, the inverting input continues above that, the comparator output again goes low, and the LED turns on. Resistors R5 and R6 show that hysteresis might be added to this circuit in a conventional manner.

If an op amp, such as an LM324 is used as the comparator, two LEDs can be implemented. The green LED will turn on when the battery voltage is within the window, and the red LED turns on when the battery voltage is outside the window.


BATTERY BUTLER

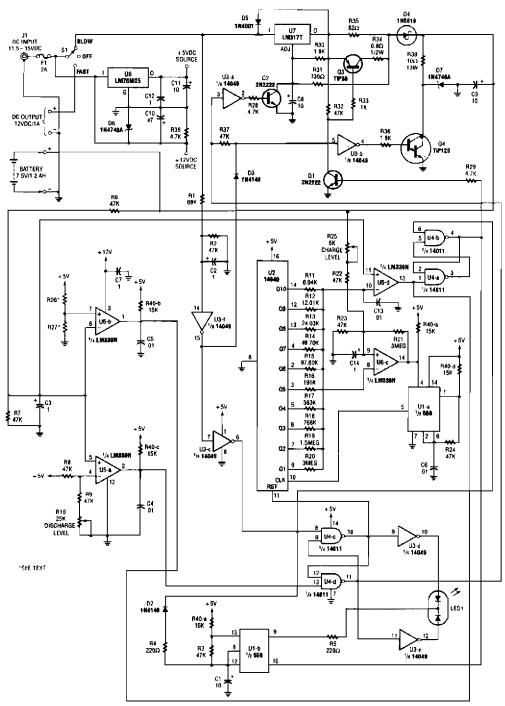

BATTERY BUTLER (Cont.)

The battery butler solves the common problems associated with the maintenance and operation of NiCad batteries. The battery butler, by initially discharging a NiCad battery to a preset point, reduces the possibility of the "memory" effect occurring. Once discharged, a battery is then usually charged at 25% and reduce the internal cell pressure increase by 40% or more. Once the battery is fully charged, a trickle charge is provided to maintain the battery in a fully charged state. The battery butler circuit can be bypassed, and the existing fast-charger used, if needed.

UNDERVOLTAGE INDICATOR FOR SINGLE CELL

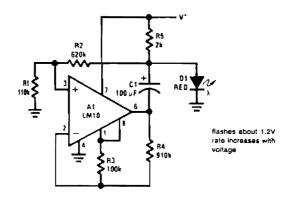

NATIONAL SEMICONDUCTOR


When operating with a single cell, it is necessary to incorporate switching circuitry to develop sufficient voltage to drive the LED. A circuit that accomplishes this is drawn in the figure shown. Basically, it is a voltage-controlled asymmetrical multivibrator with a minimum operating threshold given by:

$$V_{\rm TH} = \frac{R_4 \ (R_1 + R_2)}{R_1 \ (R_3 + R_4)} \ V_{\rm REF}$$

Above this threshold, the flash frequency increases with voltage. This is a far more noticeable indication of a deteriorating battery than merely dimming the LED. In addition, the indicator can be made visible with considerably less power drain. With the values shown, the flash rate is 1.4 sec -1 at 1.2 V with 300- μ A drain and 5.5 sec -1 at 1.55 V with 800- μ A drain. Equivalent visibility for continuous operation would require more than 5-mA drain.

Fig. 14-3

BATTERY CHARGER PROBE

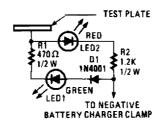


POPULAR ELECTRONICS

This battery-charger probe can keep you from damaging batteries or yourself by testing to see if the charger is already on and/or connected improperly.

To use the probe, the positive cable clamp is first connected to the positive battery terminal. Then, the test plate is touched to the negative terminal of the battery. If the battery is connected properly, current will pass from the test plate through R1, LED1, D1, the negative charger, and into the positive side of the batteries. If LED1 (the green LED) lights, you can clamp on the negative lead and turn on the charger.


If the terminals are reversed, current will flow in the opposite direction, causing LED2 to light, warning you of danger. When the cable is reversed, D1 protects LED1 from excessive reverse voltage. If that happens, immediately turn the power off, and right the cable connections. Finally, if the battery charger is on, both LEDs will light because chargers actually produce pulsating dc and rely on the battery to act as a filter.

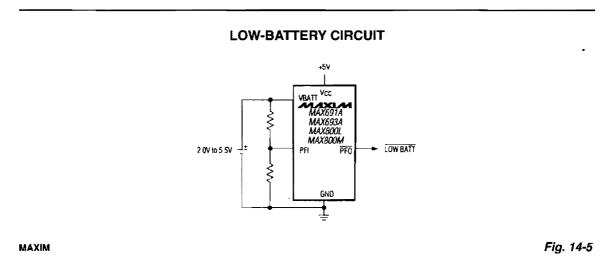

A Maxim MAX691A series IC allows low-battery detection.

Fig. 14-4

BATTERY CHARGE INDICATOR

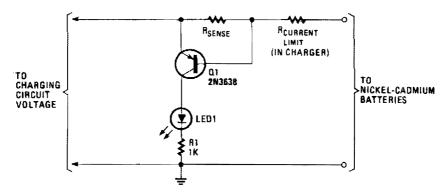


RADIO-ELECTRONICS

Fig. 14-6

When a battery is charging, a voltage drop across R_{SENSE} causes Q1 to conduct, and lights LED1. R_{SENSE} should be chosen as follows:

$$R_{\text{SENSE}} \text{ (ohms)} = \frac{0.65}{I_{\text{CHARGE}} \text{ (amps)}}$$

BATTERY STATUS INDICATOR

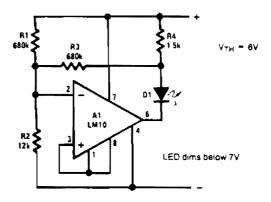


NATIONAL SEMICONDUCTOR

Fig. 14-7

In battery-powered circuitry, there are some advantages to having an indicator to show when the battery voltage is high enough for proper circuit operation. This is especially true for instruments that can produce erroneous data.

The battery status indicator is designed for a 9-V source. It begins dimming noticeably below 7 V and it extinguishes at 6 V. If the warning of incipient battery failure is not desired, R3 can be removed and the value of R_1 is halved.

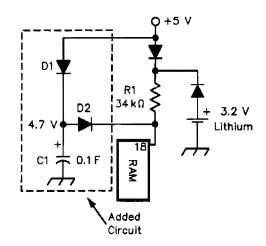LITHIUM MEMORY BACKUP BATTERY REPLACEMENT




QST

Fig. 14-8

Physically very small high-capacitance capacitors are available for memory backup. Here, a 0.1-F (100,000 μ F) capacitor and two diodes replace the lithium battery. The lithium battery can be retained as well, providing double backup.

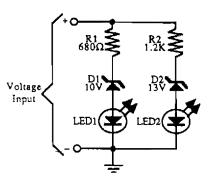BATTERY-CONDITION INDICATOR FOR 12-V BATTERIES



McGRAW-HILL

Fig. 14-9

A simple battery condition indicator. Choose the Zener diodes to provide a "window" for over/under voltage indication.


15

Bridge Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Single-Supply Bridge Amplifier Wheatstone Bridge Bridge Amplifier with Low Noise Compensation

SINGLE-SUPPLY BRIDGE AMPLIFIER

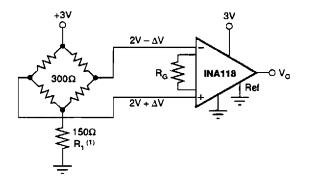

DESIRED GAIN	R . (Ω)	NEAREST 1% R ₆ (Ω)
1	NC	NC
2	50.00k	49.9k
5	12.50k	12.4k
10	5.556k	5.62k
20	2.632k	2.61k
50	1.02k	1.02k
100	505.1	511
200	251.3	249
500	100.2	100
1000	50.05	49.9
2000	25.01	24.9
5000	10.00	t0
10000	5.001	4.99

NOTE: (1) R, required to create proper common-mode voltage, only for low voltage operation — see text.

BURR-BROWN


The INA118 can be used on single-power supplies of ± 2.7 to ± 36 V. The figure shown is a basic single-supply circuit. The output Ref terminal is connected to ground. Zero differential input voltage will demand an output voltage of 0 V (ground). Actual output voltage swing is limited to approximately 35 mV above ground, when the load is referred to ground as shown. The typical performance curve "Output Voltage vs. Output Current" shows how the output voltage swing varies with output current.

With single-supply operation, $+V_{IN}$ and $-V_{IN}$ must both be 1.1 V above ground for linear operation. You cannot, for instance, connect the inverting input to ground and measure a voltage connected to the noninverting input.

To illustrate the issues affecting low-voltage operation, consider the circuit in the figure. It shows the INA118, operating from a single 3-V supply. A resistor in series with the low side of the bridge ensures that the bridge output voltage is within the common-mode range of the amplifier's inputs.

Fig. 15-1

WHEATSTONE BRIDGE

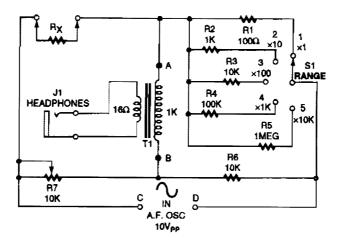

POPULAR ELECTRONICS


Fig. 15-2

This circuit can be used to measure resistances. R7 is calibrated and fitted with an indicator dial, then:

$$\frac{R_x}{(R_1 \text{ through } R_5)} = \frac{R_7}{R_6} \text{ or } R_x = \frac{R_7}{R_6} \times (R_1 \text{ through } R_5)$$

A frequency of 1 kHz for the audio oscillator is usually used.

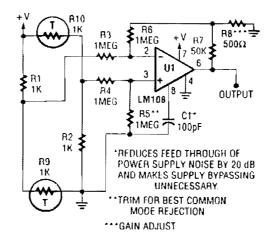BRIDGE AMPLIFIER WITH LOW NOISE COMPENSATION



POPULAR ELECTRONICS

Fig. 15-3


16

Buffer Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Unity-Gain ADC Buffer HI-Z Microphone Buffer Amplifier Wideband General-Purpose Buffer ADC Buffer Single-Supply ac Buffer Amplifier Analog Noninverting Switched Buffer Voltage Follower Simple Bidirectional Buffer Design Buffer for A/D Converters

UNITY-GAIN ADC BUFFER

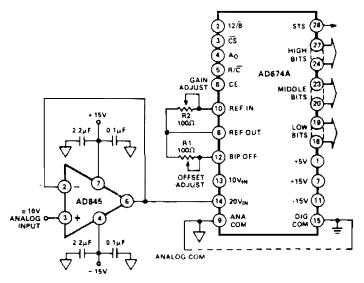


ANALOG DEVICES

Fig. 16-1

This buffer is suitable for ADCs of 12 bits with conversion times of 5 μ s or greater. The wide bandwidth of the AD845 ensures a low output impedance at higher frequencies in the voltage follower (buffer) configuration.

HI-Z MICROPHONE BUFFER AMPLIFIER

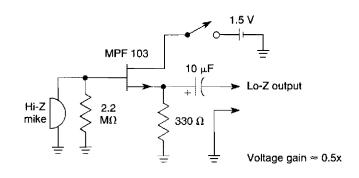


WILLIAM SHEETS

Fig. 16-2

A low impedance output from a high-Z microphone can be obtained with this circuit. No voltage gain is obtained, but a power gain is obtained because the output impedance is much lower (300 Ω), with -6-dB voltage gain.


WIDEBAND GENERAL-PURPOSE BUFFER

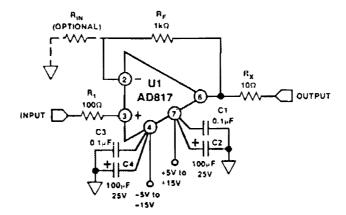

ANALOG DEVICES

Fig. 16-3

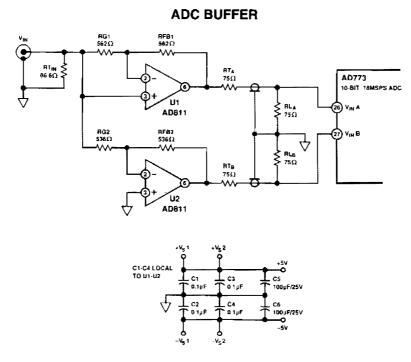This circuit has unity gain and response up to 70 MHz. U1 is an Analog Devices AD817.




ANALOG DEVICES

Fig. 16-4

Useful for driving high-speed, 10-bit ADCs, this circuit was developed to drive an 18-MSPS 10-bit ADS. It works from ± 5 -V supplies.

SINGLE-SUPPLY ac BUFFER AMPLIFIER

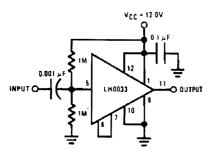


This buffer might be used with a single supply without special considerations. The input is dc biased to mid-operating point and is ac coupled. Its input impedance is approximately 500 k Ω at low frequencies. Note that for dc loads referenced to ground, this quiescent current is increased by the load current set at the input dc bias voltage.

NATIONAL SEMICONDUCTOR

Fig. 16-5

ANALOG NONINVERTING SWITCHED BUFFER

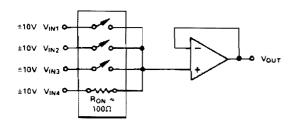


Here is noninverting solution.

ANALOG DEVICES


Fig. 16-6

VOLTAGE FOLLOWER

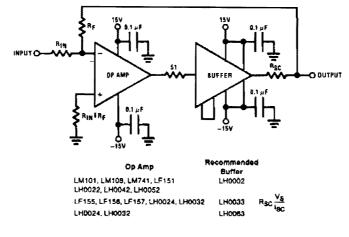

NATIONAL SEMICONDUCTOR


Fig. 16-7

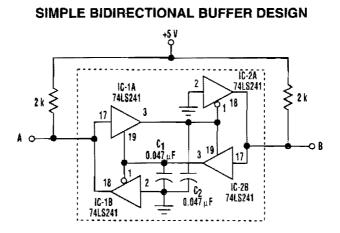

ELECTRONIC DESIGN

Fig. 16-8

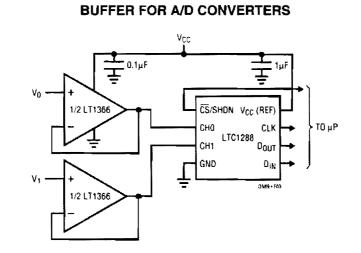This circuit shown in the figure uses two 74LS241s. When both input/output lines are high, IC-1A and IC-2B turn on, and C1 and C2 are charged to high voltage. Meanwhile, IC-1B and IC-2A are off to prevent a logic "1" latch.



LINEAR TECHNOLOGY

Fig. 16-9

This circuit uses an LT1366 driving an LTC1288 two-channel micropower A/D. The LTC1288 can accommodate voltage references and input signals equal to the supply rails. The sampling nature of this A/D eliminates the need for an external sample-and-hold, but might call for a drive amplifier because of the A/D's 12- μ s settling requirement. The LT1366's rail-to-rail operation and low-input offset voltage make it well suited for low-power, low-frequency A/D applications. In addition, the op-amp's output settles to 1% in response to a 3-mA load step through 100 pF in less than 1.5 μ s.


17

Clock Circuits

 T_{he} sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Set Time Windows within a Clock Low-Frequency Clock

SET TIME WINDOWS WITHIN A CLOCK

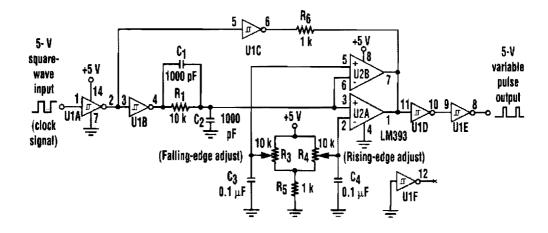

ELECTRONIC DESIGN

Fig. 17-1


At times, it is necessary to produce pulses of adjustable width and whose start times might vary with reference to a master clock. The input signal is inverted and buffered by U1A, while U1B and U1C reinvert the signal to produce square, buffered renditions of the input signal. Potentiometers R3 and R4 set references for the comparators.

The input polarity of U2A keeps its output transistor turned on until the voltage at the noninverting input exceeds the reference set by R4 (the rising edge adjustment). When this reference voltage is exceeded, the output transistor is turned off and the output signal is pulled up via $\dot{R6}$. Meanwhile, the input polarity of U2B keeps its output transistor turned off until the voltage at the inverting input exceeds the reference set by R3 (the falling edge adjustment). When this reference voltage is surpassed, the output transistor of U2B is turned on, pulling the output signal low through the wired-OR configuration of U2. The output of U2 is then double-inverted and buffered by U1D and U1E. What results is a pulse whose start time (rising edge) can be adjusted by R4, and whose stop time (falling edge) can be adjusted by R3.

The output of the comparators is pulled up to the input waveform through resistor R6 to U1C. This prevents the comparators from switching during the low cycle of the input waveform, regardless of the positions of R3 and R4. This has the effect of "locking out" changes during the low period of the input signal, and would probably require additional logic if it were done strictly in the digital domain.

The circuit, with the component values shown, works well between about 50 and 150 kHz.

LOW-FREQUENCY CLOCK

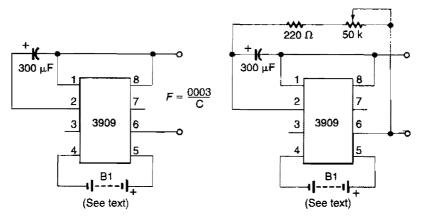

ELECTRONICS NOW



The LM3090 is an LED flasher IC that is designed to oscillate at low frequencies. The clock output of the first circuit can be changed by changing the value of the capacitor, and the second circuit lets you adjust the frequency with the trimmer. B1 can be one or two alkaline 1.5-V cells. The LM3909 can supply up to 45-mA pulses at greater than 2 V.


18

Computer-Related Circuits

 ${
m The}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

> RS-422 to RS-232 Converter Printer Port PC Password Protector Key Wireless RTS with Data **Microprocessor Supervisory Circuit** Computer-Powered RS-232 +12-V Flash Memory Programming Supply **EEPROM Programming Doubler Circuit** Monitor Power Saver for Computers

RS-422 TO RS-232 CONVERTER

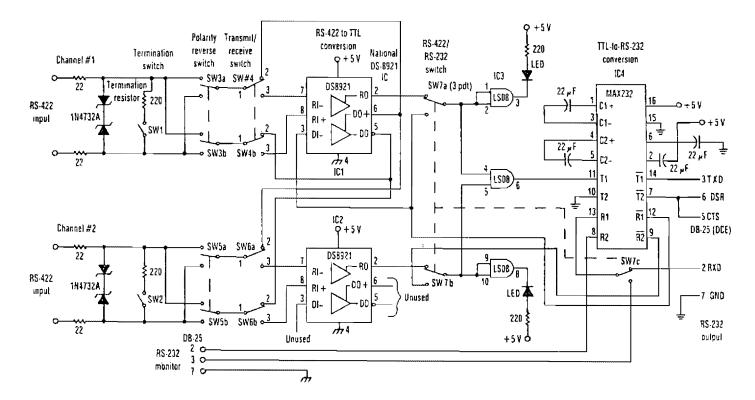


ELECTRONIC DESIGN

Fig. 18-1

The circuit supplies two LEDs for visual indication of line activity and terminating resistors when needed. The 220- Ω resistors and 5-V zeners at the RS-422 line inputs supply circuit protection.

Switch SW7 allows the circuit monitor both transmitted and received signals when tee-connected into an RS-232 line. One function of this optional feature is the ability to test a software-locking device that connects to the COM1 port on an IBM PC.

PRINTER PORT

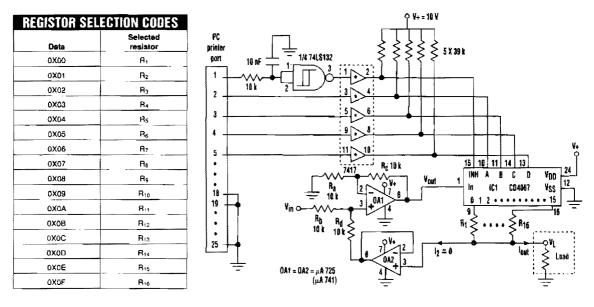

ELECTRONIC DESIGN

Fig. 18-2

A 16-step programmable current generator can be modified so that it's controllable by a printer port. This is done by switching the resistor connected between the output of the generator's OA1 op amp and the input of OA2. The CMOS single 16-channel analog multiplexer (IC1) chooses one resistor at a time, in accordance with the code sent by the printer port through four of its eight data-output lines (pins 2 to 9). In addition, one control line (pin 1) is used to enable the operation. As a result, 16 outputs can be selected by a 4-bit word (the table shows the relationship between data word and selected resistor).

The following must be fulfilled in order for the circuit to work as a true current generator:

$$R_2 \times R_d - R_h \times R_c = 0$$

The smaller the resistors' tolerance (especially R1 through R16), the greater the output resistance of the generator.

Because the OA2 is connected as a repeater, the current $I_2 = 0$, and only the load current flows through one of the R1 through R16 resistors. Therefore:

$$I_{\rm out} = \frac{V_{\rm out}}{(R_{\rm x} + R_{\rm op})}$$

PRINTER PORT (Cont.)


where $V_{out} = V_{in}$; X = 1...16; and $R_{on} \le 150 \Omega$ (for $V_{DD} = 10 \text{ V}$) is the resistance of one analog switch (CD4067) in conduction.

Therefore, the values of resistors R_1 through R_{16} can be inferred from the needed currents:

$$R_{\rm x} = \left(\frac{V_{\rm in}}{I_{\rm out}}\right) - R_{\rm on}$$

The Turbo C++ program also controls the current through the load.


PC PASSWORD PROTECTOR

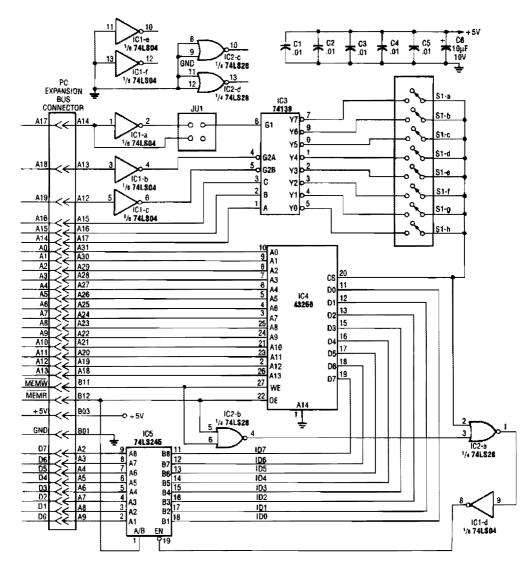

ELECTRONIC EXPERIMENTERS HANDBOOK

Fig. 18-3

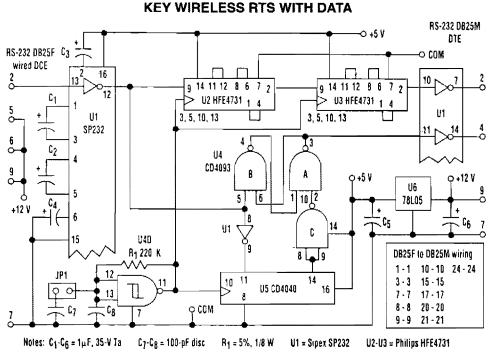IC4, a static RAM, is mounted in a "smart" built-in switch over circuitry. This retains SRAM contents when power is off. The rest of the circuitry consists of address decoding logic and jumper JU1, used to decode a 16K address space for the 32K static RAM. Software is necessary and this is contained in the original article (see reference).




ELECTRONIC DESIGN

Fig. 18-4

This simple keyer supplies both the RTS control and data delay needed to interface a digital radio with an RS-232, data-only system. It supports speeds to 19.2 kbits/s sync or async.

MICROPROCESSOR SUPERVISORY CIRCUIT

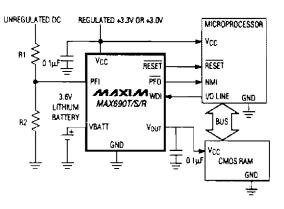


MAXIM

Fig. 18-5

This circuit provides a reset pulse during power up, down, or low-voltage battery back up, switching, a watchdog timer and a 1.25-V threshold detector for power failure or power fail warning, or to monitor another supply.

COMPUTER-POWERED RS-232

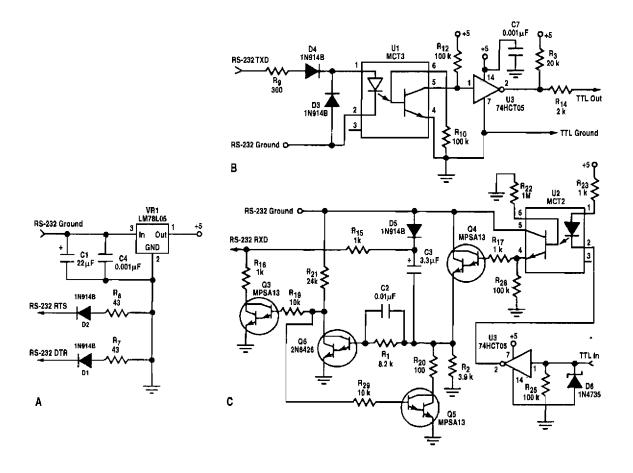

ELECTRONIC DESIGN

Fig. 18-6

COMPUTER-POWERED RS-232 (Cont.)


Commercializing battery-operated equipment that must interface to a computer via the RS-232 port runs into the problem of power consumption. To load the system batteries strictly to power the interface is unacceptable. An alternative is to let the computer that the device is connected to provide the interface's power. One snag is that the RS-232 specification doesn't have a power tap on the connector, but it does provide RTS and DTR (request to send and data terminal ready) signals that assert a negative voltage in their quiescent state.

Figure 18-6A shows a simple scheme of deriving a 5-V potential from the RTS and DTR signals. R7 and R8 and diodes D1 and D2 mix the return current to the RS-232 port so that the RTS and DTR drivers split the current drawn by the interface. This scheme, even from a laptop computer, can supply 12 mA to the interface. The only drawback is that the TTL device must be isolated from the computer's ground (earth ground) because the interface treats the RS-232 ground as a positive voltage.

A modified optocoupler system shifts the RS-232 level to TTL voltages (Fig. 18-6B). It will support up to 9600 bits/s. C3 is charged up to about 1 V less than the RTS voltage while the TTL line asserts a marking state. As the capacitor is charging, Q3 is biased into saturation, thus providing a negative voltage (with respect to RS-232 ground) to the RS-232 RXD line. When a spacing bit is driven from the TTL line, Q3 switches off and Q4 switches on. This biases Q4's emitter up to the RS-232 ground. That ground potential is summed with C3's charge to create an RS-232-compatible spacing signal (approximately 1 V less than a $-V_{\rm RTS}$).

The discharge rate on C3 is limited by R15 to prevent the signal sag from becoming a problem down to 110 bits/s. The C2/R1 time constant must be fairly close (within 4 times) to the C3/R15 time constant to ensure that Q3 turns off correctly.


+12-V FLASH MEMORY PROGRAMMING SUPPLY

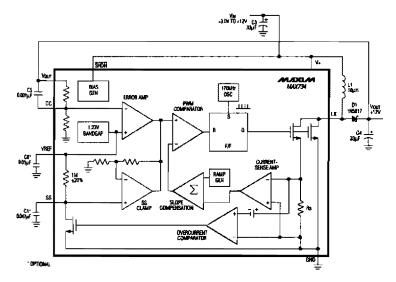

MAXIM

Fig. 18-7

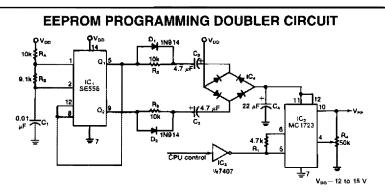The MAX734 can deliver up to 120 mA @12 V from a +5-V supply, using few external components. This supply can also be used for other applications than memory programming. A logic level is used for shutdown. Efficiency is about 85%.



ELECTRONIC DESIGN


Fig. 18-8

Even though electrically erasable PROMs offer the convenience of single-byte write and erase operations, the parts require a somewhat nonstandard programming voltage—21 V. A simple circuit that develops the appropriate voltage from a computer system's standard 12-to-15-Vdc supply, remedies the problem nicely. Moreover, it permits the programming voltage to be pulsed under the control of an external CPU.

As shown in the figure, the chip uses its complementary outputs, Q1 and Q2 to trigger a bridge rectifier through capacitors C2 and C3. Resistors R2 and R3 and diodes D1 and D2 limit the current and protect IC1 from spikes from C2 and C3. If required, the regulator will deliver up to 150 mA.

Circuit IC3 is an open-collector TTL gate whose output, when low, disables IC2 and causes it to put out 5 Vdc. The regulator delivers the 21-V programming pulse.

MONITOR POWER SAVER FOR COMPUTERS

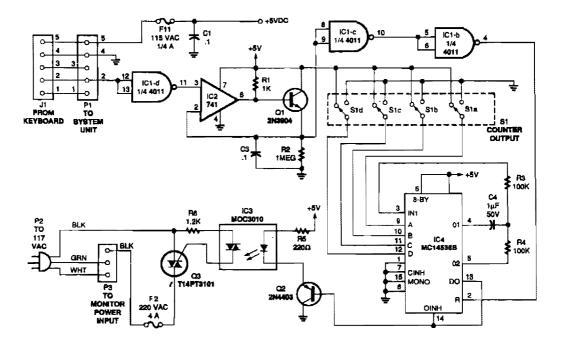

ELECTRONICS NOW

Fig. 18-9

The circuit monitors PC keyboard activity through five-pin DIN connector J1. When the user presses a key, the keyboard sends a series of negative-going pulses on pin 2. In conjunction with Q1 and C3, the op amp essentially functions as an integrator, which stretches the continually varying periods of the input pulses to a relatively constant period with a higher average dc value.

Inverters IC1-c and IC1-b buffer the peak detector's output to trigger IC4, an MC14536B programmable timer.


19

Continuity Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Short-Circuit Beeper Adjustable Continuity Tester Simple Audio/Video Cable Tester Audible Continuity Tester

SHORT-CIRCUIT BEEPER

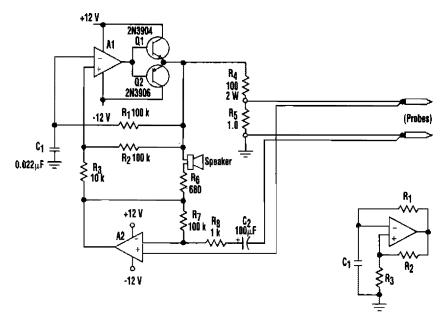

ELECTRONIC DESIGN

Fig. 19-1

This design offers a way to trace resistance in the milliohm range, right to a short between bridged traces beneath a solder mask. It simply translates resistance into an audible tone, which increases in pitch as the measured value approaches zero.

In the classic op-amp multivibrator (shown in the inset), oscillation frequency is determined not only by the R1/C1 time constant, but also by the hysteresis set by the R_2/R_3 resistance ratio. A1 in the main figure, with current boosters Q1 and Q2, is this same configuration.


Assuming a virtual ground at the output of A2, free-run frequency is about 1 kHz—quite audible through a tiny 8- Ω speaker. Q1 and Q2 deliver a ±10-V squarewave to R4, dumping a ±100 mA through a short circuit placed across the probe tips. R5 ensures that open circuit voltage never exceeds ±0.1 V.

A2 monitors the voltage between the probes. The differential input must have its own separate path to the probe tips to eliminate test lead resistance from the measurement. Miniature "zip-cord" sold as loudspeaker wire makes a tidy two-conductor test lead.

When the probes are open, A2's gain equals the R4/R5 divider loss, and the output of both amplifiers is identical. This has two effects: first, hysteresis is greatly increased and the frequency falls to a low growl; second, the loudspeaker that bridges the two in-phase outputs is effectively silenced.

The dead short across the probe tips will return nothing to A2 and the circuit will squeal at its nominal 1-kHz rate. Anything less than a perfect short produces some output from A2, increasing multivibrator hysteresis and lowering the pitch. The circuit has so much "leverage," and the ear is so sensitive to pitch changes in this range, that it's easy to resolve minute resistance differences.

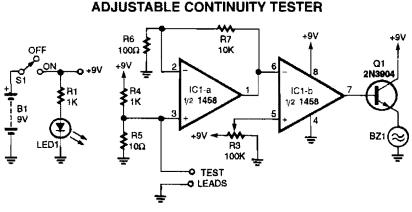
Any general-purpose op amp will suffice in this circuit—a couple of 741s or an equivalent dual.



ELECTRONICS NOW

Fig. 19-2

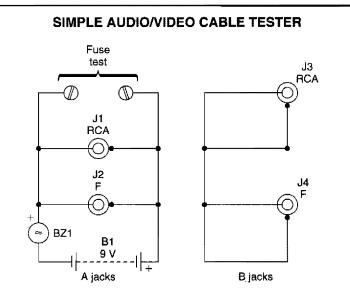A problem with most continuity testers is that the exact decision point (circuit resistance) between continuity and open is indefinite. This circuit allows setting of this point to a known resistance between 1 and 50 Ω .




ELECTRONICS NOW

Fig. 19-3

As simple as it looks, the audio/video cable tester tests cables while they are plugged in. You can flex them vigorously while listening to the built-in buzzer.

Simply plug the ends of the cable in the appropriate jack. Only one end of the cable need be plugged in for a complete short test; the other end is left free. If the buzzer sounds, there is a short circuit somewhere in the cable. If nothing is heard, test for an intermittent short by flexing the cable several times, particularly in the plug area of both the free and plugged-in ends.

AUDIBLE CONTINUITY TESTER

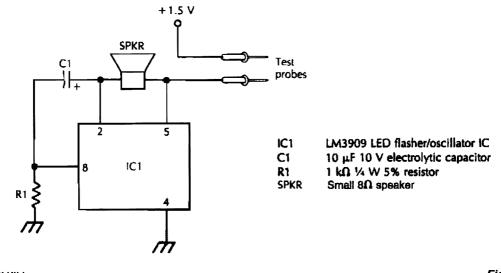

McGRAW-HILL

Fig. 19-4


20

Converter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

WWV Converter Simple HF Receive Converter 225-W, 15-V Output Converter 12-Bit DAC Driven Flyback Converter Sine-Wave Converter SCR Converter 5-V, 5-A Step-Down Converter Sync-to-Async Converter Differential Voltage-to-Current Converter Direct-Conversion 7-MHz Receiver Low-Frequency Converter Programmable Current-to-Voltage Converter Current-to-Voltage Converter with Boost Transistor Current-to-Voltage Converter for Grounded Loads Output-to-Current Converter


WWV CONVERTER

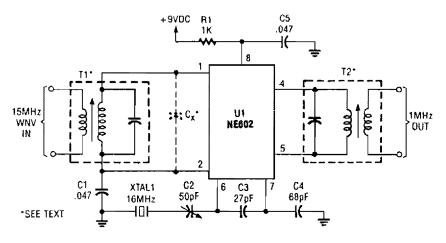

RADIO CRAFT

Fig. 20-1

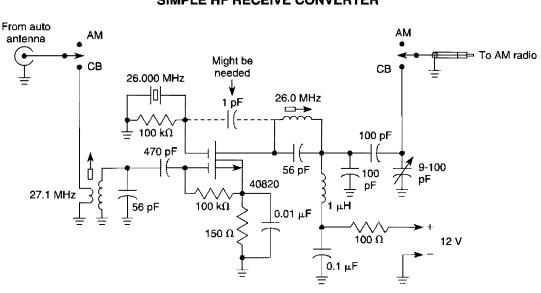This converter heterodynes the 15-MHz WWV signal with a 16-MHz oscillator so that it can be heard at 1 MHz on an AM broadcast receiver. T1 and T2 are a modified 10.7-MHz IF transformer and AM BC oscillator coil, respectively.




SIMPLE HF RECEIVE CONVERTER

WILLIAM SHEETS

Fig. 20-2

Designed for CB reception, this crystal-controlled converter uses one 40820 dual-gate MOSFET. The circuit will work with any crystal either 3rd overtone or fundamental, over 1 to 50 MHz.

225-W, 15-V OUTPUT CONVERTER

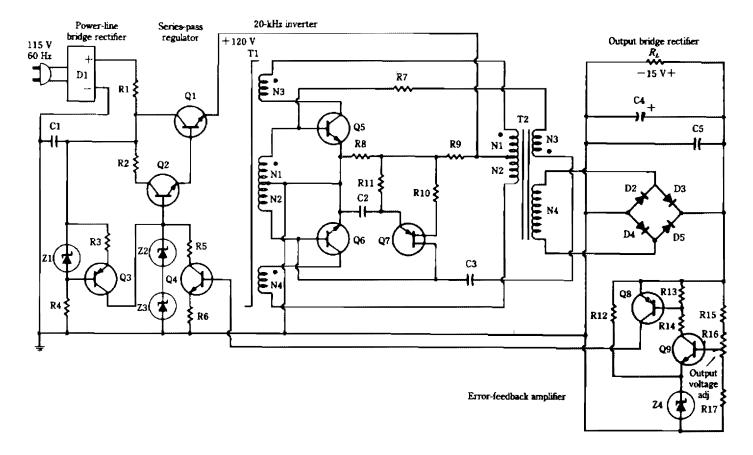

McGRAW-HILL



A converter designed to supply ±15 Vdc is shown. This converter is several times lighter in weight than an equivalent.

.

225-W, 15-V OUTPUT CONVERTER (Cont.)


C1 — 2500 μF, 350 V Electrolyic	Q1, Q5, Q6, — 2N6307
C2 — 0.1 µF Disc Ceramic	Q2, Q4 2N5052
C3 — 0.1 µF Paper	Q3 — 2N5345
C4 — 10 µF Electrolyic	Q7 — 2N4870
C5 — 0.25 μF Paper	Q8 — 2N3905
D1 — MDA-980-4 Bridge Rectifier Assembly	Q9 2N3903
D2, D3, D4, D5 — 1N5826, 20 V 15 A	

All Resistors in Ohms and 1/2 W Unless Otherwise Noted

T1 — Core — Magnetics Inc. 80623 — ¹/₂ D — 080
 N1, N2 — 20 Turns Each, No. 30 AWG (Bifilar)
 N3, N4 — 3 Turns Each, No. 20 AWG

T2 — Core — Arnold 6T 5800 D1 N1, N2 — 100 Turns Each, No. 20 AWG (Bifilar) N3 — 7 Turns No. 26 AWG N4 — 12 Turns Each, No. 12 AWG (No. 16 AWG, 3 in Parallel)

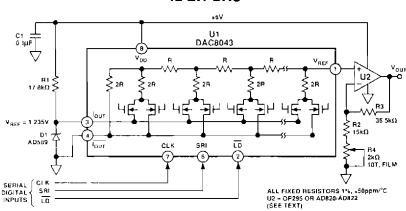- Z1 1N4733, 5.1 V
- Z2, Z3 1N4760, 68 V
- Z4 1N4736




12-BIT DAC

ANALOG DEVICES

Fig. 20-4

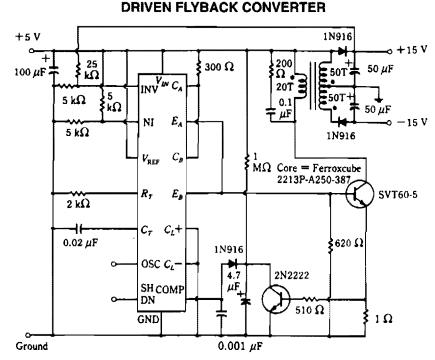
This circuit uses an Analog Devices DAC-8043 12-bit multiplying DAC. The output voltage will be $D/4096 \times V_{\text{ref}}$ where D is the numerical value of the digital input word (0 to 4095). V_{ref} is 1.235 volts in this circuit.



McGRAW-HILL

Fig. 20-5

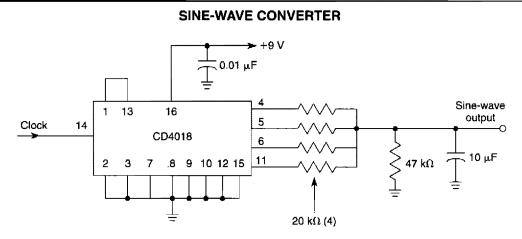
This circuit uses an SG1524 Silicon General regulating pulse width modulator and provides ± 15 V from a 5-V supply rail.



WILLIAM SHEETS

Fig. 20-6

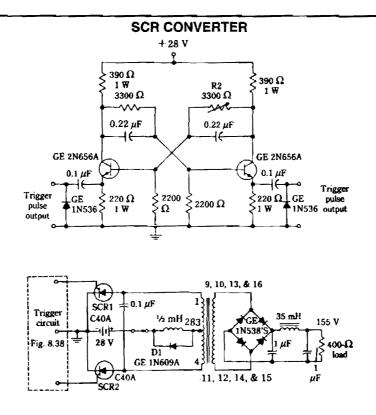
This circuit produces a sine wave with a low-frequency clock input. The clock rate should be 100 Hz or less.



McGRAW-HILL

Fig. 20-7

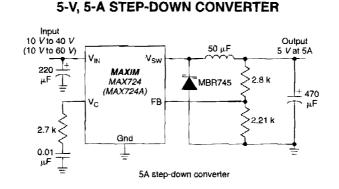Two SCR devices are used in a push-pull driver to convert 28 Vdc to 155 Vdc, using the transformer and bridge shown. A center-tapped transformer with 24 V:120 V could be used for 60-Hz applications. The trigger circuit supplies a push-pull drive signal.




МАХІМ

Fig. 20-8

This circuit is useful where power must be distributed by a higher (10 to 60 V) bus. The circuit reduces power dissipation and eliminates inefficient passive linear regulators. The switching frequency is in the 100-kHz region.

SYNC-TO-ASYNC CONVERTER

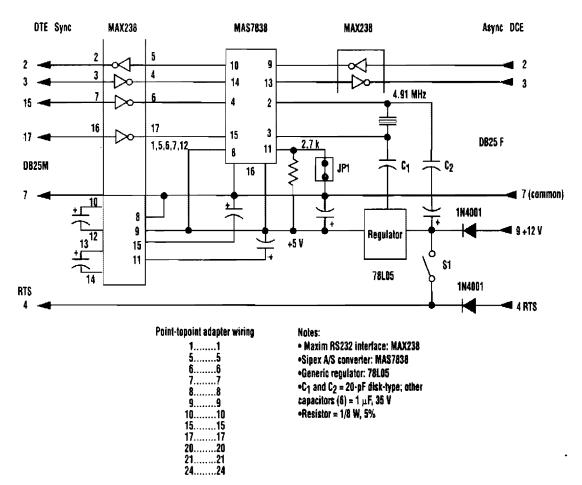


ELECTRONIC DESIGN

Fig. 20-9

This simple converter consists of two ICs and a voltage regulator. The Sipex MAS7838, which acts as the converter, selects the conversion speed to that of the synchronized data clock. It has internal switches and registers to perform the async-to-sync, or sync-to-async, conversion. The Maxim MAX238 provides the RS-232 drivers and receivers for interfacing with the data bus. These chips require a 5-Vdc power supply; a generic 78L05 reduces the +12 V at the DB25 pin 9 to the +5 V needed. A crystal frequency of 4.91 MHz is suitable for converting to 19.2 kbits or a sub-multiple (9.6, 4.8, 2.4, etc.). Two 1N4001 diodes protect the external RTS (ready to send) control circuitry if the RTS is enabled by S1. When JP1 is removed, the converter is transparent in the sync mode and no conversion will occur.

The completed unit is mounted atop a universal breakout adapter, and the control lines are jumpered according to the chart in the figure. The physical size is approximately $1 \times 2.25 \times 2.5$ inches and will easily plug into the DB25 socket on a synchronized data communications equipment (DCE) communication device.

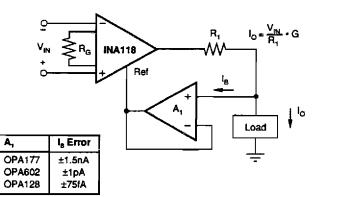DIFFERENTIAL VOLTAGE-TO-CURRENT CONVERTER




DESIRED GAIN	R _c (Ω)	NEAREST 1% R _g (Ω)
1	NC	NC
2	50.00k	49.9k
5	12.50k	12.4k
10	5.556k	5.62k
20	2.632k	2.61k
50	1.02k	1.02k
100	505.1	511
200	251.3	249
500	100.2	100
1000	50.05	49.9
2000	25.01	24.9
5000	10.00	10
10000	5.001	4.99

BURR-BROWN

Fig. 20-10

DIRECT-CONVERSION 7-MHz RECEIVER

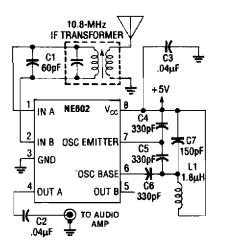


RADIO-ELECTRONICS

Fig. 20-11

An NE602 is used to mix signals in the 7-MHz range with an LO and to produce audio output.

LOW-FREQUENCY CONVERTER

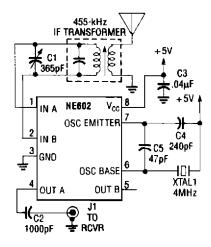


RADIO-ELECTRONICS

Fig. 20-12

This converter circuit translates the 350- to 500-kHz range to 4.35 to 4.50 MHz, enabling the frequency range to be received on a conventional shortwave receiver.

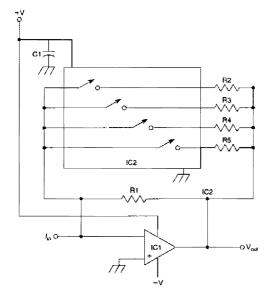PROGRAMMABLE CURRENT-TO-VOLTAGE CONVERTER




Programmable current-to-voltage converter permits you to electrically select from 16 resistor values using bilateral switches.

- IC1 741 op amp (or similar)
- IC2 CD4066 quad bilateral switch
- C1 $0.1-\mu F$ capacitor
- R1 10-k Ω , ¼-W 5% resistor
- R2 4.7-kΩ, ¼-W 5% resistor
- R3 2.2-k Ω , ¼-W 5% resistor
- R4 1.2-k Ω , ¼-W 5% resistor
- R5 100-Ω, ¼-W 5% resistor

McGRAW-HILL

Fig. 20-13

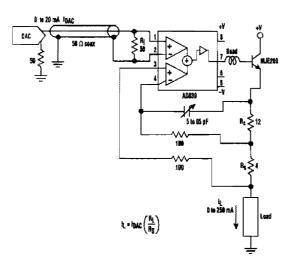CURRENT-TO-VOLTAGE CONVERTER WITH BOOST TRANSISTOR




ELECTRONIC DESIGN

Fig. 20-14

A transistor such as the MJE200 can be added to an Analog Devices AD830 to produce this current to voltage converter. Loads to 250 mA can be driven. The 5- to 65-pF trimmer is for compensation.

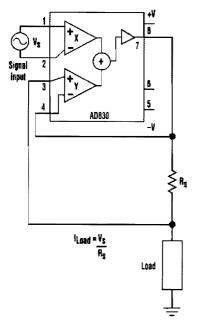CURRENT-TO-VOLTAGE CONVERTER FOR GROUNDED LOADS



This circuit uses an Analog Devices AD830 video difference amplifier. The circuit consists of two differential inputs. Unlike a conventional op amp, the AD830's output is nulled when the sum of the differences of the two inputs is zero.

The AD830's stated unity-gain bandwidth is 60 MHz, and the device is capable of driving up to ± 30 mA directly. The differential input voltage is limited to ± 2 V, while the maximum power supply is ± 15 V.


If more output current is desired, the AD830 can drive a bipolar transistor (such as an MJE200) directly. This will produce a one-sided output.

A ferrite bead can be placed on the base to prevent oscillation under some conditions. Compensation can be added by splitting R_s and adding a variable capacitor. A resistor can be positioned at the input to match the amplifier's input to a transmission line.

ELECTRONIC DESIGN

Fig. 20-15

OUTPUT-TO-CURRENT CONVERTER

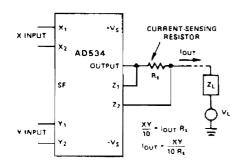

Occasionally, it is preferable to generate a current, rather than a voltage, output into the load. The availability of differential inputs allows this to be accomplished in any of the four basic modes.

If the output is to integrated, Z_L can be simple high-quality capacitor, unloaded by an op amp connected as a high-impedance follower. Note that, if desired, one side of a rest switch can be grounded.

The compliance constraint for this configuration, where $V_{\rm L}$ is an arbitrary common-mode potential, is:

$$|V_{\rm L} + I_{\rm OUT} (Z_{\rm L} + R_{\rm S})| \le 12 \text{ V}$$

ANALOG DEVICES


Fig. 20-16

21


Crystal Oscillator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

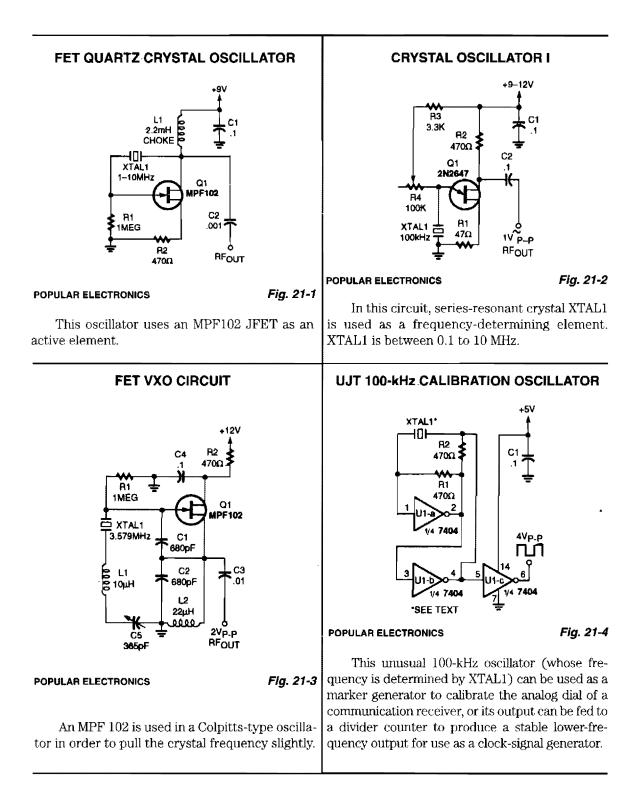FET Quartz Crystal Oscillator Crystal Oscillator I FET VXO Circuit UJT 100-kHz Calibration Oscillator Crystal Oscillator with FM Capability Crystal Oscillator II dc-Switched Crystal Oscillator Crystal Oscillator with Adjustable Frequency Frequency Doubler and Crystal Oscillator Crystal Oscillator III Colpitts Oscillator



CRYSTAL OSCILLATOR WITH FM CAPABILITY

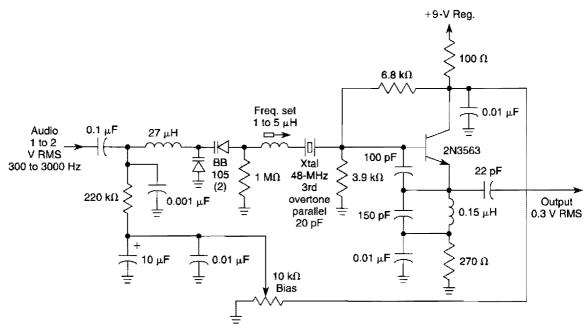


WILLIAM SHEETS

Fig. 21-5

This crystal oscillator produces a good FM signal that can be tripled to 146 MHz and produces a clean 5-kHz deviation signal for FM voice. The bias control is adjusted for cleanest audio while the 1-to 5- μ H coil is adjusted to set the oscillator frequency to the exact setting required.


CRYSTAL OSCILLATOR II

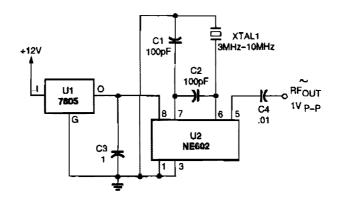

POPULAR ELECTRONICS

An NE602 can be used as a crystal oscillator.


Fia. 21-6

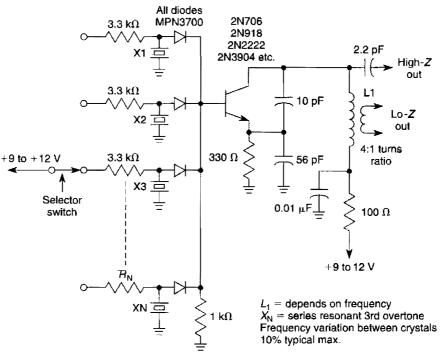


WILLIAM SHEETS

Fig. 21-7

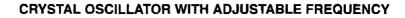This circuit is useful where several different crystal frequencies must be switched using a dc source. The values shown are typical for 40- to 60-MHz third-overtone crystals. Limitation on number of crystals depends on PIN diode capacitance and layout factors, but up to 5 or 10 crystals is possible.



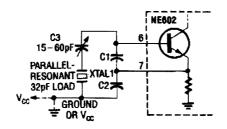


RADIO-ELECTRONICS

In this crystal oscillator circuit, C3 adjusts the frequency of the oscillator for exact netting. The crystal is a fundamental type, $C_1 = 100$ pF and $C_2 = 1000$ pF are typical.

Fia. 21-8

dc-SWITCHED CRYSTAL OSCILLATOR

FREQUENCY DOUBLER AND CRYSTAL OSCILLATOR

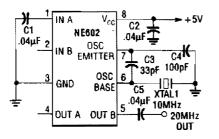


This frequency doubler produces a sine wave at twice the frequency of XTAL1. Notice that the output is taken only from OUT B (pin 5), while OUT A (pin 4) is left open.

RADIO-ELECTRONICS

RADIO CRAFT




CRYSTAL OSCILLATOR III

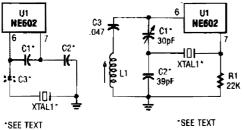

These circuits are for use with a crystal-controlled LO using the NE602. C1, C2, and C3 are for crystals in the 5-MHz region and are approximately chosen from

$$C_1 = \frac{100}{\sqrt{f_{\text{MHz}}}} \text{ pF}, C_2 = \frac{1000}{\sqrt{f_{\text{MHz}}}} \text{ pF}$$

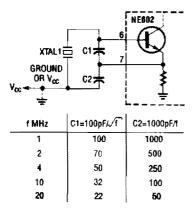C3 is for fine tuning the crystal frequency **Fig. 21-10** and will be 20 to 50 pF typically.



COLPITTS OSCILLATOR

Here: $L_1 \approx 7 \ \mu$ H/f, $C_1 \approx C_2 \approx C_3 \approx 2400 \ p$ F/f, where *f* is in MHz. In this circuit, the oscillator is free-running.

RADIO-ELECTRONICS




22

Current Source and Sink Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


Current Generator Voltage-Controlled Current Source Voltage-Controlled Current Sink Multiple Fixed Current Source

CURRENT GENERATOR

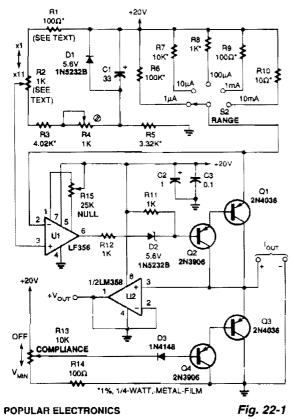

This circuit is useful for supplying constant current to test semiconductors. $V_{\rm OUT}$ from U2 reads the voltage across the load connected to $I_{\rm OUT}$. R13 adjusts the supply compliance from 1 to about 18 V.

VOLTAGE-CONTROLLED CURRENT SOURCE

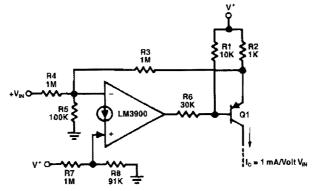


NATIONAL SEMICONDUCTOR

Fig. 22-2

A voltage-variable current source is shown in the figure. The transconductance is $-(1/R_2)$ as the voltage gain from the input terminal to the emitter of Q1 is -1. For $V_{\rm in} = 0$ Vdc, the output current is essentially 0 mA dc. Resistors R1 and R6 guarantee that the amplifier can turn OFF transistor Q1.

VOLTAGE-CONTROLLED CURRENT SINK

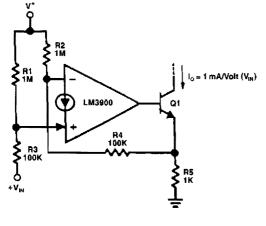


A voltage-variable current sink is shown in the figure. The output current is 1 mA per volt of $V_{\rm in}$ (as $R_5 = 1 \text{ k}\Omega$ and the gain is +1). This circuit provides approximately 0 mA output current for $V_{\rm in} = 0 \text{ V DCL}$.

NATIONAL SEMICONDUCTOR

Flg. 22-3

MULTIPLE FIXED CURRENT SOURCE

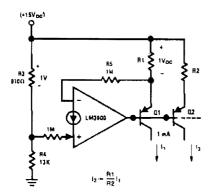

NATIONAL SEMICONDUCTOR

Fig. 22-4

A multiple fixed current source is provided by the circuit. A reference voltage (1 Vdc) is established across resistor R3 by the resistive divider (R3 and R4). Negative feedback is used to cause the voltage drop across R1 to also be 1 Vdc. This controls the emitter current of transistor Q1 and if we neglect the small current diverted into the (-) input via the 1-M Ω input resistor (13.5 μ A) and the base current of Q1 and Q2 (an additional 2% loss if the β of these transistors is 100), essentially this same current is available out of the collector of Q1.

Larger input resistors can be-used to reduce current loss and a Darlington connection can be used to reduce errors caused by the β of Q1.


The resistor, R2, can be used to scale the collector current of Q2 either above or below the 1mA reference value. 23

dc-to-dc Converter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Isolated dc-to-dc Converter dc-to-dc Converter I Ultra Low-Power dc-to-dc Converter for Personal Communications Products Negative Step-Up dc-to-dc Converter dc-to-dc Converter II


ISOLATED dc-to-dc CONVERTER

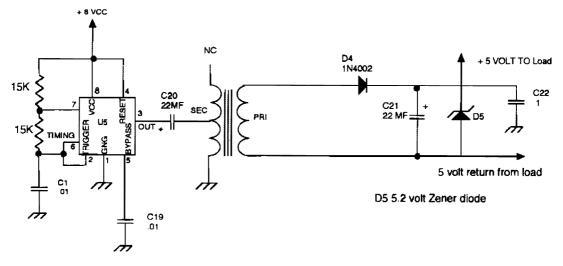

73 AMATEUR RADIO TODAY

Fig. 23-1

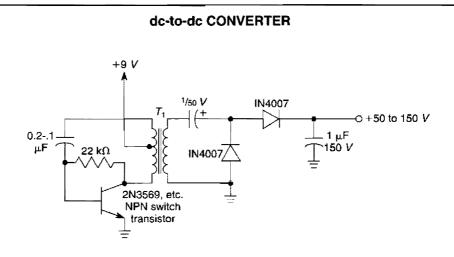A NE555 timer is used to drive a small transformer to change the 5- to 7-Vp-p output of the NE555 to a suitable value to drive a rectifier/Zener combination. This method is useful where a small isolated power source is needed.



WILLIAM SHEETS

Fig. 23-2

This converter should be useful where a few milliamperes of dc at a higher voltage than available supplies can deliver is needed. T1 is typically a 1 k Ω CT:10-k Ω transistor audio transformer. Depending on T1, about 50 to 150 Vdc can be obtained at a few milliamperes.


ULTRA LOW-POWER dc-to-dc CONVERTER FOR PERSONAL COMMUNICATIONS PRODUCTS 5 TO 7 CELL INPUT C1 15µF 12⁵V 0N L1 ViN CTX33-1 5V SHUTDOWN 120mA Vsw C3 OUTPUT C2 M8R0520L Ś 81 LTC1174CS8 33µF OFF 91k 6 8nF 20V FB PGM GND 30k C1 PANASONIC SP SERIES (201) 348-4630 C3 AVX TAJ SERIES (803) 956-0690 L1 COILTRONICS OCTAPAK (407) 241-7876

LINEAR TECHNOLOGY

Fig. 23-3


The LTC1174 step-down converter is designed specifically to eliminate noise at audio frequencies while maintaining high efficiency at low output currents. This circuit shows a 5-V, 120-mA output derived from 5 to 7 NiCad or NiMH cells. Small input and output capacitors that are capable of handling the necessary ripple currents help conserve space. In applications where shutdown is desired, this feature is available (otherwise short this pin to V_m).

The LTC1174's internal switch, connected between $V_{\rm in}$ and $V_{\rm sw}$, is current controlled at a peak of approximately 340 mA. Low peak switch current is one of the key features that allows the LTC1174 to minimize system noise compared to other chips that carry significantly higher peak currents, easing shielding and filtering requirements, and decreasing component stresses. Output current of up to 450 mA is possible with this device by connecting the 1 pgm pin to $V_{\rm in}$. This increases the peak current to 600 mA, allowing for a high average output current.

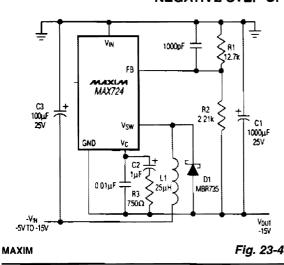

NEGATIVE STEP-UP dc-to-dc CONVERTER

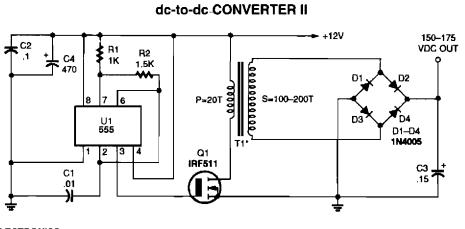A Maxim MAX724 is used in a step-up switching converter to provide $-15\mathchar`-$



POPULAR ELECTRONICS

Fig. 23-5

In this dc-to-dc converter, the 555 is used to produce a rising and collapsing field in T1's primary, generating a high voltage in T1's secondary winding. That voltage is then full-wave, bridge rectified by D1 through D4, and filtered by C3. T1 is an Amidon Associates EA-775-375E core and nylon bobbin, with #26 wire for the primary and #28 or #30 for the secondary. About 5 W of power is available.


24

Decoder Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

DTMF Decoder FM Stereo Decoder Typical NE567 Tone Decoder Circuit Video Line Decoder I Video Line Decoder II

DTMF DECODER

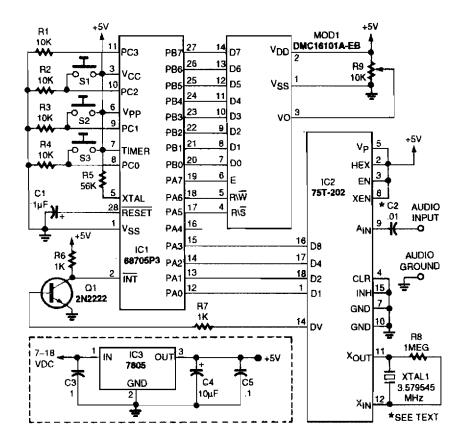


ELECTRONICS NOW

Fig. 24-1

This DTMF decoder uses a Motorola 68705P3 microcontroller and a 75T202 DTMF receiver (Silicon Systems, Inc.). An LCD module is used for the display (MOD1). Switch S1 is used to scroll the display, S2 clears the display, and S3 clears the memory.

FM STEREO DECODER

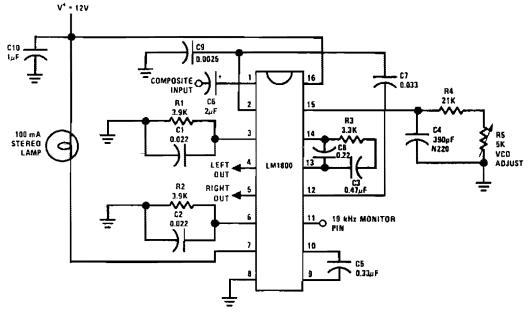


NATIONAL SEMICONDUCTOR

Fig. 24-2

Using an LM1800, this circuit takes composite baseband MPX input and recovers L7R audio channels. The VCO is set for 19 kHz (or 15.7 kHz for TV applications) or as needed.

TYPICAL NE567 TONE DECODER CIRCUIT

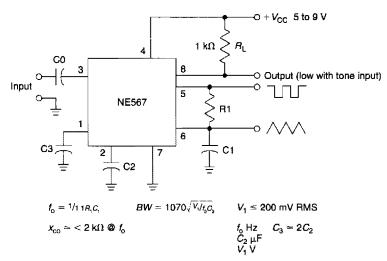


WILLIAM SHEETS

This circuit illustrates use of NE567 as a tone decoder.


Fig. 24-3

VIDEO LINE DECODER I

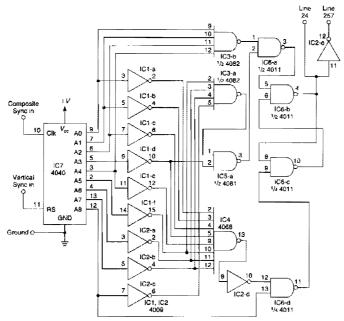

ELECTRONICS NOW

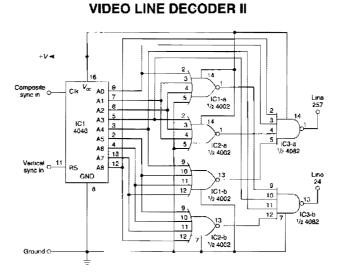This line decoder uses only one pin for the line indicator.



ELECTRONICS NOW

Fig. 24-5

This circuit will produce pulses useful for gating lines 24 and 257 of a video signal, but by changing the decoding logic, other lines can be decoded.


Fig. 24-4

25

Delay Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

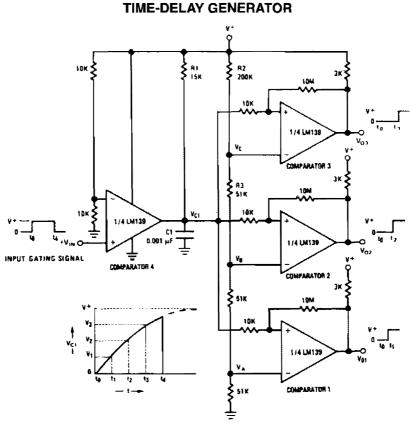
Time-Delay Generator Simple Time Delay Circuit



NATIONAL SEMICONDUCTOR

Fig. 25-1

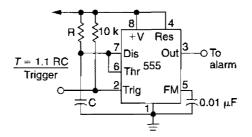This circuit uses a charging capacitor and three comparators to read the voltage across it.



SIMPLE TIME DELAY CIRCUIT

ELECTRONICS NOW

Rotating the potentiometer wiper will change the time delay from the 555 IC.

Fig. 25-2


26

Detector Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

High-Speed Peak Detector with Hold and Reset Controls Lock Detector Linearized RF Detector **Glitch Detector** VCR Video Detector Controller Grid-Leak Detector Negative Peak Detector **Double-Ended Limit Detector Positive Peak Detector** LM556 Timer Frequency Detector Single-Comparator Window Detector 15-kHz Tone Detector Crystal Radio Detector Switch Closure Circuit Air Flow Detector Low Drift Peak Detector Negative Peak Detector Positive Peak Detector 455-kHz AM Detector ac Noise Detector

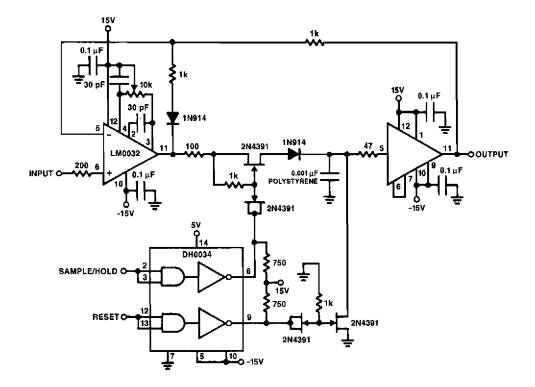HIGH-SPEED PEAK DETECTOR WITH HOLD AND RESET CONTROLS





NATIONAL SEMICONDUCTOR

Fig. 26-1

The LH0033 and LH0063 are useful in high-speed sample-and-hold or peak detector circuits because of their very high speed and low-bias-current FET input stages. The high-speed peak detector circuit shown could be changed to a sample-and-hold circuit simply by removing the detector diode and reset circuitry. For best accuracy, the circuit can be trimmed with the 10-k Ω offset adjustment pot shown. The circuit has a typical acquisition time of 900 ns, to 0.1% of the final value for the 10-V input step signal, and a droop rate of 100 μ V/ms. Even faster acquisition time can be achieved by reducing the hold capacitor value.

LOCK DETECTOR

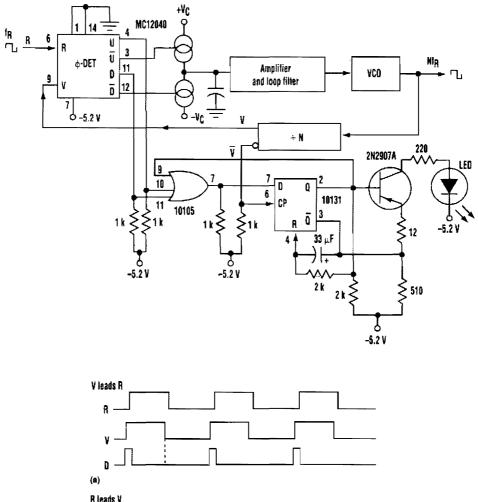

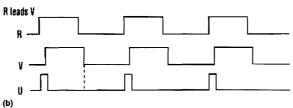

ELECTRONIC DESIGN


Fig. 26-2

LOCK DETECTOR (Cont.)

This PLL lock indicator not only can detect a "locked" or "off-of-lock" condition, but also even if a single pulse or transition has been missed.

When being sampled by the flip-flop, if the V signal leads the input reference signal R and the rising edge of R is lost, the D signal will remain high throughout the interval, allowing the flip-flop to be clocked high (Fig. 26-2A). If the R signal leads the V signal when the transition is missed, the rising edge of the V signal will trigger the D signal of the phase detector, causing the LED to blink (Fig. 26-2B).

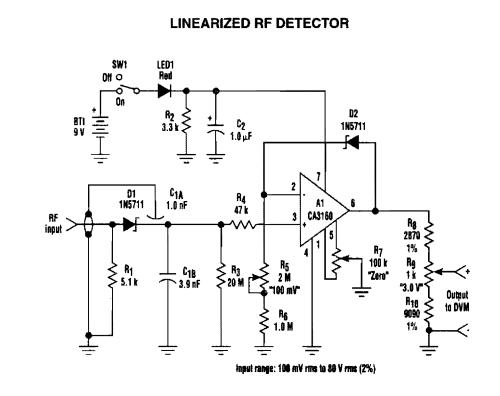
A "lock" detector often is used with a phase-locked loop (PLL) or synthesizer to indicate when the loop is phase-locked with an input signal. This circuit can be helpful, but single cycle skips usually will go undetected because of the presence of the low-pass filter.



ELECTRONIC DESIGN

Fig. 26-3

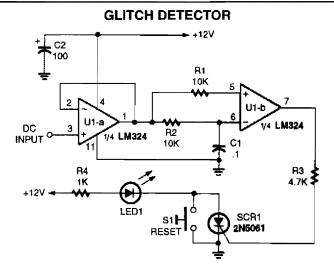
The circuit produces an extremely linear dc output for RF inputs between 80 mV rms and 4.0 mV rms. For inputs below 50 V rms, the dc output quickly drops to 0 V.



POPULAR ELECTRONICS

Fig. 26-4


In the circuit, two op amps (half of an LM324 quad op amp) and an SCR are direct coupled in a dcvoltage monitoring circuit. Op-amp U1-a is configured as a voltage follower, which feeds the bridged inputs of the second op amp, U1-b. A resistor/capacitor combination (R2/C1) connected to the negative input of UJ1-b forms an RC time-delay circuit. As long as there is no change in the dc-voltage level at either of U1-b's inputs, its output is near zero. If a voltage glitch occurs, the RC timing circuit will delay the voltage change at the op amp's inverting input, causing its output to go high, triggering SCR1 and causing LED1 to light. The circuit's sensitivity allows it-to detect voltage changes in the millivolt range. Pressing S1 diverts the SCR's holding current to ground, causing it to turn off and reset the circuit.

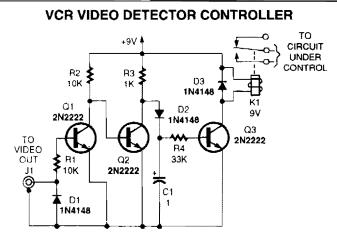


POPULAR ELECTRONICS

Fig. 26-5

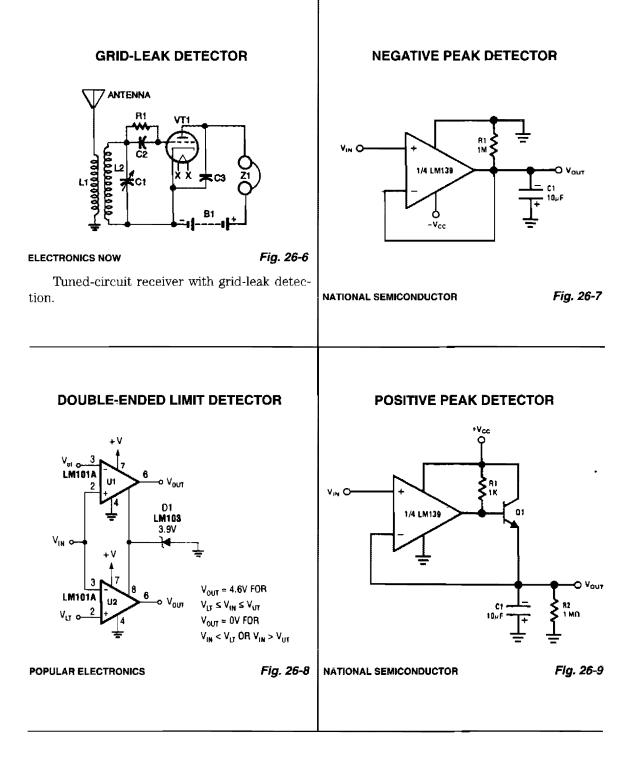This circuit uses the video output from a VCR or camera to control a relay. Video turns on Q1, cutting off Q2, allowing Q3 to be forward biased, activating relay K1. You can use the timer in your VCR and this unit to generate long time delays as well.



LM556 FREQUENCY DETECTOR

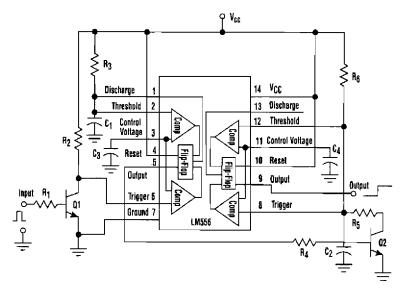

ELECTRONIC DESIGN

Fig. 26-10

The circuit (see the figure), is built around an LM556 dual-timer IC. The 556's first timer is wired as a one-shot and is used to stretch the incoming pulses into fixed-length pulses. The second timer, which is similar to an astable multivibrator (pin 13 remains disconnected), functions as follows:

The one-shot's fixed-length pulses, which are output on pin 5, turn on Q1 and discharge C2 through R5. If the frequency of the pulses is high enough, the voltage on C2 will fall below $\frac{1}{2}$ VCC and the second timer's output, pin 9, will go to a logic 1. Conversely, if the frequency is low enough or is zero, the voltage on C2 will charge through R6 to a level above $\frac{1}{2}$ VCC, and the pin 9 output will go to a logic "0."


The idea is to keep the upper and lower peak voltage on C2 below % VCC and % VCC, respectively for a logic 1, and above % VCC and % VCC, respectively, for a logic 0.

To find the one-shot values, R3 and C1, select a pulse width $(1.1 \times R_3 \times C_1)$ that's greater than the largest input pulse width and less than twice the inverse of the highest input frequency. To find R5, R6, and C2, first determine the duty cycle $(t_{\rm on}/t_{\rm eff})$ of the input signal. Next, choose a standard value for C2 and calculate R6:

$$R_6 = \frac{[(t_{\text{off}} \times 0.61)^2 + t_{\text{off}}]}{C_2}$$

Also, $R_5 = R_6 (t_{on}/t_{off})$. A tweak of resistors R5 and R6 might be needed to get the preferred response. Input signals with low duty cycles work the best. Finally, notice that capacitors C3 and C4 can be any value between 0.01 and 0.1 μ F.

SINGLE COMPARATOR WINDOW DETECTOR

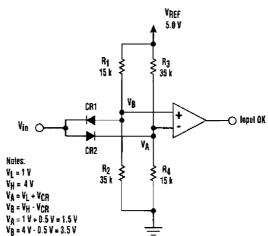


ELECTRONIC DESIGN

Fig. 26-11


Simply by adding two steering diodes, a window detector can be built using only a single comparator. The detector performs well for windows of about 1 V or greater, but it isn't suitable where extreme precision is required because the forward drops of the diodes vary.

In the basic circuit, two resistive dividers set threshold voltage levels at both the inverting and noninverting inputs of the comparator by dividing the reference voltage. The input voltage is steered to the appropriate comparator input by diodes CR1 and CR2.

When the input voltage is within the window, neither diode conducts, and the comparator is biased for a high output. When the input goes above the window, CR2 conducts and pulls the inverting input high, causing the comparator output to go low. When the input voltage goes below the window, CR1 conducts, pulling the noninverting input low, again causing the comparator output to go low. The source resistance of $V_{\rm in}$ must be low compared to the equivalent parallel resistance of each divider.

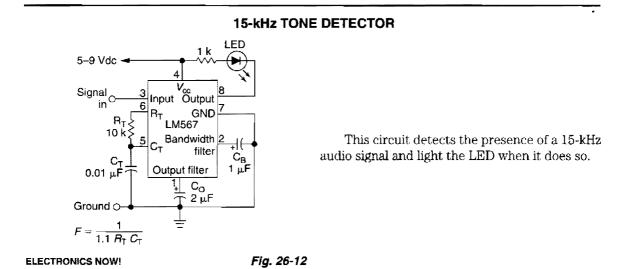


CRYSTAL RADIO DETECTOR

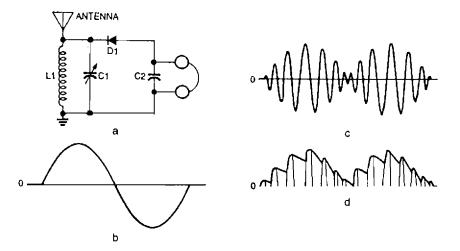

ELECTRONICS NOW!

Fig. 26-13

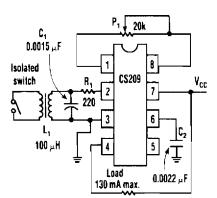This is a crystal detector receiver with headphones (Fig. 26-13A), audio-frequency signal (Fig. 26-13B), modulated signal (Fig. 26-13C), and a demodulated wave (Fig. 26-13D).




SWITCH CLOSURE CIRCUIT

ELECTRONIC DESIGN

A standard proximity detector circuit for the Cherry Semiconductor CS209 IC can detect an isolated switch closure by adding a few turns of wire around the circuit's inductor (Radio Shack 273-102). Moreover, the technique doesn't require any isolated power (see the figure). With the switch open, the potentiometer P1 is adjusted until the output switches off. When the switch is closed, the Q of the circuit changes and the output turns on. Capacitor C1 should be silvered mica, and potentiometer P1 should be a multiturn type such as the Bourns 3006P-1-203. A 9-V supply can be used for Vec.

182

Fig. 26-14

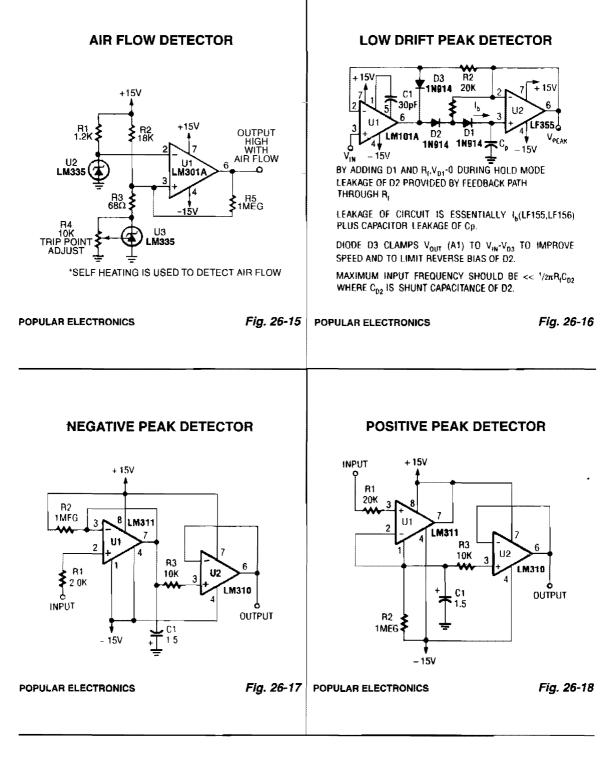

455-kHz AM DETECTOR



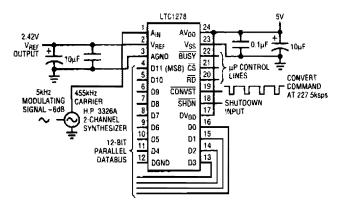



Figure A. The LTC1278 undersamples the 455-kHz carrier to recover the 5-kHz modulating signal

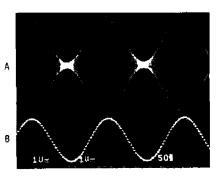

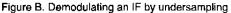

LINEAR TECHNOLOGY

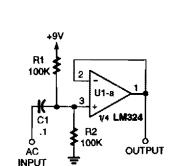The LTC1278 undersamples the 455-kHz carrier to recover the 5-kHz modulating signal. The application shown uses the LTC1278 to undersample (at 227.5 ksps) a 455-kHz IF amplitude-modulated by a 5-kHz sine wave. Figures 26-19A and 26-19B show, respectively, the 455-kHz IF carrier and the recovered 5-kHz sine wave that results from a 12-bit DAC reconstruction.



POPULAR ELECTRONICS

This circuit can be added to the glitch detector to trigger on ac noise.

ac NOISE DETECTOR

Fig. 26-20

Fig. 26-19


27

Differential Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Basic Op-Amp Differential Amplifier Precision High Gain Differential Amp

BASIC OP-AMP DIFFERENTIAL AMPLIFIER

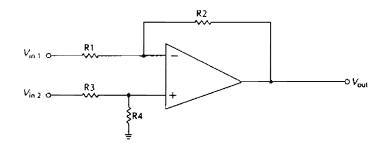

McGRAW-HILL

In most cases, R_1 is equal to R_2 , and R_3 has the same value as R_4 . These equalities don't always have to be true, but they do significantly simplify the circuit design in most practical applications. In any case, for a true differential amplifier, the $R_3:R_1$ and $R_4:R_2$ ratios must be equal. That is:

$$\frac{R_3}{R_1} = \frac{R_4}{R_2}$$

The circuit still functions even if these ratios are not maintained, but the signals at the inverting and noninverting inputs are subjected to differing amounts of gain, which would be undesirable in most practical applications.

$$R_1 = R_2$$
$$R_3 = R_4$$

These resistance ratios determine the gain of the amplifier:


$$G = \frac{R_3}{R_1} = \frac{R_4}{R_2}$$

Assuming that the resistance ratios are maintained, the output voltage is equal to the differences between the two input voltages, multiplied by the gain. That is,

$$V_{\rm OUT} = G \times (V_1 - V_2)$$

Fig. 27-1

PRECISION HIGH-GAIN DIFFERENTIAL AMP

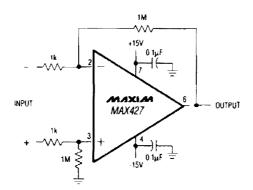

MAXIM

Fig. 27-2

This circuit has a gain of 60 dB and a gain bandwidth of 8 MHz.


28

Display Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Multiplexed BCD Decoder-Driver Circuit Color-Shifting LED Display Stereo Level Display High-Efficiency Display Contrast and Backlight Control Bar-Graph Level Gauge Simple Color Organ Voice Level Meter LCD Contrast Temperature Compensator LED Bargraph Driver Circuit


MULTIPLEXED BCD DECODER-DRIVER CIRCUIT

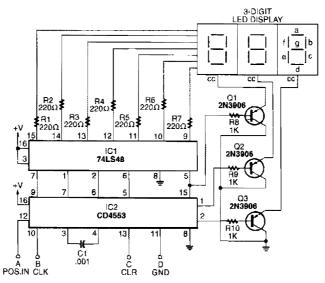

ELECTRONICS NOW

Fig. 28-1

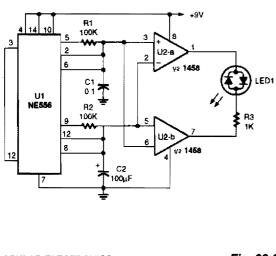The BCD decoder-driver circuit will interface with any standard BCD output to produce a digital display.




COLOR-SHIFTING LED DISPLAY

This circuit is used to make a tricolor LED gradually change color from yellow to red to yellow to green, and then back to yellow, where the cycle repeats. It is very simple to make, and the theory of operation is also simple. Both of the timers in the 556 dual oscillator/timer are configured for astable operation with a 50% duty cycle. One timer is set to oscillate much faster than the other. The timing capacitor voltage of each is sent to two comparators, which apply a voltage across the tri-color LED whose polarity depends on which capacitor voltage is higher. The rapidly changing capacitor's voltage causes the red and green elements of the LED to be alternately lit, thus giving the illusion of yellow light. As the slowly rising and falling voltage from the slower trimming capacitor changes in average value, it shifts the duty cycle to favor one color or the other. That gives the transition between colors a smooth appearance.

POPULAR ELECTRONICS


STEREO LEVEL DISPLAY

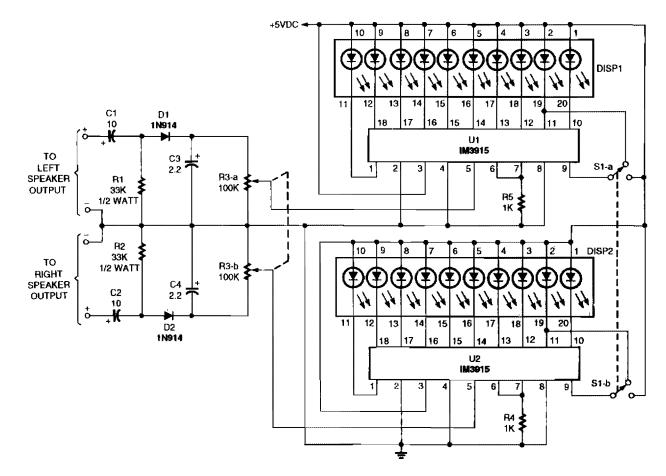

POPULAR ELECTRONICS

Fig. 28-3

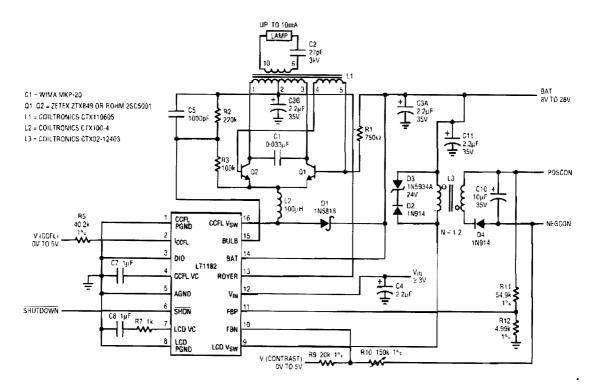Two bar graph drivers and LEDs are used in this volume (level) indicator. R3a and R3b set the sensitivity of the circuit. The LEDs can be either bar graph units or individual LEDs can be used.




HIGH-EFFICIENCY DISPLAY CONTRAST AND BACKLIGHT CONTROL

LINEAR TECHNOLOGY

Fig. 28-4

The LT1182 and LT1183 are compact high-performance solutions for powering LCD screens used in portable computers and instruments. Backlight control using a Cold Cathode Fluorescent lamp (CCFL) is accomplished with a switching regulator at efficiencies.up to 90%. A second switching regulator converts the positive input to either positive or negative bias voltages used for LCD contrast control. Both regulators allow full range of adjustment using a D/A converter, PWM or potentiometer control. Grounded bulb configurations are also easily controlled with minimal parts count. The 200-kHz switching frequency minimizes the size of transformers and external components. A shutdown mode powers down both regulators and reduces supply current to just 35 μ A.

BAR-GRAPH LEVEL GAUGE

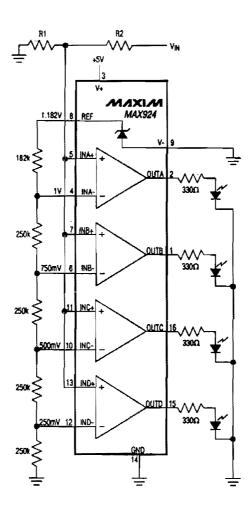


MAXIM

Fig. 28-5

A quad comparator and divider network form a 4-level comparator that drives 4 LEDs. R1 and R2 can be used to scale the basic sensitivity of 250 mV/LED to higher voltages than the basic 1 volt (for all 4 LEDs lit).

SIMPLE COLOR ORGAN

Ю	op amp
IC2, IC3, IC4	LM3909 LED flasher/oscillator
D1, D2, D3	diode (1N914, 1N4148, or similar)
D4, D5, D6	LED
TI	impedance-matching transformer (8 Ω :1 k Ω — see text)
C1, C2, C3, C4	0.1 µF capacitor
C5	0.047 µF capacitor
C6	0.01 µF capacitor
C7, C8, C9	47 μF 6 V electrolytic capacitor
R1	100 kΩ potentiometer
R2	47 kΩ ¼ W 5% resistor
R3	2.2 kΩ ¼ W 5% resistor
R4	680 Ω ¼ W 5% resistor
R5	220 kΩ ¼ W 5% resistor
R6	390 Ω ¼ W 5% resistor
R7	1.2 kΩ ¼ W 5% resistor
R8, R10, R12, R14, R16	10 kΩ ¼ W 5% resistor
R9	3.3 kn ¼ W 5% resistor
R11, R13, R15	33 kΩ ¼ W 5% resistor

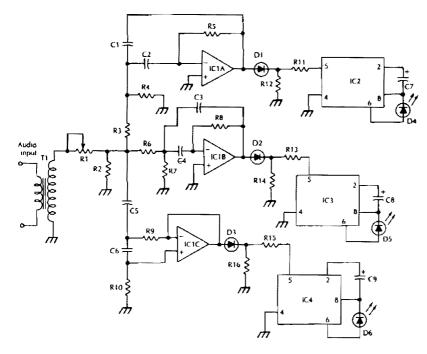


McGRAW-HILL

Fig. 28-6

Three active filters that divide the audio spectrum into three bands drive rectifiers and then drive IC2, 3, and 4, flashing the LEDs at 6 Hz. D4, D5, and D6 should be three different colors for best effect.

VOICE LEVEL METER

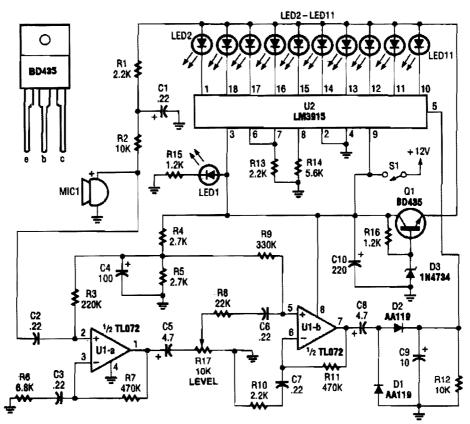


This volume meter can be handy anywhere you need to measure the relative sound level in a room. It is readily adjustable to increase its usefulness.

POPULAR ELECTRONICS

Fig. 28-7

Using an LM3915 VU meter LED bar graph driver, 10 LEDs are driven. A simple audio amplifier drives a detector circuit, which provides dc drive for the LM3915.


LCD CONTRAST TEMPERATURE COMPENSATOR

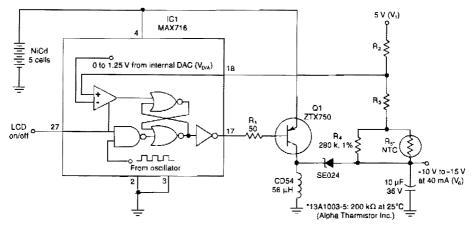

ELECTRONIC DESIGN

Flg. 28-8

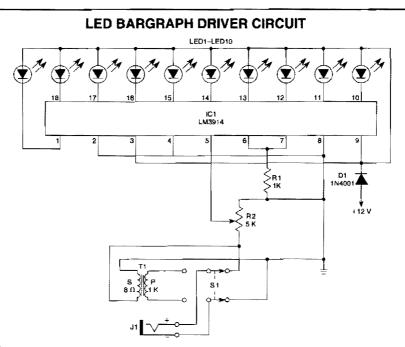Negative temperature-coefficient resistor R5 modifies feedback in this switching regulator, which results in a negative output voltage that varies with temperature. With properly chosen resistor values, the circuit produces a temperature-compensated bias voltage that ensures constant contrast in an LCD.



ELECTRONICS NOW

Fig. 28-9

This circuit is used as an audio indicator. S1 selects direct input or a $1-k\Omega$ (high impedance) audio input. R2 is a sensitivity control.


29

Driver Circuits

T he sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Two-Input Video MUX Cable Driver Impedance-Matched Line Driver with 75-Ω Load Tests Driver for Hobby Servos Stereo Line Driver High-Speed Shield/Line Driver Simple Neon Light Driver High-Side MOSFET Driver TTL-Based Speaker Driver Low-Distortion Composite ±100-mA Line Driver Video Cable Driver Coax Cable Driver Ultra Low Distortion ±50-mA Driver Very Efficient Solenoid Driver


TWO-INPUT VIDEO MUX CABLE DRIVER

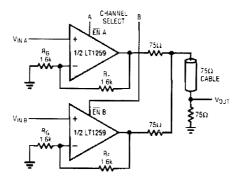

LINEAR TECHNOLOGY

Fig. 29-1

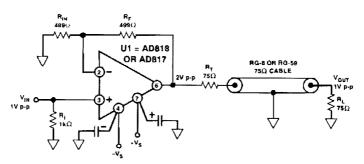IMPEDANCE-MATCHED LINE DRIVER WITH 75-Ω LOAD




ANALOG DIALOG

Fig. 29-2

.

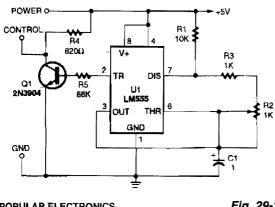This circuit is a wideband 75- Ω line driver, for video applications (1 V p-p into 75 Ω).



TESTS DRIVER FOR HOBBY SERVOS

This circuit will generate the pulse used to control hobby servos. With the components shown the servo should produce a 90° total rotation.

STEREO LINE DRIVER



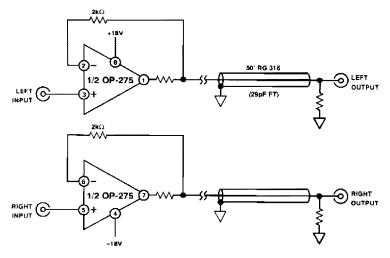


Fig. 29-4

ANALOG DEVICES

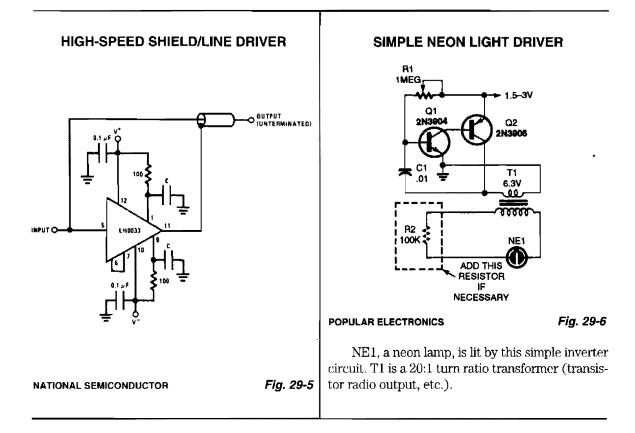One Analog Devices OP-275 can be used for stereo line driver applications.



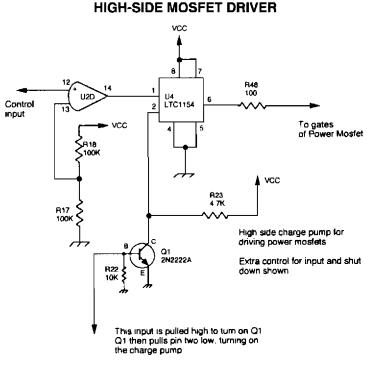


73 AMATEUR RADIO TODAY

Fig. 29-7

A Linear Technology LTC1154 is used as a charge pump to drive the gate of a high-side power MOSFET.

TTL-BASED SPEAKER DRIVER

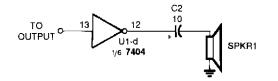


POPULAR ELECTRONICS

A TTL IC, such as a 7404, can drive a small speaker with enough audio to be used as an alarm or annunciator. The speaker can be a 32- or $100-\Omega$ unit.

Fig. 29-8

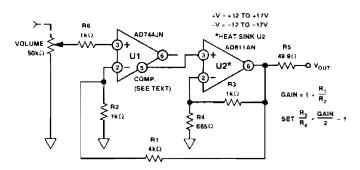
LOW-DISTORTION COMPOSITE ± 100-mA LINE DRIVER



ANALOG DEVICES

Fig. 29-9

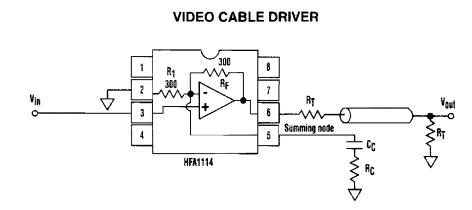This line driver combines the high input impedance of an FET-input IC and a 100-mA op amp. U1's output is left open. The compensation terminal (pins) drive U2's high-*Z* input for increased overall phase margin. Gain is 14 dB, THD +N at 5 V, and RMS output is around 0.001% below 20 kHz.




ELECTRONIC DESIGN

Fig. 29-10

The driver's frequency response is tunable for a specific cable length via components connected to the summing node. By shunting R1, R_c acts to increase the amplifier's gain, and C_c controls the cut-in frequency of the compensation.

These three components peak the amplifier's frequency response to counteract the cable's rolloff characteristic. By squeezing more bandwidth out of a given cable, higher-performance cables aren't needed.

COAX CABLE DRIVER

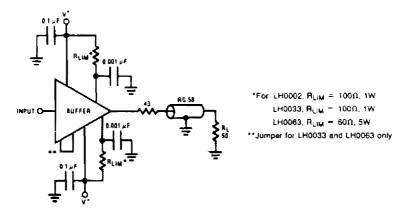


NATIONAL SEMICONDUCTOR

Fig. 29-11

Because of their high-current drive capability, the LH0002, LH0033, and LH0063 buffer amplifiers are suitable for driving terminated or unterminated coaxial cables, and high-current or reactive loads. Current-limiting resistors should be used to protect the device from excessive peak load currents or accidental short circuit. No current limiting is built into the devices other than that imposed by the limited beta of the output transistors. This figure shows a coaxial-cable drive circuit. The 43- Ω resistor is included, the output voltage to the load is about half what it would be without the near-end termination.

ULTRA LOW DISTORTION ±50-mA DRIVER

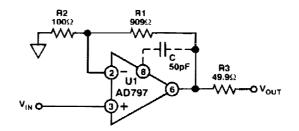


ANALOG DEVICES

Fig. 29-12

For a 600- Ω load, THD is typically -115 dB at 20 kHz, 3-V RMS output, with ±15-V supplies. The -3-dB BW is 6 MHz.

VERY EFFICIENT SOLENOID DRIVER

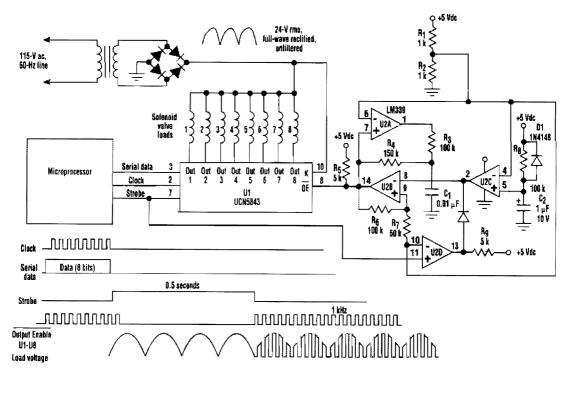

ELECTRONIC DESIGN

Fig. 29-13

In the circuit shown, the IC in the center, U1, contains a microprocessor-compatible serial-in, parallel-out shift register, with strobed latch and high-level solenoid drives (see the figure).

The strobe pulse turns on the selected loads at full power for its pulse width, which is 0.5 second. Following the strobe pulse, the driver outputs are pulse-width modulated by the multivibrator, which is set for a duty cycle of 25%. The solenoids are therefore held in the engaged position with a voltage that's 25% of the nominal supply voltage.

U2B acts as the basic multivibrator in the circuit, and U2A sets the duty cycle by setting the discharge current of capacitor C1. U2D overrides the oscillation during the strobe pulse. And U2C provides the Power-On Reset (POR), inhibiting the solenoid loads from turning on during the initialization period of the microprocessor.


30

Electronic Lock Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Electronic Lock Frequency-Based Lock Simple Lock

ELECTRONIC LOCK

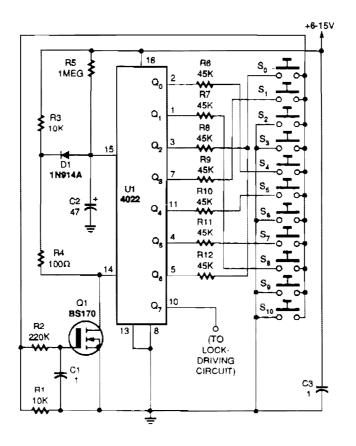


POPULAR ELECTRONICS

Fig. 30-1

The heart of the circuit is a 4022 octal counter. When first powered up, C2 is charged via R5, so the reset input of the counter is kept high. That causes output Q_o to go high while all other outputs are low. With the switches wired as shown, when S4 is pressed, the BS170 is switched on via debouncing network R2/C1, and U1 receives a clock pulse. Also, C2 is discharged via R4 and D1, removing the reset signal of the counter, allowing it to advance. The time required for C2 to charge via R5 (i.e., to reset the counter), is the maximum time that can lapse before the next key is pressed. The above cycle is therefore repeated only if S8 (connected to the Q1 output) is pressed in time. When all keys have been pressed in time and in the correct order, Q7 goes high for about four seconds to drive the "unlock" circuitry (e.g., a relay driver for an automatic door opener. A builder can change the code by reviewing the switches. The code for the lock shown in the circuit diagram is 4-8-0-1-5-7-0. However, the 4022 octal counter can be replaced by a 4017 divide-by-10 counter. That will make it possible to add two more digits to the combination.

FREQUENCY-BASED LOCK

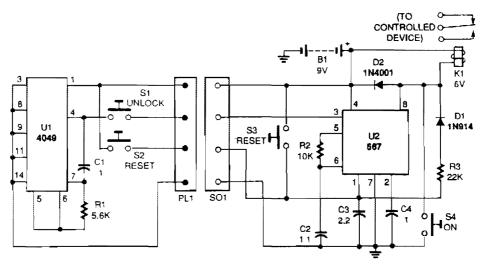


POPULAR ELECTRONICS

Fig. 30-2

The system is formed by two separate circuits—a key and a keyhole. The key engages the keyhole with a mating pair of connectors. The key is a tone-generator circuit consisting of a 4049 hex inverter CMOS IC (U1), switches (S1 and S2), a resistor (R1), and a capacitor (C1). The value of the tone generated by that circuit in Hz is determined by;

$$\frac{1}{(1.4 \times R_1 C_1)}$$

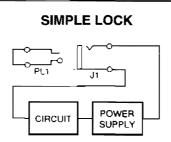The keyhole is a 567 tone-decoder circuit that can be configured to detect any frequency from 0.01 Hz to 500 kHz. The frequency it detects (f_o) , via the 567 IC, turns on the relay (K1). Components R3 and D1 are used to latch the circuit, so the output stays on even after the input tone is removed. When S2 is pressed, the system is reset. Switch S3 resets the circuit from inside.



POPULAR ELECTRONICS

Flg. 30-3

Only an appropriately wired plug of the right size will activate circuits with a nonshorting jack in their power supply circuit.


31

Fiber-Optics Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Experimental Data Transmitter for Fiber Optics Experimental Fiber-Optic Data Receiver

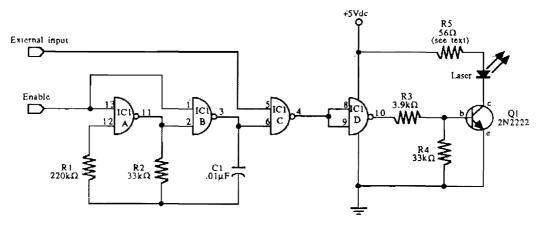
EXPERIMENTAL DATA TRANSMITTER FOR FIBER OPTICS



McGRAW-HILL

Fig. 31-1

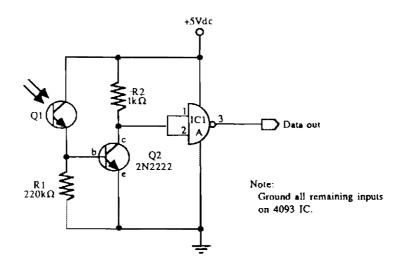This schematic for an experimental data transmitter uses optical fibers and a laser diode. Transmission frequency of the free-running oscillator is approximately 3 kHz. R5 might have to be varied to suit your laser diode. IC1 is a CD4093.



EXPERIMENTAL FIBER-OPTIC DATA RECEIVER

McGRAW-HILL

Fig. 31-2


An infrared phototransistor acts as the sensor for this receiver. IC1a is a section of a CD4093 CMOS NAND gate.

32

Filter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


State Variable Filter Sallen-Key High-Pass Filter Active Bandpass Filter Circuit High-Pass Filter Second-Order Voltage-Controlled Filter Combination Filter Shortwave Receiver IF Filter Pin Diode Filter Selection Circuit High-Pass Active Filter AM Broadcast Trap for Simple SW Receivers Shortwave Interference Trap Programmable Analog Filter Active Low-Pass Filter Two Op-Amp Bandpass Filter Single 3.3-V Supply 4-Pole State Variable Filter High-Q Notch Filter Adjustable Q Notch Filter Digital Comb Filter Voltage-Controlled Low-Pass Filter VSB Filter for LM2889 20-kHz Butterworth Active Filter Bandpass Filter Sallen-Key Low-Pass Filter Active High-Pass Filter RC Notch Filter 1-kHz 4th-Order Butterworth Filter Saw-Filter Impedance-Matching Preamplifier One Op-Amp Bandpass Filter

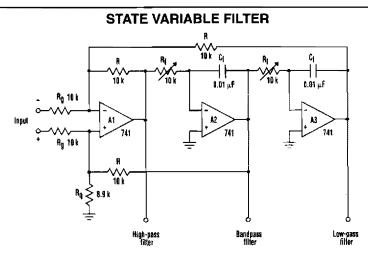

ELECTRONIC DESIGN

Flg. 32-1

The state variable filter shown consists of only three op amps and a few passive components. It provides several key features. These include the ability to simultaneously provide low-pass, high-pass, and bandpass filter functions, and adjust bandwidth in a wide range by changing the values of $C_{\rm f}$ and $R_{\rm f}$. The device also is easy to tune and simple to construct, while the quality factor (Q) of each filter is independent of each other.

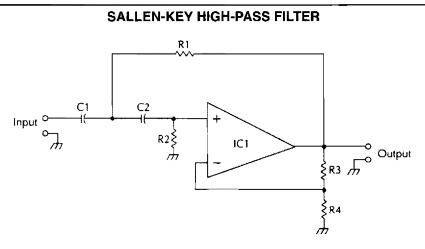

McGRAW-HILL


R3 and R4 set the circuit gain

$$f_{\rm c} = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

usually $C_1 = C_2, R_1 = R_2$

$$R_3 = 0.586 R_4$$

ACTIVE BANDPASS FILTER CIRCUIT

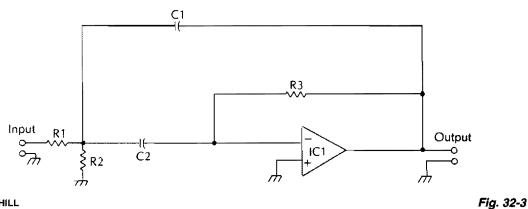


McGRAW-HILL

In this circuit,

 $C_1 = C_2 = C$

$$\begin{split} Q &= \frac{f_o}{BW} \quad K = circuit \ gain, \ f_o = center \ frequency \\ R_1 &= \frac{Q}{2\pi f_o C K} \\ R_2 &= \frac{2Q}{2\pi f_o C} \\ R_3 &= \frac{Q}{2\pi f_o C (2Q-K)} \end{split}$$

HIGH-PASS FILTER

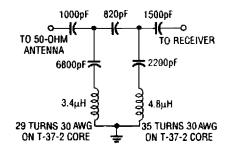


RADIO-ELECTRONICS

Flg. 32-4


This high-pass filter will attenuate AM stations by 40 dB. Its low-frequency cutoff is about 2.2 MHz. This filter is useful for SW listening in areas of high AM radio signal strength.

SECOND-ORDER VOLTAGE-CONTROLLED FILTER

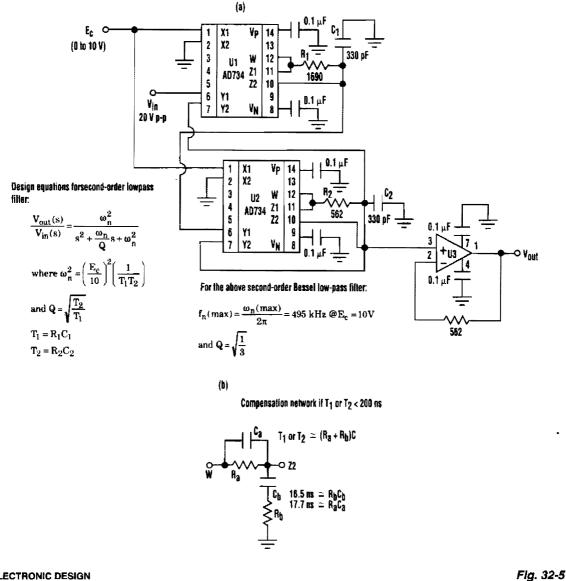

ELECTRONIC DESIGN

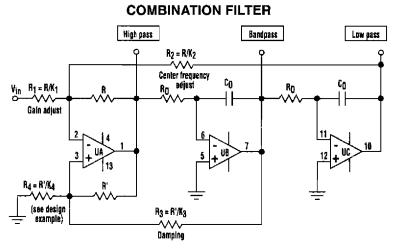Desirable second-order voltage-controlled low-pass filter response can be achieved with this voltage-controlled filter (A). By using low-distortion, wide-bandwidth multipliers, it achieves higher cutoff frequencies than switched-capacitor filters. If the circuit's RC network has a time constant less than 200 ns, it should be replaced by a lag compensator network (B).



ELECTRÓNIC DESIGN


Fig. 32-6

Fig. 32-7

The classic "state variable" two-integrator filter is known for its insensitivity to component variations, and its ability to provide three separate simultaneous outputs—low pass, high pass, and bandpass. Typically, a quad op amp is used to implement the state-variable filter. The classic configuration


uses two integrating amplifiers, a filter input amplifier, and a filter feedback amplifier.

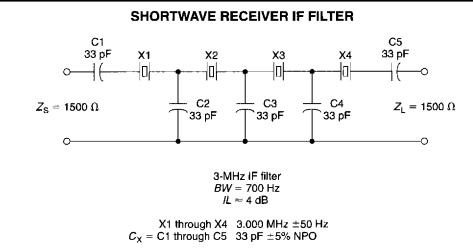The design described here combines both input and feedback amplifiers into one adder/subtractor amplifier, achieving a three op-amp filter design (see the figure).



WILLIAM SHEETS

An inexpensive filter can be made from microprocessor crystals. This filter has 700 Hz BW (3 dB) and has a flat response (<1 dB) for about 400 to 500 Hz. Although a 3-MHz crystal was used, any frequency from 2 to 15 MHz (using fundamental crystal) should work, with appropriate scaling of components. Crystal resonant frequencies should match within 20% and preferably 10% of expected bandwidth (which is narrower-as C_x increases. Impedance is reduced with wider bandwidths.

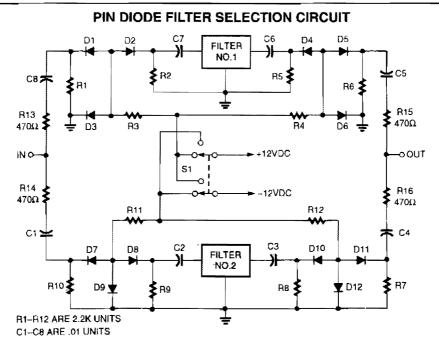


POPULAR ELECTRONICS

Fig. 32-8


Selecting IF bandpass filters via series/shunt PIN-diode switching can be accomplished with this circuit.

HIGH-PASS ACTIVE FILTER

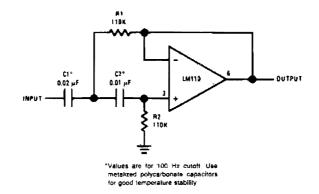

NATIONAL SEMICONDUCTOR

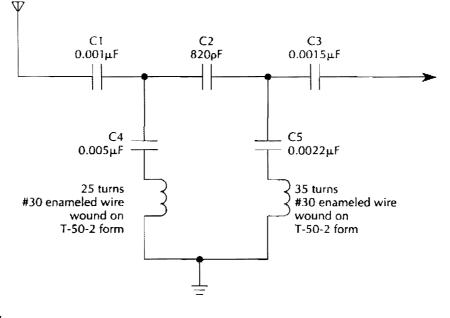
AM BROADCAST TRAP FOR SIMPLE SW RECEIVERS



McGRAW-HILL

Fig. 32-10


SHORTWAVE INTERFERENCE TRAP

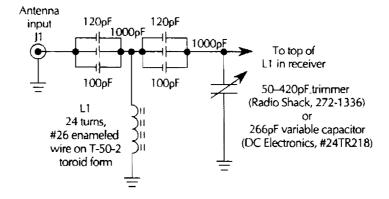

Build this interference trap to help block strong shortwave, broadcast, and FM stations from

McGRAW-HILL


coming in on the shortwave bands.

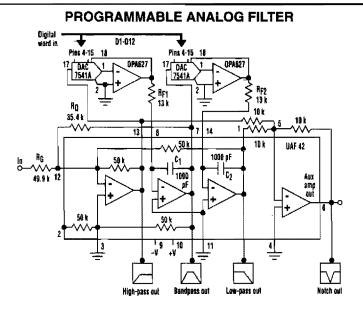

ELECTRONIC DESIGN

Fig. 32-12

The circuit in the figure shows how an analog, digitally programmable filter can be built using a UAF42. This monolithic, state-variable active filter chip provides a two-pole filter building block with low sensitivity to external component variations. It eliminates aliasing errors and clock feed though noise common to switched-capacitor filters. Low-pass, high-pass, bandpass, and notch (band-reject) outputs are available.

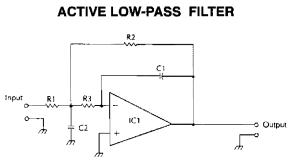

 $R_{2} = R_{4}$ $R_{3} = 2R_{1}$ $C_{1} = C_{2}$

 $f = \frac{1}{2\pi RC}$


In this circuit, $R_1 = 2$

Fig. 32-13

McGRAW-HILL

This circuit has a rolloff of 6 dB/Octave.

TWO OP-AMP BANDPASS FILTER

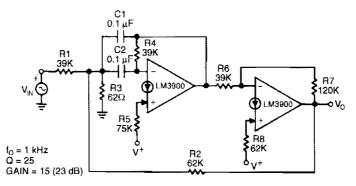


NATIONAL SEMICONDUCTOR

Flg. 32-14


This circuit uses only two capacitors. The amplifier on the right supplies a controlled amount of positive feedback for improved response characteristics. Resistors R5 and R8 are used to bias the outvoltage of the amplifiers at V+/2.

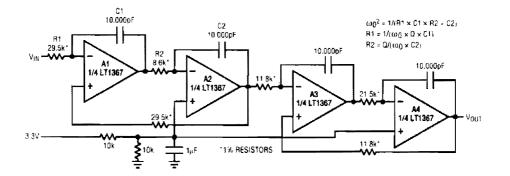
SINGLE 3.3-V SUPPLY 4-POLE STATE VARIABLE FILTER



LINEAR TECHNOLOGY

HIGH-Q NOTCH FILTER

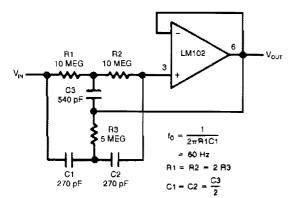

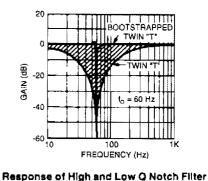

-


84

50K

NATIONAL SEMICONDUCTOR

Fig. 32-16

This shows a twin "T" network connected to an LM102 to form a high Q, 60-Hz notch filter. The junction of R3 and C3, which is normally connected to ground, is bootstrapped to the output of the follower. Because the output of the follower is a very low impedance, neither the depth nor the frequency of the notch change; however, the Q is raised in proportion to the amount of signal fed back to R3 and C3.

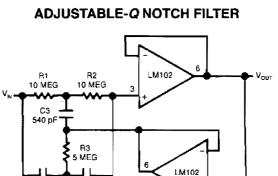

NATIONAL SEMICONDUCTOR

This figure shows a circuit where the Q can be varied from 0.3 to 50. A fraction of the output is fed back to R3 and C3 by a second voltage follower, and the notch Q is dependent on the amount of signal fed back. A second follower is necessary to drive the twin "T" from a low-resistance source so that the notch frequency and depth will not change with the potentiometer setting.

 $f_{\odot} = 60 \text{ Hz}$


C1

270 pF

C2

270 pF

DIGITAL COMB FILTER

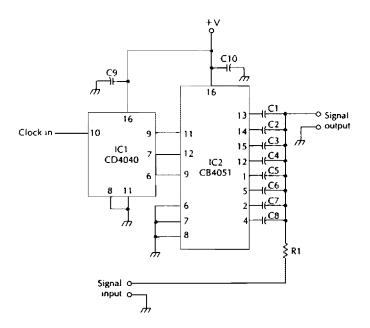

This circuit uses an eight-step switching sequence, so n=8. This makes the center frequency equal to:

$$F_{c} = \frac{1}{(2nRC)}$$
$$= \frac{1}{(2 \times 8)RC}$$
$$= \frac{1}{16RC}$$

Using the component values suggested in the parts list, the circuit has a main center frequency of:

$$F_c = \frac{1}{(16 \times 1000 \times 0.00000001)}$$

= $\frac{1}{0.00016}$
= 6250 Hz

McGRAW-HILL

 Suggested parts list for the digital comb filter

 IC1
 CD4040 BCD-ripple counter


 IC2
 CD4051 BCD-to-decimal decoder (SP8T rotary bilateral switch)

 C1-C8
 0.01 μF close tolerance capacitor C9, C10

 C1-C8
 1.01 μF close tolerance capacitor

 C9, C10
 0.1 μF capacitor


 R1
 1K ¼ W 5% resistor

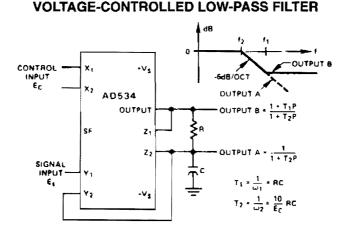

ANALOG DEVICES

Fig. 32-19


The voltage at Output A, which should be unloaded by a follower, responds as though E_s were directed to the RC filter, but the filter's break frequency were proportional to E_c [i.e., $= E_c/(20\pi RC)$]. The frequency response has a break at f_2 and the 6-dB/octave rolloff. The voltage at Output B has the same response, up to $[f_1 \ (f_1 = 1/(2\pi RC)]$, then levels off at a constant attenuation of $f_2/f_1 = E_c/10$. For example, if $R = 8 \ k\Omega$, $C = 0.002 \ \mu$ F, Output A has a pole at 100 Hz to 10 kHz and can be loaded. The circuit can be converted to high-pass by interchanging C and R.

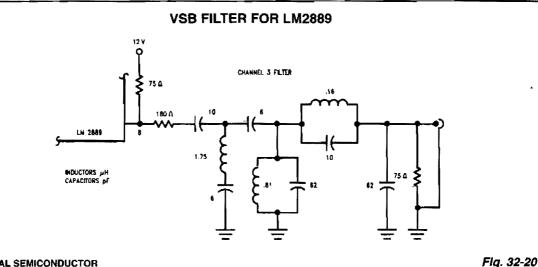

NATIONAL SEMICONDUCTOR

This filter is for CH3, in order to get a vestigial sideband TV signal. It is designed for $75 \cdot \Omega$ impedance levels.


20-kHz BUTTERWORTH ACTIVE FILTER

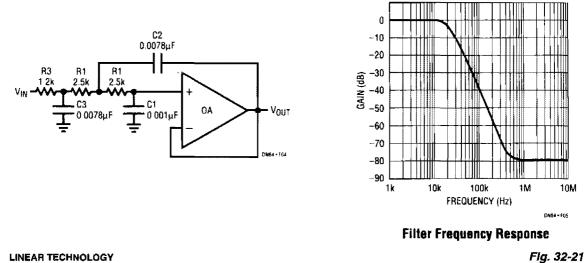

LINEAR TECHNOLOGY


This filter will be useful for anti-aliasing or band limiting in an audio system. The op amp is a Lincar Technology, LT1124, LT1355, or LT1169.

BANDPASS FILTER

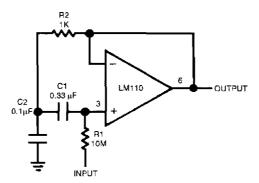

NATIONAL SEMICONDUCTOR

SALLEN-KEY LOW-PASS FILTER

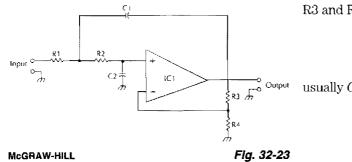


R3 and R4 set the circuit gain

$$f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}}$$

usually
$$C_1$$
 = C_2, R_1 = R_2 , R_3 = 0.586 R_4

McGRAW-HILL

ACTIVE HIGH-PASS FILTER

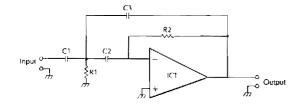


in this circuit,

$$f_{\rm CO} = \frac{1}{2\pi RC}$$

McGRAW-HILL

Flg. 32-24


RC NOTCH FILTER

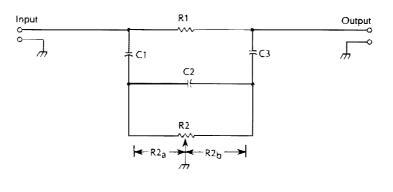

 $egin{array}{lll} C_1 = C_2 = C_3 \ R_1 = 6 R_2 \end{array}$

$$R_2 = R_{2a} + R_{2b}$$
 Reject frequency (notch),
$$F_c = \frac{1}{2\pi C \sqrt{3R_{2a}R_{2b}}}$$

McGRAW-HILL

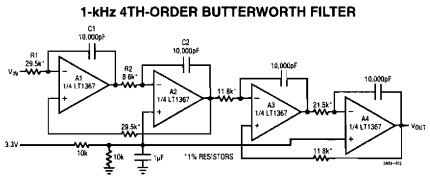

LINEAR TECHNOLOGY

Fig. 32-26


The filter is a simplified state variable architecture consisting of two cascaded 2nd-order sections. Each section uses the 360° phase shift around the two op-amp loop to create a negative summing junction at A1's positive input. The circuit has low sensitivities for center frequency and Q, which are set with the following equations:

$$\boldsymbol{\omega} \ 0^2 = \frac{1}{(R_1 \times C_1 \times R_2 \times C_2)}$$

where,

$$R_1 = \frac{1}{(\omega 0 \times Q \times C_1)}$$
 and $R_2 = \frac{Q}{(\omega 0 \times C_2)}$

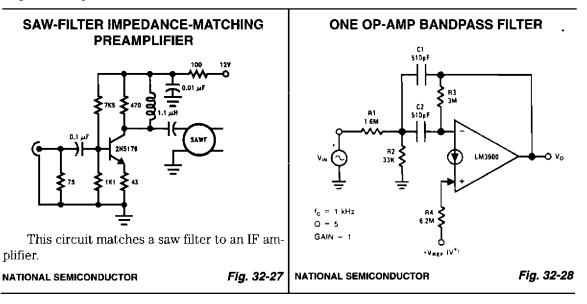The dc bias applied to A2 and A4, half supply, is not needed when split supplies are available. The circuit swings rail-to-rail in the passband making it an excellent anti-aliasing filter for A/Ds. The amplitude response is flat to 1 kHz then rolls off at 80 dB/decade.




33

Flasher Circuits and Blinker

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Random LED Strobe Flashing Neon Christmas Lights Flashing Christmas LED Display Dual Flasher Add-On for 555 Circuits Variable-Frequency High-Power LED Flasher LED Pulser LED Pulser with Audible Output Simple Lamp Pulser LED Flasher

RANDOM LED STROBE

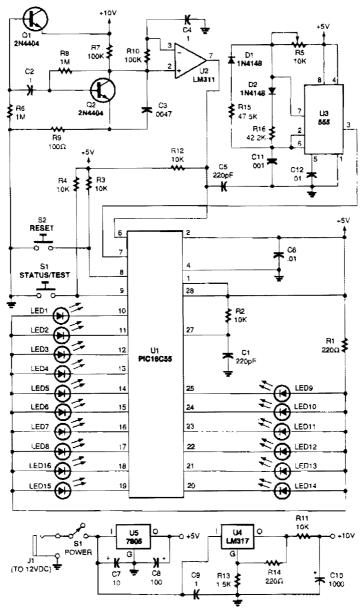


POPULAR ELECTRONICS

Fig. 33-1

This circuit generates a random output that is translated into LED "movement" by a preprogrammed PIC16C55 microcontroller, U1. That PIC also senses and records the bias of the LED's movement. This device was originally used for an application involving psychokinesis testing where the person was asked to "think" the lights in either a clockwise or counterclockwise direction.

FLASHING NEON CHRISTMAS LIGHTS

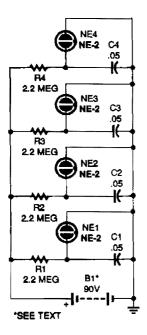


POPULAR ELECTRONICS



This flashing set of neon Christmas lights will make an attractive decoration for any time of year. B1 is made up of ten 9-V transistor radio batteries in series. The battery life can be measured in months.

FLASHING CHRISTMAS LED DISPLAY

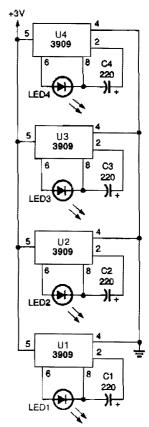


POPULAR ELECTRONICS

Fig. 33-3

Using LEDs and 3909 ICs, you can make a flashing-light circuit that will run for months on two AA batteries.


DUAL FLASHER ADD-ON FOR 555 CIRCUITS

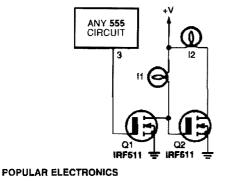

A pair of hex FETs drive two incandescent lamps in an alternating flasher circuit. The lamps can be 12-V automotive types, etc.

Fig. 33-4

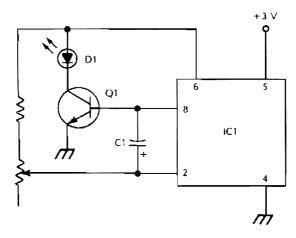
VARIABLE-FREQUENCY HIGH-POWER LED FLASHER




- IC1 LM3909 LED flasher/oscillator IC
- Q1 NPN transistor (2N3904, Radio Shack R52009 or similar)
- D1 LED
- C1 100 µF 5 V electrolytic capacitor
- R1 470 Ω ¼ W 5% resistor
- R2 50 kn potentiometer

McGRAW-HILL

Fig. 33-5

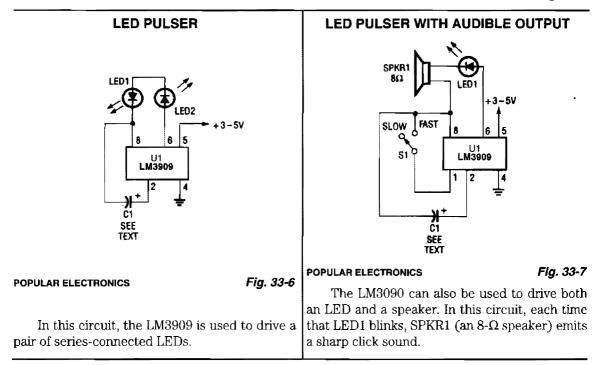

SIMPLE LAMP PULSER

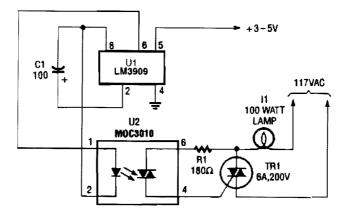


POPULAR ELECTRONICS

Fig. 33-8

Here, the LM3090 (configured as a timing oscillator) is used to control a 117-Vac lamp through an MOC3010 optoisolator/coupler.

LED FLASHER

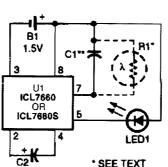

** C1 = .01, f = 1Hz;

C1 = .001, f = 10Hz

47-220

6WVDC

POPULAR ELECTRONICS

This circuit provides a low-cost way to flash an LED from a single 1.5-V source. Based on the ICL7660 dc-to-dc voltage converter, the circuit makes use of an external capacitance (C1) on the oscillator rate-control pin to decrease the charge/dump time to the desired flash rate. A dc resistance (R1) on the same pin can also be used to disable the oscillator and extend the power-cell's life. That optional dc resistance (in the form of a photoconductive cell) will shut off the oscillator in daylight.

Fig. 33-9


34

Flip-Flop Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Trigger Flip Flop Two-Amplifier Flip Flop

TRIGGER FLIP FLOP

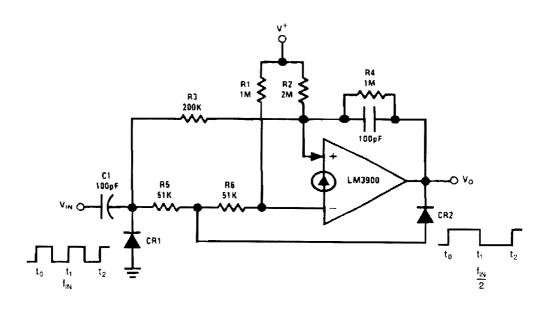


NATIONAL SEMICONDUCTOR

Fig. 34-1

Trigger flip flops are useful to divide an input frequency as each input pulse will cause the output of a trigger flip flop to change state. Due to the absence of a clocking signal input, this is for an asynchronous logic application. A circuit that uses only one amplifier is shown. Steering of the differentiated positive input trigger is provided by diode CR2. For a low-output voltage state, CR2 shunts the trigger away from the (-) input and resistor R3 couples this positive input trigger to the (+) input terminal. This causes the output to switch high. The high-voltage output state now kceps CR2 off and the smaller value of $(R_5 + R_6)$ compared with R3 causes a larger positive input trigger to be coupled to the (-) input, which causes the output to switch to the low-voltage state.

TWO-AMPLIFIER FLIP FLOP

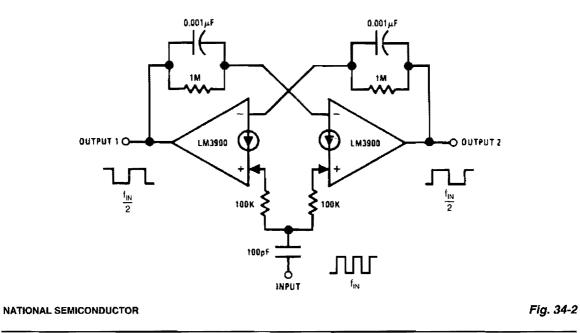


35

Frequency-to-Voltage Converter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Industrial Frequency-to-Voltage Converter Frequency-to-Voltage Converter

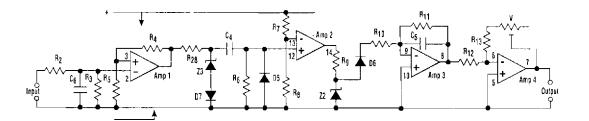INDUSTRIAL FREQUENCY-TO-VOLTAGE CONVERTER



ELECTRONIC DESIGN

Fig. 35-1

Control and process equipment often require the indication of frequency (speed or rate) of linear or rotary mechanical movement. Motion can be detected using various pulse-generating pickups and proximity detectors that output ac or dc pulsed signals.

This industrial converter can serve in a wide variety of applications. The circuit operates around a quad-FET input op amp and is designed to be self-contained or run from a bipolar supply. The input signal of dc pulses or ac waveforms is applied to R2.


Amplifier 1, which acts as a Schmitt trigger, supplies a squarewave output of fixed amplitude to C4. Resistor R3 and capacitor C6 filter out input noise, and R4 and R5 determine the switching levels, and Zener diode Z3 sets the amplitude.

Amplifier 2 gives a fixed-duration pulse on the positive transition of C4, with a time constant set by C4 and R6 and the switching level set by R7 and R8. Resistor R9 and Zener diode Z2 fix the amplitude of the pulses and amplifier 3 integrates them via R10 and C5. Diode D6 blocks negative integration and R11 discharges C5 with a long-time constant.

Hence, the dc output of amplifier 3 is proportional to the frequency applied to the input. Amplifier 4 inverts and buffers the negative output of amplifier 3 and provides amplitude adjustment voltage.

The complete circuit is linear and sufficiently accurate providing that C4 is chosen to give a pulse duration less than the maximum input frequency and that R11 > R10.

FREQUENCY-TO-VOLTAGE CONVERTER

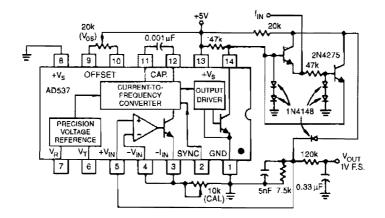

ANALOG DEVICES

Fig. 35-2


The AD537 can also be used to perform frequency-to-voltage conversion. The transistor pair shown here operates as an exclusive-or gate to perform the phase comparison. It locks onto the input frequency within two cycles. The configuration requires only 3 mA for frequencies up to 10 kHz. In most situations, an output buffer will be required to unload the filter. Use 0- to 5-V pulses or square waves with 40- μ s minimum pulsewidth.

36

Function Generator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

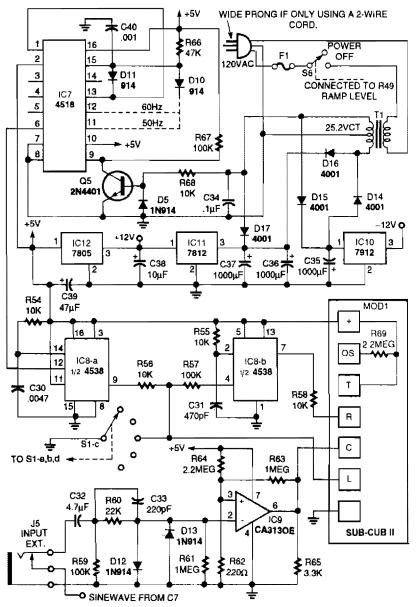Function Generator Sweep/Function Generator Simple Function Generator Accurate, Stable Function Generator Wide-Range Function Generator




FUNCTION GENERATOR

THE COUNTER MODULE (MOD1) has a 0.35-inch high, six-digit liquid crystal display. Pulses at 1-second intervals are derived from the AC power line which has a typical accuracy of 99.99 %.


ELECTRONICS NOW

Fig. 36-1

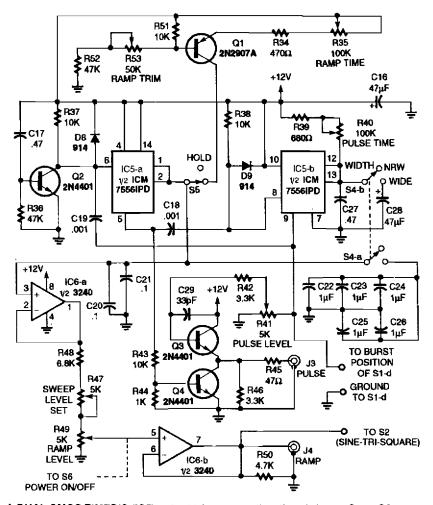These three circuits make up an audio frequency function generator and can be individually used for custom applications.




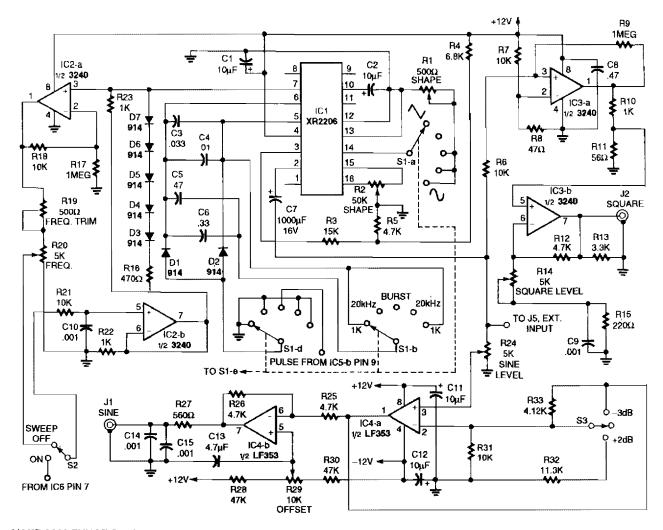A DUAL CMOS TIMER'S (IC5) output triggers another timer's input. Once Q2 starts IC5-a on initial power-up, the circuit continues to oscillate.



AN XR 2206 FUNCTION-GENERATOR CHIP provides a triangle output at pin 2 when S1-a is open.

SWEEP/FUNCTION GENERATOR

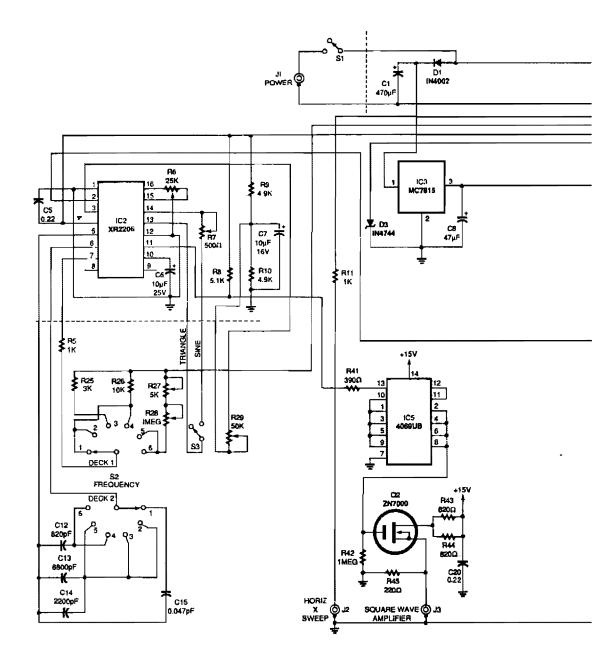

ELECTRONICS NOW

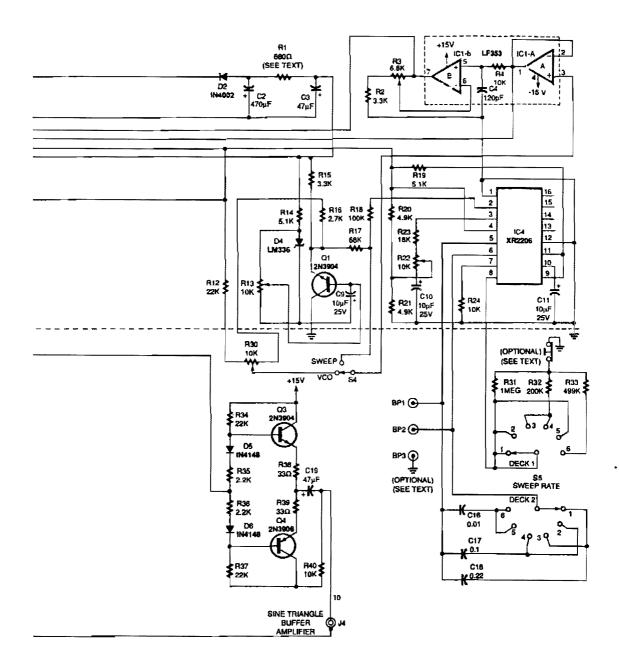


Fig. 36-2

SWEEP/FUNCTION GENERATOR (Cont.)

TABLE 1 FUNCTION GENERATOR_CHARACTERISTICS

Waveform output	Maximum P-to-P	Frequency	Conditions
Sine (1)	5V	10 Hz-100 kHz	1 VØ800 kHz
Triangle (1)	8 V	10 Hz- 50 kHz	1 V>500 kHz
Square (2)	5 V		Positive output DC-coupled ground ref: rise/fall >50 ns
Ramp (3)			Descending, 6 rates

TABLE 2 SWEEP RANGES OF THE FUNCTION GENERATOR

Switch	Condition	Frequency range
1	Preset	20Hz to >2kHz
2	Preset	<400Hz to >10kHz
3	Preset	<1kHz to >25kHz
4	Preset	5kHz to >100kHz
5*	Resistance tuned	2kHz to 100kHz
	Resistance & VCO tuned	<10Hz to >100kHz
6*	Resistance tuned	<40kHz to >800kHz
	Resistance & VCO tuned	<100Hz to >800kHz

Both IC2 and IC4 are Exar XR2206 monolithic function generators; IC4 functions as a ramp generator, and IC2 functions as a generator of sine, triangular, and square waveforms. Dual operational amplifier IC1 produces a scaled, level-shifted ramp output that is capable of deflecting an oscillo-scope's horizontal sweep.

Any frequency of interest along the horizontal axis of an oscilloscope that is coupled to this function generator can be measured with an external frequency counter by manually tuning the function generator's VCO instead of sweeping it. The performance characteristics of the sweep/function generator are summarized in the Table.

The generator's sweep rate and frequency can be set by front-panel rotary six-position switches, Sweep Rate Switch S5 and Frequency Switch S2. The VCO control R30 manually tunes the VCO. Table 2 lists the sweep ranges of the function generator. Sweep ranges not covered in ranges 1 to 4 can be set up as required on positions 5 and 6. Selecting the VCO setting on the front panel toggle switch S4 permits tuning any fixed frequency within the total frequency range of the instrument with both frequency switch S2 and VCO control R30.


The sweep rate or duration of the sweep ramp is selected by the rotary six-position Sweep Rate Switch S5. Table 3 lists the sweep rate durations for each of the six positions. Longer periods should be used for lower frequency sweeps.

SWEEP/FUNCTION GENERATOR (Cont.)

.Sweep position	Period (milliseconds)	
1	~130	
2	~ 60	
3	~ 30	
4	~ 15	
5	~ 6	
6	~ 3	

TABLE 3 SWEEP RATE OR DURATION


SIMPLE FUNCTION GENERATOR

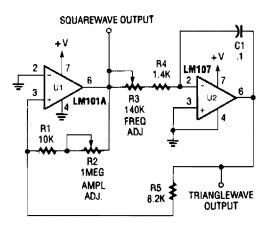

POPULAR ELECTRONICS

Fig. 36-3

ACCURATE, STABLE FUNCTION GENERATOR

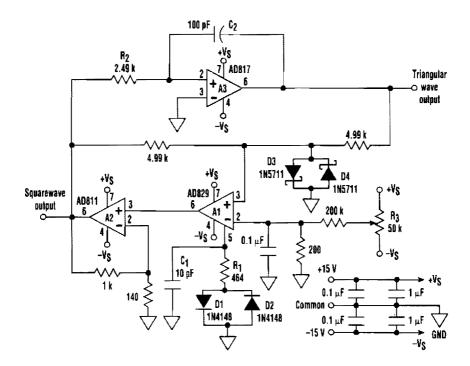

ELECTRONIC DESIGN


Fig. 36-4

Supply-limited oscillators usually are sensitive to temperature and power-supply changes, are never symmetrical, and don't operate at high frequencies because the amplifier's output is saturated when it reaches the supply lines.

The circuit shown, a function generator, can alleviate these problems. Its square-wave output boasts a rapid rise time, quick settling time, and an amplitude that's temperature insensitive. Also, its triangular output waveform features a perfectly constant rate of change throughout its range.

Amplifier A1 together with A2 generates a stable +10 V. This signal, which is integrated using A3, C2, and R2, makes a negative-going ramp. When the peak output of A3 equals -10 V, the output of A1 and A2 change state and the A3's output ramps up. When A3's output equals +10 V, the outputs of A1 and A2 change state again and new cycle starts.

WIDE-RANGE FUNCTION GENERATOR

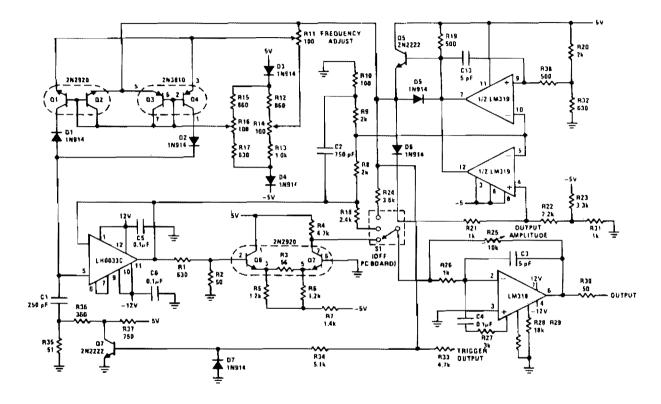

NATIONAL SEMICONDUCTOR

Fig. 36-5

The sine, square, triangle function generator is exceptionally useful. Various IC circuits have been published for generating square and triangle waveforms in an attempt to duplicate the general-purpose function generator. However, these simple circuits are usually limited to about 10 kHz and have no sine-wave output. The function generator shown here provides all three waveforms and operates from below 10 Hz to 1 MHz with usable output to about 2 MHz.


.

37

Game Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

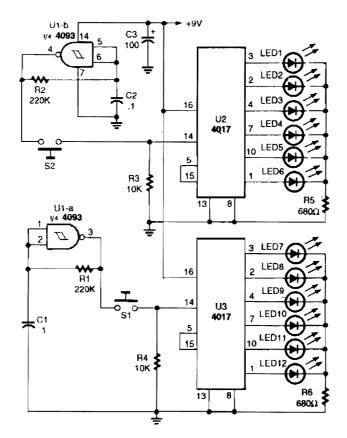Electronic Craps Game 21 Game First-Response Monitor I Z-Dice Game Three-Input First-Response Monitor Electronic Coin Toss Electronic One-Arm Bandit Digital "First-to-Respond" Box First-Response Monitor II Analog First-Response Monitor Wheel of Fortune



ELECTRONIC CRAPS GAME


POPULAR ELECTRONICS

Fig. 37-1

Two gates of a 4093 quad, 2-input NAND, Schmitt-trigger CMOS IC are connected in astable-oscillator circuits as clocks. The two 4017 ICs have six LEDs connected to its first six outputs. As the clock pulses enter pin 14 of the 4017s, the ICs count from one to six over and over as long as the clock pulses are present. When S1 and/or S2 are released, one of the LEDs in each circuit will remain on, indicating a number from one to six.

The circuit is set up so that you can roll the dice together by pressing S1 and S2 at the same time, or roll each die one at a time.

21 GAME

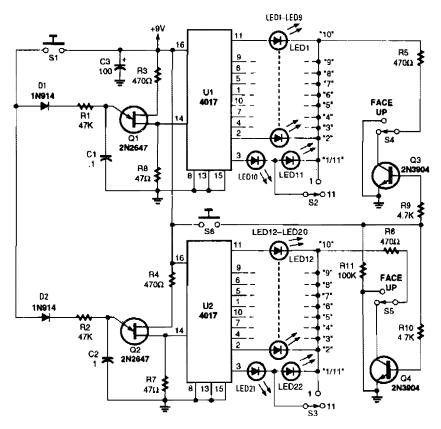

POPULAR ELECTRONICS

Fig. 37-2


Two 2N2647 unijunction transistors serve as the clock generators for the two 4017 ICs. A single "deal" push-button switch, S1, operates both clock generators at the same time. Diodes D1 and D2 isolate the two clock circuits, allowing S1 to operate both.

The 4017 counter/readout circuits are identical in circuitry and operation. As long as clock pulses enter pin 14 of each 4017, the ICs count from 1 to 10 over and over until the clock pulses stop. When S1 is released, the clock pulses stop and one LED from each IC remains on to indicate a card with a number value of 1 (1 or 11) to 10.

The position of switches S2 and S3 determines whether the number 1 ("Ace") output of the 4017s count as an 11 or a 1. Both S2 and S3 can be switched in either position before or after the cards are played.

The cards can be played either face up or face down. When switches S4 and S5 are in the position shown in the figure, the cards are dealt face down. Transistors Q3 and Q4 are turned off in this position and no current can flow through the LEDs. Pressing S6 turns both transistors on, lighting the LEDs.

FIRST-RESPONSE MONITOR I

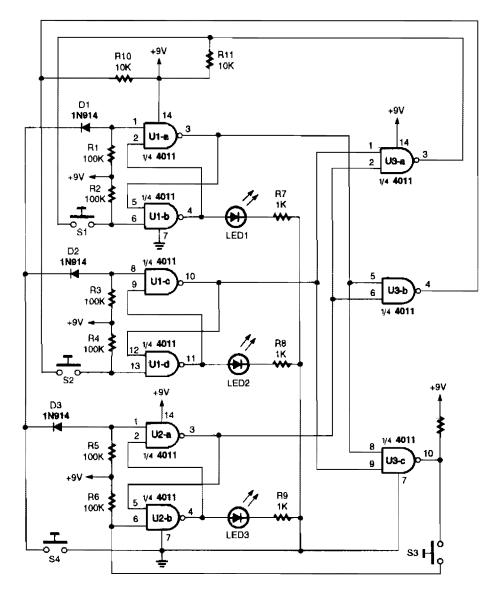


POPULAR ELECTRONICS


Fig. 37-3

Three interlocked flip-flops enable the detection of the first input. S1, S2, and S3 are inputs. Analog switches controlled by logic gates, or other logic circuitry could be sub-statement for S1, S2, and S3.

Z-DICE GAME

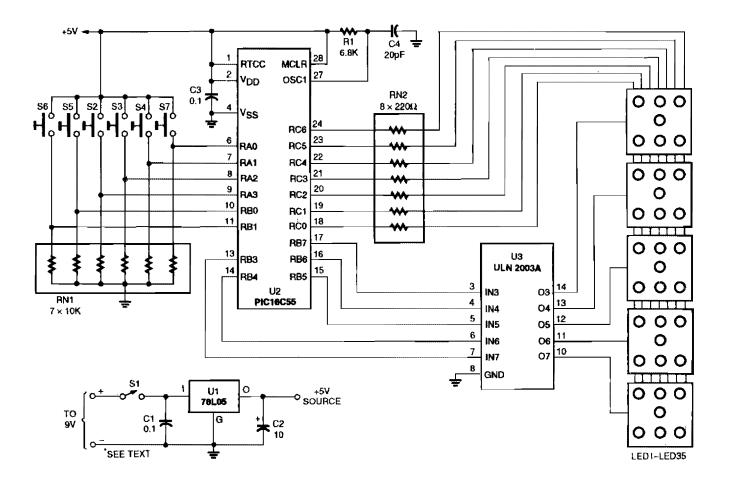

248

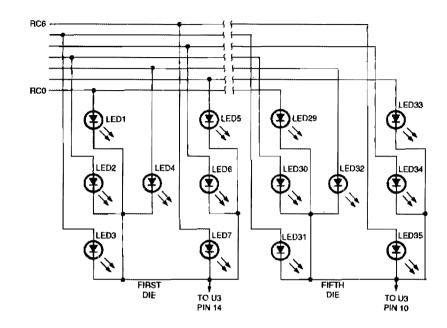


POPULAR ELECTRONICS

Using a microcontroller (U2) keeps the parts count and the cost of this 5-dice LED display relatively low. Z-dice uses five clusters of seven LEDs to represent the marks or "pips" on five dice. Buttons below each of the LED dice let the player mark a die to be rolled on the next throw. Marked dice show up as dimmed LEDs. Pressing the button to the right of the display rolls the marked dice. If the player changes his or her mind about rolling a particular die before pressing the roll button, he or she can unmark it by pressing its button a second time. If no dice are marked at the time the player presses the roll button, then all of the dice are marked to be rolled. A second press starts them rolling, animating the LEDs of the marked dice for a second or so before displaying the results of the roll. Z-Dice doesn't count rolls or keep score, so it's still up to the players to make sure that nobody cheats!

This diagram shows the wiring details of the dice display. For space and simplicity, only the first and last dice are shown. A programmed microcontroller is needed for this circuit. Refer to the original article for software.

Fig. 37-4

THREE-INPUT FIRST-RESPONSE MONITOR

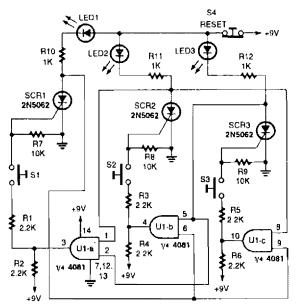

POPULAR ELECTRONICS

ELECTRONIC COIN TOSS

14

4

15

+9V

R4

680**Ω**

C2

100

3 LED2

2 ^{LED}

16

U1

4017

13 8

°s1

Q1

2N2647

R2

470Ω

R3

47Ω

₩ R1

47K

ĘC1

.1




Integrated circuit U1 is connected in a two-stage counter circuit that counts "one-two" over and over as long as clock pulses enter pin 14 of the 4017. When the clock pulses stop, one of the LEDs will remain on, indicating the last even or odd count. Designate one LED as "heads" and the other as "tails" and you have an electronic coin flipper.

Fig. 37-5

Fig. 37-6

ELECTRONIC ONE-ARM BANDIT

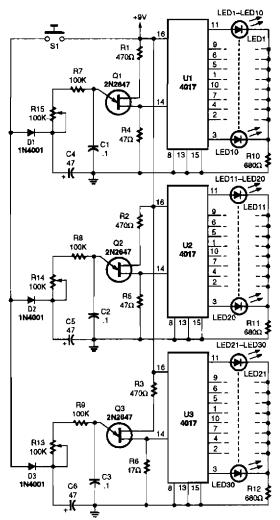


POPULAR ELECTRONICS

Fig. 37-7

The one-arm bandit circuit is made up of three clock circuits and three counter/readout circuits. A single roll switch, S1, turns on all three clocks at the same time. When S1 is closed, capacitors C4, C5, and C6 are charged through D31, D32, and D33 to about 8 V. After S1 is released, the three clocks run, taking energy from the three charged capacitors. As the capacitors discharge, the three clocks begin to slow down, producing the effect of the drums in a mechanical bandit slowing to a stop.

The 4017's 10-output LEDs can be numbered or designated as apples, cherries, bells, wild cards, or anything you like to make the game more interesting. Additional logic circuitry can be added to the 4017 outputs to sound an alert or turn on a light when any three numbers or output items match.

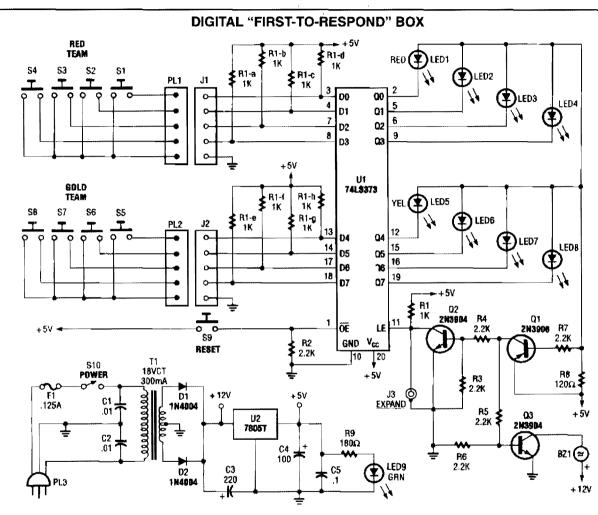
Three potentiometers, R12, R13, and R14, can be varied for each roll to change the clock's frequency and the roll rate.



POPULAR ELECTRONICS

Fig. 37-8

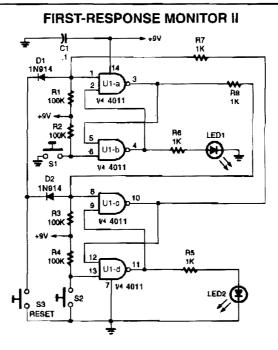This device is useful for quizzes and games to determine first response. U1 is an octal D type latch IC, an 74LS373. When a button is pushed, this circuit lights the corresponding LED. Q1 conducts, sounding an alarm (BZ1) connected to driver Q3, and Q1 supplies bias to Q2, disabling the rest of the latches in U1.




POPULAR ELECTRONICS

Fig. 37-9

Two interlocking flip flops are used to detect the first of two inputs. S1 and S2 are input devices, but a logical-level signal can be substituted.

ANALOG FIRST-RESPONSE MONITOR

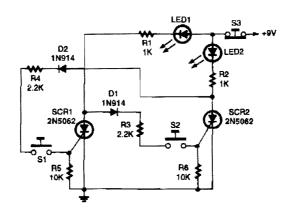


POPULAR ELECTRONICS

Fig. 37-10

The analog first-response monitor is built around a pair of cross-coupled SCRs, each of which receives its gate trigger current from the anode of the other SCR.

WHEEL OF FORTUNE

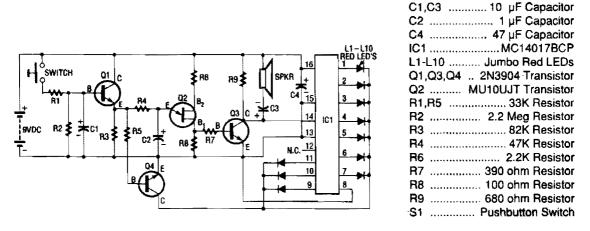

POPULAR ELECTRONICS

Fig. 37-11

The oscillation of Q2 is amplified by Q3 and fed to Johnson counter IC1. The output of IC1 drives the LEDs in sequence to give the impression of a spinning red ball.


38

Humidity Sensor Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Humidity Monitor Digital Relative Humidity Gauge

HUMIDITY MONITOR

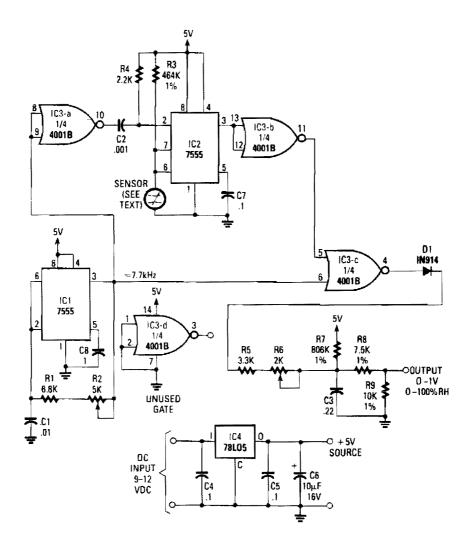


RADIO-ELECTRONICS

Fig. 38-1

This circuit uses a Phillips capacitive humidity sensor that has a ΔC variation of 45 pF over 0 to 100 pF RH. IC2 is an oscillator whose frequency is determined by the RH sensor. It is compared to fixed oscillator, and the difference frequency is taken by IC3C and rectified, outputting a 0- to 1-V signal for RH between 0 and 100%.

DIGITAL RELATIVE HUMIDITY GAUGE

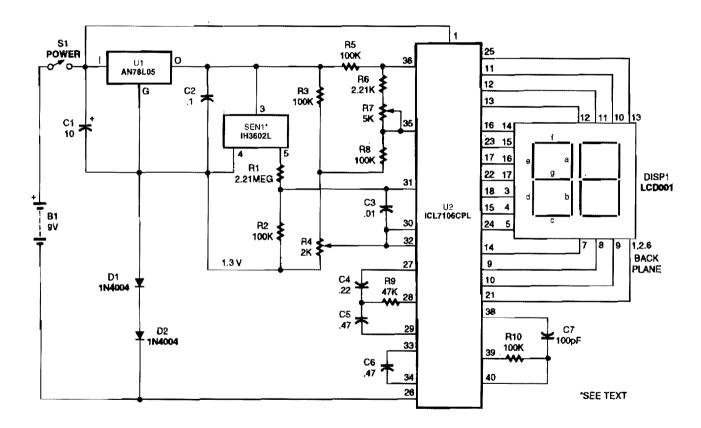

POPULAR ELECTRONICS

Fig. 38-2


Sensor SEN1 outputs a dc voltage that varies linearly with relative humidity. This dc voltage is fed through R1 and R2 to A/D converter chip U2. Zero set is performed with R4. The LCD display is calibrated with R7 to read 0 to 100 percent.

39

Indicator Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

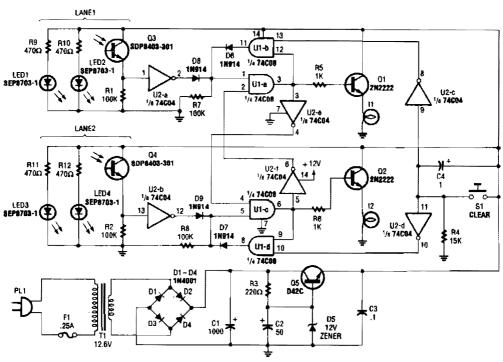Model Car Derby Winner Indicator Current Indicator Receiver Signal-Strength Indicator LED Output Indicator for 555 Circuits




MODEL CAR DERBY WINNER INDICATOR

POPULAR ELECTRONICS

Fig. 39-1

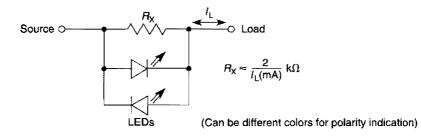This derby-winner indicator uses infrared emitters and sensors to detect a car crossing the finish line. The first car to finish locks out the data from the second car, and the system can be reset by pressing S1.






WILLIAM SHEETS

Fig. 39-2

An LED requires 1.5 to 3 V across its terminals to light. This circuit uses a resistor shunt in series with source and load to produce this drop and cause the LED to light. At higher currents (>100 mA) use limiting resistors in series with LEDs to limit current to a safe value.


RECEIVER SIGNAL-STRENGTH INDICATOR

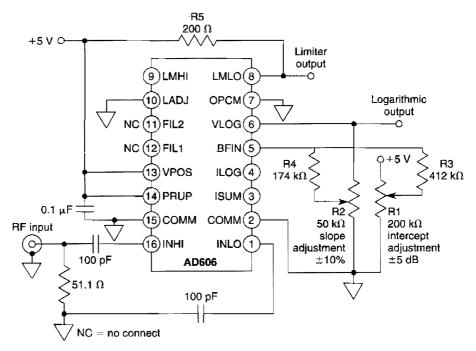

ANALOG DEVICES

Fig. 39-3

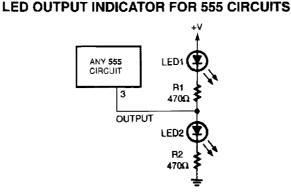Using an AD606 log amplifier, this indicator gives a logarithmic output of +0.3 V at -80-dBm input to +3.5 V at 10-dBm input. Frequency range is to 50 MHz for this IC device.



POPULAR ELECTRONICS, JANUARY 1994, P. 73

A pair of LEDs connected as shown here can be used with just about any low-frequency 555 oscillator to give high-/low-output indications. When the output goes high LED2 turns on, and when the output goes low LED1 turns on.


Fig. 39-4

40

Infrared Circuits

 T_{he} sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Audio-Modulated IR Transmitter Audible IR Detector Wireless IR Headphone Transmitter TV Remote-Control Relay Single-Tone Infrared Control Transmitter IR Illuminator for Night-Vision TV Cameras and Scopes Low-Power Infrared Data-Link Receiver Infrared Body Heat Detector **IR** Detector Circuit Steady-Tone Infrared Transmitter FM Infrared Receiver for Audio Reception General-Purpose IR Receiver Wireless IR Headphone Receiver Pulse Frequency-Modulated IR Transmitter Single-Tone Infrared Receiver Audible-Output Infrared Receiver

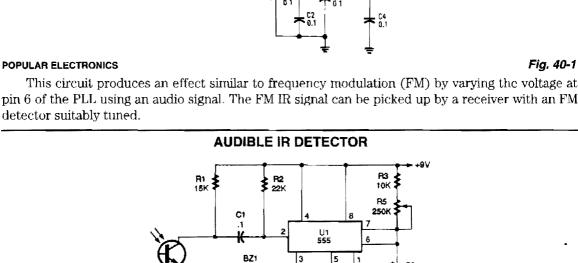

(Z

ED1

L1402

POPULAR ELECTRONICS

An IR-detector circuit offers an audible (as well as a visual) output, and also stretches the on time of the detected pulse to make the output easier to see, as shown.

4700

C2 .05 83

10K

R5 250K

¥#


Photoresistor Q1 detects a remote's IR output pulse and sends a negative-going pulse to the trigger input (pin) of the 555 IC, U1. The 555 is connected in a one-shot timer circuit; the output (pin 3) on time is set by the values of C_3 , R_3 , and R_5 . When an input pulse is detected, pin 3 goes high, lighting LED1 and activating the piezo buzzer, BZ1.


For longer output pulses, set R_5 to its maximum resistance value. To lengthen the circuit's ontime range, increase the value of C_3 , and to shorten the on-time range lower the value of C_3 .

Fig. 40-1

262

Fig. 40-2

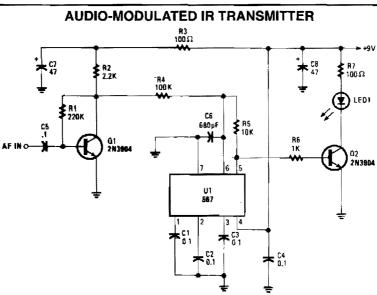

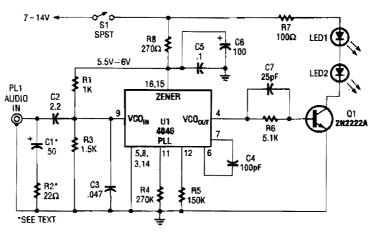


WIRELESS IR HEADPHONE TRANSMITTER

POPULAR ELECTRONICS

Fig. 40-3

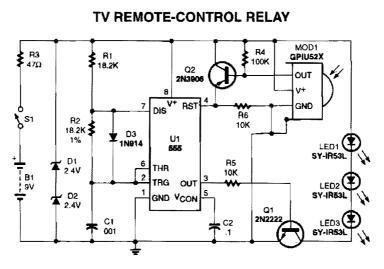
Audio input from PL1 frequency modulates the VCO section of a 4046 PLL chip. The VCO output drives Q1, a switching transistor. Q1 drives two IR LEDs. The signal produced is around 100 kHz, FM carrier VCO sensitivity is around 7.5 kHz/V.



POPULAR ELECTRONICS

Fig. 40-4

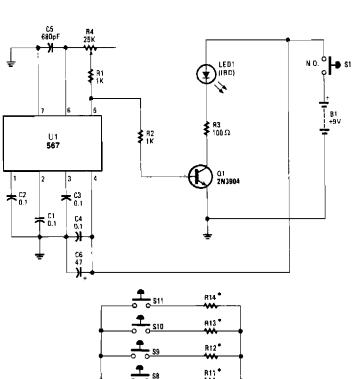This circuit functions as an IR "repeater" to extend the range of your TV remote control. MOD1 is a P/N GP1U52X IR detector and the receiver is available as Radio Shack P/N 276-137.



R10*

R9*

85*

SEE TEXT

S)

S3

SINGLE-TONE INFRARED CONTROL TRANSMITTER


POPULAR ELECTRONICS

Fig. 40-5

A modulated beam of IR light is produced by this transmitter. This circuit can be used for on/off controls or tone (CW) communications. The pot can be replaced by several pushbuttons and resistors, as shown for multitone applications.

U1 567

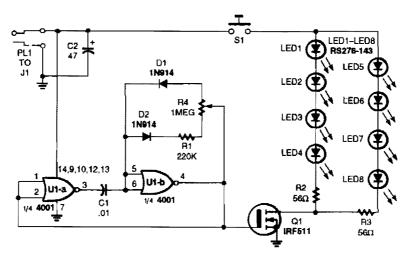IR ILLUMINATOR FOR NIGHT-VISION TV CAMERAS AND SCOPES




POPULAR ELECTRONICS

Fig. 40-6

This source uses LEDs and an astable oscillator to control the switch, duty-cycle, and effective IR illumination output.

LOW-POWER INFRARED DATA-LINK RECEIVER

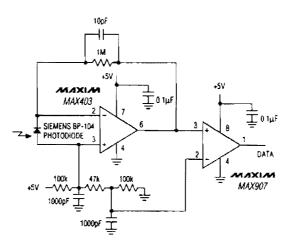


MAXIM

Fig. 40-7

The Maxim MAX403 in this circuit consumes only 1 mA and is capable of speeds over 1 MBPS.

INFRARED BODY-HEAT DETECTOR

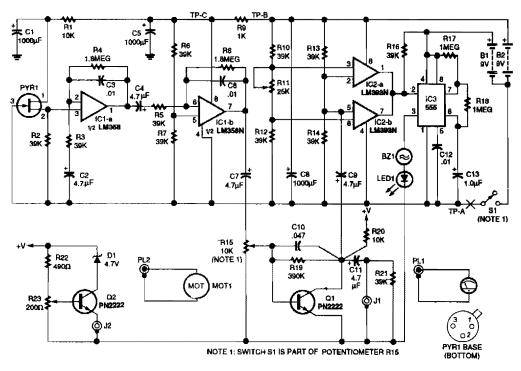


ELECTRONICS NOW

Flg. 40-8

This circuit uses a pyroelectric detector to detect IR emissions in the 6- to 14-micron range. It is useful for security or infrared experiments. PYR1 is a pyroelectric IR detector. The unit should be mounted in a case with an IR lens to focus energy on the detector.



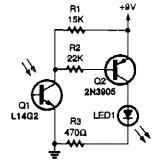
The circuit uses an IR phototransistor, Q1, to detect a remote control's IR output signal. A PNP transistor, Q2, then amplifies Q1's output and lights LED1. That indicates that an infrared signal has been detected by the phototransistor, or in other words, that your remote control works.



POPULAR ELECTRONICS

Fig. 40-9

STEADY-TONE INFRARED TRANSMITTER

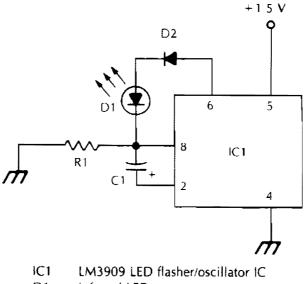


- D1 infrared LED
- D2 diode (1N4148, 1N914, or similar)
- C1 1 µF 5 V electrolytic capacitor
- R1 1.5 kΩ ¼ W 5% resistor

McGRAW-HILL

Fig. 40-10

This oscillator pulses an IR LED at about 1000 Hz. It should be useful as a test for lining up IR communications links or setting up fiber-optic cables, etc.


FM INFRARED RECEIVER FOR AUDIO RECEPTION

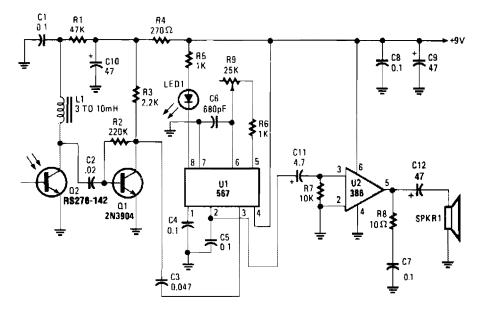

POPULAR ELECTRONICS

Fig. 40-11

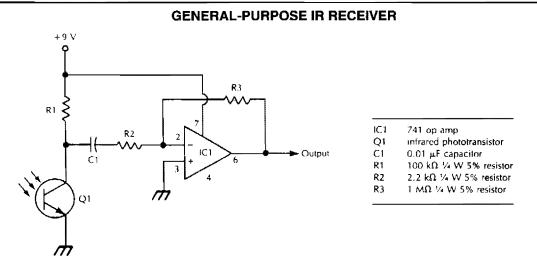Modulated IR energy strikes Q2, a phototransistor. Q1 is a tuned amplifier, and feeds PLL detector U1. U2 is an audio amplifier that drives a speaker.




McGRAW-HILL

Fig. 40-12

Suitable for amplitude-modulated IR beams, this receiver provides an audio signal that corresponds to the modulation envelope. Phototransistor Q1 should be properly mounted and shielded from stray light. This receiver should drive a small earphone directly.


WIRELESS IR HEADPHONE RECEIVER

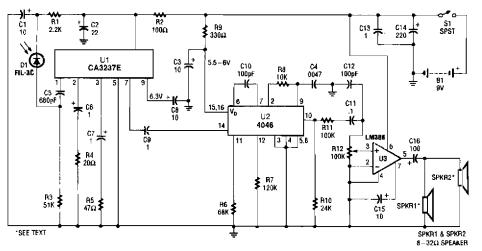

POPULAR ELECTRONICS

Fig. 40-13

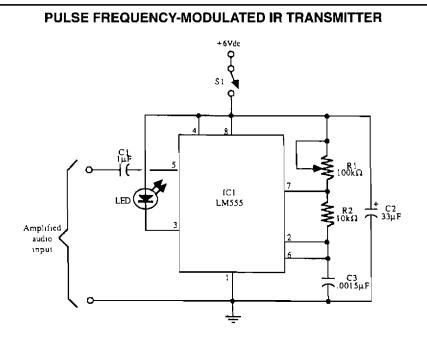A photodiode D1 feeds high gain IR remote control preamp IC, a CA3237E. U2 is a PLL FM dctector tuned to around 100 kHz. The detector output is amplified by U3 and it can drive a speaker or a set of headphones.




McGRAW-HILL

Fig. 40-14

Schematic diagram for the pulse frequency-modulated LED transmitter. Adjust the frequency by rotating R1. With components shown, the frequency range is between 8 and 48 kHz.

SINGLE-TONE INFRARED RECEIVER

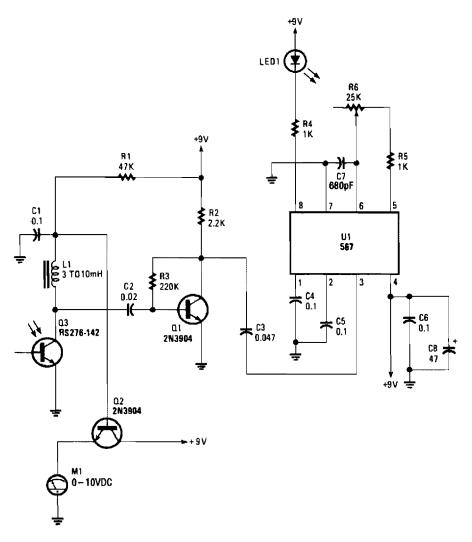


POPULAR ELECTRONICS

Fig. 40-15

Phototransistor Q3 acts as a sensor that detects modulated IR energy. Q1 is an amplifier and U1 is a tone decoder. LED1 lights on reception of an IR signal with proper tone modulation.

AUDIBLE-OUTPUT INFRARED RECEIVER

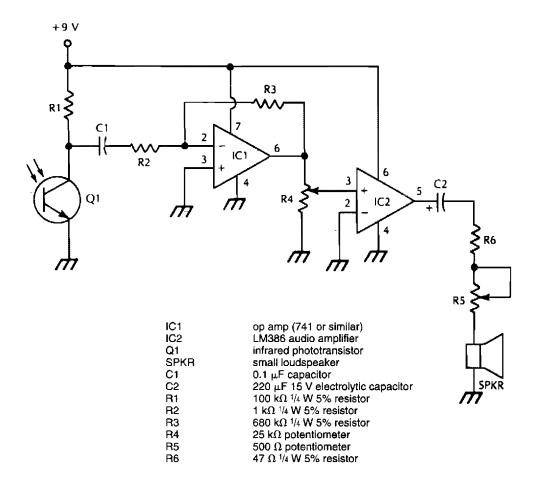

McGRAW-HILL

Flg. 40-16

This receiver is designed to demodulate amplitude-modulated (AM) IR light beams and will drive a loudspeaker. R5 is an auxiliary volume control and it could be omitted. Q1 should be suitably mounted and shielded from stray light pickup.


41

Instrumentation Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

×100 Instrumentation Amplifier Instrumentation Amplifier Variable-Gain Differential-Input Instrumentation Amplifier Programmable Gain Instrumentation Amplifier for Single-Supply Applications Differential-Input Instrumentation Amplifier High Input-Impedance Instrumentation Amplifier ac-Coupled Instrumentation Amplifier Low-Noise Instrumentation Amplifier Low-Power Instrumentation Amplifier Ultra-Low-Noise Single-Supply Instrumentation Amplifier Instrumentation Amplifier

×100 INSTRUMENTATION AMPLIFIER

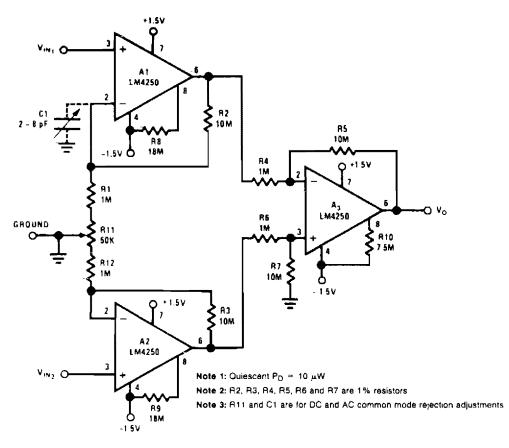


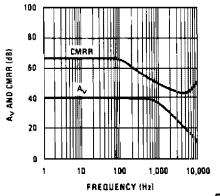


Fig. 41-1

NATIONAL SEMICONDUCTOR

CMRR vs. frequency.

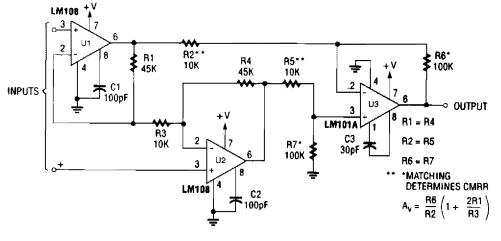


INSTRUMENTATION AMPLIFIER

LINEAR TECHNOLOGY


Fig. 41-2

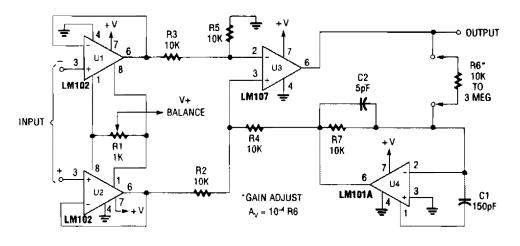VARIABLE-GAIN DIFFERENTIAL INPUT INSTRUMENTATION AMPLIFIER



POPULAR ELECTRONICS


Fig. 41-3

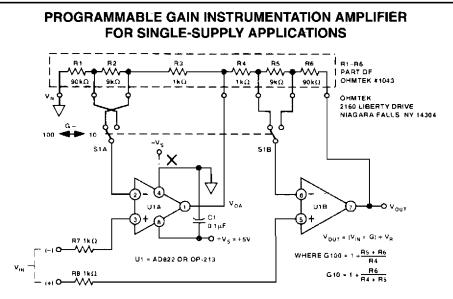


ANALOG DEVICES

Fig. 41-4

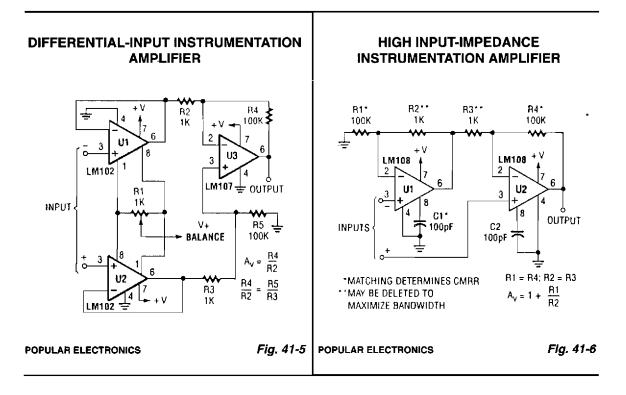This is a two-op-amp programmable-gain instrumentation amplifier for single-supply applications. U1A and U1B are Analog Devices AD822 or OP-213 ICs.




ac-COUPLED INSTRUMENTATION AMPLIFIER

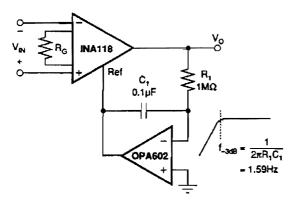


DESIRED GAIN	R _G (Ω)	NEAREST 1% R _c (Ω)
1	NC	NC
2	50.00k	49.9k
5	12.50k	12.4k
10	5.556k	5.62k
20	2.632k	2.61k
50	1.02k	1.02k
100	505.1	511
200	251.3	249
500	100.2	100
1000	50.05	49.9
2000	25.01	24.9
5000	10.00	10
10000	5.001	4.99

BURR-BROWN

Fig. 41-7

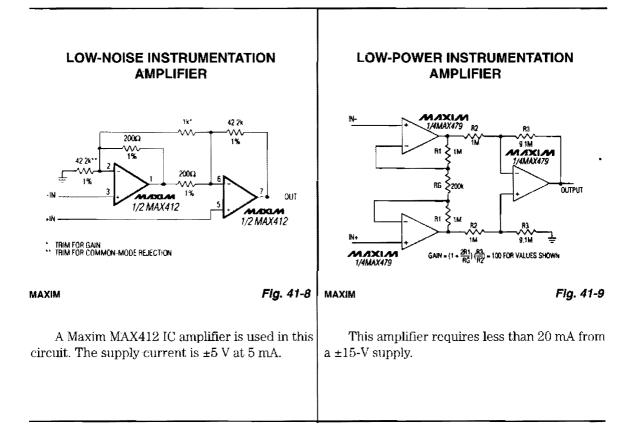

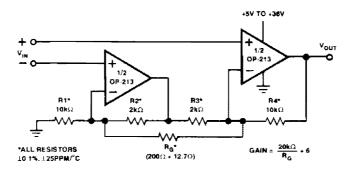
ULTRA-LOW-NOISE SINGLE-SUPPLY INSTRUMENTATION AMPLIFIER



ANALOG DEVICES

Fig. 41-10

INSTRUMENTATION AMPLIFIER

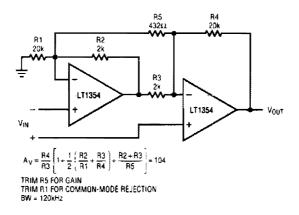


LINEAR TECHNOLOGY

Fig. 41-11


Integrator Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

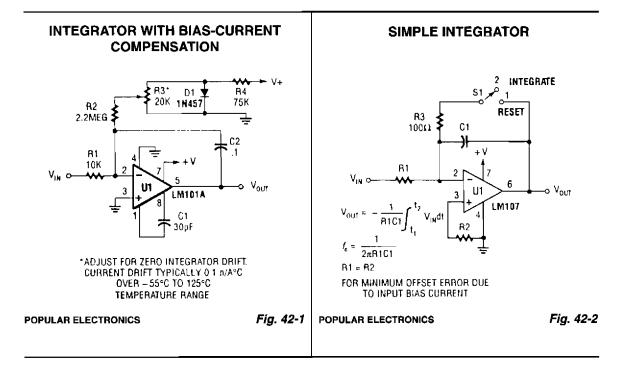Integrator with Bias-Current Compensation Simple Integrator ac Integrator



ac INTEGRATOR

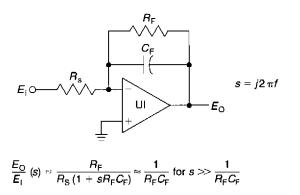

WILLIAM SHEETS

This op-amp circuit can be used with a wide variety of op amps. The values of R_i and R_i depend on gain, but will be 1 k Ω to 1 M Ω in most cases. C_i depends on the pole frequency needed. U1 is a 741-type op amp, etc.


Fig. 42-3

Interface Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Timer/ac Line Interface Interfacing Resistive Transducers

TIMER/ac LINE INTERFACE

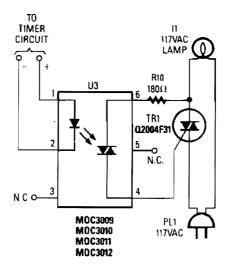


POPULAR ELECTRONICS

Fig. 43-1

This circuit illustrates the use of an optoisolator to enable the control of a triac connected to the ac line and load, while maintaining dc and ac isolation between the ac line and the timer circuit. A 555 or other timer circuit can be used.

INTERFACING RESISTIVE TRANSDUCERS

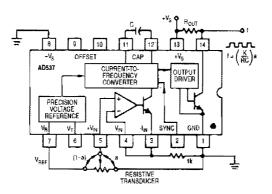

ANALOG DEVICES

All types of resistive-element transducers, such as servo-pots, level indicators, thermistors, photosensors, strain gages, and so on, can be directly connected to the AD537. The scale-correction factor, K, is a function of resistance, varying from 0.65 to 0.98 for values from 3 to 100 k Ω .


Fig. 43-2

Inverter Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

SCR Inverter and Trigger Circuit Simple Inverter Vehicle Audio Amplifier Inverter Positive-to-Negative dc/dc Inverter 1-kW 10-kHz Sine-Wave Inverter

SCR INVERTER AND TRIGGER CIRCUIT

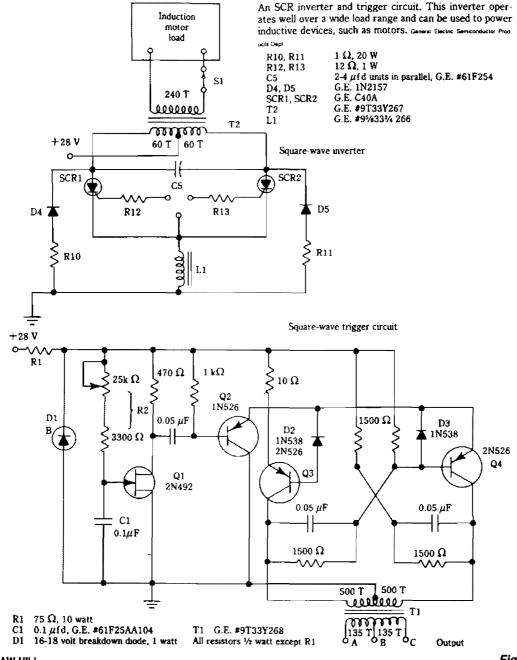


McGRAW-HILL

Fig. 44-1

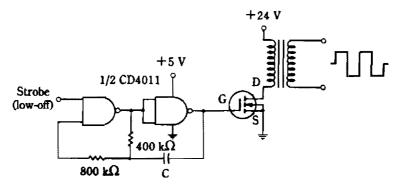
In this circuit, L1 and C5 are used as commutating elements. L1 resonates with C5 at the frequency corresponding to the half period of the waveform.





McGRAW-HILL




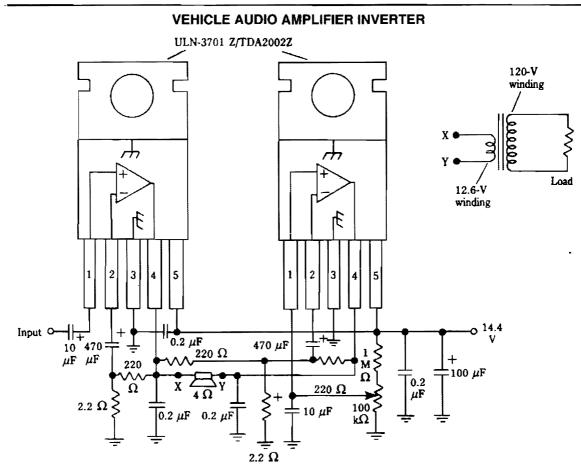

McGRAW-HILL


Fig. 44-3

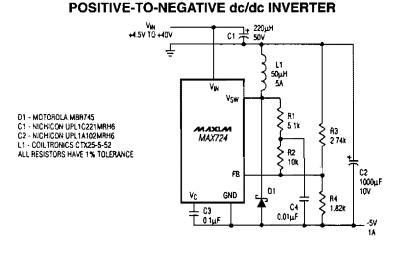An audio amplifier can drive a step-up transformer to obtain 120 Vac.



MAXIM

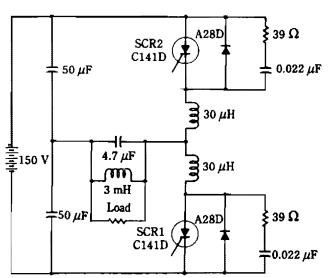If a source of negative 5 Vdc is needed and only a positive supply is available, this circuit can be used.



1-kW 10-kHz SINE-WAVE INVERTER

McGRAW-HILL

Fig. 44-5

Fig. 44-4


SCRs can produce considerable power at frequencies up to 30 kHz or more. This circuit can supply 1 kW at 10 kHz. The load is shown as an equivalent load, and practically this will be the primary of the transformer for isolation purposes. The power supply can be a 120-V bridge rectifier and filter combination.

Ion Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Negative Ion Generator Ion-Sensing Electroscope Negative Ion Generator Ion Detector

NEGATIVE ION GENERATOR

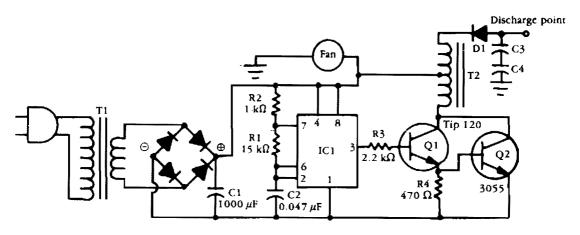


McGRAW-HILL

Fig. 45-1

An NE555 drives a Darlington connected pair of transistors. T1 is a small high-voltage transformer or auto ignition coil, B/W TV flyback, etc. C3, C4, and D1 must be rated for 10 to 15 kV. The fan blows air across the discharge point.

ION-SENSING ELECTROSCOPE

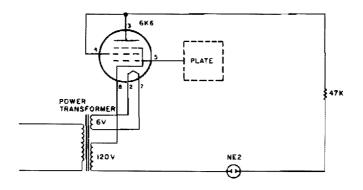


73 AMATEUR RADIO TODAY

Negative ions are sensed by a plate antenna. A negative charge induced on the plate cuts off a vacuum tube, causing the neon indicator to go out.

Fig. 45-2


NEGATIVE ION GENERATOR

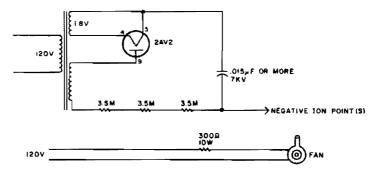

73 AMATEUR RADIO TODAY

Fig. 45-3

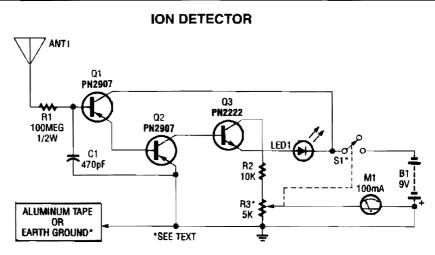In this circuit, air is circulated past a pointed electrode that has a high negative voltage applied to it. The transformer is a small 4- to 6-kV output type with a filament winding. A good source of parts is a discarded electronic bug catcher.



ELECTRONIC HOBBYISTS HANDBOOK




This circuit detects static charges and free ions in the air. It can be used to indicate the presence of ion emissions, high-voltage leakage, static electricity, electrostatic fields, etc. The ground connection is made by either an earth ground or by touching the aluminum foil electrode with your hand. M1 is a 100-µA meter. R3 is a sensitivity control.

Laser Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

High-Current Drive Circuit for Single Heterostructure Laser Diodes 12-V High-Voltage Supply for He-Ne Laser Light-Beam Receiver and Sound Effects Generator for Laser Pistols Laser Diode Transmitter IR Laser Light Detector PLL IR Laser Light Receiver Op-Amp Diode Laser Driver Laser de Supply IC Laser Diode Driver Pulsed Double Heterostructure Laser Driver

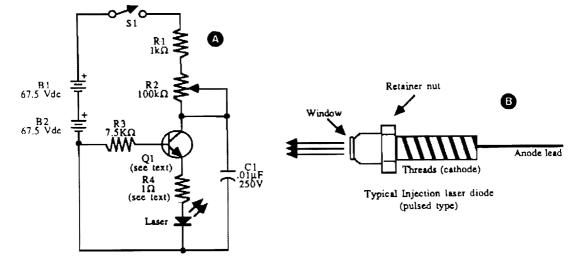HIGH-CURRENT DRIVE CIRCUIT FOR SINGLE HETEROSTRUCTURE LASER DIODES



(A) High-current drive circuit for a single heterostructure laser diode. (B) Power leads for the typical sh laser diode, showing single lead for the anode.


R 1	1 kilohm resistor
R2	100 kilohm potentiometer
R3	7.5 kilohm resistor
R4	1 ohm resistor, carbon composition, 5 watts
C1	0.01 μ F capacitor, 250 V or higher
Ql	2N2222 or equivalent; see text
B1,B2	67.5 Vdc batteries
Misc.	Single heterostructure laser diode, heatsink

McGRAW-HILL

The transistor is operated in the avalanche mode. You might need to try several 2N2222 devices before finding one that oscillates. R2 is adjusted for optimum oscillation. This supply provides pulse of 10 to 20 amps at about 50 ns.

Fig. 46-1

12-V HIGH-VOLTAGE SUPPLY FOR HE-NE LASER

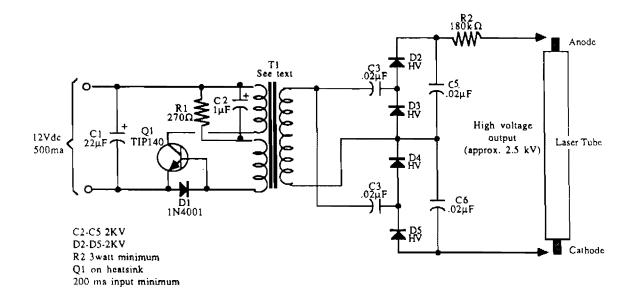

McGRAW-HILL


Fig. 46-2

T1 is a 6-V:330-V dc/dc inverter transformer with a 57.4:1 turn ratio, rated at 7 W.

$\mathbf{R1}$	$270-\Omega$ resistor
R2	180-k Ω resistor, 3 to 5 W
C1	22-µF electrolytic capacitor
C2	1-µF electrolytic capacitor
C3-C6	0.02-μF capacitor, 1 kV or more
D1	1N4001 diode
D2-D5	High-voltage diode (3 kV or more)
Q1	TIP 140 power transistor
T 1	High-voltage dc-to-dc converter transformer; see text for specifications

All resistors are 5 to 10% tolerance, % W, unless otherwise indicated. All capacitors are 10 to 20% tolerance, rated 35 V or more, unless otherwise indicated.

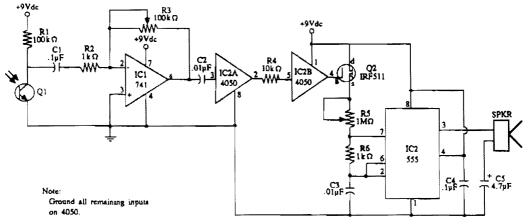LIGHT-BEAM RECEIVER AND SOUND EFFECTS GENERATOR FOR LASER PISTOLS



McGRAW-HILL

Fig. 46-3

Schematic diagram for light beam amplifier and sound-effects generator (using a 555 timer IC and speaker). The light striking Q1 generates a siren-like sound.


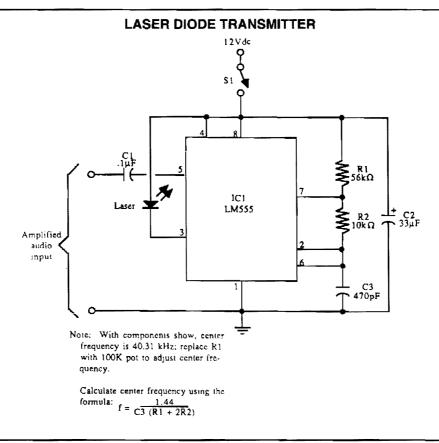


Fig. 46-4

IR LASER LIGHT DETECTOR

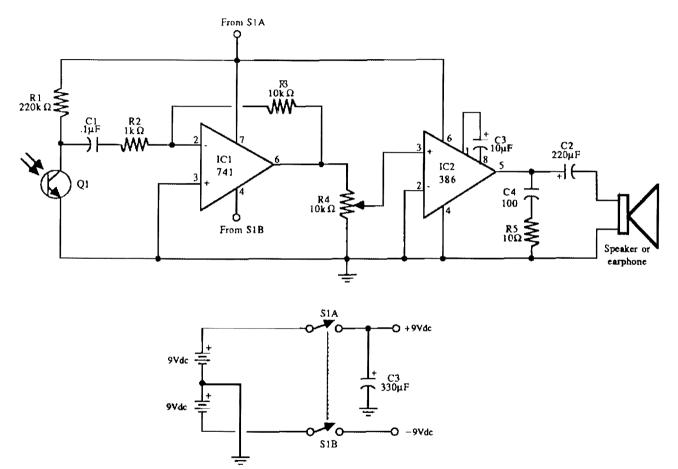


McGRAW-HILL

Fig. 46-5

The universal laser light detector. The output of the LM386 audio amplifier can be connected to a small 8- Ω speaker or earphone. Two 9-V batteries provide power. Decrease R1 to lower sensitivity; increase R3 to increase gain of the op amp (avoid very high gain or the op amp might oscillate). Q1 is an infrared phototransistor.

293

PLL IR LASER LIGHT RECEIVER

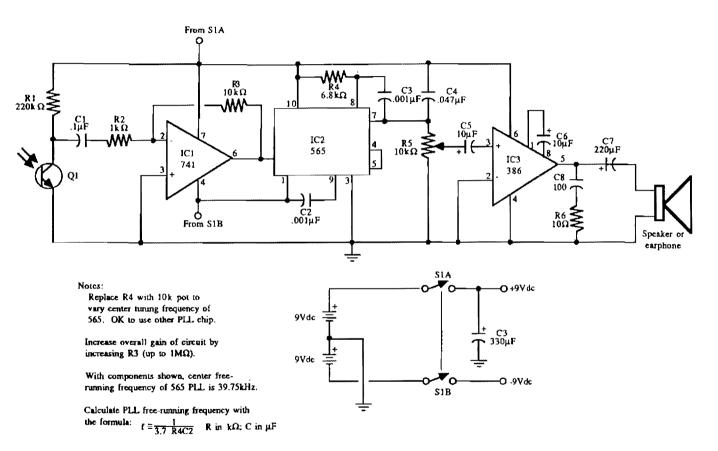


McGRAW-HILL

Fig. 46-6

Circuit schematics for the 555-based PLL laser light PFM receiver. Although R4 is shown as a resistor, you might want to substitute it with a 10-k Ω precision potentiometer so that you can "dial in" the center frequency of the transmitter. Experiment with the value of C_1 for the best high-frequency response. Notice that circuit is functionally identical to the laser light detector/receiver shown in the figure, but with the addition of the 565.

OP-AMP DIODE LASER DRIVER

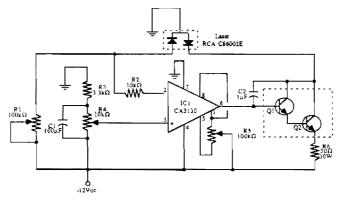


McGRAW-HILL

Fig. 46-7

This circuit is one way to automatically adjust drive current using a discrete op amp. Use the transistors specified or replace them with a suitable Darlington power transistor (such as TIP 120).

IC1	RCA CA 313 operational amplifier
R1, R5	100-k Ω potentiometer
R2	10 -k Ω resistor
R3	3.3 -k Ω potentiometer
R4	10-k Ω potentiometer
$\mathbf{R6}$	$30-\Omega$, 10-W resistor
C1	100-µF electrolytic capacitor
C2	0.1-µF disc capacitor
Q1	2N2101 transistor
Q2	2N3585 transistor
Laser	RCA C86002 (or equivalent laser diode)

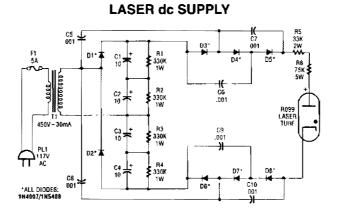


POPULAR ELECTRONICS

Fig. 46-8

The supply provides about 6 kVdc when open circuited, dropping to around 1375 Vdc when loaded. The R099 is a laser tube.


IC LASER DIODE DRIVER

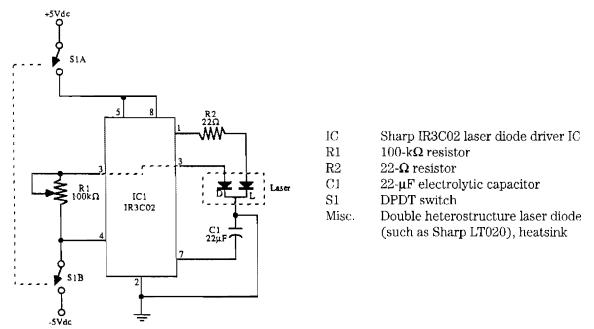

McGRAW-HILL



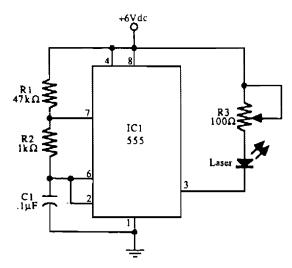PULSED DOUBLE-HETEROSTRUCTURE LASER DRIVER



- IC1 555 timer IC
- R1 47-k Ω resistor
- R2 $1-k\Omega$ resistor
- R3 100-k Ω potentiometer
- C1 $0.1-\mu F$ disc capacitor
- Misc. Double heterostructure laser diode, heatsink

All resistors are 5 to 10% tolerance, % W. All capacitors are 10 to 20% tolerance, rated 35 V or more.






Light-Controlled Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Traffic Light-Sequencer Circuit **Tachometer Adapter** Sun-Tracking Circuit for Solar Arrays **Optical Fringe Counter** Low-Noise Light Sensor with dc Servo Photodiode Amplifier Light-Switched LED Blinker Single-Supply Photodiode Amplifier Light-Controlled Monostable Darkness Monitor Programmable Light-Activated Relay Traffic Light Controller Colorimeter **Eight Decade Light Meter** LED Lightwave Communications Transmitter LED Lightwave Receiver Solar Power Supply Solar Power Supply with Linear Regulator Photodiode Log Converter/Transmitter Rechargeable Solar Power for Sun Tracker

TRAFFIC LIGHT-SEQUENCER CIRCUIT

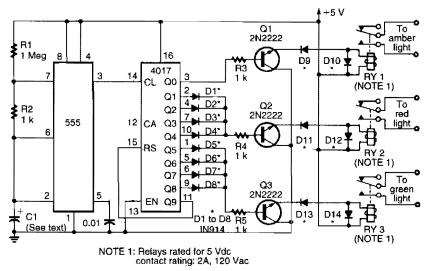


ELECTRONICS NOW

Fig. 47-1

This circuit uses a 555 timer to drive a 4017 counter. The counter outputs drive transistor relay drivers. Time lights "on" can be proportioned by changing connections of outputs of counter.

TACHOMETER ADAPTER

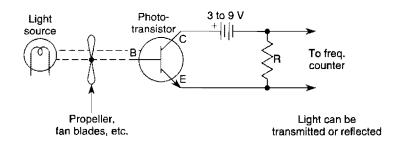

WILLIAM SHEETS


Fig. 47-2

Use of a phototransistor and light source can enable a frequency counter to act as a tachometer:

$$RPM = 60 \times \frac{Frequency \ Counter \ Reading \ Hz}{\# \ Blades \ or \ Spokes}$$

The light source is interrupted by the number of propeller blades, fan blades, spokes, or other marking. *R* can be anywhere from 1 to $100 \text{ k}\Omega$. Try several values for best results.

SUN-TRACKING CIRCUIT FOR SOLAR ARRAYS

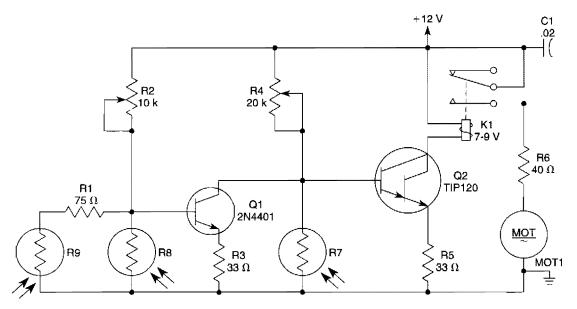

POPULAR ELECTRONICS


Fig. 47-3

The sun tracker uses a combination of three photoresistors. R7, R8, and R9, to ensure that the circuit will follow the sun during the day, but not look for it at night. Photoresistor cells, R7, R8, and R9 have a value of 160 Ω in full sunlight and 4880 Ω in the shade, that is not absolutely critical. R7 is mounted in a "well" with a narrow slit so that sunlight falls upon it only when the photoresistor is pointed directly at the sun. When that occurs, the resistance of R7 drops. That photoresistor and potentiometer R4 form a voltage divider at the base of the Darlington transistor, Q1. When R7's resistance is low, Q1 will be kept off.

When the sun swings a little westward, R7 will no longer be in sunlight, causing its resistance to go up, which raises the base voltage of Q1 and turns that Darlington on. That, in turn closes the relay, K1, providing current to the drive motor, MOT1, which is a 1.5-Vdc, low-torque hobby motor. The motor then turns slowly (resistor R6 limits the maximum current to the motor and keeps it from running too fast), putting R7 in direct sunlight again; Q1's base voltage then drops and the tracker stops. That is repeated again and again as the sun moves across the sky. Photoresistor R8 is mounted on the outside of the well so that it receives a wide angle of full sunlight. When the sun is shining, R8's resistance is low, keeping Q2 turned off, and allowing the tracker to act as described, without interference. But if the sun "slips" behind a cloud, R8's resistance goes high, producing a forward bias on the base of Q2. That turns that transistor on and sinks the base of Q1 to near ground so that Q1 then remains off. That immobilizes the tracker drive; that also keeps the drive shut down in the dark of night.

Photoresistor, R9, is the dawn sensor. It is mounted on the back of the sun tracker. When the tracker stops at sunset, pointing toward the west, R9 is pointing toward the east. When the sun rises the following morning and shines on R9, its resistance goes low, turning Q2 off and allowing Q1's base to go high. That presents current to the relay and therefore to the drive motor, causing the tracker to swing around to the east.

OPTICAL FRINGE COUNTER

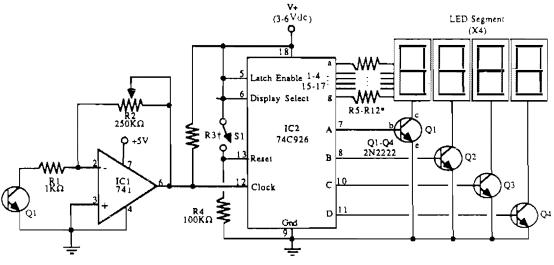

* Not required if +V is 4V or less


† Optional. 10K Ω to 10M Ω , for sensitivity

McGRAW-HILL

Fig. 47-4

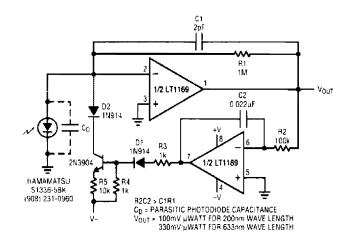For work with interferometer and optical experiments, this fringe counter can be useful. Photo transistor Q1 provides light and dark sensing. As the sensor is moved across the fringe pattern alternate light and dark areas translate to an electrical waveform. This is amplified by IC1 and counted by IC2. A Schmitt trigger circuit can be added, if desired.






LINEAR TECHNOLOGY

Fig. 47-5

PHOTODIODE AMPLIFIER

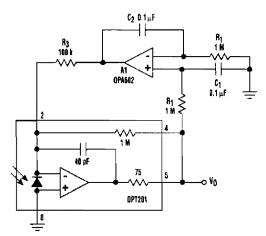


ELECTRONIC DESIGN

Fig. 47-6

A photodiode amplifier combined with a dc-restoration circuit will reject low-frequency ambient background light, easing measurement of a light signal.

LIGHT-SWITCHED LED BLINKER

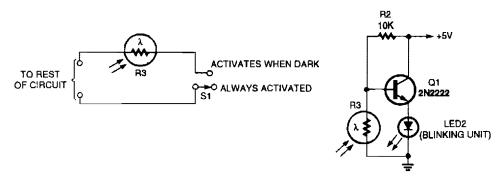


POPULAR ELECTRONICS

Fig. 47-7

This circuit can be used to flash an LED during periods of darkness. Use it for burglar alarm simulators for boats, docks, autos, etc.


SINGLE-SUPPLY PHOTODIODE AMPLIFIER

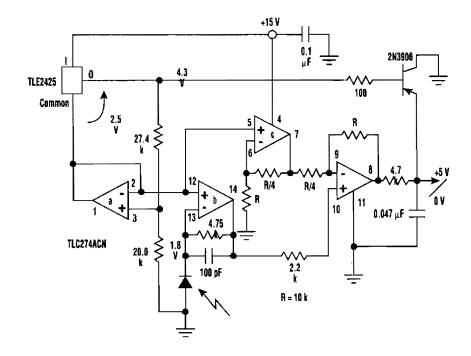

ELECTRONIC DESIGN



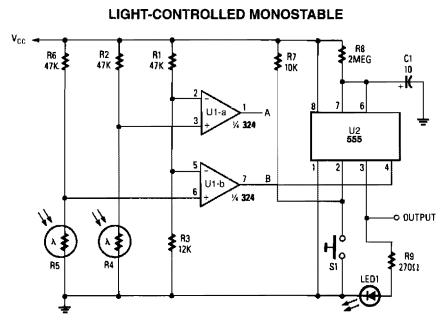
This circuit provides a reverse-bias operating point and output voltage offset and uses a singlepolarity power supply. The floating reference voltage from TLE2425 serves to bias the diode in a reverse-polarity mode. It also provides a clamping level at the output. Consequently, linear response to illumination is maintained for a 5-V range from dark current to full sunlight conditions.



POPULAR ELECTRONICS

Fig. 47-9

The light-controlled monostable was produced by combining a 555 monostable multivibrator with a pair of light-controlled comparators. The circuit can be used to enable the operation of the load device, depending on the time of day. During the daylight hours, the timer U2, is disabled, and so produces no output. However, during the nighttime hours, U2 is enabled by the output of U1-b so that pressing S1 initiates a timing cycle, which activates LED1 for a time determined by R8 and C1.

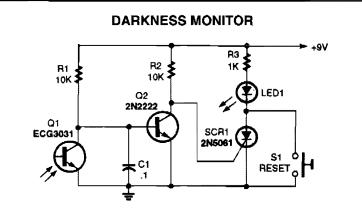


POPULAR ELECTRONICS

Fig. 47-10

When light strikes detector Q1, Q2 is cut off, allowing bias to reach SCR1, triggering SCR1 and lighting LED1. S1 resets the circuit.

PROGRAMMABLE LIGHT-ACTIVATED RELAY

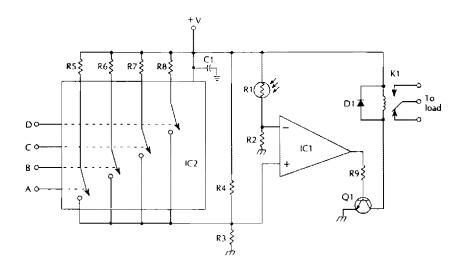


McGRAW-HILL

Fig. 47-11

Digital inputs A, B, C, D select different light levels by varying the value of bridge circuit resistance $R_4\!.$

IC1	741 op amp
IC2	CD4066 quad bilateral switch
$\mathbf{Q}1$	NPN transistor (2N2222, 2N3904, or similar)
D1	diode (1N4002, or similar)
C1	$0.1-\mu F$ capacitor
R1	photoresistor
R2, R3	390-kΩ, ¼-W 5% resistor
R4, R5	1-MΩ, ¼-W 5% resistor
R6	820-kΩ, ¼-W 5% resistor
R7	470-k Ω , ¼-W 5% resistor
R8	270-k Ω , ¼-W 5% resistor
R9	100-k Ω , ¼-W 5% resistor
K1	relay to suit load

TRAFFIC LIGHT CONTROLLER

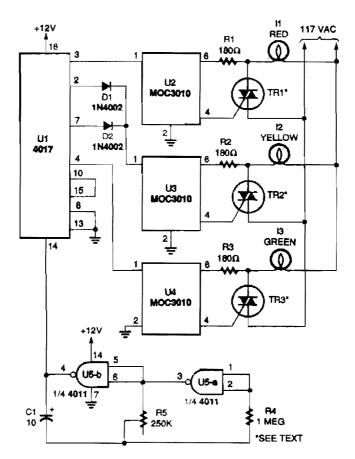

POPULAR ELECTRONICS

Oscillator U5A-B drives a 4017 divide-by-10 counter. The first output of U1 appears at pin 3, which supplies a positive voltage to U2, a MOC 3010 optocoupler/triac-driver IC, turning it and triac TR1 on. That lights I1, the red lamp. The second output appears at pin 2 and passes through D1 to the second MOC 3010, U3, thereby lighting the yellow lamp, I2. The third output at pin 4 turns on UJ4 and the green lamp, I3. The fourth output at pin 7 travels through D2 and into U3 to light the yellow lamp, I2, again.

If you would like the traffic-light system to follow the normal sequence of green, yellow, and red, make the following circuit changes: Disconnect pins 10 and 15 of U1 from each other. Remove D1 and D2 and connect pin 2 of U1 to pin 1 of U3. Then connect pins 7 and pins 15 of U1 together. Use U2 to drive I3 (the green light) and U4 for I1 (the red light).

Fig. 47-12

COLORIMETER

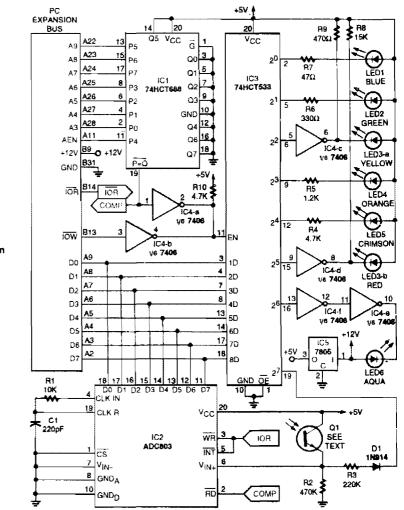


TABLE 1-LED COLORS AND CODES

LED	Wave- length	Color	Activation Value
LED1 LED2 LED3-a LED3-b LED4 LED5 LED5 LED6	470 nm 560 nm 590 nm 700 nm 630 nm 665 nm 482 nm	Blue Green Yellow Red Orange Crimsor Aqua	$2^{0} = 1$ $2^{1} = 2$ $2^{2} = 4$ $2^{3} = 8$ $2^{4} = 16$ $2^{5} = 32$ $2^{8} = 64$

ELECTRONICS NOW

Fig. 47-13

COLORIMETER (Cont.)

LISTING 1—CALIBRATION PROGRAM

10 'CALIBRAT.BAS calibration program
20 CLS:KEY OFF:N=0:ADR=512:OPEN*R*,1,*CAL1*,16:OPEN*r*,2,*ca12*,24 30 FIELD 1, 2AS B\$, 2AS G\$, 2AS Y\$, 2AS O\$, 2AS C\$, 2AS R\$, 2AS A5, 2AS AGS 40 FIELD 2,24AS IDS 50 PRINT "reference number",N+1:CUT ADR,255;BEEP:INPUT "Enter Name of Standard or 'E' To End"; TEMPIDS 50 IF TEMPIDS="E" OR TEMPIDS="e" THEN N=0: GOTO 200 or 'E' 70 IF TEMPIDS "n" THEN INPUT enter n to redo ", N:N=N-1:GOTO 50 80 N=N+1:FOR H=0 TO 7:K=0:IF H<7 THEN Z=2^H ELSE Z=194 90 OUT ADR, Z: FOR I=1 TO 500:NEXT I 100 POR J=1 TO 50:R=K+INP(ADR) :NEXT J 110 IF H=0 THEN LSET BS=MKIS(K) 120 IF H=1 THEN LSET G\$=MKI\$(K) 130 IF H=2 THEN LSET Y\$=MKI\$(K) 140 IF H=3 THEN LSET OS=MRIS(K) 150 IF H=4 THEN LSET CS=MRIS(K) 160 IF H=5 THEN LSET R\$=MKIS(K) 170 IF H=6 THEN LSET A\$=MKIS(K) 180 IF H#7 THEN LSET AGS=MKIS(K) 190 NEXT H:LSET IDS=TEMPIDS: PUT 1, N: PUT 2, N:CLS: GOTO 50 200 N=N+1:GET #1,N:GET #2,N:IF N>(LOF(1)/16) THEN END 210 B=CVI (B\$) : G=CVI (G\$) : Y=CVI (Y\$) : O=CVI (O\$) : C=CVI (C\$) : R=CVI (R\$) : A=CVI (A\$) : AG=CVI (AGS) 220 PRINT N. IDS: GOTO 200


LISTING 2—IDENTIFICATION PROGRAM

1 'IDENTIFY.BAS identification program 10 ADR=512:OUT ADR,255:PRINT:INPUT *Hit Enter To Scan/Identify Unknown Color";A 20 IF A=9 THEN RUN fcal 30 ERP=1E+20:OPEN*R*,1,*call*,16 40 FOR H=O TO 7:K=0:IF H<7 THEN 2=2^H ELSE 2=194 50 OUT ADR, 2: FOR I=1 TO 500:NEXT I 60 FOR J=1 TO 50:K=K+INP(ADR):NEXT J 70 IF H=0 THEN BU=K ELSE IF H=1 THEN GU=K ELSE IF H=2 THEN YU=K 80 IF H=3 THEN OU=K ELSE IF H=4 THEN CU=K ELSE IF H=5 THEN RU=K 90 IF H=6 THEN AU=K ELSE IF H=7 THEN AGU=K 100 NEXT H:BEEP 110 OUT 512,255: OPEN"r",2, "cal2",24: FIELD 1,2AS B\$,2AS G\$,2AS Y\$,2AS O\$,2AS C\$,2 AS R\$,2AS A\$,2AS A\$;B=LOF(1)/16 120 FOR N=1 TO B:GET #1,N:IF ABS(CVI(B\$)-BU)>400 THEN 140 130 ER=(CVI(B\$)-BU)^2+(CVI(G\$)-GU)^2+(CVI(Y\$)-YU)^2+(CVI(O\$)-OU)^2+(CVI(C\$)-ດບ ົ້າ 2+ (CVI (R\$) -RU) ^2+1*((CVI (A\$) -AU) ^2) +2*((CVI (A\$\$) -AGU) ^2) : IF ER<ERP THEN ERD-ER:NN=N 140 NEXT N 150 FIELD 2, 24AS ID\$: GET #2,NN 160 CLS:PRINT "Best Color Match", ID\$:PRINT"Relative Error", ERP:PRINT"reference number*, NN:RUN

A hardware/software combination activates. In turn, one of several LEDs emits a portion of the visible spectrum. A phototransistor measures the light reflected by the surface being measured, and an 8-bit analog-to-digital converter (ADC) translates the phototransistor's output into a digital format that the computer can interpret. Seven LEDs (blue, aqua, green, yellow, orange, crimson, and red) provide a range of readings across the visible spectrum. Lack of spectral continuity among adjacent LED colors could skew results, so the circuit provides built-in compensation for this error.

Two simple BASIC programs control the circuit's operation. One allows you to define a set of standards by measuring known color samples and recording the values with an associated name. The other program measures unknown samples and provides the best match with the defined standards, as well as a relative error factor.

EIGHT-DECADE LIGHT METER

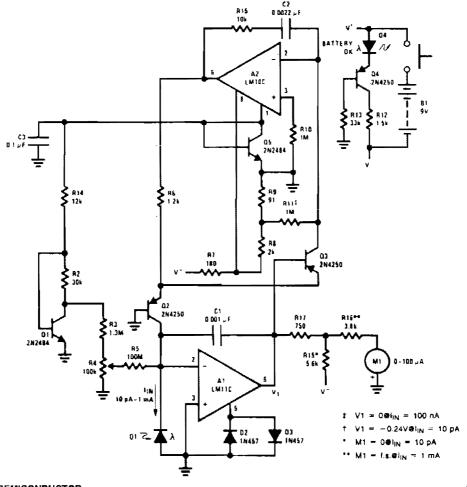


NATIONAL SEMICONDUCTOR

Fig. 47-14

A logarithmic amplifier is adapted to a battery-powered light meter. An LM10, combined op amp and reference, is used for the second amplifier and to provide the regulated voltage for offsetting the logging circuit and powering the bias-current compensation. This can provide input current resolution of better than ± 2 pA over 15 to 55° C. Because a meter is the output indicator, there is no need to optimize frequency compensation. Low-cost single transistors are used for logging because the temperature range is limited. The meter is protected from overloads by clamp diodes D2 and D3.

Silicon photodiodes are more sensitive to infrared than visible light, so an appropriate filter must be used for photography. Alternately, gallium-arsenide-phosphide diodes with suppressed IR response are becoming available.


LED LIGHTWAVE COMMUNICATIONS TRANSMITTER

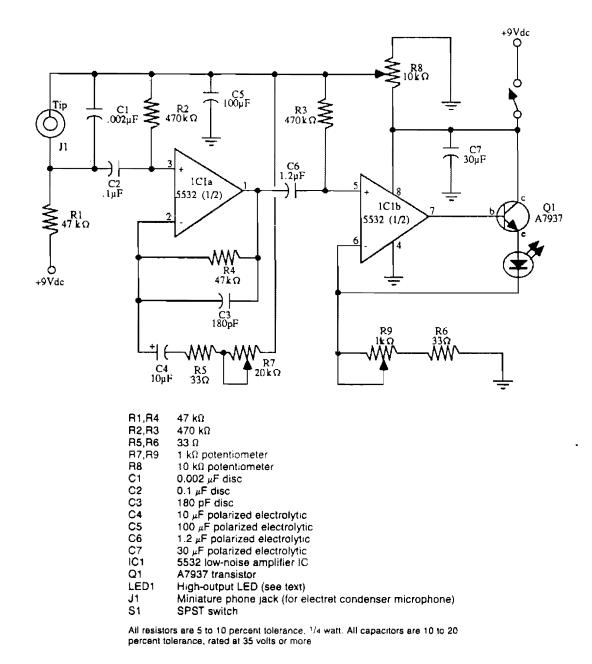

McGRAW-HILL


Fig. 47-15

LED LIGHTWAVE RECEIVER

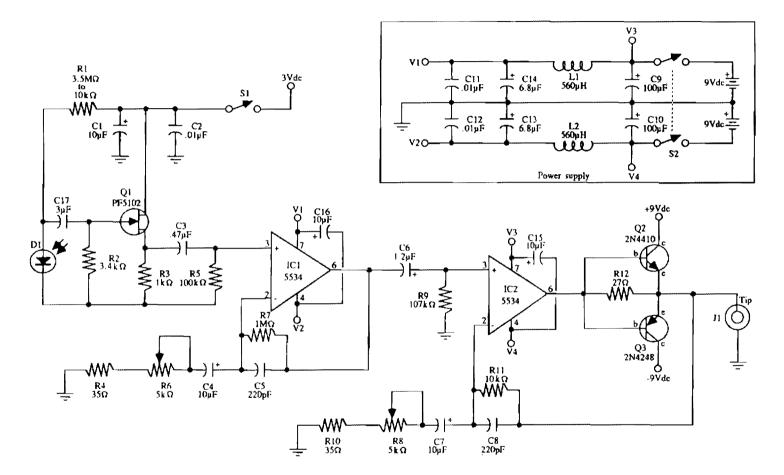


٠

Fig. 47-16

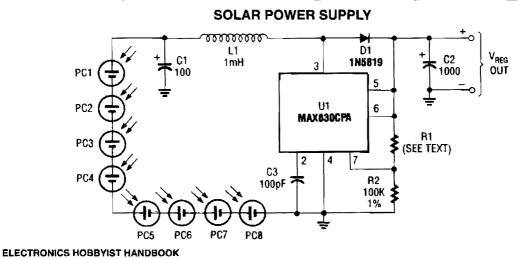



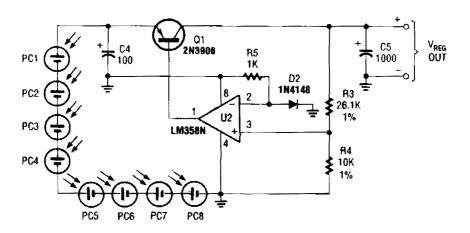This circuit delivers either 4.8 or 7.2 V regulated at 15 mA with a 3-V input from a bank of photocells. R1 should be $453 \text{ k}\Omega$ for a 7.2-V output and 274 k Ω for a 4.8-Vdc output. Regulator efficiency is around 70%. This should be considered when selecting suitable solar cells.




SOLAR POWER SUPPLY WITH LINEAR REGULATOR

ELECTRONICS HOBBYIST HANDBOOK

Flg. 47-18

This regulator delivers a constant 2.4 Vdc for powering small devices that run on two AA cells, such as cassettes and small radios. Regulator drop is about 0.3 volt. This should be considered when choosing solar cells. Load current is typically 125 mA.


PHOTODIODE LOG CONVERTER/TRANSMITTER

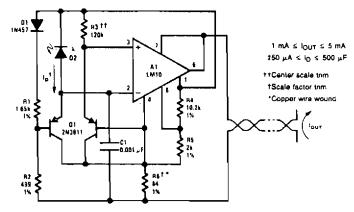

NATIONAL SEMICONDUCTOR

Fig. 47-19

A logarithmic conversion is made on the output current of a photodiode to compress a fourdecade, light-intensity variation into a standard transmission range. The circuit is balanced at midrange, where R3 should be chosen so that the current through it equals the photodiode current. The log-conversion slope is temperature compensated with R6. Setting the reference output to 1.22 V gives a current through R2 that is proportional to absolute temperature because of D1 so that this level-shift voltage matches the temperature coefficient of R6. C1 has been added so that large-area photodiodes with high capacitance do not cause frequency instabilities.

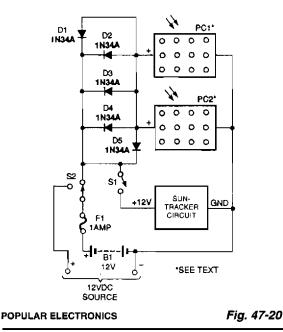

RECHARGEABLE SOLAR POWER FOR SUN TRACKER


This application circuit provides rechargeable solar power for the sun tracker, as well as for another 12-volt device. PC1 and PC2 can be mounted on sun tracker assembly.

Logic Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Logic State Change Indicator Combinatorial Logic Multiplexer AND Gate Relay "AND" Circuit Relay "OR" Circuit

LOGIC STATE-CHANGE INDICATOR

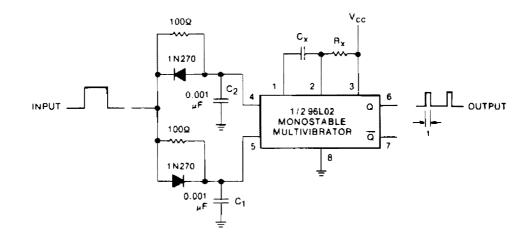

NASA TECH BRIEFS

Fig. 48-1


A circuit consisting of a one-shot multivibrator IC, a pair of diodes, and some resistors and capacitors delivers an output pulse when the logic state at its input terminal changes—either from high to low or from low to high. Thus, this circuit can serve as a state-change indicator or as a frequency doubler for a square-wave input.

Any monostable can be used; the arrangement in the figure achieves low power dissipation (80 milliwatts) by using half of a Fairchild 96L02 transistor-transistor-logic dual multivibrator. The 96L02 is triggered when pins 3 and 5 are high and pin 4 changes state from low to high. It also triggers if pin 3 is high, pin 4 is low.

The circuit shown here allows these conditions to be satisfied with a single input terminal, plus the fixed bias on pin 3; the arrangement of resistors, capacitors, and diodes automatically biases pin 5 high when transmitting a rising transition to pin 4 and biases pin 4 low when applying a falling transition to pin 5.

For example, if the input terminal has been low and then goes high, C1 charges through a forward-biased diode that shunts its 100- Ω resistor; therefore pin 5 goes high immediately. C2 charges through 100 Ω ; however, because its diode is back-biased, the rising level is not applied to pin 4 until 5 is already high. Therefore, the conditions for triggering an output pulse are satisfied.

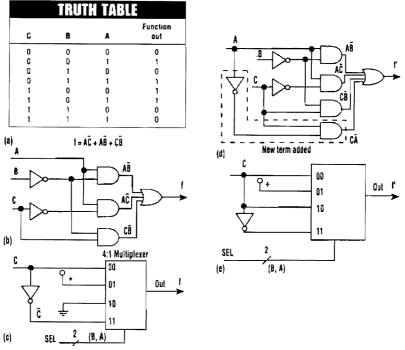The output pulse duration, t, is set by the value of time constant $R_{\rm v}C_{\rm v}$.




COMBINATORIAL LOGIC MULTIPLEXER

ELECTRONIC DESIGN

Fig. 48-2

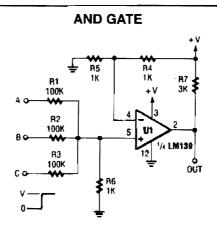
Combinatorial logic can be implemented simply by using a multiplexer instead of logic gates. Shown are the truth table (A), its logic circuit (B), and the multiplexer connections (C). If the logic circuitry is changed (D), the multiplexer would be reconnected (E).



POPULAR ELECTRONICS

Fig. 48-3

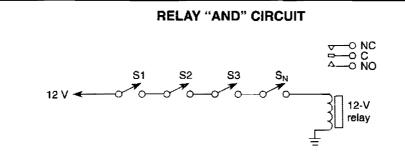An LM139 is configured as an AND gate (TTL or CMOS is usually used). With this idea, you can use leftover IC sections and save an extra package in some instances.




WILLIAM SHEETS

Fig. 48-4

All switches S1 through $\rm S_n$ must be closed to operate the relay. If one opens, the relay drops out. Use this circuit for burglar alarms, etc.

RELAY "OR" CIRCUIT

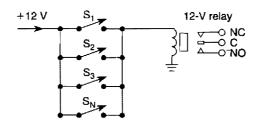

WILLIAM SHEETS

Fig. 48-5

Closing any switch S1, S2, S3, or S_n will actuate the relay (N = any number). Use this circuit for burglar alarms, etc.


49

Mathematical Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Low-Cost One-Quadrant Multiplier/Divider Low-Cost Accurate Square-Root Circuit Low-Cost Accurate Squaring Circuit Bridge Linearizing Function Square Rooter Analog Variable Multiplier/Divider Difference of Squares Approximation for Sin ϕ Simple Analog Averaging Circuit Simple Analog Multiplier $\Delta\%$ Ratio Computer

LOW-COST ONE-QUADRANT MULTIPLIER/DIVIDER

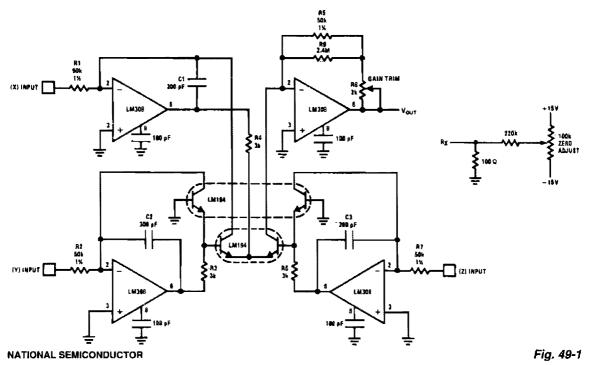

This circuit will produce an output that is proportional to the product of the (X) and (Y) inputs divided by the Z input. All inputs must be positive, limiting operation to one quadrant. For very low level inputs, the offset voltage in the LM308s might create large percentage errors referred to input. A simple scheme for offsetting any of the LM308s to zero is shown in dotted line; the positive input of the appropriate LM308 is simply tied to R_x instead of ground for zeroing. The summing mode of operation on all inputs allows easy scaling on any or all-inputs. Simply set the input resistor equal to $(V_{in(max)}/(200 \ \mu A), V_{out}$ is equal to:


$$V_{\text{out}} = \frac{\left(\frac{X}{R_1}\right)\left(\frac{Y}{R_2}\right)(R_5)}{\frac{Z}{R_5}}$$

Input voltages above the supply voltage are allowed because of the summing mode of operation. Several inputs can be summed at X, Y, and Z.

For a simple $(X) \cdot (Y)$ or (X)/Z function, the unused input must be tied to the reference voltage. Perturbations in this reference will be seen at the output as scale factor changes, so a stable reference is necessary for precision work. For less critical applications, the unused input can be tied to the positive supply, with

$$R = \frac{V+}{200 \,\mu\text{A}}$$

LOW-COST ACCURATE SQUARE-ROOT CIRCUIT

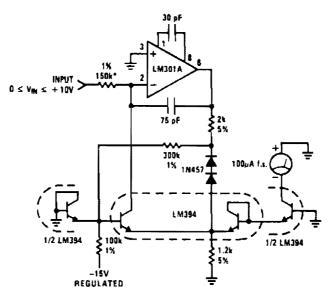


*Trim for full scale accuracy.

NATIONAL SEMICONDUCTOR

Flg. 49-2

The circuit will generate a square-root function, accurately and inexpensively. The output is a current that can be used to drive a meter directly or be converted to a voltage with a summing junction current-to-voltage converter. The -15-V supply is used as a reference, so it must be stable. A 1% change in the -15-V supply will give a ½% shift in output reading. No positive supply is required when an LM301A is used because its inputs can be used at the same voltage as the positive supply (ground). The two 1N457 diodes and the 300-k Ω resistor are used to temperature-compensate the current through the diode-connected ½LM394.

LOW-COST ACCURATE SQUARING CIRCUIT

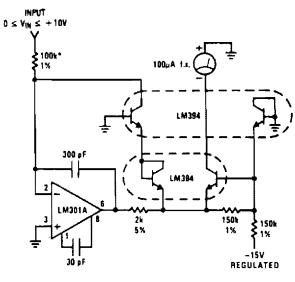


*Trim for full scale accuracy.

NATIONAL SEMICONDUCTOR

The circuit shown will square the input signal and deliver the result as an output current. Fullscale input is 10 V, but this can be changed simply by changing the value of the 100-k Ω input resistor. As in the square root circuit, the -15-V supply is used as the reference. In this case, however, a 1% shift in supply voltage produces a 1% shift in the output signal. The 150-k Ω resistor across the base-emitter of %LM394 provides slight temperature compensation of the reference current from the -15-V supply. For improved accuracy at low input signal levels, the offset voltage of the LM301A should be zeroed out, and a 100-k Ω resistor should be inserted in the positive input to provide input to provide optimum de balance.

Fig. 49-3

BRIDGE LINEARIZING FUNCTION

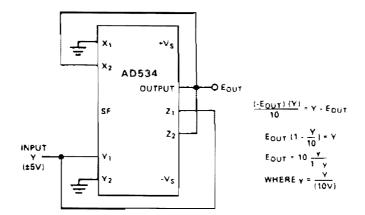

ANALOG DEVICES

If one arm of a Wheatstone Bridge varies from its nominal value by a factor, (1 + 2x), the voltage or current output of the bridge will be (with appropriate polarities):

$$y \approx \frac{x}{1+x}$$


Linear response requires very small x and, usually, preamplification. The circuit shown here enables large-deviation bridges to be used without losing linearity.

The circuit computes the inverse of the bridge function, i.e.,

$$x \approx \frac{y}{1+y}$$

Depending on which arm of the bridge varies, it might be necessary to reverse the polarity of the z connections.


Fig. 49-4

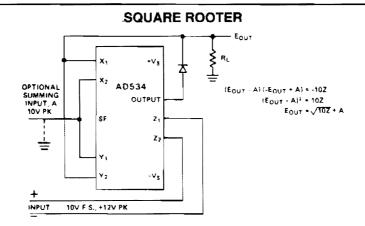

ANALOG DEVICES

Fig. 49-5

This illustration shows the connection of the AD534 for square-rooting, with differential inputs. The diode prevents a latching condition—common to this configuration—which would occur if the input momentarily changed polarity. As shown, the output is always positive; it can be changed to a negative output by reversing the diode polarity and interchanging the X inputs. Because the signal input is differential, all combinations of input and output polarities can be realized. If the output circuit does not provide a resistive load to ground, one should be connected to maintain diode conduction. For critical applications, the Z offset can be adjusted for greater accuracy below 1 V.

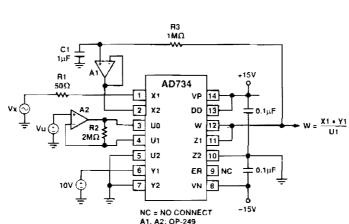


ANALOG VARIABLE MULTIPLIER/DIVIDER

ANALOG DEVICES

Fig. 49-6

An output voltage $(W = X_1 \times Y_1/U_1)$ is produced by this multiplier circuit. The AD734 is a fourquadrant multiplier.


DIFFERENCE OF SQUARES

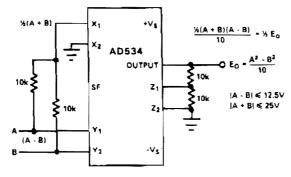

ANALOG DEVICES

Fig. 49-7

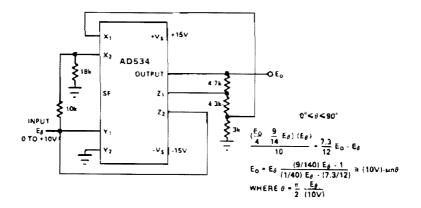A single AD534 can be used to compute the difference of the squares of two input signals. The function can be useful in vector computations, and in weighting the difference of two magnitudes to emphasize the greater nonlinearity.




APPROXIMATION FOR SIN ϕ

ANALOG DEVICES

The AD534 is remarkably easy to use in the implementation of the approximation formulas described in Chapter 2-1 of the *Nonlinear Circuits Handbook*. Many of these involve implicit loops to generate the function and previously required several additional op amps for the addition and subtraction of the various terms. This circuit is an example of what can be done with external resistors only. For ϕ between 0° and 90°, the approximation maintains a theoretical accuracy to within 0.5% of full-scale; 0.75% is practical with AD534L and 0.1% resistances were used.

Fig. 49-8

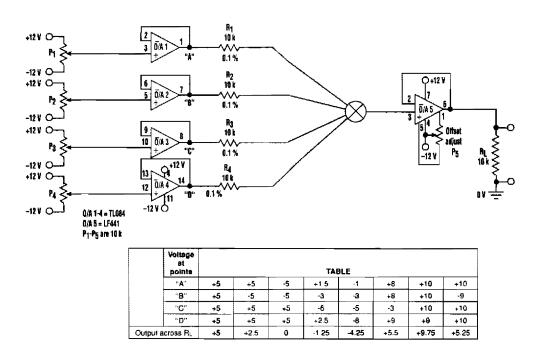

SIMPLE ANALOG AVERAGING CIRCUIT

ELECTRONIC DESIGN


Fig. 49-9

At times, an analog circuit that averages rather than sums can be quite handy. You won't usually find this type of circuit in op-amp books, possibly because the op amp is used only as a buffer. For best accuracy, an FET should be used with the offset adjusted out. In addition, the "averaging" resistors (R1 through R4) should be of close tolerance.

Looking at the test circuit, op amps 1 through 4 are used to alleviate interaction between adjustment potentiometers P1 through P4 and so that R1 through R4 see the same low impedance.

The table shows some arbitrarily set voltages and the resulting output voltage across $R_{\rm L}$.

SIMPLE ANALOG MULTIPLIER

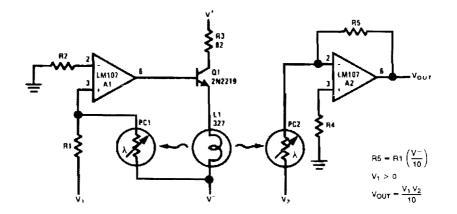

NATIONAL SEMICONDUCTOR


Fig. 49-10

Circuit operation can be understood by considering A2 as a controlled-gain amplifier, amplifying V_2 , whose gain depends on the ratio of the resistance of PC2 to R5 and by considering A1 as a control amplifier, which establishes the resistance of PC2 as a function of V1. In this way, $V_{\rm OUT}$ is a function of both V_1 and V_2 .

A1, the control amplifier, provides drive for the lamp, L1. When an input voltage, V_1 , is present, L1 is driven by A1 until the current to the summing junction from the negative supply through PC1 is equal to the current to the summing junction from V1 through R1. Because the negative supply voltage is fixed, this forces the resistance of PC1 to a value that is proportional to R1 and to the ratio of V_1 to V_2 . L1 also illuminates PC2 and, if the photoconductors are matched, causes PC2 to have a resistance equal to PC1.

A2, the controlled gain amplifier, acts as an inverting amplifier whose gain is equal to the ratio of the resistance of PC2 to R5. If R5 is chosen equal to the product of R_1 and V_- , then $V_{\rm OUT}$ becomes simply the product of V_1 and V_2 . R5 can be scaled in powers of 10 to provide any required output scale factor.

∆% RATIO COMPUTER

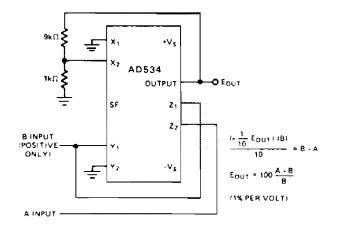

ANALOG DEVICES

Fig. 49-11

The percentage-deviation function is of practical value for many applications in measurement, testing, and control. For example, the output of this circuit might be applied to a pair of biased comparators to stimulate particular actions or displays, depending on whether the gain of a circuit under test were within limits, or deviating by a preset amount in either direction.

The indicated scale factor, 1%/V, is convenient. However, other sensitivities, from 10%/V to 0.1%/V, as required by the application, can be obtained by altering the feedback attenuation ratio, from 1 to 1%. Gain or attenuation is easily applied to the *A* signal externally for calibration to the normalized form.

50


Measuring and Test Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Electronic Level Single-Chip Digital Voltmeter Inductance with DVM Measuring Circuit Negative Reference Voltage Circuit Precision Current Source 1-kW Power Meter Logic Chip Tester Power Supply for 10-MHz Frequency Standard Three-Terminal Regulator Current Source Four-Wire Resistance Measurement Hookup Audio Frequency Meter ELF Monitor Strain-Gage Sensor Minute Marker **Digital Barometer Reference** Circuit Transistor Matching Circuit Auto-Ranging Digital Capacitance Meter Frequency Divider for 10-MHz Frequency Standard Electroscope **Optical Isolator Wattmeter Digital Three-Phase Wave Generator** Simple Test Audio Amplifier Gate Dip Oscillator I Accelerometer (G Meter) Circuit

Gate Dip Oscillator II Two Remote Meters Novel RF Power Meter Nanoammeter 1.5-V Logarithmic Light Level Meter ac Power Monitor 100-W Variable Resistor Simulator IMD Test Circuit for Pin Diodes VCO and Input Frequency Comparer ECG Amplifier with Right Leg Drive Power Transformer Tester 4- to 20-mA Process Controller Simple High-Current Measurer Analog Circuitry Calibrator Simple Signal Generator for Signal Tracing Simple Harmonic Distortion Analyzer Sound Subcarrier Generator Inductance and Capacitance Determiner with SWR Bridge Motorcycle Tune-Up Aid **50-MHz Frequency Counter** 10-MHz Frequency Standard **Programmable Capacitor Circuit** Programmable Resistor Circuit

ELECTRONIC LEVEL

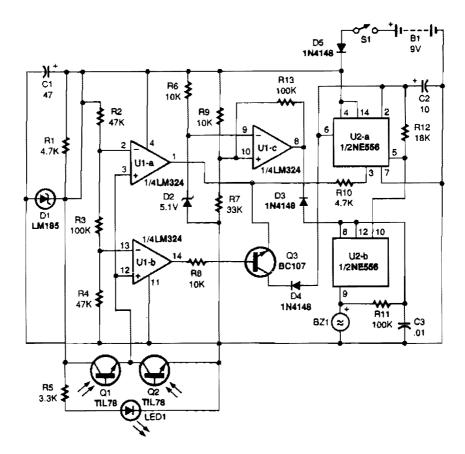


POPULAR ELECTRONICS

Flg. 50-1

The electronic level uses a pair of phototransistors and an infrared LED to sense bubble position. In this circuit, the amounts of infrared radiation received by phototransistors Q1 and Q2 are translated by op-amp U1 and dual-timer U2 into either a steady tone, or a fast- or slow-pulsing one.

SINGLE-CHIP DIGITAL VOLTMETER

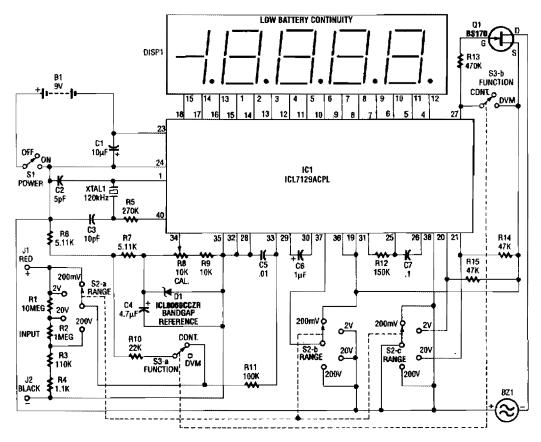


ELECTRONIC EXPERIMENTERS HANDBOOK

Fig. 50-2

This 4½-digit DVM circuit is built around a Maxim ICL7129ACPL A/D converter and LCD driver. An ICL8069 CCZR 1.2-V band-gap reference diode is used for a voltage reference. S2a-b-c select one of four ranges up to 200 V (maximum). The meter also has a piezoelectric buzzer for continuity testing. S3 selects either DVM or continuity. Crystal 1 can be changed to 100 kHz if maximum rejection of 50 Hz is desired. The crystal normally provides 120 kHz for best 60-Hz rejection. This is caused by the dual-slope conversion technique used in IC1.



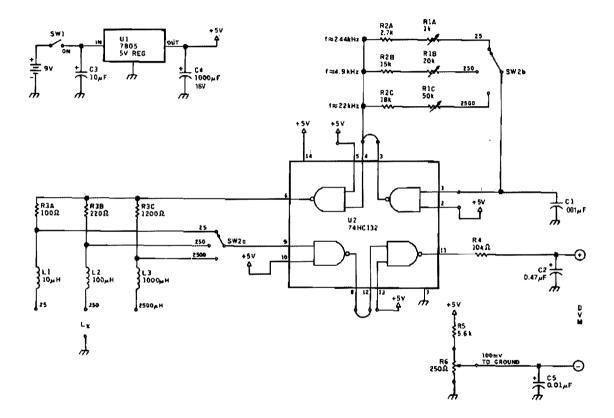


73 AMATEUR RADIO TODAY

Fig. 50-3

The inductance meter comprises an oscillator and pulse shaper. The square wave from the oscillator is differentiated and the differentiator output is shaped and read on a DVM. This will be proportional to inductance. R1A, B, C set calibration and R6 is an offset control.

.

NEGATIVE REFERENCE VOLTAGE CIRCUIT

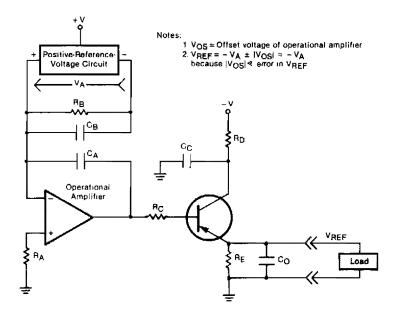

NASA TECH BRIEFS


Fig. 50-4

This figure illustrates a circuit that supplies a precise negative reference voltage. To meet requirements of accuracy and stability, it incorporates a highly precise positive reference voltage by use of a high-gain, stable feedback booster circuit.

The booster circuit includes an operational amplifier and a transistor, which handles the load current. Typically, a positive-reference-voltage circuit can handle only relatively small load currents. This consideration does not apply in the present circuit because the positive-reference-voltage unit is placed in the voltage feedback loop of the booster circuit in parallel with resistor $R_{\rm B}$. Thus, from the perspective of the positive-reference-voltage unit, $R_{\rm B}$ is a constant load. This feature enhances the stability of the circuit by removing the load regulation factor.

Provided that the offset voltage of the operational amplifier is low, the accuracy of the overall circuit depends only on the accuracy of the positive-reference-voltage unit. The overall circuit draws very little power for its own operation. It can handle unexpectedly heavy loads; the feedback configuration and the high gain provided by the combination of the operational amplifier and the transistor give the circuit a very low output impedance. The capacitors reduce the noise voltage and help stabilize the circuit. In the event that the load becomes a short circuit, $R_{\rm D}$ protects the transistor by limiting the load current.

PRECISION CURRENT SOURCE

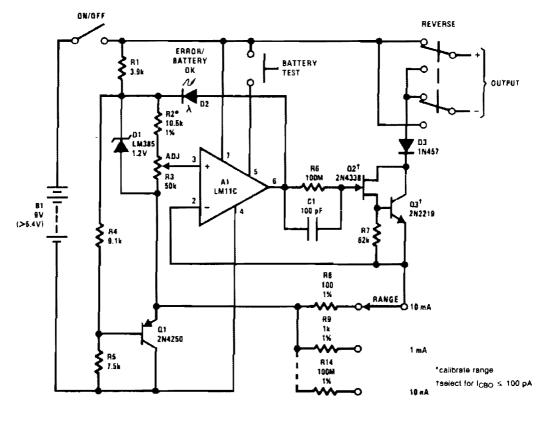

NATIONAL SEMICONDUCTOR


Fia. 50-5

A complete, battery-powered current source suitable for laboratory use is shown. The op amp regulates the voltage across the range resistors at a level determined by the voltage on the arm of the calibrated potentiometer, R3. The voltage on the range resistors is established by the current through Q2 and Q3, which is delivered to the output.

The reference diode, D1, determines basic accuracy. Q1 is included to ensure that the LM11 inputs are kept within the common-mode range with diminishing battery voltage. A light-emitting diode, D2, is used to indicate output saturation. However, this indication cannot be relied upon for output-current settings below about 20 nA, unless the value of R6 is increased. The reason is that very low currents can be supplied to the range resistors through R6 without developing enough voltage drop to turn on the diode.

If the LED illuminates with the output open, there is sufficient battery voltage to operate the circuit. But a battery test switch is also provided. It is connected to the base of the op-amp output stage and forces the output toward V_{\pm} .

1-kW POWER METER

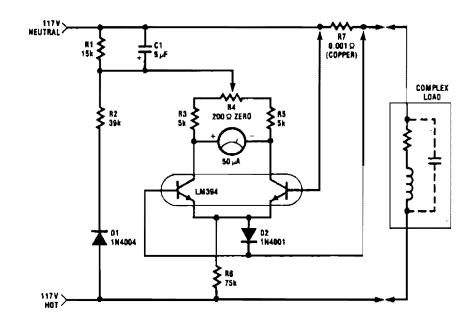


NATIONAL SEMICONDUCTOR

Fig. 50-6

The power meter shown uses only one transistor pair to provide the complete (X) (Y) function. The circuit is intended for 117 Vac \pm 50 Vac operation, but can be easily modified for higher or lower voltages. It measures true (nonreactive) power being delivered to the load and requires no external power supply. Idling power drain is only 0.5 W. The load current-sensing voltage is only 10 mV, keeping load voltage loss to 0.01%. Rejection of reactive load currents is better than 100:1 for linear loads. Nonlinearity is about 1% full scale when using a 50-µA meter movement. The temperature correction for gain is accomplished by using a copper shunt (+0.32%/°C) for load-current sensing. This circuit measures power on negative cycles only, so it cannot be used on rectifying loads.


LOGIC CHIP TESTER

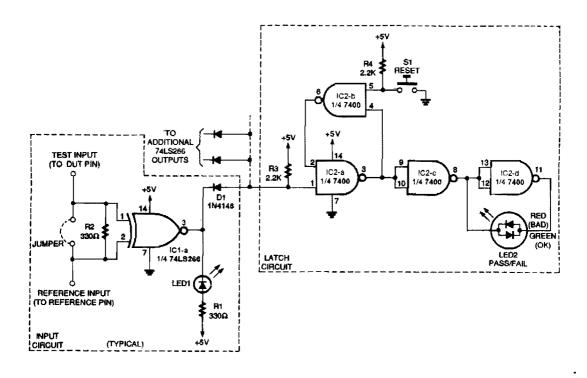


ELECTRONICS NOW

Flg. 50-7

This device compares two logic signals and indicates whether the two logic signals are the same or different. To use the tester, first connect the test input to the suspect pin of the DUT. Next, connect the reference input to the same pin of an identical reference chip that is known to be good. Push the reset button to begin the test; the green section of the bicolor LED will be illuminated. Any signal on the test device that differs from the one on the reference device will then momentarily light the LED lamp that corresponds to that pin, and also latch on the red section of the bi-color LED. That indicates that the device under test is faulty. If the reference and DUT signals are the same, the DUT is OK, and the green LED will remain lit.

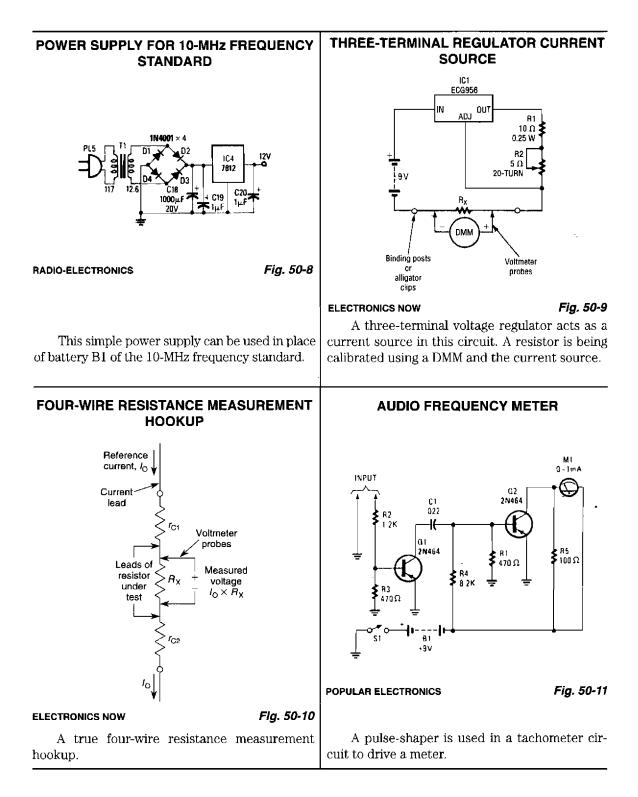


ELF MONITOR

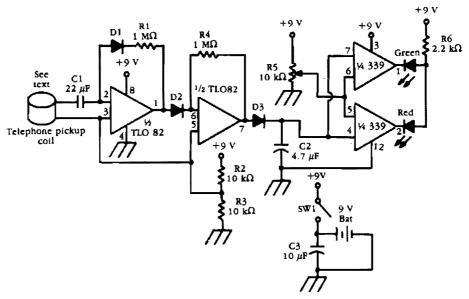

McGRAW-HILL

Fig. 50-12

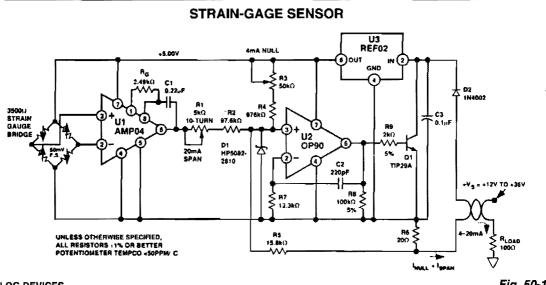A telephone pick-up coil is used as a sensor for low-frequency magnetic fields. The signal is amplified and detected, then used to drive a comparator.




ANALOG DEVICES

Fig. 50-13

In this loop-powered strain-gage sensor application, a 50-mV full-scale (FS) bridge output is amplified and calibrated for a 4-20-mA transmitter output. Power is furnished by the remote loop supply of 12 to 36 V.

MINUTE MARKER

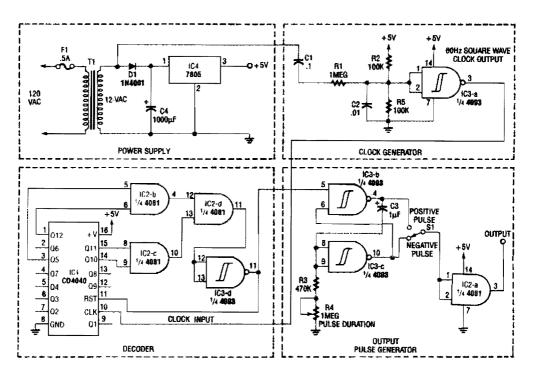

ELECTRONICS NOW


Fig. 50-14

The figure shows the schematic of a minute marker. The output of transformer T1 is 12.6 Vac at 60 Hz, which is rectified by D1 and regulated by IC4, and LM7805 regulator, to provide 5 Vdc for the circuit. The unrectified ac is bandpass-filtered by R1, R2, R5, C1, and C2. Resistors R2 and R5 also form a dc-voltage divider, which biases the input of Schmitt trigger IC3-a to 2.5 V. The Schmitt trigger generates a 60-Hz square wave, which is fed to the input of IC1, a CE4040 12-stage binary counter.

The outputs of the counter are a 4081 quad AND gate (IC2), and the decoded output is fed back to the reset input of the counter, which resets the counter when the desired count is reached.

The pulse from IC2-d is inverted by Schmitt trigger IC3-d, and passed along to the output pulse generator. The output pulse is generated by two Schmitt triggers cross-connected as an RS flip-flop (IC3-b and IC3-c). The output of the flip-flop is fed to 3, R4, and C3, whose values set the output pulse duration. The output pulse duration (*T*) can be approximated by the formula $T = 1.2 \times C_3 \times (R_3 + R_4)$. A positive or negative-going pulse is selected by S1, and buffered by the remaining AND gate (IC2-a).


DIGITAL BAROMETER

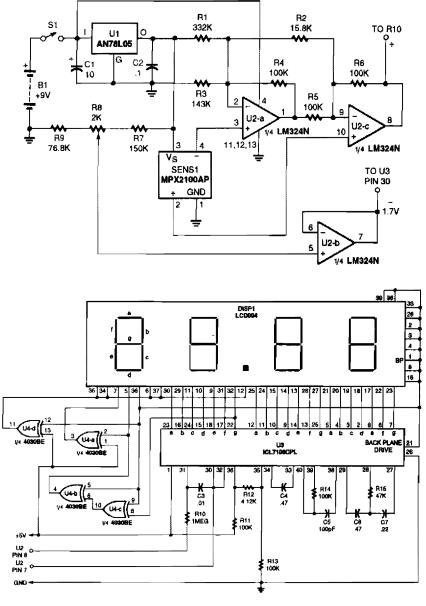

POPULAR ELECTRONICS

Flg. 50-15

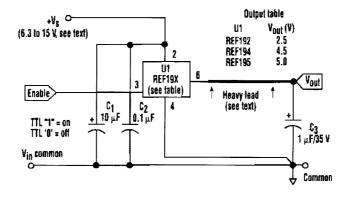A pressure sensor is used in this application. This outputs a voltage to amplifier U2, and a 3½ digit A/D converter module. It is calibrated to read barometric pressure in inches of mercury.




REFERENCE CIRCUIT

ELECTRONICS DESIGN

Fig. 50-16

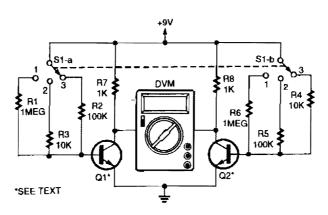In this high-performance reference circuit, U1 is a device from the REF190 series producing device-selectable outputs of 2:5, 4.5, and 5 V with simple, noncritical external circuitry. An Analog Devices REF 19 X (see the table in the figure) is used to derive a reference voltage.




TRANSISTOR MATCHING CIRCUIT

POPULAR ELECTRONICS

In order to match two transistors, select Q1 and Q2 so that they give zero readings (or as close as possible) on a DVM. The DVM acts as a null detector. An analog meter can be substituted. S1 should be set for an appropriate level of base current (approximately 8, 80, or $800 \,\mu$ A).


Fig. 50-17

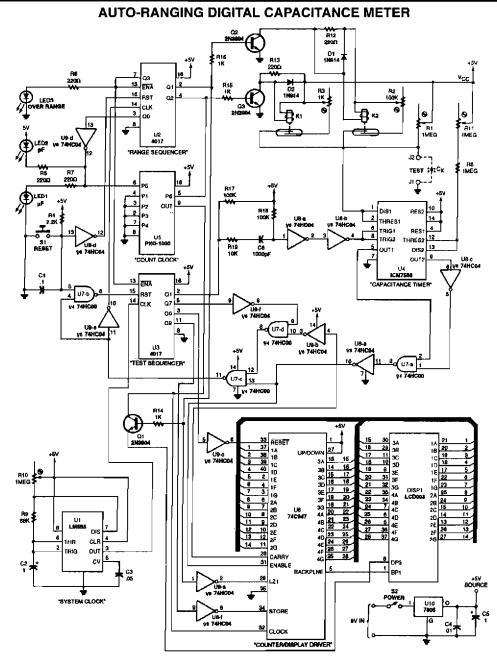

POPULAR ELECTRONICS

Fig. 50-18

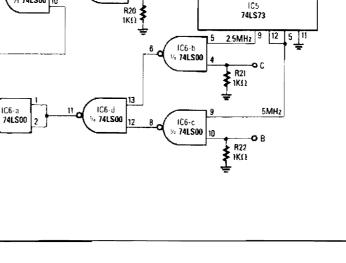This digital capacitance meter reads from 1 pF to $1000 \,\mu$ F. Basically, a timer (U4) uses the unknown capacitance to generate a pulse of duration, depending on the value of unknown capacitance, and the pulse duration is measured. The display is an LCD 0003 driven by a 74C947 counter/display driver.



FREQUENCY DIVIDER FOR 10-MHz FREQUENCY STANDARD

#C7-b

741 \$00

10MHz OUT

3

IC7-a

74LS00 14

2

2 2

Ŷ

IC6-a

2.5/5/10MHz

OUT

CHARGE COLLECTOR (SHORT BARE WIRE OR

SMALL METAL SPHERE)

Q1

MPF102

R2'

33K

RЗ

1MEG

*SEE TEXT

+9V

C1

220pF

R1

150K

M1

200µA

о Х

1C7-c

% 74LS00 10

ELECTROSCOPE

This circuit is useful for detecting electrostatic charges. In operation, C1 reduces ac noise, but lowers the sensitivity a bit. The MPF102 and R1 form a voltage divider. When the FET's gate is earthgrounded, the divider's output will be about 4.5 V giving a half-scale reading on M1, a 200-µA meter. A positively charged object (like cotton-rubbed glass) will give a positive deflection from half-scale, and a negatively charged object (a plastic comb, for example) will give a negative meter deflection.

10MHz

5V

7 10 14

6

The whole circuit (including the 9-V battery supply) should be in a metal enclosure, and a short piece of bare wire makes a fine charge collector.


POPULAR ELECTRONICS

RADIO-ELECTRONICS

Fig. 50-20

Fig. 50-19

OPTICAL ISOLATOR WATTMETER

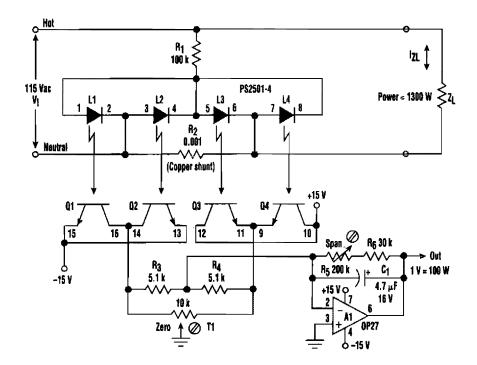


ELECTRONIC DESIGN

Fig. 50-21

The quad-channel optical isolator, consisting of LED L1 through L4 and phototransistors Q1 through Q4, is connected in a double bridge configuration. The arrangement serves to compute the four-quadrant product of ac line voltage and Z1 load current. The result is an accurate representation of the true instantaneous power delivered to the load—even if the line voltage wanders and the load is reactive and nonlinear. This wattmeter function is, of course, optically isolated from the ac line, has full-scale limit of 1300 W, and is output with scale factor of 1 V/100 W.

DIGITAL THREE-PHASE WAVE GENERATOR

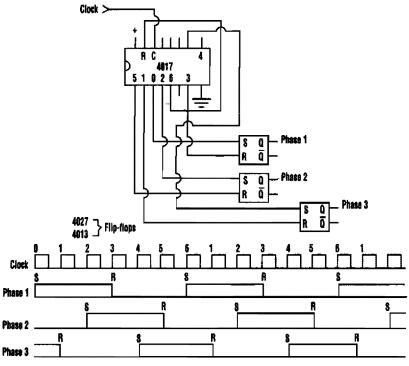


ELECTRONIC DESIGN

Fig. 50-22

With a simple digital circuit, three-phase square waves can be produced from a single-phase square-wave signal source. The timing diagram shows that the second and third phases are 120° and 240° behind the first phase, respectively.

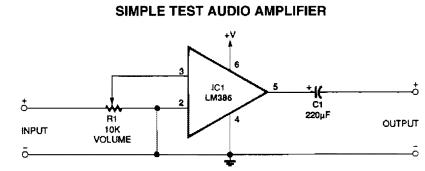The frequency range over which the three-phase outputs will occur is limited only by the capability of the logic used. The output frequency is % of the input frequency.




ELECTRONICS NOW

Fig. 50-23

This circuit has a gain of about 20. A suitable power supply voltage is 5 to 12 V, depending on the desired audio output power level.

GATE DIP OSCILLATOR I

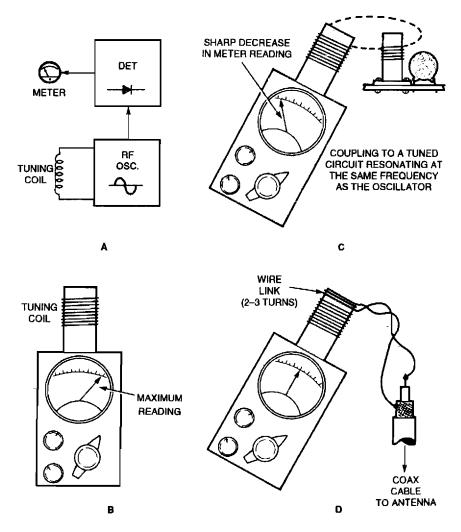


POPULAR ELECTRONICS

Fig. 50-24

The typical dip meter is comprised of a tuning coil, RF oscillator, a detector, and a meter as shown in A. When the meter's tuning coil is coupled to a tuned circuit resonating at the same frequency as the GDM, the reading dips (C). The GDM's tuning coil can be coupled to the coaxial feed line of an antenna through a few (perhaps 2 to 3) turns of wire, and used to determine the antenna's resonant frequency (D).

ACCELEROMETER (G METER) CIRCUIT

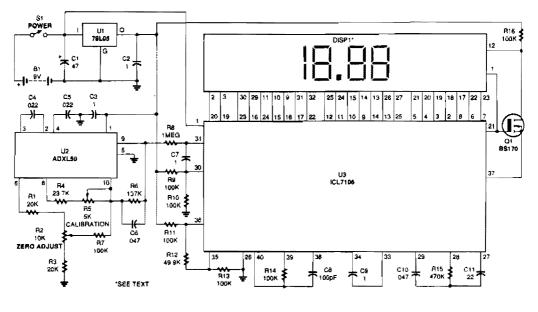

POPULAR ELECTRONICS

Fig. 50-25

As this schematic shows, the ADXL50 accelerometer, U2, interfaces with an A/D converter, U3, to drive a 3%-digit LCD module, DISP1. Because that module displays any number from -19.99 to +19.99, the circuit is designed to measure g's within that range. The heart of the circuit is U2, the ADXL50 accelerometer. The sensitivity of that chip is set to ± 20 g's in order to accommodate the full scale capability of LCD module DISP1 (19.99). Circuit gain is determined by the values of R4, R5, and R6, potentiometer R2, and R3 provides a way to manually set the zero-g voltage-output level at pin 9 of U2 to half the supply voltage—2.5 V. That output voltage will vary linearly by 0.1-V/g of acceleration.

In order to achieve good circuit performance at low g levels, the bandwidth of the amplifier is limited to about 30 Hz by C6. The digital-display section of the circuit is composed of DISP1 and U3. Included in U3 are the A/D converter, clock oscillator, storage resistors and latches, 3½-digit seven-segment decoders, and backplane generator.

The differential analog input of U3 is applied between pins 30 and 31. The positive input, pin 31, is driven by output-pin 9 of U2 through R8, a buffer resistor, and the negative input, pin 30, is biased at a fixed voltage of 2.5 V by a voltage-divider string composed of R9 and R10.


A reference voltage is required by U3. Full-scale display, 19.99, occurs when the differential, analog input voltage applied between pins 31 and 30 is equal to twice the reference voltage. The decimal point of the LCD has to be illuminated to display readings from 0.00 to 19.99. That is done by inverting the backplane square-wave drive signal appearing at pin 21 of U3, through MOSFET Q1, and applying the 180-degree out-of-phase signal to pin 12 of DISP1.

GATE DIP OSCILLATOR II

Band (MHz)	Turns	Wire Size/Type	
3.5 6.5	45	32-enameled	
6.5 11	32	26-enameled	
11 19	14	20-enameled	
15 24	10	20-enameled	
21 36	7	insulated connection wire	
32 56	4	insulated connection wire	
60 110	U-shaped*	16 enameled	

TABLE 1-COIL WINDING DATA

*1.8-inches long

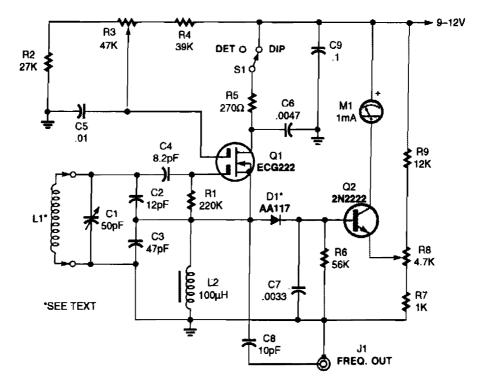


POPULAR ELECTRONICS

Fig. 50-26

Useful for measuring the resonant frequencies of antennas, tuned circuits, and also as a tuned detector, this circuit is a modern variation of the classic vacuum tube grid dip oscillator. It coupled the G.D.O. to a tuned circuit and caused RF energy to be absorbed by the unknown tuned circuit when the G.D.O. frequency was the same as that of the tuned circuit in question. This showed as a "dip" in the meter reading.

TWO REMOTE METERS

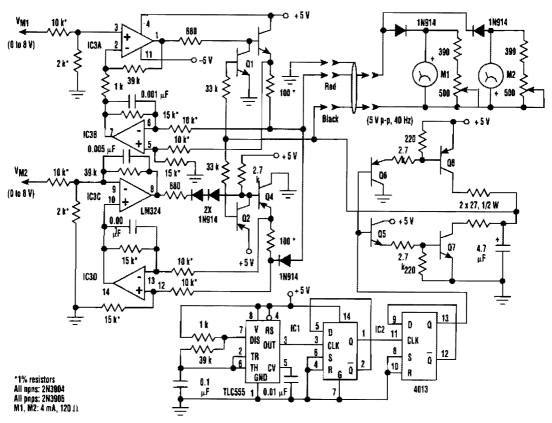

ELECTRONIC DESIGN

Fig. 50-27

Two remote meters can be driven independently using just one wire pair. This "constant current" design eliminates the effects of wire-pair resistance up to 200 Ω . Driving two remote meters independently usually requires two wire pairs (one pair for each meter).


In the circuit, IC1 and IC2 generate a 40-Hz symmetrical square wave (the frequency isn't critical). Q5 through Q8 amplify the square wave to 5 V p-p, which is applied to the "return" (black wire) for the remote meters.

Amplifier IC3A buffers the input signal voltage $V_{\rm min}$ intended for meter M1 (0 to 8 V), and sends it through emitter-follower Q3 to a 100- Ω current-sense resistor. The other end of this resistor is tied to the "supply" (red wire) of the remote meters. IC3B amplifies the voltage across the sense resistor, which corresponds to the current sent to remote meter M1, and closes the feedback loop to IC3A.

This results in a voltage of 0 to 8 V at the M1 input, generating a current of 0 to 10 mA to M1. Transistor Q1 gates this current on and off synchronous to the 40-Hz square wave so that meter M1 actually sees a 50% 0-to-+10-mA peak (0 to 5 mA average) current.

Similarly, IC3C, IC3D, Q2, and Q4 provide a 0- to -10-mA peak current for M2. M1 and M2 are isolated by the two-reverse-connected 1N914 diodes in the remote-meter box. Variable resistors across M1 and M2 permit calibration. The extra 1N914 diode in the M2 drive circuit prevents interference between M1 and M2.

NOVEL RF POWER METER

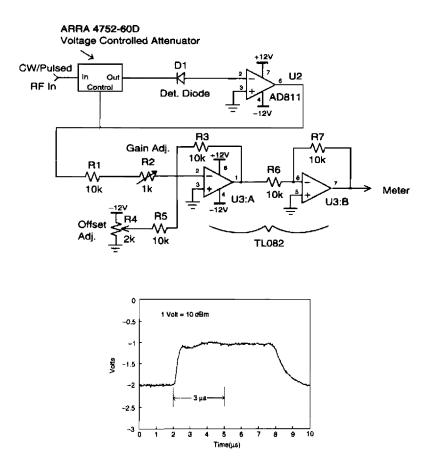

RF DESIGN


Flg. 50-28


The circuit matches the diode with a voltage-variable attenuator that has a logarithmic response. By varying the attenuation until the diode output is zero, the resulting attenuation value then corresponds to the input power level. Because the voltage-variable attenuator's output is logarithmic, diode nonlinearities become negligible.

NANOAMMETER

DC Nano and Micro Ammeter			
I FULL SCALE	R f [Ω]	R' _{f [Ω]}	
100 nA	1.5M	1.5M	
500 nA	300k	300k	
1 μA	300k	0	
5 µA	60k	0	
10 µA	30k	0	
50 µA	6k	0	
100 µA	3k	0	

Resistance Values for

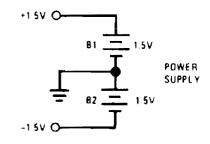

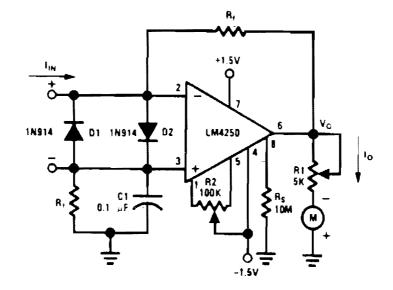


NATIONAL SEMICONDUCTOR

Fig. 50-29

Potentiometer R2 provides an electrical meter zero by forcing input offset voltage V_{os} to zero. Full-scale meter deflection is set by R1. Both R1 and R2 only need to be set once for each op amp and meter combination. For a 50- μ A 2-k Ω meter movement, R1 should be about 4 k Ω to give full-scale meter deflection in response to a 300-mV output voltage. Diodes D1 and D2 provide full input protection for overcurrents up to 75 mA.

With an R_r resistor value of 1.5 M Ω , the circuit becomes a nanoammeter with a full-scale reading capability of 100 nA. Reducing R_r to 3 k Ω in steps, as shown in the figure increases the full-scale deflection to 100 μ A, the maximum for this circuit configuration. The voltage drop across-the two input terminals is equal to the output voltage (V_o) divided by the open loop gain. Assume that an open loop gain of 10,000 gives an input voltage drop of 30 μ V or less.

1.5-V LOGARITHMIC LIGHT LEVEL METER

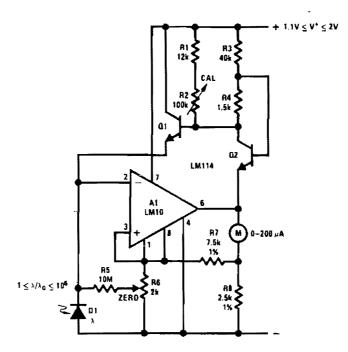

NATIONAL SEMICONDUCTOR

Fig. 50-30


A portable light-level meter with a five-decade dynamic range is shown. The circuit is calibrated at mid-range with the appropriate illumination by adjusting R2 such that the amplifier output equals the reference and the meter is at center scale. The emitter-base voltage of Q22 will vary with supply voltage; so R4 is included to minimize the effect on circuit balance. If photocurrents less than 50 nA are to be measured, it is necessary to compensate the bias current of the op amp.

The logging slope is not temperature compensated. With a five-decade response, the error at the scale extremes will be about 40% (a half stop in photography) for a $\pm 18^{\circ}$ C temperature change.

If temperature compensation is desired, it is best to use a center-zero meter to introduce the offset, rather than the reference compensation. It can be obtained by making the resistor in series with the meter a copper wire-wound unit.

If this design is to be used for photography, it is important to remember that silicon photodiodes are sensitive to near-infrared light, whereas ordinary film is not. Therefore, an infrared-stop filter is called for. A blue-enhanced photodiode or an appropriate correction filter would also produce best results.

ac POWER MONITOR

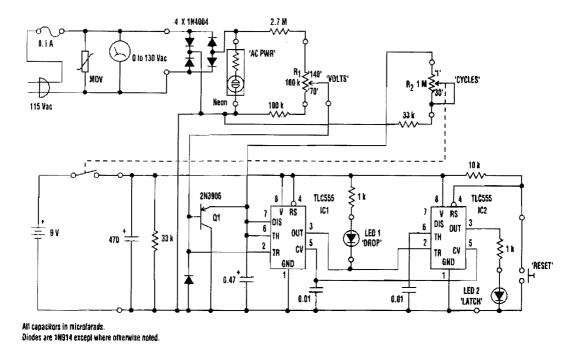

ELECTRONIC DESIGN

Fig. 50-31


The 0- to 130-V voltmeter and neon "AC PWR" lamp provide an average indication of the ac power. The fuse and metal oxide varistor (MOV) protect the monitor against overvoltage spikes.

Four 1N4004 diodes rectify the ac voltage, generating negative-going pulses twice per cycle (every 8.33 ms for 60-Hz power). Variable-resistor F1 supplies a reduced amplitude sample of these pulses to a missing pulse detector consisting of Q1, IC1, and associated circuitry. As long as the pulse amplitude exceeds the threshold value set by R1, IC1 continually triggers, keeping its output high. When the pulse amplitude drops below the threshold value, IC1 times out with a time constant set by variable resistor R2 and the 0.47- μ F capacitor. R2 is calibrated to read the number of cycles required for a dropout indication. It can be set between 1 cycle (about 17 ms) and 30 cycles (0.5 second).

When IC1 times out, its output goes low. This turns on LED1. The low output also triggers IC2, which is configured as a set-reset flip-flop. This turns on LED2. When the voltage returns to normal, IC1 again starts triggering and its output returns high, turning off LED1. LED2, however, remains on until the manual reset button is pressed.

The circuit is powered by a 9-V battery and is assembled in a plastic or grounded metal case. Notice that there's no isolation between the ac power line and the monitor circuitry. Be careful to avoid electrical shock when testing the circuitry.

100-W VARIABLE RESISTOR SIMULATOR

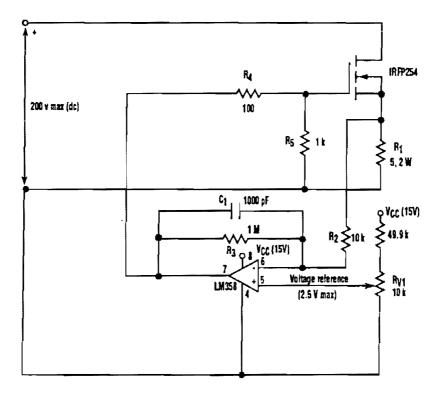

ELECTRONIC DESIGN

Flg. 50-32

Variable resistive loads with precise load steps often are required in automatic testers used to test and calibrate power supplies. The action of a high-power (100 W) variable resistor can be simulated with the circuit shown.

The voltage drop across R1, which is proportional to the FET current, is compared against a variable input voltage reference using a high-gain op amp. Error voltage developed by the amplifier drives the gate, controlling the transconductance of the FET.

Power dissipation is limited by the safe-operating-area curve of the selected FET. The FET should be mounted onto a properly sized heatsink or a heatsink-fan combination to maintain its case temperature within safe limits. The circuit is designed to dissipate a maximum power of 100 W if the FET-case temperature is maintained below 50°C. The potentiometer (RV1) can be replaced by a digital-to-analog converter so that it can adapt to the computer control for use in automatic testers.

IMD TEST CIRCUIT FOR PIN DIODES


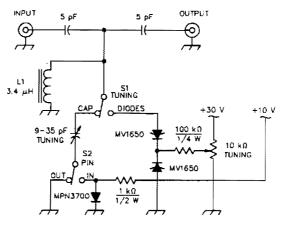


Fig. 50-33

A loosely coupled tuned circuit for testing IMD production by PIN and tuning diodes in a narrowband preselector, S1, TUNING, selects whether C1 or a pair of back-to-back MV1650 tuning diodes resonate L1. S2, PIN, adds or removes an MPN3700 PIN diode in series with C1. L1 consists of 33 turns of #28 enameled wire on a t-37-6 toroidal powdered-iron core. The MV1650, a "20-V" tuning diode, exhibits a nominal capacitance of 100 pF at a tuning voltage of 4 V.

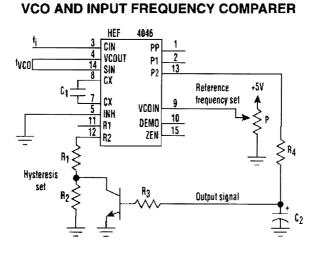


ELECTRONIC DESIGN

QST

Comparison of an input signal's frequency (f_i) with that of voltage-controlled oscillator (f_{VCO}) can be accomplished with just one CMOS phase-locked loop IC and a transistor (see figure). The phase and the frequency can be compared with a phase comparator, which, along with the VCO, is part of the HEF4046 PLL IC. The transistor helps introduce hysteresis, enabling the circuit to be used as a switch driver.

Fig. 50-34


ECG AMPLIFIER WITH RIGHT LEG DRIVE

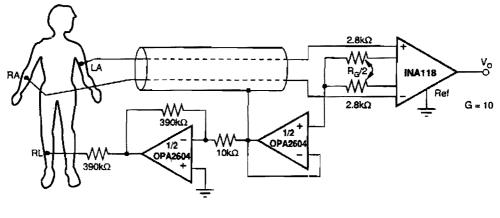

BURR-BROWN

Flg. 50-35

POWER TRANSFORMER TESTER

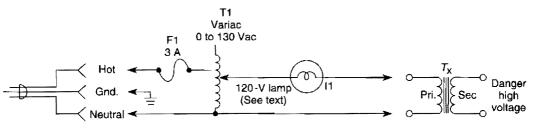


Warning: observe existing shock hazard

WILLIAM SHEETS

Fig. 50-36

Very often a power transformer is suspect and connecting a shorted transformer to an ac source can be hazardous. This test method will detect a defective or shorted transformer. The primary of the power transformer is energized through a Variac (0 to 130 Vac) and a lamp equal in wattage to about half that of the transformer under test. Connect the transformer, set Variac at zero, then energize circuit. Apply voltage to suspected transformer (Tx) as shown. The lamp should not light. If it does, Tx is shorted. Next, short the secondary of suspected Tx. This time, the lamp should light. For multiple winding transformers, repeat for each secondary winding. Beware of the shock hazard as the open windings of Tx can develop full-rated voltage.

4- TO 20-mA PROCESS CONTROLLER

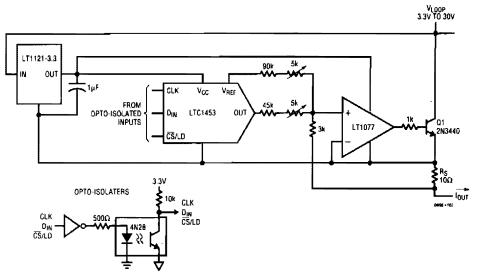


LINEAR TECHNOLOGY

Fig. 50-37

The figure shows how to use an LTC1453 to make an optoisolated digitally controlled 4- to 20-mA process controller. The controller circuitry, including the optoisolator, is powered by the loop voltage that can have a wide range of 3.3 V to 30 V. The 1.22-V reference output of the LTC1453 is used for the 4-mA offset current and $V_{\rm OUT}$ is used for the digitally controlled 0- to 16-mA current. $R_{\rm S}$ is a sense resistor and the LT1077 op amp modulates the transistor Q1 to provide the 4- to 20-mA current through this resistor. The control circuitry consumes well under the 4-mA budget at zero scale.

SIMPLE HIGH-CURRENT MEASURER

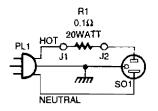


POPULAR ELECTRONICS

Testing heavy-load devices with a ten-amp maximum meter can be accomplished with this straightforward meter add-on. If done right, it could be made from a high-current extension cord. J1 and J2 are well-insulated jacks to accept meter probe tips.

Fig. 50-38

ANALOG CIRCUITRY CALIBRATOR

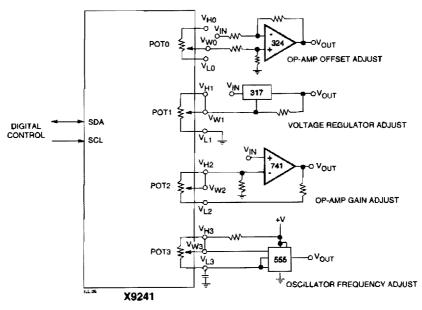


XICOR

Fig. 50-39

An XICOR X9241 Quad POT IC can be used to digitally adjust four analog circuits, as shown in the example schematic.

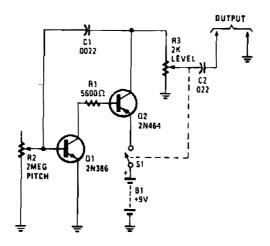SIMPLE SIGNAL GENERATOR FOR SIGNAL TRACING




POPULAR ELECTRONICS

Fig. 50-40

A simple R-C oscillator generates a harmonic-rich waveform for signal injection.

SIMPLE HARMONIC DISTORTION ANALYZER

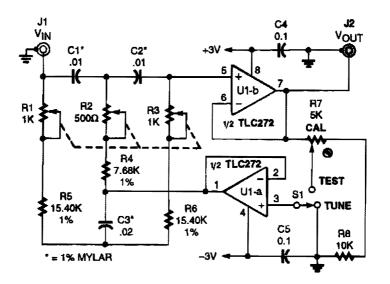

POPULAR ELECTRONICS

Flg. 50-41

This simple circuit lets you accurately measure the total harmonic distortion (THD) using your true-RMS voltmeter.


This THD circuit is somewhat different from the usual types: it can operate at the standard frequency of 1000 Hz, but it also is tunable from 970 Hz to 1030 Hz, and has an adjustable *Q* factor of 0.3 to over 50. Op-amp U1, a TLC272 CMOS unit, contains the two voltage-followers required to buffer the input to the bootstrapped twin-T notch filter. Tuning is accomplished by R1, R2, and R3, which are standard linear-taper slide pots "ganged" together by mounting them side-by-side and gluing their sliders together. The only other important construction hint is to use twisted pair at the circuit's input and output.

To calibrate the circuit, input a 1000-V RMS signal at 2000 Hz, set S1 to TEST, and adjust R7 for a reading of 0.99-V RMS on a true-RMS voltmeter at the output.

To use the circuit, set S1 to TUNE, input a 1000-Hz sine-wave signal to the amplifier under test, and set the amplifier's output to the THD adapter and tune R1/R2/R3 for the lowest output signal. Then, set S1 to TEST and read the RMS voltage. To calculate the percent THD use:

$$THD = \left(\frac{V_{\text{out}}}{V_{\text{m}}}\right) \times 100$$

SOUND SUBCARRIER GENERATOR

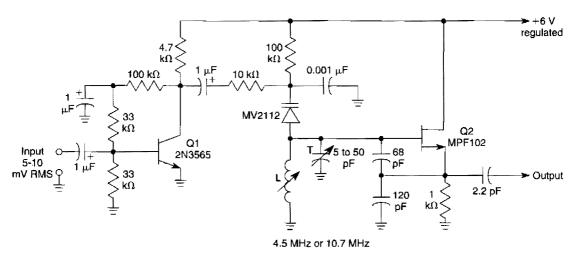


WILLIAM SHEETS

Fig. 50-42

Fig. 50-43

This circuit will generate an FM sound subcarrier at 4.5 or 10.7 MHz for FM and TV IF testing and alignment. Q1 is an audio amplifier and Q2 is a VCO modulated by an MV2112 varactor. Deviation up to 1% of frequency can be obtained. L is chosen to resonate with the circuit capacitance to either 4.5 or 10.7 MHz. The values will be around 2 to 10 μ H, depending on the frequency.

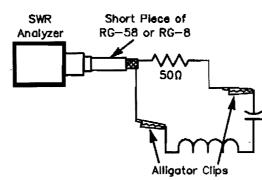INDUCTANCE AND CAPACITANCE DETERMINER WITH SWR BRIDGE




QST

At resonance, the SWR will be 1:1 with a 50- Ω resistance, as reactance is zero. If either L or C is known:

$$|X_{L}| = |X1| = \frac{1}{2\pi fC} = 2\pi fL$$

$$L_{\text{unknown}} = \frac{1}{(2\pi f)^{2}C} \qquad C_{\text{unknown}} = \frac{1}{(2\pi f)^{2}L}$$


MCTORCYCLE TUNE-UP AID

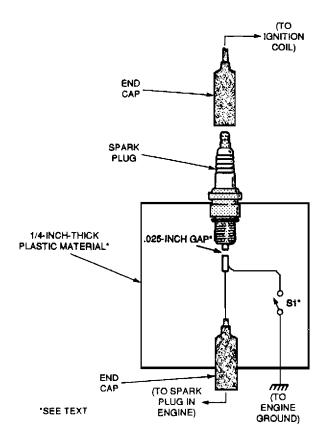

POPULAR ELECTRONICS

Fig. 50-44

Performing a tune-up on a newer bike is made a lot easier with this helpful circuit. Because of the high voltages present, make sure that S1 has an insulated handle and that the fixture is grounded. With the ignition turned off, remove one of the spark plug wires and connect it to the spark plug on the fixture. Slip the fixture's end cap over the spark plug on the cycle and you're ready to go. Open S1 and start the engine. Then, close S1; the cylinder with the fixture should not fire and a spark should be seen at the fixed gap. Be sure that the fixture is connected to the engine ground before closing S1.

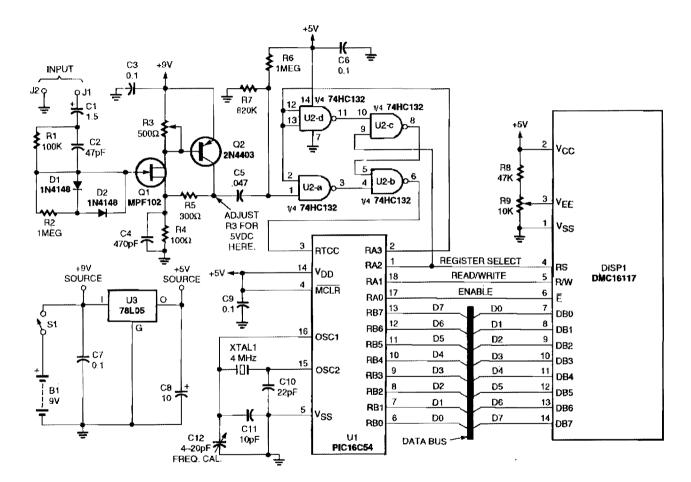


POPULAR ELECTRONICS

Fig. 50-45

This inexpensive frequency counter uses a microcontroller as the counter. The microcontroller feeds an LCD display module that accepts standard ASCII code. The frequency is displayed as Hz, kHz, or MHz and the counter is autoranging.

10-MHz FREQUENCY STANDARD

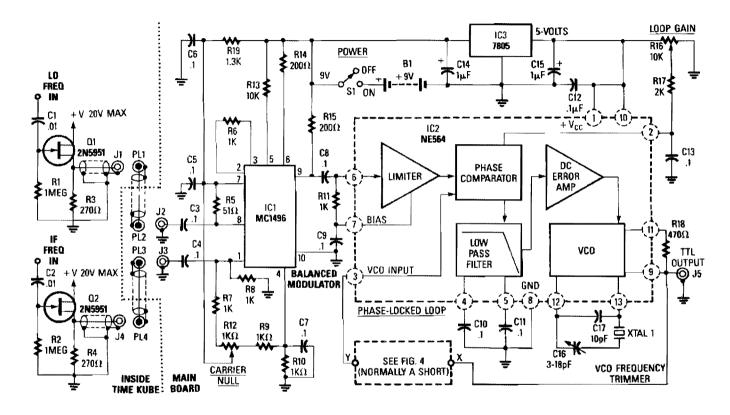


RADIO-ELECTRONICS

Fig. 50-46

A Radio Shack 10-MHz receiver is used as a basis for this circuit. The L.O. and IF frequencies are added. When the receiver is tuned to 10 MHz (WWV), the sum of the L.O. and IF are used to phase lock a VCO to the 10-MHz signal. By using a divider in the loop, 2.5 or 5 MHz can be used as well.

.

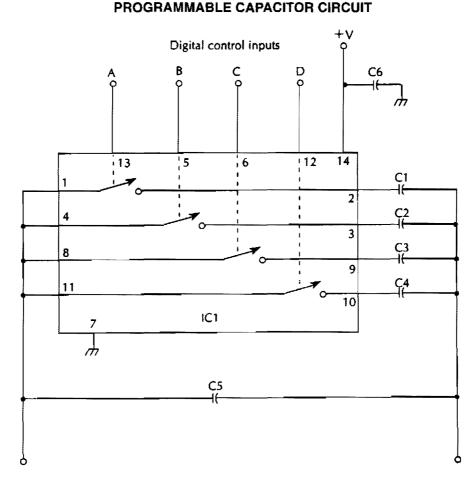


McGRAW-HILL

Fig. 50-47

- IC1 CD4066 quad bilateral switch
- C1 $10-\mu$ F, 25-V capacitor
- C2 22-µF, 25-V capacitor
- $C3 = 47-\mu F$, 25-V capacitor
- C4 $100-\mu F$, 25-V capacitor
- C5 $1-\mu F$, 25-V capacitor
- C6 $0.1-\mu F$, 25-V capacitor

The programmable capacitor can be very useful in circuits where you need to switch capacitance values. Remember that the "ON" resistance of IC1 appears in series with the capacitors and must be taken into account in some applications as it is not negligible.

PROGRAMMABLE RESISTOR CIRCUIT

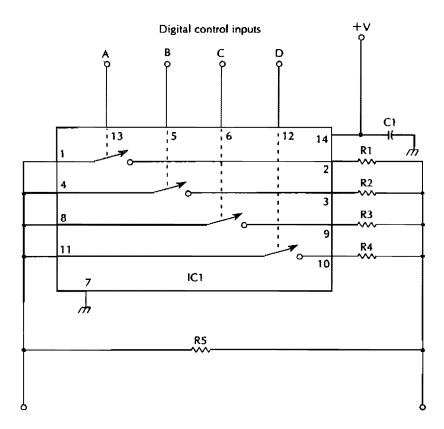

McGRAW-HILL

Flg. 50-48

- IC1 CD4066 quad bilateral switch
- C1 $0.1-\mu F$ capacitor
- R1 10-k Ω , ¼-W 5% resistor
- R2 4.7-kΩ, ¼-W 5% resistor
- R3 $2.2-k\Omega$, ¼-W 5% resistor
- R4 1-k Ω , ¼-W 5% resistor
- R5 $1-M\Omega$, %-W 5% resistor


A programmable resistor can replace a potentiometer or fixed resistor. Remember that the "ON" resistance of IC1 might have to be taken into account in some applications.

51

Metronome Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Audible Metronome Visual Metronome

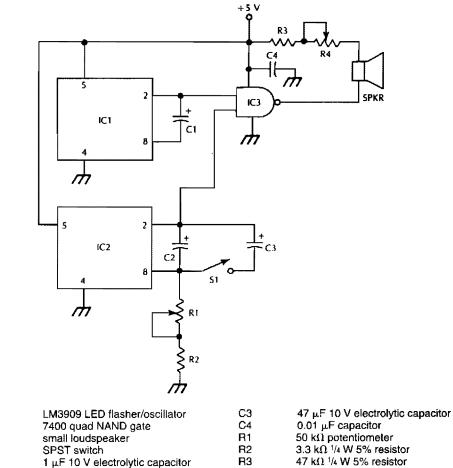

47 k	Ω 1/4	W.	5%	resistor
------	-------	----	----	----------

500 Ω potentiometer

McGRAW-HILL

IC1, IC2

IC3

S1

C1

C2

SPKR


Fig. 51-1

IC1 generates an audible frequency while a variable very low frequency is generated by IC2. R1 sets the metronome rate. The two signals are combined in IC3.

R4

100 µF 10 V electrolytic capacitor

VISUAL METRONOME

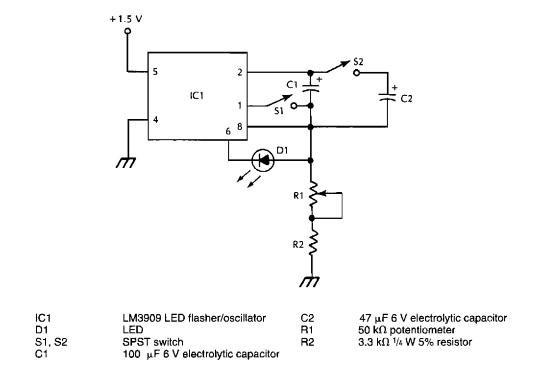

McGRAW-HILL

Fig. 51-2

52


Miscellaneous Treasures

T he sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

MOSFET Drive Current Booster Simple Event Counter Frequency Doubler Atmosphere Noise Monitor Tachometer Derived from Brushless Shaft Angle Resolver Vocal Stripper Vocal Stripper Power Supply Single-Chip Message System **Television Vertical Deflection Circuit** Tone Burst Generator Audio Volume Limiter Simple Intercom for Noisy Environments Ditherizer Triac Lamp Dimmer Circuit 500-ksps 8-Channel Data Acquisition Circuit Hydrophone Your Name in Lights

Underwater Microphone Pulse Echo Driver Simple Pseudorandom Voltage Source **TV Horizontal Deflection Circuit Muting Circuit** Simple Remote Gain Control Loop Oscillator Eliminator 1-A Voltage Follower **Electronic Fish Lure** Heartbeat Transducer **Contact Debouncer** Positive Feedback Cable Terminator ×10 Frequency Multiplier Jacob's Ladder Master-Slave Device Error Checker Ground Loop Preventer Dual Tone Generator for Audio Servicing **Diodeless Peak-Hold Circuit**

MOSFET DRIVE CURRENT BOOSTER

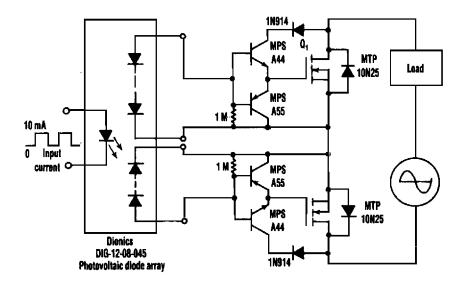

ELECTRONIC DESIGN


Fig. 52-1

A clean and inexpensive way to eliminate the floating-gate supply is to use the voltage available at the MOSFET's drain to drive its gate. Tying the collector of Q1 (a high-voltage, small-signal, 400-V NPN) to the MOSFET's drain supplies sufficient gate-drive voltage when it's needed most—when the MOSFET's drain-to-source voltage is high. Two such circuits used back-to-back form an ac relay.

Using the emitter follower attached to the drain increases gate-drive current and decreases the MOSFET's turn-on time by a factor equal to the high-voltage NPN's beta. The resulting drain-to-source voltage fall times depend on the MOSFET's size and its required gate charge. The circuit that's used gives a fall time of 200 μ s for an MTP10N2f5 10-A, 250-V MOSFET. With such fall times cutting switching losses, pulse-width modulation at frequencies under 100.Hz is possible.

During tune-on, $V_{\rm DS}$ falls rapidly until it reaches the sum of the 1N914 diode's 0.7-V drop, the collector-emitter saturation voltage of Q1, and the gate-to-source voltage required to support the load current. At that point, the diode array completes the MOSFET's turn-on, unaided by the buffer. This slows the fall of $V_{\rm DS}$ considerably when it reaches about 5 to 7 V. In high-voltage, low-frequency systems, tailing of $V_{\rm DS}$ is tolerable because the tail's voltage magnitude constitutes a small fraction of the switching voltage. The IN914 makes it possible for $V_{\rm GS}$ to exceed $V_{\rm DS}$ as the MOSFET completes turn-on.


SIMPLE EVENT COUNTER

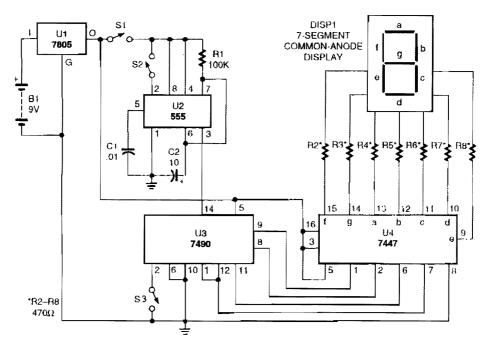

POPULAR ELECTRONICS

Fig. 52-2

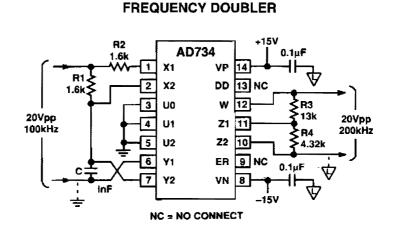S1 is a power switch. U2 drives counter U3 by producing a pulse when S2 is depressed. U4 and DISP1 read the count of counter IC U3. S3 is a reset to zero switch. The counter is a basic one-digit circuit useful as a holding block or by itself.




ANALOG DEVICES



An Analog Devices AD734 four-quadrant analog multiplier is used as a frequency doubler.

ATMOSPHERE NOISE MONITOR

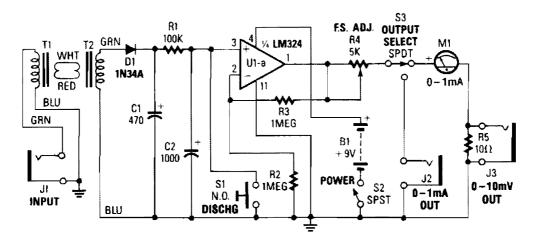

POPULAR ELECTRONICS

Fig. 52-4


Tune an unmodified transistor radio to an unused frequency near 540 kHz that's free of broadcast-station interference; the receiver is used to pick up sferics. The received signal is fed from the receiver's earphone jack through a patch cord to the input jack (J1) of the circuit. The back-to-back audio transformers, T1 and T2, provide a suitable impedance match and signal level when the unit is used with various receivers.

Diode D1 rectifies the audio input from the receiver to pulsating dc, which is filtered by C1, R1, and C2 to provide a time constant of several minutes. That dampens out fluctuations in most cases, unless lightning flashes are very infrequent.

The voltage appearing at the output of the filter is a function of signal strength transferred by C1. Switch S1 is included to provide a convenient way to discharge the capacitors, if adjustments are required during a monitoring session.

Integrated circuit U1 (one section of an LM324 quad pro op amp) is used as a high input-resistance voltmeter. Resistors R2 and R3 determine amplifier gain, and potentiometer R4 is used to adjust full-scale meter deflection for a suitable voltage level at the input. A value of 1.5 V has been satisfactory for use with several receivers tried, but they can be changed.

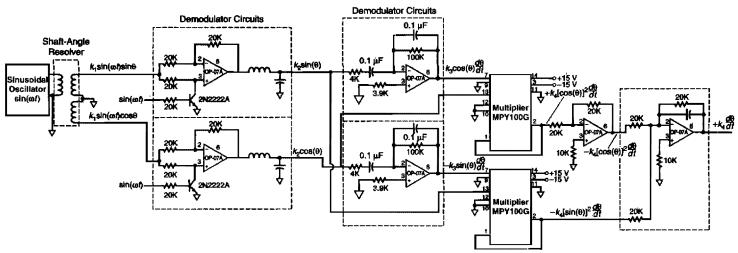If the monitor is to be used only as a meter, the milliammeter can be connected directly between R4 and chassis ground, omitting R5, S3, J2, and J3. The latter components provide suitable output for use with a chart recorder having a full-scale range of either 10 mV or 1 mA. The circuit, when powered from a 9-V battery, draws about 1 mA.



TACHOMETER DERIVED FROM BRUSHLESS SHAFT ANGLE RESOLVER

NASA TECH BRIEFS

Fig. 52-5


The tachometer circuit operates in conjunction with a brushless shaft-angle resolver. By performing a sequence of straightforward mathematical operations on the resolver signals and utilizing a simple trigonometric identity, it generates a voltage proportional to the rate of rotation of the shaft.

The figure illustrates an analog tachometer circuit that processes the input and output signals of a two-phase, brushless, transformer-type shaft-angle resolver into a signal with instantaneous amplitude proportional to the instantaneous rate of rotation of the shaft. The processing in this circuit effects a straightforward combination of mathematical operations leading to a final operation based on the well-known trigonometric identity $[\sin(x)]^2 + [\cos(x)]^2 = 1$ for any value of x.

The resolver is excited with a periodic waveform; a sinusoid is indicated in the figure, but a square, triangular, or other periodic waveform could be used instead. Thus, the two outputs of the resolver are $k_1 \sin(\omega t)\sin(\theta)$ and $k_1 \sin(\omega t)\cos(\theta)$, where k_1 is a constant proportional to the amplitude of excitation, ωt is $2\pi x$ the frequency of excitation, t is time, and θ is the instantaneous shaft angle.

The two outputs of the resolver are then processed, along with a replica of the sinusoidal excitation, by demodulators. These signals are then differentiated with respect to time in two differentiator circuits. Notice that $d\theta/dt$ is the rate of change of the shaft angle and is the quantity that one seeks to measure.

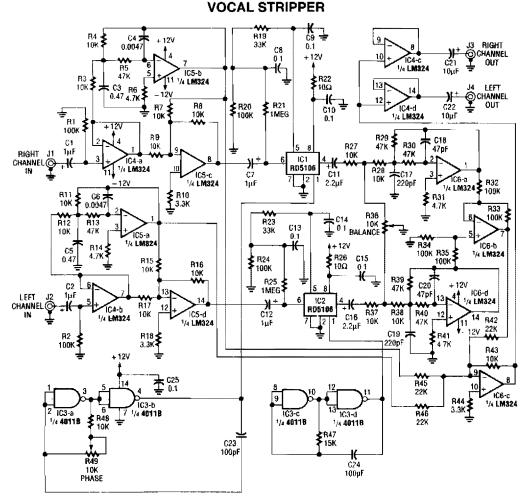Next, a multiplier circuit forms a product of the demodulator and differentiator outputs proportional to $\sin(\theta)$, and the product of the demodulator and differentiator outputs proportional to $\cos(\theta)$. The output of the cosine multiplier is fed to a unit-gain inverting amplifier.




RADIO-ELECTRONICS

Fig. 52-6


The schematic of the lead vocal filter is shown in the figure. The left and right channel signals are coupled through C1 and C2 to buffer amps IC4-a and IC4-b. From the buffer amps, the left and right channel signals pass through active crossovers IC5-a and IC5-b, sending all low frequencies to a final mixer IC6-c, and all middle and high frequencies to analog delay lines IC1 and IC2, RD5106 256-sample bucket-brigades. Integrated circuit IC2 delays the left-channel signal by 2.4 ms, set by the fixed-frequency clock generated by ½IC3, R47, and C24. The right channel signal is delayed by IC1 with a variable-frequency clock generated by ½IC3, R48, R49, and C23. Potentiometer R49 is used for phase adjustment.

The output of each delay line from IC1 and IC2 passes through low-pass filters IC6-a and -d, and their associated parts, to filter out high-frequency sample-steps produced by IC1 and IC2. Balance control R36 is adjusted for equal amplitude of the left and right channels. IC6-b is a difference amplifier that cancels all lead vocals that are common to both channels. The resulting signal from IC6-b is remixed with low frequencies by IC6-c and is then sent to the output via buffers IC4-c and IC4-d.

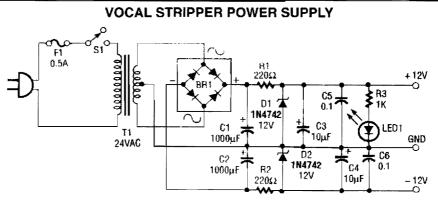

RADIO-ELECTRONICS

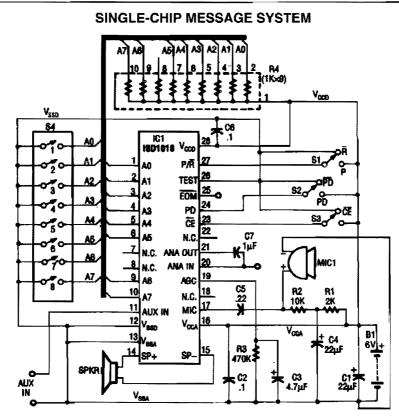The power supply schematic for the lead vocal filter circuit.




ELECTRONICS EXPERIMENTERS HANDBOOK

Fig. 52-8

Fig. 52-7

The ISD1016 is a complete analog audio record/playback system on a chip. The analog signal is sampled and the samples stored in an EEPROM as analog levels. Upon playback, the analog data is read out and amplified. Up to 16 seconds of data (audio) can be stored.

TELEVISION VERTICAL DEFLECTION CIRCUIT

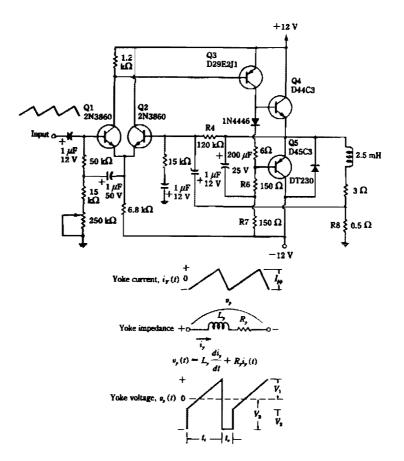


McGRAW-HILL

Fig. 52-9

Two transistors are used to drive the yoke $(2.5 \text{ mH} + 0.3 \Omega)$ in this deflection circuit. R8 samples the yoke current and provides feedback to Q2, resulting in a very linear current ramp through the yoke.

TONE BURST GENERATOR

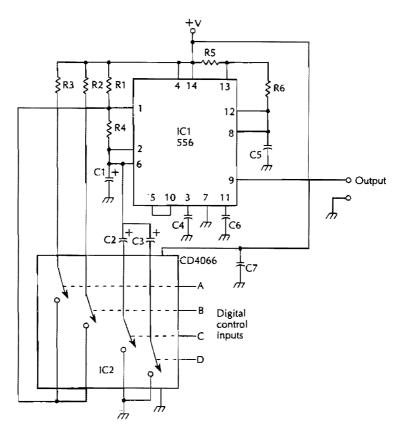


McGRAW-HILL

Fig. 52-10

The burst length is digitally controlled by inputs A, B, C, D. This input selects the necessary values of R and C. The circuit shown in the figure generates a burst of tone followed by a silent period, then another tone burst is sounded and so forth. The timing of the tone bursts is digitally controlled via the CD4066 (IC2). A parts list for this circuit is given in the table.

IC1	556 dual timer (or two 555 timers)	C5	0.047-µF capacitor
IC2	CD4066 quad bilateral switch	R1	100-kΩ, ¼-W 5% resistor
C1	1-μF, 25-V electrolytic capacitor	R2, R4	220-k Ω , ¼-W 5% resistor
C2	4.7-μF, 25-V electrolytic capacitor	R3	680-k Ω , ¼-W 5% resistor
C3	10-µF, 25-V electrolytic capacitor	R5	12-k Ω , ¼-W 5% resistor
C4, C6	0.01 - μ F capacitor	R6	4.7-kΩ, ¼-W 5% resistor

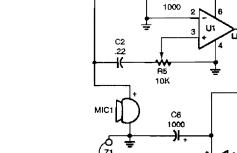






This intercom was originally designed for motorcycle to passenger communications. A simple "passenger-to-pilot" intercom circuit is shown. Two LM386 ICs are connected in a low-gain amplifier circuit with the headphone output of one paired to the microphone input of the other. The microphones are electret elements and the earphones can be of the in-ear type or of the small stereo/mono type that will fit inside a helmet. Both amplifiers in the circuit operate at a minimum gain of 20 dB.

Flg. 52-12

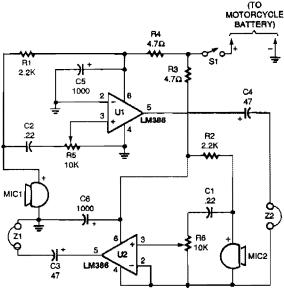
SIMPLE INTERCOM FOR NOISY ENVIRONMENTS πo



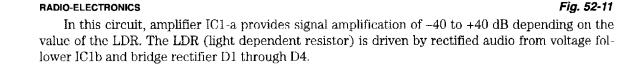

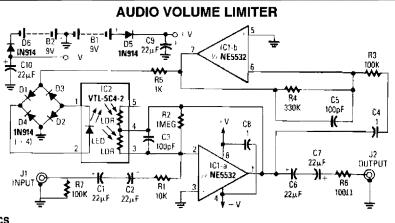


DITHERIZER

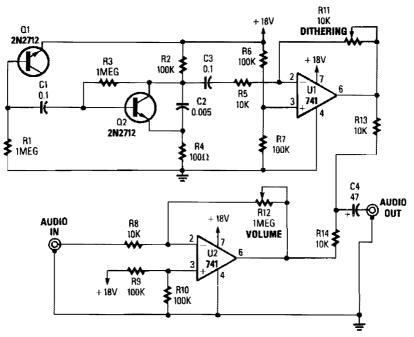

POPULAR ELECTRONICS

Fig. 52-13

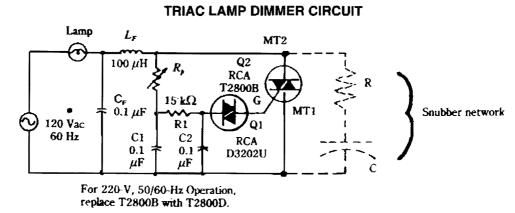In digital audio, a noise signal of amplitude less than one significant bit is often added to the audio to reduce the quantizing effect and improve the audio quality by trading digital "noise" for analog noise, which does not have the harsh sound. This circuit consists of a noise generator to add a low level of noise to an analog signal to be digitized, or an analog signal from a digital source.




McGRAW-HILL

Fig. 52-14

The brightness of a lamp or lamps can be varied with this circuit. The snubber circuit values are typically 0.1 μ F and 100- Ω . R_8 is typically 25 to 100 k Ω .

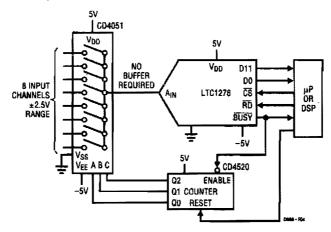
500-ksps 8-CHANNEL DATA ACQUISITION CIRCUIT



LINEAR TECHNOLOGY

Fig. 52-15

The high input impedance of the LTC1278 allows multiplexing without a buffer amplifier. Both single channel and multiplexed high-speed data acquisition systems benefit from the LTC1278/LTC1279's dynamic conversion performance. The 1.6- μ s and 1.4- μ s conversion and 200-ns and 180-ns S/H acquisition times enable the LTC1278/LTC1279 to convert a 500 ksps and 600 ksps, respectively. The figure shows a 500-ksps 8-channel data acquisition system. The LTC1278's high input impedance eliminates the need for a buffer amplifier between the multiplexer's output and the Adc's input.

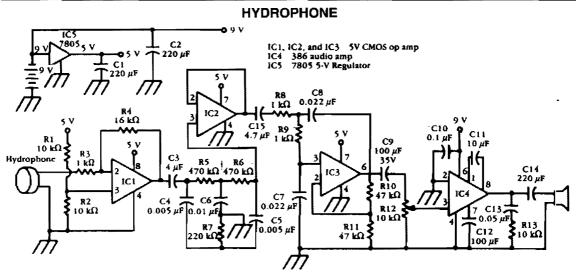


McGRAW-HILL

Fig. 52-16

A commercially available hydrophone transducer is used in this system. The transducer is connected via a cable to the amplifier, which remains out of the water. The hydrophone should be suitably mounted for intended application.


YOUR NAME IN LIGHTS

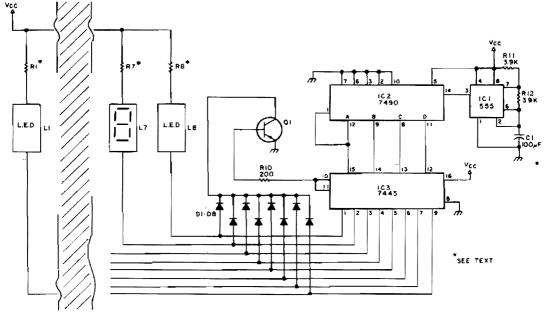

73 AMATEUR RADIO TODAY

Fig. 52-17

This circuit will enable you to put a name or callsign in lights using seven-segment LEDs. The display will spell the desired name out sequentially. Select the correct type of LED. Solder the correct leads together to form the letters you want. After mounting the appropriate current-limiting resistor, the 7445 can only sink 80 mA, so a PNP transistor is needed to handle the current required to light the letters. The heart of the circuit is a 555 oscillator into a 7490 decade counter, which is decoded by a 7445 open-collector driver chip.

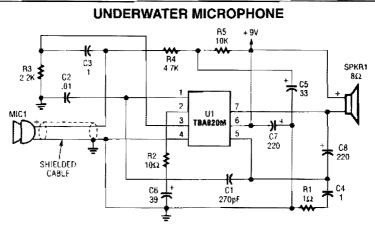


ELECTRONIC HOBBYISTS HANDBOOK

Fig. 52-18

This circuit uses a TBA820 audio IC to amplify underwater sounds. The microphone must be waterproofed. This project was originally used in a home aquarium to monitor fish sounds.

PULSE ECHO DRIVER

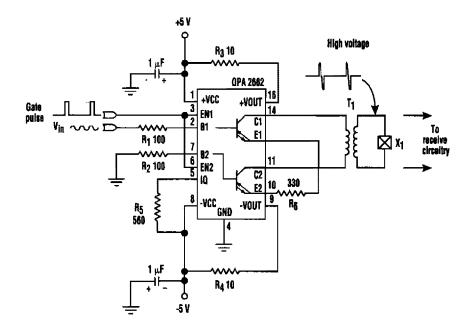

ELECTRONIC DESIGN


Fig. 52-19

This pulse-echo driver uses the OPA2662 dual operational transconductance amplifier (OTA) from Burr-Brown (the receive circuitry isn't shown). The OTA is preferable over an op amp for driving low impedances because it provides a current output rather than a voltage output.

Ultrasonic pulse-echo applications often incorporate a transformer-coupled crystal to obtain a high-voltage pulse because the echo can be orders of magnitude smaller in amplitude. The transformer turns ratio also provides tuning at the resonant frequency of the crystal, which usually means a relatively low-impedance primary winding.

An operational transconductance amplifier (OTA) is preferred over an op amp to drive such a low impedance. One particular application involves a pulse-echo driver circuit using the OPA2662.


SIMPLE PSEUDORANDOM VOLTAGE SOURCE

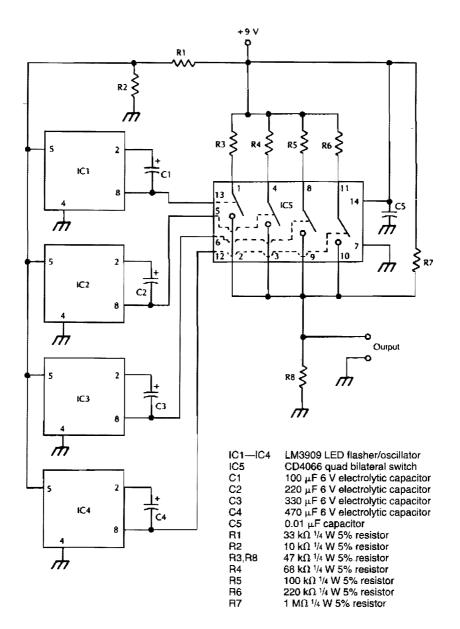

McGRAW-HILL

Fig. 52-20

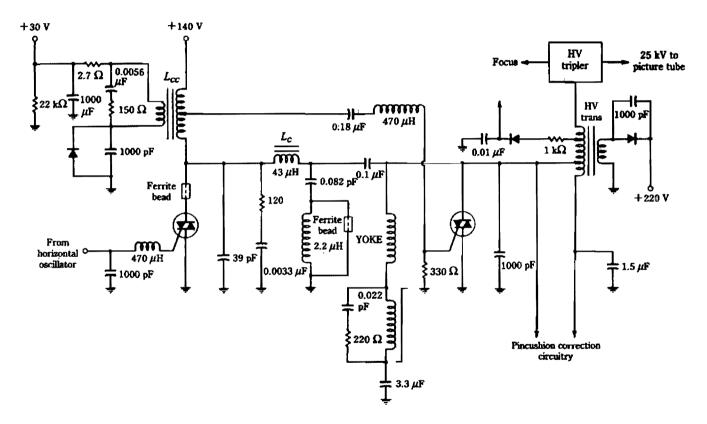An approximation to a pseudorandom voltage is produced by combining the outputs of four low-frequency oscillators with 0.3, 0.6, 0.9, and 1.4 Hz frequencies. The summing network is a quad bilateral switch and resistor network. TV HORIZONTAL DEFLECTION CIRCUIT




McGRAW-HILL

Fig. 52-21

The circuit illustrates the method of using two SCR devices in a TV horizontal deflection application. This circuit was widely used by certain TV manufacturers as an alternate to the vacuum tube or transistor deflection circuit.

,

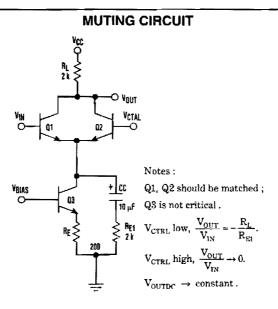

ELECTRONIC DESIGN

Fig. 52-22

The circuit operates as follows: The signal is input to $V_{\rm in}$ and a dc control voltage is applied to $V_{\rm c}$. $V_{\rm bas}$ determines the desired bias point current. Assuming the following component and voltage values:


$$\begin{split} V_{\rm cc} &= 7.6 \; \mathrm{Vdc} \\ V_{\rm bias} &= 1 \; \mathrm{Vdc} \\ V_{\rm in} &= 1 \; \mathrm{Vp-p}, \; \mathrm{ac} \; \mathrm{signal} \; \mathrm{centered} \; \mathrm{about} \; 3.8 \; \mathrm{Vdc} \; \mathrm{bias} \\ R_{\rm L} &= 2 \; \mathrm{k} \Omega \\ R_{\rm E} &= 200 \; \mathrm{k} \Omega \\ R_{\rm E1} &= 2 \; \mathrm{k} \Omega \end{split}$$

Q3 bias current is 1 mA, and dc output voltage is about 5.8 V with an ac gain of about -1, Q1 and Q2 form a current switch and Q3 acts as a constant current source.

For unmuted operation, $V_c = 0$ Vdc, and all of the bias current flows through Q1. Consequently, the circuit operates as a normal common emitter stage, with ac gain = $-R_L/R_{E1}$. When $V_c = 5$ Vdc, all of the bias current flows through Q2, reducing the signal gain to zero. However, because the same dc current flows through R_L in both cases (unmuted and muted), the bias point at the output remains fixed. The C_c/R_{E1} network is required to bypass the Q3 current source (which is a high impedance) to achieve a low ac impedance at the emitter of the Q1 common emitter stage during unmuted operation. C_c is chosen to be a short circuit at signal frequencies of interest. The circuit works best if the Q1 and Q2 pair is matched. Typical change in the output dc voltage from unmuted to muted condition is <5 mVdc.

 $R_{\rm L},R_{\rm E}$, and $V_{\rm bias}$ are chosen for desired dc operating conditions and signal dynamic range. $V_{\rm bias}$ can be generated via a $V_{\rm cc}$ voltage divider. The signal at $V_{\rm in}$ can be ac coupled, but a bias circuit must be added to Q1's base to generate a dc component. $R_{\rm E1}$ is chosen for desired ac gain. $V_{\rm in}$ must be centered about a dc component, and, to assure proper switching action, $V_{\rm CT}R_{\rm L}$ must be higher than $V_{\rm in}$ by an amount greater than one $V_{\rm BE}$ drop.

SIMPLE REMOTE GAIN CONTROL

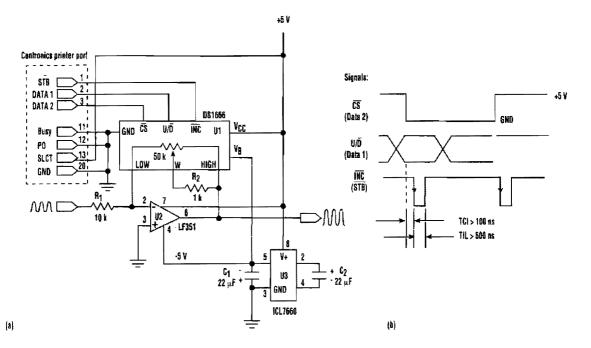


REMOTE CONTROL OF GAIN using a digital audio resistor is possible with this circuit scheme (a). It requires only three ICs and a single 5-V supply to provide gain control via a PC printer port. The input signals to U1 from the printer port are given (b).

100 REM LPGAIN.BAS 120 REM GAIN CONTROL FROM PC PRINTER PORT 200 OPEN "LPT1;" FOR OUTPUT AS \$1 210 INPUT "GAIN UP OR DOWN (1/0): "; X 220 IF X<0 OR X>1 THEN GOTO 210 300 REM 310 INPUT "NUMBER OF COUNTS: "; C 320 REM SUBROUTINE WOULD START HERE 330 PRINT \$1, CHR\$(X); 340 C = C-1 : IF C>0 THEN GOTO 330 350 PRINT \$1, CHR\$(3) 360 GOTO 210 380 RETURN

ELECTRONIC DESIGN

Fig. 52-23

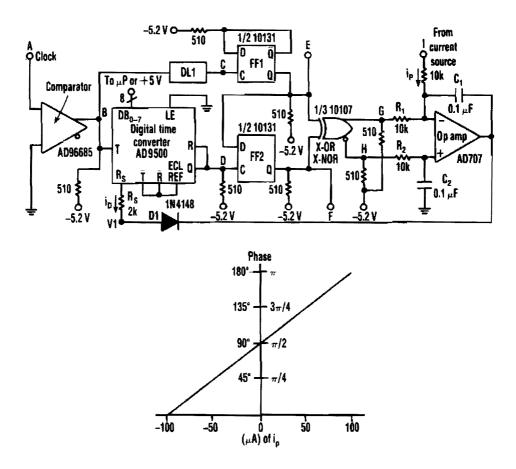The listing is a test program that demonstrates circuit operation using an IBM-compatible PC. To form a subroutine for a main program, use lines 330 to 380, deleting line 360. The calling program then would pass values for X (wiper direction) and C (number of increments).



LOOP OSCILLATOR ELIMINATOR


ELECTRONIC DESIGN

Fig. 52-24

This circuit uses negative feedback to a digital-to-time converter, and can supply a current-controlled delay to replace the oscillator in a phase-locked loop that handles input frequencies from 40 kHz to 40 MHz.

A current sourced into the inverting input of the op-amp integrator's summing node can phase shift the pulses at F in relation to those at E by up to 180° .


1-A VOLTAGE FOLLOWER

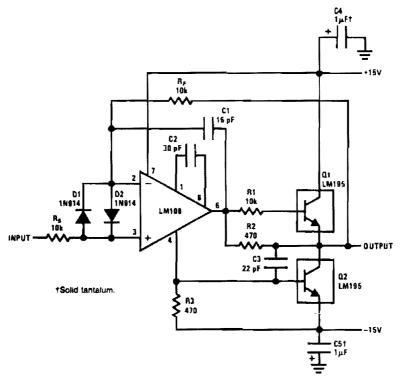

NATIONAL SEMICONDUCTOR

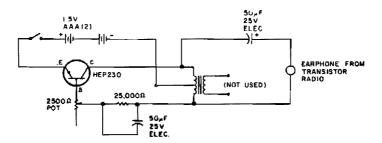This power voltage follower is good to 300 kHz.






73 AMATEUR RADIO TODAY

Fig. 52-26

Fig. 52-25

The click-click sound lures fish to the vicinity, where your bait or lure can do the rest. The transformer is a subminiature type with a 500- Ω , center-tapped primary and a 3.2- Ω secondary. Put the circuit in a watertight container and lower it into the water.

HEARTBEAT TRANSDUCER

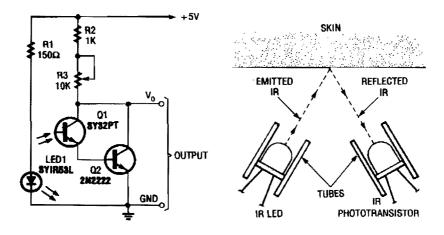


POPULAR ELECTRONICS

Fig. 52-27

A simple heart-beat transducer can be made from an infrared LED and an infrared phototransistor. It works because skin acts as a reflective surface for infrared light. The IR reflectivity of one's skin depends on the density of blood in it. Blood density rises and falls with the pumping action of the heart. So the intensity of infrared reflected by the skin (and thus transmitted to the phototransistor) rises and falls with each heartbeat.

CONTACT DEBOUNCER

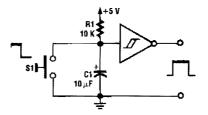


ELECTRONICS NOW

provides a Vala---- ? ----l-- f-----

A contact debouncer using a Schmitt trigger, such as a TTL7414, provides a "clean" pulse from a switch contact closing.

Fig. 52-28


POSITIVE FEEDBACK CABLE TERMINATOR

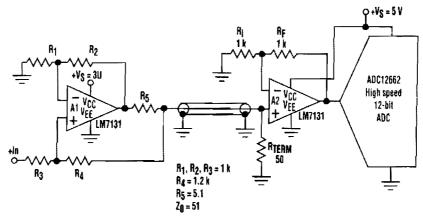

ELECTRONIC DESIGN

Fig. 52-29

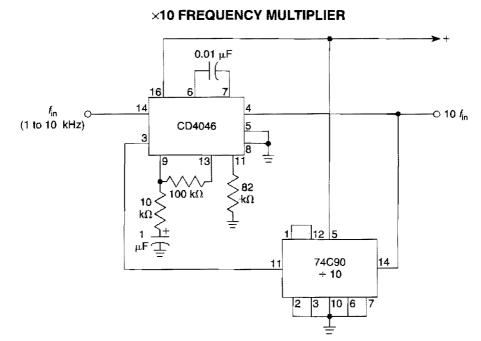Positive feedback along with a series output resistor can provide a controlled output impedance from an op-amp circuit. The circuit is useful when driving coaxial cables that must be terminated at each end in their characteristic impedance, which is often 50 Ω . Adding a 50- Ω series resistor on the op amp's output obviously reduces the available signal swing.




WILLIAM SHEETS

Fig. 52-30

In this circuit, the CD4046 is set up so that the $V_{\rm CO}$ operates at 10 to 100 kHz. The output pin (4) is fed back to a ± 10 counter. When the input frequency is $\frac{1}{10}$ the output, lockup will occur.


JACOB'S LADDER

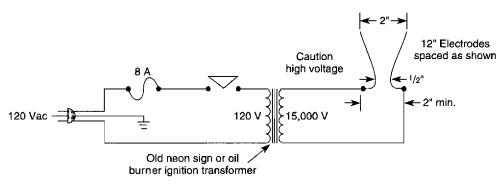

WILLIAM SHEETS

Fig. 52-31

A "Jacobs Ladder" can be made from an old neon sign or oil burner ignition transformer. A rating of 12 to 15 kV at 20 to 30 mA will be adequate. Make sure to mount the electrodes to a pair of insulators, at least 2" apart, and bent and spaced, as shown. The ladder should be enclosed in a clear plastic housing to prevent accidental contact with the high voltage and to ensure a stable arc. Vent holes should be placed top and bottom to allow gases to escape.

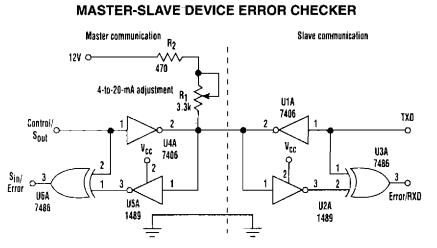


ELECTRONIC DESIGN

Fig. 52-32

An error-check mechanism introduced into master and slave communication devices can indicate mismatches when both the master and slave start sending data simultaneously. The error flag goes high and indicates a mismatch in the data.

The master is the one that can interrupt the communication from a device at the other end and force it to listen. It does this forcing a low voltage level over the communication line by raising the control line to a high level. This inhibits data flow over the lines from the slave device. As a result, the slave turns into a listen mode (not a hardware feature, but rather incorporated in the software). The slave device can transmit the data after communication from the master device ceases.

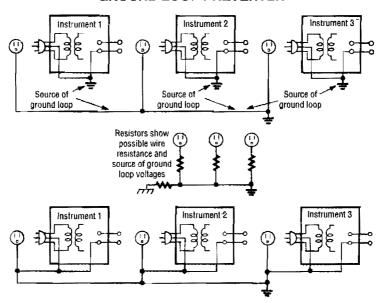


GROUND LOOP PREVENTER

ELECTRONICS NOW

Fig. 52-33

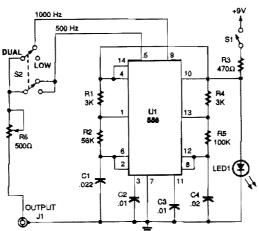Ground loops are caused by improper grounding. Ground-loop voltages can interfere with test measurements because the voltages in a ground loop can be larger than the signals you're trying to measure. To prevent ground loops, use two wire plugs to provide the line power to the test instruments and a separate wire to bring the input grounds of the instruments to a common ground.






POPULAR ELECTRONICS

Fig. 52-34

This dual-tone generator can insert a distinctive tone in the audio section of a circuit under test. That way, you can work your way back from the speaker, stage-by-stage, to locate a faulty section.

DIODELESS PEAK-HOLD CIRCUIT

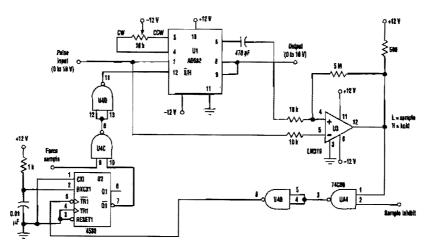

ELECTRONIC DESIGN

Fig. 52-35


The input pulse is fed into the sample-and-hold amplifier (an inexpensive AD582), as well as the comparator U3. The SHA's output also is fed into the comparator. If the input pulse is higher in amplitude than the SHA's output, the comparator output goes low and the 4538 one-shot produces a 10- μ s pulse that is fed back to cause the SHA to sample and then hold the voltage. Subsequent input voltages that are less than the held value won't cause the one-shot to fire again.

Gates U4A and U4B are used to inhibit the sampling when nccessary. Gates U4C and U4D, at the one-shot's output, can force the AD 582 into the sample mode. This feature is useful to reset the output to zero by forcing a sample when the input to the AD582 is zero. The polarity of the peak-hold circuit can be easily changed from positive-to-negative peak hold by reversing the inputs of the comparator.

Mixer Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


Simple Audio Mixer Op-Amp Audio Mixer

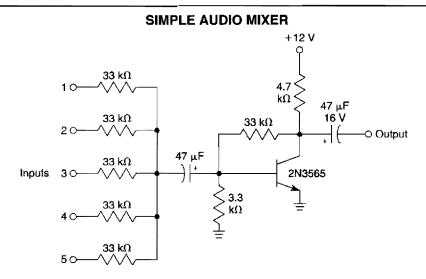

WILLIAM SHEETS

Fig. 53-1

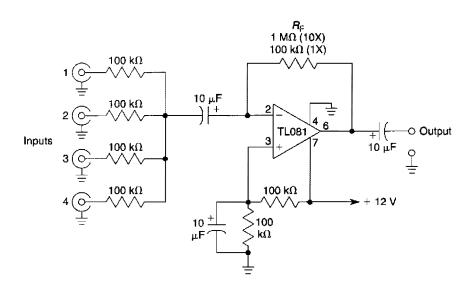A single transistor is used as an audio mixer, the transistor serving as a feedback amplifier.



OP-AMP AUDIO MIXER

WILLIAM SHEETS


Fig. 53-2

This circuit will mix several audio signals to a common output. R_p can be made 1 M Ω for 10 × (20 dB) or 100 k Ω for unity gain.

Model and Hobby Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

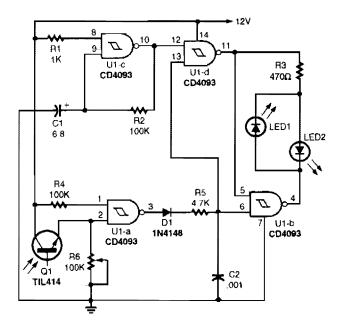Model Railroad Crossing Flasher Model Railroad Track Control Signal



MODEL RAILROAD CROSSING FLASHER


POPULAR ELECTRONICS

Fig. 54-1

Gate U1-c is set up as an oscillator whose frequency is determined by C1 and R1. Gates U1-b and U1-d are set up as an RS flip-flop that is gated on by U1-a. Gate U1-a in conjunction with Q1 operates as the control gate for the flip-flop. Components D1, C2, and IR5 act as a delay circuit to compensate for any light getting through the gaps between cars as they pass over the phototransistors. The light-emitting diodes are connected so that they operate alternately, depending on the outputs of U1-d and U1-b.

Basically, R6 is adjusted so that ambient room-light striking Q1 (and any other phototransistors connected in series) keeps the output of U1-a at pin 3 low. When a car passes over the phototransistor, which is installed between ties in the track, pin 3 goes high, allowing a high to be placed on pins 5 and 13. That allows the high output of U1-c at pin 10 to enable pin 12, which in turn allows pin 11 to go low. That makes a complete path for LED2 to operate. When pin 10 goes low, pin 11 goes high. That makes pin 5 high, and thus, enables pin 4 to go low and completes the circuit for LED1. That alternates the LEDs, which are installed in a railroad-crossing signal.

MODEL RAILROAD TRACK CONTROL SIGNAL

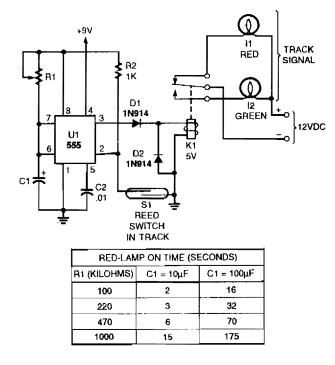

POPULAR ELECTRONICS

Fig. 54-2


When a train passes S1 (a red switch), a small magnet glued to the underside operates S1 and causes U1 to generate a pulse, activating relay K1 and changing the signal from green to red. After a time determined by R1 and C1 (see table), the relay de-energizes and the signal goes back to green.

Modulator Circuits

 $T_{\rm hc}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Varactorless HF Modulator Modulator for Video Digital Pulse-Width Modulation Circuit Four-Quadrant Multiplier as DSB Modulator Pulse-Width Modulator Linear (AM) Amplitude Modulator Video Modulator Hookup

VARACTORLESS HF MODULATOR

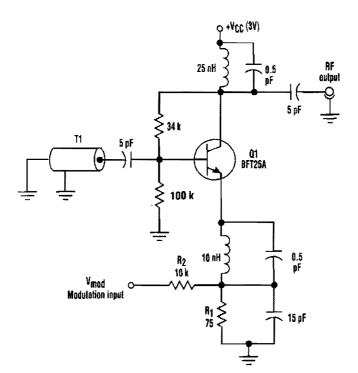

ELECTRONIC DESIGN


Fig. 55-1

Traditionally, high-frequency oscillators are frequency-modulated by using a varactor. However, varactors usually require a large voltage change to achieve a reasonable capacitance change—a problem in many battery-powered systems.

Such a problem can be overcome by employing base-charging capacitance modulation. Resistor R1 establishes Q1's current, and R2 allows control of the collector bias current by $V_{\rm mod}$. The transmission line (T1) in the negative resistance-type oscillator determines the frequency of oscillation. T1 is a high-quality, low-loss, ceramic coaxial shorted quarter-wave transmission line. Under proper terminal impedances, a negative resistance is "seen" at Q1's base. T1 reacts with this negative resistance to produce sustained oscillations.

Frequency modulation is accomplished by changing Q1's collector bias current and thus changing Q1's base-charging capacitance. This effect is "seen" at Q1's base and causes a frequency shift in the resonators quarter-wave node.


MODULATOR FOR VIDEO

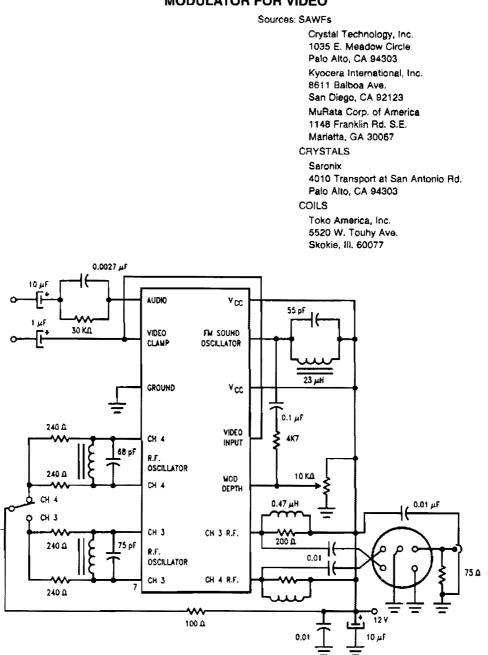

NATIONAL SEMICONDUCTOR

This circuit uses an LM2889 and a saw filter for use as a TV modulator.

Fig. 55-2

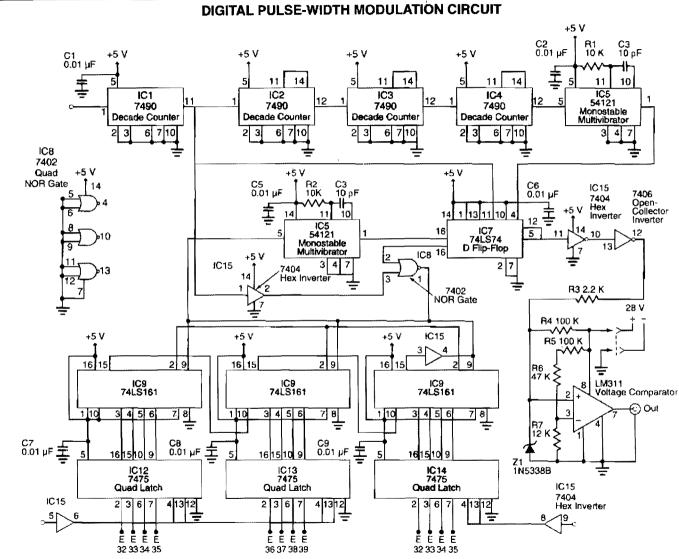

NASA TECH BRIEFS

Fig. 55-3

DIGITAL PULSE-WIDTH MODULATION CIRCUIT (Cont.)


This circuit incorporates low-power Schottky transistor/transistor-logic (TTL) devices in critical high-speed parts. The 5-MHz clock signal is converted to a 1-MHz signal by a 7490 decade counter configured to divide by 5. The 1-MHz signal is sent, via a clock synchronizer, to a three-stage binary divider that consists of three cascaded 74LS161 binary dividers. The synchronizer consists of a 74LS74 D flip-flop, a 7404 inverter gate, and a 7402 NOR gate. The dividers are programmed from the STD bus by means of three 7475 quad latches; this makes it possible to program the frequency division from 1 to 4096 (12 bits).

The 1-MHz signal is also divided by 1000 by use of three cascaded 7490 decade counters, each configured to divide by 10; this provides a 1-kHz signal, which is sent to a 54121 monostable multivibrator configured to provide a 0.1- μ s pulse, bombarded with an ion beam source in preparation for the materials about to be deposited. While the surface is bombarded with an ion beam, an electron beam source is activated so that a layer of fused silica is vapor-deposited to a total desired thickness value (typically, 1 micron or 10,000 Å). The layer of fused silica serves as a surface stabilization layer for the next step.

A metal mask with an aperture in the specified pattern of the sensor film is placed on the surface at the specified sensor location. The surface area exposed through the mask is cleaned by ion-beam bombardment for a predetermined time. Then as the bombardment continues, a metal (typically, nickel, platinum, and/or palladium) is vapor-deposited through the mask from the electron-beam source to form the sensor film. Deposition is continued until the thickness of the film reaches the value specified in the particular sensor design. A representative value for a nickel sensor film is 2500 Å.

Next, a pattern for thin film leads is defined by taping directly on the surface of the model with Kapton (or equivalent) polyimide tape. The thin film leads are fabricated by a combination of ionbeam bombardment and electron-beam vapor deposition like that used to deposit the sensor film. The metal vapor deposited in this step is typically copper, gold, or aluminum. A typical thickness for copper leads on the nickel sensor film is about 10,000 Å.

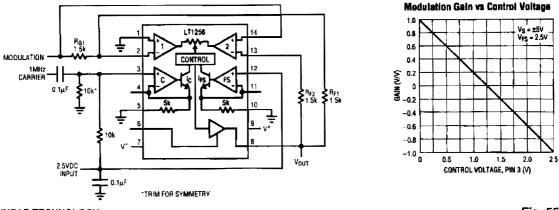
FOUR-QUADRANT MULTIPLIER AS DSB MODULATOR








PULSE-WIDTH MODULATOR

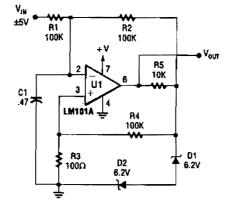

POPULAR ELECTRONICS




LINEAR (AM) AMPLITUDE MODULATOR

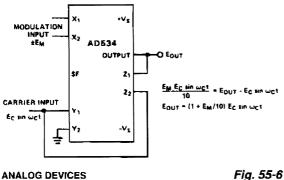

This is a very simple amplitude modulator. It makes use of the Z2 terminal to add the carrier directly to the output, thus bypassing the multiplier for zero modulation input. It has the advantage of allowing operation from a differential modulation input.

VIDEO MODULATOR HOOKUP

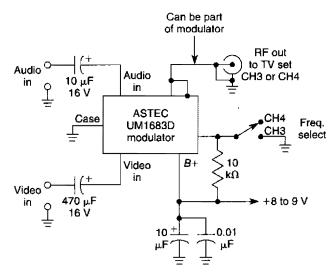

WILLIAM SHEETS


Fig. 55-7

This circuit uses an ASTEC UM1683D, but it is typical of many RF video modulators used in VCRs and satellite receivers.

Morse Code Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

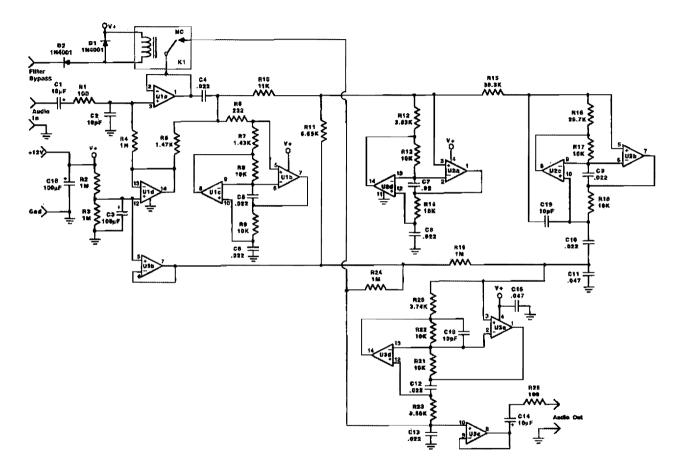Active CW Audio Filter Morse Messenger CW Identifier with Sine-Wave Audio Output Simple Code Practice Oscillator ACTIVE CW AUDIO FILTER




73 AMATEUR RADIO TODAY

Fig. 56-1

The audio filter shown has a bandpass of 200 Hz centered on 700 Hz. Resistors are 1% tolerance and capacitors should be 5% tolerance.

405

MORSE MESSENGER

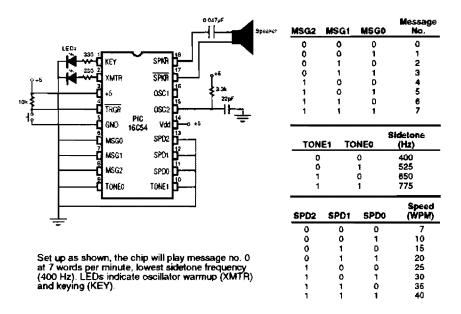


Simple hook-up diagram for the Morse Messenger chip. The table indicates the range of messages, sidetones, and keying speeds.

73 AMATEUR RADIO TODAY

Fig. 56-2


This keyer uses a PIC16C54 micro-controller to generate a Morse code message. The microcontroller must be programmed to suit users call IC or desired message.

MORSE MESSENGER (Cont.)

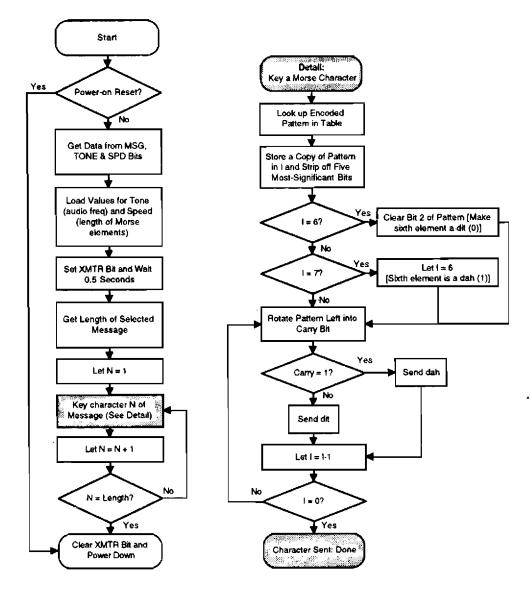

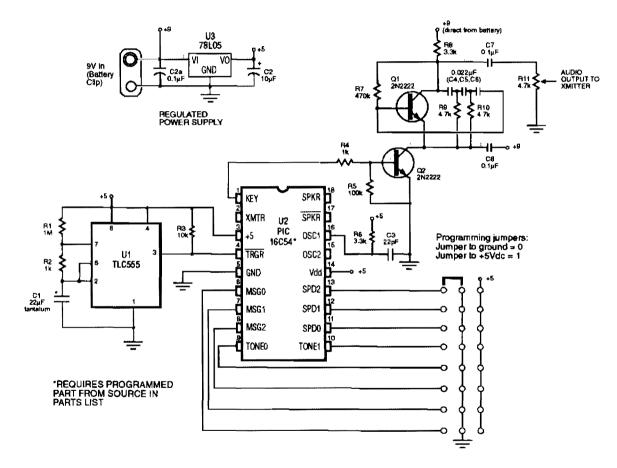Logic of the Morse Messenger's program. This algorithm can be adapted to other devices with the help of the Morse encoding table.






73 AMATEUR RADIO TODAY



This identifier can be used to drive a hidden transmitter in a radio "fox hunt" activity, where the object is to locate a hidden transmitter.

SIMPLE CODE PRACTICE OSCILLATOR

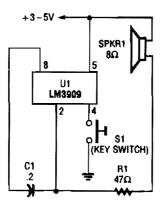

POPULAR ELECTRONICS

Fig. 56-4


With only a minor circuit change, the basic LM3909 oscillator configuration can be turned into a code-practice oscillator.

Motor-Control Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Precise de Motor Speed Controller Accurate Motor Speed Control Motor Direction Control Using Discrete Transistors Long Time-Delay Motor-Control Circuit Full-Wave Speed Control for Motors SCR Motor Speed Control Triac Motor-Control Circuit Low-Voltage de Motor-Speed Controller Motor Direction Control

PRECISE dc MOTOR SPEED CONTROLLER

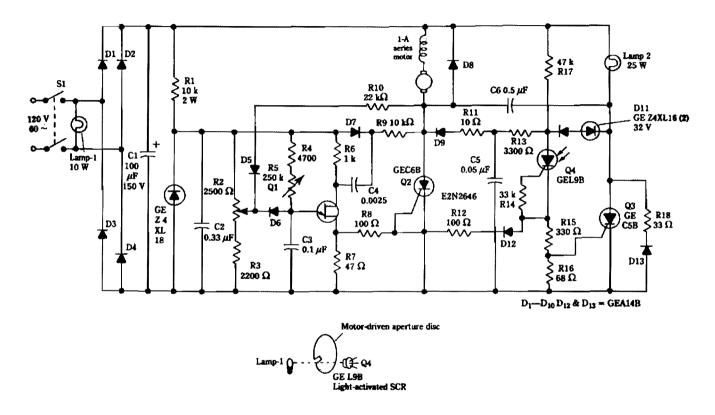


McGRAW-HILL

Fig. 57-1

A series dc motor can be made to have the same characteristics as an ac synchronous motor using this circuit. This control technique is useful where a constant motor speed is needed.

.

ACCURATE MOTOR SPEED CONTROL

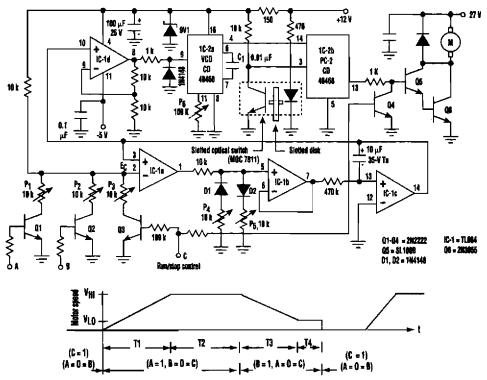

This motor velocity profile is provided by the controller. Note the smooth acceleration and deceleration profiles and the constant motor speed between the two ramps.

ELECTRONIC DESIGN


Fig. 57-2

This circuit can control dc motors used in machines that pull materials, such as wire, yarn, film, etc., from the supply rolls and rewind them onto smaller rolls. Its motor velocity profile is shown in the figure.

A lightweight disk with at least 32 slots is mounted on the motor shaft. It works in a slotted optical switch (MOC7811) to sense the motor speed. Phase comparator 2 (PC-2) of the phase-locked loop (IC-CD 4046B) compares the frequency (f_v) at the output of the VCO with the pulse rate (f_m) at the optical switch output. The PC-2 output drives the motor via the transistors when $f_v > f_m$, and removes the supply to the motor when $f_m > f_v$. The drive system quickly reaches an equilibrium condition when $f_m = f_v$.

Op amps IC-1a, 1b, and 1c form a tracking integrator whose output always smoothly reaches and remains at a voltage equal to the command voltage (E_c) presented at the inverting input of op-amp IC-1a. When the digital control inputs are set to (A = 1, B = 0 = C), the integrator generates a positive slope ramp that sweeps the VCO frequency and, thus, accelerates the motor. The acceleration rate and the constant speed $V_{\rm HI}$ can be adjusted by presents P4 and P1, respectively.

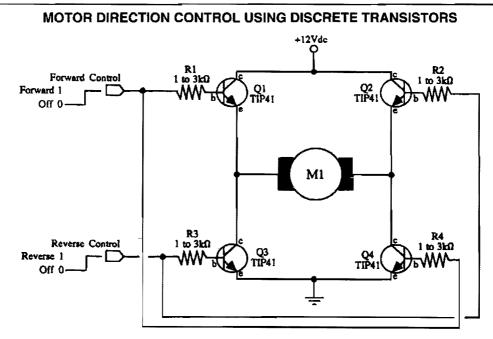Similarly, when the inputs are set to (A = 0 = C, B = 1), the integrator generates a negative slope ramp that decelerates the motor. Presets P5 and P2 can be adjusted to set the required deceleration and the constant speed V_{LO} , respectively.




McGRAW-HILL

Fig. 57-3

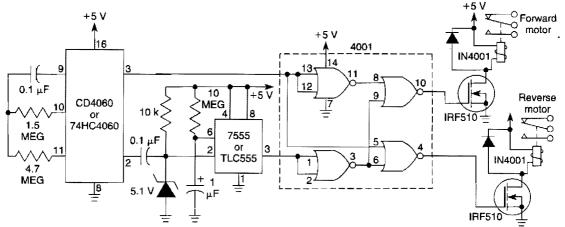For best operation, mount the transistors on heatsinks. The transistors specified are fine for small hobby motors, or up to about 6 volts dc and between 800 and 1000 mA. M1 is a small hobby motor.






ELECTRONICS NOW

Fig. 57-4

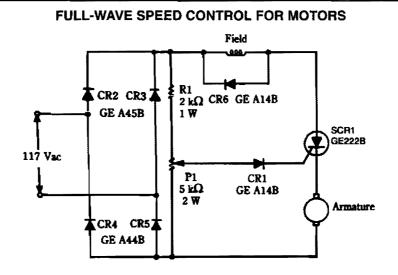
Circuit controls forward and reverse motors. Every hour, one motor runs for 10 seconds.



McGRAW-HILL

Fig. 57-5

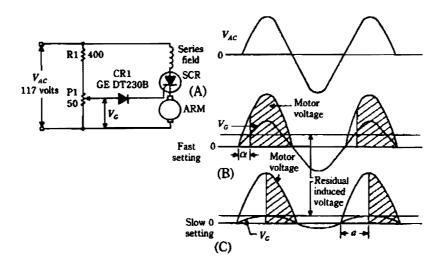A bridge rectifier provides pulsating dc to a universal motor, and the SCR is used as a phase-controlled switch. This circuit allows smoother operation of the motor at low speeds.




SCR MOTOR SPEED CONTROL

McGRAW-HILL

Fig. 57-6

An SCR is used in a phase-control type application to supply a variable pulsating dc voltage to a motor.


TRIAC MOTOR-CONTROL CIRCUIT

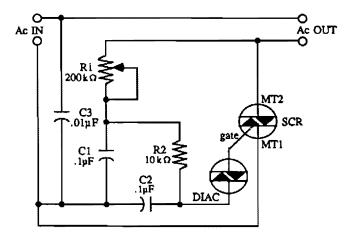

McGRAW-HILL

Fíg. 57-7

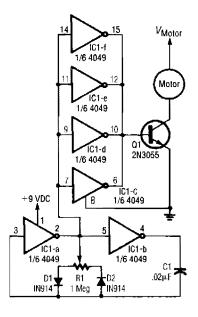An SCR-controlled ac motor control circuit. This is a full-wave circuit and is best used when the load remains constant.




LOW-VOLTAGE dc MOTOR-SPEED CONTROLLER

ELECTRONICS NOW

Fig. 57-8

This circuit varies the duty cycle, rather than the voltage. The two diodes control the positive and negative halves of the capacitor's charging cycle.

MOTOR DIRECTION CONTROL

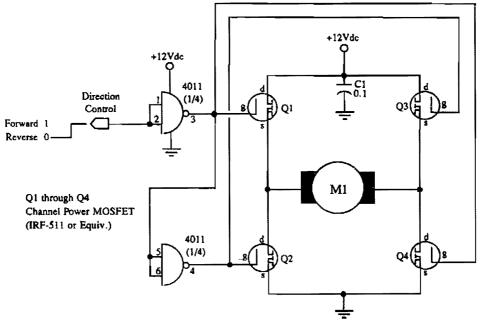

McGRAW-HILL


M1 is a small hobby dc motor.

Multivibrator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


Astable Multivibrator with Starting Network Bistable Multivibrator Astable Astable with Variable Pulse Width One-Shot Multivibrator Basic 555 Astable Multivibrator Astable Multivibrator

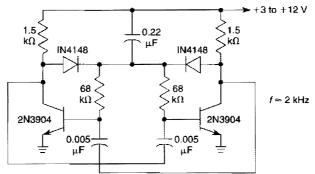ASTABLE MULTIVIBRATOR WITH STARTING NETWORK



WILLIAM SHEETS

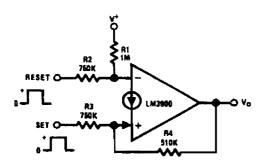This circuit will start with a slowly rising supply voltage waveform.




BISTABLE MULTIVIBRATOR

Positive feedback is provided by resistor R4, which causes the latching. A positive pulse at the "set" input causes the output to go high and a "reset" positive pulse will return the output to essentially 0 Vdc.

Fig. 58-1

NATIONAL SEMICONDUCTOR

Fig. 58-2

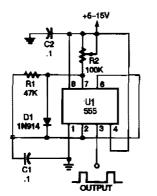


ASTABLE

At the instant that power is applied to the 555 astable, timing capacitor C1 is initially discharged, causing the output of the chip output at pin 3 to be high. Once C1 has charged to about % of the supply voltage, its output goes low, and the discharge transistor turns on, draining the charge on C1.

POPULAR ELECTRONICS



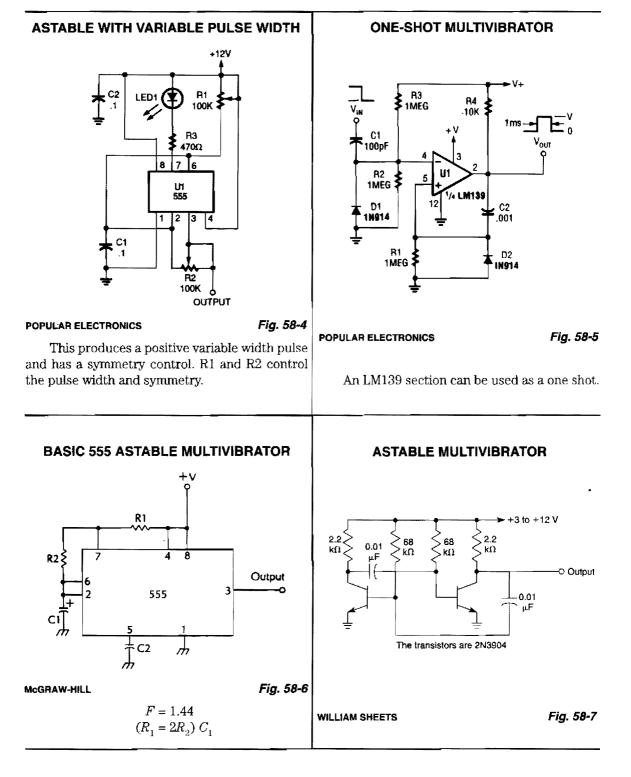


Noise Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


Noise Generator Dolby Noise-Reduction Circuit Audio Noise-Based Voting Circuit Adjustable Noise Clipper Simple Noise Limiter

NOISE GENERATOR

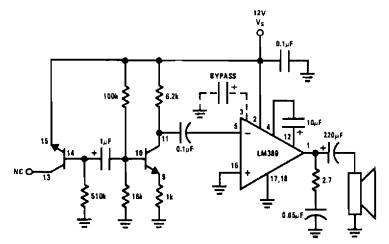

NATIONAL SEMICONDUCTOR

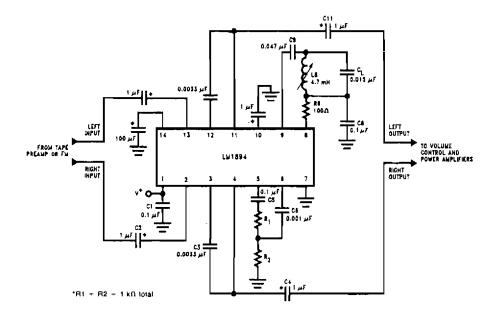This noise generator uses a Zener diode. The transistors are part of the LM389.




DOLBY NOISE-REDUCTION CIRCUIT

NATIONAL SEMICONDUCTOR


Fig. 59-1

AUDIO NOISE-BASED VOTING CIRCUIT

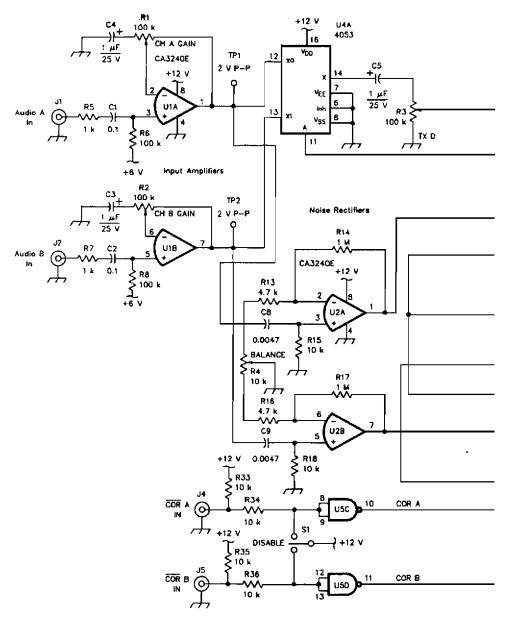


QST

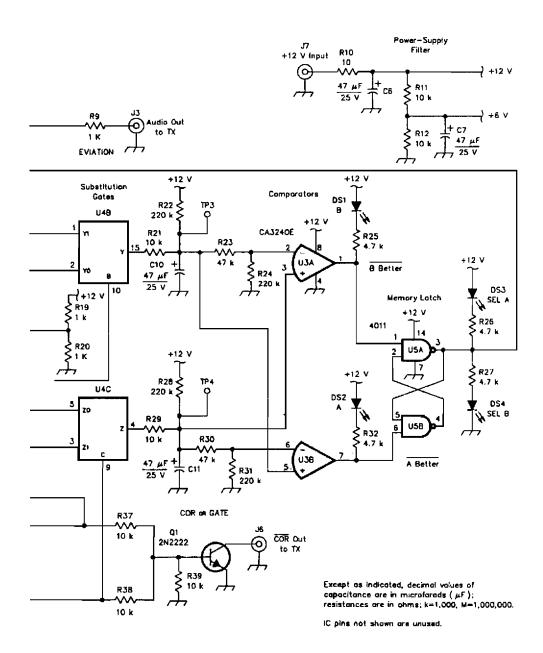The purpose of this circuit is the selection of the output of two receivers, tuned to the same channel, that has the better signal to noise ratio. This circuit compares the two noise leads from the receivers and selects the one with the lower audio noise level.




ADJUSTABLE NOISE CLIPPER

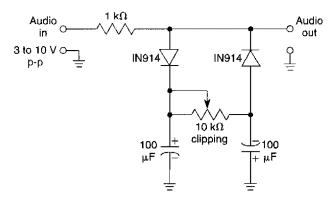

WILLIAM SHEETS

Fig. 59-4

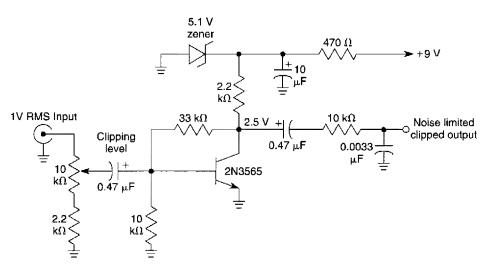This circuit uses two diodes and is a peak-to-peak limiter. The capacitors charge up to a dc level determined by the peak-to-peak audio signal and the clipping control. A positive or negative peak or spike is clipped if it exceeds this level plus the diode drops. The circuit should be operated at several volts level for best results.



SIMPLE NOISE LIMITER

WILLIAM SHEETS

Fig. 59-5

This circuit uses a symmetrical limiter obtained by biasing a transistor to a Q point that is half of the supply voltage and driving it into saturation and cutoff. An input of 1 to 2 V RMS is sufficient. This output will be approximately 4 V p-p into a high-impedance load.


60

Operational Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Basic Op-Amp Circuits Op Amps with Long RC Time Constants Op-Amp Offset Null Basic Op-Amp Audio Amplifier Input Guarding for HJ-Z Op Amps Enhanced Op-Amp Balanced Amplifier Paralleled Power Op Amps Single-Supply Op-Amp Applications Current Regulator Op Amp Op-Amp Resistance-Multiplication Circuit Pseudoground

BASIC OP-AMP CIRCUITS

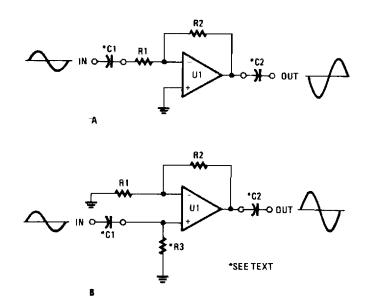


RADIO-ELECTRONICS

Fig. 60-1

Fig. 60-2


The two simplest op-amp configurations are the inverting (A) and the noninverting (B). Resistor R3 is needed only if C1 is used in the noninverting circuit.

OP AMPS WITH LONG RC TIME CONSTANTS

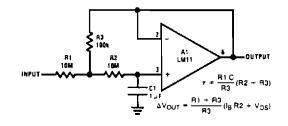

NATIONAL SEMICONDUCTOR

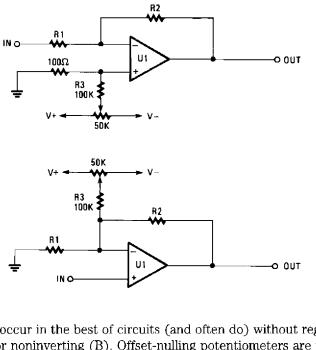This circuit multiplies RC time constant to 1000 seconds and provides low output impedance. Cost is lowered because of reduced resistor and capacitor values.




OP-AMP OFFSET NULL

RADIO-ELECTRONICS

A

Fig. 60-3

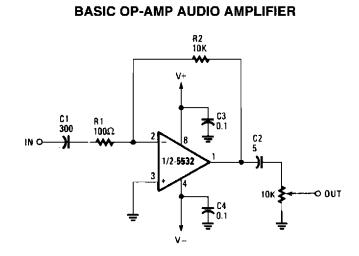Offset problems can occur in the best of circuits (and often do) without regard to whether the circuit is inverting (A), or noninverting (B). Offset-nulling potentiometers are useful in correcting the output to zero, but their effectiveness will vary under different conditions.




RADIO-ELECTRONICS


Any general-purpose op amp can be used in this application.

Fig. 60-4


INPUT GUARDING FOR HI-Z OP AMPS

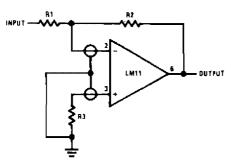



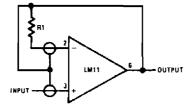


b. follower

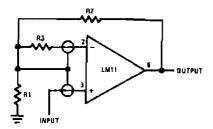

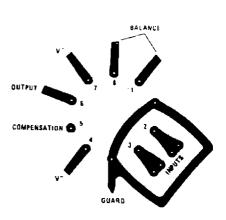c. non-inverting amplifier

Input guarding for various op amp connections. The guard should be connected to a point at the same potential as the inputs with a low enough impedance to absorb board leakage without introducing excessive offset.






Bottom view

Input guarding can drastically reduce surface teakage. Layout for metal can is shown here. Guarding both sides of board is required. Bulk leakage reduction is less and depends on guard nng width.

Fig. 60-5

ENHANCED OP-AMP BALANCED AMPLIFIER

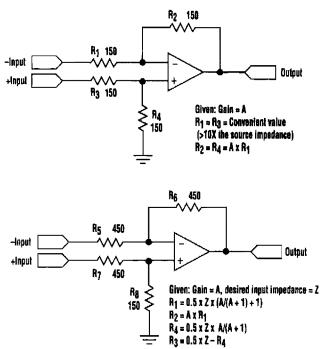


ELECTRONIC DESIGN

Fig. 60-6

The classic single op-amp balanced circuit works well in low-source-impedance configurations, but tends to struggle in higher-source-impedance applications because of the varying input impedance of the inputs referred to ground.

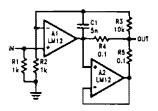A modified version of the classic op-amp configuration of the figure uses a different set of formulas to determine the resistor values. It equalizes the impedance of both inputs by considering the op amp's active participation.






NATIONAL SEMICONDUCTOR

Fig. 60-7

Two power op amps can be paralleled using this master/slave arrangement, but high-frequency performance suffers.

SINGLE-SUPPLY OP-AMP APPLICATIONS

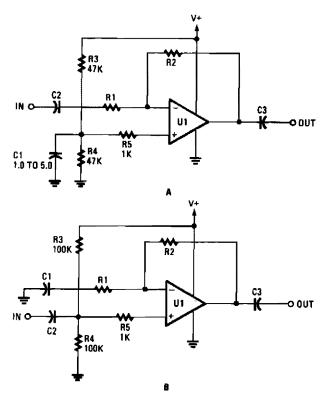

RADIO-ELECTRONICS

Fig. 60-8

An op amp that normally needs two supplies can be used when only a single supply is needed. The value of V+ should be twice the minimum allowable values of the positive and negative voltages normally needed. For example, a 12-V single-supply application would require an op amp capable of \pm 6-V operation.


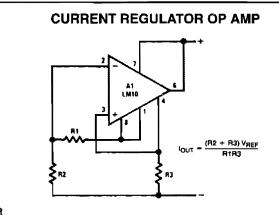


Fig. 60-9

OP-AMP RESISTANCE MULTIPLICATION CIRCUIT

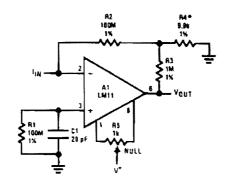


NATIONAL SEMICONDUCTOR

Fig. 60-10

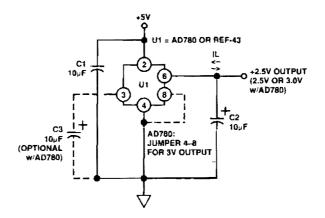Equivalent feedback resistance is 10 G Ω , but only standard resistors are used. Even though the offset voltage is multiplied by 100, output offset is actually reduced because error is dependent on offset current, rather than bias current. Voltage on summing junction is less than 5 mV.





ANALOG DEVICES

Fig. 60-11


For op-amp circuits, a "pseudo ground" is often needed; a voltage reference IC can be used. The Analog Devices AD780 is used here for this application. This can sink or source current.

61

Oscillators (Audio)

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

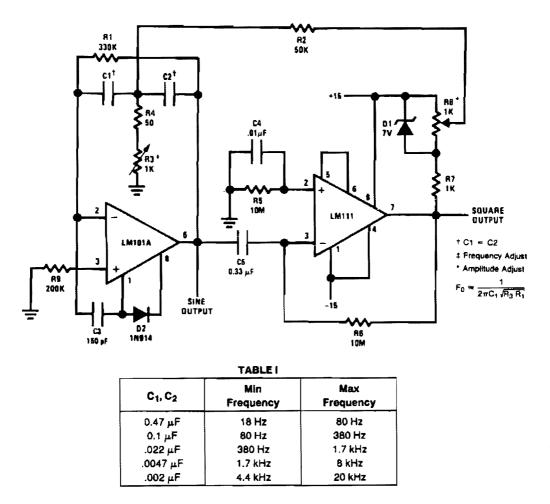Easily Tuned Sine-Wave Oscillator Quad Tone Oscillator One-Transistor Phase-Shift Oscillator Basic LM3909 Audio Oscillator Low-Distortion Sine-Wave Oscillator Low-Frequency Astable TTL-Based Audio Oscillator Variable Duty Cycle from Astable Simple Variable-Frequency Oscillator Wien-Bridge Oscillator I Wien-Bridge Oscillator II Logic-Gate Sine-Wave Oscillator EASILY TUNED SINE-WAVE OSCILLATOR




NATIONAL SEMICONDUCTOR

Fig. 61-1

The circuit will provide both a sine- and square-wave output for frequencies from below 20 Hz to above 20 kHz. The frequency of oscillation is easily tuned by varying a single resistor. This is a considerable advantage over Wien bridge circuits, where two elements must be tuned simultaneously to change frequency. Also, the output amplitude is relatively stable when the frequency is changed.

An operational amplifier is used as a tuned circuit, driven by square wave from a voltage comparator. Frequency is controlled by R1, R2, C1, C2, and R3, with R3 used for tuning. Tuning the filter does not affect its gain or bandwidth, so the output amplitude does not change with frequency. A comparator is fed with the sine-wave output to obtain a square wave. The square wave is then fed back to the input of the tuned circuit to cause oscillation. Zener diode, D1, stabilizes the amplitude of the square wave fed back to the filter input. Starting is ensured by R6 and C5, which provide dc negative-feedback around the comparator. This keeps the comparator in the active region.

QUAD TONE OSCILLATOR

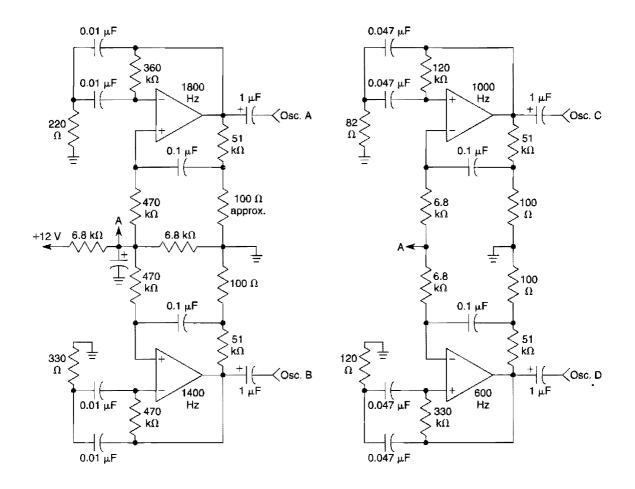


WILLIAM SHEETS

Fig. 61-2

A quad op amp (TL084, etc.) can be used to produce four audio tone generators for use in a test setup. The circuit uses a 12-V supply.



ONE-TRANSISTOR PHASE-SHIFT OSCILLATOR

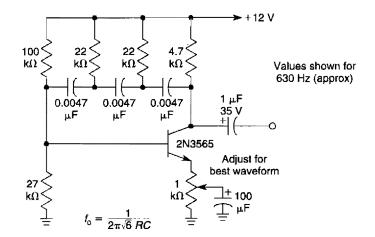

WILLIAM SHEETS

A single transistor is used as an active element in an RC phase shift oscillator.




+v



The LM3909's oscillator frequency can be fine-tuned by adding a resistor to a basic circuit.

R1 NC NC ₹r2 С 7 6 8 5 Speaker LM 3909 2 3 1 4 Ι NC NC ħ

Fig. 61-4

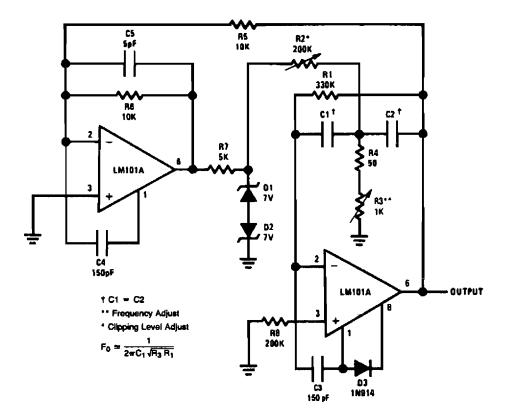


LOW-DISTORTION SINE-WAVE OSCILLATOR

NATIONAL SEMICONDUCTOR

C1, C2	Min. Frequency	Max. Frequency
0. 4 7 µF	18 Hz	8 0 Hz
0.1 µF	80 Hz	380 Hz
$0.022 \mu\text{F}$	380 Hz	1.7 kHz
$0.0047 \mu F$	1.7 kHz	8 kHz
0.002 µF	4.4 kHz	20 kHz

LOW-FREQUENCY ASTABLE

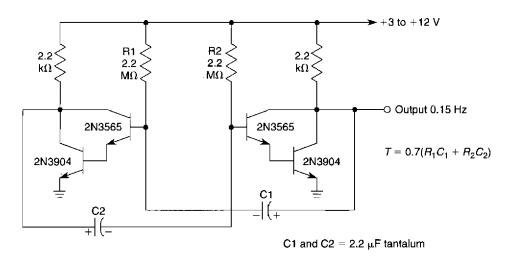


WILLIAM SHEETS

Flg. 61-6

By using a high-gain low-current transistor, such as the 2N3565, a pair of Darlington-connected transistors (2N3565 and 2N3904) can be used in a high-impedance configuration.


TTL-BASED AUDIO OSCILLATOR

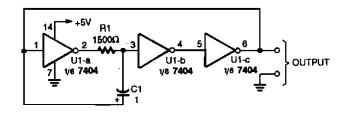

POPULAR ELECTRONICS

Half a 7404 will produce a tone around 1000 Hz with this circuit.

VARIABLE DUTY CYCLE FROM ASTABLE

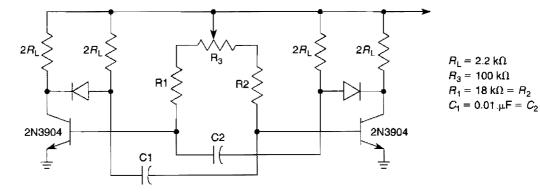

WILLIAM SHEETS

If $R_1 = R_2 = R_3$ and $C_1 = C_2 = C_3$

If potentiometer R3 is set at N% of rotation, then

 $T_{\text{TOTAL}} \approx 0.7 \ [(R + NR_3)C + [R + (1 - N)R_3C]]$

 $T_{\text{TOTAL}} \approx 1.4 \ (R + R_3)C$ and the duty cycle can be varied without changing frequency.

R1 4.7K

> C1 47

83

50)

SIMPLE VARIABLE-FREQUENCY OSCILLATOR

+3-5V

U1 LM3909

2


SPKR1


POPULAR ELECTRONICS

In this variable audio frequency oscillator, the output of U1 at pin 2 is used to drive an $8-\Omega$ speaker through R2 (which functions as a current-limiter).

R2 47Ω Fig. 61-8

WIEN-BRIDGE OSCILLATOR I

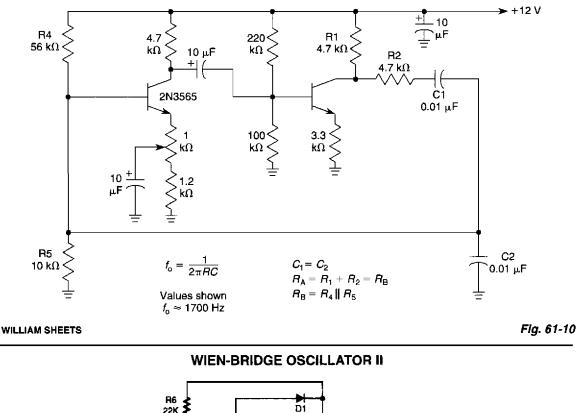

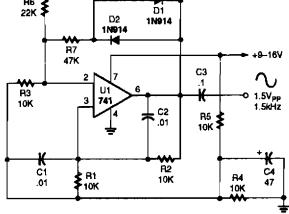


POPULAR ELECTRONICS

Fig. 61-11

The operating frequency of this Wien-bridge oscillator is determined by C1, C2, R1, and R2. It can easily be modified to act as a tunable oscillator by substituting a dual-gang linear potentiometer for R1 and R2.

LOGIC-GATE SINE-WAVE OSCILLATOR

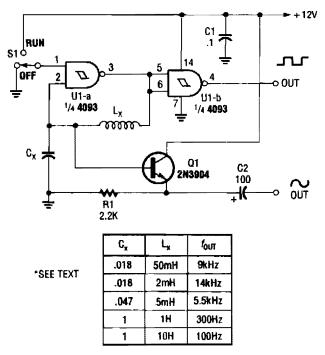

POPULAR ELECTRONICS




An inductor and capacitor are used here as frequency-determining elements in an LC oscillator.

62

Oscillators (Miscellaneous)

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

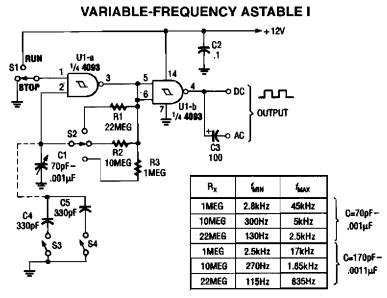Variable-Frequency Astable I Astable Oscillator I Astable Oscillator II Variable-Frequency Astable II Quadrature-Wave Oscillator Stabilized Wien-Bridge Oscillator Digitally Controlled Square-Wave Oscillator 50% Duty-Cycle 555 Circuit Varied Rep Rate, Duty Cycle with 555 DDS Digital VFO




POPULAR ELECTRONICS

Fig. 62-1

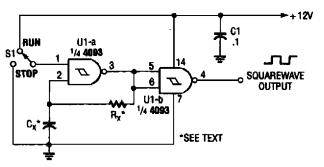This circuit is a variable-frequency oscillator using a trimmer capacitor or a three-gauge AM broadcast capacitor salvaged from an old AM radio. The three sections must be paralleled.





POPULAR ELECTRONICS

Flg. 62-2


In this circuit, two gates from the quad 4093 package are used to form a simple astable squarewave oscillator.

The values for R_x and C_x are approximately as follows:

C _x	R _x	f_{0}
0.001 µF	$1 \ M\Omega$	3 kHz
0.1 μF	1 MΩ	30 Hz
$1 \mu F$	$10 \text{ M}\Omega$	$0.03~\mathrm{Hz}$

These values can be scaled for other frequencies.


ASTABLE OSCILLATOR II

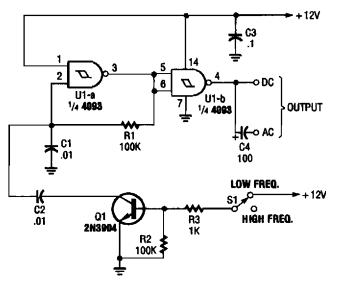


POPULAR ELECTRONICS

Fig. 62-3

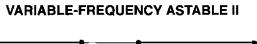By using transistor switch Q1/R2/R3, the frequency of an astable oscillator can be changed with a dc voltage or logic level.



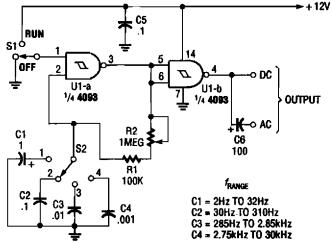


POPULAR ELECTRONICS

Fig. 62-4

This circuit uses a single potentiometer and switched capacitors to cover 2 Hz to 30 kHz.


QUADRATURE-WAVE OSCILLATOR

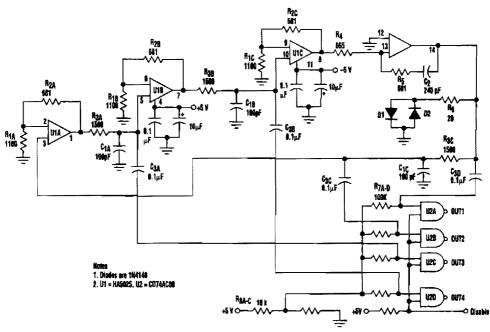

ELECTRONIC DESIGN

Flq. 62-5

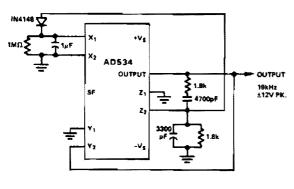By using a high-frequency quad current-feedback amplifier (the HA5025) as an RC oscillator, four quadrature sine waves can be generated. The HA5025's four separate amplifiers generate the sine waves, and the quad NAND gate, U2, is biased at its threshold, so it acts as a sine-wave to square-wave converter when the sine waves are ac coupled into its input.




STABILIZED WIEN-BRIDGE OSCILLATOR

Fig. 62-6

In this application, the AD534 is used as a variable-gain amplifier for the feedback signal from the output to the Y input, via the Wien bridge. The peak-rectifier and filter combination applies sufficient voltage to the X (denominator) input to maintain a stable oscillation-amplitude (with about 0.2% ripple). At startup, because X is small (divider mode), the gain is high, and the oscillation builds up rapidly. This is but one of several possible schemes, involving no external active elements. Its forte is simplicity, rather than high performance; nevertheless, the amplitude is not greatly affected by supply and temperature variations, about 0.003 dB per volt, and 0.005 dB per degree.

ANALOG DEVICES



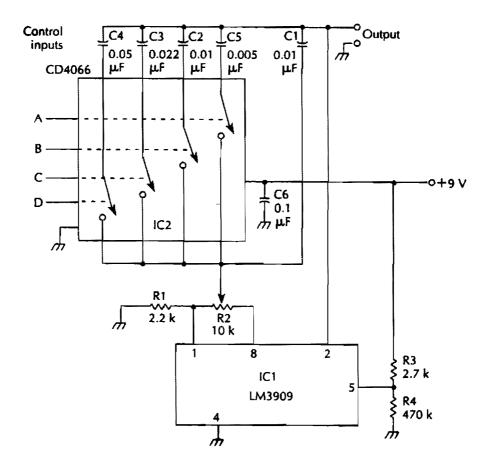


McGRAW-HILL

Flg. 62-7

IC1 LM3909 LED flasher/oscillator C5, C6 0.1-µF capacitor	
IC2 CD4066 quad bilateral switch R1 2.2-kΩ, ¼-W 5% resist	tor
C1, C2 $0.1-\mu$ F capacitor R2 $10-k\Omega$ potentiometer	
C3 $0.033 - \mu$ F capacitor R3 $2.7 - k\Omega$, 4-W 5% resist	tor
C4 0.047 - μ F capacitor R4 470- Ω , $\%$ -W 5% resist	or


50% DUTY-CYCLE 555 CIRCUIT

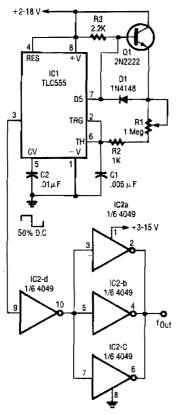


Using an external charge transistor and diode enables a 50% duty cycle and easy frequency control. When the 555's discharge transistor is cut off, the 2N2222 acts as an emitter follower. When the discharge transistor turns on, the 2N2222 turns off and C1 discharges through $(R_1 + R_2)$ at the same rate. The IN4148 provides temperature compensation.

ELECTRONICS NOW


Fig. 62-8

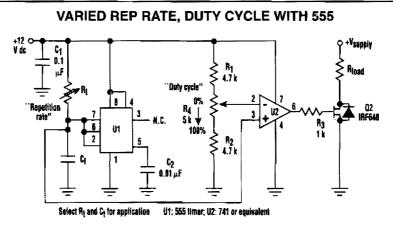

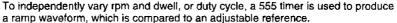

ELECTRONIC DESIGN

DDS DIGITAL VFO

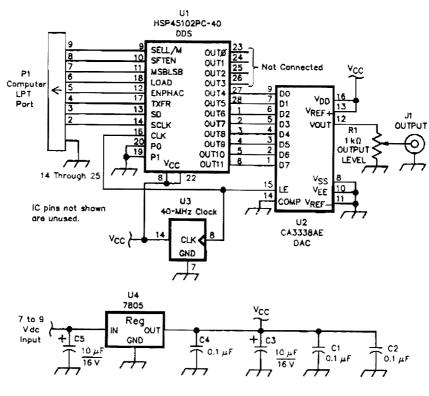

QST

Fig. 62-10

The DDS chip (U1) generates a data stream that is converted by D/A converter U2 into a sine wave. U1 is programmed via the input from P1, from the LPT port of an IBM PC. The system uses a 40-MHz TTL output clock module.


63

Oscillators (RF)

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Frequency Modulated Oscillator JFET Variable-Frequency Oscillator AM Oscillator for Wireless Microphones Reinartz Oscillator Remote-Oscillator High-Frequency VFO Beat-Frequency Oscillator for AM/SW Radios Butler Oscillator Circuit 455-kHz Oscillator Circuit 455-kHz Oscillator Modified Hartley Oscillator VLF LC Oscillator Grounded-Base Tuned Collector Oscillator for AM Broadcast Band HF VFO Circuit Darlington Transistor Oscillator FM HF Oscillator With No Varactor Tunable UHF Oscillator "Universal" VFO Oscillator Circuits Colpitts Oscillator Clapp Oscillator for 100 kHz Tuned Collector Oscillator Hartley Oscillator


FREQUENCY MODULATED OSCILLATOR

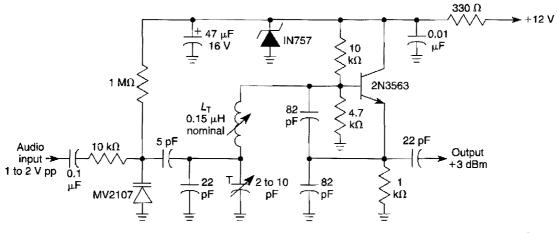

WILLIAM SHEETS

Fig. 63-1

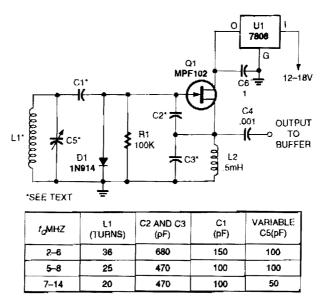This circuit can be used for FM wireless audio, microphone, and part-15 applications where a stable frequency modulated oscillator is needed. LT can be varied to cover 75 to 150 MHz, as needed.




JFET VARIABLE-FREQUENCY OSCILLATOR

POPULAR ELECTRONICS

This simple JFET-based variable-frequency oscillator can be used in receiver and transmitter circuits.


Fig. 63-2

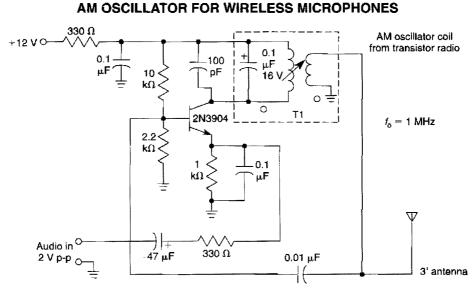

WILLIAM SHEETS

Fig. 63-3

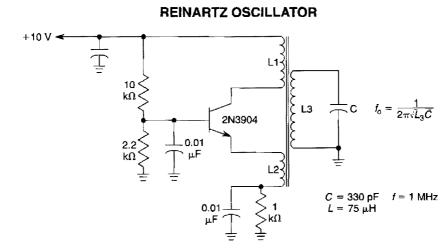This circuit will generate an AM-modulated signal in the AM broadcast band that can be picked up on a receiver. About 2 V of audio input will produce about 30% modulation of the oscillator signal. An old AM broadcast oscillator coil or other two-winding coil with about a 10:1 turn ratio and about 50 to 150 μ H inductance can be used for T1.



WILLIAM SHEETS

Fig. 63-4

This oscillator uses inductivity coupled emitter and collector windings to its main tank circuit. Take care so that L1 and L2 are not coupled to each other, otherwise this circuit is susceptible to parasitic oscillation at other frequencies. Typically, L1 has 5 to 10 times the number of turns that L2 has. L1, L2, L3 are wound on same coil form. This oscillator is more suited to lower frequencies, ≤ 10 MHz.


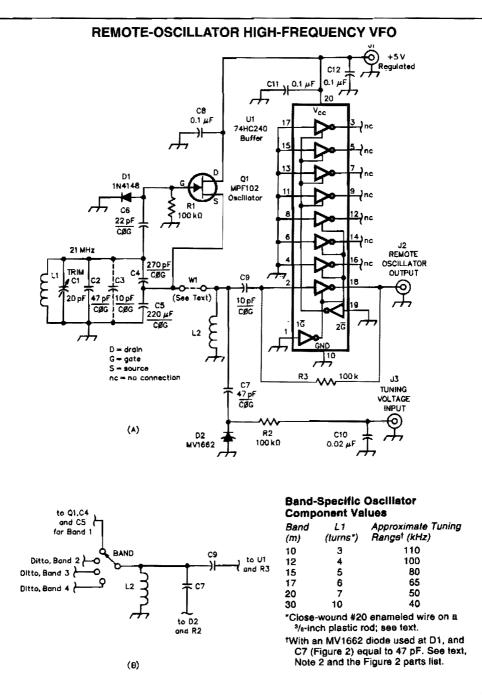


Fig. 63-5

A remote VFO is sometimes used to control a transmitter or receiver. The circuit shown uses an MPF102 FET and is controlled by a dc voltage at J3. The table shows values for L_1 for various bands from 30 to 10 meters. U1 serves as a buffer amplifier.


OST

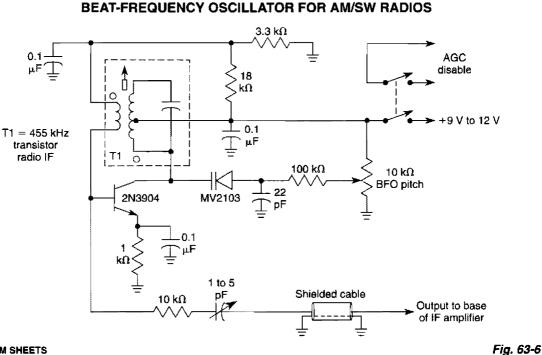

WILLIAM SHEETS

This BFO can be added to inexpensive AM/SW receivers to enable reception of CW signals. Output couples to base of last IF stage. T1 is any 455-kHz IF transformer. The BFO switch should be a DPDT type (as needed), and the radio AGC circuit will probably have to be disabled for CW reception.

BUTLER OSCILLATOR CIRCUIT

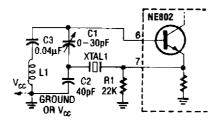


BADIO-ELECTRONICS

Fig. 63-7

This circuit uses an overtone crystal in a Butler oscillator. L1 is approximately 1300 μ H, and the crystal frequency should be from 20 to 50 MHz.


455-kHz OSCILLATOR

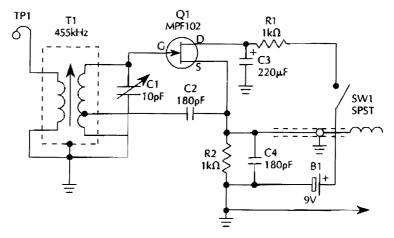

McGRAW-HILL

Fig. 63-8

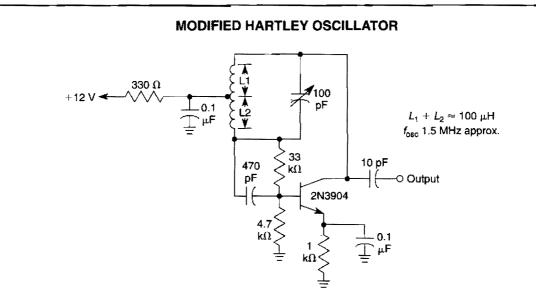The 455-kHz oscillator circuit uses a field-effect transistor (FET) for Q1. The output signal is taken from the source circuit of Q1. T1 is a 455-kHz IF transformer.




WILLIAM SHEETS

Fig. 63-9

This oscillator uses a tapped coil in the collector circuit, with the tap grounded for the signal. L1 and L2 are coupled inductively and typically have a 3:1 turn ratio, and generally are sections of one entire winding.

VLF LC OSCILLATOR

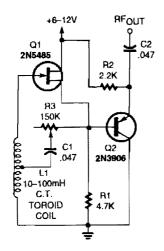


The VLF oscillator uses a large toroid coil as the frequency-determining component and a 2N5485 FET as the active device. R3 is used as a feedback control and also by running the circuit with slightly less feedback than needed for oscillation, can serve as a regenerative amplifier or detector.

POPULAR ELECTRONICS

Fig. 63-10

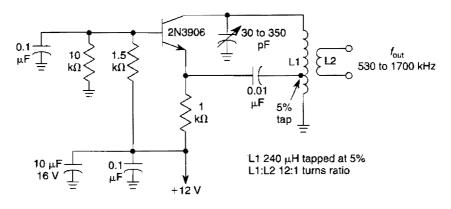
GROUNDED-BASE TUNED COLLECTOR OSCILLATOR FOR AM BROADCAST BAND



WILLIAM SHEETS

Fig. 63-11



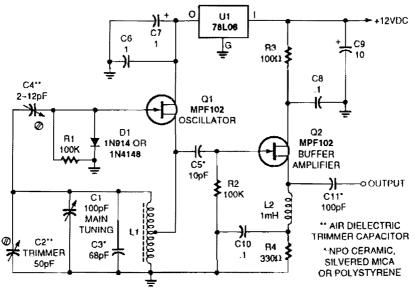


HF VFO CIRCUIT

POPULAR ELECTRONICS

Fig. 63-12

This typical HF VFO circuit has several stability-enhancing features, including well-chosen capacitor types. The frequency of the VFO is approximately $2\pi (C_1 + C_2 + C_3) L_1$. L1 should be an aircore type coil, rigidly mounted, with high (>200 value) value of Q.

DARLINGTON TRANSISTOR OSCILLATOR

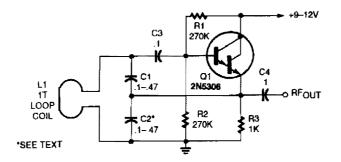


POPULAR ELECTRONICS

Fig. 63-13

This oscillator uses a very large capacitance-to-inductance ratio. L1 is a one-turn coil consisting of a loop of #12 wire 12" in diameter. This circuit is useful for metal detectors, etc., where a loop antenna is used.


FM HF OSCILLATOR WITH NO VARACTOR

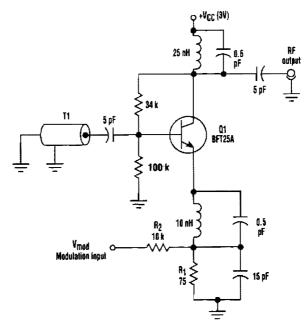

ELECTRONIC DESIGN

Instead of using a varactor to frequency-modulate a high-frequency oscillator, this circuit uses base-charging capacitance modulation. Consequently, the large voltage change required by a varactor, which can be a major problem in battery-powered systems with limited supply voltages, is eliminated. T1 is a ceramic coaxial quarter-wave resonator.

TUNABLE UHF OSCILLATOR

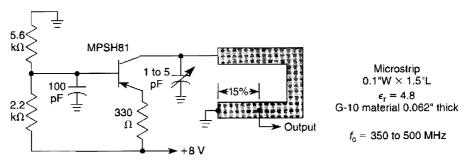


WILLIAM SHEETS

Fig. 63-15

This oscillator is typical for 350- to 500-MHz operation. The microstrip inductor is a PC board trace. The tap is typically 15% from the bottom end. The output power is 55 to 100 mW into 50 Ω , with the frequency stability typically 0.1% over 0 to 50°C.

"UNIVERSAL" VFO

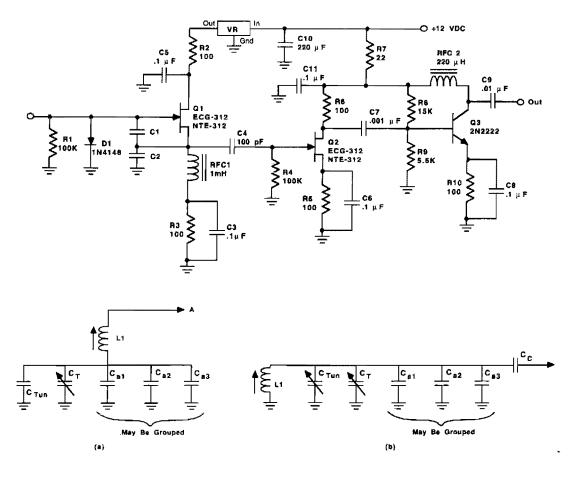


73 AMATEUR RADIO TODAY

Fig. 63-16

Figure 63-16A shows the basic circuit for the VFO, except for the tuning circuits (which are shown in Fig. 63-16B). Transistor Q1 is a junction field-effect transistor (JFET) oscillator stage. The device to use at Q1 includes MPF-102, 2N4416, and the replacement devices from the popular lines of "service" parts e.g., ECG and NTE).


Two different oscillator configurations can be accommodated by this design (i.e., both Clapp and Colpitts oscillators can be built). Both oscillators are the same from point A in Fig. 63-16C forward, and both depend on a capacitor voltage-divider feedback network. The Clapp oscillator (Fig. 63-16A) is series-tuned and the Colpitts oscillator is parallel-tuned (Fig. 63-16B).

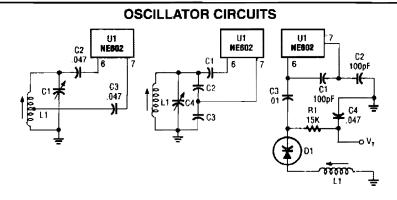The dc voltage supplied to the oscillator transistor (Q1) is voltage-regulated. The voltage regulator can be any 78Lxx series from 78LO5 to 78LO9.



RADIO CRAFT

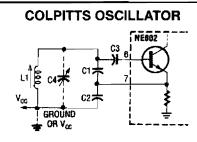These are methods of using an NE602 with a tunable VFO.




RADIO-ELECTRONICS

$$\begin{split} L_1 &\approx 7 \; \mu \text{H/}f(\text{in MHz}) \\ C_1 &\approx C_2 \approx C_3 \approx 2400 \; \text{pF/}f \end{split}$$

In this circuit, the oscillator is free-running.

CLAPP OSCILLATOR FOR 100 kHz

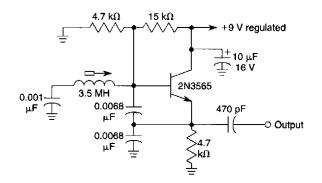


WILLIAM SHEETS

Flg. 63-19

This Colpitts oscillator is very stable and usable where good stability is needed, but crystal control is not desirable. It is capable of 1 part in 104 to 105 with good-quality components.

Flg. 63-18


Fig. 63-17

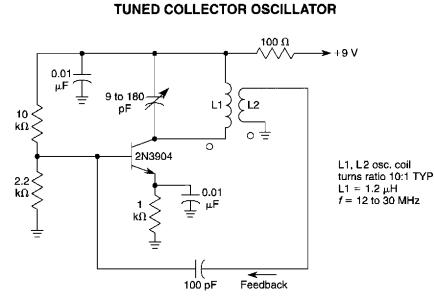

WILLIAM SHEETS

Fig. 63-20

HARTLEY OSCILLATOR

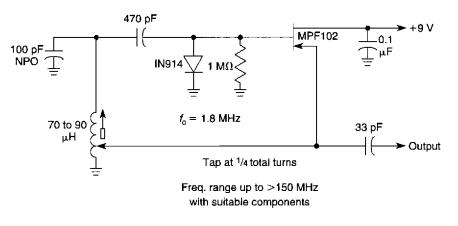

WILLIAM SHEETS

This circuit uses a tapped inductor in a Hartley oscillator circuit. The tap is generally at 25 to 35% total turns in most instances.

459

Fig. 63-21


64

Oscilloscope Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Scope Voltage Cursor Adapter Sampling-Rate Phase Lock Differential Amplifier for Scopes Delayed Video Trigger for Scopes

SCOPE VOLTAGE CURSOR ADAPTER

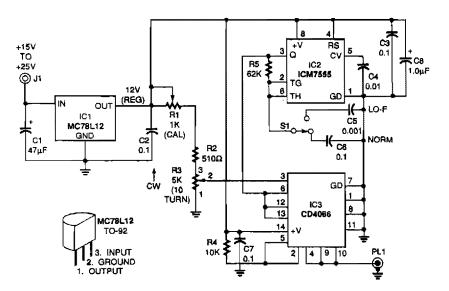

ELECTRONICS NOW

Fig. 64-1


The voltage cursor adapter superimposes horizontal cursor lines on the top and bottom of the waveform—a kind of electronic calipers—to permit direct readout of the voltage value. The cursor lines extend across the entire screen. The MC78L12 voltage regulator (IC1) supplies regulated 12-Vdc to the rest of the circuit. The ICM7555 timer (IC2) drives the CD4066B, a CMOS bilateral switch (IC3). This drive frequency can either be a normal frequency (NORM) of 100 Hz or a low-frequency (LO-F) of 10 kHz, depending on the setting of switch S1. Set S1 to LO-F for inputs below 500 Hz.

The dc reference voltage supplied to pin 3 of IC3 is set by R3, a 10-turn, $5000-\Omega$ precision potentiometer. The voltage can be read directly from a turns counter dial coupled directly to the potentiometer's wiper. The accuracy of this reading can be 1% or better. Trimmer potentiometer R1 permits the voltage to R3 to be calibrated to precisely 10 V.

The circuit is calibrated by setting the digital reading on the turns counter of R3 to the full clockwise position and adjusting R1 for a reading of 10 V at the wiper of R3 with a digital voltmeter.

Bilateral switch IC3 converts the dc reference to a square wave with exactly the same wiper amplitude. The square-wave output appears on common pins 4, 9, and 10 of IC3 and coaxial plug PL1.

SAMPLING-RATE PHASE LOCK

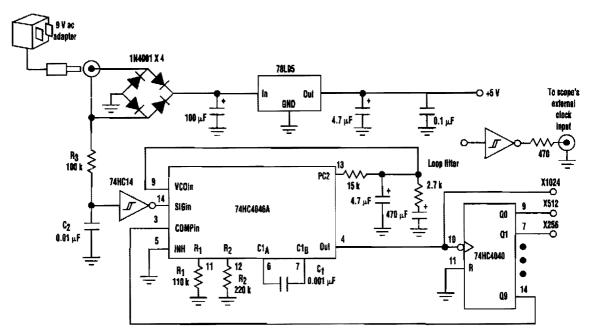

ELECTRONIC DESIGN

Fig. 64-2

Most digital scopes have record lengths that are power of 2 (e.g., 1024 points) and sampling rates constrained to a 1-2-5 sequence. This can lead to measurement errors on power-line waveforms because an integral number of line cycles can't be captured. Digital scopes that calculate measurements, such as the rms level, across the entire record will be in error.


One solution to this problem is to phase-lock the scope's sampling rate to the line frequency by exploiting the external clock input found on some digital scopes. Phase-locking the sampling to line frequency also tracks variations in the power-line frequency.

A 9- or 12-Vac wall transformer provides the circuit's power and the frequency reference. The negative output of the diode bridge refines the circuit ground. The 78L05 regulator provides the +5-V supply for the three ICs. R3 and C2 create a low-pass filter on the half-cycles from one of the floating transformer outputs. R3 also limits the current into the internal diode clamps of the inverter gate. The inverter output becomes the power-line frequency reference and is one input (SIG in to the phase comparator) of the Signetics 74HC4046A phase-locked loop (PLL). The 74HC4040 divides the PLL output frequency by 1024 and feeds the divided clock back to the other PLL phase-comparator input (COMP in). The phase-comparator output (PC2) is filtered and drives the PLL's control voltage (VCO in) so that the output frequency is 1024 times the reference frequency.

With the loop filter shown, the output frequency locks to the line frequency in about 10 s. The oscillator is locked to both 50- and 60-Hz inputs using a 74HC4046A and the values shown for resistors R1 and R2 and capacitor C1.

The output signal is buffered and sent to the scope's external clock input, which is typically a TTL-compatible input. A different tap from the 74HC4040 can be selected to control the number of cycles captured in one scope record.

DIFFERENTIAL AMPLIFIER FOR SCOPES

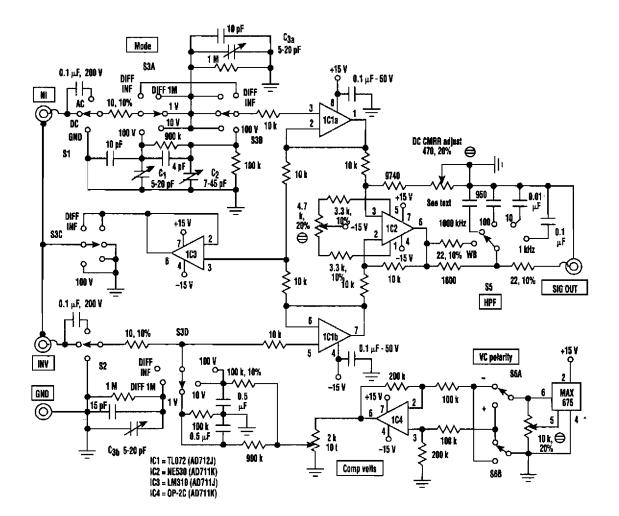


ELECTRONIC DESIGN

Fig. 64-3

Differential inputs and comparator modes can be added to any general-purpose oscilloscope using this circuit setup. Calibration doesn't change because the circuit operates in unity gain in most modes. Amplifier noise level is low enough not to degrade low-level signals, and its dynamic range can handle signals up to ± 12 V peak. Notice that all of the resistors are 1%, unless specified otherwise.

DELAYED VIDEO TRIGGER FOR SCOPES

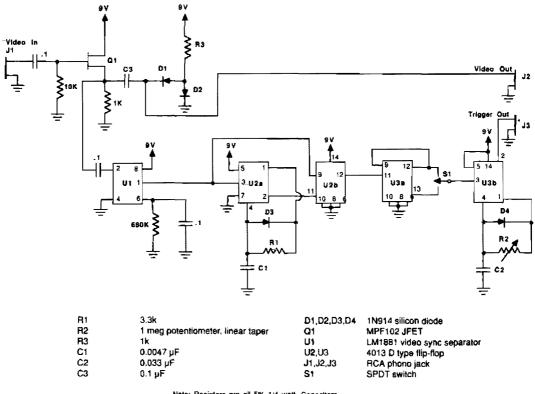

Note: Resistors are all 5% 1/4 wath. Capacitors are all polyester type.

73 AMATEUR RADIO TODAY

Fig. 64-4

This circuit will extract vertical sync from a video signal, produce a vertical sync pulse, and add an adjustable delay. This permits a delayed sweep effect to enable a scope to look at any particular horizontal line. It is useful for older scopes.

65

Photography-Related Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Charger for Photoflash Capacitor Slide Stepper Photo Super Strobe

CHARGER FOR PHOTOFLASH CAPACITOR

C1-0.2 μ F ±20%, 100 V C (Load Capacitor)-480 µF, 500 V D1, D2-MR814 (Fast-Recovery Rectifier) Q1-MP\$6520 (Selected) Q2-MPS6563 (Selected) Q3~MP\$6562 (Selected) Q4-MP3613 (Selected) VR-Neon Lamp (Selected 5 AG) R1--39K R2-100Ω R3-1.0K R4-120Ω R5-150Ω R6-2701 ±5% R7-7.50 ±5% RB-1.0 MΩ R9--2.0 MΩ Pot R10-390K ±5% Note: All resistors ±10%, 1/4 W, Unless Otherwise Specified

L1: Timing Inductor


Core:	Ferroxcube	266T125-3E2A		
Winding:	145 Turns,	No. 36 Wire		

L2: Drive-Oscillator Transformer

Core:	Ferroxcube No. 18/11PL00-3B7
Bobbin:	1811F2D
Air Gap:	0.005 in
Windings:	W1: 40 Turns, No. 28 Wire
-	W2: 20 Turns, No. 30 Wire
	W3: 140 Turns, No. 36 Wire

L3: Output Transformer


Core:	Ferroxcube No. 26/16P-L00-3B7
Bobbin:	Ferroxcube No. 26/16F2D
Windings:	N1: 11 Turns, No. 18 Wire
	N2: 1100 Turns, No. 38 Wire
Air Gap:	0.030 in

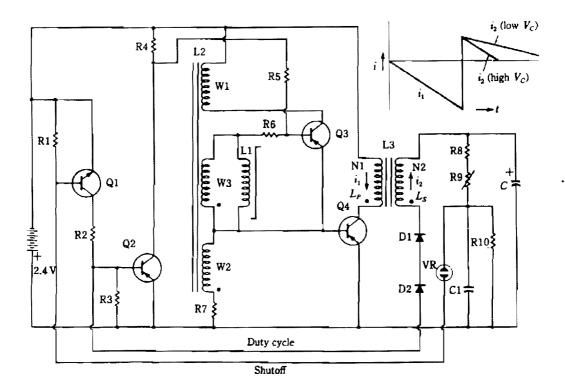


McGRAW-HILL

Fig. 65-1

This circuit charges photoflash capacitor C (480 µF, 500 V) for photoflash usage.

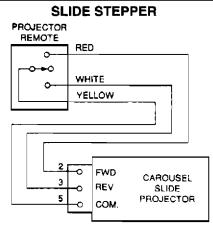

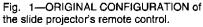

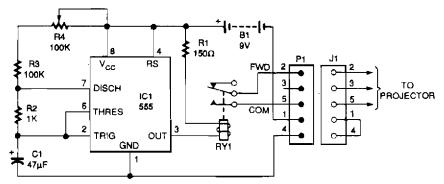


Fig. 2—SCHEMATIC DIAGRAM. The stepper circuit replaces the remote and will automatically advance the slides with a variable time delay.

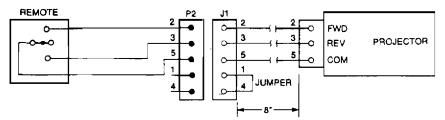



Fig. 3—CABLE MODIFICATION. This will allow the remote and the stepper circuit to be swapped easily.

ELECTRONICS NOW

Fig. 65-2

This stepper circuit replaces remote controls and will automatically advance slides in a projector. The time delay is variable with R4. The cable connections are for a Kodak carousel slide projector.

PHOTO SUPER STROBE

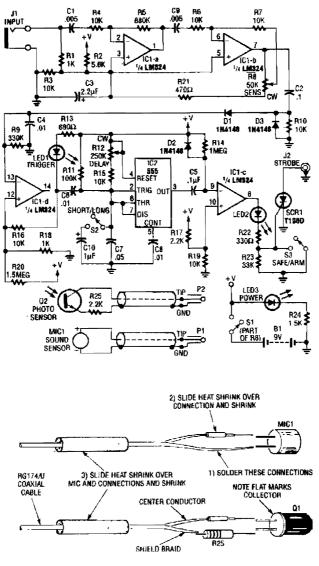

MAKE THE SENSOR ASSEMBLIES with heat-shrink tubing and small diameter coaxial cable such as RG-174/U. The space between the coaxial cable and the outer heat-shrink tubing is filled with a little silicone rubber.

ELECTRONICS NOW!

Fig. 65-3


A change in audio or light level on the sensor connected to J1 is amplified by IC1-a and IC1-b (rectified), and used to trigger IC2. R12 sets the delay between the trigger and the flash. IC1-c drives indicator LED2 and triggers SCR1, which sets off the strobe connected to J2. A photo cell or a microphone can be used as a sensor.

66

Piezo Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

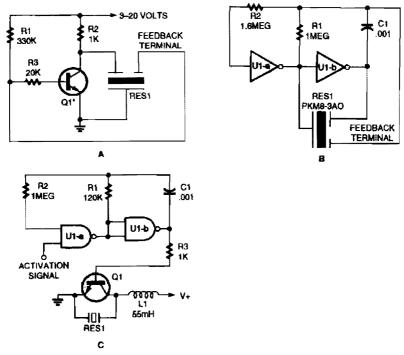Piezoelectric Driver Circuit Piezoelectric Buffer




PIEZOELECTRIC DRIVER CIRCUIT

POPULAR ELECTRONICS

Fig. 66-1

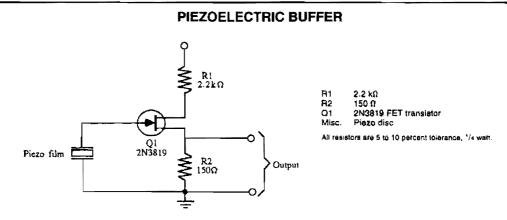Three-terminal piezoelectric elements are typically driven by transistor circuits (A), or logic gates (B). Two-terminal devices can be driven by two NAND gates. A booster coil is used to compensate for the sound-pressure attenuation caused by the case.



McGRAW-HILL

Fig. 66-2


This circuit will serve as a buffer for experiments with Kynar film, a piezoelectric material, or with piezo devices.

67

Power Line Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

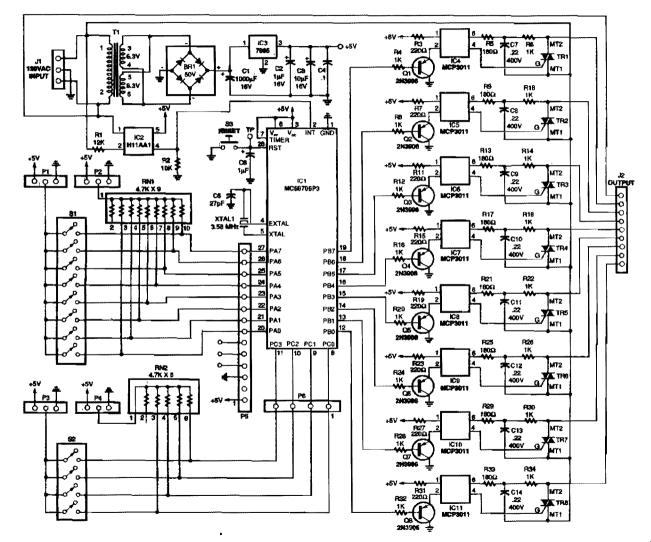ac Power Controller ac Power-Line Monitor Power-Line Modem for Computer Control Low-Voltage Power Controller ac POWER CONTROLLER




ac POWER CONTROLLER (Cont.)

This circuit is used to vary the power delivered to a 120-Vac load under software control. A 68705 micro controller can control eight discrete power triacs, each of which delivers power in 32 smoothly graduated steps, ranging from 0 to 97% of full power. The value delivered to one channel is independent of the value delivered to any other channel. Loads can include light displays, universal motors, heaters, and other appliances.

The power level is set by software, not a potentiometer. The software includes a basic set of routines for processing interrupts and setting the power level. The software also includes five test and demonstration routines for putting the circuit through its paces. Moreover, there's plenty of room to add your own routines to the 68705's built-in EPROM.

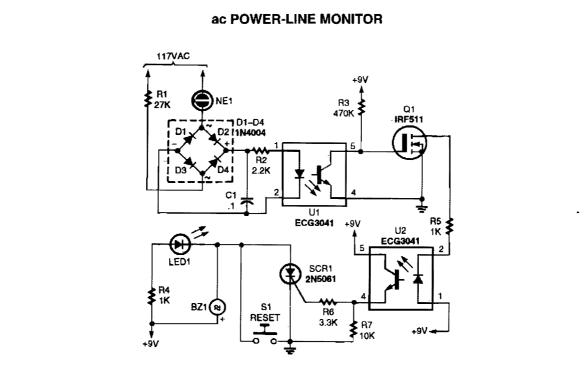The basic circuit is simple, yet versatile enough to accept inputs from on-board DIP switches; alternatively, the inputs can be driven from a microcomputer bus or parallel port, or a stand-alone device with TTL-compatible outputs. There are 12 input bits to set modes and specify values.



POPULAR ELECTRONICS

Fig. 67-2


When the power-line voltage source fails, Q1 turns on, activates optoisolator U2, and triggers SCR1. For small SCRs, U1 might directly trigger SCR1.

POWER-LINE MODEM FOR COMPUTER CONTROL 1+5V +5V **B11** R7 20 2200 iK VCC 1A1 1Y1 ~~ R12 ₩ R8 LED 1A2 16 22002 6 1K 1A3 *** 1Y2 **S1** P0 0 39 8 IC3 R13 P10 1A4 LED2 74LS240 22011 P0 1 38 143 14 2 11 P1.1 2A1 *** R9 37 3 B14 LED3 13 1K P1 2 P0.2 2A2 12 22052 36 4 15 P1 3 P0 3 243 1Y4 *** 5 35 9 1 **R10** 914 P04 2Y1 I FD4 ١K +5V 34 6 IC1 7 P0 5 1G 2Y2 **B1** 21.5 87C51 7 33 19 5 4.7K P1.6 P0.6 2Y3 2G SO2 *** 8 32 10 з P1 7 (SEE P0 7 2Y4 ٧_{SS} +5V NOTE) R2 D1 9 AESET P2 0 100 1N914 12 C3 22 +5V P2 * 10µF D2 23 P2 2 -dINT1 Vcc 1N914 c5 🛱 C1+ C6 3 14 24 ÷ R6 τо P2.3 **≭**10µF 10K IC2 MAX232 4 15 25 10µF P2 4 V. +5V 16 26 92.5 V. C7 ----**d** wR C2+ 17 **≤**10μF R3 C4 Z 27 C1 BD P2 6 -----10uF 4.7K D3 -5 30pF 28 C2 Vss 18 1N914 P2 7 X2 10 HXD LL OUT RS IN XTAL1 TRANSMIT 84 D4 10 TXD I IN RS OUT 100Ω 1N914 +)| _{C2} 19 ALE/P X1 COMMON 31 RECEIVE +5V 30pF PSEN EA/VP 40 +5V ۷сс R5 SO1 э VSS D5 1K 20 0 00 0 O. 0 0 0 000 Ò o 1N914 +5V IC4 o 0 0 0 0 00 00000 LM7805CT NOTE: X-10 INPUT FROM TW-523 JIQ VIN D6 1N914 GND 1. ZERO CROSS C8 2. COMMON 2 10µF 3. RECEIVE 4. TRANSMIT

ELECTRONICS NOW

Fig. 67-3

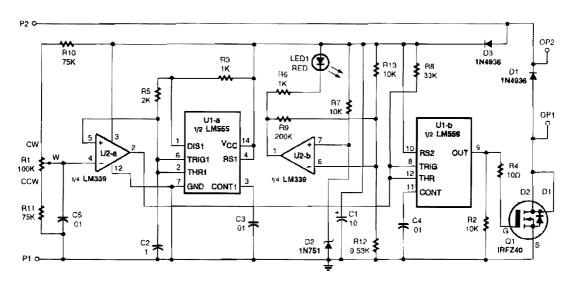This circuit uses an 87C57 microcontroller and a few peripherals to condition X-10 power-line carrier-code formats from a personal computer to use an X-10 power-line interface in a home-control system. Software details are available in the reference.



LOW-VOLTAGE POWER CONTROLLER

POPULAR ELECTRONICS

Fig. 67-4

The circuit has a duty-cycle generator that will produce an output varying from fully off to fully on and pulses of any duty cycle in between the two extremes.

This method of operation is called *PWM (pulse width modulation)*. The circuit can be fed from any dc supply source of between 10 to 15 V. Half of an LM556 dual oscillator/timer and U2-a (¼ of an LM339 quad comparator) combine to form a voltage-to-pulse-width converter. The first half of the dual oscillator/timer (U1-a) is configured as an astable oscillator, generating a continuously oscillating ramp voltage. Op amp U2-a compares the voltage at its noninverting input (pin 5)—which is connected to pins 2 and 6 of U1-a—to the voltage at its inverting input (pin 4). The op amp will produce a low output if R1's wiper voltage is higher than the instantaneous voltage that is present at pins 2 and 6 of U1-a. The output of U2-a at pin 2 will have an on/off ratio that is proportional to the voltage at R1's wiper.

The output of U2-a is fed to U1-b, which is used to buffer the signal. The low-impedance, pulsed output of U1-b at pin 9 is fed to the gate of MOSFET Q1, driving it on or off. The circuit also has a power-input detector, built around U2-band and LED1. If the input power is OK, LED1 will shut off.

Diode D1 is used to suppress the reverse voltage spikes that are generated by inductive loads during turn off; without that diode, the MOSFET might be destroyed. If the circuit will not be used to drive inductive loads (motors), D1 can be eliminated.

68


Power Supply Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Foldback Current Limiter **Current-Limiting Regulator Circuit** Switching Power Supply Transformerless dc Power Supply I +5-V at 1.5- to 3-A Supply, +6- to +15-V Input Transformerless dc Power Supply II Fast 3.3-V Regulator Power Supply for High-Power Autosound Amp **IC Regulator Protection** 3.3-V Switching Regulator NE602 Power-Supply Options Simple 9-V Power Supply Tracking Power Supply Power Efficient Voltage Regulator Low Drop-Out Regulator SCR Switching Supply for Color TV Receivers **Regulator** Circuit for Bilateral Source/Load Power System Fast 3.3-V Adjustable Regulator

Two-Terminal 100-mA Current Regulator **Two-Phase Rectifier** Low-Noise 5-V Supply Positive Regulator with 0- to 70-V Output Simple 12-V Power Supply 3.3 V from 5-V Logic Supplies 12-V Supply 4- to 70-V Regulator Switched Power-Control Circuits Multiple On-Card Regulator Adjuster Simple 9-V Power Supply +5-V at 1-A Supply with +3- to +5-V Input 5-Vdc Regulated Supply **Buffered Reference Supply** 5-V Logic Regulator with Electronic Shutdown 12-Vdc Regulated Supply Junked Transistor Regulators **Teleprinter Loop Supply** 5-A Constant-Voltage Supply


FOLDBACK CURRENT LIMITER

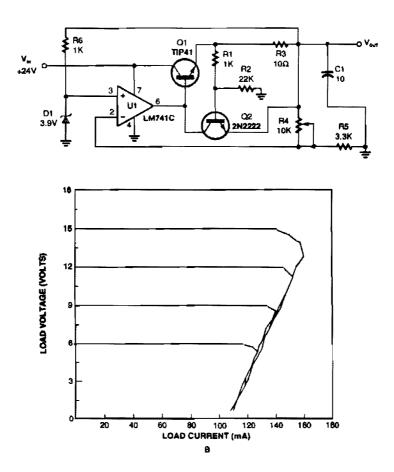

POPULAR ELECTRONICS

Flg. 68-1

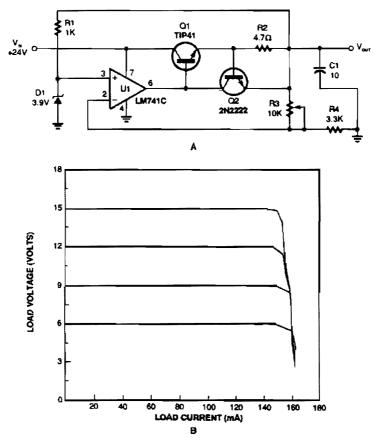This regulator uses the drop across R3 to sense current draw, turning on Q2, removing drive from Q1, and lowering the output voltage. Limiting occurs when Q2 has 0.65 V across the base-emitter junction. This circuit has foldback characteristics as seen from the figure.



CURRENT-LIMITING REGULATOR CIRCUIT

As shown in B, maximum load current is practically the same at all supply voltages with constant current limiting.

POPULAR ELECTRONICS


Fig. 68-2

This regulator uses the drop across R2 to turn on Q2, removing base drive from Q1 and reducing the current through R1. About 0.65 V must be dropped across R2 before limiting occurs. To set limit current,

$$R_{2} \approx \frac{0.65}{I_{\text{LIMIT (amps)}}}$$

$$Output \ voltage = V_{\text{OUT}} = (3.9) \ \frac{(R_{3} + R_{4})}{R_{4}}$$

SWITCHING POWER SUPPLY

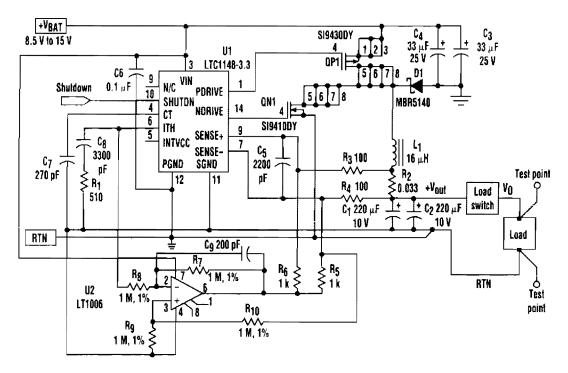

ELECTRONIC DESIGN

Fig. 68-3

In many switching-regulator applications for portable computers, the microprocessor is located some distance from the power supply. With the latest processors, total load currents range into several amperes. Thus, regulation at the load can become a problem.

The $I_{\rm TH}$ pin (pin 6) of the LTC1148 is approximately proportional to the load current. It scales nearly linearly from 0 V at no load to 2.0 V at current limit. U2, acting as a unity-gain differential amplifier, inverts the U1 pin 6 voltage (referenced to SENSE---, pin 7) and causes a current proportional to load current to flow in resistors R5 and R6. A small voltage drop appears across current-sense filter resistors R3 and R4. This makes the voltage measured by the internal feedback divider appear low. The duty factor is adjusted to bring this back to the correct voltage. As a result, the output is increased slightly as a function of load. Capacitor C9 rolls off the high-frequency gain of the correction amplifier.

$$R_{\rm comp} = \frac{(V_{\rm pin6} \times R_{\rm filt})}{V_{\rm corr}}$$

where: $R_{\text{comp}} = R_5 = R_6$ $R_{\text{filt}} = R_3$ and R_4 $V_{corr} = Measured \ drop.$

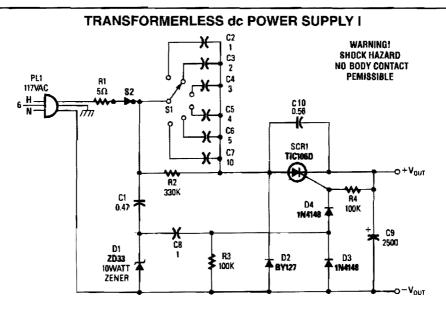



TABLE 1-OUTPUT CURRENT/VOLTAGE AT SPECIFIED LOADS

Capacitance (µF)	Load						
	100 Ohms		200 Ohms		1000 Ohms		
	V _{OUT} (V)	Current (mA)	V _{OUT} (V)	Current (mA)	V _{OUT} (V)	Current (mA)	
1	3.2	31	6.0	29	25	24	
2	6.4	61	11.2	54	41	41	
3	9.0	87	16.1	78	52	52	
4	11.8	113	20.7	100	61	61	
5	15.5	147	24.7	120	67 ·	67	
6	17.8	169	28.8	140	68	68	
7	18.5	176	31.9	155	69.4	68	
8	20.3	195	36.8	173	70	71	
9	22.8	220	41.0	193	70	71	
10	24.9	238	42.0	204	71	71	
11	27.1	259	44.9	219	- 1		
14	33.0	317	52.7	257			
20	43.5	422	65.8	322			


POPULAR ELECTRONICS

Fig. 68-4

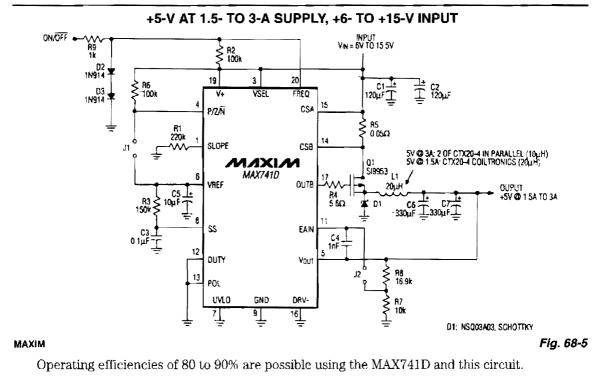An SCR fires on the positive half cycles of the ac line voltage. Switched capacitors are used to select the output voltage. These must all be ac-rated, nonpolarized types.




TRANSFORMERLESS dc POWER SUPPLY II

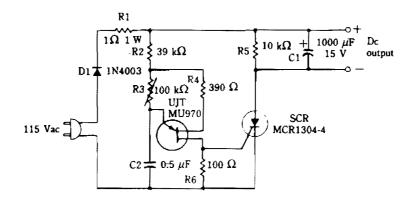

McGRAW-HILL

Flg. 68-6

Although it is simple, this supply can provide 10 to 15 V at 100 mA directly from the ac lines. This circuit has no isolation from the ac line; therefore, there is a shock hazard and it should only be used where no possibility of contacting external devices, circuits, or personnel exists.

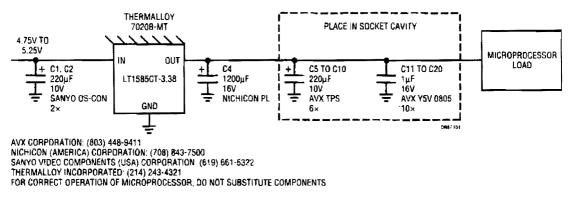

FAST 3.3-V REGULATOR

LINEAR TECHNOLOGY


Fig. 68-7

New high-performance microprocessors require a fresh look at power-supply transient response. The LT1585 linear regulator features 1% initial accuracy, excellent temperature drift and load regulation, and virtually perfect line regulation. Complementing superb dc characteristics, the LT1585 exhibits extremely fast response to transients. Transient response is affected by more than the regulator itself. Stray inductances in the layout and bypass capacitors, as well as capacitor ESR dominate the response during the first 400 ns of transient.

The figure shows a bypassing scheme developed to meet all the requirements for the Intel P44C-VR microprocessor. Input capacitors C1 and C2 function primarily to decouple load transients from the 5-V logic supply. The values used here are optimized for a typical 5-V desktop computer "silver box" power-supply input. C5 to C10 provide bulk capacitance at low ESR and ESL, and C11 to C20 keep the capacitance at low ESR and ESL low at high (>100 kHz) frequencies. C4 is a damper and it minimizes ringing during setting. Trace C is the load current step, which is essentially flat at 4 A with a 20-ns rise time.

Trace A is the output settling response at 20 mV per division. Cursor trace B marks -46 mV relative to the initial output voltage. At the onset of load current, the microprocessor socket voltage dips to -38 mV as a result of inductive effects in the board and capacitors, and the ESR of the capacitors. The inductive effects persist for approximately 400 ns. For the next 3 μ s, the output droops as the load current drains the bypass capacitors. The trend then reverses as the LT1585 catches up with the load demand, and the output settles after approximately 50 μ s. Running 4 A with a 1.7-V drop, the regulator dissipates 6.8 W.

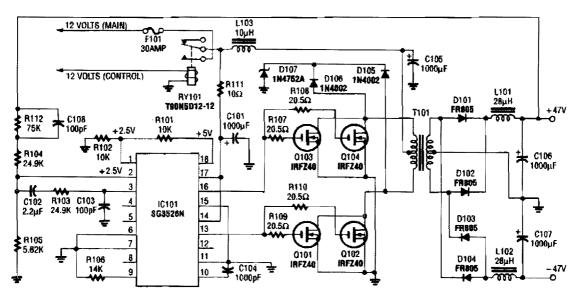
POWER SUPPLY FOR HIGH-POWER AUTOSOUND AMP



RADIO-ELECTRONICS

Fig. 68-8

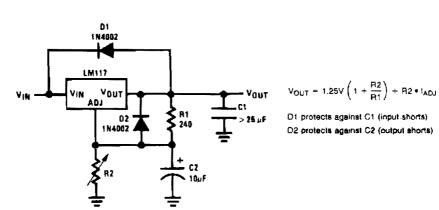A switching mode inverter is used with a pulse-width modulation voltage regulator (SG35260). Four IRF240 power MOSFETs are used as switches. The output is ± 47 V at about 5 A peak. Transformer T101 is a four-turn center tapped primary, and 16-turn center tapped secondary on a Ferrox cube ETD-34 core.




IC REGULATOR PROTECTION

NATIONAL SEMICONDUCTOR

This circuit protects an IC regulator against various fault conditions.


Fig. 68-9

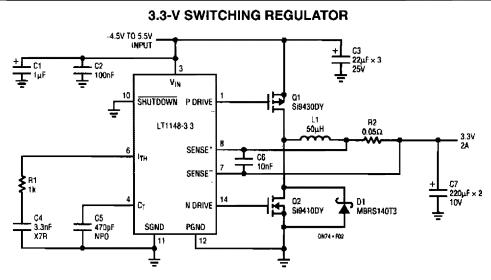

LINEAR TECHNOLOGY


Fig. 68-10

For the LT1129-3.3, dissipation amounts to a little under 1.5 W at full output current. The 5-lead surface-mount DD package handles this without the aid of a heatsink, provided that the device is mounted over at least 2500 mm² of ground or power-supply plane. Efficiency is around 62%; dissipation in linear regulators becomes prohibitive at higher current levels, where they are supplanted by high-efficiency switching regulators. The synchronous buck converter is implemented with an LTC1148-3.3 converter. The LTC1148 uses both Burst Mode[™] operation and continuous, constant off-time control to regulate the output voltage, and maintain high efficiency across a wide range of output loading conditions.

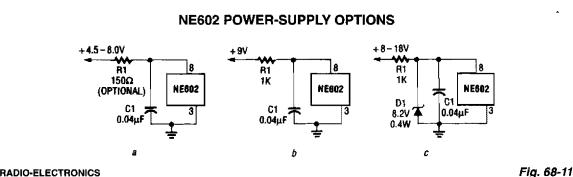

RADIO-ELECTRONICS


Here, Figs. 68-11A through 68-11C show an RC-filter used as both current limiter (R1) and integrator (C1), as well as for isolation. In Fig. 68-11A, +4.5 to 8.0 Vdc is the normal operating range of the NE602. In Fig. 68-11B, R1 drops voltage, and is used because a +9-V battery can go higher, and a +9-V wall supply can produce up to 11 V. In Fig. 68-11C, a +8- to 18-Vdc supply is regulated using a 8.2-V Zener for D1.

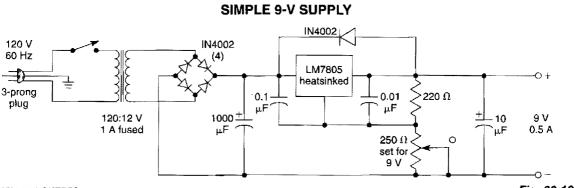

WILLIAM SHEETS

Fig. 68-12

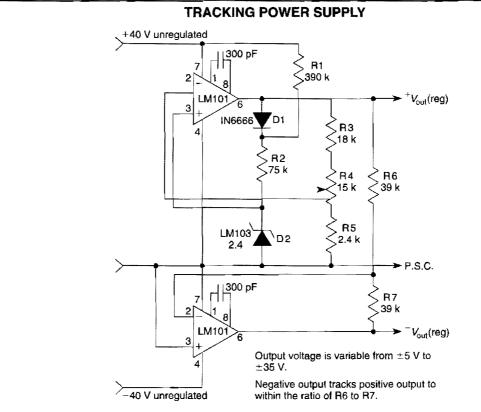
This circuit uses an LM7805 with a resistive voltage divider in the common leg of the regulator. The regulator can be "fooled" into producing an apparent higher output voltage in this manner. This supply is useful for running radios, tape recorders, or other 9-V devices.



NATIONAL SEMICONDUCTOR

Fig. 68-13

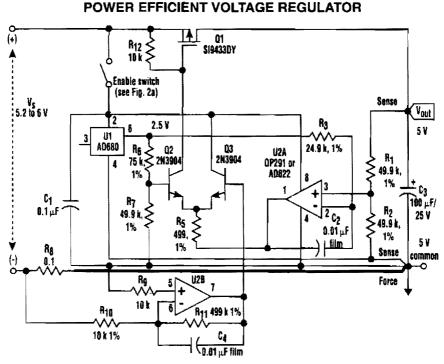
Two op amps are used in this basic op-amp regulator circuit. The outputs can be fed to current amplifier stages or emitter followers, if needed.



ELECTRONIC DESIGN

Fig. 68-14

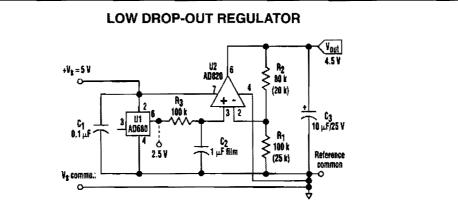Included in the many features of this power-efficient, voltage-regulator circuit is shutdown power control with a current output up to several hundred milliamperes (expandable to amperes, if desired). Current limiting can be preset to a fixed level for controlled dissipation in Q1 and the circuit requires no auxiliary voltage supply for the pass transistor.




ELECTRONIC DESIGN

Fig. 68-15

This low-dropout reference produces a 4.5-V output from a supply just a few hundred millivolts greater. With 1-mA dc loading, it maintains a stable 4.5-V output for inputs down to 4.7 V.

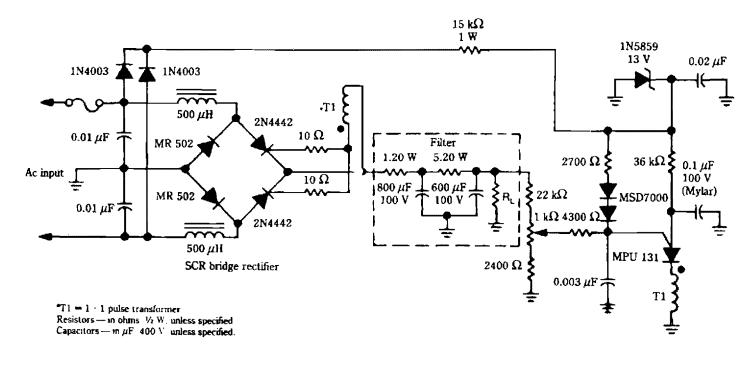SCR SWITCHING SUPPLY FOR COLOR TV RECEIVERS




McGRAW-HILL

Fig. 68-16

An output +80 V at up to 1.5 A is available from this supply. A minimum load of 200 mA is required because of the SCR holding current. Notice that no ac line isolation is provided and a shock hazard exists.

٠

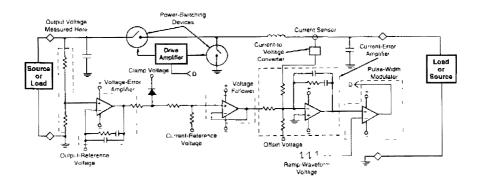REGULATOR CIRCUIT FOR BILATERAL SOURCE/LOAD POWER SYSTEM



NASA TECH BRIEFS


Fig. 68-17

The figure shows a circuit that regulates an output voltage, regardless of the direction of flow of output current. More specifically, it regulates the voltage at the left source or load, which can either supply power to or receive power from the right load or source, depending on the voltages and the direction of flow of current at the load/source terminals.

The overall system can be characterized as a voltage-controlled current source with bilateral current capability. The current flowing between the two source/loads, averaged over a power-switching cycle, is made to depend on the pulse-width modulation that governs the operation of the two power-switching devices, and this pulse-width modulation is, in turn, a function of amplified current-error and voltage-error signals. The voltage error is the difference between the actual output voltage and the output-reference voltage, which is the nominal output voltage at zero current. The pulse-width modulation is varied to increase or decrease the current, as needed, to limit the excursion of output voltage from the reference value.

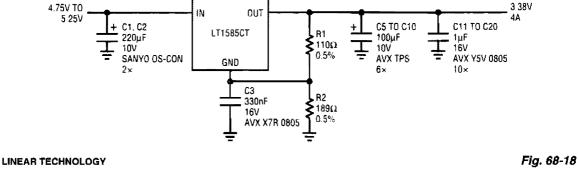An additional feature of this control circuit is that the maximum current in either direction can be limited by limiting the excursion of the output voltage from the zero-current value. Thus, external current-limiting circuitry is not necessary.






The adjustable version of the LT1585 makes it relatively easy to accommodate multiple microprocessor power-supply voltage specifications. To retain the tight tolerance of the LT1585 internal reference, a 0.5% resistor adjustment is recommended. R1 is sized to carry approximately 10 mA idling current ($\leq 124 \Omega$), and R2 is calculated from:

$$R_2 = \frac{V_{o} - V_{\text{ref}}}{\frac{V_{\text{ref}}}{R_1}} + 1_{\text{ADJ}}$$

where:

 $1_{\text{ADM}} = 60 \ \mu \text{ and } V_{\text{ref}} = 1.250 \ \text{V}.$

TWO-TERMINAL 100-mA CURRENT REGULATOR

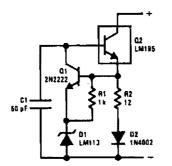


NATIONAL SEMICONDUCTOR

Fig. 68-19

The circuit has a low temperature coefficient and operates down to 3 V. The reverse base current of the LM195 biases the circuit.

A 2N2222 is used to control the voltage across current-sensing resistor, R2 and diode D1, and therefore the current through it. The voltage across the sense network is the $V_{\rm BE}$ of the 2N2222 plus 1.2 V from the LM113. In the sense network, R2 sets the current and D1 compensates for the $V_{\rm BE}$ of the transistor. Resistor R1 sets the current through the LM113 to 0.6 mA.

TWO-PHASE RECTIFIER

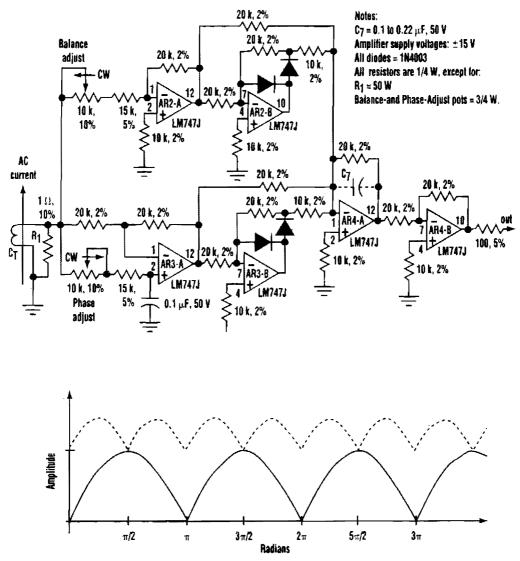


A single-phase AC signal can be converted to two phase with this circuit. It rectifies and sums the signal to a dc voltage level.

ELECTRONIC DESIGN

Fig. 68-20

The waveform generated by the two-phase rectifier illustrates that the ripple is less than half that of a conventional single-phase circuit's waveform. Also, the ripple frequency is double that of the conventional circuit. The circuit will follow amplitude changes in the ac input signal very rapidly, and it works equally well with current or voltage inputs.

LOW-NOISE 5-V SUPPLY

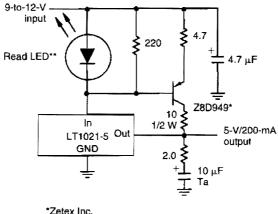

**Glows in current limit. Do not omit.

ELECTRONIC DESIGN


Fig. 68-21

Standard three-terminal regulator ICs can be noisy. The key is the noise over the 10-Hz to 10kHz band; measurements revealed a 40-dB improvement over standard three-terminal regulators.

The regulator is built around a 5-V buried-Zener reference. It's the buried Zener's inherently low noise that makes the finished supply so quiet. Measured over a 10-Hz to 10-kHz band, the 5-V output contains just 7 μ V rms of noise at full load. The 10-Hz to 10-kHz noise can be further reduced to 2.5 μ V rms by adding a 100- μ H, 1000- μ F output filter. The noise characteristics of the reference are tested and guaranteed to a maximum of 11 μ V over the band of interest.

An external boost transistor, the ZBD949, provides gain to meet a 200-mA output current requirement. Current limiting is achieved by ballasting the pass transistor and clamping the base drive. Although the oscillator only requires 200 mA, it's possible to extend the output current to at least 1 A.

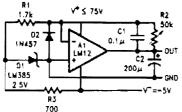POSITIVE REGULATOR WITH 0- TO 70-V OUTPUT




NATIONAL SEMICONDUCTOR

reference current drawn from its summing junction. With this arrangement, the output voltage is proportional to setting resistor R2. A negative supply is used to operate the op amp within its common-mode range, providing zero output with sink current and power a low-voltage bandgap reference, D1. The current drawn from this supply is under 150 mA, except when sinking a load current. The output load capacitor, C2, is part of the op-amp frequency compensation.

The op amp has one input at ground and a

SIMPLE 12-V POWER SUPPLY

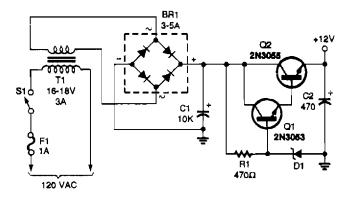


POPULAR ELECTRONICS

Flg. 68-23

This 12-V power supply is easy-to-build, and it produces a smooth output. D1 is a 14-V, ½-W Zener diode. The voltage can be varied by a few volts up or down to change the output voltage.


3.3 V FROM 5-V LOGIC SUPPLIES

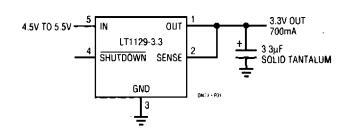

LINEAR TECHNOLOGY

Fig. 68-24

Microprocessor chip sets and logic families that operate from 3.3-V supplies are gaining acceptance in both desktop and portable computers. Computing rates, and in most cases, the energy consumed by these circuits, show a strong improvement over 5-V technology. The main power supply in most systems is still 5 V, necessitating a local 5-V to 3.3-V regulator. Linear regulators are viable solutions at lower ($I_o \leq 1$ A) currents, but they must have a low dropout voltage in order to maintain regulation with a worst-case input of only 4.5 V. The figure shows a circuit that converts a 4.5-V minimum input to 3.3 V with an output tolerance of only 3% (100 mV). The LT1129-3.3 can handle up to 700 mA in surface-mount configurations, including both 16- μ A shutdown and 50- μ A standby currents for system sleep modes. Unlike other linear regulators, the LT1129-3.3 combines both low-dropout and low-voltage operation. Small input and output capacitors facilitate compact, surface-mount designs.

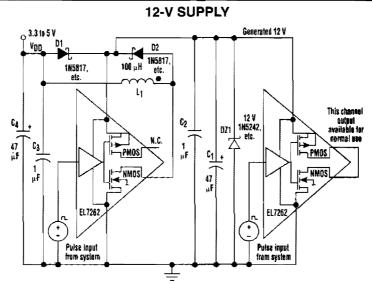

ELECTRONIC DESIGN


-Fig. 68-25

When driving a power MOSFET from a 5-V or 3.3-V system, a significant number of components usually are needed to generate an extra +12 V.

It's possible, however, to apply the second channel in a typical dual MOSFET driver to derive a +12-V power supply. By using a driver with the drains brought to separated pins, you can connect an inductor between the n-channel drain and the logic supply without connecting the p-channel device.

The driver operates as a standard flyback-style switched-mode circuit (see the figure). When the output n-channel device is on, current starts flowing in the inductor, which stores energy. When the n-channel device is turned off, current must continue flowing. Therefore, it flows through diode D2 to charge up C1 and C2. As the cycle repeats, the C1 and C2 voltage rises until the Zener diode prevents further voltage rise. This is needed to prevent the driver's derived supply from exceeding the part's maximum voltage rating.



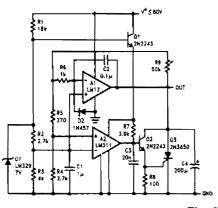


NATIONAL SEMICONDUCTOR

Fig. 68-26

This regulator operates from a single supply. If the op amp is not able to control an overvoltage condition, the SCR will crowbar the output.


SWITCHED POWER-CONTROL CIRCUITS

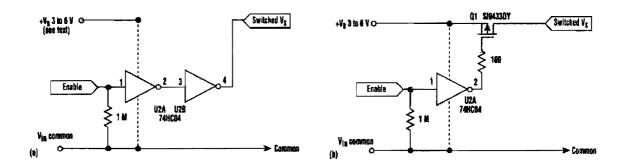

ELECTRONICS DESIGN

Fig. 68-27

Load currents of a few milliamperes to amperes can be turned on and off by these switched power-control circuits. The U2 CMOS inverter stage works as a simple power switch for load currents less than 5 mA (Fig. 68-27A), allowing easy reference shutdown. If appreciably higher switched output currents are called upon, an alternate CMOS inverter driving a low-threshold PMOS device can be used to switch currents of up to 1 A or more (Fig. 68-27B).

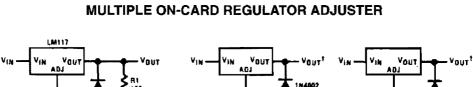

*All outputs within ± 100 mV †Minimum load -- 10 mA

120


R2

NATIONAL SEMICONDUCTOR

Fig. 68-28

This circuit allows one pot to control several on-card regulators for adjustment within ± 100 mV of each other.


SIMPLE 9-V POWER SUPPLY

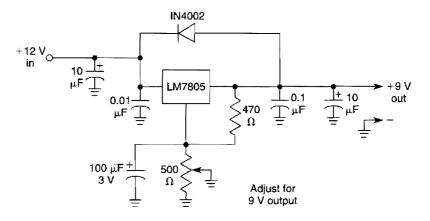

WILLIAM SHEETS

Fig. 68-29

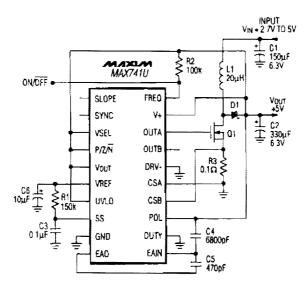This supply will provide 9-V transistor radios or cassettes from a 12-V auto electrical system.



+5-V AT 1-A SUPPLY WITH +3- TO +5-V INPUT

MAXIM

Fig. 68-30

A MAX741U switching-mode power-supply controller and a switching FET Q1 are used to provide +5 V at 1 A.

5-Vdc REGULATED SUPPLY


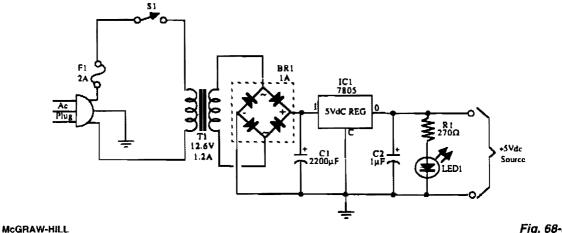


Fig. 68-31

BUFFERED REFERENCE SUPPLY

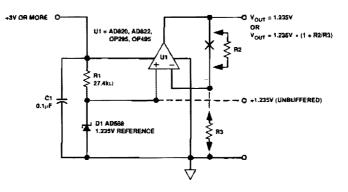


ANALOG DEVICES

Fig. 68-32

This buffered reference (for 1.23 V or more) uses a supply voltage of greater than 3 V.

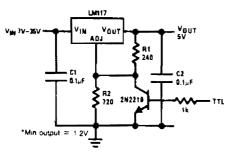
5-V LOGIC REGULATOR WITH ELECTRONIC SHUTDOWN




The circuit will shut down to 1.2 V under fault conditions.

NATIONAL SEMICONDUCTOR

Fig. 68-33

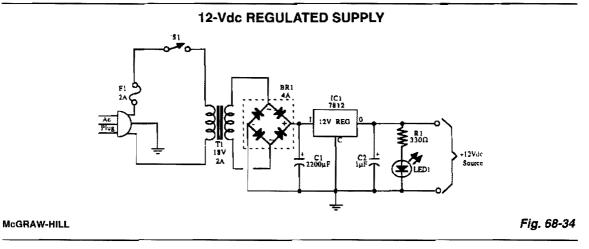


JUNKED TRANSISTOR REGULATORS

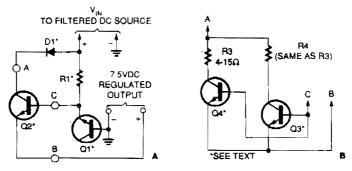

POPULAR ELECTRONICS

Fig. 68-35

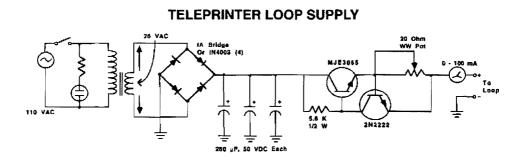Old transistors can make excellent regulators. Simply use one as a Zener to control the base current to another transistor (Fig. 68-35A). If the pass transistor cannot supply enough current, you can use two pass transistors in its place (Fig. 68-35B).



73 AMATEUR RADIO TODAY

Fig. 68-36

A circuit to power a teleprinter, using transistors as current-controlling devices. The power supply used provides a constant current in a loop, normally 60 mA or 20 mA, depending on the machine.

5-A CONSTANT-VOLTAGE SUPPLY ---- Hiah R4 0.27 Ω R3 0.27 Ω o-o Low s2 2W 2W Q1 MJ2955 Q2 2N6549 Q1 R5 2Ω 2W D1 1N4003 7805 Ön Out 2 in o GND Off Regulated 120 3 Ē dc voltage 000 BR1 Vac 17 o 2 C1 C2 0.01μF C3 0.01 µ.F + C4 100 μ.F **π**1000 μF R2 741 10 K 50 V 3 Output 50 V R1 n1-100Ω≹ level

ELECTRONICS NOW

Fig. 68-37


This constant-voltage supply has a variable output. It can supply more than 5 A, and has two switchable current limits.

69

Power Supply Circuits (High Voltage)

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

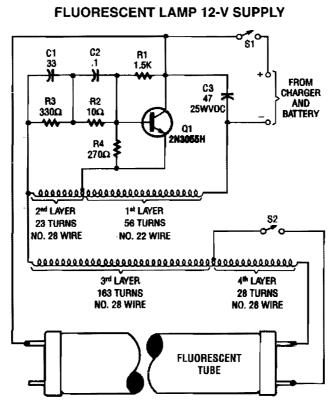
Fluorescent Lamp 12-V Supply High-Voltage Regulator Night-Vision Scope Power Supply High-Voltage Power-Supply Control Circuit -100-Vdc Supply ac-Operated He-Ne Power Supply HV Regulator with Foldback Current Limit Kirlian Device Supply High-Voltage Tripler 200-V Regulator Pulse-Width Modulated Laser Supply



POPULAR ELECTRONICS

Fig. 69-1

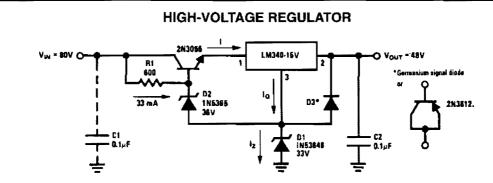This high-voltage power supply can operate fluorescent tubes from a 12-V source, even if the tube has a defective filament. It essentially is an oscillator that excites a home-made autotransformer. T1 is wound on a ferrite rod %" diameter by 1%" long, in layers. S2 is an optional lamp filament switch.




NATIONAL SEMICONDUCTOR

Fig. 69-2

This circuit produces 48 V from an 80-V input.

NIGHT-VISION SCOPE POWER SUPPLY

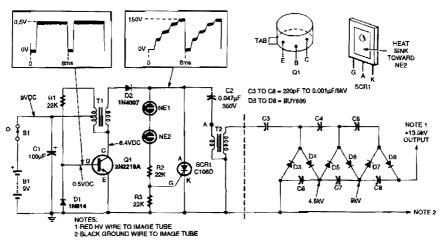


ELECTRONICS NOW

Fig. 69-3

This high-voltage power supply has an inverter around Q1 that supplies 150-V pulses to the converter of SCR1 and C2. The output of T2 is a 4.5-kV pulse that is multiplied by the voltage-tripler network (right) to produce 13.5 kV.

T1 is a 3-k Ω to 500- Ω CT transistor audio transformer, T2 is a flash tube trigger transformer with a 6-kV secondary.

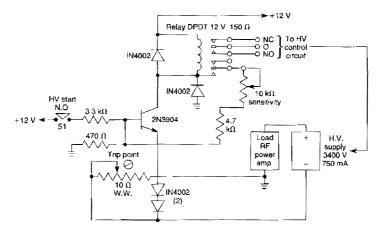
HIGH-VOLTAGE POWER-SUPPLY CONTROL CIRCUIT



WILLIAM SHEETS

Fig. 69-4

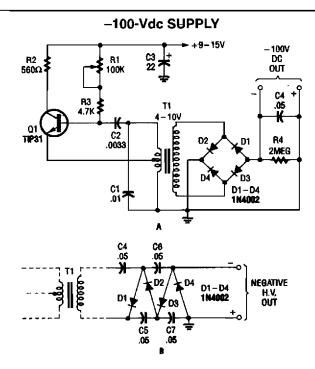
To start the HV supply, S1 is pressed, latching the relay. The 10-k Ω pot is set so that the relay just latches. When HV current becomes excessive (arc-over, etc.), an excessive voltage is developed across the 10- Ω WW pot, cutting off the 2N3904, causing the relay to unlatch. This circuit was used in a 1000-W linear RF power amplifier.



POPULAR ELECTRONICS


Fig. 69-5

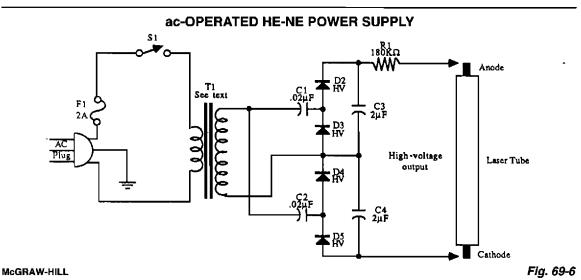The combination Hartley oscillator/step-up transformer shown in A can generate significant negative high-voltage—especially if the voltage output of the transformer is multiplied by the circuit in Fig. 69-5B. T1 is a small low-voltage filament transformer of around 4- to 10-Vac output, 120-V primary.



T1 is a 120-V to 1000-V step-up 60-Hz transformer. C1, C2, C3, C4 and D2 through D5 form a voltage quadrupler. The initial voltage is 4 to 5 kV, which drops when the laser tube fires.


HV REGULATOR WITH FOLDBACK CURRENT LIMIT

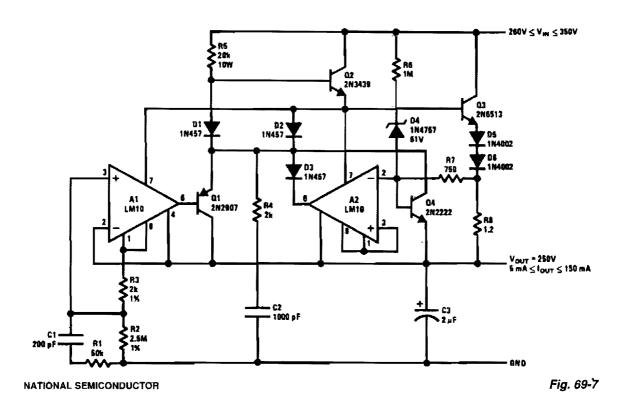

The output current is sensed across R8. This is delivered to the current-limit amplifier through R7, across which the foldback potential is developed by R6 with a threshold determined by D4. The values given limit the peak power below 20 W and shut off the pass transistors when the voltage across them exceeds 310 V. With unregulated input voltages above this value, start-up is initiated solely by the current through R5. Q4 is added to provide some control on current before A2 has time to react.

The circuit is stable with an output capacitor greater than about 2 μ F. Spurious oscillations in current limit are suppressed by C2 and R4, while a strange, latch-mode oscillation coming out of current limit is killed with C1 and R1.

KIRLIAN DEVICE SUPPLY

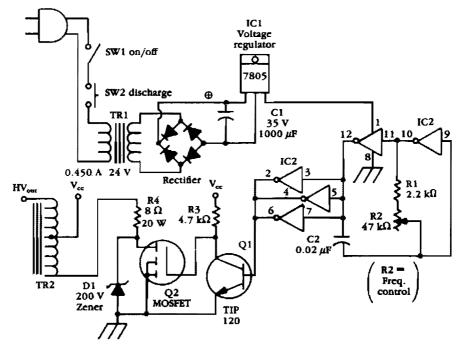


McGRAW-HILL

Fig. 69-8

This device is essentially a high-voltage variable-frequency ac supply. A CD4049 IC multivibrator circuit drives a Darlington connected transistor pair, which drives TR2, an HV transformer.

HIGH-VOLTAGE TRIPLER

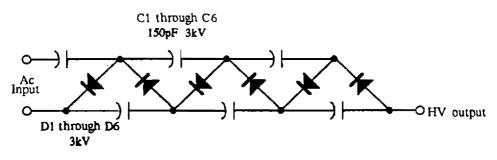


McGRAW-HILL

Flg. 69-9


This tripler is useful for low-current and high-voltage applications. The capacitors can be 0.001- μ F, 3- to 6-kV discs, and the diode's 3-kV units, or three each IN4007 in series.

200-V REGULATOR

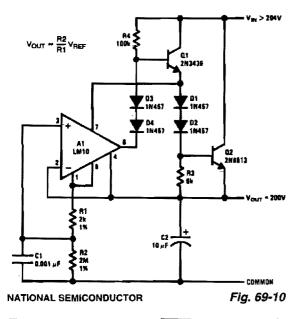

With high-voltage regulators, powering on the IC through the drive resistor for the pass transistors can become quite inefficient. This is avoided with the circuit shown. The supply current for the IC is derived from Q1. This allows R4 to be increased by an order of magnitude without affecting the dropout voltage.

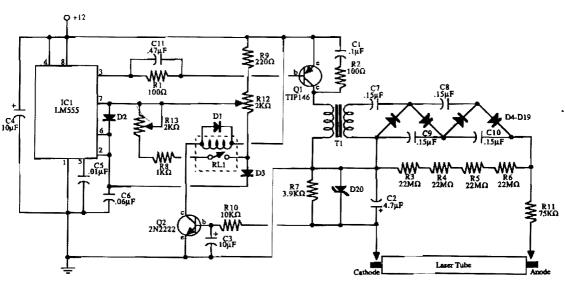Selection of the output transistors will depend on voltage requirements. For output voltages above 200 V, it might be more economical to cascade lower-voltage transistors.



PULSE-WIDTH MODULATED LASER SUPPLY

McGRAW-HILL

Fig. 69-11


IC1 initially provides drive for Q1 and HV transformer T1, and it rectifies D4 through D19. When the laser tube ignites, Q2 is triggered; this activates relay RL1, reducing the duty cycle. R13 controls the duty cycle of the pulses through the laser tube.

70

Power Supply Circuits (Multiple Output)

The sources of the following circuits are contained in the Sources section, which begins on page 706. The figure number in the box of each circuit correlates to the entry in the Sources section.

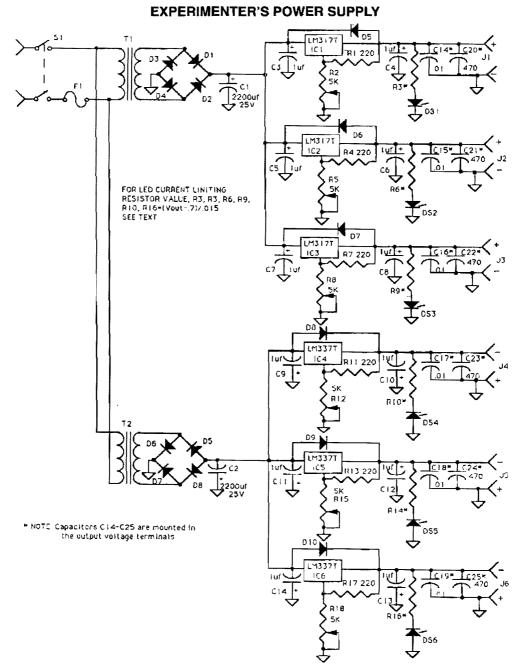Experimenter's Power Supply Quad Power Supply Activate Back-Up Power Supply CCFL Supply with Variable Contrast dc Power Source for Experiments Stable VFO Power Supply High-Efficiency Triple-Output Supply for Notebook Computers General-Purpose Power Supply for Automotive Projects ±15-V Power Supply





73 AMATEUR RADIO TODAY


Fig. 70-1

Passive linear IC regulators are used to make up a supply delivering +12, +9, +5, -5, -9, and -12 Vdc. T1 and T2 are 12-V, 3-A transformers.

QUAD POWER SUPPLY

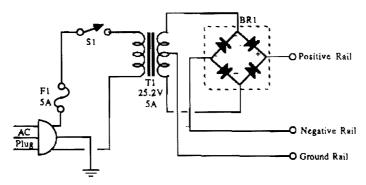

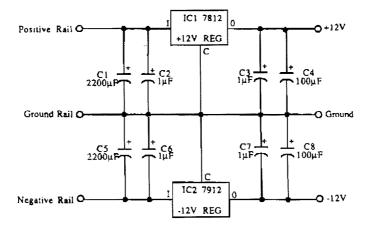


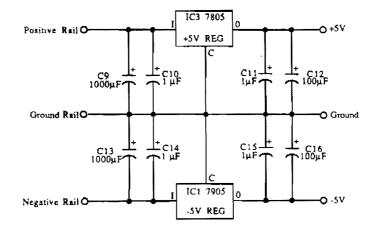

McGRAW-HILL

Fig. 70-2

ACTIVATE BACK-UP POWER SUPPLY

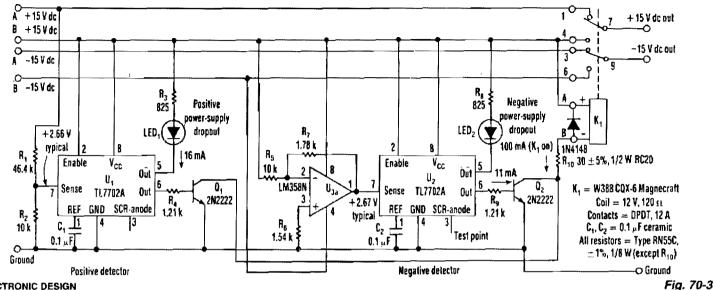

ELECTRONIC DESIGN


A circuit, which can be built around two TI TL7702 chips, monitors a 15-V power supply and activates a relay to turn on a back-up supply if the voltage drops below ± 14.1 V. With the back-up in place, the malfunctioning supply can be replaced without any down time. The TL7702 power-supply voltage supervisor chips are intended for use as reset controllers in microprocessor systems, but they work well in their modified form for this application.

One chip detects the positive supply (U1), and the other is used for the negative (U2). A pair of output-relay drive transistors, Q1 and Q2, form a wired OR circuit so that relay K1 is activated by the positive or negative voltage detector that switches U1 or U2 on.

The supervisor chips have a direct connection to the input comparator so that the trigger level is set by a resistor-divider network (R1 and R2) at the sense-input pin. These chips also have an internal, stable, reference-voltage source set at +2.53 V, typical. The positive-sensed voltage drops enough to activate the comparator, its output goes low, switches the internal gate, and triggers the siliconcontrolled rectifier (SCR). The output comparator then forces the two output transistors to switch, one high and one low. The output transistor (pin 5) turns on the light-emitting diode (LED), and the output transistor (pin 6) turns on the relay driver, Q1.

The negative detector is preceded by half of the dual op amp LM358N (U3a)—an inverting amplifier with a gain of -0.178. R5 connects to the -15 Vdc being sensed. The output of U3a is usually set at 2.67 V, higher than the +2.53-V reference voltage. Therefore, no switching occurs. If the -15-Vdc voltage decreases, U2 switches Q2 and activates K1 in the same manner as described for the U1-Q1 positive detector. R3, R4, and R8 through R10 serve as current-limiting resistors.


CCFL SUPPLY WITH VARIABLE CONTRAST

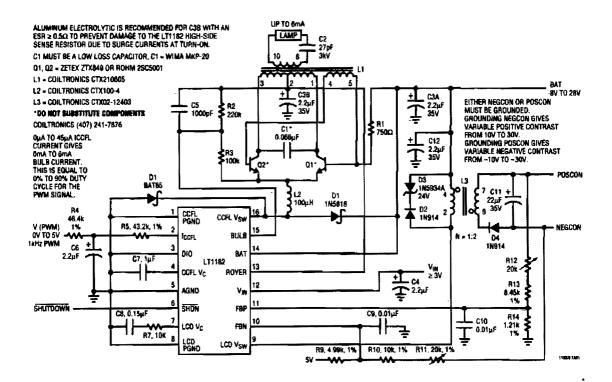

LINEAR TECHNOLOGY


Fig. 70-4

The figure is a complete floating CCFL circuit with variable negative/variable positive-contrast voltage capability, based on the LT1182. Lamp current is programmable from 0 mA to 6 mA using a 0- to 5-V 1-kHz PWM signal at 0% to 90% duty cycle. LCD contrast output voltage polarity is determined by which side of the transformer secondary (either POSCON or NEGCON) the output connector grounds. In either case, LCD contrast output voltage is variable from an absolute value of 10 V to 30 V. The input supply voltage range is 8 V to 28 V. The CCFL converter is optimized for photometric output per watt of input power. CCFL electrical efficiency up to 90% is possible and requires strict attention to detail. LCD contrast efficiency is 82% at full power.

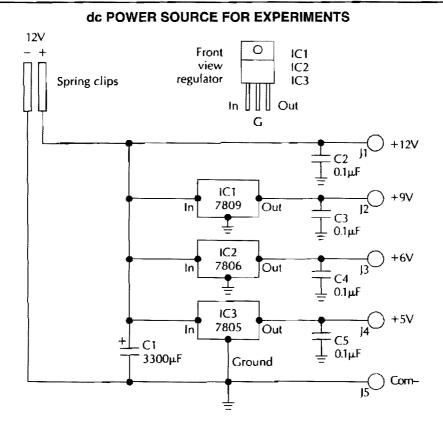

McGRAW-HILL

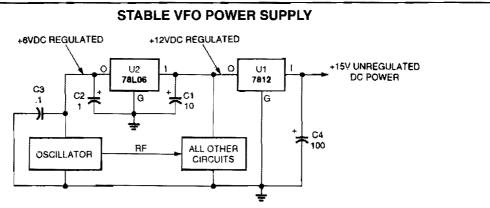This supply uses IC regulators to supply +5, +6, +9, and +12 volts regulated from a nominal 12-V supply.




POPULAR ELECTRONICS

Fig. 70-6

Fig. 70-5

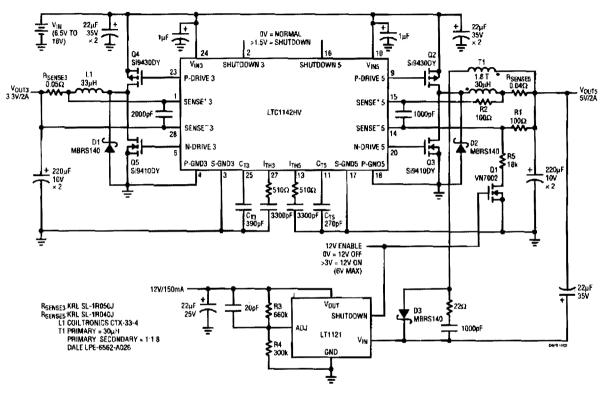A de power-distribution system for a stable oscillator should use a separate voltage regulator just for the oscillator circuit.




LINEAR TECHNOLOGY

Fig. 70-7

The circuit is configured to provide output voltages of 3.3 V, 5 V, and 12 V. The current capability of both the 3.3-V and 5-V outputs is 2 A (2.5 A peak). The logic controlled 12-V output can provide 150 mA (200 mA peak), which is ideal for flash memory applications. The operating efficiency shown in the figure exceeds 90% for both the 3.3-V and 5-V sections.

The 3.3-V section for the circuit in the figure is comprised of the main switch Q4, synchronous switch Q5, inductor L1, and current shunt R_{SENSE} . Current-sense resistor R_{SENSE} monitors the inductor current and is used to set the output current according to the formula $OUT = 100 \text{ mV}/R_{\text{SENSE}}$. Advantages of current control include excellent line and load transient rejection, inherent short-circuit protection, and controlled start-up currents. Peak inductor currents for L1 and T1 for the circuit in the figure are limited to 150 mV/ R_{SENSE} or 3.0 A and 3.75 A, respectively.

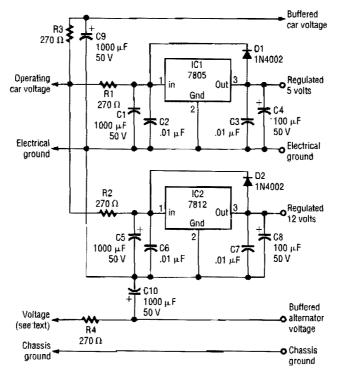
GENERAL-PURPOSE POWER SUPPLY FOR AUTOMOTIVE PROJECTS



ELECTRONICS NOW

Fig. 70-8

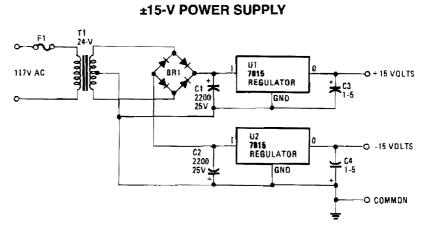This supply produces 12 V and 5 V for a variety of automotive projects. F4 is connected directly to the alternator field winding (usable only if your car has a separate regulator).



RADIO-ELECTRONICS

Fig. 70-9

A simple bridge rectifier feeds two IC regulators. This circuit should be useful for op-amp circuitry.


71

Power Supply Circuits (Variable Output)

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

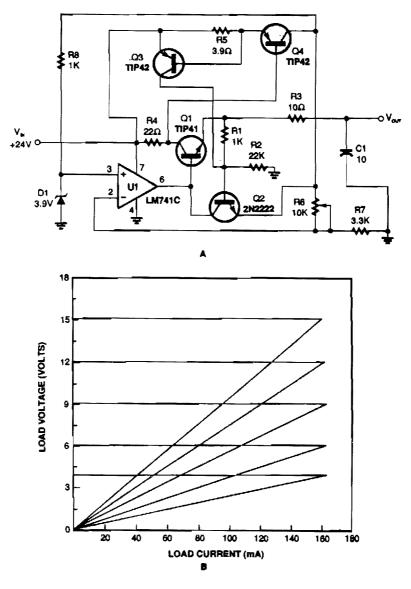Variable Voltage Regulator with Current Crowbar Limiting Adjustable 0- to 5-V Supply Transceiver Power Supply for Variable Lab Source Adjustable Power Supply Variable-Voltage Regulator with Wide-Range Current Limiting General-Purpose 0- to 30-V Power Supply Adjustable Positive Regulator Adjustable Bias Regulator






POPULAR ELECTRONICS

Fig. 71-1

The variable voltage regulator with current-crowbar limiting, shown in Fig. 71-1A, overcomes the disadvantages of constant and foldback limiting. As you can see in the graph (Fig. 71-1B), the current crowbar quickly shuts down the supplied power when a preset current is exceeded. It also has excellent load regulation over its operating range.

ADJUSTABLE 0- TO 5-V SUPPLY

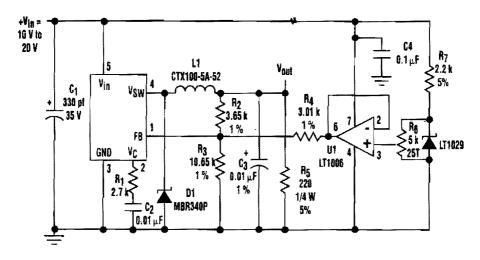

ELECTRONIC DESIGN

Fig. 71-2

Although linear-regulator ICs are frequently used in variable power-supply applications, they might not always be the best choice. At low output voltages, power losses in these regulators can cause headaches for designers. For example, if an output current of 1.25 A is required at 1.25 V from an input of 8 V. a regulator (such as the LT317) dissipates more than 10 W.


The figure depicts a dc-dc converter that functionally replaces a linear regulator in the just described application. The converter not only eliminates the problem of power loss, but it can be adjusted for output voltages (as low as 25 mV) while delivering an output current of 1.5 A.

The circuit uses a basic positive-buck topology with one exception. A control voltage is applied through R4 to the feedback summing node at pin 1 of the LT1076 regulator IC, making it possible to adjust the output from 0 V to approximately 6 V. This range encompasses the 3.3-V and 5-V logic supply voltages for portable and desktop equipment, as well as battery-pack combinations of one to four cells.

As R4 is driven from 0 to 5 V by the buffer (U1), more or less current is required from R2 to satisfy the loop's desire to hold the feedback summing point at 2.37 V. This forces the converter's output to swing over the range of 0 to 6 V.

The LT1076 is capable of 1.75-A guaranteed output current in this application, and 2 A is typical. If more current is required, the LT1074 can be substituted for the LT1076.

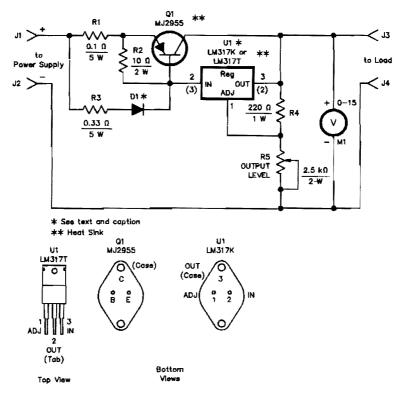TRANSCEIVER POWER SUPPLY FOR VARIABLE LAB SOURCE




QST

Fig. 71-3

A variable voltage regulator provides 1 to 11 Vdc for lab bench work, using an existing 13.8-V transceiver supply.

ADJUSTABLE POWER SUPPLY

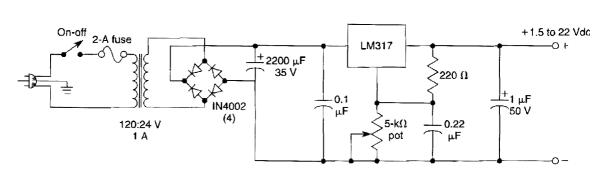


WILLIAM SHEETS

Fig. 71-4

Using an LM317, this supply delivers 1.25 to 22 Vdc for various purposes. The LM317 should be heatsinked. This supply will deliver 600-mA output current.

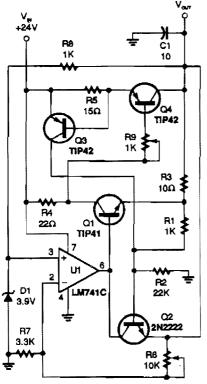VARIABLE-VOLTAGE REGULATOR WITH WIDE-RANGE CURRENT LIMITING




In this circuit, R9 acts as a control to set current limiting. If $R_9 = 0$, limiting occurs at 47 mA. Input is 24 V, output is

$$\frac{(R_6 + R_7)}{R_7} \times$$
(3.9)


depending on the setting of R6.



Fig. 71-5

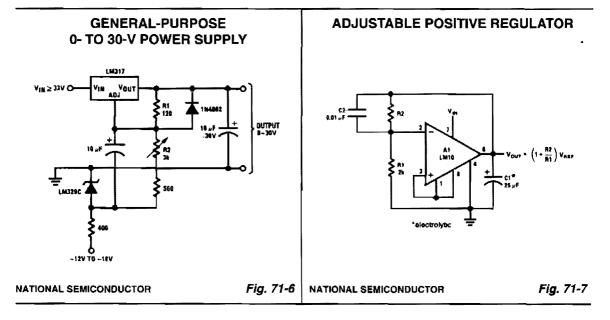

ADJUSTABLE BIAS REGULATOR

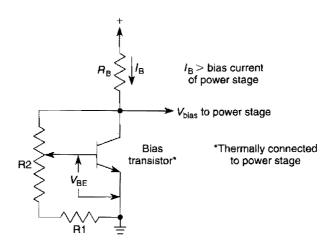

WILLIAM SHEETS

If the wiper of R2 is set at N% rotation, the bias voltage will be:

$$\begin{split} V_{\rm BIAS} &= V_{\rm BE} \left(\frac{R_1 + NR_2}{R_1 + R_2} \right) \\ V_{\rm BIAS \ MIN} &= V_{\rm BE} \qquad V_{\rm BIAS \ MAX} = \left(\frac{R_1}{R_1 + R_2} \right) \qquad V_{\rm BE} \end{split}$$

This method derives a bias voltage that tracks $V_{\rm BE}$ of this bias transistor. If the bias transistor is thermally linked to the power stage, tracking over a wide temperature range will result.

Fig. 71-8


72

Probe Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Current Probe Amplifier Simple Logic Probe with Alphanumeric Display Simple RF Probe 125-MHz Logic Probe pH Probe Amplifier 8-Digit 100-MHz Frequency Probe

CURRENT PROBE AMPLIFIER

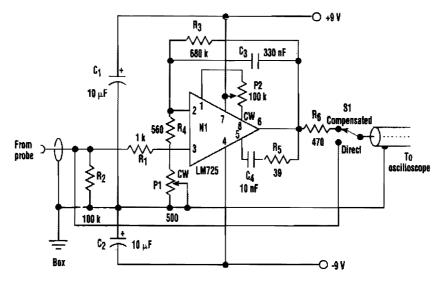

ELECTRONIC DESIGN

Fig. 72-1


A clamp-on current probe, such as the Tektronix P6021, is a useful means of displaying current waveforms on an oscilloscope. A less-expensive and simple alternative is shown in the figure.

The more sensitive range on the P6021 is 2 mA/mV, but it has a roll-off of 6-dB per octave below 450 Hz. The purpose of the compensator is to counteract the low-frequency attenuation, which is achieved by means of C3 and R4 + P1 in the feedback around op amp N1. It's important that the latter is a low-noise type, such as the LM725 shown in the figure. On top of that, it's necessary at some point to limit the increasing gain with decreasing frequency; otherwise, amplifier noise and drive will overcome the signal. The values shown for C_a and R_a give a lower limit of less than 1 Hz.

A test square wave of ± 1 mA is fed to the current probe so that P1 can be adjusted for minimum droop or overshoot in the output waveform. It's vital that the sliding core on the probe is fully closed. At high frequencies, the response begins to fall off at 100 kHz. Therefore, for most waveforms, switch S1 is moved to "direct," above a fundamental frequency of, for example, 10 kHz.

This circuit's current consumption is quite low, and it can be battery powered. If a mains power supply is built-in, it must be well screened to prevent hum problems.

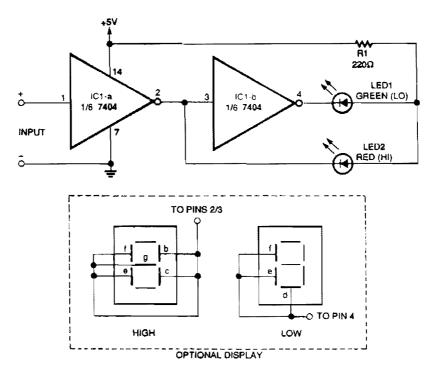
SIMPLE LOGIC PROBE WITH ALPHANUMERIC DISPLAY



ELECTRONICS NOW

Fig. 72-2

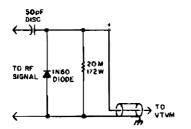A logic probe also includes BCD decoder module. The red LED lights to indicate a logic high, and the green LED lights to indicate a logic low. This probe circuit will light a green (low) or red (high), and if desired, an alphanumeric display can be obtained with two 7-segment LED displays.




SIMPLE RF PROBE

Your VTVM can measure peak voltage up to 200 MHz by using this probe. The maximum RF that can be measured is determined by the diode; with a 1N60, the probe is limited to 30 V. To increase the capacity, substitute a higher-voltage small-signal detector diode. House the circuit in a metal enclosure and use shielded wire.

73 AMATEUR RADIO TODAY

Fig. 72-3


125-MHz LOGIC PROBE

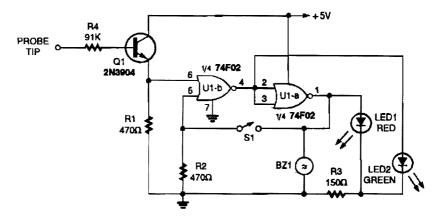

POPULAR ELECTRONICS

Fig. 72-4

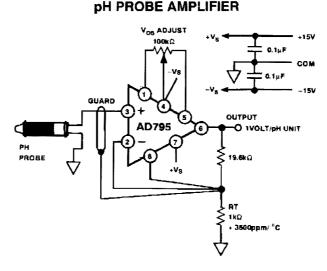This logic probe features either high-low (LED) indication or latching operation. When S1 is closed, the indication of a pulse is latched and the red LED1 stays on. Piezoelectric buzzer BZ1 is used as a beeper to sound that a logic high is preset.




ANALOG DEVICES

Fig. 72-5

The low-noise precision FET op-amp AD795 has around 1014- Ω common-mode impedance, low-offset voltage (250 μV_{max}) and L13 μV_C drift make this device ideal for low-voltage measurements from high-impedance sources.

8-DIGIT 100-MHz FREQUENCY PROBE

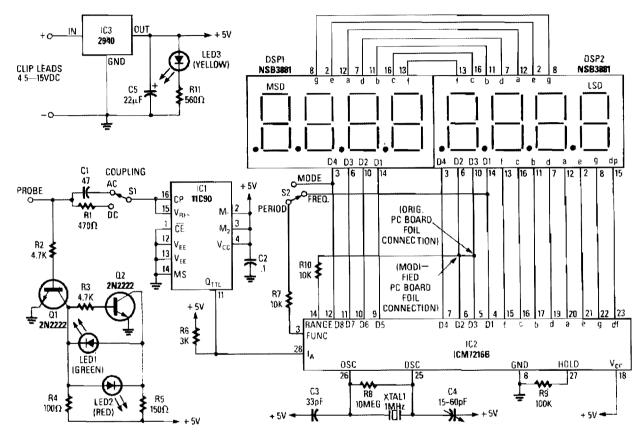

RADIO-ELECTRONICS

Fig. 72-6

Small enough to mount in a probe, this frequency counter circuit is good to 100 MHz. It operates from +5 to +15 Vdc. An 11C90 prescaler drives a 10-MHz counter chip (ICM7216B). Note the dotted line connecting R10 with pins 5 and 6 of IC2; that variable connection controls the decimal point and total count appearing on DSP1 and DSP2. The relative intensities and durations of ON/OFF time for LED1 (green) and LED2 (red) give a rough indication of logic level and duty cycle.


73

Protection Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

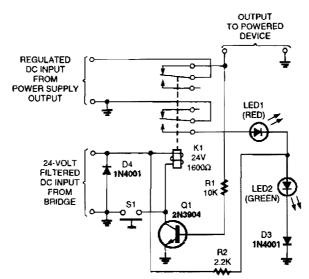Short-Circuit Protection Circuit Polarity Protector





POPULAR ELECTRONICS

When S1 is pressed, the coil of K1 is energized, closing its normally open contacts. If the regulated dc input is between 1 and 24 V, that voltage feeds the base of Q1 through R1, turning on the transistor, and latching the relay. When that occurs, LED2 glows indicating that all is okay.

If there is a short to ground at the circuit's output (i.e., in the device being powered), the voltage that feeds the base of Q1 goes to zero, turning off the transistor. Then, LED1 glows because K1 is de-energized to indicate the short circuit.

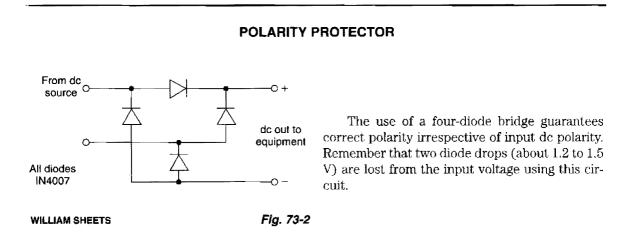


Fig. 73-1


74

Radar Detector Circuits

 $T_{\rm he}$ sources of the following circuits arc contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Display Board for Radar Gun 2.6-GHz Oscillator for Radar Speed Gun

DISPLAY BOARD FOR RADAR GUN

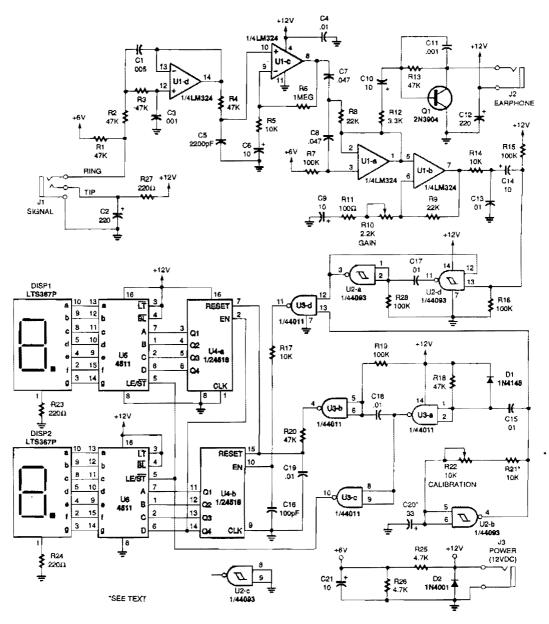


POPULAR ELECTRONICS

Fig. 74-1

This circuit takes signal (doppler) from a radar gun, amplifies and limits it, and feeds the frequency into a counter (U4) and display circuit (DISP1, DISP2, U5, U6). Counter calibration is set by clock circuit U2B. Calibration is obtained via R21 and R22. R21 can be changed if kilometers/hour readout is desired.

2.6-GHz OSCILLATOR FOR RADAR SPEED GUN

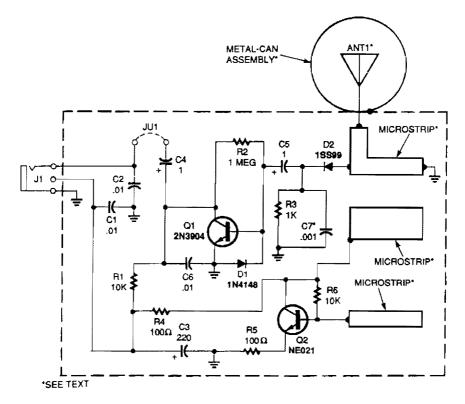

POPULAR ELECTRONICS

Fig. 74-2

This circuit consists of 2.6-GHz oscillator Q2, a coupling microstripline to ANT1, a 1.1" ¼-wave probe, detector D2, and audio amp Q1. The oscillator feeds power to the antenna, which radiates the signal. The reflected signal from a moving target mixes with the oscillator signal in D2. The resultant beat note (doppler shift) is amplified by Q1 and fed to jack J1, which is used to feed the circuit 12 Vdc.


75

Radiation Detector Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Geiger Counter Voltage Tripler for Radon Detector Ionization Chamber Flyback Power Supply for Radon Monitor Radon Monitor Amplifier and Head Ion Detector


GEIGER COUNTER

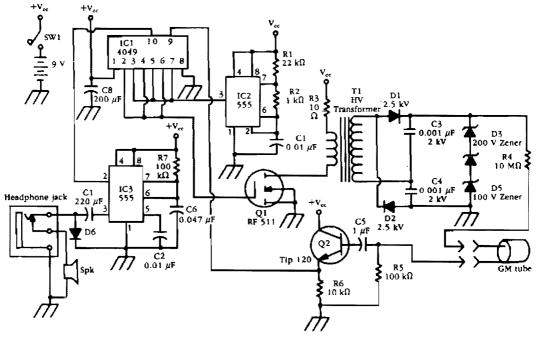

McGRAW-HILL


Fig. 75-1

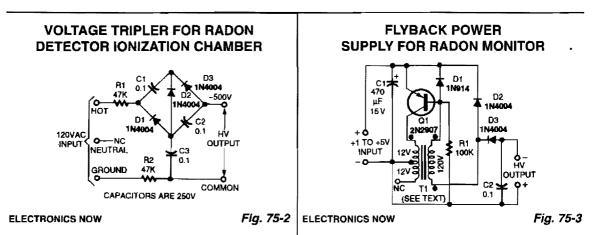An HV generator (IC1, IC2, Q1, T1, and associated components) power a G-M tube. A pulse from the GM tube is interfaced through Q2 and IC1 to pulse generator IC3, which drives a speaker.




The voltage tripler charges the ionization chamber capacitor. It is powered from the 120-Vac line. Warning: Shock hazard exists. This blocking-oscillator flyback circuit is an alternative for charging the ionization chamber capacitor.

RADON MONITOR AMPLIFIER AND HEAD

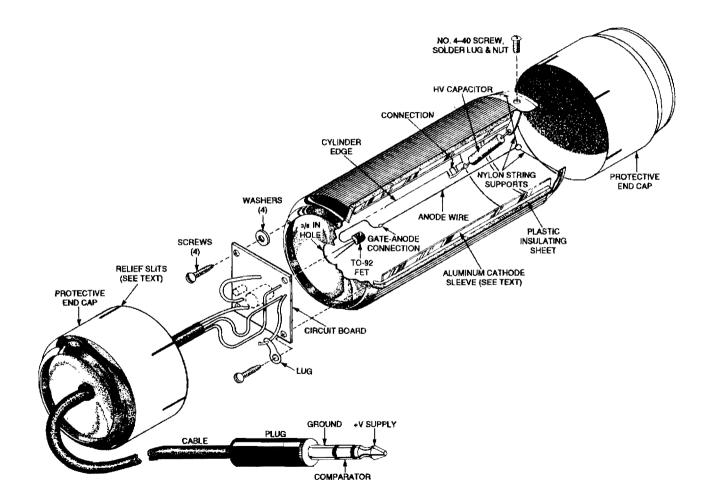

RADON MONITOR AMPLIFIER AND HEAD (Cont.)

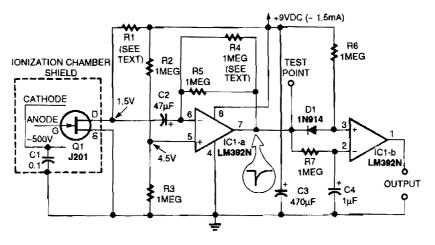


ELECTRONICS NOW

Fig. 75-4

A positively charged anode wire attracts electrons and a negatively charged cathode attracts positively charged ions. The recombination of electrons and ions causes a current that produces a voltage pulse. The cathode is maintained at -500 V by a charge on the $0.1-\mu$ F capacitor.

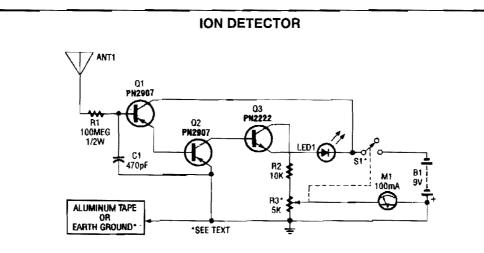A beverage can forms the chamber, an aluminum can forms the cathode, and half cans form protective end covers. The amplifier circuit board is shown to the left of center.



POPULAR ELECTRONICS

Fig. 75-5

ANT1 is a short whip antenna from a junked radio or other device. R_3 is adjusted to bring the meter on scale. This device should be grounded to operate properly. A length of aluminum or copper foil tape attached to the instrument case makes contact with the hand, and the body serves as a ground via hand contact with this tape.


76

Receiving Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

AM Radio

ac/dc Vacuum-Tube AM and Shortwave Receiver WWV Receiver Shortwave Receiver AM/FM Receiver Circuit 118- to 136-MHz Aircraft Receiver Dual-Inverter Line Receiver Dual-Inverter Line Receiver Toroidal-Core TRF Shortwave Receiver Nine-Band Shortwave Receiver One-Tube Regenerative SW Receiver One-Tube Regenerative AM Receiver Two-Band Radio Simple Crystal Radio Video Line Receiver Two-Chip AM Receiver Relay Interface to RC Receivers Basic Regenerative Receiver Simple Radio Receiver One-Tube AM Receiver Balanced Line Receiver Superhet Front End Receiver Preamp Regenerative Receiver for 6 to 17 MHz Two-Stage TRF Regenerative Receiver Economy Shortwave Receiver Variometer-Tuned Radio Old-Fashioned Crystal Radio WWV Receiver AM RADIO

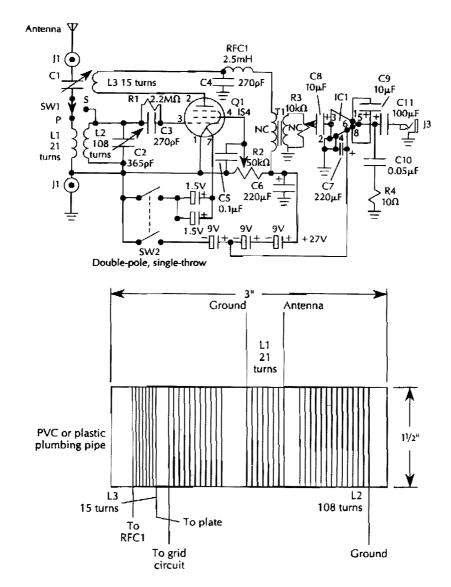


The primary winding of L1 has 21 turns of #24 or #26 enameled wire; L2 has 108 turns; and L3 has 15 turns of wire. All are wound on 1½-inch PVC pipe form.

McGRAW-HILL

Fig. 76-1

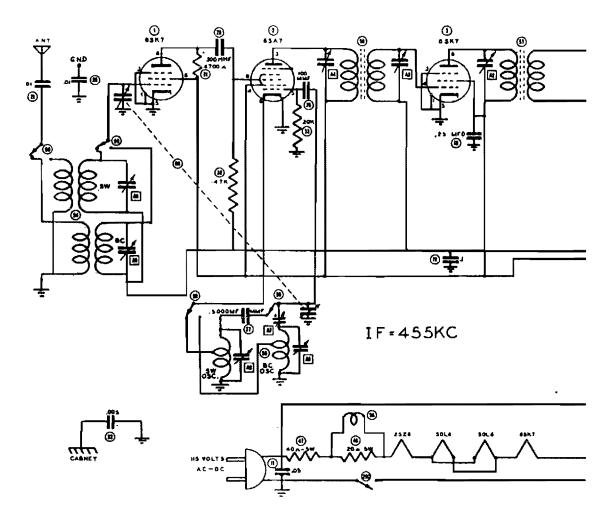A 1S4 regenerative detector feeds an LM386 audio IC (IC1). 1.5-V D cells and three 9-V batteries are used for a power supply.



ac/dc VACUUM-TUBE AM AND SHORTWAVE RECEIVER

POPULAR ELECTRONICS

This circuit was used in a World War II vintage AM/SW (6 to 18 MHz) receiver and shows typical circuits used in receivers at that time.



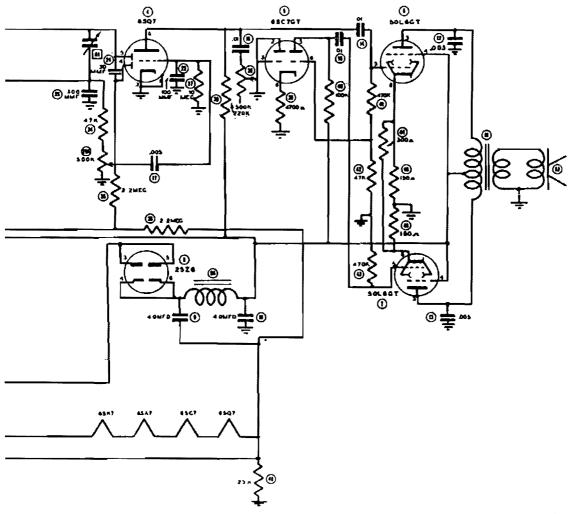



Fig. 76-2

WWV RECEIVER

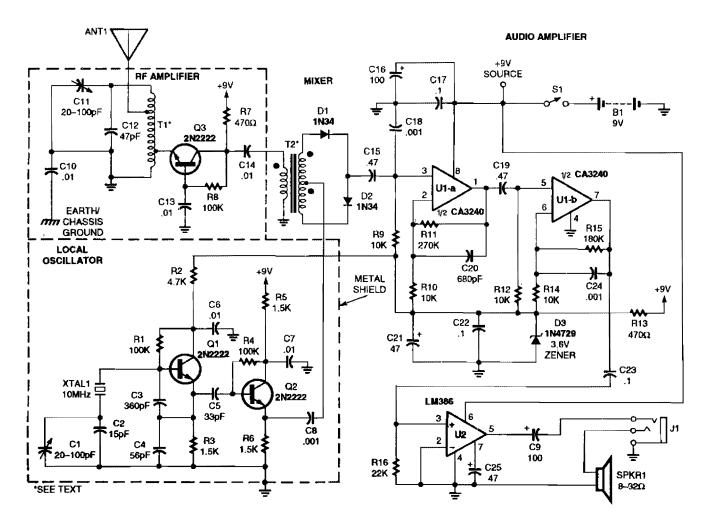

538

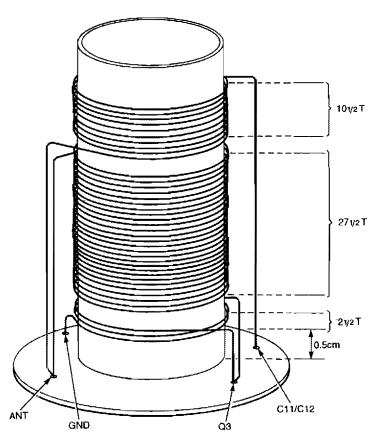

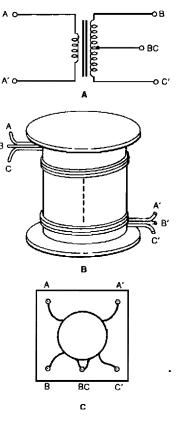


Transformer T1 is a home-made unit comprised of 40 closely wound turns of #26 AWG enameled wire on a $\frac{3}{100}$ turns form, with taps at 2 $\frac{3}{100}$ and 10 $\frac{3}{100}$ turns from each end; after each tap, the winding continues in the same direction.

Construction details for T2 (the mixer transformer) are shown here. The diagram in A is a schematic representation of the unit once completed; B illustrates how the three lengths of wire are wound as a set on the bobbin; and C shows how the bobbin is connected to the pinned base.

RF amplifier Q3 feeds diode mixer D1–D2 and Q1–Q2 provide 10-MHz L.O. injection to D1 through T1 and T2. U1A, U1B and U2 are audio amplifiers. Details of T1 and T2 are shown.

SHORTWAVE RECEIVER

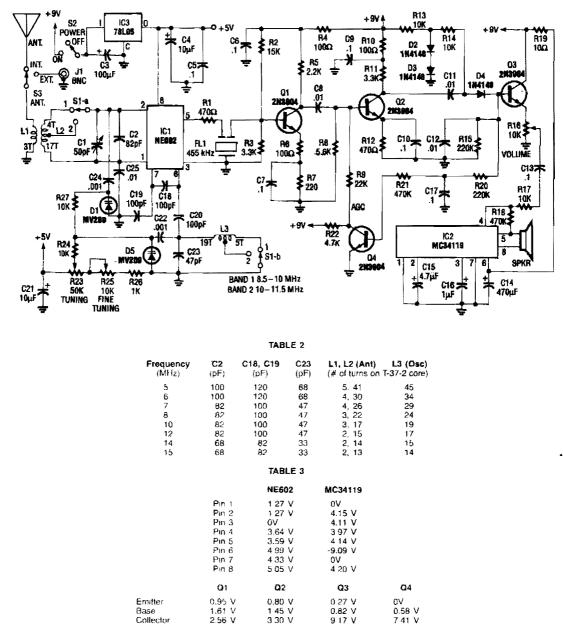


RADIO-ELECTRONICS

Fig. 76-4

This receiver covers 8.5 to 11.5 MHz in two bands and has a sensitivity of under 1 μ V. An NE602 mixer feeds a 455-kHz IF amplifier (Q1 and Q2), detector D4, and audio amplifier IC2. Q4 serves as an AGC amplifier coil data is given in the table. The LO is varactor tuned.

AM/FM RECEIVER CIRCUIT

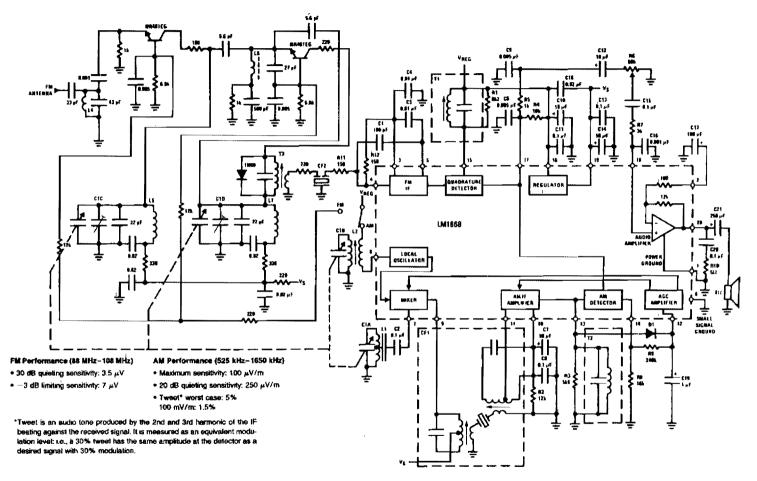


NATIONAL SEMICONDUCTOR

Fig. 76-5

This circuit shows the LM1868 as a complete AM radio and FM IF section. An external FM front end is used for the 88- to 108-MHz band. Audio output is 0.5 W and either 9-V battery or line operated supply can be used.


118- TO 136-MHz AIRCRAFT RECEIVER

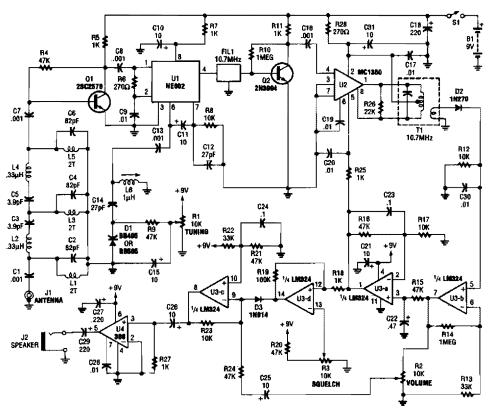

RADIO CRAFT

Fig. 76-6

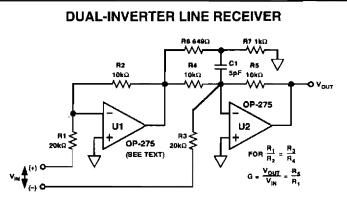
This receiver covers the 118- to 136-MHz AM aviation band. It has a 10.7-MHz IF amplifier. L1, L3, and L5 are 1½ turns of #24 wire. F1L1 is a 10.7-MHz ceramic filter. IF bandwidth will be about 250 kHz.



ANALOG DEVICES

This circuit is for audio applications.

Fig. 76-7

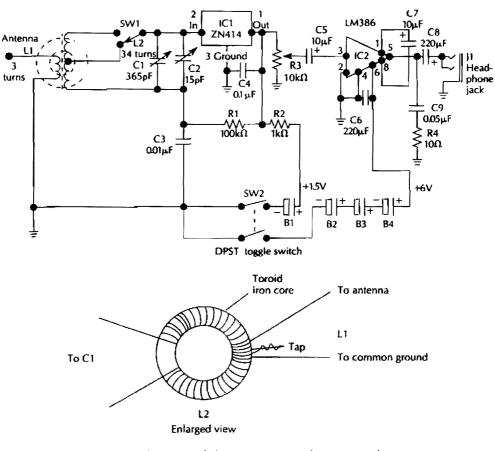

TOROIDAL CORE TRF SHORTWAVE RECEIVER

L1--3 turns of #24 enameled magnet wire wound over center of L2. L2--34 turns of #24 enameled wire--coils wound on toroid iron core form T-50-2---tapped at the 17th turn. Form has only ½-inch diameter.


Wind 34 turns, with a tap at the 17th turn, for L2 on the small ½-inch diameter iron core form.

McGRAW-HILL

Fig. 76-8


A ZN414 IC feeds an LM386 audio amplifier in this TRF circuit. SW1 is a band-switch. Coverage is up to 18 MHz.

NINE-BAND SHORTWAVE RECEIVER

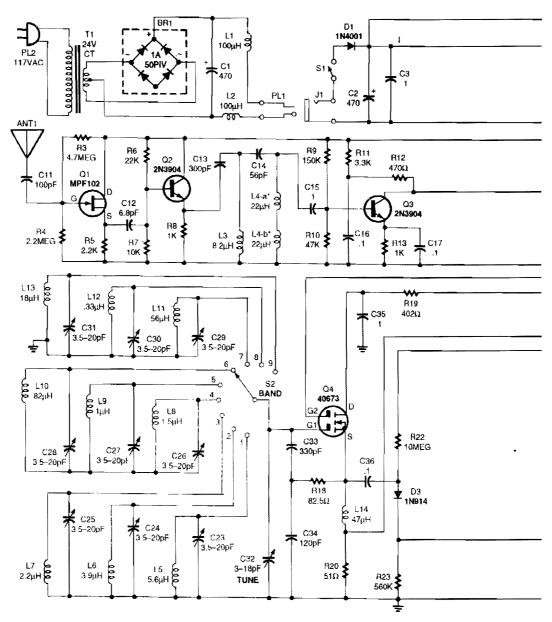


POPULAR ELECTRONICS

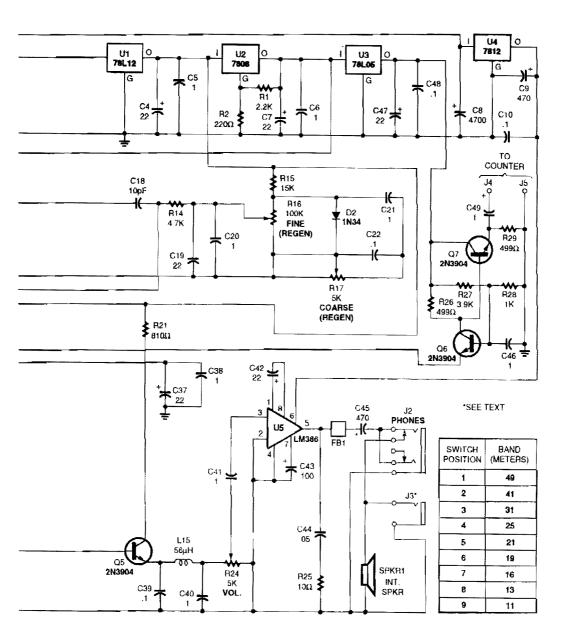Dual-gate MOSFET Q4 is used as a regenerative amplifier in this circuit. An active antenna feeds the signal to Q4, and a short whip antenna is adequate. Detector Q5 feeds volume control R24, and audio amplifier U5, an LM386. The frequency range is 49 to 11 meters in nine bands (6 to 27 MHz).



ONE-TUBE REGENERATIVE SW RECEIVER

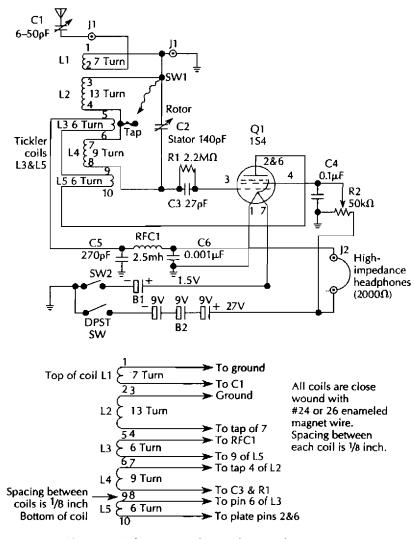


How to wind L1, L2, and L3 with taps. This receiver tunes in the 40- and 80-meter range of frequencies.

McGRAW-HILL

Fig. 76-10

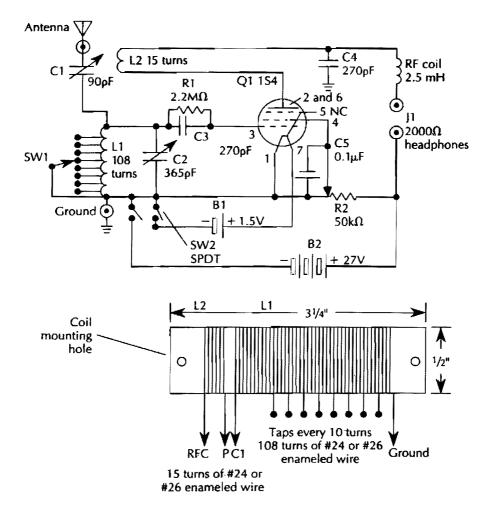A 154 tube is used in a regenerative detector circuit. Details for coils are shown and frequency range can be shifted within 1.5 to 20 MHz by proportionally adjusting the number of turns on coils.






Wind both coils on PVC pipe using either #24 or #26 enameled wire. For coil L1, wind 108 turns on the pipe, and tap every 10 turns.

McGRAW-HILL

Fig. 76-11

Suitable for AM reception and as a simple radio project, this circuit uses a single tube as a regenerative detector.

TWO-BAND RADIO

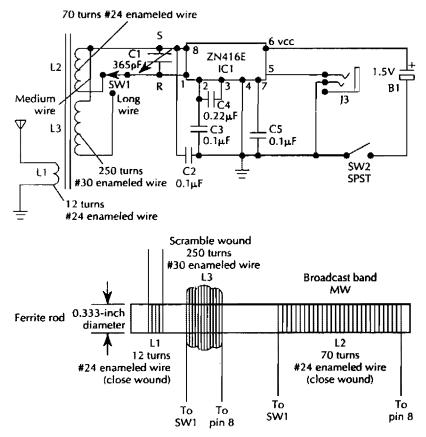


All three coil windings are wound on one long ferrite form. Two different coils are switched into the circuit, covering the longwave (lw) and medium-wave (mw) broadcast band.


McGRAW-HILL

Fig. 76-12

This TRF receiver covers the AM broadcast band and longwave bands (used in Europe and Asia for broadcasting). A loop antenna is used for reception and an external antenna can be connected. Frequency coverage is 150 to 1600 kHz.

SIMPLE CRYSTAL RADIO

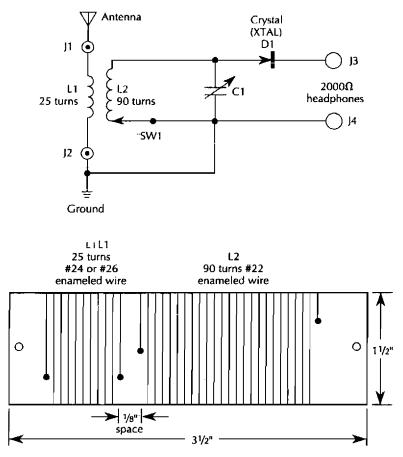

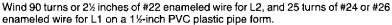


McGRAW-HILL

Fig. 76-13


An IN34A (D1) is used as a detector in this crystal radio. A good outdoor antenna should be used.

VIDEO LINE RECEIVER

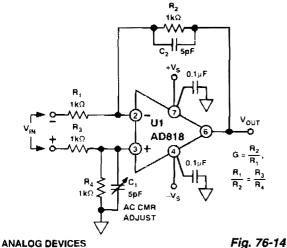

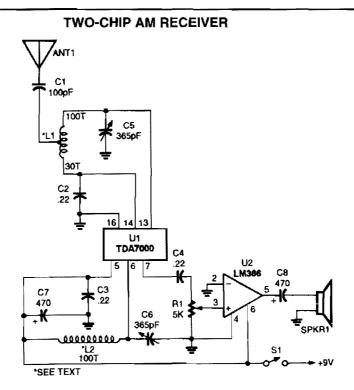This circuit can achieve 46-dB commonmode rejection if R1, R2, R3, and R4 are matched to 1%. C1 is adjusted for best CMR above 1 MHz.






POPULAR ELECTRONICS


Fig. 76-15

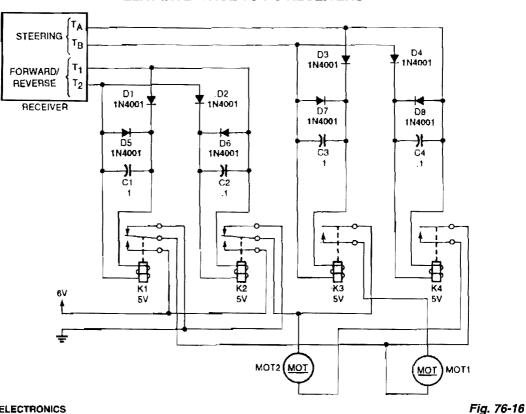This receiver is comprised of a TDA7000 single-chip FM receiver (U1), an LM386 low-voltage audio-power amplifier (U2), a pair of hand-wound coils (L1 and L2), and a few additional components. L1 and L2 are 100 turns of #28 wire on toroidal cores (about 240 µH each). L1 is tapped at 30 turns.




POPULAR ELECTRONICS

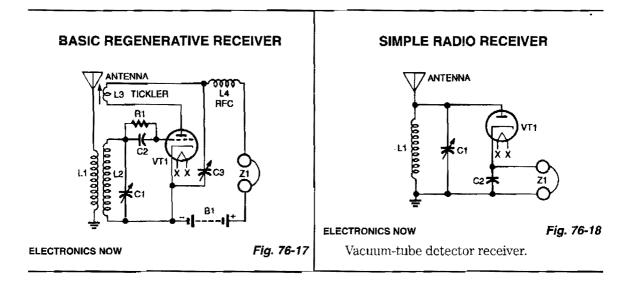You can add relays to some inexpensive RC receivers to operate your own chassis.



ONE-TUBE AM RECEIVER

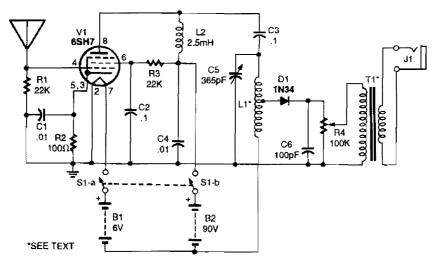


POPULAR ELECTRONICS

Fig. 76-19

This radio uses an untuned RF stage to boost the signal voltage up to the linear portion of the crystal diode's characteristic curve. The circuit's distortion and wide bandpass and a good-quality transformer make for a great-sounding AM radio. L1 is a winding of #22 enamelled wire 2" long on a 2" diameter plastic pipe. T1 is a tube-type radio output transformer, rated at 2000 Ω to the speaker voice coil.

BALANCED LINE RECEIVER

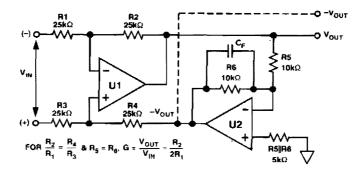


ANALOG DEVICES

Fig. 76-20

Unity-gain inverter U2 drives R4 (usually grounded at $-V_{out}$, equalizing currents in ±input legs, and provides a choice of balanced p-p output with a gain of R_2/R_1).

SUPERHET FRONT END

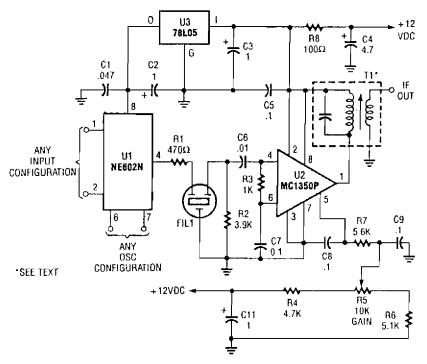


RADIO CRAFT

Fig. 76-21

This superhet receiver front end is simple and uses an NE602 followed by an MC1350 IF amplifier.

RECEIVER PREAMP

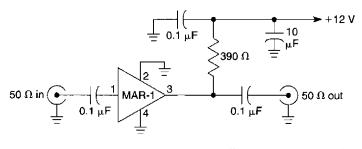


Freq. range 0.5-500 MHz Power gain $G_{\rm p}$ = 17 dB @ 50 MHz

WILLIAM SHEETS

Fig. 76-22

Suitable for HF and VHF receivers, this preamplifier can be mounted on the back of the receiver for a boost in gain. Useful gain is about 17 dB at 50 MHz.


REGENERATIVE RECEIVER FOR 6 TO 17 MHz

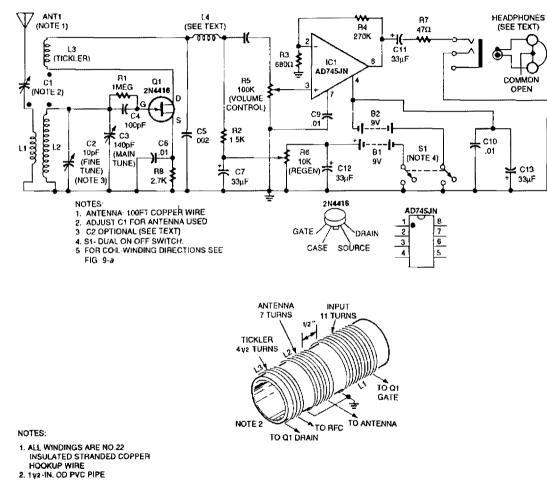

ELECTRONICS NOW!

Fig. 76-23

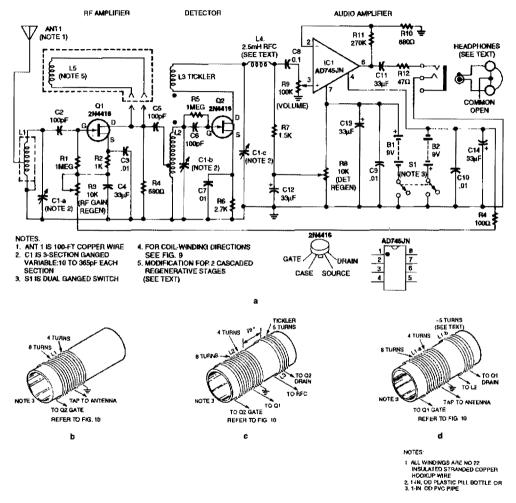The headphones are 32- Ω stereo types. The common lead is left floating so that the two sides are in series, giving 64 Ω .




TWO-STAGE TRF REGENERATIVE RECEIVER

Fig. 76-24

ELECTRONICS NOW

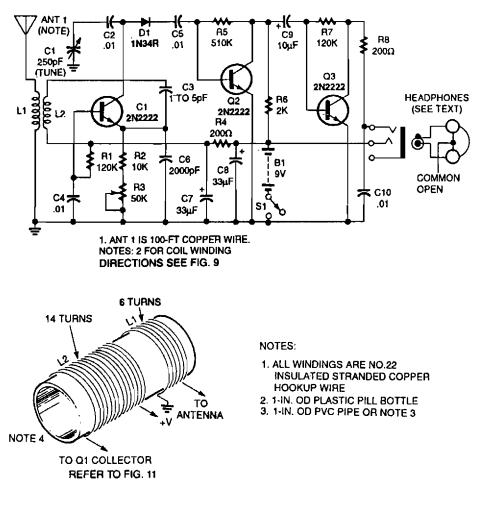This regenerative receiver uses a tuned RF stage to improve performance. The coil in Fig. 76-24D is for the purpose of adding a second regenerative stage (RF amp). This coil is L5 in the schematic.




ECONOMY SHORTWAVE RECEIVER

ELECTRONICS NOW

Fig. 76-25


Using three transistors, this receiver covers the range of 6 to 17 MHz. Coils can be altered to change the range to a lower or higher frequency.

VARIOMETER-TUNED RADIO

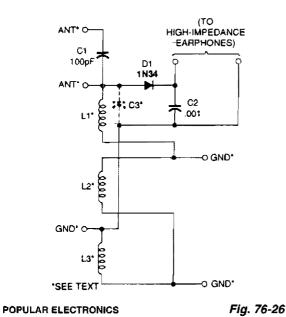

The two fixed coils of the variometer, L1 and L3, are wound on an 8%-inch-long piece of 1-inchdiameter plastic pipe (its outer diameter is about 1% inches). Each coil is 2% inches long. The number of turns is not critical, but 86 tightly wound turns of #22 enameled wire were used. When winding the coils, make sure you start at a point that will allow them to be placed 2 inches apart on the pipe. Drill holes in the pipe and run the leads of the coils out the end of the pipe that is closest to each.

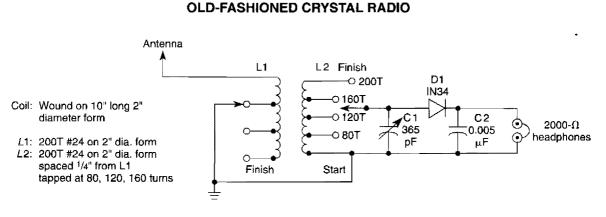The movable coil, L2, is wound on a piece of 1%-inch plastic pipe (its outer diameter is about 1% inches). The winding is 2 inches long. Like L1 and L3, the actual number of windings of this coil are not critical, as long as the winding is approximately the right length.




WILLIAM SHEETS

Flg. 76-27

L1 and L2 are wound on 4" diameter 10" form and are 200 turns of #24 wire. PVC pipe can be used.

WWV RECEIVER

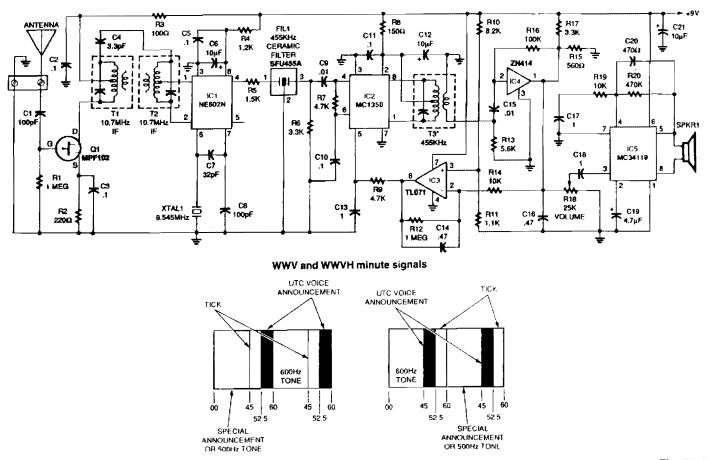

ELECTRONICS NOW

Fig. 76-28

This receiver for 10-MHz WWV signals uses a 10.7-MHz FM receiver IF transformers as front-end components. It is a superhet with a 455-kHz IF frequency. By changing the front-end components 5- or 15-MHz reception could be obtained. A 3- to 6-foot antenna is usually adequate.


77

Reference Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Low-Voltage Reference Positive Voltage Reference Negative Voltage Reference


LOW-VOLTAGE REFERENCE

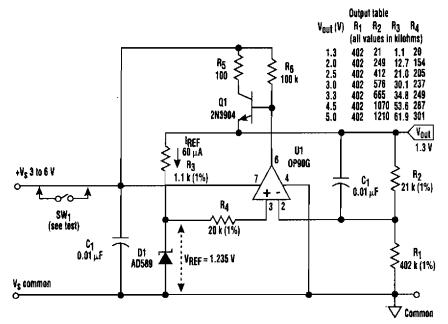

ELECTRONIC DESIGN

Fig. 77-1

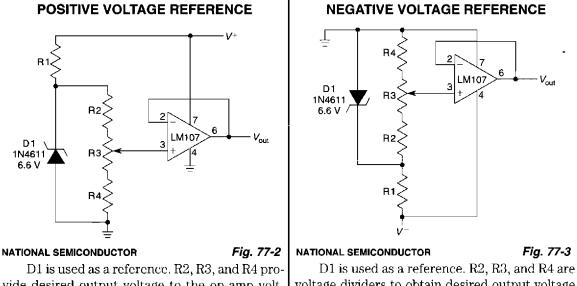This circuit illustrates a number of techniques that are useful for low-voltage, series-mode, power-efficient references. Intended for output currents of up to 10 mA, this design has an enabled standby current of about 100 μ A; it can be easily programmed over a wide range of output voltages.



vide desired output voltage to the op-amp voltage follower.

voltage dividers to obtain desired output voltage to the op-amp voltage follower.


78

Regulator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

3.3-V 1-A Surface-Mount Regulator
Logic Control of 78XX Regulator
Low-Cost Step-Down Regulator
Dual-Output Regulator
Low-Noise Regulator (5 to 3.3 V)
Reducing Ripple in a Switching Voltage Regulator
Low-Dropout Three-Terminal Regulators for New Microprocessor Applications
Low-Dropout Regulator
Positive Regulator Sinks Current
5- to 3.3-V Surface-Mount Switching Regulator

3.3-V 1-A SURFACE-MOUNT REGULATOR

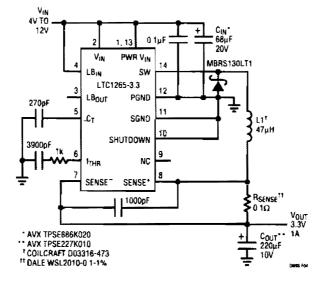


LINEAR TECHNOLOGY

Fig. 78-1

Fig. 78-2

This figure shows a typical LTC1265 surface-mount application. It provides 3.3 V at 1 A from an input voltage range of 4 V to 12 V. The peak efficiency approaches 93% at mid-current levels.

LOGIC CONTROL OF 78XX REGULATOR

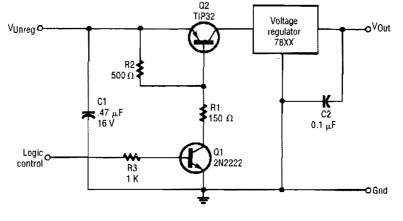

ELECTRONICS NOW

Transistors can be used to control any 78xx series regulator with logic signals. Both transistors are controlled by the logic level present at the base of Q1.

LOW-COST STEP-DOWN REGULATOR

Output (V)

12,54

12.52

12.49

12.45

Output (V)

12.53

12.46

12.37

12.20

Input (V)

150

18.0

21.0

Input = 18.0 V, Output taken at C3

Input = 18.0 V, Output taken at C4

Load (Ohm)

1k

90.9

47.6

24.4

Load (Ohm)

1k

90.9

47.6

24.4

Output (V)

12.35

12.45

12.53

Output taken at C3, Load = 24.4 Ohms

Ripple

Ripple

Ripple

(kHz)

4

112

58

31

(kHz)

08

.....

.....

_

(kHz)

17.8

31.0

43.3

(mVpp)

50

25

40

70

(mVpp)

58

1.5

1.5

5

(mVPP)

73

70

75

Eff. (%)

67

86.5

88.9

91.8

Eff. (%)

67

86 5

88.4


90.4

Eff. (%)

93.4

91.8

90.8

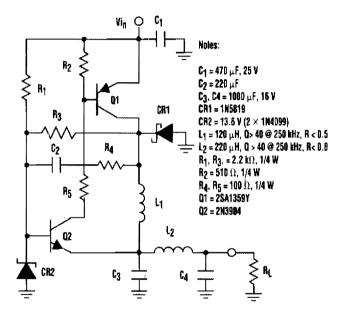


ELECTRONIC DESIGN

Fig. 78-3

This inexpensive and efficient discrete step-down regulator is based on a complementary transistor arrangement that uses both positive and negative feedback and is referenced to a Zener diode. Inductor L1 is selected to maintain the switching frequency above the audible range for the intended operating load. The output filter L2 and C4 reduces ripple to less than 10 mV p-p over a large range of loads, with only a slight decrease in efficiency.

DUAL-OUTPUT REGULATOR

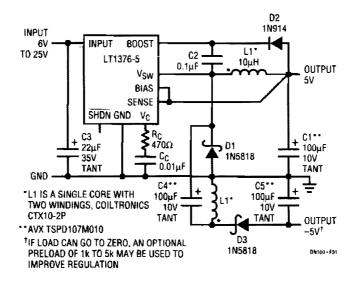


LINEAR TECHNOLOGY

Fig. 78-4

If load can go to zero, an optional preload of 1 to 5 k Ω can be used to improve regulation. Many modern circuit designs still need a dual polarity supply. Communication and data acquisition are typical areas where both 5 V and -5 V are needed for some of the IC chips.

The current mode architecture and saturating switch design allow the LT1376 to deliver up to 1.5-A load current from the 8-pin SO package. L1 is a 10- μ H surface-mount inductor from Coiltronics. The second winding is used to create a negative-output SEPIC (Single-Ended Primary Inductance Converter) topology using D3, C4, C5, and the second half of F1. This converter takes advantage of the fact that the switching signal driving L1 as a positive buck converter is already the correct amplitude for driving a -5-V SEPIC converter. During switch-off time, the voltage across L is equal to the 5-V output plus the forward voltage of D1. An identical voltage is generated in the second winding, which is connected to generate -5 V using D3 and C5. Without C4, this would be a simple flyback winding connection with modest regulation. The addition of C4 creates the SEPIC topology. Note that the voltages swing at both ends of C4 is theoretically identical—even without the capacitor. The undotted end of both windings goes to a zero ac voltage node, so the equal windings will have equal voltages at the opposing ends. Unfortunately, coupling between windings is never perfect, and load regulation at the negative output suffers as a result. The addition of C4 forces the winding potentials to be equal and gives much better regulation.

LOW-NOISE REGULATOR (5 TO 3.3 V)

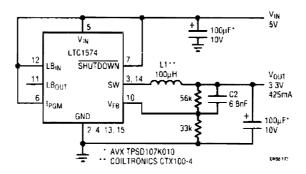


LINEAR TECHNOLOGY

Fig. 78-5

In some applications, it is important not to introduce any switching noise within the audio frequency range. To circumvent this problem, a feed-forward capacitor can be used to shift the noise spectrum up and out of the audio band with C2 being the feed-forward capacitor. The peak-to-peak output ripple is reduced to 30 mV over the entire load range. A toroidal surface mount inductor L1 is chosen for its excellent self-shielding properties.

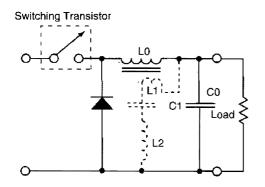REDUCING RIPPLE IN A SWITCHING VOLTAGE REGULATOR



NASA TECH BRIEFS




Simple additional circuitry that consists of relatively small components can reduce the output ripple by a factor of about 10. The additional components are indicated by the dashed lines.

A current opposing the ripple is injected into the filter capacitor. The essence of the present technique is to inject, into this capacitor, a current opposite to that which already flows into this capacitor. A small additional winding, L1, in inductor L0 provides transformer coupling to generate the current that opposes the original ripple current. The circuit from L1 through C0 is completed by a small additional external inductor L2 and coupling capacitor C1.

LOW-DROPOUT THREE-TERMINAL REGULATORS FOR NEW MICROPROCESSOR APPLICATIONS

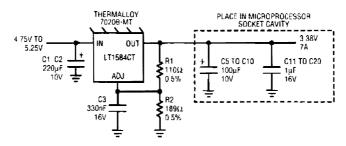
Recommended LT1584 Adjustable Circuit for the Intel P54CT Microprocessor



LINEAR TECHNOLOGY

Flg. 78-7

The LT1584/LT1585/LTL1587 are high-performance, low-dropout regulators designed to meet the demands of the newest high speed, low voltage microprocessors. These devices are designed to regulate from 5-V supplies to output voltages between 1.25 V and 3.6 V. The LT1584 can provide up to 7 A of current, making it ideal for powerful Pentium processor or similar applications. The LT1585 can supply up to 4 A, while the LT1587 supplies up to 3 A. The excellent transient response capability allows them to maintain good regulation even with significant load steps. Fixed 3.3 V, 3.45 V, 3.6 V and adjustable output voltages are available.

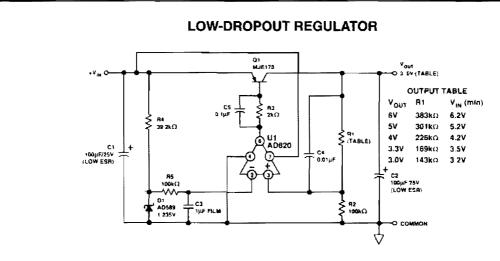


ELECTRONIC DESIGN

Fig. 78-8

This low-dropout reference produces a 4.5-V output from a supply just a few hundred mV greater. With 1-mA dc loading, it maintains a stable 4.5-V output for inputs down to 4.7 V.

POSITIVE REGULATOR SINKS CURRENT

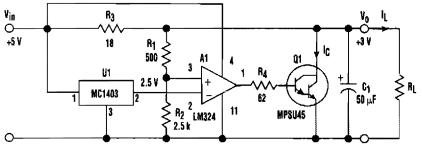

ELECTRONIC DESIGN

Fig. 78-9

Generally speaking, conventional positive voltage regulators can only source current; they can't sink it. However, the positive regulator shown breaks that rule because it can perform both functions. The idea is to have the control transistor Q1 in shunt so that the regulator can either source or sink current.

The circuit provides +3-V output from a +5-V supply. U1 is a bandgap reference that supplies a stable +2.5-V reference to the error amplifier (A1). The output voltage (V_0) is sampled by the resistor network (R1 and R2). If V_0 were to increase, A1 will drive the base of Q1 harder, increasing the collector current (I_c).

This increases the drop across R3 and V_0 decreases, thus regulating the output voltage. The output voltage is given by $V_0 = 2.5(1 + R_1/R_2)$.

Under no load conditions, Q1 draws 110 mA $[(V_{in} - V_0)/R_3]$. With a load connected, and as the regulator begins to source load current (I_L) , I_c decreases to keep the drop across R3 constant.

At $I_{\rm L} = 100$ mA, Q1 carries 10 mA. If $\bar{R}_{\rm L}$ is connected to the positive supply higher than V_0 , then the regulator must sink current, and $I_{\rm L}$ becomes negative. At $I_{\rm L} = -100$ mA, Q1 carries 210 mA while maintaining the output voltage at +3 V. The output voltage will remain constant at +3 V—even if the load current changes sign.

With the proper heatsink on Q1, the regulator can sink more than 300 mA. If a "sink only" option is desired, the dissipation in Q1 can be reduced by using a 180- Ω resistor for R3. R4 limits the base current drive for Q1 and prevents the output of A1 from being clamped at 2 $V_{\rm BE}$.



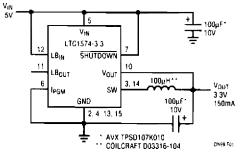


Fig. 78-10


This converter provides 3.3 V at 150 mA from an input voltage of 5 V. Peak inductor current is limited to 340 mA by connecting pin 6 (I_{PGM}) to ground. For applications requiring higher output current, connect pin 6 to $V_{\rm m}$. Under this condition, the maximum load current is increased to 425 mA.

Relay Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Latching Relay Alarm Circuit Momentary Relay Circuit Latching Relay Driver for +12-V Loads High-Impedance Relay Driver Latching Relay Driver Transistor Relay Driver Fast Turn-On/Delayed-Off Relay Circuit Low-Frequency Relay Oscillator

LATCHING RELAY ALARM CIRCUIT

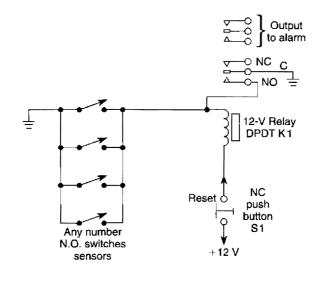


WILLIAM SHEETS

Fig. 79-1

Momentarily closing any sensors will cause K1 to latch. S1 must be depressed to reset circuit. If any sensor is still closed circuit will not reset.

MOMENTARY RELAY CIRCUIT

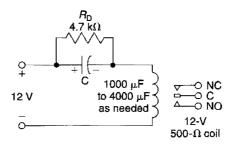


WILLIAM SHEETS

The charging current of a capacitor can be used if a momentary relay-on circuit is needed. Depending on the relay characteristics, C will vary from 1000 to 4000 μ F or so for a 1-s hold time if a 500- Ω relay is used. $R_{\rm D}$ discharges capacitor C to ready the circuit for the next operation. The value should be high enough so as not to maintain the relay closure at highest expected supply voltage.

Fig. 79-2

LATCHING RELAY DRIVER FOR +12-V LOADS

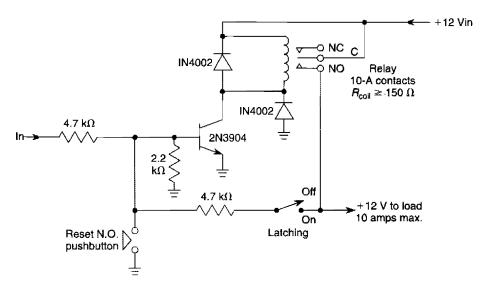


WILLIAM SHEETS

Fig. 79-3

Fig. 79-4

A 4-V signal will cause the relay to pull in when Q1 turns on. Latching is obtained by feedback through a 4.7-k Ω resistor. A switch is used to select latching or nonlatching operation. A NO pushbutton releases the circuit.


HIGH-IMPEDANCE RELAY DRIVER

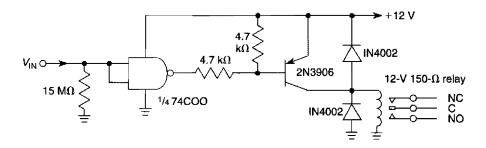

WILLIAM SHEETS

A CMOS gate is used to drive a switching transistor and relay.

LATCHING RELAY DRIVER

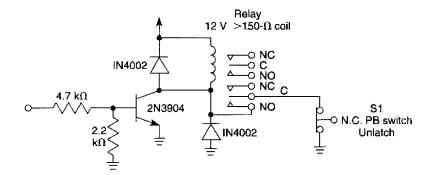


WILLIAM SHEETS

Fig. 79-5

An input of 4 V or greater will drive this circuit. When the relay pulls in, one pair of contacts is used to latch the relay closed. It will remain closed until S1 is pressed.

TRANSISTOR RELAY DRIVER

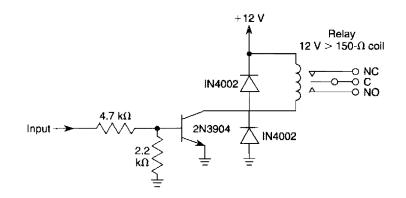


WILLIAM SHEETS

An input of 4 V or greater will drive this relay circuit.

Fig. 79-6

FAST TURN-ON/DELAYED-OFF RELAY CIRCUIT

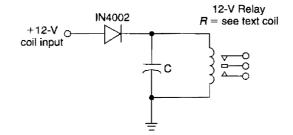


WILLIAM SHEETS

Fig. 79-7

Fig. 79-8

C is a large capacitor that has a charge time of $R_{\text{supply}} C$, assuming $R_{\text{supply}} < R_{\text{coil}}$. The discharge time will be $R_{\text{coil}} C$ neglecting relay coil inductance. With $C = 10,000 \ \mu\text{F}$ and $R_{\text{coil}} = 500 \ \Omega$, a release time constant of 5 seconds might be obtained. Many relays will hold in until the coil current decays to 25% of the pull-in current so that the actual time constant depends on the relay holding current.

LOW-FREQUENCY RELAY OSCILLATOR

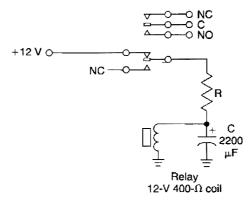

WILLIAM SHEETS

Depending on the value of C and the resistance of the relay coil, and the difference in pull-in and drop-out voltage, this circuit will oscillate at a low frequency. R limits in rush current to capacitor C to a level that the relay contacts can handle. Typically, for a 400- Ω relay, R can be 20 to 440 ohms. Flash rate is approximately 1 cycle/second, depending on the relay.


572

Sample-and-Hold Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Micropower 4-Channel Sample-and-Hold Circuit Low-Drift Sample and Hold

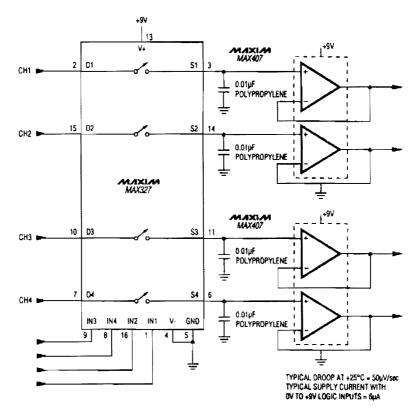MICROPOWER 4-CHANNEL SAMPLE-AND-HOLD CIRCUIT




MAXIM

Fig. 80-1

.

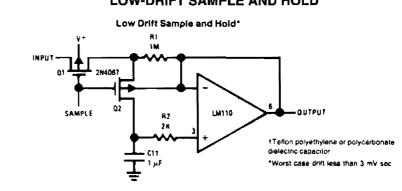Three Maxim ICs make up this sample-and-hold circuit. The supply current is only 6 µA.



LOW-DRIFT SAMPLE AND HOLD

NATIONAL SEMICONDUCTOR


Flg. 80-2

Sawtooth Generator Circuits

 T_{he} sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Op-Amp Linear Sawtooth Generator Sawtooth Generator

OP-AMP LINEAR SAWTOOTH GENERATOR

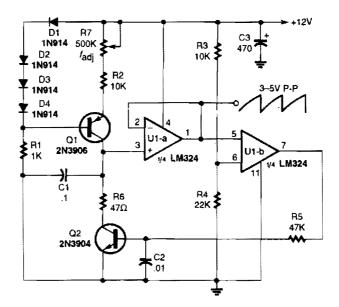

POPULAR ELECTRONICS

Q1 is connected in a simple constant-current generator circuit. The value of Q1's emitter resistor sets the constant-current level flowing from the transistor's collector to the charging capacitor, C1.


One op amp of an LM324 quad op-amp IC, U1-a, is connected in a voltage-follower circuit. The input impedance on the voltage follower is very high and offers little or no load on the charging circuit. The follower's output is connected to the input of U1-b, which is configured as a voltage comparator. The comparator's other input is tied to a voltage-divider setting the input level to about 8 V.

The output of U1-b at pin 7 switches high when the voltage at its positive input, pin 5, goes above 8 V. That turns on Q2, discharging C1. The sawtooth cycle is repeated over and over as long as power is applied to the circuit.

The sawtooth's frequency is determined by the value of C_1 and the charging current supplied to that capacitor. As the charging current increases, the frequency also increases, and vice versa. To increase the generator's frequency range, decrease the value of C_1 , and to lower the frequency, increase the value of C_1 . The output is about 3 to 5 V.

Fig. 81-1

SAWTOOTH GENERATOR

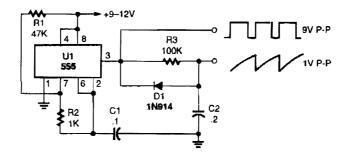

POPULAR ELECTRONICS

Fig. 81-2

A sawtooth waveform generator circuit using a 555 IC is shown. The IC is connected in an astable oscillator circuit with the majority of the output contained in the positive portion of the cycle. The negative output is a very brief pulse.

Capacitor C2 charges through R3 in a positive direction during the time that the IC's output (at pin 3) is high. When the output goes negative, C2 is rapidly discharged through D1 and the IC's output.


Peak-to-peak sawtooth output is about 1 V. The linearity of this circuit is best when R3 is as large as possible. The oscillator's frequency is about 200 Hz and can be increased by lowering either the value of R_1 or C_1 ; to decrease the frequency, increase the values of those components.

Scanner Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

FM Scanner Noise Squelch Scanner Silencer Shortwave Converters for Scanners


FM SCANNER NOISE SQUELCH

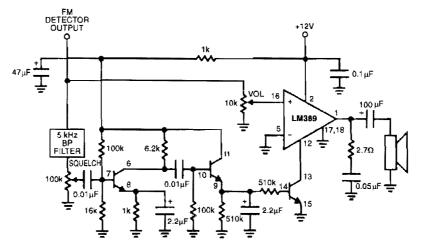

NATIONAL SEMICONDUCTOR

Fig. 82-1

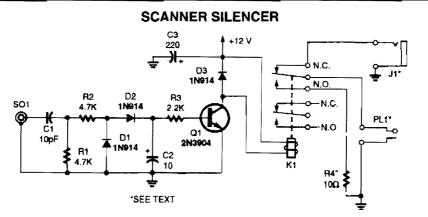The LM389 is operated in the cut-off mode with pin 12 grounded via one of the internal transistors. A sample of detected noise is taken through a 5-kHz filter. Upon reception of signal, the detector output quiets, and noise level drops. This increases impedance at pin 12 of the LM389, causing audio to be passed. The three transistors are part of the LM389.




POPULAR ELECTRONICS

When a scanner is used at amateur radio or CB stations, the scanner sometimes picks up transmitted signal and howls or squeals. When RF is detected, Q1 turns on, energizing K1 and disconnecting the scanner speakers. SO1 is connected to the transmit antenna lead via a tee fitting. C1 is optimum for 5- to 10-W 30-MHz use. For higher power or higher frequencies, reduce C1 to as low as needed. If C1 is so small as to be impractical, R1 can be shunted with a 10- or 22-pF capacitor, as needed.

Fig. 82-2

SHORTWAVE CONVERTERS FOR SCANNERS

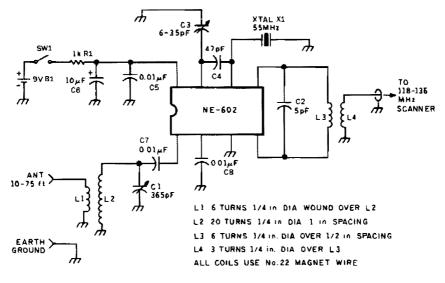

73 AMATEUR RADIO TODAY

The AM aircraft band at 118 to 136 MHz is used in this converter design as an IF output. The sec-

Fig. 82-3


ond harmonic of the 55-MHz crystal (110 MHz) mixes with the shortwave input of 8 to 36 MHz. An NE602 IC is used for the mixer. Sensitivity is about 3 μ V. If desired, a crystal tuning circuit for fine tuning can be obtained using a varactor.

Siren, Warbler, and Wailer Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Fire Siren Warble Oscillator Electronic Siren Wailing Sound Generator Two-Tone Siren

FIRE SIREN

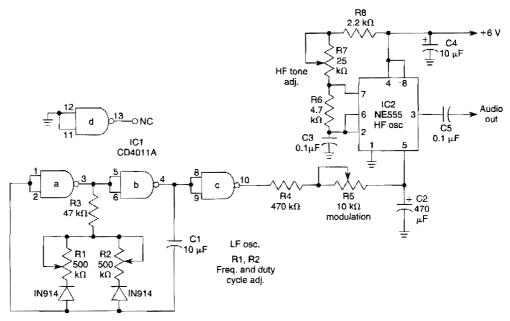


WILLIAM SHEETS

Fig. 83-1

IC1 is an LF oscillator that is variable in attack and decay time with R1 and R2. The LF output modulates HF oscillator IC2. R5 varies the modulation depth. By proper control adjustment, sirens of various types can be simulated.


WARBLE OSCILLATOR

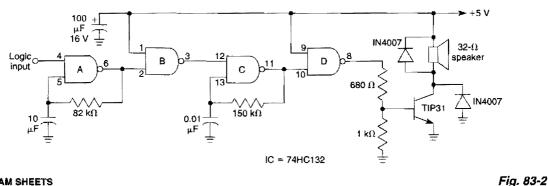

WILLIAM SHEETS

Sections A & B form an oscillator running at 2 Hz, which gates sections C and D, a 1-kHz oscillator. This drives the TIP31 speaker driver.

ELECTRONIC SIREN

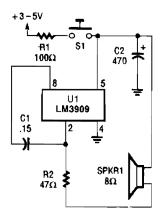


In this circuit, the LM3909 is used in a simple electronic siren. When S1 is closed, C2 begins to charge rapidly through R1. When the charge on C2 reaches about 1 V, the oscillator starts. As the voltage across C1 increases toward +V, the oscillator's output frequency also increases. Releasing (opening) S1 removes power from the circuit. The oscillator continues to operate, with a decline in output volume and frequency until C1 discharges to about the 1-V level.

Experiment with the siren circuit by selecting different R_1/C_2 combinations to obtain a desired rise and fall output. Change the value of C_1 to vary the oscillator's frequency. Keep the value of R_2 at or above 47 Ω to protect the IC from drawing too much current.

POPULAR ELECTRONICS

Fig. 83-3

WAILING SOUND GENERATOR

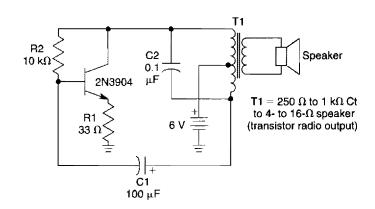


WILLIAM SHEETS

Fig. 83-4

In this circuit, C2 and T1 determine the tone generated and C_1/R_2 control the blocking rate. The signal produced is an interrupted tone, like a police whistle or toy ray gun, depending on C1 and C2.

TWO-TONE SIREN

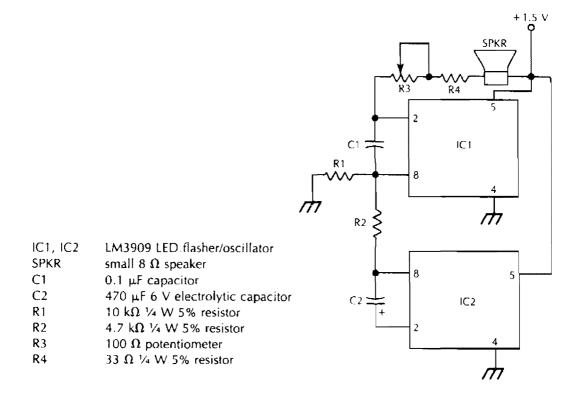

McGRAW-HILL

Fig. 83-5


IC1 generates the main siren tone while IC2 generates a low-frequency square wave, switching IC1 between two different tones. \cdot

Sound-Effects Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Complex Sound-Effect Generator Dual-Tone Generator Surf Man Sound Generator Electronic Whistle Bird-Chirp Sound-Effect Generator Robotic Chatter Sound Generator Electronic Wind Chime Gunshot Sound-Effects Generator

COMPLEX SOUND-EFFECT GENERATOR

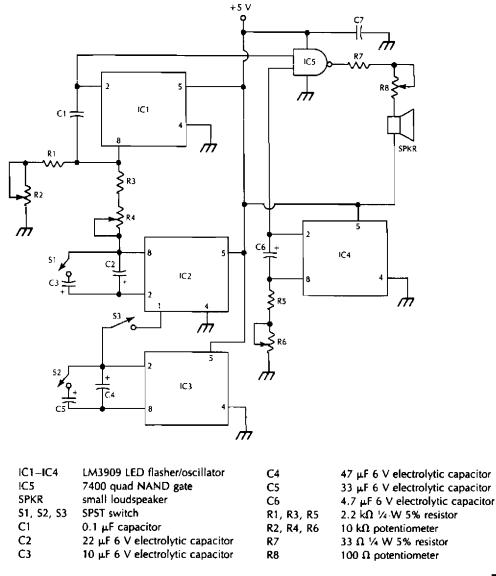


McGRAW-HILL

Fig. 84-1

This system uses four free running oscillators to produce a wide variety of complex sounds. LF oscillator IC3 modulates IC2, which modulates IC1. The audio from IC1 is combined with a variable frequency from IC4. Switches at various points allow oscillators IC3 to be switched in or out, IC1 and IC2 to be varied in frequency, and IC4 also can be varied in frequency. The circuit is not critical and different arrangements can be tried to produce various sound effects.

DUAL-TONE GENERATOR

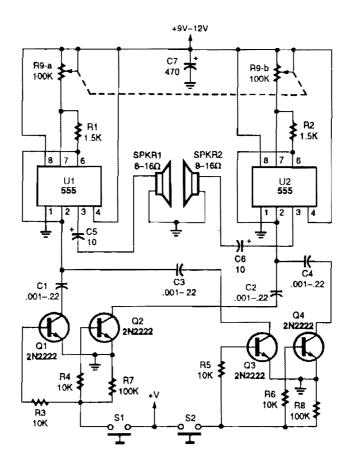


POPULAR ELECTRONICS

Fig. 84-2

Two 555 oscillator/timers are configured similarly as audio oscillators, with each oscillator feeding a separate speaker.

A dual 100-k Ω potentiometer is use to tune the two oscillators simultaneously. The oscillators' frequency range is controlled by a dual-transistor switch, which selects the timing capacitor for both oscillators. Although the circuit only shows two range-switching circuits, any number can be added by simply duplicating the two-transistor switching circuit.

SURF MAN SOUND GENERATOR

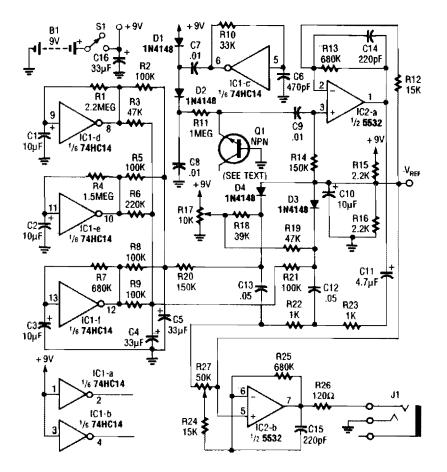


ELECTRONICS NOW

Fig. 84-3

Three low-frequency oscillators (IC1d, e, f) are used to simulate "wave action" of the surf. Q1 is an emitter-base junction used as a diode noise generator, biased by dc derived from oscillator IC1-c. The noise is fed into two voltage-controlled filters R22, R23, C12, C13, with D3 and D4 as "tuning" elements. The low-frequency oscillator signals randomly vary the filters, therefore, the spectrum of the noise signal fed through them. This simulates the sound of a surf.


ELECTRONIC WHISTLE

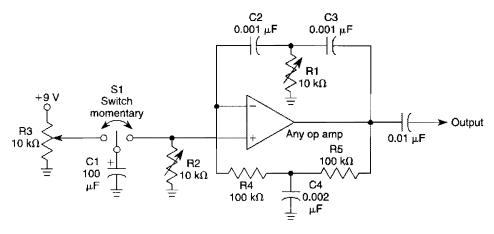

WILLIAM SHEETS

Fig. 84-4

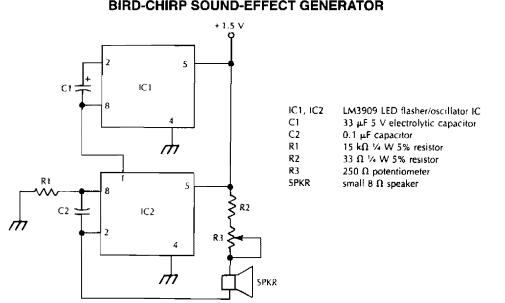The circuit shown is a twin-tec oscillator. R1 varies the pitch, R2 the duration, and R3 the format (bell, rise & fall time, etc.). Vary R4, R5, C4 and C2, C3 for large shifts in frequency.




BIRD-CHIRP SOUND-EFFECT GENERATOR

McGRAW-HILL

Fig. 84-5

A low-frequency oscillator modulates a higher frequency oscillator, which drives the speaker.

ROBOTIC CHATTER SOUND GENERATOR

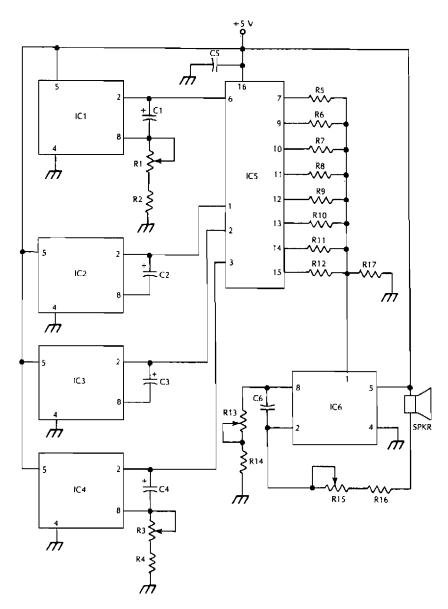


McGRAW-HILL

Fig. 84-6


This circuit simulates sound effects of a robot, for toy or novelty applications.

ROBOTIC CHATTER SOUND GENERATOR (Cont.)

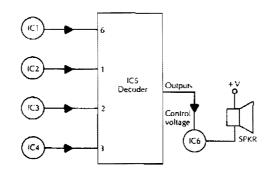

IC1-IC4, IC6	LM3909 LED flasher/oscillator	R5	6.8 kΩ ¼ W 5% resistor
IC5	74L5138 three-line to eight-line decoder	R6	10 k Ω potentiometer
SPKR	smalt loudspeaker	R7	2.2 kΩ ¼ W 5% resistor
C1	10 μF 10 V electrolytic capacitor	R8	33 kΩ ¼ W 5% resistor
C2	22 μF 10 V electrolytic capacitor	R9	3.9 kΩ ¼ W 5% resistor
C3	33 μF 10 V electrolytic capacitor	R10	4.7 kΩ ¼ W 5% resistor
C4	100 µF 10 V electrolytic capacitor	R11	100 kΩ ¼ W 5% resistor
C5	0.01 µF capacitor	R12	470 kΩ ¼ W 5% resistor
C6	0.1 µF capacitor	R15	100 Ω potentiometer
R1, R3, R14	10 kΩ potentiometer	R16	33 Ω ¼ W 5% resistor
R2, R4, R13	3.3 kΩ ¼ W 5% resistor	R17	1 M Ω ¼ W fixed resistor


ELECTRONIC WIND CHIME

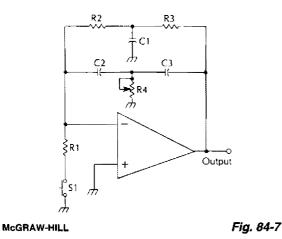

The value of R_4 controls the damping or decay time of the feedback circuit (a twin Tee oscillator). When S1 is closed, the circuit breaks into oscillation. When S1 is opened, the circuit stops oscillating generating a decaying tone like a bell. The frequency is approximately $\[mu]{RC}$. C1, C2, and C3 are typically in the 0.01- μ F range.

591

GUNSHOT SOUND-EFFECTS GENERATOR

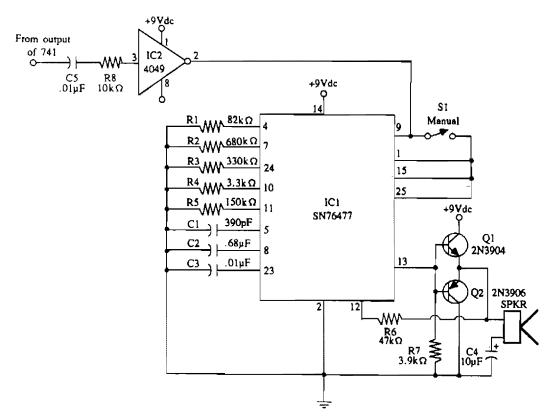

McGRAW-HILL

Fig. 84-8


Gunshot sound-effects generator built around a Texas Instruments SN76477 sound chip. An input pulse causes IC1 to generate a gunshot sound.

Square-Wave Generator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Square-Wave Generator Sharp Square Waveforms from Multivibrator

SQUARE-WAVE GENERATOR

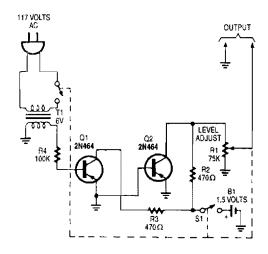


POPULAR ELECTRONICS

Fig. 85-1

A 60-Hz waveform from T1 drives an audio amplifier to clipping. Output is 60 Hz with about 0- to 1.4-V p-p amplitude.

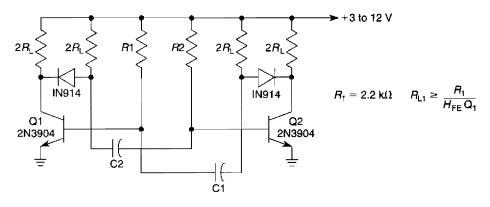SHARP SQUARE WAVEFORMS FROM MULTIVIBRATOR



WILLIAM SHEETS

Fig. 85-2


By using diodes as shown, the loading effect on the collector of the transistors caused by the timing capacitors can be avoided. As the collector of the transistors rises toward $V_{\rm CC}$, the diode disconnects the timing capacitors.

Staircase Generator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Stepped Triangle Waveform Generator Video Staircase Generator Free-Running Staircase Wave Generator Up/Down Staircase Wave Generator

STEPPED TRIANGLE WAVEFORM GENERATOR

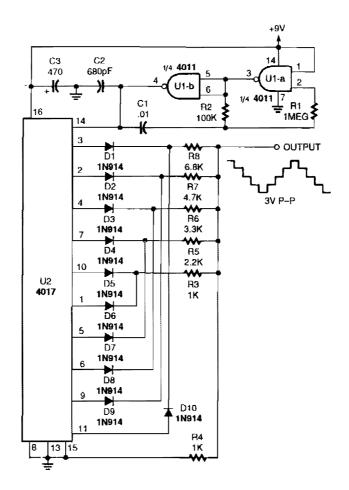


POPULAR ELECTRONICS

Fig. 86-1

Two gates of a 4011 quad two-input NAND gate (U1) are connected in a pulse generator circuit. The square output at pin 4 of U1-b, connects to the clock input, pin 14, of a 4017 decade counter IC (U2). For each input clock pulse, the 4017 takes a single step. Because the 4017 counter is set up to count ten and then repeat the count, the stepped output frequency will only be $\frac{1}{10}$ of the clock frequency. For a 100-Hz output, the clock generator must operate at 1 kHz.

The 4017's positive output pulses begin at pin 3 and progress to pin 11 in a serial manner. The first output pulse, at pin 3, passes through D1 and R8 and appears across R4 to produce the first step up the triangle. The second pulse is routed through D2 and R7 to produce the second step. The outputs at pins 10 and 1 form the top of the waveform and outputs at pins 5, 6, 9, and 11 produce the down steps.

VIDEO STAIRCASE GENERATOR

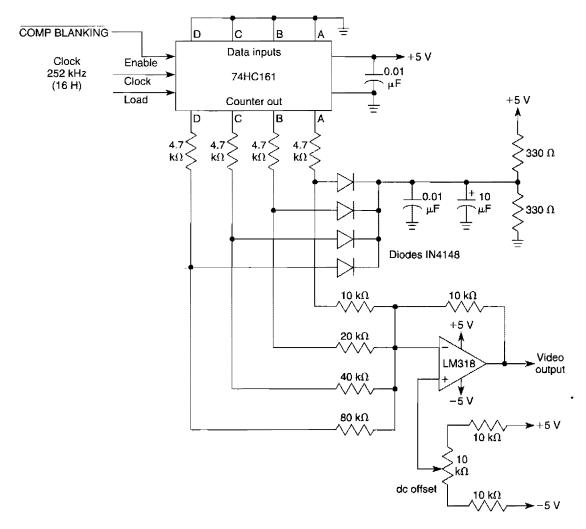


WILLIAM SHEETS

Fig. 86-2

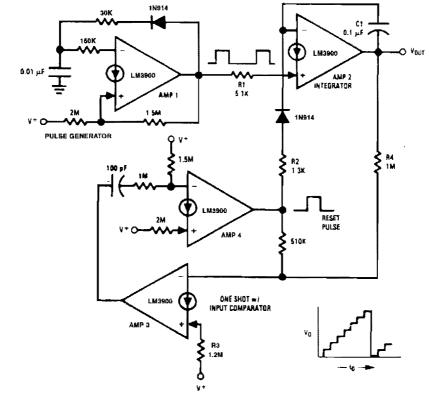Using a 74HC161 counter and a simple D-A converter using an op amp and resistor network, a very simple video staircase generator for gray-scale generation (12 bars) can be obtained. The output is clean and mostly free of "glitches."






NATIONAL SEMICONDUCTOR

Fig. 86-3

This free-running staircase generator uses all four of the amplifiers, which are available in one LM3900 package. Amp 1 provides the input pulses that "pump up" the staircase via resistor R1. Amp 2 does the integrate and hold function and also supplies the output staircase waveform. Amps 3 and 4 provide both a compare and a one-shot multivibrator function. Resistor R4 is used to sample the staircase output voltage and to compare it with the power supply voltage (V+) via R3. When the output exceeds approximately 80% of V+ the connection of Amps 3 and 4 causes a 100-µs reset pulse to be generated. This is coupled to the integrator (AMP2) via R2 and causes the staircase output voltage to fall to approximately 0 V. The next pulse out of Amp 1 then starts a new stepping cycle.

UP/DOWN STAIRCASE WAVE GENERATOR

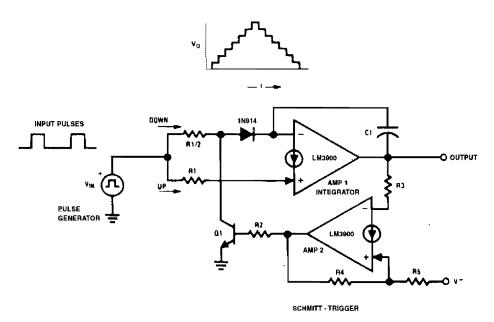

NATIONAL SEMICONDUCTOR

Fig. 86-4


This staircase waveform first steps up and then steps down by the circuit shown. An input pulse generator provides the pulses that cause the output to step up or down, depending on the conduction of the clamp transistor, Q1. When this is ON, the "down" current pulse is diverted to ground and the staircase then steps "up." When the upper voltage trip point of Amp 2 is reached, Q1 goes OFF and as a result of the smaller "down" input resistor (one-half the value of the "up" resistor, R1), the staircase steps "down" to the low-voltage trip point of Amp 2. The output voltage, therefore, steps up and down between the trip voltages of the Schmitt Trigger.

Stepper Motor Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Stepper Motor Pulse Generator Stepper Motor as Shaft Encoder Stepper Motor Encoder Circuit

STEPPER MOTOR PULSE GENERATOR

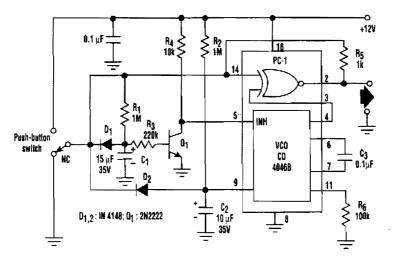


ELECTRONIC DESIGN

Fig. 87-1

When the switch is in its normally closed (NC) position, capacitors C1 and C2 are held discharged by diodes D1 and D2. Switching off transistor Q1 inhibits the voltage-controlled oscillator of the PLL. The two inputs and, hence, the output of the EX-OR gate (phase comparator 1) of the PLL remain at the logic 0 level.


When the pushbutton is pressed, C1 and C2 are allowed to charge via resistors R1 and R2. The VCO is enabled only after a time delay (≈ 0.5 second) set by R1, R3, and C1. During this delay period, the EX-OR gate output follows the logic level at the switch output. As a result, one-shot pulses can be generated by pressing the pushbutton, then releasing it within 0.5 second. R5 provides the switch-debouncing function.

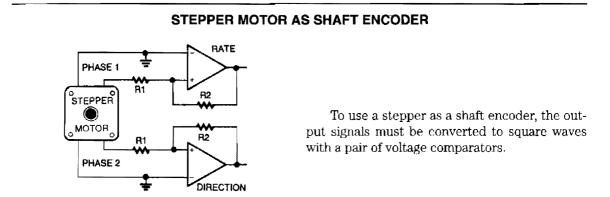If the pushbutton is pressed for more than 0.5 second, the VCO is enabled. The rising voltage at the control input (pin 9) causes a linear increase in VCO frequency and thus accelerates the stepper motor. Releasing the pushbutton discharges C1 and C2 and inhibits the VCO.



ELECTRONICS NOW

STEPPER MOTOR ENCODER CIRCUIT

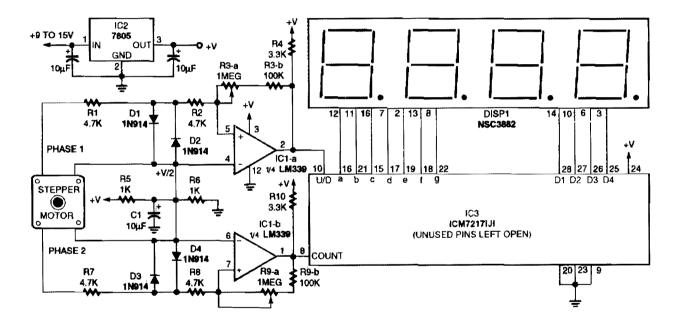

ELECTRONICS NOW

Fig. 87-3

This circuit translates shaft rotation and direction to a readout on an LED display. A stepper motor is used as an encoder.

.


88

Switching Circuits

T he sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Isolated Switch Analog Switched Inverter Analog Switch Circuit Low Output Impedance Multiplexer Op-Amp and Analog Switch RON Compensator Oscillator Triggered Switch Basic Zero-Crossing Switch Circuit Analog Switch Shunt Pin-Diode Switch Receiver Bandswitching Resistor Pin-Diode Switch Digitally Controlled One-of-Four Analog Switch Pin Diode Switch Transceiver T/R Switch Series/Shunt Pin-Diode RF Switch Auto-Off Power Switch Switch-On Delay Circuit HEXFET Switch Circuits Alternating On/Off Control Audio-Controlled Switch Switch Debouncers Simple Switch Debouncer Analog Switch Circuit

ISOLATED SWITCH

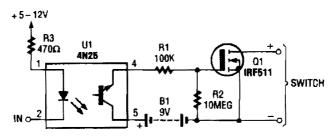


POPULAR ELECTRONICS

Fig. 88-1

This dc-controlled switch uses an optoisolator/coupler, U1, to electrically isolate the input signal from the output control device.


ANALOG SWITCHED INVERTER

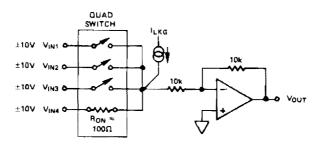

ANALOG DEVICES

Fig. 88-2


ANALOG SWITCH CIRCUIT

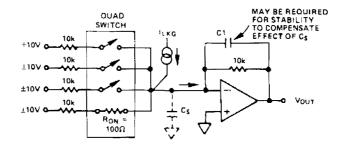

ANALOG DEVICES

Fig. 88-3


LOW OUTPUT IMPEDANCE MULTIPLEXER

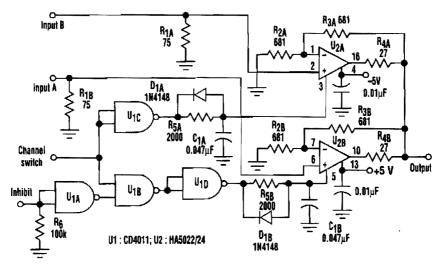

ELECTRONIC DESIGN

Flg. 88-4

Both inputs are terminated in their characteristic impedance; 75 Ω is typical for video applications. Because the output cables usually are terminated in their characteristic impedance, the gain is 0.5. Consequently, amplifiers U2A and U2B are configured in a gain of +2 to set the circuit gain at 1. R_2 and R_3 determine the amplifier gain; if a different gain is desired, R_2 should be changed according to the equation $G = (1 + R_3/R_2)$. R5, LCL1, and D1 make up an asymmetrical charge/discharge time circuit that configures U1 as a break-before-make switch to prevent both amplifiers from being active simultaneously. The multiplexer transition time is approximately 15 µs with the component values shown.

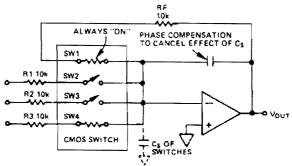


27

OP-AMP AND ANALOG SWITCH RON COMPENSATOR

ANALOG DEVICES

This switch is in series with feedback resistor to compensate gain.

Fig. 88-5

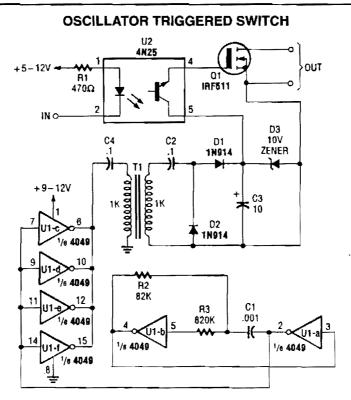


POPULAR ELECTRONICS

Fig. 88-6

In this circuit (the oscillator-triggered switch), the HEXFET's base bias is provided by a signal generated by an astable oscillator.

BASIC ZERO-CROSSING SWITCH CIRCUIT

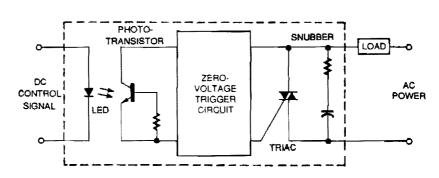


ELECTRONICS NOW

Fig. 88-7

Here is the schematic of a solid-state ac relay with zero-crossing. The triac permits the relay to switch to ac directly.

ANALOG SWITCH

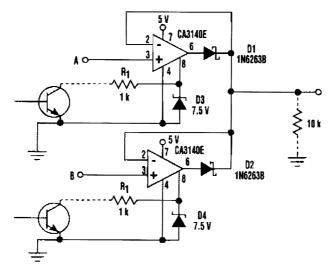

ELECTRONIC DESIGN

Fig. 88-8

This design takes advantage of the strobed output stage of a CA3140 amplifier. With the strobing capability, the circuit's output voltage can be set to either of the input voltages by grounding one of the control inputs, either A or B.


When the strobe input at pin 8 is taken below 1 V, that amplifier is disabled. The remaining amplifier then acts as a unity-gain high-impedance buffer.

The 10-k Ω output resistor enables the output voltage to swing down to 20 mV from ground. The Zener-diode clamps and associated resistors connected at the strobe inputs can be omitted for the lowest-cost applications. However, experience has shown that they allow the amplifiers to shrug off the effect of high transient voltages.


The circuit is particularly suited to 8-bit microcontroller applications, where the strobe inputs can be driven directly from two open-collector output ports under software control.

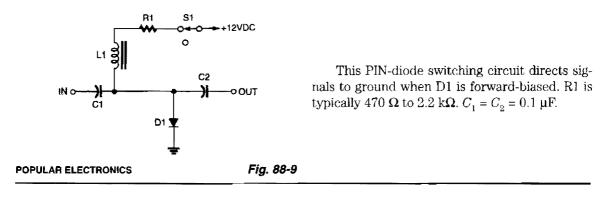The use of Schottky diodes for D1 and D2 makes possible an output swing of 2.5 V when the circuit is powered from a 5-V supply.





RECEIVER BANDSWITCHING

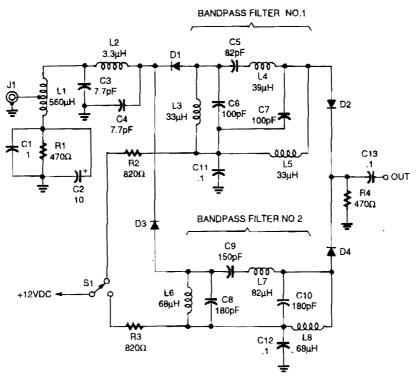


POPULAR ELECTRONICS

Fig. 88-10

Eight-band receiver front-end selection can be accomplished by using PIN diode switches.

RESISTOR PIN-DIODE SWITCH

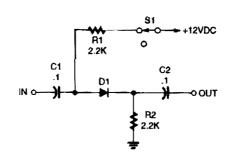


POPULAR ELECTRONICS

Fig. 88-11

This circuit uses resistors instead of RF chokes to keep costs low. The values of R_1 and R_2 should be no lower than about 1 k Ω to minimize loss.

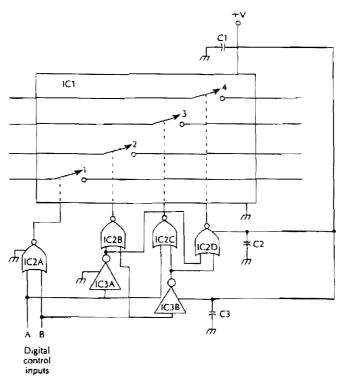
DIGITALLY CONTROLLED ONE-OF-FOUR ANALOG SWITCH



McGRAW-HILL

$$\begin{split} IC1 &= CD4066\\ IC2 &= CD4001\\ IC3 &= CD4049\\ All \ capacitors &= 0.1\ \mu F \end{split}$$

PIN DIODE SWITCH

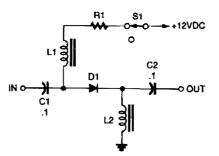

POPULAR ELECTRONICS

Fig. 88-13

Fig. 88-12

This PIN diode switch uses RF chokes and a single diode. R1 is typically 470 Ω to 2.2 k Ω .





A combination of series and shunt switching, like that shown here, results in superior isolation between the input and output when in the off condition.

This transceiver's transmit/receive switch uses PIN-diode instead of a relay. On receive, D1 is cut off, D2 is cut off and the antenna connects to the receiver. During transmit, D1 is forward-biased, as is D2. This connects the receiver input. This causes the input impedance of the transmission line to be high, so little transmitter power reaches the receiver. Although not shown in the schematic, the 12-V supply should have a series resistor of 100 Ω to 2.2 k Ω , depending on diode current, to limit diode current to a safe value.

POPULAR ELECTRONICS



C1

Ľ

D1

D2

D3

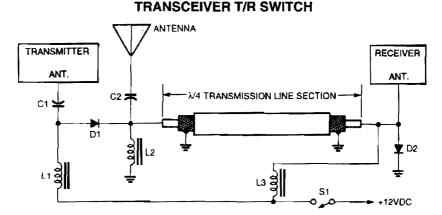


Fig. 88-14

Fig. 88-15




+12VDC

12VDC

ο ουτ


AUTO-OFF POWER SWITCH

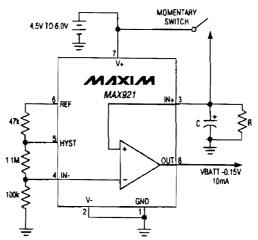

MAXIM

Flg. 88-16

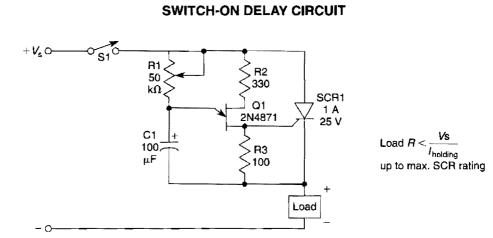This timed switch circuit can be used where a timed power source is needed. The on-time is approximately 4.6 RC.




WILLIAM SHEETS

When S1 is turned on, a very small current flows through the load. Almost the entire supply voltage appears across the SCR. When C1 changes up to the firing voltage of Q1 (approximately the standoff ratio of Q1 times V_s usually 0.4 to 0.6 V_s) through R1, Q1 fires, turning on SCR1. This delivers full voltage to load, minus SCR drop (about 1.2 V). Notice that load current must exceed SCR holding current.

Fig. 88-17


HEXFET SWITCH CIRCUITS

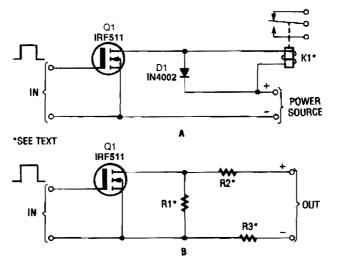

POPULAR ELECTRONICS

Fig. 88-18

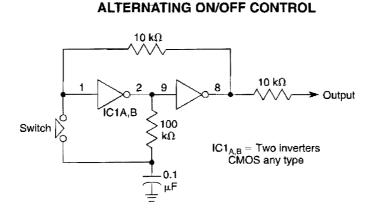The HEXFET can switch dc power to relays (as shown in A), motors, lamps, and numerous other devices. That arrangement can even be used to switch resistors in and out of a circuit, as shown in Fig. 88-18B. R1, R2, and R3 are possible load resistors and represent load configurations that can be used.




WILLIAM SHEETS

Fig. 88-19

When the switch is closed, it causes a change in the state of pins 1 through 8. This will provide a toggle flip-flop action.


AUDIO-CONTROLLED SWITCH

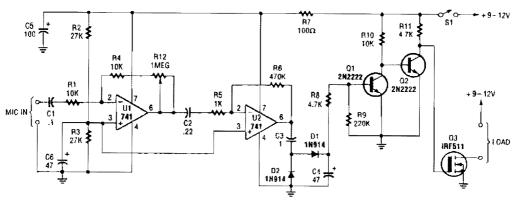

POPULAR ELECTRONICS

Fig. 88-20

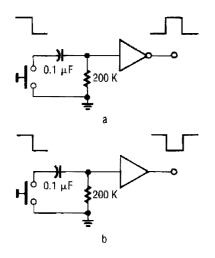The audio-controlled switch combines a pair of 741 op amps, two 2N222 general-purpose transistors, a HEXFET, and a few support components to produce a circuit that can be used to turn on a tape recorder, a transmitter, or just about anything using sound.




SWITCH DEBOUNCERS

These circuits will cure problems caused by switch-contact bounce. The one shown in Fig. 88-21A provides you a positive output pulse, and the one shown in Fig. 88-21B provides you a negative output pulse.

ELECTRONICS NOW!

Fig. 88-21

SIMPLE SWITCH DEBOUNCER

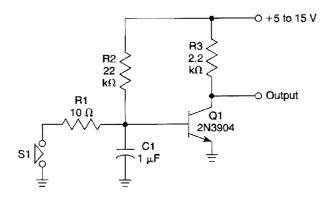


Pressing S1 discharges C1 through R1, causing Q1 to cut off, forcing the output high. Once C1 is discharged below the $V_{\rm BE}$ (ON) of Q1, switch bounce will have no effect on the output.

WILLIAM SHEETS

Fig. 88-22

ANALOG SWITCH CIRCUIT

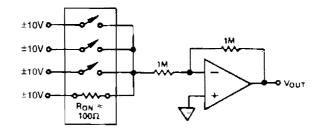

ANALOG DEVICES


Fig. 88-23

89

Sync Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

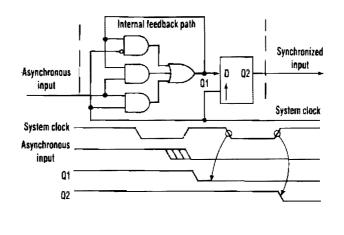PLD Synchronizes Asynchronous Inputs Sync Tip de Restorer Sync Stretcher Circuit Synchronizer Circuit



PLD SYNCHRONIZES ASYNCHRONOUS INPUTS

ELECTRONIC DESIGN

Fig. 89-1

A programmable electrically erasable logic (PEEL) device can easily supply the synchronizing function. Digital systems often require synchronization of asynchronous inputs to avoid the potential metastability problems caused by setup-time violations. A common synchronization method uses two rippled 74LS72 D-type flip-flops.


In this circuit, the asynchronous input feeds into the D.input of the first flip-flop and its Q output feeds into the D of the second. Because the first flip-flop latches on the falling edge of the system clock, to avoid setup-time violations, the D input signal to the second flip-flop will be stabilized before the rising edge of the clock. Even experienced programmable-logic device designers often resort to such a TTL flip-flop circuit to handle the synchronization function, because of the architectural limitations of standard PLDs.

A programmable electrically erasable logic (PEEL) device, such as the PEEL18CV8 from ICT, however, can easily supply the function. The user-programmable 12-configuration I/O macrocells in the device can internally feed back a signal before the output register. With this feedback arrangement, designing a two-stage input is simple.

A gated-latch internally latches the asynchronous input on the falling edge of the system clock, generating signal Q1. ANDing the input with Q1 through the internal feedback path, eliminates a possible hazard condition during the clock's high-to-low transition time. The latch then holds Q1 stable to ensure meeting the setup-time requirement of the subsequent D flip-flop, which, as before, registers the signal on the next rising system clock edge.

If by chance the input pulse width violates the set-up time of the gated latch, the clock's low time will give more time for settling.


SYNC TIP dc RESTORER

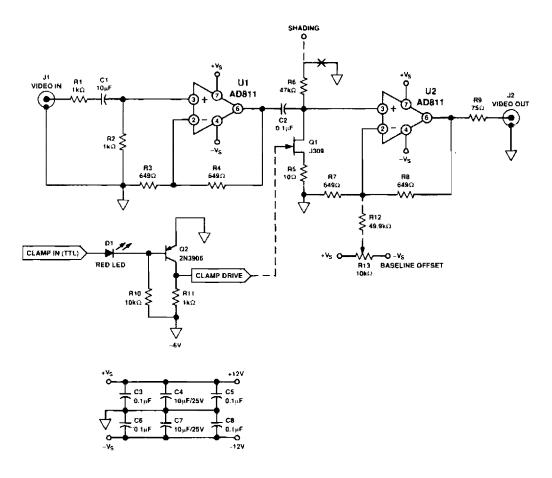

ANALOG DEVICES

Fig. 89-2

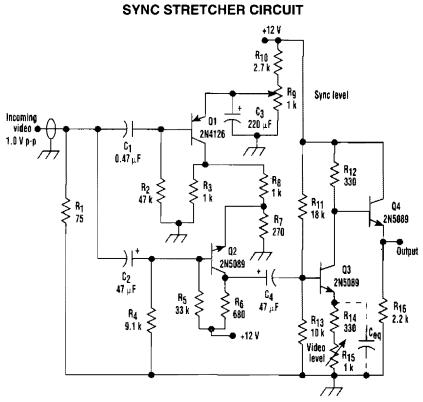
The dc restorer shown supplies a video signal with sync tips clamped to a baseline level. Clamp drive signal is supplied from clsewhere, usually a sync generator or a sync separator.



ELECTRONIC DESIGN

Fig. 89-3

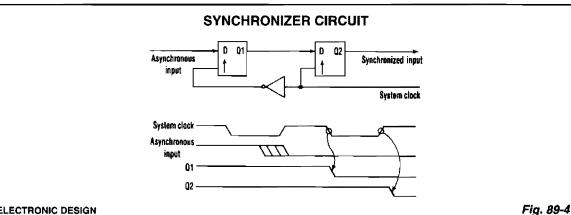Q1, Q2, and Q3 comprise a simple video amplifier and sync stretch circuit. Transistor Q1 sync strips the incoming video, which is amplified and mixed with the stripped sync in Q2. Q3 supplies inversion and video amplitude control.



ELECTRONIC DESIGN

This common synchronization method uses two rippled 74LS74 D-type flip-flops.


90

Telephone-Related Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Telephone Line Tester Caller ID Circuit Telephone Call Restrictor Telephone Scrambler Universal Telephone Hold Circuit Telephone Ring Amplifier Bell System 202 Data Encoder Telephone/Audio Interface Telephone Recording Circuit Telephone Bell Amplifier Phone Line Simulator Phone Helper Telephone Ring Signal Detector Telephone Hold Circuit

TELEPHONE LINE TESTER

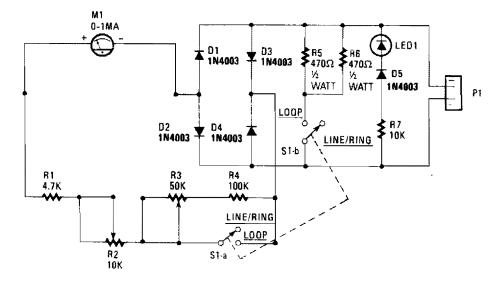

RADIO-ELECTRONICS


Fig. 90-1

The telephone-line tester shown in the figure is connected to the telephone line through modular connector P1. Because the tester's LED polarity indicator is always connected when the tester is plugged in, the instant that the unit is connected, you will have an indication of the polarity. If it is correct—that is, if the green wire is the positive side and the red wire is the negative side—nothing will happen. If the situation is reversed, the LED will light.


With switch S1 set for LINE/RING, both S1-a and S1-b are open and the meter indicates the condition of the line voltage. Any line-voltage reading in the LINE OK range (more on the meter in a moment) indicates a line voltage that is higher than 40 Vdc. If the telephone is caused to ring, either by using a ringback number or by dialing from another phone, the meter will indicate RING OK, and the LED will pulse (indicating ac), if the ringing voltage/current is correct. The actual position of the meter's pointer depends on how many ringers are connected across the line.

When S1 is closed the voltage range of the meter is changed and a nominal load resistance of 230 Ω (R5 and R6) is connected across the line to emulate the off-hook load of the telephone. If the meter indicates LOOP OK, you can be certain that you have sufficient loop voltage for satisfactory telephone operation. If you place another load on the line, perhaps by taking an extension telephone off hook, the meter reading will almost invariably drop below the LOOP OK range. If lifting the hand-set causes the meter reading to drop, you can at least be certain that the telephone's hook switch is working and that the repeat coil is connected to the line.

CALLER ID CIRCUIT

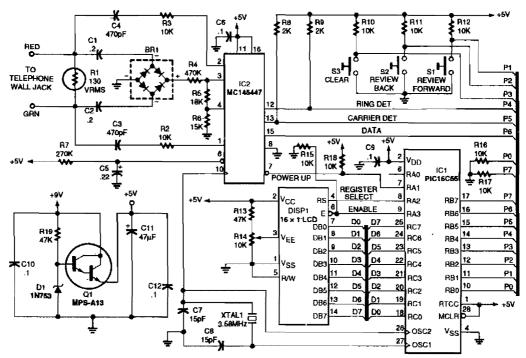

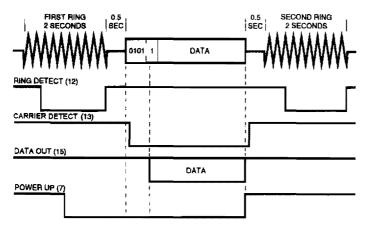THE NEART OF THE CALLER ID circuit is microcontroller IC1 which processes the serial data from IC2, outputs ASCII characters to DISP1, and monitors switches S1–S3.




TIMING RELATIONSHIPS between the data present on the phone line (top), and the output pins of IC2.

ELECTRONICS NOW

Fig. 90-2

This circuit requires programming of the microcontroller. Software information is available from the reference in the original article.

TELEPHONE CALL RESTRICTOR

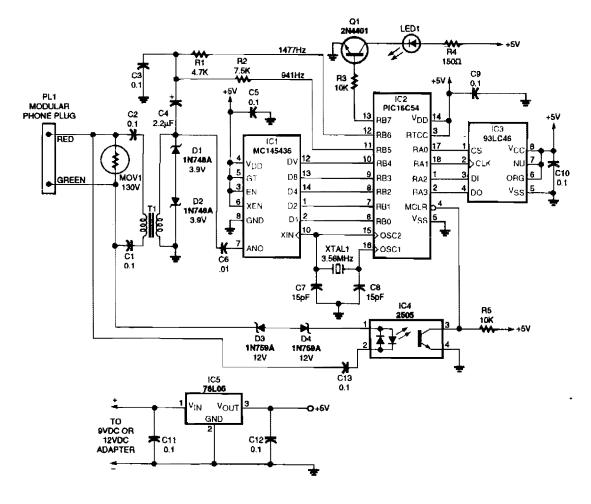


ELECTRONICS NOW

Fig. 90-3

This circuit is designed to restrict phone calls with the area codes: 900, 976, and 540. This device uses a microcontroller to compare the DTMF decoded tones with telephone numbers stored in EEP-ROM (IC3). This device requires a programmed microcontroller. Software and details of programming can be found in the original magazine article.

TELEPHONE SCRAMBLER

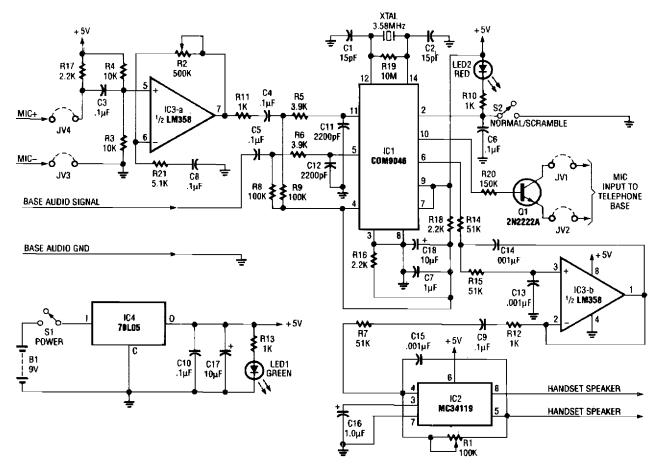


ELECTRONICS EXPERIMENTERS HANDBOOK

Fig. 90-4

This circuit uses the usual speech inversion algorithm, implementing it with a COM9046 ASIC. This unit is designed to fit between the handset and base of a standard telephone. It is powered by a 9-V battery.

٠

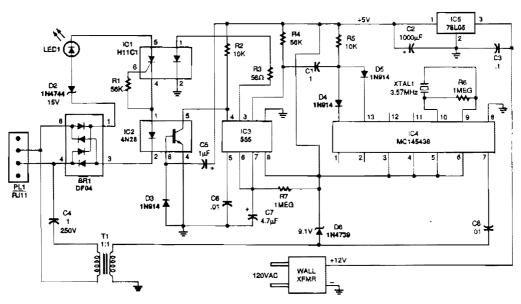


UNIVERSAL TELEPHONE HOLD CIRCUIT

ELECTRONICS NOW

Fig. 90-5

The telephone line is connected to the hold components through bridge rectifier BR1 so that the input is not polarity sensitive. If you have touch-tone telephone service, you can now put a call on hold from any phone in your house by plugging this simple device into any telephone jack. The universal hold circuit works with any phone that has a key pad with a # key. To put a call on hold, press the # key and hang the phone up. A timer extends the #-key function while you hang up phones that have a keypad built into the handset.

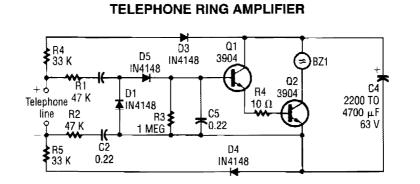


ELECTRONICS NOW

Fig. 90-6

This circuit takes its operating power from the telephone line. BZ1 is a piezoelectric transducer.


BELL SYSTEM 202 DATA ENCODER

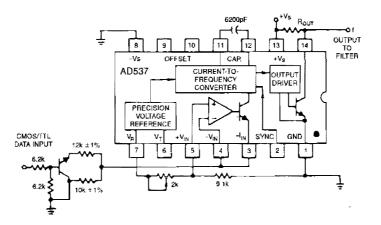

ANALOG DEVICES

Fig. 90-7

The AD537 is well-suited for frequency-shift modulator and demodulator applications. Requiring little power, it is especially appropriate for using phone-line power. The Bell-System 202 data encoder shown here delivers the mark frequency of 1.2 kHz with the data input low. When the input goes high, the timing current increases to 165 μ A and generates the space frequency of 2.2 kHz. The trim shown provides a ±10% range of frequency adjustment. The output goes to the required bandpass filter before transmission over a public telephone line. A complementary demodulator is easy to implement.

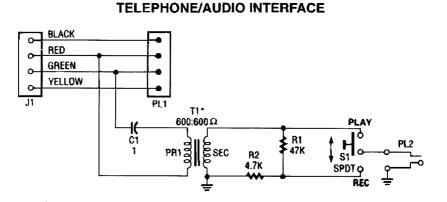


POPULAR ELECTRONICS

The telephone audio interface—essentially, a simple isolation/couple circuit—isolates the phone line from any connected audio circuit without presenting any danger to the phone line, the equipment, or the user.

Fig. 90-8

TELEPHONE RECORDING CIRCUIT

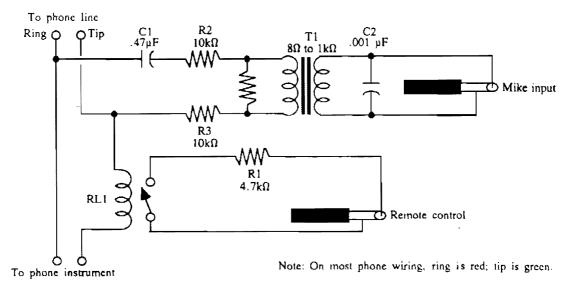


R1	4.7 kΩ
R2,R3	10 kΩ
C1	0.47 µF disc
C2	0.001 µF disc
T1	8 kΩ-to-1 kΩ impedance-matching transformer
RL1	SPST reed relay

All resistors are 5 to 10 percent tolerance, 1/4 watt. All capacitors are 10 to 20 percent tolerance, rated at 35 volts or more.

McGRAW-HILL

Fig. 90-9

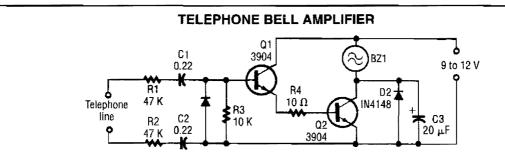
This device will automatically record telephone calls. An ordinary cassette recorder can be hooked to it.



ELECTRONICS NOW

Fig. 90-10

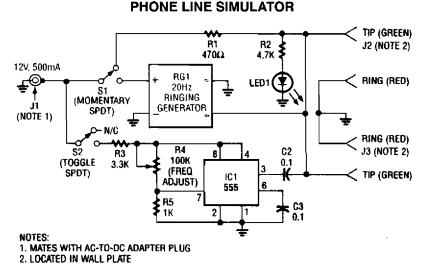
Telephone "bell" amplifier circuit will let you hear (or see) an enhanced alarm if you are away from your telephone.



ELECTRONICS NOW

Flg. 90-11

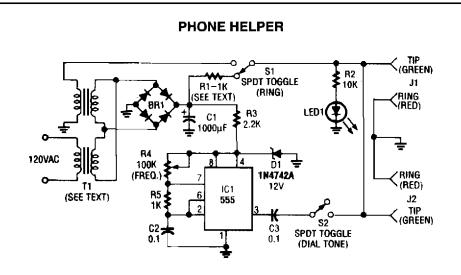This device contains a ringing generator and a tone oscillator. The tone oscillator is set to either 350 or 440 Hz. The ringing generator is a potted module delivering 86 Vac at 20 Hz. It is available from a source listed in the reference.




RADIO-ELECTRONICS

Fig. 90-12

This phone-line simulator uses a 60-Hz transformer instead of a ring generator. The dial tone is provided by an NE555 astable oscillator.

TELEPHONE RING SIGNAL DETECTOR

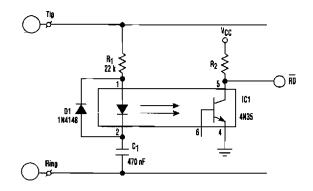

ELECTRONIC DESIGN

Flg. 90-13


Discriminating between telephone-ring signals on a phone line can be accomplished by using dedicated ICs, such as AT&T's LB1006AB or Texas Instruments' TMS1520A. However, if the system already is using a microcontroller, those dedicated chips can be replaced with simpler hardware and a few bytes of code.

Looking at the setup, the ringing voltage pulses the optoisolator's LED; which, in turn, pulses the low-asserted RD line to the microcontroller. The firmware analyzes the pulses to determine whether a valid ringing signal is present.

The frequency limits of a valid signal are 20 to 80 Hz, which is modulated 2 seconds on and 4 seconds off (with distinctive ringing, though, this cadence can vary). Therefore, the simplest analysis is to count down at least 20 pulses of RD in 1 second.

The routine could be expanded to determine what type of ring signal is present in a distinctive ring setting. Such a system could switch the phone line to various output jacks. As a result, several phone devices could use the same line without first picking up the line to determine if it's a voice, fax, or data call.

TELEPHONE HOLD CIRCUIT

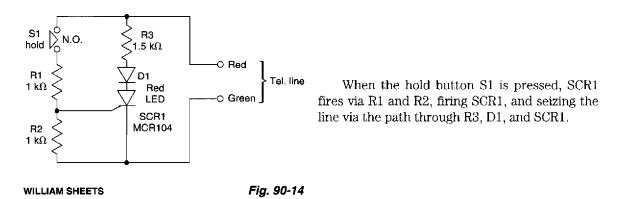


91

Temperature-Related Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Electronic Thermostat Temperature Controller Manual Control for Heater **Proportional Temperature Controller** Eight-Input A/D Converter for Temperature Measurements Cold Junction Compensation for a Grounded Thermocouple Absolute Temperature Log with RS-232 Centigrade Thermometer with Cold-Junction Compensation 1.5-V Electronic Thermometer Two-Wire Temperature Sensor Output Referenced to Ground Two-Wire Remote Temperature Sensor with Sensor Grounded Single-Supply Temperature Sensor (-50 to $+300^{\circ}F$ Basic Fahrenheit Temperature Sensor

Temperature-to-Frequency Converter (Celsius) Temperature-to-Frequency Converter (Kelvin) Differential Thermometer **Optoelectronic** Pyrometer Bar-Graph Room-Temperature Display LM3911 Temperature Controller Thermocouple Amplifier with Cold-Junction Compensation Precision RTD Amplifier Circuit for +5 V Full-Range Fahrenheit Temperature Sensor Improved Thermostatic Relay Circuit Thermocouple Cold-Junction Compensation **Temperature Differential Detector** Thermostatic Relay Application Temperature Controller Temperature-to-Digital-Output Converter Freeze-Up Sensor Zero-Voltage Switching Temperature Regulator

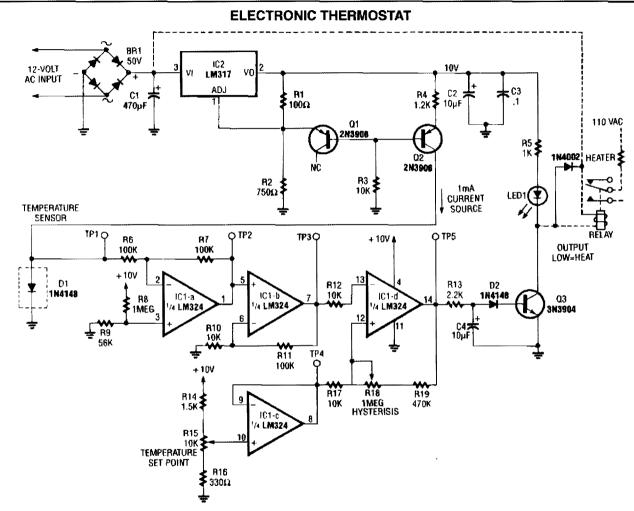


ELECTRONICS EXPERIMENTERS HANDBOOK

Fig. 91-1

Using a 1N914 diode as a temperature sensor, this straightforward circuit has hysteresis and set-point adjustments. Usable range is about -50 to +150 °C.

TEMPERATURE CONTROLLER

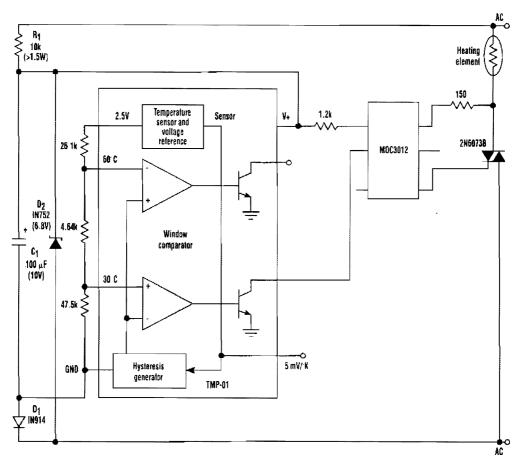

ELECTRONIC DESIGN




The temperature sensor/controller (the TMP-01) is a monolithic device whose low power allows it to operate with a simple half-wave rectified power supply directly from the ac line. Such an arrangement greatly simplifies the power-supply design requirement to the point of only needing a few low-cost components to provide a single +6-Vdc supply.

The TMP-01 is essentially a "thermostat on a chip." It includes a linear temperature sensor (5 mV/K), and also has two comparators that switch at externally determined set points. These set points are established by resistively dividing the internal 2.5-V reference to set appropriate voltages on the inputs to the comparators.

One comparator is used in this circuit to turn on the heating element when the temperature drops below 30°C; it corresponds to a voltage of 1.52 V on the comparator's input.

MANUAL CONTROL FOR HEATER

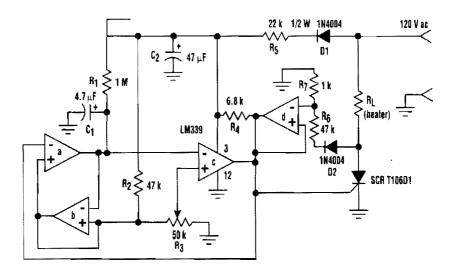

ELECTRONIC DESIGN

Fig. 91-3

Built around an LM339 quad comparator, this circuit provides manual control of the output of a resistive heater or other load with a long time constant. The circuit's design uses minimal parts, thus it's inexpensive, and generates very low RFI.


Comparators a, b, and c form a low-frequency pulse-width modulator. Sections a and b form a sawtooth oscillator (of approximately 0.25 Hz), with capacitor C1 being charged through R1 and discharged through section a's open collector output. R2 and R3 set the upper voltage limit for the sawtooth wave. The hysteresis means that C1 is discharged to nearly 0 V, creating a voltage swing that is identical to the adjustment range of R3.

Comparator c, in conjunction with potentiometer R3, converts the sawtooth wave form to a variable duty-cycle drive for the silicon-controlled rectifier.

Increasing voltage at R3's wiper means increasing the "on" time. Section d holds the SCR gate low if the line voltage is above approximately 3.5 V, preventing turn on at mid-cycle and ensuring low RFI.

The oscillator frequency is roughly determined by $1/0.7R_1C_1$. Resistance R_1 must be greater than $4R_2$ or the oscillator will lock up. Reducing R_2 will increase the lower voltage limit of the sawtooth; increasing it might cause lock-up.

PROPORTIONAL TEMPERATURE CONTROLLER

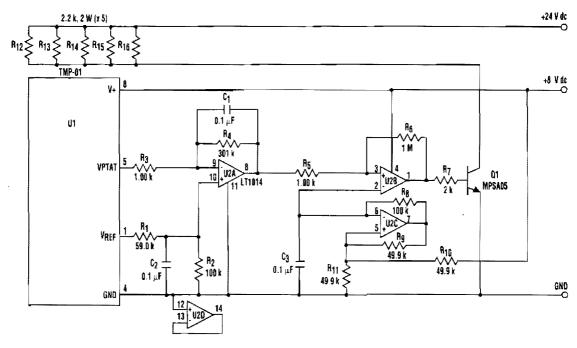

ELECTRONIC DESIGN

Fig. 91-4

Most temperature-controller circuits use upper and lower trip points to control a heater element, with the heater power full on and full off. Usually, this results in a temperature hysteresis of several degrees. This relatively large temperature hysteresis effect might cause modulation in the output of the circuit that's being controlled.


A proportional temperature controller eliminates this problem by continuously providing the power needed to maintain the "oven" at the desired temperature--within 1°C. From a cold start, maximum power is applied until the temperature is within 2°C of the set point.

The circuit's mechanical construction is important. The five heater resistors (R12 through R16), the temperature-sensor IC (U1), and the circuit being controlled are mounted with thermal epoxy to a small piece of aluminum. This provides excellent heat transfer between the components. The heater resistors must be selected to raise the temperature from ambient to the set point within an acceptable warm-up time.

U1 is Analog Devices' TMP-01 temperature-controller IC. The voltage proportional to absolute temperature (VPTAT) has a temperature coefficient of exactly 5 mV/°C. The set point is determined by the R_1/R_2 ratio. U2 is a Linear Technology LT1014 quad precision op amp. U2C is an oscillator with a 50% duty cycle that supplies a triangle wave between $\frac{1}{3}$ and $\frac{3}{3}$ of the supply voltage at U2-2.

U2B compares the amplified VPTAT to the triangle wave, which drives Q1 at a duty cycle of 100% or less. Because the triangle wave's peak-to-peak amplitude is 2.7 V, and VPTAT is amplified by a factor of 300, a temperature change of approximately 2 mV moves the duty cycle from 100% to 0%.

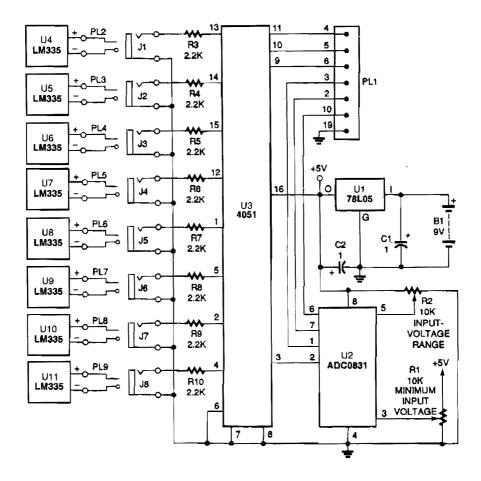EIGHT-INPUT A/D CONVERTER FOR TEMPERATURE MEASUREMENTS




POPULAR ELECTRONICS


Flg. 91-5

The actual processing circuitry of this A/D converter consists of only four parts: U2, U3, R1 and R2. Eight temperature probes are used with the circuit; however, they can be replaced with other types of sensors, as long as resistors R3 through R10 are removed.

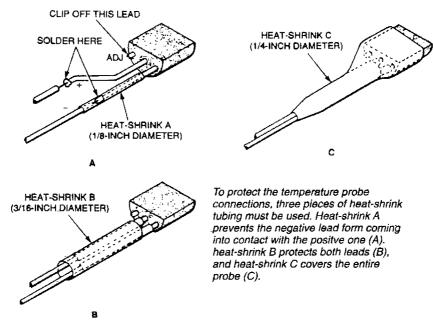EIGHT-INPUT A/D CONVERTER FOR TEMPERATURE MEASUREMENTS (Cont.)



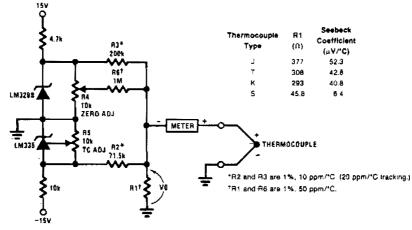COLD-JUNCTION COMPENSATION FOR A GROUNDED THERMOCOUPLE




NATIONAL SEMICONDUCTOR

Fig. 91-6

A circuit for use with grounded thermocouples is shown. To trim, short out the LM329B and adjust R5 so that $V^{\circ} = \alpha T$, where α is the Seebeck coefficient of the thermocouple and T is the absolute temperature. Remove the short and adjust R4 so that V° equals the thermocouple output voltage at ambient. A good grounding system is essential here, for any ground differential will appear in series with the thermocouple output.

ABSOLUTE TEMPERATURE LOG WITH RS-232

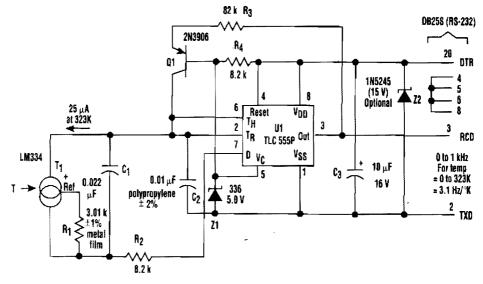

ELECTRONIC DESIGN


Fig. 91-7

In the setup, T1 (an LM334 temperature sensor) generates a constant current that's proportional to absolute temperature, and equal to $25 \,\mu\text{A}$ at 323 Kelvin (50°C). R1 sets this constant of proportionality. The current discharges the parallel combination of C1 and C2 connected to the trigger and the threshold pins of U1, which is a CMOS implementation of the venerable 555 analog timer. The negative-going ramp is compared by U1 to an internal 2.5-V trigger level controlled by Z1. When the ramp gets there, U1 triggers. The output pin (3) will go high, presenting a "start" bit to the connected communications port, which causes Q1 to source 100 μ A to the timing node. At the same time, the discharge pin (7) will open, allowing R2 and the bottom end of C1 and T1 to be supplied by C1, and isolates it from C2.

Consequently, the current supplied by transistor Q1 will go solely to C2 so that when the resulting positive-going ramp reaches 5 V, exactly 25 nC ($2.5 \text{ V} \times C2$) will have been deposited in the timing node by the recharge cycle because its threshold level (6) will have been reached. This causes both the output pin to return to the negative rail, restoring the "marking" condition of the R2-232 interface, and Q1 to stop recharging C2. U1's discharge pin (7) now connects R2 to the negative rail, causing the charge that was deposited by T1 on C1 during the recharge interval to rapidly redistribute between C1 and C2. This arrangement creates a very linear (0.01%) relationship between T1 current and pulse output frequency.

While this is happening, the PC's communications port hardware assembles a valid (although meaningless) character because the positive pulse output by U1 looks like the start bit of a character. A simple program running in the PC can then count the frequency of these characters and convert the resulting rate into a direct readout of temperature. Because of the 3.1-Hz/degree slope of frequency versus temperature, a 30-second average suffices for 0.01° resolution.

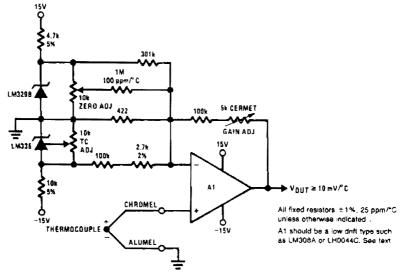
CENTIGRADE THERMOMETER WITH COLD-JUNCTION COMPENSATION




NATIONAL SEMICONDUCTOR

Fig. 91-8

This electronic thermometer has a 10-mV/°C output from 0°C to 1300°C. The trimming procedure is as follows: first short out the LM329B, the LM335 and the thermocouple. Measure the output voltage (equal to the input offset voltage times the voltage gain). Then apply a 50-mV input voltage and adjust the GAIN ADJUST pot until the output voltage is 12.25 V above the previously measured value. Next, short out the thermocouple again and remove the short across the LM335. Adjust the TC ADJUST pot so that the output equals 10 mV/°K times the absolute temperature. Finally, remove the short across the LM329B and adjust the ZERO ADJUST pot so that the output voltage equals 10 mV/°C times the ambient temperature in °C.

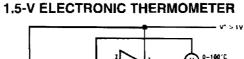


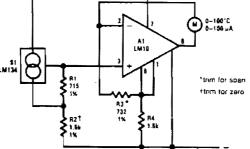


NATIONAL SEMICONDUCTOR

Fig. 91-9

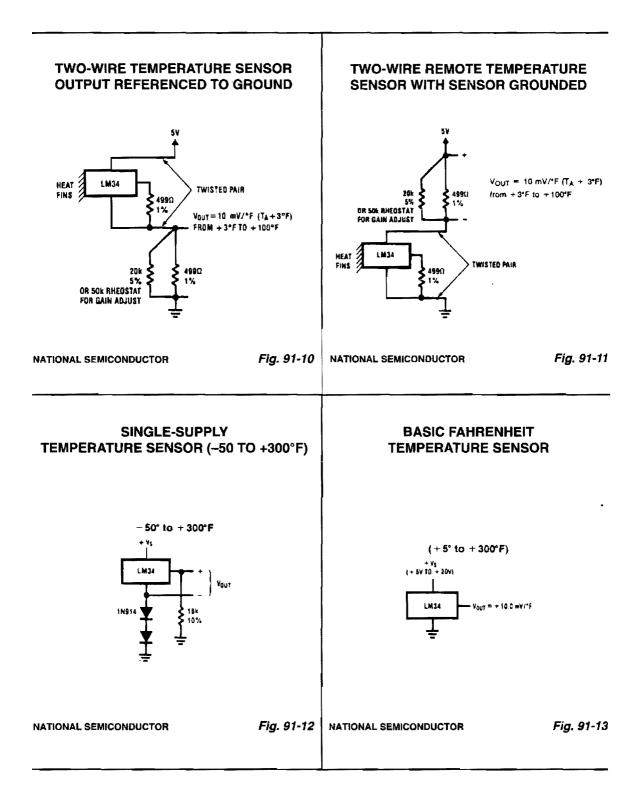An electronic thermometer design, useful in the range of -55° C to 150° C, is shown. The sensor, S1, develops a current that is proportional to absolute temperature. This is given the required offset and range expansion by the reference and op amp, resulting in a direct readout in either °C or °F.



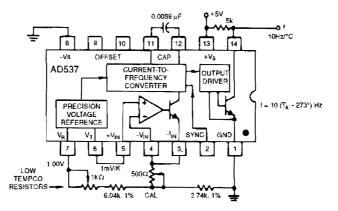


TEMPERATURE-TO-FREQUENCY CONVERTER (CELSIUS)

ANALOG DEVICES

Flg. 91-14

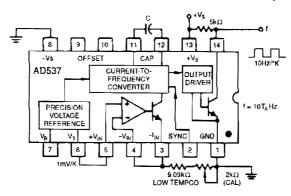The 1.00-V reference output can be combined with the 1-mV/°K output to realize various temperature scales. For the Celsius scale, the lower end of the timing resistor must be offset by 273 mV. This is easily accomplished, and it results in an output from 0 to 1 kHz for temperatures from 0°C to ± 100 °C. Other offsets and scale factors are equally easy to implement.




TEMPERATURE-TO-FREQUENCY CONVERTER (KELVIN)

ANALOG DEVICES

This simple connection results in a direct conversion of temperature to frequency. The 1-mV/°K temperature output serves as the input to the buffer amplifier, and the oscillator drive current is scaled to be 298 μ A at 298°K (+25°C). Use of a 1000-pF capacitor results in a corresponding frequency of 2.98 kHz. A single-point trim for calibration is normally sufficient to give errors less than $\pm 2^{\circ}$ C from -55°C to +125°C. An NPO capacitor is preferred to minimize nonlinearity that results from capacitance drift.

Fig. 91-15


DIFFERENTIAL THERMOMETER

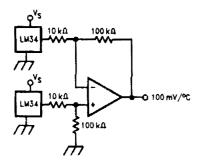

The differential thermometer shown in the figure produces an output voltage which is proportional to the temperature difference between two sensors. This is accomplished by using a difference amplifier to subtract the sensor outputs from one another and then multiplying the difference by a factor of 10 to provide a single-ended output of 100 mV per degree of differential temperature.

NATIONAL SEMICONDUCTOR


Fig. 91-16

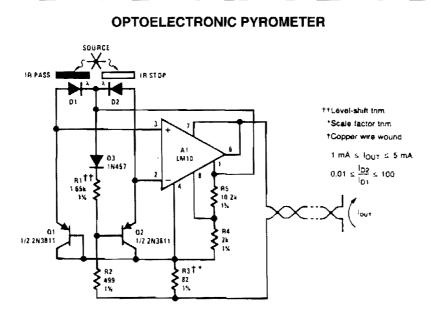

NATIONAL SEMICONDUCTOR

Fig. 91-17

This setup optically measures the temperature of an incandescent body. It makes use of the shift in the emission spectrum of a black body toward shorter wavelengths, as temperature is increased. Optical filters are used to split the emission spectrum, with one photodiode being illuminated by short wavelengths (visible light) and the other by long (infrared). The photocurrents are converted to logarithms by Q1 and Q2. These are subtracted to generate an output that varies as the log of the ratio of the illumination intensifies. Thus, the circuit is sensitive to changes in spectral distribution, but not intensity.

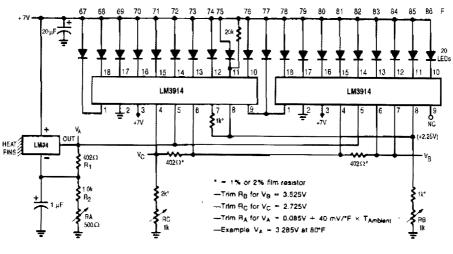


BAR-GRAPH ROOM TEMPERATURE DISPLAY

NATIONAL SEMICONDUCTOR

Fig. 91-18

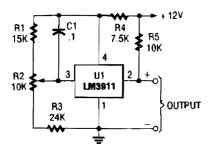This display shows temperature as a bar graph. The range is 67°F to 86°F.





The LM3911 requires only a few resistors and a capacitor to turn into a full-function temperature controller. The LM3911 requires very few external components to implement a fullfunction temperature controller. The figure illustrates the simplicity of the freeze fighter circuit. The resistor network consisting of R1, R2, and R3 is used to provide the set point voltage for the feedback input of the LM3911.


Resistor R4 limits the current through the internal voltage reference of the LM3911 and can be selected from a wide range of values. 7.5 k Ω is specified in most of the application notes.

Resistor R5 pulls the output of the IC high when the temperature is below the set point. The internal resistor is in series with a diode that allows a switching voltage up to 35 V to be used with the device.

POPULAR ELECTRONICS

Fig. 91-19

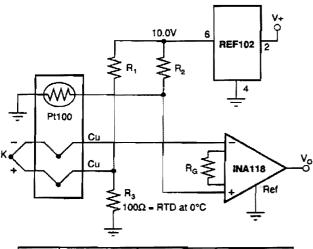THERMOCOUPLE AMPLIFIER WITH COLD-JUNCTION COMPENSATION




ISA TYPE	MATERIAL	SEEBECK COEFFICIENT (µV/°C)	R ₁ , R ₂
E	+ Chromel - Constantan	58.5	66.5kΩ
J	+ Iron - Constantan	50.2	76.8kΩ
к	+ Chromei - Alumei	39.4	97.6kΩ
Т	+ Copper - Constantan	38.0	102kΩ

DESIRED	R.	NEAREST 1% R _g
GAIN	(Ω)	(Ω)
1	NC	NC
2	50.00k	49.9k
5	12.50k	12.4k
10	5.556k	5.62k
20	2.632k	2.61k
50	1.02k	1.02k
100	505.1	511
200	251.3	249
500	100.2	100
1000	50.05	49.9
2000	25.01	24.9
5000	10.00	10
10000	5.001	4.99

BURR-BROWN

Fig. 91-20

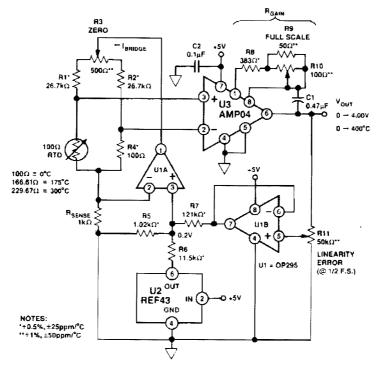


PRECISION RTD AMPLIFIER CIRCUIT FOR +5 V


ANALOG DEVICES

Fig. 91-21

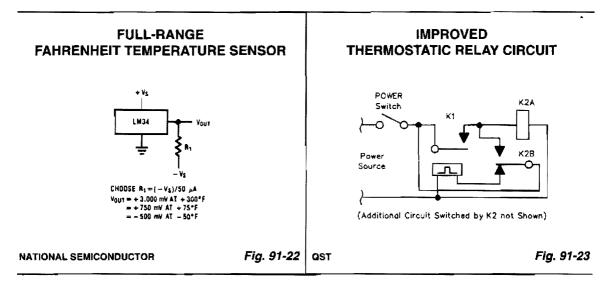This circuit uses a platinum resistance temperature device to sense temperature. It has a range of 0 to 300°C. The RTD bridge is driven with a regulated 200- μ A current to minimize self heating of the RTD. A 5-V supply is used.



THERMOCOUPLE COLD-JUNCTION COMPENSATION

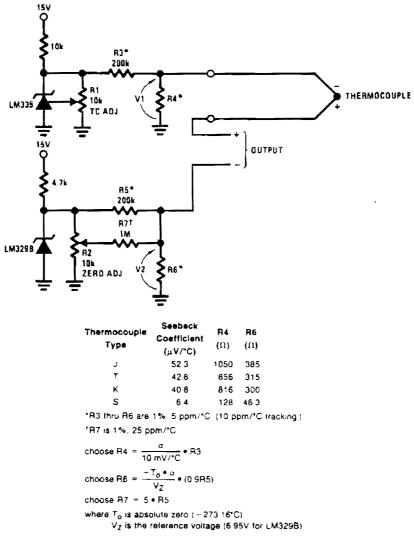


NATIONAL SEMICONDUCTOR

Fig. 91-24

A single-supply circuit is shown. R3 and R4 divide down the 10-mV/°K output of the LM329B and its associated voltage divider provide a voltage to buck out the 0°C output of the LM335. To calibrate, adjust R_1 so that $V_1 = \alpha T$, where α is the Seebeck coefficient and T is the ambient temperature in degrees Kelvin. Then, adjust R_2 so that $V_1 - V_2$ is equal to the thermocouple output voltage at the known ambient temperature.

TEMPERATURE DIFFERENTIAL DETECTOR

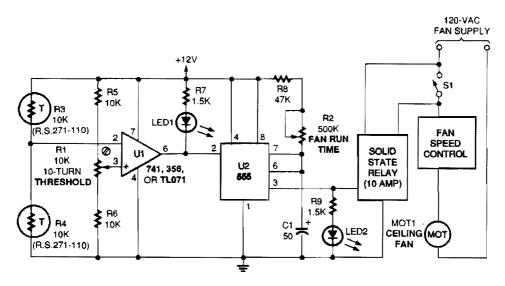


POPULAR ELECTRONICS

Fig. 91-25

This circuit measures temperature differences, not temperature. Once the difference passes a certain threshold, the timer is triggered, activating the solid-state relay.

Op amp U1 is placed in a comparator configuration with two thermistors—one located at the ceiling, one at the floor. The IC senses the temperature difference between the ceiling and floor, but is unaffected by the overall room temperature differential increases. The upper thermistor will decrease in resistance, eventually causing the voltage at pin 2 of U1 to exceed that pin 2 of U1 to go low and trip the timer. This adds hysteresis to the op amp's output, preventing the motor from chattering. When tripped, the timer activates the relay, which activates the fan.




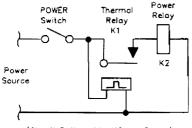

(Circuit Switched by K2 not Shown)

K1, the thermostatic relay, energizes power relay K2, which handles the circuit's power switching. The drawing doesn't show K2's powerswitching contacts.


TEMPERATURE CONTROLLER

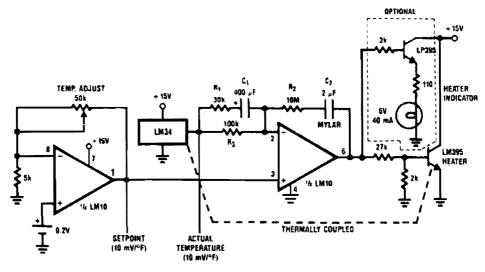

NATIONAL SEMICONDUCTOR

Fig. 91-27

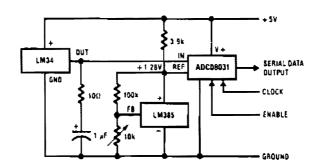A proportional temperature controller can be made with an LM34 and a few additional parts. The complete circuit is shown. Here, an LM10 serves as both a temperature-setting device and as a driver for the heating unit (an LM395 power transistor). The optional lamp, driven by an LP395 transistor, is for indicating whether or not power is being applied to the heater.




TEMPERATURE-TO-DIGITAL-OUTPUT CONVERTER

NATIONAL SEMICONDUCTOR

Fig. 91-28

FREEZE-UP SENSOR

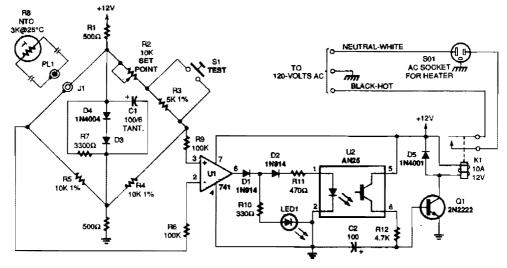


POPULAR ELECTRONICS

Fig. 91-29

Using a bridge circuit to provide an accurate activation temperature, this circuit will turn on a heating unit or other device when the temperature drops below the trip point set by R2. Use a 10-k Ω resistor in place of the thermistor to calibrate it for 32°F activation.

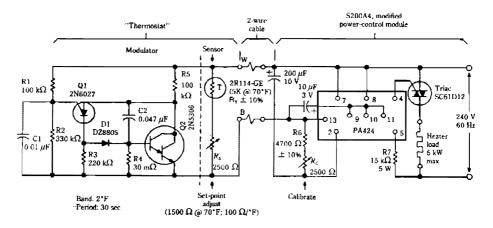ZERO-VOLTAGE SWITCHING TEMPERATURE REGULATOR



McGRAW-HILL

Fig. 91-30


In this arrangement, an integral number of cycles of ac is fed to the heater. No RFI or EMI is generated with this method. The thermostat uses a thermistor as a sensor. The PA424 (GE) device generates trigger pulses for the triac only at zero crossings of the ac line cycle.

Timer Circuits

 T_{he} sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Alarm Clock Timer Lamp Timer Long-Period Timer


ALARM CLOCK TIMER

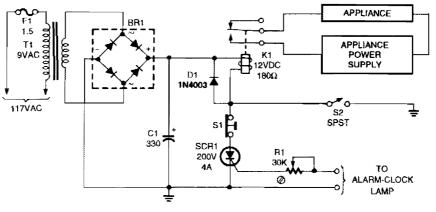

POPULAR ELECTRONICS

Fig. 92-1

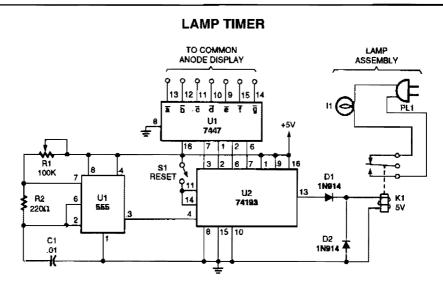Turn your alarm clock into a specialized timer with this simple circuit. The clock used with the circuit should be the kind that turns on a little lamp when the alarm is activated.




POPULAR ELECTRONICS

Fig. 92-2

A timed switch uses a 555 oscillator/timer wired to operate in the astable mode. The timer supplies a positive pulse to the clock input of a 74193 4-bit binary up/down count every five minutes. Because the 74193 is set to operate in the count-down mode, the output of the 555 is connected to the count-down input of the 74193.

As the binary counter is reset, it starts counting at nine and counts down to zero with each clock pulse. When the counter hits zero, the output from the 74193 goes low, turning off the relay and the light. The light can be turned back on by pressing the reset button again.

LONG-PERIOD TIMER

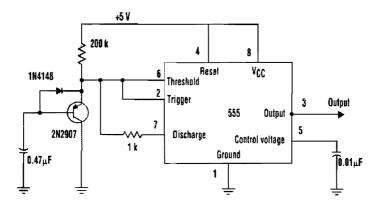

ELECTRONIC DESIGN

Fig. 92-3

Adding a transistor to the 555 timer can create long timer periods, which is a key factor when the timer is operating at low speed. The transistor basically acts as a current divider or capacitance multiplier. The problem with low speed, however, is that the timing resistors and capacitors must be large and the charging current must be small, particularly when the desired timing period is in the range of seconds.

Typically, electrolytic capacitors are used in these situations, but their leakage current tends to aggravate or even prohibit operation at very low charging currents.

This problem can be solved by adding a transistor. In effect, the transistor is used as a current divider or a capacitance multiplier. The normal charging current (emitter current) is divided by the transistor's current gain so that the capacitor charging current (base current) is reduced considerably. For example, $10 \,\mu\text{A}$ of emitter current will require approximately 0.1 μA of base current, based on a current gain of 100.

In this circuit, the capacitor will be charged with such a low charging current that timing periods will typically be 100 times longer than usual. This means that substantial time periods can be achieved with film or ceramic capacitors that have much better leakage characteristics and are physically smaller.


The circuit's output period was approximately 6 seconds, compared to 80 ms without the transistor. The transistor multiplied the normal time period by a factor of approximately 75.

Tone Control Circuits

 T_{he} sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Treble-Control Circuit Bass Tone-Control Circuit Combined Bass and Treble Control Active Bass- and Treble-Tone Control

TREBLE-CONTROL CIRCUIT

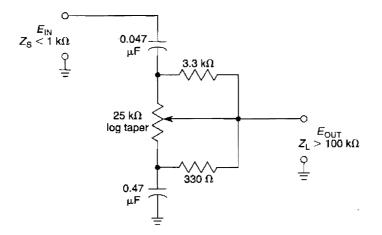


WILLIAM SHEETS

Fig. 93-1

This tone control has an insertion loss of 20 dB at flat setting and is effective above 1 kHz. It has little effect below about 1 kHz.


BASS TONE-CONTROL CIRCUIT

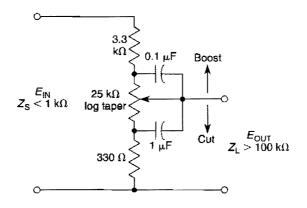

WILLIAM SHEETS

Fig. 93-2

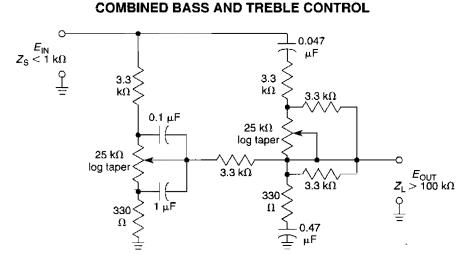
This tone control has an insertion loss of 20 dB at flat setting and is effective below 350 Hz. The control has little effect above this frequency.



WILLIAM SHEETS

Fig. 93-3

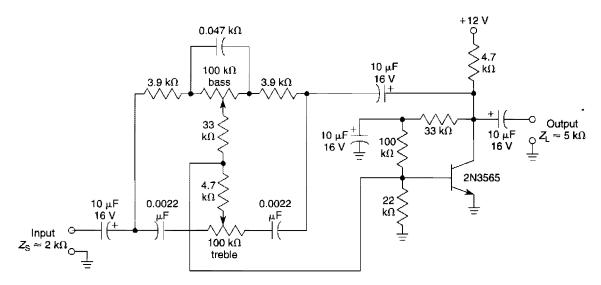This positive tone control system uses two pots to control bass and treble.



ACTIVE BASS- AND TREBLE-TONE CONTROL

WILLIAM SHEETS

Fig. 93-4


A single transistor used as a feedback amplifier is connected with ac feedback through the tone controls, which determine the frequency response of the stage.

Touch/Proximity Control Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.


Simple Touch Switch Simple Timed Touch Switch Capacitive Sensor System Touch Switch Proximity Alarm

SIMPLE TOUCH SWITCH

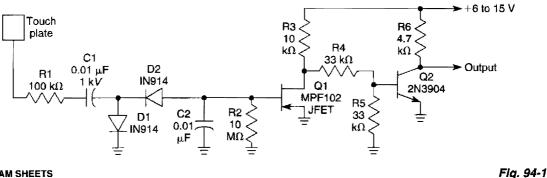

WILLIAM SHEETS

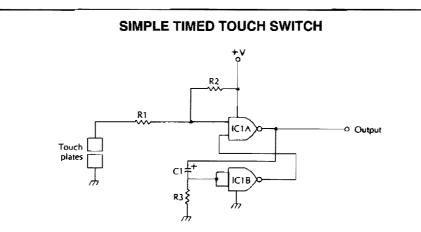Q2 is held cut off since Q1 normally is conducting. When the touch plate is contacted by a large object (human body, etc.), stray 60-Hz pickup is rectified by D1 and D2, and produces a negative voltage across R2-C2 and the gate of Q1. Q1 cuts off, causes Q2 to conduct, and the output goes low.




McGRAW-HILL

Fig. 94-2

This circuit produces an output for a time approximately equal to time constant R_3C_1 .

IC1, IC2	CD4011 quad NAND gate
IC3	CD4066 quad bilateral switch
C1	47-μF, 25-V electrolytic capacitor
C2	100-µF, 25-V electrolytic capacitor
C3	220-µF, 25-V electrolytic capacitor
C4	470-µF, 25-V electrolytic capacitor
C5, C6, C7	0.1-µF capacitor
R1, R3, R4, R6	100-k Ω , ¼-W 5% resistor
R7, R9, R10, R12	
R2, R5, R8, R11	10 -M Ω , ¼-W 5% resistor

CAPACITIVE SENSOR SYSTEM

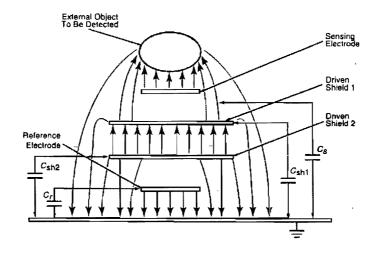

NASA TECH BRIEFS

Fig. 94-3

This figure illustrates the electric-field configuration of a capacitive proximity sensor of the "capaciflector" type. It includes a sensing electrode driven by an alternating voltage, which gives rise to an electric field in the vicinity of the electrode; an object that enters the electric field can be detected by its effect on the capacitance between the sensing electrode and electrical ground.

Also, it includes a shielding electrode (in this case, driven shield 1), which is excited via a voltage follower at the same voltage as that applied to the sensing electrode to concentrate more of the electric outward from the sensing electrode, increasing the sensitivity and range of the sensor. Because the shielding electrode is driven via a voltage follower, it does not present a significant electrical load to the source of the alternating voltage.


In this case, the layered electrode structure also includes a reference electrode adjacent to ground, plus a second shielding electrode (driven shield 2), which is excited via a voltage follower at the same voltage as that applied to the reference electrode. Driven shield 2 isolates the reference electrode from the electric field generated by driven shield 1 and the sensing electrode so that a nearby object exerts no capacitive effect on the reference electrode.

The excitation is supplied by a crystal-controlled oscillator and applied to the sensing and reference electrodes via a bridge circuit. Fixed capacitors C1 and C2 (or, alternatively, fixed resistors R1 and R2) are chosen to balance the bridge; that is, to make the magnitude of the voltage at sensing-electrode node S equal the magnitude of the voltage at reference-electrode node R.

The voltages at S and R are peak-detected and fed to a differential amplifier, which puts out voltage $V_{\rm u}$ proportional to the difference between them. When no object intrudes into the electric field of the sensing electrode, the bridge remains in balance, and $V_{\rm u} = 0$. When an object intrudes, it changes $C_{\rm s}$, unbalances the bridge, and causes $V_{\rm u}$ to differ from zero. The closer the object comes to the sensing electrode, the larger $(V_{\rm u})$ becomes.

An additional output voltage KV_r is available, where K is the amplification and V_r is the voltage on the reference electrode.

TOUCH SWITCH

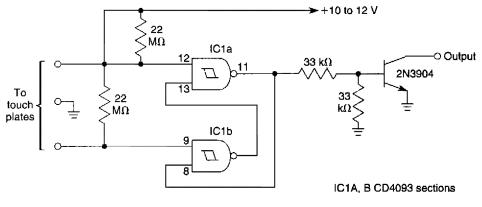


WILLIAM SHEETS

Fig. 94-4

Two NAND Schmitt triggers are used as a flip-flop to produce a bridged touch switch.

PROXIMITY ALARM

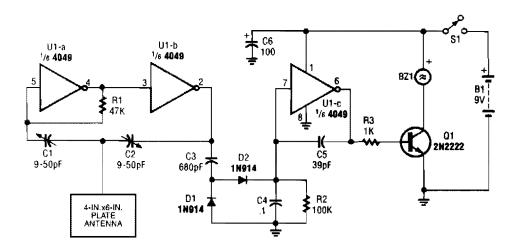

POPULAR ELECTRONICS


Fig. 94-5

Tracer Circuits

 $T_{\rm he}$ sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Wire Tracer Cable Tracer Signal Tracer

WIRE TRACER

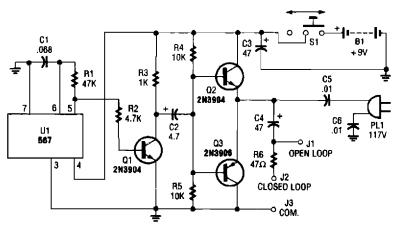


At the heart of the McTrak is a 567 tone decoder, configured as a simple squarewave oscillator, operating at about 250 Hz.

ELECTRONICS HOBBYIST HANDBOOK

Fig. 95-1

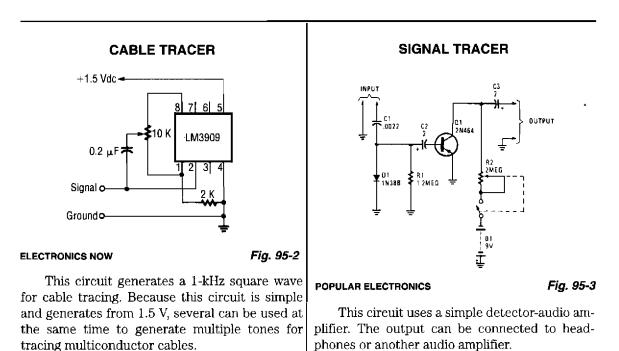This tracer works by placing a square-wave signal on the line to be traced. The square wave is rich in harmonics. A small transistor radio placed close to a wire carrying this signal will buzz. The radio, therefore, is used as a probe to trace out the wire.




Transmitter and Transceiver Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Wireless Guitar Transmitter Micro TV Transmitter Wireless Microphone FM Stereo Transmitter FM Bug Low-Power VHF Beacon Transmitter Low-Cost 6-W, 40-M CW Transmitter

WIRELESS GUITAR TRANSMITTER

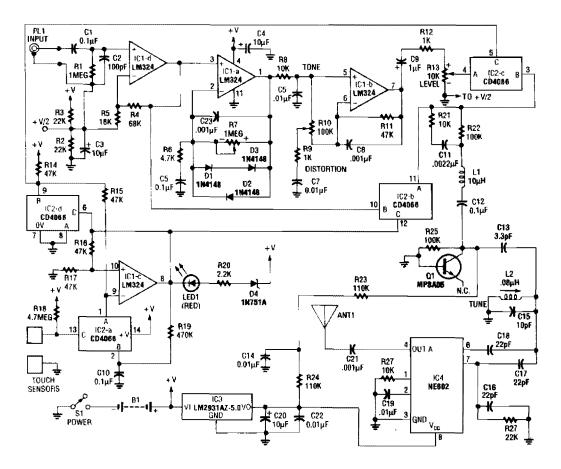


ELECTRONICS NOW

Fig. 96-1

This transmitter has a built-in distortion effects unit and a touch switch to switch effects off and on. The circuit operates from a 9-V battery. IC1-a and IC1-b are used in the effects circuitry. IC1-d is an input preamp and IC2 is a quad analog switch to handle audio switching. Q1 acts as a varactor, diode modulator while IC-4 is an 88- to 108-MHz FM oscillator.

MICRO TV TRANSMITTER

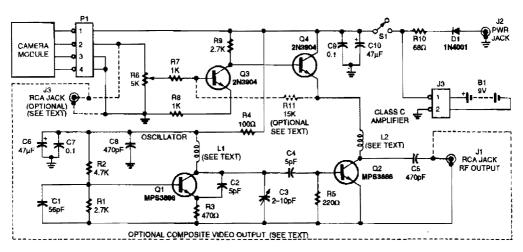


ELECTRONICS NOW

Fig. 96-2

For very low power, noncritical applications, this small TV modulator can be useful as a short-range (50 feet) transmitter for video signals. A small camera module can be used as a source. R11 is used to vary dc offset of the modulator.


WIRELESS MICROPHONE

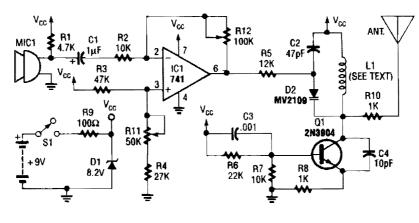

ELECTRONICS EXPERIMENTERS HANDBOOK

Fig. 96-3

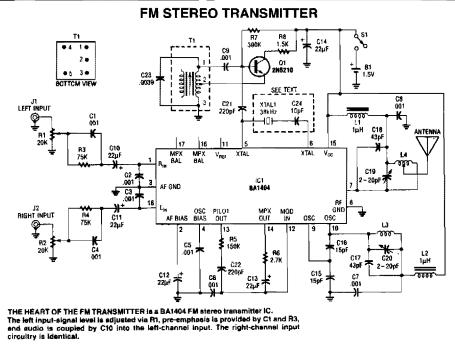
An op-amp IC (741) amplifies the audio signal from MIC1, and R12 controls its gain. Audio is fed to the oscillator circuit Q1 and related components. D2 is a varactor diode. Audio fed to D2 causes FM of the oscillator signal. L1 is 2% turns of #18 wire on a %" diameter form. The antenna is a 12" whip.




ELECTRONICS NOW

Flg. 96-4

An FM stereo transmitter can be built around the BA1404 IC. This IC has all the functions nccessary to generate an FM MPX signal. A separator oscillator circuit uses a 2N5210 transistor instead of the difficult-to-find 38-kHz crystal that is normally used. T1 is a 455-kHz IF transformer with $0.0039-\mu$ F capacitance added across it to enable tuning to 38 kHz. With this circuit, oscillator stability should be adequate.

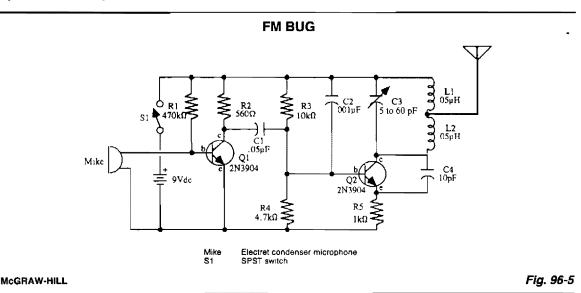



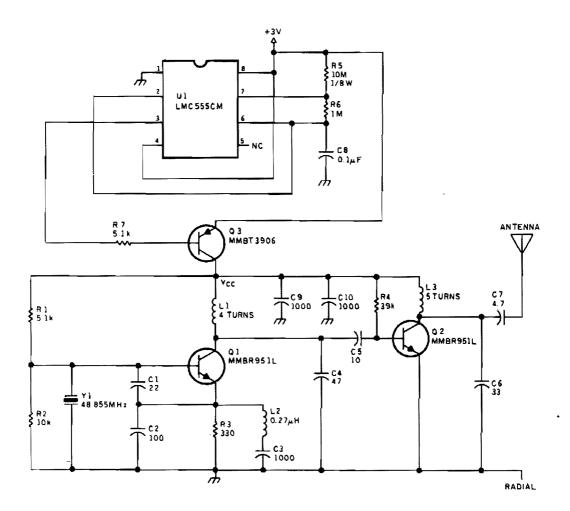


73 AMATEUR RADIO TODAY

Fig. 96-6

A crystal oscillator and tripler make up the low power beacon transmitter. U1 generates a pulse that keys the transmitter at a 10:1 duty cycle (100 ms on, 1 s off) to conserve battery power. This transmitter was used as a locator beacon.

LOW-COST 6-W, 40-M CW TRANSMITTER

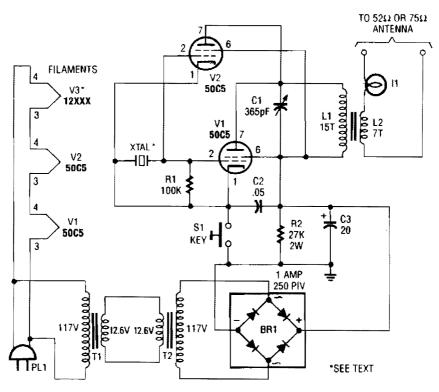

POPULAR ELECTRONICS

Fig. 96-7


.

L1 and L2 are wound on a %" diameter form. L1 is 15 turns #22 plastic-covered wire, and L2 is 7 turns #22 plastic-covered wire.

Ultrasonic Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

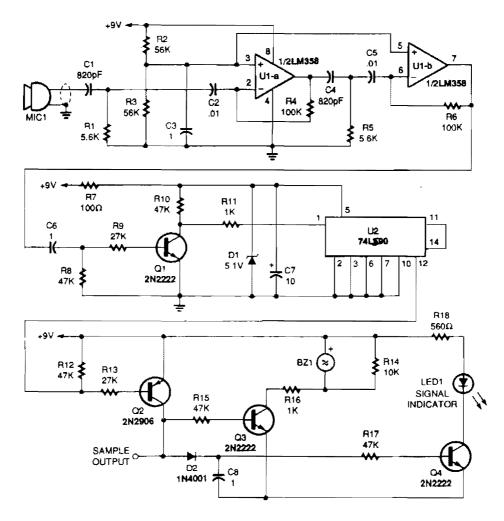Ultrasonic Remote-Control Tester Ultrasonic Motion Detector Ultrasonic CW Transceiver Ultrasonic Proximity Sensor Simple Ultrasonic Generator Ultrasonic Sound Receiver




ULTRASONIC REMOTE-CONTROL TESTER

POPULAR ELECTRONICS

Flg. 97-i

This circuit picks up the ultrasonic tone via MIC1, amplifies it, and divides it by 10 in IC U2, a 74LS90. The output of U2 drives an audio amplifier and a piezoelectric element is used as a speaker.

ULTRASONIC MOTION DETECTOR

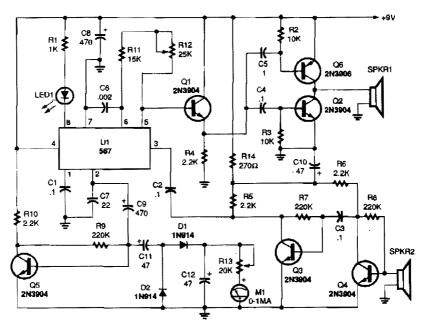

POPULAR ELECTRONICS

Fig. 97-2

A 567 PLL IC operates in a dual-function mode as a signal generator and an FM receiver. The 567's square-wave output at pin 5 is coupled to the base of Q1, and from Q1's emitter to the input of the power amplifier (Q2 and Q6). The output drives the piezo speaker, SPKR1.

The receive portion of the circuit operates as follows: transistors Q3 and Q4 are connected in a two-stage, high-gain, audio-frequency amplifier circuit, with the input connected to a second piezo speaker (SPKR2) operating as a sensitive microphone. The amplifier's output is coupled to the 567's input at pin 3. When an in-band signal is received, the LED lights.


The 567's FM output is coupled from pin 2 to the input of a very-low-frequency single-transistor amplifier, Q5. The amplifier's output at Q5's collector drives a voltage-doubler circuit (C11, D1, D2, and C12). The dc output feeds a 0- to 1-mA analog meter.

By placing the two piezo speakers one foot apart and aiming them in the same direction, toward a nonmoving solid object, the signal from the transmitter's speaker will reflect back into the receiver's speaker, and the frequency at the 567's input will be the same as the one being transmitted.

The ac output at pin 2 is zero when the outgoing and incoming frequencies are the same. However, when the signal is reflected from a moving object, the received frequency will be either lower or higher than the transmitted one. If the object is moving away from the speakers, the received frequency will be lower; if the object is moving toward the speakers, the frequency will be higher.

The pin-2 signal is fed through a 470- μ F capacitor to the base of Q5, where the signal is amplified and fed to a voltage doubler, and then on to a meter circuit.

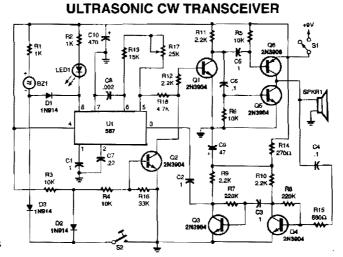
If you wish, the voltage doubler and meter can be removed and replaced with headphones connected between the negative side of C11 and circuit ground. That will allow you to listen to the difference-frequency signal as objects move in front of the speakers.



POPULAR ELECTRONICS

With the telegraph key at S2 "up" (open), the 567 PLL's input at pin 3 is coupled to the output of Q3. Transistors Q3 and Q4 are operating in a high-gain, two-stage audio-amplifier circuit. The piezo speaker is coupled to the input of the amplifier though a 0.1-µF capacitor and a 680- Ω isolation resistor.

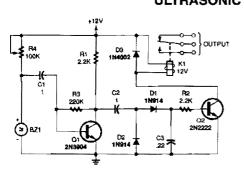In the receive mode, the piczo speaker operates as a sensitive microphone. Ultrasonic signals travel from the microphone through the two-stage amplifier to the input of the 567, and, if the signal's frequency is within the IC's bandwidth, the LED will light and piezo-sounder BZ1 will sing out for



POPULAR ELECTRONICS

Fig. 97-4

A 100-k Ω potentiometer, R4, sets the current fed to the Sonalert sounder. The potentiometer is adjusted to a point where the sounder

each "dit" and "dah" received. The receiver can be tuned to the incoming ultrasonic signal by adjusting R17. Of course, adjusting that potentiometer also changes the transmitter's frequency.


The transmitter operates each time the S2 is closed. When the key is closed, diode D3 supplies a path to ground for BZ1, causing that sounder to produce an audible signal for each "dit" and "dah" transmitted. Also, Q2's bias is taken to ground through D2, allowing Q1 to pass the 567's squarewave signal on to the input of the power amplifier and out through the speaker.

ULTRASONIC PROXIMITY SENSOR just begins to make an audible sound. A singletransistor audio amplifier (Q1) is coupled to the positive side of the sounder and its output is fed to a voltage-doubler circuit. The doubler's dc output drives the base of Q2, which, in turn, operates the relay (K1). As long as the Sonalert is producing a sound, the relay stays energized.

When a solid object is moved in close proximity to the front of the sounder, the Q of the piezo element is lowered and the Sonalert's internal circuit ceases to operate; as a result, the relay drops out. By carefully adjusting R4, the circuit can be made quite sensitive.

Fig. 97-3


SIMPLE ULTRASONIC GENERATOR

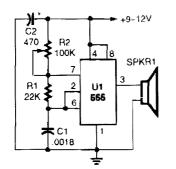

This basic ultrasonic generator can be built easily and quickly. An NE555 drives a speaker. The frequency range is 12 to 50 kHz. SPKR1 is a piezo tweeter, etc.

POPULAR ELECTRONICS



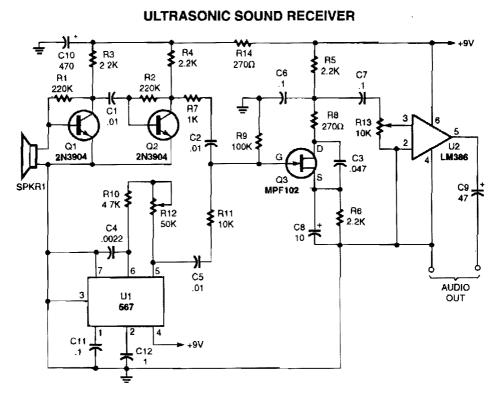

POPULAR ELECTRONICS

Fig. 97-6


You won't be disappointed with the performance of this sensitive ultrasonic receiver. It can let you listen to bugs, bats, engines, and virtually any other source of ultrasonic sounds. This circuit uses a piezo tweeter as an ultrasonic microphone, amplifier stages Q1, Q2, and an LO using a 567 IC. Q3 is a mixer that heterodynes the ultrasonic sounds down to the audible range. U2 is an amplifier that will drive a pair of headphones.

Video Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Video Titler Video Amplifier **RGB Video Amplifier** One-of-Two Video Selector NTSC-to-RGB Converter Video IF Amplifier/Detector Video Cable Driver Simple NTSC Gray-Scale Video Generator LM1201 Video Amplifier Simple Video Gray-Scale Generator European Line Standard Video Switch Adjustable Video-Cable Equalizer Video Summing Amplifier Video Amplifier Twisted-Pair Video Driver/Receiver Circuit 250-mA 60-MHz Current-Feedback Amplifier for Video Applications Video Driver/Amplifier Video Line Driver

VIDEO TITLER

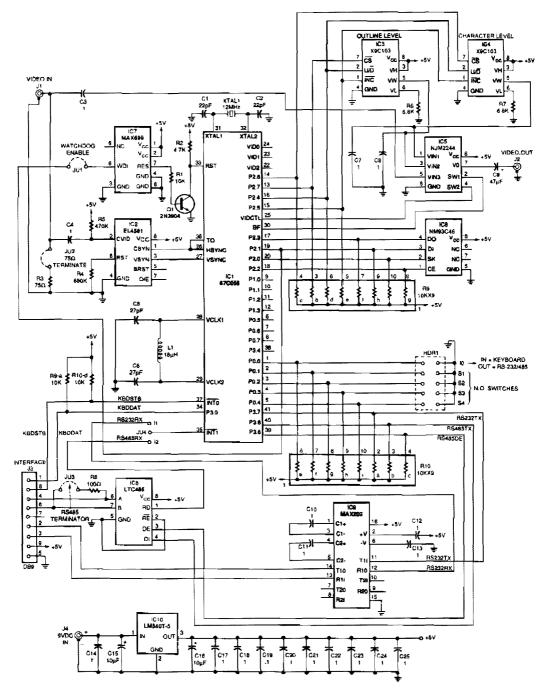


ELECTRONICS NOW!

Fig. 98-1

VIDEO TITLER (Cont.)

IBM PC/AT RS232 SERIAL CABLE

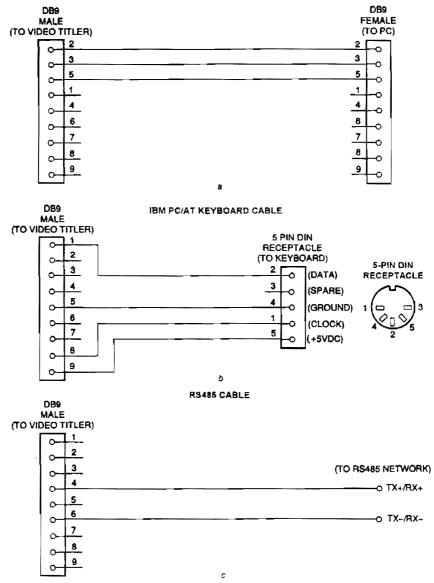

There is a different cable for each interface. The RS-232 serial cable is shown in a, the PC/AT keyboard cable is shown in b, and the RS-485 cable is shown in c.

VIDEO TITLER (Cont.)


The figure shows the schematic of the video titler circuit. The power-on reset function is generated by IC7, a Maxim MAX699 reset, and watchdog pulse generator. That device supplies a reset pulse of 140 to 500 ms at power-up. This is accomplished with some external parts, as well as the OSD controller in IC1. First, the horizontal and vertical sync from the composite video input is detected by IC2, which is set for NTSC specification horizontal and vertical synchronization timing via resistor R4.

The detected horizontal and vertical sync is fed to IC1. The OSC controller in IC1 uses these signals to internally synchronize the overlay text to the incoming video. The frequency of the dot clock is controlled by components L1, C5, and C6. Text is overlaid by video multiplexer IC5, which is controlled by IC1.

The overlay character outline and intensity are controlled via solid-state potentiometers, allowing the microcontroller to control the position of their wipers and store the settings in an onboard EEPROM. The microcontroller's OSC logic controls the multiplexer timing from the BF (IC1, pin 30) and VIDCTL (IC1, pin 25) signals. The BF signal switches the video multiplexer between character and character-outline video, and VIDCTL switches the multiplexer between the input video and the overlay video from IC1. The dc levels from IC3 and IC4 set the character and outline intensity, and these levels are fed to video multiplexer IC5.

The video titler can store and recall text from EEPROM IC6, which has enough capacity to store one overlay screen and other required data, such as network address, horizontal and vertical overlay fine position, and type of interface.

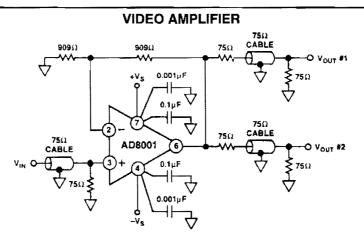The RS-232 interface is provided by a MAX202 transceiver. The RS-485 interface is provided by an LTC485 transceiver that provides both transmit and receive functions. The keyboard interface is basically a direct connection to the microprocessor.




ANALOG DEVICES

Fig. 98-2

The AD8001 has been designed to offer outstanding performance as a video line driver. The important specification of differential gain (0.01%) and differential phase (0.025°) meet the most exacting HDTV demands for driving one video load. The AD8001 also drives up to two back-terminated loads with equally impressive performance (0.01%, 0.07°). Another important consideration is isolation between loads in a multiple-load application. The AD8001 has more than 40 dB of isolation at 5 MHz when driving two 75- Ω terminated loads.


RGB VIDEO AMPLIFIER

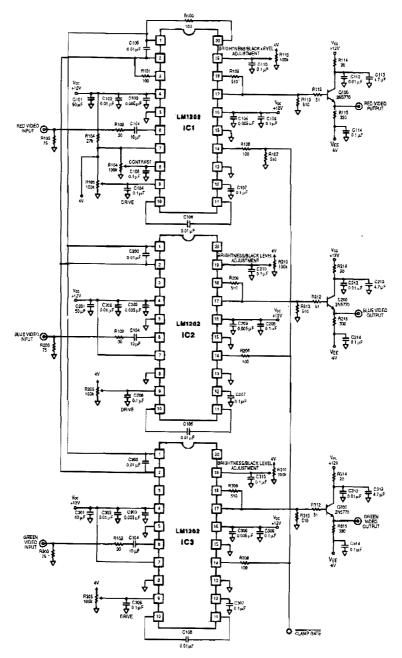

NATIONAL SEMICONDUCTOR


Fig. 98-3

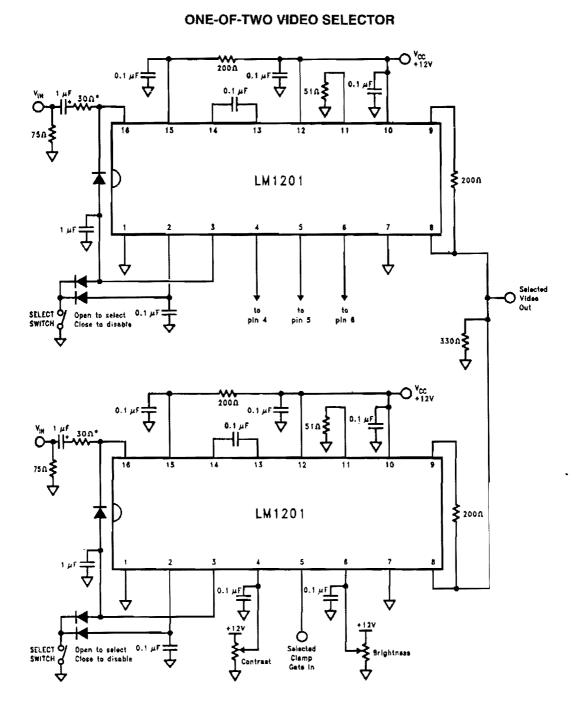This circuit is a three-channel RGB video amplifier with individual brightness, black level and drive controls.



NATIONAL SEMICONDUCTOR

NTSC-TO-RGB CONVERTER

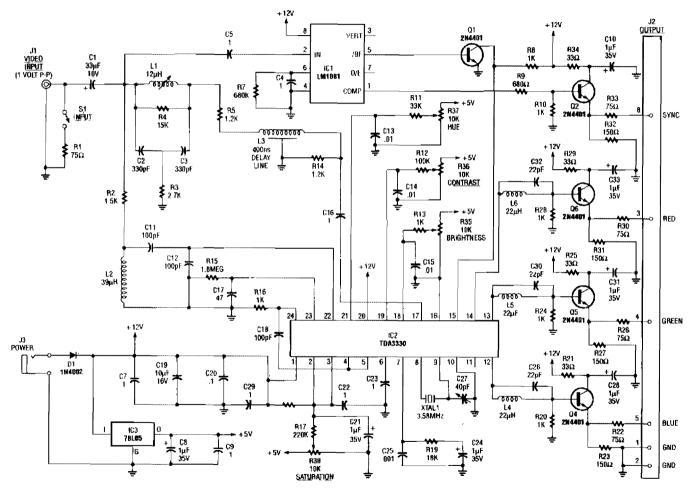



RADIO-ELECTRONICS

Fig. 98-5

This circuit takes baseband NTSC video, decodes it, and derives RGB video suitable for driving a color multisync computer monitor. This enables the user to take advantage of the generally better resolution of computer monitors.

VIDEO IF AMPLIFIER/DETECTOR

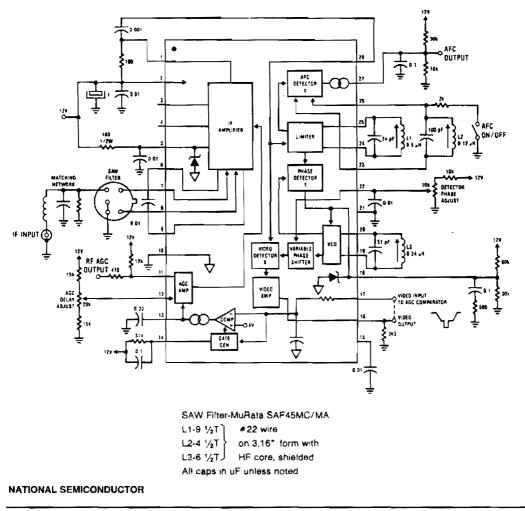

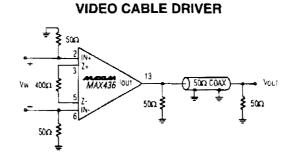


MAXIM

This is a MAX436 coaxial-cable driving circuit.

Fig. 98-6


Fig. 98-7

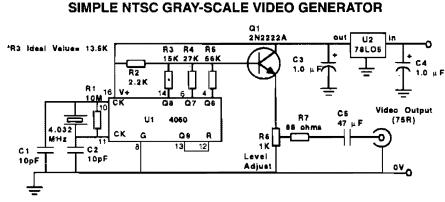

73 AMATEUR RADIO TODAY

Fig. 98-8

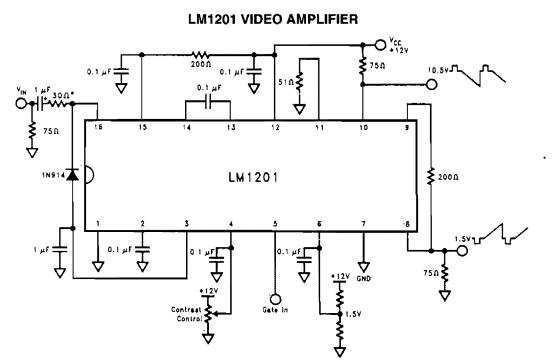A 4.032-MHz crystal oscillator ($256 \times horizontal line scan rate$) drives a BCD counter. The binary outputs of the counter are fed to R2 through R5, a simple weighting network for D/A conversion, resulting in a staircase video output with a rep rate of 15.75 kHz. This circuit should be useful for amateur TV linearity testing and setup purposes.




NATIONAL SEMICONDUCTOR

This video amplifier has $75-\Omega$ bi-phase outputs.

Fig. 98-9

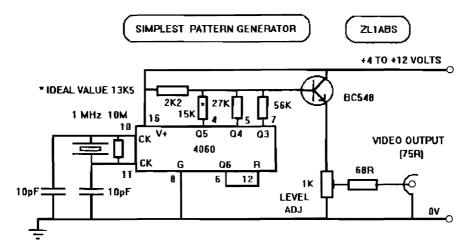
SIMPLE VIDEO GRAY-SCALE GENERATOR EUROPEAN LINE STANDARD



73 AMATEUR RADIO TODAY

Fig. 98-10

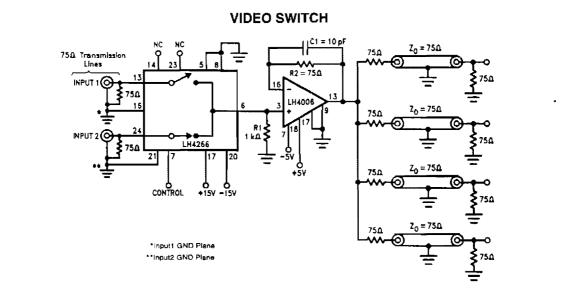
A simple gray-scale generator (staircase waveform) can be obtained with a CD4060 counter, a 1-MHz crystal oscillator, and several resistors to act as an elementary D/A converter to convert the binary count output to analog equivalent. This circuit is for European (PAL) standards.



NATIONAL SEMICONDUCTOR


Fig. 98-11

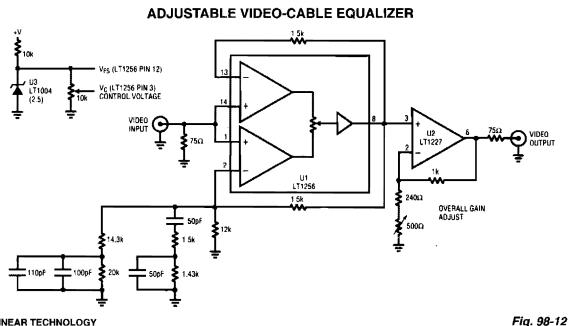Using National Semiconductor LH4266 and LH4006, this circuit switches one of two inputs to four output (75 Ω) lines.




LINEAR TECHNOLOGY

The figure is a complete schematic of the cable equalizer. The LT1256 (U1) is a two-input/oneoutput 40-MHz current feedback amplifier with a linear control circuit that sets the amount that each input contributes to the output. One amplifier (input pins 13 and 14) of the LT1256 is configured as a gain of one with no frequency equalization. The other amplifier (input pins 1 and 2) has frequency equalizing components in parallel with the 12-k Ω gain resistor. An additional amplifier (U2, LT1227) is used to set the overall gain. Two amplifiers were used here to make setting the gain a single adjustment, but in a production circuit, the LT1256 can be configured to have the necessary gain and the whole function can be done with one chip.

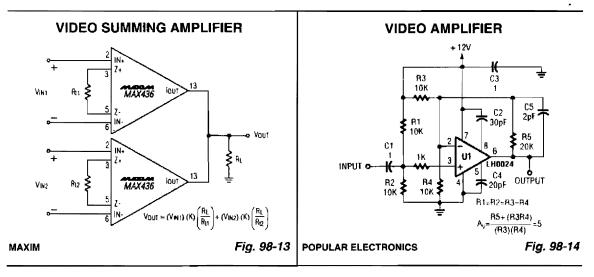

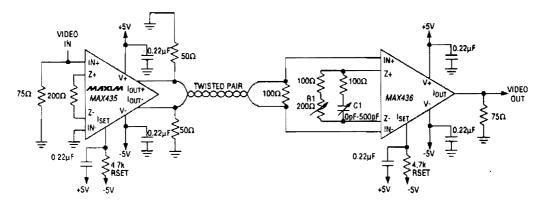TWISTED-PAIR VIDEO DRIVER/RECEIVER CIRCUIT




МАХІМ

Fig. 98-15

This circuit should be useful where a twisted-pair video line is to be used. R1 is adjusted for proper gain (monitor brightness and contrast) and C1 is adjusted for best color.

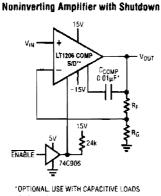250-mA 60-MHz CURRENT-FEEDBACK AMPLIFIER FOR VIDEO APPLICATIONS



OPTIONAL USE WITH CAPACITIVE LO. GROUND SHUTDOWN PIN FOR NORMAL OPERATION

LINEAR TECHNOLOGY

Large-Signal Response, CL = 10,000pF


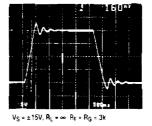


Fig. 98-16


VIDEO DRIVER/AMPLIFIER

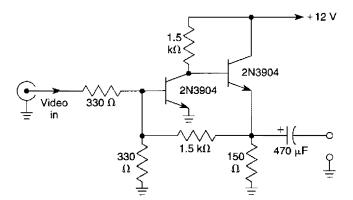

WILLIAM SHEETS

Fig. 98-17

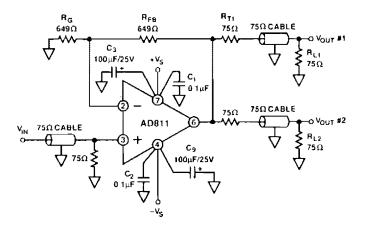This simple circuit has a voltage gain of about 5× and will drive low-impedance loads (75 Ω) to 1.5 V p-p or better.



VIDEO LINE DRIVER

ANALOG DEVICES

Fig. 98-18

This video buffer/line driver operates at a gain of +2 and drives a pair of 75- Ω lines with 75- Ω back terminations. The overall terminated gain is unity.


99

Voltage-Controlled Amplifier Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Voltage-Controlled Amplifier Voltage-Controlled Audio Amplifier

VOLTAGE-CONTROLLED AMPLIFIER

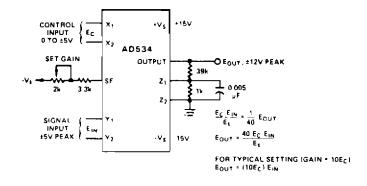


ANALOG DEVICES

Fig. 99-1

A constant or varying signal applied to the X input, E_c , controls the gain for a constant or variable signal applied to the Y input, E_{in} . The inputs could be interchanged.

For this circuit, the "set gain" potentiometer is typically adjusted to provide a calibration for gain of Z 10 per-V-of- E_c . The bandwidth is dc to 30 kHz, independent of the gain. The wideband noise (10 Hz to 30 kHz) is 3 mV rms, typically, corresponding to full-scale signal-to-noise of 70 dB. Noise, referred to the signal input ($E_c = \pm 5$ V) is 60 μ V rms, typically.

VOLTAGE-CONTROLLED AUDIO AMPLIFIER

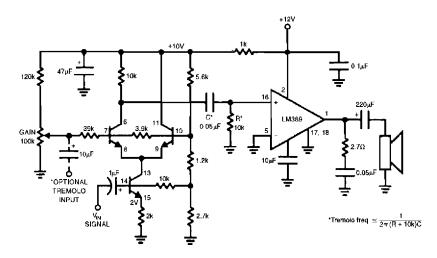

NATIONAL SEMICONDUCTOR

The LM389 has internal transistors used in this circuit.


Fig. 99-2

100

Voltage-Controlled Oscillator Circuits


The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

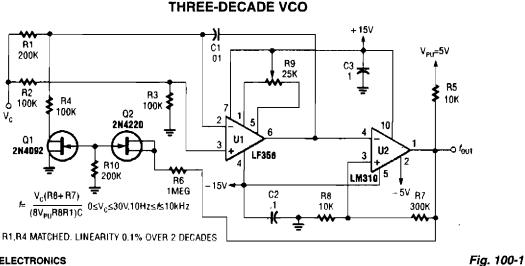Three-Decade VCO Voltage-Controlled Two-Phase Oscillator



POPULAR ELECTRONICS

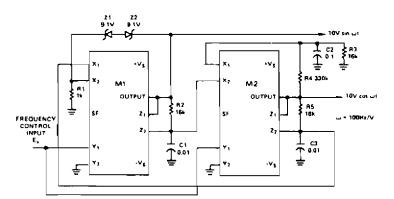A range of 10 Hz to 10 kHz is covered by this circuit.



VOLTAGE-CONTROLLED TWO-PHASE OSCILLATOR

ANALOG DEVICES

Flg. 100-2


This circuit uses two multipliers for integration-with-controllable-time-constants in a feedback loop. R2 and R5 will be recognized in the AD534 voltage-to-current configuration; the currents are integrated in C1 and C3, and the voltages they develop are connected at high impedance in proper polarity to the X inputs of the "next" AD534. The frequency-control input, EY, varies the integrator gains, with a sensitivity of 100 Hz/V, and frequency error typically less than 0.1% of full scale from 0.1 V to 10 V (10 Hz to 1 kHz). C2 (proportional to C1 and C3), R3, R4 provide regenerative damping to start and maintain oscillation. Z_1 and Z_2 stabilize the amplitude at low distortion by degenerative damping above ± 10 V.

101

Voltage-Measuring Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 706. The figure number in the box of each circuit correlates to the entry in the Sources section.

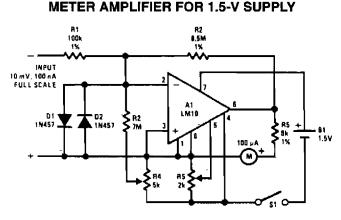
Meter Amplifier for 1.5-V Supply Voltage Monitor ac Voltmeter Has Unique Features dc Voltmeter Expanded-Scale dc Meter for 12-V Systems Simple 3-Digit DVM Inexpensive Voltage Calibrator Double-Ended Voltage Monitor Audible Voltage Indicator Low-Drain Meter Amplifier



NATIONAL SEMICONDUCTOR

Flg. 101-1

An LM10 is used as a meter amplifier. Accuracy can be maintained over a 15°C to 55°C range for a full-scale sensitivity of 10 mV and 100 nA. The offset voltage error is nulled with R5, and the bias current can be balanced out with R4. The zeroing circuits operate from the reference output and are essentially unaffected by changes in battery voltage, so frequent adjustments should not be necessary. Total current drain is under 0.5 mA, giving an approximate life of 3 to 6 months with an "AA" cell and over a year with a "D" cell. With these lifetimes, an ON/OFF switch might be unnecessary. A test switch that converts to a battery-test mode might be of greater value.

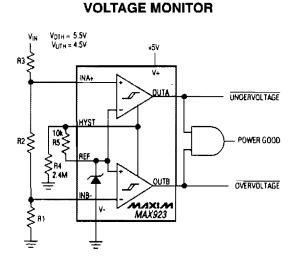



MAXIM

Fig. 101-2

A MAX923 dual comparator is used as a window detector. For a threshold of 4.5 V and 5.5 V, $R_1 = 1.068 \text{ M}\Omega$, $R_2 = 61.9 \text{ k}\Omega$, and $R_3 = 1 \text{ M}\Omega$.

ac VOLTMETER HAS UNIQUE FEATURES

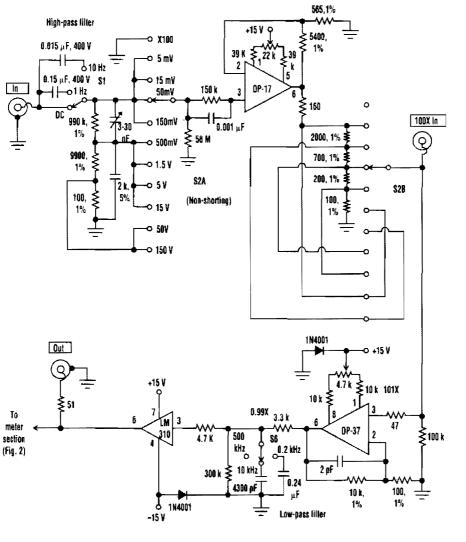


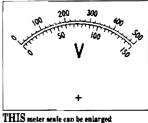

THIS meter scale can be enlarged on a copier and attached to a meter face for the dual-scale ac voitmeter.

ELECTRONIC DESIGN

Fig. 101-3

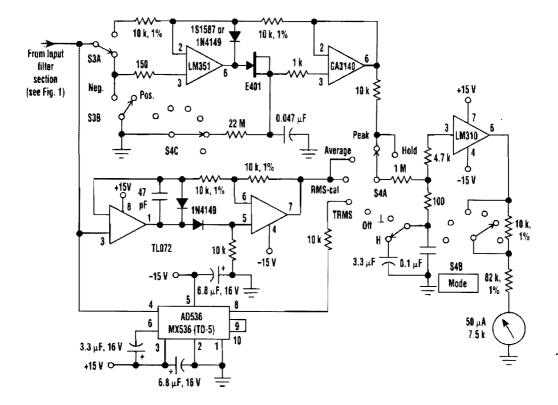

ac VOLTMETER HAS UNIQUE FEATURES (Cont.)


Though it's built with standard components, this ac voltmeter contains many features not typically found in commercial meters; the most unusual is a selection of rectification modes. The meter responses available include true RMS (TRMS), average, RMS-calibrated average responding, positive peak, negative peak, positive-peak hold, and negative-peak hold.

High- and low-pass filters (S1 and S6, respectively) allow the -3-dB-passband to be varied from as little as 10 Hz to 200 Hz, to as wide as dc to 500 kHz. The low-pass filter also is effective in the 100× amplifier mode, where the input equivalent noise level is only 0.3μ V, with 10-kHz roll-off.

dc VOLTMETER

V FULL SCALE	R _V [Ω]	R _f [Ω]	R' f [Ω]
10 mV	100k	1.5M	1.5M
100 mV	1M	1.5M	1.5M
1V	10M	1.M	1.5M
10V	10M	300k	0
100V	10M	30k	O


Resistance Values for a DC Voltmeter

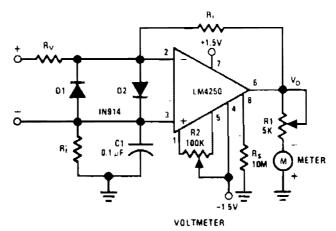


NATIONAL SEMICONDUCTOR

Fig. 101-4

A wide-range voltmeter circuit. This inverting amplifier has a gain varying from -30 for the 10-mV full-scale range to -0.003 for the 100-V full-scale range. Diodes D1 and D2 provide complete amplifier protection for input overvoltages as high as 500 V on the 10-mV range, but if overvoltages of this magnitude are expected under continuous operation, the power rating of R_v should be adjusted accordingly.

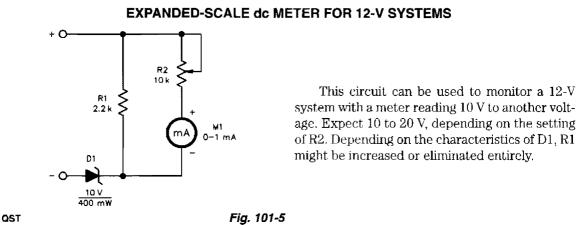

SIMPLE 3-DIGIT DVM

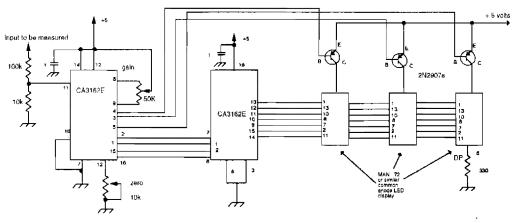


73 AMATEUR RADIO TODAY



A CA3162ZE A-D converter drives a CA3161 BCD decoder/driver and LED display to form a simple DVM circuit. The 50-k Ω gain control and 100-k Ω /10-k Ω voltage divider determine full-scale range.

INEXPENSIVE VOLTAGE CALIBRATOR

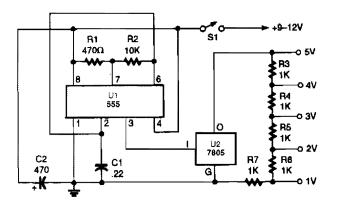


POPULAR ELECTRONICS

Fig. 101-7

In the voltage calibrator, two low-cost ICs—a 555 oscillator/timer and a 78055 5-V 1.5-A voltage regulator—along with a precision voltage divider network are used to provide outputs of 1- to 5-V peak-to-peak.

DOUBLE-ENDED VOLTAGE MONITOR

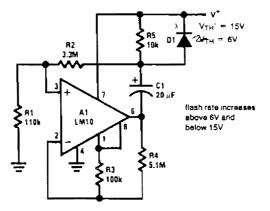

NATIONAL SEMICONDUCTOR


Fig. 101-8

This circuit has the added feature that it can sense an over-voltage condition. The lower activation threshold is given by equation (1), but above a threshold,

$$V_{\rm TH} = \frac{R4(R_1 + R_2) V_{\rm REF}}{R_1(R_3 + R_4) - R3(R_1 + R_2)}$$

oscillation again ceases. Below $V_{\rm TH}$, the op amp output is saturated negative, but above $V_{\rm TH}$, it is saturated positive. The flash rate approaches zero near either limit.

AUDIBLE VOLTAGE INDICATOR

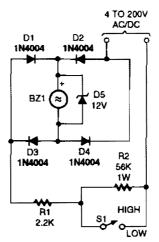


POPULAR ELECTRONICS

Fig. 101-9

The audible voltmeter can be used to test for ac or dc voltages in a circuit. With S1 closed, the circuit can be used to test for voltages between 4 and 24 V, and when S1 is open, it can be used to check for the presence voltages of up to 200 V.

LOW-DRAIN METER AMPLIFIER

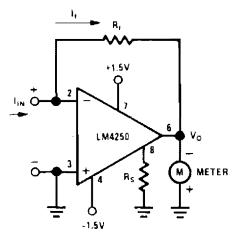

NATIONAL SEMICONDUCTOR

Fig. 101-10

Meter amplifiers normally require one or two 9-V transistor batteries. Because of the heavy current drain on these supplies, the meters must be switched to the OFF position when not in use. The meter circuit described here operates on two 1.5-V flashlight batteries and has a quiescent power drain so low that no on/off switch is needed. A pair of Eveready No. 950 "D" cells will serve for a minimum of one year without replacement. As a dc ammeter, the circuit will provide current ranges as low as 100 nA full-scale.

The basic meter amplifier circuit shown is a current-to-voltage converter. Negative feedback around the amplifier ensures that currents $I_{\rm IN}$ and $I_{\rm f}$ are always equal, and the high gain of the op amp ensures that the input voltage between pins 2 and 3 is in the microvolt region. Output voltage $V_{\rm o}$ is therefore equal to $-I_{\rm f}R_{\rm f}$. Considering the ±1.5-V sources (±1.2 V end of life) a practical value of $V_{\rm o}$ for full-scale meter deflection is 300 mV. With the master bias-current setting resistor ($R_{\rm s}$) set at 10 M Ω , the total quiescent current drain of the circuit is 0.6 μ A for a total power supply drain of 1.8 μ W. The input bias current, required by the amplifier at this low level of quiescent current, is in the range of 600 pA.


102

Waveform Generator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Simple Triangle Waveform Generator Triangle-Wave Generator Generate Accurate PWM Signals Triangle-Wave Generator Low-Frequency Pulse Generator Sine/Cosine Audio Generator for Galvanometer Experiments Basic 555 Monostable Op-Amp Sawtooth Generator Digital Sine-Wave Generator Signal Source for Audio Amplifier/Inverter Simple Test Signal Generator

SIMPLE TRIANGLE WAVEFORM GENERATOR

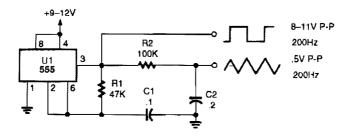


POPULAR ELECTRONICS

Fig. 102-1

The circuit is a triangle waveform-generator circuit that uses as few parts as possible. A 555 timer IC, two resistors, and two capacitors make the triangle waveform. The IC is connected in a 50% duty-cycle astable square-wave oscillator circuit. The square-wave output is fed from pin 3 of the IC to an RC shaping circuit.

When the 555's square-wave output goes high, C2 begins to charge through R2 and the voltage across C2 increases as long as the output remains high. When the IC's output goes low again, C2 begins to discharge through R2 reducing the voltage across C2 as long as the output remains low. The resulting waveform across C2 takes the shape of a triangle. The best waveform linearity is obtained when R_2 and C_2 are made as large as possible. With the component values shown, the peak-to-peak output is 0.5 V at a frequency of about 200 Hz.

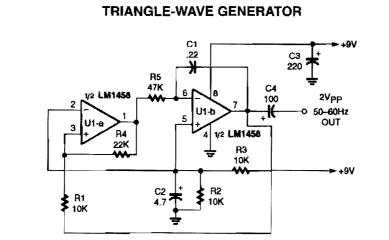


POPULAR ELECTRONICS

Fig. 102-2

This oscillator, which is built around an LM1458 dual op amp and a few inexpensive components, produces a 2-V peak-to-peak, triangular waveform.

GENERATE ACCURATE PWM SIGNALS

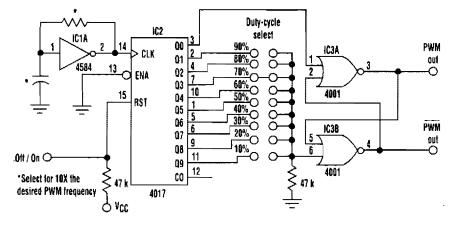

ELECTRONIC DESIGN


Fig. 102-3

Accurate 10 to 90% duty-cycle PWM signals can be generated using this simple circuit setup. The desired duty cycle is selected by a single jumper block. PWM clock IC1 runs at 10× the desired pulse drive frequency. IC2, a 4017 divide-by-10 counter, decodes the clock pulses into one of 10 outputs. Output 0 resets IC3, the PWM latch. The latch stays reset until the desired duty-cycle output set by the jumper block is reached. At this point, the PWM latch is set, and the PWM output line remains high until output 0 is decoded again.

By calling IC2's output (0) the "reset" line for the latch, the PWM output is forced inactive if the jumper strap is removed to change duty cycles without first powering down.

Using the zero-state reset allows IC2's reset pin to be used as an on/off control line for the circuit. The complementary PWM output could be used in a full bridge design.

TRIANGLE-WAVE GENERATOR

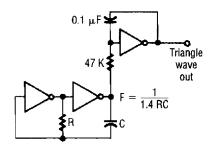


ELECTRONICS NOW

Fig. 102-4

The first two gates are set up as a square-wave oscillator, and the last one makes the conversion to triangle waves.

LOW-FREQUENCY PULSE GENERATOR

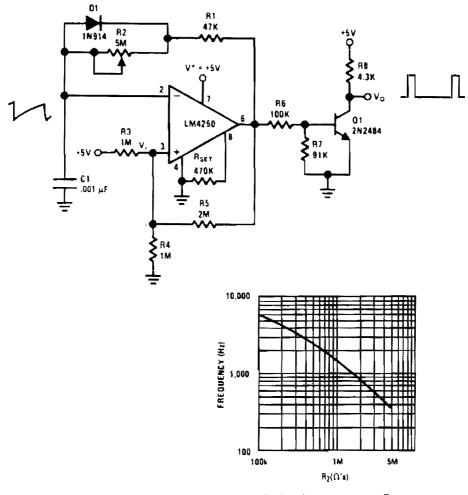


Pulse frequency vs. R_2

NATIONAL SEMICONDUCTOR

Fig. 102-5

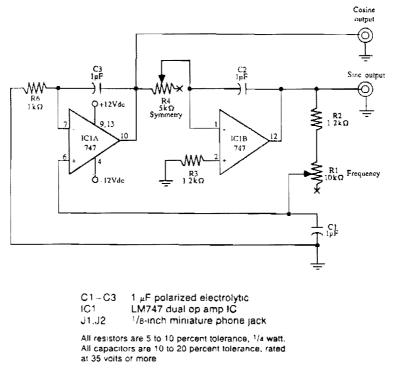
SINE/COSINE AUDIO GENERATOR FOR GALVANOMETER EXPERIMENTS



-McGRAW-HILL

Flg. 102-6

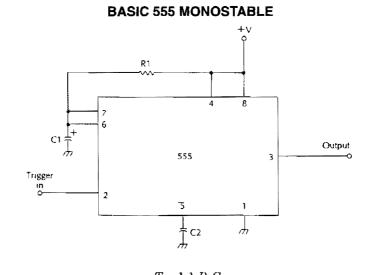
This circuit shows how to implement a sine/cosine audio generator for operating two galvanometers.



McGRAW-HILL

 $T + 1.1 R_1 C_1$



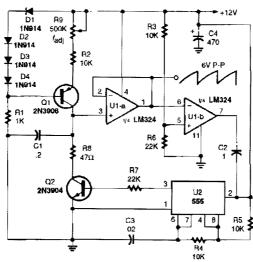


POPULAR ELECTRONICS

Fig. 102-8

The sawtooth generator circuit shown is reset at the end of each cycle. The result is a constant peak-to-peak output throughout the circuit's frequency range.

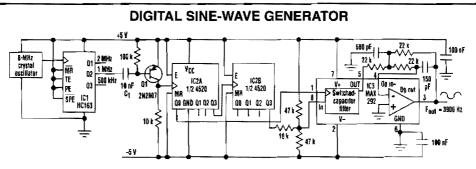The constant-current generator circuit, the voltage-follower circuit, and the comparator circuit produce the waveform. A 555 timer IC (U2) is configured as a one-shot multivibrator that's triggered by the comparator's negative output pulse.



ELECTRONIC DESIGN


Fig. 102-9

The sine-wave generator starts with an 8-MHz signal and divides it by eight to obtain 1 MHz at C1 (IC1's 2-MHz and 500-kHz outputs can serve as alternate drive signals). Q1 level-shifts the 1-MHz pulses so that they can drive the bipolar circuitry necessary for producing a bipolar output. Synchronous counter IC2 divides 1 MHz by 256 to give the desired output frequency (3906 Hz), and IC3 filters the harmonic frequencies.

The filter's clock is taken from the first divide-by-2 tap of IC2 to assure a 50% duty cycle. IC2 further divides this signal by 128 to ensure that the filter's input signal (1 MHz/256) falls within the flat portion of the filter response.

The output of the switched-capacitor filter resembles a sampled sine wave. It can be smoothed by building a first- or second-order low-pass filter around the otherwise uncommitted output op amp.

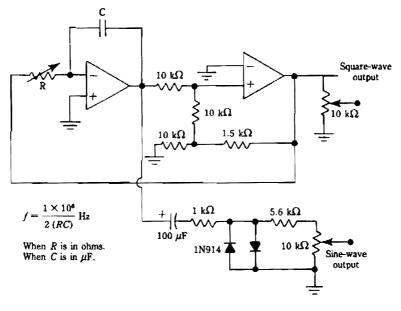
SIGNAL SOURCE FOR AUDIO AMPLIFIER/INVERTER



McGRAW-HILL

Fig. 102-10

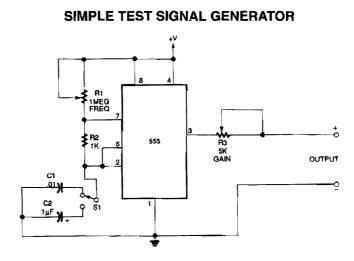Two op amps (741, etc..) are used in this oscillator circuit. A square wave is available and a sine wave, obtained by shaping the triangle waveform, is also provided.



ELECTRONICS NOW

Fig. 102-11

An NE555 generates signals for test purposes. Frequency range is from 20 Hz to 10 kHz, depending on the setting of S1. +V is 5 V.


103

Waveguide Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

10-GHz Waveguide Detector for Amateur Radio Use 10-GHz Waveguide Transition for Amateur Radio Use

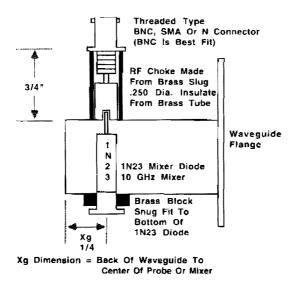10-GHz WAVEGUIDE DETECTOR FOR AMATEUR RADIO USE




73 AMATEUR RADIO TODAY

Fig. 103-1

This shows the construction of a waveguide detector for use at the 10-GHz amateur radio frequencies.

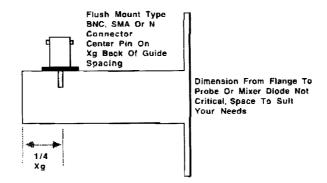10-GHz WAVEGUIDE TRANSITION FOR AMATEUR RADIO USE



73 AMATEUR RADIO TODAY

Fig. 103-2

A transistor adapts the waveguide to coaxial cable or other types of transmission lines.


104

White-Noise Generator Circuits

The sources of the following circuits are contained in the Sources section, which begins on page 707. The figure number in the box of each circuit correlates to the entry in the Sources section.

Zener-Diode White-Noise Generator White-Noise Generator

ZENER-DIODE WHITE-NOISE GENERATOR

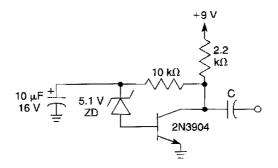


WILLIAM SHEETS

Fig. 104-1

Fig. 104-2

This circuit uses a Zener diode as a noise source. C is chosen to pass the lowest-desired frequency components of the noise.

WHITE-NOISE GENERATOR

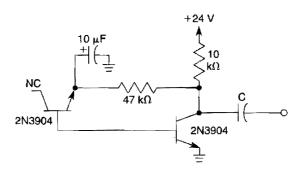

WILLIAM SHEETS

Here, a 2N3904 E-B junction is used as a noise generator, reversed bias. C is chosen to pass the lowest-desired frequency components of the noise.

Sources

Chapter 1

- Fig. 1-1. QST, 2/95, p. 58.
- Fig. 1-2. Analog Devices, Analog Dialogue, Vol. 26, No. 2, p. 5.
- Fig. 1-3. Reprinted with permission from Electronic Design, 2/95, p. 108. Copyright 1995, Penton Publishing, Inc.
- Fig. 1-4. 1994 Experimenters Handbook, p. 113.

Chapter 2

- Fig. 2-1. Reprinted with permission from Electronic Design, 10/94, p. 90. Copyright 1994, Penton Publishing, Inc.
- Fig. 2-2. Reprinted with permission from Popular Electronics, 1/94, p. 37. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 2-3. Reprinted with permission from Popular Electronics, Fact Card No. 270.(C) Copyright Gernsback Publications, Inc.

Chapter 3

- Fig. 3-1. Reprinted with permission from Popular Electronics, 9/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 3-2. Reprinted with permission from

Popular Electronics, 10/94, p. 48. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 3-3. Reprinted with permission from Popular Electronics, 10/94, p. 35. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 3-4. Reprinted with permission from Popular Electronics, 10/94, p. 49. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 3-5. Reprinted with permission from Popular Electronics, 5/95, pp. 69–70. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 3-6. Reprinted with permission from Popular Electronics, 9/94, p. 24. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 3-7. Reprinted with permission from Popular Electronics, 2/94, p. 37. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 3-8. Reprinted with permission from Popular Electronics, 5/95, p. 70. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 3-9. Reprinted with permission from Popular Electronics, 9/94, p. 25 (C)

Copyright Gernsback Publications, Inc., 1994.

- Fig. 3-10. Reprinted with permission from Popular Electronics, 4/95, p. 70. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 3-11. Reprinted with permission from Popular Electronics, 5/95, p. 71. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 4

- Fig. 4-1. QST, 12/94, p. 36.
- Fig. 4-2. QST, 12/94, p. 35.
- Fig. 4-3. QST, 12/94, p. 34.
- Fig. 4-4. QST, 5/89, pp. 25–27.
- Fig. 4-5. 73 Amateur Radio Today, 5/94, pp. 58–59.
- Fig. 4-6. 73 Amateur Radio Today, 8/89, p. 60.
- Fig. 4-7. QST, 4/95, p. 56.
- Fig. 4-8. QST, 7/94, p. 24.
- Fig. 4-9. QST, 3/95, p. 28.
- Fig. 4-10. QST, 10/94, p. 65.
- Fig. 4-11. 73 Amateur Radio Today, 1/95, p. 32.
- Fig. 4-12. 73 Amateur Radio Today, 6/83, p. 99.
- Fig. 4-13. 73 Amateur Radio Today, 10/94, p. 14.
- Fig. 4-14. 73 Amateur Radio Today, 5/94, p. 10.
- Fig. 4-15. William Sheets.
- Fig. 4-16. QST, 4/95, p. 61.
- Fig. 4-17. QST, 10/94, p. 42.
- Fig. 4-18. 73 Amateur Radio Today, 6/94, p. 48.
- Fig. 4-19. 73 Amateur Radio Today, 6/94, pp. 32–34.

Chapter 5

- Fig. 5-1. Reprinted with permission from Electronics Now, 7/94, p. 34. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 5-2. Reprinted with permission from Electronics Now, 7/94, p. 39. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 5-3. Reprinted with permission from Electronics Now, 7/94, p. 36. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 5-4. William Sheets.

- Fig. 5-5. 73 Amateur Radio Today, 9/94, p. 62.
- Fig. 5-6. QST, 11/94, p. 23.
- Fig. 5-7. QST, 12/94, p. 28.
- Fig. 5-8. Rudolf F. Graf and William Sheets.
- Fig. 5-9. Reprinted with permission from Radio-Electronics, September 1992, p. 79. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 6

- Fig. 6-1. Reprinted with permission from Electronic Design, 11/93, p. 102. Copyright 1993, Penton Publishing, Inc.
- Fig. 6-2. Reprinted with permission from Radio-Electronics, Experimenters Handbook, p. 4. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 6-3. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-17.
- Fig. 6-4. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-17.
- Fig. 6-5. Reprinted with permission from Electronics Now, 2/94, p. 75. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 6-6. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 492.
- Fig. 6-7. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, pp. 104–105.
- Fig. 6-8. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 107.
- Fig. 6-9. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-30.
- Fig. 6-10. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-18.
- Fig. 6-11. Linear Technology, 2/95.
- Fig. 6-12. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-18.
- Fig. 6-13. Linear Technology, 2/95.
- Fig. 6-14. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 594.
- Fig. 6-15. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 127–128.

- Fig. 6-16. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 501.
- Fig. 6-17. Reprinted with permission from Electronics Now, 6/94, p. 12. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 6-18. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-19.

Chapter 7

- Fig. 7-1. Analog Devices, AD8001 Data Sheet.
- Fig. 7-2. Reprinted with permission from Popular Electronics, 4/94, p. 47. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 8

- Fig. 8-1. 73 Amateur Radio Today, 12/93, p. 32.
- Fig. 8-2. Reprinted with permission from Electronic Design, 2/95, p. 107. Copyright 1995, Penton Publishing, Inc.
- Fig. 8-3. Reprinted with permission from Electronics Now, 11/93, p. 31. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 8-4. Reprinted with permission from Electronics Now, 5/94, p. 49. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 8-5. QST, 5/95, p. 35.
- Fig. 8-6. QST, 5/95, p. 35.
- Fig. 8-7. William Sheets.

Chapter 9

- Fig. 9-1. QST, 10/94, p. 47.
- Fig. 9-2. Reprinted with permission from Popular Electronics, 12/94, p. 88. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 10

- Fig. 10-1. Reprinted with permission from Electronics Now, 6/94, p. 34. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 10-2. Reprinted with permission from Electronics Now, 5/93, p. 65. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 10-3. William Sheets.
- Fig. 10-4. William Sheets.

- Fig. 10-5. Reprinted with permission from Popular Electronics, 12/94, p. 31. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 10-6. William Sheets.
- Fig. 10-7. William Sheets.
- Fig. 10-8. Reprinted with permission from Electronics Now, 8/94, p. 12. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 10-9. Analog Devices, The Best of Analog Dialogue, 1967–1992, p. 180.
- Fig. 10-10. Analog Devices, Analog Dialogue, Vol. 27, No. 2 (1993), p. 22.
- Fig. 10-11. Reprinted with permission from Popular Electronics, Fact Card No. 229.(C) Copyright Gernsback Publications, Inc.
- Fig. 10-12. William Sheets.
- Fig. 10-13. William Sheets.
- Fig. 10-14. William Sheets.
- Fig. 10-15. William Sheets.
- Fig. 10-16. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 180.
- Fig. 10-17. William Sheets.
- Fig. 10-18. William Sheets.
- Fig. 10-19. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 329.

Chapter 11

- Fig. 11-1. William Sheets.
- Fig. 11-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 1058.
- Fig. 11-3. William Sheets.
- Fig. 11-4. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 1060.
- Fig. 11-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 253.
- Fig. 11-6. William Sheets.
- Fig. 11-7. Reprinted with permission from Popular Electronics, 1/95, p. 54. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 11-8. Reprinted with permission from

Popular Electronics, 1/95, p. 54. (C) Copyright Gernsback Publications, Inc., 1995.

- Fig. 11-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 1-14.
- Fig. 11-10. William Sheets.
- Fig. 11-11. William Sheets.
- Fig. 11-12. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 199.
- Fig. 11-13. William Sheets.
- Fig. 11-14. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Lincar Applications Handbook, 1991, p. 198.
- Fig. 11-15. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Edge, #8, p. 14.
- Fig. 11-16. William Sheets.
- Fig. 11-17. QST, 12/94, p. 44.
- Fig. 11-18. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 1059.
- Fig. 11-19. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 1059.
- Fig. 11-20. Reprinted with permission from Popular Electronics, 5/94, p. 80. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 12

- Fig. 12-1. Reprinted with permission from Popular Electronics, 4/95, p. 47. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-2. Reprinted with permission from Popular Electronics, 3/95, p. 67. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-3. William Sheets.
- Fig. 12-4. William Sheets.

- Fig. 12-5. Reprinted with permission from Popular Electronics, 4/95, p. 70. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-6. Electronics Now, 4/94, p. 25.
- Fig. 12-7. Reprinted with permission from Popular Electronics, 5/95, p. 69. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-8. Reprinted with permission from Radio-Electronics, June 1984, p. 39. (C) Copyright Gernsback Publications, Inc., 1984.
- Fig. 12-9. Reprinted with permission from Radio-Electronics, 1994 Electronics Experimenters Handbook, p. 37. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 12-10. William Sheets.
- Fig. 12-11. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 104.
- Fig. 12-12. Reprinted with permission from Popular Electronics, 6/95, p. 32. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-13. Reprinted with permission from Popular Electronics, 4/95, p. 68. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-14. Reprinted with permission from Popular Electronics, 4/95, p. 68. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 12-15. Electronics Now, 4/95, p. 18.
- Fig. 12-16. Reprinted with permission from Popular Electronics, 6/95, p. 30. (C) Copyright Gernsback Publications, Inc., 1995.

- Fig. 13-1. Reprinted with permission from Electronics Now, 5/95, p. 65. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 13-2. Reprinted with permission from Electronics Now, 10/94, pp. 65–66. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 13-3. William Sheets.
- Fig. 13-4. Reprinted with permission from

Electronic Design, 6/94, pp. 42–43. Copyright 1994, Penton Publishing, Inc.

- Fig. 13-5. Reprinted with permission from Popular Electronics, 6/95, p. 32. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 13-6. Reprinted with permission from Electronic Design, 6/94, p. 42. Copyright 1994, Penton Publishing, Inc.
- Fig. 13-7. Linear Technology, Design Note #98.
- Fig. 13-8. 73 Amateur Radio Today, 6/93, p. 41.
- Fig. 13-9. 73 Amateur Radio Today, 6/93, p. 35.
- Fig. 13-10. Reprinted with permission from Electronic Design, 6/94, p. 42. Copyright 1994, Penton Publishing, Inc.
- Fig. 13-11. Reprinted with permission from Popular Electronics, 6/93, p. 76. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 13-12. 73 Amateur Radio Today, 5/93, p. 69.

Chapter 14

- Fig. 14-1. Reprinted with permission from Electronic Design, 1/95, pp. 81–82. Copyright 1995, Penton Publishing, Inc.
- Fig. 14-2. Spring 1994 Electronics Hobbyist Handbook.
- Fig. 14-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 499.
- Fig. 14-4. Reprinted with permission from Popular Electronics, 3/92, p. 74. (C) Copyright Gernsback Publications, Inc., 1992.
- Fig. 14-5. Maxim, Vol. III, New Releases Data Book, 1994, p. 529.
- Fig. 14-6. Reprinted with permission from Radio-Electronics, June 1984, p. 90.
- Fig. 14-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 498.
- Fig. 14-8. QST, 10/94, p. 75.
- Fig. 14-9. Laser Cookbook, McGraw-Hill, p. 183.

Chapter 15

- Fig. 15-1. Reprinted with permission of Burr-Brown Corporation, Burr-Brown Data Sheet INA118, (C) 1989–1995 Burr-Brown Corporation.
- Fig. 15-2. Reprinted with permission from Popular Electronics, 3/94, p. 83. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 15-3. Reprinted with permission from Popular Electronics, Fact Card No. 248.(C) Copyright Gernsback Publications, Inc.

Chapter 16

- Fig. 16-1. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 180.
- Fig. 16-2. William Sheets.
- Fig. 16-3. Analog Devices, Analog Dialogue, -Vol. 26, No. 2, 1992, p. 17.
- Fig. 16-4. Analog Devices, Analog Dialogue, Vol. 26, No. 1, 1992, p. 12.
- Fig. 16-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 542.
- Fig. 16-6. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 117.
- Fig. 16-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 543.
- Fig. 16-8. Reprinted with permission from Electronic Design, 8/94, p. 104. Copyright 1994, Penton Publishing, Inc.
- Fig. 16-9. Linear Technology, Design Note #89.

Chapter 17

- Fig. 17-1. Reprinted with permission from Electronic Design, 11/94, p. 115. Copyright 1994, Penton Publishing, Inc.
- Fig. 17-2. Reprinted with permission from Electronics Now, 3/95, p. 8. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 18

Fig. 18-1. Reprinted with permission from Electronic Design, 4/89, p. 108. Copyright 1989, Penton Publishing, Inc.

- Fig. 18-2. Reprinted with permission from Electronic Design, 10/94, pp. 107–108. Copyright 1994, Penton Publishing, Inc.
- Fig. 18-3. 1994 Electronic Experimenters Handbook, p. 99.
- Fig. 18-4. Reprinted with permission from Electronic Design, 12/94, p. 115. Copyright 1994, Penton Publishing, Inc.
- Fig. 18-5. Maxim, Vol. III, New Releases Data Book, 1994, p. 5-17.
- Fig. 18-6. Reprinted with permission from Electronic Design, 10/94, p. 101. Copyright 1994, Penton Publishing, Inc.
- Fig. 18-7. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-107.
- Fig. 18-8. Reprinted with permission from Electronic Design, 1/84, p. 440. Copyright 1984, Penton Publishing, Inc.
- Fig. 18-9. Reprinted with permission from Electronics Now, 5/95, p. 44. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 19-1. Reprinted with permission from Electronic Design, 3/95, p. 111. Copyright 1995, Penton Publishing, Inc.
- Fig. 19-2. Reprinted with permission from Electronics Now, 8/94, p. 8. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 19-3. Reprinted with permission from Electronics Now, 4/95, p. 83. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 19-4. Sound Light and Music, Delton T. Horn, McGraw-Hill, p. 168.

Chapter 20

- Fig. 20-1. Radio Craft, 1993, p. 64.
- Fig. 20-2. William Sheets.
- Fig. 20-3. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 97.
- Fig. 20-4. Analog Devices, Analog Dialogue, Vol. 27, No. 2 (1993), p. 21.
- Fig. 20-5. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 103.
- Fig. 20-6. William Sheets.
- Fig. 20-7. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 170–173.

- Fig. 20-8. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-79.
- Fig. 20-9. Reprinted with permission from Electronic Design, 11/93, p. 89. Copyright 1995, Penton Publishing, Inc.
- Fig. 20-10. Reprinted with permission of Burr-Brown Corporation, Burr-Brown Data Sheet INA118, (C) 1989–1995 Burr-Brown Corporation.
- Fig. 20-11. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 76. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 20-12. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 76. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 20-13. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, pp. 65–66.
- Fig. 20-14. Reprinted with permission from Electronic Design, 3/95, p. 96. Copyright 1995, Penton Publishing, Inc.
- Fig. 20-15. Reprinted with permission from Electronic Design, 3/95, pp. 94–96. Copyright 1995, Penton Publishing, Inc.
- Fig. 20-16. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.

- Fig. 21-1. Reprinted with permission from Popular Electronics, 2/94, p. 80. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-2. Reprinted with permission from Popular Electronics, 2/94, p. 81. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-3. Reprinted with permission from Popular Electronics, 2/94, p. 81. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-4. Reprinted with permission from Popular Electronics, 2/94, p. 80. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-5. William Sheets.
- Fig. 21-6. Reprinted with permission from Popular Electronics, 2/94, p. 90. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 21-7. William Sheets.
- Fig. 21-8. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 75. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-9. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 76. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 21-10. Radio Craft, 1993, p. 63.
- Fig. 21-11. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 76. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 22-1. Reprinted with permission from Popular Electronics, 5/95, pp. 30–31.
 (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 22-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 245.
- Fig. 22-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 245.
- Fig. 22-4. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 245.

Chapter 23

- Fig. 23-1. 73 Amateur Radio Today, 3/95, p. 62.
- Fig. 23-2. William Sheets.
- Fig. 23-3. Linear Technology, Design Note #86.
- Fig. 23-4. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-92.
- Fig. 23-5. Reprinted with permission from Popular Electronics, 1/94, p. 73. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 24

Fig. 24-1. Reprinted with permission from Electronics Now, 11/93, p. 53. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 24-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook 1991, p. 300.
- Fig. 24-3. William Sheets.
- Fig. 24-4. Reprinted with permission from Electronics Now, 3/95, p. 86. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 24-5. Reprinted with permission from Electronics Now, 3/95, p. 86. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 25

- Fig. 25-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Lincar Applications Handbook 1991, p. 267.
- Fig. 25-2. Reprinted with permission from Electronics Now, 8/93, p. 12. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 26-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 541.
- Fig. 26-2. Reprinted with permission from Electronic Design, 12/94, p. 129. Copyright 1994, Penton Publishing, Inc.
- Fig. 26-3. 1994 Analog Application Issue, Electronic Design, June 27, 1994.
- Fig. 26-4. Reprinted with permission from Popular Electronics, 10/94, p. 82. (Č) Copyright Gernsback Publications, Inc., 1994.
- Fig. 26-5. Reprinted with permission from Popular Electronics, 12/94, p. 30. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 26-6. Reprinted with permission from Electronics Now, 3/94, p. 68. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 26-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 271.
- Fig. 26-8. Reprinted with permission from Popular Electronics, Fact Card No. 249.(C) Copyright Gernsback Publications, Inc.

- Fig. 26-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 271.
- Fig. 26-10. Reprinted with permission from Electronic Design, 9/94, p. 136. Copyright 1994, Penton Publishing, Inc.
- Fig. 26-11. Reprinted with permission from Electronic Design, 1/95, p. 81. Copyright 1995, Penton Publishing, Inc.
- Fig. 26-12. Reprinted with permission from Electronics Now, 11/93, p. 8. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 26-13. Reprinted with permission from Electronics Now, 3/94, p. 67. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 26-14. Reprinted with permission from Electronic Design, 5/90, p. 79. Copyright 1990, Penton Publishing, Inc.
- Fig. 26-15. Reprinted with permission from Popular Electronics, Fact Card No. 270.(C) Copyright Gernsback Publications, Inc.
- Fig. 26-16. Reprinted with permission from Popular Electronics, Fact Card No. 270.(C) Copyright Gernsback Publications, Inc.
- Fig. 26-17. Reprinted with permission from Popular Electronics, Fact Card No. 269.(C) Copyright Gernsback Publications, Inc.
- Fig. 26-18. Reprinted with permission from Popular Electronics, Fact Card No. 269.(C) Copyright Gernsback Publications, Inc.
- Fig. 26-19. Linear Technology, Design Note 88.
- Fig. 26-20. Reprinted with permission from Popular Electronics, 10/94, p. 82. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 27-1. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 37.
- Fig. 27-2. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-45.

Chapter 28

- Fig. 28-1. Reprinted with permission from Electronics Now, 3/95, p. 64. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 28-2. Reprinted with permission from Popular Electronics, 1/94, p. 24. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 28-3. Reprinted with permission from Popular Electronics, 1/94, p. 25. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 28-4. Linear Technology, Advertisement.
- Fig. 28-5. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-127.
- Fig. 28-6. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 132–135.
- Fig. 28-7. Reprinted with permission from Popular Electronics, 2/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 28-8. Reprinted with permission from Electronic Design, 12/93, p. 74. Copyright 1993, Penton Publishing, Inc.
- Fig. 28-9. Reprinted with permission from Electronics Now, 3/95, p. 61. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 29-1. Linear Technology, 2/95.
- Fig. 29-2. Analog Devices, Analog Dialogue, Vol. 26, No. 2, 1992, p. 18.
- Fig. 29-3. Reprinted with permission from Popular Electronics, 10/94, p. 24. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 29-4. Analog Devices, Analog Dialogue, Vol. 26, No. 2, 1992, p. 12.
- Fig. 29-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 542.
- Fig. 29-6. Reprinted with permission from Popular Electronics, 1/94, p. 24. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 29-7. 73 Amateur Radio Today, 3/95, p. 62.

- Fig. 29-8. Reprinted with permission from Popular Electronics, 11/94, p. 31. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 29-9. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 17.
- Fig. 29-10. Reprinted with permission from Electronic Design, 7/94, p. 62. Copyright 1994, Penton Publishing, Inc.
- Fig. 29-11. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 541.
- Fig. 29-12. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 16.
- Fig. 29-13. Reprinted with permission from Electronic Design, 9/94, p. 135. Copyright 1994, Penton Publishing, Inc.

- Fig. 30-1. Reprinted with permission from Popular Electronics, 4/95, pp. 29–30.(C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 30-2. Reprinted with permission from Popular Electronics, 4/95, p. 31. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 30-3. Reprinted with permission from Popular Electronics, 4/95, p. 30. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 31

- Fig. 31-1. Laser Cookbook, McGraw-Hill, p. 231.
- Fig. 31-2. Laser Cookbook, McGraw-Hill, p. 231.

- Fig. 32-1. Reprinted with permission from Electronic Design, 2/95, p. 115. Copyright 1995, Penton Publishing, Inc.
- Fig. 32-2. Amplifiers, Waveform Generators, & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 186.
- Fig. 32-3. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 193.

- Fig. 32-4. Radio-Electronics Experimenters Handbook, p. 66.
- Fig. 32-5. Reprinted with permission from Electronic Design, 12/94, p. 134. Copyright 1994, Penton Publishing, Inc.
- Fig. 32-6. Reprinted with permission from Electronic Design, 9/94, p. 79. Copyright 1994, Penton Publishing, Inc.
- Fig. 32-7. William Sheets.
- Fig. 32-8. Reprinted with permission from Popular Electronics, 12/94, p. 42. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 32-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1202.
- Fig. 32-10. Radio Receiver Projects You Can Build, McGraw-Hill, p. 165.
- Fig. 32-11. Radio Receiver Projects You Can Build, McGraw-Hill, p. 291.
- Fig. 32-12. Reprinted with permission from Electronic Design, 8/94, p. 102. Copyright 1994, Penton Publishing, Inc.
- Fig. 32-13. Amplifiers, Waveform, Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 178.
- Fig. 32-14. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 229.
- Fig. 32-15. Linear Technology, 2/95.
- Fig. 32-16. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1187.
- Fig. 32-17. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1187.
- Fig. 32-18. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 222.
- Fig. 32-19. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 79.
- Fig. 32-20. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1032.

Fig. 32-21. Linear Technology, Design Note #84.

- Fig. 32-22. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1202.
- Fig. 32-23. Amplifiers, Waveform Generators, & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 186.
- Fig. 32-24. Amplifiers, Waveform Generators, & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 185.
- Fig. 32-25. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 201.
- Fig. 32-26. Linear Technology, Design Note #89.
- Fig. 32-27. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1015.
- Fig. 32-28. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 228.

Chapter 33

- Fig. 33-1. Reprinted with permission from Popular Electronics, 5/95, pp. 57–59.
 (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 33-2. Reprinted with permission from Popular Electronics, 6/95, p. 77. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 33-3. Reprinted with permission from Popular Electronics, 6/95, p. 78. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 33-4. Reprinted with permission from Popular Electronics, 1/94, p. 73. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 33-5. Sound Light and Music, Delton T. Horn, McGraw-Hill, p. 34.
- Fig. 33-6. Reprinted with permission from Popular Electronics, 5/93, p. 70. (C)

Copyright Gernsback Publications, Inc., 1993.

- Fig. 33-7. Reprinted with permission from Popular Electronics, 5/93, p. 70. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 33-8. Reprinted with permission from Popular Electronics, 5/93, p. 72. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 33-9. Reprinted with permission from Popular Electronics, 2/94, p. 25. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 34

- Fig. 34-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 241.
- Fig. 34-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 241.

Chapter 35

- Fig. 35-1. Reprinted with permission from Electronic Design, 2/94, p. 115. Copyright 1994, Penton Publishing, Inc.
- Fig. 35-2. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.

- Fig. 36-1. Reprinted with permission from Electronics Now, 4/94, pp. 41–45. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 36-2. Reprinted with permission from Electronics Now, 5/95, pp. 53–55. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 36-3. Reprinted with permission from Popular Electronics, Fact Card No. 249.(C) Copyright Gernsback Publications, Inc.
- Fig. 36-4. Reprinted with permission from Electronic Design, 10/94, p. 110. Copyright 1994, Penton Publishing, Inc.

Fig. 36-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 368.

Chapter 37

- Fig. 37-1. Reprinted with permission from Popular Electronics, 9/94, p. 81. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-2. Reprinted with permission from Popular Electronics, 9/94, p. 83. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-3. Reprinted with permission from Popular Electronics, 4/94, p. 79. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-4. Reprinted with permission from Popular Electronics, 12/94, pp. 44–47.
 (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-5. Reprinted with permission from Popular Electronics, 4/94, p. 80. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-6. Reprinted with permission from Popular Electronics, 9/94, p. 81. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-7. Reprinted with permission from Popular Electronics, 9/94, pp. 83 and 92. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-8. Reprinted with permission from Popular Electronics, 5/93, p. 62. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 37-9. Reprinted with permission from Popular Electronics, 4/94, p. 78. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-10. Reprinted with permission from Popular Electronics, 4/94, p. 78. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 37-11. Reprinted with permission from

Popular Electronics Hobbyist Handbook, 1991, p. 4. (C) Copyright Gernsback Publications, Inc., 1991.

Chapter 38

- Fig. 38-1. Reprinted with permission from 1987 Radio-Electronics Experimenters Handbook, p. 63. (C) Copyright Gernsback Publications, Inc., 1987.
- Fig. 38-2. Reprinted with permission from Popular Electronics, 1/94, p. 62. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 39

- Fig. 39-1. Reprinted with permission from Popular Electronics, 6/93, p. 74. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 39-2. William Sheets.
- Fig. 39-3. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 21.

- Fig. 40-1. Reprinted with permission from Popular Electronics, 4/90, p. 102. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 40-2. Reprinted with permission from Popular Electronics, 6/95, p. 76. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 40-3. Reprinted with permission from Popular Electronics, 12/93, p. 31. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 40-4. Reprinted with permission from Popular Electronics, 5/94, p. 69. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 40-5. Reprinted with permission from Popular Electronics, 4/90, p. 90. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 40-6. Reprinted with permission from Popular Electronics, 4/94, p. 34. (C)

Copyright Gernsback Publications, Inc., 1994.

- Fig. 40-7. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-100.
- Fig. 40-8. Reprinted with permission from Electronics Now, 2/94, p. 38. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 40-9. Reprinted with permission from Popular Electronics, 6/95, p. 76. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 40-10. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 140-142.
- Fig. 40-11. Reprinted with permission from Popular Electronics, 4/90, p. 103. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 40-12. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 144–146.
- Fig. 40-13. Reprinted with permission from Popular Electronics, 12/93, p. 32. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 40-14. Laser Cookbook, McGraw-Hill, p. 187.
- Fig. 40-15. Reprinted with permission from Popular Electronics, 4/90, p. 91. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 40-16. Sound Light and Music, Mc-Graw-Hill.
- Fig. 40-17. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 209.

Chapter 41

- Fig. 41-1.
- Fig. 41-2. Linear Technology, 2/95.
- Fig. 41-3. Reprinted with permission from Popular Electronics, Fact Card No. 248.(C) Copyright Gernsback Publications, Inc.
- Fig. 41-4. Analog Devices, Analog Dialogue, Vol. 27, No. 2 (1993), p. 17.
- Fig. 41-5. Reprinted with permission from Popular Electronics, Fact Card No. 248.(C) Copyright Gernsback Publications, Inc.

- Fig. 41-6. Reprinted with permission from Popular Electronics, Fact Card No. 247.(C) Copyright Gernsback Publications, Inc.
- Fig. 41-7. Reprinted with permission of Burr-Brown Corporation, Burr-Brown Data Sheet INA118, (C) 1989-1995 Burr-Brown Corporation.
- Fig. 41-8. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-33.
- Fig. 41-9. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-69.
- Fig. 41-10. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 20.
- Fig.-41-11. Linear Technology, 2/95.

Chapter 42

- Fig. 42-1. Reprinted with permission from Popular Electronics, Fact Card No. 247.(C) Copyright Gernsback Publications, Inc.
- Fig. 42-2. Reprinted with permission from Popular Electronics, Fact Card No. 249.(C) Copyright Gernsback Publications, Inc.
- Fig. 42-3. William Sheets.

Chapter 43

- Fig. 43-1. Reprinted with permission from Popular Electronics, 4/90, p. 78. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 43-2. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.

- Fig. 44-1. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 173–174.
- Fig. 44-2. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 126.
- Fig. 44-3. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 128.
- Fig. 44-4. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-92.
- Fig. 44-5. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 152–153.

- Fig. 45-1. Fantastic Electronics, McGraw-Hill, pp. 36–38.
- Fig. 45-2. 73 Amateur Radio Today, 7/82, p. 53.
- Fig. 45-3. 73 Amateur Radio Today, 7/82, p. 53.
- Fig. 45-4. Spring 1994 Electronic Hobbyists Handbook.

Chapter 46

- Fig. 46-1. Laser Cookbook, McGraw-Hill, pp. 165–167.
- Fig. 46-2. Laser Cookbook, McGraw-Hill, pp. 157–158.
- Fig. 46-3. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 125.
- Fig. 46-4. Laser Cookbook, McGraw-Hill, p. 201.
- Fig. 46-5. Laser Cookbook, McGraw-Hill, p. 190.
- Fig. 46-6. Laser Cookbook, McGraw-Hill, p. 200.
- Fig. 46-7. Laser Cookbook, McGraw-Hill, p. 170.
- Fig. 46-8. Reprinted with permission from Popular Electronics, 6/93, p. 78. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 46-9. Laser Cookbook, McGraw-Hill, p. 169.
- Fig. 46-10. Laser Cookbook, McGraw-Hill, p. 168.

- Fig. 47-1. Reprinted with permission from Electronics Now, 5/94, p. 12. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 47-2. William Sheets.
- Fig. 47-3. Reprinted with permission from Popular Electronics, 6/95, p. 54. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 47-4. Laser Cookbook, McGraw-Hill, pp. 140–141.
- Fig. 47-5. Linear Technology, 2/95.
- Fig. 47-6. Reprinted with permission from Electronic Design, 12/93, p. 75. Copyright 1993, Penton Publishing, Inc.

- Fig. 47-7. Reprinted with permission from Popular Electronics, 9/94, p. 24. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 47-8. Reprinted with permission from Electronic Design, 10/94, p. 92. Copyright 1994, Penton Publishing, Inc.
- Fig. 47-9. Reprinted with permission from Popular Electronics, 4/90, p. 77. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 47-10. Reprinted with permission from Popular Electronics, 9/94, p. 83. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 47-11. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, pp. 82–83.
- Fig. 47-12. Reprinted with permission from Electronics New, 5/94, p. 45. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 47-13. Reprinted with permission from Popular Electronics, 1995, p. 77. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 47-14. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, pp. 589– 590.
- Fig. 47-15. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 218.
- Fig. 47-16. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 219.
- Fig. 47-17. Spring 1994 Electronics Hobbyist Handbook.
- Fig. 47-18. Spring 1994 Electronics Hobbyist Handbook.
- Fig. 47-19. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 493.
- Fig. 47-20. Reprinted with permission from Popular Electronics, 6/95, p. 56. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 47-21. Reprinted with permission from Electronics Now, 9/94, p. 66. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 48-1. NASA Tech Briefs, Spring 1977.
- Fig. 48-2. Reprinted with permission from Electronic Design, 12/93, p. 73. Copyright 1993, Penton Publishing, Inc.
- Fig. 48-3. Reprinted with permission from Popular Electronics, Fact Card No. 268.(C) Copyright Gernsback Publications, Inc.
- Fig. 48-4. William Sheets.
- Fig. 48-5. William Sheets.

Chapter 49

- Fig. 49-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 520.
- Fig. 49-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, pp. 519–520.
- Fig. 49-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 519.
- Fig. 49-4. Analog Devices, The Best of Analog.Dialogue, 1967–1991, p. 78.
- Fig. 49-5. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 79.
- Fig. 49-6. Analog Dialogue, Analog Devices, Vol. 26, No. 1, pp. 14–15.
- Fig. 49-7. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 78.
- Fig. 49-8. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 78.
- Fig. 49-9. Reprinted with permission from Electronic Design, 3/95, p. 116. Copyright 1995, Penton Publishing, Inc.
- Fig. 49-10. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 27.
- Fig. 49-11. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 77.

Chapter 50

Fig. 50-1. Reprinted with permission from Popular Electronics, 4/95, p. 54. (C) Copyright Gernsback Publications, Inc., 1995.

- Fig. 50-2. 1994 Electronic Experimenters Handbook, p. 89.
- Fig. 50-3. 73 Amateur Radio Today, 7/93, p. 34.
- Fig. 50-4. NASA Tech Briefs, November 1993, p. 56.
- Fig. 50-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 588.
- Fig. 50-6. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, pp. 519–520.
- Fig. 50-7. Reprinted with permission from Electronics Now, 3/95, p. 42. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-8. Reprinted with permission from Radio-Electronics, February 1989, p. 64. (C) Copyright Gernsback Publications, Inc., 1989.
- Fig. 50-9. Reprinted with permission from Electronics Now, 5/95, p. 10. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-10. Reprinted with permission from Electronics Now, 5/95, p. 10. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-11. Reprinted with permission from Popular Electronics, Fact Card No. 221.(C) Copyright Gernsback Publications, Inc.
- Fig. 50-12. Fantastic Electronics, McGraw-Hill, pp. 52–60.
- Fig. 50-13. Analog Devices, Analog Dialogue, Vol. 27, No. 2, p. 20.
- Fig. 50-14. Electronics Now, 9/94, pp. 73-74.
- Fig. 50-15. Reprinted with permission from Popular Electronics, 1/94, pp. 31–36. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-16. Electronics Design, June 27, 1994, p. 33.
- Fig. 50-17. Reprinted with permission from Popular Electronics, 10/94, p. 90. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-18. Reprinted with permission from Popular Electronics, 11/94, p. 62. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 50-19. Radio-Electronics, Feb. 1989, p. 64.
- Fig. 50-20. Reprinted with permission from Popular Electronics, 11/94, p. 91. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-21. Reprinted with permission from Electronic Design, 10/94, pp. 102–104. Copyright 1994, Penton Publishing, Inc.
- Fig. 50-22. Reprinted with permission from Electronic Design, 12/94, p. 132. Copyright 1994, Penton Publishing, Inc.
- Fig. 50-23. Reprinted with permission from Electronics Now, 3/95, p. 63. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-24. Reprinted with permission from Popular Electronics, 5/95, pp. 47–48.
 (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-25. Reprinted with permission from Popular Electronics, 5/95, pp. 47-48.
 (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-26. Reprinted with permission from Popular Electronics, 11/94, p. 38. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-27. Reprinted with permission from Electronic Design, 10/94, pp. 92–94. Copyright 1994, Penton Publishing, Inc.
- Fig. 50-28. RF Design, August 1994, p. 78.
- Fig. 50-29. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 206.
- Fig. 50-30. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 500.
- Fig. 50-31. Reprinted with permission from Electronic Design, 11/94, pp. 116–118. Copyright 1994, Penton Publishing, Inc.
- Fig. 50-32. Reprinted with permission from Electronic Design, 10/94, pp. 107. Copyright 1994, Penton Publishing, Inc.
- Fig. 50-33. QST, 12/94, p. 27.
- Fig. 50-34. Reprinted with permission from Electronic Design, 8/94, pp. 109. Copyright 1994, Penton Publishing, Inc.

- Fig. 50-35. Reprinted with permission of Burr-Brown Corporation, Burr-Brown Data Sheet INA118, (C) 1989–1995 Burr-Brown Corporation.
- Fig. 50-36. William Sheets.
- Fig. 50-37. Linear Technology, Design Note 96.
- Fig. 50-38. Reprinted with permission from Popular Electronics, 11/94, p. 31. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-39. Reprinted with permission of XI-COR, XICOR Data Sheet, p. 7. (C) Copyright XICOR, Inc.
- Fig. 50-40. Reprinted with permission from Popular Electronics, Fact Card No. 221.(C) Copyright Gernsback Publications, Inc.
- Fig. 50-41. Reprinted with permission from Popular Electronics, 11/94, p. 30. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-42. William Sheets.
- Fig. 50-43. QST, 10/94, P. 75.
- Fig. 50-44. Reprinted with permission from Popular Electronics, 5/95, p. 69. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 50-45. Reprinted with permission from Popular Electronics, 11/94, p. 33. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 50-46. Reprinted with permission from Radio-Electronics, February 1989, pp. 63–65. (C) Copyright Gernsback Publications, Inc., 1989.
- Fig. 50-47. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 45.
- Fig. 50-48. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, pp. 40-41.

- Fig. 51-1. Sound Light and Music, Delton T. Horn, McGraw-Hill, p. 123.
- Fig. 51-2. Sound Light and Music, Delton T. Horn, McGraw-Hill, p. 120.

- Fig. 52-1. Reprinted with permission from Electronic Design, 5/94, pp. 79–80. Copyright 1994, Penton Publishing, Inc.
- Fig. 52-2. Reprinted with permission from Popular Electronics, 1/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-3. Analog Devices, Analog Dialogue, Vol. 26, No. 1, 1992, p. 15.
- Fig. 52-4. Reprinted with permission from Popular Electronics, 8/89, pp. 33–35. (C) Copyright Gernsback Publications, Inc., 1989.
- Fig. 52-5. NASA Tech Briefs, March 1995, pp. 39-40.
- Fig. 52-6. Reprinted with permission from Radio-Electronics Experimenters Handbook, pp. 98–99. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-7. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 99. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-8. 1994 Electronics Experimenters Handbook, p. 57.
- Fig. 52-9. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 119–123.
- Fig. 52-10. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, pp. 121–122.
- Fig. 52-11. Reprinted with permission from Radio-Electronics Experimenters Handbook, pp. 36–38. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-12. Reprinted with permission from Popular Electronics, 4/95, p. 70. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 52-13. Reprinted with permission from Popular Electronics, 4/90, p. 37. (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 52-14. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 175–177.
- Fig. 52-15. Linear Technology, Design Note 88.

- Fig. 52-16. Fantastic Electronics, McGraw-Hill, p. 59.
- Fig. 52-17. 73 Amateur Radio Today, 6/83, p. 99.
- Fig. 52-18. Spring 1994 Electronic Hobbyists Handbook.
- Fig. 52-19. Reprinted with permission from Electronic Design, 1/95, p. 78. Copyright 1995, Penton Publishing, Inc.
- Fig. 52-20. Sound Light and Music, Delton T. Horn, McGraw-Hill, p. 123.
- Fig. 52-21. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 140–145.
- Fig. 52-22. Reprinted with permission from Electronic Design, 3/95, pp. 111–112. Copyright 1995, Penton Publishing, Inc.
- Fig. 52-23. Reprinted with permission from Electronic Design, 3/95, p. 94. Copyright 1995, Penton Publishing, Inc.
- Fig. 52-24. Reprinted with permission from Electronic Design, 4/89, p. 107. Copyright 1989, Penton Publishing, Inc.
- Fig. 52-25. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 367.
- Fig. 52-26. 73 Amateur Radio Today, 6/83, p. 99.
- Fig. 52-27. Reprinted with permission from Popular Electronics, 4/94, p. 52. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-28. Reprinted with permission from Electronics Now, 2/94, p. 16. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-29. Reprinted with permission from Electronic Design, 3/95, p. 91. Copyright 1995, Penton Publishing, Inc.
- Fig. 52-30. William Sheets.
- Fig. 52-31. William Sheets.
- Fig. 52-32. Reprinted with permission from Electronic Design, 7/94, p. 96. Copyright 1994, Penton Publishing, Inc.
- Fig. 52-33. Reprinted with permission from Electronics Now, 4/94, p. 11. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 52-34. Reprinted with permission from Popular Electronics, 5/95, p. 30. (C)

Copyright Gernsback Publications, Inc., 1994.

Fig. 52-35. Reprinted with permission from Electronic Design, 12/94, pp. 115–116. Copyright 1994, Penton Publishing, Inc.

Chapter 53

- Fig. 53-1. William Sheets.
- Fig. 53-2. William Sheets.

Chapter 54

- Fig. 54-1. Reprinted with permission from Popular Electronics, 10/94, p. 28. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 54-2. Reprinted with permission from Popular Electronics, 10/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 55

- Fig. 55-1. Reprinted with permission from Electronic Design, 10/94, pp. 94–96. Copyright 1994, Penton Publishing, Inc.
- Fig. 55-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1033.
- Fig. 55-3. NASA Tech Briefs, January 1995, pp. 28–29.
- Fig. 55-4. Linear Technology, 2/95.
- Fig. 55-5. Reprinted with permission from Popular Electronics, Fact Card No. 249. (C) Copyright Gernsback Publications, Inc.
- Fig. 55-6. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.
- Fig. 55-7. William Sheets.

Chapter 56

- Fig. 56-1. 73 Amateur Radio Today, 5/94, p. 12.
- Fig. 56-2. 73 Amateur Radio Today, 6/94, pp. 46–48.
- Fig. 56-3. Reprinted with permission from Popular Electronics, 5/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.

Chapter 57

- Fig. 57-1. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 167–169.
- Fig. 57-2. Reprinted with permission from Electronic Design, 10/94, pp. 104–105. Copyright 1994, Penton Publishing, Inc.
- Fig. 57-3. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 355.
- Fig. 57-4. Electronics Now, 5/95, p. 8.
- Fig. 57-5. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 166–167.
- Fig. 57-6. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 163–166.
- Fig. 57-7. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 48.
- Fig. 57-8. Reprinted with permission from Electronics Now, 5/94, p. 10. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 57-9. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 357.

Chapter 58

- Fig. 58-1. William Sheets.
- Fig. 58-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 240.
- Fig. 58-3. Reprinted with permission from Popular Electronics, 1/94, p. 72. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 58-4. Reprinted with permission from Popular Electronics, 1/94, p. 73. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 58-5. Reprinted with permission from Popular Electronics, Fact Card No. 268.(C) Copyright Gernsback Publications, Inc.
- Fig. 58-6. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 24.
- Fig. 58-7. William Sheets.

Chapter 59

Fig. 59-1. Reprinted with permission of Na-

tional Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 1-38.

- Fig. 59-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor NSLAH 1991, p. 998.
- Fig. 59-3. QST, 10/92, p. 22.
- Fig. 59-4. William Sheets.
- Fig. 59-5. William Sheets.

Chapter 60

- Fig. 60-1. Reprinted with permission from Radio-Electronics, June 1987, p. 69.(C) Copyright Gernsback Publications, Inc., 1987.
- Fig. 60-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Handbook, 1991, p. 578.
- Fig. 60-3. Reprinted with permission from Radio-Electronics, June 1987, p. 70. (C) Copyright Gernsback Publications, Inc., 1987.
- Fig. 60-4. Reprinted with permission from Radio-Electronics, June 1987, p. 75. (C) Copyright Gernsback Publications, Inc., 1987.
- Fig. 60-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, P. 576.
- Fig. 60-6. Reprinted with permission from Electronic Design, 12/94, p. 118. Copyright 1994, Penton Publishing, Inc.
- Fig. 60-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Handbook, 1991, p. 1058.
- Fig. 60-8. Reprinted with permission from Radio-Electronics, June 1987, p. 75. (C) Copyright Gernsback Publications, Inc., 1987.
- Fig. 60-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 491.
- Fig. 60-10. Reprinted with permission of National Semiconductor Corporation,

National Semiconductor Linear Applications Handbook, 1991, p. 578.

Fig. 60-11. Analog Devices, Analog Dialogue, Vol. 27, No. 2 (1993), p. 17.

Chapter 61

- Fig. 61-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, p. 1209.
- Fig. 61-2. William Sheets.
- Fig. 61-3. William Sheets.
- Fig. 61-4. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 17.
- Fig. 61-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, P. 1210.
- Fig. 61-6. William Sheets.
- Fig. 61-7. Reprinted with permission from Popular Electronics, 11/94, p. 31. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 61-8. William Sheets.
- Fig. 61-9. Reprinted with permission from Popular Electronics, 5/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 61-10. William Sheets.
- Fig. 61-11. Reprinted with permission from Popular Electronics, 3/94, p. 83. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 61-12. Reprinted with permission from Popular Electronics, 12/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 62-1. Reprinted with permission from Popular Electronics, 12/93, p. 70. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 62-2. Reprinted with permission from Popular Electronics, 12/93, p. 68. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 62-3. Reprinted with permission from

Popular Electronics, 12/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 62-4. Reprinted with permission from Popular Electronics, 12/93, p. 70. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 62-5. Reprinted with permission from Electronic Design, 11/94, pp. 130–132. Copyright 1994, Penton Publishing, Inc.
- Fig. 62-6. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 79.
- Fig. 62-7. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 116.
- Fig. 62-8. Reprinted with permission from Electronics Now, 12/93, p. 16. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 62-9. Reprinted with permission from Electronic Design, 7/94, p. 94. Copyright 1994, Penton Publishing, Inc.
- Fig. 62-10. QST, 5/95, p. 50.

Chapter 63

- Fig. 63-1. William Sheets.
- Fig. 63-2. Reprinted with permission from Popular Electronics, 3/94, p. 84. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 63-3. William Sheets.
- Fig. 63-4. William Sheets.
- Fig. 63-5. QST, 4/95, pp. 38-39.
- Fig. 63-6. William Sheets.
- Fig. 63-7. Reprinted with permission from Radio-Electronics Experimenters Handbook, p. 75. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 63-8. Radio Receiver Projects You Can Build, McGraw-Hill, p. 237.
- Fig. 63-9. William Sheets.
- Fig. 63-10. Reprinted with permission from Popular Electronics, 2/94, p. 90. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 63-11. William Sheets.
- Fig. 63-12. Reprinted with permission from Popular Electronics, 11/94, p. 42. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 63-13. Reprinted with permission from Popular Electronics, 2/94, p. 90. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 63-14. Reprinted with permission from Electronic Design, 10/94, p. 96. Copyright 1994, Penton Publishing, Inc.
- Fig. 63-15. William Sheets.
- Fig. 63-16. 73 Amateur Radio Today, 5/94, p. 66.
- Fig. 63-17. Radio Craft, 1993, p. 63.
- Fig. 63-18. Radio-Electronics Experimenters Handbook, 1992, p. 76.
- Fig. 63-19. William Sheets.
- Fig. 63-20. William Sheets.
- Fig. 63-21. William Sheets.

Chapter 64

- Fig. 64-1. Reprinted with permission from Electronics Now, 5/95, pp. 65–66. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 64-2. Reprinted with permission from Electronic Design, 11/94, pp. 118–120. Copyright 1994, Penton Publishing, Inc.
- Fig. 64-3. Reprinted with permission from Electronic Design, 9/94, p. 84. Copyright 1994, Penton Publishing, Inc.
- Fig. 64-4. 73 Amateur Radio Today, 7/94, p. 39.

Chapter 65

- Fig. 65-1. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 107–108.
- Fig. 65-2. Reprinted with permission from Electronics Now, 5/95, p. 91. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 65-3. 1994 Electronics Experimenters Handbook, p. 67.

- Fig. 66-1. Reprinted with permission from Popular Electronics, 3/94, p. 70. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 66-2. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 94.

- Fig. 67-1. Reprinted with permission from Electronics Now, 5/95, pp. 67–68. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 67-2. Reprinted with permission from Popular Electronics, 10/94, p. 84. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 67-3. Reprinted with permission from Electronics Now, 3/94, p. 59. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 67-4. Reprinted with permission from Popular Electronics, 12/94, pp. 57–59.(C) Copyright Gernsback Publications, Inc., 1994.

Chapter 68

- Fig. 68-1. Reprinted with permission from Popular Electronics, 4/95, p. 60. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 68-2. Reprinted with permission from Popular Electronics, 4/95, p. 60. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 68-3. Reprinted with permission from Electronic Design, 11/94, p. 133. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-4. Reprinted with permission from Popular Electronics, 4/90, pp. 45–46.
 (C) Copyright Gernsback Publications, Inc., 1990.
- Fig. 68-5. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-131.
- Fig. 68-6. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 133.
- Fig. 68-7. Linear Technology, Design Note #87.
- Fig. 68-8. 1994 Electronics Experimenters Handbook, p. 39.
- Fig. 68-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 449.
- Fig. 68-10. Línear Technology, Design Note #74.
- Fig. 68-11. Reprinted with permission from

Radio-Electronics Experimenters Handbook 1992, p. 74. (C) Copyright Gernsback Publications, Inc., 1992.

- Fig. 68-12. William Sheets.
- Fig. 68-13. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 30.
- Fig. 68-14. Reprinted with permission from Electronic Design, 7/94, p. 34. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-15. Reprinted with permission from Electronic Design, 6/94, p. 32. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-16. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 161–163.
- Fig. 68-17. NASA Tech Briefs, August 1994, p. 39.
- Fig. 68-18. Lincar Technology, Design Note #87.
- Fig. 68-19. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 367.
- Fig. 68-20. Reprinted with permission from Electronic Design, 12/94, p. 130. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-21. Reprinted with permission from Electronic Design, 10/94, pp. 108–110. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-22. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1063.
- Fig. 68-23. Reprinted with permission from Popular Electronics, 6/95, p. 78. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 68-24. Linear Technology, Design Note #74.
- Fig. 68-25. Reprinted with permission from Electronic Design, 9/94, p. 140. Copyright 1994, Penton Publishing, Inc.
- Fig. 68-26. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1063.
- Fig. 68-27. Reprinted with permission from

Electronic Design, 7/94, p. 30. Copyright 1994, Penton Publishing, Inc.

- Fig. 68-28. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 450.
- Fig. 68-29. William Sheets.
- Fig. 68-30. Maxim, Vol. III, New Releases Data Book, 1994, p. 4-131.
- Fig. 68-31. Laser Cookbook, McGraw-Hill, p. 172.
- Fig. 68-32. Analog Devices, Analog Dialogue, Vol. 27, No. 2, p. 19.
- Fig. 68-33. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 450.
- Fig. 68-34. Laser Cookbook, McGraw-Hill, p. 172.
- Fig. 68-35. Reprinted with permission from Popular Electronics, 5/95, p. 94. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 68-36. 73 Amateur Radio Today, 5/93, p. 51.
- Fig. 68-37. Reprinted with permission from Electronics Now, 12/93, p. 14. (C) Copyright Gernsback Publications, Inc., 1993.

Chapter 69

- Fig. 69-1. Reprinted with permission from Popular Electronics, 6/93, p. 77. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 69-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 351.
- Fig. 69-3. Reprinted with permission from Electronics Now, 10/94, pp. 58–61. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 69-4. William Sheets.
- Fig. 69-5. Reprinted with permission from Popular Electronics, 6/93, p. 77. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 69-6. Laser Cookbook, McGraw-Hill, p. 163.

- Fig. 69-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 498.
- Fig. 69-8. Fantastic Electronics, McGraw-Hill, p. 177.
- Fig. 69-9. Gordon McComb's Gadgeteer's Goldmine, p. 269.
- Fig. 69-10. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 497.
- Fig. 69-11. Laser Cookbook, McGraw-Hill, pp. 160–161.

Chapter 70

- Fig. 70-1. 73 Amateur Radio Today, 5/93, p. 32.
- Fig. 70-2. Laser Cookbook, McGraw-Hill, p. 172.
- Fig. 70-3. Reprinted with permission from Electronic Design, 5/90, p. 80. Copyright 1990, Penton Publishing, Inc.
- Fig. 70-4. Linear Technology, Design Note #99.
- Fig. 70-5. Radio Receiver Projects You Can Build, McGraw-Hill 4256, p. 241.
- Fig. 70-6. Reprinted with permission from Popular Electronics, 11/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 70-7. Linear Technology, Design Note #78.
- Fig. 70-8. Reprinted with permission from Electronics Now, 2/94, p. 83. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 70-9. Reprinted with permission from Radio-Electronics, June 1987, p. 75. (C) Copyright Gernsback Publications, Inc., 1987.

- Fig. 71-1. Reprinted with permission from Popular Electronics, 4/95, p. 96. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 71-2. Reprinted with permission from Electronic Design, 6/94, p. 62. Copyright 1994, Penton Publishing, Inc.

- Fig. 71-3. QST, 10/92, p. 50.
- Fig. 71-4. William Sheets.
- Fig. 71-5. Reprinted with permission from Popular Electronics, 4/95, p. 96. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 71-6. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 450.
- Fig. 71-7. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 495.
- Fig. 71-8. William Sheets.

- Fig. 72-1. Reprinted with permission from Electronic Design, 1/95, p. 133. Copyright 1995, Penton Publishing, Inc.
- Fig. 72-2. Reprinted with permission from Electronics Now, 3/95, p. 64. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 72-3. 73 Amateur Radio Today, 6/83, p. 99.
- Fig. 72-4. Reprinted with permission from Popular Electronics, 2/94, p. 58. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 72-5. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 20.
- Fig. 72-6. Reprinted with permission from Radio-Electronics Experimenters Handbook, pp. 77–82. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 73

- Fig. 73-1. Reprinted with permission from Popular Electronics, 11/94, pp. 31 and 91. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 73-2. William Sheets.

Chapter 74

- Fig. 74-1. Reprinted with permission from Popular Electronics, 6/95, p. 38. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 74-2. Reprinted with permission from

Popular Electronics, 6/95, p. 39. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 75

- Fig. 75-1. Fantastic Electronics, McGraw-Hill, pp. 67–73.
- Fig. 75-2. Reprinted with permission from Electronics Now, 1/94, p. 61. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 75-3. Reprinted with permission from Electronics Now, 1/94, p. 61. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 75-4. Reprinted with permission from Electronics Now, 1/94, p. 59. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 75-5. Reprinted with permission from Popular Electronics, 5/93, p. 40. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 76-1. Reprinted with permission from Popular Electronics, 5/95, p. 66. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 76-2. Reprinted with permission from Popular Electronics, 1/95, p. 49. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 76-3. Radio Receiver Projects You Can Build, McGraw-Hill 4256, pp. 122–129.
- Fig. 76-4. Radio-Electronics-Experimenters Handbook, p. 65.
- Fig. 76-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 2-38.
- Fig. 76-6. Radio Craft, 1993, p. 50.
- Fig. 76-7. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), pp. 15-16.
- Fig. 76-8. Reprinted with permission from Popular Electronics, 3/94, p. 35. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-9. Radio Receiver Projects You Can Build, McGraw-Hill, pp. 158–165.
- Fig. 76-10. Radio Receiver Projects You Can Build, McGraw-Hill, pp. 138–147.

- Fig. 76-11. Radio Receiver Projects You Can Build, McGraw-Hill, pp. 102–109.
- Fig. 76-12. Radio Receiver Projects You Can Build, McGraw-Hill, pp. 196–203.
- Fig. 76-13. Radio Receiver Projects You Can Build, McGraw-Hill, pp. 32–41.
- Fig. 76-14. Analog Devices, Analog Dialogue, Vol. 26, No. 2, 1992, p. 19.
- Fig. 76-15. Reprinted with permission from Popular Electronics, 5/94, p. 79. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-16. Reprinted with permission from Popular Electronics, 10/94, p. 25. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-17. Reprinted with permission from Electronics Now, 3/94, p. 68. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-18. Reprinted with permission from Electronics Now, 3/94, p. 67. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-19. Reprinted with permission from Popular Electronics, 10/94, p. 62. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-20. Analog Devices, Analog Dialogue, Vol. 27, No. 1 (1993), p. 15.
- Fig. 76-21. Radio Craft, 1993, p. 64.
- Fig. 76-22. William Sheets.
- Fig. 76-23. Reprinted with permission from Electronics Now, 3/94, p. 69. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-24. Reprinted with permission from Electronics Now, 3/94, p. 69. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-25. Reprinted with permission from Electronics Now, 3/94, pp. 70–72. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 76-26. Reprinted with permission from Popular Electronics, 5/95, pp. 55-56. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 76-27. William Sheets.
- Fig. 76-28. Reprinted with permission from Electronics Now, 3/95, p. 50. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 77-1. Reprinted with permission from Electronic Design, 6/94, p. 29. Copyright 1995, Penton Publishing, Inc.
- Fig. 77-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 26.
- Fig. 77-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 26.

Chapter 78

- Fig. 78-1. Linear Technology, Design Note #98.
- Fig. 78-2. Reprinted with permission from Electronics Now, 7/94, p. 12. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 78-3. Reprinted with permission from Electronic Design, 2/95, p. 118. Copyright 1995, Penton Publishing, Inc.
- Fig. 78-4. Linear Technology, Design Note #100.
- Fig. 78-5. Linear Technology, Design Note #98.
- Fig. 78-6. NASA Tech Briefs, August 1994, p. 38.
- Fig. 78-7. Linear Technology, Advertisement LT/1294.
- Fig. 78-8. Reprinted with permission from Electronic Design, 7/94, p. 32. Copyright 1994, Penton Publishing, Inc.
- Fig. 78-9. Reprinted with permission from Electronic Design, 1/95, pp. 133–134. Copyright 1995, Penton Publishing, Inc.
- Fig. 78-10. Linear Technology, Design Note #98.

- Fig. 79-1. William Sheets.
- Fig. 79-2. William Sheets.
- Fig. 79-3. William Sheets.
- Fig. 79-4. William Sheets.
- Fig. 79-5. William Sheets.
- Fig. 79-6. William Sheets.
- Fig. 79-7. William Sheets.

- Fig. 80-1. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-30.
- Fig. 80-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1202.

Chapter 81

- Fig. 81-1. Reprinted with permission from Popular Electronics, 11/94, pp. 75–76.(C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 81-2. Reprinted with permission from Popular Electronics, 11/94, pp. 74–75.(C) Copyright Gernsback Publications, Inc., 1994.

Chapter 82

- Fig. 82-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 1-37.
- Fig. 82-2. Reprinted with permission from Popular Electronics, 9/94, p. 73. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 82-3. 73 Amateur Radio Today, 4/95, pp. 54–58.

Chapter 83

- Fig. 83-1. William Sheets.
- Fig. 83-2. William Sheets.
- Fig. 83-3. Reprinted with permission from Popular Electronics, 5/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 83-4. William Sheets.
- Fig. 83-5. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 105–106.

Chapter 84

- Fig. 84-1. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 106–110.
- Fig. 84-2. Reprinted with permission from Popular Electronics, 1/94, p. 75. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 84-3. 1994 Electronic Experimenters Handbook, p. 53.
- Fig. 84-4. William Sheets.
- Fig. 84-5. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 98–100.
- Fig. 84-6. Sound Light and Music, Delton T. Horn, McGraw-Hill, pp. 114–115.
- Fig. 84-7. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 147.
- Fig. 84-8. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 127.

Chapter 85

- Fig. 85-1. Reprinted with permission from Popular Electronics, Fact Card No. 221. (C) Copyright Gernsback Publications, Inc.
- Fig. 85-2. William Sheets.

Chapter 86

- Fig. 86-1. Reprinted with permission from Popular Electronics, 11/94, pp. 76 and 91. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 86-2. William Sheets.
- Fig. 86-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 235.
- Fig. 86-4. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 236.

Chapter 87

- Fig. 87-1. Reprinted with permission from Electronic Design, 7/94, p. 94. Copyright 1994, Penton Publishing, Inc.
- Fig. 87-2. Reprinted with permission from Electronics Now, 2/94, p. 55. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 87-3. Reprinted with permission from Electronics Now, 2/94, p. 57. (C) Copyright Gernsback Publications, Inc., 1994.

Chapter 88

Fig. 88-1. Reprinted with permission from Popular Electronics, 6/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.

- Fig. 88-2. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 117.
- Fig. 88-3. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 117.
- Fig. 88-4. Reprinted with permission from Electronic Design, 7/94, pp. 96–97. Copyright 1994, Penton Publishing, Inc.
- Fig. 88-5. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 117.
- Fig. 88-6. Reprinted with permission from Popular Electronics, 6/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 88-7. Reprinted with permission from Electronics Now, 5/95, p. 63. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 88-8. Reprinted with permission from Electronic Design, 1/94, p. 118. Copyright 1994, Penton Publishing, Inc.
- Fig. 88-9. Reprinted with permission from Popular Electronics, 12/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-10. Reprinted with permission from Popular Electronics, 12/94, p. 42. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-11. Reprinted with permission from Popular Electronics, 12/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-12. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 72.
- Fig. 88-13. Reprinted with permission from Popular Electronics, 12/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-14. Reprinted with permission from Popular Electronics, 12/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-15. Reprinted with permission from Popular Electronics, 12/94, p. 41. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 88-16. Maxim, Vol. III, New Releases

Data Book, 1994, p. 3-125.

- Fig. 88-17. William Sheets.
- Fig. 88-18. Reprinted with permission from Popular Electronics, 6/93, p. 71. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 88-19. William Sheets.
- Fig. 88-20. Reprinted with permission from Popular Electronics, 6/93, p. 72. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 88-21. Electronics Now, 8/93, p. 12.
- Fig. 88-22. William Sheets.
- Fig. 88-23. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 117.

Chapter 89

- Fig. 89-1. Reprinted with permission from Electronic Design, 10/88, pp. 126-128. Copyright 1988, Penton Publishing, Inc.
- Fig. 89-2. Analog Devices, Analog Dialogue, Vol. 26, No. 1, 1992, p. 12.
- Fig. 89-3. Reprinted with permission from Electronic Design, 11/93, p. 99. Copyright 1993, Penton Publishing, Inc.
- Fig. 89-4. Analog Devices, Analog Dialogue, Vol. 26, No. 1, 1992, p. 13.
- Fig. 89-5. Reprinted with permission from Electronic Design, 10/88, p. 128. Copyright 1988, Penton Publishing, Inc.

- Fig. 90-1. Reprinted with permission from 1987 Radio-Electronics Experimenters Handbook, p. 51. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 90-2. Reprinted with permission from Electronics Now, 2/94, p. 33. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 90-3. Reprinted with permission from Electronics Now, 10/94, p. 53. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 90-4. 1994 Electronics Experimenters Handbook, p. 123.
- Fig. 90-5. Reprinted with permission from Electronics Now, 4/95, pp. 39–40. (C) Copyright Gernsback Publications, Inc., 1995.

- Fig. 90-6. Reprinted with permission from Electronics Now, 8/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 90-7. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.
- Fig. 90-8. Reprinted with permission from Popular Electronics, 12/93, p. 62. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 90-9. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, pp. 335–336.
- Fig. 90-10. Reprinted with permission from Electronics Now, 2/94, p. 16. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 90-11. Reprinted with permission from Electronics Now, 8/93, pp. 58–63. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 90-12. Reprinted with permission from Radio-Electronics, August 1993, pp. 58–63. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 90-13. Reprinted with permission from Electronic Design, 8/94, p. 116. Copyright 1994, Penton Publishing, Inc.
- Fig. 90-14. William Sheets.

- Fig. 91-1. 1994 Electronics Experimenters Handbook, p. 63.
- Fig. 91-2. Reprinted with permission from Electronic Design, 7/94, p. 93. Copyright 1994, Penton Publishing, Inc.
- Fig. 91-3. Reprinted with permission from Electronic Design, 11/93, pp. 90–92. Copyright 1993, Penton Publishing, Inc.
- Fig. 91-4. Reprinted with permission from Electronic Design, 1/95, pp. 80–81. Copyright 1995, Penton Publishing, Inc.
- Fig. 91-5. Reprinted with permission from Popular Electronics, 6/95, p. 48. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 91-6. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 524.
- Fig. 91-7. Reprinted with permission from Electronic Design, 1/94, pp. 118–119.

Copyright 1994, Penton Publishing, Inc.

- Fig. 91-8. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 524.
- Fig. 91-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 500.
- Fig. 91-10. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1076.
- Fig. 91-11. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1076.
- Fig. 91-12. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1076.
- Fig. 91-13. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1076.
- Fig. 91-14. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.
- Fig. 91-15. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 75.
- Fig. 91-16. Reprinted with permission of National Semiconductor Corporation, National Semiconductor, NSLAH 1991, p. 1079.
- Fig. 91-17. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 493.
- Fig. 91-18. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1077.
- Fig. 91-19. Reprinted with permission from Popular Electronics, 5/93, p. 43. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 91-20. Reprinted with permission of Burr-Brown Corporation, Burr-Brown Data Sheet INA118, (C) 1989–1995 Burr-Brown Corporation.

- Fig. 91-21. Analog Devices, Analog Dialogue, Vol. 27, No. 2, p. 22.
- Fig. 91-22. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1076.
- Fig. 91-23. QST, 5/95, p. 85.
- Fig. 91-24. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications.Handbook, 1991, p. 523.
- Fig. 91-25. Reprinted with permission from Popular Electronics, 1/95, p. 28. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 91-26. QST, 5/95, p. 85.
- Fig. 91-27. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 1079.
- Fig. 91-28. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Lincar Applications Handbook, 1991, p. 1076.
- Fig. 91-29. Reprinted with permission from Popular Electronics, 1/95, p. 29. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 91-30. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, pp. 163–164.

- Fig. 92-1. Reprinted with permission from Popular Electronics, 9/94, p. 26. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 92-2. Reprinted with permission from Popular Electronics, 2/94, p. 25. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 92-3. Reprinted with permission from Electronic Design, 3/95, pp. 114–116. Copyright 1995, Penton Publishing, Inc.

Chapter 93

- Fig. 93-1. William Sheets.
- Fig. 93-2. William Sheets.
- Fig. 93-3. William Sheets.

Fig. 93-4. William Sheets.

Chapter 94

- Fig. 94-1. William Sheets.
- Fig. 94-2. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, McGraw-Hill, p. 92.
- Fig. 94-3. NASA Tech Briefs, August 1994, pp. 34–35.
- Fig. 94-4. William Sheets.
- Fig. 94-5. Reprinted with permission from Popular Electronics, Fact Card No. 270.(C) Copyright Gernsback Publications, Inc.

Chapter 95

- Fig. 95-1. Spring 1994 Electronics Hobbyist Handbook.
- Fig. 95-2. Reprinted with permission from Electronics Now, 5/95, p. 8. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 95-3. Reprinted with permission from Popular Electronics, Fact Card No. 221.(C) Copyright Gernsback Publications, Inc.

- Fig. 96-1. Reprinted with permission from Electronics Now, 6/93, pp. 41–46. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 96-2. Reprinted with permission from Electronics Now, 12/93, p. 29. (Č) Copyright Gernsback Publications, Inc., 1993.
- Fig. 96-3. 1994 Electronics Experimenters Handbook, p. 105.
- Fig. 96-4. Reprinted with permission from Electronics Now, 1994 Experimenters Handbook, p. 77. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 96-5. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, pp. 340–341.
- Fig. 96-6. 73 Amateur Radio Today, 5/93, p. 56.
- Fig. 96-7. Reprinted with permission from Popular Electronics, 8/92, p. 45. (C) Copyright Gernsback Publications, Inc., 1992.

- Fig. 97-1. Reprinted with permission from Popular Electronics, 5/95, p. 29. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 97-2. Reprinted with permission from Popular Electronics, 1/95, pp. 72–73.
 (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 97-3. Reprinted with permission from Popular Electronics, 1/95, p. 71. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 97-4. Reprinted with permission from Popular Electronics, 1/95, p. 73. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 97-5. Reprinted with permission from Popular Electronics, 12/94, p. 72. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 97-6. Reprinted with permission from Popular Electronics, 12/94, pp. 74–75.(C) Copyright Gernsback Publications, Inc., 1994.

Chapter 98

- Fig. 98-1. Reprinted with permission from Electronics Now, 5/95, pp. 50–51. (C) Copyright Gernsback Publications, Inc., 1995.
- Fig. 98-2. Analog Devices, AD8001 Data Sheet.
- Fig. 98-3. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 3-50.
- Fig. 98-4. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 3-33.
- Fig. 98-5. Reprinted with permission from Radio-Electronics Experimenters Handbook, pp. 83–88, 1994. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 98-6. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, p. 1021.

- Fig. 98-7. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-16.
- Fig. 98-8. 73 Amateur Radio Today, 7/93, p. 74.
- Fig. 98-9. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 3-32.
- Fig. 98-10. 73 Amateur Radio Today, 7/93, p. 74.
- Fig. 98-11. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 3-13.
- Fig. 98-12. Linear Technology, Design Note #92.
- Fig. 98-13. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-16.
- Fig. 98-14. Reprinted with permission from Popular Electronics, Fact Card No. 268. (C) Copyright Gernsback Publications, Inc.
- Fig. 98-15. Maxim, Vol. III, New Releases Data Book, 1994, p. 8-19.
- Fig. 98-16. Linear Technology, 2/95.
- Fig. 98-17. Analog Dialogue, Analog Devices, Vol. 26, No. 1, 1992, p. 11.

Chapter 99

- Fig. 99-1. Analog Devices, The Best of Analog Dialogue, 1967–1991, p.75.
- Fig. 99-2. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Application Specific IC's Databook 1993, p. 1-37.

Chapter 100

- Fig. 100-1. Reprinted with permission from Popular Electronics, Fact Card No. 269.(C) Copyright Gernsback Publications, Inc.
- Fig. 100-2. Analog Devices, The Best of Analog Dialogue, 1967–1991, p. 79.

Chapter 101

Fig. 101-1. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 500.

- Fig. 101-2. Maxim, Vol. III, New Releases Data Book, 1994, p. 3-126.
- Fig. 101-3. Reprinted with permission from Electronic Design, 11/94, pp. 127–128. Copyright 1994, Penton Publishing, Inc.
- Fig. 101-4. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 207.
- Fig. 101-5. QST, 4/95, p. 61.
- Fig. 101-6. 73 Amateur Radio Today, 3/95, p 63.
- Fig. 101-7. Reprinted with permission from Popular Electronics, 5/94, p. 80. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 101-8. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 499.
- Fig. 101-9. Reprinted with permission from Popular Electronics, 5/94, p. 79. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 101-10. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 206.

- Fig. 102-1. Reprinted with permission from Popular Electronics, 11/94, p. 74. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 102-2. Reprinted with permission from Popular Electronics, 5/94, p. 90. (C) Copyright Gernsback Publications, Inc., 1994.

- Fig. 102-3. Reprinted with permission from Electronic Design, 12/94, pp. 118–119. Copyright 1994, Penton Publishing, Inc.
- Fig. 102-4. Reprinted with permission from Electronics Now, 8/93, p. 14. (C) Copyright Gernsback Publications, Inc., 1993.
- Fig. 102-5. Reprinted with permission of National Semiconductor Corporation, National Semiconductor Linear Applications Handbook, 1991, p. 208.
- Fig. 102-6. Gordon McComb's Gadgeteer's Goldmine, McGraw-Hill, p. 197.
- Fig. 102-7. Amplifiers, Waveform Generators & Other Low-Cost IC Projects, Mc-Graw-Hill, p. 21.
- Fig. 102-8. Reprinted with permission from Popular Electronics, 11/94, pp. 76 and 91. (C) Copyright Gernsback Publications, Inc., 1994.
- Fig. 102-9. Reprinted with permission from Electronic Design, 7/94, p. 96. Copyright 1994, Penton Publishing, Inc.
- Fig. 102-10. Power Supplies, Switching Regulators, Inverters, and Converters, Mc-Graw-Hill, p. 129.
- Fig. 102-11. Reprinted with permission from Electronics Now, 3/95, p. 63. (C) Copyright Gernsback Publications, Inc., 1995.

Chapter 103

- Fig. 103-1. 73 Amateur Radio Today, 12/93, p. 70.
- Fig. 103-2. 73 Amateur Radio Today, 12/93, p. 72.

- Fig. 104-1. William Sheets.
- Fig. 104-2. William Sheets.

Index

Numbers preceded by an "I", "II", "IV", "V", or "VI" are from *Encyclopedia of Electronic Circuits* Vol. I, II, III, IV, V, or VI respectively.

A

absolute-value circuits, I-37, IV-274 amphfier, I-31 full wave rectifier, II-528 Norton amplifier, III-11 precision, I-37, IV-274 ac amplifier, high input impedance, VÎ-55 ac hne/timer interface. VI-281 ac motors (see also motor control circuits) control for, II-375 power brake, II-451 three-phase driver for, II-383 two-phase driver for, I-456, II-382 ac power monitor, VI-351 ac/dc indicator, IV-214 ac-to-de converters, I-165 fixed power supplies, IV-395 full-wave, IV-120 high-impedance precision rectifier, Ĩ-164 acceleronicter, VI-345 acid rain monitor, II-245, III-361, V-371 acoustic field generator, V-338-341 acoustic sound receiver/transmitter, IV-311 active antennas (see antennas, active) active filters (see also filter circuits) band reject, II-401 bandpass, III-190, II-221, II-223 variable bandwidth, 1-286 digitally tuned low-power, II-218 five pole, 1-279 fourth-order low-pass, V-184 high-pass, V-180, V-188 fourth-order, V-188 second-order, I-297 low-pass, V-178, V-181, V-188 digitally selected break frequency, II-216 unity-gam, V 187 low-nower digitally selectable center frequency, III-186 digitally tuned, I-279 programmable, III-185 RC, up to 150 kHz, 1-294 speech-range filter, V-185 state-variable, III-189 ten-band graphic equalizer using, II-684 three-amplifier, I-289 tunable, I-289 universal, II-214 adapters (see also conversion and converters) de transceiver, hand-held, III-461 line-voltage-to-multimeter adapter, V-812

program, second-audio, ill-142 traveller's shaver, I-495 adder circuits, III-327 binary, fast-action, IV-260-261 AFSK generator, one chip, VI-23 AGC (see automatic gam control (AGC) air conditioner, auto, smart clutch for, 111-46 aircraft receiver, 118- to 136-MHz, VI-542 air motion and pressure barometer, VI-338 electronic anemometer, VI-6 flow-detector, I-235, II-240-242, III-202-203, IV-82, V-154, VI-4-6, VI-183 flow-meters (anemometers) hot-wire, III-342, V-5, VI-4-6. VI-183 thermally based, II-241 pressure change detector, IV-144 motion detector, I-222, III-364 airplane propeller sound effect, II-592 alarms (see also annuclators; sirens). I-4, III-3-9, IV-84-89, V-1-16, VI-7-16 555-based alarm, V 11 alarm-tone generator, V-563 amateur radio on-alarm and timer, VI-32 audio-sensor alarm, V-8 auto burglar, I-3, 1-7, I-10, II-2, III-4, IV-53 alarm decoy, VI-13 automatic-arming, IV-50 automatic turn-off, 8 minute delay, IV-52 CMOS low-current, IV-56 horn as loudspeaker, IV-54 motion-actuated car/motorcycle, I-9 security system, I-5, IV-49-56, VI-9, VI-11 single IC, III-7, IV-55 auto-arming automotive alarm, IV-50 automatic turn-off, IV-54 8 mmute delay, IV-52 baby-alert transmitter/receiver, V-95-96 backup battery low alarm, VI-110 bells, electronic, II-33, I-636 blown fuse, I-10 boat, I-9 body-heat detector, VI-266 burgiar alarms, III-8, III-9, IV 86, VI-8 burglar chaser, V-16 latching circuit, I-8, I-12 NC and NO switches, IV-87 NC switches, IV-87

one-chip, III-5 self-latching, IV-85 timed shutoff, IV-85 camera triggered, III-444 capacitive sensor, III-515 current monitor and, III-338 dark-activated alarm, pulsed tone output, V-13 delayed alarm, V-4 differential voltage or current, II-3 digital clock circuit with, III-84 door-ajar, 11-284, III-46, VI-14 Hall-effect circuit, III-256 door minder, V-5 doorbells (see annuciators) driver, high-power alarm driver, V-2 exit delay for burglar alarms. V-10 fail-sale, semiconductor, III-6 field disturbance, II-507 flasher signal, V-197 flashing brake light for motorcycles, VI-12 flex switch alarm sounder, V-15 flood, 1-390, III-206, IV-188, V-374 freezer meltdown, I-13 headlights-on, III-52, V-77 heat-activated alarm, V-9 high/low-limit, I-151 home security system, I-6, IV-87, VI-10-11 ice formation, II-58 infrared wireless system, IV-222-223latching relay alarm circuit, VI-569 light-activated, V-9, V-273 high-output, pulsed tone, V-14 precision design, V-12 precision with hysteresis, V-14 self-latch, tone output, V-15 with latch, V-12 light-beam intruder-detection alarm, V-11, V 13 loop circuit alarms closed-loop, V-3 multi-loop parallel alarm, V-2 parallel, V-3 series/parallel, V-3 low-battery disconnect and, III-65 low-battery warning, ill-59 low-volts, II-493 motorcycle alarm, VI-13 motorcycle burglar alarm, VI-15 motorcycle horn alarm, VI-14, VI-15 multiple circuit for, II-2 no-doze alarm, V-8 one-chip, III-5 photoelectric, II-4, II-319 piezoelectric, 1-12, V-10 power failure, 1-581, I-582, III-511 printer error, IV-106 proximity, II-506. III-517, V-485-486, VI-657

pulsed-tone, I-11, V-559 purse-snatcher, capacitance operated, 1-134 rain, I-442, 1-443, IV-189 road ice, II-57 security, I-4, III-3-9 self-arming, 1-2 sensor amplifier, sensor amplifier, VI-52 shutoff, automatic, I-4 signal-reception, receivers, III-270 silent alarm, V-16 siren, V-559 smoke alarms, II-278, III-246-253 gas, 1-332 ionization chamber, I-332-333 line-operated, IV-140 operated ionization type, I-596 photoelectric, line-operated, I-596 SCR, III-251 solar powered, I-13 sonic defenders, IV-324 spaceship alarm, V-560 speed, I-95 Star Trck red alert, II-577 strobe flasher alarm, IV-180, V-6 tamperproof burglar, I-8 temperature (see also temperaturerelated circuits), H-4, II-643 adjustable threshold, II-644 light, radiation sensitive, II-4 timer, II-674 trouble tone alert, II-3 turn signal use alarm, VI-100 varying-frequency warning, II-579 wailing, II-572 warbling, II-573, V-7 watchdog timer/alarm, IV-584 water leakage/level (see also fluid and moisture), I-389, IV-190, V-374allophone generator, III-733 alternators battery-alternator monitor, car, III-63 regulator for automobile alternator. V-76 altmeter, digital readout, V-296 AM radio-related circuits, 1-544 AM and shortwave, ac/dc vacuumtube design, VI-536-537, VI-536 AM-modulated oscillator for wireless microphones, VI-450 amplitude modulator, II-370 broadcast band signal generator, IV-302 car radio to shortwave converter, IV-500 demodulator, II-160 detector, 455-kHz AM, VI-184 cuvelope detector, IV-142 linear (AM) amplitude modulator. VI-402 microphone, wireless AM microphone, I-679 modulation monitor, IV-299 power amphfier for, J-77 receivers, II-525, III-81, III-529, III-535, IV-455 V-496, VI-535 1 5 V broadcast, V-497 mixer/oscillator for AM receiver. V-412 transistor radio, V-502 carrier-current, III-81 FM/AM receiver, VI-541 integrated, III-535 one-tube, VI-552

regenerative, one-tube, VI-547 two-chip, VI-550 shortwave radio AM broadcast trap, VI-214 signal generators, IV-301, IV-302 tuned collector oscillator, for AM broadcast band, VI-454 AM/FM-related circuits clock radio, II-543, III-1 squelch circuit, II-547, III-1 amateur radio related circuits (see also amateur television), VI-17-32 AFSK generator, one-chip, VI-23 amplifier control circuitry, 1.2-kW 144-MHz, VI-19 amplifier power supply, 1.2-kW 144-MHz, VI-18 audio breakout box, VI-26-27 battery pack and reverse polarity protection, VI-30 CW audio filter, VI-29 CW identifier, programmable, VI-24 CW transmitter keying circuit, VI-22-23 CW transmitter, one-watt, VI-27 identifier circuit, VI-31 inear amp, 2-30 MHz 140-W, III-260 Incar amplifier, VI-1.2-kW 144-MHz, VI-20 mobile radio on-alarm timer, VI-32 Morse code circuits, VI-404-409 PTT control from receiver audio, VI-28 receiver for, Ill-534 RF line sampler/coupler, VI-30 rf variable-frequency oscillator (VFO), V-532 SSB receiver, VI-80-meter, VI-29 superhet receiver, four-stage 75meter, VI-21 SWR detector adapter, audible, VI-25 transceiver memory backup, VI-28 transceiver relay interface, V-243 transmit keyer interface circuit, VI-31 transmitter, 80-M, III-675 voice identifier, V-550 amateur television (ATV) circuits, 33-45, VI-33 downconverter, 420 to 450 MHz, VI-44-45, VI-44 downconverter, 902 to 928 MHz, VI-40-41, VI-40 dummy load for transmitter tests, VI-37 horizontal deflection circuit, VI-382 mini transmitter, VI-36 parabolic dish microphone amplifier, VI-82 preamp, mast-mounted, VI-37 switching supply for color TV, SCR. VI-487 transmitter for 440 MHz, VI-5-watt, VI-34 transmitter, VI-5-watt, VI-35 transmitter, three-channel, 420- to 450-MHz, VI-4, VI-42 transmitter, three-channel, 902-to 928-MHz, VI-38, VI-38 UHF scanner active antenna, VI-67 vertical deflection circuit, VI-374 video detector for transmitter tests, VI-37 ambience amphfier, rear speaker, II-

mbience amphfier, rear speaker, ll-458

ambient hght effects, cancellation circuit, II-328 ambient light-ignoring optical sensor, 111-413 anuneter, I-201 low-current, V-307 nano, 1-202 pico, II-154, II-157, I-202 guarded input circuit, II-156 six-decade range, II-153, II-156 amplifiers (see also audio amplifiers). II-5-22, III-10-21, V-17-26, VI-46-57 1 watt/2.3 GHz, II-540 2 to 6-W, with preamp, II-451 2 to 30 MHz, 140W amateur radio linear, I-555 4W bridge, 1-79 5W output, two-meter, I-567 6W 8-ohm ouput-transformerless, I-10 dB-gain, III-543 10 W power, I-76 10 x buffer, I-128 12-W low-distortion power, I-76 16-W bridge, I-82 25-watt, II-452 30 MHz, I-567 40 dB gain, IV-36 60 MHz, I-567 80 MHz cascade, I-567 80W PEP broadband/linear, I-557 100 MHz/400 MHz neutralized common source, I-565 100W PEP 420-450 MHz push-pull, 1-554 100x buffer, 1-128 135 to 175 MHz, I-564 160W PEP broadband, I-556 200 MHz neutralized common source, 1-568 450 MHz common-source, I-568 600-W rf power, I-559 absolute-value, 1-31 ac amplifier, noninverting, V-18. V-19 ac amplifier, high input impedance, VI-55 ac servo, bridge type, III-387 ac-coupled, dynamic, III-17 acoustic field generator, V-338-341 AF drive indicator, V-346 AGC. II-17 squeich control, III-33 wide-band, III-15 adjustable-gain noninverting, 1-91 amateur radio, linear, 2 to 30 MHz, 140W, I-555 ambience, rear speaker, II-458 AM radio power, I-77 attenuator and, digitally controlled, I-53 audio (see audio amplifiers) autho converter, two- to four-wire, II - 14aucho hmiter, low-distortion, II-15 audio power amps (see audio and sound circuits, power amps) audio signal amps (see audio and sound circuits, signal amps) audio-to-UHF preamp, V-24 automatic fade circuit for, II-42 automatic level control, II-20 automotive audio amplifier, IV-66 Av/200, stereo, I-77 balance, II-46

amplifiers, continued inverting, I-33 loudness control, II-47, II-395 bandpass amplifier, VI-54 bootstrap circuit, V-356 bridge, I-74 4 watt. 1-79 16 watt, I-82 ac servo, I-458 audio power, I-81 high-impedance, I-353 transducer, III-71, 11-84, 1-351 broadband low-noise, I-562 PEP, 160-W, I-556 linear/PEP, 80W, 1-557 bridge amphfier, VI-122, VI-123 huffers 10x, I-128 100x, I-128 ac, single-supply, 1-126 battery-powered, 1-351 rf amp with modulator, IV-490 sine-wave output, 1-126 unity-gain, stable design. II-6 car stereo booster amp, V-72 cascade, III-13 80 MHz, I-567 cascode, rf amplifiers, IV-488 CD4049 and o signal amp, IV-40 chopper, $\pm 15V.$, III-12 chopper channel, I-350 stabilized, fl-7 clamp-limiting, active, III-15 color video, I-54, III-724 common source 450 MHz, 1-568 low-power, II-84 complementary-symmetry audio, Icomposite, II-8, III-13 compressor/amplifier, lowdistortion, IV-24 constant-bandwidth, III-21 control circuitry, 1.2-kW 144-MHz, VI-19 cool-down circuit, V-354, V-357 crystal tuned amp, VI-57 current feedback amp, 100 mA at 100 MHz, V-25 current-shunt, III-21 current collector head, II-11, Il-295 current probe amplifier, VI-521 current-to-voltage, high-speed, I-35 Darlington, push-pull, V-22 dc servo, I-457 dc-stabilized, fast, III-18 de-to-video log, I-38 detector, MC1330/MC1352, TV IF, 1-688difference amplifier, V-18, V-21, VI-53 differential, I-38, III-14 high-impedance, I-27, I-354 high-input, high-impedance, II-19 instrumentation, I-347, III-283 instrumentation, biomedical, 111-282 programmable gam, III-507 two op amp bridge type, II-83 discrete current-booster, V-23 distribution amplifiers aucho, I-39, II-39, V-59 signal, I-39 dual power supply, V-465 dynamic, ac-coupled, Ili-17 car protector circuit, V-482

electrct nucrophone preamp, V-21 electrometer, overload protected, 11-155 fast-inverting, high-input Impedance, V-18 FET input, II-7 offset gate bias, V-22 video, cascade, I-691 flat response, I-92, III-673 forward-current booster, III-17 four-quadrant photo-conductive detector, I-359 frequency counter preamp, V-24 gain, 10 dB. III-543 gam-controlled, III-34 gate, 1-36 guitars, matching audio signal amps, IV-38 harmonic distortion analyzer, V-291 harmonic distortion meter, V-312 hi-fi compander as, II-12 hi-fi expandor, II-13 high-frequency amphfiers, III-259-265 29-MHz, III-262 3-to-30 MHz. 80-W, 12.5-13 6 V, 111-261 amateur radio, Imear, 2-30 MHz 140-W, III-260 noninverting, 28-dB, III-263 RF, broadcast band, III-264 UHF, wideband with highperformance FETs, III-264 wideband, III-265 high-impedance/high-gain/highfrequency, I-41 high-impedance/low-capacitance, I-691 high-input-high-impedance amplifiers, II-19, II-44 high-side current-sensing amp, VI-54 highpass amplifier, VI-49 IF amplifiers, 1-690, 1V-459 455-kHz, V-522, V-523, V-524 45-MHz, crystal filter, V-527 AGC system, IV-458 preamp, IV-460 receiver, IV-459 quadrature detector, TV sound IF, I-690 two-stage, 60 MHz, I-563 wideband, I-689 infinite sample and hold, II-558 input-inverting, fast, high-impedance, V-19 input/output buffer for analog multiplexers, III-11 instrumentation amplifiers, I-346, I-348, 1-349, I-352, II-293-295, **III-278-28**4, IV-229-234 V-233-235 ±100 V common mode range, III-294 current collector head amplifier, II-295 differential, 1-347, 1-349, 1-353, 1-354, III-282, III-283 extended common-mode design, IV-234 high-impedance low-drift, I-355 high-speed, I-354 low-drift/low-noise dc amplifier, IV-232 low-signal level/high-impedance. T 35Ö

low-power, III-284 meter driver, 11-296 preamps, 111-283, IV-230-231 precision FET input, 1-355 saturated standard cell amplifier, 11-296 stram gange, 111-280 triple op amp, I-347 ultra-precision, III-279 variable gam, differential input, I - 349very high-mpedance, I-354 wideband, III-281 inverting, 1-42, 11-41, 111-14 ac, high-gain, 1-92 balancing circuit in, I-33 gain of 2, lag-lead compensation, UHF, I-566 low-power, digitally selectable gain, II-333 power amplifier, I-79 programmable-gain, III-505 unity gain amplifier, I-80 widehand unity gain, I-35 ISD 1000A record/playback circuit, VI-50 isolation capacitive load, 1-34 level-shifting, I-348 medical telemetry, I-352 rf, II-547 JFET, V-20 500-Mohm input impedance, V-28 hipolar eascade video, I-692 current source biasing, V-21 preamplifier, V-22 line amps, 111-37 duplex, tclephone, III-616 universal design, IV-39 linear amplifiers 2-kW 144-MHz, VI-20 2-30 MHz, 140W PEP amateur radio, I-555 100 W PEP 420-450 MHz pushpull, 1-654 160 W PEP broadband, I-556 amateur radio, 2-30 MHz 140-W, 111-260 audio power amphfiers, V-51 CMOS inverter, II-11 inverter, linear amp from inverter, II-11 rf, IV-480-481, IV-484-485 load-line protected, 75W audio, I-73 logarithmic amplifiers, I-29, I-35, II-8 de to video, I-38 log-ratio amplifier, I-42 op amp, VI-56 logic amplifiers, II-332-335 low-power binary, to 10n gain low-frequency, II-333 low-power inverting, digitally sclectable gain, II-333 low-power noninverting, digitally selectable input and gain, II-334 precision, digitally programmable input and gam, II-335 programmable amplifier, II-334 log ratio, 1-42 loudness control, II-46 low-level video detector circuit and, I-687 low-noise design, IV-37 lowpass amphfier, VI-49 medical telemetry, isolation, I-352

meter-driver, rf, 1-MHz, III-545 micro-powered, high-input/highimpedance, 20 dB, Il-44 micro-sized, III-36 microphone, I-87, III-34 electronically balanced input, I-86 microwave amplifiers, IV-315-319 5.7 GHz, IV-317 bias supply for preamp, IV-318 preamplifiers, IV-316-319 mini-stereo amplifier, V-583 monostable, II-268 MOSFET high-impedance biasing method, V-19 push-pull amplifier, VI-55 neutralized common source, I-565, I-568 noninverting amplifiers, I-32, I-33, I-41, 111-14 ac power, 1-79 adjustable gain, I-91 comparator with hysteresis in, 1-153 high-frequency, 28-dB, III-263 hysteresis in, I-153 low-power, digitally selectable input and gain, II-334 power, 1-79 programmable-gain, III-505 single supply, I-74 split supply, I-75 Norton, absolute-value, III-11 op amp (see operational amphfiers) oscilloscope sensitivity, III-436 output, four-channel D/A, III-165 pH probe amplifier, VI-523 phono, I-80, I-81, I-89 photodiode, I-361, II-324, III-19, III-672, VI-301, VI-302 phototransistor amplifier, V-409 playback, tape, III-672 polarity-reversing low-power, III-16 power (see power amps) power supply, V-464, V-465, VI-18 pre-amps (see preamplifiers) precision amplifier, 1-40, 11-335 precision RTD, for +5 V, VI-643 programmable amplifiers, II-334, III-504-508 differential-input, programmable gain, III-507 inverting, programmable-gain, III-505 noninverting, programmablegain, III-505 precision, digital control/ programming, III-506 programmable-gain, I-32, II-9 variable-gain, wide-range digital control, III-506 programmable gain, I-32, II-9, VI-51 programmable input, VI-52 pulse-width proportional controller circuit for, II-21 push-pull Darlington, V-22 MOSFET, VI-55 PEP 100-W, 420-450 MHz, I-554 FWM servo, III-379 recording amplifier, I-90 reference voltage, I-36 remote, I-91, VI-50 remotely powered sensor amplifier, VI-52 rf (see rf amplifiers) sample-and-hold, I-587, II-558

selectable input, programmable gain, 1-32 servo amplifiers (see also motor controls), I-452 400 Hz, ff-386 bridge type ac, I-458 dc, I-457 motor drive amplifier, II-384 signal amplifiers, audio, II-41-47, IV-34-42 signal distribution, I-39 sound-activated, gain-controlled, IV-528 silicon-controlled amplifiers (SCA), V-535-536 decoder, 1-214, II-166, II-170 demodulator, II-150, III-565 subcarrier adapter, FM taner, V-536 sinewave output buffer, I-126 sound mixer and, II-37 source follower bootstrapped, V-20 JFET, V-20 speaker amplifiers, II-16, III-39 specch compressor, II-15 storeo amplifiers, I-77, II-9, III-34 bass tone control, V-584 subwoofer power supply, V-464 summing, 1-37, 111-16 fast-action, 1-36 inverting, V-18, V-20 precision design, 1-36 video, III-710, VI-681 switching power, 1-33 tape playback, I-92, IV-36 tape recording, 1-90 telephone, III-621, IV-555, IV-560. V-614 telephone ring amplifier, VI-624, VI-626 test bench amplifier, V-26 tester, VCR head amplifier, VI-48 thermocouple, I-654, III-14 cold junction compensation in, II-649, VI-642 high-stability, J-355 transducer, I-86, III-669-673 transformerless, 6-W, 8-ohm output, I-75 transistorized, I-85, II-43 tremolo circuit, voltage-controlled, 1-598tube amplifier, high-voltage isolation, IV-426 tuned amplifier, VI-53 TV audio, III-39 two-meter, I-562, I-567 two-stage, I-563, I-689 UHF, 1-560, I-565 unity gain, I-27, II-7 noninverting, V-21, V-22 variable-gain, for oscilloscopes, V-426VHF, single-device, 80-W/50-ohm, I-558 video, I-692, III-708-712 V-655, V-656, V-657, V-658 V-662, VI-674, VI-679, VI-681, VI-683 75-ohm video pulse, III-711 250-mA 60-MHz current feedback, VI-682 buffer, low-distortion, III-712 color, I-34, III-724 de gain-control, III-711

FET cascade, I-691

gain block, III-712 IF, low-level video detector circuit, I-689, II-687 JFET bipolar cascade, I-692 line driving, III-710 log amplifier, I-38 RGB, 111-709, VI-675 summing, III-710, VI-681 video IF amplifier/detector, VI-678 voice activated switch, I-608 voice-operated circuits, V-553 voltage, differential-to-singleended, IIJ-670 voltage indicators/meters, VI-689 voltage-controlled (see voltagecontrolled amplifiers) voltage-follower, signal-supply operation, III-20 voltineter amplifier, low-drain, VI-695volume, II-46 walkman, II-456 write, III-18 amplitude modulation (see AM radiorelated circuits; AM/FM) analog circuits counter circuit, II-137 delay line, ectio and reverb, IV-21 multiplexers, II-431, III-396 multiplier, II-392 switch, differential analog switch, I-622analog-to-digital converter, II-23-31, III-22-26, IV-5-6, V-27-30, VI-58-60 3-bit, high-speed, I-50 8-bit, I-44, I-46 8-bit successive approximation, I-47 10-bit, II-28 10-bit serial output, II-27 12-bit, high-speed, II-29 16-bit, II-26 board design, IV-6 buffer circuit, I-127, VI-128 capacitance meter, 3.5 digit, III-76 cyclic, II-30 differential input system for, II-31 eight-channel, for PC clones, V-29-30, V-29 fast precision, I-49 four-digit (10,000 count), II-25 half-flash, III-26 high-speed system, VI-59 IC, low-cost, I-50 LCD display, 3.5 digit, 1-49 personal computer A/D converter, VI-60 poller, V-28 successive approximation, II-24, II-30. I-45 switched-capacitor, III-23 temperature measurement converter, VI-234-235, VI-634 three-decade logarithmic, I-48 three-IC, low-cost, I-50 tracking, III-24 video converter, IV-610-611 analyzer, gas, II-281 AND gate, I-395, V-216, VI-315 large fan-m, I-395 relay circuit, VI-316 ancmometers (see also air motion/pressure), VI-4-6 hot-wire, III-342, VI-5 thermally based, II-241

angle-of-rotation detector, II-283

annunciators (see also alarms; sirens), II-32-34, III-27-28, IV-710 ac line-voltage, III-730 bell, electronic I-636, II-33, IV-9 buzzers, I-11, I-12, IV-8, V-170 chime circuit, low-cost, II-33 door buzzer, IV-8 doorbells/chimes, I-218, I-443, IV-8 buzzer, V-170 buzzer, two-door, IV-10 musical-tone, IV-522 rain alarm, I-443 single-chip design, IV-524 sliding tone, II-34 twin-bell, V-170 large fan-in, I-395 SCR circuit, self-interrupting load, IV-9 twin-bell doorbell, V-170 iwo-door annunciator, IV-10 answering machines (see also telephone-related circuits) beeper, IV-559 antennas, IV-11-14, V-31-38, VI-61-67 active, III-1-2, IV-1-4 wideband rod, IV-4 with gain, IV-2balun, V-34 FM automobile radio diversity antenna, VI-64-65 FM tunable antenna booster, VI-65 HF broadband antenna preamp, V-36 HF/VHF switchable active unterna. V-524 loop antenna, 3 5 MHz, IV-12-13 dual band, 80-16-M, V-32 preamp, V-38 matchbox antenna tuncr, VI-66 muniature broadband (3 to 30 MHz), VI-63 preamps HF broadband, V-36 VLF 60 kHz, V-33 wideband antenna, V-35 remote tuned active HF, VI-62 selector switch, IV-538-539 TR switch, automatic, V-37 tamer, VI-66 1- to 30-MHz, IV-14 low-power, V-38 UHF scanner active antenna, VI-67 VLF 60-kHz antenna preamp. V-33 VLF/VHF wideband, low-noise, active, V-33 wideband antenna, preamp, V-35 antitheft device, I-7 are lamp, 25-W, power supply for, II-476 are welding inverter, ultrasome, 20 kHz, III-700 arc-jet power supply, starting circuit, 111-479astable multivibrators. II-269, II-510. III-196, III-233, III-238, V-387, V 388, VI-418, VI-419 op amp, 111-224 free-running square-wave oscillator, V-386 programmable-frequency, III-237 square wave generation with, II-597 starting network, VI-418 variable pulse width, VI-419 attendance counter, II-138 attenuators, III-29-31, VI-68-70

analog signals, microprocessorcontrolled, III-101 digitally programmable, III-30 digitally selectable, precision design, I-52 programmable, III-30 programmable (1 to 0.00001), I-53 rf, IV-322 switchable power, VI-69 variable, I-52 variable voltage, VI-70 voltage-controlled, II-18, III-31 audio amplifiers (see also amplifiers; audio and sound circuits, audio power aniplifiers), II-41-47, III-32-39, IV-34-42, VI-71-82 10-watt amplifier, VI-85 20-dB gain amp, VI-78 40 dB gain design, IV-36 AGC, squelch control, III-33 audio compressor, 11-44 automotive stereo system, highpower, IV-66, VI-101 balance, II-46, II 47. IV-215 Baxandall tone control, IV-588 booster, 20 dB, III-35 CD4049 design, IV-40 circuit bridge load drive, III-35 class AB single-supply amp, complementary, VI-81 complementary-symmetry, I-78 compressor, IJ-44 distribution, 1-39, II-39 electric guitar, IV-38 electronic-ear low noise amp, parabolic dish nucrophones, VI-82 fader, automatic, II-42 fixed power supplies. IV-398, IV-407 high-gain amp, VI-80 high-slew rate power op amp, I-82 gain-controlled, stereo, III-34 line amplifier, III-37, IV-39 linear amp, micropower, VI-73 load line protection, 75W, 1-73 loudness, II-46 low-level amp, VI-78 low-noise design, IV-37 low-power, II-454 nucro-sized, III-36 microphone, II-45, III-34, VI-81 micropower high-input-impedance 20-dB amplifier, II-44 mini-stereo, III-38 NB FM audio amp, VI-74 personal stereo amplifier, VI-75 power (see audio power amplifiers) power supply, V-465, VI-483 pre-amps 1000x. low-noise, IV-37 AGC, VI-2 balanced microphone, VI-77 dynamic microphone. VI-76, VI-79 FET phono cartridge, VI-79 general-purpose. IV-42 impedance-matching, IV-37 low-noise, IV-41 magnetic phono cartridge, IV-35 microphone, IV-37, IV-41, IV-42 NAB tape playback, professional, III-38 phono, III-37, IV-35, IV-36 RIAA, III-38, VI-80 single-ended high-z_microphone, VĪ-78 stereo, II-43, II-45

transistor RIAA for telephone, VI-76 Q-multiplier, II-20 RIAA line amplifier/driver, VI-77 signal (see audio signal amplifiers) signal source for audio amplifier/inverter, VI-702 speaker, hand-held transceivers, III-30 tape playback amplifiers, IV-35 television type, III-39 test circuit, VI-343 tone control, II-686 transistor headphone amplifier, II-43 two-transistor design, VI-74 ultra-high-gain, I-87 vacuum tube amplifier, VI-72-73 vehicle audio amplifier inverter, VI-284volume indicator, II-46, IV-212 audio and sound circuits (see also audio amplifiers; sound generators; sound-operated circuits) acoustic field generator, V-398-341, V-338 acoustic sound receiver/transmitter, IV-311 AF drive indicator, V-346 amplifiers (see audio amplifiers) audio-frequency generator, V-416-417 audio frequency meter, V-305, V-320audio-rf signal tracer probe, I-527 audio-sensor alarm, V-8 audio-test oscillator, V-420 audio-to-ADC interface, V-242 audio-to-UHF preamp, V-24 automatic gain control (AGC), II-17 automatic level control (ALC), V-62 AGC system for CA3028 IF amp, IV-458 rf amplifier, wideband adjustable, 111-545 squelch control, III-33 wide-band amplifier, III-15 booster, II-455, III-35 biquad filter, III-185 bridge load drive, III-35 carrier-current transmitter, III-79 chpper, precise, II-394 compressor. II-14 continuity tester, I-550 converter, two- to four-wire, II-14 CW audio filter, VI-405 CW identifier, VI-408 distribution amplifier, 1-39, 11-39 ditherizer, VI-377 dual tone generator, VI-390 expander, V-582 filters (see filters) frequency doubler, IV-16-17 frequency meter, I-311, VI-335 gain control, remote, VI-384 generators (see sound generators) LED bar peak program meter display, I-254 level meters, sound levels, III-346, III-614, IV-305, IV-307 leveler, ALC, VI-3 limiters, II-15, V-335 millivolsmeter, III-767, III-769 mixers (see mixers) muting circuit, VI-383

noise-based voting circuit, VI-422-423 notch filter, IJ-400 octave equalizer, V-353 oscillators, I-64, II-24, III-427, IV-374, IV-375, VI-432-440 20 Hz to 20 kHz, variable, I-727 light-sensitive, III-315 sine wave, II-562 power (see aucho power amplifiers) power meter, I-488 power supply for auto sound amp, VI-483 Q multiplier, II-20 receivers (see receivers) rf signal tracer probe, I-522 scramblers, IV 25-27 selector, digital, V-158 signal amplifiers (see autho signal amplifiers) sine wave generator, II-564 squelch, II-394 switches eight-channel, V-588-589 video/audio switch, V-586 switching/mixing, silent, I-59 telephone/audio interface, VI-625 transmitters (see transmitters) waveform generators, III-230 audio generators (see sound generators) audio-operated circuits (see soundoperated cucuits) audio power amplifiers, II-451, III-454, IV-28-33, V-39-51, VI-83-93 1.5 watt, VI-12 V, VI-84 6-W. with preamp, III-454 10-watt, VI 85 18-W bridge, V-49 20-W, III-456 33-W bridge composite, V-46 40 W, V-41 50-W, III-451 70 W, composite, V-44-45 80-watt IC, VI-91 90-V 10-A high power, VI-93 AF amplifier, VI 92 audio amplifier, IV-32 basic design, V-51 bridge, I-81, V-49, VI-88 bridge connection of two power op amps, VI-92 bridge composite, V-46 bull horn. IV-31 class-AB amp, VI-86 complementary amp circuit, VI-91 composite, 33-W bridge, V-46 70 W, V-44-45 inverting 10W, V-47 noninverting 10W, V-47 dual, V-42-43 general-purpose, 5-W, ac, IV-30 half-watt, single-channel, V-41 inverting composite, 10W, V-47 line-operated, VI-86 linear, fast, high-voltage, V-51 mini-megaphone, VI-93 MOSFET, V-47 noninverting composite 10W, V-47 op amp, simple design, IV-33 parallel power op amp, VI-84 personal-stereo type, V-48 phono amp, VI-90 power bridge amp with singleended output, VI-85

quasi-complementary, VI-90 quasi-complementary, split power supplies, VI-89 receiver audio circant, IV-31 RF1-proof, VI-88 RIAA phono amphfier, VI-89 stereo amp, IV 29, V-40 subwooler amp, V-49, V-50 vacuum tube amplifier, VI-87 audio signal amplifiers, II-41-47. IV-34-42, V 52-59 booster, V-58 compressor, audio, V-57 audio signal amplifiers, constantvolume, V-55 distribution amplifier, V-59 dual preamp, V-58 headphone amphfier, V-53 headphone amplifier, JFET, V-57 line driver, V-54 mini-amp, V-55 phonograph, magnetic pickup, V-58 tunable-filter design, V-56 volume limiter, V-59 audio-frequency generator, V-416-417 audio-frequency meter, V-305, V-320 audio to-UHF preamp, V-24 audio/video switcher circuit, IV-540-541 auto-advance projector, II-444 autodrum sound effect, II-591 auto-lade circuit, II-42 auto-flasher, 1-299 auto-zeroing scale bridge circuits, III-69 automatic gain control (AGC), II-17, VI-1 AGC system for CA3028 IF amp, IV-458 audio preamp, VI-2 IF network AGC, VI-3 low-noise 3-MHz AGC, VI-2 rf amplifier, wideband adjustable, III-545 squelch control, III-33 wide-band amplifier, III-15 automatic level control (ALC), V-60-62, VI-1 AGC system for audio signals, V-62 basic design, V-62, VI-3 digital design, V-61 automotive circuits, II-48-63, III-40-52, IV-43-67, V-63-77, VI-94-104 accessory-power controller, V-70 alarms (see also alarms/security circuits), V-1 automatic-arming, IV-50 automatic turn off, IV-52 CMOS design, low-current. IV-56 decoy, VI-13 horn as loudspeaker, IV-54 single-IC design, IV-55 air conditioner smart clutch, III-46 alternator/battery monitor, III-63. V-88, VI-97 alternator regulator, V-76 AM radio to shortwave converter, IV-500 amplifier, booster for car sterco, V- $\hat{72}$ analog expanded-scale meter, IV-46 audio-amplifier, high-power, IV-66. VI-101 audio amphfier inverter, VI-284 audio system power supply, VI-103

back-up beeper, III-49, IV-51, IV-56

current analyzer, I 104 electric vehicle battery saver. 111-67 isolator circuit, VI-104 monitor, 1-106, 1-222, III-60-67 supply circuit, ± 15- and 5-V, IV-391 battery cranking-amps tester, V-84 battery/alternator momtor, V-88 brake and turn indicator, V-74 brake lights, V-65 delayed extra, ill-44 flashing, V-69, VI-12 flashing third, IU-51 night-safety light for parked car, IV-61 third brake light, IV-60 burghar alarms, I-3, I-7, I-10, II-2, 111-4, 111-7, IV-53 cassette recorder power circuit, IV-548 cigarette lighter 9-V adapter, VI-97 courtesy lights delay switch, III-42 light extender, III-50 de power adapter, V-70 digi-tach, II-61 directional signals monitor, III-48 door ajar monitor, III-46 electric vehicles, hattery saver. III-67 electrical monitor, VI-96 clectrical tester, IV-45 electronic circuits, IV-63-67 engine-block heater reminder, V-74 exhaust emissions analyzer, II-51 fan thermostatie switch, V-68 FM radio diversity antenna, VI-64-65 fog light controller with delay, IV-59 fuel gauge, digital readont, IV-46 fuse monitor, V-77 garage stop light, II-53 generator regulator, V-76 glow-plug driver, 11-52 headlights, IV-57-62 alarm, III-52, V-77 automatic-off controller, IV-61, V-75 delay circuit, I-107, II-59, III-49 dimmer, II-57, II-63 flasher, V-73 monitor, VI-104 on-lights reminder, V-74, V-77 switching circuit, V-75 headlight/spotlight control, V-67 high-speed warning device, I-101 ice formation alarm, II-58 ignition circuit, V-64 capacitor discharge, VI-102-103 cut-off, IV-53 electronic ignition, IV-65 substitute ignition, III-41 tuning light, II-60 ımmobilizer, II-50 kill-switch for battery, timedelayed, V-71-72 light circuits, IV-57-62 lights-on warning, II-55, III-42, IV-58, IV 60, IV-62 locator, automobile locator, III-43

bar-graph voltmeter, # 54

charger, ni-cad, I-115 condition checker, I-108

battery-related circuits)

battery chargers/monitors (see also

automatic level control (ALC), continued motorcycle alarm, VI-13 burglar alarm, VI-15 flashing brake light, VI-12 headlight monitor, VI-12 horn alarm, VI-14, VI-15 tune-up aid, VI-359 turn-signal system, VI-98 night-safety light for parked car, IV-61 oil pressure gauge, digital readout, IV-44, IV-47 PTC thermistor automotive temperature indicator, II-56 power supply, VI-483, VI-513 radio receiver, 11-525 radio WWV converter, V-119 read-head pre-amplifier, III-44 road ice alarm, II-57 security system, 1-5, IV-49-56, VI-9, VI_11 spotlight/headlight control, V-67 stethoscope for automobiles, VI-95 tachometers, I-94, I-100, I-102, II-175, III-335, III-340, III-347, V-65, VI-98 analog readout, IV-280 calibrated, III-598 closed loop feedback control, II-390 digital readout, fl-61, III-45, IV-268-269, IV-278 dwell meter/tachometer, Ill-45 feedback control, II-378, II-390 frequency counter, 1-310 low-frequency, III-596 minimum-component design, I-405 motor speed controllers, II-378, II-389 optical pick-up, III-347 set point, III-47 temperature gauge digital readout, IV-48 PTC thermistor, II-56 test light, high-Z, VI 104 thermostatic switch for auto fans, V-68 turn signals, V-65 alarm. VI-100 motorcycle, VI-98 audible reminder, V-74 monitor, III-48 sequential flasher for, II-109, III-1 smart, V-66-67, VI-99 reminder, V 73 vacuum gauge, digital readout, IV-45 voltage gauge, IV-47 voltage regulator, III-48, IV-67 voltmeter, bargraph, 1-99 water temperature gauge, IV-44 windshield wiper circuits, 1-105, II-55, II-62 control circuit, I-103, I-105, II-62 delay circuit, II-55, IV-64 hesitation control unit, I-105 intermittent, dynamic braking, 11-49 interval controller, IV-67 slow-sweep control, II-55 windshield washer fluid watcher, I-107 WWV converter for radio, V-119 averaging circuit, VI-324

B

B-field measurer, IV-272 baby monitor, V-370-371 baby-alert transmitter/receiver, V-95-96 back-biased GaAs LED light sensor, II-321 back-EMF PM motor speed control, II-379 backup-light beeper, car, IV-51, IV-56 bagpipe sound effect, IV-521 balance indicator, audio amps, IV-215 balance meter, stereo, V-583 balancer, stereo, I-619 balance amplifiers, III-46 loudness control in, Il-395 balance indicator, bridge circuit, II-82 balun, V-34 band reject filter, active, II-401 bandpass filter (see also filter circuits), II-222, V-180, V-181, VI-2200.1 to 10 Hz. I-296 160 Hz, I-296 active, II-221, II 223, III-190, VI-210 1 kHz, I-284 20 kHz, 1-297 60 dB gain, I-284 variable bandwidth, I-286 amplifier, VI-54 biguad. 1-285, III-188, V-190 Chebyshev fourth-order, III-191 high-Q, I 287, V-179 MFB, multichannel tone decoder, I-288 multiple feedback, I-285, I-297, B $22\dot{4}$ notch, II-223 one op-amp design, VI-222 Sallen-Key, 500 IIz, I-291 second-order biquad, III-188 speech-range filter, V-185 state variable, I-290 tunable, IV-171 two op-amp design, VI 216 variable bandpass, V-184 variable-frequency, V-186 bandswitching for receiver, VI-608 bang-bang power controllers, IV-389 bar-code scanner, III-363 bar-expanded scale meter, II-186 bar graphs ac signal indicator, II-187 voltmeters, ll-54, ll-99 barricade flasher, 1-299 barometer, IV-273, VI-338 bass tone control in storeo amplifier, V-584 bass tuner. II-362 12 V, I-111 200 mA-hour, 12V Ni-Cad, J-114 automatic shutoff for, I-113 battery-operated equipment (see also battery-related circuits) ac power control switch, IV-387 automatic shutoff, III-61 bipolar power supply, II-475 black light, V-281 huffer amplifier for standard cell, I-351 calculators/radios/cassette players, power pack, 1-509 cassette deck power circuit, car, IV-548 fence charger, II-202

flasher, high-powered, II-229 lantern circuit, I-380 light, capacitance operated, I-131 On indicator, IV-217 undervoltage indicator for, 1-123 warning light, II-320 battery-related circuits (see also battery-operated equipment), V-82-89 12-V battery status indicator, VI-120AA cells, +5 V/+3.6 V power supply. V-452 alarm, VI-110-111 automotive battery isolator, VI-104 battery-life extenders, IV-72, V-87 9-V, III-62 disconnect switch, IV-75 electric vehicles, III-67 butler, battery builer, VI-116-117 capacity tester, III-66 car battery/alternator monitor, V-88 chargers, I-113, II-64, II-69, III-53-59. IV-68-72, V-78-81, VI-105-113, VI-118 12-V charger, IV-70 constant voltage, current limited, I-115 controller for charger, VI-107 current limiter for charger, VI-108 intelligent circuit, V-81 lead-acid trickle charger, VI-112 lithium charger, VI-108, VI-109, VI-112 mobile charger, +12 Vde, IV-71 m-cad, I-112, I-116, III-57, VI-109, VI-111, VI-113 photoflash capacitor, VI-466 rf type, V-79 smart charger circuit, VI-106 solar-powered, V-81 temperature sensing charger, IV-77 trickle charger, lead-acid, V-79 checkers (see battery monitors, below) condition checker, I-108, I-121 control for 12V, [-112 converter, dc-to-dc, IV-119 cranking-amp test circuit, V-84 current limited 6V, I-118, IV-70 current monitor, 0-2 A batteries, V-87 disconnect switch, life-extender, IV-75 dynamic constant current test, II-75 fixed power supply, 12-VDC/120-VAC, III-464 gel cell, II-66 high-voltage generator, III-482 indicators (see battery monitors, below) internal resistance tester, IV-74 kill-switch, time-delayed, V-71-72 lead/acid, III-55 level indicator, II-124 lithium, II-67 backup battery replacement, VI-120 charge indicator, II-78 low-battery detection/warning, I-124, II-77, III-56, III-59, III-63, III-65, IV-56, IV-80, VI-118 low cost trickle for 12V storage, I-117

monitors, 1-106, 1-222, 11 74-79, III-60-67, IV-73-80, V-82-83, VI-110 111, VI-114-120 m-cad batteries, 1-118 analyzer for, III-64 charger, I-112, I-116, III-57, VI-109, VI-111, VI-113 12 v, 200 mA per hour, 1114 current and voltage limiting, 1-114 fast-acting, I-118 portable, IV-69 temperature-sensing, IV-77 thermally controlled, II-68 packs, automotive charger for, I-115 portable, III-47, IV-69 protection circuit, III-62 simpli-cad, I-112 temperature-sensing charger, IV-77 test circuit, IV-79 thermally controlled, II-68 zappers, I-6, II-66, II-68 power supply and, 14V, II-73, III-42probe for battery charger, VI-118 protection circuit, ni-cads, III-62 PUT. III-54 rechargeable LED flashlight, VI-107 regulator, I-117 relay fuse, V-88 reverse polarity protection, VI-30 saver circuit, V-87 sensor, quick deactivating, III-61 simpli-cad, I-112 solar cell, II-71 splitter, III-66 status indicator, II-77 step-up switching regulator, 6-V, II-78 supply-voltage monitor, V-85 test circuits, IV-78, V-83, V-86 LED bargraph, V-89 ni-cad, IV-79 thermally controlled ni-cad, II-68 threshold indicator, I-124 UJT. III-56 undervoltage indicator, I-123, VI-117 universal battery, fII-56, III-58 versatile battery, II-72 voltage indicators/monitors, II-79, IV-80, V-86 automotive batteries, IV-47 detector relay, II-76 HTS, I-122 regulator, IV-77 solid-state design, I-120 watchdog circuit, V-85 wind powered, II-70 zapper, simple ni-cad. I-116 Baxandall tone-control audio amp. IV-588 BCD decoder/driver, multiplexed. VI-189BCD rotary switch, digital, V-160 BCD-to-analog converter, 1-160 BCD-to-parallel converter, multiplex, I-169 beat-frequency oscillator, VI-452 beacon transmitter, III-683 beep transformer, III-555, III-566 beepers, I-19, III-49, VI-143 bells, electronic (see also alarms; annuciators), I-636, II-33

bench top power supply, II-472bicycle speedometer, IV-271, IV-282 bilateral current source, III-469 binary counter, II-135 biomedical instrumentation differential amplifier, III-282 bipolar dc-dc converter with no mductor, II-132 bipolar power supply, II-475 bipolar voltage reference source, III-774 biquad audio filter, III-185 second-order bandpass, III-188 RC active bandpass, I-285 bird-chirp sound effect, II-588, III-577 bird feeder monitor, V-371 bistable multivibrators, I-133, II-465, VI-228-230, VI-418 inverter, III-103 debouncer, IV-108 flasher, 1-299, 11-234 lamp driver, IV-160 pushoutton trigger, V-388 RS flip-flop, 1-395 SCR. 11-367 SR flip-flop, IV-651 touch-triggered, 1 133 trigger flip-flop, VI-229 two-amp flip-flop, VI-230 bit grabber, computers, IV-105 black light, battery-operated, V-281 blender-motor control circuit, V-379 blinkers (see flashers and blinkers) blown-fuse alarm, I-10 boiler control, 1-638 bongos, electronic, II-587 boosters 12 ns, ll-97 ac line voltage boost, V-349 audio, 11-455, 111-35, V-58 booster/buffer for reference current, IV-425 electronic, high-speed, II-96 forward-current, III-17 LED, 1-307 power booster, op amp design, IV-358 rl amp, broadcast band boost, IV-487shortwave FE'f, 1-561 bootstrap circuit, V-356 source follower, V-20 cable, 1-34 brake lights (see automotive circuits) brake, PWM speed control/energy recovering, III-380 breakers 12 ns, II-97 high-speed electronic, II-96 breaker power dwell meter, 1-102 breakout box amateur radio, VI-26-27 buffer, II-120, breath alert alcohol tester, III-359 breath monitor, III-350 bridge balance indicator, II-82 bridge circuits, I-552, II-80-85, III-68-71, IV-81-83, VI-121-123 ac, II-81 ac servo amplifier with, III-387 accurate null/variable gain circuit, 111-69 air-flow-sensing thermistor, IV-82 amplifier, 16-watt, VI-85, VI-88, VI 122, VI-123

auto-zeroing scale, III-69

balance indicator, II-82 bridge transducer amplifier, III-71 crystal-controlled oscillator, IV-127 differential amplifier, two op-amp, 11-83 inductance bridge, IV-83 linearizing function circuit, VI-321 load driver, audio circuits, III-35 low-power common source amplifier, II-84 one-power supply design, IV-83 QRP SWR, III-336 rectifier, fixed power supply, IV-398 remote sensor loop transmitter, III-70 rf bridge, V-50-MHz, V-303 strain gauge signal conditioner, II-85, III-71 transducer, amplifier for, II-84 Wheatstone bridge, VI-123 Wien-bridge (see Wien-bridge) brightness controls, III-308, III-316 contrast meter, I-472, II-447 LED, I-250 low-loss, I-377 broadband communications (see radio/rf circuits) buck converter, 5V/0.5A, I-494 buck/boost converter, III-113 bucking regulators add 12-V output to 5-V, V-472 high-voltage, III-481 buffer amplifiers, V-91 10x, I-128 100x, I-128 ac, single supply, I-126, VI-127 battery powered, standard cell, II-351 MOSFET design, V-93 sme wave output, I-126 VFO design, V-92 buffers, IV-88-90, V-90-93, VI-124-128amplifiers (see buffer amplifiers) ac, single-supply, high-speed. I-127-128 ADC buffers, I-127, VI-125, VI-126 A/D, 6-bit, high-speed, I-127 A/D converter buffer, VI-128 analog noninverting switched huffer, VI-127 bidirectional design, VI-128 booster/buffer for reference current, IV-425 capacitance buffers low-input, III-498 stabilized low-input, III-502 data/clock line serial bus for PCs, V-110 hex-buffer crystal oscillator, V-136 high-current, V-92 input/output, for analog multiplexers, III-11 mverting, II-299, IV-90 microphone buffer amplifier, high-Z, VI-125 oscillator buffers, IV-89 piezoelectric, VI-470 precision-increasing design, IV-89 rail-to-rail single-supply buffer, V-93 rf amp, buffer amp with modulator, IV-490 stable, high-impedance, I-128 umty gain, stable, good speed, highinput impedance, II-6

buffer amplifiers, continued VFO buffer amplifier, V-92 video buffer, III-712, V-93 voltage follower, VI-127 wideband buffer, I-127, VI-126 buffered breakout box, II-120 bug detector, III-365, V-150 bug tracer, III-358 buil horn, 11-453, IV-31 burglar alarms (see alarms; annuciators, sirens) burst generators (see also function generators; sound generators; waveform generators), II-86-90, III-72-74 multi-, square waveform, II-88 rf, portable, III-73 single timer IC square wave, II-89 single tone, II-87 strobe tone, II-90 tone, II-90, III-74 burst power control, III-362 bus interface, eight bit µP, II-114 Butler oscillator, VI-452 aperiodic, I-196 common base, I-191 crystal, I-182 emitter follower, II-190-191, II-194 Butterworth filter, VI-220 fourth-order, 1-kHz, VI-222 fourth order high-pass, I-280, V-179 fourth order low-pass, V-180 order low-pass, V-181 buzzers (see annuciators)

С

cable bootstrapping, I-34 coax cable driver, VI-201 driver, VI-678 terminator, positive feedback, VI-388 test circuit, III-539, V-299 tester, audio/video cable, VI-144 tracers, VI-659 twisted-pair video driver/receiver circuit. VI-682 two-mput video MUX cable driver, VI-197 video cable driver, VI-200 calibrated circuit, DVM auto, I-714 calibrators analog circuits, VI-356 crystal, 100 kHz, I-185 electrolytic-capacitor reforming, IV-276ESR measurer, IV-279 oscilloscope, II-433, III-436 portable, I-644 square wave, 5-V, I-423 standard for calibration, I-406 radio calibrator, V-298 tester, IV-265 wave shaping, high-slow rates, IV-650 cameras (see photography-related circuits: television and video) capary sound simulator, V-557 canceller, central image, III-358 capacitance buffers low-input, III-498 stabilized low-input, III-502 capacitance controller, digital, V-159 capacitance meters, I-400, II-91-94, III-75-77, VI-340 A/D, 3 5 digit, III-76 capacitance-to-voltage, II-92

digital, II-94 capacitance multiplier, I-416. II-200, V-205, V-347 capacitance tester, one-IC design, V-306, VI-358 capacitance-to-pulse width converter, II-126 capacitance-to-voltage meter, II-92 capacitor discharge high-voltage generator, III-485 ignition system, II-103 capacitors hysteresis compensation, V-353 programmable, VI-362 capacity tester, battery, III-66 car port, automatic light controller for, 11-308 cars (see automotive circuits) carrier-current circuits (see also radio/rf circuits), III-78-82, IV-91-93, V-94-96 AM receiver, III-81 audio transmitter, III-79 baby alert receiver/transmitter, V-95. V 96 data receiver, IV-93 data transmitter, IV-92 FM receiver, III-80 mtercom, I-146 power line modem, III-82 receivers, 1-141, 1-143 IC, I 146 single transistor, I-145 relay, 1 575, IV-461 remote control. 1-146 transmitters, I-144 IC. I-145 on/off 200 kHz line, I-142 cascaded amplifier, III-13 cassette bias oscillator, II-426 cassette interface, telephone, III-618 centigrade thermometer, I-655, Il-648.11-662 central image canceller, III-358 charge pool power supply, III-469 charge pumps positive input/negative output. I-418. III-360 regulated for fixed power supply, IV-396 chargers (see battery-related circuits, chargers) chase circuit, I-326, III-197 Chebyshev filters (see also filter circuits) bandpass, fourth-order, III-191 fifth order multiple feedback low pass, II-219 high-pass, fourth-order, III-191 chime circuit, low-cost, II-33 chopper circuits amplifier, II-7, III-12, I-350 de output, V-349 JFET, V-352 checkers (see measurement/test circuts) chroma demodulator with RGB matrix, III-716 chug-chug sound generator, III-576 circuit breakers (see also protection circuits) 12 ns, II-97 ac, III-512 high-speed electronic, 11-96 trip circuit. IV-423 circuit protection (see protection carcuits)

clamp on-current probe compensator, II-501 clamp lumiting amplifiers, active, III-15 clamping circuits video signal, III-726 video summing amplifier and, III-710 Clapp oscillator, VI-458 class-D power amplifier, III-453 clippers, II-394, JV-648 andio-powered noise, II-396 audio-chpper/linuter, IV-355 noise clipper, adjustable, VI-423 zener design, fast, symmetrical, IV-329 clock circuits, II-100-102, III-83-85, V-97-99, VI-129-131 60 Hz clock pulse generator, II-102 adjustable TTL, I-614 binary clock, V 98-99 buffer senal bus, V-110 comparator, I 156 crystal oscillator, micropower, IV-122 digital, with alarm, III-84 gas discharge displays, III-12-hour. 1-253low-frequency clock, VI-131 oscillator/clock generator, III-85 phase lock, 20-MHz to NuBus, III-105 run-down clock for games, IV-205 sensor touch switch/clock, IV-591 set time windows within clock, VI-130 single op amp, 11-85 source, clock source, 1-729 stepper motors, V-573 three-phase from reference, II-101 TTL, wide frequency, Ili-85 Z80 computer, II-121 clock generators oscillator, 1-615 precision, 1-193 pulse generator, 60 Hz, II-102 clock radio, I-542, I-543 **CMOS** circuits 555 astable true rail-to-rail square wave generator, II-596 9 bit, III-167 coupler, optical, III-414 crystal oscillator, III-134 data acquisition system, II-117 dimmer, V-270 flasher, III-199 inverter, linear amplifier from. II-11 line receiver, V-497 nuxer, I-57 multivibrators, V-385 optical coupler, III-414 oscillator, I-187, 1-615, 1-199, III-429, III-430, V-420 piezoelectric driver, V-440 programmable precision timer, III-652 short-pulse generator, III-523 touch switch, I-137 universal logic probe, III-499 variable-frequency oscillator (VFO), V-418 coaxial cable drivers, coaxial cable, I-266, I-560 five-transistor pulse booster. II-191 test circuit, V-299 Cockcroft-Walton cascaded voltage doubler, IV-635

code-practice oscillators, I-15, I-20, I-22, II-428-431, IV-373, IV-375, IV-376, V-100-103, VI-404-409 keyer, "bug" type, V-102 Morse code practice, V-103 optoisolator design, V-101 QRP sidetone generator, V-102 single-transistor design, V-103 VFO design, V-103 coil drivers, current-limiting, III-173 coin flipper circuit, III-244 coin toss game, VI-250 color amphfier. video, III-724 color-bar generator, IV-614 color organ, II-583, II-584, V-104-105, VI-193 color video amplifier, 1-34 colorímeter, VI-306-307 Colpitts crystal oscillators, I-194, I-572, II-147, V-411, VI-160, VI-458 1-to-20 MHz, IV-123 frequency checker, IV-301 harmonic, I-189-190 two-frequency, IV-127 comb filter, VI-218 combination locks, electronic, II-196 three-dual, II-195 commutator, four-channel, II-364 companders (see compressor/expander circuits) comparators, I-157, II-103-112, III-86-90 demonstration circuit, II-109 diode feedback, I-150 display and, II-105 double-ended limit. II-105. I-156 dual limit, I-151 four-channel, III-90 frequency, II-109, II-110, VI-353 frequency-detecting, III-88 high-impedance, I-157 high input impedance window comparator, II-108 high-low level comparator with one op amp, II 108 hysteresis, I-157 inverting, I-154 noninverting, I-153 inverting, [154 jitter suppression, V-342 latch and, III-88 LED frequency, II-110 limit, I-156, II-104 low-power, less than 10 µV hysteresis, II-104 microvolt dual limit, III-89 hysteresis, III-88 monostable using, II-268 opposite polarity input voltage, I-155 oscillator, tunable signal, I-69 power supply overvoltage, glitches detection with, II-107 precision balanced input/variable offset, 111-89 photodiode, I-360, I-384 time out. I-153 TTL-compatible Schmitt trigger, II-111 three-input and gate, op amp design, IV-363 variable hysteresis. I-149 voltage comparator, IV-659 voltage monitor and, II-104 window, I-152, I-154, II-106, III-87,

III-90, III-776-781, IV-656-658, VI-181 compass digital design, IV-147 Hall-effect, III-258 talking Hall-offect compass, V-221 compensator, clamp-on-current probe, II-501 composite amplifier, II-8, III-13 composite-video signal text adder, **III-716** compressor/expander circuits, III-91-95, IV-94-97 amplificr/compressor, lowdistortion, IV-24 audio, II-44, V-57 audio compressor/audio-band splitter, IV-95 clock circuit, I-156 guitar, sound-effect circuit, IV-519 hi-fi, II-12, II-13 de-emphasis, III-95 pre-emphasis, III-93 low-voltage, III-92 protector circuit, IV-351 speech, II-2 universal design, IV-96-97 variable slope, III-94 computalarm, I-2 computer circuits (see also interfaces), II-113-122, III-96-108, V-106-110, VI-132-141 ADC. eight-channel, for PC clones. V-29-30 analog signal attenuator, III-101 analog-to-digital converter for PC, VI-60 alarm, I-2 ASCII triplex LCD, 8048/IM80C48. II-116 bit grabber, IV-105 buffered breakout box, II-120 buffer senal-bus for data/clock lines, V-110 bus interface, 8-bit µP, II-114 clock phase lock, 20-MHz-to-NuBus, III-105 CMOS data acquisition system, II-117 contrast and backlight control, high-efficiency, VI-191 CPU interface, one-shot, IV-239 data acquisition circuit, VI-378 data separator for floppy disks, II-122 deglitcher, IV-109 display, eight-digit, III-106 dual 8051s execute in lock-step circuit, IV-99 DVM adapter for PC, V-310 EEPROM programming doubler circuit, VI-138 EEPROM pulse generator, 5Vpowered, III-99 eight-channel mux/demux system, '∐-115 eight-digit microprocessor display, III-106 error checker, master/slave device, VI-389 flash memory programming supply, +12 volt, VI-138 flip-flop inverter, spare, III-103 high-speed data acquisition system, II-118

interface, 680x, 650x, 8080 families,

III-98

keyboard matrix interface, IV-240 laptop computer power supply, V-463LCD, CCFL supply with variable contrast, VI-510 line protectors, 3 µP 1/O, IV-101 logic-level translators. IV-242 logic line monitor, III-108 long delay line, logic signals, III-107 memory/protector power supply monitor, Iv-425 memory saving power supply, II-486 microcomputer-to-triac interface, V-244 microprocessor selected pulse width control, Il-116 modem protector circuit, V-479 modem/fax protector for two computers, V-482 multiple inputs detector, III-102 one-of-eight channel transmission system, III-100 oscilloscope digital levels, IV-108 password protection circuit, V-109, VI-135 power line modem for computer control, VI-474 power saver for monitors, VI-139 power supply for notebook computer, triple-output, VI-512 power supply watchdog, II-494 pulse width control, II-116 printer error alarm, IV-106 printer port, VI-134-135 printer sentry, V-107-108 reset protection, childproof, IV-107 RGB blue box, III-99 RS-232, computer-powered, VI-138-139RS-232 dataselector, automatic, III-97 RS-232C line-driven CMOS circuits, IV-104 RS-232-to-CMOS line receiver, III-102 RS-232C LED circuit, III-103 RS-422 to RS-232 converter, VI-133 short-circuit sensor, remote data hnes, IV-102 signal attenuator, analog, III-101 sleep-mode sound-operated circuits, V-547 socket debugger, coprocessor, III-104 speech synthesizer for, III-732 stalled output detector, IV-109 supervisory circuit, VI-136 switch debouncer, IV-105 auto-repeating, IV-106 teleprinter loop supply, VI-497 triac array driver, II-410 voltage regulator for new microprocessors, VI-566 Vpp generator for ÉPROMs, II-114 wireless RTS keyer with data, VI-136 XOR gates, IV 107 up/down counter, III-105 280 bus monitor/debugger, IV 103 280 clock, II-121 contact switch, I-136 continuity testers, 1-550, 1-551, II 533, Îl-535, III-345, Îll-538-540, IV-287, IV-289, IV-296, VI-142-145

interval timer, programmable, II-

678

buffer amplifiers, continued adjustable continuity tester, VI-144 audible, II-536, V-317, VI-145 audio/video cable tester, VI-144 buzz box, I-551 cable tester, III-539 latching design, IV-295 low-resistance circuits, V-319 ohmmeter, linear, III-540 PCB, II-342, II-535 ratiometric, I-550 RC decade box, V-294-295 resistance-ratio detector, II-342 short-circuit beeper, VI-143 single chip checker, II-534 visual, V-293 contrast meters, II-447 automatic, I-472 brightness controls, 1-250, 1-377, III-308 control circuits (see fluid and moisture; light-controlled circuits; motor control circuits; speed controllers; temperaturerelated circuits; tone controls) controller circuit, IV-142 conversion and converters, 1-503, II-123-132, III-109-122, IV-110-120. V-116-128, VI 146-155 3-to-5 V regulated output, III-739 4-to-18 MHz, III-114 4-to-20 mA current loop, IV-111 5V-to-isolated 5V at 20 MA, III-474 5V-to-0.5A buck, I-494 9-to-5-V converter, IV-119 12-to-9 V, 7 5, or 6 V, I-508 12-to-16 V, III-747 28-to-5 Vdc converter, V-127 50+ V feed forward switch mode, I-495 50+ V push-pull switched mode, I-494 100 MHz, II-130 100 V-to-10.25 A switch mode, I-501 225-W 15-V output converter, VI-148-149 800-to-1000 MHz scanner converter, V-122 ac-to-dc converters, I-165 fixed power supplies, IV-395 full-wave, IV-120 high-impedance precision rectifier, I-164 amateur TV downconverter, 420 to 450 MHz, VI-44-45 anateur TV downconverter, 902 to 928 MHz, VI-40-41 analog-to-digital (see analog-todigital conversion) ATV downconverter, V-125, V-126 ATV rf receiver/converter, IV-420 BCD-to-analog, I-160 BCD-to-parallel, multiplexed, I-169 buck/boost, III-113 calculator-to-stopwatch, I-153 capacitance-to-pulse width, II-126 crystal-controlled, one-chip, V-117 current-to-frequency, IV-113 wide-range, I-164 current-to-voltage, I-162, I-165, V-127, VI-154, VI-155 grounded bias and sensor, II-126 photodiode, II-128 de automobile power adapter, V-70 dc-to-dc, IV-118, V-119, V-128, VI-164-167

1-to-5 V. IV-119 3-to-5 V battery, IV-119 3-to-25 V, III-744, IV-118 bipolar, no inductor, II-132 fixed 3- to 15-V supply, IV-400 isolated +15V, III-115 push-pull, 400 V/60 W, I-210 regulating, I-210, I-211, II-125, III-121 step-up/step-down, III-118 dc/ac inverter, V-669 de/de converter, V-669 differential voltage-to-current converter, VI-153 digital-to-analog (see digital-toanalog conversion) direct-conversion 7-MHz receiver, VI-153 driven flyback converter, VI-150 fixed power supply, III-470 flyback, I-211 self oscillating, I-170, II-128, **III-748** voltage, high-efficiency, III-744 frequency, 1-159, V-123 frequency-to-voltage (see frequency-to-voltage conversion) HF receive converter, VI-147 high-to-low-impedance, I-41 intermittent converter, power saver, IV-112 IR-pulse-to-audio converter, V-224 light intensity-to-frequency, I-167 line-voltage-to-multimeter adapter, V-312 logarithmic fast-action, 1-169 temperature compensated, V-127 low-frequency, Ill-111, VI-153 ohms-to-volts, 1-168 oscilloscope, I-471 output-to-current converter, VI-155 NTSC-to-RGB converter, VI-677 period-to-voltage, IV-115 photochode log converter/ transmitter, VI-312 pico-ampere, 70 V with gain, 1-170 PIN photodiode-to-frequency, III-120 polar-to-rectangular converier/ pattern generator, V-288 polarity, l-166 positive-to-negative, III-112, III-113 power supplies, inductorless, V-456 pulse height-to-width, III-119 pulse train-to-sinusoid, III-122 pulse width-to-voltage, III-117 radio beacon converter, IV-495 rectangle-to-triangle waveform, IV-116-117 regulated 15-V_{eqt} 6-V driven, III-745 resistance-to-voltage, I-161-162 rl'converters, IV-494-501 ATV receiver/converter, 420 MHz, low-noise, IV-496, IV-497 radio beacon converter, IV-495 receiver frequency-converter stage, IV-499 SW converter for AM car radio, IV-500 two-meter, IV-498 up-converter, TVRO subcarrier reception, IV-501 VLF converter, IV-497 WWV-to-SW converter, IV-499 receiving converter, 220 MHz, IV-500

RGB-composite video signals, III-714 RMS-to-dc, I-167, II-129 50-MHz thermal, III-117 RGB-to-NTSC, IV-611 sawtooth wave converter, IV-114 scanner converter, V-800-to-1000 MHz, V-122 SCR converter, VI-151 shortwave, III-114, V-118 simple LF, I-546 sine-wave converter, VI-150 sinc-to-square wave, 1-170, IV-120, V-124, V-125, V-569, V-570 square-to-sine wave, III-118 square-to-triangle wave, TTL, II-123 step-down converter, 5-V 5-A, VI-151 sync-to-async. VI-152 temperature-to-digital, V-123, VI-646 temperature-to-frequency, J-168, V-121, VI-639 temperature-to-time, III-632-633 transverter, V-2-to-6 meter, V-124 triangle-to-sine wave, II-127 TTL-to-MOS logic, II-125, I-170 two-wire to four-wire audio, II-14 unipolar-to-dual voltage supply, III-743 video converters a/d and d/a, IV-610-611 RGB-to-NTSC, IV-611 VLF converters, I-547, V-121 rf converter, IV-497 voltage (see voltage converters) voltage multipliers, V-668-669 WWV converter, V-119, VI-147 WWV-to-SW rf converter, IV-193 cool-down circuit, V-354, V-357 coprocessor socket debugger, III-104 countdown timer, II-680 counters (see also dividers), II-133-139, III-123-130, V-129-133 analog circuit. II-137 attendance, II-138 binary, II-135 divide-by-N 1+ GHz, IV-155 1.5+ divide-by-n, IV-156 CMOS programmable, I-257 7490-divided-by-n, IV-154 divide-by-odd number, IV-153 event counter, VI-369 frequency counters, VI-360 2 MHz, V-130-131 10 MHz, V-132-133 preamp, V-24 frequency dividers, I-258, II-251, II-254, III-213-218, III-340, III-768 1.2 GHz, fil-129 10-MHz, III-126 clock input, IV-151 decade, I-259 divide-by-1.5, III-216 low-cost, III-124 low-frequency, II-253 preamp, III-128 programmable, IV-152-153 staircase generator and, I-730 tachometer and, I-310 fringe counter, VI-300 Geiger, I-536-537, V-217-219 microfarad counter, IV-275 minimum/maximum selector, fourmput, V-332

odd-number divider and, III-217 preamplifier, oscilloscope. III-438 precision frequency, 1-253 programmable, low-power widerange, III-126 ring counters 20 kHz, II-135 incandescent lamp, I-301 low-cost, I-301 low-power pulse circuit, IV 437 SCR, 111-195 variable timing, II-134 time base, function generators, 1 Hz, IV 201 universal 10-MHz, I-255, II-139 40-MHz, III-127 up/down counters 8-digit, II-134 extreme count freezer, III-125 XOR gate, III-105 coupler circuits luicar couplers ac analog, II-412 analog, II-413 dc. II-411 optocoupler, instrumentation, II-417 optical couplers/optocouplers, V-407CMOS design, III-414 interface circuits, V-406-407 linear, instrumentation, II-417 stable, II-409 TTL design, III-416 photon, II-412 RF line sampler/coupler, VI-30 transmitter oscilloscope for CB signals, I-473 courtesy lights (see automotive circuits) craps game, VI-245 CRO doubler, III-439 cross fader, II-312 cross-hatch generator, color TV, III-724 crossover networks, II-35 5V. I-518 ac/dc lines, electronic, I-515 active, I-172 asymmetrical third order Butterworth, I-173 electronic circuit for, II-36 crowbars, I-516 electric, III-510 electronic, II-99 SCR, II-496 voltage regulator, variable, with crowbar limiting, VI-515 crystal oscillators (see also oscillators), I-180, I-183-185, I-195, I-198, II-140-151, III-131-140, IV-121-128, V-134-140, VI-156-160 1-to-20 MHz, TTL design, IV-127 1-to-4 MHz, CMOS design. IV-125 10 MHz, II-141 10-to-150 kHz, IV-125 10-to-80 MHz, IV-125 50-to-150 MHz, IV-126 96 MHz, I-179 150-to-30,000 kHz, IV-126 330 MHz, IV-125 activity tester, V-138 amplifier, tuned, VI-57 aperiodic, parallel-mode, I 196 basic design, V-135

bridge, crystal-controlled, IV-127 Butler oscillator, I-182 calibrator, 100 kHz, I-185, IV-124 ceramic, 10 MHz, varactor tuned, Il-141 clock, micropower design, IV-122 CMOS crystal oscillators, 1 187, III-134 1-to-4 MHz, IV-125 Colpitts crystal oscillators, I-194, I 572, II 147, VI 160 1-to-20 MHz, IV-123 frequency checker, IV-301 harmonic, I-189-190 two-frequency, IV-127 crystal-controlled oscillator as, II-147 crystal-stabilized IC timer for subharmonic frequencies, II-151 erystal tester, I-178, I-186, II-151 de-switched, VI-159 doubler and, I-184 casy start-up, III-132 FET, 1 MHz, II-144 FET quartz crystal oscillator, VI-157FET VXO, VI-157 FM capable, VI-158 frequency adjustable, VI-159 frequency doubler, VI-160 fundamental-frequency, III-132 Hartley oscillator, V-140 hex-buffer, V-136 high-frequency, I-175. II-148 high-frequency signal generator as, ÌI-150 IC-compatible, II-145 impedance checker, V-136 LO for SSB transmitter controlled by, II-142 low-frequency, I-184, II-146, V-135 10 kHz to 150 kHz, II-146 low-noise, II-145 marker generator, III-138 mercury cell crystal-controlled oscillator as, II-149 OF-1 HI oscillator, international, I-197 OF-1 LO oscillator, international, I-189 overtone oscillators, I-176. I-177, I-180, I-183, I-186, II-146, III-146 50 MHz to 100 MHz, I-181 100 MHz, IV-124 crystal, I-176, I-180, II-146 crystal switching, I-183 fifth-overtone, I-182 third-overtone oscillator, IV-123 Pierce oscillator, V-140 1-MHz, III-134 crystal, I-195, II-144 harmonic, I-199, II-192 JFET, I-198 low-frequency, III-133 quartz, two-gate, III-136 radio detector, VI-182 reflection oscillator, crystalcontrolled, III-136 Schmitt trigger, I-181 signal source controlled by, II-143 sine-wave oscillator, I-198 stable low-frequency, I-198 standard, 1 MHz, I-197 temperature-compensated, I-187, II-142, III-137 test circuit, V-139 third-overtone, I-186, IV-123

time base, III-133, IV-128, V-137, V-138TTL design, 1-179, IV-127 TTL-compatible, I-197 transistorized, I-188 tube-type, I-192 LLT 100-kHz calibration oscillator. VI-157 VHF crystal oscillator, III-138-140 voltage-controlled (VĆO), III-135, IV 124 wide-range, V-139 crystal radio receiver, VI-549, VI-557 crystal switching, overtone oscillator with, 1-183 current analyzer, auto battery, I-104 current booster, I-30, I-35 current collector head amplifier, II-11, 11-295 current feedback amp, 100 mA at 100 MHz, V-25 current limiter, V-146 foldback current, VI-477 inrush current, V-358 regulator, VI-478 current loops 4-to-20-mA converter, IV-111 controller, SCR design, IV-387 current meters and monitors, I-203, II-152-157, III-255, III-338, IV-284, V-144-146, VI-259, VI-355 alarm and current monitor, III-338 ac current indicator, IV-290 current sensing in supply rails, II-153 electrometer amplifier with overload protection, II-155 Hall-effect sensors, III-255, IV-284 high-gain current sensor, IV-291 line-current monitor, III-341 picoammeter. I-202, II-154. II-157. III-338 guarded input. II-156 range ammeter, six-decade, II-153, II-156 current probe, VI-521 current readout, rf, I-22 current regulators, op amp, VI-430, VI-489 current sensing, supply rails, II-153 current sink, I-206 1 mA for fixed power supplies, IV-402voltage-controlled, IV-629 current sources, I-205, I-697, V-141-143, VI-161-163, VI-332, VI-335 0-to-200-nA, IV-327 bilateral, I-694-695, 111-469, V-143 bipolar sources inverting, I-697 noninverting, I-695 constant, I-697, III-472 fixed power supplies bootstrapped amp, IV-406 differential-input, fast-acting, IV-405 low-current source, IV-399 generator, VI-162 limiter, V-146 low-resistance measurements, V-142 multiple fixed current source, VI- $16\bar{3}$ negative, V-143 offset-adjusting, V-145 positive, V-142 precision, 1-205, 1-206

current sources, continued regulator, variable power supply, III-490 variable power supplies, voltage-programmable. IV-420 voltage-controlled, III-468, VI-162, VI-163 current-limiting regulator, V-458 current-shunt amplifiers. III-21 current-to-frequency converter, IV-113 wide range, I-164 current-to-voltage amplifier, highspeed, I-35 current-to-voltage converter, I-162, I-165, V-127, VI-154. VI-155 grounded bias and sensor in, II-126 photodiode, II-128 curve tracer, V-300 diodes, IV-274 FET, I-397 CW-related circuits audio filter, VI-29, VI-405 CW/SSB receiver, 80- and 40-meter, V-499 filter, razor sharp, II-219 identifier, VI-24, VI-408 keying circuits, IV-244 offset indicator, IV-213 SSB/CW product detector, IV-139 transceiver, 5 W, 80-meter, IV-602 transmitters 1-W, III-678 6-W 40-M, VI-664 20-M low-power, V-649 40-M. III-684, V-648 902-MHz, III-686 HF low-power, IV-601 keying circuit, VI-22-23 one-watt, VI-27 QRP, 111-69 ultrasonic transceiver, VI-669 cyclic A/D converter, II-30

D

dark-activated (see light-controlled circuits) darkroom equipment (see photography-related circuits) Darlington amplifier, push-pull, V 22 Darlington regulator, variable power supplies, IV-421 Darlington transistor oscillator, VI-455 data-manipulation circuits, IV-129-133 acquisition circuits, IV-131, VI-378 CMOS system, II-117 four-channel, I-421 high-speed system. II-118 analog-signal transmission isolator, IV-133 link, IR type, I-341 prescaler, low-frequency, IV-132 read-type circuit, 5 MHz, phaseencoded, II-365 receiver, carrier-current circuit design, IV-93 receiver/message demuxer, threewire, IV-130 selector, RS-232, III-97 separator, floppy disk, II-122 transmission circuits, IV-92 dc adapter/transceiver, hand-held, 111-461

de generators, high-voltage, III-481 de motors (see also motor control circuits) direction control, I-452 driver controls fiberoptic control, II-206 fixed speed, III-387 servo, bipolar, II-385 reversible, II-381, III-388 speed control, I-452, I-454, III-377, III-380, III-388 dc restorer, video, III-723 de servo drive, bipolar control input, II-385 de statie switch, II-367 dc-to-ac inverter, V-247, V-669 dc-to-dc conversion, IV-118, V-669, VI-164-167 1-to-5 V (V-119 3-to-5 V battery, IV-119 3-to-25 V, III-744, IV-118 3.3 and 5-V outputs, V-128 3 A, no heatsink, V-119 bipolar, no inductor, II-132 fixed 3- to 15-V supply, IV-400 isolated, VI-165 isolated +15V, III-115 negative step-up converter, VI-166 push-pull, 400 V/60 W, I-210 regulating, I-210, I-211, II-125, III-121 step-up/step-down, III-118 ultra low-power for personal communications, VI-166 dc-to-dc inverter, VI-285 dc-to-dc SMPS variable power supply, II-480 debouncers, III-592, IV-105, V-316, VI-387, VI-613, VI-614 auto-repeat, IV-106 computer applications, IV-105, IV-106, IV-108 flip-flop, IV-108 debugger, coprocessor sockets. III-104 decibel level detector, audio, with meter driver, III-154 decoders, II-162, III-141-145, VI-168-171 10.8 MHz FSK, I-214 24-percent bandwidth tone, I-215 BCD decoder/driver, multiplexed, VI-189 direction detector, III-144 DTMF decoder, VI-169 dual-tone, I-215 encoder and, III-144 FM stereo decoder, VI-170 frequency division multiplex stereo, II-169 PAL/NTSC, with RGB input, III-717 radio control receiver, I-574 SCA, I-214, III-166, III-170 second-audio program adapter, III-142sound-activated, III-145 stereo TV, II-167 tíme division multiplex stereo, II-168tone alert, I-213 tone dial, I-630, I-631 tone decoders, I-231, III-143, VI-170 24% bandwidth, I-215 dual time constant. II-166 relay output, I-213 tone-dial decoder, I-630, I-631

video, NTSC-to-RGB, IV-613 video line decoders, VI-171 weather-alert detector/decoder, IV-140 deglitcher circuit, IV-109, V-336-337 delay circuits/ delay units, III-146-148, V-147-148, VI-172-173 adjustable, III-148 analog delay line, echo and reverb offects, IV-21 door chimes, I-218 echo and reverb effects, analog delay line, IV-21 exit delay for burglar alarms, V-10 headlights, I-107, II-59 leading-edge, III-147 long duration time, I-217, I-220 power-on delay, V-148 precision solid state, I-664 pulse, dual-edge trigger, III-147 pulse generator, II-509 relay, ultra-precise long time, II-211 timed delay, I-668, II-220 time-delay generator, VI-173 constant-current charging, II-668 windshield wiper delay, I-97, II-55 demodulators, II-158-160. III-149-150 5V FM, I-233 12V FM, I-233 565 SCÁ, III-150 AM demodulator, II-160 chroma, with RGB matrix, III-716 FM demodulator, I-544, II-161, V-151, V-155 narrow-band, carrier detect, II-159 linear variable differential transformer driver, I-403 LVDT demodulators, II-337, III-323-324stereo, II-159 telemetry, I-229 demonstration comparator circuit, II-109 demultiplexers (see also multiplexers), III-394 differential, I-425 eight-channel, I-426, II-115 descramblers, II-162 gated pulse, II-165 outband, II-164 sine wave, II-163 derived center-channel stereo system, IV-23 detect-and-hold circuit, peak, I-585 detectors (see fluid and moisture; light-controlled circuits; motion and proximity; motor control circuits; peak detectors; smoke detectors; speed controllers; temperature-related circuits; tone controls; zero-crossing) deviation meter, IV-303 dial pulse indicator, telephone, III-613 dialers, telephone pulse-dialing telephone, III-610 pulse/tone, single-chip, III-603 telephone-line powered repertory. I-633 tone-dialing telephone, III-607 dice, electronic, I-325, 111-245, IV-207 differential amplifiers, I-38, III-14, V-18, V-21, VI-185-287 high-impedance, I-27, I-354 high-input high-impedance, II-19

instrumentation, I-347, III-283 instrumentation, biomedical, III-282 oscilloscopes, VI-463 programmable gain, III-507 two op amp bridge type, II-83 wide input common-mode range. VL53 differential analog switch, I-622 differential capacitance measurement circuit, II-665 differential hold, I-589, II-365 differential multiplexers demultiplexer/, 1-425 wide band, 1 428 differential thermometer, II-661, III-638 differential voltage or current alarm, 11-3 differentiators, I-423, V-347 negative-edge, 1-419 positive-edge, I-420 digital-capacitance meter, II-94 digital-IC, tone probe for testing, II-504 digital-frequency meter, III 344 digital-logic probe, III-497 digital audio tape (DAT), ditherizing circuit, IV-23 digital circuits, V-156-160 audio selector, V-158 BCD rotary switch, V-160 capacitance control, V 159 entry lock, V-157 inverters, V-246 potentiometer control, V-158 resistance control, V-159 digital multimeter (DMM), IV-291, V-291 digital voltmeters (DVM), III-4 3.5-digit, J-713, III-761 3.75-digit, 1-711 4 5-digit, I-717. III-760 auto-calibrate circuit, 1-714 automatic nulling, 1-712 calibrated circuit, DVM auto, I-714 interface and temperature sensor, II-647LED readout, IV-286 digital-to-analog converters, I-241, II-179-181, III-163-169, V-120 D-to -5V output, resistor terminated, I-239 3-digit, BCD, 1-239 8-bit, 1-240-241 high-speed, I-240 output current to voltage, I-243 to 12-bit, two, II-180 9-bit, CMOS, III-167 10-bit, I-238 4-quad, offset binary coding, multiplying, I-241 +10V full scale bipolar, 1-242 +10V full scale unipolar, 1-244 12-bit binary two's complement, III-166 DAC, VI-149 precision, I-242 variable step size. II-181 14-bit binary, I-237 16-bit binary, I-243 fast voltage output, I-238 high-speed voltage output, I-244 multiplying, III-168 octal converter, V-350 output amplifier, four-channel, III 165

video converter, IV-610-611 digitizer, tilt meter. 111-644-646 dimmer switches, I-369, II-309, IV-247, IV-249, VI-377 800 W. II-309 de lamp, II-307 four-quadrant, IV-248-249 halogen lamps, III-300 headlight, II-57, II-63 low-cost, 1-373 soft-start, 800-W, I-376, III-304 tandem, II-312 triac, I-375, II-310, III-303 diode emitter driver, pulsed infrared, II-292 diode tester, I-402, II-343, III-402 go/no-go, I-401 zener diodes, I-406 diode-matching circuit, IV-280 dip meters, I-247, II-182-183 basic grid, I-247 dual gate IGFET, I-246 httle dipper, II-183 varicap tuned FET, I-246 diplexer/mixer, IV-335 direction detectors/finders, IV-146-149 compasses digital design, IV-147 Hall effect, III-258 talking Hall effect, V-221 decoder, III-144 directional-signals monitor, auto. 111-48 optical direction discriminator, V-408thermally operated, IV-135 radio-signal direction finder, IV-148 - 149direction-of-rotation circuit, III-335 directional-signals monitor, auto, III-48 disco strobe light, II-610 discrete current booster, II-30 discrete sequence oscillator, III-421 discriminators multiple-aperture, window, III-781 pulse amplitude, III-356 pulse width, II-227 window, III-776-781 display circuits, II-184-188, III-170-171, V-161-167, VI-188-195 3% digit DVM common anode, II-71360 dB dot mode, II-252 audio, LED bar peak program meter, II-254 bar-graph indicator, ac signals, II-187bar-graph level gauge, VI-192 bar graph room temperature, VI-641 BCD decoder/driver, multiplexed. VI-189 brightness control, III-316 cascaded counter/display driver, V 163 color organ, VI-193 color shifting LED display, VI-189 common cathode, 4033-based, V-162common-anode, V-167 comparator and, II-105 contrast and backlight control, high-efficiency, VI-191 exclamation point, II-254

II-186 fluorescent tube, V-167 gas-discharge tube, V-167 ĽCD 7-segment, V-165 contrast temperature compensator, VI-195 large-size, V-164 LED 7-segment, V-166 audio, peak program meter, II-254 bargraph driver, VI-195 Christmas lights. VI-225 common-cathode, V-167 driver, II-188 leading-zero suppressed, V-165 two-variable, III-171 oscilloscope, eight-channel voltage. III-435 stereo level display, VI-190 voice level meter, VI-194 dissolver, lamp, solid-state, III-304 distribution circuits, II-35 distribution amplifiers audio, I-39, II-39, V-59 signal, I-39 ditherizer, VI-377 dividers, IV-150-156 binary chain, I-258 divide-by-2-or-3 circuit, IV-154 divide-by-N 1+ GHz. IV-155 1.5+ divide-by-n, IV-156 CMOS programmable, I-257 7490-divided-by-n, IV-154 divide-by-odd number, IV-153 frequency dividers, I-258, II-251, II-254, III-213-218, III-340, III-768, V-343 1.2 GHz, III-129 10-MHz, III-126 clock input, IV-151 decade, I-259 divide-by-1.5, III-216 low-cost, III-124 low-frequency, II-253 preamp, III-128 programmable, IV-152-153 staircase generator and, I-730 tachometer and, I-310 mathematical, one trim, III-326 multiplier/divider, one-quadrant, VI-318 multiplier/divider, variable analog, VI-322 odd-number counter and, III-217 pulse, non-integer programmable, II-511, III-226 Dolby noise reduction circuits, III-399, VI-421 decode mode, UI-401 encode mode, III-400 doorbells/chimes (see annuciators) door-open alarm, 11-284, 111-46, 111-256 door opener, III-366 door minder security circuit, V-5 dot-expanded scale meter, II-186 double-sideband suppressed-carrier modulator, III-377 rf, 11-366 doublers 0 to 1 MHz, II-252 150 to 300 MHz, I-314 audio-frequency doubler, IV-16-17

expanded scale meter, dot or bar,

doublers, continued broadband frequency, I-313 CRO, oscilloscope, III-439 crystal oscillator, I-184 EEPROM programming doubler circuit, VI-138 frequency, I-313, III-215, VI-369, VI-160 broadband, I-313 digital, III-216 GASFET design, IV-324 single-chip, III-218 low-frequency, I-314 voltage doublers, III-459, IV-635 cascaded. Cockcroft-Walton, IV-635 triac-controlled, III-468 downbeat-emphasized metronome, III-353-354 downconverter, ATV, VI-40-41, VI-44-45 drivers and drive circuits, I-260, II-189-193, III-172-175, IV-157-160, VI-196-202 50 ohm, I-262 alarm driver, high-power, V-2 bar-graph driver LED, II-188 transistorized, IV-213 BCD decoder/driver, multiplexed, VI-189 BIFET cable, I-264 bridge loads, audio circuits, III-35 cable driver, VI-678 capacitive load, I-263 Christmas lights driver, IV-254 coaxial cable, I-266, I-560, VI-201 five-transistor pulse boost, II-191 coil, current-limiting, III-173 CRT deflection yoke, I-265 demodulator, linear variable differential transformer, I-403 diode-emitter driver, II-292 FET driver, IV-241 fiberoptie, 50-Mb/s, III-178 flash slave, 1-483 glow-plug, II-52 high-impedance meter. I-265 high-impedance relay driver, VI-570 indicator lamp driver, III-413 instrumentation meter. II-296 lamp drivers, I-380 flip-flop independent design. IV-160 low-frequency flasher/relay, I-300 optical coupling, III-413 neon lamps, I-379 short-circuit-proof, II-310 laser driver high speed, I-263 IC-based, VI-296 op-amp circuit, VI-295 pulsed double-heterostructure laser, VI-296 single heterostructure diode. VI-290 latching relay driver, VI-571 LED drivers bar graph, II-188, VI-195 cmitter/follower, IV-159 line drivers, I-262 50-ohm transmission, II-192 600-olun balanced, II-192 audio, V-54 impedance-matched with 75 Ohm load, VI-197

low-distortion composite 100mA, VI-200 line-synchronized, III-174 load drivers audio, III-35 timing threshold, III-648 LVDT demodulator and, II-337, III-323-324 meter drivers, II-296 rf amplifier, 1-MHz, III-545 microprocessor triac array, II-410 MOSFET driver current booster, VI-368 high-side, VI-199 motor drivers (see motor control, drivers) multiplexer, high-speed hne, I-264 neon lamp, 1-379, VI-198 op amp power driver, IV-158-159 optoisolated, bigh-voltage, 11-482 piezoelectric driver, V-440, VI-470 555 oscillator, V-441 CMOS, V-440 micropositioner, V-440 full rail excursions in, II-190 high-output 600-ohm, II-193 synchronized, III-174 video amplifier, III-710 power driver, op amp, IV-158-159 pulse echo driver, VI-380 pulsed infrared diode emitter, II-292 relay, I-264 delay and controls closure tune. II-530 low-frequency, I-300 with strobe, I-266 RIAA hne amplifier/driver, VI-77 rf drivers, low-distortion, II 538 RS-232C, low-power, III-175 shield/line driver, high speed, VI-198 shift register, I-418 solenoid. I-265, III-571-573, VI-202 SSB, low-distortion 1.6 to 30 MHz, 11-538 stepping motor, II-376, III-390, IV-349, ĨV-350 stereo hne driver, VI-198 test driver for hobby servos, VI-197 three-phase motor driver. II 383 totem-pole, with bootstrapping, III-175transformer driver, I-403 transistor relay driver, VI 571 triac array driver, II-410 twisted-pair video driver/receiver circuit, VI-682 two-mput video MUX cable driver. VI-197 two-phase motor driver, 1-456, II-382 ultra low distortion 50-mA driver, VI-201 VCO driver, op-amp design, IV 362 video driver, VI-683 video cable driver, VI-200 drop-voltage recovery for long-line systems, IV-328 drum sound effect, II 591 DTMF decoder, VI 169 dual-tone decoding, II-620 dual-tracking regulator, fll-463 duplex line amplifier, telephone, III-616 duty-cycle related circuits

555 circuit, VI-446 detector, IV-144 meter, IV-275 monitor, III-329 multivibrator, 50-percent, III-584 oscillators, VI-438, VI-446 50-percent, III-426 variable, fixed-frequency, III-422 DVM adapter for PC, V-310 dwell meters breaker point, I-102 digital, III-45

E

ear protector, V-482 eavesdropper, telephone, wireless, III-620 ECG amplifiers with right leg drive, VI-354 echo effect, analog delay line, IV-21 edge detector, 1-266, III-157 EEPROM pulse generator, 5V-powered, III-99 EKG simulator, three-chip, III-350 elapsed-time timer. II-680 electric-fence charger, II-202 electric-vehicle battery saver, III-67 electrolytic-capacitor reforming circuit, IV-276 electromagnetic-field sensor, V-308 electrometer, IV-277 amphfier, overload protected, II-155 electroscope, VI-341 ion-sensing, VI-287 electrostatic detector, III-337 ELF monitor, VI-336 emergency lights, I-308, I-378, IV-250 emissions analyzer, automotive exhaust, II-51 emitter follower circuit, complementary/bilateral ac, V-353 emulators, 11-198-200 capacitance multiplier, II-200 JFET ac coupled integrator, II-200 resistor multiplier, II-199 simulated inductor, II-199 encoders decoder and, III-14 telephone handset tone dial, 1-634, III-613 tone encoders, 1-67, 1-629 two wire, ll-364 two tone, V-629 enlarger timer, II-446, III-445 envelope detectors, III-155 AM signals, IV-142 full-wave, V-152 low-level diodes, IV-141 envelope generator/modulator, musical, IV-22 EPROM, Vpp generator for, Il-114 equalizers, I-671, IV-18 octave equalizer, V-353 ten-band, graphic, active filter in, II-684 ten band, octave, Ill-658 video equalizers, VI-681 equipment-on reminder, 1-121 error checker, master/slave device, VI-389 event counter, VI-369 exhaust emissions analyzer, II-51 exit delay for burglar alarms, V-10 expanded-scale meters

analog, III-774 dot or bar, II-186 expander circuits (*sca* compressor/expander circuits) experimenter's power source, VI-507, VI-511 extended-play circuit, taperecorders, III-600 extractor, square-wave pulse, III-584

F

555 timer circuits (see also timers) alarm based on 555 timer, V-11 astable, low-duty cycle, II-267 beep transformer, III-566 dual flasher, VI-225 duty cycle oscillator, VI-446 FM modulator, V-367 integrator to multiply, II-669 missing-pulse detector, V-152 monostable multivibrator, VI-700 output indicator, LED, VI-260 ramp generator, V-203 RC audio oscillator from, II-567 square wave generator using, II-595 fader circuits, II-42, II-312, IV-17, V-658 fail-safe semiconductor alarm, III-6 fans infrared heat-controlled fan, IV-226 speed controller, automatic, III-382 thermostatic switch, V-68 Fahrenheit thermometer, I-658 fault monitor, single-supply, III-495 fax circuits, V-171-173 modem/fax protector for two computers, V-482 fax/telephone switch, remotecontrolled, IV-552-553 feedback oscillator, I-67 fence chargers, II-201-203 battery-powered, II-202 electric, II-202 solid-state, II-203 FET circuits amplifier, offset gate bias, V-22 crystal oscillators, VI-157 de controlled switch, V-592 hexFET switch, V-592, V-593 dual-trace scope switch, II-432 input amplifier, II-7 microphone mixer, V-363, V-364 preamp for phono cartridge, VI-79 probe, III-501 voltmeter, III-765, III-770 fiberoptics, II-204-207, III-176-181, vi-206-207 data receiver, VI-207 data transmitter, VI-207 driver, LED, 50-Mb/s, III-178 interface for, II-207 LED lightwave communications receiver, VI-310 LED lightwave communications transmitter, VI-309 link, I-268, I-269, I-270, III-179 motor control, dc, II-206 receivers 10 MHz, II-205 50-Mb/s, III-181 digital, III-178 high-sensitivity, I-270 low-cost, 100-M baud rate, III-180 low-sensitivity, I-271

very-high-sensitivity, lowspeed, 3nW, I-269 repeater, I-270 speed control, II-206 transmitter, III-177 field disturbance sensor/alarm, II-507 field-strength meters, II-208-212, III-182-183, IV-164-166. V-174-176 1.5-150 MHz, I-275 adjustable sensitivity indicator, I-274 amplified field, V-175 high-sensitivity, II-211 LF or HF, II-212 nucrowave, low-cost, I-273 remote, V-175 rf sniffer, II-210 sensitive, I-274, III-183 signal-strength meter, IV-166 simple design, three versions, V-176 transmission indicator, II-211 tuned, I-276 UHF fields, IV-165 untuned, I-276 filter circuits, II-213-224, III-184-192, IV-167-177, V-177-191, VI-208-222 active (see active filters) analog, programmable, VI-215 antialiasing/sync-compensation, IV-173audio filters biquad, I-292-293, HI-185 tunable, IV-169 andio range filter, V-190 bandpass (see bandpass filters) bandpass amplifier, VI-54 band-reject, active, II-401 biquad, I-292-293 audio, I-292-293, III-185 RC active bandpass, I-285, V-190 bridge filter, twin-T, programmable, II_{-221} Butterworth active, VI-220 fourth-order, 1-kHz, VI-222 high-pass, fourth-order, I-280, V-179 low-pass, fourth-order, V-180, V-181 Chebyshev (see Chebyshev filters) comb filter, digital, VI-218 combination filter, VI-212 CW filter, II-219, VI-29, VI-405 dynamic filter, III-190 four-output filter, V-182 full wave rectifier and averaging, I-229, V-191 high pass (see high-pass filters) highpass amplifier, VI-49 IF filters narrow-band, V-189 shortwave receiver, VI-212 L filters, V-181 low-pass (see low-pass filters) lowpass amplifier, VI-49 LP filter, active, VI-215 networks of, I-291 noise, dynamic, III-190 noisy signals, III-188 notch filters, 1-283, 11-397-403, III-402-404 4.5 MHz, 1-282 550 Hz, II-399 1800 Hz, II-398 active band reject, II-401

adjustable Q, II-398, V-179 audio, II-400 bandpass and, II-223 high-Q, III-404, V-178, VI-213, VI-217, VI-220 RC, VI-221 selectable bandwidth, I-281 three-amplifier design, I-281 tunable, II-399, II-402, V-179 passive-bridged differentiator, II-403 hum-suppressing, I-280 op amp, II-400 twin T notch for 1 kHz, V-183 twin-T, III-403 shortwave receivers, V-185 Wien bridge, II-402 passive L filters, V-181 passive PI filters, V-181 passive T filters, V-190 Pi filters, V-181 PIN diode filter selection circuits, VI-213 programmable, twin-T bridge, II-221 rejection, I-283 ripple suppressor, IV-175, IV-396 rimble, III-192, III-660, IV-175 LM387 in, I-297 turntable, IV-170 rumble/scratch, III-660 Sallen-Key filters 10 kHz, I-279 500 Hz bandpass, I-291 current-driven, V-189 high-pass, VI-209 low-pass, active, IV-177, VI-221 low-pass, equal component, 1 - 292saw-filter impedance-matching preamp, VI-222 scratch filters, III-189, III-660, IV-175 LM287 in, I-297 second-order voltage-controlled, VI-211 shortwave AM broadcast trap, VI-214 shortwave interference trap, VI-214 simulated inductor, V-180 speech filters bandpass, 300 Hz 3 kHz, I-295 second-order, 300-to-3,400 Hz, IV-174 two-section, 300-to-3,000 Hz, IV-174 speech-range filter, bandpass, V-185 state-variable filters, II-215, III-189. VI-209, VI-216 multiple outputs, III-190 second-order, 1 kHz, Q/10, 1-293 universal, 1-290 T filters, V-190 tone filter, V-1 kHz, V-191 turbo, glitch free, Ill-186 twin-T bridge filter, ll-221 Wien-bridge, III-659 variable Q filter, V-183 variable-frequency bandpass filter. V-186 variable-state, universal, V-178 voltage-controlled filters, III-187, IV-176, VI-211 VSB filter for LM 2880, VI-219 First-Response game, VI-247, VI-250, VI-262, VI-253

751

fish lure, electronic, VI-386 fixed power supplies, III-457-477, IV-390-408 12-VDC battery-operated 120-VAC, III-464 +24 V, 1.5 A supply from +12 V source, IV 401 ± 35 V ac, IV-398 ± 35 V, 5 A, mobile, IV-407 15 V isolated to 2,500 V supply, IV-407 ac motors, IV-395 automotive battery supply, ±15 V and 5 V, IV-391 auxiliary supply, IV-394 bias/reference applications, auxiliary negative dc supply, IV-404 bilateral current source, III-469 bridge rectifier, IV-398 charge pool, III-469 charge pump, regulated, IV-396 constant-current source, safe, III-472 converter, III-470 5V-to-isolated 5V at 20MA, III-474 ac-to-dc, IV-395 dc-to-dc, 3-to-15 V, IV-400 current sink, 1 mA, IV-402 current sources, IV-399, IV-405, IV 406 dc adapter/transceiver, hand-held, III-461 dual-tracking regulator, III-462 **GASFET** power supply, IV-405 general-purpose, Ill-465 inverter, 12 V input, IV-395 isolated feedback, III-460 LCD display power supply, IV-392, IV-403 linear regulator, low-cost, lowdropout, III-459 low-current source, IV-399 low-power inverter, III-466 negative rail, GET, with CMOS gates, IV-408 negative supply from +12 V source, TV-401 negative voltage from positive supply, IV-397 output stabilizer, IV-393 portable-radio 3 V power supply, IV-397 positive and negative voltage power supplies, IV-402 pnp regulator, zener mereases voltage output, II-484 programmable, III-467 rectifiers, III-471, IV-398 regulated supplies, III-462, III-463, IV-401 mpple suppressor, IV-396 RTTY machine current supply, IV-400 stabilizer, CMOS diode network, IV-406 switching supplies, HI-458, III-473, IV-403, IV-404, IV-408 three-rail, III-466 uninterruptible +5V, III-477 voltage doubler, III-459, III-468 voltage regulators (see voltage regulators) voltage-controlled current source/ grounded source/load, III-468 fixed-frequency generator, III-231

flame ignitor. III-362 flame monitor, III-313 flash/flashbulb circuits (see photography-related circuits) flashers and blinkers (see also lightcontrolled circuits, photographyrelated circuits), I-304, II-225, III-103-210, IV-178-183, V-192-197, VI-223-227 1.5 V, minimum power, I-308 1 kW flip-flop. II-234 1A lamp, 1-306 2 kW, photoelectric control in. II-232 3V. I-306 ac, III-196 alternating, I-307, II-227 astable multivibrator, III-196 auto, I-299 automatic safety, 1-302 automotive turn signal, sequential, 1 - 109bar display with alarm, 1-252 barricade, 1-299 boat, 1-299 brake light flasher, V-69 Christmas tree light flasher. V-197, V-264-265 CMOS, III-199 dc, adjustable on/off timer, 1-305 dual flasher for 555 circuits, VI-225 dual LED CMOS, I-302 electronic, II-228 emergency lantern, I-308 fast-action, I-306 flash light, 60-W, III-200 flicker light, IV-183 flip-flop, 1-299 four-parallel LED, I-307 headlight flasher, V-73 high-efficiency parallel circuit, I-308 high-voltage, safe, I-307 high-power battery operated, II-229 incandescent bulb, I-306, III-198 lamp pulser, VI-227 LED flashers, IV-181, V-195, V-196 2- to 10-LED, V-196, VI-226, VI-227 alternating, III-198, III-200 Christmas tree lights, V-197, VI-225 control circuit, IV-183 dark-activated, V-195 driver. V-194 light-switched, VI-301 multivibrator design, IV-182 pulser, VI-226 PUT used m, II-239 ring-around, III-194 sequential, reversible-direction. IV-182 strobe, VI-224 three-year, III-194 UJT used in, II-231 low-current consumption, II-231 low-voltage, I-305, II-226 miniature transistorized, II-227 minimum-component, III-201 model railroad crossing flasher, VI-395 motorcycle brake light flasher, VI-12neon flashers, I-303, VI 225 five-lamp, III-198 two-state oscillator, III-200 tube, I-304

oscillator/flashers high-drive, II-235 low-frequency, II-234 photographic flashes slave-flash trigger, SCR design, IV-380, IV-382 time-delay flash trigger, IV-380 relay driver, low-frequency lamp, I-300 running lights, V-269 SCR flashers, II-230, III-197 chaser, III-197 relaxation, II-230 ring counter, III-195 sequencer, V-263, V-264-265 sequential, II-233, II-238, IV-181, V-193pscudorandom simulated, IV-179 signal alarm, V-197 single-lamp, III-196 strobe alarm, IV-180 telephone, II-629, IV-556, IV-558, IV-559, IV-561 transistorized, I-303, II-236, III-200 variable, I-308 xenon light, IV-180 flashlight, rechargeable LED light, VI-107 flashlight finder, I-300 flex switch, alarm sounder circuit, V-15 flip-flops (see bistable multivibrators) flood alarm, 1-390, III-206, IV-188 flow-detectors, 11-240-242, 111-202-203 air, II-242 hquids, 11-248, 111-202-203 low-rate thermal, III-203 thermally based anemometer, II-241fluid and moisture detectors, I-388, I-390, 1-442, II-243-248. III-204-210, IV-184-191, V-373-375 acid rain monitor, II-245, V-371 alarm, water-activated, V-374 checker, Ill-209 control, 1-388, III-206 cryogenic fluid-level sensor, I-386 dual, III-207 Bood alarm, III-206, IV-188, V-374 flow-of liquid. II-248, III-202-203 full-bathtub indicator. IV-187 full-cup detector for the blind. IV-189 humidity, II-285-287, III-266-267, VI-255-257 hydrophone, VI-378 indicator, II-244 level of liquid, I-107, I-235, I-387, I-388, I-389, I-390, II-174, II-244, II-246, III-205, III-206, III-207. III-209, III-210, IV-186, IV-190, IV-191 moisture detector, I-442, IV-188, V-375 monitor, III-210 plant water, II-245, II-248, III-208 pump controller, single-chip, II-247 rain alarm, II-244, IV-189 sensor and control, II-246 soil moisture, II-245, II-248, III-208 temperature monitor, II-643, III-206 water-leak alarm, IV-190 windshield-washer level, I-107

fluorescent lamos high voltage power supplies, coldcathode design, IV 411 inverter, 8-W, III-306 vacuum, fluorescent display, II-185 flyback converters, I-211 self oscillating, I-170, II-128, III-748 voltage, high-efficiency, III-744 flyback power supply, VI-531 flyback regulator, off-line, II-481 FM-related circuits (see also radio/ rf circuits) 5 V, I-233 12 V. I-233 antenna booster, tunable, VI 65 antenna for automobile radio, VI-64.65bug, VI-662 clock radio, AM/FM, 1-543 decoder, VI-170 demodulators, I-544, II-159, II-161, V-151 FM-modulated oscillator, VI-449 FM/AM receiver, VI-541 high frequency oscillator, VI-456 IF amplifier with quadrature detector, TV sound IF, 1-690 infrared FM audio reception, VI-268 generators, low-frequency, III-228 modulators, V-366 555-based circuit, V-367 NB FM audio amplifier, VI-74 radio, 1-545 receivers 27.145 MHz, V-495 earrier-current circuit, III-80 light-beam, V-259 MPX/SCA receiver, III-530 narrow-band, III-532 optical receiver/transmitter, 50 kHz, I-361 zero center indicator. I-338 SCA subcarrier adapter, V-536 scanner noise squelch, VI-579 snooper, III-680 speakers, remote. carrier-current system, I-140 squelch circuit for AM, I-547 stereo demodulation system, I-544 transmitters, I-681, V-641 27.125-MHz NBFM, V-637 49-MHz, V-643 infrared, voice-modulated pulse, IV-228 light-beam, V-259 multiplex, III-688 one-transistor, III-687 optical, I-367, II-417 optical receiver/transmitter, 50 kHz, I-361 radio, V-648 snooper, III-680 stereo, V-575, V-580, VI-662 voice, III-678 tamer. I-231, III-529 wireless microphone. III-682, III-685, III-691 FM/AM clock radio, I-543 fog-light controller, automotive, IV-59 foldback current, HV regulator limting, II-478 followers, III-211-212 inverting, high-frequency, III-212 noninverting, high-frequency, III-212 source, photodiode, III-419

unity gain, I-27 voltage, III 212 forward-current booster, III-17 free-running multivibrators, II-485 100 kHz, 1-465 programmable-trequency, III 235 free-running oscillators, I-531 square wave, I-615 freezer, voltage, III-763 freezer-meltdown alarm, I-13 frequency comparators, II-109, III-88 LED, II-110 VCO and input, VI-353 frequency control, telephone, II-623 frequency converter, I-159 Trequency counters, III-340, III-768. (v-300, V-129-133, VI-360 1.2 GHz, III-129 2 MHz, V-130-131 10-MHz, III-126, V-132-133 100 MHz, period and, II-136 low-cost, III-124 preamp, III-128, V-24 precision, 1-253 tachometer and, I-310 frequency detectors, II-177, III-158, VI-180 beat indicator, I-336 boundary detector, III-156 comparator, III-88 digital, III-158 limit, frequency limit, II-177 window, frequency window, III-777 frequency dividers, 1-258, II-251, II-254, III-213-218, III-340, III-768, V-343 1.2 GHz, III-129 10-MHz, III-126 10-MHz frequency standard, VI-341 clock input, IV-151 decade, I-259 divide-by-1.5, III-216 low-cost, III-124 low-frequency, II-253 preamp, III-128 programmable, IV-152-153 staircase generator and, I-730 tachometer and, I-310 frequency-division multiplex stereo decoder, II-169 frequency doublers, I-313, III-215, VI-369 broadband, I-313 digital, III-216 GASFET design, IV-324 low-frequency, I-314 single-chip, III-218 to 1 MHz, 11-252 frequency generators, fixedfrequency, III-231 frequency indicator, beat, I-336 frequency inverter, III-297 frequency meters, I-310, II-249-250, IV-282, IV-301, VI-335 analog, V-307 audio-frequency meter, V-305, V-320 audio, I-311 linear, I-310 low-cost, II-250 power, II-250 frequency multipliers, II-251, III-213-218, V-198-199, VI-388 counter, odd-number, III-217 doublers, I-313, III-215 broadband, I-313 digital, 01-216

GASFET design, IV-324 single-chip, III-218 low-frequency, 1-314 to 1 MHz, 0-252 pulse-width, III-214 tripler, nonselective, II-252 frequency-boundary detector, III-156 frequency oscillator, tunable, II-425 frequency probe, VI-524 frequency-ratio monitoring circuit, W-202 frequency shift key (FSK) communications data receiver, III-533 decoder, 10 8 MHz, 1-214 generator, low-cost design, III-227 keying circuits, IV-245 frequency standard, VI-10-MHz, VI-361 frequency synthesizer, programmable voltage controlled, II-265 frequency-to-voltage converter, I-318, II-255-257, III-219-220, VI-231-233 de, 10 kHz, I-316 digital meter, I-317 optocoupler input, IV-193 sample-and-hold circuit, IV-194 single-supply design, IV-195 zener regulated, I-317 fuel gauge, automotive, IV-46 full-wave rectifiers, IV-328, IV-650 absolute value, II-528 averaging filter, V-191 op amp circuit, V-403 precision, I-234, III-537 silicon-controlled (SCR), I-375 function generators (see also burst generators; sound generators; waveform generators), I-729, II-271, III-221-242, III-258-274. IV-196-202, V-200-207, V-309, VI-234-243 555 astable, low-duty cycle, II-267 acoustic field generator. V-338-341, V-338 AM broadcast-band signal generator, IV-302 AM/IF signal generator, 455 kHz,+ IV-301 astable multivibrators, II-269, II-510, II-597, III-196, III-224, III-233, III-237, III-238 audio function generator, IV-197 audio-frequency generator, V-416-417, V-416 bistable multivibrators, I-133, I-299, I-395, II-367, II-465, III-103, IV-108, ÍV-651 bistable multivibrators, I-133, II-465 capacitance multiplier, V-205 clock generator/oscillator, I-193, I-615 complementary signals, XOR gate, III-226 DAC controlled, I-722 debouncer, IV-108 emitter-coupled RC oscillator, II-266fixed-frequency, III-231 flasher, I-299, II-234 FM, low-frequency, III-228 free-running multivibrator, programmable-frequency, III-235 frequency-ratio monitoring circuit, IV-202

function generators, continued frequency synthesizer, programmable voltage controlled, 11-265 FSK, low-cost, III-227 harmonic generators, I-24, III-228, IV-649 high-frequency, II-150 inverter, III-103 lamp driver, IV-160 hne/bar generator, video, V-662 linear ramp, II 270 linear triangle/square wave VCO. II-263logarithmic dynamic-range, V-201 fast acting, V-202 monostable multivibrators, 1-465, III-229, III-230, III-235, III-237 input lockout, 1-464 linear-ramp, III-237 photocell, monostable, II-329 positive-triggered, III-229 TTL, monostable operation, I-464 UJT, monostable operation, 1-463 video amplifier and comparator, II-268 multiplying pulse width circuit, Il-264 multivibrators low-frequency, III-237 single-supply, H1-232 nonhnear potentiometer outputs, IV-198 one-shots, I-465, VI-419 digitally controlled, I-720 precision, III-222 retriggerable, ill-238 oscillator/amplifier, wide frequency range, 11-262 pattern generator/polar-to-rect. converter, V-288 polynomial generator, V-287 potentiometer-position V/F converter, IV-200 precise wave, 11-274 programmed, 1-724 pseudo-random bit sequence generator, V-351 pulse generators, II-508-511 2-ohn. III-231 300-V, III-521 555-circuit, IV-439 astable multivibrator, II-510 clock, 60 Hz, II-102 CMOS short-pulse, III-523 delayed-pulse, II-509, IV-440 divider, programmable, II-511, 111-226 EEPROM, 5V-powered, III-99 free running, IV-438 interrupting pulse-generation, 1-357logic, III-520 logic troubleshooting applications, IV:436 programmable, I-529 sawtooth-wave generator and, III-241 single, II-175 train, pulse train, IV-202 transistorized, IV-437 two-phase pulse, I-532 unijunction transistor design, I-530very low-duty-cycle, III-521

voltage-controller and, III-524 wide-ranging, III-522 quad op amp, four simultaneous synchronized waveform, II-259 ramp generators, I-540, II-521-523, III-525-527, IV-443-447 555 based, V-203 accurate, III-526 integrator, initial condition reset, III-527 linear, II-270 variable reset level, II-267 voltage-controlled, II-523 rf oscillator, V-530-531 root extractor, V-207, V-288 RS flip-flop, I-395 sawtooth generators, V-491 linear, V-205 triggered, V-204 sawtooth and pulse, III-241 Schunitt tragger, transistorized, V-204 SCR, II-367 self-retriggering timed-on generator, V-343 signal generators, V-204 AM broadcast band, IV-302 AM/IF, 455 kHz, IV-301 high-frequency, II-150 square-wave, III-583-585 staircase, III-586-588 two-function, III-234 sine-wave generators, IV-505, IV-506, V-542, V-543, V-544 60 Hz, IV-507 audio, II-564 battery power, V-541 LC, IV-507 LF, IV-512 oscillator, audio, III-559 square-wave and, tunable oscillator, III-232 VLF audio tone. IV-508 sine/cosine (0.1-10 kHz), II-260 sine/square wave oscillators, I-65 TTL design, IV-512 tunable, I-65, III-232 single control, III-238 single supply. II-273 square-wave generators, II-594-600, III-225, III-239, III-242, III-583-585. IV-529-536, V-568-570 1 kHz, IV-536 2 MHz using two TTL gates, II-598 555 timer, II-595 astable circuit, IV-534 astable multivibrator, II-597 CMOS 555 astable, true rail-torail, II-596 duty-cycle multivibrator, III-50-percent, UI-584 four-decade design, IV-535 high-current oscillator, III-585 line frequency, II-599 low-frequency TTL oscillator, II-595 multiburst generator, II-88 multivibrator, IV-536 oscillators, 1-612-614, I-616, II-596, II-597, II-616, IV-532, IV 533 phase-tracking, three-phase, II-598 pulse extractor, III-584 quadrature-outputs oscillator, W-585 sine-wave and, tunable oscillator, III-232

three-phase, II-600 tone-burst generator, single timer IC, II-89 triangle-wave and, III-239 precision, III-242 programmable, III-225 wide-range, III-242 TTL, LSTTL, CMOS designs, IV-530-532 variable duty-cycle, IV-533 variable-frequency, IV-535 SR flip-flop, IV-651 stable function generator, VI-242 staircase generators, I-730, II-601-602, III-586-588, IV-443-447 sweep generators, I-472, III-438, VI-238-241 timebase 1 Hz, readout and counter applications, IV-201 oscilloscopes, V-425 time-delay generator, 1-217-218 tone burst generator, repeater, V-629 triangle-wave, III-234, V-203, V-205 clock-driven, V 206 square wave, III-225, III-239, İII-242 timer, linear, III 222 triangle/square wave generator, V-206 tunable,-wide-range, III-241 two-function, III-234 UJT monostable circuit insensitive to changing bias voltage, Il-268 variable duty cycle timer output, III-240 voltage controlled high-speed one shot, II-266 waveform (see waveform generators) white noise generator, IV-201 wide-range function generator, VI-243 funk box, II-593 furnace exhaust gas/smoke detector, temp monitor/low-supply detection. III 248 furnace fuel miser, V-328-329 fuses battery-charger relay fuse, V-88 electronic, V-477 monitor for car fuses, V-77 relay fuse, V-478 fuzz box, III-575 fuzz sound effect, II-590 G GaAsFET circuits amphfier, power, with single supply, İI-10 fixed power supplies, IV-405 gain control circuits amplifier, stereo, gain-controlled, II-9, 111-34 automatic audio gain control, II-17 automatic gain control (AGC), II-17 AGC system for CA3028 IF amp, IV-458 rf amplifier, wideband adjustable, III-545 squelch control, III-33

- wide-band amplifier, III-15
- gain block, video, III-712
- galvanometer, sine/cosine generator, VI-700

game feeder controller, II-360 game roller, I-326 games, II-275-277, III-243-245, IV-203-207, V-208-211, VI-244-254 coin flipper, III-244 coin toss game, VI-250 craps game, VI-245 electronic dice, III-245, IV-207 electronic roulette. II-276, IV-205 First-Response Monitor, VI-247, VI-250, VI-252, VI-253 fish lure, electronic, VI-386 Jacob's Ladder, VI-389 lie detector, II-277, IV-206 model car derby winner indicator, VI-259 one-arm bandit game, VI-251 quiz master, V-210 reaction timer, IV-204 ring launcher, electromagnetic, V-209 roulette, II-276, IV-205 run-down clock/sound generator, IV-205 slot machine, V-211 Twenty-One game, VI-246 Wheel-of-Fortune, IV-206, VI-254 who's first, III-244 Z-Dice game, VI-248-249 garage stop light, II-53 gas detectors (see also smoke alarms and detectors), 1-332, II-278-279, III-246-253, V-212-214 analyzer and, II-281 combustible gas detector, V-214 explosive gas detector, V-213 furnace exhaust, temp monitor/lowsupply detection, III-248 methane concentration, linearized output, III-250 toxic, II-280 SCR, III-251 smoke/gas/vapor detector, III-250 gate dip oscillator, VI-344, VI-346 gated oscillator, last-cycle completing, III-427 gated-pulse descrambler, II-165 gates, V-215-216 AND, I-395, V-216 OR, I-395 programmable, I-394 syne gating circuit, V-595 XOR gate, IV-107 Geiger counters, I-536-537, V-217-219, VI-531 high-voltage supply, II-489 pocket-sized, II-514 gel cell charger, II-66 generators, electric-power corona-wind generator, IV-633 de generator, V-443 high-voltage generators, IV-413 ion generator, V-248-249 battery powered, III-482 capacitor-discharge, III-485 de voltage, III-481 negative-ions, IV-634 regulator for automobile generator, V-76 ultra-high-voltages, II-488 generators (see function generators; sound generators; waveform generators) glitch-detector, comparator, II-107 glow-plug driver, II-52 gong, electronic, V-563

graphic equalizer, ten-band, active filter in, II-684 grid-dip meters, I-247, II-182-183 bandswitched, IV-298 basic grid, I-247, IV-298 dual gate IGFET, I-246 little dipper, II-183 varicap tuned FET, I-246 grid-leak detector, VI-179 grounding ground loop preventer, VI-390 tester, II-345 ground-fault Hall detector, IV-208 209ground-noise probe, batterypowered, III-500 pseudoground, VI-431 guitars compressor, sound-effect circuit, IV-519 matching aucho signal amplifiers, IV-38 mixer, low-noise, four-channel, V-360-361 treble boost for, II-683 tuner, II-362 gun, laser, visible red and continuous, III-310 Н half-duplex information transmission link. III-679 half-flash analog-to-digital converters, III-26 half-wave ac phase controlled circuit, I - 377half-wave rectifiers, I-230, III-528, IV-325fast, I-228 Hall-effect circuits, II-282-284, III-254-258, V-220-222 angle of rotation detector, II-283 compass, III-258 compass, talking, V-221 current monitor, III-255, IV-284 door open alarm, II-284 ground-fault detector, IV-208-209 oscillators, V-222 security door-ajar alarm, III-256 switches using, III-257, IV-539 halogen lamps dimmer for, III-300 protector, V-271 handitalkies, I-19 two-meter preamplifier for, I-19 hands-free telephone, III-605 hands-off intercom, III-291 handset encoder, telephone, III-613 harmonic distortion analyzer, V-291, VI-357 meter, V-312 harmonic generators, 1-24, III-228, IV-649 Hartley oscillator, I-571, V-140, Vi-453, VI-459 HC-based oscillators, III-423 HCU/HTC-based oscillator, III-426 headlights (see automotive circuits, headlights) headphones amplifier for, II-43 car protector circuit, V-482 infrared (IR) receiver, V-227, VI-269 infrared (IR) transmitter, V-227, VI-263

signal amplifier, V-53, V-57 heart rate monitor, II-348, II-349, V-342 heat-activated alarm, V-9 heat sniffer, electronic, III-627 heaters/heater controls (see also temperature-related circuits), I-639 element controller, II-642 induction heater, ultrasonic, 120kHz 500-W, III-704 protector circuit, servo-sensed, III-624 temperature sensitive, I-640 hee-haw siren, II-578, III-565 hexFET switch, V-592 dual-control, V-593 hi-fi circuits (see stereo circuits) high-pass filters, I-296, VI-210, VI-221 active, I-296, V-180, V-188, VI-213 fourth-order, V-188 second-order, I-297 amplifier, VI-49 Butterworth, fourth-order, I-280, V-179Chebyshev, fourth-order, III-191 equal components second-order, V-188 fourth-order, 100-Hz, IV-174 Sallen Key, VI-209 second-order, 100-Hz, IV-175 sixth-order elliptical, III-191 unity-gain second-order, V-187 variable, V-186 wideband two-pole, II-215 high-voltage power supplies (see also generators, electrical power; power supplies), II-487-490, III-486, IV-409-413, V-442-447, VI-499-505 9- to 15-Vde input, V-456 -100-Vdc supply, VI-502 12-V supply for fluorescent lamp, VI-500 10,000 V dc supply, IV-633 ac operated He-Ne laser power supply, VI-502 arc-jet power supply, starting circuit, III-479 basic circuit, V-446 battery-powered generator, III-482 bucking regulator, III-481 control circuit, VI-501 dc generator, III-481, V-443 de supply, 120-240 Vdc, single-chip eircuit, V-446 fluorescent-lamp supply, V-444 cold-cathodc design, IV-411, V-447 Geiger counter supply, II-489 generators (see generators, electrical power) inverter, III-484 40 W, 120 V ac. IV-410-411 Kirlian device supply, VI-504 laser circuits, V-253 negative supply, V-445 negative-ion generator, IV-634 night-vision scope power supply, VI-501 optoisolated driver, III-482 photomultiplier supply, V-444, V-445 preregulated, III-480 pulse supply, IV-412 pulse-width modulated laser supply, VI-505

high-voltage power supplies continued regulators, III-485 foldback-current limiting, II 478 solid-state, remote adjustable. III 486 strobe power supply, IV-413 tripler, VI-504 tube amplifier, high-volt isolation, IV-428 ultra high-voltage generator, II-488 voltage regulators, VI-500, VI-508, VI-505 hobby circuits (see model and hobby circuits) hold button, telephone, I 612, II-628 home security systems (see alarms; annuciators) horizontal deflection circuit, VI-382 horn, automobile, III-50, IV-54 hour/time delay sampling circuit, II-668 Howland current pump. II-648 hum reducer circuit, receivers, V-347 humdity sensor, II-285-287. III-266-267, VI 255-257

hybrid power amplifier, III-455 hydrophone, VI-378

I

IC product detectors, IV-143 IC timer, crystal-stabilized, subharmonic frequencies for, II-151 ice formation alarm, I-106, II-57, II-58 ICOM IC-2A battery charger, II-65 IF amphfiers, I-690, IV-459 AGC system, IV-458 preamp, IV-460 receiver, IV-459 quadrature detector, TV sound IF, I-690 two-stage, 60 MHz, I-563 video IF amplifier/detector. VI-678 wideband, I-689 ignition circuits, automotive, V-64 capacitor discharger, I-103 cut-off circuit, automotive, IV-53 electronic. IV-65 substitute ignition, III-41 timing light for ignition system, II-60 ignitor, III-362 illumination stabilizer, machine vision, II-306 image canceller, III-358 immobilizer. II-50 impedance checker, V-136 impedance converter, high-to low, I-4 impedance sensor, nanoampere, 100 megohm input. I-203 indicators (see measurement/test circuits) in-use indicator, telephone, II-629 inductance meter/tester, V-316, VI-330, VI-358 induction heater, ultrasonic, 120-kHz 500-W, III-704 unductors active, I-417 simulated, II-199, V-180 infrared circuits (*see also* light controlled circuits: remote control devices), II-288-292, III-271-277, IV-219 228, V-223-229, VI-261 271

data link, I-341 detector, 11-289, 111-276, IV-224, V-225, VI-262, VI-266 emitter drive, pulsed, II-292 fan controller, IV-226 filter circuit, narrow-band, V-189 headphone receiver, V-227 headphone transmitter. V-227 ion detector, VI-267 IR pulse-to audio converter, V-224 laser light detector, VI-293 laser rifle, invisible pulsed, II-291 long-range object detector, III-273 loudspeaker link, remote, I-343 low-noise detector for, II-289 night-vision illuminator, VI-265 object detector, long-range, III-273 people-detector, IV-225 preamplifier for IR photodiode, V-226proximity switch, infraredactivated, IV-345 receivers, 1-342, 11-292, 111-274, IV-220-221, V-226, V-229, VI-268 audible-output, VI-271 data-link, low power, VI-265 FM audio reception, VI-268 light, VI-294 pulse frequency modulated. VI-269 single-tone, VI-264, VI-270 steady-tone, VI-267 wireless headphones, VI-269 remote A/B switch, V-225 remote controller, I-342, IV-224, V-229remote-control analyzer, V-224 remote-control tester, IV-228, V-228, V-229 remote-extender, IV-227 transmitters, I-343, II-289, II-290, III-274, III-276, III-277, IV-226-227 audio-modulated, VI-262 digital, III-275 pulsed for on/off control, V-228 remote-control, I-342 voice-modulated pulse FM, IV-228 wireless headphones, VI-263 TV remote control relay, VI-263 wireless speaker system, III-272, IV-222-223 injectors three-in-one set: logic probe, signal tracer, injector, IV-429 injector-tracers, I-521, I-522, II-500 input selectors, audio, low-distortion, II-38 input/output buffer, analog multiplexers, III-11 input/output circuits, NE602-based, V-355 instrumentation amplifiers, 1-346, 1-348, 1-349, 1-352, 11-293-295, 111-278-284, IV-229-234, V-233-235, VI-272-277 ±100 V common mode range, ill-294ac-coupled, VI-276 current collector head amplifier. II-295 differential. 1-347, 1-354, III-283 biomedical, III-282 high-gain, 1-353 input, 1-254, VI-275 variable gain, 1-349

body-heat detector, VI-266

extended common-mode design, IV-234 high mput-impedance, VI-275 high-impedance low-drift, I-355 high-speed, I-354 LM6218-based, high-speed, V-235 LMC6062-based, V-234 low-drift/low-noise de amplifier, IV-232 low-signal level/high-impedance, I-350 low-noise, VI-276 low-power, 111-284, VI-276 meter driver, II-296 preamps oscilloscope, IV-230-231 thermocouple, III-283 precision FET input, I-355 programmable gain, VI-275 saturated standard cell amplifier, H-296stram gauge, III-280 triple op amp, I-347 ultra low-noise, VI-277 ultra-precision, III-279 variable gain, differential input, I-349, VI-274 very high-impedance, I-354 wideband, III-281 instrumentation meter driver, II-296 integrators, II-297-300, III-285-286, V-236-237, VI-278-279 ac integrator, VI-279 active, inverting buffer, II-299 bias-current compensated. VI-279 JFET ac coupled, II-200 gamma ray pulse, 1-536 long time, II-300 low-drift, I-423 noninverting, improved, II-298 photocurrent, II-326 programmable reset level, III-286 ramp generator, initial condition reset, III-527 resettable, III-286 intercoms, I-415, II-301-303, III-287-292, V-238-240, VI-376 bidirectional, III-290 carrier current, I-146 hands-off, III-291 party-line, II-303 pocket pager, III-288 telephone-intercoms, IV-557, V-239, V-240 two-way, III-292 two-wire design, IV-235-237 voice-activated, one-way, V-239 intercoms (see also telephonerelated circuits), V-238 interfaces (see also computer circuits), IV-238-242, V-241-244, VI-280-281 680x. 650x, 8080 families, III-98 amateur radio transceiver, relay interface, V-243 audio/telephone interface, VI-625 audio-to-ADC interface, V-242 cassette-to-telephone, III-618 CPU interface, one-shot design, IV-239DVM, temperature sensor and, II-647 FET driver, low-level power FET, IV-241 fiberoptic, II-207 keyboard matrix interface, IV-240 logic-level translators, IV-242

microcomputer-to-triac interface. V-244 optical sensor-to-TTL, III-314 optocouplers, V-406-407 optoisolators, V-406-407 preamp receiver interface, V-243 process control, I-30, V-242 RC receiver relay interface, VI-551 remote-control transmitter interface, V-511 resistive transducer interface, VI-281 RS-232, computer-powered, VI-138-139 RS-422 to RS-232 converter, VI-133 tape recorder, II-614 telephone audio interface, V-612 telephone-line interface, V-605 timer/ac line interface, VI-281 transmit keyer interface circuit, VI-31 video interface with sync stripper, V-659 interrupter, ground fault, I-580 interval timer, low-power, microprocessor programmable, II-678[°] intruder-detector, light beam activated, V 11 preamp, V-13 inverters, III-293-298, V-245-247, VI-282-285 250 watt, V-246 analog switched inverter, VI-604 dc-to-ac, V-247 dc-to-dc/ac, I-208 digital, V-246 fast, I-422 fixed power supplies, 12 V input, IV-395 flip-flop, III-103 fluorescent lamp, 8-W, III-306 frequency inverter. III-297 high-voltage, III-484 40 W, 120 V ac, IV-410-411 low-power, fixed power supplies, III-466 on/off switch, III-594 picture, video circuits, III-722 positive-to-negative dc/dc inverter, VI-285 power, III-298 12 VDC-to-117 VAC at 60 Hz, III-294 medium, III-296 MOSFET. III-295, V-247 rectifier/inverter, programmable op-amp design. IV-364 signal source for audio amplifier/inverter. VI-702 ultrasonic, arc welding. 20 kHz, III-700 variable frequency, complementary output, III-297 voltage, precision, III-298 inverting amphfiers. I-41-42, III-14 ac, high-gain, I-92 balancing circuit in, I-33 gain of 2, lag-lead compensation, UHF. 1-566 low-power, digitally selectable gain, II-333 power amplifier. I-79 programmable-gain, III-505 SCR inverter and trigger, VI-283 sine-wave inverter. VI-285

unity gain amphfier, I-80 vehicle audio amplifier inverter. VI-284 wideband unity gain, I-35 ion detector, VI-267, VI-533 ion generator, V-248-249, VI-286-288 isolated feedback power supply, III-460isolation amplifiers capacitive load, I-34 level shifter, 1-348 medical telemetry, I-352 rf, II-547 isolation and zero voltage switching logic, II-415 isolation transformer, V-349, V-470 isolators analog data-signal transmission, IV-133 digital transmission, II-414 stimulus, III-351 л Jacob's Ladder, VI-389 JFET circuits ac coupled integrator, III-200 amplifiers 500-Mohm input impedance, V-23 current source biasing, V-21 chopper circuit, V-352 headphone audio signal amplifiers, V-57 oscillator, variable frequency, VI-449 preamplifier, V-22 source follower, V-20 voltmeter, V-318 jitter suppression, V-342 к kaleidoseope, sonie, V-548-549 Kelvin thermometer, I-655 zero adjust. III-661 key illuminator, V-333 keyer, electronic CW "bug" keyer, V-102keying circuits, IV-243-245

APSK generator, one-chip, VI-23 automatic operation, II-15 automatic TTL Morse code, I-25 CW keyer, IV-244 CW transmitter, VI-22-23 electronic, I-20 frequency-shift keyer, IV-245 negative key line keyer, IV-244 PTT control from receiver audio, VI-28 transmit keyer interface circuits,

- VI-31 wireless RTS keyer with data, VI-136
- Kirlian device supply, VI-504

L

lamp-control circuits (see lights/lightactivated and controlled circuits) laser circuits (see also lights/lightactivated and controlled circuits; optical circuits), II-313-317, III-309-311, V-250-254, VI-280-296 ac operated He-Ne laser power supply, VI-502 dc supply, VI-295 diode sensor, IV-321

discharge current stabilizer. II-316 drivers IC-based, VI-296 op-amp, VI-295 pulsed double-heterostructure laser, VI-296 single heterostructure diode, VI-290 gun, visible red, III-310 handheld laser, V-252 high-voltage supply for He-Ne laser, VI-291 IR laser light detector, VI-293 light detector, II-314 power supply, IV-636, V-251, V-254 high-voltage, V-253 with starter circuit, V-252 pulse-width modulated laser supply, VI-505 pulsers, laser diode, I-446, III-311 receiver, IV-368 PLL IR, VI-294 sound effect generator for laser pistol, VI-292 rifle, mvisible IR pulsed, fi-291 simulated laser using LED, V-253 transmitter, VI-292 latches, V-356 12-V, solenoid driver, III-572 comparator and, III-88 latching relays, dc, optically coupled, 111-417 latching switches double touchbutton, I-138 SCR-replacing, III-593 LCD display 7-segment, V-165 contrast temperature compensator, VI-195 fixed-power supply, IV-392, IV-403 large-size, V-164 lead-acid batteries (see also batteryrelated circuits) battery chargers, III-55 life-extender and charger, IV-72 low-battery detector, III-56 leading-edge delay circuit, III-147 LED circuits 7-segment, V-166 ac-power indicator, IV-214 alternating flasher, III-198, III-200 back-biased GaAs LED light sensor, II-321 bar graph driver, II-188, VI-195 battery-charger test circuit, V-89 blinker, light-controlled, VI-301 brightness, I-250 Christmas tree light flasher, V-197 VI-225 color shifting LED display. VI-189 common-cathode display, V-167 driver, emitter/follower, IV-159 flashers, V-195, V-196, VI-226, VI-227alternating, III-198, III-200 Christmas tree lights, V-197 control circuit, IV-183 dark-activated, V-195 driver, V-194 multivibrator design, IV-182 PUT used in, II-239 ring-around, III-194 sequential, reversible-direction, IV-182 three-year, III-194 UJT used m. II-231 frequency comparator, II-110

LED circuits continued light sensor, back-biased GaAsFET. П-321 leading-zero suppressed display, V-165 matrix display, two-variable, III-171 millivoltmeter readout, IV-294 multiplexed common-cathode display ADC. III-764 output indicator for 555 circuits, VI-260panel meter, III-347 peakmeter, III-333 pulser, VI-226 receivers for lightwave communications, VI-310 ring-around flasher, III-194 RS-232C, computer circuit, III-103 simulated-laser circuit, V-253 strobe, random, VI-224 three-year flasher, III-194 transmitter for hghtwave communications, VI-309 voltmeter, IV-286 VU meter, IV-211 level, electronic, II-666, IV-329, VI-328 level controllers/detectors (see also fluid and moisture), II-174 alarm, water, I-389 audio, automatic, II-20 audio (ALC), V-60-62 cryogenic fluid, I-386 hysteresis in, I-235 level of liquid, I-107, I-235, I-387, I-388, I-389, I-390, II-174, II-244, II-246, III-205, III-206, WI-207, 1-209, III-210, IV-186, IV-190, IV-191 meter, LED bar/dot, I-251 peak, I-402 sound, I-403 three-step, I-336 visual, III-269 warning audio output, low, I-391 high-level, I-387 level shifter, negative-to-positive supply, I-394 LF or HF field strength meter, II-212 LF receiver, IV-451 lie detector, II-277, IV-206, V-255-256 light-beam communication circuits, V-257-261 receivers audio, visible-light, V-261 FM light-beam, V-259 modulated light, V-258 voice-communication, V-260 transmitters audio, visible-light, V-261 FM light-beam, V-259 modulated light, V-258 voice-communication, V-260 light-controlled circuits (see also laser circuits; optical circuits), Il-304-312, II-318-331, III-312-319, V-262-283, VI-297-312 860 W limited-range light control, I-376 alarms, V-9, V-273 dark-activated alarm, pulsed tone. V-13 high-output, pulse-tone, V-14 precision design, V-12 self-latch, tone output, V-15 with hysteresis, V-14 with latch, V-12

light-beam intruder-detection. Vñ. v-13 ambient-light cancellation circuit, 11-328 ambient-light ignoring optical sensor, III-413 audio oscillator, light-sensitive, III-315 back-biased GaAs LED sensor, II-321black light, battery-operated, V-281 battery-powered light, capacitance operated, I-131 brightness control, I-377, III-316 carport light, automatic, II-308 chaser lights, sequential activation, IV-251, IV-252 Christmas light driver, IV-254 Christmas tree lights sequencer, V-264-265 colorimeter, VI-306-307 complementary, I-372 controller, IV-252 cross lader, II-312 darkness monitor, VI-303 detectors of light, I-362, IV-369 dimmers, 1-369, II-309, IV-247, IV-249, V-266, VI-377 800 W, 11-309 CMOS touch dimmer, V-270 de lamp, 11-307 four-quadrant, IV-248-249 halogen lamps, III-300 headlight, II-57, II-63 low-cost, 1-373 phase-controlled, V-267 soft-start, 800-W, I-376, III-304 tandem, II-312 triac, I-375, II-310, III-303 dissolver, solid-state, III-304 drivers, lamp drivers, I-380 Ilip-flop independent design. IV-160 low-frequency flasher/relay, I-300 MOS lamp driver, V-269 optical coupling, III-413 neon lamps, I-379, V-270, V-459 short-circuit-proof. II-310 emergency light, I-378, I-581, II-320, III-317, III-415, IV-250 exposure meter, photo enlarger, V-438 flame monitor, III-313 Easher, dark-activated, V-195 floodlamp power, I-373 fluorescent-lamp high-voltage power supplies, IV-411, V-444, V-447, VI-500 fringe counter, VI-300 lualogen lamp protector, V-271 holiday lights sequencer, V-264-265 indicator-lamp driver, optically coupled, III-413 infrared circuits (see infrared circuits, remote control) interruption detector, 1-364 inverter, fluorescent, 8-W, III-306 key illuminator, V-333 lamp pulser, VI-227 lamp timer, VI-649 LEDs (see LED circuits) level of light, I-365, I-367, I-376, I-377, I-380, I-389, III-313, III-316 hfe-extender for hghtbulbs, III-302 light meter, VI-308, VI-350 light-bulb changer, automatic

design, IV-253 lights-on warning, IV-58, IV-62, IV-250hght-seeking robot, II-325 logarithmic light sensor, 1-366 logic circuit, I-393 machine vision illumination stabilizer, II-306 marker light, III-317 meters, light-meters, I-382, I-383, V-305 photo enlargers, V-434-435 modulator, III-302 monostable multivibrator, lightcontrolled, VI-303 monostable photocell, self-adjust trigger, II-329 mooring light, automatic, II-323 name in lights, VI-379 neon Christmas light flashers, VI-225neon light drivers, I-379, V-270, V-459, VI-198 rught lights automatic, 1-360, 11-306 telephone-controlled, III-604 night-vision illuminator, IR, VI-265 night-vision scope power supply, VI-501 on/off relay, I-366 on/off reminder automotive lights, 1-109 with ice alarm, I-106 one-shot timer. III-317 optical interruption sensor, IV-366 oscillator, light-controlled, V-279 outdoor light control, V-275 phase control, II-303, II-305 photo alarm, II-319 photocell, monostable, self-adjust trigger, II-329 photocurrent integrator, II-326 photodiode amplifier, VI-301, VI-302 photodiode log converter/ transmitter, VI-312 photodiode sensor amplifier, II-324 photoelectric controller, IV-369 photoelectric sensor, V-277 photoelectric switches, ll-321, ll-326, 111-319 phototransistor, V-279 porch light control, V-266, V-276 projector-lamp voltage regulator, II-305 power outage light, ine-operated. III-415 pulse-generation interruption, I-357 receivers, LED lightwave communications, VI-310 relays, 1-366, V-275, V-278, V-279, VI-304 remote-controller, 1-370 robot eyes, II 327 hight-seeking robot, II-325 running light sequencer, V-269 sensors, 1-367 ambient-light ignoring, III-413 back-biased GaAs LED, II-321 dc servo, VI-300 logarithmuc, 1-366 multiple-input, V-273 optical sensor-to-TTL interface, 111-314 photoelectric, V-277

sequencer, V 263, holiday lights, V-264-265 pseudorandom, III-301 running light, V 269 shimmering light, V 268 short-circuit proof lamp driver, II-210 signal conditioner, photodiode design, II-330 solar power supply, VI-311, VI-312 solid-state light sources, V-282-283 sound-controlled lights, I-609, V-552 speed controller, IV-247 starry light, 1-579 strobe light, VI-468 high-voltage power supplies, IV-413 photo strobe, V-435, V-437 random LED, VI-224 trigger, V-436 variable, 111-589-590 sun tracker, III-318, VI-299, VI-312 switches, II-320, III-314 adjustable, I-362 capacitance switch, I-132 dark activated, V-274, V-276 light-/dark activated, V-274 light-activated, self-latching, V-278 light-controlled, II-320, III-314 photoelectric, II-321, II-326. 111-319 solar triggered, III-318 zero-point triac, II-311 tachometer adapter, VI-298 traffic light controller, VI-298, VI-305 transmitter, LED lightwave communications, VI-309 telephone in-use light, II-625 three-way light control, IV-251 touch lamp, three-way, IV-247 triac circuit, V-268 triac controller, V-267, V-271 triac switch, inductive load, IV-253 turn-off circuit, SCR capacitor design, IV-254 twilight-triggered circuit, II-322 video, low-level video IF amplifier, 1-687-689 voltage regulator for projection lamp, 11-305 wake-up call light, II-324 warning lights, II-320, III-317 light-seeking robot, II-325 limit comparators/detectors, I-156, 111-106 alarm, high/low, I-151 double ended, I-156, I-230, I-233, II-105 micropower, I-155 frequency-limit detector, II-177 limiters, III-320-322, IV-255 257 audio limiter, V-335 clipper/limiter, IV-355 low-distortion, II 15 dynamic noise reduction circuit, III-321 hold-current, solenoid driver, III 573 noise, 11-395, 111-321 one-zener design, IV-257 output, Ill-322 power-consumption, III-572 transmit-time limiter/timer, IV-580

voltage limiter, adjustable, IV-256

line amplifiers, III-37 duplex, telephone, III-616 RIAA line amp/driver, VI-77 universal design, IV-39 line drivers, I-262 50-ohm transmission, II-192 600-ohm balanced, II-192 audio signal amplifiers, V-54 full rail excursions in, II-190 high-output 600-ohm, II-193 impedance-matched with 75 Ohm load, VI-197 low-distortion composite 100 mA, VI-200 line receiver, balanced, VI-552 line receiver, dual-inverter, VI-542 shield/line driver, high-speed, VI-198 stereo line driver, VI-198 synchronized, III-174 video amphfier, III-710 video line driver, VI-683 video line receiver, VI-550 line-dropout detector, II-98 line-frequency square wave generator, II-599 line receivers, VI-542, VI-552 digital data, III-534 low-cost, III-532 line-sync, noise immune 60 Hz, II-367 line-current detector/monitors, III-341 optically coupled, III-414 line-hum touch switch, III-664 line-synchronized driver circuit, III-174line-voltage announcer. ac, III-730 line-voltage monitor, III-511 line-voltage-to-multimeter adapter. V-312 linear amplifiers 1.2-kW 144-MHz, VI-20 2-30 MHz, 140W PEP amateur radio, I-555 100 W PEP 420-450 MHz push-pull, I_{-554} 160 W PEP broadband, I-556 amateur radio. 2-30 MHz 140-W, III-260audio power amplifiers, V-51 CMOS inverter, II-11 inverter, linear amp from inverter, II-11 nucropower, VI-73 rf amphfiers 6-m, 100 W, IV-480-481 903 MHz, IV-484-485 ATV, 10-to-15 W, IV-481 linear couplers ac analog, II-412 analog, II-413 dc. II-411 optocoupler. instrumentation, II-417 linear IC sıren, III-564 hnear ramp generator, II-270 hnk, fiberoptic, III-179 hquid-level detectors (see fluid and moisture detectors) lithum batteries charger for, II-67 state of charge indicator for, II-78 little dipper dip meter, II-183 load-sensing circuits, V-284-285 locator, lo-parts treasure, I-409 lock detector, VI-176-177

locks, electronic, II-194-197, IV-161-163, VI-203-205 combination, I-583, II-196 digital entry lock, IV-162, V-157 frequency-based lock, VI-204 keyless design, IV-163 lock detector, VI-176-177 three-dial combination, II-195 locomotive whistle, II-589 logarithmic amplifiers, 1-29, 1-35, II-8, V1-56 de to video, I-38 log-ratio amplifier, I-42 logarithmic converter, last, 1-169 logarithmic light sensor, 1-366 logarithmic sweep VCO, 111-738 logic/logic circuits, VI-313-316 amplifiers, logic amplifiers, II-332-335 low-power binary, to 10n gain low-frequency, II-333 low-power inverting, digitally selectable gain, II-333 low-power noninverting, digitally selectable input and gain, II-334 precision, digitally programmable input and gain, II-335 programmable amplifier, II-334 AND gate, VI-315 audible pulses, II-345 chip tester, VI-334 combinatorial logic multiplexer, VI-315 converter, TTL to MOS, 1-170 four-state, single LED indeator, II-361 isolation and zero voltage switching, II-415 level shifter, negative-to-positive supply, I-394 light-activated, 1-393 line monitor, III-108 logic control for 78xx regulator, VI-562 overvoltage protection, 1-517 power supply, 3.3-V from 5-V, VI-492probes, logic probes, 1-520, J-525, I 526, IV-430-431, IV-434, VI-522, VI-523 CMOS, I-523, I-526, III-499 digital, III-497, V-310 four-way operation, IV-432 memory-tester, installed, I-625 single-IC design, IV-433 three-in-one set: probe, signal tracer, injector, IV-429 pulse generator for logictroubleshooting, IV-436 pulser, III-520, V-489 regulator, 5-V, with electronic shutdown, VI-496 relay AND circuit, VI-316 relay OR circuit, VI-316 signals, long delay line for, 111-107 sine wave oscillator, VI-440 state change indicator, VI-314 testers audible, III-343, V-313 TTL, I-527 translators, logic-level translators, IV-242 long-duration timer, PUT, II-675 long-range object detector, III-273 loop antennas 3 5 MHz, IV-12-13

logic/logic circuits continued dual band, 80-160 m, V-32 preamp, V-38 loop oscillators, VI-385 loop transmitter, remote sensors, IIIloop-thru video amphfier, IV-616 loudness controls, II-46, II-47 amplifier, loudness amp, 11-46 balance amplifier with, II-395 loudspeakers coupling circuit, 1-78 horn as loudspeaker, IV-54 protector circuit, V-483 remote link, I-343 low-distortion input selector for audio use, II-38 low-frequency oscillators, 111-428 crystal, I-184, II-146 oscillator/flasher, II-234 Pierce oscillator, III-133 TTL oscillator, II-595 low-pass filters, I-287 active, V-178, V-181, V-188 digitally selected break frequency. II-216 fourth-order, V-184 amplifier, VI-49 Butterworth, V-180, V-181 Chebyshev, fifth-order, multifeedback, II-219 clock-tunable, monolithic, 1 mV, V-187pole-active, I-295 fast-response, fast settling, IV-168-169fast-settling, precision, II-220 precision, fast settling, 11-220 Sallen Key, VI-221 10 kHz, I-279 active, IV-177 equal component, I-292 second order, I-289 second-order, V-188 second order Sallen-Key, 1-289 unity-gain second-order, V-187 variable, V-186 voltage-controlled, VI-219 low-voltage alarm/indicator, I-224, II-493, III-769 low-voltage power disconnector, II-97 LVDT circuits, II-336-339. III-323-324 driver demodulator, II-337 signal conditioner, II-338

М

machine vision, illumination stabilizer for, II-306 magnetometer, II-341 magnets current sensor, magnetic currents, III-341 electromagnetic-field sensor, V-308 permanent-magnet detector, IV-281 preamplifiers, magnetic, I-89, I-91, III-37, III-673, IV-35, IV-36 proximity sensor, V-308 transducer, magnetic transducer, I-233mains-failure indicator, IV-216 marker generator, iii-138 marker light, III-317 mathematical circuits, III-325-327, IV 258-263, V-286-288, VI-317-326

adder circuits, III-327 binary, fast-action, IV-260-261 averaging circuit, VI-324 bridge linearizing function, VI-321 difference of squares, VI-323 divider circuits, IV-150-156 binary cham, I-258 divide-by-2-or-3 circuit, IV-154 divide-by-N 1+ GHz, IV-155 1.5+ divide-by-n, IV-156 CMOS programmable, I-257 7490-divided-by-n, IV-154 divide-by-odd number, IV-153 frequency dividers, I-258, II-251, II-254, III-213-218, III-340, III-768 1.2 GHz. III-129 10-MHz, III-126 clock input, IV-151 decade, I-259 divide-by-1.5, III-216 low-cost, III-124 low frequency, II.253 preamp, III-128 programmable, IV-152-153 staircase generator and, I-730 tachometer and, I-310 odd-number counter and, III-217 one trim, III-326 pulse, non-integer programmable. H-511, III-226 minimum/maximum selector, fourinput, V-332 multiplier circuits, IV-325, VI-325 low-frequency multiplier, IV-325 precise commutating amp, IV-262-263 voltage multipliers, IV-631-637 2,000 V low-current supply, IV-636-637 10,000 V dc supply, IV-633 corona wind generator, IV-633 doublers, III-459, IV-635 cascaded, Cockcroft-Walton, IV-635 triac-controlled, III-468 laser power supply, IV-636 negative-ion generator, highvoltage, IV-634 tripler, low-current, IV 637 multiplier/divider, VI-318, VI-322 percentage-deviation ratio computer, VI-326 polar-to-rectangular converter/pattern generator, radio direction, V 288 polynomial generator, V-287 root extractor, V-207, V-288 sm approximation, VI-323 slope integrator, programmable, IV-259 square-root circuit, VI 319, VI-320, VI-322 subtractor, III-327 MC1330/MC1352 television IF amplifier, I-688 measurement/test circuits (see also monitors, prohes), II-340, III-268 270, III-328-348, IV-210-218, IV-264-311, V-230-232, V-289-321, VI-258-260, VI-327-363 100 K megaohm dr., I-524 3-m-1 test set, III-330 555 circints, LED output indicator, VI-260 absolute-value circuit, JV-274

ac hot wire, J-581 ac-current indicator, IV-290 ac-power indicator, LED display, IV-214 ac/dc indicator, IV-214 ac outlet tester, V-318 ac power monitor, VI-351 ac wiring locator, V-317 ac-watts calculator, V-304 accelerometer, VI-345 acoustic-sound receiver, IV-311 acoustic-sound transmitter, IV-311 activity tester, crystal oscillators, V-138 alarm and, I-337 altimeter, digital, V-296 anuneter, low-current, V-307 ancmometer, hot-wire, III-342 atmosphere noise monitor, VI-370 audible logic tester, III-343 audible TTL, I-524 audio amplifier tester, VI-343 audio frequency meter, I-311, V-305, V-320, VI-335 audio millivolt, III-767, III-769 audio power, I-488 audio-rf signal tracer, 1-527 automatic contrast, I-479 antomotive electrical tester, IV-45 automotive-temperature indicator, PTC thermistor, II-56 B field measurer, IV-272 balance indicator, IV-215 balance nictor for stereo, V-583 barometer, IV-273, VI-338 battery indicators/testers, I-108, I-121, 1-122, I-124, IV-74, IV-78, IV-79beat frequency, I-336 breath alert alcohol tester, III-359 broadband ac active rectifier, IV-271 buzz box continuity checker, I-551 cable tester, III-539, V-299 calibrator (see calibrators) capacitance buffer low-input, III-498 stabilized low-input, III-502 capacitance meters, I-400, II-91-94, III-75-77, VI-340 A/D, 3.5 digit, III-76 capacitance-to-voltage, II-92 digital, II-94 capacitor testers, IV-265, IV-279, V 306, VI-358 clamp-on-current compensator, II-501 CMOS logic, I-523 continuity testers, I-550, I-551, II 342, II-533, II-534, II-535, III-345, HI-538, H-958, H-978, H-979, H-979, HI-538-540, IV-287, IV-289, IV-295, IV-296, V-293, V-317, V-319 crystal tester, I-178, I-186, II-151, V-139 current meters and monitors, I-203. II-152-157, III-338, VI-259, VI-355 ac current indicator, IV-290 current sensing in supply rails. II-153 electrometer amplifier with overload protection, II-155 Hall-effect sensors, III-255, IV-284 high-gain current sensor, IV-291 picoammeter, I-202, II-154, II-157, HI-338 guarded input, II-156

range ammeter, six-decade, II-153, II-156 curve tracer, I-397, IV-274, V-300 CW offset indicator, IV-213 deviation meter, IV-303 dial pulse, III-613 digital frequency meter, III-344 digital multimeter (DMM), iV-291, V-291 digital voltmeters (DVM), III-4 3.5-digit, I-713, III-761 3.75-digit, I-711 4.5-digit, I-717, III-760 adapter for PC, V-310 auto-calibrate circuit, I-714 automatic nulling, I-712 interface and temperature sensor, II-647 LED readout, IV-286 temperature sensor and DVM, 647 diode tester, I-401, I-402, I-406, II-343, III-402 dip meters, I-247, II-182-183 bandswitched, IV-298 basic grid, I-247, IV-298 dual gate IGFET, I-246 little dipper. II-183 varicap tuned FET, I-246 direction-of-rotation circuit, III-335 diode-curve tracer, IV-274 diode-matching circuit, IV-280 dosage rate, I-534 driver, meter-driver rf amplifier, 1-MHz. III-545 duty-cycle meter, III-329, IV-265, IV-275, IV-280 dwell meter, I-102, III-45 E, T, and R measurement/test circuits, IV-283-296 ECG amplifiers with right leg drive. VI-354 electrolytic-capacitor reforming circuit. IV-276 electromagnetic-field sensor, V-308 electrometer, IV-277 electroscope, VI-341 electrostatic detector, III-337 ELF monitor, VI-336 energy consumption monitor, V-290 expanded-scale analog meters, II-186, III-774, IV-46 FET probe, III-501 FET voltmeter, III-765, III-770 field-strength meters, II-208-212, III-182-183, JV-164-166 V-174-1761 5 150 MHz, I-275 adjustable sensitivity indicator, I 274 high-sensitivity, II-211 LF or HF, II-212 microwave, low cost, I-273 rf sniffer, ff-210 sensitive, 1-274, III-183 signal-strength meter, IV 166 transmission indicator, II-211 tuned, I-276 UHF fields, IV-165 untuned, 1-276 filter analyzer, audio filters, IV-309 flash exposure meter, 1-484, III-446 frequency comparator, VCO and input, VI-353 frequency counter, III-340, IV-300, <u> Ŵ-360</u>

frequency divider, VI-10-MHz

frequency standard, VI-341 frequency meters, 1-310, II-249-250, IV-282, IV-301 analog, V-307 audio, I-311 linear, I-310 low-cost, II-250 power, II-250 power-line, I-311 frequency shift keyer tone generator, 1-723 frequency standard, 10-MHz, VI-361 gate dip oscillator, VI-344, VI-346 Geiger counters, I-536-537, II-489, II-514, V-217-219 general purpose rf detector, II-500 go/no-go test circuits, I-401, I-157 grid-dip meters, I-247, IV-298 ground, I-580, II-345 ground-noise, battery-powered, III-500 harmonic distortion analyzer, V-291, VI-357 meter, V-312 impedance checker, V-136 in-use indicator, telephone, II-629 inductance meter, linear, V-316, VI-330, VI-358 infrared detector, low-noise, II-289 injectors. IV-429 ion detector, VI-267, VI-533 ion-sensing electroscope, VI-287 high-frequency and rf tester, IV-297-303 LC checker, III-334 LED meters, I-251, III-347 level indicators (see fluid and moisture, level) line-current monitor, III-341 light meters, I-382, 1-383, V-302, VI-308, VI-350 line-voltage-to-multimeter adapter, V-312 logic chip tester, VI-334 logic probes, I-520, I-525, I-526, IV-430-431, IV-434 CMOS, I-523, I-526, III-499 digital, III-497, V-310 four-way operation, IV-432 memory-tester, installed, I-525 single-IC design, IV-433 three-in-one test set: probe. signal tracer, injector, IV-429 logic tester, I-527, II-345, III-343, V-313 low-current measurement, III-345 low-ohms adapter, IV-290 low-voltage, III-769 magnet/magnetic detectors, III-341, IV 266, IV 281, V-308 magnetometer, II-341 mams failure indicator, IV-216 measuring gauge, linear variable differential transformer, I-404 meter tester, IV-270 metronomes, I-411-413, II-353-355, III 353 354, IV 312-314, V-392 microammeter, dc, four-range, IV-292 microfarad counter, IV-275 microvolt, II 499 millivoltmeters, III 767, III 769, IV-289, IV-294, IV-295 ac, 1-716

audio, III-767, III-769

dc. IV-295 four-range, IV-289 high-input impedance, I-715 LED readout, IV-294 minute marker, VI-337 model car derby winner indicator, VI-259 modulation monitor, III 375, IV-299 mono audio-level meter, IV-310 motion sensor, unidirectional, II 346 motor hour, III-340 motorcycle tune-up aid, VI-359 multiconductor-cable tester, IV-288 multimeters, IV-291, IV-293 nanoammeter, VI-349 negative voltage reference, VI-331 noise generator, IV-308 ohumeters, I-549, III-540, IV-290 On indicator, IV-217 on-the-air, III-270 op-amp de offset shift tester, V-319 optical light probe, IV-369 oscilloscope adapter, four-trace, IV-267overspeed, I-108 overvoltage protection, I-150, I-517, II-96, II-107, II-496, III-513, III-762, IV-389 paper sheet discriminator, copying machines, III-339 peak detectors, II-174, II-175, II-434-436, III-771, IV-138, IV-143 analog, with digital hold, III-153 decibel peak meter, III-348 digital. III-160 high-bandwidth. III-161 high-frequency peak, II-175 high-speed peak, I-232 LED design, peak meter, III-333 level detector, I-402 low-drift, III-156 negative, I-225, I-234 op amp, IV-145 positive, 1-225, I-235, II-435, III-169 true rms, I-228 ultra-low-drift peak, I-227 voltage, precision, I-226 wide-bandwidth, III-162 wide-range, III-152 pH tester, I-399, 111-501 phase detection/manipulation circuits detectors, I-406, I-476, II 344, II-439, II-441, II-442, III-440-442. IV-127 10-bit accuracy, II-176 digital VOM, IV-277 phase-difference detector, 0 to 180-degree, II-344 phase selector/sync rectifier/balanced modulator, **Ⅲ-441** sequencers, phase sequence, I-476, II-437-442, III-441 re circuit, phase sequence reversal detection, II-438 reversal, re circuit to detect, II-438 three-phase tester, II-440 shifters, phase shifters, IV-647 0-180 degrees, I-477 0-360 degrees, I-477 single transistor design, I-476 splitter, precision, III-582

measurement/test circuits continued tracker, three-phase square wave generator, II-598 picoammeters, I-202, II-154, III-338 circuit for, II-157 guarded input circuit, II-156 HIN diode tester, VI-353 polarity indicator, V-231 power gain meter, 60 MHz, I-489 power line frequency tester, I-311 power meter, I-489, VI-333 power supply test load, constantcurrent, IV-424 power supply, 10-MHz frequency standard, VI-335 power transformer tester, VI-354 prescaler, 650 MHz amplifying, II-502 prossure gauge, digital, V-314 probes, 4-to-220 V, III-499 process controller, VI-4- to 20-mA, VI-355 proximity sensor, magnetic, V-308 pulse-width meter, III-336 QRP SWR bridge, III-336 radon detectors, VI-531-533 RC decade box, V-294-295 receiver-signal alarm, III-270 receiver signal-strength indicator, VI-260 reference circuit, VI-339 reflectometer, I-16 remote-control infrared device, IV-228 remote meters, VI-347 resistance measurement, II-342, IV 285, VI-335 resistor simulator, 100-W, VI-352 resistors, programmable, VI-363 resistance/continuity meters (see continuity tester, above) rf bridge, V-303 rf output indicator, IV-299 rf power indicator, I-16, III-332, VI-348 rf probe, I-523, III-498, III-502, IV-433 rf test oscillator, V-412 rf voltmeter, III-766 rf-actuated relay, III-270 S meter for communications receivers, V-311 scale, electronic, V-297 SCR tester, III-344 short-tester, V-313, V-315 shutter, I-485 signal generators, V-309 AM broadcast-band, IV-302 AM/IF, 455 kHz, IV-301 signal strength meter, III-342, IV-166 signal tracer, IV-429, V-309 signal tracking signal generator, VI-356 simulated, I-417 single injector-tracer, II-500 soil moisture, III-208 sound-level meters, III-346, IV-305, IV-307 telephone, Ill-614 sound sensor, IV-218 sound subcarrier generator, VI-358 sound-test circuits (see also sound generators), IV-304 speedometer, bike, IV-271, IV-282 static detector, IV-276 stereo test circuits

audio-level meter, IV-310 audio-power meter, III-331, IV-306balance indicator, I-618-619 reception indicator. III-269 stud finder, III-339 strain-gauge sensor, VI-336 supply-voltage monitor, V-320 suppressed zero, I-716 SWR power, I-16, I-22, IV-269 tachometers, I-94, I-100, I-102, II 175, III-335, III-340, III-347, V-65, V-596-598 analog readout, IV-280 calibrated, III-598 closed loop feedback control, II-390 digital readout, II-61, III-45, IV-268-269, IV-278 dwell meter/tachometer, III-45 feedback control, II-378, II-390 frequency counter, I-310 low-frequency, III-596 minimum-component design, I-405motor speed controllers, R-378, 11-389 optical pick-up, III-347 set point, III-47 iclephone in-use indicator, II-629, IV-560, IV-563 line-tester, V-615 off-hook, I-633 temperature (see temperaturerelated circuits) temperature indicator, IV-570 test driver for hobby servos, VI-197 test probe, 4-220 V, III-499 tester, IV-270 thermometers, III-637-643 three-in-one set, logic probe, signal tracer, injector, IV-429 three-phase tester, II-440 tilt meter, III-644-646, V-302 tone, digital IC testing, II-504 transistor tester, I-401, IV-281, V-306 transistor-matching circuit, VI-339 transmitter-output indicator, IV-218 tri-color indicator, V-232 TTL logic tester, I-527 universal test probe, IV-431 UHF source dipper, IV-299 undervoltage, battery operated equipment, I-123 universal test probe, IV-431 VCR head amplifier tester, VI-48 vibration meter, I-404 video-signal amplitude measurer, V-309 visual modulation, 1-430 visual level, III-269 voice level meter, VI-194 voltage level indicators, 1-335, I-337, 1-338, 1-718, III-758-772, V-301, V-315 voltage probes, V-474 voltaters, III-758 3.5 digit, I-710, I-713, III-761 4.5-digit, III-760 5-digit, III-760 ac, I-716, III-765, III-772 add-on thermometer for, III-640 bar-graph, 1-99, 11-54 dc, III-762, III-763, V-301

digital voltmeters (DVM), III-4 3 5-digit, common anode display, I-713 3.5-digit, full-scale, four-decade, III-761 3.75-digit, I-711 4.5-digit, III-760 4.5-digit, LCD display, I-717 auto-calibrate circuit, I-714 automatic nulling, I-712 interface and temperature sensor, II-647 LED readout, IV-286 temperature sensor and DVM, 647 FET, I-714, III-765, III-770 high-input resistance, III-768 JFET, V-318 LED expanded scale, V-311 millivoltmeters (see nullivoltmeters) rf, I-405, III-766 single-chip digital, VI-329 voltohmmeters (VOM) field strength, I-276 phase meter, digital readout, IV-277 volume indicator, audio amplifier, IV-212 VOR signal simulator, IV-273 VU meters, I-715, II-487, III-487, IV-211 watch tick timer, V-292 water-level measurement circuit, IV-191 waitmeter, optical isolator, VI-342 wave generator, three-phase digital, VI-343 wavemeter, tuned RF, IV-302 wideband test amplifier, IV-303 wire tracer, II-343 zener diode test set, V-321 zener diode tester, 1-400, 1-406 zero center, FM receivers, I-338 medical electronic circuits, II-347-349, III-349-352 biomedical instrumentation differential-amp, III-282 breath monitor, III-350 ECG amplifiers with right leg drive, VI-35Â EKG simulator, three-chip, III-350 heartbeat transducer, VI-387 heart rate monitor, II-348, II-349, V-342 preamplifier for, II-349 stimulator, constant-current, III-352 stimulus isolator, III-351 thermometer, implantable/ ingestible, III-641 megaphone circuit, VI-93 melody generator, single-chip design, IV-520 memo alert, V-352 memory-related circuits EEPROM pulse generator, 5V-powered, III-99 flash memory programming supply, +12 volt, VI-138 lithium backup battery replacement, VI-120 memory protector/power supply monitor, IV-425 memory-saving power supply, II-486 transceiver memory backup, VI-28 messenger circuit

Morse code, VI-406-407 single-chip, VI-373 metal detectors, II-350-352, IV-137, V-322-324 low-cost design, V-323 mcropower, 1-408 pipe detector, V-323 meters (see measurement/test circuits) methane concentration detector, lmearized output, III-250 metronomes, I-413, II-353-355, III-353-354, IV-312-314, V-392, VI-364-366 ac-line operated unijunction, H-355 accentuated beat, I-411 audible metronome, VI-365 downbeat-emphasized, III-353-354 electronic, IV-313 low-power design, IV-313 novel design, IV-314 sight and sound, I-412 simple, II-354 top octave generator, V-393 version II, II-355 visual metronome, VI-366 microammeter, dc, four-range, IV-292 microcontroller, musical organ, preprogrammed single-chip, I-600 microphone circuits AM-modulated oscillator for wireless microphones, VI-450 amplifiers, I-87, III-34 electronic balanced input, I-86 buffer amplifiers, high-Z, VI-125 electret, preamp circuit, V-21 external mic circuit for transceivers, V-351 FM wireless, III-682, III-685, III-691 high-unpedance input circuit, VI-81 mini-megaphone circuit, VI-93 mixer, II-37, V-363, V-364 parabolic dish mikes, electronic-ear amp, VI-82 preamplifiers, II-45, IV-37, IV-42 balanced mic, VI-77 dynamic mic, VI-76, VI-79 low-impedance, IV-41 low-voltage, VI-56 tone control for, II-687 transformerless, unbalanced input, I-88 transformerless, unbalanced input, I-88 underwater microphone, VI-379 wireless, I-679, IV-652-654, VI-661 microprocessors (see computer circuits) microvolt comparators dual limit, III-89 hysteresis-including, III-88 microvolt probe, II-499 microwave amplifiers, IV-315-319 5.7 GHz, IV-317 bias supply for preamp, IV-318 preamphfiers 2.3 GHz, IV-316 3.4 GHz, IV-316 bias supply, IV-318 single-stage, 10 GHz, IV-317 two-stage, 10 GHz, IV-319 microwave field strength meter, I-273 MIDI (see musical circuits) Miller oscillator, I-193 millivoltmeters, III-767, III-769, IV-289, IV-294, IV-295

ac, [716 audio, III-767. III-769 dc, IV-295 four range, IV-289 high-input impedance, I-715 LED readout, IV-294 mmu-stereo audio amplifiers, III-38 minimum/maximum selector, fourinput, V-332 mixers, III-367-370, IV-330-336, V-359-364, VI-392-393 1- MHz, I-427 audio, I-23, I-59, II-35, IV-335, V-362, V-364 CMOS, 1-57 common-source, I-427 digital mixer, IV-334 diplexer, IV-335 doubly balanced, I-427 dynamic audio mixer, IV-331 tour-channel, I-56, I-60, II-40, III-369, IV-333 tour input, I-55, IV-334 guitar mixer, low-noise, four-channel, V-360-361 HF transceiver/mixer, IV-457 hybrid, I-60 input-buffered, III-369 local oscillator, double-balanced mixer, V 415 nucrophone, II-37, V-363, V-364 mixer/oscillator for AM receivers, V-412 multiplexer, 1-427 one-transistor design, I-59 passive, 1-58 preamplifier with tone control, I-58 signal combiner, III-368 silent audio switching, 1-59 sound amplifier and, II-37 stereo mixer, pan controls, IV-332 unity-gain, four-input, IV-334 utility-design mixer, IV-336 universal stage, III-370 video, high-performance operation, IV-609 mobile equipment, 8-amp regulated power supply. II-461 model and hobby circuits, IV-337-340, VI-394-396 controller, model-train and/or slotcar, IV-338-340 railroad crossing flasher, VI-395 railroad track control signal, VI-396 rocket launcher, II-358 modems power-line, carrier-current circuit, III-82power line modem for computer control, VI-474 protector, V-479, V-482 modulated readback systems, disc/tape phase, I-89 modulation indicator/monitor, 1-430 CB, I-431 modulators, I-437, II-368-372, III-371-377, V-365-367, VI-397-403 455-kHz, V-366 +12V dc single supply, balanced, I-437 AM, I-438, II-370 balanced, III-376, III-441 digital pulse width modulation, VI-400-401 double-sideband suppressedcarner, III-377

DSB modulator, four-quadrant, VI-402FM, V-366, V-367 high-frequency, varactorless, VI-398 linear (AM) amplitude modulator. VI-402 linear pulse-width, I-437 monitor for, III-375 musical envelope generator, I-601 pulse-position, I-435, III-375 pulse-width, I-435, I-436, I-438-440 III-376, IV-326, VI-402 rf, I-436, II-369, III-372, III-374 saw oscillator, III-373 TTL oscillator for television display, II-372 TV, I-439, II-433. II-434 VHF, I-440, III-684 video, I-437, II-371, II-372, VI-399, VI-403. VI-399 moisture detector (see fluid and moisture detectors) monitors for computers (see computer circuits) monitors (see also alarms; fluid and moisture; light-controlled circuits, motor control circuits; speed controllers; temperaturerelated circuits; tone controls), V-368-372 ac power line monitor, VI-473 acid rain, III-361, V-371 baby monitor, V-370-371 battery monitors, I-106, I-222, II-74-79, III-60-67, IV-73-80 bird feeder monitor, V-371 blinking phone light, II-624 breath monitor, III-350 current, III-255, IV-284 alarm and, III-338 directional signals, auto, III-48 door-ajar, automotive circuits, III-46 duty cycle, III-329, IV-275 flames, III-313 home security system, I-6 line-current, III-341 line-voltage, III-511 logic line, III-108 modulation, III-375, IV-299 overvoltage protection, I-150, I-517, II-96, II-107, II-496, III-513, III-762. IV-389 power-supply monitors, II-491-497, III-493-495, IV-422-427 backup supply, drop-in mainactivated, IV-424 booster/buffer, boosts reference current, IV-425 circuit breaker, trip circuit, IV-423 connections monitor, ac lines, 111-510 fault monitor, single-supply, III-495 memory protector/supply monitor, IV-425 polarity-protection relay, IV-427 SCR design, IV-385 test load, constant current, IV-424 triac for ac-voltage control, IV-426 tube amplifier, high-voltage isolation, IV-426 voltage monitors (see voltage monutors)

monitors continued radon detectors, VI 531-533 room monitor, V 369 monostable multivibrators, I-465, III-229, III-230, III-235, III-237, V-386, V-387, VI-700 input lockout, I-464 light-controlled, VI-309 linear-ramp, III-237 photocell, monostable, II 329 positive-triggered, III-229 TTL, monostable operation, I-464 UJT. monostable operation, 1-463 video amplifier and comparator, Il-268 mooring light, automatic, 11-323 Morse code circuits, VI-404-409 code practice oscillator, VI-409 CW audio filter, VI-405 CW identifier, VI-408 messenger circuit, VI-406-407 MOSFETs amplifier, high-impedance biasing, V-19 audio power amplifiers, V-47 biasing, high-impedance method, V-19 buffer amplifier, V-93 drive current booster, VI-368 driver, high-side, VI-199 frequency converter, V-123 mixer/oscillator for AM receivers, V-412 power control switch, IV-386 power inverter, III-295, V-247 push-pull amplifier, VI-55 mosquito repeiling circuit, I-684 motion/proximity detectors, I-135-136, 1-344, 11-135, 11-136, 11-505-507, III-514-518, IV-341-346, V-376-377, V-484-486 acoustic Doppler motion detector, IV-343 aların for, II-506, VI-657 auto alarm, 1-9 capacitive, III-515 capacitive sensor touch switch system, VI-656 field disturbance sensor/alarm, II-507 inirared-reflection switch, IV-345 light-beam intruder-detection alarm, V-11, V-13 low-current-drain design, IV-342-343 magnetic, V-308 microwave circuit, V-377 motorcycle alarm, I-9 object detector, long-range, III-273 optical detector circuit. V-405 optical interruption sensor, IV-366 people-detector, infrared-activated, IV-225 proxinuty switch, infraredactivated. IV-345 relay-output, IV-345 room monitor, V-369 SCR alarm, III-517 solf-biased, changing field, I-135 switch. III-517 UHF, III-516, IV-344 ultrasonic motion detector, VI-668 ultrasonic proximity detector, VI 669 unidirectional, II-346 motor control circuits, IV-347-353, V-378-381, VI-410-416 400 Hz servo amplifier, II-386 ac motors, II-375 ac servo amplifier, bridge-type. III-387 bidirectional proportional control. II-374 blender control circuit, V-379 compressor protector, IV-351 dc motors direction controls, I-452 driver controls, fixed speed, III-387 reversing, II-381 servo, bipolar control input, II-385 speed-controlled reversible, III-388 fiberoptic controls, II-206 speed control, VI-411 direction controller, VI-413, VI-416 de motors, I-452 series-wound motors, J-448 shunt-wound motors, 1-456 stepper motor, IV-350 driver controls ac motors three-phase, II-383 two-phase, I-456, II 382 constant-speed, III-386 de motors fixed speed, III-387 reversing, II-381 servo, bipolar control input, II-385 speed-controlled reversible, III-388 N-phase motor, II-382 piezo drive, V-380 PWM, V-380 reversing, dc control signals, II-381 servo motor amplifier, I-452, II-384 stepper motors, III-390 half step, IV-349 quarter-step, IV-350 two-phase, II-456 fiber optic. dc, variable, II-206 hours-in-use meter, III-340 induction motor, I-454 load-dependent, universal motor, I-451 mini-drill control, IV-348 model train and/or car, I-453, I-455 phase control, hysteresis free, I-373 piezo motor drive, V-380 power brake, ac, II-451 power-factor controller, threephase, II-388 power-tool torque, I-458 PWM motor controller, III-389 PWM servo amplifier, III-379 PWM speed control, II-376 PWM speed control/energyrecovering brake, III-380 self-timing control, built-in, universal motor, I-451 servo motor amplifier. I-452, II-384 servo system, III-384 speed control (see speed controllers) start-and-run motor circuit, III-382 stepper motors, V-571-573, VI-600 602 half-step, IV-349 quarter-step, IV-350

speed and direction, IV-350 tachometers, I-94, I-100, I-102, II-175, III-335, III-340, III-347 V-65, V-596-598, VI-98, VI-298, VI-371 analog readout, IV-280 calibrated, III-598 closed loop feedback control, II-390 digital readout, II-61, III-45, IV-268-269, IV-278 dwell meter/tachometer, III-45 feedback control, II-378, II-390 frequency counter, I-310 low-frequency, III-596 minimum-component design, I-405 motor speed controllers, II-378, II-389 optical pick-up, III-347 set point, III-47 three-phase controls, II-383, II-388 time-delay motor-control, long time, VI-413 two-phase controls, I-456, II-382 motorcycles (see automotive circuits) multiburst generator, square waveform, II-88 multimeters (see also digital multimeters (DMM), IV-291, IV-293multiple-input detector, III-102 multiplexers, III-391-397, V-382-383 1-of-8 channel transmission system, III-395 analog, II-392, V-383 0/01-percent, II-392 buffered mput and output, III-396 input/output buffer for, III-11 single- to four-trace converter, II-431 capacitance, iI-200, II-416 combinatorial logic, VI-315 common-cathode LED-display ADC, III-764 de-, III-394 differential multiplexer, 1-425, 1-428. II-428 driver, high-speed line driver, I-264 eight-channel data acquisition circuit, VI-378 eight-channel mux/demux, I-426, II-115 four-channel, low-cost, III-394 frequency, III-213-218 line driver, 1-264 low output impedance, VI-605 mathematical, one trim, III-326 oscilloscopes, add-on, III-437 pulse-width, III-214 resistor, II-199 sample-and-hold, three-channel, III-396 two-level, III-392 video, 1-of-15 cascaded, III-393 wideband differential, II-428 multiplier circuits, IV-325 capacitance multiplier, V-205, V-347 low-frequency multiplier, IV-325 photomultipliers, high-volt power supply, V-444, V-445 precise commutating amp, IV-262-263resistance multiplication circuit, op amp, VI-431

voltage multipliers, IV-631-637 2,000 V low-current supply, IV-636-637 10,000 V dc supply, IV-633 corona wind generator, IV-633 doublers, III-459, IV-635 cascaded, Cockcroft-Walton, IV-635 triac-controlled, III-468 laser power supply, IV-636 negative-ion generator, highvoltage, IV-634 tripler, low-current, IV-637 multivibrators, V-384-388, VI-417-419 100 kHz free running, II-485 astable multivibrators, II-269, II-510, II-597, III-196, III-224, III-233, III-237, III-238, V-386-388, VI-418-419 bistable multivibrators, I-133, II-465, VI-418 inverter, III-103 debouncer, IV-108 flasher, 1-299, 11-234 lamp driver, IV-160 pushbutton trigger, V-388 RS flip-flop, I-395 SCR, II-367 SR flip-flop, IV-651 touch-triggered, I-133 car battery, II-106 CB modulation. II-431 CMOS, V-385 current, II-203 duty-cycle, 50-percent, III-584 free-running 100 kHz, I-465 programmable-frequency, III-235 with op amp, V-388 low-frequency, III-237 low-voltage, II-123 modulation, II-430 monostable multivibrators, I-465, III-229, III-230, III-235, III-237, V-386, V-387 input lockout, I-464 linear-ramp. III-237 photocell, monostable, II-329 positive-triggered, III-229 TTL, monostable operation, I-464 UIT, monostable operation, I-463 video amplifier and comparator, II-268 one-shot, I-465, I-720, II-266, II-465. III-222, III-238, III-317, III-654, V-388, VÍ-419 oscilloscope, II-474 single-supply, III-232 sound level, II-403 square-wave generators, IV-536 telephone line, II-628 very-low-frequency, V-385 wideband radiation, II-535 music circuits (see also sound generators), V-389-393 envelope generator/modulator, IV-22instrument tune-up, audio generator, V-390 melody circuit, V-393 melody generator, single-chip design, IV-520 metronome (see metronomes) MIDI receiver, V-392 MIDI transmitter, V-393 multi-tone generator, V-566

musical chimes, I-640 musical envelope, modulator, I-601, IV-22 octave equalizer, V-353 perfect pitch circuit, V-391 synthesizer, V-10-note, V-561 telephone music-on-hold circuit, V-601, V-605 wireless guitar transmitter. VI-661 mux/demux (see multiplexers) N N-phase motor drive, III-382 NAB preamps record, Ill-673 two-pole, III-673 NAB tape playback pre-amp, III-38 nanoammeter, I-202, VI-349 NE602 de power circuit, V-358 input/output circuits, V-355 negative-ion generator, IV-634 neon flashers, I-303 Christmas light flashers, VI-225 five-lamp, III-198 two-state oscillator, III-200 tube, I-304 networks crossover networks, I-172-173, II-35 5V, I-518 ac/dc lines, electronic, I-515 active, I-172 asymmetrical third order Butterworth, I-173 electronic circuit for, II-36 filter, I-291 speech, telephone, II-633 ni-cad batteries, I-118 analyzer for, III-64 charger, I-112, I-116, III-57 12 v, 200 mA per hour, I-114 current and voltage limiting, I-114 last-acting, 1-118 portable, IV-69 temperature-sensing, IV-77 thermally controlled, II 68 packs, automotive charger for, I 115 portable, III-47, IV-69 protection circuit, III-62 simph-cad, I-112 temperature-sensing charger, IV-77 test circuit, IV-79 thermally controlled, II-68 zappers, I-6, II-66, II-68 night lights (see lights/light-activated and controlled circuits) night-vision illuminator, IR, VI-265 night-vision scope power supply, VI-501no-doze alarm, V-8 noise generators (see sound generators) noise detector for ac circuits, VI-184 noise reduction circuits, II 393 396, III-398-401, IV-354-356, V-396-398, VI-420-424 amplified noise limiter for SW receivers, V-397 audio clipper/linuter, IV-355 audio dynamic system, V-397 audio shunt noise limiter, IV-355 audio squelch, II-394 balance amplifier with loudness control, II-395

music maker circuit, III-360, IV-521

blanker, IV-356 clipper, II-394 adjustable, VI-423 audio-powered, III-396 Dolby, VI-421 Dolby B. decode mode, III-401 Dolby B, encode mode, III 400 Dolby B/C, 111-399 dynanuc noise reduction, III-321 filters (see filters) limiter, II-395, 111-321, VI 423 low-level signal noise, V-398 noise generator, VI-421 noise-based voting circuit, VI-422-423 receiver application, V-398 shortwave receiver noise limiter, V-397noise monitor, VI-370 noninverting amplifiers, I-32, I-33, I-41, III-14 ac power, I-79 adjustable gain, I-91 comparator with hysteresis in, I-153 high-frequency, 28-dB, III-263 hysteresis in, I-153 low-power, digitally selectable input and gain, II-334 power, I-79 programmable-gain, III-505 single supply, I-74 split supply, I-75 nonselective frequency tripler, transistor saturation, II-252 Norton amplifier, absolute value, III-11 notch filters (see also filter circuits), 1-283, II-397-403, III-402 404 4.5 MHz, 1-282 550 Hz, II-399 1800 Hz, II-398 active band reject, II-401 adjustable Q, II-398, V-179, VI-217 audio, II-400 bandpass and, II-223 high-Q, III-404, V-178, VI-213, VI-217, VI-220 RC, VI-221 selectable bandwidth, I-281 shortwave receiver filter, V-185 three-amplifier design, 1-281 tunable, II-399, II-402, V-179 passive-bridged differentiator, II-403hum-suppressing, I-280 op amp, II-400 twin-notch for 1 kHz, V-183 twin-T, III-403 Wien bridge, II-402 NTSC gray-scale video generator, VI- $67\bar{9}$ NTSC-to-RGB converter, VI-677 NTSC-to-RGB video decoder, IV-613 nuclear particle detector, I-537 null circuit, III-69 op amp offset null, VI-427 null detector, 1-148, 111-162

0

octal D/A converter, V-350 ohmmeters, I-549 linear, III-540 linear scale, I-549 five-range, IV-290 ohms-to-volts converter, I-168 oil-pressure gauge, automotive, IV-44, IV-47 on/off control, I-665 on/off inverter, III-594 on/off touch switches. II-691, III-663 one-arm bancht game, VI-251 one-of-eight channel transmission system, III-100 one-shot function generators, I-465, V-388, VI-419 digitally controlled, I-720 precision, III-222 pulse generator, V-490-491 retriggerable, III-238 one-shot timers, III-654 light-controlled, III-317 voltage-controlled high-speed, II- $26\overline{6}$ op amps, II-404-406, III-405-406, IV-357-364, V-399-403, VI-425-431 x10, 1-37 x100, I-37 astable multivibrator, III-224 audio amplifier, IV-33, VI-427 balanced amplifier, VI-429 bandpass filter, VI-216, VI-222 bidirectional compound op amp, IV-361 bridge connections for power op amps, VI-92 clamping for, II-22 clock circuit using, III-85 comparator, three-input and gate comparator, IV-363, composite amplifier, V-401, V-403 compound op-amp, IV-364 current regulator, VI-430 dc offset-shift tester, V-319 differential amplifier, VI-186 driver, IV-158-159 feedback-stabilized amplifier, IV-360 free-running multivibrator, V-388 full-wave rectifier design, V-403 gain-controlled op amp, IV-361 high-gain/bandwidth, V-403 input guard for high-Z op amps, VI-428 intrinsically safe protected, III-12 inverter/rectifier, programmable, IV-364 laser driver, VI-295 logarithmic amplifier, VI-56 long RC time constants, VI-426 microphone mixer, V-364 mixer circuit, VI-393 offset null, VI-427 on/off switch, transistorized, IV-546 paralleled power op amps, VI-84, VI-429 polarity gain adjustment, V-400 power op amp, V-402 power booster, IV-358 power driver circuit, IV-158-159 pseudoground, VI-431 quad, simultaneous waveform generator using, II-259 resistance multiplication circuit, VI-431 sawtooth generator, VI-701 single potentiometer to adjust gain over bipolar range, II-406 single-supply applications, VI-430 swing rail-ray, LM324, IV-363 temperature-compensated breakpoint, nonlinear, V-19, V-401

transconductance op amp, with booster, VI-47 tunable notch filter with, II-400 V- and I-protected, V-25 variable gain, II-405, V-402 VCO driver, IV-362 video op amp circuits. IV-615 optical circuits (see also lasers; lights/light-activated and controlled circuits), II-407-419, IV-365-369, V-404-409 50 kHz center frequency FM transmitter, II-417 ac relay, III-418 two photon couplers, II-412 ac switcher, high voltage, III-408 ambient light-ignoring optical sensor, III-413 CMOS coupler, III-414 communication system, II-416 couplers/ontocouplers, II-409, II-417 analog coupler, linear ac, II-412 analog coupler, linear, II-413 CMOS design, III-414 de linear coupler, II-411 instrumentation, linear, II-417 optocouplers, II-409, II-417 stable, II-409 TTL design, III-416 de latching relay, III-417 digital transmission isolator, II-414 direction discriminator, V-408 high-sensitivity, NO, two-terminal zero voltage switch, II-414 indicator lamp driver, III-413 integrated solid state relay, II-408 interfaces, optocouplers/ optoisolators, V-406-407 interruption sensor, IV-366 isolation and zero voltage switching logic, II-415 isolators/optoisolators, IV-475 driver, high-voltage, III-482 telephone status monitor using, I-626 light-detector, IV 369 line-current detector, III-414 microprocessor triac array driver, II-410 optocoupler, V-407 interface circuits, V-406-407 optoisolator interface circuits, V-406-407 relay circuit, IV-475 paper tape reader, II-414 photoelectric light controller, IV-369 photoreceiver, optimized noise/ response, V-405 phototransistors amplifier, V-409 variable-sensitivity, V-409 power outage light, line-operated, III-415 probe, IV-369 proximity detector, V-405 pyrometer, 1654 receivers, 1-364, 11-418 50 kHz FM optical transmitter. II-418 light receiver, IV-367 optical or laser light, IV-367, IV-368

relays, III-412, III-417, III-418

dc solid-state, open/closed. III-412 safety-circuit switch, V-409 Schmitt trigger, 1-362 sensor, ambient light ignoring, III-413 sensor-to-TTL interface, III-314 source follower, photodiode, III-419 telephone ring detector, III-611 transmitter, I-363, I-367, IV-368 hght transmitter, IV-368 triggering SCR series, Ill-411 TTL coupler, optical, III-416 zero-voltage switching closed half-wave, 111-412 solid-state, III-410 solid-state relay, III-416 optocouplers (see optical circuits, couplers) optoisolators (see optical circuits, isolators) OR gate, I-395 relay circuit, VI-316 organ, musical, I-415 preprogrammed single chip microcontroller for, I-600 stylus, I-420 oscillators, II-420-429, III-420-432, IV-370-377, V-410-421, VI-432-459 1 kHz, II-427 1 MHz, 11-427 1.0 MHz, 1-571 2 MHz, 11-571 5-V, 111-432 50 kHz, I-727 400 MHz, 1-571 500 MHz, 1-570 800 Hz, I-68 adjustable over 10.1 range, II-423 AF power oscillator, V-412 AM-modulated oscillator for wireless microphones, VI-450 astable, I-462, V-420, VI-437, VI-438, VI-442, VI-443 audio, I-245, 11-315, 11-427. IV-374, IV-375 audio-frequency generator, V-416-417 audio-test oscillator, V-420 basic designs, V-414 beat-frequency audio generator, IV-371 beat-frequency oscillator, VI-452 buffer circuits, IV-89 Butler oscillator, VI-452 aperiodic, I-196 common base, I-191 crystal, I-182 emitter follower, II-190-191, II-194 calibration oscillator, UJT, 100-kHz, VI-157 cassette bias, II-426 Clapp oscillator, VI-458 clock generator, 1-615, III-85 CMOS, I-615, III-429, III-430 1 MHz to 4 MHz, I-199 crystal, I-187 code practice, I-15, I-20, I-22, II-428, III-431, IV-373, IV-375, IV-376, V-100-103, VI-409 Colputs crystal oscillators, I-194, I-572, II-147, V-411, VI-160, VI-458 1-to-20 MHz, IV-123 frequency checker, IV-301 harmonic, I-189-190 two-frequency, IV-127

crystal (see crystal oscillators) Darlington transistor oscillator, VI-455 double frequency output, I-314 discrete sequence, III-421 duty-cycle 50-percent, III-426 555 circuit, VI-446 variable, III-422, VI-438 emitter-coupled big loop, II-422 RC, II-266 exponential digitally controlled, I- $\frac{1}{728}$ feedback, I-67 flasher and oscillator high-drive, II-235 low-frequency, II-234 FM high frequency oscillator, VI-456 FM-modulated oscillator, VI-449 free-running, I-531 square wave, 1-615 frequency doubled output from, II-425, 11-596 frequency switcher, V-418 gate dip oscillator, VI-344, VI-346 gated, I-728, V-413, V-419 last-cycle completing, III-427 Hall effect circuits, V-222 Hartley, 1-571, V-140, VI-453, VI-459he-based, III-423 HCU/HCT-based, III 426 high-current, square-wave generator, III-585 high-frequency, III-426 crystal, I-175, II-148 LC audio oscillator, V-411 LF oscillator, V-413 light-controlled, V-279 load-switching, 100 mA, 1-730 local oscillator, double-balanced mixer, V-415 loop oscillator eliminator, VI-385 low-distortion, 1-570 low-duty-cycle pulse circuit, IV-439low-frequency oscillators, III-428 crystal, I-184, II-146 oscillator/flasher, II-234 Pierce oscillator, III-133 TTL oscillator, II-595 low-noise crystal, II-145 Miller, I-193 MOSFET mixer/oscillator for AM receivers, V-412 NE602 local oscillator, V-411 neon flasher, two-state, III-200 one-second, 1 kHz, II-423 one-shot, voltage-controlled highspeed, II-266 overtone oscillators, 1-176, I-177, I-180, I-183, I-186, II-146, III-146 50 MHz to 100 MHz, I-181 100 MHz, IV-124 crystal, I-176, I-180, II-146 crystal switching, I-183 fifth-overtone, I-182 third-overtone oscillator, IV-123 phase-locked, 20-MHz, IV-374 phase-shift oscillator, VI-435 Pierce oscillator, V-140 1-MHz, III-134 crystal, II-144 harmonic, I-199, II-192

JFET, I-198 low-frequency, III-133 quad tone oscillator, VI-434 quadrature, 1-729, III-428, VI-444 square-wave generator, III-585 quartz, III-136 R/C, I-612 reflection, crystal-controlled. III-136 Reinartz oscillator, VI-450 relaxation, IV-376 SCR, III-430 remote oscillator high-frequency VFO, VI-451 resistance-controlled digital, II-426rf oscillators, I-550-551, I-572, V-528-532, VI-448-469 6 5 MHz VFO, V-529 5 MHz VFO, II-551 ham band VFO, V-532 NE602 circuit, V-531 rf-genic, II-421 shortwave pulsed-marker, V-532 sidetone, rf-powered, I-24 signal generator, V-530-531 test oscillator, V-412 transmitter and, 27 MHz and 49 MHz, I-680 RLC, III-423 sawtooth wave, modulator. III-373 Schmitt ingger crystal, I-181 sine-wave (see sine-wave oscillators) sine-wave/square wave, tunable, I-65, III-232, IV-512 single op amp, 1-529 siren oscillator, V-567 square-wave, I-613-614, II-597, II-616. IV-532, IV-533. V-569, VI-445 0.5 Hz. I-616 1 kHz, I-612 astable multivibrator and, V-386 start-stop oscillator pulse circuit, IV-439 switch, oscillator-triggered, V-590, VI-606 switching, 20 ns, 1-729 temperature-compensated, III-137 crystal, I-187 low-power 5v-driven, II-142 temperature-stable, II-427 third overtone, I-186, IV-123 time base, crystal, III-133, IV-128 timer, 500 timer, 1-531 tone-burst, decoder and, I-726 transmitter and, 27 MHz and 49 MHz rf, I-680 triangle-wave oscillator, V-205 triangle/square wave, 1-616, II-422 TTL, I-179, I-613, IV-127, VI-437 1 MHz to 10 MHz, I-178 1 MHz to 20 MHz, IV-127 crystal, TTL-compatible, I-179 sine wave/square oscillator, IV-512 television display using, II-372 tube type crystal, 1-192 tunable frequency, 11-425 tunable single comparator, I-69 tuned collector oscillator, VI-454, VI-459 UHF oscillator, tunable, VI-456 varactor tuned 10 MHz ceramic

resonator, II-141

variable frequency oscillator, VI-438, VI-442, VI-443, VI-449, VI-451, VI-455, VI-457 variable oscillators, II-421 audio, 20 Hz to 20 kHz, II-727 four-decade, single control for, II-424 sine-wave oscillator, super lowdistortion, III-558 wide range, 1-730, II-429 variable-duty cycle, III-422, V-419 VHF crystal oscillator 20-MHz, 111-138 50-MHz, III-140 100-MHz, III-139 VLF LC oscillator, VI-454 voltage-controlled (VCO) (see voltage-controlled oscillators) warble oscillator, VI-582 wide-frequency range, II-262 wide-range, I-69, III-425 variable, I-730, II-429 Wien-bridge oscillators, I-62-63, I-66, I-70, II-566, JH-429, III-558, IV-371, IV-377, IV-511, V-415, V-419, VI-439, VI-444 CMOS chip in, II-568 low-distortion, thermally stable. III-557 low-voltage, 111-432 sine wave, 1-66, 1-70, 11-566, IV-510, IV-513 single-supply, III-558 thermally stable, III-557 three-decade, IV-510 variable, III-424 very-low-distortion, IV-513 XOR-gate, III-429 yelp, II-577 oscilloscopes, II-430-433, III-433-439, V-422-426, VI-460-464 analog multiplexer, single- to fourtrace scope converter, II-431 beam splitter, 1-474 calibrator, 11-433, 111-436 converter, I-471 CRO doubler, III-439 delayed video trigger, VI-464 differential amplifier, VI-463 eight-channel voltage display, III-435 extender, Ill-434 FET dual-trace switch for, II-432 four-trace oscilloscope adapter, IV-267 monitor, I-474 multiplexer, add-on, Ill-437 preamplifier, Ill-437, V-423 counter, III-438 instrumentation amplifiers, IV-230-231 sampling rate phase lock, VI-462 scope voltage cursor adapter, VI-461 sensitivity amphfier, III-436 spectrum analyzer adapter, V-424 timebase generator, V-425 trigger selector for timebase, V-425 triggered sweep, III-438 variable-gain amp, V-426 voltage-level dual readout, IV-108 outband descrambler, II-164 out-of-bounds pulse-width detector, III-158 outlet tester, V-318 output limiter, III-322

output-gaing circuit, photomultuplier, II-516 ontput-stage booster, III-452 output-to-current converter, VI-155 over/under temperature monitor, dual output, II-646 overload indicator, V-478 overload protector, speaker, II-16 overspeed indicator, I-108 overtone oscillators, I-176, I-177, I-180, 1-183, I-186, II-146, III-146 50 MHz to 100 MHz, I-181 100 MHz, IV-124 crystal, 1-176, I-180, II-146 crystal switching, I-183 fifth-overtone, I-182 third-overtone oscillator, IV-123 overvoltage protection, I-150, I-517, II-96, II-107, II-496, III-513, III-762, IV-389, V-480 comparator to detect, II-107 monitor for, III-762 protection circuit, II-96, II-496, III-513 undervoltage and, indicator, I-150, III-762

P

_pager, pocket-size, III-288 PAL/NTSC decoder, RGB input, III-717 palette. video, III-720 panning circuit, two-channel, I-57 paper-sheet discriminator, copying machines, III-339 paper-tape reader, II-414 parallel connections, telephone, III-611 party-line intercom, II-303 password protection circuit, PCs, V-109, VI-135 pattern generator/polar-torectangular converter for radio direction, V-288 PCB continuity tester, II-342, II-535 peak detectors, II-174, II-175, II-434-436, III-771, IV-138, IV-143 analog, with digital hold, III-153 closed-loop, V-153 decibel peak meter, III-348 digital, Îll-160 high-bandwidth, III-161 high-frequency peak, II-175 high-speed peak, I-232, VI-175 LED design, peak meter. III-333 level detector, I-402 low-drift, III-156, V-155, VI-183 negative, I-225, I-234, V-154, VI-179, VI-183 op amp, IV-145 open-loop, V-153 positive, I-225, I-235, II-435, III-169, VI-179, VI-183 true rms, I-228 ultra-low-drift peak, I-227 voltage, precision, I-226 wide-bandwidth, III-162 wide-range, III-152 peak program detector, III-771 peak converter, precision ac/dc, II-127peak/hold circuit, VI-391 people-detector, infrared-activated. IV-225 percentage-deviation ratio computer, VI-326

period counter, 100 MHz, frequency and, II-136 period-to-voltage converter, IV-115 pest-repeller, ultrasonic, III-699, III-706, III-707, IV-605-606, V-427-428 pH meters/probe, I 399, III-501, VI-523phase detection/manipulation circuits detectors, 1-406, I-476, 11-344, II-439. II-441, II-442, III-440-442, IV-127 10-bit accuracy, II-176 digital VOM, IV-277 lock detector, VI 176-177 phase-difference detector, 0- to 180-degree, II-344 phase selector/sync rectifier/ balanced modulator, III-441 sequencers, phase sequence, I-476, II-437-442, III-441 re circuit, phase sequence reversal detection, II-438 reversal, re circuit to detect, II-438 three-phase tester, II-440 slufters, phase shifters, IV-647, V-429-431 0-180 degree, 1-477 0-360 degree, I-477 eight-output, V-431 single-transistor design, 1-476 splitter. III-582, V-430 long-tail pair, V-430 phase-locked loop, V-347 infrared laser light receiver, VI-294 lock detector, VI-176-177 tracker, three-phase square wave generator, II-598 phasor gun, I-606, IV-523 phonograph-related circuits (see stereo/phonograph circuits) photo-conductive detector amplifier, four quadrant, 1-359 photo memory switch for ac power control, I-363 photo stop action, I-481 photodiode/photoelectric circuits ac power switch, III-319 alarm system, I-13, II-4 amplifiers, I-361, II-324, III-19, III-672, VI-301, VI-302 battery charger, solar, II-71, V-327 comparator, precision, I-360 controller, IV-369 current-to-voltage converter, II-128 flasher, photocell-controlled, II-232 integrator, photocurrent, II-326 level detector, precision, I-365 light controller, IV-369 log converter/transmitter, VI-312 monostable photocell, self-adjust trigger, 11-329 output-gating circuit. photomultiplier, II-516 PIN, thermally stabilized signal conditioner with, II-330 PIN-to-frequency converters, III-120preamplifier for IR photodiode, V-226sensor amplifier, II-324 smoke alarm/detectors, 1-595, 1-596 solar power supply, VI-311, VI-312 source follower, III-419 sun tracker, VI-299, VI-312

switches, II-321, II-326, III-318, III-319 photoelectric.sensor. V-277 photography-related circuits, II-443-449, III-443-449, IV-378-382, V-432-438, VI-465-468 auto-advance projector, II-444 camera alarm trigger, III-444 camera trip circuit, IV-381 charger for photoflash capacitor, VI-466 contrast meter, II-447 darkroom enlarger timer, III-445 darkroom timer, V-436 electronic flash trigger, II-448, III-449 enlarger exposure meter, V-438 enlarger light meter, V-434-435 enlarger timer, II-446 exposure meter, I-484, V-438 flash meter, III-446 flash slave driver, I-483 flash slave unit, V-433 flash triggers electronic, II-448 remote, I-484 sound-triggered, II-449 time delay, V-433 xenon flash, III-447 light meter, VI-308, VI-350 hght meter, chlargers, V-434-435 photo-event timer, IV-379 photoflash, electronic, III-449 picture fixer/inverter, III-722 shutter speed tester, II-445 slave-flash unit trigger, IV-380, IV-382, V-433, V-436 shde projector auto advance, IV-381 shde-show timer, III-444, III-448 slide stepper for projector, VI-467 sound trigger for flash unit, II-449, IV-382 strobe, V-435, V-436, V-437, VI-468 time-delay flash trigger, IV-380, V-433photomultipliers high-voltage power supply, V-444, V-445 phototransistor, V-279 amplifier, V-409 variable-sensitivity, V-409 timer, I-485 xenon flash trigger, slave, III-447 picoammeters, I-202, II-154, III-338 circuit for, II-157 guarded input circuit, II-156 picture fixer/inverter, III-722 Pierce oscillators, V-140 1-MHz, III-134 crystal, 1-195, II-144 harmonic, I-199, II-192 JFET, I-198 low-frequency, III-133 piezoelectric circuits, V-439-441, VI-469-470 alarm, I-12, V-10 buffer circuit, VI-470 drivers, V-440, VI-470 555 oscillator, V-441 CMOS, V-440 micropositioner, V-440 temperature controller, fan-based, 111-627 PIN diodes filter selection circuit, VI-213 test circuit, VI-353

PIN photodiode-to-frequency converters, III-120 pink noise generator, I-468 pipe detector, metal pipes, V-323 plant-watering accessories, I-443, II-245, II-248 playback amplifier, tape, I-77 PLL/BC receiver, II-526 pocket pager, III-288 polar-to-rectangular converter/ pattern generator, radio direction finder, V-288 polarity converter, I-166 polarity gain adjustment, op amp circuit, V-400 polarity indicator, V-231 polarity-protection relay, IV-427 polarity protector, VI-526 polarity-reversing amplifiers, lowpower, III-16 poller, analog-to-digital converters, V-28 polynomial generator, V-287 position indicator/controller, tape recorder, II-615 positive input/negative output charge pump, III-360 positive regulator, NPN/PNP boost. III-475 potentiometers, digital control, V-158 power amplifiers, II-450-459, III-450-456 2- to 6-watt audio amplifier with preamp, II-451 10 W, J-76 12 W low distortion, I-76 25 W, II-452 90 W, safe area protection. II-459 AM radio, 1-77 audio, 11-451, 111-454, IV-28-33 20-W, III-456 50-W, III-451 6-W, with preamp, III-454 booster, II-455 bridge audio, 1-81 bull horn, II-453 class-D, III-453 GaAsFET with single supply, II-10 hybrid, Ill-455 inverting, I-79 low-distortion, 12 W, J-76 low-power audio, II-454 noninverting, I-79 op amp/audio amp, high-slew rate, 1-82 output-stage booster, III-452 portable, III-452 rear speaker ambience amplifier, II 458 rf power amplifier 1296-MHz solid state, III-542 5W, II-542 600 W, I-659 switching, I-33 two-meter 10 W, 1-562 walkman amplifier, II-456 power line circuits, VI-471-475 ac power controller, VI-472-473 ac power line monitor, VI-473 low voltage power controller, VI-475 modern for computer control, VI-474 power meter, VI-333 power supplies (see also voltage indicators/meters), II-460-486, III-464, V-448-472, VI-476-498, VI-506-519

0- to 30-V supply, VI-518 0- to 5-V supply, VI-516 +1.5-V supply for ZN416E circuits, V-469 3.3-V from 5-V logic supplies, VI-492+5 V supply, V-471. VI-481, VI-491, VI-495 5-A constant-voltage supply, VI-498 ± 5 to ± 35 V tracking, V-469 0- to 12-V, V-1 A variable, V-460 9-V supply, VI-485, VI-495 10-MHz frequency standard, VI-335 12-V supply, VI-492, VI-493 12-Vdc regulated supply, VI-497 13.8-Vdc, V-2 A regulated, V-459 ±15-V supply, VI-513 20-V adjustable, V-461 5V power supply with momentary backup, II-464 5V, 0.5A power supply I-491 8- from 5-V regulator, V-469 2,000 V low-current supply, IV-636 637 AA cells, +5 V/+3 6 V, V-452 ac outlet tester, V-318 ac power controller, VI-472-473 ac power line monitor, VI-473 ac wiring locator, V-317 ac-watts calculator, V-304 adjustable current limit and output voltage, I-505 adjustable 20-V, V-461 adjustable supply, VI-517 amateur radio amplifier. 1.2-kW 144-MHz, VI-18 amplifiers, audio, dual power supply, V-165 subwooler power supply, V-464 antique radio de filament supply, V-470 are lamp, 25W, II-476 arc-jet, starting circuit. III-479 automotive-accessory power controller, V-70 automotive audio system supply, VI-103, VI-483 automotive power supply, VI-513 balance indicator. III 494 battery (see battery-related circuits) battery charger and, 14V, 4A, II-73 battery power pack, 1-509 bench top, II-472 benchtop, dual output, 1-505 bias regulator, VI-519 bipolar battery instruments, II-475 tracking double-output, V-449 booster, I-28, I-33, V-349 buck regulator, add 12-V output to 5-V, V-472 CCFL supply with variable contrast, VI-510 charge pool, III-469 configurable, V-455 connections-monitor, ac lines, III 510 consumption limiters, III-572 consumption monitor, V-290 controllers, IV-383-389, V-111-115 ac switches, IV-387, V-112, V-115 ac voltage control, V-114 automotive-accessory power, V-70 bang-bang controllers, IV-389

current-loop control, SCR design, IV-387 dual-control ac switch, V-115 high-side switches, 5 V supplies, IV-384, IV-385 monitor, SCR design, IV-385 MOSFET switch, IV-386 overvoltage protection, I-150, I-517, II-96, II-107, II-496, III-513, III-762, IV-389 power controller, universal design, IV-388 power-down circuit, V-114 pushbutton switch, IV-388 three-phase, power factor control, II-388 converter 225-W 15-V output, VI-148-149 inductorless, V-456 current limiter, V-146, V-358, V-458 current regulator, 100-mA, VI-478, VI-489 current sources, I-205, I-697, V-141-143, VI-161-163 0-to-200-nA, IV-327 bilateral, III-469, I-694-695, V-143 bipolar sources, I-695, I-697 constant, I-697, III-472 fixed power supplies, IV-405, IV-406 low-current source, IV-399 low-resistance, V-142 negative, V-143 offset-adjusting, V-145 positive, V-142 precision, I-205, I-206 regulator, variable power supply, İII-490 variable power supplies, voltageprogrammable, IV-420 voltage-controlled, grounded source/load, III 468 dc-to-dc SMPS variable 18V to 30 V out at 0 2A, II-480 de power circuit, NE602-based, V-358 de power source, VI-511 dc supply, VI-480, VI 481, VI-496_ delay circuit, V-148 differential voltage-to-current converter VI-153 disconnector, low-voltage, II-97 dual polarity, I-497 dual power supply, amplifiers, V-465 ELF monitor, VI-336 experimenter's power source. Vf 507, VI-511 failure/outage alarms/monitors, I-581-582, II-107, II-486, II-175, U 491-497, III-493-495, III-511, TV-422-427 backup supply, drop-in main-activated, IV-424 balance monitor, 111-494 booster/buffer, boosts reference current, IV-425 circuit breaker, trip circuit, IV-423 connections monitor, ac lines III-510 fault monitor, single-supply, III-495memory protector/supply monitor, IV-425 polarity-protection relay, IV-427

burst-type control, III-362

power supplies continued SCR design, IV-385 test load, constant-current, IV-424 triac for ac-voltage control, IV-426 tube amplifier, high-voltage isolation, IV-426 voltage sensor, IV-423 fixed power supplies (see fixed power supplies) flash memory programming supply, +12 volt, VI-138 flyback power supply for radon detector, VI-531 foldback current limiter, VI-477 frequency, power/frequency meter, 11-250 fuses, V-477, V-478 gain, power-gain test circuit, 60 MHz, I-489 general-purpose, III-465 glitch detector, II-107, VI-178 grid leak detector, VI-179 high-voltage (see high-voltage power supplies) IC regulator protector, VI-483 increasing zener diode power rating, II-485 inductorless converter, V-456 inverters, III-298, V-457 12 VDC-to-117 VAC at 60 Hz, III-294medium, III-296 MOSFET, III-295 isolated feedback, III-460 isolation transformer, V-349, V-470 laptop-computer supply, V-463 laser power supplies, IV-636, V-251, V-252, V-253, V-254, VI-291, VI-295 level sensor, voltage level, ill-770 logic regulator, 5-V, with electronic shutdown, VI-496 loss detector, II-175 low-ripple, I-500 low-voltage power controller, VI-475 LTC, single supply, V 454 meters, power meters, 1-489 audio, I-488 frequency and, II-250 rf. I-16 SWR, 1-16 memory save on power-down, II-486. IV-425 micropower bandgap reference, II-470 microprocessor power supply watchdog, II-494 modem, power-line, III-82 monitors, II-491-497, III-493-495, IV-422-427 backup supply, drop-in man-activated, IV-424 balance monitor, 111-494 booster/huffer, boosts reference current, IV-425 circuit breaker, trip circuit, IV-423 connections monitor, ac lines, III-510 fault monitor, single-supply, III-495 memory protector/supply monitor, IV-425 polarity-protection relay, IV-427 SCR design, IV-385

test load, constant-current, IV-424 true for ac-voltage control, IV-426 tube amplifier, high-voltage isolation, IV-426 voltage monitors (see voltage indicators/meters) multiple output, VI-506-513 multivoltage supply, V-458 NE602 power supply options, VI-484 negative supply, V-457 neon lamp driver, V-5- to 15-V supplies, V-459 noise detector for ac circuits, VI-184 notebook computer triple-output supply, VI-512 subply, Visit inter-operated, lil-415 overload indicator, V-478 overvoltage protection, I-150, I-517, II-96, II-107, II-96, III-513, III-762, IV-389, V-480 polarity protector, VI-526 power saver for computer monitors, VI-139 power-down circuit, V-114 programmable, III-467 protection circuits, I-515, I-518, II-98, II-107, II-474, II-486, II-496, II-497, III-511, IV-425, IV-427 push-pull, 400V/60W, II-473 quad power supply, VI-508 rectifiers, V-464, V-466, VI-490 reference, I-694, VI-496 regulated power supplies 8-amp, for mobile equipment operation, II-461 10 A, current and thernul protection, II-474 12-14 V, 3A, II-480 13.8-Vdc, V-2 A, V-459 +15V 1-A, III-462 -15V 1-A, III-463 spht, I-492 regulator loss cutter, V-467 regulators (see voltage regulators) reset circuit, II-366 short-circuit protection circuit, VI-526short-tester, V-313, V-315 solar power supply, VI-311, VI-312 solenoid driver, VI-202 split, I-512 stand-by, non-volatile CMOS RAMs, II-47Ž subwoofer amplifier power supply, V-464 sun tracker power supply, VI-312 supply-voltage monitor, V-320 switching power supplies, II-466, II-470, III-458, V-453, V-461, V-462, V-468, VI-479 50-W ott-line, 111-473 500 kHz switching inverter for 12V, II-474 complementary ac switch, I-379 control circuits, VI-494 power-switching circuit, II-466 regulator, VI-484 SCR, for color TV receiver, VI-487 variable, 100-kHz multiple-output, III-488 synchronous stepdown switching regulator, V-468 telecom converter -48 to +5 V at 1 A, V-472

teleprinter loop supply, VI-497 three-rail, III-466 tracking power supply, VI-485 transceiver supply for lab source, VI-517 transformer tester, VI-354 undervoltage detector/monitor, Ill-762. IV-138 uninterruptible, II-462, III-477, V-471 universal laboratory supply, V-450-451 vacuum-tube amplifier supply, VI-87 variable power supplies, III-487-492, IV-414-421, VI-514-519 VFO supply, VI-511 0- to 12-V, V-1 A, V-460 current source, voltage-programmable, IV-420 dc supplies, IV-418 dual universal supply, 0-to-50 V, 5 A, IV-416-417 switch-selected fixed-voltage supply, IV-419 switching regulator, low-power, III-490 switching, 100-kHz multiple-output, III-488 tracking preregulator, III-492 transformerless supply, IV-420 universal 3-30V, III-489 voltage regulators for variable supplies, III-490, III-492, IV-421 vocal stripper power supply, VI-373 voltage doubler, V-460 voltage probes, V-474 voltage/current regulator, V-455 voltage regulators (see voltage regulators) voltage sensor, power supplies, IV-423 voltage-level, III-770 voltage sources millivolt, zenerless, I-696 programmable, 1-694 voltage splitter, III-738 preamplifiers, I-41, V-26 AGC audio preamp, VI-2 amateur TV, mast-mounted, VI-37 antenna preamp HF broadband, V-36 loop antenna, V-38 VLF 60-kHz, V-33 wideband, V-35 6 meter, 20 dB gain and low-NF, 11-543 1000x, low-noise design, IV-37 audio preamplifiers, II-45 2-10 6-watt II-451 6-W and, III-454 audio-to-UHF preamp, V-24 balanced microphone preamp, VI-77 bias supply, IV-318 dual audio signal amplifiers, V-58 electret microphone preamp, V-21 equalized, for magnetic phono cartridges, III-671 FET phono cartridge, VI-79 frequency counter/divider, III-128, V-24 GAasFET, rf amplifiers, V-516 general purpose, I-84, IV-42 handitalkies, two-meter, I-19 HF, rf amplifiers, V-515

IF, 30 MHz, IV-460 IR photodiode preamp, V-226 impedance-matching, IV-37 instrumentation amphilier, IV-230-231 JFET, V-22 light-beam activated alarm circuit, V-13 LM382 phono, I-91 low-noise, I-88, I-561, 1V-41 magnetic, I-89, I-91, III-673, IV-35, IV-36 medical instrument, II-349 nucrophone preamplifiers, 1J-45, IV-37, IV-42, VI-56 dynamic microphones, VI-76, VI-79 low-impedance, IV-41 tone control for, II-687 transformerless, unbalanced input. I-88 transformerless, unbalanced input, I-88 microwave preamplifiers, IV-316-319 maxers, I-58 NAB preamplifiers tape playback, professional, III-38 record, III-673 two-pole, III-673 oscilloscope preamplifiers, III-437, III-438, IV-230-231, V-423 oscilloscope/counter, III-438 power amplifier with preamp, ll-451, III-454 read-head, automotive circuits, Ill-44 receiver interface, V-243 receiver preamp, VI-553 rf amplifiers, V-526, V-527 RIAA, III-38, VI-80 RIAA/NAB compensation, I-92 saw-filter impedance-matching preamp, VI-222 stereo/phonograph preamps, I-91, II-43, II-45, V-584 low-noise, IV-36 magnetic, I-91, III-37, III-673, IV-35, IV-36 tone control, V-581 tape, 1-90 thermocouple instrumentation amplifier, III-283 tone control preamplifiers, I-675 high-level. II-688 IC, 1-673, III-657 mixer, 1-58 transistor RIAA for magnetic phone cartridges, VI-76 transmit/receive sequencer, V-348 UHF-TV, III-546 ultra-low-leakage, I-38, II-7 VHF, I-560 VHF/UHF, rf amplifiers, V-515 video, V-660 preregulators high-voltage power supplies, III-480 tracking, III-492 prescalers data circuits, low-frequency, IV-132 probe, amplifying, 650 MHz, II-502 preselectors, rf amplifiers, IV-483, IV-485, IV-488 pressure gauge, V-314 printer-error alarm, computer circuits, IV-106

printers port, VI-134-135 printer-error alarm, IV-106 printer sentry, computer circuits, V-107-108 two-sheets in printer detector, IV-136probes (see also measurement/test circuits), II-498-504, III-496-503, IV-428-434, V-473-474, VI-520-524 100 K megaohm dc, 1-524 ac hot wire, I-581 audible TTL, I-524 audio-rf signal tracer, I-527 capacitance buffer low-input, III-498 stabilized low-input, III-502 clamp-on-current compensator, II- 50^{1} CMOS logic, I-523 current probe amplifier, VI-521 FET. III-501 frequency probe, 8-digit, 100-MHz, VI-524 general purpose rf detector, II-500 ground-noise, battery-powered, lif-500 logic probes, I-520, I-525, I-526, IV-430-431, IV-434, VI-522, VI-523 CMOS, I-523, I-526, III-499 chgital, III-497 four-way operation, IV-432 memory-tester, installed, I-525 single-IC design, IV-433 three-in-one test set: probe, signal tracer. injector, IV-429 microvolt, II-499 optical light probe, IV-369 pH, I-399, III-501, VI-523 prescaler, 650 MHz amplifying, II-502rf, 1-523, III-498, III-502, IV-433, VI-522 single mjector-tracer, II-500 test, 4-220V, III-499 three-in-one test set: logic probe, signal tracer, injector, IV-429 tone, digital IC testing, II-504 universal test probe, IV-431 process control interface, I-30, V-242, VI-355 processor, CW signal. I-18 product detector, I-223 programmable amplifiers, II-334, III-504-508 differential-input, programmable gain, 111-507 inverting, programmable-gain, III-505noninverting, programmable-gain, III-505 precision, digital control/programming, III-506 programmable-gain, selectable input, I-32 variable-gain, wide-range digital control, III-506 projectors (see photography-related circuits) protection circuits, II-95-99, III-509-513, V-475-483, VI 525-526 12 ns circuit breaker, II-97 automatic power down, II-98 circuit breakers ac, III-512

electronic, high-speed, II-96 compressor protector, IV-351 crowbars, electronic, II-99, III-510 ear protector, V-482 fuse, electronic, V-477 halogen lamp protector, V-271 heater protector, servo-sensed. III-624 IC regulator protector, VI-483 line protectors, computer I/O, 3 µP, IV-101 line dropout detector, II-98 line-voltage monitor, III-511 loudspeaker protector, V-483 low-voltage power disconnector. Il-97 modem protector, V-479 modem/fax protector for two computers, V-482 optical safety-circuit switch, V-409 overload indicator, V-478 overvoltage protection, I-150, I-517, II-96, II-107, II-496, III-513, III-762, IV-389, V-480 password protection for PCs, V-109 polarity protector, VI-526 polanty-protection relay for power supplies, IV-427 power-down, II-98 power-failure alarm. III-511 power-line connections monitor, ac, III-510 power supply, II-497, I-518 relay fuse, V-478 reset-protection for computers, IV-100 reverse polarity protection for battery pack, VI-30 safety circuit, V-477, V-481, V-483, V-589 short-circuit protection circuit, VI-526short-tester, V-313, V-315 shutdown circuits, V-537-538 speaker protector, V-476, V-479 proximity sensors (see motion/proximity detectors) pscudorandom sequencer, III-301, V-351 pulse circuits, IV-435-440 amplitude discriminator, III-356 coincidence detector, II-178 converters height-to-width, III-119 pulse train-to-sinusoid converters, III-122 counter, ring counter, low-power, IV-437 delay, dual-edge trigger, III-147 detectors fast pulse, V-154 missing pulse, V-152 out-of-bounds pulse width, III-158 sequence detector, II-172 divider, non-integer programmable, II-511, III-226 extractor, square-wave, III-584 generators, pulse generators, II-508-511, V-487-492, VI-699 2-ohm, III-231 300-V, III-521 555-circuit, IV-439 add-on, V-488 astable multivibrator, II-510 basic, V-488 clock, 60 Hz, II-102

pulse circuits continued CMOS short-pulse, III-523 dclayed-pulse, II-509, IV-440, V-492 divider, programmable, II-511, III-226 EEPROM, 5V-powered, III-99 free running, IV-438 interrupting pulse-generation, I 357 logic, III-520, V-489 logic troubleshooting applications, IV-436 one-shot, V-490-491 programmable, I-529 sawtooth-wave generator and, III-241, V-491 single, II-175 train, pulse train, IV-202 transistorized, IV-437 two-phase pulse, I-532 unijunction transistor design, 1-530 variable duty cycle, V-492 very low-duty-cycle, III-521 voltage-controller and, III-524 wide-ranging, III-522 missing-pulse detector, V-152 modulators pulse-position, III-375 pulse-width (PWM), III-376, IV-326, VI-400-401, VI-402 brightness controller, III-307 control, microprocessor selected, II-116 motor speed control, II-376, III-389 multiplier circuit, II-264, III-214 out-of-bounds detector, III-158 proportional-controller circuit, II-21 servo amplifier, III-379 signal generator, VI-698 speed control/energyrecovering brake, III-380 very short, measurement circuit, III-336 oscillators fast, low-duty-cycle, IV-439 start-stop, stable design, IV-438 pulse-position modulator, III-375 stretchers, IV-440 negative pulse stretcher, IV-436 positive pulse stretcher, IV-438 supply circuit, high-voltage power supplies, IV-412 width, out-of-bounds pulse width detector, III-158 pulse-dialing telephone, III-610 pulse-width-to-voltage converters, 111-117 pulse-width modulators (PWM), III 376, IV-326 brightness controller, III-307 control, microprocessor selected, if 116 motor speed control, II-376, III-389 multiplier circuit, II-264. III-214 out-of-bounds detector. III-158 proportional-controller circuit, II-21 servo amplifier, III-379 speed control/energy-recovering brake, III-380 very short, measurement circuit, 111-336 pulse/tone dialer, single-chip, III 603 pulsers, laser diode, III-311

pump circuits controller, single chip, II-247 positive input/negative output charge, I-418 push switch, on/off, electronic, II-359 push-pull amplifier, Darlington, V-22 push-pull power supply, 400V/60W, II-473 pushbutton power control switch, IV-388 PUT circuits battery chargers, III-54 long-duration timer, II-675 pyrometer, I-654, VI-640

Q

Q-multiphers

 audio, II-20
 transistorized, I-566
 QRP circuits
 ts. V-21-, V-24-MHz, V-644-645.
 CW transmitter, III-690
 sidetone generator/code practice
 oscillators, V-102
 SWR bridge, III-336
 transmitters, V-10-M DSB with
 VFO, V-638-639
 quad op amp, simultaneous waveform
 generator using, II-259
 quadrature oscillators, III-428, VI-444
 square-wave generator, III 585
 quiz master game. V-210

R

race-car motor/crash sound generator, III-578 radar detectors, II-518-520, IV 441-442, VI-527-529 one-ctup, II-519 radar guns, VI-528, VI-529 radiation detectors, II-512 517, VI-630-533 alarm, II-4 Geiger counter, VI-531 ion detector, VI-533 micropower, II-513 monitor, wideband, I-535 photomultiplier output gating circuit, II-516 pocket-sized Geiger counter, II-514 radon detector, VI-531, VI-532-533 radio/rf circuits aircraft receiver, VI-118- to 136-MHz, VI-542 AM and shortwave, ac/dc vacuumtube design, VI-536-537 AM radio broadcast trap, SW receivers, VI-214car-radio to short-wave radio converter, IV-500 demodulator, II-160 detector, 455-kllz, VI-184 power amplifier, 1-77 receivers, II-525, III-81, III-529, III-535, IV-455, V-496, V-497, V-502, VI-535, VI-547, VI-550, VI-552 AM/FM racho clock radio, 1-543 squelch circuit, ii-547, III-1 amateur radio, III-260, III-534. III-675 transceiver relay interface, V-243 VFO, V-532

voice identifier, V-550 amplifiers (see rf amplificrs) antique radio de filament power supply, V-470 antenna, remote tuned active HF, VI-62 attenuator, IV-322 automotive receiver, II-525 beat-frequency oscillator, VI-452 bridge, 50-MHz bridge circuit, V-303 broadband, II-546, III-264, IV-271 broadband antenna, miniature (3 to 30 MHz), VI-63 burst generators, portable, III-73 calibrator, V-298 carrier-current circuits, III-78-82, IV-91-93 AM receiver, III-81 audio transmitter, III-79 data receiver, IV-93 data transmitter, IV-92 FM receiver, III-80 intercom, I-146 power-line modern, III-82 receivers, I 141, I-143, I-145, I-146 relay, I-575, JV-461 remote control, I-146 transmitters, I-144 IC, I-145 on/off 200 kHz line, I-142 clock, I-542 converters, IV-494-501 ATV receiver/converter, 420 MHz, low-noise, IV-496, IV-497 HF receiver, VI-147 radio beacon converter, IV-495 receiver frequency-converter stage, IV-499 SW converter for AM car radio, IV-500 two-meter, IV-498 up-converter, TVRO subcarrier reception, IV-501 VLF converter, IV-497, V-121 WWV converter, VI-147 WWV for car radio, V-119 WWV-to-SW converter, IV-499 receiving converter, 220 MHz, IV-500 crystal radio detector, VI-182 crystal radio receiver, VI-549, VI-557 current readout, I-22 **CW-related** circuits filter, II-219, VI-405 identifier, VI-408 keying circuits, IV-244 offset indicator, IV-213 SSB/CW product detector, IV-139 SSB/CW receiver, V-499 transceiver, 5 W, 80-meter, IV-602 transmitters, III-678, III-684, III-686, III-690, IV-601, VI-664 detector, II-500, IV-433 direction finder, radio signals, IV-148-149 polar-to-rectangle converter/ pattern generator, V-288 double-sideband suppressed-carrier modulator, III-377 rf. II-366 FM radio, I-545 5 V. I-233 12 V, I-233 automobile racho diversity antenna, VI-64-65

bug, VI-662 clock radio, AM/FM, I-543 demodulators, 1-544, II-159, II-161 high frequency oscillator, VI-456 IF amplifier with quadrature detector, TV sound IF, I-690 generators, low-frequency, III-228 receivers, 1-338, 1-361, III-80, III-530, III-532, V-495 scanner noise squelch, VI-579 snooper, III-680 speakers, remote, carrier-current system, I-140 squeich circuit for AM, I-547 stereo demodulation system, I-544, 11-159 sterco transmitter, VI-662 FM/AM receiver. VI-541 transmitters, 1-361, I-367, I-681, II-417, III-687-688, IV-228 tuner, 1-231, III-529 wireless microphone, III-682, III-685, III-691 genie, If-421 input circuits, NE602, V-500 IF filter for shortwave receiver, VI-212 line sampler, VI-30 linearized RF detector, VI-177 measurement/test circuits, IV-297-303, V-412 modulators, 1-436, II-369, III-372, 111-374 Morse code circuits, VI-404-409 oscillators, 1 550-551, I-572, V-528-532, VI-448-459 5 MHz VFO, II-651 6.5 MHz VFO, V-529 ham band VFO, V-529 NE602 circuit, V-531 transmitter and, 27 MHz and 49 MHz, 1-680 rf-genie, II-421 shortwave pulsed-marker, V-532 sidctone, rf-powered, I-24 signal generator, V-530-531 output indicator, ÍV-299 NB FM audio amplifier, VI-74 power meters, I-16, I-24, III-332, III-592portable-radio 3 V fixed power supplies, IV-397 probe, I-523, III-498, III-502, VI-522 radio beacon converter, IV-495 radio-commercial zapper, V-334-335 RC receiver relay interface, VI-551 receivers, VI-551 AM radio, II-525, III-81, III-529, III-535, IV-455, V-496, V-497, V-502 automotive receiver, II-525 carrier-current, I-141, I-143, I-145. I-146 CW/SSB receiver, V-80- and 40meter, V-499 data receiver, IV-93 FM radio, I-338, I-361, III-80, III-529, III-530, III-532, V-495 old-time design. IV-453 radio-control receiver/decoder, I-574 reflex radio receiver, IV-452 regenerative receiver, VI-551, VI-554. VI-555 short-wave receiver, IV-454

signal-strength indicator, VI-260 superheterodyne, V-503 TRF radio receiver, IV-452 VLF whistler, V-496 RF power meter, VI-348 scanner silencer circuit, VI-579 scanners, VI-578-580 series/shunt PIN-diode RF switch, VI-610 shortwave transmissions converters, III-114, IV-500 FET booster, I-561 interference trap, VI-214 receiver, IV-454, VI-540, VI-543, VI-544-545, VI-546, VI-556 single-sideband (SSB) communications CW/SSB product detector, IV-139 driver, low-distortion 1 6 to 30 MHz. II-538 generators, IV-323 transmitter, crystal-controlled LO for, II-142 signal tracer probe, audio, I-527 sniffer, II-210 static detector, IV-276 superheterodyne receivers, V-503, VI-553 switch, low-cost, III-361 tuned collector oscillator, for AM broadcast band, VI-454 two-band radio receiver, VI-548 UHF scanner active antenna, VI-67 vaeuum tube amplifier, VI-72-73, VI-87 variometer-tuned radio receiver, VI-557 VHF/UHF diode switch, IV-544 VLF converter, V-121 VLF whistler receiver, V-496 voltmeter, I-405, III-766 waveguides, VI-703-704 WWV converter for car radio, V-119 WWV receiver, VI-538-539, VI-558 radio beacon converter, IV-495 radio-control circuits (see also remote control devices) audio oscillator, II-567, III-555 motor speed controller, I-576 phase sequence reversal by, II-438 oscillator, enutter-coupled, II-266 receiver/decoder, 1-574 single-SCR design, II-361 radioactivity (see radiation detectors) radon detector, VI-531, VI-532-533 rain warning beeper, II-244, IV-189 RAM, non-volatile CMOS, stand-by power supply, II-477 ramp generators, I-540, II-521-523, III-525-527, IV-443-447 555 based, V-203 accurate, III-526 integrator, initial condition reset, 111-527 linear, fl-270 variable reset level, II-267 voltage-controlled, II-523 ranging system, ultrasonic, III-697 RC decade box, V-294-295 RC receiver relay interface, VI-551 reaction timer. IV-204 read-head pre-amplifier, automotive circuits, III-44 readback system, disc/tape phase modulated, I-89

receivers, (see also transceivers; transmitters), II-524-526, III-528-535, IV-448-460, V-493-503. VI-534-558 50 kHz FM optical transmitter, I-361 acoustic-sound receiver, IV-311 AGC system for CA3028 IF amplifier, IV-458 aircraft receiver, 118- to 136-MHz, VI-542 AM and shortwave, ac/de vacuum-tube design, VI-536-537 AM radio, II-525, III-81, III-529, III-535, IV-455, V-496, V-497, V-502, VI-535, VI-547, VI-550, VI-552 mixer/oscillator for AM receivers. V-412 analog, I-545 ATV rf receiver/converter, 420 MHz, low-noise, IV-496, IV-497 audio circuit, IV-31 audio receiver, visible-light, V-261 automotive radio, II-525 automobile security system, VI-11 haby-alert, carrier-current circuit, V-96 bandswitching for receiver, VI-608 carrier current, I-141, I-143, I-145. I-146 carrier-operated relay (COR), IV-461CMOS line, I-546 crystal radio receiver, VI-549, VI-557 CW/SSB receiver, 80- and 40-meter, V-499 data receiver/message demuxer, three-wire design, IV-130 direct-conversion receiver 7-MHz receiver. VI-153 160-to-20 meters, V-494 hum reducer, V-347 NE602, V-498 fiberoptic receivers 10 MHz, II-205 50-Mb/s, III-181 data receiver, VI-207 digital, III-178 high-sensitivity, 30nW, I-270 low-cost, 100-M baud rate. III-180 low-sensitivity, 300nW, I-271 very high-sensitivity, low-speed 3nW, 1-269 FM radio, 1-338, 1-361, III-80, III-529, III-530, III-532, V-495 light-beam, V-259 FM/AM receiver, VI-541 FSK data, III-533 ham-band, III-534 hum reducer, V-347 IF amplifier/receivers, IV-459, IV-460'infrared, I-342, II-292, HI-274, IV-220-221, V-226, V-229, VI-268, VI-294 audible-output, VI-271 data-link, VI-265 FM audio reception, VI-268 headphones, V-227 single-tone, VI-270 wireless headphones, VI-269 laser, IV-368. VI-292 LED lightwave communications, VI-310

receivers continued LF receiver, IV-451 lme-type, III-532, III-534, V-497, VI-542, VI-552 MIDI receiver, V-392 modulated-light receiver, V-258 monitor for, 11-526 optical receivers, I-364, II-418, IV-367, IV-368 photoreceiver, optimized response, V 405 PLL/BC, 11-526 preamp for receiver, VI-553 preamp receiver interface, V-243 PTT control from receiver audio, VI-28 pulse-frequency modulated, IV-453 radio control, decoder and, I-574 radio (see radio/rf circuits, receivers) RC receiver relay interface, VI-551 receiver/scanner preamp with MAR-1 MMIC, V-521 regenerative receiver, IV-449, VI-551, VI-554, VI-555 remote-control, V-510, V-513 rf input circuits, NE602, V-500 RS-232 to CMOS, III-102 S meter, V-311 shortwave receiver, IV-454, V-501. VJ-540, VI-556 AM broadcast trap, VI-214 mne-band, VI-544-545 regenerative, one-tube, VI-546 toroidal core TRF, VI-543 noise limiter circuit, V-397 signal-reception alarm, III-270 signal-strength indicator, VI-260 SSB receiver, VI-80-meter, VI-29 superheterodyne receiver, IV-450-451, V-503, VI-21, VI-553 tracer, III-357 transceiver memory backup, VI-28 transceiver T/R switch, VI-610 transceiver/mixer, HF, IV-457 transmit/receive sequencer, preamp, V-348 twisted-pair video driver/receiver ctreud, VI-682 two-band radio receiver, VI-548 ultrasonic, III-698, III-705, VI-670 CW transceiver, VI-669 ultrasound, Doppler, V-651 variometer-tuned radio receiver, VI-557 VI.F whistler receiver, V-496 video line receiver, VI-550 voice-communication, light-beam, V-260 WWV receiver, VI-538-539, VI-558 zero center indicator for FM, I-338 recording devices (see tape-recorder circuits) rectangular-to-triangular waveform converter, IV-116-117 rectifiers, II-527-528, III-536-537 absolute value, ideal full wave. II-528 averaging filter, I-229 bridge rectifier, fixed power supplies, IV-398 broadband ac active, IV-271 diodeless, precision, III-537, V-466 dual voltage-rectifier, V-464 full-wave rectifiers, IV-328, IV-650 averaging filter, V-191 op amp design, V-403

absolute value, II-528 precision, 1-234, III-537 subcon-controlled (SCR), I-375 half wave, I-228, I-230, II-528, IV-325 high impedance precision, for ac/de converter, I-164 inverter/rectifier, programmable op-amp design, IV-364 low-forward-drop, III-471 precision, I-422 stheon-controlled rectifiers (SCR) annunciator, self-interrupting load, IV-9 chaser, III-197 crowbar, II-496 flashers. II-230, III-195, III-197 flip-flop, II-367 gas/smoke detector, III-251 preregulator, II-482 proximity alarm, III-517 radio control using, II-361 relaxation flasher, II-230 relaxation oscillator, III-430 ring counter, III-195 tester, III-344 time delay circuit with, II-670 truggering series, optically coupled, III-411 synchronous, phase detector-selector/balanced modulator, III-441 two phase, VI-490 reduit, electronic telephone set with. III-606 reference voltages, I-695, III-773-775. VI-339, VI-559-560 + 10V. I-696 +3V, 1-696 ±5V, 1-696 0 to 20 V power, I-694, I-699 amplifier, 1-36 bipolar output, precision, I-698 dual-output regulator, VI-564 dual tracking voltage, precision, I-698 high stability, I-696 logic control for 78xx regulator, VI-562 low-dropout, VI-566 low-noise buffered, precision, I-698 low-noise regulator, VI-565 low-power regulator, I-695 low-voltage reference, VI-560 micropower 10 V, precision, I-697 negative reference, VI-331, VI-560 positive voltage, VI-560, VI-567 power supply, buffered, VI-496 rupple reduction in switching regulator, VI-565 square wave voltage, precision, I-696 standard cell replacement. precision, I-699 step-down regulator, VI-563 surface-mount regulator, 3.3-V 1-A, VI 562 surface-mount switching regulator, 5- to 3.3-V, VI-567 switching regulator, VI-567 variable-voltage reference source, IV-327 reference clock, three phase clock from, II-101 reflection oscillator, crystalcontrolled, III-136 reflectometer, I-16

regenerative receiver, one-transistor design, IV-449 registers, shift, 1-380, II-366 driver, 1-418 regulated power supplies 8-amp, II-461 10-amp, current/thermal protection, It-474 12 to 14V at 3 A, II-480 13.8-Vdc, 2 A, V-459 +15V1 A, JII-462 -15V 1-A, III-463 spht power supplies, I-492 regulators (see voltage regulators) Remartz oscillator, VI-450 rejection filter, I-283 relaxation oscillator, III-430, IV-376 relays, 11-529-532, IV-471-475, V-504-507, VI-568-572 ac relays optically coupled, III-418 photon coupler in, II-412 solid-state latching, IV-472 AND circuit relay, VI-316 aucho operated, 1-608 hattery charger relay fuse, V-88 bidirectional switch, IV-472 capacitance, I-130 carrier-operated relays (COR), I-575, IV-481 dark activated, V-275, V-279 de latching, optically coupled, III-417 delay-off circuit, IV-473 drivers, 1-264 delay and controls closure time, 11-530 with strobe, I-266 fast turn-on/delayed off relay, VI-572fuse, V-478 high-impedance driver, VI-570 latching relay alarm circuit, VI-569 latching relay driver, VI-570, VI-571 latching relay, solid-state, V-505 light-beam operated on/off, I-366 light-sensitive, V-278, VI-304 low-frequency relay, VI-572 momentary relay, VI-569 monostable relay, low-consumption design, IV-473 optically coupled relays ac, III-418 de latching, III-417 optoisolator, IV-475 OR circuit relay, VI-316 polarity-protection for power supplies, IV-427 pulser, sensor-activated, V-507 rf-actuated, III-270 ringer, telephone, III-606 solid-state relays, 1-365, I-623, II-408, DI-412, III-416, III-569-570, IV-472, IV-474, V-505-506 sound actuated, 1-576, 1-610 telephone, I-631 thermostatic relay circuit, VI-643, VI-645 time delayed, 1-219, 1-663, V-506 tone actuated, 1-576 TR circuit, ll-532 transistor relay driver, VI-571 triac, contact protection, II-531 remote control devices (see also infrared; radio-control circuits), IV-224, V-229, V-508-513 A/B switch, IR-controlled, V-225

ac switch hookup, two-way, V-592 amplifier, 1-99 analyzer, V-224 carner, current, I-146 drop-voltage recovery for long-line systems, IV-328 extender, infrared, IV-227, V-512 fax/telephone switch, IV-552-553 infrared circuit, IV-224 IR TV remote relay, VI-263 lamp or appliance, 1-370 loudspeaker via IR link, 1-343 loop transmitter for, III-70 or/off switch, I-577 receiver, V-510, V-513 ringer, telephone, III-614 sensor, temperature transducer, I-649servo system, I-576 telephone monitor, II-626 temperature sensor, II-654 tester, infrared, IV-228, V-228, V-229 thermometer, II-659 transmitter, V-509, V-513 interface, V-511 ultrasonic, V-512 transmitter/receiver, IR, 1-342 ultrasonic tester, VI-667 video switch, IV-619-621 repeaters beeper, 1-19 European-type, tone burst generator for, III-74 fiberoptic link, 1-270 telephone, III-607 reset buttons child-proof computer reset, IV-107 power-on, II-366 protection circuit for computer, IV-100 resistance controller, digital, V-159 resistance/continuity testers, 1-550, 1-551, II-342, II-533, II-534, II-535, III-345, III-538-540, IV-287, IV-289, IV-295, IV-296 audible, V-317 audible, adjustable, II-536 buzz box, I-551 cable tester, III-539 four-wire hookup, VI-335 latching design, IV-295 low-resistance circuits, V-319 ohummeter, linear, III-540 PCB, II-342, II-535 ratiometric, I-550 RC decade box, V-294-295 resistance-ratio detector, II-342 single chip checker, II-534 visual, V-293 resistance-to-voltage converter, I-161-162 resistors multiplier, II-199 programmable, VI-363 simulator, 100-W, VI-352 voltage-controlled, I-422 resonator oscillator, varactor tuned 10 MHz ceramic, II-141 restorer, video de, III-723 reverb effect analog delay line, IV-21 stereo system, 1-602, I-606 reversing motor drive, de control signal, II-381 rf amplifiers, II-537-549, III-542-547, IV-476-493, V-514-527

1 W, 2.3 GHz, II-540 2 meter FET power amplifier. V-521 10 W, 225-400 MHz, II-548 10 W, 10-M linear amplifier, V-520 10 dB-gain, III-543 2 to 30 MHz, III-544 4 W amp for 900 MHz, IV-477 5 W 150-MHz, III-546 5 W power, II-542 6-meter kilowatt, II-545 6-meter preamp, 20 dB gain and low-NF, II-543 20-W, V-1296-MHz module, V-522 20-W, V-450 MHz amplifier, V-519 30-MHz, V-519 60 W 225-400 MHz, III-547 125 W, 150 MHz, II-544 455-kHz (F amplifier, V-522, V-523, V-524 500 MHz, IV-491 1,296 MHz, IV-486 1.500 W, IV-478-479 AGC, wideband adjustable, III-545 broadcast-band, II-546, III-264, IV-487, V-516, V-517 buffer amplifier with modulator, IV-490 cascode amplifier, IV-488 common-gate, 450-MHz, III-544 GAasFET preamplifier, V-435 MHz, V-516 HF preamphfier, V-515 HF/VHF switchable active antenna, V-524 IF amplifier, 455-kHz, V-522, V-523, V-524 IF amphfiers, 45-MHz, crystal filter, V 527 isolation amplifier, II-547 LC tuned, V-525 linear amphfiers, IV-480-485, V-520 low-distortion 1.6 to 30 MHz SSB driver, II-538 meter-driver, 1-MHz, III-545 MOSFET rf-amp stage, dual-gate, IV-489 power amplifiers, I-559, II-542, III-542, V-517, V-519, V-521, V-525 preamplifiers, V-527 GasFET, V-516 HF, V-515 receiver/scanner with MAR-1 MMIC, V-521 VHF/UHF, V-515 wideband, V-526 preselectors, IV-483, IV-485, IV-488 receiver/scanner preamp with MAR-1 MMIC, V-521 TV sound system, V-519 UHF, V-523 UHF-TV amp/preamp, III-546, IV-482, IV-483 VHF/UHF preamplifier, V-515 wideband amplifiers, IV-479, IV-489, IV-490-493, V-518, V-519, V-526rf circuits (see radio/rf) RGB video amplifier, III-709 RGB-composite video signal converter, III-714 RGB-to-NTSC converter, IV-611 RIAA line amplifier/driver, VI-77 RIAA preamp, VI-80 ring counters 20 kHz, II-135 incandescent lamps, I-301

low-cost, I-301 pulse circuit, low-power, IV-437 SCR, III-195 variable timing, II-134 ring launcher game, electromagnetic, V-209 ring-around flasher, LED, III-194 ringers, telephone, I-628, IV-556 detectors, ring detectors, I-634, I-635, III-611, III-619 extension-phone ringer, IV-561 high-isolation, II-625 multi-tone, remote programmable. 11-634 musical, II-619 piezoelectric, I-636 plug-in, remote, II-627 relay, III-606 remote, II-627, III-614. IV-562 silencer, IV-557 tone, I-627, I-628, II-630, II-631 ripple suppressor, IV-175 fixed power supplies, IV-396 RLC oscillator, III-423 rms-to-dc converter; I-167, II-129 thermal, 50-MHz, III-117 true rms detector, I-228 road ice alarm, II-57 robots eyes for, II-327 light-seeking, II-325 rocket launcher, II-358 RON compensator, op amp and analog switch, VI-605 room monitor, V-369 root extractor, V-207, V-288 rotation detector, II-283 roulette, electronic, II-276, IV-205 RS-232 interface CMOS-to, line receiver, III-102 dataselector. automatic, III-97 drive circuit, low-power, III-175 LED circuit, III-103 line-driven CMOS circuits, IV-104 RS flip-flop, I-395 **RTD** signal conditioners 5V powered linearized platinum, II-650 precision, linearized platinum, II-. 639 RTTY machines, fixed current supply, IV-400 rumble filters, III-192, III-660, IV-175 LM387 in, I-297 turntable, IV-170

S

S meter, III-342, V-311 safe area protection, power amplifier with. III-459 safety circuits (see protection circuits) safety flare, II-608 Sallen-Key filters 10 kHz. I-279 500 Hz bandpass, I-291 current driven, V-189 high pass, VI-209 low pass, VI-221 active, IV-177 equal component, I-292 second order, I-289 sample-and-hold circuits, I-590, II-552-559, III-548-553, IV-502-503, V-533-534, VI-573-574

sample-and-hold circuits continued x 1000, I-589 4-channel micropower, VI-574 charge-compensated, II-559 de-glitch circuit, V-336-337 fast and precise. II-556 filtered, III-550 frequency-to-voltage conversion, IV-194 high-accuracy, I-590 high-performance, II-557 mgh-speed, 1-587-588, 1-590, III-550 mfinite, II-558 inverting, III-552 JPET, I-586 low-drift, 1-586, VI-574 offset adjustment for, I-588 three-channel multiplexer with, III-396track-and-hold, III-549, III-552 sampling circuit hour time delay, II-668 RF line sampler/coupler, VI-30 saturated standard cell amplifier, II-296saw filter, VI-223 sawtooth waves, VI-575-577 converter, IV-114 generator, VI-577 digital design, IV-444, IV-446, V-491 linear, V-205 op amp design, VI-576, VI-701 triggered, V-304 oscillator modulator. III-373 pulse generator and, III-241 SCA (see silicon-controlled amplifiers) scale, I-398, V-297 scaler, inverse, I-422 scanner, bar codes, III-363 scanners, VI-578-580 FM scanner noise squelch, VI-579 receiver/scatter preamp with MAR-1 MMIC, V-521 shortwave converter for scanner, VI-580 stlencer circuit, VI-579 Schnutt triggers, I-593, III-153, V-356 crystal oscillator, I-181 programmable hysteresis, I-592 square-wave generators, V-569, V 570 transistorized, V-204 TTL-compatible, II-111 without hysteresis, I-592 SCR (see silicon-controlled rectifiers) scramblers, audio (see also sound generators, voice-activated circuits), IV-25-27 telephone, II-618 voice scrambler/descrambler, IV-26, IV-27 scratch filters, III-189, IV 175 LM287 m, I-297 second-audio program (SAP) adapter, III-142 security circuits (see alarms; annunciators) sense-of-slope tilt meter, II-664 sensors (see alarms; fluid and moisture; light controlled circuits; motion/proximity detectors; motor control circuits. smoke detectors, speed controllers; temperature-related circuits; tone controls)

sequence indicator, phase, I-476 sequencer, pseudorandom, III-301 sequential flashers, 1-109, II-233, II-238sequential timer, III-651 series connectors, telephone, III-609 servo amplifiers (see also motor controls), 1-452 400 Hz, II-386 hndge type ac, 1-458 dc, I-457 motor drive amplifier, II-384 servo systems (see also motor controls) controller, III-384 remote control, I-575 shaper, sine wave, II-561 shielding, shield/line driver, highspeed, VI-198 shift registers, 1-380, II-366 driver for, J-418 shifter, phase (see phase) ship siren, electronic, II-576 short-circuit proof lamp driver, II-310 short-circuit protection circuit, VI-526 short-circuit tester/sensor, V-315 computer remote data lines, IV-102 for 120-V equipment, V-313 shortwave transmissions AM broadcast trap, VI-214 AM and shortwave, ac/de vacuumtube design, VI-536-537 converters, III-114, IV-500, V-118 FET booster, 1-561 IF filter for shortwave receiver, VI-212interference trap, VI-214 noise limiter, V-397 notch filter, V-185 pulsed marker rf oscillator, V-532 receiver, IV-454, V-501, VI-540, VI-543, VI-544-545, VI-546, VI-556 scanner converted to shortwave, VI-580 shant, multimeter shunt, IV-293 shutdown circuits (see protection circuits) shutofl, automatic, battery-powered projects, III-61 shutter speed tester, II-445 sidetone oscillator, rf-powered, I-24 signal amplifiers, audio, II-41-47. IV-34-42 signal attenuator, analog. microprocessor-controlled, III-101 signal combiner, III-368 signal conditioners, IV-649 5V powered linearized platinum RTD. II-650 bridge circuit, strain gauge. II-85 linearized RTD, precision design, II-639 LVDT, II-338 thermally stabilized PIN photodiode, II-330 signal distribution amplifier, 1-39 signal generators (see function generators; sound generators: waveform generators) signal injectors, III-554 555 signal sources, crystal controlled, II-143 signal tracer, V-309 three-m-one set: logic probe, signal tracer, injector, IV-429

signal strength meters, III-342, IV-166 silent alarm, V-16 silicon-controlled amplifiers (SCA), V-535 converter, VI-151 decoder, I 214, II-166, II-170 demodulator, fl-150, III-565 MPX-SCA receiver, III-530 subcarner adapter for FM tuners, V-536 silicon-controlled rectifiers (SCR) circints annunciator, self-interrupting load, JV-9 chaser, III-197 crowbar, II-496 flashers, II 230, III-197 chaser, III 197 relaxation, II-230 ring counter, III-195 flip-flop, II-367 full-wave, I-375 gas/smoke detector, III-251 inverter and trigger, VI-283 motor speed controller, VI-414 preregulator, II-482 proximity alarm, III 517 radio control using, II-361 relaxation flasher, II-230 relaxation oscillator, ill-430 ring counter, III-195 tester, III-344 time delay circuit with, II-670 truggering series, optically coupled. ĬĨĬ-411 switching supply for color TV, VI-487 simulators EKG, three chip, III-350 inductor, II-199 VOR signals, IV-273 sine approximation circuit, VI-323 sine-to-square wave converter, IV-120, V 124, V-125, V-569, V-570 sine-wave converter, VI-150 sine-wave descrambler, II-163 sme-wave generators, IV-505, IV-506, V 542, V-543, V-544, VI-701 60 Hz, IV-507 audio, 11-564 battery powered, V-541 LC, IV-507 LF, IV-512 oscillator, audio, III-559 square-wave and, tunable oscillator. 111-232 VLF audio tone, IV-508 sinc-wave inverter, VI-285 sinc-wave oscillators, I-65, II-560-570, III-556-559. III-560, IV-504-513, V-539-544, VI-433 1-Hz, V-542 60-Hz, highly stable, V-540 555 used as RC audio oscillator, li 567adjustable, II-568 audio, II-562, II-564, III-559 generators (see sme-wave generators) LC oscillator, low-frequency, IV-509 logic gate design, VI-440 low-distortion, II-561, VI-436 one-IC audio generator, 11-569 phase-shift, audio ranging, IV-510 programmable-frequency, III-424

relaxation, modified UJT for clean audio sinusoids, II-566 shaper, sine-wave, V-543 sinc wave shaper, II-561 sine/square wave TTL oscillator, IV-512 two-tone generator, II-570 two-transistor design, IV-508 variable, super low-distortion, III-558 very-low-distortion design, IV-509 voltage-controlled oscillator, V-666 Wien-bridge, 1 66, 1-70, II-566, IV-510, IV-513, V-541 sine-wave output buffer amplifier, I-126 sinc/cosine generator, II-260, VI-700 sine/square wave converter, I-170 sine/square wave oscillators, I-65 easily tuned, 1-65 TTL design, IV-512 tunable, III-232 sinks (see current sources) single-pulse generator, II-175 single-sideband (SSB) communications CW/SSB product detector, IV-139 CW/SSB receiver, V-499 driver, low-distortion 1.6 to 30 MHz, II-538 generators, IV-323 receiver, 80-meter, VI-29 transmitter, crystal-controlled LO for, II-142 sirens (see also alarms; sound generators), I-606, II-571, III-560-568 alarm using, II-572, II-573, IV-514-517, VI-581-584 7400, II-575 adjustable-rate programmablefrequency, III-563 electronic, III-566, IV-515, IV-517. VI-583 fire siren, VI-582 generator for, II-572 hee-haw, II-578, III-565 high-power, II-578 linear IC, III-564 low-cost design, IV-516 multifunction system for, II-574 ship, electronic, II-576 sonic defender, IV-324 Star Trek red alert, II-577 tone generator, II-573 toy, II-575 T'l'L gates m, II-576 two-state, III 567 two-tone, III-562, Vi-584 varying frequency warning alarm, 11-579wailing, 111-563, VI-583 warble-tone siren, IV-515, IV-516, V-7, VI-582 whooper, IV-517 yelp oscillator, II-577, III-562 slave-flash trigger, IV-380, IV-382 slide timer, 111-444, 111-448 slot machine, electronic, V-211 smart clutch, auto air conditioner, III-46 smoke alarms and detectors, II-278, 111-246-253 gas, 1-332 ionization chamber, I-332-333 line-operated, IV-140

operated ionization type, I-596 photoelectric, I-595, I-596 sniffers heat, electronic, III-627 rf, II-210 snooper, FM, III-680 socket debugger, coprocessor, III-104 soil heater for plants, V-333 soil moisture meter, III-208 solar circuits (see photodiode/photoelectric circuits) soldering iron control, V-327 soldering station, IR-controlled, IV-225 solenoid drivers, I-265, III-571-573, VI_{-202} 12-V latch, III-572 hold-current limiter, III-573 power-consumption limiter, III-572 solid-state devices ac relay, III-570 electric fence charger, II-203 high-voltage supply, remote adjustable, III-486 light sources, V-282-283 load-sensing switch, V-285 relays, III-569-570, V-505, V-506 stepping switch, II-612 switch, line-activated, telephone, III-617 some defender, IV-324 sound-activated circuits (see soundoperated circuits) sound effects (see sound generators) sound generators (see also burst generators; function generators, sirens, waveform generators), I-605, II-585-593, III-559-568, III-575, IV-15-24, IV-518-524, V-394-395, V-556-567, VI-585-592 acoustic field generator, V-338-341 alarm-tone generator, V-563 amplifier, voltage-controlled, IV-20 amplifier/compressor, low-distortion, IV-24 allophone, III-733 audio-frequency generator, V-416-417 audio tone generator, VLF, IV-508 autodrum, II-591 bagpipes, electronic, III-561, IV-521 beat-frequency, IV-371 beeper, V-558 bird chirp, I-605, II-588, III-577, VI-589 bongos, II-587 canary simulator, V-557 chime generator, II-604, IV-524 chug-chug, III-576 color organ, VI-193 complex sound-effect generator, VI-586 dial tone, I-629. III-609 ditherizing circuit, digital audio use, IV-23 doorbell, musical tones, IV-522 doubler, audio-frequency doubler, IV-16-17 dual-tone sounder, V-564, VI-390, VI-587 echo and reverb, analog delay line, IV-24 electrome, III-360 envelope generator/modulator, II-

601

equalizer, IV-18 fader, IV-17 fish lure, electronic, VI-386 frequency-shift keyer, tonegenerator test circuit, 1-723 funk box, II-593 fuzz box, 11-590, 111-575 gong, electronic, V-563 guitar compressor, IV-519 gunshot sound effect, VI-592 harmonic generator, I-24, IV-649 high-frequency signal, III-150 hold for telephone, II-623 instrument tune-up, audio generator, V-390 laser pistol sound effect generator/receiver, VI-292 low-level sounder, V-564 muting circuit, VI-383 noise generators, 1-467, 1-468, 1-469, IV-308, V-395, VI-421 octave-shifter for musical effects, IV-523 onc-IC design, II-569 perfect pitch circuit, V-391 phasor sound generator, IV-523 pink noise, 1-468 portable, I-625 pulse echo driver, VI-380 pulsed-tone alarm, V-559 quad tone oscillator, VI-434 race-car motor/crash, III-578 robotic chatter, VI-590-591 run-down clock for games, IV-205 sound effects, III-574-578 siren, V-559, V-565, V-567 sound-effects generator, V-565 sound subcarrier generator, VI-358 space-age sound machine, V-562 spaceship alarm, V-560 speech detectors, Il-617, III-615 steam locomotive whistle, II-589, III-568steam tram/prop plane, II-592 stereo system, derived center-channel. IV-23 super, III-564 surf sound generator, VI-588 synthesizer, II-599, V-561 telephone call-tone generator, IV-562telephone ringer, II-619 tone burst generator, VI-375 tone burst generator, repeater. V-629 tone chime, V-560 tone generators, I-604, I-625 top octave generator, V-393 Touchtone dial-tone, telephone, III-609 train chuffer, II-588 tremolo circuits, III-692-695, IV -589 twang-twang, II-592 two-tone, fl-570, V-629, VI-584 ultrasonic sound source, IV-605 very-low-frequency, I-64 vocal eliminator, IV 19 voice circuits, III-729-734 waa-waa circuit, II-590 wailer, VI-583 warbling tone, il-573. VI-582 whistle, VI-589 white noise generators, IV-201, VI-705-706 wind chimes, VI-591

sound-operated circuits (see also ultrasonic circuits; voiceoperated circuits), II-580-584, III-579-580, IV-525-528, V-545-555 amplifier, gain-controlled, IV-528 color organ, II-583, II-584 decoder, III-145 fader, V-549 flash triggers, I-481, II-449, IV-382 kaleidoscope, sonic, V-548-549 lights, I-609, V-552 memo alert, V-352 noise clipper, I-396 relay, I-608, I-610 sleep-mode circuit, V-547 switch, II-581, III-580, III-600, III-601, IV-526-527, V-553, V-555, V-590, VI-613 ac, II-581 two-way, I-610 voice-operated, III-580, IV-527 speech activity detector, telephone. III-615 voice-operated switch, III-580 vox box, II-582 whistle-activated switch, V-551 sources (see current sources, voltage sources) source followers bootstrapped, V-20 JFET. V-20 photodiode, III-419 SPDT switch, ac-static, II-612 space-age sound machine, V-562 space war, I-606 spaceship alarm, V-560 speaker systems FM carrier current remote, I-140 hand-held transceiver amplifiers, III-39 overload protector for, II-16 protection circuit, V-476, V-479 wireless, IR, III-272 speakerphone, II-611, Ill-608 spectrum analyzer adapter, oscilloscopes, V-424 speech-related circuits activity detector, Il-617, III-619 compressor, II-15 filter 300 Hz-3 kHz bandpass, I-295 second-order, 300-to-3,400 Hz, IV-174 speech-range bandpass filter, V-185 two-section, 300-to-3,000 Hz, IV-174 network, II-633 scrambler, V-554 speed alarm, I-95 speed controllers (see also motor control), I-450, I-453, II-378, II-379, II-455, V-380, V-381, VI-412. VI-414 accelerometer, VI-345 back EMF PM, II-379 cassette-deck motor speed calibrator, IV-353 closed-loop, III-385 dc motor speed controller, VI-411 fans, automatic, III-382 feedback speed, I-447 dc motors, I-452, I-454, III-377, III-380, III-388, VI-415 de variable, fiberoptic, II-206

feedback, I-447 fixed, III-387 high-efficiency, III-390 high-torque motor, I-449 light-activated/controlled, IV-247 load-dependent, I-451 model trains and/or cars, 1-453, 1-455, IV-338-340 motor (see motor controls, tachometers) power tool torque, I-458 PWM, II-376, III-380, V 381 radio-controlled, I-576 series-wound motors, 1-448, 11-456 shunt-wound motors, II-456 stepper motors, direction and speed control. IV 350 switched-mode, III-384 tachometers, I-94, I-100, I-102, II-175, III-335, III-340, III-347, VI-98, VI-298, VI-371 analog readout, IV-280 calibrated, III-598 closed loop feedback control, II-390 digital readout, II-61, III-45, IV-268-269, IV-278 dwell meter/tachometer, III-45 feedback control, II-378, II-390 frequency counter, 1-310 low-frequency, III-596 minimum-component design, I-405 motor speed controllers, II-378, II-389 optacal pick-up, III-347 set point, III-47 tachometerless, III-386, IV-349 tools and appliances, I-446 universal motors, I-457, II-451 speed warning device, I-96, I-101 speedometers, bicycle, IV-271, IV-282 sphtters, 11-581-582 battery, III-66 phase, precision, III-582 precision phase, I-477 voltage, III-738, III-743 wideband, III-582 squarer, precision, I-615 square-root circuit, VI-319, VI-320, VI-322 square-wave generators, II-594-600, III-583-585, IV-529-536, V-568-570, VI-593-594 1 kHz, IV-536 2 MHz using two TTL gates, II-598 10-Hz to 10-kHz VCO, V-570 60-Hz, V-569 555 timer, II-595 astable circuit, II-597, IV-534 CMOS 555 astable, true rail-to-rail, 11-596 duty-cycle multivibrator, III-50percent, III-584 four-decade design, IV-535 high-current oscillator, III-585 line frequency, II-599 low-frequency TTL oscillator, II-595 multiburst generator, II-88 multivibrator, IV-536 oscillators, I-613-614, II-597, II-616, IV-532, IV-533, V-569 0.5 Hz, I-616 1 kHz, I-612 frequency doubled output, II-596 phase-tracking, three-phase, II-598

pulse extractor, III-584 quadrature-outputs oscillator, III-585Schnutt trigger, V-569, V-570 sine-wave and, tunable oscillator, 111-232 sine-to-square wave converter, V-569, V-570 three-phase, II-600 tone-burst generator, single timer IC, II-89 triangle-wave and, III-239 precision, III-242 programmable, III-225 wide-range, III-242 TTL, LSTTL, CMOS designs, IV-530-532 variable duty-cycle, IV-533 variable-frequency, IV-535, V-570 square wave oscillator, VI-445 astable multivibrator and, V-386 square-to-sine wave converters, III-118 squelch circuits, II-394 AM/FM, I-547 FM scanner noise squelch, VI-579 voice-activated circuits, IV-624 squib firing circuits, II-367 stabilizers, fixed power supplies, IV-393, IV-406 staircase generators,(see also function generators; waveform generators), I-730, II-601-602, III-586-588, JV-443-447, VI-595-599 free-running, VI-598 stepped triangle wave, VI-596 up-down staircase, VI-599 video staircase generator, VI-597 stand-by power supply, non-volatile CMOS RAMs, II-477 standard, precision calibration, I-406 standard-cell amplifier, saturated, II-296standing wave ratio (SWR) detector adapter, audible signal, VI-25meter, IV-269 power meter, I-16 QRP bridge, III-336 warning indicator, I-22 Star Trek red alert siren, II-577 start-and-run motor circuit, III-382 state-of-charge indicator, lithium battery, II-78 state-variable filters, II-215, III-189, VI-209 multiple outputs, III-190 sccond-order, 1 kHz, Q/10, I-293 single 3.3-V supply, 4-pole, VI-216 universal, I-290 static detector, IV-276 steam locomotive sound effects, II-589, II-592, III-568 step-up switching regulator, 6V battery, II-78 step-up/step-down dc-dc converters, **III-**118 stepper motors (see also motor control circuits), V-571-573, VI-600-602 direction control, IV-350 drivers, II-376, II-390 bipolar, V-572 FÉT-based, V-573 half-step, IV-349 quarter-step, IV-350

dual clock circuit, V-573 encoder circuit, VI-602 pulse generator, VI-601 shaft encoder use, VI-601 speed and direction, IV-350 stepping switch, solid state, II-612 stereo/phonograph (hu-fi) circuts, V-574-584 acoustic field generator, V-338-341 amplifiers, I-77, I-80-81, I-89, I-670, II-9, II-43, II-45, III-34, III-37, III-38, IV-29, IV-35, IV-36, IV-66, VI-75 bass tone control, V-584 mini-stereo amplifier, V-583 audio level meter, IV-310 aucho power amplifiers, V-40, V-48, VI-90 audio power meter, IV-306 audio signal amplifier, V-58 balance circuits, I-618-619, II-603-605, V-583 buoster amplifier for car stereo, V-72compander, II-12, III-93, III-95 expander, II-13, III-93, III-95, V-582 decoders, II-18, III-167-169, VI-170 demodulators, I-544, II-159 derived center channel stereo system. IV 23 FM bug, VI-662 FM stereo transmitter, V 575, V-580, VI-662 frequency decoder, II-169 frequency division multiplex, II-169 level display circuit, VI-190 line driver, VI-198 loudspeaker protector circuit, V-483 mixers, 1-55, IV-332 power meter, III-331 preamplifiers, 1-90, 1-91, 11-43, 11-45, III-37, III-671, III-673, IV-35, IV-36, V-581, V-584, VI-79 reception indicator, III-269 reverb systems, 1-602, 1-606, 11-9 RIAA phono amplifier, VI-89 speaker driver, TTL-based, VI-199 speaker protection circuit, V-476, V-479 TDM decoder, II-168 test circuits, I-618-619, III-269, III-331, IV-306, IV-310 tone control circuit, high-Z input, l-676 TV-stereo decoder, II-167, V-576-579, V-580 volume limiter, VI-376 stethoscope for automobiles. VI-95 stimulator, constant-current, III-352 stimulus isolator, III-351 stop light, garage, II-53 strain gauges, VI-336 bridge excitation, III-71 bridge signal conditioner, II-85 instrumentation amplifier, III-280 strobe circuits, II-606-610, VI-468 alarm system, V-6-7 disco-, II-610 high-voltage power supplies, IV-413 safety flare, II-608 tone burst generator, II-90 trip switch, sound activated, I-483 variable strobe, III-589-590 stud finder. III-339

subharmonic frequencies, crystalstabilized IC timer, II-151 subtractor circuit, III-327 subwoofer amplifier, V-49, V-50 successive-approximation A/D converter, I-45, II-24, II-30 summing amplifiers, I-37, III-16 fast action, I-36 inverting, V-18, V-20 precision design, I-36 video, clamping circuit and, III-710 sun tracker, III-318 superheterodyne receivers, VI-553 3.5-to-10 MHz, IV-450-451 amateur radio, four-stage 75-meter, VI-21 supply rails, current sensing in, II-153 suppressed-carrier, double-sideband, modulator, III-377 sweep generators (see also function generators, waveform generators), VI-238-241 10.7 MHz, I-472 add-on truggered, I-472 oscilloscope-triggered, III-438 switches and switching circuits, II-611-612, III-591-594, IV-537, V-585-593, VI-603-614 ac switches, III-408. IV-387 ac power switch, V-112, V-115 analog switches, I-621, I-622, III-593, VI-604, VI-607, VI-609, VI-614 antenna selector, electronic. IV-538-539 audio switch, eight-channel, V-588-589 audio-controlled switch, V-590, VI-613 audio/video switcher circuit, IV-540-541 auto off power switch, VI-611 auto-repeat switch, bounce-free, IV-545 bandswitching for receiver, VI-608 bidirectional relay switch, IV-472 bistable switch, mechanically controlled, IV-545 closure circuit, VI-182 contact, I-136 controller, III-383 dark-activated, V 274, V-276 dc controlled, V-586, V-592 dc static, 11-367 debouncers, 111-592, IV-105, IV-106, IV-108, V-316, VI-387, VI-613, VI-614 delay, auto courtesy light, III-42 delay circuit for switch on, VI-611 dimmer switches, 1-369, II-309, IV-247, fV-249 800 W, II-309 dc lamp, 11-307 four-quadrant, IV-248-249 halogen lamps, III-300 headlight, 11-57, 11-63 low-cost, i-373 soft-start, 800-W, 1-376, 111-304 tandem, II-312 triac, I-375, II-310, III-303 DTL-TTL controlled buffered analog, I-621 fax/telephonc switch, IV-552-553 FET. dc controlled, V-592 FET dual-trace (oscilloscope), II-432

flex switch, alarm sounder circuit. V-15 frequency switcher/oscillators, V-418 Hall-effect, HI 257, IV-539 headlight switching circuit, V-75 hexFET switch, V-592, V-593, VI-612 high frequency, I-622 high-side power control switch, 5 V supply, IV-384, IV-385 infrared-activated, IV 345 inverter, analog, VI-604 IR-controlled A/B switch, V-225 isolated switch, VI-604 kill-switch for batteries, V-71-72 latching, SCR-replacing, III-593 light-operated, II-320, III-314. V-274, V-278 adjustable, 1-362 capacitance switch, I-132 light-controlled, II-320, III-314 photoelectric, II-321, II-326. III-319 self-latching, V-278 solar triggered, III-318 zero-point triac, II-311 load-disconnect switch, V-591 load-sensing, solid-state, V-285 mercury-switch tilt detector, V-302 MOSFET power control switch, IV-386 multiplexer, low output impedance, VI-605 on/off inverter, III-594 on/off switch, 1-577, II-359, JV-543, IV-546. VI-612 optical safety-circuit switch, V-409 optically coupled, III-408, III-410 oscillator-triggered switch, V-590, VI-606 over-temperature switch, IV-571 photocell memory, ac power control, I-363 photoelectric, II-321, II-326 PIN diode switch, VI-609 proximity, III-517 push on/off. II-359 pushbutton power control switch. IV-388 remote switches, I-577, I-630. V-592resistor PIN-diode switch, VI-608 rf switches, III-361, III-592 RON compensator, op amp and analog switch, VI-605 rotary switch, BCD digital, V-160 safety switch, V-589 satellite TV audio switcher, IV-543 series/shunt PIN-diode RF switch, VI-610 shint PIN-diode switch, VI-607 solar-traggered, III-318 solid-state stepping, II-612 sonar transducer/, III-703 sound-activated, I-610, II-581, III-580, III-600, III-601, IV-526-527. V-553, V-555, V-590 speed, I-104 SPDT, ac-static, II-612 switching controller, III-383 temperature control, low-power, zero-voltage, II-640 thermostatic, for auto fan. V-68 tone switch, narrowband, IV-542 touch switches, I-131, I-135-136, II-

switches and switching circuits continued 690-693, III-661-665, IV-590-594, V-270 touchomatic. II-693 TR switch for antennas, automatic, V-37 transceiver T/R switch, VI-610 triac switches, I-623, II-311, IV-253 two-channel, I-623 two-way switch wirmg, V-591 ultrasonic, I-683 under-temperature switch, IV-570 VHF/UHF diode rf switch, IV-544 video switches, III-719, III-725, III-727, III-728, IV-618-621, V-587, VI-680 video/audio switch, V-586 voice-operated, I-608, III-580, IV 527, V-553 whistle-activated switch, V-551 wiring for two-way switch, V-591 zero crossing, I-732, VI-606 zero point, I-373, II-311 zero-voltage switching, I-623, III-410. III-412 switched-mode power supplies, II-470, III-458, VI-479 24- to 3.3-V, V-462 5- to 3.3-V, V-462 50 W. off-line, III-473 100 kHz. multiple-output, III-488 color TV receiver, SCR, VI-487 control circuits, VI-494 converter, V-461 synchronous stepdown regulator, V-468 voltage regulators for switched supplies, V-453, VI-484 3 A, III-472 5 V, 6 A, 25 kHz, separate ultrastable reference, I-497 6 A variable output, 1-513 200 kHz, I-491 application circuit, 3W, I-492 fixed power supplies, 3 A, IV-408 high-current inductorless, III-476 low-power, III-490 multiple output MPU, I-513 positive, I-498 step down. 1-493 step-up, 6V battery, II-78 converter, +50V push pull, I-494 inverter, 500 kHz, 12 V, II-474 power amplifier, I-33 switched light, capacitance, I-132 switching/mixing, silent audio, 1-59 sync circuits, V-594-595, VI-615-618 combiner, V-595 gating circuit, V-595 PLD synchronizes asynchronous inputs, VI-616 separators, III-715, IV-616 stretcher circuit, VI-618 syne tip de restorer, VI-617 synthesizers (see also musical circuits; sound generators) four-channel, I-603 frequency, programmable voltagecontrolled, II-265 music, I-599

Т

tachometers, I-94, I-100, I-102, II 175, III-335, III-340, III-347, V-65, V-596-598, VI-98, VI-298, VI 371

adapter, VI-298 analog readout, IV-280, V-597-598 calibrated. III-598 closed loop feedback control, II-390 digital readout, II-61, III-45, IV-268-269, IV-278 dwell meter/tachometer, III-45 feedback control, II-378, II-390 frequency counter, I-310 low-frequency, III-596 minimum-component design, I-405 motor speed controllers, II-378, II-380 optical pick-up, III-347 set point. III-47 signal-conditioning circuit, VI-98 tandem dimmer, II-312 tap, telephone, III-622 tape-recorder circuits, I-21, I-419, III-599-601, IV-547-548 amplifiers, I-90, IV-36 audio-powered controller, IV-548 automatic tape-recording switch, I-21, II-21 automotive-battery power circuit, IV-548 cassette-deck motor speed calibrator, IV-353 extended-play circuit, III-600 flat-response amplifier, III-673 interface for, II-614 personal message recorder, V-330-331 playback amplifier, III-672, IV-36 position indicator/controller, II-615 preamplifier, I-90 sound-activated switch, III 600, III-601 starter switch, telephone-activated, 1-632telephone-activated starter switch, I-632, II-622, III 616 telephone-to-cassette interface, Ill-618 telecom converter -48 to +5 V at 1 A, V-472 telemetry demodulator, 1-229 telephone-related circuits (see also intercoms), 11-616-635, III-602-622, IV-549-564, V-599-615, VI-619-628 alarm dialer, V-612 amphfier, 11f-621, IV-560, V-614 answering machine beeper, IV-559 auto answer and ring indicator, I-635 automatic recording device, II-622 basic telephone circuit, V-615 bell simulator, V-604 Bell System 202 data encoder, VI-625 blinking phone light monitor, II-624, 11-629 call-tone generator, IV-562 cali restrictor, VI-622 caller ID, V-613, VI-621 cassette interface. III-618 converter, ultra low-power for personal communications, VI-166 decoder, touch-tone, IV-555 dial pulse indicator, III-613 dial-tone circuit, 5-V, V-610 dialed-phone number vocalizer, III-731dialer emergency dialer, V-603 pulse/tone, single-chip. III-603

dual tone decoding, II-620 duplex audio link, IV-554 duplex line amplifier, III-616 eavesdropper, wircless, III-620 emergency dialer, V-603 fax-machine switch, remotecontrolled, IV-552-553 flashers, II-629 phone-message, IV-556 tell-a-bell, IV-558 visual ring indicator, IV-559, IV-561 frequency and volume controller, II-623 hands-free telephone, III-605 handset encoder, 1-634, III-613 helper/simulator, VI-627 hold button, II-628. III-612 hold circuit, V-614, VI-624, VI-628 in-use indicator, II-629, IV-560, IV-563, V-602 intercom, IV-557, V-239, V-240 interface audio, V-612, VI-625 FCC Part 68, V-613 for phone-line, V-605 hght for, II-625 hne interface, autopatch, I-635 line monitor, I-628 line simulator, VI-627 line tester, V-615, VI-620 message-taker, IV-563 monitors, 1-625, II-626 musical hold, II-623, V-601, V-605 musical ringer, II-619 night light, telephone controlled. III-604 off-hook indicator, I-633 optoisolator status monutor, I-626 pager, V-609, V-611 parallel connection, III-611 personal message recorder, V-330 331 piezoelectric ringer, I-636 power switch, ac, IV-550 preamp, transistor RIAA for magnetic cartridges, VI-76 pulse-dialing, III-610 recording calls, I-632, III-616, IV-553, IV-558, V-600, VI-626 redial, III-606 relay, 1-631 remote monitor for, II 626 repeater, III-607 repertory dialer, hne powered, I-633 ring amplifier, VI-624, VI-626 ring converter, V-802 ring detectors, II-623, III-611, III-619. IV 664, VI-628 ring indicator, V-604 ringers, IV 556, V-600 extension-phone ringer, IV-561 high-isolation, II-625 multi-tone, remote programmable, 11-634 musical, II-619 piezoelectric, 1-636 phig-m, remote, II-627 relay, III-606 remote, II 627, III-614, IV-562 tone, I-627, I-628, II-630, II-631 scrambler, Il-618, V-608, VI-623 series connection, III-609 silencer, IV-557 sound level meter monitor, III-614

speaker amplifier, IV-555 speakerphone, II-632, III-608 speakerphone adapter, V-606-607 speech activity detector, II-617, III-615 speech network, II-633 status monitor using optoisolator, I-626 switch, solid-state, line-activated, III-617 tap, III-622 tape-recorder starter controlled by. I-632 telecom converter -48 to +5 V at 1 A, V-472 timer, tele-timer, V-623 toll-totalizer, IV-551 tone-dialing, III-607 tone ringers, I-627, I-628, II-630, II-631 Touchtone generator, III-609 touch-tone decoder, IV-555 vocalizer. dialed-phone number, III-731 voice-mail alert, V-607 teleprinter loop supply, VI-497 television (see amateur television; video circuits) temperature-related circuits (see also thermometers), I-641-643, I-648, I-657, II-645, III-629-631, IV-565-572, V-616-620, VI-629-647 0-50 C, four-channel temperature, I-648 A/D converter for temperature measurement, VI-234-235, VI-634 absolute temperature log with RS-232, VI-636 alarms, II-4. II-643, II-644, V-9 amplifier, precision RTD. for +5 V, VI-643 automotive water-temperature gauge, II-56, IV-44, IV-48 body-heat detector, VI-266 boiler temperature control, I-638 compensation adjuster, V-617 control circuits, I-641-643, II-636-644, III-623-628, IV-567, VI-631, VI-641, VI-646 defrost cycle, IV-566 heater element, II-642 heater protector, servo-sensed, III-624 heat sniffer, electronic, III-627 liquid-level monitor, II-643 low-power, zero-voltage switch, $11-6\hat{4}0$ piezoelectric fan-based, III-627 proportional, III-626 signal conditioners, II-639 single setpoint, I-641 thermocoupled, IV-567 zero-point switching, III-624 converters logarithmic, V 127 temperature-to-digital, V-123 temperature-to-frequency, I-168, I-646, I-656, II-651-653, V-121 temperature-to-time, III-632-633 cool-down circuit for amplifiers, V-354, V-357 defrost cycle and control, IV-566 differential temperature, 1-654, 1-655, VI-645 flame temperature, III-313 freeze-up sensor, VI-647

furnace fuel miser, V-328-329 heater control, I-639, I-640, II-642, III-624, VI-632 heat sniffer, III-627 hi/lo sensor, II-650 hook sensor on 4- to 20-mA loop, V-618 IC temperature, I-649 indicator, II-56, IV-570 isolated temperature, I-651 LCD contrast temperature compensator, VI-195 logarithmic converter, V-127 low-temperature sensor, V-619 measuring circuit/sensors, II-653. IV-572 meters/monitors, I-647, III-206, IV-569op amp, temp-compensated breakpoint, V-401 oscillators, temperature-controlled, I-187, II-427, III-137 over-temperature switch, IV-571 over/under sensor, dual output, II-646 proportional temperature controller, VI-633 pyrometer, optoelectronic, VI-640 regulator, zero-voltage switching, VI-647 remote sensors, I-649, I-654, V-619 room temperature display, bar graph, VI-641 sensors. I-648, I-657, II-645-650, III-629-631, IV-568-572, V-619 -50 to 300 F, single supply, VI-638 0-50-degree C four channel, I-648 0-63 degrees C, III-631 5 V powered linearized platinum RTD signal conditioner, II-650 automotive-temperature indicator. PTC thermistor, II-56 Centigrade thermometer, II-648 coefficient resistor, positive, I-657 differential, I-654, I-655 full-range Fahrenheit, VI-643 output referenced to ground, twowire, VI-638 over/under, dual output. II-646 DVM interface, II-647 hi/lo, 11-650 integrated circuit, I-649 isolated, I-651, III-631 low-temperature, V-619 remote, I-649, I-654, V-619, VI-638 soil heater for plants, V-333 soldering iron control, V-327 thermal monitor, IV-569 thermocouple amplifier, cold junction compensation, II-649 thermocouple multiplex system, III 630 zero-crossing detector, I-733 signal conditioners, II-639 single-setpoint, temperature, I-641 temperature to digital converter, V 123, VI-646 temperature-to-frequency converter, 1-168, 1-646, 1-656, II-651-653, V-121, VI-639 temperature-to-time converters, III-632-633 thermocouples amplifier, cold junction compensation, II-649, VI-635, VI-

642. VI-644 control, IV-567 multiplex system, III-630 thermometers (see thermometers) thermostat (see thermostats) thermostatic fan switch. V-68 thermostatic relay circuit, VI-643, VI-645 transconducer, I-646, I-649 under-temperature switch, IV-570 zero-crossing detector, I-733 temperature-to-frequency converter. I-168, I-656, II-651-653, VI-639 temperature-to-frequency transeonducer, linear, I-646 temperature-to-time converters, III-632-633 ten-band graphic equalizer, active filter, II-684 Tesla coils, III-634-636 test bench amplifier, V-26 test circuits (see measurement/test circuits) text adder, composite-video signal, III-716 theremins, II-654-656 digital, II-656 electronic, II-655 thermal flowmeter, low-rate flow, III-203 thermocouples, II-649, VI-635, VI-642, VI-644 amplifiers, I-355, I-654, II-14, II-649 digital thermometer using, II-658 multiplex, temperature sensor system, III-630 pre-amp using, III-283 thermometers (see also temperaturerelated circuits), II-657-662, III-637-643, IV-573-577 0-50 degree F, I-656 0-100 degree C, I-656 1.5-V, VI-637 5-V operation, V-617 adapter, III-642 add-on for DMM digital voltmeter. III-640 centigrade, I-655, II-648, II-662 calibrated, I-650 ground-referred, I-657 differential, I-652, II-661, III-638, VI-640 digital, I-651, I-658, V-618, VI-637 temperature-reporting, III-638 thermocouple, II-658 µP controlled, 1-650 electronic. II-660, III-639, IV-575, IV-576 Fahrenheit, I-658 ground-referred, I-656 high-accuracy design, IV-577 mplantable/ingestible, III-641 Kelvin, I-653, I-655, II-661 lmear, III-642, IV-574 low-power, I-655 meter, trimmed output, I-655 remote, II-659 single-dc supply, IV-575 variable offset, I-652 thermostats, I 639, I-640, V 60, VI 630 third-overtone oscillator, I-186, IV 123three-in-one test set, III-330 three-minute timer, III-654 three-rail power supply, III-466

threshold detectors, precision, III-157 tilt meter, II-663-666, III-644-646 differential capacitance measurement circuit, II-665 mercury-switch, V-302 sense of slope, II-664 ultra-simple level, II-666 time bases crystal oscillator, III-133, IV-128, V-137, V-139 function generators, 1 Hz, readout/counter applications, IV-201oscilloscopes timebase generator, V-425 trigger selector for oscilloscopes timebase, V-425 time constants, operational amplifiers, RC time constants. VI- $42\hat{6}$ time delays, 1-668, 11-220, 11-667-670. III-647-649 metuit, precision solid state, I-664 constant current charging, II-668 electronic, III-648 generator, I 218 hour sampling circuit, II-668 integrator to multiply 555 timers, low-cost, II-669 long-duration, 1-220 motor controller, VI-413 relay, I-219, I-663 timing threshold and load driver, II-670, III-648 time division multiplex stereo decoder, II-168 timers (see also 555 timer circuits), I-666, I 668, II-671-681, III-650-655, IV-578-586, V-621-627, VI-648-650 0.1 to 90 second, 1-663 2- to 2000 minute, V-624 555-based alarm, V-11 741 timer, I-667 ac line/timer interface, VI-281 adjustable, II 681, IV-585 alarro, II-674, VI-649 appliance-cutoff timer, IV-583 CMOS, programmable precision, III-652 countdown, V-627 darkroom, I-480, V-436 elapsed time/counter timer, II-680 electronic egg, 1-665 enlarger timer, II-446, III-445 extended on-time, V-627 IC, crystal-stabilized, II-151 interval, programmable, 1-660, II-678 lamp timer, VI-649 long-delay, 1-219, V-626 long-duration, II-675, IV-585 long-interval, I-667, IV-581, IV-582 long-period, V-624, VI-650 long-term, II-672, III-653 mains-powered, IV-579 numute marker, VI-337 mobile radio on-alarm timer, VI-32 one-shot, II-266, III-317, III-654 photographic, I-485 darkroom enlarger, III-445 photo-event timer, IV-379 reaction timer, game circuit, IV-204 reflex timer, V-622 SCR design, IV-583 self-retriggering timed-on

generator, V-343 sequential, I-661-662, I-663, III-651, Ŷ-623 slide-show, III-444, III-448 solid-state, industrial applications, 1-664 tele-timer, V-623 ten-minute ID timer, IV-584 three-minute, III-654 three-stage sequential, V-623 thumbwheel-type, programmable interval, I-660 time-out circuit, IV-580, IV-586 triangle-wave generator, linear, III-222 variable duty-cycle output, III-240 voltage-controlled, programmable, 11-676 washer, I-668 watch tick timer, V-292 watchdog timer/alarm, IV-584 wide-range, V-1-mmute to 400 hours, V-625 timing light, ignition, II-60 timing threshold and load driver, III 648 tone alert decoder, I-213 tone annunciator, transformerless, III-27-28 tone burst generators, I-604, II-90, III-74 tone circuits (see function generators, sound generators) controls (*see also* sound generators), I-677, II-682-689, III 656-660, IV-587-589, V-334, V 630-631, VI-651-653 500-Hz. III-154 active control, IV-588 amateur radio amplifier controls, 1 2-kW 144-MHz, VI-19 audio amplifier, II-686 automatic level control (ALC), V-60-62 bass, I-670, V-584, V-631, VI-652 bass and treble, I-674, V-631, VI-653 Baxandall tone-control audio amplifier, IV-588 decibel level detectors, III-154 equalizers, 11-684, 111-658 filter circuit, V-1 kHz, V-191 guitar treble booster, II-683 high-quality, I-675 high-z mput, hi fi, I-676 level meters, sound levels, III-346, III-614, IV-305, IV-307 loudness, II-46 microphone preamp, I-675, II-687 mixer preamp, I-58 passive circuit, II-689 preamplifiers, I-58, I-673, I-675, II-687, II-688, III-657 rumble/scratch filter, III-660 stereo level display circuit, VI-190 stereo preamp with tone control, V 581 three-band active, I-676, III-658 three-channel, I-672 tone detector, 15-kHz, VI-181 trebel control, V-631, VI-652 tremolo circuit, IV-589 volume limiter, V-59, VI-376 Wien-bridge filter, III-659 tone decoders. I-231, III-143, VI-170 dual time constant, II-166

24 percent bandwidth, I-215 relay output, I-213 tone-dial decoder, I-630, I-631 tone detectors, 500-Hz, III-164 tone-dial generator, I-629 tone-dialing telephone, III-607 tone encoder, I-67 subaudible, I-23 tone-dial encoder, I-629 two-wire, II-364 tone generators (see sound generators) tone probe, digital IC testing with, II-504 tone ringer, telephone, II-630, II-631 totem-pole driver, bootstrapping, III-175 touch switches, I-131, I-135-136, I-137, II-690-693, III-661-665, IV-590-594, V-632-635, VI-654-657 CMOS, I-137 bistable multivibrator, touchtriggered, I-133 bridging touch plate sensor, V-634 capacitive sensor touch switch system, VI-656 dimmer, CMOS based, V-270 double-button latching, I-138 hum-detecting touch sensor, IV-594lamp control, three-way, IV-247 low-current, I-132 On/Off, II-691, III-663, IV-593 latching switch, V-635 line-hum, III-664 momentary operation, I-133 negative-triggered, III-662 on-only switch, V-635 positive-triggered, III-662 sensor switch and clock, IV-591 single-plate sensor, V-633 switch, V-633, V-634, V-635 time-on touch switch. IV-594 timed touch switch, VI-655 touchomatic, II-693 two-terminal, III-663 Touchtone generator, telephone, III-609 toxic gas detector, II-280 toy siren, II-575 TR circuit, II-532 TR switch for antennas, automatic, V-37 tracers, VI-658-659 audio reference signal, probe, I-527 bug, III-358 cable tracer, VI-659 closed-loop, III-356 receiver, III-357 signal tracer, VI-659 wire tracer, VI-659 track-and-hold circuits, III-667, III-668 sample-and-hold circuit, III-549, III-552tracking circuits, III-666-668 positive/negative voltage reference, III-667 preregulator, III-492 track-and-hold, III-667, III-668 tracking power supply, VI-485 train chuffer sound effect, II-588 transceivers (see also receivers; transmitters), IV-595-603 1750-meter, V-646 CE, 20-m, IV-596-598

CW, 5 W, 80-meter, IV-602 external microphone circuit, V-351 hand-held, III-39, III-461 HF transceiver/mixer, IV-457 memory backup, VI-28 power supply for lab source, VI-517 T/R switch, VI-610 ultrasonic, III-702, III-704 transducer amplifiers, I-86, III-669-673 flat-response, tape, III-673 NAB preamp, III-673 photodiode amplificr, III-672 preamp, magnetic phono, III-671, III-673 tape playback, III-672 voltage, differential-to-singleended, III-670 transducers, I-86 bridge type, amplifier, II-84, III-71 detector, magnetic transducer, I-233interfacing resistive transducers, VI-281 sonar, switch and, III-703 temperature, remote sensor, I-649 transformers isolation transformer, V-349, V-470 power tester, VI-354 transistors and transistorized circuits flashers, II-236, III-200 frequency tripler, nonselective, saturated, II-252 headphone amplifier, II-43 on/off switch for op amp, IV-546 phototransistor, V-279 amplifier, V-409 variable-sensitivity, V-409 pulse generator, IV-437 sorter, I-401 tester, I-401, IV-281, V-306 turn-on circuit, V-345 transistor-matching circuit, VI-339 transmission indicator, II-211 transmitters (see also receivers; transceivers), III-674-691, IV-595-603, V-636-649, VI-660-665 2-meter, IV-600-601 10-meter DSB, V-647 27.125-MHz NBFM, V-637 acoustic-sound transmitter, IV-311 amateur radio, 80-M, III-675 amateur TV, IV-599, VI-34-36 ATV JR transmitter, V-440 MHz, V-640 audio, visible-light, V-261 automobile security system, VI-9 baby-alert, carrier-current circuit, V-95 beacon, III-683, IV-603 broadcast, 1-to-2 MHz, I-680 carrier current, I-144, I-145, III-79 computer circuit, 1-of-8 channel, III-100 CW transmitters, I-681, III-684, III-686, III-687, III-690, IV-601, V-648, V-649, VI-22-23, VI-27, VI-664 DSB, 10-meter, V-647 dummy load for transmitter tests, VI-37 fiberoptic, III-177, VI-207 FM transmitters, I-681, V-641 27.125-MHz NBFM, V-637 49-MHz, V-643 bug, VI-662

infrared, voice-modulated pulse, IV-228 light-beam, V-259 multiplex, III-688 one-transistor design, III-687 optical, I-361, I-367, II-417 radio, V-648 snooper, III-680 stereo, V-575, V-580, VI-662 voice, III-678 wireless microphone, III-682, III-685, III-691 half-duplex information transmission link, low-cost, III-679 HF, low-power, IV-598 infrared, 1-342, 1-343, II-289, II-290. 111-275, III-277, IV-226-227, IV-228audio-modulated, VI-262 headphones, V-227 pulsed for on/off control, V-228 pulse frequency modulated, VI-269single-tone, VI-264 steady-tone, VI-267 wireless headphones, VI-263 keyer interface circuit, amateur radio, VI-31 laser diode-based, VI-292 LED lightwave communications, VI-309 lme-carrier, with on/off, 200 kHz, I-142 low-frequency. III-682 MIDI transmitter, V-393 memory backup, VI-28 modulated-light transmitter, V-258 Morse code transmitter, V-6-W for 7-MHz, V 641 multiplexed, 1-of-8 channel, III-395 negative key-line keyer, IV-244 optical, 1 361, I-363, II-417, II-418, IV 368 oscillator and, 27 and 49 MHz, I-680 output indicator, IV-218 photodiode log converter/transmitter, VI-312 QRP, V-638-639, V-644-645 remote control, V-509, V-513 interface, V-511 ultrasonic, V-512 remote sensors, loop-type, III-70 television, III-676 tracking transmitter, V-642 transceiver, 1750-meter, V-646 transceiver T/R switch, VI-610 transmit/receive sequencer, preamp, V 348 ultrasonic 40 kHz, I-685 CW transceiver, VI-669 Doppler, V 651 vacuum-tube, low-power, 80/40-M, V-642 voice-communication, light-beam, V-260 VHF, III-681, III-684, VI-663 video detector for transmitter tests, VI-37 wireless guitar transmitter, VI-661 wireless microphone, VI-661 transverter, 2-to-6 meter, V-124 treasure locator, lo-parts, I-409 treble booster, guitar, ll-683 tremolo circuits, 1-59, 1-598, 10 692-695, IV-589

tri-color indicator, V-232 triac circuits, V-268 ac-voltage controller, IV-426 contact protection, II-531 controller circuit, V-267, V-271 dimmer switches, I-375, II-310, III-303 drive interface, direct dc, I-266 microcomputer-to-triac interface, V-244 microprocessor array, II-410 relay-contact protection with, II-5**3**1 switch, inductive load, IV-253 trigger, I-421 voltage doubler, III-468 zero point switch, II-311 zero voltage, I-623 triangle-to-sine converter, II-127 triangle/square wave oscillator, II-422, V-206 triangle-wave generators, III-234, V-203, VI-596, VI-697, VI-698 10-Hz to 10-kHz VCO, V-570 clock-driven, V-206 square/triangle-wave, III-225, III-239, III - 242timer, linear, III-222 triangle-wave oscillator, V-205 trickle charger. 12 V battery, I-117 triggers 50-MHz, III-364 camera alarm, III-444 flash, photography, xenon flash, III-447 load-sensing, V-285 optical Schnitt, I-362 oscilloscope-triggered swccp, III-438remote flash, I-484 SCR series, optically coupled, III-411 sound/light flash, I-482 triac, I-421 triggered sweep, add-on, I-472 tripler, nonselective, transistor saturation, II-252 trouble tone alert, II-3 TTL circuits clock, wide-frequency, III-85 coupler, optical, III-416 gates, siren using, II-576 Morse code keyer, II-25 oscillator, VI-437 speaker driver, VI-199 square-to-triangle wave converter, 11-125 TTL-to-MOS logic converter, II-125TTL oscillators, I-179, I-613, IV-127 1 MHz to 10 MHz, I-178 1 MHz to 20 MHz, IV-127 crystal, TTL-compatible, I-179 sine wave/square oscillator, IV-512 television display using, II-372 tube amplifier, high-voltage isolation. IV-426 tuners antenna tuner, IV-14, V-38, VI-66 FM, I-231 guitar and bass, II-362 turbo circuits, glitch free, III-186 turn-on circuit, V-345 twang-twang circuit, II-592 twilight-triggered circuit, II-322 twin-T notch filters. III-403

Twenty-One game, VI-246 two state siren, III-567 two-tone generator, III-570 two tone siren, III-562 two way intercorn, III-282 two's complement, D/A conversion system, binary, 12-bit, III-166

υ

UA2240 staircase generator, III-587 UHF-related circuits (see also radio/rf circuits) antenna for UHF scanners, VI-67 amplifier, I-560-565 audio-to-UHF preamp, V-24 broadband rf amphfiers, V-523 field-strength meters, IV-165 oscillator, tunable, VI-456 rf amphfiers, UHF TV-line amplifier, IV-482, IV-483 source dipper, IV-299 TV preamphfier, III-546 VHF/UHF rf diode switch, IV-544 VHF/UHF rf preamplifier, V-515 wideband amphfier, 1-560, III-264 UJT circuits battery chargers, III-56 calibration oscillator, 100-kHz, VI-157 metronome, II-355 monostable circuit, bias voltage change insensitive, II-268 ultrasonic circuits (see also soundoperated circuits), III-696-707, IV-604-606, V-650-653, VI-666-670 arc welding inverter, 20 kHz, III-700 cleaner, V-652-653 CW transceiver, VI-669 generator, VI-670 induction heater, 120-kHz 500-W, 111-704 motion detector, VI-668 pest-control/repel, I-684, II-685, III-699, III-706, III-707, IV-605-606 proximity sensor, VI-669 ranging system, III-697 receiver, III-698, III-705, VI-670 Doppler ultrasound, V-651 remote-control receiver, V-513 remote-control tester, VI-667 remote-control transmitter, V-512 sonar transducer/switch, III-703 sound source, IV-605 switch, I-683 transceiver, III-702, III-704 transmitter, I-685 Doppler ultrasound, V-651 undervollage detector/monitor, III-762, IV-138, VI-117 uninterruptible power supply, II-462, 111-477, V-471 unity-gain amplifiers inverting, I-35, I-80 noninverting, V-21, V-22 ultra high-Z, ac, II-7 unity-gain buffer stable, speed and high-input impedance, II-6 unity-gain follower, I-27 universal counters 10 MHz, I-255, II-139 40-MHz, III-127 universal maxer stage, III-370 universal power supply, 3-30V, III 489 up/down counters 8 digit, II-134 extreme count freezer, III-125 XOR gate, III-105

V

vacuum fluorescent display circuit, II-185 vacuum gauge, automotive, IV-45 vacuum tube amplifier, VI-72-73, VI-87 vapor detector, II-279 varactor-tuned 10 MHz ceramic resonator oscillator, II-141 variable current source, 100 mA to 2A, II-471 variable-frequency inverter, complementary output, III-297 variable-frequency oscillators (VFO) 5 MHz design, II-551 4093 CMOS, V-421 adjustable temperature compensation, V-420 amateur radio, V 532 buffer amplifier, V-92 CMOS design, V-418 code practice oscillators, V-103 rf, V-6.5 MHz, V-529 variable-gain amplifier, voltagecontrolled, 1-28-29 variable-gain and sign op amp, II-405 variable gain circuit, accurate null, 111-69 variable state filters universal, V-178 variable oscillators, II-421 audio, 20 Hz to 20 kHz, II-727 duty-cycle, III-422 four-decade, single control. II-424 sine-wave oscillator, low-distortion, 111-558wide range, II-429 variable power supplies, III-487-492. IV-414-421 0- to 12-V, V-1 A, V-460 current source, voltage programmable, IV-420 de supply SCR variable, IV-418 step variable, IV-418 dual universal supply, 0-to-50 V, 5 A. IV-416-417 regulated supply, 2.5 A, 1.25-to-25 V switch-selected fixed-voltage supply, IV-419 switching regulator, low-power, III-490 switching, 100-kHz multiple-output, 111-488 tracking preregulator, III-492 transformerless supply, IV-420 universal 3-30V, III-489 voltage regulators for variable supplies, III-490, III-492. IV-421 variable current source, 100mA to 2A, II-471 voltage regulator, III-491 VCR/TV circuits. ISD 1000A record/playback circuit, VI-50 on/off control, V-113 tester for VCR head amplifier. VI-48 video detector controller, VI-178 vehicles (see automotive circuits) vertical deflection circuit, VI-374

VHF related circuits (see also radio/rf; television; UHF) amplifiers, I-558 beacon transmitter, VI-663 crystal oscillators, III-138-140 HF/VHF switchable active antenna, V 524 modulator, 1-440, III-684 tone transmitter, III-681 transmitters, III-681, III-684 VHF/UHF dode rf switch, IV-544 VHF/UHF rf preamplifier, V-515 video circuits (see also amateur television (ATV)), III-713-728, IV-607-621, V-654-662, VI-671-583 amateur TV (ATV) down converter. V-125, V-126 amplifiers, video, I-688, I-690, I-692, III-39, III-708-712, IV-482, IV-483. V-656, V-662, VI-674, VI-675, VI 679, VI-681, VI-682 75-ohm video pulse, III-711 buffer, low-distortion, III-712 color, I-34, III-724 de gain-control, III-711 differential video loop-through, V-657 FET cascade, I-691 gain block, III-712 IF, I-689, II-687, V-655 JFET bipolar cascade, 1-692 line driving, 11-710 log amplifier, 1-38 output, V-655 RGB, 111-709 summing, clamping circuit and, III-710 TV amplifiers, I-688, I-690, III-39, IV-482, IV-483 variable-gain video loop-through. V-658 amplifier/driver, VI-683 ATV video sampler circuit, V-656 audio/video switcher circuit, IV-540-541 automatic TV turn-off, I-577 buffers, V-93 cable driver, VI-200, VI-678 camera-image tracker, analog voltage, IV-608-609 camera link, wireless, III-718 chroma demodulator with RGB matrix, III-716 coax cable driver, VI-201 color amplifier, III-724 color-bar generator, IV-614 conuncrcial zapper, V-334-335 composite-video signal text adder. III-716 converters RGB-to-NTSC, IV-611 video a/d and d/a, IV-610-611 cross-hatch generator, color TV, III-724data interface, TTL oscillator, II-372 dc restorer, III-723, V-659 decoders NTSC-to-RGB, IV-613 stereo TV, II-167, V-576-579, V-580 video line decoders, VI-171 delayed video trigger for oscilloscopes, VI-464 detectors IF, MC130/MC1352 design, I-688

low-level video, I-687-689 transmitter tests, VI-37 downconverter, VI-40-41, VI-44-45 differential video loop-through amplifier, V-657 driver, two-input video MUX cable driver, VI-197 dummy load for transmitter tests, VI-37 equalizer, VI-681 fader, V-658 filter, VSB filter for LM 2880, VI-219 gray-scale generator. European line standard, VI-680 gray-scale video generator, NTSC, VI-679 high-performance video switch, III-728 horizontal deflection circuit, VI-382 IF amplifier, 4.5-MHz sound, V-655, VI-678 IF detector, amplifier, MC130/MC1352, I-688 ISD 1000A record/playback circuit, VI-50 line driver, VI-683 line pulse extractor, IV-612 line receiver, VI-550 line/bar generator, V-662 loop-thru ampliñer, IV-616 master circuit, video master, V-661 mixer, high-performance video mixer, IV-609 modulators, I-437, I-439, II-371, II-372, II-433, II-434, VI-399, VI-403 monitors, RGB, blue box, III-99 monochrome-pattern generator, IV-617 multiplexer, cascaded, 1-of-15, III-393 MUX cable driver multi input, V-657 two-input, V-657 NTSC-to-RGB converter, VI-677 one-of-two video selector, VI-676 op amp circuits, IV-615 output amplifier, V-655 PAL/NTSC decoder with RGB input, III-717 palette, III-720 picture fixer/inverter, III-722 preamplifier, III-546, V-660, VI-37 remote control, IR relay, VI-263 rf amplifiers, TV sound system, V-519 rf up-converter for TVRO subcarrier reception, IV-501 RGB-composite converter, III-714 sampler circuit, ATV video, V-656 satellite TV audio switcher, IV-543 selector, V-660 signal-amplitude measurer, V-309 signal clamp, III-726 sound, IF/FM IF amplifier with quadrature, 1-690 staircase generator, VI-597 stereo-sound decoder, II-167 stereo TV decoder, V-576-579, V-580summing amplifier, VI 681 sweep/function generator, VI-238-241 switching circuits, III-719, III-725, III-727, IV-618-621, VI-680 video/audio switch, V-586 wideband for RGB signals, V-587

switching power supply for color TV, SCR, VI-487 sync circuits, VI-615-618 sync separator, III-715, IV-616 sync stripper/video interface, V-659 tester for VCR head amplifier, VI-48 titler. VI-672-674 transmitter, TV, III-676, IV-599, VI 34, VI-35, VI-36, VI-38-39, VI-42-43 TV sound system, rf amplifiers, V-519 twisted-pair video driver/receiver circuit, VI-682 variable-gain video loop-through amphfier, V-658 VCR video detector controller, VI-178VCR/TV on-off control, V-133 vertical deflection circuit, VI-374 video, power, channel-select signal carrier. V-344-345 UHF oscillator, tunable, VI-456 VHF beacon transmitter, VI-663 wireless camera link, III-71 VLF/VHF wideband antenna low-noise, active, V-33 vocal eliminator, IV-19 voice communications light-beam transmitter/receiver, V-260personal message recorder, V-330-331 voice-mail alert for telephone, V-607 voice scrambler/descrambler, IV-26, IV-27 voice substitute, electronic, III-734 voice-activated circuits (see also sound-operated circuits; telephone-related circuits), III-729-734, IV-622-624, V-545-555 ac line-voltage announcer, III-730 allophone generator, III-733 amplifier/switch, I-608 computer speech synthesizer, III-732 dialed phone number vocalizer, III-731 disguiser for voices, V-326-327 intercoms, V-239, VI-376 level meter, VI-194 message system, single-chip, VI-373 scanner voice squelch, IV-624 scrambler, V-554 speech detector, II-617, III-615 stripper, vocal stripper, V-546-547 switches, III-580, IV-527 switch/amplifier, I-608, V-553 vocal stripper, V-546-547, VI-372, VI-373 voice identifier for amateur radio use, V-550 voice substitute, electronic, III-734 VOX circuit, IV-623 voltage bias regulator, VI-519 voltage-controlled amplifier (VCA), I-31, I-598, IV-20. VI-684-685 attenuator for, II-18 differential-to-single-ended, III-670 reference, I-36 tremolo circuit, 1-598 variable gain, 1-28-29 voltage-controlled oscillators (VCO), I-702-704, II-702, III-735, IV-625-630, V-663-667, VI-685-687

3.5 V regulated output converter, III-739 10 Hz to 10 kHz. J-701, III-735-741 three-decade, V-666 555-VCO, IV-627 audio-frequency VCO, IV-626 basic circuit, V-666, V-667 crystal oscillator, III-135, IV-124 current sink, voltage-controlled, IV-629 DDS digital, VI-447 driver, op-amp design, IV-362 linear, I-701, IV-628 triangle/square wave, II-263 logarithnuc sweep, III-738 one-shot, II-266 precision, I-702, III-431 restricted-range. IV-627 sine-wave oscillator, V-666 semisoidal 3-Hz to 300-kHz, V-664-665 stable, IV-372-373 square-wave generators, V-570 supply voltage splitter, III-738 three-decade, I-703 -based, V-665 'rMOS, balanced, III-736 two-decade, high-frequency, I-704 varactorless, IV-630 variable-capacitance diode-sparked, **III-73**7 VHF oscillator, voltage-tuned, IV-628 waveform generator, III-737 wide-range, IV-627, IV-629 voltage-controller, pulse generator, 111-524 voltage converters/inverters, III-742-748, V-668-669 12-to-16 V, III-747 dc-to-ac inverter, V-669 de-to-de, III-744, III-746, V-669 flyback, lugh-efficiency, III-744 flyback-switching, self-oscillating. 111-748 negative voltage, µP-controlled, IV-117 offline, 1.5-W, III-746 regulated 15-V_{out} 6-V driven, III-745 splitter, III-748 unipolar-to-dual supply, III-743 voltage-to-current converters, I-163, 1-166, 11-124, III-110, III-120, IV-118, VI-153 voltage-to-frequency converters, I-707, 111-749-757, IV 638-642 1 Hz-to-10 Milz, III-754 1 Hz-to-30 MHz, III-750 1 Hz-to-1.25 MHz, III-755 5 kHz-to-2 MHz, III-752 10 Hz to 10 kHz, I-706, III-110 accurate, III-756 differential-input, III-750 function generators. potentiometer-position, IV-200 low-cost, III-751 low-frequency converter, IV-641 negative input, I-708 optocoupler, IV-642 positive input, I-707 precision, II-131 preserved input, III-753 ultraprecision, I-708 wide-range, III-751, III-752 voltage-to-pulse duration converter, II-124

voltage converters/inverters, continued voltage-ratio-to-frequency converter, III-116 voltage detector glitch detector, VI-178 grid leak detector, VI-179 voltage detector relay, battery charger, II-76 voltage doublers, III-459, IV-635, V-460 caseaded, Coekeroft-Walton, IV-635 triac-controlled, III-468 voltage followers, I-40, III-212, VI-127, VI-386 fast, I-34 noninverting, I-33 signal-supply operation, amplifier, . III-20 voltage inverters, precision, III-298 voltage indicators/meters (see also voltmeters), III-758-772, IV 423, VI-688-695 amplifiers, VI-689, VI-695 audible voltage indicator, VI-694 automotive battery voltage gauge. IV-47 battery-voltage measuring regulator, IV-77 calibrator, VI-693 comparator and, II-104 dc meter, expanded scale, VI 692 five-step level detector, I-337 frequency counter, III-768 HTS, precision, I-122 level detectors, I-338, II-172, III-759, IH-770 low-voltage indicator, III 769 monitor, V-315, VI-689, VI-694 multiplexed common-cathode LED ADC, III-764 over/under monitor, III 762 peak program detector, III-771 solid-state battery, I-120 ten-step level detector, 1 335 visible, 1-338, III-772 voltage freezer, III-763 voltage-level circuit, V-301 voltage multipliers, IV-631-637, V-670-672 2,000 V low-current supply, IV-636-637 10,000 V de supply, IV-633 corona wind generator, IV-633 doublers, III-459, IV-635 cascaded, Cockcroft-Walton, IV-635 dc, V-672 triac-controlled, III-468 high-voltage tripler, VI-504 laser power supply, IV-636 low-frequency multiplier, IV-325 negative-ion generator, highvoltage, IV-634 quadrupler, dc, V 671 tnpler, IV-637, V-671, VI-504, VI-531 voltage probes, V-474 voltage references, III-773-775 bipolar source, III-774 digitally controlled, ill-775 expanded-scale analog meter, III-774 positive/negative, tracker for, III-667 variable-voltage reference source, IV-327

voltage regulators, I-501, I-511, Il-484, III-485, VI-482, VI-486, VI-561-567 0- to 10-V at 3A. adjustable, I-511 0- to 22-V, I-510 0- to 30-V. I-510 3 A. III-472 3 3-V adjustable, VI-489 4- to 70-V, VI-493 5 V, low-dropout, III-461 5 V, 1 A, I-500 5 V, ultrastable reference, I-497 6 A, variable output switching, I-513 8- from 5-V regulator, V-469 10 A, I-510 10 A, adjustable, III-492 10 V, high-stability. III-468 15 V, I A, remote sense, I-499 15 V, slow-turn-on, III-477 -15 V negative. I-499 45 V, 1 A switching, I-499 90 V rms voltage regulator with PUT, II-479 100 Vrms. I-496 200 kHz, I-491 200-V. VI-505 ac, III-477 adjustable output, 1-506, 1-512 application circuit, I-492 automotive circuits, III-48, IV-67 battery power suppliers, I-117, IV-77bilateral source/load power system, VI-488 bucking, high-voltage, III 481 combination voltage/current regulator, V-455 common hot-lead regulator, IV-467 constant voltage/constant current, J-508 current and thermal protection, 10 amp, 11-474 Darlington, IV-421 dual-tracking, III-462 efficiency-improving switching, IV-464 fixed pnp, zener diode increases output, II-484 fixed-current regulator, IV-467 fixed supplies, III-461, III-468, III-471-477, IV-408, IV-462-467 flyback, off-line, II-481 foldback-current lumiting, II-478 high- or low-input regulator, IV-466 high-stability, I-499, I-502, III-468 high-voltage power supplies, I-509. II-478, III-485, III-490, VI-500, VI-503IC regulator protector, VI-483 inductorless, ill-476 junk transistors, VI-497 LM317 design, IV-466 loss cutter, V 467 low-dropout, 5-V. III-461, VI-486 low-power, I-695, III-490 low-voltage, I-502, I-511 linear, II-468, III-459 mobile, I-498 MPU, multiple output, I-513 multiple on-card adjuster, VI-494 negative, 1-498, 1-499, 111-474, IV-465 npn/pnp boost, III-475 off-line flyback regulator, II-481 pnp, Il-484

positive, I-498, III-471, III-475, VI-491, VI-518 pre-regulators, II-482, III-480, III-492 programmable, IV-470 projection lamp, II-305 PUT, 90 V rms, II-479 radiation-hardened 125A linear regulator, II-468 remote shutdown, I-510 SCR preregulator for, II-482 single supply voltage regulator, II-471 sensor, LM317 regulator sensing, IV-466 short-circuit protection, lowvoltage, I-502 single-ended, I-493 single-supply, II-471 slow-turn-on 15 V, I-499 step-down, I-493 step-up, II-78 switching supplies, I-491, I-492, I-493, I-497, I-498, I-513, II-78, III-472, III-476, III-490, IV-408, IV-463, V-453, VI-484 3-A, III-472 3 W, application circuit, I-492 5 V, 6 A 25 kHz, separate ultrastable reference, I-497 6 A, variable output, I-513 200 kHz, I-491 high-current inductorless, III-476 low-power, III-490 multiple output, for use with MPU, I-513 step down, I-493 variable current source with voltage regulation, IV-470 variable supplies, III-490, III-491, III-492, IV-421, IV-468 470 crowbar limiting, VI-515 current linuting, VI-518 current source, HI-490 zener design, programmable, IV-470 voltage sources millivolt, zenerless, I-696 programmable, I-694 pseudorandom, VI-381 voltage splitter, III-738 voltmeters, III-758 3.5 digit, I-710 full scale, III-761 true rms ac, I-713 4.5-digit, III-760 5-digit, III-760 ac, III-765, VI-690-691 wide-band, I-716 wide-range, III-772 add-on thermometer for, III-640 bar-graph, I-99, II-54 dc, III-763, VI-692 high-input resistance, III-762 low-drift, V-301 digital voltmeters (DVM), III-4, VI-693, VI-329 3.5-digit, common anode display, I-713 3.5-digit, full-scale, four-decade, HI-761 3.75-digit, I-711 4.5-digit, 111-760 4.5-digit, LCD display, I-717 auto-calibrate circuit, I-714 automatic nulling, 1-712 interface and temperature sensor, II-647

LED readout, IV-286 temperature sensor and DVM, 647 FET, 1-714, III-765, III-770 high-input resistance, III-768 JFET, V-318 LED expanded scale, V-311 millivoltmeters, III-767, III-769, IV-289, IV-294, IV-295 ac. 1-716 audio, III-767, 111-769 dc, IV-295 four-range, IV-289 high-input impedance, I-715 LED readout, IV-294 rf, I-405, III-766 voltohnumeters (VOM) field strength, I-276 phase meter, digital readout, IV-277 volume amplifier, II-46 volume control circuits, IV-643-645 telephone, II-623 volume indicator, aucho amphfier, IV-212 volume limíter, audio signal amplifiers, V-59 VOR signal simulator, IV-273 voting circuit, noise-based, VI-422- $4\bar{2}3$ vox box, Il-582, IV-623 Vpp generator, EPROM, II-114 VU meters, III-487 extended range, II-487, I-715 LED display, IV-211

W

waa-waa circuit, 11-590 wailers (see alarms; sirens) wake-up call, electronic, II-324 walkman amplifier, II-456 warblers (see alarms, sirens) warning devices auto lights-on warning, II 55 high-level, I-387 high-speed, I-101 light, II-320, III-317 low-level, audio output, I-391 speed, I-96 varying-frequency alarm, II-579 water-level sensors (see fluid and moisture detectors) water-temperature gauge, automotive, IV-44 wattmeter, I-17, VI-342 wave-shaping circuits (see also waveform generators), IV-646 651 capacitor for high-slew rates, IV-650 chpper, glitch-free, IV-648 flip-flop, S/R, IV-651 harmonic generator, IV-649 phase shifter, IV-647 rectifier, full-wave, IV-650 signal conditioner, IV-649 waveform generators (see also burst generators, function generators; sound generators; square-wave generators; wave-shaping circuits), II-269, II-272, V-200-207, VI-696-702 AM broadcast-band, IV-302 AM/IF, 455 kHz, IV-301 audio, precision, III-230 four-output, III-223 harmonic generators, I-24, III-228, IV-649

high-frequency, II-150 high-speed generator, I-723 monostable multivibrator, VI-700 pattern generator/polar-to-rect. converter, V-288 precise, II-274 pulse generator, VI-699 PWM signal generator, VI-698 ramp generators, I-540, II-521-523. lll-525-527, IV-443-447 555 based, V-203 accurate, III-526 integrator, initial condition reset, 111-527 linear, 11-270 variable reset level, II-267 voltage-controlled, II-523 sawtooth generator, III-241, IV-444, IV-446, V-204, V-205, V-491, VI-575-577, VI-701 signal source for audio amplifier/inverter, VI-702 sine-wave generators, IV-505, IV-506, V-541, V-542, V-543, V-544, VI-701 60 Hz, IV-507 audio, II-564 LC, IV-507 LF, IV-512 oscillator, audio, ID-559 square-wave and, tunable oscillator, III-232 VLF audio tone, IV-508 sme/cosine generator, VI-700 sine/square wave generators, I-65, III-232, IV-512 square-wave generators, 11-594-600, 111-225, 111-239, 111-242, 111-583-585, IV-529-536, V-568-570, VI-593-594 1 kHz, IV-536 2 MHz using two TTL gates, II-598 555 timer, II-595 astable circuit, IV-534 astable multivibrator, II-597 CMOS 555 astable, true rail-to rail, II-596 duty-cycle multivibrator, III-50percent, Ill-584 four-decade design, IV-535 high-current oscillator, III-585 hne frequency, II-599 low-frequency TTL oscillator, II-595 multiburst generator, II-88 multivibrator, IV-536 oscillators, I-613-614, I-616, II-596, II-597, II-616, IV-532, IV-533 phase-tracking, three-phase, II-598 pulse extractor, III-584 quadrature-outputs oscillator, III-585 sine-wave and, tunable oscillator, III-232 three-phase, II-600 tone-burst generator, single timer IC, II-89 triangle-wave and, III-225, III-239, Ш-242 TTL, LSTTL, CMOS designs, IV-530-532 variable duty-cycle, IV-533 variable-frequency, IV-535 staircase generators, I-730, II-601-602, III-586-588, IV-443, VI-595-599

stepped waveforms, IV-447 sweep generators, I-472, III-438 test signal generator, VI-702 three-phase digital, VI-343 triangle-wave, III-234, V-203, V-205, V-206, VI-697, VI-698 stepped, VI-596 square wave, 1-726, 111-225, 111-239, III-242, V-206 timer, linear, III-222 two-function, III-234 VCO and, III-737 waveguide circuits, VI-703-704 wavemeter, tuned RF, IV-302 weather-alert decoder, IV-140 weight scale, digital, II-398 Wheatstone bridge, VI-123, VI-148 Wheel-of-Fortune game, IV-206, VI-254whistle, steam locomotive, II-589, III-568 who's first game circuit, III-244 wide-range oscillators, I-69, I-730, III-425 wide-range peak detectors, III-152 hybrid, 500 kHz-1 GHz, III-265 instrumentation, III-281 miniature, III-265 UHF amplifiers, high-performance FETs, III-264 wideband amplifiers low-noise/low-drift, I-38 two-stage, I-689 rf, IV-489, IV-490, IV-491 HF, IV-492 **JFET**, IV-493 MOSFET, IV-492 two-CA3100 op amp design, IV-491 unity gam inverting, I-35 wideband signal splitter, III-582 wideband two-pole high-pass filter, II-215Wien-bridge filter. III-659 notch filter, II-402 Wien-bridge oscillators, I-62-63, I-66, 1-70, II-566, III-429, III-558, IV-371, IV-377, IV-511, V-415, V-419, V-541 VI-439, VI-444 CMOS chip in, II-568 low-distortion, thermally stable, III-557 low-voltage, III-432 sine wave, I-66, I-70, II-566. IV-510, IV-513 single-supply, III-558 thermally stable, III-557 three-decade, IV-510 variable, III-424 very-low-distortion, IV-513 wind chimes, electronic, VI-591 wind-powered battery charger, II-70 windicator, I-330 window circuits, II-106, III-90, III-776-781, IV-655-659, V-673-674 comparator, IV-656-657, IV-658, IV-659, V-299, V-674 detector, I-235, III-776-781, IV-658, VI-181 digital frequency window, III-777 discriminator, III-781, V-674 generator, IV-657 high-input-impedance, II-108 windshield woper circuits (see automotive circuits) wire tracer, II-343

wireless microphones (see microphones) wreless speaker system, IR, III-272 wring ac outlet tester, V-318 ac wring locator, V-317 two-way switch, V-591 write amplifiers, III-18 WWV converter, VI-147 WWV receiver, VI-538-539, VI-558

Х

xenon flash trigger, slave, III-447 XOR gates, IV-107 complementary signals generator, III-226 oscillator, III-429 up/down counter, III-105

Y

yelp oscillator/siren, II-577, III-562

Z

280 clock, II-121 Z-Dice game 248-249, VI-248 zappers, battery, II-64, II-66, II-68 zener diodes clipper, fast and symmetrical, IV-329

increasing power rating, 1-496, II-485

limiter using one-zener design, IV-257test set, V-321 tester. 1-400 variable, 1-507 voltage regulator, programmable, IV-470 zero crossing detector, I-732, I-733, II-173 zero crossing switch, VI-606 zero meter, suppressed, I-716 zero point switches temperature control, III-624 truac, II-311 zero-voltage switches closed contact half-wave, III-412 solid-state, III-410, III-416

_

ABOUT THE AUTHORS

Rudolf F. Graf has 45 years of engineering, sales, and marketing experience in the electronics field. He has written more than 30 books (about three million copies printed) and well over 100 articles. He is a senior member of the IEEE, a licensed amateur radio operator (KA2CWL), and has a BSEE degree from Polytechnic Institute of Brooklyn and an MBA from NYU. He is self-employed.

William Sheets is a self-employed circuit design engineer. He has more than 25 years of experience in RF, analog, and digital electronics. He has written numerous articles in electronics publications and co-authored five books with Graf. His interests include amateur radio (K2MQJ), photography, and travel. He has designed and built numerous items, including a satellite TV system, many transmitters and receivers, and a computer. He has an MEE degree from NYU, is married, and lives in upstate New York.