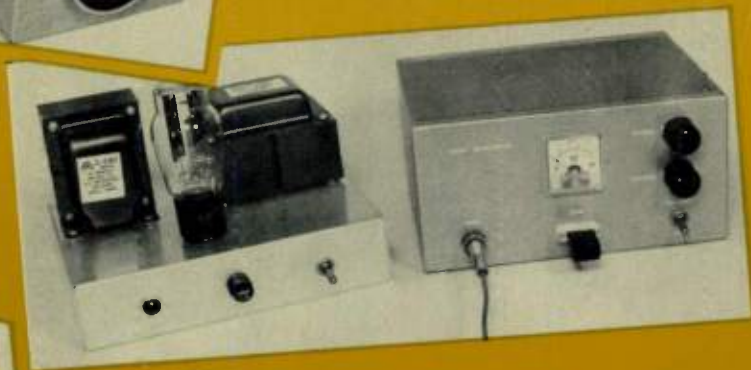


A *Herb W. Samz* PHOTOFACT PUBLICATION

# AMATEUR RADIO

## Construction Projects



by CHARLES CARINGELLA  
W6NJV

Complete instructions, including circuit description, construction techniques, parts lists, tuning, and operation, for 11 useful devices. Projects of value to every ham.



# AMATEUR RADIO Construction Projects

by CHARLES CARINGELLA

W6NJV

Amateur radio is a rewarding and enjoyable hobby. For many hams the greatest thrill comes from constructing and operating their own "home-brew" rigs. There is something about being able to lean back and say, "I built it myself," that isn't engendered by ownership of a commercial unit.

**Amateur Radio Construction Projects** is a book for every amateur, whether he wants to build all his equipment or just a unit or two to supplement what he already owns. Starting with many helpful construction hints (some of which will benefit the "old-timer"), the book progresses from simple projects to more complicated ones. Each chapter contains a complete circuit description, chassis layout, tuning procedure, and operating instructions, supplemented by schematic and pictorial diagrams and complete parts lists.

The projects given in this book include: a 2-band novice transmitter; 3-band novice transmitter; antenna matching balun; 10-, 15-, or 20-meter converter; 6-meter and 2-meter converters; 2-meter and 6-meter walkie-talkies; 6-meter mobile converter-transmitter; all-band phone-CW transmitter; and a 2-meter phone transmitter. In short, useful devices for all amateurs—novice-, technician-, and general-class—are covered. Presented in the author's popular style and extensive use of photos and drawings, **Amateur Radio Construction Projects** is a book that all amateurs will want to own.

## ABOUT THE AUTHOR

Charles Caringella has been a licensed radio amateur and holder of a commercial radiotelephone license for 14 years. He is an avid "do-it-yourself" fan, a fact reflected in his writing. Each project has been designed and built right in his own home lab. Chuck is well known as a free-lance author, having had numerous articles published in many national magazines.



HOWARD W. SAMs & CO., INC.  
THE BOBBS-MERRILL COMPANY, INC.

\$2.50

ARP-1



**\$2.50**

**Cat. No. ARP-1**

# AMATEUR RADIO CONSTRUCTION PROJECTS

by  
**Charles Caringella**  
**W6NJV**



**HOWARD W. SAMS & CO., INC.**

**THE BOBBS-MERRILL COMPANY, INC.**

*Indianapolis • New York*

**FIRST EDITION**

**FIRST PRINTING — JUNE, 1963**

**AMATEUR RADIO CONSTRUCTION PROJECTS**

**Copyright © 1963 by Howard W. Sams & Co., Inc., Indianapolis 6, Indiana. Printed in the United States of America.**

**Reproduction or use, without express permission, of editorial or pictorial content, in any manner, is prohibited. No patent liability is assumed with respect to the use of the information contained herein.**

**Library of Congress Catalog Card Number: 63-19105**

## PREFACE

Amateur radio has afforded thousands of radio enthusiasts the opportunity to acquire skills in radiocommunications and technology. For many, amateur radio has been the start of a professional career in electronics, as well as providing hours of enjoyment as a hobby.

Constructing your own equipment is rewarding as an educational experience. In addition, there's always the feeling of accomplishment when operating your own "home brew" rig, not to mention the satisfaction which comes from saving money.

Construction projects for the beginner, as well as the pro, are described in this book. Included are projects for the Novice, Technician, and General-Class amateurs.

For instance, the simple novice transmitter for 80 and 40 meters described in Chapter 2 is a typical beginner's project. The beginner is helped along by the pictorial wiring diagrams, in addition to schematic diagrams, chassis cutout location drawings, photos, and complete parts lists.

The latest techniques are incorporated in the low-noise 6- and 2-meter converters described in later chapters. For the advanced amateur the all-band, phone-CW transmitter, and the 2-meter phone transmitter described in the last two chapters should be of special interest.

Here's hoping you enjoy building and operating these projects as much as I did in preparing them for this book.

CHARLES CARINGELLA, W6NJV

May, 1963





# CONTENTS

## CHAPTER 1

- CONSTRUCTION TECHNIQUES** ..... 7  
The basic principles of construction, including tool requirements and their use, laying out chassis and panels, mounting components, wiring, and soldering techniques.

## CHAPTER 2

- NOVICE TRANSMITTER FOR 40 OR 80 METERS** ..... 14  
A simple one-tube, two-band crystal-controlled transmitter and separate power supply. An excellent beginners project.

## CHAPTER 3

- 30-WATT NOVICE TRANSMITTER FOR 80, 40, AND 15-METERS** .... 27  
A low-cost, easy-to-build, three-band, crystal-controlled transmitter. Uses same power supply as unit in Chapter 2.

## CHAPTER 4

- BALUN ANTENNA MATCHING UNIT** ..... 37  
A simple, easy-to-assemble unit for matching an unbalanced output to an unbalanced or a balanced antenna.

## CHAPTER 5

- CRYSTAL-CONTROLLED CONVERTER FOR 10, 15, OR 20 METERS** .. 44  
An excellent, low-cost "front end" with a self-contained power supply. Output is 7-mc, making it ideal to use with low-frequency government surplus receivers.

## CHAPTER 6

- 6-METER, CRYSTAL-CONTROLLED CONVERTER** ..... 55  
An inexpensive, easy to construct unit utilizing a low-noise Nu-vistor tube. Output is in the 7-mc region, making it ideal for use with low-frequency government-surplus receivers.

## CHAPTER 7

- LOW-NOISE, CRYSTAL-CONTROLLED, 2-METER CONVERTER . . . . 65  
Incorporating a low-noise *Nuvistor* front-end, this two-tube, crystal-controlled converter is suitable for novice-, technician-, or general-class amateurs. Output is in the 7-mc region.

## CHAPTER 8

- A DELUXE, 2-METER WALKIE-TALKIE . . . . . 77  
A small 2-meter-transceiver employing 6 subminiature tubes. Powered by batteries or optional transistorized DC-DC power pack. Power output in 100 milliwatts.

## CHAPTER 9

- A 6-METER WALKIE-TALKIE . . . . . 90  
A 4 subminiature-tube, 6-meter transceiver delivering 250 milliwatts power output. Incorporates a transistorized power supply which operates on flashlight cells.

## CHAPTER 10

- CONVERTER-TRANSMITTER FOR 6-METER MOBILE . . . . . 101  
A compact 6-meter converter, transmitter, and self-contained power supply. Output is in broadcast band so it can be fed to auto receiver. Incorporates switch for broadcast receiver input switching and relay for transmit-receive switching.

## CHAPTER 11

- ALL-BAND PHONE-CW TRANSMITTER . . . . . 112  
A 40-watt 10 through 80-meter transmitter. Suitable for phone or CW operation, it is crystal controlled, but a VFO may be used with it. All bandswitching and tuning controls are on front panel.

## CHAPTER 12

- 2-METER PHONE TRANSMITTER . . . . . 126  
A 15-watt crystal-controlled transmitter suitable for fixed-station or mobile operation. Contains 6 tubes, plus a separate AC power supply.

# 1 Construction Techniques

The amateur radio construction projects described in the following pages were all built with the simple hand tools, materials, and techniques outlined in this chapter. Contrary to what some people may think, it doesn't take a large selection of specialized tools for the amateur to build neat-appearing, professional-quality equipment. As a matter of fact, only a few basic hand tools, and a little time and patience, are required. Of course, the amount of effort and energy expended is greatly reduced with a complete assortment of tools, particularly machine tools; however, they are not entirely necessary.

The availability of chassis, cabinets, and other types of enclosures made of aluminum makes the job much easier for the amateur. Aluminum is relatively soft, so it is easy to work with hand tools—in many instances, ordinary wood-working tools can be employed. The tools illustrated in Fig. 1-1 represent the minimum requirement in hand tools necessary for the mechanical construction of the projects in this book. Each one is identified by a number in the photo. The tools, and their purpose are as follows:

1. Hand drill—should have a 3-jaw chuck that will accommodate up to  $\frac{1}{4}$ -inch drill bits.
2.  $\frac{1}{4}$ -inch drill bit—used for drilling mounting holes for slug-tuned coil forms and to drill pilot holes for the reamer (item 6).
3. No. 25 drill bit—used for drilling holes for 6-32 screws.
4. No. 30 drill bit—used for drilling holes for 4-40 screws. This drill bit should also be used to drill pilot holes for the  $\frac{1}{4}$ -inch drill.
5. Small pen knife—used for removing burrs around drilled holes. A pen knife works quite well on soft aluminum.
6. Reamer—this unit fits into a standard woodworking brace; however, models with a handle are available. The model shown will cut any size hole up to  $\frac{7}{8}$  inch in diameter.
7. Chassis punch— $1\frac{5}{32}$ -inch diameter, used in punching holes for octal sockets and plugs used in projects in this book.

8. Spiral coping saw blades and holder—this device will cut any shape hole in aluminum or steel.
9. Half-round wood file—for cleaning holes cut with the spiral coping saw.

For the beginner without tools, the foregoing list will represent a rather small outlay of capital. The "old timer" may also find some useful tips in this chapter, particularly since several techniques are described which have not appeared in other handbooks.

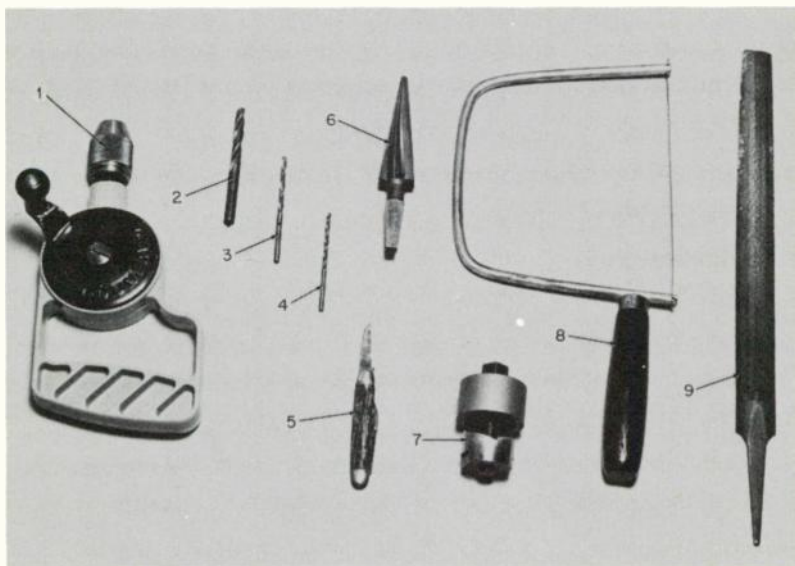


Fig. 1-1. Basic hand tools needed for drilling and cutting holes.

### Chassis and Panel Layout

The key to successfully completing a neat-appearing piece of electronic equipment begins with the accurate layout of hole locations and, therefore, the proper location of components. In some circuits, such as high-frequency RF circuits, the proper placement of components can mean the difference between success or failure in the performance of the units. Each project in this book is accompanied by a chassis and panel layout drawing. Follow the dimensions listed very carefully, and take enough time to lay them out accurately.

First cover the chassis or panel with a piece of graph paper. (If graph paper is not available, a piece of ordinary wrapping paper

will suffice.) The paper should be drawn tightly and taped into place. It serves a dual purpose—all the dimension lines can be drawn on it directly, yet it will protect the chassis or panel finish from marks and scratches.

With the aid of a ruler or square, locate all the center lines of the holes on the paper. Once all of the center lines have been drawn, double check to make sure they are correctly located, then center punch each one of them through the paper. If a regular center punch is not available, anything with a sharp point, such as an ice pick or nail, will suffice. Aluminum is quite soft and will mark easily, so only a gentle tap to the center punch with a hammer is necessary. Anything more than a gentle tap may put a large dent in the aluminum, resulting in a messy job.

After all the holes have been center punched, remove the paper, and you're ready for the next operation.

### **Drilling and Cutting the Holes**

Components such as tube sockets, RF connectors, transformers, and other parts used in the projects are mounted with either 4-40 or 6-32 screws. A No. 30 drill bit is used for drilling the mounting holes for 4-40 screws, and a No. 25 drill bit for the 6-32 screws. These are clearance drills, slightly oversize, to allow for minor inaccuracies in layout and drilling. Where mounting holes are needed, either a No. 30 or a No. 25 drill is called for in the layout drawing.

A  $\frac{5}{8}$ -inch hole is required for the seven-pin miniature tube sockets and a  $\frac{3}{4}$ -inch hole for the nine-pin sockets. These holes, or for that matter any size hole up to  $\frac{7}{8}$ -inch in diameter, can be made with the reamer shown in Fig. 1-1. This versatile tool eliminates the need for several smaller chassis punches, and it is capable of making a very "clean" hole.

The best method for making these larger holes is to first draw an outline of the hole on the chassis with a compass. The previously made center-punch marks serve as the center point for the compass. Next, a pilot hole is drilled with the No. 30 drill, followed by the  $\frac{1}{4}$ -inch drill. Finally, the reamer is used to enlarge the hole; the compass outline serves as the stop guide. Remove all burrs with a pen knife when the hole has been completed.

A  $1\frac{1}{32}$ -inch chassis punch is the only one that needs to be purchased. This size is used for all the octal-socket and octal-plug holes employed in this book.

The spiral-blade coping saw shown in Fig. 1-1 is used to cut large meter holes, and the like. This saw is an extremely versatile tool; it will literally cut any shape and size hole in aluminum,

steel, wood, plastic, etc. Fig. 1-2 illustrates its use. The outline of the meter hole has been drawn on a panel and the spiral coping saw is used to cut the hole, while following the guide line, in the aluminum.

Finally, a half-round wood file can be used to "clean" up the rough line made by the coping saw blade, as shown in Fig. 1-3. The wood file works quite well on the soft aluminum.

### **Mounting the Components and Wiring**

A complete parts list for each project in the following chapters is given at the end of the chapter. Fig. 1-4 shows the tools necessary for mounting the components, installing the wiring, and soldering the connections. As for Fig. 1-1, each item in Fig. 1-4 is identified by a number. They are as follows:

1. Rosin-core solder—used for soldering all electrical connections.

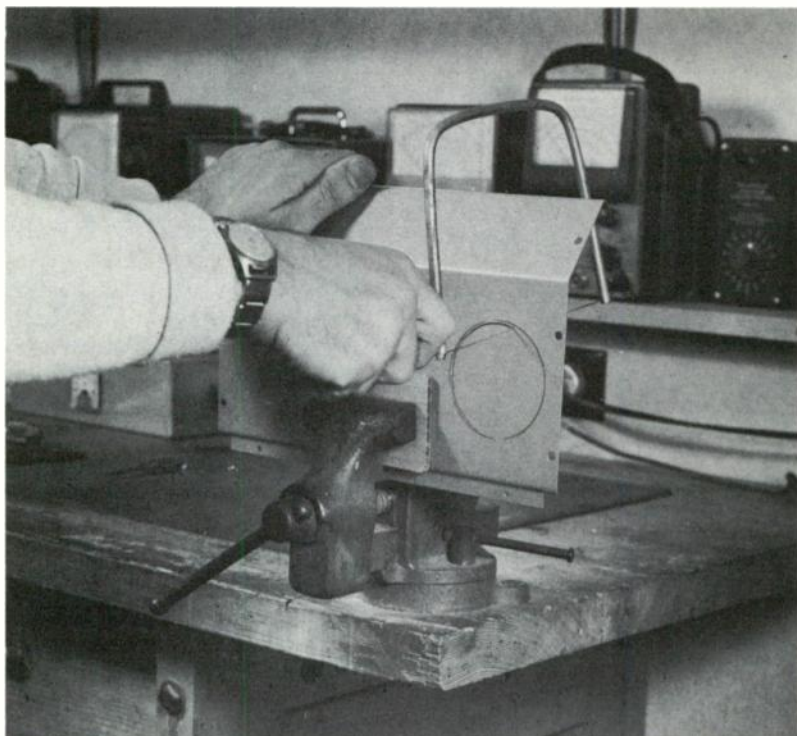


Fig. 1-2. Cutting a large meter hole on a panel with a spiral-blade coping saw.



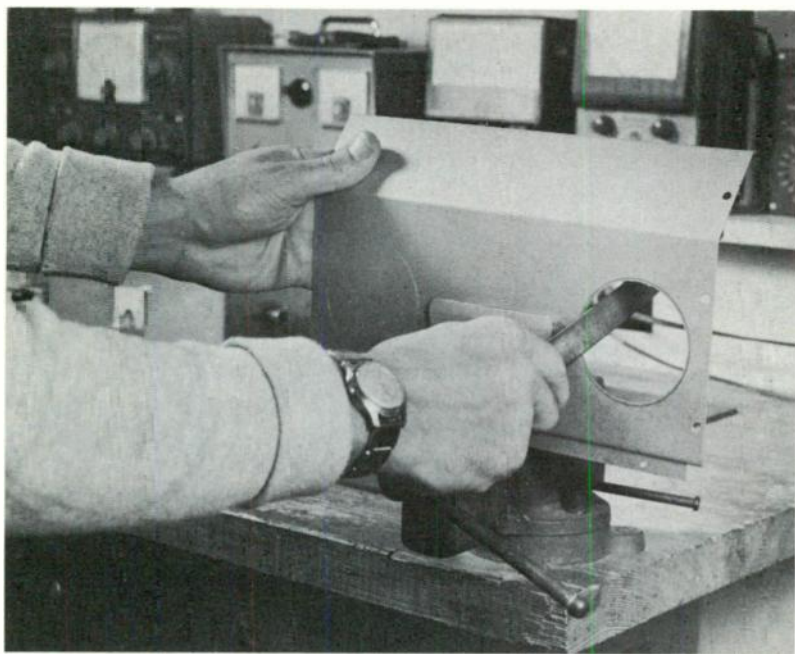


Fig. 1-3. Using a half-round wood file to "clean" up the rough edge made by the coping-saw blade.

2. Soldering iron—this pencil-type iron is sufficient for all projects in this book.
3. Wire strippers—used to remove the insulation from hook-up wire.
4. Screwdriver—used for mounting screws and components.
5. Needle-nose pliers—used for mounting wires to terminals.
6. Side cutters—used for cutting hook-up wire.

In addition to the tools illustrated, an adjustable wrench will be needed to tighten the hex nuts used to mount switches, coil forms, phone jacks, etc.

A small quantity of hook-up wire will be needed to wire the units. It is preferable to use assorted colors, such as red for high-voltage lines, green for filament leads, black for grounds, etc. This will simplify circuit tracing if the unit should ever require troubleshooting. No. 20 stranded hook-up wire will be adequate for all wiring purposes in this book. However, for wiring high-frequency RF circuits it is advisable to use either No. 18 or No. 20 bare, tinned-copper wire. RF leads should be kept as short as possible. They should be run directly from point to point in the circuit and

right angle bends should be avoided. Make sure the wire does not short to the chassis or to other leads.

Component leads and wiring in general should not depend on solder joints for mechanical support. The wire lead should be wrapped around the solder terminal at least once, and crimped tight with the needle-nose pliers, as shown in Fig. 1-5. Solder only insures a good electrical path between the wire and the terminal, and it should not be counted on for mechanical support.

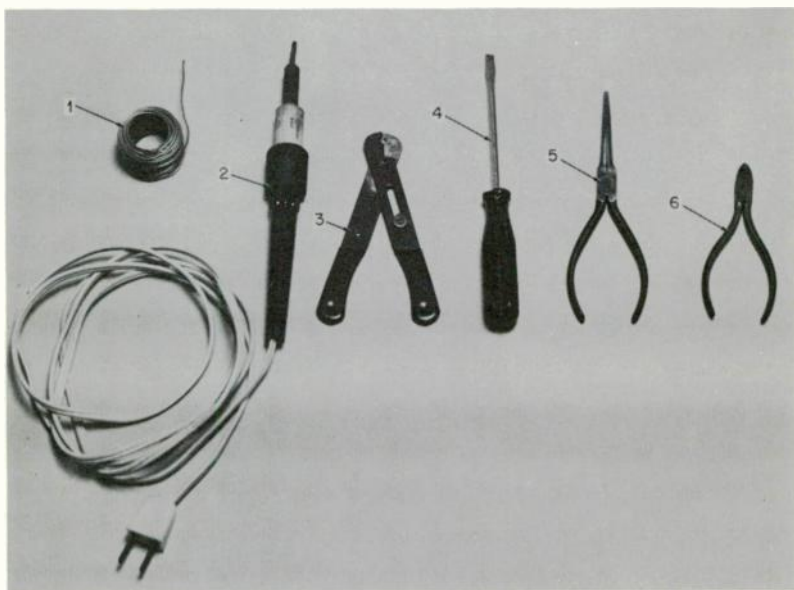



Fig. 1-4. Tools needed for making electrical connections.

## Soldering

The successful performance of home-built electronic equipment depends on the workmanship used in making soldered connections. Proper solder connections are not at all difficult to make, if the following precautions are observed.

First and foremost, it is most important to use the proper solder. Rosin-flux core solder is the only type of solder to use in electronic equipment. Rosin flux is completely noncorrosive and electrically nonconductive when it is cold and in the solid state. Acid-core solder should not, under any circumstances, be used. This type of solder is extremely corrosive and electrically conductive, even when it has cooled, causing shorts between points in the wiring and shorts from the wiring to the chassis.



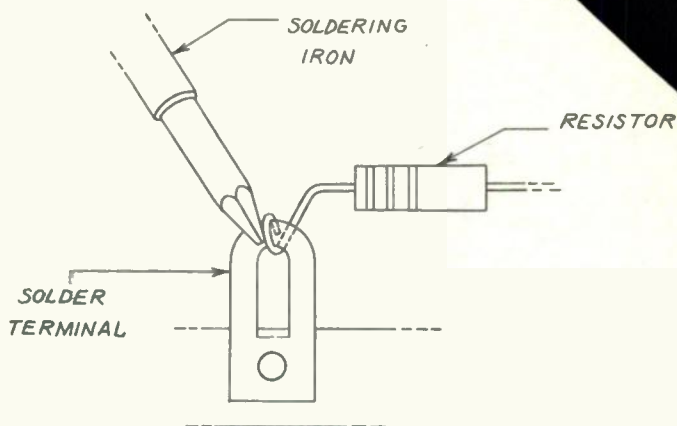

**Fig. 1-5.** The proper method of making a connection to a terminal.

A good quality soldering iron or soldering gun, between 50 and 100 watts, should be used to make the soldered connections. The tip of the iron should be bright and clean, and free of excess solder. Apply the tip of the soldering iron directly to the work, touching both the wire and the solder terminal simultaneously. The solder should be applied to the point of contact between the iron and the work. Avoid the excessive use of solder; use just enough to flow around the wire and onto the terminal. Also, avoid overheating the connection. Some components can be damaged easily if they are subjected to excessive heat. The finished connection should be smooth and semiglossy in appearance.

# e Transmitter for 80 Meters

The FCC Rules and Regulations governing the Amateur Radio Service provide for novice-class operation in segments of the 80-, 40-, 15-, and 2-meter amateur bands. Novice operators have only limited privileges. For example, only A1-type emission (telegraphy) is allowed in the novice segments of the 80-, 40-, and 15-meter bands and the maximum allowable power input to the stage supplying power to the antenna is 75 watts. In addition, the novice transmitter must be crystal controlled.


The crystal-controlled CW transmitter (telegraphy transmitter) described in this chapter will operate in the 80- and 40-meter novice bands. Band changing is accomplished by simply changing the crystal and the output tank coil to the band desired. The DC power input is approximately 10 watts; thus, it meets the FCC requirements with respect to both power input and crystal-controlled carrier emission. Frequency limitations in the 80-meter band are 3,700 to 3,750 kilocycles (kc), and in the 40-meter band, 7,150 to 7,200 kc.

## Circuit Description

The one-tube transmitter described here is actually an oscillator-transmitter unit: that is, the tube functions as a crystal oscillator and also delivers RF power to the antenna. This one-tube, two-band transmitter makes an excellent beginner's construction project. The transmitter and power supply are built on a separate chassis. In addition, the power supply and some of the transmitter components can be utilized in the higher-power, three-band novice transmitter described in Chapter 3.

The schematic of the transmitter section is given in Fig. 2-1, and a close-up view of it can be seen in the photo of Fig. 2-2. A complete parts list is given at the end of this chapter. V1 is a beam-power pentode; it operates in a Colpitts-oscillator configuration. The Colpitts oscillator was picked for several reasons. It will oscillate over a wide frequency range by simply changing crystals and tuning the output circuit. The current flowing through the crystal

Fig. 2-1. Schematic of the 40-80 meter, crystal-controlled novice transmitter.

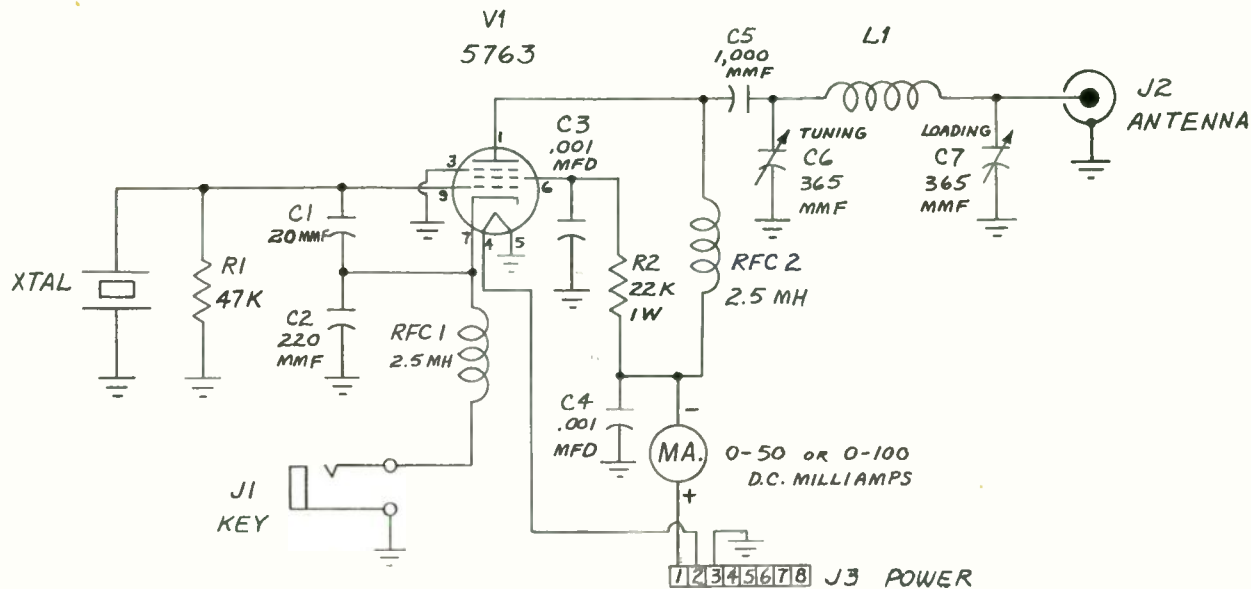

ALL RESISTORS 1/2 WATT,  
UNLESS OTHERWISE NOTED

- #1 - B+, 350 V.
- #2 - FILAMENT, 6.3 V.A.C.
- #3 - CHASSIS GROUND

is very low; therefore crystal damage due to excessive current is prevented. The Colpitts oscillator will operate on the crystal fundamental frequency without frequency pulling, and its output circuit can be readily tuned to the second, third, and even the fourth harmonic of the crystal frequency. Harmonic operation of this circuit is the basis for the multiband transmitters described in later chapters.

The output circuit, consisting of C6, C7, and L1, is known as a pi-section tank circuit. The pi tank is a versatile impedance matching network that allows a number of antenna schemes to be used. The tank circuit will couple most efficiently into an antenna having an unbalanced 50- or 70-ohm transmission line; i.e., 50- or 70-ohm coax cable. It will, however, satisfactorily load a random length of wire.

The transmitter is operated in the CW mode by returning the cathode of the tube to ground through the telegraph key, which plugs into J1. Thus, when the key is up, the tube cannot conduct; when the key is depressed, the tube conducts and oscillation takes place. A DC milliammeter is used in the B+ lead to monitor the plate current. This meter is also used to tune the output circuit.

The schematic of the power supply is shown in Fig. 2-3. It is conventional in all respects: V1 is a full-wave rectifier; C1, C2,

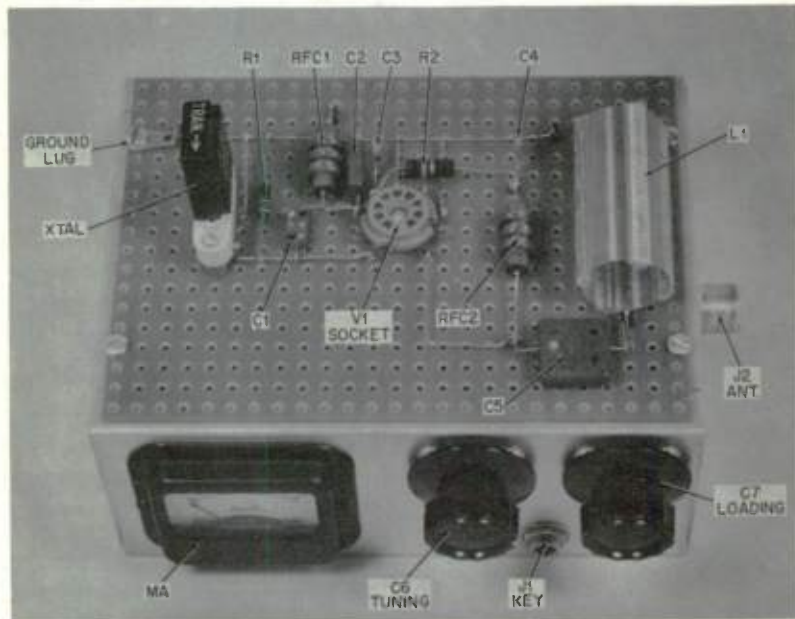


Fig. 2-2. Close-up view of the transmitter chassis.

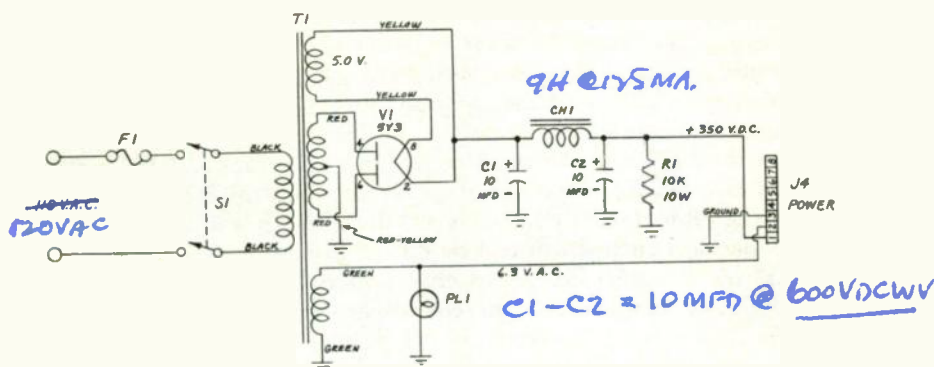


Fig. 2-3. Schematic of the power supply chassis.

and CH1 comprise the filter circuit. R1 is a bleeder resistor; its function is to discharge the filter section when there is no load on the power supply. It also maintains a partial load on the supply, helping to keep the output voltage somewhat constant during keying of the transmitter. The power supply is fused by F1 as a safety precaution. A pilot light (PL1) is utilized in the filament line to indicate when the supply is turned on. An interconnecting cable is used to connect power-supply socket J4 to the power plug (J3) on the transmitter (Fig. 2-1).

### Construction

The oscillator-transmitter circuit is assembled on a 5" by 7" piece of punched phenolic board (Vectorbord). This phenolic-board subchassis is then mounted on a standard 5" by 7" by 3" aluminum chassis as shown in Fig. 2-2. The chassis, which serves now as the base for the subchassis, is inverted with the bottom flange serving as the support for the circuit board. The circuit board is fastened to the aluminum chassis with 6-32 screws.

Key jack J1, tuning capacitor C6, loading capacitor C7, antenna jack J2, power plug J3, and the DC milliammeter are mounted on the aluminum chassis base. The hole layout drawing is given in Fig. 2-4. The mounting hole for antenna connector J2 is not shown in the layout drawing. A  $\frac{5}{8}$ -inch diameter hole is used for mounting this connector. The hole can be located anywhere on the right-hand side of the chassis, or, if desired, it may even be mounted on the rear of the chassis. If located on the rear, it should be placed as close as possible to the end of tank coil L1.

Wire the circuit board by following the pictorial wiring diagram in Fig. 2-5, and the schematic diagram in Fig. 2-1. At the frequen-

cies involved in this unit, lead lengths are not particularly critical; however, they should be kept as short as possible. When wiring the meter, observe the polarity indications given in Figs. 2-1 and 2-5. Meter polarity markings will be found near the terminal studs on the rear of the meter.

Tank coil L1 is made from prewound coil stock (B & W 3016 or Air Dux 832T). The coil stock is available in 3-inch lengths. Since the 80-meter coil calls for a 2-inch length and the 40-meter coil calls for 1 inch. Both can be cut from one piece of stock.

A 5" by 7" by 3" aluminum chassis is also used for the power supply. Hole locations for the chassis are given in Fig. 2-6 and a

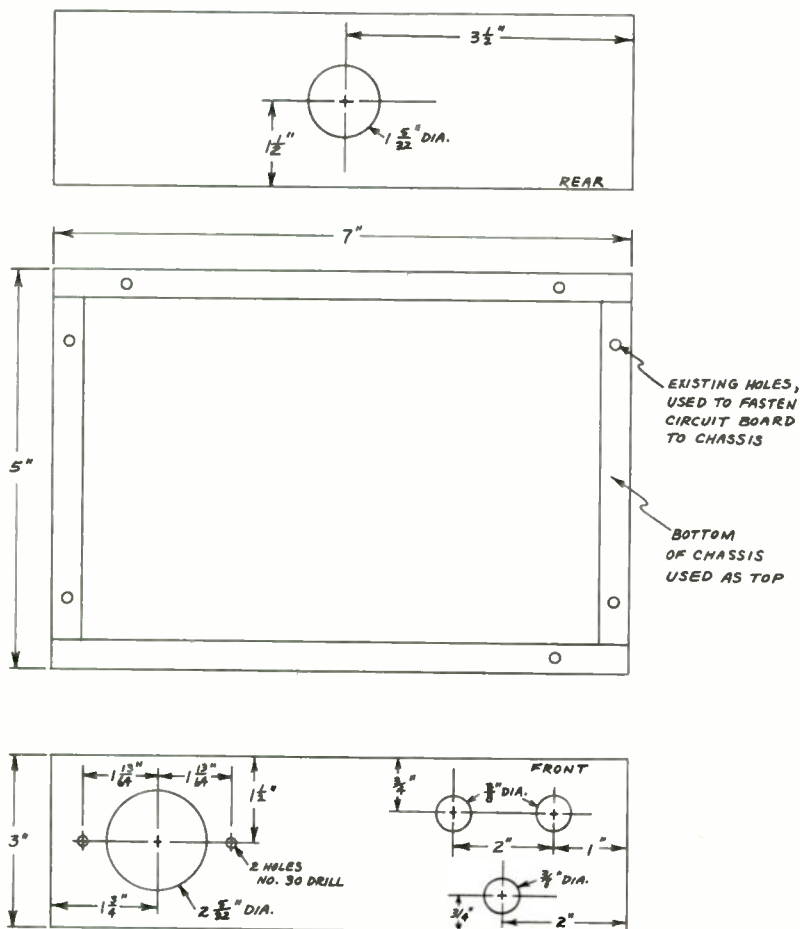


Fig. 2-4. Transmitter layout and hole-drilling guide.

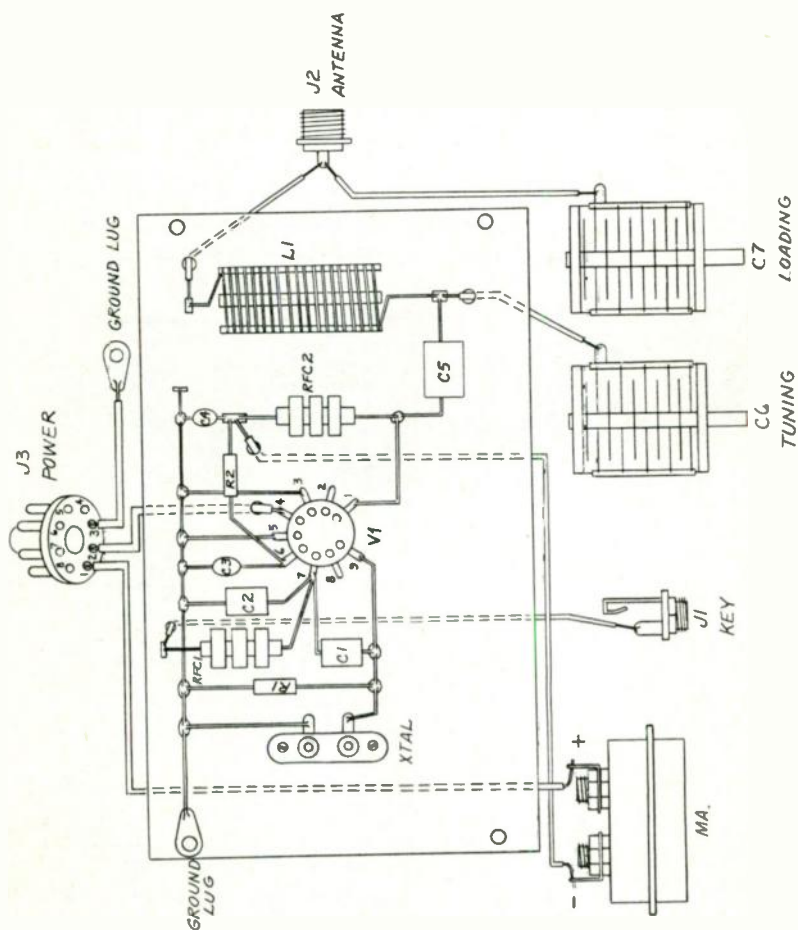


Fig. 2-5. Pictorial wiring diagram of the 40-80 meter novice transmitter.







pictorial diagram of the chassis is given in Fig. 2-7. The AC power cord enters through a  $\frac{3}{8}$ -inch rubber grommet mounted on the rear of the chassis. It should be knotted directly inside the chassis as shown in Fig. 2-8. This knot acts as a strain relief to prevent the cord from being pulled and broken at the soldered connections. The transformer leads should be twisted together as shown in the pictorial diagram and the photo. Be sure to observe the correct polarity for electrolytic filter capacitors, C1 and C2.

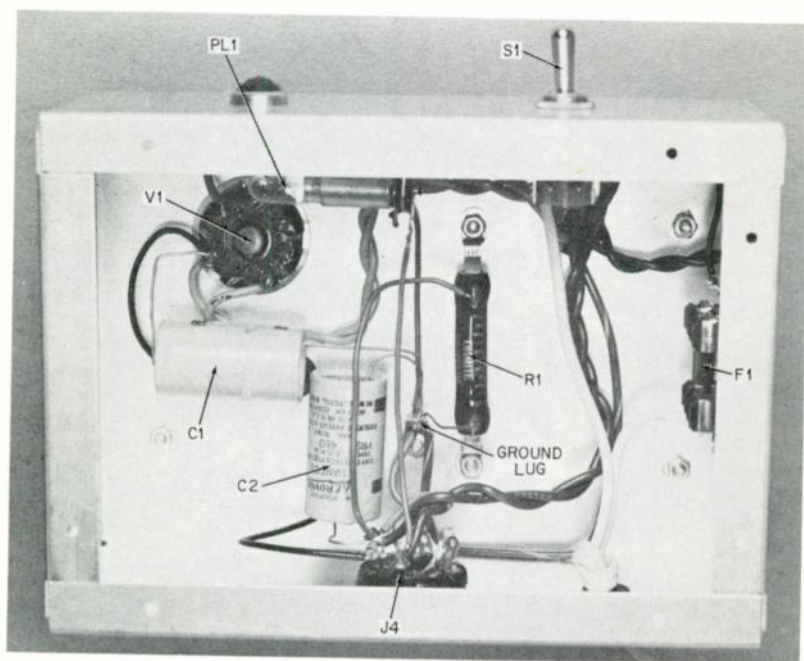



Fig. 2-8. Bottom view of the power supply chassis.

The construction of the interconnecting cable between the transmitter and the power supply is given in Fig. 2-9. It consists of an octal socket and plug and three 16" lengths of hook-up wire which have been twisted together. Connect pins 1, 2, and 3 as shown.


Recheck the wiring against both the schematic and pictorial wiring diagrams before attempting to "fire" the unit up, or before performing the following tests.
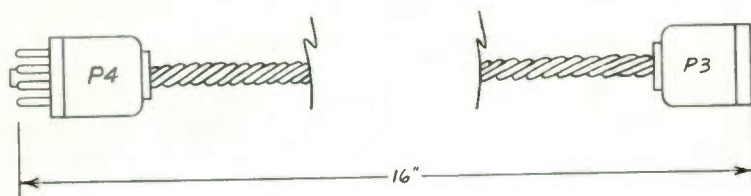
### Testing the Transmitter

Using the interconnecting cable, connect the power supply to the transmitter and insert a crystal into the crystal socket. For 80-



(A) Pictorial.

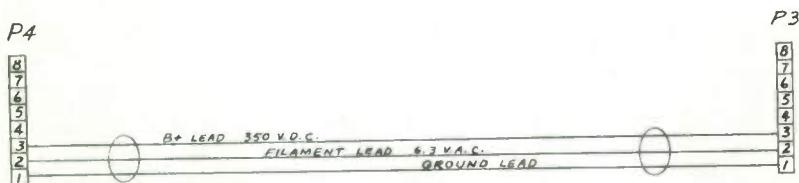

(B) Schematic.

Fig. 2-9. Construction of the interconnecting cable.

meter operation a crystal between 3,700 and 3,750 kc will be needed; for 40-meter operation a crystal between 7,150 and 7,200 will be needed. Next, connect an ordinary light bulb (between 10 and 50 watts) to the antenna output jack on the transmitter (J2). This lamp bulb will serve as the "dummy" load. Solder a wire to the center terminal of the base of the light bulb, and another wire to the outer shell of the base. Connect the wire from the center terminal of the light bulb to the antenna jack and the other wire to ground (chassis). Set a receiver beside the transmitter as shown in Fig. 2-10.

Turn power switch S1 on, and allow the tubes to warm up for approximately a minute. Now close the key and tune the receiver to the transmitting frequency (crystal frequency). A signal should be heard in the receiver. Next, tune tuning capacitor C6 slowly through its range. At some point the meter should dip toward zero, and the light bulb should light. The signal heard in the receiver will also be much louder at this point. Finally, tune loading capacitor C7 through its range. At some point the light will become still brighter, and the meter reading will peak. The transmitter is now ready for "on the air" operation.

### Operating the Transmitter

Connect an antenna to antenna jack J2. If a conventional antenna is not available, a 33-foot length of wire can be loaded up as a temporary measure. One end should be tied to an insulator

and suspended from a tall tree or post; the other end should be connected to the antenna jack. This temporary antenna will operate on both 40 and 80 meters.

Use the tuning procedure outlined previously; however, this time tuning will be accomplished by watching the meter only. Tune C6 for a dip or minimum reading, and tune C7 for a peak

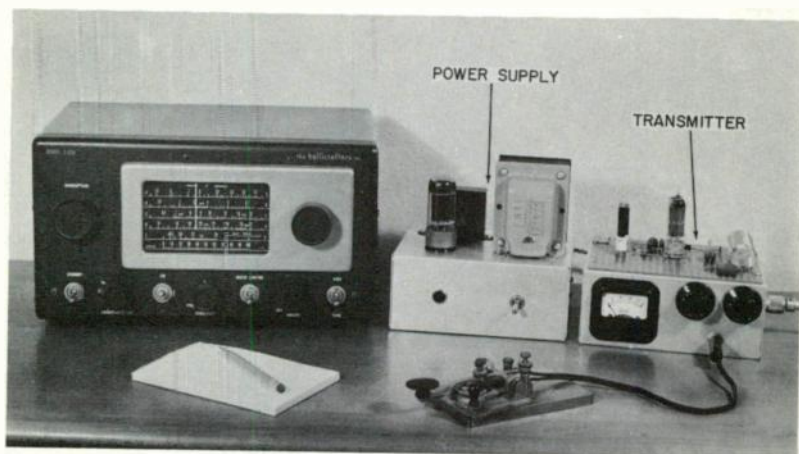


Fig. 2-10. The complete novice station.

or maximum reading. As a last step, redip C6, and the transmitter is ready for "on the air" operation.

To change bands the crystal must be changed to the desired frequency, and tank coil L1 must be changed. The 40- and 80-meter coils are soldered in and out of the circuit for band changing.

Refer to Chapter 4 for construction details on a balun all-band antenna matching unit and details on suitable antennas for this transmitter.

### Transmitter Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | C1       | 20-mmF, 5%, 500V, silvered-mica capacitor.                                   |
| 1        | C2       | 220-mmF, 5%, 500V, silvered-mica capacitor.                                  |
| 2        | C3, C4   | .001-mF, GMV, 1000V, disc-ceramic capacitor.                                 |
| 1        | C5       | 1,000-mmF, 5%, 500V, silvered-mica capacitor.                                |
| 2        | C6, C7   | 10-365-mmF, midjet variable capacitor (broadcast receiver replacement type). |
| 1        | R1       | 47,000-ohm, 1/2-watt, 10%, carbon resistor.                                  |
| 1        | R2       | 22,000-ohm, 1-watt, 10%, carbon resistor.                                    |

## Transmitter Parts List—cont'd

| Quantity | Item No.   | Description  |
|----------|------------|--|
|          | L1         | 80 meters—64 turns of No. 24 tinned-copper wire, wound 32 turns per inch, 1-inch diameter (2-inch length of B & W 3016 or Air Dux 832T coil stock, or equiv.).<br>40 meters—32 turns of No. 24 tinned-copper wire, wound 32 turns per inch, 1-inch diameter (1-inch length of B & W 3016 or Air Dux 832T coil stock, or equiv.). |
| 2        | RFC1, RFC2 | 2.5 millihenry RF chokes (National R-50, Miller 4666, or equiv.).  |
| 1        | Xtal       | 80 meters—3,700- to 3,750-kc crystal.<br>40 meters—7,150- to 7,200-kc crystal.   |
| 1        | V1         | 5763 beam-power tube.  |
| 1        | J1         | Microphone jack (standard phone jack).   |
| 1        | J2         | Coaxial chassis-mount plug SO-239 (Amphenol Type 83-1R or equiv.).   |
| 1        | J3         | Octal chassis-mount plug (Amphenol 86-CP8 or equiv.).  |
| 1        | MA         | 0-50 or 0-100 DC milliammeter (Shurite Model 950 or equiv.).   |
| 1        |            | Crystal socket (Millen 33102 or equiv.).   |
| 1        |            | 9-pin miniature tube socket.   |
| 2        |            | Knobs (E.F. Johnson 116-221 or equiv.).  |
| 2        |            | Solder lugs.   |
| 1        |            | 5" X 7" piece of phenolic punched board (Vector 32AA18 or equiv.).   |
| 6        |            | Push-in terminals for "Vectorbord" (Vector T9.4 or equiv.).  |
| 1        |            | 5" X 7" X 3" aluminum chassis (Bud AC-429, Cal-Chassis A-150, or equiv.).<br>6-32 machine screws and nuts.<br>4-40 machine screws and nuts.<br>Hook-up wire.<br>Solder.  |

## Power Supply Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 2        | C1, C2   | 10-mfd, 450-volt DC, electrolytic capacitor. <i>600VDC WV</i>  |
| 1        | R1       | 10,000-ohm, 10-watt, wirewound resistor.   |
| 1        | CH1      | Filter choke, 9 Henrys @ 125 ma (Triad C-10X, Stancor C-2704, or equiv.).  |
| 1        | T1       | Power transformer—Secondaries: 350-0-350 VAC @ 125 ma; 5VAC @ 3A; 6.3 VAC @ 4.5A (Triad R-14A, Stancor P-8176, Merit P-3153, or equiv.). |
| 1        | S1       | DPST toggle switch.  |
| 1        | F1       | 2-amp, Type 3AG fuse.  |
| 1        | PL1      | 6.3-volt pilot lamp (No. 47).  |
| 1        | V1       | 5Y3GT rectifier tube.  |
| 1        | J4       | Octal socket (Amphenol 78-S8 or equiv.).<br>5" X 7" X 3" aluminum chassis (Bud AC-429, Cal-Chassis A-150, or equiv.).                    |

### Power Supply Parts List—cont'd

| Quantity | Item No. | Description   |
|----------|----------|---|
| 1        |          | Solder lug.   |
| 2        |          | $\frac{3}{8}$ " rubber grommets.                          |
| 1        |          | Fuse mounting (Buss Type 4405 or equiv.).                 |
| 1        |          | Pilot light assembly (E. F. Johnson 147-306-2 or equiv.). |
| 1        |          | Octal tube socket (Amphenol 78-S8 or equiv.).             |
| 1        |          | AC power cord (length as required).                       |
| 1        |          | AC power plug.  |
|          |          | 6-32 machine screws and nuts.                             |
|          |          | 4-40 machine screws and nuts.                             |
|          |          | Hook-up wire.   |
|          |          | Solder.   |

### Interconnecting Cable Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | P3       | Octal connector socket (Amphenol 78-PF8 or equiv.).                        |
| 1        | P4       | Octal connector plug (Amphenol 86-PM8 or equiv.).                          |
| 3        |          | 16-inch lengths of hook-up wire (twisted together to form cable assembly). |

# 30-Watt Novice

## 3 Transmitter for 80-, 40-, and 15-Meters

This unit is ideal for the novice who wants a transmitter for all three of the lower-frequency bands he is allowed to operate on (80, 40, and 15 meters). It is easy to build and operate and is low in cost. The rig runs approximately 30 watts of power. Band changing is accomplished by simply switching oscillator coils and plugging different tank coils in the output power amplifier. The power supply used in Chapter 2 is also used with this transmitter; for those who built the transmitter in Chapter 2, the oscillator tube and most of the associated components can be reused in this rig.

### Circuit Description

The schematic of the 30-watt transmitter is given in Fig. 3-1, and a photo of the completed unit is given in Fig. 3-2. Two tubes are used: V1 is a 5763 beam-power tube operating in a Colpitts oscillator configuration, and V2 is a 6L6 beam-power tube operating as a Class-C power amplifier. The Colpitts oscillator (V1) is quite similar to the one described in Chapter 2. The only difference is in the plate circuit. A pi-section tank circuit was used in Chapter 2; however, conventional parallel-resonant tank circuits are used in this circuit. One tuned circuit is used for each band: L1-C4 for 15 meters, L2-C5 for 40 meters, and L3-C6 for 80 meters. The plate of the 5763 is series fed; that is, the B+ is fed directly through the coil to the plate. Single-pole, three-position rotary switch S1 is the bandswitch that connects the plate of V1 to the proper coil for the desired operating frequency.

The signal from the oscillator is amplified by V2, which delivers approximately 30 watts of RF to the transmitting antenna. The plate of the 6L6 is shunt fed; that is, the B+ is fed to the plate through an RF choke (RFC2), and the RF energy is coupled via C11 to the parallel-resonant tank circuit (L4-C12). L4 is a pre-wound tank coil which is mounted on a five-pin plug, along with





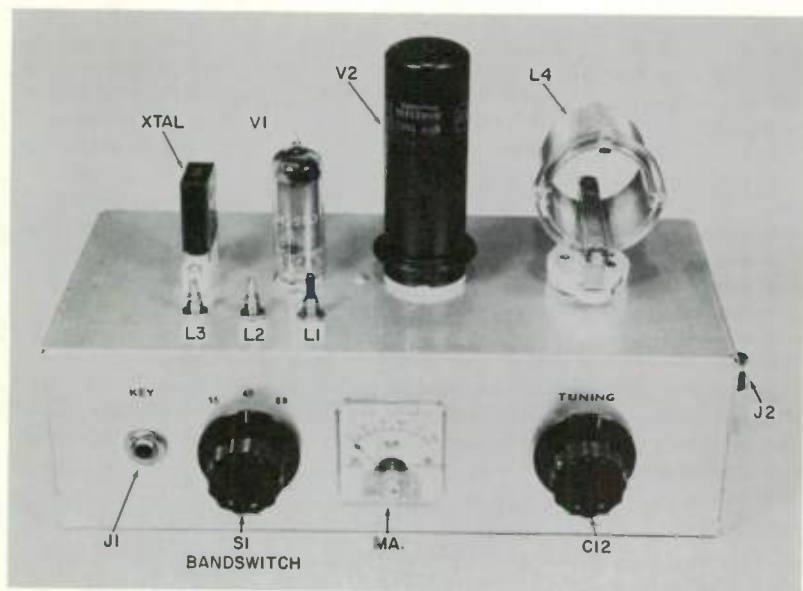


Fig. 3-2. Close-up view of the transmitter.

a multiturn link coil, which couples the RF to the antenna. Three coil assemblies are used—one for each band. A DC milliammeter is used to monitor the V2 plate current, and to tune the output tank circuit. The filaments of V1 and V2 are paralleled for 6-volt operation; power for the filaments is taken from the 6-volt winding in the power supply transformer.


The cathodes of both tubes are run to the key jack; thus, both the oscillator and final amplifier are keyed together. Bypass capacitor C14 helps to cut out key clicks in the transmitted signal.

For 15-meter operation a crystal between 10,550 and 10,625 kc is required. The oscillator frequency is doubled in the oscillator output circuit, since L1 and C4 are resonant in the 21-mc region. With the crystals specified for 15-meter operation the oscillator output will be in the novice segment of that band—21.10 to 21.25 mc. The oscillator operates “straight through” on 80 and 40 meters. A crystal between 3,700 and 3,750 kc is needed for 80-meter operation, and one between 7,150 and 7,200 kc is needed for 40-meter operation.

### Construction

The transmitter is constructed on a 5" by 10" by 3" chassis. Make all the holes needed for mounting the capacitors, tube sock-

Fig. 3-3. Transmitter layout and hole-drilling guide.

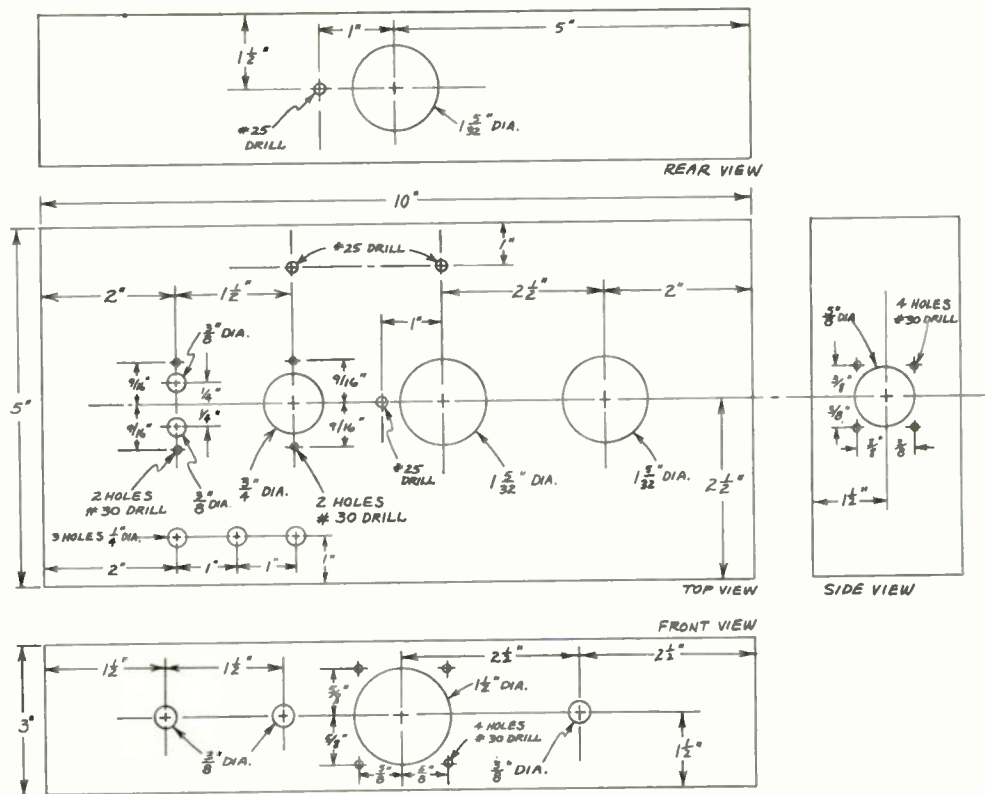

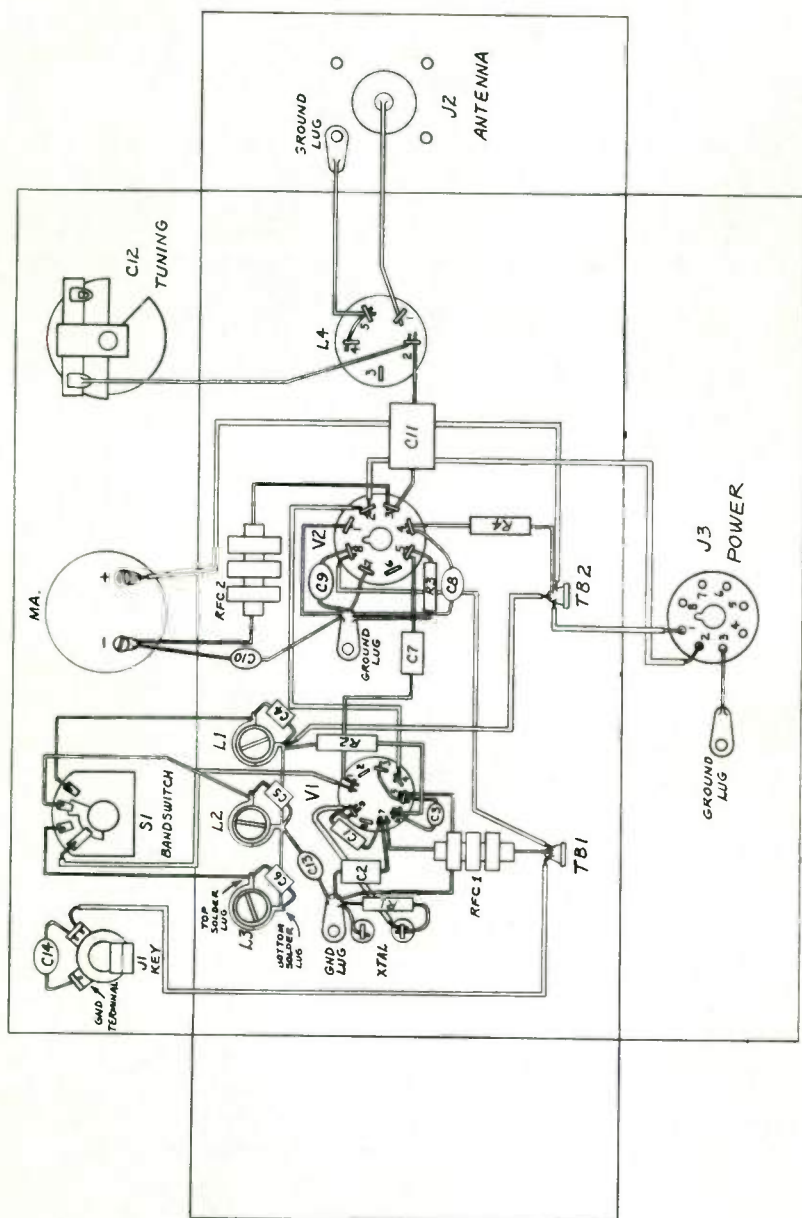


Fig. 3-4. Pictorial wiring diagram of the 3-band novice transmitter.

ets, meter, etc. by following the layout shown in Fig. 3-3. Coils L1, L2, and L3 are mounted under the chassis with the tuning screws sticking out of the top so that they can be conveniently tuned from the top side. Orient the coils as shown in the pictorial wiring diagram (Fig. 3-4). A detailed drawing of the coils is given in Fig. 3-5.

Orient the tube sockets, the socket for tank coil L4, and power plug J3 as shown in the pictorial diagram of Fig. 3-4. Use the numbers stamped on the bottom of the sockets and the plug as a guide. All the ground connections are made to ground lugs. Keep the leads as short as practical when mounting the resistors

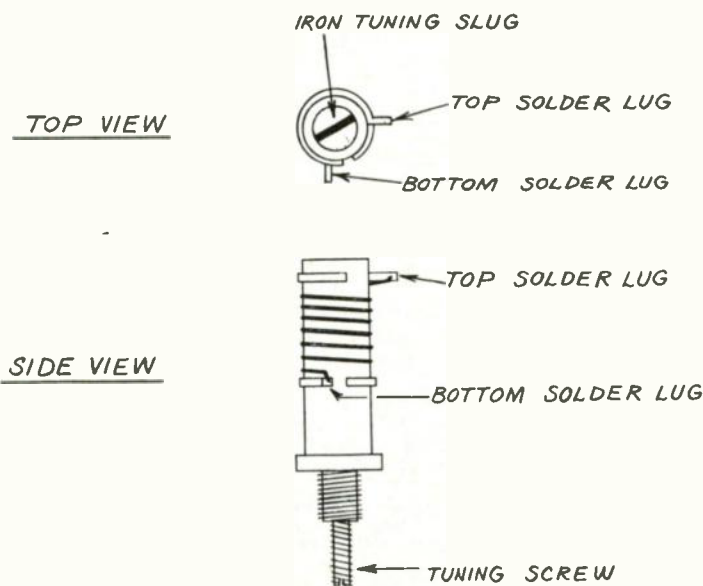


Fig. 3-5. Detailed drawing of slug-tuned coils.

and capacitors. Make sure the leads do not short to each other or to the chassis. Observe the polarities indicated in Fig. 3-1 and 3-4 when connecting to the meter. No. 18 or No. 20 bare, tinned-copper wire should be used for the leads from L4 to tuning capacitor C12, antenna jack J2, and to the ground lug. Make these connections direct, from point to point, keeping them as short as possible. A photo of the underside of the chassis is given in Fig. 3-6.

The slug-tuned coils (L1, L2, and L3) are available prewound; however, if you want to wind them yourself, the specifications for the 15- and 40-meter ones are listed in the parts list at end of

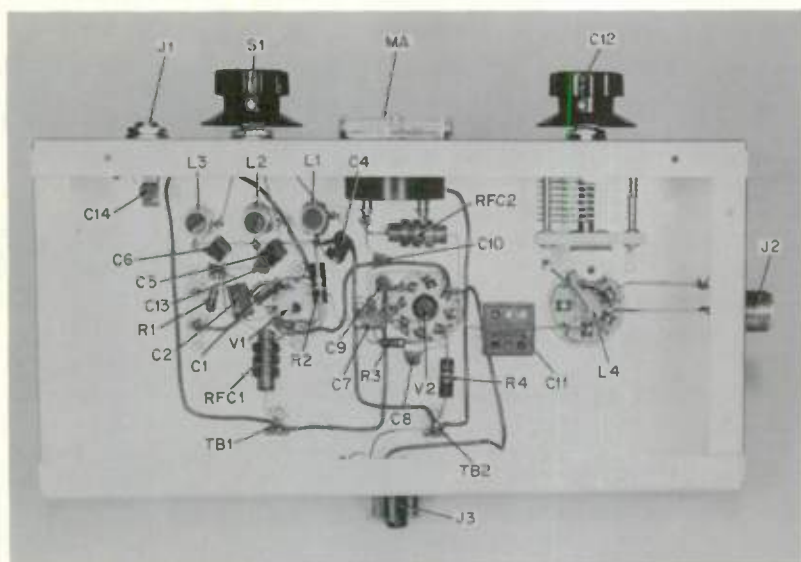


Fig. 3-6. Bottom view of the transmitter chassis.

this chapter. The 80-meter coil requires considerable inductance and is wound in a special manner to achieve a reasonable value of  $Q$  at the operating frequency; therefore, home construction of this coil should not be attempted. This coil is lattice or "pie," wound, with very fine Litz wire.

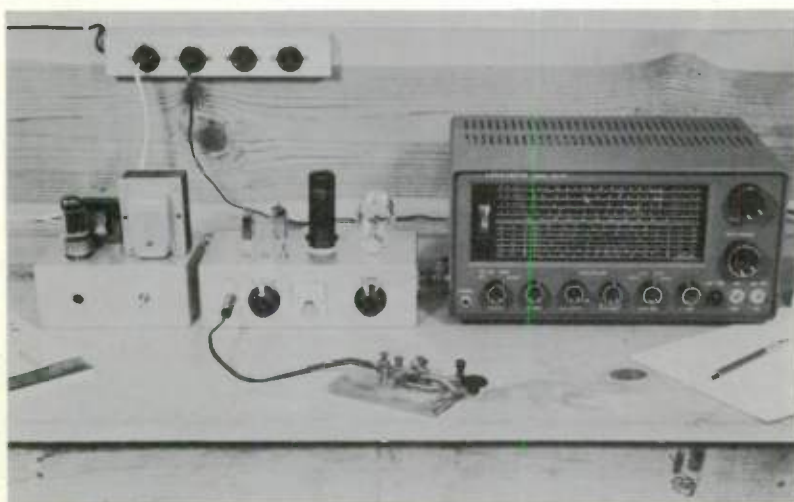


Fig. 3-7. Typical station setup.

## Tuning

A typical station setup is shown in Fig. 3-7. Use the power supply and the interconnecting cable described in Chapter 2 (or their equivalent) with this transmitter. This power supply delivers the needed voltage and has an adequate current capacity for the transmitter in this chapter.

Turn the power switch on, and allow the tubes to warm up for approximately a minute. Solder a length of hook-up wire to the center terminal in the base of a 50-watt light bulb, and hook this lead to antenna jack J2. Solder a second length of hook-up wire to the outer shell of the light-bulb base and hook this to transmitter ground (chassis). Plug an 80-meter crystal into the crystal socket and insert the 80-meter tank coil into its socket. Set the bandswitch to the 80-meter position. Close the key, and tune tuning capacitor C12 for a dip or minimum reading on the meter. Then adjust the 80-meter oscillator coil (L3) for a maximum indication on the meter. When the meter dips, the lamp should light up to about half its normal brilliance. The light should glow a little brighter when L3 is peaked to the operating frequency. Once L3 has been peaked, it does not have to be touched again. The only adjustment that has to be made is retuning C12 for a dip on the meter whenever the crystal frequency is changed. The slug-tuned coils are broad band; therefore, they do not require retuning within the band.

Repeat the foregoing procedure for the 40- and 15-meter bands, adjusting C13 for a dip and peaking L2 (40 meters) and L1 (15 meters). If a grid-dip meter is available, the slug-tuned coils can be set to the approximate operating frequency before this procedure is started.

## Operation

Connect the transmitter to a suitable antenna. The transmitter output will work most efficiently into an antenna with an unbalanced low-impedance line, such as a 50- or 72-ohm coaxial transmission line. Refer to Chapter 4 for suitable antennas, and for construction details on an all-band balun matching unit, which will give this rig added versatility for working into a variety of antenna types.

Without any load on the transmitter output (no antenna connected) the meter should dip to a very low value when C12 is tuned to resonance. When the antenna is connected, it should "load" the final; that is, the meter current reading will be higher at the point where C12 causes a dip in the meter reading.

To change bands, insert the appropriate crystal, change the bandswitch to the band desired, and plug in the tank coil for the band desired. Always dip the final tank circuit with C12 whenever you change frequencies within a band, or when you change bands.

### Parts List

| Quantity | Item No.                     | Description   |
|----------|------------------------------|---|
| 1        | C1                           | 20-mmf, 5%, 500V, silvered-mica capacitor.  |
| 1        | C2                           | 220-mmf, 5%, 500V, silvered-mica capacitor.   |
| 6        | C3, C8, C9,<br>C10, C13, C14 | .001-mfd, GMV, 1,000V, disc-ceramic capacitor.  |
| 1        | C4                           | 47-mmf, 5%, 500V, silvered-mica capacitor.  |
| 3        | C5, C6, C7                   | 100-mmf, 5%, 500V, silvered-mica capacitor.   |
| 1        | C11                          | 1,000-mmf, 5%, 500V, silvered-mica capacitor.   |
| 1        | C12                          | 7.1 to 102-mmf variable capacitor (E.F. Johnson 149-5 or equiv.).   |
| 1        | R1                           | 47,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R2                           | 22,000-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | R3                           | 18,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R4                           | 18,000-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | L1                           | 15 meters—0.9 to 1.6 $\mu$ h coil. (Miller 4403 or equiv., or 9 1/4 turns No. 28 enameled copper wire close-wound on 3/8" diameter powdered-iron slug coil form).                   |
| 1        | L2                           | 40 meters—3.1 to 6.8 $\mu$ h coil (Miller 4405 or equiv., or 18 1/4 turns No. 28 enameled copper wire close-wound on 3/8" diameter powdered-iron slug coil form).                   |
| 1        | L3                           | 80 meters—14.8 to 31 $\mu$ h coil (Miller 4407 or equiv.).  |
| 3        | L4                           | Tank coils with end links:<br>15 meters (B & W Type JEL, No. 3102 or equiv.).<br>40 meters (B & W Type JEL, No. 3104 or equiv.).<br>80 meters (B & W Type JEL, No. 3105 or equiv.). |
| 2        | RFC1, RFC2                   | 2.5 mh RF choke (National R-50, Miller 4666 or equiv.).   |
| 1        | S1                           | 1-pole, 3-position rotary switch (Centralab 1461 or equiv.).  |
| 3        | Xtal                         | 15 meters—10.55 to 10.625 mc crystal.<br>40 meters—7.150 to 7.200 mc crystal.<br>80 meters—3.700 to 3.750 mc crystal.   |
| 1        | V1                           | 5763 beam-power tube.   |
| 1        | V2                           | 6L6 beam-power output tube.   |
| 1        | J1                           | Standard phone jack.  |
| 1        | J2                           | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).   |
| 1        | J3                           | Octal chassis-mount plug (Amphenol 86-CP8 or equiv.).   |
| 1        | MA                           | 0-100 DC miniature milliammeter (Lafayette TM-403 or equiv.).   |
| 2        | TB1, TB2                     | 1-lug terminal strips (Cinch-Jones Type 51 or equiv.).  |
| 1        |                              | Crystal socket (Millen 33102 or equiv.).  |
| 1        |                              | 9-pin miniature ceramic tube socket (Millen 33409 or equiv.).   |

### Parts List—cont'd

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        |          | Octal ceramic tube socket (Amphenol 49-SS8 or equiv.).                     |
| 1        |          | 5-pin ceramic tube socket (Amphenol 49-SS5 or equiv.).                     |
| 2        |          | Knobs (E.F. Johnson 116-221 or equiv.).                                    |
| 4        |          | Solder lugs  |
| 1        |          | 5" X 10" X 3" aluminum chassis (Bud AC-404, Cal-Chassis A-103, or equiv.). |
|          |          | 4-40 machine screws and nuts.  |
|          |          | 6-32 machine screws and nuts.  |
|          |          | Hook-up wire.  |
|          |          | Solder.  |



## 4 Balun Antenna Matching Unit

The center-fed, half-wave dipole is probably the most popular low-frequency amateur antenna. A good deal of its popularity stems from the fact that a dipole is a basic antenna which is simple to construct and easy to install. Even more, it is easy on the pocketbook! Properly tuned, this antenna makes a very efficient radiator for RF energy.

The center-fed dipole is inherently a balanced antenna. The transmission (feed) line is tied in at the center of the antenna; thus, both halves of the antenna are symmetrical with respect to the transmission line. In order to maintain this symmetry, particularly with respect to earth ground, this type of antenna must be fed with a balanced transmission line.

Running a balanced transmission line to a balanced antenna keeps unbalanced currents from appearing on the line. Unbalanced currents in a transmission line give rise to undesired radiation from the line. This radiation is in addition to the desired radiation from the antenna proper.

Most of today's transmitters, such as the units described in this book, and most commercially available rigs run single-ended outputs; that is, one side of the output circuit is grounded. Thus, the transmitter output is unbalanced. Grounding one side of the output circuit in a transmitter is usually desirable because it reduces radiations which might cause TVI (television interference). Some means, then, must be provided to couple the unbalanced transmitter output to the balanced transmission line of the balanced antenna. One method of doing this is with a coil-type balun.

The balun unit described in this chapter is a wide-band device; it will work on all frequencies from 3 to 30 mc without the need for tuning. Therefore, once it has been installed, it can be forgotten. The balun unit provides a means for coupling the unbalanced transmitter output to the balanced transmission line. Also, it acts as an impedance transformer at RF frequencies and, depending on how the coils are hooked up, will provide impedance ratios of 1 to 1, or 1 to 4. Thus, it can be used to couple a transmitter whose output impedance might nominally be 75 ohms, to an

antenna having a 75-ohm transmission line, or one having a 300-ohm transmission line.

It must be kept in mind that a coil-type balun will not correct for deficiencies elsewhere in the antenna system: i.e., if the transmission line is not properly matched to the antenna. Figs. 4-1 and 4-2 illustrate typical dipole antennas.

### Dipole Antennas

The basic half-wave dipole antenna is shown in Fig. 4-1. For all practical purposes the radiation resistance at the center of a half-wave dipole is in the order of 70 ohms. A close enough match is provided by a 72-ohm, twin-lead transmission line to the center point of the antenna. The antenna "top" is made from No. 14 enameled or bare-copper wire. Lighter or heavier wire may be used; however, No. 14 is recommended as the best compromise between weight and strength. Insulators are used on both ends of the antenna, and another one is inserted at the midpoint. The ends should be suspended as high as possible. The transmission line between the antenna and the transmitter can be as long as needed since its length is not critical.

If 72-ohm, twin-lead transmission line is not available, ordinary AC cord (zip cord) or a simple twisted pair can be used as a tem-

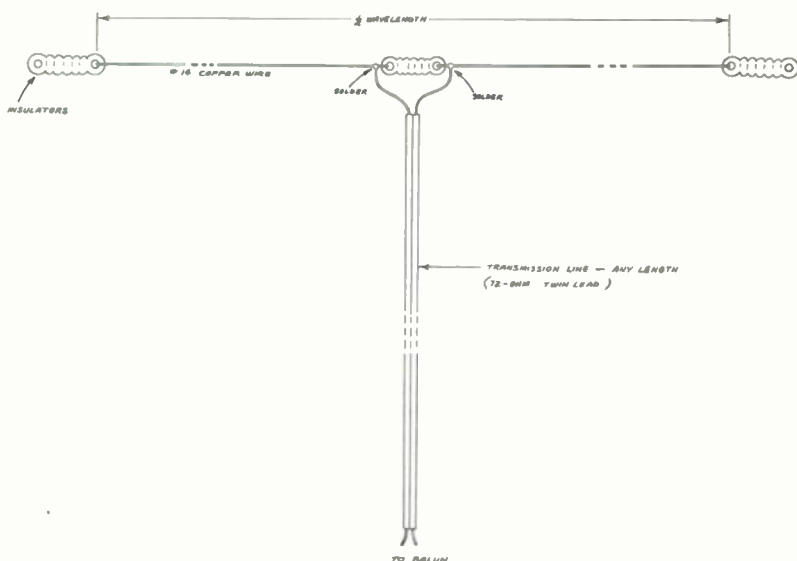


Fig. 4-1. Basic dipole antenna, fed with 72-ohm twin lead.



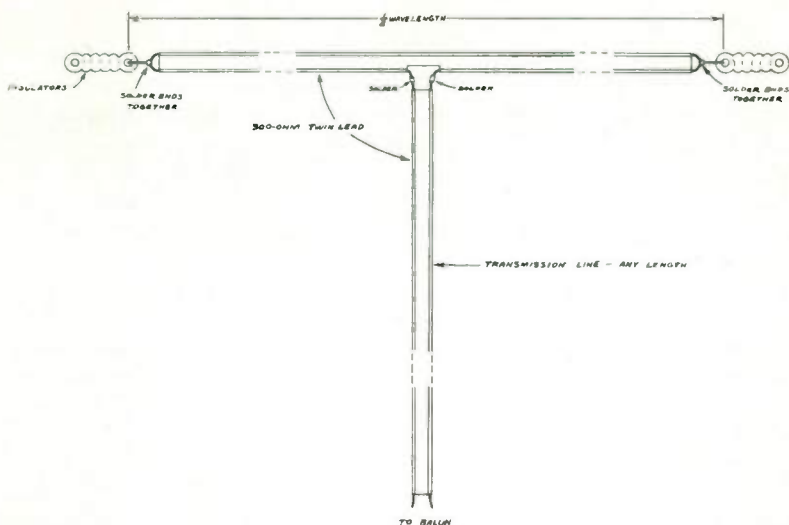


Fig. 4-2. Folded-dipole antenna constructed of 300-ohm twin lead.

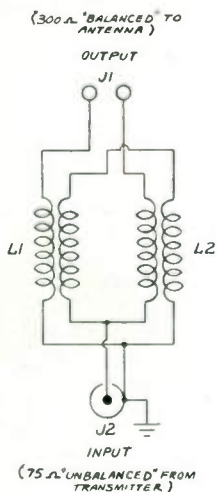porary measure. The characteristic impedances of these lines are approximately 70 ohms. When using a temporary line of this nature, operation should be restricted to low-power transmitters. Any of the transmission lines mentioned provide the balanced dipole with a balanced feed line.



(A) 75- to 300-ohm.

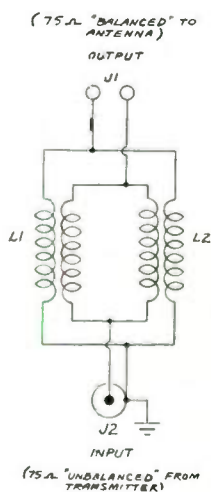

(B) 75- to 75-ohm.

Fig. 4-3. Schematic of the two wiring configurations for the balun.

The 300-ohm folded dipole makes a very efficient antenna for the lower frequency bands. Such an antenna (Fig. 4-2) can be constructed from the ordinary 300-ohm twin lead used extensively as the feed line for TV antennas. Such an antenna is available for only pennies a foot!

Both the antenna proper and the transmission line in Fig. 4-2 are made of 300-ohm line. As before, the transmission line can be any length. The conductors at each end of the top part are soldered together and fastened to insulators. One of the conductors is broken at the center of the top section, and the resulting two ends are soldered to the conductors of the transmission line.

The one-half wavelength dimensions for both antennas (Figs. 4-1 and 4-2) are as follows:

80 meters — 136 ft.

40 meters — 66 ft.

15 meters — 22 ft.

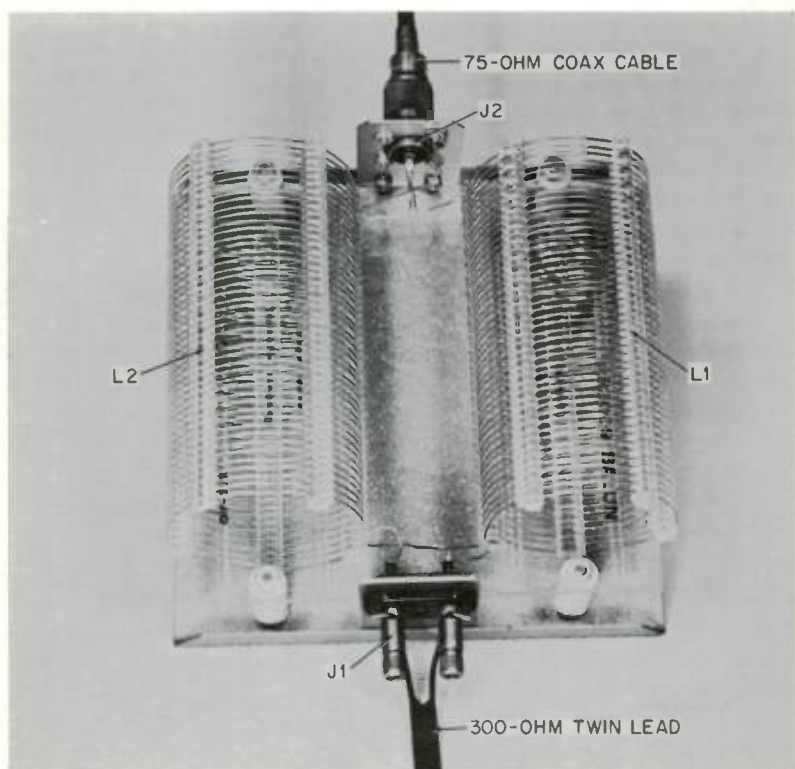


Fig. 4-4. Photo of the completed balun unit.

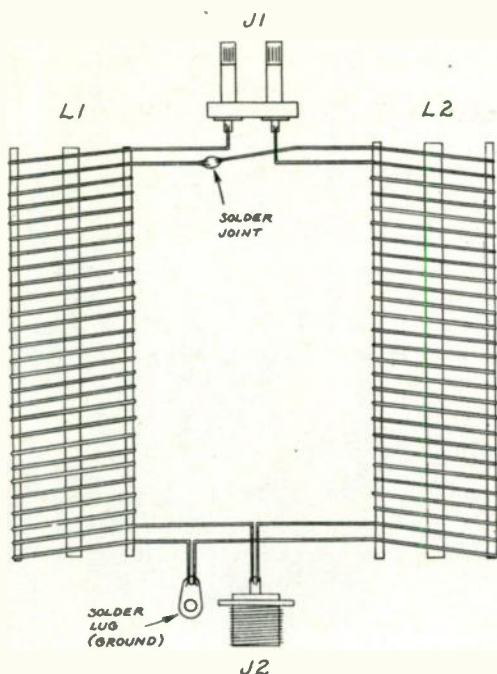


Fig. 4-5. Pictorial wiring diagram of balun unit. This unit corresponds to Fig. 4-3A.

These dimensions are approximate and represent values which fall in about the middle of each band. The actual value for a half-wave antenna for any amateur band between 10 and 80 meters can be calculated from the following equation:

$$\text{Length (feet)} = \frac{468}{\text{Freq. (mc)}}$$

The values derived from this equation will be adequate for all practical purposes.

### The Balun

The coil-type balun is shown schematically in Fig. 4-3. Fig. 4-3A shows the hook-up of the balun coils for coupling the unbalanced 75-ohm output of a transmitter to a 300-ohm balanced transmission line. This configuration provides an impedance transformation of 1 to 4 and will work in conjunction with the 300-ohm folded dipole in Fig. 4-2. Fig 4-3B shows the hook-up of the balun coils for coupling the unbalanced 75-ohm output of a transmitter to a balanced 72-ohm transmission line. This configuration is designed

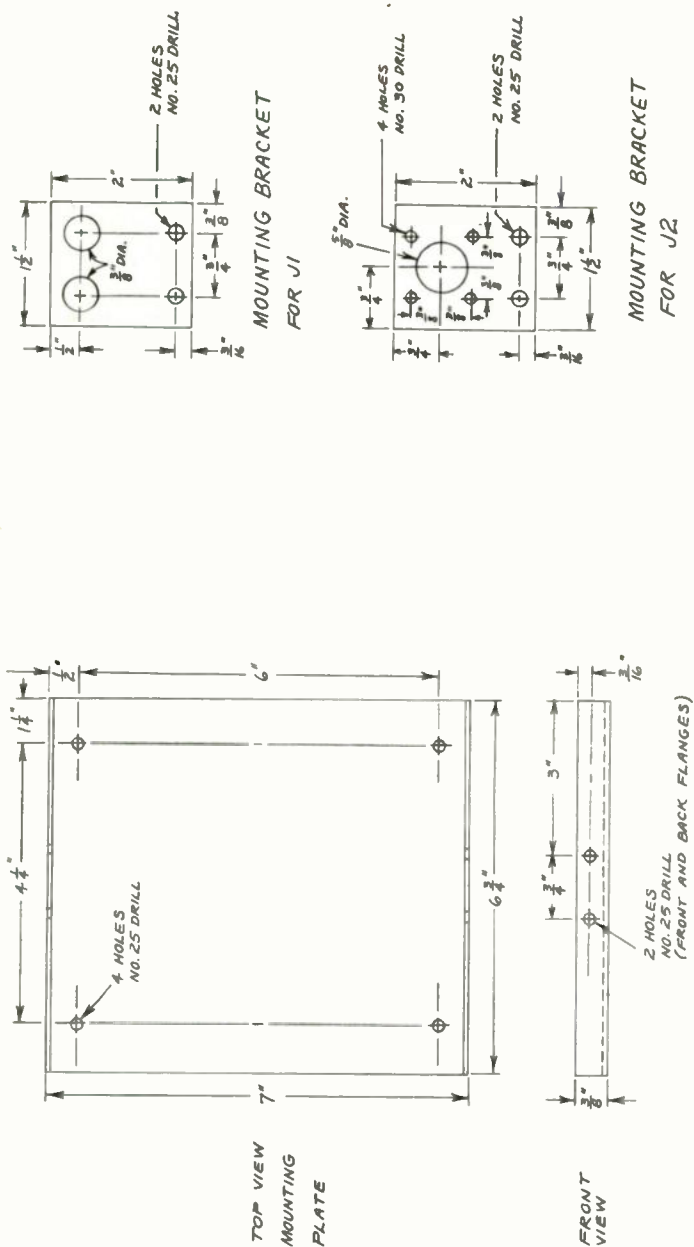


Fig. 4-6. Mounting plate layout and hole-drilling guide.

for the straight dipole of Fig. 4-1. In this case the balun offers an impedance transformation of 1 to 1.

The balun consists of two identical coils (L1 and L2). Each coil is actually two coils in one, wound in a bifilar fashion. A bifilar coil is made by placing two conductors side by side and simultaneously winding them into a coil while keeping the spacing between the turns constant. Thus, the completed coil has two leads at each end. Complete winding data for the balun coils is given in the parts list at the end of this chapter, if you feel brave enough to wind your own. The coils are commercially available already wound. A photo of a completed balun unit with commercial coils is shown in Fig. 4-4.

The unit shown in Fig. 4-4 was wired to operate into a 300-ohm, twin-lead transmission line. The coils are mounted on a plate fabricated from a piece of sheet aluminum. The wiring is shown pictorially in Fig. 4-5, which corresponds to the schematic diagram in Fig. 4-3A. The chassis layout is given in Fig. 4-6.

The balun unit is connected to the transmitter with a short piece of coax cable, which connects to J2. The antenna is connected to binding-post-type connector J1.

Dipole antennas are not the only antennas which can be used with the transmitters described in this book. There are many other types. The antennas described in this chapter were chosen as a convenience to the beginner, and also to point out the method for properly matching an unbalanced transmitter to a balanced antenna. The balun unit can be used with other antennas.

### Parts List

| Quantity | Item No. | Description   |
|----------|----------|---|
| 2        | L1, L2   | Bifilar-wound coil [Illumintronic Engineering No. B2009 Air Dux Balun or equiv., or constructed as two separate interwound coils, 23 turns per subcoil (46 turns per coil assembly) of No. 20 tinned-copper wire, wound 2½ inches in diameter and spaced to a 5-inch length, with constant spacing between all coil turns]. |
| 1        | J1       | Binding post connection (National FWH or equiv.).   |
| 1        | J2       | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).   |
| 1        |          | Solder lug.   |
| 1        |          | Piece sheet aluminum for coil mount (6" X 6¾" with ¾" lip).   |
| 2        |          | 1½" X 2" pieces of sheet aluminum for J1 and J2 mounting brackets.  |
| 4        |          | Ceramic standoff insulators.  |
|          |          | 6-32 machine screws and nuts.   |
|          |          | 4-40 machine screws and nuts.   |
|          |          | Solder.   |

# Crystal-Controlled

## 5 Converters for 10, 15, or 20 Meters

The crystal-controlled converter described here makes an excellent "front end" for low-frequency war surplus receivers or for some of the older communications receivers. Surplus receivers have been available at very reasonable prices for a number of years; when used in conjunction with the converter described in this chapter, the combination offers inexpensive, yet high-performance, receiving equipment for the higher frequencies. A common ailment among the older communications receivers is oscillator drift at the higher frequencies. If a crystal-controlled converter is used ahead of the receiver, it can be used as a tunable IF at the lower frequencies, where it tends to be more stable. The inherent stability of the crystal in the converter is thus utilized, thereby saving the old receiver from the "junk pile."

The self-powered converter circuit is shown in Fig. 5-1. It is completely self contained, including its own AC power supply. This arrangement is more convenient than having to tap into the receiver or some other external power supply. To cut costs, however, the power supply can be omitted, and power can be obtained elsewhere. In either instance, the converter requires 150 volts DC at approximately 35 milliamperes and 6.3 volts AC at 0.625 ampere.

This converter offers an inexpensive, yet high-quality, means for the novice to receive 15-meter CW signals. When used along with a low-frequency receiver, the converter provides the necessary stability required for CW reception at the higher frequencies.

### Circuit Description

V1 is a 6AK5 RF pentode and serves as the RF amplifier. Grid coil L2 and plate coil L3 both resonate in the received band. Both are slug-tuned coils with suitable bandpass characteristics to allow reception over the entire band without having to be retuned. The signal is coupled into grid coil L2 from the antenna



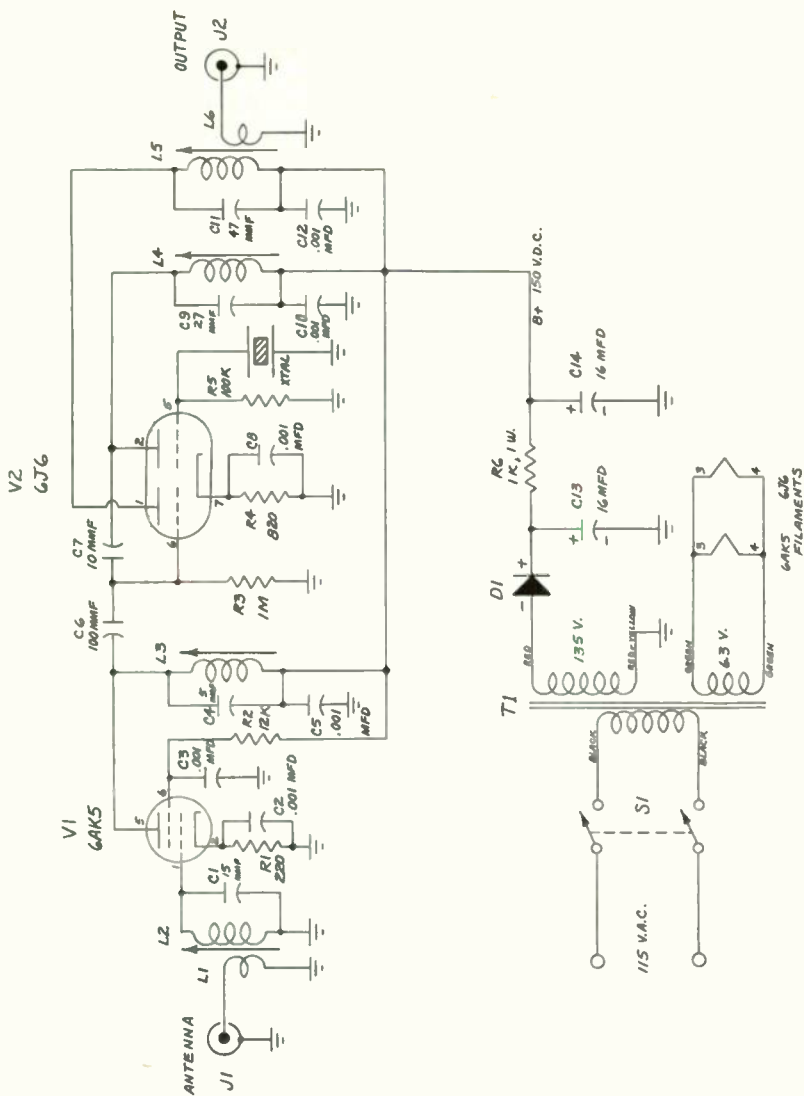


Fig. 5-1. Schematic of the converter, including built-in power supply.

by means of a two-turn link (L1) wound around the ground end of the grid coil.

One section of the 6J6 dual-triode tube serves as a crystal-controlled oscillator and the other section as the mixer. Another slug-tuned coil (L4) is tuned to the crystal frequency. The generated oscillator signal is coupled into the grid of the mixer via a 10-mmf ceramic capacitor (C7). Here the oscillator signal and the amplified incoming signal are mixed; the resulting IF (intermediate frequency) signal appears across the mixer plate coil (L5). L5 resonates at the IF frequency and a link (L6) couples the signal from L5 to the receiver.

### IF Frequency

The IF output frequency of the converter is in the 7-mc region. In Fig. 5-2, the converter is shown hooked up to a surplus "Command" receiver. This receiver is typical of the surplus receiver types available. It covers a frequency range of 6 to 9.1 mc, and makes an excellent tunable IF section for the converter. Of course, any receiver with coverage in the 7-mc IF region will do.

The IF frequency is the difference between the incoming signal frequency and the crystal frequency. For example, 10-meter reception requires a 21-mc crystal. A signal being received at 28 mc in the converter appears at 7 mc on the receiver. The upper end of the 10-meter band, which is 29.7 mc, would appear at 8.7 mc

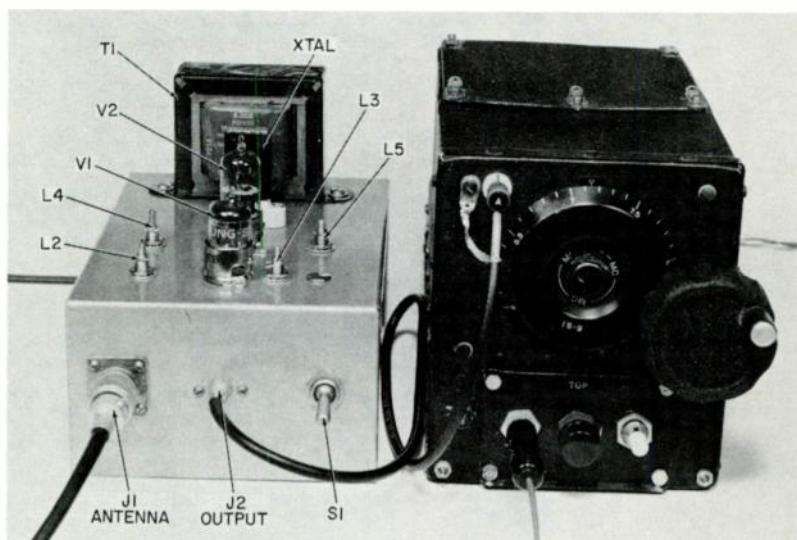


Fig. 5-2. The converter hooked up to a surplus command receiver.

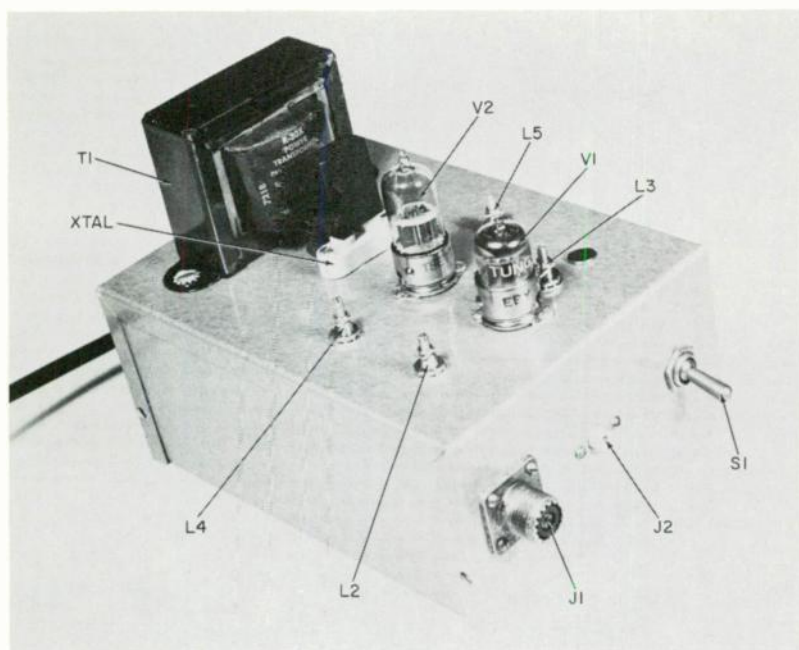


Fig. 5-3. Location of major components on converter chassis.


on the receiver ( $29.7 \text{ minus } 21.0 = 8.7$ ). Therefore the 10-meter band is tuned from 7.0 to 8.7 mc on the receiver serving as the tunable IF.

For 15-meter reception a crystal frequency of 14 mc is required. The limits of the 15-meter band are 21.0 to 21.45 mc; therefore, the receiver is tuned from 7.0 to 7.45 mc. The 20-meter band lies between 14.0 and 14.35 mc, and the crystal frequency required is 7 mc. The IF receiver tunes from 7.0 to 7.35 mc in this case.

Output coil L5 is a slug-tuned coil tuned to the IF output frequency. It is a fairly broadband coil; once it has been tuned to the approximate center of the IF tuning range, it does not require retuning from one end of the IF range to the other.
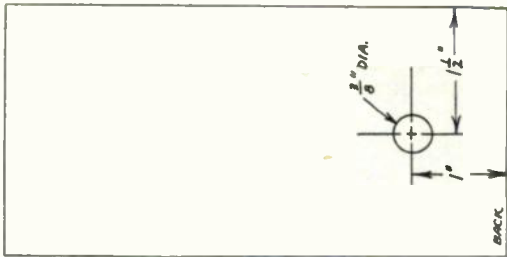
### Construction

The converter is housed in a 7" by 5" by 3" aluminum chassis box (Fig. 5-3). If the components given in the parts list at the end of this chapter are used, follow the hole location drawing in Fig. 5-4 and make all the holes necessary to mount the components. After the holes have been completed, mount the major components, such as the tube sockets, slug-tuned coils, transformer, etc.



World Radio History

A top view of the completed chassis is given in Fig. 5-5. Orient these parts as shown in the pictorial wiring diagram (Fig. 5-6). The links (L1 and L6) should be wound around their respective coils prior to installing the coil. Fig. 5-7 illustrates the method of winding the link around the coil; the end of the coil on which the link should be wound is given in the coil data found in the parts list. Coil tuning capacitors C1, C4, C9, and C11 are all silvered mica capacitors soldered directly across the coil terminals. It might be easier to solder these across the coils before installing them.

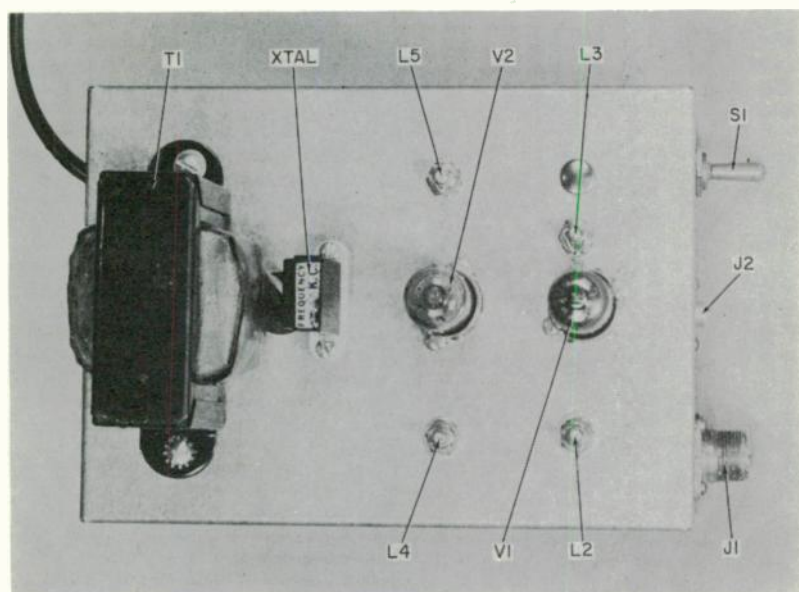


Fig. 5-5. Top view of the converter.

The .001 bypass capacitors are all small disc ceramics ( $\frac{1}{4}$ -inch diameter); only this type should be used. They were chosen because their small size and inherently low series inductance make them ideal for RF bypassing at high frequencies.

The unit should be wired by following both the schematic diagram (Fig. 5-1) and the pictorial wiring diagram (Fig. 5-6). A piece of zip cord (AC power cord) should be run in through the  $\frac{3}{8}$ -inch rubber grommet located on the rear panel of the chassis, knotted directly inside the box, and soldered to the power switch S1 as shown in Fig. 5-8. The knot serves as a "strain relief" for the power cord, preventing an accidental pull on the cord from breaking the soldered connections on the switch.

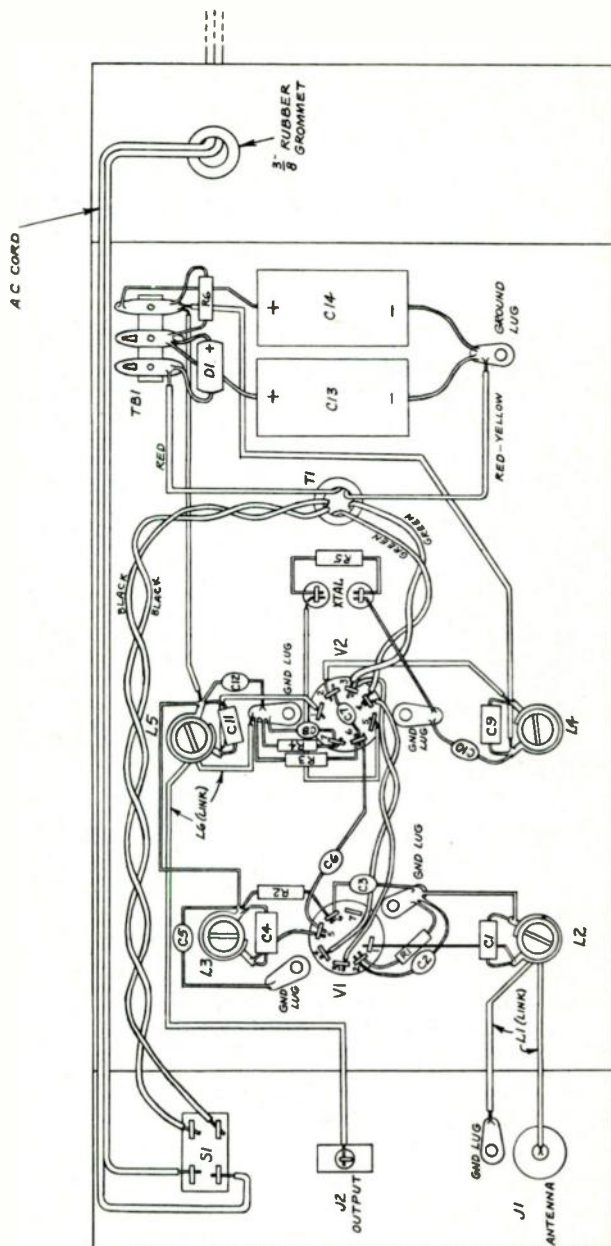


Fig. 5-6. Pictorial wiring diagram of the converter.

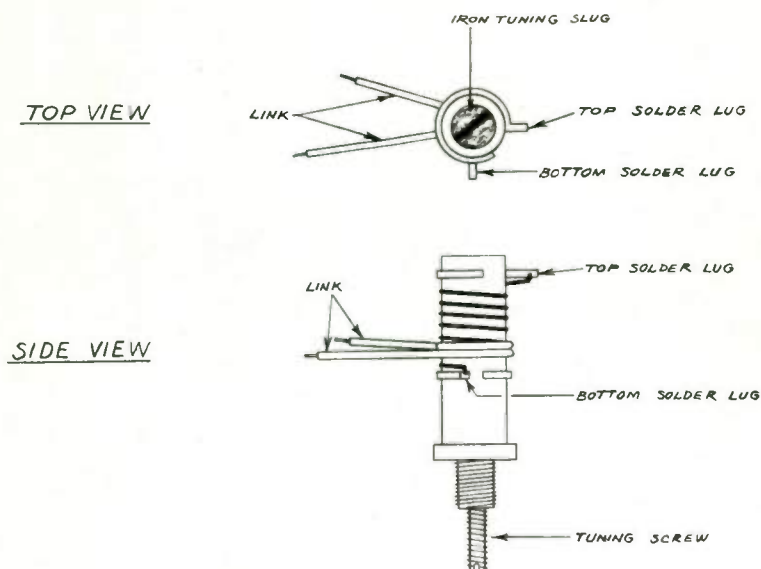


Fig. 5-7. Detailed drawing of slug-tuned coils and coupling link.

The leads from the power transformer are also run into the box through a  $\frac{3}{8}$ -inch rubber grommet, located on the top of the box. Twist the two black leads together, run them along the edge of the chassis to the power switch, and solder them. The black leads are the AC input leads to the transformer. Also twist the green filament leads together and solder them to the respective tube-socket pins as shown in the diagrams.

When wiring the power supply, be sure to observe the polarity of the silicon rectifier (D1) and electrolytic capacitors C13 and C14. The leads of the resistors and capacitors should all be kept as short as possible. Also, when wiring the small components, avoid overheating them during the soldering operation—they can easily be damaged.

### Converter Alignment

Before you attempt to "fire up" the converter, recheck the wiring to make sure no mistakes have been made. Make sure that none of the leads are shorting to ground or to other leads.

Turn the power switch on and let the filaments warm up for approximately a minute. Insert a VOM or VTVM between the junction of R6 and C14 and ground to check the high voltage. The measured voltage should be approximately 150 volts DC.



The next step is to set up the oscillator. If a general coverage receiver is available, tune it to the crystal frequency. A signal should be heard at that spot. Tune L4 for maximum signal in the receiver. If a receiver is not available, the coil can be tuned to the crystal frequency with the aid of a grid-dip meter. With the converter turned off, the coil is resonated in the conventional manner by watching for a "dip" in the grid-dip meter indication when the coil is tuned to the proper frequency. The grid-dip meter can also be used in the wave-meter mode of operation. The converter is turned on, and the signal from the oscillator is detected by the grid-dipper. L4 is then tuned for a maximum indication on the meter.

Once the oscillator has been peaked, the remainder of the converter can be aligned. The converter should now be hooked up to the receiver, which is going to serve as the tunable IF. A short piece of shielded cable should be used from the converter to the receiver. The shielded wire will keep out signals that would normally be received at the IF frequency.

A signal located approximately in the middle of the band on which the converter has been wired to receive should now be run into the converter. The signal can come from a signal generator, a grid-dip meter, or from a friend across town who operates on the band which the converter receives. Of course, if using an "on-the-air" signal, an antenna should be hooked up to the converter.

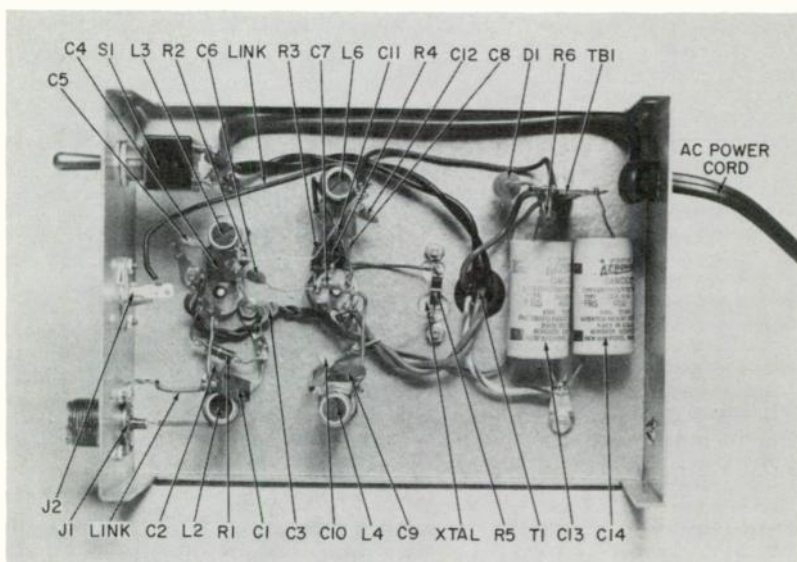


Fig. 5-8. Bottom view of chassis.



Tune coils L2, L3, and L5 for a maximum signal output from the receiver. If the receiver is equipped with an S meter, the alignment will be much easier. Simply tune for a maximum indication on the meter.

Hook an antenna up to the converter, and it's ready for operation!

### Parts List

| Quantity | Item No.                    | Description   |
|----------|-----------------------------|---|
| 1        | C1                          | 15-mmF, 5%, 500V silvered-mica capacitor.   |
| 6        | C2, C3, C5,<br>C8, C10, C12 | .001-mfd GMV, 1,000V, 1/4-inch dia. disc-ceramic capacitors.  |
| 1        | C4                          | 5-mmF, 5%, 500V silvered-mica capacitor.  |
| 1        | C6                          | 100-mmF, 10%, 1,000V disc-ceramic capacitor.  |
| 1        | C7                          | 10-mmF, 10%, 1,000V disc-ceramic capacitor.   |
| 1        | C9                          | 27-mmF, 5%, 500V silvered-mica capacitor.   |
| 1        | C11                         | 47-mmF, 5%, 500V silvered-mica capacitor.   |
| 2        | C13, C14                    | 16-mfd, 450VDC, electrolytic capacitors.  |
| 1        | R1                          | 220-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R2                          | 12,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R3                          | 1-megohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R4                          | 820-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R5                          | 100,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R6                          | 1,000-ohm, 1-watt, 10%, carbon resistor.  |
| 1        | L1                          | 2-turn link of small hook-up wire wound around grounded end of L2 (see Fig. 5-7).   |
| 2        | L2, L3                      | <p><b>10 meters</b>—0.9 to 1.6 <math>\mu</math>h, set for 1.2 <math>\mu</math>h (Miller 4403 or equiv., or constructed by 9 1/4 turns of No. 24 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p> <p><b>15 meters</b>—1.5 to 3.2 <math>\mu</math>h, set for 2.5 <math>\mu</math>h (Miller 4404 or equiv., or constructed of 12 1/4 turns of No. 26 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p> <p><b>20 meters</b>—3.1 to 6.8 <math>\mu</math>h, set for 5.5 <math>\mu</math>h (Miller 4405 or equiv., or constructed by 18 1/4 turns of No. 28 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p> |
| 1        | L4                          | <p><b>10 meters</b>—0.9 to 1.6 <math>\mu</math>h, set for 1.2 <math>\mu</math>h (Miller 4403 or equiv., or constructed of 9 1/4 turns of No. 24 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p> <p><b>15 meters</b>—1.5 to 3.2 <math>\mu</math>h, set for 2.2 <math>\mu</math>h (Miller 4404 or equiv., or constructed of 12 1/4 turns of No. 26 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p> <p><b>20 meters</b>—6.7 to 15 <math>\mu</math>h, set for 10 <math>\mu</math>h (Miller 4406 or equiv., or constructed of 26 1/4 turns of No. 32 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).</p>   |

## Parts List—cont'd

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | L5       | 6.7 to 15 $\mu$ h, set for 8 $\mu$ h (for 7-mc output) (Miller 4406 or equiv., or constructed by 26 $\frac{1}{4}$ turns of No. 32 enameled copper wire closewound on $\frac{3}{8}$ " diameter slug-tuned coil form). |
| 1        | L6       | 2-turn link of small hook-up wire wound around B+ end of L5 (see Fig. 5-7).  |
| 1        | T1       | Power transformer—Secondaries; 135 VAC @ 50 ma; 6.3 VAC @ 1.5A (Triad R-30X, Merit P-3045, Stancor PA-8421, or equiv.).  |
| 1        | S1       | DPST toggle switch.  |
| 1        | Xtal     | Crystal (International Crystal Type FA-9 or equiv.) Frequencies: 10 meters, 21 mc; 15 meters, 14 mc; 20 meters, 7 mc.  |
| 1        | D1       | Silicon rectifier (Sarkes Tarzian 2F4 or equiv.).  |
| 1        | V1       | 6AK5 RF pentode.   |
| 1        | V2       | 6J6 Dual triode.   |
| 1        | J1       | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).  |
| 1        | J2       | Shielded phono jack (Allied Radio 46 H 213, Lafayette MS-168, or equiv.).  |
| 1        | TB1      | 3-lug terminal strip (Cinch-Jones Type 53 or equiv.).  |
| 1        |          | Crystal socket. (Millen Type 33102 or equiv.).   |
| 6        |          | Solder lugs.   |
| 1        |          | Shielded phono plug (Allied Radio 46 H 212, Lafayette MS-167, or equiv.).  |
| 2        |          | 7-pin miniature tube sockets (Amphenol Type 147-913 or equiv.).  |
| 1        |          | 7" X 5" X 3" aluminum chassis (Bud CU-2108 or equiv.).   |
| 2        |          | $\frac{3}{8}$ " rubber grommets.   |
| 1        |          | AC power cord (length as needed).  |
| 1        |          | AC power plug.   |
|          |          | 6-32 machine screws and nuts.  |
|          |          | 4-40 machine screws and nuts.  |
|          |          | Hook-up wire.  |
|          |          | Solder.  |

# 6 6-Meter, Crystal-Controlled Converter

The 6-meter converter described in this chapter has several desirable design features: (1) it incorporates an extremely low-noise tube as an RF amplifier, (2) it is crystal controlled for exceptional stability, (3) the design is straightforward for ease of construction, (4) neutralizing the RF amplifier is very simple, and (5) it is inexpensive to build.

For fixed-station operation the converter works into any receiver that covers the 7-mc region. Any of the popular war-surplus receivers which cover that frequency region or any general-coverage communications receiver can be used. A built-in power supply eliminates the need for tapping into the receiver for power; however, the power supply can be omitted if desired. Power requirements are conservative, and the necessary voltages can be obtained from the receiver without any problem.

The converter circuit is ideal for mobile applications. However, since the converter is designed to work into a 7-mc IF, it must work into a 7-mc mobile converter, which, in turn, works into the car radio. There are two important reasons for not running the 6-meter converter directly into the car radio and using the broadcast band as the variable IF. First and foremost is the fact that images become a problem. Second, only a 1-mc portion of the 6-meter band could be tuned. For mobile use the AC power supply is left out, and the converter is packaged into a smaller box. Power for the converter can be tapped from the car radio, or a transistorized DC-DC inverter can be built.

## Circuit Description

The circuit for the 6-meter converter, and the AC power supply, is given in Fig. 6-1. A signal from the antenna is link-coupled by L1 to the grid coil (L2) of V1. The link consists of 1 turn of small hook-up wire wound around the ground end of L2, as shown in the schematic diagram. L2 is a slug-tuned coil that resonates with the input capacity of V1 and the C1-C2 combination in the 50-mc or a transistorized DC-DC inverter can be built.

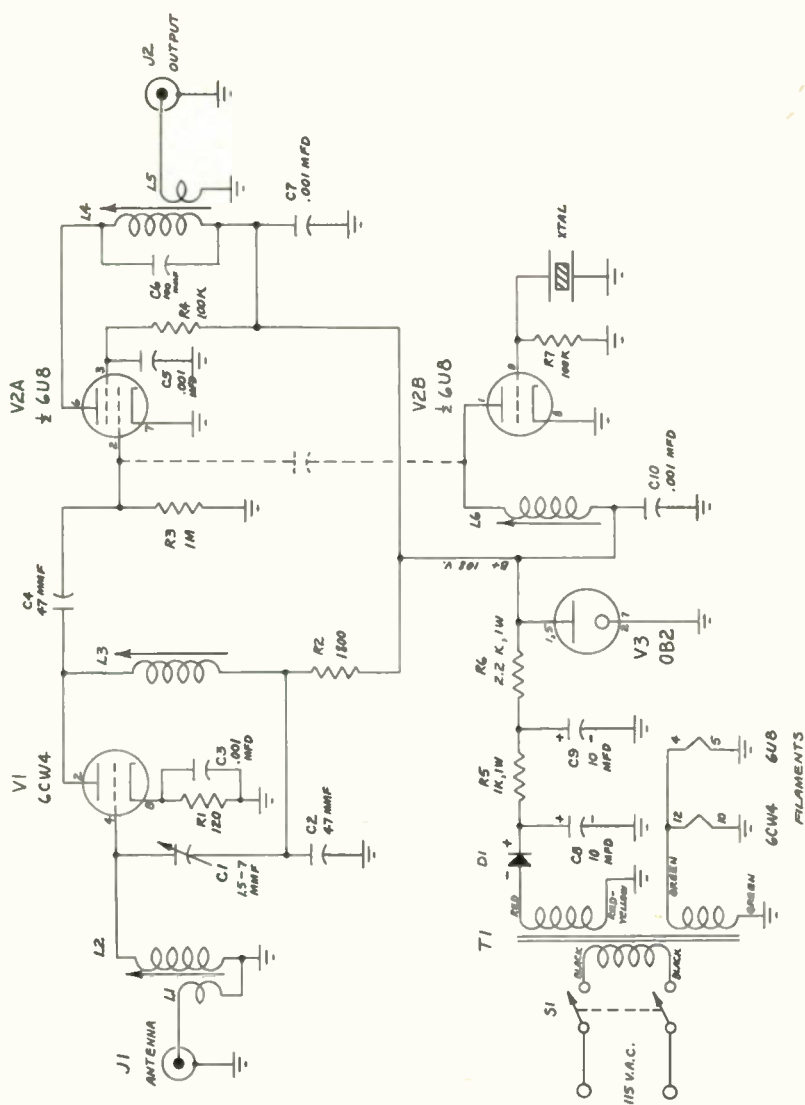


Fig. 6-1. Schematic of the low-noise 6-meter converter.

50 mc. C1 and C2 act as an RF voltage divider and form a capacitive-type neutralizing network between the plate and grid of V1 to keep the stage from oscillating. Once C1 has been set, it needs no further adjustment. Coils L2 and L3 exhibit broad-band characteristics, however, it is impossible to make their bandpass broad enough for the 6-meter band (50 to 54 mc, or a 4-mc bandwidth) and still maintain a reasonable Q for the coils. Therefore, these coils are peaked in the lower half of the band. If you intend to operate mostly in the upper portion of the band, the coils must be repeaked for the upper half.

A special low-noise high- $\mu$  triode is utilized for the RF amplifier (V1). It is a type 6CW4, commonly known as a *Nuvistor*. The amplified 50-mc signal from V1 is capacitively coupled to the grid of mixer V2A—the pentode section of a 6U8 triode-pentode.

The triode section of the 6U8 serves as the crystal-controlled oscillator; its output is mixed at the grid of the mixer along with the amplified 50-mc signal to form the IF signal. The IF frequency is the difference between the incoming signal frequency and the crystal frequency. The author used a third-overtone type 44.000-mc crystal. Using the crystal frequency specified, the IF tuning range is actually 6 to 10 mc. (50 mc minus 44 mc = 6 mc, and 54 mc minus 44 mc = 10 mc). The output frequency can be shifted to meet individual requirements, and a crystal other than the 44-mc one can be substituted. For instance, a 43.000-mc crystal will produce an IF tuning range of 7 to 11 mc.

The mixer plate coil (L4) is tuned to the IF region. It is also a broad-band, slug-tuned coil, and as in the case of L2 and L3, it is peaked in the lower half of the IF tuning range. It must be retuned to the upper portion of the IF tuning range if reception in the upper half of the 6-meter band is desired. The converter output signal is link-coupled through L5 to the input of the receiver. L6 is tuned to the crystal frequency only.

A coupling capacitor between the oscillator-plate circuit and the mixer grid has been intentionally left out. Since both halves of the 6U8 are in the same glass envelope, their proximity along with associated circuitry provides enough coupling for oscillator injection into the mixer.

The power supply is conventional in all respects. A small instrument power transformer is used, and a silicon diode serves as a half-wave rectifier. C8, R5, and C9 form a pi-section RC filter and R6 is a current-limiting resistor for the voltage-regulator tube (V3). If the AC power supply is left out, R6 and V3 should remain in the circuit. If this is done, then any voltage from 150 to 250 VDC can be applied to R6, yet the output voltage for the converter from V3 will remain at a constant 108 volts.

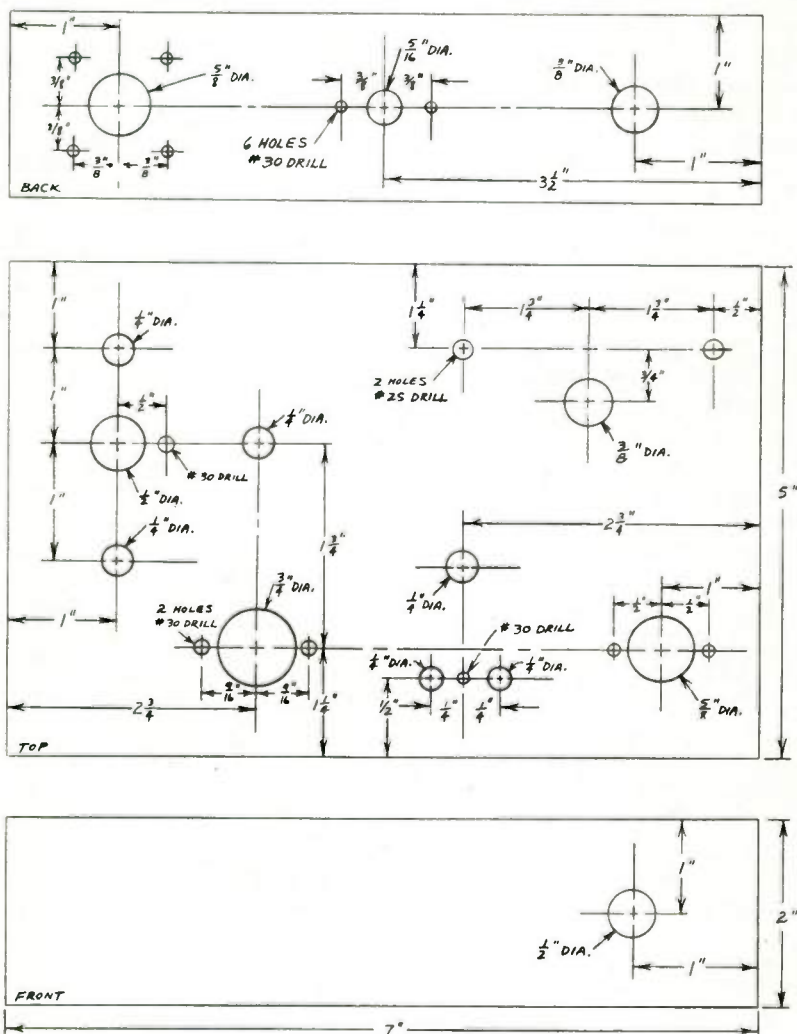


Fig. 6-2. Chassis layout and hole-drilling guide.

## Construction

A 5" by 7" by 2" aluminum chassis houses the converter circuitry. If the device is constructed for mobile operation, a small aluminum chassis box can be used instead. Fig. 6-2 serves as a guide for locating and making the required mounting holes. Fig. 6-3 shows the components mounted on the chassis.

The 6CW4 *Nuvistor* requires a special socket which mounts into a  $\frac{1}{2}$ -inch hole. The socket has two small tabs which must be bent over against the chassis to hold it in place. Two small slots must be filed along opposite sides of the  $\frac{1}{2}$ -inch mounting hole to clear the mounting tabs.

Mount the major components, such as tube sockets, coils, etc., orienting them according to the pictorial diagram in Fig. 6-4. Coil links L1 and L5 should be wound around their respective coils prior to installation of the coils. Be sure to wind the links on the proper end of the coil winding, as designated in the schematic diagram. The proper manner for placing the link around the coil was shown in Fig. 5-7.

Direct, point-to-point wiring is used for the RF circuitry. All RF lead lengths must be kept as short as possible, especially for

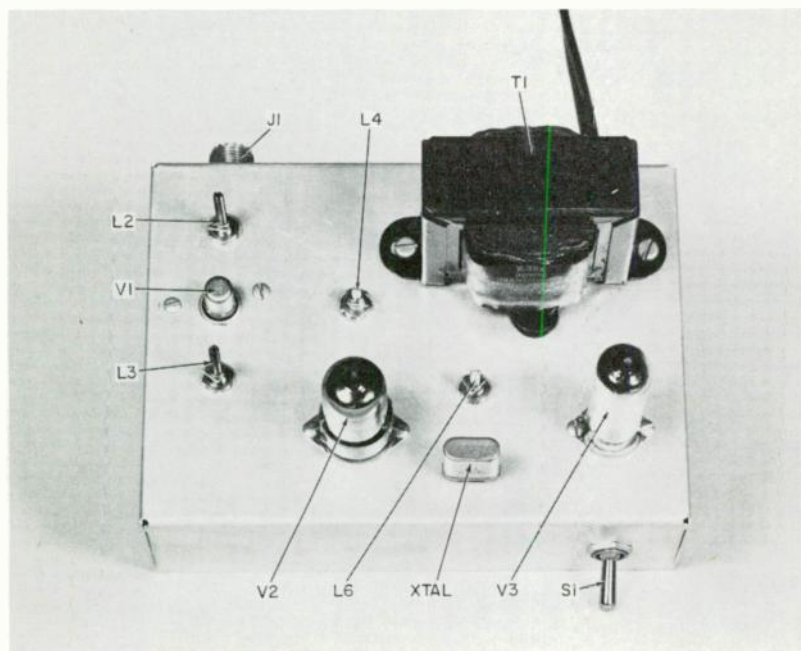


Fig. 6-3. Top view of the converter.

Wire the circuit by following the schematic diagram (Fig. 6-1) and the pictorial diagram (Fig. 6-4). Run the AC cord through





the  $\frac{3}{8}$ -inch rubber grommet on the rear of the chassis and up to the power switch (S1). The cord should be run along the edge of the chassis away from the converter circuitry. Put a knot in the power cord directly inside the chassis to keep it from accidentally being pulled off the soldered connections on S1. A bottom view of the completed chassis is given in Fig. 6-5.

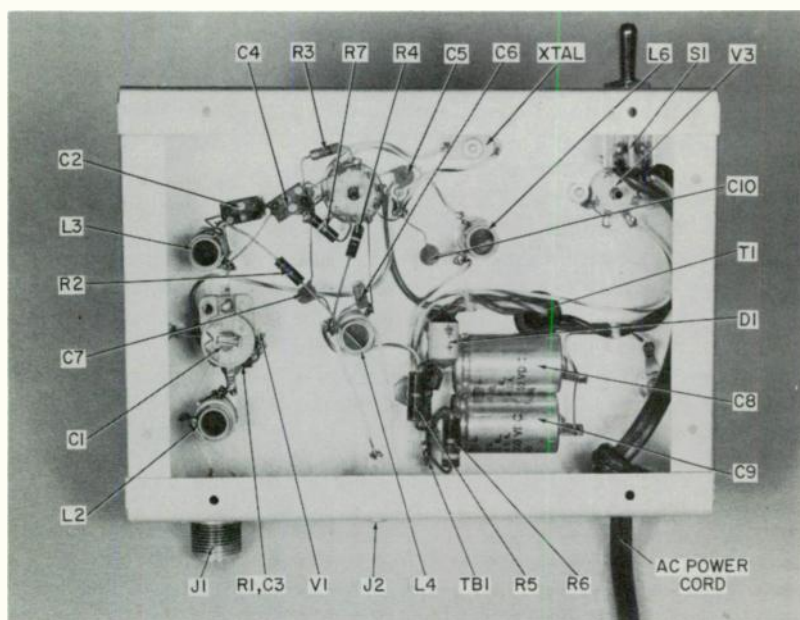


Fig. 6-5. Bottom view of the converter.

The leads from the power transformer are also run into the chassis through a  $\frac{3}{8}$ -inch rubber grommet. R5, R6, and D1 are mounted on a five-lug terminal strip; one of the lugs is a ground terminal. Observe the polarity of the silicon rectifier and C8 and C9 when wiring them into the circuit. Avoid overheating any of the components when soldering to them—they can easily be damaged.

### Aligning and Neutralizing the Converter

Check the circuit to make sure it has been wired properly before turning the power on. Also make sure no leads are shorting together or to ground. Turn the power on; the voltage regulator tube should light up immediately. Check the voltage across V3 (from the plate to ground) with a VOM; it should read 108

volts. If this voltage checks out properly, continue with the rest of the test.

Let the tubes warm up for several minutes before proceeding with the alignment of the converter. If a grid-dip meter is available, it is a good idea to set the coils first. L2 and L3 should be tuned to around 51 mc, and L4 should be set to approximately 8 mc. With the converter turned on, the oscillator should be oscillating. Switch the grid-dipper to the wavemeter mode of operation, and tune L6 for a maximum indication on the meter. If a grid-dip meter is not available and you can borrow a 6-meter receiving setup, tune the oscillator coil for the loudest signal heard in the receiver.

Once the coils have been approximately set to the proper frequencies, the next step is to neutralize the RF amplifier (V1). Remove the filament lead from V1, and couple a signal into the converter. This test signal can come from a grid-dip meter, signal generator, nearby 6-meter transmitter, or even a signal from another 6-meter station across town. In the latter case, an antenna will have to be connected to the converter.

Connect the converter to the receiver with a short piece of shielded cable (Fig. 6-6). The shielded cable will prevent stray signals at the IF frequency from getting into the receiver. With a 6-meter signal going into the converter, adjust C1 for minimum

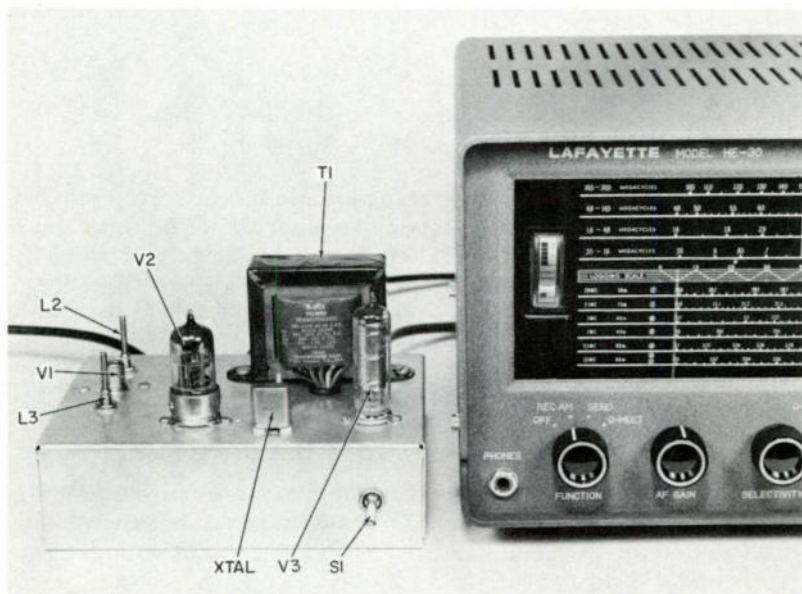


Fig. 6-6. Converter connected to a communications receiver.

signal output from the receiver, or minimum indication on the receiver S meter. There will be a sharp dip in the signal strength when the proper point in the tuning range of C1 is reached. The stage is now neutralized. Attach the filament lead once more to V1. **Warning:** remove the converter power cord from the AC outlet when removing and replacing the V1 filament lead to avoid getting a shock from the B+ or from the AC line. The converter is now ready for final alignment.

With the 6-meter signal still being fed into the converter, peak L2, L3, and L4 for a maximum signal in the receiver. The converter is now ready for operation.

### Parts List

| Quantity | Item No.        | Description  |
|----------|-----------------|--|
| 1        | C1              | 1.5 to 7-mmF, ceramic-trimmer capacitor (Centralab Type 822-EZ or equiv.).   |
| 2        | C2, C4          | 47-mmF, 5%, 500V, silvered-mica capacitors.  |
| 4        | C3, C5, C7, C10 | .001-mfd GMV, 1,000V, disc-ceramic capacitors.   |
| 1        | C6              | 100-mmF, 5%, 500V, silvered-mica capacitor.  |
| 2        | C8, C9          | 10-mfd, 350VDC, electrolytic capacitors.   |
| 1        | R1              | 120-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R2              | 1,800-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R3              | 1 megohm, 1/2-watt, 10%, carbon resistor.  |
| 2        | R4, R7          | 100,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R5              | 1,000-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | R6              | 2,200-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | L1              | 1-turn link of small hook-up wire wound around ground end of L2.   |
| 3        | L2, L3, L6      | 0.9 to 1.6 $\mu$ h coils (Miller 4403 or equiv., or constructed of 9 1/4 turns of No. 24 enameled copper wire closewound on 3/8" diameter slug-tuned coil form). |
| 1        | L4              | 3.1 to 6.8 $\mu$ h coil (Miller 4405 or equiv., or constructed of 18 1/4 turns of No. 28 enameled copper wire closewound on 3/8" diameter slug-tuned coil form). |
| 1        | L5              | 1-turn link of small hook-up wire wound around B+ end of L4.   |
| 1        | T1              | Power transformer—Secondaries: 135 VAC @ 50 ma.; 6.3 VAC @ 1.5A (Triad R-30X, Merit P-3045, Stancor PA-8421, or equiv.).   |
| 1        | S1              | DPST toggle switch.  |
| 1        | Xtal            | 44,000 third-overtone type crystal (International Crystal Type FA-5 or equiv.).  |
| 1        | D1              | Silicon rectifier (Sarkes Tarzian 2F4 or equiv.).  |
| 1        | V1              | 6CW4 "Nuvistor" triode.  |
| 1        | V2              | 6U8 triode-pentode tube.   |
| 1        | V3              | OB2 voltage-regulator tube.  |
| 1        | J1              | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).  |

## Parts List—cont'd

| Quantity | Item No. | Description   |
|----------|----------|---|
| 1        | J2       | Shielded phono jack (Allied Radio 46 H 213, Lafayette MS-168, or equiv.). |
| 1        | TB1      | 5-lug terminal strip (4 insulated terminals, 1 ground terminal).          |
| 1        |          | Crystal socket (Millen 33302 or equiv.).                                  |
| 6        |          | Solder lugs.  |
| 1        |          | Shielded phono plug (Allied Radio 46 H 212, Lafayette MS-167, or equiv.). |
| 1        |          | "Nuvistor" tube socket (Cinch-Jones Type 5NS or equiv.).                  |
| 1        |          | 9-pin miniature tube socket (Amphenol 59-406 or equiv.).                  |
| 1        |          | 7-pin miniature tube socket (Amphenol 147-500 or equiv.).                 |
| 1        |          | 5" X 7" X 2" aluminum chassis (Bud AC-402, Cal-Chassis A-101, or equiv.). |
| 2        |          | $\frac{3}{8}$ " rubber grommets.  |
| 1        |          | AC power cord (length as required).                                       |
| 1        |          | AC power plug.  |
|          |          | 6-32 machine screws and nuts.   |
|          |          | 4-40 machine screws and nuts.   |
|          |          | Hook-up wire.   |
|          |          | Solder.   |

# 7 Low-Noise, Crystal-Controlled, 2-Meter Converter

Because of the crowded condition of the low-frequency amateur bands, interest in the VHF-UHF regions of the radio spectrum has grown in recent years. Also, activity in the 2-meter amateur band has increased with the opening of the band to novice- and technician-class amateurs, as well as the general-class operators already operating there. The frequency limits of the 2-meter band are 144 to 148 mc, making a total of 4 mc available to the general-class amateur. Novice- and technician-class operators are allowed to operate in a 2-mc portion of the band: 145 to 147 mc.

A 6CW4 *Nuvistor* is used as an RF amplifier in the converter to be constructed in this chapter. This tube is responsible for the low-noise characteristics of the converter. The "state of the art" in VHF-UHF techniques had advanced in recent years. The low-noise *Nuvistor* is an example of the low-cost, low-noise tubes now available for work in this region. The *Nuvistor* was originally

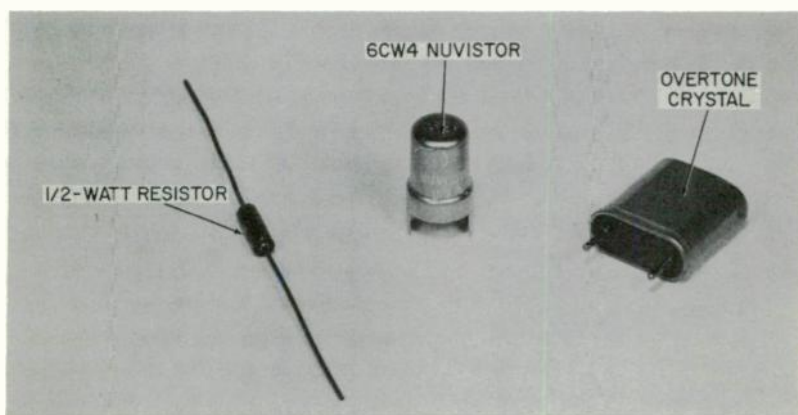


Fig. 7-1. The 6CW4 "Nuvistor" compared in size to an ordinary 1/2-watt resistor and a Type FA-5 overtone crystal.

developed for use in TV tuners; however, since its exceptionally low-noise qualities were enhanced by an equally low price tag, it was quickly adopted by ham circuit designers. A close-up view of the 6CW4 is shown in Fig. 7-1, along with a  $\frac{1}{2}$ -watt resistor and a Type FA-5 overtone crystal to illustrate its small size. The tube is enclosed in a metal shield can.

Besides having an extremely low-noise front end, the converter is crystal controlled for exceptional stability. It is designed to work into any receiver that covers the 7-mc region—the IF output frequency of the converter. Any general-coverage communi-

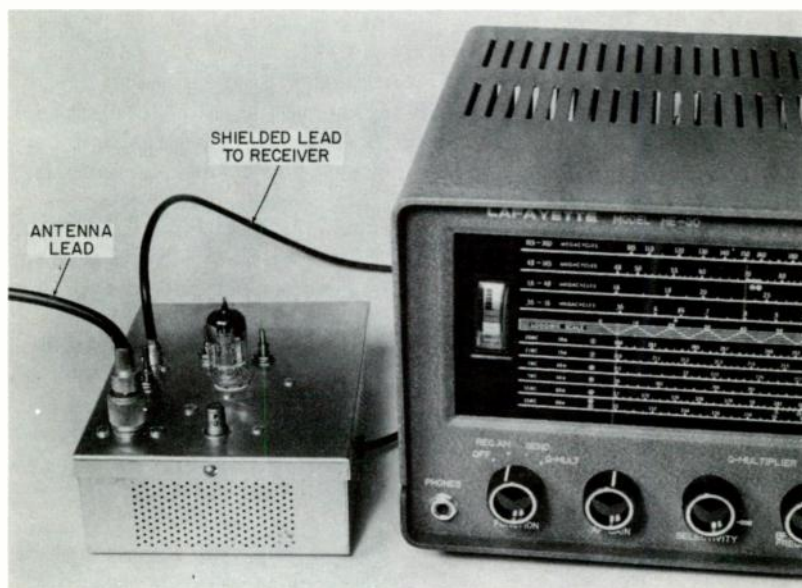


Fig. 7-2. The converter connected to a communications receiver.

cations receiver will do the job, or any of the popular war surplus receivers covering the 7-mc region can be used. In any case, a shielded lead is used between the converter output and the receiver input to keep any 7-mc signals from entering the receiver through the interconnecting cable. The photo in Fig. 7-2 shows the completed converter hooked up to a typical general-coverage communications receiver.

The converter is completely self-contained, including its own built-in AC power supply. This eliminates the need to tap into the receiver or another external supply for power. If desired, the power supply can be eliminated. Power requirements for the converter are nominal: 6.3 VAC at approximately 0.6 ampere for the



filaments, and 150 VDC at approximately 30 milliamperes for B+ requirements.

Mobile operation is fairly popular on the 2-meter band; the circuit given in this chapter is suitable for mobile applications. If used in mobile applications, power can be supplied by the car radio or an external transistorized DC-DC inverter. Without the power supply shown in the accompanying diagrams, the converter can be repackaged into a much smaller enclosure and mounted under the dash. As explained in Chapter 6, it is not desirable to run such a converter directly into the broadcast band for an IF frequency. Images become a problem when this is done, therefore, the 2-meter converter should be run into a "ham-band" converter which covers the 7-mc region.

### How It Works

Fig. 7-3 shows the schematic of the converter and the AC power supply. V1 is the 6CW4 Nuvistor RF amplifier. The signal from the antenna is coupled to the tap on grid coil L1. L1 resonates in the 2-meter band with the stray capacity in the circuit and the input capacity of the tube. Plate coil L3 resonates with the output capacity of the tube in the 2-meter band. A copper shield is used to isolate the grid circuit from the plate circuit. L2, a subminiature, slug-tuned coil, serves as the neutralizing coil; once it has been set, it requires no further adjustment, unless the tube is changed.

The triode section of a 6U8 (V2A) serves as the mixer. The mixer grid coil (L5) resonates at 2-meters with the input capacity of the tube. L4 is a 2-turn link wound around the B+ end of L3; it couples the amplified incoming signal to the tap on L5. The output coil (L6) is tuned to the IF output frequency in the 7-mc region, and the 3-turn link (L7) couples the output signal to the receiver via the output jack (J2).

The pentode section of the 6U8 (V2B) serves as the crystal-controlled local oscillator. This oscillator employs a circuit not commonly found; however, it is ideal for use with overtone crystals, and especially where multiples of the overtone frequency are desired. A self-resonant, slug-tuned coil is connected to the screen grid. This coil (L8), is tuned to 45.666 mc—the crystal frequency. The plate coil (L9) is tuned to a frequency three times that of the crystal frequency, or approximately 137 mc. The IF frequency is equal to the difference between the incoming signal (144 mc) and the oscillator output frequency (137 mc), or 7 mc. Therefore the IF tuning range is 7 to 11 mc (144 minus 137 = 7 mc, and 148 minus 137 = 11 mc). The IF output frequency can be

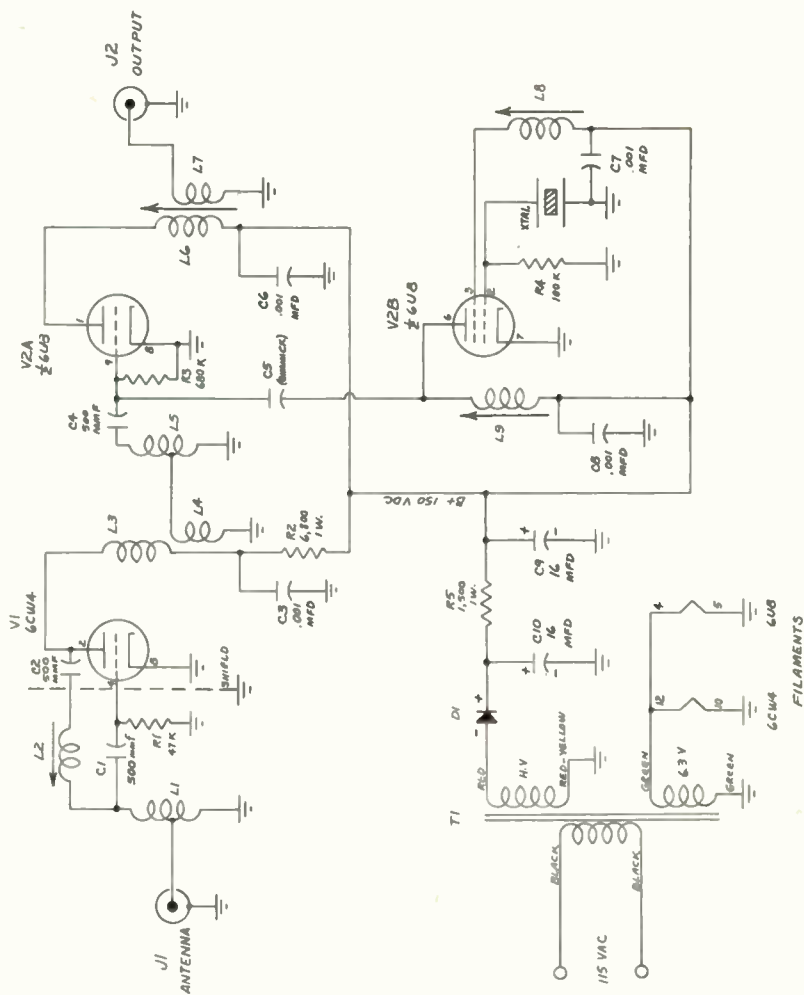


Fig. 7-3. Schematic of the crystal-controlled 2-meter converter.



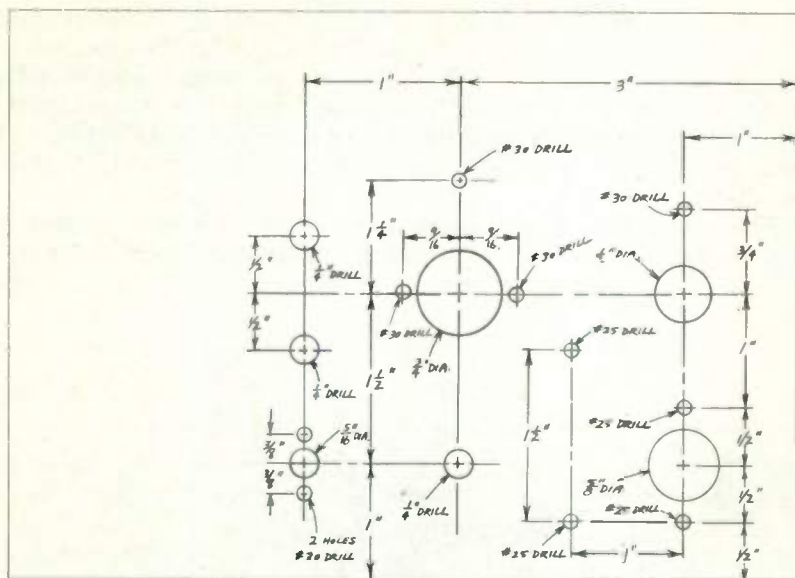


Fig. 7-4. Chassis cover layout and hole-drilling guide.

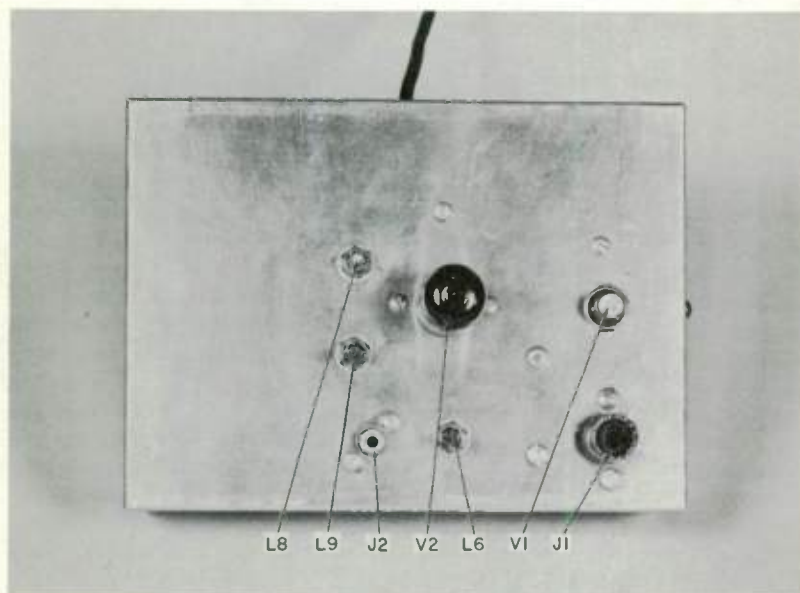


Fig. 7-5. Top view of the converter showing location of components.

shifted to meet individual requirements simply by changing the crystal frequency and retuning coils L6, L8, and L9. The oscillator output signal is coupled to the mixer via gimmick capacitor C5. This capacitance is formed by twisting two pieces of insulated hook-up wire together (making sure the wire ends do not touch each other), each piece of wire should be approximately 1 inch in length.

The power supply is conventional. A small instrument power transformer is employed for the high voltage and filament power.

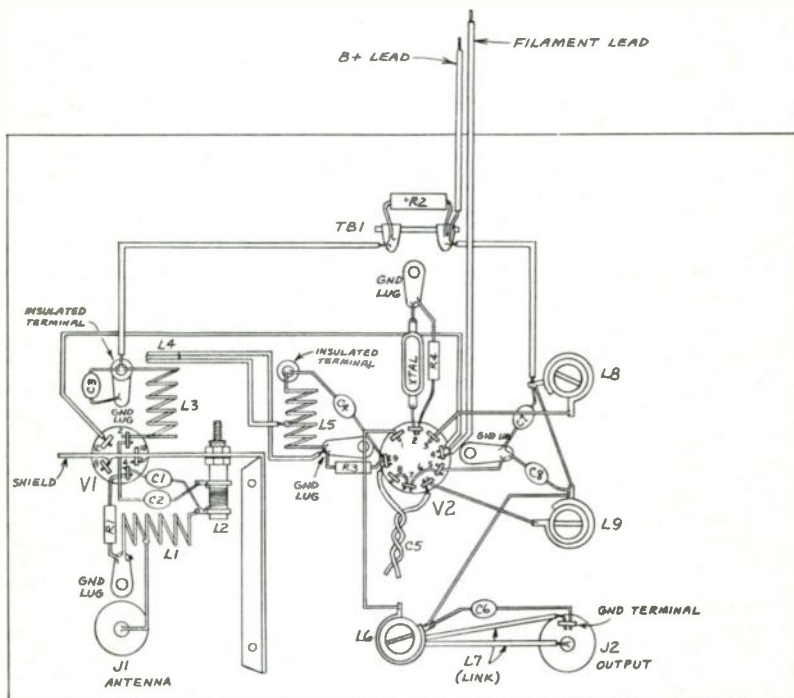


Fig. 7-6. Pictorial wiring diagram of the converter section.

A silicon rectifier (D1) serves as a half-wave rectifier and C9, C10, and R5 form a pi-section RC filter.

No power on-off switch is employed in the circuit of Fig. 7-3. This was not an oversight; the switch was intentionally left off. Many communications receivers have an accessory AC outlet on their rear deck which is controlled by the receiver power switch. If your receiver has an accessory AC outlet you can merely plug the converter into this outlet and the receiver switch will control both the converter and the receiver. If your receiver has no ac-

cessory outlet, an on-off switch should be added in the primary circuit of the power transformer.

### Construction

A special 5" by 7" by 2" aluminum chassis with cap cover (Fig. 7-2) is used to house and completely shield the converter. If such a chassis is not available in your area, an ordinary aluminum chassis with the same dimensions can be substituted. The chassis is inverted to serve as the base and a top cover is made from alumi-

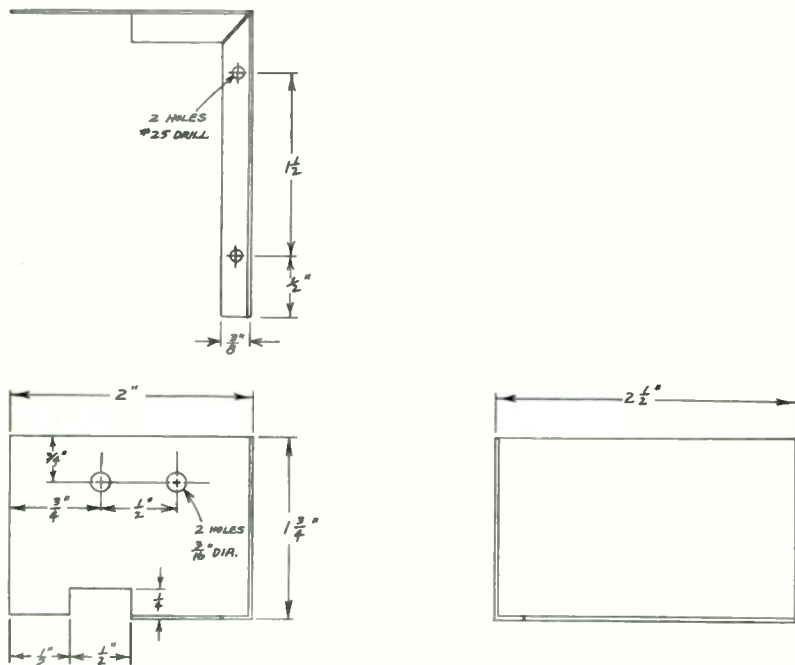


Fig. 7-7. Detailed drawing of the copper shield.

num sheet stock. For mobile applications a smaller chassis box will serve the purpose.

The RF circuitry is constructed on the top cover. The hole locations are given in Fig. 7-4, and Fig. 7-5 shows a top view of the completed chassis. A special socket which mounts into a  $\frac{1}{2}$ -inch hole is required for the 6CW4 tube. Two slots must be filed on opposite sides of the mounting hole to allow two small tabs on the socket to clear. These tabs are then bent over against the chassis to hold the socket in place.

The major components are mounted and oriented as shown in the pictorial diagram in Fig. 7-6. Link coil L7 is wound around the B+ end of L6, prior to installing L6. The method of winding and positioning of the link was given in Fig. 5-7. Be sure to mount the *Nuvistor* tube socket with the pins pointing in the direction shown in Fig. 7-6. The copper shield shown in Fig. 7-7 is installed so that one side runs down the middle of the *Nuvistor* socket. Pins 8 and 10 are soldered directly to the copper shield. Capacitor C2 is run through a hole in the shield—make sure the capacitor leads do not short out to the shield. Coil L2 is mounted on the shield assembly.

Follow the pictorial wiring diagram in Fig. 7-6 and the photo of Fig. 7-8 as a guide, and use direct, point-to-point wiring in the RF section. Keep the lead lengths as short as possible, particularly the RF bypass capacitor leads. Small disc-ceramic capacitors ( $\frac{1}{4}$ -inch diameter) should be used by RF bypasses (0.001 mfd). Their small size and low series inductance make them ideal at these high frequencies.

The power supply is built into the chassis base. The components in the power supply and the RF circuit components in the top cover are arranged so that they clear each other when the top

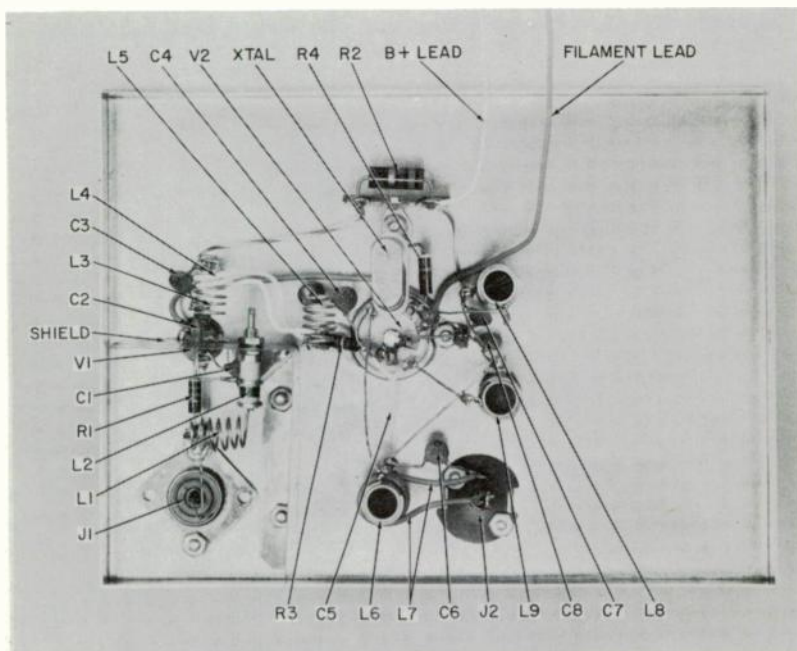


Fig. 7-8. Bottom view of the converter wiring.

cover is fastened to the chassis base. The pictorial wiring diagram (Fig. 7-9) and the photo (Fig. 7-10) of the power supply can be followed when wiring this portion. Lead lengths are not critical; however, observe the polarity of the electrolytic capacitors and

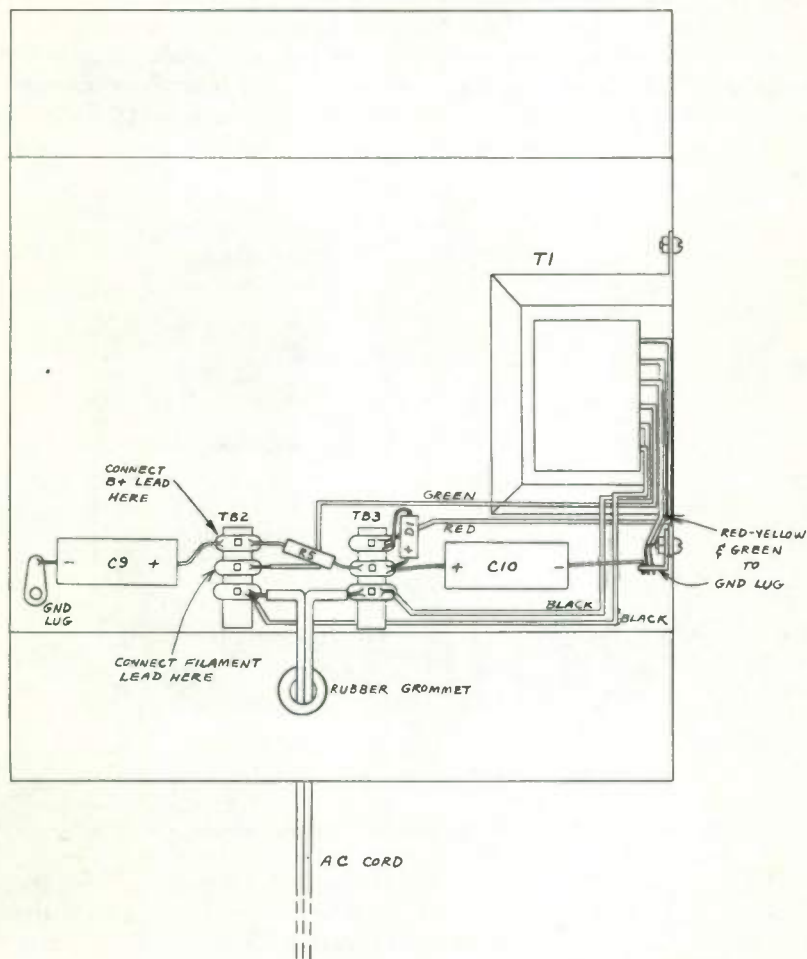


Fig. 7-9. Pictorial wiring diagram of the power supply section.

the silicon rectifier when wiring them into the circuit. Also avoid overheating the silicon rectifier when soldering to the leads. It is best to hold the diode lead near the body with a pair of needle-nose pliers while soldering; this helps conduct the heat away from the body of the diode rectifier.

### Aligning the Converter

Before attempting to use the converter, check the wiring against both the schematic and pictorial diagrams to make sure it is correct. Make sure no leads are shorting to ground. If a grid-dip meter is available, it is best to set all the coils to their operating frequencies before turning on the converter. The coils should be peaked in the vicinity of the band where you intend to operate the most. It is impossible to make the tuned circuits broad enough to cover the entire band, and insure a reasonable value of  $Q$  for the coils.

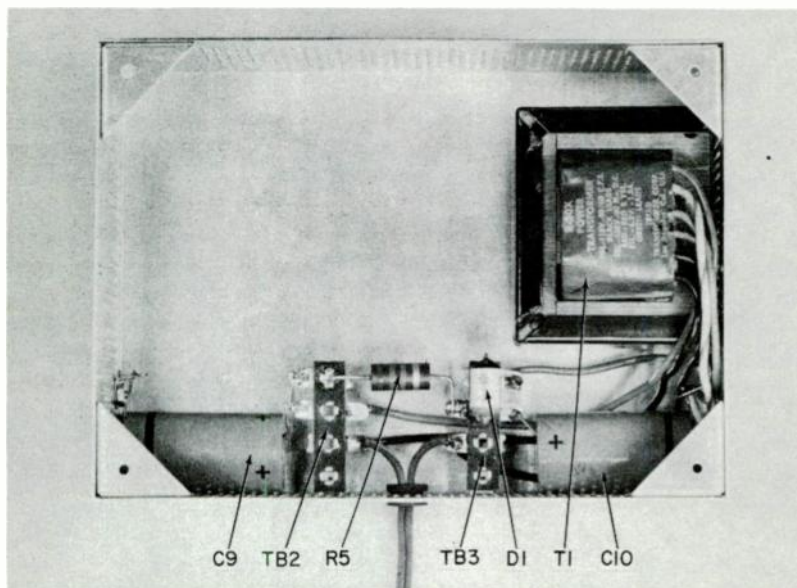


Fig. 7-10. View of the power supply wiring.

After the coils have been set to the proper frequency, turn the converter on. Allow the tubes to warm up for a minute. Check the  $B+$  with a VOM connected across capacitor C9 (from the positive end of C9 to ground). The  $B+$  should be approximately 150 volts. The oscillator coils can be peaked up with a wave meter, or with the grid-dip meter operating in the wave-meter mode.

The final step is to neutralize RF amplifier, V1. Connect the converter to the receiver with a length of shielded wire (Fig. 7-2). Turn the converter off, remove the filament lead from V1, and then turn the converter back on. Next, couple a test signal into the converter. This can come from a grid-dip meter, signal gener-



ator, nearby transmitter, etc. Tune the receiver so that the signal can be heard. Adjust L2 for minimum signal output heard from the receiver or, if the receiver is equipped with an S meter, tune for a sharp dip in the meter reading. The stage is now neutralized. Connect the filament lead to V1 once again, and the converter is ready for operation.

### Parts List

| Quantity | Item No.       | Description   |
|----------|----------------|---|
| 3        | C1, C2, C4     | 500-mmf, 10%, 1,000V, disc-ceramic capacitors.  |
| 4        | C3, C6, C7, C8 | .001-mfd GMV, 1,000V, disc-ceramic capacitors.  |
| 1        | C5             | Gimmick capacitor (see text for details).   |
| 2        | C9, C10        | 16-mfd, 350VDC, electrolytic capacitors.  |
| 1        | R1             | 47,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R2             | 6,800-ohm, 1-watt, 10%, carbon resistor.  |
| 1        | R3             | 680,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R4             | 100,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R5             | 1,500-ohm, 1-watt, 10%, carbon resistor.  |
| 1        | L1             | 6-turns of No. 20 tinned copper wire, air-wound 3/8" diameter, spaced to 1/2" length, tapped 1 3/4 turns from ground end.                                     |
| 1        | L2             | 1.5 to 2.57 $\mu$ h neutralizing coil (Miller 4306 or equiv., or 17 1/4 turns No. 33 enameled copper wire close-wound on 1/4" diameter slug-tuned coil form). |
| 1        | L3             | 6 turns of No. 20 tinned-copper wire, air-wound 3/8" diameter, spaced to 1/2" length.   |
| 1        | L4             | 2-turn link of small hook-up wire wound around B+ end of L3.  |
| 1        | L5             | 6 turns of No. 20 tinned copper wire, air-wound 3/8" diameter, spaced to 1/2" length, tapped 1 1/2 turns from ground end.                                     |
| 1        | L6             | 14.8 to 31.0 $\mu$ h (Miller 4407 or equiv.).   |
| 1        | L7             | 3-turn link of small hook-up wire wound around B+ end of L6.  |
| 1        | L8             | 1.5 to 3.2 $\mu$ h coil (Miller 4404 or equiv., or 12 1/4 turns of No. 26 enameled copper wire closewound on 3/8" diameter slug-tuned coil form).             |
| 1        | L9             | 3 turns of No. 24 enameled copper wire closewound on 3/8" diameter slug-tuned coil form (Miller 4400, or equiv. coil form).                                   |
| 1        | T1             | Power transformer—Secondaries: 135 VAC @ 50 ma; 6.3 VAC @ 1.5A (Triad R-30X, Merit P-3045, Sencor PA-8421, or equiv.).  |
| 1        | Xtal           | 45.666-mc third-overtone crystal (International Crystal FA-5 or equiv.).  |
| 1        | D1             | Silicon rectifier (Sarkes Tarzian 2F4 or equiv.).   |
| 1        | V1             | 6CW4 "Nuvistor" triode.   |
| 1        | V2             | 6U8 triode-pentode tube.  |
| 1        | J1             | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).   |

## Parts List—cont'd

| Quantity | Item No. | Description   |
|----------|----------|---|
| 1        | J2       | Shielded phono jack (Allied Radio 46 H 213, Lafayette MS-168, or equiv.). |
| 1        | TB1      | 2-lug terminal strip, both terminals insulated from ground.               |
| 2        | TB2, TB3 | 3-lug terminal strips, all terminals insulated from ground.               |
| 1        |          | Crystal socket (Millen 3302 or equiv.).                                   |
| 7        |          | Solder lugs.  |
| 1        |          | Shielded phono plug (Allied Radio 46 H 212, Lafayette MS-167, or equiv.). |
| 1        |          | "Nuvistor" socket (Cinch-Jones Type 5NS or equiv.).                       |
| 1        |          | 9-pin miniature tube socket (Amphenol 59-406).                            |
| 1        |          | 5" X 7" X 8" aluminum chassis with cap cover (LMB Type 572 or equiv.).    |
| 1        |          | $\frac{3}{8}$ " rubber grommet.   |
| 2        |          | Miniature standoff insulators.  |
| 1        |          | Piece of sheet copper for shield (see Fig. 7-6).                          |
| 1        |          | AC power cord (length as required).                                       |
| 1        |          | AC power plug.  |
|          |          | 6-32 machine screws and nuts.   |
|          |          | 4-40 machine screws and nuts.   |
|          |          | Hook-up wire.   |
|          |          | Solder.   |



## 8 A Deluxe, 2-Meter Walkie-Talkie

Walkie-talkies can be a lot of fun on camping trips, outings in the mountains, or just around town. They are also handy to have around for emergency purposes, such as during a disaster when the power is blacked out, or for CD operation.

The deluxe, 2-meter walkie-talkie pictured in Fig. 8-1 features a crystal-controlled, plate-modulated transmitter; a tunable receiver which covers the entire band; and an audio section which more than adequately drives a speaker. Six subminiature tubes are used in the unit. These tubes and similar types have been used by the military for a number of years in VHF and UHF walkie-talkies; they are rugged and very reliable in such applications. Also, they are now quite inexpensive and can usually be found selling for less than a dollar each.

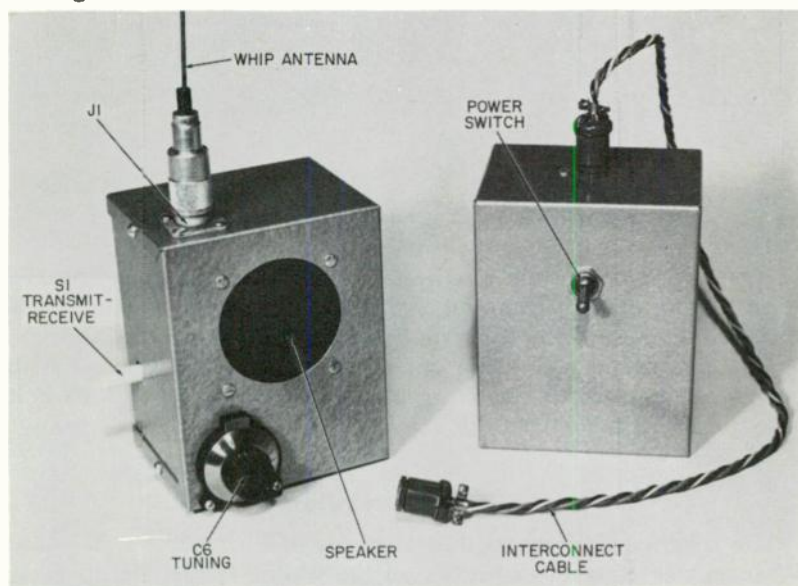


Fig. 8-1. The complete 2-meter walkie-talkie. The power pack, shown on the right, fastens to the operator's belt with a clip located on the back side.

The battery power pack is housed in a separate enclosure and is connected to the main unit with a 2-foot interconnecting cable. The power pack consists entirely of batteries; two ordinary flashlight batteries provide filament power, and two B batteries in series provide the high voltage. A schematic of the battery pack is given in Fig. 8-2. A transistorized DC-DC power pack is described in Chapter 9. The wiring configuration of the transistorized power pack and the battery power pack are identical; therefore, both power packs are interchangeable. The transistorized power pack uses six heavy-duty flashlight batteries—two to provide the filament power and four for the transistor inverter circuit. The in-

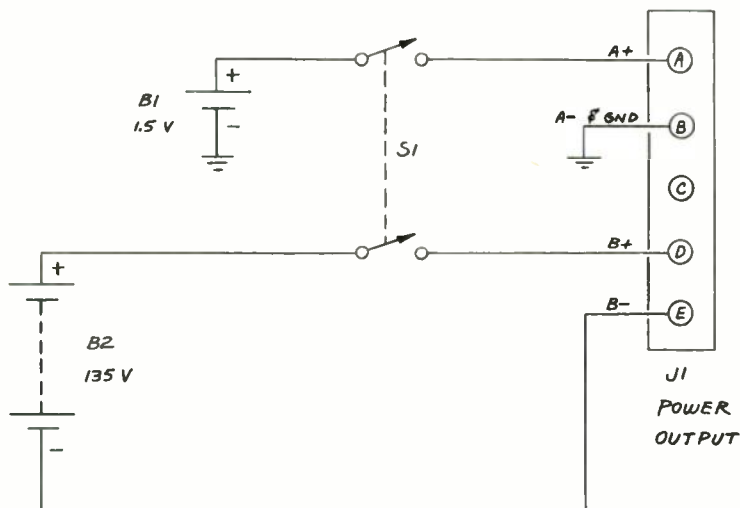


Fig. 8-2. Schematic of the battery pack.

verter circuit boosts the low voltage to high voltage for the B+ supply. A detailed description of this circuit is given in Chapter 9. As mentioned earlier, both supplies are interchangeable, and you can take your pick. A small clip is attached to the rear of both power packs; thus, the pack can be attached to the operator's belt when the unit is being used.

### Circuit Description

The schematic of the circuit is given in Fig. 8-3. V1, V2, and V3 form the transmitter portion of the walkie-talkie. V1 operates as a crystal oscillator in the 36-mc region. V2 serves as a doubler, so its output is at 72 mc. A beam pentode (V3) serves as the final


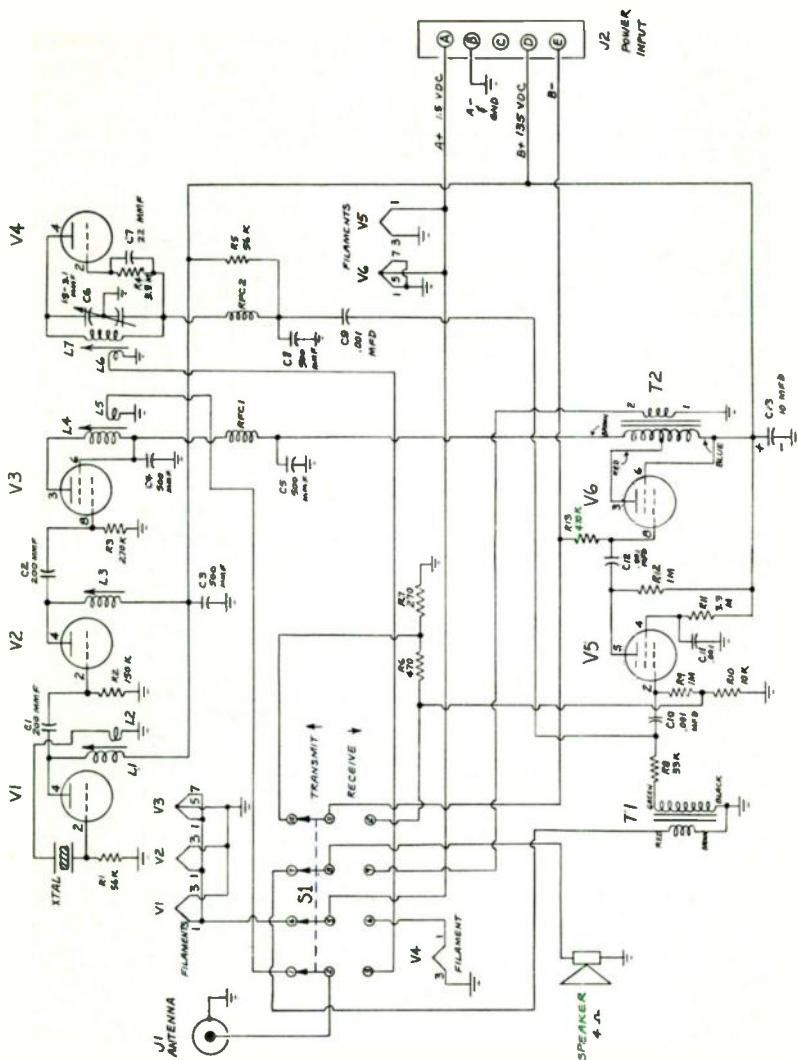



Fig. 8-3. Schematic of the RF and audio amplifier-modulator sections of the 2-meter walkie-talkie.

amplifier and also as a doubler; its output is in the 144-mc region. The crystal frequency is determined by dividing the desired operating frequency by four (for example:  $146.0 \text{ mc} \div 4 = 36.5 \text{ mc}$ ). A third-overtone type crystal is used in the circuit.

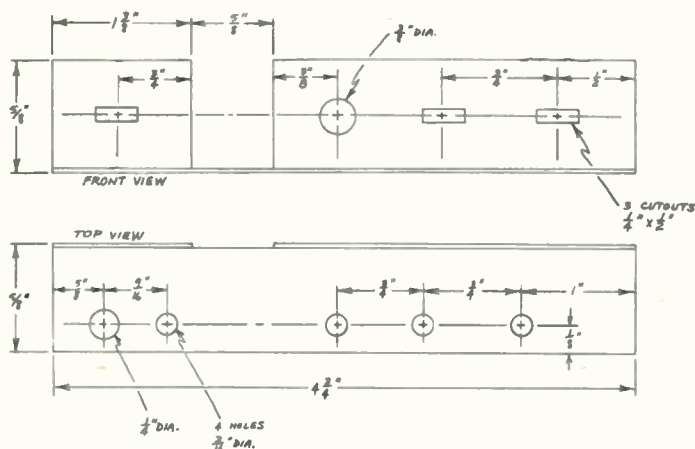V4 is a superregenerative detector; it serves as the receiver. R5 controls the amount of regeneration; once the proper value has been determined, a fixed resistor is wired into the circuit. The author found that a 56,000-ohm resistor was needed in the



(A) RF section.

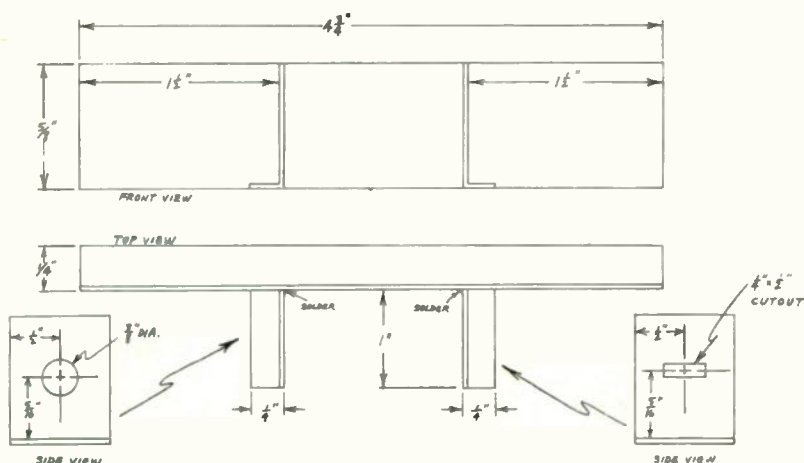

(B) Audio section.

Fig. 8-4. Detailed drawing of the tube and transformer mounting brackets.

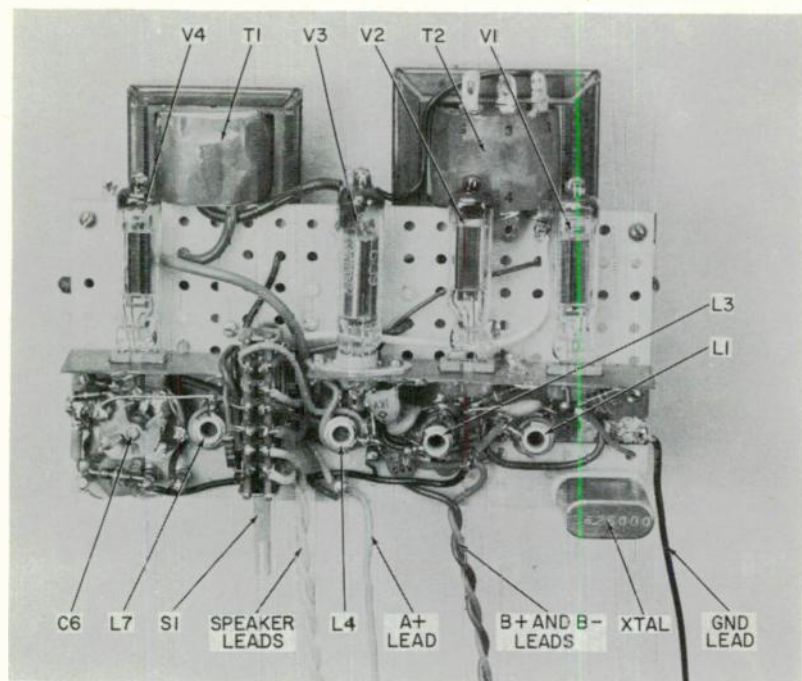


Fig. 8-5. The RF side of the walkie-talkie subassembly.

original model; however, this may vary from unit to unit. The procedure for determining this value is detailed later in this chapter.

V5 and V6 form a two-stage audio amplifier for the receiver and the modulator for the transmitter section. It operates as a Heising plate modulator and is capable of providing approximately 75% modulation for the transmitter.

Switching from transmit to receive (and vice versa) is done with one switch (S1), a 4PDT switch. The operation of S1 should be studied very carefully and understood before attempting to construct the unit. Contacts 1, 2, and 3 connect the antenna to the transmitter or the receiver. In both cases, the antenna is link coupled to the respective coils. Contacts 4, 5, and 6 are employed to switch the tube filaments of the transmitter and receiver on and off. The filaments of these tubes are instant-heating types; it is quite common in equipment of this type to switch filaments rather than B+ for transmit-receive operation. The reason for this is quite simple. If all the filaments run all the time, unnecessary power is consumed. In this type of tube, no time is lost waiting for the filament to warm up. They heat up very







quickly—the tube is conducting within about 1 second. The filaments of V5 and V6 in the audio section operate at all times since they function in both the transmit and receive position. They are turned off when the power switch in the power pack is turned off. B+ is applied to all the tubes all the time and is also turned off in the power pack.

Contacts 7, 8, and 9 switch the speaker. In the transmit mode of operation the speaker is connected to the input of the audio section and is used as a microphone. At this time the audio section is serving as the modulator. During the receive mode the speaker is connected to the output of the audio section. Contacts 10, 11, and 12 switch in two different resistors in the B- lead to change the bias point of the audio section during receive and transmit.

Negative bias voltage is provided for the audio tubes by inserting a resistance between the B- side of the high voltage and ground. This is the reason the B- side of the high voltage is not grounded directly.

### Construction

The walkie-talkie unit and the power pack are both packaged in 3" by 4" by 5" aluminum enclosures. A 2½" by 5" piece of punched phenolic board serves as a subchassis on which the

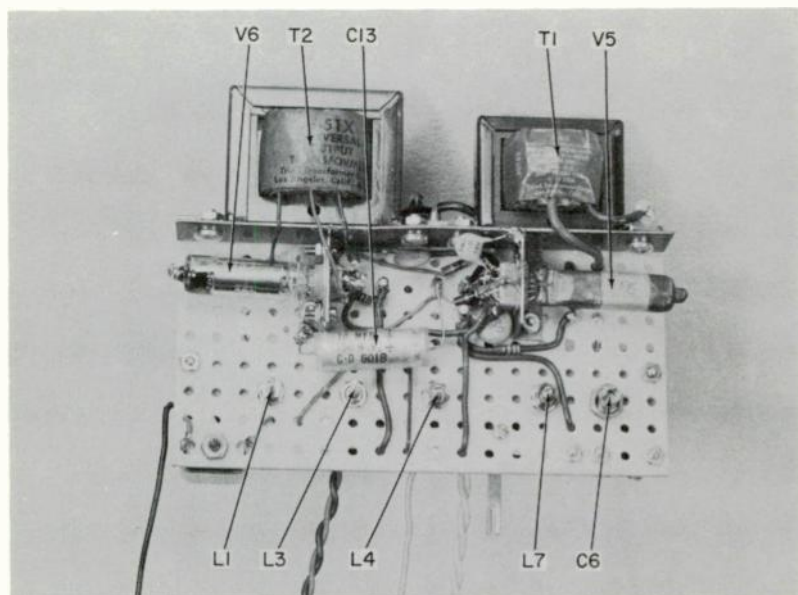


Fig. 8-8. The audio amplifier and modulator side of the walkie-talkie subassembly.

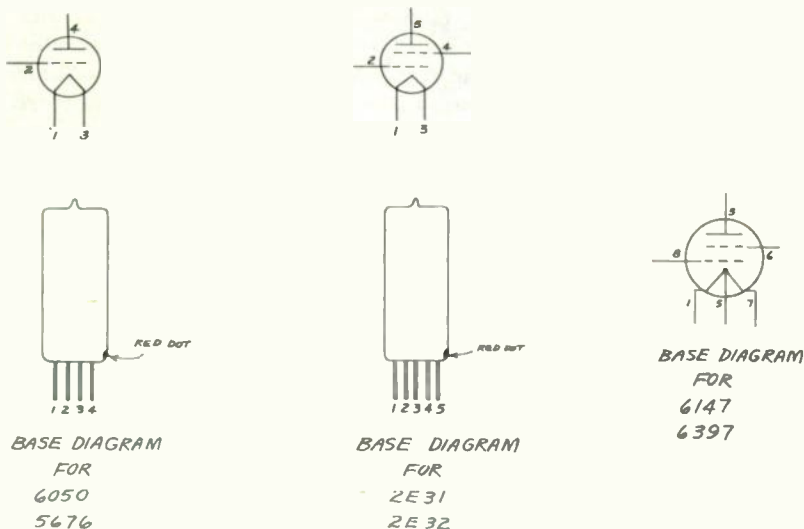


Fig. 8-9. Base diagram of the subminiature tubes used in the unit.

circuitry of the walkie-talkie is constructed. The RF section, consisting of V1, V2, V3, and V4, along with transmit-receive switch S1, are all mounted on one side of the board. A sheet copper bracket (Fig. 8-4A) holds the tube sockets. The photo in Fig. 8-5 shows a close-up view of this side of the subchassis.

T1, T2, V5, and V6 are mounted on another copper bracket, and this bracket is mounted on the back side of the board. Fig. 8-4B shows details of this bracket.

A pictorial wiring diagram of the RF section is given in Fig. 8-6 and one of the audio section is given in Fig. 8-7. A photo of the audio section is shown in Fig. 8-8. Mount all the components as shown. Where a ground connection is indicated for a component lead, solder it directly to the copper bracket, keeping the leads as short as possible. It is a good idea to clean the copper thoroughly with steel wool prior to mounting the components so that the solder will flow easier. Make sure that the two copper brackets are connected together with a ground wire, and that they are also grounded to the aluminum enclosure. The tubes generally come with long leads. These should be cut down to about  $\frac{1}{4}$ " in length so they can be plugged into the sockets. The basing diagrams for the tubes are given in Fig. 8-9. The 6050, 5676, 2E31, and 2E32 tubes all have in-line pins.

Coils L2, L5, and L6 are 1-turn links of hook-up wire wrapped around L1, L4, and L7. The proper method of placing these links around the slug-tuned coils was given in Fig. 5-7.

Keep all component leads, particularly bypass capacitor leads, as short as possible. Use only small ( $\frac{1}{4}$ -inch diameter) capacitors. Their small physical size and low series inductance make them ideal for bypassing. The resistors are all  $\frac{1}{4}$ -watt units. They were chosen because of their small size.

The receiver tuning capacitor (C6) has a  $\frac{3}{16}$ " shaft. In order to couple it to the vernier dial, which accepts  $\frac{1}{4}$ " shafts, a modification must be made. An adapter made from  $\frac{1}{4}$ " O.D. (outside diameter) copper tubing is pressed over the capacitor shaft and soldered to it. The length of the copper-tubing adapter can be determined once the subchassis has been installed.

Use a small diameter hook-up wire throughout the unit. This is most important since quite a bit of circuitry is being built into a limited amount of space. Also, space is pretty tight around the transmit-receive switch and around the tube sockets.

### **Alignment and Operation**

Check all the wiring, and make sure none of the leads are shorting to each other, especially at the tube sockets. After you are satisfied the unit has been wired correctly, connect the power cable between the power pack and the walkie-talkie.

The first step is to check out the receiver and audio section. Turn the power switch on; a "rushing" noise should be heard in the receiver. If this noise is not heard, it is possible the regeneration point of the receiver is not right. Regeneration is set in the following manner: Disconnect R5 and connect a 1-meg potentiometer in its place. Turn the power on and vary the 1-meg pot until a rushing sound is heard in the speaker; then advance the pot setting until the unit breaks into oscillation. The point on the pot, just before oscillation takes place, is the proper setting, and the most sensitive point of operation for the receiver. Remove the pot and measure the resistance value with an ohmmeter. Finally, solder in a resistor equal to the ohmmeter reading.

To check out the receiver, connect a  $\frac{1}{4}$ -wave whip antenna to antenna jack J1. A  $\frac{1}{4}$ -wave antenna for 2 meters is approximately 19" long. A 19" length of heavy copper wire can be soldered to a coax connector to form the whip antenna. A short piece of insulating tubing or plastic bushing should be used where the copper wire enters the coax connector to keep the two from shorting to each other.

The test signal to check out the receiver can come from a grid-dip meter, a generator, or a nearby transmitter. If an unmodulated signal is employed, the receiver noise should be blocked out completely when the signal is received.

Aligning the transmitter is very simple. Depress the transmit-receive switch to the transmit position. A wavemeter, field-strength meter, or receiver can be used to monitor the signal. Tune L1, L3, and L4 for maximum output. The power output of the author's model was measured at almost 100 milliwatts on a commercial power meter.

The power drain of the 2-meter walkie-talkie is as follows: Filament drain is 240 ma in the receive position and 440 ma in the transmit position. B+ drain is 11 ma in the receive position and 25 ma in the transmit position.

### Walkie-Talkie Parts List

| Quantity | Item No.          | Description  |
|----------|-------------------|--|
| 2        | C1, C2            | 200-mmF, 10%, 1,000 V, disc-ceramic capacitors.  |
| 4        | C3, C4, C5, C8    | 500-mmF, 10%, 1,000V, disc-ceramic capacitors.   |
| 1        | C6                | 1.5 to 3.1 mmF, butterfly variable capacitor (Johnson 3MB11 or equiv.).  |
| 1        | C7                | 22-mmF, 10%, 1,000V, disc-ceramic capacitor.   |
| 4        | C9, C10, C11, C12 | .001-mmF GMV, 1,000V disc-ceramic capacitors.  |
| 1        | C13               | 10-mF, 150VDC, miniature electrolytic capacitor.   |
| 1        | R1                | 56,000-ohm, 1/4-watt, 10%, carbon resistor.  |
| 1        | R2                | 150,000-ohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | R3                | 270,000-ohm, 1/4-watt, 10%, carbon resistor.   |
| 2        | R4, R11           | 3.3-megohm, 1/4-watt, 10%, carbon resistors.   |
| 1        | R5                | 56,000-ohm (approx.), 1/4-watt, 10%, carbon resistor (see text for value selection).   |
| 1        | R6                | 470-ohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | R7                | 270-ohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | R8                | 33,000-ohm, 1/4-watt, 10%, carbon resistor.  |
| 2        | R9, R12           | 1-megohm, 1/4-watt, 10%, carbon resistors.   |
| 1        | R10               | 10,000-ohm, 1/4-watt, 10%, carbon resistor.  |
| 1        | R13               | 470,000-ohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | L1                | 1.5 to 2.57 $\mu$ h subminiature RF coil (Millen 4306 or equiv., or constructed of 17 1/4 turns of No. 33 enameled copper wire closewound on 1/4" slug-tuned coil form).           |
| 1        | L2                | 1-turn link of small hook-up wire wound around B+ end of L1.   |
| 1        | L3                | 0.94 to 1.55 $\mu$ h subminiature RF coil (Millen 4305 or equiv., or constructed of 13 1/4 turns of No. 32 enameled copper wire closewound on 1/4" slug-tuned coil form).          |
| 2        | L4, L7            | 0.17 to 0.27 $\mu$ h subminiature RF coils (Millen 4301 or equiv., or constructed of 5 1/4 turns of No. 24 enameled copper wire closewound on 1/4" diameter slug-tuned coil form). |
| 1        | L5                | 1-turn link of small hook-up wire wound around B+ end of L4.   |
| 1        | L6                | 1-turn link of small hook-up wire wound around B+ end of L7.   |

## Walkie-Talkie Parts List—cont'd

| Quantity | Item No.   | Description  |
|----------|------------|--|
| 2        | RFC1, RFC2 | 3.3 $\mu$ h microminiature iron-core molded RF chokes (Millen 9230-32 or equiv.).                |
| 1        | T1         | Voice coil to grid transformer—Primary: 4/8 ohms; Secondary: 50,000 ohms (Triad A-6X or equiv.). |
| 1        | T2         | Universal output transformer (Triad S-51X or equiv.).  |
| 1        | S1         | Miniature 4PDT locking-type push-button switch (Lafayette SW-89 or equiv.).                      |
| 1        | Xtal       | 36-mc third-overtone crystal (International Crystal Type FA-5 or equiv.).                        |
| 3        | V1, V2, V4 | 5676 or 6050 subminiature triode tubes.  |
| 2        | V3, V6     | 6147 or 6397 subminiature beam-pentode tubes.  |
| 1        | V5         | 2E31 or 2E32 subminiature pentode tube.  |
| 1        | J1         | Coaxial cable receptacle SO-239 (Amphenol 83-1R or equiv.).                                      |
| 1        | J2         | 5-pin male miniature panel connector (Amphenol 126-010 or equiv.).                               |
| 1        |            | Crystal socket (Millen 33302 or equiv.).   |
| 1        |            | Solder slug.   |
| 1        |            | 2 1/4" diameter, 3-ohm voice coil speaker (Lafayette SK-65 or equiv.).                           |
| 4        |            | 7-pin subminiature tube sockets (Cinch-Jones 2H7 or equiv.).                                     |
| 2        |            | 8-pin subminiature tube sockets (Cinch-Jones 8SMP or equiv.).                                    |
| 1        |            | 2 1/2" X 5" piece of phenolic punched board (Vector 32AA18 or equiv.).                           |
| 10       |            | Push-in terminals for punched board (Vector T9.4 or equiv.).                                     |
| 1        |            | 1 1/2" diameter, 8-to-1 ratio vernier dial (Lafayette F-348 or equiv.).                          |
| 1        |            | 3" X 4" X 5" aluminum enclosure (Bud CU-2105-A, LMB TF-779, or equiv.).                          |
| 1        |            | Sheet of copper (see Fig. 8-4).  |
|          |            | 6-32 machine screws and nuts.  |
|          |            | 4-40 machine screws and nuts.  |
|          |            | Hook-up wire.  |
|          |            | Solder.  |

## Interconnecting Cable Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        |          | 5-pin male miniature cable connector (Amphenol 126-217 or equiv.).             |
| 1        |          | 5-pin female miniature cable connector (Amphenol 126-223 or equiv.).           |
| 4        |          | 24" lengths of hook-up wire twisted together to form cable (connect to plugs). |

## Battery Supply Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | S1       | DPST toggle switch.  |
| 2        | B1       | 1.5-volt, size-D, flashlight cells (connect in parallel for 1.5 volts).        |
| 2        | B2       | 67½-volt batteries (connect in series for 135 volts) (Burgess XX45 or equiv.). |
| 1        | J1       | 5-pin female miniature panel connector (Amphenol 126-011 or equiv.).           |
| 1        |          | 3" X 4" X 5" aluminum enclosure (Bud CU-2105-A, LMB TF-779, or equiv.).        |

## 9 A 6-Meter Walkie-Talkie

The 6-meter walkie-talkie described in this chapter is similar, in certain respects, to the 2-meter walkie-talkie in Chapter 8. The transmitter is crystal controlled and the final amplifier is plate modulated. The receiver is tunable; however, tuning is limited to a 2-mc segment of the band. It is a simple matter to set the center frequency of the receiver to that part of the band which is most active in your area. The audio amplifier drives a speaker in the receiving mode of operation. A carbon mike element is used as a microphone during the transmit mode, and the audio amplifier doubles as a plate modulator for the final. Four subminiature tubes are used.

The power pack is a solid-state version of the common vibrator-type power supply. Transistors, rather than a mechanical vibrator, are used in a circuit which converts the 3-volt battery supply to 135 volts DC to power the subminiature vacuum tubes. The initial cost to construct this supply is considerably more than the simple battery supply described in Chapter 8. However, since low-voltage, flashlight cells are much cheaper to replace than high-voltage B batteries, the higher cost of the transistorized supply is justified over a long period of time. The wiring configuration of the power output jacks of the simple battery pack in Chapter 8 and the transistor pack in this chapter are identical, therefore both supplies are interchangeable. A small clip is attached to the back of the supply. This enables the supply to be hung from the operator's belt when the unit is in operation. A complete description of the operation of the power supply is given later in this chapter.

### Circuit Description

The schematic diagram of the walkie-talkie is shown in Fig. 9-1. V1 and V2 form the transmitter section. V1 operates as a crystal-controlled oscillator in the 50-mc region. A third overtone crystal is used; the desired operating frequency, and the actual crystal frequency are one in the same. V2 is a beam pentode that operates



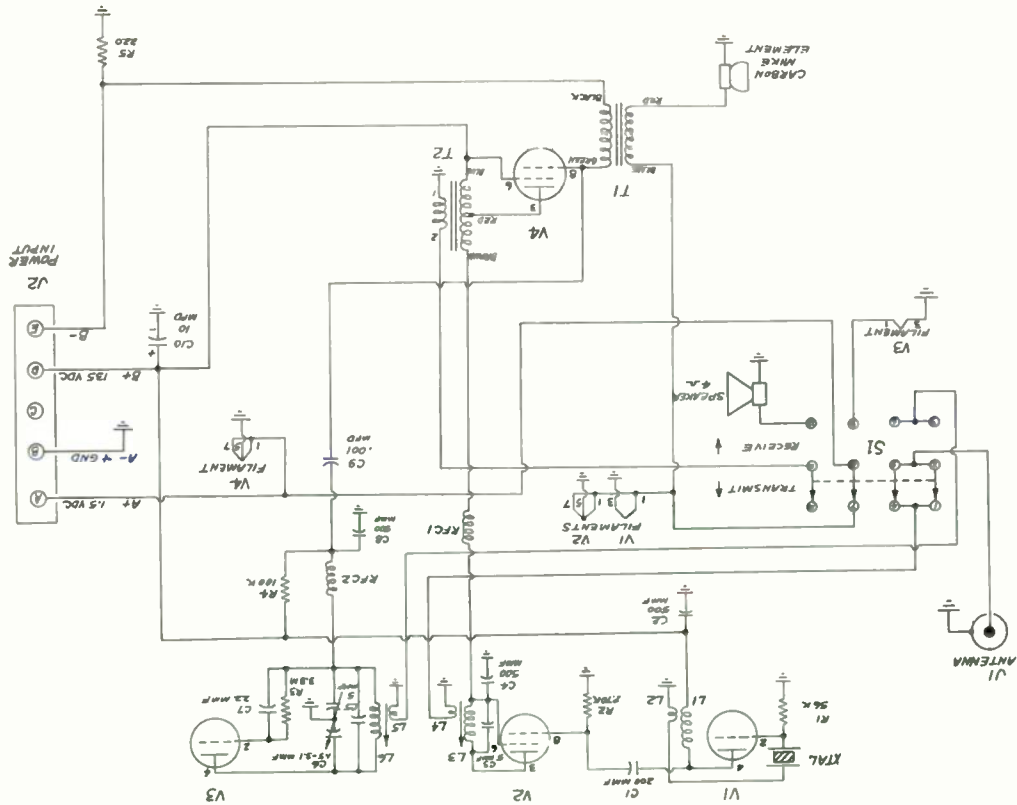


Fig. 9-1. Schematic of the 6-meter walkie-talkie unit.

straight through in the 50-mc region. It serves as the final amplifier and supplies power to the antenna.

V3 operates as a superregenerative detector and serves as the receiver. Receiver tuning is accomplished with C6. The center frequency of the receiver is set with slug-tuned receiver coil L6. The regeneration level of the receiver is set with R4, which may have to be changed from unit to unit. The author found that 100,000 ohms was needed in the original model. This can be changed and the simple procedure for determining the proper value is detailed later in the chapter.

V4 functions as a one-tube audio amplifier that drives a speaker and as a Heising plate modulator. As a modulator it is capable of providing approximately 75% modulation for the transmitter, and the quality of the audio is very good. In the transmit position a carbon mike, operating through a mike transformer (T1), drives V4. Speaker volume during the receiving mode is enough for all practical purposes.

Changeover from receive to transmit is accomplished with a 4PDT push-button switch (S1). The function of S1 is as follows: Contacts 1, 2, and 3 are paralleled with 4, 5, and 6; they switch the antenna from the transmitter to the receiver. Link coils, L4 and L5 couple the antenna into their respective coils in the transmitter and receiver.

B+ is applied to all the tubes at one time; it is turned on and off in the power pack. Since the tubes have quick heating filaments, they are switched on and off rather than the B+ for transmit-receive operation. Filament power is switched between the transmitter tube filaments and the receiver tube filament with contacts 7, 8, and 9 of switch S1. The audio tube filament remains on at all times during operation and is turned off with the switch in the power pack. The primary winding of the mike transformer is also tied in with the transmitter filaments. Thus, current flows through the carbon mike and activates it in the transmit position. Contacts 11 and 12 switch the speaker into the circuit during the receive mode.

It can be seen from the schematic diagram that the B- line is not directly grounded; instead, it is returned to ground through resistor R5. This provides about 6 volts of negative bias for V4 and eliminates the need for a separate bias battery.

The schematic diagram of the transistorized power supply is seen in Fig. 9-2. Transistors Q1 and Q2 may be thought of as switches which alternately close, thereby "chopping" the primary supply voltage (B2) into a square wave with a frequency of about 1 kc. Inverter transformer T2 furnishes the necessary feedback voltages to the transistor bases to accomplish the switching ac-

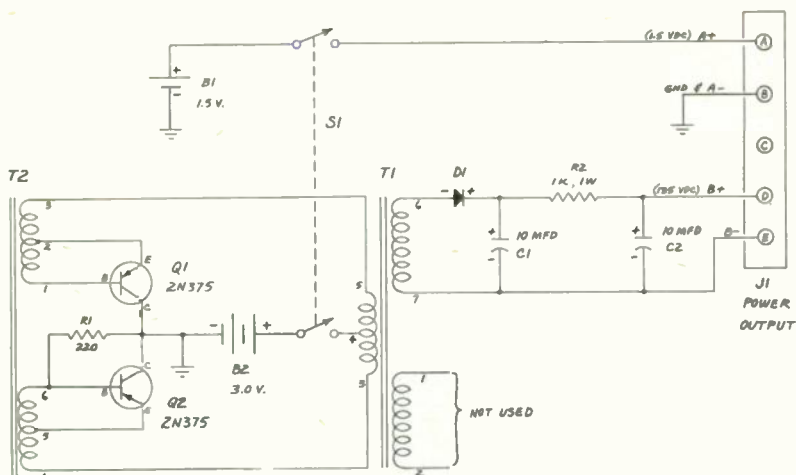


Fig. 9-2. Schematic of the transistorized power pack.

tion. T1 is the power transformer; it boosts the 3-volt, 1 kc voltage in the primary to 150 volts in the secondary. D1 rectifies the secondary voltage, which is then filtered by C1, R2, and C2. The transformers specified for this job were intended by the manufacturer to be used in photoflash power supplies, but due to their small size, they appeared to be a natural for this application.

B2 consists of four heavy-duty size-D flashlight cells. Two are connected in series to obtain 3.0 volts; then these two are paralleled with the remaining two, which are also connected in series. Battery life should be approximately 5 hours if used continuously. B1, the filament supply, consists of two flashlight batteries connected in parallel.

### Construction

The walkie-talkie unit is packaged in a 3" by 4" by 6" aluminum enclosure. Cutouts are made on the front panel, and the speaker and carbon mike element are mounted. Fig. 9-3 shows the location of these parts. The antenna jack is mounted on the top of the case, the power connection on the bottom, and the vernier dial on the side. A  $\frac{3}{8}$ " hole is made directly below the vernier dial for the switch shaft (S1).

The walkie-talkie circuitry is constructed on a 3" by 5" piece of phenolic punched board. The tube sockets are mounted on a copper bracket. Details and dimensions of this bracket are given in Fig. 9-4. The pictorial wiring diagram (Fig. 9-5) and the photo (Fig. 9-6) show the location of all the components. The only items

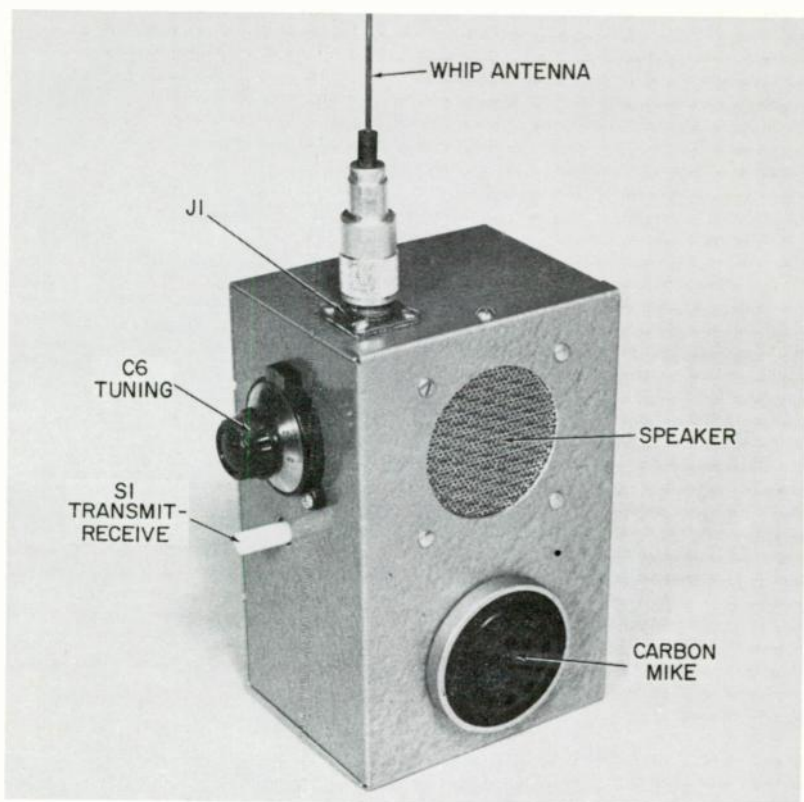


Fig. 9-3. The completed 6-meter walkie-talkie.

not visible are the two transformers (T1 and T2)—these are mounted directly to the board on the back side.

The components should be mounted as shown in the illustrations. Ground connections are made by soldering the lead directly to the copper bracket. Clean the copper bracket with steel wool

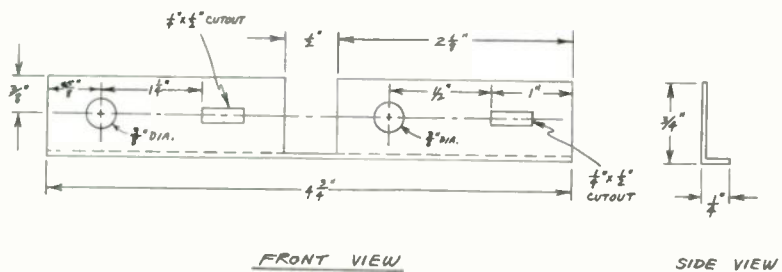


Fig. 9-4. Detailed drawing of the tube mounting bracket.



first so that the solder will flow easily. Make sure the copper bracket is grounded to the aluminum case with a short piece of wire. If the tubes have been supplied with long leads, cut them down to about  $\frac{1}{4}$ " in length so they can be plugged into the sockets. The biasing diagrams for the tubes were given in Fig. 8-9.

Use only the capacitors specified in the parts list or their direct equivalents; they are used because of their small size and inherently low series inductance (important in bypass applications). Keep all component leads as short as possible, and use point-to-point wiring. Because of their small size,  $\frac{1}{4}$ -watt resistors are

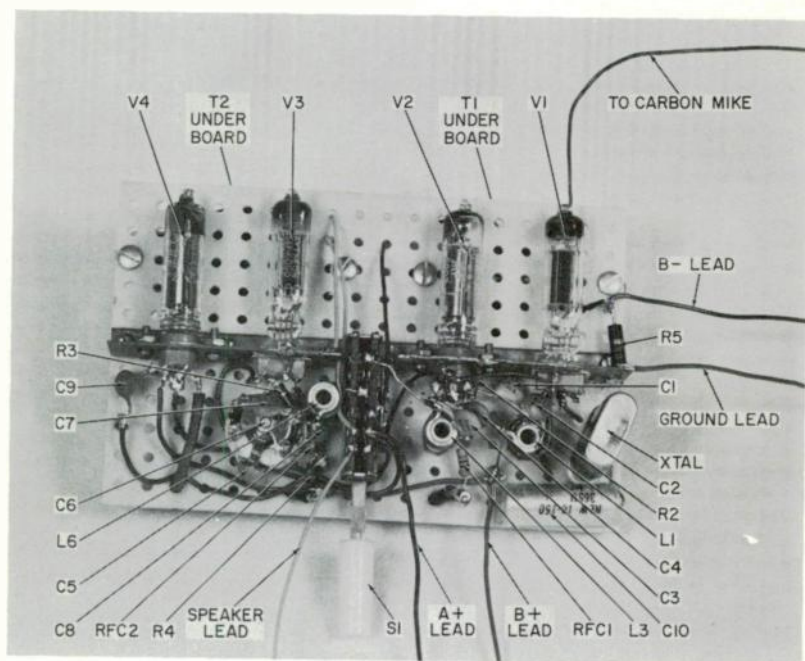


Fig. 9-6. Close-up view of the subchassis assembly.

used throughout. Use a small diameter hook-up wire when connecting the circuit. Link coils L2, L4, and L5 are made of hook-up wire wrapped around the slug-tuned coils as was shown in Fig. 5-7.

The receiver tuning capacitor (C6) has a  $\frac{3}{16}$ " shaft which must be modified before it can be coupled to the vernier dial, which accepts  $\frac{1}{4}$ " shafts. Follow the procedure outlined in Chapter 8 for adding a  $\frac{1}{4}$ " shaft to the capacitor. Since the vernier dial is located on the side of the case in this model, the author has used a flexible cable to connect the capacitor to the vernier dial, and  $\frac{1}{4}$ " shaft



couplings were used on the cable. Location of the vernier dial is optional; it can be located wherever it suits the builder.

After the phenolic punched-board subchassis has been completed, it can be mounted in the aluminum case with small right-angle brackets.

The transistorized power pack is constructed in a 3" by 4" by 5" aluminum enclosure. Layout of the major components is shown in the photos in Figs. 9-7 and 9-8. Since the collectors of both transistors are directly grounded, the transistors can be bolted to

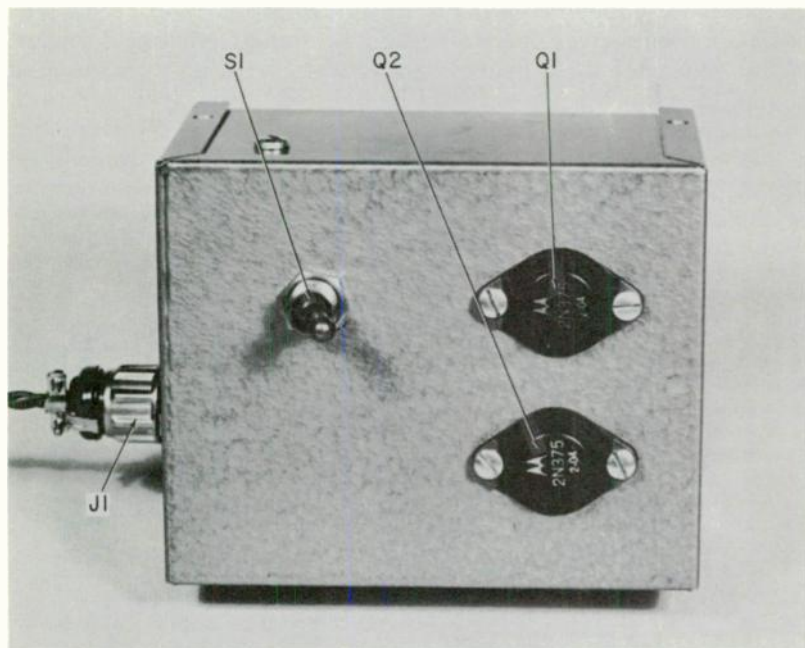


Fig. 9-7. Outside view of the transistor power pack.

the aluminum case without using insulating washers. The case provides a very good heat sink for the transistors. Wiring and lead lengths are not critical; however, good construction practices should be observed.

### Alignment and Operation

First, check out the power supply. Turn the power switch on, and check the high voltage with a VOM. It should read about 150 volts DC without a load on it. This will drop down to about 135 volts when connected to the walkie-talkie.



Make sure the unit has been wired correctly before applying power to it. If you are satisfied that no mistakes have been made, connect the cable between the power pack and the walkie-talkie. Turn the power switch on and a "rushing" noise should be heard in the speaker. It is possible the regeneration point of the receiver is not correct and the value of resistor R4 may have to be changed. Follow the same procedure outlined in Chapter 8 for setting the regeneration of the receiver to the proper point.

Connect a  $\frac{1}{4}$ -wave whip antenna to the antenna jack. It can be constructed from a piece of heavy copper wire, approximately 55 inches for 6 meters.

Check the receiver out with a signal coming from a grid-dipper, signal generator, or a nearby transmitter. With an unmodulated signal, the receiver noise should be blocked out when tuned to it.

Aligning the transmitter is a simple matter. Use a wavemeter, a field-strength meter, or a receiver to monitor the transmitted signal. Tune L1 and L3 for maximum output. The power output, of the author's model, measured on a commercial power meter, was a full 250 milliwatts!

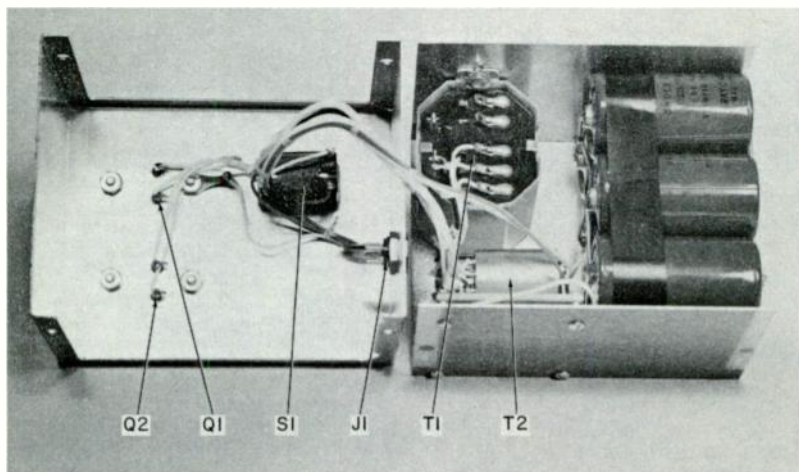


Fig. 9-8. Inside view of the transistor power pack.

### Walkie-Talkie Parts List

| Quantity | Item No.   | Description   |
|----------|------------|---|
| 1        | C1         | 200-mmF, 10%, 1,000V, disc-ceramic capacitor.                           |
| 3        | C2, C4, C8 | 500-mmF, 10%, 1,000V, disc-ceramic capacitors.                          |
| 2        | C3, C5     | 5-mmF, 10%, 1,000V, disc-ceramic capacitors.                            |
| 1        | C6         | 1.5- to 3.1-mmF butterfly variable capacitor (Johnson 3MB11 or equiv.). |

## Walkie-Talkie Parts List—cont'd

| Quantity | Item No.   | Description   |
|----------|------------|---|
| 1        | C7         | 22-mmf, 10%, 1,000V, disc-ceramic capacitor.  |
| 1        | C9         | .001-mfd GMV, 1,000V, disc-ceramic capacitor.   |
| 1        | C10        | 10-mfd, 150VDC, electrolytic capacitor.   |
| 1        | R1         | 56,000-ohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | R2         | 270,000-ohm, 1/4-watt, 10%, carbon resistor.  |
| 1        | R3         | 3.3-megohm, 1/4-watt, 10%, carbon resistor.   |
| 1        | R4         | 100,000-ohm, 1/4-watt, 10%, carbon resistor (see text).   |
| 1        | R5         | 220-ohm, 1/4-watt, 10%, carbon resistor.  |
| 3        | L1, L3, L6 | 0.94 to 1.55 $\mu$ h subminiature RF coils (Millen 4305 or equiv., or constructed of 13 1/4 turns of No. 32 enameled copper wire closewound on 1/4" diameter slug-tuned coil form). |
| 1        | L2         | 1-turn link of small hook-up wire wound around B+ end of L1.  |
| 1        | L4         | 1-turn link of small hook-up wire wound around B+ end of L3.  |
| 1        | L5         | 1-turn link of small hook-up wire wound around B+ end of L6.  |
| 2        | RFC1, RFC2 | 10 $\mu$ h microminiature iron-core molded RF chokes.   |
| 1        | T1         | Carbon mike to grid transformer (Triad A-1X or equiv.).   |
| 1        | T2         | Universal output transformer (Merit A-2900 or equiv.).  |
| 1        | S1         | Miniature 4PDT locking-type push-button switch (Lafayette SW-89 or equiv.).   |
| 1        | Xtal       | 50-mc, third-overtone crystal (International Crystal Type SK-65 or equiv.).   |
| 2        | V1, V3     | 5676 or 6050 subminiature triode tubes.   |
| 2        | V2, V4     | 6147 or 6397 subminiature beam pentode tubes.   |
| 1        | J1         | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).   |
| 1        | J2         | 5-pin miniature panel connector (Amphenol 126-010 or equiv.).   |
| 1        |            | Crystal socket (Millen 33302 or equiv.).  |
| 1        |            | 2 1/4" diameter, 3-ohm voice coil, speaker (Lafayette SK-65 or equiv.).   |
| 2        |            | 7-pin subminiature tube sockets (Cinch-Jones 2H7 or equiv.).  |
| 2        |            | 8-pin subminiature tube sockets (Cinch-Jones 8SMP or equiv.).   |
| 1        |            | 3" X 5" piece of phenolic punched board (Vector 32AA18 or equiv.).  |
| 5        |            | Push-in terminals for punched board (Vector T9.4 or equiv.).  |
| 1        |            | 1 1/2" diameter, 8-to-1 ratio vernier dial (Lafayette F-348 or equiv.).   |
| 1        |            | 3" X 4" X 6" aluminum enclosure (Bud CU-2108-A, LMB-141, or equiv.).  |
| 1        |            | Type F-1 carbon mike element (Available at most surplus stores).  |

### Walkie-Talkie Parts List—cont'd

| Quantity | Item No. | Description   |
|----------|----------|---|
| 1        |          | Sheet of copper (See Fig. 9-4).<br>6-32 machine screws and nuts.<br>4-40 machine screws and nuts.<br>Hook-up wire.<br>Solder. |

### Power Pack Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 2        | C1, C2   | 10-mfd, 150 VDC, electrolytic capacitors.  |
| 1        | R1       | 220-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | R2       | 1,000-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | T1       | Power transformer (UTC Type PF-5 transistor photoflash transformer or equiv.).               |
| 1        | T2       | Transistor inverter transformer (UTC Type PF-6 transistor photoflash transformer or equiv.). |
| 1        | S1       | DPST toggle switch.  |
| 6        | B1, B2   | Heavy-duty size-D flashlight cells (Burgess Type 210 or equiv.).                             |
| 1        | D1       | Silicon rectifier (Sarkes Tarzian 2F4 or equiv.).  |
| 2        | Q1, Q2   | 2N375 power transistors.   |
| 1        | J1       | 5-pin, female, miniature panel connector (Amphenol 126-011 or equiv.).                       |
| 1        |          | 3" X 4" X 5" aluminum enclosure (Bud CU-2105-A, LMB TF-779, or equiv.).                      |

### Interconnecting Cable Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        |          | 5-pin, male, miniature cable connector (Amphenol 126-217).                     |
| 1        |          | 5-pin, female, miniature cable connector (Amphenol 126-223).                   |
| 4        |          | 24" lengths of hook-up wire twisted together to form cable (connect to plugs). |

# Converter-

## 10 Transmitter for 6-Meter Mobile

The mobile rig described in this chapter solves the problem of having 3 or 4 separate pieces of equipment scattered about the family car for mobile operation. This compact 6-meter mobile rig (Fig. 10-1) combines the converter, transmitter, and power supply in one package. All you have to do is connect it to the auto's 12-volt system, feed the output of the converter into the car radio, hook a 6-meter antenna up to it, and you're on the air.

The heart of the unit is the transistorized supply used to furnish the high voltage. This compact, yet highly efficient power supply eliminates the need for a bulky external dynamotor or vibrator-type supply. A transistorized supply of this type is commonly referred to as a DC to DC converter. It converts the 12-volt primary voltage to high voltage for the transmitter and other circuitry. In this case the high-voltage output of the supply is in the order of 275 volts DC. More will be said about the function of this circuit later in the chapter.

The 6-meter converter used by the author in this rig is a commercially available unit, being sold either as a kit or completely wired and tested. Any number of converter circuits could be used in its place, even the circuit described in Chapter 6, with some modifications. In any event, the converter IF output frequency should be in the broadcast band so that it will work directly into the car radio. This is not the most ideal IF frequency due to the image problems which are encountered; however, in the interest of simplicity and compactness, it will suffice.

The transmitter section uses only two tubes. Actually, these are dual-purpose tubes, and therefore the transmitter is equivalent to one with four tubes. A 6U8 triode-pentode is used in the RF section, and another 6U8 is used for the plate modulator. There is a practical reason for using two 6U8's—the filaments can be wired in series for operation directly from 12 volts without dropping resistors or current balancing resistors.

This unit is designed to operate in automobiles that have a 12-volt, negative ground ignition system only. Most of the cars on the road today have this type of system; however, there are a few exceptions.

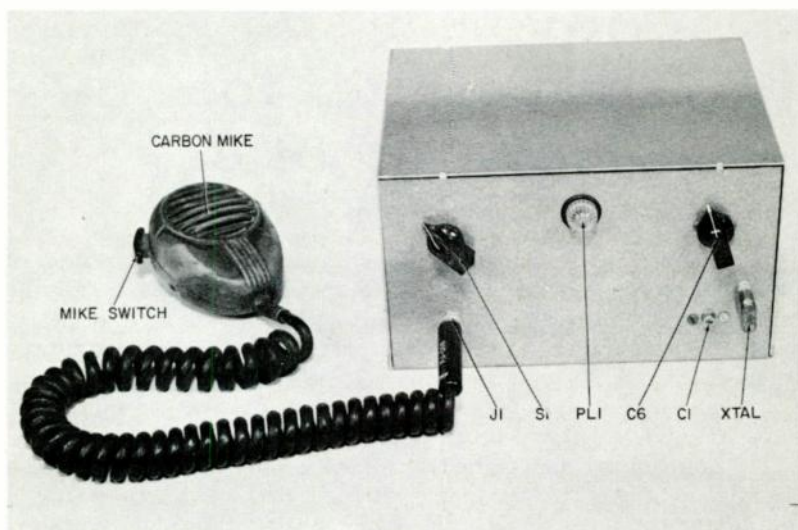


Fig. 10-1. The completed 6-meter transmitter-converter mobile unit.

### How It Works

The schematic of the transmitter and power-supply sections, and the connections to the commercial converter is given in Fig. 10-2. V1, a 6U8, serves as the transmitter. The triode section (V1A) is the oscillator which operates in the 50-mc region; a third overtone crystal is used and L1 and C1 resonate at 50 mc. The oscillator output is capacitively coupled to the grid of V1B, the pentode section, which serves as the final amplifier of the transmitter. The final tank circuit (L2 and C6) also resonates in the 50-mc region. L3 is a link that couples the RF output from the transmitter to the transmit-receive relay (RLY).

The transmit-receive relay (RLY) is a DPDT relay with one set of contacts switching the 6-meter whip antenna between the transmitter and the receiving converter. The remaining set of contacts switch the B+ from the transmitter to the converter.

V2 serves as the modulator. V2A, the triode section, is a grounded-grid amplifier with the carbon mike operating directly in the cathode circuit. Current for the carbon mike is supplied through the tube, eliminating the need for a carbon mike trans-

former. The carbon mike can be thought of as a variable resistor with the resistance varying at an audio rate. V2B, the pentode section, amplifies the audio signal from V2A. In addition, it acts as a Heising plate modulator, modulating the final amplifier in the transmitter through T1.

The transistorized power supply is relatively simple. Transistors Q1 and Q2 act as switches which alternately close and open, thereby "chopping" the 12-volt primary voltage into a 1-kc square wave. This 1-kc square wave, now actually an AC voltage, powers the primary of transformer T2. The feedback windings turn the transistors on and off; actually, the entire primary circuit is basically an oscillator operating at about 1 kc. The secondary of T2 is the high-voltage winding. Since a center tap is provided in the secondary winding, only two rectifiers are needed. Rectifiers D1 and D2 operate as a full-wave rectifier. Filtering is provided by C14. C13 helps to cut out voltage spikes which are a natural result of the switching action in the primary. The output voltage of the supply is about 275 VDC; it is capable of delivering 125 ma of current.

As mentioned before, the converter is available commercially. Since the mobile rig is designed for 12-volt operation, it will be necessary to use tubes with 12-volt filaments in it. There is another scheme, though, which can be used. A 7.5-ohm, 10-watt resistor can be inserted in the filament line, and 6-volt tubes can then be used in the converter. This value resistor, of course, applies only to the converter specified in the parts list.

DPDT switch S1 performs two functions. One set of contacts turns the 12-volt power on and off. When the power is off, the other set of contacts routes the auto's broadcast antenna to the radio so that its normal operation is not impaired. When the power switch is on, the converter IF output is fed to the car radio.


Push-to-talk operation is accomplished in the following manner. One side of the relay field coil is connected to power switch S1. When the switch is turned on, 12 volts is supplied to this side of the coil winding. The other lead is returned to ground through the switch in the carbon microphone. Closing the switch activates the relay.

### Construction


The entire mobile rig is packaged in an 8" by 6" by 4½" aluminum enclosure. The transmitter is constructed on an aluminum subchassis; the hole location guides for the front and rear panels is given in Fig. 10-3 and a detail drawing of the RF and transmitter subchassis is given in Fig. 10-4. The pictorial wiring diagram in



Fig. 10-2. Schematic of the 6-meter

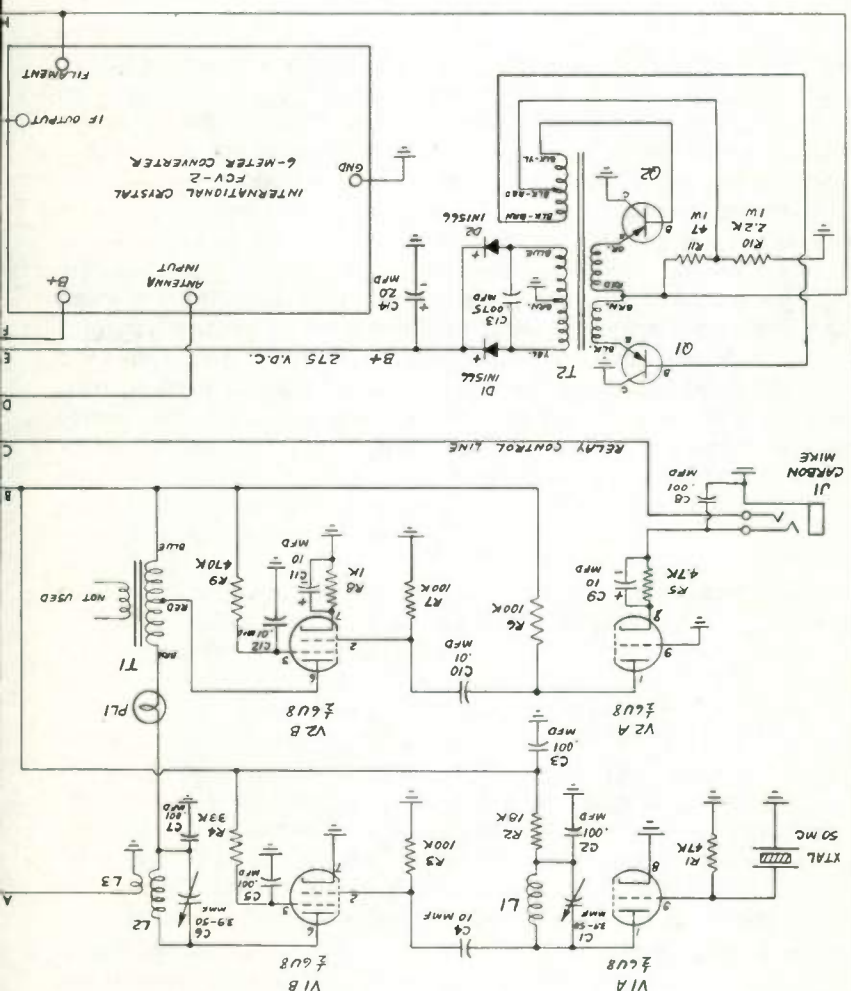



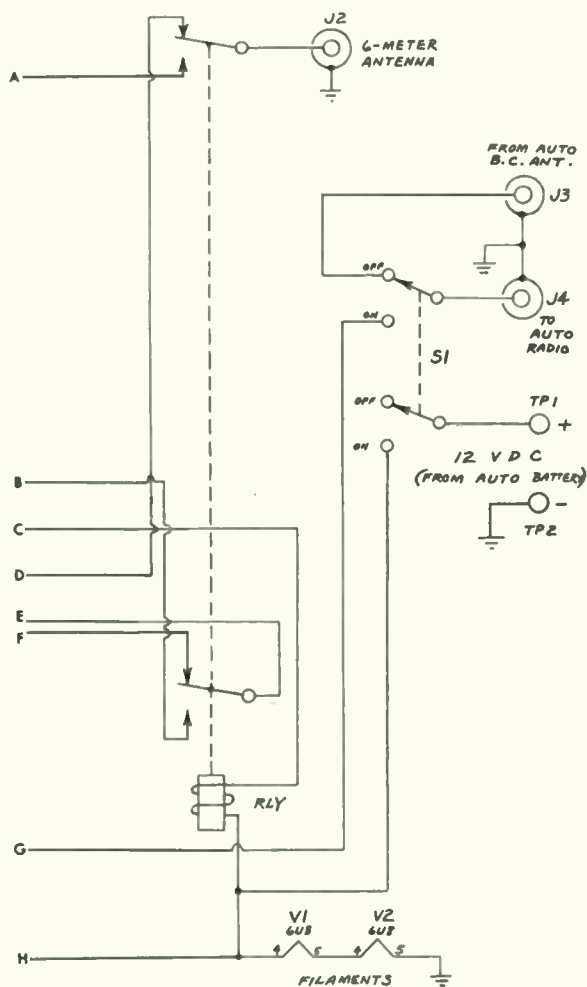

transmitter-converter mobile unit.

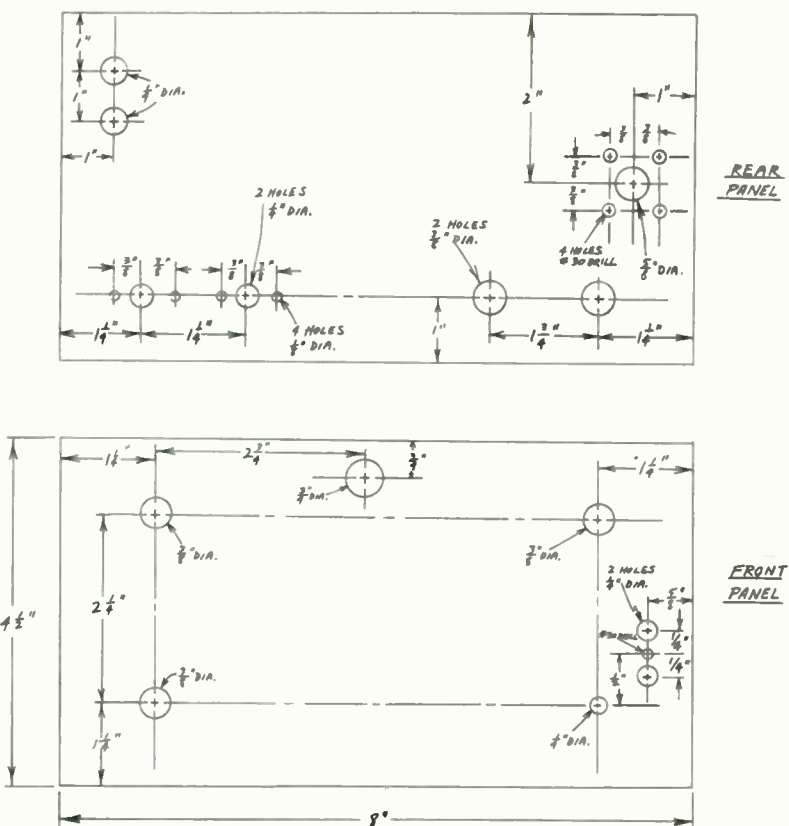


Fig. 10-3. Chassis layout and hole location guide for the front and rear panels.

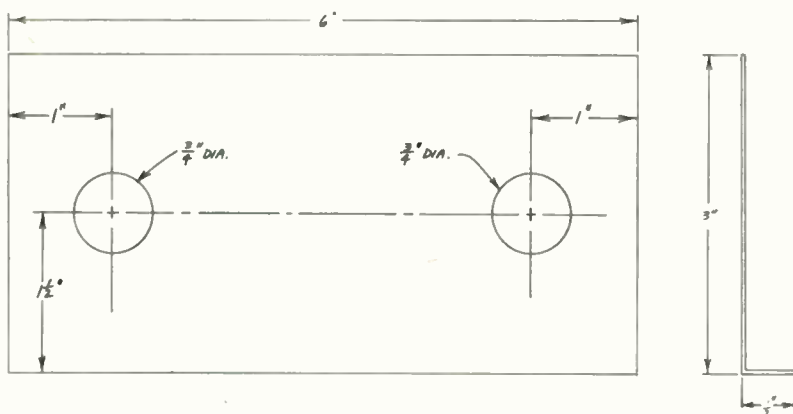


Fig. 10-4. Detail drawing of the RF and modulator subchassis.

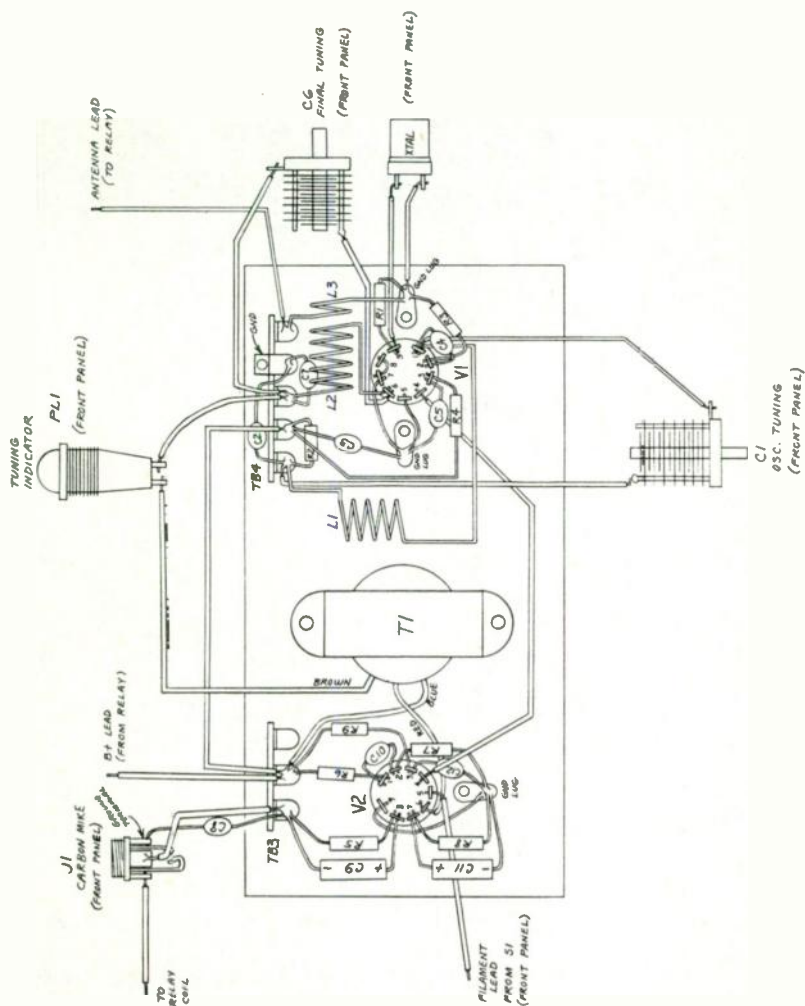


Fig. 10-5. Pictorial wiring diagram of the RF and modulator subchassis.

Fig. 10-5 can be followed when wiring it. Remember to keep RF leads as short as possible. Wiring leads for the remainder of the circuit are not critical. A pictorial wiring diagram of the power-supply section is given in Fig. 10-6. Transistors Q1 and Q2 are mounted directly to the aluminum enclosure as shown in Fig. 10-7

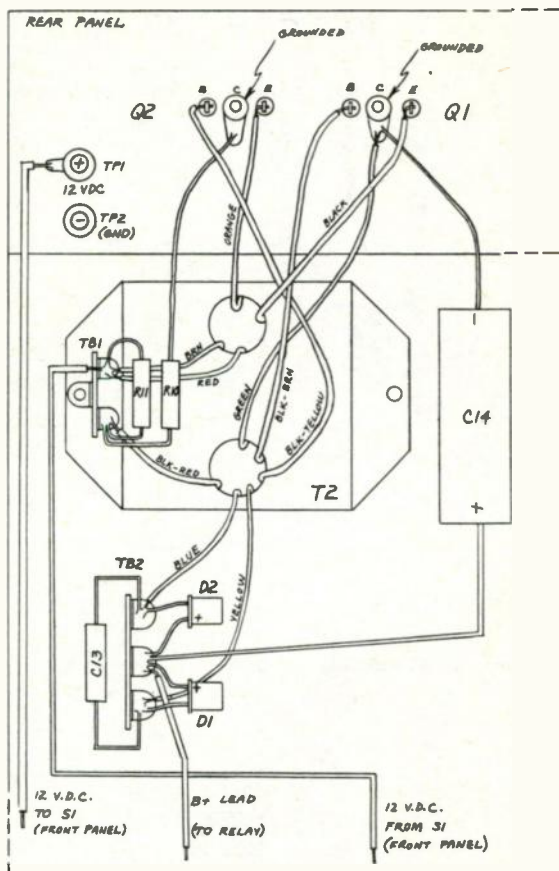


Fig. 10-6. Pictorial wiring diagram of the transistorized DC-DC power supply.

for heat sinking. Since the transistor collectors are grounded in the circuit, there is no need to electrically insulate them from the case.

### Operation

Make sure the unit has been properly wired before attempting to fire it up. A photo of the complete wiring is given in Fig. 10-8.

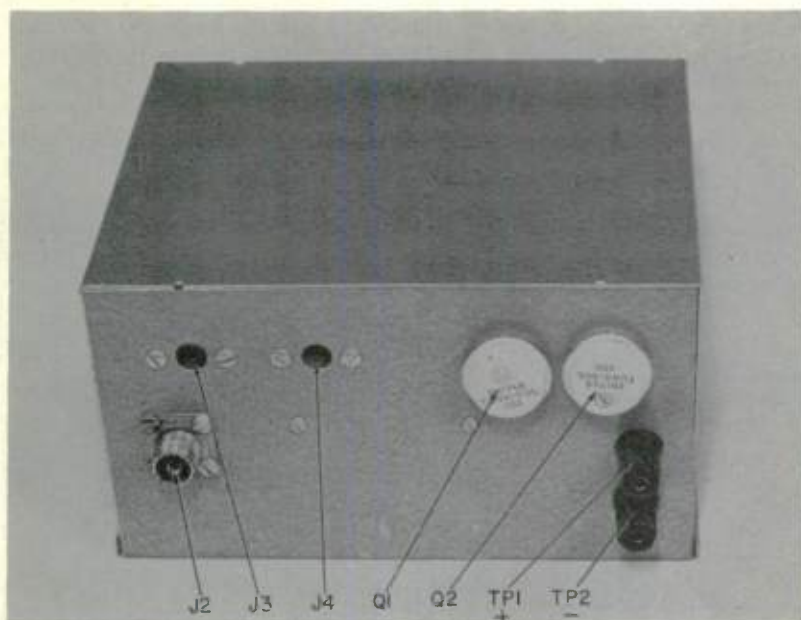


Fig. 10-7. Rear view of the unit.

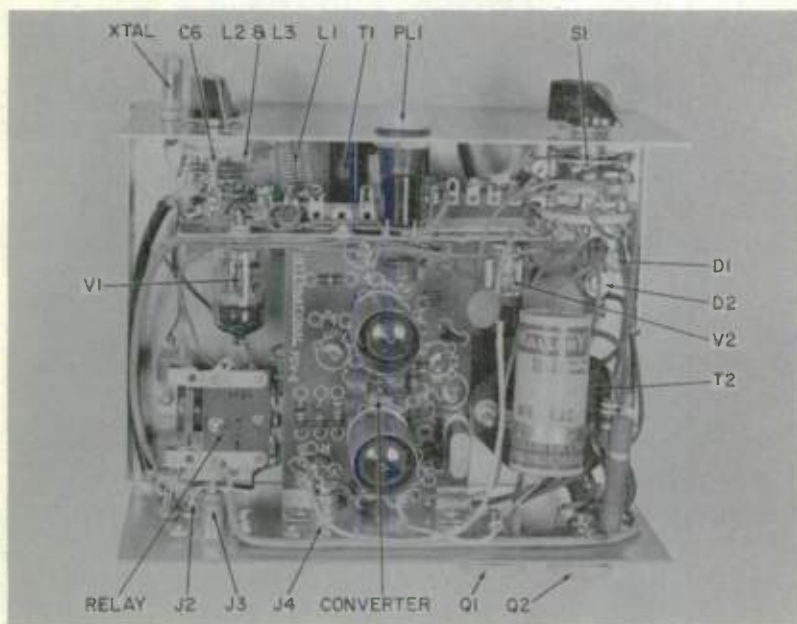


Fig. 10-8. Inside view of the unit.

The first step is to check out the power supply to make sure it is operating properly. The output voltage should be checked with a VOM.

The transmitter is tuned by looking for a "dip" in the glow of the indicator lamp or using a wavemeter or field-strength meter and tuning for maximum output. The transmitter will deliver about 1-watt output.

Caution: there is high voltage on the shafts of the tuning capacitors, and care should be exercised when tuning the transmitter.

### Parts List

| Quantity | Item No.           | Description  |
|----------|--------------------|--|
| 2        | C1, C6             | 3.9 to 50-mmF variable capacitors (Hammarlund APC-50 or equiv.).   |
| 5        | C2, C3, C5, C7, C8 | .001-mfd GMV, 1,000V, disc-ceramic capacitors.   |
| 1        | C4                 | 10-mmF, 10%, 1,000V, disc-ceramic capacitor.   |
| 2        | C9, C11            | 10-mfd, 50VDC, electrolytic capacitors.  |
| 2        | C10, C12           | .01-mmF GMV, 1,000V, disc-ceramic capacitors.  |
| 1        | C13                | .0075-mfd GMV, 1,000V, disc-ceramic capacitor.   |
| 1        | C14                | 20-mfd, 450VDC, electrolytic capacitor.  |
| 1        | R1                 | 47,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R2                 | 18,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 3        | R3, R6, R7         | 100,000-ohm, 1/2-watt, 10%, carbon resistors.  |
| 1        | R4                 | 33,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R5                 | 4,700-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R8                 | 1,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R9                 | 470,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R10                | 2,200-ohm, 1-watt, 10%, carbon resistor.   |
| 1        | R11                | 47-ohm, 1-watt, 10%, carbon resistor.  |
| 2        | L1, L2             | RF coils (8 turns, No. 20 tinned-copper wire, 1/2" diameter, spaced to 1/2" length, or cut from Air Dux 416T, B&W 3003, or equiv. coil stock). |
| 1        | L3                 | Output link. (3 turns, No. 20 tinned-copper wire, 1/2" diameter, or cut from Air Dux 416T, B&W 3003 or equiv. coil stock).                     |
| 1        | T1                 | Universal output transformer (Triad S-51X or equiv.).  |
| 1        | T2                 | Transverter transformer (Chicago Standard Transformer Type DCT-1 or equiv.).   |
| 1        | S1                 | DPDT toggle or rotary switch.  |
| 1        | PL1                | 35-ma, bayonet-base, pilot lamp used as tuning indicator (General Electric 1819 or equiv.).  |
| 1        | Xtal               | 50-mc, third-overtone crystal (International Crystal Type FA-5 or equiv.).   |
| 2        | D1, D2             | Silicon rectifiers (Motorola 1N1566 or equiv.).  |
| 2        | Q1, Q2             | 2N174A power transistors.  |
| 2        | V1, V2             | 6U8 triode-pentode tubes.  |
| 1        | Rly                | 12-volt DC DPDT relay (Advance PC/2C/12VD or equiv.).  |
| 1        | J1                 | 3-conductor mike jack (Switchcraft 12B or equiv.).   |

### Parts List—cont'd

| Quantity | Item No. | Description   |
|----------|----------|---|
| 1        | J2       | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).   |
| 2        | J3, J4   | Auto-radio antenna jacks (Allied Radio 41 H 144 or equiv.).   |
| 2        | TP1, TP2 | 5-way binding or terminal posts (input power connections).  |
| 1        |          | Crystal socket (Millen 33302 or equiv.).  |
| 6        |          | Solder lugs.  |
| 2        |          | 9-pin miniature tube sockets (Amphenol 59-406 or equiv.).   |
| 2        |          | Knobs   |
| 1        |          | Pilot-light holder assembly (Dialco 81410 or equiv.).   |
| 1        |          | Carbon microphone with built-in push-to-talk switch.  |
| 1        |          | 8" X 6" X 4½" aluminum enclosure (LMB 146 box chassis or equiv.).   |
| 1        |          | 6-meter converter (International Crystal FCV-2 with 49.4-mc crystal for broadcast band IF output or equiv.) (see text). |
|          |          | 6-32 machine screws and nuts.   |
|          |          | 4-40 machine screws and nuts.   |
|          |          | Hook-up wire  |
|          |          | Solder.   |



# 11 All-Band, Phone-CW Transmitter

The all-band transmitter described in this chapter is ideal as a station transmitter, either as the main transmitter or as a standby unit. Since it is a compact, completely self-contained unit, it is also handy to take along on a vacation trip. Though this unit is ideal for the beginning amateur, its construction should be tackled only by those who have had some practical experience with circuits of this nature.

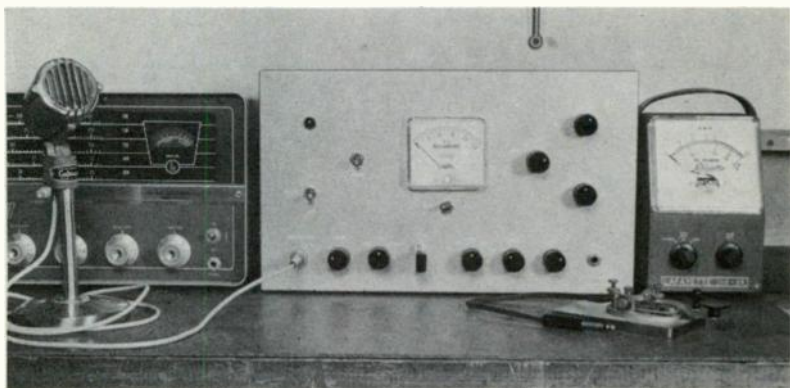


Fig. 11-1. The complete all-band station.

The all-band transmitter covers the 10- through 80-meter amateur bands, and runs approximately 40 watts on phone and CW. It is crystal controlled; however, a VFO can be used with it. A complete power supply and a plate modulator, which includes a preamp section for crystal microphone operation are included in the transmitter package. Fig. 11-1 shows a photograph of the transmitter in a typical station setup, with the receiver on the left, and a SWR-power meter on the right. The crystal mike and key are seen in the foreground.

For ease of operation, all the necessary controls for bandswitching and tuning are located on the front panel. A close-up view of the front panel is shown in Fig. 11-2. All of the controls have been

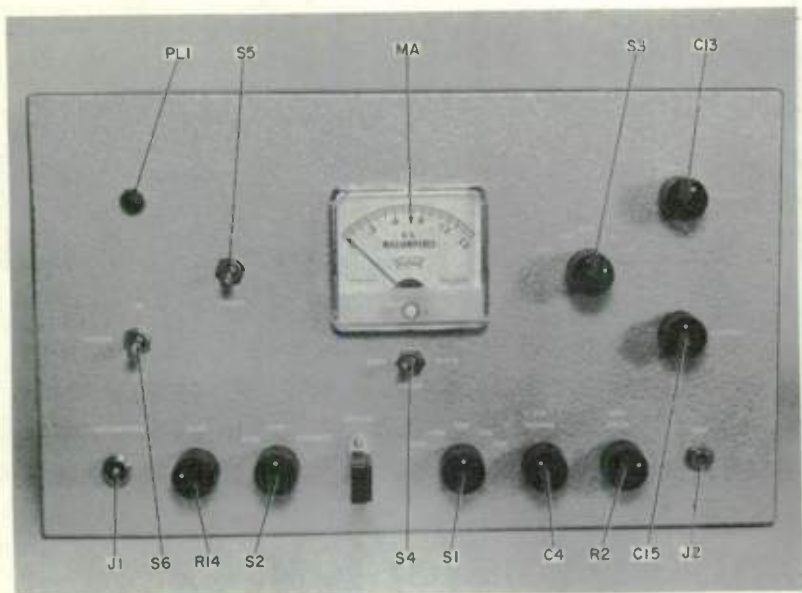



Fig. 11-2. Close-up view of the transmitter.


clearly marked with decals. The meter monitors either the final grid current or the final plate current and is used as the tuning indicator.
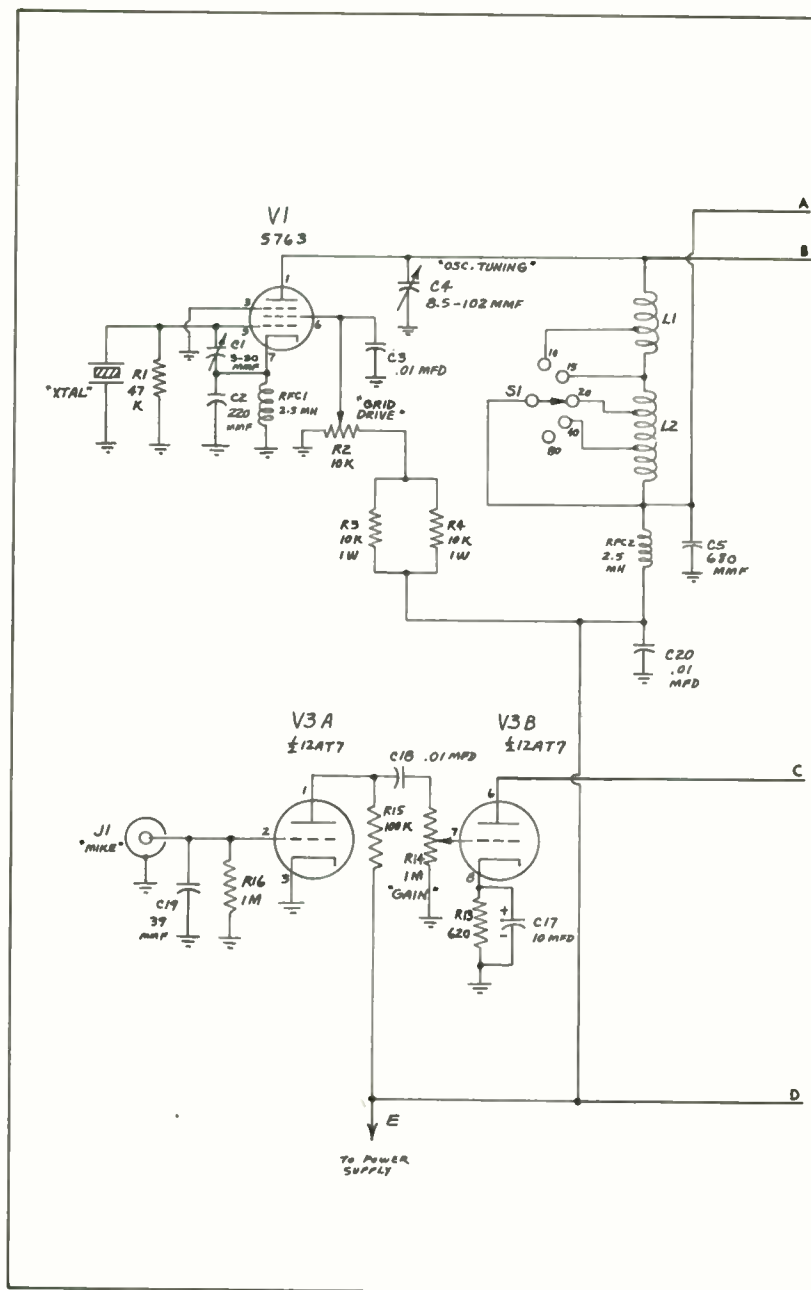
### How It Works

The transmitter schematic is shown in Fig. 11-3, and the power supply schematic in Fig. 11-4. V1, a 5763, serves as a crystal oscillator. The plate circuit, consisting of C4, L1, and L2, is tuned to the crystal frequency or one of its harmonics. For instance, an 80-meter crystal can be used for both 80- and 40-meter operation. In this case the oscillator doubles into the 40-meter band. A 40-meter crystal is used when operating in the 40-, 20-, 15-, and 10-meter bands. The oscillator operates straight through on 40 meters. It is tuned to the second harmonic on 20 meters, the third harmonic on 15 meters, and the fourth harmonic on 10 meters. L1 and L2 are tapped coils, and switch S1 selects the proper tap for the desired operating frequency.

The grid drive to the final amplifier is changed by varying the screen voltage on the 5763 oscillator tube with R2. This change in screen voltage varies the output power of the oscillator and, hence, the input of the final amplifier. The oscillator signal is capacitively coupled to the grid of the 6DQ6 (V2) which operates



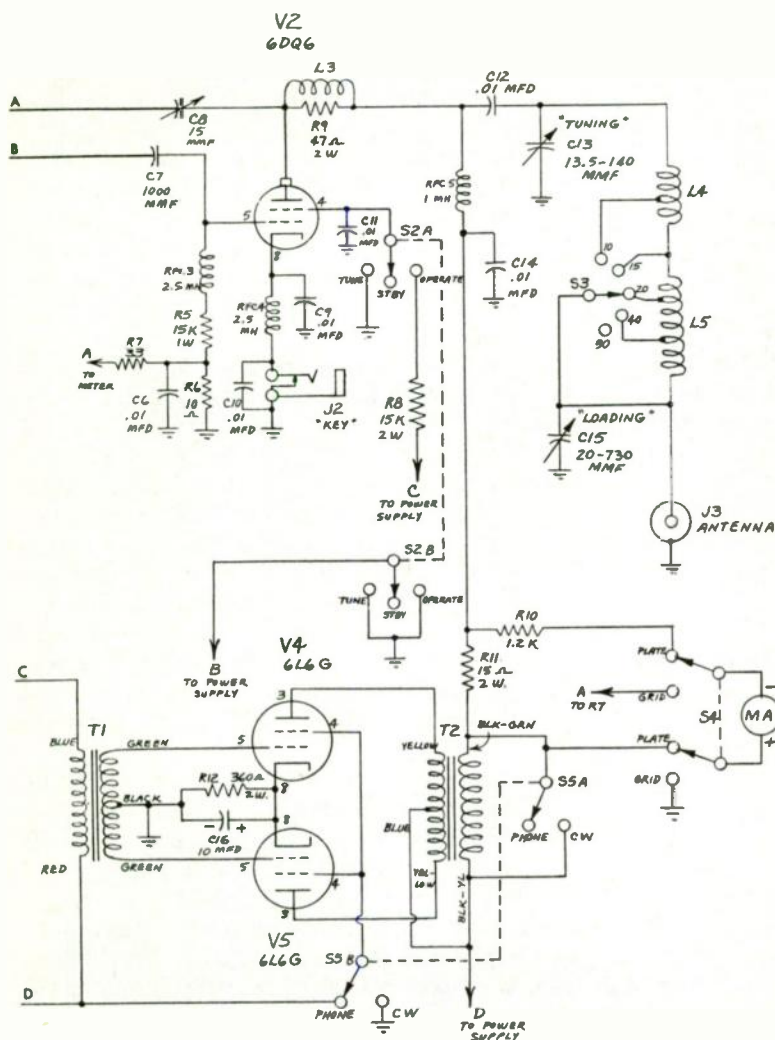

10-80 meter, phone-CW rig.

as a Class-C power amplifier. The final amplifier is grid-leak biased. The pi-tank circuit in the output, or plate side, of the final amplifier enables the rig to be matched into a variety of antennas. C13 serves as the tuning capacitor, and C15 as the loading capacitor for the pi-tank circuit. The pi-tank actually consists of two coils which are tapped. The proper tap for the desired band of operation is selected by S3. In operation both S1 and S3 are set to the same band.

Since the 6DQ6 is a very high-gain tube, it is neutralized to avoid oscillation. Capacitors C5 and C8 form the neutralizing network between the plate and grid of the final amplifier. The cathode of the 6DQ6 is returned to ground through a closed-circuit phone jack. For CW operation a key is inserted into this jack, and only the final is keyed. Thus, the oscillator runs continuously when operating CW.

A 2-pole, 3-position rotary switch is used to switch the screen grid of the 6DQ6 and the high-voltage center tap of the power transformer simultaneously. This switch (S2) serves as the Standby-Operate control and is also used to "tune" the oscillator. In the Standby position, the center tap of the power-supply, high-voltage winding is ungrounded, and, therefore, B+ is removed from the transmitter. In the Tune position, the screen grid of the 6DQ6 is grounded thereby preventing the final from drawing excessive current which could damage it, while the oscillator is being tuned. At this time, the high voltage center tap is grounded. In the Operate position the center tap is again grounded, and power is fed to the screen of the 6DQ6. L3 and R9, which are in the plate circuit of the 6DQ6, form an RF choke used to suppress parasitic oscillations.

V3 is a two stage preamp which amplifies the audio from the crystal microphone. The driver transformer (T1) couples audio from the plate of V3B to the grids of the push-pull, Class-B 6L6 output stage, (V4 and V5). This section is the plate modulator for the final amplifier. T2 is a universal modulation transformer. This transformer is provided with a number of taps making possible a variety of impedance matching. The leads used here were selected to provide an impedance match of 6,000 ohms to the modulator and 4,000 ohms to the final amplifier. During CW operation, S5 shorts the secondary of the modulation transformer, and also removes high voltage from the screen grids of the 6L6's, and grounds them. This action disables the modulator.

A 1.5 DC milliammeter is used for the transmitter tuning indicator; it is switched to the grid or the plate circuit of the 6DQ6 final amplifier tube. Meter shunts are provided in the respective circuits; when the meter is reading grid current, the actual full-



scale reading of the meter is 15 ma, and when switched to the plate circuit, the actual full-scale meter reading is 150 ma.

The power supply is conventional in all respects. It provides approximately 400 volts DC for the final amplifier and the modulator-output stage. 250 volts DC is provided for the oscillator tube, the screen grids of the modulator tubes, etc. RF bypass capacitors are used in the primary of the power transformer to keep RF from being coupled back into the power line. S6 serves as the power switch, and pilot light, PL1, indicates when the power is on.

### Construction

The transmitter is housed in a cabinet measuring  $9\frac{1}{2}$ " by  $16\frac{1}{4}$ " by 11". An 11" by 16" by 3" aluminum chassis fits into this enclosure, and the transmitter circuitry is constructed on it. The hole location drawing in Fig. 11-5 gives the locations of all the controls and the meter on the front panel. The layout drawing of the chassis is given in Fig. 11-6. The front panel is held to the chassis by means of the various controls, switches, and jacks located along the bottom row of the front panel. Holes should be made on the front side of the chassis corresponding to those along the bottom row on the front panel. The holes on the back side of the chassis are shown in Fig. 11-7. The major components can be mounted and located by referring to Figs. 11-8 and 11-9.

In the photo of the top of the chassis (Fig. 11-8) 5881 tubes have been substituted for the 6L6's. Either 6L6 or 5881 tubes may be used in this application. Although not shown in the photo of the top of the chassis, the entire final amplifier circuit should be shielded from the meter and surrounding tubes. The final amplifier output circuit located above the chassis can be enclosed in a shielded enclosure made of perforated aluminum stock. One side of the shield should run between L5 and the meter, and the other side between V2 and T3.

The oscillator coils (L1 and L2, Fig. 11-9) and the pi-tank coils (L4 and L5, Fig. 11-8) are supported directly by their leads, which are cut as short as practical and soldered to the rotary switches. All RF leads should be kept short, particularly those of bypass capacitors. The power cord is run in through the back panel through a rubber grommet. A knot should be tied in the cord directly inside the grommet.

### Transmitter Operation

Make sure the transmitter has been properly wired before applying power to it. Set switch S2 to the Tune position and switch



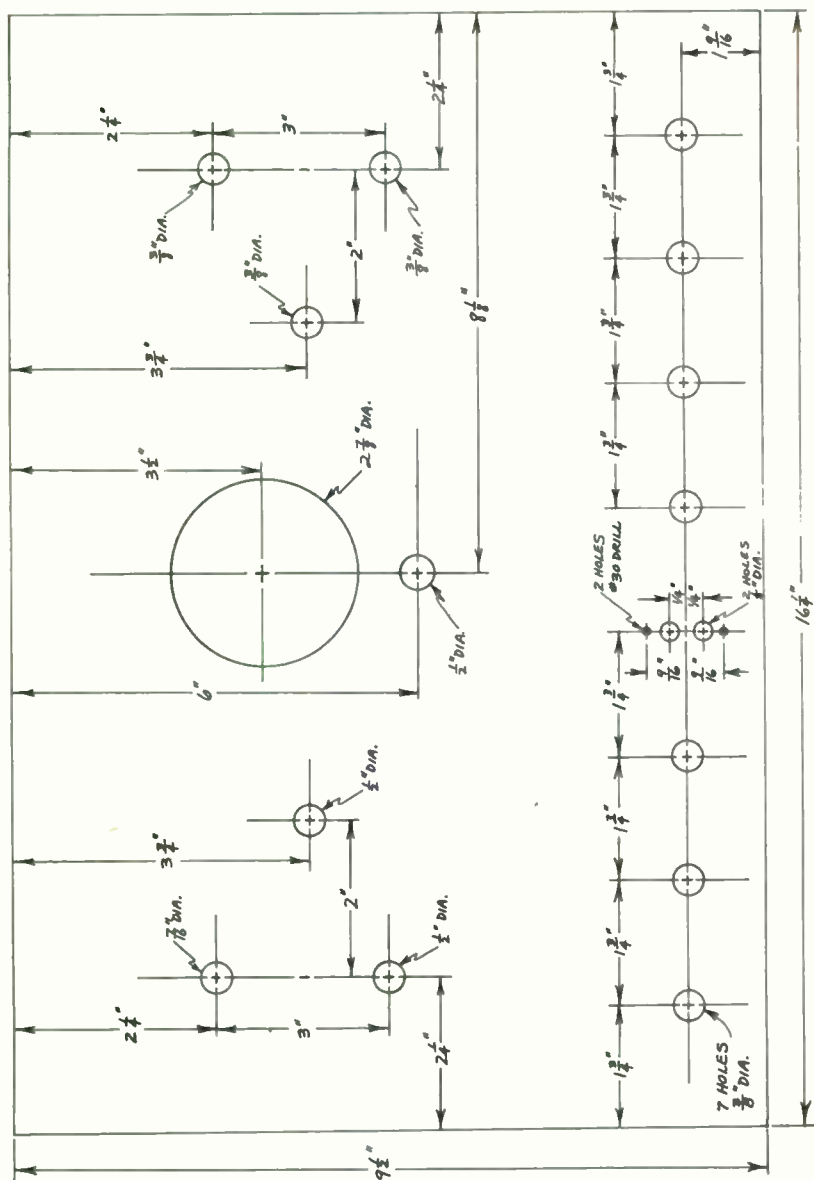


Fig. 11-5. Hole location drawing of the front panel.

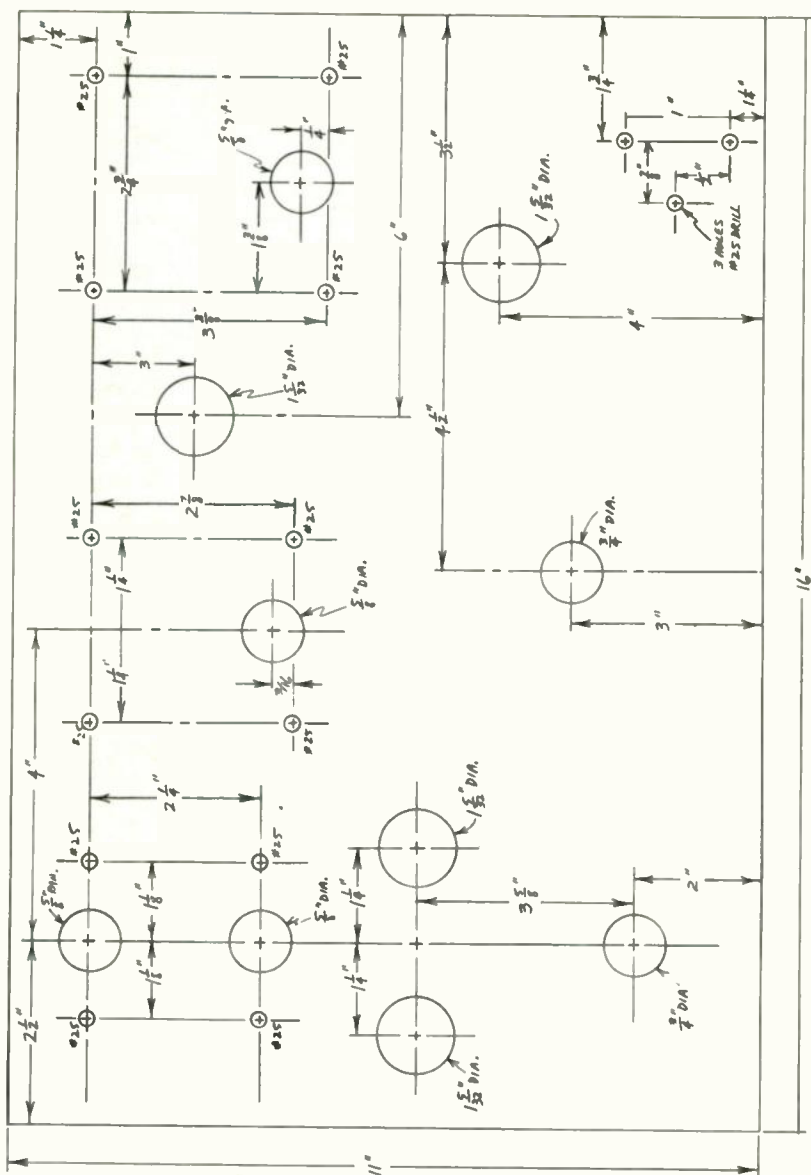


Fig. 11-6. Hole location drawing of the chassis.

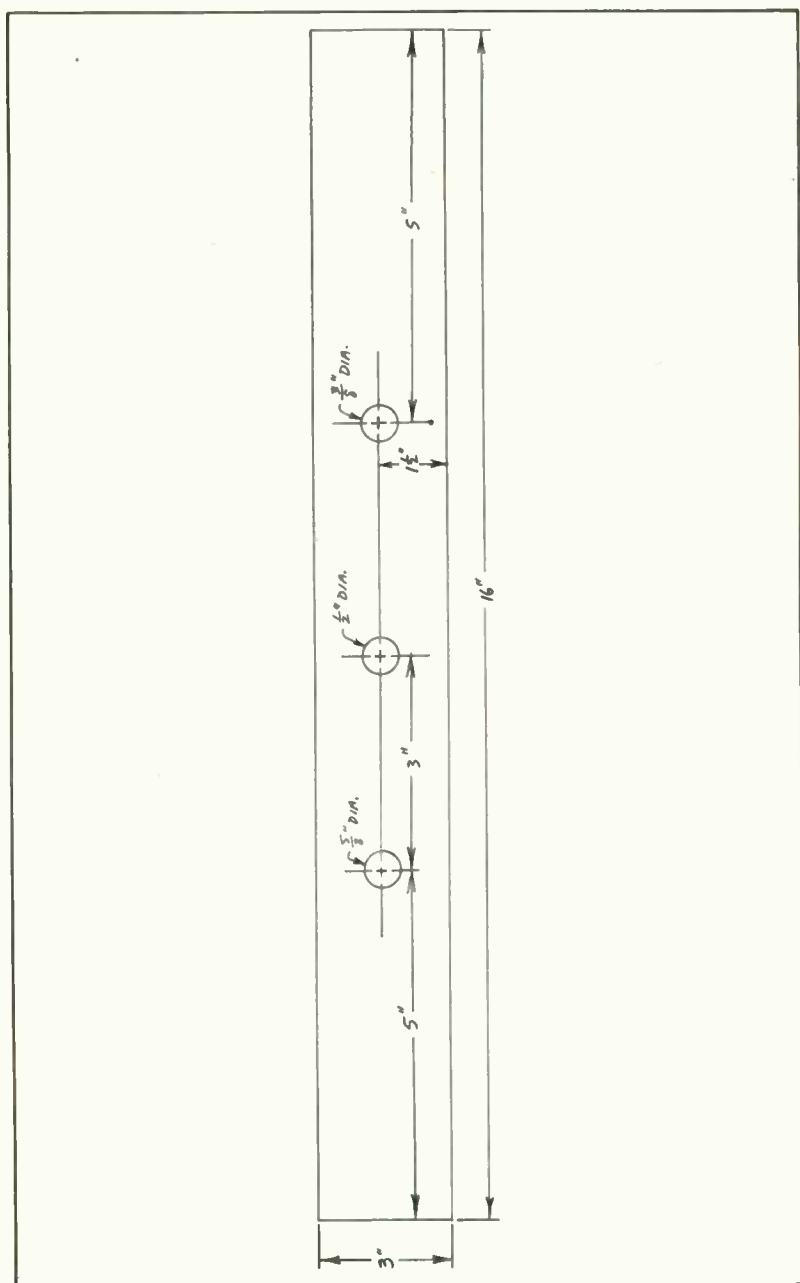


Fig. 11-7. Hole location drawing of the rear apron of the chassis.

S5 to the CW position. Insert a crystal into the crystal socket and set the bandswitches to the proper band. Now, turn the power on and check the high voltage with a VOM. The reading at the junction of CH1 and R18 should be approximately 400 volts. If this reading is obtained, proceed with the next step, which is adjusting the low-voltage output of the power supply. It is measured across C25 and the slider on R18 varied until a reading of approximately 250 volts is obtained. R18 is an adjustable wirewound resistor. Be sure to turn the power off each time you move the setting of this resistor.

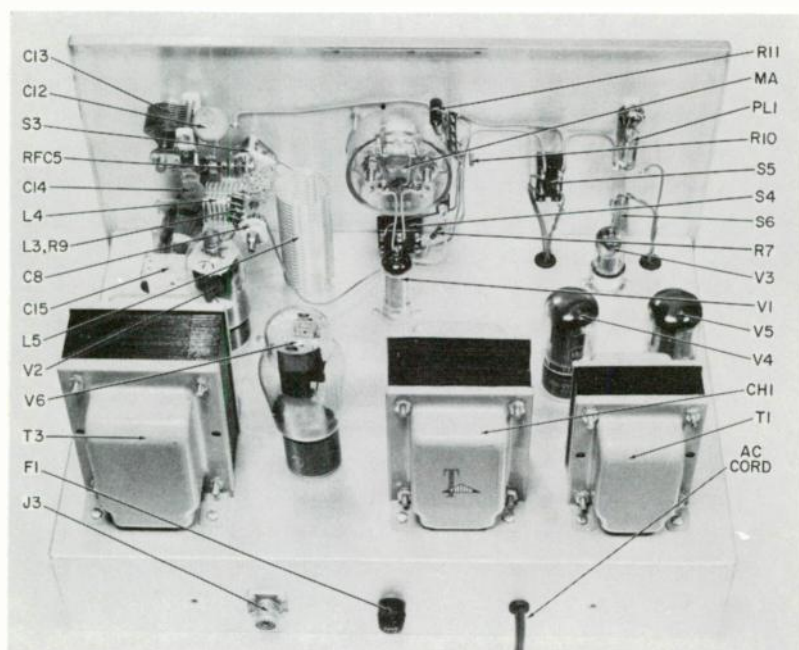


Fig. 11-8. Top view of the chassis.

With S2 still in the Tune position, adjust the oscillator by switching S4 to the Grid position, and tuning C4 for a maximum indication on the meter. In actual operation, the grid current should be held to 3 mils or less by adjusting the Grid Drive control (R2).

Connect a suitable antenna or dummy load, such as a 60-watt light bulb, to the antenna jack J3. Set switch S2 to Operate and S4 to the Plate position. Adjust the final tank circuit by tuning C13 for a dip in the meter reading and C15 for loading or maximum current. Always go back and redip C13 after C15 has been

tuned. It is a good idea to monitor the signal with a receiver when making these adjustments. The transmitter has now been checked out in the CW mode.

The final amplifier is neutralized in the following manner. Disconnect the high-voltage lead (400-volt lead) to the final amplifier and modulator. This removes the high voltage from the plate and screen of the final amplifier. Turn the power on and monitor the final amplifier grid current. Tune C13 through resonance and observe the grid current. The meter will flicker as C13 is tuned.

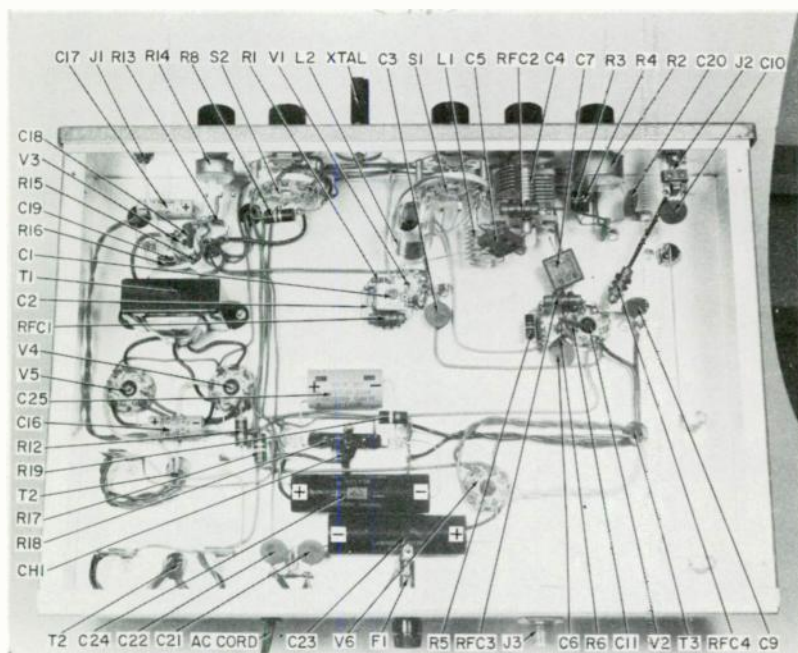


Fig. 11-9. Bottom view of the chassis.

Carefully adjust neutralizing capacitor C8, until this flickering is minimized. Turn the power off and attach the high-voltage lead once again. The final is now neutralized, and the modulator can be checked out.

Attach a crystal microphone to J1 and set S5 to the Phone position. The signal should be monitored by a fellow ham across town, and the optimum modulator gain setting determined by an on-the-air test.

For VFO operation, an 80- or 40- meter VFO can be run directly into the crystal socket.

## Parts List

| Quantity | Item No.   | Description  |
|----------|--|--|
| 1        | C1   | 3-30—mmf standard trimmer capacitor.   |
| 1        | C2   | 220-mmF, 5%, 500V, silvered-mica capacitor.  |
| 10       | C3, C6, C9<br>C10, C11, C14,<br>C18, C20, C21<br>C22 | .01-mfd GMV, 1,000V, disc-ceramic capacitors.  |
| 1        | C4   | 8.5-102—mmF variable capacitor (Johnson 149-5 or equiv.).  |
| 1        | C5   | 680-mmF, 5%, 500V, silvered-mica capacitor.  |
| 1        | C7   | 1,000-mmF, 5%, 500V, silvered-mica capacitor.  |
| 1        | C8   | 15-mmF midget variable capacitor (Johnson 15J12 or equiv.).  |
| 1        | C12  | .01-mfd GMV, 1.2kv, disc-ceramic capacitor.  |
| 1        | C13  | 13.5-140—mmF variable capacitor (Johnson 149-6 or equiv.).   |
| 1        | C15  | 2-section 10-365—mmF midget variable broadcast capacitor (both sections paralleled).   |
| 1        | C16  | 10-mfd, 50VDC, electrolytic capacitor.   |
| 1        | C17  | 10-mfd, 25VDC, electrolytic capacitor.   |
| 1        | C19  | 39-mmF, 10%, 1,000V, disc-ceramic capacitor.   |
| 2        | C23, C24   | 10-mfd, 600VDC, electrolytic capacitors.   |
| 1        | C25  | 16-mfd, 450VDC, electrolytic capacitor.  |
| 1        | R1   | 47,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R2   | 10,000-ohm, 5-watt potentiometer.  |
| 2        | R3, R4   | 10,000-ohm, 1-watt, 10%, carbon resistors.   |
| 1        | R5   | 15,000-ohm, 1-watt, 10%, carbon resistor.  |
| 1        | R6   | 10-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R7   | 33-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R8   | 15,000-ohm, 2-watt, 10%, carbon resistor.  |
| 1        | R9   | 47-ohm, 2-watt, 10%, carbon resistor.  |
| 1        | R10  | 1,200-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R11  | 15-ohm, 2-watt, 10%, carbon resistor.  |
| 1        | R12  | 360-ohm, 2-watt, 5%, carbon resistor.  |
| 1        | R13  | 620-ohm, 1/2-watt, 5%, carbon resistor.  |
| 1        | R14  | 1-megohm potentiometer.  |
| 1        | R15  | 100,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R16  | 1-megohm, 1/2-watt, 10%, carbon resistor.  |
| 2        | R17, R19   | 100,000-ohm, 2-watt, 10%, carbon resistors.  |
| 1        | R18  | 5,000-ohm, 10-watt, adjustable wirewound resistor.   |
| 1        | L1   | 8 turns No. 18 tinned-copper wire, wound to 5/8" diameter, spaced to 1-inch length, tapped 5 turns down from plate end (Air Dux 508T or B & W 3006 coil stock, or equiv.).     |
| 1        | L2   | 40 turns No. 24 tinned-copper wire, wound to 1" diameter, spaced to 1 1/4" length, tapped 7 to 15 turns down from plate end (Air Dux 832 or B & W 3016 coil stock, or equiv.). |
| 1        | L3   | 4 turns of No. 14 copper wire wound around R9.   |
| 1        | L4   | 8 turns No. 16 tinned-copper wire, wound to 1 1/4" diameter, spaced to 1" length, tapped 5 turns down  |

## Parts List—cont'd

| Quantity | Item No.               | Description   |
|----------|------------------------|---|
| 1        | L5                     | from plate end (Air Dux 1008T or B & W 3018 coil stock, or equiv.).<br>25 turns No. 16 tinned-copper wire, wound to 1 1/4" diameter, spaced to 3" length, tapped 8 to 18 turns down from plate end (Air Dux 1008T or B & W 3018 coil stock, or equiv.). |
| 4        | RFC1, RFC2, RFC3, RFC4 | 2.5 mh RF chokes (Millen 6302 or equiv.).   |
| 1        | RFC5                   | 1.0 mh RF choke (Millen 4527 or equiv.).  |
| 1        | CH1                    | 10 henry, 200ma, DC choke (Triad C-16A or equiv.).  |
| 1        | T1                     | Plate to p-p grids driver transformer (Triad A-85X).  |
| 1        | T2                     | 30-watt multimatch modulation transformer (Triad M-15A or equiv.).  |
| 1        | T3                     | Power transformer—Secondaries: 400-0-400VAC @ 200 ma; 5VAC @ 3A; 6.3VAC @ 6A (Triad R-121A or equiv.).  |
| 2        | S1, S3                 | 1-pole, 5-position ceramic rotary switches (Centralab 2501 or equiv.).  |
| 1        | S2                     | 2-pole, 3-position ceramic rotary switch (Centralab 2505 or equiv.).  |
| 2        | S4, S5                 | DPDT toggle switches.   |
| 1        | S6                     | SPST toggle switch.   |
| 1        | F1                     | 3-amp, 3AG fuse.  |
| 1        | PL1                    | 6.3VAC, No. 47, bayonet-base pilot lamp.  |
| 1        | Xtal                   | Crystal (3.5 mc for 80 or 40 meters; 7 mc for 40, 20, 15, or 10 meters).  |
| 1        | V1                     | 5763 pentode tube.  |
| 1        | V2                     | 6DQ6 beam-power output tube.  |
| 1        | V3                     | 12AT7 speech amplifier tube.  |
| 2        | V4, V5                 | 6L6G beam power tubes.  |
| 1        | 5R4                    | Rectifier tube.   |
| 1        | J1                     | Microphone connector (Amphenol 75 PC1M or equiv.).  |
| 1        | J2                     | Closed-circuit phone jacks.   |
| 1        | J3                     | Coaxial chassis receptacle SO-239 (Amphenol 83-1R).   |
| 1        | MA                     | 1.5-ma, DC meter, 30-ohm internal resistance (Triplett 327-PL or equiv.).   |
| 1        |                        | Crystal socket (Millen 33102 or equiv.).  |
| 8        |                        | Knobs (National Type HR or equiv.).   |
| 1        |                        | 9 1/2" X 16" X 11" equipment cabinet, including 11" X 16" X 3" chassis, aluminum (California Chassis Co. Type LTC-472 or equiv.).   |
| 1        |                        | Fuse holder.  |
| 3        |                        | 3/8" rubber grommets.   |
| 4        |                        | Ceramic octal tube sockets.   |
| 2        |                        | 9-pin ceramic miniature tube sockets.   |
| 8        |                        | Solder lugs.  |
|          |                        | 6-32 machine screws and nuts.   |
|          |                        | 4-40 machine screws and nuts.   |
|          |                        | Hook-up wire.   |
|          |                        | Solder.   |



# 12 Two-Meter Phone Transmitter

The 2-meter phone transmitter described in this chapter can be used as a fixed station or mobile transmitter. It is crystal controlled and plate modulated, and it is capable of running approximately 15 watts of power. The rig is ideal for the novice or technician as well the general-class amateur; however, its construction should be tackled only by those who have had some experience in construction of VHF circuits.

The transmitter and the separate AC power supply for fixed station operation are pictured in Fig. 12-1. The transmitter proper is a rather compact unit and is ideally suited for mobile operation, being easily mounted under the dash of the auto. Any number of schemes for supplying power can be used for mobile operation. For instance, a dynamotor, vibrator supply, or transistorized DC-DC converter may be employed. In any case, the supply should be capable of delivering approximately 250 to 300 volts DC, at currents of 150 to 200 ma. For fixed-station operation, tubes with 6-volt filaments, powered by the 6-volt winding in the power transformer are employed. Naturally, if your automobile has a

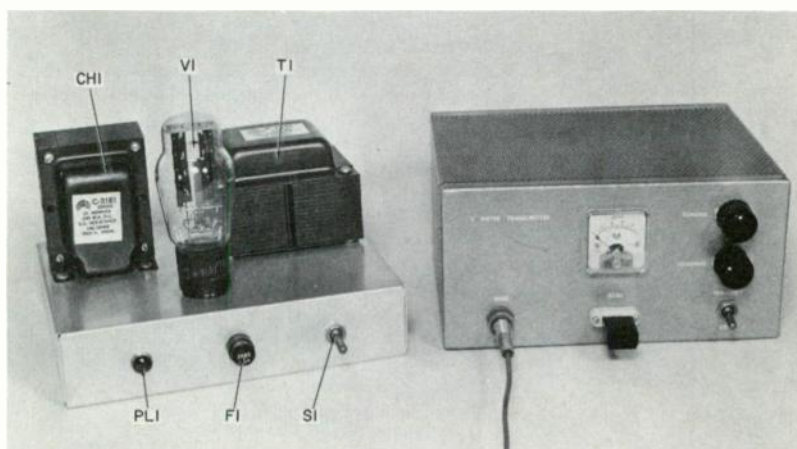


Fig. 12-1. The completed 2-meter transmitter with AC power supply.

6-volt ignition system, the tubes can be powered directly from the auto battery. If you car has a 12-volt system, a direct equivalent tube with a 12-volt filament is specified. More about these substitutions later.

### Circuit Description

The schematic diagram of the rig is shown in Fig. 12-2, and one of the AC power supply is shown in Fig. 12-3. The oscillator (V1) is crystal controlled and is identical to the oscillators used in previous chapters. A standard 8-mc crystal, or 24-mc third-overtone type crystal may be used. L1 resonates with the plate capacity of V1 and the grid capacity of V2 to a frequency of 24 mc. In the case of the 8-mc crystal, L1 is tuned to the third harmonic, or the oscillator is tripling. When a 24-mc crystal is used, the oscillator runs "straight through," with L1 still tuned to the 24 mc frequency.

The oscillator output is capacitively coupled to the grid of V2, which functions as a tripler. The output of V2 is tuned to 72 mc by L2 and C9. The final amplifier (V3) is a beam-power pentode and also serves as a doubler with an output at 144 mc. L3 and C12 form a series-resonant tank circuit for V3. The RF output from the final stage is link coupled by L4 to the antenna. C13 is used to tune out the reactance of the link.

Tuning the transmitter for maximum output is done independently of the actual circuit. The tuning indicator is actually an untuned field-strength meter, or wavemeter. It consists of a germanium diode (D1) for rectifying the RF, a DC milliamp meter (MA), and a current limiting resistor (R8). The component leads are left long, and soldered to form a closed loop. This closed loop, being in proximity with the final tank circuit, picks up the RF, rectifies it, and indicates the relative output on the meter. In operation, C12 and C13 are both tuned for maximum meter indication.

V4 serves as a microphone preamplifier for the modulator section. This circuit provides enough gain to allow a crystal mike to be employed for fixed station operation. However, since a crystal mike is very delicate, a dynamic mike should be used for mobile operation. Either type of microphone will work in the circuit. The push-pull, modulator-output stage consists of V5 and V6.

The power supply (Fig. 12-3) is conventional. V1 serves as a full-wave rectifier working into a pi-type filter consisting of C1, C2, and CH1. The bleeder resistor (R1) keeps the output voltage from surging to a high value when the load is removed. It also


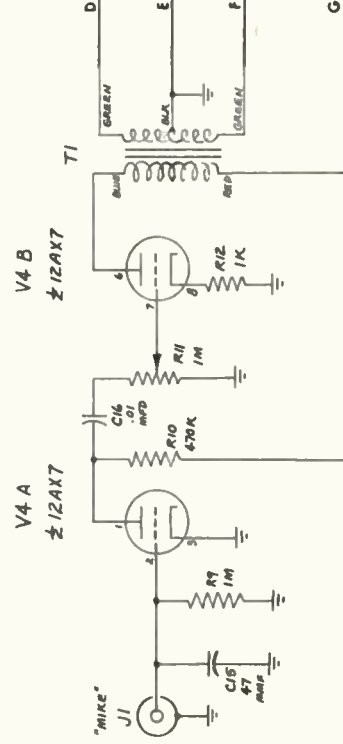
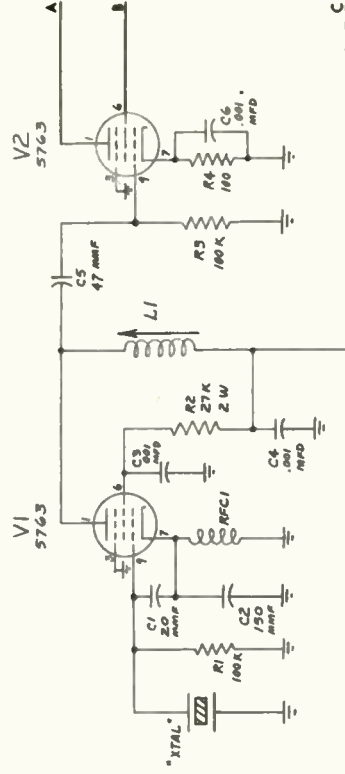


Fig. 12-2. Schematic of

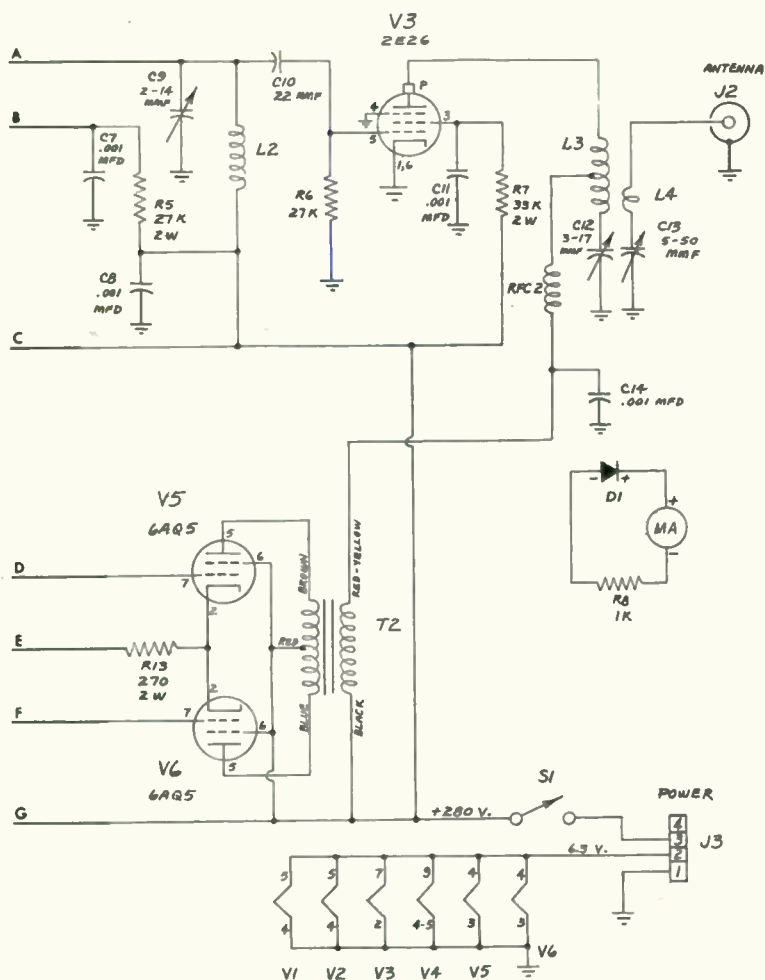

the 2-meter phone transmitter.

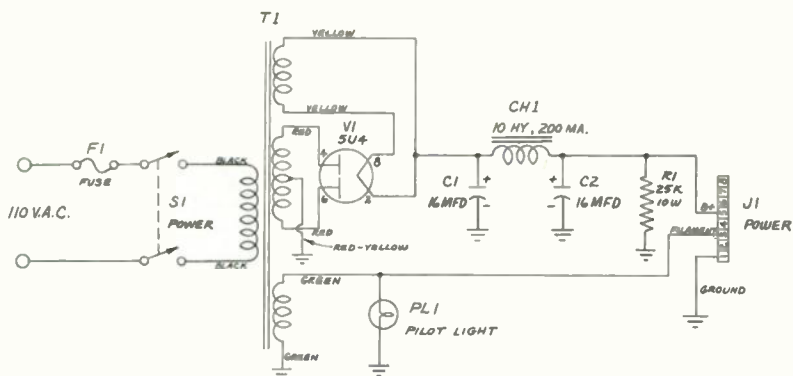


Fig. 12-3. Schematic of the power supply.

discharges the capacitors when there is no load on the supply, and the power is turned off. The pilot light indicates the power is on.

### Construction

The hole location drawing for the front panel is given in Fig. 12-4, while the one for the top of the chassis in Fig. 12-5 and for the rear apron of the chassis in Fig. 12-6.

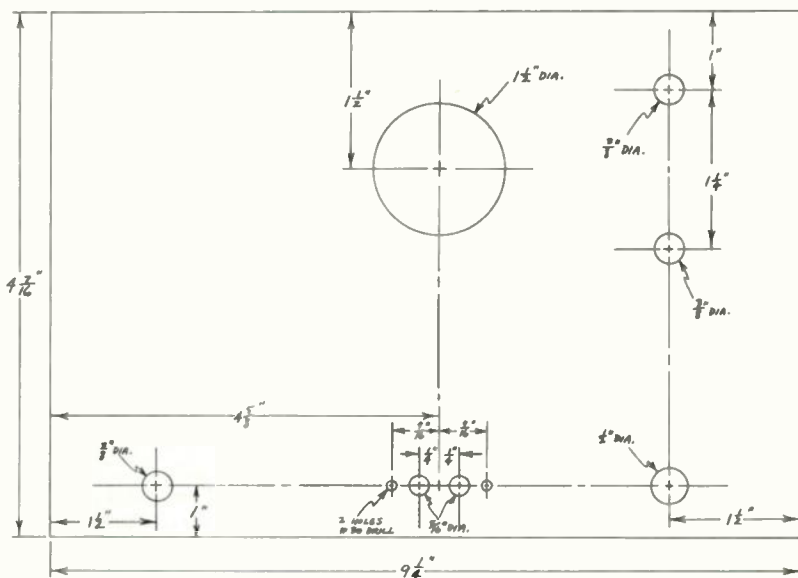


Fig. 12-4. Hole location drawing of the front panel.

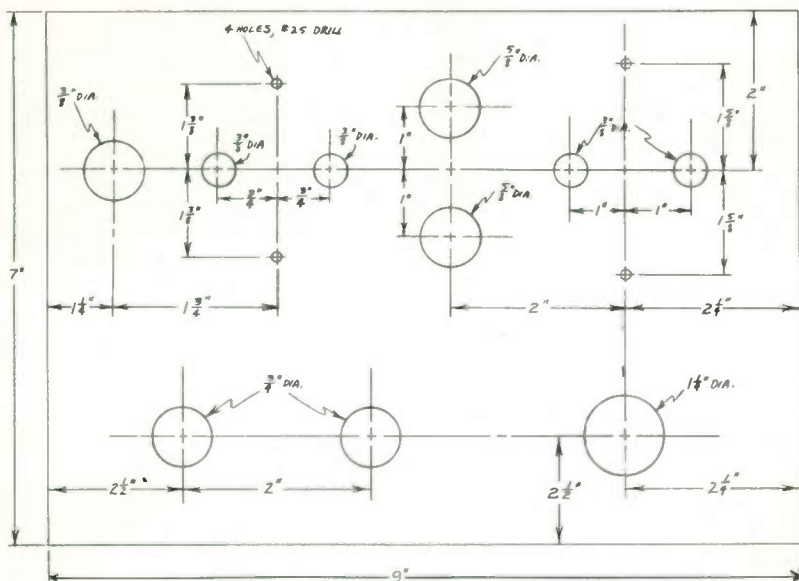


Fig. 12-5. Hole location drawing of the chassis.

The transmitter is packaged in an enclosure measuring  $4\frac{7}{16}$ " by  $9\frac{1}{4}$ " by  $7\frac{1}{4}$ " and an aluminum chassis measuring 7" by 9" by  $1\frac{1}{2}$ ". The tube socket for V3 is recessed approximately  $\frac{1}{2}$  inch below the chassis. The photos in Figs. 12-7 and 12-8 show the location of all the components, both above and below the chassis. The layout of the front panel is shown in Fig. 12-9. When wiring the RF

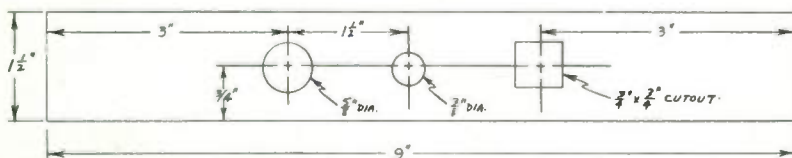


Fig. 12-6. Hole location drawing of the chassis rear panel.

section of the transmitter, keep the component leads as short as possible and use direct, point-to-point wiring; this is very important at VHF frequencies. The wiring of the modulator and power supply is not critical. The power supply is connected to the transmitter with an interconnecting cable made by twisting together three 24" lengths of heavy hook-up wire and connecting the plug and socket to the ends.

A piece of shielded wire should be run from the mike jack (J1) to the grid of V4. This is a fairly long run, and shielded wire is

recommended. C15 is an RF bypass capacitor; it is needed to keep any stray RF out of the modulator circuit. However, in some installations this bypass capacitor may not be adequate and it may be necessary to insert a 2.5-mh RF choke in series with the shielded line at the mike jack.

A piece of RG-58 coax is used to connect link coil L4 to antenna jack, J2. RG-58 is small diameter 52-ohm coax.

As mentioned previously in this chapter, the tubes specified for this unit have 12-volt filament equivalents. The 5763 can be replaced by a 6417 for 12-volt operation, the 2E26 by a 6893, and the 6AQ5 by a 12AQ5. These substitutions require no wiring changes. However, V4, the 12AX7, has a split filament for either 6-volt operation or 12-volt operation. The wiring configuration in the schematic diagram shows the filament hooked up for parallel or 6-volt operation. If the rig is to be used in a 12-volt system, it will be necessary to change the wiring of the 12AX7 filament. This is done very simply. Pin 9 on the tube is the center tap; for 12-volt operation no connections are made to this pin and connections are made to pins 4 and 5 only.

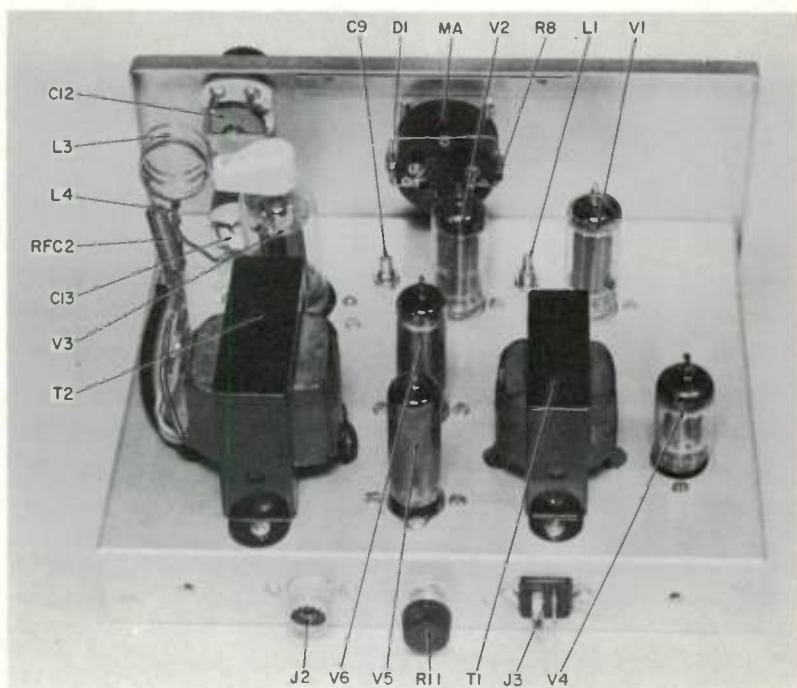


Fig. 12-7. Inside top chassis view of the transmitter.



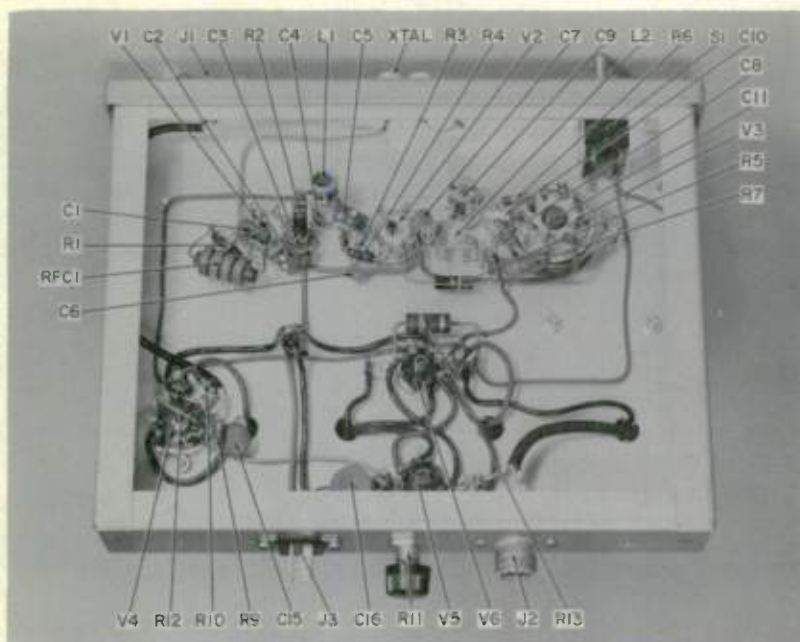


Fig. 12-8. Bottom view of the transmitter.

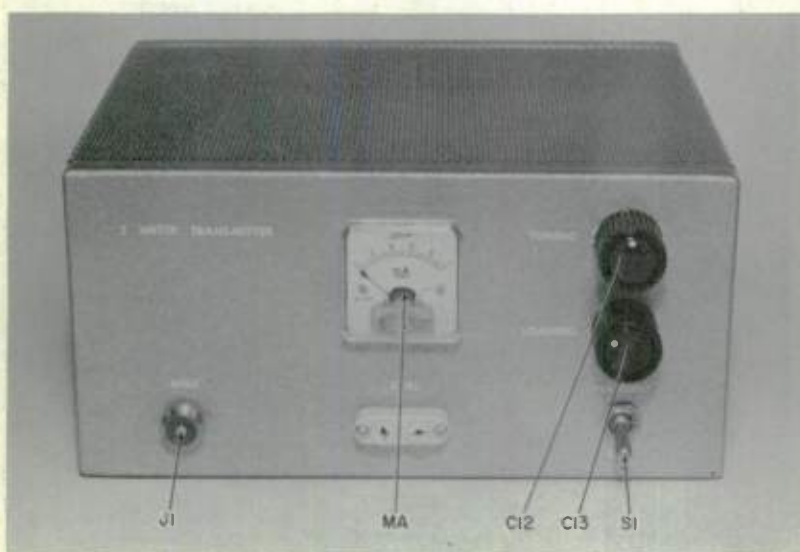


Fig. 12-9. Close-up view of the front panel.

## Operation

Aligning the transmitter is a relatively easy task. The coils should be checked and set to their operating frequencies first with the aid of a grid-dip meter. The stages can then be peaked with a wavemeter or by monitoring with a receiver (with the power turned on). The output tuning indicator can also be used to peak the stages preceeding the final amplifiers, by tuning for a peak reading on the meter. A cross-town on-the-air check with another station is best for checking the optimum setting of the modulator gain control (R11).

## Transmitter Parts List

| Quantity | Item No.                        | Description   |
|----------|---------------------------------|---|
| 1        | C1                              | 20-mmF, 5%, 500V, silvered-mica capacitor.  |
| 1        | C2                              | 150-mmF, 5%, 500V, silvered-mica capacitor.   |
| 7        | C3, C4, C6, C7,<br>C8, C11, C14 | .001-mfd GMV, 1,000V, disc-ceramic capacitors.  |
| 1        | C5                              | 47-mmF, 5%, 500V, silvered-mica capacitor.  |
| 1        | C9                              | 2-14-mmF, miniature variable capacitor Johnson 160-107 or equiv.).  |
| 1        | C10                             | 22-mmF, 10%, 1,000V, disc-ceramic capacitor.  |
| 1        | C12                             | 3-17-mmF variable capacitor (Johnson 157-2 or equiv.).  |
| 1        | C13                             | 5-50-mmF variable capacitor (Johnson 157-4 or equiv.).  |
| 1        | C15                             | 47-mmF, 10%, 1,000V, disc-ceramic capacitor.  |
| 1        | C16                             | .01-mfd GMV, 1,000V, disc-ceramic capacitor.  |
| 2        | R1, R3                          | 100,000-ohm, 1/2-watt, 10%, carbon resistors.   |
| 2        | R2, R5                          | 27,000-ohm, 2-watt, 10%, carbon resistors.  |
| 1        | R4                              | 100-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R6                              | 27,000-ohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R7                              | 33,000-ohm, 2-watt, 10%, carbon resistor.   |
| 2        | R8, R12                         | 1,000-ohm, 1/2-watt, 10%, carbon resistors.   |
| 1        | R9                              | 1 megohm, 1/2-watt, 10%, carbon resistor.   |
| 1        | R10                             | 470,000-ohm, 1/2-watt, 10%, carbon resistor.  |
| 1        | R11                             | 1 megohm potentiometer.   |
| 1        | R13                             | 270-ohm, 2-watt, 10%, carbon resistor.  |
| 1        | R15                             | 1.5 to 3.2 $\mu$ h coil. (Millen 4404 or equiv., or 12 1/4 turns of No. 26 enameled copper wire closewound on 3/8" slug-tuned coil form).     |
| 1        | L2                              | 3 turns No. 20 tinned-copper wire, wound 5/8" diameter, spaced to 3/16" length, or cut from Air Dux 516T or B & W 3007 or equiv. coil stock). |
| 1        | L3                              | 3 turns No. 16 tinned-copper wire, wound 1" diameter, spaced to 3/4" length, center-tapped.   |
| 1        | L4                              | 1-turn link of small hook-up wire wound around center of L3.  |
| 1        | RFC1                            | 2.5 $\mu$ h RF choke (Millen 4666, National R-50, or equiv.).   |
| 1        | RFC2                            | 7.0 $\mu$ h RF choke (Ohmite Z-50 or equiv.).   |
| 1        | T1                              | Driver transformer (Triad A-85X or equiv.).   |

### Transmitter Parts List—cont'd

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | T2       | Modulation transformer (Triad M-6X or equiv.).   |
| 1        | S1       | SPST toggle switch.  |
| 1        | Xtal     | 8- or 24-mc crystal.   |
| 1        | D1       | 1N34 or 1N38 germanium diode.  |
| 2        | V1, V2   | 5763 (6V) or 6417 (12V) pentode tubes.   |
| 1        | V3       | 2E26 (6V) or 6893 (12V) output tube.   |
| 1        | V4       | 12AX7 dual-triode tube (6 or 12V).   |
| 2        | V5, V6   | 6AQ5 (6V) or 12AQ5 (12V) beam-power tubes.   |
| 1        | J1       | Microphone connector (Amphenol 75PC1M or equiv.).  |
| 1        | J2       | Coaxial chassis receptacle SO-239 (Amphenol 83-1R or equiv.).  |
| 1        | J3       | Four-connector chassis-mounting plug (Cinch-Jones P-304 or equiv.).  |
| 1        | MA       | 0-1 ma DC miniature milliammeter (Lafayette TM-400 or equiv.).   |
| 1        |          | Crystal socket (Millen 33102 or equiv.).   |
| 2        |          | Knobs (National Type HR or equiv.).  |
| 1        |          | 4 7/16" X 9 1/4" X 7 1/4" cabinet, including 9" X 7" X 1 1/2" aluminum chassis (California chassis LTC-464 or equiv.). |
| 1        |          | Plate cap for 2E26 tube.   |
| 1        |          | Ceramic octal tube socket.   |
| 2        |          | Ceramic 9-pin miniature tube socket.   |
| 1        |          | Bakelite 9-pin miniature tube socket.  |
| 2        |          | Bakelite 7-pin miniature tube socket.  |
| 2        |          | 1/2" spacers for V3 socket mounting.   |
|          |          | 6-32 machine screws and nuts.  |
|          |          | 4-40 machine screws and nuts.  |
|          |          | Hook-up wire.  |
|          |          | Solder.  |

### Interconnecting Cable Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        |          | Octal connector plug (Amphenol 86-PM8 or equiv.).            |
| 1        |          | 4-pin cable socket with clamp (Cinch-Jones S-304 or equiv.). |
| 3        |          | 24" lengths of heavy wire twisted together to form 1 cable.  |

### Power Supply Parts List

| Quantity | Item No. | Description  |
|----------|----------|--|
| 2        | C1, C2   | 16-mfd, 450VDC, electrolytic capacitors.             |
| 1        | R1       | 25,000-ohm, 10-watt, wirewound resistor.             |
| 1        | CH1      | 10 henry, 200 ma, DC choke (Merit C-3181 or equiv.). |

## Power Supply Parts List—cont'd

| Quantity | Item No. | Description  |
|----------|----------|--|
| 1        | T1       | Power transformer—Secondaries: 280-0-280 VAC @ 200 ma; 6.3 VAC @ 8A; 5VAC @ 3A (Merit P-2842 or equiv.). |
| 1        | S1       | DPST toggle switch.  |
| 1        | F1       | 2-amp fuse.  |
| 1        | PL1      | No. 47 bayonet-base 6.3V pilot lamp.   |
| 1        | V1       | 5U4G rectifier tube.   |
| 1        | J1       | Octal socket (Amphenol 78-S8 or equiv.).   |
| 1        |          | 7" X 9" X 2" aluminum chassis.   |
| 1        |          | Fuse holder.   |
| 1        |          | Octal tube socket for V1 (Amphenol 78-S8 or equiv.).   |
| 1        |          | Pilot-light assembly (E.F. Johnson 147-306-2 or equiv.).   |
| 1        |          | AC power cord (length as required).  |
| 1        |          | AC power plug.   |
|          |          | 6-32 machine screws and nuts.  |
|          |          | Hook-up wire.  |
|          |          | Solder.  |