

with ANISOTROPIC ALNICO

HEART OF MODERN LOUDSPEAKERS The following complete range now available:-

Model 3C, size 3": Personal Portables and Midget Standard Receivers.

Model 5C, size 5": Standard Small Radios.

Model 5CH, size 5": Intercom. Systems, 20-ohm Voice Coil.

Model 5H, size 5": Super-sensitive for standard small radios.

Model 5HH, size 5": Super-sensitive for intercom. systems, 20-ohm Voice Coil

Model 6H, size 6": Standard small radios.

Model 6K, size 6": Super-sensitive speaker for car radios, portables, and standard battery receivers.

New Zealand Manufacturers.

Model 6J, size 6": Sensitive speaker for battery sets and car radios.

Model 8H, size 8": Low-priced speaker for standard receivers and extensions.

Model 8K, size 8": Sensitive speaker for standard radios and extensions.

Model 8M, size 8": Super-sensitive for battery sets and high-quality mantel standard radios.

Model 10M, size 10": Sensitive speaker for large standard mantel radios.

Model 10/42, size 10": Super-sensitive speaker for public address and quality console receivers.

Model 12M, size 12": Low-priced speaker for console radios.

Model 12/0, size 12": **Ouality super-sensitive speaker** for console radios and radio grams.

Model G12, size 12": High-fidelity 15 watt speaker for quality public address and radio grams.

Model 12/U, size 12": As G12, but still higher quality for super radio grams.

Model 6-9H, size 6" x 9": Oval speakers.

Model 6-9L, size 6" x 9": Oval speakers.

Order from Dealers

wan Electric Co.

AUCKLAND • WELLINGTON • CHRIST CHURCH • DUNEDIN

Are YOU a Subscriber to Radio & Electronics?

The circuits of this *Digest* are taken from *Radio and Electronics* over a period of three years. Every month *Radio and Electronics* appears complete with new circuits and full data.

If the material in this Digest of Circuits appeals to you, then you will want to be a regular subscriber to RADIO AND ELECTRONICS.

Be abreast of radio development—Subscribe NOW—PLACE YOUR ORDER with your usual bookseller or radio dealer.

SUBSCRIPTION 23/- p.a. POST FREE—12 ISSUES

This "Digest of Circuits" and "Radio and Electronics" are published by RADIO AND ELECTRONICS (N.Z.), LTD.

Offices and Laboratory:

46 Mercer Street, Wellington.

P.O. Box 22, Government Buildings, Wellington. Telephone 44-919

ONLY 50 ORDERS CAN BE TAKEN!



THIS OFFER CANNOT BE REPEATED

Place Your Order For Your Model 640

'EDDYSTONE'

NOW!

The famous British firm of Stratton & Co., Ltd., as a goodwill gesture to the amateurs of the world and in order to reintroduce their post-war products, produced the 640 Eddystone Receiver at a price far below its real value. The very large-planned production is now completed, and the verdict of amateurs all over the world is that it is a triumphant success! Of course, the 640 offer cannot be repeated.

So, our advice is to get in now and procure one of these outstanding receivers at the 'rock-bottom' price they are offered at—it's the lowest-priced receiver, considering its features, you're likely to see for many a long day.

£52/6/6

WITH 688 SPEAKER



Every amateur enthusiast knows the set-up of the "Eddystone" Model 640, but if you're in doubt write for illustrated leaflet and descriptive literature.

Place an order now with your local dealer or

FEAR'S RADIO AND CYCLE CO., LTD., Wellington
TRICITY HOUSE. Christchurch

THICHT HOUSE, CHISTOMICA

ECLIPSE RADIO LTD., Dunedin

N.Z. Distributors:

ARNOLD & WRIGHT LTD., Auckland, Wellington, Christchurch

CONTENTS

RECEIVER SECTION

Pa	ige	Page
Some Crystal Sets	7	A High-quality Six-valve Dual-wave Re-
Using a Wave-trap with a Crystal Set	8	ceiver 33
Improving "Crystal" Sets by Using a Valve		A High-quality Broadcast Tuner 36
Instead of the Crystal	9	An Experimental Two-stage I.F. Amplifier 37
A Simple One-valve Regenerative Set	9	A High-gain, Low-noise Preamplifier Using
	10	An Advanced Super-regenerative Receiver
	11	for Six Metres 42
	12	A High-performance 10-Metre Converter 43
	14	The Radel Dual-wave Six 44
	18 20	An Idea for a High-fidelity Tuner 47
mi p 11 III P	21	A Seven-valve Quality Broadcast Receiver 50
COL D 11 1 C D 1 D'	22	A Radio Tuner with Multi-point Selectivity
m P II P II P	24	for High-fidelity Reproduction 54
THE DOLL DE LIE D'	27	The Radel All-wave Eight 56
	30	The Radel DX Broadcast 12 58
THE RUCCI RUMOCK DUM WAVE THE MAIN	00	The Marie Die Production 12 mm mm 30
AMPLIF	IER	SECTION
Pa	ige	Page
	ige 63	Page A Very High-quality 20-Watt Amplifier 77
A Compact 4½-Watt Gramophone Amplifier	- 4	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier	63	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation	63 64	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier	63 64 64	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier	63 64 64 65	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier	63 64 64 65 68 73	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Con-
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier	63 64 64 65 68	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio	63 64 64 65 68 73	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Con-
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio	63 64 64 65 68 73 75	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio	63 64 64 65 68 73 75	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers	63 64 64 65 68 73 75	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers	63 64 64 65 68 73 75	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other Low-output) Pick-ups 83 T SECTION
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers INSTRUM	63 64 64 65 68 73 75 76	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other Low-output) Pick-ups 83 T SECTION
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers INSTRUM INSTRUM Pa An A.C./D.C. 24-Range Multi-meter	63 64 64 65 68 73 75 76	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other Low-output) Pick-ups 83 T SECTION Page A 3 in. Service Oscilloscope 91
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers INSTRUM Pa An A.C./D.C. 24-Range Multi-meter A Bridge-type Capacity Analyser	63 64 64 65 68 73 75 76	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other Low-output) Pick-ups 83 T SECTION Page A 3 in. Service Oscilloscope 91 A 5 in. Service Oscilloscope 92
A Compact 4½-Watt Gramophone Amplifier A Two-valve Battery-operated Amplifier A Small Amplifier for Vibrator Operation A Quality 6A3 Amplifier A Response-compensated 6L6 Amplifier The Enlarged 6A3 Amplifier A New Triode Audio Amplifier Some Tested Circuits for 807's as Audio Amplifiers INSTRUM Pa An A.C./D.C. 24-Range Multi-meter A Bridge-type Capacity Analyser	63 64 64 65 68 73 75 76	A Very High-quality 20-Watt Amplifier 77 A 50-Watt Amateur's Modulator Using P-P 807's 79 Two Excellent Volume Expanders 82 A Cathode-follower Audio Mixer Circuit 83 An Additional R-C Amplifier Stage for Using a Guitar Pick-up with a Conventional Amplifier 83 A Pre-amplifier for Moving-coil (and Other Low-output) Pick-ups 83 T SECTION Page A 3 in. Service Oscilloscope 91

FOREWORD

In presenting a new publication it seems to be a convention that the Editor should, in his preface or foreword, explain to his readers the aims and objects of the new book, and give a brief indication of the scope of the material. In our case, this is particularly easy to do, and for readers of the monthly periodical *Radio and Electronics* it will hardly be necessary. However, we hope that many who purchase this book will be among the non-readers of the former, and for those a word of explanation might not go amiss.

Radio and Electronics was first published in April, 1946. Since then, over a period of over three years, there have been presented in its pages a wide variety of subject matter, some of which has been of interest to radio hobbyists, some to amateur transmitters, and some to those professionally engaged in the many types of commercial radio activity that exist in this country. Unfortunately, a small country like New Zealand, with a population of less than two million, cannot support a number of technical periodicals, each on the limited field of Radio, and each addressed to only one section of the total number of people interested in working with thermionic valves. Because of this, which is no more than an undeniable economic fact, we, as the only publishers of technical radio and electronic data in the country, are compelled to issue only a single monthly magazine, which must attempt to appeal, through its reader material, to all the classes of person we have detailed above, not to mention others that have not been singled out for classification.

As a result of all these things, the pages of Radio and Electronics have, over a three-year period, been graced by practical design information on a very wide variety of topics. For example, in the way of receiver circuits alone, we have covered the field from the simplest crystal and one-valve sets to highly complex superheterodynes, suitable only for building by the more experienced constructors. While from time to time new receivers are published in Radio and Electronics, and will continue to be, it is clearly impossible to keep on repeating ourselves except at reasonably long intervals. Thus, for the reader predominantly interested in, say, receivers, there might be a considerable period during which the sort of constructional article in which he is mainly interested is not featured very often.

It is mainly to cater for constructors who would like to have on hand a comprehensive range of circuits for a variety of types of equipment, ranging from simple receivers to complex test equipment, that this collection of circuits is being published, and it is hoped, too, that many who have not hitherto been acquainted with the parent publication, Radio and Electronics, will realize from a perusal of the Digest, that the former caters for all tastes in radio matters.

The information in this book has been stripped down to what may be termed its bare bones. Circuits, photographs of completed equipment, and working drawings for the necessary metal-work are included, where all these things have been originally featured in complete descriptive articles. The information here is complete in itself, but there is no room in a book of this kind to go into detailed appreciations of the merits of individual circuits, or to give detailed explanations of how the more abstruse of them work. All this has been done, and can be found in the appropriate copy of Radio and Electronics, to which reference is made in each title. No doubt many readers of this Digest will wish to obtain copies of the original articles, and the references to them have been included because, except for one issue, which is completely out of print, and for a few others, of which only a few copies are left, all back numbers of Radio and Electronics are available.

Any reader who wishes to obtain back numbers can do so either by asking any bookseller or radio dealer who stocks the journal to obtain it for him, or if he is too far from one of these, by writing direct to the publishers, "Radio and Electronics" (N.Z.) Ltd., Box 22, Government Buildings P.O. Wellington. As mentioned above, some issues are in rather short supply, so that readers are recommended to place orders for any they might want as soon as possible, in order to avoid disappointment.

We had hoped to have room to include in this volume some commonly used reference material, such as valve socket diagrams for the valve types appearing in the text, but space has unfortunately prevented this. Also, while all the most important featured articles up to December 1948 have been included, space has again compelled us to omit a few of them.

This Digest is, in the first instance, by way of being an experiment. We hope it will turn out to be a very useful one as far as our readers are concerned, but we are under no illusions that it could not be improved. As with all new ventures, experience will tell, and we hope after a suitable time interval to publish a second edition, with new material throughout, and possibly amplified by the inclusion of data and material that will be useful for reference purposes. Whether further digests make their appearance will depend mainly upon the response of readers to this one, and in launching this new publication, we would like to assure readers that we are always open to suggestions as to material that they would like included in future books of the same kind, and as to the presentation. After all, the book is being published for our readers' approval, and anything we can do to make succeeding issues of the Digestmore valuable to them, we will be only too happy to do.



Wide-range Signal Generator



ELECTRICAL TESTING INSTRUMENTS



Electronic Testmeter



High-resistance Multimeter

Circuit building requires dependable instruments. Radio enthusiasts the world around make AVO electrical testing instruments their first choice for dependability, versatility, and trouble-free service.

Products bearing this famous name are in constant demand throughout New Zealand, and we take pleasure in advising the immediate availability of a wide range of instruments, including those illustrated here.

here.
Ask for AVO electrical instruments by name.



Avo Test Bridge



Valve Characteristic Meter



NATIONAL WEED ELECTRICAL

AND ENGINEERING COMPANY LIMITED

Sole New Zealand Agents for ACWEECO Products.

Auckland

Wellington

Christchurch

Dunedin

Hamilton

Wanganui

Hastings

Matching the finest




Manufactured in New Zealand by

THIRNESHIEL AND JONES

AUCKLAND, WELLINGTON, CHRISTCHURCH, DUNEDIN, HAMILTON, PALMERSTON NORTH AND INVERCARGILL.

RECEIVERS - Some Crystal Sets

No. 3

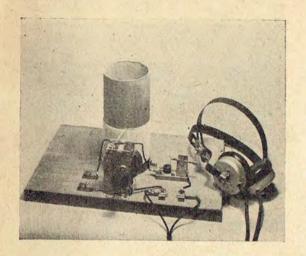

NOTES ON THESE CIRCUITS


IMPORTANT


All tuning coils can consist of 70 turns of 24 gauge D.C.C. wire, close-wound on a 3 in. former. The tuning condenser can be 0.0003 mfd, or larger. If slightly different sizes of wire are used for the coil it will not

In all cases, the aerial coil can have 30 turns of the same wire, and can be wound above the tuning coil, as shown in the right-hand photo. The taps are made simply by twisting the wire for about half an inch, and proceeding with the winding. After the whole coil is wound, the cotton is stripped from the wire so that connection can be made to the taps with an alligator clip. The photo shows the aerial coil for Circuit No. 2, where the taps are made every 5 turns.


No. 1. This is the simplest of all crystal sets. It gives quite strong signals, but is not selective. Can be used with advantage when only one station can be received, and there is no interference from another. No. I also suffers from alteration of the tuning, depending on the length of the aerial. With a long one, some stations might be off the dial. The photo above shows No. 1 built up and ready to go.

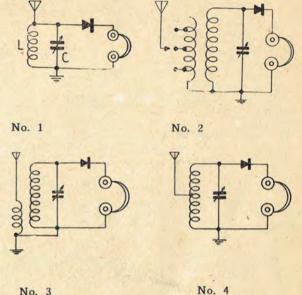No. 2. This is a simple but good circuit. The tapped aerial coil enables better selectivity to be had with a long aerial. The aerial coil has 30 turns tapped every 5 turns. Where it is difficult to separate two stations, the aerial should be connected to one of the lower taps, but for getting in weak stations, it is better to have the aerial connected to one of the higher taps.




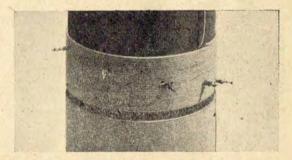

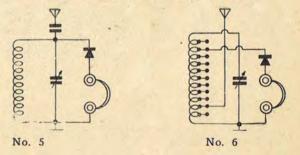This picture shows the tapped aerial coil at the top of the tuning coil. Note how the tappings are spaced round the former so that they do not come too close to each other. This is done simply by allowing about an inch extra after each five turns has been wound on, before the twist is made in the wire.



USING A WAVE-TRAP WITH A CRYSTAL SET

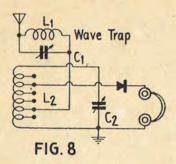

No. 3. This is simply the circuit for No. 2, with the aps left out. It will be quite good for most locations, but where more selectivity is needed, No. 2 should be used.


No. 4. Another way of getting the same results as with No. 3. Here a single tap is put on the tuning coil, and no aerial coil is used.

No. 5. Still another way of getting better selectivity than No. 1 will give. The condenser in series with the aerial should be about 0.0001 or less, and should be smaller the longer the aerial.


No. 6. A very flexible arrangement, which is much more selective than any of the others on this page. No aerial coil is used, but the tuning coil is tapped every 5 turns. The more the crystal and aerial are tapped down towards the earthed end, the more selective the set will be, but the weaker the signal becomes. For best signal strength combined with the best selectivity, this circuit is hard to beat, especially when a long, high aerial is used.

The wave-trap is a device for helping to weaken the signal from a strong station, which is interfering with a weak station. Circuit No. 7 shows a wave-trap, L₁ C₁, connected to the set of Circuit No. 6, but the trap can be placed in the aerial lead of any of the other sets on page 7. C₁ should be identical with the tuning condenser, while L₁ can be a coil exactly similar to the tuning coil. To work the trap, the interfering station is tuned in with the tuning condenser, until it is loudest. Then the wave-trap condenser is tuned until the station is as weak as possible. After this, the trap is left alone, and the set is tuned in the usual way as though the trap were not there at all.

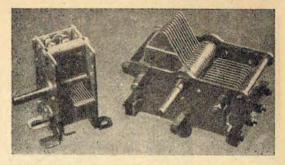No. 8 is another selective circuit. L₁ and L₂ are identical, and so are C₁ and C₂. The same sizes are used as in all the other crystal sets. The unmarked condenser should be very small—no bigger than 50 mmfd. Both condensers are tuned to make the station as loud as possible.



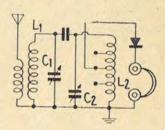Two types of tuning condenser that can be used to build any of these crystal sets.



WORLD RADIO HANDBOOK

No Short-wave Listener or D-Xer can afford to be without it

Contains details of all shortwave broadcast stations in the world, call signs, frequencies, schedules, English language transmissions, station addresses, interval signals, and a host of other interesting information.


ACCLAIMED BY BROADCASTING AUTHORITIES, RADIO CLUBS, and LISTENERS EVERYWHERE AS THE MOST UP-TO-DATE CALL BOOK PUBLISHED

Send 6,6 to-day for this most necessary book to-

"WORLD RADIO HANDBOOK"

10 KORAHA STREET, REMUERA, AUCKLAND, S.E.2

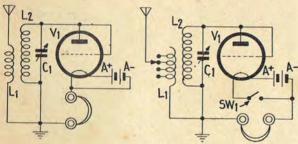Improving 'Crystal' Sets by using a Valve Instead of the Crystal



These two circuits show how a crystal detector can be replaced by a triode valve connected as a diode. All that is needed is a battery to light the filament, and a valve socket. For old-fashioned 2-volt valves a 1½ volt torch cell can be used, and for 4-volt valves a 4½-volt torch battery. The left-hand circuit shows Crystal set No. 3 altered to use the valve, and the right-hand one, crystal set No. 2. In the latter a switch has been added to turn the valve filament on and off.

V₁ can be any of the valves shown in the table 30 etc.



1. Fil 1. N.C. 2. P. 2. Fil 3 6 3. P. 4. N.C. 4. Fil .


5. G. 6. (absent)


7. Fil. 8. N.C.

These diagrams show the pins to which the various elements of the valves given in the table are connected.

.. N.C. stands for No Connection, and is used when the pin is present, but has nothing inside the valve connected to

A SIMPLE I VALVE REGENERATIVE SET

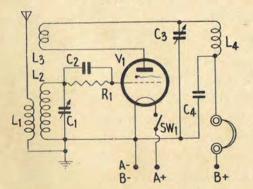

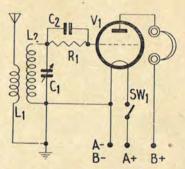

The above circuit shows a more sensitive one-valve arrangement, which uses a B battery as well as the filament or A battery. The former can be a 45-volt B battery, or can be made from a few 4½-volt torch batteries in series. Three of them, giving 13½ volts will give very good results. L₁, L₂, same as aerial and tuning coils in any of the crystal sets. C₂, 0.00025 to 0.0005 mfd. C₂ same as tuning condenses in capstal. 0.0005 mfd. C1, same as tuning condensers in crystal sets. V1, any of the valves shown in the table below.

Tube Type.	Fil. Voltage	Fil. Current.	Type of Base.
1G4-GT	1.4	0.05 amp.	Octal
1H4-G	2.0	0.06 amp.	Octal
30	2.0	0.06 amp.	4-pin
A-415	4.0	0.06 amp.	4-pin
A-409	4.0	0.06 amp.	4-pin
PM2DX	2.0	0.06 amp.	4-pin

NOTE.—The last three types are old Philips or Mullard battery valves, which may sometimes be bought quite cheaply second-hand. Even if very cheap, they should be tested before buying.

 C_1 O.0003 to 0.0005 μ f. variable. C₂ 0.00025 to 0.0005 μf. fixed.

0.00025 µf. Can be air or mica-spaced.

Any of the types in the above table. L₃, Tickler coil. 10 turns of 30 D.C.C., wound over the lower ten turns of L₁.

C. 0.0005 mfd. fixed.

L₁, L₂, same as for aerial and tuning coils or any of the crystal sets. See page 7.


A Battery, to suit valve used. B battery, 13½ to 45 volts. L₄ Broadcast R.F. choke.


SW₁ On/off switch.

Note.—If the three windings are all wound in the same direction, on the former, connecting the bottom of the tickler to the plate will be right. If the set will not oscillate at all, try reversing the tickler connections, because the direction of winding might not be right.

Regenerative Detector Circuits

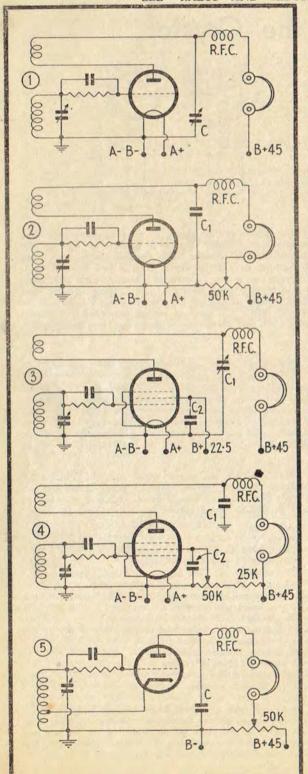SEE "RADIO AND ELECTRONICS," AUGUST, 1946



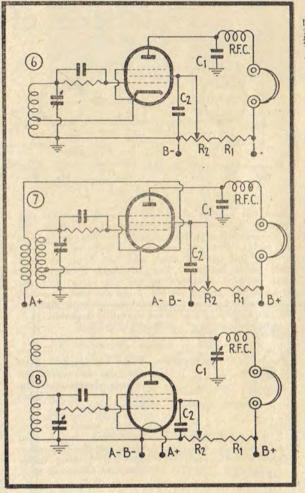

These eight circuits are a representative selection of the many that have been developed over a long period. All will work well if properly built, and they give a choice of valve types, methods of controlling reaction, and of coil winding methods. In the case of pentodes, the B+ can be maximum recommended in the valve books for the valve used, but in all cases, the maximum screen voltage should not be allowed to go higher than 45 volts. For triode circuits, no more than 45 volts is needed, or desirable, for any valve type, if best results are to be had.

In all pentode circuits, R1 can be 50 to 100k., with R2 at 50k.

C1 should be 0.00025 or larger, whether fixed or variable if the set is to work on the broadcast band. For shot-wave a value of 0.0001 is better.

Nos. 6 and 7 are suitable only for heater-cathode


Nos. 6 and 7 are suitable only for heater-cathode type valves, but all the other circuits can also be used for these valves, as well as for filament valves. To use Nos. 1, 2, 3, 4, 7, and 8 for cathode valves, all that has to be done is to earth the cathode pin and one side of the heater.


The Radel One

FULLY DESCRIBED IN "RADIO AND ELECTRONICS," MAY AND JUNE, 1946



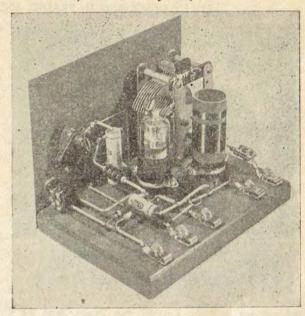Two views of the completed set. The coil-formers are made by glueing 14in. bakelized paper tubing to Amphenol four-pin plugs, with the covers removed. A four-pin valve socket is used to plug the coils into. It does not matter which coil pins are used for which connection, as long as the coil socket is wired accordingly, and all coils are arranged in the same way.



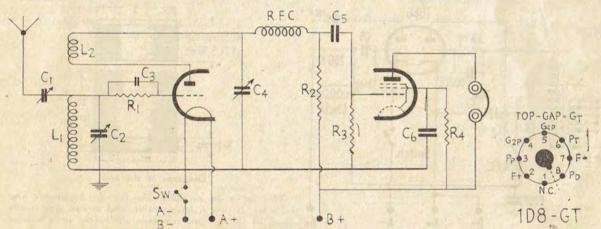

C1, 30uµf. max. trimmer.

C2 0.00035 µf. max. variable.

C3, 0.0001 µf. fixed.

C4, 0.0003 µf. max. variable.

C5, C6, 0.1 \(\mu \)f.
R1, 2 Megs.
R2, 50,000 ohms.
R3, 5 Megs.

R4, 20,000 ohms.

COIL DATA

Broadcast

L1, 105 turns 36 gauge enamelled wire, close wound. L2, 30 turns of same wire, close wound.

Short-Wave A (approx. 30m.-90m.)

L1 16 turns 24 gauge enamelled wire, double spaced. L2 10 turns of same wire close-wound.


Short-Wave B (approx. 19m.-60m.)

L1 6 turns 24 gauge enamelled wire, double spaced. L2 10 turns of same wire close-wound.


Note.-All tickler coils spaced sin. from top of grid


The Rade! Single-twin

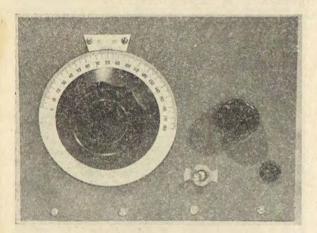FULLY DESCRIBED IN "RADIO AND ELECTRONICS," DECEMBER, 1948



Front panel view of the set.

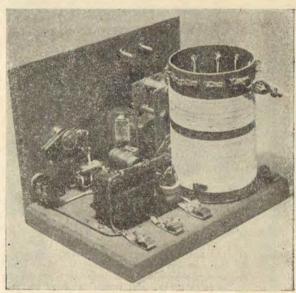

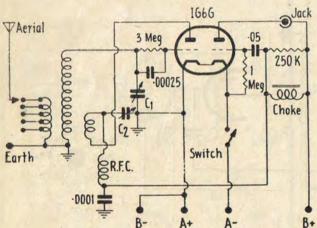



Above: Base connections of the 1G6G when viewed from under the socket "N.C." means "No Connection." Left: Circuit diagram of the set. The choke is the primary winding of an old audio transformer. This can be bought second-hand for only a shilling or two.

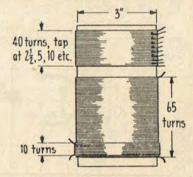


Diagram of the coil.

This set is an excellent one for the beginner's first valve set. It uses a double valve, and so can give results B+ equal to those from two separate valves in a similar 45v circuit.

The audio frequency choke can be the primary of an old audio transformer. These are picked up quite cheaply for only a few shillings, and as long as the primary winding is intact, the secondary's condition does not matter. The jack is where the headphones are connected, and, if desired, terminals can be used instead.

The A battery should be one of 1.5 volts. More than 45 volts for the B battery is not recommended, as a higher voltage battery is more expensive, and will not noticeably improve the results.

If a few more turns are put on the tickler, B battery as low as 12.5 volts will work the set quite well.


Note.—If the set will not oscillate when first turned on, reverse the connections to the tickler (10-turn) winding.

The Radel "Progressive" Battery Three


FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, OCTOBER, NOVEMBER, AND DECEMBER, 1946

This set was designed for those starting off to learn about the practical side of radio sets. The three stages of the construction are complete sets in themselves, each being excellent of its kind. The chassis was

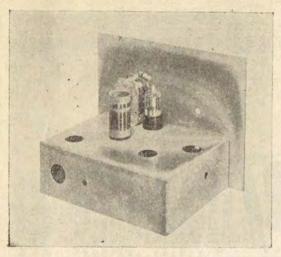designed so that all three stages of the construction could be built on it. Only after the final stage has been reached are all the chassis holes filled up.



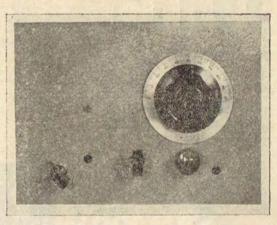Showing the layout of parts for the first stage of the construction.



The front panel, with controls mounted for the first stage of construction.

C1, 30 µµf. max. trimmer.

C2, 0.00035 µf. max. variable.


C3, 0.0001 µf. fixed.


C4, 0.0003 \(\mu f.\) max. variable. C5, C6, 0.1 \(\mu f.\) R1, 2 Megs.


R2, 50,000 ohms.

R3, 5 Megs.

R4, 20,000 ohms.

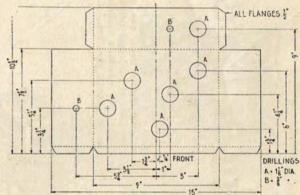

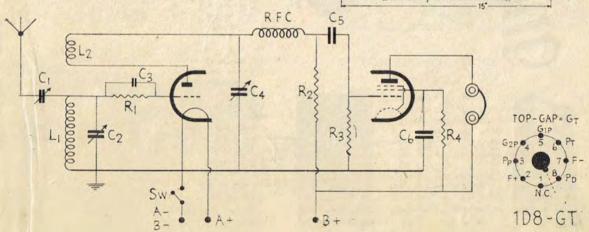


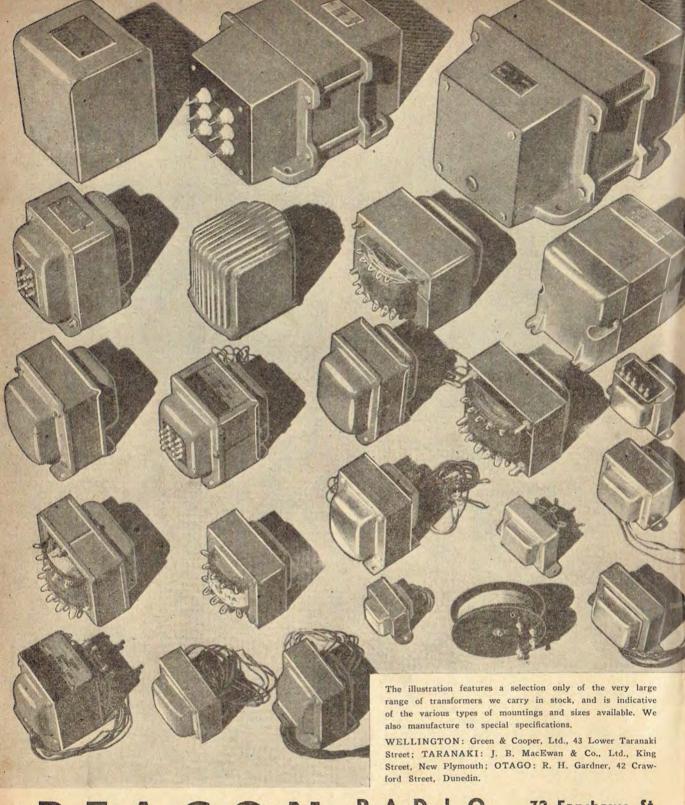

BEACON RADIO

32 Fanshawe St.
AUCKLAND

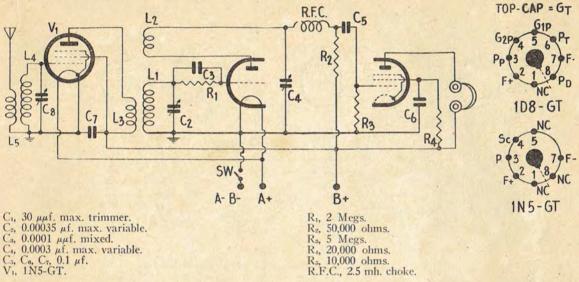THE SECOND STAGE OF THE "PROGRESSIVE" THREE




C₁, 30 μμf. max. trimmer. C₂, 0.00035 μf. max. variable. C3, 0.0001 µµf. mixed.


C₄, 0.0003 μf. max. variable. C₅, C₆, C₇, 0.1 μf. V₁, 1N5-GT.


00

B= 3" "



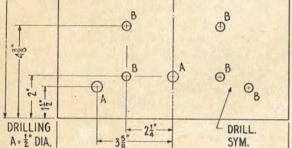

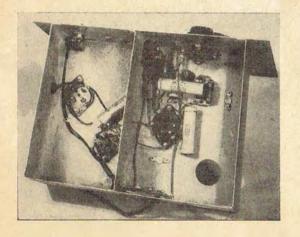

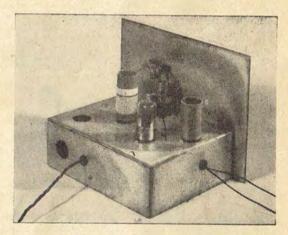

COIL SPECIFICATIONS FOR STAGES 1 AND 2

The coil specifications are as follows. It will be noted that, with the exception of the primaries, numbers of turns are identical with those used previously.

Broadcast

Li, 105 turns 36-gauge en. close-wound.

L₂, 30 turns same wire, close-wound ½ in. from top of Li.


L₃, 40 turns same wire, wound over bottom end of L₁. Short-Wave A (approx. 30–90m.)

L₁, 16 turns 24-gauge en. or D.C.C. double-spaced. L₂, 10 turns same wire, close-wound ½ in. from top

of L1. La, 6 turns 36-gauge en. inter-wound at bottom of L1.

(Continued on next page.)

FINAL STAGE OF THE "PROGRESSIVE THREE"

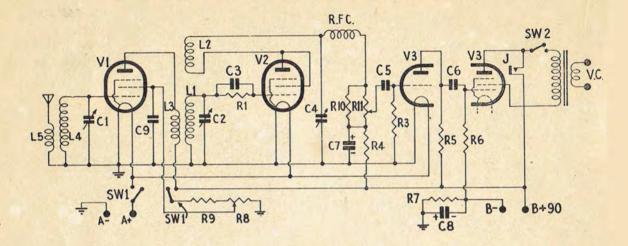

R₁, 2 Meg.

Ra, 10 Meg.

R4, 25k.

Rs, 100k.

R., 0.5 Meg.

Rr. 1.5k.

Rs, 50k. pot.

R, 10k.

R10, 50k.

R11, 100k. pot.

C₁, C₂, 0.00035 μf. max. variable.

Ca, 0.0001 µf.

C₄, 0.0003 µf. max. variable.

Cs. 0.01 uf.

Co, Co, 0.1 µf.

C7, 8 µf. electro.

C₈, 25 µf. 25v. electro.

SW₁, Double-pole on/off.

SW₂, Single-pole on/off.


R.F.C., 2.5 mh. choke.

J, open cct. phone jack.

V₁, V₂, IN5-GT or 1P5-GT.

Va, 1D8-GT.

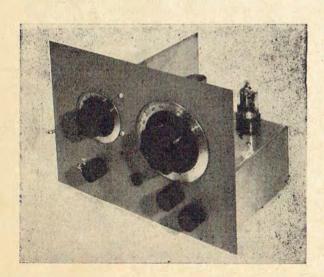Output Transformer, 12,000 ohms-voice coil.



COIL SPECIFICATIONS—Continued

Short-Wave B (approx. 19-60m.)

L₁, 6 turns 24-gauge en, or D.C.C. double-spaced. L₂, 10 turns same wire, close-wound \(\frac{1}{2} \) in, from to

of L₁.

L₃, 4 turns 36-gauge en- inter-wound at bottom c

L₁.

Note.—All coils wound on 1½ in, diam, tubing.

The completed "Progressive Three." The dial on the right is the detector tuning, while the smaller one on the left is the R.F. tuning control. The knobs from left to right are: R.F. gain, regenerator control, and audio gain. In the centre is the phone jack, and on the extreme left is the on/off switch.

SPECIFICATION OF AERIAL COILS FOR STAGE THREE

The output from the 1D8 is ample on strong stations, both broadcast and shortwave, to drive a small loudspeaker. The phone jack and switch are included so that the phones can be used instead of the speaker for DX listening.

Broadcast:

Li, 105 turns 36-gauge en. close-wound.

L₅, 20 turns same wire, wound over bottom end of L₄.

Short-Wave A (approx. 30-90m.)

L₁ 16 turns 24-gauge en. or D.C.C. doubled spaced.
 L₅ 5 turns 36-gauge en, inter-wound at bottom of L₁.


Short-Wave A (approx. 19-60m.)

L₄ 6 turns 24-gauge en. or D.C.C. double spaced.

3 turns 36-gauge en. inter-wound at bottom of

L₄.

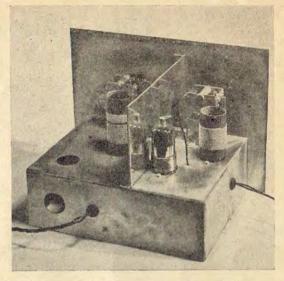
The winding should be terminated on the pins of the plug as follows: Pin No. 1, top of L₁; pin No. 2, bottom of L₅; pin No. 3, top of L₅; pin No. 4, bottom of L₄.



This photograph shows the position of the aluminium shield that must be added on top of the chassis when the tuned R.F. stage is added, When the R.F. stage is untuned, this shielding is not needed.

Straight Line Frequency Variable Condensers


THIS range of low loss condensers is fitted with a special type of bearing which prevents side play and noise on rotation at high frequencies. Losses are kept to an absolute minimum by the use of a polystyrene end plate. The vanes are shaped to give approximately straight-line-frequency tuning and minimum capacities have been kept as low as possible consistent with sound mechanical construction. Although designed primarily for receiving work these condensers are suitable for use in the early stages of transmitters. Under normal conditions, the spacing of the vanes is adequate for 500 volts D.C.

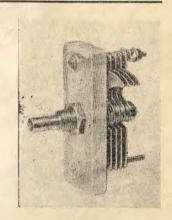

Type No.	Capacity PF		New
Type No.	Max.	Min.	Price
VCR 15	15	2.9	11/-
VCR 25	25	3.2	11/8
VCR 50	50	3.5	12/6
VCR 100	100	5.5	13/6

TYPE 1—COILS AND FORMERS

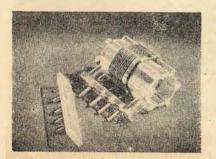A RANGE of 4 or 6 pin plug-in coils in which losses are reduced to a minimum by the use of polystyrene ribbed formers and bases. The horizontal mounting ensures leads of minimum lengths.



DIMENSIONS:


Bases 4-pin width 0.375" (95 mm.) Coil height includ-2.0 " (51 mm.) Bases 6-pin width 0.875" (22.5 mm.) ing pins Former length 2.0 " (51 mm.) Former average 2.0 " (51 1.125" (28.5 mm.) Bases length diameter Ranges 7 and 8 are on 3" diameter formers fitted to the normal 4-pin base Former fitted to sub-base 4 pin Ref. IF/1004 4/6 Former fitted to sub-base 6 pin Ref. IF/1005 5/-Socket base 4 pin Ref. 5S/1000 2/2 Ref. 5S/1001 1/10 Socket base 6 pin


RADIO REPAIRS LTD.

7A GREAT NORTH ROAD, AUCKLAND

The Radel "Rimlock" T.R.F. Four

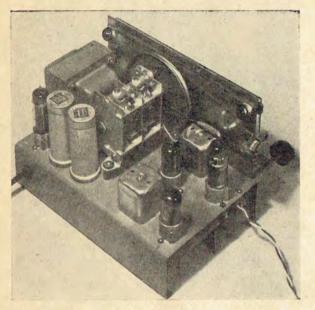FULLY DESCRIBED IN "RADIO AND ELECTRONICS," AUGUST, 1948




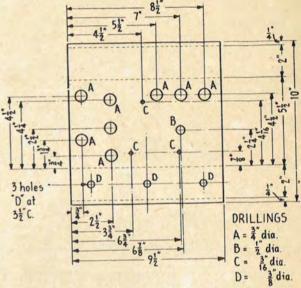


Chassis diagram of the T.R.F. receiver.

This set is a modern version of the A.C. operated three-valve T.R.F. The fourth valve is, of course, the rectifier. Note carefully the position of the underneath shield, which is taken across the socket of V1, the R.F. amplifier, so as to isolate the grid pin from

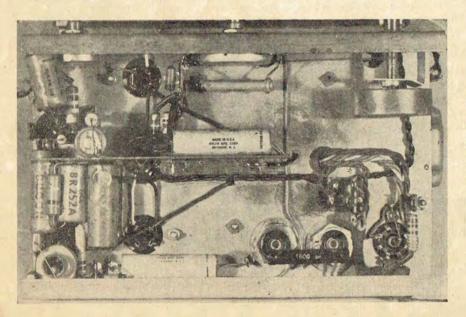the plate pin. These pins are on opposite sides of the shield, the grid circuit on the front side of it. The valve between the coil cans is the R.F. amplifier, and the detector is at the back left-hand corner of the chassis.



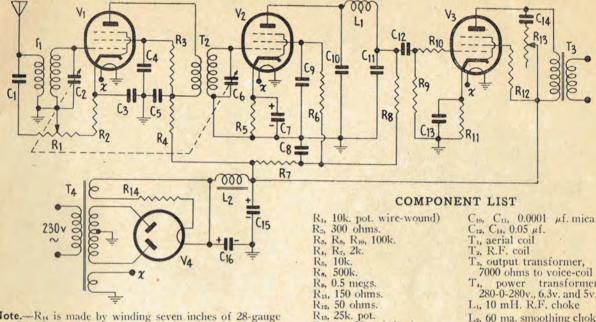Under-chassis view of the receiver. The back edge is at the top of the picture. The baffleshield crosses the valve socket, while the detector valve is at the extreme top right-hand corner, under the R.F. choke. The rectifier is at the top left-hand corner.



Note.—R₁₁ is made by winding seven inches of 28-gauge S.W.G. nichrome wire on to a 3-watt carbon resistor, used as a former. The required resistance is 1.6 ohms.

R11 (see Note below). C1, 0.0005 µf.

C₂, C₆, gang condenser. C₃, C₄, C₅, C₈, 0.05 µf. paper C₇, C₁₃, 50µf. 25v. electro. Co. 0.1 µf.

T₄, power transformer, 280-0-280v., 6.3v. and 5v.

L₂, 60 ma. smoothing choke or preferably 1500-ohm 5w. resistor V1, V2, EF41

Va, EL41 V., AZ41.

Market Committee Committee

Y High-fidelity Loudspe



This is a twin loudspeaker system consisting of a direct radiator low-frequency unit and a hornloaded high-frequency unit fed from a carefully designed cross-over network. The response of both units is intrinsically level and the wide-frequency range is not obtained by "trick" effects, such as cone break-up or diaphragm resonance. The design of the low-frequency cone which forms the final section of the high-frequency horn is such that an even distribution of the high frequencies is obtained over a wide angle. In order that the low-frequency diaphragm shall move more nearly as a piston, the body thickness has been increased and the surround is treated to prevent the setting-up of subsidiary resonances. In the design of this loudspeaker, great care has been taken to ensure that the entire system is aperiodic, which, together with the wide frequency range, results in good transient response and faithful reproduction.

Voice Coil Dia. LF, 2 in.
Voice Coil Dia. HF, 2 in.
Voice Coil Impedance LF D.C. 9 ohms, 12 ohms at 400 cps.
Voice Coil Impedance HF D.C. 8 ohms, 12 ohms at 2000 cps.
Power handling capacity (peak), 20 watts.
Impedance via Cross-over Network, 15 ohms.
Frequency response, 25-20,000 cps. plus minus 3 db. 40-12,000 cps.
Intermodulation products less than 2 per cent.

Bass response will depend on baffle size or volume of enclosure if infinite baffle is used, details for which can be supplied.

DIMENSIONS

PRICE £39/5/-

Overall diameter, 15.25 in. Depth, 11 in. Fixing holes P.C.D., 15.5 in. Weight, including matching transformer and cross-over network, 30 lb.

Sole New Zealand Agents for Tannoy Twin Concentric High-Fidelity Speakers:



Phone 54-418 ::


43 Lower Taranaki Street, Wellington, C.3


?????


:: Telegrams "Fidelatone"

The Radel A.C. Broadcast Five

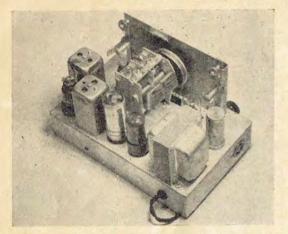FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JULY, 1946



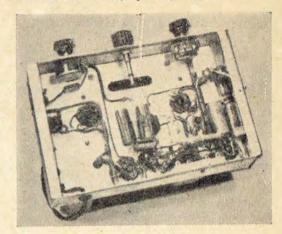

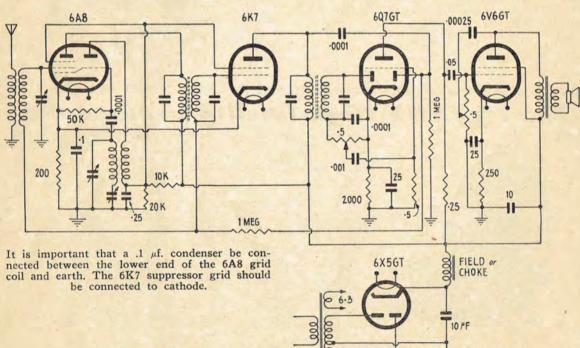


This is a very suitable set for one's first A.C. superhet. It has a minimum of parts and so is inexpensive as well as being a good performer. The photograph shows how the set is laid out. In the right-hand back corner (looking at the chassis from the front) is the 6K7, with the I.F. transformers on either side of it, Then, along the back of the chassis are the 6Q7GT, with its shield-can, and the 6V6 output tube. The 6K8 can just be glimpsed behind the gang condenser in the photograph. The coils can

be seen in the under-chassis view. The oscillator coil can be seen mounted on the side, at the right, while the aerial coil is on the chassis itself, just in front of the 6K8 socket. For a suitable chassis drawing, see page 23. Here, all that would have to be changed is the positions of the control holes in the chassis front. There are only three in the broadcast set, and their positions can be seen in the photograph on this page.

The Radel Vibrator Four

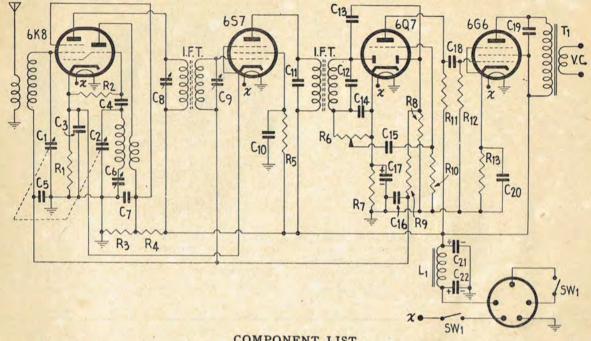FULLY DESCRIBED IN "RADIO AND ELECTRONICS," MARCH, 1947



R₁, 166 ohms (1000 and 200 in parl.)

R₂, 50k, ½w. R₃, 20k, 1w. R₄, 2.5k, 1w. R₅, 70k. (100k, and 250k, in parl.).


Re, 0.5 meg. pot.

R7, 5k. 1w.

 R_8 , R_9 , 1 meg. $\frac{1}{2}$ w. R_{10} , 0.5 meg. $\frac{1}{2}$ w.

R11, 250k. 2w.

R₁₂, 0.5 meg. ½w. R₁₃, 500 ohms 1w.

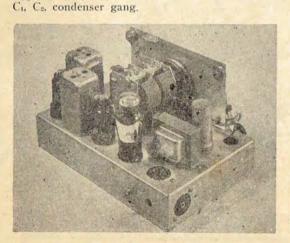

View of the completed receiver. Note the sockets for connection of the speaker and power cable. The latter is plugged into the five-pin socket on side of the chassis.

COMPONENT LIST

C₃, C₇, 0.25 μf. paper. C₄, C₁₃, C₁₄, 0.0001 μf. mica. C₅, C₁₀, C₁₅, C₁₈, 0.1 μf. paper. C₆, 600 μμf. padder.

Cs, Co, C11, C12, I.F. trimmers.

C₁₆, 0.01 µf. paper. C₁₇, C₂₀, 25 µf. 25v. electro.


C10, 0.002 µf. paper.

C21, C22, dual 10 µf. 450v. electro.

L₁, 40 ma. vibrator choke.

SW1, double pole on/off.

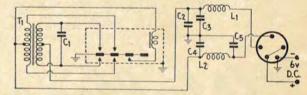T₁, output transformer, 10,000 ohms to V.C.



Circuit and Component Valves for the Vibrator power supply unit


T1, 6v. vibrator transformer, centre-tapped primary, output 135v. D.C. C₁, 0.05 μf. 500v. mica. C₂, C₄, C₅, 0.1 μf. C₃, 0.001 μf. mica.

L₁, 10 \(\mu\)f. R.F. choke. L₂, R.F. choke (see text).

This is really a vibrator version of the A.C. Broadcast Five. The chassis can be the same as that for the Dual-wave Five, and a scale drawing is given on page 23. In this set the smoothing choke is mounted where the power transformer can be seen on the Broadcast Five, and there is also room for the speaker socket, which can be seen behind the choke in the photograph on this page.


The Radel A.C. Dual Wave Five

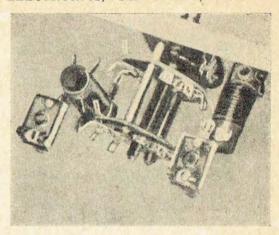
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, 1946



This set is the dual-wave version of the "A.C. Broadcast Five." The mounting of the shortwave coils and wave-change switch is illustrated in the photograph above. The broadcast coils are mounted in the same positions that they occupy in the "Broadcast Five." (Please see note on page 20.)

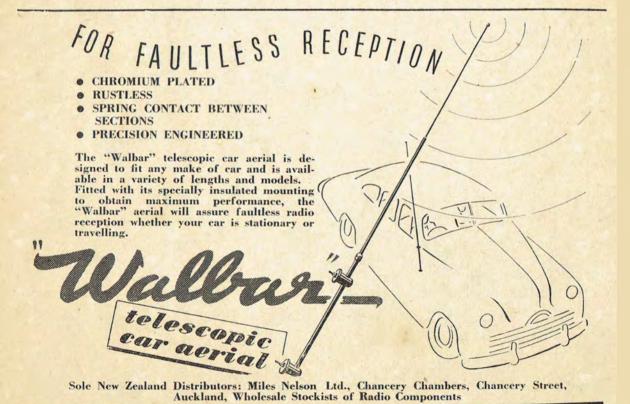
Showing how the shortwave coils and wavechange switch are mounted before wiring them up.



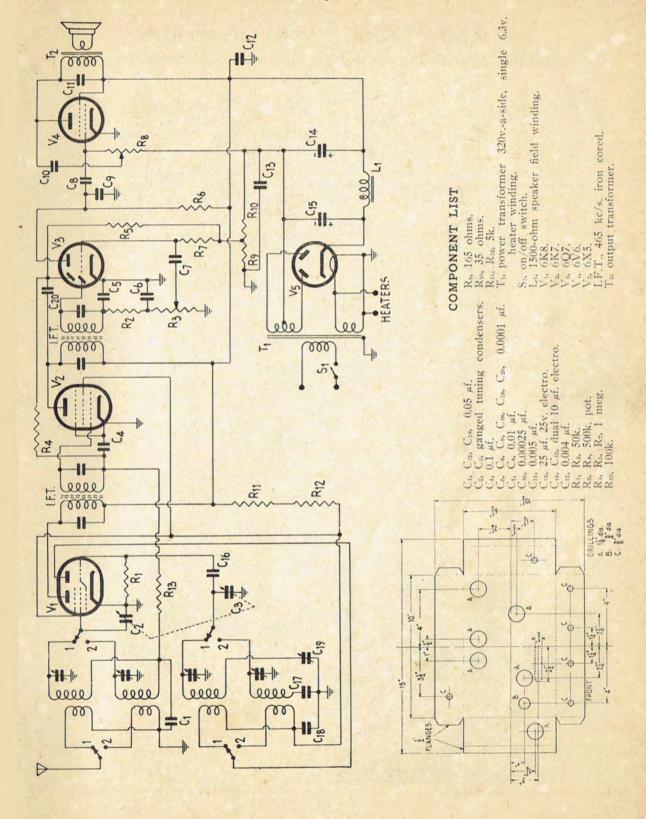

The Radel Portable Four

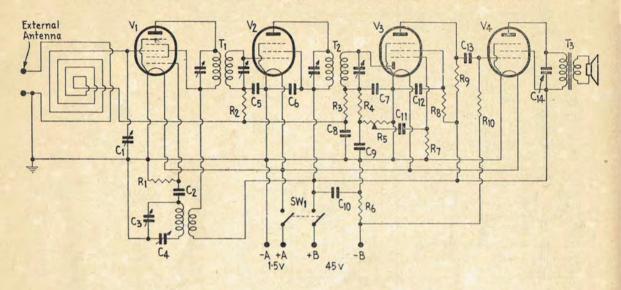FULLY DESCRIBED IN "RADIO AND ELECTRONICS," DECEMBER, 1947



COMPONENT LIST

R₅, 1 meg. pot. R₆, 500 ohms. R₇, 10 megs.


Rs, 3 megs.
Re, 1 meg.
T1, T2, 465 kc/sec. I.F. transformers.
T3, output transformer 8000 ohms to V.C.
SW1, D.P.S.T. on/off.
V1, 1R5.


V₂, 1T4. V₃, 1S5. V₄, 1S4.


C₁, C₂, 2-gang condenser. C₂, 50 μμf.

C₄, 600 μμf. padder. C₅, C₈, 0.05 μf.

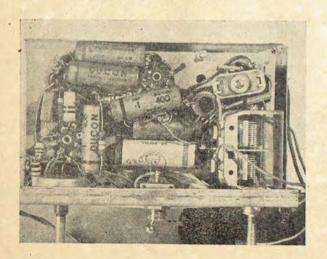C₅, C₅, 0.05 μt. C₆, C₁₂, 0.1 μf. C₇, C₉, 100 μμf. C₁₀, 8 μf. 50v. electro. C₁₁, C₁₄, 0.002 μf. C₁₃, 0.0005 μf. R₁, R₂, 100k. R₃, R₁₀, 2 megs. R₄, 50k.



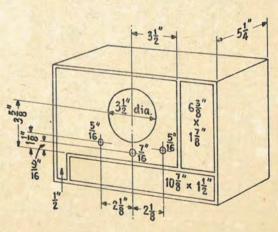

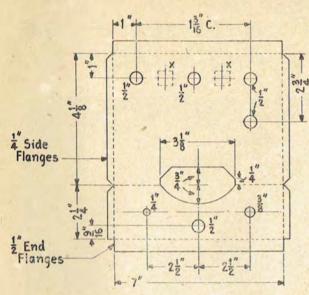

Above is a working drawing for the chassis of the Portable Four.

This four-valve portable was designed for ease of building rather than extreme compactness. The large A battery that can be used is a great advantage.

The speaker is mounted on the chassis with two small angle-brackets, so that the speaker screws hold the whole chassis to the cabinet. The front edge of the chassis rests on the shelf above the A battery. Along the back of the chassis, looking at the chassis diagram, are, from left to right, the 1R5, V1, the 1T4, V2, and the 1S5, V3. The output tube, V4, is in front of the row.

Performance is improved in this set by the use of full-sized I.F. transformers. Note how the loop is well away from the metal parts of the set, increasing its sensitivity on that account.

Back and current numbers of "Radio and Electronics" may be obtained from—

Te Aro Book Depot, Courtenay Place, Wellington. S.O.S. Radio Service Ltd., Queen St., Auckland. Tricity House, 209 Manchester St., Christchurch. Ken's Newsagency, 133–135 Stuart St., Dunedin. S.O.S. Radio, Ltd., Hamilton.

3 Lines of interest to Amateurs . . .

S.G.Brown Headphones

Test Equipment COLLARO Radiogram Units

Inquire at your Local Dealer or write for Leaflet to:

N.Z. Distributors:

Russell Import Co. Ltd.

55-57 Dixon St., Wellington


G.P.O. Box 102, Wellington

Telegrams: RIMCO

Denco leads the way with the FAMOUS CT4 TURRET

A TECHNICAL DESCRIPTION

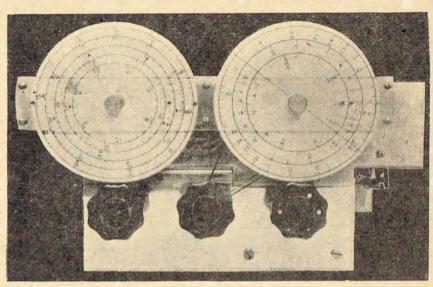The C.T.4 is a complete allwave tuning unit, mainly for use in communication receivers, having one highgain R.F. stage, mixer and separate oscillator, and covering, in six ranges, 175 kc/s. to 36 me/s. with an I.F. of 1.6 mc/s. The wellknown Denco turret assembly arrangement is used.



IMPORTANT FEATURES

(1) Constant gain characteristic from 1.65 to 36 mc/s., made possible by the use of a special circuit arrangement for coupling between R.F. and mixer stages. When the recommended input circuit is used, the gain variation is not more than 6 db. over this range, thus going a long way to overcome the familiar discrepancies in "S" meter readings.

(2) Calibrated bandspread of all amateur bands by means of mechanical partial rotation of the stator vanes of the threegang tuning condenser. Bandspread on intermediate frequencies is also possible on

logging scale.

(3) Coils wound on low-loss Polystyrene,

with adjustable iron-dust cores. (4) Polystyrene insulation used throughout

(5) Accurate tracking of signal and oscillator circuits, all condensers, etc., being provided.

(6) Concentric air-spaced trimmers for each coil in the unit.(7) Provision for matching a number of varying aerial impedances over the three highest frequency bands.

(8) Six bands covered by the turret are as follows:-

175- 525 Kc/s. 1650.0-5.0 Mc/s. 515-1545 Kc/s. 4.8-9.6 Mc/s.

9.4-18.8 Mc/s. 18.0-36.0 Mc/s.

(9) Designed for high-slope tubes from 4 to 9 ma/v. THE NEXT SHIPMENT IS ON THE WAY

Write for details to-


Also from-

RADIO REPAIRS LTD.

7A GREAT NORTH RD., AUCKLAND 209 MANCHESTER ST., CHRISTCHURCH

The Radel Portable Five

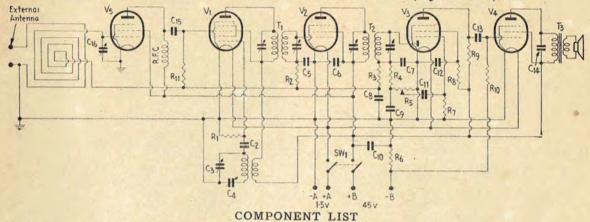FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JANUARY, 1948



C3, C16, midget two-gang condenser.

C2, 50 μμf. mica.

C4, 600 µµf. padder.

C₅, C₆, C₈, C₁₂, 0.02 μf. paper. C₇, C₉, C₁₅, μμf. 100 μμf. mica. C₁₀, 8 μf. 50v. electro. C₁₁, C₁₄, 0.002 μf. paper.

C13, 0.005 µf. R1, R2, 100k.


Rs, R10, 2 megs.

R4, 50k.

R₅, 1 meg. pot. R₆, 500 ohms.

R₇, 10 megs.

Rs, 3 megs.

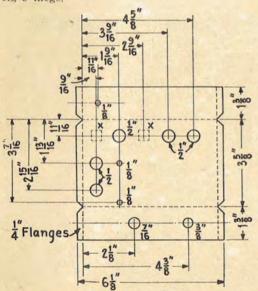

R₉, R₁₁, 1 meg.


T1, T2, midget 465 kc/ses. I.F. transformers.

T₈, output transformer, 8000 ohms to V.C. SW₁, D.P.S.T. on/off. V₁, 1R5.

V₂, V₅, 1T4. V₃, 1S5.

V₄, 1S5.
V₄, 1S4.
"A" battery, type No. 742.
"B" battery, type No. 482.
Note.—If desired, a 67.5v. battery type may be used instead of type 482 for the "B," and will give higher output power. The only change necessary would be to increase the rating of C₁₀ to a value higher than 67.5 volts.

higher than 67.5 volts.

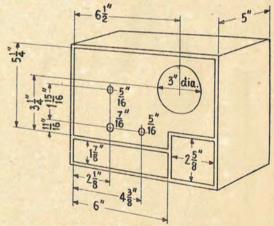

At left: Working drawing of chassis.

Above: Skeleton drawing showing layout of partitions in the cabinet, and the placement of the necessary holes in the front. All measurements are INSIDE dimensions.

This is a compact five-valve portable which is none the less easy to construct. Photographs of the completed set appear on the next page.

Note the untuned coupling between the R.F. amplifier and the mixer. Looking at the chassis diagram, the set starts at the bottom left-hand

corner with the R.F. stage, with the 1R5 behind it. In the left-hand back corner is the first I.F. transformer (midget), after which the set progresses along the back of the chassis, exactly following the circuit. The 1 in. holes on the chassis are the mounting holes for the midget gang condenser,



Back view of the receiver, showing the physical layout of the chassis, speaker, and batteries. Although the set is quite small, there is plenty of space available.



Front view of the receiver, showing the location of the controls,

I-QUALITY-LO-COST"

WHAT'S YOUR INTEREST? RECEIVERS OR TRANSMITTERS—AMPLIFIERS OR ELECTRONIC DEVICES?

Well, we can supply or buy your needs at the lowest ruling prices. Don't go to town, "Let our speedy mail order service" bring it to your door. Below are a few lines we have available at very attractive prices.

CONDENSERS: 8 mfd. 450v. wk. English Pigtail (made 1949), 2/6; 16 mfd., 3/6; .25 600v. Sprague, 9d.; Solar Mica .01, 1/3; .002, 6d.; Aerovox Mica, .02, 1/3; .001, 5d.; Philips Air Trimmers, 1/3; Trimmers, ceramic, 0-30 p.f., 1/-; 385 p.f. 3-gang, \(\frac{1}{2}\) in. shaft American, 9/6.

METERS, Great Value: 0-500 uA (0-1 ma.), Ferranti, 21 in. round. The real foundation for a 2000-ohm per volt test meter, 12/6. Copper Oxide 0-5 ma. Rectifier, 7/11.

TUBES: 6X5GT, 2/11; 6U7G, 2/6; 2X2/879, 4/3; EBL31, EL3NG (Good 6V6 sub.), 4/9 each; 954, 956, 959, 3/6; 955, 3/-; 6J5, 8/6.

TRANSMITTING TUBES: 807 Radiotron, 6/6; 834 RCA, 10/-; 808 GE 39/6; 866A, 22/6.

VALVE SOCKETS: S8 Amphenol Octal, 3/11 doz.; 4, 5, 6 pin, 6d. each; 7 wafer, 3d.; Johnson Acorn

plated contacts, 7/-; ICA Acorn, 3/6.

ZCI SPARES: Dynamic Phones, 75 ohm, flex and plug, 6/6; Stromberg Carlson 100 ohm, 6/6; 2000 ohm ditto, 15/6; Filter Chokes, 100 ma., 7/11; I.F. Transformers, 465 kc. Iron Core, 7/6; Knobs, 4d.; Heavy-duty Vibrator Packs, 12v.-300v., 57/6; Remote Control Units (Buzzer, Key, Switches, Condensers, Cast Aluminium Case), 7/11 each; Carbon Mics., flex and plug, 6/6; Dynamic Type, 3/6 each; BFO Coil Units, 2/11; Phone Plug, Dynamic 1/6, Standard 2/6; Morse Keys, 2/6; Calibrated Dial and Knob, 1/-; Single Relays, 4/-; plus many others.

WHIP AERIAL: Copper plated, 16 ft., in 4 sections, 12/6 (first quality fishing rod); rubber base, 5/6.

ZC1 TRANSCEIVERS: New MKI Models, complete with 13 tubes, only £10. WE INVITE ALL INQUIRIES AND ORDERS. We cannot print a full catalogue here. MONEY BACK if not satisfied, 10-day period from dispatch.

P.O. BOX 53, name



We are busy collecting names for the latest Companion Price List . . . and quite frankly we'd like to have YOURS too. Simply let us have your name and address right away . . . we will add it to our regular Mailing List and post your Free Price List direct to you.

In case you forget—Companion Products are available from all leading radio dealers.

JOHNS LTD

Radio and Sound Engineers, Johns Bldgs., Chancery St., Auckland, Box 471. Also at Pukekohe.

SPECIAL **TRANSFORMERS?**

Yes-

Consult

RADIART Co.


22 BRANDON STREET. WELLINGTON

Specialists in the odd varieties including Audio Transformers and Smoothing Chokes.

"Radiart" for prompt attention.



THE RADEL RIMLOCK DUAL-WAVE FIVE

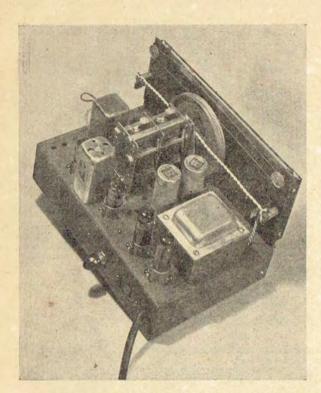

A general view of the receiver. The tone control can be seen at the back of the chassis next the speaker socket.

This set is a compact one for a dual-wave five-valve, but is not cramped. It is an excellent performer in all respects, and the use of the new single-ended Rimlock valves does not introduce any difficulties for the

The AZ41 rectifier has been used in order to keep the Rimlock types throughout. Unfortunately, this valve has a 4v. filament, so that, if a transformer with a 4v. filament winding is not available, it will be necessary to use a home-made dropping resistor, as described under the "Radel T.R.F. Four," which also uses an AZ41 rectifier. If it is desired to avoid this trouble, one can use any ordinary small rectifier which has a 5v. filament.

COMPONENT LIST

R1, R1, R11, R18, 50k.

R2, 200 ohms.

Rs, Rs, 30k.

R₆, 300 ohms.

R₇, R₈, R₁₄, 1 meg. R₉, R₁₅, R₁₆, R₂₁, 100k.

R10, 2k.

R12, R17, 500k. pot.

R₁₃, 1200 ohms.

R10, 150 ohms.

R20, 1200 ohms, 5w.

C₁, C₂₁, two-gang condenser, 420 μμf. max. C₂, C₃, C₄, C₆ C₇, C₉, C₁₀, C₁₁, C₁₁, C₁₀, 0.05 μf.

Cs, padder in coil unit.

C₅, padder in coil unit. C₈, C₂₂, 50 $\mu\mu$ f, mica. C₁₂, C₁₃, 100 $\mu\mu$ f, mica. C₁₅, 25 μ f. 25v. electro. C₁₇, 500 $\mu\mu$ f, mica. C₁₈, 50 μ f. 25v. electro. C₁₉, C₂₉, 32 μ f. 250v. electro. T₁, T₂, aerial and oscillator coils, in coil unit. T₃, T₄, I.F. transformers, 465 kc/sec.

Ts, output transformer, 7000 ohms to voice-coil.


T₆, power transformer, 280-0-280v., 60 ma., 6.3v. 2 amp., 5v. 1 amp. (See text.)


DRILLING

V1, ECH41.


V₂, V₃, EAF41. V₄, EL41.

V5. AZ41. (See text.)

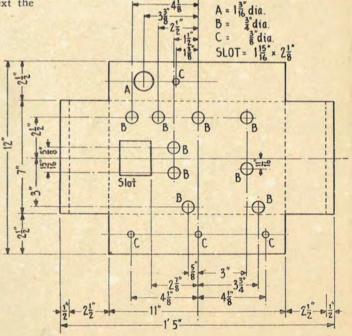

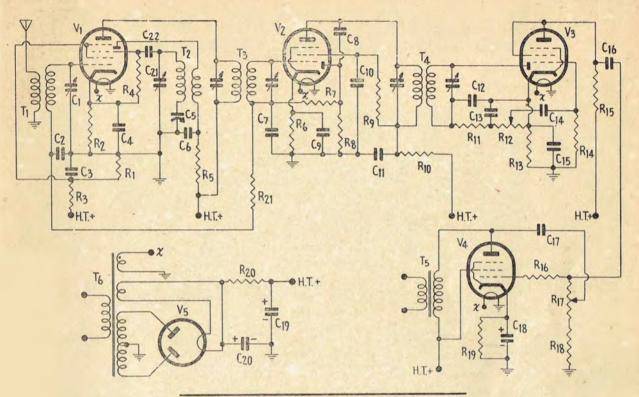

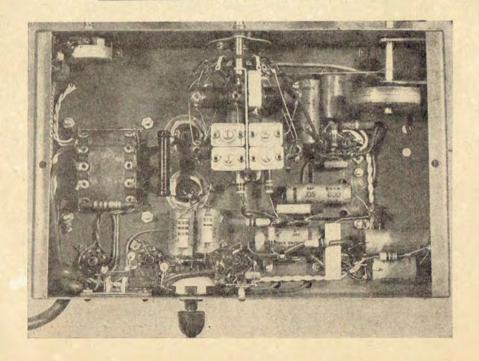Note.—For the AZ41 rectifier, a dropping resistor not shown on the diagram, of 1.6 ohms must be used in series with the filament if a 5v. winding is used for the rectifier.



Memo for— DESIGNER • ENGINEER • RUYER •

DAWE INSTRUMENTS

MEASURING INSTRUMENTS of precision for research, development, design, industrial measurements, and maintenance.

COLLINS RADIO CO.

World famous makers of COMMUNICATION and BROADCAST equipment, from well-known V.F.O. 70E–8 to a complete 50kW FM Broadcast station.

MACKIE

A British firm specialising in MOTORS, GENERATORS, ROTARY TRANSFORMERS, etc., for the most exacting service.

BROOKES CRYSTALS

Manufacturers of QUARTZ CRYSTALS for filter or reference. Control crystals from 50 kc/s to 15 mc/s.

BRITISH COMMUNICATIONS CORP.

Manufacturers in Britain of the only officially approved V.H.F. WALKIE-TALKIE and HANDIE-TALKIE SETS, etc.

WIMBLEDON ENGIN-EERING Makers of high serviceability VIBRATORS. Tested for noise level. REVERSIBLE VIBRATORS eliminating input polarity problems.

ELECTRO METHODS

Specialists in ELECTRONIC DEVICES and SWITCHING SYSTEMS, including RELAYS, THERMOSTATS, HUMIDISTATS, MINIATURE RELAYS, TIMERS, EARTH PROTECTION SYSTEMS. Developers of the HIGH LINEARITY MAGNETIC AMPLIFIER.

CLIFFORD & SNELL

MARINE "LOUDHAILERS," POWER STATION INTERCOM. SYSTEMS. Sound equipment for heavy duty purposes.

ALDER HARDWARE


A company concentrating on small hardware particularly for the RADIO and ELECTRICAL industries. B.A., B.S.F., and Whitworth threads.

INDUSTRIAL ELECTRONICS LTD. COMMUNICATIONS & ELECTRONIC ENGINEERS


Specialists in V.H.F. Mobile Radio P.O. Box 1W., AUCKLAND, N.Z.

A High-Quality Six-Valve Dual-Wave Receiver

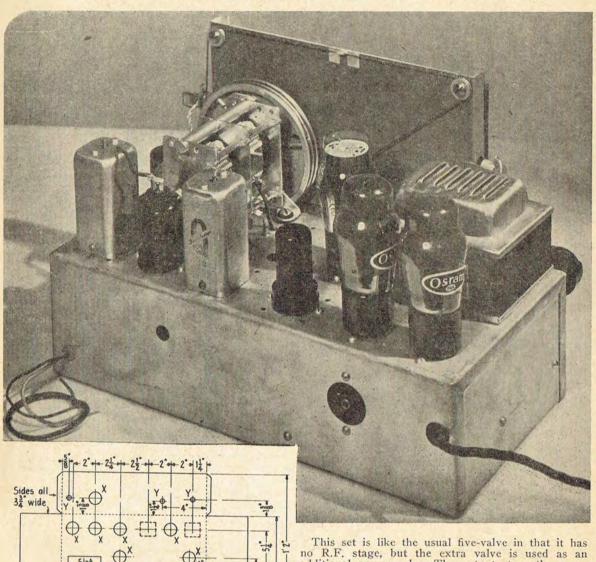FULLY DESCRIBED IN "RADIO AND ELECTRONICS," MARCH, 1948




This set is like the usual five-valve in that it has no R.F. stage, but the extra valve is used as an additional power valve. The output stage thus consists of two Osram KT61's in parallel, giving an undistorted output of 8 watts, with good fidelity. This is excellent where more than the usual power output is wanted, without the additional expense usually incurred by using a push-pull output stage. Tone control by means of adjustable negative feedback is incorporated. The layout is straightforward, and follows the circuit along the back of the chassis, with the exception that the 6SA7 oscillator-mixer is in front of the first I.F. transformer, at the left-hand end in the photograph.

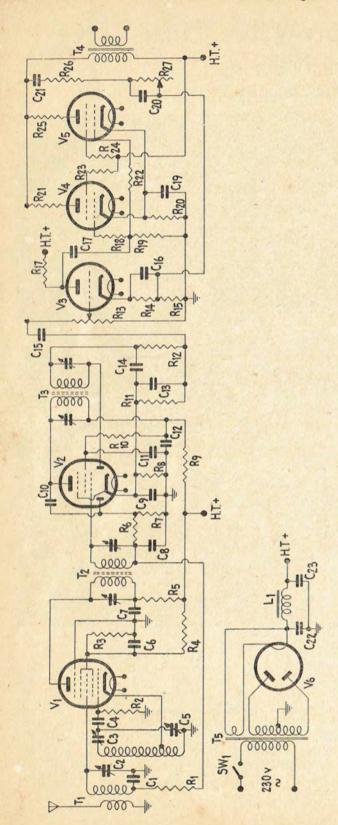

COMPONENT LIST


R₁₀, 50k. 20k. R₁₂, R₁₇, R₁₈, R₂₉, 100k. meg. pot. (volume). R23, R24, R25, 25 ohms. 2 meg. pot. (tone). 15k. Rs, 2k. Rr, Ru, 1 meg. 250 ohms. V5, KT61. 0 ohms. R26, 200k. Ren, 2 SW1, Rai, J 5v. L3, I.F. transformers, 465 kc/sec., iron-cored. 100 ma., T4, output transformer, 3000 ohms to voice-coil. T5, power transformer, 330-0-330v., 100 ma., C, C1, C12, C13, 0.05 µf. paper. amp., 6.3v. 2 amp. ma., 20 H. smoothing choke. 1 μf. paper. 19, 50 μf. 25v. electro. 16 µf. 450v. electro. 0.0001 µf. mica. 6.3v. 2 amp. V₂, 6B8-G or 6B8 metal. V₃, 6J5 metal or 6J5-G. padder, in coil unit. μf. paper. mica. paper.

aeria (8)

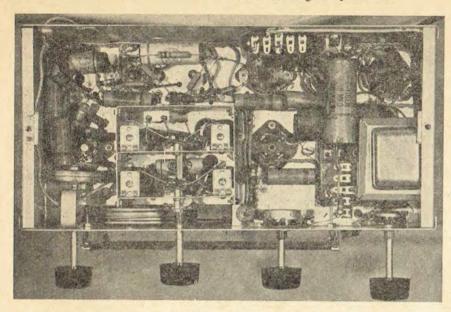

Under-chassis view of the set. The smoothing choke can be seen in the right-hand corner of the photograph. The right-hand knob is the tone control, and the next one is the volume control.

it's here! the new WESTON 779

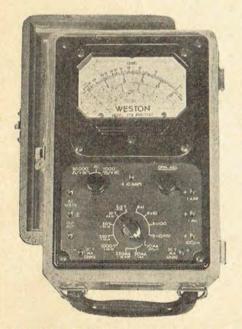

MAXIMUM RANGES MINIMUM SIZE

Weston Instruments are renowned throughout the world.

SUPER-SENSITIVE ANALYSER

1000 or 20,000 ohms per volt

Small . . . Light . . . Compact . . . Heavy moulded bakelite panel . . . Rugged solid oak case . . . Removable cover . . . 26 Ranges . . . 5 D.C. Voltage Ranges at a sensitivity of either 1,000 or 20,000 ohms per volt . . . A.C. temperature compensated . . . Precision resistors throughout . . . A.C. accuracy within 3 per cent. . . . D.C. accuracy within 2 per cent. up to 1,000 volts; 3 per cent. on 1,000 volt range.

RANGES

Volts		Current	Decibels	Ohms
D.C.	A.C.	D.C. Only	-14 to + 2	0.3000
2.5	2.5	.1 Ma.	-2 to + 14	0.30,000
10	10	1 Ma.	+12 to +28	0.300,000
50	50	10 Ma.	+26 to +42	0.30 Meg.
250	250	50 Ma.	+38 to +54	
1000	1000	250 Ma.		
	1	& 10.1 Amp.		

Size: 63 in x 47 in. Approx. Weight: 6 lb.


For full details about all Weston Instruments, write now to:

Standard Telephones & Cables Pty. Ltd.

Box 638, Wellington Box 91w, Auckland Box 293, Wanganui Box 983, Christchurch

A High-Quality Broadcast Tuner

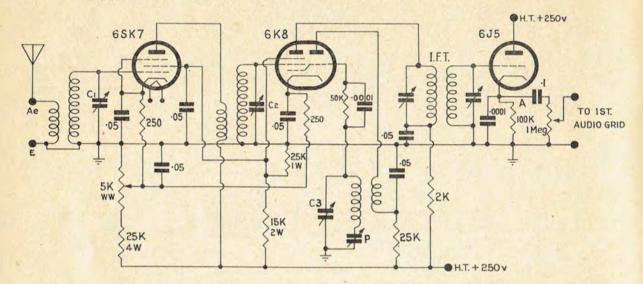FULLY DESCRIBED IN "RADIO AND ELECTRONICS," DECEMBER, 1946



This tuner circuit is a conventional one using an R.F. stage and an oscillator-mixer, but in order to increase the bandwidth and give better response to high audio frequencies, the I.F. stage has been omitted, a low-distortion infinite-impedance detector being used straight after the one and only I.F. transformer.

Please note that there is an important error on the circuit diagram. The 50k, oscillator grid leak should have its lower end connected directly to the cathode of the 6K8, and not to the coil, as shown. The I.F. is 455 kc/sec., or near it, depending on the coils used. These, together with gang, trimmers, and padder, are ordinary broadcast aerial, R.F. and oscillator coils, and the tuner is aligned in the usual way.

One useful feature of the infinite-impedance detector is the low output impedance, which enables the output connection to be made up to 100 feet long without requiring shielding. If this is done, the output should be taken from the point A (the cathode of the 6J5) and the 0.1 μ f. condenser and the volume control should be placed right at the audio amplifier input. If this is not done, the output no longer has a low impedance, and therefore possesses no hum-reducing properties.

Training for Today's Opportunities in Radio

Authorities on Radio write I.C.S. Courses. Radio is too great, too broad and vast for one man to write all about it, or to teach all there is to it.

I.C.S. Courses bring to you the knowledge of outstanding authorities.

Here are some of the Courses:

Complete Radio

Radio Serviceman's Examination Amateur Operators'

1st and 2nd Class Radio Telegraph Operators


1st and 2nd Class Radio Technology


International Correspondence Schools


Dept. 10, Wakefield Chambers,
182 WAKEFIELD STREET, WELLINGTON

An Experimental Two-Stage Amplifier

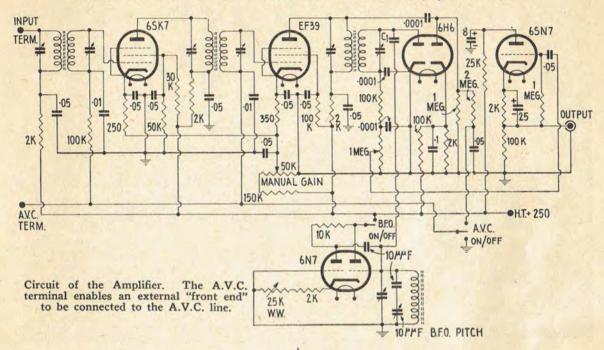
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JANUARY, 1947



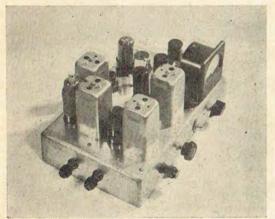

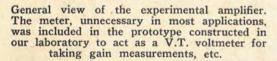

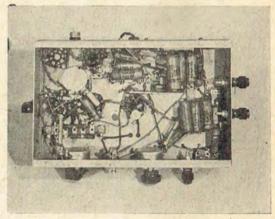This unit was designed for use as the "back end" of a communications receiver, or as an experimental unit with which to test experimental "front ends." It has A.V.C. and manual gain control and a cathode-follower output after the diode detector, so that it can readily be used to feed an external audio amplifier. An A.V.C. terminal is provided so that the R.F.



Underneath view of the amplifier. The terminals on the side are in the plate circuit of the 6SK7, and enable the first stage to be left out of circuit for experiments where only one stage is required.

and mixer stages can have A.V.C. applied to them if desired. The B.F.O. circuit is unusual, and is a very useful one because it does not need a coil with a second winding, or tapping for regeneration. It is a so-called "two-terminal" oscillator, needing only a tuned circuit, which can be made from one winding of an old I.F. transformer.



The above is a photo of the well-stocked shop of S.O.S. Radio Ltd.

The House of a Million Parts

Buy your Radio Components and Kitsets from

S URE

O_F

S ERVICE

RADIO

LTD.


We provide the largest range of Radio Parts and Kitsets with the fastest Mail Order Service in New Zealand, and we pay postage on all orders over £1. We have a large mailing list. Have your name added now.


283 QUEEN STREET, AUCKLAND, C.1

BRANCH SHOP-No. 1 WARD ST., HAMILTON

A High-Gain Low-Noise Preamplifier Using 6AC7's

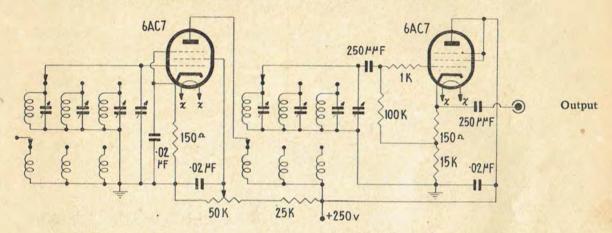FULLY DESCRIBED IN "RADIO AND ELECTRONICS," AUGUST, 1947



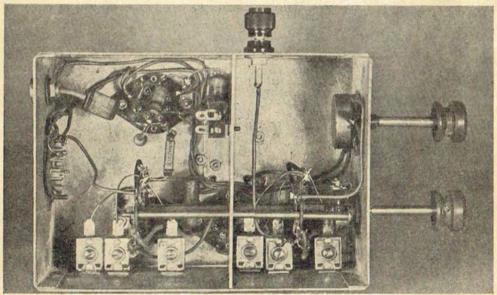

Underneath view, showing layout of trimmers and the placement of the baffle-shield.

This pre-amplifier is intended as an addition to any receiver, and will improve the overall gain considerably, but, WHAT IS MORE IMPORTANT, it will give the whole set a greatly improved signal-to-noise ratio, and will enable weak DX stations to be copied that could only just be heard before. As can be seen from the photograph on this and the next page, it uses triple-wave coils in cans and a wave-change switch. It covers from broadcast to 20 mc/sec. inclusive.


It has a very efficient form of output coupling-

namely, a cathode follower, which matches the impedance of the aerial terminal of the set to which it is attached, without causing any loss of signal voltage. The output lead should be as short as possible, and shielded. The shielded type of connector should be used at the output and the shield braid of the wire

should be firmly earthed to the plug.

Note that an aluminium shield partition is placed across the R.F. amplifier's socket in such a way that grid and plate pins are on opposite sides of it.

This is essential for stable operation.

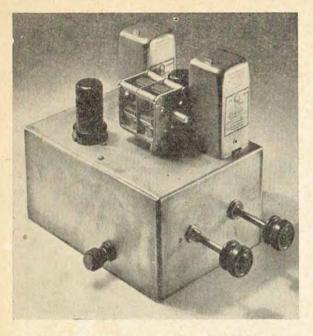

General view of the preamplifier. The right-hand control is the wave-change switch, and that on the left is the gain control. No dial arrangements are shown, but space is available for fitting any type of movement.

Aluminium Radio Aerials HIGH STRENGTH WITH

LOW WEIGHT!

B.A.21 Non-corroding Aluminium Alloy Tubing in sizes ½ in. to 1 in. outside diameters in 16, 18 and 20 gauge wall thickness in 10/12 foot lengths.

With high non-corrosive properties, this tubing is light and efficient, and recommended for radio aerials.

Being of non-heat-treated alloy it is easily weldable and ready for immediate erection.

For your supplies—
CORY-WRIGHT AND SALMON
LTD.

AUCKLAND WELLINGTON DUNEDIN Box 1650, Box 1230, Box 800

RADIO & ELECTRICAL SERVICES Limited, AUCKLAND

OFFICE: Wright's Bldgs., Fort Street. PHONE: 31-687.
FACTORY AND WORKSHOPS: Cr. Gundry St. & Karangahape Rd.,
Newton.

Consulting Radio and Electronic Engineers
ALL REPAIRS AND SERVICE TO HOME RECEIVERS
MANUFACTURERS OF "MINITONE" RADIOS AND "R.E.S."

"CUSTOM-BUILT" RADIOGRAMS

Special Hi-fidelity Sound Reproduction, Coils and I.F. Transformers to order. Industrial Electronics. Photo-cell Counters and Warning Devices. Radio Frequency Heating.

Ship and Small Craft, Radio Phone Installation and Maintenance.

SPECIALISTS IN-F.M. MOBILE RADIO

Office Inter-communication and Paging. Music-while-you-work and Public Address.

Inquiries are welcomed on all matters dealing with Electronics. Our Technical Staff is always available to assist in your problems, and we welcome inquiries from Dealers.

Mullard THE MASTER VALVE



Manufacturers and users of electronic equipment who fit Mullard valves and tubes add to their own wide experience the benefits of Mullard research and development. To the purchaser of such equipment the advantages are clear. He enjoys a double assurance of efficiency and service—he reaps the harvest of Mullard Leadership in Electronics.

MULLARD WILL FILL YOUR NEEDS

AGENTS:


Auckland: Johns Ltd., Chancery Street Wellington: F. J. W. Fear & Co., 31 Willis Street Christchurch: Swan Electric Co., Ltd., 83 Lichfield Street Dunedin: R. H. Gardner, 42 Crawford Street

New Zealand Distributors:

THE C. & A. ODLIN CO., LTD., WELLINGTON

AN ADVANCED SUPER-REGENERATIVE RECEIVER FOR SIX METRES

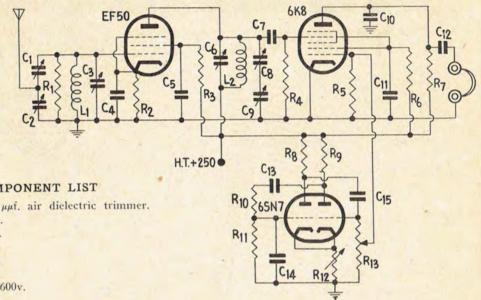FULLY DESCRIBED IN "RADIO AND ELECTRONICS," FEBRUARY, 1948



COMPONENT LIST

C1, C3, C6, C8, 3-30 μμf. air dielectric trimmer.

C2. 100 μμf. variable.

C4. C5, 0.01 µf. 600v.

C₇, 10 μμf. mica.

Co. 25 µµf. variable.

C10, 0.002 µf. 600v.

C11, C12, C15, 0.1 µf. 600v.

C13, C14, 250 µµf.

R1, 9k.

R2, R3, 150 ohms.

R4, 2 meg.

Rs. 50k.

Ro, Rr, Rs, Rs, 25k.

R10, R11, 10k.

R12, 10k. pot. in series with 10k. fixed.

R13, 50k, pot.

L1, L2, see text.

This receiver for the 50-54 mc/sec, band has all the virtues of the super-regenerative set without its drawbacks. The EF50 acts as an R.F. stage, while the 6K8 is a super-regenerative detector, separately quenched by the 6SN7 quench oscillator. The latter has an adjustment for waveform (R12) and injection amplitude (R13), and these can be set for best results. The use of the R.F. stage prevents radiation and eleminates aerial loading on the detector.


The input circuit is novel. C3 is the tuning condenser, and is pre-set to the centre of the band. The resistive loading of R1 then sees that the response at the band edges is no more than 3 db. down on that at the centre. C1 and C2 are also pre-set, and act as an impedance transformer to match the aerial to the grid circuit of the EF50. Different ratios of C1 to C2 are tried, and C3 is retuned at every trial until the setting of C1 and C2 is found that gives the best results for the particular aerial in use.

10 METRE CONVERTER


The converter shown on the opposite page was specially arranged to have exceptionally good signalto-noise ratio for achieving the best possible performance on weak signals in the 10-metre band. It also has remarkable frequency stability and full bandspread. The first detector is an infinite-impedance mixer using a triode-connected 6J7, which is tuned separately from the oscillator. A high-gain I.F. stage on 4 mc/sec. follows, so that, in use, the main receiver is tuned to this frequency. The oscillator circuit is built up separately and then inserted in the small box in the centre of the chassis, and the tube itself is mounted on the side of the box to keep the heat of the valve away from the circuit, thereby minimizing drift. The bandspread condensers have their shafts coming through the front panel, while the shafts of the band-setting condensers come through under the chassis. The coils are wound as follows and mounted on midget stand-off insulators. The windings are self-supporting, except for four in, wide celluloid strips, one of which is used to mount the whole to the insulators. It is recommended that intending builders should consult the original article in "Radio and Electronics" referred to at the heading.

A HIGH-PERFORMANCE 10-METRE CONVERTER

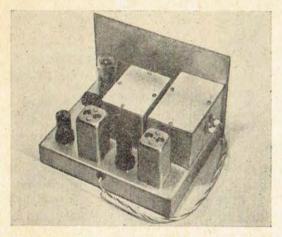
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JULY, 1946



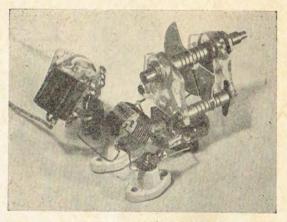Back view of the converter. The oscillator valve can be seen mounted on the side of the central box, which contains the oscillator circuit.



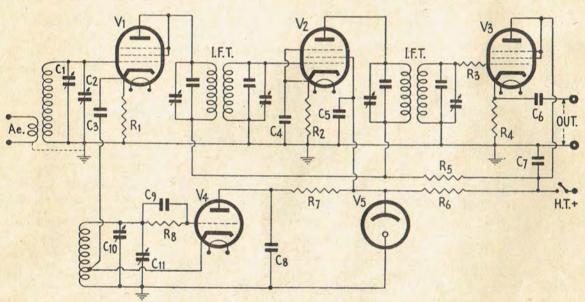View of the oscillator circuit, which was wired up and slipped into the box afterwards, since the box was too small to work in comfortably with the soldering-iron.



C1, C10, 3-25 µµf. pre-set.

C2, C11, 3-10 μμf. variable.

Cs, Cp, 100 µµf. mica.

C1, C5, C7, C8, 0.1 µf.

Ce, 0.001 µf.

R₁, 100k.

R₂, 150 ohms.

Rs, 500 ohms.

R4, 1000 ohms.

R5, 2000 ohms.

Re, 2500 ohms 5w.

R₇, 2500 ohms.

Rs, 25k.

V1, 6J7.

V2, V3, 6AC7/1852.


V4, 6J5.


V5, VR 150/30.

All resistors are 1 watt except R6, which is 5 watt.


The Radel Dual-Wave Six

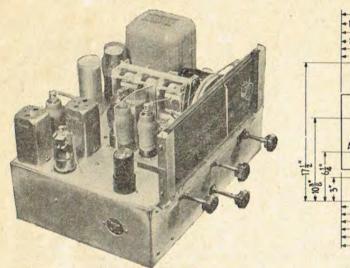FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JUNE, 1947



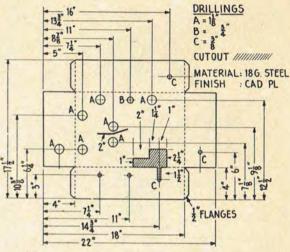

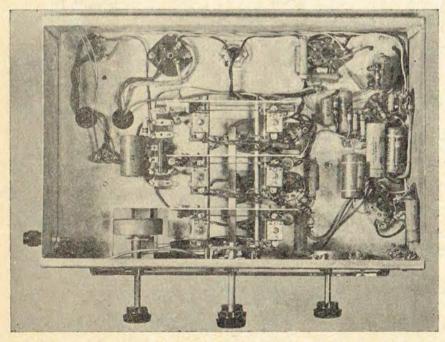General view of the Dual-wave Six. Note the aluminium baffle-shield between the EF39 R.F. stage and the 6F8-G oscillator-mixer.



Left: The under-chassis arrangement. The controls, left to right, are tuning, tone control switch, and volume. The wave change switch shaft is directly beneath the tone control shaft. The tube at the right front of the chassis is the 6V6 output stage. The sockets for the R.F. and oscillator-mixer stages may be seen in the two back compartments of the coil unit. Directly behind the 6V6 socket is that of the 6Q7-GT, while the ones at the back of the chassis are the I.F. amplifier, with the rectifier at the left near the power transformer leads.

Below: Chassis diagram. Note the position of the baffle-shield between the R.F. and mixer stage sockets.

This set is a six-valve dual or triple-wave receiver designed for a console cabinet. It uses a commercial dual or triple-wave coil unit, and is notable for its excellent shortwave performance, which is due largely to the use of the low-noise infinite-impedance mixer. The latter is one-half of a 6F8-G, the other half of which is used as the local oscillator. Coils and I.F. transformers are designed for an I.F. of 455 to 465 kc/sec.

6.3v.,


L1, 1500-ohm speaker field.

C6, three-gang condenser. (See text.) C8, C10, C11, C22, 0.05 μ f. 600v. paper. C13, C14, 100 μ uf. mica.

b), (c), each 25k. 2w.

R17, 1 meg. 3w.

20, 500k. 4w.

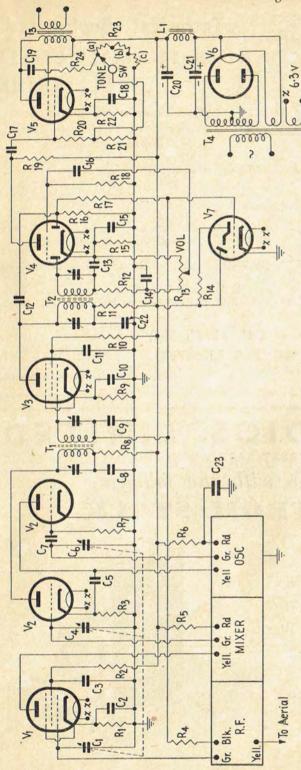

COMPONENT LIST

350 ohms 1w. R3, R6, R10, 100k. ½w. R12, R21, 50k. ½w.

C9, C16, 0.1 μf. 600v. paper.
C12, 50 μμf. mica.
C15, C18, 25 μf. 25v. electro.
C17, 0.25 μf. 600v. paper.
C19, 0.02 μf. 600v. paper.
C20 + C21, dual 10 μf. 450v. electro.
C23, 8 μf. 450v. electro.
V1, V3, EF39.
V2, 6F8-G.
V4, 6Q7-GT.
V5, 6V6.
V6, 80.
V7, 6U5 or 6G5.
T1, T2, 465 kc/sec. I.F. transformers.
T3, speaker transformer, 5000 ohms to V.C.
T4, power transformer, 385-0-385v. 80 ma.,

FOR AMATEUR FOR EXPFRT FOR TRADESMAN

MAIL ORDER SPECIALISTS



Technical Books Ltd. 11 WALTER STREET WELLINGTON

New Zealand's Leading Importers of technical and reference books.

The latest and best books on Radio and Electronics are always stocked, or will be obtained promptly at your request.

Have you these standard r	eference	books?	
A.R.R.L. Radio Amateur Handbook	Engineers) 22/6 22/6 22/6 20 20 20 20 20 20 20 20 20 20 20 20 20	HICKS Principles and Practice of Radio Servicing 3 GREENLEES Amplification and Distribution of Sc 2 BEGUN Magnetic Recording	0/-

TECHNICAL BOOKS LIMITED

Suppliers to anywhere in New Zealand

Phone 56-101

Our address is our show window

WEBB'S RADIOS LIMITED

11 WELLESLEY STREET EAST, AUCKLAND

CAN SUPPLY you with the fo'lowing

KIT-SETS FROM STOCK


- 5 valve Bedside Radio £13/15/-
- 5 valve A.C. and Battery Portable, with plastic case £17/5/-
- 6 valve Dual Wave £17/10/-
- 6 valve Car Radio £17/10/-

ALL kit-sets complete in every detail and contain only the best quality components.

WE can also supply all parts necessary to build up any circuit described in this book at very keen prices.




11 WELLESLEY ST. E, AUCKLAND

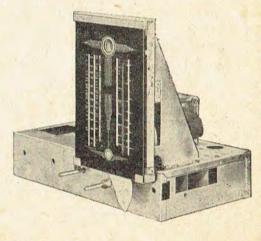

An Idea For A High-Fidelity Tuner

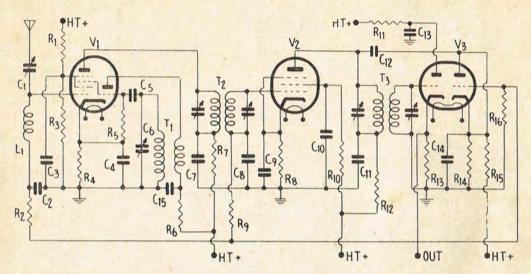FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JULY AND AUGUST, 1948



This tuner is a superhet, circuit with a high-frequency I.F. of 2 mc/sec. This gives it a wide pass-band, and therefore excellent fidelity from local stations. The input to the mixer is untuned, and tuning is done on the oscillator only. The oscillator coil can be a home-made one. Its frequency range is 2.5 to 3.5 mc/sec., so that a 50 μμf. tuning condenser suffices for tuning over the whole broadcast band. Instead of a home-made coil, it is possible to use a commercial coil of the kind used for the oscillator in the intermediate band in all-wave coil units. The method of finding the correct capacities for covering the broadcast band is as follows: Capacity is added in parallel with the coil until the oscillator frequency is 3.5 mc/sec. This should be between 300 and 400 µµf. A variable condenser of approximately 150 to 200 µµf, should then tune the oscillator to 2.5 mc/sec. at maximum capacity.

At the right is an untuned R.F. amplifier which can be added in front of the mixer for situations where the signal-strength of the nearest stations is on the low side.

SWINBURNE'S RADIO SERVICE

Matt. T. Swinburne, Qualified Radio Serviceman


Expert Repairs to All Makes of Radios Manufacturers of Avalon Portable, Electric and Car Radios Phone 31-990

85-87 NEW NORTH ROAD, EDEN TERRACE, AUCKLAND, C.3.

COMPONENT LIST

R1, 25k. 1 watt. R2, R9, R13, 100k. R3, R10, 30k. 1 watt. R4, 350 ohms. R5, R6, R11, 50k. R7, R12, 2k. R14, 7.5k. R8, 200 ohms. R15, 250k. R16, 1 meg. C1, 3–30 µµf. pre-set. C2, C4, C7, C8, C9, C10, C11, 0.05 µf. C5, C12, 50 µµf.

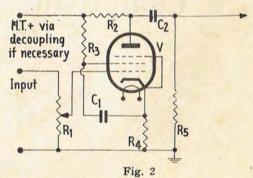
C6, 50 µµf, variable, in series with 3-30 uuf. pre-set. C13, 8 µf. 450v. electro. C3, C14, C15, 0.1 µf. V1, ECH35. V2, 6SG7. V3, 6SN7. T1, osc. coil. (See text) T2, T3, I.F. transformers, 1.6-2.0 mc/sec. L1, 10 µH. R.F.C. H.T., 250v.



R1, not critical, say, 1000 ohms pot.

R2, 10k. R3, 20k.

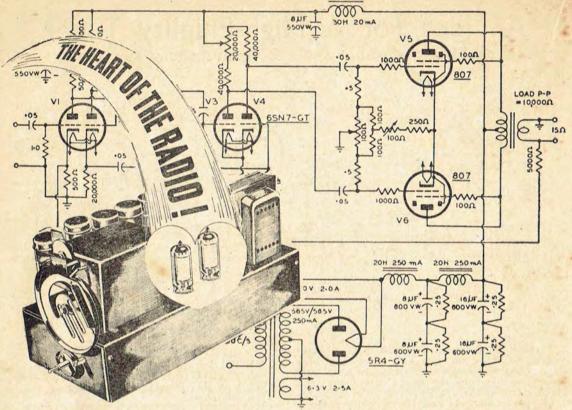R4, 200 ohms. R5, 100k. C1, C2, 0.01 μf. V, EF50,



For utmost efficiency in the application of circuits in this Handbook we recommend Radiotrons—the world's standard radio valves.

Because Radiotrons are manufactured to unvarying standards you will be certain of dependable performance. And because supplies of Radiotrons are coming forward regularly you can be assured of a wide range of available supplies.



Distributors-




AND ENGINEERING COMPANY LIMITED

Auckland, Wellington, Christchurch, Dunedin, Hamilton, Wanganui, Hastings.

Leaders in their respective fields

SOUNDMIRROR 'MAGIC RIBBON' RECORDER

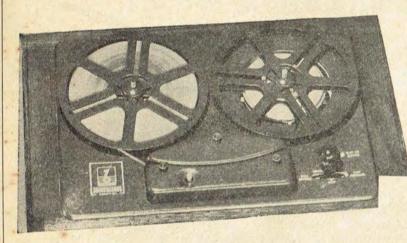

Here it is! The amazing new SOUNDMIRROR Magic Ribbon Recorder, containing everything new in the field of magnetic recording. Now you can record full symphonies right from your radio . . . make permanent recordings of your children's voices . . . in fact, record anything you wish . . . simply, quickly, inexpensively, with

SOUNDMIRROR 'Magic Ribbon' Home Recorder

ERSIN MULTICORE SOLDER

The finest cored solder in the world

THE 7 lb. REEL 13 S.W.G. 45-55% tin-lead alloy highquality radio solder List price 9/4 per pound

THE RED CARTON 18 S.W.G. 60% tin, 40% lead List price 7/8 per carton THE GREEN CARTON 13 S.W.G. 40% tin, 60% lead List price 6/5 per carton



Sole New Zealand Distributors:

GILES & ELLIOTT


9-11 Blair Street

G.P.O. Box 1647

Wellington

Seven-Valve Quality Broadcast Receiver

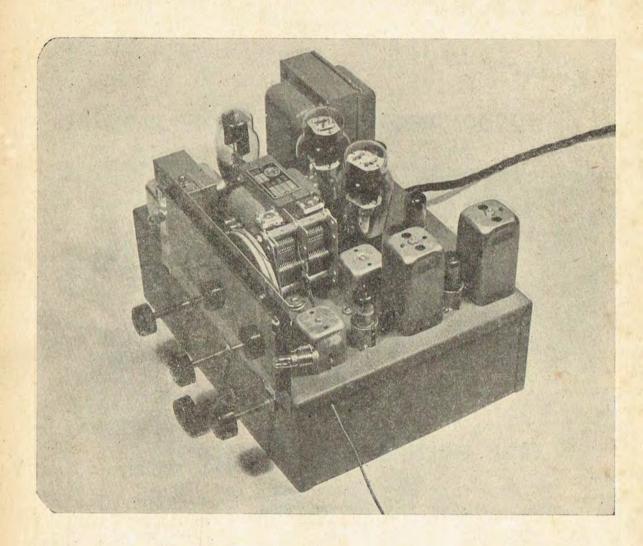FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, 1948





This receiver is one for quality enthusiasts, and, owing to the excellent push-pull triode amplifier which is incorporated in it, it makes an admirable radio-gram unit. Provision is made for the use of two-position variable selectivity I.F. transformers. Rimlock valves are used in the R.F. end, and give the set ample sensitivity for distant as well as for local broadcast reception. An R.F. stage has been purposely omitted so that the constructor will be unlikely to get undesired regeneration, which could completely vitiate the extra bandwidth of the I.F. amplifier in the "broad" position, thereby defeating

the purpose of the set.

Provision is made for a built-in radio/gram, switch which opens the cathode of the I.F. amplifier on the "gram" position, thus preventing all chance of radio break-through.

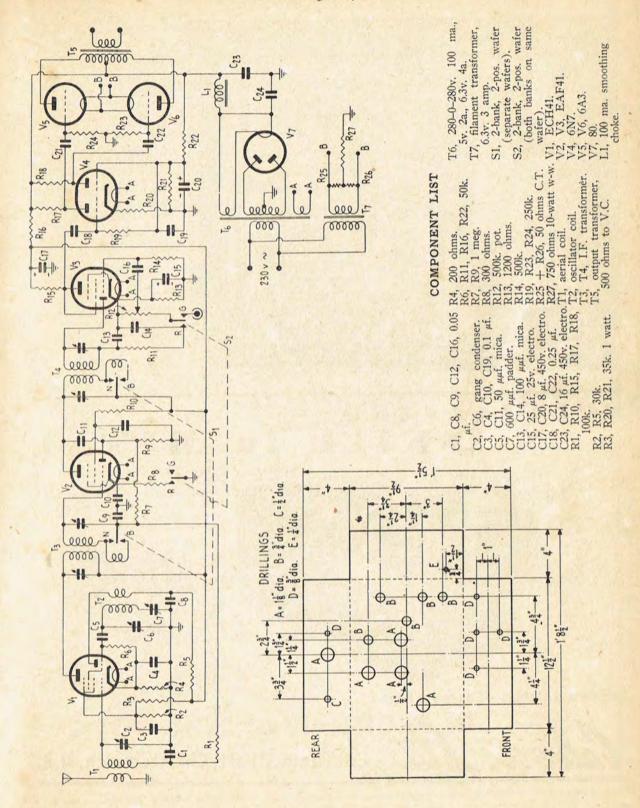
The mixer valve, V1, can be seen in the front right-hand corner of the set, between the aerial coil and the first I.F. transformer. The oscillator coil is between the gang condenser and the first I.F. transformer. The 6N7 phase-inverter is almost obscured in the photographs by the 6A3's, but V3 can be seen directly behind the right-hand 6A3.



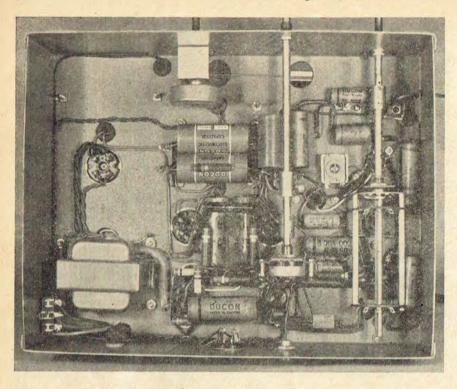

Under-chassis view. Note how the bandwidth switch is mounted in line with the I.F. transformers with the wafers one over each transformer. Note also that the volume control is operated by an extension shaft and is mounted on a bracket just in front of the V3 socket. The radio/gram switch is also on this bracket immediately under the pot. Its extension shaft cannot be seen in the photograph.

SPECIALIZED SKILL in METAL

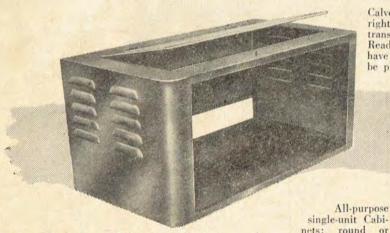


single-unit Cabinets; round or square ends; wrinkle

finish; round ends: 22" x 10" x 12"; square ends: 194" x 10" x 12". **£2/5/- each**

Cabinets - Panels - Chassis - Racks

Calverts Ltd. 138 Tuam Street, Christchurch, N Z.

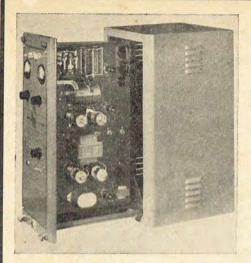Calverts can supply you with the right Chassis or Cabinet to give your transmitter the professional touch. Read our prices and order now. If you have a special job in mind, we would be pleased to quote.



Electronic Navigation Ltd.

Presents

The Eyes and Ears on Land and Sea

To aid the Mariner, Harbour Board, Power Board, Transport, Taxi Co., Communications Engineer, Fire Brigade, Ambulance,

WITH RADAR

RADIO DIRECTION FINDERS

OR RADIO-COMMUNICATION EOUIPMENT

Maintenance of-

Marine Gyro-Compass, Depth-recording Equipment, and All Navigation and Elec-

tronic Equipment.

RADIO PHONE

TRANSMITTER:

- (1) 3-channel, crystal controlled
- (2) Frequency range, 1.5 to 4 mc/sec.
- (3) Power output, 65 watts in Ant.
- (4) Battery or mains operated

PORTABLE FIELD

TRANSMITTER:

Phone and M.C.W., special non-corroding alloy cabinet and chassis. Power output, 30 watts in the Ant. 2 channel crystal controlled. Frequency range 1.5 to 4 mc/sec. or 4 to 6 mc/sec. Battery operated.

MARINE RADIO DIRECTION FINDER:

Sensitive superhet, receiver, Frequency range, 200 to 400 kc/sec. Effective balance control. Visual bearing indicator. Specially designed deviation correctors will reduce a 20 deg. error to zero. 6-12-24v. D.C. supply.

FOR ALL INDUSTRIES! INDUSTRIAL ELECTRONIC EQUIPMENT INSTRUMENTAL PANELS MACHINE AND NAME PLATES SIGNS AND NOTICES

ELECTRONIC NAVIGATION LTD.

NAGEL HOUSE, COURTHOUSE LANE, Code AUCKLAND

P.O. Box 1905. Phone: 40-576



RADAR

For Dial Scales
Remember
Rotoscreen

"Rotoscreen" for Perfect Finish

ROTOSCREEN LIMITED

BOWEN HOUSE
BOWEN STREET - WELLINGTON
Phone 44-386

A Radio Tuner with Multi-Point Selectivity for High-Fidelity Reproductions

FULLY DESCRIBED IN "RADIO AND ELEC-TRONICS, OCTOBER AND NOVEMBER, 1948

This is an advanced circuit in which variable selectivity is obtained by using two separate tuned circuits, coupled by capacity networks. The slugtuned coils are aligned in the ordinary way with the switch in the "narrow" position—i.e., with the condensers C12, C14, C17 in circuit. Thereafter, no adjustments are needed when the switch is moved to the intermediate and wide positions. If this is to work out properly in practice, the network condensers must be accurate to within 5 per cent., as indicated on the circuit diagram.

A cathode-follower output valve is used to enable a long line to be run to the amplifier, without danger of picking up hum. The line can also be shielded without any danger of losing high-frequency response if the cathode-follower is used. It is strongly recommended that the above-mentioned articles in "Radio and Electronics" be consulted by intending builders.

To Radio Enthusiasts

We can supply all the components to build any circuit in this book.

SINCE its inception, the name of our firm has always been associated with quality. Every line we stock is the product of leading makers and, at all times, we buy components and parts from manufacturers who are leaders in their respective fields.


IN consequence, we carry no "job" or bargain lines; this, in our opinion, is a wise step because our big clientele, including those who buy by mail, know that if we stock it, then it's good.


WE CARRY NEW ZEALAND'S LARGEST SELECTION OF QUALITY RADIO COMPONENTS.


TRICITY HOUSE

209 MANCHESTER ST., BOX 1410. (L. D. Hepburn Ltd.)

PHONE 35-051 CHRISTCHURCH

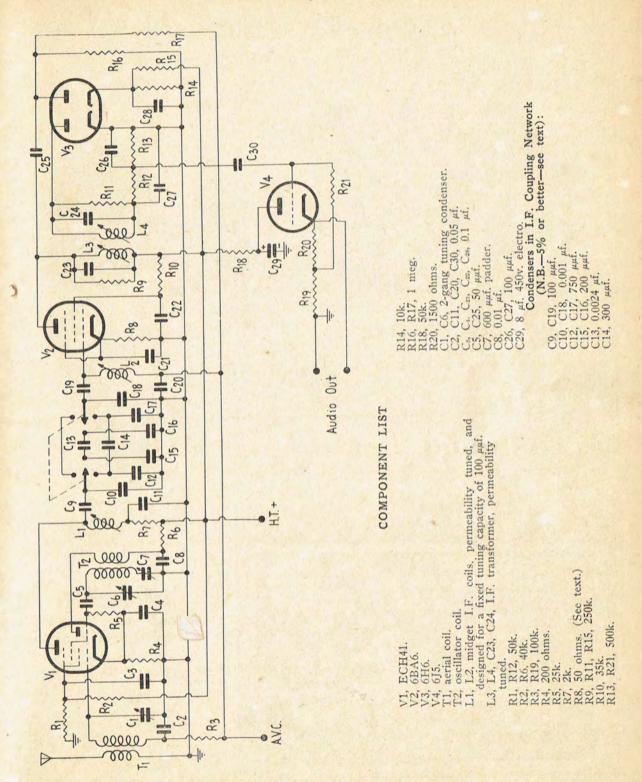

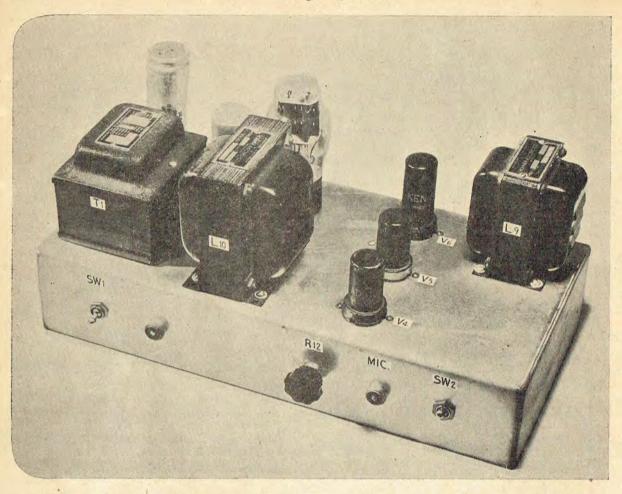

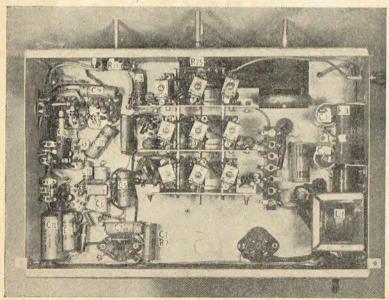

Under-chassis view of the All-wave Eight. The coil unit is in the exact centre of the chassis, with the tonecontrol mounted directly underneath the wave-change switch shaft.

The Radel All-Wave Eight

Fully described in "Radio and Electronics", November, 1947

This set is an excellent all-purpose receiver for broadcast, shortwave, and gramophone reproduction. The chassis is the same size as that of the "Radel Dualwave Six," an extra pair of valve holes being drilled between the two at the left-hand edge of the chassis.

Important Note.—There is an error in the circuit diagram which shows the cathode of V4 and the upper and of P11.

Important Note.—There is an error in the circuit diagram which shows the cathode of V4 and the upper end of R11 joined to the H.T. line. The dot which indicates this should be replaced by a cross-over to correct the diagram.

DRILLINGS $A = \frac{1}{8}$ $B = \frac{3}{4}$ $C = \frac{3}{8}$

C


TELANGES

CUTOUT /////////

MATERIAL: 186. STEEL FINISH : CAD. PL.

18 9

- 12

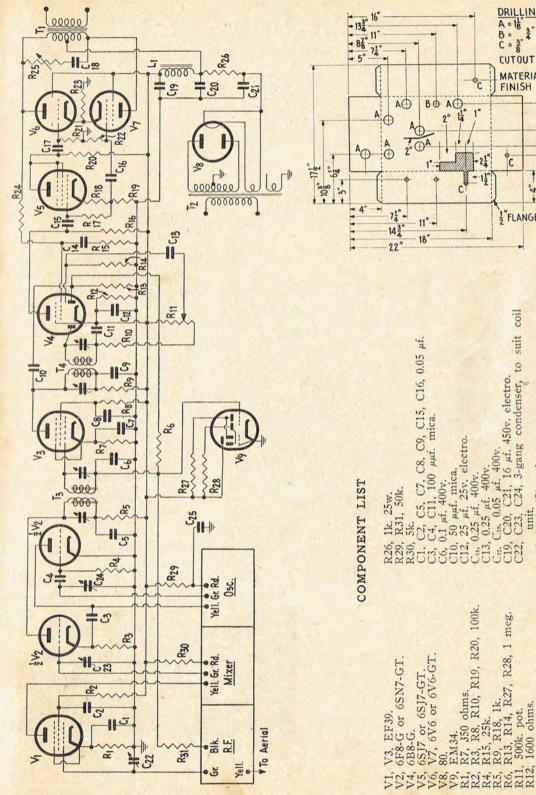

0.25 μf. 400v. Cs. 0.05 μf. 400v. C20, C21, 16 μf. 450v. electro. C23, C24, 3-gang condenser, to suit coil

unit. C25, 8 µf. 450v. electro. T1, output transformer 10,000 ohms to V.C. T2 power transformer 385-0-385v., 5v. 2 amp.,

6.3v. 4 amp.

125 ohms 2 watts.

1.2 megs. 50k. pot.

1600 ohms. R17, 250k. R22, 500k.


> R16, R21, R23, R24, R25,

500k. pot.


L1, 20H. 50 ma. T3, T4, I.F. transformers, iron-cored.

The Radel DX Broadcast 12

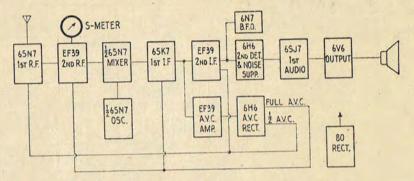FULLY DESCRIBED IN "RADIO AND ELECTRONICS," APRIL, MAY, JUNE, 1947



Block diagram of the receiver

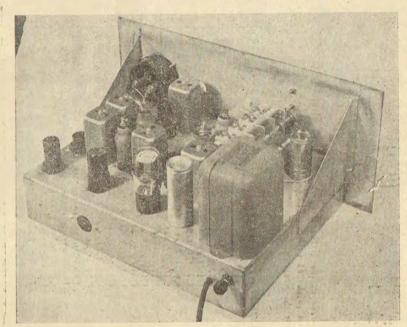


This is quite the most ambitious receiver in this book, but many have been built by amateur constructors with complete success.

We strongly recommend that the relevant articles in "Radio and Electronics" are consulted by intending builders, although very complete details are given here.


This set was specially designed for broadcast DX work, and has many features only to be found in communications receivers.

The block diagram indicates most of its outstanding features, which include triode first R.F. and mixer stages for good signal-to-noise ratio and amplifier A.V.C. In addition, there is a noise-limiter, and a beat frequency oscillator which can be used for detecting the presence of weak carriers.

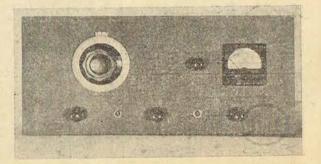The controls from left to right are: Tone, A.V.C. on/off, R.F. gain, noise-limiter on/off, and audio gain. The B.F.O. pitch condenser is at the left of the S-meter.



Front panel

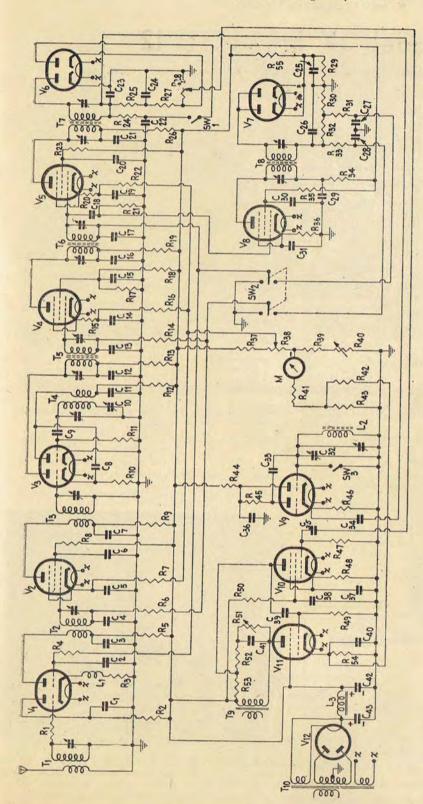

25 µf. 25v. electro; C42, C43, dual 8 µf. electrolytic;; push-back wire twisted together for * inch. C33, 0.00001 µf.: C15, variable: C26, 0.0001 µf.; 0.0005 µf pieces of

R45, 50k.; R6, R8, R18, 25k.; R15, R20

R26, R34, 2000 ohms; R3, R7, R48, R54, 500 ohms; R4, R14, R17, R25, R30, R32, R37, R44, R45, 50k; R6, R10, R23, R27, R35, R53, 100k; R17, D18, oct., D18

1500 ohms; R2, R5, R9, R13,

Resistances: R1.

150 ohms; R21, R49, R50, R52, 500k.; R24, R33, R47, 1 meg.; R28, 1 meg. potentiometer; R29, 10k.; R31, R55, 250k.; R36, ohms; R39, R43, 200 ohms; R40, 100-ohm potentiometer;

R42, 350 ohms; R46, 5000 ohms; R38, 10k

potentiometer; R51, 2 meg. potentiometer.

R41, 3000 ohms;

4000

.; SW2, toggle switch D.P.D.T. V4, 6SK7; V8, EF39; Switches: SW1, toggle switch S.P.S.T V3, V9, 6SN7GT; Mcters: M, 0-1 ma. Transformers: T5, T6, T7, Valves: V1,

T8, 465 kc. I.F.'s; T9, speaker trans-

380-0-385v.-6.3v.-5v.;

transformer,

power


L2, B.F.O. coil

former:


Condensers: C1, C4, C17, C25, 0.02 µf.; C3, C5, C6, C7, C11, C36, 0.05 µf.; C2, C13, C14, C16, C19, C20, C21, C22,

The valve holes are for use as follows: Looking at the chassis diagram, and reading from left to right, we have:

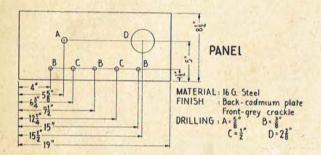
Back row: V12, V11, V10. Second row: V4, V5, V6. Third row: V3, V8, V7. Front row: V1, V2, V9.




Working drawing for front panel.

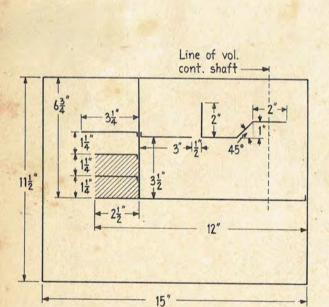


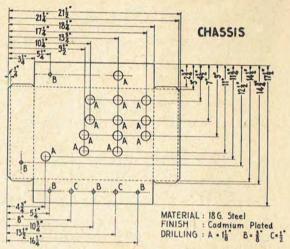Under-chassis diagrammatic view of the "Broadcast 12," showing the layout of baffle-shielding. This is most important to the stability of the receiver, and should be installed exactly as shown. The cross-lined portion is explained in the text.




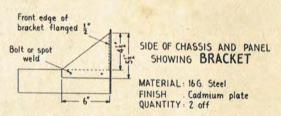

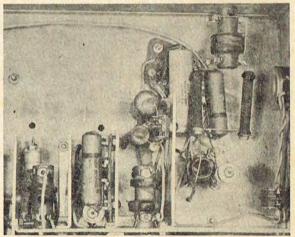Working drawings for chassis and panel mounting bracket.



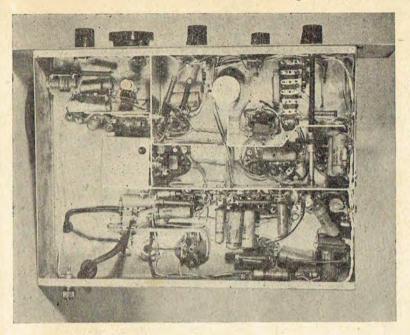Detailed view of the mounting of R.F. aerial and oscillator coils. In this photograph, the right-hand edge is the front of the chassis. Along the bottom edge of the picture can be seen the 63 in. baffle-shield,



General underneath view. The portion enlarged in the photograph on the preceding page is the left-hand upper corner in this photo. Here the 6\frac{3}{4} in. baffle, which runs vertically at the right of the other picture, can be seen at right-angles to the front edge of the chassis, with the second R.F. stage and oscillator mixer sockets on the right, and the R.F. compartments to the left. The potentiometer near the centre front of the chassis is the zero-adjuster for the S-meter. The audio gain control can be seen at the right, with its extension shaft to the main baffle-shield at the back, where the potentiometer is located, close to the second detector circuit. The valve sockets just in front of this baffle-shield and at the right of the chassis are those of the A.V.C. amplifier and rectifier.

The Accent is on Quality!

COMPONENTS

ACCESSORIES

MATERIALS · TESTING EQUIPMENT

For the manufacture, installation and maintenance of electronic apparatus.

ALLUM ELECTRICAL COMPANY LIMITED

A U C K L A N D
Pukemiro Buildings,
Anzac Avenue, C.1
P.O. Box 2219
Telephone 32-160
4 lines

WELLINGTON Nathan's Building,

Grey Street, C.1 P.O. Box 980 Telephones 43-590, 46-651 CHRISTCHURCH

Somerset House Hereford St., C.1 P.O. Box 1193 Telephone 36-736 DUNEDIN

Marshall Chambers, 399 Moray Place, C.1 P.O. Box 384 Telephone 11-531

LAMPHOUSE RADIO BOOKS!



"The Lamphouse" RADIO CIRCUIT BOOK

An 80-page booklet containing nearly 200 different Circuits. Circuits of all types, from Crystal Sets to a 26-valve De Circuits of all types, from Crystal Sets to a 26-valve De Luxe Receiver. Amplifiers, power packs, electric fence units, testing equipment, shortwave converters, wave traps, oscillators, aerial systems—in short, a Circuit to meet every requirement. Schematic diagrams only are given and not constructional details. No claim is made that this book contains any new Circuits, all having previously been published in Lamphouse Annuals or Radiograms.

Enthusiasts, whether beginners or experienced servicemen, will find this book invaluable as a reference medium. Your Radio Library will not be complete without a copy.

Cat. No. EB100—Radio Circuit Book. Priced at 2/6 (Postage, etc., 1d. extra.)

"The Lamphouse" RADIO DATA BOOK

A 96-page booklet containing a veritable goldmine of both Radio and Electrical Data, Facts, Figures, and Charts gathered from various Radio and Electrical Text-books and Manuals, and placed botween two covers to form the handiest reference guide an experimenter or serviceman could wish for BE SURE AND GET YOUR COPY.

Cat. No. EB103-Lamphouse Data Book 3/6 (Postage, etc., 2d. extra.)

"The Lamphouse" RADIO INSTRUCTION BOOK

This 48-page attractively covered booklet contains a simple yet most thorough Radio Course. Compiled from previous Lamphouse publications, revised and rewritten in simple, everyday language for those enthusiasts starting out in Radio as a hobby or a career. Devoid of any deep technical terms as used by Radio veterans. Just a straightout study in basic radio principles and theory. Questions set and answers given on each chapter. Cat. No. EB101—Lamphouse Instruction Course 2/6 (Postage, 1d. extra.)

THE LAMPHOUSE ANN

Published Yearly!

The biggest publication of its kind in New Zealand. Contains nearly 130 pages crammed from cover to cover with useful Radio and Electrical information.

Apart from containing one of the most up-to-date STATION LOGS, covering Australian, New Zealand, and shortwave stations, the Annual contains many proven circuits of different types of sets, workshop hints and kinks for the hobbyist, reference tables, etc.

PLUS

Descriptions and illustrations of the hundreds of bargains available from THE LAMPHOUSE, NEW ZEA-LAND'S LARGEST RADIO AND ELECTRICAL HOUSE.

COPIES AVAILABLE!

POSTAGE, Etc., 3d. each


TA MIPHIDUSE

Mail Order Section, 11 MANNERS ST., WELLINGTON, C.1.




A Compact 4½-Watt Gramophone Amplifier

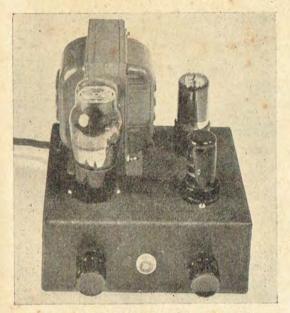FULLY DESCRIBED IN "RADIO AND ELECTRONICS," NOVEMBER, 1946



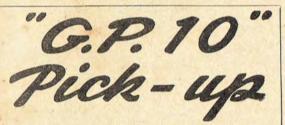GENERAL VIEW OF THE AMPLIFIER
The control on the left is the bass boosting pot.,
while the volume control is on the right.






Limited quantities of this "ACOS" product are still available at 44/- complete. Includes the famous G.P.9 Crystal Cartridge, which is unique in that it is virtually impossible to break the crystal.

Order from Dealers

New Zealand Distributors:

SWAN ELECTRIC Co. Ltd.

AUCKLAND WELLINGTON DUNEDIN CHRISTCHURCH

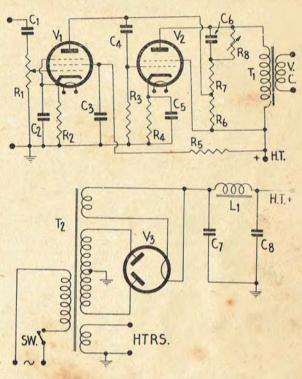

COMPONENT LIST

R1, 1 meg. pot.

R2, 500 ohms.

R3, R5, R7, 500k.

R4, 250 ohms.

R6, 100k.

R8, 500k. pot.

C1, C4, 0.1 µf. 600v.

C2, C5, 50µf. 25v. electro.

C3, 0.5 µf. 600v.

C6, 0.001 mica.

C7, C8, 16 µf. 450v. electro.

T1, output transformer, 5000 ohms to voice-coil.

T2, power transformer, 385-0-385v. 80 ma., 6.3v. 3 amp.., 5v. 2 amp.

V1, 6SJ7.

V2, 6V6-GT.

V3, 80.

L1, 2000 ohms speaker field.

Note.—If greater effective bass-boost is required from the bass-boosting type of tone-control used, C6 can be decreased in value (say, to 0.0005 μ f.) and R8 increased to 2 meg.

A Two-Valve Battery-Operated Amplifier

FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JANUARY, 1947

COMPONENT LIST

(a) For 1C5 Output Stage:

R1, 1 meg. pot.

R2, 10 meg.

R3, 250k. R4, 0.5 meg. R5, 800 ohms.

R6, 25k. pot. C1, C4, 0.1 μf. C2, 0.05 μf.


C3, 0.0001 µf. C5, 25µf. 25v. electro.

C6, 0.01 µf. V1, 1H5-GT. V2, 1C5-G or GT. T1, 9000 ohms—V.C.

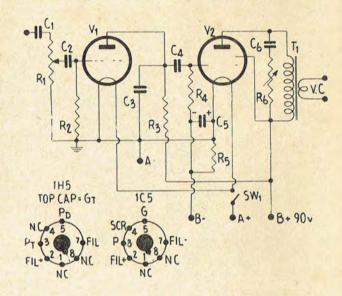(b) For 105-GT Output Stage:


All values the same except for-

V2, 1Q5-GT. T1, 8000 ohms—V.C. R5, 400 ohms.



A Small Amplifier for Vibrator Operation

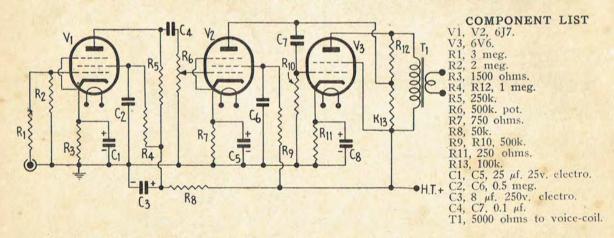
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, 1948



Note.—This amplifier is arranged for working from a crystal microphone, or similar low-output type. If it is wanted for gramophone use only, the first 6J7 stage can be omitted. The output power will depend on the H.T. voltage used, but if the vibrator power pack can deliver 60 ma. at 250 volts, a full 42 watts will be obtained. Lower H.T. voltages giving somewhat less power output can be used without change of circuit values.


A QUALITY 6A3 AMPLIFIER

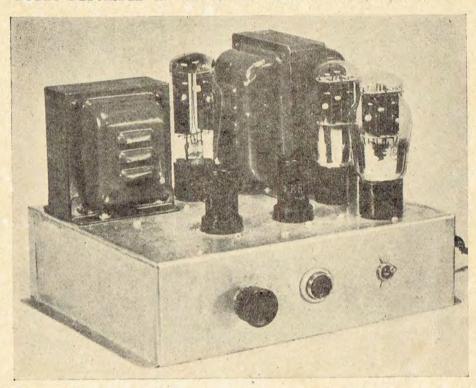
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," APRIL, 1946



This is an excellent amplifier for those who do not want anything very elaborate and yet want better than average quality. It can be used, as can most of the following circuits, either as a gramophone amplifier or as part of a complete set. It can also be used as a driver for a Class B high-powered amplifier. The power output is great enough to drive most Class B tubes rated to deliver 100 watts of audio. In this application, the only modification to the amplifier circuit would be to replace the output transformer by a Class B input transformer, which would feed the grids of the Class B stage.

This amplifier was designed when electro-magnetic speakers were available, and it will be noted that the second smoothing choke in the power supply filter has been specified as a 750-ohm field winding. These days, E.M. speakers are the exception rather than the rule, and most constructors will wish to replace the field winding with a second choke. This can be done quite successfully, as long as a resistor is used in series with it so that the total resistance (choke plus resistor) is 750 ohms. If this is not done, the H.T. voltage will be rather on the high side. An alternative arrangement is to use a different power transformer, of only 320-volts-a-side. In this case, no extra resistance will be needed in series with the second choke.

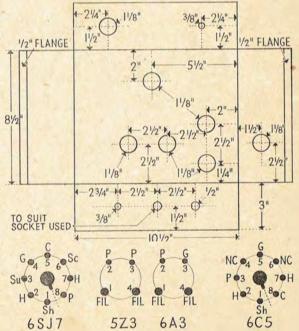


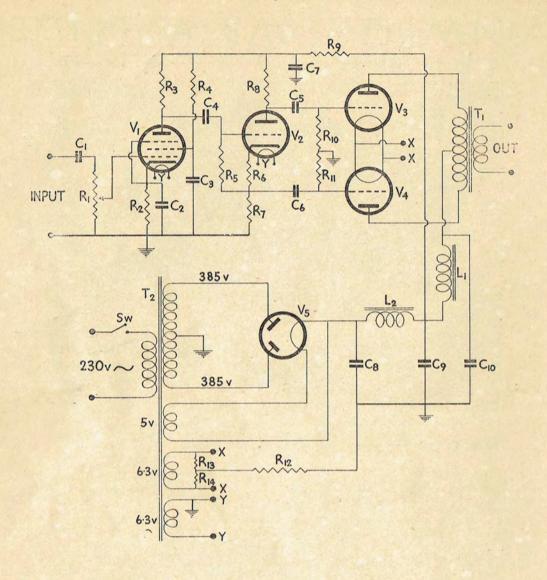

COMPONENT LIST

- C1, C4, C5, C6, 0.1 600v.
- C2, 50 µf. 25v. electrolytic.
- C3, 1 µf. 600v.
- C7 to C10 inclusive, 8 µf. 450v. electrolytic.
- V1, 6SJ7.
- V2, 6C5.
- V3, V4, 6A3.
- V5, 5Z3.
- L1, 1000 ohm speaker field.
- L2, 120 ma. 30 H choke.

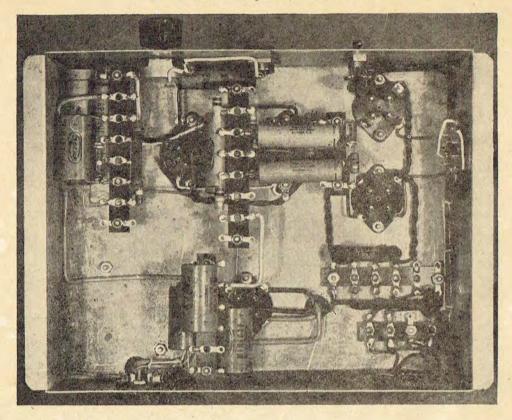- T1, output transformer to match 5000 P-P to voice-
- T2, Power transformer, 120 ma.
- R1, 1 meg. pot.
- R2, 500 ohms.
- R3, 100k.
- R4, R10, R11, 500k.
- R5, 1 meg.
- R6, 10k.
- R7, R8, 100k.
- R9, 25k.
- R12, 750 ohms 10 watts, wire-wound.
- R13, R14, each made up of two 50-ohm ½-watt resistors in parallel.



Special Electronic Equipment WELLINGTON ELECTRONICS LTD

33 Harris Street WELLINGTON

ARE MANUFACTURERS OF AND CONSULTING ENGINEERS FOR ALL TYPES OF ELECTRONIC CONTROL, MEASURING, AND INDICATING DEVICES.


Electronic Counting, Sorting, Detecting, and Timing Equipment—Industrial Temperature Controls— Stroboscopes — General and Special Purpose Oscilloscopes.

FOR THAT SPECIAL ELÊCTRONIC PROBLEM
Consult

Note only address— WELLINGTON ELECTRONICS LTD.,
33 Harris Street, Wellington Phone 45-756

A Response-Compensated 6L6 Amplifier

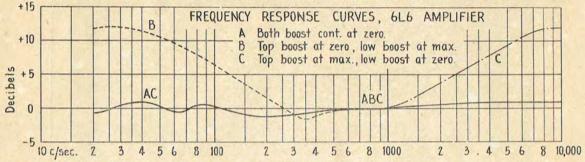
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JANUARY, 1948




Response curves of the amplifier, taken on loud speaker load.

This amplifier fills the requirement for one with independent bass and treble boost controls. The response curves above show the different types of response that can be got with the controls at their maximum positions. Of course, intermediate settings

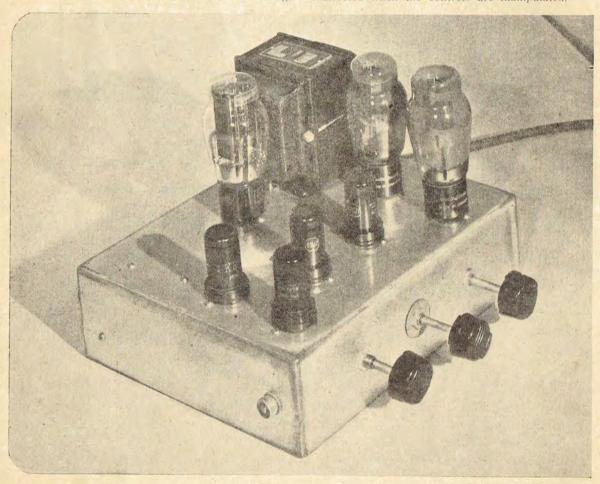will give intermediate degrees of boost between the flat curve and the maximum boost curves. The controls act in such a way as to leave the overall volume unaffected when the controls are manipulated.



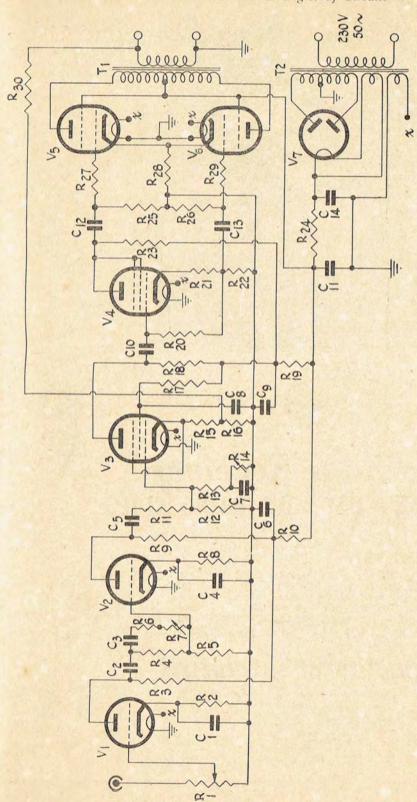

COMPONENT LIST

R10, 100k. 1 watt.
R15, 1500 ohms.
R16, 10 ohms.
R19, 50k. 1 watt.
R22, R23, R27, R29, 100k.
R10, C10, C2, C5, ohms.
R24, R25, R26, 500k.
R30, 250 ohms.
C1, C4, 25 µt. 25v. electro.
C2, C5, C1 µt. 600v.

5 meg. pot.

2 meg. pot.

C6, C9, 16 μ f. 350v. electro.

C7, C10, 0.01 μ f. 600v.


C8, 0.5 μ f. 600v. paper.

C11, 50 μ f. 350v. electro.

C12, C13, 0.25 μ f. 600v.

C14, two 8 μ f. 450v. electros. in series, each shunted

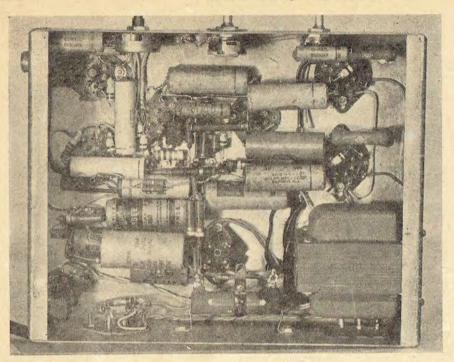
by 1 meg, T1, output transformer 5000 ohms p-p to voice coil. T2, 400-0-400v. 150 ma.; 5v. 3 amp.; 6.3v. 4 amp.



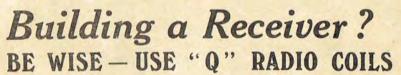Under-chassis view of the amplifier, showing how the output transformer is mounted in the right-hand corner of the chassis.









HERE'S THE REASON WHY

(1) We are New Zealand's only specialists in Radio Coils.

(2) We list and stock the largest range of Coils in New Zealand.
(3) All Coils are tested and matched to ensure perfect operation.
(4) Full technical data are available covering our Coils and "Basic Kits."
(5) Matched kits are available for equipment described in this publication.

Write for our List - Free, Post Free.

Wellington, N.1.





Ducon Condensers are functioning in every applicable field and have done so for many years.

Available now from our New Zealand works is a comprehensive range which includes:—

- Standard paper tubular
- Midget paper tubular
- D.C. Electrolytic
- Motor Start Electrolytic
- Oil or wax filled D.C. metal cased
- Oil filled A.C. metal cased
- Noise suppression
- Ignition
- Ceramicons



DUCON (N

WORKS: 25-35 Haining St.


(N.Z.) LTD.

OFFICE: 21 Grey St., P.O. Box 630.

WELLINGTON


The Enlarged 6A3 Amplifier

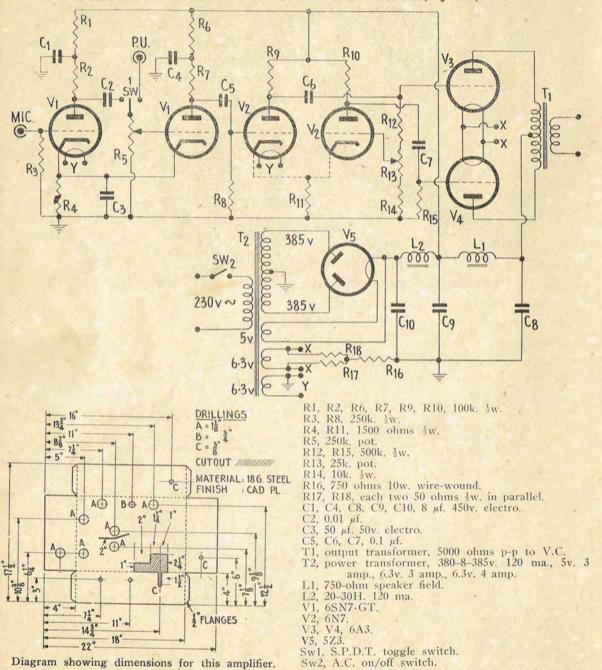FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JUNE, 1947



This amplifier has two input connections, one at low gain, for a radio tuner or gramophone pick-up, and the other, at high gain, for a low-level microphone. No mixing circuit is used, but instead a switch is incorporated so that either channel can be selected at will. The 750-ohm speaker field can be

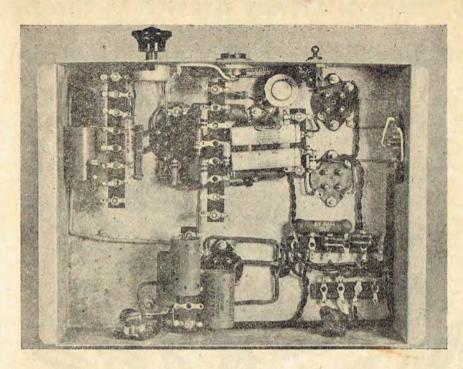replaced by a second choke if a permanent-magnet speaker is to be used, but resistance should be placed in series with the second choke to bring its total resistance up to 750 ohms. Unless this is done, the H. T yoltage will be rather on the high side,



Under-chassis view of the amplifier on the previous page. The use of strips to mount the small parts contributes to the clean and even empty-looking appearance of the chassis and to the ease with which access is gained to every part should servicing be necessary at any time.

ARTHUR D. RILEY & Co., Ltd.

Represent:

FERRANTI, LTD., England: Industrial and Radio Instruments; Watthour Meters; Industrial and Radio Condensers; Electric Clocks; Current and Distribution Transformers; Voltage Regulators; Electronic Equipment; Clip-on Voltammeters.

FERGUSON PAILIN, LTD., England: Indoor and Outdoor Switchgear for Low, High, and Extra High Voltages; Rotary Control Switches; Instrument Switches; Industrial and Mining Switchgear.

BULLERS, LTD., England:

Porcelain Insulators and Ironwork for Electrical Transmission and Distribution Systems; Radio Ceramics.

GREENGATE & IRWELL RUBBER CO., LTD., England:

Wires and Cable.

THE MACFARLANE ENGINEERING CO., LTD., Scotland:

A.C. and D.C. Motors; Arc Welding Generator Sets; Motor Alternators; also the MAGNICON for High-speed Control Applications of Weak Signals for Remote Control of Heavy Power Equipment.

TUNSTONE PRODUCTS, LTD., England: Secondary Batteries for Works, Telephone Exchanges, Country Houses, Cinemas, Yachts, and Train Lighting.

CONTRACTOR SWITCHGEAR, LTD., England: Automatic Starters; Controllers; Push-Button Switches; Pressure Switches; Limit Switches.

AC-ELEC (PTY.), LTD., Australia: Burndy Quicklug Cable Connectors; D.C. Circuit reakers; Steel Towers and Structures.

LINE MATERIAL COMPANY, Canada and U.S.A.: Lightning Arrestors; Line Construction Equipment, etc.


ARTHUR D. RILEY & CO., LTD.

124 Hobson Street, AUCKLAND

WELLINGTON 66-68 The Terrace,



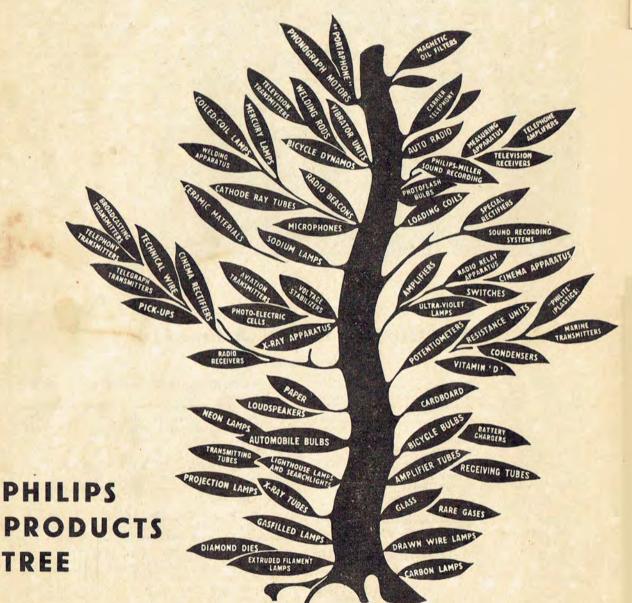60 years of steady growth in the fields of Electricity, Radio and Electronics




PHILIPS ELECTRICAL INDUSTRIES of N.Z. LTD.

Head Office: CORNER WILLIS & BOND STS. WELLINGTON. P.O. BOX 1673

Branches at AUCKLAND - WELLINGTON - CHRISTCHURCH - DUNEDIN

A New Triode Audio Amplifier

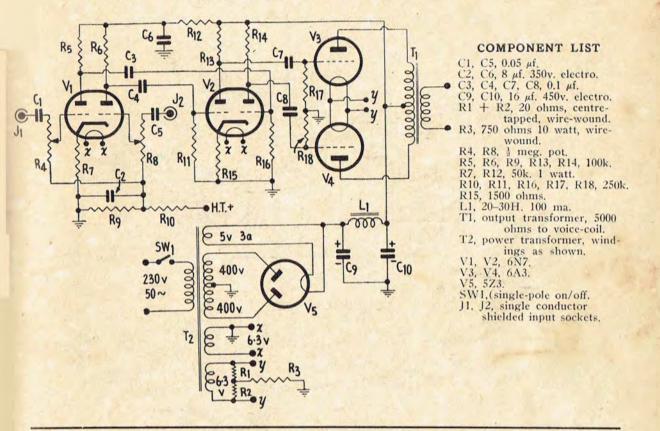
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JUNE, 1948



Nelson,
Canterbury,
Wellington,
Hawke's Bay,
Taranaki
Provincial Distributors

AUTOCRAT DISTRIBU-TORS, LTD., 20 Victoria St., Wellington

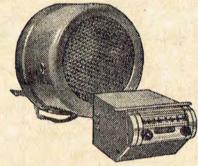Otago and Southland: ELECTRIC & PLUMBING SUPPLIES, Ltd. 149 Stuart St., Dunedin



'AUTOCRAT' CAR RADIO

Retail Price £34-9-0

SIX-VALVE RECEIVERS BUILT TO WITH-STAND THE ROUGHEST CONDITIONS TO BE EXPERIENCED IN NEW ZEALAND.

Special and exclusive Autocrat features ensure perfect reception under the most adverse conditions. We stand confidently behind any demonstration a prospective buyer may require. Note these features: High gain aerial circuit, latest metal type valves, low current drain—4½ amps. 6 volt or 2½ amps. 12 volt.


Manufacturers:

AUTOCRAT RADIO LTD.

PHONE 48-180 :: 118 VICTORIA STREET, AUCKLAND

Some Tested Circuits For 807's As Audio Amplifiers

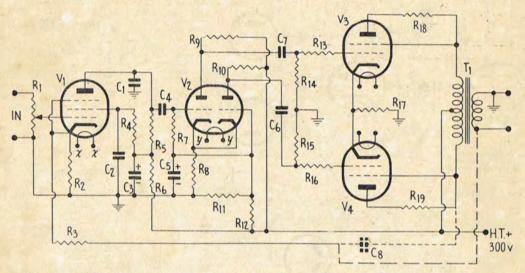FULLY DESCRIBED IN "RADIO AND ELECTONICS," SEPTEMBER, 1948



COMPONENT LIST

R1, 1 meg. pot. R2, 1600 ohms. R3, 250k. (min.) (see text). R4, R7, 250k. R5, R9, R13, R16, 100k. R6, R11, 25k. R8, 20k.

R10, 120k.


R12, 50k. R14, R15, 275 ohms 2 watts. R18, R19, 50 ohms.

C1, 100 µµf. C2, 0.5 µf.

C3, C5, 8 µf. 450v. electro.

C4, 0.05 µf. C6, C7, 0.1 µf.

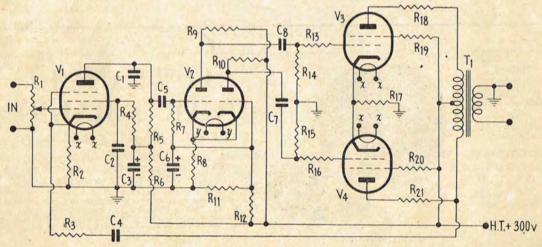C8, 4 µf. 500v. oil-filled. V1, 6J7 or EF37. V2, 6SN7. V3, V4, 807. T1, 9000 ohms to voice-coil.



COMPONENT LIST

R1, 1 meg. pot.

R2, 1600 ohms, R3, 250k, min. (see text). R4, R7, 250k. R5, R9, R13, R16, 100k.

R6, R11, 25k.

R8, 20k.

R10, 120k. (see text).

R12, 50k.

R14, R15, 500k. R17, 120 ohms 2 watts. R18, R19, R20, R21, 50 ohms

V1, 6J7 or EF37.

V2, 6SN7. T1, 4750 ohms to voice-coil. C8, 4 µf. 500v. oil-filled. V3, V4, 807.

C1, 100 µµf. C2, 0.5 µf.

C3, C5, 8 µf. 450v. electro.

C4, 0.05 µf.

C6, C7, 0.1 µf.


Block

Diagram of the

Amplifier.

A Very High-Quality 20-Watt Amplifier

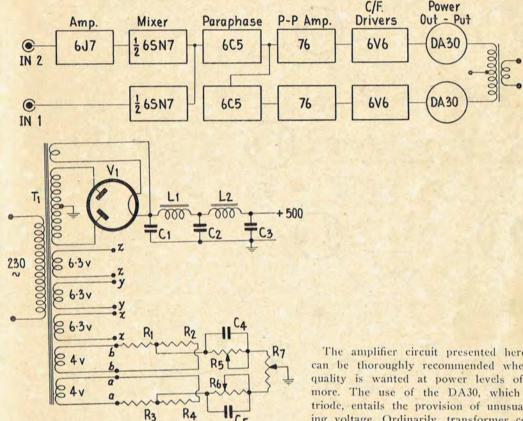FULLY DESCRIBED IN "RADIO AND ELECTRONICS," AUGUST, 1947




Circuit of the power supply. Note that C4 and C5, the bias bypass condensers, should have been returned to earth, and not to the ends of R7 in this diagram.

two DA308's. However, these are generally sold in matched pairs, so that separate adjustments are not always needed. Note also that separate heater windings are used for the 6V6's, so as to prevent having a high D.C. voltage between the heaters and cathodes of these valves.

It is suggested that the output transformer for this amplifier should be of the highest obtainable quality so that the best advantage can be taken of the excellence of he amplifier itself. Hum level in the amplifier is exceedingly low, and should meet the most stringent requirements.

The amplifier circuit presented here is one that can be thoroughly recommended where very good quality is wanted at power levels of 20 watts or more. The use of the DA30, which is a 30-watt triode, entails the provision of unusually high driving voltage. Ordinarily, transformer coupling would be needed to get the 134 volts peak signal that is needed for each side of the push-pull output stage, but here the difficulty is overcome by using a pair of 6V6's as cathode follower buffers between the DA30's and the last voltage amplifier. An ingenious use of the cathode follower enables a distortionless audio mixing circuit to be incorporated so that microphone and gramophone pick-up can be used simultaneously for special effects, such as are often needed in sound-recording. The amplifier does not use negative feedback, and probably represents the best possible in the way of resistance-coupled amplifiers of 20 watts output rating without such feedback.

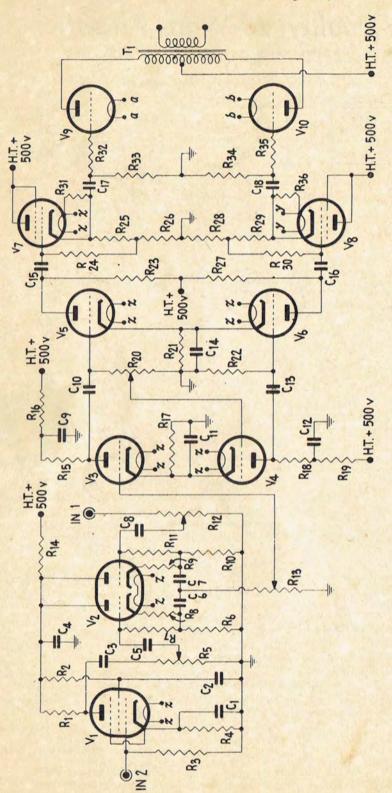On this page is a bock-diagram of the whole arrangement, together with a suitable power supply circuit. It will be noticed that arrangements have been made for separately adjusting the bias on the




COMPONENT LIST

righ-fidelity output transformer 9000 ohms to C17, C18, 0.5 µf. 600v. paper. 450v. electro. 0.05 μf. 600v. paper. 87, R11, R24, R30, R31, R36, 1 meg.

C14, 25 µf. 25v. electro.

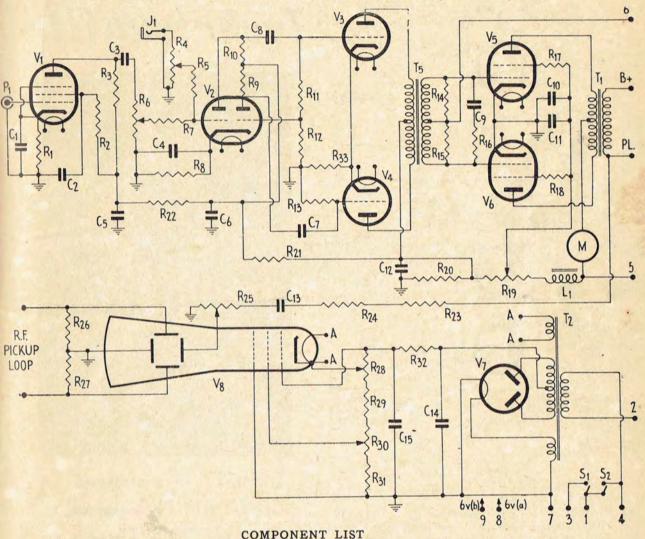A 50-Watt Amateur's Modulator Using P-P 807's FULLY DESCRIBED IN "RADIO AND ELECTRONICS," AUGUST, 1946



R1, R8, 1000 ohms. R2, R23, R24, R26, R27, 1 meg. R3, R11, R13, R34, R35, 250k. R4, R6, R25, 50k. pot. R5, R7, 500k.

R9, R10, R22, 100k.

R12, R14; R15, R21, 10k.

R16, 5k.

R17, R18, 100 ohms.

R19, 5k. 20w., adjustable. R20, 20k. 20w.

R28, 25k. w-w pot.

R29, R32, 20k.

R30, 50k., w-w pot.

R31, 150k.

R33, 500 ohms.

R33 (on power supply circuit), 1000 ohms w-w pot. C1, C4, 25 μ f. 25v. electro. C2, C3, C7, C8, C13, 0.01 μ f. 600v. C5 + C6, dual 10 μ f. 450v. electro.

C9, 0.005 μf.
C10, 0.01 μf. mica.
C11, C12, C18, C19, 8 μf. 450v. electro.
C14, C15, 0.5 μf. 600v.
C16, C17, 50 μf. 50v. electro.

T1, mod. transformer (see text).

T2, 385v.-a-side receiving transformer, with 4v. heater


winding, A-A. T3, main H.T. transformer, 690v.-a-side 400 ma.

T4, heater and bias transformer; windings as indicated.

T5, driver transformer.

50-Watt Modulator

(Continued from previous page.)

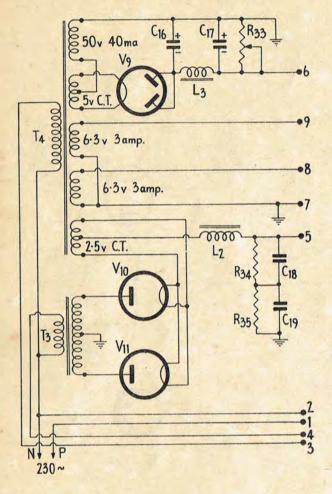

M, 0-250 ma. D.C. meter.

J1, open circuit jack.

P1, single conductor mike socket.

Note.—Microphone load resistor (not shown) should be connected between grid of V1 and earth; value dependent on mike used.

V1, 6SJ7.

V2, 6N7.

V3, V4, 6J5.

V5, V6, 807.

V7, V8, 5Y3-G.

V8, C.R. tube.

V10, V11, 866 or 866A.


L1, 30H. 100 ma. choke.

L2, 10-15H. 400 ma.

L3, 40 ma. vibrator choke.



Techniquality

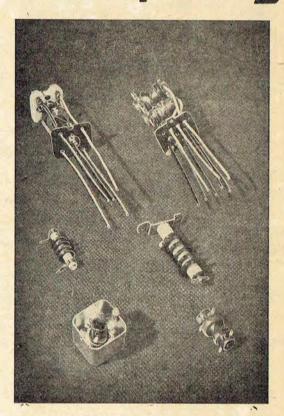

QUALITY
CONFORMITY
ADVANCEMENT

New Zealand's Best Radio Coils!!

Inductance Specialists

Now—you'll be wanting Parts

Mail us your list or let us quote— We can supply practically every component required for the many circuits illustrated in this "Circuit Digest".

- CALL FEAR'S FIRST -

Leading Distributors to the Trade, "Hams" and Experimenters throughout New Zealand


Get your copy of our illustrated 1949 Catalogue. It lists thousands of radio components.

FEAR'S Radio & Cycle Co., Ltd.


31 Willis Sreet, Wellington

Two Excellent Volume Expanders

No. 1.—FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JUNE, 1946

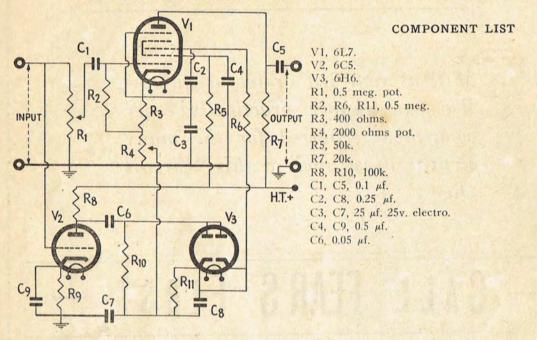

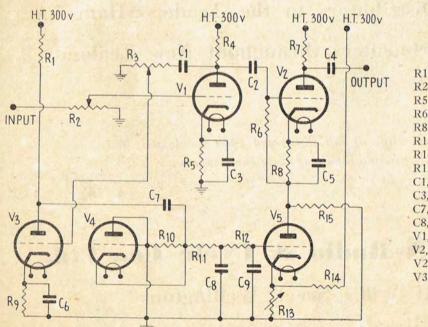No. 2.—FULLY DESCRIBED IN "RADIO AND ELECTRONICS," NOVEMBER, 1948



COMPONENT LIST

R1, R4, R7, R10, 100k. R2, R3, 1 meg. pot.

R5, 5k.

R6, R11, R12, 500k.

R8, R9, 2k.

R13, 2k. w-w pot.

R14, 50k. 2w.

R15, 125k.

C1, C2, C4, 0.05 µf.

C3, C5, C6, 25 µf. 25v. electro.

C7, 0.02 µf.

C8, C9, 0.1 µf.

V1, 6C5.


V2, V3, V4, V5, 6SN7.

V2 and V5, 6SN7

V3 and V4, 6SN7

A Cathode Follower Audio Mixer

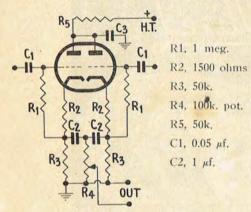FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, 1947




This circuit is capable of mixing two audio signals without introducing distortion in either of them; the output potentiometer, R4, can be used as an overall gain control, while individual controls can be placed in each channel to adjust the relative strengths of the two signals.

Additional R.C. Amplifier Stage for using a Gultar Pick-up with a Convential Amplifier


SEE "RADIO AND ELECTRONICS,"
NOVEMBER, 1948

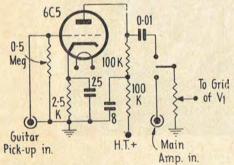
The circuit below is described as additional, because most of the amplifiers in this book have not quite enough voltage gain to work a guitar pick-up, and a simple low-gain stage like this can be added and will more than make up the deficiency. This circuit can also be used to make it possible to use a medium-level microphone.




Circuit of the additional stage for using when the guitar pick-up is in use. Note the de-coupling in the plate circuit and the switch for cutting the extra stage when a pick-up is being used with the main amplifier.

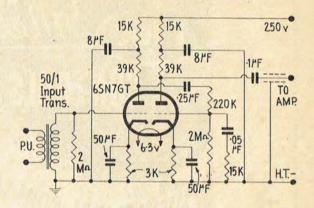A Pre-amplifier for Moving-coil Pick-ups SEE "RADIO AND ELECTRONICS," MARCH, 1947



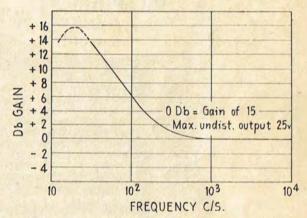

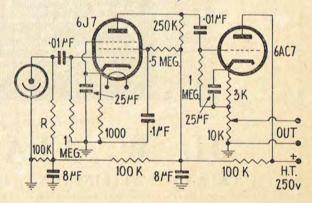Circuit for a Sound-head Pre-amplifier SEE "RADIO AND ELECTRONICS," SEPTEMBER, 1946





New Zealand Distributors:

H. W. CLARKE LTD.


AUCKLAND

WELLINGTON

CHRISTCHURCH

DUNEDIN

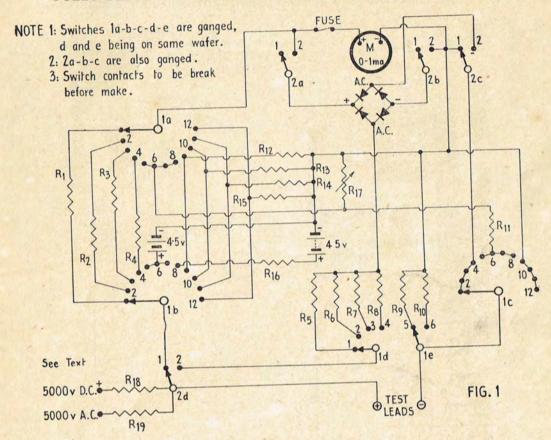An ACIDC 24 Range Multi-meter FULLY DESCRIBED IN "RADIO AND ELECTRONICS," AUGUST, 1946



COMPONENT LIST

S2a-S2c, A.C./D.C. switch.

R1 10k


SWITCH POSITIONS

	SI			
Position	Range			
1 .	10v.			
2	100v.			
3	500v.			
4	1000v.			
5	$R \div 100.$			
6	R ÷ 10.			
7	$R \times 1$.			
-8	$R \times 10$.			
9	1 amp.			
10	500 ma.			
11	100 ma.			
12	10 ma.			
	S2			
Position	Range			
1	D.C. volts-maohms			
2	A.C. volts.			

A Bridge-type Capacity Analyser

FULLY DESCRIBED IN "RADIO AND ELECTRONICS," SEPTEMBER, 1946

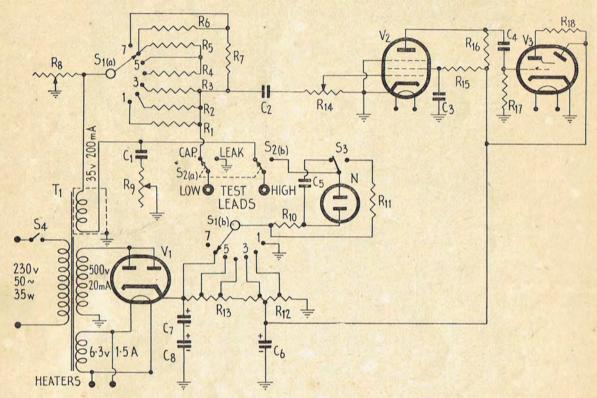This capacity analyser measures capacity, with a bridge circuit, and also tests for power factor and leakage. A neon lamp is used in the latter function, and indicates the goodness of the dielectric by the rate of flashing. Full details are given in the original article, to which intending builders are referred.




COMPONENT LIST

C6, C8, 8 µf. 450v. electro.

R7, 0.9965 ohms. T1, power transformer (windings as indicated). V1, 6X5. V2, 6J7. V3, 6E5. N, 4-watt neon lamp. R8, 10k. w-w pot. R9, 15k. w-w pot. R10, 120k. R11, 30k. S1(a) and S1(b), range switch. R12, R13, 25k. voltage divider, two taps. R14, 1 meg. pot. S2(a) and S2(b), leakage/capacity switch. R15, 2 megs. R16, R17, 500k. S3, paper or mica/electrolytic switch. S4, on/off switch on R14. R1, R18, 1 meg. R2, 100k. C1, 0.099 µf. C2, C4, 0.01 µf. R3, 10k. C3, 0.25 µf. R4, 900 ohms. C5, 0.5 µf. R5, 90 ohms. R6, 9 ohms.

The Radel Service Oscillator

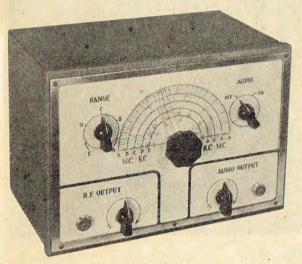
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," JULY, 1947



COMPONENT LIST

R1, R12, R13, R18, 25k. R2, 500 ohms. R3, 10k. R8, R9, 50k R10, R17, 15k R11, 250 ohms. R4, 100k. R14, 50 ohms. R5, R15, 1000 ohms. R19, 10k. 25w. w-w. R6, 500k. L1 to L10, see text. R7, R16, 5k. SW1, 2-bank 11-position wafer switch (see text).
C1, 350 μμf. max. variable.
C2, C3, 50 μμf. mica.
C4, C7, C10, 0.01 μf. paper.

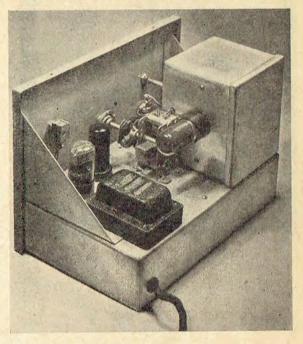C5, 25 μμf. mica. C6, 100 μμf. mica. C8, C9, 0.004 μf. mica.





C11, 8 µf. 450v. electro. C12, 40 µf. 450v. electro.


C13, 0.1 µf. paper.

T1, 250-0-250v., 6.3v. power transformer. V1, 6V6-GT (screen tied to plate). V2, 6J7. V3, 6N7.


V4, 6X5-GT.

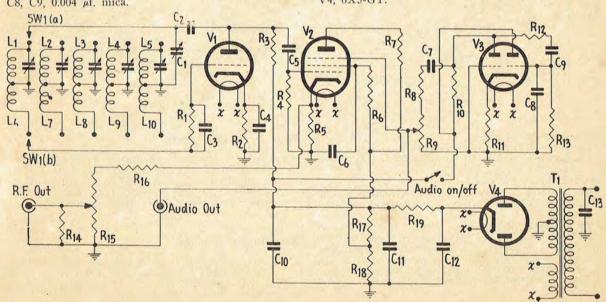


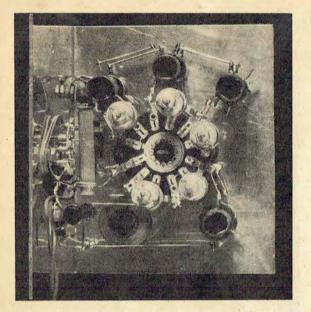

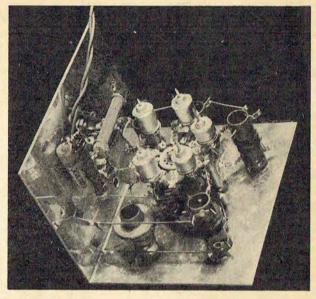

Figs. 1 and 2: The coil unit.

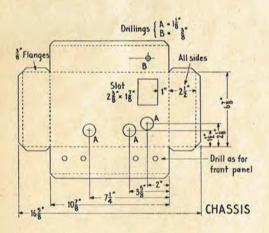

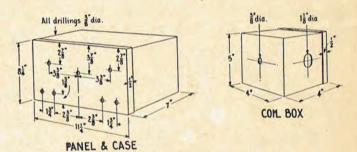

Working drawings of metal-work required for the oscillator.

Band A 11-30 mc/sec.

L1, 5 turns 24 S.W.G. enamelled, double spaced. L6, 3 turns 30 S.W.G. D.S.C. interwound at earthy end of L1.

Band B 4.3-11 mc/sec.:

L2, 22 turns 24 S.W.G. enamelled, double spaced. L7, 10 turns 30 S.W.G. D.S.C., interwound at earthy end of L2.

Band C 1.7-4.3 mc/sec.

L3 and L8, standard broadcast oscillator coil designed for 420 µµf, gang and 6K8 tube. Tickler used as L8, unaltered. Grid winding used as L3, with turns removed until, with all tuning capacity in circuit, frequency of oscillation is 1.7 mc/sec.

Band D 665-1700 kc/sec.

L4 and L9, standard broadcast R,F. coil. Secondary, unaltered, used as L4. Primary used as L9, but modified by sliding along former till as close as possible to the primary. Turns are then removed until the winding depth is one-third that of L9.


Band E 280-670 kc/sec .:

L5, single winding from 465 kc/sec. I.F. bobbin, designed for 140 μμf. tuning capacity.
 L10, 130 turns of 34 S.W.G. enamelled wire,


jumble-wound as close as possible to L5.

A Frequency-modulated Test Oscillator for use with an Oscillosope

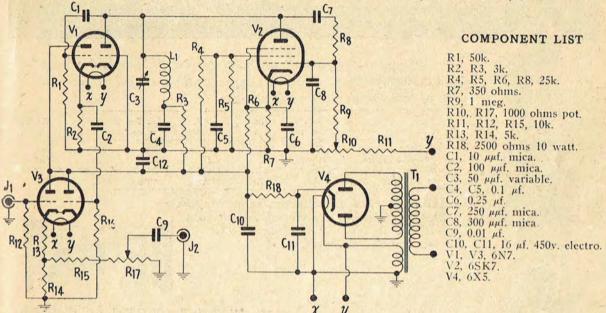FULLY DESCRIBED IN "RADIO AND ELECTRONICS," FEBRUARY, 1948



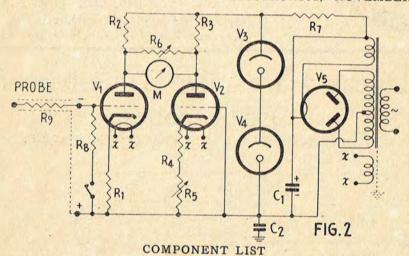Vacuum-tube Voltmeter For D.C. Measurements FULLY DESCRIBED IN "RADIO AND ELECTRONICS," NOVEMBER, 1946



- R1, 500 ohms. R2, R3, 50k.
- R4, 250 ohms.
- R5, 500 ohms w-w pot.
- R6, 200 ohms w-w pot.

- R7, 4500 ohms 5w. w-w. R8, 200k. (for 0-50v. range). R9, 5 megs.

- C1, 16 µf. 450v. electro.
- C2, 1 µf. 600v.
- V1, V2, 6AC7/1852, screen and suppressor tied to
- V3, VR105/30. V4, VR150/30.
- M, 0-1 ma, moving-coil meter.
- Power transformer, 300-0-300v. 40 ma.

VALVE TYPES HAVE BEEN ADDED AND WE JON SUPPLY

The Brimar valve factory at Standard Telephones and Cables Ltd., London, have added new types to their range. Here is a list of some of the types available now.

	R.F. Tubes	Mixer Tubes	I.F. Tubes	2nd De- tector	Output Tubes	Rectifier Tubes
1.4-volt Battery Types	1T4	1R5	1T4	1U5	3V4	_
6.3-volt Loctal Types	7H7	787	7H7	7K7	7C5	7Z4
6.3-volt Octal Types	6K7GT	6K8GT	6K7GT	6B8GT	6V6GT	5Y3GT
6.3-volt All Glass Types	6BA6	6BE6	6BA6	6AT6	_	6X4

Additional types in the above ranges together with other British Brimar made American replacement types, including 12-volt loctals are also available.



For any information concerning British Brimar Valves, write without obligation to:


STANDARD TELEPHONES & CABLES

Pty. Ltd. (Inc. N.S.W.)

VET US HELP YOU WITH YOUR PROBLEM Wellington, Box 638-Christchurch, Box 983, Wanganui, Box 293-Auckland, Box 91W

A Linear Hard-valve Time-base for Oscilloscopes

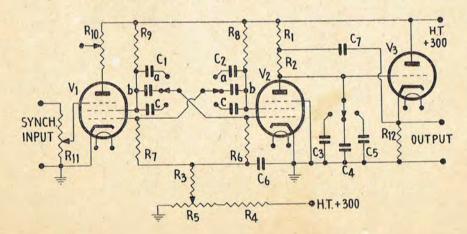FULLY DESCRIBED IN "RADIO AND ELECTRONICS," APRIL, 1948



R1, R2, R3, 50k. R4, R8, R9, 25k.

R5, 100k. pot.

R6, 1 meg. R7, R12, 100k.

R10, 50k. pot.

R11, 500k. pot.

Cla, C2a, 0.01 µf.

C1b, C2b, 0.001 µf. C1c, C2c, 0.0001 µf.

C3, 0.5 µf.

C4, 0.05 µf.


C5. 0.005 µf.

C6, C7, 1 µf.

V1, V2, V3, 6AC7/1852

Service Oscillope



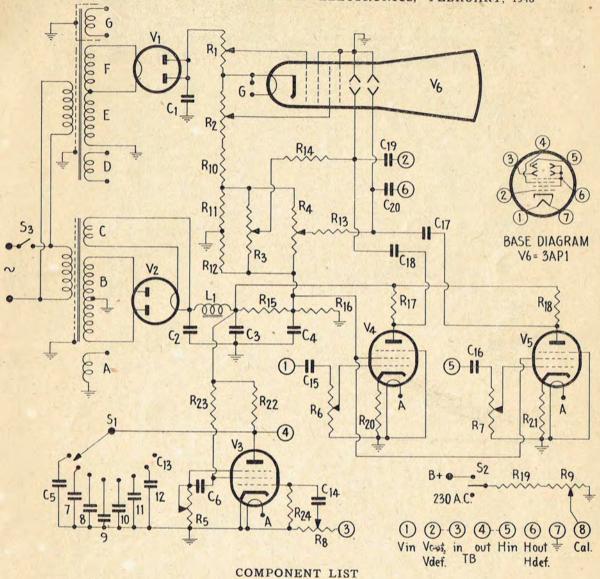

- C1, 1 \(\mu f. \) 1000v. C2, C3, C4, 8 \(\mu f. \) 450v. electro in parallel with 0.5 µf. paper.

- parallel with 0.5 μt, pap C5, C6, 1 μf. 600v. C7, 0.25 μf. 600v. C8, C19, C20, 0.05 μf. 600v. C9, 0.01 μf. 600v. C10, 0.002 μf. 600v. C11, 0.0005 μf. mica. C12, 0.0001 μf. mica. C13 stray capacities

- C13, stray capacities. C14, C15, C16, C17, 0.1 \(\mu \text{f}\), 600v
- C18, 0.004 µf. mica. V1, V2, 80.


- V3, V4, V5, 6AC7/1852. V6, 3AP1 or 906, R1, 50k, pot. R2, 0.25 meg. pot. R3, R4, R5, 2 meg. pot. R6, R7, R8, 0.5 meg. pot.
- R9, 1 meg. pot.


- R10, 250k, ½w, R11, R12, 100k, ½w, R13, R14, 2 meg, ½w, R15, R16, R19, 20k, 2w, R17, R18, 15k, 2w, R20, R21, 150 ohms 1w.
- R22, 150k. 1w.

- R23, 100k. 1w.
- R24, 50k. 1w.
- S1, single-pole 11 position.

- S2, S.P.D.T. S3, S.P.S.T. L1, 50ma, smoothing choke.
- Transformer windings.
- A, 6.3v. 2 amp.
- B, 300-0-300v. 60 ma.
- C, 5v. 2 amp.
- D, 6.3v. 1 amp. E, 750v. 5 ma. F, 5v. 2 amp.
- G, 2.5v. 2.5 amp. (not used).

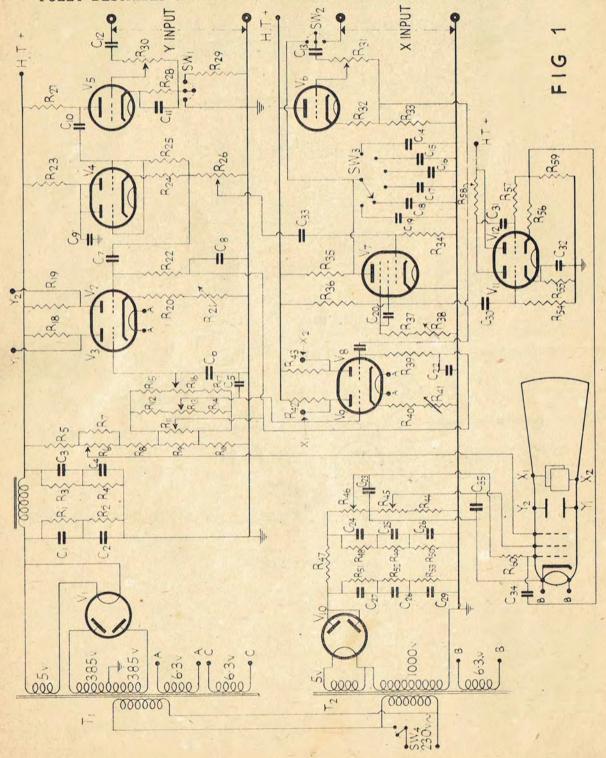5" Service Oscilloscope ED IN "RADIO AND ELECTRONICS," MAY, JUNE, JULY, 1946



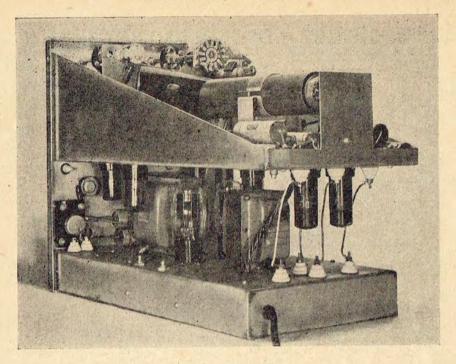

COMPONENT LIST

C1 to C4, 16 µf. electrolytic.

C5, C6, C14, C20, C23, C24 to C29, 1 µf. 600v. paper.

C9, 8 µf. electrolytic.

C11, C32, 50 µf. 50v. electrolytic.

C15, 0.25 µf. 600v.

C16, 0.05 µf. 600v.

C17, C33, 0.01 µf. 600v.

C13, C30, C31, 0.1 µf. 600v.

C18, 0.002 µf. mica.

C19, 0.0005 µf. mica.

C34, 0.25 µf. 1200v. (see text).

R1 to R4, R22, R25, R39, R44, R54, R57, R60, 1 meg.

R5, R8, 10k.

R9, R10, R12, R15, 25k.

R14, R17, R34, R37, R55, R58, R59, 50k.

R18 to R20, R27, R29, R33, R36, R40, R42, R43, R47, 100k.

R23, 75k.

R24, R28, R32, 5k.

R35, 150k. 2w.

R48 to R53, 5 meg.

R56, 600 ohms.

V1, V10, 80.

V2 + V3 V4, V8 + V9, 6N7.

V5, V6, 6J5.

V7, 6AC7/1852.

V11 + V12, 6SN7.

POTENTIOMETERS

R6, R11, 0.5 meg.

R13, R16, 50k.

R21, R26, R41, 25k.

R30, R31, R38, 2 meg.

R45, 1 meg.

R46, 1 meg. pot. with 100k. fixed, in parallel.

T1, power transformer, 385v.-a-side.

T2, high voltage transformer.

SW1, Y gain switch.


SW2, X input switch.

SW3, coarse freq. selector.

SW4, on/off switch.

A Sensitive Absorbtion Wavemeter

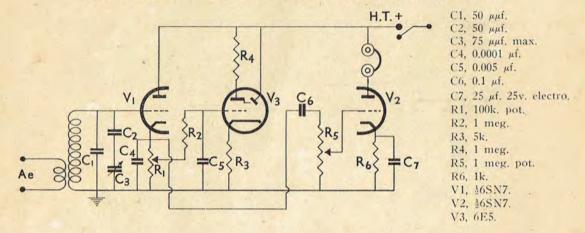
FULLY DESCRIBED IN "RADIO AND ELECTRONICS," APRIL, 1946



This little unit can be used as a wave-meter, phone monitor, and carrier-shift over-modulation indicator.

Note that the magic eye works backwards. That is, increased signal opens the eye instead of closing it. The control in the magic-eye grid circuit alters the

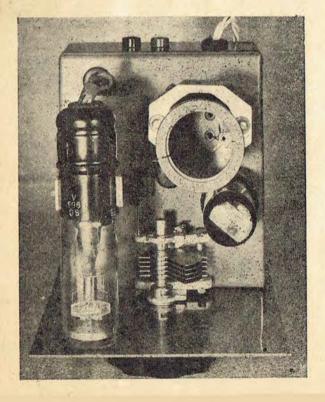sensitivity by enabling the shadow to be set at any convenient closure without signal applied. The condenser values enable 100 per cent, bandspread to be had on the 80m. band, but, as with other wavemeters, any convenient tuning condenser can be used with a range of plug-in coils to suit all bands.



MODERNISE YOUR EQUIPMENT WITH "S-M" ETCHED BRASS TITLE PLATES







MODERN DESIGN FULL RANGE OF TITLES MODEST COST

Give your equipment that professional look Available from leading dealers and distributors everywhere, or direct from Master Agents:

S. D. MANDENO & CO. LTD.


114-121 CHANGERY CHAMBERS, AUGKLAND, C.1

PHONE

44-265

A 5" Oscilloscope Employing Unit Construction

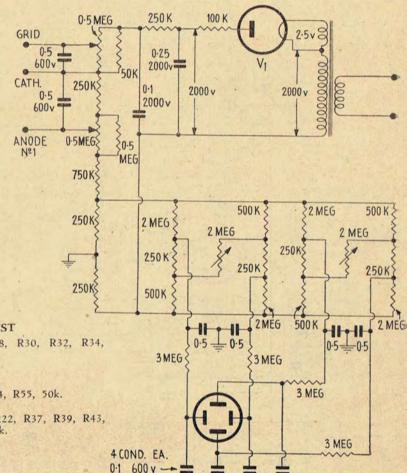FULLY DESCRIBED IN "RADIO AND ELECTRONICS," NOVEMBER, DECEMBER, 1948, and JANUARY, 1949



COMPONENT LIST

R1, R3, R5, R7, R14, R15, R28, R30, R32, R34, R36, R40, 2 meg.

R2, R6, R29, R33, 200k.

R4, R8, R23, R31, R35, R46, 20k.

R9, R10, R41, R42, R50, R53, R54, R55, 50k.

R11, R38, 500k, pot.

R12, R13, R17, R18, R19, R20, R22, R37, R39, R43, R44, R45, R48, R59, 100k.

R16, R51, R52, R58, 25k.

R21, R47, 1000 ohms.

R24, R25, R26, R27, 250k.

R49, 2 meg. pot.

R56, 1 meg.

R57, 100k. pot.

C1, C2, C11, C14, C30, C35, 0.1 \(\mu f. \) 600v.

C3, C6, C15, C34, 8 µf. 450v. electro.

C4, C5, C12, C13, 0.5 µf. 600v.

C7, C8, C9, C10, 16 µf. 450v. electro.

C16, C20, C25, 0.02 µf. 600v.

C17, C22, 100 µµf.

C18, C23, 500 µµf.

C19, C24, 0.003 µf.

C21, 0.05 \mu f.

C26, 0.25 µf.

C27, C28, C33, 1 µf. 600v.

C29, 0.5 µf.

C31, 0.03 µf. 600v.

C32, 0.005 µf. 600v.

V1, V4, 6SN7.

V2, V5, 6N7.

V3, 80.

V6, V7, 6AC7 or 6SJ7.


V8, 6AC7.

T1, power transformer; heater windings as indicated; H.V. winding 385v.-a-side, 80 ma.

L1, L2, smoothing chokes, 50 ma.

SW1, SW2, each two two-pole, three position wafers actuated from the same shaft.

SW3, three-pole, five positions.

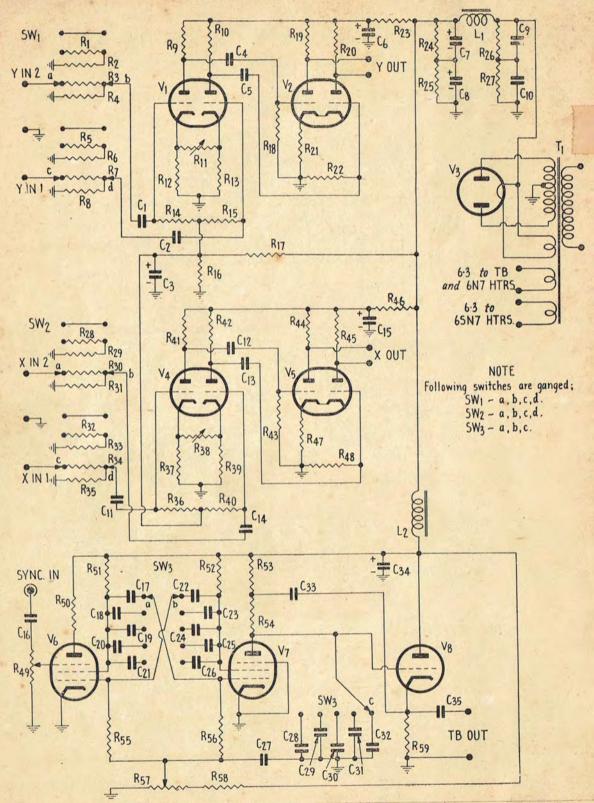

Printed by Harry H. Tombs Ltd., Wellington,

REQUIREMENTS

Be Purchased From Us

STOCKISTS OF

Batteries and Battery Plugs
Condensers — Electrolytic, Paper,
Tubular, Mica
Coils, Coil Kits, etc., Inductance
Specialists'
Dials and Dial Movements
Knobs
Resistances and Volume Controls

Screws and Radio Hardware
Selenium Rectifiers
Speakers, Celestion, Rola and Philips
Switches, Spaghetti
Transformers, Power and I.F.
Valves and Dial Lamps
Valve Sockets and Dial Lamp Holders
Wires—all types

PEERLESS ELECTRIC WATER HEATERS
IRON AND TOASTER ELEMENTS



MEGANN LIMITED

60 VICTORIA STREET WELLINGTON
C.P.O. Box 12 Phone 45-863 Telegrams "PIALBA"



Address your inquiry for new Price List to Sales Dept. WESTONHOUSE RADIO LTD.

Manufacturers of Radio and Electronic Equipment, General Metal Works Specialists
in Fluorescent Lighting Equipment.

Phones: 42-577, 49-012. Box 8, Wellesley St., Auckland. Telegrams: WESTRAD.