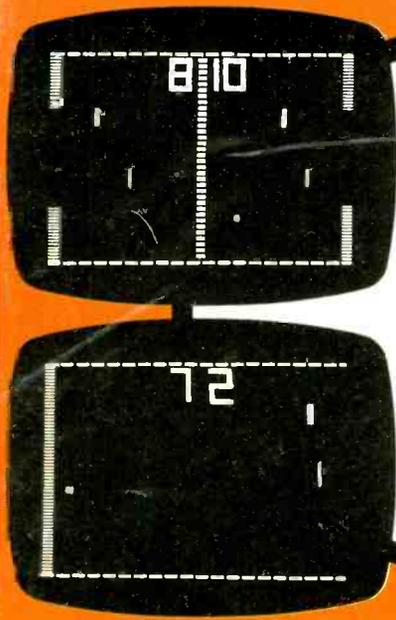


# electronics today international

MAY 1977

35p



## 4 IN 1 TV GAMES UNIT


FULL CONSTRUCTIONAL DETAILS OF THIS  
EASY-TO-BUILD PROJECT FEATURING:

- ◆ Full sound effects ◆ On screen scoring ◆ Variable angle
- ◆ Two bat sizes ◆ Ball speed control ◆ 'Rifle' option
- ★ Special offer on IC.

**PROJECTS: HI-FI SPEAKERS  
SYSTEM 68 - THE PSU  
METRONOME  
INJECTOR TRACER**

**ALSO: THE VALVES  
THAT WON THE WAR  
I<sup>2</sup>L EXPLAINED  
ELECTRONICS: 2000 A.D.**

**£15.95  
INC.**

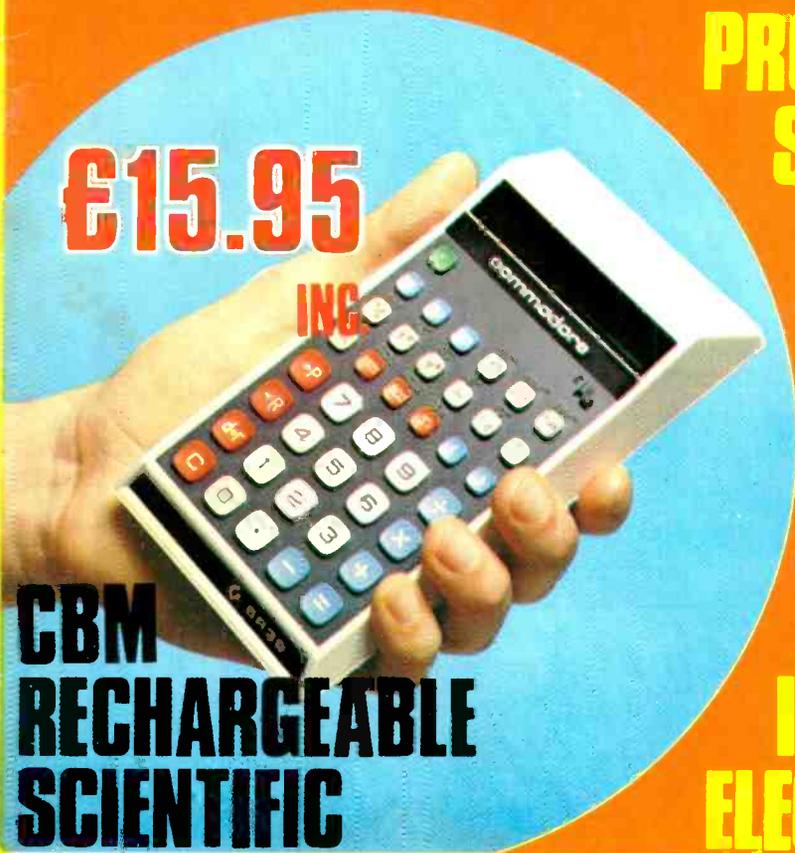

**CBM  
RECHARGEABLE  
SCIENTIFIC**



# electronics today

international

MAY 1977

vol. 6 No 5

## Features

I <sup>2</sup> L EXPLAINED <i>All you ever wanted to know about this new technique</i>	19
ELECTRONICS 2000 AD — PART 3 <i>A look at communications of the future</i>	25
THE VALVES THAT WON THE WAR <i>Magnetrons (title applicable only if you supported the Allies)</i>	41
COMPONENTS — PART 10 <i>Cermet and other less common types are covered</i>	60
TIP OF THE MONTH! <i>How to save the cost of this magazine!</i>	53
ELECTRONICS — IT'S EASY — PART 39 <i>Coupling electronics stages</i>	64
TECH-TIPS <i>Three pages crammed with circuits</i>	73

## Projects

TV GAMES UNIT <i>Four games using one main chip to plug into your TV</i>	12
ERII SPEAKERS <i>Hi-Fi speaker enclosures for the handyman</i>	31
SHORT CIRCUITS: INJECTOR/TRACER	37
METRONOME	39
SYSTEM 68 — POWER SUPPLY <i>Getting powered up for your home MPU</i>	55

## Data Sheet

LM1812 <i>An ultrasonic transceiver chip from National</i>	48
TDA1022 <i>A C.C.D. delay line from Mullard</i>	49

## News

NEWS DIGEST	6
ELECTRONICS TOMORROW	69

## Information

ETI TOP PROJECTS 1 & 2	10
SPECIAL PUBLICATIONS FROM ETI	36
TOWERS TRANSISTOR BOOK	46
ETI BOOK SERVICE	47
A LOOK AT ETI JUNE ISSUE	52
TRANSDUCERS IN MEASUREMENT AND CONTROL	67
ETI DIGITAL CLOCK	72
BINDERS	82
READERS SERVICES	82

## Special offer

CBM RECHARGEABLE SCIENTIFIC CALCULATOR <i>A beautiful machine for only £15.95</i>	51
--	----

## EDITORIAL AND ADVERTISEMENT OFFICES

25-27 Oxford Street  
London W1R 1RF  
Telephone 01-434 1781/2  
Telex 8811896

**HALVOR W. MOORSHEAD**  
Editor

**RON HARRIS B.Sc**  
Assistant Editor

**JIM PERRY**  
Specials Editor

**TONY ALSTON**  
Project Development

**JULIAN ZINOVIEFF**  
Production

**MAREE BREEN**  
Technical Drawing

**SANDRA ZAMMIT-MARMARA**  
Subscriptions

**MARGARET HEWITT**  
Administration

**DAVID LAKE (Manager)**  
**BRENDA GOODWIN**  
**KIM HAMBLIN**  
Reader Services

For Advertising Enquiries ring  
**MARK STRATHERN**  
on 434 1781/2

## INTERNATIONAL EDITIONS

AUSTRALIA: Collyn Rivers  
Publisher  
Steve Braidwood  
Assistant Editor

HOLLAND: Anton Kriegsman  
Editor-in-chief

CANADA: Mike Kenward  
Editor

FRANCE: Denis Jacob  
Editor-in-chief

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

PUBLISHED BY  
Modmags Ltd.  
25-27 Oxford Street, W1R 1RF



DISTRIBUTED BY  
Argus Distribution Ltd (British Isles)  
Gordon & Gotch Ltd. (overseas)

PRINTED BY  
QB Newspapers Limited, Colchester.

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur, a correction will be published as soon as possible afterwards in the magazine.

# SEMICONDUCTORS - COMPONENTS

## TRIACS

2 Amp			10 Amp		
No.	TO5 Case	Price	No.	TO48 Case	Price
100	TR12A/100	£0.31	100	TR110A/100	£0.77
200	TR12A/200	£0.51	200	TR110A/200	£0.92
400	TR12A/400	£0.71	400	TR110A/400	£1.12

6 Amp			10 Amp		
No.	TO66 Case	Price	No.	TO220 Case	Price
100	TR16A/100	£0.51	400	TR110A 400P	£1.12
200	TR16A/200	£0.61			
400	TR16A/400	£0.77			

## DIACS

BR100 £0.23 D32 £0.23

## CARBON POTENTIOMETERS

SINGLE GANG with wire end terminations. 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer and nut. Tolerance  $\pm 20\%$  of resistance.

### LINEAR TRACK

Value	No.	Price
1K	1831	£0.22
2K	1832	£0.22
4K7	1833	£0.22
10K	1834	£0.22
22K	1835	£0.22
47K	1836	£0.22
100K	1837	£0.22
220K	1838	£0.22
470K	1839	£0.22
1M	1840	£0.22
2M2	1841	£0.22

### LOG TRACK

Value	No.	Price
4K7	1842	£0.22
10K	1843	£0.22
22K	1844	£0.22
47K	1845	£0.22
100K	1846	£0.22
220K	1847	£0.22
470K	1848	£0.22
1M	1849	£0.22
2M2	1850	£0.22

DUAL GANG. These high quality pots are fitted with wire end terminations. 6mm x 50mm plastic shaft 10mm bushes supplied with shakeproof washer and nut. Track tolerance  $\pm 20\%$  but matched to within 2dB of each other.

### LINEAR TRACK

Value	No.	Price
4K7	1851	£0.68
10K	1852	£0.68
22K	1853	£0.68
47K	1854	£0.68
100K	1855	£0.68
220K	1856	£0.68
470K	1857	£0.68
1M	1858	£0.68
2M2	1859	£0.68

### LOG TRACK

Value	No.	Price
4K7	1860	£0.68
10K	1861	£0.68
22K	1862	£0.68
47K	1863	£0.68
100K	1864	£0.68
220K	1865	£0.68
470K	1866	£0.68
1M	1867	£0.68
2M2	1868	£0.68

SINGLE GANG SWITCHED. Fitted with double pole on-off switches. The switch action is incorporated within the rotary action of the pot. Switch rating 1.5 amps at 250V AC.

### LINEAR TRACK

Value	No.	Price
4K7	1870	£0.48
10K	1871	£0.48
22K	1872	£0.48
47K	1873	£0.48
100K	1874	£0.48
220K	1875	£0.48
470K	1876	£0.48
1M	1877	£0.48
2M2	1878	£0.48

### LOG TRACK

Value	No.	Price
4K7	1879	£0.48
10K	1880	£0.48
22K	1881	£0.48
47K	1882	£0.48
100K	1883	£0.48
220K	1884	£0.48
470K	1885	£0.48
1M	1886	£0.48
2M2	1887	£0.48

## SUPER UNTESTED PAKS

PAK No.	Description	Order No.	Price
U50	100 Germ. Gold bonded OA47 diode	16130	£0.60
U51	150 Germ. OA70/81 diode	16131	£0.60
U52	100 Silicon Diodes 200mA OA200	16132	£0.60
U53	150 diodes 75mA 1N4148	16133	£0.60
U54	50 Sil Rect Top Hat 750mA	16134	£0.60
U55	20 Sil Rect Stud Type 3 Amp	16135	£0.60
U56	50 400mW Zeners DO7 Case	16136	£0.60
U57	30 NPN Trans BC107/8 Plastic	16137	£0.60
U58	30 PNP Trans BC177/178 Plastic	16138	£0.60
U59	25 NPN TO39 2N697/2N1711 sil	16139	£0.60
U60	25 PNP TO59 2N2905 silicon	16140	£0.60
U61	30 NPN TO18 2N706 silicon	16141	£0.60
U62	25 NPN BFY50 51	16142	£0.60
U63	30 NPN Plastic 2N3906 silicon	16143	£0.60
U64	30 PNP Plastic 2N3905 silicon	16144	£0.60
U65	30 Germ. 0071 PNP	16145	£0.60
U66	15 Plastic Power 2N3055 NPN	16146	£1.20
U67	10 TO3 Metal 2N3055 NPN	16147	£1.20
U68	20 Unijunction trans 1N543	16148	£0.60
U69	10 1 amp SCR TO39	16149	£1.20
U70	8.3 amp SCR TO66 case	16150	£1.20

Code No.s mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

## COMPONENT PACKS

Pack No.	Qty.	Description	Order No.	Price
C1	200	Resistor mixed value approx. (Count by weight)	16164	£0.60
C2	150	Capacitors mixed value approx. (Count by weight)	16165	£0.60
C3	50	Precision resistors Mixed values	16166	£0.60
C4	80	1/4W Resistors mixed preferred values	16167	£0.60
C5	5	Pieces assorted ferrite discs	16168	£0.60
C6	2	Tuning gangs MW 1W VHF	16169	£0.60
C7	1	Pack wire 50 metres assorted colours single strand	16170	£0.60
C8	10	Reed switches	16171	£0.60
C9	3	Micro switches	16172	£0.60
C10	15	Assorted pots	16173	£0.60
C11	5	Metal jack sockets 3 x 3.5mm 2 x standard switch types	16174	£0.60
C12	30	Paper condensers preferred types mixed values	16175	£0.60
C13	20	Electrolytics trans types	16176	£0.60
C14	1	Pack assorted hardware - Nuts, bolts, grommets etc.	16177	£0.60
C15	5	Mains slide switches ass.	16178	£0.60
C16	20	Assorted tag strips and panels	16179	£0.60
C17	15	Assorted control knobs	16180	£0.60
C18	4	Rotary wave change switches	16181	£0.60
C19	2	Relays 6 - 24V operating	16182	£0.60
C20	1	Pak copper laminate approx. 200 sq ins.	16183	£0.60
C21	15	Assorted fuses 100mA-5 amp	16184	£0.60
C22	50	Metres PVC sleeving assorted size and colour	16185	£0.60
C23	60	1/2 watt resistors mixed preferred values	16188	£0.60
C24	25	Presets assorted type and value	16189	£0.60
C25	30	Metres stranded wire assorted colours	16187	£0.60

## SLIDER PAKS

Pack No.	Qty.	Description	Order No.	Price
S1	6	Slider potentiometers mixed values	16190	£0.60
S2	6	Slider potentiometers all 470 ohms	16191	£0.60
S3	6	Slider potentiometers all 10k in	16192	£0.60
S4	6	Slider potentiometers all 22k in	16193	£0.60
S5	6	Slider potentiometers all 47k in	16194	£0.60
S6	6	Slider potentiometers all 47k log	16195	£0.60

## CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors Unrepeatable value

MC1	24	miniature ceramic capacitors 3 of each value - 22pf 27pf 33pf 39pf 47pf 68pf 82pf	16160	£0.60
MC2	24	miniature ceramic capacitors 3 of each value - 100pf 120pf 150pf 180pf 220pf 330pf & 390pf 270pf	16161	£0.60
MC3	24	miniature ceramic capacitors 3 of each value - 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf & 3300pf	16162	£0.60
MC4	24	miniature ceramic capacitors 3 of each value - 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf & 3300pf	16163	£0.60

## ORDERING

Please word your orders exactly as printed not forgetting to include our part number

## V.A.T.

Add 12 1/2% to prices marked \* Add 8 1/2% to others excepting those marked † these are zero

## VEROBOARDS

### DRILLED COPPER P.C.B.

1 Pitch			15 Pitch		
Size	No.	Price	Size	No.	Price
2.5 x 5	2201	£0.46	2.5 x 17	2209	£1.13
2.5 x 3.75	2202	£0.39	2.5 x 5	2210	£0.42
2.5 x 17	2203	£1.42	2.5 x 3.75	2211	£0.31
3.75 x 5	2204	£0.52	3.75 x 17	2212	£1.51
3.75 x 3.75	2205	£0.46	3.75 x 5	2213	£0.57
3.75 x 17	2206	£1.82	3.75 x 3.75	2214	£0.42
4.75 x 17.9	2207	£2.34	2.5 x 1	2216	£0.52
2.5 x 1	(pack of five)	2208			

### DRILLED PLAIN P.C.B.

1 Pitch			15 Pitch		
Size	No.	Price	Size	No.	Price
3.75 x 17	2218	£1.18	2.5 x 17	2221	£0.78
3.75 x 2.5	2219	£0.26	3.75 x 5	2222	£1.00
5 x 3.75	2219	£0.42	2.5 x 5	2223	£0.26
			2.5 x 3.75	2224	£0.21
			5 x 3.75	2225	£0.36

### VERO SPOT-FACE CUTTER

Coax No. 2231 Price £0.68

## PLUGS AND SOCKETS

PLUGS			CHASSIS SOCKETS				
No.	Price		No.	Price			
P1	DIN CSP 2 pin speaker	1689	£0.08	C51	DIN 3.5 pin loudspeaker	1652	£0.08
P2	DIN 3-pin	1690	£0.12	C52	DIN 3-pin	1653	£0.10
P3	DIN 4-pin	1691	£0.16	C53	DIN 5-pin	1654	£0.10
P4	DIN 5-pin 180	1692	£0.14	C54	DIN 5-pin 240	1655	£0.12
P5	DIN 5-pin 240	1693	£0.15	C55	Jack 3mm	1656	£0.06
P6	DIN 6-pin	1694	£0.20	C56	Jack 4.5mm	1657	£0.06
P7	DIN 7-pin	1695	£0.20	C57	Jack Mono switched	1658	£0.15
P8	Jack 2.5mm screened	1696	£0.12	C58	Jack Stereo switched	1659	£0.18
P9	Jack Plug 3.5mm plastic	1697	£0.10	C59	Phono single	1660	£0.08
P10	Jack Plug 3.5mm screened	1698	£0.15	C60	Phono double	1661	£0.10
P11	Jack Plug mono plastic	1699	£0.28	C61	Coax surface	1662	£0.21
P12	Jack Plug mono screened	1700	£0.28	C62	Coax flush	1663	£0.25
P13	Jack Plug stereo screened	1701	£0.32	C63	Jack switched Mono	1664	£0.20
P14	Phono	16102	£0.10	C64	Jack socket DPDT switch	1665	£0.32
P15	Car aerial	16103	£0.16	C65	Car aerial	1666	£0.10
P16	Coax free TV	16104	£0.16	C66	AC mains US type	1667	£0.16
P17	Right angle jack	16105	£0.12	C67	Phono 4-way	1668	£0.16
P18	Jack 2.5mm plastic	16106	£0.12	C68	D.C. power	1669	£0.18
P19	Jack stereo plastic	16107	£0.20	C69	AC switched	1670	£0.32
P20	Phono free screened	16108	£0.14	C70	Phono 8-way	1671	£0.32
P21	D.C. 2.1 plug	16109	£0.12				
P22	D.C. 2.5mm plug	16110	£0.12				
P23	2-pin AC plug U.S. type	16111	£0.18				
P24	AM aerial	16112	£0.13				
P25	Cassette mains plug	16113	£0.15				
P26	FM 300 ohms plug	16114	£0.13				

### INLINE SOCKETS

No.	Price		
IS1	DIN 3 pin speaker	1672	£0.10
IS2	DIN 3 pin	1673	£0.18
IS3	DIN 4 pin	1674	£0.17
IS4	DIN 5 pin	1675	£0.18
IS5	Jack 3mm	1676	£0.08
IS6	Jack 4.5mm	1677	£0.08
IS7	Jack mono plastic	1678	£0.14
IS8	Jack mono Chrome	1679	£0.28
IS9	Jack stereo plastic	1680	£0.20
IS10	Jack stereo Chrome	1681	£0.42
IS11	Phono screened	1682	£0.12
IS12	Car aerial	1683	£0.22
IS13	Coax television	1684	£0.40
IS14	Coax back pack	1685	£0.1
IS15	2-pin AC connector U.S.	1686	£0.21
IS17	Phono plastic	1687	£0.12
IS18	Back to back phono	1688	£0.24

Just a selection from our huge stocks!  
**SEE OUR 1977 CATALOGUE**  
 126 pages packed with valuable information  
**ORDER NOW ONLY 50p**  
 plus 15p p&p

## LINEAR PAKS

Manufacturer's Fall Outs which include Functional and part Functional Units. These are classed as out-of-spec from the maker's very rigid specifications but are ideal for learning about IC's and experimental work.

**U721 30 ASSORTED LINEAR TYPES**  
 709 741-747 748-710-588 Etc.  
 ORDER No. 16227 Price £1.50

**U765D FM STEREO DECODER**  
 511C 576110 Etc to MC1310P MA767 Data supplied with pak.  
 ORDER No. 16229 Price £1.50

**U76A AUDIO POWER OUTPUT AMPLIFIERS**  
 8 Assorted types 5L403 76013 76003 Etc Data supplied with pak.  
 ORDER No. 16228 Price £1.00

## 74 SERIES PAKS

# BI-PAK

High quality modules for stereo, mono and other audio equipment.



**NEW**

## PUSH-BUTTON STEREO FM TUNER

OUR PRICE ONLY

**£20.45**

Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

**Typical Specification:**  
Sensitivity 3µ volts  
Stereo separation 30db  
Supply required 20-30v at 90 Ma max.

## MPA 30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

**£2.85**

## STEREO PRE-AMPLIFIER



## PA 100

OUR PRICE  
**£13.75**

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response + 1dB 20Hz 20KHz. Sensitivity of inputs  
1. Tape Input 100mV into 100K ohms  
2. Radio Tuner 100mV into 100K ohms  
3. Magnetic P.U. 3mV into 50K ohms  
P.U. Input equalises to R1AA curve with, 1dB from 20Hz to 20KHz.  
Supply — 20-35V at 20mA.

Dimensions —  
299mm x 89mm x 35mm.

**MK. 60 AUDIO KIT:** Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs, 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £29.55** plus 85p postage

### TEAK 60 AUDIO KIT:

Comprising Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £10.70** plus 85p postage.

### SPECIFICATION:


- Harmonic Distortion  $P_o = 3$  watts  $f = 1$  KHz 02.5%
- Load Impedance 8-16ohm
- Size: 75mm x 63mm x 25mm
- Frequency response  $\pm 3$ dB  $P_o = 2$  watts 50Hz-25Hz
- Sensitivity for Rated O/P —  $V_s = 25$ v.  $R_L = 8$ ohm  $f = 1$  KHz 75mV. RMS

AL30 10w R.M.S. **£3.45**

## AL-30
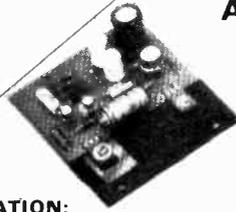
### AUDIO AMPLIFIER MODULE

The versatility of the design makes it ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.



**VAT  
ADD  
12 1/2%**

### POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

## STEREO 30

COMPLETE AUDIO

7+7 WATTS  
R.M.S.



P & P 45p

**£16.25**

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

TRANSFORMER **£2.45** plus 62p p & p  
TEAK CASE **£5.25** plus 62p p & p.

## AL 60 25 Watts (RMS)

★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load — 3,4,8, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



**NEW PA12**  
NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL 30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

**£6.70**

**£4.35**

## PS12

Power supply for AL20/30, PA12, SA450 etc.

OUR PRICE

**£1.30**

## Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80  
**£2.60 + 62p postage**

**£3.75**

Input voltage 15-20v A.C. Output voltage 22-30v D.C.  
Output current 800 mA Max. Size 60mm x 43mm x 26mm.  
Transformer T538 **£2.30**

# BI-PAK

P.O. BOX 6,  
WARE,  
HERTS


SHOP AT 18 BALDOCK ST., WARE, HERTS  
OPEN 9 to 5.30 Mon. / Sat.

# news digest
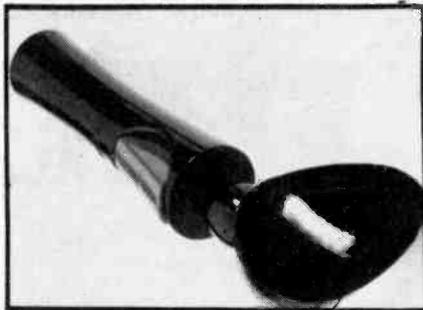
## MOVEMENT IN THE STATIC FIELD



Looking rather like a toothbrush for 'Jaws', this device is actually a new method of cleaning L.P.s. The method it adopts is a cross between an anti-



static pistol and a record brush. In fact — it's both!

The piezo-electric cell is mounted in the handle, and ionisation takes place within the head cavity from a needle electrode. The makers say this loosens any dirt present, allowing it to be swept up onto the velvet pad by the brush.

In a field bristling with sweeping claims, this looks ion-clad! It will be shown at the Hi-Fi Exhibition at the Heathrow Hotel for the first time, is called the EARC and costs £11.50. *Sounds Professional, 49 Theobald St., Boreham Wood, Herts.*

## A CHIP OFF THE OLE MPU

Fairchild have developed a one-chip version of their F8 MPU called the 'F8 Micromachine', aimed at low-cost and a wide range of consumer and industrial applications.

The Micromachine 1 will be available in sample quantities in April. Designated as the 3859, this circuit provides all the functions of the earlier two chip F8 system consisting of the 3850 CPU and the 3851 PSU (Program Storage Unit). The F8 Micromachine is aimed to provide the most effective solution for applications that can be accomplished with 1-kilobyte of memory. This covers a wide range of equipment such as home appliances, television tuning, video games, industrial and home heating, utility meters and thermostatic controls.

## CLIPPING CHEATER WINGS (AND TICKETS)

EMI and GEC Elliot have a contract to develop a ticket inspection system for British Rail. Eventually it will be installed in 600 stations, if successful.


A pilot scheme is about to be run between Waterloo and Staines. Five stations will have the equipment installed as a test run. An automatic gate reads the magnetically encoded ticket checking date, type and destination, and decides whether to let you through or not, and whether to give you back the ticket. A Ferranti 16-bit MPU is around in there somewhere.

Ticket sizes will be standardised and season tickets may well become credit card sized, and even plastic perhaps. With this system BR expect to save the cost of the system eventually out of the £6M now lost to frauds.
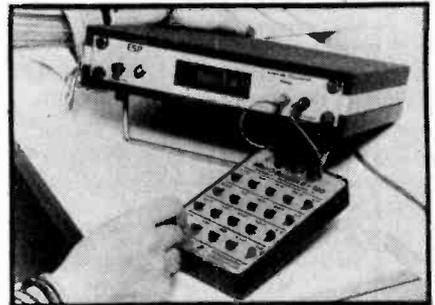
## USING ESP TO BOOST EXPORTS?

Lurking in the wilds or otherwise of Daventry is a new small company called Electronic Services and Products about whom we had heard some disturbing rumours. In these days of almost total British business pessimism they are apparently daring to *export* (whisper it softly) and export successfully at that.

The firm was started by three electronic enthusiasts who also happen, not coincidentally, to be brothers. Speciality is capacitance measurement, and ESP produce a range of automatic capacitance bridges. The photo below is of their 300 A, which possesses a range of 1 pF to 2000  $\mu$ F. Autorang-



ing. Accuracy of 0.5%. Time taken to arrive at a measurement is about 1/10th that of the old (well-hated!) ratio bridges.

Exports are by far the largest part of their business, with France and Germany being the main customers.

The firm has plans to expand its field of interest soon, maybe into consumer electronics - although exactly how, they're keeping very much behind a screen at present. Plans on the lab side include an LCR instrument, with the same autoranging and identification facilities as the 300 A, and even a 'smart' component tester.

There is an unshakable air of optimism about the whole operation which must send the poker-faced prophets of impending doom running for their tombs, and provide a welcome fillip for our apparently ailing industry.

## 741 AND 741 AND 741 AND 741

A new four-in-one op amp is announced by Precision Monolithics Inc. The PM 4136 series provides four 741-type operational amplifiers in a single 14-pin DIP package. Each of the amplifiers has the SSS741 advantages of low noise, low drift and excellent long term stability. *Bourns (Trimpot) Ltd., Hodford House, 17/27 High Street, Hounslow, Middx., TW3 1TE.*

## DIP-ING INTO PROBES

### MOTOROLA A2D

The MC 14433B is a new  $3\frac{1}{2}$  digit A>D converter from Motorola. Both analogue and digital CMOS circuitry are present on the chip. It is designed to minimise the need for external components.

With two Rs and two Cs and a 14433B you have a dual-slope A>D converter with auto zero connection and polarity detection. *Motorola Ltd., York House, Empire Way, Wembley, Middx.*


### A CASE FOR SERVICE?

Measuring 15 x 12 $\frac{3}{4}$  x 8 ins overall, the case is from the Industrial Division of Link-Hampson Ltd., 5 Bone Lane, Newbury, Berks. It is based on the Link-MK storage system.




In addition to space for a selection of tools, the case contains 8 small, 3 medium and 1 large full-width drawers. Each is removable and with provision for dividing into two or more compartments. A strong carrying handle and side-straps are fitted. Price is £24.95 plus VAT.

### ...AND ONE 4 MODS?

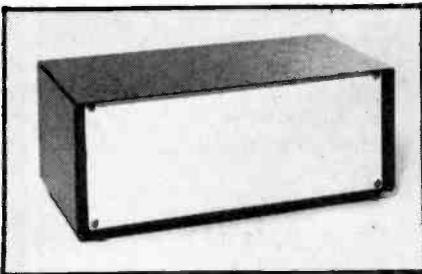

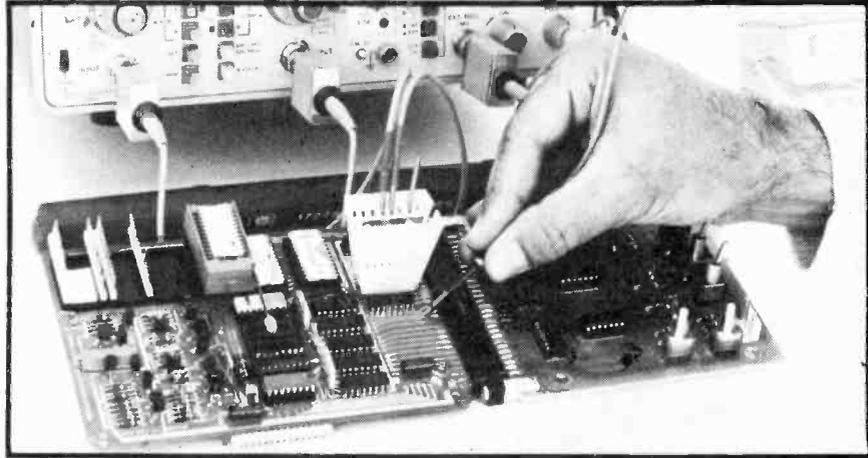
West Hyde let loose another range of Contil-Mod cases this month, the 'Mod 4' range, starting at £3.33 inc. p.+p. (and feet!!). Assembly is simple, and follows the well-known Contil style. The cases are black with a white steel front panel. *W.H. Developments, Ryefield Crescent, Northwood, Middx.*



HP's solution to the problem consists of a clip that encompasses an entire DIP, and an accompanying set of demountable probes, believed the smallest yet commercially offered. The basic part of each probe can be inserted by itself into the DIP clip at any pin position; indeed, 15 of them can be inserted simultaneously into a DIP clip; one position is used with a grounding pin, so any pin on the DIP can be used as probe ground, holding lead inductance to a minimum.

The series includes high-impedance dividing probes suitably compensated for most oscilloscopes with input capacitances of 9 to 14 pF. 1:1 probes are also available. Each is offered with a choice of 1-metre or 2-metre length cable. The HP miniature divider probes are £70 each. 1:1 probes are £27. The companion 10024A IC Test Clip is £12. *Hewlett-Packard Ltd., King Street Lane, Winnersh, Wokingham, Berkshire RG11 5AR.*

## EVEN I CAN TELL THE DIFFERENCE!

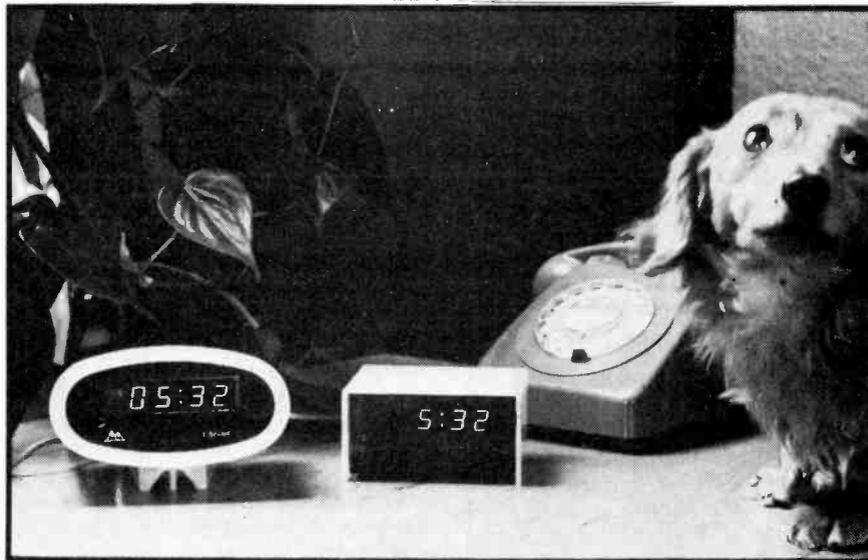

*We were rightly collared over this. Last month we lead our readers astray by mixing up the photographs in the Metac advertisements. We had the oval clock where the rectangular kit should have been, and the kit where..... precisely.*


*We apologise for any misunderstanding and inconvenience this may have caused.*

## A VACUUM IN CAR LEDS

Chrysler have given the elbow to LED displays in their forthcoming car clocks. Instead Futaba will be supplying them

with fluorescent 0.3 in. blue-green displays, some 500,000 in fact, next year. The logical bits will be National.

## DON'T FORGET DE-FUSE!

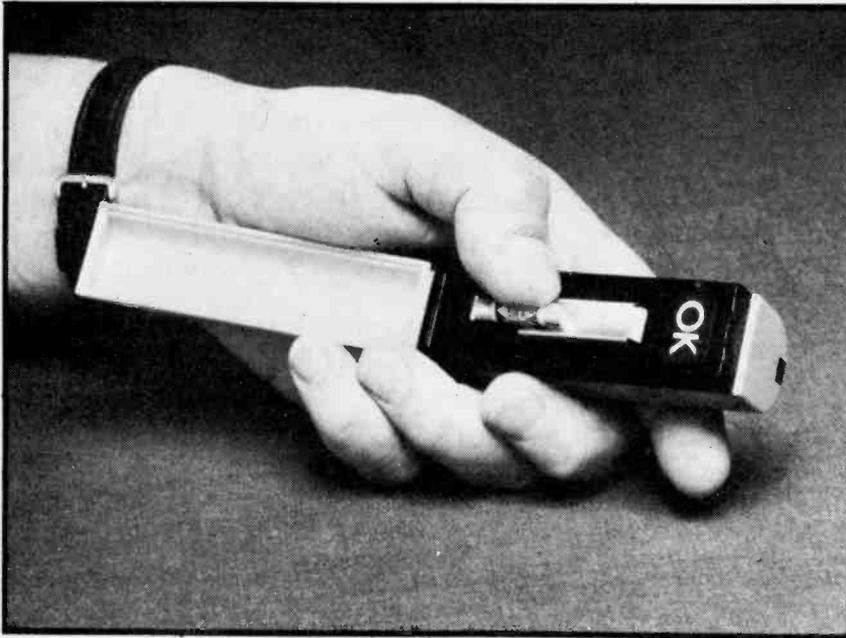

The first thing to check when a piece of mains equipment dies in its tracks is the fuse. Many an engineer has gone gibbering into a white coat with straps because he can't find the fault on a stubbornly inert heap of apparently perfect circuitry, while lurking in the plug is a burned out un-linking fuse.

Well, there is a very simple way of avoiding the farm, and it's called an

'MP4 Fuse Checker'. As you can see it's *really* pocket-sized, and gives a good clear indication if the thing is still a fuse as opposed to a piece of ceramic junk. Checks all fuses from 500 mA upward. To get one, write to: Moulds for Plastics Ltd., Watchmead, Welwyn Garden City, Hertfordshire, AL7 1AP. They'll charge you £1.25 all inc. for the privilege

## QUARTZ CRYSTAL CRISIS

This time last year U.S. crystal manufacturers were busy ordering yachts and private jets on the strength of the huge shortages prevalent in the field. However, in the past year the worm has spun rather than turned, and sackcloth is now the order of the day. As usual the Japs are the culprits, and stiff imported competition has beached the yachts good and proper.

Prices have hit the bottom so hard, it is threatening to fall out, and watch companies are buying more and more from the land of the rising LCD.

Intriguing eh?

## T.V. GAMES DUEL IN THE ROM.

Magnavox, who hold exclusively the Sanders original patent for T.V. games, have made a 'strong suggestion' to Fairchild and RCA that they cough up a license fee for producing their programmable T.V. games. Their claim is that their control extends to these games. So far Magnavox has trampled just about everybody else into the dust — perhaps Fairchild should hire Clint Eastwood to carry out the negotiations ... or play them 'T.V. Tennis' for it.

## TAKING THE MAINS TEMPERATURE?

Designed for bench- or rack-mounted temperature measurement applications, the Model 7005 digital thermometer from Jenway has an operational temperature range from  $-75^{\circ}\text{C}$  to  $999^{\circ}\text{C}$  with an accuracy of 0.1% of reading.




The Model 7005 has automatic cold junction compensation, and incorporates either three or four 14 mm gas discharge displays for clarity of temperature indication. The Model 7005 is housed in a rugged metal 96 mm din standard panel mounting case, and operates from an ac mains power supply at 110 V / 240 V 50 Hz. Jenway Ltd., 26 Broomhills Industrial Estate, Rayne Road, Braintree, Essex.
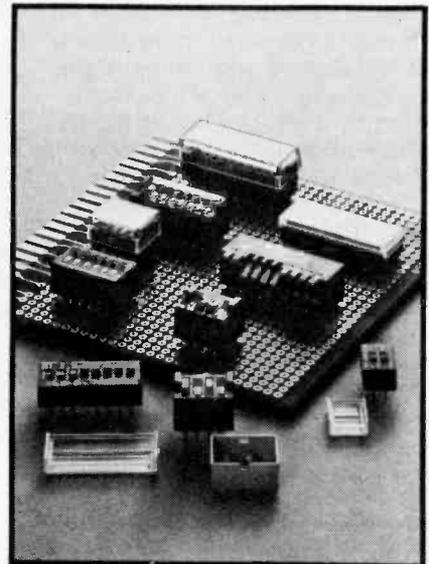
## BOARD MEETING AT THE POLES?

The new DIP switches are designed for use on printed circuit boards where they should find application in counters, computers, test gear or any situation demanding a simple programming or switching function. Up to 10 single pole switches can be specified in a single module, all with self-cleaning, gold-plated contacts capable of handling 100 mA at 50 V dc.

The pole positions are clearly numbered on the body of the switch to facilitate easy setting. Dust caps and locking mechanisms prevent accidental operation. The switches can be used with sockets or soldered directly to the printed circuit board; the design is such that soldering cannot contaminate the contacts. *Contraves Industrial Products Ltd., Times House, Station Approach, Ruislip, Middx.*



## MULL OVER TELETEXT HARD

Mullard will be shoving four dedicated teletext ICs onto the market in June. The chips are N-MOS, and are now being done in sample quantities. Numbered SAA 5020, 30, 40 and 50, and

when coupled with 7 k of RAM and 3 standard TTL packs, they produce a fully Viewdata compatible decoder.

Meanwhile back in Texas...

# Metac Digital Clock

## SEND NO MONEY


We will invoice you with the clock. Try it out for 7 days then send your payment or return the clock in original condition.

## SAME DAY DESPATCH

Clock orders received before 2.00 p.m. are posted on the same day.
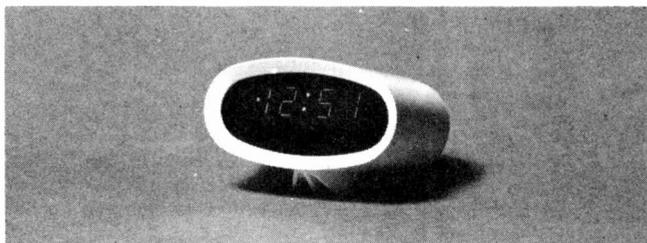
## 2 YEAR GUARANTEE

A commitment by us to repair or replace at our discretion any METAC clock failing to give satisfactory service for two years.



● Precise time-keeping accuracy. ● Solid-state long life reliability.

OUR  
PRICE  
COMPLETE

# £13.95

NO  
MORE  
TO  
PAY

In choice of orange planar gas or soft green fluorescent digit displays. Green model has 24-hour readout. Orange model has 12-hour readout and AM/PM indicator. Both models have flashing second indicator, 24-hour bleeper alarm, 5-minute repeater, main failure indicator, 5" across x 3½" deep. Attractive white case. Thousands sold. Please state choice.

An electronic clock is silent and extremely reliable; because there are no moving parts it is impervious to dust or vibration and will continue to work indefinitely. Timing signals are derived from the 50 or 60Hz domestic electricity supply which in all the developed countries has to be held to very high levels of accuracy.

A bleeper alarm sounds until the clock is tipped forwards. The "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc., until you switch the alarm off.

An indicator on the display tells you if the alarm is set, another indicator tells you if it's in the 'snooze' mode.

This remarkable clock even tells you if the electricity supply has momentarily failed.

**STOP PRESS** our **UXBRIDGE** shop is now open. Visit Metac-Electronics, Time Centre

**3 NEW ARCADE, HIGH ST., UXBRIDGE, MIDDX.** and see for yourself the full range of top quality watches, clocks and other consumer electronic products.

Please send your order to:

**METAC, ELECTRONICS AND TIME CENTRE**  
67 HIGH STREET, DAVENTRY, NORTHANTS.  
Tel. Daventry (03272) 76545 Shops open 9-5.30 daily

# Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.



# £6.20

plus 80p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated

Also available -- a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

# £4.20

plus 80p P. & P

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

**Guarantee—no risk to you**

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To Cambridge Learning Enterprises, Dept. DIG, FREEPOST  
Rivermill House, St. Ives, Huntingdon, Cambs. PE17 4RR  
\*Please send me . . . set(s) of Design of Digital Systems at £7.00 each  
p & p included

\*or . . . set(s) of Digital Computer Logic and Electronics at £5.00 each,  
p & p included

or . . . combined set(s) at £10.50 each, p & p included

Name

Address


\*delete as applicable

No need to use a stamp -- just print FREEPOST on the envelope

ET15

*now available: special reprint*

# TOP PROJECTS 1 + 2

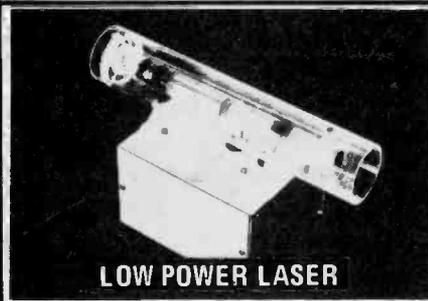


**LOW POWER LASER**



**MASTER MIXER**



**PRINTIMER**

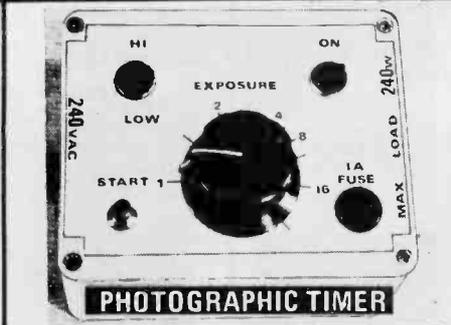

**PHOTOGRAPHIC TIMER**



**AUDIO WATTMETER**



**DIGITAL STOPWATCH**



**AUDIO ATTENUATOR**



**SPRING REVERB UNIT**



**WIDE-RANGE VOLTMETER**




**TRANSISTOR TESTER**



**MIXER PREAMP**



**LOGIC PROBE**

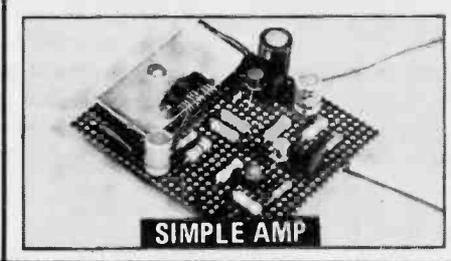

**SIMPLE AMP**



**NICKEL-CADMIUM BATTERY CHARGER**

**ALSO:** SIMPLE LOUDHAILER; OSCILLOSCOPE CALIBRATOR; ELECTRONIC TRANSISTORISED IGNITION; BATTERY CHARGER; AUTOMATIC CAR THEFT ALARM; TURN INDICATOR; CANCELLER; BRAKE LIGHT WARNING; THE REVEALER; METER BEATER; SOUND OPERATED FLASH; TEMPERATURE METER; USING THE LM380; TEMPERATURE ALARM; AERIAL MATCHER; UHF TV PREAMP; EARTH RESISTIVITY METER; ETI COIN COLLECTOR; EASIER WAY TO MAKE YOUR PCB; FOUR INPUT MIXER; LOGIC PROBE; SUPER STEREO; IC POWER SUPPLY; RUMBLE FILTER; IC TESTER; IGNITION TIMING LIGHT; TAPE/SLIDE SYNCHRONISER; THE FAMILY FERRY; HI-POWER STROBE; PLUS TWO ADD-ON DECODER; 100 W GUITAR AMP; 50 W STEREO AMP.


All ETI Top Projects books have sold well - so well that No.1 and No.2 are out of print. We've mentioned the fact many, many times but so many people have continued to request them that we've combined No.1 and No.2 in a massive 180 page reprint containing all the original projects. This is **ONLY** available at present direct from: ETI Specials, 25-27 Oxford Street, London W1R 1RF.

Price is £2.50 + 20p postage, sterling only please
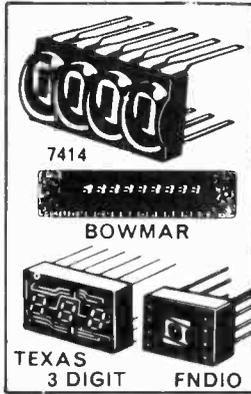
## CALCULATOR DISPLAYS

1 7/8" digit height, bright red LED 7 segment displays for calculators, digital watches, miniature clocks, DVMs, timers etc.

- \* Fairchild FND-10, single digit common cathode £1.00 (+vat 8p) 6 for £5.00 (+vat 40p)
- \* HP 7414 4 digit, common cathode 12 pin d.i.l. pin out 99p (+vat 8p) 6 for £5.00 (+vat 40p)
- \* Bowmar 8 1/2 digit, common cathode with pc connector, and red bezel £1.85 (+vat 15p) 6 for £10 (+vat 80p)
- \* Texas 3 digit common cathode 12 pin d.i.l. pin out 85p (+vat 7p) 6 for £4.00 (+vat 32p)
- \* Texas 4+5 digit, common cathode 2x14 pin d.i.l. £1.85 pair (+vat 15p)
- \* 30 pin termination board for all types except FND-10/20p (+vat 2p)
- Texas calculator keyboards, 19 gold plated 'snap' type key contacts on gold plated pcb. 75p (+vat 6p) p & p on all the above 25p.



## TAPE HEADS


**BX12E343; TRACK ERASE HEAD - £1.25 (+vat 15p)**  
**BX12RP63 WITH BX12E343 - £2.95 (+vat 36p)**  
**STEREO CASSETTE R/RP HEAD (200 ohm) - £2.25 (+vat 28p)**  
**TWIN STAGGERED MARRIOTT HEADS R/RP1 - £1.50 (+vat 18p)**  
**MARRIOTT RECORD/REPLAY & ERASE HEAD - £1.75 (+vat 21p)**  
**MINIFLUX R9N ERASE - £2.25 (+vat 28p)**  
**GX11 E388 ERASE 675 ohms 2 mA - £0.88 (+vat 11p)**  
**GX12 E387 ERASE 675 ohms 2 mA - £0.88 (+vat 11p)**  
**GX20 E362 ERASE 90 ohms 90 mA - £0.88 (+vat 11p)**  
**R/RP1/3 TAPE HEAD; TRACK - £0.65 (+vat 8p)**

## MULLARD TUNER MODULES -

**LP1171 combined AM/FM IF strip - £4.20 (+vat 53p)** \* LP1179 FM front end with AM tuning gang, used with LP1171 - £4.20 (+vat 53p) \* LP1171 & 79 pair - £8.00 (+vat £1.00) \* LP1157 complete AM strip - £2.05 (+vat 26p) \* Ferrite Aerial - 95p (+vat 7p)  
 p & p all modules 25p each

**HR-RP TAPE HEAD SINGLE TRACK £0.55 (+vat 6p)**  
**XRPS17; TRACK - £3.25 (+vat 40p)**  
**XRPS18; TRACK RED - £3.25 (+vat 40p)**  
**XRPS36; TRACK - £0.75 (+vat 79p)**  
**XES11; TRACK ERASE - £1.25 (+vat 15p)**  
**BX/RP/63; TRACK - £2.25 (+vat 28p)**

## HENELEC RADIO CONTROL SYSTEM

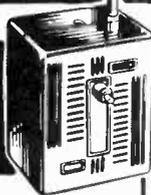

Specially designed to provide aircraft and boat modelmakers with a low-cost easy-to-use radio control. The Henelec system gives you everything from single channel, up to sophisticated 7 channel Digital Proportional System! Buy the components you want. Ideal for any radio control application. \* Simple

transmitter - £11.75 (+vat £1.47) \* Single ch. add on for receiver - £2.95 (+vat 37p) \* PC board for above - 75p (+vat 6p) \* Case for transmitter - £1.25 (+vat 16p) \* Basic receiver - £0.95 (+vat 97p) Send now for leaflet No. 8 (35p) for full details. Post etc 50p each

## HENRY'S GREAT NEW CATALOGUE

For this latest edition, we have made hundreds of changes and additions. Containing virtually everything for amateurs and professionals, Henry's Radio Catalogue is also a "must" for manufacturers. Again, we have included a complete alphabetical index, as well as a sectional index, so that you'll have no trouble at all in finding what you need.



IT'S THE BEST EVER!

**★ OVER 5,000 ITEMS**  
**★ OVER 200 PAGES**  
**★ DISCOUNT VOUCHERS**  
**★ QUANTITY DISCOUNTS ON MOST ITEMS**

**ONLY 85p PLUS 20p p&p**

FREE - to educational establishments and manufacturers when ordered on official headed notepaper.

**BULK PURCHASE - EXCLUSIVE TO HENRY'S**  
**ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

**QUALITY ITEMS**  
 Compare performance and specification with units costing 3 times as much!

## DIGITAL 24 HOUR CLOCK




WITH BUILT-IN ALARM

AS USED IN BRAUN DIGITAL CLOCKS

NORMALLY £24 WITH CASE

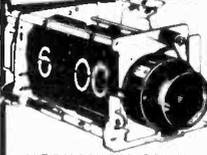**● SILENT RUNNING**  
**● LARGE ILLUMINATED NUMERALS**  
**● AC MAINS ● SIZE 6 3/8" x 2 3/8" x 2 3/8"**



**MECHANISM ONLY**  
**£6.00** + VAT 48p  
 P&P 25p  
**THREE FOR £16.50**  
 + VAT £1.32 POST FREE



**MECHANISM AND CASE** Inc. assembly instructions  
**£7.99** + VAT 64p  
 P&P 25p  
**THREE FOR £22.00**  
 + VAT £1.76 POST FREE



**COMPLETE UNIT**  
**£8.99** + VAT 72p  
 P&P 25p  
**THREE FOR £25.00**  
 + VAT £2.00 POST FREE

## TEXAN AMPLIFIER

featured by PRACTICAL WIRELESS  
 still the best selling amp in the UK.

**Build it yourself**  
**£29.95** + VAT £3.74  
 P&P £1 Built £39.95 - VAT £4.93

Build the Texan stereo amplifier, and be doubly proud! You'll own a superb home entertainment unit. And the pleasure of doing it yourself. Look at the Texan specification Fully integrated stereo preamp and power amp, 6IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibre pcb; Gardners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS.



The natural follow on!

## TEXAN FM TUNER KIT £20.95 + VAT £2.62

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

HC6U (USA 2M) METAL CASED HERMETICALLY SEALED. CRYSTAL ACCURACY 0.005%. TWO PIN 0.5" PIN SPACING. ALL TYPES THIRD-OVERTONE ALSO SUITABLE FOR USE ON THEIR FUNDAMENTAL FREQUENCY (i.e. DIVIDE BY 3). OVERALL SIZE 3/4" x 11/16" x 5/16"				
53.675 Kc/s	39.5555 Mc/s	40.0740 Mc/s	40.8519 Mc/s	50.1000 Mc/s
66.986	39.5926	40.1481	40.8889	
	39.6296	40.1852	40.9259	
31.111T Mc/s	39.6667	40.2222	40.9633	
31.6667	39.7037	40.2593	41.1111	
32.2222	39.7778	40.2963	44.3000	
33.3333	39.8148	40.3333	44.5000	
36.6667	39.8519	40.3704	45.7000	
37.7778	39.8889	40.4017	46.5000	
38.0000	39.9259	40.5926	46.7000	
38.3337	39.9630	40.7407	46.1200	
39.5185	40.0370	40.8148	45.9000	

PRICE EACH 95p + 12p VAT p & p 15p

**Henry's Radio** All mail to: Henry's Radio 404 Edgware Rd, London W2  
 LONDON W2: 404 '6 Edgware Road. Tel: 01-723 1008

MAKE YOUR TELEVISION WORK FOR ITS WATTS WITH OUR

# TV GAMES UNIT

This low-cost yet sophisticated TV game contains just one main IC plus a handful of other components yet out-performs virtually all other units currently on the market.

SINCE THE ADVENT OF television games in this country, we have met with a steady tide of requests to produce a project for one ourselves. However, even with the higher integration allowed in CMOS chips, and no-one in their right minds would contemplate using TTL, it was still not viable for the home constructor. We were waiting for the single control chip to arrive on the open, as opposed to industrial, market.

At long last it has, in the form of the GI AY-3-8500, and so here is *our* version of a game utilising it. Figure 1 shows the kind of display produced by the chip, with its on-screen scoring facility and all. The games playable are:

1. PRACTISE: The ball reflects off the end and side walls, and the player has to stop it passing him. Every time it does, the machine scores a point.
2. SQUASH: A second bat is added to the display, and you play against each other. When it is your opponents turn, your bat will not affect the ball.
3. TENNIS: Television tennis is widely known and played, but see the specification section for the unusual features of our game.
4. FOOTBALL: The ball reflects off all four sides of the court, except the goal-mouth. This must be defended by the goalie to prevent the opposition scoring. In addition, each player has a forward on the screen, who acts as a normal bat when the ball is heading for his own goal, but allows the ball to pass through him, deflecting it in the process, when it is moving

towards the opposite goal.

## Rifling the screen

In addition, there are two rifle games included on the chip, but these need a special attachment to operate, which we are not including in this article (but will probably 'do up' later — especially if there is sufficient demand).


Some circuitry, additional to the main IC, in the form of two extra ICs, is required to build the basic game unit, but the complexity is still way way down on any other

method of obtaining 'the same display.

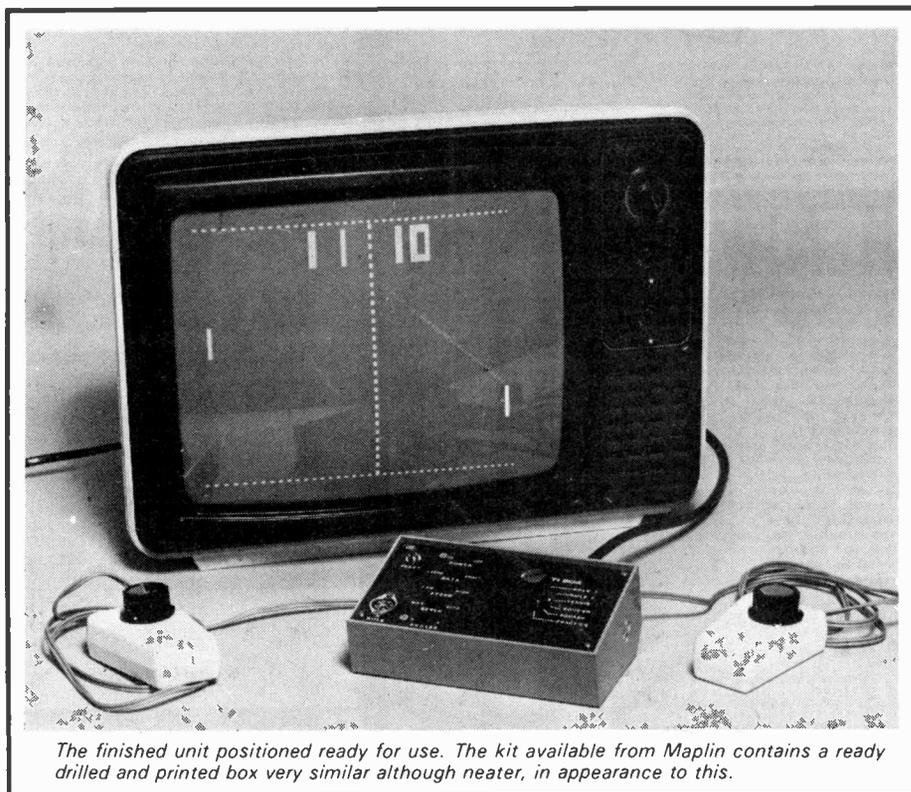
## Construction

Assemble the pcb, fitting the passive components and links first, along with the socket to the main chip. Leave this in its packing until you need it. Handle the CMOS chips carefully, and when fitting these, either use sockets or solder the power supply pins (7 and 14) first.


The switches will fit directly onto the board, and the rotary is



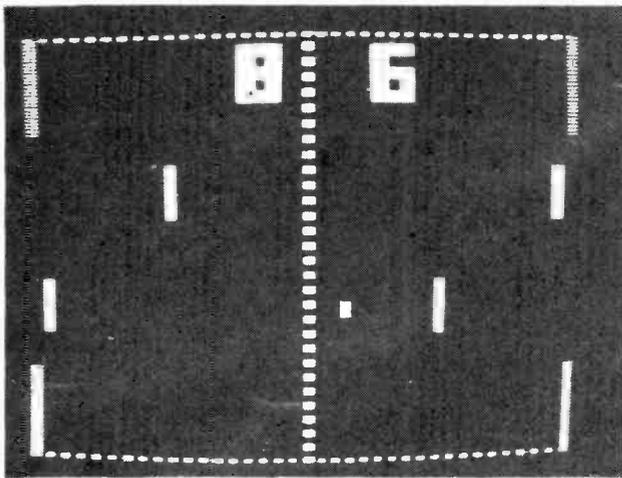
The finished unit positioned ready for use. The kit available from Maplin contains a ready drilled and printed box very similar although neater, in appearance to this.




Soccer

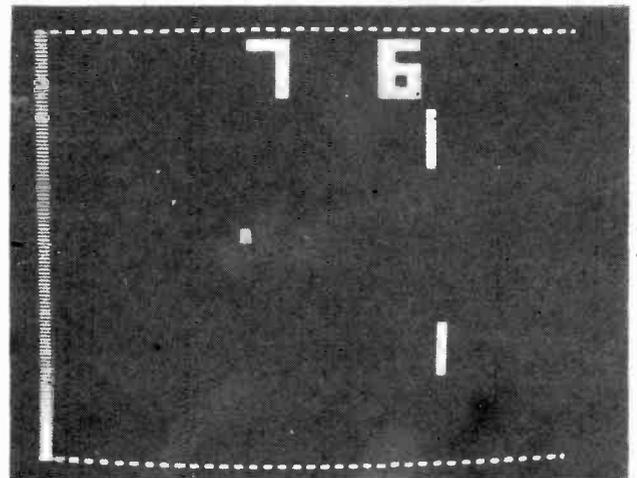

Squash

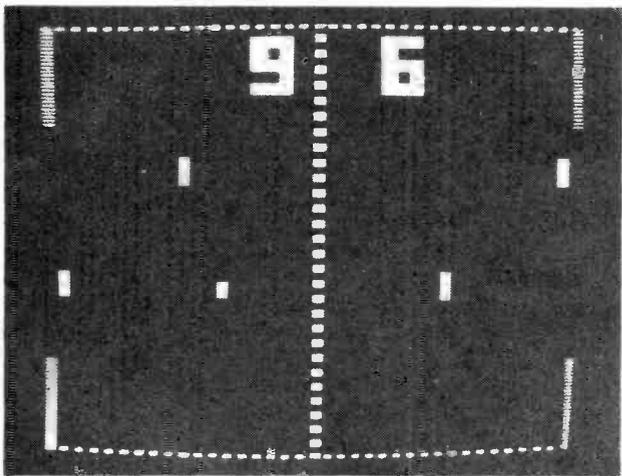

Soccer with small bats

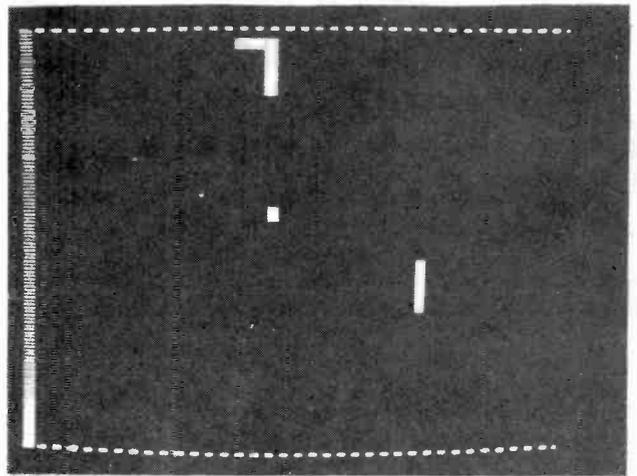

Practice

An illustration of some of the other displays produced by the unit. Note how much smaller the bats are on the soccer display — this facility is available on all the games.


## Specification

<b>Output</b>	<b>Picture:</b> TV signal (can be set up on any channel). <b>Sound:</b> Three audio tones indicate hit, bounce and score.
<b>Players' Controls</b>	Each player uses a single rotary control to position his bat/men on the screen. In the practice game one control operates; for tennis, soccer and squash two players each have a control. For the rifle games a special rifle is needed (not described in this article).
<b>Game Selection</b>	<b>Basic Games:</b> 1) Practice                      2) Squash 3) Soccer                        4) Tennis <b>Other Games (these cannot be played without a special rifle):</b> 5) Rifle-1                        6) Rifle-2
<b>Scoring</b>	On-screen scoring up to a maximum of 15 points.
<b>Other Features</b>	Two ball speeds Two bat sizes Two angles $\pm 20^\circ$ ; or four angles $\pm 20^\circ$ & $\pm 40^\circ$ . Manual or automatic service


used to hold the board to the front panel, so check your soldering carefully here. Fit the link to the modulator, and the wires out to the hand-held Vero boxes which contain the control and serve button for each player. Push these out through the (hopefully grommets) holes, tying a knot in each to make sure it doesn't strain the joint if pulled, and connect up the control boxes.

Once all the connections to the board are made, attach it to the front panel using the rotary switch, and two spacers on the switches for power and angle change.

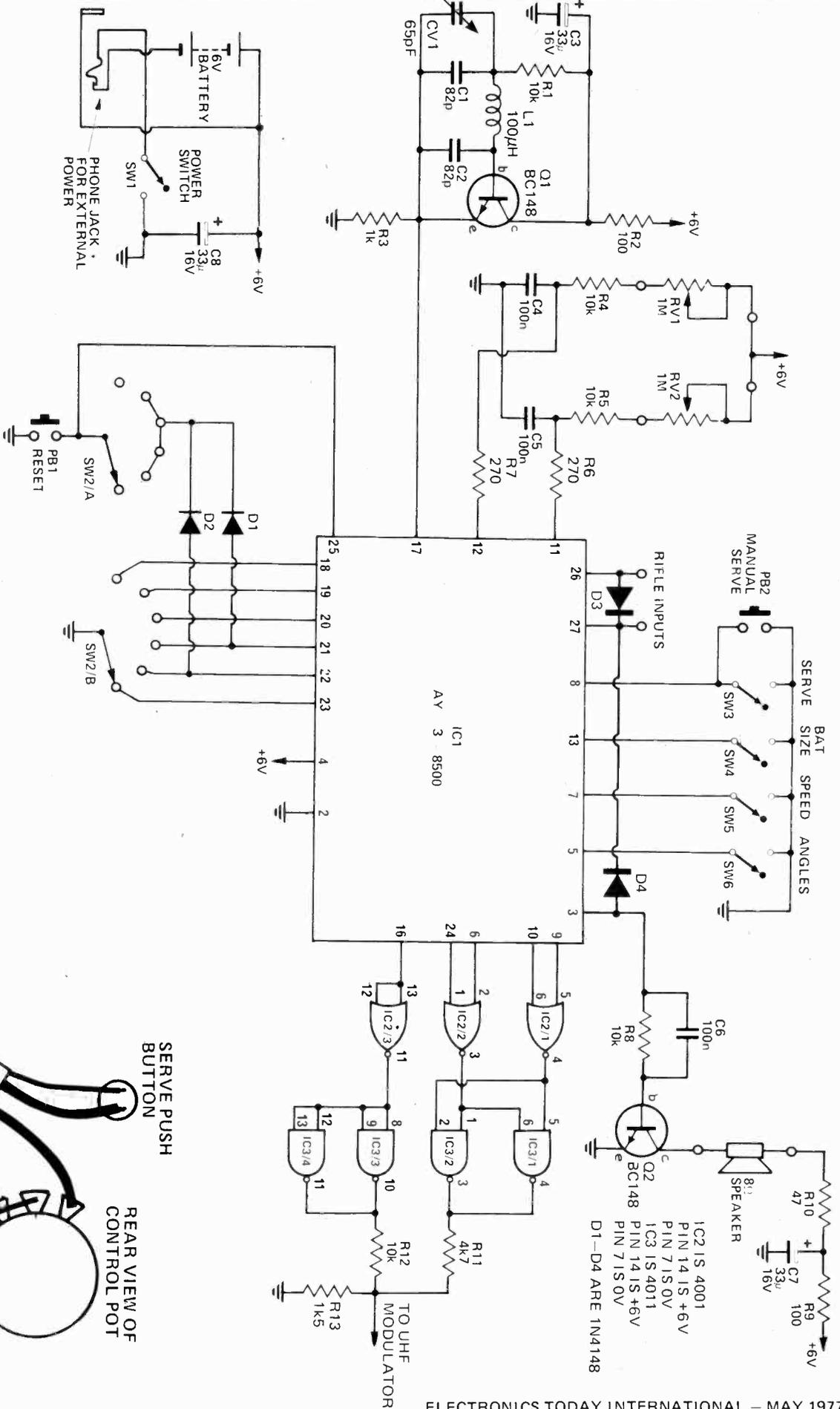If you use our kit from Maplin, the modulator is ready built, and there is no 'tuning up' to do. Simply bolt it in to the box through the hole provided, connect up power and video, and tune in a



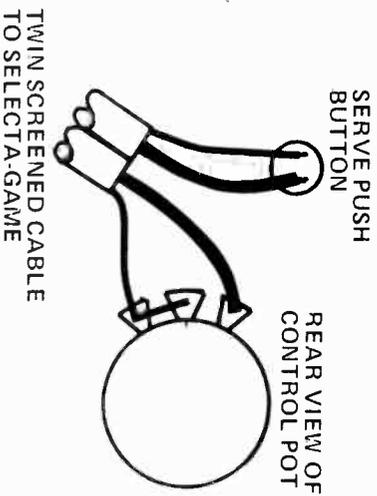
Circuit Diagram and control pot wiring. We had a suggestion, made on the eve of going to press as all the best suggestion are, that wire wound pots would be better as the bat controls. We leave it to you to decide for yourselves. Our carbon tracks have given us no trouble so far!



Component Overlay for the T.V. game. Use UHF cable to connect up the modulator block to the board, and screened cable to wire up the hand-held boxes, connecting the screens and inners of the two "serve" wires to the pins in the center of the board.

Maplin Electronic Supplies are making up a kit of parts for this project which includes a ready assembled modulator, p.c.b., ready drilled box which is also printed up, and all components. All inc. price is £24.60

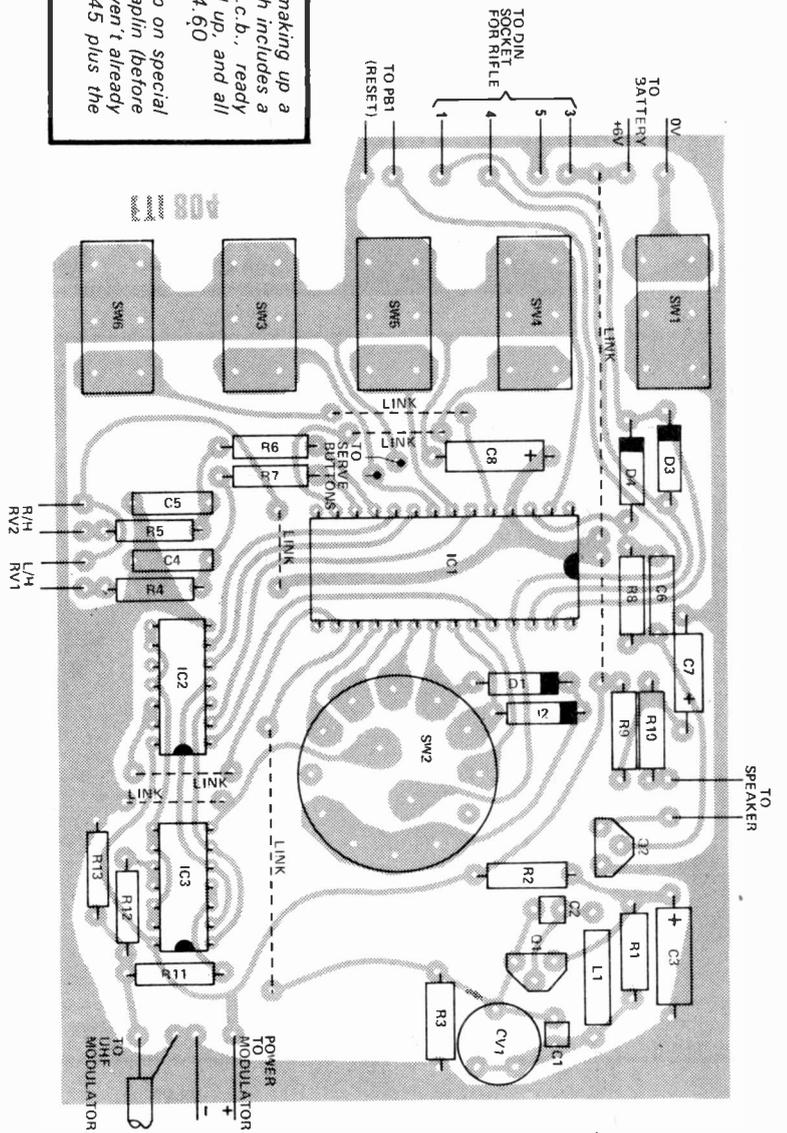For those who obtained the chip on special offer at £8.99 all inc. from Maplin (before April 18th so be quick if you haven't already got one!) the kit price is £13.45 plus the voucher sent with the chip.



## How it works

Unfortunately the manufacturers don't give much information on how the main IC works — we are only told how to use it. The chip is obviously a digital IC (because there are two ball speeds, the rebound angles are defined and there is no provision for variable speed or bounce).

A 2 MHz oscillator is required for the chip to derive the synchronising pulses required for line and frame synchronisation of the TV set. This oscillator is provided by Q1 and its associated components with CV1 providing calibration.

The bats are simply one megohm potentiometers connected as variable resistors which effectively vary the charging time of capacitors C4 and C5. The capacitors C4 and C5 are discharged by the chip at each frame sync pulse and the time taken to charge again (as set by the bat pot setting) determines the vertical position of the bats on the screen. The bat size, ball speed, deflection angles and serve are simply selected by connecting the appropriate pin of the IC to '0' volts.



Outputs from the chip are left and

right bat, sync, ball, score and sound — all on separate pins. The bats, ball and score outputs are combined by IC2/1, 2 and IC3/1, 2 to produce a composite video signal. The sync pulse is buffered by IC2/3 and IC3/3, 4. The sync and information pulses are then added by R11, 12 and 13. The sound output is buffered by Q2 to provide the power necessary to drive the speaker.

So that the game may be fed into the antenna terminals of a TV receiver the video signal must be modulated onto an RF oscillator

## Parts List

- |                              |                           |                |
|------------------------------|---------------------------|----------------|
| <b>RESISTORS</b> , all ½W 5% | R1                        | 10k            |
|                              | R2                        | 100            |
|                              | R3                        | 1k             |
|                              | R4,5                      | 10k            |
|                              | R6,7                      | 270            |
|                              | R8                        | 10k            |
|                              | R9                        | 100            |
|                              | R10                       | 47             |
|                              | R11                       | 4k7            |
|                              | R12                       | 10k            |
|                              | R13                       | 1k5            |
| <b>POTENTIOMETERS</b>        | RV1,2                     | 1 M lin rotary |
| <b>CAPACITORS</b>            | C1,2                      | 82 p ceramic,  |
|                              | C3                        | 33 µ16 V       |
|                              | C4,5,6                    | 1 µ polyester  |
|                              | C7,8                      | 33 µ16 V       |
| <b>VARIABLE CAPACITOR</b>    | CV1                       | 65 pF trimmer  |
| <b>TRANSISTORS</b>           | Q1,2                      | BC148          |
| <b>DIODES</b>                | D1 - D4                   | 1N4148         |
| <b>INTEGRATED CIRCUITS</b>   | IC1                       | AY-3-8500      |
|                              | IC2                       | 4001 (CMOS)    |
|                              | IC3                       | 4011 (CMOS)    |
| <b>INDUCTORS</b>             | L1                        | 100 µH         |
| <b>MISCELLANEOUS</b>         | pcb ETI 804               |                |
|                              | 2 pole 6 position switch  |                |
|                              | 5 slide switches          |                |
|                              | 8 ohm speaker             |                |
|                              | 3.5 mm jack socket        |                |
|                              | 5 pin DIN socket type 'A' |                |
|                              | 3 miniature push buttons  |                |
|                              | 3 knobs                   |                |
|                              | 1 box                     |                |
|                              | 2 small boxes             |                |
|                              | Single 6 V battery holder |                |
|                              | 28 pin IC socket          |                |

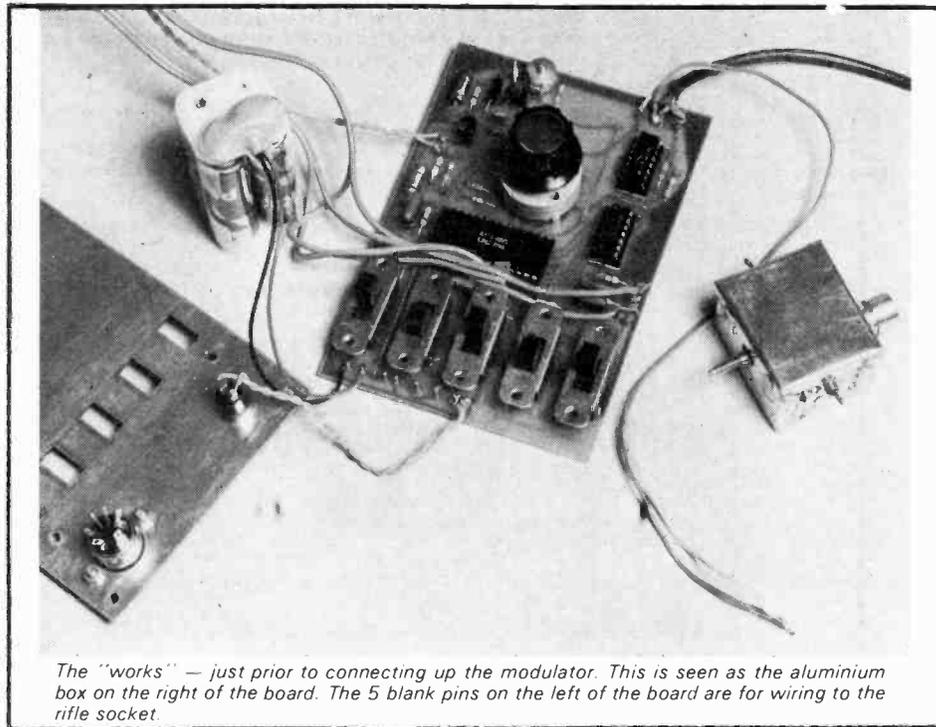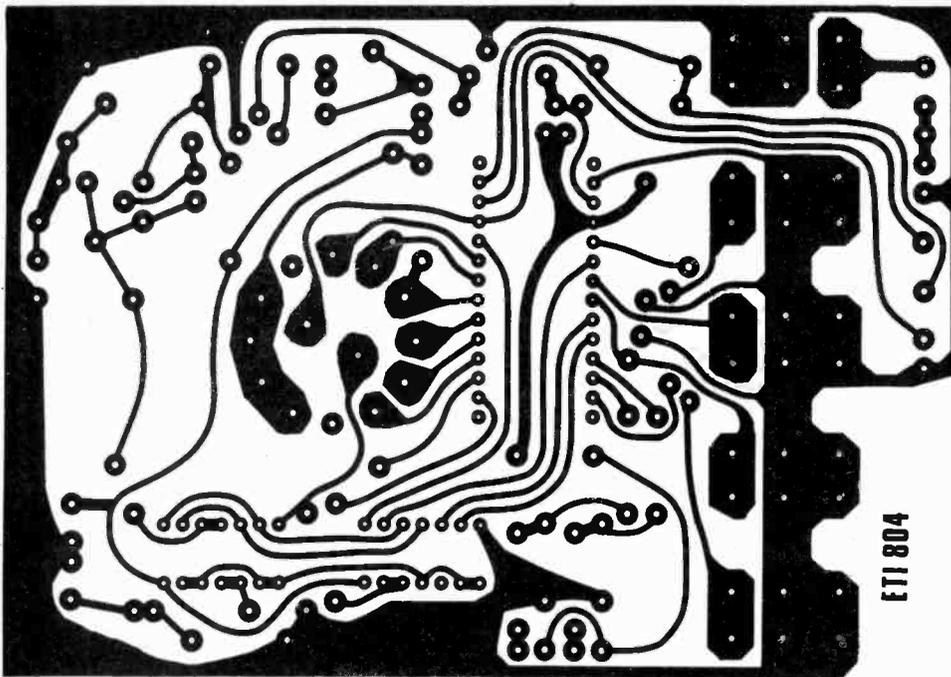

The "works" — just prior to connecting up the modulator. This is seen as the aluminium box on the right of the board. The 5 blank pins on the left of the board are for wiring to the rifle socket.

spare button on your TV to give a picture. Adjust C2 until the picture locks.

Use UHF cable to link board and modulator and box and TV. Screened cable is all that is required to link control boxes and main unit.

### Play the game

With the angles switch at '2', the ball moves at  $\pm 20^\circ$  across the screen. When hitting the side boundaries the laws of reflection

are obeyed. When the ball hits the bat this isn't always the case: a ball hitting the top half of the bat will leave with an upward trajectory, and downwards from the bottom half.

With the angles switch at '4' the game becomes much more awkward! The bat is now divided into four sections. Starting from the top, the ball emerges at an angle of  $+40^\circ$ ,  $+20^\circ$ ,  $-20^\circ$ ,  $-40^\circ$ . If you think that is easy, try playing with small bats and high speed.

### NEW COMPONENTS SERVICE

**Resistors** 5% carbon E12 2.7 $\Omega$  to 10M  $\frac{1}{4}$ W 1p. 1W 2p. **Presets** POTS subminiature 0.1W E3 100 $\Omega$  to 4M7. Vertical 9p. Horizontal 9p. **Potentiometers** 0.25W E3 4K7 to 2M2 log or lin. Single 24p. Dual 7.5p. **Polyethylene capacitors** E12 63V 22pF to 8200pF 3 $\frac{1}{2}$ p. **Ceramic capacitors** vert. 50V E6 22pF to 4700pF 3p. **Mylar capacitors** 100V 001, 002, 005 4p, 01, 02, 025 4 $\frac{1}{2}$ p. **Polyester capacitors** 250V E6 01 to 1mf 5 $\frac{1}{2}$ p., 15, 22mf 7p., 47mf 11p. **Electrolytics** 50V 47, 1, 2mf 5p. 25V 5, 10mf 5p. 16V 22, 47mf 6p. 100mf 7p. 220mf 9p. 470mf 11p. 1000mf 18p. **Zener diodes** 400mW E24 3V3 to 33V 8 $\frac{1}{2}$ p.

### MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p. 18V 1A £1.95 0/12/15/20/24/30V 1A £3.65. 12-0-12V 50mA 94p. 0/12/15/20/24/30V 2A £4.95. 6-3V 1 $\frac{1}{2}$ A £2.10. 6-0-6V 1 $\frac{1}{2}$ A £2.55. 9-0-9V 1A £2.19. 12-0-12V 1A £2.49. 15-0-15V 1A £2.69. 30-0-30V 1A £3.39.

### PRINTED CIRCUIT KITS ETC ★

Contains etching dish, 100 sq ins of pc board, 1lb ferric chloride, etch resist pen, drill bit and laminate cutter £3.65. 100 sq ins pc board 75p. 1lb FeCl<sub>3</sub> 95p. Etch resist pen 75p.

### S-DECS AND T-DECS ★

S-DeC £1.94. T-DeC £3.61. u-DeCA £3.97. u-DeCB £6.97. IC carriers with sockets. 16 dil £1.91. 10T05 £1.79.



### SINCLAIR CALCULATORS, WATCHES AND POCKET TV ★

Sinclair pocket TV £165. Cambridge Scientific £8.95. Cambridge Memory £5.95. Oxford Scientific £13.30. Mains adaptors (state model) £3.20. Assembled grey watch with free stainless steel bracelet £16.45. White watch £13.95.

### BATTERY ELIMINATOR BARGAINS

#### 3-WAY MODELS

With switched output and 4-way multi-jack connector. Type 1 3 / 4 $\frac{1}{2}$  / 6V at 100mA £2.30. Type 2 6 / 7 $\frac{1}{2}$  / 9V at 300mA £2.90.

#### 100mA RADIO MODEL

With press-stud connectors. 9V £3.45. 6V £3.45. 9V + 9V £5.45. 6V + 6V £5.45. 4 $\frac{1}{2}$ V + 4 $\frac{1}{2}$ V £5.45.

#### CASSETTE MAINS UNIT

7 $\frac{1}{2}$ V with 5 pin DIN plug. 150mA £3.65.

#### FULLY STABILIZED MODEL £5.45

Switched output of 3 / 6 / 7 $\frac{1}{2}$  / 9V 400mA stabilized.

#### CAR CONVERTORS £5.10

Input 12V DC. Output 6 / 7 $\frac{1}{2}$  / 9V DC 1Amp stabilized.

### BATTERY ELIMINATOR KITS

Send sae for free leaflet on range.

**100mA radio types** with press stud battery terminals. 4 $\frac{1}{2}$ V £2.10. 6V £2.10. 9V £2.10. 4 $\frac{1}{2}$ V + 4 $\frac{1}{2}$ V £2.50. 6V + 6V £2.50. 9V + 9V £2.50.

**Cassette type:** 7 $\frac{1}{2}$ V 100mA with DIN plug £2.10.

**Transistor stabilized 8-way type** for low hum. 3 / 4 $\frac{1}{2}$  / 6 / 7 $\frac{1}{2}$  / 9 / 12 / 15 / 18V 100mA £3.20. 1 Amp £6.50.

**Heavy duty 13-way types** 4 $\frac{1}{2}$  / 6 / 7 / 8 $\frac{1}{2}$  / 11 / 13 / 14 / 17 / 21 / 25 / 28 / 34 / 42V. 1 Amp model £4.95. 2 Amp model £7.95.

**Car convertor kit:** Input 12V DC. Output 6 / 7 $\frac{1}{2}$  / 9V DC 1A transistor stabilized £1.95.

**Stabilized Laboratory power kit.** Switched 1 to 30V in 0.1V steps. 1 Amp £12.45. 2 Amp £14.95.

### SINCLAIR PROJECT 80 AUDIO MODULES

P25 £4.95. Z40 £5.75. Project 805Q £20.95.

#### BI-PAK AUDIO MODULES

S450 tuner £20.95. AL60 £4.60. PA100 £14.95. MK60 audio kit £31.95. Stereo 30 £16.95. SPM80 £3.65. BMT80 £3.32. Send sae for free data.

#### SAXON ENTERTAINMENTS MODULES

SA1208 £16.95. SA1204 £11.95. SA608 £11.45. PM1201 / B £10.95. PM1202 / B £15.95.

### SINCLAIR IC20

IC20 10W + 10W stereo integrated circuit amplifier kit with printed circuit and data £4.95.

PZ20 Power supply kit for above £3.65.

VP20 Volume, tone-control and preamp kit £8.95. Send sae for free leaflet on the whole system.

### JC12 AND JC40 AMPLIFIERS

JC12 6W IC audio amp with free data and printed circuit £1.95.

Also new JC40 20W model with pcb

£3.95. Send sae for free leaflet on both models and associated power supply and pre-amp kits.



### FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

### SWANLEY ELECTRONICS

Dept. ETI, PO Box 68, 32 Goldsail Road  
Swanley, Kent

Mail order only. No callers. Send sae for free data on kits. Post 30p on orders under £4.50, otherwise free. Prices include VAT. Official orders welcome. Overseas customers please deduct 7% on items marked ★ and 11% on others.

# SC/MP Rules O.K!

In addition to SCRUMPI Bywood supports SC/MP in these other kits from National Semiconductors—  
**INTROKIT:** Eurocard PCB with SC/MP chip, 256x8 RAM, 512x8 PROM (with KITBUG monitor), Xtal, TTY interface, etc. Requires +5, -12v supply. If you have access to a TTY machine then this kit is a great start in microprocessors. If you do not have access to a TTY then you may consider using NS's new KBOKIT, replace the KITBUG PROM in an INTROKIT with the PROM supplied, add a few other components (supplied) and you have a portable microprocessor.

### INTROKIT £66.33, KBOKIT £66.50

**LCDS:** National's Low Cost Development Kit for SC/MP. Uses a Hex keyboard and digital display or a TTY to communicate with the 2K monitor programs in PROM. The CPU application card supplied plugs into one of the sockets on the main mother PCB. Additional PROM and RAM application cards are available to allow expansion up to its full 64K capacity. RUN/STEP/HALT run modes allow for simple debugging.

### Low Cost Development System £349.30

BITS & PIECES		74C00 SERIES CMOS	
MM2112.2 256x4 RAM	£4.30	74C00 25p	74C04 25p
MM2102.2 1Kx1 RAM	£2.95	74C10 25p	74C42 200p
2513 ASCII char gen ROM	£9.00	74C157 200	74C163 130p
DM8678 9x7 char gen + PISO	£15.20	74C164 110p	74C165 115p
DM8095 6 bit buffer (Uni-Di)	£1.90	74C173 100p	
DS8833 4 bit buffer (Bi-Di)	£2.10		
SC/MP Microprocessor chip	£14.50	Power Supply P297 [+5, -5, -12] Kit form	£11.50
		Floppy disks SA400 Mini/floppy	£495.00
		Floppy disks SA800 Standard	£625.00

### BOOKS AND DATA

SC/MP Technical Description	£1.95
SC/MP Programmers Guide	£6.30
SC/MP Applications Guide	£2.95
SCRUMPI Data Sheets	£0.75
FB Data (Xerox)	£0.75

All prices exclude VAT at 8%

Oi loikes SCRUMPI

Don't let the grass grow under your feet!

SCRUMPI Bywood's Evaluation Kit for the SC/MP Microprocessor chip

Kit contains—

SC/MP MPU 40 pin DIL IC.  
 256 x 8 bit RAM chips.  
 2 four bit I/O latches.  
 24 LED lamps and drivers.  
 16 Data and Control switches.  
 PCB, IC sockets, cable, caps, Resistors, etc. Requires simple Power Supply.

The switches allow you to enter a program into the RAM and then exec that program, several operating modes allow for ease of testing. SCRUMPI can be extended to address up to 64K bytes and can be inter-faced to ROM, PROM, RAM, EAROM or many types of I/O device. SCRUMPI can also be used to replace a SC/MP in another circuit to give full in-circuit testing facilities.

SCRUMPI KIT £64.81 plus VAT



### LATEST ADDITIONS

**FLOPPY DATA.** Set of manuals for SA 400 Mini-Floppy, includes circuit diagrams, interface circuits, timing data, etc. Set **£8.00** (No VAT).  
**DM81L597 8 bit Tri-State Buffer** **£1.60**

## CLOCK CHIPS & KITS

TYPE	SPECIAL FEATURES	£CHIP	£KIT
MM5309	7seg + BCD. RESET ZERO	6.50	8.80
MM5311	7seg + BCD	6.50	8.80
MM5312	7seg + BCD 4 DIGIT ONLY	5.65	
MM5313	7 seg + BCD	6.50	
MM5314	7seg + BASIC CLOCK	4.88	7.00
MM5315	7 seg + BCD REST ZERO	£6.50	
MM5316	Non-mpx ALARM	10.17	
MM5318	7seg + BCD External digit select	4.10	8.00
MM5371	ALARM. 50Hz	10.15	
MM5377	CAR clock. Crystal control. LCD	8.40	
MM5378	CAR clock. Crystal control. LED	7.55	14.00
MM5379	CAR clock. Crystal control. Gas discharge	7.55	
MK5025	ALARM. SNOOZE	5.60	9.00
MK50395UP	/DOWN Counter — 6 Decade	12.10	15.10
MK50396UP	/DOWN Counter—HHMMSS	12.10	15.10
MK50397UP	/DOWN Counter—MMSS.99	12.10	15.10
FCM7001	ALARM. SNZ. CALENDER. 7seg	9.00	12.50
FCM7002	ALARM. SNZ. CALENDER. BCD	9.00	
CT7003	ALARM. SNZ. CALENDER. Gas discharge	9.00	
FCM7004	ALARM. SNZ. CALENDER. 7seg	9.00	12.50
AY5 1202	7seg. 4 digit	4.76	
AY5 1230	7seg. ON and OFF ALARM	5.25	TBA

All above clock kits include clock PC board, clock chip, socket and CA3081 driver IC. MH15378 also includes crystal and trimmers. When ordering kit, please use prefix MHI, e.g. MHI 5309.

## OLDE CLOCKS

In kit form or built these clocks are based on designs hundreds of years old. Wood stone and iron are used to reproduce authentic "olde worlde" wall clocks in full detail. The kits contain all you need including glue, screws, etc. and very comprehensive instructions. Stones for weights are excluded.

PRICES		KIT	BUILT
Gothic Clock	Diam 6 1/2"	26.95	42.00
Rotating Dial	Diam 6"	23.50	39.50
Wrought Iron	Diam 5 1/2"	54.25	79.95
Wooden Wheel	Diam 6 1/2"	36.95	52.00
Knight Clock	7 1/2"	48.50	77.50
Oak Foliot	Diam 14"	123.95	145.00

For coloured brochure please send 15p stamps

## DISPLAYS

		Litronix class 2 product	
DL707, 704, 701 0.3"	1.48	DL707E	0.70
DL727, 728, 721 0.5" (2 dig.)	3.75	DL727E (2 dig)	1.80
DL747, 750, 746, 0.6"	2.45	DL747E	1.50

## MHI DISPLAY KITS

MHI707/4 digit 0.3"	6.60	MHI707E/4	3.50
MHI707/6	9.50	MHI707E/6	4.50
MHI727/4 0.5"	8.50	MHI727E/4	4.50
MHI727/6	12.00	MHI727E/6	6.00
MHI747/4 0.6"	9.80	MHI747E/4	6.00
MHI747/6	14.70	MHI747E/6	8.10

Any one or two of the above MHI display kits will interface directly with any of the MHI clock kits.

## CASES (with perspex screen)

VERO 1. 8" x 5 1/2" x 3"	3.00
VERO 2. 6" x 3 1/4" x 2 1/4"	3.00

## SOCKETS

24, 28 or 40 pin	0.60
Soldercon strip skts, 50 pins	0.30

## CLOCK MODULES

MA1002F (12Hr) or MA1002H (24Hr) with Alarm	
Module only	7.97
MTX1001 transformer	0.90
Kit including case	13.00

## PAYMENT TERMS

Cash with order. Access, Barclaycard (simply quote your number). Credit facilities to accredited account holders. 15% handling charge on goods ordered and paid for then cancelled by customer.

All prices exclude 8% VAT

PLEASE SEND 30p POST AND PACKING



# BYWOOD

BYWOOD ELECTRONICS  
 68 Ebbens Road  
 Hemel Hempstead  
 Herts HP3 9QR  
 Tel. 0442 62757

# Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD. DEPT. E.T.I.  
LONDON — 40-42 Cricklewood Broadway, NW2 3ET  
Tel. 01-452 0161 Telex 21492

GLASGOW — 85 West Regent Street, G2 2QD  
Tel. 041-332 4133

BRISTOL — 1 Straits Parade, Fishponds Rd. BS16 2LX  
Tel. 0272 65420†

**NEW 1977  
CATALOGUE**

**168  
PAGES**

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome. Catalogue price 55p post paid 40p to callers.

## SEE US AT THE ALL ELECTRONIC SHOW GROSVENOR HOUSE 19-21 APRIL

Top 600 Semiconductors from the largest range in the UK — all devices manufacturers' branded stock from, Texas, National, Mullard, Motorola, RCA, Siemens.

2N696 0.35	2N3704 0.15	40362 0.48	BC161 0.50	BD135 0.37	BFX99 1.25	CA3020 1.78	LM3301N 0.85	TAA661B 1.32
2N697 0.30	2N3705 0.15	40363 1.20	BC167 0.12	BD136 0.34	BFY50 0.34	CA3020A 2.29	LM3302N 1.40	TAA700 3.81
2N698 0.62	2N3706 0.16	40406 0.58	BC168 0.12	BD137 0.38	BFY51 0.38	CA3020B 1.29	LM3401 0.70	TAA930A 1.00
2N699 0.55	2N3707 0.18	40407 0.45	BC169 0.12	BD138 0.38	BFY52 0.36	CA3028B 1.01	LM3900 0.70	TAA930B 1.05
2N706 0.24	2N3708 0.16	40408 0.65	BC170 0.16	BD139 0.40	BFY53 0.34	CA3030 1.24	LM3905 1.60	TAD100 1.95
2N706A 0.12	2N3709 0.18	40409 0.65	BC171 0.14	BD140 0.40	BFY90 1.37	CA3030A 1.89	LM3909 0.68	TBA120 0.65
2N708 0.21	2N3710 0.16	40410 0.65	BC172 0.12	BD239 0.40	BRV39 0.50	CA3045 1.40	MC1035 1.75	TBA400 1.50
2N709 0.50	2N3711 0.18	40411 2.85	BC173 0.20	BD240 0.45	BSX20 0.31	CA3046 0.89	MC1303 1.47	TBA500 2.21
2N718 0.27	2N3712 1.20	40594 0.75	BC178 0.20	BD241 0.45	BSX21 0.32	CA3048 2.23	MC1304 1.85	TBA500Q 2.30
2N718A 0.50	2N3713 2.30	40595 0.85	BC179 0.23	BD242 0.47	BU105 1.50	CA3049 1.66	MC1305 1.85	TBA510 2.21
2N720A 0.80	2N3714 2.45	40673 0.73	BC182 0.11	BD243 0.60	BU205 2.20	CA3052 1.62	MC1306 1.00	TBA510Q 2.30
2N914 0.35	2N3715 2.55	40674 0.73	BC182L 0.14	BD244 0.62	ME0402 0.20	CA3053 0.60	MC1310 1.91	TBA520 2.31
2N916 0.30	2N3716 2.80	AC127 0.44	BC183 0.11	BD245 0.65	ME0404 0.15	CA3080 0.68	MC1312 1.98	TBA520Q 2.30
2N918 0.38	2N3717 1.85	AC128 0.37	BC183L 0.14	BD246 0.65	ME0412 0.20	CA3080A 1.88	MC1327 1.94	TBA530 1.98
2N929 0.25	2N3718 2.00	AC151V 0.35	BC184 0.14	BD246 0.65	ME0412 0.20	CA3086 0.51	MC1330 0.92	TBA530Q 2.07
2N930 0.26	2N3719 2.90	AC152V 0.50	BC184L 0.14	BD530 0.47	ME4104 0.10	CA3088 1.59	MC1350 1.75	TBA540 2.21
2N1131 0.60	2N3789 2.90	AC153 0.49	BC207 0.12	BDY20 1.13	MJ480 1.35	CA3088 1.59	MC1350 1.75	TBA540Q 2.30
2N1132 0.60	2N3790 3.10	AC153K 0.55	BC208 0.11	BF115 0.38	MJ481 1.55	CA3089 2.52	MC1351 1.20	TBA540Q 2.30
2N1613 0.35	2N3791 3.10	AC176 0.40	BC212 0.14	BF117 0.70	MJ490 1.70	CA3090 3.80	MC1352 0.97	TBA550 3.13
2N1711 0.37	2N3792 3.50	AC176K 0.60	BC212L 0.17	BF121 0.55	MJ491 1.85	CA3130 0.94	MC1357 1.45	TBA550Q 3.22
2N1893 0.38	2N3793 2.50	AC187K 0.55	BC213 0.14	BF123 0.55	MJ2955 1.25	LM301A 0.65	MC1458 0.91	TBA560Q 3.22
2N2102 0.60	2N3794 2.00	AC188K 0.55	BC213L 0.16	BF125 0.25	MJ340 0.58	LM301N 0.44	NE555 1.05	TBA570 1.29
2N218 0.33	2N3820 0.38	AD161 0.85	BC214 0.16	BF153 0.25	MJ370 0.58	LM307N 0.65	NE565 1.20	TBA570 1.29
2N218A 0.37	2N3823 0.75	AD162 0.85	BC214L 0.17	BF154 0.25	MJ371 0.60	LM308C 1.82	NE566 1.85	TBA641B 2.50
2N2219 0.30	2N3904 0.21	AF106 0.55	BC237 0.14	BF159 0.35	MJ520 0.45	LM308N 1.17	NE567 1.60	TBA651 1.80
2N2219A 0.32	2N3906 0.22	AF109 0.75	BC238 0.12	BF160 0.30	MJ521 0.65	LM309N 2.10	NE567 1.60	TBA700 1.52
2N2220 0.35	2N4036 0.67	AF124 0.65	BC239 0.15	BF161 0.60	MJ2955 1.40	LM309N 2.10	SAS560 2.50	TBA700Q 1.61
2N2221 0.22	2N4037 0.55	AF125 0.65	BC253 0.25	BF166 0.40	MJ3055 0.85	LM317N 2.25	SAS570 2.50	TBA720Q 2.30
2N2221A 0.25	2N4058 0.20	AF126 0.65	BC253 0.25	BF167 0.38	MPB11 0.35	LM318N 2.25	76001N 1.57	TBA750 1.98
2N2222 0.25	2N4059 0.20	AF127 0.65	BC257A 0.17	BF173 0.38	MPB12 0.40	LM323K 6.40	76003N 2.55	TBA750Q 2.07
2N2222A 0.25	2N4060 0.20	AF139 0.69	BC258A 0.17	BF177 0.30	MPB13 0.45	LM329N 1.75	76008K 2.50	TBA800 1.20
2N2368 0.25	2N4061 0.17	AF186 0.50	BC259B 0.18	BF178 0.35	MPF102 0.30	LM348N 1.91	76013N 1.70	TBA810 1.16
2N2369 0.25	2N4062 0.18	AF200 0.70	BC261A 0.21	BF179 0.35	MPSA05 0.23	LM360N 2.75	76013ND 1.57	TBA820 1.03
2N2369A 0.25	2N4126 0.17	AF239 0.74	BC262 0.19	BF180 0.40	MPSA06 0.24	LM370N 3.00	76018K 2.50	TBA920 1.79
2N2640 0.75	2N4270 0.20	AF240 0.15	BC263C 0.24	BF181 0.40	MPSA12 0.35	LM371N 2.25	76023ND 1.57	TBA920Q 2.99
2N2647 1.40	2N4919 0.65	AF279 0.80	BC263C 0.24	BF182 0.45	MPSA55 0.24	LM372N 2.15	76033N 2.55	TBA940 1.62
2N2904 0.36	2N4920 0.70	AF280 0.85	BC301 0.45	BF183 0.45	MPSA56 0.24	LM373N 2.25	76110N 1.46	TCA160C 1.85
2N2904A 0.37	2N4921 0.50	BC107 0.15	BC303 0.60	BF184 0.38	MPSU05 0.60	LM374N 2.25	76114N 1.87	TCA160B 1.61
2N2905 0.37	2N4922 0.55	BC108 0.15	BC307 0.25	BF185 0.35	MPSU06 0.56	LM377N 1.75	76116N 2.06	TCA270 2.25
2N2905A 0.38	2N4923 0.70	BC109 0.15	BC307 0.25	BF186 0.40	MPSU06 0.56	LM378N 2.25	76131N 1.30	TCA280A 1.30
2N2906 0.28	2N5190 0.60	BC113 0.17	BC309C 0.20	BF195 0.13	MPSU55 0.60	LM379N 2.95	76228N 1.94	TCA290A 3.13
2N2906A 0.25	2N5191 0.70	BC115 0.19	BC317 0.14	BF196 0.14	TIP29A 0.45	LM380N 0.98	76227N 1.51	TCA420A 1.84
2N2907 0.21	2N5192 0.75	BC116 0.19	BC318 0.12	BF197 0.17	TIP30A 0.49	LM380N 0.98	76228N 1.51	TCA730 3.22
2N2907A 0.22	2N5195 0.90	BC116A 0.20	BC327 0.20	BF198 0.18	TIP31A 0.50	LM381A 2.45	76530N 0.91	TCA740 2.76
2N2924 0.15	2N5245 0.35	BC117 0.22	BC328 0.19	BF199 0.18	TIP32A 0.50	LM381N 1.60	76532N 1.50	TCA750 2.30
2N2926 0.13	2N5294 0.40	BC118 0.16	BC337 0.19	BF200 0.25	TIP33A 0.50	LM382N 1.25	76533N 1.00	TCA760 1.38
2N3019 0.55	2N5295 0.40	BC119 0.16	BC338 0.21	BF244 0.35	TIP34A 0.50	LM384N 1.44	76544N 1.44	TCA800 3.13
2N3053 0.30	2N5296 0.40	BC121 0.45	BC347 0.12	BF245 0.34	TIP35A 2.90	LM386N 0.80	76545N 2.09	UAA100 2.00
2N3054 0.60	2N5298 0.40	BC132 0.30	BC348 0.12	BF246 0.75	TIP36A 3.75	LM387N 1.05	76546N 1.44	UAA150 2.00
2N3055 0.70	2N5447 0.15	BC134 0.15	BC349 0.13	BF254 0.24	TIP41A 0.30	LM388N 1.00	76550N 0.41	
2N3390 0.25	2N5448 0.15	BC135 0.15	BC350 1.03	BF255 0.37	TIP42A 0.60	LM389N 1.00	76552N 0.65	
2N3391 0.25	2N5449 0.19	BC136 0.19	BCY31 1.06	BF257 0.37	TIP29c 0.60	LM702C 0.75	76570N 2.08	
2N3391A 0.25	2N5457 0.32	BC137 0.14	BCY32 1.20	BF258 0.45	TIP30c 0.65	LM709C 0.65	76620N 1.10	
2N3392 0.16	2N5458 0.33	BC140 0.40	BCY33 1.00	BF259 0.49	TIP31c 0.66	LM709N 0.65	76650N 1.10	
2N3393 0.15	2N5459 0.29	BC141 0.45	BCY34 1.20	BF459 0.45	TIP32c 0.75	LM710C 0.60	76660N 0.60	
2N3394 0.15	2N5484 0.34	BC142 0.30	BCY38 2.00	BFR39 0.28	TIP33c 1.10	LM710N 0.60	76666N 0.92	
2N3439 0.88	2N5486 0.38	BC143 0.30	BCY42 0.80	BF259 0.28	TIP34c 1.20	LM723C 0.85	TAA301A 1.50	
2N3440 0.64	2N6021 0.72	BC147 0.12	BCY58 0.25	BF225 1.04	TIP34c 1.20	LM729N 0.75	TAA320A 1.50	
2N3441 0.85	2N6101 0.65	BC148 0.12	BCY59 0.25	BF561 0.30	TIP42c 0.95	LM741C 0.65	TAA350A 2.48	
2N3442 1.35	2N6107 0.42	BC149 0.13	BCY70 0.25	BF598 0.27	TIP2955 0.85	LM741N 0.50	TAA521 1.00	
2N3638 0.16	2N6109 0.42	BC153 0.27	BCY71 0.26	BFX29 0.38	TIP3055 0.55	LM741R 0.40	TAA522 1.90	
2N3638A 0.16	2N6121 0.38	BC154 0.27	BCY72 0.24	BFX30 0.40	TIS43 0.30	LM747N 0.90	TAA550 0.60	
2N3639 0.30	2N6122 0.41	BC157 0.12	BD115 1.20	BFX40 0.40		LM748N 0.50	TAA560 1.60	
2N3641 0.20	2N6123 0.43	BC158 0.11	BD116 1.20	BFX41 0.40		LM748B 0.50	TAA570 2.30	
2N3702 0.17	2N6126 0.45	BC159 0.14	BD131 0.51	BFX87 0.40		LM1800 1.76	TAA611B 1.85	
2N3703 0.15	40361 0.45	BC160 0.50	BD132 0.54	BFX88 0.40		LM1808 1.92	TAA621 2.15	
						LM1828 1.75	TAA661A 1.32	

### CLOCK MODULES

MA1002F 12hr 5" display	11.90
MA1002H 24hr 5" display	11.90
MA1010E 12hr 84" display	17.00
MA1010G 24hr 84" display	17.00

Transformers £1.50

### CAR CLOCK MODULE

Built and tested — Crystal Controlled — 12 volt supply  
Easily installed — DIMS 3x1 75ins with 4 digit 3ms display  
Type MA 1003 Module — price £17.50 + VAT  
Data Sheet 5p + SAE

### TRIACS

4 amp	0.70	10 amp	0.90
6 amp	0.75	12 amp	1.10
8 amp	0.80	16 amp	1.60

### THYRISTORS

5 amp 100V	0.35	8 amp 100V	0.43
5 amp 200V	0.40	8 amp 200V	0.49
5 amp 400V	0.49	8 amp 400V	0.62

### BRIDGE RECTIFIERS

W05	0.30	BY164	0.57
W01	0.32	840C1500	0.48
W02	0.34	840C3200	1.10
W04	0.40	880C1500	0.75
W06	0.50	880C3200	1.15

## SEE MARSHALL'S FOR CMOS

CD4000 0.24	CD4018 1.15	CD4042 0.96
CD4001 0.24	CD4019 1.15	CD4043 1.15
CD4002 0.24	CD4020 1.27	CD4044 1.06
CD4006 1.34	CD4021 1.15	CD4045 1.59
CD4007 0.24	CD4022 1.10	CD4046 1.52
CD4008 0.10	CD4023 0.24	CD4047 1.15
CD4009 0.64	CD4024 0.84	CD4048 0.64
CD4010 0.64	CD4025 0.24	CD4050 0.64
CD4011 0.24	CD4026 0.64	CD4510 1.56
CD4012 0.24	CD4028 1.02	CD4511 1.79
CD4013 0.64	CD4029 1.30	CD4516 1.56
CD4014 1.15	CD4030 0.64	CD4518 1.43
CD4015 1.15	CD4031 2.53	CD4520 1

# The challenge of

# I<sup>2</sup>L

A FEW YEARS AGO THERE WAS one principal technique used in the manufacture of logic circuits, namely TTL or Transistor-Transistor Logic. Devices using this technology have the advantage of being able to switch very quickly, but they are not suitable for applications like electronic watches where the logic circuits must consume very little power and occupy the minimum possible area on the silicon chip.

The development of the Complementary Metal Oxide Semiconductor technology known as CMOS (or COS/MOS) by RCA about 1970 provided devices which have an extremely high component packing density on the silicon chip and which operate at a very low quiescent current. The complementary MOS field effect transistors used in CMOS devices take appreciable current only for the time taken to switch logic states. Silicon-on-sapphire is a variation of the basic CMOS technology which offers relatively high speeds of operation, but at the present time such devices are expensive to manufacture.

## I<sup>2</sup>L

Integrated injection logic or I<sup>2</sup>L now provides serious competition to CMOS circuits where minimum current and high component packing density is required. Devices using I<sup>2</sup>L circuitry can be produced very economically and the speed of operation rivals that of TTL.

I<sup>2</sup>L is being used for mass production of LSI ICs, but little has been said about the theory behind this new technology.

In this article Brian Dance explains how it works...

This new technology is being used by some of the major semiconductor manufacturers for products ranging from microprocessors to quartz-controlled electronic watch devices. All I<sup>2</sup>L devices are large scale integration LSI products — they contain a very large number of components on a single silicon chip.

I<sup>2</sup>L was developed quite separately (in Europe) by Philips and IBM around 1972. It employs bipolar devices (that is, devices like conventional transistors rather than FETs) in circuits which have been derived from the early DCTL (Direct Coupled Transistor Logic). It is only quite recently that developments

in the I<sup>2</sup>L production processes have made this circuit technique economically attractive.

A DCTL circuit is shown in Fig. 1. Three transistors are shown in each of the three NOR gates with the output of Gate 1 feeding one of the inputs of both gates 2 and 3. Other connections, which are not shown, are made to the other inputs of the gates. Circuits of this type were used in simple SSI (small scale integration) devices, but suffered from the disadvantage that the current was unequally divided among the transistors in any one gate owing to minor differences in their base-emitter voltages. In addition, the load resistor had to be separated from the transistors and this used up a considerable area of the chip.

Note that in the circuit of Fig. 1 there are direct connections between corresponding regions of the transistors: all of the emitters are joined together, whilst the two bases which are driven from the collectors of gate 1 are common. The current to these bases passes through the load resistor of the gate 1 circuit. In an I<sup>2</sup>L circuit, these common electrodes share the same area on the chip.

A cross section through an I<sup>2</sup>L gate is shown in Fig. 2 and the circuit is shown in Fig. 3. A single pnp transistor is employed as a current source to supply current to many transistor bases without the use of a load resistor. The whole of the emitter region is a

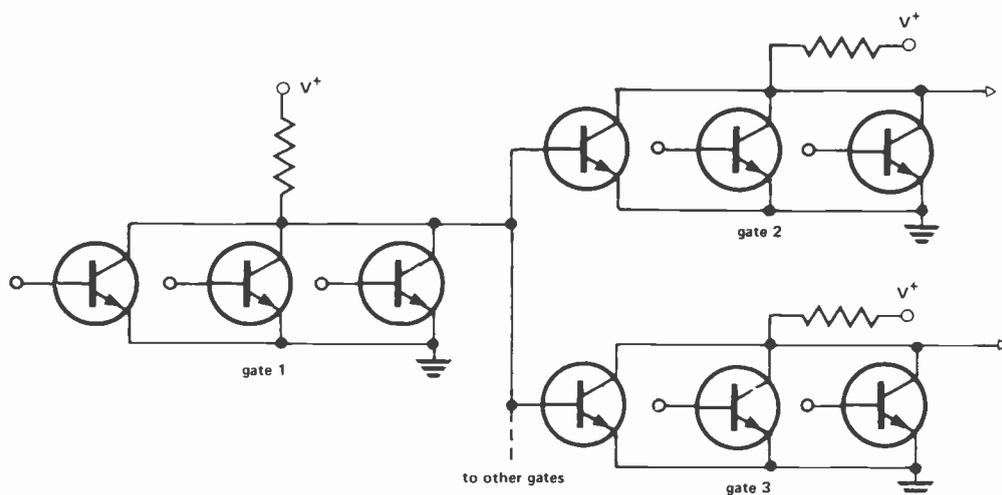


Fig. 1. A Direct Coupled Transistor Logic circuit (DCTL).

# The challenge of I<sup>2</sup>L

common one beneath the surface structure on the chip. This eliminates the need for surface metallisation for each separate ground connection. In addition, the area required per transistor is greatly reduced. IBM initially used the name Merged Transistor Logic (MTL) instead of I<sup>2</sup>L.

It should be noted that the pnp transistor is formed laterally along the surface of the silicon chip. The other component is a multi-collector npn transistor characteristic of I<sup>2</sup>L devices. However, this npn transistor is formed vertically in the silicon. The n-type epitaxial layer acts as the grounded emitter of the npn transistor and also as the grounded base of the lateral pnp device. The p-type base of the multi-collector transistor also serves as the collector of the pnp device. Thus the two devices do not exist as separate structures.

## Injection

The pnp transistor 'injects' current into the base of the multi-collector transistor — hence the name Integrated Injection Logic. Current from a current source (not shown in Fig. 3) passes to the emitter of the pnp transistor and hence to the collector. Switching of the logic state occurs when this current is switched to or from the base of the multi-collector transistor.

If the input at the base of the multi-collector transistor is low (less than about +0.7 V), this potential will be inadequate to overcome the natural forward junction potential of the npn base-emitter junction and the npn device will be non-conducting. The injected current will flow out of the input connection to the collector of the previous circuit (not shown in Fig. 3). The multi-collector transistor outputs will therefore rise to the 'high' logic level, this voltage being determined by the collector circuitry.

If the input voltage now becomes 'high' (that is, over +0.75 V), the npn transistor will be biased to saturation and the output of the collector will be 'low'. This low value can be about 0.02 V. Thus the change of the logic level is represented by a voltage swing of around 0.7 V.

## Power Supply

The positive power supply line of I<sup>2</sup>L circuits is connected only to the emitters of the pnp injection transistors. The base of these transistors is earthed, so the I<sup>2</sup>L circuit as viewed from the

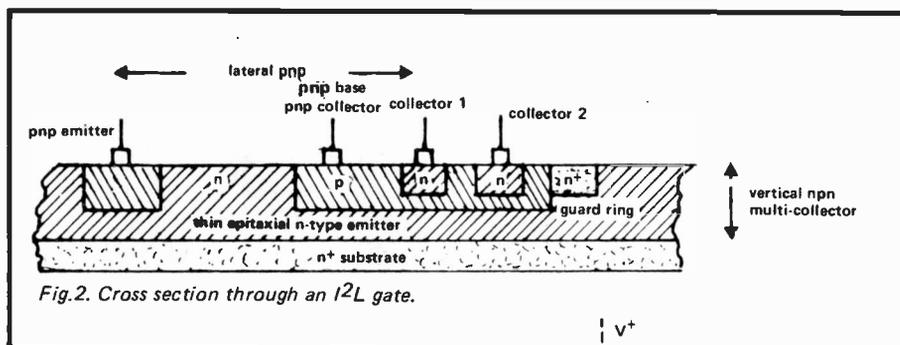


Fig. 2. Cross section through an I<sup>2</sup>L gate.

power supply line is effectively just a forward-biased silicon diode. The total power supply current is therefore the sum of the currents fed to the injection transistor emitters.

The voltage levels in I<sup>2</sup>L circuits can be very low; indeed, such circuits can operate from a supply of 0.85 V upwards. The supply current per gate can be very low (about 1 nA), but the injected current can be increased in value up to about 1 mA to permit switching of the circuit at a much higher speed.

Although the I<sup>2</sup>L circuits can operate at such low voltages, the input and output circuits normally included in the same package require a higher supply voltage and their requirements normally determine the operating voltage of the whole device. A series voltage-dropping resistor is used in the power supply line of some I<sup>2</sup>L devices, whilst other devices incorporate a voltage regulator on the chip to eliminate the need for an external resistor.

The use of an internal regulator circuit also enables various injector current levels to be obtained at different points in the circuit so that each part can operate at the minimum power level for the switching speed required by that particular part. For example, the fast frequency dividing circuits of a quartz controlled watch can operate at a high injection current for a satisfactory performance at 32 kHz, whereas the following frequency dividing circuits operating at a low frequency can use lower injection current levels. The increased cost of fabricating such circuits may be well worth while when current consumption must be minimised.

In many applications a single dry cell can be an ideal power source for I<sup>2</sup>L circuitry.

A guard ring of n+ material (shown in Fig. 2) is required in I<sup>2</sup>L devices to reduce cross-talk between adjacent

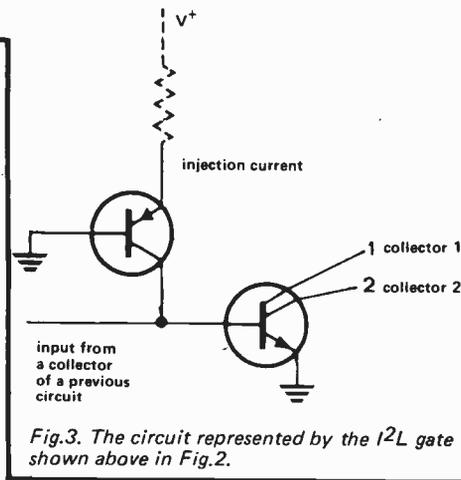


Fig. 3. The circuit represented by the I<sup>2</sup>L gate shown above in Fig. 2.

gates. However, this ring can touch the base of the npn device and it occupies little surface area.

## Gates

I<sup>2</sup>L gates can be made by "wire-ORing" the isolated collector outputs as shown in Fig. 4. Similarly NAND gates can be made by using the multiple collector outputs of the npn transistor connected as shown in Fig. 5.

## Input/Output Circuits

I<sup>2</sup>L is almost always used in conjunction with other circuitry. The voltage change when an I<sup>2</sup>L circuit switches is only about 0.7 V at current levels which may be very low. If the inputs and outputs of the I<sup>2</sup>L circuits were brought out directly to external connecting pins, any small stray noise pulses or interference picked up by the circuit would be likely to trigger the I<sup>2</sup>L circuitry, owing to its great sensitivity to low amplitude pulses.

Buffer interfacing circuits are therefore used between the input and output connections of a device and the I<sup>2</sup>L circuitry itself. A typical input buffer which can accept TTL input pulses and convert them into pulses suitable for the operation of an I<sup>2</sup>L circuit is shown in Fig. 6. The input buffer circuit used with some of the older logic systems can be even simpler.

## Discovery of I<sup>2</sup>L

The discovery of I<sup>2</sup>L is quite a story in itself. Horst H. Berger and Siegfried K. Wiedmann of the IBM Boeblingen Laboratory in Germany reported on their MTL (or I<sup>2</sup>L) circuitry at the International Solid State Conference in Philadelphia in February 1972. However, the next paper at the Conference was by Cornelius M. Hart and Arie Slob of Philips Research Laboratories of Eindhoven, in which they disclosed details of their I<sup>2</sup>L circuits.

The IBM workers produced their circuit designs after a long, but rational, effort. On the other hand, the Philips workers evolved their basic ideas within a few days in what was essentially a flash of inspiration. Within three months the Philips Laboratories were producing large scale I<sup>2</sup>L chips.

Hart and Slob saw I<sup>2</sup>L from the physicist's point of view in which minority carriers from a p region

were injected into an npn device in order to solve the problem of the high current and large limiting resistors required with conventional bipolar logic. On the other hand, Berger and Wiedmann saw their circuits from the point of view of a circuit designer in which the individual devices on a chip were merged together.

The Philips organisation produced a pocket calculator using I<sup>2</sup>L technology as early as 1971. It contained over 1000 gates in an area of 4x4mm. Even in the first I<sup>2</sup>L chips, the elimination of the physically large resistors and the thermal dissipation in these resistors showed the main advantages of I<sup>2</sup>L technology. Each logical operation required about one picojoule of energy; this may be compared with the estimated value of 0.2 picojoule required to operate the logic cells (the "neurons") of a human brain.



The Sinclair Black Watch was one of the first commercial applications using I<sup>2</sup>L.

## I<sup>2</sup>L

The symbol I<sup>2</sup>L is a trade mark used by the Fairchild Company for their Isoplanar Integrated Injection Logic technology. It is employed in such products as the Fairchild 9408 microprogram sequencer which controls the order in which micro-instructions are fetched from a

control memory having up to 1024 words; it is fully compatible with TTL devices.

### Applications

I<sup>2</sup>L devices are used in such applications as electronic games, frequency synthesisers, microprocessors, high speed calculators,

computer interfaces, counters, timers, telephone switching, tone generators, electronic organs, remote control systems for TV sets, analogue to digital converters, digital voltmeters, vehicle anti-skidding, fuel injection control, etc. In Europe it can be used in the "Teletext" and "Viewdata" decoders.


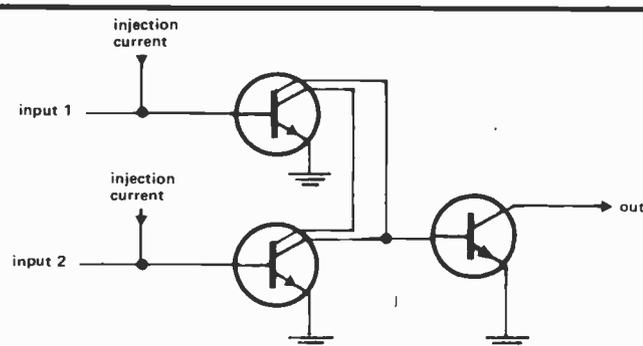


Fig.4. (above). I<sup>2</sup>L gates can be made by 'wire-ORing' the isolated collector outputs.

Fig.5. (right). NAND gates can be made by using the multiple collector outputs of the npn transistor.

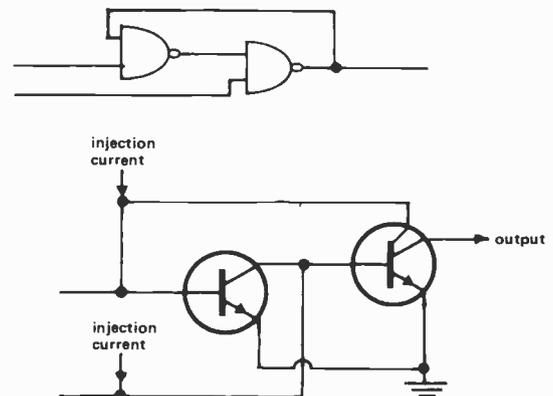

An output buffer circuit which can amplify the low voltage pulses from the output of an I<sup>2</sup>L circuit and provide enough current and voltage to drive a TTL input is shown in Fig. 7.

### Technology Comparison

An I<sup>2</sup>L gate can be made with what is effectively a single component on a chip area about one tenth of that required for a normal three-component CMOS


gate. In addition, I<sup>2</sup>L is one of the most economical technologies used in device fabrication, since the number of masking and diffusion operations on the silicon slices are less than in most comparable techniques.

One of the advantages of I<sup>2</sup>L technology is that it is so very similar to that of other standard linear and Schottky TTL manufacturing processes that it is easy to fabricate other types of

component on the same chip. For example, light emitting diode driver circuits can be built on the same chip as I<sup>2</sup>L circuitry; this enables a single chip to be used to drive the display of a watch or a calculator as well as to carry out the required logic operations. Operational amplifiers, oscillators, voltage regulators, etc. can be fabricated on chips containing I<sup>2</sup>L circuitry.

The CMOS process is essentially

# The challenge of I<sup>2</sup>L

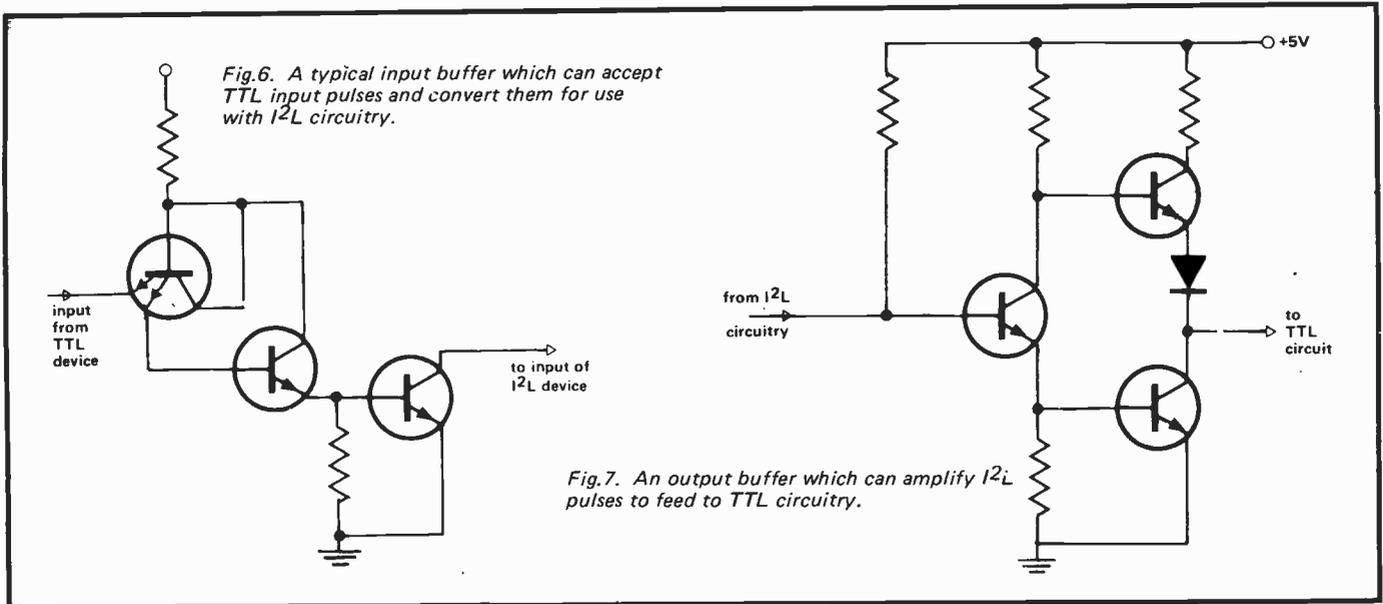

suitable only for the production of purely digital devices, although simple devices such as transistors and diodes can be fabricated on the chip. In contrast, Schottky TTL devices can be combined with I<sup>2</sup>L circuits on a single chip to produce products which are faster and which have higher component densities than can be achieved in other ways. The Texas Instruments SN74S201 and SN74S301 256 bit random access memories are examples of such products.

The power consumption of I<sup>2</sup>L circuits increases linearly with the speed of operation required and in practice you can use the minimum injection current required for maximum speed at which the circuits will ever operate. CMOS circuits consume very little power in the quiescent state, but the power required increases with the switching speed. Thus no circuit adjustments or settings need be made if

minimum power consumption is important and the maximum operating speed is always available. In other words, CMOS circuits always consume minimum power at low operating speeds, but have a high speed capability "on demand" whereas I<sup>2</sup>L circuits must be adjusted for low power or high speed or some intermediate value of power consumption and speed.

I<sup>2</sup>L is faster than CMOS, whilst Schottky-clamped I<sup>2</sup>L is even faster still. The silicon-on-sapphire version of CMOS is another way of obtaining faster logic devices, but emitter coupled logic (ECL) offers the highest speed at the expense of ease of use.

The susceptibility of I<sup>2</sup>L devices to noise pulses has already been mentioned. CMOS devices require input pulses with an amplitude of about half the supply voltage used and are therefore very resistant to spurious operation by stray

noise pulses. It is difficult to see how future I<sup>2</sup>L can be fabricated without input and output buffer circuitry because of the noise problem.

A comparison between the various logic systems is given in Table 1.

## Applications

I<sup>2</sup>L is employed in a wide range of applications which require large scale integration. It is unsuitable for making devices with only a few gates, so it seems most unlikely that simple I<sup>2</sup>L logic devices will become available (like those one meets using CMOS and TTL technologies).

I<sup>2</sup>L devices are expected to have a wide range of applications in the computer field. Although most of the larger semiconductor manufacturers are considering whether to become involved in I<sup>2</sup>L device manufacture, a few (such as Texas Instruments) are already producing devices in quantity. The SBPO400, for example, is Texas' 4-bit parallel binary processor element in I<sup>2</sup>L. I<sup>2</sup>L computer and microprocessor devices satisfy fairly high speed requirements, but they meet competition from fast versions of CMOS and silicon-on-sapphire devices.

I<sup>2</sup>L technology is likely to be used in many consumer applications where its relatively low price is a vital factor. ITT are already producing their ITT 7170 device in England for the Sinclair "Black Watch" which is a very economical product. The 7170 chip incorporates over 2000 transistors on a piece of silicon only 3mm by 3mm in area. It is used in the first watch to

Table 1. A Comparison of TTL, CMOS and I<sup>2</sup>L

Type of logic	Packing density (Gates/mm <sup>2</sup> )	Typical Quiescent dissipation per gate	Typical Dissipation per gate at 1 MHz	Logic voltage swing
I <sup>2</sup> L	140 to 220	5 nW	100 μW	0.7 V
CMOS	70 - 80	5 nW	150 μW	Varies with supply voltage
TTL	20	10 mW	10 mW	3.5 V



<p><b>MARCONI TF675F</b> <b>WIDE RANGE</b> <b>PULSE GENERATOR</b> + / - variable outputs up to 50V. Optional delay. Small compact unit. <b>£18 each</b></p>	<p><b>AVO VALVE TESTER</b> <b>CT160</b> <b>"THE SUITCASE"</b> Size approx. 15" wide x 10" high x 11" deep. Limited quantity <b>£25 each</b></p>	<p><b>MARCONI NOISE</b> <b>GENERATOR</b> <b>TF987/1</b> 4 Ranges 0-5; 0-10; 0-15; 0-30. <b>ONLY £15 each</b></p>	<p><b>AVO TRANSISTOR</b> <b>ANALYSER CT446</b> Suitcase style. <b>NOW £27.50 each</b></p>
---	---	--	---

<p><b>HONEYWELL MAGNETIC TAPE UNITS</b> Self-contained, complete with heads, magnetic tape, leads, etc. Tested. Carriage paid <b>£57.50</b></p>	<p><b>WE ARE BREAKING COMPUTERS</b> <b>UNIVAC/HONEYWELL/ICL 1900 etc.</b> Boards, Power Supplies, Core Stores and many other items available. <b>CALL AND SEE</b> Spools of 1/2" Mag Tape approx. 2000 ft <b>50p each. P.P. £1</b></p>	<p><b>FOR THE VDU BUILDER</b> New stock of Large Rectangular Screen 30 x 20cm tube Type M38 at the ridiculous price of <b>£4 ea.</b> And also still available the CME1220, 24 x 15cm at <b>£9 ea.</b> Base connections for both tubes supplied.</p>
---	--	---

<p><b>TRANSFORMERS — All 240V 50HZ</b> Inputs Type A. 170-17V 250MA; 7.5-0-7.5V 250MA; 0-20V 5 Amps; 0-4V 5 Amps; 0-1-1.5V 5 Amps <b>£2 each</b>; P&amp;P £1.25. Type B 17-0-17V 250MA; 8-0-8V 250MA; 0-12 5-13.5V 5 Amps; 0-1.5-2V 5 Amps <b>£1.50 ea.</b> P&amp;P £1. Type C. 19-0-19V 250MA; 8-0-8V 250MA 0-7.5V 5 Amps; 0-1 4V 5 Amps <b>£1.25 ea.</b> P&amp;P £1.25. Type E. 3V 1 Amp <b>25p ea.</b> P&amp;P 50p. Type G 20-0-20V 200MA; 0-6V 100MA <b>75p ea.</b> P&amp;P 75p. Atlantic series. All brand new (APT surplus types A, B, C, Honeywell surplus type E, Parmeko Atlantic Series type G). *<b>POT PACK.</b> All Brand New Modern. Single and Ganged. Our choice. <b>7 for 25p.</b> P&amp;P 48p. <b>SEMICONDUCTORS —</b> Now all at <b>5p ea.</b> * P&amp;P extra. Guaranteed all full spec. devices. Manufacturer's markings: BC147; 2N3707; BC107; BF197; BC327; 2N4403; BC172B; BC261B; BC251B; BC348B; BC171A/B; BF183; BC108; 2N5879 with 2N5881 Motorola 150 Watt.</p>	<p>Comp. pair <b>£2 pr.</b> P&amp;P 15p. *Linear Amp 709 <b>25p ea.</b> P&amp;P 8p. *<b>TTL 7475 15p ea.</b> <b>VARIACS</b> 240V input 0-230V output 8 amp <b>£18 ea.</b>; 20 amp <b>£30 ea.</b> Carr. extra. <b>TUBES.</b> All Brand New Boxed. Electrostatic deflection. Type DB7/36 3" dia. (Replacement for Telequipment S31) <b>£11 ea.</b> P&amp;P £1.50 Type GEC 924F 3 1/2" dia. (Replacement for Telequipment D33 &amp; Solartron 1016 scopes) <b>£25 ea.</b> P&amp;P £1.50. Type GEC 924E 3 1/2" dia. (Replacement for Solartron 1015 scope) <b>£17.50 ea.</b> P&amp;P £1.50. <b>FIBREGLASS BOARD PACK.</b> More board — less money. Larger pieces. Not less than 2.5 sq. ft. for <b>95p.</b> P&amp;P 65p. <b>NEW — UPGRADED CONTENTS — FOR LESS MONEY</b> *31b Electronic Goodies <b>£1.60</b> post paid. *High Value Printed Board Pack — hundreds of components, transistors, etc. — no flat to the board transistors <b>£1.65</b> post paid. <b>VERY SPECIAL PRICES</b> *1000F Feed thru Capacitors <b>10 for 30p.</b> P&amp;P 15p.</p>	<p>*<b>BEEHIVE TRIMMERS</b> 3/30pf. BRAND NEW. 10 off <b>40p</b> P&amp;P 15p; 100 off <b>£3.50</b> P&amp;P 75p; 500 off <b>£15</b> P&amp;P £1.25; 1,000 off <b>£25</b> P&amp;P £1.50. <b>PHOTOMULTIPLIER</b> Type 931A <b>£4 ea.</b> P&amp;P 75p. Other types available. <b>HIVAC</b> Miniature NEONS App. 60V Brand New. 10 off <b>20p.</b> P&amp;P extra. *<b>Meter PACKS —</b> 3 different meters <b>£2.</b> P&amp;P £1. <b>DON'T FORGET YOUR MANUALS.</b> S.A.E. with requirements. <b>GRATICULES</b> 12 x 14 cm. high quality plastic <b>15p ea.</b> P&amp;P 10p. *<b>CAPACITOR</b> Pack. 50. Brand New components only <b>70p.</b> P&amp;P 48p. *<b>TRIMMER PACK.</b> All Brand New. 2 Twin 50/200pf ceramic; 2 Twin 10/60pf ceramic; 2 min. steps with 4 preset 5/20pf on each; 3 air spaced preset 30/100pf on ceramic base <b>25p the lot.</b> P&amp;P 15p. *<b>POTENTIOMETERS —</b> All <b>5p ea.</b> P&amp;P extra. Metal bodied AB Linear. PCB Mount. Brand New 10K single; 100K ganged; 250K ganged; 100K ganged, concentric shafts.</p>	<p><b>LARGE RANGE ELECTROSTATIC VOLTMETERS,</b> from 0.300V; 2" <b>£3;</b> to 20KV Max. General guide 5KV 3 1/2" <b>£5;</b> thereafter <b>£1</b> per KV. P&amp;P 75p. <b>MARCONI TF1101</b> Audio Oscillator. 20c/s to 200k/s. Low distortion. 60dB step attenuator <b>£50 each.</b> * <b>SPECIAL OFFER</b> Guaranteed full spec. devices. Manufacturer's markings. <b>POWER TRANSISTOR</b> 2N3055 <b>40p ea.</b> P&amp;P 8p. * <b>TELEPHONES</b> Post Office Style 746 black or two-tone Grey <b>£6.50 ea.</b> Modern Style 706 Black or two-tone Grey <b>£4.60 ea.</b> older BLACK Style <b>£1.50 ea.</b> All telephones complete with standard dial and bells. P&amp;P all styles 75p ea. handsets complete with 2 inserts and lead <b>£1.75 ea.</b> P&amp;P 65p. <b>OLDER STYLE HANDSET</b> <b>£1 ea.</b> P&amp;P 65p. <b>ROYAL INVERTORS</b> manufactured USA 28V DC input. Output 115V AC 400HZ up to 2KVA. Brand new. Crated <b>£12.50 ea.</b></p>
--	---	---	---

**SUPERB PROFESSIONAL VDU CASES**

Size 23" x 16" x 27" on stands. Hammer grey. BRAND NEW.  
SCHLUMBERGER Surplus **£40 each.** Carriage £2.50.

<p><b>LINE PRINTERS — VARIOUS MODELS</b> <b>£100 each.</b> Carriage £15. <b>MINIATURE — OXLEY PATCH PANELS</b> BRAND NEW — EX DYNAMCO 10 x 10 complete with pins. <b>£10 each.</b> P&amp;P 50p.</p>	<p><b>C.D.C. DISK DRIVES</b> Complete with electronics, power supply etc. condition with Disk Pack. <b>£100 each.</b> Carriage £15.</p>	<p><b>QUANTITY OF CABINETS</b> Approx. 5ft. 6in. and smaller. Computer types — very smart. Prices from <b>£4 to £20</b> dependent on size. Carr. £2.50.</p>
---	---	---

<p><b>SURPLUS — BRAND NEW — REPLACEMENT TUBES FOR DYNAMCO 7100 SERIES OSCILLOSCOPES. TYPE BRIMAR D13-51GH</b> Mesh P.D.A. Transistor Scan. Wide Bandwidth 60MHZ+ Rectangular 6 x 10cm — 1KV EHT. X Sensitivity 15V/CM. Y Sensitivity 6V/CM. Standard heaters. Length 13 1/4". THIS IS A MUST AS A SPARE FOR THE DYNAMCO 7100 SCOPE OR IDEAL FOR THE HIGH QUALITY TRANSISTOR SCOPE BUILDER. <b>At £65 each.</b> Carriage £2.50. Numetal Shields available at £2.50. Also available TUBE type BRIMAR D10/210GH/32. Rectangular 7 x 5cm. Mesh P.D.A. Short 9 1/2". 30MHZ+ Sensitivity X 14V/CM; Y 10V/CM. BRAND NEW at <b>£70 ea.</b> Carriage £2.50.</p>	<p><b>DATA LOGGERS BY DYNAMCO</b> These are BRAND NEW — not finished. They are completed but for the plug-in boards. The case with hinged lid is quite superb and extremely adaptable. It contains as well as the mother board an equally superb Power Supply with the following voltages: +28V; +15V; +5V (2.5A) — this supply is crowbar protected; —5V; —14V; —20V; —24V; —48V and other supplies including auto 110V. This unit supplied in its original cardboard box complete with original manual must be of serious interest to the professional constructor and anyone considering the construction of a micro processor system. Unit size 7 1/2" high x 19" wide x 23" deep. <b>Price £45 each.</b> Carriage £2.50.</p> 
--	---

**LARGE QUANTITY DYNAMCO TEST UNITS**

OSCILLOSCOPE TUBES, RESISTORS, CAPACITORS, TRANSISTORS, PUNCHES, READERS, PATCH PANELS, PATCH PANEL PLUGS, ASSEMBLIES, FERRITE CORES, KNOBS, FREQUENCY COUNTERS, DVM's, SCHLUMBERGER BATTERY PACKS, 74 HUNDRED IC BOARDS, COMPUTER PANELS, FIBREGLASS BOARD, TRANSFORMER C CORES, CITENCO REDUCTION GEARED MOTORS, AB POTENTIOMETERS — VARIOUS VALUES, KEYBOARDS, TUNING CAPACITORS, TRIMMERS, SMOOTHING CAPACITORS and VARIOUS TEST EQUIPMENT including SOME UNFINISHED OSCILLOSCOPES and other ITEMS. Available for your inspection NOW.

**CALL — SEE AND BE TEMPTED**

Minimum Mail Order £2. Excess postage refunded. Unless stated — please add £2.50 carriage to all units. Value added tax not included in prices — goods marked with \* 1 1/2% VAT. otherwise 8% Official orders welcomed. Gov./Educational depts., authorities etc., otherwise cash with order. open 9 a.m. to 5.30 p.m. Mon. to Sat.

**CHILTMHEAD LTD**   
7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel. Reading 582605

## PART 3

# ELECTRONICS

IN THE YEAR  
**2000**

## EVOLUTION OR REVOLUTION

By Peter Sydenham

In this third part, we take a look at the communications systems of the future. These may well include systems which are totally new, not simply extensions of our present methods. These include gravity waves and even ESP.

MAJOR CHANGES THAT COME about in our lifestyle and attitudes are usually the result of basic needs being recognised by some agency that has the resources to bring such changes about. We begin to use new products of technology when both the need emerges and the technological availability to fulfil it is available. Progress can come from either direction: either as technology developed to meet a big enough need or a need being exploited because a new technology has become available. In both instances our society has generally, in the past, helped this process where economic or political gains are to be had. Not all developments are as good as they are promoted to be and many excellent concepts fail to catch on because the cost expended cannot be regained. In too many instances the quality of the promotion given to a new device or technique is the key to its acceptance. In numerous instances the inherent quality of the product is not a factor in people's minds when selection — the act of helping the idea gain a hold — is made. Communication and its off-shoot, entertainment, are

aspects of life which are very susceptible to over-promotional effort (what Dorothy Parker once described as worship of the fecund rate).



In order to extrapolate and, perhaps, predict some breakthroughs in communication method in the future century we can and should look at ideas from the two progress motivations above — what we need and what we could be given.

### The Role of Communication

Communication is needed to enable information to be imparted from one person to another person (Fig. 1). It is the act of passing information from point to point. An energy medium is always needed for information to pass. Some messages mean more than others, even though they may have the same number of words — a phenomenon not definable in scientific terms. We do have a good idea, however, of the carrying capacity, of a given communication channel. To do this we ignore the *meaning* of messages and concentrate on their 'bit' content. On this basis — the Shannon concept —

it is easy to see that facts containing many 'bits' of information will need a communication method having the required 'bit'-carrying capacity — this turns out to be the available frequency bandwidth in electronic communication techniques. Increasing the bandwidth usually means an increase in cost, so many potential communication needs are limited by economic reasons, not technological ability to provide bandwidth. As an example, for cost reasons, we make do with telex and telegram messages written in stilted format doing without the facial and tonal expression of face-to-face communication. A better alternative would be to use a video-link (such as may one day be in widespread use) instead of the teleprinter, though such a thing requires around 10 000 times more bandwidth. Figure 2 shows a unit that has been on trial since 1971.

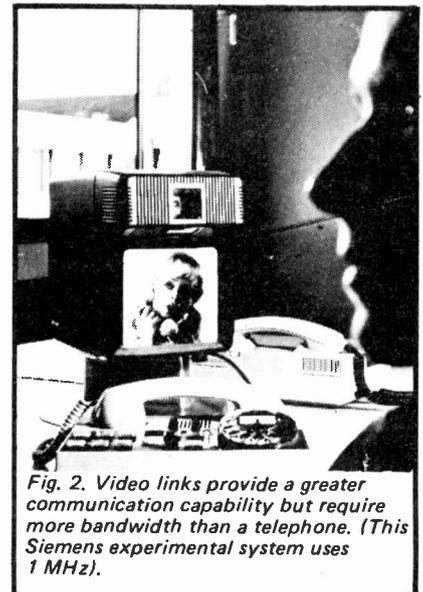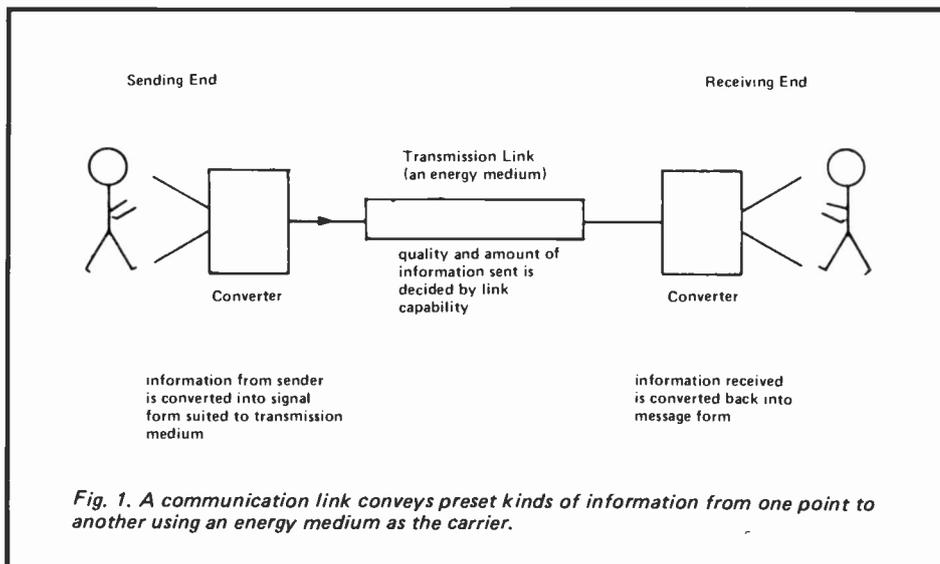The pattern of current civilisation requires people to interact as a living system of coordination, cooperation and coexistence. This means people need to communicate with each other. Usually the closer that a man-made



# Electronics 2000

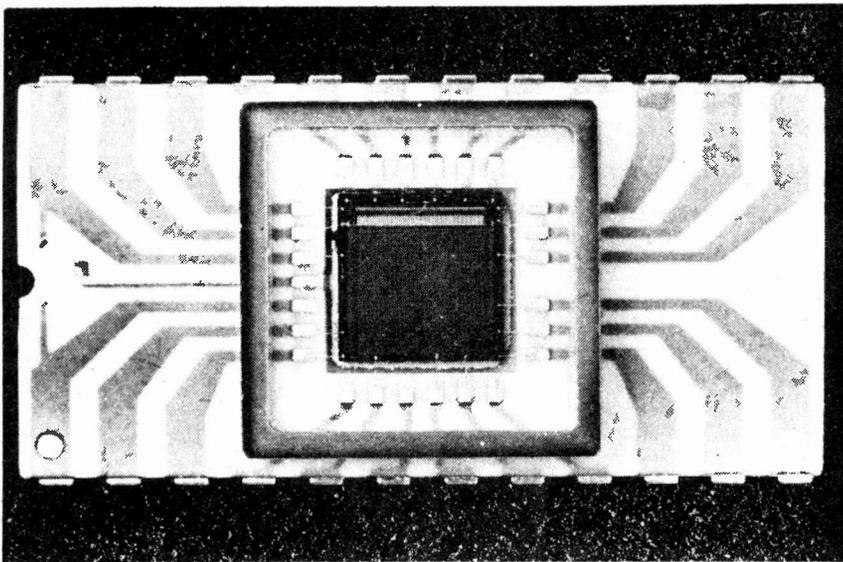


Fig. 3. Solid-state sensing array research is paving the way to tricolour LED panel televisions of the future. This unit has 64 x 64 photo diodes integrated into 6 mm square.

communication link can approach the real face-to-face case the better. Our awareness is enhanced as the simulation provided by the communication link is made more and more a true image of real contact.

Distances, cost and time often make direct communication unrealistic, so technology is brought to bear to reduce the inconveniences. Communication is needed to make commercial and political decisions, to fulfil social needs, to provide education and to entertain. In each of these the hardware

forms are similar — it is the use to which they are put that may influence improvement.

The telephone grew from commercial needs for faster and more informative communication than was offered by telegraphy (which, in itself, was a vast improvement over hand-carried letters) but by contrast television grew because of its consumer market in the entertainment and news media fields. A few video-links have been established but the great operating cost limits them at present more to mass-audience needs,

such as inter-city television interviews, than to telephone replacement.

## Expected Hardware of the Future

The area where greatest development in communications will be seen must be in the forms and use of the domestic television receiver. The receiver itself is sufficiently inexpensive for the majority of people in the developed countries to expect to own a set. We would, therefore, expect little more development on the receiver itself from the point of view of need-induced research.

Styling and operation changes will be prevalent in keeping with promotionally-induced change brought about by manufacturers who must keep seeking markets. Future receivers will most surely incorporate solid-state screens comprising millions of light emitting diodes giving the three primary colours. These screens will be flat and of insignificant thickness — they will be suitable for wall mounting like a picture. The receiving and processing circuits will be integrated onto the same panel. The concept of a television set as a piece of furniture will vanish. This development is currently at the very small monochrome (black and white system) stage — see Fig. 3 — with cameras, rather than displays, being the point of emphasis. The size will gradually increase to acceptable proportions after or during which colour solid-state systems will emerge. The cost of the technology, not its capability, limits this approach at present. IBM have made a 1 m x 1 m area of light sensitive diodes that has close to the current television resolution.

At present, however, the cathode-ray tube method is the only economic technique for generating the picture in a television set.

Because visual experience is in three dimensions, not two, development will not rest with the current 2-D systems. A 3-D cathode ray oscilloscope trace representation was demonstrated back in the 60's using a rotating phosphored disc as shown in Fig.4. Holography using coherent light enables 3-D images to be generated in colour as well as in the usual red experienced when using the helium-neon laser source.

Barriers to the introduction of 3-D television are both cost and the lack of a suitable technique. We have no obviously acceptable systems in existence at present. We can expect the usual period of multiple source development which will generate many alternatives

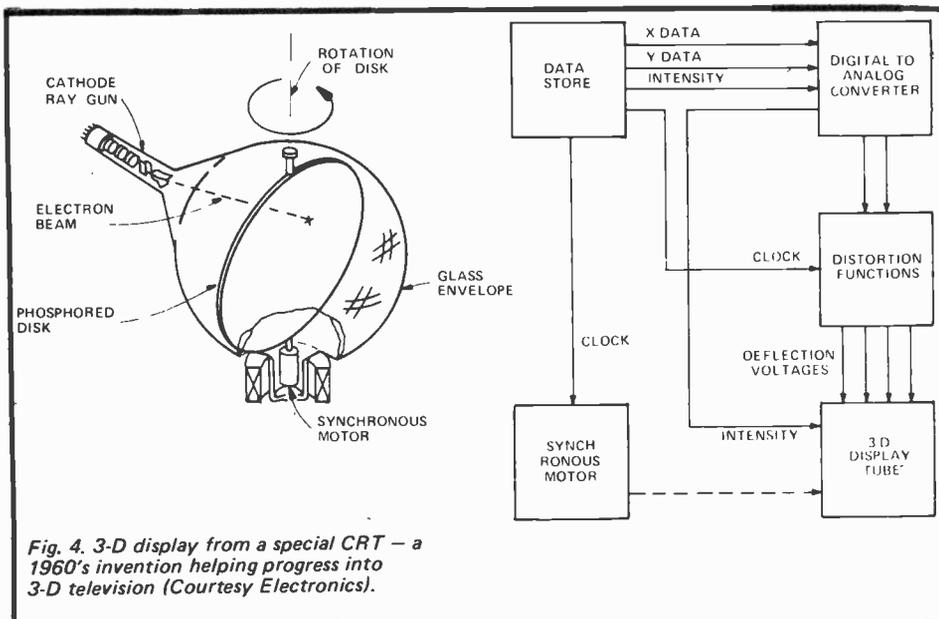


Fig. 4. 3-D display from a special CRT — a 1960's invention helping progress into 3-D television (Courtesy Electronics).

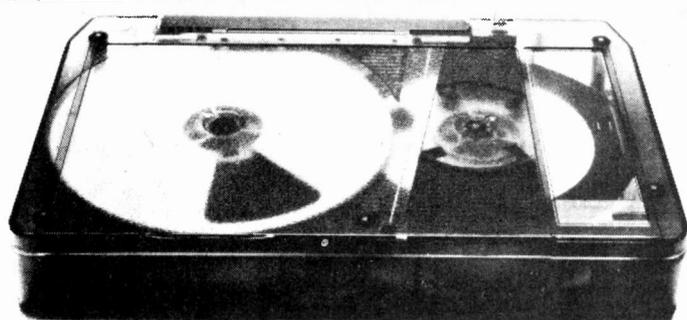
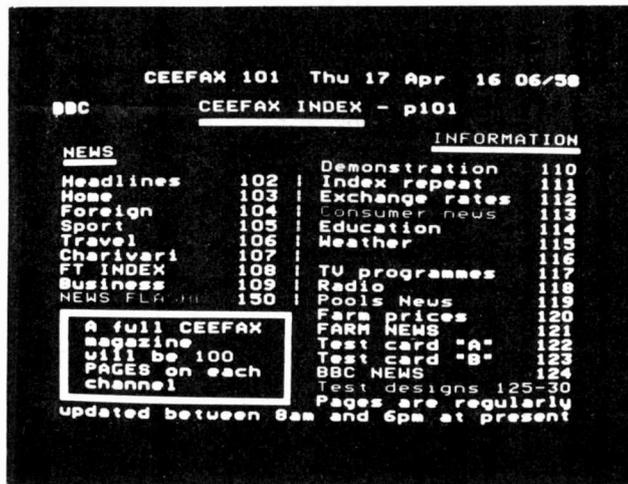


Fig. 6. This Sony cassette gives one hour of colour television with sound-tracks using a domestic television receiver to display the output of a special replay tape deck.

Fig. 5. Index page of earlier CEEFAX page system now available on domestic television in the U.K.

in the outset before one or two methods settle-out to become the norm.

Returning to more obvious extras for use with the domestic television set we will very soon see widespread use of the currently developed systems which transmit information over a spare part of the television channel. In the CEEFAX and ORACLE systems the data is stored until a complete single frame of written or pictorial information is ready to show. These are now combined as TELETEXT. Television networks in Britain have systems now well past the prototype test-state. Any television set owner (who can build or purchase a decoder unit) in Britain can today obtain up to several hundred full 'page' items on the screen. Items such as the weather forecast, share prices, programmes, time and programme reviews are listed. Figure 5 gives just one of the selection. It is not hard to see that this offering logically extends to giving access to an enormous amount of information.

The TV monitor of the future will also become the domestic equivalent of the micro-film/micro-fiche reader now rapidly replacing the book in libraries

and storehouses. Recorded video-tapes can be quite cheap to replay on special purpose replay-only units. Such units have been available for about five years now and it will not be long before the cost will be such that we will be buying video as well as audio cassettes in the music shop. Video discs are also close to being marketed in large volume. Figure 7 shows one market contender for the consumer market - prototype development having been reported three years ago.

One day in the future we will be visited by salesmen selling encyclopaedias in video cassette form instead of as bulky books. The publishers will also be able to offer an exchange service - old cassettes can have their facts updated at minimal expense.

Perhaps, too, the monitor will become the terminal for optimal video-links added to the telephone. For this to occur we would need low-cost very-wide bandwidth telephone channels. Current open wire and cable telephone systems have inadequate bandwidth handling capabilities on a single line so the change to video phones would need an entirely new concept of transmission or a complete replacement of the tele-

phone cable network including the switching and processing plant installed within the telephone system. The bigger the capital invested the longer it can take to change to new technology.


The bi-motional mechanical selector switches (see Fig. 8) used in telephone exchanges were first patented by Strowger in 1891. Many are still in use today.

A spread of the currently introduced cable TV systems - small networks wherein other than broadcast television programmes are 'sold' to clients connected to a specific suburban network of coaxial cables might duplicate all local telephone cables with adequate video-bandwidth networks. This would set the scene for a gradual change to video-phones. There will still, however, remain the immense task of providing national and international bandwidth capability that is 10 000 times its current provision for not much more in cost to the user.

Laser beams sent along fibre-optic paths are often reported to be the answer to bandwidth needs: considerable research and development is being performed today on these technologies. If and



Fig. 7. Video record playing equipment is already developed. Records provide 10-45 minutes of colour television.

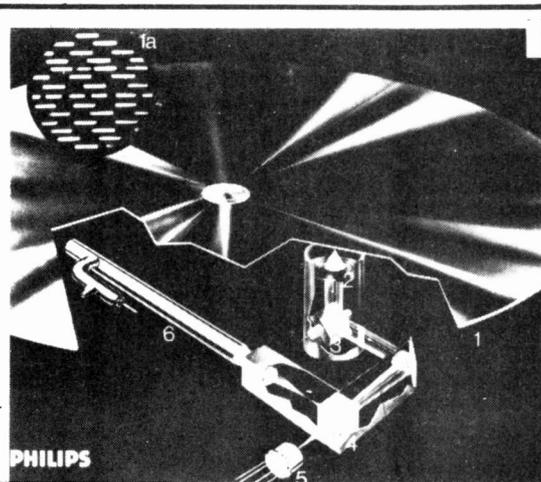

# Electronics 2000

## New Forms of Transmission Medium may Emerge

It is instructive to go back in history and try to imagine the attitudes of 18th century people to the likelihood of a communication form other than by message or word of mouth. To people of that era, sending messages over electro-magnetic (EM) waves would have been fantasy indeed. They knew and had some understanding of acoustic waves but knew nothing of radio waves. In the 19th century Maxwell predicted from his mathematical understanding of magnetic fields and their observed local-field behaviour, that it was possible to radiate a field away from a source — the energy literally escapes from the generator. It took about thirty years for this idea to be verified (by Hertz) by a crude experiment (see Fig. 9) and out of this was born radio. Once the concept of the electromagnetic spectrum was realised, EM frequencies other than in the radio region were exploited for communication purposes. Even today we have not completely filled in our use of all EM radiation wavelengths.

Field theory is a generalised theory that handles any kind of effect that can be experienced in space — magnetic, electric, gravity and force fields are examples. The operative word is 'experienced'. Until Hertz demonstrated radio waves no one had experienced them and, therefore, they did not exist as a tool of technology. Perhaps, today there are similarly other methods of radiation, so small in magnitude and so alien to any detectors we possess at present that we do not know of their existence. There is much evidence to suggest this is the case. Theory predicts the existence of gravity waves which are force fields propagated from exploding galaxies. On a closer basis we know that a mass exerts a force on another mass by gravitational attraction (but why is an unknown of science). The force falls off as the square of the distance between the masses. In theory a small mass (the transmitter) vibrating

rapidly causes a minute varying attractive force on another mass (the receiver). These forces can be calculated and the sums show that they are exceedingly small if the masses are of reasonably small size. To date many scientific research projects have tried to detect macro gravity — wave effects from the galaxies but now it appears that the current mechanical detectors being used are clouded by their own internal Brownian motion, which appears as a noise source. A new detection principle is needed — a second Hertz type historical event will occur one day when, and if, the generation and detection of gravity waves is demonstrated providing practical experience of the effect.

Moving on to less theoretically based fields there are the photographs made of energy fields of objects. These are unexplained but it is fact that photographs taken in a special way reveal an 'aura' surrounding the object. Lack of understanding of such phenomena is not an adequate basis for saying they are necessarily fakes.

Extra sensory perception (ESP) also may be part of potential future communication. Perhaps it, too, makes use of an energy field we do not yet recognise. It is sobering to remember we only understand experiences that our physiological senses and brain allow us to observe.


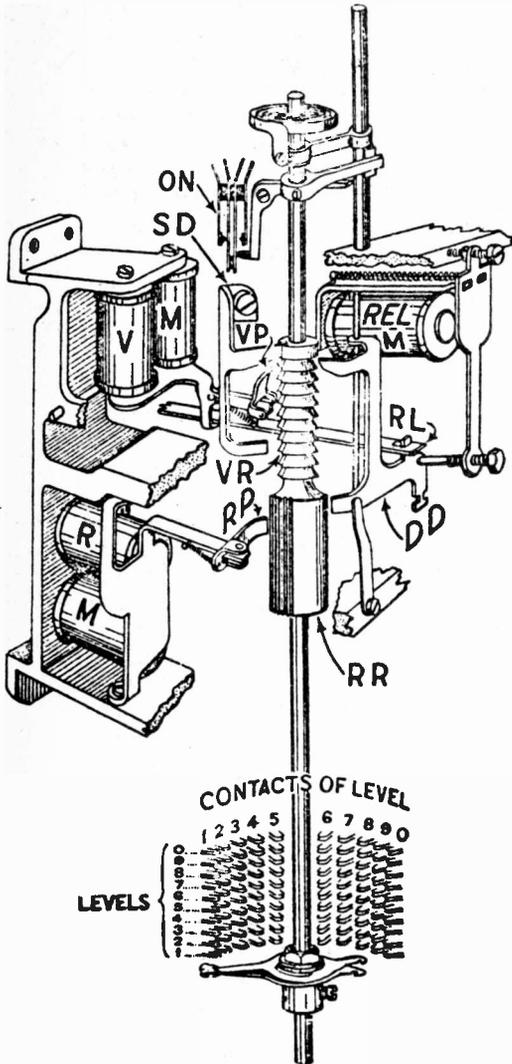


Fig. 8. Strowger bi-motional selector switches were first patented in 1891. Today many telephone exchanges still use them because it is uneconomic to change to new technology.

when their price falls enough to be competitive with other wide-band systems the first places of application will most likely be in heavy-traffic telephone and video links between cities. Domestic application, on the other hand, (in the form of cable TV) is an area where developers will be able to influence change more rapidly due to the smaller clientele to satisfy and persuade.

Fig. 9. Hertz oscillator (upper) and resonator (lower) of 1894. Until Hertz proved radio waves could be generated, transmitted and detected, communication by EM waves was fantasy even though they existed.

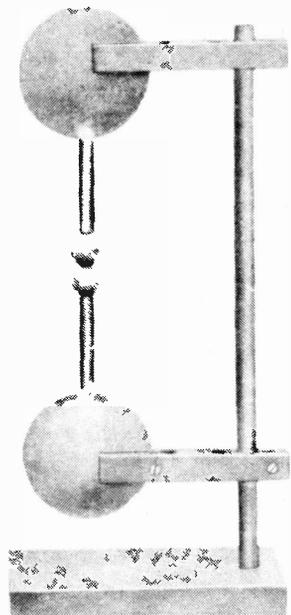

ESP, mental-telepathy, clairvoyance, precognition and parapsychology contribute physical experiences such as levitation, materialization, automatic writing, spirit photographs, psychokinesis, apparitions, poltergeists, miracles and voice recording. These are observed (perhaps apparently observed?) facts. It is quite in order to expect them to have a rational basis, one which we cannot understand as yet. It must be remembered that fantasy is only fact

actions of the body. Progress of understanding these rhythms is positive but slow. No doubt at some time in the future brain rhythms will be used to produce extensive communication as a direct thought process between people and machines — see Fig. 10. If we could hook up to another person by a wirelink it would be clearly feasible to do so without wires using wireless techniques of today. Typewriters that write directly from thought waves will

reveal the existence of radiated energy waves which are allied to the brain rhythms.

Assuming another form of energy field were discovered we could surmise that it might have direct person-to-person communication ability over global ranges rather than over the several metres experienced by our acoustic talking and hearing communication system. If this were so then the bandwidth problem of current systems might not be the limitation of the future. We would then have a breakthrough discovery that would completely change our attitude to what is feasible. Attitudes to community participational behaviour would be completely upset by such a finding.


For example, consider the experiences arranged in a theatrical show. Instead of having to relay the performance over cable or EM systems we might be able to 'attend' from remote distances. The whole concept of theatre would change. For this to be an adequate experience the "distance attendance" form of participation must fully simulate actual participation in the audience. Such a capability would obviate a vast amount of travel necessity and vastly reduce the need for transport mechanisms.

The live theatre is one form of entertainment that has changed little since its inception — at least until recent times. Lighting has improved beyond the lime-light of the last century to computer-controlled electric lighting of today. Electronic amplification of players' voices is still often avoided but electronic effects are used extensively in musical productions.

Current moves in the industry are to automate set changing. At the command of a mini-computer the several tonne sets will soon trundle out from the wings to their correct positions on stage without the aid of any stagehands. Will the players one day become automatons controlled by computer also?

We have seen in this and the previous part that electronic facility is a major influence on change. The mass-production of integrated circuits by photo replication methods enables many identical parts to be made most cheaply. Cheap data processing will continuously influence the kinds of ideas that are exploited and promoted in the future. One interesting question to ask, however, is whether electronics is the only discipline for powerful information handling. In the 1940s mechanical elements were thought to be the answer; today it is electronics. Could tomorrow see a change to electrochemical or some other system of signalling not yet known?

In the next part we shall investigate likely medical developments and the impact of the computer on our life style.

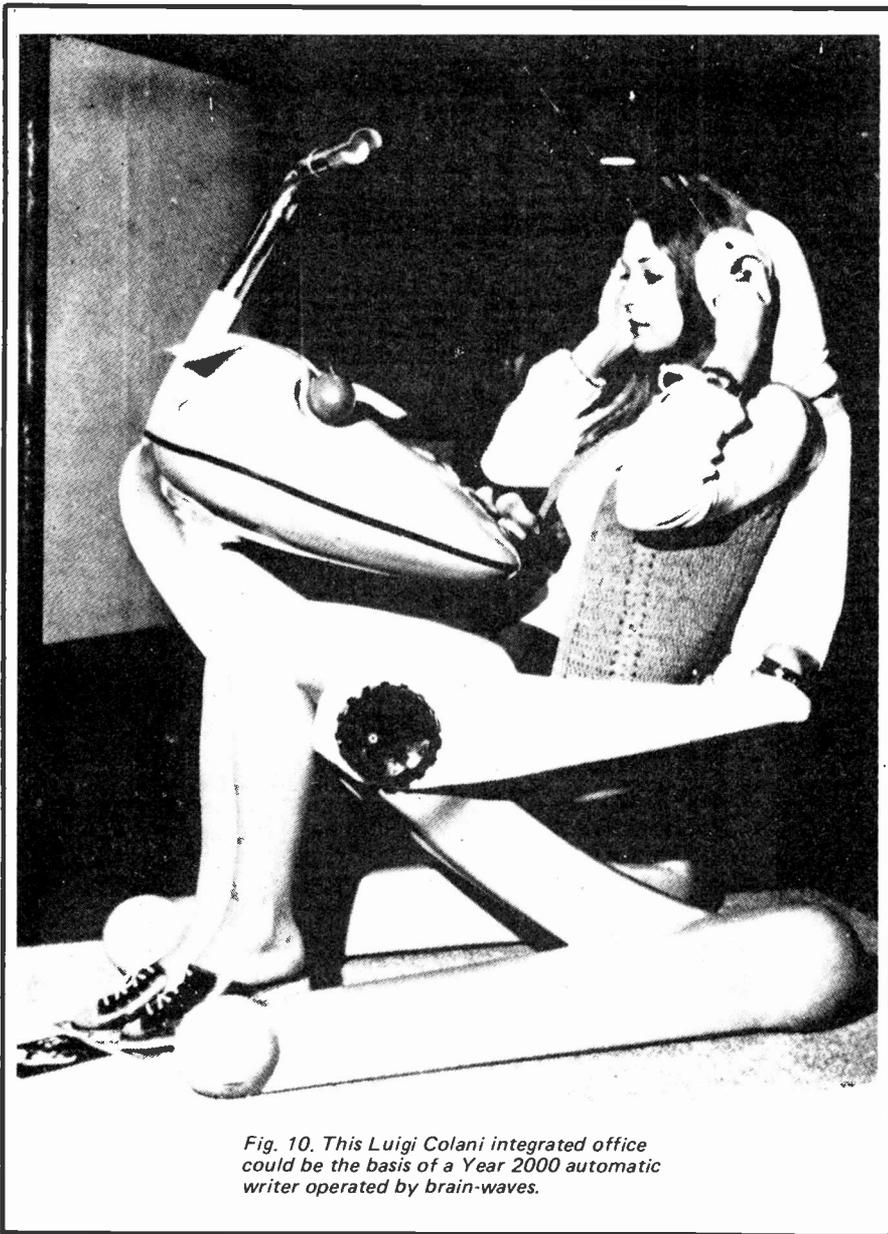

*Fig. 10. This Luigi Colani integrated office could be the basis of a Year 2000 automatic writer operated by brain-waves.*

unexplained. There is no reason to think all knowledge is known at this point in time.

The brain produces electrical signals — one kind is known as alpha rhythms. These can be recorded and a little is known that enables the signals to be associated with certain physiological

emerge to speed up the tedious task of transducing thought into clearly printed text. Here the hold-up is a scientific knowledge barrier for we cannot adequately decode the rhythms to obtain any more than the most simplistic data about the person's functions. Perhaps allied research will

TTLs by TEXAS*		7485 130p		74191 160p		OP. AMPS		8 pin DIL		40p		
7400	16p	7486	36p	74192	130p	301A	Ext. Comp	8 pin DIL	40p	AC125	20p	
7401	18p	7489	340p	74193	160p	1458T	FET Op. Amp	TO 99	300p	AC126	20p	
7402	18p	7490	43p	74194	130p	709	Ext. Comp.	8/14 pin DIL	36p	AC127	20p	
7403	18p	7491	81p	74195	96p	741	Int Comp	8/14 pin DIL	25p	AC128	18p	
7404	25p	7492	55p	74196	120p	747	Dual 741	14 pin DIL	70p	AC176	20p	
7405	25p	7493	43p	74197	120p	748	Ext. Comp.	8/14 pin DIL	40p	AC187	20p	
7406	45p	7494	96p	74198	220p	776	Prog Op Amp	TO 99	200p	AC187K	20p	
7407	45p	7495	76p	74199	220p	1454	Dual Op. Amp	8 pin DIL	108p	AC188	20p	
7408	25p	7496	90p	C-MOS 12A		3130	CMOS Op. Amp	8 pin DIL	108p	AD149	54p	
7409	27p	7497	340p	4000	21p	3140	BIMOS/FET input	8 pin DIL	108p	AD161	39p	
7410	18p	74100	116p	4001	21p	3900	Quad Op Amp	14 pin DIL	70p	AD162	39p	
7411	28p	74104	60p	4002	21p	LINEAR I.C.s				AF115	22p	
7412	27p	74105	60p	4006	120p	AY-1-0212	Tone Generator	16 pin DIL	650p	AF116	22p	
7413	38p	74107	36p	4007	21p	CA3028A	Diff Cascade Amp	TO99	112p	AF117	22p	
7414	96p	74109	96p	4009	67p	CA3046	5 Transistor Array	14 pin DIL	85p	AF139	43p	
7416	34p	74110	55p	4011	21p	CA3048	4 Lo Noise Amp	16 pin DIL	250p	AF239	48p	
7417	40p	74116	216p	4012	120p	CA3053	Diff Cascade Amp	TO5/DIL	70p	BC107/B	10p	
7420	18p	74118	90p	4013	55p	CA3080	Op Transcond Amp.	8 DIL	97p	BC108/B	10p	
7421	43p	74120	130p	4015	90p	CA3089E	FM IF System	16 pin DIL	250p	BC109/C	11p	
7422	24p	74121	32p	4016	54p	CA3090A	FM Stereo Decoder	QIL	500p	BC147	9p	
7423	40p	74122	52p	4017	110p	ICL8038CC	VCO Fun Gen	16 pin DIL	370p	BC149	10p	
7425	33p	74123	73p	4018	247p	LM3801	2W Audio Amp	14 pin DIL	115p	BC157	11p	
7427	40p	74126	75p	4020	140p	LM3811	Stereo Pre Amp.	18 pin DIL	175p	BC158	13p	
7428	39p	74132	75p	4022	180p	LM389N	Aud Amp +3 Trs Array	18 pin DIL	175p	BC159	13p	
7430	18p	74136	81p	4023	19p	M252	Rhythm Generator	16 pin DIL	850p	BC169C	15p	
7432	37p	74141	80p	4024	10p	MC1310P	FM Stereo Decoder	14 pin DIL	180p	BC171	12p	
7437	37p	74142	300p	4025	19p	MC1351P	Lim/Det. Aud Pre amp	8 pin DIL	104p	BC172	12p	
7438	37p	74145	90p	4026	207p	MC3340P	Electronic Attenuator	8 pin DIL	180p	BC173	13p	
7440	18p	74148	173p	4027	81p	MFC4000B	4W Audio Amp	TO5	175p	BC178	20p	
7441	85p	74150	155p	4028	152p	NE540L	Aud Pwr Driver	PCB	90p	BC179	20p	
7442	75p	74151	77p	4029	130p	NE555V	Timer	TO5	175p	BC182	12p	
7443	116p	74153	92p	4030	59p	NE555	Dual 555	14 pin DIL	98p	BC183	12p	
7444	116p	74154	164p	4042	150p	NE561B	PLL with AM Demod.	16 pin DIL	425p	BC184	14p	
7445	108p	74155	96p	4043	218p	NE562B	PLL with VCO	16 pin DIL	425p	BC187	32p	
7446	108p	74156	96p	4046	180p	NE565	PLL Fun Gen	8 pin DIL	200p	BC212	14p	
7447	90p	74157	97p	4047	110p	NE567	PLL VCO	8 pin DIL	200p	BC213	12p	
7448	85p	74160	120p	4049	68p	NE568V	PLL Tone Decoder	8 pin DIL	400p	BC214	17p	
7451	20p	74161	120p	4050	50p	NE57V	Dual 567	16 pin DIL	200p	BC247	32p	
7453	20p	74162	120p	4054	130p	SG3402N	Ring Modulator	14 pin DIL	275p	BC257	24p	
7454	20p	74163	130p	4055	140p	SN72710	Diff Comparator	14 pin DIL	54p	BC270	22p	
7460	20p	74164	130p	4058	145p	SN72733	Video Amp	5 pin DIL	150p	BCY71	24p	
7470	32p	74166	136p	4060	130p	SN76003N	Aud Pwr Amp with HS	16 pin DIL	275p	BD124	140p	
7472	32p	74167	370p	4069	30p	SN76008	10W Amp in 4 ohms	5 pin Plastic	280p	BD131	39p	
7473	36p	74174	131p	4071	29p	SN76013N	Aud Pwr Amp with HS	16 pin DIL	175p	BD132	43p	
7474	36p	74175	92p	4072	29p	SN76023N	Aud Pwr Amp with HS	16 pin DIL	175p	BD135	54p	
7475	48p	74176	131p	4081	21p	SN76033N	Aud Pwr Amp with HS	16 pin DIL	275p	BD139	54p	
7476	37p	74177	120p	4082	29p	TAA621A	Aud Amp for TV	QIL	150p	BD140	60p	
7480	54p	74180	120p	4510	142p	TAA661B	FM/IF Amp Lim/Det	QIL	100p	BDY55	22p	
7481	108p	74181	322p	4511	200p	TBA800	5W Audio Amp	QIL	100p	BF115	24p	
7482	85p	74182	89p	4516	140p	TBA810	7W Audio Amp	QIL	125p	BF173	27p	
7483	99p	74185	145p	4518	140p	TBA820	2W Audio Amp	QIL	375p	BF173	27p	
7484	103p	74190	155p	4528	130p	TDA2020	20W Audio Amp	16 pin DIL	400p	DRIVERS:		
VOLTAGE REGULATORS		Fixed-Plastic 3 Terminals		1 Amp +ve		-ve		OPTO-ELECTRONICS		PHOTO-TRANSISTORS		
5V	7805	130p	7905	215p	5V	7812	130p	7912	215p	OC70	90p	
12V	7812	130p	7912	215p	12V	7815	150p	7915	215p	OC71	120p	
15V	7815	150p	7915	215p	24V	7824	150p	7924	215p	2N5777	50p	
LM309K	5V	1 Amp	TO3	150p	LM309H	5V	100mA	TO5	97p	LDrs	120p	
TBA625H	12V	0.5A	TO5	106p	LM323K	5V	3A	TO3	85p	ORP12	70p	
Variable	723	14pin DIL							ORP60	90p		
									ORP61	90p		
LOW PROFILE DIL SKTS BY TEXAS		28 pin 60p		28 pin 80p		28 pin 14p		40 pin 75p		SEVEN SEGMENT DISPLAYS		
8 pin	12p	16 pin	14p	28 pin	60p	14 pin	13p	24 pin	54p	3015F	200p	
											DL704	180p
											DL707	160p
											DL747	250p

VAT INCLUSIVE PRICES. Add 20p P&P — no other extras  
 MAIL ORDER ONLY. GOVT. COLLEGES ORDERS WELCOME

# TECHNOMATIC LTD

54 Sandhurst Road, London NW9  
 Tel. 01-204 4333  
 Telex 922800

## THE OPEN DOOR TO QUALITY

Electrovalue Catalogue No. 8 (Issue 4 up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases. Access and Barclaycard orders are accepted

**PLUS FREE POSTAGE**  
 on all C.W.O. mail orders in U.K. over £2.00 list value (excluding VAT). If under, add 15p handling charge.

**UP-DATED 4th EDITION**  
 Prices stabilised minimum 3-month periods

**144 pages, 40p** Post paid, inc. refund voucher for 40p

### ELECTROVALUE LTD

All communications please to Head Office, Egham address. Dept. ETI.5

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Tel. Egham 3603. Telex 264475. Shop 9.5-3.0, 9.1-1 pm Sats. NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Tel. (061) 432 4945. Shop 9.5-3.0 pm, 1 pm Sats.

## NEW 1977 WATCHES

FAIRCHILD TIMEBAND LCDs  
 BATTERY HATCH  
 FREE REPLACEMENT BATTERY  
 LOWER PRICES

Now you can change the battery yourself — a considerable saving

5 + 4 functions. Continuously displays Hours, Minutes and Second Colon. Press command button for Month, Date. Press twice for second readout. Setting for alternating Time/Date display. Automatic 28, 30, 31 day Calendar. Backlight

NEW small round watch on strap  
 T441 Chrome plated £23.50  
 Round watch on strap  
 TC411 Chrome Plated £25.95  
 TC410 Gold Plated £28.95  
 On matching adjustable bracelet  
 TC413 Chrome Plated £31.00  
 TC412 Gold Plated £33.95  
 NEW Digital Alarm Clock (snooze button) £14.95

**NEW**  
 National Semiconductor Available in Summer  
 5 + 3 functions, 6 digit display Watch and Scientific Calculator operated with pencil, ball pen, etc.)  
 NEW 6 digit 6 + 3 functions + Chronograph  
 Full range of LCDs  
 DAC5 Series (strap or bracelet)  
 DAB5 WB (illustrated) £35.50  
 All Stainless Steel and matching Bracelet

**NEW** CASIO CO-1 CLOCK, ALARM, STOPWATCH, CALCULATOR NOW ONLY £29.50 (Black or White), AC Adaptor £3 SUPERB 1977 CASIO CASIOTRON WATCHES

Arguably the best watches in the world. All stainless steel. Mineral glass. 7 + 2 functions (incl backlight) £43.50, RRP £59.95  
 With STOPWATCH, SECOND CHANNEL TIME MEMORY from £58.50  
 NEW. Lower prices for IBICCC 403NS £38.50, 450HS £68.50  
 NEW MODEL. 4051LB (2 yr. battery) £34.50, 4051S £35.50  
 NEW. IBICO ANALOGUE WATCH. Latest technology (3 yr. battery) £34.50

Send 10p for our ILLUSTRATED CATALOGUE. Prices include VAT, P&P

# TEMPUS

DEPT. ETI  
 15/21 FITZROY STREET  
 CAMBRIDGE CB1 1EH  
 TEL. 0223 312866

RON HARRIS INTRODUCES

# THE ETI ER II LOUDSPEAKER

a high-quality design for the home constructor


LOUDSPEAKER ENCLOSURES are perhaps the least understood, and understandable, of hi-fi components for the home constructor. Crossover networks for example look deceptively simple on paper, but can be more complex to design properly than a digital system comprising 100 IC's. Enclosures too commonly called "the bloody box," are all too often taken too lightly with the result that a great deal of effort expended in the design of the crossover unit and quality inherent in the units is thrown to the wind.

Our design is a two-unit home system, designed to give a very high quality sound output, allied with the advantages of easy construction and reasonable cost (about £70 a pair in cash, and whatever blood sweat and tears prove appropriate).

## Getting Cross Over Components?

Frequency division networks for loudspeaker use are generally required to overcome six main problems. These are:

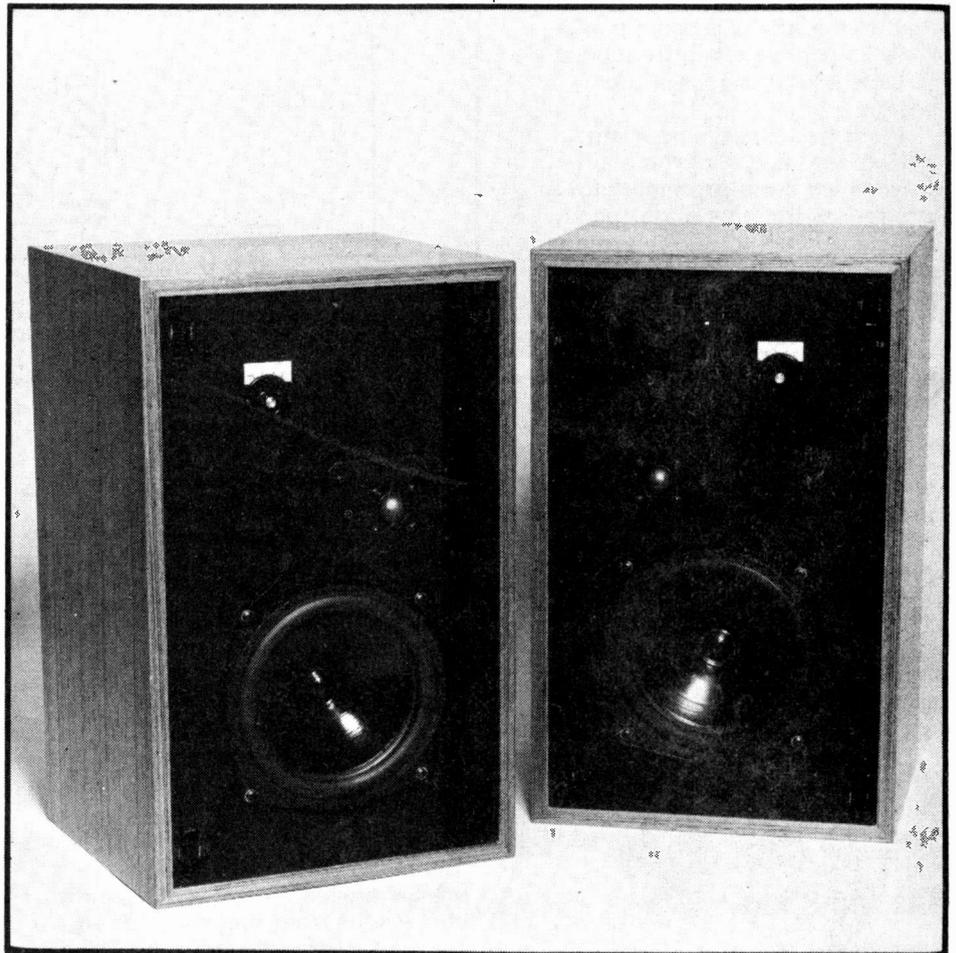- (1) Voice coil impedances are very much lower than is usually met in communications theory (for which most standard filter designs were evolved) and this makes termination difficult.
- (2) Power requirements are high, although this is relatively easily overcome by use of high rated components, correct gauge wire etc.
- (3) Drive unit impedance varies greatly with frequency, and the reactive component changes very rapidly near resonance. The filter load thus changes appreciably with frequency.
- (4) The network will introduce phase shift i.e. delay, and if poorly designed this may be significant on transient waveforms, ringing occurring at some frequencies.
- (5) It is convenient to have the network 'level out' the efficiencies



## Specification

**FREQUENCY RESPONSE:** 50Hz-25kHz  $\pm$  4dB  
**EFFICIENCY:** approx 16W required to generate 96dB (test room conditions)  
**POWER HANDLING:** Min. 15W per channel recommended, max 40W programme.  
**DIMENSIONS:** 21 1/4" h x 13 1/4" w x 12" d.  
**APPROX COST:** £70 a pair.

of the different drive units, and this involves controlled dissipation in the network. Also any variation in the amplitude response should be, if at all possible, minimised.  
(6) Reactive elements within the network may well resonate with

loudspeaker motor reactive elements at some frequencies. This could present a much reduced impedance to the power amplifier, which in turn might show its displeasure in some, unpleasant, tangible form or other.

# ER II LOUDSPEAKER

## Pointing Things Out

Number four of the preceding is one aspect of the now abating furor that the so-called linear phase loudspeakers caused upon their release.

In every case with these designs, the reason for their audible quality can be more easily ascribed to the fact that they (B&W DM6, B&D M70, Leak 3000 range etc) are simply damned good speakers in their own right, rather than to the dubious benefits of a linear time delay with frequency.

Ours is not a linear-phase design.

Point five is very important indeed, and is one of the main reasons we are recommending, as strongly as the nibs of our pens will stand, that you do not attempt to fabricate the crossovers for this project yourselves. Badger Sound Services can supply the complete unit off the shelf, and you are advised to look thence! (Deliveries are superb.)

Several of the components in the network are chosen to compensate for 'meanderings' in the units. For example the two 5 $\mu$ F capacitors are selected tolerance components, and the 2mH coil across the B200 has a very critical impedance to present. Also important is the grade of ferrite employed in the cores, as this will determine saturation level, a nasty parameter to fall foul of!

I hope that has convinced most of you. For those adamant souls still set on the winding path — good luck 'cos yer gonna need it!

## Closed Shop

And so to the boxes they come in. Ideally a speaker enclosure should do precisely that and no more — it should enclose without reacting. It should do — but naturally doesn't. The volume of air within the enclosure acts as a mechanical resistance to cone movement, especially at bass frequencies. When using the "Infinite Baffle" design, as we are here, the cabinet volume must be set to match the bass unit.

If the mid-range is not a 'sealed-back' or dome unit (a la Celestion which is both!) then this too will be affected by the air load. An acceptable solution is to provide a tube within the main cabinet for the mid-range driver to work in. (Both Kef and Wharfedale

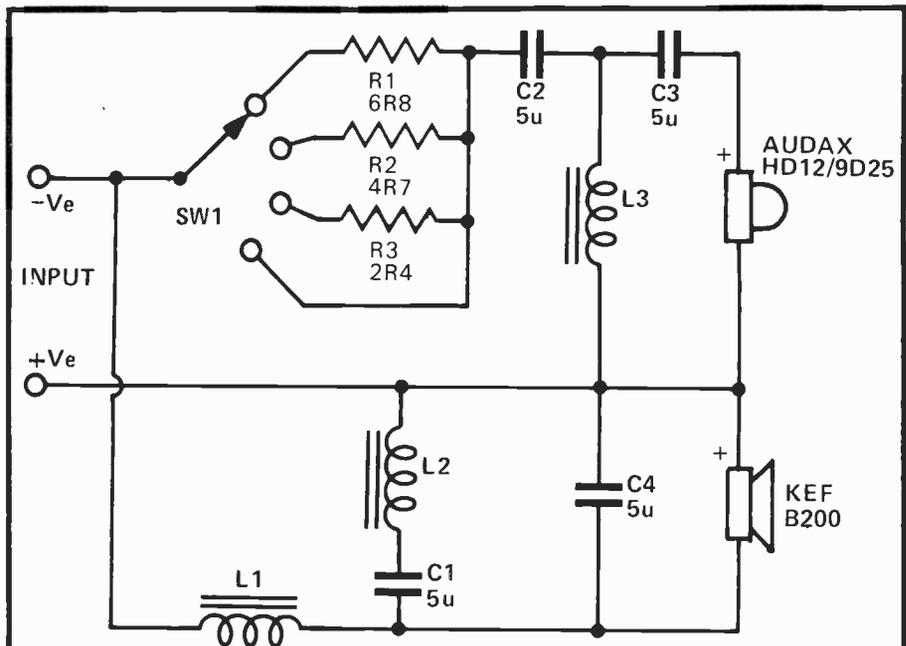


Fig 1. Circuit diagram of the crossover network. Component values are nominal. Note that R1-3 are mounted off board on to SW1 which is the h.f. level control. The units are wired in 'antiphase.'

adopt this solution in their speakers.)

The type of wood, or more honestly chipboard, that constitutes the cabinet is also an important factor. What you want to hear is the sound from the flapping cones — not from flapping cabinet sides. The denser the better is the rule here. This 'flexing' of panels can be a major source of colouration in a design, and it is surprising commercial firms do not pay more attention to bracing or stressing their enclosures. As you can see from the drawings and 'Construction' text, our enclosure is heavily braced, and if you want the best results from your work don't be tempted to leave any out. The volume of the batten used has been allowed for in the calculation of cabinet air load on the bass units, so don't worry about it!

## Specifics

The actual construction design presented here is intended for use in rooms up to about 2000 cu. ft., with amplifiers of up to 50W r.m.s output — but be careful with the volume control when using amplifiers of more than 35W or so. Efficiency is slightly higher than average — see table. The main design criteria throughout was how it *sounded*, not how it measured or looked, but how musical was the noise emanating from the grille cloth!

## Construction

Woodwork is the main problem facing the constructor. When cutting the baffle keep the units themselves in exactly the same place as the drawing shows them. If you change the positioning you'll change the sound, and we cannot guarantee the result!

Perhaps the best way to give constructional details is a list of DO's and DON'T's!

Here goes:

- DON'T omit any of the enclosure bracing shown.
- DON'T attempt to 'bodge up' your own crossover network.
- DON'T mount the drive units on the back of the baffle because its easier — it will show up as soon as you switch on!
- DON'T leave any gaps in the joints of the enclosure.
- DON'T commit the cardinal sin of using hardboard for the back panel.

DO fit the bracing *across* the grain of the veneer. It is best to have the grain running vertically on the sides and back panel, and parallel to the baffle on the top and bottom. DO leave a small hole in the back panel no larger than 1/16in diameter, to allow any changes in air pressure within the enclosure due to temperature etc to equalise. This will not affect the sound at all.

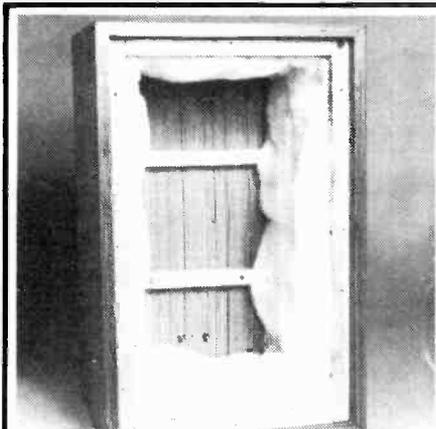


Fig 2. Internal shot with the wadding fitted to the sides. The back panel has not yet been lined. The bracing across the panel can be seen, and this continues around the sides.



Fig 3. Here the cabinet is complete, and the final wadding has been folded into place. This loosely fills the enclosure. You'll have to attach the wires to the input sockets first though!

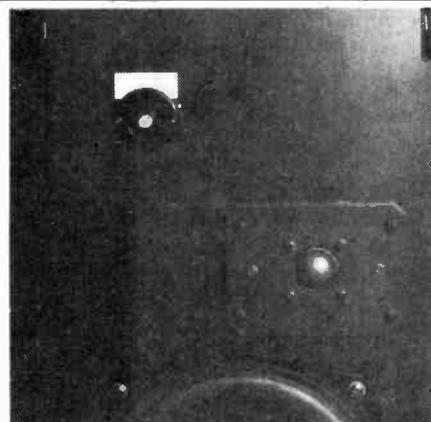


Fig 4. Front panel detail. The h.f. level control at the top is set to +2dB. From this the relative position of the drive units can be seen. When attaching these to the front panel, seal them off airtight.

DO use chipboard veneered on both sides.

DO 'glue and screw' all joints to ensure that other than the above hole the enclosure is totally air-tight. Evo-stick Woodworking Adhesive is particularly suitable for the job. DO mount the baffle as close to front edge of the enclosure sides as possible. This minimises diffraction effects and greatly aids dispersion of high frequencies. Take care however with the dome of the Sonaudax. Put *that* too close to the front and it'll get 'grilled'!

DO use best quality chipboard — 5/8" min 'flooring quality' etc or even hard wood if your bank balance can stand the shock and your floorboards the weight!

We mounted the crossover unit on the rear of the baffle next to the level control, so that wiring is kept to a minimum. The back panel is sealed when passing wires through the enclosure, make sure they can't 'rattle' on the sides of the box, or on the units.

Once the woodwork is complete line the enclosure using BAF wadding or the like (1in thick). Stick one layer on all the sides and *two* layers on the back panel. Taking care with the wiring, fold in sufficient wadding to just fill the remaining space, making sure it doesn't foul the B200 cone.

When screwing up the baffle put some draught excluder around the frame if you can, it helps the sealing.

We haven't shown a grille design on our prototypes, as we thought all you lot out there would do it your own way anyway! This is not critical, provided you use proper grille cloth or even better acoustic foam. Grannys old net curtains may have a nice pattern and match the

3-piece, but it'll sound awful. Gag the missus if need be, but don't give in!

### Use and Abuse

The speakers should really be used on stands if free standing, of no less than 10in in height. Stand them at least a foot from a wall, and not in a corner, as this will introduce 'boom' at the low end that these enclosures don't need to help the bass response.

They can be used on a shelf against the wall, and in this mode set the tweeter at 'ear level' (when you're seated of course). Keep the enclosures about 6ft-8ft apart — never further if you want stereo in preference to two sound puddles around the boxes.

As with all speakers, damping from the amplifier is best preserved by using as thick a connecting lead as possible, say a minimum of 5A cable. And no, screened lead is neither suitable nor necessary.

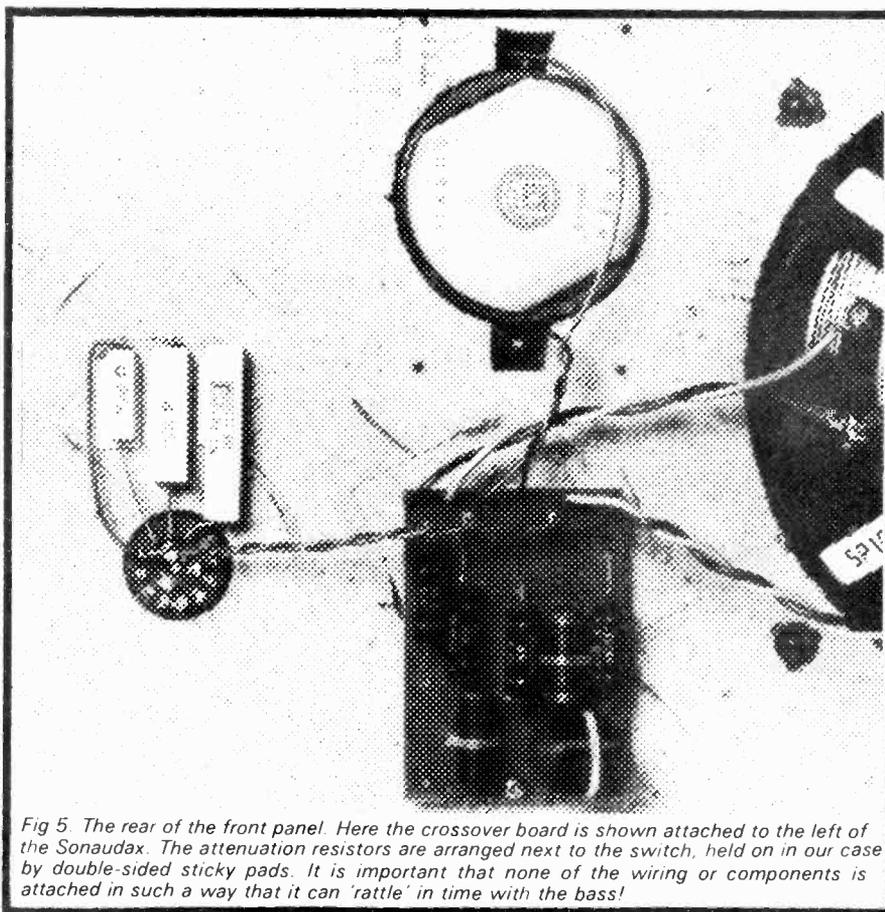


Fig 5. The rear of the front panel. Here the crossover board is shown attached to the left of the Sonaudax. The attenuation resistors are arranged next to the switch, held on in our case by double-sided sticky pads. It is important that none of the wiring or components is attached in such a way that it can 'rattle' in time with the bass!

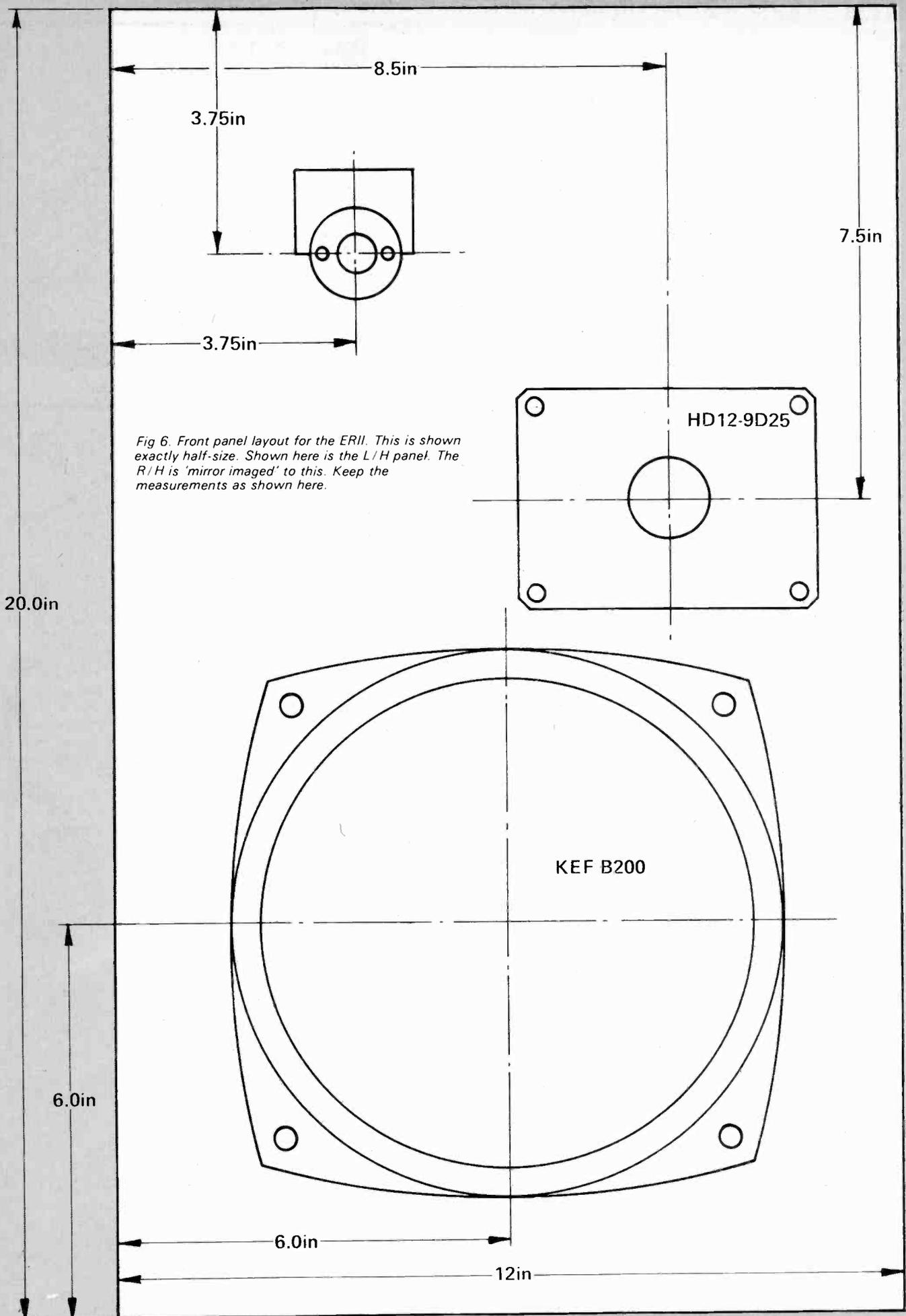


Fig 6. Front panel layout for the ER11. This is shown exactly half-size. Shown here is the L/H panel. The R/H is 'mirror imaged' to this. Keep the measurements as shown here.

20.0in

8.5in

3.75in

7.5in

3.75in

HD12-9D25

KEF B200

6.0in

6.0in

12in

# ER II LOUDSPEAKER

## Last But Not Least!

As we said before the main criteria for the design was how the things sounded. It is hard if not impossible to convey a subjective impression on paper, and a long string of well-nigh standard, albeit strange, adjectives have been developed for the task, such things as 'boxy', 'chesty', 'wooden' etc etc ad nauseam. And now of course we have 'musical' and 'un-musical'. Forgive us if we use any of these insults to English herein!

For the purpose of final evaluation, the ER II's were wired up next to a known reference speaker, in this case Celestion Ditton 66's, in order to better assess their subjective performance. It is all very well to listen to an unknown design on its own and gain some general impression of its fidelity, but to come to a definite decision, there must be something there to compare it with, and something of known vices at that.

The rest of the reference system comprised a Technics SL120 and SME3009 V15III and G900SE record deck, Pioneer SA 9100 and

Per pair:	
2x	HD12 - 9D25
2x	B200
2x	CN104/ETI crossover networks
2x	3 pole 4 way switch
2x	recessed flange and matching knob for switches.
2x	2R4
2x	4R7 10 W or greater
2x	6R8
2x	4 mm banana skt. red
2x	4 mm banana skt. black

**Our thanks go out to our friend David Pickler of Barnet, who produced the woodwork for the prototype ER II's. We changed the cabinets quite a few times before settling on the final design. We can only say he showed patience! Nice one David.**

Quad 22/II (just to keep valve enthusiasts happy!) amplifiers, a Revox A77 Mk IV tape deck and of course the Celestions. A calibrated power output meter (based on our level meter ETI March 1976) was also used to gain some impression of subjective efficiency. Several pairs of hi-fi and concert going ears were assembled at various times to comment on the ER II's, in order to

## Parts List

Chipboard & battening to suit method of construction: see text  
BAF wadding to fill cabinets, approx. 12 yds. at 24" x 1".  
Badger Sound Services, of 38A St. Andrews Road South, St. Annes, Lytham St. Annes, Lancs FY8 1PS can supply the crossovers at £4.99 + 35p p+p each, and just about everything else for this project too. Ring them on St. Annes 729247 to check prices and availability before ordering.

see if we were pleasing all of the people all of the time, or none of the people none of the time.

## Verdict

Direct comparison with the reference showed the ER II's to be very musical indeed in their output. Naturally, due to the much smaller size of the enclosure, deep bass level was down on that from the reference, but not seriously so, and it was quite possible to advance the bass control on the amplifier without boxes squawking out in protest. Bass quality is good, with notes being well defined and boom conspicuous by its absence.


The Sonaudax tweeter showed itself to be a very smooth unit indeed, and gave the speaker a slightly bright sound, which was present on both amplifiers (lest the valve brigade began to nod their heads sagely), although in no way objectionable. Setting the control to -2dB position tended to remove this anyway. The room in which the tests were carried out was in any case 'hard' in character, with little absorption, and doubtless the ER II's are a great deal less guilty than the room.

Considering their price of around £70 the ER II's produced a remarkable performance, and one that some listeners commented bettered their commercial units, all of which cost in excess of £150 a pair.

All in all then a good little speaker, and one well worth considering if you're in the market to upgrade, or even about to set foot on the slippery incline of hi-fi for the first time.



# SPECIALS FROM ETI

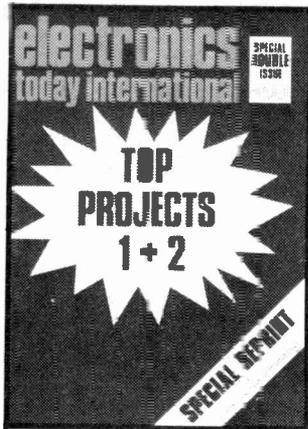


## TOP PROJECTS No. 1 + No. 2

Tens of thousands of our first two projects books have been sold — finally we ran out but all is well. We've reprinted No. 1 and No. 2 in a massive 180-page book. At present this is only available direct from us. It is a limited print run but we have adequate stocks at the moment.

See our ad elsewhere in this issue listing the projects included.

£2.50 + 20p P&P

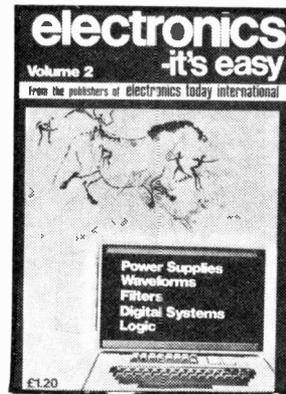


## ELECTRONICS — IT'S EASY

Our unbelievably successful series, now drawing to a close, is available complete in three parts — not surprisingly known as Volumes 1, 2 and 3.

At the time this issue goes to press, we only have Volume 2, but Volume 3 will be available in early April and a reprint of Volume 1 (which we sold out of completely) will be available late April. Orders can be accepted now for immediate despatch upon delivery to us.

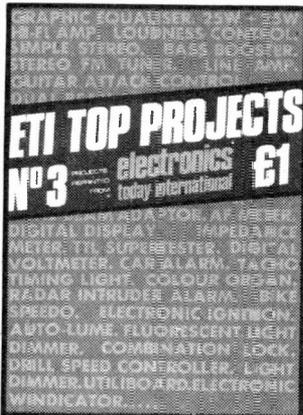
Each £1.20 + 20p P&P  
Complete set £2.50 + 35p P&P



## TOP PROJECTS No. 3

Originally published in March 1976, Top Projects No 3 contains 27 constructional projects including Graphic Equaliser, International 25W Stereo Amp, Simple Stereo, New Sound for your Guitar, Bass Booster, Line Amplifier, Loudness Control, Electronic Ignition, Tacho Timing Light, Car Alarm, Dual-Beam Adaptor, AF Meter, Impedance Meter, Digital Display, Digital Voltmeter, TTL Supertester, Fluorescent Light Dimmer, Radar Intruder Alarm, Light Dimmer, FM Tuner, Colour Organ, Drill Speed Controller plus many more.


£1.00 + 20p P&P

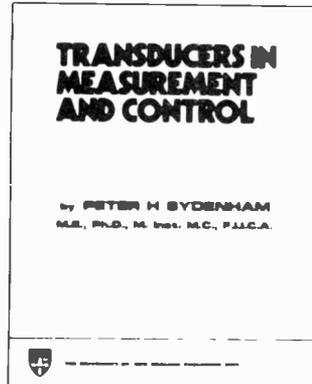

## TRANSDUCERS IN MEASUREMENT AND CONTROL

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine and was so highly thought of by the University of New England that they have re-published the series splendidly for use as a standard textbook. Written by Peter Sydenham M.E. Ph.D. M. Inst. M.C. F.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead Editor.


£2.55 + 20p P&P

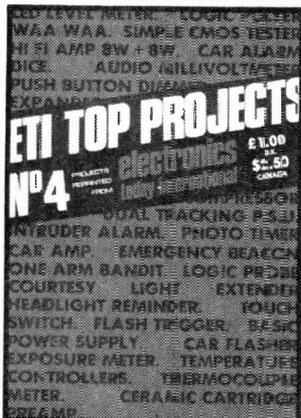

## TOP PROJECTS No. 4

Available at your newsagents or from ETI direct. Published October 1976. This includes Sweet-Sixteen Stereo Amp, Waa-Waa, Audio Level Meter, Expander-Compressor, Car Anti-Theft Alarm, Headlight Reminder, Dual-Tracking Power Supply, Audio Millivoltmeter, Thermocouple Meter, Intruder Alarm, Touch Switch, Push-Button Dimmer, Exposure Meter, Photo Timer, Electronic Dice, High Power Beacon, Temperature Controller, Electronic One-Armed Bandit plus many more.


£1.00 + 20p P&P

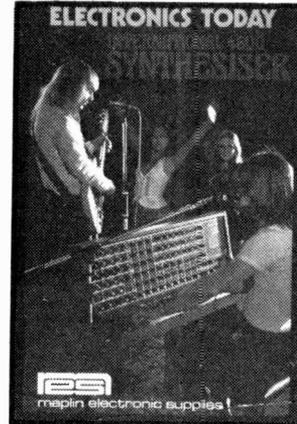

## ETI 4600 SYNTHESISER

A complete reprint of our superb synthesiser design, published with Maplin Electronics (who also supply the parts). This reprint will also be of interest to those not specifically wanting to build the unit as the circuitry is highly original and is in fact patented by ETI!


£1.50 + 20p P&P

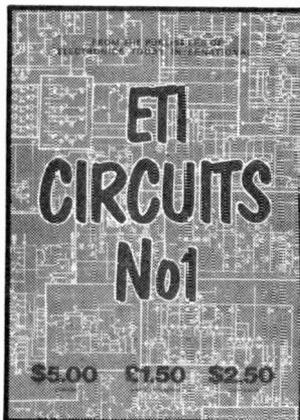

## ETI CIRCUITS No. 1

Just published and available from your newsagent as well as from us direct is this new concept in Specials. ETI Circuits No. 1 contains over 200 circuits, largely based on the Tech-Tips section and Data Sheet but great care has been taken to index each circuit carefully to enable rapid selection. This publication is likely to be regarded as a bible by the experimenter for not only does it contain complete circuits but also ideas and circuit sub-assemblies.

£1.50 + 20p P&P

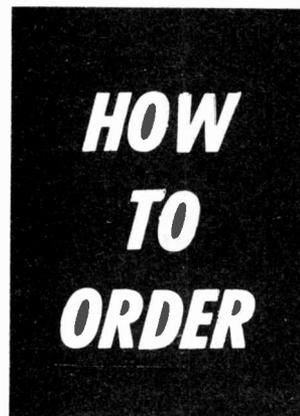

## HOW TO ORDER

ETI Circuits No. 1 and Top Projects No. 4 are available at newsagents or direct from ETI. Others are available only direct from ETI.


Postage and packing is 20p for the first, 15p for each subsequent issue (Overseas 25p and 20p respectively). Send remittance (in Sterling only) to:

ETI Specials,  
ETI Magazine,  
25-27 Oxford Street,  
London W1R 1RF.

Please mark the back of your cheque or PO with your name and address.

# SHORT CIRCUITS

## INJECTOR/TRACER

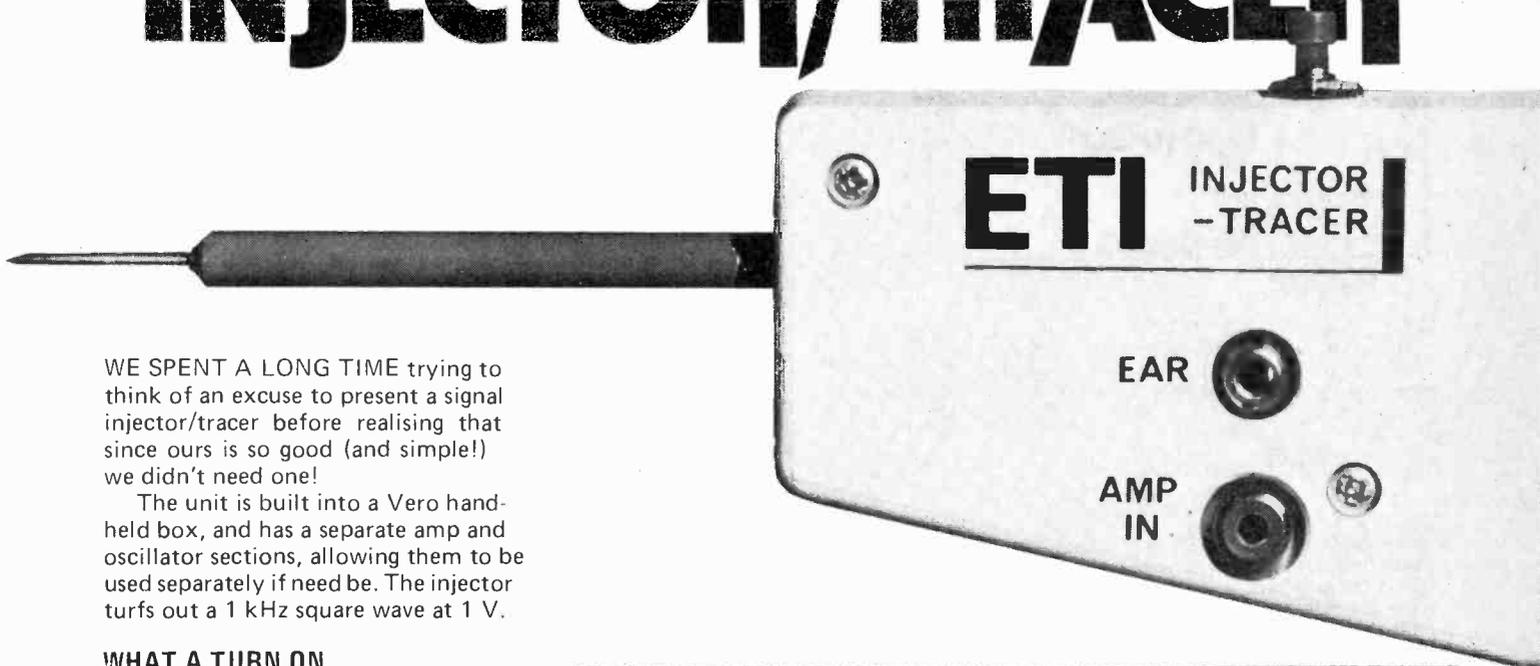

WE SPENT A LONG TIME trying to think of an excuse to present a signal injector/tracer before realising that since ours is so good (and simple!) we didn't need one!

The unit is built into a Vero hand-held box, and has a separate amp and oscillator sections, allowing them to be used separately if need be. The injector turfs out a 1 kHz square wave at 1 V.

### WHAT A TURN ON

The output is to a crystal earpiece, and the 3.5 mm jack socket is modified to switch on the amp upon insertion. To inject a signal shove the button on the top down. Everything is mounted onto a single pcb within the box which also contains a PP3 battery.

Access to the amplifier section is provided via the phono socket which is also bolted to the board. The quality of this stage might just surprise you, incidentally.

### MOUNTING TROUBLES

The board is held within the box by the pillars (designed for the job!), and to get the PP3 in, you'll have to file these down a bit - have a look at the photograph to see what we mean. Apart from this the project is ridiculously easy to build, and should pose no real problems.

### How it works

Eyes down for the shortest How It Works ever.

The injector is a multivibrator running at 1 kHz, with R5 and R6 dividing down the output to a suitable level ( $\approx 1$  V).

The tracer is a single-stage BC108 amp, current biased, and feeding into SK4 to drive the high impedance earpiece. C4 decouples the input.

Enough said?

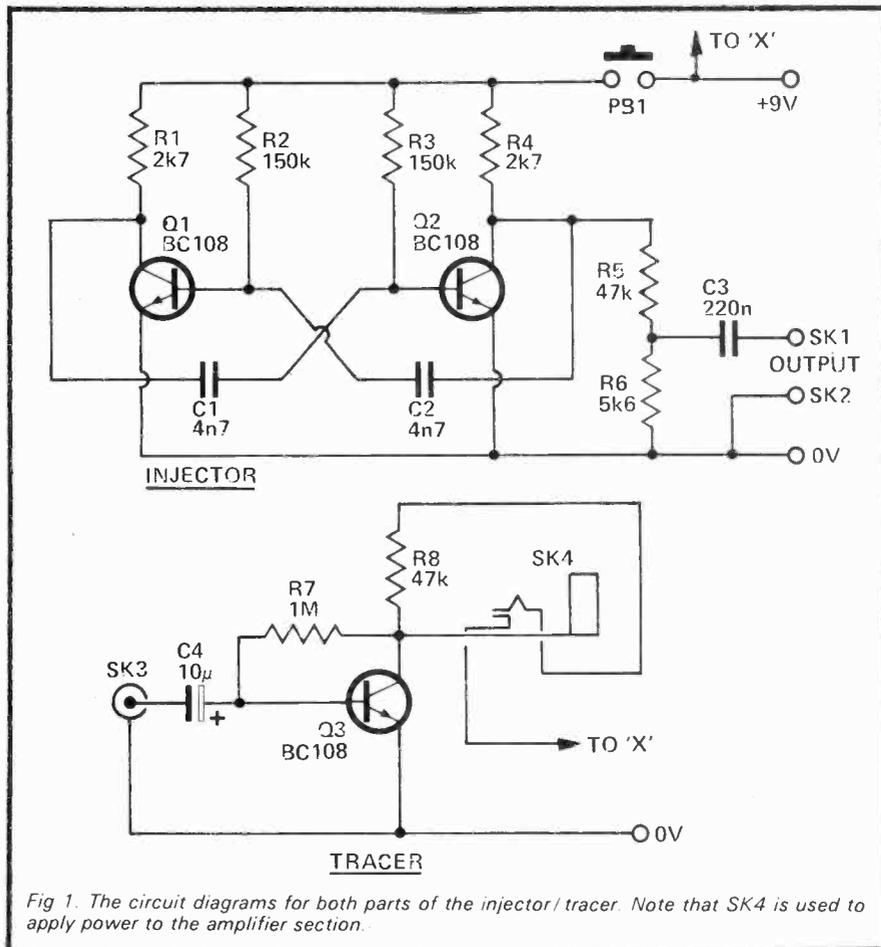


Fig 1. The circuit diagrams for both parts of the injector/tracer. Note that SK4 is used to apply power to the amplifier section.

# Short Circuits

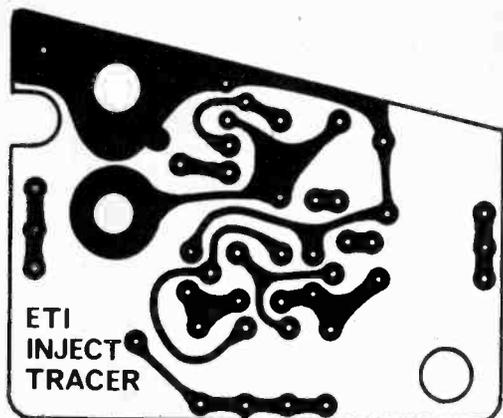


Fig 2. Pcb foil pattern for the circuit. Shown full size. The large areas of copper are where the sockets fix directly to the board.

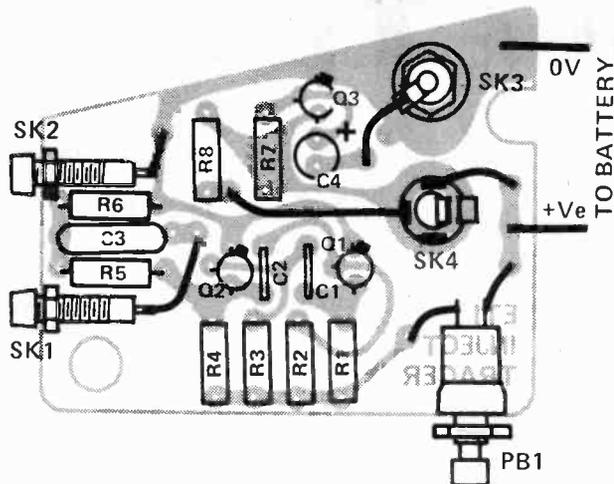


Fig 3. Component overlay. Note that SK2 and SK1 are held in place by the Verobox closing around them. SK3 and SK4 are attached directly onto the pcb, and face out of the box on the copper side of the board.

In order to get the PP3 to fit into the hand-held box, it will be necessary to file down the pillar within the box. Drop the pcb over the retaining stubs as shown, so that when the other half of the box is clipped onto it, the fins on it will hold the board in place. It is these fins which will need to be filed almost flat.

SK2 and SK1 can be seen in place on the front of the box. Here also a little filing will help, in as much as the sockets will then be flat and the probe be perpendicular to the verobox body.

## Parts List

### RESISTORS — all ¼ W 5%

R1,4	2k7
R2,3	150 k
R5,8	47 k
R6	5k6
R9	1 M

### CAPACITORS

C1,2	4n7 polyester or ceramic
C3	220 n polyester
C4	10 µ 10 V electrolytic

### SEMICONDUCTORS

Q1,2,3	BC108 or similar
--------	------------------

### SWITCH

PB1	Push to test type
-----	-------------------

### SOCKETS


SK1,2	2 mm panel type
SK3	Phono socket (Doram 477-848)
SK4	3.5 mm chassis jack socket (see text)

### CASE

Verobox	'Hand Held' type (75/1799E)
---------	-----------------------------
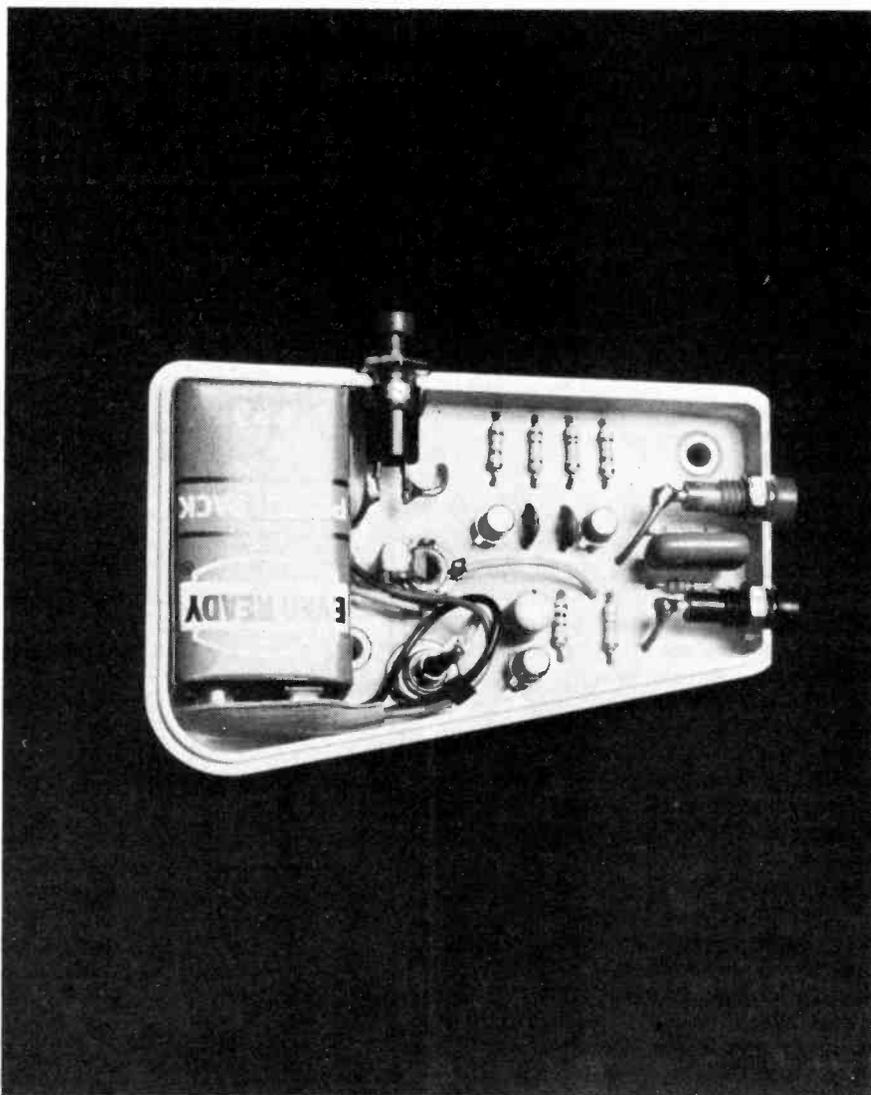
### MISCELLANEOUS

PP3 battery, battery clip, 2 mm plugs, probe, phono plug, screened wire, flex, crystal ear-piece fitted with 3.5 mm jack plug.  
Cost ≈ £3.50.



# METRONOME

THE TRADITIONAL metronome is well-known to those who have learnt the piano for beating out the time - these mostly operate by clockwork.

A variable beat with a far greater range than the mechanical types is very easily produced electronically, especially if a unijunction transistor is used as a relaxation oscillator.

In our circuit we have opted for a tantalum capacitor for C1; an electrolytic can be used but due to the enormous tolerance spreads (usually +100% to -50%) the range can be very different from that of our prototype.

A volume control is hardly necessary but we have included a preset control which can be adjusted from outside the box which can be used to attenuate the level considerably: a low volume is almost essential when using an earphone.

RV1 sets the 'beat' and can be log or lin but a log type wired as reverse log gives a smooth calibration over the range which varies from 30 beats per minute to 400 beats per minute. Calibration can easily be done using a watch.

The normal nominal impedance of small speakers is 8 ohms and that is what we have used but higher impedance types will work.

Construction is very straightforward. We have used a small pcb but there's nothing to prevent other constructional methods from being used.

## USES

The use of a metronome for a musician is well-known but there are other applications. People learning to touch-type now sometimes use a regular beat to improve performance.

There are other areas where a metronome may be of use - in curing stammering. We know of someone who was helped enormously by the use of a metronome set at the fairly critical frequency of 50 beats per minute. We have marked this as an asterisk on our calibration.

However we have checked with a qualified speech therapist and it seems that this use of a metronome is not so widely recognised as an aid as it once was. What they would say was that 'In some cases, it could help, but not always.'

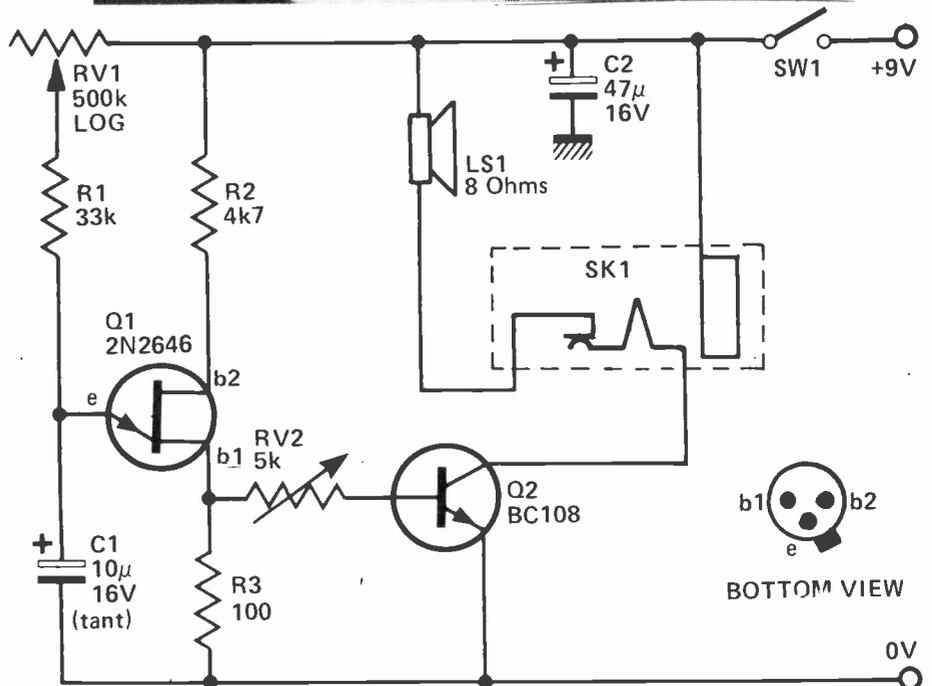
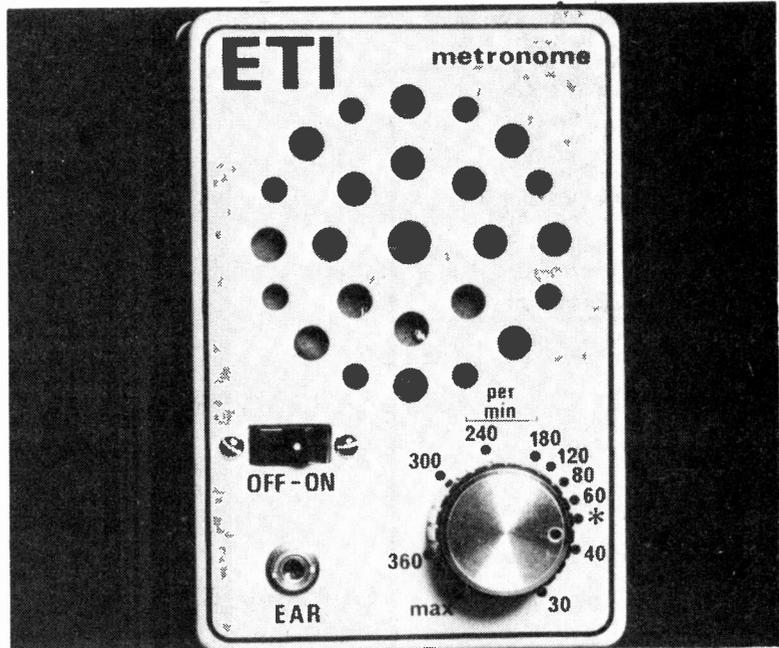


Fig 1. Circuit diagram for the metronome. SK1 switches off the L.S. upon insertion of the earpiece. The connection diagram is for the 2N2646.

## How it works


The circuit makes use of the special properties of a unijunction transistor, Q1. When voltage is applied to the circuit, C1 charges up through RV1 and R1, the rate at which it charges depending on the setting of RV1.

When the voltage is at the emitter of Q1 reaches a certain level, this effectively shorts out the two bases. This raises the voltage at

the junction of R3/RV2 briefly and C1 is discharged through R3 enabling the cycle to start again. The waveform across R3 appears as a series of short spikes.

RV2 acts as a crude volume control as it passes these spikes to Q2 which is switched on and off in sympathy in turn passing the burst of voltage to the speaker or the earphone.

# Short Circuits

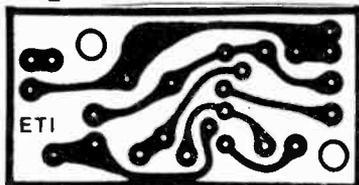

## Parts List

RESISTORS all ½ W, 5%

R1 33 k  
R2 4k7  
R3 100

CAPACITORS

C1 10µ 16 V tantalum electrolytic  
C2 47µ 16 V electrolytic

SEMICONDUCTORS

Q1 2N2646 unijunction  
Q2 BC108 or similar

POTENTIOMETERS

RV1 500 k log rotary  
RV2 5 k lin trim type

SWITCH

SW1 On-off rocker switch

SOCKET

SK1 3.5mm panel jacket socket

SPEAKER

LS1 8 Ω (2½" - 2¾") type

CASE

Norman P.B.1 or similar  
(4½" x 3" x 1½" / 115mm x 75mm x 35mm)

MISCELLANEOUS

PP3 battery, battery clip, knob, nuts, bolts, etc, pcb as pattern, wire, 8Ω earpiece with 3.5mm plug.


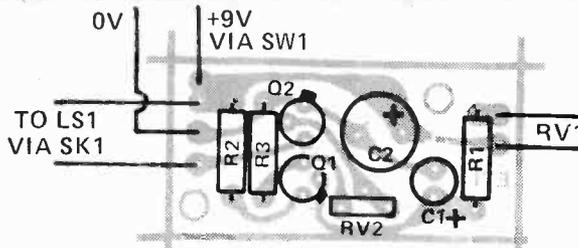


Fig 2. Overlay for the metronome. RV2 is mounted vertically to allow adjustment. Take care with the semiconductor connections.

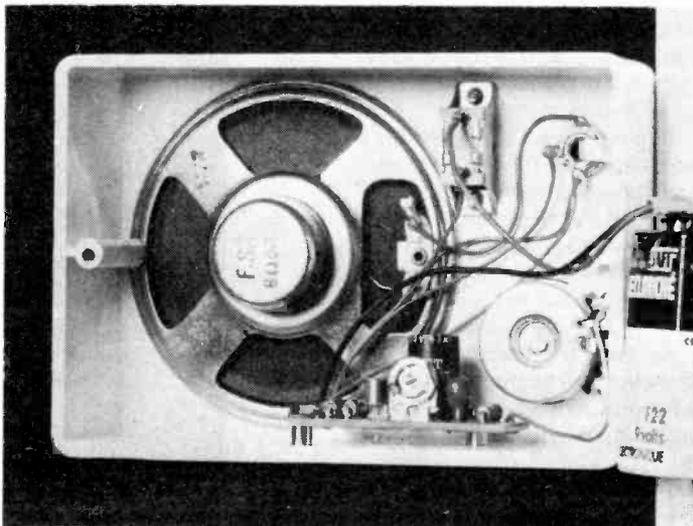

RV2, the preset volume control can be clearly seen on the pcb. A hole is drilled in the back panel to allow this to be adjusted by screwdriver when need be, which is surely infrequently. The rate control down on the right works most effectively if a log control wired in 'reverse log' is employed.


## A MINIATURE POWER TOOL

*to speed your building*

- Super 30 Kit (30 Tools)  
(incl. drill without stand).  
**£17.62** plus P&P 85p
- Mk. II Drill Stand  
**£4.40** plus P&P 35p
- Mk. II Drill only  
**£8.79** plus P&P 35p
- Flexible Drive Shaft  
**£5.46** plus P&P 25p
- Transformer 240V  
a.c./12V d.c.  
**£6** plus P&P 70p
- Variable Speed Transformer.  
**£8.25** plus P&P 70p

Replacement drills, stones, burrs, etc., 40p each. Circular saw blades 50 each. £2 per set of 4 sizes. P&P any quantity 20p.

All VAT inclusive

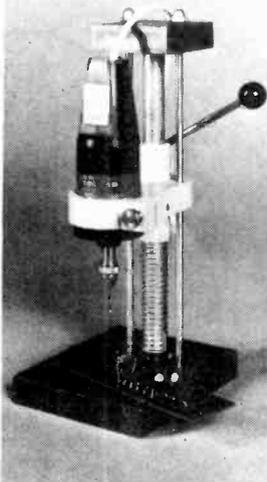

## PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11

8HG Tel. 01-977 0878 (24-hour answering service)


9" x 4" S.A.E. please for leaflet and order form

## DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

## POWER SUPPLY

**£19.95**  
+ S

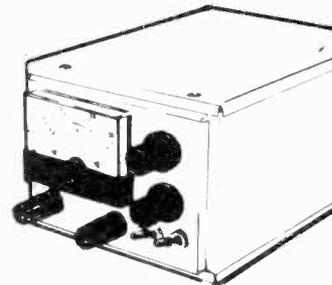

An invaluable piece of equipment for the enthusiasts workshop. This 3-30V d.c. power supply fulfills virtually all experimentation requirements. Avoid frustration and circuit damage with the variable current limit (0.1A max). Regulation typically better than 0.5% (max 3%). Ripple voltage typically better than 20mV (max 120mV).


£19.95 + S VAT (Order 997-027). Subject to availability

Overseas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD.  
P.O. BOX TR8, WELLINGTON RD IND. EST., LEEDS LS12 2UF

An Electrocomponents Group Company

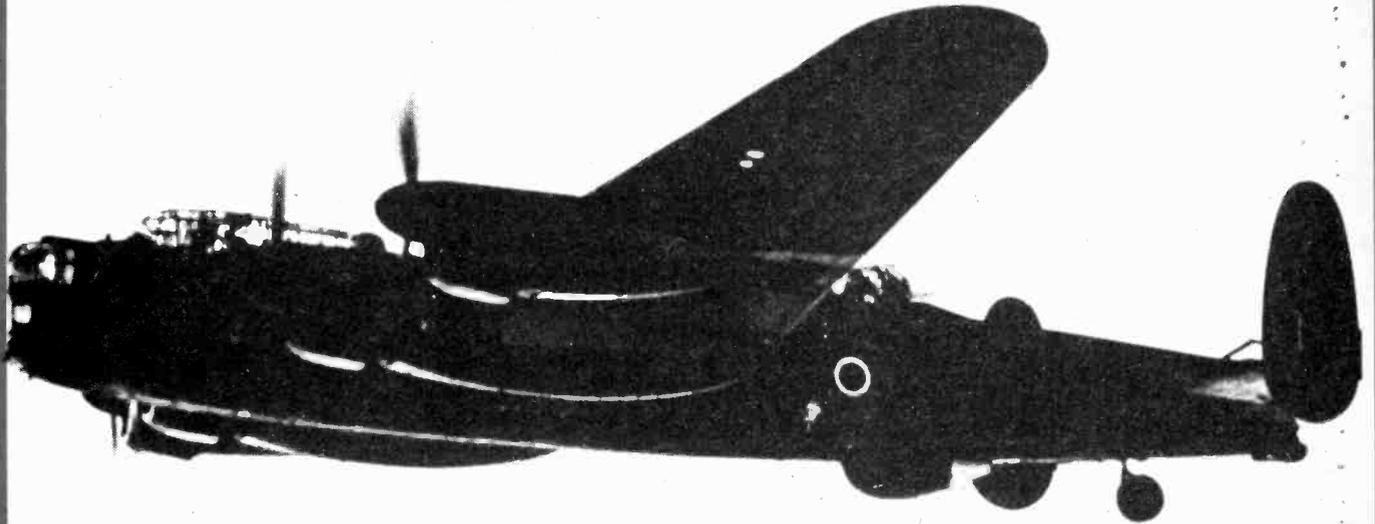AS A RECENT TELEVISION SERIES DEMONSTRATED, THE USE OF RADAR BY BOTH SIDES IN WORLD WAR II WAS OF CONSIDERABLE STRATEGIC IMPORTANCE, WITH THE ADVANTAGE SHIFTING FROM ONE SIDE TO THE OTHER WITH EACH NEW DEVELOPMENT. THIS IS THE STORY OF ONE KEY INVENTION WHICH SWUNG THE BALANCE CONSIDERABLY AND WHICH CONTRIBUTED MUCH TO OUR UNDERSTANDING OF ELECTRONICS.



# THE VALVES THAT WON THE WAR

BY IAN SINCLAIR

# THE VALVES THAT WON THE WAR

THE ESSENCE OF RADAR is that radio signals sent out from a transmitter will reflect from a target which is large compared to the wavelength of the signals, and the reflected signals can be picked up on a receiver.

The time delay between transmission and reception is then a measure of the range of the object which is reflecting the waves. The wavelength which can be used is of considerable importance, since short wavelengths can detect smaller targets and also need smaller aerials. If we want to use reasonably small aerials and to detect objects about the size of an aircraft, then we must use wavelengths of about one metre or less. The methods which we use to generate these wavelengths are therefore of great importance, and the amount of power which can be delivered to the aerial will decide what range is usable, since the received signal can be detected only if it has an amplitude greater than the noise level of the input stage of the receiver.

Thanks to the use of low-noise input stages, pulse gating, and correlation techniques, we can now recover signals which have apparently been lost in noise, but these techniques were not available in the years of the war.

## REFLECTIONS AND SHORTENING

Early radar experiments used standard or slightly modified short-wave radio transmitters, with power output stages which were usually large air-cooled triodes with conventional inductor-capacitor tank circuits. In the early experiments, detection was considered more important than range-finding, and the received signal was allowed to beat with a fraction of the transmitted signal to form a slowly changing beat note from a moving target. These arrangements were sufficient to show that the reflected waves could be detected, but the wavelength was too long (frequency too low) and the power too small for radar as we now know it.

What was needed was a generator of waves of much higher frequency and much greater power. In addition, if such a generator could be made small enough to be carried in an aircraft, a substantial advantage in night bombing would be obtained.

Using conventional triodes, this was impossible. The stray capacitances of a large triode are so large that even the inductance of a short piece of straight wire gives a tuned circuit whose frequency is too low (assuming that oscillation takes place). The power output of such a valve at extremes of frequency is too low in my case.

Fortunately, as so often happens, the foundations for a new type of construction were already laid. These foundations were the magnetron effect on electron beams, and the resonant cavity tuning system.

## MAGNETIC SPACES

When electron beams travel from a hot cathode to a positively charged anode, the speed of the electrons is decided by the voltage applied between anode and cathode. Equating the potential energy,  $eV$ , with the kinetic energy  $\frac{1}{2}mv^2$ , for each electron we get:

$$eV = \frac{1}{2}mv^2, \text{ where } \begin{array}{l} e = \text{electron charge} \\ V = \text{accelerating voltage} \\ m = \text{electron mass} \\ v = \text{electron speed} \end{array}$$

From this equation, the electron speed,  $v = \sqrt{\frac{2eV}{m}}$

Using modern units, the ratio  $e/m$ , the specific charge of the electron, is  $1.76 \times 10^{11} \text{ C kg}^{-1}$ , so that for 5kV accelerating voltage, the speed of the electron is about  $4.2 \times 10^7 \text{ ms}^{-1}$ , some 42 million metres per second. At this speed, an electron will cover a distance of 1 cm in 0.24 ns, so that we should have no trouble in generating oscillations of a comparable wavetime if we can use such a beam in an oscillating system.

Now if we apply a magnetic field to such a beam, and direct the magnetic field so that it is at right angles to the direction of motion of the electrons as they enter the field, the path of the electrons will be an arc of a circle whose axis is the magnetic field direction. Equating the magnetic force,  $Bev$ , on a moving electron with the force needed to move an electron in a circular path,  $\frac{mv^2}{r}$  we have:  $Bev = \frac{mv^2}{r}$ , so that  $r = \frac{mv}{Be}$

## BEAM BENDING

Using the value of speed given above, to bend the electron beam into a circle of radius 1 cm needs a magnetic field strength of about  $2.4 \times 10^{-2} \text{ Wb m}^{-2}$ , about one thousand times the magnetic field strength of the Earth. This is not a particularly large field strength, and it was attainable by either permanent or

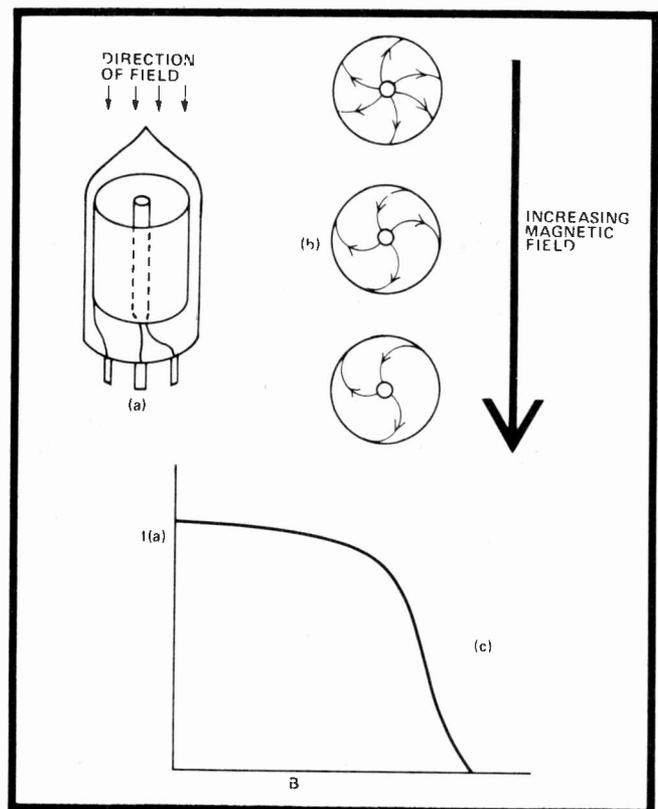


Fig 1. The magnetron effect. (a) Simple magnetron valve, magnet not shown. (b) Paths of electrons as the strength of the magnetic field is progressively increased. (c) Graph of anode current against magnetic field.


electro magnets. All of this basic theory has been known since early in the century due to the work of J. J. Thomson on the specific charge of the electron.

Later work had made use of the magnetron effect to measure the specific charge of the electron in a different way, as shown in Fig. 1. A tubular cathode emits electrons which are accelerated to a circular anode coaxial with the cathode. When a magnetic field is directed along the axis of the tube, the path of the electrons curves, and becomes more curved as the strength of the magnetic field is increased. If we plot a graph of anode current against magnetic field strength, the graph shows current dropping as fewer electrons reach the anode, and then reaching zero when the magnetic field is strong enough to prevent the fastest electrons from reaching the anode. Using such a "magnetron" valve made to accurately known dimensions, the value of  $e/m$  for the electron could be found to very close limits. The great breakthrough in radar was to realise that this valve structure could be combined with resonant cavities to enable us to generate oscillations in the GHz region.
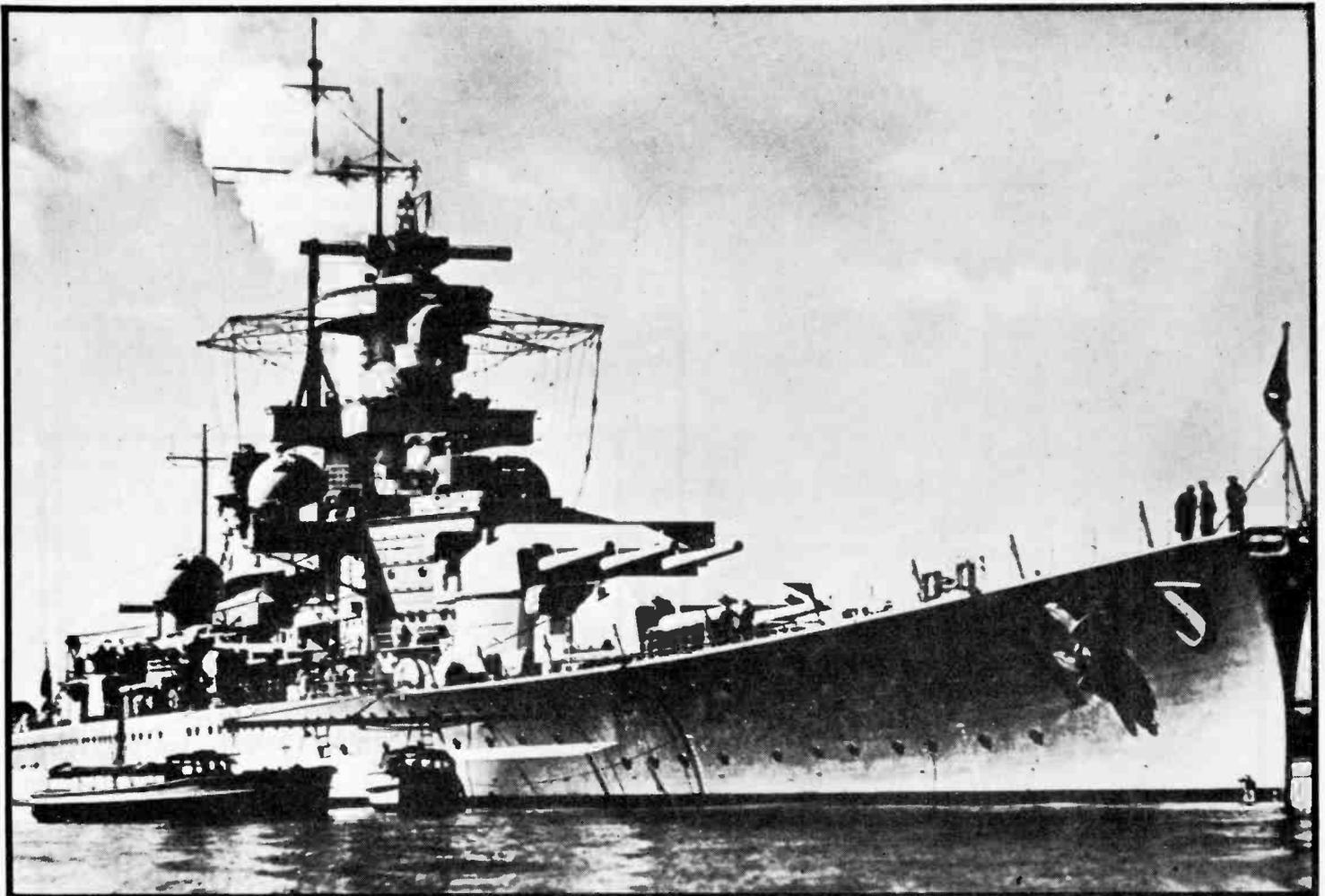
## RESONANCE

In the study of sound waves, any space may have resonances, meaning that sound waves of certain wavelengths, related to the dimensions of the space, will be emphasised; these are resonant frequencies, and designers of loudspeakers go to great lengths to get rid of them. A tube is one type of resonant space, and organ pipes and other wind instruments are examples of resonant tubes used to generate sound waves of various frequencies.

A tube which is resonant to one particular frequency will generate this frequency if the air in the tube is set into oscillation by any disturbance. An example of particular interest in this case is the flute. In this instrument, the player blows air across a small hole in a resonant tube. Air striking the edge of the hole (controlled by the players mouth-shape) builds up a pressure wave which sets the air in the tube into oscillation at its resonant frequency, and the resonant waves in the tube then make the air passing across the hole flutter, keeping up the oscillation. What we have here, translating into familiar electronic terms, is a d.c.



*The mighty Scharnhorst. One of Germany's new generation of capital ships. As modern as anything then afloat, fast enough to outrun anything which could outgun her, and armed sufficiently to sink anything fast enough to catch her. Yet the Scharnhorst fell victim to the Magnetron!*

*The battle of North Cape was the battle which proved the importance of radar in surface engagements. Leaving Norway to attack convoy JW 55B the Scharnhorst was dogged by a series of disasters and unfortunate decisions by High Command which led her, on December 26th 1943 in appalling weather to face the British cruisers Belfast, Norfolk and Sheffield — all radar equipped and using it! Scharnhorst herself had radar equipment, but standing orders prevented its use (as a measure against breaking radio silence!) In the engagement which followed the British ship directed their fire with radar, and by chance destroyed the Scharnhorst radar!*

*They followed her on radar until the battleship Duke of York came up to engage, also using radar, with her superior armament. Scharnhorst was sunk. Her superior speed and firepower were of no avail.*

*On New Year's Day 1944 Admiral Dönitz reported to Hitler "Without serviceable radar equipment it is no longer possible for surface forces to fight the enemy."*

# THE VALVES THAT WON THE WAR

supply (the player's breath), a resonant tuned circuit (the tube of the instrument), and positive feedback (the effect of the resonant waves on the breath stream).

A similar effect can be expected using a beam of electrons. A circular cavity cut into a block of metal will act as a tuned circuit, using the inductance of the conducting material and the stray capacitance between sections at (momentarily) different potentials. This is a resonant cavity, and the wavelength of resonance is related to the size of the cavity. When such a cavity oscillates, both electric and magnetic fields will exist, and these will be rapidly alternating fields, going through a cycle of building up in one direction, dying away, reversing, building up in the reverse direction, dying away and so repeating millions of times per second.

Can we carry the similarity a little further, and imagine a small slot in the cavity? At such a slot, alternating electric and magnetic fields will exist, and these will alternately repel and attract an electron beam which is just skimming past the slot like the breath of the flautist. Would such an arrangement give enough positive feedback to keep a resonant cavity oscillating? At the beginning of the war, only experiment could decide, and it fell to Randall and Boot, working at

Birmingham, to perform the crucial experiment, so creating the first cavity magnetron oscillator. This valve was capable of supplying U.H.F. oscillations at power levels greatly in excess of any previously obtained at such frequencies, the perfect answer to the demands of the radar system.

## CAVITY MAGNETRON

The cavity magnetron combines the principles of the resonant cavity with the earlier magnetron valve. The cathode is a tube coated with electron emitting material, and with a heater winding inside for starting the electron emission. The anode is metal block, finely machined to a circular profile with a set of resonant cavities breaking into the inner surface of the block. The whole valve is evacuated and sealed, and then mounted between the poles of a strong permanent magnet. Since it would be inconvenient to run the cathode at earth potential and have the metal anode and its cooling fins positive, the anode is earthed (and connected to waveguide through a thin "window") and the cathode run at a negative voltage.

When an accelerating voltage exists between the anode and the cathode, the electrons are accelerated from the cathode, and the magnet shapes the beam so that its shape is circular, brushing past the ends of the cavities as it tries to reach the anode. For a given strength of magnet, the voltage between anode and cathode would have to be the correct value for the beam to take the correct path, but this value is fortunately not too critical. The movement of the beam excites the cavities into oscillation, and the oscillating cavities in turn will alternately repel and attract the beam.



Fig 3. A coastal defence tower. Standing some 360 ft high, the apparatus was used to detect low flying intruding aircraft which were flying too low for normal stations to detect them. Lone raiders often adopted this tactic to reach specified targets, or to make photographic records.


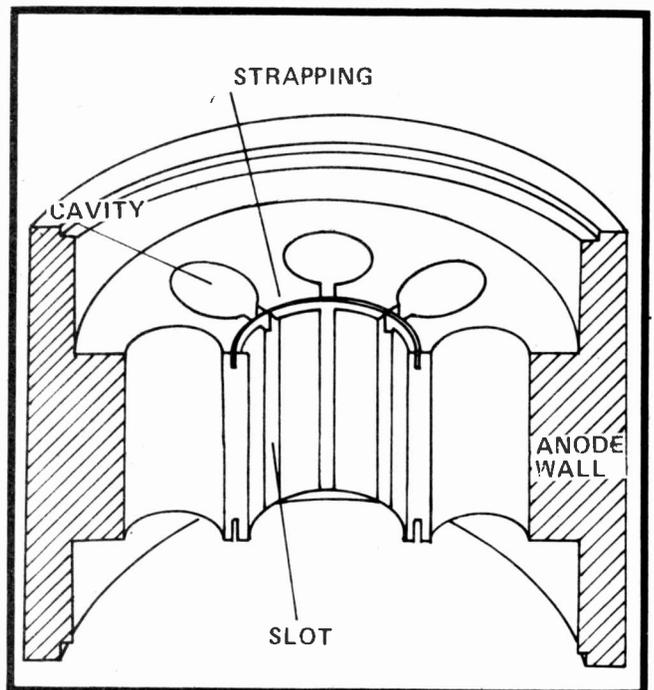


Fig 4. Cross-section of a cavity magnetron, which in this case uses cavities of cylindrical shape, linked to the anode by slots. The strapping links can also be seen. Other cavity shapes are also used.

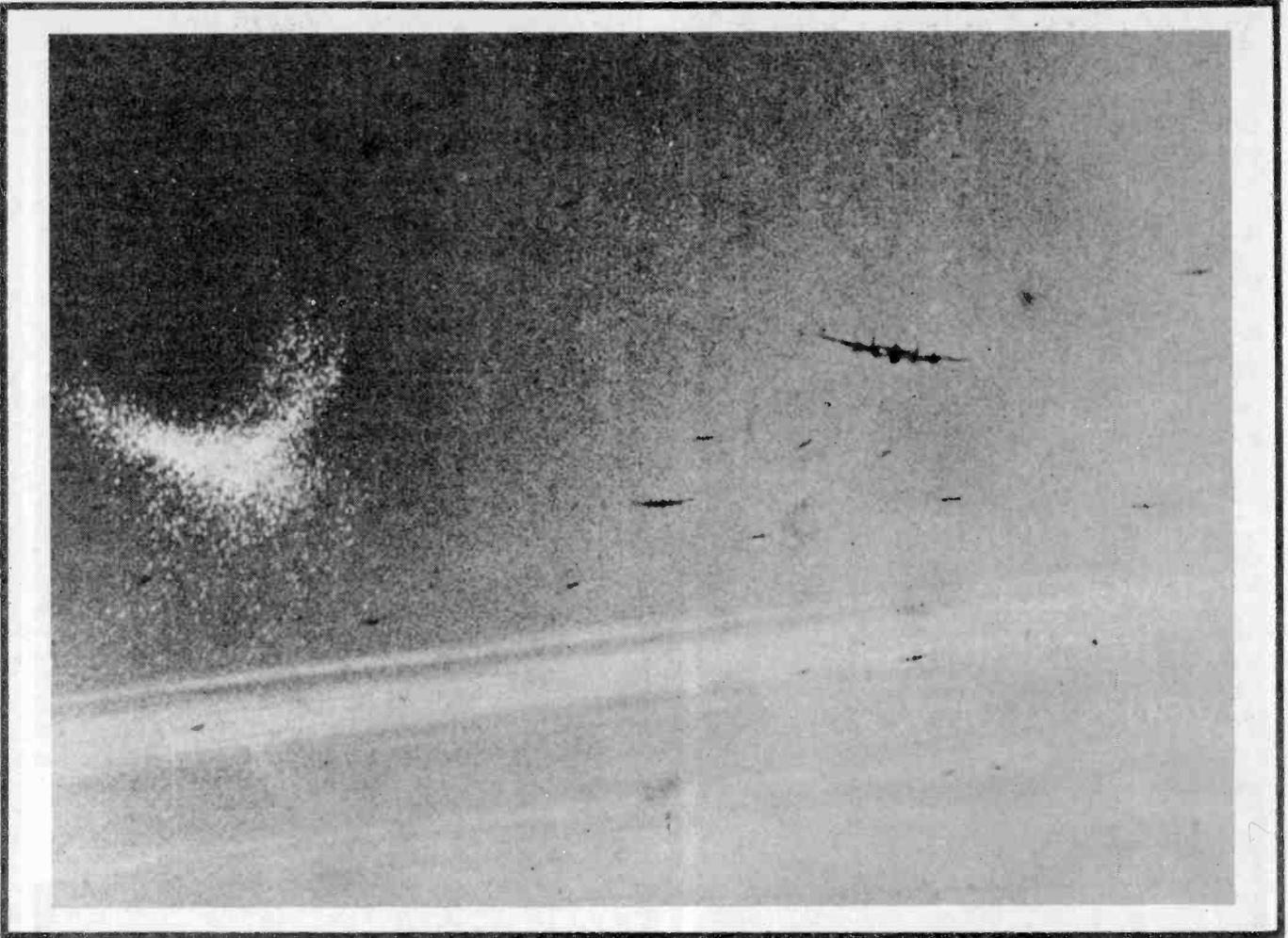

The photograph shows a Lancaster bomber dropping "window." This was shredded aluminium foil, dropped to confuse German ground radar. The beams were scattered by the foil, giving totally erroneous readings upon re-receipt. In the background can be seen some of the other aircraft in the raid, in this case a 1,000 bomber attack on Essen.

The foil is the silvery shimmer to the left of the photograph, scattering as it falls.

## COMBINATION LOCK

The combination of these effects causes the beam alternatively to strike and then be repelled from the anode, so that the oscillations in the cavities can have very large voltage amplitude, of the order of the applied voltage. Similarly, by using a large cathode, high beam currents are possible so that the peak power developed in one cycle of oscillation can be very large. At the same time, the size of the magnetron is modest, since the radius of curvature of the electron beam is small, and the power dissipated would melt the anode if the beam were applied continuously. The answer here was to pulse the beam by applying a short (1  $\mu$ s or less) negative pulse of several kV amplitude to the cathode at a repetition rate of 1 000 pulses per second or so. By using this technique, the power developed during a pulse, which could be of thousands of cycles of the microwave frequency, could be many kilowatts, giving excellent range, yet the average power, and hence the heat dissipation, would be only a thousandth of this value, since the valve would be on (in this example) for only one/microsecond in each millisecond.

## DEVELOPMENTS

Inevitably some development was needed. The early cavity magnetrons were unstable, changing frequency for no apparent reason. This is a problem which also

afflicts those learning to play wind instruments, because all resonant cavities will resonate to harmonics (multiples of frequency) of the lowest note which is possible (the fundamental). The resonant cavities of the magnetron have the further complication that two sets of oscillations are taking place in them, oscillations of magnetic field and oscillations of electric field. The cure was to shape each cavity to make one mode of oscillation dominant, and to use cavities which were interconnected, with alternate cavities "strapped" so as to reinforce the desired frequency of oscillation.


In addition, the tendency of magnetrons to burn out their cathodes too quickly was found to be due to the extra heating caused by the beam current. This could be counteracted by using the heater only for starting the tube, switching it off whenever the magnetron started to oscillate so that the beam current could then provide the heating.

## FROM THE NORTH CAPE TO OVENS

Nowadays, the magnetron is still the high power, high frequency microwave signal source, used in radar, in microwave ovens, and in materials research. The advantage which the cavity magnetron gave us during the war was of major importance, and the advantage, unlike so many others before and since, was never quite lost.
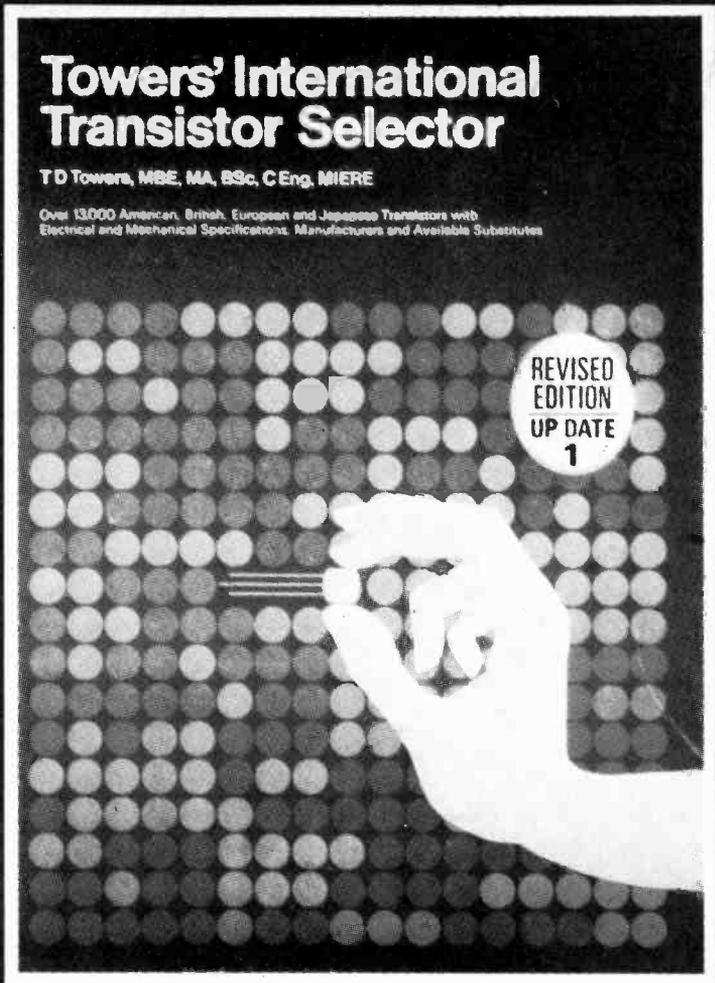
# UPDATE 1: 3,4000 more Transistor Substitutes

The most  
comprehensive,  
low-cost,  
single volume  
coverage  
of transistors  
you can buy.



# We've got the new one!

**COMPLETELY REVISED. 30% MORE COVERAGE. ONLY £5.00 INC. P & P.**

When the first edition of this excellent book was published in 1975 ETI was the first to offer it.

We are doing it again!

UPDATE 1 increases the coverage of transistors by about 30% on the first edition.

European Proelectron Standard devices increase by 1500 and now ensure a very comprehensive coverage of Philips, Siemens, Telefunken and Texas Instruments in Europe.

The Japanese 2S Standard Devices coverage has been increased from 1,850 to 3,000 and a further 800 American 2N devices have been selected.

The original 10,000 entries have been fully edited and this new production has been clearly printed from new computer setting.

Your order will be processed on the day of receipt.

**To: ETI BOOK SERVICE  
PO. BOX 79, MAIDENHEAD, BERKS SL6 2EG**

Please send me \_\_\_\_\_ copies of  
Towers' International Transistor Selector  
Revised Edition Up Date 1 at £5.00 each inc. p&p.

I enclose cheque/postal order for £ \_\_\_\_\_  
made payable to ETI BOOK SERVICE.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

ET15

# TECHNICAL BOOKS FROM ETI

## CALCULATORS

**99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR**  
L. Frenzel £4.50

**SCIENTIFIC ANALYSIS ON YOUR POCKET CALCULATOR**  
Smith £9.85

## COMPUTERS AND MICROPROCESSORS

**COMPUTER CIRCUITS AND HOW THEY WORK**  
B. Wells £1.80

Become acquainted with the various parts of a computer and its technology

**COMPUTER TECHNICIANS HANDBOOK**  
B. Ward £3.25  
This giant volume compares to a 1 000 hour course on computer mechanics

**DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS**  
N. M. Morris £2.90

The ideal book for the enthusiast confused by logic and digital techniques

**MICROPROCESSORS** £11.75  
L. Altman  
Gives a general overview of the technology design ideas and practical application

**MICROPROCESSORS** £8.30  
D. C. McGlynn  
Technology Architecture and Applications. This introduction provides a clear explanation of this important new device

**MICROPROCESSORS AND MICROCOMPUTERS** £18.00  
B. Soucek  
Describes the application programming and interfacing techniques common to all microprocessors

## ELECTRONICS

**ACTIVE FILTER COOKBOOK**  
D. Lancaster £10.75

Everything you need to know to build and use active filters

**ELECTRONIC ENGINEERS REFERENCE BOOK — 4th EDITION**  
L. W. Turner £27.60

A completely new and up-to-date reference book for all engineers and students

**BASIC MATHS COURSE FOR ELECTRONICS**  
H. Jacobowitz £1.75

Quick short cut way to learn the language of maths as applied to electronics

**DESIGNING WITH TTL INTEGRATED CIRCUITS**  
Texas Instruments £8.95

Covers the entire family of TTL and practical applications of circuits in digital systems

**ELECTRONIC MEASUREMENTS SIMPLIFIED**  
C. Hallmark £2.10

Covers just about every conceivable test or measurement you will need

**ELECTRONICS POCKET BOOK**  
P. McGoldrick £4.15

**ELECTRONICS AND PHOTOGRAPHY**  
R. Brown £2.20

Practical circuit projects devoted to photography

**ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS**  
N. M. Morris £1.20

Handy reference book includes a section on SI units, resistor colour codes and preferred values

**FIRE AND THEFT SECURITY SYSTEMS**  
B. Wells £1.90

Selection and installation, home maintenance and business security devices

**HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS**  
B. Brown £1.85

Everything you need to know from basic circuit components to integrated circuits

**HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS**  
J. Shields £3.25

A practical do-it-yourself book

**HOW TO USE IC CIRCUIT LOGIC ELEMENTS**  
J. Streater £3.55

Helps those unfamiliar with digital logic circuits

**INTEGRATED ELECTRONICS**  
J. Millman £7.60

Using an IC approach the text leads the reader step by step from semiconductor physics to devices, models, circuits and systems

**IC OP-AMP COOKBOOK**  
W. Jung £9.20

Covers the basic theory of IC op-amps in great detail, also includes 250 practical circuit applications

**LINEAR INTEGRATED CIRCUIT APPLICATIONS**  
G. Clayton £4.90

A practical approach is emphasised throughout, encouraging the reader to try out devices himself

**LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS**  
E. M. Noll £6.20

An introduction to one of electronics most exciting devices

**110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85

Outlines the essential characteristics of op amps and presents useful projects

**110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85

Introduces the reader to FET's, SCR's and IC's with full construction details of many useful circuits

**110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £3.10

**110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85

All the projects have been devised, built and fully evaluated by the author

**110 THYRISTOR PROJECTS USING SCR'S**  
R. M. Marston £2.85

A companion to the author's previous books

**MOS DIGITAL IC'S**  
G. Flynn £4.50

This book contains information about MOS and CMOS from basic construction to circuit application

**OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS (Burr Brown)**  
G. Tobey £7.30

Covers the entire field of operational amplifiers

**PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES**  
L. Garner £2.85

Complete information on circuit operations, troubleshooting charts and service procedures

## NEW BOOKS

**THE OSCILLOSCOPE IN USE**  
Ian Sinclair £3.00

A practical handbook aimed at the more advanced enthusiast

**110 ELECTRONIC ALARM PROJECTS**  
R. M. Marston £3.35

The latest in this popular series

**MICROELECTRONICS**  
C. L. Hallmark £3.80

How they're fabricated, how to test them

**TV TYPEWRITER COOKBOOK**  
Don Lancaster £7.00

All the circuitry and explanations for making your own VDU

**PRACTICAL ELECTRONIC CIRCUIT BUILDING**  
Ainslie and Colwell £2.35

A concise introduction to some of the modern methods of project building

**PRINTED CIRCUIT ASSEMBLY**  
Hughes and Colwell £2.35

Abundant information on making and assembling PCBs

**ELECTRONIC DIAGRAMS**  
M. A. Colwell £2.35

Comprehensive information on circuit symbols and diagrams

**ELECTRONIC COMPONENTS**  
M. A. Colwell £2.35

Information on the different types of components and their selection

**OP AMP CIRCUIT DESIGN & APPLICATIONS**  
I. Carr £3.90

\*Design your own functional circuits as well as adapt the author's designs to your own requirements

**PRACTICAL SOLID STATE D.C. SUPPLIES**  
Towers £6.10

Up-to-date, state-of-the-art, coverage of D.C. supplies

**PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER**  
R. Fox £2.15

Thyristor theory and practical circuits with low cost SCR TRIAC's and DIAC's

**PRINCIPLES OF TRANSISTOR CIRCUITS**  
S. Amos £4.40

Generally accepted as being a standard textbook on fundamental principles underlying the design of circuits and using transistors

**RAPID SERVICING OF TRANSISTOR EQUIPMENT**  
G. King £2.85

A systematic guide to the servicing of transistor radio, television, tape and hi-fi equipment

**SEMICONDUCTOR CIRCUIT ELEMENTS**  
T. D. Towers £6.30

Gives readers an account of all semiconductor devices commercially available, for each device it covers a general description, circuit diagram symbols and working principles

**SOLID STATE CIRCUIT GUIDE BOOK**  
B. Ward £2.15

Step by step instructions to design circuits to your own specifications

**TRANSISTOR CIRCUIT DESIGN**  
Texas £9.25

**TTL COOKBOOK**  
O. Lancaster £7.00

Complete and detailed guide to TTL, how it works, how to use it and practical applications

**UNDERSTANDING ELECTRONIC CIRCUITS**  
R. Sinclair £4.00

Describes various circuits encountered today with a strong emphasis on fault finding and servicing procedures

**UNDERSTANDING ELECTRONIC COMPONENTS**  
R. Sinclair £4.00

Explains about components and bridges the gap between elementary textbooks and unapproachable advanced treatments

**UNDERSTANDING CMOS INTEGRATED CIRCUITS**  
R. Melon £3.80

Begins with basic digital IC's, covers semiconductor physics, CMOS fabrication technology and design

**UNDERSTANDING SOLID STATE CIRCUITS**  
N. Crowhurst £1.90

Written to service the interests of anyone at sub-engineering level

## ELECTRONIC ORGAN BOOKS

**TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR**  
A. Douglas £4.90

Written in a simple style, this gives a complete explanation of everything to do with transistorized organs and is profusely illustrated with clear diagrams

**THE ELECTRONIC MUSICAL INSTRUMENT MANUAL**  
A. Douglas £8.00

A comprehensive guide to the theory and design of electronic musical instruments

## SEMICONDUCTOR DATA

**POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE** £2.15

Substitution data for both valves and transistors in one new volume

**RADIO VALVE AND SEMICONDUCTOR DATA**  
A. M. Ball £2.50

Characteristics of 1 000 valves, cathode ray tubes, transistors, diodes, rectifiers and optical semi-conductors. This new edition (1975) is right up to date and over 450 000 copies have been sold

## RADIO AND TELEVISION

**FOUNDATIONS OF WIRELESS AND ELECTRONICS**  
M. G. Scroggie £4.35

(New 1975 edition). Covers the whole basic theory, no previous technical knowledge is assumed

**COLOUR TELEVISION THEORY** £6.10  
Hutson

## TEST EQUIPMENT AND OSCILLOSCOPES

**BASIC ELECTRONIC TEST PROCEDURES**  
I. M. Gottlieb £2.35

Shows how to get accurate measurement with VOM's, meters and oscilloscopes

**THE OSCILLOSCOPE**  
G. Zwick £2.10

Starts from the first principles and takes the reader to an advanced level

**PRACTICAL TEST EQUIPMENT YOU CAN BUILD**  
W. Green £2.15

For technicians, radio, TV service operators and serious experimenters

**TEST INSTRUMENTS FOR ELECTRONICS**  
M. Clifford £2.30

Easy modifications to your VOM, VTVM and scope with the aid of this book

**WORKING WITH THE OSCILLOSCOPE**  
A. Saunders £1.85

Includes workshop test projects with large size drawings

**SERVICING WITH THE OSCILLOSCOPE**  
G. King £5.00

Includes a unique series of photographs showing oscilloscope traces to be found in normal and faulty equipment, stereo radio, colour TV. Circuits servicing is dealt with

### HOW TO ORDER

All prices are correct at the time of going to press but are subject to alteration without notice. All prices include postage. Please print your name and address clearly and list each title and price separately. Cheques and postal orders should be made payable to ETI Book Service. Books are sent on seven days approval against a full cash remittance, plus postage. Book stock is not held at ETI's London offices and orders should be sent to: ETI BOOK SERVICE, P.O. BOX 79, MIDDEHEAD, BERKS SL6 2EG.

# ETI DATA SHEET

## LM1812 ULTRASONIC TRANSCIVER

NATIONAL

The LM1812 is a special monolithic IC which consists of a 12W ultrasonic transmitter circuit, which uses novel circuitry to eliminate costly alignment adjustments, a selective receiver which uses only one external LC network, impulse noise rejection circuitry, a 10W display driver, and a keyed modulator. The system operates from a 12V battery, drives power into a transducer, receives an echo and drives a display lamp. A single LC network is time shared between the receiver and the transmitter to reduce external parts, to eliminate alignment labour and to guarantee that the received signal is always of the proper frequency.

### TRANSDUCERS

Transducers are available for use either in water or air. The appropriate transducer is important for proper functioning in the intended application; for example, the high frequency attenuation in air usually requires a lower operating frequency. The modifications for a 40 kHz system are shown.

### LAYOUT

As the LM1812 contains both a transmitter and a receiver in proximity, PC layouts or breadboarding has to be done with special attention to ground loops and common coupling paths. The use of three ground pins on the IC package helps reduce grounding problems, but at the time of transmission, with the display driver also ON, there can be 1-2A of peak current passed into the ground trace.

### INTERFERENCE


Local sources of High energy impulse noise, if not locally shielded, can cause an unwanted display "blip."

A small valued capacitor (approximately 30 pF) can be connected across the first receive stage (between pins 3 and 4) to reduce the bandwidth and filter out these noise pulses.

Impulse noise is rejected by the combined action of the "Pulse Train Detector" and the "Integrator" circuits. The integrator requires a number of cycles of valid returns to be received before turning ON the display driver. The pulse train detector will dump the integrator if a continuous train of pulses is not received (if 2 or 3 are missing, the integration capacitor is discharged to ground).
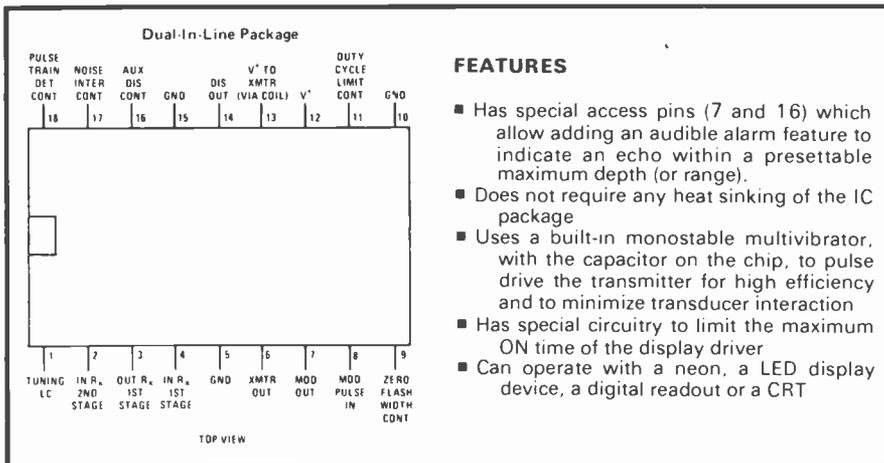
### POWER LEVELS

For ranging applications, large transmit power levels are necessary due to the two-way path and the resulting received echo power falling as the fourth power of range (additional external receiver gain can be used to extend the range). One way communication links can use reduced power. Transmit power can be checked by measuring the voltage swing across the transducer (of known impedance) during the transmit mode. The magnitude of the transmitter power depends on the transducer impedance as presented to the transmitter power amplifier (usually a transformer is used to couple the transducer to the power amplifier). A minimum value of 10Ω causes



### FEATURES

- Has special access pins (7 and 16) which allow adding an audible alarm feature to indicate an echo within a presettable maximum depth (or range).
- Does not require any heat sinking of the IC package
- Uses a built-in monostable multivibrator, with the capacitor on the chip, to pulse drive the transmitter for high efficiency and to minimize transducer interaction
- Has special circuitry to limit the maximum ON time of the display driver
- Can operate with a neon, a LED display device, a digital readout or a CRT

### DISPLAY CONTROL


The collector of a grounded-emitter NPN transistor can be tied to pin 16 to allow an auxiliary control of the display driver. This transistor should normally be held OFF and should go ON for a time interval no longer than 1 ms if a neon display is used, due to the rapid current build-up in the primary of the step-up transformer. If a LED is used as a display device with a series limiting resistor, this ON time can be made longer as it is now limited only by the increased dissipation of the IC which results from the saturation voltage at pin 14 and the ON current of the LED.

### AUDIO

An IC audio amplifier can be used to amplitude modulate the carrier for an AM commu-

approximately 1A peak current pulses out of this power amplifier. The inductance of the secondary should be designed to resonate with the sum of the capacitance associated with the cable feeding the transducer and that of the transducer. The low Q resonance allows transducer replacement without tuning.

An internal one-shot multivibrator with a fixed time of 1 μs is used to drive the transmitter power amplifier into saturation for this time period once for each cycle of the transmit frequency. At a frequency of 200 kHz, this results in a high efficiency class-C type of operation for the power amplifier. The transmit frequency is equal to the natural resonance of the external LC network which is tied to pin 1. This network is also used to establish the centre frequency and the selectivity of the receiver.

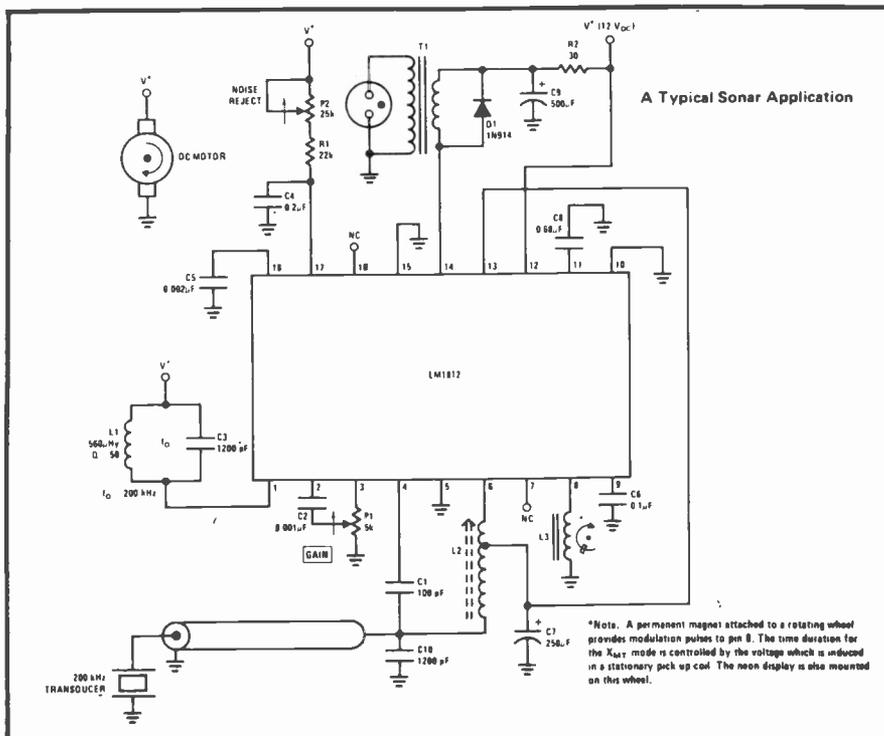


nication link. A high-input impedance detector and audio amplifier attach to pin 1 for the receiver. One audio amplifier can be switched between the modulator and the receiver section. FM or pulse modulation techniques can also be used to reduce the modulator power requirements.
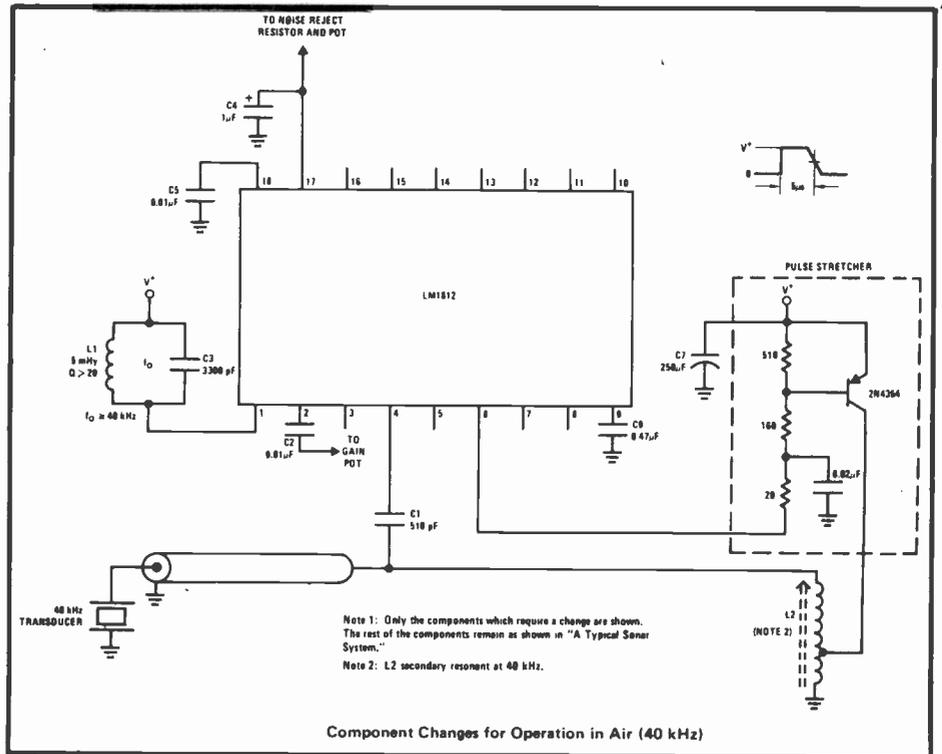
### DIGITAL DISPLAY

A digital depth (or range) readout can be used with the OLM1812. This eliminates the requirement for the constant speed dc motor. The modulator, pin 8, is electronically pulled ON for approximately a 1 ms transmit time at a repetition rate which controls the updating of the displayed information. The "neon driver," pin 14, will provide a negative output pulse (from V+ to approximately +1Vdc) if a load resistor (5.1 kΩ) is used from pin 14 to V+. This pulse is used to latch the output of a counter. This output is decoded and then drives a 7-segment LED display. The repetition rate of the clock input to the counter provides a direct conversion from elapsed time (total count) to depth (or range).

The LM1812 is available from **A. Marshall (London) Ltd., 42 Cricklewood Broadway, London NW2 3ET**. Price is £6.50 inclusive, delivery time about 3 weeks. Further details of Ultrasonic transducers available from **Vernitron Limited, Thornhill, Southampton SO9 5QF**.




## TDA 1022 BUCKET BRIGADE-DELAY LINE

MULLARD

The TDA 1022 is a charge-coupled delay line with 512 stages. The principle of operation is transfer of charge from stage to stage under the control of a two phase clock pulse. The descriptive title of 'Bucket Brigade' sums this up neatly. Just think of it as a line of buckets in fire fighting — the water gets passed along the line by pouring it into the next line, eventually it reaches the end. In the TDA 1022 the input signal is sampled at the rate of the clock pulse and passed along the line at this rate also.
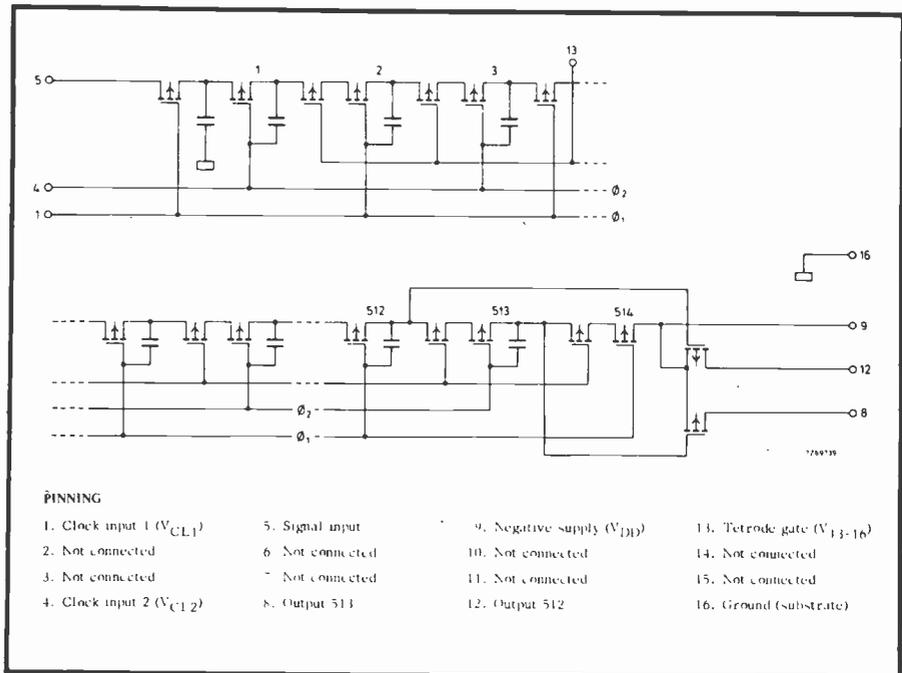
### AUDIO

For audio use the sampling (clock) frequency should be at least twice the highest frequency you want to process. This means that for good quality audio with a high of 20 KHz the clock rate is 40 KHz, however, 100 KHz gives far better quality. The delay produced at this rate is 5.12mS. This may not seem very much but devices can be cascaded to produce longer delays. Also if a reduced bandwidth is acceptable longer delays can be produced, for example with a clock rate of 5 KHz (usable bandwidth of 2 KHz) the delay is a healthy 51.2 mS. This can be useful for speech processing.



#### PINNING

- |                                |                  |                                 |                                   |
|--------------------------------|------------------|---------------------------------|-----------------------------------|
| 1. Clock input 1 ( $V_{CL1}$ ) | 5. Signal input  | 9. Negative supply ( $V_{DD}$ ) | 13. Tetraode gate ( $V_{13-16}$ ) |
| 2. Not connected               | 6. Not connected | 10. Not connected               | 14. Not connected                 |
| 3. Not connected               | 7. Not connected | 11. Not connected               | 15. Not connected                 |
| 4. Clock input 2 ( $V_{CL2}$ ) | 8. Output 511    | 12. Output 512                  | 16. Ground (Substrate)            |

#### QUICK REFERENCE DATA

Supply voltage (pin 9)	$V_{DD}$	nom.	-15 V
Clock frequency	$f_{\phi}$		5 to 500 kHz
Number of buckets			512
Signal delay range	$t_d$		51.2 to 0, 512 ms
Signal frequency range	$f_s$		0 (d.c.) to 45 kHz
Input voltage at pin 5 (peak-to-peak value)	$V_{5-16(p-p)}$	typ.	7 V
Line attenuation		typ.	4 dB

**OTHER APPLICATIONS**





Other applications for this neat device include variable compression and expansion of speech in tape recorders, speech scrambling in communication systems, vibrato and chorus effects in organs, reverberation units and to equalise delay in public address systems.

**PROTECTION AND USE**

A couple of things to watch when using the device are that it uses a positive earth arrangement — unusual in modern circuits, and is MOS — handle with care. In respect of this it is advisable to use a 741 buffer before the device as well as the 741 output buffer, this makes sure signals can't blow it up if the power is off.

The clock pulses are out of phase and a suggested circuit is shown. In the main circuit the 741 output buffer, also acts as a lowpass filter, to get rid of residual high frequency noise from the clock.

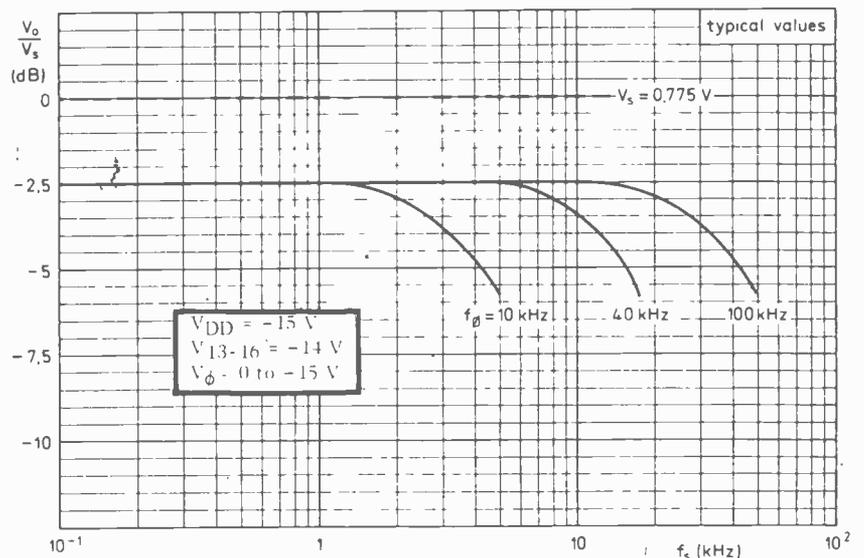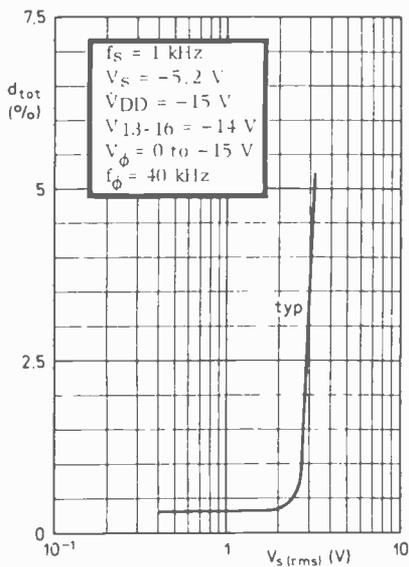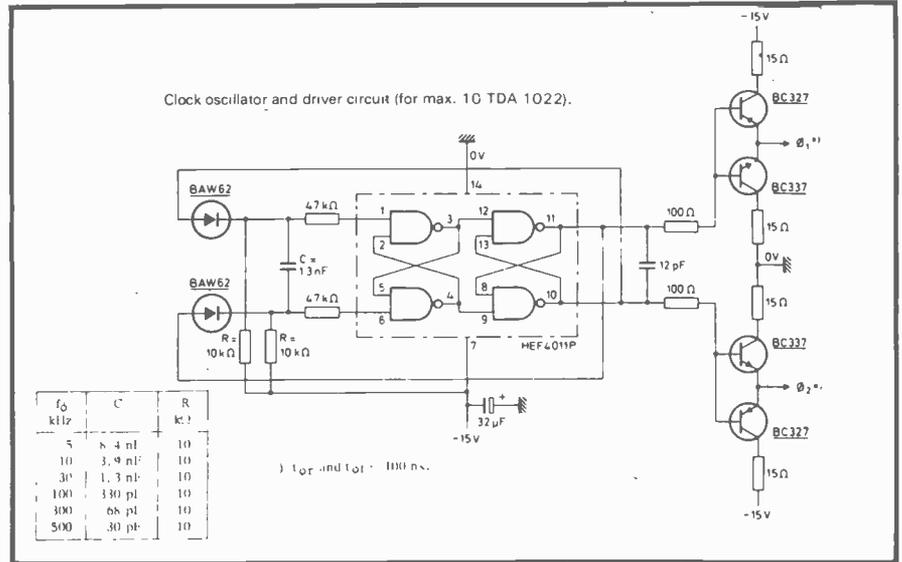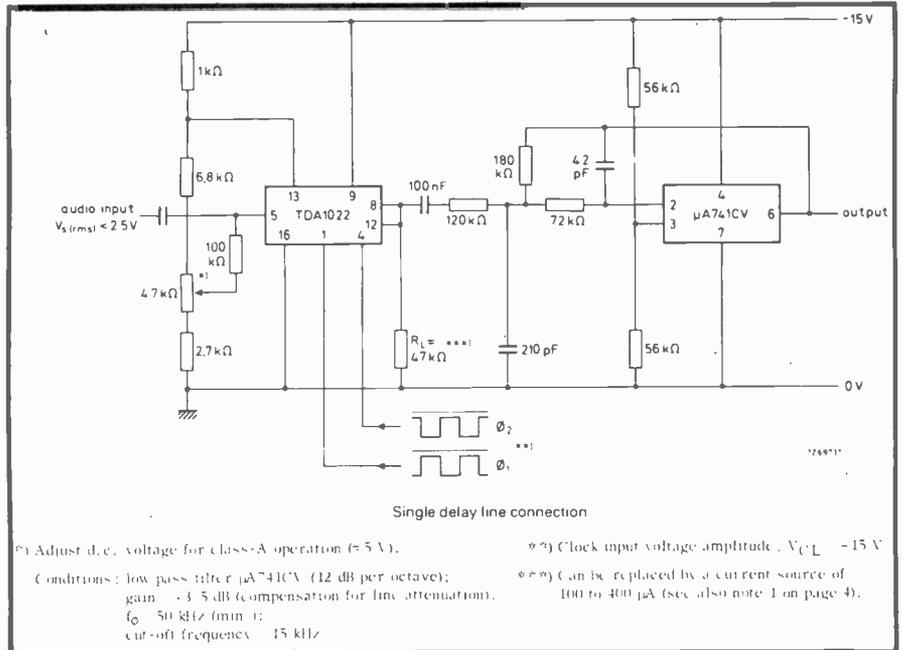The TDA 1022 is available from **A. Marshall (London) Ltd, 42 Cricklewood Broadway, London NW3 3ET.** Price £7.50 inclusive, delivery time about 2 weeks.



**ETI READER OFFER**

# **CBM 5R39 SCIENTIFIC CALCULATOR**

**RRP  
£24.60**

**£15.95  
inc**



**FEATURES:** sin, cos, tan and inverse, change sign, exchange register,  $x^2$ ,  $y^x$ ,  $\log_e$ ,  $\log_{10}$ ,  $\sqrt{x}$ ,  $\sqrt{y}$ , rectangular and polar coordinates,  $e^x$ ,  $10^x$ , standard deviation and mean value, two memories, summation to memory,  $1/x$ , parenthesis, full arithmetic functions. Algebraic logic is employed.

Now you may have seen calculators cheaper, and you WILL have seen machines with more facilities, but you have NEVER seen a rechargeable scientific (with charger) AND such facilities anywhere NEAR this price!

Our price includes p+p, VAT, and the mains unit. No batteries to buy, now or ever, which makes the machine effectively cheaper still! The calculator has all the facilities of the better known CBM SR-1800, but is considerably cheaper.

To obtain your 5R39 fill in the coupon below, add a cheque or P.O. for £15.95 and send the whole lot to us at the address shown. Then throw away the abacus.

# electronics today

international

What to look for in the June issue: On sale May 6th


## Master-Mind

THE GAME 'MASTERMIND' — not that on TV but the 'peg' game — has caught on like wildfire. If you don't know it, one player sets up a code for the other to break: it's a game which really tests your ability to think logically. Next month we

describe an electronic version. Press a button and the circuit sets the problem — it will also reveal to you the necessary clues. It uses ump-teen IC's but construction has been enormously simplified by the use of pcb's.
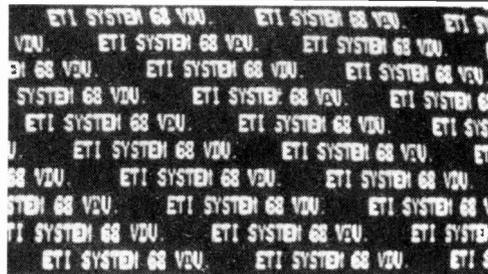
## System 68 VDU

THE FIRST PART of our System 68 VDU project, covering the Video and Character generation board. Part 2 will cover the Interface and RAM board.



FEATURES include 64 character by 16 line display, parallel I/O with less than 1/4 second for full screen from memory, White on Black or Grey or any combination plus character flash. e.g. Black letters on grey flashing background. All built into a 2in module on two Eurocards!

## Valve Sound

AUDIO TECHNOLOGY marches on — distortion figures grow ever more negligible with the passing days. Transistor and IC amplifiers are rapidly approaching the frontiers of design possibility (on paper). Every now and then problems appear to become significant as their (smaller) contribution to final sound quality becomes the largest remaining.

Yet in the wake of this sweep to

perfection, professional musician's are hanging on with tooth and nail to their aged and totally outdated VALVE amplifiers. Why? Simple; they say it sounds better.

Why? Has modern technology missed something? What is the vital factor that valve designs possess and solid-state designs don't? Next month we'll tell you — and the answer is **very** controversial!

## DFM

AN ETI short circuit. A 3-Digit LED display is used to give coverage from 1Hz to 9.99MHz in five ranges. Input sensitivity is 100mV. A short circuit? Yes; although complex in its theory we've reduced the problem to a minimum by using carefully designed pcb's.

## Bass Enhancer

IF YOU'RE just starting in Hi-Fi, or would like to improve the sound of your present bookshelf enclosures — this project is for you. This is *not* simply a bass boost circuit: it is an active filter design which compensates for the falling response of most small speakers below 100Hz. Part of the design eliminates rumble and warp signals below 15Hz so that fidelity is preserved.

P.S. Also a must if you hate your neighbours!!

## LCD

LIQUID CRYSTAL DISPLAYS were practically unknown a few years ago

ETI - MARSHALL'S - NATIONAL

# tip of the month!



For some time now a printed circuit resist pen, A in the photograph, has been on sale. The price varies a bit, but 65 - 75p is typical.

They're good. We've used them; it dries fast, is certainly acid resistant, and is easy to clean off afterwards.

A paper label is wrapped around the barrel and being of a curious disposition, we decided to remove it – shown as B. Rather odd, we thought, that someone should go to all the trouble to sand off part of the barrel. Apart from this area, the rest of the barrel carries Japanese wording which happens to be identical to the Pentel Pen (C) sold in stationers, not for 65 - 75p but for 30 - 35p – and they're available in many colours. Wishing to take nothing for granted, we tried the Pentels as resists. They're good too!

So far we have been unable to discover the advantages of the paint-free area on the barrel – and 35 - 40p extra does seem rather a lot, doesn't it? We couldn't resist telling ETI readers about this!

## DON'T BLAME YOUR NEWSAGENT



British newsagents are among the best in the world. No, we're not trying to butter them up but we are an international magazine and are in a position to make comparisons. But they've got a tough job – they don't know how many of you want ETI, so they've got to guess, and since they're bound to order conservatively, this leads to shortage. The February, March and April editions of ETI were total sell-outs within a few days in most areas. We don't like it, you don't like it, and your newsagent doesn't like it.

Please help us all, place a regular order; your newsagent will normally be delighted to help.

# SINTEL for KITS - CMOS - BOOKS

Components from  
Leading Manufacturers only

## A NEW RANGE OF SINTEL INDUSTRIAL MODULE KITS



Using only the highest quality components — Fibreglass roller-tinned PCBs — ICs and Displays direct from "Blue chip" Manufacturers.

### KITS FOR TTL LATCHED COUNTER MODULES

Each kit includes a set of displays (0.5" Red LED type TIL321/FND507) and two PCBs, one each per digit of 7447, 7475 and 7490, plus brackets, resistors, capacitors, a single in-line plug and socket, nuts, screws, washers, instructions, etc. Sockets are NOT included and we recommend that you order Soldercon Pins separately (112 for a 2 digit module, 224 for a 4 digit module and 336 for a 6 digit module).

Each module consists of one vertical PCB holding the displays, fixed by two brackets to a horizontal PCB, which holds the remaining components.

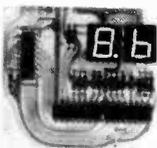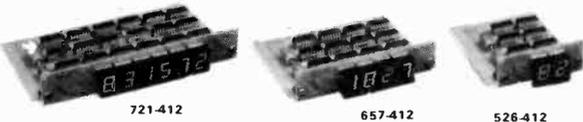Full Kit for 2 digit TTL Counter with Latch Order as **526-412** £12.50  
Full Kit for 4 digit TTL Counter with Latch Order as **657-412** £22.50  
Full Kit for 6 digit TTL Counter with Latch Order as **721-412** £32.50



**KIT FOR SINGLE PCB CMOS COUNTER MODULE WITH LATCH**  
A complete kit for building a 2 digit, single PCB, CMOS Counter Module with Latch. Includes PCB, 2 x TIL322 or FND500, 2 x 4511, 1 x 4518, Rs, socket pins, etc. Size h.67mm w.71mm d.18mm.  
Order as **142-269** £8.60

### SETS OF JUMBO DISPLAYS WITH DISPLAY HOLDING PCB

Each kit consists of the appropriate number of 0.5" red LED displays (either common anode TIL321/FND507s or common cathode TIL322/FND500s) and a display holding PCB. OPTIONS: PCBs wired for multiplexing or non-multiplexing, clock format or counter format.

TYPE	COMMON ANODE		COMMON CATHODE		
	Part No	Price	Part No.	Price	
Non-Multiplexed	2 digit Counter	574-822	£3.37	446-822	£2.97
	4 digit Counter	777-822	£6.63	128-822	£5.83
	6 digit Counter	684-822	£9.89	271-822	£8.69
Multiplexed	4 digit Clock	801-822	£6.66	262-822	£5.86
	6 digit Clock	417-822	£10.15	452-822	£8.95
	8 digit Counter	119-822	£13.09	515-822	£11.49

## DISPLAYS

These Jumbo LED displays take no more current than 0.3" types. All our common cathode (C.C.) digits can be used in place of any other C.C. display (DL704, D1750, MAN3640, etc.) since they are all electrically identical (but may have different pin-outs). Similarly our common anode digits may be used in place of any other C.A. types (DL707, DL747, RS/Doram 586/699, etc.)



**FND500 C.C. £1.30**  
Red 0.5" by Fairchild



**TIL321 C.C. £1.50**  
**TIL322 C.C. £1.49**  
Red 0.5" by TI

### 5LT01 £5.80

A very attractive four digit display with large 0.5" green digits, AM/PM and colon. Phosphor diode (vacuum fluorescent)



## DATABOOKS

RCA CMOS and Linear IC Combined Databook	£6.70
National Semiconductor 7400 series TTL Databook, c. 200 pages	£3.45
TTL Pin-Out Card Index	£2.95
Intel Memory Design Handbook, c. 280 pages	£5.20
Intel 8080 Microcomputer Systems Users Manual, c. 220 pages	£5.25
Motorola MicroMOS Databook (Vol 5 Series B), c. 500 pages	£3.50
Motorola M6800 Micro Applications Manual, c. 650 pages	£12.95
Motorola M6800 Programming Manual, c. 200 pages	£5.35
Motorola Booklet introducing Microprocessors	£1.80
National SC/MP Introkit: Users Manual	£0.75
Zilog Z80-CPU Technical Manual	£5.60
Zilog Z80-CTC Product Specification	£0.80
Zilog Z80-P10 Technical Manual	£3.30
<b>DATASHEETS on Microprocessors, etc. (usually Xerox Copies)</b>	
Intersil IM6100 12 bit	£0.75
National SC/IMP 8 bit	£0.75
Signetics 2650 8 bit. Low cost	£0.75
TMS 8080	£0.75
9131 Memory	£0.75
RCA CMP 1802 8 bit CMOS	£0.75
Zilog Z80 (enhanced 8080)	£0.75
Motorola MC 6800	£0.75
TMS 5501 for 8080	£0.75

Our offices are at Link Property, 209 Cowley Road, Oxford, but please do not use this as a postal address.

**FAST SERVICE.** We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.

**ORDERS:** C.W.O. add VAT @ 8% + 25p p&p TELEPHONE and CREDIT (invoice) Orders add VAT @ 8% + 50p p&p and please see FAST SERVICE EXPORT Orders welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For Export postage rates on heavy items — contact us first.

A FREE CATALOGUE requested by post or phone, will be sent by return giving full details of our range of CASES ● KITS ● DISPLAYS ● MPU ● MPU KITS ● and other components not listed here, with same day despatch for goods in stock. All prices valid until 31st August, 1977

## COMPONENTS

### CMOS

Mainly RCA	CD4026	1.75	CD4052	0.94	CD4083	0.92	
CD4001	0.17	CD4027	0.58	CD4053	0.94	CD4084	1.34
CD4000	0.17	CD4028	0.92	CD4054	1.20	CD4095	1.08
CD4002	0.18	CD4029	1.18	CD4055	1.36	CD4096	1.08
CD4006	1.20	CD4030	0.58	CD4056	1.36	CD4097	3.85
CD4007	0.18	CD4031	2.30	CD4059	4.93	CD4098	1.13
CD4008	1.00	CD4032	1.02	CD4060	1.15	CD4099	1.90
CD4009	0.58	CD4033	1.44	CD4063	1.13	CD4502	1.24
CD4010	0.58	CD4034	1.97	CD4066	0.63	CD4510	1.41
CD4011	0.20	CD4035	1.22	CD4067	3.85	CD4511	1.72
CD4012	0.23	CD4036	3.29	CD4068	0.23	CD4514	2.84
CD4013	0.58	CD4037	0.98	CD4069	0.23	CD4515	3.24
CD4014	1.04	CD4038	1.10	CD4070	0.51	CD4516	1.40
CD4015	1.04	CD4039	3.20	CD4071	0.23	CD4518	1.25
CD4016	0.58	CD4040	1.11	CD4072	0.23	CD4520	1.19
CD4017	1.04	CD4041	0.86	CD4073	0.23	CD4527	1.64
CD4018	1.03	CD4042	0.86	CD4075	0.23	CD4532	1.39
CD4019	0.58	CD4043	1.01	CD4076	1.34	CD4555	0.90
CD4020	1.28	CD4044	0.96	CD4077	0.45	CD4556	0.90
CD4021	1.04	CD4045	1.45	CD4078	0.23	MC14528	1.22
CD4022	0.94	CD4046	1.37	CD4081	0.23	MC14553	4.68
CD4023	0.23	CD4048	0.58	CD4082	0.23	IM6508	8.05
CD4024	0.80	CD4049	0.58	CD4085	0.74		
CD4025	0.23	CD4050	0.58	CD4086	0.74		
		CD4051	0.94	CD4089	1.60		

### VEROCASES

751410J	3.36	3 7/8" x 5" (2 per pack)			
751411D	4.10				
751237J	2.50	103/P16xPK	1.12	1000	4.00
751238D	3.00	4 7/8" x 17 9/16"		3000	10.50
751239K	3.58	126/P16	2.55		

### VEROBOARDS


### SOLDERCON IC PINS


### SUNDRIES

CA3130	0.94
µA741	0.40
78L12WC	0.77

### CLOCK CHIPS

AY51202	3.10
AY51224	3.50
MK50253	5.60

### TRANSFORMERS

LEDTRF	1.95
5LTRF	1.95

### CRYSTALS

32 768kHz	3.50
5.12MHz	3.60

### FLAT CABLE

20w 1m	1.00
10m for	8.00

### MEMORIES

9131 (new)	19.50
2102A-6	3.10
2112A-4	4.10
6508	8.05

### MPU KITS

6800	24.84
SC/MP CPU	
ISPBA/5000	14.50
Z80	48.50
ISP8K/200E	68.61

## HIGH QUALITY KITS



**ACK**  
£27.80

### ATTRACTIVE SIX DIGIT ALARM CLOCK KIT

A complete kit including slim white case h.40mm w.205mm d.140mm with deep red panel. Features bleep alarm, snooze, automatic intensity control and high brightness display driving twelve or twenty-four hour format (easy to add a switch to switch between them). Touch switch snooze.

This alarm clock is also available with CRYSTAL CONTROL and BATTERY BACKUP. If mains power is disconnected (deliberately or accidentally) the clock will keep perfect time. Accuracy to within a few seconds a month. While on backup, the displays are off to conserve battery but the alarm remains fully operational.  
Order as **ACK + BBK + XTK** £34.33

## DIGITAL CAR CLOCKS



**CCK**

**AUT-CK**

**CRYSTAL CONTROLLED 6 DIGIT CAR CLOCK WITH INDEPENDENT JOURNEY-TIMER**  
Shows time or elapsed time in hrs. mins. secs ● Runs off car 12v supply ● Nine push buttons for Start/Stop/Reset, selecting display to show time or elapsed time ● All controls functional irrespective of display mode ● Kit complete with case h.40mm w.205mm d.140mm  
Order as **CCK** £42.00

### THE SINTEL CAR CLOCK KIT

Four 0.5" red digits ● Neat white case ● Crystal control ● Battery backup ● Suitable for all 12v negative earth cars ● Size h.40mm w.154mm d.85mm. Complete less battery  
Order as **AUT-CK** £17.85

### GCK CLOCK KIT

Four bright green 0.5" digit mantelpiece or office clock ● Crystal control ● Battery backup ● White case ● Size h.40mm w.154mm d.85mm. Complete less mains cable, plug and battery  
Order as **GCK + BBK + XTK** £19.65  
Also available less crystal control and battery backup.  
Order as **GCK** £14.40




### 50Hz CRYSTAL TIMEBASE KIT

Use to improve accuracy of your digital clock ● As a 50Hz source in a clock with battery backup ● Accurate to within a few seconds a month ● Size h.14mm w.64mm d.49mm  
Order as **XTK** £6.28

SEND YOUR ORDER TO  
**SINTEL**  
PO BOX 75A OXFORD  
Tel: 0865 49791



**SINTEL**

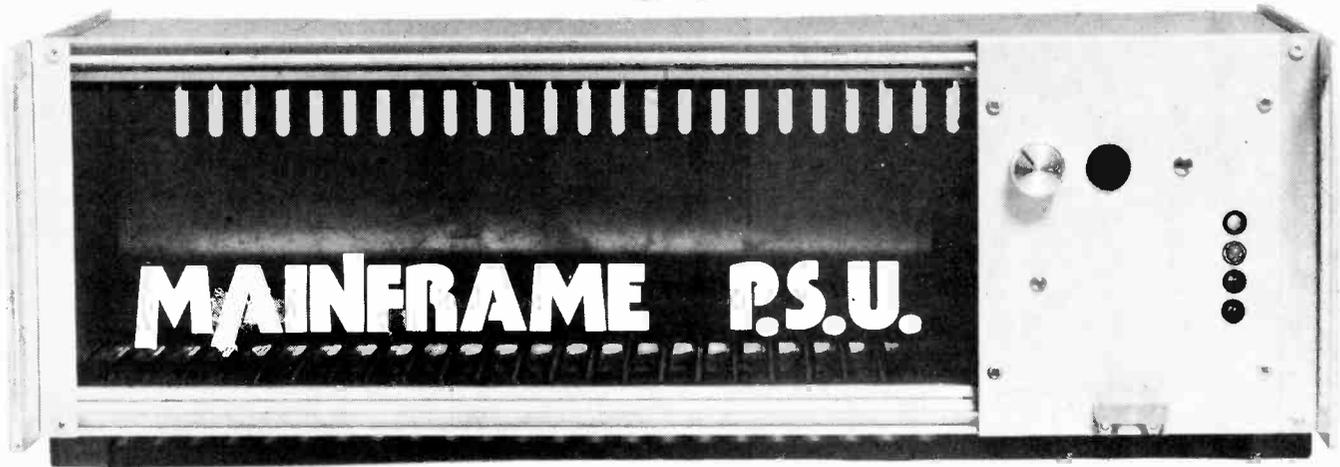

## Modular supply for the System 68 Computer system. Described by Jim Perry

THE ETI MAINFRAME PSU has four output voltages, +5 for the CPU and TTL, CMOS circuits; this is capable of supplying about 2½ amps. The other voltages are -7, -12 and -20 volts for various bias requirements in RAM's etc. All the negative voltage rails can supply up to 100 mA less the monitor LED current, which is about 10mA. The main considerations in the design were size and reliability. The final version is indeed very small, fitting into a 4in. module! All outputs are overload proof, if a supply rail is short circuited the front panel LED will extinguish.

Connections are provided via a

*Fig 1 and 2. Two views of the assembled module, note the use of insulated sleeving and 'p' clips in figure 1. The transformer mounting can be seen in both figures, figure 2 also shows the ribbon cable to the front panel LED's.*

standard 31 way plug and socket, which will be used for the rest of the system. The advantage of this is cost, the disadvantage is that with 31 ways all 'bus' wiring will be 'hardwired', meaning that for example the VDU module has to be plugged into a particular position in the rack.

### Construction

Construction is reasonably straightforward if the sequence outlined is followed. The PCB can be assembled at virtually any time, we did it first, make sure all components are as low in profile as possible. If you leave 1in. leads on the capacitors, the module won't fit!

Front panel drilling is not shown, but positioning can be seen from the heading photograph.


The drilling of metal work and

fabrication of brackets should be done next. The dimensions are all quite precise, so if a dimension is 13mm — we mean it! The case can also be assembled at this point, don't forget the end plates — which take ½in. off the front panel.
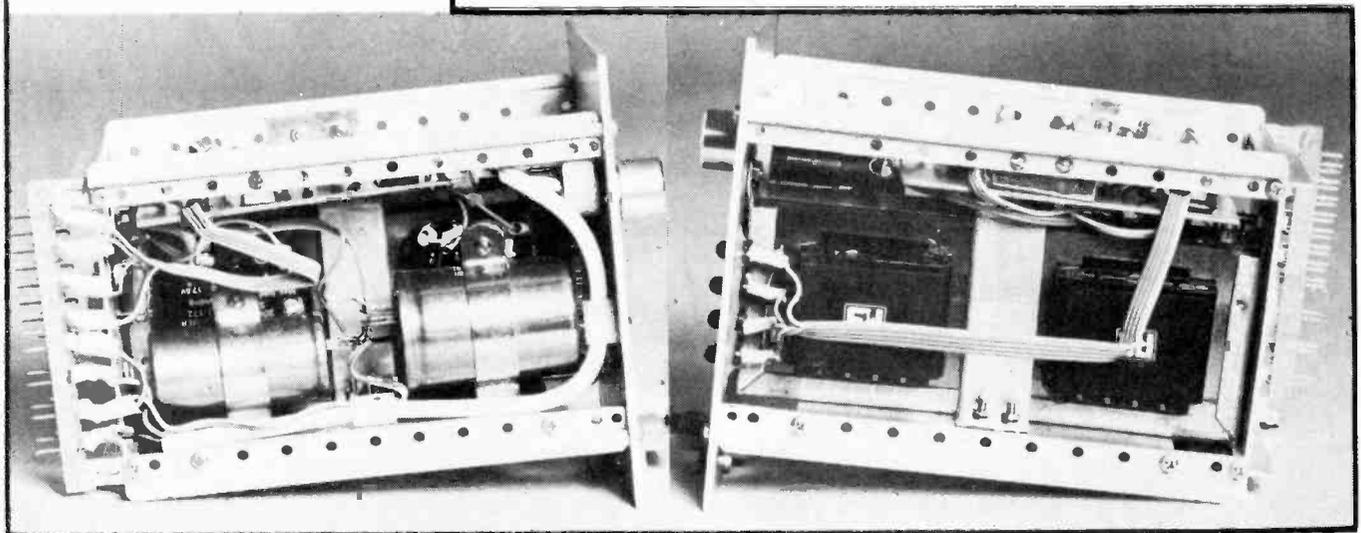
### Mains Input

Mains input should be fitted to the frame, this uses bracket A and plastic guard B. Also a 'U' shaped notch should be made in the case back panel. Figures 3, 4, 5 show the mains input in closeup, note that the spare pins in between low voltage and mains, and LNE are snipped off the 31-way socket and plug.

The base plate, back plate and front panel of the 4in. module, when drilled, can have various compon-



# MAINFRAME P.S.U.


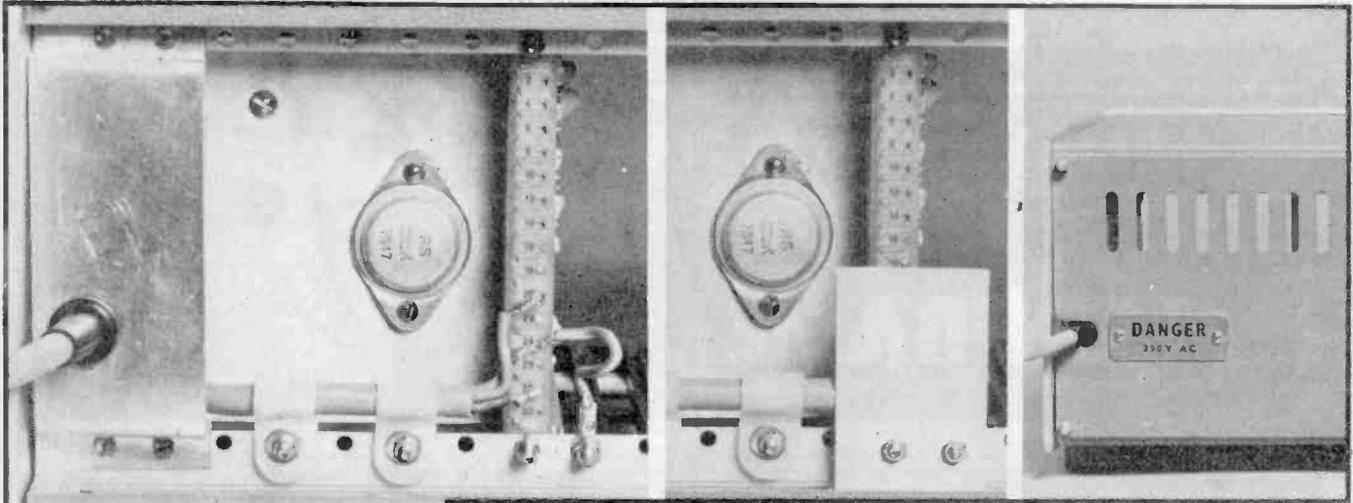


Fig. 3, 4, 5, the mains input on the back panel, note the positioning of 'p' clips and plastic guard. The sign came from a piece of surplus P.O. equipment.

ents attached — before being bolted together. The back plate is fitted with Reg 1, complete with mica insulating kit, and C3, C7 are soldered in place on the regulator.

Fig. 6, general view of opened out module, again note extensive use of insulating sleeves and transformer mounting.

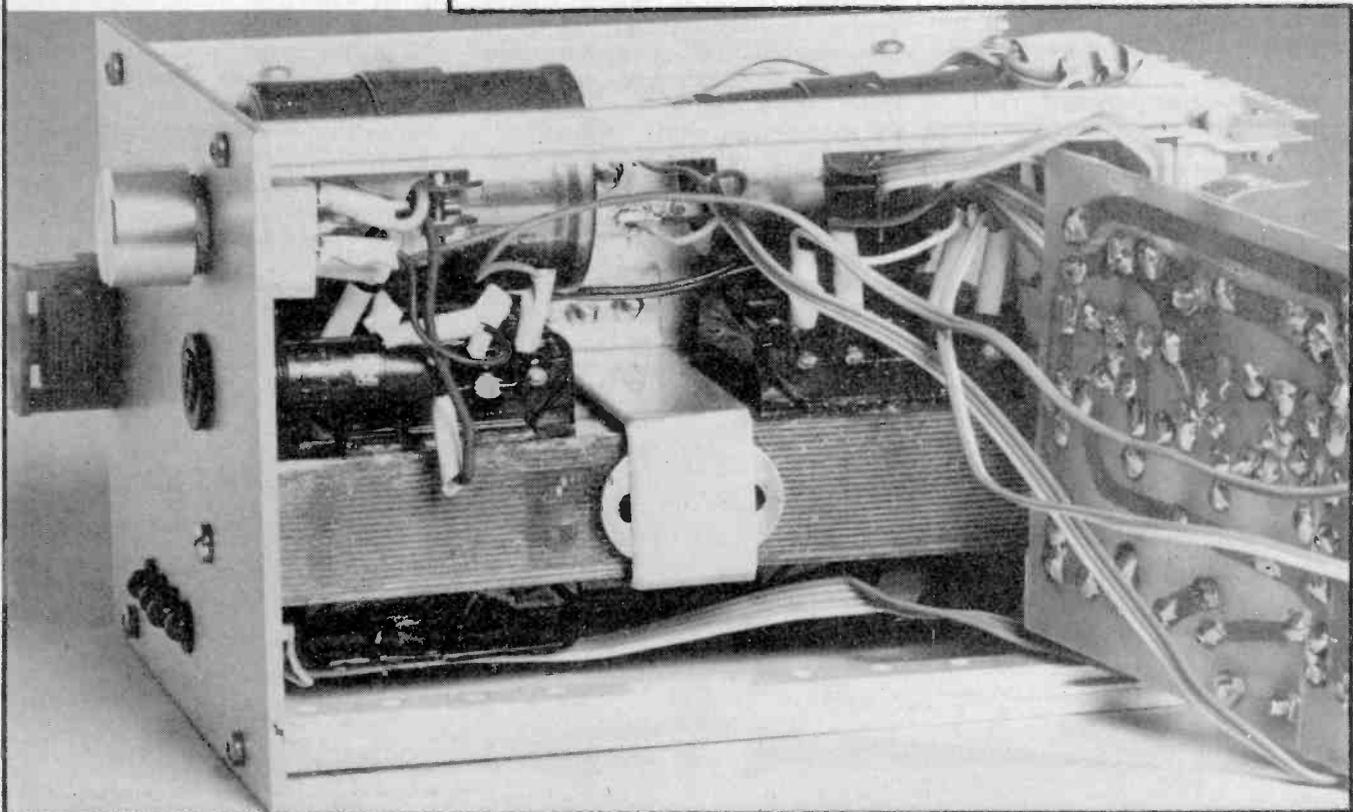

FS1, SW1 and LED 1-4 can be mounted on the front panel of the module. Ribbon cable and sleeving should be soldered to the LEDs (see figure on page 59). The two mains transformers can be strapped to the base plate, but first their mounting lugs must be bent. One lug is bent down through 90° and the other through 170°, see photographs to see how they mount. The two lugs bent through 170° are strapped under the mounting bracket. Both transformers should be wired up before C1 and C2 are mounted.

## Module Assembly

The module can now be assembled by bolting and screwing the base plate, front and back together. Fit the snipped 31-way plug at the same time as the back plate. The mains wiring from connector to FS1 and SW1 can now be soldered, use insulating sleeving on all exposed connections. The mains lead from T1, T2 can also be wired into SW1. The remainder of the wiring can now be installed, including the PCB — which is mounted with two brackets as shown.


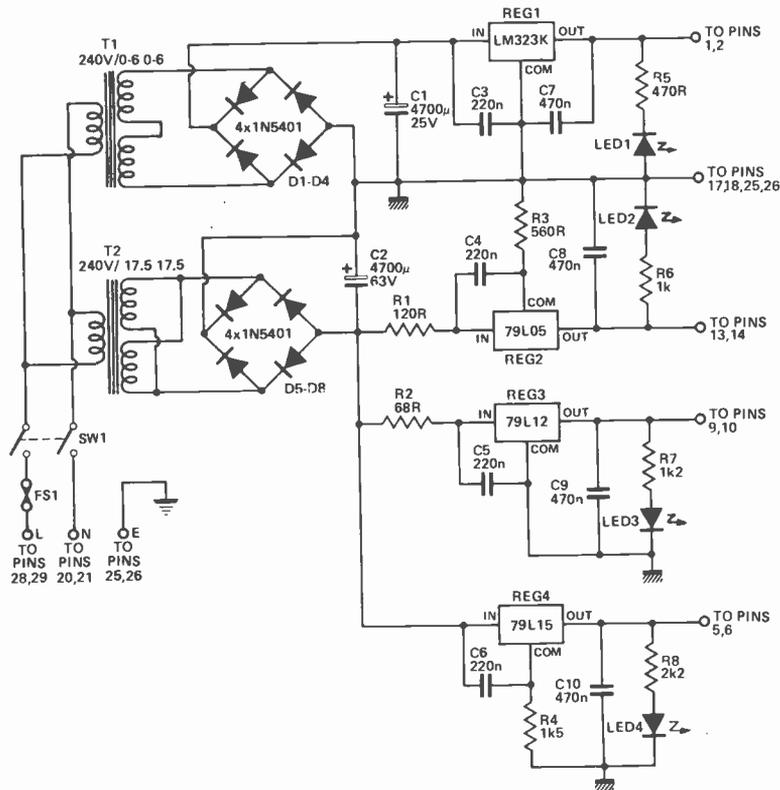


Fig. 7. Circuit diagram of the P.S.U.

Fig. 8 Component overlay and off board connections.

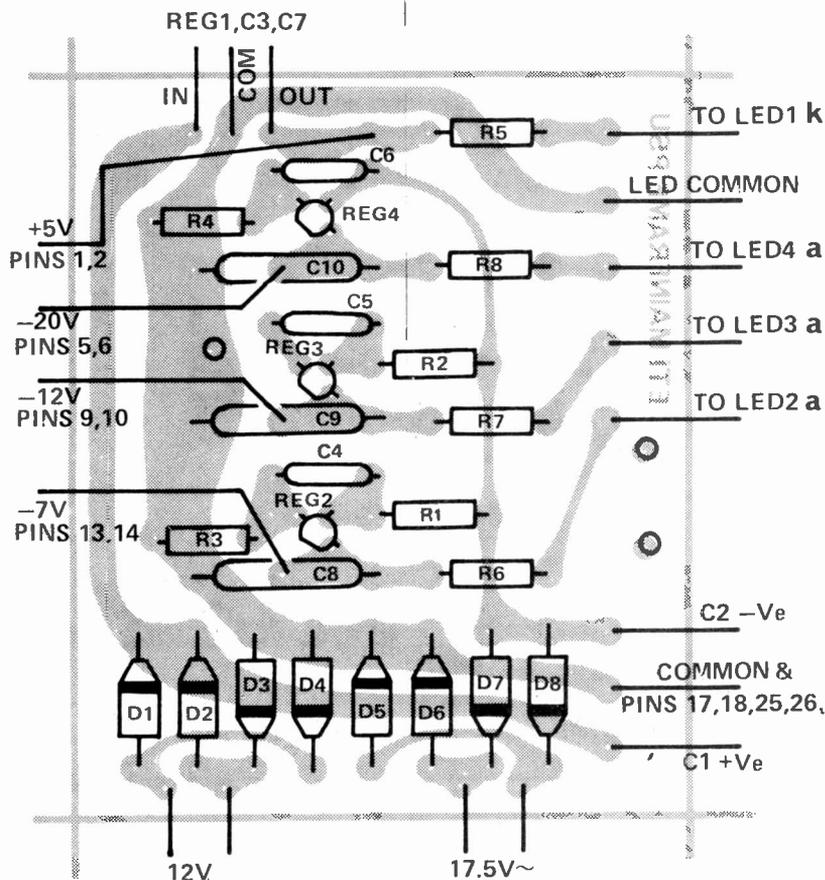

## How it works

The circuit is based around four monolithic regulator IC's. Two types are used, the +5 volt supply is provided by a TO3 cased 3A device, all the negative supplies are provided by TO92 100mA regulators. Separate transformers and bridge rectifiers are used for positive and negative supplies.

All the regulators work in the same manner, all are fixed voltage with overload and short circuit protection, in addition the TO92 regulators have thermal overload shutdown.

To produce a non-standard output voltage Reg 2 and Reg 4 have resistors in their common leads, Reg 2 is raised from -5 to -7 and Reg 4 from -15 to -20. In addition Reg 2 and Reg 3 have resistors in series with their inputs to reduce to voltage across them, and hence reduce power dissipation in them.

The 220n capacitors are to help stability by preventing RF oscillation. The 470n capacitors are to improve transient response.

## Parts List

### Resistors

R1	120	2.5WW/W
R2	68	2.5WW/W
R3	560	
R4	1K5	
R5	470	
R6	1K	
R7	1K2	
R8	2K2	

All 1/2W 5% except R1, 2

### Capacitors

C1	4700u 25V	(.102-774)
C2	4700u 63V	(.103-064)
C3, 4, 5, 6	220n min polyester	
C7, 8, 9, 10	470n	

### Semiconductors

D1-8	1N5401 (3A 100V)
REG1	LM323K
REG2	79L05
REG3	79L12
REG4	79L15
LED1	Green (586-481)
LED2, 3, 4	Red (586-475)

### Card Frame/Module

71-3841L	Card frame/case including guides
71-3842F	1 pair end plate angles
71-3844G	4 inch module
17-0267H	Connector plug 31 way
17-0268C	Connector socket 31 way

### Miscellaneous





T1 0-6, 0-6 @ 1.6A (207-138)  
 T2 0-17.5, 0-17.5 @ 0.5A (207-172)  
 SW1 DPST 250v4A (316-800)  
 FS1 20mm fuseholder (412-879)  
 Mounting clips for C1 + C2 (543-052, 543-383) 20mm 500mA fuse, 18mm knob, mounting kit for Reg 1, Heatshrink sleeving (1.6m + 3.2mm), 4 'p' clips (543-355), sleeved grommet, ribbon cable, 6BA + 4BA nuts + bolts, anti-shake washers. Aluminium for brackets, mains cable, etc.

All numbers in brackets eg. (207-138) are Doram type numbers.


Card frame/Module numbers are Vero Electronics reference codes.

# MAINFRAME

# P.S.U.

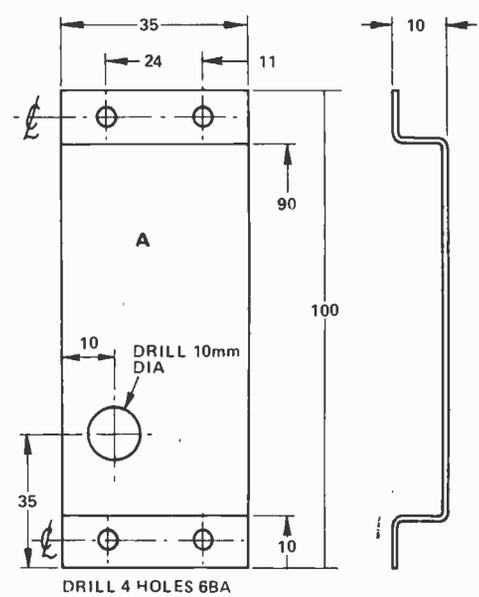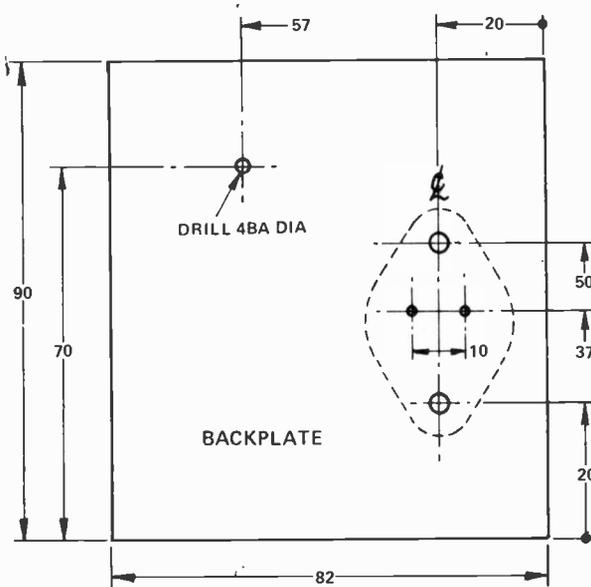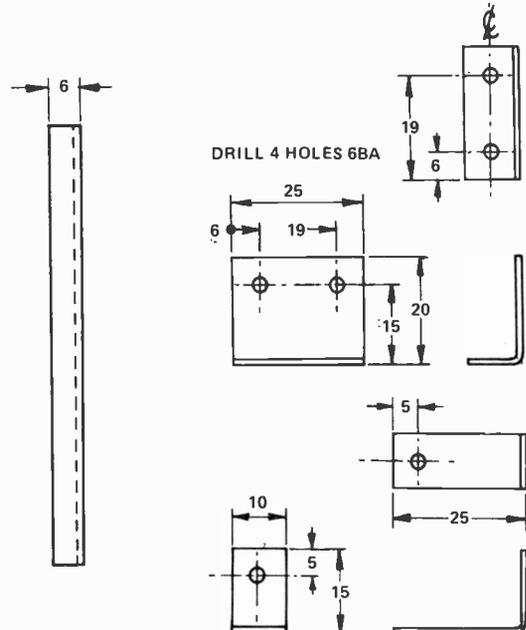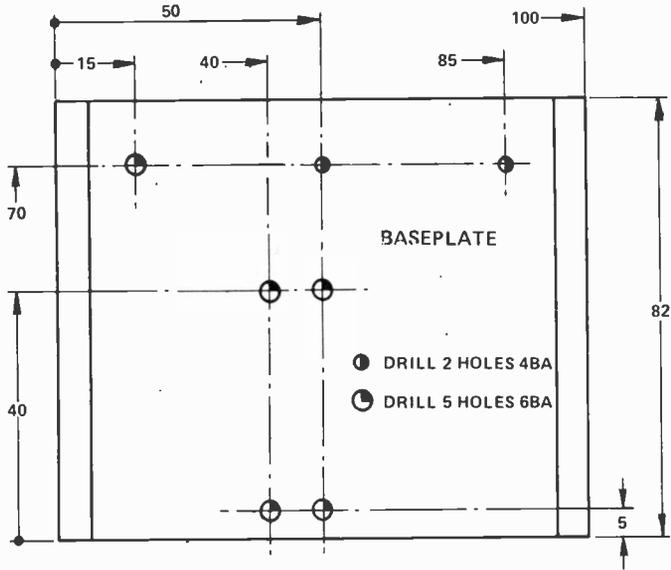

MODULE PARTS

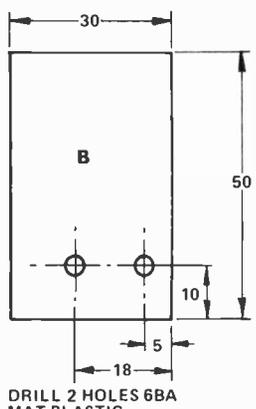

MATERIAL 18 SWG ALUM.  
UNLESS OTHERWISE SPECIFIED

ALL DIMENSIONS IN MILLIMETRES  
UNLESS OTHERWISE SPECIFIED

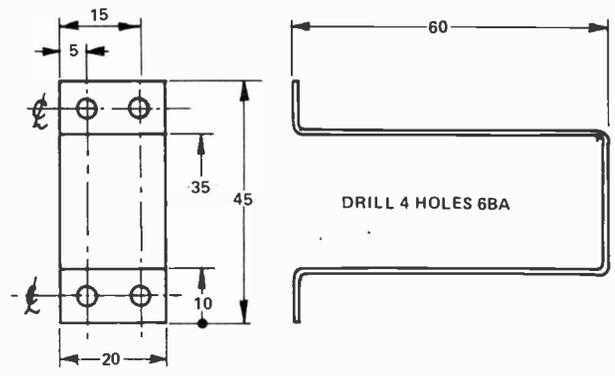


Fig. 9 Metal work details, front panel is not shown as exact positioning can be varied to allow for different components. See text.

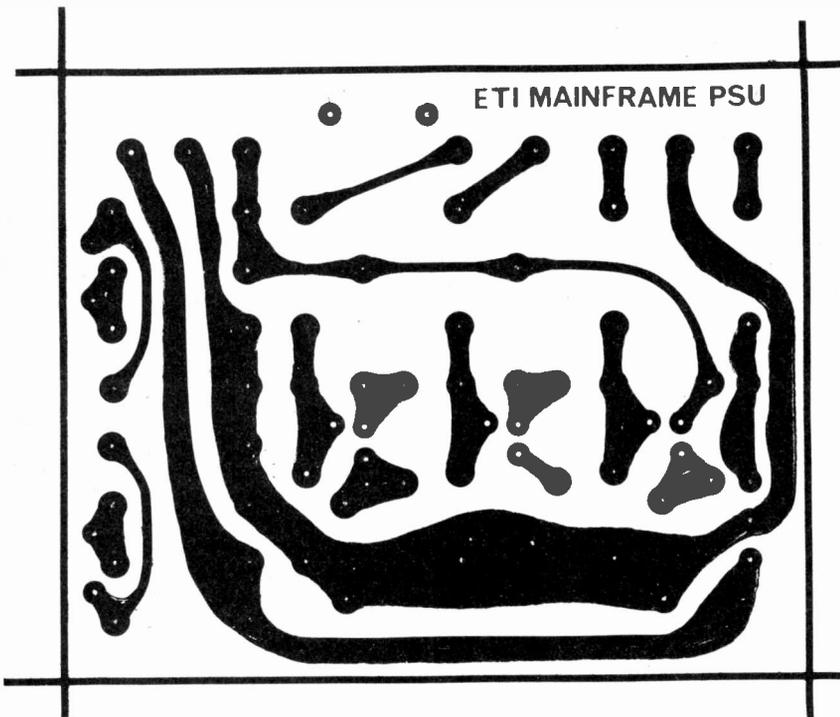


Fig. 10 PCB shown full size.

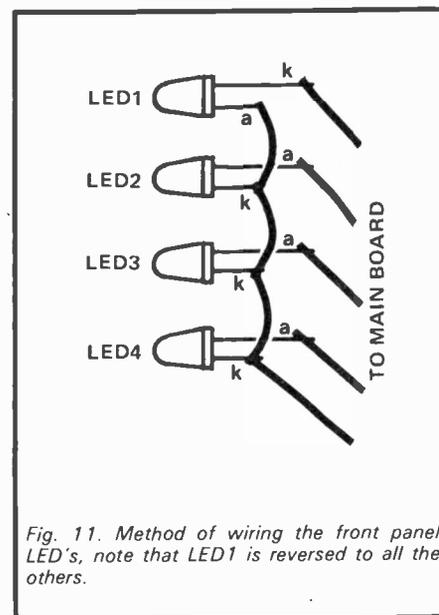


Fig. 11. Method of wiring the front panel LED's, note that LED1 is reversed to all the others.

### GLASS FIBRE P.C.B.s

ETI 480 50/100w Amp	£1.35	ETI 155D Digital Voltmeter	£1.15
ETI 480 Power Supply	£1.45	Set of above 4 Boards	£2.90
ETI 444 5w Stereo Amp	£1.50	ETI 549 Metal Detector	75p
ETI 155A Digital Voltmeter	45p	ETI 544 Heart Monitor	75p
ETI 155B Digital Voltmeter	55p	ETI 445 G.P. Pre-Amp	55p
ETI 155C Digital Voltmeter	£1.05	ETI 446 Audio Limiter	85p
		ETI 447 Audio Phaser	85p

#### SEMI-CONDUCTORS

BC107	9p	BC114	10p	BD520	50p	1N1191	35p
BC107B	10p	BC116	17p	BD609	70p	BCY32	20p
BC108	9p	BC478	25p	ZTX109	10p	BYX36-300	6p
BC109	9p	BD519	50p	UC734E	20p	1N4150	3p
						2N5457 FET	35p

#### INTEGRATED CIRCUITS

7472	22p	7473	25p	7474	25p	NE555V	40p
7447	80p	7493	45p	CA3046	50p	UA741	25p
LM339	£1.50	TCA220	£1.85	CA3052 stereo Pre-Amp	£1.50		

(The CA3052 consists of 4 independent unconnected amplifiers. Provision is made for introducing discrete equalisation and tone control circuits. It needs only a single supply rail of not more than 16V. Full data supplied.)

Davian D4A Voltage Regulator 1.45V at up to 4A TTL shut down **£8.00**

This regulator is complete with its own electrically isolated decaheat sink and normally sells at more than £13.00. Provision is made for current limiting and voltage setting and it can be shut down by TTL logic. Full connection data and a suggested circuit is supplied free with this device.

#### OPTO-ELECTRONICS

Jumbo LED Red 0.2" dia	16p	Green 0.2" Dia	25p
Minitron 3015F 7-segment Display	£2.00	LED Array (10 LEDs in 20 pin DIL pack)	£4.00
Opto Isolator, 6-pin DIL 100KHz			

#### RESISTORS 5% C.F. HIGH STAB

1/4	1p ea	100 Same Value	80p	1/2W	1.5p ea	100 Same Value	£1.00
-----	-------	----------------	-----	------	---------	----------------	-------

#### ELECTROLYTIC CAPACITORS CAPACITY/VOLTAGE

10/12 5p, 47/40 9p, 100/10 6p, 100/16 7p, 100/250 25p, 150/25 8p, 330/25 10p, 470/63 30p, 500/10 10p, 640/16 14p, 1000/63 80p, 4700/50 60p. Very special 33 000/40 £1.80.

#### SWITCHES

Miniature Glass Reed Switches, 10 for 50p, 100 for £4.50.  
Toggle DPST by Arrow (Black dolly) 17p. Slide Switches SPST 8p.  
Both the above Switches suitable 250V at 3 Amps.

#### ITEMS OF INTEREST TO MPU AND COMPUTER ENTHUSIASTS

Printed circuit board for up to 14 digit display — comprises a 40-bit serial in parallel out shift register expandable to 56-bit, together with the necessary decoder drivers for 9-7 segment displays expandable to 14.

Price, P.C.B. with Logic **£14.00**  
If 9 Minitrons ordered same time total price **£20.00**


Momentary Action Illuminated Square Bezel Push Switches with choice of the following legends: END OF RECORD RESET, ENTER, ERASE, RESERVE, DISCHARGE, ISSUE, RENEW. Ex. new equipment **50p**

Matching Indicator Lamps Green Bezel Legend READY, Red Bezel Legend ERROR Amber Bezel Legend TRAP (You can easily fit your own Legend to these Lamps and switches). Price Lamp only **50p**

Complete Terminal Units comprising display as described above, 12 position touch keyboard 0.9 with two spare positions, 3-Indicator Lamps, 8-push Switches Stabilised Power Pack (requires low voltage A/C input) and all the TTL for outputting to recorder or MPU/CPU PLEASE NOTE THAT WE ARE UNABLE TO SUPPLY COMPLETE CIRCUIT INFORMATION. These units are new and unused. Price **£25.00 + £1.00 P&P**

P&P on all Orders except where stated otherwise **20p**  
New Spring List **10p**

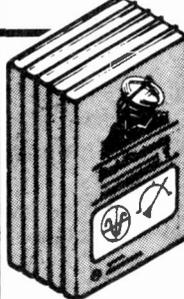**R.F. EQUIPMENT SPARES LIMITED**  
3 LACY CLOSE, WIMBORNE, DORSET



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.  
Bound in stiff linen. Cover size 8 1/2 in x 5 in.  
Price £7.50 per set (we pay the postage).

**Book 1. Introducing Electronics**    **Book 4. Meters/Voltage-dividers**  
**Book 2. Resistors/Capacitors**    **Book 5. Transistor Project Circuitry**  
**Book 3. Inductors/Diodes**

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm, etc., etc.

**FREE.** A list of components for constructing the projects.

Order now:  
**Selray Book Company**  
 60 Hayes Hill  
 Bromley  
 BR2 7HP

**OUR 100% GUARANTEE**  
 Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £ \_\_\_\_\_

Name: \_\_\_\_\_

Address: \_\_\_\_\_

ETI 2

# METAL GLAZE RESISTORS

## PART 10

THIS ARTICLE TAKES A LOOK AT CERMET RESISTORS, AND MOVES ON TO CONSIDER THERMISTORS AND VDR's.

THESE RESISTORS ARE MADE BY fusing a suspension of metal and glass particles to a ceramic rod at temperatures between 750°C and 930°C. This forms a thick resistive film, fused with the surface of the ceramic former, resulting in a resistance element that is virtually impervious to environmental extremes of moisture, temperature, shock and vibration.

The fusion of the metal resistive material and the ceramic rod gives rise to the common name 'CERMET' resistor.

The construction of cermet resistors is generally the same as for film resistors: the desired resistance is obtained by spiralling the resistive element.

Owing to the high firing temperatures, these resistors may be rated for higher temperatures and loads than similar sized film resistors. Conduction of heat away from the resistance element is superior, owing to the better thermal contact possible between the resistance element on the rod and the metal end-caps. Body temperature rise is lower than for comparably-sized resistors of other types having similar ratings. As a

result of these characteristics, cermet resistors are generally smaller than other resistors of the same rating.

The temperature coefficient of cermet resistors is generally comparable with most metal-film and metal-oxide resistors, common types having a TC of  $\pm 100$  ppm/°C. Some types exhibit a TC of +50 ppm/°C and may be as low as  $\pm 25$  ppm/°C. This characteristic shows little variation with the value of the resistor.

Noise level for these resistors is generally higher than for other types, typically ranging from 0.4  $\mu$ V/V to 1.0  $\mu$ V/V, which is worse than other types but far below the level of carbon composition resistors. This level of noise is rarely a problem.

The voltage coefficient is generally better than 100 ppm/V, similar to most other film resistors and is not a consideration in the majority of applications. Generally, the voltage coefficient is only a consideration with carbon composition resistors.

As the construction of cermet resistors is similar to the other types of

film resistors they have similar frequency characteristics. Values below 10k show little variation in value well into the UHF region.

Cermet resistors have excellent stability owing to body temperature being low for the amount of power dissipated. Figures of 0.5 — 1.0% are common. Generally, cermet resistors are manufactured in standard tolerances of  $\pm 2\%$  and  $\pm 5\%$ . Tolerances of  $\pm 1\%$  are available on special order.

Like the common types of metal film resistors, metal glaze or cermet resistors have a hotspot or zero load temperature rating between 150°C and 160°C. They are derated linearly from 70°C as is standard with other film resistors. The derating curve for common types of cermet resistors is given in Figure 1. The miniature 0.5 W type (GLP), and some similar types by other manufacturers, have a hotspot temperature of 155°C, in common with various styles of metal film resistors and are derated according to the curve in Figure 2. Some styles have a dual rating. These are derated linearly from full power at 70°C to half power at 125°C, and then from there to 160°C, the hotspot temperature. The curve for these types is given in Figure 3.

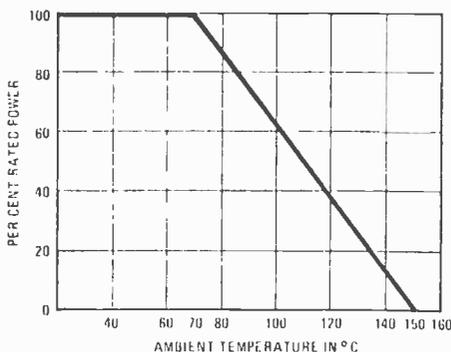


Fig. 1. Derating curve for most common metal glaze resistors - common to the majority of film resistors.

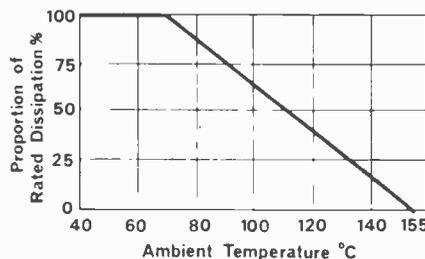


Fig. 2. Derating curve for miniature 0.5 W cermet resistor, type GLP; also applicable to some other manufacturers.

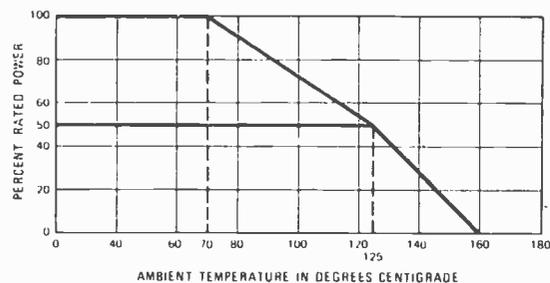


Fig. 3. Derating curve for dual-rated styles of cermet resistors.

# Metal glaze (cermet) resistors

Cermet resistors are generally available in ratings from 0.1 W to 0.5 W, and some less common types up to 5 W. Cost is comparable to most types of film resistors which makes them very attractive where their small size and high power rating is required or in applications where they are likely to experience moisture and temperature extremes, etc. Trimpots are manufactured having cermet resistance elements to take advantage of the ruggedness and resistance to environmental extremes that this type of element offers. The general characteristics of metal glaze or cermet resistors are illustrated in Table 1.

envelope or coated in a special varnish. The helical element provides a uniform pitch allowing a uniform voltage gradient between turns throughout the length of the resistor.

They find application in voltage-multiplier probes, high voltage bleeders, CRT circuits, photocell circuits, ionization equipment etc. They can be obtained in voltage ratings up to 50 kV and wattage ratings from 2 W to 100 W.

Ferrule, terminal lugs and wire lead terminations are available depending on style and application.

Typical temperature coefficients range between 50 ppm/°C and 700 ppm/°C for low resistance values

resistance contact. Axial-lead, terminal lug or ferrule terminations are attached to the silver bands, as required. A protective coating encapsulates the entire resistive film.

These resistors maintain their value well into the UHF region, mounting usually limiting its performance. Values up to 300 ohms vary less than 20% from their nominal dc value up to 400 MHz. Values up to 3k3 vary less than 20% up to 200 MHz. The nominal value decreases with frequency.

These resistors find extensive application as RF dummy loads, antenna terminating resistors etc, and in radar pulse equipment. They are available in wattage ratings up to 100 W and as low as 1 W; values from 20 ohms to 130 M (useful at low frequencies to 100 kHz)

**TABLE 1. General Characteristics of Metal Glaze (Cermet) Resistors**

Rated Wattage @ 70°C	Max. Working Voltage	Max. Operating Temp.	Critical Resistance	Typical Sizes		Typical Resistance Ranges
				Length	Diameter	
0.125 W (@125°C)	250 V	160°C	0.36 M	6.4 mm	2.3 mm	10Ω - 301 k
0.25 W	250 V	160°C	0.36 M	6.4 mm	2.3 mm	10Ω - 301k
0.33 W	350 V	150°C	0.12 M	10 mm	3 mm	10Ω - 270k
0.5 W*	250 V	155°C	0.36 M	5.5 mm	2 mm	2.2Ω - 470k
0.5 W	250 V	150°C	0.36 M	6.4 mm	2.3 mm	6.2Ω - 1 M
0.5 W	500 V	150°	82 k	14.3 mm	5.7 mm	10Ω - 270 k

\*IRC type GLP - see text, miniature 0.5 W resistor.

(1) Wattage rating assumes voltage limit not exceeded.

(2) Max. Working Voltage assumes wattage rating not exceeded.

(3) Max. Operating Temperature is equal to hot-spot temperature.

(4) Sizes given are body sizes for axial-lead types.

## Miscellaneous Special Types

Special applications call for resistors having particular characteristics. Special resistors are manufactured, taking advantage of certain properties of different materials or construction techniques, to meet the requirements of applications outside those normally found with ordinary resistors.

High voltage circuitry requires resistors having very high maximum working voltages (up to 50 kV in some cases). RF applications require resistors that substantially maintain their dc value up to quite high frequencies as well as being able to dissipate considerable power. Various special resistors having controlled non-linear temperature or voltage characteristics are also useful in a variety of circuit applications.

## High Voltage Resistors

High voltage resistors generally have higher values than the normal range of resistor types. Values up to  $10^{13}$  ohms are available.

They are constructed of a carbon-composition film applied in helical form to a ceramic tube, resulting in a long conducting path. The element may be mounted in an evacuated glass

and high resistance values respectively.

High voltage resistors generally have a hotspot temperature of 100°C although this is much greater for forced-air cooled and oil-cooled types occasionally encountered. Those operated in free air are derated from 25°C as indicated in Figure 4. Note that it is non-linear.

These resistors are available in values ranging from 2k5 to 10<sup>5</sup>M generally, higher values by special order.

Dimensions depend on wattage rating and intended application.

## High Frequency Resistors

These resistors have a specially designed resistance film which provides optimum performance on all desired characteristics while operating up to quite high frequencies. The cross-sectional area of the resistive element is kept small (less than 0.3 mm!) to assure low inherent capacitance and freedom from skin effect. The resistance element is generally not spiralled in order to reduce inductance effects.

Terminal bands of colloidal silver are deposited over the ends of the resistive element, forming a permanent, low-

and voltage ratings to about 10 kV. They are derated from 25°C in free air, as per Figure 4, and have a hotspot temperature of 100°C - more if forced-air cooled or oil cooled.

## Thermistors

Thermistors belong to a group of resistors made from semiconductor materials and are thermally sensitive, having a controlled temperature co-

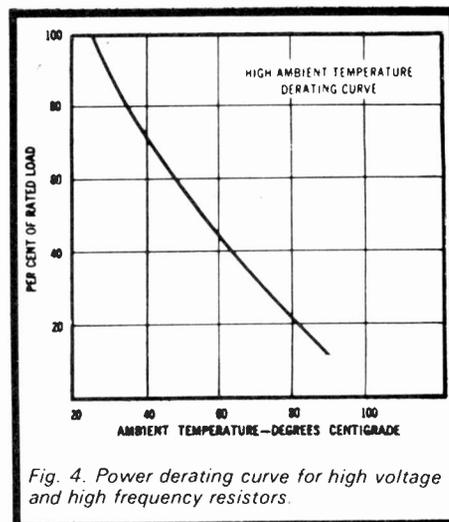


Fig. 4. Power derating curve for high voltage and high frequency resistors.

efficient that may be positive (PTC thermistors) or negative (NTC thermistors).

Thermistors are widely used for temperature measurement and control, temperature stabilisation, current surge suppression, and a wide variety of other applications. They are non-reactive and non-polarised and are therefore suitable for use in either ac or dc circuits.

The resistive element consists of barium titanate in PTC thermistors and various metal oxides in NTC thermistors. The compounds are sintered into special shapes, depending on the required application. They are formed into small elements in a variety of shapes -- generally discs, rods, blocks or tubes. They may be encapsulated simply with a varnish or epoxy or inside a glass or metal tube. Some types are not encapsulated at all.

PTC thermistors are available in two basic characteristics. The 'A' characteristic type exhibits linear change of logarithmic resistance values against temperature. The 'B' characteristic exhibits abrupt increase of resistance when the temperature increases above a specified value, showing only small change in resistance below this temperature.

Some typical PTC thermistors are illustrated in Figure 6. Individual characteristics are best obtained from manufacturers' literature.

NTC thermistors are available covering a wide range of values and temperature ranges. They are available as two basic types -- directly heated and indirectly heated. The directly heated types consist simply of the NTC element with two leads (see Figure 7). Some types have a metal or glass header surrounding the element. A typical

type, made as a water temperature sensor, is also illustrated in Figure 9. Indirectly-heated types consist of an NTC element integrally mounted with a heater.

### Voltage Dependent Resistors

These resistors are generally known as 'Varistors' and are another type of semiconductor resistor. They are principally used as voltage surge suppressors, some types being used in voltage stabiliser applications.

The element generally consists of a sintered ceramic material, the most common types zinc oxide as the main ingredient. Other types employ elements containing titanate ceramic (sometimes known as 'variatite') or silicon carbide (SiC varistors). The common types are often referred to as ZNR varistors from Zinc Oxide Nonlinear Resistor.

The general characteristics of varistors is illustrated in Figure 5. They are available in a wide variety of encapsulations, some are illustrated in Figure 8. They are often found as 'spike' suppressors in solid state TV sets, as back-emf suppressors across relays, and in rectifier circuits protecting rectifiers from voltage surges.

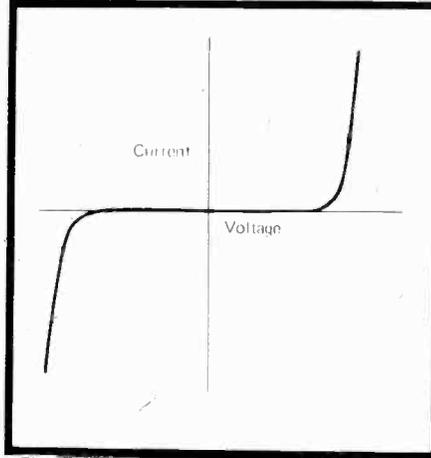


Fig. 5. Varistor voltage-current characteristics.

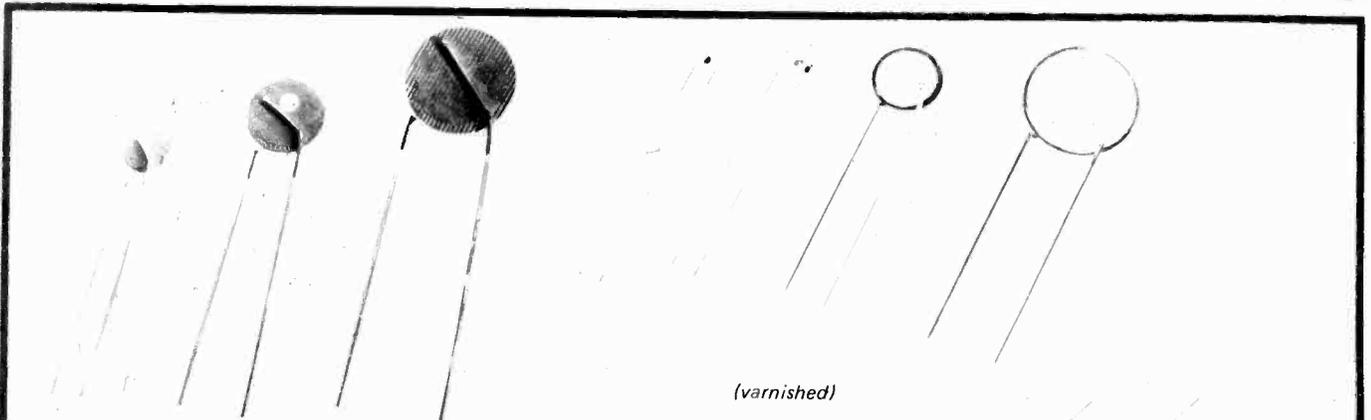


Fig. 6. Typical PTC thermistors (actual size).

Fig. 7. Typical NTC thermistors.

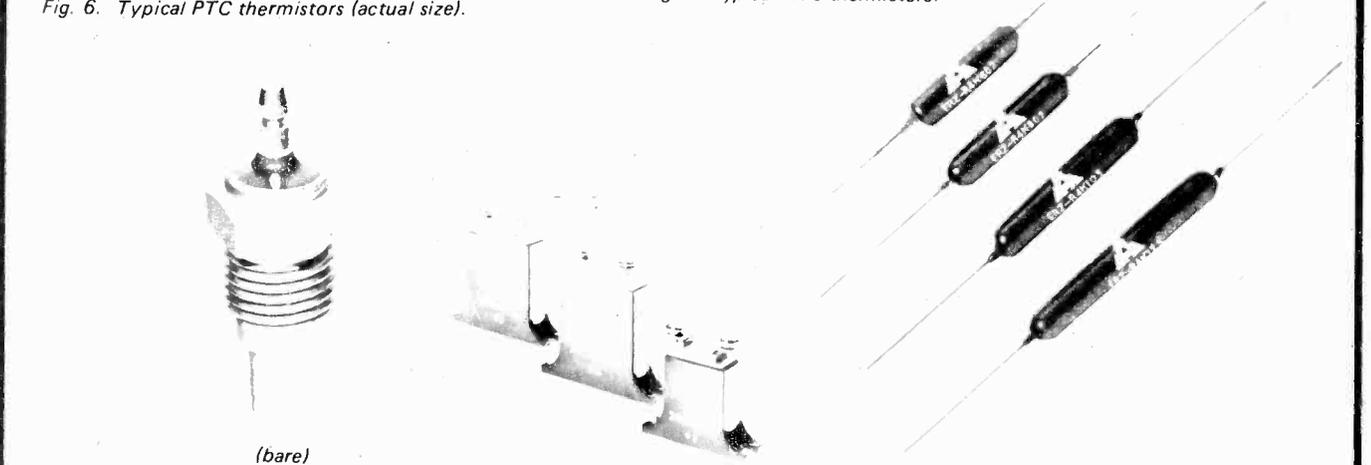


Fig. 9. NTC element as automotive water temperature sensor.

Fig. 8. Various types of varistor encapsulations for different applications.

Worth  
30p


# NEW! For the home constructor

Worth  
30p



Circuit diagram to circuit board in minutes. Layout circuit plan on .1" graph paper. Select Blob Board, lay components out with leads on copper strip. Blob of solder onto lead and your circuit is complete. Blob Boards normally half price of competitive boards. Roller tinned to solder components directly. No drilling or mounting. Modifications in seconds. Blob Board is re-usable.

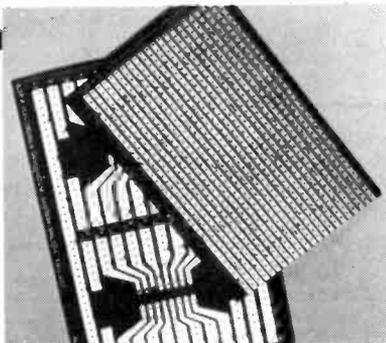Blob Boards are circuit boards designed exclusively for the home constructor and prototype engineer and are normally half the price of competitive boards. Blob Boards are roller tinned for ease of soldering, most require no cutting or breaking of contact rails. HALF PRICE AND RE-USABLE. That is NEW!




## FREE BLOB BOARD!

Blob Board .1" or .15"	1 off	3 off
All approx. inch sizes		
ZB1V 2.5 x 5	£0.30	£0.75
ZB2V 2.5 x 3.75	£0.23	£0.57
ZB3V 3.75 x 5	£0.46	£1.14
ZB4V 10 x 6	£1.51	£3.78
Discrete Blob Board	1 off	3 off
ZB5D 3.6 x 2.4	£0.20	£0.51
ZB6D 2.4 x 7.3	£0.42	£1.05
ZB7D 4.9 x 7.3	£0.69	£1.75
ZB8D 9 x 7.5	£1.62	£4.05
Dip Blob Boards	1 of	3 off
ZB11C 4.5 x 3	£0.36	£0.90
ZB21C 4.8 x 3.2	£0.40	£0.96
ZB41C 4.75 x 7.5	£0.85	£2.13
ZB81C 9.5 x 7.5	£1.70	£4.26

Sample pack: 1 off ZB1V + 1 off ZB8D + 1 off ZB21C normally £2.32 only £2.00 + free Blob Board.

Many other sizes and patterns available add 30p post + 8% VAT to all orders.



## S-DeC

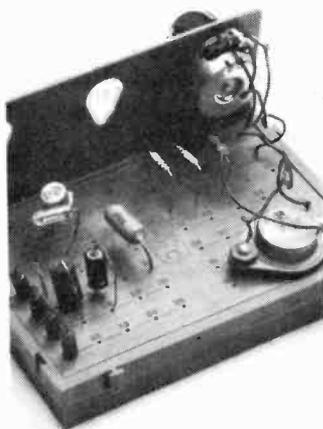

Take an S-DeC, take a small stock of components, insert into S-DeC, no soldering, make a radio receiver, light operated switch, 3 stage amplifier. When circuit is made unplug components and use them again to make a morse practice oscillator, LC oscillator, binary counter and any other discrete circuitry. See Practical Wireless for new series of S-DeC projects. S-DeC + step by step instructions to build above projects and 3 more + which components to use + free control panel for mounting switches, lamps etc. + free Blob Board. S-DeC only £1.98 + 37p (VAT + post) send only £2.35.

If you are using IC's to build circuits use T-DeC for 1 chip circuits and U-DeC A for 2 chip circuits. Draw circuit on graph paper, plug IC into Adaptor and plug into DeC. No soldering, no bent leads, no wasted IC chip. Lines on DeC show contact rails, plug discrete components in. Cross overs, connections are made using different coloured leads. Circuit completed and working unplug components and use for next circuit. No soldering, no damage to components. Use your DeC and small stock of components over and over again. T-DeC send £4.30. U-DeC "A" send £4.60. Adaptor send £2.30.

## T-DeC

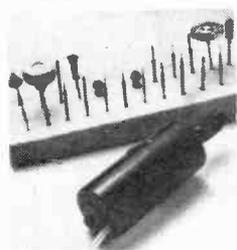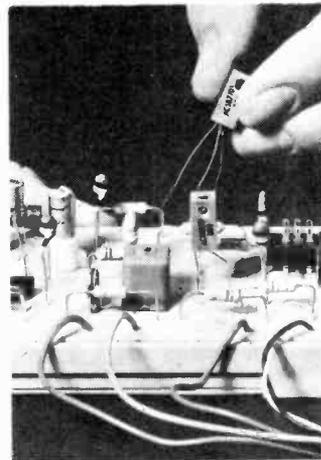

## DRILL · SAW GRIND · BURR BRUSH · POLISH

PB announce a precision British built drill for the home constructor. Works better than most bigger drills and can be used for fine detailed work. Drills through any circuit board, need to break copper strip simply grind it off. 9000 RPM Drill + 20 Assorted tools £11.20 (+VAT + post) send £13.00. 9000 RPM Drill only £5.22 + post + VAT send £6.00. Multi-purpose Drill stand £10.60 + post + VAT send £12.00.



For leaflets and further information please send stamped addressed envelope.

PB Electronics Scotland Ltd.  
57 High Street,  
Saffron Walden Essex.  
CB10 1AA

Mr. Trader please exchange for 1 Blob Board ZB1V worth 30p when purchasing any of the above items.  
Trade enquiries please contact Bandridge, London.  
Mr. John Evans Tel: 01-228 9227

# 30p

# ELECTRONICS —it's easy!

# PART 39

## Coupling electronic stages

### Connection arrangements

As was pointed out in the discussion of meters, electronic subsystems must be cascaded intelligently or loading of the output of a stage by the input impedance of that following may degrade the signal. Output configuration of the various stages involved in instrumentation can take many forms depending on how the earth is connected and if the signal is symmetrical or asymmetrical connected. The six commonly encountered source output schemes are shown at the top of Figure 1. On the left-hand side are seven common kinds of amplifier connection (any other form of black box could be regarded similarly). On the right-hand side are leader lines that show a link between the output of the chosen amplifier and one of

the two most commonly used instrument connections — fully isolated circuit with case only grounded, or one pole grounded to earth. Using the legend, the chart shows the applicability of connections between chosen combinations of source arrangement, amplifier and output device. Not-possible situations usually arise because the earth connection shorts out one of the source arms.

### Matching

Three basic matching criteria exist when connecting two stages together. Figure 2 summarizes these.

If the need is for maximum power transfer, as when driving a loudspeaker from an output stage of an amplifier, the output impedance (usually thought of as an average value of resistance) of the driving stage must equal the input of the stage being driven. When maximum voltage transfer is required, as occurs when a pick-up cartridge or other voltage generating transducer is used or when measuring a voltage in a circuit, the rule is to ensure the connecting stage has a much higher input resistance than the output resistance of the stage producing the voltage signal. A factor of ten to one

Fig. 1a. Chart showing common combination possibilities of various output to input cascaded schemes incorporating amplifier stages of various kinds between the first stage and the two commonly used output recording / monitoring connections. (Courtesy Siemens Industries)

Measuring source		Type of amplifier								Applicability of the amplifier	
		Earthed asymm.	Isolated asymm.	Asymm. on common-mode voltage	Earthed symm.	Isolated symm.	Symm. on common-mode voltage	Isolated follow-up unit	Earthed follow-up instrument		
Type of amplifier	Earthed asymm.	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Isolated asymm.	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Earthed symm.	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Isolated symm.	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Isolated asymm. screened	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Isolated symm. screened	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]
	Isolating amplifier	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Diagram]	[Legend]



hundred times is usually sufficient.

The opposite situation, that is, loading a high output impedance stage with a low input impedance, arises when the maximum current transfer is required.

In many cases the appropriate buffer amplifier is required to provide the desired matching condition. In certain ac coupled systems — those which do not require a dc patch between stages — a transformer can provide an adequate impedance match in an economic way. Transformers, however, have limited frequency response and must be chosen carefully to suit the signal requirements.
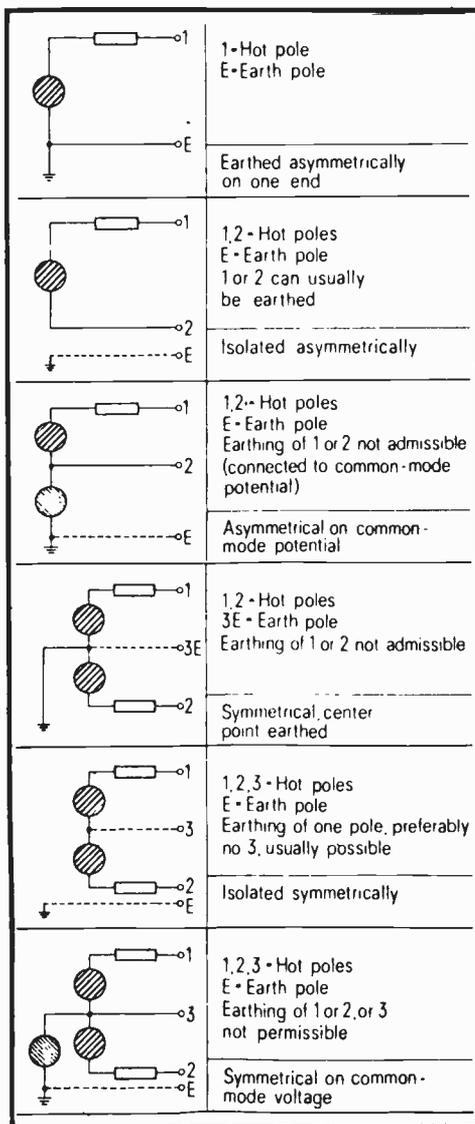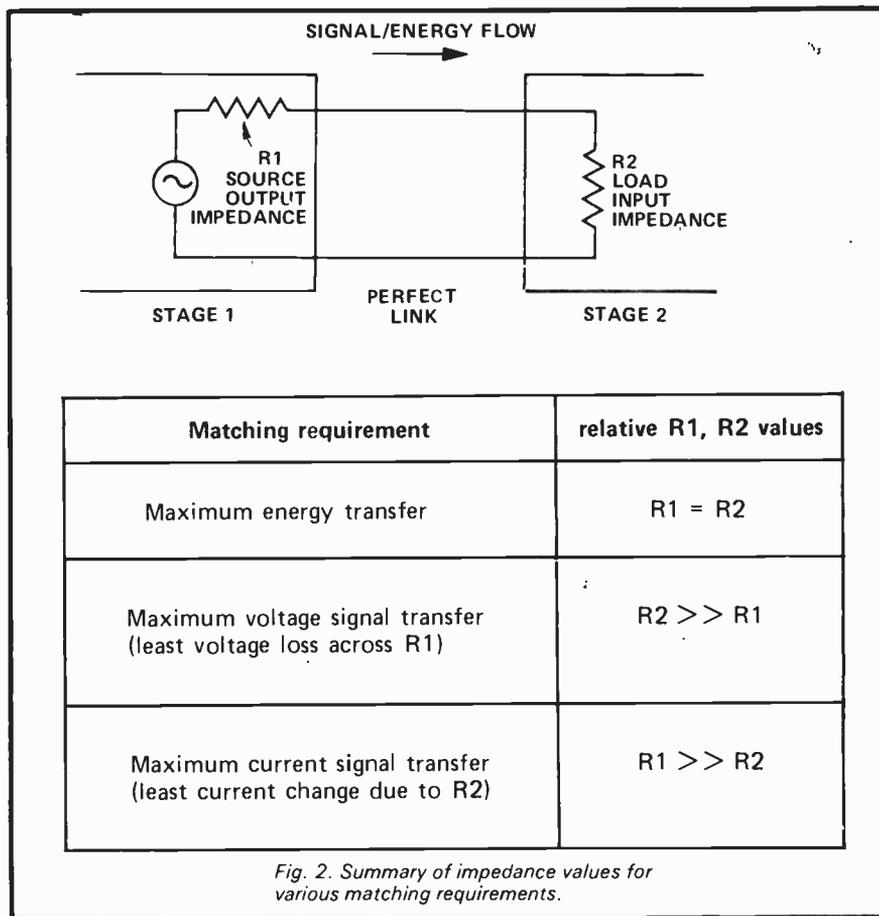
### Eliminating noise

In the ideal situation any circuit added after another should add no more noise energy to the signal than is fed to it. We specify the ratio of the two as the signal/noise or S/N ratio. In practice all circuits, including



connections, will add a finite amount of noise — degrading the S/N ratio. An amplifier or other cascaded stage should ideally increase or modify the signal amplitude without reducing the S/N ratio (input noise will be amplified equally with the signal).

A common unit used to describe the degree of degradation is the noise-figure NF which is calculated as  $NF = 10 \lg (\text{Signal in} / \text{Noise in}, \text{divided by Signal out} / \text{Noise out})$ ; the ratio being expressed in decibels (dB). The perfect additional stage has  $NF = 0$  dB, so-called low-noise amplifier stages will have noise figures better than 3 dB (S/N ratio reduced to half). NF is a function of device characteristics, frequency of operation, source resistance and temperature — the correct choice of components to yield a low NF is a skilled task.

Connections between stages are most common source of noise addi-

tion. Observing several basic rules will usually greatly reduce the noise pick-up in wiring between and within stages.

### Grounding and Shielding

When wiring circuits and interconnections the circuit diagram shows a signal ground. (Terms ground and earth are used somewhat synonymously). This line is assumed to be at exactly the same potential at all points where a ground symbol is indicated. From the electricity supply authority's viewpoint any good low resistance connection to mother earth is a good ground or earth point. But this is not so for instrument stages operating at millivolt and microvolt signal levels. Signals as large as volts can be induced, or dropped, between two points of a metal chassis! The rule for avoiding this ground loop problem is to attach all circuit points required to be grounded to a substantial size copper bus bar — the circuit ground — that is grounded to earth at one place. Better still, use a single common connection point.

Shields of cables are too often assumed to have the same potential at each end, both ends being presumably at ground potential. This is often incorrect for the shield becomes an earth-loop having a

# ELECTRONICS—it's easy!

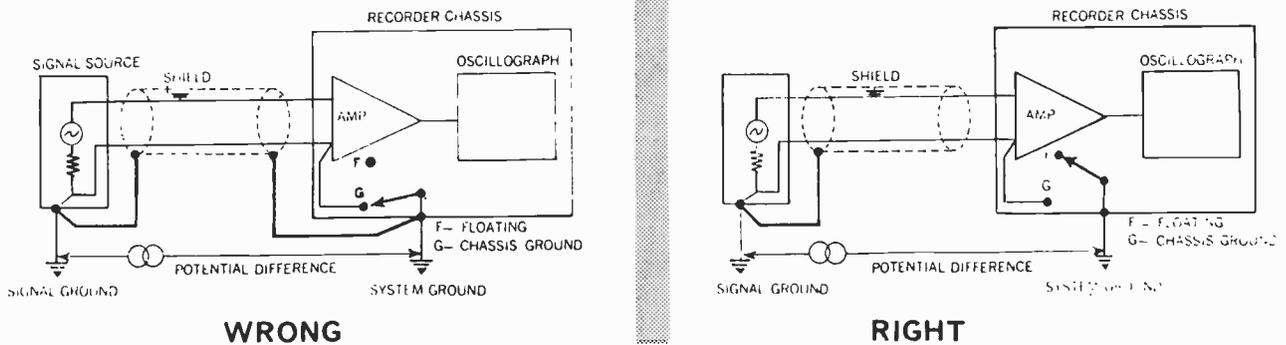


Fig. 3. Correct and incorrect methods of joining a sensor to a recorder. Most output instruments offer the user the choice of leaving the instrument floating above ground or grounding it.

finite resistance when both ends are grounded. Only one end, the input end, should be earthed and the shield should be insulated against earth at all other points. Figure 3 shows the right and wrong ways to connect two stages together with a shielded two-core lead. Special quality low-level signal cables are available. These incorporate an inner twisted-pair that is wrapped inside a multi-layer metal foil along with a bare copper drain wire, the whole being well insulated.

## Common-mode rejection

Before other aspects of connections with cables can be appreciated we need to study the principle of common-mode signal rejection.

We begin by looking at the noise pickup from supply mains radiation by two open wires used to complete a link, as shown in Fig. 4. If both wires are at the same potential above earth, that is, neither is earthed, the noise pickup in each wire will be closely similar. One wire, however, passes signal currents in the opposite direction to the other so noise induced in each wire will add to the signal in one wire and subtract in the other — the result is that the noise just about balances out. This is known as a common-mode rejection arrangement.

It is a balanced system as far as unwanted signals are concerned because of the use of a differential arrangement.

The same concept is used in low-noise, high gain, dc amplifiers — to eliminate transistor defects. A slight disadvantage of differential configurations is that many testing instruments operate with one grounded input. Connecting an oscilloscope to

probe a differential-mode circuit may short out a line to ground in certain connections. For such work a differential input amplifier is essential in the oscilloscope.

Once the signal level has been amplified well above the ambient noise levels the symmetrical dual output can be converted to a single pole with earth output, using a suitably connected operational amplifier.

For the best low-level signal transfer, wiring between stages should observe the common-mode principle, the aim being to make each wire of the pair appear as identical as is possible to the interfering noise sources present. Figure 5 demonstrates why the twisted pair is better than two separate lines to connect a symmetrically-connected source to a following differential input stage. The distributed capacitances of the two wires are different (with resultant different pickup noise) in the open-wire case than they are in the twisted line.

Shielded two-core cables used with a symmetrical outputs source should have the shield grounded at the source, not at the following stage. The latter option degrades the common-mode rejection capability.

Common-mode principles must be carried through completely in exacting low-level signal applications, even to providing identical terminating conditions at the wire ends — similar length open wire ends, similar, dissimilar-metal, conditions at terminal posts with identical temperature for each to ensure identical thermo-electric currents are generated in each lead.

Active devices, such as amplifiers, have a limit to the common-mode signal levels that they can handle. If the induced signals are too great in amplitude, they may saturate the amplifier, removing its ability to operate correctly. It is, therefore, always best to reduce interference at source rather than attempt to eliminate it by common-mode rejection alone.

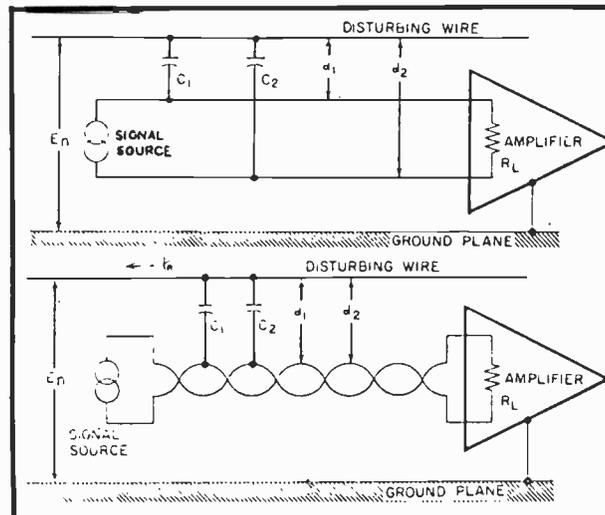


Fig. 4. Common-mode pick-up of noise is balanced out by the differential system.

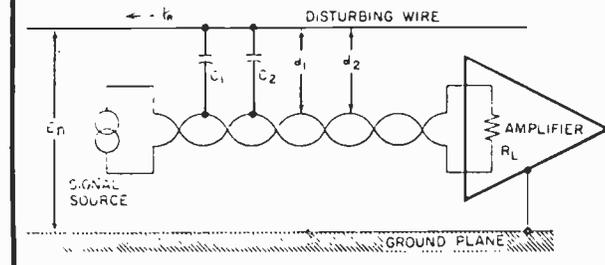


Fig. 5. Twisted wires provide best common-mode rejection when making connections between stages in which a symmetrical signal source is joined to a differential input amplifier.

## RF Shielding

Mains frequency interference (50 Hz) is comparatively easy to eliminate from or retain within equipment by using low conductivity enclosures. RF interference, however, tends to penetrate the best designed enclosure — remember waveguides transmit RF — through apertures of size similar to wavelength. Cracks, where covers join, may act as waveguides for UHF signals. As modern circuits operate with transition times of nanoseconds they too generate considerable quantities of RF energy. By way of example of what can be achieved by careful mechanical construction Figure 6 compares different instrument enclosure designs of a manufacturer. Slots introduced into frame elements form wave-traps (as opposed to waveguides) when the metal covers are bolted in. Modern instrument enclosure design is as much a case of containing RF radiation *inside* the unit as it is to prevent it entering. ●


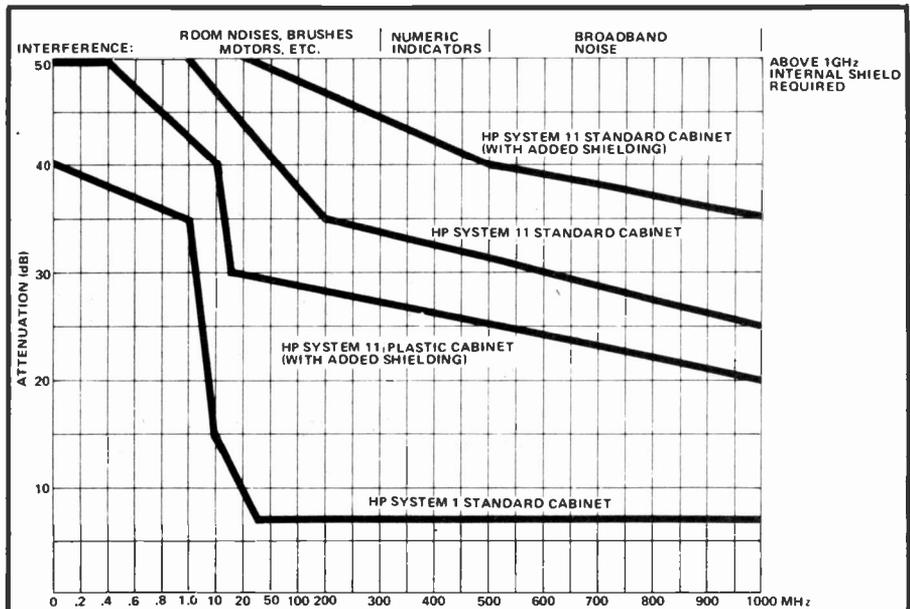


Fig. 6. Shielding of RF energy by various designs of enclosure used for H.P. instruments. The actual value of a particular unit depends upon the need for holes and shafts through the panels.
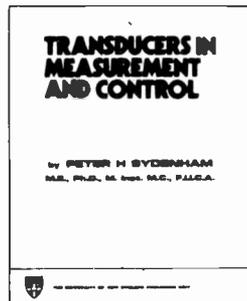
## TRANSDUCERS IN MEASUREMENT AND CONTROL



This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have re-published the series splendidly for use as a standard textbook.


Written by Peter Sydenham, M.E., Ph.D., M.Inst.M.C., F.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book.

ETI-UK has obtained a quantity of this fine book, and it is available at present only from us. Send to: Transducers in Measurement and Control, ETI Specials, Electronics Today International, 25-27 Oxford Street, London W1R 1RF.

**£2.75 inc. postage**

Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead, Editor.

## The GALAXY 2000 (CQ-1) by CASIO

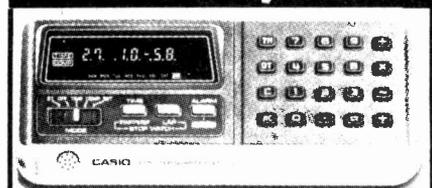

'IT'S 10.58 WEDNESDAY, 27TH'

Executive Pocket Secretary  
5oz, 1 1/4" H x 5 1/4" W x 2 1/2" D

### DIGITAL ALARM CLOCK

Now you can be electronically reminded of up to 4 important appointments per day, perform time and date calculations, perform events timing and routine calculations — all in a lightweight (only 5oz) pocket-sized unit. Ideal for time pressed executives, engineers and students. No more annoying wake-up calls on business trips.

### STOPWATCH

Times up to 10 hours in 0.1 second increments in 3 modes: elapsed time with/without pauses, and cumulative lap times. Display may be unclashed after recording.

### TIME/DATE CALCULATIONS

The CQ-1's special base 60 logic allows time and date difference calculations, time, conversions and a perpetual calendar. You can calculate the number of days left until a contract date or what date and day of the week a payment is due.

### CALCULATOR

Performs the standard 4 functions: +, -, x, / in a full 8 digits. Also constant calculations.

### DISPLAY/POWER SUPPLY

An easy to read green digitron display shows all CQ-1 time, date, stopwatch and calculator outputs. The timer circuitry is powered by 2 digital watch batteries (1 yr. life). The display is run by a standard 1.5v penlight battery (11 hr. life). When the optional AC adaptor is connected a microswitch is tripped, displaying the time constantly.

### A Compact Digital Clock, Calendar, Stopwatch, Calculator, Personal Alarm ... All for

**£29.95**

Adaptor £3.30 for continuous display


All prices inc. VAT and P & P.

Kramer will match any advertised lower price; simply clip the ad and send with order.

### KRAMER & CO.

9 October Place, Holders Hill Road, London NW4 1EJ  
Telex: 888941 ATTN KRAMER. Tel. 01-203 2473  
Mail Order only. SAE for brochures. Export enquiries welcome.

# Greenbank

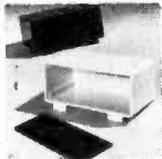

**TIME BOX.** Digital Clock Case 56 x 131 x 71.5 mm with red acrylic window. Choice of case colour, white, red, orange, blue. £2.25.

**"E" LED DISPLAYS.** Class II devices, but fully guaranteed by us, for even segment brilliance, etc. — money back or exchange if not satisfied.

DL-704 0.3in	70p	DL-727E 2 x 0.5in	£1.80
DL-707E 0.3in	70p	DL-750E 0.6in	£1.50
DL-728E 2 x 0.5in	£1.80	DL-747E 0.6in	£1.50

**SOLDERCON PINS** 100 60p  
1000 £4.00  
2500 £8.75  
10,000 half price (£30.00)

**DIL SOCKETS** 15p  
8/14/16 pin

**CMOS WITH DISCOUNTS!** Any mix  
10% for 25+ 25% for 100+ 33% for 1000+

74C00 Series					
74C00 0.25	74C85 1.96	74C1651.31	74C9070.72		
74C02 0.25	74C86 0.69	74C1731.21	74C9082.63		
74C04 0.25	74C89 4.65	74C1741.21	74C9091.74		
74C08 0.25	74C90 0.90	74C1751.21	74C9107.18		
74C10 0.25	74C93 0.90	74C1921.48	74C9141.51		
74C14 1.51	74C95 1.31	74C1931.48	74C9182.89		
74C20 0.25	74C1071.29	74C1951.31	74C9258.28		
74C30 0.25	74C1512.63	74C2007.19	74C9268.28		
74C32 0.25	74C1543.92	74C2211.49	74C9278.28		
74C42 1.93	74C1572.35	74C9901.72	74C9282.28		
74C48 2.37	74C1601.48	74C9902.72	80C95 0.72		
74C73 0.70	74C1611.48	74C9030.72	80C97 0.72		
74C74 0.63	74C1621.48	74C9040.72	88C29 4.13		
74C76 0.70	74C1631.48	74C9057.70	88C30 4.13		
74C83 1.96	74C1641.31	74C9060.72			

4000 Series					
4000 0.20	4027 0.60	4051 1.04	4081 0.24		
4001 0.20	4028 1.00	4052 1.04	4082 0.24		
4002 0.20	4029 1.27	4053 1.04	4085 0.80		
4006 1.31	4030 0.60	4054 1.29	4086 0.80		
4007 0.20	4031 2.45	4055 1.46	4089 1.74		
4008 1.07	4032 1.19	4056 1.46	4093 0.89		
4009 0.60	4033 1.55	4057 29.81	4094 2.08		
4010 0.60	4034 2.11	4059 6.20	4095 1.16		
4011 0.20	4035 1.31	4060 1.24	4096 1.16		
4012 0.20	4036 3.09	4061 25.60	4097 4.13		
4013 0.60	4037 1.06	4062 10.10	4098 1.22		
4014 1.12	4038 1.20	4063 1.22	4099 2.03		
4015 1.12	4039 3.09	4066 0.69	40101 1.76		
4016 0.60	4040 1.19	4067 4.13	40102 2.16		
4017 1.12	4041 0.82	4068 1.24	40103 2.16		
4018 1.12	4042 0.93	4069 0.24	40104 2.26		
4019 0.60	4043 1.12	4070 0.65	40107 0.86		
4020 1.24	4044 1.04	4071 0.24	40108 6.18		
4021 1.12	4045 1.56	4072 0.24	40109 2.21		
4022 1.07	4046 1.48	4073 0.24	40181 4.30		
4023 0.20	4047 1.01	4075 0.24	40182 1.73		
4024 0.87	4048 0.60	4076 1.71	40194 2.26		
4025 0.20	4049 0.60	4077 0.65	40257 2.26		
4026 1.92	4050 0.60	4078 0.24			

14100 and 14400 Series			
14160 1.18	14175 1.04	14415 7.35	14450 2.67
14161 1.18	14194 1.17	14419 2.67	14451 2.67
14162 1.18	14410 5.70	14422 4.98	14490 6.51
14163 1.18	14411 9.54	14435 7.93	
14174 1.08	1441217.07	1444011.58	

1450 Series			
14501 0.20	14518 1.39	1453713.17	14561 0.70
14502 1.38	14519 0.57	14539 1.24	14562 5.59
14503 0.75	14520 1.39	14541 1.82	14566 1.67
14505 4.38	14521 2.77	14543 1.82	14568 3.15
14506 0.57	14522 2.15	14549 4.10	14569 3.72
14507 0.60	14526 2.15	1455210.50	14572 0.27
14508 3.08	14527 1.76	14553 4.66	14580 8.35
14510 1.51	14528 1.22	14554 1.67	14581 4.30
14511 1.74	14529 1.72	14555 1.01	14582 6.64
14512 1.03	14530 0.95	14556 1.01	14583 0.84
14514 3.47	14531 1.74	14557 4.65	14584 0.71
14515 3.47	14532 1.39	14558 1.25	14585 1.10
14516 1.51	14534 8.15	14559 4.10	
14517 4.02	14536 4.00	14560 2.17	

**VEROBOARD**  
0.1" Pitch with copper strips  
2 1/2" x 1" (pack of 5) 61p  
2 1/2" x 3 1/2" 42p  
2 1/2" x 5" 50p  
2 1/2" x 7" £1.54  
3 1/2" x 3 1/2" 50p  
3 1/2" x 5" 56p  
3 1/2" x 7" £1.98  
4.7" x 17.9" £2.55

**CLOCK CHIPS**  
AY-5-1224A 3.50  
MK 50253 £5.50  
MK 50362 £8.00  
MK 50366 (coming)

**OP-AMPS**  
CA 3130 (COS/MOS) £1.00  
CA 3140 (BI MOS) 95p  
741 Minidp 25p

**TIMER IC**  
NE 555 45p

**LIQUID CRYSTAL DISPLAYS**  
4 X 0.5" digits, 40 pin £13.95

**CATALOGUE.** Free on request  
Terms: CWO Add VAT to all prices at 8%  
Post, etc. UK 25p (+2p = 27p) per order. Export add 75p  
(Europe) £2.50 elsewhere, no VAT  
Polys, universities, regd. Cos., etc., can telephone their orders for immediate despatch

**GREENBANK ELECTRONICS (Dept. T5E)**

94 New Chester Road, New Ferry  
Wirral, Merseyside L62 5AG  
England. Tel: 051-645 3391

# BUILD THE TREASURE TRACER MK III



METAL  
LOCATOR

AS SEEN  
ON BBC-1  
& BBC-2  
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz.; handle/knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil **£14.75**

Plus £1.00 P&P  
Plus £1.18 VAT (8%)

Built, tested and Guaranteed **£19.75**

Plus £1.00 P&P  
Plus £1.58 VAT (8%)

**MINIKITS ELECTRONICS,**  
6d Cleveland Road, South Woodford,  
LONDON E18 2AN  
(Mail order only)

# Wilmslow Audio

THE firm  
for  
speakers!



Baker Group 25 3 B or 15 ohm	£13.00
Baker Group 35 3 B or 15 ohm	£14.50
Baker Deluxe 8 or 15 ohm	£17.50
Baker Major, 3 B or 15 ohm	£15.00
Baker Regent, 8 or 15 ohm	£12.50
Baker Superb, 8 or 15 ohm	£22.50
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
Coles 400 1 G super tweeter	£5.90
Coles 400 1 K super tweeter	£5.90
EMI 14" x 9" bass 14A/700 8 ohm	£12.50
EMI 8 x 5, 10 watt, d/c roll/s 8 ohm	£3.95
Elac 59RM 109 15 ohm, 59RM114 8 ohm	£3.50
Elac 6 1/2" d/c roll/s 8 ohm	£3.95
Elac 10" 10RM239 8 ohm	£3.95
Fane Pop 15 watt 12"	£5.75
Fane Pop 55, 12" 60 watt	£16.95
Fane Pop 60 watt, 15"	£19.95
Fane Pop 70 watt 15"	£21.75
Fane Pop 100 watt, 18"	£33.95
Fane Crescendo 12A or 8, 8 or 15 ohm	£42.95
Fane Crescendo 15, 8 or 15 ohm	£54.95
Fane Crescendo 18, 8 or 15 ohm	£75.95
Fane 801T 8" d/c roll/s 8 ohm	£9.50
Goodmans 8P 8 or 15 ohm	£6.50
Goodmans 10P 8 or 15 ohm	£6.95
Goodmans 12P 8 or 15 ohm	£16.50
Goodmans 12P-D 8 or 15 ohm	£18.75
Goodmans 12P-G 8 or 15 ohm	£17.75
Goodmans Audiom 200 8 ohm	£14.95
Goodmans Axent 100 8 ohm	£8.50
Goodmans Axiom 402 8 or 15 ohm	£22.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.60
Kef T27	£8.50
Kef T15	£10.75
Kef B110	£10.95
Kef B200	£11.95
Kef B139	£24.95
Kef DN8	£2.75
Kef DN12	£7.25
Kef DN13	£4.95
Baker Major Module, each	£18.00
Goodmans Mezzo Twinkit, pair	£51.95
Goodmans DIN 20, 4 ohm, each	£15.75
Heime XLK30, pair	£21.95
Heime XLK35, pair	£26.75
Heime XLK40, pair	£38.50
Kefkit I, pair	£59.50
Kefkit III, each	£56.00
Peerless 20-50, pair	£43.95
Peerless 20, 60, pair	£58.50
Richard Allan Twinkit, each	£13.95
Richard Allan Triple 8, each	£20.75
Richard Allan Triple 12, each	£25.95
Richard Allan Super Triple, each	£29.50
Richard Allan CG8T 8" d/c roll/s	£7.95
Wharfedale Denton 2 XP kit, pair	£23.25
Wharfedale Linton 3 XP kit, pair	£49.50
Wharfedale Glendale 3 XP kit, pair	£49.50
Castle Super B RS/DD	£9.95
Jordan Watts Module 4, 8 or 15 ohm	£16.25
Tannoy 10" Monitor HPD	£78.75
Tannoy 12" Monitor HPD	£85.00
Tannoy 15" Monitor HPD	£99.00

Prices correct at 11/3/77

**ALL PRICES INCLUDE VAT**

Cabinets, wadding, Vynair, crossovers etc.

Send stamp for free 38 page booklet  
"Choosing a Speaker"

**FREE with all orders over £10 —**  
"HiFi Loudspeaker Enclosures" Book

All units are guaranteed new and perfect

Prompt despatch

Carriage Speakers up to 12" 60p, 12" £1, 15" £1.75;  
18" £2.50. Kits £1 each (£2 per pair). Tweeters and  
Crossovers 33p each.

**WILMSLOW AUDIO**  
Dept. ETI

Swan Works, Bank Square, Wilmslow,  
Cheshire SK9 1HF. Tel. Wilmslow 29599  
(Discount HiFi, PA and Radio at 10 Swan  
Street, Wilmslow)

Access and Barclaycard orders accepted by  
phone

# ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

A COUPLE OF YEARS ago I mentioned the time code being transmitted from MSF Rugby on 60KHz. This gave BCD time of day information each minute in GMT 24 hour format, there is also a very accurate one pulse per second transmission which can be used for seconds counting. The time is based on the official GMT standard and is corrected for changes of millionths of a second per year.

The problem with this system is that the data is recognised by a cut in the 60KHz carrier and this absolute cut rather than a modulation of the carrier can cause problems in phase locked loop decoders. Changes to allow for BST rather than GMT must be made by the user and this adds further complexity to the circuit. At the time someone sent me a copy of a German magazine with an article on the German DCF77 system which is a similar system being transmitted from near Frankfurt. This is even more complex as it gives time of day (Central European Time), day of the week, day of the month, day of the year and month number. As the 77.5KHz carrier is modulated it would seem that a PLL system could be used to decode the data which is transmitted at one bit per second (this also gives you the option of a seconds counter). The circuit obviously contained a plethora of counters, latches and LEDs and was virtually too complex to consider building. Last year at the Watch and Clock fair in Basle I saw a clock working from DCF77 and it was to say the least very effective to see a clock which had just been plugged in come up with time and date and day, etc.

## Rugby On Line

It was only recently that someone mentioned that they were going to try to feed MSF Rugby into a SC/MP that it occurred to me that feeding DCF77 in as serial data might be a much better idea. The SC/MP could do all of the decoding and displaying whilst checking each bit of data, and comparing it to the previous minute data, as a double check against rubbish.

## Wake me on Thursday

If we now have an MPU with regularly updated, correct time and date (corrected by the MPU for GMT or BST) we can easily add a few alarm features such as:

- 1 Wake me every morning at 7.30 except Saturdays,

Sundays and Bank or personal holidays.

- 2 Remind me of my wife's birthday, anniversaries and more important remind my wife of my birthday.
- 3 Don't wake me on April 1st until after 12.00.
- 4 Correct yourself for GMT/BST changes on the appropriate days.

Add on a few addition features such as one alarm for you, and one half an hour earlier for your wife, snooze alarms which become louder or faster or operate buckets of water, remote displays to other parts of the house and suddenly you have quite a clock.

I should keep your Mickey Mouse Alarm for old times sake — it might be an antique one day!

Now comes the crunch — I have lost (mis-filed) the original data on DCF77. I have the MPU, the displays, etc but I cannot build the receiver (aerial, PLL, etc) nor can I decode the data as I do not know what sequence it is transmitted in. If anybody has this info I would be very glad of a copy and I will publish said info in a future column. On the other hand, if any one has circuits to make up into an article please let us know at ETI.

## Coding distances

One last point on these transmitted time codes, as they are VLF (Very Low Frequency) the reception distance are phenomenal. If MSF can be received and decoded in Athens (quote National Physical Laboratory) then there should be no trouble in picking up DCF77 over most of the UK, does anyone have any figures on this?

## Same device, but —

One of the most annoying things that can happen is when you remove an IC from a circuit and replace it with a brand new identical component and it just sits there and laughs quietly to itself (or even better, decides to start smoking.)

The MM5311 series of clock chips are not known for smoking but they do have a habit of not liking a circuit in which an identical device from another batch works perfectly. Take the MM5314 for example, out of several thousand devices I have known one *literally* blow up! and two others to be faulty — one gold star for National. National are also the sort of company that will redesign a product if they think that they can make it better, another gold star for NS.

Unfortunately in designing some of the later chips in this family National decided to change the design of all of the family to make them all as compatible as possible. This means that a three or four-year-old circuit for the early MM5311, 12, 13 or 14 will not necessarily operate with one of the later batches of chips.

The usual problem is that the new chip will only display one digit at a time or will multiplex very slowly giving an unsettling flashing effect. The cure for this is to change the values of the components connected to the multiplexing input from the typical 100K and 0.01uF to something more like 470K and 0.01uF or even 0.005uF. To my knowledge NS have never published this change and their latest data on these devices still refers to the old component values:

It seems a shame that one of the first clock chips on the market which is still probably one of the most popular with amateur constructors should be treated this way. I suspect that NS have had some disappointed customers with these devices for the sake of a resistor change, black mark and lose two gold stars NS. ●

# Sparkrite mk2

Capacitive discharge  
electronic ignition kits

VOTED BEST  
OF 8 SYSTEMS  
TESTED BY  
'POPULAR  
MOTORING'  
MAGAZINE  
Oct. '74



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service - phone (0922) 33008.

### Improve performance & economy NOW

Note: Vehicles with **current** impulse tachometers (Smiths code on dial R.V. 1) will require a tachometer pulse-slave unit. PRICE £3.35

**PRICES INCLUDE VAT, POST AND PACKING.**

**POST TODAY!**

**Quick installation**  
No engine modification  
required

Electronics Design Associates, Dept. ET5.  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....  
Address .....

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQUIRED
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's  
for **£**

Cheque No. ....

Send SAE if brochure  
only required.

## THE METAC DIGITAL CLOCK

★ COMPLETE KIT ★



- Pleasant green display. 12/24 Hour readout
- Silent Synchronous Accuracy. Fully electronic
- Pulsating colon. Push-button setting
- Building time 1 hr. Attractive acrylic case
- Easy to follow instructions. Size 10.5 x 5, 7 x 8 cm
- Ready drilled PCB to accept components

**KIT PRICE £9.60 + 76p VAT**

**SAME DAY DESPATCH: ORDERS RECEIVED BEFORE 2.00 P.M. ARE POSTED ON THE SAME DAY**

SEND YOUR ORDER TO

**DAVENTRY**

**UXBRIDGE**

### METAC ELECTRONIC AND TIME

67 HIGH STREET CENTRE 3 THE NEW ARCADE



DAVENTRY

NORTHANTS.

TEL. (032 72) 76545

HIGH STREET

UXBRIDGE

MIDDLESEX

TEL. UXBRIDGE (0895) 56961

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering. Shops open 9-5.30 daily.

# Electronic Components

There are now 2 shops in Tottenham Court Rd. specialising in Electronic Components and Audio Accessories.

### MOTOROLA NATIONAL SIGNETICS

4001	22p	4029	£1.08
4002	22p	4046	£1.62
4007	22p	4049	60p
4011	22p	4050	60p
4012	22p	4059	22p
4013	60p	4070	22p
4015	£1.05	4071	22p
4016	60p	4077	22p
4017	£1.00	4081	22p
4020	£1.08	4093	87p
4023	22p	4511	£1.95
4025	22p	4518	£1.51
4027	60p	M.C14553	£4.59

All items plus 25p P & P unless otherwise stated

All prices inclusive of VAT

Prices correct at time of going to press

### SEVEN SEGMENTS L.E.D. DISPLAYS

Size	Red	Green	C Anode	C Cathode	XAN	£
0 3"						363 1.57
0 3"						364 1.57
0 3"						352 1.89
0 3"						354 1.89
0 6"						662 2.12
0 6"						664 1.89

### ZEN R.D.ODES

400MW 5% 2 7V 30V 13p

1N4148 GENERAL PURPOSE 6p

L.E.D.s 0.125" 17p 0 2" 17p RED ONLY

### PANEL METERS

Size 2 1/2" X 1 1/2" X 1 1/2"	Size 4 1/4" X 3 1/4" X 1 1/2"	£
50 a	50 a	} £4.86
100 a	100 a	
1 MA		
1 MA EDGEWISE	£4.32	3 1/2" X 1 3/4" X 2 1/4"

### VERO BOARD

0 1" 2 1/2" X 3 1/2"	46p	0 1" 3 1/4" X 5" 62p
0 1" 2 1/2" X 5"	50p	0 1" 3 1/4" X 1 1/2" £2.14
0 1" 3 1/4" X 3 1/4"	54p	

### ANTEX SOLDERING IRONS

Model C.15W Model X.25.25W £3.46

### TEST EQUIPMENT

ICE Microtest 80	£15.66	
ICE Super tester 680G	£19.98	+ 50p P & P
ICE Super tester 680R	£24.30	
SINCLAIR DM2 Digital Multimeter	£52.92	
SINCLAIR Mains Unit for above	£3.24	+ £1.75 P & P
SINCLAIR Rechargeable Battery	£12.96	
SINCLAIR Carrying Case	£5.40	

### AMTRON

Electronic Ignition Kit	£18.44	+ £1.00 P & P
Radio Control Transmitter 4-ch	£14.76	+ 85p P & P
Radio Control Receiver	£8.84	+ 50p P & P

Amtron cases in stock. Send SAE for details.

### TTL

NATIONAL TEXAS ITT ETC

7400	18p	7474	38p
7401	18p	7475	50p
7402	18p	7490	50p
7403	18p	7492	50p
7404	18p	74121	54p
7410	18p	74190	£1.62
7413	38p	74191	£1.72
7447	92p	74192	£1.72
7473	42p		

**HIFI CARE (Retail) LTD.**

Dept ET5

7 & 245 Tottenham Court Road  
London, W.1.

Phone: 01-637 0371/8911 Mail Order Dept.  
01-580 7592/4532

Allow 7-14 days for delivery

# COMPONENTS & KITS

from


# Catronics

including

AMATEUR RADIO BULK BUYING GROUP

## LOW COST V.D.U.

as described  
AUG.-SEPT.-OCT.  
issues

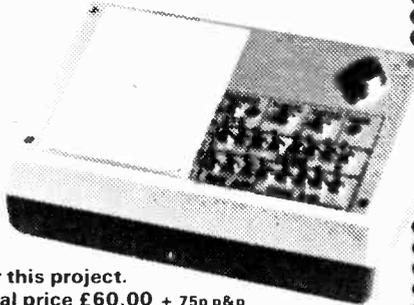


All items available for this project.

Complete Kit at special price £60.00 + 75p p&p

Components also available separately — PCB set, £6.65; 2112-2, £4.50; 2513, £9.25; 555, 47p; 7400 series — see below.

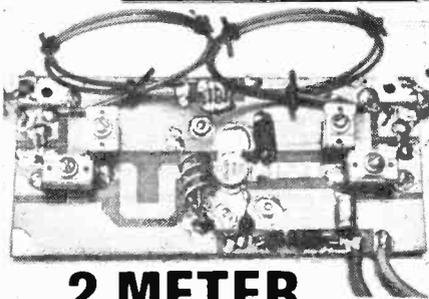Mains transformer — £2.75; Mains on/off switch, 68p; Min. S.P. toggle switch, 54p; Min. push-to-make switch, 34p; High quality plastic case with aluminium front panel (as illustrated in E.T.I. article), £5.65.



**2 METER  
POWER  
AMP**  
as described  
SEPTEMBER  
ISSUE  
(page 19)

## 2 METER POWER AMPLIFIER

Complete Kit to build this 40 watt power amplifier — £18.25

Components available separately — PCB £1.25; 2N6084, £13.95; BAV10, 12p; RG174/U coax, 38p/m.

### PLESSEY SL600, etc. I.C.s

SL610C £2 24	SL611C £2 24	SL612C £2 24	SL613C £3 85
SL620C £3 38	SL621C £3 38	SL622C £8 30	SL623C £6 12
SL624C £3 12	SL630C £2 11	SL640C £3 75	SL641C £3 75
SL1496 £1 05	SL78L06 99p	SL301 £2 19	SL3046 80p

Full data sheets on all SL600 Devices are included in our Data Catalogue (30p + 14p S.A.E.)

### NATIONAL / SIGNETICS / TEXAS TTL

— ALL INCLUDING VAT —

7400 18p	7412 24p	7474 34p	74164 £1.38
7402 19p	7420 19p	7475 56p	74174 £1.19
7403 19p	7421 26p	7483 £1.23	74177 £1.21
7404 22p	7427 29p	7486 35p	74180 £1.17
7406 44p	7428 35p	7490 58p	74H00 35p
7408 26p	7430 21p	7493 65p	74H04 44p
7410 21p	7442 84p	74121 43p	74H10 39p

Quantity discount: 25-99 less 10%; 100 or more, 20%

Send S.A.E. for full price list or 30p plus large 14p S.A.E. for your copy of our Data Catalogue. All prices include VAT at current rates. Please note our minimum U.K. post and packing charge, except where indicated, is 20p. EXPORT ORDERS welcomed — write for export price list.

### COMMUNICATIONS HOUSE

DEPT. 755 **20 WALLINGTON SQUARE**  
WALLINGTON, SURREY, SM6 8RG  
Tel: 01-869 6700 (9 a.m. to 6 p.m., 1 p.m. Sat.)

## ENGINEERS

# FREE

YOURSELF FOR A

# BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

#### ELECTRICAL & ELECTRONICS

- Practical Radio & Electronics (with Kit)
- Electronic Engineering Certificate
- General Elect. Eng. Certificate
- C & G Elect. Installations
- Elect. Install. & Work
- C & G Elect. Technicians

#### RADIO AND TELE-COMMUNICATIONS

- Colour TV Servicing
- C & G Telecoms. Technician's Cert.
- C & G Radio, TV & Electronics Mech. Certificate
- Radio & TV Engineering Course
- Radio, Servicing & Repairs
- Radio Amateur's Exar

#### AUTO & AERO

- Motor Mechanics
- C & G Motor V Mechanics
- General Auto Engineering
- A.M.I.M.I.
- Air Registration Board Certs.
- MAA/IMI Dip.

#### MECHANICAL

- A.M.S.E. (Mech.)
- General Mech. Eng.
- Inst. Engineers & Technicians
- Maintenance Engineering
- Welding

#### MANAGEMENT & PRODUCTION

- Computer Programming
- Inst. of Cost & Management Accts.

#### CONSTRUCTIONAL

- Heating Ventilating & Air Conditioning
- Architectural Draughtmanship & Design
- L.I.O.B.
- Carpentry & Joinery
- Plumbing Technology
- General Building
- Painting & Decorating

#### DRAUGHTSMANSHIP & DESIGN

- General Draughtmanship
- A.M.I.E.D.
- Electrical Draughtmanship



#### G.C.E.

—58 'O' & 'A' Level Subjects  
—over 10,000 Group Passes!

## Aldermaston College

Dept. TET 21, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals) .....

ADDRESS .....

Postcode .....

Other subjects of interest .....

Age .....

Accredited by C.A.C.C.


Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# Doram kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

## 50W PA/Guitar AMP

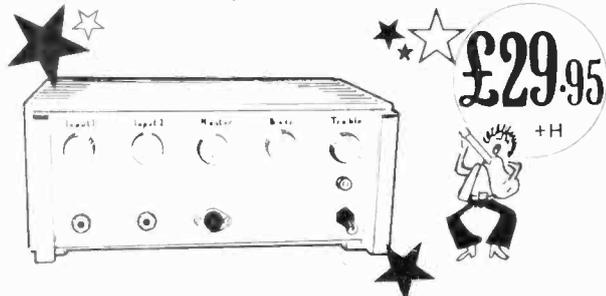

Especially designed for general purpose use with guitars, PA systems etc. This amp will provide 50 Watts RMS into 8 ohms with harmonic distortion level as low as 0.15%. Robust case and load fault protection contribute to the rugged design, which incorporates an IC mixer pre-amp (giving 2 separate inputs) and a thermally compensated power amplifier. Overall freq response (-3dB) is 15Hz to 100KHz with sensitivity 30mV for full output and 52dB sig. to noise ratio.

£29.95 +H VAT (Order 997-011)

O'seas orders — add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD., P.O. BOX TR8  
WELLINGTON ROAD INDUSTRIAL ESTATE, LEEDS LS12 2UF  
An Electrocomponents Group Company

# BE AN ETI GUY (OR GAL)



Some people say that we would sell you the shirt of our back — we guarantee that we haven't worn the T-shirts we mail order!

Be the first on your block with these garish yellow and black beauties!

Send £2.00, payable to ETI, to:

**ETI T-Shirts**  
25-27 Oxford Street  
London W1R 1RF

P.S.: Say if you want small, medium or large!

# ETI CLOCK £13.95

THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE **INCLUDES** VAT AND POST & PACKING



Full size = 5in across and 3 1/2in deep

Our clock shows the time 0.7in. high on bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A bleeper alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc., until you switch the alarm off. The clock also features a mains-failure indicator, and is 12hr. — the alarm being 24 hour.

We have a large number of units in stock for this offer but please allow 28 days for delivery.


**CLOCK OFFER**  
ETI MAGAZINE  
25-27 OXFORD STREET  
LONDON W1R 1RF

I enclose cheque/P.O. for £13.95 (payable to ETI) for an Alarm Clock. Please write your name and address on the back of your cheque to speed processing of your order.

Name .....

ADDRESS .....

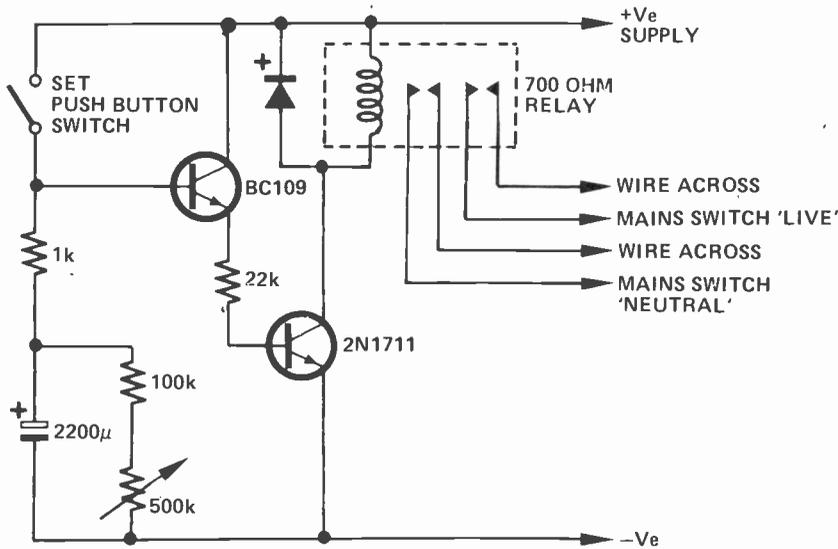
Those not wishing to cut their magazine may order on their own notepaper.


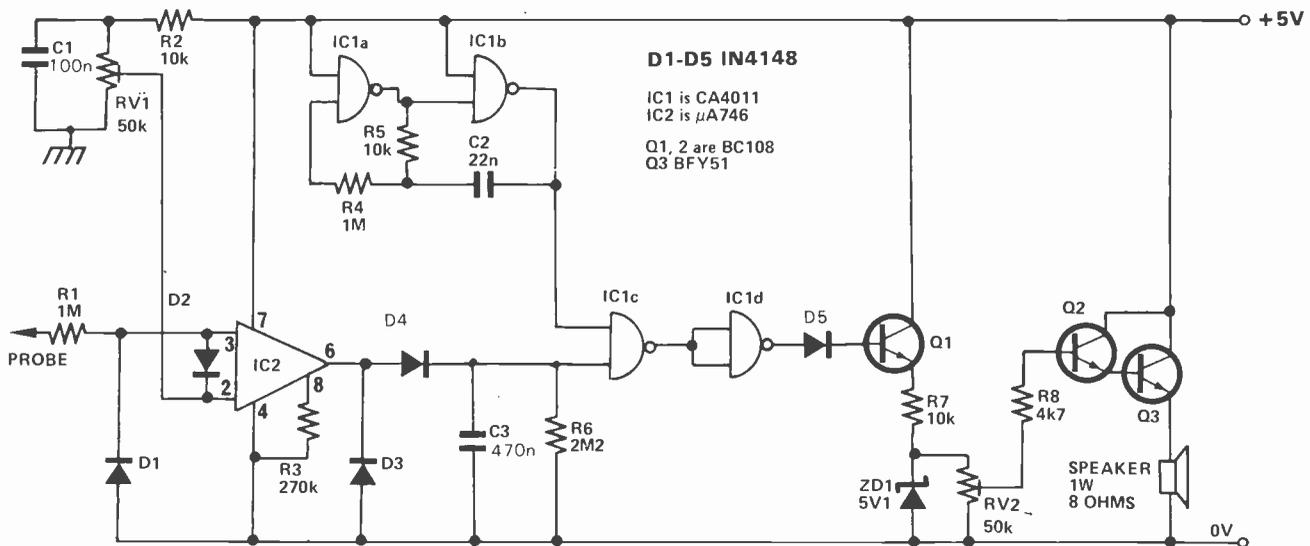
## 'SNOOZE' DELAY UNIT

When the Set switch is depressed the large electrolytic capacitor is charged via the limiting resistor (1k). This charge causes the BC109 to conduct which supplies enough base current to switch on the 2N1711 space and operate the relay. The relay contacts are wired in parallel with the mains switch so that if the mains switch is now turned off, the equipment will continue.

The supply voltage is taken from the equipment in which the unit is fitted and will determine the choice of relay. The maximum delay being 1.75 hours.



## AUDIBLE LOGIC STATE INDICATOR


The indicator will work with either TTL or CMOS circuits. A useful feature is that the unit can be powered by the same supply as the one supplying

the circuit under test. Logic state 1 at the probe will produce an audible tone on the loudspeaker. A switching signal at the probe also activates the loudspeaker.

RV1 sets the threshold level at which IC2 will switch on. This is

normally set at maximum (wiper at the R2 end). RV2 sets the volume of the audible tone, and can be adjusted as required.

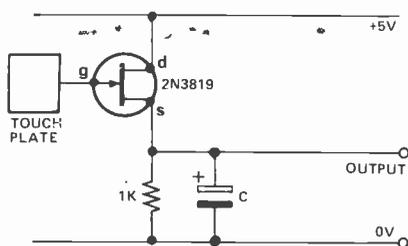IC2 can be substituted by the equivalent LM748, but R3 must be removed first.



## TOUCH-SWITCH FOR LOGIC

An n-channel field-effect transistor is the basis of this simple trigger. In its quiescent state the voltage at the output is about 3V. When the plate is briefly touched with a finger, the minute currents between the body and the plate alter the electric field at the gate of the transistor. The effect is to cause a drop in output voltage. It falls almost to zero and can be used to

trigger a TTL flip-flop. This can be constructed in the usual way, using two NAND gates from a 7400 IC. If several triggering circuits are required, it is more convenient to use the 74118 sextuple bistable latch.

The value of the capacitor is not critical, but 10µF is convenient. The touch-plate can be an area of copper etched on a circuit-board, a square of aluminium foil, or simply a drawing-pin pressed into an insulating support.

# complete DIGITAL CLOCK KITS TEAK CASES



NON ALARM £10.65 VAT + £0.85

ALARM £13.43 + £1.07

## "DELTA"

GENUINE TEAK OR PERSPEX CASE

**DELTA DATA:** 4 Radiant Red 1/2 inch high LEDs. 12 hr display with AM/PM indication. Beautiful Burma Teak Case or Pretty Perspex in White, Black, Blue, Red, Green. Power failure is indicated by flashing display.


**MODULES:** Kits can be bought without case Non Alarm £9.00. Alarm £12.50 incl.

**READY BUILT:** Buy a working tested module and fit your own case Non Alarm £9.50. Alarm £13.00. Or put it with our case parts @ £4.32 and save on complete clock price. Complete Clock ready built 2 yr. guarantee. Non Alarm £13.50. Alarm £16.50

**ALARM FEATURES:** Pulsed tone. Tilt operated 10 minute 'Snooze' period. Single switch setting. Optional extra mercury switch (45p) allows Alarm reset by tilting clock. Digit brightness is automatically controlled to suit lighting level.

**"ALPHA" SPECIAL OFFER** 4 Glowing Green 1/2" High Digits 12 or 24 hr Non Alarm | Built & Tested Module - Plus Perspex Case **£11.00** incl

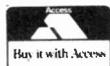Send payment with order S.a.e. for complete range of clocks, calculators & components



### PULSE ELECTRONICS LTD.

DEPT. E4, 202 SHEFFORD ROAD  
CLIFTON, SHEFFORD, BEDS.  
Telephone: Hitchin (0462) 814477

# SD Sol Invictus Detectors Limited

The makers of the famous Viking and Probe detectors bring you... **THE SID DETECTOR KIT**


Enjoy one of the world's most exciting hobbies with this high quality metal detector. Use it to search for gold, silver, coins, jewellery and other valuable articles. The kit is simple to assemble and contains the latest in electronics and design features. It's performance is comparable with detectors costing up to twice as much. The kit includes all components, circuit board speaker and aluminium frame incorporating search head with faraday screen.

Circuit diagram & instructions (included in kit) available separately.
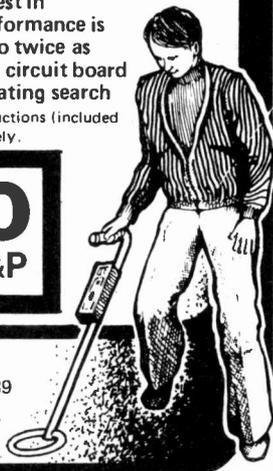
# £14.00

65p P&P

Mail Orders to: 81 Moorgate Street  
Blackburn, Lancs. 0254 62561 & 664789  
Showroom: 3 Sudell Cross, Blackburn,  
Lancs. 0254 56917



# ambit INTERNATIONAL Trade Mark

The Wireless Specialists for components & modules.

EF5800, 7030 & 91196 - .9uV/30dB S/N., 0.2% THD  
Our top three FM tunermodules. (EF5800 shown with cap off).



From left to right, the EF5800 6 circuit varicap FM tunerhead with the 7030 linear phase IF and the 91196 PLL stereo decoder with integral 55kHz 'birdy' filter. The system provides afc muting, meter drives, agc, auto stereo switch, & a specification that exceeds broadcast requirements. Now available with a new EF5801 tunerhead, with FET buffered oscillator output for synthesiser/frequency readout facilities.

EF5801...£17.45; EF5800...£14.00; 7030...£10.95; 91196...£12.99

Complete FM tuner kits/systems (Carriage £3 extra.)

*The Mark 8 Signalmaster - by Larsholt Electronics*

This tuner is based on the popular 7252 tuner set, and provides an incomparable combination of style and performance that can be built by even the relatively inexperienced constructor. Complete kit...£85.00; matching 25+25W amplifier...£79.00.

*International Mark 2 Tuner kits:*

Complete tuner kit, based around the 7253 tuner set, £65.00. Or just the chassis, cabinet, heavy aluminium front panel - for your own choice of modules - see our new info. leaflet on the International Tuner. (SAE please)

## NEW NEW NEW NEW NEW NEW NEW NEW BIONIC FERRET METAL LOCATOR

Ambit has designed a new approach to cost effective sensitive metal locators, and now we proudly present the first of the family of 'Bionic Ferrets'. Details OA, but we can say it will detect a 10p piece at 8-10 inches. Coupled with low power consumption and many innovations, this is the first radically advanced detector that can be made from a kit. £37.99

Radio module selection: (Prices for kits in our catalogue & PL)

EF5800	Ambit 6 stage varicap 88-108MHz tunerhead	£14.00
EF5600	TOKO 5 stage varicap	£12.95
EC3302	TOKO 3 stage varicap	£7.50
7020	Dual ceramic filter FM IF system module	£6.95
92310	MPX decoder, with stereo filter and preamp	£6.95
93090	MPX decoder with CA3090AQ + filter stage	£7.35
91197	MW/LW varicap AM tuner module	£11.35
771	New 'Off-Air' UHF varicap TV sound tuner module with mute, AFC, dual conversion, PSU	£27.00
9014	MW/LW/Stereo FM tuner chassis. Mech. tuned	£26.00

Components: ICs, coils, filters, trimmers, diode law pots etc.

HA1137W/3089E	FM IF	1.94	TOKO AM IFTs:	
TBA120	FM IF and demod	0.75	455/470kHz types	0.30
MC1350	FM IF preamp	0.97	10.7MHz types	0.33
SN76660N	FM IF and det.	0.75	(10mm square, with int. cap.)	
MC1310/4400	PLL MPX	2.20	455kHz ceramic IF filters	
CA3090AQ	PLL MPX	3.75	4 or 7 kHz bandwidths	1.95
HA1196	PLL MPX	4.20	455kHz ceramic IF filters	
UA720	AM radio system	1.40	6 or 8 kHz bandwidth CFT	0.55
TBA651	AM radio system	1.81	SFD455 (Murata)	0.75
HA1197	AM radio system	1.40	455kHz dual ceramic CFX	1.80
LM1496	balanced mixer	1.25	10.7MHz filters for WBFM:	
11C90	600MHz decade ctr	14.00	3132A 6 pole lin phase	2.25
LM380N	2 W Audio	1.00	3125N 4 pole lin phase	1.30
LM381N	audio preamp st.	1.81	CFS ceramic filters	0.50
TD2020	20W audio amp	2.99	Pilot tone (MPX) filters:	
TC940	10W audio amp	1.80	BLR3107N stereo	1.90
NE723	voltage reg IC	0.80*	BLR2007N	1.95
TD1412	12v 600mA reg	0.95*	BLR3152/mono	0.97
78M20	20v 500mA	1.20*	BLR3172N tape bias trap, with 85 or 100kHz pole	0.97
TA4550B	varicap regulator	0.50*	various chokes etc. see price list	
NE560/1/2B	PLL ICs	3.50*		
ICL8038CC	function gen	4.50*		


22turn 100k diode law trim pots, with integral knob 40p  
270° rotary 100k diode law tuning pot 32p  
Also...meters for tuners, AM tuning varicaps, MOSFETs etc....

post/packing 22p per order - except where indicated

General: All prices shown here exclude VAT, which is generally 12 1/2% (Except where marked\*). The latest price leaflet is available FOC with an SAE. Please send a (large) SAE with any enquiries. Full catalogue still 40p.

37 High Street, Brentwood, Essex. CM14 4RH.  
TELEPHONE (0277) 216029 - after 3pm if possible please.

# tech-tips

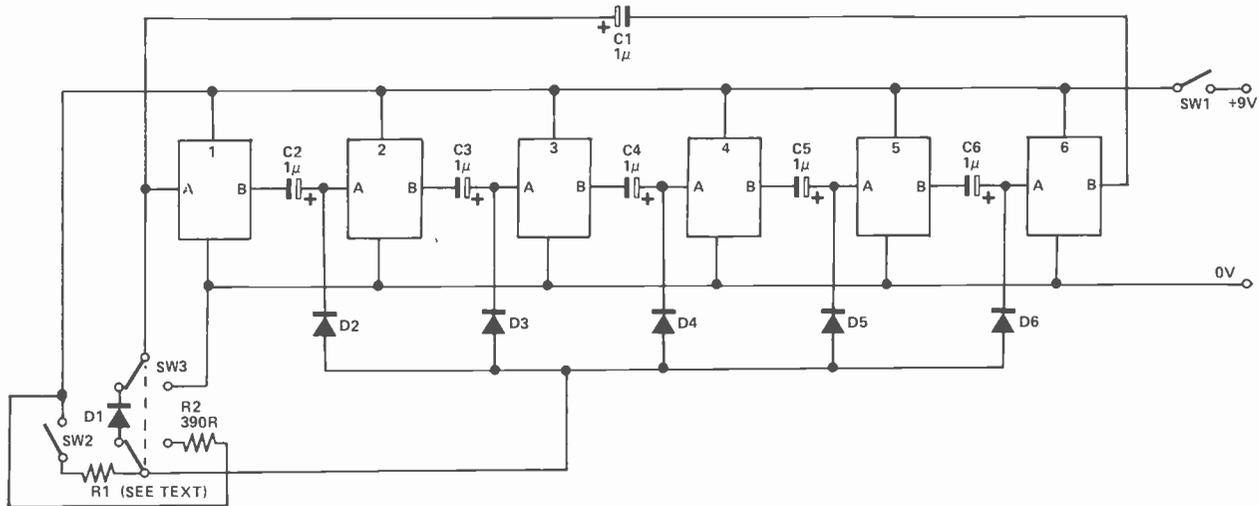

## 'FREEZING' SEQUENTIAL OSCILLATOR


After switch on SW3 (a dpco) is operated and then returned to its normal position. This switches off the first module, and switches on all the others via the diodes. A biased switch may be used.

On the closure of SW2, a number of LEDs will flash in sequence. On the opening of SW2, the circuit will 'freeze' in whatever state it was in, the LED remaining on.

The basic circuit consists of a number of transistor pairs, one for each LED. They are connected in a 'ring' by capacitors from the emitter of one pair to the base of the next. The LED associated with each pair is driven by the inverter-driver transistor Q3.


The rate of oscillation is dependent on R1, a value of 10 k gives a rate just faster than the eye can perceive.

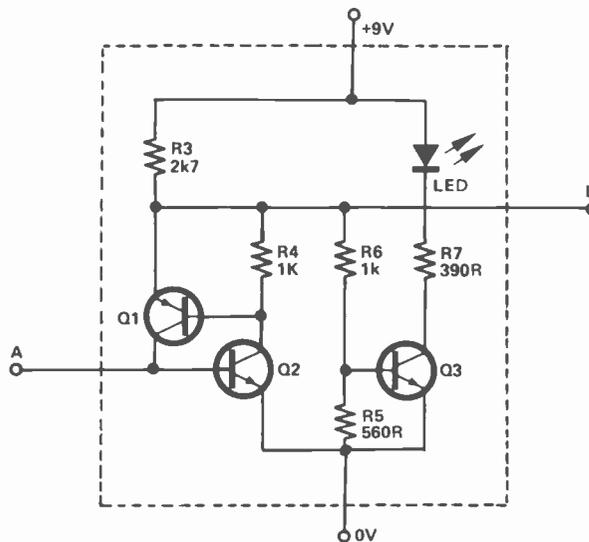Q1 is a BC212. Q2, Q3 are BC108s. All diodes are 1N4148s.


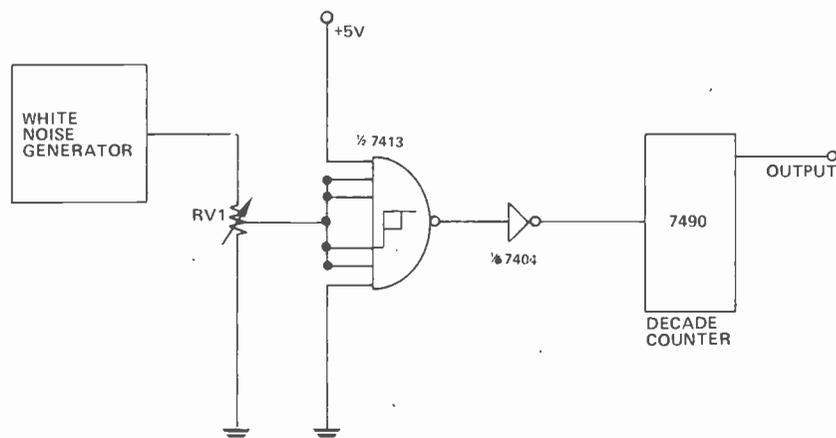
## RANDOM PULSE GENERATOR

The 7413 provides a means of 'squaring up' waveforms before applying them to logic circuits. A reverse biased germanium diode is used to provide random 'sine-wave' type pulses, i.e. white noise. The output from the white noise generator is fed into the input of the 7413. When the output from the generator attains the value of 1.8V, the output goes low and the output from the hex inverter goes high. This output is then fed to the counter. By making the output from the white noise generator variable, via a potentiometer, some degree of control over the 'randomness' may be obtained.



# Stirling Sound

## QV MODULES FOR COST-CONSCIOUS CONSTRUCTORS

STIRLING SOUND QV Modules are our own designs manufactured in our own Essex factory. Production standards are carefully controlled and you, the constructor, benefit directly from our many years of experience in meeting demand for components as well as by buying direct from us.


### PRE-AMPS & CONTROL MODULES

#### Unit One

Combined pre-amp with active tone-control circuits. 200mV output for 50mV in. Runs on 10 to 16V supply, treble  $\pm 15$ dB at 10KHz, bass  $\pm 15$ dB at 30Hz. Stereo bal., vol., treble & bass controls.

**SS.100** Active tone control, bass & treble. **£7.80**  
**£1.60**

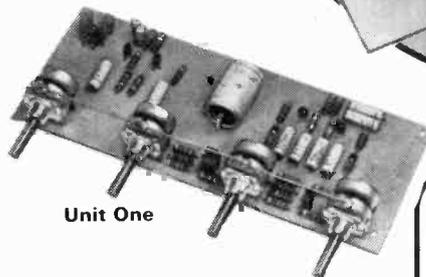**SS.101** Pre-amp for ceramic cartridges, etc., passive tone control circuit shown in data supplied. **£1.60**



Unit One

**SS.102 STEREO PRE-AMP**  
R.I.A.A. corrected for mag. p/ups, tape, radio, etc. **£2.65**

### POWER AMPLIFIERS

**SS.103** A 3 watt amplifier using single I.C. type SL 60745 with built-in short circuit protection. **£1.75**  
**SS.103-3.** Stereo version (2 I.C.s) of above. **£3.25**

**SS.105** 5 watts R.M.S. into 4 ohms using 12V supply. Ideal for use in in-car entertainment. Size: 89 x 51 x 19mm. **£2.25**

**SS.110** Similar in size and design to SS.105, this QV module delivers 10 watts R.M.S. into 4 ohms using a 24V supply, e.g. SS.324. Of great use in domestic applications. **£2.75**

**SS.120** Using a 34 volt supply, such as SS.334, this amplifier will deliver 20 watts into a 4 ohm load. Same dimensions as above. **£3.25**

*There are suitable Stirling Sound power supplies for all the above. When ordered with above amplifier VAT becomes 12½%.*

### FM TUNING

**SS.201** FM Front End with geared slow motion tuning and A.F.C. facility 88-108MHZ. **£5.00**

**SS.202** 1 F amp A meter and/or A.F.C. can be connected (size 3" x 2"). For use with SS.201. **£2.65**

**SS.203** Stereo decoder (illustrated). For use with Stirling Sound modules or with any other good mono FM tuning section. A LED beacon can be added (Price 18p) to indicate when a stereo signal is tuned in (3" x 2"). **£3.85**

### †THE BUILT-IN QV FACTOR

means Stirling Sound's guarantee of quality and value which gives you today's best buys all round. That's why you'll do better with QV Modules!

# Stirling Sound

A member of the BI-PRE-PAK Group

220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF  
Phone: Southend (0702) 46344. **PERSONAL CALLERS WELCOME**




**SS.140**  
Heavy duty power amplifier giving 40 watts R.M.S. into 4 ohms using 45V. With output capacitor. Good for small discos or P.A.

**£3.95\***

### TODAY'S BEST VALUE IN POWER SUPPLY UNITS

ALL AT 8% VAT

with 13-15V take-off points

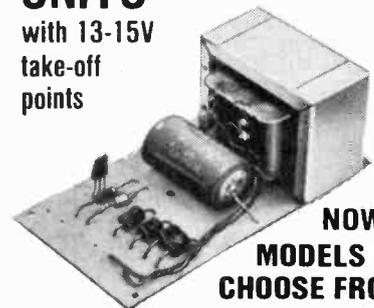

NOW 8 MODELS TO CHOOSE FROM

Compare these guaranteed power packs for power and price. Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take-off point (except SS.312) at around 13-15V adds to their usefulness (P/P 50p any model except SS.370 - £1.)

**SS.312** 12V/1A **£3.75\***

**SS.318** 18V/1A **£4.15\***


**SS.324** 24V/1A **£4.60\***

**SS.334** 34V/2A **£5.20\***

**SS.345** 45V/2A **£6.25\***

**SS.350** 50V/2A **£6.75\***

**SS.300.** Add-on power supply stabilising unit. Short-circuit protected. Ensures stabilised output variable from 12V/2A to 50V max. at 8A. Ideal for workbench and experimenting. **£3.25\*** (P&P 35p)

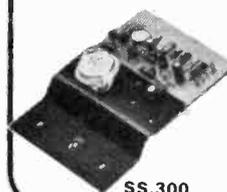

SS.300


### SS.310/350 VARIABLE OUTPUT STABILISED SUPPLY

With continuous variable output at 2A from 10 to 50 V.D.C. With built-in protection against shorting and fully adequate heat sink. Guaranteed. Superb value at **£11.95\***.

### WHEN ORDERING

Add 35p to your order for P&P for mail orders. VAT add 12½% to total value of order unless shown\*, then the rate is 8%. Make cheques, etc., payable to BI-PRE-PAK LTD. Every effort is made to ensure correctness of information at time of going to press. Prices subject to change without notice.

# tech-tips

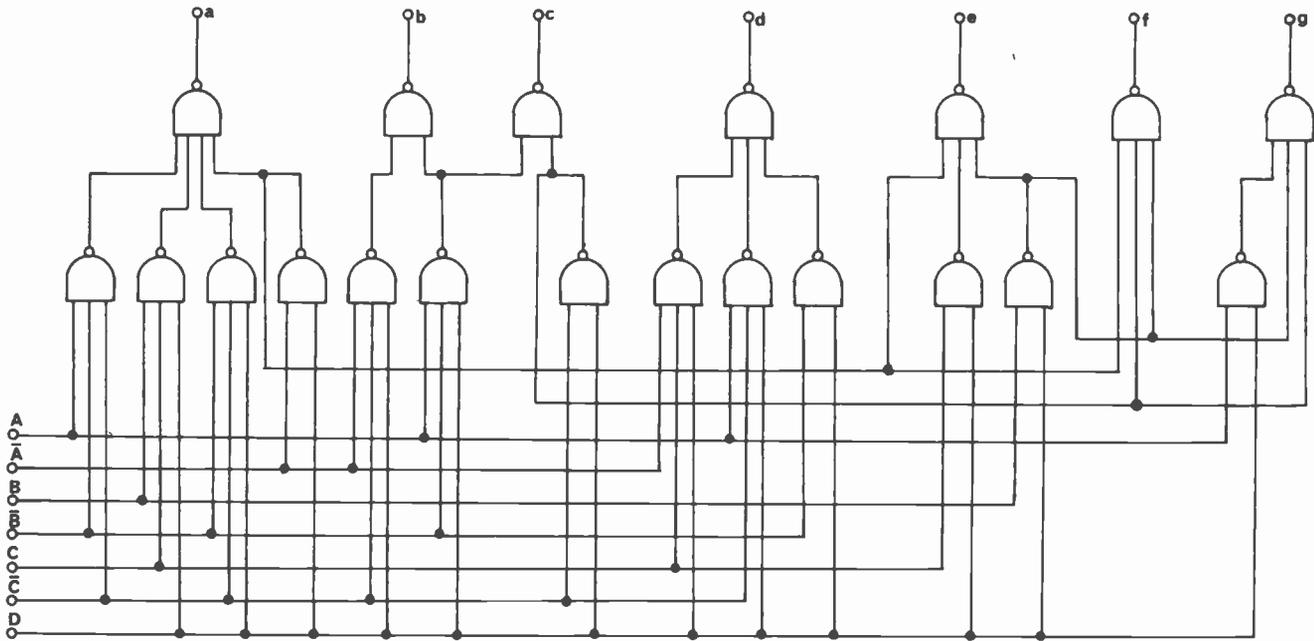

## HEXADECIMAL TO 7-SEGMENT DECODER.


(Inputs of  $A, \bar{A}, B, \bar{B}, C, \bar{C}, \bar{D}$  are needed with an inverting buffer - fan out 30 - on the  $\bar{D}$  input.)

The circuit described below provides an extension to the 7448 BCD to seven-segment decoder, converting it into a hexadecimal to seven-segment decoder which will give the numerals 0-9 and the characters A,B,C,D,E, and F as output for a four bit binary input.

The 7448 is disabled by bringing the blanking input low when the input is greater than  $0111_2$  (i.e.  $\bar{D}$  is connected to B1/RB0 on the 7448.) Outputs from the 7448 and the add-on decoder are OR-ed together creating a single seven-segment output.

D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0
0	1	1	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

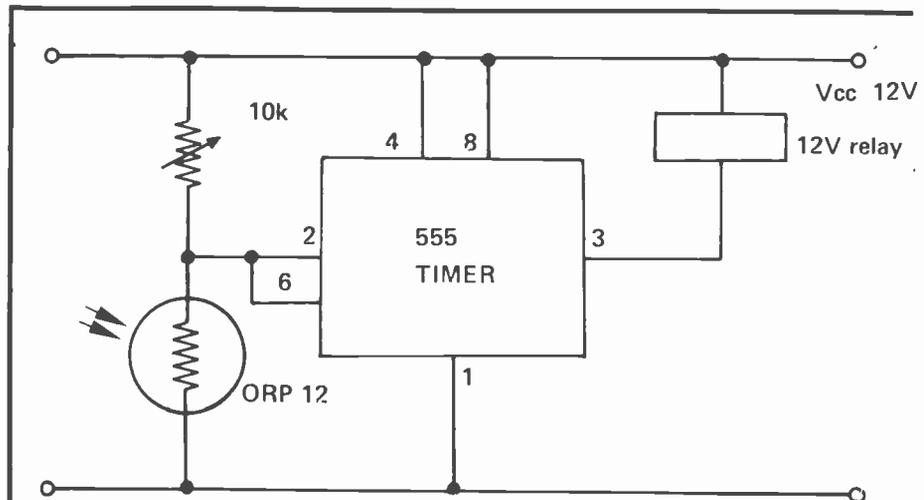TRUTH TABLE for the 'add-on' decoder. Note that when the input is  $0110_2$  ( $6_{10}$ ) a logical one is inserted in the 'a' column to provide the resulting seven-segment '6' with a cap, thus differentiating it from a 'B'.



## SCHMITT TRIGGER

A very useful schmitt trigger can be made by utilising a single 555 timer with its trigger and threshold inputs connected together. The schmitt has a very low input current (1.5uA) and can directly drive a relay taking up to 200mA of current.

The circuit shows a 555 schmitt being used to energise a relay when the

light level on a photoconductive cell falls below a preset value; the relay energises when the voltage on pins 2 and 6 is greater than  $2/3V_{cc}$  and de-energises when the voltage falls below  $1/3V_{cc}$ . This gives a hysteresis of  $1/3V_{cc}$ . The circuit can be used in many other similar applications where a high input impedance and low output impedance are required with the minimum component count.

# 15 — 240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

**APPLICATIONS:** Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV.

**Auxiliary:** 3-100mV; input impedance 47k $\Omega$  at 1kHz

**OUTPUTS:** Tape 100mV, Main output 500mV R.M.S.


**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz

**DISTORTION:** 0.1% at 1kHz, Signal/Noise Ratio 68dB

**OVERLOAD:** 38dB on Magnetic Pick-up, **SUPPLY VOLTAGE:**  $\pm$  16-50V

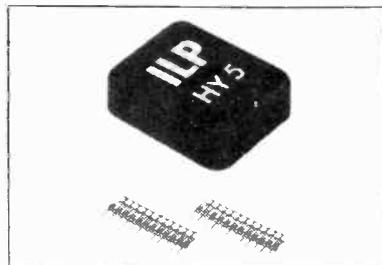**Price £5.22 + 65p VAT P&P free**

HY5 mounting board B1 48p + 6p VAT P&P free



## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P., it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

**APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator


**SPECIFICATIONS:**

**OUTPUT POWER:** 15W R.M.S. into 8 $\Omega$ , **DISTORTION:** 0.1% at 15W

**INPUT SENSITIVITY:** 500mV, **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB.

**SUPPLY VOLTAGE:**  $\pm$  18V

**Price £5.22 + 65p VAT P&P free.**

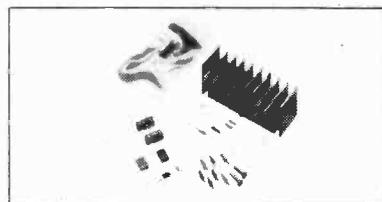

## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

**APPLICATIONS:** Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 25W RMS in 8 $\Omega$  **LOAD IMPEDANCE:** 4-16 $\Omega$ , **DISTORTION:** 0.04% at 25W at 1kHz.

**SIGNAL/NOISE RATIO:** 75dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

**SUPPLY VOLTAGE:**  $\pm$  25V, **SIZE:** 105.50 x 25mm.

**Price £6.82 + 85p VAT P&P free**



## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

**APPLICATIONS:** Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ.

**SPECIFICATIONS:**


**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 60W RMS into 8 $\Omega$ , **LOAD IMPEDANCE:** 4-16 $\Omega$ , **DISTORTION:** 0.04% at 60W at 1 kHz.

**SIGNAL/NOISE RATIO:** 90dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE:**  $\pm$  35V.

**Size:** 114 x 50 x 85mm.

**Price £15.84 + £1.27 VAT P&P free.**

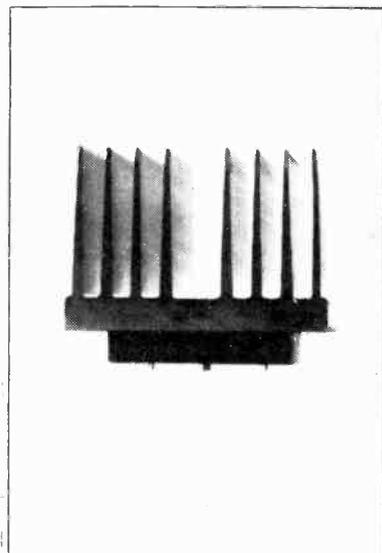

## HY200 120 Watts into 8 $\Omega$

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown — Very low distortion — Load-line protection — Integral Heatsink — No external components

**APPLICATIONS:** Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 120W RMS into 8 $\Omega$ , **LOAD IMPEDANCE:** 4-16 $\Omega$ , **DISTORTION:** 0.05% at 100W at 1kHz.

**SIGNAL/NOISE RATIO:** 96dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE:**  $\pm$  45V.

**SIZE:** 114 x 100 x 85mm

**Price £23.32 + £1.87 VAT P&P free.**

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — No external components

**APPLICATIONS:** Public address — Disco — Power slave — Industrial.


**SPECIFICATIONS:**

**OUTPUT POWER:** 240W RMS into 4 $\Omega$ , **LOAD IMPEDANCE:** 4-16 $\Omega$ , **DISTORTION:** 0.1% at 240W at 1 kHz.

**SIGNAL/NOISE RATIO:** 94dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE:**  $\pm$  45V.

**INPUT SENSITIVITY:** 500mV, **SIZE:** 114 x 100 x 85mm

**Price £32.17 + £2.57 VAT P&P free.**

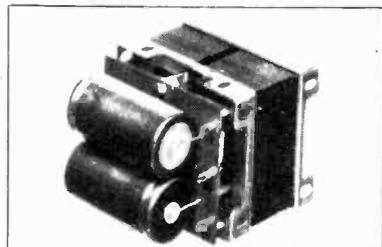

## POWER SUPPLIES

PSU36 suitable for two HY30's **£5.22** plus 65p VAT P/P free  
 PSU50 suitable for two HY50's **£6.82** plus 85p VAT P/P free  
 PSU 70 suitable for 2 HY 120's **£13.75** plus £1.10 VAT P/P free  
 PSU90 suitable for one HY200 **£12.65** plus £1.01 VAT P/P free  
 PSU180 suitable for two HY2000's or one HY400 **£23.10** plus £1.85 VAT P/P free  
 — 48p plus 6p VAT

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd  
 Crossland House  
 Nackington, Canterbury  
 Kent CT4 7AD  
 Tel (0227) 63218

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number \_\_\_\_\_  
 Name & Address \_\_\_\_\_  
 Signature \_\_\_\_\_

# TV-Computersystem 6800 8080 SC/MP

## ROTEX-EMMEN-HOLLAND



The microcomputersystem specially for:



**Education** – schools

– selfstudy

**Industry** – program – development

– systems – development

– terminal

**Hobby** – entertainment

– games



### P.C.B.s FOR ETI PROJECTS

February:		Short Circuits:	
ET1 448	119p	L.E.D. Dice	22p
ET1 448A	26p	Door Bell	56p
ET1 445	29p	Bench Amp	43p
ET1 449	31p		
ET1 449A	58p		
ET1 549	57p		
March:			
ET1 480	94p	Temp Alarm (2 Brds.)	48p
ET1 480PS	106p	Functione Gen.	42p
ET1 155A	26p	Drill Speed Control	52p
ET1 155B	35p		
ET1 155C	88p		
ET1 155D	94p		
April:			
ET1 631F	129p	Bench Supy. PSU	25p
ET1 631R	155p	Fuzz Box	25p
ET1 630	30p	Burglar Alarm	41p
ET1 444A	22p		

All ETI P.C.B.s available from January 1977. Send S.A.E. for price list or telephone. Prices include VAT and post and packing.

Trade enquiries welcome for prototype P.C.B.s and screen printing of front plates, etc

### CLARK SCREEN PRINTERS CLOVELLY, CHELMSFORD ROAD BATTLESBRIDGE, WICKFORD, ESSEX Telephone: Wickford 66751

CARBON FILM RESISTORS. 5% E12 Series, 1/8W, 1/4W, 1/2W. Mixed to your choice, 100 for 90p. Electrolytics 50/15v, 7p. MICRO-PROCESSORS SC/MP £18. MM6800 £33. P&P 15p. Mail Order Only. **CANDAR, 8 Almond Drive, Caversham Park, Reading.**

VHF pocket portable radio tuning 108 to 138 MHz. Very sensitive. Easily adjusted to tune over the 144MHz band. £16.50 (inc. post and VAT). Romak Eng. Ltd., 10 Hibel Road, Macclesfield, Cheshire.

**TURN YOUR SURPLUS** capacitors, transistors, etc., into cash. Contact COLESHARDING & CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

**MPU BUILDERS.** Where else can you get an 8-track, 150 chara./sec. self-contained tape reader like the GEC 66 1A? (Power requirements 235v 50 c/s). Order yours now whilst stocks last! £25 plus £2 carr. plus 8% VAT. Data sheets only 50p. **T. M. & C. Services, 89 Grove Road, South Benfleet, Essex SS7 1JH.**

### Brand New Components

#### Electrolytic Capacitors

25V	25V	25V0V	50V	50V	50V
10	22	100	1.0	4.7	22
	47	250	2.2	10	47
4 1/2	5p	6p	4 1/2p	5p	6p

**Polyester Capacitors.** 250V PC mounting 0.01, 0.015, 0.022, 0.033, 0.047, 3 1/2p; 0.068, 0.1, 4p; 0.15, 0.22, 5p; 0.33, 0.47, 8p; 0.68, 11p; 1.0, 13p; 2.2uF, 22p.

**Carbon Film Resistors.** 0.33W 5% Hi-stability E12 series 4 7/2 = 1M. Any selection. 0.9p each. 0.8p 100+, 0.75p 1000+. Special pack 10 of each value (650 resistors) £4.95.

#### Semiconductors

AC126/7/8	14p	BF194/5	11p	2N1711	18p
AD161/2	35p	BF196/7	13p	2N2219	18p
BC107/8/9	8p	BFY50/51	15p	2N2904/5, 6	15p
BC147/8/9	8p	BFX29	26p	2N2926(R)	7p
BC157/8/9	10p	BFX84	20p	2N2926(G)	7p
BC167/8/9	10p	MJ2955	96p	2N3053	14p
BC177	11p	MPF102	33p	2N3054	42p
BC178/9	12p	1N4001/2	3p	2N3055	38p
BC182/3/4L	10p	1N4003/4	4p	2N5457	33p
BC212/3/4L	11p	1N4005/6	6p	2N5459	38p
BCV70/71/72	13p	1N4148	3p	NE555	37p
BD139	35p	2N697	12p	uA741 DIL	20p
BD140	37p	2N706	9p	LM380	98p

Complete semiconductor kits for ETI projects 50W Power Amp £3.20 Temperature alarm 72p. 100W Power Amp £4.55. Drill speed control 65p.

We are able to supply complete semiconductor kits for most ETI projects. Please write for details stating your requirements. Prices VAT inclusive. Please add 15p carriage. Export enquiries welcome.

C.N. Stevenson (ETI), 304 Avery Hill Road, London SE9 2JN. (ETA 21)

### SAME-DAY DISPATCH

Orders received before 2.00 p.m. are posted on same day

Vero Cases, 60 x 108 x 180 mm	£2.40 + 19p VAT
Push-button Switches	20p + 2p VAT
LED DL707 3"	60p + 4p VAT
Futaba 5LT01 Green Clock Display	£4.60 + 36p VAT
Clock Chip AY1202	£2.80 + 22p VAT
Clock Chip DIL socket	30p + 2p VAT
Clock Printed Circuit Board	75p + 6p VAT
Clock Case	£2.50 + 20p VAT
Clock Circuit Diagram and Assembly Details	45p

+ 30p P & P per order

Barclay and Access welcome  
Send card number with order

### METAC-ELECTRONICS & TIME CENTRE

<b>Uxbridge</b> 3 New Arcade High Street Uxbridge, Middx Tel. (0895) 56961	<b>Daventry</b> 67 High Street Daventry Northants Tel. (032 72) 76545
--	---

Shops open 9 to 5.30 daily

## WANTED

BY

## MARSHALL

A. MARSHALL (LONDON) LTD  
42 Cricklewood Broadway  
LONDON NW2

A young deputy to help our buyer. Methodical, numerate, accurate and conscientious. Maintain law and order in our stock control.

REWARD £2,500 per annum  
(a.a.e.)

RING G. CLIFTON on  
01-452 0161

### TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touch Plates. All with easy to follow instructions.

**NEW! TSD300K — TOUCHSWITCH and DIMMER combined.** ONE touchplate to switch light on or off. Brightness controlled by small knob. **ONLY — £5.95.**

**TS300K — TOUCHSWITCH.** TWO touch plates ON and OFF. **ONLY — £3.67.**

**TSA300K — AUTOMATIC.** One touch plate. Light turns off after preset delay. **ONLY — £3.67.**

LD300K — LIGHT DIMMER KIT — £2.45.

#### SPECIAL OFFER

3-555 TIMER ICs for **ONLY £1.00.**

#### CMOS (Motorola)

4000	16p	4013	51p	4040	97p
4001	16p	4015	91p	4049	48p
4002	16p	4016	51p	4077	45p
4007	16p	4017	91p	4501	20p
4011	16p	4023	17p	4519	56p
4012	17p	4025	17p	4566	155p

TRIACS 400V TO220 Case isolated tab	NE555 8 pin dill	38p
6 5A 80p 8 5A 85p	741 B pin dill	24p
Diac 21p	2N6027 (PUT)	34p
	2N3055	36p

QUANTITY DISCOUNTS ON REQUEST  
Add 8% VAT + 25p P&P. Mail Order Only to.

### T. K. ELECTRONICS (ETI)

106 Studley Grange Road, London W7 2LX

## ADVERTISEMENT INDEX

Ambit	74
Bandridge	83
BIET	71
Bi Pak	5 & 6
Bywood	17
Cambridge Learning	9
Catronics	71
Chiltmead	23
Clarke Screen Printers	Mini ad
C. N. Stevenson	Mini ad
Crofton	Mini ad
Doram	40 & 72
EDA	70
Electrovalue	30

Henry's Radio	11
HiFi Care	70
ILP	78
Kramer	67 & 82
Island Devices	Mini ad
Lynx	23
Maplin	84
Marco	Mini ad
Marshall's	18 & Mini ad
Metac	9, 70 & Mini ad
Minikits	68
P. B. Electronics	63
Pulse	74

Radio Rotex	79
Ramar	Mini ad
R.F. Equipment	59
Selray	59
Sintel	54
Sol Invictus	74
Sterling Sound	76
Swanley	16
Tamtronik	Mini ad
Technomatic	30
Tempus	30
T.K. Electronics	Mini ad
Watford	2
Wilmslow	68

# electronics today reader services

international

## BACK NUMBERS

These cost 40p each. Postage and packing costs 15p for the first, and 10p for each subsequent issue. Orders to ETI BACK ISSUES Dept. please. We CANNOT supply the following issues: All 1972; January, February, April, August, October and November 1973; January, March, September, October, November and December 1974; January, June, July, August, September, November and December 1975; January, March 1976.

## PHOTOCOPYING SERVICE

Due to the steady pressure on our back numbers department, and the dwindling number of issues available, we have set up a photocopying service. This involves our staff in considerable time consuming endeavour, so we hope our readers understand our decision to apply a flat charge of 50p inclusive. This covers any article, regardless of the number of pages involved, from any ONE issue of ETI.

Please state clearly NAME of article, and from which issue the copy you require is taken. Address envelope to 'ETI Photocopy Service'.

## EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your envelope ETI QUERY... Telephone queries can only be answered when technical staff are free, and NEVER before 4 p.m.

## BINDERS

Binders, for up to 13 issues, are available for £2.50 including VAT and carriage. Send orders to ETI BINDERS DEPT. . . .

## SPECIAL ISSUES

Presently we produce six specials. See our ads on pages 10 and 36.

## T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £2.00 each. Send orders to ETI T-SHIRTS Dept. . . .

## BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, P.O. Box 79, Maidenhead, Berks.

## NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

## SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £6. The current rate for readers overseas is £7. Send orders to ETI SUBS Dept. PAYMENT IN STERLING ONLY PLEASE.

## PCBS

PCBs are available for our projects from companies advertising in the magazine.

**NEW ADDRESS FOR ALL ETI DEPARTMENTS:  
25-27 OXFORD STREET, LONDON W1R 1RF**

**PLEASE MARK REVERSE OF EACH CHEQUE  
WITH NAME & ADDRESS AND ITEMS  
REQUIRED.**

**ALLOW 10 TO 14 DAYS FOR DELIVERY**

# STAFF POST ON ETI

## CIRCUIT TRACER/ DETAILER

We require someone to prepare the circuits, pcb patterns and other drawings for ETI. Examples of the type of work can of course be seen in the magazine. A knowledge of pcbs would be useful but not essential.

The successful candidate is likely to have had at least two years' experience and preference will be shown to someone in their mid-20's.

This position has to be filled as soon as possible in order to give a minimum of two month's overlap with Maree Breen who's returning to Australia via a 'walkabout' on the continent.

Salary is negotiable. Apply as soon as possible in writing to:  
**Halvor Moorshead - Editor  
25-27 Oxford Street,  
London W1R 1RF**

*Now there's a  
better way to  
keep your ETI  
copies*



We reckon ETI is worth keeping and our surveys indicate that a staggering 97% of readers keep their copies for at least three months. Now we can offer you a binder which holds 12 issues whose quality befits the magazine: excellent. Send £2.50 which includes VAT and postage) to: **ETI Binders, 25-27 Oxford Street, London, W1R 1RF.**

## Save on Calculators

<b>TEXAS:</b>	
SR52 (mag card, prog, 20 memories) @	£194.37
SR52 (key prog, 100 steps) @	£55.40
PC100 (Printing Unit for SR52 / SR56) @	£177.00
SR51-11 (3 memories / stats) @	£44.40
SR41 (Financial / Business) @	£28.40
SR40 (successor to SR50A) @	£24.40
T130 (15 bracket levels) @	£15.93
T12550 III (sq. mem. / rech.) @	£20.40
T15040PD (Print / Display) /	£84.00
Card Libraries for SR52 @	£27.00
RK2 (each kits for T130) @	£8.10
<b>CASIO:</b>	
FX202P (Key prog., continuous memory	£69.95
FX201P (Key prog., 127 steps, 11 mems.)	£49.95
FX1000 (6+2, sci. / fraction LCD)	£20.40
FX102 (8+2, sci. / fraction)	£17.95
FX21 (6+2 Scientific) @	£15.94
LC820 (LCD 1500 hr bat life) @	£17.95
Micromemory (LCD matchbox size) @	£19.95
Personal M1 (memory + %) @	£7.95
MR121 (12 digit)	£25.95
MR103 (10 digit)	£18.00
CQ1 (Clock + cal + stopwatch)	£29.90

**WE OFFER ALL CASIO LCD WATCHES S.A.E.**

<b>HEWLETT PACKARD:</b>	
21 (8+2) @	£60.00
27 Scientific / management @	£129.00
29 (prog.) (Key programmable 48 steps) @	£105.27
25C (Continuous memory programmable scientific) @	£142.00
67 (mag. card prog.) @	£322.00
97 (mag. card + Printer) @	£580.00
55 (Programmable scientific with timer)	£200.00
9 (Portable scientific with printer) @	£300.00
<b>CBM:</b>	
4 5190R @	£30.40
4148R @	£22.40
PR0100 (8+2, key prog, 72 steps, 10 mems.)	SAE for price
N60 (Navigator) M55 (Maths) S6 (Stats) @	SAE for price
<b>ROCKWELL:</b> 64RD @	£21.50
<b>REALTONE:</b> SC60 (3 mem / stat 10 + 2) @	£24.00
<b>REALTONE:</b> SC6010 (13 mem / stat) @	£42.00


We can match any calculator price in ETI  
**THE REALTONE E4 @ £39.70 p&p £1**



(1382mm x b 178mm x h 116mm) Colour Off-white

- \* Ultimate in new design
- \* AM / FM - FM Stereo Clock Radio
- \* Digitron (Green) Clock
- \* Dimmer Control (use as night light or just for glow)
- \* Automatic Frequency Control
- \* 2 Balanced Speakers
- \* Unique Alarm System
- \* Wake up / Sleep Control up to 59 minutes
- \* Either Alarm, Music or both
- \* Used Display ASA Stopwatch
- \* Display Hrs. + Mins or Min. + Secs.
- \* At £39.70, P&P £1

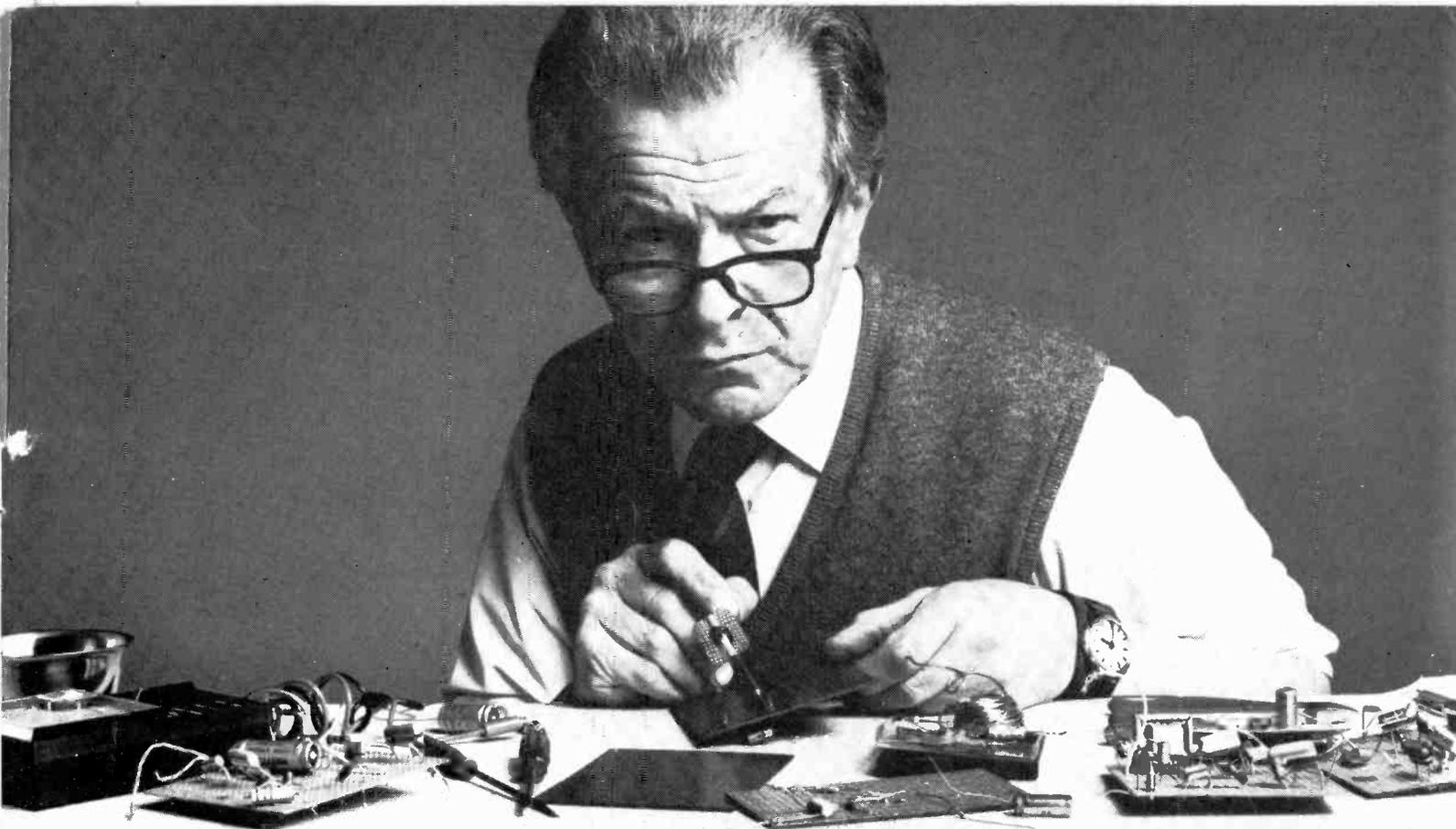All calculator prices inc. VAT & P&P, C.W.O. to:  
**KRAMER & CO.**  
9 October Place, Holders Hill Road, London NW4 1EJ  
Telex: 888941 ATTN KRAMER, Tel: 01-203 2473  
Mail Order only SAE for data sheets. Export enquiries welcome



# Still soldering on?

You may be that rare person who gets his circuit designs right first time, everytime.

But it's much more likely that you experiment to see what works, and what doesn't.

In which case you ought to know about Bandridge Decs.

Bandridge Decs enable you to try almost any number of possible circuits, without having to use your soldering iron.

You simply push the wires of your circuit components into the holes in the Dec to make a perfect solderless contact.

Which means that you can use the components over and over again.

And, of course, we don't have to tell you how much time it will save you.

There are four Decs available

to suit every possible circuitry requirement.

From simple discrete work to 2xDIL or 4xTO5 Station work.

And for larger or more complex circuits you can use any number of Decs linked together.

Eventually of course, you'll need that soldering iron to make up the permanent version of your circuit design.

And when you do you'll probably want to use one of the matching Bandridge Blob boards, to make your job that much easier.

But until then we suggest you put your soldering iron aside and get yourself a Bandridge Dec.

Bandridge Decs - Available at all good component stockists, where you see the Bandridge sign.



S-DEC: for use with discrete components only. (70 contacts)



T-DEC: for discrete work, or linear ICs. (208 contacts)

U-DEC 'B': As DEC A but includes two 16 lead IC sockets. (208 contacts)

U-DEC 'A': allows 2xDIL or 4xTO5 Stations but also takes discrete components. (208 contacts)


A free circuit design booklet is supplied with every Dec.

For your nearest stockist contact Bandridge Ltd., 80a Battersea Rise, London SW11 1EH. Tel: 01-228 9227.
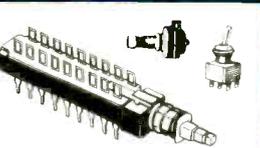
# MAPLIN




The only organ you can build in stages and tailor to your requirements as you go along — and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet — they're coming soon), but we have got the most beautiful sounds — you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system, which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches — there are dozens to choose from, but it's only a tiny part of our fantastic range.



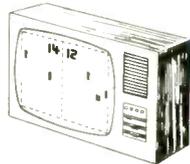A completely self-contained pedal unit. 13-note, 2-octave range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist! Full construction details in our catalogue — post the coupon below now!



Play fascinating games NOW on your own TV in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets — anyone could win — with Maplin's prices everyone can win. Get the May edition of Electronics Today International now — then get all the parts from us at a remarkably low price (I.C. alone £11.99). All prices include V.A.T. and P & P.



This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers (they save you pounds) — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

**MAPLIN ELECTRONIC SUPPLIES**  
 P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR  
 Telephone: Southend (0702) 715155  
 Shop: 284, London Road, Westcliff-on-Sea, Essex  
 (Closed on Monday) Telephone: Southend (0702) 47379

**IT'S A FANTASTIC BESTSELLER!**  
 216 big (11" x 8") pages! Over a thousand illustrations!  
 Over 30 pages of complete projects to build!  
 Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!  
**DON'T MISS OUT! SEND 50p NOW!**

**POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 50p**

Please rush me a copy of your 216 page catalogue by return of post. I enclose 50p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 50p refunded immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

