

electronics today

AUGUST 1978

INTERNATIONAL

45p

LCD DIGITAL MULTIMETER



**NEED
SOME
SCOPE?**

SPECIAL OFFER INSIDE.....

Lab Power Supply


Motoring Electronics

Designing Super-fi Amps

... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...

200 + 200W Dual Channel Amplifier

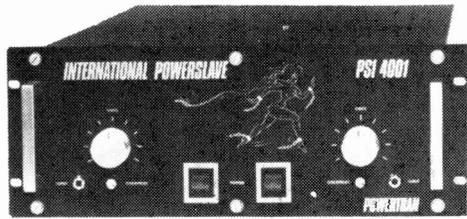COMPLETE KIT AS FEATURED IN APRIL ISSUE OF E.T.I.



PSI 4001 SLAVE MODEL

SPECIAL PRICES FOR COMPLETE KITS!

PSI 4001 — £205.00 + VAT
PSI 4002 — £220.00 + VAT



PSI 4002 STUDIO MODEL

400W rms continuous — 800W peak!
0.03% THD at FULL power!
PLUS all the following features too!

- ★ Each channel totally independent with its own stabilised power supply driven by custom designed TOROIDAL transformers!
- ★ Inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection!
- ★ Ultra low feedback (an incredibly low 14dB overall!) super high slewing rate (20V/μs) 200W rms continuous to 4 ohm from EACH channel, input sensitivity 0.775V (0dB)
- ★ Professional quality components sturdy 19" rack mounting chassis complete with sleeve and feet for free standing work too
- ★ Easy to build — plenty of working space with ready access to all components minimal wiring extensive instructions suitable for both experienced constructors and newcomers to electronics
- ★ Value for money — quality and performance comparable with ready built amplifiers costing over £600!

Pack		Price
1	Fibre glass printed circuit board for power amp	£4.20
2	Set of capacitors, metal oxide resistors, thermistor, cornet pre-sets for power amp	£6.40
3	Set of semiconductors for power amp with mounting hardware, cooling tabs	£27.60
4	Pair of monster black drilled heat sinks, transistor mounting bracket	£6.90
5	Toroidal transformer: Primary 0-117V-234V. Secondaries 42-0-42V, 0-15V, 0-15V. Electrostatic screen	£19.20
6	Set of all parts for stabilised power supply including fibre glass printed circuit board, mounting bracket, semiconductors, resistors, capacitors, etc.	£20.50
7A	Set of all parts for buffer/overdrive unit including fibre glass printed circuit board, semiconductors, resistors, capacitors, controls — required for PSI 4001 only	£3.80
7B	Set of parts for peak power meter including professional quality meter, fibre glass printed circuit boards, components, control — required for PSI 4002 only	£11.50
8	Set of all miscellaneous parts including sockets, illum. mains switches, fuse holders, fuses, cut-outs, cable, etc.	£12.10
9	Cabinet including chassis, anodised silver on black panels, fixing parts, etc. Please state whether Slave or Studio model required	£27.50
10	Handbook £0.50 or free on request when ordering any of above packs. 2 each of packs 1-7 (A or B). 1 each 8, 9 and 10 are required for complete 200 + 200W professional amplifier	PSI 4001 £216.80 PSI 4002 £232.20
Total cost of individually purchased packs		



Kit also available as separate packs

TRANSCENDENT 2000


As featured in July/August issues

COMPLETE KIT ONLY £186.50 + VAT

We are producing a superb kit, at an irresistible price, for the latest and most practical design ever published. Our kit includes fully finished metalwork, pre-assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibre glass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesiser comparable in performance and quality with ready built units selling for between £500 and £700!

MANY MORE KITS ALSO AVAILABLE — ASK FOR OUR FREE CATALOGUE

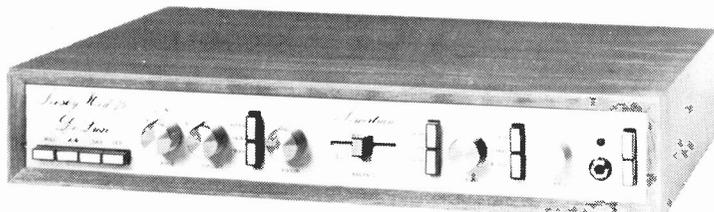Amplifiers (20-200W), Tuners, Cassette Deck, Quadraphonics, etc., etc.



De Luxe Linsley-Hood 75w Amplifier

20 + 20w AMPLIFIER COMPLETE KIT ONLY


Based on P.W. TEXAN £33.10 + VAT

30w VERSION (T30+30) ONLY £38.40 + VAT

75 + 75w AMPLIFIER COMPLETE KIT ONLY £99.30 + VAT

Kit also available as separate packs

T20 + 20 AMPLIFIER

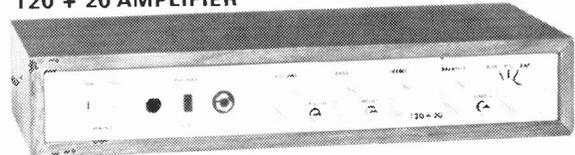

Kit also available as separate packs

PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until September 30th, 1978. If ETI August 1978 issue is mentioned with your order. Errors and VAT rate changes excluded.

U.K. ORDERS: Subject to 12 1/2% surcharge for VAT (i.e. add 1/4 to the price) No charge is made for carriage or at current rate if changed

SECURICOR DELIVERY. For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit

SALES COUNTER: If you prefer to collect your kit from the factory, call at Sales Counter (at rear of factory) Open 9 a.m. - 4.30 p.m. Monday Thursday

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM


ANDOVER
(STD 0264) 64455

electronics today

AUGUST 1978 VOL 7 NO 8 **INTERNATIONAL**



Help a leaf today p.61

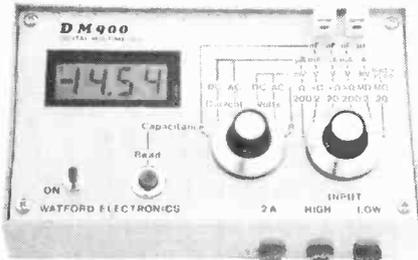

High capacity p.23



Power for all p.75

FEATURES

DESIGNING HI-FI AMPS	15	How the best is designed
ELECTRONICS IN MOTORING	33	New developments abound
TRS 80 HOME COMPUTER REVIEW	39	Tandys entry into the field
VFETS FOR EVERYONE Pt 2	67	Circuits to build and why they work
TECH TIPS	89	Your ideas for you to use

PROJECTS

LCD DIGITAL MULTIMETER	23	Compact multirange design
TRANSCENDENT 2000 Pt 2	45	Putting the synthesiser together
AUTO PLANT WATERER	61	What a drip!
POWER SUPPLY	75	Module based general purpose design

NEWS

NEWS DIGEST	7	Who's up to what
DATA SHEET	57	You can count on this
AUDIOPHILE	79	Goldring G900SE Mk 2 — how good?
MICROFILE	83	Interfacing to be faced
ELECTRONICS TOMORROW	87	Lens an ear to cameras

INFORMATION

SPECIALS	10	Our other publications
SUBSCRIPTIONS	11	Saves all the trouble
ETI PRINTS	13	Others ways make you board
MARKET PLACE	30	Oscilloscope super-bargain.
ETI BOOK SERVICE	44	Fine print to be read
SEPTEMBER PREVIEW	54	Next month we have
PROJECT BOOK SIX	64	Its new and its the best!
COMPUTER BOOKS	77	Some very-soft wares

INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Les Bell Acting Editor
Holland	Anton Kriegsman Editor-in-Chief
CANADA	Steve Braidwood Editor Graham Wideman Assistant Editor
GERMANY	Udo Wittig Editor



EDITORIAL AND ADVERTISEMENT OFFICE

25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 8811896

Halvor W. Moorshead	Editor
Ron Harris B.Sc	Assistant Editor
Gary Evans	Projects Editor
Jim Perry	Specials Editor
Phil Cohen B.Sc, William King	Editorial Asslstants
John Koblanski	Project Design
Steve Ramsahadeo	Project Development
Paul Edwards	Technical Illustrator
Margaret Hewitt	Administration
Andrew Scott	Office Manager
Kim Hamlin, Bren Goodwin	Reader Services
Tim Salmon, Val Tregidgo	Advertising
Mark Strathern (Manager), Tom Moloney	

PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF
 DISTRIBUTED BY Argus Distribution Ltd. (British Isles)
 Gordon & Gotch Ltd. (Overseas)
 PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

SUPER SEMICONDUCTOR SELECTION

SOCKETS

1611	8 pin DIL	£0.13
1612	14 pin DIL	£0.14
1613	16 pin DIL	£0.15
1614	24 pin DIL	£0.40
1615	28 pin DIL	£0.45
1616	TO-18 Transistor	£0.12
1617	TO-3 Transistor	£0.35
16117	TO-5 Transistor	£0.12

VOLTAGE REGULATORS

Positive		
MVR7805	µA7805 TO220	£1.00
MVR7812	µA7812 TO220	£1.00
MVR7815	µA7815 TO220	£1.00
MVR7818	µA7818 TO220	£1.00
MVR7824	µA7824 TO220	£1.00
Negative		
MVR7905	µA7905 TO220	£1.40
MVR7912	µA7912 TO220	£1.40
MVR7915	µA7915 TO220	£1.40
MVR7918	µA7918 TO220	£1.40
MVR7924	µA7924 TO220	£1.40
5sp		
µA723C	T099	£1.50
12723	14 pin DM	£1.50
LM309K	T03	£1.50

ZENER DIODES

400mw (Bv_Z) DO7 Glass encapsulated range of voltages available. 1.3v 2.2v 2.7v 3.3v 3.9v 4.3v 4.7v 5.1v 5.6v 6.2v 6.8v 7.5v 8.2v 9.1v 10v 11v 12v 13v 15v 16v 18v 20v 22v 24v 27v 30v 33v 39v

No. Z4 2p ea.

1w-1.5w Plastic and metal encapsulated. Range of voltages available. 1.3v 2.2v 2.7v 3.3v 3.9v 4.3v 4.7v 5.1v 5.6v 6.2v 6.8v 7.5v 8.2v 9.1v 10v 11v 12v 13v 15v 16v 18v 20v 22v 24v 27v 30v 33v 39v 43v 47v 51v 68v 72v 75v 82v 91v 100v.

No. Z13 15p ea.

10w Metal stud type SO10 case. Range of voltages available. 1.3v 2.2v 2.7v 3.3v 3.9v 4.3v 4.7v 5.1v 5.6v 6.2v 6.8v 7.5v 8.2v 9.1v 10v 11v 12v 13v 15v 16v 18v 20v 22v 24v 27v 30v 33v 39v 43v 47v 51v 68v 72v 75v 82v 91v 100v.

No. Z10 35p ea.

SILICON RECTIFIERS


200mA		
IS920	50v	£0.06
IS921	100v	£0.07
IS922	150v	£0.08
IS923	200v	£0.09
IS924	300v	£0.10
1 Amp		
IN4001	50v	£0.04
IN4002	100v	£0.05
IN4003	200v	£0.06
IN4004	400v	£0.07
IN4005	600v	£0.08
IN4006	800v	£0.09
IN4007	1000v	£0.10
1.5 Amp		
IS015	50v	£0.09
IS020	100v	£0.10
IS021	200v	£0.11
IS023	400v	£0.13
IS025	600v	£0.14
IS027	800v	£0.16
IS029	1000v	£0.20
IS031	1200v	£0.25
3 Amp		
IN5400	50v	£0.14
IN5401	100v	£0.15
IN5402	200v	£0.16
IN5404	400v	£0.17
IN5406	600v	£0.21
IN5407	800v	£0.25
IN5408	1000v	£0.30
10 Amp		
IS10	50 50v	£0.19
IS10/100	200v	£0.21
IS10/200	200v	£0.23
IS10/400	400v	£0.35
IS10/600	600v	£0.42
IS10/800	800v	£0.51
IS10/1000	1000v	£0.60
IS10/1200	1200v	£0.69
30 Amp		
IS30/50	50v	£0.56
IS30/100	100v	£0.69
IS30/200	200v	£0.93
IS30/400	400v	£1.25
IS30/600	600v	£1.76
IS30/800	800v	£1.94
IS30/1000	1000v	£2.31
IS30/1200	1200v	£2.88
60 Amp		
IS70/80	50v	£0.75
IS70/100	100v	£0.84
IS70/200	200v	£1.20
IS70/400	400v	£1.75
IS70/600	600v	£2.25
IS70/800	800v	£2.50
IS70/1000	1000v	£3.00
IS70/1200	1200v	£3.50
IS70/1500	1500v	£4.50
IS70/1800	1800v	£5.50
IS70/2100	2100v	£6.50
IS70/2400	2400v	£7.50
IS70/2700	2700v	£8.50
IS70/3000	3000v	£9.50
IS70/3300	3300v	£10.50
IS70/3600	3600v	£11.50
IS70/3900	3900v	£12.50
IS70/4200	4200v	£13.50
IS70/4500	4500v	£14.50
IS70/4800	4800v	£15.50
IS70/5100	5100v	£16.50
IS70/5400	5400v	£17.50
IS70/5700	5700v	£18.50
IS70/6000	6000v	£19.50
IS70/6300	6300v	£20.50
IS70/6600	6600v	£21.50
IS70/6900	6900v	£22.50
IS70/7200	7200v	£23.50
IS70/7500	7500v	£24.50
IS70/7800	7800v	£25.50
IS70/8100	8100v	£26.50
IS70/8400	8400v	£27.50
IS70/8700	8700v	£28.50
IS70/9000	9000v	£29.50
IS70/9300	9300v	£30.50
IS70/9600	9600v	£31.50
IS70/9900	9900v	£32.50
IS70/10200	10200v	£33.50
IS70/10500	10500v	£34.50
IS70/10800	10800v	£35.50
IS70/11100	11100v	£36.50
IS70/11400	11400v	£37.50
IS70/11700	11700v	£38.50
IS70/12000	12000v	£39.50
IS70/12300	12300v	£40.50
IS70/12600	12600v	£41.50
IS70/12900	12900v	£42.50
IS70/13200	13200v	£43.50
IS70/13500	13500v	£44.50
IS70/13800	13800v	£45.50
IS70/14100	14100v	£46.50
IS70/14400	14400v	£47.50
IS70/14700	14700v	£48.50
IS70/15000	15000v	£49.50
IS70/15300	15300v	£50.50
IS70/15600	15600v	£51.50
IS70/15900	15900v	£52.50
IS70/16200	16200v	£53.50
IS70/16500	16500v	£54.50
IS70/16800	16800v	£55.50
IS70/17100	17100v	£56.50
IS70/17400	17400v	£57.50
IS70/17700	17700v	£58.50
IS70/18000	18000v	£59.50
IS70/18300	18300v	£60.50
IS70/18600	18600v	£61.50
IS70/18900	18900v	£62.50
IS70/19200	19200v	£63.50
IS70/19500	19500v	£64.50
IS70/19800	19800v	£65.50
IS70/20100	20100v	£66.50
IS70/20400	20400v	£67.50
IS70/20700	20700v	£68.50
IS70/21000	21000v	£69.50
IS70/21300	21300v	£70.50
IS70/21600	21600v	£71.50
IS70/21900	21900v	£72.50
IS70/22200	22200v	£73.50
IS70/22500	22500v	£74.50
IS70/22800	22800v	£75.50
IS70/23100	23100v	£76.50
IS70/23400	23400v	£77.50
IS70/23700	23700v	£78.50
IS70/24000	24000v	£79.50
IS70/24300	24300v	£80.50
IS70/24600	24600v	£81.50
IS70/24900	24900v	£82.50
IS70/25200	25200v	£83.50
IS70/25500	25500v	£84.50
IS70/25800	25800v	£85.50
IS70/26100	26100v	£86.50
IS70/26400	26400v	£87.50
IS70/26700	26700v	£88.50
IS70/27000	27000v	£89.50
IS70/27300	27300v	£90.50
IS70/27600	27600v	£91.50
IS70/27900	27900v	£92.50
IS70/28200	28200v	£93.50
IS70/28500	28500v	£94.50
IS70/28800	28800v	£95.50
IS70/29100	29100v	£96.50
IS70/29400	29400v	£97.50
IS70/29700	29700v	£98.50
IS70/30000	30000v	£99.50
IS70/30300	30300v	£100.50
IS70/30600	30600v	£101.50
IS70/30900	30900v	£102.50
IS70/31200	31200v	£103.50
IS70/31500	31500v	£104.50
IS70/31800	31800v	£105.50
IS70/32100	32100v	£106.50
IS70/32400	32400v	£107.50
IS70/32700	32700v	£108.50
IS70/33000	33000v	£109.50
IS70/33300	33300v	£110.50
IS70/33600	33600v	£111.50
IS70/33900	33900v	£112.50
IS70/34200	34200v	£113.50
IS70/34500	34500v	£114.50
IS70/34800	34800v	£115.50
IS70/35100	35100v	£116.50
IS70/35400	35400v	£117.50
IS70/35700	35700v	£118.50
IS70/36000	36000v	£119.50
IS70/36300	36300v	£120.50
IS70/36600	36600v	£121.50
IS70/36900	36900v	£122.50
IS70/37200	37200v	£123.50
IS70/37500	37500v	£124.50
IS70/37800	37800v	£125.50
IS70/38100	38100v	£126.50
IS70/38400	38400v	£127.50
IS70/38700	38700v	£128.50
IS70/39000	39000v	£129.50
IS70/39300	39300v	£130.50
IS70/39600	39600v	£131.50
IS70/39900	39900v	£132.50
IS70/40200	40200v	£133.50
IS70/40500	40500v	£134.50
IS70/40800	40800v	£135.50
IS70/41100	41100v	£136.50
IS70/41400	41400v	£137.50
IS70/41700	41700v	£138.50
IS70/42000	42000v	£139.50
IS70/42300	42300v	£140.50
IS70/42600	42600v	£141.50
IS70/42900	42900v	£142.50
IS70/43200	43200v	£143.50
IS70/43500	43500v	£144.50
IS70/43800	43800v	£145.50
IS70/44100	44100v	£146.50
IS70/44400	44400v	£147.50
IS70/44700	44700v	£148.50
IS70/45000	45000v	£149.50
IS70/45300	45300v	£150.50
IS70/45600	45600v	£151.50
IS70/45900	45900v	£152.50
IS70/46200	46200v	£153.50
IS70/46500	46500v	£154.50
IS70/46800	46800v	£155.50
IS70/47100	47100v	£156.50
IS70/47400	47400v	£157.50
IS70/47700	47700v	£158.50
IS70/48000	48000v	£159.50
IS70/48300	48300v	£160.50
IS70/48600	48600v	£161.50
IS70/48900	48900v	£162.50
IS70/49200	49200v	£163.50
IS70/49500	49500v	£164.50
IS70/49800	49800v	£165.50
IS70/50100	50100v	£166.50
IS70/50400	50400v	£167.50
IS70/50700	50700v	£168.50
IS70/51000	51000v	£169.50
IS70/51300	51300v	£170.50
IS70/51600	51600v	£171.50
IS70/51900	51900v	£172.50
IS70/52200	52200v	£173.50
IS70/52500	52500v	£174.50
IS70/52800	52800v	£175.50
IS70/53100	53100v	£176.50
IS70/53400	53400v	£177.50
IS70/53700	53700v	£178.50
IS70/54000	54000v	£179.50
IS70/54300	54300v	£180.50
IS70/54600	54600v	£181.50
IS70/54900	54900v	£182.50
IS70/55200	55200v	£183.50
IS70/55500	55500v	£184.50
IS70/55800	55800v	£185.50
IS70/56100	56100v	£186.50
IS70/56400	56400v	£187.50
IS70/56700	56700v	£188.50
IS70/57000	57000v	£189.50
IS70/57300	57300v	£190.50
IS70/57600	57600v	£191.50
IS70/57900	57900v	£192.50
IS70/58200	58200v	£193.50
IS70/58500	58500v	£194.50
IS70/58800	58800v	£195.50
IS70/59100	59100v	£196.50
IS70/59400	59400v	£197.50
IS70/59700	59700v	£198.50
IS70/60000	60000v	£199.50
IS70/60300	60300v	£200.50
IS70/60600	60600v	£201.50
IS70/60900	60900v	£202.50
IS70/61200	61200v	£203.50
IS70/61500	61500v	£204.50
IS70/61800	61800v	£205.50
IS70/62100	62100v	£206.50
IS70/62400	62400v	£207.50
IS70/62700	62700v	£208.50
IS70/63000	63000v	£209.50
IS70/63300	63300v	£210.50
IS70/63600	63600v	£211.50
IS70/63900	63900v	£212.50
IS70/64200	64200v	£213.50
IS70/64500	64500v	£214.50
IS70/64800	64800v	£215.50</

High quality audio modules for Stereo and Mono

S450

**STEREO
FM TUNER**
Fitted with
phase lock-loop

£22.30
+ 40p p&p
+ 12½% VAT

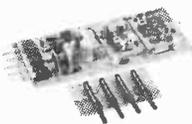

The S450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose. Simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning Switched AFC LED Stereo Indicator.

FREQUENCY RANGE	88 — 108 Mhz
SENSITIVITY	3.0µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

MPA30 MAGNETIC CARTRIDGE PRE-AMPLIFIER



£2.95
25p p&p
+ 12½% VAT

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality preamplifier/enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—re earth
DIMENSIONS	110x50x25mm (inc DIN socket)

Stereo 30

**COMPLETE
AUDIO
CHASSIS**

£18.95
+ 40p p&p
+ 12½% VAT



7 + 7w R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck, etc. Simple to install, capable of producing really first-class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than 5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dBs
tone CONTROL RANGE	± 12dBs at 100 Hz and 10 kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V.A.C. rated at 1A
DIMENSIONS (Less controls and PARTS)	200mm x 130mm x 33mm

PA12

**STEREO
PRE-AMPLIFIER**



£7.10
30p p&p
+ 12½% VAT

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features included on/off volume, Balance, Bass and Treble controls. Complete with tape output.

FREQUENCY RESPONSE	20 Hz — 20 kHz (—3dB)
BASS CONTROL	± 12 dB at 60 Mhz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	— 60 dB
SIGNAL/NOISE RATIO	— 65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 35mm

AL60

**AUDIO
AMPLIFIER
MODULE**
25 Watts RMS

£4.55 + 25p p&p
+ 12½% VAT



25w
R.M.S.

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than 1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz × 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

AL80

**AUDIO
AMPLIFIER
MODULE**

£7.15 + 25p p&p
+ 8% VAT



35w
R.M.S.

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

OUTPUT POWER	35 Watts RMS
SUPPLY	40—60 V
LOAD IMPEDANCE	8—16 ohms
TOTAL HARMONIC DISTORTION	Less than 1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

PS12 POWER SUPPLY

Designed for use with the AL30A S 450 and MPA30 in conjunction with transformer T538.

INPUT VOLTAGE 17-20v AC
OUTPUT VOLTAGE 27-30v DC
OUTPUT CURRENT 800mA
Size 60mm x 43mm x 26mm

£1.30
+ 12½% VAT
25p p&p

AL250

**POWER
AMPLIFIER**

£17.25 + 40p p&p
+ 8% VAT



125w
R.M.S.

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50—80V
LOADS	4—16 ohms
FREQUENCY RESPONSE	25 Hz — 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS	450mV
O/P AT 1 kHz	33K ohms
INPUT IMPEDANCE	
TOTAL HARMONIC DISTORTION	into 4 ohms 0.1%
50 WATTS	into 8 ohms 0.06%

GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ± 12dB. Max. Voltage handling 2 V RMS, T.H.D. 0.05%, input Impedance 100 K. Output impedance less than 10 K. Frequency response 20 Hz-20 KH (3dB). The nine gain controls are centred at 50, 100, 200, 400, 800, 1,600, 3,200, 6,400 and 12,800 Hz. The suggested + 12½% VAT gain controls are 10 K LIN sliders (not supplied with the module) See Paks S31 and 16192.

£22
+ 12½% VAT
p&p 25p

SG30 POWER SUPPLY BOARD FOR GE100 15-0-15 VOLT
£5.50 + 12½% VAT. p&p 25p

Siren Alarm Module

American Police sreamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. Order No. S15. **Only £3.50**

+ 8% VAT p&p 25p

AL30A

**AUDIO
AMPLIFIER
MODULES**

£3.75
+ 25p p&p
12½% VAT



10w
R.M.S.

These low cost 5 and 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

MAXIMUM SUPPLY VOLTAGE	30V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8 — 16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

SPM80

**STABILISED
POWER SUPPLY**

£4.25 + 25p p&p
+ 12½% VAT



Designed to power two AL60's at 15 Watts per channel simultaneously. Circuit Techniques include full short protection.

INPUT A.C. VOLTAGE	33—40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA—1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm.

PA100

**STEREO
PRE-AMPLIFIER**



£15.80
+ 40p p&p
+ 12½% VAT

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution for the front end requirements of stereo amplifiers or audio units. The six push-button selector switch gives a choice of inputs together with two filters for high and low frequencies.

FREQUENCY RESPONSE	20Hz to 20 kHz x 1dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY 1. TAPE	100 mV/100 K ohms) For an
INPUTS	1. RADIO TUNER
3. MAGNETIC P.U.	100 mV/100K ohms) output
EQUALISATION	3.5 mV/50 K ohms) 250mV
	Within ± 1 dB from
	20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10—20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300x90x33mm (less controls)

TRANSFORMERS

T538 For use with S.450 AL30A MPA30
Order No. 2036 Price **£3.20** + 55p p&p + 12½% VAT
T2050 For use with Stereo 30
Order No. 2050 Price **£3.25** + 55p p&p + 12½% VAT
BMT80 For use with AL60 SPM80
Order No. 2034 Price **£5.40** + 86p p&p + 12½% VAT
BMT250 For use with AL250
Order No. 2035 Price **£6.35** + £1.10 p&p + 12½% VAT

BI-PAK

DEPT. ET18, P.O. Box 6, Ware
Herts.

OSTS [®] new from ambit international


One Stop Technology Shopping starts here :

TTL Standard AND LP Schottky

	'N'	'LSN'		'N'	'LSN'		'N'	'LSN'		'N'	'LSN'
7400	13p	22p	7455	35p	36p	74136		59p	74194	105p	187p
7401	13p	26p	7460	17p		74138		160p	74195	95p	137p
7402	14p	26p	7470	28p		74139		160p	74196	99p	
7403	14p	26p	7472	28p		74141		56p	74197	85p	153p
7404	14p	29p	7473	32p		74142		265p	74198	150p	
7405	18p	29p	7474	27p	56p	74143		312p	74199	160p	
7406	38p		7475	38p		74144		312p	74251		153p
7407	38p		7476	37p		74145		65p	74253		153p
7408	17p	29p	7480	48p		74147		175p	74257		153p
7409	17p	29p	7481	86p		74148		109p	74258		153p
7410	15p	26p	7482	69p		74150		99p	74259		420p
7411	20p	29p	7484	97p		74151		64p	74260		26p
7412	17p		7485	104p	141p	74153		64p	74266		59p
7413	30p		7486	31p	59p	74154		96p	74279		73p
7414	51p		7489	205p		74155		54p	74290		134p
7416	30p		7490	33p	99p	74156		80p	74293		134p
7417	30p		7491	76p		74157		67p	74295		196p
7420	16p	26p	7492	38p	99p	74158		82p	74298		176p
7421	29p	26p	7493	32p	99p	74159		210p	74365		72p
7422	24p	26p	7494	78p		74160		82p	74366		72p
7423	27p		7495	65p	119p	74161		92p	74367		72p
7425	27p		7496	58p		74162		92p	74368		72p
7426	36p		7497	185p		74162		92p	74670		421p
7427	27p	29p	74100	119p		74163		92p			
7428	35p		74104	63p		74164		104p			
7430	17p	26p	74105	62p		74165		105p			
7432	25p	26p	74107	32p		74167		20p			
7433	40p		74109	63p	56p	74170		230p			
7437	40p	42p	74110	54p		74172		625p			
7438	33p	42p	74111	68p		74173		170p			
7440	17p	29p	74112	88p	56p	74174		87p	137p		
7441	74p		74116	198p		74175		87p	127p		
7442	70p	114p	74118	83p		74176		75p			
7443	115p		74119	119p		74177		78p			
7444	112p		74120	115p		74180		85p			
7445	94p		74121	25p		74181		165p	491p		
7446	94p		74122	46p		74182		160p			
7447	82p		74123	48p		74184		135p			
7448	56p		74125	38p	64p	74185		134p			
7450	17p		74126	57p	64p	74188		275p			
7451	17p	26p	74128	74p		74190		115p	229p		
7453	17p		74132	73p	136p	74192		105p	229p		
7454	17p	36p	74133		29p	74193		105p	229p		

Return of post service whenever humanly possible - and sometimes even when it isn't! All our goods are manufacturers' first quality, so you may build in complete confidence, backed with our own investment in lab facilities, for the complete Tecknowledgey service.

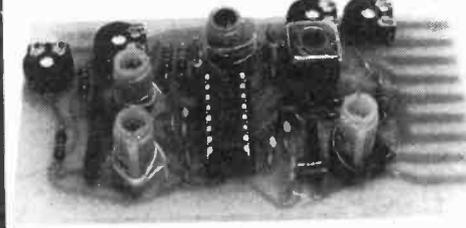From the World's leading radio innovation source:



The EF5400, the first VHF tunerhead with one IC. It includes PIN diode agc loop, balanced osc/mixer, RF stage. Tunes 88-108 with only 2-Bv DC bias, and is adaptable up to 230MHz. £9.75 built/tested. Special frequency ranges on applic.

The Reference series of FM tuner modules

- 7130 2 or 3 pole linear phase IF filters, The CA3189E IC, two agc'd MOSFET IF preamps and all features. 0.07% thd 30% mod. Now the leading IF module available. Built and aligned. £16.25
- 91196B The HA1196 stereo decoder in an optimum application, with two LM380N monitor 2W PA stages built in. £16.45
- EF5803 The Latest EF series from Ambit. 3 MOSFET circuit, with extra loose inter-stage coupling and amplified LO op. £19.75
- EF5801 The original 6 varicap(doublet) FM tunerhead with LO op. £17.45
- EF5600 TOKO's 5 cct varicap FM tunerhead. MOS input stage. £14.95
- EC3302 TOKO's budget 3 cct FM varicap tunerhead. JFET RF. £8.25
- 7252 Larsholt's MOS frontend/CA3089E IF system HiFi complete varicap tunerhead for 88-108. Mute, AFC, AGC etc. £26.50
- 7253 Larsholt's FET frontend/CA3089E/MC1310 stereo tunerhead with varicap tuning. Like 7252, signal level/tuning meter drives. £26.50

Linear ICs for audio and radio applications - Old ones, new ones etc.

- CA3089E / KB4402 classic FM IF system. Includes mute, afc, agc, metering. £1.94
- HA1137W/KB4420A as CA3089E, with improved deviation muting and S/N. £2.20
- CA3189E Update, though not replacement for 3089. inc af gain. £2.75
- TBA120A/SN76660N Limiting DC coupled IF amp plus balanced detector. £0.75
- TBA120S Hi gain version of TBA120A. £1.00
- uA7200C/CA3123E AM radio IC, useful gain controlled RF/IF gain block. £1.40
- TBA651 low voltage, hi gain AM radio cum linear RF/IF gain. £1.81
- HA1197 Complete HiFi am radio inc detector wide agc range. £1.40
- MC1350 AGC wideband IF amplifier block for AM/FM/SSB. £1.20
- MC1330 Synchronous AM/video detector. £1.35
- LM1496/SG1496 Classic double balanced mixer for DC to 300MHz. £1.25
- LM374N National's multimode communications IF/detector. £3.45*
- MC1495 Precision four quadrant multiplier system. £6.86*
- TDA1062NEW Complete DC to 200MHz front end system. £1.95
- TDA1083NEW Complete DC to 30MHz AM/FM +80mW AF radio ic. £1.95
- TDA1090NEW Complete AM radio to 30MHz, with built in 3089 type FM IF and function system for HiFi. £3.35
- KB4406 NEW Differential AM/FM IF gain. £0.50
- KB4412 NEW 2 balanced mixers, agc 55dB gain IF amp cooms device. £2.55
- KB4413 NEW Comp to KB4412, AM, FM, SSB detector, ANL, mute AGC driver, meter driver. Complex function comms ic. £2.75
- KB4417 NEW 3mV niike preamp, limiter, vogad for comms. £2.55
- SD6000 Dual DMOS RF/Mixer mosfet pair. £3.75

Transistors for RF: The latest UHF T pack types eg. 1.8GHz PNP only 0.86p. 2N4427* £1.30, BF900 latest generation MOS 0.80* As usual, you get the latest information and ideas from AMBIT.

DAZZLING OPTO BARGAINS
LED size 2.5x5mm 5mm clip
red 17p 14p 2p
green 20p 15p 2p
yellow 20p 16p 2p
(clip for 5mm types only) All first grade

PUSH BUTTON SWITCH SYSTEMS
Easy assembly, professional quality PB type with range of buttons. Shadow compatible ALPs SUB series, and the very flexible new dialistat from Lipra & Isostat. Low cost eg 4 module 6pole, 15mm = £1.74 in SUB
TOKO COILS, FILTERS, PVCs, ICs
Space has run out here, but all in the catalogue. The biggest range in Europe

Linear non radio/audio

BIMOS		NE531T		120p	
CA3130E	84p	NE531N	105p		
CA3130T	90p	NE550A	73p		
CA3140E	35p				
CA3140T	72p				
CA3160E	90p				
CA3160T	99p				
Misc functions					
		NE555	35p		
		NE556	70p		
		LM3909N	72p		
MPU - 6800					
		MC6800P	£13		
		MC6820P	£6		
		MC6850P	£75p		
		MC6810AP	£40p		
		MC6850P	£8		
		MC6852	£15		
MEMORIES					
		2102-1	170p		
		2112	340p		
		2513	754p		
		4027	578p		
		2114	£10		
		2708	1055p		
8080 - CPUs					
		8080ACE	£16		
		Full range of support kits DA for 8080/6800			

CD4000 CMOS

All prime, all guaranteed

4000	17p	4059	563p	4501	99p
4001	17p	4060	115p	4502	120p
4002	17p	4063	109p	4503	69p
4006	109p	4066	53p	4506	51p
4007	18p	4067	400p	4507	55p
4008	80p	4068	25p	4508	248p
4009	58p	4069	20p	4510	99p
4010	58p	4070	20p	4511	149p
4011	17p	4071	20p	4512	98p
4012	17p	4072	20p	4513	206p
4013	55p	4073	20p	4514	260p
4016	52p	4075	20p	4515	300p
4017	80p	4076	90p	4516	125p
4018	80p	4077	20p	4517	382p
4019	60p	4078	20p	4518	103p
4020	93p	4081	20p	4519	57p
4021	82p	4082	20p	4520	109p
4022	90p	4085	82p	4521	236p
4023	17p	4086	82p	4522	149p
4024	76p	4089	150p	4527	157p
4025	17p	4093	50p	4528	102p
4026	180p	4094	190p	4529	141p
4027	55p	4096	105p	4530	90p
4028	72p	4097	372p	4531	141p
4029	100p	4098	110p	4532	125p
4030	58p	4099	122p	4534	614p
4031	250p	4160	90p	4536	380p
4032	100p	4161	90p	4538	150p
4033	145p	4162	90p	4539	110p
4034	200p	4163	90p	4541	141p
4035	120p	4174	104p	4543	174p
4036	250p	4175	95p	4549	399p
4037	100p	4194	95p	4553	440p
4038	105p	4501	23p	4554	153p
4039	250p	4502	91p	4556	77p
4040	83p	4503	76p	4557	386p
4041	90p	4507	60p	4558	117p
4042	85p	4510	128p	4559	388p
4043	85p	4511	163p	4560	218p
4044	80p	4512	116p	4561	65p
4045	150p	4514	325p	4562	530p
4046	130p	4515	325p	4566	159p
4047	99p	4516	128p	4568	281p
4048	60p	4517	403p	4569	303p
4049	55p	4518	119p	4572	25p
4050	55p	4519	58p	4580	600p
4051	65p	4520	120p	4581	319p
4052	65p	4528	122p	4582	164p
4053	65p	4553	440p	4583	84p
4054	120p			4584	63p
4055	135p			4585	100p

PC DRAFTING AIDS:

You may now also obtain all Chartpak PC drafting aids from AMBIT. Price as list, details on request. Also details of our low cost fast prototyping service for PCB - log graph paper, Smith diagrams etc.

ABRIDGED INFORMATION:

Postcode CM14 4HN. Tel. 216029. VAT extra at 12.5% except *-8% Catalogue 45p inc. Postage 25p. Admin open Mon-Fri 8am-5pm, Sales/technical 9am-8pm inc Sat.

2 Gresham Road, Brentwood, Essex.

& finishes here.

news digest.

light to sound units

Phillips have demonstrated a new digital sound system, incorporating a solid-state laser mounted in a semi-conventional pickup arm. The system uses a 110mm disc with a playing time of one hour per side, the audio is digitally encoded to provide very high fi. Phillips have christened the system 'Compact Disk', and hope to have it ready for the consumer market in the early 1980s. RCA have also been experimenting with a similar, but

incompatible, system as an offshoot of their video disc developments.

A bit nearer to the present is the Sony digital recording system. This is an add on to their U-matic or Betamax video recorders, which encodes the audio as a signal on the videotape. Quality is said to be orders of magnitude better than conventional recording systems. Price is expected to be around the £700 range available from late summer.

strike detector

An ultra-simple method of determining the force in lightning strikes has been developed at NASA. All it consists of is a 4 foot length of magnetic tape inside a plastic tube! An 9kHz tone is prerecorded on the tape, and the tube mounted perpendicular to an exposed conductor — such as a guy wire. When lightning strikes a magnetic field is produced, which erases

part of the signal. The amount of erasure is proportional to the field strength and hence the current in the lightning strike. To find out how strong the strike was, or indeed if there has been any strike, you simply play the tape. Current as high as 17 000 Amps has been measured on a single guy wire with the device. Why is it that all the best ideas are so simple?

mars bars and chips

Mars Money Systems (relation) are starting to take delivery of a new device from AMI Microsystems. The fiendishly clever hunk of silicon is a dedicated one bit (bite?) MPU with onboard PROM, it is to be used in vending machines for coin acceptance and change giving. It not only counts how much you feed into the machine, it also works out the correct change and gives you it (if there is not enough money in the change chute it returns all your money).

Coin sensing is done with 3 coil like inductors, embedded in the wall of the coin path, frequency shifts are produced as the coins roll past—and the IC compares them with reference data stored in the PROM. The one bit brain can check far more precisely than any mechanical system, and the PROM can be pre-peed for any currency in use in a particular country. AMI Microsystems, 3800 Homestead Road, Santa Clara, CA 95051, US of A.

alas, poor capek

It seems that we made an omission in the recent Robot issue, as the following from Mr D. B. Pitt points out . . . In analysing the word 'Robot' we forgot to mention Capek, equivalent to analysing the word 'chortle' without Lewis Carroll.


Robot represents the first two syllables of the Czech word for worker, and, allowing for slight vowel shifts, the rule applies to all the other Slavonic languages.

The word officially entered the English language in April 1923 with the first presentation of the play R.U.R. (Rossom's

Universal Robots) by Karel Capek, the famous Czech playwright, at the St. Martin's Theatre, London. The translator, Mr P. Selver, wisely left the word robot unchanged from the original Czech.

In practice, the word was already current in certain circles before that date, as the fame of Capek's political satire had preceded it, thanks to the popular press, which was quick to seize on the sensational aspects of the play's theme, a world taken over by a revolt of man-made factory workers.

boris challenges challenger

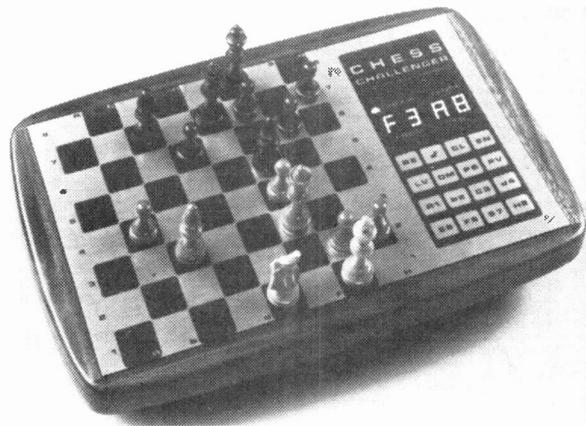

Up until recently the computer chess field was dominated by the manufacturers of the Chess Challenger — Fidelity Electronics of Chicago. After the tremendous success of the original model came the improved 3 level version, now they have introduced a 10 level version with lots of new features. The response time varies from 5 seconds on the beginners level, to a 24 hour response (suggested only for postal games!), because you may not notice when the computer makes a move it makes a couple of beeps when it has.

Now another company has entered the chess arena, with a machine called Boris, and they claim that Boris is the King of

the computer chess world. Manufactured by a company called Chafitz in Rockville, Boris can even play with itself (and not go blind!). Other nice features include an 8 digit alpha-numeric display and completely variable response time, the alpha capability is used to display pieces as pictures (illegal move, good move, etc) — the response time can be set from 1 second up to 99 hours, so you can program it/him to very specific skill levels.

Price of the Challenger 10 is expected to be in the region of £200; Boris will probably be about the same. Neither machine is expected to be available in the U.K. until 1979.



WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
 MAIL ORDER CALLERS WELCOME.
 Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P add 30p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12 1/2%.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in µF)
 400V: 0.001, 0.0015, 0.0022, 0.0033 7p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 10p; 0.047, 0.068 14p; 0.1 15p; 0.15, 0.2, 0.22, 0.22p; 0.33, 0.47 39p; 0.68 45p.
 100V: 0.039, 0.15, 0.22 11p; 0.33, 0.47 19p; 0.68, 1.0 22p; 2.2 32p; 4.7 39p.
 50V: 0.01, 0.015, 0.022, 0.033 7p; 0.047, 0.068, 0.1 11p; 0.15, 0.2 11p; 0.22, 0.33 13p; 0.47 15p; 0.68 18p; 1.0 24p; 1.5 27p; 2.2 31p.

POLYESTER RADIAL LEAD (Values in µF): 250V:
 0.01, 0.015, 0.022, 0.027 5p; 0.033, 0.047, 0.068, 0.1 7p; 0.15 11p; 0.22, 0.33 13p; 0.47 15p; 0.68 18p; 1.0 24p; 1.5 27p; 2.2 31p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF)
 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22, 33, 47, 32, 50, 11p; 63, 100, 27p; 50V: 100, 7p; 50, 10p; 20, 25p; 47, 50p; 100, 22p; 200, 33p; 400, 47p; 2.2, 3.3, 7p; 100, 11p; 330, 62p; 470, 64p; 35V: 10, 33, 7p; 33, 47, 32p; 100, 49p; 250, 10, 22, 47, 6p; 80, 10, 16p; 80, 20, 25p; 130, 6p; 40, 25p; 100, 27p; 150, 30p; 200, 34p; 330, 52p; 470, 64p; 16V: 10, 40, 47, 6p; 7p; 100, 12p; 8p; 47, 16p; 100, 15p; 200, 22p; 330, 34p; 10V: 4, 10, 6p; 64, 10p; 100, 14p.

TANTALUM BEAD CAPACITORS:
 35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2µF, 3.3, 4.7, 6.8, 25µF, 1.5, 10, 20V: 1.5, 15µF, 10µF, 1µF each, 2.2 25p, 4.7µF, 100 40p.

Mylar Film Capacitors:
 100V: 0.001, 0.002, 0.005, 0.01µF 5p
 0.015, 0.02, 0.04, 0.05, 0.05µF 7p
 0.1µF, 0.15, 0.2 9p, 50V: 0.47µF 11p

CERAMIC CAPACITORS 50V:
 Range: 0.5pF to 10,000pF 3p
 0.015µF, 0.022µF, 0.033µF 4p
 0.047µF 4p, 0.1µF 6p.

SILVER MICR (Values in pF): 3.3, 4.7, 6.8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220, 9p each
 250, 300, 330, 360, 390, 8p each
 600, 820, 16p each
 1000, 1800, 2000, 2200, 20p each

POLYSTYRENE CAPACITORS:
 10pF to 1nF 8p, 1.5nF to 47nF 10p

CERAMIC TRIMMER CAPACITORS:
 2-7pF, 4.15pF, 6.25pF, 8-30pF 20p

MINIATURE TYPE TRIMMERS:
 2.5-6pF, 3.10pF, 10-40pF 22p
 5-25pF, 5-45pF, 60pF, 88pF 30p

COMPRESSION TRIMMERS:
 3-40pF, 10-80pF, 25-190pF 25p
 100-500pF, 1250pF 45p

JACKSONS VARIABLE CAPACITORS:
 Dielectric 0.2 365pF with slow
 100p/300pF 105p motion Drive 325p
 500pF 125p 00 208/176 285p

DENCO COILS:
 DP VALVE TYPE RDT2 92p
 Range 1.5 B.Y.R.W. RFC 5kcheps 91p
 RFC 7 (19mH) 96p
 1FT 13/14/15/16 86p
 6.7 B.Y.R. 75p 11 85p
 1.5 B.Y.R.W. 92p 1FT 18/1 6 or 46p
 B9A Valve Holder TOC1 86p
 MW5FR 82p
 MW/LW 5FR 103p

RF CHOKES:
 1µH 4.7, 10, 22, 33, 47, 100, 200, 470, 750, 1mH 2.5, 5, 10 35p each
 43mH 100 60p each

VEROBARD: D 0.1 0.15 0.15 (copper clad) (platin)
 2 1/2 x 3 1/4 41p 33p 22p
 2 1/2 x 5 49p 45p 28p
 3 1/2 x 3 1/4 49p 45p
 3 1/2 x 5 56p 60p 39p
 2 1/2 x 17 152p 121p 75p
 3 1/2 x 17 195p 163p 107p
 4 1/2 x 17 252p 163p 107p
 Pkt of 35 pins 30p
 Split face cutter 75p
 Pin insertion tool 99p

VERO WIRING PEN: + Spool 325p
 Spare spool (wire) 80p, Combs 10p each

FERRIC CHLORIDE: 1lb bag Anhydrous 65p + 30p p. & p.

DALO ETCH RESIST PEN: + spare tip 75p

COPPER CLAD BOARDS:
 Fibre Single Double SRBP
 Glass sided sided 8 x 10.5
 6 x 8 75p 75p
 8 x 8 75p 75p
 6 x 12 130p 175p

DIL SOCKETS: Low Profile (TEXAS)
 8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 13p; 20 pin 27p; 22 pin 30p; 24 pin 30p; 28 pin 42p; 40 pin 55p; 60 pin 245p.

SOLDERCON PINS: 100 pins 50p; 1000 pins 350p

TRANSISTORS

AC107*	23	BC169C	12	BF167	25	MPSA56	24	TI543	36	2N217	48
AC117*	25	BC169D	12	BF173*	25	MPSA70	34	TI545	45	2N218A*	31
AC125*	19	BC170	17	BF174	25	MPSJ02	58	TI546	45	2N219A*	22
AC126*	19	BC171	11	BF178*	25	MPSJ06	54	TI547	50	2N220A*	26
AC127*	11	BC172	10	BF179*	20	MPSJ50	54	TI548	50	2N221A*	23
AC128*	18	BC177*	15	BF180*	20	MPSJ55	55	TI549	50	2N222A*	20
AC141*	24	BC178*	14	BF181*	20	MPSJ55	53	TI550	50	2N223A*	45
AC141K*	38	BC179*	14	BF182*	30	MPSJ56	56	TI574	47	2N2368	21
AC142*	24	BC182	9	BF183*	30	OC141*	150	TI575	47	2N2369*	15
AC142K*	38	BC183	9	BF184*	30	OC25*	120	TI591	22	2N2483*	28
AC176*	18	BC184	9	BF194	10	OC25*	120	TI591	22	2N2484*	30
AC187*	20	BC182L	10	BF195	10	OC25*	120	ZX107	11	2N2646*	48
AC188*	20	BC183L	10	BF196	10	OC28*	99	ZX108	11	2N2784	55
AC191	40	BC187*	28	BF197	10	OC29*	160	ZX109	28	2N2904*	22
AC198	40	BC186	21	BF198	10	OC34*	20	ZX112	18	2N2905*	27
AC199	40	BC187*	28	BF199	18	OC36*	99	ZX130	13	2N2907*	20
AC200	40	BC212	9	BF200*	32	OC41*	48	ZX131	16	2N2907*	18
AC211	35	BC213	10	BF224A	10	OC42*	32	ZX132	21	2N2907*	22
AC222	40	BC121L	9	BF244	24	OC43*	55	ZX133	21	2N2926G	10
AC238	40	BC213L	10	BF244B	30	OC44*	31	ZX134	24	2N3011*	24
AC239	78	BC214	9	BF257	26	OC46*	26	ZX135	24	2N3053*	20
AC241	39	BC214K	19	BF257*	26	OC46*	26	ZX136	24	2N3054*	49
AC244	39	BC214L	10	BF258*	30	OC70*	19	ZX137	30	2N3055*	55
AD149*	40	BC307B	14	BF259*	37	OC71*	25	ZX138	40	2N3108	39
AD161*	42	BC308	13	BF336	33	OC72*	30	ZX139	20	2N3442*	131
AD162*	42	BC327	15	BF394	22	OC74*	45	ZX140	14	2N3663*	20
AF106*	70	BC328	13	BF394	22	OC75*	45	ZX141	14	2N3614*	169
AF111*	25	BC348	25	BF595	38	OC76*	36	ZX150	19	2N3615*	135
AF115*	25	BC431	30	BF595	38	OC77*	76	ZX150	19	2N3663*	20
AF116*	25	BC461*	30	BF595	38	OC79*	76	ZX150	19	2N3702	10
AF117*	25	BC462*	30	BF595	38	OC81*	28	ZX151	25	2N3703	11
AF118*	45	BC547	11	BF595	38	OC82*	48	ZX152	25	2N3704	10
AF121*	48	BC548	11	BF595	38	OC83*	48	ZX153	25	2N3705	11
AF124*	11	BC549C	13	BF595	38	OC84*	44	ZX154	25	2N3706	10
AF125*	35	BC557	13	BF595	38	OC122*	48	ZX155	25	2N3707	10
AF126*	35	BC558	12	BF595	38	OC123*	48	ZX156	25	2N3708	10
AF127*	35	BC559	20	BF595	38	OC124*	48	ZX157	25	2N3709	10
AF139*	35	BCY30	57	BF595	38	OC125*	48	ZX158	25	2N3710	16
AF178*	70	BCY34*	75	BF595	38	OC126*	48	ZX159	25	2N3711	10
AF179*	70	BCY39*	180	BF595	38	OC127*	48	ZX160	25	2N3712*	170
AF186*	50	BCY40*	75	BF595	38	OC128*	48	ZX161	25	2N3713*	288
AF239*	42	BCY42	48	BF595	38	OC200*	48	ZX162	25	2N3819	22
AFZ11	128	BCY43	75	BF595	38	OC201*	75	ZX163	25	2N3820	32
ASV26*	40	BCY58	22	BF595	38	OC202*	75	ZX164	25	2N3821	22
ASV27*	45	BCY59	22	BF595	38	OC203*	75	ZX165	25	2N3822	60
ASV28*	45	BCY60	22	BF595	38	OC204*	75	ZX166	25	2N3823	95
ASV29*	45	BCY61	22	BF595	38	OC205*	75	ZX167	25	2N3824	95
ASV30*	45	BCY62	22	BF595	38	OC206*	75	ZX168	25	2N3825	95
ASV31*	45	BCY63	22	BF595	38	OC207*	75	ZX169	25	2N3826	95
ASV32*	45	BCY64	22	BF595	38	OC208*	75	ZX170	25	2N3827	95
ASV33*	45	BCY65	22	BF595	38	OC209*	75	ZX171	25	2N3828	95
ASV34*	45	BCY66	22	BF595	38	OC210*	75	ZX172	25	2N3829	95
ASV35*	45	BCY67	22	BF595	38	OC211*	75	ZX173	25	2N3830	95
ASV36*	45	BCY68	22	BF595	38	OC212*	75	ZX174	25	2N3831	95
ASV37*	45	BCY69	22	BF595	38	OC213*	75	ZX175	25	2N3832	95
ASV38*	45	BCY70	22	BF595	38	OC214*	75	ZX176	25	2N3833	95
ASV39*	45	BCY71	22	BF595	38	OC215*	75	ZX177	25	2N3834	95
ASV40*	45	BCY72	22	BF595	38	OC216*	75	ZX178	25	2N3835	95
ASV41*	45	BCY73	22	BF595	38	OC217*	75	ZX179	25	2N3836	95
ASV42*	45	BCY74	22	BF595	38	OC218*	75	ZX180	25	2N3837	95
ASV43*	45	BCY75	22	BF595	38	OC219*	75	ZX181	25	2N3838	95
ASV44*	45	BCY76	22	BF595	38	OC220*	75	ZX182	25	2N3839	95
ASV45*	45	BCY77	22	BF595	38	OC221*	75	ZX183	25	2N3840	95
ASV46*	45	BCY78	22	BF595	38	OC222*	75	ZX184	25	2N3841	95
ASV47*	45	BCY79	22	BF595	38	OC223*	75	ZX185	25	2N3842	95
ASV48*	45	BCY80	22	BF595	38	OC224*	75	ZX186	25	2N3843	95
ASV49*	45	BCY81	22	BF595	38	OC225*	75	ZX187	25	2N3844	95
ASV50*	45	BCY82	22	BF595	38	OC226*	75	ZX188	25	2N3845	95
ASV51*	45	BCY83	22	BF595	38	OC227*	75	ZX189	25	2N3846	95
ASV52*	45	BCY84	22	BF595	38	OC228*	75	ZX190	25	2N3847	95
ASV53*	45	BCY85	22	BF595	38	OC229*	75	ZX191	25	2N3848	95
ASV54*	45	BCY86	22	BF595	38	OC230*	75	ZX192	25	2N3849	95
ASV55*	45	BCY87	22	BF595	38	OC231*	75	ZX193	25	2N3850	95
ASV56*	45	BCY88	22	BF595	38	OC232*	75	ZX194	25	2N3851	95
ASV57*	45	BCY89	22	BF595	38	OC233*	75	ZX195	25	2N3852	95
ASV58*	45	BCY90	22	BF595	38	OC234*	75	ZX196	25	2N3853	95
ASV59*	45	BCY91	22	BF595	38	OC235*	75	ZX197	25	2N3854	95
ASV60*	45	BCY92	22	BF595	38	OC236*					



Introducing DM900 - The DIGITAL MULTIMETER with "Hidden Capacity" - It measures Capacitance too!

(as published in E.T.I. August 1978)
 Away with analogue meters for with some of these you may often as not use a crystal ball to make circuit measurements instead gaze into our crystal - not a ball but the 3 1/2 0.5 LIQUID CRYSTAL DISPLAY - on our amazingly accurate DMM incorporating

- 5 AC & DC Voltage ranges; 6 resistance ranges
- 5 AC & DC Current ranges; 4 Capacitance ranges

The prototype accuracy is better than 1%

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by only one PP3 battery. There is also a battery check facility.

The DM900 is an attractive hand-held, light weight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.

Never before have all these features been offered to the electronics enthusiast in a single unit.

Special introductory price **£49.95*** (p&p insured 80p) (probes optional extra). (Demonstration on at our shop)

(additional carrying case £1.50*)

TANK BATTLE

Build this fantastic T.V. Game with realistic battle sounds generated from your T.V. speaker, steerable tanks, controllable shell trajectory and minefields to avoid. A really exciting and skillful game simply constructed with our easy to follow instructions. Order now - avoid disappointments.

Basic Kit (just add controls) only **£19.50** inc. VAT (p&p 45p insured).

Complete Kit including controls & Mains Power Supply. No extras required. Only **£26.25** inc. VAT (p&p 45p insured).

IC AY-3-8710 **£10.50** inc. VAT.


(Demonstration on at our shop)

JACK PLUGS	SOCKETS			SWITCHES*	SLIDE 250V:
Screened chrome	Plastic body	open metal	moulded with break	TOGGLE 2A, 250V	1A DPDT 14p
2.5mm 12p	8p	8p	11p	SPST 28p	1A DPDT c/over 15p
3.5mm 15p	10p	8p	12p	DPST 34p	1/2A DPDT 13p
MONO 23p	15p	13p	18p	DPDT 38p	4 pole 2-way 24p
STEREO 31p	18p	15p	22p	4 pole on/off 54p	PUSH BUTTON
					Spring loaded
					SPST on/off 59p
					SPST biased 55p
					DPDT 6 tags 70p
					DPDT centre off 79p
					DPDT Biased 115p
DIN	PLUGS	SOCKETS	In Line	SUB-MIN TOGGLE	SPRING LOADED
2 PIN Loudspeaker 3, 4, 5 Audio	13p	8p	20p	SP changeover 59p	SPST c/over 60p
				SPST on/off 54p	DPDT 6 Tag 85p
				SPST biased 55p	MINIATURE
				DPDT 6 tags 70p	Non Locking
				DPDT centre off 79p	Push to Make 15p
				DPDT Biased 115p	Push Break 25p
CO-AXIAL (TV)	14p	14p	14p	ROTARY	
				Make your own multiway Switch. Adjustable Stop Shunting Assembly. Accommodate up to 6 Wafers 69p	
				Mains Switch DPST to fit 34p	
				Break Before Make Wafers. 1 pole/12 way 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way 47p	
				Spacer and Screen 5p	
PHONO	9p	5p single	15p	ROTARY (Adjustable Stop)	
assorted colours	12p	10p 3-way	—	1 pole/2 to 12 way, 2p/2 to 6 way, 3p/2 to 4 way, 4 pole/2 to 3 way 41p	
Metal screened				ROTARY : Mains 250V AC, 4 Amp 45p	
BANANA	10p	12p	—		
4mm	10p	10p	—		
2mm	8p	8p	—		
1mm					
WANDER	8p	8p	—		
3mm	15p	20p	—		
OC Type	15p	15p	—		
AC 2-pin American					

VOLTAGE ★ REGULATORS	TRANSFORMERS* (Mains Prim. 220-240V)	ALUM. BOXES WITH LID*	PANEL METERS*
TO3 Can Type P	6.0-6V 100mA 90p	3x2x1 45p	FSD 60x46x35mm 68p
1A +ve 5V, 12V, 15V, 18V 145p	9.0-9V 75mA 95p	4x4x1 1/2 68p	0-50µA 60p
LM309K 135p	12.0-12V 100mA 98p	4x2x1 1/2 60p	0-100µA 60p
LM323K 625p	12.0-12V 150mA 140p	4x5x1 1/2 78p	0-1mA 60p
MVR5 or 12 180p	0.6-0.6V 280mA 160p	4x2x2 82p	0-5mA 60p
1A -ve 5V, 12V, 15V, 18V 220p	0.15-0.15V 0.3A 260p+	5x4x2 88p	0-10mA 60p
Plastic (TO92)	0.4-5.0-4.5V 0.6A 260p+	6x4x2 114p	0-100mA 60p
+ve 0.1A 5V, 6V, 8V, 12V, 15V, 30V 275p+	12.0-12V 0.5A 280p+	7x5x2 1/2 114p	0-500µA 60p
+ve 1A (TO220)	15.0-15V 0.5A 260p+	8x6x3 148p	0-1A 60p
5V, 12V, 15V, 18V, 24V, 99p	24.0-24V 0.5A 280p+	10x7x3 172p	0-2A 60p
-ve 0.5A 5V, 6V, 8V, 12V, 15V, 95p	9.0-9V 1A 275p+	12x5x3 210p	0-25V 60p
-ve 1A 5V, 12V, 15V, 175p	12.0-12V 1A 275p+		0-300V AC 410p each
5V 12V 15V 60p	LM309K 135p		
LM320-12 165p	LM323K 625p		
LM320-15 165p	MVR5 or 12 180p		
LM304H 240p	1A -ve 5V, 12V, 15V, 18V 220p		
LM317H 100p	Plastic (TO92)		
LM317K 350p	+ve 0.1A 5V, 6V, 8V, 12V, 15V, 30V 275p+		
LM325N 240p	+ve 1A (TO220)		
LM326N 240p	5V, 12V, 15V, 18V, 24V, 99p		
LM723 45p	-ve 0.5A 5V, 6V, 8V, 12V, 15V, 95p		
	-ve 1A 5V, 12V, 15V, 175p		
EARPHONES	5V 12V 15V 60p		
Magnetic	LM320-12 165p		
2.5mm 18p	LM320-15 165p		
3.5mm 18p	LM304H 240p		
Crystal 33p	LM317H 100p		
	LM317K 350p		
	LM325N 240p		
	LM326N 240p		
	LM723 45p		
CRYSTAL MICROPHONE INSERT 46p			
ULTRASONIC TRANS-DUCERS			
Receiver and Transmitter 40KHz 480p per pair			

news... digest

sub ton kit

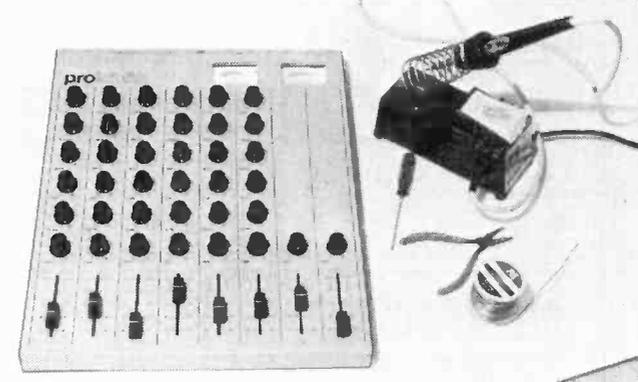

R E W Audio Visual have been given exclusive distribution rights on a new kit for budding rock & roll stars in the U.K. Called Prokit 62, it is a 6 into 2 audio mixer with features not normally found on mixers in the sub £100 range (at £99.95 it just creeps into this bracket). Each input channel has bass and treble equalisation, pan control, echo and cue busses, with choice of line or mike inputs. Distortion is claimed to be less


than 0.1% and noise is said to be less than -65dBm. The unit needs an external power supply to feed it with the + and -15V at 50mA it lives on (not supplied). Construction time is estimated to be a couple of evenings, and a 32 page manual is supplied with each kit. Further details from R E W Limited, 10/12 High Street, Colliers Wood, London SW19 2BE.

odds & ends

★ A. Marshall (London) Ltd., are moving their mail-order department from their Cricklewood Broadway premises. The new address for main offices, industrial sales, central stores and mail-order will be: Kingsgate House, Kingsgate Place, London N.W.6. The telephone number will change to 01-624 0805/6/6/8, the old premises at 40 Cricklewood Broadway have been refitted as a new branch. ★ A Single hand ASCII keyboard, called "Writehander", has been developed in the States. In use you place 4 fingers on switches representing the lower 4 ASCII bits and the thumb selects the remaining 3 bits, the machine looks like a hedgehog and is said to be both cheap and fast. ★ The National Enterprise Board is in the process of funding a new electronics company. Capital of £30-£50 million is to be used in the attempt to bring VLSI technology to the U.K., typical products would be 64K memories. The brains behind the scheme include British and American engineers in the States and at home.

★ Visual indication of FM station, automatically, is made possible with a new system developed by Phillips and the Dutch Broadcasting Corporation. A display indicates the result of decoding a signal superimposed on the transmitted signal, the signal is different for each station. Phillips are hoping for international agreement and cooperation to get the system off the ground (into the air). ★ The more you cram onto a silicon chip the more pins needed on the package. Up until now manufacturers of MSI and LSI have used modifications of the standard DIL, making it longer and/or wider. Problems produced by this approach include parasitic capacitance, which seriously limits the operating speed, and density of circuitry on PCBs. JEDEC, the organisation that registers all standard packages and specifications, are considering the details on a proposed new standard square package to be used in high density/speed applications.

ETI SPECIALS

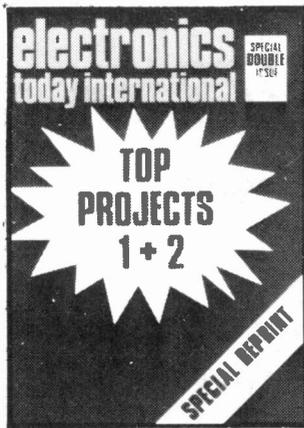

£2.50 + 25p P&P

1 + 2—Top projects include: Master mixer, 100 W guitar amp., low power laser, printmeter, transistor tester, mixer preamp, logic probe,



£1.00 + 25p P&P

Ni-Cad charger, loudhailer, 'scope calibrator, electronic ignition, car theft alarm, turnindicator canceller, brake

light warning, LM380 circuits, temperature alarm, aerial matcher, UHF TV preamp, metal locator, four-input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50 W stereo amp. plus many more. . . .


3—This issue was so popular that it is now sold out!
4—Includes:
Sweet sixteen stereo amp., waa-waa, audio level meter, expander/compressor, car theft alarm, headlight reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit! . . .
5—Twenty-two complete projects, including:
5 W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, gen.-purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter. . . .
6—Just published. Includes:
Graphic equaliser, 50-100 W amp. modules, active crossover, flash trigger, "star and dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show. . . .

SEE PAGE 64



75p + 25p P&P

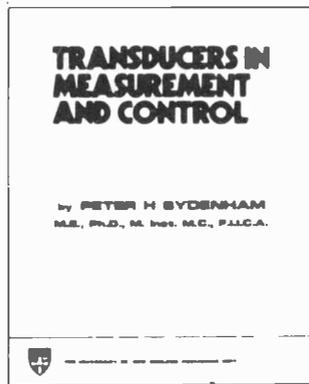Comprised entirely of new material, the edition covers such diverse subjects as Star Wars and hi-fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, Audio, Calculators and Video. How can you not read it?



£3.00 + 25p P&P

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have re-published the series

splendidly for use as a standard textbook. Written by Peter Sydenham, M.E., Ph.D., M.Inst.M.C., F.I.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead, Editor.

HOW TO ORDER

Postage and packing also refers to overseas. Send remittance in sterling only.

ETI Specials
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please mark the back of your cheque or PO with your name and address.

Please supply me with the following ETI Specials:

.....
.....
.....
.....
.....
.....

Total cheque/PO enclosed = £ ..

Address:

M

.....
.....
.....


(Please allow four weeks for delivery)



£1.50

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs. and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each! Each volume costs:

£1.50 + 25p P&P

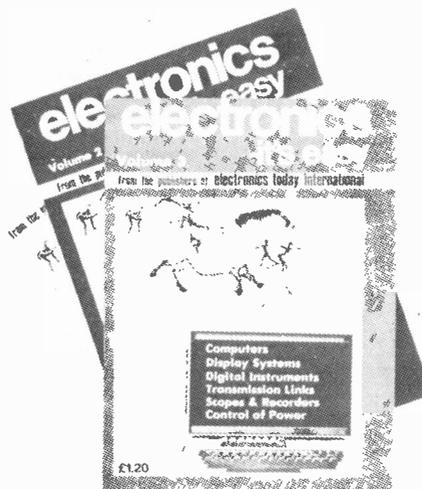


£1.20

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics. Each volume costs.

£1.20 + 25p P&P

NON-SUBSCRIBERS START HERE

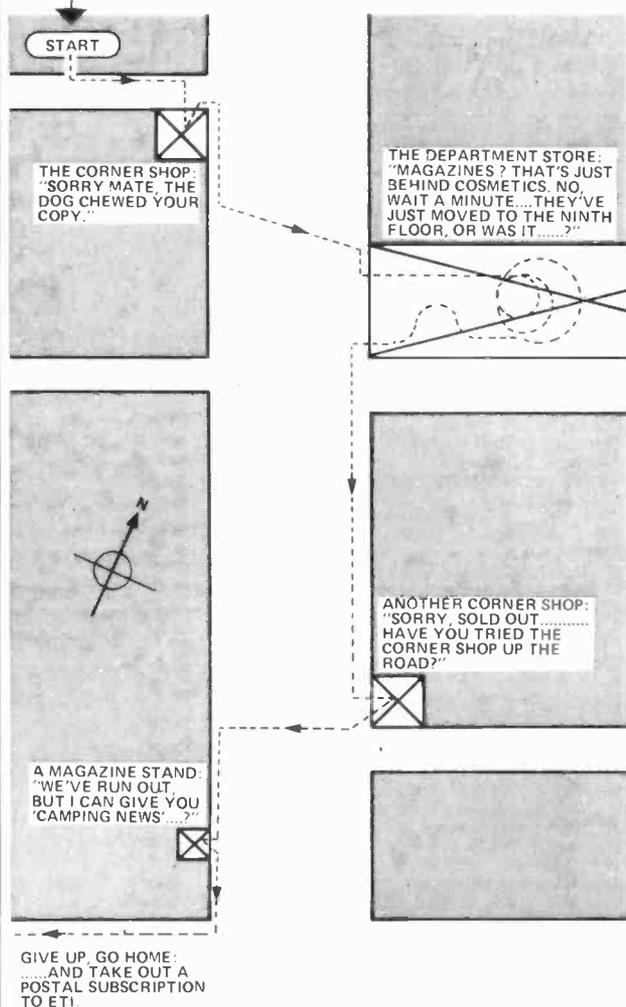

It can be a nuisance can't it, going from newsagent to newsagent? "Sorry squire, don't have it — next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsagent's going to be sure to cut his order for the next issue — but we're glad to say it doesn't happen very often.

Do yourself, your newsagent and us a favour. Place a regular order for ETI; your newsagent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember — we'll do it for you.

For a subscription, send us £7.00 (£8.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscription Service
Electronics Today International
25-27 Oxford Street, London W1R 1RF

... news digest..

solid state speech



If the latest goodie from Texas Instruments is as successful as we think it will be, the next generation will speak with an American accent! Called 'Speak & Spell' it is a box that talks to the kids (with a 'standard' American accent), and theoretically helps them pronounce new words correctly — it also compares how the kids spell the word with the correct (American) spelling, and indicates whether they gave the right answer.

The 200 words in the machine were selected by educators for the 7 to 12 year old, further sets of words are to be made available as plug-in modules. In its main mode of operation it selects a word at random and 'speaks' it. The user then types


in their version of how it is spelt, and the machine either says well done, or please try again (or noises to that effect). After 10 words the 'Speak & Spell' talks and displays a score. Various other modes of operation are also available, including a version of 'Hangman'.

Heart & Throat of the machine is a 128K ROM, the word library is stored as a series of sound values—representing the various word characteristics. Priced at 50 dollars in the States, it will be available from July onwards, although no date has been given for U.K. release. Methinks the ETI office could use one usulli. Texas Instruments Inc., Consumer relations, P.O. Box 53, Lubbock, Texas 79408.

national phoenix

National Semiconductor have recently opened the first plant in the world to process 4 inch silicon wafers. The production facility has been built on the ashes of their previous factory in Greenock, which burnt down a year ago. The builders estimated that it would take between 2 and 2½ years to rebuild, National were determined to do it in 12 months and succeeded. The advantage of 4 inch over the more normal 3 inch wafer is simple — they get a lot more usable ICs in the same time.

A touch of humour was added when Peter Sprague, a director of National and also of Aston Martin, failed to arrive in a brand new Aston Martin Lagonda (yours for £32,000). The sophisticated electronics in the car were not functioning, or as he remarked to some reporters "The *©£&()* + electronics don't work", the *©£&()* + electronics are made by a company that has just built a rather large factory in Scotland.

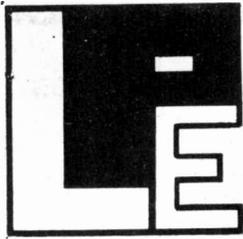

Room ET1/8
313 Kingston Road, Ilford
Essex IG1 1PJ, England
01-553 1001

L.P. ENTERPRISES

From the representatives in Europe . . . for America's leading Micro-computer magazines and books, for the hobbyist, educationist and professional alike, we bring you a little light browsing!
Reading maketh a full man . . . Francis Bacon (1561-1626)

Tick or indicate quantity ordered.		Tick or indicate quantity ordered		Price	Price
From Adam Osborne Associates		* From Creative Computing Press		UK	Overseas
INTRODUCTION TO MICROCOMPUTERS		Best of Creative Computing Volume 1		£6.95	If Different
Volume 0: The Beginners Book	£5.95	Best of Creative Computing Volume 2		£6.95	
Volume 1: Basic Concepts	£5.95	101 BASIC Games (Revised & Reprinted Feb. 78)		£5.50	
Volume 2: Some Real Products (Revised Late 1977)	£11.95	The Colossal Computer Cartoon Book		£3.95	
6800 Programming for Logic Design	£5.95	Computer-Rage (A new Board Game)		£6.95	
8080 Programming for Logic Design	£5.95	Artist and Computer		£3.95	
Z80 Programming for Logic Design	£5.95	* From Everyone Else			
8080A/8085 Assembly Language Programming	£6.95	Magazine storage boxes (hold 12 minimum)		£1.75	
6800 Assembler Language Programming	£6.95	Sybox: Microprocessors from Chips to Systems by R. Zacs		£7.95	
Some Common BASIC Programs	£5.95	Sybox Microprocessors Interfacing Techniques by R. Zacs		£7.95	
BUSINESS PROGRAMS IN BASIC		Dilithium: Home Computers Volume 1: Hardware		£6.50	
Payroll With Cost Accounting	£9.95	Dilithium: Home Computers Volume 2: Software		£5.95	
Accounts Payable & Accounts Receivable (Available from Midsummer '78)	£9.95	Getting Involved With Your Own Computer		£4.75	
General Ledger (Available from late summer 78)	£9.95	TV Typewriter Cookbook by Don Lancaster		£7.50	
From Scelbi Computer Consulting Inc.		TTL Cookbook		£7.50	
6800 Software Gourmet Guide & Cookbook	£7.95	CMOS Cookbook		£7.95	
8080 Software Gourmet Guide & Cookbook	£7.95	IC Timer Cookbook		£7.50	
8080 Programmers Pocket Guide	£2.25	IC OP-AMP Cookbook		£9.50	
8080 Hex Code Card	£2.25	RTL Cookbook		£4.25	
8080 Octal Code Card	£2.25	Computer Programs that Work (in Basic)		£2.55	
8080 Guide and One 8080 Code Card	£4.20	* From Basic Software Library			
8080 Guide and Both Code Cards	£6.00	(from Scientific Research Instruments)			
SCELBAL High Level Language for '8008/8080' Systems	£39.25	Vol 1: Business and Personal Booking Programs		£17.50	
SCELBAL String Handling Supplement	£8.00	Vol 2: Maths and Engineering Programs		£17.50	
SCELBAL Extended Maths Supplement	£4.00	Vol 3: Advanced Business Programs		£26.95	
Understanding Microcomputers & Small Computer Systems	£7.95	Vol 4: General Purpose Programs		£7.95	
SCELBI 'BYTE' Primer	£9.95	Vol 5: Experimenters Programs (General Purpose)		£7.95	
8080 Standard Assembler (In Book Format)	£15.95	Vol 6: General Ledger Program		£32.50	
8080 Standard Editor (In Book Format)	£9.95	Vol 7: Professional Programs		£26.95	
From Peoples Computer Company		Magazines: Back Issues			
Reference Books of Personal & Home Computing	£4.95	Personal Computing		£1.75	
What to Do After You Hit Return	£7.00	Interface Age		£2.25	
Dr. Dobbs Journal Volume 1	£10.00	Dr. Dobbs Journal		£1.75	
*From Kilobaud/73 Magazine Inc.		Computer Music Journal		£2.50	
Hobby Computers Are Here	£3.95	Peoples Computers		£1.75	
New Hobby Computers	£3.95	*BYTE		£2.25	
From Dymax Inc.		Creative Computing		£1.75	
Instant BASIC by Jerald R. Brown	£4.95	Calculators & Computers		£1.75	
Your Home Computer by James White	£4.95	ROM		£1.75	
My Computer Like Me . . . When I Speak BASIC By Bob Albrecht	£1.65	Kilobaud		£2.25	
Games With A Pocket Calculator by Thiagarajan & Stilovitch	£1.75	73		£2.25	
Games, Tricks and Puzzles For a Hand Calculator by W Judd	£2.49	MAGAZINES: Subscriptions			
*From BYTE Publications Inc.		Personal Computing (Twelve Issues Yearly)		£16.00	£17.00
Paperbytes:		Interface Age (Twelve Issues Yearly)		£20.00	£20.50
Tiny Assembler for 6800 Systems	£5.75	Dr. Dobbs Journal (Ten Issues Yearly)		£13.00	£13.50
Bar Code Loader for 6800, 8080, Z80 & 6502 Micros	£1.75	Computer Music Journal (Four Issues Yearly)		£8.50	£9.00
Best of BYTE Volume 1	£8.95	Peoples Computers (Six Issues Yearly)		£8.00	£8.50
		Kilobaud (Twelve Issues Yearly)		£20.00	£21.00
		*BYTE (Twelve Issues Yearly) via USA		£15.00	
		BYTE (Twelve Issues Yearly) via UK		£21.00	
		Creative Computing (Six Issues Yearly)		£8.50	£9.00
		Calculators & Computers (Seven Issues Yearly)		£10.00	£10.50
		73 (Twelve Issues Yearly)		£20.00	£21.00

Due to fluctuations of the dollar, prices are subject to change

LPE/578/VC

HOW TO ORDER

Please note our prices include postage and packing, but not insurance, if wanted add 12p for every £10 of books ordered. Make cheques, POs etc payable to:

L.P. Enterprises
CREDIT CARDS accepted
BARCLAYCARD VISA/ACCESS/
DINERS CLUB/AMERICAN EXPRESS

Phone: 01-553 1001 for Credit Card orders (24-hour service).

Send to address above for the attn. of David, Room ET1/8
Indicate Payment Method:

..... My cheque, P.O., I.M.O. is enclosed in Sterling on U.K. Bank
..... Charge to Barclaycard/Visa/Access/Diners/American Express

Credit Card No. Expiry date

Name

Address

POSTCODE

Signature

All Orders must be Prepaid
Total Enclosed £.....

All publications are published in U.S.A. and shipped air-freight by L.P. Enterprises. In unusual cases, processing may exceed 30 days.
*BYTE subscriptions are processed in USA and are air-freighted & posted from Amsterdam and will take 3 months to start.

U.K. subscriptions start within three weeks

TRADE ENQUIRIES WELCOME

Ever feel you need a good rub down before you start one of our projects? Perhaps you need—

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects. ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172). The following are available in the ETIPRINTS series.

001 3 Channel Tone Control Spirit Level Clock A Digital Thermometer Skeet Game Compander	Oct 77 Oct 77 Nov 77 Oct 77 Nov 77 Nov 77	004 Metal Locator Mk II Ultrasonic Tx/Rx 5 Watt Stereo Amp (modified) Metronome Porch Light Shutter Timer	Feb 78 Feb 78 Jan 77 Feb 78 Feb 78 Feb 78	007 Star Trek Radio CD Ignition CCD Phaser White Line Follower	May 78 May 78 May 78 April 78
002 House Alarm Rev Monitor Clock B	Jan 78 Dec 77 Dec 77	005 Op-Amp Supply Frequency Shifter LCD Panelmeter Light Dimmer (3 times)	Mar 78 Mar 78 Mar 78 Mar 78	008 Tank Battle Helping Hand	May 78 May 78
003 Race Track Game Hammer Throw Freezer Alarm	Jan 78 Jan 78 Dec 77	006 CMOS Switched Preamp Experimenters PSU 555 Boards (twice)	From "Electronics Tomorrow"	009 AM/FM Radio Bridge Oscillator CMOS Stars & Dots	June 78 June 78 June 78
				015 UFO Detector Torch Finder (twice) Etiwet (twice)	July 78 July 78 Aug 78

From Project Book 6:

010 Bench Amplifier Freezer Alarm Marker Generator LED Dice Watchdog (2 PCBs) Stars & Dots PSU	011 Noise Generator General Preamp Flash Trigger Compander Active Crossover (2 PCBs)	012 Disco Lightshow Stereo Simulator Digital Thermometer Amplifier Module Amplifier PSU Equaliser Equaliser PSU	014 Skeet Game Sweep Oscillator Burglar Alarm GSR Monitor
---------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------

ORDER TODAY

Send a cheque or P.O. (payable to ETI Magazine) to—

ETI PRINT
ETI MAGAZINE,
25/27 OXFORD STREET, LONDON W1R 1RF.

75p Each, including
VAT and P&P.



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

Marshall's

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
Express Mail Order Tel. orders on credit cards £1.00 min.
Trade and export enquiries welcome

A. Marshall (London) Ltd., Dept. ETI. Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel. 01-624 0805. Retail Sales London: 40-42 Cricklewood Broadway, NW2 3ET. Tel. 01-452 0161/2. Telex 21492. London: 325 Edgware Road, W2. Tel. 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel. 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, BS16 2LX. Tel. 0272 654201

TRANSISTORS		2N3393		2N4037		2N5192		2N6124		8C108A		8C178B		8C213C		8C337		8D240A		8F160		8F879		ME4001		11P30C	
2N696	0.39	2N2218	0.35	2N4037	0.60	2N5192	0.80	2N6124	0.45	8C108A	0.16	8C178B	0.35	8C213C	0.15	8C337	0.20	8D240A	0.49	8F160	0.33	8F879	0.30	ME4001	0.16	11P30C	0.70
2N697	0.31	2N2218A	0.38	2N4058	0.22	2N5193	0.75	2N6125	0.47	8C108B	0.17	8C179	0.25	8C213A	0.17	8C338	0.23	8D240C	0.59	8F161	0.65	8F880	0.30	ME4002	0.16	11P31A	0.54
2N698	0.49	2N2219	0.38	2N4059	0.17	2N5194	0.80	40061	0.55	8C108C	0.17	8C179A	0.25	8C213B	0.17	8C339	0.23	8D241C	0.49	8F162	0.37	8F881	0.30	ME4003	0.16	11P32A	0.72
2N699	0.58	2N2219A	0.39	2N4060	0.22	2N5195	0.97	40062	0.55	8C109	0.16	8C179B	0.25	8C213C	0.17	8C340	0.23	8D242A	0.55	8F173	0.37	8F882	0.34	ME4101	0.11	11P32A	0.59
2N706	0.30	2N2220	0.39	2N4338	0.85	2N5246	0.38	40408	0.82	8C109C	0.18	8C182	0.12	8C214	0.17	8C548	0.13	8D242A	0.55	8F177	0.27	8F884	0.34	ME4102	0.11	11P32C	0.82
2N706A	0.30	2N2221	0.25	2N4341	0.75	2N5247	0.44	40409	0.82	8C140	0.30	8C182A	0.12	8C214B	0.17	8C549	0.14	8D243A	0.65	8F179	0.33	8F885	0.38	ME4104	0.11	11P31C	0.97
2N709	0.30	2N2221A	0.25	2N4341A	0.92	2N5248	0.44	40410	0.82	8C141	0.32	8C182B	0.13	8C214C	0.17	8C549B	0.14	8D243C	0.67	8F180	0.37	8F886	0.38	ME6101	0.22	11P32A	1.08
2N718	0.30	2N2222	0.25	2N4342	1.45	2N5249	0.44	40411	0.81	8C147	0.13	8C182C	0.15	8C214D	0.18	8C549C	0.15	8D244A	0.67	8F181	0.37	8F887	0.38	ME6102	0.22	11P32C	1.08
2N718A	0.54	2N2222A	0.25	2N4342A	1.45	2N5249A	0.44	40412	0.81	8C147B	0.13	8C182A	0.15	8C214E	0.18	8C550	0.14	8D244B	0.67	8F182	0.37	8F888	0.38	ME6103	0.22	11P32C	1.08
2N720A	0.85	2N2223	0.27	2N4343A	0.17	2N5296	0.44	40456	0.58	8C148	0.13	8C182B	0.15	8C214C	0.18	8C558	0.13	8D245A	0.69	8F183	0.44	8F889	1.37	ME6104	0.22	11P32C	1.08
2N727	0.50	2N2264	0.80	2N7302	0.14	2N4124	0.19	40673	0.80	8C148B	0.13	8C183	0.12	8C237B	0.15	8C559	0.15	8D245C	0.65	8F184	0.41	8F890	1.37	ME6105	0.22	11P32C	1.08
2N914	0.38	2N2647	1.55	2N7304	0.14	2N4126	0.19	40669	1.30	8C148C	0.13	8C183A	0.12	8C238A	0.13	8C570	0.21	8D246A	0.72	8F185	0.47	8F891	1.37	ME6106	0.22	11P32C	1.08
2N916	0.33	2N2903	1.60	2N7305	0.14	2N4284	0.38	40669	1.30	8C149	0.15	8C183B	0.13	8C238B	0.13	8C571	0.26	8D246B	0.93	8F186	0.47	8F892	1.37	ME6107	0.22	11P32C	1.08
2N917	0.38	2N2904	0.31	2N7306	0.14	2N4286	0.22	40670	1.30	8C149B	0.15	8C183C	0.13	8C238C	0.13	8C572	0.18	8D433	0.44	8F187	0.46	8F893	1.37	ME6108	0.22	11P32C	1.08
2N918	0.45	2N2905	0.31	2N7307	0.14	2N4287	0.22	40671	1.30	8C150	0.15	8C183D	0.15	8C239	0.16	8D434	0.44	8F188	0.46	8F196	0.16	8F894	1.37	ME6109	0.22	11P32C	1.08
2N919	0.37	2N2906	0.31	2N7308	0.14	2N4288	0.22	40672	1.30	8C151	0.15	8C183E	0.15	8C240	0.17	8D435	0.46	8F197	0.18	8F895	1.37	ME6110	0.22	11P32C	1.08		
2N929A	0.37	2N2905A	0.31	2N7309	0.12	2N4289	0.22	40673	1.30	8C152	0.15	8C183F	0.15	8C257A	0.18	8D436	0.46	8F198	0.18	8F896	1.37	ME6111	0.22	11P32C	1.08		
2N930	0.37	2N2906A	0.25	2N7311	0.16	2N4347	2.20	40674	1.30	8C153	0.15	8C183G	0.15	8C258	0.19	8D437	0.55	8F199	0.19	8F897	1.37	ME6112	0.22	11P32C	1.08		
2N930A	0.95	2N2906A	0.25	2N7312	2.20	2N4348	2.65	40675	1.30	8C154	0.15	8C183H	0.15	8C259	0.19	8D438	0.55	8F200	0.19	8F898	1.37	ME6113	0.22	11P32C	1.08		
2N1171	0.30	2N2907	0.25	2N7313	3.15	2N4918	0.65	40676	1.30	8C155	0.15	8C183I	0.15	8C260	0.43	8D439	0.41	8D529	0.49	8F201	0.22	8F899	1.37	ME6114	0.22	11P32C	1.08
2N1189	0.30	2N2907A	0.25	2N7314	3.15	2N4919	0.70	40677	1.30	8C156	0.15	8C183J	0.15	8C261	0.43	8D530	0.41	8D530	0.49	8F202	0.22	8F900	1.37	ME6115	0.22	11P32C	1.08
2N1190	0.30	2N2907A	0.25	2N7315	3.15	2N4920	0.75	40678	1.30	8C157	0.15	8C183K	0.15	8C262	0.43	8D531	0.41	8D531	0.49	8F203	0.22	8F901	1.37	ME6116	0.22	11P32C	1.08
2N1193	0.30	2N2907A	0.25	2N7316	3.15	2N4921	0.80	40679	1.30	8C158	0.15	8C183L	0.15	8C263	0.43	8D532	0.41	8D532	0.49	8F204	0.22	8F902	1.37	ME6117	0.22	11P32C	1.08
2N1202	0.50	2N2925	0.17	2N3900	0.28	2N4922	0.90	40680	1.30	8C159	0.15	8C183M	0.15	8C264	0.43	8D533	0.41	8D533	0.49	8F205	0.22	8F903	1.37	ME6118	0.22	11P32C	1.08
2N1203	0.58	2N2926	0.17	2N3901	0.28	2N4923	0.75	40681	1.30	8C160	0.15	8C183N	0.15	8C265	0.43	8D534	0.41	8D534	0.49	8F206	0.22	8F904	1.37	ME6119	0.22	11P32C	1.08
2N1293	0.50	2N3053	0.25	2N3902	0.20	2N4924	1.15	40682	1.30	8C161	0.15	8C183O	0.15	8C266	0.43	8D535	0.41	8D535	0.49	8F207	0.22	8F905	1.37	ME6120	0.22	11P32C	1.08
2N1353A	0.52	2N3054	0.72	2N3903	0.18	2N5086	0.30	40683	1.30	8C162	0.15	8C183P	0.15	8C267	0.43	8D536	0.41	8D536	0.49	8F208	0.22	8F906	1.37	ME6121	0.22	11P32C	1.08
2N1354	0.42	2N3055	0.75	2N3904	0.18	2N5087	0.30	40684	1.30	8C163	0.15	8C183Q	0.15	8C268	0.43	8D537	0.41	8D537	0.49	8F209	0.22	8F907	1.37	ME6122	0.22	11P32C	1.08
2N1944	0.45	2N3390	0.50	2N3905	0.18	2N5088	0.30	40685	1.30	8C164	0.15	8C183R	0.15	8C269	0.43	8D538	0.41	8D538	0.49	8F210	0.22	8F908	1.37	ME6123	0.22	11P32C	1.08
2N195	0.40	2N3391	0.40	2N3906	0.15	2N5089	0.30	40686	1.30	8C165	0.15	8C183S	0.15	8C270	0.43	8D539	0.41	8D539	0.49	8F211	0.22	8F909	1.37	ME6124	0.22	11P32C	1.08
2N195A	0.40	2N3391A	0.45	2N4032	0.65	2N5190	0.85	40687	1.30	8C166	0.15	8C183T	0.15	8C271	0.43	8D540	0.41	8D540	0.49	8F212	0.22	8F910	1.37	ME6125	0.22	11P32C	1.08
2N217	0.55	2N3392	0.17	2N4033	0.72	2N5191	0.75	40688	1.30	8C167	0.15	8C183U	0.15	8C272	0.43	8D541	0.41	8D541	0.49	8F213	0.22	8F911	1.37	ME6126	0.22	11P32C	1.08

For discount quantity prices contact us now

FULL RANGE IN OUR NEW CATALOGUE



LINEAR CIRCUITS

CA3018	0.75	LM7379S	4.25	LM7815K	1.75	TB4530	2.35
CA3018A	1.10	LM3808N	0.96	LM7824K	1.75	TB4530Q	2.45
CA3020	2.20	LM3808N1A	1.00	LM7824K0C2	0.30	TB4540	2.60
CA3020A	2.50	LM3818AN	2.08	LM7812ZC2	0.30	TB4540Q	2.70
CA3026A	0.90	LM3818AN	1.68	LM7815CZ	0.30	TB4550	3.60
CA3026B	1.25	LM3828N	1.32	MM5314	4.50	TB4550Q	3.80
CA3030	1.50	LM3848N	1.55	MM5316	4.60	TB4550Q000	3.00
CA3030A	2.20	LM3868N	0.88	NE555	0.33	TB4570	2.10
CA3038	2.90	LM3878N	1.10	NE556	0.85	TB4570Q	2.20
CA3038A	4.10	LM3888N	1.00	NE568N	1.98	TB4700	2.08
CA3045	1.55	LM3898N	0.75	NE568	4.50	TB4720Q	2.06
CA3046	0.77	LM702C	0.81	NE568	4.50	TB4720Q	2.06
CA3048	2.45	LM709	0.70	NE562	4.50	TB4750	2.45
CA3052	1.78	LM709B	0.50	NE565	1.39	TB4800	1.30
CA3080	0.85	LM7091A	0.49	NE566	1.75	TB4810S	1.30
CA3080A	1.20	LM710	0.67	NE567	1.90	TB4820	0.80
CA3086	0.30	LM7101A	0.64	NE571N	4.95	TB4820Q	2.99
CA3086B	1.87	LM7111C	0.22	NE568	4.50	TB4750	2.36
CA3089B	2.90	LM723C	0.75	SA5570	2.70	TA1806	2.55
CA3090Q							

DESIGNING HIGH(EST)-FI AMPS

Audio amplifier design has come a long long way since its move into semiconductors. Stan Curtis, who has been responsible for such excellent examples of the art as the Cambridge Audio and Lecson, explains here the black arts of super-fi designing.

CAREFUL LISTENING TESTS have shown that while an amplifier that measures badly is *unlikely* to sound good one that measures well *cannot* be guaranteed to sound good. Thus it is apparent that the traditional measurements of power distortion and frequency response need supplementing by new and more powerful laboratory tests. Such tests should more closely relate to the conditions prevailing when the amplifier is driving realistic loads and using music signals rather than sine-waves, which of course represent only one special case.

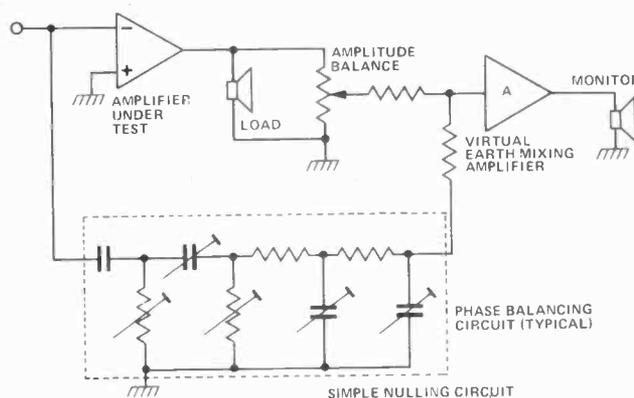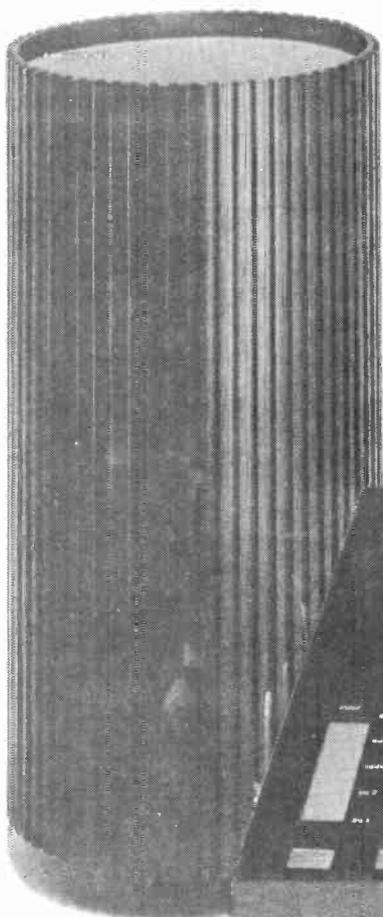

Block diagram of the Peter Walker balancing test.

Balancing Act

The first such test was popularised by Peter Walker of Quad. It is a simple nulling system which attempts to cancel the output and input signals of an amplifier. With full cancellation whatever remains must be distortion, i.e. signals added to or subtracted from the original. The ideal, or perfect, amplifier will produce no residual at the output of the nulling circuit and any imperfections will be monitored during a piece of music.

In practical terms the balancing of this circuit is very difficult if a significant degree of accuracy is required. Thermal drifts can aggravate the problem and generally it is difficult to set up for more than one amplifier type as usually the whole phase balancing network needs to be re-calculated and re-adjusted each time. However, this simple circuit is useful for showing just how often amplifiers are clipping the signal in the course of a piece of music and how frequently some amplifiers slow-rate limit the signal.

lecon

However, with such high current capability it is essential that the amplifiers have speaker muting to prevent switch-on "thumps" (or more accurately, earthquakes) and DC offset protection to protect the loudspeakers from the effects of 20 Amps of pure DC!

Offsetting Long Tails!

DC offset has been a major problem with many DC coupled amplifiers (i.e. those having no output capacitor). The offset voltage measured across the output terminals should not be any more than ± 50 mV. Once this voltage starts to rise the loudspeaker is subjected to a DC bias which moves the coil out of the central position. This in turn causes the coil to heat up and the power-handling capability of the loudspeaker to be restricted.

Eventually (and often sooner) the loudspeaker will blow. Many amplifiers have an offset voltage that is acceptable when the amplifier is first switched on but which starts to increase as the amplifier heats up. Such amplifiers are subject to thermal drift and this drift is normally due to a component mismatch in the circuit. The conventional amplifier, with a long-tailed pair at the input, is "theoretically" free of thermal drift as these will be automatically compensated for by the DC feedback.

However, this is on the assumption that the first two transistors (or FETs), forming the long-tailed pair, are perfectly matched.

The input offset voltage (upon which the output offset voltage is dependent) is related to the base-emitter voltage V_{BE} of each transistor.

$$\text{e.g. } V_{OS} = V_{BE1} - V_{BE2}$$

This difference can be made almost insignificant by using a dual-transistor or a monolithic integrated-circuit differential stage where matching is provided by the simultaneous adjacent fabrication of the two transistors. With discrete transistors, however, a close match is unlikely.

Similarly unbalanced output loading or mismatch of the collector resistors also increases the offset voltage. These mismatches also worsen the linearity (and hence the distortion) of this stage. Thus well designed amplifiers usually use 1% tolerance resistors in these positions and adopt balanced circuitry throughout.

The offset voltage is considerably reduced by the application of local DC feedback that occurs when emitter resistors are fitted. In this case;


$$V_{OS} = V_{BE1} - V_{BE2} + I_{E1}R_{e1} - I_{E2}R_{e2}$$

and so by adjusting the balance between R_{e1} and R_{e2} with a trimpot a balance can be achieved.


Emitter Resistance

Note that $R_e = R_e + r_e$ is the total external emitter resistance and r_e is the transistor dynamic emitter resistance. Thus it can be seen that in the earlier typical example of a stage without emitter resistors, an imbalance of r_e and r_e will cause a worsening of the offset voltage. More importantly it can reduce the common mode rejection of the stage. In this case the common mode is the HT lines with their ripple to appear at the output of the amplifier.

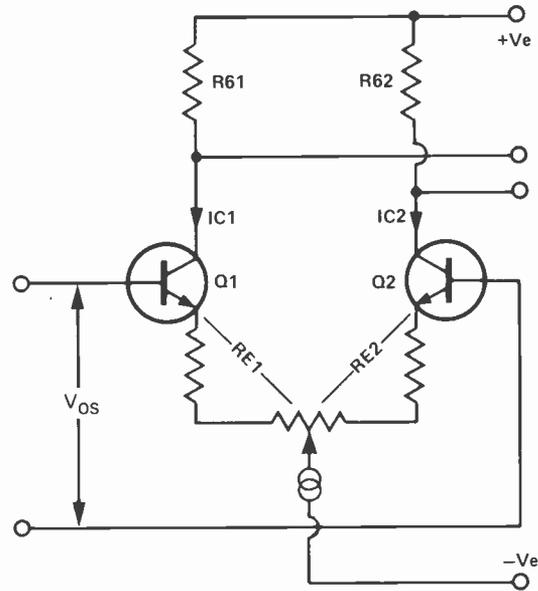
Of course the presence of emitter resistors also lowers the AC gain of the stage. For reasons to be discussed later this is not such a bad thing but in some amplifiers, for



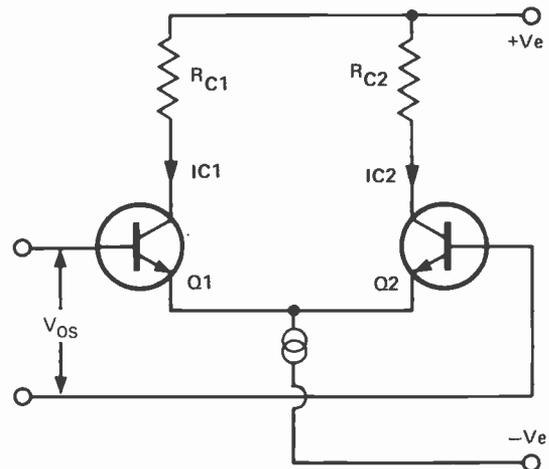
Differential pair with variable emitter resistances balanced by variation of the potentiometer.



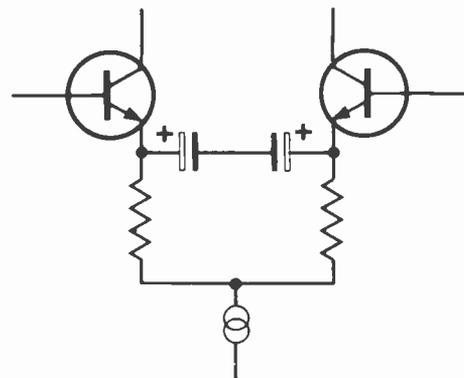
In this circuit the input offset voltage is related to the base-emitter voltage of this transistor.



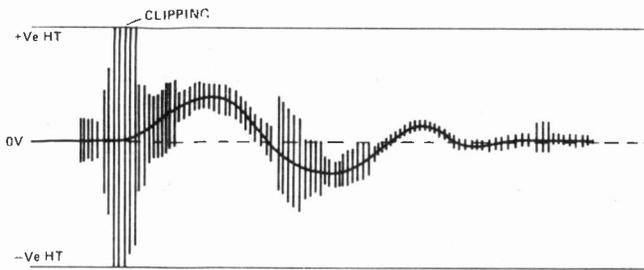
Recovering lost gain by use of bypass capacitors across the emitter resistances.



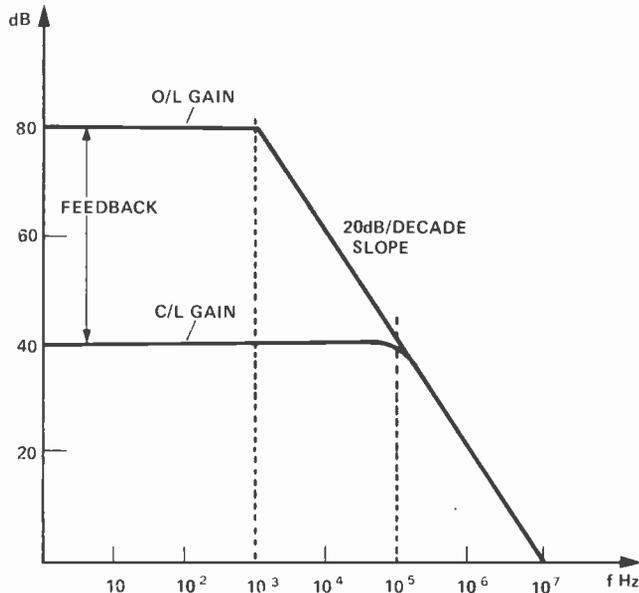Effect of a sine wave of varying amplitude as signal upon the DC offset voltage at the output.



In the case shown in the diagram (unconditional stability) the open-loop response of the amplifier is stabilised by rolling it off at a slow 20 dB/decade slope with a single pole at 1 KHz. This amplifier would be stable with any amount of resistive feedback. However it will be seen that at higher audio frequencies the amount of feedback available reduces and so the distortion of the amplifier will increase. For this reason many amplifiers are of the "marginally stable" type.

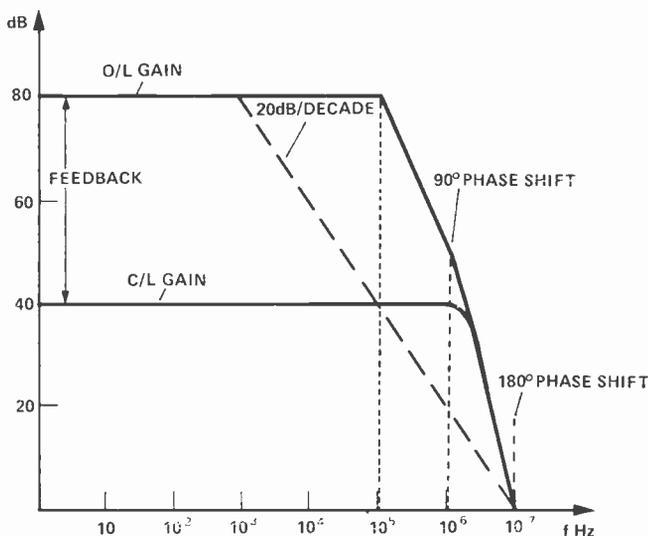

In this case the amplifier has a fast roll-off which allows an improved closed loop performance at higher frequencies but without careful compensation they are not stable under all conditions of feedback. Once the phase shift reaches 180° the amplifier will become unstable so it can be seen that our example is only marginally stable.

example the GAS Ampzilla. This gain can be recovered by using bypass capacitors.

Clip-on Off Set

Another situation where abnormal DC offset voltages occur is following a clipping overload of the amplifier. When many amplifiers are driven into clipping, the DC voltage of output rises towards one of the HT lines and then when the signal comes out of clipping the amplifier takes a finite time (often several seconds) to recover with the output DC voltage often oscillating between a positive and negative voltage before finally settling back to its nominal zero. Of course, when the amplifier is driven into clipping the normal negative feedback system ceases to control the amplifier.

Thus the DC instability is indicative of poor low frequency stability in the amplifier. Some of the worst (but not all) amplifiers in this respect, have separate AC and DC feedback loops and so have big electrolytic capacitors (decoupling the AC loop) which take time to charge and discharge.

The old Cambridge P100 amplifier had this problem and the effect on the reproduction of a loud bass note can be imagined to be as waffley and uncontrolled as it is. Regrettably many amplifiers still suffer from this problem.

Quite often some amplifiers go unstable without their owners becoming aware of the problem. Sometimes the oscillation may be moderate in level and at a very high frequency; the only symptom being that the amplifier seems to run hotter and next-door's electric drill causes more TV interference than before!

Compensation Phase

To know why some amplifiers are potentially unstable it is necessary to understand the principles of phase compensation. Much of the low distortion characteristics of amplifiers are achieved through negative feedback. If the phase shift around the feedback loop reaches 360° at any frequency at which the loop gain (i.e. the overall amplifier gain) is unity the result is a self-sustaining oscillation at that frequency.


The phase-inversion to provide negative feedback produces a stabilizing 180° (eg. "out of phase") phase shift, but an additional 180° can be developed in the amplifier.

The phase shift developed through an amplifier is the combined phase shift of its several stages, and it usually develops 180° at higher frequencies. To ensure frequency stability under feedback conditions, phase compensation *reduces* the amplifier gain at those frequencies for which phase shift is high and it reduces high frequency phase shift by accepting a greater phase shift at low frequencies. This is accomplished by adding response poles and zeros in the form of resistor-capacitor networks (real or inherent in the transistors) in the amplifier circuitry.

Equally important, to the owner of an expensive pair of loudspeakers, is the problem of high-frequency instability. These days very few high quality amplifiers are so unstable that they break into oscillation. However, quite a few respected units are on the edge of instability and so can potentially become unstable following a shift in operating conditions or of output loading. ▶

Sum Theory

The author used another technique at Cambridge Audio to investigate the changes in amplifier performance that are dependent upon the loudspeaker load. The two channels of a stereo amplifier are driven in mono but one channel is converted to become non-inverting. The outputs of both channels are summed and the resulting signal is monitored. Theoretically both channels should transmit the signal in the same way and (for a given circuit design) any distortion, time aberrations etc. should be the same for both channels. It is often quite possible to balance the two channels (driving 8 Ohm resistive loads) so that the residual is inaudible. However when one 8 Ohm load is replaced by a real

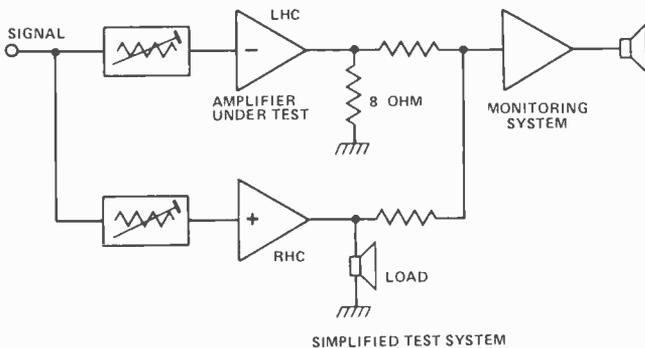

Using one channel as an inverting amplifier to monitor distortion produced by the design.

"live" loudspeaker the residual betrays problems caused by the new load. In a refined form the test works well and it did reveal two interesting things;


i) the two channels of the average amplifiers are rarely identical

ii) some amplifiers work better in the inverting mode than in the non-inverting.

These tests serve best to indicate imperfections without generating much data to help the designer. Two simple but useful tests do generate an awful lot of usable data. The first is an HF Intermodulation Test.

IM High

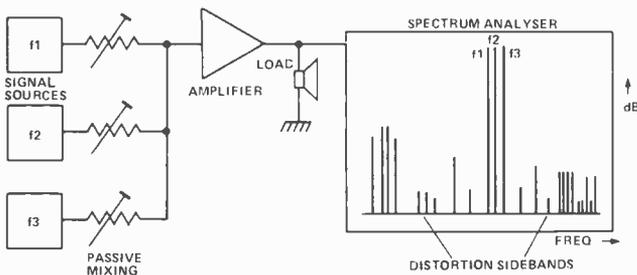The conventional IM test uses an LF (50 Hz) and an HF (7 kHz) tone in a 4 to 1 ratio and then measures the sum-total of the sideband (e.g. distortion) components. This is of little practical value unless the amplifier is particularly non-linear.



Intermodulation distortion testing using three frequencies.


The HF IM test uses two tones of, say, 15 000 Hz and 15 100 Hz and the resulting side-bands are viewed on a spectrum analyser. The frequencies can be altered to

suit whatever simulation that is desired, e.g. two sopranos trying to sing the same note.

By repeating the tests at different levels it can be seen that many amplifiers have a performance which varies appreciably with signal level, and the test results correlate very well in identifying amplifiers with an aggressive "top end."

Dynamically Noisy

The second test is similar but attempts to measure the amplifiers' performance under more varying, "dynamic" conditions. A white noise source has a harmonic and amplitude structure which is variable and random and thus provides a better simulation of a music signal than does a sine-wave. The noise signal is passed through a bandpass filter to define its frequency response. The bandwidth and centre-frequency can be altered to suit the investigation as can the overall operating level. The output of the amplifier is fed to a spectrum analyser where the out of band components can be studied. Again this test is very useful for studying the effects of different loudspeaker loads but more significantly for subjecting the amplifier to random momentary "clipping" overloads.

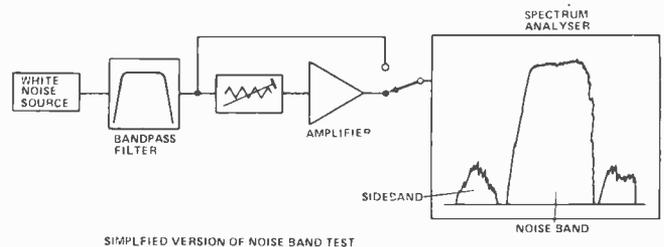


Noiseband testing with a spectrum analyser, the sidebands produced by the amp are clearly visible.

A Channel and A Log

Possibly the most complex type of testing in use is a form of input and output signal comparison used by Analog Engineering Associates in the U.S.A. and, in a simplified form, by Mission Electronics in the U.K. AEA have developed a Transient Distortion measurement system that uses music as a test signal to evaluate circuit performance under dynamic conditions. This system consists of a dual channel analogue to digital converter which is designed to have a resolution of 1 part in 65 536 or 0.0015%.

One channel of this is used to sample the input music signal whilst the second channel samples the output signal via a precision attenuator. The digitally encoded output of the converters is fed to a computer memory system for later analysis. Instead of trying to compensate for the amplifiers phase and frequency response with a passive circuit (as in the earlier simple nulling circuit) a frequency sweep is made through the amplifier to generate a "transfer function" which the computer can use to correct the data during the subsequent error analysis.

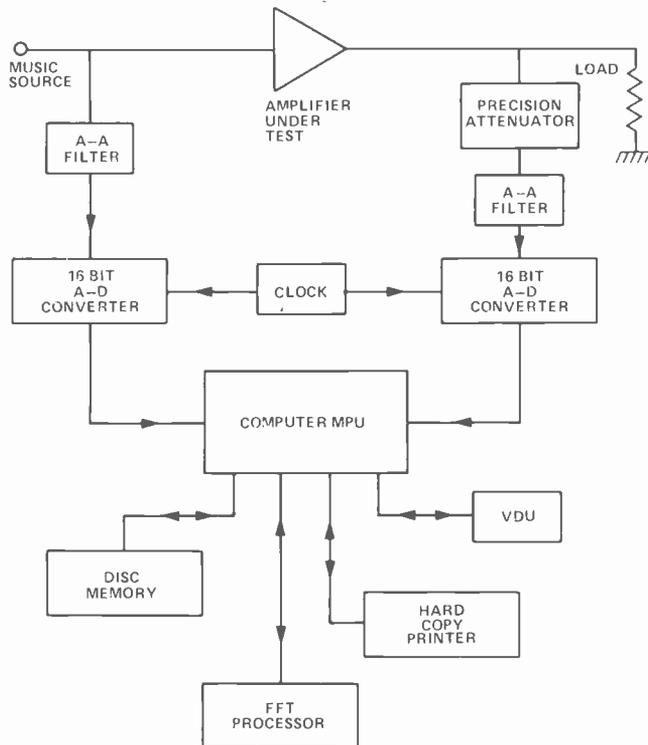Once a series of measurements have been made in the course of playing a passage of music the resultant data can be subjected to a series of Fourier and Coherence analytical calculations. Put simply, this means that any difference between the input and output



Analog Engineering's Transient Intermodulation Distortion Measurement System, used in Britain by Mission Electronics.

signals can be described in a form that is useful to the engineer and related to the structure of the music signal at that instant. Unfortunately this test show that, as yet, no perfect amplifier exists — each type of amplifier circuit produces its own particular types of "transient error."


Out of The Rut

A few years ago power-amplifier design had settled into a satisfying rut. In the U.K., the Quad 303 and the Cambridge P-Series had achieved very satisfactory performance figures and they were generally considered to be good amplifiers. In the U.S.A. the Crown DC300 had achieved an almost theoretically perfect specification and was hailed as "State of the Art."


However, the first crack to appear was caused by new loudspeaker designs. Some had very demanding impedance curves which in some cases presented a 2 Ohm load to the amplifier. Such a low value of load (almost a short circuit to some minds!) operated protection circuits in many amplifiers, limiting the current to protect the output transistors.

The operation of these caused a very unpleasant "clipping" sound in some cases and even strange "clicks" and "bangs" in other cases. Thus alerted it became apparent to some designers that conventional protection circuits were turning partly-on quite frequently in the course of a piece of music and so giving a sort of premature clipping action.

Without any doubt the best results are achieved when the output stage is devoid of any protection AT ALL. The output stage should be designed to deliver all the current a load demands without limiting. Consider the reproduction of a bass drum. If the amplifier starts to limit the start of the "thump" the sound pressure will collapse and the bass-drum will appear to have no body and thus sound unrealistic.

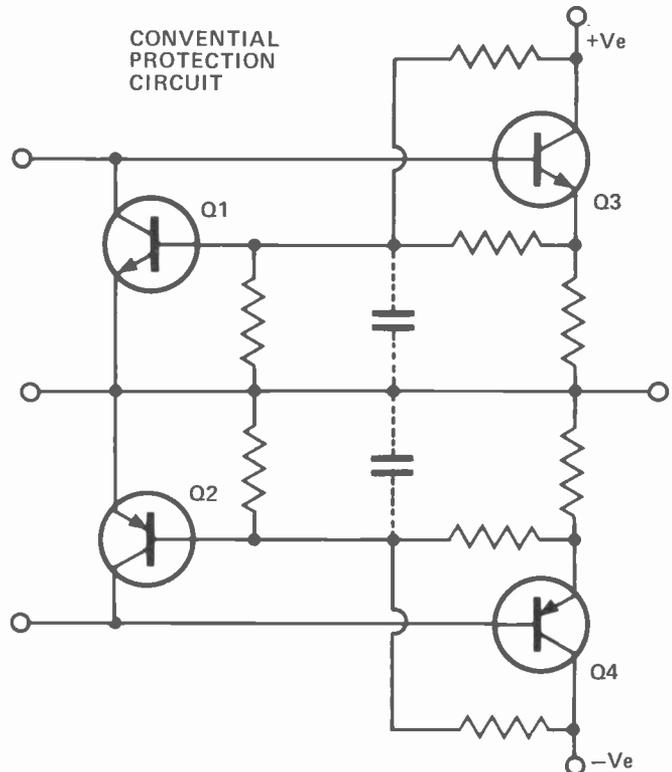


A study of the circuit of a conventional V-I protection circuit will show that as the protection transistors turn-on they become a 'non-linear resistor' across the bases of output transistors Q3 and Q4 and as such create unpleasant distortion. One solution tried by some companies was to slug the bases of Q1 and Q2 with a capacitor to provide a time-delay to prevent the protection operating except during a sustained short-circuit.

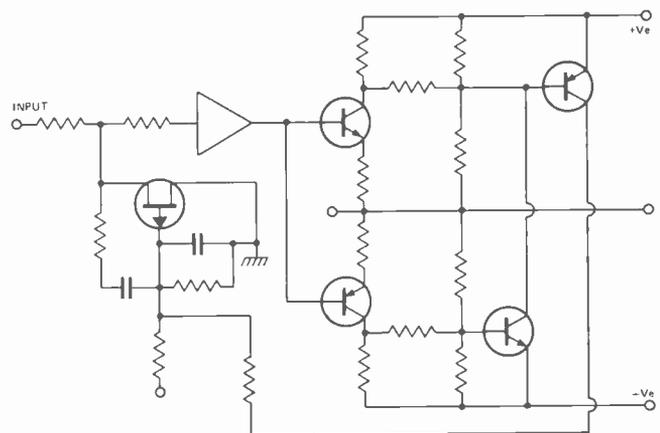


In this protection circuit the FET starts to turn-on when full-power is delivered into a 2 Ohm load. The main advantage over a conventional protection circuit is that the limiting is "soft" (i.e. very gradual) and thus audibly acceptable and secondly that the distortion is much lower — and still only about 0.1% at limiting.

The output-stage should ideally be able to sink the full energy of the power-supply until its regulation causes the current to limit progressively. So in a good amplifier design the output-stage and the power-supply must be designed as a single item and not as separate circuits. Several amplifiers are designed like this. The Lecson AP3 Mk II, the BGW models 500 and 750, and the Mission Power Amplifier. The Lecson AP3/11 can, for instance, deliver nearly 20 Amps to the load before the mains fuse blows and the BGW model 750 even more.

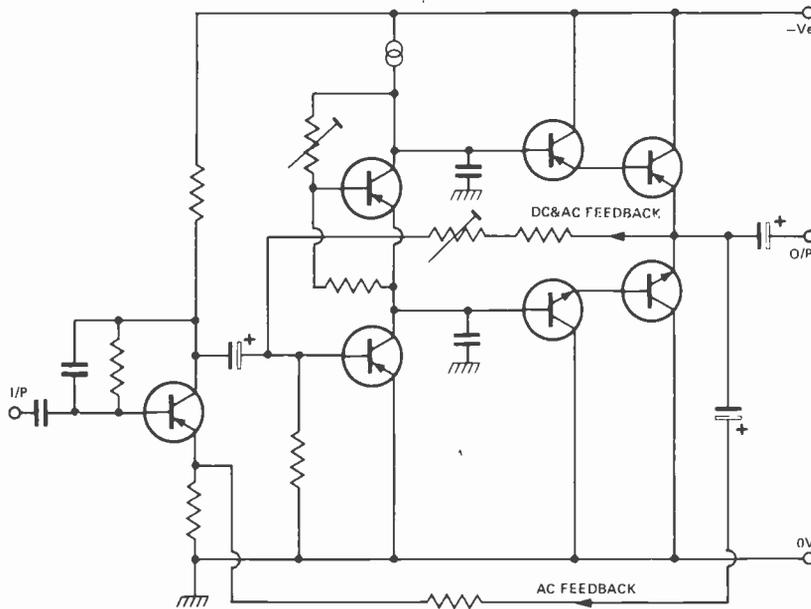


Circuit diagram showing a typical circuit which would prove to be prone to DC instability when in use. Note that separate paths exist for AC and DC feedback.

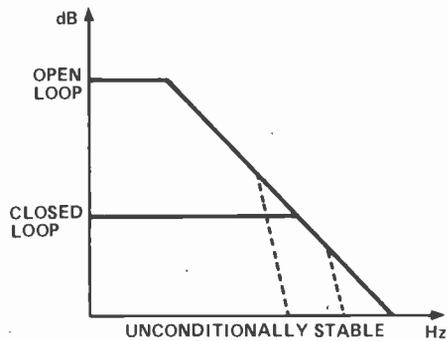
If the amplifier now has to drive a capacitive load eg. electrostatic speakers, or complex crossover networks; another pole is added at the output eg. —



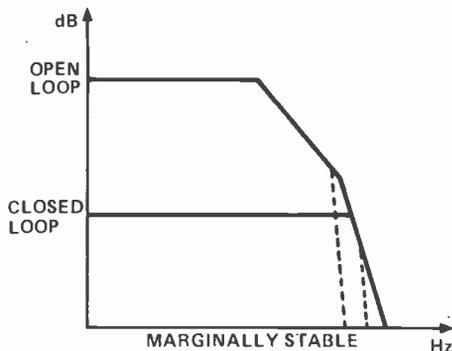Above: Effect of adding an extra pole at the output of an unconditionally stable amplifier, such as might be added by a complex crossover network. Below: Same condition applied to marginally stable type. Phase shift now borders on 180°, i.e. oscillation.



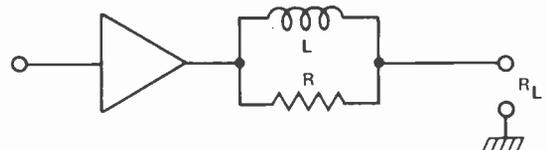In the case of the inconditionally stable amplifier the only ill-effect will be some "ringing" in the closed loop step response — but in the case of the marginally stable amplifier it may go completely unstable. The most popular "belt and braces" solution to this problem is to fit a resistor-inductor network at the output to "cancel-out" the effect of the capacitive loading, thus.




Ever wondered what this circuit in the output of an amplifier is for? Wonder no more — it's to aid the output stage in handling a capacitive loading by partially cancelling the effect.


It is interesting to note that some marginally stable amplifiers omit those components as, in the practise, most speaker cables have sufficient resistance and inductance. However, some of the new "Super-Cables" (Litz and Lucas, etc) have a very low resistance and almost no inductance but some capacitance — and their use with certain amplifiers has caused instability, with the amplifier (or speakers) eventually blowing-up!

ETI

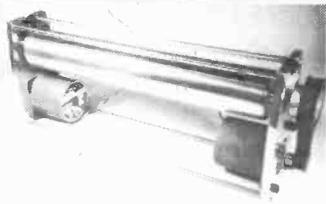
Next month Stan Curtis goes on to consider the effects of phase and bandwidth (amongst other odd things) upon amplifier performance and asks what do we want from an amplifier? — The answer may surprise you all!



BARREL TYPE X-Y PLOTTER ASSEMBLY

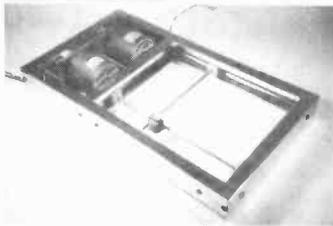

X-Y PLOTTER ASSEMBLY

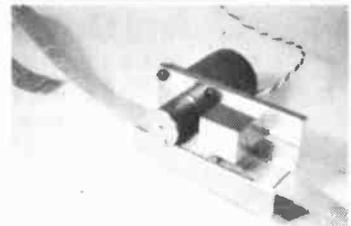

PAPER TAPE READER ASSEMBLY

BARREL TYPE X-Y PLOTTER ASSEMBLY

120V Stepping Motors. Provision for Pen (Pen NOT supplied). As Picture **£55** ea. Alternative motor for non-reversible requirements. Recorder/Printer applications etc **£48** ea. P&P both versions **£2.50**.

X-Y PLOTTER ASSEMBLY

Due to large purchase we have an assembly consisting of frame with X & Y assemblies (no pen — but provision provided). Two high quality STEPPING MOTORS Bed size 12" x 9" Motor options 120V only **£39.50** ea. 120V (can be changed to 12/24V), data supplied **£46.50** ea. 12/24V **£64** ea. P&P all versions **£2**. 10% Price Increase on orders after July 14.

PAPER TAPE READER ASSEMBLY

Rigid alloy frame. 8 hole. High quality stepping motor Directly driven from 120V reads 30 char. per sec. Reversible. Can be DC Stepped faster or slower. Steel paper guides. Without Opto-sensor **£27.50** ea. With Optics **£45** ea. P&P **£2**.

STEPPING MOTORS ONLY

Motors as used in plotters etc. All motors 200 steps per revolution. 20 oz. inch torque. 120V 1000-0-1000 ohm. Can be changed with care to 12/24V. Data supplied **£8** ea. P&P **£1**. Supplied for 12/24V operation **£13** ea. P&P **£1**. Just think about the uses!

NOW—INCREASE AREA GIVEN TO

PICK-A-PACK AT 50p per lb

LARGER VOLUME OF NEW COMPONENTS YOU CAN'T AFFORD TO MISS

OSCILLOSCOPE TUBES

Brand New Boxed — Carriage all tubes **£3.25**. Telequipment S52, **£10** ea. D51, **£15** ea. S42, **£10** ea. D53A, **£20** ea. D52, **£15** ea. S31, **£10** ea. Bradley 200, **£85** ea. Advance OS3000, **£85** ea. GEC types 924F, **£25** ea. 924E, **£17.50** ea. 1496B, **£75** ea. Brimar D13-51GH, **£65** ea. D10-210GH/32, **£40** ea. D13-46GM, **£35** ea.

NOT BOXED — NEW — WARRANTED. Telefunken D14-131 replacement for Soloran CD1740, Cossor CDU150, S.E. Labs SM112 and GEC/MOV 1474 at **£55** ea.

LOOK AT THESE PRICES

ROTRON CENTAUR FANS. Size 4.5" x 4.5" x 1.5" 115V 5 blade. **£4** ea. P&P 75p.
Min. PLUG-IN type RELAYS. Plastic covers. 2-pole c/o 24V 25p ea. P&P 15p.
CROUZET/MURTEN SCHWEIZ MOTORS. 110V 50HZ 4 rpm. Gear box can be removed. 75p ea. P&P 75p.
FRAMCO MOTORS. 115V 50HZ Input single phase. 1/12th HP. 1450 rpm; on silent mount. New condition **£2.75** ea. P&P **£1.75**.
PYE DYNAMICS THICK FILM 1MHZ Clocking Oscillator. 5V supply. Size 19x25x6mm. Drives one TTL load. 72p ea. P&P 15p.
COMPRESSOR UNIT. Compact. 115V 50HZ single phase 1.5A continuous 1425 rpm. Outside piston housing approx 3" **£18** ea. P&P **£12**.
BROOKE CROMPTON & PARKINSON extractor fan assembly 240V operation **£2.75** ea. Carr **£3.25**.
MAGNETIC DEVICES. Plug-in RELAYS 240V AC. 3-pole c/o. Heavy duty 10 amp. Complete with base. Ex brand new equipment. NOT USED. 3 on sub assembly **£2.50** P&P **£1** or **£1.25** ea. P&P 45p.
SMALL MAINS TRANSFORMER 240V Pri. 12V 100MA sec. 60x40x42mm 50p ea. P&P 75p.
G.I. BRIDGE RECTIFIER type W01 (ideal for above) 17p ea.
FAIRCHILD FND10 7 segment display 0.15 Red. Common cathode 65p ea. P&P 15p.
MULLARD TUNER MODULES — with data
LP1171 combined AM/FM IF strip 10.7MHz. **£3.50** ea. P&P 50p.
LP1179 FM front end with AM tuning and 87.4MHz to 104.5MHz tuning. 10.7MHz IF. **£3.50** ea. P&P 50p.
The Pair **£5.75** P&P 75p.
POWER UNIT MODULE containing 2 small, 3 med & 1 large ferrite cores, 3-T03 power transistors, caps, resistors, high powered diodes, 9 transistors, 3 min fuse holders, etc. **£1.50** ea. P&P **£1.25**.
GENERAL ELECTRIC OPTO-ISOLATORS type H15VX504. 65p ea. P&P 15p. 10 for **£5**. P&P **£1**.

★ TRANSISTORS/DIODES/RECTIFIERS, ETC. ★

Guaranteed all full spec devices. Manufacturers Markings.
At 5p each
 BC147; 2N3707; BC172B; BC251B; BC348B; BC171A/B; BC413; D10; BC1B2; BAX13; 1N937; BA102BE; BZX83; TIS61; 2N5040.
At 10p each
 BFX85; 1N4733A; SN7451N; BYX10-15KV 0.36A; BYZ10 15p ea. TIP30 — 20p ea. TIP34A — 50p ea. BD53B — 40p ea. Heavy Duty Bridge Rectifier — 20p ea. CA3123E — **£1** ea. BDY55 — **£1** ea. 2N3055 — 40p ea. TIP31B 12p ea. TBA560CO **£2** ea. 1N4436T-T03 Flat mount 10A 200piv **£1** ea. 2N5879 with 2N58B1 Motorola 150W Comp, pair **£2**.
 BD535; BD538 Comp. pair — 75p.
 Linear Amp 709 — 25p ea.
 High Speed Voltage Comparator 710 — 15p ea.
 P&P Extra on all items.
FINNED HEAT SINK — single T03 — size 4 3/4" x 3 1/4" **50p** ea. P&P 75p.
 Texas Bridge Rectifier 5SB05-50V 5A 60p ea. P&P 20p.
MOTOROLA POWER TRANSISTORS type W0993/441. T03 Min voltage 500. 20p ea. P&P 15p.

TELEPHONES. Post Office style 746 Black or two-tone **£6.50** ea. Modern style 706 Black or two-tone grey **£4.50** ea. P&P **£1** each. Old black style **£1.50** each. P&P **£1**.
HANDSETS only 706 style **£1.75** each. Older style **£1.1**. P&P 75p.
TELEPHONE EXCHANGES. Eg 15-way automatic exchange only from **£95**.
 ★ 1000F Feed thru Capacitors 10 for 30p. P&P 15p.
HIVAC Miniature NEONS. App 60V Brand New 10 off 20p. P&P extra.
GRATICULES 12 x 14cm high quality plastic 15p ea. P&P 10p.
LARGE RANGE OF ELECTROSTATIC VOLT-METERS. From 0-300V 2" **£3**, to 20KV max. General guide 5KV 3 1/2" **£5**. Thereafter **£1** per KV. P&P 75p.
DON'T FORGET YOUR MANUALS. S.A.E. with requirements.

POWERFUL MINIATURE GERMAN 12V REVERSIBLE MOTOR. No load current 70MA, excessive load 400MA. Size 1 1/2" x 1 3/16" dia. Shaft 5/16" x approx 1/16" dia. 50p each. P&P 40p.

A MILLION MUST GO

HIGH NOISE IMMUNITY LOGIC. DUAL IN LINE 16-PIN CERAMIC. 12V Rail. Conventional TTL package. Guaranteed full spec. devices. Full data. 2p ea.
MIXED PACKAGE — **£1** P&P 25p.

BUILD YOUR OWN BUS

Approx 1 1/2 metre multiway ribbon cable terminated each end with a 50-way female edge connector. Takes 0.1 printed circuit board **£2** ea. P&P 75p.

LOOK AT THESE PRICES

BURROUGHS 9 digit PANAPLEX numeric display. 7 segment 0.25" digits with red bezel. **£1.95** ea. P&P 30p.
MINIATURE NIXIE TUBE type ITT 5870ST. Digit size 0.5". Wire ended. 50p each P&P 20p. 4 for **£1.75** P&P 35p.
TRANSFORMERS 115V AC input. Secondary 30V and 2.6V 10VA. 50p ea. P&P 50p.
CALCULATOR CHIP. GENERAL INSTRUMENTS type GIMT4 with Data. **£1.60** ea. P&P 20p.
21-WAY SELECTOR SWITCH. Single pole with reset coil 240V AC coils. Additional switch contacts for auto reset etc. **£1.75** each. P&P 75p.
SNAIL BLOWER 110V AC 500 MA. Brand new by Airflow Developments. Quiet and very good looking. **£3.50** ea. P&P **£1**.
POTTER & BRUMFIELD 18-48V DC Relay. 3 pole c/o. Heavy Duty. Plug-in type with base 50p ea. P&P 25p.
MINIATURE KEYBOARD. Push contacts. Marked 0-9 and A-F and 3 user definable keys. **£1.75** ea. P&P 35p.
MULLARD CORE LA4245 at 15p ea. P&P 10p.
CLARE REED RELAYS 24V DC Coil. Single pole make. Size 1 1/8" x 7/16" x 7/16" at 25p ea. P&P 10p.

ITT-CREED

Punches and Prints on 3/8" paper. Complete with Power Supply Solid State. Size 15x11 1/4"x22" deep **£13** ea.

TRIPODS WITH PAN AND TILT HEAD

will take 56lb load **£22.50** ea.

EX-MINISTRY MARCONI 0-6 WATTS

Multi Range. Multi Impedance POWER METERS **£25** ea.

MARCONI VALVE VOLTMETER

TF428B NOW **£12.50** ea.

1/2" MAG TAPE

Approx. 2,000 ft. NOW 25p each. P&P **£1**. Or 5 for **£1**, carr. **£2.75**.

FOR THE VDU BUILDER tube M28-13GH 23 x 17cm at **£12**. Base connections supplied. Heads for PERTEC 6000/7000 — enquiries.

PLESSEY VDU. No keyboard — weird electronics. **£60** ea.
TELETYPE KSR33 from **£275** each. Polished Wooden Cases to take normal 'QWERTY' KEYBOARDS, or can be carefully cut to take any size **£3** each. P&P **£1.50**.
 Odd 33RO not cased — can be demonstrated **£160** ea.
 Limited quantity of 35R0 — 20ma loop — can be changed to ASC11 code (3 hours' simple work and £10 parts) **OUR PRICE EXCLUDING PARTS REQUIRED £70** ea.

Ex-Ministry Teletype Punches 8 level 110 char per sec. **£50** each.
AMPLEX TM7. Nice condition **£225**.
TELETYPE ASR33 with 20ma loop. Good condition. **Special low price £395** ea.

Minimum Mail Order **£2**. Excess postage refunded. Unless stated — please add **£3.25** carriage to all units **VALUE ADDED TAX** not included in prices — Goods marked with ★ 12 1/2% VAT, otherwise 8% Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order. Open 9 a.m. to 5.30 p.m. Monday to Saturday



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS (near Technical College, King's Road). Tel: Reading 582605

AUDIO AND TEST EQUIPMENT CENTRE

BRAND NEW STOCKS — NO RECONS.

Only regular stocks listed — other makes and models available.

Telephone your order with Access and Barclaycards



4D10A



DM2



SWR

LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm


SCOPES

CI-90 1MHz single beam with probes	79.50
MS15 15MHz Batt./mains, portable	260.00
4S6 Scope x 6MHz single beam	129.50
4D10A Scope x 10MHz Dual beam	205.00
4D25 Scope x 25MHz Dual Beam	310.00

PROBES x 1 x TD12.95, x 10 9.95 x 1 7.95. For 4S6/4D10A/4D25 and Gould Advanced

DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit	52.90
DM35 Sinclair Pocket 3 1/2 digit	29.95
DM2 Sinclair Portable 3 1/2 digit	48.95
(Mains adaptors 3.95, DM2 carrycase 6.48)	
LM3A 3 Digit Miniature with large LED displays	79.50
LM3.5A 3 1/2 Digit Recharge Batts and charger 17 ranges	92.50
LM40A 4 Digit	136.00
LM300 3-digit Miniature battery operated 17 ranges	79.50
LM350 3 1/2-digit with LCD displays 1 1/2 A/mV resolution	93.50

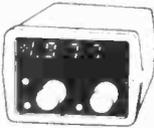

LM3.5A

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/IT1-2/T12/TM3A (TM3 AC volts only), some with AC current etc.

TM11 incredible 120 Range Electronic Multi-meter	130.00
TM3B AC Microvoltmeter 3MHz > 4 Megohm	117.50
TM6B Broadband voltmeter 300KHz-400MHz	178.00
380TR 100k/volt 23 Range (plus transistor checker), Large scale	32.50
PRDE 20k/volt 26 Range, Large scale	29.95
70B1 50k/volt 36 Range Multi-meter	22.50
Tmk500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	19.95
680R 20k/volt 52 Range Pocket Multi-meter	34.50
7200 20k/volt 22 Range Double Multi-meter	16.95
Micro80 20k/volt 26 Range Pocket Multi-meter	17.90
IT1-2 20k/volt 16 Range Popular Multi-meter	10.95
LT22 20k/volt 19 Range Pocket Multi-meter with carry case	14.60
T12 5k/volt 13 Range Pocket Multi-meter	8.50
T1/IT1 101 1k/volt 12 Range Pocket Multi-meter	8.95
K200 FET Multi-meter 38 Ranges 3MHz	77.70
GT101, 20k/Volt 23 Ranges/Transistor Checker/Continuity Checker	19.95

AVO 8s and a large range of replacement tests leads in stock

GENERAL EQUIPMENT

SWR50 SWR/Power Meter	19.50
TE200 500MHz RF Gen	49.50
LP30 30MHz Low Pass Filter	4.95
CX3A 150watt 3-way AE Switch	7.50
OC25KV 100 Meg HV Probe	11.95
9 Value CAP Subs Box	2.95
FX2000 Xtal Marker	11.95
LC1 Univ Logic Checker	26.00
CT1 Continuity Checker	21.00
MOD83 Signal Injector	7.50
TT169 In Circuit TR Checker	49.95
LB1 Transistor/Diode Checker	18.95
3101 Clamp Meter 0/1 K ohm 0/150/300/600 AC Volts 0/300 Amp	29.50
C3042 SWR & PS Meter	9.95
MS319 2x100 Watt Audio Watt Meter	17.50
500V Megohmmeter 500 Megohms	48.00
1000V Megohmmeter 1000 Megohms	55.00
2 1/2 Amp Variable Transformer	18.00
5 Amp Variable Transformer	29.00
10 Amp Variable Transformer	40.00
TM12 Multi-range Transistor/Diode checker, Adjustable Volts etc.	130.00
100 Range Capacitance Decade	48.60
1 ohm - 11 Meg Resistance Decade	48.60

LEVEL RC OSCILLATORS

TG152 Series RC Oscillators	
Sine/Square output, 3Hz-300KHz	
TG152D	69.95
TG152 Dm (with meter)	117.50
TG200 Series RC Oscillators	89.95
Sine/Square output, 1Hz-1MHz	
TG200D	93.85
TG200 Dm (with meter)	112.50
TG200 Dmp (Meter & Fine control)	117.50
TG66A Digital Sine Wave Decade control	
0.2Hz-1.22MHz	249.50


CSC LOGIC PROBES AND MONITORS

LM1 Monitor	31.00
LP1 Probe 10MHz	33.48
LP2 Economy 1.5MHz	19.44

ALL PRICES INCLUDE VAT
Correct at time of preparation

EXPORT AND E & O E
QUANTITY DISCOUNTS

MICROPHONES, SPEAKERS AND COMPONENTS LARGE RANGE IN STOCK

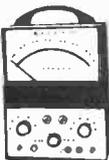


TM11



TMK500



FM7 7 Digit 60MHz Recd. Batt. Freq. counter
MAX 100 100 MHz 8 digit batt operated counter £83.75

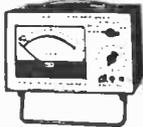

TM3

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS


301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.

ELECTRONIC COMPONENTS AND EQUIPMENT

FREE CATALOGUE

SEND STAMPED (12" x 6")
ADDRESSED ENVELOPE (MIN 9" x 6")
FOR YOUR COPY NOW

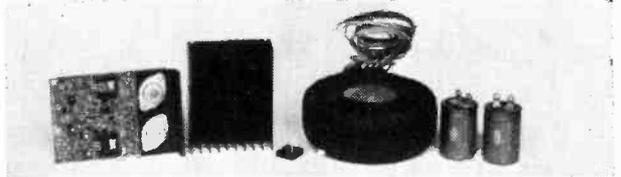TWO NEW SUPERMODULES 170W INTO 4 OR 8 OHMS



By popular demand we have designed higher powered versions of our well known modules. The CE 1704 which gives 170W into 4 ohms and the CE 1708 which gives 170W into 8 ohms are physically similar to the original types and have the same combination of compatible performance features which makes CRIMSON amplification audibly superior to the competition and the only choice if you have an ear for music. We have also produced suitable power supplies which again use our superb TOROIDAL TRANSFORMERS, only 50mm high, with a 120-240 primary and single bolt fixing.

Write or phone for more information and biased opinions.

	Home	Europe	T.H.O.	Typically <.01% any power, 1kHz, 8 ohms
POWER AMPLIFIER MODULES				
CE 608 60W/8 ohms 35-0-35V	£16.30	£16.60		
CE 1004 100W/4 ohms 35-0-35V	£19.22	£19.30		
CE 1008 100W/8 ohms 45-0-45V	£23.22	£23.00		
CE 1704 170W/4 ohms 45-0-45V	£29.12	£28.46		
CE 1708 170W/8 Ohms 60-0-60V	£31.90	£31.04		
TOROIDAL POWER SUPPLIES				
CPS 1 for 2 x CE 608 or 1 x CE 1004	£14.47	£18.40		
CPS 2 for 2 x CE 1004 2/4 x CE 608	£16.82	£20.57		
CPS 3 for 2 x CE 1008 or 1 x CE 1704	£17.66	£21.35		
CPS 4 for 1 x CE 1008	£15.31	£19.18		
CPS 5 for 1 x CE 1708	£22.68	£26.50		
CPS 6 for 2 x CE 1704 or 2 x CE 1708	£23.98	£27.70		
HEATSINKS				
Light Duty 50mm 2°C/W	£0.90	£1.30		
Medium Power 100mm 1.4°C/W	£1.60	£2.40		
Osico/Group 150mm 1.1°C/W	£2.30	£3.65		
THERMAL CUT-OUTS				
Recommended for improved reliability				
70°C for use with free air heatsink	£1.60	£1.90		
40°C for use with fan cooled heatsink	£1.60	£1.90		

CRIMSON ELEKTRIK


Please note our new address and telephone number: Stamford House, Stamford Street, Leicester LE1 6NL. Telephone (0533) 537722.

Home prices include V.A.T. and postage. C.O.D. 90p extra, £100 limit. Export no problem. European prices include carriage, insurance and handling, payment in Sterling by bank draft, P.O., International Giro or Money Order. Outside Europe, please write for specific quote by return. Send SAE or two International Reply Coupons for full literature. Favourable trade quantity price list on request. High quality pre-amp circuit 20p.

ALMARC & VECTOR GRAPHIC

"Nobody Does It Better"

INTRODUCING THE VECTOR 1 COMPUTER

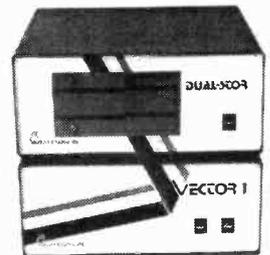

- S-100 BUS
- HIGH QUALITY
- LOW PRICE

Whatever your application Vector Graphic and Almarc have the answer. Mainframes, Memory, I/O Boards, Disk Systems, Processors, and the unmatched High Resolution Graphics board. Send for our catalogue today.

OTHER PRODUCTS:

Solid State Music, including 8k Static Ram Board. £98.95.

ALSO:

Cromenco, North Star, Dynabyte, and, our best product, "Service".

Write for details to:

ALMARC DATA SYSTEMS LTD.
24 CHESTERFIELD DRIVE
BURTON JOYCE, NOTTINGHAM
TEL. 0602 248565

LCD DIGITAL MULTIMETER

A Digital Multimeter is, in our opinion, a must in any well equipped electronics workshop and A. S. Webb BSc, of Watford Electronics, has designed just such a meter that can be built for less than half the cost of an equivalent commercial unit.

PSST! — WANT A DMM that has five DC and five AC ranges of both voltage and current as well as six resistance and four capacitance ranges at a price that is far less than any equivalent commercial unit? You'll have to build it yourself of course—but then that's half the fun and if you follow the construction information exactly and make use of the calibration service we have arranged, your meter should perform accurately and reliably for many years.

The basis of the DMM is the Intersil 7106 digital panel meter IC (featured in October / March '77) which has excellent linearity and auto zero facilities and directly drives the 3½ digit Liquid Crystal Display. The low current consumption of this device enables the unit to be battery powered and hence completely floating from the circuit under test.

This project is aimed at the more experienced constructor due to the fairly high component density and reasonably intricate switch wiring, and should not be attempted unless a soldering iron bit of less than ¼in and small pliers and cutters are available.

Handling Of Components

The usual precautions must be observed when handling the MOS devices used in this project, but it may not be realised that other components are liable to damage through mal-treatment. The 1% precision resistors should be handled with respect, their wires bent with pliers and soldered in as quickly as possible, since excessive heat may permanently alter their resistance values and the switch wafers should be handled with care prior to ▶

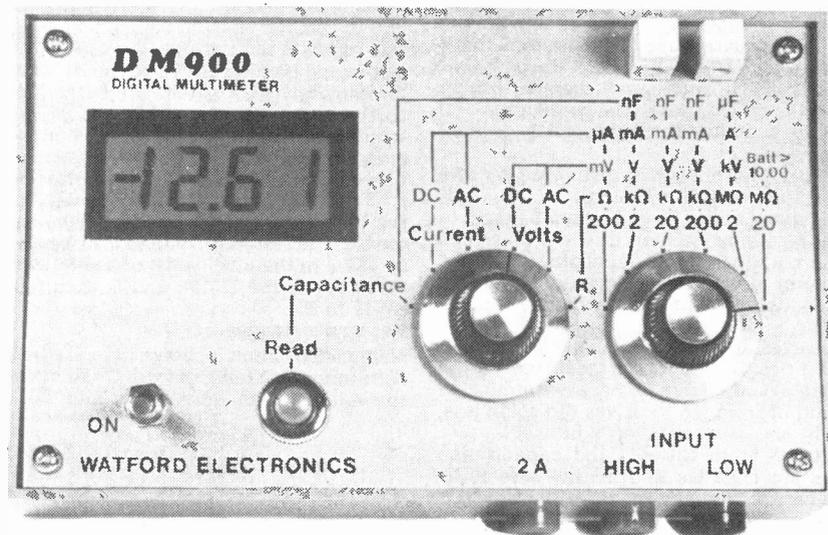


Fig. 1. View of the final unit. Note, in order to ensure that the input sockets do not foul the PCB yet allow the probes to be inserted, the sockets should be mounted 10mm from the bottom of the case.

SPECIFICATION

Input Impedance	10M
Display	3½ digit LCD
DC & AC volts	200 mV to 1 000 V in 5 ranges, resolution to 0.1 mV
DC & AC current	200 uA to 2 A in 5 ranges, resolution to 0.1 uA. Max. voltage drop 200 mV. RMS reading on sine waves only.
Resistance	200R to 20M in 6 ranges, resolution to 0R1.
Capacitance	2n0 to 2u0 in 4 ranges, resolution to 10p
Accuracy	1% ± 1 digit (on prototype)
Overrange Indication	1 in MSD, other digits blank
Polarity Indication	
Autozero	
Display Test	
Input Protection	
Power Consumption	5mA average, single 9 V supply

HOW IT WORKS

DISPLAY DRIVES

The segments of the LCD display are directly driven by the ICL7106 (pins 2-19 and 22-25) in conjunction with pin 21 (backplane drive). Liquid Crystal Displays will become damaged if a DC voltage is continuously applied to them and must be driven with an AC signal. To turn on a segment a wave form of equal amplitude but 180 degrees out of phase with the square wave backplane drive must be applied to that segment.

The 7106 generates the appropriate segment drives for all digits internally, but the drive signals for the decimal points and polarity indication segments are generated by external circuitry.

The decimal point drives are provided by the components around IC2C,D and IC3D. These are two input exclusive OR gates driven by the backplane square wave and by voltages from the range switch.

Consideration of the truth table of an exclusive OR gate will show that with the backplane square wave applied to one input we can produce an output from the gate that is the inverse of this signal (segment on) by taking the other input to the gate high.

SW2D activates the appropriate decimal point.

Polarity indication is provided by the circuitry around IC3A,B and C.

The signal at pin 20 of IC1 can be used to drive the minus segment directly, that is its output is a square wave out of phase with the backplane drive when a negative signal is applied to the 7106, in phase when the input is positive.

However, in this circuit we provide a + sign for positive inputs (formed from - and - segments) and a - sign for negative inputs. As the output from pin 20 drives the colon it is, usually, necessary to invert it in IC3B.

Outputs from the AC and capacitance stages are negative and in this case IC3D takes care of blanking the polarity display.

The resistance range is arranged to show only the colon.

The control inputs of the decimal point gates and the wiper of SW1G are connected to IC1 pin 37. This pin is normally held at a voltage 5V below V+. By taking this pin to +V supply all segments of the display will be "turned on". This display test, enabled by shorting the two pins on the PCB, should only be activated for a few seconds as prolonged operation will drastically reduce display life.

A stable source of reference voltage is required at many points in the DMM circuit. The 7106 provides just such a voltage, PIN 32 (common) being maintained at a voltage 2.8 V below the positive rail.

This reference voltage, as well as being used elsewhere in the circuit, provides the basic reference voltage for the 7106's input circuitry. The 7106 is calibrated to a 200mV full scale — to accomplish this 100mV potential difference must be set up between Ref Hi and Ref Lo (pins 36 and 35 respectively).

This voltage is derived from the potential divider formed by RV1 and R26.

C9 and R27 set up the 7016's internal oscillator frequency while C7, 8 and R25 are concerned with the auto zero and polarity circuits.

Having dealt with the components intimately associated with IC1 we now move on to deal with the rest of the DMM circuit.

DC Voltage & Current Ranges.

SW1 is the function switch and when set to DC volts, the five DC voltage ranges are


selected by SW2B, which is connected to the input alternator. The input resistance is always more than 10M, and exact division is achieved by using precision 1% resistors throughout the chain. The voltage selected by the wiper is fed via SW1F and a 1M resistor to pin 31. This resistor and a capacitor to ground serve to filter any noise, and also to limit the current fed into the input should an overload voltage be applied. With SW1 set to DC current ranges, the input current is passed through one of the five current measuring resistors. The maximum voltage across one of these is 200 mV at full scale. The 2 A range is connected by a third socket on the front of the case, since a few milli ohms of switch contact resistance would produce a significant error. The unit is protected from excessive currents by a 2 A fuse in the common line.

AC Voltage + Current Ranges

On AC voltage ranges, a 10nF capacitor is switched in series with the input line to remove any DC component present. The signal is fed through the attenuator as before and then via SW1E to the AC converter. Similarly AC currents are fed via SW1E to the AC converter. This is a precision rectifier IC4 using a TL081 J-FET input op amp, so that there are no problems with input bias current. The gain of the circuit is set by RV2 and the negative component sampled by the 10M resistor and filtered by 100nF capacitor C4. The resulting voltage may be RV2 to be equal to the RMS value of a sine wave to the input of the DMM, and is then fed via SW1F to IC1.

Resistance Ranges

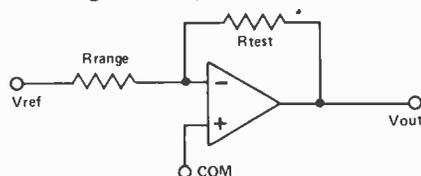A simplified circuit is shown here, the op amp IC6 is another TL081 and will try to maintain the voltage at its input at common voltage.



Hence the output voltage must be:

$$V_{out} = R_{Test} \cdot \frac{V_{Ref}}{R_{Range}}$$

and is proportional to the resistor being measured (R_{Test}).

V_{Ref} is derived from a potential divider between +Ve and common, and is set by RV3. IC5 is a voltage follower, and is fed via SW1D to the bottom of the resistor chain in the attenuator. SW2A selects the range in reverse order to the voltage ranges, and its wiper is connected to the input socket by SW1A and to the input of IC6 by SW1C and another R-C network for filtering and protection. The output of IC6 is boosted by an emitter follower Q1, since the current on the 200 ohms range is quite high, and then fed to the other end of R_{Test} via SW1B. The offset voltage of the op-amp is zeroed by RV4, but a small offset from zero exists on the 200 ohm range because of the switch contact and the fuse resistances. The voltage output proportional to R_{Test} is attenuated by about ten times and fed to IC1 via SW1F.


BATTERY TEST

The unused position of SW2 on the DC voltage range is fed from a potential divider between common and the battery negative (OV) rail so a voltage governed by, though not proportional to the battery voltage is fed to IC1. The resistor values are arranged to

give a reading of 10.00 when the battery voltage has dropped to 7 volts, but at other voltages the readings are meaningless due to the 2.8V reference voltage.


Capacitance Ranges

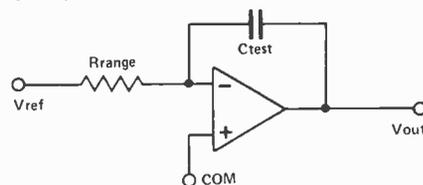Using a simplified circuit, if V_{Ref} is joined to V_{Out} , then V_{Out} will equal the common voltage since the op-amp is acting purely as a voltage follower. Hence C test is



fully discharged. If V_{ref} is now suddenly taken to a positive voltage, the output will begin to ramp negative at a rate determined by R_{Range} and C_{Test} , and for a given R_{Range} the time taken to reach a given negative voltage is determined by and is proportional to C_{Test} . In practice, a quad J-FET op amp type TL084 is used for IC9. The first stage IC9A is the integrator just described and in the rest state with Q2 off, the output and input are joined by the range resistor selected by SW2E. IC7 is a hex C MOS inverter which produces the timing control signals. IC7A and B form a monostable, triggered by pressing the READ button SW4. Having connected C Test but before pressing SW4, the op-amp will have discharged C_{Test} as above. IC8 is a CMOS analogue switch type 4016, which in the rest state has both stages OFF. IC9D is another integrator which due to the very high input impedance of the TL084 and low leakages of the 4016 will hold any voltage on C17 for many seconds. When the button is pressed, the output of IC7B goes low, unaffected IC7D and E but making the output of IC7C go high, thus turning on IC8B shorting the capacitor and making the op amp output equal to common voltage. At the end of the monostable period, C17 will be fully discharged and IC7B output goes high, in turn turning off IC8B. Simultaneously IC7D and E are triggered by the positive edge and IC7D output goes low, turning on Q2 and hence connecting the range resistor to the positive rail, causing IC9A output to start ramping negative. IC7E drives IC7F output high, and causes IC9B output (which was previously at the +Ve rail) to go negative from the common rail an amount determined by the two resistors R45 and R46. This voltage is an exact multiplication of the common to +Ve voltage, and is fed to the inverting input of IC9C, a comparator. Since the non-inverting input is fed from IC9A output which is still ramping negative, the output of IC9C switches positive, turning IC8A on and hence connecting the input of IC9D to the +Ve rail via a resistance. Hence IC9D output will also start to ramp negative. Remember this has all happened within microseconds of the end of the monostable period.

After a while, IC9A output will go more negative than IC8A and isolates the input of IC9D completely. The voltage on IC9D output is proportional to the value of C Test, and will only be discharged by leakage. This voltage is fed via an attenuator to SW1F and then to IC1. Since IC9 is a quad op amp, no provision is made for offset nulling, so a negative current is fed into the attenuator to counteract any offset. Calibration is achieved by adjusting the current fed into IC9D input during the measuring period by RV5.

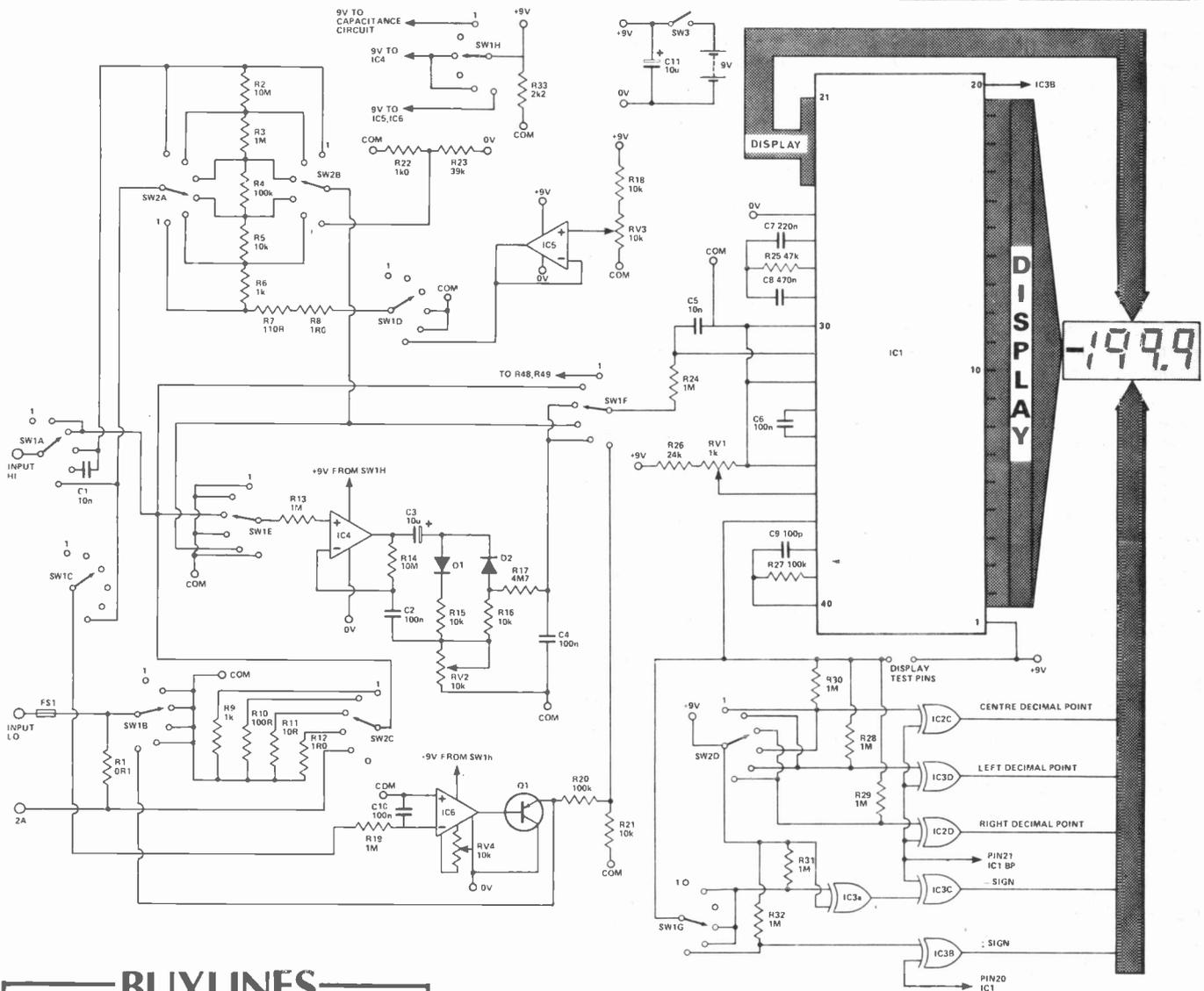


BUYLINES

Watford Electronics, 33 Cardiff Road, Watford, can supply a complete kit of parts for this project. The kit, which includes predrilled case and punched and screened front panel, will be sold at a special introductory price of £49.95 plus 8% VAT and £1 p&p and ins. Test Leads are available for an additional £1.50.

Watford are also to offer a calibration service. This service will apply to **working** units only and will cost £5.75 all inc.

Fig. 2. Full circuit diagram of the DMM excluding the capacitance measuring circuitry. R1 and FS1 are not mounted on the main PCB. Note that although a protection network is incorporated, it is wise to ensure that a high range is selected before the meter is applied to the circuit under test.

Fig. 3. Below, left and right, circuit diagrams of the capacitance section, a patent has been applied for in respect of this design.

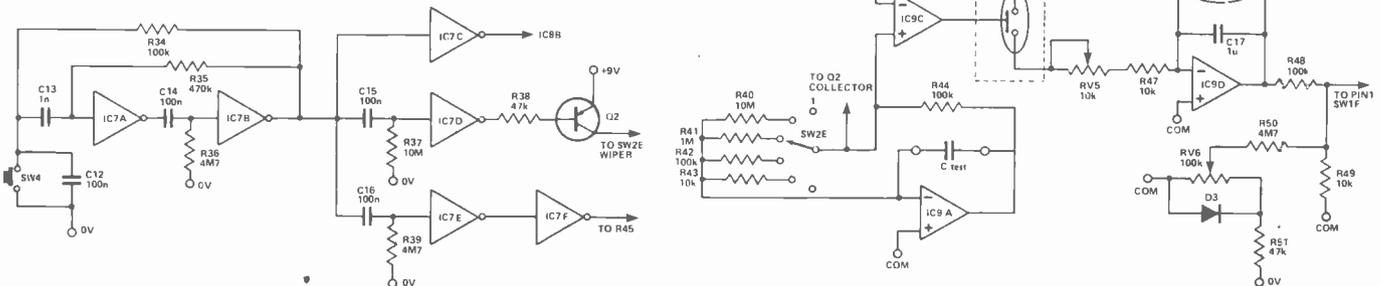

assembly and the wipers only rotated to position 1 if necessary since it is possible to bend fixed contacts without noticing, the damage not being discovered until testing of the DMM takes place. To replace a damaged wafer after assembly is complete is an extremely difficult operation.

The most delicate part by far is the display itself. This should be examined carefully for defects in the glass and then kept in its cardboard wrapper until ready for use. It must be pressed into its socket with extreme care, and easing the soldercon pins with a piece of tinned copper wire before insertion is recommended.

Note the LCD display should not be subject to temperatures greater than about 60°C and should not be exposed to strong sunlight for any period of time.

Construction

If it is hoped that a DMM will result with a similar specification to the prototype, the parts list must be followed closely, as must these instructions. The use of a double sided board makes construction a less onerous task than would have been the case with a single sided design. However, to avoid the considerable expense of plated through holes connections from one side of the board to the other are made with copper wire or, better still, with pins designed for this purpose.

The resistors should be fitted to the PCB first, noting that there are three types specified, carbon film for non critical applications, metal oxide for long term stability and the 1% components. Interchanging of these would cause loss of accuracy. The capacitors and transistors may be fitted next, together with the pots and IC sockets. The use of these is strongly recommended. Do not fit the soldercon pins for the display yet, since subsequent handling of the PCB will almost certainly cause damage to them. Fit the vero pins, noting that the two for the capacitance socket wiring are inserted from the opposite side of the board.

The switches may now be prepared. The knob shafts should be cut down to 9mm in length, and then turned fully anti-clockwise to the end stop (viewed from the front). Next the nut and washer are removed and the ring to fix the number of positions set to the six hole. Rotate the shaft five

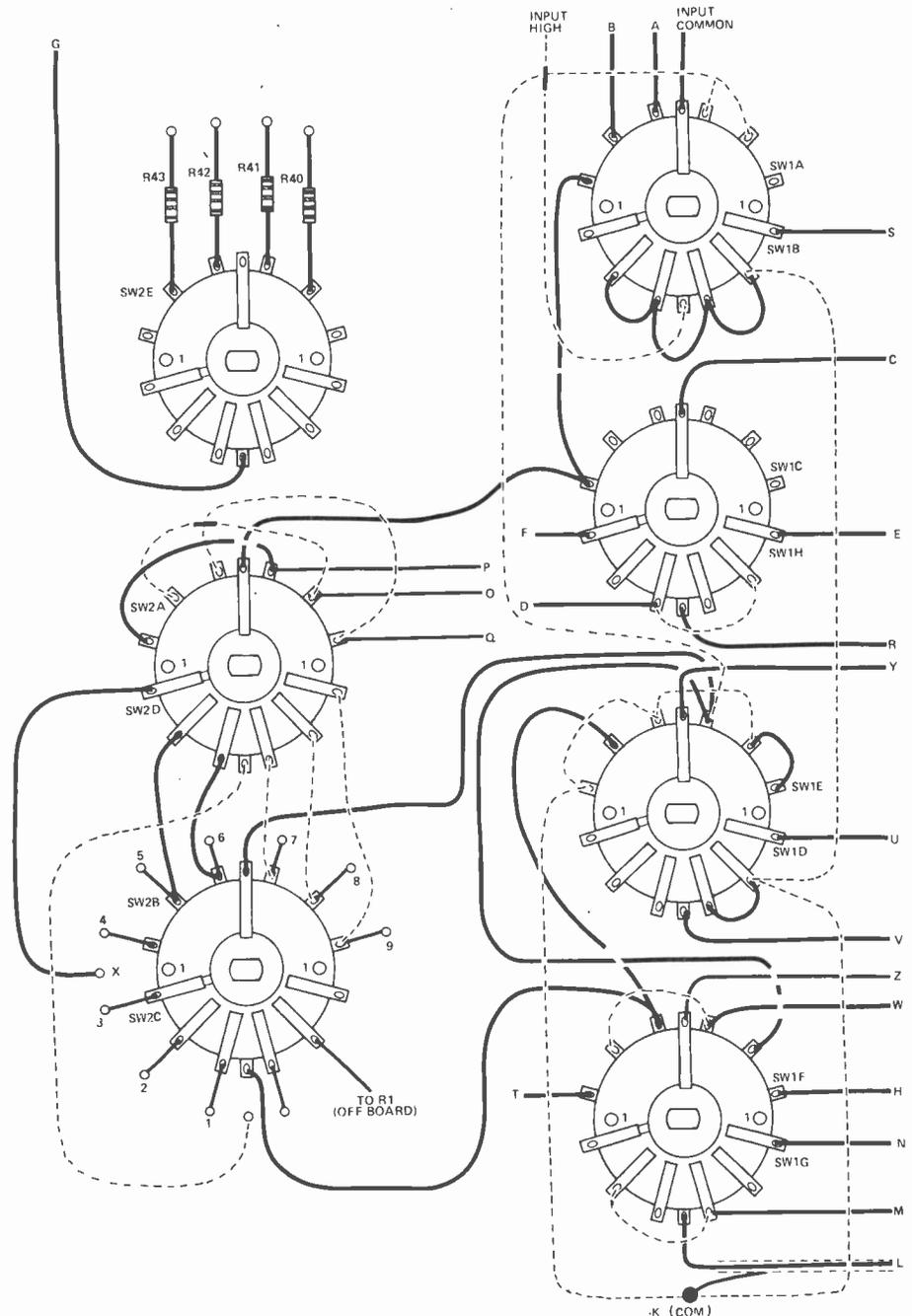


Fig. 4. Diagram showing the interconnections between the wafers of SW1 and 2.

positions clockwise to check that there are only six positions in all, then rotate back to the original position and replace the nut and crinkle washer. Repeat with the other switch assembly.

Prior to removing the studding carefully pull out the wafer drive shaft and cut to a length of 30mm, remove any burrs and reinsert. Next unscrew the 8BA nuts from the four lengths of studding, and cut these to a length of 37mm each. Fit a nut to

one end of each piece of studding, putting the remaining washers and nuts aside for use later. Beware—the centre of the assembly will push out very easily in this state causing a loss of springs, balls and temper.

Place the switch operating mechanism on the non component side of the PCB with the number '2' on the casting nearest to the display location and pass two studs through, the switch and PCB. It is possible to fit the wafers in any of four positions.

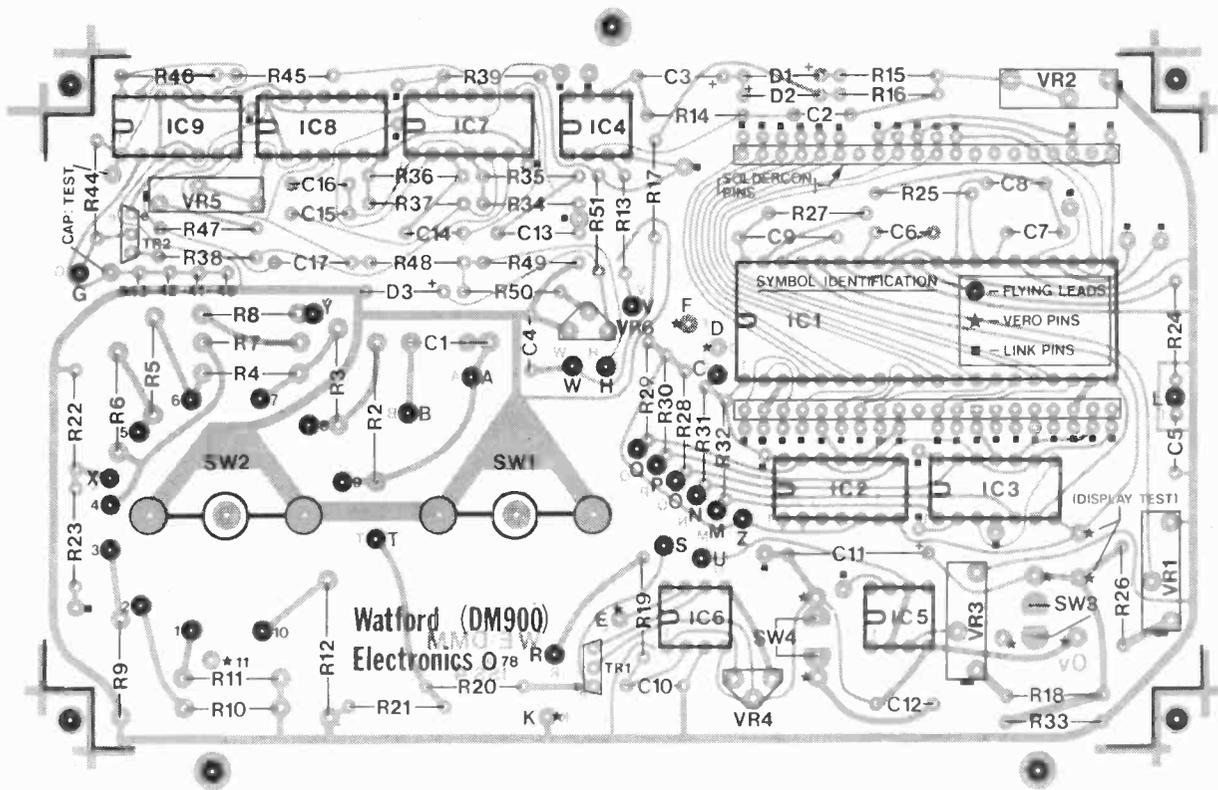


Fig. 5. Component overlay for the DMM circuit board, points marked ■ are through board links and points marked ★ are terminal pins. Only one side of the pattern is shown for clarity.

PARTS LIST

RESISTORS († 1% Hi-stab, † ¼W MO 2%, other ½W 5%)

R1	OR1
R2, 40	10M
R3, 41	1M0
R4, 42	100k
R5, 43	10k
R6, 9	1k0
R7	110R
R8	1R0
R10	100R
R11	10R
R12	1R0
R13, 19, 24, 28, 29, 30, 31, 32	1M0
R14, 37	10M
R15	10k
†R16, 18, 21, 47, 49	10k
R17, 36, 39, 50	4M7
†R20, 48	100k
R22	1k0
R23	39k
†R25	47k
†R26	24k
R27, 34, 44, 46	100k
R33	2k2

R35	470k
R38, 51	47k
R45	150k
POTENTIOMETERS	
multi turn ¼in cermet	
RV1	1k0
RV2, 3, 5	10k
min. vert.	
RV4	10k
RV6	100k

CAPACITORS

C1	10n 2kV disc ceramic
C2, 4, 6, 10, 12, 14, 15, 16	100n 100 V polycarbonate
C3, 11	10u 16V electrolytic
C5	10n 100 V polycarbonate
C7	220n 100 V polycarbonate
C8	470n 100 V polycarbonate
C9	100p polystyrene
C13	1n0 polystyrene
C17	1u0 100 V polycarbonate

SEMICONDUCTORS

IC1	ICL7106
IC2, 3	CD4070B
IC4, 6	TL081
IC5	741
IC7	CD4069B
IC8	CD4016B
IC9	TL084
Q1, 2	BC214L
D1, 2, 3	1N914

SWITCHES

SW1	8 pole 6 way
SW2	5 pole 6 way
SW3	miniature toggle
SW4	push button

MISCELLANEOUS

3½ Digit LCD display, PCB, IC sockets, 2A 20mm fuse plus chassis mounting holder, battery connector, case (type NJSF 1), display filter, 4mm sockets, knobs, wire, 50 link pins, 12 connecting pins, handle, screened cable.

only one of which is correct. Place the wafers on the bench with the visible wiper contact away from you, ensure the wiper tongue on the centre ring is to the left and that the flats in the centre hole lie parallel to a line joining the fixing holes. Hold the PCB component side uppermost while supporting the switch and studs and with IC1 to the right, slide the wafer over the studs and drive

shaft. SW2 (the left hand switch) has three wafers and SW1 has four wafers. Fig. 7 will clarify this. With the wafers in position, the fibre washers and nuts may be fitted and tightened. The switches should now be tested with an ohmmeter before proceeding to ensure no damage has been done during assembly.

The switches are now wired, using tinned copper wire and silicone

rubber sleeving, since using PVC insulated wire would promote the possibility of melting due to the close proximity of the switch contacts, and with up to 1KV around this is highly undesirable. An exploded view of the switch wiring is shown in Fig. 4, and this should be studied very closely. ▶

The switches should be wired starting at the wafers nearest the PCB

and working upwards. The end of the tinned copper wire should be soldered to the first tab, a length of silicone rubber sleeving cut to the exact distance between the tags to be joined and slid over the wire, and finally the other end soldered. The signal input to IC1 is brought from the switch by a screened lead, with the braid soldered to the 'common' pin adjacent to the relevant switch tag, and cut off and sleeved at the other end.

As stated above tracks on opposite sides of the board are joined by tinned copper wire or special pins which are inserted and then broken off short before soldering. The holes next to the display socket must be joined before the soldercon pins are fitted, since soldering close to them on the wrong side of the PCB can cause wicking of solder into the socket making it unusable. Having fitted these, the display socket pins may be fitted in the normal manner.

Having checked the board for assembly and wiring errors, the IC's may be inserted, being especially careful with IC1 which requires quite a high insertion force. Finally poke a piece of 20 SWG wire into each pin of the display socket to ease them and then fit the display. There is normally no indication of which pin is number 1, but by holding it at an angle to the light and looking for an outline of the digits, the correct way up may be found.

The unit is now ready for testing.

Testing and calibration

Connect up a 9 V battery and select the DC voltage range with 20V FSD. The current consumption should be about 5mA, and the display should read 0.00, with the plus and minus signs alternating. Check the voltage between the common and positive rails, which should be $2.8V \pm 0.4$. No measurements should be attempted with the DMM until calibration is complete as these will be meaningless. The accuracy of the whole instrument depends upon the setting of RV1 so this must be set first. It may be adjusted by comparison with a meter of known accuracy or by using a Weston standard cell (1.0186 volts), and it is likely that advertisers will be offering a calibration service. Which ever method is chosen, two wires are attached to SW1A and B wipers, positive and negative respectively and connected to the test circuit. Select the correct DC range and adjust RV1 until the correct reading


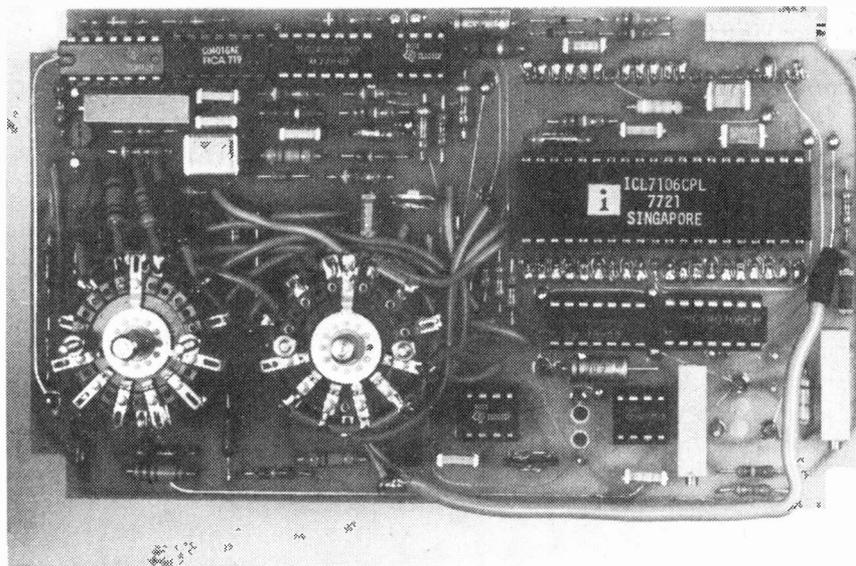


Fig. 6. Above, view of completed circuit, and Fig. 7 below, view of wiring around the range switches.

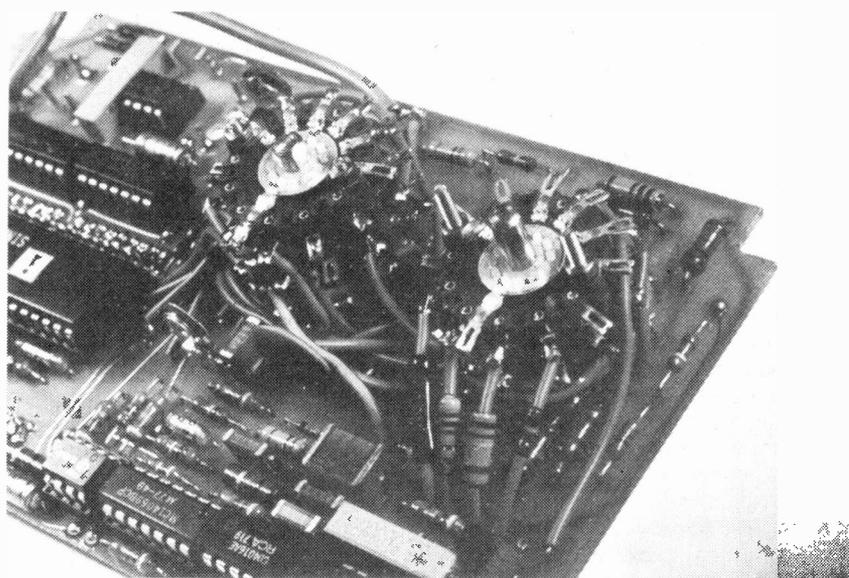

is obtained. If 1% resistors have been used where specified, changing to the next range should give a reading of exactly one tenth, and the next one hundredth, allowing for the plus or minus one digit accuracy. Calibration should ideally be done on the 200 mV range since this does not involve the attenuator, but this is not

normally very easy. As many ranges as possible should be checked to ensure overall accuracy. The DC current ranges may be checked also, and should agree to a high accuracy — but remember the 2A range resistor is not yet connected.

The AC voltage ranges may also be calibrated by a comparison

PROJECT : LCD Multimeter

method, preferably starting with a low voltage transformer or a signal generator. The frequency response should be good over the audio spectrum, but this has not been measured accurately. As before, the potentiometer, RV2 this time, is adjusted until the desired reading is obtained. When switching down ranges, the response will probably fall off at reading of 10 or so due to the rectifier, so the instrument should not be used at such low readings. The mains voltage may be checked with care, and mind fingers on the switches. There should be no polarity indication on AC ranges, but the colon may occasionally flash with no input since the minus sign is blanked.

The ohms ranges should be calibrated with a standard 1% resistor, and possibly those in the capacitance circuit may be left out for this purpose. First switch to the 20k range, when the colon to indicate resistance range will be seen and only the left hand 1 and decimal point to indicate overrange, i.e. infinite resistance. This overrange is the same on all ranges incidentally. Shorting the input leads together should give a low reading which may be reduced to 0.00 by adjusting RV4. Now insert the 10K-1% resistor and adjust VR3 to read 10.00, switching ranges should read 1.00 and .10. Check with the other resistors that calibration is correct. On the 200R range a small offset from zero will be observed, this being due to the switch wiring and contacts, and should not exceed 0.5R it should be taken into account when measuring low resistances however.

In order to calibrate the capacitance range, it is essential to have an accurate capacitor of value between 1n and 10n. This will probably be a polystyrene or silvered mica type. Switch to the 2n capacitance range and short the two read button pins. The reading should be unstable for a second or two and then settle to a low reading. Now connect the test capacitor across the two pins for the capacitance test sockets. Shorting the read pins should now give a much higher reading and by adjusting RV5 and again shorting the pins the reading should be adjusted to the value of the capacitor under test. (If it is more than 2n, obviously the 10n range will be used). Now switch up a range and short the pins when a reading of one tenth of the previous one should be achieved by adjusting RV6 and a

reading of one hundredth on the next range.

Re-check the setting of RV5 which may have altered slightly and then re-check RV6. This has set the capacitance ranges for best linearity, but due to stray capacitance, significant on the lowest range, an offset reading of three or four will be shown without a test capacitor. This is purely an offset, and capacitance readings down to 10pF or so can be made ignoring this offset.

All ranges should be checked as rigorously as possible to catch any faults before the unit is used in earnest. The battery condition may be checked by switching to DC volts and the fully clockwise position of SW1. The resistor network has been arranged to give a reading of 10.00 at 7 volts, below which the instrument will malfunction and the battery should be replaced.

Final assembly

To protect the display, a piece of clear perspex or Darvic approx. 65 x 40mm and no more than 1.5 mm thick is required. This is stuck to the reverse side of the front panel with Evostick or similar adhesive. Mount the push button with its pins orientated to line up with the holes in the PCB. Similarly mount the on-off switch with only a single lockwasher behind the panel. Fit the two capacitance terminals and line up the solder tags with the vero pins on the reverse of the PCB. Offer the board up to the front panel and with only a lockwasher on each rotary switch, the panel and board should be parallel to each other, with the display just clear of the perspex and central in the window. Now fit the switch nuts and knobs, and wire the toggle and push switches and capacitance terminals to their respective pins. Solder the battery connector leads to the pins adjacent to the on off switch, and three wires to the wipers of SW1A and B and the 2 amp position of SW2C. Mount the three 4mm sockets in the front of the box and connect the OR1 ohm resistor and fuse holder as shown on the diagram, then finally connect the wires from SW1 and 2. The battery may be held in position with a simple aluminium bracket. It is also possible to adapt certain types of battery holder to take six batteries of the HP 7 size. Finally screw in the front panel and your digital multimeter is ready for use. Make up a couple of leads using very flexible wire and use probes which will stand the voltages and currents to be measured. **ETI**

SAVE £££s WITH THE MONITEL

Telephone call charge calculator and clock. See separate advertisement.

FREE Spare battery / s with Casio (on request)

NEW

CASIO MQ-5


Clock / Calendar plus Two Alarms, Alarm Timer, Time Memory and Calculator.

24-hour Alarm and Timer (with count-down). Time and Date calculations. LCD display. Around 18 months' battery life. ± 15 seconds/month accuracy.

Superb case, hinged cover. ½ x 2¼ x 3¼. 2.6oz.

CASIO MQ-2. As MQ-5 but ¾ x 4¾ x 1¾

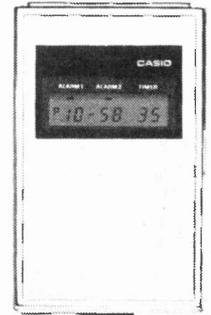CASIO LC78 MINI CARD (illustrated). LCD. 1000 hrs batteries. ½ x 3½ x 2½




£39.95

£34.95

£16.95

FX-48 SCIENTIFIC MINI CARD

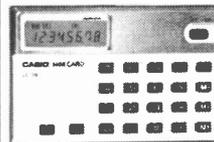

Similar to LC78 but also have scientific functions.

Available July / Aug.

£24.95

CASIO QUALITY AND VALUE



31QR-17B (left)

RRP £35.95 **£29.95**

Stopwatch, Dual Time Zone. 8.4mm thick



31QR-16B (right)

RRP £44.95 **£34.95**

Stopwatch, Dual Time Zone. 7.45mm thick



31QS-12B (left)

RRP £49.95 **£39.95**

Stopwatch, Dual Time Zone. 7.7mm thick



38CS-14B (right)

RRP £64.95 **£49.95**

Chronograph. Normal, net. lap and 1st-2nd place times to 1/100 second. 7.9mm thick

Also **CASIO** Sports, Alarm, World Time and Ultra-Slim models. **LADIES' WATCHES**

SEIKO Calculator Watch (£165) **£135**

CITIZEN Multi Alarm (£135) **£108**

CASIO CALCULATORS

ST.1 Four-way stopwatch £24.95. LCD LC822 £10.95. LC78 £16.95. AQ-1000 Clock, Alarm, Stopwatch £19.95.

CASIO SCIENTIFICS

Digitron FX-31 £11.95. FX-39 £15.95. FX-140

£17.95. FX-120 £19.95. FX-360 £49.95. LCD:


DX-2200 £19.95. FX-3000 £25.95.

NEW!! FX-8000. Available July/August. Scientific similar to FX-3000 plus 1/100 second stopwatch, 5 different timers, etc. **£29.95.**

Send 25p for our illustrated catalogue. Prices include VAT and P&P. Send your cheque, PO or phone your credit card no. to

TEMPUS Dept. E.T.I.
19/21 Fitzroy Street
Cambridge CB1 1EH
Telephone (0223) 312866

4" Oscilloscope

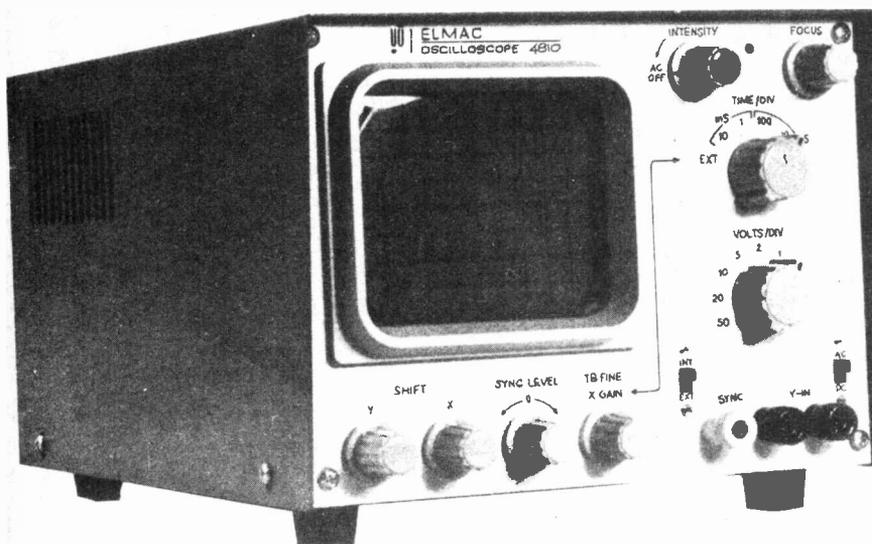

£99

+ VAT

SPECIFICATIONS

ELECTRICAL DATA

VERTICAL AXIS (Y)
 Deflection Sensitivity — 100m V/division
 Bandwidth (between 3 dB points) — DC — 5MHz
 Input Attenuator — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50V/div
 Input Impedance — 1Meg/40 pf in shunt
 Input Voltage — Max — 600V P.P.

HORIZONTAL AXIS (X)
 Deflection Sensitivity — 0-400mV/division
 Bandwidth (between 3 dB points) — 1Hz-350KHz
 Gain Control — Continuous; when time base in EXT position
 Input Impedance — 1Meg
 Input Voltage — Max — 600V p.p.

TIME BASE
 Sweep Range (calibrated) — 100msec/div to 1 μ sec/div in 5 steps
 FINE Control — Variable between steps — includes time-base calibration position
 Blanking — Internal — on all ranges

SYNCHRONIZATION
 Selection — Internal, external
 Synchronization Level — Continues from positive to negative

POWER SUPPLY
 Input voltage — 115/220V AC \pm 10% at 50/60Hz
 Power Dissipation — 18W

CRT DATA
 — 4in. — flat face, single beam
 — Maximum high voltage — 1.5kV
 — Fitted with 8x10 division blue filter graticule

PHYSICAL DATA
 Dimensions — 14cm (h) x 20.5cm (w) x 28cm (d)
 Weight — 4.3Kg (approx)
 Stand — 2 position flat and inclined
 Case — Steel, epoxy enamelled
 Front Panel — Aluminium, enamelled epoxy printing

OSCILLOSCOPE

To:
 Oscilloscope Offer
 ETI Magazine
 25-27 Oxford Street
 London W1R 1RF

Please find enclosed my cheque for £109.00 (including VAT and carriage) made payable to ETI Magazine for my 4in. oscilloscope.

Name

Address

Please allow 14 days for delivery.

In our recent survey, 25% of readers requested an oscilloscope offer or project. Well, here it is — a full specification 4in. 'scope for under £100!

An example of this oscilloscope can be seen and examined in our reception at our Oxford Street offices.

KET PLACE

Digital Alarm



Size: 105mm wide 115mm deep x 55 mm high.

OUR PREVIOUS digital alarm clock offer (which we have run for several years) was a real success — over 10% of ETI readers own these. We have been searching around for one of even better value and have come up with a winner — with an equally good spec and at a much reduced price: the Unik Time Digital Alarm.

This clock features a large, bright LED display in a really stylish case. It's really easy to set — lift up the hinged panel on the top and all the controls are there including fast and slow setting buttons. The hinged panel, when down, acts as the snooze switch — easily found by that early morning groping hand to give you 9 minutes extra in bed.

Mains operation only (240V/50Hz) with a 12 hour display. "AM/PM" and "Alarm set" indicators are on the front while an internal switch enables you to display the last significant minute and seconds if you wish.

£8.95

(Inclusive of VAT and Postage)

An example of this clock can be seen and examined in our reception at our Oxford Street offices.

DIGITAL ALARM

To:
Unik Time Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed my cheque/PO for £8.95 (payable to ETI Magazine) for a Unik Time Digital Alarm Clock.

Name

Address

.....

Please allow 14 days for delivery

LCD Watch



The enormous numbers involved in ETI offers has enabled us to arrange a real bargain — a full spec LCD watch with adjustable metal bracelet for under half the going rate.

This watch gives continuous display of hours and minutes — press the button once and you'll get the date (American style). After a couple of seconds the display automatically reverts to time but if you press again you'll get a continuous seconds display.

Press another button and you get a back light, enabling you to see the display in the dark. Setting, or resetting is simplicity itself and a 'hold' facility allows you to set the watch spot on. The accuracy is magnificent, as with all the current range of digital watches and battery life is well in excess of a year.

£9.95

(Inclusive of VAT and Postage)

An example of this watch can be seen and examined in our reception at our Oxford Street offices.

LCD WATCH

To:
LCD Watch Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed my cheque/PO for £9.95 (made payable to ETI Magazine) for my LCD Digital Watch.

Name

Address

.....

Please allow 14 days for delivery

SINCLAIR PRODUCTS'

Microvision TV now in stock. PDM35 digital multimeter £25.95, mains adaptor £3.24, deluxe padded case £3.25, new DM235 digital multimeter P.O.A., Cambridge programmable calculator £13.15, prog. library £2.45, mains adaptor £3.20.

S-DECS AND T-DECS'

S-DeC £3.39, T-DeC £4.44, µ-DeCA £4.52, µ-DeCB £6.73, 16 diil or 10T05 adaptors with sockets £2.14.

CONTINENTAL SPECIALTIES PRODUCTS'

EXP300 £6.21, EXP350 £3.40, EXP600 £6.80, EXP650 £3.89, EXP48 £2.48, PB6 £9.94, PB100 £12.74, LM1 £30.99, LP1 £33.48, LP2 £19.44.

TV GAMES

Send s.a.e. for free data. New racing car tv games chip AY-3-8603 plus economy kit £20.60, Tank battle chip AY-3-8710 plus economy kit £17.95, stunt motor cycle chip AY-3-8760-1 plus economy kit £17.95, 10 game paddle 2 chip AY-3-8800 plus economy kit £14.70, AY-3-8500 chip plus economy kit £8.85, modified shoot kit £4.96, rifle kit £4.95, colour generator kit £7.50. Attractively cased assembled tv games 4 game models (tennis, football, squash and pelota) black and white £11.95. Colour, £14.50. Deluxe 6 game colour model with pistol attachment £21.95. TV games mains adaptors £3.10.

MAINS TRANSFORMERS

6-0-6V 100ma 79p, 1 1/2a £2.35, 6.3V 1 1/2a £1.89, 9-0-9V 75ma 79p, 1a £1.99, 2a £2.60, 12-0-12V 50ma 79p, 100ma 90p, 1a £2.49, 1.3V 15a 95p, 15-0-15V 1a £2.79, 30-0-30V 1a £3.50.

JC12, JC20 AND JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1.60, JC20 10 watts £2.95, JC40 20 watts £4.20. Send s.a.e. for free data on our range of matching power and preamp kits.

FERRANTI ZN414

IC radio chip £1.85. Extra parts and pcb for radio £3.85, case £1. Send s.a.e. for free data.

PRINTED CIRCUIT MATERIALS

PC etching kits economy £1.70, standard £3.82. 50 sq ins pcb 40p, 1 lb FeCl3 £1.05, etch resist resin economy 45p, dalo 73p, small drill bits 1/32 ins or 1mm 20p each, etching dish 68p, laminate cutter 75p.

BATTERY ELIMINATOR BARGAINS

3-way power unit stabilized 7.7V 100ma £3.10, 3-way models with switched output and 4-way multi-jack 3/4 1/2 1V 100ma £2.92, 6 1/2 7 1/2 9V 300ma £3.30, 100ma radio models same size as a PP3 battery with press stud connectors, 9V £2.85, 6V £2.85, 4 1/2V £2.85, 9V + 9V £4.50, 6V + 6V £4.50, 4 1/2V + 4 1/2V £4.50, cassette recorder mains unit 7 1/2V 100ma with 5 pin din plug £2.85, car converters 12V dc input, output 9V 300ma £1.50, output 7 1/2V 300ma £1.50.

BATTERY ELIMINATOR KITS

Send s.a.e. for free leaflet on range. 100ma radio types with press and stud connectors. 4 1/2V £1.80, 6V £1.80, 9V £1.80, 4 1/2 + 4 1/2V £2.50, 6 + 6V £2.50, 9 + 9V £2.50, cassette type 7 1/2V 100ma with din plug £1.80, heavy-duty 13 way type 4 1/2 6 7 8 9 11 13 14 17 21 25 28 34 42V 1 Amp £4.65, 2 Amp £7.25, transistor stabilized 8-way types for low hum. Amp £6.40, Variable voltage stabilized models 2.18V 100ma £3.60, 2.30V 1A £9.95, 2.30V 2A £14.95. Car converters 12V dc input, output 9V 300ma £1.50, output 7 1/2V 300ma £1.50.

BI-PAK AUDIO MODULES

Send s.a.e. for data. S450 tuner £23.51, AL60 £4.86, PA100 £16.71, SPM80 £4.47, MTB80 £5.95 MK60 £38.74, Stereo 30 £20.12.

BULK BUY OFFERS

Minimum purchase £10 any mix from this section. 1N4148 1.3p, 1N4002 3.6p, BC212 8p, 741 8p, 15p, NE555 Bdl 29p, 723 14dl 43p, Dalo pens 59p, AC76023N exact equiv of SN76023N with improved heat sink 79p. Plastic equivs of popular transistors BC108 3.8p, BC109 4.4p, BCY71 4.7p, BCY72 4.4p, 2N3055 8p. Fuses 20mm x 5mm cartridge 2.5, 5, 1, 2, 3, 5-Amp quick-blow type 0.7p, antisuurge type 3.4p. Resistors 5% E12 10 ohm to 10M, 1/4W 0.8p, 1W 1.9p. Polyester capacitors 250V 0.1, 0.22, 0.33, 0.47mf 2.2p, 0.15mf 1.1p, 0.68mf 1.4p, 0.1mf 1.5p, 0.22mf 3p, 0.33mf 2.5p, 0.47mf 4.8p. 1 1/2% Ceramic capacitors 50V E12 22pf to 1000pf 1.7p, E6 1500pf to 33000pf 1.7p, 47000pf 2p. Electrolytics 50V, 47 1 2mf 5p, 25V 5mf 5p, 10mf 4p, 16V 22mf 5p, 33 1 2mf 100mf 8p, 220, 330mf 9p, 470mf 11p, 1000mf 8 1/2p. Zeners 4 400mV £24, 2V7 to 3V 5.5p. Preset pots sub-miniature 0.1W hor or ver 100 to 4M7 6.8p. Potentiometers 1/4W 4K7 to 2M2 log or lin single 26p, dual 76p.

MAINS OPERATED

ELECTRONIC DIGITAL ALARM CLOCK

IMMEDIATE DELIVERY

£8.95

INCL V.A.T. POST PAID

THREE FOR £26.00 POST FREE

ETI RECOMMEND THIS MODEL

- Unik Time Stylish Design
- Large Bright LED display
- Choice of black or white case
- All with red display on black background
- Tilted front panel for easy viewing
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- A.M./P.M. indicator
- Seconds Display
- Size 105mm x 115mm x 55mm high
- Fully guaranteed



HENRY'S RADIO

**All mail to: Henry's Radio
404 Edgware Rd. London W2
PHONE (01)723 1008**

SWANLEY ELECTRONICS

DEPT. ETI, 32 GOLDSL ROAD, SWANLEY, KENT BR8 8EZ

Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome.

BRAND NEW COMPONENTS

Linear Circuits	20p	LM382N	105p	TTL	7400	10p	7496	48p	1702A	420p	MC6800	950p	
709 DiL8	20p	LM1303	110p	7401	12p	7497	24p	2101	2101(2450ns)	90p	MC6810	310p	
741 DiL14	35p	LM3900	50p	7402	10p	74100	95p	2107	2107	350p	MC6820	450p	
747C DiL14	50p	LM3909	60p	7403	12p	74104	40p	2708	2708	750p	MC6850	525p	
748C DiL8	30p	MC1310P	105p	7404	10p	74105	40p	AYS-1013	380p	750p	MC6850	595p	
CA3011	80p	MC1312P	180p	7405	13p	74107	25p	AC125	18p	BC547	18p	TIP34A	95p
CA3014	130p	MC1314P	300p	7406	29p	74109	45p	AC126	18p	BC548	11p	TIP34B	128p
CA3018	80p	MC1315P	320p	7407	29p	74110	40p	AC127	17p	BC549	11p	ZTX107	14p
CA3020	190p	MC1330	100p	7408	12p	74111	10p	AC128	18p	BC550	14p	ZTX108	14p
CA3028	125p	MC1458N	35p	7409	14p	74116	160p	AC176	18p	BC558	12p	ZTX109	14p
CA3035	140p	MC1496N	60p	7410	10p	74118	82p	AC186	24p	BC559	13p	ZTX300	16p
CA3036	170p	NE555	80p	7411	18p	74119	130p	AD161	38p	BCY70	14p	ZTX301	16p
CA3042	170p	NE566	80p	7412	21p	74121	25p	AD162	38p	BCY71	14p	ZTX302	23p
CA3043	180p	NE560	300p	7413	25p	74123	45p	AF124	27p	BCY72	14p	ZTX303	23p
CA3046	180p	NE618B	350p	7414	48p	74125	45p	AF125	25p	BD115	52p	ZTX304	25p
CA3052	150p	NE562B	350p	7416	27p	74126	48p	AF126	27p	BD131	35p	ZTX310	13p
CA3054	115p	NE565A	120p	7417	27p	74132	70p	AF127	27p	BD132	35p	ZTX311	14p
CA3075	180p	NE566V	150p	7420	10p	74141	45p	AF139	36p	BD133	44p	ZTX314	22p
CA3080	70p	NE567V	170p	7421	28p	74142	202p	AF239	40p	BD135	38p	ZTX341	21p
CA3081	125p	SN7603N	200p	7422	17p	74145	65p	AF124	27p	BC107	14p	ZTX500	16p
CA3089	190p	SN76013N	140p	7423	25p	74147	135p	BC107B	10p	BD137	38p	ZTX501	16p
CA3090	400p	SN76023N	140p	7425	22p	74148	120p	BC108	8p	BD138	38p	ZTX502	20p
CA3123	150p	SN76033N	200p	7426	25p	74150	62p	BC108B	8p	BD139	35p	ZTX504	25p
CA3130	90p	TAA621A	215p	7427	25p	74151	48p	BC108C	10p	BD140	35p	ZTX505	30p
CA3140	90p	TBA120S	85p	7428	34p	74153	60p	BC109	8p	BF248	36p	ZTX506	30p
LM300H	130p	TBA540	200p	7430	10p	74154	106p	BC109C	10p	BF249	25p	ZTX507	25p
LM301AN	30p	TBA641	240p	7432	24p	74155	48p	BC147	7p	BFX84	20p	ZTX508	20p
LM304H	150p	TBA800	70p	7433	32p	74156	63p	BC148	7p	BFX87	20p	ZTX509	20p
LM308H	90p	TBA920	320p	7437	24p	74157	40p	BC149	8p	BFX88	20p	ZTX510	20p
LM318CN	170p	TCA270SQ	200p	7438	24p	74160	60p	BC157	9p	BFY50	15p	ZTX511	15p
LM324N	75p	TDA1002	450p	7440	13p	74161	80p	BC158	9p	BFY51	15p	ZTX512	15p
LM339	60p	TD1022	570p	7441	52p	74162	90p	BC159	9p	BFY52	15p	ZTX513	15p
LM390N	50p	TD2020	320p	7442	40p	74163	80p	BC167	8p	BU105	170p	ZTX514	22p
LM381N	105p	ZN414	75p	7443	90p	74164	60p	BC168	8p	BU205	140p	ZTX515	22p
				7444	90p	74165	90p	BC169	8p	BU208	160p	ZTX516	22p
				7445	70p	74166	100p	BC169C	9p	MU2955	98p	ZTX517	22p
				7446	70p	74167	270p	BC170	9p	MFF102	36p	ZTX518	22p
				7447	55p	74170	170p	BC171	9p	MPSA06	30p	ZTX519	22p
				7448	50p	74172	400p	BC172	7p	MPSA56	30p	ZTX520	20p
				7450	13p	74173	120p	BC173	9p	P1P29	40p	ZTX521	20p
				7451	13p	74174	90p	BC177	14p	TIP29A	44p	ZTX522	20p
				7452	13p	74175	70p	BC178	14p	TIP29B	40p	ZTX523	20p
				7454	13p	74176	90p	BC179	14p	TIP29C	40p	ZTX524	20p
				7460	13p	74177	90p	BC182	10p	TIP30	60p	ZTX525	20p
				7470	28p	74178	120p	BC182L	10p	TIP30A	48p	ZTX526	20p
				7472	22p	74181	195p	BC183	10p	TIP30B	55p	ZTX527	20p
				7473	22p	74182	75p	BC183L	10p	TIP30C	70p	ZTX528	20p
				7474	20p	74185	120p	BC184	10p	TIP31	50p	ZTX529	20p
				7475	20p	74190	70p	BC194	10p	TIP31A	50p	ZTX530	20p
				7476	20p	74191	100p	BC207	10p	TIP31B	60p	ZTX531	20p
				7483	75p	74192	70p	BC208	8p	TIP31C	65p	ZTX532	20p
				7485	90p	74193	70p	BC209C	10p	TIP32	55p	ZTX533	20p
				7486	26p	74194	92p	BC212	10p	TIP32A	60p	ZTX534	20p
				7489	100p	74195	70p	BC212L	10p	TIP32B	75p	ZTX535	20p
				7490	24p	74196	70p	BC213	10p	TIP32C	80p	ZTX536	20p
				7491	65p	74197	92p	BC213L	10p	TIP33	75p	ZTX537	20p
				7492	45p	74198	150p	BC214	10p	TIP33A	80p	ZTX538	20p
				7493	24p	74199	150p	BC214L	10p	TIP33B	103p	ZTX539	20p
				7494	80p	74200	150p	BC477	19p	TIP33C	118p	ZTX540	20p
				7495	55p			BC478	19p	TIP34	98p	ZTX541	20p

Carbon Film Resistors
High stability, low noise. 0.25W 5% E12 series from 4.7 ohms to 1 Megohm. 10% tolerance. Any selection.
each 100+ 1000+ 5000+

ELECTRONICS IN MOTORING

It is only a matter of time before the 'smart' car comes along — cars have been relatively simple hydromechanical machines without the intelligence that a powerful electronic system could provide . . . but that simple era is about to end.

THE ELECTRONIC REVOLUTION in the car industry is with us — the level of electronic sophistication in production cars is increasing at a surprising rate, bringing with it improved performance and high reliability.

In the past the electrical system in cars was a well known area for failure, wouldn't complex electronics be even more failure prone?

At first sight it seemed that failures would be inevitable. Cars offered an environment far more hostile to computers than the air-conditioned and dehumidified chambers they had been used to. Temperatures under the bonnet range from -40°C to 140°C . Salt spray, dust and vibration are constant menaces. And the car has a power supply "which, by computer industry standards, has limited capacity, minimal regulation, and is quite noisy," as a General Motors' engineering report put it. The odds against success seemed heavy at first.

Gradually techniques were worked out that promised success. Manufacturing methods became exacting — and expensive. When building the 'Lean Burn' electronics package, said Chrysler's Huntsville general manager, Arthur E. Douyard, "We actually try to make the unit fail during assembly. We expose it to 185° -degree temperatures three times, including a final period up to 10 hours. We also pass-fail the unit by computer five times. Finally, we audit ten per cent of the units we ship to grade our quality control standards."

The ten-hour test figure was not casually arrived at. "Any malfunction with an electronic device should show

up quickly — usually within the first ten hours," says Sidney L. Terry, vice president for public responsibility and consumer affairs of Chrysler. "After that the electronic components should never wear out. Chrysler engineers estimate that for every pound the industry has invested in electronic voltage regulators, the customer has saved nine pounds in replacement costs, and that customers have saved four pounds for every pound we have invested in electronic ignition."

This is a good record — for relatively simple devices. For more complex systems, serviceability suited to the auto repair shop will have to be worked out. "Repair of computer-type equipment will of necessity be at the module replacement level to be practical," the SAE was told by Frank P. Caiati and James F. Thompson of GM's Engineering Staff. "Isolation to a failed module will be the technological challenge. It is very necessary that a high percentage of module failures be self-indicating," so the usual vagaries of trial-by-replacement troubleshooting could be avoided.

"The MSI and LSI semiconductor technology of today lends itself to modularity," Caiati and Thompson added. Like car radios, the first complex electronic system used in a production car — the Bendix fuel injection for 1957 — used valves. Soon thereafter the valve was replaced by the transistor, much smaller and less power-hungry, while back in the semiconductor labs, the age of the integrated circuit was being ushered in.

"In 1959," explains Chrysler's Terry, "a commer-



cially available chip contained only one component of a circuit. By 1964, the number of components per chip was up to ten. By 1970, the number of components was up to about 1000, and by 1976, up to 82,000. At the same time, the cost per unit dropped sharply."

The electronics industry soon discovered that the most efficient way to use those 80,000 components was to organise them into a computer-like general purpose logic chip — the microprocessor. With that much power available in a very small package, the car industry had to pay attention to microprocessors. "These new LSI microprocessor chips, as used in calculators, started the industry looking at applications in which their added cost could be handled," says Donald E. Colvill, staff engineer for electronic engine controls of GM's Delco Electronics Division. "To an engineer," he adds, "a computer is always attractive from a technology standpoint."

It was one thing to decide to use this know-how of the semi-conductor industry, and quite another to decide exactly how to use it. There are two main types of computer, analogue and digital, and each has its strengths and limitations. The car industry started with analogue computers, but it is moving rapidly and irrevocably towards digital computers today.

The analogue computer was initially the most popular because it is simpler and well suited to doing many of the jobs that the car system requires. As its name hints, it works through the setting up of an electronic circuit that is analogous to the conditions in the mechanism that it's controlling. In an analogue computer, multiplication by a constant, for example, would be done by an amplifier of fixed, pre-set, gain. Analogue circuitry 'mimics' the motions of the machine and/or the mathematical equations that describe what it does. Analogue computers can be quite versatile, but for use in cars they're usually tailored in design to suit just the job they have to do.

Analogue Circuitry

Analogue circuits started strong in cars and are still doing many important jobs in them. The Bosch and Bendix electronic fuel injection systems use analogue

computers, for example. Analogue designs were chosen because they're fairly easy to change and adjust during vehicle development and during the evolution of the fuel injection system. For similar reasons Chrysler chose an analogue computer to control its Lean Burn spark-adjustment system. First launched in the 1976 model year, this functioned with 99.9% reliability on the initial field of 60,000 cars. Now in 1978 it's available on all Chrysler's eight-cylinder engine families.

Analogue circuitry also does the computing in the black boxes used in the closed-loop Lambda-sensing controls that make the so-called three-way catalysts work in the cars now on the US roads. Such systems were first marketed by Volvo and Saab at the end of 1976, using Robert Bosch electronics. Now for 1978 Ford's Pintos and Bobcats with automatic transmissions for the California market have such closed-loop or feedback controls. Both Motorola and Ford's own plant supply their analogue electronics. GM's Delco Electronics Division makes analogue controls for the similar air/fuel ratio control being fitted to some Buick, Oldsmobile and Pontiac subcompact models, also for the California market. Ford uses Bosch exhaust pipe sensors, while GM's come from the AC Spark Plug Division.

Two 1978 GM models have new spark control systems that also have analogue computer circuitry. One is Delco Electronics' Electronic Spark Control, which is called the Turbo Control Centre by its user, Buick, which employs it on its turbo-supercharged V-6 engines in the Regal and LeSabre sports coupés. This ingenious device uses a Delco Remy vibration sensor mounted on top of the inlet manifold to tell when the engine is detonating. Electronic filters on the sensor's output pass the high vibration peaks in the range of five to seven kilohertz that GM considers to be the signature of pinking or detonation. Analogue circuitry in the Electronic Spark Control modifies the spark dwell, and thus the spark timing, by a signal it sends to a special electronic module in the High Energy Ignition. Working every other crank revolution, it can retard the spark up to 20 degrees in two-degree increments until the detonation stops. It is designed to cope with extreme conditions in the running of the


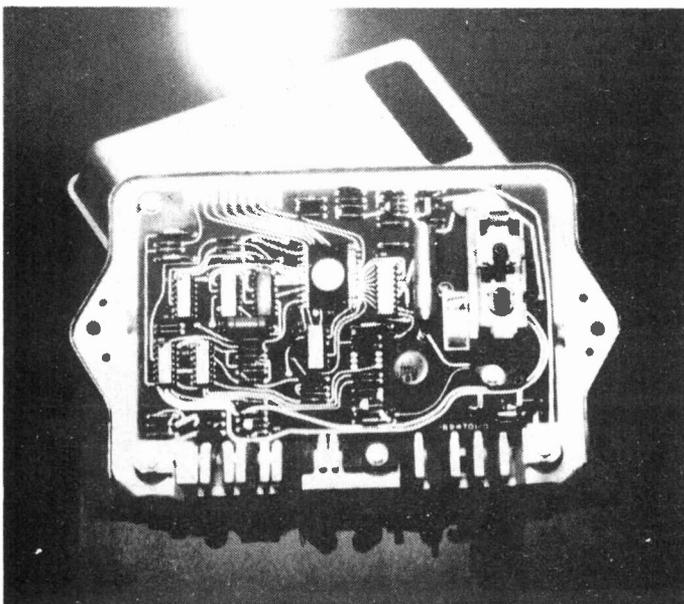


Fig. 1. Left, a Delco Remy module, part of an electronic controller for the GN 3-way catalyst system.

Fig. 2. Below, the spark control computer, part of the Chrysler Lean Burn System.

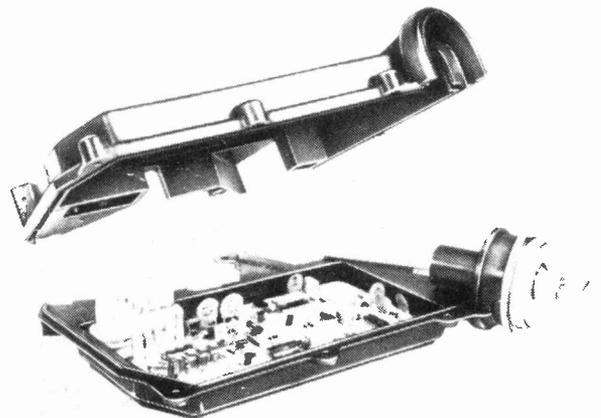

FEATURE : Electronics In Motoring

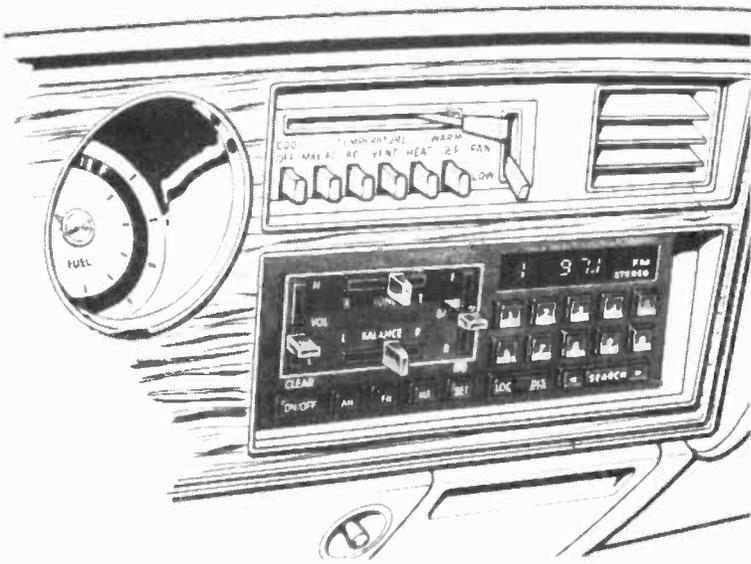


Fig. 3. Microprocessor control circuitry allows Chrysler's new AM/FM Stereo Search radio to recall ten stations from its internal memory. A LED display shows the frequency and number of the selected station.

gallon from its use. And the Electronic Spark Selector is built to "fail soft". Should it stop working, the engine simply keeps running with the last spark curve it was using before the failure.

Both Cadillac and Buick offer yet another engineering feature that combines analogue-type electronics with a simple logic chip. The new GM application is in the Automatic Level Control for the rear suspension, developed jointly by Delco Electronics and Delco Products. It uses an Optron diode sensor to measure the distance from the axle to the frame, and then through the analogue and logic circuits, it adds or subtracts compressed air (from a 150 psi supply) in the special shock absorbers to bring the rear of the car to the correct level.

sensitive supercharged engine, such as a very heavy load on a very hot day.

This spark control system is a closed-loop device, the first of its kind to be placed in volume production. Delco Electronics' other new spark controller is an open-loop design, the Electronic Spark Selector used on 1978 Cadillac Seattles (except for the diesels, of course). This has sensors that tell it engine speed, manifold vacuum, coolant temperature and the engine cranking condition. From these, an analogue computer advances or retards the whole spark curve to suit the running conditions. During engine warmup, for example, it retards the spark so the catalyst will reach working temperatures more quickly. Like the detonation sensor, this too allows the engine to be run with a great spark advance under most conditions, favourably affecting mileage. Cadillac expects an overall improvement of about one mile per

Number Crunching

With all these applications, analogue computation is well established in the electronic systems of today's cars. But it has a strong and promising competitor: digital computation. It reaches similar ends in a different way. While the analogue system is computing by making comparisons between different voltage and/or current levels, the digital system is carrying out the various calculations mathematically, just as you would on a scratch pad or calculator. You might say that digital computation is to analogue as a desk calculator is to a

Fig. 4. The Aston Martin Lagonda, below, has the driver's seat computer controlled through servomotors. The seat can be pre-programmed with two sets of adjustments (for husband and wife drivers).



slide rule. Actual physical relationships play a part in the analogue circuit's findings, while the digital computer gets its results by doggedly doing the actual math — very quickly.

While the digital device gives results that are inherently accurate, the electronic components of the analogue device must be "trimmed", during assembly and testing, to make sure that the complete circuit gives the right answers. This seems to show an edge for the digital device, but that's not necessarily so. Many of the inputs to digital computers will begin as analogue signals, such as a varying voltage from a temperature or throttle position sensor, and will need to be converted into digital language that the computer can understand. Such an analogue-to-digital converter will also need to be trimmed, or calibrated, for accuracy. And digital-to-analogue converter will also need to be trimmed, or calibrated, for accuracy. And digital-to-analogue converters for the computer's output will also be needed so it may perform automotive tasks.

Until recently it was simply unthinkable to fit a digital computer into a production car, because it was too big, too expensive, or both. Now, with the arrival of the microprocessor that limitation is beginning to be removed. A digital computer needs a central processing unit (CPU) to do the work. It also needs a fixed or permanent memory (known as ROM for read-only memory) of substantial size to tell it what to do and when to do it, and in addition to that a temporary memory, or RAM (random-access memory), in which it can store data it needs for continuing its calculations. All this can now be etched on one or more small LSI chips, forming a microcomputer.

Small and powerful though it may be, such a microprocessor doesn't come cheaply. It costs tens of thousands of dollars just to tool up to make the special masks needed to etch them in production. Also, to avoid needless waste they must be tailored as closely as possible to the applications for which they're needed. A nervous period of courting between the motor and semi-conductor industries is now ending, as each better understands the needs of the other, and microprocessor uses are increasing rapidly. From one in 1977 the number of applications has jumped to five in 1978, and there'll be many more in 1979, after the technique proves its value and reliability.

MISAR Sparks It Off

The beachhead for microprocessors in cars was established in the '77 model year by Oldsmobile and Delco-Remy with their MISAR spark control system used in Toronto. Standing for Microprocessed Sensing and Automatic Regulation, MISAR senses crankshaft rotation, manifold vacuum and coolant temperature, and from these decides which of more than 200 ignition advance points on a "map" of possibilities suits the engine best at that instant. These points are stored in a ROM with a capacity of 1024 ten-bit data words. Two LSI chips are at the heart of the Rockwell CPU that computes which point will be used at any moment. It completes the 335-odd instructions its program requires in about 12 milliseconds giving a fresh spark timing at that interval. MISAR works by switching the HEI distributor's own electronic module on and off.

Three other microprocessors are used to do jobs that are less vital to the running of the car. One is another Chrysler Huntsville development, an advanced solid-state search-tune radio. It has a ten-digit keyboard that



Fig. 5. Fifth among the digital microprocessors in the 1978 cars is the miles-to-empty system used, as an option, in the Lincoln Continental Mark V. Its LSI chip carries the equivalent of 3600 transistors on a surface less than a quarter-inch square. Picking up indications of car speed and fuel tank level, it calculates the distance travelled, fuel used and the resulting miles per gallon. Then it multiplies fuel mileage by the amount of fuel left in the tank to get the miles-to-empty reading shown on the dash.


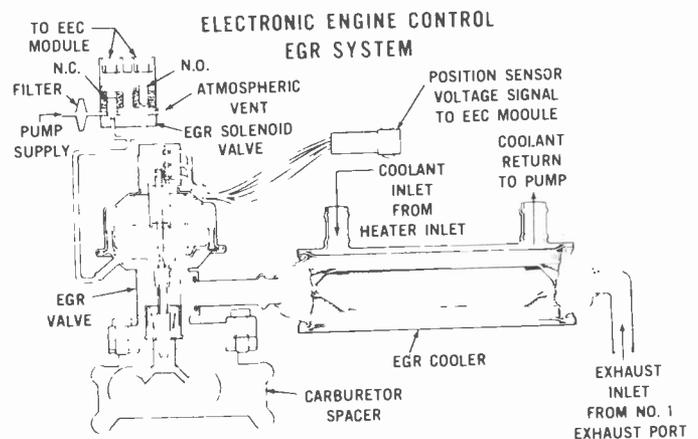


Fig. 6. Above, diagram of the Electronic Engine control system featured in the 1978 Lincoln Versaille.

Fig. 7. Below, diagram of the Delco Electronic Spark Control as used on the Buick turbo-charged V-6 engines.

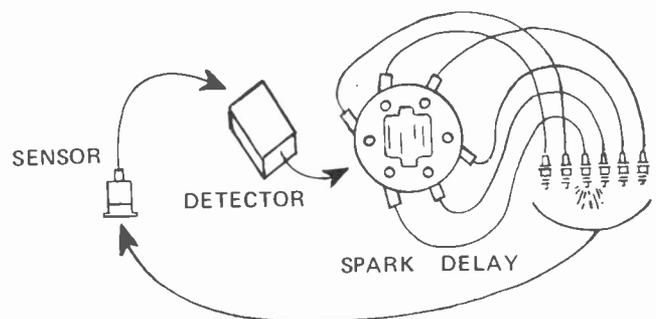

can be used to choose stations directly by their frequency, or from the radio's computer memory by a push of a single button. Automatic searching for other stations, at two sensitivity levels, can be initiated by a foot switch. The frequency chosen is shown by a

light-emitting diode display. This "thinking" AM/FM stereo radio is offered in such top-line models as the Dodge Diplomat and Magnum and the Chrysler LeBaron, Cordoba, Newport and New Yorker Brougham.

The fourth microprocessor available in the '78 models is an option on the 1978-1/2 Cadillac Seville, those without diesel engines. It's at the heart of a system called Tripmaster, which uses a large LED display made by AC Spark Plugs in place of the conventional speedometer and introduces LED displays for the fuel level and, at the right of the dash, for engine speed, coolant temperature or time of day — whichever the driver selects by pushing a button. A small panel holds a dozen pushbuttons for selecting operating modes or entering data into Tripmaster.

Its CPU, a Motorola 6800 microprocessor, allows the Tripmaster to do many navigational tasks. It can handle time, distance and average speed calculations, and it can relate them to the rate of fuel consumption and the amount of fuel left in the tank. Drawing information from the electronic fuel injection, it can read out the instantaneous fuel mileage and the average mileage for the journey. Its present ROM capacity of 4000 eight-bit words is enough to let the Tripmaster handle these jobs, and it be expanded by several multiples in the future, using the same CPU, to permit it to take over all engine functions and many other control tasks in the car.

Looking Forward

This is a promising array of digitally-controlled auto systems. Many more are waiting on the sidelines. We can expect, for example, that most and perhaps all of the present analogue car computers will be converted to digital operation in the course of the next several years. Speaking to the SAE about electronic fuel injection in 1976, Jerome G. Rivard, then of Bendix and now with Ford, said that "In the interests of cost reduction and higher production volume, the current hybrid analogue design will undoubtedly be replaced ultimately by a design based on digital EFI controller to be in production for the 1979 model year and to be in wide use in 1980. United Technology's Essex Group has also built and tested a digital injection computer, while Chrysler will use such a controller with its forthcoming Electronic Fuel Metering system. Its key microprocessor suppliers are expected to be the RCA Corp. and Texas Instruments.

The systems on the 1978 cars are the exploratory first wave for the mass invasion of microprocessors that's coming on the 1981 models. To meet the tougher emissions and economy standards then, the tiny LSI chips will take over control of all main engine variables: spark timing, EGR valve flow, choke control on carburetted cars, fuel preparation and fuel/air mixture control. The Motorola 6800 microprocessor, used already in Tripmaster, will be the key CPU for General Motors and, apparently, for Ford as well.

Those responsible for developing these new systems make no secret of the fact that the central brain, the CPU, has raced far ahead, in design, of the sensors and actuators that are the eyes and muscles of the brain. These are still relatively primitive, and all too susceptible to inaccuracy or failure under automotive operating conditions. Also many of them produce analogue outputs instead of the digital data that the microprocessor would prefer to receive. This is the area in which the mechanical and electronics engineers will have to cooperate most genially if good results are to be achieved.

ETI

SINTEL

THE SINTEL SIX DIGIT MAINS CLOCK KIT

with BLEEP ALARM and TOUCH SWITCH SNOOZE

- HIGH BRIGHTNESS DISPLAY
- AUTOMATIC INTENSITY CONTROL
- DEEP RED DISPLAY FILTER
- SLIM WHITE CASE 205mm x 40mm x 140mm
- BATTERY BACKUP
- CRYSTAL CONTROL FOR IMPROVED ACCURACY



Order as **ACK + BBK + XTK** £34.50
 The ACK is also available without battery backup and crystal control. Order as **ACK** £28.80
 The kit is supplied complete with the exception of a mains plug, cable and battery

DATABOOKS


Illustrating Basic	£2.45
Intel Memory Design Handbook	£5.20
Intel 8080 Microcomputer Systems User's Manual	£6.50
Intel 8085 Microcomputer Systems User's Manual	£6.50
Motorola Booklet From the Computer to the Microprocessor	£1.80
Motorola CMOS Databook (Vol. 5 Series B)	£3.50
Motorola M6800 Microprocessor Applications Manual	£12.95
Motorola M6800 Programming Manual	£5.35
National SC/MP Introtit User's Manual	£0.75
National SC/MP Technical Description	£1.80
National Semiconductor TTL Databook	£2.10
RCA CMOS and Linear IC Databook	£5.45
Texas Instruments Pin Configuration Guide (A very useful set of gloss cards showing top and bottom pin-out views of 7400 ICs plus many others (T1 Memories Op-Amps etc.)	£2.95
Z80 Assembly Language Programming Manual	£7.50
Zilog Z80-CPU Technical Manual	£5.60
Zilog Z80 CTC Product Specifications	£0.80
Zilog Z80-P10 Technical Manual	£3.30
DATASHEETS at 75p each on IM6100, 6800 SC/MP CDP 1802, 2650, TMS5501 TMS80B0 9131, Z80+P Intel 8085. Also free data on some components	
BEST OF BYTE Volume 1 300 pages	£11.95

Some Popular Memories available from SINTEL

(See ETI DATA SHEET SPECIAL July 1978)

2102 450 nsec 1K STATIC RAM	£1.85
2102 650 nsec STATIC RAM	£1.85
2708 1K x 8 bit UV ERASABLE ROM	£8.80
6508 600 nsec 1K STATIC RAM	£8.05

ASSEMBLED LATCHED COUNTER MODULES

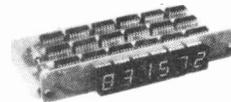

Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LEDs, displays, and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue.

	TTL				CMOS			
	Part No	Built	Part No	Kit	Part No	Built	Part No	Kit
2 digit	401-484	£13.22	528-412	£10.52	985-568	£13.02	548-470	£10.42
4 digit	715-484	£23.38	657-412	£17.98	512-568	£22.63	869-470	£18.11
6 digit	293-484	£33.76	721-412	£25.86	393-568	£32.31	191-470	£25.85

NEW PRICES AND SOME NEW CMOS ADDITIONS

If you need your CMOS by return — buy it from SINTEL

CD4000	0.15	CD4027	0.44	CD4051	0.82	CD4086	0.84	CD40182	1.40
CD4001	0.17	CD4028	0.77	CD4052	0.82	CD4089	1.39	CD40192	1.40
CD4002	0.17	CD4029	1.03	CD4053	0.82	CD4093	0.80	CD40193	1.40
CD4006	1.04	CD4030	0.50	CD4054	1.04	CD4094	1.69	CD40194	1.19
CD4007	0.18	CD4031	2.00	CD4055	1.18	CD4095	0.94	CD40257	1.48
CD4008	0.87	CD4032	0.89	CD4056	1.18	CD4096	0.94	CD40502	0.81
CD4009	0.50	CD4033	1.25	CD4059	4.29	CD4097	3.35	CD4510	1.01
CD4010	0.50	CD4034	1.71	CD4060	1.00	CD4098	0.98	CD4511	1.25
CD4011	0.18	CD4035	1.06	CD4063	0.98	CD4099	1.85	CD4514	2.47
CD4012	0.20	CD4036	2.86	CD4066	0.55	CD40100	2.50	CD4515	2.82
CD4013	0.43	CD4037	0.85	CD4067	3.35	CD40101	1.61	CD4516	1.01
CD4014	0.83	CD4038	0.96	CD4068	0.20	CD40102	2.13	CD4518	0.97
CD4015	0.83	CD4039	2.78	CD4069	0.20	CD40103	2.13	CD4520	1.04
CD4016	0.48	CD4040	0.97	CD4070	0.46	CD40104	1.10	CD4527	1.43
CD4017	0.79	CD4041	0.75	CD4071	0.20	CD40105	1.06	CD4532	1.21
CD4018	0.83	CD4042	0.89	CD4072	0.20	CD40106	0.82	CD4555	0.78
CD4019	0.50	CD4043	0.88	CD4073	0.20	CD40107	0.69	CD4556	0.78
CD4020	1.11	CD4044	0.84	CD4075	0.20	CD40108	5.36	MC14528	0.93
CD4021	0.90	CD4045	1.26	CD4076	1.17	CD40109	1.03	MC14553	4.43
CD4022	0.82	CD4046	1.20	CD4077	0.39	CD40160	1.19	IM6508	8.05
CD4023	0.18	CD4047	0.89	CD4078	0.20	CD40161	1.19		
CD4024	0.70	CD4048	0.50	CD4081	0.20	CD40162	1.19		
CD4025	0.20	CD4049	0.50	CD4082	0.20	CD40163	1.19		
CD4026	1.55	CD4050	0.43	CD4085	0.64	CD40181	3.40		


For our full range of components send for Free Catalogue
 Our Offices are at 209 Cowley Road, Oxford, but please do not use this as a postal address
 PRICES VALID UNTIL 31st AUGUST 1978

OFFICIAL ORDERS ARE WELCOME from Companies Govt Depts Natn Inds. Univs Polyts
 ORDERS: C W O add VAT @ 8% + 35p p&p TELEPHONE and CREDIT (Invoice) ORDERS add VAT @ 8% + 60p
 p&p minimum charge (the balance will be charged at cost). Please see FAST SERVICE EXPORT ORDERS welcome,
 no VAT but add 10% (Europe) 15% (Overseas) for Air Mail p&p. For Export postage rates on heavy items — contact
 us first.

ORDERS TO: SINTEL, PO BOX 75A, OXFORD
 Tel: 0865 49791

FAST SERVICE: We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.

SINTEL

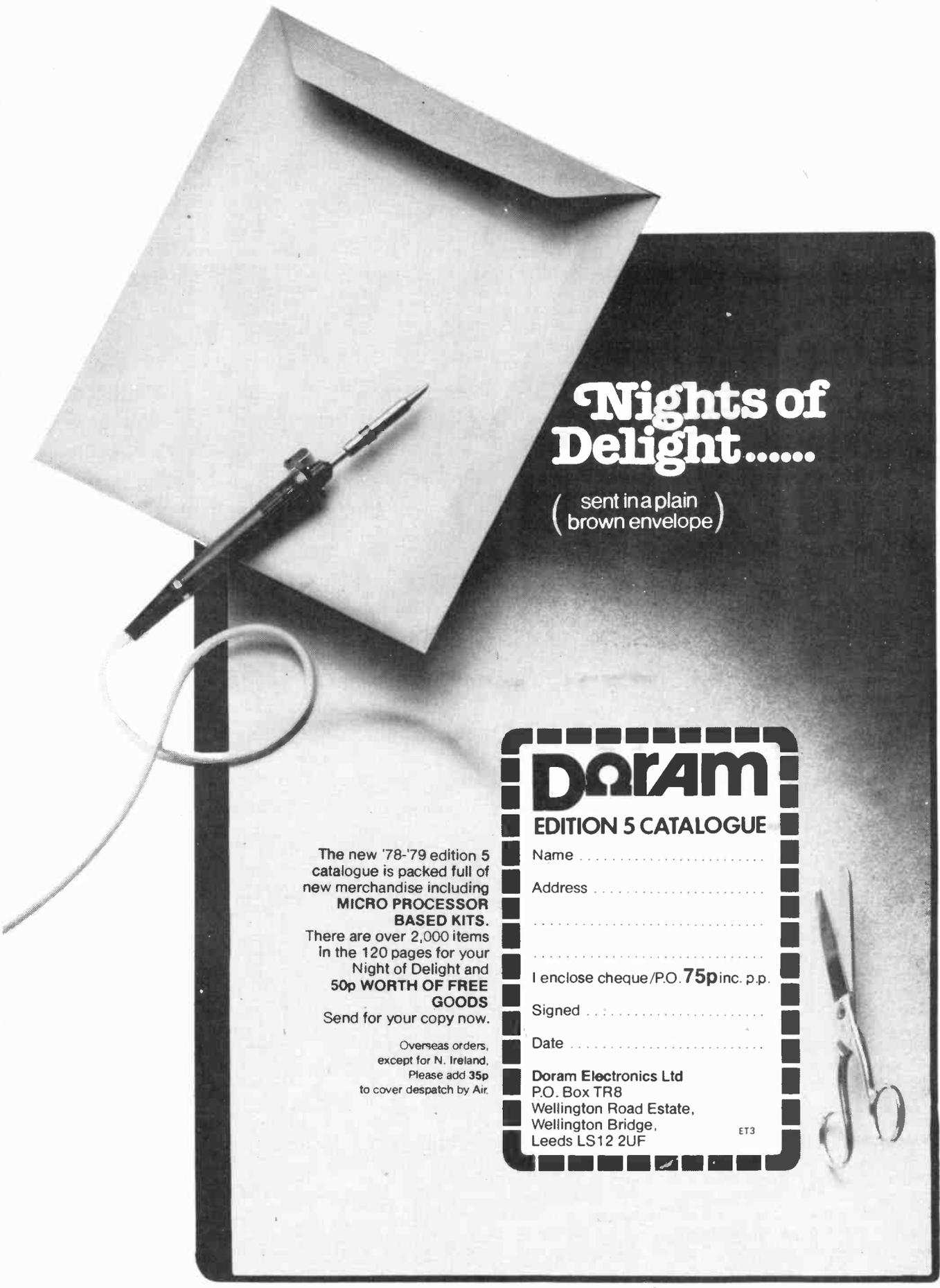

Nights of Delight.....

(sent in a plain
brown envelope)

The new '78-'79 edition 5
catalogue is packed full of
new merchandise including
**MICRO PROCESSOR
BASED KITS.**

There are over 2,000 items
in the 120 pages for your
Night of Delight and
**50p WORTH OF FREE
GOODS**

Send for your copy now.

Overseas orders,
except for N. Ireland,
Please add 35p
to cover despatch by Air.

DORAM

EDITION 5 CATALOGUE

Name

Address

.....

.....

I enclose cheque / P.O. **75p** inc. p.p.

Signed

Date

Doram Electronics Ltd
P.O. Box TR8
Wellington Road Estate,
Wellington Bridge,
Leeds LS12 2UF

ET3



HOME COMPUTER

Tandy have recently introduced the Radio Shack TRS-80 computer system to this country. Phil Cornes, Gary Evans, Graham Wideman and Mark Czerwinski have been putting the machine (pity it wasn't time sharing) through its paces.

THE NAME TANDY will be familiar to many of you. Of American parentage the company have over the past few years opened up a large number of retail outlets in this country dealing mainly with audio equipment and in most cases, components. Those of you who frequent the larger Tandy stores may well have noted the appearance of a home computer, as Tandy's TRS-80 home computer system has been on demonstration in many since March. So what is the TRS-80 and how does it compare with similar systems?

What You Get

The TRS-80 system comprises of four separate units. The first, a standard 'Realistic' CTR 41 portable mains/battery cassette recorder, is used for long term storage of programs, information and data files.

The second is a video display unit which provides up to 16 lines of 64 alpha numeric characters. Each of these 1024 character locations can be further sub-divided into a 2 x 3 matrix giving an overall 128 x 48 matrix. The 6144 resulting positions on the screen can be individu-

ally lit or dimmed as required, from within a program, to produce all manner of continuous or interrupted graphics.

Thirdly we have the power supply unit, which gives a 17 volt AC output, used to power the last item of hardware, the CPU, memory and keyboard package.

The CPU is a Z80, the memory comprises of level 1 BASIC in 4K ROM, 4K of dynamic RAM for program storage and 1K static RAM for the video display. Also included are the voltage regulators, the cassette and video interfaces and the integral standard 'QWERTY' keyboard. Also supplied are a 232 page instruction manual and two cassettes, one blank for retaining your first efforts in programming the other with two games programs — Blackjack and Backgammon. In addition all leads required to connect the four units together and to the mains are provided.

Initial set-up is quite easy — simply put all four units on the same table and plug them all together. All three connections to the keyboard/CPU unit are made via five-pin DIN plugs and **ARE** interchangeable. The

sockets are labelled and we are assured that swapping leads will not cause any damage. Plugging into the cassette recorder is less obvious since two of the plugs can be interchanged with no identification other than being of different colours.


Having said all this though, after setting up the system a couple of times one will be familiar with all these points and in practice we don't see many problems with these connections.

First Impressions

Switching the system on requires the pushing of two on/off switches. The first is on the front of the video display and the second is on the back of the microcomputer itself adjacent to the plug and socket which connect the power to the main unit. With this done it takes only three or four seconds for

READY
> -
to appear in the top left corner of the screen. The > symbol is presented to inform you that the system is in the state in which it can accept entries from the keyboard, the symbol itself is called a 'prompt'. The - is called the cursor and is presented to show you where the next character input will be displayed. A quick flick through the manual revealed on page 225, the listing of what appeared to be a very useful program, a combined function and RAM test which it is claimed "Puts the TRS-80 through its paces — All of them" and having looked through the program we could well believe it.

The program starts off by using every statement and function that level 1 BASIC is capable of with checks in the program to make sure that all is as it should be and with error messages printed for a failure. The program then goes on to write numbers into all empty RAM locations, reading them back to check that they were written correctly and finally it displays a sort of simple test card that can be used to check the alignment and centering of the picture on the screen. Care should be taken when typing this program in as there an error in the manual which has to be corrected as you enter the program. (There is a slip of paper included with the manual which corrects the few printing errors that have crept in). It is well worth dumping this program onto tape (see below) as if you are anything like us it takes about half an hour to put it in (using the well tried and trusted single finger poke and hope method).

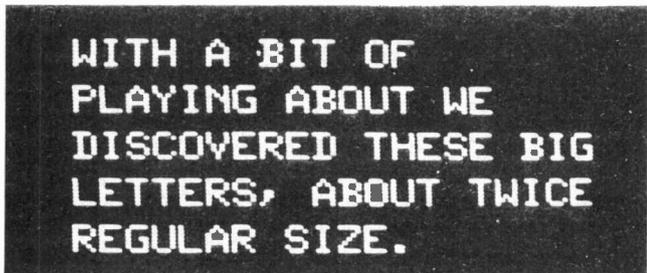

WITH A BIT OF
PLAYING ABOUT WE
DISCOVERED THESE BIG
LETTERS, ABOUT TWICE
REGULAR SIZE.

The TRS-80 passed the test, this was the point at which we considered the system to be well and truly commissioned. The command CSAVE is the one used to dump programs to tape but the one you'll most likely want at first is CLOAD, the magic word for loading one of the programs included with the machine. Having amused ourselves with these for an hour or four we can take a look at the hardware and software in more detail.

Looking at the total system, there are advantages and disadvantages to having four separate units. The main "pro" is the flexibility of being able to move the keyboard, video monitor and cassette recorder to suit your convenience (and making it easier for Tandy to provide machines for different markets), although longer leads would have helped on some units. It might have been better, however, to combine the cassette record and power supply with keyboard thus reducing the packages to two.

Not For Hard Types

The keyboard itself, while not of "professional" quality is more than adequate being a full QWERTY typewriter style design. One point to watch is that the keyboard will not accept a new key entry until the previous key has been fully released. Even an inexperienced typist, when entering often encountered groups of letters (eg. key words) will notch up speeds that will lead to displays such as RN, LST etc. Level II BASIC (see later) will remove this problem.


As mentioned above, the keyboard case also includes the CPU, memory and other assorted circuitry.

We don't feel that this system would be much fun for hardware enthusiasts. It's difficult to manage when taken apart, the keyboard and main board are attached to an easy to break flexible cable with no plug. No I/O ports are on board, which rules out simple add-ons, such as switching devices on and off, hooking up a speaker, and other popular experiments and applications. The back connector brings out the address, data and control buses. Thus a separate box with interface adapter could be added. Also on this connector are the keyboard lines, which would presumably facilitate adding more keyboards (possible numeric pad) in parallel with the existing one. The keyboard interface is done not with a Peripheral Interface chip as might be expected, but with ordinary buffers and latches, a cheap but less flexible system.

To summarize, this product does not appear to be aimed at the serious hardware person. Add-ons are difficult, although Radio Shack is coming out with an I/O unit. In addition, an S-100 interface is in the works, according to Radio Shack literature. The TRS-80 must then be best suited to software type, keyboard plus video and printer applications.

Data may be recorded on cassettes by means of the built in cassette interface which converts the data to a series of audio tones. Thus, any reasonable quality cassette recorder will do the trick. The cassette itself should also be fairly good since any tape "drop-outs" mean lost data. Tandy will supply five minute-per-side cassettes for this purpose although we have used C60s with no problems.

The recorder supplied with the TRS-80 (the CTR-41) has connections from the keyboard to the "AUX" input, "EAR" output, and also the remote on/off jack. Thus, when recording or playing cassettes, the operator (you) pushes the desired keys on the recorder and the TRS-80 switches the recorder on and off at appropriate times. You also need to set the volume level when playing back tapes. When recording, a dummy plastic plug must be stuck in the MIC jack to deactivate the built-in condenser microphone. The CTR-41 features a tape counter, very handy for finding your programs.

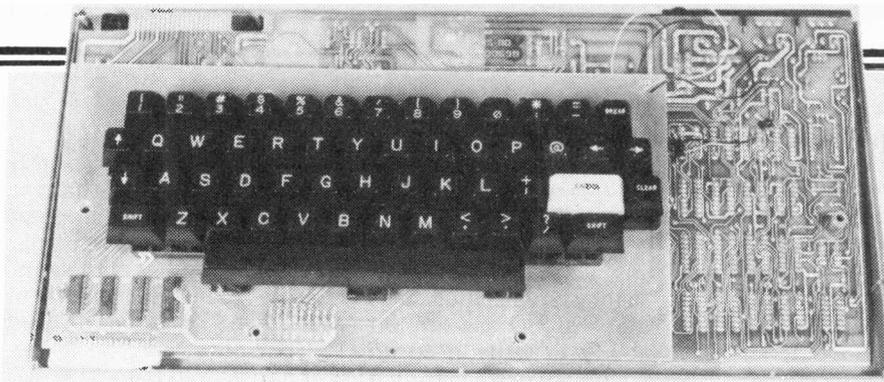

The interior of the TRS-80 reveals two PCBs, one of which carries the keyboard while the other deals with the rest of the TRS-80's circuitry. The flexible connector that joins the two boards can be seen bottom left while the expansion bus is at top left.

One dislike about the cassette system was the fact that the TRS-80 maintains control of the cassette machine at all times as long as the remote plug is left in you have to keep removing the plug to fast forward or rewind a tape to the desired position (This could easily be overcome by fitting a simple on/off switch in the main unit to short the remote jack and thereby provide a computer control/manual override switch).

Video Display

Designed specifically for the TRS-80 the video monitor accepts the signal from the keyboard unit and displays it on a 12 inch CRT. The video signal is fairly standard with 0V for sync level, 0.6V for black level with peak white at 2V. Impedance is 75Ω. The circuitry is isolated from the rest of the system by an opto isolator.

Power Supply

Nothing much to say about this, it converts the mains to a 17V AC unsmoothed output.

The Manual

This item is almost as invaluable as the Z80 MPU itself even if you've known BASIC all your life. It starts off by assuming you have never seen a computer before and it takes you easily and clearly through everything that you could ever want to know about BASIC and its implementation on this machine, starting with switching the machine on and ending with how to set up data files.

One thing we particularly liked about the manual was the trouble Tandy have taken to make sure that some of the sample programs don't work so that they can then go on to fully explain the error messages that the TRS-80 can give and how to interpret them and then go on from this to learn how to correct (de-bug) your own programs.

Another very useful section of the manual is an appendix which gives the listings of 11 subroutines to enable the TRS-80 to perform all the scientific and trig. functions that the interpreter can not do directly. These routines are numbered and arranged in such a way that they fit easily into any program you are writing that needs them while at the same time requiring only half a dozen lines of program each so they don't take up too much program memory.

Software


As a home computer system, the TRS 80 is probably the least hardware oriented we have seen. There are two points which support his thinking: you can't get at the internal hardware without voiding the warranty and there is no hardware interface capability other than to the display and the cassette recorder.

In the market at which the TRS-80 is aimed however the potential customer will be influenced by what he sees (ie packaging) and by what he can be led to believe about it (by advertising, by friends, by using the system, and even by reading electronics magazines). That customer's attention will be focused on the keyboard and display not on the internals. It won't matter to him that a Z-80 incorporates efficient machine language instructions for data searching and moving or that it's a microprocessor that can run at a 2MHz clock rate. He will be more interested in what it can do as opposed to how it does it (he's buying capability, fun and perhaps even status, not speed).

A Look At What You Get On The Soft Side

The TRS 80 comes with "Radio Shack Level 1 BASIC" in 4K ROM. Level 1 claims to support "standard BASIC statements". But whose standard? It seems to be Tandy's since some important capabilities are missing (for example exponentiation and array dimensioning). All calculations are performed in floating point with 5 or 6 decimal place accuracy. Twenty-six numeric variables are available (A to Z) along with one numeric array variable. Two 16-character string variables can also be used. Actually, these are more properly called "string things", since they cannot be compared, manipulated, indexed or used in any but the most mundane ways. You can input and output using them, but that's all folks.

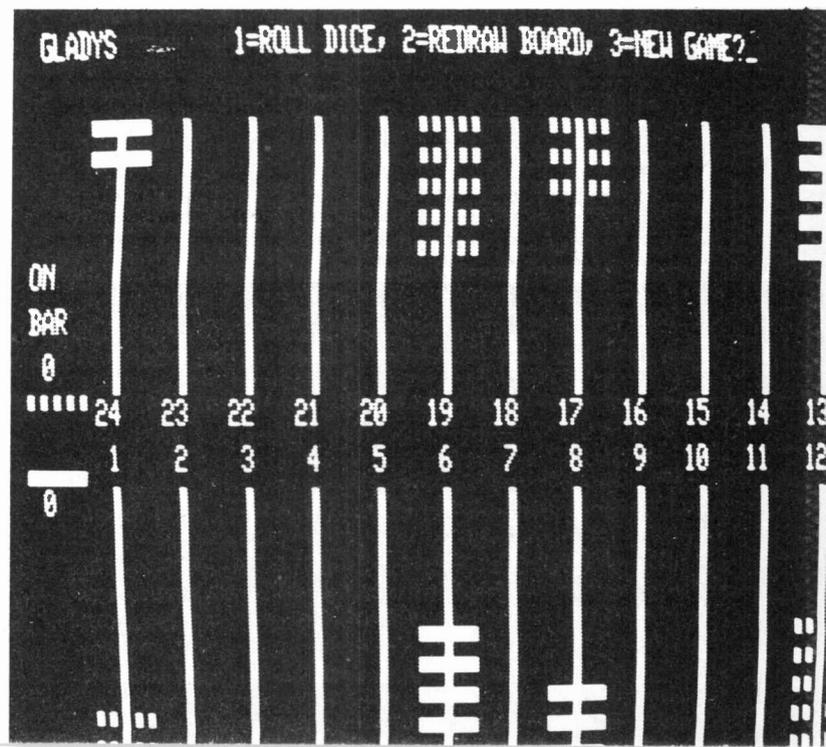The display produced by the TRS-80's version of backgammon makes use of the (limited) graphics capability of the machine. However, as can be seen, a quite acceptable display can be produced by the system.



Cassettes can be used to handle programs (CSAVE and CLOAD commands) or data (PRINT# and INPUT# statements). Since whatever you have in memory will be wiped out if you cut off the power (intentionally or otherwise), having a cassette recorder to store your information permanently is invaluable. And it makes entering of other people's programs (such as the Backgammon and Blackjack games supplied by Tandy) especially convenient.

Speaking of which, the Backgammon game makes extensive use of the TRS 80's rather limited graphics capability: there are virtually no special graphics characters — you've got to construct whatever image you have in mind by turning on some points on the display (48 points vertically by 128 points horizontal). This can be tedious. Mind you, in the low cost home computer system field this is not unusual. To compensate you can write sub-routines which draw vertical and horizontal lines, draw patterns, fill them in etc.

You And Your Program

Immediately after powering up your display and keyboard, the following will appear:

READY

At this point you can:

- 1) do simple calculator type computations (immediate execution)
- 2) bring in a program from tape.
- 3) type NEW and enter a program

Program statements are preceded by line numbers to distinguish them from immediate execution statements and keep them in order. A LIST command is available to display the program. Unfortunately the cursor control keys cannot be used to edit this display, so if you want to change a line in a program, you must retype the entire line.

Output which would otherwise stream by while your program is executing can be frozen by depressing any key. Unfortunately, if you interrupt the program itself, you cannot modify the variables it is using and then return to the point of interruption. So your only alternative is to rerun the program and in many cases, that's a nuisance.

As for error messages, they are confined to WHAT? HOW? or SORRY (along with an indication of where the problem is). These terse messages are not unexpected when you consider that the interpreter was written to fit into 4K of ROM. In a tradeoff of readability against the amount of program code you can fit into the standard 4K of RAM, Level 1 has a "shorthand dialect". For example: G.=GO TO, N.=NEXT, and P.=PRINT. However, REA. seems to be a shortform of dubious value for READ (probably done for consistency).

The TRS-80 character set is shown below, note that some minor variations between this set and those on current production machines may be noted. In addition to these characters, the screen is divided into 6144 cells each of which may be lit or dimmed to form graphic characters.

THE TEXT ON THE TRS-80 LOOKS LIKE THIS. EACH CHARACTER IS A FIVE BY SEVEN DOT MATRIX. THE COMPLETE SET LOOKS LIKE THIS:

ABCDEFGHIJKLMN OPQRSTU VWXYZ1234567890:~;.,/
! " # \$ % & ' () * + - = < > ? [\] ^

SIXTEEN LINES OF SIXTY-FOUR CHARACTERS ARE AVAILABLE.

Make It Fit

The overriding philosophy controlling the design of this interpreter seems to have been "make it fit". It's hard to believe that a 4K interpreter is anything but "stripped down" after you've used this one and it is somewhat unrealistic (no pun intended) for Radio Shack to claim, as they have in their sales literature, that "applications of the TRS 80 are limited only by the imagination and ability to write programs". Try something quite unimaginative like sorting a list of names. Good luck! You'll need it.

Level II

From the sketchy details available on Level II BASIC, an interpreter written by Microsoft, the statements and functions to be available would appear to make this version of BASIC at least as powerful as PET's including many editing features. In fact we would go so far as to say that Level II is the most significant upgrade for the TRS-80. We wonder how logical it is to sell a home computer with such a limited BASIC and then offer the upgrade as an option. Will this turn people off computing, or will most of them jump for BASIC II anyway?

Level II BASIC will cost you £79 when it appears in July. We also understand that a Level II machine is to cost £79 more than a Level I model. This combined with the £229 pounds Tandy are asking for converting a 4K system to 16K seems to indicate that in these areas at any rate expanding your system with Tandy's help will prove expensive. As far as the RAM goes, however, you could buy the devices yourself, conversion involves taking the 4Kx1 devices from their sockets and replacing them with 16Kx1 chips. Change a few jumpers and your machine is now a 16K model. Cost — about £100.

Other hardware items are planned but there are no firm dates or UK prices fixed yet though we do have some US prices from which we can make an educated + or - 10% guess.

1. SCREEN PRINTER reproduces anything displayed on the screen including graphics at 2200 chars./sec (price about £480)
2. LINE PRINTER 110 chars./sec, 5x7 dot matrix commercial standard impact printer (price about £1000)
3. MINI DISK of which the TRS-80 can operate 4. 80K bytes per disc. 125K bytes per sec transfer rate. 1/2 sec average access time (price each about £400)

We were not as impressed with the TRS-80 as some of the other machines in this price bracket we have looked at. Lack of hardware access, and software which is primitive, combined to make it a less attractive product to anybody with even a little experience in home (or for that matter any) computers.

The Level II BASIC would make the machine a far more attractive proposition than at present and even with the additional £79, still an attractive choice on the grounds of cost.

The end result is that if you're in the market for a machine like this you should look very carefully at what you need and what you can get for the money.

During the review it was discovered that it was possible to get 32 characters to the line from the display (fat letters) by recording a string onto tape as a data file and then CLOADing this as a program. Sometimes using this method you lose some of the facilities of the TRS-80 and have to remove the power to restore them. (This is a standard facility of level 2 BASIC by the way).

Anyone for a users club?

ETI

15 — 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV.

Auxiliary 3-100mV, input impedance 47k Ω at 1kHz.

OUTPUTS: Tape 100mV, Main output 500mV R.M.S.


ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0.1% at 1kHz, Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE:** \pm 16.50V.

Price £5.22 + 65p VAT P&P free.

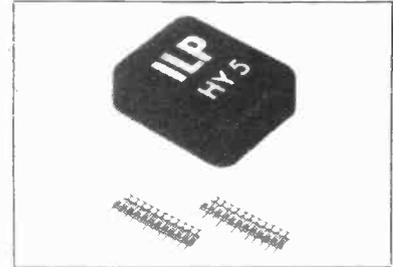HY5 mounting board B1 48p + 6p VAT P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. — it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build. **APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator.


SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω ; **DISTORTION:** 0.1% at 15W.

INPUT SENSITIVITY: 500mV; **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB.

SUPPLY VOLTAGE: \pm 18V.

Price £5.22 + 65p VAT P&P free.

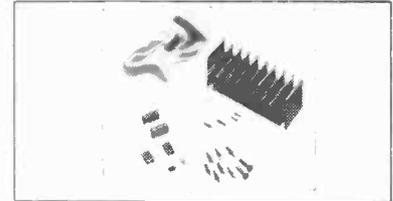

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components.

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier.

SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV.

OUTPUT POWER: 25W RMS in 8 Ω ; **LOAD IMPEDANCE:** 4-16 Ω ; **DISTORTION:** 0.04% at 25W at 1kHz.

SIGNAL/NOISE RATIO: 75dB; **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB.

SUPPLY VOLTAGE: \pm 25V; **SIZE:** 105.50 x 25mm.

Price £6.82 + 85p VAT P&P free.



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range — designed to meet the most exacting requirements including load line and thermal protection — this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components.

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ.

SPECIFICATIONS:


INPUT SENSITIVITY: 500mV.

OUTPUT POWER: 60W RMS into 8 Ω ; **LOAD IMPEDANCE:** 4-16 Ω ; **DISTORTION:** 0.04% at 60W at 1kHz.

SIGNAL/NOISE RATIO: 90dB; **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB; **SUPPLY VOLTAGE:** \pm 35V.

Size: 114 x 50 x 85mm.

Price £15.84 + £1.27 VAT P&P free.

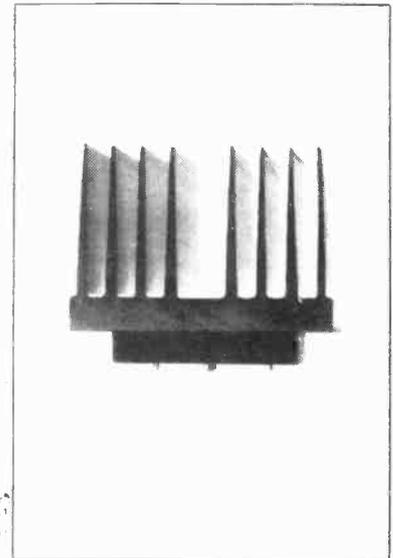

HY200 120 Watts into 8 Ω

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components.

APPLICATIONS: Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address.

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV.

OUTPUT POWER: 120W RMS into 8 Ω ; **LOAD IMPEDANCE:** 4-16 Ω ; **DISTORTION:** 0.05% at 100W at 1kHz.

SIGNAL/NOISE RATIO: 96dB; **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB; **SUPPLY VOLTAGE:** \pm 45V.

SIZE: 114 x 100 x 85mm.

Price £23.32 + £1.87 VAT P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components.

APPLICATIONS: Public address — Disco — Power slave — Industrial.


SPECIFICATIONS:

OUTPUT POWER: 240W RMS into 4 Ω ; **LOAD IMPEDANCE:** 4-16 Ω ; **DISTORTION:** 0.1% at 240W at 1kHz.

SIGNAL/NOISE RATIO: 94dB; **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB; **SUPPLY VOLTAGE:** \pm 45V.

INPUT SENSITIVITY: 500mV; **SIZE:** 114 x 100 x 85mm.

Price £32.17 + £2.57 VAT P&P free.

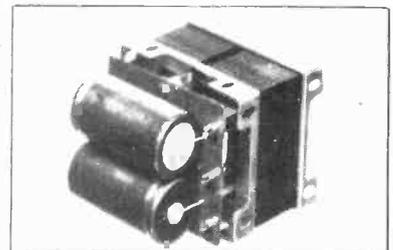

POWER SUPPLIES

PSU36 suitable for two HY30's £5.22 plus 65p VAT P.P. free.

PSU50 suitable for two HY50's £6.82 plus 85p VAT P.P. free.

PSU 70 suitable for 2 HY 120's £13.75 plus £1.10 VAT P.P. free.

PSU90 suitable for one HY200 £12.65 plus £1.01 VAT P.P. free.

PSU180 suitable for two HY2000's or one HY400 £23.10 plus £1.85 VAT P.P. free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 64723

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name & Address _____
Signature _____

ETI BOOK SERVICE

BEGINNERS

- Beginners Guide to **Electronics** Squires £2.65
Beginners Guide to **Transistors** Reddihough £2.55
Electronic Measurement Simplified C Hallmark £2.20
Electronics Self Taught Ashe £4.40
Beginners Guide to **Integrated Circuits** Sinclair £3.15
Principles of Transistor Circuits S. Amos £4.75
Understanding Electronic Circuits Sinclair £4.10
Understanding Electronic Components Sinclair £4.10
Beginners Guide to **Radio** King £3.15
Beginners Guide to **Audio** Sinclair £3.10
Beginners Guide to **Audio** L R Sinclair £3.20

COOKBOOKS

- TV Typewriters Cookbook £7.40
CMOS Cookbook £8.00
TTL Cookbook £7.55
Active Filters £11.00
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £9.40

APPLICATIONS

- Advanced Applications for **Pocket Calculators** J Gilbert £4.20
Build Your Own Working **Robot** D. Heiseman £3.35
Electronics and Photography R. Brown £2.30
Fire and Theft Security Systems B. Wels £2.00
How To Build **Proximity Detectors and Metal Locators** J Shields £3.35
How To Build **Electronics Kits** Capel £2.10
Linear Integrated Circuit Applications G. Clayton £5.00
Function Circuits Design & Applications Burr Brown £15.95
110 **Electronic Alarm Projects** R. M. Marston £3.45
110 **Semiconductor Projects for the Home Constructor** R. M. Marston £2.95
110 **Integrated Circuit Projects for the Home Constructor** R. M. Marston £3.25
110 **Thyristor Projects Using SCRs** R. M. Marston £2.95
Handbook of IC Circuit Projects Ashe £2.30
Practical Electronic Project Building Ainslie and Colwell £2.45

TV AND HI-FI

- Audio Handbook** G King £6.50
Cassette Tape Recorders J. Earl £5.25
Solid State Colour TV Circuits G. R. Wilding £6.35
Hi-Fi Loudspeakers and Enclosures Cohen £8.20
How To Build **Speaker Enclosures** Badmearff £3.10
Master Hi-Fi Installation King £2.80

LOGIC

- Logic Design Projects Using Standard ICs** J Wakerly £5.10
Practical Digital Design Using ICs J Greenfield £12.50
Designing With TTL Intergrated Circuits Texas Instruments £9.05
How To Use **IC Circuit Logic Elements** J Streater £3.65
110 **COSMOS Digital IC Projects for the Home Constructor** R. M. Marston £3.20
Understanding CMOS Integrated Circuits R. Melen £3.90
Digital Electronic Circuits and Systems R. M. Morris £3.50
MOS DIGITAL ICs G Flynn £4.60

COMPUTING

- Microprocessors and Microcomputers** B. Sowick £18.00
Microprocessor/Microprogramming Handbook B. Ward £4.10
Microprocessors D. C. McGlynn £8.40
Introduction to Microprocessors Aspinall £5.90
Modern Guide to Digital Logic (Processors, Memories and Interfaces) £4.30

OP-AMPS

- Applications of Operational Amplifiers** Graeme (Burr Brown) £8.30
Designing With Operational Amplifiers Burr Brown £13.75
Experiments With Operational Amplifiers Clayton £3.40
110 **Operational Amplifier Projects for the Home Constructor** R. M. Marston £2.95
Operational Amplifiers Design and Applications G. Tobey (Burr Brown) £7.40
Op-Amp Circuit Design & Applications I. Carr £4.00

TEST INSTRUMENTS

- Build It Book of **Minature Test Instruments** R. Haviland £3.55
The Oscilloscope In Use Sinclair £3.10
Test Instruments for Electronics M. Clifford £2.40
Working With the Oscilloscope A. Saunders £1.95
Servicing With the Oscilloscope G. King £5.60
Radio Television and Audio Test Instruments King £5.90

SERVICING

- Electronic Fault Diagnosis** Sinclair £3.20
Rapid Servicing of Transistor Equipment G. King £2.95
Tape Recorder servicing Manual Gardner Vol 1: 1968-70 £8.50
Vol 2: 1971-74 £8.50
FM Radio Servicing Handbook King £4.80
Basic Electronic Test Procedures I. M. Gottlieb £2.45

COMMUNICATIONS

- Communication Systems Intro To Signals & Noise** B. Carlson £7.50
Digital Signal Processing Theory & Applications L. R. Rabiner £23.80
Electronic Communication Systems G. Kennedy £8.50
Frequency Synthesis. Theory & Design Mannassewitsch £20.40
Principles of Communication Systems H. Taub £8.10

THEORY

- Introduction to Digital Filtering** Bogner £9.40
Transistor Circuit Design Texas Instruments £9.35
Essential Formulae for Electrical and Electronic Engineers N. M. Morris £1.65
Modern Electronic Maths Clifford £6.70
Semiconductor Circuit Elements T. D. Towers £6.40
Foundations of Wireless Electronics M. G. Scroggie £4.45
Colour Television Theory Hudson £6.20

REFERENCE

- Transistor Tabelle (Includes physical dimensions)** £4.10
Electronic Engineers Reference Book (Ed. 4) L. W. Turner £27.70
Solid State Circuit Guide Book B. Ward £2.25
Electronic Components M. A. Colwell £2.45
Electronic Diagrams M. A. Colwell £2.45
Indexed Guide to Modern Electronic Circuits Goodman £2.30
International Transistor Selector T. D. Towers £5.25
International FET Selector T. D. Towers £4.35
Popular Valve/Transistor Substitution Guide £2.25
Radio Valve and Semiconductor Data A. M. Bell £2.60
Master Transistor/Integrated Circuit Substitution Handbook £5.60
World Radio TV Handbook 1978 (Station Directory) £8.00
Radio, TV and Audio Technical Reference Amos £24.85
TV Technicians Bench Manual (New Ed.) Wilding £5.10

MISCELLANEOUS

- Integrated Electronics** J. Milman £7.70
Microelectronics Hallmark £3.90
Practical Solid State DC Supplies I. D. Fowers £6.20
Practical Triac/SCR Projects for the Experimenter R. Fox £2.25
Printed Circuit Assembly Hughes & Colwell £2.45

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy
way of getting your hands
on the right title.

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

MUSIC SYNTHESIZER

PART 2—CONSTRUCTION

In this concluding part of the article we cover the assembly procedure for this compact design.

DESPITE the high complexity of this project, its construction should pose no *electronic* problems to the competent hobbyist. As with any synthesiser however, fitting the keyboard and its associated mechanics will prove the most onerous task.

Getting Board

Since you have to start somewhere, the PCBs are the obvious place. There are five boards all together; power supply, keyboard contact mounting (X3) and main synthesiser. The keyboard we will deal with later.

Above: the finished article all set to be played. This prototype was assembled using the Powertran Electronics kit, which includes the woodwork. Below: an internal view showing the alignment of PCB and keyboard. Note very carefully

the relation of the two as there is not much space to spare. As you can see from this photo, we used IC sockets on all devices as it makes things so much easier if anything untoward should occur.



Assembly of the PSU board is very straightforward, but take care fitting the heatsinks to Q1 and Q3. Wire up the board to the transformer, and check that you can obtain the correct voltages at the output. Adjust RV1 until +12V is obtained on the red output wire.

Set to as close +12V as you can possibly measure. Check that an accurate -12V is present on the blue output wire. The power supply is now complete.

Main Line

For the main assembly we're going to assume that you're using the Powertran board. Fitting the components to this is straightforward with the exception of the switches and pots.

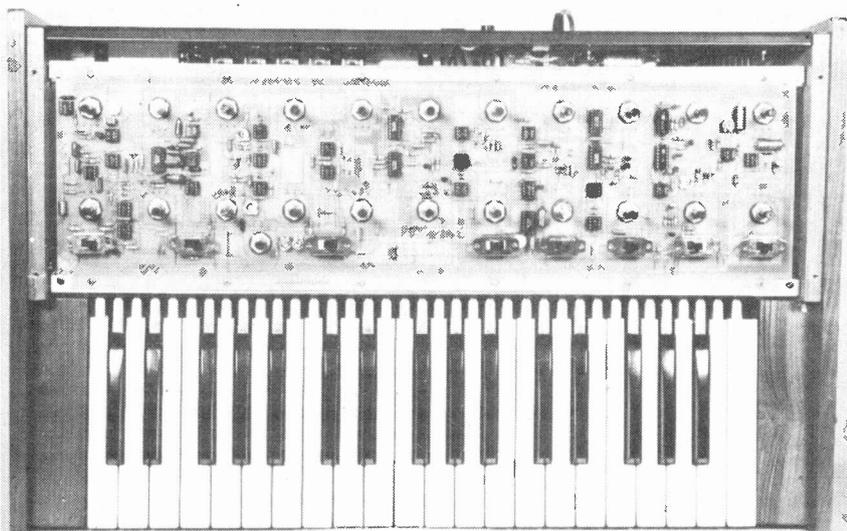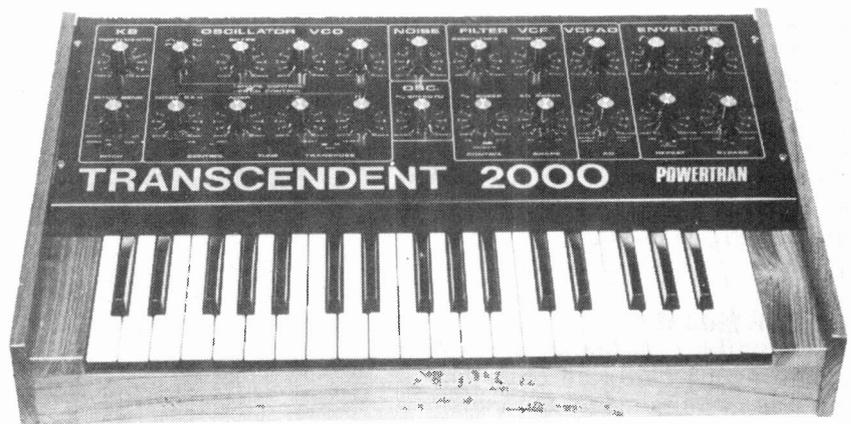In order to line up the switches with the front panel and pots, it is necessary to space these from the board — the kit contains suitable



spacers for this purpose. Non-kit types have to work out the height of their front panels from the board and act accordingly. The switch toggles must come level with the pot spindles, when cut to take the control knobs.

In either event glue the spacer to the board — use some powerful adhesive such as Super-Glue etc.

Cut the pot spindles before you fix them to the PCB: it's just too big to handle and too expensive to crack. The terminals should be top soldered onto the board, as should the chirpins used to mate up with the connector. Take care the solder does not run down the pins, else the plug may not fit at all.


Use insulated wire to link the dual gang pot RV30 and the waveform switch to the board. The PCB cannot be mounted into place until the alignment procedures have been carried out, so there is no excuse for not checking the assembly very carefully indeed, especially the IC orientation and soldering quality. This is a BIG board which means there is more space to be careless:—check it!

Powerfull Mount

Following the rear panel wiring diagram, fit the hardware onto the case, taking care to mount the transformer as low down—away from the main PCB—as possible. This will lessen the chance of hum being induced into the circuit.


Insulate the mains wiring wherever possible, and take careful note of the earth wiring arrangements—lest the demon hum return to plague thee! Anything with mains voltage on should have a rubber sleeve over it.

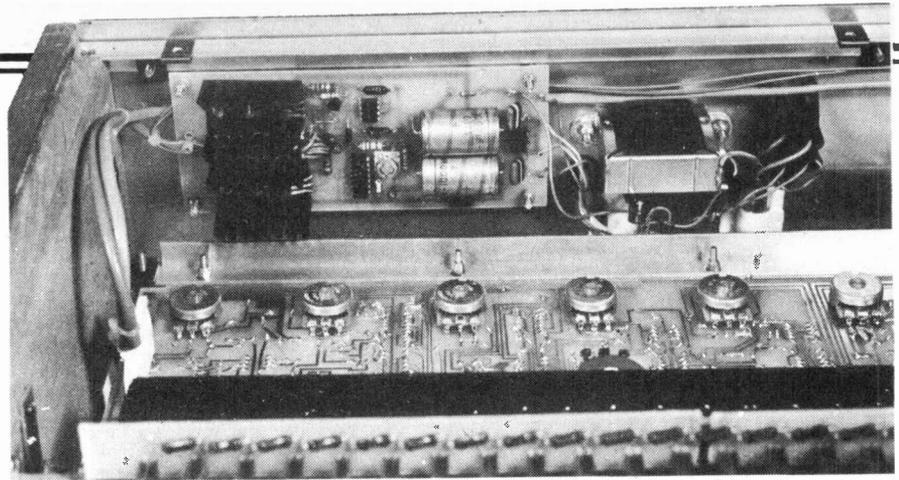The photograph shows the arrangement of PSU and transformer on the back panel.



Above: close up of the PSU board mounting within the case. Positioning the transformer is important to reduce the risk of hum. Mount this as low down, away from the board, as possible. In the foreground the resistor chain for the keyboard can be seen. Below: overall

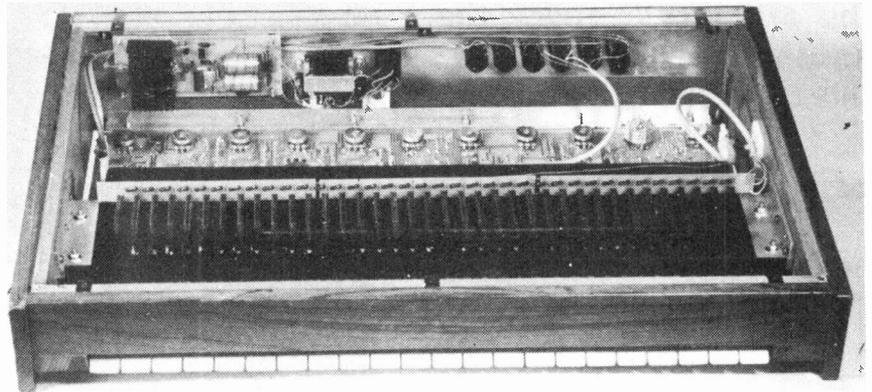view of the machine, to give an idea of what goes where in the box. Note the three Chiri connectors which fit onto the PCB on the end of these wires snaking across the photo. The black area to the front is the line of keyboard contact blocks.





Keyed Up?

Now for the tricky bit. The keyboard. This has to be mounted in the casing first. For this the front panel should be in position. Fix the brackets to the ends of the keyboard assembly, and lower it into place. Follow the diagram below to adjust the spacing at either end of the keyboard. If the



gap is more than 0.1", the woodwork underneath the fixing screws will need countersinking.

Set the gap between the black notes and the front panel as shown.

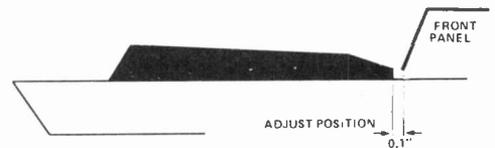
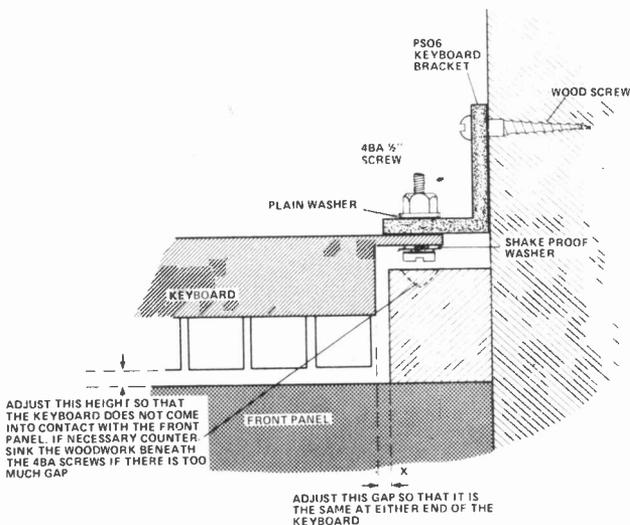
Once the alignment is correct, screw the brackets into the woodwork.



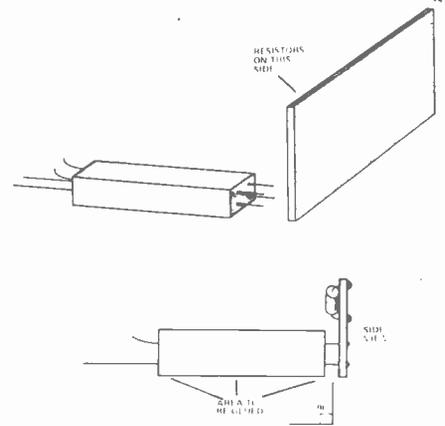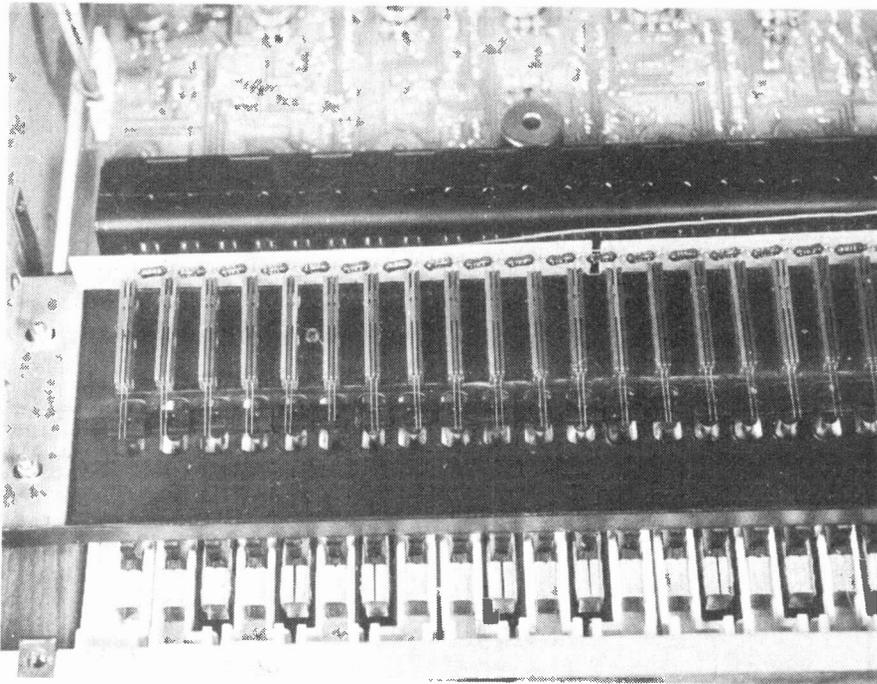On the left is the diagram you'll need to line up the keyboard assembly with the casing and front panel. Follow this as carefully as you can, as if the keys are not in the right places, the contact blocks will not line up with the plungers, and the keys themselves will probably foul the front panel. Above is shown the alignment of keys and panel.



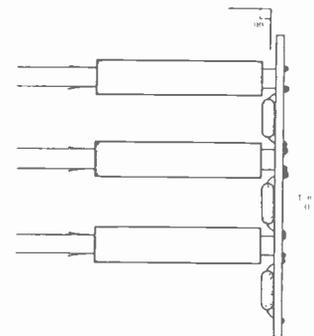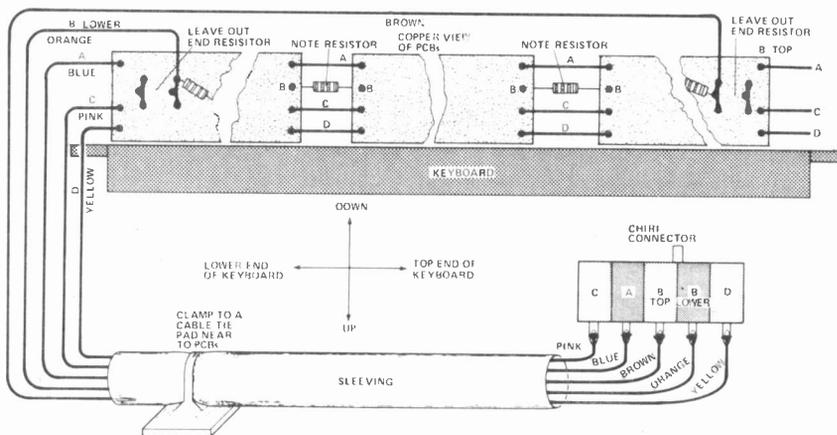Contact blocks and resistors and where to put 'em. Follow the drawing above to fit the block to the PCB, and then line up the angle as shown below. On the lower left is the keyboard wiring diagram which shows the connecting together of the boards and the placing of the two spare resistors. The photograph shows what it all looks like when you've finished.



Onto the contacts. Fit and solder the 27R4 resistors to the three PCBs as shown on the diagram above. One will be full with 12 resistors and the other two have eleven each, one missing at the right end on one PCB, and one missing at the left end of the other. (There are two resistors left over at this stage.)

Close Contacts Of The Key Kind
Solder in the contact assemblies, but make very sure that right angles exist between the block and the PCB. This is important. Graph paper may help in lining up.

Leave out a contact block where the resistors are omitted the diagram may help.

All three PCBs are wired together as shown in the keyboard wiring diagram taking care to place the 'gaps' correctly. Get the spacing correct by lining up the contact blocks with the keyboard plungers. Note the positioning of those two spare resistors.

Sand down one side of the contact strip, and lay some contact adhesive all over it, and the same with the soldered-in contact blocks. Make very sure that before you affix the strip onto the blocks that you have lined it up properly, as once the glue gets hold you've had it.

The contact blocks are very delicate, so handle them carefully, and don't touch the wires with your

fingers. If you do you'll leave a deposit behind which may well cause malfunction. When satisfied that the assembly is O.K. position it over the plungers, and screw it down to the metalwork. Check that every plunger operates a contact, and that both contacts in each block operate when the key is depressed.

Keyboard completed — wasn't that bad after all (was it?)

The contact assembly for the keyboard should be the last thing you fit into place before wiring up all the boards as per the interconnection and wiring diagrams. With this in place fit the base plate.

Alignment is best carried out with the front panel removed, and the PCBs fixed in. Before commencing alignment though, check everything very carefully.

When attaching the front panel to the machine, check that it does not foul the keyboard, and that the gap between it and the woodwork is the same at either end.

Alignment

This will be dealt with in sections. To aid setting up and alignment procedures, test point waveforms are given for important nodes throughout the design.

VCO Alignment

There are several pitch controls for the VCO. All control voltages are injected via large resistors and are thus suitably attenuated. The pitch bend pot uses a couple of diodes to produce a dead zone in the middle of its motion. This control voltage is then fed in via a 180k resistor and mixed with all the other control voltages.


Pitch Spread

The keyboard sample and hold produces 830mV/octave. This has to be attenuated to 18mV to produce octaves. To do this, a resistor of 46k is required. R31 and RV3 constitutes a variable resistor (39k2 to 49k2) that should enable the keyboard pitch spread to be aligned.

Turn RV6, 7, 8, 9 fully anticlockwise. Put the transpose switch in its central position. Set RV5, 4 to their central position. Play the top note on the keyboard and measure its frequency, using a scope or a frequency meter, or maybe if you are a musician just listen to it! Now play a note one octave below it and adjust RV3 until the interval is one octave below it and adjust RV3 until the interval is one octave. Recheck the top note and then try the tracking for two or three octaves down, making any necessary adjustments to RV3. Note that the top note on the keyboard is not affected by RV3 adjustments. Now put the transpose switch to +2 octaves and adjust RV12 for a 2 octave increase. Then switch to -2 octaves and adjust RV13 for a 2 octave decrease.

VCO Shape Modulation

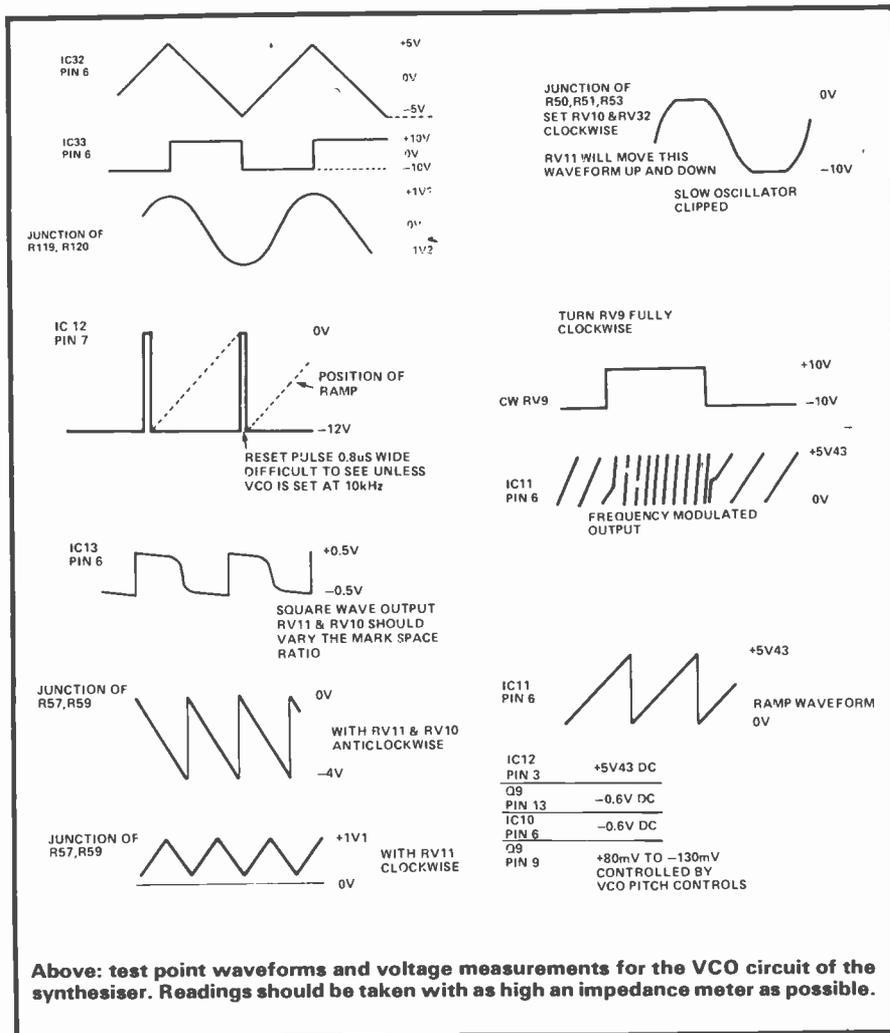IC14, 13, 15 is the VCO shape modulation circuitry. IC14 is a half wave rectifier, and is used to sum together the manual shape voltage



Above: test point waveforms and voltage measurements for the VCO circuit of the synthesiser. Readings should be taken with as high an impedance meter as possible.

(RV14), and the sine wave voltage from the slow oscillator. The output from this circuit is limited to a range of 0 V to about -10 V. As the manual shape pot is rotated clockwise the waveform at the junction of R57, R59 will change from a ramp into a triangle, this being due to the full wave rectification. With RV14 fully clockwise and RV15 anticlockwise adjust RV15 so that the waveform is a symmetrical triangle.

The last shape generator is a fast comparator. The ramp waveform plus the modulation voltage are fed into the comparator input. The modulation voltage shifts the DC level of the ramp and in doing so the comparator levels change resulting in a varying markspace ratio output, IC15 pin 6. The diodes limit the voltage excursion to about ± 0.5 V.

Set the VCO to +2 octaves, tune the keyboard high and play the highest note. Now set RV10 anticlockwise, RV14 clockwise and monitor

the squarewave output, IC13 pin 6. Adjust RV11 until a very thin pulse is generated. Rotate RV14 anticlockwise and the markspace ratio will revert to 1 to 1. Now set RV14 to 5 on the dial and slowly rotate RV15. The markspace ratio will be modulated at the speed of the slow oscillator.

There may be some problems with control breakthrough in the VCA but this can be minimised with a preset adjustment, RV22. Turn the VCO and noise levels to 0. Make sure that the filter is not oscillating. Put the ADSR on a fast repeat with fast attack and decay and no sustain level. Set the BY-PASS switch to ADSR and look at the synthesiser output. There will probably be some control breakthrough caused by the ADSR, which will sound like a series of thumps. By adjusting RV22 a minimum in the thump level will be found. Just like the 3080s in the VCF, best performance can be obtained by carefully selecting IC22.

PARTS LIST

RESISTORS (all 1/4W 5% unless stated)

R1, 18, 55, 58, 120, 127	4k7	
R2, 8, 43	10k	(0.5%)
R3, 49, 133	12k	
R4, 7	3R3	
R5, 37, 38	6k8	(1%)
R6, 83, 96	1k0	
R9	4k75	(1%)
R10, 80, 81	680R	
R11, 78, 61	27k	
R12, 16, 22, 23, 70	39k	
R13, 84	100R	
R14, 27, 48, 60, 69, 136	220k	
R15	1k5	
R17, 28, 29	10M	
R19, 51, 56, 64, 75, 77, 79, 89, 90, 93-95, 97, 101, 103-108, 122, 128, 137	100k	
R20	470k	
R21, 57, 102, 114, 119, 132	22k	
R24, 30, 47, 86, 118, 121, 126, 131, 134	47k	
R25, 36, 59, 85, 87, 88, 91, 109, 113 115-117	10k	
R26, 35, 39, 82, 92, 98, 100, 135	1M0	
R31, 65	39k2	(1%)
R32	680k	
R33, 66	130R	
R34	870R	(RTC)
R39	1M	(0.5%)
R40, 62, 138	56k	(2%)
R41	470R	
R42, 74	15k	
R44	12k1	(1%)
R45	2k7	
R46	309k	(0.5%)
R50, 130	150k	
R52	120k	
R53, 54	7k5	
R63, 71	390R	
R67	820R	(RTC)
R68	15k	
R72, 73, 110	2k2	
R99	3k9	
R111	390k	
R112, 123	82k	
R124	330R	
R125	8k2	
R129	68k	
Keyboard chain (37 off)	27R4	(0.5%)

POTENTIOMETERS

RV1, 3	10k	cermet
RV2, 23-27	1M	log
RV4, 5, 15, 21	100k	lin
RV6-10, 14, 17, 18, 28, 29	10k	lin
RV11 22, 28	100k	lin preset
RV12, 13	50k	cermet
RV16, 32	100k	log
RV19, 33	10k	log
RV20	10k	lin preset
RV30, 31	10k	lin (ganged)

CAPACITORS

C1, 2, 10, 18, 26, 27, 29, 30, 32, 34		
43, 45	100n	polyester
C3, 4	1000u	25V electrolytic
C5, 7, 8, 37	2u2	25V tantalum
C6	330p	polystyrene
C9	1u0	25V electrolytic
C11, 14, 15, 17	22n	polyester
C12, 19-21, 35, 36, 31, 48	10n	polyester
C13	330n	polystyrene
C16, 28, 33, 46	1n0	polystyrene
C22, 44	3n3	polystyrene
C23	22p	ceramic
C24	5p0	ceramic
C25, 41, 42, 47	1u0	25V tantalum
C39, 40	100u	25V electrolytic

SEMICONDUCTORS

IC1	uA 723C
IC2, 3-5, 7, 8, 10, 14, 15, 18, 21, 29, 31-33	741
IC6, 9, 11, 17, 20, 30	CA 3140
IC12	LM311
IC13	748
IC16, 19, 22	CA3080
IC25, 26	CD 4001
IC27, 28	CD 4016
IC34	CD 4030
IC35	CD 4006
Q1	TIP 29A
Q2	BC 213
Q3	TIP 30A
Q4, 5	BF 244C
Q6, 13, 15, 20-22	BC 182
Q7, 9, 10, 12	CA 3046 (2 off)
Q8	2N 4859
Q11, 14, 16-19	BC 212
D1-37	1N 4148
ZD1	4V7 400mW
ZD2, 4	5V6 400mW
ZD3	3V3 400mW
BR1	RS 261 772 (1A at 400V)

SWITCHES

SW1	DPDT 250V AC
SW2, 3, 6, 8, 9	single pole slide changeover
SW4	1 pole (2 way) rotary
SW5, 7, 10	double pole slide changeover

MISCELLANEOUS

Five 1/4" mono jack sockets, one 1/4" stereo jack socket (all panel mounting), 37 note keyboard with contact blocks, woodwork and case to suit, PCBs, three core mains lead, knobs to suit, OA5 fuse with holder, 240V to 15-0-15V at 200mA transformer, three five-pin Chiri connectors, eight spacing blocks for switches, one foot pedal unit with cable (optional), grommets.

VCF Alignment

The VCF pitch spread should be set up as follows. Turn off RV16 and RV33. Switch the filter 'CONTROL' to KB, the 'RESONANCE' to 'OSC' and the 'AD SWEEP' to 0. Play the top note on

the keyboard and adjust the 'FREQUENCY' pot to give a 1kHz sinewave output. Now play a note, one octave below the top note and adjust the present RV20 for a one octave decrease. Check the lower octaves making any necessary adjustments to RV20.

Turn the Resonance pot anticlockwise until the filter stops oscillating. Turn up the VCO level and insert a ramp waveform at a frequency of about 100Hz. Now switch the VCF 'Control' to RANDOM. The tone of the filtered signal should now vary randomly.

Main overlay for the Transcendent 2000 synthesiser design. As you may notice only a little over half the board is shown here. The other half you'll find over the page.


The reason for this is simply that with a PCB of this size our pages are too small to hold the diagram and still have it readable.

Foil patterns are not shown here, and the PCB is available from Powertran — see BUYLINES for details.

The two sets of contacts shown are mated with the Chiri connectors from the back panel wiring. Make sure the pins are straight, and that no solder has run down from the board, or the plug will not fit properly.

On the lower right is shown the PSU board overlay. Note that Q3 and Q1 require to be heat-sinked for correct operation.

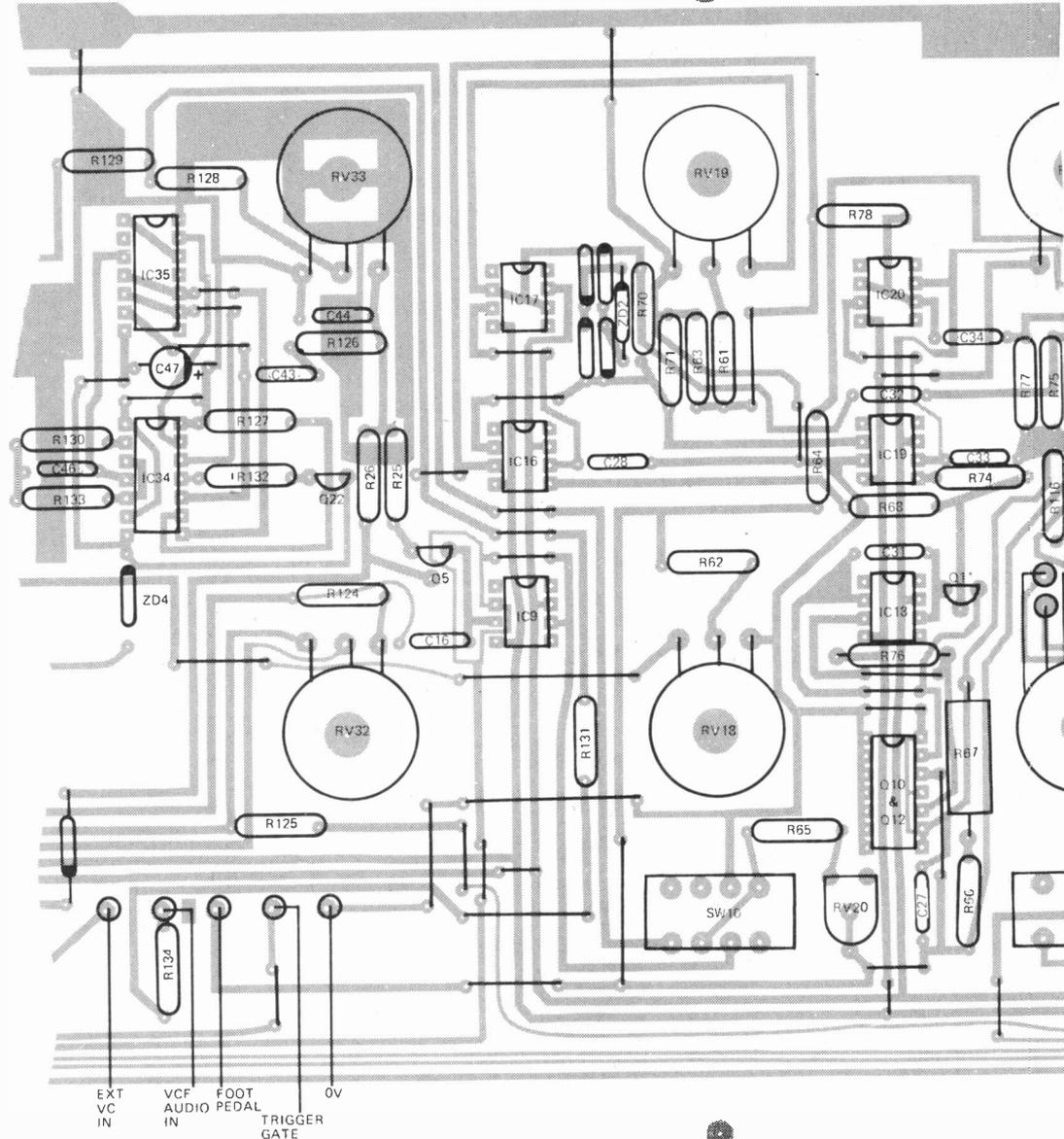Both the boards should be checked very carefully during assembly, and make sure you use the switch spacers on the main PCB. Cut the pot spindles *before* mounting them.



Problems?

Any problems in the VCF circuitry are likely to emanate from IC16 or IC19. If there are any large input offset voltages or current mirror imbalances or output leakage currents, then these will degrade the VCF performance. What will probably occur is that there will be a large DC offset voltage on the outputs that varies as the resonant frequency varies. This may cause severe signal dipping at certain frequencies and will only be cured by replacing the errant 3080.

The filter has two outputs, a bandpass and a lowpass. The signal volume will generally be less from the bandpass output because this output

attenuates all but the harmonics that lie close to its own resonant frequency, whereas the lowpass output has a flat response area which extends from somewhere just below resonance down towards low frequencies, and harmonics in this region are not affected.

Sweeping Statement



The 'synthesiser sound' is generated by sweeping the VCF resonant frequency with an AD waveform. This sweep voltage is variable in both depth and direction. The sweep pot is a dual pot; on one of its tracks there is an AD waveform at one end and the inverse at the other. Thus the wiper


will pan from a sweep going upwards to one going downwards. Two diodes provide a dead zone in the middle so that a pot position of No Sweep can be easily found. The second track on the AD sweep pot is used to provide a compensating DC level shift so that the frequency pot doesn't need to be returned when the AD sweep depth is altered.

ADSR Alignment

Set up the VCO and VCF so that a ramp waveform at 500 Hz is presented to the VCA. Turn the RELEASE pot fully clockwise and put the BYPASS switch in the ADSR position. Listen to the VCA output

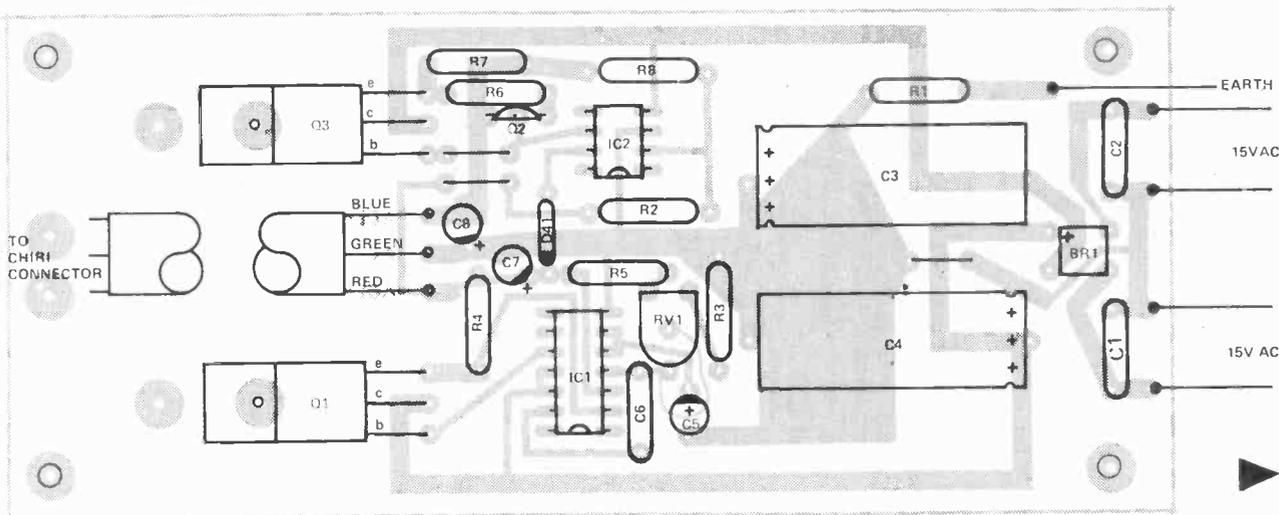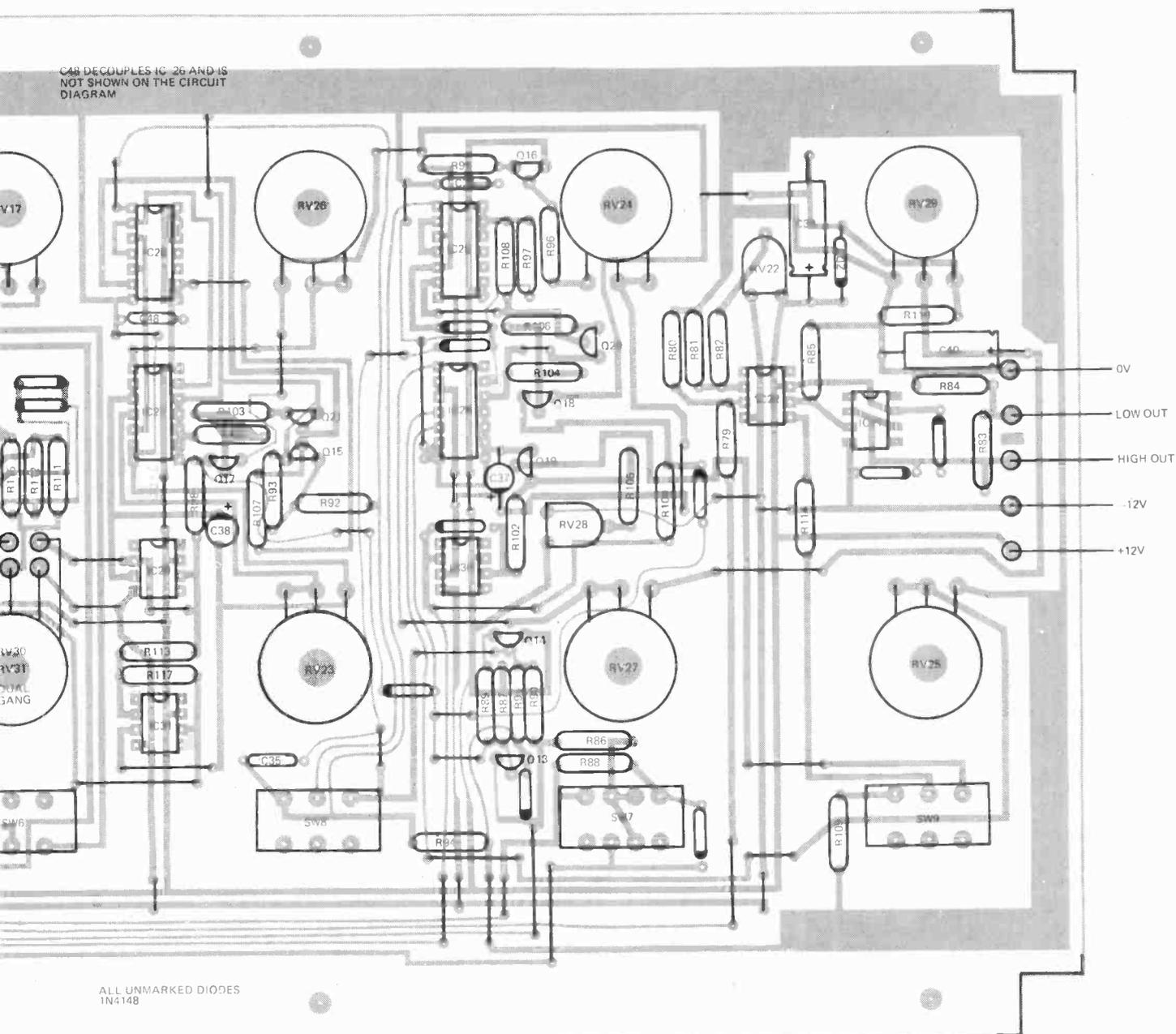C48 DECOUPLES IC 26 AND IS NOT SHOWN ON THE CIRCUIT DIAGRAM



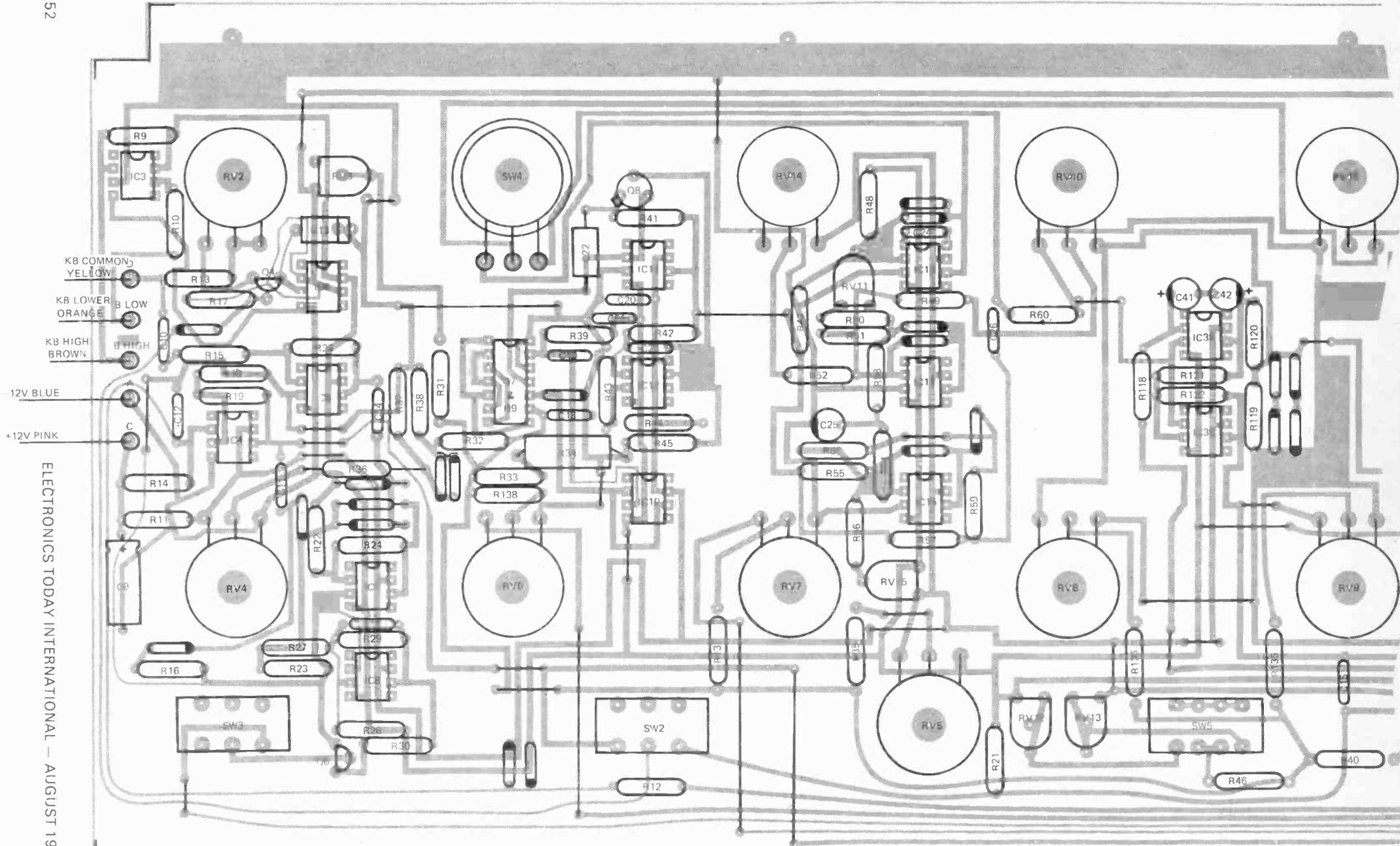

Above: the other half of the synthesiser PCB Connections is made to the pins in the upper left-hand corner by the keyboard wiring Chiri connector.

ALL UNMARKED DIODES
1N4148

and adjust RV28 so that the signal only just disappears. Now you can play the keyboard and experiment with different sounding envelopes.

This completes the alignment procedures for the design, and the front panel can now be fitted over the main PCB and the control knobs added.

Take care with the panel and keyboard positioning. See the diagrams where applicable.

Program Sheets


Once your machine is up and running, you will find that if you use it frequently, some method of recording various settings would be useful. This gives the ability to return to a particular sound very quickly and can be particularly useful in stage work.

As an aid to usage ETI is making available Program Sheets for the Transcendent 2000. These allow *all* control settings to be recorded for any configuration, and each sheet will record three completely independent sound settings. These cost 50p for six, including postage, from our 25-27 Oxford Street address. Mark the envelope "2000 Program Sheets".


Clearing Points

Play testing since last month's article has shown that the synthesiser works better if. (numbers referred to circuit diagrams and overlay) C17 is changed in value to 4n7, as this increases the NPD sensitivity and C9 is removed entirely from the circuit, this preventing 'clicking' which sometimes arose upon operation of the keyboard.

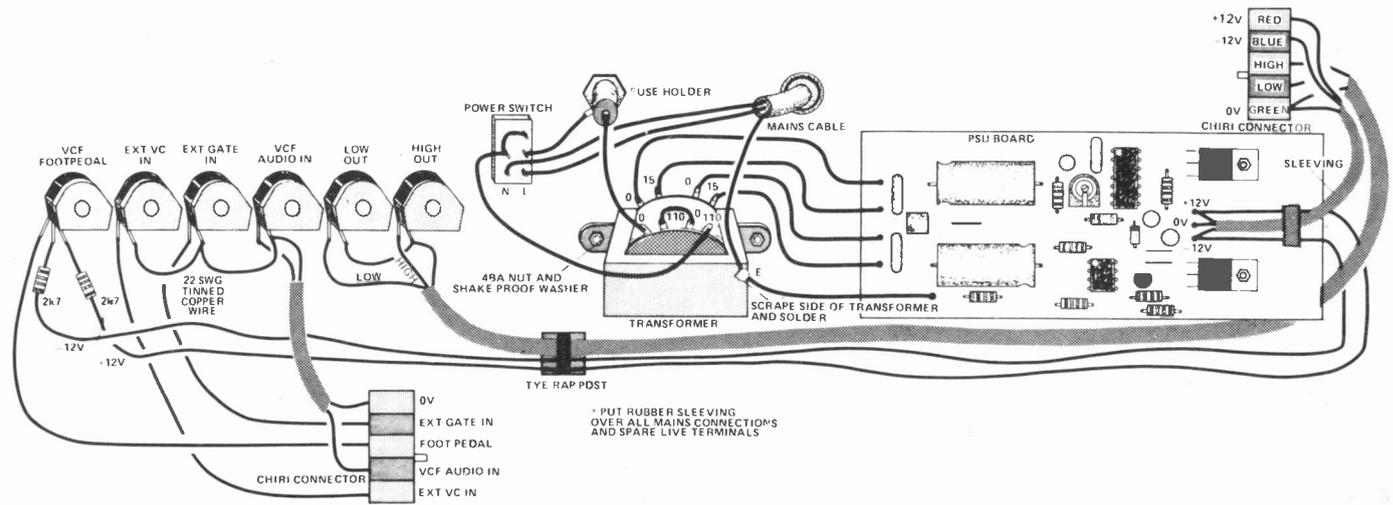Two minor gremlins to be laid to rest. Last month we gave (on the circuit) the circuit reference for the Transpose switch as SW3. It should be SW5. Also the undesignated KB/Noise switch is in fact SW10. **ETI**



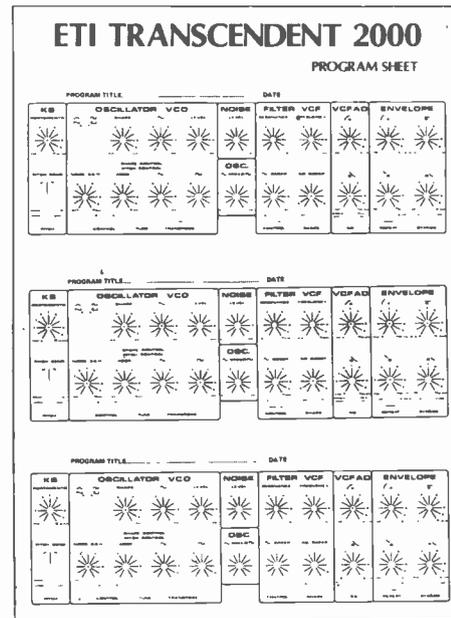Above: back panel wiring diagram. The connectors attach to the main PCB as shown on the overlay. The mains switch supplied with the kit contains a neon and the wiring takes account of this. If you use a different type of switch, the wiring will be different. Below: an example of the program sheets for the Transcendent 2000. These are used by simply marking on the settings for each control.



BUYLINES

A complete set of parts for this project, including all woodwork, metalwork, nuts and bolts, PCBs and components will be available from Powertran Electronics.

The machine used to illustrate this article was assembled using this kit, and constructional details will be based upon it. Kits will **only** be available from Powertran, as will the PCB. Because the design is based upon a single board construction, we cannot

offer advice to people wishing to modify the synthesiser to a 'modular' form.

The price of the complete kit, including keyboard, will be £186.50 + VAT. However, if you're quick and put in your order before July 30th you can take advantage of an introductory offer at an even lower price of £172 + VAT.

Powertran Electronics, Portway Industrial Estate, Andover, Hants.

electronics today

international

SEPTEMBER ISSUE: ON SALE 4th AUGUST



THE SHUTTLE

NASA's Shuttle seems to have been hidden in the wake of the Apollos: although it represents the next (and very important) step in the colonisation of space, the details of this dumpy 'space bus' have up till now been somewhat neglected. We take the wraps off the Shuttle and show that there's still plenty of high-technology innovation taking place in the States.



Stage Lighting Unit

A professional-quality unit suitable for a studio theatre: a two-master control desk allows the lighting for the next scene to be set up ready for an instant change-over; 19"-rack modular SCR power handling units allow a choice of 2.5 kW per channel with easy maintenance and the capability to drive fluorescent lamps without ballast resistors; a modified control curve gives a subjectively more linear light output response; a minimum-output control gives extended bulb life. All of these features have been designed into a unit which, without technical compromise, is still very cheap indeed compared to current commercial systems.

CROSS-HATCH GENERATOR

Setting up a TV set can be a worrying task. At least with this design you don't have to worry about test equipment as well — it produces a UHF signal for direct insertion into the aerial socket.



FEATURE: Rock Sound

Concert sound systems come in many different sizes, shapes and forms and we've yet to find two that sound identical. So how much do you go about designing a state-of-the-art system which will stand up to the rigours of the road? We take a look at the 28 ton (yes, ton!) system used by Abba and Rod Stewart when they toured Australia last year.

Wheel of Fortune

An electronic roulette wheel — not just another LED dice unit, but an all-singing, all-dancing sonic and visual wheel of fortune electronic simulation! Step right this way, folks.

THE MK14 REVIEWED

At under £50 the Science of Cambridge MK 14 microprocessor evaluation kit must surely be the cheapest on the market — how good is it?

Features mentioned here are in an advanced state of preparation but circumstances may affect the final contents.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rets and zeners may all be included. These are being offered at the incredibly low price of **£1.25/1,000** — or a bag of 2,500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

SPECIAL SUMMER OFFERS

Audio IC's

76003N	£1.40	76013N	£1.00
76023N	£1.00	76033N	£1.40
LM380	80p	TBA8108	90p

Linear ICs etc.

741 (8DIL)	18p	BD131	24p
555	25p	BD132	28p
1N4148	2p	2N3819	18p

TTL PANEL

52 logic ICs including 32 x 74161 (4 bit binary counter) + 16 tant bead caps, R's, C's, etc. Over £30 worth of TTL alone!! ONLY **£3.00**.

DISC CERAMIC PACK

Amazing variety of values and voltages from a few pF to 2.2uF! 3V to 3kV! 200 **£1.500** £2.25, 1,000 **£4.00**.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.25**.

EDGE CONNECTORS

Special purchase of these 0.1 pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!
18 way **41p**; 21 way **47p**; 32 way **72p**; 40 way **90p**.

VEROCASES

Plastic top and bottom, ally panels front and back.

1237	154x85x40	£2.53
1238	154x85x60	£2.79
1239	154x85x80	£3.32
3007	180x120x40	£3.30
3008	180x120x65	£3.50
3009	180x120x90	£3.74
1410	205x140x40	£3.51
1411	205x140x75	£4.05
1412	205x140x110	£5.12

VERO PLASTIC BOXES

Professional quality two tone grey polystyrene with threaded inserts for mounting PC boards

2518	120x65x40	£2.17
2520	150x80x50	£2.45
2522	188x110x60	£3.23

SLOPING FRONT BOXES

1798	171x121x75/37.5	£4.19
2523	220x174x100/53	£6.90

Potting box, 71x49x24mm black or white **40p**

Hand controller box 94x61x23mm, white **64p**

VERO PINS AND TOOL

Spot face cutter for 0.1 or 0.15 pitch **75p**
0.1 pins single sided **30p/100**
0.1 pins double sided **35p/100**
0.15 pins single sided **30p/100**
0.15 pins double sided **35p/100**

We keep a very large range of VERO products — inc. their recently introduced G range of cases, and Series II boxes. SAE for their catalogue.

LOW COST PLASTIC BOXES

Made in high impact ABS. The lids are retained by 4 screws into brass inserts. Interior of box has PCB guide slots (except V219).

V210	80x62x40mm black	58p
V213	100x75x40mm black	72p
V216	120x100x45mm black	86p
V219	120x100x45mm white	86p

STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls Bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2.00** — or buy the amp, case and transformer for **£10.00** and get DIN speaker sockets and knobs free!!

AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and vol./on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add **£2.20** for suitable transformer) Blue vinyl covered aluminium case to suit (W372) **£1.30**.

1977/8 CATALOGUE

48 BIG pages packed with over 4,000 items, many of them illustrated. Discount vouchers worth 50p. PRICE **30p + 15p** post. (Overseas send **60p** surface of **£1** airmail.) Also included is our current Bargain List. Send SAE for bargain list alone.

SIRENS

Use in cars, houses, anywhere that a powerful noise will frighten off would-be intruders. Uses 4 HP7 bats. Overall size 100x72x60mm. Only **£1.70**.

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

* **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

* **SAVE ON MONEY** — Bulk buying means lowest prices — just compare with others!

* **HAVE THE RIGHT PART** — No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC BRAND NEW, MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5% 10 of each value 22pF to 1000pF. Total 210. **£3.35**

K002 Extended range, 22pF to 0.1µF. 330 values **£4.90**

K003 Polyester capacitors, 10 each of these values 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4.75**

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**

K009 Extended mylar pack. Contains all values from 1000pF to 0.47µF. Total 290 capacitors to **£11.25**

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 Series 5% 160V. Total 370 for **£12.30**

K006 Tantalum bead capacitors, 10 each of the following 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V. 10/25, 15/16, 22/16, 33/10, 47/6, 100/3. Total 170 tants for **£14.20**

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**

K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.00**

K022 Extended range, total 850 resistors from 1R to 10M **£8.30**

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V. E24 series. Total 280 for **£15.30**

K042 As above but 5 of each value **£8.70**

PET 2001

SOFTWARE

AVAILABLE NOW!

SOPHISTICATED, INTENSELY PRACTICAL AND EASY-TO-USE SOFTWARE, covering:

- 01 Investment Decisions
- 02 Statistics
- 03 Mathematics
- 04 Personal Finance Management
- 05 Small Business Management
- 06 Appointment Scheduling
- 07 Stock Exchange Portfolio Management
- 08 P.A.Y.E.

For further details, please apply:

**DAVID JAMES
EDINSMITH COMPUTER SERVICES
11 STOKE HILL
STOKE BISHOP
BRISTOL, BS9 1JL**

data sheet

7208 COUNTER/DECODER/DRIVER

INTERMIL

The ICM 7208 is available ex stock from Rapid Recall Ltd, 9 Betterton Street, Drury Lane, London, WC2.

Features:

- Useful for:
 - a. Unit counter
 - b. Frequency counter
 - c. Period counter
- Low operating power dissipation < 10mW
- Low quiescent power dissipation < 5mW
- Counts and displays 7 decades
- Wide operating supply voltage range
 $2V \leq V_{DD} - V_{SS} \leq 6V$
- Drives directly 7 decade multiplexed common cathode LED display
- Internal store capability
- Internal inhibit to counter input
- Test speedup point
- All terminals protected against static discharge

Description

The ICM 7208 is a fully integrated seven decade counter-decoder-driver and is manufactured using the Intersil low voltage metal gate C-MOS process. As such it has applications as either a unit, frequency or period counter. For unit counter applications the only additional components are a 7 digit common cathode display, 3 resistors and a capacitor to generate the multiplex frequency reference, and the control switches.

Specifically the ICM 7208 provides the following on chip functions: a 7 decade counter, multiplexer, 7 segment decoder, digit & segment drivers, plus additional logic for display blanking reset, input inhibit, and display on/off.

The ICM 7208 is intended to operate over a supply voltage of 2 to 6 volts as a medium speed counter or over a more restricted voltage range for high frequency applications.

As frequency counter it is recommended that the ICM 7208 be used in conjunction with the ICM 7207 Oscillator Controller which provides a stable HF oscillator, and output signal gating.

Testing Procedures

The ICM 7208 is provided with three input terminals: 7,23,27 which may be used to accelerate testing. The least two significant decade counters may be tested by applying an input to the 'COUNTER INPUT' terminal 12. 'TEST POINT'

terminal 23 provides an input which bypasses the 2 least significant decade counter. Similarly terminals 7 and 27 permit rapid counter advancing at two points further along the string of decade counters.

Counter Input Definition

The internal counters of the ICM 7208 index on the negative edge of the input signal at terminal #12.

Format Of Signal

The noise immunity of the Signal Input Terminal is approximately 1/3 the supply voltage. Consequently, the input signal should be at least 50% of the supply in peak to peak amplitude and preferably equal to the supply. NOTE: The amplitude of the input signal should not exceed the supply; otherwise, damage

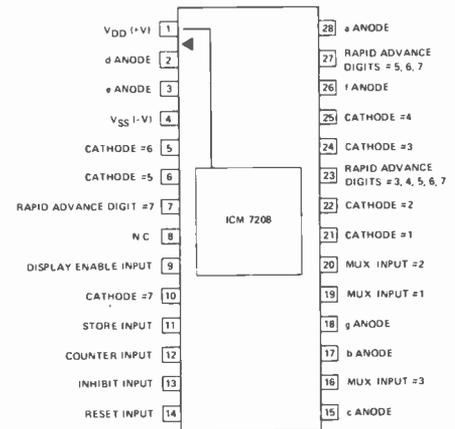


Fig. 1. Pinout.

Fig. 2. Absolute maximum ratings.

Power Dissipation (Note 1)	1 watt
Supply voltage $ V_{DD} - V_{SS} $ (Note 2)	6 V
Output digit drive current (Note 3)	150 mA
Output segment drive current	30 mA
Input voltage range (any input terminal)	Not to exceed the supply voltage
Operating temperature range	-20°C to +70°C
Storage temperature range	-55°C to +125°C

*Absolute maximum rating define parameter limits that if exceeded may permanently damage the device.

Fig. 3. Typical operating characteristics.

($V_{DD} - V_{SS} = 5V$, $T_A = 25^\circ C$, TEST CIRCUIT, display off, unless otherwise specified)

PARAMETER	SYMBOL	CONDITIONS	MIN	TYP	MAX	UNITS
Quiescent Current	I_{DD1}	All controls plus terminal 20 connected to V_{DD} . No multiplex oscillator		30	100	μA
Quiescent Current	I_{DD2}	All control inputs plus terminal 20 connected to V_{DD} except store which is connected to V_{SS}		70	150	μA
Operating Supply Current	I_{DDS}	All inputs connected to V_{DD} , RC multiplexer osc operating $f_{in} = 25KHz$		210	500	μA
Operating Supply Current		$f_{in} = 2MHz$			700	μA
Supply Voltage Range	V_{DD}	$f_{in} = 2MHz$	3.5		5.5	V
Digit Driver On Resistance	R_D			4	12	ohm
Digit Driver Leakage Current	I_D				500	μA
Segment Driver On Resistance	R_S			40		ohm
Segment Driver Leakage Current	I_S				500	μA
Pullup Resistance of Reset or Store Inputs	R_p		100	400		Kohms
Counter Input Resistance	R_{IN}	Terminal 12 either at V_{DD} or V_{SS} potentials			100	Kohms
Counter Input Hysteresis Voltage	V_{HIN}			25	50	mV

NOTE 1 This value of power dissipation refers to that of the package and will not be obtained under normal operating conditions.

NOTE 2 The supply voltage must be applied before or at the same time as any input voltage. This poses no problems with a single power supply system. If a multiple power supply system is used, it is mandatory that the supply for the ICM 7208 is not switched on after the other supplies otherwise the device may be permanently damaged.

NOTE 3 The output digit drive current must be limited to 150 mA or less under steady state conditions. (Short term transients up to 250 mA will not damage the device.) Therefore, depending upon the LED display and the supply voltage to be used it may be necessary to include additional segment series resistors to limit the digit currents.

may be done to the circuit.

The optimum input signal is a 50% duty cycle square wave equal in amplitude to the supply. However, as long as the rate of change of voltage is not less than approximately $10^{-4} V/\mu\text{sec}$ at 50% of the power supply voltage, the input waveshape can be inusoidal, triangular, etc.

Display Considerations

Any common cathode multiplexable LED display may be used. However, if the peak digit currents exceeds 150 mA for any prolonged time, it is recommended that resistors be included in series with the segment outputs (terminals 2, 3, 15, 17, 18, 26, 28) to limit current to 150 mA.

The ICM 7208 is specified with $500 \mu\text{A}$ of possible digit leakage current. With certain new LED displays that are extremely efficient at low currents, it may be necessary to include resistors between the cathode outputs and the positive supply V_{DD} to bleed off this leakage current.

Display Multiplex Rate

The multiplex frequency reference is divided by eight to generate an 8 bit sequencer. Thus the display multiplex rate is one eighth of the multiplex frequency reference.


The ICM 7208 has approximately $0.5 \mu\text{s}$ overlap between output drive signals. Therefore, if the multiplex rate is very fast, digit ghosting will occur. The ghosting determines the upper limit for the multiplex frequency reference. At very low multiplex rates flicker becomes visible.

It is recommended that the display multiplex rate be within the range of 50 Hz to 200 Hz which corresponds to 400 Hz to 1600 Hz for the reference frequency.


Control Input Definitions

INPUT	TMNL	VLTG	FUNCTION
1. Display	9	V_{DD}	Display on
		V_{SS}	Display off
2. Store	11	V_{DD}	Counter Inform. Stored
		V_{SS}	Counter Inform. Transferring
3. Inhibit	13	V_{DD}	Input to Counter Blocked
		V_{SS}	Normal Opertn.
4. Reset	14	V_{DD}	Normal Opertn. Counters Reset
		V_{SS}	Counters Reset

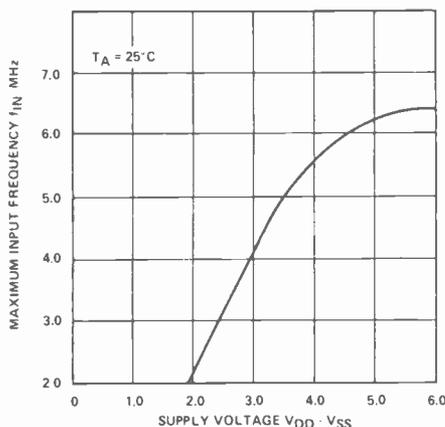
MAXIMUM COUNTER INPUT FREQUENCY AS A FUNCTION OF SUPPLY VOLTAGE



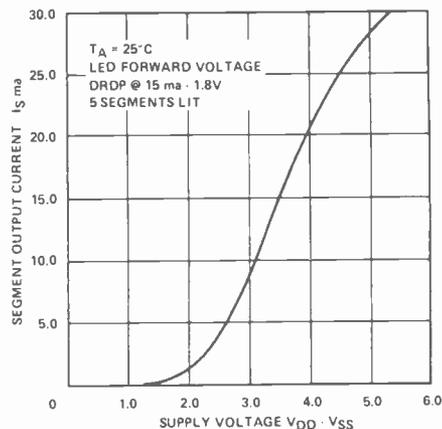SEGMENT OUTPUT CURRENT AS A FUNCTION OF SUPPLY VOLTAGE



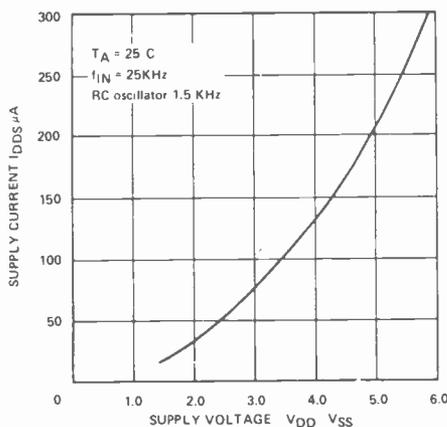SUPPLY CURRENT AS A FUNCTION OF SUPPLY VOLTAGE



SUPPLY CURRENT AS A FUNCTION OF COUNTER INPUT FREQUENCY

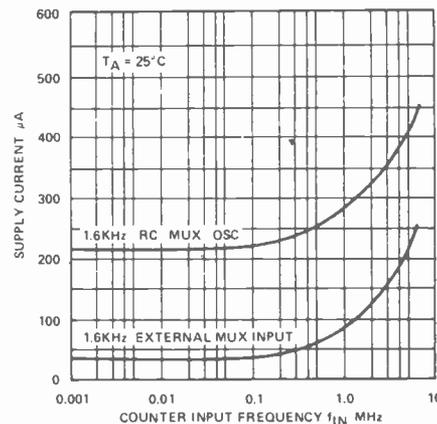


Fig. 4. Typical performance characteristics

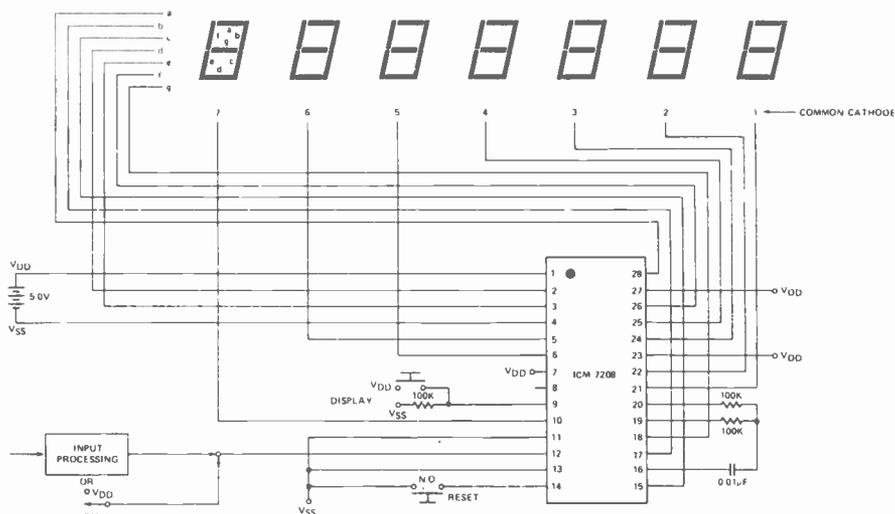


Fig. 5. Unit counter schematic.

ETI

DIODES/ZENERS				SOCKETS/BRIDGES				TRANSISTORS, LEDS, etc.						
1N914	100v	10mA	.05	8-pin	pcb	.20	ww	.35	2N2222	NPN (2N2222 Plastic .10)	.15			
1N4005	600v	1A	.08	14-pin	pcb	.20	ww	.40	2N2907	PNP	.15			
1N4007	1000v	1A	.15	16-pin	pcb	.20	ww	.40	2N3906	PNP (Plastic - Unmarked)	.10			
1N4148	75v	10mA	.05	18-pin	pcb	.25	ww	.75	2N3904	NPN (Plastic - Unmarked)	.10			
1N4733	5.1v	1 W Zener	.25	22-pin	pcb	.35	ww	.95	2N3054	NPN	.35			
1N753A	6.2v	500 mW Zener	.25	24-pin	pcb	.35	ww	.95	2N3055	NPN 15A 60v	.50			
1N758A	10v	"	.25	28-pin	pcb	.45	ww	1.25	T1P125	PNP Darlington	.35			
1N759A	12v	"	.25	40-pin	pcb	.50	ww	1.25	LED Green, Red, Clear, Yellow		.15			
1N5243	13v	"	.25	Molex pins .01	To-3 Sockets	.25			D.L.747	7 seg 5/8" High com-anode	1.95			
1N5244B	14v	"	.25	2 Amp Bridge	100-prv	.95			MAN72	7 seg com-anode (Red)	1.25			
1N5245B	15v	"	.25	25 Amp Bridge	200-prv	1.95			MAN3610	7 seg com-anode (Orange)	1.25			
									MAN82A	7 seg com-anode (Yellow)	1.25			
									MAN74A	7 seg com-cathode (Red)	1.50			
									FND359	7 seg com-cathode (Red)	1.25			

C MOS		- T T L -									
4000	.15	7400	.10	7473	.25	74176	.85	74H72	.35	74S133	.40
4001	.15	7401	.15	7474	.30	74180	.55	74H101	.75	74S140	.55
4002	.20	7402	.15	7475	.35	74181	2.25	74H103	.55	74S151	.30
4004	3.95	7403	.15	7476	.40	74182	.75	74H106	.95	74S153	.35
4006	.95	7404	.10	7480	.55	74190	1.25			74S157	.75
4007	.20	7405	.25	7481	.75	74191	.95	74L00	.25	74S158	.30
4008	.75	7406	.25	7483	.75	74192	.75	74L02	.20	74S194	1.05
4009	.35	7407	.55	7485	.55	74193	.85	74L03	.25	74S257 (8123)	1.05
4010	.35	7408	.15	7486	.25	74194	.95	74L04	.30		
4011	.20	7409	.15	7489	1.05	74195	.95	74L10	.20	74LS00	.20
4012	.20	7410	.15	7490	.45	74196	.95	74L20	.35	74LS01	.20
4013	.40	7411	.25	7491	.70	74197	.95	74L30	.45	74LS02	.20
4014	.75	7412	.25	7492	.45	74198	1.45	74L47	1.95	74LS04	.20
4015	.75	7413	.25	7493	.35	74221	1.00	74L51	.45	74LS05	.25
4016	.35	7414	.75	7494	.75	74367	.75	74L55	.65	74LS08	.25
4017	.75	7416	.25	7495	.60			74L72	.45	74LS09	.25
4018	.75	7417	.40	7496	.80	75108A	.35	74L73	.40	74LS10	.25
4019	.35	7420	.15	74100	1.15	75491	.50	74L74	.45	74LS11	.25
4020	.85	7426	.25	74107	.25	75492	.50	74L75	.55	74LS20	.20
4021	.75	7427	.25	74121	.35			74L93	.55	74LS21	.25
4022	.75	7430	.15	74122	.55			74L123	.85	74LS22	.25
4023	.20	7432	.20	74123	.35	74H00	.15			74LS32	.25
4024	.75	7437	.20	74125	.45	74H01	.20	74S00	.35	74LS37	.25
4025	.20	7438	.20	74126	.35	74H04	.20	74S02	.35	74LS38	.35
4026	1.95	7440	.20	74132	.75	74H05	.20	74S03	.25	74LS40	.30
4027	.35	7441	1.15	74141	.90	74H08	.35	74S04	.25	74LS42	.65
4028	.75	7442	.45	74150	.85	74H10	.35	74S05	.35	74LS51	.35
4030	.35	7443	.45	74151	.65	74H11	.25	74S08	.35	74LS74	.35
4033	1.50	7444	.45	74153	.75	74H15	.45	74S10	.35	74LS86	.35
4034	2.45	7445	.65	74154	.95	74H20	.25	74S11	.35	74LS90	.55
4035	.75	7446	.70	74156	.70	74H21	.25	74S20	.25	74LS93	.55
4040	.75	7447	.70	74157	.65	74H22	.40	74S40	.20	74LS107	.40
4041	.69	7448	.50	74161	.55	74H30	.20	74S50	.20	74LS123	1.00
4042	.65	7450	.25	74163	.85	74H40	.25	74S51	.25	74LS151	.75
4043	.50	7451	.25	74164	.60	74H50	.25	74S64	.15	74LS153	.75
4044	.65	7453	.20	74165	1.10	74H51	.25	74S74	.35	74LS157	.75
4046	1.25	7454	.25	74166	1.25	74H52	.15	74S112	.60	74LS164	1.00
4049	.45	7460	.40	74175	.80	74H53J	.25	74S114	.65	74LS193	.95
4050	.45	7470	.45			74H55	.20			74LS367	.75
4066	.55	7472	.40							74LS368	.65

4069/74C04	.25
4071	.25
4081	.30
4082	.30
MC 14409	14.50
MC 14419	4.85
4511	.95
74C151	1.90

9000 SERIES			
9301	.85	95H03	1.10
9309	.35	9601	.20
9322	.65	9602	.45

MICRO'S, RAMS, CPU'S, E-PROMS			
74S188	3.00	8214	8.95
1702A	4.50	8224	3.25
MM5314	3.00	8228	6.00
MM5316	3.50	8251	8.50
2102-1	1.45	8255	10.50
2102L-1	1.75	8T13	1.50
2114	9.50	8T23	1.50
TR1602B	3.95	8T24	2.00
TMS 4044	9.95	8T97	1.00
		2107B-4	4.95
8080	8.95	2708	9.50
8212	2.95	Z80 PIO	8.50

LINEARS, REGULATORS, etc.			
MCT2	.95	LM320T5	1.65
8038	3.95	LM320T12	1.65
LM201	.75	LM320T15	1.65
LM301	.45	LM324N	1.25
LM308 (Mini)	.95	LM339	.75
LM309H	.65	7805 (340T5)	.95
LM309K (340K-5)	.85	LM340T12	.95
LM310	.85	LM340T15	.95
LM311D (Mini)	.75	LM340T18	.95
LM318 (Mini)	1.75	LM340T24	.95
LM320K5(7905)	1.65	LM340K12	1.25
LM320K12	1.65		
		LM340K15	1.25
		LM340K18	1.25
		LM340K24	1.25
		78L05	.75
		78L12	.75
		78L15	.75
		78M05	.75
		LM373	2.95
		LM380 (8-14 PIN)	.95
		LM709 (8, 14 PIN)	.25
		LM711	.45
		LM723	.40
		LM725N	2.50
		LM739	1.50
		LM741 (8-14)	.25
		LM747	1.10
		LM1307	1.25
		LM1458	.65
		LM3900	.50
		LM75451	.65
		NE555	.35
		NE556	.85
		NE565	.95
		NE566	1.25
		NE567	.95

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, CA 92111 U.S.A.
No Minimum

All prices in U.S. dollars. Please add postage to cover method of shipping. Orders over \$100 (U.S.) will be shipped air no charge.
Payment should be submitted with order in U.S. dollars.
All IC's Prime/Guaranteed. All orders shipped same day received.

	SPECIAL DISCOUNTS
	Total Order Deduct
	\$35 - \$99 10%
	\$100 - \$300 15%
	\$301 - \$1000 20%

Phone (714) 278-4394 BarclayCard / Access / American Express / BankAmericard / Visa / MasterCard

TTLs by TEXAS		74LS251 200p		4000 SERIES		4514 250p		LM733 100p		TRANSISTORS		TIP41C 78p		DIODES		3A 600V 72p										
7400 13p	74105 65p	74283 190p	74LS257 120p	4000 15p	4516 110p	LM741 22p	AC127/8 20p	BFY51/2 22p	TIP42A 70p	'N4125/6 22p	'N4289 20p	'BY127 12p	3A 100V 95p	7401 14p	74107 34p	74284 400p	74LS257 120p	4001 17p	4518 100p	LM747 70p	AD149 70p	BFY90 90p	TIP42C 82p	'N4401/3 27p	'OA47 9p	4A 400V 100p
7402 14p	74109 55p	74285 400p	74LS298 245p	4002 17p	4520 100p	LM748 35p	AD161/2 45p	BFY56 33p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7403 14p	74110 55p	74286 400p	74LS298 245p	4006 95p	4528 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	6A 100V 100p
7404 17p	74111 70p	74287 150p	74LS373 200p	4007 18p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7405 18p	74112 200p	74288 150p	74LS373 200p	4008 95p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	6A 400V 120p
7406 32p	74118 130p	74289 150p	74LS374 195p	4008 95p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7407 32p	74119 210p	74290 150p	74LS374 195p	4009 40p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7408 19p	74120 110p	74291 150p	74LS374 195p	4009 40p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7409 19p	74121 210p	74292 150p	74LS374 195p	4010 50p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7410 15p	74122 48p	74293 150p	74LS374 195p	4011 17p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7411 24p	74123 55p	74294 150p	74LS374 195p	4012 18p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7412 20p	74125 55p	74295 150p	74LS374 195p	4013 50p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7413 30p	74128 80p	74296 150p	74LS374 195p	4014 84p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7414 60p	74132 75p	74297 150p	74LS374 195p	4015 84p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7416 27p	74136 75p	74299 150p	74LS374 195p	4016 45p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7417 27p	74141 70p	74300 150p	74LS374 195p	4017 25p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7418 27p	74147 190p	74301 150p	74LS374 195p	4018 89p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7420 17p	74142 200p	74302 150p	74LS374 195p	4019 45p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7421 40p	74147 190p	74303 150p	74LS374 195p	4020 100p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7422 22p	74145 90p	74304 150p	74LS374 195p	4021 110p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7423 34p	74148 150p	74305 150p	74LS374 195p	4022 100p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7425 30p	74148 150p	74306 150p	74LS374 195p	4023 22p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7426 40p	74150 100p	74307 150p	74LS374 195p	4024 65p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7428 36p	74153 70p	74308 150p	74LS374 195p	4025 20p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7430 40p	74151A 70p	74309 150p	74LS374 195p	4026 130p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7430 17p	74154 100p	74310 150p	74LS374 195p	4027 50p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7431 30p	74155 90p	74311 150p	74LS374 195p	4028 84p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7432 30p	74155 90p	74312 150p	74LS374 195p	4029 100p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7433 40p	74156 90p	74313 150p	74LS374 195p	4030 55p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7435 35p	74157 70p	74314 150p	74LS374 195p	4031 200p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7437 35p	74159 100p	74315 150p	74LS374 195p	4032 65p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7438 35p	74159 190p	74316 150p	74LS374 195p	4033 180p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7440 17p	74160 100p	74317 150p	74LS374 195p	4034 200p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7440 17p	74160 100p	74318 150p	74LS374 195p	4035 110p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7441 70p	74161 100p	74319 150p	74LS374 195p	4036 100p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7442A 60p	74162 100p	74320 150p	74LS374 195p	4038 84p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7443 112p	74163 100p	74321 150p	74LS374 195p	4040 400p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7444 112p	74164 120p	74322 150p	74LS374 195p	4041 80p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7445 100p	74165 120p	74323 150p	74LS374 195p	4042 80p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7446A 93p	74166 140p	74324 150p	74LS374 195p	4043 90p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7447A 70p	74167 200p	74325 150p	74LS374 195p	4044 90p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7448 80p	74170 240p	74326 150p	74LS374 195p	4046 130p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7449 80p	74171 240p	74327 150p	74LS374 195p	4047 100p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7450 17p	74172 72p	74328 150p	74LS374 195p	4048 55p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7451 17p	74173 72p	74329 150p	74LS374 195p	4049 40p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7453 17p	74174 93p	74330 150p	74LS374 195p	4050 48p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7454 17p	74175 85p	74331 150p	74LS374 195p	4051 80p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7457 17p	74176 90p	74332 150p	74LS374 195p	4052 80p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7458 17p	74177 90p	74333 150p	74LS374 195p	4053 80p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7460 17p	74178 90p	74334 150p	74LS374 195p	4055 125p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7461 17p	74179 90p	74335 150p	74LS374 195p	4056 135p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7470 36p	74177 90p	74336 150p	74LS374 195p	4058 60p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7472 30p	74178 90p	74337 150p	74LS374 195p	4060 115p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7473 34p	74180 93p	74338 150p	74LS374 195p	4063 120p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7474 30p	74181 200p	74339 150p	74LS374 195p	4066 55p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7475 36p	74182 90p	74340 150p	74LS374 195p	4068 22p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7476 35p	74184 150p	74341 150p	74LS374 195p	4069 20p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7478 50p	74185 150p	74342 150p	74LS374 195p	4070 30p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4125/6 22p	'N4401/3 27p	'OA81 15p	4A 50V 90p	7479 50p	74186 70p	74343 150p	74LS374 195p	4071 22p	4532 100p	LM748 35p	AD161/2 45p	BFY90 90p	TIP42E 82p	'N4401/3 27p	'OA81 15p	10A 400V 200p
7481 100p																										

ETIWET PLANT WATERER

WATER, WATER, EVERYWHERE and not a drop to drink runs an old poem, well plants need to quench their thirst as well as humans — and during holiday time most are left to wilt. In the interests of flower power we decided to produce a unit that would refresh the plants that owners could not reach, hence the ETI WET.

The unit consists of a sensor, timer and electric water pump. The sensor is embedded in the soil and when dry the electronics operate the water pump for a preset time — thus infusing the plant with thirst quenching water. When the plant has drunk its fill and the sensor is dry again the cycle repeats. In this way you can soak up the sun in the knowledge that your prize plant is getting its fair share at home.

Construction And Calibration

The electronics are mounted on the PCB, using a socket for the IC. We used a plastic card filing box for the case and a 5 litre container to hold the water supply. Make sure you drill an extra small hole in the cap of the water container — so that air can replace water when the pump operates.

We used a small 6V pump (see buy lines) but other pumps can be used. For example a pet shop can probably supply small pumps (used in fish tanks) and pumps are available from most car accessory shops (used for windscreen water). If the pump you use needs 12V the battery will need changing — the electronics will work at this higher voltage.

The moisture control and water

If your plants suffer from a drink problem let our ETI WET look after them when you are away, ensuring that they get their daily dose of life giving liquid.





Head on view of the completed prototype, the LED can be left out if you want extended battery life.

flow control need careful setting — to ensure that the plant gets enough water, but not too much. When first switched on the ETI WET will pump water for the time set by the water flow control — use this water to wet

the soil around the plant, with the probe in position.

With a properly watered plant, adjust the moisture control until the ETI WET feeds more water — then reduce the setting. ▶

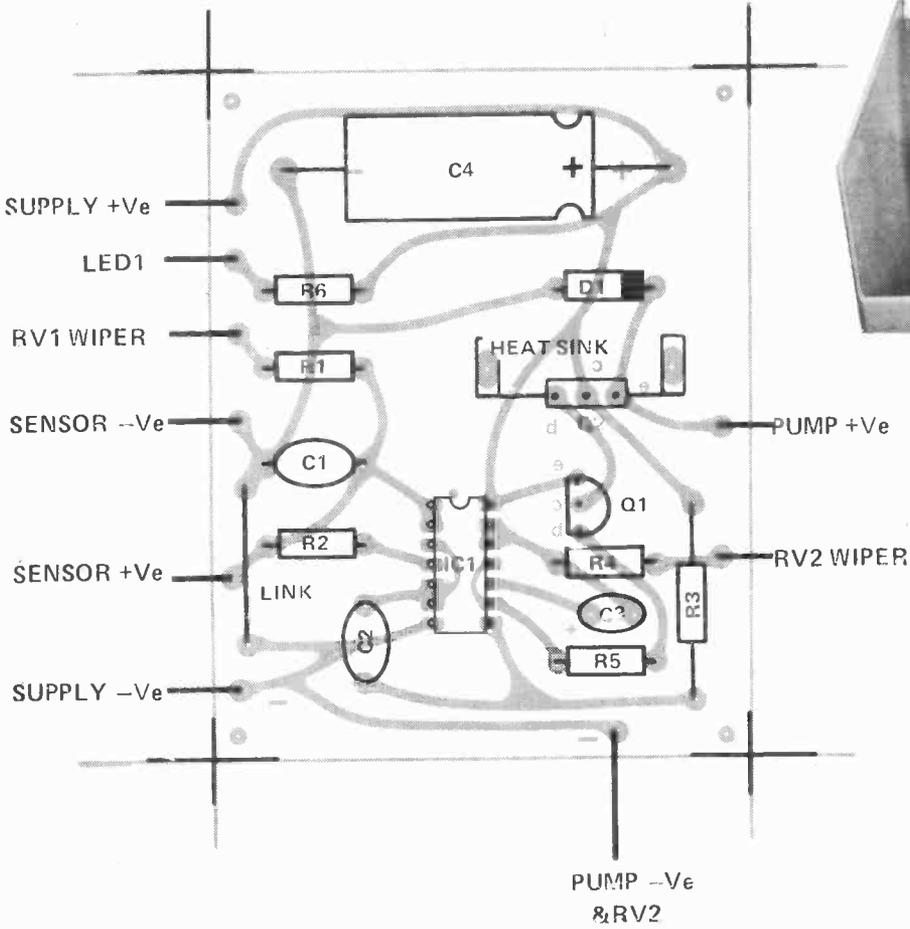
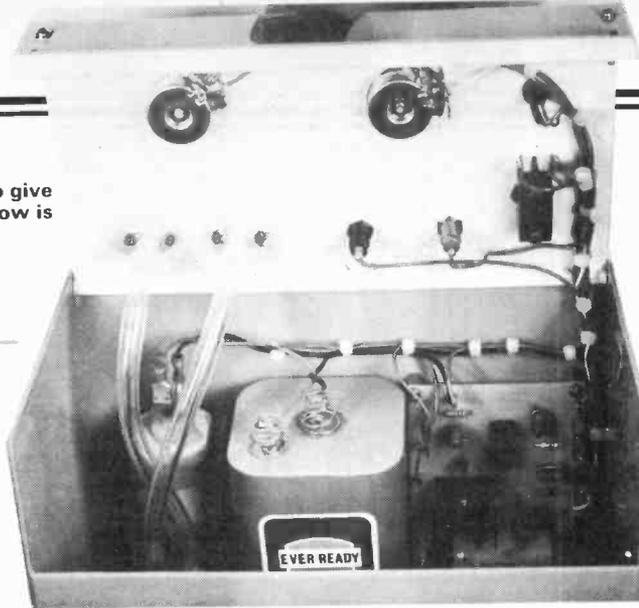
On the left is an internal shot of our prototype, notice how we used screws to give extra 'bite' to the epoxy holding the tube connections on the front panel. Below is the overlay for the PCB.




PARTS LIST

RESISTORS (all 1/4w 5%)	
R1, 3	100k
R2	4M7
R4	47k
R5	22k
R6	470R
POTENTIOMETERS	
RV1	500k linear
RV2	100k linear
CAPACITORS	
C1, 2	100n polycarbonate
C3	100u 10V tantalum
C4	2200u 16V electrolytic
SEMICONDUCTORS	
IC1	CD4011
Q1	BC214L
Q2	BD131
D1	1N914
D2	TIL209
MISCELLANEOUS	
Toggle switch, Battery (PJ996), Box to suit, PCB, water pump, tubing, water container, etc.	

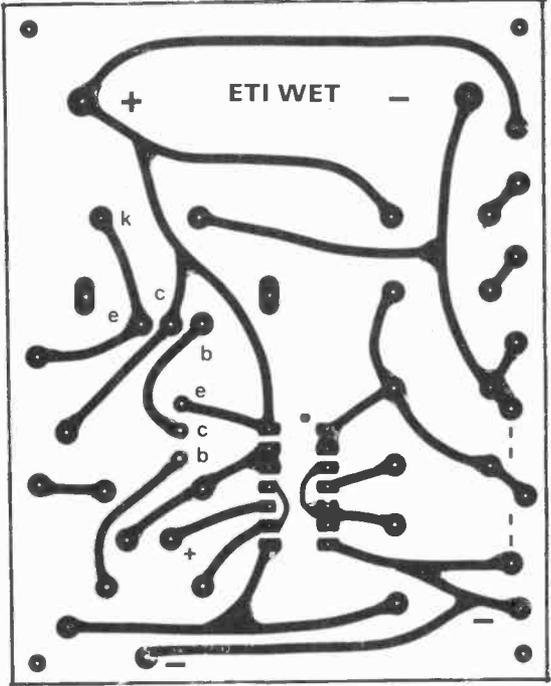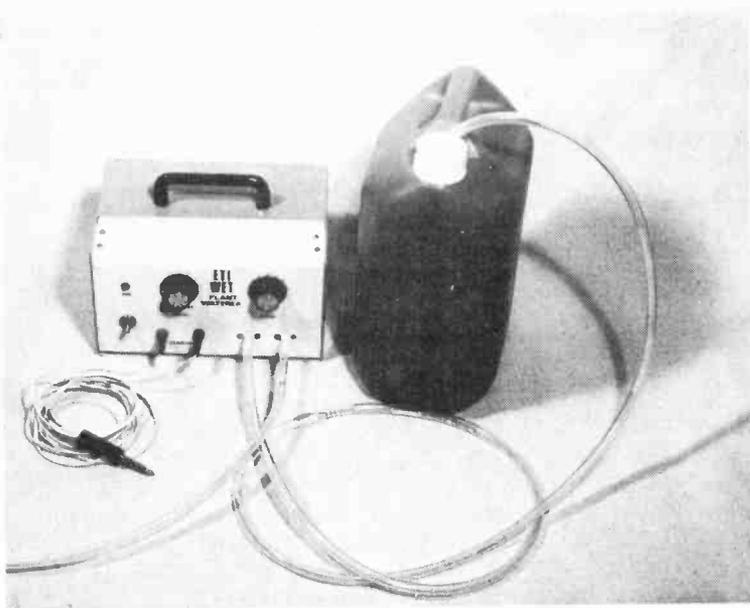Below is the complete system, the probe used was made from a jack plug. On the right is the PCB shown full size (70mm by 90mm).



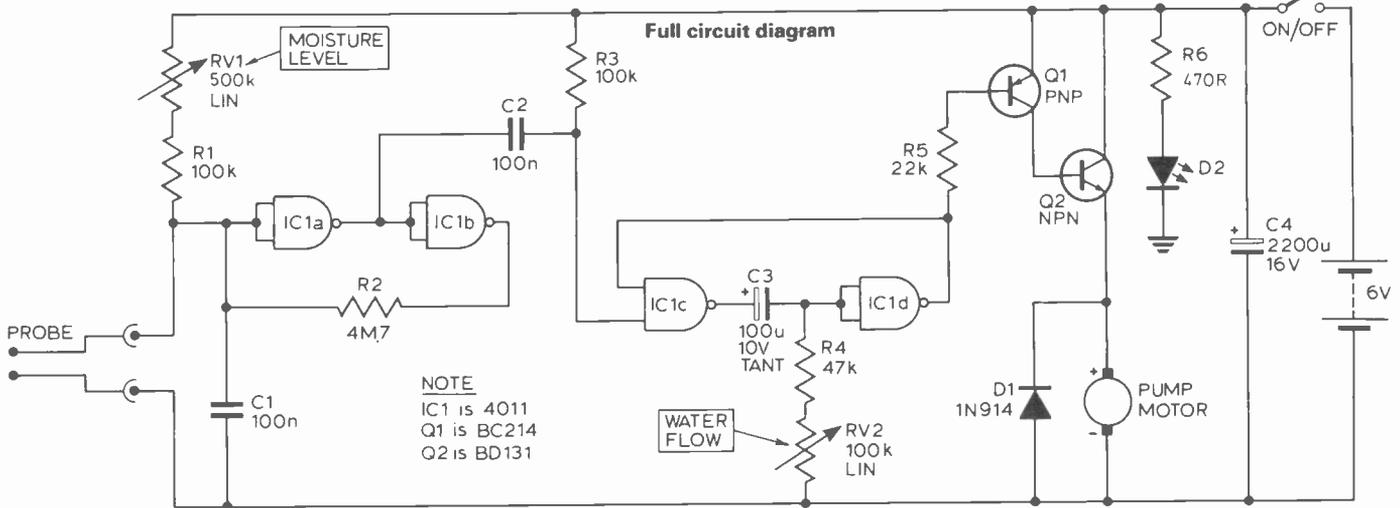

BUYLINES

The electronic parts for this project should present few problems. Sources for tubing and the connectors include chemical equipment suppliers and your local home brewing shops. The pump we used came from Proops Bros. Ltd, The Hyde Industrial Estate, Edgware Road, Hendon, London NW9 6JS and costs £2.30 inclusive of VAT and postage.

HOW IT WORKS

The circuit is composed of three main sections: Level sensitive Schmitt trigger, variable time monostable and output driver. The level sensitive Schmitt is formed from IC1a and IC1b with the probe and R1, RV1 forming a potential divider on its input. When the resistance across the probe increases beyond a set value (ie the soil dries), the Schmitt is triggered. C2 feeds a negative going pulse to the monostable when the Schmitt triggers and R2 acts as feedback, to ensure a fast

switching action.

The monostable (IC1c and IC1d) time period is determined by the values of C3 and R4, RV2. When triggered by the Schmitt the monostable turns on Q1, Q2 which drive the water pump. The monostable will only trigger with negative going input pulses, and therefore unless the probe has been shorted (by water) the Schmitt cannot retrigger the monostable. This acts as a fail safe to prevent the plant from drowning!

TRAMPUS ELECTRONICS LTD.

SEMICONDUCTOR DISTRIBUTORS

Cheque or cash orders over £5 Post Free. Other orders add 20p Post & Packing. Credit Card orders £5 min. by post or phone. + Post & Packing 20p. UK add 8% to prices marked. Add 12 1/2% VAT to all other prices. Free price list send S.A.E.

All devices to makers specifications. Please quote ETI ad as prices may change. E. & O. E. 1978. Callers welcome Tues to Sat (Lunch 1-2).

ELECTRONIC COMPONENT CENTRE
58-60 GROVE ROAD, WINDSOR, BERKS
SL4 1HS (TRADE AND EXPORT WELCOME)
HOTLINE FOR TELEPHONE CREDIT CARD ORDERS -
WINDSOR S4525

ETI READERS OFFER: OVER £10 DISCOUNT 5% OFF. (THIS MONTH)
QUANTITY DISCOUNT FOR 100 OF ONE TYPE 10% OFF 1 UP PRICE

TRANSISTORS		7400N SERIES TTL		CMOS TOP VALUE	
AC127 17p* 8F50 16p*	Look at our Pak T. Ten Plastic Power £1	7400 8p*	7475 44p*	4000 15p*	4066 58p*
AC176 10p* 8F51 16p*	Dr Pak C: 4 x 2N3055 £1*	7401 9p*	7476 35p*	4001 15p*	4067 £4*
AC187 20p* 8F29 28p*	Matching 20p*. Ins Kit 10p*	7402 10p*	7480 39p*	4002 17p*	4069 22p*
AD161 40p* 8S20 18p*		7403 10p*	7481 1p*	4006 £1*	4070 32p*
AF162 40p* MJ2955 £1*		7405 9p*	7483 1p*	4007 18p*	4071 21p*
AF239 42p* MJE340 44p*		7406 28p*	7485 £1*	4008 92p*	4072 21p*
BC107 8p* MJE2955 £1*		7407 28p*	7486 35p*	4009 58p*	4073 21p*
BC108 8p* MJE3055 80p*		7408 12p*	7490 36p*	4010 58p*	4075 23p*
BC109 9p* MPU131 35p*		7409 12p*	7491 75p*	4011 15p*	4076 £1.29*
BC109C 15p* ORP12 55p*		7410 10p*	7492 35p*	4012 18p*	4077 40p*
BC147 12p* TIP41A 60p*		7411 22p*	7493 35p*	4013 55p*	4078 21p*
BC148 12p* TIP42A 65p*		7412 22p*	7494 75p*	4015 93p*	4081 22p*
BC149 12p* TIP2955 60p*		7413 28p*	7495 75p*	4016 52p*	4082 21p*
BC157 15p* TIP3055 50p*		7416 28p*	7496 85p*	4017 99p*	4089 £1.50*
BC158 15p* TI543 35p*		7417 28p*	74100 £1.15*	4018 99p*	4093 85p*
BC159 15p* 2N2646 39p*		7420 10p*	74107 29p*	4020 1p*	4507 55p*
BC167 10p* 2N2905 22p*		7423 26p*	74121 27p*	4021 1p*	4508 £3*
BC168 11p* 2N2926Y 10p*		7425 26p*	74123 59p*	4022 90p*	4510 £1.35*
BC169 12p* 2N3053 16p*		7426 26p*	74141 95p*	4023 20p*	4511 £1.68*
BC177 18p* 2N3055 45p*		7440 14p*	74147 £1.69*	4024 76p*	4512 98p*
BC178 16p* 2N3614 £1*		7441 79p*	74152 £2*	4025 19p*	4514 £2.65*
BC179 18p* 2N3702 9p*		7442 87p*	74154 £2*	4027 55p*	4516 £1.28*
BC182 10p* 2N4370A 9p*		7445 69p*	74155 80p*	4028 90p*	4518 £1.05*
BC183 10p* 2N3706 9p*		7446 88p*	74156 80p*	4029 1p*	4520 £1.10*
BC184 10p* 2N3819E 18p*		7447 82p*	74157 £1*	4030 58p*	4521 £2.68*
BC212 12p* 2N3820 38p*		7448 £1*	74164 £1*	4032 £1*	4522 £2*
BC213 12p* 2N3904 15p*		7450 15p*	74174 £1*	4034 £2*	4528 98p*
BC214 12p* 2N3906 15p*		7451 15p*	74176 £1*	4035 £1.20*	4534 £7.88*
BCY71 20p* 2N4347 50p*		7453 15p*	74190 £2*	4038 £1.08*	4536 £3.60*
BD131 37p* 2N5457 32p*		7454 15p*	74192 £2*	4040 £1.05*	4541 £1.50*
BD132 37p* 2N5477 44p*		7455 15p*	74193 £2*	4041 86p*	4543 £1.75*
BO695 69p* TL131 £2*		7460 15p*	74195 £2*	4042 81p*	4553 £4.49*
BO696 69p* TL163 £1*		7464 15p*	74199 £2*	4043 96p*	4556 78p*
		7470 29p*	74194 £2*	4044 95p*	4558 £1.17*
		7472 26p*	74196 £1.30*	4046 £1.30*	4566 £1.59*
		7473 25p*	74197 £1*	4047 99p*	4569 £3.50*
		7474 29p*	74198 £2*	4049 52p*	4583 £1.10*
				4060 £1.15*	4585 £2.05*
				4063 £1.10*	

DIODES & BRIDGE

1A 50v Bridge 22p*

IN4148 or IN914 4p*

0A81 or 0A91 5p

0A200 & 202 10p

IN4001 1A50v 5p*

IN4004 7p*. IN4007 15p*

DIL SOCKETS

8 pin 12p* 28 Pin £1

24 Pin 50p 40 Pin £1.50

Profile 14 or 16 Pin 15p

TOP TWSOME!

555 8 Pin Timer 27p*

741C Full spec 01L 8. Branded Op Amp 19p*

NEW LINEARS Data 10p

TL170 Half effect 69p*

TL071 Lo noise 741 75p*

TL081 FET Op. 741 69p*

TL083 FET 747 £1.49*

TL080 FET 748/308 £1.15*

IC SUPERMARKET

301 Op Amp 30p*

555 Timer (NE555) 27p*

556 Dual 555 70p*

710 Comparator 40p*

723 Regulator 45p*

741C 8 Pin OIL DPA 19p*

741C T099 or OIL 14 39p*

748C Op Amp 33p*

3900 Quad Op Amp 55p*

7805 1 Amp 5v 95p*

7805 T03(T09K) £1*

7808 or 7812 £1.25*

7815 15 volt plastic 69p*

7900 Negative Series £2.50*

8038 Sig Generator £3.55*

76013 & 76023 11.35

CA3130 & CA3140 94p*

LM380 1 watt Amp 85p

LM3801 Dual Preamp £1.55

LM387 Dual Preamp £1

LM3900 Quad OPA 55p*

MC1310 Oscillator £1

MC1460, 1461 & 1469 £3*

MCMS0 14433, A/D £5

NE536 FET OPA £4*

NE555 Timer 27p*

NE556 Dual 555 70p*

T8A810 7w FET £1

2N414 Radio 65p

OUR LATEST SPECIAL

CONTENTS

Graphic Equalizer
RF Attenuator
ETI Watchdog
Sweep Oscillator
£2 Sound Improver
Stereo Simulator
Freezer Alarm
General Preamplifier
Stars & Dots Game
GSR Monitor
Burglar Alarm
Headlight Reminder
Bench Amplifier
CCTV Camera
Audio-visual Metronome
Expander-Compressor
Power Amplifier Modules
Digital Thermometer
Headphone Adaptor
Hear & Tell unit
Led dice
Active Crossover
Marker Generator
Skeet Game
Flash Trigger
Disco Lightshow Unit
Pink Noise Generator

— £1

Graphic Equaliser.....Marker Generator
Power Amplifier Modules.....£2 Sound
CCTV Camera..... Headphone Adaptor
LED Dice.....Sound-Light Flash Trigger
Expander-Compressor..... Skeet Game

ETI TOP PROJECTS

PROJECTS REPRINTED FROM

NO 6 electronics today £1

Burglar Alarm...Digital Thermometer
Stars & Dots Logic Game.....Lightshow
Active Crossover.... Hear and Tell Unit
Pink Noise Generator.....GSR Monitor
Sweep Oscillator.....Stereo Simulator

Top Projects 6 is the latest special in the 'Top Projects' series, with reprints of 27 projects from past issues of ETI. TP6 is available soon at your local newsagents or direct from ETI now. Send a cheque or PO for £1 plus 25p p&p, to:

ETI TP6
25/27 Oxford Street
London W1R 1RF

Please write your name and address on the reverse of your cheques or POs.

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 3/4" X 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step by step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems



£8

plus £1 packing and surface post anywhere in the world. Overseas customers should send for Proforma invoice. Payment by credit cards accepted.

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics
In 4 volumes

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.60

plus 90p P & P

Offer Order both courses for the bargain price £12 plus £1 P&P.

A saving of £1.50.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

FLOW CHARTS & ALGORITHMS — The Algorithm Writer's Guide — Construction, content, form, use, layout of algorithms and flow charts. Vital for computing, training, wall charts, etc. Size: A5, 130 pages. **£2.95** plus 45p P&P

Guaranteed — If you are not entirely satisfied your money will be refunded.

CAMBRIDGE LEARNING ENTERPRISES, Unit 15 Freeport, RIVERMILL LODGE, ST. IVES, HUNTINGDON, CAMBS, PE17 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446
PROPRIETORS DRAYBRIDGE LTD. REG. OFFICE RIVENHALL LODGE, ST. IVES, GIRO AC. No. 278 9815. REGD. IN ENGLAND NO. 1328762.

Cambridge Learning Enterprises, Unit 15 Freeport
Rivermill Lodge, St. Ives, Huntingdon, Cambs, PE17 4BR, England
Please send me the following books

- sets Digital Computer Logic & Electronics @ £5.50 p&p included
- sets Design of Digital Systems @ £9.00 p&p included
- Combined sets @ £13.00 p&p included
- The Algorithm Writer's Guide @ £3.40 p&p included

Name

Address

I enclose a cheque / PO payable to Cambridge Learning Enterprises for £

Please charge my Access / Barclaycard / Visa / Eurocard / Mastercharge / Interbank account number

Signature delete as appropriate

Telephone orders from credit holders on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank.

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safebloc

Miniature & Sub Miniature					50 VOLT (Pri. 220-240V) Sec. 0-19-25-33-40-50V			
Volts	Milli-amps	Ref. No.	Price £	P&P	Amps	Ref. No.	Price £	P&P
3-0-3	200	238	1.95	55	0.5	102	3.20	70
0-6-0-6	1A 1A	212	2.60	55	1.0	103	4.20	85
9-0-9	100	13	1.85	40	2.0	104	6.10	100
0-9-0-9	330 330	235	1.95	40	3.0	105	7.85	100
0-8-9 0-8-9	500 500	207	2.35	55	4.0	106	9.80	110
0-8-9 0-8-9	1A 1A	208	3.50	55	6.0	107	14.95	130
0-15-0-15	200 200	236	1.95	40	8.0	118	15.75	150
0-20-0-20	300 300	214	2.35	70	10.0	119	20.50	200
20-12-0-12-20	700(DC)	221	3.10	70	60 VOLT (Pri. 220-240V) Sec. 0-24-30-40-48-60V			
0-15-20-0-15-20	1A 1A	206	4.20	85	Price			
0-15-27-0-15-27	500 500	203	3.65	70	Amps	Ref. No.	£	P&P
0-15-27-0-15-27	1A 1A	204	4.75	85	0.5	124	3.40	70
12 AND/OR 24 VOLT Pri. 220-240 Volts					1.0	126	4.65	85
Amps					2.0	127	6.50	100
12V	24V	Ref.	Price £	P&P	3.0	125	9.15	110
0.5	0.25	111	1.95	55	4.0	123	11.25	130
1.0	0.5	213	2.30	70	5.0	40	11.80	130
2	1	71	2.90	70	6.0	120	14.75	140
4	2	18	3.75	70	AUTO TRANSFORMERS Input / Output Tapped 0-115-210-240V			
6	3	70	5.35	85	VA	Price		
8	4	108	6.25	100	(Watts)	Ref. No.	£	P&P
10	5	72	6.95	100	20	113	2.25	70
12	6	116	7.85	100	75	64	3.50	70
16	8	17	9.25	110	150	4	5.35	85
20	10	115	12.75	130	Input / Output Tapped 0-115-210-220-240V			
30	15	187	16.60	130	300	66	7.15	100
60	30	226	22.90	160	500	67	10.75	130
30 VOLT (Pri. 220-240V) Sec. 0-12-15-20-24-30V					1000	84	17.00	140
Amps	Ref. No.	Price £		P&P	Also 1500 / 2000 / 3000VA			
0.5	112	2.45		70	MAINS ISOLATING (Centre Tapped & Screened) Pri. 120 / 240 Sec. 120 / 240V			
1.0	79	3.05		70	VA	Price		
2.0	3	4.80		85	(Watts)	Ref. No.	£	P&P
3.0	20	5.80		100	60	149	5.75	85
4.0	21	6.85		100	100	150	6.40	100
5.0	51	7.75		100	200	151	10.00	110
6.0	117	9.50		100	250	152	11.95	130
8.00	88	11.35		130	350	153	14.45	140
10.0	89	12.00		130	1000	156	35.00	300
CATALOGUE 30p								

Please add VAT at 8%
Barclaycard and Access facilities
available
Trade and Education Welcome

BAYDIS

54a Mortimer Street
Herne Bay, Kent
Herne Bay GA4588

FREE CATALOGUE/ORDER FORM

SEND S.A.E

Send stamped addressed envelope for catalogue/order form and up to four priced lists of components for ETI projects from January, 1978. Examples from Ace Range.

741 ONLY 30p

555 ONLY 50p

TIL209 ONLY 15p

IN4001 ONLY 5p

All prices include VAT. P&P FREE over £2.

Name _____
Address _____

ACE

ACE MAILTRONIX LTD
Dept. ETI 8, Tootal Street
Wakerfield, W. Yorkshire WF1 5JR

Get an ACE up your sleeve!

Cambridge Learning Enterprises

SUMMER OFFER

Until 1st August, 1978

Just send this token with your order for a 10% discount which entitles you to books at the following prices:

Digital Computer Logic and Electronics **£4.95**

Design of Digital Systems **£8.10**

Combined set **£11.70**

Algorithm Writer's Guide **£3.06**

MK14-the only low-cost keyboard-addressable microcomputer!

The new Science of Cambridge MK14 Microcomputer kit

The MK14 National Semiconductor Scamp based Microcomputer Kit gives you the power and performance of a professional keyboard-addressable unit - for less than half the normal price. It has a specification that makes it perfect for the engineer who needs to keep up to date with digital systems or for use in school science departments. It's ideal for hobbyists and amateur electronics enthusiasts, too.


But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

MK14 Specification

- * Hexadecimal keyboard
- * 8-digit, 7-segment LED display
- * 512 x 8 Prom, containing monitor program and interface instructions
- * 256 bytes of RAM
- * 4MHz crystal
- * 5V stabiliser
- * Single 6V power supply
- * Space available for extra 256 byte RAM and 16 port I/O
- * Edge connector access to all data lines and I/O ports

Free Manual

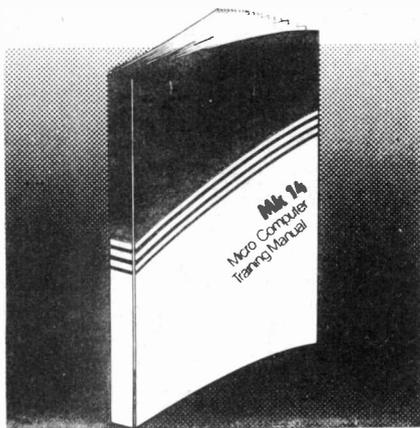Every MK14 Microcomputer kit includes a free Training Manual. It contains



Just
£39.95
(+ £3.20 VAT, and p&p)

operational instructions and examples for training applications, and numerous programs including math routines (square root, etc) digital alarm clock, single-step music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings. Further software packages, including serial interface to TTY and cassette, are available, and are regularly supplemented.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

Tomorrow's technology - today!

"It is not unreasonable to assume that within the next five years... there will be hardly any companies engaged in electronics that are not using microprocessors in one area or another."

Phil Pittman, Wireless World, Nov. 1977.

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, even purely mechanical forms of control systems.

The Science of Cambridge MK14 Standard Microcomputer Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microcomputer in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade,
Cambridge,
Cams., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd,
6 Kings Parade, Cambridge,
Cams., CB2 1SN.

Please send me an MK14 Standard
Microcomputer Kit. I enclose cheque/
Money order/PO for £43.55 (£39.95
+ 8% VAT and 40p p&p).
Allow 21 days for delivery

Name _____

Address (please print) _____

Science of Cambridge

ET18

V-FETS FOR EVERYONE PART 2

In the second half of this article, reprinted from our Canadian edition, the practicalities of VFET circuitry are explained.

In general these devices may use any of the types of output circuits in general use with valves and bi-polars, including transformer coupled (Fig. 12) where the benefits of the absence of charge carrier storage become apparent in the absence of severe ringing at the crossover point, conventional series output such as in Fig. 1 which is a straightforward transformation from a bi-polar circuit (1), and single-ended output with current source, also transposed from an excellent bi-polar circuit (2) (Fig. 2).

Bias and Drive

These series of devices are *n*-channel, enhancement type MOSFETS, and may be biased and driven using methods appropriate to signal types and bi-polars. The drain is made positive with respect to the source and the gate enables conduction by being forward biased with respect to the source, that is to say it is biased in a positive direction. Unlike bi-polars, however, they are voltage, rather than current controlled, and circuit values are selected to provide the required voltage. Any current drawn is by the bias network itself.

Three bias methods are shown; Fig. 3 shows bias supplied from a fixed bias supply. It is the simplest possible method, allows extremely high input impedances, since R_g may be almost any very high value desired, and its stability is limited only by the stability of the bias supply.

The design shown in Fig. 4 has the advantage of requiring no extra supply voltage since it is taken from V_{dd} . Disadvantages are those of impedance and stability. Input impedance consists of the parallel combination of R_1 and R_2 (disregarding input capacitance of the MOSFET and the very low input leakage). There are practical limits as to how high this combination can become; if for example, we have a 60 volt supply and require 6 volts bias, we might have some difficulty obtaining higher values than 9 megohms and one megohms for R_1 and R_2 .

Higher values become more difficult to obtain, stability becomes less reliable, internal inductance and distributed capacitance become problems, and overcoming these difficulties usually costs money. In addition, if V_{dd} is subject to variation, then bias varies. In a class AB amplifier this could be quite

We have just received a note from Siliconix giving the following changes in type number — VMP-11 becomes 2N6656; VMP-1:2N6657; VMP-12:2N6658; VUP-21:2N6659; VMP-2:2N6660; VMP-22:2N6661.

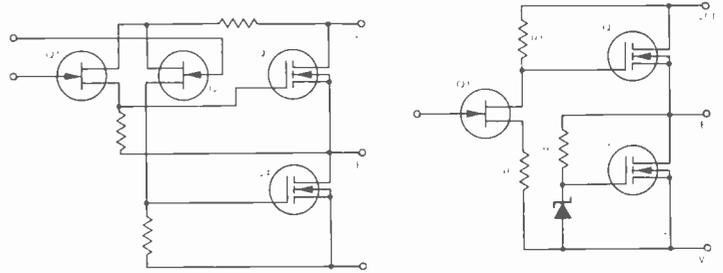


Fig. 1. Series output arrangement and Fig. 2 single-ended output with current source.

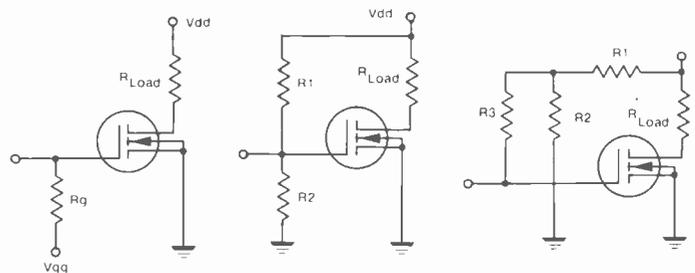


Fig. 3. High-impedance separate bias supply, Fig. 4 moderate impedance supply and Fig. 5 high-impedance common supply.

serious, since V_{dd} varies considerably with output level; at high levels, V_{dd} can be expected to drop, causing a reduction in bias.

While this may reduce the danger of over-driving the device, it will be forced to operate in its non-linear region which may result in unacceptable performance characteristics unless taken into consideration in the overall circuit design (e.g. choice of feedback values). It does provide some degree of overload protection, and with correct choice of values can

provide for class AB operation at low levels, shifting to class B at high levels. With these considerations in mind, and/or where moderate impedances are required, it offers a low cost, simple, and reasonably reliable method of establishing the operating point.

The method used in Fig. 5 is similar except that with the addition of R3 higher input impedances are possible. Its configuration is similar to a noiseless biasing system frequently used in low-level bi-polar amplifiers and integrated circuits (e.g. National LM381A) but its function is somewhat different. Resistors R1 and R2 form a voltage divider as in Fig. 4 but their junction now forms a fixed bias source as in Fig. 3. Resistor R3 can be quite high since no current flows. Meanwhile, since the parallel combination of R1 and R2 are effectively in series with R3 they can be reduced to more manageable values. Alternatively R2 can be replaced by a zener diode for stability comparable to Fig. 3.

Input Protection

Unlike most signal MOSFETS, the gate of each of these devices, with the exception of the VMP 4, is protected with an internal 15 volt, 10mA zener diode. Most signal MOSFETS, as well as the VMP 4 are unprotected, or where extremely high impedances are not required, are protected by back to back zeners. I have no information as to why this different technique is used, but it is obvious that a negative signal swing on the gate will result in forward current through the zener. If the device is to be driven beyond cutoff, the driver must be capable of delivering current during its negative swing. Alternatively a constant current source can be used, a series limiting resistor or a driver biased to the same class of operation as the V-MOSFET.

A constant current source (we'll examine an example of its use a little later) will limit current drive to the value of the constant current diode used; a series resistance will drop the drive voltage as the diode draws current. In both cases, diode current must be limited to 10mA maximum. Higher currents will damage the protective. Higher currents will damage the protective zener diode.

However, if a class B output is used, conduction only occurs during positive half-cycles. Therefore, drive signal is not required during negative half-cycles. If a source or emitter follower driver stage is biased so as to pass no negative drive, the problem does not occur. However, great care must be exercised in the design of such a stage to ensure that drive does not disappear before the output device is cut off.

This is not too difficult with a class B or near class B stage; if the output device is operated at zero bias, then a small amount of bias on the driver will ensure conduction during slightly more than 180 degrees. Class AB operation is a little more tricky. If conduction is to occur for 270 degrees, for example, the driver should conduct for slightly more than this period.

Two types of drive circuits familiar to designers of bi-polar circuits are the Darlington and Super beta, commonly used together to provide a quasi-complementary circuit. Both circuits are current amplifiers designed to provide a compound device with very high hfe and provide base current to the output device. However, similar circuits can be used


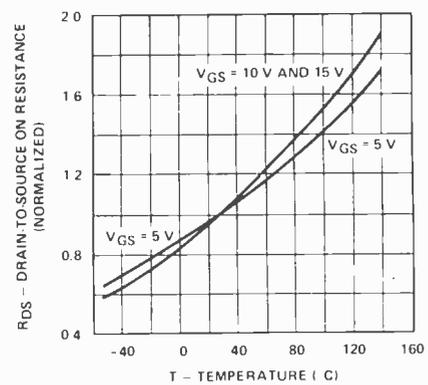


Fig. 6. Drain to source resistance against temperature (Siliconix).

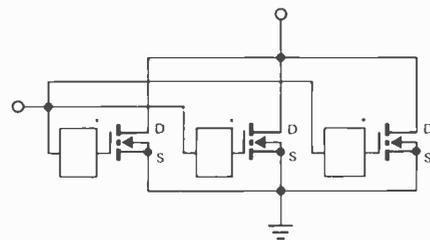

*TO PREVENT SPURIOUS OSCILLATIONS, A 500 Ω 1K Ω RESISTOR OR FERRITE BEAD (FOR HIGHER SPEED) SHOULD BE CONNECTED IN SERIES WITH EACH GATE

Fig. 7. Basic circuit for parallel operation.

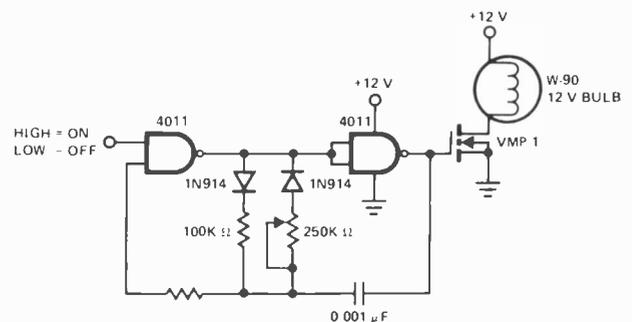


Fig. 8. Circuit of a high-efficiency light dimmer.

with these devices to provide phase inversion in a series output stage.

Thermal Considerations

As described earlier these devices exhibit a negative temperature coefficient with respect to current, so that as temperature rises, current is reduced, thus providing a self-inhibiting action which provides some protection against overload. However, this is not an unconditional effect. Fig. 6 show the

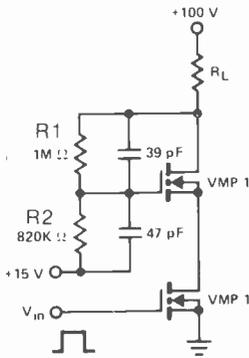


Fig. 9. Diagram for series operation.

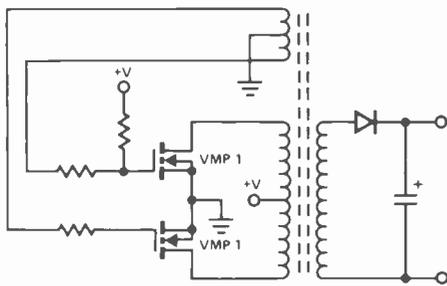


Fig. 10. A DC to DC converter (Siliconix).

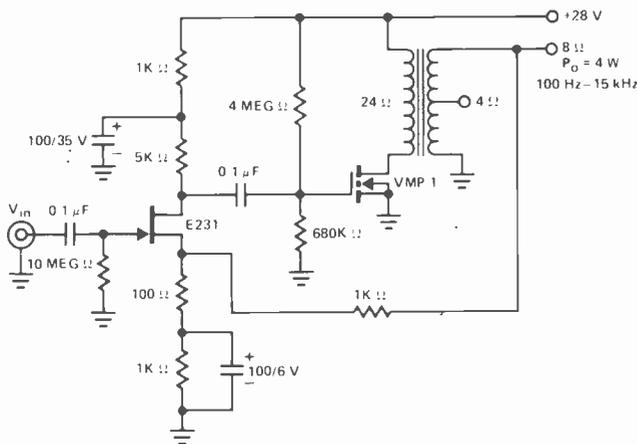


Fig. 11. Simple single-ended transformer-coupled audio power amplifier (Siliconix).

relationship between $R_{DS(on)}$ and temperature (3), based on a worst case temperature coefficient of 0.7 per cent per degree C.

Suppose that the device when on passes a current of 1 amp which causes it to heat up. The on resistance increases (which is why current drops), increasing the voltage drop across the device and the device dissipation. Now, if adequate heat sinking is used there is no real problem but if it isn't, the on resistance and junction temperature will rise to the

point where extra charge carriers are generated, thus stabilizing $R_{DS(on)}$. That's great, except for the fact that this doesn't occur until the maximum safe junction temperature of 150 degrees has been exceeded.

You'll remember that we said earlier that the device was free of thermal runaway problems because of its negative temperature coefficient, but it isn't free of thermal destruction problems, and in any case, excessive temperatures will reduce output conductance. Heat-sinking requirements are, therefore, similar to those of bi-polars. The calculations of thermal operating conditions are beyond the scope of this article, but interested readers are referred to the Siliconix literature listed in the references, (4).

Extending The Ratings

The current handling capacity and therefore total dissipation capability may be easily increased by simply connecting several devices in parallel (Fig. 7). No ballast resistors are needed to ensure proper current sharing since if one device draws more current than another it simply gets a little warmer which causes it to draw less (assuming adequate heat sinking, of course). The only major precaution needed is to keep lead inductance in the gate and source connections to a minimum to prevent parasitic oscillations, unless the devices are driven from a low impedance source.

It may be advisable to insert "stoppers" – small resistors (100 to 1000 ohms) in series with each gate, wired directly to the socket, or ferrite beads mounted on the leads close to the socket terminals. An additional plus when paralleling several devices is that the g_m is multiplied by the number of devices used. Mutual conductance g_m is specified as the ratio of a large change in current to a small change in control voltage. If, for example, a change of 0.4 volts on the gate produces a change of 0.1 amp through one device, connecting two devices in parallel will give us an output swing of 0.2 amps, but it will still require only the original 0.4 volts gate swing. Since voltage gain $A = g_m \times R_L$, if g_m is increased, A is increased.

In real use, of course, the internal resistance of two devices in parallel is less than of one, the optimum load is less, so in amplifier applications, the net amplification A is the same. But notice that the drive requirements have not changed. With bi-polars current would have to be supplied to each base, thus increasing the output requirements of the drivers. Indeed, with many high-power amplifiers using multiple output devices the drivers are also power devices.

We can also extend the voltage ratings by series operation of two or more devices; Fig. 9 shows the technique. Resistors R_1 and R_2 bias Q_2 on while C_1 and C_2 ensure fast switching. Input control signal is inserted between gate and source of Q_1 . Ordinarily the bottom of the divider chain is at ground potential for signal frequencies, so that circuit is really a cascode.

Maximum current and g_m are the same as for one device. ▶

Some Practical Applications

An efficient light dimmer circuit as proposed by Siliconix is shown in Fig. 8. The 4011 acts as a pulse width modulated oscillator whose duty cycle is determined by the ratio of R1 to R2, with R2 adjusted to control the brightness of the bulb. Of special interest here is the fact that with its fast switching time, the VMP1 is especially suited to pulse width modulation at power levels and suggests it as being suitable for use in switching, or class D linear amplifiers.

A DC to DC converter is outlined in Fig. 10. The VMP1s form an oscillator with positive feedback provided by the additional coil in the gate circuits. In operation the upper V-MOSFET is biased on, and the lower V-MOSFET is off. When power is applied the upper device conducts causing current to flow from Vdd through the upper half of the transformer primary and the upper V-MOSFET to ground. The induced current flow through the feedback coil develops a voltage such as to shift the bias in the upper device off (if the winding is connected with the correct polarity) and the lower device on. This causes current flow from Vdd through the lower half of the transformer primary and the lower V-MOSFET to ground.

The secondary circuit consists of a single rectifier and filter. The resistor in the upper gate prevents shorting out of gate bias, and the one in the lower gate keeps both sides balanced. In addition, each resistor limits current through the protective diodes. These are expensive devices for such an application, but the high reliability, the reduced RF radiation (due to reduced switching transients) and the circuit simplicity easily make up for the cost. The very high circuit impedance allows for running frequency to be set by the self resonance of the transformer.

A single ended and push-pull transformer coupled amplifier for audio applications are shown in Figs. 11 and 12. Both designs utilise the biasing system described in Fig. 4. A load-line drawn on the output characteristic will show the optimum load to be 24 ohms. In Fig. 11 gate drive is supplied by a single junction FET, and voltage feedback is taken from the output transformer secondary and series fed to the source of the input device. Distortion is under 2 per cent at full output (try to get *that* with a single ended valve or bi-polar) and could probably be reduced even further by adopting a source follower output stage.

A push-pull version of Fig. 11 is shown in Fig. 12 using a differential input to provide phase splitting, drive, and a feedback point. Although the transformer winding ratio implies the use of a low impedance loudspeaker, a step-up ratio could be used for direct coupling to an electrostatic speaker, a balanced transmission line (both with some modification of the feedback circuit) an unbalanced transmission line, or a 70 volt speaker distribution line.

Notice in both circuits, and in the biasing circuits shown that no source resistors have been used, either for local feedback or for bias setting. In valve and bi-polar circuits it's a useful technique, and with bi-polars can be used to stabilize bias and control thermal runaway by using the increased current flow to increase the voltage drop, thus reducing base-emitter voltage. However, if used with these devices, it will actually impair the self-limiting action of its negative temperature co-efficient. If temperature

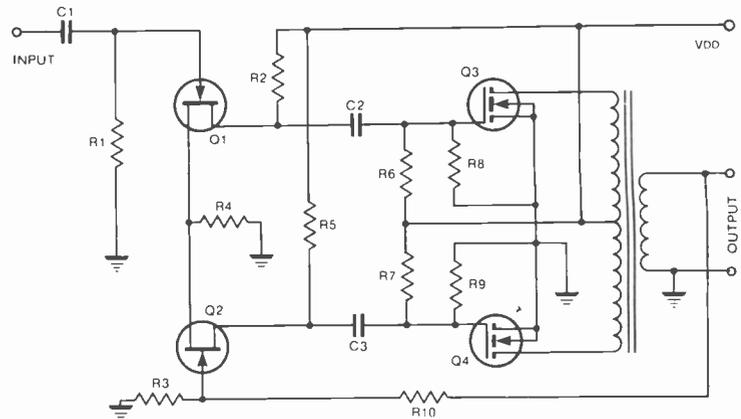


Fig. 12. Transformer-coupled output.

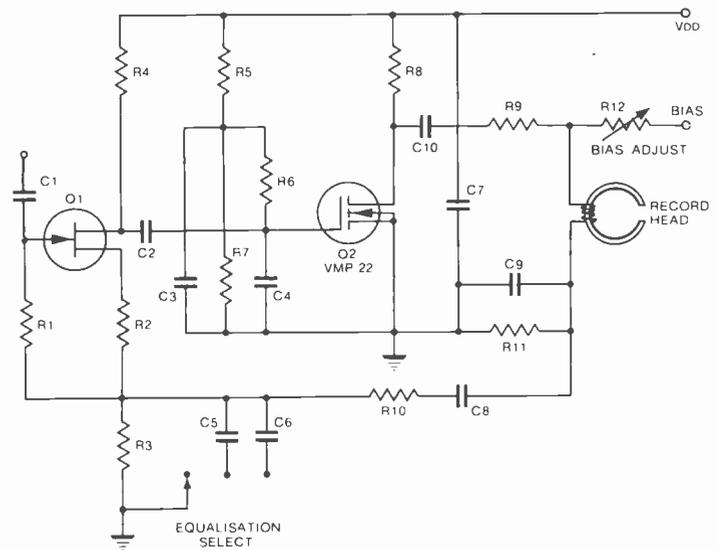


Fig. 13. Tape recording amplifier.

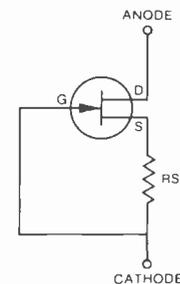


Fig. 14. A FET as a constant-current source.

rises due to high current, current flow is reduced. This would reduce the voltage drop across a source resistor, lowering the source voltage and increasing the gate-to-source voltage, causing an increase in current flow. The circuit would work great while it lasted — which wouldn't be for long.

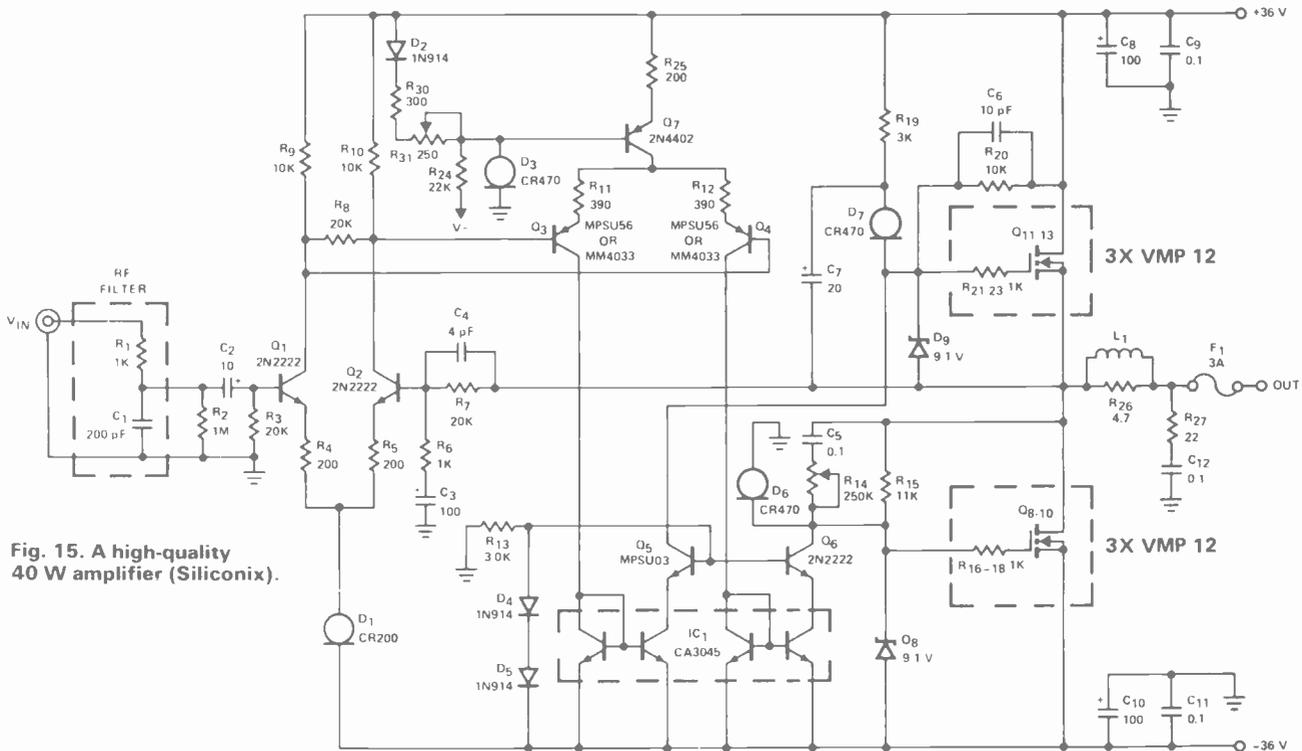


Fig. 15. A high-quality 40 W amplifier (Siliconix).

Power Amp

In Fig. 15 we have a high quality power amplifier designed by Lee Shaeffer of Siliconix Inc. (5) and described in their application notes. Output current capability is increased by using three VMP12s in parallel; providing for 6 amp current, 75 Watt dissipation and optimizing the load at 8 ohms. Q11-13 operate as a source follower, while Q8-10 form a quasi source follower. This is accomplished by applying local feedback from drain to gate via R14, R15, and driving the gate by a modified current source. This consists of a cascode circuit with a constant current diode as the load.

For the benefit of those not familiar with these devices, a constant current diode is really a FET connected internally as shown in Fig. 14. Since current in a FET is controlled essentially by the gate-to-source voltage, changes in load or in applied drain to source voltage have negligible effect since gate-to-source voltage is held constant. This is a current analogue to the zener diode and is described in detail in Siliconix literature (6).

The design is push-pull from input to output, thanks to differential circuitry throughout, prior to the drivers. Open loop distortion is low, bandwidth wide, allowing satisfactory performance with only 22dB of feedback.

Complete construction plans including PCB layout are available from Siliconix (7). A word of caution, however. Readers accustomed to construction articles in which the writer does everything but hold your soldering iron will find these plans rather sketchy. They consist of a spec sheet, schematic, board and parts layout, two paragraphs of construction suggestions, initial adjustments, and a parts list. Parts, generally, are specified as to value and rating, and that's it. These plans are excellent, but they

assume some knowledge and experience on the part of the constructor. Regular 'eti constructors' should have little difficulty.

Finally, how about something elegant for its simplicity, such as the Tapered Current Voltage Limited battery charger shown in Fig. 16. This is especially useful with Ni-Cad batteries which are intended for stand-by use and are permanently on charge, such as

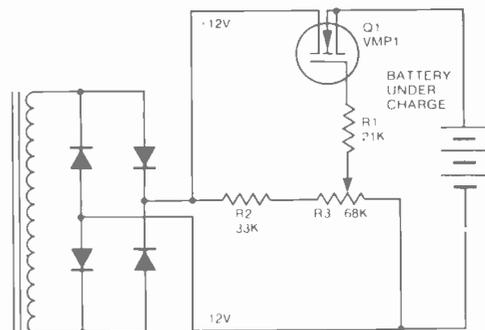


Fig. 16. Tapered-current voltage-limited battery charger.

electronic clocks. Overnight shut-downs of a few hours are occasionally but irregularly experienced. You know what this can do to clocks. Especially alarm clocks which are supposed to make noises, turn on radios, start the coffee at a pre-set time in the morning so you can go to work. Battery operation is not too satisfactory if the readout is on continuously, and Ni-Cads should not be on permanent floating charge. ▶

With this little device current is supplied to the battery via the VMP-1. Gate voltage is set at a value equal to the desired end of charge voltage. As the battery charges its voltage increases, reducing gate-to-source voltage, thus reducing charging current. When the battery reaches full charge its voltage and that of the source equals gate voltage, and charge is terminated. If a load is placed across the battery it will draw current, and as the battery voltage drops slightly below gate voltage, charging at a trickle rate occurs – automatic.

Experimentation

The various applications shown are intended as suggestions for further experimentation on the part of the reader. They are mainly designed to illustrate various characteristics of the device under consideration, and are not necessarily representative of commercial practice or of finished designs. In some cases this may be just as well. But we would be delighted to hear of any readers' experience with any of these or other circuits.

The author's own feeling is that V-MOS constitutes a genuine breakthrough in semi-conductor technology, as important as the silicon transistor and the FET itself. We'll be seeing more of these devices, with higher ratings (a 10A 200V unit is already under development) and specialized characteristics. They are said already to be in use commercially as magnetic core drivers.

Digital enthusiasts may be somewhat impatient with the strong emphasis on audio applications in this piece but other literature has placed great emphasis on digital applications, with little attention paid to linear techniques beyond the 40 watt amplifier described here. The serious reader in all areas is referred to the references at the end.


Further literature may be obtained from the manufacturer, Siliconix Inc., 2201 Laurelwood Rd., Santa Clara, CA 95054, California. They have been most helpful in providing information for the preparation of this article.

Have fun.

ETI

REFERENCES

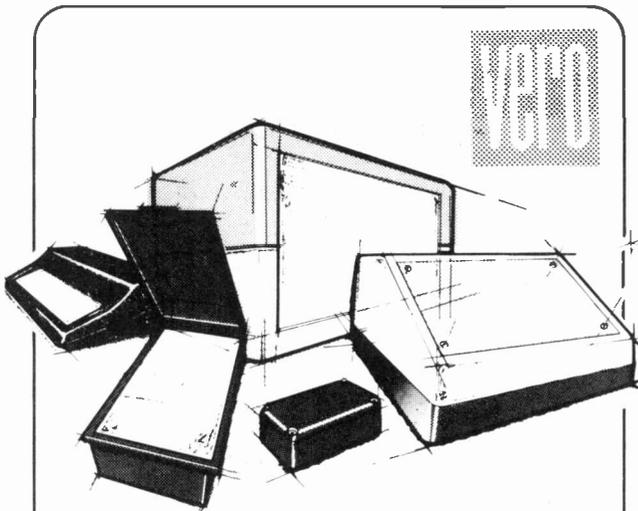1. W. Marshall Leach: "Construct a Wide Bandwidth Preamplifier" Audio, Feb 1977, p. 39.
2. Nelson Pas: "Build a Class A Amplifier" Audio, Feb. 1977, P. 29.
- 3,4. Lee Shaeffer: "VMOS-A Breakthrough in Power MOSFET Technology" Application Note AN76-3, May 1976, Siliconix Inc.
- 5, 7 Lee Shaeffer: "The MOSPOWER FET Audio Amplifier" Design Aid DA76-1, May 1976, Siliconix Inc.
6. "The FET Constant Current Source" Design Idea D171-1, January 1976. Siliconix Inc. Also Siliconix Field Effect Transistors Data Book.
7. Ref. 5.
8. Bascom H. King: "Power FETs" Audio, Feb. 1975, p. 42.
9. Ed Oxner: "A New Technology: Application of MOSPOWER FETs For High-Frequency Communications" Technical Article TA-76-2, Nov. 1976. Siliconix Inc.



Our new 1978 catalogue lists a whole range of plastic boxes to house all your projects. And we've got circuit boards, accessories, module systems, and metal cases – everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

TAMTRONIK LTD.

PCB AND COMPONENTS FOR ETI PROJECTS

	Component Kit*	P.C.B.
Metal Locator II †	5.91	0.92
House Alarm A	11.60	1.91
House Alarm B	2.39	0.79
Frequency Shifter	6.52	1.46
F/S Omp Amp Supply	4.14	0.63
Stars and Dots	5.76	1.83
Spectrum Analyser	36.51	A 4.46 B 3.86

† 2 1/2" Speaker, 8Ω, for metal locator MK. II 83p each

Prices above are VAT inclusive. P&P 20p. Send large SAE for full details of available Component Kits, P.C.B.'s our Component Catalogue and any specified kit list.

* Kits include ONLY Resistors, Potentiometers, Capacitors and Semi Conductors.

Shop: 32 Market Place, Greatbridge, Tipton, West Midlands
Mail Order: 217 Toll End Road, Greatbridge, Tipton, West Midlands

**217 TOLL END ROAD, TIPTON
WEST MIDLANDS DY4 0HW
TEL. 021-557 9144**



The latest kit innovation!


from **Sparkrite**

Sparkrite is featured by Shaw Taylor in "DRIVE IN"

the quickest fitting

CLIP ON

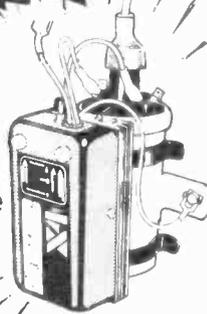capacitive discharge electronic ignition in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.

Electronics Design Associates, Dept. ET 8
82 Bath Street, Walsall, WS13DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D

Send SAE if brochure only required.

X4 KIT	£14.95	
TACHS PULSE SLAVE UNIT	£3.35	

I enclose cheque/PO's for

£

Cheque No.

Access or Barclaycard No.

CHROMASONIC electronics

56 FORTIS GREEN ROAD, MUSWELL HILL, N10 3HN
TELEPHONE: 01-883 3705

OUR LATEST CATALOGUE

CONTAINS FREE

45 pence WORTH

OF VOUCHERS



CONTAINS MICROPROCESSORS + BOARDS, MEMORIES, TTL, CMOS, ICs, PASSIVES, ETC., ETC.

SUPERSAVERS

ALL FULL SPEC DEVICES

TEXAS

TIMER

RED LED

741

555

TIL209

5 for

4 for

10 for

£1.00

£1.00

£1.00

VAT INCLUSIVE PRICE + 25p P. & P.

A4 IC BOOKLET

SUPPLIED FREE WITH ORDERS OF ANY ICs WORTH £5.00 OR MORE, CONTAINS CIRCUITS, PIN CONNECTIONS AND DATA (35p + SAE IF SOLD ALONE).

DORAM

Quality Range of Products
from The Doram Catalogue include:

Single Semiconductors

Wide range of single diodes, zener diodes, rectifiers and general purpose transistors.

Integrated Circuits

Quality linear and digital IC's, regulators etc.

Mains Transformers

Comprehensive top quality selection of low voltage transformers.

Switches

A switch for most applications.

Hand Tools

We stock a large range of tools for most electronic projects.

Books

We can supply a wide range of books from simple projects to detailed text books.

Wire & Cable

Small or large quantities



Send now for the NEW '78 - '79 edition 5 catalogue. ETI
New merchandise including MICRO PROCESSOR BASED KITS.

Over 2,000 items - 120 pages. **75p** incl. p.p.

Name

Address

DORAM

Doram Electronics Ltd,
PO Box TR8,
Wellington Road Estate,
Wellington Bridge, Leeds LS12 2UF

Overseas orders, except for N.Ireland, Please add 35p to cover despatch by Air.

COMPONENT BARGAINS FROM COMMUNICATIONS MEASUREMENT

Capacitors

50uF 10V elect.	5 for 50p
64uF 10V elect.	5 for 50p
150uF 16V elect.	8 for 50p
15uF 16V elect.	8 for 50p
1000uF 16V elect.	3 for 50p
1.5uF 63V Wima	5 for 50p
0.1uF 100V Wima poly	10 for 50p
0.033uF 100V Wima	10 for 50p
1uF 100V ITT	7 for 50p
0.33uF 100V ITT	7 for 50p
0.01uF 125V GEC	10 for 50p
0.1uF 250V Mull 344	8 for 50p
0.01uF 250V Mull 344	8 for 50p
100pF Lemco 350V	10 for 50p
120pF Lemco 350V	10 for 50p
150pF Lemco 350V	10 for 50p
220pF Lemco 350V	10 for 50p

BNC plugs crimp 30p ea*

Pre-set pots

68k Ohms	10p ea
500 Ohms	10p ea

Dil IC sockets 16-pin 10p ea*

Please add VAT at 12½% (8%) on all items and 50p post and package on all orders under £5 (UK), minimum order £2.
Terms — Cash with order

Send s.a.e. for a list of our large range of components

Enquiries and orders to

Communication Measurement Ltd
15 MALLINSON OVAL, HARROGATE, YORKS.

BUILD THE TREASURE TRACER



MK III

METAL
LOCATOR

**AS SEEN
ON BBC-1
& BBC-2
TV**

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components siting printed on.
- Complete after sales service.
- Weighs only 22oz.: handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil

£15.95

Plus £1.20 P&P
Plus £1.37 VAT (8%)

Built, tested and Guaranteed

£20.95

Plus £1.20 P&P
Plus £1.77 VAT (8%)

MINIKITS ELECTRONICS,
6d Cleveland Road, South Woodford,
LONDON E18 2AN
(Mail order only)

AIRAMCO LTD. MICRO COMPUTER PRODUCTS

All products brand new with full industrial specification

555 Timer MDIP	30
AY51013 UART	5.35
AY52376 Keyboard Encoder	13.75
21L02-1 1024 x 1 SRAM	1.35
SPECIAL OFFER: 21L02-1 8 for	9.60

2104 4096 x 1 DRAM 16 pin 300 ns	3.50
SPECIAL OFFER: 2104's 8 for	26.00
2107B 4096 x 1 DRAM 22 pin 200 ns	3.50
SPECIAL OFFER: 2107Bs 8 for	26.00
4116 16,384 x 1 DRAM 16 pin	20.00
SPECIAL OFFER: 8 for	144.00

1702A 256 x 8 UVEPROM	4.85
2708A 1024 x 8 UNVERPROM	9.99
2716A 2048 x UVEPROM TI	21.00
SFF 96364 VDU & Keyboard chip	18.00

We are now the U.K. Distributors for Jade Computer Products. All S100 items shown in Jade advertisement (ETI May '78) and many others available from Airamco Ltd.

Discounts for quantity P.O.A.

Trade enquiries and orders welcome
P&P ADD 40p THEN ADD VAT @ 8%



MAIL ORDER ONLY



24 hr. Ansaphone order service with ACCESS or BARCLAYCARD No

AIRAMCO LTD.
30 WITCHES LINN, ARROSSAN
AYRSHIRE KA22 7BR
Tel: 0294 65530

ELECTRONIC CALCULATORS SCIENTIFIC

*TEXAS PC100B (Printing Unit for T159, T158)	£181.22
HP & TEXAS Libraries and Accessories avail	POA
*TEXAS T1-59 (Card Progs. 960 steps of 100 Mem.)	£207.00
plus Applied Statistics Model	£74.00
*TEXAS T1-58 (Key Progs. 480 steps or 60 Mem.)	£74.00
*TEXAS T157 (Key Progr. 8 Mem. up to 150 Keystrokes — 50 Progr. steps)	£29.95
*TEXAS T1-45 (new updated version of T140)	£22.40
*TEXAS T1-33 (spec. as T1-30 but 3 Mem.)	£13.95
*TEXAS 42 MBA (10 Dig. Fin/Stat Progr. 12 Mem. 32 Keystrokes)	£40.00
*TEXAS SR51-III (New 8 Dig. + Exp 10 Mem. 32 Progr. Steps Stat/Sci)	£30.00
TEXAS T1 Programmer (Hexadecimal/Oct)	£46.00
*TEXAS T158 (Complete with Master Module plus Applied Statistics Module)	£94.00
*CBM 4190R (Scient. Pre-prog. 14 dig./EXP)	£25.50
*CBM PR100 (100 Mem. 72 step prog.)	£29.50
*CBM S61 (stat. plus sci 6 mem M and S div. chi sq. DIS. LIN. Regn. etc.)	£54.00
Commodore PET Computer (complete as mfg specification)	£643.00
*HP 19C (Continuous mem. key prog. printer)	£183.00
*HP29C (as 19C but no printer)	£115.00
*HP27 (10 mem. sci./fin./stat. 8 digit + exp)	£104.00
*HP 67 (card prog. 224 steps 26 mem.)	£260.00
*HP 97 (card prog. 224 steps print 26 mem.)	£432.00
All HP range available including NEW 'E' Range. Prices on request	
CASIO CO1 (Cal. Dig. Alarm Clock)	£23.00
CASIO 3000 (LCD Sci-Std./Div. Polar Rec., etc.)	£22.50
*CASIO FX201P (sci. 11 mem. 127 step prog.)	£45.00
*FORTIAN SYSTEM	£45.00
*CASIO PROFXL (as above but card prog.)	£99.00
FREE Mains charger included	

SPECIAL OFFER

Texas T159 with PC100B £356
(Price includes all items as mfg. specification)

SPECIFICATION LISTS ON REQUEST (Send S.A. Envelope)

GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 8%) BUT INC. P&P CHEQUE WITH ORDER
Company, Hospital and Government orders accepted by phone

EXPORT ORDERS ACCEPTED
Barclaycard. Access order accepted by phone

Tel. 01-455 9855

MOUNTAINDENE LTD
22 Cowper Street, London, EC2
(Near Old St. Station) Tel. 01-455 9855

ALL PURPOSE POWER SUPPLY

The ETI project team presents a high performance Power Supply Unit based on an encapsulated regulator block.

THOSE OF YOU who threw up various parts of your anatomy at the sight of yet another power supply design probably fall into two groups. One will use batteries, will always have used batteries and won't see why they shouldn't continue to use batteries ad infinitum. There will be others who have a power supply — be it ever so humble — and are fed up with four-part articles describing the construction of same.

What is this fetish with PSUs?

Cell Your Batteries

We appeal to those of you in the first category to give batteries the old heave ho if only on financial grounds — batteries really are a very expensive way of buying power. They also come in fixed voltages and any current limiting attributes are limited to dying a death at the first sign of the short circuits that are bound to occur in even the most ordered of development work.


Supply And Demand

To those of you who fall into our second group we ask you to take a look at your present Power Supply. Is it up to the job? Does it have variable current limiting (0-1 A)? Can it provide an adjustable output of up to 30 volts? Does it have a couple of LEDs to indicate its mode of operation (voltage/current)? Can you isolate the DC output? Does it provide for remote voltage sensing?

Needless to say our design meets all these criteria.

Meg A Mania

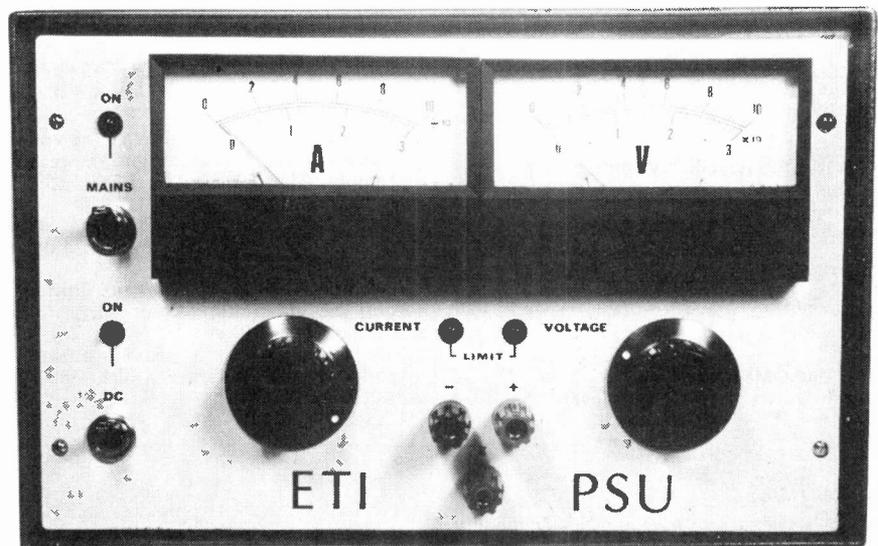The unit is easy to build as it is based on an encapsulated Power Supply Module. The module itself



takes care of nearly all the work but in its naked form can only provide a 100m A output, Q1, acting as a series pass element, means that up to 1 A output can be provided.

The photographs show that we did not use a PCB for this project but mounted components directly to the PSU module or on a small strip of tag board.

Construction

Construction should be self-explanatory if the circuit diagram is followed through, about the only point to watch is the gauge of wire used in the current carrying sections of the design, make sure it's of adequate rating. Also make sure that the sense wires are taken to a point as near to the output sockets as near to the output sockets as possible. A switch jack socket inserted in the

sense leads will provide a remote voltage sense option.

The meters are an optional extra, but we felt that these added that extra touch of professionalism to the device.

ETI ►


BUYLINES

THE regulator module is available from Doram Electronics for £13.05.

The case used in the prototype was an Alson type 23 (10½ x 6½ x 6½). Alson are at 5/7 Long Street, London.

The other components should be generally available.

FIG. 1. Circuit diagram of the power supply. The components are mounted either on the module itself or on a small tag strip — see photograph below.

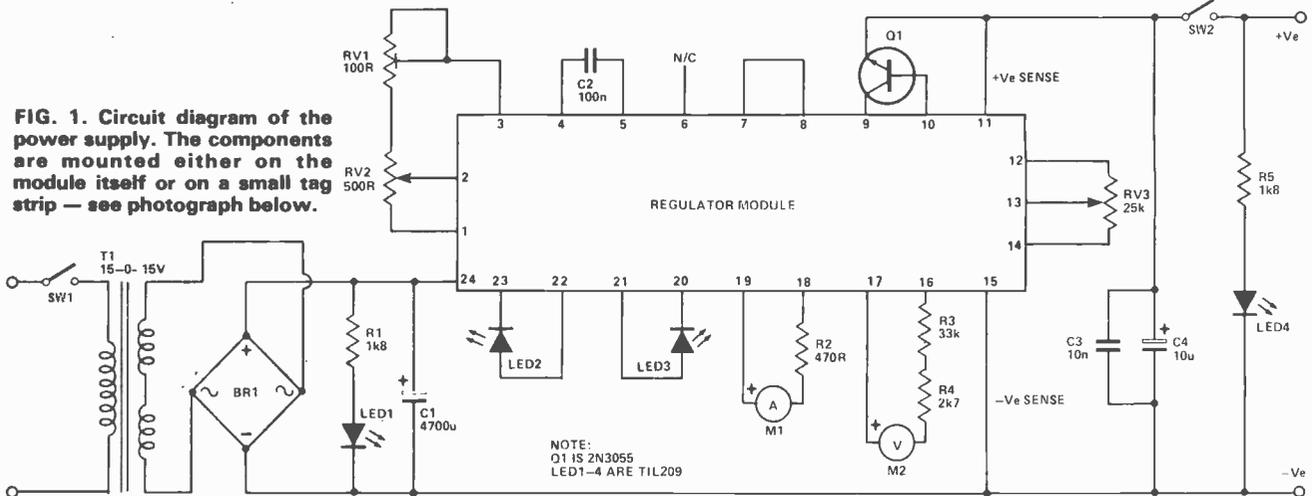

PARTS LIST

RESISTORS (all 5% 1/4W unless * 2% MO).

R1, 5	1k8
R2*	470R
R3*	33k
R4*	2k7

POTENTIOMETERS

RV1	100R preset
RV2	500R
RV3	25k

CAPACITORS

C1	4700u 50V electrolytic
C2	100n 250V polyester
C3	10n 250V polyester
C4	10u 50V electrolytic

SEMICONDUCTORS

Q1	2N 3055
LED1-4	TIL 209
BR1	2A 50V

TRANSFORMER

T1	15-0-15 1.5A
----	--------------

SWITCHES

SW1, 2	Single pole on off
--------	--------------------

MISCELLANEOUS

1-30V, 100mA regulator module, tag strip, 100uA meters, case

HOW IT WORKS

THE AC mains is stepped down to 30 volts by transformer T1. This AC signal is rectified and smoothed by BR1 and C1. LED1 indicates the unit is on.

The regulator module provides all the control functions associated with a Power Supply.

RV1 and RV2 set the current limit, RV1 setting the maximum output current. RV3 sets the output voltage.

The basic module can provide outputs of up to 100mA only, Q1 increase the module's output capability to 1A.

LEDs 2 and 3 indicate which mode of

operation the supply is in (LED2 is current mode, LED3 is voltage).


The resistors in series with the meters should be selected to ensure that the meters are calibrated, the values given are for our prototype and may need slight alteration.

C2 is included to improve the stability of the design.

The output from the module is further smoothed by C3, C4.

SW2 is the DC isolation switch and LED4 indicates that a DC output is present at the unit's output terminals.

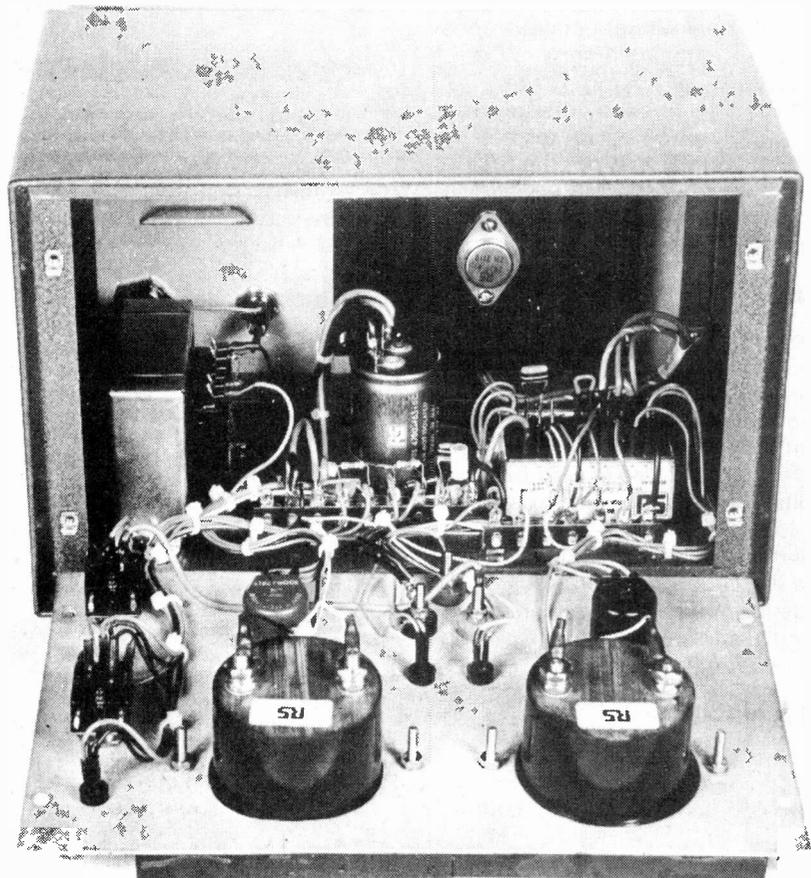The photograph, right, shows clearly the method of construction adopted in our prototype. Ensure that the wires carrying high currents are of adequate rating.



ETI BOOK SERVICE

computing

BASIC: A Self Teaching Guide (2nd Edition) £4.50
by ALBRECHT, R. L.

Teach yourself the programming language BASIC. You will learn how to use the computer as a tool in home or office and you will need no special maths or science background.

Illustrating BASIC £2.20
by ALCOCK, D.

This book presents a popular and widely available language called BASIC and explains how to write simple programs.

Microprocessors £10.65
by ALTMAN, L.

Gives a general overview of the technology design ideas and explains practical applications.

Applying Microprocessors £12.00
by ALTMAN, L.

Follow up volume which takes you into the second and third generation devices.

Intro to Microprocessors £6.00
by ASPINALL, D.

Explains the characteristics of the component.

How to Buy and Use Minicomputers and Microcomputers £7.50
by BARDEN, W.

Discusses these smaller computers and shows how they can be used in a variety of practical and recreational tasks in the home or business.

How to Program Microcomputers £6.75
by BARDEN, W.

This book explains assembly-language programming of microcomputers based on the Intel 8080, Motorola MC6800, and MOS Technology MC6502 microprocessors.

Introduction to Microcomputers and Microprocessors £7.50
by BARNA, A.

Provides the basic knowledge required to understand microprocessor systems. Presents a fundamental discussion of many topics in both hardware and software.

Microprocessors in Instruments and Control £11.80
by BIBBERO, R. J.

Introduces the background elements, paying particular regard to the dynamics and computational instrumentation required to accomplish real-time data processing tasks.

Basic BASIC £7.50
by COAN, J. S.

An introduction to computer programming in BASIC language.

Microprocessor Programming for Computer Hobbyists £7.00
by GRAHAM, N.

The Computer Book £6.20
by HAVILAND, R. P.

Building super calculators and minicomputer hardware with calculator chips.

Microcomputers, Microprocessors, Hardware Software and Applications £14.25
by HILBURN, J. L.

Complete and practical introduction to the design, programming, operation, uses, and maintenance of modern microprocessors, their integrated circuits and other components.

Microprocessor Systems Design £14.35
by KLINGMAN, E.

Outstanding for its information on real microprocessors, this text is both an introduction and a detailed information source treating over a dozen processors, including new third generation devices. No prior knowledge of microprocessors or microelectronics is required of the reader.

BASIC Programming £6.10
by KEMENY, J. G.

A basic text.

Microprocessor and Small Digital Computer Systems for Engineers and Scientists £19.00
by KORN, G. A.

This book covers the types, languages, design, software and applications of microprocessors.

TV Typewriter Cookbook £7.40
by LANCASTER, D.

An in-depth coverage of tv typewriters (tv'ts)—the only truly low-cost microcomputer and small-system display interface. Covers tvt terminology, principles of operation, tv configurations, memories, system design, cursor and update circuitry and techniques, hard copy, color graphics, and keyboards and encoders.

Microprocessors — Technology, Architecture, and Applications £8.00
by McGLYNN, D. R.

This introduction to the "computer-on-a-chip" provides a clear explanation of this important new device. It describes the computer elements and electronic semiconductor technologies that characterize microprocessors.

Programming Microprocessors £5.50
by McMURRAN

A practical programming guide that includes architecture, arithmetic/logic operations, fixed and floating-point computations, data exchange with peripheral devices/compilers and other programming aids.

Microcomputer Based Design £18.00
by PEATMAN, J. B.

This book is intended for undergraduate courses on microprocessors.

Microprocessor and Microprocessor Systems £20.50
by RAO, G. U.

A completely up-to-date report on the state of the art of microprocessors and microcomputers, written by one of the leading experts. It thoroughly analyzes currently available equipment, including associated large scale integration hardware and firmware.

The 8080A Bugbook: Microcomputer Interfacing and Programming £7.60
by RONY, P. H.

The principles, concepts and applications of an 8-bit microcomputer based on the 8080 microprocessor IC chip. The emphasis is on the computer as a controller.

6800 Software Gourmet Guide and Cookbook £7.80
by SCELBI

8080 Software Gourmet Guide and Cookbook £7.80
by SCELBI

Understanding Microcomputers £7.60
by SCELBI

Microprocessors and Microcomputers £18.00
by SOUCEK, B.


Here's a description of the application, programming, and interfacing techniques common to all microprocessors. It concentrates on detailed descriptions of representative microprocessor families and includes explanations of digital codes, logical systems, and microcomputer organization.

Microcomputer Primer £6.05
by WAITE, M.

Introduces the beginner to the basic principles of the microcomputers. Discusses the five main parts of a computer — central processing unit, memory, input/output interfaces, and programs. The important characteristics of several well-known microprocessors are given and a chapter is included on programming your own microcomputer.

Microprocessor/Microprogramming Handbook £6.00
by WARD

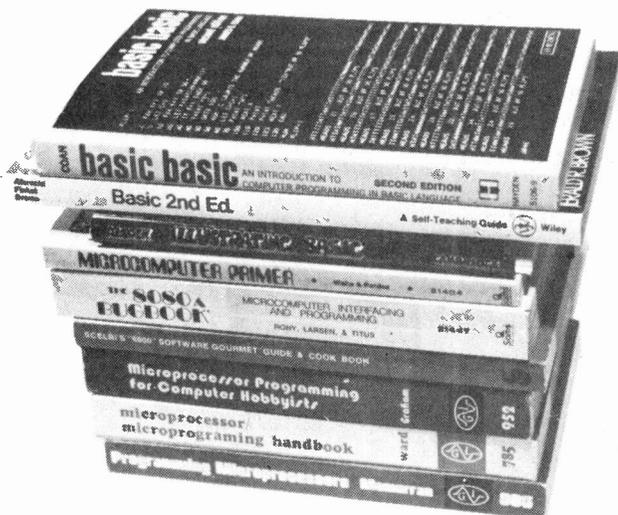Authoritative practical guide to microprocessor construction, programming and applications.



HOW TO ORDER:
Make cheques etc payable to ETI Book Service.
Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks.
All prices include P & P.

ANNOUNCING THE **MICROS**

JOIN THE MICRO REVOLUTION



£399 for a Z80 based microcomputer, built and tested

Designed for educational establishments, personal computing and small business users

- * Includes 1K monitor Eprom, 47 key solid state keyboard, video, TV, cassette and teletypewriter interfaces, serial i/o, 2 parallel i/o ports, 2K bytes RAM, power supplies and instrument housing.
- * Connect to domestic TV or video monitor to complete the system
- * 48 x 16 character video matrix
- * 47 key contactless ASC11 keyboard
- * Hard copy on teletypewriter
- * 2 TTL compatible parallel i/o ports
- * RS232 serial i/o port
- * Load and dump programmes on unmodified cassette recorder
- * Up to 16K byte mixed RAM and Eprom in table top housing
- * Expandable up to 64K bytes
- * Security locked power switch
- * British designed and built
- * Available in kit form for £360
- * Credit terms available

THE MICRONICS COMPANY


1, STATION ROAD TWICKENHAM MIDDLESEX

PART OF THE MICRO REVOLUTION

Prices exclusive of VAT and carriage

audiophile.....

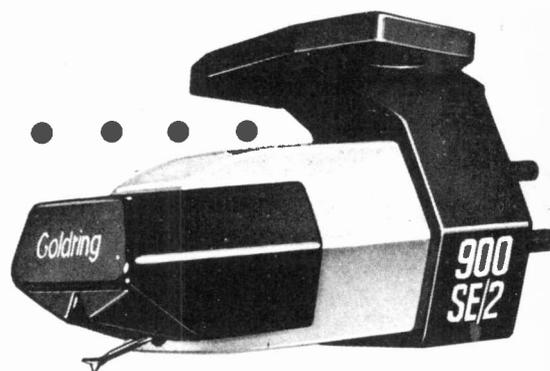Ron Harris examines a top of the range offering from Goldring Products — a new version of the G900SE — and asks whether or not this is the



BEST OF BRITISH?

GOLDRING ARE ONE of the best known names in the hi-fi industry. Most of us have at some time or other undoubtedly possessed one of their G800 series cartridges, sometimes without realising it! (Checked the end of that package deal arm recently?)

In the lower price ranges the company has been more than able to hold its own against all comers, but the higher strata have seemed beyond their reach of late. Last year they launched the G900SE, which sold at a ridiculous £25 or thereabouts, and produced an excellent sound quality. The unit never received the acclaim it deserved.

One can't help feeling that had one of the American cantilever giants produced the G900, we would be hearing about it still. Goldring, however, had themselves some financial difficulties to overcome — which they now seem to have risen above — and this could not have helped.

This month sees the release of the 900E, a lower priced cartridge, and a Mk 2 of the G900SE itself. It is this we concern ourselves with here.

Time To Mark Two?

Basically the unit is a low mass moving magnet design of high compliance, intended for use only in arms of low inertia. The cartridges weigh only 4g, and the reduction in mass over its predecessor has been achieved by what Goldring describe as "formerless winding" of the coils within the body.

More important still though, tip mass is also low at 0.32mg. A tie wire is fitted to dampen stylus movement(?) and also to act as a leakage path for static on the record surface. Quite a bit of innovation going on here, and it was to prove interesting to discover what effect, if any, this was going to have on the sound of this new Goldring.

Sound Results

As can be seen from the test results, technically the unit acquitted itself well with good separation, well balanced outputs and a good smooth frequency response. The rising (extreme) top end response may well be engineered to suit the unit to CD-4 usage. In stereo mode the resonance should not prove a problem.


The sample was fitted into an SME Series III for test purposes, and initially the mounting method raised suspicions as to its rigidity. These proved to be unfounded, however — but it still *looks* wrong!

With a mass of only 4g, the Goldring would pose no problems to arms capable of doing it justice.

Off The Beaten Track?

Once balanced out, and with no damping applied to the arm, tracking checks were undertaken using the ubiquitous HFS 75 and several of our own torture tracks. At Goldring's stated 1g, all bands except the highest level were handled with confidence. Band C could just be tracked at around 1.1g, but only just. No improvement was apparent with increase in excess of this and so we left the tracking weight at 1.1g throughout the listening tests. ▶

SPECIFICATION

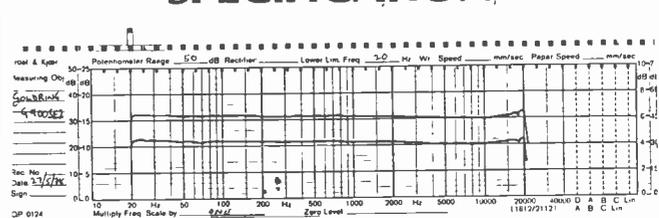

Above: frequency response plot for our sample of the G900SE. Upper trace is the left channel, and the lower the right.

Below: Specification and test results for the same sample of the Goldring cartridge.

Frequency Response:	20Hz to 20kHz \pm 2dB	see graph
Playing Weight Range:	0.75 to 1.5 grams	best at 1.1g
Tip Mass:	0.32mg	—
Channel Separation:	25dB	30dB (L on R 1kHz)
Output at 5cm/sec, 1kHz:	4.5mV	L—5.4mV; R—5.2mV
Weight:	4 grams	—
Inductance (1kHz):	570mH	—
(10kHz):	540mH	—

Test conditions — tracking force 1.1g, load 47k, 150p.

This result, while not as good as the best that say a V15 can manage, is still very commendable and a great deal better than the moving coil devices available at present. No change was observed in tracking ability with damping applied to the arm.

Resulting Sound

With all the test completed - and no gremlins apparent - down to listening. Initially we simply wired it up, switched it on and got on with it! First impressions were of a smooth sound with no obvious vices and a well controlled bass extension. Slight recession of extreme treble perhaps.

Over an extended listening period however we came to appreciate just how good this new Goldring can be. It has depth and it has an open quality which puts you in with the music, without ever being bright or hard.

Comparisons were made between the G900 and several other top-flight devices, including an Ultimo 20A, Sonus Blue and the new Entré moving coil unit. These showed without doubt that the G900SE is a match for any of them! At this level of fidelity it comes down more than ever to a case of personal taste. On a subjective level the Goldring was preferred to the Ultimo for its smoother presentation, although the 20A did have greater depth. The Sonus likewise came out second best, for no other reason than that the G900SE sounded better! The bass was tighter and the mid-range less aggressive.

Battle With The Coil

The most interesting comparison was between the Entré and the G900 however. The latter has many of the qualities so beloved by the devotees of the moving coil, but just fails to match the best of them in terms of delicacy of presentation. The Entré did provide a greater sense of detail throughout the frequency spectrum, but its bass response was never as well defined, and the Goldring tracks better. You pay your money and you take your choice. . . .

What A Load Of . . .

Our main reservation concerns the specified loading for the cartridge.


This is 47k and 150p, and this was the figure the cartridge was tested at. However most amplifier and pickup lead combinations will exceed this, usually providing around 200p-250p. This could have an effect on the top end response of the cartridge, especially if the capacitance offered is higher than the upper specified limit of 200p.

We varied the load the cartridge saw to gain an idea of its performance on this parameter, and only when we reached about 350p could we honestly say a subjective difference was present, this manifesting itself most clearly on cymbals.

In practise then anything between 100p and 300p should be fine. It is interesting to note that Shure specify a load of 450p for the V15 III, and the fact that this is rarely met may account in some measure for the "bright" reputation that unit has made for itself, since lower values will act to boost hf response.

Impact And All That

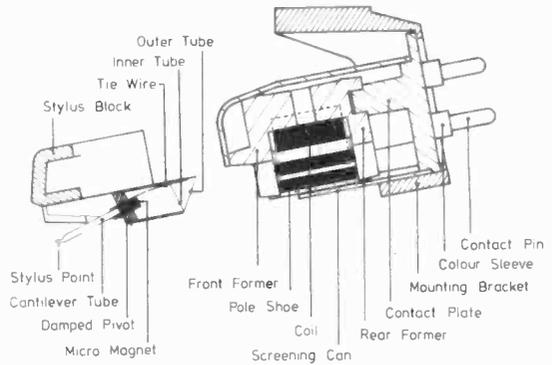Overall then the sound of the Goldring can be described as smooth, detailed with plenty of depth and good extension into the bass. It will undoubtedly come



What goes where inside the Goldring G900SE2. The tie wire is claimed to control stylus movement in the 'unwanted modes' — whatever they are — and to provide a leakage path for surface static. In practice the G900SE did prove highly insensitive to surface noise, whether this was due to the little wire . . .

as a surprise to many devotees of the "bright-is-beautiful" school, but extended listening will pay even them dividends. The sound perhaps lacks an immediate nature a little *too* much, but again that is for you to decide. Impact it has — but only when the music does!!

It is good to see a British manufacturer produce a product of this quality, and be able to retail it at a price less than esoteric. At its expected cost of around £50 the G900SE disposes of similarly priced opposition with a disdainful waggle of the cantilever, and indeed takes its place with the very best moving magnet designs of the day.

ETI

the MIGHTY MIDGETS

S · R · B
MINIATURE
SOLDERING IRONS AND ACCESSORIES



	RETAIL PRICE each inc. v.a.t.	POSTAGE extra.
18 WATT IRON inc. No.20 BIT	£3.78	22p
SPARE BITS	44p	—
STANDS	£3.25	65p
SOLDER: SAVBIT 20'	52p	9p
" 10'	26p	4p
LOWMELT 10'	65p	9p
I.C. DESOLDERING BIT	88p	9p

BIT SIZES: No.19 (1.5 mm) No. 20 (3 mm)
No. 21 (4.5 mm) No. 22 (6 mm)

From your Local Dealer or Direct from Manufacturers

S & R. BREWSTER LTD

86-88 Union St · Plymouth PL1 3HG

Tel: 0752 65011 TRADE ENQUIRIES WELCOME

FANTASTIC BARGAINS

SAVE! SAVE! SAVE! £££££££s

FIRST COME, FIRST SERVED / LIMITED QUANTITIES
ALL MUST BE SOLD — TOP QUALITY KITS + PARTS

* SAVE UP *
* TO 50% *

G.I. INTEGRATED CIRCUITS

with application sheet
AY-3-8710 Tank
~~£10.90~~ **£6.90**
AY-3-8600 10 game
~~£8.90~~ **£5.90**
AY-3-8500 6 game
~~£5.50~~ **£3.90**
AY-3-8760 Motorbike
~~£11.90~~ **£6.90**
AY-3-8603 Car Race
£5.90 New

TV GAME KITS

ETI Tank complete B&W
~~£27.90~~ **£22.90**

ETI Tank colour add on
~~£5.90~~ **£4.50**
ETI Tank Basic B&W
~~£19.90~~ **£14.90**
Stunt Cycle complete B&W
~~£25.90~~ **£19.90**
Stunt Cycle Basic B&W
~~£18.90~~ **£12.90**
10 Game complete col.
~~£34.90~~ **£25.90**
10 Game Basic col.
~~£20.90~~ **£14.90**
6 Game Basic col.
~~£16.50~~ **£8.90**

Complete Kits include power supply boxes - cables - controls - no extras

Basic Kits - PCB and all PCB Components

PRINTED CIRCUIT BOARDS

10 Game colour ~~£3.90~~ **£1.90**
10 Game B&W ~~£1.90~~ **70p**
Tank Battle ~~£3.90~~ **£1.90**
All ready drilled and tinned

SOUND & VISION MODULATORS

Built and guaranteed
~~£5.50~~ **£3.90**

JOYSTICK CONTROLS

Pair ~~£3.50~~ **£2.60**
(200Klin)

MAINS ADAPTOR

9V 150mA ~~£3.25~~ **£2.90**

BOXES

Tank Box Set ~~£4.90~~ **£3.25**
10 Game Set ~~£4.90~~ **£3.25**
The main box in each set has a printed fascia plate

STUNT CYCLE

(4 Games)
Ready made and guaranteed with power supply
~~£29.90~~

£22.90 **JUST PLUG IN AND GO**

All prices include VAT. For orders under £10 add 20p p&p. Cheques and postal orders to be made payable to TELEPLAY, send your order (No stamp needed,) to Teleplay, Freepost, Barnet, EN5 2BR. or telephone your order quoting your Barclaycard or Access number



SHOP OPEN - 10am to 7pm - Monday to Saturday


CLOSE TO NEW BARNET BR STATION - MOORGATE LINE



teleplay

14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922

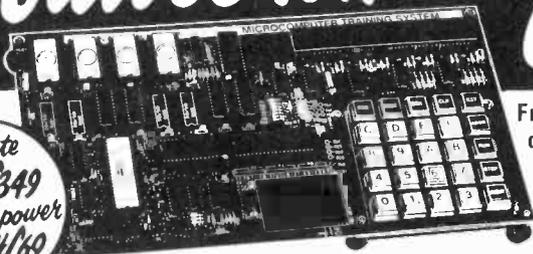You'll be at home with our Micro Computer Course



Complete course **£349**
Optional power supply **£69**

From the Learning Tree comes the first fully assembled, complete SELF-STUDY MICRO COMPUTER TRAINING COURSE. Now you can learn all about Micros, and how to use them, in the comfort of your own home, office or school. THE COURSE COMES COMPLETE WITH A 650 PAGE WORK/TEXT BOOK AND A READY BUILT MICRO COMPUTER

WITH THE ICS EDUCATIONAL MONITOR PROGRAMME. The work book is organised into step-by-step sections covering Software and Hardware from fundamentals to advanced techniques. There are many exercises covering Programming and Construction which can all be performed using the Micro Computer supplied and the extensive Debug facilities of the Educational Monitor.

Course content

- SOFTWARE AND HARDWARE FUNDAMENTALS
- MICRO INSTRUCTIONS
- PROGRAMMING TECHNIQUES
- SUBROUTINES
- INTERFACING (CASSETTE, TTY, etc.)
- MATHEMATICAL ROUTINES (INCLUDING FLOATING POINT)
- REAL TIME APPLICATIONS
- INTERRUPT HANDLING
- ADVANCED I/O TECHNIQUES

Micro Computer

- 1K Bytes of RAM
- 1Kb PROM. CONTAINING THE EDUCATIONAL MONITOR PROGRAMME
- KEYBOARD AND DISPLAY ON BOARD
- FREE AREA FOR HARDWARE UPGRADES
- 3 PROGRAMMABLE 8-bit PARALLEL I/O PORTS
- 2 SERIAL I/O PORTS (110 Baud.)
- 1 EXTERNAL INTERRUPT
- USES THE 8080A MICROPROCESSOR

Using these features you will be guided through a logical syllabus, learning both Hardware and Software techniques. When you have finished you will have a working Micro Computer. And the knowledge to use it.



Another I.C.S.P. product available exclusively through—

COMPUTER MARKETING Ecfild House, 641 London Rd., West Thurrock, Essex. Tel: Purfleet 7161 Telex 896786

Greenbank Electronics

CMOS

Cut prices for Amateur users and Export only. Note: Industrial users - No % discount available on these prices. Instead use franchised distributors standard prices. List available on request.

Mostly Motorola, RCA

4000	15p	4050	52p	40107	65p	4514	£2.65
4001	17p	4051	52p	40108	£5.36	4515	£2.99
4002	£1.05	4052	75p	40109	£1.08		
4003	11p	4053	75p	40181	£3.39	4517	£3.82
4007	18p	4054	£1.20	40182	£1.40	4518	£1.02
4008	52p	4055	£1.34	40192	£1.40	4519	51p
4009	58p	4056	£1.34	40193	£1.40	4520	£1.08
4010	58p	4057	£25.70	40194	£1.18	4521	£1.08
4011	19p	4059	£4.80	40257	£1.48	4522	£1.08
4012	18p	4060	£1.15	4160	£1.08	4524	N/S
4013	55p	4061	£15.67	4161	£1.08	4526	£1.08
4014	99p	4062T	£10.00	4162	£1.08	4527	£1.52
4015	53p	4063	£1.09	4163	£1.08	4528	99p
4016	52p	4064	N/S	4174	£1.08	4529	£1.14
4017	99p	4065	N/S	4175	99p	4530	85p
4025	19p	4066	57p	4194	£1.17	4531	£1.45
4018	99p	4067	£3.80	4408	£6.59	4532	£1.27
4019	60p	4068	22p	4409	£6.59	4534	£5.13
4020	£1.02	4068	22p	4410	£5.73	4536	£3.69
4021	94p	4069	23p	4411	£9.58	4537A	£13.23
4022	86p	4070	21p	4412L	£12.92	4538	91p
4023	20p	4071	21p	4412L	£12.92	4539	91p
4024	76p	4072	21p	4415F	£7.50	4541	£1.14
4025	19p	4073	23p	4415F	N/S	4543	£1.59
4026	£1.80	4075	£1.05	4419	£2.68	4549	£3.69
4027	55p	4076	23p	4422	£5.00	4552	£10.55
4028	81p	4077	21p	4431	TBA	4553	£3.87
4029	£1.09	4078	22p	4432	£11.32	4554	£1.19
4030	58p	4081	21p	4435	£7.93	4555	78p
4031	£2.30	4082	73p	4450	£2.67	4556	78p
4032	£1.00	4085	£1.50	4451	£2.67	4558	£1.14
4033	£1.45	4086	63p	4452	TBA	4559	£3.69
4034	£1.96	4089	£1.90	4490P	£6.54	4560	£1.84
4035	£1.20	4093	£1.05	4493P	£4.92	4561	65p
4036	£2.45	4094	£1.90	4493P	£6.54	4560	£1.84
4037	£1.00	4095	£1.05	4700	£1.75	4562	£5.33
4038	£1.00	4096	£1.05	4700	£1.75	4562	£5.33
4039	£2.45	4097	£3.72	4500	£5.96	4566	£1.59
4040	£1.05	4098	£1.10	4501	17p	4568	£2.38
4041	85p	4099	£1.90	4502	91p	4569	£2.57
4042	81p	4096	N/S	4503	79p	4572	25p
4043	94p	4010	£2.50	4505	£5.71	4580	£5.74
4044	99p	4011	£1.61	4506	51p	4581	£2.62
4045	£1.45	4012	£2.12	4507	96p	4582	96p
4046	£1.30	4013	£2.12	4508	£2.48	4583	76p
4047	99p	4014	£1.09	4510	£1.29	4584	43p
4048	58p	4015	£1.06	4511	£1.38	4585	£1.01
4049	52p	4016	71p	4512	81p	4599	£2.06

7400 Series (National)

7400	26p	74015A	£3.93	740307	74p	740325	£8.20
7402	26p	74017	£2.36	740308	£2.63	740326	£8.28
7404	26p	74018	£1.49	740309	£1.74	740327	£8.28
7406	26p	74016	£1.49	740310	£7.20	740328	£8.28
7410	26p	74012	£1.49	740312	£9.52	740329	£15.80
7414	£1.51	74013	£1.48	740314	£1.50	740330	£15.80
7420	26p	74014	£1.31	740315	£1.20	80036	£1.20
7430	26p	74015	£1.31	740318	£2.90	80036	92p
7432	26p	74017	£1.21	740320	£11.83	80037	87p
7442	£1.20	74014	£1.21	740321	£11.83	80038	92p
7448	£2.37	74015	£1.21	740322	£4.93	80029	£6.21
7473	74p	74012	£1.48	740324	£1.49	80029	£6.21
7474	63p	74013	£1.49	740325	£3.03	80030	£6.21
7476	74p	74019	£1.31				
7483	£1.97	74020	£7.20				
7485	£1.97	74021	£1.50				
7486	69p	74023	£2.30				
7489	£4.65	74030	74p				
7490	92p	74032	74p				
7493	92p	74033	74p				
7496	£1.31	74034	74p				
74107	£1.31	74035	£7.71				
74150	£4.17	74036	74p				
74151	£2.63						

TIMEBOX. Digital Clock Case, 56 x 131 x 71.5 mm with red acrylic window. Choice of case colour, white, red, orange, blue. £2.06.

VEROBOARD

0.1" Pitch with copper strips
 2 1/2" x 1" (pack of five) 52p
 2 1/2" x 3/4" 36p
 2 1/2" x 5/8" 43p
 2 1/2" x 1 1/2" £1.34
 3 1/4" x 3/4" 43p
 3 1/4" x 5/8" 48p
 3 1/4" x 1 1/2" £1.73
 4 7/8" x 9/8" £2.22

0.1" Plain board (no strips) 28p
 3 1/4" x 2 1/2" 45p
 3 1/4" x 5 1/2" £1.28
 Terminal pins £1.50/500
 V-Q DIP board 89p
 DIP breadboard £2.42
 Spot face cutter 69p
 Pin insertion tool 89p

SOLDERCON PINS

100 50p
 1000 £3.50

DIP SOCKETS

8/14/16 pin 10p/12p/13p

TIMER IC'S

NE 555/556 36p/70p

OP-AMPS

CA 3130 (COS/MOS) 94p
 CA 3130 (Plastic) 84p
 CA 3140 (Plastic) 75p
 741 MiniMidi 22p
 100 off 741s £17.50

LED DISPLAYS

FND 500/507 Jumbo 0.1 7-segment £1.30
 FND 357 0.35 c.a. 7-segment £1.40

"E" LED DISPLAYS. Class II

devices, but fully guaranteed by us for even segment brilliance, etc. - money back or exchange if not satisfied.

DL-704E 0.3in ca. 85p
 DL-707E 0.3in ca. £2.00
 DL-728E 2 x 0.5in ca. £5.00
 DL-727E 2 x 0.5in ca. £2.00
 DL-750E 0.6in ca. £1.80
 DL-747E 6in ca. £1.80

LIQUID CRYSTAL DISPLAY

4 x 0.5in digital 40 pin DIL £9.00

CLOCK CHIPS

AY-5 1224A £3.50
 MK 50253 £5.50
 MK 50362/50366 £6.95
 MC 14440 (LCD) £11.58

SIX DECADE COUNTER

MK 50395/6/7 £6.75
 MK 50398/9 £6.20

TOP OCTAVE GENERATOR

MK 50240 £10.35

LINE'S FROM OUR VAST STOCK Please add post 35p per order. THESE ARE ALL SPECIAL OFFERS BELOW MANUFACTURERS' PRICES. ALL NEW STOCK. FULLY GUARANTEED. EXPORT ENQUIRIES INVITED ON ALL ITEMS.

CALCULATOR CHIPS - GENERAL INSTRUMENT GIMT4 on anti-static foam £1.75 ea, 10 for £15.00, 100 for £125.00. For use with multiple Bowmar display.

Six button selector switch with built-in 100K pots. Self cancelling buttons. Ideal for use with varicap tuned FM sets and TVs 120x64x55mm £2. 10 for £15.

BOWMAR 9 digit calculator display with P.C. connector 0.2" digits, common cathode with red bezel £1.25. 10 for £10. 100 for £90.

TEXAS 19 gold plated snap key contacts on gold plated P.C. Board - all kinds of useful applications. Size 70x80x2mm high. 65p, 10 for £5.

OSMOR change-over reed relay with 12V coil. Approx. 20mA operating current. 59x17x13mm 75p. 10 for £6. 100 for £50. 1,000 for £400.

Small mains transformers with 240V pri. 12V@100mA 60x40x42mm 95p. 10 for £7.50. 100 for £65. Valve type 40 1 Output TX 61x15x42mm 75p. 10 for £6. Output TX EL84 80x53x34mm 95p. 10 for £8.

Clacking oscillator PYE DYNAMICS thick film 1MHz 5V supply 19x25x6mm 85p. 10 for £7. FAIRCHILD FND 10 0 15" 7 segment display. Common Cathode 50p. 10 for £5.00. 100 for £30.

6 + 6 WATT STEREO 24/28V 8 ohm Input 50/60 M/V into 500K. Tone Controls on P/C £4.95. Size 15.5x14x4.5 cm WITH CIRCUIT

T4/R/Low-MEDIUM & F/M TUNER WITH MC1310 DECODER * 3-BUTTON SELECTOR SWITCHES * INPUT SELECTORS FOR GRAM AND TAPE * Supplied complete with FRONT END LIPHEX AND FERRITE AERIAL * SIMPLE INTERCONNECTIONS * Size 19x13cm THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT

POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95.

Built 5 watt power amplifier Gould-Advance. 4-8 ohms output. up to 24V supply. 500mV into 2K input. Complete with instructions. 11.5x6x3cm £3.00. 10 for £22.50. Power supply kit £2.20.

HONEYWELL Proximity Detector Integral Amplifier 8V DC £2.50 ea. 10 for £22.

SMITHS INDUSTRIES AUDIBLE TRANSISTORISED WARNING DEVICE 6-12 volts. Size 30mm x 10mm. Polysided 50p ea. 10 for £4. 100 for £35.

SUPPLY PANEL containing 6 high quality 0.1µF 10% 1 KV poly capacitors. 102x19x75mm 10 for £2.50.

ALMA pushbutton reed switches, push to make. High reliability 18x27x18mm 35p. 25 for £7. 100 for £25. 1000 for £225.

BURROUGHS 9 digit Panalex Calculator display, 7 segment 0.25 digits, neon type with red bezel, socket and instructions £2.50, 10 for £22.50, 100 for £200.00.

I.C. Audio Power by TOSHIBA 35 WATT module. 8 ohms o/p 200mV into 47K for full output. 0.3% distortion (max) 60V power supply required. £8.50, 10 for £75.

10.7MHz crystal filters. Size 35x25x20mm. 25KHz band width for NBFM £7. 10 for £60.

TEXAS 4 + 5 Digit C. Cathode Display with 16 pin DIL Base. 0.2" digits. Pair £1.50. 10 pairs £12.50. 100 pairs £100.

2 1/2" 40 ohm speaker 250 M.Watt - Ideal for that small space. 75p. 10 for £6. 100 for £50.

3 DIGIT 7 SEGMENT DISPLAYS. C cathode pack of 2 with data segments are missing) 60p each. TBA 120A 75p. 10 for £7. 100 for £55. TBA 120S. 75p. 10 for £7. 100 for £55.

SOLDER at half price. 5 packs of 2 metres 18 gauge Servisol £1.20. 20 packs £10.

JOYSTICK CONTROLS. (Ideal for TV Games, model control), sturdily constructed compact controls giving full 360° movement and control. Each unit fitted 4-off 100K linear controls. Pair £5.00.

AVO meter movements for a military version of the Avo 8. Precision 37.5 micro Amp (50µA with Integral shunt) movement. Electronic voltmeter circuit available on request. £8.50.

28 pin calendar/clock chip type MK501 78B common cathode LED display (with circuit). £4.49.

INDUSTRIAL RELAYS

By I.M.O. OMRON
 At less than Distributor prices

	Prices	Prices	£ p
	ea.	10	100+
60 43 24V DC			
2-Pole Open	£1.10	£9.00	£85.00
60 13 48V AC			
Octal Plug in type enclosed	£1.20	£10.00	£90.00
60 02 12V AC			
2-Pole C. Over Octal Enclosed type	85p	£7.50	£65.00

All Relays are 250V 6 Amp AC Current Rating

PACKS ALL NEW TESTED GUARANTEED

	Pack	Ten Packs	Hundred Packs
10-8C171A Plastic 8C107 type	75p	£6	£50
TTL 8-Gates 7420, 7430, 7451	80p	£5	£40
TTL 6-Gates and Complex Mixed	75p	£6	£50
15 1/2 Watt Zeners 3.9-91 volt mixed	89p	£7.50	£65
10-10 watt Zeners mixed voltages	95p	£8.50	£75
10-40 M/W Zeners 3.3-33 volts	65p	£5.50	£45
50 Germanium & Silicon Diodes	55p	£5	£40
25 Mixed Transistors	55p	£5	£40

5012 12 digit calculator chip. 4 functions with circuits and data. £2.50.

VITALITY 12V 0.15 amp. MES Bulbs. 100 for £5. 1,000 for £40.

BECKMAN 500KHZ triggerable clocking oscillator for use with calculator chips. 25x10x12mm £1. 10 for £8. 100 for £65.

Resettable thermostatic switch. A pushbutton on/off switch which automatically drops out when the ambient temperature exceeds 72°C 47x29x46mm 75p. 10 for £6.50.

FT243 crystal packs. 10 crystals of mixed frequencies between 5800 and 8500 KHz. (Our choice of frequencies). Ideal for re-grinding. £1.50 per pack, 10 packs £10, 100 packs £85.

Ditto. 10X packs of 10 crystals. 250 kc/s-50 mc/s. £1 pack. 12 packs £10. 100 packs £70.

Calculator chip CT5002 12 digit four functions for common cathode multiplex displays. ONLY £1.95 complete with circuit.

1 MHz HCGU quartz crystal £3. Frequency meters, clocks, frequency references. 17 x 19 x 7mm £3.

TAPE HEADS 1/4 track. Record Marriot XRP536 £5. XES11 erase £1.25. XRP518 £3.50.

MULLARD TUNER MODULES with data LP1171 combined AM/FM IF strip - £4. LP1179 FM front end with AM tuning gang, used with LP1171 - £4. LP1171 and 79 pair - £6.50. LP1157 complete AM strip - £2.05. Ferrite Aerial - 95p

MINIATURE ORP12 (Equivalent - RPY30). 2 for £1.

SEVEN DIGIT MINIATURE COUNTER by Durant 12.24 volts D.C. 3 Watts. Size 40x25x55L mm £1 each. 10 for £9. 100 for £80.

QUARTZ

32.768 KHz (Motorola)	£4.50
32.768 KHz (Equivalent)	£2.95
60 KHz	£4.50
100.0 KHz	£3.62
200.0 KHz	£3.92
204.8 KHz	£3.92
262.144 KHz	£3.62
307.2 KHz	£3.62
312.5 KHz	

microfile.....

Gary Evans has been going round in circles this month in search of more MPU news items.

THIS WORLD IS full of vicious things, circles and dogs spring immediately to mind. I've had experience of both, the latter in the bundle of fluff that's the nearest I get to a pet and of the former, it seems, in everything I do. At any rate it's an example of the former that I'd like to dwell upon for a moment.

The situation concerns anyone considering the development of a microprocessor based control system. As a first step in any such development program, our likely lad will look around at the various development systems, that most of the major manufacturers produce, to help potential micro users to get to grips with their particular processor.

When It's All Assembled

Having chosen one of the various kits he can now get down to the real business of developing the control algorithms and, finally, the machine code that will drive the completed implementation of his system. That's if all goes well. Many of the basic development kits come supplied with a monitor that can only be described as rudimentary, allowing only a simple memory examine/modify type instructions. The development of any routine over a few hundred bytes with such a system has been known to drive many a hardened engineer to throw down his soldering iron and go for some knitting needles.

Fear not we say to our, by now, disheartened fellow, for we can provide you with an assembler. From now on you will not have to wrestle with machine code, but can deal with mnemonics which at least makes the task of coding much easier, and if you're lucky your assembler will also take care of a few labels in our program. At this point though, our man hears of a marvellous thing called an interpreter, whereby he can program his system in a high level language that is, by all accounts, far easier to pick up than either machine or assembly code. As time is money and personnel with experience in machine/assembly programming are difficult to come by, the choice seems to lie with a BASIC INTERPRETER. We know the final system will operate slower than a machine language program, but it will be fast enough for most applications.

All is well, the final program is soon written and debugged and the time has come to dump the object code into the PROM that will reside in the final hardware configuration. It's here that we observe the beginnings of our vicious circle (you were starting to wonder weren't you).

Things Looking Up?

The crunch comes when we realise that an interpreter does not in fact produce any object code, instead,

looking at a string of stored instructions line by line, it consults a lookup table within the interpreter which then directs the micro to another area of the interpreter's ROM where the routines to carry out the required instructions are located. It is important to note that this takes place on a line by line basis and at no stage is anything that remotely resembles an object code generated. Thus our poor chap has his BASIC program ready to go, but to run it on any system he will require not only to dump the program itself to ROM but also the entire BASIC interpreter. To add insult to injury, most BASICs require a fair sized stack which will also have to be provided.

So attractive as it may seem in terms of development time an interpreter supporting a high level language is no way to undertake software development in most control systems applications. So it's back to the assembler, or, if you feel like withdrawing from life for a while, machine code.

Heard The One About

Now for a few quick news items

A new addition to the ranks of places offering micro systems, along with the advice necessary to help choose between the many products around, is the Byte Shop at 426/428 Cranbrook Road, Gants Hill, Ilford, Essex. IG2 6HW. Sounds like an offshoot of the American Byte Shop chain, a franchise operation that has been going in the States for some time now. A SAE to the Byte Shop at the above address should get you details of their product range.

This issue of ETI goes to press on the eve of the DIY Computer show and a report of this event, which follows the successful show held last year, will appear in next month's Microfile. I do hear however that another computer magazine is to be launched at the show. The title I've heard is Practical Computing, but by the time you read this the thing may be on the news stands. I look forward to reading the first issue with interest.

Chip Off The Old

You may recall my mentioning the 8048 single chip MPU from Intel a while back. Well no sooner was that in print than a new product information sheet landed on my desk describing the latest addition to the Intel stable. The 8022 is a derivative of the 8048 being a single chip MPU, but with the important plus of having two on board A-D converters. Add to this an eight bit input port with variable threshold (just right for decoding touch keyboards) and the usual complement of 28 I/O lines and onboard memory and you have a product that should find its way into more products than I care to think of over the next year or so.

DISCO RANDOM LIGHT UNITS

-SPECIAL OFFER-



-LIMITED SUPPLY-

These units are ideal for a Disco, Group or home party. The lamps are never off, each one is dimmed for a second and then back to full brightness.

500mm long, designed for 3 x 100W lamps (not included), complete with 2 metres of cable and 12 months guarantee. Fully suppressed, all electronic (not bi-metal).

£6.25 each + 75p Post or
TWO for £12.50 post free

Send now to:

M. D. MARKETING
P.O. Box 4, Hinckley, Leics.

Reg. office 22 Station Road, Hinckley

NASCOM 1 Microcomputer for the Hobbyist

THE ONLY COMPLETE MICROCOMPUTER AVAILABLE TO THE HOME CONSTRUCTOR

FEATURES:

- ★ Supplied in Kit Form for Self-Assembly
- ★ Full documentation supplied
- ★ Includes Printed Circuit Board
- ★ Full Keyboard included
- ★ Interfaces to Keyboard, Cassette Recorder & T.V.
- ★ 2K x 8 RAM
- ★ 1K x 8 Eprom Monitor Program
- ★ Powerful Z80 CPU, Mostek
- ★ 16 line x 48 Character Display Interface to standard, unmodified T.V. set
- ★ On board expansion to 2K x 8 Eprom
- ★ On Board Expansion Facility for Additional 16 Lines I/O
- ★ Total expansion to 256 Input Ports and 256 Output Ports

SOFTWARE FEATURES:

- ★ 1K x 8 Nasbug Program in Eprom
- ★ Provides 8 Basic Operator Commands including single step
- ★ Expandable Software System via additional user Programs in Ram of Eprom

Manuals Separately
£3.50

Complete Kits
NOW IN STOCK

£197.50
+VAT 8%
POST £2 50

Sole Appointed
London
Stockists

After sales service available

HENRY'S
RADIO

All mail to: Henry's Radio 404 Edgware Rd, London W2

LONDON W2: 404 6 Edgware Road. Tel: 01-723 1008

7400 TTL	7497	2.38	74196	.90	74LS153	.50	4024	.66	4516	1.02	400mW ZENER	80133	.50	TP418	.70	2M4058	.12	ELECTROLYTICS
7401	74100	.94	74197	.90	74LS154	1.20	4025	.15	4518	1.89	DIODES	80135	.44	TP41C	.80	2M4062	.12	uf 16r 25v .0v .63v
7402	74104	.40	74198	1.48	74LS155	.86	4026	1.28	4519	.50	2.7V-33V .09 each	80139	.46	TP42A	.72	2M4124	.16	1 .045 .05 .055 .06
7403	74105	.40	74199	1.48	74LS156	.86	4027	.50	4520	1.05	.80 hr 10: 3.50 for	80140	.48	TP42B	.78	2M4126	.16	2.2 .045 .05 .055 .06
7404	74107	.28	74221	1.50	74LS157	.47	4028	.87	4521	2.00	50: 6.50 for 100	80189	.80	TP42C	.86	2M5133	.16	3.3 .045 .05 .055 .06
7405	74109	.45	74273	2.15	74LS158	.53	4029	.86	4522	1.35	(any mix)	8F241	.25	TP3055	.50	2M5136	.16	4.7 .045 .05 .055 .06
7406	74110	.46	74274	1.25	74LS160	1.22	4030	.40	4527	1.60	S.C.R.'s	8F258	.24	TR543	.22	2M5142	.18	6.8 .05 .055 .06 .07
7407	74111	.70	74283	1.70	74LS161	.89	4031	2.34	4528	.92	1Amp 200V .30	8F334	.85	ZTX107	.10	2M5148	.28	10 .05 .06 .07 .09
7408	74118	1.80	74284	6.85	74LS162	1.22	4033	1.25	4529	1.10	4Amp 200V .40	8F385	.23	ZTX304	.20	2M5153	.16	2.2 .06 .07 .08 .10
7409	74119	1.80	74285	6.85	74LS163	.89	4034	2.00	4536	3.56	7Amp 100V .50	8F386	.22	ZTX450	.20	2M5156	.16	3.3 .06 .07 .08 .10
7409B	74119	1.30	74298	1.85	74LS164	1.20	4035	1.00	4553	4.20	7Amp 100V .50	8F388	.22	ZTX502	.20	2M5158	.16	6.8 .09 .12 .16 .23
7410	74120	.82	74390	1.82	74LS168	2.00	4036	2.40	4555	.85	10Amp 200V .60	8F389	.20	ZTX504	.20	2M5162	.18	100 .10 .13 .18 .26
7411	74121	.25	74393	2.12	74LS169	2.00	4037	.99	4556	.85	16Amp 100V .75	8F391	.18	TR550	.20	2M5164	.16	150 .11 .15 .20 .28
7412	74122	.40			74LS170	1.76	4038	1.00	4558	1.25		8F392	.18	TR552	.20	2M5166	.16	2.2 .06 .07 .08 .10
7413	74123	.55			74LS173	1.95	4039	2.80	4566	1.40		8F394	.18	TR553	.20	2M5168	.16	6.8 .05 .055 .06 .07
7414	74125	.44	74LS00	.19	74LS174	1.12	4040	.88	4568	.75		8F395	.18	TR554	.20	2M5170	.16	10 .05 .06 .07 .09
7415	74126	.45	74LS01	.19	74LS175	1.05	4041	.77	4585	1.03		8F396	.18	TR555	.20	2M5172	.16	2.2 .06 .07 .08 .10
7416	74128	.62	74LS02	.19	74LS180	2.85	4042	.40	4587	.75		8F397	.18	TR556	.20	2M5174	.16	3.3 .06 .07 .08 .10
7417	74132	.68	74LS03	.19	74LS189	.81	4043	.82	4588	.75		8F398	.18	TR557	.20	2M5176	.16	6.8 .09 .12 .16 .23
7420	74135	.68	74LS04	.20	74LS191	.81	4044	.82	4589	.75		8F399	.18	TR558	.20	2M5178	.16	100 .10 .13 .18 .26
7421	74136	.75	74LS05	.20	74LS192	1.80	4045	1.40	4590	1.40		8F400	.18	TR559	.20	2M5180	.16	2.2 .06 .07 .08 .10
7422	74137	.94	74LS08	.19	74LS193	1.80	4046	1.32	4591	1.40		8F401	.18	TR560	.20	2M5182	.16	6.8 .05 .055 .06 .07
7423	74141	.58	74LS09	.19	74LS195	1.12	4047	.96	4592	.75		8F402	.18	TR561	.20	2M5184	.16	10 .05 .06 .07 .09
7425	74142	2.00	74LS10	.19	74LS196	1.20	4048	.88	4593	.75		8F403	.18	TR562	.20	2M5186	.16	2.2 .06 .07 .08 .10
7426	74143	2.00	74LS11	.19	74LS197	1.20	4049	.42	4594	.75		8F404	.18	TR563	.20	2M5188	.16	6.8 .09 .12 .16 .23
7427	74144	2.00	74LS12	.19	74LS221	1.12	4050	.42	4595	.75		8F405	.18	TR564	.20	2M5190	.16	100 .10 .13 .18 .26
7428	74145	.84	74LS13	.46	74LS247	.97	4051	.84	4596	.75		8F406	.18	TR565	.20	2M5192	.16	2.2 .06 .07 .08 .10
7430	74147	1.30	74LS14	1.10	74LS248	.97	4052	.84	4597	.75		8F407	.18	TR566	.20	2M5194	.16	6.8 .05 .055 .06 .07
7430B	74148	1.18	74LS15	.19	74LS249	.97	4053	.84	4598	.75		8F408	.18	TR567	.20	2M5196	.16	10 .05 .06 .07 .09
7432	74150	.99	74LS20	.19	74LS251	1.00	4054	1.10	4599	.75		8F409	.18	TR568	.20	2M5198	.16	2.2 .06 .07 .08 .10
7433	74151	.99	74LS21	.19	74LS253	1.05	4055	1.00	4600	.75		8F410	.18	TR569	.20	2M5200	.16	6.8 .09 .12 .16 .23
7434	74152	.99	74LS22	.19	74LS257	1.05	4056	.98	4601	.75		8F411	.18	TR570	.20	2M5202	.16	100 .10 .13 .18 .26
7436	74154	1.05	74LS25	.24	74LS258	1.05	4057	1.40	4602	.75		8F412	.18	TR571	.20	2M5204	.16	2.2 .06 .07 .08 .10
7438	74155	.83	74LS27	.40	74LS266	.99	4057	3.50	4603	.75		8F413	.18	TR572	.20	2M5206	.16	6.8 .05 .055 .06 .07
7441	74156	.63	74LS30	.19	74LS273	2.50	4058	2.4	4604	.75		8F414	.18	TR573	.20	2M5208	.16	10 .05 .06 .07 .09
7442	74157	.63	74LS32	.25	74LS279	.50	4059	.76	4605	.75		8F415	.18	TR574	.20	2M5210	.16	2.2 .06 .07 .08 .10
7443	74159	1.70	74LS37	.27	74LS283	1.00	4070	.17	4606	.75		8F416	.18	TR575	.20	2M5212	.16	6.8 .09 .12 .16 .23
7444	74160	.80	74LS38	.27	74LS289	2.85	4071	.17	4607	.75		8F417	.18	TR576	.20	2M5214	.16	100 .10 .13 .18 .26
7445	74161	.80	74LS40	.19	74LS293	.90	4072	.17	4608	.75		8F418	.18	TR577	.20	2M5216	.16	2.2 .06 .07 .08 .10
7446	74162	.80	74LS42	.53	74LS298	1.60	4073	.17	4609	.75		8F419	.18	TR578	.20	2M5218	.16	6.8 .05 .055 .06 .07
7447A	74163	.80	74LS47	.97	74LS352	.92	4075	.17	4610	.75		8F420	.18	TR579	.20	2M5220	.16	10 .05 .06 .07 .09
7448	74164	.89	74LS48	.97	74LS353	1.05	4076	1.05	4611	.75		8F421	.18	TR580	.20	2M5222	.16	2.2 .06 .07 .08 .10
7450	74165	.89	74LS49	.97	74LS365	.50	4077	.46	4612	.75		8F422	.18	TR581	.20	2M5224	.16	6.8 .09 .12 .16 .23
7451	74166	.99	74LS51	.19	74LS366	.50	4078	.22	4613	.75		8F423	.18	TR582	.20	2M5226	.16	100 .10 .13 .18 .26
7453	74167	2.70	74LS54	.57	74LS367	.50	4081	.22	4614	.75		8F424	.18	TR583	.20	2M5228	.16	2.2 .06 .07 .08 .10
7454	74170	1.60	74LS55	.20	74LS368	.50	4082	.20	4615	.75		8F425	.18	TR584	.20	2M5230	.16	6.8 .05 .055 .06 .07
7460	74172	1.00	74LS73	.30	74LS369	.37	4085	.76	4616	.75		8F426	.18	TR585	.20	2M5232	.16	10 .05 .06 .07 .09
7470	74173	4.18	74LS74	.34	74LS370	2.00	4086	.76	4617	.75		8F427	.18	TR586	.20	2M5234	.16	2.2 .06 .07 .08 .10
7472	74174	.89	74LS75	.45			4089	1.55	4618	.75		8F428	.18	TR587	.20	2M5236	.16	6.8 .09 .12 .16 .23
7473	74175	.68	74LS76	.32			4090	.85	4619	.75		8F429	.18	TR588	.20	2M5238	.16	100 .10 .13 .18 .26
7474	74175A	4.70	74LS76	.32			4091	1.10	4620	.75		8F430	.18	TR589	.20	2M5240	.16	2.2 .06 .07 .08 .10
74S74	74176	.88	74LS83	.78			4092	.16	4621	.75		8F431	.18	TR590	.20	2M5242	.16	6.8 .05 .055 .06 .07
7475	74177	.88	74LS85	.90			4096	.92	4622	.75		8F432	.18	TR591	.20	2M5244	.16	10 .05 .06 .07 .09
7476	74178	1.20	74LS86	.35			4097	.16	4623	.75		8F433	.18	TR592	.20	2M5246	.16	2.2 .06 .07 .08 .10
7480	74179	1.10	74LS89	.95			4098	.92	4624	.75		8F434	.18	TR593	.20</			

JAYEN

FG-1



BUILD THIS ADVANCED DESIGN FUNCTION GENERATOR

- ★ Designed around 8038 Waveform Generator I.C.
- ★ DC Coupled Amplifier
- ★ 1 Hz to 100 kHz
- ★ Sine, Triangle and Square Wave output

JAYEN Developments, 25 Westgate, Louth Lincs LN11 9YD

Please send a JAYEN FG-1 PC board complete with instructions, photo anodised Front Panel and Component Shopping List at £3.85 incl VAT and P&P

Name _____

Address _____

MEMORIES

21L02 (450ns) (1K x 1 Static RAM)	£1.07
4027 (250ns) (4K x 1, 16 pin, Dynamic RAM)	£2.02
2107 (4K x 1, 22 pin, Dynamic RAM)	£3.83
4116 (16K x 1, Dynamic RAM)	£20.25
2708 1K x 8 UVEPROM)	£7.87
8080A (CPU)	£7.45
81LS95 (Buffer TriS)	75p
81LS96 (Buffer TriS)	75p

All VAT inclusive
35p for p&p orders under £5
Please write for discounts
over 100 pieces

(Mail Order only)

LOTUS SOUND

4 MORGAN STREET
LONDON E3 5AB

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4½in **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90 and 130 (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals ½in kit or ¼in kit. **£1** complete. State size.

All orders dispatched promptly
All post and VAT paid
Ex U.K. add 50p for air mail
Shop and Trade enquiries welcome
Special Transfers made to order

**E. R. NICHOLLS
P.C.B. TRANSFERS
DEPT. ET1/8
46 LOWFIELD ROAD
STOCKPORT, CHES.061-480 2179**

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
6 3V 1 5A £2.45; 3A £2.85; 6A CT £5.30; 12V 1 5A £2.85; 3A CT £5.30; 6A CT £6.85; 18V 1 5A CT £5.30; 24V 1 5A CT £5.30; 3A CT £6.85; 5A CT £7.30; 20V 1 5A + 20V 1 5A £7.30; 40V 3A CT £9.75; 50V 6A £27.00

TWIN SEC TRANSFORMERS: Prim 240V ac.
6V 0 6A + 6V 0 6A, 9V 0 4A + 9V 0 4A, 12V 0 25A + 12V 0 25A, 20V 0 15A + 20V 0 15A, all at £3.25 each, 15V 0 75A + 15V 0 75A £4.85; 15V 1 5A + 15V 1 5A £6.85; 18V 1A + 18V 1A £8.10; 18V 1 5A + 18V 1 5A £7.30; 20V 1 5A + 20V 1 5A £7.30; 12V 4A + 12V 4A £8.10; 25V 2A + 25V 2A £8.10

MIDGET RECTIFIER TRANSFORMERS: 240V ac.
6-0-6V 1 5A or 9-0-9V 1A £2.45 each, 12-0-12V 1A or 20-0-20V 0 75A £2.95 each, 9-0-9V 0 3A or 12-0-12V 0 25A or 20-0-20V 0 15A £2.95 each

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
0-10-12-14-16-18V 2A £4.85; 4A £6.50; 0-12-15-20-24-30V 2A £5.85; 4A £8.90; 0-5-20-30-60V 1A £6.75; 2A £9.75; 0-40-50-60-80-100-110V 1A £9.70

MAINS TRANSFORMERS SPECIAL OFFER: Prim 240V ac.
250-0-250V 60Ma 6 3V 1A £1.50; 250V 100Ma 6 3V 2A £2; 9V 3A £2; 23V 0 5A £1.25; 20W Auto 110/240V £1.75

SPEAKER AUTO MATCHING TRANSFORMERS
12W, 3 to 8 or 15 up or down £2.50.

LOUDSPEAKERS
38 or 45mm or 2¼in 8Ω, 8 or 25Ω, 2¼in 8 or 80Ω, 3in 35Ω, 3¼in 3 16 or 80Ω all at £1.10 each 5 x 3in 3, 8, 15 or 25Ω £1.25; 7 x 4in 3, 8, 16, 25 or 80Ω, £1.75. 8 x 5in 4, 8 or 25Ω £2.50; 8in 8Ω, £2.50

"INSTANT" BULK CASSETTE/TAPE ERASER
Instant erasure of cassettes and tape spools, any diameter, demagnetises tape heads, 200/240V ac £5.50.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.
New, British manufacture smoothed d.c. output 20V 1 5A plus stabilised output of 15V 100ma, plus 12V ac 0 5A output, complete with diagram £3.30.

CONDENSERS
Electrolytic 1000/50V 30p; 2000/30V 30p; 1200/75V 50p; 3900/100V £1.25; paper tubular W/E 0 47/600V, 2 2/250V, 4 7/160V all at 25p each, £15 per 100

EDGEWISE LEVEL METER FSD 200 μA
Size 19 x 18 x 20mm 800Ω, £1.10.

SYNCHRONOUS GEARED MOTORS, 240A ac.
Brand new built in gearbox, 1, 6, 8 or 20 RPH, all at £1.20 each, O/P TRANSFORMERS FOR VALVE POWER AMPLIFIERS P.P. sec tapped 3-8-15, A-A 6K 30W £11.50; A-A 3K 50W £17.00; 100W (EL34 KT88 etc) £22.00.

E.C.C. MANUAL OF POWER AMPLIFIERS
Covers valve amplifiers 30W to 400W 75p.

MULTI WAY CABLE, SCREENED PVC COVERED
36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; fig 8 stereo 15p per metre, 4 way individually screened 25p per metre, 4 way unscreened mains 30p per metre

TWIN FIG 8 CABLE
Polarsed, 100 metre £4.50.

MINI 3 CORE CIRCULAR CABLE, 19 x .10mm
Ideal for speakers intercoms telephones etc £4.50 100m

ALL PRICES INCLUDE V.A.T. CARRIAGE EXTRA ON ALL ORDERS

Callers by appointment only
S.A.E. enquiries, lists
46 Kenilworth Road, Edgware, Middx HA8 8YG
Tel: 01-958 9314

Save on Calculators

TEXAS	
T1504Q (print display, 10 digits mem printing calc)	£72.00
PC100B (Print Cradle for TI prog. calculators)	£174.12
SR51-3 (10 mems 8 + 2, 32 prog steps)	£33.48
T157 (Key Prog. 150 Prog. steps, 8 Mem)	£32.35
T158 (480 Prog. steps/60 mem)	£79.32
T159 (960 Prog. steps/100 mem)	POA
Software for T159 & 58 (each) (four available)	£25.40
TI Programmer (Hex to Oct conversions)	£49.95
Little Professor (child's calculator)	£10.80
CASIO	
FX2200 (6 + 2, scientific/fraction, LCD, 1000 hours)	£19.95
FX120 (10 dig. full sci + 6 brkts + Polar/rect coordinates)	£19.95
FX39 (6 + 2 otherwise as FX140)	£15.50
ST-1 (4-way Stopwatch function & %)	£24.95
MQ5 (L.C.D. Clock, two Alarms, Calendar, Calc.)	£34.95
AQ1000 (L.C.D. Calc., Timer Clock, Alarm, 1 year bat.)	£19.90
HEWLETT PACKARD	
H.P.31E at £37, H.P.33E (supercedes HP2A)	£64.00
H.P.22 Business/Management Calculator. Low Price	POA
H.P.25C (Continuous memory programmable scientific)	£106.95
H.P.29C (new combo H.P.27 + H.P.25C)	£123.83
H.P.67 £287.04, H.P.97	£474.05
CBM	
4130R (90 functions 10 + 2)	£27.54
PRO100 (8 + 2 key prog. 72 steps, 10 memories)	£30.45
M55 (Maths) S61 (Stats) N 60 (Navigator)	£58.32
LCSK1 (L.C.D., 5.000hr bat life)	£10.80
Sinclair Programmable Calculator	£13.44
A.C. Adaptor £3.00 Program Library	£4.82
SHARP EL8130, LCD musical calc. — great, no keys	£18.80
CT550 L.C.D. Clock Calc. 24 time zones (Alarm)	£44.00
ROCKWELL 44RD (5 + 2) (Scientific)	£13.90
Master Chess Challenger (60,000 moves)	£124.95
Gammon Master II (Computer backgammon). Low price	POA
Computer Checkers (Drafts)	POA
CBM Pot 2001 (8K) (Company orders only)	£695

WE SUPPLY ALL SEIKO WATCHES
Also available L.C.D./Alarm watches

THE SINCLAIR PDM35 digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

D.C. VOLTS 1mv-1000v (1% - 1 count) 10mΩ input.

A.C. VOLTS 1v-500v 40Hz-5kHz (1% + 2 counts).

D.C. CURRENT 1inA-200mA (1% count)

RESISTANCE 1Ω-20mΩ (1% + 1 count)

£28.80-£29.85



purchase order both inc. VAT and P&P

A.C. Mains adaptor £3.20
deluxe padded carrying case £3.20
30kV probe £18.64

THE SINCLAIR MICROVISION



The amazing pocket T.V. that will pick up programs throughout the world, complete with rechargeable batteries.

£196 inc. V.A.T.

Sae (for detailed Brochure ex-stock)

SINCLAIR DM235



Portable 3½ digit 6 function Multimeter

DC volts 1mV to 1000V

AC volts 1mV to 750V

AC & DC current 1μA to 1A

Resistance 1Ω to 20MΩ

Diode test 0.1μA to 1mA

10mΩ input, DC acc. 1.0% AC acc. 1.5% 30Hz-10kHz

£52.80 inc VAT

CASIO AQ1000



LCD Watch / Stopwatch

Calculator and Alarm

Time hours, mins, secs, am/pm

Stopwatch u/s to 9 hrs, 59 mins, 59 secs

Alarm sounds at the preset time everyday till cleared

Calculator four functions including constants, memory calculations, %

£19.90 inc VAT

MODEL MCC-8

LCD Chronograph with adjustable bracelet. 8-functions hours, minutes, seconds, month, date, day, stopwatch, lap time and total elapsed time. Stopwatch timing shown in minutes, seconds, tenths and hundredths of seconds. Pushbutton backlight.

We accept govt./company purchase orders on all goods

KRAMER & CO

9 October Place, Holders Hill Road, London NW14 1EJ.
Telex: 888941. ATTN. KRAMER, K7. Tel. 01-203 2473
MAIL ORDER ONLY. S.A.E. for data sheets
Export enquiries welcome
Telephone and Telex orders accepted

electronics tomorrow.....

by John Miller-Kirkpatrick,

AS YOU SWELTER in the sun this Summer (?) think forward to Christmas 1978 and the never ending task of trying to think of new and original presents for Aunt Mavis and Uncle Eric. If you think that you have problems spare a thought for the manufacturers of gimic presents who have the problem this year of what form to present an electronic goody. Should they come up with a super calculator which calculates, tells the time and date in all 24 time zones, checks your pulse and biorhythm, etc. etc. — bit old hat really! What about a new gadget for the kitchen which slices cucumber, carrots, potatoes, picks up crumbs and nails and checks your pulse and biorhythm?

Auto-focus for cameras and . . . ?

Electronic cameras have been with us for some years with automatic light sensors, shutter timers, etc. The latest development is a self-focusing device which is now being fitted to some cameras, the device is from Honeywell and goes under the name of Visitronic. The type of rangefinder or auto-focuser fitted to some cameras at present is based on two mirrors, one fixed and one

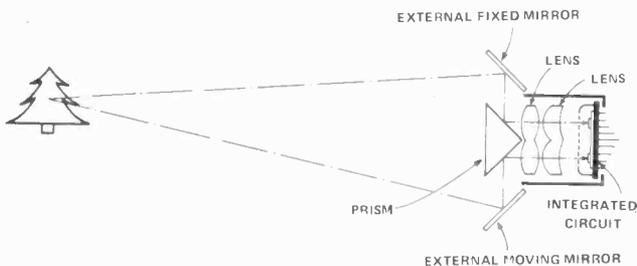


Fig. 1. External arrangement of mirrors for the Visitronic.

moveable, which reflect the images onto the viewfinder. Adjusting the focus screw moves one of the mirrors until the images reflected from the two mirrors become a single image and at this point the image is assumed to be in focus. A similar system is used in the Visitronic except that the images are reflected onto the surface of an IC with two photosensor arrays, one at each end of the IC. As the mirror is moved the images presented at the two photo arrays are compared and a signal is produced which is relative to the comparative matches in the two arrays with a peak at the best match. The movement of



Fig. 2. The Visitronic module, with prism, two lenses and linear IC chips.

the mirror is linked to the focussing ring of the camera and thus is capable of continuously adjusting the focus of the camera so that it is centred on the most obvious subject in view. The speed at which this happens is fast enough to operate during the time that the shutter is open for a still camera and thus is capable of 'instant' focus for cine or TV cameras.

The whole unit is packaged in a TO-8 can with a sophisticated plastic over which also incorporates two plastic lenses and a prism to transmit the light from the external mirrors onto the photo arrays, the mirrors, mirror motor, and controls are not included. The actual chip measures 100 x 250 mils and contains sensors, amplifiers, voltage regulator, reference voltage, peak detector and output driver. The photosensor arrays are each broken down into four parallel sensors on each side of the chip, the use of four sensors in each array increases the sensitivity of the device and allow for more accurate calculation of the best image match.

Eye Technology

Applications of the Visitronic are not limited to use in cameras. Your average run of the mill Robot uses light or ultrasonics to find its way around obstacles, it might now be possible to use one or more Visitronic devices to give the Robot something approaching the concept of an eye. With an MPU backing up the Visitronic it may be possible to differentiate between similar objects of different sizes, different textures or colours. This might well be a beginning to the answer to one Robot problem which has always fascinated me — unless you know different. If you show a young child a picture of a male lion standing under a tree the child has no difficulty in relating this to your own small tabby kitten and will not mistake it for a dog. The Robot can be persuaded to recognise the picture of the lion and can inform you that it is the picture of the lion, and can inform you that it is the picture you have told it is called lion on any subsequent showing of the picture. If your kitten wanders into the viewing range of the Robot it will not recognise it at all unless the kitten decides to strike up a pose similar to that of the lion under the nearest hat stand. Is the problem of recognising a pattern from a different angle, size, colour, etc really that difficult?

SERVICE TRADING CO

WHY PAY MORE?!

MULTI RANGEMETER Type MF15A. A.C./D.C. volts. 10, 50, 250, 500, 1000. Ma 0.5, 0.10, 0.100. Sensitivity 2000V. 24 ranges, dimensions 133 x 93 x 46mm. Price £6.50 plus 50p P&P (£7.56 inc. VAT & P).



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 p.w. Glass passivated plastic triac. Swiss precision product for long term reliability. £1.25 P&P 10p (£1.46 inc. VAT & P) (inclusive of date and application sheet). Suitable Diac 22p.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC. Contacts (no dial) £1.50. P&P 30p (£1.94 inc. VAT & P).

MERCURY SWITCH

Size 27mm x 5mm. 10 for £5.00 (inc. VAT £5.72) Min quantity 10




230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with 5 blade 6 1/2" aluminium fan. New reduced price £3.00 P&P 65p (£3.94 inc. VAT & P)



21-WAY SELECTOR SWITCH with reset coil

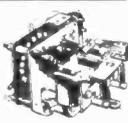The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil 230/240v. A.C. operation. Unit is mounted on strong chassis. Complete with cover. Price £5.50 P&P 75p (£6.75 inc. VAT & P).



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced to fully enclosed 9" rotor with max. air delivery of 1.5 cubic metres per min. Max static pressure 600mm WG. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115v a.c. motor mounted on alloy base with fixing facilities. Dimensions Length 22cm x width 25cm x height 25cm.



These units are re-equipment but have had minimum use. Fully tested prior to despatch. Price £12 + £1.50 P&P (£14.58 inc. VAT & P). Suitable transformer for 230/240v a.c. £6 + £1 P&P (£7.56 inc. VAT & P).

CENTRIFUGAL BLOWER

Smith type FFB 1606 022 220/240v. A.C. Aperture 104/102mm overall size 16x14cm. Price £3.75 p&P 75p (inc. VAT £4.86). Other types available phone for details.



CROUZET 230V A.C.

2 R.P.M. synchronous motor, brand new £2.90, p&p 30p (£3.46 inc. VAT)

NI-CAD BATTERY

35 AH 1.2v Metal	Height (mm)	Width (mm)	Length (mm)
	219	75	29

£7.50 + P.P. 50p (£8.64) inc. V.A.T

MINIATURE UNISELECTOR

12v 11 way 4 bank (3 non-bridging, 1 homing) £2.50 P&P 35p (£3.08 inc. VAT & P)



BIG INCH

Tiny precision built 3 rpm USA motor size only 1 x 1 1/4 inch AC op. supplied with resistor for 230 volt AC price £2.37 p&p 20p 4 for £5.40 post paid. New Manufacturer's Surplus.




MICRO SWITCHES

Sub min lever m/switch type MML46 10 for £2.50. Type 3 115M 906T 10 for £2.50 post paid (£2.70 inc. VAT & P). BP lever operated 20a c/o. mfg by Unimax USA. 10 for £4.00 plus 50p P&P (min. order 10) (£4.86 inc. VAT & P). D.P. C/O lever m/switch. mfg by Cherry Co., USA. Precious metal. low resistance contacts. 10 for £2.50. P&P 30p. Total inc. VAT £3.02 (min 10). New Manufacturer's Surplus.



NEW HEAVY DUTY SOLENOID

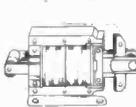Mfg. by Magnetic Devices. 240v A.C. Operation approx. 10lb. pull at 1.25. Price £4.00 P&P 80p (£4.96 inc. VAT)



24 VOLT D.C. SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb. pull at 1 in travel. 2 solenoids of approx. 1 lb. pull at 1/2 in travel. 8 solenoids of approx. 4 oz. pull at 1/2 in travel. Plus 1 24V D.C. 1 heavy duty 1 make relay. Price £3.00 Post £1.00 (£4.32 inc. VAT & P)



240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made British mfg. PRICE £3.50 Post 50p (£4.32 inc. VAT & P)



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260v. A.C.



Carriage extra

BRAND NEW. All types.
200W (1 Amp) fitted A/C
volt meter £14.50
0.5 KVA (Max. 2 1/2 Amp) £17.00
1 KVA (Max. 5 Amp) £22.50
2 KVA (Max. 10 Amp) £37.00
3 KVA (Max. 15 Amp) £45.50
4 KVA (Max. 20 Amp) £70.00

LT TRANSFORMERS

0-10.15v at 3 amp (ex new equl) £2.50 P&P 50p (£3.24 inc. VAT)
13-0-13v at 1 amp £2.50 P&P 50p (£3.24 inc. VAT)
25-0-25v at 2 1/2 amp £4.50 P&P 75p (£5.67 inc. VAT & P)
0.4v/6v/24v/32v at 12 amp £15.00 P&P £1.50 (£17.82 inc. VAT & P)
0.6v/12v at 20 amp £13.50 P&P £1.50 (£15.20 inc. VAT & P)
0-12v at 20 amp or 0-24v at 10 amp £12.00 P&P £1.50 (£14.58 inc. VAT & P)
0.6v/12v at 10 amp £8.25 P&P £1.25 (£10.26 inc. VAT & P)
0.6v/12v/17v/18v/20v at 20 amp £16.50 P&P £1.50 (£19.44 inc. VAT & P)
0.10v/17v/18v at 10 amp £10.00 P&P £1.40 (inc. VAT £12.31)
0.6v/12v at 20 amp £11.85 P&P £1.00 (£13.88 inc. VAT & P)
Other types in stock, phone for enquiries or send see for leaflet.

COMPRESSOR, precision built by Emerson USA.

Horizontally opposed twin head diaphragm type producing 20lts. Plus P.S.I. per head 3.5 plus C.F.M. Output virtually pulse free. Powered by 110v A.C. motor size 30x23x15cm. Weight 7 kilos. Price £20 p&p £2.00 (inc. VAT £23.76). Suitable transformer for 230, 240v A.C. £8.00 p&p £1.00 (inc. VAT £9.72). New Manufacturer's Surplus.



STROBE! STROBE! STROBE!


HY-LIGHT STROBE KIT Mk. IV
Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s. Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Price £18.00 post £1 (£20.56 inc. VAT & P). Specially designed case and reflector for Hy-Light £8.25 Post £1.00 (£9.99 inc. VAT & P)

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES
4ft. 40 watt £7.75 (callers only) 2ft. 20 watt £5.50. Post 60p (For use in stan bi-pin fittings). Mini 12in. 8 watt £2.50. Post 25p (£2.97 inc. VAT & P). 9in. 6 watt £2.00 Post 25p (£2.43 inc. VAT & P). 6in. 4 watt £1.75 Post 25p (£2.16 inc. VAT & P). Complete ballast unit. Either 6", 9" or 12" tube 230V A.C. op. £3.50 plus P&P 40p (£4.21 inc. VAT & P). Also available for 12V D.C. op. £3.50 plus P&P 40p (£4.21 inc. VAT & P)

WIDE RANGE OF DISCO LIGHTING EQUIPMENT
S.A.E. (Footscap) for details

XENON FLASH GUN TUBES

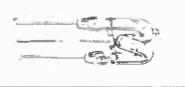Range of Xenon tubes available from stock S.A.E. for full details



RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries

230/240V A.C. Relays: Arrow. 2 c/o. 15 amp £1.50 (£1.84 inc. VAT & P). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.40 inc. VAT & P). Omron or Keyswitch 1 c/o. 7 amp £1.00 (£1.30 inc. VAT & P).

D.C. Relays: Open type 9/12V 3 c/o. 7 amp £1.00 (£1.30 inc. VAT & P). Sealed 12V 2 c/o. 7 amp octal base. £1.25 (£1.56 inc. VAT & P). Sealed 12V 3 c/o. 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P). 24V Sealed 3 c/o. 7 amp 11-pin £1.35 (£1.67 inc. VAT & P) (amps = contact rating). P&P on any Relay 20p. Other types available — phone for details

RESET COUNTER

230 volts AC 3 digits mfg. Veeder Root type LL 144L £1.75 P&P 25p (£2.16 inc. VAT & P). 7lg. 24v d.c. non set £1.50 P&P 25p (£1.89 inc. VAT & P). 6 lg. 24v d.c. resettable £3.00 P&P 25p (£3.51 inc. VAT & P). New Manufacturer's Surplus.



INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work. constant speed clutch. Size L 8 in. W 4 in. H 6 in. weight 6 lb

500 VOLTS 500 megohms £49.00 Post 80p (£57.78 inc. VAT & P)
1000 VOLTS 1000 megohms £55.00 Post 80p (£60.26 inc. VAT & P) SAE for leaflet




VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

ACCOUNT CUSTOMERS MIN. ORDER £10.00

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

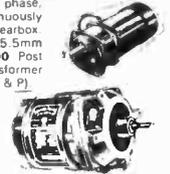115 lb ins. 110 volt, 50Hz, 2.8 amp, single phase, split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm. Length 145mm. equipment tested £12.00 Post £1.50 (£14.58 inc. VAT & P). Suitable transformer 230/240 volt £8.00 Post 75p (£9.45 inc. VAT & P)



BODINE TYPE GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle. 38 amp. This U.S.A. motor is offered in with transformer for 230/240v A.C. input. Price type £6.25 Post 75p (£7.56 inc. VAT & P) or less transformer £3.75 Post 65p (£4.75 inc. VAT & P). (Type 3) 71 r.p.m. 230 volt A.C. Continuously rated. Non reversible £6.50 Post 75p (£7.83 inc. VAT & P). 25 r.p.m., 20lb. inch approx. 115 v a.c. Reversible similar to above drawing. Mfg. by Wylstroms. Price £4.75 + 75p p&p. Total inc. VAT £5.94. Supplied complete with transformer for 240v AC operation £7.25 P&P £1.10 inc. VAT £8.91. New Manufacturer's Surplus.

FRACMO

56rpm 50lbs inch 240vAC reversible. 0.7 amp sharp length 35mm. dia. 16mm, weight 6 kilos 600 grams. Price £15.00 P&P £1.50 (£17.82 inc. VAT). New Manufacturer's Surplus.




PARVALUX GEARED MOTOR

Type SD18 240v AC reversible 30 rpm 50lbs inch. Price £15.00 P&P £1.50 (£17.82 inc. VAT). New Manufacturer's Surplus.



A.E.G. WATER PUMP

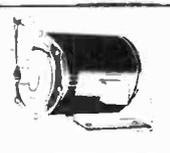200/240v a.c. motor. 2850 rpm. 480w approx. 1.3 hp. driving a centrifugal pump with 1 1/2" inlet and outlet delivering approx 40 galls per min at 10ft. head. Ideal for pumping or circulating any non corrosive light viscosity liquid. Dozens of uses in industrial labs etc. Note this pump is not self-priming. Price £15 + 75p P&P (£17.01 inc. VAT & P). New Manufacturer's Surplus.



CITENCO 19 RPM

FHP motor type C 7333/15 220/240v a.c. 19 rpm reversible motor, torque 14.5 kg. Gear ratio 144:1. Brand new incl. capacitor our price £14.25 + £1.25 P&P (£16.74 inc. VAT & P). New Manufacturer's Surplus.




REVERSIBLE MOTOR 230V A.C.

General Electric 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 90mm. Spindle 5/16 dia. 20mm long. Ex-equipment tested £3.00. Post 50p (£3.78 inc. VAT & P).

METERS 90mm Diameter

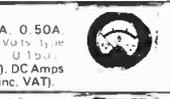DC type 65C5, 0-2A, 0-20A, 0-20A, 0-50A. AC type 65C12, 0-1A, 0-5A, 0-50A. DC volts type m65 0-15, 0-30, 0-150, 0-300. AC volts type 65V1, 0-150, 0-300. All at £3.50 P&P 50p (£4.32 inc. VAT). DC Amps type 65C5 0-100 at £5.00 P&P 50p (£5.94 inc. VAT).



'VENNER TYPE' ERD TIME SWITCH

200/250V A.C. 30 amp 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour spring reserve and day omitting device. Built to highest Electricity Board specification. Price £7.75 P&P 75p (£9.18). Reconditioned and tested.



SANGAMO WESTON TIME SWITCH

Type 5251 200/250v a.c. 2 on/2 off every 24 hours. 20 amp contacts with 36 hour spring reserve. Price £6.00 P&P 50p (£7.02 inc. VAT & P). Also available in 10 amp. Reconditioned and tested.


A.E.G. TIME SWITCH

200/250V A.C. 1 on/1 off every 24 hrs. 80 amps contacts (ideal storage heater), spring reserve. Price £10.00 P&P 50p (£11.34). Reconditioned and tested.

11 pin top entry plug complete with 11 pin PC socket £3.80 for 10 pair, p&p 60p + VAT (£4.43). Min. 10 pair.

A.C. MAINS TIMER UNIT

Based on an electric clock with 25 amp. single-pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 mm. audible timer is also incorporated. Ideal for Tape Recorders, Lights Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p (Total inc. VAT & Post £2.87).

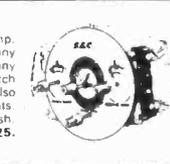


POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £2.40 Post 20p (£2.81 inc. VAT & P). 50 WATT 100, 500, 1k ohm £2.90 Post 25p (£3.40 inc. VAT & P). 100 WATT 1/5, 10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm £5.90. Post 35p (£6.75 inc. VAT & P). Black silver skirted knob calibrated in Nos. 1-9. 1/4 in. dia brass bush. Ideal for above Rheostats. 24p ea.

600 WATT DIMMER SWITCH

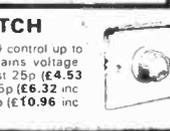Easily fitted. Fully guaranteed by makers. Will control up to 600w of lighting except fluorescent at mains voltage. Complete with simple instructions £3.95 Post 25p (£4.53 inc. VAT & P). 1000 watt model £5.60 Post 25p (£6.32 inc. VAT & P). 2000 watt model £9.75 Post 40p (£10.96 inc. VAT & P).



ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.


SERVICE TRADING CO.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

tech tips

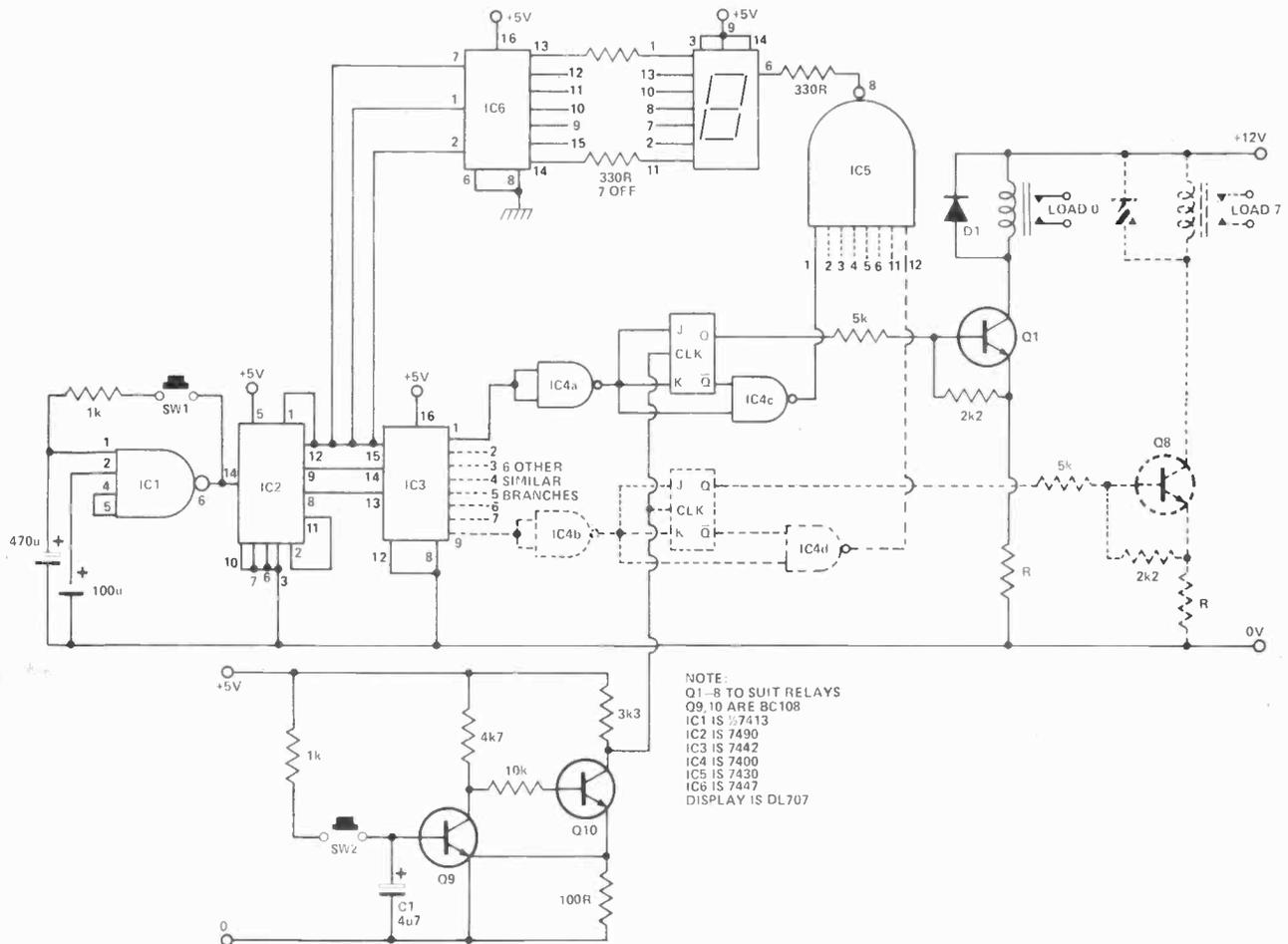

Electronic Switch

S. Yacu

This circuit provides remote switching of up to eight loads, and uses only two switches for selection. One switch is used to select the load to be controlled, the second controls whether the load is energised or not. If the state of one of the loads needs to be changed,

SW1 is depressed until the number of the load appears on the 7-segment display. The decimal point then indicates whether or not the load is energised. To change the state of the load, SW2 is depressed (pressing SW2 again will change the loads state again).

The circuit is based on a 7442, 1 of 8 multiplexer and a 7490 binary counter. When SW1 is closed, the

Schmitt trigger IC1 will oscillate and clock the 4-bit counter. This drives the 7-segment decoder and the 1 of 8 multiplexer. The outputs from the multiplexer are inverted and fed to the J-K flip-flops. When SW2 is pressed and released, a pulse will occur at the collector of Q10. The pulse will clock the selected flip-flop and activate or deactivate the relevant relay driver transistor (Q1-8).

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

B. BAMBER ELECTRONICS

DEPT. ETI, 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE
Tel. ELY (0353) 860185 (Tues. to Sat.)

CASH WITH ORDER. (MINIMUM ORDER £2.00)
PLEASE ADD VAT AS SHOWN
POST PAID (UK ONLY), SAE WITH ENQUIRIES
CALLERS WELCOME BY APPOINTMENT ONLY

ALL BELOW — ADD 8% VAT

MAINS TRANSFORMERS, TYPE 15/300 240V input, 15V at 300mA output, £1.50 each.
MAINS TRANSFORMERS, TYPE 45/100, 240, 220, 110, 20 0V input, 45V at 100mA output, £1.50 each.
MECHANICAL COUNTERS, 4 digit Resettable, 60p each.
SLOW-MOTION MOTORS, 120V 50Hz 1RPM. Size approx 2 dia 1 1/2 deep, with 1/2 spindle, 60p each, or 2 for £1.00.
1 1/2V DC MOTORS (Ideal for model makers, quite powerful), 50p each.
6BV6 VALVES (BRAND NEW), 85p each, or 2 for £1.50.
SUB-MINIATURE ROTARY SWITCHES, 4 x 5-way make contacts. Size approx. 3/4 dia, 1 deep, 3/16 spindle, 50p each.
30p BEHIVE TRIMMERS, Brand new, 4 for 50p.
Min. 5p AIR SPACE TRIMMERS, approx. 1/4 square, 3 for 50p.
Min. 5p COMPRESSION TRIMMERS, 1/2 x 5/16, 4 for 50p.
SMITHS CLOCK MOTORS, 200-250V 50Hz 2 watts, 1 rev. every 2 mins., 3 hole fixing, 1/2 spindle, £1.00 each.
LARGE ELECTROLYTIC PACKS, Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3.00 per pack (+ 12 1/2% VAT).

FULL RANGE OF BERNARDS/BABINI ELECTRONICS BOOK IN STOCK S.A.E. FOR LIST

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES

Aluminium Boxes with Lids		
AB10	5 1/2 x 4 x 1 1/2	75p
AB13	6 x 4 x 2	£1.00
AB14	7 x 5 x 2 1/2	£1.25
AB15	8 x 6 x 3	£1.50
AB16	10 x 7 x 3	£1.75
AB17	10 x 4 1/4 x 3	£1.50
AB25	6 x 4 x 3	£1.25

Vinyl Coated Instrument Cases Blue Tops with Plain Lower Sections Very smart finish

WB1	5 x 2 1/2 x 2 1/4	75p
WB2	6 x 4 1/2 x 1 1/4	£1.35
WB3	8 x 5 x 2	£1.80
WB4	9 x 5 1/4 x 2 1/2	£2.00
WB5	11 x 6 1/4 x 3	£2.25
WB6	11 x 7 1/2 x 3 1/2	£2.50
WB7	12 x 6 x 5 1/4	£2.85
WB853	8 x 5 1/2 x 3 1/2	£2.25

ALL BELOW — ADD 8% VAT

MIXED COMPONENT PACKS, Containing resistors, capacitors, switches, pots, etc. All new, and hundreds of items, £2.00 per pack, while stocks last.
A NEW RANGE OF SPEAKERS & CABINETS, BRAND NEW & BOXED, AT BARGAIN PRICES.
TELEFUNKEN HIGH QUALITY SPEAKERS, 3 ohm, 8 watt RMS, 9 3/4 dia Full range type £6.00 each (or 2 for £11.00) + 12 1/2% VAT.
TYPE L2 TRIANGULAR CORNER CABINETS, Smart woodgrain Formica type finish with nylon grille, Overall height 23 x 12 wide, Contain three 15 ohm 6 1/2 x 4 full range speakers in parallel + 100V line transformer (easily disconnected for 5 ohm operation) £7.50 each (or 2 for £14.00) + 12 1/2% VAT.
TYPE M704 CEILING SPEAKERS, White plastic fascia 10 square, for recess mounting into ceiling, with 8 dia. 15 ohm full range speaker, £4.00 each + 12 1/2% VAT.
TYPE L4 PORTABLE SPEAKER CABINET, Smart woodgrain Formica type finish with nylon grille, 15 high x 14 wide x 7 deep (tapering), containing 10 round, 15 ohm full range speaker + 100V line transformer, £7.00 each + 12 1/2% VAT.
TYPE HT4 HOTEL SPEAKER CABINET, wood veneered, 12 1/4 wide x 5 1/4 high x 3 1/4 deep, with aluminium grille + volume control and 4 way + off switch panels on front. Very smart, contains 3 ohm 5 x 3 elliptical speaker + 100V line transformer, £5.00 each + 12 1/2% VAT.

TRANSISTORS

BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
BSX20 (VHF osc/mult.), 3 for 50p.
BC107 (metal can) 4 for 50p.
BC108 (metal can) 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BF152 (JHF amp/mixed), 3 for 50p.
2N3819 Fet., 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAV31 Signal Diodes, 10 for 35p.
741CG RCA OP Amps 4 for £1.00.
SCRS400V at 3A, stud type, 2 for £1.00.
TIP2955 Silicon PNP power transistor, 60V at 15A, 90 Watts, Flat pack type, 2 for £1.50.
GERMANIUM DIODES, approx 30 for 30p.
1N4148 (1N914) diodes 10 for 25p.

VALVES

QQV05/20A (ex. equipment), £3.00
QQV03/10 (ex. equipment), 75p or 2 for £1.20.
6BH6 (ex. equipment), 2 for 50p
All the above valves are untested, except for heaters, and no guarantee of percentage of emission is given.
Sorry, no returns.

ALL BELOW — ADD 8% VAT

MULLARD 85A2 85V STABILISER VALVES (brand new) 70p each or 2 for £1.20.
RED LEDs (Min. type), 5 for 70p.
VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base, £6.50 each Brand new.
AEI CS10B/R MICROWAVE DIODES, up to X-Band, max. noise figure 8.5dB at 9.375GHz, 80p each.
DIE-CAST BOXES
Size approx.
4.3 x 2.3 x 1.2 (111 x 60 x 30mm) £1.10
4.8 x 2.3 x 1.5 (121 x 60 x 38mm) £1.65
4.8 x 3.8 x 1 (121 x 95 x 25mm) £1.90
4.8 x 3.8 x 2 (121 x 95 x 51mm) £2.20
6.8 x 4.8 x 2 (171 x 121 x 51mm) £2.75
4.8 x 3.8 x 3 (121 x 95 x 78mm) £3.00
6.8 x 4.8 x 4 (171 x 121 x 101mm) £4.20
8.6 x 5.8 x 2 (222 x 146 x 51mm) £3.75
10.6 x 6.8 x 2 (273 x 171 x 51mm) £4.85

SPIRALUX Tools for Electronics enthusiasts SAE for list

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz), Our selection only £1.00 pack.
SOLDER SUCKERS (Plunger Type) Standard Model, £5.50.
Skirted Model, £6.00.
Spare Nozzles, 65p each.
MULTICORE SOLDER 1/2kg (1.1lb.) 60/40 20 SWG on plastic reel, £3.00.
WELLER WP600 Mains operated temperature control, soldering iron, £15.00.
SPARE TIPS (for WP600): Two types available TYPE CC7 (W60D) Standard, TYPE AA7 (W6DD) Finer tip, £1.60 each.
WELLER TCP2 temperature controlled soldering iron, and PLU2D power unit (replaces Weller TCP1), iron + PSU £30.00 Spare tips CC7 (standard), or K7 (finer tip) £1.50 each.
Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

PLASTIC PROJECT BOXES, with screws on lids (in black ABS) with brass inserts

Type NB1 approx. 3 x 2 1/4 x 1 1/2 45p each
Type NB2 approx 3 1/4 x 2 1/4 x 1 1/2 55p
Type NB3 approx 4 1/2 x 3 1/4 x 1 1/2 65p each
Slider Switches 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.
OSMOR 10V REED RELAY COILS (1k ohm coil) to fit 1/4 reeds (not supplied), 2 for 50p.
HF CHOKES wound on 1/4 x 1 long ferrites, 4 for 50p.
VHF CHOKES wound on 6-hole tubular ferrites, 5 for 40p.

ALL BELOW — ADD 8% VAT

DUAL TO 18 HEATSINKS 1 x 1/2 x 1/4 with screw-in clamps, 3 for 50p.
GLASS BEAD FEEDTHROUGH INSULATORS, solder-in type, overall dia. 5mm, pack of approx. 50 for 50p.
LARGE GLASS BEAD FEEDTHROUGH INSULATORS, as above but 8mm dia. pack of approx. 50 for 70p.
12V CONTINENTAL-TYPE PLUG-IN RELAYS, 2 pole change-over, 700ohm coil, 60p each. Bases to fit (only supplied with relays), 10p each.
1 1/2V DC MOTORS, small but powerful (ideal for modelmakers), 50p each.
20V RELAYS, PCB mounting type, single pole change-over, 35p each.
BSR AUTOCHANGE RECORD PLAYER DECKS with cue device, 33-45-78 rpm, for 7, 10, 12 records. Fitted with SC12M Stereo Ceramic cartridge and stylus. Brand new, £14.00 + 12 1/2% VAT.
GARRARD AUTOCHANGE RECORD PLAYER DECKS, Model 6300, with cue device, 33-45-78 rpm, for 7, 10, 12 records. Fitted with K541B Stereo Ceramic cartridge and stylus. Brand new, £16.00 + 12 1/2% VAT.
Please note: record decks sent by Roadline, allow 14 days for delivery.
10.7MHz SSB XTAL FILTERS (2.4kHz Bandwidth) Low imp. type. Carrier and unwanted sideband rejection min. -40dB (need 10.69835 & 10.70165 xtals for USB/LSB, NOT SUPPLIED). Size approx 2 x 1 x 1, £10.00 each.
LOW PASS FILTERS (low imp. type), 2-9MHz, small metal encapsulation, size approx 1 1/2 x 3/4 x 3/4, 75p each.
CELESTION 8 x 5 ELLIPTICAL SPEAKERS, 20 ohm, 3 watts rated, £1.50 each + 12 1/2% VAT.

ALL BELOW — ADD 12 1/2% VAT

VARICAP TUNERS, Mullard type, ELC1043/05, Brand new, £5.00.
TV Plugs (metal type), 4 for 60p.
3-pin Din Plugs, 4 for 50p.
Din 3-pin Line sockets, 15p each.
Din Speaker Sockets, 2-pin, 4 for 30p.
Dubilier Electrolytics, 500uF 450V, 2 for 50p.
Dubilier Electrolytics, 100uF 275V, 2 for 50p.
Plessey Electrolytics, 470uF F 63V, 3 for 50p.
TCC Electrolytics, 1000uF 30V, 3 for 60p.
Dubilier Electrolytics 5000uF F 35V, 50p each.
Dubilier Electrolytics, 5000uF F 50V, 60p each.
ITT Electrolytics, 6800uF F 25V, high grade, screw terminals, with mounting clips, 50p each.
Resistor PKS approx 300 pieces 1/2 to 2 watt types, mixed values, our selection, £1.00 each.
A RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. SAE FOR LIST.

NEW FROM BI-KITS!

AL120 AUDIO AMPLIFIER

(WITH INTEGRAL HEAT SINK)

BETTER THAN 50w RMS!

Out Power THD 1%	50 watts min.
Supply Voltage Max.	70 volts
Operating voltage range	50-70
Load	8-16ohms
Frequency Response ± 1 db	25Hz—20kHz
Sensitivity for 50 watts into 8 ohms	500 mV
Input Impedance	35kohms
THD at all power levels up to clipping	.05% max. typically .02%
S/N ratio	100dBs
Max. ambient operational temp.	45 deg C
S/C Complement	13 transistors 3 diodes
Size overall	192 x 89 x 40 mm
Weight	240 gms

FOR ONLY

£11.95

+ 8% VAT, 25p P&P

ALSO SPM120 Stabilised Power Supply

AVAILABLE IN THREE ALTERNATIVE VOLTAGES — 45, 55, 65 volts.

TO POWER THE FOLLOWING BI-PAK AMPLIFIERS:

- SPM 120/45 Two AL60s up to 25w per channel simultaneously £4.95 + 12 1/2% VAT
- SPM 120/55 Two AL80s up to 35w per channel simultaneously £4.95 + 12 1/2% VAT
- SPM 120/65 Two AL120s up to 50w per channel simultaneously £5.95 + 12 1/2% VAT
- SPM 120/65 One AL250 up to 125w £5.95 + 12 1/2% VAT. Please add 25p P&P to all orders.

AC INPUT:

AL 120/45 40-48v ● AL 120/55 50-55v ● AL 120/65 60-65v ● OUTPUT CURRENT 2.5A ● RIPPLE @ 1A 100mV ● 2A 150mV.

USE YOUR SPM 120 WITH ANY OF THESE!

- AL 60. 25w (RMS) AMPLIFIER £4.55 + 12 1/2% VAT 25p P&P
- AL 80. 35w (RMS) AMPLIFIER £7.15 + 8% VAT 25p P&P
- AL 250. 125w (RMS) AMPLIFIER £17.25 + 8% VAT 40p P&P
- PA200. Pre-amplifier for use with all the above modules £16.30 + 12 1/2% VAT 40p P&P

BI-PAK

DEPT. ETI.8, P.O. Box 6, Ware, Herts.
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

Constant Current Source



J Macaulay

The circuit shown will provide 3 preset currents which will remain constant despite variations of ambient temperature or line voltage.

ZD1 produces a temperature stable reference voltage which is applied to the non inverting input of IC1.

100% DC feedback is applied from the output to the inverting input holding the voltage at Q2's emitter at the same potential as the non inverting input.

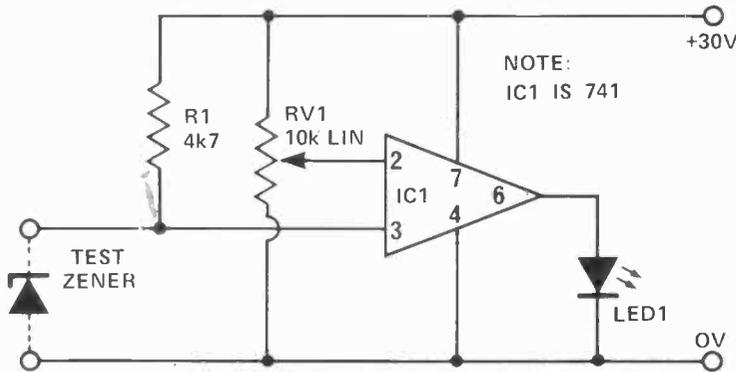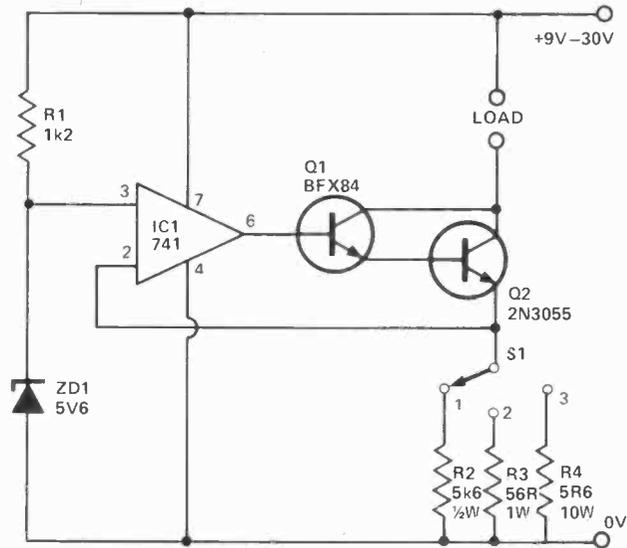The current flowing into the load therefore is defined solely by the resistor selected by S1. With the values employed here, a preset current of 10mA, 100mA or 1A can be selected. Q2 should be mounted on a suitable heatsink.



NOTE:
IC1 IS 741

Zener Tester

M Ibions

This circuit is to provide a cheap and reliable method of testing zener diodes.

RV1 can be calibrated in volts, so that when LED 1 just lights, the voltage on pins 2 & 3 are nearly equal. Hence the zener voltage can be read directly from the setting of RV1.

The supply need only be as high a value as the zener itself. For a more accurate measurement, a precision pot could be added and calibrated.

Simple Dual Power Supply


L Swann

This circuit offers a cheap and simple way of obtaining a split power supply (for Op-amps etc.), utilising the quasi-complementary output stage of the popular LM380 audio power IC.

The device is internally biased so that with no input the output is held mid-way between the supply rails.


R1, which should be initially set to mid-travel, is used to nullify any imbalance in the output. Regulation of V_{OUT} depends upon the circuit feeding the LM380, but the positive and negative outputs will track accurately irrespective of input regulation and unbalanced loads.

The free-air dissipation is a little

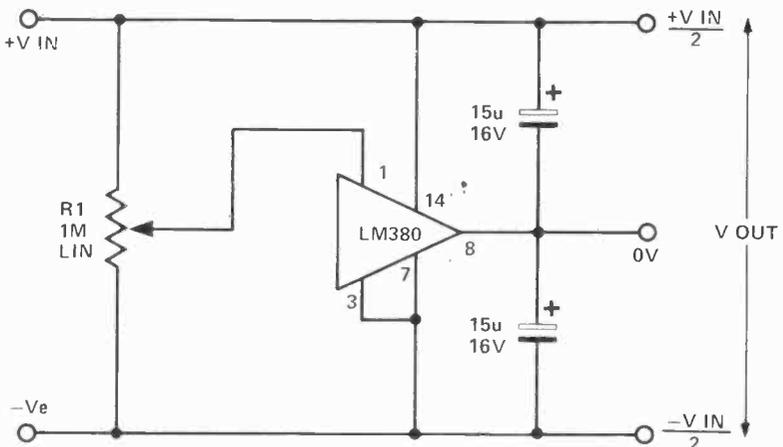

over 1 watt, and so extra cooling may be required. The device is fully protected and will go into thermal shut-down if its rated dissipation is exceeded, current limiting occurs if the output current exceeds 1A3.

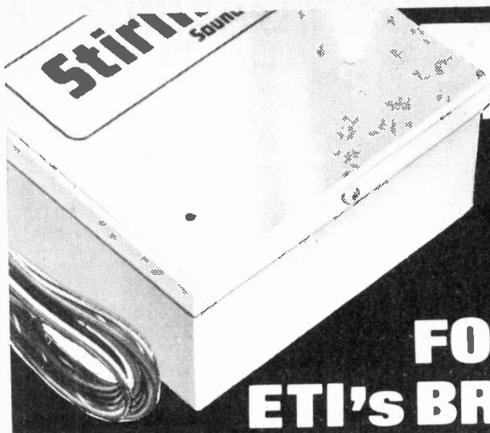The input voltage should not exceed 20 V.



OFFER EXTENDED

**TO AUG.
31st**

ONLY £9.95

**INC. VAT
AND
POST FREE**

**FOR THIS MARK 2 VERSION OF
ETI'S BRILLIANT CAR IGNITION UNIT**

**E.T.I. APPROVED FOR
USE WITH NORMAL
IGNITION SYSTEMS
REVERT TO NORMAL
SWITCH CAN BE MOUNTED
ON DASHBOARD
NO MORE BURNT CONTACT
POINTS
REV LIMITER
NEON LIGHT INDICATOR
NEG EARTH**

The best value ever — so why pay more?

Because of the outstanding success of this ETI/STIRLING SOUND project, we are extending this exclusive offer to ETI readers until August 31 next. This gives you the chance to fit your ETI ignition unit during the longer hours of daylight and in time for your holidays. It gives us the opportunity to keep our factory going at full capacity over what is usually a quiet period. This is beneficial all round — to you, to our staff, to our suppliers of material and so on (not forgetting the tax man!). And in case you need reminding, the Stirling Sound ETI Mk. 2 electronic ignition unit can give you better mileage per gallon of petrol, easier starting in Winter, cleaner plugs and an end to burnt contact points plus instant switching back to normal ignition if required — in fact, it's an investment in better motoring you cannot afford to ignore. And it's so easy to fit, too!

Easy to build complete kit inc. drilled and titled P.C.B. aluminium case, leads, etc., and simple instructions.

KIT Complete kit as recommended by E.T.I. (May 78). Inc. VAT and post free U.K. **£9.95**
(After Aug. 31st £12.75)

BUILT AND TESTED inc. VAT post free U.K. **£12.75**
(After Aug. 31st, £15)

The BETTER catalogue

Modules — power amps 3 to 100 watts R.M.S., power supplies, control units, etc. — D.I.Y. disco/P.A. — bargain disco assemblies — plenty to choose from with technical gen. diagrams and good instructions. Send only 20p for postage and handling for your copy by return. You can't be without it!

YOUR MONEY-SAVING COUPON

Please send ETI's Mk 2 Kit/Ready-built and Catalogue

For which I enclose £ + 20p

Name

Address

BLOCK LETTERS PLEASE

ET18

**Stirling
Sound**

All communications to Dept. ET18
37 Vanguard Way, Shoeburyness, Essex (03708) 5543 Shop 222/224 West Road, Westcliff-on-Sea

PRICES INC. VAT & POST FREE IN U.K.

To order send cheque or money order crossed and made payable to Stirling Sound. (Cash must be sent by regd. post only). Allow 28 days delivery.

**TO ORDER BY ACCESS OR BARCLAYCARD JUST LET US
KNOW YOUR NUMBER.**

**STRATHAND
SECURITY**

Holidays coming? Worried about your house? Why not fit an alarm and have a relaxed holiday. We supply the parts — all top quality professional items as used by major alarm companies. Easy to install, e.g.

- 101. Magnet and reed switch. Flush fitting. 4 wire. Requires hole 12mm diameter by 34mm deep **80p**
- 102. Magnet and reed switch. Flush fitting screw terminals. Requires hole 15mm diameter by 14mm deep **£1.05**
- 103. Magnet and reed switch. Surface fitting. 4 wire. Size 65mm by 13mm by 11mm **90p**
- 104. Magnet and reed switch Heavy duty. Size 103mm by 20mm by 18mm. Two hole fixing **£3.00**
- 105. Pressure pad — stair tread 22½" by 6½" **£1.35**
- 106. Pressure pad — large 29½" by 15" **£2.05**
- 107. Window foil — self adhesive — top quality. 70 roll ¼ wide **£3.17**
- 108. Foil blocks — self adhesive. (Joins foil to cable) **£3.70**
- 110. Keyswitches with mounting plate and cover **£3.70**
- 111. Bell boxes heavy duty plastic coated metal **£8.05**
- 112. Bell 6" heavy duty — very loud 12v D.C. **£10.25**
- 116. 4 core cable 100m — white **£10.75**
- 123. Control panel to British Standard. Mains/battery, silent entry/exit. Anti-false alarm circuitry **£46.40**

All prices include VAT and postage

PLUS

Radar (microwave) units, automatic 999 dialling units with tape message, and many other items.

This month's Special Offer:

Completely self-contained Smoke Detector for house or caravan. Loud penetrating sounder. Battery included. Our Price while stocks last — **£19.95** including VAT and P&P.

STRATHAND SECURITY
44 St. Andrew's Square
Glasgow, G1
Tel: 041-552 6731/2



Callers Welcome

Don't let your environment dehydrate you, BUY OUR "HONEYWELL HUMIDITY CONTROLLER". Membrane actuated, adjustable by ¼ shaft. Ideal for greenhouses, offices, centrally heated homes, etc. 3.75A contacts at 250V. Build Humidifiers or dehydration alarms with this novel gadget at a fraction of original cost. £1 each, 3 for £2.50.

BARGAIN PACKS

- Miniature transformer F.M. front-end with integral tuning gang BB-108MHz, 10.7MHz, I.F. output £2.50
- Miniature Veritron™ FM4 10.7MHz ceramic filters 50p each, 3 for £1
- Crystal earpieces with lead 40p each 3 for £1
- Magnetic earpieces with lead and plug 25p each 5 for £1
- Ultrasonic transducers transmitter and receiver, 14mm diam 40 kcs £4.25 per pair
- 4 aluminium boxes 128 x 44 x 38mm, ideal for signal injectors, etc £1.00
- Self-fluxing enamelled copper wire 22 swg on 2oz. reels 60p ea.
- 100 miniature reed switches, ideal for burglar alarms, model railways, etc £3.30
- 6.6-pole 12 volt reed relays on board £2.45
- High quality computer panels smothered in top-grade components £4.75
- 5lbs £8.95
- 10lbs.
- New U.H.F. transistor TV tuners. Rotary type with slow motion drive £2.50
- Aluminium TV coax plugs 10 for £1.00
- Miniature mains transformers, fully shrouded, ex new equipment 240V in 6-0-6v out at 100 mA Complete with mains lead and plug on input and short leads on output 90p
- Miniature edgewise panel mounting level meters 200µ A F S D 90p
- 300 mixed resistors ½ & ¼ watt £1.50
- 300 modern mixed caps most types £3.30
- 100 mixed electrolytics £2.20
- 300 mixed printed circuit components £1.50
- 300 mixed printed circuit resistors £1.00
- 100 high-wattage resistors, W.W., etc £2.20
- 20 assorted VDR's and thermistors £1.20
- 25 assorted presets, skeleton, etc £1.20
- 25 assorted pots and presets £1.50
- 470 µF 25v radial modern type 5 for £1
- 200 mixed 1- and 2-watt resistors £1.50
- 100k sliders, mono or stereo 50p each 3 for £1
- 100k varicap pots, can be banked side by side, very compact 5 for £1
- 160 µF 25v axial leads 10 for £1
- 300 mixed modern caps, most types £3.30
- 100 mixed modern miniature ceramic and plate caps £1.20

Semiconductor Bargains

- 100 new and marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95
- 200 new and marked transistors including 2N3055, AC128, BFY50, BD131, etc. £6.95
- 100 mixed diodes IN4148, etc. £1.20
- 100 mixed diodes including zener, power and bridge types £3.30
- BR 101 full spec. 5 for £1.00
- ITT 25kV ctv eht triplers for Decca "Bradford" chassis brand new £2.50, 5 for £10
- BD131 3 for £1.00
- SN76115N (equivalent MC1310) £1.00
- TBA120A 2 for £1.00
- BD140 3 for £1.00
- Motorola Audio I.C., 1 watt+ into B-16Ω. Operates between 9-16v. 10-400MV sensitivity S.C. proof, no heat-sink req. With data and circuits £1.20
- Data and circuits 20p + S.A.E.

Deluxe Fibre Glass Printed Circuit Etching Kits

- Includes 150 sq ins. copper clad 1/4 g board, 1lb. ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions Only £5.30
- 150 sq ins. fibre glass board £2.00
- Dalo pen 90p
- 1lb. ferric chloride to mil spec £1.25
- 5lbs. ferric chloride to mil spec £5.00
- Instruction sheet 20p

30p P & P ON ALL ABOVE ITEMS SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY DEPT. ETI, 149A BROOKMILL ROAD DEPTFORD, LONDON, SE8

Callers by appointment only



Wilmslow Audio

THE firm for speakers!

Send 15p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list

- ATC ● AUDAX ● BAKER ● BOWERS & WILKINS
 ● CASTLE ● CELESTION ● CHARTWELL ●
 COLES ● DALESFORD ● DECCA ● EMI ● EAGLE
 ● ELAC ● FANE ● GAUSS ● GOODMAN'S
 HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN
 WATTS ● KEF ● LEAK ● LOWTHER ●
 McKENZIE ● MONITOR AUDIO ● PEERLESS ●
 RADFORD ● RAM ● RICHARD ALLAN ● SEAS ●
 TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO Dept. ET1

SWAN WORKS, BANK SQUARE, WILMSLOW,
 CHESHIRE, SK9 1HF
 Discount HiFi, etc., at 5 Swan Street and 10 Swan
 Street
 TEL: WILMSLOW 29599 FOR SPEAKERS
 WILMSLOW 26213 FOR HIFI

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCB and full instructions. **£13.75**
 Special white box (56 x 131 x 71mm) with red Acrylic window — undrilled £2.20 ready drilled for kit £2.50

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated touch plates. Complete with easy to follow instructions
TSD300K TOUCHSWITCH and DIMMER combined ONE touchplate to switch light on or off. Brightness controlled by small knob **£5.20**
TS300K — TOUCHSWITCH, TWO touch plates. One for ON, one for OFF **£4.00**
TSA300K — AUTOMATIC TOUCHSWITCH. ONE touch plate. Touch for ON and light stays on for preset time (variable from 2 secs to 3½ mins). Ideal for stairs and hall **£4.00**

LD300K — 300W LIGHT DIMMER KIT. Replaces conventional light switches **£2.80**

AY-5-1230 Clock Appliance Timer I.C. **£4.85**
 LM3911 Thermometer/Temperature Control I.C. (with data) **£1.00**
 NE555 Timer I.C. 8 pin dill **36p** (3 for £1.00)
 741 Op. Amp I.C. 8 pin dill **24p** (5 for £1.00)

BC147 **8p**, BFY50 **15p**, 2N6027 PUT **34p**
 BC148 **8p**, 2N3055 **40p**, TIS43 UJT **24p**
 BC158 **10p**, TIP31A **50p**, 1N4148 **4p**
 BC182L **8p**, TIP32 **50p**, 1N4004 **4p**

CMOS LOW PRICES.

4000 **18p**, 4012 **18p**, 4023 **18p**, 4077 **45p**
 4001 **18p**, 4013 **51p**, 4025 **18p**, 4501 **20p**
 4002 **18p**, 4015 **91p**, 4040 **97p**, 4510 **150p**
 4007 **18p**, 4016 **51p**, 4049 **50p**, 4516 **150p**
 4011 **18p**, 4017 **91p**, 4050 **50p**, 4519 **56p**

TRIAC BARGAINS

400V Plastic isolated tab
 3A **63p**
 6.5A with trigger** **80p**
 8.5A** **79p**
 12A **84p**
 16A **105p**
 20A **165p**
 25A **190p**
 DIAC **21p**
 C106D 5A/400V SCR **50p**

MINI MAINS TRANSFORMERS

6-0 6V 100mA **85p**
 12-0-12V 100mA **95p**

OPTO ELECTRONICS

0.2" Red L.E.D. **10p**
 0.2" Green L.E.D. **21p**
 0.2" Yellow L.E.D. **25p**
 DL727 Dual 0.5" Display **£1.50**

C280 Polyester Capacitors 250V d.c. (values in uF)
 01 4p; 022, 033, 047, 068 5p; 0.16p; 15
 7p; 22 8p; 33 11p; 47 12p; 68 17p; 1.0
 20p; 2.2 36p
 RESISTORS 33W 5% 22ohm to 10Mohm 1½p
 Push Button, push to make **20p**

QUANTITY DISCOUNTS ON REQUEST
 Add 8% (1½%) V.A.T. plus 25p P&P. MAIL ORDER ONLY TO

T.K. ELECTRONICS (ET1)
 106 STUDLEY GRANGE ROAD, LONDON, W7 2LX

1N4148 Diodes by ITT/Texas. 100 for **£1.50**. These are full spec. devices.

Unencoded Hexadecimal 19 keyboard 1-10 ABCDEF. 2 optional keys. Shift key. **£12.50**.

MM2102 AN-4L 1024 x 1 Bit. 450 nano sec. Static Ram. **£1.60** each. 4/ **£6.00**. 8/ **£11.60**.

2112 256 x 4 Bit Static Ram 450 nanosec. **£2.95** each. 4/ **£11.60**. 8/ **£22.60**.

AY5-1013 UAR/T. **£6.00**.

FND 500 Seven Segment Common Cathode Display **£1.30** each. 4/ **£5.00**.

Red Leds 0.125" or 0.2" 10 for **£1.20**. 100/ **£9.00**. 1,000/ **£60.00**.

Murata Ultrasonic Transducer. **£2.50** each. **£4.00** pair.

741 Op Amp. **25p** each. 10/ **£2.00**.

555 Timer. **28p** each. 10/ **£2.50**.

4001	14p	4029	110p
4007	16p	4047	100p
4011	14p	4049	40p
4012	14p	4060	120p
4013	50p	4066	55p
4015	90p	4069	20p
4016	40p	4071	16p
4017	90p	4072	16p
4020	100p	4081	16p
4022	90p	4082	16p
4023	16p	4510	120p
4024	65p	4511	150p
4025	16p	4516	110p
4026	160p	4518	130p
4027	50p	4528	100p
4028	90p		

Prices include Post and VAT

T. POWELL

Access/Barclaycard
 306 ST PAUL'S ROAD
 Highbury Corner, London N.1.
 Tel: 01-226 1489

SAVE £££s WITH MONITEL



Displays the accumulating cost of your telephone conversation

See your money ticking away day or night, local or long distance

Monitel is programmed by a punched card to calculate the exact cost of your call, including VAT, for all three Post Office charge bands and adjusts itself to peak, standard and cheap rate periods, including weekends. International Monitel covers all UK and international charge bands.

When not in use as a charge calculator the Monitel becomes an accurate digital desk clock — no need to dial TIME!

A touch of a button will recall the cost at any time before your next call. Styled to match, the Monitel sits unobtrusively under the standard P.O. telephone and is available in all seven matching colours.

UK Model **£28.95**
 International Model **£38.50**


Please state colour when ordering
 Quantity discounts available
 Prices include VAT and P & P

For high-quality electronic watches and calculators at substantially discounted prices, see our separate advertisement.

Send cheque, P.O. or phone your credit card no. to

Dept. ET1
TEMPUS 19/21 Fitzroy Street
 Cambridge CB1 1EH
 Telephone (0223) 312888

INTER-LOCKING PLASTIC STORAGE DRAWERS

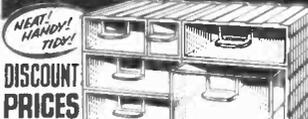

Neatest, neatest systems ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up to any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE INDUSTRY AND GOVERNMENT DEPTS.

SINGLE UNITS (1D) (5in x 2¼in x 2¼in) **£2.90** DOZEN

DOUBLE UNITS (2D) (5in x 4½in x 2¼in) **£4.90** DOZEN


TREBLE (3D) **£4.90** for 8

DOUBLE TREBLE 2 drawers, in one outer case (6D2) **£7.25** for 8

EXTRA LARGE SIZE (6D1) **£6.25** for 8

PLUS QUANTITY DISCOUNTS

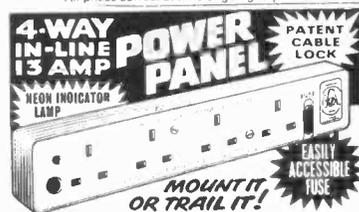Orders over £20, less 5%
 Orders over £60, less 7½%
 PACKING/POSTAGE/CARRIAGE Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage.
 QUOTATIONS FOR LARGER QUANTITIES
 Please add 8% V.A.T. to total remittance.
 All prices correct at time of going to press.




Modern slim-line power panel. countless uses in home, office, factory showrooms. Perfectly safe, unbeatable. Can be mounted on wall or trailed anywhere in room. Neat rubber base. Smart PVC outer cover. Black **£2.90**, White **£3.25**. P&P 60p each. Slate cable length required. 20p per yard.

FLAIRLINE SUPPLIES (Dept. ET1 8)
 124 Cricklewood Broadway, London N.W.2
 Telephone 01-450 4844

SECOND GENERATION INDUCTION BALANCE METAL DETECTOR

DESIGNED SPECIALLY
FOR THE HOME
CONSTRUCTOR

EASY
TO
BUILD.

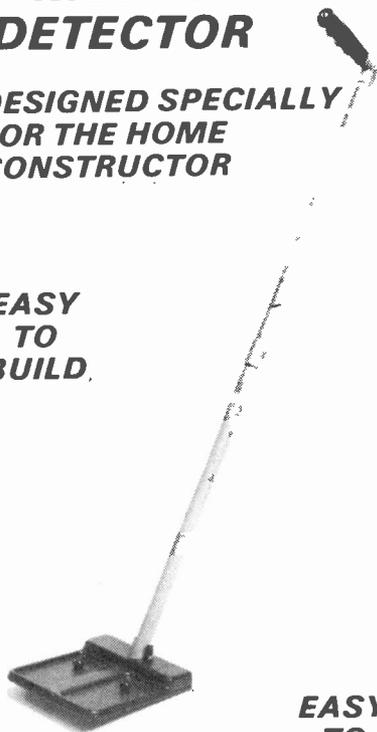

EASY
TO
USE

- A second generation Induction Balance system with improved Variable-Tone detection.
 - Designed by professionals for easy assembly by amateurs but with very good performance.
 - The search coils are fully assembled and adjusted for you.
 - Coils pre-assembled and tested wedge shaped search field
- Uses include:
- ★ Treasure hunting — it's amazing what you can find in the garden or on the beach.
 - ★ Finding lost metallic items.
 - ★ Locating waterpipes and cables under floorboards on in walls.
 - ★ Checking old timber for nails before cutting, etc., etc., etc., etc.

**KIT - COMPLETE WITH PRE-
ASSEMBLED SEARCH COILS**

£16.50

Plus £1-00p&p Plus £1-32 VAT


ASSEMBLED & TESTED

£22.50

Plus £1-00p&p Plus £1-80 VAT

Communication Measurement Ltd
15 MALLINSON OVAL, HARROGATE, YORKS.

LCD PORTABLE CLOCK/RADIO ALARM

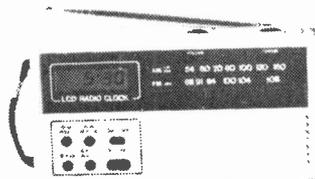

This stylish 6 3/4" x 1 3/4" x 3 1/2" unit features an AM/FM radio and a highly accurate LCD clock which controls the unit so that it can operate as an alarm clock with 4-minute snooze, or you can wake up to your favourite programme. It can also turn the radio off when you go to sleep!

£27.00 + £1 p. & p.
inc. V.A.T.

We accept gov./company purchase orders on all goods

KRAMER & CO.

9 October Place, Holders Hill Road
London, NW14 1EJ

Telex: 888941. ATTN: KRAMER, K7. Tel. 01-203 2473
MAIL ORDER ONLY. S.A.E. for data sheets
Export enquiries welcome

PRICE SMASH

741 (RCA 8 DIL full spec), **17p.**
LM711CH + Data (to 5, voltage compa-
rator), **25p.** TBA 810S **65p.**

Penny and Giles, 5k Slider Faders, **£4.50.**
Signetics 2102B (500s) 1.20 **2708.**
£8. Cannon D type plugs/skts: 25-way
skit., **60p.** 37-way plug or skt, **80p.**
15-way plug or skt, **50p.** Lambda LX
S-A-5-OV-RV1, modular regulated, power
supply 5v DC 4 amps, 240V input, brand
new, cased, 160 mmL x 90 mm WX
80mmH, **£15.** TMS3128NC (shift reg.),
80p. SN74188AN (few only), **£2.50.**
MC10102P, **25p;** MM5241ABV/J,
£2.50. DIL switches, 4-way, **55p.** 7-way,
80p. Red Led .2", **9p.** LM340T plastic
1A voltage regulators, +5V, **95p** + 12v,
85p.

P&P on above 10p

POCKET PAGER

Miniature crystal controlled FM RX Single
Superhet around 30MHZ 450 KHZ IF
contains various tone detectors. Ideal for
modification to 27 MHZ Radio Control OR
28MHZ Amateur Band. Complete, with-
out 2.5v DEAC + circuit of similar type,
£3.95. P&P 25p.

L.B. ELECTRONICS
43 WESTACOTT, HAYES
MIDDLESEX UB4 8AH

SEMICONDUCTOR OFFERS ALL FULL SPEC.

BC212, BC182, BC237, BF197, BC159, BCY71, all 8p each. RCA
2015 TO3 Power Transistor (Sim to 2N3055) 35p. ACY18 18p.
BF200 20p. Motorola MRF 3051 Photo Transistors 35p. N.
Channel F.E.T.s. similar to 2N3819 18p. Mosfet Sim to 40673
35p. 3N140 Mosfets 50p. M203 Dual Matched Pairs Mosfets
Single Gate per F.E.T. 40p. Intel 1024 bit MOS Rams 95p. Mullard
BB113 Triple Varicap Diode 35p. MC1310 Stereo Decoder I.C.s
£1.20. TBAB00 I.C. Amps 90p. CD4051 CMOS 50p. 741 8-pin
D.I.L. 23p. 500v 600mA Bridge Rect. (ex. equip.) 25p. 1N4002
100v 1A Diodes 4p. 14005 800v 1A Diodes 7p. E.H.T. SIL Rec
15KV 2.5mA, 15mm x 5mm 85p. 7812 12v 1A Plastic V. Res
95p. Min. Nixies ITT 58705i 13 x 6mm Fig Size 85 Nixies ITT
GN/9A 13 x 8mm 65p. 0.2 or 0.125 Red LEDs 12p each.
MAN3A 3mm LED Displays 50p. Murata 40KHz transducers
15mm diam. £2.95 pair. NE555 35p. 741S (wide bandwidth)
35p. LM380 80p. LM381 90p. ZN414 75p.

CONDENSER MIKES. EM506 Condenser Mikes. Uni-directional,
F.E.T. Amp Dual imped., 50K/600ohms, 30-18KHz, on/off
switch, £11.00. Miniature Tie Pin Condenser mike 1K imp.,
omni-directional, uses hearing aid battery (supplied) £4.95.

MICROPHONES. Grundig Electret Inserts with built-in F.E.T.
Preamp £1.50. Crystal Mike Inserts 37mm 45p. Electret
Condenser Mikes 1K Imp. with std. Jack Plug £2.85. Cassette
Condenser Mikes with 2.5 and 3.5 Jack Plugs £2.85. Standard
Cassette Mikes 200 ohm imped. with 2.5 and 3.5 Jack Plugs
£1.20. Min E.H.T. Sil. Recs. 115KV 2.5MA 30p.

MORSE KEYS—Hi-speed Type, all metal, £2.25. Belling Lee
L4305 Masthead Amplifiers and 240V AC power unit Group "A"
UHF. Only £7.50.

CRYSTALS. 300KHz HC6U 40p. 4.43MHz C.T.V. Xtals 45p.
01 Edge Connectors, 64 way 65p. 32 way 40p.

RELAYS. Min. 220v AC Sealed Relay 2 pole C/O 45p. 240v AC
Sealed Relay 3 pole C/O 5 amp Contacts 11-pin base 80p. 12 volt
4 pole N.O. Reed Relay 20p. Min. 240v DC Sealed 2-pole C/O
relays 3-amp contacts New 55p.

MOTORS. 1.5 to 6v DC Model 20p. 115v AC min. 3 R.P.M. with
Gearbox 30p. 240v AC Synch Motor 1/5th R.P.M. 65p. 240v AC
Synch. Motor 1/24th R.P.M. 65p. Crouzet 115v AC 4 R.P.M.
Motors, new 95p. 12v DC 5-pole 35p.

BOXES. Black A.B.S. Plastic with brass inserts and lid, 75 x 56 x
35mm 40p. 95 x 71 x 35mm 49p. 115 x 95 x 16mm 57p.

TOOLS. Radio pliers, 5in, insulated handles £1.40. Diagonal side
cutters, 5in, insulated handles £1.40.

TRANSFORMERS. .6-0-6v 100mA, 9-0-9v 75mA, 12-0-12v
50mA 75p each 12-0-12v 100mA 95p. 1 1 Triac Xenon Pulse
Transformer 30p

TIL305 Alpha-numerical Displays, with data, £2.75.
8 WAY RIBBON-CABLE, min solid core, 15p metre.

SWITCHES—Min Toggle, SPST 8 x 5 x 7mm 45p. DPDT 8 x 7 x
7mm 60p. DPDT Centre Off 12 x 11 x 9mm 75p. DPDT C/O
Sliders 20p. R.S. Single Pole C/O Push Buttons 45p. Roller Micro
Switches 15p. Min. Micro Switches 13 x 10 x 4mm 20p. G.P.O.
Keyswitch Assy. 3 Switches 2-3 way, 1-2 way multipole 35p. Min.
Push to make or push to break Switches 16 x 6mm 15p.

SOLDER SUCKER. Plunger type, eye protection, replaceable
nozzle, high suction, £4.95. Reed switches 28mm norm. open, 6p
each.

TAPE HEADS—Cassette Stereo £3.00 BSR MN 1330 1/4 Track
Dual Impedance Rec./Playback 50p. BSR SRP90 1/4 Track Stereo
Rec./Playback £1.95. T010 Assemblies, two heads, 1/4 Track
Rec./Playback Staggered Stereo with built-in erase per head
£1.20 Tape Head Demag 240v AC £1.95.

BUZZERS—GPO Type 6-12v 20p. Min. Solid State Buzzers
6-9-12 or 24v 15mA 75p. All Metal Buzzer, 30mm diam. 6-12
volts, high tone, 25p

U.H.F. TV Transistorised Push Button Tuners (not Varicap), new
and boxed, £2.50.

AEROSOL "TOUCH-UP" PAINT. One colour only. Yellow/
Grey, 6oz can. 35p.

METERS—Stereo Tuning Meters 100µa per movement £2.75.
Grundig Batt. Level Meter 1mA 40 x 40mm £1.10. Min. Level
Meter 200µa 25 x 15mm 75p. Ferranti 600v AC Meter £3.95.

POT CORE UNIT. Has 6-pot cores, including 1 FX2243 (45mm)
and 2 FX2242 (35mm), 3 20mm Panel Fuseholders, 3 T03 SIL
Power Transistors on heat sink, panel with various transistors and
diodes with a 5-amp plastic S.C.R. New £1.75 + 75p P&P

AEROSOLS—Servisol Switch Cleaner + Lubricant 8ozs 55p
Freezer 6ozs 50p. Gear Cleaner & Tar Remover 14ozs 85p

SOLENOIDS—240v AC 45p 12v DC H Duty 75p.

12-WAY MOTORISED CAM UNITS. 50v AC low rev. motor
driving 12 C/O micro switches, supplied with a capacitor for 240v
AC use Ex. equip. £1.95 + 35p P&P

POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS
POSTAGE REFUNDED WITH ORDER) OVERSEAS POST AT
COST VAT INCLUDED IN ALL PRICES

S A E. FOR LISTS

ORDER ADDRESS.

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL 2
051-236 0982

MORE BARGAINS FROM METAC

TV GAMES 4 game B&W

£9.95

TV GAMES 4 game Colour

£13.50

(Suit any TV. Fully guaranteed)

NEW DIGITAL ALARM CLOCK

Model 102

SILENT — ELECTRONIC

- ★ 4in. across x 4½ x 2in.
 - ★ Large red digits
 - ★ 24-hour alarm
 - ★ 9 min. repetition
 - ★ Switched seconds display
- IMMEDIATE DELIVERY



£8.95

★ SPECIAL OFFER ★

5 FUNCTION LCD WATCH (same as ET1 offer)

ONLY £9.95

Post included
1 year guarantee

NEW METAL DETECTOR

ROLLMAST ALERT

£39.95

Features include . . .



£39.95

INC. BAT., BATTERY & EARPIECE

Features: Loudspeaker, Visual Meter, Volume & Tuning Control, 7" White Search Head, Long Battery Life (PP3), Headphone Socket (Phones optional). Reacts negatively to ferrous metal (iron), fully adjustable stem.

ALSO AT £12.95
STANDARD VERSION . . .

- ★ BFO PRINCIPAL
- ★ 5" DEPTH
- ★ 36" STEM ADJUSTABLE
- ★ SINGLE PP3 BATTERY

Sinclair Programmable Scientific Calculator + Free Library

£12.95

Full range of Ladies' LCD Watches from

£18.95

11 FUNCTION CHROME LCD. Screwback, superb strap, fully guaranteed

£17.95

LCD ALARM CLOCK
BATTERY OPERATED
LARGE DISPLAY



- ★ Alarm
- ★ Snooze
- ★ Back light
- ★ Travel pouch

Offer **£17.95**

LCD CALCULATOR

6 functions + case

ONLY £8.95

Please add 30p
P&P all orders

All prices include
VAT

METAC Electronics & Time Centre

67 HIGH STREET
DAVENTRY, NORTHANTS
Tel. (032 72) 76545

327 EDGWARE ROAD
LONDON W2
Tel. (01) 723 4753

Barclay & Access
welcome
Send Card Number
with order



TRANSFORMERS

DUAL VOLTAGE


Primary 220—240v 50HZ
Secondary Voltage and Current Available
Parallel Connection. Details Enc.

Age	Current	£	P/P
12	3A each	4.50	75p
15	2A each	4.40	75p
20	1.5A each	4.35	75p
28	1.1A each	4.30	75p
-20	1A each	4.60	75p
-20	1A each		
12	2A each	3.50	70p
15	1.6A each	3.40	70p
20	1.2A each	3.30	70p
6	1.6A each	2.30	65p
12	0.8A each	2.75	65p
15	0.6A each	2.70	65p
17	0.5A each	2.65	65p
	1.0A each	2.00	60p
	0.6A each	2.05	60p
	0.5A each	2.10	60p
	0.4A each	2.15	60p
	0.25 each	2.20	60p
	0.65A each	1.85	50p
	0.3A each	1.80	50p
	0.25A each	1.75	50p
	1A	2.95	70p
	2A	4.70	1.00
	3A	5.60	1.00
	2A	4.80	1.00

PAYMENT TERMS
W.O. Cheques
Postal Orders
Please Add 8% VAT
per Post & Packing

DORAM

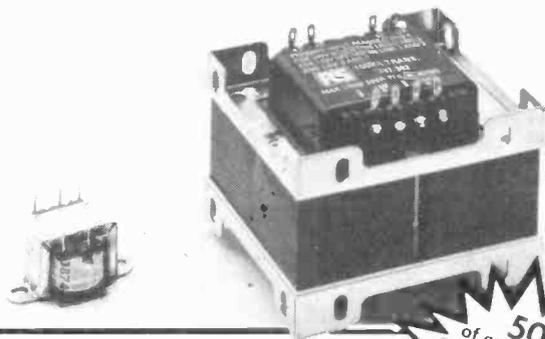SEE THE EXTENDED RANGE OF
TRANSFORMERS IN OUR
NEW EDITION 5 CATALOGUE



Please forward my edition 5 catalogue
I enclose **75p** which covers p. & p.

Name

Address

50p
of goods FREE
for details see your
edition 5 catalogue


ET 2

DORAM Doram Electronics Ltd
PO Box TR8 Leeds LS12 2UF

Overseas orders, except for N. Ireland, please add 35p
to cover despatch by Air.

MINI-ADS & CLASSIFIED

LOW COST BOXES

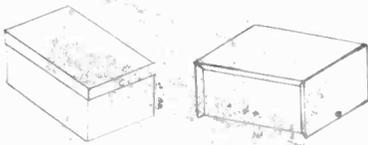

AND INSTRUMENT CASES

Size	Price	Size	Price
3x2x1	42p	6x4½x2	£1.25
4x3x1½	49p	8x5½x2½	£1.50
4x3x2	56p	10x6½x3	£1.95
6x4x2	62p		
6x4x3	72p		
8x6x2	97p		
8x6x3	1.08p		

all prices incl. p&p

Sheet aluminium standard and cut to size, self-tapping screws, nuts bolts and washers. Pamphlet on our full range of cases supplied with every order or send a stamped self addressed envelope to **HARRISON BROS., P.O. Box 55, Westcliff-on-Sea, Essex.** Manufacturing service of sheet metal parts for trade: send drawing and s.s.a.e. for quotation.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components. Full range of ETI printed circuit boards, normally ex-stock, same day despatch at competitive prices. P.C. Boards to individual designs. Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASONS ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

TRANSFORMERS

Twin Primaries 115/230V
Twin Isolated Secondaries
0-4, 5-0-4.5
0-6-0-6 6VA
0-15-0-15

British made — Great Value

Inc. VAT **£1.95** Inc. P&P

Try us for all your Component Requirements

★
T.D. COMPONENTS
Unit Four, Staincliffe Mills
Dewsbury, W. Yorks.
0924 409040

OUR LATEST NOVELTY!



The first LCD Ballpen Chronograph. A clip-on ball point pen with chronograph watch incorporated. A useful gift in an attractive presentation case.

Only **£29.95 + VAT** (in chrome or gilt)

- ★ 6 Digit display
- ★ 8 functions: hour, minute, second, month, date, day of week, stop watch, lap time with backlight
- ★ runs on Ever-ready 393, or equivalent battery (year's life under typical use)
- ★ accurate to 5 seconds a month
- ★ simple to use
- ★ with 12 month guarantee.

Contact **KRAMER & CO.** for details

WE SUPPLY ALL SEIKO WATCHES

We accept govt./company purchase orders on all goods.

KRAMER & CO.

9 October Place, Holders Hill Road
London NW14 1EJ
Telex 888941 Attn Kramer K7
Tel: 01-203 2473

Mail order only SAE for data sheets
Export enquiries welcome

LOW-PRICE CALCULATORS

TEXAS
TI-45 Logs; Trig; 1 memory **£23.50**
SR-51-III Prog—20 steps; Hyperbolic; Rect/Polar; Conversion; Statistics; 10 Memories **£31.75**
TI-57 Prog—50 steps; Logs; Trig; Statistics; 8 memories **£31.75**
TI-58 Prog—480 steps or 60 mems; software module of 25 progs **£78.50**
TI-59 Prog—960 steps or 100 mems; software module; mag card prog **£215.45**
PC-100A Mains printer unit for TI-58/59; Alphanumeric; data plotting **£170.75**

- ★ All prices include VAT and postage
- ★ Calculators complete with AC Adaptor/Charger

MAIL ORDER ONLY
SKAD ELECTRONICS
12 Chalgrove End, Stoke Mandeville
Aylesbury, Bucks.



SKAD
electronics

ETI PCB's

Buy it with Access



Available for all ETI projects from day one of ETI, phone your order

SPECIAL OFFER—Single sided Pax PCB mat, four off, 4½" x 6½", 99p all up

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

NOW!

11 Micro projects for you to build in our new micro box

- ★ M.W. Receiver
- ★ Ultra Sonic Tx
- ★ Heads or Tails
- ★ Electro Magnet
- ★ Metronome
- ★ Signal Injector
- ★ F.M. Tx
- ★ Plant Moisture Unit
- ★ Insect Repeller
- ★ Hunt the Bleep

All these great micro projects will, including batteries into our 60x40x15mm box (you can fit two in this advert).

Just 75p brings all 11 circuits, a Micro Box and a £1 voucher for our lists.

Send to:

M. D. MARKETING

P.O. Box 4, Hinckley, Leicestershire

SPECIAL OFFER

If you can buy the same for less, we will refund the difference. Brand new and full specification pots, transformers, switches, linears, TTL, CMOS, transistors, opto electronics and other semiconductors. Send large SAE for catalogue.

DELTA TECH (E) & CO.
62 NAYLOR ROAD
LONDON N20 0HN

HEXADECIMAL KEYBOARD. High quality keys on fibreglass board, TTL encoded with strobe. £17.50 inc. Individual keys 70p. 2 digit Hex display with latch £9 inc. Sinclair scientific calculators £3.75 inc. SAE for details. Mail order only. LINTRONICS, 313 Green Lane, Ilford, Essex.

SOLARTRON CT436 OSCILLOSCOPE, double beam, DC 6MHZ, 10mv, 240v mains. Full documentation. Telephone (0793) 37461 (Swindon). Offers around £100.

Please mention ETI when replying to Adverts

SPECIAL OFFER: If you can buy the same for less, we will refund the difference. Brand new and full specification pots, switches, transformers, linears, TTL, CMOS, transistors, and other semiconductors. Send large SAE for catalogue. **DELTA TECH (E) & CO., 62 NAYLOR ROAD, LONDON N20.**

OPPORTUNITY to take over profitable established radio component business due to retirement. A capital of only £5,000 required for basic stock. Busy No. London main road. Box No. 61.

AERIAL BOOSTERS improve weak vhf radio and television reception, price £4.50, S.a.e. for leaflets. Electronic Mailorder Ltd., Ramsbottom, Bury, Lancs., BL9 9AG.

THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

MINI-ADS: 31/4" x 21/8", 1-3 £31, 4-11 £29, 12 or more £28 per insertion. CLASSIFIED DISPLAY: 15p per word. Minimum 25 words. No P.O. Box Numbers can be accepted without full address. Enquiries to: Advertising Department, 01-437 5982. 25-27 Oxford Street, London W1R 1RF.

DELTA DISTRIBUTION CO.

75 WILLOWTREE AVENUE, GILESGATE MOOR
DURHAM DH1 1DZ. Tel: (0385) 62760 or 61785

TRANSFORMERS (P/P 35p each)	£
240V 12V (or 6-0-6) 200mA	0.98
220V 12V (or 6-0-6) 200mA	0.86
240V 12V, 12V (or 24) both 250mA	1.95
240V 12V 2A	3.95
VOLTAGE REGULATORS	
LM 342 P-5 +5V 3 pin TO-202 200mA	0.79
LM 342 P-12 +12V 3 pin TO-202/200mA	0.79
LM 342 P-24 +24V 3 pin TO-202-200mA	0.79
LM 317 MP Adjustable 3 pin TO-202 500mA	1.48
ICs	
LM 555 CN Timer 8 DIL	0.33
LM 741 CN-8 Op. Amp 8 DIL	0.27
LM 348 N Quad 741 14 DIL	1.13
HEF 4001 P Quad NOR 14 DIL	0.19
HEF 4011 P Quad NAND 14 DIL	0.19
RESISTORS	
1/2 W 100R to 10M	0.02
CSC BREADBOARD AND TEST EQUIPMENT	
Experimenter 300	6.20
Experimenter 600 (accepts wide chips)	6.55
Logic Monitor LM1	28.40
Logic Probe LP1	30.55
Protoboard 6	9.45
Protoboard 100	11.95
Protoboard PB 203A	72.22
Max 100 (Digital Frequency Meter)	74.95
VEROBX	
71 x 49 x 19mm - Black	0.44

Cash/Cheques/Drafts/P.O.S./ACCESS No. accepted Telephone us with your ACCESS No. for really fast service
Post/Packing 25p unless otherwise stated + VAT 8% (except Export Orders)

TRADE AND EXPORT ENQUIRIES WELCOME MAIL ORDER ONLY

SAVE POUNDS on test equipment with MLC modules and kits. Free data sheets. MLC(E), 116 College Road, Southwater, Horsham, Sussex.

PERSONAL COMPUTING MAGAZINES FOR HOBBYIST AND BUSINESS: Dr. Dobbs, Personal Computing, Creative Computing, ROM — £1.50 (some back issues — £1.25). Byte, Interface Age, Kilobaud — £2.00 (some back issues — £1.50). P&P on any one MAGAZINE — 45p. Microcomputing books also in stock. INTERAM Computer Systems Ltd., 59 Moreton Street, London, SW1 (01-834 0261/2733).

P.C. BOARD OFFCUTS. No small pieces. Approx. 400 sq. in. (2lbs.), £1.60 inc. postage. T.S.E., 6 Ainsworth Road, Swindon SN3 2DJ.

ELECTRONIC KITS.—SAE for new catalogue, and clearance list of obsolete kits.—AMTRON UK, 7 Hughenden Road, Hastings, Sx.

6800 SINGLE BOARD COMPUTER

Features: crystal controlled V.D.U., C.P.U. with memory decoder, CUTS interface 1k user RAM, 1k Mikbug compatible ROM buffered outputs for easy expansion parallel input.

All you need for a working computer is a TV, ASC11 keyboard, tape recorder and P.S.U.

**£185 + VAT
+ £3.24 postage**

Mail order only; see for leaflet

Write to:
HEWITT ELECTRONICS LTD.
95 Blakelaw Road
Macclesfield
Cheshire

MANTELET GAS MONITOR KIT

IDEAL FOR BOATS — CARAVANS — WORKSHOPS, ETC. WILL DETECT MOST INFLAMMABLE GASES AND VAPOURS. SENSITIVITY CAN BE SET FOR VERY SMALL CONCENTRATIONS

Kit includes T.G.S. Head, P.C.B. and all necessary comps. Construction details supplied.

Price kit (less case) **£12.45 inc. VAT.**

Case with punched front plate **£3.60 inc. VAT.**

Send S.A.E. for full details to:

Mantelet Electronics Ltd.
8 The Square, Horndean, Hants

TRS-80? If you have the machine, we have the SOFTWARE. BUSINESS/FINANCE/SCIENTIFIC GAMES, etc. Send SAE for list to GENERAL SOFTWARE, 15 ROCKWOOD AVENUE, CREWE CW2 8LU.

PART BUILT 16 CHANNEL E.T.I. MASTER MIXER, cabinet, pots, 20 meters, 5 band e.g., PCBs, power amp, some wiring, coils, knobs, plans: **NEEDED TO FINISH:** components for 8 pre-amps, 2 mixer PCBs, input sockets. Materials cost £330 will accept **£260 o.n.o. 76 GEORGE ROAD, NEW MALDEN, SURREY. 01-942 9034 after 2000 hrs.**

MICROCOMPUTER I.C.s. New, 2708 EPROM, 1k x 8 450ns, now down to **£7.60.** 21L02 low power RAM, 1k x 1 450ns, **£1.00.** Prices each, inc. postage, etc. **A. C. GIDLOW, 7 Cypress Road, Newport, Isle of Wight PO30 1EY.**

1.2V NICADS

All UK orders over £5 post free, under £5 add 15% All prices include VAT

BUTTON CELLS

	Dia.	Hgt.	Price/Cell
225mAh	25.0	7.5	0.65
600mAh	34.5	10.0	1.15

VENTED CELLS

(for fast change)


			Price
0.45 Ah	17.5	28.0	0.95
0.5 Ah	HP7 or	Size "AA"	1.10
1.2 Ah	22.5	49.0	1.45
1.8 Ah	HP11 or	Size "C"	1.95
2.5 Ah	32.5	43.0	2.35
4.0 Ah	HP2 or	Size "D"	2.50
10.0 Ah	41.5	90.0	5.00
6.0V Pack	5x1.2 Ah nicads		7.50

Tags available at extra 10p per cell for 1.2 Ah and 1.8 Ah nicads only.

Charger — Suitable for any of the above vented nicads — charges up to twelve similar cells in series at a 50mA or 200mA rate **£9.95**

Sizes approx. in mm
Mail order only

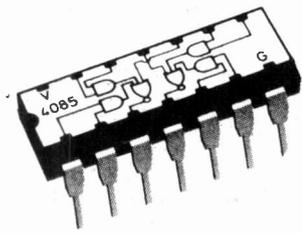V&F SMALLCRAFT (POPLAR) LTD.
38 Stoneleigh Road, Clayhall, Ilford
Essex
01-550 6642



NEW! HOBBY-PACK STICKIES

Professionals worldwide use STICKIES — for building and debugging prototypes, faultfinding — even designing PCB layouts.

Now, for amateurs, comes the **hobby pack — 120 STICKIES for 80p.** Make projects less sweat, more fun. Why not try a pack?

Just to remind you — STICKIES are self-adhesive printed labels which immediately identify pin-outs for a carefully-selected range of 4000- or 7400-series IC's. Also **480-label pack £2.80** (Discounts for quantities). Prices include VAT, p&p. Please state whether TTL or CMOS required. Official orders welcome.

CONCEPT ELECTRONICS
8 Bayham Road, Sevenoaks, Kent O283 514110

100 WATT GUITAR/PA/MUSIC AMPLIFIER

With superb treble, bass, Overdrive, slimline, 12 months guarantee. Unbeatable offer at **£39.** Also twin channel with separate treble/bass per channel **£48.** Money returned if not absolutely delighted within 7 days. Also fuzz boxes great sound robust construction **£6.60.** Also 100 watt 12 in. speakers **£22.60.**

All inclusive of P.P. Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION
82, THORNCLIFFE AVENUE, DUKINFIELD,
CHESHIRE. TEL: 061-344 5007

TROUBLESHOOTING, PROGRAMMING AND DESIGN help offered for 6800 micro-computers especially S68. Also assistance with hardware interfacing and monitor writing (expansion to Z80 soon). 01-960 2042.

CORE MEMORY PLANES, ex-equip, without drive circuits, 4K (64x64) per plane, 99p each plus 25p p&p, £7.50 post free for 8, £12 post free for 12. G. Langley, 31 Bakers Lane, Woodston, Peterborough.

COMPONENT BARGAINS

741 I.C.s	25p each	£1.00/5
555 I.C.s	30p each	£1.25/5
7404 I.C.s	12p each	50p/5
7475 I.C.s	30p each	£1.25/5
7490 I.C.s	35p each	£1.50/5
74141 I.C.s	50p each	£2.00/5
Diodes IN4148	3p each	25p/10
IN4001	4p each	30p/10
IN4004	5p each	40p/10
Zeners 400mW 5v1, 5v6, 12v	10p each	
5v 600mW Voltage regulators	90p each	
100v 2 Amp Bridge rectifiers	40p each	
Transistors BC107	9p each	80p/10
2N3055	50p each	
0.2" Red L.E.D.s with holder	10p	
1mH R.F. chokes	10p each	85p/10
10 way ribbon cable	50p/m	£4.50/10m
100µA Meters 2 1/2" x 1 1/4"		£3.85
DIL Sockets 14 pin		£12p
16 pin		13p
FND500 7 segment L.E.D. displays		£1.30
Soldercon I.C. Socket Pins		50p/100

Prices include VAT. P&P 20p per order

Stephen Instrumentation
49 Hucknall Avenue
Ashgate, Chesterfield
Derbyshire S40 4BZ

The Reynard The Fox
HEIGHT OF KING 7/8
Chess Pieces



RETAILS IN SHOPS FOR APPROX. £50.00. BUY NOW AND SAVE

G.I. CK3000 **BIMDRILL**
4 Digit Alarm Clock **MAINS POWERED**
I.C. → PLASMA DISPLAY **7500 R.P.M.** **£12.95**
Complete with 3 Cells

Features:

- 12 Hour clock, 24 Hour alarm setting
- AM/PM indication
- 50 or 60 Hz operation
- Snooze (Sleep-over) alarm
- Direct display driving
- CK3000-Plasma
- No display interface components
- Seconds flashing colour
- Alarm, set, and snooze medication
- Power interrupt indication
- Low current consumption
- Alarm output line — direct drive with magnetic speakers

ONLY £4.90 I.C. AND DISPLAY

Many uses — ideal p.c.b. drilling

CHEQUE P/O's TO **N.I.C. MODELS** (Mail Order)
27 SIDNEY ROAD, LONDON N22
OTHER CHESS SETS AND BOARDS AVAILABLE — 15p ILLUSTRATED LISTS

ALLOW UP TO 21 DAYS FOR DELIVERY

Situations Vacant

COMMODORE SYSTEMS DIVISION need an experienced digital engineer to be responsible for the service of their 6502 based PET Computer. The position is London based, conditions are excellent and salary is negotiable. Please contact Mr. Roe on 01-388 5702. We will also require a technician to assist the above on the same equipment. Salary for this position is dependent on age and experience.

FIELD SERVICE ENGINEERS

Enthusiastic people with knowledge of electronics required to service Video Games.

We are a nationwide Company looking for people capable of working on their own initiative within a small team. In return we offer good prospects, private use of company vehicle (a clean driving licence is essential) and a salary circa £3000 p.a. depending on age and experience.

There is an immediate vacancy in Central London, but, as we are expanding very rapidly we would be interested in hearing from applicants in all areas.

Phone **Derrick Morgan** or **John Brown** on 01-459 2236, or write to: **Cherry Leisure (UK) Ltd., 387 High Road, Willesden, London NW10 2JR.**

ADVERTISEMENT INDEX

Ace	65	LB Electronics	94
Advanced Computer Products	55	LP Enterprises	13
Airamco	74	Lotus Sound	86
Almarc	22		
Ambit	6	Maplin	100
Astra-Pak	85	Marshalls	14
Audio Electronics	22	MD Marketing	85
		Metac	95
Bamber	90	Micronics	78
Baydis	65	Minikits	74
Bi-Pak	4, 5, 90	Mountandene	74
Brewster S&R	80		
		Nicholls	86
Cambridge Learning	65		
Chiltmead	21	Osmabet	86
Chromasonics	73		
C. N. Stevenson	32	Powertran	2
Communications Mea	74, 94	Progressive Radio	94
Computer Marketing	81		
Crimson Elektrik	22	RE Equipment	84
Doram	38, 73, 95	Science of Cambridge	66
EDA	73	Service Trading	88
Edinsmith Computer Services	56	Suntel	37
Electrovalue	84	Sterling Sound	92
		Strathand Sec	92
Fladar	95	Swanley	32
Flairline	93		
		Tamtronik	72
Greenbank	82	Technomatic	60
Greenweld	56	Teleplay	81, 99
		Tempus	29, 93
Henrys	32, 82, 85	TK Electronics	93
ILP	43	T. Powell	93
Integrated Circuits Ltd	59	Trampus	62
Jayen	86		
		Vero Electronics	72
Kramer	86, 94	Videotime	60
		Watford	8, 9
		Wilmslow Audio	93

Mini-Ads pages 96, 97 and 98

Teleplay now presents COLOURSTARS WITH FREE STAR OFFERS

A whole library of easy to assemble cartridge games for you and all the family to enjoy
 - all in full colour - works OK on Black and White TV
 - will save you pounds in the long run.

Our INTRODUCTORY OFFER consists of a bargain that cannot be snuffed at - a Kit consisting of a Professional Finished Inject Moulded Box - Joystick Hand Controls - one cartridge on which consists of 10 games - Football, Tennis, Solo Squash (1 & 2 players), Hockey, Basketball (1 & 2 players), Shoot etc. Mains Adaptor. All holes are pre-drilled - No Special equipment required. You'll be surprised how easy it is to assemble this superbly enjoyable kit!

We offer
 all this to you
 for ONLY
£28-90
 inc. VAT and P&P.
 Fully Assembled
 Add £7.00

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.

Additional Cartridges NOW available include:
 Stunt Cycle - 4 games - Cartridge and Hand Controls - £14.90
 Tank Battle - Cartridge and Hand Controls - £15.90
 Road Race - 2 games - Cartridge - Controls already with basic kit - £12.90

Watch this page each month for new cartridges, as they become available.

Electrical knowledge is not a necessity to assemble this project - just simple soldering.

Cheques and Postal Orders to be made payable to TELEPLAY: send your order (No Stamp Needed) to Teleplay, Freepost, Barnet, EN5 2BR or telephone your order quoting your Barclaycard or Access number. Queries and Technical Advice offered either by phone or by calling at our shop.



SHOP OPEN - 10am to 7pm - Monday to Saturday

CLOSE TO NEW BARNET BR STATION - MOORGATE LINE



All parts fully guaranteed.

EUROPE'S LARGEST STOCKIST OF TV GAME COMPONENTS.

teleplay

14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922


MAPLIN

everything for the modern D.I.Y. electronics enthusiast and more.



THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists... an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £65 including smart leak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES49, price 25p.

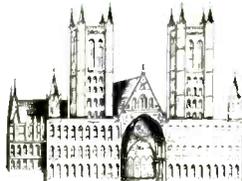

REVERBERATION SYSTEMS

High quality spring line driver module uses 4 integrated circuits and two transistors. Built and tested circuit board with wiring instructions for spring line. XB85G, price £6.00. Power supply to suit drive module costs around £2.50 and construction details are in catalogue, or ask for leaflet MES24. Mechanical spring lines: Short line (XL08J) £4.49; Long line (XB84F) £10.39. (All prices include V.A.T. and p. & p.)



BOARDS AND PCB'S

Pages 59 to 61 of our catalogue show you our range of Veroboard and S-Decs or if you prefer to make your own PCB's a range of etching systems including the novel etch-in-a-bag system, plus printed circuit transfers for the professional finish to your boards.




9-CHANNEL RADIO CONTROL SYSTEM

A comprehensive model control system, featuring nine independent fully proportional channels achieved by a design using very few components thus keeping the cost to a minimum. Full construction details in our booklet (XF030) price £1.20.



AUDIO MIXER

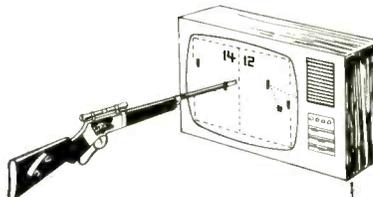A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.




T.V. GAME

A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 25p. Add on rifle kit only £10.60. (All prices include V.A.T. and p.&p.)




MASSIVE RANGE OF COMPONENTS

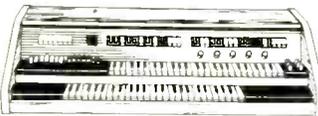For instance the capacitor section in our catalogue includes non-polarised electrolytics and our resistor section includes even 1% tolerance types. Get our fascinating catalogue now - you won't regret it.



ELECTRONIC ORGAN

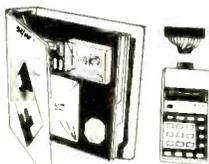The only organ you can build in stages and tailor to your requirements as you go along - and at each stage you'll have a fully working instrument! We haven't got the gimmicks yet - (they're coming soon) but we have got the most beautiful sounds - you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



MICROPROCESSOR

Build a mini-computer with our microprocessor kit. Features: 46 different instruction types; 256 bytes of read/write memory (more are easily added); microprocessor can address up to 65,536 8 bit bytes. Complete kit for use with teletype etc. (XB91Y) £74.10. 20-key keyboard for use with above (in place of teletype) (XB92A) £71.11. Both kits with detailed instruction books. See our newsletter for details of additional RAM's, tri-state interfacing chips, number-cruncher and standard cassette tape-recorder interface to store your programmes. (All prices include V.A.T. and p. & p.)



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately

NAME

Neal Crook

ADDRESS

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157