

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

July 1983 85p

GET A PERMANENT WAVE! Use Your TV As A Storage Scope

NEW PROJECTS

MULTIPLE
FLASH UNIT FOR
PHOTOGRAPHERS

PORTABLE
INDUCTION LOOP

MICROCOMPUTER
OUTPUT DRIVER



**EIGHT PAGES
OF TECH TIPS
Readers' Designs
Galore!**

...AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS...

Star sounds ** Star quality ** Star features **

Free
SECURICOR
DELIVERY
on all orders over
£100 (UK mainland
only) Add just £2.50
on lower price
orders



DJ90 Stereo Mixer — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything the whole works — AND — under £100 complete! Complete kit £97.50 + VAT



This versatile modular mixer, featured as a construction article in Practical Electronics can be built up to a maximum of 24 inputs, 4 outputs and an auxiliary channel. Each input channel has Mic and Line inputs, variable gain, bass and treble controls and a parametric middle frequency equalizer. There are send and return jacks, auxiliary, pan and fader controls and output and group switching. The output channels have PPM displays and record and studio outputs. The auxiliary channel also has a PPM display and there is a headphone monitor jack and a built-in talk-back microphone. The mixer modules plug into base units each of which takes up to 6 channels. To eliminate hum, the power supply is in a separate cabinet.

KIT PRICES

Input channel	£19.90	Base unit and wooden front	£27.50
Output channel	£18.50	Pair of mahogany end cheeks	£12.50
Auxiliary channel	£22.50	Power Supply and cabinet	£19.50
Blank Panel	£3.00		

All prices are VAT exclusive

TRANSCENDENT POLYSYNTH — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.

Complete kit £275.00 plus VAT (single voice)
Extra voice (up to three more) £42.00 plus VAT



TRANSCENDENT 2000 — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it — play it! You will know you have made the right choice.

Complete kit £165.00 + VAT



BIG NEWS
ABOUT OUR
LATEST
ADVANCES IN
ROBOTICS
SEE INSIDE
BACK COVER

SALES
COUNTER
Contact your order
from the factory.
Open 9-12 1-4.30
Mon-Thurs. Easy
parking, no
waiting

Digital Delay Line — With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo &



vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB.

Compare with units costing over £1,000!

Complete kit (400 mS delay)

£130 + VAT

Parts for extra 400 mS delay

£9.50 + VAT

Free Soldering
Practise Kit on
request with your
first kit — useful
tips, well
illustrated.

MPA 200 — is a low price, high power 100W amplifier, its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first time builder. Complete kit £49.90 + VAT.
Chromathec 5000 — a 5 channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single board design. Complete kit £49.50 + VAT

ETI VOCODER — 14 channels, each with independent level control, for maximum versatility and intelligibility. Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual is within the capability of most enthusiasts. Complete kit £175.00 + VAT

SP2 200 twice the power with two of the reliable, durable and economic amps from the MPA 200; fe 4 cy separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over) the standard of high prices factor-built units! Complete kit £64.90 + VAT



Component
packs for most
kits are available
See our great free
catalogue, full
details of all
our range

WORLD
LEADERS
IN
ELECTRONIC
KIT DESIGN
AND SUPPLY

PORTWAY INDUSTRIAL ESTATE

ANDOVER, HANTS SA10 3NM.

ORDER BY PHONE (0264) 64455

Simply request your chosen kit and quote your Access or Barclaycard Number.

electronics today

INTERNATIONAL

JULY 1983 VOL 12 NO 7



Dave Bradshaw: Editor
Peter Green: Deputy Editor
Phil Walker: Project Editor
Jerry Fowler: Technical Illustrator
David Kitchener: Advertisement Manager
Joanne James: Assistant Advertisement Manager
Ron Harris B.Sc: Managing Editor
T.J. Connell: Managing Director

PUBLISHED BY:
 Argus Specialist Publications Ltd.,
 145 Charing Cross Road, London WC2H 0EE.

DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd.,
 12-18 Paul Street, London EC2A 4JS
 (British Isles)

PRINTED BY:
 QB Limited, Colchester
COVERS PRINTED BY:
 Alabaster Passmore.

OVERSEAS EDITIONS and their EDITORS
 AUSTRALIA — Roger Harrison
 CANADA — Halvor Moorshead
 GERMANY — Udo Wittig
 HOLLAND — Anton Kriegsman



Member of the
 Audit Bureau
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription Rates. UK £13.15 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.

EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5.
 Telex 8811896.

FEATURES

- | | |
|--|--|
| DIGEST 11 | CONFIGURATIONS 57 |
| We've waded through several tons of waste paper (ie, press releases) to bring you this month's news. | Here's Ian Sinclair's swansong for this popular series, devoted to simple logic gates, AND, OR, and NOT. |
| BUYER'S GUIDE TO 'SCOPES . . . 34 | AUDIOPHILE 76 |
| If you're not inclined to build our TeleScope project, but you still want to know what's really going on in your circuits, then this guide could be handy. | Vivian Capel guest-writes our regular (well nearly regular) audio spot to tell us about Holophony. Holoadawhat? You'd better see what he has to say, hadn't you? |
| TECH TIPS SPECIAL 42 | READ/ WRITE 81 |
| Eight pages of pure genius from the country's (possibly the world's) largest design team — yourselves! | FEVAs and the Real Time Clock have both received a fair amount of your attention of late. |

PROJECTS

- | | |
|--|--|
| TELESCOPE 21 | FLASH SEQUENCER 63 |
| In true ETI tradition, a fabulous project with an appalling pun for a name (TELEvision oscilloSCOPE, geddit?). | Ever wondered what equipment photographers use to get multiple exposures? Here's ETI's answer, in hardware, just as you'd expect. |
| OUTPUT DRIVER 28 | FLASH TRIGGER 70 |
| In our continued campaign against microcomputers that just sit there and do nothing (or, even worse, play silly games), a project to get your micro to flex its muscles. | This can be used on its own or with the Flash Sequencer, as you please; it does exactly what it says — triggers flashes, from sound or light, or from an infra-red beam. |
| PORTABLE INDUCTION LOOP . . . 52 | SWITCHED MODE PSU 83 |
| Vivian Capel's article on Induction Loops in February raised quite a lot of interest, so here's a practical design. | Constructional details of the switched mode PSU commenced last month. |

INFORMATION

- | | |
|---------------------------------------|----------------------------------|
| NEXT MONTH'S ETI 7 | READER SERVICES 86 |
| BREADBOARD EXHIBITION . . . 20 | ETI PCB SERVICE 91 |
| THERMETER UPDATE 20 | ETI BOOK SERVICE 93 |

SWITCHES

TOGGLE 2A, 250V	44p
SPST	33p
DPDT	44p
SUB-MIN TOGGLE	
SPST on/off	54p
SPDT c/o/over	80p
SPDT centre off	80p
SPDT biased both	106p
DPDT 6 tags	78p
DPDT centre off	80p
DPDT biased both	148p
DPDT 3 positions on/off	185p
3 pole 2 way	208p
SLIDE 250V:	
DPDT 1A	14p
DPDT 1A c/o	15p
DPDT 1/2A	13p

PUSHBUTTONS

With 10mm Button	99p
SPDT latching	148p
DPDT latching	148p
SPDT moment	99p
DPDT moment	148p
Mini Non Locking	18p
Push to Make	18p
Push to Break	25p

ETI PROJECTS

We stock most of the parts	
JUMPER LEADS (Ribbon Cable Assembly)	
Length	14 pin 16 pin 24 pin 40 pin
Single ended DIP (Header Plug) Jumper	14p 16p 24p 30p
Double ended DIP (Header Plug) Jumper	14p 16p 24p 30p
6 inches	185p 205p 300p 485p
12 inches	198p 218p 315p 498p
24 inches	210p 235p 345p 540p
36 inches	230p 250p 375p 585p
IDC Female Header Socket Jumper Leads 36"	
Single ended	20 pin 26 pin 34 pin 40 pin
Double ended	180p 200p 280p 300p
	290p 370p 480p 525p

TRANSFORMERS:

3-0-3V, 0-0-4V, 9-0-9V, 12-0-12V, 15-0-15V	100mA	12p
pcb mounting, Miniature, Split Bobbin		
3VA: 2x0V-0.25A, 2x0V-0.15A, 2x12V-0.12A		22p
2x15V-0.1A		25p
6VA: 2x0V-0.5A, 2x0V-0.3A, 2x12V-0.25A		27p
2x15V-0.2A		27p
Standard Split Bobbin type:		
6VA: 2x0V-0.5A, 2x0V-0.3A, 2x12V-0.25A		22p
12VA: 2x0.5V-1.3A, 2x0V-1A, 2x9V-0.6A, 2x12V-0.5A, 2x15V-0.4A, 2x20V-0.3A		25p
24VA: 2x0V-1.5A, 2x9V-1.2A, 2x12V-1A, 2x15V-0.8A, 2x20V-0.6A		33p (160p p/p)
30VA: 2x0V-2A, 2x9V-1.5A, 2x12V-1.2A, 2x15V-0.8A, 2x20V-1A, 2x25V-0.8A		40p (160p p/p)
Specialty wound for Multirail Computer PSUs		
50VA Outputs: -5V/5A, +12V, -15V, -5V, -12V at 1A		575p (250p p/p)
100VA: 2x12V-4A, 2x15V-3A, 2x20V-2.5A, 2x25V-2A, 2x30V-1.5A, 2x50V-1A		820p (160p p/p)
p/p charge to be added over and above our normal postal charge.		

CMOS

4000	10	4075	13	4841	140
4001	10	4076	13	4543	70
4002	10	4077	13	4544	180
4003	10	4078	13	4545	60
4006	60	4081	13	4549	370
4007	14	4082	13	4553	240
4008	32	4085	50	4554	180
4009	34	4086	50	4555	35
4010	24	4093	125	4556	35
4011	10	4094	20	4557	320
4012	16	4095	70	4558	120
4013	20	4096	70	4559	385
4014	48	4097	280	4560	180
4015	48	4098	75	4561	104
4016	20	4099	110	4562	108
4017	32	4100	85	4563	280
4018	45	4101	85	4564	175
4019	25	4102	85	4565	30
4020	42	4103	85	4566	280
4021	40	4104	85	4567	280
4022	40	4105	85	4568	280
4023	13	4106	105	4569	80
4024	32	4107	105	4570	80
4025	13	4108	790	4571	80
4026	80	4109	790	4572	80
4027	20	4110	725	4573	330
4028	38	4111	675	4574	280
4029	45	4112	775	4575	280
4030	16	4113	480	4576	42
4031	125	4114	280	4577	42
4032	80	4115	770	4578	215
4033	125	4116	850	4579	140
4034	140	4117	980	4580	175
4035	45	4118	4450	4581	175
4036	275	4119	4450	4582	85
4037	115	4120	4450	4583	85
4038	110	4121	4500	4584	85
4039	280	4122	4501	4585	85
4040	40	4123	4502	4586	85
4041	40	4124	4503	4587	85
4042	40	4125	4504	4588	85
4043	40	4126	4505	4589	85
4044	40	4127	4506	4590	85
4045	105	4128	4507	4591	85
4046	105	4129	4508	4592	85
4047	40	4130	4509	4593	85
4048	40	4131	4510	4594	85
4049	25	4132	4511	4595	85
4050	25	4133	4512	4596	85
4051	45	4134	4513	4597	85
4052	80	4135	4514	4598	85
4053	80	4136	4515	4599	85
4054	85	4137	4516	4600	85
4055	85	4138	4517	4601	85
4056	85	4139	4518	4602	85
4057	1915	4140	4519	4603	85
4058	435	4141	4520	4604	85
4059	435	4142	4521	4605	85
4060	45	4143	4522	4606	85
4061	1185	4144	4523	4607	85
4062	885	4145	4524	4608	85
4063	85	4146	4525	4609	85
4064	34	4147	4526	4610	85
4065	245	4148	4527	4611	85
4066	14	4149	4528	4612	85
4067	14	4150	4529	4613	85
4068	14	4151	4530	4614	85
4069	14	4152	4531	4615	85
4070	13	4153	4532	4616	85
4071	13	4154	4533	4617	85
4072	13	4155	4534	4618	85
4073	16	4156	4535	4619	85

OPTO

LS400C	255
OCF71	120
ORP12	80
ORP61	85
2N5777	45
BP225	185
BP221	185
BP225	270
REFLECTIVE	
Switch type TIL139	Optical
SLOTTED	Optical
Switch similar to RS	185p
Comp. 's	185p

VEROBOARD

0.1in	185p
clad plain	395p
2 1/2 x 3 1/2	85p
2 1/2 x 5	100p
3 1/2 x 5	100p
3 1/2 x 11	115p
3 1/2 x 17	200p
4 1/2 x 17	275p
Pkt. of 100 pins	55p
Spot face cutter	185p
Pin insertion tool	185p

VERO WIRING

Pen + spool	340p
Spare spool	75p
Combs	6p

FERRIC CHLORIDE

1 lb bag Anhydrous	195p
+ 50P P&P	

COPPER CLAD BOARDS

Fibre glass	Single sided	Double sided	S.R.P.
6 x 6	100p	125p	9.5 x 8.5
6 x 12	175p	225p	

DIL SOCKETS

Pin	Low	Wire
8pin	8p	25p
14pin	10p	35p
16pin	10p	42p
18pin	10p	42p
20pin	20p	80p
22pin	20p	80p
24pin	25p	70p
26pin	25p	80p
40pin	30p	95p

EDGE CONNECTORS

2 x 15 way	140p
2 x 18 way	145p
2 x 22 way	180p
2 x 23 way	175p
2 x 26 way	225p
2 x 28 way	190p
2 x 30 way	245p
2 x 36 way	295p
2 x 40 way	315p
2 x 45 way	395p
2 x 75 way	550p

ANTEX SOLDERING IRON

C-15W	495p	CS17W	495p
G18W	520p	XS25W	525p
Spare tips, assorted sizes			85p
Spare elements			225p
Iron Stand with sponge			175p

ALUM BOXES

3 x 2 x 1"	85p
4 x 2 x 2"	105p
4 x 2 x 2 1/2"	105p
4 x 4 x 2"	120p
5 x 4 x 1"	80p
5 x 4 x 2"	120p
5 x 2 x 2"	80p
5 x 2 x 2 1/2"	130p
6 x 4 x 2"	120p
6 x 4 x 3"	180p
7 x 5 x 3"	210p
8 x 6 x 3"	210p
10 x 4 x 3"	275p
10 x 7 x 3"	280p
12 x 6 x 3"	280p
12 x 8 x 3"	285p

OPTO ELECTRONICS

LEDs with Clips	10
TL209 Red	10
TL211 Grn	14
TL212 Yel	14
TL220 2" Red	12
2" Green, Yellow or Amber	14
0.2" Bi colour	85
Red/Green	85
Green/Yellow	85
0.2" Tri colour	85
Red/Green/Yellow	85
Hi-Brightness Red	85
Flashing red	85
0.2" red	85
Square LEDs, Red, Green, Yellow	30
Rectangle Stackable LEDs	40
Red, Green or Yell Triangular LEDs	18
Red	18
Green or yellow	22
LD271 Infra Red	46
SF205 Detector	118
TL32 Infra Red	68
TL78 Detector	80
TL138	45
TL100	80
BARGRAPH, Red 10 segments	225
ISOLATORS	
IL74	95
IL074	95
IL074	185
TL111/2/4	80
TL117	125
4N33 Photo Darlington	135
7 Segment Displays	
TIL312 3" CA	105
TIL313 3" CC	105
TIL321 5" CA	115
TIL322 5" CC	115
DL704 3" CC	80
DL707 3" CA	80
FND357 Red	120
FND500	115
3" Green CA	215
3" Green CA	180
3" x 1 Red CA	180
3" x 1 Green CA	180
DVM176	22
LC0 34 Digits	485
LC0 4 Digits	530
LC0 6 Digits	625
PN DIODE	
SD4478-002	810p
REFLECTIVE	
Switch type TIL139	Optical
SLOTTED	Optical
Switch similar to RS	185p
Comp. 's	185p

COMPUTER CORNER

- EPSON FX80 PRINTER, 10" 160 cps, Tractor/Friction feed, Bi-directional, logic seeking, 9 x 11 matrix, Hi-res bit image, normal, italic & Elite car. Super & Superscript, proportional spacing, underlining, 2K buffer. £395 (£7 carr)
- MX100 EPSON Printer, 136 Column, 15" carriage, plus all the features of MX80FT/3. Only £425 + carr.
- SEIKOSHA GP100A, 10" Tractor Feed, 80 Colmn, 30CPS, Normal and Double Width Char. Dot Res Graphics. £175 (£7 carr)
- SEIKOSHA GP250X, 10", 50 CPS, Normal and Double width and height Char. RS232 and Centronix Infr. standard £240 (£7 carr)
- Printer Cable for our printers and BBC. £12
- SOFTY II, An intelligent Erom Programmer and Emulator. Accepts a 24 pin 5V Erom. Has Memory Map TV Display, RS232 and Centronics I/P & O/P. Copies, Emulates and programs. RS 232 and centronics routines standard. PSU included. £169
- TEX EPROM ERASER Erases up to 32 ICs in 15-30 minutes. £33
- TEX EPROM ERASER with a safety switch. £36
- TEX EPROM ERASER plus our Solid State ELECTRONIC TIMER. £44
- ELECTRONIC TIMER, Solid state, 15-30 min. Connects directly to above Erasers. Protects your expensive Chips from overcooking. Our timer pays for itself in no time. £15
- SPARE 'UV' Lamp bulb. £8
- POWER SUPPLY, Regulated with Overload protection. Variable Output, 5V to 15V at 4A. Professionally finished. £38
- MULTIRAIL POWER SUPPLY KIT, Especially designed for Micros. Tested output: +5V/5A; +12V; +25V; -12V of 1A £37
- C12 COMPUTER GRADE CASSETTES in library cases. 40p
- 8 1/2" & 9 1/2" Fan Fold paper (1000 sheets). £7 + 150p carr

FLOPPY DISC DRIVES TEAC (BBC Compatible)

- FD50A - Uncased Single, 40 track, 5 1/4", S/S, 100K £130
- CS50A - Single Cased with PSU, 40 track, 5 1/4" S/S 100K £180
- CD50A - Twin Cased with PSU, 40 Track, 5 1/4" S/S 200K £350
- CS50E - Single Cased with PSU, 80 Track, 5 1/4" S/S 200K £250
- CD50E - Twin Cased with PSU, 80 track, 5 1/4" S/S 400K £475
- CS50F - Single Cased with PSU, 80 track, 5 1/4" D/S 400K £330
- CD50F - Twin Cased with PSU, 80 track, 5 1/4" D/S 800K £599
- MITSUBISHI SLIM LINE: Uncased, Double track, Double Density One Megabytes. 5 1/4". Track Density 96TPI, Track to track access time 3mSec. £225
- Drive Cables for BBC. Single £8; Double £12
- 10 Verbatim Diskettes 5 1/4" S.S.D. (5 yrs warranty). £20
- 10 Verbatim Diskettes 5 1/4" D.S.D. (5 yrs warranty). £30
- 10 Verbatim Diskettes 8" S.S.D. (5 yrs warranty). £28

N.B. Carriage is extra on all Disk Drives and Peripherals

IDC CONNECTORS

	PCB Plug with latch	Female Header Plug	Female Card Edge Connect
	Pins Start	Pin Angle	
10 way	80p	85p	120p
16 way	130p	160p	110p
20 way	145p	185p	125p
26 way	175p	200p	180p
34 way	205p	230p	185p
40 way	230p	260p	180p
50 way	235p	270p	200p
60 way	—	—	230p

electronics today

INTERNATIONAL

NEXT
MONTH

THE "MARVIN" MICROCONTROLLER

The microprocessor is so strongly identified with the micro-computer that most people forget that it started life as an industrial control device. We haven't forgotten, though: next month we present a multi-purpose Z80-based control computer that you can use for a wide variety of domestic, laboratory or industrial control functions. The system is modular, consisting of an MPU board and two types of interface board, and a variety of control boards will be available.

I think you should know I'm feeling very depressed.

GRAPHIC EQUALISER


The circuit diagram in the March '83 Audiophile has led to so much interest that we've decided to publish it as a full project. The unit is a very high quality device offering one-third octave

intervals, as required for professional applications, and an impressive noise and distortion performance. For reasons that will be obvious when you see the size of the thing, this is a mono unit; two are required for stereo.

EPROM PROGRAMMER

Hands up all those readers who'd prefer the convenience of programs stored in EPROM, but are put off by the sheer inconvenience caused by erasure and programming difficulties. Next month's ETI will feature a project that is cheap to build and capable of blowing every single-supply EPROM in the 27- and 25-series up to and including 256K bit devices. The appropriate driving software for 6502-based computers will also be provided.

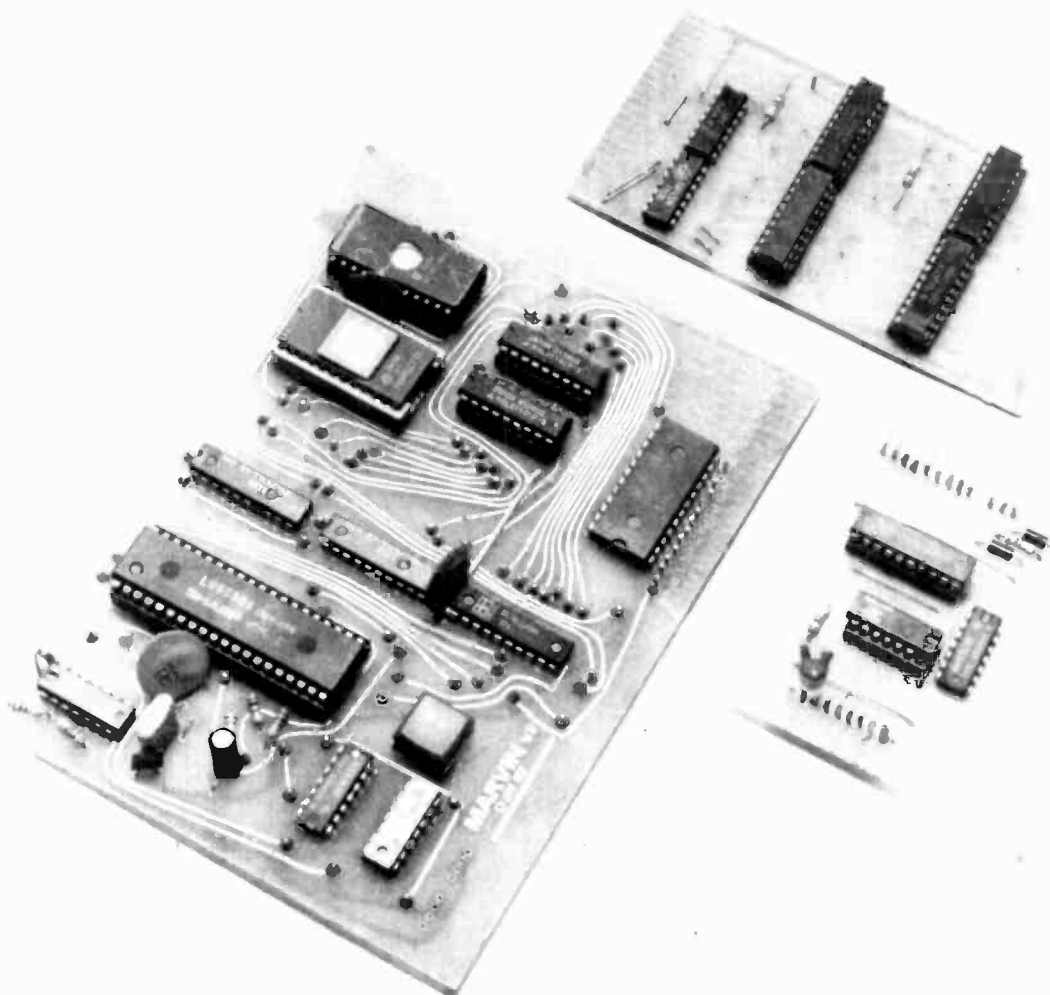LOOK OUT FOR THE AUGUST ISSUE
ON SALE JULY 1st



Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.

CRICKLEWOOD ELECTRONICS LTD.

40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET. Tel: 01-452 0161. TELEX: 914977 CRICKEL G

SUPERIOR QUALITY CARBON FILM RESISTORS H.T.B. LOW NOISE

1W 10% 100Ω 5% E24	2p
1W 10% 100Ω 5% E24	2p
1W 10% 100Ω 5% E12	1p
1W 10% 100Ω 5% E12	1p

METAL DRIDE FILM RESISTORS

Very high thermal & electrical stability. Extremely low noise	
0.4W 10% 100Ω 5% E24	2p
0.4W 10% 100Ω 5% E24	2p

LOW OHMIC VALUE RESISTORS

0.22Ω to 2.2Ω E12	1p
0.22Ω to 2.2Ω E12	1p

WIRE WOUND RESISTORS

1W 0.22Ω 330Ω E12	2p
1W 0.22Ω 330Ω E12	2p

LOW NOISE RESISTORS

1W 0.22Ω 330Ω E12	2p
1W 0.22Ω 330Ω E12	2p

MINI MICRO 100V CERAMIC PLATE CAPS

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

SIEMENS 83V MINI MULTIMETER

100V 1000pF	1p
100V 1000pF	1p

Veroboard 1" Copper clad

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

Grade One Single Sided

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

Ferric Chloride Etch Resist

1" x 12" x 0.0625"	1p
1" x 12" x 0.0625"	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

1000VDC 1000pF	1p
1000VDC 1000pF	1p

1000VDC Caps

CRICKLEWOOD — STOCKING OTHER STORES CANNOT REACH!

Items not fully covered on this list include: OPTO 7 seg LEDs, LCDs bezzelled LEDs, Lamps, Lampholders, FUSES: 20mm 1 1/2 inch, slow or quick blow. Fuseholders. CONNECTORS: DIL DIN SWITCHES: Toggle, Biased, Rocker, Rotary, Slide, DIL, Push. METERS: LCD, Analogue. Test and Panel. TOOLS: Pliers, Cutters, Strippers, Trimmers, Cable Cutters. And much, much more. All in stock items (that's 95%) posted same day. OFFICIAL ORDERS FROM SCHOOLS, GOVT DEPTS ETC WELCOME OVERSEAS ORDERS WELCOME (CWO + ADEQUATE POSTAGE). QUANTITY DISCOUNTS BY NEGOTIATION. CRICKLEWOOD ELECTRONICS LTD., 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET. TEL: 01-452 0161. Telex 514977

★ THE LAZY WAY Phone your order through on Access, Barclaycard, Visa or American Express for immediate service; no extra charge, no minimum order.
★ THE TRADITIONAL WAY Send cheque, PO or credit card number. Cash not encouraged but accepted (no coins please). All in stock items shipped same day.
★ THE IDEAL WAY Call in and collect. We are on the main Edgware Rd (A5) just 1 1/2 miles from Staples Corner and approx 3 miles from Marble Arch.
VAT Please add VAT at the current rate to all orders except books. VAT not chargeable abroad.
POST, PACKING & INSURANCE Standard small order charge is 70p (more for heavier goods). Export orders minimum £1.50.

44p	IN1192	1.75	8 amp type	GLASS FUSES	100mA 5Amp	1.45	MC3340	1.45	TDA1004	2.87	74159	75p	74LS280	50p	74C164	1.15	4553	2.30	2804UMA	6.75	10 00MHz	1.75
67p	IN1194	1.85	Square with hole	100mA 10Amp	1.45	NE543N	2.50	TDA1010A	2.87	74160	40p	74LS281	40p	74C165	2.00	4555	2.30	2804PIO	2.70	10 00MHz	1.80	
60p	IN1194A	1.80		State value in	1.45	NE544N	1.95	TDA1012	4.15	74161	40p	74LS282	40p	74C166	2.00	4556	2.30	2804S	2.70	20 00MHz	1.80	
62p	IN1196A	2.41	PV01 (100)	amps and we will	1.45	NE555	1.6p	TDA1014	1.19	74162	40p	74LS283	40p	74C167	2.00	4557	2.30	2804T	2.70	20 00MHz	1.80	
78p	IN1197A	2.86	PV02 (200)	supply nearest	1.45	NE556	45p	TDA1016	3.28	74163	40p	74LS284	40p	74C168	2.00	4558	2.30	2804V	2.70	20 00MHz	1.80	
30p	IN1201A	1.75	PV04 (400)	to above	1.45	NE557	45p	TDA1018	2.75	74164	40p	74LS285	40p	74C169	2.00	4559	2.30	2804W	2.70	20 00MHz	1.80	
30p	IN1204A	1.00	PV06 (600)		1.45	NE558	45p	TDA1020	2.75	74165	40p	74LS286	40p	74C170	2.00	4560	2.30	2804X	2.70	20 00MHz	1.80	
54p	IN1206	1.20			1.45	NE559	45p	TDA1022	2.75	74166	40p	74LS287	40p	74C171	2.00	4561	2.30	2804Y	2.70	20 00MHz	1.80	
54p	IN1208	1.20			1.45	NE560	45p	TDA1024	2.75	74167	40p	74LS288	40p	74C172	2.00	4562	2.30	2804Z	2.70	20 00MHz	1.80	
54p	IN1210	1.20			1.45	NE561	45p	TDA1026	2.75	74168	40p	74LS289	40p	74C173	2.00	4563	2.30	2804A	2.70	20 00MHz	1.80	
54p	IN1212	1.20			1.45	NE562	45p	TDA1028	2.75	74169	40p	74LS290	40p	74C174	2.00	4564	2.30	2804B	2.70	20 00MHz	1.80	
54p	IN1214	1.20			1.45	NE563	45p	TDA1030	2.75	74170	40p	74LS291	40p	74C175	2.00	4565	2.30	2804C	2.70	20 00MHz	1.80	
54p	IN1216	1.20			1.45	NE564	45p	TDA1032	2.75	74171	40p	74LS292	40p	74C176	2.00	4566	2.30	2804D	2.70	20 00MHz	1.80	
54p	IN1218	1.20			1.45	NE565	45p	TDA1034	2.75	74172	40p	74LS293	40p	74C177	2.00	4567	2.30	2804E	2.70	20 00MHz	1.80	
54p	IN1220	1.20			1.45	NE566	45p	TDA1036	2.75	74173	40p	74LS294	40p	74C178	2.00	4568	2.30	2804F	2.70	20 00MHz	1.80	
54p	IN1222	1.20			1.45	NE567	45p	TDA1038	2.75	74174	40p	74LS295	40p	74C179	2.00	4569	2.30	2804G	2.70	20 00MHz	1.80	
54p	IN1224	1.20			1.45	NE568	45p	TDA1040	2.75	74175	40p	74LS296	40p	74C180	2.00	4570	2.30	2804H	2.70	20 00MHz	1.80	
54p	IN1226	1.20			1.45	NE569	45p	TDA1042	2.75	74176	40p	74LS297	40p	74C181	2.00	4571	2.30	2804I	2.70	20 00MHz	1.80	
54p	IN1228	1.20			1.45	NE570	45p	TDA1044	2.75	74177	40p	74LS298	40p	74C182	2.00	4572	2.30	2804J	2.70	20 00MHz	1.80	
54p	IN1230	1.20			1.45	NE571	45p	TDA1046	2.75	74178	40p	74LS299	40p	74C183	2.00	4573	2.30	2804K	2.70	20 00MHz	1.80	
54p	IN1232	1.20			1.45	NE572	45p	TDA1048	2.75	74179	40p	74LS300	40p	74C184	2.00	4574	2.30	2804L	2.70	20 00MHz	1.80	
54p	IN1234	1.20			1.45	NE573	45p	TDA1050	2.75	74180	40p	74LS301	40p	74C185	2.00	4575	2.30	2804M	2.70	20 00MHz	1.80	
54p	IN1236	1.20			1.45	NE574	45p	TDA1052	2.75	74181	40p	74LS302	40p	74C186	2.00	4576	2.30	2804N	2.70	20 00MHz	1.80	
54p	IN1238	1.20			1.45	NE575	45p	TDA1054	2.75	74182	40p	74LS303	40p	74C187	2.00	4577	2.30	2804P	2.70	20 00MHz	1.80	
54p	IN1240	1.20			1.45	NE576	45p	TDA1056	2.75	74183	40p	74LS304	40p	74C188	2.00	4578	2.30	2804Q	2.70	20 00MHz	1.80	
54p	IN1242	1.20			1.45	NE577	45p	TDA1058	2.75	74184	40p	74LS305	40p	74C189	2.00	4579	2.30	2804R	2.70	20 00MHz	1.80	
54p	IN1244	1.20			1.45	NE578	45p	TDA1060	2.75	74185	40p	74LS306	40p	74C190	2.00	4580	2.30	2804S	2.70	20 00MHz	1.80	
54p	IN1246	1.20			1.45	NE579	45p	TDA1062	2.75	74186	40p	74LS307	40p	74C191	2.00	4581	2.30	2804T	2.70	20 00MHz	1.80	
54p	IN1248	1.20			1.45	NE580	45p	TDA1064	2.75	74187	40p	74LS308	40p	74C192	2.00	4582	2.30	2804U	2.70	20 00MHz	1.80	
54p	IN1250	1.20			1.45	NE581	45p	TDA1066	2.75	74188	40p	74LS309	40p	74C193	2.00	4583	2.30	2804V	2.70	20 00MHz	1.80	
54p	IN1252	1.20			1.45	NE582	45p	TDA1068	2.75	74189	40p	74LS310	40p	74C194	2.00	4584	2.30	2804W	2.70	20 00MHz	1.80	
54p	IN1254	1.20			1.45	NE583	45p	TDA1070	2.75	74190	40p	74LS311	40p	74C195	2.00	4585	2.30	2804X	2.70	20 00MHz	1.80	
54p	IN1256	1.20			1.45	NE584	45p	TDA1072	2.75	74191	40p	74LS312	40p	74C196	2.00	4586	2.30	2804Y	2.70	20 00MHz	1.80	
54p	IN1258	1.20			1.45	NE585	45p	TDA1074	2.75	74192	40p	74LS313	40p	74C197	2.00	4587	2.30	2804Z	2.70	20 00MHz	1.80	
54p	IN1260	1.20			1.45	NE586	45p	TDA1076	2.75	74193	40p	74LS314	40p	74C198	2.00	4588	2.30	2804A	2.70	20 00MHz	1.80	
54p	IN1262	1.20			1.45	NE587	45p	TDA1078	2.75	74194	40p	74LS315	40p	74C199	2.00	4589	2.30	2804B	2.70	20 00MHz	1.80	
54p	IN1264	1.20			1.45	NE588	45p	TDA1080	2.75	74195	40p	74LS316	40p	74C200	2.00	4590	2.30	2804C	2.70	20 00MHz	1.80	
54p	IN1266	1.20			1.45	NE589	45p	TDA1082	2.75	74196	40p	74LS317	40p	74C201	2.00	4591	2.30	2804D	2.70	20 00MHz	1.80	
54p	IN1268	1.20			1.45	NE590	45p	TDA1084	2.75	74197	40p	74LS318	40p	74C202	2.00	4592	2.30	2804E	2.70	20 00MHz	1.80	
54p	IN1270	1.20			1.45	NE591	45p	TDA1086	2.75	74198	40p	74LS319	40p	74C203	2.00	4593	2.30	2804F	2.70	20 00MHz	1.80	
54p	IN1272	1.20			1.45	NE592	45p	TDA1088	2.75	74199	40p	74LS320	40p	74C204	2.00	4594	2.30	2804G	2.70	20 00MHz	1.80	
54p	IN1274	1.20			1.45	NE593	45p	TDA1090	2.75	74200	40p	74LS321	40p	74C205	2.00	4595	2.30	2804H	2.70	20 00MHz	1.80	
54p	IN1276	1.20			1.45	NE594	45p	TDA1092	2.75	74201	40p	74LS322	40p	74C206	2.00	4596	2.30	2804I	2.70	20 00MHz	1.80	
54p	IN1278	1.20			1.45	NE595	45p	TDA1094	2.75	74202	40p	74LS323	40p	74C207	2.00	4597	2.30	2804J	2.70	20 00MHz	1.80	
54p	IN1280	1.20			1.45	NE596	45p	TDA1096	2.75	74203	40p	74LS324	40p	74C208	2.00	4598	2.30	2804K	2.70	20 00MHz	1.80	
54p	IN1282	1.20			1.45	NE597	45p	TDA1098	2.75	74204	40p	74LS325	40p	74C209	2.00	4599	2.30	2804L	2.70	20 00MHz	1.80	
54p	IN1284	1.20			1.45	NE598	45p	TDA1100	2.75	74205	40p	74LS326	40p	74C210	2.00	4600	2.30	2804M	2.70	20 00MHz	1.80	
54p	IN1286	1.20			1.45	NE599	45p	TDA1102	2.75	74206	40p	74LS327	40p	74C211	2.00	4601	2.30	2804N	2.70	20 00MHz	1.80	
54p	IN1288	1.20			1.45	NE600	45p	TDA1104	2.75	74207	40p	74LS328	40p	74C212	2.00	4602	2.30	2804P	2.70	20 00MHz	1.80	
54p	IN1290	1.20			1.45	NE601	45p	TDA1106	2.75	74208	40p	74LS329	40p	74C213	2.00	4603	2.30	2804Q	2.70	20 00MHz	1.80	
54p	IN1292	1.20			1.45	NE602	45p	TDA1108	2.75	74209	40p	74LS330	40p	74C214	2.00	4604	2.30	2804R	2.70	20 00MHz	1.80	
54p	IN1294	1.20			1.45	NE603	45p	TDA1110	2.75	74210	40p	74LS331	40p	74C215	2.00	4605	2.30	2804S	2.70	20 00MHz	1.80	
54p	IN1296	1.20			1.45	NE604	45p	TDA1112	2.75	74211	40p	74LS332	40p	74C216	2.00	4606	2.30	2804T	2.70	20 00MHz	1.80	
54p	IN1298	1.20			1.45	NE605	45p	TDA1114	2.75	74212	40p	74LS333	40p	74C217	2.00	4607	2.30	2804U	2.70	20 00MHz	1.80	
54p	IN1300	1																				

BRADLEY MARSHALL LTD

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

325 EDGWARE ROAD, LONDON W2 1BN Tel: 01-723-4242 Tlx: 295441

CRIMSON ELEKTRIK

No	Modules	Price
2580	CE 608 40W Mono	18.26
2581	CE1004 100W 4 Mono	21.30
2582	CE1008 100W 8 Mono	23.90
2583	CE1704 170W 4 Mono	30.43
2584	CE1708 170W 8 Mono	30.43
2585	CE3004 300W 4 Mono	42.60
2585a	FE 908 90W FET Mono	25.65
2585b	FE1704 170W FET Mono	33.48
2585c	BD1 Bridge Unit for Modules	7.13
2608	CPR 1X Pre-Amp Module	41.70

**WE ALSO STOCK
ALL THE POWER
SUPPLIES TO DRIVE
THESE MODULES
PS. THESE KITS AND
MODULES ARE
EXCLUSIVE OF VAT**

PLEASE NOTE ALL CRIMSON MODULES ARE GUARANTEED FOR 2 YEARS.

JOIN THE PROFESSIONALS

No	Complete Pre-Amp Kit	CK1010	Price
2615	Complete 40W Stereo Amp Kit	CK1040	£80.00
2616	Complete 80W Stereo Amp Kit	CK1080	£105.00
2616a	Complete 100W Stereo Amp Kit	CK1100	£116.00
2617	Add on Moving Coil Kit	MC12K	£131.00
2618	Pre-Amp Power Supply Kit	PSK	£21.74
2619	TS70 70 Thermal Switch		£17.39
	HS50 50mm Heatsink		
	HS100 100mm Heatsink		
	14.95 150mm Heatsink		

VELLEMAN KITS

No	Description	Price
K610	Mono UU using LEDs	10.05
K1798	Stereo UU using LEDs	18.77
K1874	Running Light Kit	14.95
K2571	Light Computer with EPROM	36.23
K2569	Three Tone Chime	8.57
K2575	Microprocessor Doorbell 25 tunes	15.53
K2544	Complex Sound Generator	10.26
K2032	Digital Panel Meter	16.61
K2557	Digital Thermometer	26.57
K2545	50Hz Crystal Time Base	12.00
K615	High Precision Stopwatch	50.29
	Description	Price

**WE STOCK A WIDE
RANGE OF BOXES
TO HOUSE THESE
KITS IN. FROM
VERY SMALL TO
VERY LARGE
19" MAXIMUM**

**PS. ALL KITS
INCLUDE VAT**

Some are easy some are hard

No	Transistor Ignition	11.16
K2543	Digital Freq Counter for Receivers	45.40
K2555	3 Channel Coloured Light Organ	19.19
K2566	Universal Stereo Pre-Amplifier	6.56
K2572	Universal 4 Digit U/D counter with memory	44.72
K2574	Electric Motor Speed Control	11.17
K2577	Universal Start/Stop Timer	7.45
K2579	Heating Controller	81.45
K2583	Microprocessor Universal Timer (no case)	61.72
K1682	Electronic Power Switch Dimmer	12.37
K2580	Central Alarm Unit	15.48
K2551		

TELETEXT KIT

This unit will make your TV fully remote control (infra-red) and bring you closer to the amazing world of teletext. The kit can also be updated to incorporate full Prestel, and with a keyboard this can give you full message facilities for ordering foods or sending and receiving messages (E.G.) Booking your Holidays!

With a microcomputer as an alternative keyboard the world is even greater adding bulk updating to viewdata computers and receiving telesoftware for implementation to any personal computer.

Even without the Prestel option, Telesoftware from the Teletext pages free!

The full features of Teletext, including subtitles are all included in the basic kit.
An attractive stylish case is available to complement the finished kit.

Basic Teletext Kit (no box) £130 + VAT P/P £2.50
with box £144.95 + VAT P/P £3.00
box by itself £14.95 + VAT P/P 75p

PRESTEL ADAPTOR

A Prestel microcomputer adaptor to give full autodialling to your microcomputer. All the usual Prestel facilities are added via this unit, plus many more, and, can operate to any viewdata computer.

You can shop from home, bank transmitt messages and receive software, which means that the uses your micro can be put to are limitless.

The unit is not restricted to just the UK, for at least 28 countries use the Prestel viewdata format, so you can also mail-order from anywhere. The Prestel unit is suitable for most micro computers even the ZX-81, so at the push of a button, the technology of tomorrow is in your home today.

NEW

ANTEX

Soldering Irons

XS25	25W	5.46+
CX	17W	5.30+
C "iron"	15W	5.20+
CCN "ceramic"	15W	5.00+
Wide range of bits and elements in stock now.		
Soldering iron stand 2.40		
We stock multicore solder for normal use or fine.		

Iso-tip Cordless Iron	31.90+
Miniature low voltage soldering station	13.95+
Oryx50 50W temp controlled	15.50
Oryx super 30	5.90+
All irons are 240V mains. Earth Leakage current is less than 3 ua.	
The temperature controlled iron can be controlled within $\pm 2\%$ temperature range from 200°C to 400°C.	

ORYX

COMPONENTS

Device	Price
Z80A	3.20
Z80A PIO	3.20
Z80A CTC	3.20
6800	6.50
6810	3.00
6821	4.25
6502CPU	7.50
2114(200ns)	1.80
2708	3.00
2716	3.20
2732	7.50
2532	3.50
2764 (200ns)	11.00
ADC0816 (8 bit)	14.90

We also stock 74 series 74LS, C mos, transistors, capacitors, resistors, LED's, zeners, diodes, jack plugs, mains plugs XLR plugs, cannon plugs, arrow switches BNC connectors, reducers, photolok developer, PC board, sensitive & normal boxes, wire cutters, strippers, Edge connectors, pots, batteries, digital pulsers, logic probes, proto-boards, vero board.

This is just a small sample of what we stock, if you like to see more send £1.00 to us for our NEW 1983 CATALOGUE.

EDGE CONNECTORS

ZX81 E.C.	2.98
Spectrum E.C.	3.78
VIC 20 E.C.	3.78
50 Way E.C.	3.30
18 Way E.C.	2.80
64 Way E.C. Plug	2.50
64 Way E.C. Socket	4.80
31 Way E.C. Plug	2.00
31 Way E.C. Socket	2.10

We stock a very wide range of opto-devices, from Infra-Red to LED's to Opto-Couplers.

Check us out for competitive prices and helpful service.

BOOKS

*New Books

Please Note: Books are VAT exempt but add £1.00 to cover P/P

The 9900 Family Data Book	10.00
The Opto-Electronics Data Book	4.00
The Bipolar Microcomputer Databook	4.50
The Interface Circuits Data Book	7.00
The TTL Data Book	8.50
MDS Memory Data Book	3.95
The Linear Control Circuits Data Book	4.00
The Voltage Regulator Data Book	4.50
The Power semiconductor Data Book	9.00
*TTI Data Book Volume I	9.00
*TTI Data Book Volume II	8.00
301 Circuits	5.00
Towers Transistor Equivalent	9.50
Towers Digital Selector	9.95
Towers Linear 10 Selector	7.50

Why not try our mail order service, it's fast and efficient. We take Barclay, Access, Am Exp, Diners or Cheque. Cheques made payable to Bradley Marshall Ltd.

PLEASE REMEMBER TO ADD VAT AT 15% + 70p P&P

DIGEST

Hyconomiser

Would all those readers who've rung us, sent telexes, telegrams, telemessages, letters, carrier pigeons and so on, please note that you can get information on dealers in your area from the manufacturers, who are: Atwell Construction Ltd, Station Road, Wrington, Avon (telephone Bristol 719441). (Yes, we know, we should have said so in the first place . . .)

Static RAM Lookalike

Integrated RAMs offering all the advantages of a static RAM but with the higher circuit density and lower cost of dynamic RAMs are shortly to be available from

Jermyn.

The Intel 2186 is a 64K IRAM organised as an 8K x 8 device but having the major advantage that it requires no external refreshing circuitry. All the DRAM refresh control circuitry is integrated on the chip allowing the user to treat the IRAM as a purely static device yet with all the advantages and performance of Intel's high volume HMOS dynamic RAM production technology.

Incorporating many systems oriented features such as low power dissipation, automatic initialisation, extended cycle operation and two-line bus control to eliminate bus contention, the 2186 is particularly suited to microprocessor systems applications where higher integration yet lower cost is required.

For further information contact Jermyn Distribution, Vestry Estate, Sevenoaks, Kent.

Government Unveils Cable Plans

Work on advanced cable systems in up to 12 areas could start this year under proposals published recently by the Government in the White Paper, "The Development of Cable Systems and Services".

The White Paper, presented to Parliament jointly by the Home Secretary and the Secretary of State for Industry, is a comprehensive statement of Government policy across the range of cable issues. In the broadcasting field, it sets out the Government's response to the Hunt Report, published last October.

In outline, the broad strategy is:

- Cable investment should be privately financed and marketed.
- Regulation should be as light as possible to allow the development of a wide range of services and facilities.
- The regulatory framework should be flexible so that it can adapt as technology changes.
- Key safeguards are needed to ensure that existing broadcasting and telecommunications services are not impoverished and to take account of the fact that cable services will be directly available in the home.

Legislation will be introduced to establish a new Cable Authority to award franchises, supervise programme services and promote cable development. If this then goes ahead as the White Paper envisages, the Government will be prepared to authorise up to 12 pilot cable systems each covering



Man Overboard!

We're sad to report that Peter Green will be leaving the ETI fold, taking his hideous puns with him. He won't be going far, though, just across the corridor in fact, to the Computing Toady, whoops, I mean Today, office, where he'll be assuming the editor's chair (and funny little

peaked cap too). The things some people will do for a bigger desk . . .

Unfortunately, until we find a successor to Peter, our ability to answer technical enquiries will be severely restricted, so we'd appreciate it if you could try and sort out the problem yourself before writing. If you do write, it would help enormously if you could follow the guidelines given our Reader Services page, page 86.



The ex-deputy editor unwinds after a hard day battling against broken typewriters, Space Invaders and colour-blind artists.

a maximum of about 100,000 homes. The systems will have to offer a positive contribution to advanced technology, comprehensive programme services, and interactive capability. In the interim, the pilot projects will be set up under existing legislation. The Department of Industry will assess technological and telecommunications proposals, while programme services will require Home Office approval.

Existing relay operators will be

allowed to offer new programme services over their systems for a transitional period, pending the installation of advanced technology. (Most relay services are limited to 4 or 6 channels.) Where necessary, the normal "must carry" rule — under which they have to relay current broadcast services — will be relaxed if customers are provided with alternative means of receiving BBC and IBA channels at no extra cost.

First Come . . .

Competition for our attention can be pretty hot, you know, and PR companies sometimes resort to dirty tricks, like, having noticed that ETI has an all male staff, sending us pictures of scantily clad women adorning their products. They really should know better, because here, at ETI, it's the naked truth about electronics we are after.

What has provoked this little

diatribe is the near simultaneous announcement of two companies that they were the first to introduce legal cordless telephones.

We think that the fact that Fidelity (left) look so relaxed probably means it was them, and that's also the reason why British Telecom didn't send us a photo, for fear of giving the game away with their false smiles . . .


No, we're not going to give you any addresses — both phones will be very widely available.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

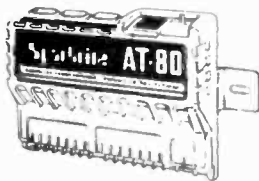


AT-80 Electronic Car Security System

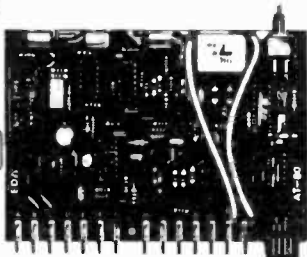- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble





VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
- Affords 12 functions centred, on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories 2,000 miles 180 gallons 100 hours
- Full Imperial and Metric calibrations
- Over 300 components to assemble

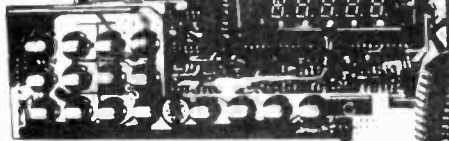

SX1000 Electronic Ignition

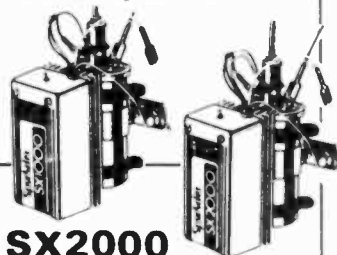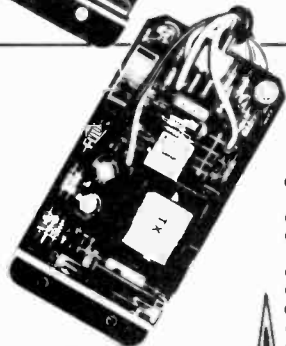- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg earth vehicles




SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg earth vehicles

TX1002 Electronic Ignition

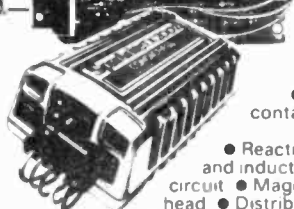- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble




TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents.

SPECIAL OFFER

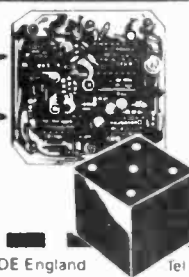"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE 82 Bath Street, Walsall, West Midlands WS1 3DE England

tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£64.95
MAGIDICE	£9.95

PRICES INC VAT POSTAGE & PACKING

NAME _____

ADDRESS _____

ETI/7/83

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF _____

CHEQUE NO _____



BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!



Yes, Ma'am?

A new robot, designed to work alongside rather than replacing a human being, has been launched by Patscentre International and Prutec. Yes-Man (he's the one in the middle, without a silly grin) is the latest development from the association between Patscentre, the science and technology division of PA International, the management consultancy group, and Prutec, the high technology funding subsidiary of the Prudential Assurance Company.

The importance of Yes-Man lies in its ability to work with an operator in 'mixed assembly' tasks. Yes-Man carries out the more routine portions of the task leaving the human being free to exercise his skills in the cognitive and manipulative elements to which he is best suited. This specialisation is claimed to both improve productivity and contribute to a more rewarding working environment.

Shorts

● Non-volatility in Sinclair memory has its advantages, or so think Cambridge Microelectronics Ltd, because they've just released the CRAMIC-81 upon an unsuspecting world. For £79.95 (plus VAT, but including p&p), you can have 16K of long-life (10 years) of memory retention on your ZX81... they must have seen our PseudoROM project. If you want complete permanence, Cambridge Microelectronics are also offering an EPROM programmer for the '81, called PROMER-81.

Cambridge Microelectronics Ltd may be found at One Milton Road, Cambridge CB4 1YU.

● Looking for a way to get rich? The National Computing Centre, Oxford Road, Manchester M1 7ED, have launched a management training package entitled 'Profits from Microchips'. Mind you, you've got to be fairly well off to start off with, as the package will cost you a cool £800.

● Ferranti have extended their range of microphone amplifier ICs by introducing three new products, the ZN475E, ZN476E and ZN477E, designed for piezo-electric, moving coil and simple electret transducers. Ferranti Electronics Ltd, Fields New Road, Chadderton, Oldham, Lancashire OL9 8NP.

● They've been busy at ILP, as they've recently launched a new range of regulated power supply modules, as well as a new range of modular power units. Do they ever sleep? ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.

● NEC Electronics (UK) Ltd, of 116 Stevenson Street, New Stevenson, Motherwell ML1 4LT, have launched a new 1F (yes, one farad) super-cap, specifically for on-board memory power back-up. Rated at 5V DC, the unit occupies less than 1 cubic inch in volume.

● Why buy when you can hire? Aughton Automation Ltd have written a brochure on their range of computers, peripherals and robots that you can hire. Aughton Hire, Woodward Road, Kirkby Industrial Estate, Kirkby, Liverpool L33 7UZ.

● OK Industries UK Ltd, Dutton Lane, Eastleigh, Hants SO5 4AA have launched a new desoldering station, the SA-4, for production, prototype or laboratory use.

● Also from OK, a desolder pump that has a bronze alloy tip in order to avoid CMOS static problems.

● Litesold also have a new product, the MG self-feeding soldering gun, which allows the option of using solder from a bench-mounted reel or from a reel mounted on the gun itself. Light Soldering Developments Ltd, Spencer Place, 97/99 Gloucester Road, Croydon, CR0 2DN.

● Enclosure Technology of Unit G, Southampton Airport, Southampton SO2 2HG have launched two new product ranges: the Chassis Europe, a range of chassis kits in 11 height ranges and four depths and the Harmonite instrument cases, in five heights, three widths and three depths, and also with a range of accessories.

● First of this month's rash of catalogues: this one's from HB Electronics, of Lever Street, Bolton, BL3 6BJ, and features Ungar soldering and de-soldering equipment.

● Not exactly a catalogue, but 'a new 8pp colour brochure' is available from BICC-Vero Packaging, Industrial Estate, Chandlers Ford, Eastleigh, Hants SO3 3ZR, and it describes Speedwire, as reviewed in your very own ETI in June 1982.

● There seem to be a lot of small companies based in Cambridge and specialising in ZX peripherals. Here's another one, called (original name, this) Cambridge Computing. They're ever

so excited about their new, 'totally unique' joystick for both the '81 and the Spectrum, that they say will work with all software. They won't be launching the thing till June, though (they're at 1 Benson Street, Cambridge).

● We mentioned Southampton Universities' computer holidays a couple of months ago in Digest. They now tell us that they are able to offer places to disabled people, due to their having a purpose built hall for disabled students. For more information write to M.A.P.S., 37 University Road, Southampton SO2 1TL (tel 0703 558621).

● Why do suppliers seem to shy away from calling a catalogue a catalogue? Latest offenders (again) are Elkan Electronics, Freepost, 11 Bury Road, Prestwich, Manchester M25 8JZ, who call their catalogue of soft and hardware for the Dragon computer the 'Dragon Supermarket'. Well, really.

● Cetron Components Ltd have issued a brochure on their wirewound resistors and potentiometers. Free to trade people, your copy may be had from Cetron Components Ltd, Hoddesdon Road, Stanstead Abbots, Ware, SG12 8EL.

● The Computer Trade Association inform us that if you managed to join them before June 1st, then the membership would have cost you £20, whereas after it'll set you back £50. The association aims to represent all sections of the industry, including retailers, distributors, software houses, manufacturers and consultants, and may be found at 108 Margaret Street, Coalville, Leicestershire LE6 2LX.

● Pronto Electronic Systems, 466-478 Cranbrook Road, Gants Hill, Ilford, Essex have released two new ultra-low noise op-amps, the OP-27 and the OP-37. Depending on their availability, we're hoping to bring you a data sheet on these in the near future.


● Feeling boxed in? You may be a case for assistance from Boss Industrial Mouldings Ltd, who have extended their range of ABS potting boxes. Boss Industrial Mouldings Ltd, James Carter Road, Mildenhall, Suffolk IP28 7DE.

● At last! Someone who calls their catalogue a catalogue, and not a short-form supermarket file system. Rafi Electronics, 98 Croydon Road, London SE20 7AB present a range of professional DIN standard keyboards with considerable scope for customisation.

● The Irish Amateur Computer Club has written to inform us of their existence, and to say that our readers will get a warm welcome from them. In particular, they say that they are keen to recruit people with a good knowledge of hardware. The club may be reached via Nigel Carry (general secretary), 166 McKee Avenue, Finglas East, Dublin 11.

● Last but by no means least on our list (actually, it was at the top of the pile until it fell on the floor) comes Towers' International Digital IC Selector. From IL311 to ZN74119F, it lists a very large number of ICs (no, we didn't count) with brief details of use, an indication of the pin-out, and any substitutes that are available. Published by W. Foulsham & Co, it should be available through any good technical bookshops. (Note that it doesn't cover microprocessor ICs, these have a volume of their own in the series).

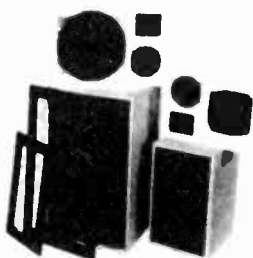● We would tell you that the British Amateur Electronics Club, c/o Dickens, 26 Forrest Road, Penarth, South Glamorgan, have just published their latest newsletter... we would tell you, but they addressed the accompanying letter to 'The Editor, Electronics and Music Maker...'



MULLARD SPEAKER KITS

Purposely designed 40 watt R.M.S. and 30 watt R.M.S. 8 ohm speaker systems recently developed by MULLARD'S specialist team in Belgium. Kits comprise Mullard woofer (8" or 5") with foam surround and aluminium voice coil. Mullard 3" high power domed tweeter. B.K.E. built and tested crossover based on Mullard circuit, combining low loss components, glass fibre board and recessed loudspeaker terminals. **SUPERB SOUNDS AT LOW COST.** Kits supplied in polystyrene packs complete with instructions. 8" 40W system — recommended cabinet size 240 x 216 x 445mm. Price £14.90 each + £2.00 P & P. 5" 30W system — recommended cabinet size 160 x 175 x 295mm. Price £13.90 each + £1.50 P & P.

Designer approved flat pack cabinet kits, including grill fabric. Can be finished with iron on veneer or self adhesive vinyl etc. 8" system cabinet kit £8.00 each + £2.50 P & P. 5" system cabinet kit £7.00 each + £2.00 P & P.

STEREO CASSETTE TAPE DECK MODULE

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Autostop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V. Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish. Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

LOUDSPEAKERS

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See Photo). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Prices.**


15" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P.
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P.
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille Price: £9.99 each. P&P £1.50.

12" 85 watt R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 96dB. Price: £22.00 + £3 carriage.
12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £22 + £3 carriage.
15" 150 watt R.M.S. MCKENZIE C16 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price: £47 + £4 carriage.



PIEZO ELECTRIC TWEETERS - MOTOROLA

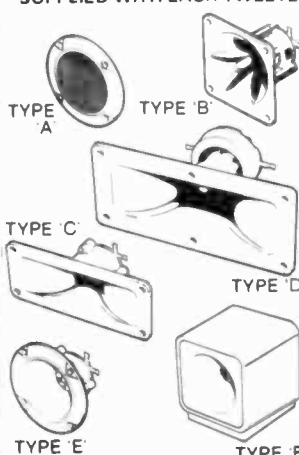Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.29 each.


TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.99 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £7.99 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.99 each.

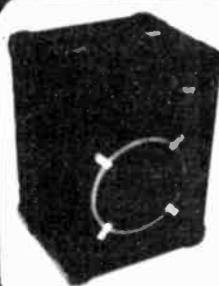TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. P&P 20p ea. (for SAE for Piezo leaflets).



OMP 80 LOUDSPEAKER

The very best in quality and value.

Ported tuned cabinet in hard-wearing black vinylite with protective corners and carry handle. Built and tested, employing 10in British driver and Piezo tweeter. Spec: 80 watts RMS; 8 ohms; 45Hz-20KHz; Size: 20in x 15in x 12in; Weight: 30 pounds.

Price: £49.00 each
£90 per pair
Carriage: £5 each £7 per pair

PANTEC

HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 5 x 46 x 14mm (9 volt) Price: £7.99p

DIGITAL THERMOMETER -9.9°C to +99.9°C LED display. Complete with sensor. 70 x 70 mm (9 volt) Price: £27.60p

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled. professional performance. Range up to 3 miles 35 x 84 x 12 mm (12 volt) Price: £12.49p

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22 mm (9/12 volt) Price: £16.49 Transmitter 80 x 50 x 15 mm (9/12 volt) Price £10.29 P&P All Kits +50p. S.A.E. for complete list.



3 watt FM Transmitter


BSR P256 TURNTABLE

P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti-skate (bias device) • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price £31.35 each. £2 50 P&P



OMP POWER AMPLIFIER MODULE

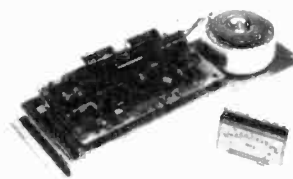

New model.
Improved specification

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

SPECIFICATION
Output Power: — 110 watts R.M.S.
Loads: — Open and short circuit proof 4/16 ohms.
Frequency Response: — 15Hz - 30KHz -3dB. T.H.D. — 0.01%
S.N.R. (Unweighted): — -118dB ±3.5dB.
Sensitivity for Max. Output: — 500mV @ 10K.
Price: — £31.99 + £2.00 P&P.
Vu Meter Price: — £7.00 + 50p P&P.

HOME PROTECTION SYSTEM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit — Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch — off — test — armed. 30 second exit and entry delay.

Indoor alarm — Electronic swept freq. siren. 104dB output.

Outdoor Alarm — Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE OVER £100 Usual price £228.85

— **B.K.E.'s BARGAIN PRICE £128.00**

+ £5.00 P&P

S.A.E. for colour brochure.



SAFGAN DT-520 DUAL TRACE OSCILLOSCOPE. New British model. 12 month guarantee. 20 MHz Band Width. **Specification:** • CH1, CH2, 5mV/div-20V/div. • Time Base: 1 Sec/div-100ns/div. • XY Facility. Matched XY inputs. • Trigger: Level control ± slope selection. • Auto, normal TV Triggering. • Z-Modulation. • CAL output 1V 1KHz. • Sweep output 0-9V. • Graticule blue ruled 10 x 8 cm. (5" C.R.T.) Very sharp trace. • Size: H235mm, W177mm, D360mm • Weight: 6.5 Kgs. • Supply: 200-24V, 40-60Hz. • Price: £241.50. **FREE Securicor Delivery.** Probes: X1 £8.05, X1/X10 Switched £10.93.




FREE SECURICOR DELIVERY

B.K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR

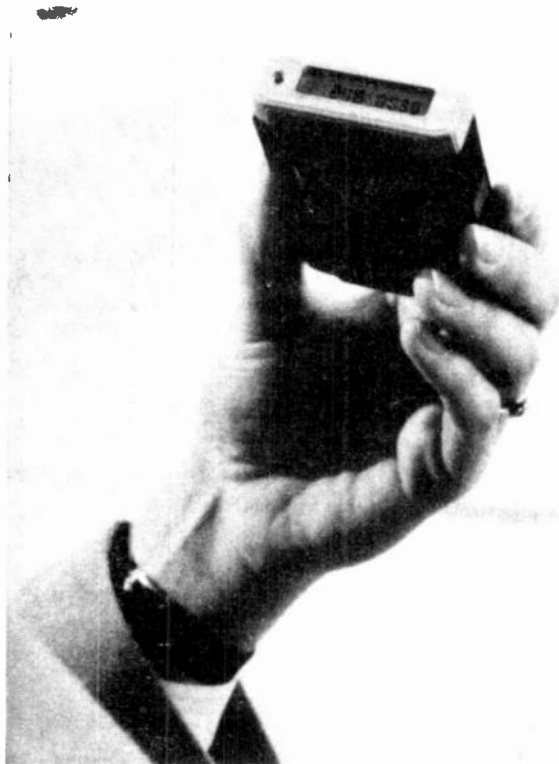★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed where applicable in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702 527572





Extended Bleep

Britain's first wide-area radiopager with a message display was launched by British Telecom Radiopaging in April.

A ten-digit liquid crystal display on the new pager can be used to identify the caller (by giving a phone number), or to convey a message. The last two messages are stored in its memory

and can be displayed at the touch of a button.

Like a tone pager, the new version gives a distinctive bleep to alert users. It also has a tiny lamp which flashes in response to a call. This enables users to keep in touch even when the bleep is muted to avoid disturbing others.

Display Page is the name of British Telecom Radiopaging's new service. For the first time it makes it practical for customers to advertise their paging numbers so that anyone may call them.

Guildford Gets The Wire

Discussions have been taking place between Rediffusion and Guildford Borough Council on a proposal by the company to install and operate an advanced multi channel cable television system in the city.

The proposed network would be a modern switched star cable system providing initially up to 30 television channels together with up to 20 FM channels. The system would be interactive, offering the


community opportunities for several new information technology services. These include teleshopping, telebanking, security and education in the home.

If central government approval is given, Rediffusion's plans could make Guildford the first city in Britain to possess a system which, while providing a wide range of national and other tv programmes, would enable a new concept in community television to be developed. As such it would become a model for other similar systems both in the UK and abroad.

Modular Security

Riscomp Limited announce an addition to their range of security modules and accessories with an infra-red system known as the IR 1470. The unit, which operates from a conventional supply, consists of a separate infra-red transmitter and receiver, and provides a modulated beam of infra-red light over distances of up to 53ft. In the event of the beam being interrupted, a relay in the receiver unit is energised, which if connected to an appropriate warning device can be used to sound an alarm. Both transmitter and receiver are housed in compact moulded enclosures and easily mounted on most surfaces.

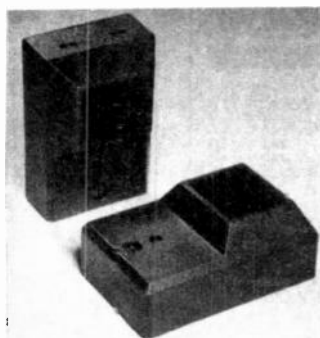The system which is British made and fully guaranteed, is supplied with comprehensive data and costs £25.60 + VAT. For further information contact Riscomp Limited, 21 Duke Street, Princes Risborough, Bucks HP17 0AT.



EMI Joins CD

As you may have seen in the newspapers, EMI have decided to join in on the compact disc bandwagon. They had been a significant absentee from the furore of the CD launches, but it looks as though the fact that all the players have sold out wherever they've been put on

sale has persuaded EMI to adopt the medium.

They say that they will be building a catalogue strength of over 200 titles during the first twelve months. Though this is a tiny proportion of just the new releases from EMI and its subsidiaries, it would still represent a 100% increase on the CD launch catalogue.

Guildford is considered by Rediffusion to be ideally suited to this new enterprise with a demographically well balanced community (we think that means rich). It encompasses a wide range of activities and interests with opportunities for cultural and educational services provided by the university, the cathedral and other local organisations.

Watch With The BBC

Digiturst's latest vision analysis product has been designed to run with the BBC microcomputer. It enables the Model B BBC computer to be linked to a standard home video recorder and pre-packaged images to be transferred into the micro.

The interface, known as

MicroEye, enables pictures to be digitised with a 256 x 256 resolution, although with the BBC Model B only 128 x 128 pixels are used. Digiturst decided to go for a high resolution as it feels users will want to upgrade the system when they add a second processor to their BBC kit. The interface is supplied as a total package providing the cable connections to both the video recorder and the BBC user port. A complete suite of software is supplied

allowing the user to analyse captured images, and to dump them onto the disk or a printer.

As well as running with the BBC machine the above package can also be connected to a range of other microcomputers such as Research Machine 380Z, Apple, Commodore, Hewlett Packard, IBM, Sirius, etc.

The package price is £295 + VAT. Digiturst Ltd, Leaden Hill, Orwell, Royston, Herts, SG8 5QH.



No Mail Order Orics

Oric Products' own mail order operation for the Oric 1 and all peripherals has stopped accepting orders, and Oric is putting its promotional strength behind retailers with a £50,000 advertising campaign for the April-June period and full colour point of sale kits available to all stockists. Oric 1 is now available from W. H. Smith, Dixons, Greens, Laskys, Micro C, Micro Peripherals, Spectrum, Computers for A11 and other specialist outlets.

Play the AMBIT numbers game

The long awaited implementation of on-line order processing is with us at last, and whilst this means that orders for in-stock items can now be processed more efficiently, it also means that orders should be submitted using stock codes for best results. Our current catalogue (75p) includes all order codes (watch out for the new expanded Spring edition), but here's an abstract from some of the more popular lines to use as a quick reference.

Remember that you can also access our catalogue via REWSHOP on REWTEL, which now includes on-line current price and delivery information. You need a 300 baud MODEM and RS232 terminal, (various suitable configurations based on popular micros have been published in recent past issues of Radio and Electronics World).

Prices shown here exclude VAT, and the P&P charge is currently 60p per order (unless otherwise indicated). Remember that our telesales service operates with human beings (not 'dumb' machines) from 8am to 7pm (and frequently later) Monday to Friday, and 9am to 6pm on Saturdays. REWSHOP operates 24 hours a day, 365 days a year with full price and delivery information.

ALWAYS USE STOCK NUMBERS WHEN ORDERING PLEASE


4000 CMOS				Type				Type				Type				Type				Type			
Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price		Type	Stock No.	Price	
4000UB	22.0000	0.11		74LS181	21.74181	0.87		74HC194	29.74914	1.10		74ALS123	01.12273	1.15		74LSK34	00.00134	0.31		74ALS104	01.00664	0.10	
4001	22.00001	0.11		74LS183	21.74183	1.05		74AC198	29.74918	1.30		HA11225	01.11225	1.45		74SK135	00.00135	4.25		74V12	02.00028	0.10	
4002	22.00002	0.12		74LS190	21.74190	0.39		74C925	29.74925	0.00		HA12002	01.01028	2.11		74C227	00.00227	3.55		9V1	02.00918	0.10	
4003	22.00003	0.13		74LS191	21.74191	0.39		74C927	29.74927	6.00		HA12017	01.02017	0.80		SD50753	00.00753	2.34		10	02.01008	0.10	
4008	22.00008	0.50		74LS192	21.74192	0.39		74C929	29.74929	6.00		HA12402	01.12402	1.95						11	02.01008	0.10	
4009UB	22.00009	0.25		74LS193	21.74193	0.39					HA12411	01.12411	1.95		01F50	00.00500	0.22		12	02.01008	0.10		
4011UB	22.00011	1.11		74LS194	21.74194	0.39		74HC00	30.70400	0.50		HA12412	01.12412	1.95		01F51	00.00501	0.18		15	02.01008	0.10	
4012	22.00012	0.14		74LS195	21.74195	0.39		74HC02	30.70402	0.50		HA12417	01.12417	1.95		01F52	00.00502	0.18		22	02.02708	0.10	
4013	22.00013	0.25		74LS196	21.74196	0.39		74HC10	30.70410	0.50		HA12420	01.12420	1.95		01F53	00.00503	0.18		27	02.02708	0.10	
4015	22.00015	0.50		74LS197	21.74197	0.47		74HC12	30.70420	0.50		HA12421	01.12421	1.95		01F54	00.00504	0.18		33	02.02708	0.10	
4016	22.00016	0.22		74LS221	21.74221	0.50		74HC13	30.70430	0.50		HA12422	01.12422	1.95		01F55	00.00505	0.18		37	02.02708	0.10	
4017	22.00017	0.22		74LS222	21.74222	0.50		74HC14	30.70440	0.74		HA12423	01.12423	1.95		01F56	00.00506	0.18		40	02.02708	0.10	
4020	22.00020	0.55		74LS223	21.74223	0.50		74HC15	30.70450	0.74		HA12424	01.12424	1.95		01F57	00.00507	0.18		47	02.02708	0.10	
4021	22.00021	0.55		74LS224	21.74224	0.50		74HC16	30.70460	0.74		HA12425	01.12425	1.95		01F58	00.00508	0.18		54	02.02708	0.10	
4022	22.00022	0.55		74LS225	21.74225	0.50		74HC17	30.70470	0.74		HA12426	01.12426	1.95		01F59	00.00509	0.18		55	02.02708	0.10	
4023	22.00023	0.15		74LS226	21.74226	0.50		74HC18	30.70480	0.74		HA12427	01.12427	1.95		01F60	00.00510	0.18		56	02.02708	0.10	
4024	22.00024	0.15		74LS227	21.74227	0.50		74HC19	30.70490	0.74		HA12428	01.12428	1.95		01F61	00.00511	0.18					

Ambit international

200 North Service Road
Brentwood, Essex
CM14 4SG

E.C.I.S. DISTRIBUTOR OF THE YEAR

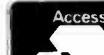Telecom directory:
Consumer 0277-230909
Industrial 0277-231616
Telex 995194 AMBIT C
DATTEL 0277-232628



TELEPHONE SALES 8 am - 7 pm MON - FRI 9 am - 6 pm SAT

Bistromathics?

A new restaurant management system being introduced by Automatic Revenue Controls claims to be easier for table staff to use and give more accurate control over inventories than comparable systems. But will it stop you getting soup spilt on your lap?

Dart is the name of the system which has been on field trial in the UK for six months and has undergone several improvements to software as a result.

Waiter terminals, where staff enter their orders instead of rushing them to the kitchen or bar physically, are not the con-

ventional off-putting numeric keypads. Instead, what waiters and waitresses see is a mimic of the menu itself, with page turnover just like the folder the guest uses at the table. Every menu item is identified by name and one-button selections are possible for most, if not all, of them. Up to 350 different individual items can be ordered at each terminal in this way. Those items may be varied between terminals — no point in having a key for Rump Steak rare in the bar, for example.

Details from Automatic Revenue Control Ltd, Home Park Estate, Station Road, Kings Langley, Hertfordshire WD4 8LZ.



Get Taped With Aiwa

Aiwa, renowned for their high specification cassette decks,

have introduced three new top line decks. According to Aiwa, these decks will capture on tape the crystal clear sound of the Compact Disc. We do hope that this doesn't mean they're en-

couraging our readers to break the copyright law. All three machines — the AD-F990, AD-F770 and the AD-F660 — feature Dolby HX Professional Circuitry and Micro-grain Dual Capstan Tape Transport. Dolby HX Pro is a specially developed anti-saturation circuit that prevents high frequency loss, and therefore greatly improves the dynamic range at the top end of the frequency response curve.


It is claimed that a metal tape-like performance can be achieved with Dolby HX Pro, even when recording with normal tapes, so the sound quality on play-back is excellent, even through a car stereo. Dolby HX Pro is not a noise reduction system — Dolby B & C noise reduction systems are also incorporated into the decks for improving the dynamic range over a wider frequency range.

Aiwa developed the Micro-grain Dual Capstan Tape Transport to increase the contact between tape and capstan. The Micro-grain surface which is in-

corporated in the AD-F990 is composed of millions of uniform hemispheric domes, each only 2µ (micron) in diameter to ensure correct tape tension and reduced modulation noise, plus reduced wow and flutter — 0.025% (WRMS).

At a cool £349 or so, the AD-F990 is Aiwa's top-of-the-range Digital Era (for so they are called) cassette deck, which as well as featuring Dolby HX Pro and Dolby B & C has high performance 3 head technology and introduces a newly developed amorphous alloy combination head. Also new for the AD-F990 is the auto noise reduction detector, which selects the correct noise reduction system automatically for tapes previously recorded on it.

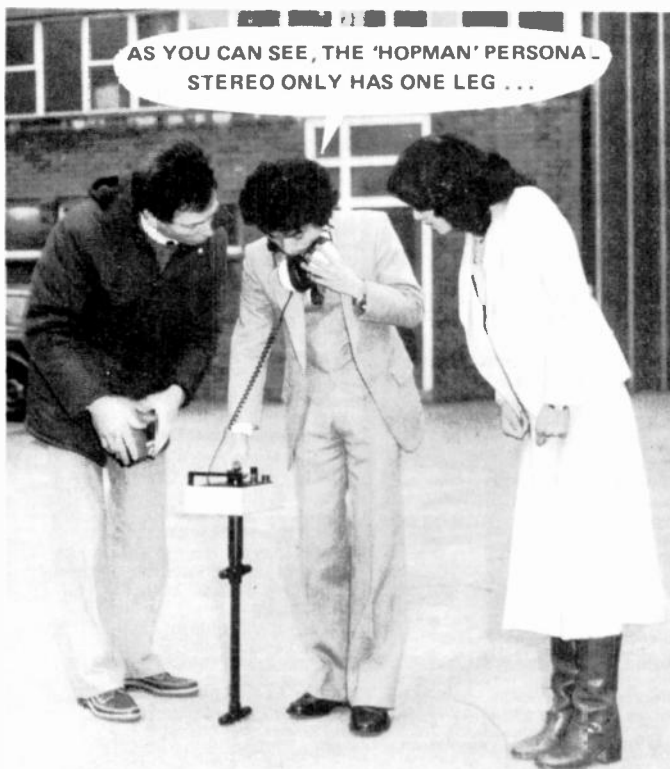Offering most of the features of the above, is the AD-F770 that weighs in at £279.95. Slightly lower down the market (but only very slightly) is the AD-F660, at £229.95. All these should be available through Aiwa dealers.



Digivision

ITT Television & Video have announced the results of a 10 year 20 million pound investment project which, they say, has led to a revolutionary new system of television receiver technology known as Digivision. According to ITT, this represents not one but a series of quantum jumps in the design, giving the consumer enhanced performance, reliability and greatly increased flexibility.

Digivision is not simply an extension of the digital techniques already incorporated in the tuning and remote control sections of some receivers, but a completely new European development which will transform television receiver design world-wide.

In the first production designs up to 300 components of a comparable analogue technology receiver will be replaced by seven VLSI chips, bringing increased reliability, greater stability of per-

formance and extended yet simplified control features, together with quicker and more certain diagnosis and servicing. Later designs will include improved picture displays, with zoom and picture-in-picture facilities, noise and ghost suppression and direct digital inputs from data networks and other signal sources.

A recent study of the market for TV, by Mackintosh International, has predicted that digital technology will be taken up by a large proportion of TV manufacturers, resulting in up to 40% of the market of colour receivers sold in the developed nations being taken by TVs with digital chassis. These results are in the company's report, 'Television Receivers: The Next Ten Years', which also analyses trends in other areas, such as display technology, cable TV and DBS. Unfortunately, this report is not publically available (well, they wouldn't give us a copy).

ETI

COMPUTER WAREHOUSE

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished Diablo/DRE Series 30 2.5 mb hard disk drive for DEC RK05, NOVA, TEXAS etc.
Front load £550.00 - Top load £295.00
PSU type ME3029 for 2 drives £125.00
DRE 44A/4000A/B 10 mb 5+5 all configurations from £995.00. Call sales office for details.

5 AMP MAINS FILTERS

Cure those unnerving hang ups and data glitches caused by mains interference. Matchbox size - Up to 5 amp 240 v load. As recommended by the ZX81 newsletter. Suppression Devices SD5A £5.95.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.

ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95.
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95
BUHLER 69.11.22 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or BRAND NEW 240 v at £10.50. 1000's of other fans EX Stock. Call for Details. Post & Packing on all fans £1.60

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.

DON'T MISS THOSE BARGAINS
CALL NOW, IT'S FREE!

01-683 1133 7 days per week 24 hrs. per day
8 BIT WORD - NO PARITY

COMPUTER 'CAB'



All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available LESS PSU with internal dim. 19" w. 16" d. 10.5" h. £19.95. Carriage & insurance £9.50.

8" FLOPPY DISK DRIVES



Unbelievable value the DRE 7100 8" floppy disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today. The only difference being our PRICE and the superb manufacturing quality! The 7100 single sided and 7200 double sided drive accept hard or soft sectoring IBM or ANSI standard formats giving a massive 0.8 MB (7100) 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc. compatible. Supplied BRAND NEW with user manual and full 90 day warranty. Carriage and insurance £9.75.

7100 Single sided £225.00 + Carr. 7200 Double sided £295 + Carr. Optional accessories: Full technical manual £20.00 alone, £10.50 with drive. Refund of difference on drive purchase. DC and AC power connector and cable kit £8.45. 50 way IDC connector £5.50. 50 way ribbon cable £3.20 per metre.

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah will deliver over 300 amps on short circuit!! Brand new at only £2.95

VIDEO MONITORS

12" CAGED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit, 240 volt AC operation. ONLY £45.00 PLUS £9.50 CARR.

24" CAGED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition. ONLY £55.00 PLUS £9.50 CARR. & INS.

14" COLOUR superb chassis monitor made by a subsidiary of the HITACHI Co. Inputs are TTL, RGB with separate sync, and will plug direct into the BBC micro etc. Exceptional bandwidth with good 80 col definition. Brand new and guaranteed. Complete with full data & circuit 240 v AC working. Dim. 14" x 13" x 13" ONLY £199.00 PLUS £9.50 CARR.

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed, 50+ £2.95 100+ £3.15.

TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.90

CALLING DEC USERS

Brand new and boxed RSX11M 3.2 Documentation kits, fill 3 feet of your bookshelf! Under half price only £120.00 carr. £6.50 0 vat on manuals. We are always keen to buy all types of used or surplus DEC equipment.

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY £499+ VAT

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUE command compatibility and full control via CPM Wordstar etc. Many other features include bi directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable £10.00. Tech manual £7.50. Tractor feed £120.00. Spare daisy wheel £3.00. Carriage & Ins. (UK Mainland) £10.00.



TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT. KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator, Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only £169.00 pp £1.95 Data sheet on request

DATA MODEMS

Join the communications revolution with our range of EXTECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to P.O. lines.

MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only £75.00

MODEM 2B/C Fully fledged, up to 300 baud async, ANSWER & CALL modes, auto answer, auto switching, ideal networks etc. Just 2 wire connection to comms line. £85.00

MODEM 20-1 Compact unit for use with PRESTEL or full duplex 2 wire link. 75 baud transmit - 1200 baud receive. Auto answer. £130.00

MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. £130.00

MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. £130.00 Carriage 13A £4.50. 2B/C & 20 £9.50.

DATA PUMP MODEM compact unit upto 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data £85.00 carr. £4.50.

For more information or details of other types of ex. stock modems contact sales office.

8" WINCHESTER price SLASH

Worldwide purchasing brings you two amazing Winchester SCOOPS at prices that will likely NEVER be repeated. **BASF 6172 8" 24 Mb.** Complete unit consists of micro-processor controlled logic on 3 PCBs for all read/write and servo control functions. Fast data transfer is by the BASF 'Disk Bus' interface on a single 40 way multiplexed i/o bus. Units have been carefully removed from believed working equipment, but at the staggering price of ONLY £99.00 are sold without guarantee. Supplied complete with 200 page + tech. Manual. Dim 45 x 22 x 11 cm. DC requirements +-5v, +-12v, +24v. Carriage and ins. £10.00

S100 Bus 19 Mb. Subsystem. A cancelled order and change of policy by a major British disk drive manufacturer enables us to offer you 'last year's model' at a plug in and ready to go SUPER LOW PRICE. Our own custom controller pugs direct into the S100 bus and will control 2 disk drives, offering a total storage of OVER 36 Mbs! and at data transfer rates in excess of 7 Mb/sec seeing is believing!! Supplied complete with user configurable BIOS etc. Save a fortune, Limited quantity only.

3100 19 Mb. Disk drive £499.00 PSU unit £165.00
CD1100 controller & BIOS £345.00 PSU extension cable £9.95
Full tech Manual £20.00

Special SUBSYSTEM prices. 1 x 3100 disk + PSU + Controller £799.00
or 2 x 3100 disks + 2 PSU + Controller £1295.00
All prices + VAT and carriage. 90 day guarantee. Data on request.


ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD 80p + VAT. Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
01-689 7702 - 01-689 6800 Telex 27924



DISPLAY
-ELECTRONICS-

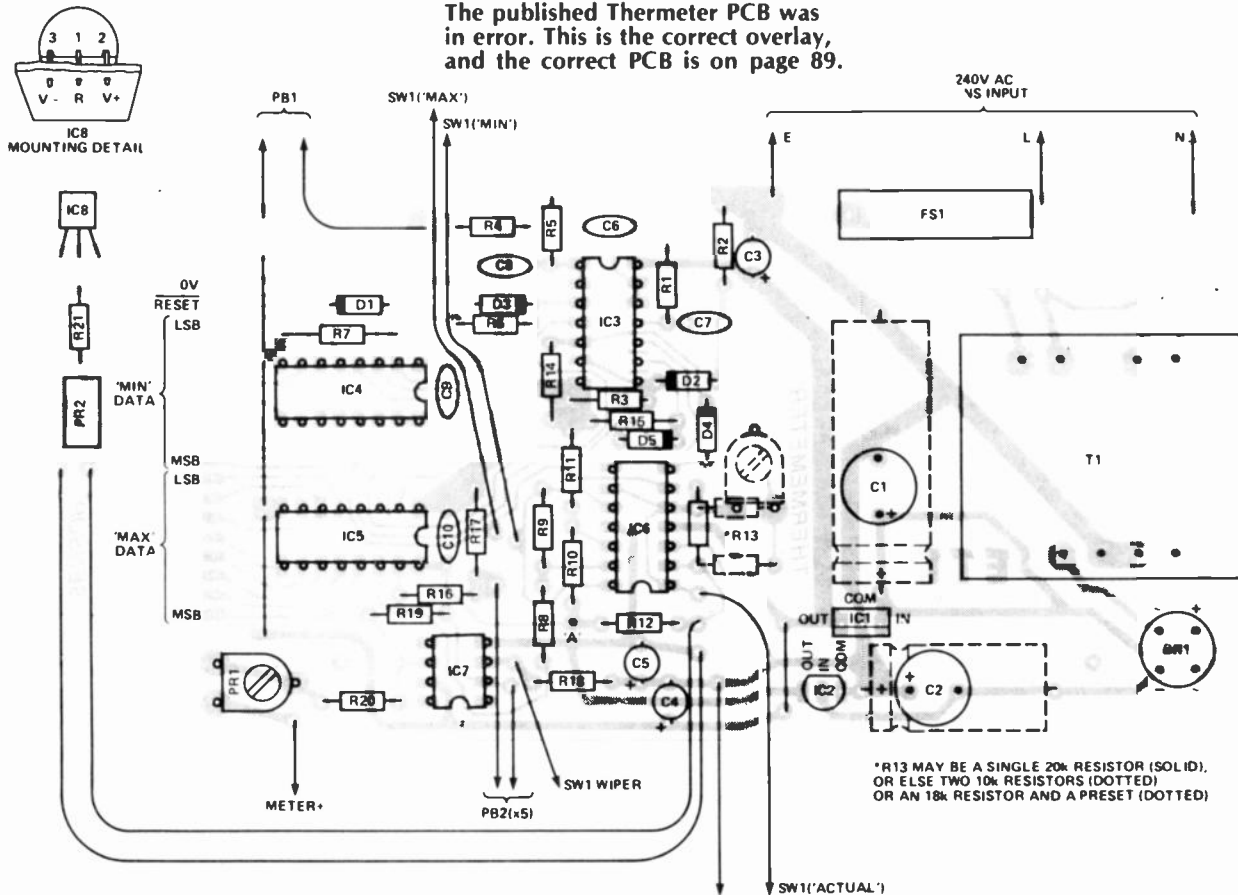

If you missed
out on Breadboard
'79, '80, '81 and '82.....
Now's the time to catch up
with **BREADBOARD '83**



The premier electronics show for the enthusiast.
Moved this year for your convenience and comfort
to the Cunard International Hotel, Hammersmith,
London W6

Friday November 25th 10am - 6pm
Saturday November 26th 10am - 6pm
Sunday November 27th 10am - 4pm

Why not bring the family to the show and enjoy a
weekend in London? We have arranged a complete
hotel package for our visitors to the exhibition. All
inclusive rail tickets also available. Send now for
details of what we, the organisers, can offer you.

Write to:
Breadboard '83
ASP Exhibitions
145 Charing Cross Road
London WC2H 0EE

This year's features include

- Computer controlled model railway competition.
(send off for entry form now)
- Kits to build all sorts of projects.
- Magazines and books covering most aspects of
electronics.
- Components and tools at bargain prices.
- Technical advice on electronics projects and Ham
Radio technique.
- Clubs/User groups for amateur electronics and
computing
- Lectures by professionals on a wide range of
topics. eg. Basic Tuition For Beginners,
- Holography and Producing Printed Circuit
Boards.

TV STORAGE SCOPE

The ETI Telescope is so simple, it's surprising no-one thought of it before. Well, they did, but the new range of high-speed A-to-Ds from Ferranti have made it possible to get the 'scope to work at over 1 MHz, while keeping the price within acceptable limits.

The project splits into two main sections: the logic board, featured here, and the memory board, to be featured next month. Unfortunately, you need both circuit diagrams in front of you to understand how the creature works, so we'll have to save the overall explanation until then.


BUYLINES

Hawk Electronics Test Equipment supply a full kit of parts for this project. All PCBs, the case (drilled and screen-printed), the ZN441 and all the other components are included, together with a comprehensive manual. The kit price is £89. The 'TeleScope' is also available built and tested for £109.

The manual may be purchased separately for £1.50, refunded on the subsequent purchase of a kit or finished circuit.

Prices exclude 15% VAT, and postage and packing is £2.95 extra. The case, A-to-D converter, and the PCBs may all be purchased separately.

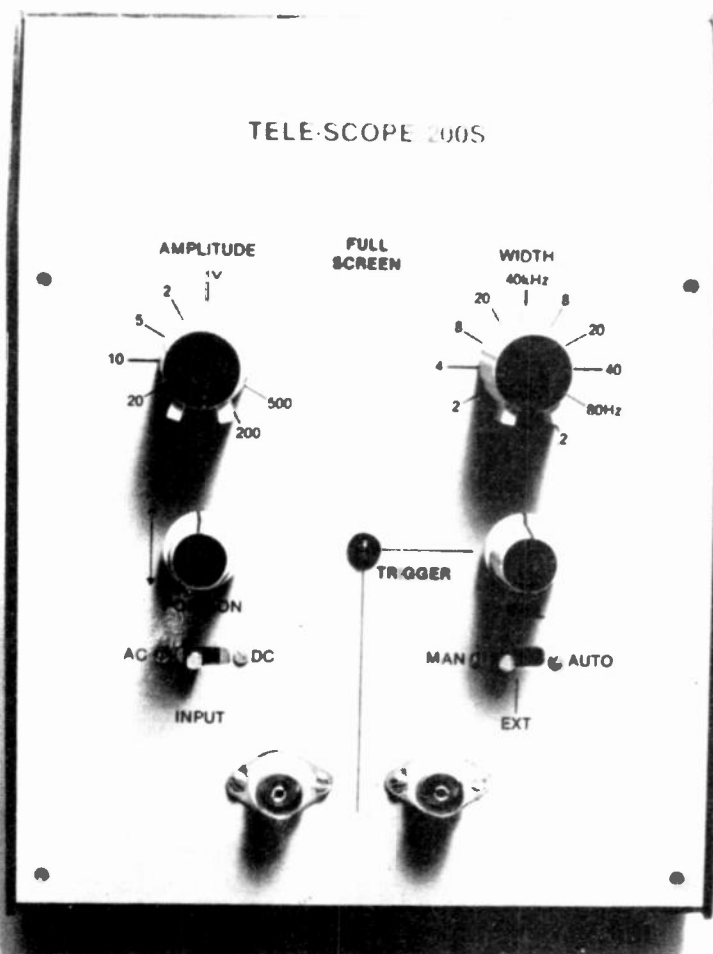Hawk Electronic Test Equipment,
Unit 1,
Park Wood Industrial Estate,
Bircholt Road,
Maidstone,
Kent.



HOW IT WORKS

The input attenuator is a series chain of resistors to ground, whose collective resistance is 1M Ω . The front panel amplitude switch (SW2) provides the voltage range select by tapping from this chain. The capacitors connected to the chain (C2-7) compensate for the inductive effects of the resistors at high frequencies.

The input may be AC or DC-coupled by switching C1 in and out of circuit with SW1.

The trigger select switch SW3 provides either an input signal trigger, an auto trigger (a 2 kHz signal derived from the sample rate switch), or an external trigger.

Q1 is a source-coupled FET which buffers the input signal between the input series chain variable attenuator and the flash A-to-D converter (which will be described in the next article). Q2 acts as a current source, enabling a DC offset to be added to the input signal. This offset is adjusted by RV1 and is used to shift the vertical position of the displayed trace. Q3 and RV2 set the trigger level, and LED1 is lit when the trigger is running.

IC2a is a D-type flip-flop, which enables the input address clock (IC3a) on

the leading edge of the input data via the trigger level. It is held in the reset state by a signal on pin 1 (from inter-board link 5) when the input addressing is completed.

IC4a-c and the crystal XTAL1 form a 10 MHz oscillator and ICs 6 to 10 provide a series dividing network at divide-by-5 and divide-by-2 stages, thus producing division in steps of 10, 5, and 2 etc down to 100 Hz. The sampling rate is selected from this chain by the rotary switch on the front panel. IC13a is a divide-by-2 and is used as the output address clock at 5 MHz. It is also used to re-time the data out to the modulator via IC11a.

IC2b is a D-type flip-flop which is enabled by a line synchronisation pulse thus enabling IC3b. IC3b then allows IC14 to count eight pulses, each of one microsecond duration, before the output clock cycle is started (by IC7b). This produces an eight microsecond delay at the beginning of each line, so all data is displayed and none of the output is outside the video display area. When the output address cycle is completed (50 microseconds later), this counter resets and waits for the

reset line sync pulse.

In the same manner, IC18, 12b and 19 count line synchronisation pulses at the beginning of each field scan to enable the video output only during the middle 256 lines of interlaced scanning.

By dividing the 1 MHz signal by 16 using IC15 and IC16a, we produce a signal of 15.625 kHz, and IC17a, a monostable, then produces the line synchronisation pulses (4.7 microseconds wide), which are mixed into the UHF modulator by IC12c and 12d. IC17b produces the field synchronisation pulses from the 50 Hz clock provided by IC16b: these are approximately 50 microseconds wide. IC11b provides the control lines to switch over the memories and addressing. This changeover occurs when the input address counter has completed its cycle and the frame scan is completed.

The summing circuits used to mix the video data and the line and field synchronisation pulses are the open-collector gates IC12c and 12d at the UHF modulator input, with the resistor network providing the DC offset and modulation depth required to drive the video circuitry.


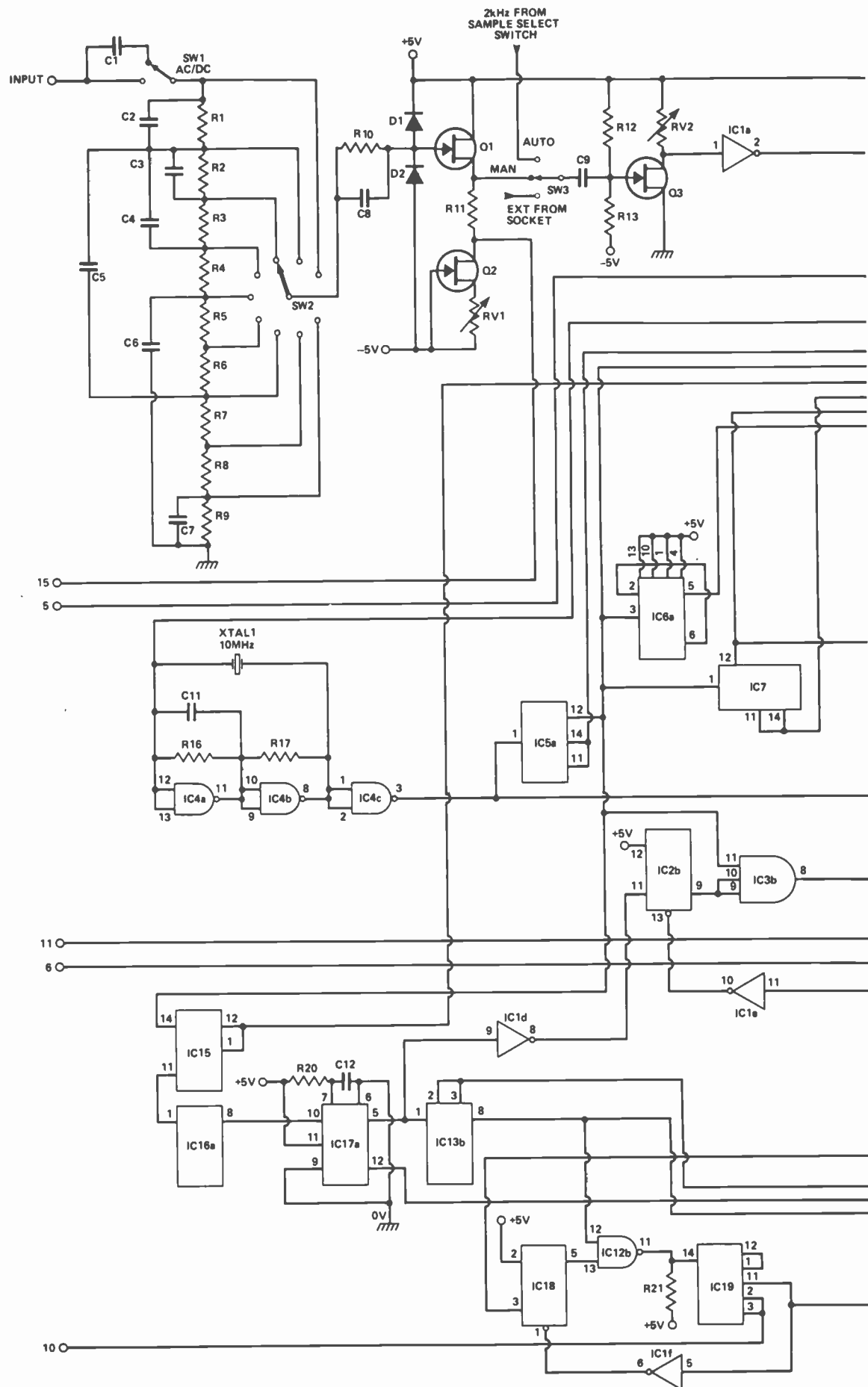


Fig. 1 Circuit diagram of the ETI 'TeleScope' logic board.

PROJECT : Oscilloscope

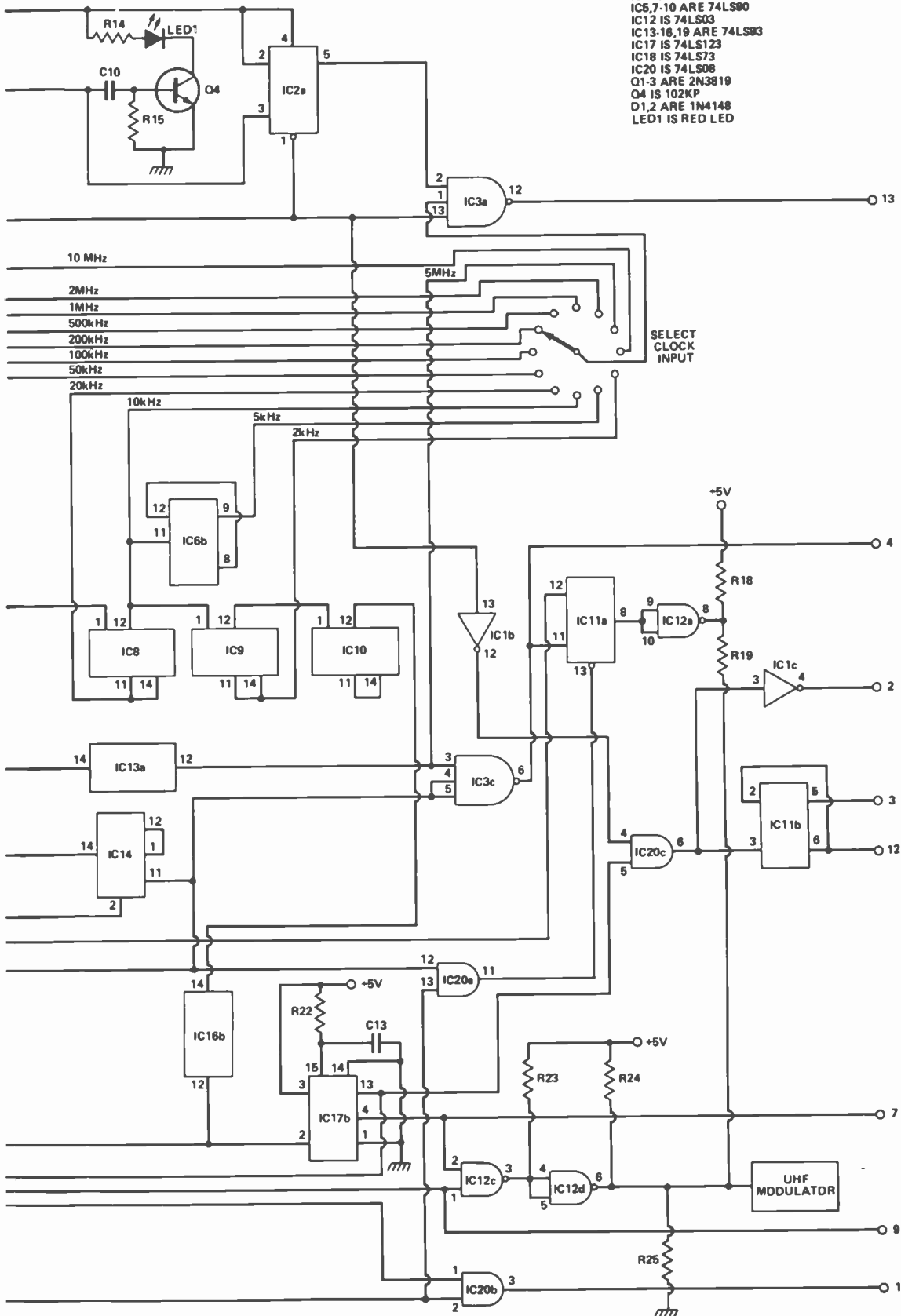NOTE:
 IC1 IS 74LS04
 IC2,8,11 ARE 74LS74
 IC3 IS 74LS10
 IC4 IS 74LS00
 IC5,7,10 ARE 74LS90
 IC12 IS 74LS03
 IC13-16,19 ARE 74LS93
 IC17 IS 74LS123
 IC18 IS 74LS73
 IC20 IS 74LS08
 Q1-3 ARE 2N3619
 Q4 IS 102KP
 D1,2 ARE 1N4148
 LED1 IS RED LED



Do you think that designing and understanding electronic circuits is beyond you?

The summer edition of Electronics Digest, *Gateway To Circuit Design*, provides a step-by-step introduction for the newcomer to the art of circuit design. Firstly, you'll be introduced to the commoner electronic components — but not in a passive way. Electronics is a practical subject, so *Gateway To Circuit Design* will enable you to build simple circuits for yourself, and take measurements on them (along the way learning how to use a multimeter). Once these introductions are over, *Gateway To Circuit Design* shows you what goes into the design of a wide range of electronic equipment — for audio, computing and electronic music, for instance.

Gateway To Electronics is an occasional popular series in Electronics Digest, published by Argus Specialist Publications. Previous issues in the series have concentrated on projects; now we'd like you to design your own!

At all good newsagents now or available by post from Electronics Digest, 513 London Road, Thornton Heath, Surrey.


We'd like to show you that you're wrong



£1.85

NEW POSTER PROGRAMS No. 2 75p

FROM THE PUBLISHERS OF ZX COMPUTING

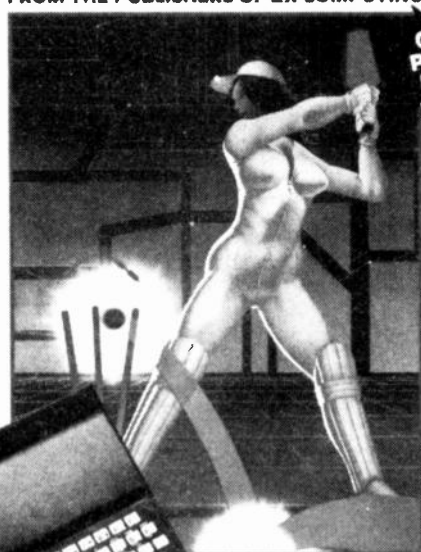

GIANT POSTER INSIDE

An exciting graphics/text simulation game for the ZX-81

NEW!

COMPUTER PROGRAM PLUS GIANT POSTER

Test
MATCH

75p from all good newsagents

OUT NOW

pantechnic

THE POWERFET
SPECIALISTS

OEM USERS

Pantechnic present the most adaptable high powered amplifier ever.

FET SYSTEM AMP

Features:

- HIGH POWER. 1.2KW (single ended).
 - LOW VOLUME. 1/15 Cubic foot inc. Heat Sink.
 - VERSATILE. Delivers more than 1KW into 1/2 to 8 ohms.
- OR 2 x 600W into 2 to 8 Ω
OR 4 x 300W into 2 to 4 Ω (200W into Ω)
1 x 600W into 2 to 8 Ω
OR 1 x 300W into 2 to 4 Ω
1 x 150W into 4 to 8 Ω

Etc. Etc.

Having been closely involved in a wide variety of OEM applications of their amp boards, Pantechnic became aware of numerous implementation problems often left untackled by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The **SYSTEM** Amp offers 1.2KW of power in a space of 102mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the **PANTECH 74** Heat Exchanger, newly designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heat sinks, heat sinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2KW amp stems from its division into 4 potentially separate amplifiers of 300W each (downrateable with cost savings to 150W.) These can be paralleled, increasing current capability or seriesed (bridged in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

As ever Pantechnic offer a full range of customising options including DC coupling, ultra high slew etc. Contact Phil Rimmer on 01-800 6667 with your particular application problem.

P.S. Specs, as ever, are exemplary.

OTHER POWERFET AMPLIFIER MODULES

Model	Price	Range (Rms)	Dyn-loads	Notes
*PFA100	20.65	50-150W	4 Ω , 8 Ω	Physically small (32 x 78 x 108mm)
*PFA200	27.35	100-300W	4 Ω , 8 Ω	High watts/£ ratio
PFA/HV	36.04	200-300W	4 Ω , 8 Ω , 16 Ω	5dB dynamic headroom Drives 70V line direct.
*PFA500	42.00	250-600W	2 Ω , 4 Ω , 8 Ω	25A cont. output current.
	52.50	mounted on type 74 Heat Exchanger (see below)		

*The power output of these amplifiers can be increased by approx 15% with no diminution in quality by adding PSU102 (£7.61) to your existing power supply.

Some Other Products & Components

Type 74 Heat Exchanger. Dissipates 300 W (1.2KW fan cooled) £7.50

25A 400V Bridge Rect. £2.17

10,000uF 80v electrolytic with clip £4.13

PAN20 Pre-amplifier module. Very low noise and distortion £7.61

PAX2/24 2 Way active crossover (specify frequency) £10.10

PSU103 Powers 2 x PAN20 + 2 x PAX2/24 £8.91

PAN1397 20W power amp. (LOW THD) £5.04

PSU101 Powers 2 x PAN1397 £3.43

Transformer for above £4.30 (inc. postage)

TOROIDAL TRANSFORMERS

with special low flux windings

Nom. VAC	160VA	225VA	300VA	500VA	625VA	750VA
40-0-40	10.43	12.00	13.04	—	—	—
45-0-45	—	12.00	13.04	18.96	—	—
50-0-50	—	—	—	18.96	19.84	22.00
70-0-70	—	—	—	18.96	—	—

(for PFA/HV)
Transformer prices include postage. Ask for leaflet "Choosing a Transformer."

Carriage 75p. Add VAT at 15% to all prices.

THE POWERFET SPECIALISTS
pantechnic

Mail order only to:


Dept ET1/7 148 Quarry Street, Liverpool L25 6HC

Telephone: 051-428 8485

Technical enquiries

Phil Rimmer 01-800 6667

BRITISH LOW COST PRECISION OSCILLOSCOPES

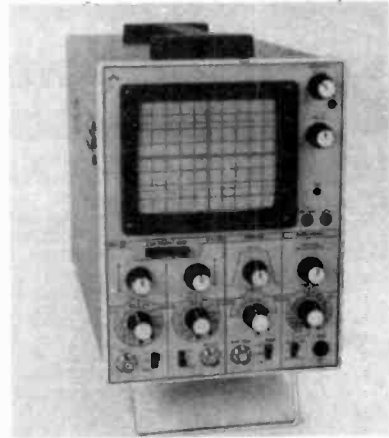

Safgan Electronics Ltd., a small British company specialising in the design and manufacture of Oscilloscopes, are pleased to announce the introduction of the DT-500 Series of 5" Tube Oscilloscope.

They believe that the new range offers a Specification ideally suitable for Colleges, Training Establishments and Service Engineers, due to the easy to use logical lay-out of the front panel, combined with the lowest cost for any dual trace precision Oscilloscope available in the U.K. The DT-520 has an 8x10 cm display, 5 mv/cm sensitivity, a timebase range from 1 second/cm to 100 nanosecond, T/V trigger, X-Y, and Z modulation input, with a sweep output socket and is priced at £210. —

The DT-525 has the same specification plus an add/invert facility and 25 MHz bandwidth, at £230. —

Both versions are available with 4mm sockets if required.

Please contact

Safgan Electronics Ltd.,
Omega Road, Woking, Surrey GU21 5DY
Tel: (04862) 24731 or 24736

SIMPLE PLUG-IN CENTRONICS INTERFACE



- Recognises LLIST and LPRINT which allows programs to be listed directly from your Spectrum
- Also allows printout direct from BASIC listings without the need for special user calls
- Completely self contained with 1 metre of ribbon cable and connectors
- Works with any Centronics Interface including all Epsoms, Seikosha 100A, OKI Microline 80 etc
- Includes driving software which allows up to 128 characters per line
- Full range of business software available
- Fully tested and guaranteed for 12 months

Plus £1.00 P + P

Trade Enquiries
Welcome

KEMPSTON
MICRO ELECTRONICS

Dept ET1 7, 180a Bedford Road, Kempston, Bedford MK42 8BL

electronize

AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT

TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION



IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "miss, misfires" whilst an electronic filter smooths out the effects of contact bounce etc.
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:
Performance at only 6 volts (max. supply 16 volts)
 SPARK POWER — 140W, SPARK ENERGY — 36mJ
 SPARK DURATION — 500µS, STORED ENERGY — 135mJ
 LOADED OUTPUT VOLTAGE
 50pF load — 38kV, 50pF + 500k — 26kV
 We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **All ELECTRONIZE electronic ignitions feature:**
EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most NEW CARS already have electronic ignition. Update YOUR CAR

PROTECT YOUR CAR WITH AN ELECTRONIZE ELECTRONIC ALARM



- ★ **2000 COMBINATIONS** provided by an electronic key - a miniature jack plug containing components which must match each individual alarm system. (Not limited to a few hundred keys or a four bit code).
 - ★ **60 SECOND ALARM PERIOD** flashes headlights and sounds horn, then resets ready to operate again if needed.
 - ★ **10 SECOND ENTRY DELAY** allows owner to dis-arm the system, by inserting the key plug into a dashboard mounted socket, before the alarm sounds. (No holes in external bodywork, fiddly code systems or hidden switches). Re-closing the door will not cancel the alarm, before or after it sounds, the key plug must be used.
 - ★ **INSTANT ALARM OPERATION** triggered by accessories or bonnet/boot opening.
 - ★ **30 SECOND DELAY** when system is armed allows owner to lock doors etc.
 - ★ **DISABLES IGNITION SYSTEM** when alarm is armed.
 - ★ **IN KIT FORM** it provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, CMOS IC's, random selection resistors to set the combination, in fact everything down to the last nut and washer plus easy to follow instructions.
- FITS ALL 12 VOLT NEGATIVE EARTH VEHICLES.
 SUPPLIED COMPLETE WITH ALL NECESSARY LEADS
 AND CONNECTORS PLUS TWO KEY PLUGS**

Don't Wait Until Its too Late ~
Fit one NOW!

fill in the coupon and send to:

ELECTRONIZE DESIGN Dept D · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

TOTAL ENERGY DISCHARGE (6 or 12 volt negative earth)

- ☐ Assembled ready to fit £26.70 £19.95
☐ D.I.Y. parts kit £15.90 £14.95

TWIN OUTPUT for cars and motor cycles with dual ignition

- ☐ Twin, Assembled ready to fit £36.45 £29.95
☐ Twin, D.I.Y. parts kit £24.55 £22.95

INDUCTIVE DISCHARGE (12 volt only)

- ☐ Assembled ready to fit £15.95 £12.75

Prices Include VAT.

P+P £1.00 (UK)

CAR ALARM

- ☐ Assembled ready to fit £37.95
☐ D.I.Y. parts kit £24.95

I enclose cheque/postal order OR debit my Access/Visa card




Name _____

Address _____

Code _____

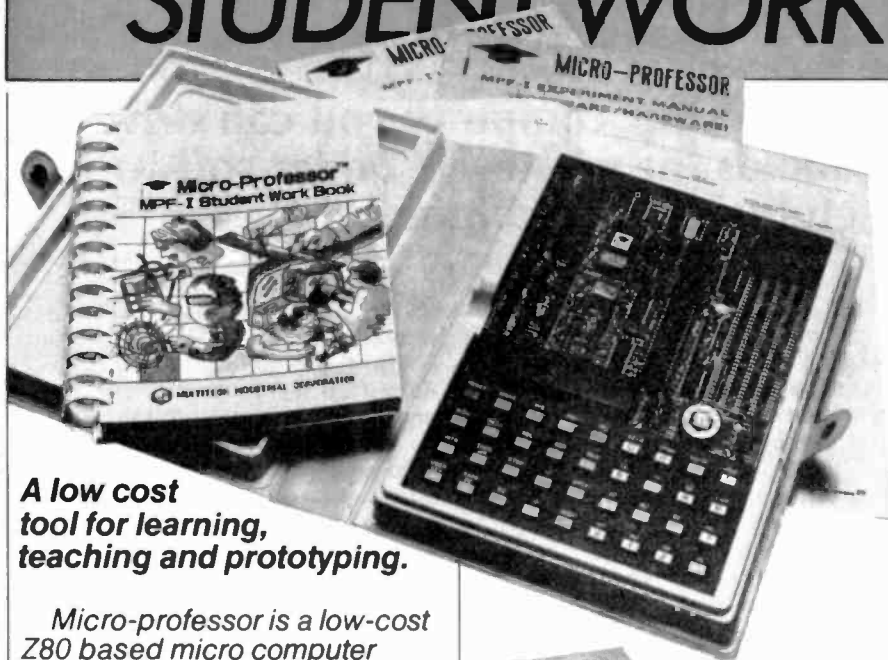THE COMPLETE PACKAGE! MICROPROFESSOR PLUS THE STUDENT WORK BOOK



**A low cost
tool for learning,
teaching and prototyping.**

Micro-professor is a low-cost Z80 based micro computer which provides you with an interesting and inexpensive way to understand the world of microprocessors.

Micro-Professor is a complete hardware and software system and is a superb learning tool for students, hobbyists and microprocessor enthusiasts, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.


Micro-Professor **£99.50**
(+£4.00 p&p)

Now with the Student Work Book available Flight offer you the complete package. An easy to follow manual that will help further your understanding of microprocessors.

Student Work Book **£16.00**

FLIGHT
Electronics Ltd.

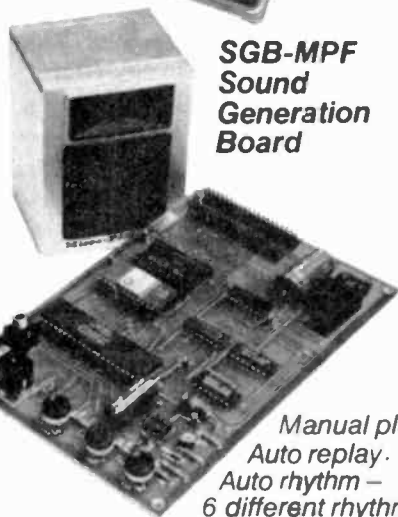Micro-Professor is a trade mark of Multitech Industrial Corporation. Z80 is a trade mark of Zilog Inc.




**SGB-MPF
Sound
Generation
Board**

Manual play,
Auto replay.
Auto rhythm –
6 different rhythms,
Sound Synthesizer
and Hi-fi speaker.




**EPB-MPF EPROM
Programming Board**

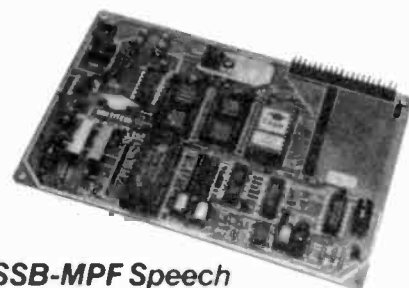For all +5V 1KB/2KB/4KB EPROMS
Read/Copy/List/Verify Capability.



**SSB-MPF Speech
Synthesizer Board**

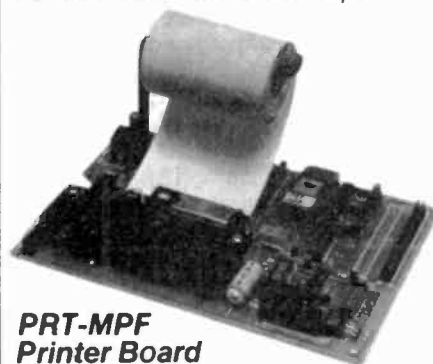A vocabulary of up to 400 words
based on the TMS 5200 chip.



**PRT-MPF
Printer Board**

Memory dump utility. BASIC
program listing. Z80 disassembler.

Please send me	Qty
Micro-Professor	£99.50
	(+£4.00 p&p)
Student Work Book	£16.00
SGB-MPF board	£79.50
EPB-MPF board	£99.50
SSB-MPF board	£99.50
PRT-MPF board	£86.25
I enclose cheque/P.O. for £.....	

Name

Address

Mail Order only
Prices include VAT. Please
allow 28 days for delivery.



By phone or post

FLIGHT ELECTRONICS LTD.
Quayside Rd. Southampton,
Hants SO24AD. Telex. 477793.
Tel. (0703) 34003/27721.

COMPUTER OUTPUT DRIVER

With this project hooked up to your computer you can drive relays, motors, lamps, solenoids, or whatever, under software control. Do something useful with your computer! Design by Geoff Nicholls.

A personal computer need not necessarily be used for playing games, learning programming or producing computer club newsletters. With this project, you can put it to some *practical* use. Just what that is I'll have to leave to your imagination and ingenuity!

Two independent groups of eight outputs are provided. Each of the 16 output driver circuits is configured to run from a 12 V supply, although higher supply voltages may be used. Each can be configured to sink up to 3 A. Simple address selection for the board is provided by an on-board DIP switch. It's a pretty straightforward project and you can vary things to suit your application(s).

Component Options

The component values shown in the circuit diagram are for output currents of up to 2 A. If other load currents are desired, then a few components need changing in order to reduce power dissipation in the output transistors.

For currents of less than 1 A, the TIP31Bs (Q17-32) may be replaced by BD139s — which have the distinct advantage of costing considerably less than TIP31Bs. However, note that BD139s have a different pinout such that the metal face on BD139s is on the opposite side of the package to the TIP31Bs.

The base current drive to the output devices is determined by R17 and R32 and may be optimised for different loads. The table here (Table 1) summarises component values for various output currents.

If the total output current is expected to exceed 20 A for more than a few minutes, then it is advisable to make the following changes:

(a) Use a terminal strip capable of passing half of the total load current through each terminal OR solder the power ground directly to the PCB ground plane.

(b) Solder several lengths of tinned copper wire to the heavy power ground track on the PCB.


Intermittent use over 20 A should not require these changes. The power dissipation calculations for transistors Q17 to Q32 were based on data for RCA-manufactured TIP31Bs. The prototype transistors developed a collector-emitter voltage of 0V65 at 2 A, which does not necessitate heatsinking the transistors. If high current loads are to be used, measure $V_{CE} \times I_C$.

The TIP31B can dissipate 2 W at 25°C ambient without heatsinking. Continuous use at high currents may require a small flag heatsink on each TIP31B.

The entire electronics for this project is mounted on a double-

sided PCB. During the early design phase, it was found that a single-sided PCB would require an unacceptably huge number of links. To keep the cost down, through-hole plating was not specified for this board and connections between top and bottom side tracks are made with links of 22 swg tinned copper wire, of which there are a total of 61. IC sockets were installed on the prototype, but these are not essential.

Commence construction by giving the PCB a good inspection, looking for broken tracks and undrilled holes. Make sure the tracks are clean and bright so that soldering is easily carried out. Insert all the links first. These are identified on the component overlay diagram by a ●. Note that a large star is next to a '62nd' link more or less in the centre of the board. This is the optional 0 V link — see the text under the heading 'Power supplies'.

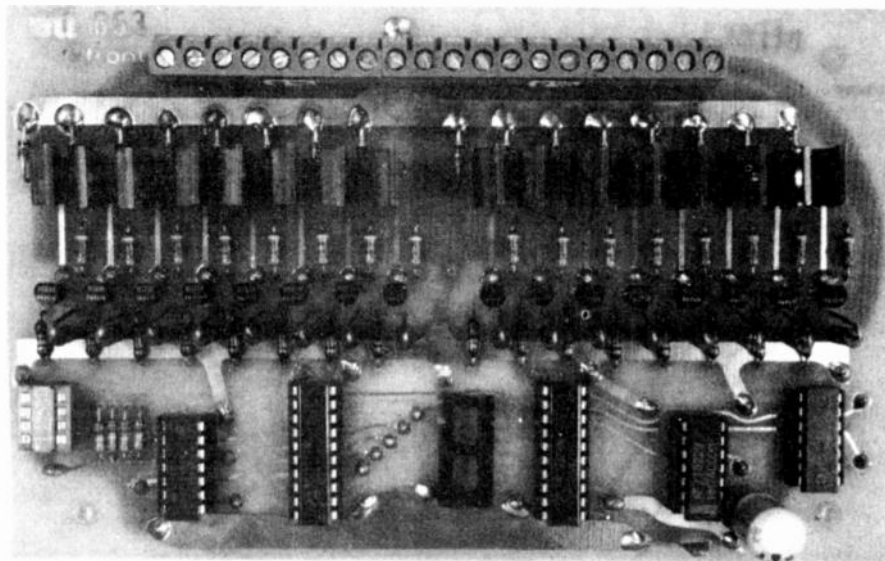

The project is built on a board measuring 103 × 165 mm.

HOW IT WORKS

First of all, note that the component values shown on the circuit diagram are for the 2 A output version. Other output current versions are possible, as explained in the text, but basic circuit operation is the same.

The host processor connects to the driver board via the 16-pin DIL socket. IC5 compares the logic levels present on the DIL socket pins 14 (A1), 11 (A2), 13 (A3) and 12 (STROBE) to the settings of SW1a-d respectively. When a match is found, pin 10 of IC1 goes high. The STROBE input should receive a pulse edge timed to coincide with a valid data bus (pins 1 to 8 of the DIL socket) and a valid address (pins 11, 13, 14). Note that either a positive-going or a negative-going edge of the strobe pulse may be used, according to whether the setting of SW1d is closed or open, respectively.


The A0 input on pin 10 of the DIL socket determines which of the two on-board latches are being addressed. When pin 10 is low, IC4 is selected ('B outputs active'), if high, then IC3 ('C outputs active').

Each driver circuit buffers one of the 16 latch outputs and provides an open collector current sink of up to 3 A (see the text on 'Component options').

To simplify the description of the driver circuits, consider the one comprising R1, Q1, R17, R33, Q17 and D1. Diode D1 is a flywheel diode and protects transistor Q17 from excess back emf voltage when turning off inductive loads, such as a solenoid. When the latch output is low, Q1 is held off via R1 and Q17 is held off by R33. Resistor R33 speeds up the turn-off time of Q17 by providing a path to remove stored charge in the base-emitter junction.

When the latch output is high, about 5 mA of current flows into the base of Q1, thus turning it on. R17 sets the base current of Q1 and is chosen according to the output current requirement. Transistor Q17 must be saturated in order to reduce power dissipation and up to 300 mA of base current may be required for 3 A loads (see component options in main text).

Fig. 1 Circuit diagram for the ETI Computer Output Driver. Our artist drew the line (!) at reproducing 16 identical driver circuits, so we've shown just the one.

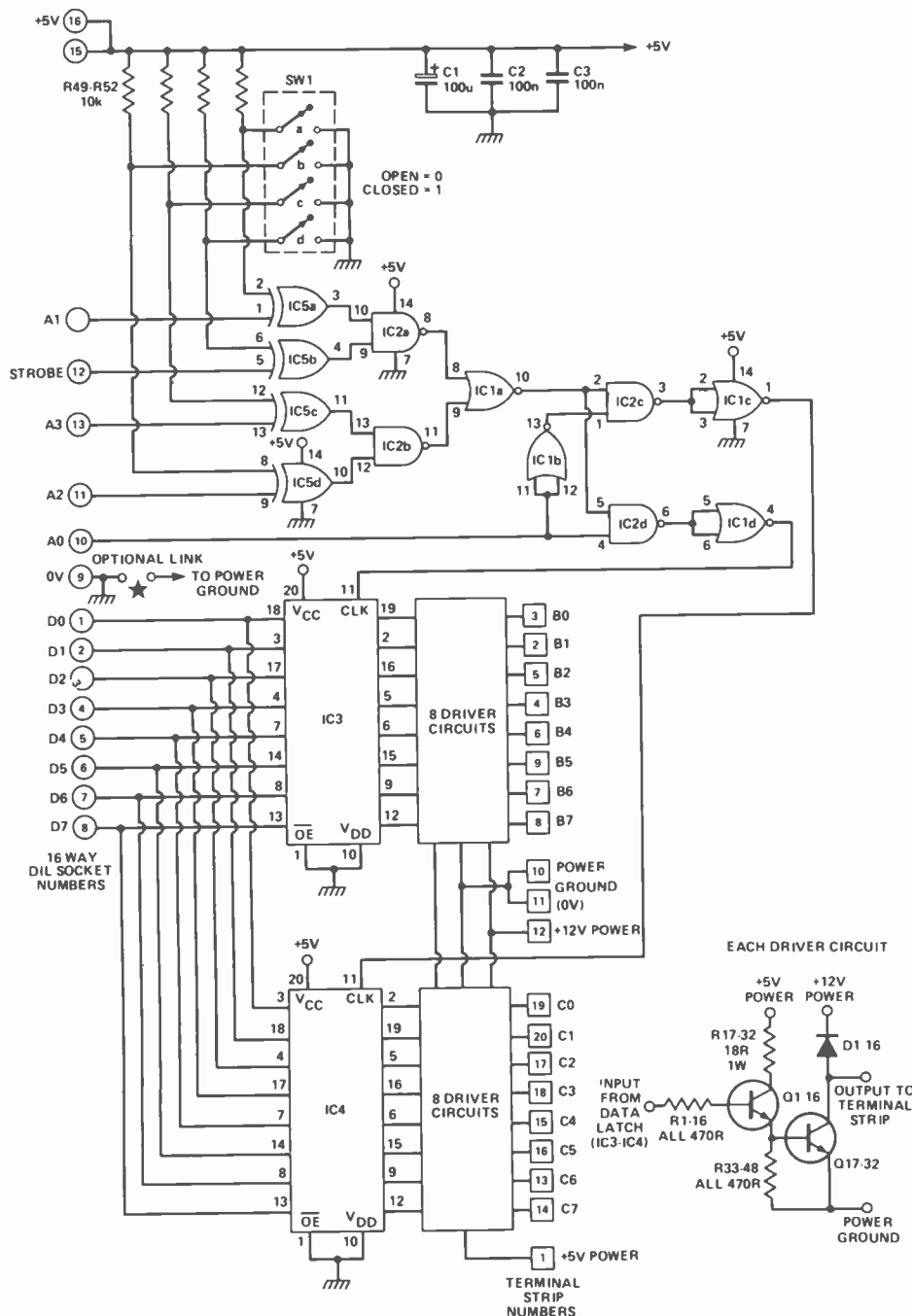

Next, solder diodes D1 to D17 in place. Note that the cathodes of these diodes are soldered on the component side of the board. Solder resistors R1 through R16, then R33 through R48 in place next. Mount and solder the BFR39 transistors, Q1 to Q16, in place next. All the 1 W resistors, R17 through R32, stand up on end and these may be soldered in place after the transistors. Follow with the remaining four resistors and the three capacitors. Now you can mount and solder in the output devices, Q17 to Q32. Watch orientation.

Now mount SW1, but take care you put it round the right way. The ON position of the switches should be adjacent to the edge of the board. If you're using IC sockets, put these on next. If not, solder the ICs in place. A 16-pin DIL IC socket is used for the input connections and this can be mounted now. Last of all, mount and solder in the output terminal strip or strips. We used one 12-way and one 8-way strip as we could not obtain a single 20-way strip.

Having completed the construction, go over the board very carefully, looking for missed

links and components, bad joints or mis-oriented semiconductors. Fix any faults and, if you're satisfied all is well, the best way to test the board is to hook it up and try it out!

Power Supplies

The logic power supply of +5 V should be supplied from the host computer V_{cc} rail through the DIL socket pins 15 and 16. The computer's ground (0 V) should be connected to pin 9.

The +5 V power to the drive circuits should not come from the host computer unless it has the

PARTS LIST

Resistors (all $\frac{1}{2}$ W, 5% except where stated)

R1-16, 33-48 470R
R17-32 18R, 1W
R49-52 10k

Capacitors

C1 100uF 16 V PCB electrolytic
C2,3 100n ceramic

Semiconductors

IC1 74LS02
IC2 74LS00
IC3,4 74LS374
IC5 74LS86
Q1-16 BFR39
Q17-32 TIP31B, BD139 (see text)
D1-16 1N4002, 1N4004 etc

Miscellaneous

SW1 4-way SPST DIP switch
PCB (see Buylines); 16-pin DIL socket; 2 off 16-pin DIP headers; one off 12-way and one off 8-way PCB-mounting terminal strips; 16-way ribbon cable; 22 swg tinned copper wire.

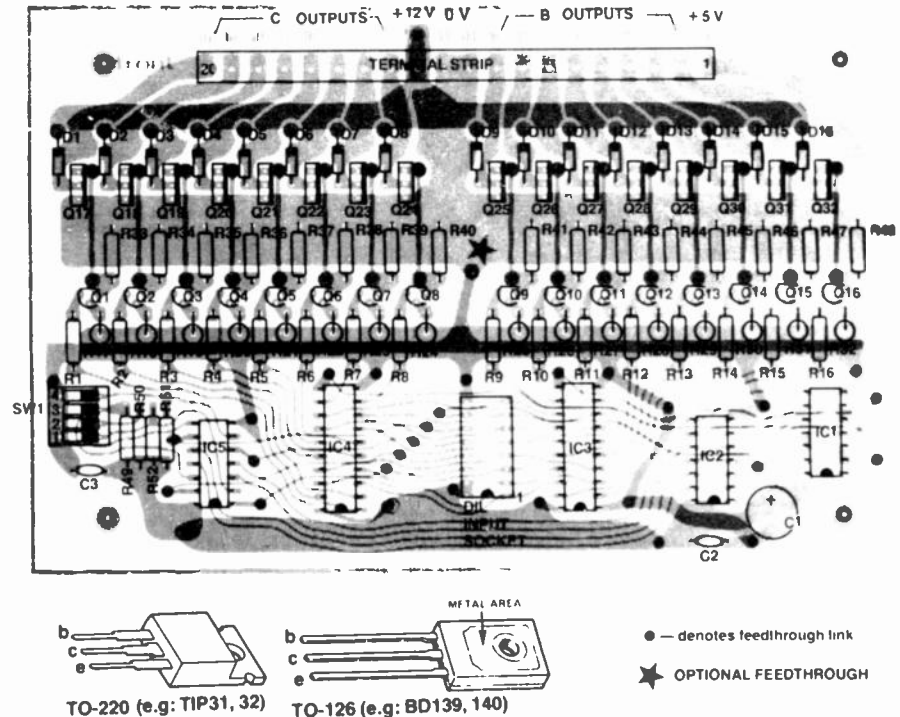


Fig. 2 Component overlay for the driver board, and lead details for some suitable output transistors.

BUYLINES

No severe supply problems are anticipated with anything we've used for this project. The hardest thing to find will probably be the PCB-mounting terminal strips, but Maplin, at least, stock a suitable type, and you may be able to find other suppliers too. The PCB will, as usual, be available from the PCB Service as advertised on page 91.

TABLE 1

OUTPUT CURRENT (amps)	Q17-32	R17-32	R1-16	+5V SUPPLY CURRENT (maximum)
3	TIP31B	15R, 1W	330R	3A4
2	TIP31B	18R, 1W	470R	2A8
1	TIP31B	22R, $\frac{1}{2}$ W	470R	2A3
<1	BD139	33R, $\frac{1}{2}$ W	470R	1A6

capability to supply at least an extra 3 A. In any case, heavy wire should be used (at least 24 x 0.2 mm hookup wire) for the power connections to the terminal strip to minimise voltage drop.

The optional 0 V link (marked with a star) should only be used for light loads. Normally, the connection between 0 V logic and power should be at the power supply.

The output drivers' power supply is shown as +12 V, but other voltages may be used, up to about 70 V. The PIV rating of diodes D1 to D16 should not be exceeded, however (best use 400 V diodes here, at least).

Hooking It Up

This project has been designed to allow up to eight boards to be connected to a computer through a single ribbon cable. In order to do this a special strobe signal must be

supplied by the computer whenever any of the driver boards are being selected. This will probably require a small hardware circuit, unless your computer is favoured by the famous Murphy! If there is sufficient interest we may publish a general purpose interface board, but until then you will have to work out for yourself how to connect a particular computer from the following guidelines.

Assuming that the computer has an I/O scheme with eight I/O address lines — AD0 to AD7 — then the driver board inputs A0 to A3 are connected to the lowest four I/O address lines of the computer, ie AD0 to AD3. Each driver board is then set up at a different address via the DIL switches, SW1a-d. This means that the driver boards will occupy 16 consecutive I/O ports. Now for the hard part!

The STROBE input (A4) must have a positive or negative going edge (see the How it Works box)

that occurs when an I/O WRITE to the driver boards is taking place. In order to fully decode the I/O port address space, the other I/O address lines (AD4 to AD7) must be gated with the I/O control signals to produce the STROBE signal. In order to get the STROBE transition timing correct, a signal such as WRP (write pulse) should also be gated in the STROBE logic. This allows the data bus to settle before the latches are locked.

The ribbon cable requires a buffered driver for each wire carrying logic signals, especially if multiple driver boards or long cable runs are envisaged.

A simpler interconnection may be implemented if a couple of I/O ports are available. In this case, the D0-D7 inputs can connect to one output port and the A0-A4 inputs to another output port. The timing of the STROBE pulse is then a matter of software driving routines.

ETI

The Proto-Board®

Now circuit designing is as easy as pushing a lead into a hole ...
 No soldering
 No de-soldering
 No heat-spoilt components
 No manual labour
 No wasted time



For quick signal tracing and circuit modification
 For quick circuit analysis and diagramming
 With or without built-in regulated power supplies
 Use with virtually all parts — most plug in directly, in seconds.
 Ideal for design, prototype and hobby

NO.	MODEL NO.	NO OF SOLDERLESS TIE-POINTS	IC CAPACITY (14-pin DIPs)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB6	630	6	11.00	13.80	Kit
2	PB100	760	10	14.25	17.53	Kit
3	PB101	940	10	19.65	24.32	
4	PB102	1240	12	24.95	30.42	
5	PB103	2250	24	40.95	48.82	
6	PB104	3060	32	51.45	61.47	
7	PB105	4560	48	74.50	87.98	
8	PB203	2250	24	76.00	89.70	5V@1A
9	PB203A	2250	24	105.00	124.20	5V±15V
10	PB203AK	2250	24	85.00	100.05	5V±15V & Kit

Tomorrow's tools for today's problems

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 9U
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477

G.S.C. (UK) Limited, Dept. 9U, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

1 ☐ Only Req 2 ☐ Only Req 3 ☐ Only Req 4 ☐ Only Req 5 ☐ Only Req 6 ☐ Only Req 7 ☐ Only Req 8 ☐ Only Req 9 ☐ Only Req 10 ☐ Only Req

Name Address


Enclose Cheque/P.O. for £ or debit my Barclaycard, Access.

American Express card no exp date

FOR IMMEDIATE ACTION — The G.S.C. 24-hour 5 day a week service
 Telephone (0799) 21682 and give us your Barclaycard, Access.
 American Express number and your order will be in the post immediately

For FREE catalogue tick box ☐

Sinclair ZX Spect

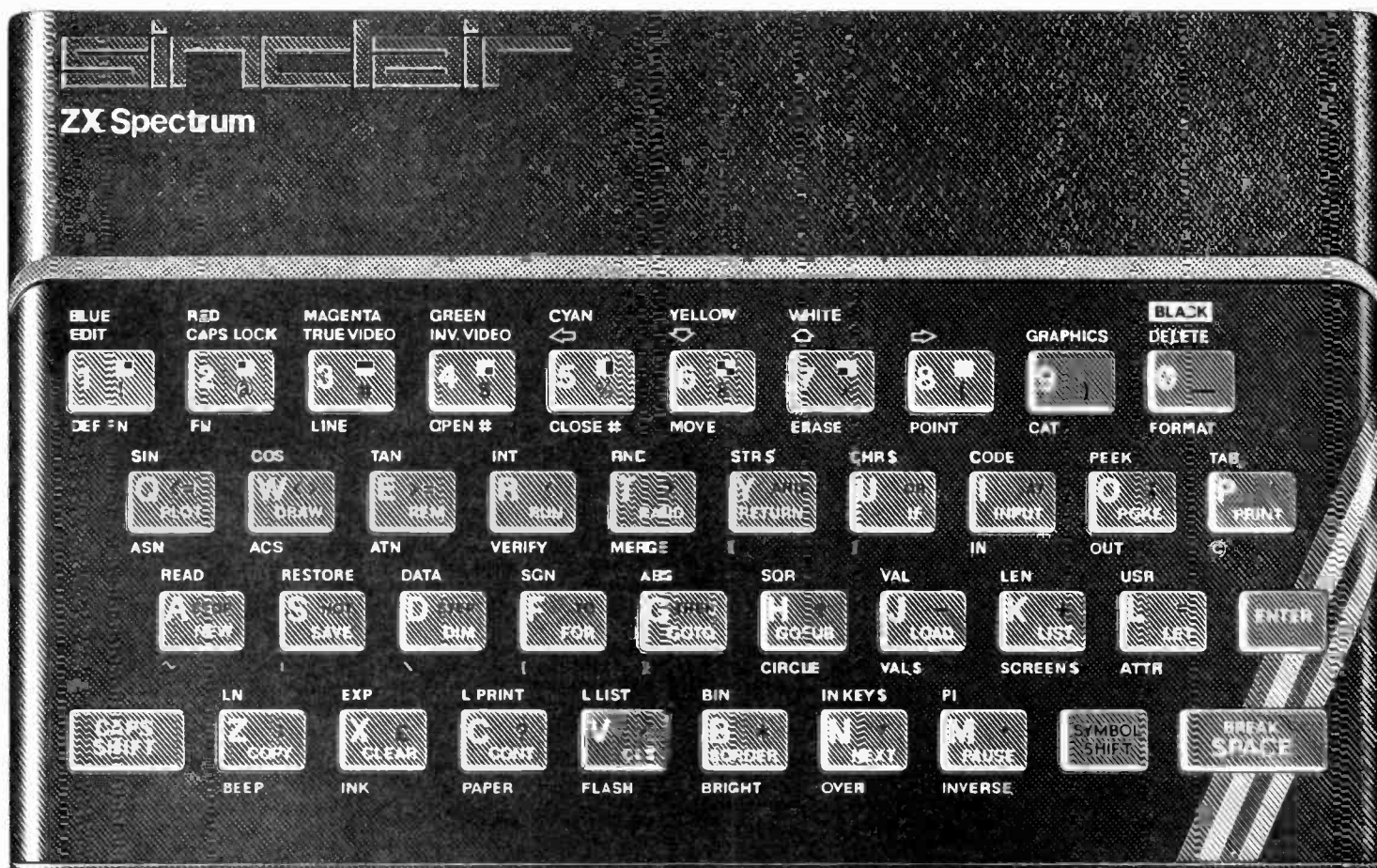

The growing range of Spectrum Software



You'll know already that the Spectrum has generated an enormous range of peripherals and independent software. Our own range is growing very fast and is shown in the Sinclair Software Catalogue – free with every ZX Spectrum.

rum - news!

**16K now
£99^{·95}**
Previously £125.

**48K now
£129^{·95}**
Previously £175.

At last, a 16K colour computer with graphics for under £100!

Why have we done it?


Partly because the sheer volume of Spectrums sold (over 300,000 so far) has brought down unit production costs.

And partly, of course, because we hope you'll buy a Sinclair computer – and not some competitor's promise! We've all heard about colour computers breaking the £100 barrier. Here's the computer that's done it. A colour computer with advanced graphics that's fully supported, and widely available.

Right now, you can order a Sinclair Spectrum at these prices direct from Sinclair on the order form below. And to make it even easier to handle high-level computing at the

lowest possible price, we've cut the cost of the printer, too. At £39.95, it's almost unbelievable!

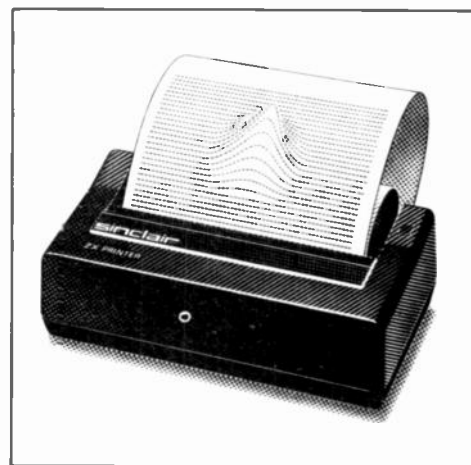At prices like these, there's really no reason to wait.



**ZX Printer now
£39.95**
Previously £59.95

How to order your ZX Spectrum
Access, Barclaycard or Trustcard holders – call 01-200 0200 24 hours a day, every day. By FREEPOST – use the coupon below. Please allow up to 28 days for delivery. 14-day money-back option.

sinclair ZX Spectrum

**Sinclair Research Ltd., Stanhope Road,
Camberley, Surrey, GU15 3PS.
Tel: 0276 685311. Reg no. 1135105.**

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.

Qty	Item	Code	Item Price £	Order
				Total £
	Sinclair ZX Spectrum – 16K RAM version	3000	99.95	
	Sinclair ZX Spectrum – 48K RAM version	3002	129.95	
	Sinclair ZX Printer	1014	39.95	
	Printer paper (pack of 5 rolls)	1008	11.95	
	Postage and packing: orders under £90	0028	2.95	
	orders over £90	0029	4.95	
			Total £	

Please tick if you require a VAT receipt

* I enclose a cheque/postal order payable to Sinclair Research Ltd for £

* Please charge to my Access/Barclaycard/Trustcard account no.

* Please delete/complete as applicable.

Signature

PLEASE PRINT

Name: Mr/Mrs/Miss

Address

ETI 907


FREEPOST – no stamp needed.

Prices apply to UK only.

Export prices on application.

BUYER'S GUIDE TO TEST EQUIPMENT

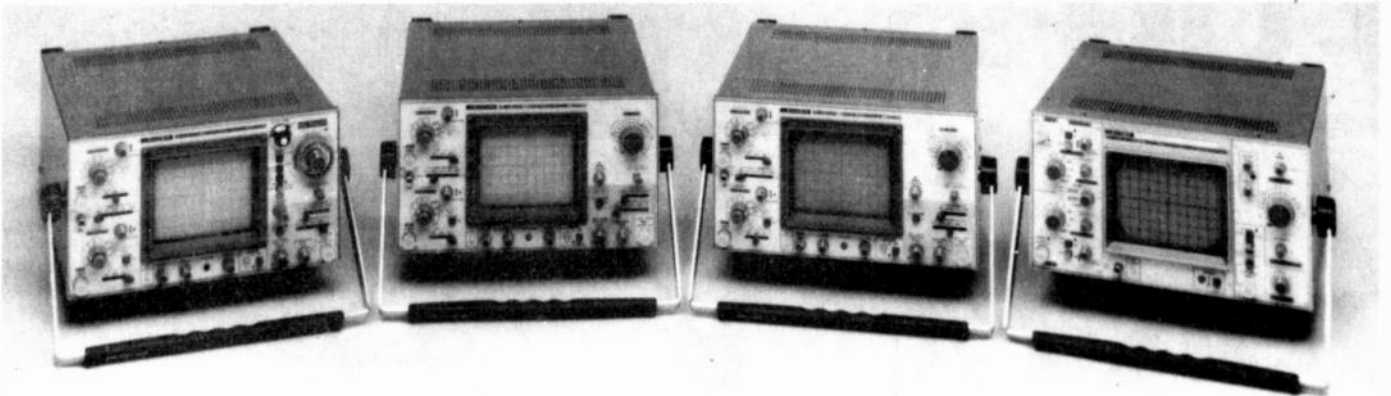This month, all you ever wanted to know about oscilloscopes



but were afraid to ask the man in the shop.

Next to a multimeter, an oscilloscope is the most basic measuring instrument of electronics, yet comparatively few hobbyists possess one. It's true that they're not cheap, we didn't find a single one for less than £100, but they're not that expensive either. In this survey, we've found a very wide choice of instruments is available for around £350 or less (excluding VAT).

All the oscilloscopes in the table have the following basic facilities: a Y-amplifier, with switched calibrated ranges, switchable AC or DC coupling, and a shift control; a timebase generator, with switched ranges, position control, and some means of synchronising sweep commencement at a particular point on the input Y-waveform; an on-off switch, and brightness and focus controls. (None of these features is listed in the table).

All the sensitivities are given in volts per division (note that unless a 'scope has a 130 mm screen, 1 division will be smaller than a centimetre), but not all the sweep speeds are in seconds per division: the two cheapest 'scopes (the Leader LBO-310A and the Trio CS1303D) give sweep frequencies. These two 'scopes, and the Leader LBO-512B, have relatively few calibrated Y and sweep ranges, so you would have to

rely a lot on the variable controls to view, but would not be able to measure intermediate waveforms.

All the other 'scopes have their sweep and voltage ranges in 1, 2, 5 sequences, eg 1 mV/div, 2 mV/div, 5 mV/div, 10 mV/div, etc.

Expansion Options

Scopes with X and Y expansion options (features E and F) will have maximum sweep rates and sensitivities higher than those quoted in the calibrated range columns; expansions are typically $\times 5$ or $\times 10$. However, note that Y-expansion amplifiers usually have a lower bandwidth than the main Y amplifier, sometimes less than 1 MHz, and often decrease the accuracy as well. Variable gain controls, on the other

hand, nearly all decrease sensitivity and variable sweep controls nearly all increase sweep times (from calibrated positions).

As all the scopes have DC coupling, the bandwidth quoted is just the upper limit; in AC coupled modes, the lower -3 dB point is typically 2 Hz.

Trigger Happy


After finding the on/off switch, the next most difficult task on any oscilloscope is persuading the thing to trigger when and where you want it to. The 'scopes we've looked at have a wide variety of trigger facilities, mostly in an attempt to be user-friendly.

Firstly, in nearly all cases you can select triggering from the Y-channel or from an external trigger input. Most dual trace 'scopes allow you to select which Y-channel the triggering comes from as well. Usually the threshold signal level at which you can get any scope to trigger is equivalent to around 0.3 to 1 division on the screen. The vast majority of trigger circuits are AC coupled; DC coupled types are easier to get to trigger on slowly rising waveforms.

A level control and a slope polarity control will allow you to move the trigger point along a waveform. Some 'scopes have a single control that sets

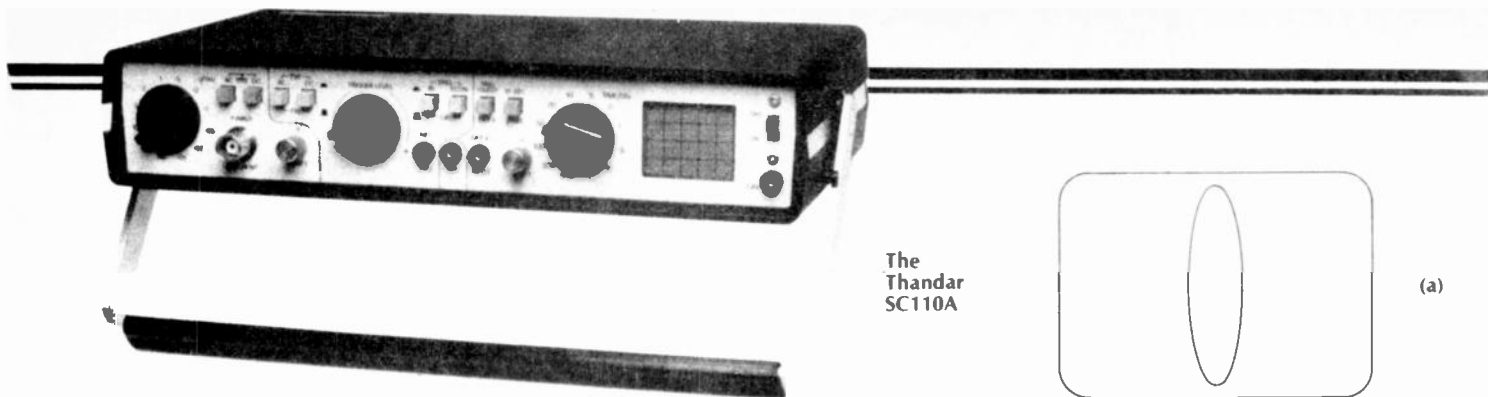The Trio CO-1303D: not quite our cheapest 'scope





The
Thandar
SC110A

both the level and slope polarity (eg, Scopex 4S6, Trio CS1575). A few 'scopes have trigger delay facilities, so that you can delay triggering for a pre-selected time: this is particularly useful for observing pulses with a low but regular repetition rate, because you can set the 'scope to trigger on one pulse, yet wait until just before the next pulse before commencing the sweep. One 'scope in the survey, the Hitachi V302F, achieves this in another manner, by delaying the signal slightly; however, this will only be of use on very high frequency pulses. In any case, trigger delay is extremely useful for general digital work, so that you can pick out sections of words to examine.

Many 'scopes have TV video signal filters (also called LF filters by some manufacturers) that will enable the scope to synchronise to line or frame pulse signals embedded in the video signal. The Scopex 14D10V (similar to the 14D15 in the table) takes this a stage further, by having a delay system that allows any line between number 17 and 312 to be selected and examined.

Some scopes give you the choice between bright line (or auto-triggering) where the 'scope free runs in the absence of a signal, and normal triggering, where the trace is only present when there is sufficient signal to trigger the 'scope. Also available on some 'scopes is a line triggering option, where the sweep free runs all the time, with or without a signal. The battery-operated Thandar SC110A has a further, economy option, that shuts down unused sections of the scope in the absence of a signal, so reducing the average power consumption (in this mode) to 350 mW.

None of the new dual beam 'scopes in this survey are true two beam types; that is they all have just one beam that is switched between the two traces, either by chopping the beam or by switching it at the end of each sweep. Which mode is appropriate depends on the sweep rate, and some 'scopes will switch between the two modes automatically, depending on the setting of the sweep control (feature P); the others have manual selection of display mode (feature M).

Other Features

Some 'scopes have a component testing facility (feature T); in this mode, the scope itself applies a low frequency (usually 50 Hz or 1 kHz) signal to a component connected to it, and displays the resultant V/I graph on the screen automatically. Some waveforms for the component tester on the Crctech 3131 are shown in Fig. 1.

Oscilloscopes with an internal graticule will enable you to make parallax free measurements, because the graticule is actually on the same side of the screen glass as the phosphor.

Direct connection to the 'scope plates can be a handy facility on occasions, as this will allow much higher frequencies to be examined than the Y or X amplifiers can cope with. Z-modulation can also be a handy facility, particularly when the 'scope is used for less orthodox measurements.


Hanging On?

Most 'scopes are normally supplied with a short or medium persistence phosphor tube as standard. To our knowledge, the following manufacturers offer a choice of persistences: Farnell, Gould, Hameg, Scopex. It may be worth approaching other manufacturers if you want a particular 'scope but with a longer persistence tube.


Oscilloscope probes are usually designed to feed an input impedance of 1M Ω in parallel with 30 pF, with some adjustment usually available to compensate for slightly different impedances. Using an oscilloscope with a significantly different impedance will lead to ringing at high frequency, and possibly other problems. If the input capacitance is on the low side, you can always increase it, but if it's high, then you will have to use a probe that is designed specially for the input impedance.

All Singing . . .

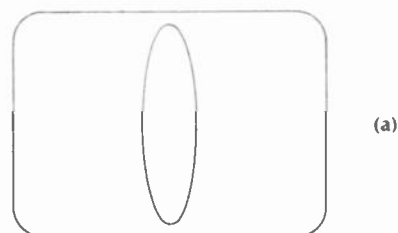
Trio don't seem to have been content with offering just normal 'scope features on their CS1575, because it has the facility to do phase comparisons at the same time as observing the two Y channels. In fact, as you may guess from its relatively




(a)

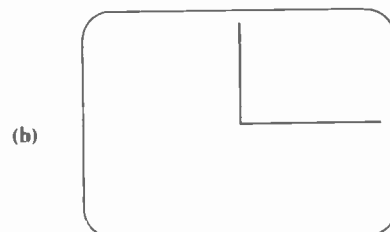

(b)

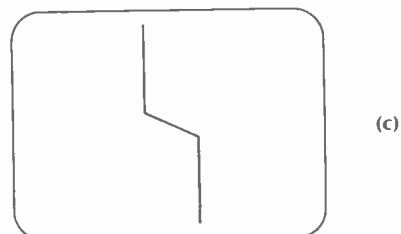


(c)

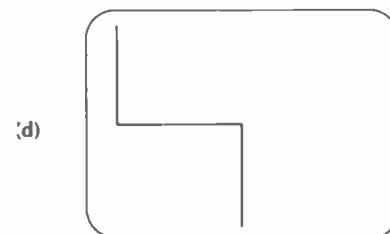

(d)

Fig. 1 Above: some typical traces for the 3131; (a) when looking at a capacitor; (b) a diode; (c) diodes back to back; (d) a J-FET source to drain. Below: the beast itself in action on a transistor.

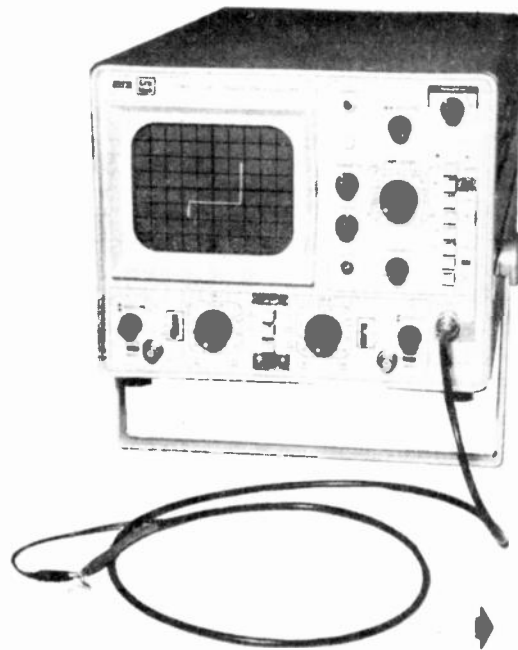

OSCILLOSCOPES

Price £ ex VAT
Similar Models
Single or Dual Trace
Calibrated Y Sensitivities, V/div
(Number of Ranges)
Basic Y Accuracy, %
Bandwidth (—3 dB), MHz
Input Impedance, M/ Ω /pF
Calibrated Sweep Speeds, sec/div
(Number of Ranges)

1	Crotech 3030	154	3033,3035	Single	5m to 20(12)	3	15	1//35	0.5u to 200m(18)
2	Crotech 3131	250	3034	Dual	5m to 20(12)	3	15	1//35	0.5u to 200m (18)
3	Farnell DTC12	345	DT12	Dual	5m to 20(12)	3	12	1//30	0.5u to 500m (19)
4	Gould OS300	325	—	Dual	2m to 10(12)	3	20	1//28	0.5u to 200m(18)
5	Hameg HM103	158	—	Single	5m to 20(12)	3	10	1//28	0.5u to 200m(18)
6	Hameg HM203-4	264	—	Dual	5m to 20(12)	3	20	1//28	0.5u to 200m(18)
7	Hitachi V152F	260	V302	Dual	5m to 5(10)	5	15	1//30	0.2u to 200m(19)
8	Hitachi V203F	355	V2102	Dual	5m to 5(10)	3	20	1//30	0.2u to 200m(19)
9	Kikusui COS5020	265	—	Dual	5m to 5(10)	NS	20	1//30	0.2u to 500m (20)
10	Leader LBO-310A	119	LBO-510B	Single	20m to 2(3)	NS	4	1//40	10Hz to 100kHz(4)
11	Leader LBO-512B	223	LBO-510B	Single	10m to 10(4)	3	10	1//30	1u to 1m(4)
12	Leader LBO-514A	313	LBO-513A	Dual	5m to 10(11)	3	15	1//30	0.5u to 200m(18)
13	Leader LBO-522	338	—	Dual	5m to 5(10)	3	20	1//30	0.2u to 200m(19)
14	Philips PM3207	385	—	Dual	5m to 10(11)	5	15	1//35	0.5u to 200m(9x2)
15	Safgan DT420	183	DT410,415	Dual	5m to 20(12)	5	20	1//22	0.5u to 200m(18)
16	Scopex 4S6	148	—	Single	10m to 50(12)	5	6	1//35	1u to 100m(16)
17	Scopex 14D15	230	14D10,SG315	Dual	5m to 20(12)	3	15	1//33	1u to 100m(16)
18	Thandar SC110A	149	—	Single	10m to 50(12)	3	10	1//47	0.1u to 500m(21)
19	Trio CO1303D	120	CO1303G	Single	10m to 1(3)	NS	5	1//35	10Hz to 100kHz(4)
20	Trio CS1560A	324	—	Dual	10m to 20(11)	NS	15	1//22	0.5u to 500m(19)
21	Trio CS1562A	258	CS1559A	Dual	10m to 20(11)	NS	10	1//22	1u to 500m(18)
22	Trio CS1575	298	—	Dual	10m to 3(6)	NS	5	1//27	0.5u to 2m(12)

SECOND HAND OSCILLOSCOPES

23	Advance OS1000B	330	—	Dual	5m to 20(12)	3	20	1//28	0.5u to 1(20)
24	Solartron CD1400	125	—	Dual	100m to 50(9)	5	15	1//35	0.5u to 200m(18)
25	Tektronix 545B	100	—	Dual	50m to NS	NS	33	NS	0.1u to 5(24)
26	Telequipment D63	300	—	Dual	1m to 20(12)	3	15	1//29	0.2u to 1(21)

Note: prices in italics are for equipment that has not been reconditioned.

Basic Sweep Accuracy %
Trigger Facilities

General Features

Screen: shape/size (mm)/
number of divisions

5 (AM)(BN)ES	CGRTUW	Rect/95/8×10	1
5 (AM)(BN)CELST	CDGIMRSTWYZ	Circ/130/8×10	2
3 BCEMNST	ACDEIMRSTVWYZ	Rect/130/8×10	3
3 BCEMNST	CDEGIPRSVWYZ	Rect/130/8×10	4
5 (AM)(BN)EST	CGKRTVWX	Rect/95/6×7	5
3 (AM)(BN)EFLST	CDEGIKLMORSTVWY	Rect/130/8×10	6
5 BCELMNST	CDEFGJOPRSVWYZ	Circ/140/8×10	7
3 BCELMNST	CDEFGJKLOPRSVWYZ	Rect/140/8×10	8
NS ABCDEMNOT	CDEFGIJKLMOPRSUWY	Rect/152/8×10	9
NS AM	VWXZ	Circ/75/8×10	10
5 BEMS	CVWXY	Circ/130/8×10	11
5 (AM)(BN)CEFST	CEFGMORVWYZ	Circ/130/8×10	12
3 (AM)(BN)CEFLST	CDEFGIKLMORSVWYZ	Rect/130/8×10	13
5 BCEMST	CDEIOPSY	Rect/130/8×10	14
5 BCEMNST	CEGOPYZ	Circ/102/8×10	15
5 (BS)EMN	GX	Circ/100/6×8	16
3 BEMNST	CDEGHIPRSYZ	Rect/130/8×10	17
3 BELMNST	BCY	Rect/41/4×5	18
NS EN	GQVWZ	Circ/75/8×8	19
NS (AM)(BN)CET	ACDEGOPRSVWY	Circ/130/8×10	20
NS (AM)(BNS)CET	CEGOPVWY	Circ/130/8×10	21
NS (BS)CEJM	CGOPUVWY	Circ/130/8×10	22

5 (AM)(BN)CDEFLST	ACDEFGIJLOPSVWYZ	Rect/130/8×10	23
5 ABCEFPS	ACEFLYW	Circ/130/8×10	24
3 (AM)(BN)DEFGOT	ACEFKLYW	Circ/130/8×10	25
3 (AM)(BN)DELOS	ACEFGHVWXZ	Rect/115/8×10	26

Key to Trigger Facilities

- A Automatic or preset level control
- B Manual level control
- C Trigger source channel selectable
- D DC coupling of trigger available
- E External trigger available
- F HF trigger facility
- G Delay facility
- H Sweep hold-off facility
- J Separate trigger level controls for two Y channels
- L Line triggering available
- M Automatic (or bright line) triggering available
- N Normal triggering available
- O One shot triggering available
- T TV sync pulse separator available

Where facilities are bracketed together, they are only available together.

General Features

- A Astigmatism control
- B Operates from batteries
- C Calibrator output provided
- D Difference of two Y channels can be displayed
- E Expansion facility on sweep
- F Expansion facility on Y channel(s)
- G Facility to ground Y input
- H Trace locate function
- I Inverting facility on one or both Y channels
- J Y output socket provided
- K Internal graticule
- L Illuminated graticule
- M Manual selection on chopping or alternating
- O Y channel turn-off facility
- P Auto selection of chopping or alternating
- Q Direct connection to deflection plates
- R Trace rotation adjustable
- S Sum of two traces can be displayed
- T Component testing facility
- U Variable sweep length control
- V Variable Y gain control
- W Variable sweep rate control
- X Access to X amplifier (ie for X-Y mode)
- Y One Y channel can be used as X amplifier
- Z Z modulation available

* = maximum value

modest bandwidth, this 'scope is specially designed for audio test work.

New Or Second Hand?

There is quite a healthy market in second hand oscilloscopes, and you can get a slightly outdated but still very useful 'scope for a fraction of the price that a new 'scope with similar specs would cost you. Newish 'scopes do turn up on the second hand market from time to time, but they don't tend to spend very long on the shelves before being snapped up. So, if you're buying a 'scope it's well worth taking a look at the second hand market.

The 'pro' of buying a second hand oscilloscope is, then, price; however, there are a few 'cons' that you should consider:

- **Size:** due to integration and rectangular tubes, new 'scopes are typically smaller, lighter and more economical on power (ie, don't get as hot) than older models (particularly 'scopes with valves).

- **Guarantees:** with any new 'scope, you will get a guarantee, though the length of the guarantee will vary from manufacturer to manufacturer, and sometimes from supplier to supplier. In addition, the manufacturer has a legal obligation to provide goods of a merchantable quality. With a second hand 'scope, you may get a warranty for up to a year if the instrument has been fully reconditioned, or no warranty at all if you're buying the 'scope "as seen". We'd advise that unless you know what you're doing, you should steer well clear of the latter option.

- **Parts:** older scopes will probably be more unreliable and more easily damaged by a knock than new 'scopes, so you could find yourself having to scour the country while searching for a vital yet elusive bit.

- **Information:** though good dealers will do their best to give you reliable information, you're unlikely to get a glossy brochure to take away and peruse at your leisure. So, to an extent, unless you are already well acquainted with instruments of that type, you will possibly be purchasing an unknown quantity.

To give you an idea of what you can get second hand, we've included in the table a few 'scopes that do turn up on this market fairly often. However, dealers can't predict what their stocks will be, and that's why we can't give you a full break-down of what's available; the only way is to go to (or telephone) a dealer for up-to-date information.

The Gould Advance OS1000B is



The Trio CS-1559A (left) and the CS-1662A (right): spot the difference.

a conventional 'scope with fixed features; the other second hand 'scopes are all modular, ie you can buy different Y and, in the case of the Solartron and Telequipment, different X modules, so the actual specs you get depend on what modules the 'scope you buy has. And a word of warning: we'd like beginners to beware the Tektronix, as you need at least a pilot's licence to fly that thing (go and look at one and you'll see what we mean).

Similar Models

(all prices ex VAT)

Crotech 3033 (287) rechargeable battery-powered version of the 3030, but without component tester

Crotech 3035 (174) similar to 3030, but with lower bandwidth (10 MHz), larger screen (130 mm) and calibrator output

Crotech 3034 (370) similar spec to 3131, but rechargeable battery powered and smaller screen (95 mm)

Farnell DT12-55 (235) as DTC12, but without component tester, sum and difference Y modes, and a slightly lower accuracy (5% on Y deflection)

Farnell DT12-14J (255) as DTC12 but without component tester

Hitachi V302F (350) similar to V152F, but with 30 MHz bandwidth and signal delay line

Hitachi V202F (220) as V203F but without delay sweep facility

Leader LBO-510B (164) vertical amplifier has same specs as LBO-310; rest as LBO-512 (tube not identical but similar)

Leader LBO-513A (263) single trace version of LBO-512

Safgan DT-410 (164), **Safgan DT-415** (172) 10 MHz and 15 MHz versions of the DT-420

Scopex 14D10V (260) similar to 14D15, but lower bandwidth (10 MHz), 2 mV/div max. sensitivity, TV delay system (see text) and no Z modulation

Scopex SG315 (270) as 14D15, but with integral function generator

Trio 1303G (161) as 1303D but with 1.8-54 MHz two-tone generator

Trio CS1559 (235) single trace version of the CS1562A

Addresses

Crotech Instruments Ltd, 5 Nimrod Way, Elgar Road, Reading, Berkshire RG2 0EB

Farnell Instruments Ltd, Sandbeck Way, Wetherby, West Yorkshire LS22 4DH

Gould Instruments Ltd, Roebuck Road, Hainault, Essex IG6 3EU

Hameg Oscilloscopes Ltd, 74-78 Collingdon Street, Luton, Bedfordshire LU11 1RX

Hitachi: Reltech Instruments, Coach Mews, St Ives, Huntingdon, Cambridgeshire

Kikusui: Martin Associates (see secondhand 'scopes)

Leader: Thandar (see below)

Philips Instrument Dept, Pye Unicam Ltd, York Street, Cambridge CB1 2PX

Safgan Electronics Ltd, Omega Road, Woking, Surrey GU21 2PX

Scopex Instruments Ltd, Pixmore House, Pixmore Avenue, Letchworth, Herts SG6 1HZ

Thandar Electronics Ltd, London Road, St Ives, Huntingdon, Cambridgeshire PE17 4HJ

Trio: House of Instruments Ltd, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE

Suppliers of secondhand oscilloscopes

Carston Electronics Ltd, Shirley House, 27 Camden Road, London NW1 9NR (Tel 01-267 5311)

Martin Associates, Parthia, Beckhampton, Nr Marlborough, Wiltshire SN8 1JQ (Tel 06723-219)

P F Ralfe (Electronics), 10 Chapel Street, London NW1 (Tel 01-723 8753)


Stewarts of Reading, 110 Wykenham Road, Reading, Berkshire RG6 1PT (Tel 0734-6804)

ETI

The SCOPEX SG315

A new range of test capabilities

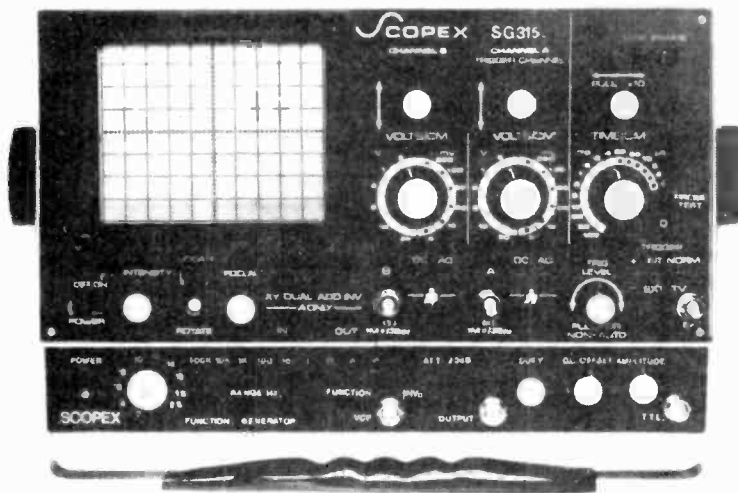Combined Oscilloscope and Function Generator
in one Precision Instrument



SCOPEX Instruments Limited
Pixmore House, Pixmore Avenue, Letchworth,
Herts. SG6 1HZ Tel: (04626) 72771 Telex: 825644

The Scope
15 MHz bandwidth
5 mV sensitivity
Timebase range
1 μ s-100 ms/cm
8x10 cm screen
vertical display
A+B B Invert
X-Y display,
X deflection
through A channel
for max.
sensitivity
Normal, TV and ext.
trigger

**The Function
Generator**
0.2 Hz-250 KHz
Sine
Square
Triangular
DC offset variable
Duty cycle variable
Output 20V,
600 ohms
20 dB attenuator
plus variable
VCF input
TTL sync output

Function Generator can be supplied
separately for you to fit to any Scopex
Dual Trace scope, just state type when
ordering, FG4, FG14/25.

Function Generator also available in an
Instrument case, FG1.

Prices:

SG315—£295+VAT. Price includes
Probes and Mains Plug and carriage UK
mainland.

Function Generator for mounting
on Scopex Dual Trace Scopes:

FG4, FG14/25—£69+VAT

Function Generator: FG1—
£79+VAT

NEW!
SG315

ULP-1 MEMORY LOGIC PROBE.

Specification:

Logic thresholds (switch selectable) DTL/TTL/CMOS.

— Logic "1" thresholds (HI-LED): TTL/DTL $2.25V \pm 0.15V$,
CMOS $70\% V_{CC} \pm 10\%$

— Logic "0" thresholds (LO-LED): TTL/DTL $0.8V \pm 0.10V$,
CMOS $30\% V_{CC} \pm 10\%$

Pulse detect mode: High speed pulse train or single events
(+ or - transitions) activate 1/3 sec. pulse stretcher.

Memory mode: Latches pulse LED for catching low rep-
events and one shot events.

Input impedance: 100k Ohms

Minimum detectable pulse width: 50 nanosec.


Maximum input signal frequency: More than 10 MHz

Probe Power: 5V Vcc. 30mA, 15V Vcc 40mA

Probe power protection: 30V max., with power leads
reverse protection.

Input overload protection: 100V continuous, 117 VAC for 10
sec, 240V for 5 sec.

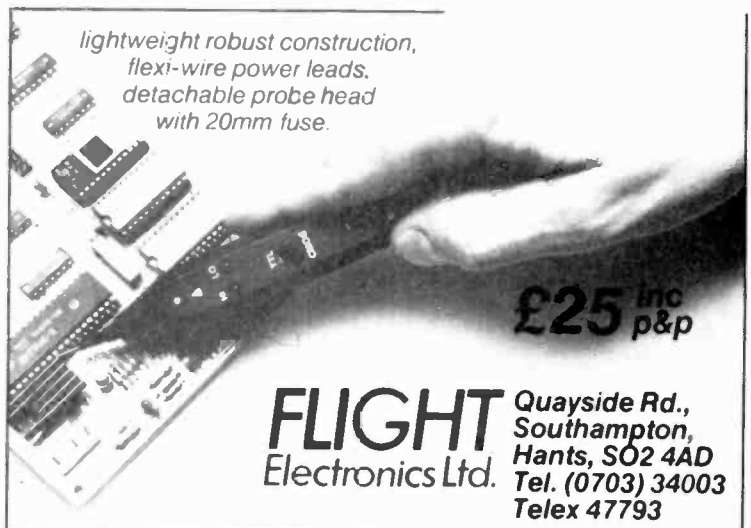Price includes VAT • Mail Order Only •  phone
or post



**£25 inc
p&p**

FLIGHT Quayside Rd.,
Electronics Ltd. Southampton,
Hants, SO2 4AD
Tel. (0703) 34003
Telex 47793

JUST OUT

OUR NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.

The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

BI-PAK

Dept E11, 7
Catalogue PO Box 6
Ware, Herts SG12 9AD



Access & VISA accepted
Ring 0920 3182 for
immediate despatch

CIRCUIT BOARD ELECTRONICS

THE NEW EXCITING

NAME IN PCB'S

FOR THE HOME ENTHUSIAST

COMPARE OUR PRICES

FOR COMPLETE PRICE LIST

WRITE TO
CIRCUIT BOARD COMPONENTS
55 MURDOCK ROAD
BEDFORD
TEL. BEDFORD 214219

CALL IN AND SEE
FOR YOURSELF

AUDIO ELECTRONICS

ALL PRICES
INCLUDE
VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY
OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS
3 1/2 DIGIT
UNLESS
STATED



HAND HELD With free carry case
K025C=13 range 0.2A DC 2 meg ohm £24.95
K030S=16 range 10A DC 2 meg ohm £29.95
K030C=26 range 1A AC/DC 20 meg ohm £34.95
K055C=28 range 10A AC/DC 20 meg ohm £39.95
6010=28 range 10A AC/DC 20 meg ohm £34.40
7030=As 6010 but 0.1% basic £41.30
K0615=16 range 10A DC 2 meg plus Hfe tester £39.95
189M 30 range 10A AC/DC 20 meg plus Hfe tester £69.95
HAND HELD AUTO RANGE
DM2350=21 range 10A AC/DC 20 meg ohm (Miniature) £49.95
H030 16 range 0.2A AC/DC 2 meg ohm £41.95
H030/B As above plus cont. buzzer £44.50
H031 22 range 10 AC/DC 2 meg ohms plus cont. buzzer £58.95
+Optional carry case £2.95

BENCH MODELS

TM353=27 range LCO 2A AC/DC £86.25
TM355=29 range LEO 10A AC/DC £86.25
TM351=29 range LCO 10A AC/DC £113.85
2001 28 range LCO 10A AC/DC plus 5 range Cap Meter with case £108.00
TM451 4 1/2 digit LCD every facility (0.02%) £171.00
1503a 4 1/2 digit LCD every facility (0.05%) £171.00
1503Ma 0.03% basic version of above £189.00
*Optional carry case £6.84

BECKMAN HAND HELD

T100 34 range 10A AC/DC 20 meg ohm £58.35
T110 As above plus Cont. test etc. £67.85

FREQUENCY COUNTERS



PFM200A 200 MHz hand held pocket 8 digit LED £67.50
8110A 8 digit LED bench 2 ranges 100 MHz £77.00
8610B 9 digit LED bench 2 ranges 600 MHz £113.85
8000B 9 digit LED 3 ranges 1 GHz £178.00
TF040=8 digit LCO 40 MHz £126.50
TF200=9 digit LCO 200 MHz £166.75
+Optional carry case £6.84
Prescalers - Extended range of most counters
TP600 600 MHz £43.00
TP1000 1 GHz £74.00

SIGNAL GENERATORS

(220/240v AC)



FUNCTION: All sine/square/triangle/TTL etc
TG100 1 Hz - 100 KHz £90.00
TG102 0.2 Hz - 2 MHz £166.75
PULSE
TG105 Various facilities 5 Hz - 5 MHz £97.75
AUDIO: Multiband Sine/Square
LA627 10 Hz to 1 MHz £90.85
AG202A 20 Hz to 200 KHz (List £94.50) £83.50
RF
SG402 100 KHz to 30 MHz (List £79.50) £69.50
LSG17 100 KHz to 150 MHz £79.35

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100M with carry case £63.00

MULTIMETERS (UK C/P 65p)

KRT 100 1K/V £5.95
12 range pocket
HM102Z 20 K/V £14.95
22 range & cont buzzer
ETC5000/5001 21 ranges, 50K/V, Range doubler, 10A DC £18.95
TMK500 23 ranges 30K/V, 12A DC plus cont. buzzer £24.75
NH56R 20K/V, 22 range pocket £10.95
ETU 102 14 range 2K/V pocket £6.50
830A 26 range 30K/V, 10A AC/DC overload protection, etc. £23.95
360TR 23 range 100K/V, Large scale 10A AC/DC plus Hfe £39.95
AT1020 18 range 20K/V, Deluxe plus Hfe tester £18.95
YN 360TR 19 range 20K/V plus Hfe tester £15.95

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241 0/12/24V, 0/1A £35.00
PP243 3 amp version £59.95
PS 1307S 8/15V 7 amp twin meter £24.95

DIGITAL THERMOMETER

TH301 LCO -50°C to +750°C with thermocouple £68.43

AC CLAMPMETER

ST300 0/300A, 0/600 VAC, 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBES

LP10 10 MHz £28.50
LOPD76 50 MHz with carry case and accessories £71.30

AUDIO • RF • FUNCTION • PULSE

OSCILLOSCOPES



Full specification any model on request, SAE by post.
HM Series HAMEG: SC THANDAR:
CS TRIOD: 3' CROTECH 'DT' Salgan
SINGLE TRACE UK C/P £3.00
3030 15 MHz 5mV, 95mm tube plus component tester C/P £3.00 £177.10
SC110A= Miniature 10 MHz battery portable Post free £171.00
HM103 15 MHz 2mV, 6 x 7 display plus component tester C/P £3.00 £181.70
+Optional carry case £6.84 AC adaptor E6 69 Nicade £12.50
DUAL TRACE (UK C/P £4.00)
DT 520 Dual 20 MHz £241.50
HM203/4 Dual 20 MHz plus component tester £287.50
CS1562A Dual 10 MHz (List £321.00) £269.50
3131 Dual 15 MHz + component tester £276.00
CS1566A Dual 20 MHz All facilities (List £401.35) £349.50
HM204 Dual 20 MHz plus component tester sweep delay £419.75
CS1820 Dual 20 MHz with extra facilities (List £508.30) £485.00
OPTIONAL PROBE KITS
X1 £7.95 X1-X10 £10.50 X10 £9.45 X100 £16.95

HIGH VOLTAGE METER

Direct reading 0/40 KV 20K/Volt (UK C/P 65p) £23.00

DIGITAL CAPACITANCE METER

0.1 pF to 2000 mF LCD 9 ranges DM6013 £52.75 (Carry case £2.95)

TRANSISTOR TESTER

Direct reading PNP: NPN, etc. TC1 (UK C/P 65p) £21.95

AUDIO ELECTRONICS

Cubegate Limited

301 EDGWARE ROAD, LONDON W2 1BN, TEL: 01-724 3564
ALSO AT HENRY'S RADIO
404/406 EDGWARE ROAD, LONDON W2, TEL: 01-723 1008

FREE CATALOGUE!
SEND LARGE
SAE (UK 20p)
ALL PRICES
INCLUDE
VAT
Order by Post with CHEQUE/MACCBUS
VISA or you can telephone your orders.
All orders despatched within 5 days
unless advised.

64K RAM
AS STANDARD!

POWERTRAN COMPUTING TODAY ELECTRONICS TODAY INTERNATIONAL

COMBINE THEIR TALENTS TO BRING YOU

CORTEX

SELF-
ASSEMBLY
KIT
£295
- VAT
CARRIAGE FREE

MASSSES OF SOFTWARE

Pascal, Forth, Mdex, Nos, Meta
CP/M compatible QBasic, SPL,
Wlndow, Spell + range of business
packages. Please contact:

Microprocessor Engineering Ltd,
21 Hanley Road, Southampton
SO1 5AP 0703 775482

READY
BUILT
£395
+ VAT
CARRIAGE FREE

OPTIONAL EXTRAS

RS232C interface kit £9.20
Floppy disc interface £86.50
Pair of 5 1/4" disc drives & hardware kit £366.00

READY BUILT

CORTEX B - Basic machine + RS232C £410.00
CORTEX C - As above + disc drives £896.00

All items carriage free - prices exclusive of VAT



CORTEX WITH OPTIONAL DISC DRIVES FITTED

16 BIT COLOUR COMPUTER

ALL THESE FEATURES PROVIDED AS STANDARD!

High speed 24K byte extended basic interpreter
Powerful TMS9995 16 bit microprocessor
48 bit floating point gives 11 digit accuracy
High resolution (256 x 192) colour graphics
Memory-mapped video controller for 3D simulation
Independent 16K video RAM
16 colours available on the screen together in
Graphic mode
Fast line drawing and point plotting basic commands
High speed colour shape manipulation from basic
Full textural error messages
String and Array size limited only by memory size
Real time clock included in basic
Interval timing with 10mS resolution via TIC function
Named load and save of basic or machine code programs
Auto-run available for any program
Powerful machine code monitor

Assembler & Disassembler
Auto line numbering facility
Full renumber command
Simple but powerful line editor
Buffered i/o allows you to continue executing the
program while still printing
Flexible CALL statement allows linkage to machine
code
routines with upto 12 parameters
Basic programs may contain spaces between keywords
to make programs readable without using more memory
64K RAM using latest technology 64K DRAMS
Over 34K bytes available for basic programs even when
extended basic includes IF-THEN-ELSE
Supports up to 16 output devices
Screen and cassette included as standard
Supports bit manipulation of variables from basic
Error trapping to a basic routine included
Basic supports Hexadecimal numbers

ULTRA POWERFUL 24K BASIC

COMMANDS	LOG	KEY	?	RANDOM	SGET
RUN	SQR	STATEMENTS	UNIT	ENTER	MAG
SIZE	SYS	IF	BAUD	LIST	TOF
CONT	TIC	ELSE	CALL	PURGE	TON
MON	SON	ON	DATA	NUMBER	DIM
	BIT	GOTO	READ	RENUM	DEF
	CRB	GOSUB	RESTOR	BOOT	NEW
ABS	CRF	POP	RETURN	GRAPH	END
ADR	MEM	REM	STOP	TEXT	BIT
ASC	MWD	FOR	TIME	PLOT	CRB
ATN	LEN	NEXT	WAIT	UNPLOT	CRF
SIN	MCH	ERROR	SAVE	COLOUR	MEM
COS	POS	INPUT	LOAD	CHAR	MWD
EXP	COL	PRINT	ESCAPE	SHAPE	BASE
FRA	MOD		NOESC	SPOT	
INT	RND				

Export enquiries to: Powertran International, Hollom Down Farm,
Lopcombe, Salisbury, Wilts SP5 1BP 0264 781545 Telex 4774G7 Zenmon

To: Powertran Cybernetics, Portway Industrial Estate,
Andover, Hants. SP10 3NM. 0264 64455

Please send me:

I enclose a cheque for

Please charge to my Access/Barclay Card no

Name

Address

.....

.....


TECH TIP SPECIAL

Cheap Photodiodes

Donald Hopkins, Tarves

This circuit was evolved using an LED in place of a photodiode. Diode D1 can be any run-of-the-mill green or yellow LED. Red LEDs do not work, presumably because of their spectral response.

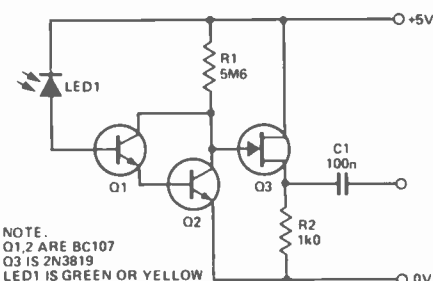When the light source to D1 is interrupted, its reverse leakage current decreases sufficiently to cause the Darlington pair Q1, Q2 to switch off. This in turn causes the FET to conduct giving a pulse at the output.



for a ± 6 V power supply, and the inclusion of IC3, 4 means that ± 7 V5 should never be exceeded.

Why is IC5 wired in the inverting mode, when the non-inverting mode would give better results? The offset adjustment of a non-inverting low-gain amplifier using the method shown here would affect the gain. Also, the inputs should not be left open-circuit as this will cause notches on the traces. The inputs should therefore be connected to an inverting amplifier, preferably with an attenuator due to the low sensitivity.

Eight Traces On A Single Trace Scope


Tore Solheim, Norway

This simple and inexpensive circuit can display up to eight traces on a single beam oscilloscope. Even though the capacity of such a simple circuit is limited, it will be fine as part of a home workshop. The frequency response is DC to 100 kHz with the circuit shown, and the scope sensitivity should be 0V5 per division, preferably DC-coupled.

IC1 is the clock oscillator: SW1 selects chopped or alternate mode. RV1 allows the frequency to be adjusted over the range 10-30 kHz or 200-700 Hz depending on the setting of SW1. The counter IC2 controls the two analogue multiplexers IC3, 4. One, two, four or eight traces may be selected using SW2, which couples one of the counter outputs back to the reset pin to reset the IC after the desired count length. The analogue inputs of IC3 are connected to a voltage divider, R3-9, and the output is connected, via R10 and RV2, to the negative input of the op-amp, IC5. This allows the offset voltage of the op-amp to be adjusted over a wide

range. The trace changes position by changing the offset voltage, which has no effect on the gain of the op-amp. RV2 allows the voltage offset between the upper and lower traces to be adjusted from ± 0 V3 to ± 3 V, ie RV2 is the position control. Separate controls aren't needed here. The eight channel inputs are connected to the analogue inputs of IC4.

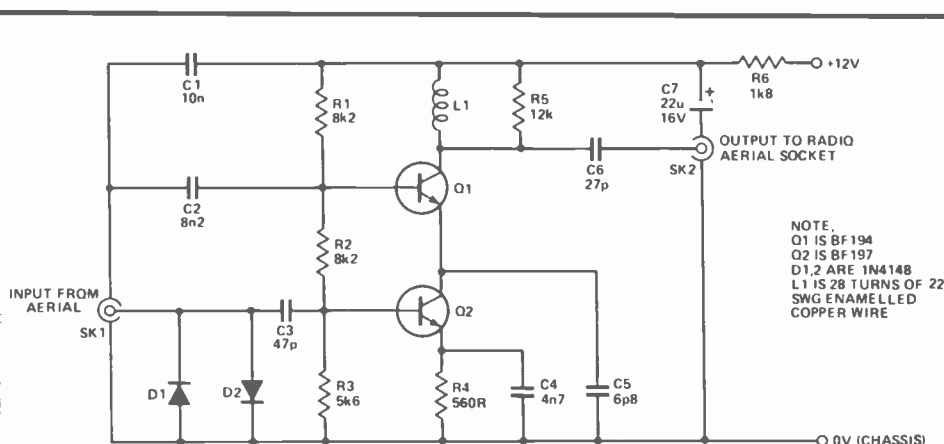The circuitry around Q1 and SW3 is to allow external triggering of the scope. This circuit isn't strictly necessary, but will often give a better display. The whole circuit is designed



Adding Preset Channels To A Tuner

A. Cassarrubios, London

The following circuit is a modification I made to my Audiophile FM Tuner (ETI January 81). My main design concept was to increase the number of preset channels to 10 but not increase the number of push-buttons on the front panel, and if possible reduce the number to one. Some form of indication of which channel is selected must also be


provided.

The operation of the circuit is simple to understand and is as follows. IC1 along with R1 and C1 provide switch debouncing to produce clean pulses for IC2's clock input. IC2 is a decade counter with 10 decoded outputs. The outputs from IC2 are taken to PR1-PR10 which along with R2-R11 provide a potential divider from which to tap off the required tuning voltage. The tuning voltage ranges from about 1V5 to about 10 V with the values shown, which is adequate for most tuners. Diodes D1-D10 stop any interaction between channels. The tuning

voltage output is taken from the cathode end of these diodes and is fed to the varicaps on the tuner.

Diodes D11-D25 are a decoding matrix for IC3, which is a seven-segment decoder driver. When pin 11 of IC2 is high, there are no logic signals on any of the binary inputs of IC3, so a zero is displayed. The logic signal from pin 11's output drives Q1, which in turn illuminates the figure '1' in the display. PR11 is set so that the intensity of the figure '1' matches that of the seven-segment display.

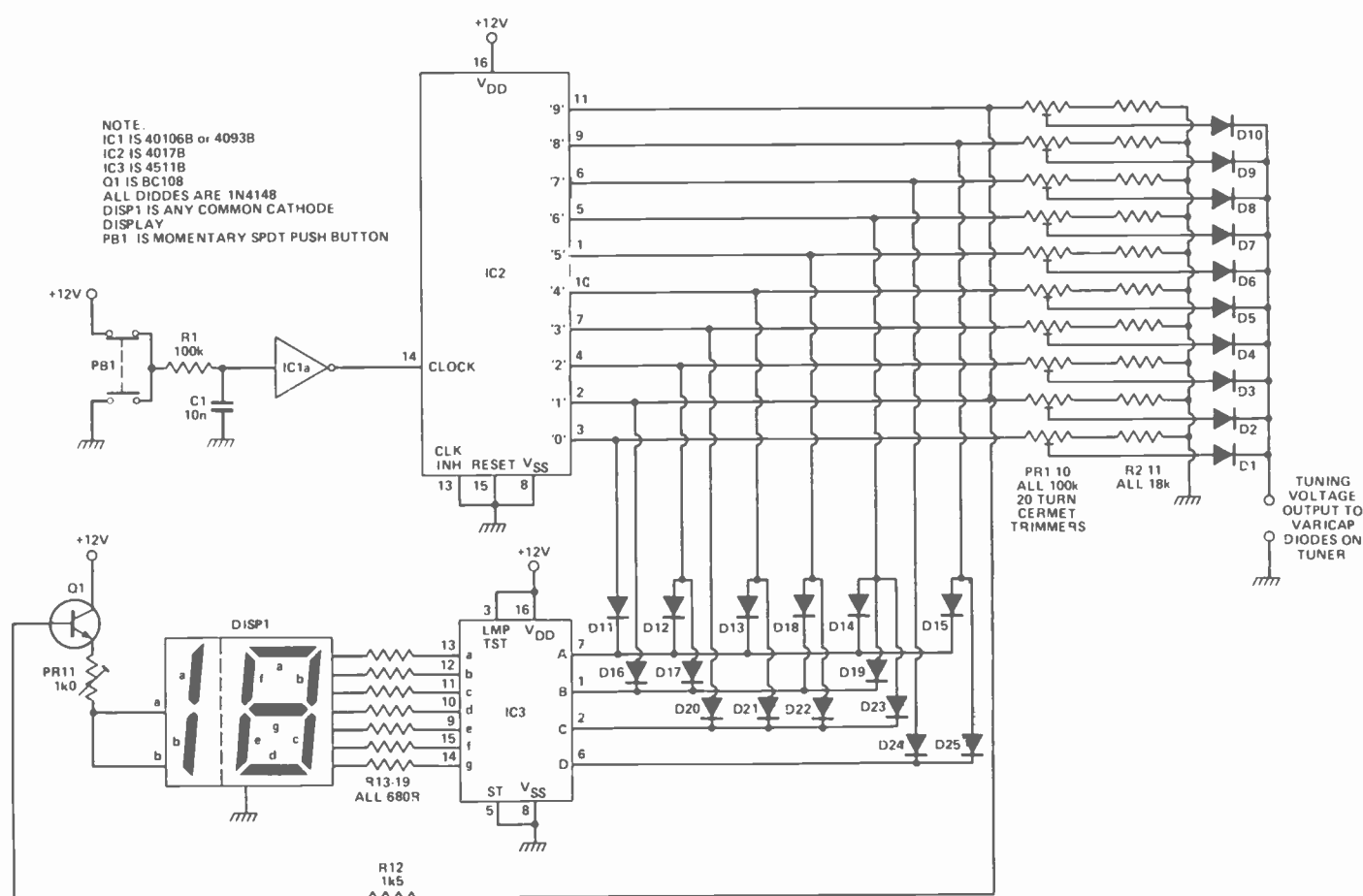The circuit is relatively easy to construct and component layout is not critical.



Car Radio Aerial Preamplifier

Neil Dobson,
Newcastle-Upon-Tyne

This circuit is a very high gain, high frequency amplifier using two NPN transistors in cascode. The input is taken via SK1 and C3 to the base of Q2. The amplified signal (between 200 kHz and 200 MHz) is passed to the base of Q1, which is connected in the common base mode, giving a very good gain at high frequencies.

R1-3 set the bias voltages for the two transistors, while R4 and C4 provide negative feedback and help increase the bandwidth of the stage.

Capacitor C1 and C7, along with R6, are the supply decoupling components and also help to filter out any noise generated by the engine. Note that L1 is a radio frequency choke, which can be made by winding 28 turns of 22 swg copper wire on resistor R5; this will give a lower gain on long and medium wave, but as the desired frequency increases (ie VHF) the reactance of L1 will increase,


allowing more of the amplified signal to pass through capacitor C6.


The two diodes connected across the input socket are to protect the transistors against static discharges and overloading. If it is found that the gain is too high, then by changing C4 to, say, 500pF, the gain can be reduced to a lower level.

The amplifier has been in use for over five months now and has proven to be very stable and surprisingly quiet as regards adding any noise to signals in low signal-strength areas especially on VHF.

Michael Jones, Dorset

The given circuit will work on any Z80A system running at 4 MHz without automatic I/O cycle wait state insertion. It will work with slower clock frequencies with corresponding increases in conversion time. Decoding occurs on port 0FFH only; this may be changed by placing inverters on the appropriate input to IC9. There is no need for a status port since the circuit is constantly converting and latching the result in IC6. It returns the result of the most recent conversion when read, unless it has already been read, in which case it inserts wait states until the current conversion is complete. In this way continuous reading will guarantee one result per 10 microseconds. It is not possible, because of time constraints, to use polling software. In addition, this arrangement permits a DMA device to carry out the transfer in the background. By adjusting the clock reduction circuit around IC3 it should be possible to cater for frequencies of 2 MHz or less, but still having 100,000 conversions per second.

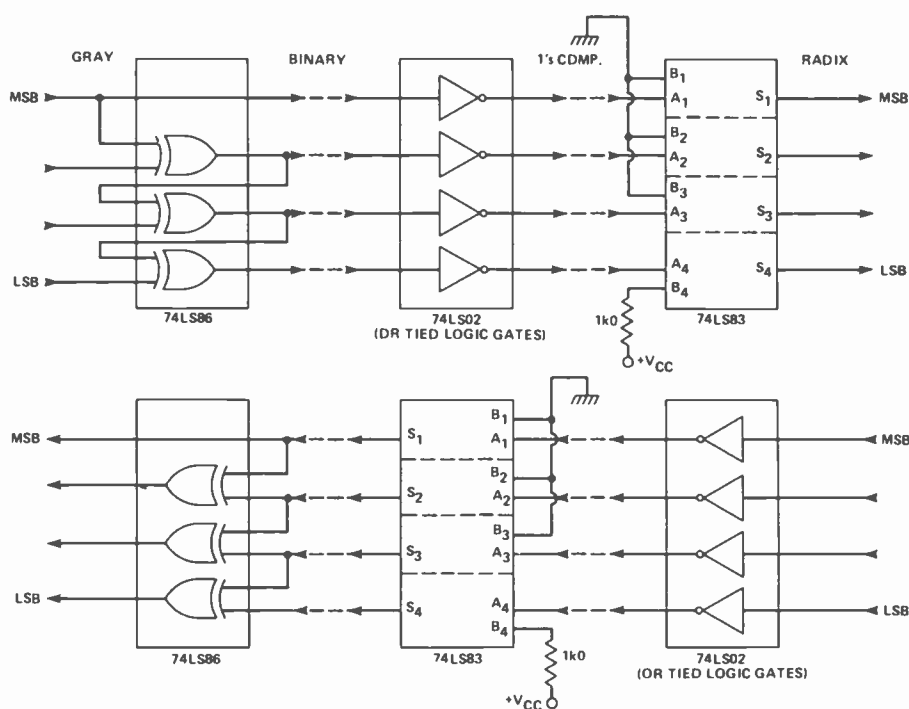[illegible]

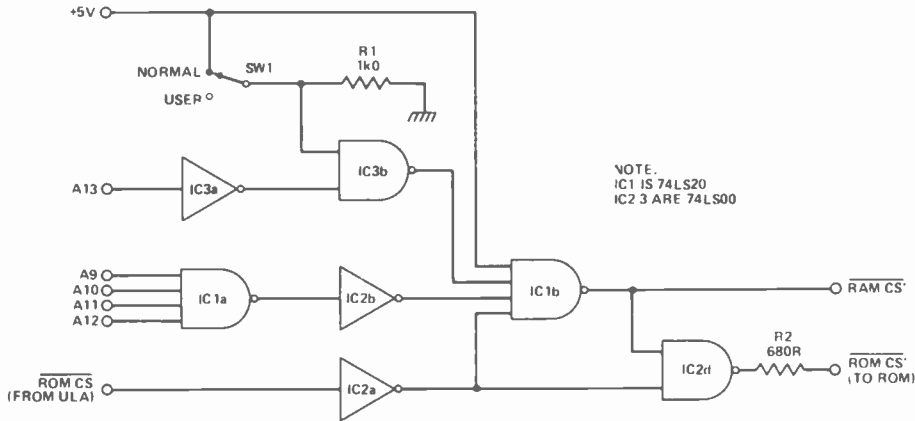

addition of the two NAND gates as shown, the character RAM appears in the memory map at both 7680-8191 and 15872-16383. However, when the switch is set to 'normal', the RAM only appears at 15872-16383. This means that the graphics set can be PEEKed from ROM and POKEd straight into the character RAM without having to be loaded into the user RAM first and does not require switching midway through the setting up program.

If R1 is removed from the ET1 board and placed together with IC3 on a separate piece of Veroboard, then connect the output of IC3b to the connection originally used by the switch on the ET1 board. No further

changes need to be made to this PCB and it can then be sold at a later date in pristine condition! Note that the switch functions are now reversed.

Incidentally, when PEEKing from the ROM, if the value PEEKed is subtracted from 255 and the remainder is POKed to the character RAM, then on switching to 'user' the whole screen will be inverted except for the border.

Four-digit Multiplexed BCD to ZX81 Adaptor

W.K. Todd, Colchester

This device interfaces a four-digit common-cathode multiplexed BCD output device, such as the 7217 counter IC, with a ZX81. The circuit is

based around IC1, a 74LS670 4 × 4 register file. The digit select inputs address the Write Address pins, WA and WB, via diodes D1-4. The Write Enable pin, $\overline{WE}$, is pulled low by diodes P5-8 when any digit is selected.


The ZX81 address decoding is performed by IC3a, b and IC2d in the same manner as the A-to-D interface in ET1, January '83. When an address between 12288 and 16383 is PEEKed, the output of IC2b goes low and enables the outputs of IC1 via the RE pin: the data is output onto the data bus on lines D0-3. Data lines D4-7 are pulled low via the diodes D9-12, allowing the computer to read the data bus directly. The Read Address of the register file is driven directly by the address lines A0 and A1. IC2a disables the internal ROM via D13 when the device is being PEEKed.

Common anode devices could be used with this circuit if the digit select lines were driven by transistor inverters.

discharges via R3 and as soon as the voltage at pin 2 falls below the 3V3 reference, IC1 is reset by a high at pin 15.

All the output pins except the one currently switched high by the count are held at ground by IC1. This causes a problem, as it would be impossible to advance the counter since the respective switch would be grounded before it could be released and so reset the count to zero. C1 holds the charge on it during clocking, long enough for the key to be released. The diode prevents any discharge through R2. R3 discharges C1 and provides a bias path for the diode. The value of the capacitor can be altered to suit your needs, but R3 is a part of the voltage divider R1, 2, 3 and its value cannot be changed.

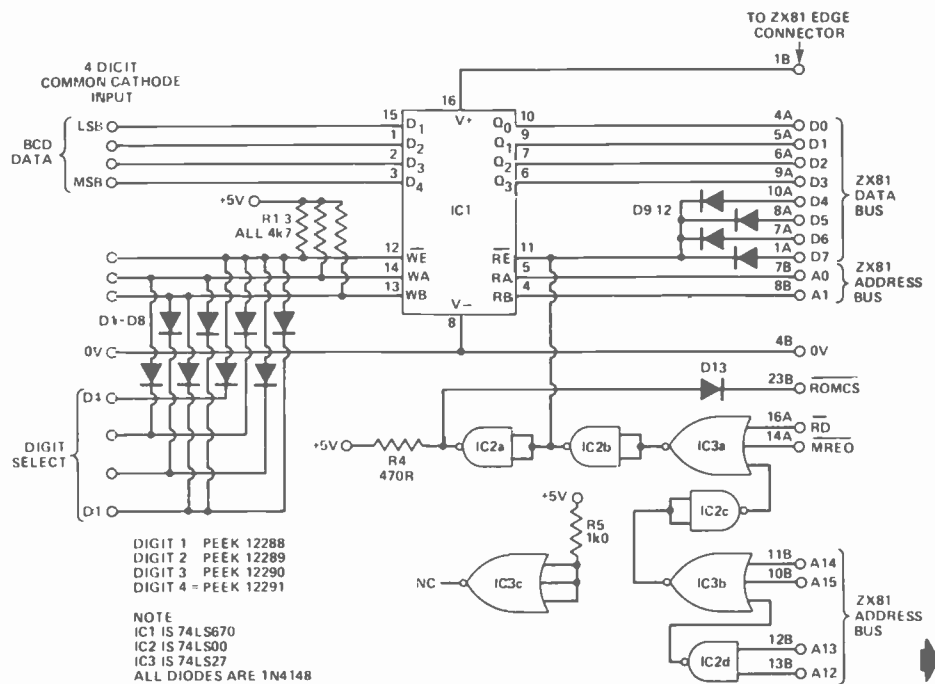R4-12 are current limiters which prevent damage to IC1 if more than one key is pressed. To reset the system after the output has been enabled, just press any key.



Digital Audio Switch

J. W. Harris, Macclesfield

The circuit uses a CMOS 555 which oscillates at a frequency determined by the equation:

$$F = \frac{1.46}{C1(R1 + R2)}$$



The output from IC1 is decoded by IC2, a decade counter divider, which is activated by PB1. When PB1 is pressed, IC2 produces a positive voltage at one of its four outputs, each of which controls two of the eight switches in ICs 3 and 4, and an LED circuit.

When a switch control goes high, the corresponding audio input is selected, and an LED lights to indicate which input has been selected.

Output 5 on IC2 is connected to RESET, so when pin 10 of IC2 goes high the decoder resets and the next pulse from IC1 selects input A.

The chosen values for R1, R2, and C1 produce a frequency of 4 Hz, so IC2 selects each audio input and then resets in 1 second. If PB1 is kept pressed, the input will change every quarter of a second.

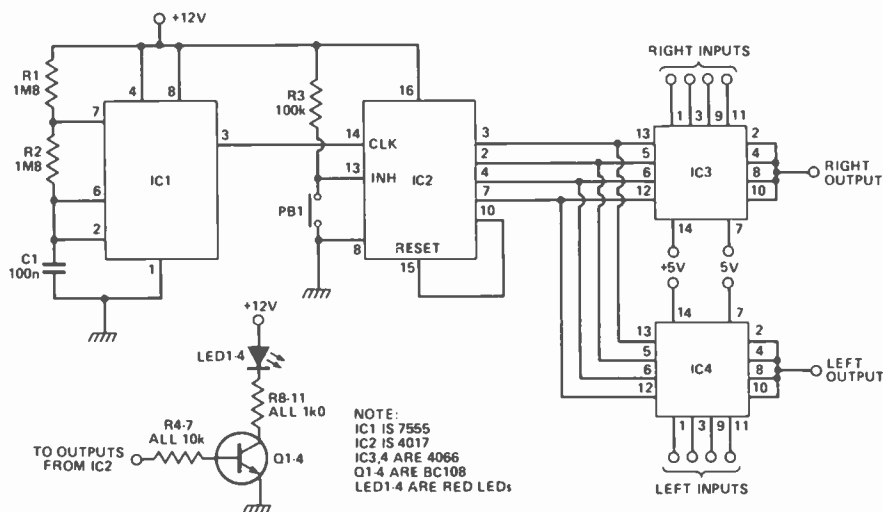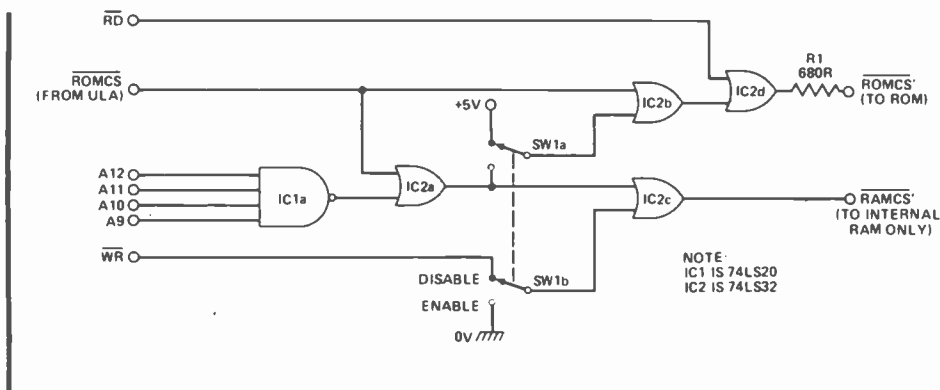ICs 1 and 2 are powered from +12 V, and ICs 3 and 4 are powered from +5 V and -5 V.



Logic State Analyser

L. V. Barker, Swansea

When testing a logic circuit, it is sometimes necessary to know the simultaneous state of several nodes. A logic probe or oscilloscope will not easily tell this and the best solution is usually a logic analyser. These are, unfortunately, rather expensive; a

solution presented here is a logic state analyser. This is an eight bit latch controlled by an input from the circuit under test and easily expandable to more input lines.

The heart of the circuit is the 74LS373, IC3: an eight bit latch. It is controlled by pin 11; when this pin is high (logic 1) the output data is equal to the input data, but when it is taken low, the device latches the data then on the input pins, thereby remember-


ing it. In this application the input pins are connected to the circuit under test and the outputs drive light emitting diodes LED3-10.

IC1 is a D-type flip flop used to control IC3. In its reset state, achieved by pressing PB1, Q1 is at logic 1 as is IC3 pin 11. The LEDs now follow the input data. When a rising edge appears on IC1 pin 3, Q1 goes to logic 0 causing the data on the input pins to be latched. It stays in this condition until PB1 is pressed. LED1 and LED2 give readouts on the state of IC1.

IC2 is a quad exclusive-OR gate; IC2c is used as either a buffer or as an inverter depending on the position of SW1. Three triggering modes exist; these are:

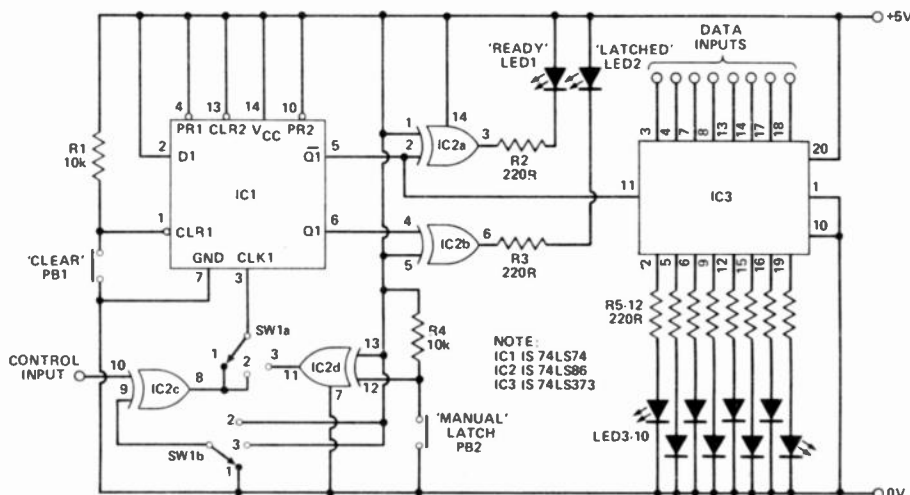- 1) SW1 in position 1: latch on rising edge on control input
- 2) SW1 in position 2: latch on falling edge on control input
- 3) SW1 in position 3: latch when PB2 is pressed

To increase the number of channels, more 74LS373 devices can be connected, with the pin 11 of each connected to pin 6 of IC1. The prototype used five devices giving 40 channels of input.



ZX Graphics Board Modification No. 2

M. Austen B.Sc, Hatfield

I must congratulate G.N. Hill on an extremely simple and clever circuit for obtaining user-defined graphics from a ZX81. However, I was a little disappointed that the idea had not been thought out a little more carefully to provide an improved circuit. The problem with the published circuit is that of having to first read the character data from the ROM and store it in memory, and then enable the character RAM before writing the stored character data into this RAM. A slightly different circuit will allow data to be written to the RAM without it being 'selected', and without causing a bus contention with the ROM. The revised circuit has a lower component count (by one), but does require two further connections to the ZX81 circuit board.

When the address lines A9, A10, A11 and A12 all go high, the output of IC1a will go low. If ROMCS from the ULA is low also, the output of IC2a will be low too. With the switch in the position shown, the output of IC2c (and hence RAMCS') will go low only if a write operation is being performed by the CPU. The output of IC2d, and hence ROMCS', will only go low if a read operation is being carried out. With the switch in the alternative position, RAMCS' will go low whenever the output of IC2a goes low, and ROMCS' will not go low when IC2a goes low.

This means that when the switch is in the disable position as shown, the character ROM can only be read from, and the character RAM can only be written to. With the switch in the enable position, the character ROM is effectively disabled and the character RAM can be read from and written to.

Therefore, to transfer the character data from ROM to RAM, simply read from the appropriate location and then write the data to the same location. When the RAM is then enabled, it will contain the required character data. The BASIC program given will illustrate this.

```
10 FOR I = 7680 TO 8191
20 POKE I, (PEEK (I))
30 NEXT I
```

Keyboard Auto-Repeat Circuit



G Franklin, Mid-Glamorgan

This circuit is intended for use with keyboards that do not have a 'repeat' facility. It is not only simple to install, but gives the user the repeat facility on every key on the keyboard.

Basically, the strobe line from the keyboard activates the monostable (IC2); this disables the output of the 555 and prevents its pulses reading the new strobe line. After approximately 3 seconds, the output of IC2 changes state and the signal from the

555 is passed on to the new strobe line. If the key is released before the monostable finishes its timing period, only one character will be sent. For a key press of longer than 3 seconds, approximately 10 characters per second will be entered (the frequency being set by the 555, used in its astable mode). The circuit is shown for use with a positive-going strobe signal: for a negative strobe, simply move the last NAND gate (used as an inverter) to the input strobe line.

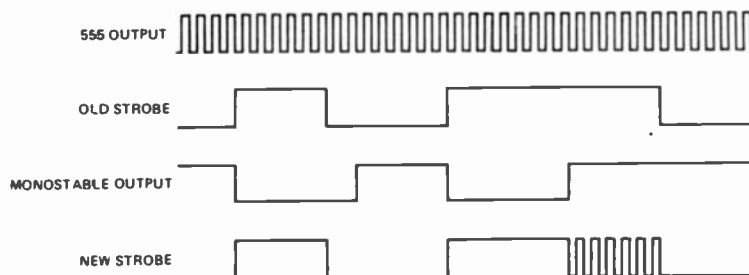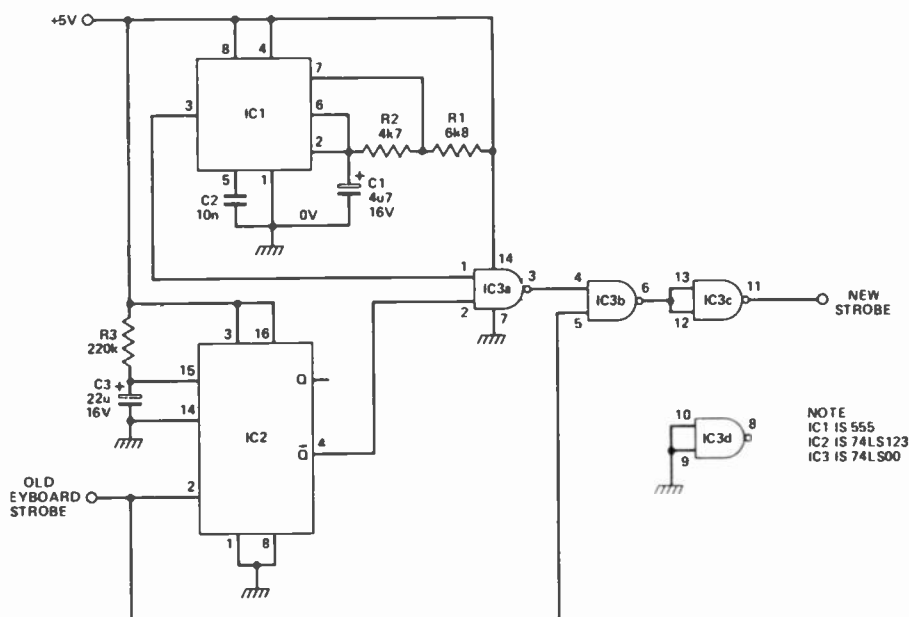
Connecting the circuit into your computer requires the removal of the current strobe line from your keyboard and re-routing it through the circuit.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ITI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for at a competitive rate.

Drawings should be as clear as possible and the text should be typed. Text and drawings must be on separate sheets. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

ETI

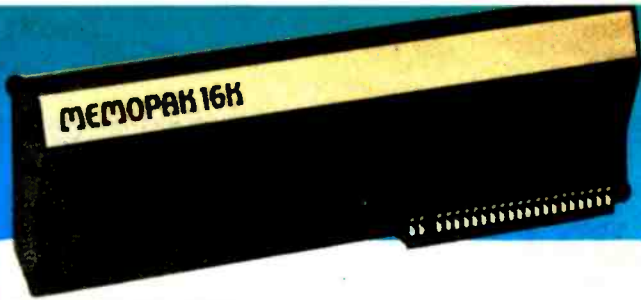

MEMOPAK 16K

MEMOPAK 16K For those just setting out on the road to real computing, this pack transforms the ZX81 from a toy to a powerful computer. Data storage, extended programming and complex displays become feasible.

For even greater capacity, memory packs can be added together (16 + 16 + 16K or 16 + 32K). The MEMOPAK 32K and the MEMOPAK 64K offer large memories at economical prices.

MEMOTECH

MEMOCALC The screen display behaves as a 'window' on a large sheet of paper on which a table of numbers is laid out. The maximum size of the table is determined by the memory capacity, and with a MEMOPAK 64K a table of up to 7000 numbers with up to 250 rows or 99 columns can be specified. Each location in the table can be either a number which is keyed in or a formula which generates a number. Every time the command to 'calculate' is given, all the formulae in the table are re-evaluated. Spreadsheet analysis started as an aid to cash-flow analysis, but this powerful tool has now been generalised and MEMOCALC with its special ability to perform iterative calculations is invaluable in the performance of numerical tasks.

The Memotech approach to microcomputing is to take the well-proven and popular ZX81 as the heart of a modular system. This small computer houses the powerful Z80A processing unit and acts as the central processor module through which the MEMOPAKS operate.

Memotech has a reputation for professional quality, producing units which are designed to fit perfectly, to look well-balanced, and to work efficiently and reliably.

The modular approach gives ZX81 owners the freedom to design the system they really need. Furthermore, the intercompatibility of the modules ensures that later additions will click straight in, to give you a system that grows with your ambitions and abilities.

As one example, a system with 16K of memory and MEMOCALC is all that is required to perform sophisticated numerical calculations giving the same results as a computer at 10 times the price. The problem may be as complicated as a cash flow or production schedule, or as simple as household accounts or pocket money budgeting. If the bank manager wants to see the cash flow, then a single print instruction to the Centronics I/F will give a printout which is more than acceptable to any bank.

The example system which is shown, on the other hand, would satisfy the needs of someone who wanted to enter data via a light-touch keyboard, construct and label graphs, and then copy the screen to an 80-column printer. Only 16K of memory is used here but with additional memory, more than one video page can be stored. Up to 7 successive pages can be displayed cyclicly to give animated displays.

16K £26.00 + £3.90 VAT £29.90

32K £43.43 + £6.52 VAT £49.95

64K £68.70 + £10.30 VAT £79.00

HRG £34.70 + £5.20 VAT £39.90

CI/F £34.70 + £5.20 VAT £39.90

MEMOCALC £26.00 + £3.90 VAT £29.90

Z80 ASSEMBLER £26.00 + £3.90 VAT £29.90

KEYBOARD

WITH BUFFER £43.43 + £6.52 VAT £49.95

Memotech products are available at larger branches of WHSMITH



MEMOPAK HRG This pack breaks down the constraints imposed by operating at the ZX81 character level and allows high definition displays to be generated. All 248×192 individual pixels can be controlled using simple commands, and the built in software enables the user to work interactively at the dot, line, character, block and page levels. Scrolling, flashing and animation are all here.




MEMOPAK Centronics I/F The BASIC commands LPRINT, LLIST and COPY are used to print on any CENTRONICS type printer. All ASCII characters are generated and translation takes place automatically within the pack. Reverse capitals give lower case. Additional facilities allow high resolution printing. The full capabilities of your printer are now under the control of the ZX81.

REALISES THE ZX81 POTENTIAL



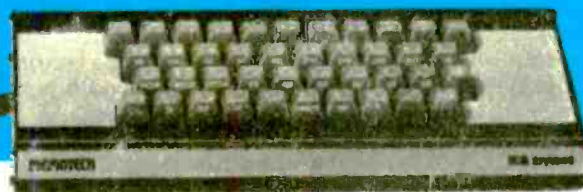MEMOPAK Z80 Assembler This click-in EPROM based pack accepts standard Z80 assembly language mnemonics to allow you to write faster and more compact programs. It has its own ADD, EDIT, LIST, ASSM and QUIT functions, the editor allowing insertion, deletion, automatic line renumbering and error checking. Source code and object code listings can be displayed and printed in decimal or hex format.



MEMOTECH Keyboard The light-touch positive stop keys of this elegant typewriter-pitch keyboard allow you to work faster, more accurately and more confidently. To speed you along we have added an extra SHIFT key to the array at top right. The keyboard is attached by a cable to the Keyboard Buffer which fits in amongst your other Memopaks or straight onto the back of your ZX81.

To ensure that your expectations are realised, care is taken at every stage to design features into the system to anticipate your frustrations and to forestall them. For example:

- A) Memories are cumulative e.g. 16K and 32K can be added to the MEMOPAK 16K or even to the Sinclair 16K RAM pack.
- B) The HRG firmware allows commonly used constructions (such as scrolling, shading and labelling graphs), which might otherwise be beyond the user's programming capabilities, to be evoked by a few simple commands.
- C) The Centronics I/F converts ZX81 character codes into ASCII and extends the print line to the width of the printer, still using the LLIST, LPRINT and COPY commands.

Looking forward, Memotech will continue to back the ZX81 through 1983 with fast storage devices, pressure sensitive electronic drawing boards and more software packs including a wordprocessor and an RS232 interface.

MEMOPAKS may be ordered by post (cheque, Access/Barclaycard quoting number) or by telephone. Please make cheques payable to Memotech Ltd. and please include £2.00 per unit for packaging and postage inland (overseas £3.00).

Memotech products are available from major branches at W.H. Smith and John Menzies.

We want to be sure you are satisfied with your Memopak - so we offer a 14-day money back guarantee on all our products.

MEMOTECH

MEMOTECH LIMITED, WITNEY, OXON. OX8 6BX
TELEPHONE (0993) 2977 TELEX 83372 MEMTEC G

PORTABLE INDUCTION LOOP

A few months ago we highlighted the problems of the hard-of-hearing when attending public performances. Now Vivian Capel shows how a do-it-yourself system can be easily implemented for small halls.

The problems of the hard-of-hearing when trying to listen to a public address system in hall, and how these can be eliminated by the installation of an induction loop was fully covered in the article contained in the February 83 issue of ETI. For the benefit of readers who might have missed it we will give a brief recap.

When listening through a hearing-aid hall acoustics are emphasised, as also are nearby audience sounds. This makes the PA sound almost unintelligible. For the past few years, most NHS hearing-aids have an internal induction coil which can be switched in in place of the microphone: this enables the user to pick up electromagnetic fields directly from some telephones and so avoid the distortion of double conversion from electrical signal to sound and from sound back to electrical signal. The switch on the hearing-aid is labelled T (telephone) and M (microphone).

If an induction loop is wired around the hall and fed from the PA system, any such hearing aids switched to T will pick up the programme free from acoustics and all extraneous noises. The design of a loop depends on the area to be enclosed, total length of loop wire,

resistance of suitable cable, number of turns in the loop, available output impedance of amplifier and output power available. Optimum vertical displacement from the hearing aid is 3-4 feet, which for a seated audience puts it at skirting board or floor level. This gives a fairly even field intensity over the whole loop area. Wiring over obstructions such as doorways has little effect, nor do intervening objects such as chairs, even if these are metal framed.

In short, the induction loop is an ideal method of enabling the hard-of-hearing to hear perfectly via their own hearing-aids and with few problems in design or installation.

Having enjoyed the facility in halls where loops are installed, disappointment has been expressed by some hearing aid users when attending meetings or functions in premises not so equipped. Where the halls are hired for one-off occasions, installing a loop is hardly practical, especially in a large auditorium unless of course it was

to remain permanently thereafter. Even then, the installation would take time, and the design some advance measurement and calculations.

Loop the Loop

A solution which has been devised and proved highly successful is that of a portable loop of fixed length, which is run to enclose a selected block of seating. Although the whole hall is not covered, the block is large enough to be more than adequate to serve those needing it along with their friends and families, thus avoiding segregation.

The loop is housed in a Portabloc cable drum (or similar) and consists of 30 yards of three-core 16/0.2 mains cable. One end is connected to a socket on the side of the drum, while the free end is terminated in a matching plug. When the plug is inserted in the socket, the three cores are connected in series to form a three-turn loop.

PARTS LIST

One Portabloc empty cable drum (see Buylines).
One MT 10 10 watt 100 V line transformer, Eagle or similar (see Buylines).
One pair of three (or more) contact plug and socket (socket to be chassis-mounting).
One red LED with mounting clip.
One silicon diode (any type).
One 68R $\frac{1}{2}$ W resistor.
One pair of screwed terminal blocks.
30 yards of three-core 16/02 mains cable (see Buylines).

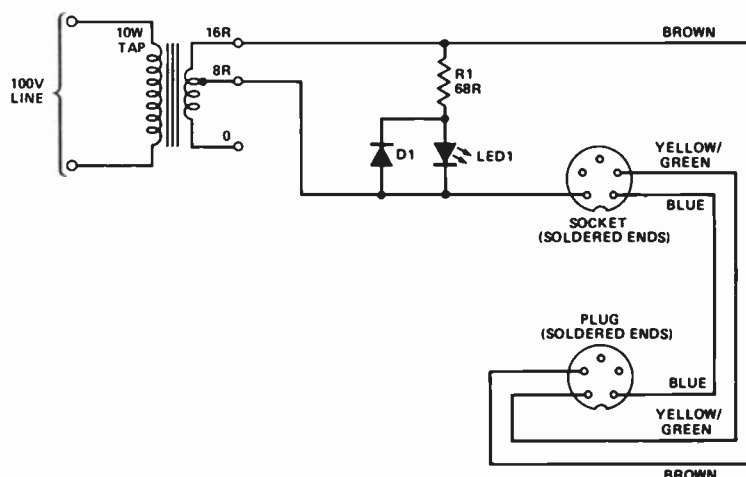


Fig. 1 Circuit diagram for the portable induction loop.

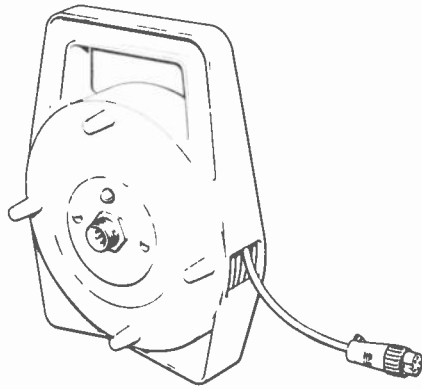


Fig. 2 Assembling the self-contained loop. The socket and the LED are mounted on the central plate on this side, the terminal block for the 100 V line connection on the other.

The 30 yards of cable is about the maximum that the drum will hold, and when paid out will give a loop of some 28 yards circumference. A couple of yards must be allowed going to and from the drum. The cable is just run around the desired area, laying it on the floor. If required it can be secured to a wooden floor at certain points with masking tape to keep it in place, especially the ends leading to the drum which should be placed at a convenient nearby position. It is not usually necessary to tape it excessively.

A feature of this arrangement is the flexibility of the shape of the area served. On average, seating rows are a yard apart, and along the row there are two seats to the yard. So if the loop is formed into a square with 7-yard sides, it will serve seven rows of 14 seats each, a total of 98 seats. Another configuration could be a 10 x 4 yard rectangle which would enclose four rows of 20 seats. Of course, any combination up to the maximum loop length can be accommodated. There need be little cable left over, as each extra row takes only a further 2 yards approximately, irrespective of its length. So the number of rows can be selected to take almost the full length of cable.

Got A Match?

Loop resistance is 3.2 ohms total. This might appear to present a matching problem for the amplifier: however, there is a simple solution. As the loop will be fed from a PA amplifier, it is assumed that the output will be 100 V line; so the matching is done by a 100 V transformer. The 10 watt MT 10 unit supplied by Eagle will just fit inside the hub of the Portabloc drum.

BUYLINES

There are some specialist items in this project, but nothing that could cause great difficulties. The cable drum is supplied by RS Components, order code 488-668, but as RS do not supply to the public you will have to buy this through a local component supplier or radio shop. Eagle, too, will not supply small orders direct to the public, but if you ring them at 01-902 8832 they will give you the address of your nearest local distributor. The mains cable can be expensive if bought by the yard at a local shop; in addition to the profit there is also a mark-up for the cutting wastage. It will be cheaper to buy a 50 metre drum and keep the extra for something else.

There are two taps on the secondary, 16 ohms and 8 ohms, but it is often overlooked that taking the output from between the 16 and 8 ohm taps does not, as might be expected, result in an impedance of a further 8 ohms but a much lower value.

When the tapings are accurate, the impedance between the 16 and 8 ohm connections is a surprising 1.37 ohms. In practice, the tapings are often higher than the nominal value. With the transformer used for the prototype they measured 8.7 and 22.5 ohms. The formula for calculating intertapping impedance is:

$$Z = (\sqrt{Z_1} - \sqrt{Z_2})^2$$

where Z is the unknown impedance, Z_1 is the impedance of the higher tap and Z_2 the impedance of the lower one.

Remarkably, the value for the transformer used worked out to 3.2 ohms, an exact match for the loop resistance. However, any impedance from this value down to the 1.37 ohms would drive the loop satisfactorily. This method of obtaining low impedance outputs by intertapping connection is a useful one which could be applied for driving other unconventional loads. Using the 4 and 8-ohm taps gives lower impedances still, of the order of 0.68 ohms.

The primary of the transformer is set to the 10 watt tap, and the loop takes 8 watts from the line. With a lower impedance output between the tapings, power consumption would be less. Most PA amplifiers would have enough reserve power to drive this, so it can be connected to any convenient amplifier in the system.

Connections are brought out from the transformer in the drum

hub to a terminal block on the outside, this being the opposite side to the socket for the loop itself. The Portabloc drums have aluminium discs on each side which can easily be drilled to take sockets or component mountings.

The final feature is the provision of an LED to indicate that the loop is working. This is connected across the loop via a 68-ohm resistor and with a shunt reverse-connected diode to protect it from inverse voltages. It can be mounted on the aluminium disc bearing the loop socket, and the drum placed when in use so that the LED can easily be seen. It will flicker on and off in sympathy with the sound and so indicate whether power is reaching the loop. If it is brighter than usual, the loop may be open-circuit somewhere.

The plug and socket used was a metal clad five-pin pair obtained quite reasonably from the local electronics emporium. This gives a couple of spare contacts in case of future trouble, but only three contacts are required and any suitable plug combination will serve. Robustness is the main consideration, and some means of securing the plug in the socket by a screwed ring or latch is desirable.

Installation


This is simple and can be done in very little time. First select the area to be served: count the number of seats in the row, subtract from 28, and halve the remainder. The result will be the number of rows that can be covered, unless the seats or rows are wider than normal. Start paying out the cable at the point where the drum will rest, and circumnavigate the block until you return to the starting point. If there is more than a couple of yards left, the loop can be extended to another row; if it doesn't quite make it, the loop will have to be brought forward a row. Secure to the floor where necessary with masking tape.

Plug in the cable plug to the socket, then run a twin pair from the connecting block back to the PA amplifier and connect to the 100 V output. Put some music and check that the LED is flickering and that's it.

Remind the ushers to direct users to the right place and tell them to switch their hearing aids over to the T position. A notice to this effect can also be displayed in the foyer or somewhere where potential users will see it.


ETI

GET BIG POWER

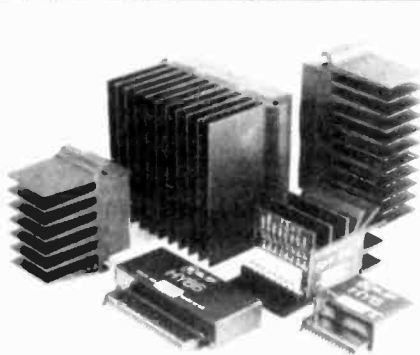

Modular Amplifiers the third generation

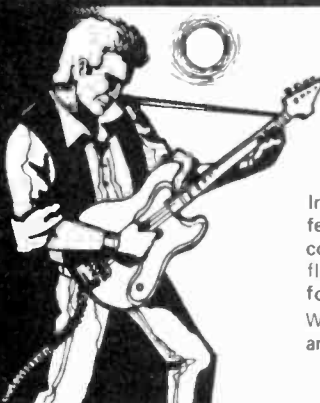Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY 30	15	4-8	<0.005%	<0.005%	± 18	76 x 68 x 40	240	£8.40
HY 60	30	4-8	<0.015%	<0.005%	± 25	76 x 68 x 40	240	£9.55
HY 60/60	60 x 30	4-8	<0.015%	<0.005%	± 25	120 x 78 x 40	420	£18.69
HY 120	60	4	<0.01%	<0.005%	± 25	120 x 78 x 40	410	£20.75
HY 120	60	4	<0.01%	<0.005%	± 35	120 x 78 x 40	410	£20.75
HY 240	120	4	<0.01%	<0.005%	± 35	120 x 78 x 50	520	£25.47
HY 360	180	4	<0.01%	<0.005%	± 50	120 x 78 x 50	520	£25.47
HY 360	180	4	<0.01%	<0.005%	± 45	120 x 78 x 100	1030	£38.41
HY 360	180	8	<0.01%	<0.005%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/μs. Risettime: 5μs. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz > 400.

PRE AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY 6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY 140	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY 71	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.86
HY 70	Stereo pre-amp	As HY 66 less tone controls	20mA	£13.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY 6 - HY 13 £1.05 (inc. VAT) and the B66 for modules HY 66 - HY 78 £1.29 (inc. VAT)

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY 30	£11.93
PSU 41X	1 or 2 HY 60, 1 x HY 60/60, 1 x HY 120	£13.83
PSU 42X	1 x HY 120	£15.90
PSU 43X	1 x MOS 128	£16.70
PSU 51X	2 x HY 120, 1 x HY 240	£17.07

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.005%	± 35	120 x 78 x 40	420	£10.41
MOS 248	120	4-8	<0.005%	<0.005%	± 50	120 x 78 x 50	450	£10.86
MOS 364	180	3	<0.005%	<0.005%	± 50	120 x 78 x 100	1025	£35.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice). Slew rate: 20V/μs. Rise time: 3μs. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz > 400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB. Load impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 52X	2 x HY 120	£17.07
PSU 53X	2 x MOS 128	£17.86
PSU 54X	1 x HY 248	£17.86
PSU 55X	1 x MOS 248	£19.52
PSU 71X	2 x HY 240	£21.75

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY 248	£22.54
PSU 73X	1 x HY 364	£22.54
PSU 74X	1 x HY 368	£24.20
PSU 75X	2 x MOS 248, 1 x MOS 368	£24.20

WITH A LOT OF HELP FROM



PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.



Hi Fi Separates

UC1 PRE AMP UNIT: Incorporates the HY78 to provide a "no frills", low distortion, ($<0.01\%$), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

POWER AMPS: The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.

Power Slaves

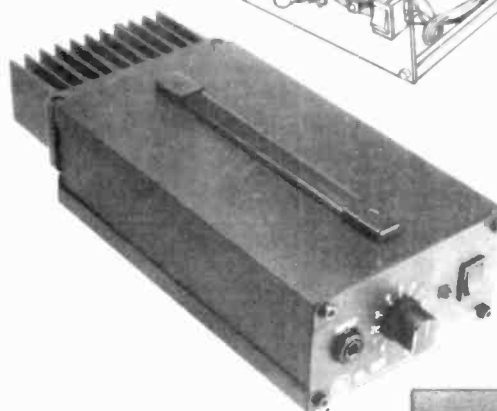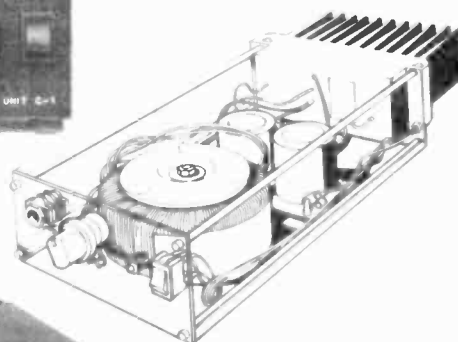Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED

UNICASES

HIFI Separates						Price inc. VAT
UC1	Preamp					£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi		£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi		£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi		£54.95
UP4X	120W/4Ω	Bipolar	Mono	HiFi		£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi		£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi		£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi		£84.95
Power Slaves						
US1X	60W/4Ω	Bipolar	Power	Slave		£59.95
US2X	120W/4Ω	Bipolar	Power	Slave		£79.95
US3X	60W/4-8Ω	MOS	Power	Slave		£69.95
US4X	120W/4-8Ω	MOS	Power	Slave		£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.) All units except UC1 incorporate our own toroidal transformers.



Post to: ILP Electronics Ltd., Freeport 4,
Graham Bell House, Roper Close,
Canterbury CT2 7EP, Kent, England.
Telephone: (0227) 54778.
Technical: (0227) 64723.
Telex: 965780.

Please send me the following _____

Total purchase price _____

I enclose Cheque ☐ Postal Orders ☐ Int. Money Order ☐

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

ELECTROVALUE

THE LARGEST RANGE OF WORLD-FAMOUS
SIEMENS COMPONENTS IN THE U.K -
24 HOUR NORMAL DESPATCH TIME - BETTER
PRICES - BETTER SERVICE - BETTER CHOICE

I.C.s DIGITAL AND ANALOGUE

DIGITAL

74LS	7400	4017	34
74LS00	11 7400	11 4017	42
74LS02	11 7401	11 4018	24
74LS04	12 7402	12 4020	40
74LS05	12 7403	12 4021	40
74LS08	12 7404	12 4022	30
74LS10	12 7405	20 4023	32
74LS11	12 7406	20 4024	20
74LS12	12 7407	20 4025	13
74LS13	12 7408	14 4026	75
74LS14	23 7409	14 4027	20
74LS20	12 7410	18 4028	36
74LS30	12 7411	18 4029	36
74LS32	13 7412	24 4030	15
74LS37	14 7413	17 4041	10
74LS38	14 7430	17 4042	35
74LS42	28 7440	17 4043	35
74LS47	42 7443	32 4046	46
74LS51	14 7444	60 4049	21
74LS73	18 7447	39 4050	21
74LS74	18 7448	36 4060	45
74LS76	15 7450	17 4069	13
74LS85	40 7451	18 4070	13
74LS86	15 7453	16 4071	13
74LS90	28 7454	17 4072	13
74LS92	10 7455	17 4081	13
74LS93	23 7470	24 4082	13
74LS107	20 7472	16 4093	20
74LS112	20 7473	24 4510	40
74LS123	34 7474	20 4511	40
74LS125	24 7475	20 4512	95
74LS126	25 7476	30 4516	45
74LS132	34 7480	35 4518	45
74LS136	18 7482	65 4520	45
74LS137	90 7483	38	
74LS138	27 7485	60	
74LS139	27 7486	19	
74LS145	60 7489	110	
74LS148	75 7490	24	
74LS151	32 7491	20	
74LS153	36 7492	27 709C5	55
74LS155	30 7493	27 709C14	44
74LS156	36 7494	35 723C14	36
74LS157	27 7495	29 741C5	57
74LS181	36 7496	40 741C8	18
74LS183	36 74100	85 741C14	47
74LS184	36 74104	37 741C14	85
74LS185	50 74107	22 748C8	35
74LS166	60 74121	24 145C8C	62
74LS173	55 74123	30 145C8C14	60
74LS174	36 74125	29 7106	500N
74LS175	40 74126	29 7107	500N
74LS191	40 74141	35 555	18N
74LS193	39 74151	30 7555	80N
74LS196	39 74154	55 556	50
74LS198	40 74155	35 CA3046	70N
74LS199	58 74156	35 CA3080C	70N
74LS221	45 74157	30 CA3130C	90N
74LS240	50 74190	45 CA3140C	45N
74LS241	55 74192	45 LM301AN	25N
74LS242	55 74193	45 LM308N	80
74LS243	58 74393	78 LM317K	295
74LS244	55	LM324AN	32
74LS245	75	LM348N	55
74LS251	36 4000	10 LM380N	68
74LS253	30 4001	10 LM380N8	80
74LS257	32 4002	12 LM381N	195
74LS259	55 4006	48 LM382N	45
74LS266	24 4007	14 LM3900N	50
74LS273	60 4008	38 LM3914N	200
74LS279	30 4009	24 LM3915N	200
74LS299	150 4010	22 NE555V	18N
74LS367	29 4011	11 NE556A	50
74LS368	33 4012	14 NE567N	104
74LS373	55 4013	20 RC4151N8	86
74LS374	55 4014	40 S041E	290
74LS378	60 4015	38 S041P	121
74LS393	48 4016	20 S042E	364

ANALOGUE

74LS	7400	4017	34
74LS00	11 7400	11 4017	42
74LS02	11 7401	11 4018	24
74LS04	12 7402	12 4020	40
74LS05	12 7403	12 4021	40
74LS08	12 7404	12 4022	30
74LS10	12 7405	20 4023	32
74LS11	12 7406	20 4024	20
74LS12	12 7407	20 4025	13
74LS13	12 7408	14 4026	75
74LS14	23 7409	14 4027	20
74LS20	12 7410	18 4028	36
74LS30	12 7411	18 4029	36
74LS32	13 7412	24 4030	15
74LS37	14 7413	17 4041	10
74LS38	14 7430	17 4042	35
74LS42	28 7440	17 4043	35
74LS47	42 7443	32 4046	46
74LS51	14 7444	60 4049	21
74LS73	18 7447	39 4050	21
74LS74	18 7448	36 4060	45
74LS76	15 7450	17 4069	13
74LS85	40 7451	18 4070	13
74LS86	15 7453	16 4071	13
74LS90	28 7454	17 4072	13
74LS92	10 7455	17 4081	13
74LS93	23 7470	24 4082	13
74LS107	20 7472	16 4093	20
74LS112	20 7473	24 4510	40
74LS123	34 7474	20 4511	40
74LS125	24 7475	20 4512	95
74LS126	25 7476	30 4516	45
74LS132	34 7480	35 4518	45
74LS136	18 7482	65 4520	45
74LS137	90 7483	38	
74LS138	27 7485	60	
74LS139	27 7486	19	
74LS145	60 7489	110	
74LS148	75 7490	24	
74LS151	32 7491	20	
74LS153	36 7492	27 709C5	55
74LS155	30 7493	27 709C14	44
74LS156	36 7494	35 723C14	36
74LS157	27 7495	29 741C5	57
74LS181	36 7496	40 741C8	18
74LS183	36 74100	85 741C14	47
74LS184	36 74104	37 741C14	85
74LS185	50 74107	22 748C8	35
74LS166	60 74121	24 145C8C	62
74LS173	55 74123	30 145C8C14	60
74LS174	36 74125	29 7106	500N
74LS175	40 74126	29 7107	500N
74LS191	40 74141	35 555	18N
74LS193	39 74151	30 7555	80N
74LS196	39 74154	55 556	50
74LS198	40 74155	35 CA3046	70N
74LS199	58 74156	35 CA3080C	70N
74LS221	45 74157	30 CA3130C	90N
74LS240	50 74190	45 CA3140C	45N
74LS241	55 74192	45 LM301AN	25N
74LS242	55 74193	45 LM308N	80
74LS243	58 74393	78 LM317K	295
74LS244	55	LM324AN	32
74LS245	75	LM348N	55
74LS251	36 4000	10 LM380N	68
74LS253	30 4001	10 LM380N8	80
74LS257	32 4002	12 LM381N	195
74LS259	55 4006	48 LM382N	45
74LS266	24 4007	14 LM3900N	50
74LS273	60 4008	38 LM3914N	200
74LS279	30 4009	24 LM3915N	200
74LS299	150 4010	22 NE555V	18N
74LS367	29 4011	11 NE556A	50
74LS368	33 4012	14 NE567N	104
74LS373	55 4013	20 RC4151N8	86
74LS374	55 4014	40 S041E	290
74LS378	60 4015	38 S041P	121
74LS393	48 4016	20 S042E	364

AN EXCITING EV SPECIAL!

'SIPMOS' MOSFET POWER TRANSISTORS BY SIEMENS

Type	Case	V	A	W	PRICE
Buz 10	TO22	50	12	45	£4.78
Buz 10A	TO22	50	12	45	£4.78
Buz 15	TO3	50	45	125	£18.70
Buz 20	TO220	100	12	45	£6.25
Buz 23	TO3	100	10	62.5	£8.82
Buz 24	TO3	100	32	125	£16.20
Buz 30	TO220	200	6.5	0.75	£5.68
Buz 32	TO220	200	8.8	62.5	£8.11
Buz 33	TO3	200	7.2	78	£11.57
Buz 35	TO3	200	9.9	78	£10.52
Buz 36	TO3	200	22	125	£23.60
Buz 41A	TO220	500	4.3	62.5	£7.77
Buz 43	TO3	500	2.8	78	£8.11
Buz 44A	TO3	500	4.8	78	£11.57
Buz 45	TO3	500	9.6	100	£18.18
Buz 46	TO3	500	4.2	78	£9.32
Buz 48	TO238	500	7.3	83.3	£14.58
Buz 50A	TO220	1000	2.3	75	£10.42
Buz 54A	TO3	1000	4.6	125	£20.45
Buz 60	TO220	400	5.5	62.5	£8.71
Buz 64	TO3	400	11.5	100	£22.89
Buz 80	TO220	800	2.6	75	£9.78
Buz 80A	TO220	800	3	75	£16.23
Buz 83A	TO3	800	3.4	78	£15.29
Buz 84	TO3	800	5.3	125	£26.45
Buz 84A	TO3	800	6	125	£23.58


METERS Large range of types in stock; also probes, leads, accessories, etc.
PANEL MOUNTING in 50, 100, 500µA; 1, 5, 10, 50, 100, 500mA; 1A either model.



T Range
60 x 45mm
£5.95



MU Range
50 x 45mm
£2.68

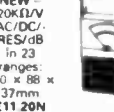

MULTIMETERS
NH56A
NEW -
20KΩ/V
AC/DC/
dB/Trans-
RES/ΩB
in 23
130 x 88 x
37mm
£11.20N



YN360TR
20KΩ/V
AC/DC/
dB/Trans-
tor Test
in 23
145 x 96 x
45mm
£16.45N

SWITCHES

Type CK - 1P/12 way, 2P/5 way, 3P/4 way, 4P/3 way 48p; Min Toggles - 57101 SPDT 57p; 57201 DPDT 80p; 57301 3PDT £1.84; 57203 DPDT 96p; PB min 8531 mk 8533 br 62p; 8225 DPDT £1.34.
DUAL IN LINE ERG colour coded 0.3" x 0.1" format. On/Off single throw 2P SDS2 54p; 4P SDS4 95p; 6P SDS6 £1.38; 8P SDS8 £1.87; 10P SDS10 £2.10. Low cost D-I-L 4P DNS04 65p; DNS08 £1.00.

CAPACITORS

Polystyrene, Siemens 5% Tolerance 160V 5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF 15p; 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF. 1n, 1n2, 1n5, 1n8, 2n2, 2n7, 3n3, 3n9, 4n7, 10p; 5n6, 6n8, 8n2, 10n, 13p.
Ceramic Very small 1.8, 2.2, 2.7 etc up to 1n, 5p each. 1n5, 2n2, 3n3, 4n7, 6n8, 5p; 10n, 22n, 6p; 33n, 47n, 7p; 100n, 8p.
Polyester, Siemens Layer Type 7.5mm lead spacing 100V. 1n, 1n5, 2n2, 3n3, 4n7, 6n8, 8n2, 10n, 12n, 15n, 18n, 22n, 33n, 47n, 7p; 56n, 68n, 7p; 82n, 100n, 9p; 120n, 150n, 15p; 180n, 220n, 12p; 270n, 330n, 130n, 390n, 470n, 15p; 560n, 680n, 24p; 10mm spacing 1uF 25p; 15mm spacing 2uF 35p; 22.5mm, spacing 1uF 400V 50p; 3.33uF 100V 65p; in depth stocks.

ELECTROLYTICS

4.7/63	11	100/3	63	1000/16	26	4.7/35	18
4.7/100	14	100/10	12	1000/25	36	6.8/16	16
6.8/40	9	100/16	12	1000/40	44	6.8/25	24
10/25	9	100/25	12	1000/63	76	10/6.3	16
10/40	11	100/40	15	2200/6	99	10/16	18
10/63	12	100/63	20	2200/16	44	10/25	18
10/100	15	100/100	27	2200/25	60	22/6.3	18
22/10	9	220/10	16	2200/40	73	22/16	30
22/25	12	220/25	16	4700/16	72	22/25	30
22/40	12	220/25	16	4700/25	90	33/6.3	24
22/63	15	220/40	20			33/10	30
22/100	16	220/28	28	TANTALUM		47/6.3	30
47/3	63	220/100	42	BEARS		100/10	66
47/10	11	470/10	19	0.1/35	13	100/3	30
47/25	10	470/16	19	0.2/35	13		
47/40	15	470/25	19	0.47/35	13		
		470/40	27	1.0/35	13		
		470/63	45	2.2/16	13		

CONFIGURATIONS

It's been a year since Configurations started, and now Ian Sinclair brings the series to a close, shutting the AND, OR, and NOT gates behind him.

For anyone who has worked with linear circuits for a long time, the first contact with digital circuits always comes as a shock because the action of digital circuits is unfamiliar, and the way in which the circuits respond to signals is equally unfamiliar. In this final part of Configurations, therefore, we shall concentrate on the most basic of digital circuit, the gate, and how the two most common of 'families' of digital circuits, TTL and CMOS, carry out gate action. For once, also, we're going to assume rather less in the way of background knowledge than we've taken for granted in previous parts, because all the problems in adapting to digital circuitry are at the start — once you have had some experience, this sort of message is not needed!

Let's be clear from the start what we mean by digital circuits and gates. A digital circuit is, strictly speaking, one which works with signals that consist of several separate voltage levels, so that a voltage which is to be counted as a signal must be at or near one of these levels. The digital circuits that we make most use of are binary digital circuits, meaning that the signals into them and from them consist of only two voltage levels which we refer to as a matter of convenience as 0 and 1. What the actual voltages happen to be is unimportant — the important feature is that there should be just these two levels. Most logic circuits operate with what we call positive logic, in which 0 means zero volts and 1 means a positive voltage; a few older circuits can still be found which use negative logic, in which 1 is a negative voltage.

The advantages of using just two voltage levels are considerable. We don't have to worry about bias, for example, in the design of circuits, provided that we arrange for each active device in a circuit to be turned on at one voltage level and off at the other. This encourages the use of ICs, because bias is difficult to arrange reliably inside ICs. We don't need much in the way of voltage amplification, because with only two voltage levels to consider, the output signals can be of about the same voltage levels as the input signals. The only voltage amplification we need to consider is as much as is needed to restore the 1 level to normal when it has been reduced by, say, the 0V6 drop across a conducting diode (Fig. 1). The third major factor is that tolerances in component values have much less effect

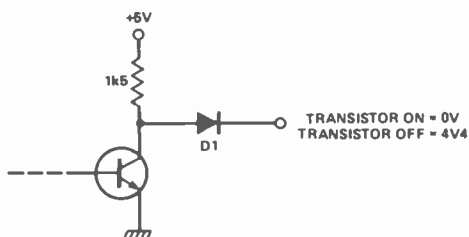


Fig. 1. Voltage levels. The presence of a diode, or a transistor junction, in the path of an output can change the output level by 0V6 or so. The tolerance of voltage must be enough to make allowances for this.

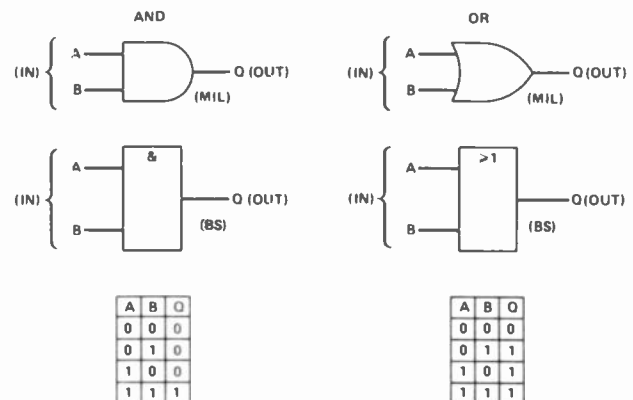


Fig. 2. The two main gate types, with International (MIL) symbols, and the BS symbols that are used for TEC and C & G courses. The truth tables describe the gate actions.

on signals than they have in linear circuits. A logic 1 voltage which is nominally 5 V can drop as low as 3V6 and still be useable as a logic 1 voltage. The logic 0 voltage can rise as high as 0V8 and still be useable as a logic 0 voltage.

Since the normal concern of linear circuits, amplification with low distortion, is simply not necessary for digital circuits, the actions that digital circuits perform are necessarily quite different. One of the fundamental actions of a digital circuit is gating, and it is gating that we shall look at in the rest of this article.

Digital Gates

A digital gate is a circuit which has inputs that are digital signals and an output (or more than one output) which is also a digital signal. Since the output is a digital signal, it must have a voltage level at any instant which is at logic 0 or at logic 1, and what the level actually is depends entirely on the combination of inputs that happens to be present at that instant. It is for this reason that the gate circuit is often referred to as a **combinational** circuit. The two most important types of gate circuits are referred to as AND and OR gates respectively, and we can describe their actions by a table that shows what the output will be for every possible combination of inputs. Such a table is called a 'truth table', and the truth tables for AND and OR gates with two inputs are illustrated in Fig. 2. These tables show that for the two-input AND gate, the output will be at logic level 1 only when both inputs are at level 1: for the OR gate, the output will be at level 1 when either or both inputs are at level 1.

Truth tables become less useful when a gate has a large number of inputs, because the number of lines needed for a truth table is 2^n , where n is the number of inputs to the gate. The same rules apply, however, irrespective of the number of inputs, so that the action of the AND and the OR gates can be described in ways that are more compact

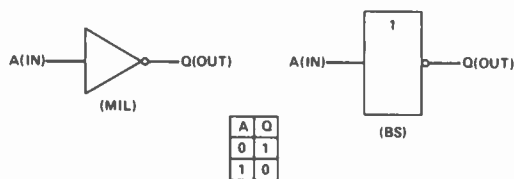


Fig. 3. The inverter or NOT gate.

than truth tables, using what is called Boolean Algebra. We haven't space to deal with this here.

Another circuit which is usually classed among the gates is the inverter, sometimes called a NOT gate. Its truth table (Fig. 3) is simple — the logic voltage output is the inverse of its logic voltage input. Circuits which combine the action of the NOT gate with the action of AND are called NAND gates; circuits which combine NOT action with OR action are called NOR gates, and the truth tables for these types are shown in Fig. 4. One further gate which is less important as a basic circuit, but which is needed in arithmetic circuits, is the exclusive-OR gate, or EXOR-gate, whose action is illustrated in Fig. 5. The name comes from the fact that the action is like that of the OR gate but excluding the case where both inputs are 1.

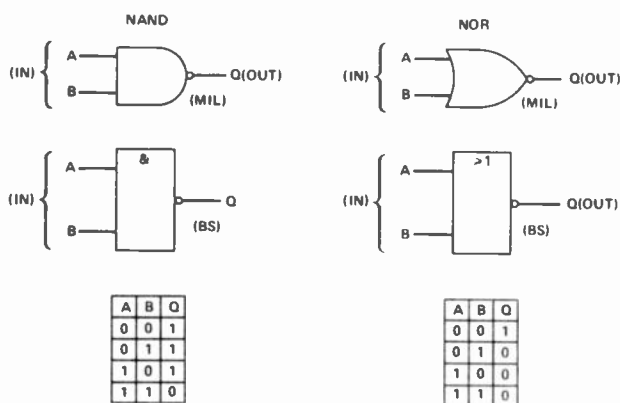


Fig. 4. NAND and NOR gates, formed by combining AND/OR gates with inverters.

Logic circuits which make use of gates are connected so that the output of one gate can pass signals to the input of the next gate in the circuit — we say that one output can **drive** one or more inputs. This usually means that the output has to be able to supply (**source**) or absorb (**sink**) current, and the number of inputs that can be driven by one output is called the **fanout** of that gate. The size of the

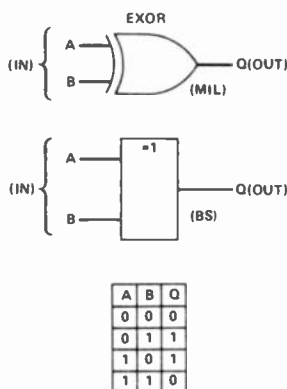


Fig. 5. The exclusive-OR (EXOR) gate and its truth table.

fanout depends on the design of the input and the output stages of the gates. A fanout of 10 is generally considered to be satisfactory, meaning that 10 gate inputs can reliably be driven from one gate output.

TTL Gates

The old-style 'standard' TTL gate uses bipolar transistors, but using a common-base circuit rather than the more familiar common-emitter. The inputs (Fig. 6) are to the emitters of transistors whose bases are connected through a current-limiting resistor to the supply positive voltage of 5 V. A common feature of the IC construction is the creation of several emitters on to one base, so that several inputs are fed in by the same transistor. An input stage like this will draw no current when the input voltage is logic 1, because such an input biases the transistor off. An input which is at logic 0, however, has the effect of earthing the input terminal, and current will flow through the base-emitter junction of the transistor to earth. Unlike our linear circuits, this input current comes *out* from the input! Standard TTL is constructed so that this current is about 1.6 mA, so the resistance between the input terminal and earth must be low enough to ensure that when this amount of current flows, the input voltage at the terminal must not rise above the maximum voltage level permitted for logic 0, usually around 0V8.

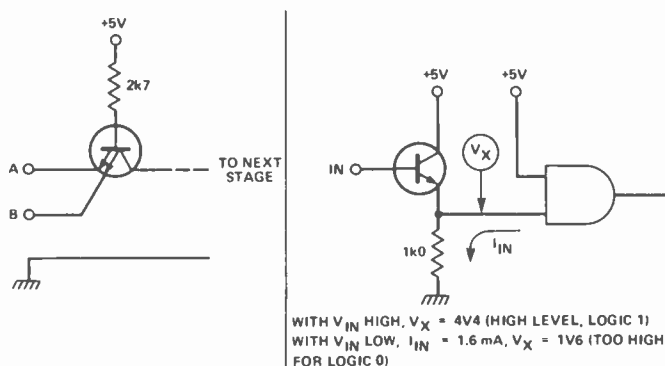


Fig. 6 (Left) TTL input. The base of the transistor is connected to + 5 V through a resistor, and the inputs are to emitters — more than one emitter (and as many as 13) can be formed on to one base.

Fig. 7 (Right) Driving a TTL stage from an NPN emitter-follower. The logic 0 voltage is likely to be too high because of the current from the input of the gate.

The requirement to have current flowing *out* from the input at logic 0 means that not all driving circuits are useable. In particular, the NPN emitter-follower, which is so often the automatic choice for many purposes, is unsuitable because (Fig. 7) when the input is at logic 0, the current from the gate will flow through the emitter resistor. A PNP emitter-follower, arranged as shown in Fig. 8, can allow a satisfactory logic 0 voltage, but only if the voltage at the base of the emitter follower can be taken low enough — preferably to a negative voltage, because of the inevitable 0V6 difference between base and emitter voltage levels. The most satisfactory simple driving stage is the straightforward common-emitter amplifier circuit as shown in Fig. 9.

No driving problems should exist if the input of a gate is driven by the output of another gate of the same family. Figure 10 shows the conventional circuit arrangement for a standard TTL gate output, which uses two transistors and a diode in series. A logic 1 output corresponds to having

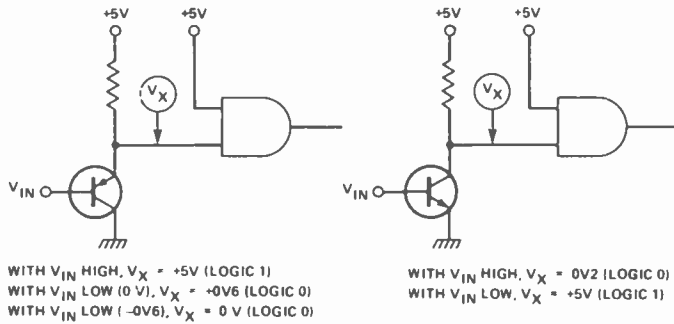


Fig. 8. (Left) Using a PNP emitter follower as a driving stage — a better approach.

Fig. 9. (Right) Driving a gate from a common-emitter stage — the most satisfactory single-transistor drive stage.

the top transistor of the pair conducting and the bottom transistor shut off, and because the base voltage of this top transistor cannot be more than the supply voltage of +5 V, the emitter voltage must be no more than 4V4-4V5, which makes the output voltage (because of the diode) only around 3V8-4V0. Don't be surprised, then, if you find that the logic 1 output from a gate is lower than the supply voltage. The logic 0 voltage from this circuit will be the voltage across the bottom transistor when it is fully conducting, which can be as low as 0V2, depending on the load.

The layout of the output stage is such that only one of the output pair of transistors will be conducting at any time during normal operation. If two gate outputs are connected together, however, it would be possible to have one output at logic 1 (top transistor conducting) and the other at logic 0 (bottom transistor conducting), so that at a low resistance path for current was created (Fig. 11). This would have the effect of burning out one transistor in each gate, so that for the few applications in which gate outputs have to be connected together, special gate ICs described as open-collector types are used. These have no 'top' transistor in the output stages, and are designed to work with an externally connected resistor load (Fig. 12).

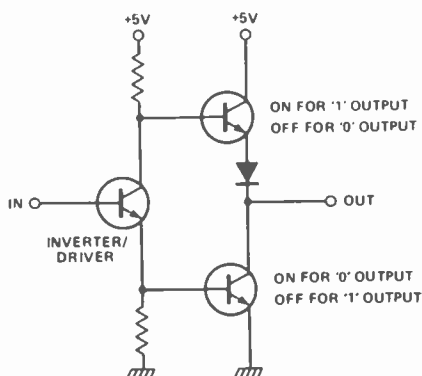


Fig. 10. The usual TTL output stage. One of the pair of output transistors will conduct to connect the output to either 0 or 1 levels.

Standard TTL, though still circulating in very large numbers, has been replaced in production by the low-power Schottky TTL chips, distinguished by the letters LS in the type numbers. These LS chips make use of a component, the Schottky diode, which is not particularly well known, so that some description is called for. The Schottky diode uses a combination of metal (usually aluminium) and semiconductor in its junction to obtain a very low for-

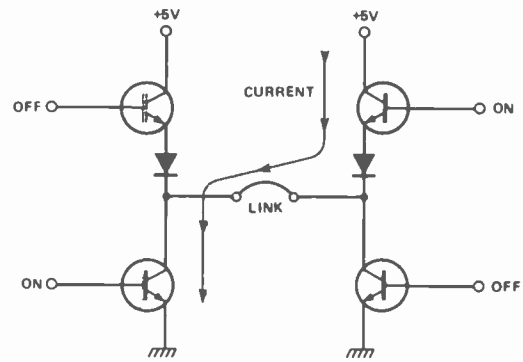


Fig. 11. Why gate outputs should not be connected together.

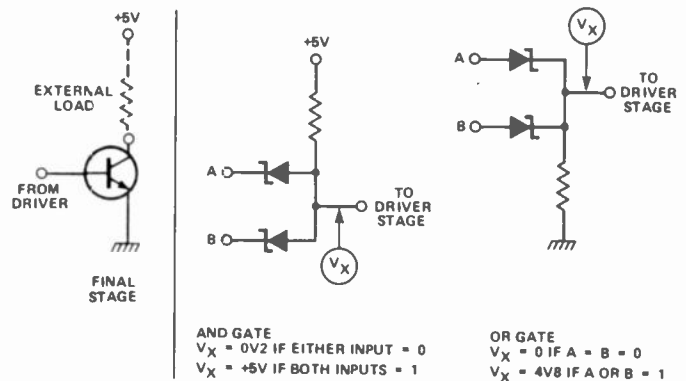


Fig. 12. (Left) The output stage of an 'open-collector' stage. These stages need an external load resistor.

Fig. 13. (Right) Using Schottky diodes as logic elements.

ward voltage, between 0V1 and 0V2 as compared to the 0V6 for a silicon diode. This makes these diodes ideal for use in logic circuits, as illustrated in Fig. 13, and also makes it possible to construct transistor stages which do not saturate. Saturation occurs in a conventional transistor stage when the base current of a transistor, which has a collector load, is so high that the collector voltage bottoms. The effects of saturation are to achieve a very low collector voltage, around 0V2, but also to flood the base junction with charge carriers (electrons or holes depending on whether the transistor is PNP or NPN). When the base voltage is suddenly removed from such a saturated transistor, this charge takes some time to clear, so that the transistor remains conducting — it will not switch rapidly from the conducting state to the non-conducting state. The time is usually less than a microsecond, but it limits the speed at which a gate circuit can operate reliably.

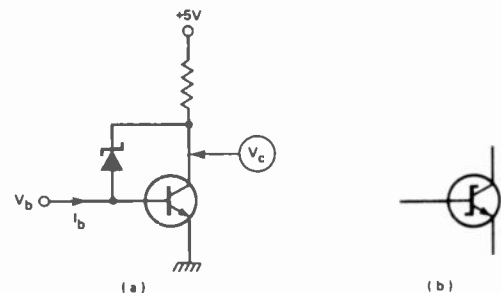


Fig. 14. (a) Using a Schottky diode to prevent transistor saturation. (b) The symbol for a transistor into which a Schottky diode has been incorporated.

A Schottky diode placed between the collector and the base of a transistor (Fig. 14) will prevent such saturation. When the collector voltage reaches a level which is about 0V2 lower than the base voltage, the Schottky diode will conduct, connecting the base and the collector circuits and so bypassing the base. By avoiding saturation in this way, the transistor can be made to switch very much more rapidly at the minor expense of having a collector voltage which does not reach quite so low as that of a standard TTL stage. Figure 15 shows the internal circuitry of a typical LS type of gate circuit in which the presence of Schottky diodes is indicated by the modification to the shape of the base symbol in the transistors.

CMOS

Finally among the commonly-used logic gate circuits we have the CMOS types. These depend on the use of MOSFETs rather than bipolar transistors, and the inputs are invariably to the gates of the MOSFETs as compared to the emitters of the transistors in TTL stages. For this reason, no measurable current flows either into or out from the input of a CMOS gate when we use low-frequency signals, and the fanout under these conditions can be very high. The size of fanout is limited by the ability of the outputs of CMOS gates to supply currents of more than a milliamp or so, because the capacitance of each CMOS input is fairly high, and rapid switching demands that each capacitance be charged and discharged rapidly, calling for current which the output of a CMOS gate may not be able to supply. The operating currents and the dissipation of a CMOS gate will therefore increase as the operating frequency is increased, and it is this factor which limits the fanout and the speed of these gates. A typical CMOS gate circuit is shown in Fig. 16.

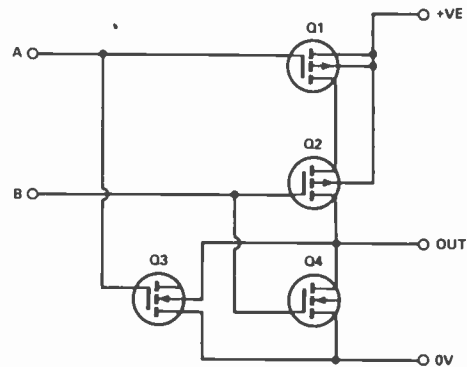


Fig. 16. Circuit of a typical CMOS gate — this one is an AND gate.

low consumption, lower operating speeds and small power outputs, CMOS is the more likely choice, but LS TTL chips are essential for many computing operations in which a high clock-rate is used — you may even find that you need the still-faster (and more power-consuming) 74H types.

We have now reached the end of Configurations, having covered a large number of devices and circuits. I hope that you have found the descriptions and the hints useful, and that some of them will have opened up new frontiers in circuit design for you, because that was the aim of the series. All I can do now is to wish that your circuits will always do what you want them to!

ETI

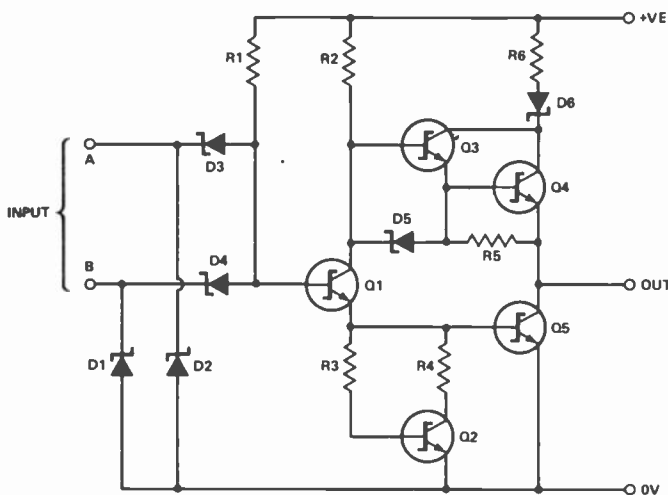


Fig. 15. Circuit for a NAND gate using Schottky diodes.

CMOS gates have a convincing list of advantages for many purposes. The supply voltage can be in the range + 3 V to + 15 V rather than the fixed + 5 V of the TTL circuits. The currents that are required by CMOS gates are very much smaller, so that CMOS is almost an automatic choice when battery operation is required.

For most practical purposes, your choice of logic circuits will be between LS TTL types and CMOS types, with the CMOS types chosen from the 4000 family (RCA), or from the less-well known 74C series (National Semiconductor) in which the type numbers correspond to those of the 74 series of TTL chips. For all purposes which require

Due to promotion

electronics today
INTERNATIONAL

is seeking an Assistant or Deputy Editor

We need someone who will help us to maintain the high technical and journalistic standards of the magazine. The successful applicant will be an accurate, speedy worker who keeps to deadlines, but maintains a sense of humour through thick and thin. A knowledge of electronics and/or microcomputers is needed. Experience in magazine layout would be an advantage.

A competitive salary awaits the right person.

Because of the key nature of this post, we are anxious to make an early appointment, so do not delay in writing, with your cv.

All applications will be treated in strict confidence.

Apply to:
Ron Harris,
Managing Editor,
Argus Specialist Publications,
145 Charing Cross Road,
London WC2H 0EE.

MAKE YOUR OWN P.C.B's. & FRONT PANELS



AT LEAST
10% OFF
NORMAL REC. PRICE

PHOTO RESIST KIT (Ref: HB2)

Complete kit containing artwork PCB, and all necessary process materials
NORMAL REC. PRICE £24.60

UV EXPOSURE UNIT (Ref: UV1)

Perfect results everytime. Kit contains: Lamp, Holder & Shade together with full instructions for DIY Unit which offers PCB, Precision Photo, Label & Panel manufacture
NORMAL REC. PRICE £27.60

UV EXPOSURE UNIT AND ARTBOX (Ref: UV2)

A portable ready made unit containing two 8 watt UV tubes giving a 6" x 9" exposure area which may also be used as a light box with the UV filter supplied.

NORMAL REC. PRICE £64.60

FOTOTOOL KIT (Ref: HB3)

Containing artwork, film and all the necessary process materials required for professional quality labels and panels. CAN ALSO BE USED TO PRODUCE PRECISION PCB PHOTOMASTERS

NORMAL REC. PRICE £23.10

OFFERS VALID UNTIL AUGUST 31st 1983

Please send me the following as quickly as possible

QTY	DESCRIPTION	Price Ea.	TOTAL
	PHOTO RESIST KIT (HB2)	£21.50	£ :
	UV EXPOSURE UNIT (UV1)	£24.00	£ :
	UV ARTBOX (UV2)	£58.00	£ :
	FOTO TOOL KIT (HB3)	£20.00	£ :
	TOTAL	£ :	£ :
	Cheque/PO	£ :	£ :

(Cheques or Postal Orders only please for Special Offers).

Please send full catalogue ☐ Price includes VAT & Carriage.

Name

Address

hobbyboard

a division of
KELAN ENGINEERING LTD
Hookstone Park
Harrogate, N. Yorks

complete P.C.B. workshop

ET1/7B3

T.V. SOUND TUNER

BUILT AND TESTED

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 11 1/2" x 8 1/2" x 3 1/4". E.T.I. kit version of above without chassis, case and hardware. £12.95 plus £1.50 p&p.



£24.95 + £2.00p&p.

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT COMPLETE WITH CASE

SPECIAL OFFER!

ONLY £31.00 plus £2.75 p&p

• NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook up wire. Featured in April P.E. reprint 50p. Free with kit.




STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial AM-ferrite rod, FM-75 or 300 ohms. Stabilised power supply with C core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagram and instructions. SPECIAL OFFER! £13.95 + £2.50 p&p. Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/2" x 8 1/2" x 3 1/4". £3.50 Plus £1.50 p&p.



STEREO CASSETTE DECK

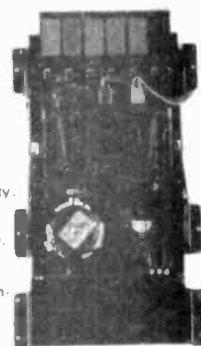
Stereo cassette tape deck transport with electronics. Manufacturer's surplus — brand new and operational — sold without warranty. £11.95 plus £2.50 p&p. Just requires mains transformer and input/output sockets and a volume control to complete. Supplied with full connection details.



125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PCB board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

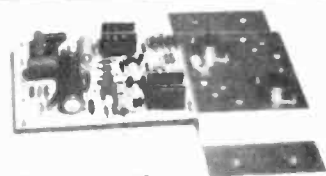ACCESSORIES: Stereo/mono mains power supply kit with transformer: £10.50 plus £2.00 p&p.



SPECIFICATIONS: Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £10.50 + £1.15 p&p. BUILT £14.25 + £1.15 p&p.

BSR RECORD DECK

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45rpm spindle adaptor ideally suited for home or disco. £12.95 + £1.75 p&p.



13" x 11" app.

SPECIAL OFFER! Replacement Stereo cassette tape heads — £1.80 each. Mono: £1.50 each. Erase: £0.70 each. Add 50p p&p to order.

All mail to: 21E HIGH STREET, ACTON, W3 6NG.

Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/5/83, and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

SPEAKER BARGAINS

2 WAY 10 WATT SPEAKER KIT

8" bass/mid range and 3 1/2" tweeter. Complete with screws, wire, crossover components and cabinet. All wood pre-cut — no cutting required. Finish - chipboard covered wood simulate. size 14 1/2" x 8 1/2" x 4". PAIR for ONLY £12.50 plus £1.75 p&p.



ALL CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01 723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 6. Prices include VAT



TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

***Gold service available.**
21 days manufacture for urgent deliveries.

***Orders despatched within 7 days of receipt for single or small quantity orders.**

***5 year no quibble guarantee.**

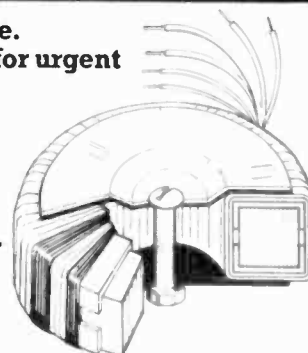

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
NEW! 15 VA 0x010 6+6 1.25 62 x 34mm 0x011 9+9 0.83 0.35Kg 0x012 12+12 0.63 Regulation 0x013 15+15 0.50 19% 0x014 18+18 0.42 0x015 22+22 0.34 0x016 25+25 0.30 0x017 30+30 0.25 £5.12 + p & p £0.78 + VAT £0.89 TOTAL £6.79 (encased in ABS plastic)					120 VA 4x010 6+6 10.00 90 x 40mm 4x011 9+9 6.66 1.2Kg 4x012 12+12 5.00 Regulation 4x013 15+15 4.00 11% 4x014 18+18 3.33 4x015 22+22 2.72 4x016 25+25 2.40 4x017 30+30 2.00 4x018 35+35 1.71 4x028 110 1.09 4x029 220 0.54 4x030 240 0.50 £7.42 + p & p £1.72 + VAT £1.37 TOTAL £10.51					300 VA 7x013 15+15 10.00 110 x 50mm 7x014 18+18 8.33 2.6Kg 7x015 22+22 6.82 Regulation 7x016 25+25 6.00 6% 7x017 30+30 5.00 7x018 35+35 4.28 7x019 40+40 3.75 7x025 45+45 3.33 7x033 50+50 3.00 7x028 110 2.72 7x029 220 1.36 7x030 240 1.25 £10.88 + p & p £2.05 + VAT £1.94 TOTAL £14.87				
30 VA 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 0.45Kg 1x012 12+12 1.25 Regulation 1x013 15+15 1.00 18% 1x014 18+18 0.83 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50 £5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58					160 VA 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 8% 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66 £8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67					500 VA 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 4% 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08 £14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30				
50 VA 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20 £6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60					225 VA 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93 £9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64					625 VA 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60 £17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62				
80 VA 3x010 6+6 6.64 90 x 30mm 3x011 9+9 4.44 1Kg 3x012 12+12 3.33 Regulation 3x013 15+15 2.66 12% 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x028 110 0.72 3x029 220 0.36 3x030 240 0.33 £6.66 + p & p £1.72 + VAT £1.26 TOTAL £9.64					ALSO AVAILABLE Sizes up to and including 5KVA are manufactured to order.									

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage

For 110V primary insert '0' in place of 'X' in type number

For 220V primary (Europe) insert '1' in place of 'X' in type number

For 240V primary (UK) insert '2' in place of 'X' in type number

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.

For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 547778 Telex 965780



ILP TRANSFORMERS
(a division of ILP Electronics Ltd)


LOW COST PROFESSIONAL TEST INSTRUMENTS



Belemic

Hand Held
Analogue and
Digital
Multimeters

16 Models
from £18.75

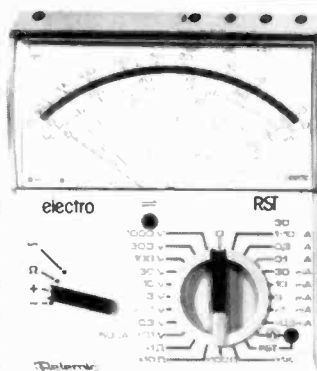

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
9A, Crown Street
St. Ives, Huntingdon
Cambs. PE17 4EB
Tel: (0480) 62440 Telex 32339



FLASH SEQUENCER

Astound your friends, freak out your budgie and out-do David Bailey (who?) with the ETI Flash Sequencer (trick photos a speciality). Design by Phil Walker.

This unit has been designed to be used either on its own or with the multi-function trigger unit described on page 70.

It can be used with up to four separate flashguns connected directly to it and will enable you to get some very interesting action shots.

The delay between each flash can be set by means of the single control over a range of about 1 millisecond to 1 second. This should cover most needs of this sort of shot, but could be altered easily by changing component values.

Use

This is, of course, up to the individual user but with the basic unit described here it would probably be reasonable to set up camera and flash guns on tripods or similar firm supports. Then connect the trigger unit to the camera flash socket (use a suitable adaptor if necessary) and the flashguns to the unit. Set up the focus and aperture

The ETI Flash Sequencer can control up to four flashguns.

to suit the subject and flashguns used and set the shutter speed so that it is longer than the TOTAL delay on the unit. This usually means that you will have to work on a dark night or indoors if you use long delay times.

You will probably have to find the proper aperture setting by trial and error at first, but if you use a black or very dark background and


your subject moves between flashes, the normal or slightly smaller aperture is a good starting point.

With the multi-function trigger unit all sorts of interesting possibilities open up for photographing wildlife or transient events, especially if a solenoid-operated shutter release can be arranged.

The Circuit

The main parts of the circuit are the input latch configured around IC1e and f, the sequence generator consisting of IC2, IC1a, b, c and d, and the output pulse generators IC3, 4, 5, 6, 7 and Q2, 3, 4 and 5. The input latch can be reset to the READY condition by SW2 and will force the timing network to discharge all its capacitors by means of Q1 and D4 to 7. This state is indicated by the LED.

A negative-going pulse at the input or a press on SW1 will make the latch change state and allow the sequence to start. After the first delay period the LED in IC4 will be turned on for about 10 mS, causing its associated SCR (or triac) to turn on and trigger the flashgun to which it is connected. This action occurs when C3 has been charged by the current through RV1 and R6 to the upper threshold voltage of IC1b. The output from IC1b is coupled via a differentiating network (C7 and

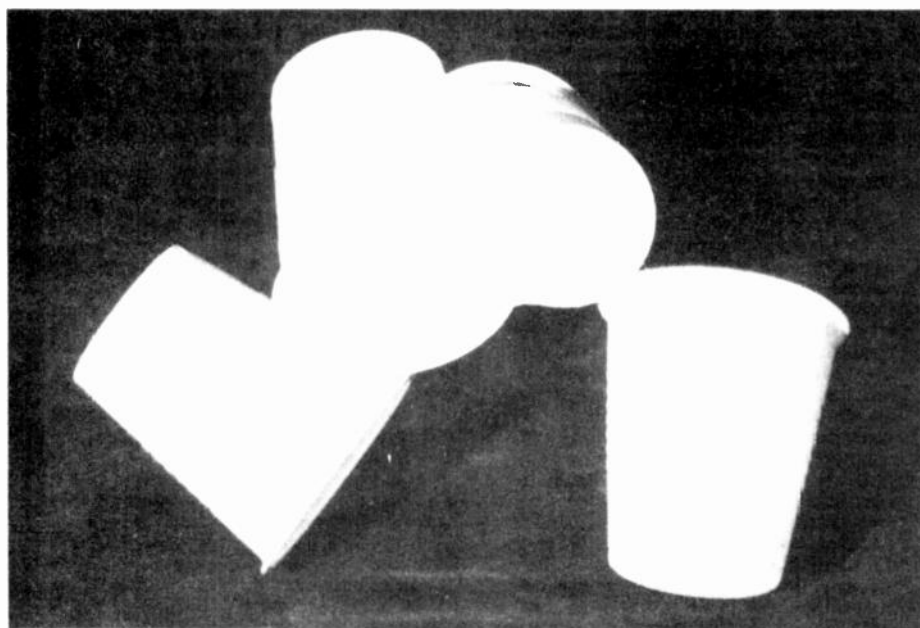

Not four, but one. This bouncing plastic cup was captured at various points in its flight using the sequencer.

NOTE:
IC1 IS 40106B
IC2 IS 4053B
IC3 IS 4093B
IC4,5,6,7 ARE H11C4 or MOC3020
Q1 IS BC214L
Q2,3,4,5 ARE BC212L
D1-11 ARE 1N4148
LED1 IS ANY RED LED

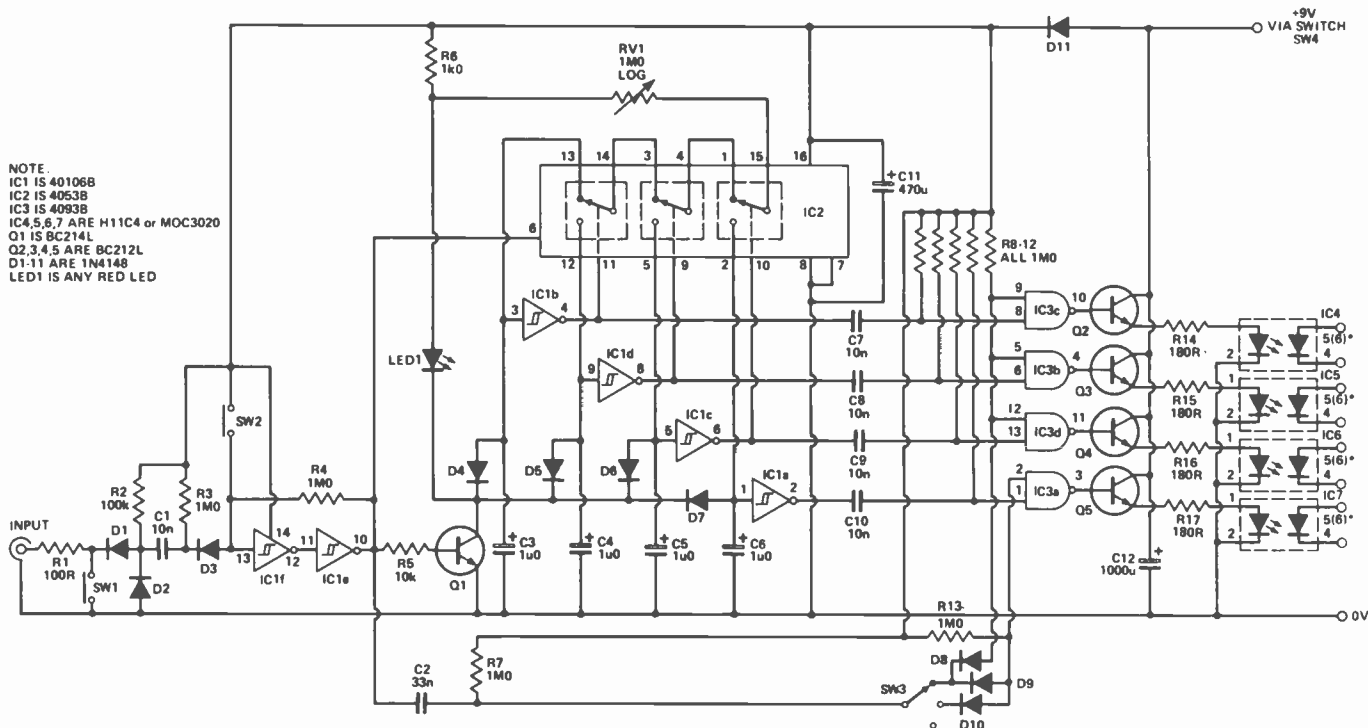


Fig. 1 Circuit diagram. The output connections (marked with an asterisk) depend on the opto device used — see text.

HOW IT WORKS

R8) to IC3c — also a Schmitt trigger. This negative-going pulse causes the output from IC3c to go high for about 10 mS, thus turning Q2 on and hence IC4.

IC1b having changed state, the current from RV1 is now diverted to C4 and will charge this up at the same rate until its voltage reaches the upper threshold of IC1d. A similar set of actions now occurs in IC3b and IC5, resulting in another flashgun being triggered and the timing current being diverted yet again to C5.

The sequence ends when C6 charges and the final flashgun triggers. The circuit is now ready to be reset for another operation.

By means of SW3, a negative pulse generated by C2 and R7 can be routed to the sections of IC3 such that one or all the outputs can be triggered with no delay. This could be used to advantage if the unit is triggered direct from a camera socket and no other lighting is used for special effects or just to get as much light as possible. Beware when using this facility with long delay times set on RV1, as one or more flashguns may recharge and trigger again as the delay operates.

The circuit should not take more than about 10 mA when READY and much less than that when timed out.

The negative-going input pulse to trigger the unit can be derived from a switch or logic source.

IC1e and f are connected together to form a simple latch: R4 is included to avoid shorting the output of IC1e. When SW2 is pressed the output from this latch is set high, this will cause C2 to discharge via R7 and turn Q1 on. Q1 will discharge C3, 4, 5, 6 via D4, 5, 6 and 7 while lighting LED1 via R6. At the same time IC2 will be disabled by the high level on pin 6 from the input latch. This prevents LED1 from being bypassed by the switches in IC2.

In this condition the outputs from IC1a, b, c and d will be high and C7, 8, 9 and 10 can discharge via their associated resistors. This will set the inputs to IC3a, b, c and d to high levels and thus the outputs to a low. Q2, 3, 4 and 5 will be off and the outputs of IC4, 5, 6 and 7 will not conduct.

Assume for the moment that SW3 is in the open position (delayed sequence). If SW1 is now closed or a negative-going pulse appears at the input, this will be passed on via C1 and D3 to the latch formed by IC1e and f causing its output to go low. Q1 will now turn off, extinguishing LED1 and releasing C3, 4, 5 and 6. IC2 will now be enabled and current can now flow in C3 via R6, RV1 and the three switch sections of IC2. This capacitor will charge up until its voltage reaches the upper threshold of IC1b (this is a Schmitt trigger device), whereupon IC1b output will go low. This causes the current to be diverted to C4, where a similar process occurs. At the same time the high-to-low transition is passed through C7 to IC3c whose output will go high from 10 mS or so. This will turn Q2 on and thus IC4 will turn on.

Some time later C4 will charge up to the Schmitt threshold and IC1d will go

low, diverting the current into C5 while also causing IC5 to conduct. The cycle of events will continue with IC1c/IC6 and IC1a/IC7. The result of all this is that flashguns connected to the outputs of IC4, 5, 6 and 7 will be fired in sequence with a delay between each one determined by R6 and the setting of RV1 (and the residual resistance of IC2). IC2 is in fact a triple CMOS changeover switch with a typical on state resistance of 200 ohms.

C7, 8, 9 and 10 have been included to ensure that the opto-coupler LED inputs are not driven continuously, as this would take a lot of current. These capacitors and R8, 9, 10 and 11 define the 'on' time to be about 10 mS. C12 will hold enough charge to provide this even from an aging battery. C11 and D11 isolate the rest of the circuitry from the LED drivers to maintain proper operation.

C2 and R7 (via SW3, D8, 9, 10) provide the alternative operating modes. The initial trigger pulse can be fed via these components to the sections of IC3 such that IC7 will turn on immediately or all the outputs will come on together. Care must be used here as the outputs may pulse again after the set delay time and thus trigger the flashgun(s) again if they recharge in time.

You may notice that the inputs to IC1a, b, c and d will only have their capacitors connected, and no DC path exists to bias them, once the switches have been operated. This will not cause any problems over the 5 seconds maximum of the timing period, as the leakage of the tantalum bead capacitors is quite low and they will have to discharge a long way before the Schmitt trigger gates change state.

PROJECT : Flash Sequencer

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)

R1 100R
R2 100k
R3,4,7-13 1M0
R5 10k
R6 1k0

Potentiometer

RV1 1M0 logarithmic

Capacitors

C1 10nF miniature disc ceramic
C2 33nF miniature polyester
C3-6 1u0 35 V tantalum bead
C7-10 10nF miniature polyester
C11 470uF 10 V aluminium PCB electrolytic
C12 1000uF 10 V aluminium axial electrolytic


Semiconductors

IC1 40106B
IC2 4053B
IC3 4093B
IC4-7 H11C4 (opto-SCR) or MOC3020 (opto-triac). See text.
Q1 BC214L
Q2-5 BC212L
D1-11 1N4148
LED1 any red LED

Miscellaneous

SW1,2 miniature push-to-make push-button switch
SW3 three-way slide switch
SW4 miniature on/off slide switch

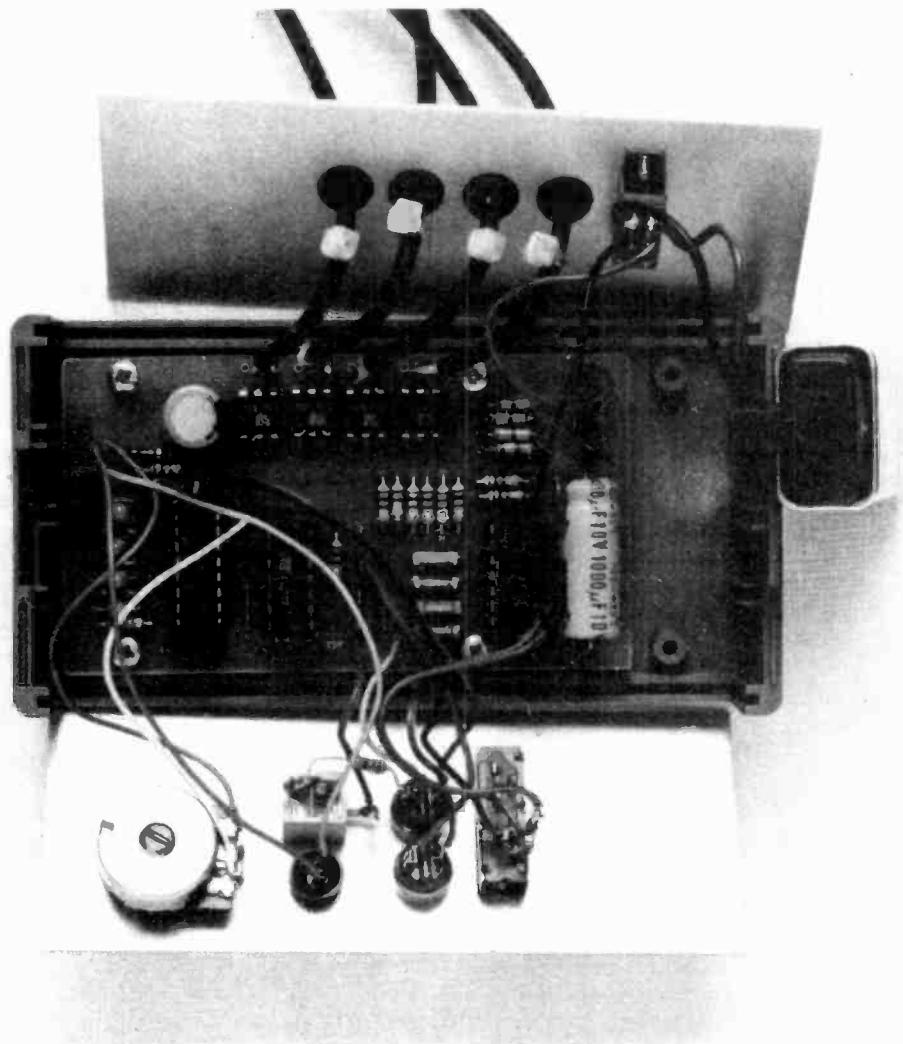PCB (see Buylines); box — Verocase 125 x 65 x 50 mm (order ref. 202-21049A); 3.5 mm jack socket and plug; PP3 battery and clip; four small grommets; four off 1 metre flash extension cables; wire, cable ties etc.



Inside the sequencer.

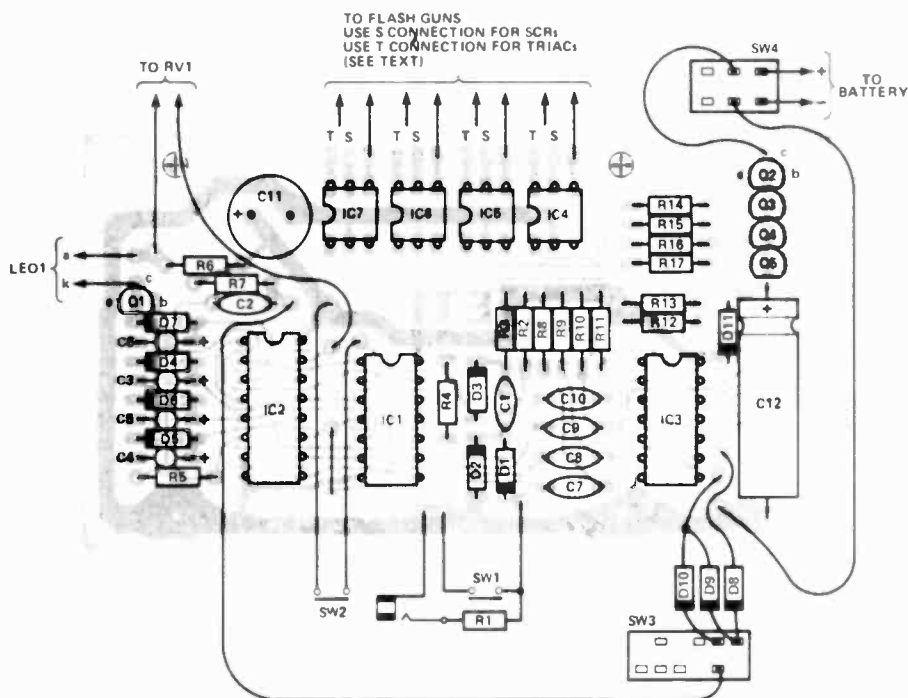


Fig. 2 Component overlay of the ETI Flash Sequencer.

ETI JULY 1983

Construction


Construction of this project should pose no great problems. Take care when positioning the front panel components that they do not foul the parts on the assembled PCB. Note that R1, D8, 9 and 10 are mounted on the panel. It is essential that all the diodes, ICs, and any other polarised components are mounted the correct way round.

We recommend that IC holders are used for the CMOS devices and that care is taken to avoid static discharge damage to these devices.


BUYLINES

The MOC3020 is available from Technomatic and is much easier to obtain than the H11C4. Everything else is standard and readily available, although if you can't find the specified case in the catalogue of your favourite supplier, it can be bought direct from BICC-Vero Electronics, Retail Dept., School Close, Industrial Estate, Chandlers Ford, Eastleigh, Hants SO5 3ZR. The PCB can be bought from our PCB Service as advertised on page 91.


PROJECT : Flash Sequencer

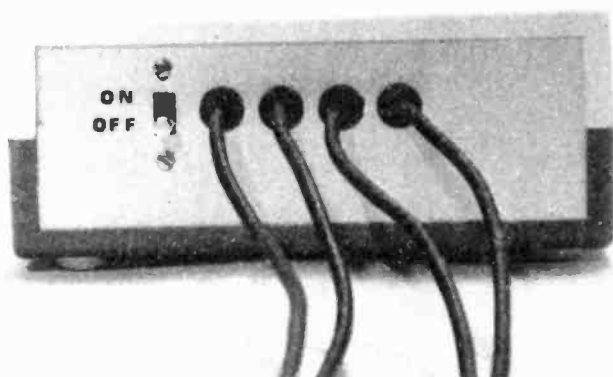

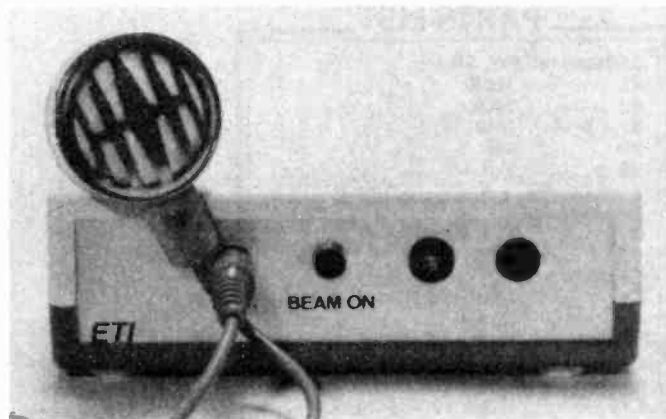The rear of the sequencer carries the on-off switch. We bought four flash extension cables in order to get the right connectors.



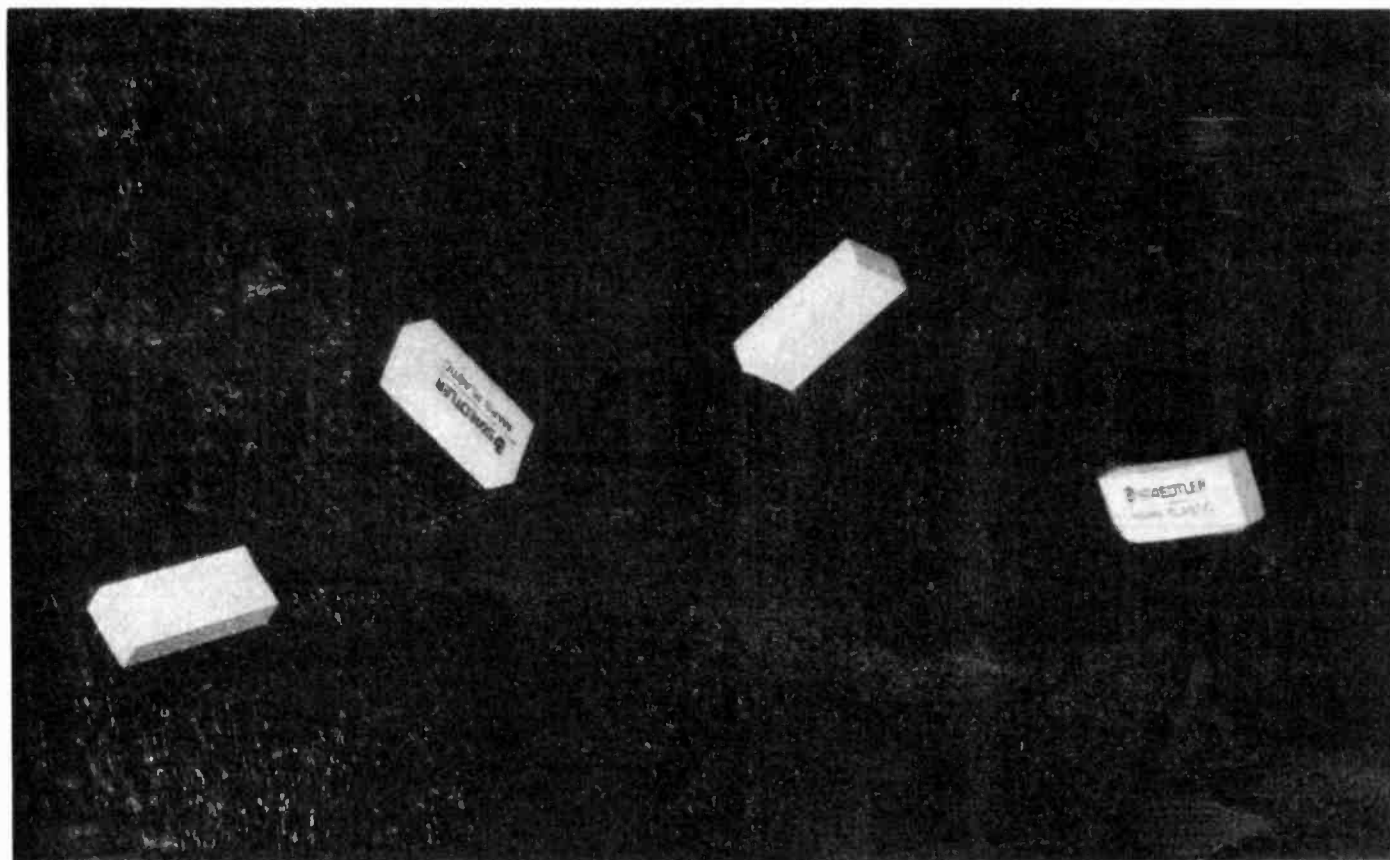The picture on page 63, and the one below of an eraser bouncing from right to left, were shot using the sequencer and the trigger unit above. See page 70.



Output Connections

There are two different connection points for the output from the opto-couplers. This is to accommodate either opto-SCR or opto-triac devices. If opto-SCR devices are used, the flashgun trigger leads must be connected across pins 4 and 5 with pin 4 negative and pin 5 positive. You will have to check the polarity of the connections to the base of the flashguns you use, and this will vary from make to make (ours had a positive inner). If you connect up for one particular make, the trigger unit may not work on another.

If you use opto-triacs, the

flashgun trigger leads should be connected across pins 4 and 6; polarity is unimportant, which will save all the above messing about, so we recommend this option.

Other Points

As we found that sockets for flashgun connectors are unobtainable (unless already connected to something such as a camera) we bought four flash extension cables and cut the unwanted ends off. These were then taken into the box via small grommets and wired directly to the proper terminals. A small cable tie on each lead just inside the box served to take the strain off the

connections. It may be a good idea to buy three one-metre extension cables and one much longer one, so that you can use the extra length from this for the camera-to-unit link (it will have the correct connector).

For greater protection the unit could be built inside a diecast box. This may also be necessary if static discharge causes premature triggering of a flashgun.

Calibration of the delay control would need special apparatus and would depend on the quality of RV1. But the type of device specified should give a reasonable subjective control over the required range.

ETI

BBC
OFFICIAL
DEALER

Micro Computer System

Please phone for availability



WORD PROCESSOR 'VIEW'
16K ROM £52

TELETEXT ADAPTOR
£195.00

BUSINESS, EDUCATION & FUN SOFTWARE IN STOCK

FLOPPY DISC INTERFACE
Incl. 1.2 operating system
£95 + £20 installation

BBC FLOPPY DISC DRIVES

Single drive 5 1/4" 100K £235 + £6 carr.
Dual drive 5 1/4" 800K £799 + £8 carr.

BBC COMPATIBLE DRIVES

These are drives with TEAC FD50 mechanism and are complete with power supply
SINGLE: 100K £190; 200K £260; 400K £340
DUAL: 200K £360; 400K £490; 800K £610
Drive Cables: Single £8 Dual £12
Disc Manual & Formatting Diskette £17.50

Phone or send for our BBC leaflet

CASSETTE RECORDER

BBC Compatible Cassette Recorder with Counter and Remote Control
£26.50 + £1.50 carr.
Cassette Leads £3.50
Computer Grade Cassette
£0.50p each £4.50 for 10 + £1 carr.

MONITORS

MICROVITEC 1431 14" Colour Monitor.....£249 + £8 carr.
MICROVITEC 2031 20" Colour Monitor.....£319 + £8 carr.
KAGA 12" RGB Monitor.....£255 + £8 carr.
Lead for KAGA RGB.....£10
SANYO 12" Hi Res Green Monitor.....£95 + £6 carr.

BBC BOOKS

Basic on BBC £5.95
30 Hour Basic £5.95
Programming the BBC Micro £6.50
BBC Micro An Expert Guide £6.95
Assy. Lang. Prog for BBC £8.95
6502 Machine Codes for Beginners £6.95 (No VAT)

NEC PC 8023 BE-C

Features include:
80 cols 100CPS,
Bi-Directional, Logic seeking,
Proportional Spacing,
Forward & Reverse Line
Feed, Hi-Res and Block
Graphics, International
and Greek characters,
Auto-Underline, Super & Sub
Scripts, Friction & Tractor,
2K Buffer, Cartridge Ribbon.



£345 + £8 carr.

PRINTERS

SEIKOSHA GP 100A

80 Cols 30 CPS
Full ASCII & GRAPHICS
10" Wide paper

Now only £180+ £6 carr.
GP250A £235 plus £8 carr.

Parallel Printer lead for BBC/Atom to most printers £13.50
Variety of interfaces, ribbons in stock
2,000 fan fold sheets 9 1/2" x 11" £13.50 + £3 p & p

EPSON RX80 and FX80



RX80 100CPS 80COL
Tractor Feed £298
FX80 160CPS 80COL
F&T Feed £438
MX100 F/T3 £425
(Carr./printer £8)
Full specification
on request

RUGBY ATOMIC CLOCK

This Z80 micro controlled clock/calender receives coded time data from NPL Rugby. The clock never needs to be reset. The facilities include 8 independent alarms and for each alarm there is a choice of melody or alternatively these can be used for electrical switching. A separate timer allows recording of up to 240 lap times without interrupting the count. Expansion facilities provided. See July/August ETI for details. Complete Kit £145 + £2.00 p&p

MICROTIMER

6502 Based Programmable clock timer with
• 224 switching times/week cycle
• 24 hour 7 day timer
• 4 independent switch outputs directly interfacing to thyristor/triacs
• 6 digit 7 seg. displays to indicate real time, ON/OFF and Reset times
• Output to drive day of week switch and status LEDs.
Full details on request. Price for kit £57.00

ID CONNECTORS

Header	Recep.	Edge
Plug	tacle	Conn
10 way	90	85 120p
20 way	145	125 195p
26 way	175	150 240
34 way	200	160 320
40 way	220	190 340
50 way	235	200 390

D-CONNECTORS

No of Ways	9	15	25	37
Male				
Solder	80p	105p	160p	250p
Angled	150p	210p	250p	365p
Female				
Solder	105p	160p	200p	335p
Angled	165p	215p	290p	440p
Hoods	90p	85p	90p	100p
IDC 25 way plug	385p			
Socket	450p			

TEXTUOL ZIF	DIL SWITCHES
Sockets	4 way 70p
24 pin £5.75	6 way 85p
28 pin £8.00	8 way 90p
40 pin £9.75	10 way 140p

CONNECTOR SYSTEMS

JUMP LEADS

4in Ribbon Cable with headers	14 pin	16 pin	24 pin	40 pin
1 end	145p	165p	240p	380p
2 ends	210p	230p	345p	540p
24in Ribbon Cable with sockets	20 pin	26 pin	34 pin	40 pin
1 end	160p	200p	280p	300p
2 ends	290p	370p	480p	525p
24in Ribbon Cable with D. Conn	25 way Male	500p	Female	550p

AMPHENOL CONNECTORS

36 way plug Centronics Parallel	Solder	£5.25	IDC	£4.95
36 way socket Centronics Parallel	Solder	£5.50	IDC	£5.20
24 way plug IEEE	Solder	£5.00	IDC	£4.75
24 way socket IEEE	Solder	£5.00		

RIBBON CABLE

Grey/meter	
10 way	40p
16 way	60p
20 way	85p
26 way	120p
34 way	160p
40 way	180p
50 way	200p
64 way	280p

Test Clips

14 pin 275p
16 pin £3
40 pin £6

EURO CONNECTORS


DIN 41617	Plug Skt
21 way	160p 165p
31 way	170p 170p
DIN 41612	
2x32 way St. Pin	220p 275p
2x32 way Ang. Pin	275p 320p
3x32 way Ang. Pin	260p 300p
	375p 350p

EDGE CONNECTORS

0.1" 0.156"	
2x18 way	140p
2x22 way	190p 240p
2x23 way	175p
2x25 way	225p 220p
2x28 way	190p
1x43 way	260p
1x43 way	395p
1x77 way	600p
5100 Con n	600p

MICRODOCTOR

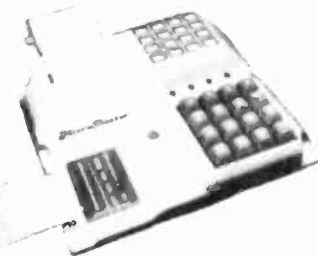This is not a logic analyser or an oscilloscope. It tests a microsystem and gives a printed reprint on RAM, ROM and I/O — it will print memory map, search for code, check dataline shorts and operates peripherals
Microdoctor complete with PSU, Printer, probe cable and two configuration boards. £295.



SOFTY II INTELLIGENT PROGRAMMER

The complete micro processor development system for Engineers and Hobbyists. You can develop programs, debug, verify and commit to EPROMS or use in host computer by using softy as a romulator. Powerful editing facilities permit bytes, blocks of bytes changed, deleted or inserted and memory contents can be observed on ordinary TV. Accepts most 5V Eproms.
Softy II complete with PSU, TV Lead and Romulator lead £169

UV ERASERS

UVIB up to 6 Eproms £47.50
UVIT with Timer £60.00
UV140 up to 14 Eproms £61.50
UV141 with Timer £78.00
(Carr £2/eraser)
All erasers are fitted with mains switches and safety interlocks

E.T.I. PROJECTS

Semiconductors inc. I.C., Transistors, Displays, Connectors and Sockets for most projects are stocked by us.

SPECIAL OFFER

2114L	80p
2716 (+5v)	250p
2532	350p
4116-2	80p
4164-2	450p
6116P-3	350p


BOOKS (No VAT p&p £1)

CRT Controller H/Book £8.50
Programming the Z80 £11.50
Z80 Microcomp. handbook £6.95
Programming the 6502 £10.25
6502 Assy. Lang. £12.10
6502 Applications £10.20
6502 Software Design £9.05
6502 Games £10.52
Large selection of databooks, interfacing books, books on BBC, etc in stock. As for our list.

PLEASE SEND SAE FOR PRICE LIST

74 SERIES									
7400	11p	74198	80p	74LS251	35p	40244	160p		
7401	11p	74221	55p	74LS253	35p	40245	160p		
7402	11p	74251	45p	74LS257	30p	4019	25p		
7403	12p	74259	100p	74LS258	35p	4020	48p		
7404	12p	74265	45p	74LS259	50p	4021	45p		
7405	12p	74273	120p	74LS260	20p	4022	45p		
7406	18p	74276	30p	74LS261	130p	4023	13p		
7407	18p	74278	30p	74LS266	20p	4024	32p		
7408	14p	74283	50p	74LS273	225p	4025	13p		
7409	14p	74284	160p	74LS279	30p	4027	20p		
7410	14p	74285	160p	74LS280	100p	4028	40p		
7411	16p	74290	75p	74LS283	40p	4029	45p		
7412	14p	74293	80p	74LS290	45p	4030	15p		
7413	16p	74298	100p	74LS293	40p	4031	125p		
7414	18p	74301	150p	74LS295	20p	4032	80p		
7415	18p	74305	30p	74LS297	900p	4033	125p		
7416	18p	74306	30p	74LS298	90p	4035	45p		
7417	18p	74307	30p	74LS299	180p	4036	275p		
7418	18p	74308	30p	74LS321	100p	4037	110p		
7419	18p	74309	75p	74LS322	160p	4038	110p		
7420	18p	74310	75p	74LS323	160p	4039	110p		
7421	18p	74311	75p	74LS324	160p	4040	110p		
7541	18p	74431	75p	74LS444	160p	4160	110p		
7542	18p	74432	75p	74LS445	160p	4161			

TRIGGER UNIT

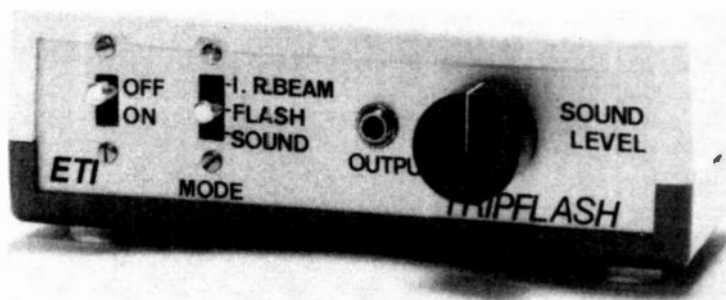

If you're building the ETI Flash Sequencer described elsewhere in this issue, a unit to fire it on various stimuli is a must. This design triggers on sound, light or an infra-red beam. Design by Phil Walker.

This project has been designed to drive the ETI Flash Sequencer and provide facilities to trigger one or more flashguns and get the effect of a multiple exposure at one go. It can be used to trigger on the breaking of an invisible infra-red light beam up to 1 metre in length, on the sound of a pin dropping or even when another flashgun goes off. These functions add a new dimension to creative photography, especially on action shots.

Use

The visible light trigger will normally be used as a slave trigger, allowing up to four extra flashguns to be set off by one which may be fitted to the camera. This will allow 'filling in' or special effects to be created by using relatively cheap flashguns.

The sound trigger option allows all sorts of things to be captured on film, such as objects being thwacked by hammers, drops of water being thrown in all directions and many other noisy events.

Lastly the infra-red beam will allow many other events to be recorded in which the object of the picture is not broken, mangled, or disturbed except by the flash. The content of your pictures can now explore new fields.

If you wish to use this unit to trigger the camera shutter, there are two possibilities open. The first is

that you have an electrical release on your camera, in which case the maker's handbook should be consulted to see whether it can be used.

The second is that a small extra circuit will be necessary, consisting of a power switch and solenoid. Some mechanical linkage could connect the solenoid to a cable or air release and thus release the shutter. The flashgun or flash sequencer would then connect to the camera in the normal way. These methods will avoid the shutter being open for long periods, which might cause unwanted images if all the extraneous light has not been kept out.

Construction

Construction of this unit is relatively straightforward but care must be taken that the components on the front panel do not foul the PCB or battery when assembled. The most critical part in this respect is the three-way mode-select switch. If you use the case specified it will be found necessary to cut off the screw pillars on the lid portion of the box so that the battery and switches fit in. It is recommended that thin screened wire is used for the PCB-to-panel connections (except LED and power) as there are two high-gain amplifiers on board which will probably pick up any stray signals.

Keep the transistor leads short (not more than 5 mm above board) and take full anti-static precautions when fitting IC1 into its socket. Make sure all the diodes, transistors and electrolytics etc are fitted the right way round.

The infra-red photodiode should have its leads kinked before soldering in place so that it can be positioned properly in front of the hole in the back panel. It will be about 8 to 10 mm above the board. The visible light photodiode is mounted in a small grommet and connected to the PCB with flying leads.

It may be advisable to use a panel-mounting LED as the infra-red beam indicator, or paint the rear of an ordinary one black to prevent light from it reaching the photodiode. From this point of view it may be a good idea to paint the whole interior of the case black or line it with black light-proof tape.

Transmitter

This is very easy to assemble so long as the components are put in the right way round. The leads of the IR transmitter LED should be left long enough so that the LED can be bent round and fitted through the case. Make sure that there is enough room for this when fitting the switch. There should be enough space to fit the PCB into the box vertically but a little filing may be needed.

HOW IT WORKS

RECEIVER

The circuit can be considered in three sections. First the modulated infra-red receiver circuit starts with the detector diode D1. This converts the incoming light pulses to small current changes through R1. The resulting voltage is greatly amplified by Q1 and Q2 before being converted to a suitable logic signal in Q3. The output from Q3 is shaped by IC1f before triggering the 700 μ S monostable formed by IC1a and b. When the infra-red beam is being received the output from this monostable consists of a train of pulses 700 μ S low and 300 μ S high (approximately). This train of pulses is applied via R13, 14 and D4 to C6. The time constant for C6 charging is about 1 mS while for discharging it is about 10 μ S. This means that the voltage on C6 is always low while the IR beam is

being received. Thus the output from IC1c is normally high and LED1 will be lit to indicate this condition. If the beam is broken for more than 1 mS a pulse will be missed, the monostable will not discharge C6 and will allow it to charge to the threshold of IC1c. This is a Schmitt trigger device and its output will change state sharply to a low level. This will be transferred via C7 and may be selected by SW1 as the required trigger signal.

Secondly, any sound in the area may be picked up by the crystal microphone and amplified by Q5 and Q6. A portion of this is tapped off by RV1 (acting as a sensitivity control) to drive Q7 which converts it to a suitable logic signal. This may now be selected by SW1 as the desired trigger.

Thirdly, D6 may selected as the

signal source. This will respond to bright lights such as other flashguns to give a 'slave' capability. Any of these signals can be selected by SW1 and used to drive the monostable formed by IC1d and e. This provides a low-going output pulse each time the required trigger conditions are met — that is, on a broken IR beam, a loud noise or a bright light.

THE INFRA-RED TRANSMITTER

This produces a 1 μ S pulse through the IR transmitter diode every 1 mS. The pulse width is determined by R2 and C2 while the repetition rate is set by R1 and C2. IC1 is a 555 timer IC whose output drives the LED via R3 to limit the current a little. D1 and C1 isolate the timing network from the effect of the high current pulses on the battery supply. C3 also helps to reduce these effects.

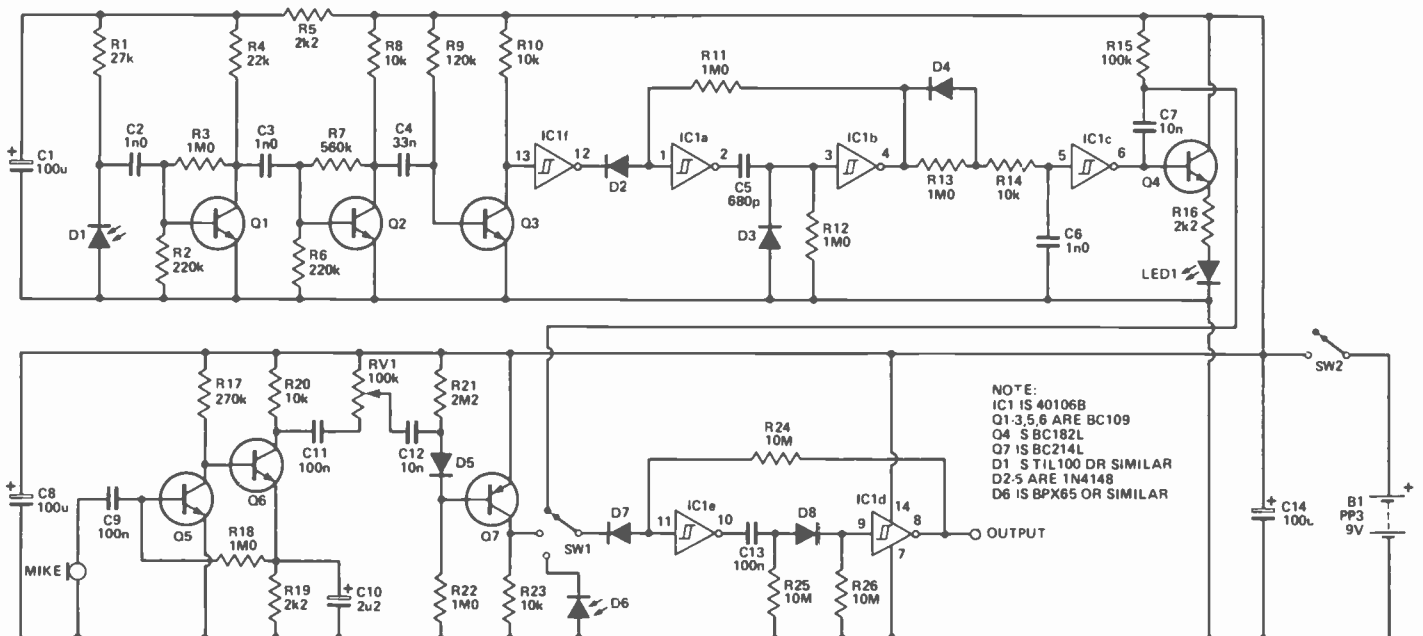


Fig. 1 Circuit diagram for the main board.


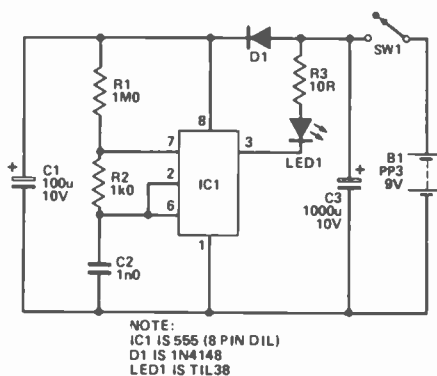


Fig. 2 Circuit diagram for the separate transmitter.

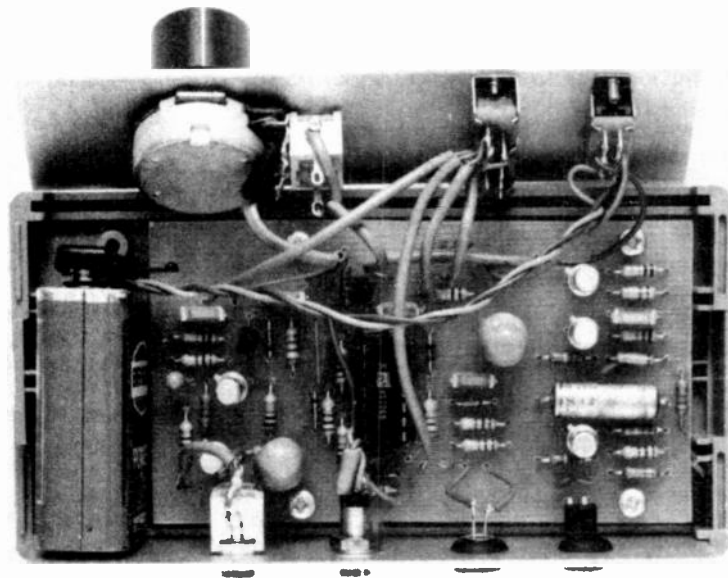Right: Inside the main unit. Take care when wiring to the switches.



PROJECT: Trigger Unit

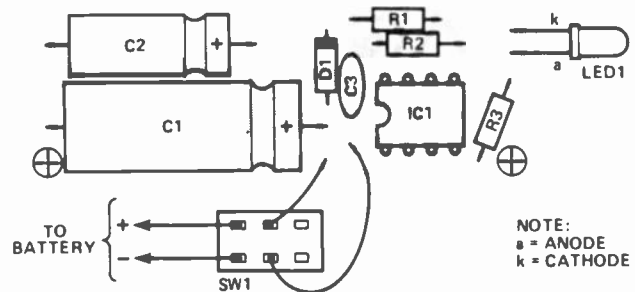
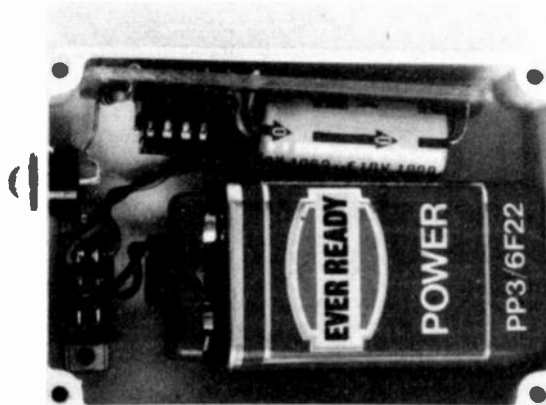


Fig. 3 Component overlay for the transmitter.

Left: A tight squeeze but it will all fit in!

PARTS LIST

Resistors (all $\frac{1}{4}$ W, 5%)

R1 1M0
R2 1k0
R3 10R

Capacitors

C1 100uF 10 V axial
aluminium electrolytic
C2 1n0 miniature disc
ceramic
C3 1000uF 10 V axial
aluminium electrolytic

Semiconductors

IC1 555
D1 1N4148
LED1 TIL38 IR transmitter diode

Miscellaneous

SW1 miniature on/off slide
switch
PCB; box — Verocase 71.5 x 49 x 25.4
mm (order ref. 202-21025K); PP3 battery
and clip; M2 x 5 mm screws, wire etc.

PARTS LIST — RECEIVER

Resistors (all $\frac{1}{4}$ W, 5%)

R1 27k
R2,6 220k
R3, 11-13,
18, 22 1M0
R4 22k
R5,16,19 2k2
R7 560k
R8,10, 14,
20, 23 10k
R9 120k
R15 100k
R17 270k
R21 2M2
R24-26 10M

Potentiometer

RV1 100k logarithmic

Capacitors

C1 100uF 10 V axial
aluminium electrolytic
C2,3,6 1n0 ceramic
C4 33nF ceramic
C5 680pF ceramic

C7,12 10nF ceramic

C8,14 100uF 10 V tantalum

C9,11,13 100nF ceramic

C10 2u2 35 V tantalum

Semiconductors

IC1 40106B
Q1-3,5,6 BC109
Q4 BC182L
Q7 BC214L
D1 TIL100 IR receiver
photodiode
D2-5,7,8 1N4148
D6 BPX65 or similar visible
light photodiode

Miscellaneous


SW1 three-way slide switch
SW2 on/off slide switch
PCB; box — Verocase 125 x 65 x
39 mm (order ref. 202-21048D); two off
3.5 mm miniature jack sockets and
plugs; miniature crystal microphone;
PP3 9 V battery; M2 x 5 mm screws,
wire etc.

Setting up

The infra-red beam link may need a little adjustment for best operation. While doing this it will be necessary to shade the receiver from room lights and other sources. First, switch on the transmitter and place its LED close to the unmarked side of the photodiode (this should be the side nearest the rear panel and visible through the hole in it). Make sure that the 'beam-on' LED lights up. Keeping the transmitter LED pointing toward the receiver, move it away until the indicator LED goes out. Adjust the receiver LED so that it comes on again. Repeat this until a range of about 1 metre is achieved.

The visible light photodiode should not need much attention unless it is too sensitive. If this is the case, it can be de-sensitised with a small piece of masking tape or similar material over the front surface.

Fig. 4 Component overlay for the trigger unit main board.

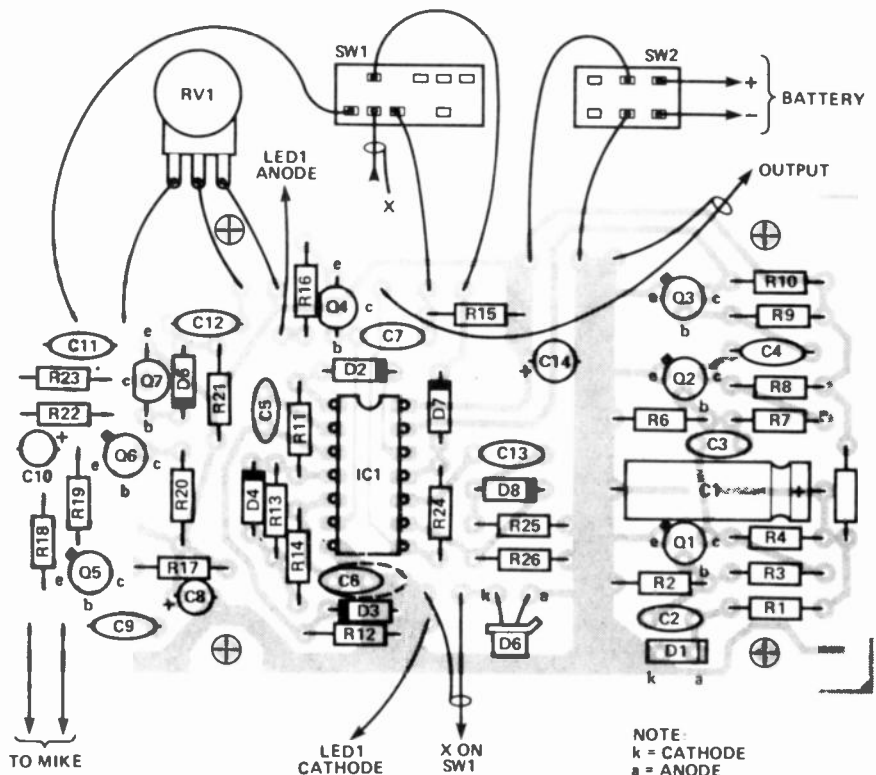

ETI

USED EXTENSIVELY THROUGHOUT THE ELECTRONICS INDUSTRY AND NOW AVAILABLE FOR THE FIRST TIME TO THE AMBITIOUS CONSTRUCTOR, THE R50 DIY COMPUTER FROM RADE SYSTEMS. HERE'S WHAT YOU GET...

- Z80A BASED PROCESSOR ● FULL 64K OF DYNAMIC RAM ● DUAL SERIAL PORTS ● PARALLEL PRINTER PORT
- UNLIMITED EXPANSION VIA TWO EXPANSION CONNECTORS ● FULL 4MHZ CPU ● FULL CPM SUPPORT VIA ADD-ON FLOPPY OR HARD DISC OPTION BOARDS ● USER MANUAL


You can make it.

DOZENS OF APPLICATIONS INCLUDE: ● AUTOMATION DEVICES ● CONTROL APPLICATIONS ● COMMUNICATIONS EQUIPMENT ● BUSINESS MACHINES ● WORD PROCESSORS ● GRAPHICS DISPLAYS ● SCIENTIFIC AND EDUCATIONAL

OPTION BOARDS INCLUDE:

- FLOPPY DISK CONTROLLER £80
 - SPRITE COLOUR GRAPHICS BOARD £99
 - R50 TECHNICAL MANUAL £6.50
- PRICES INCLUDE P+P

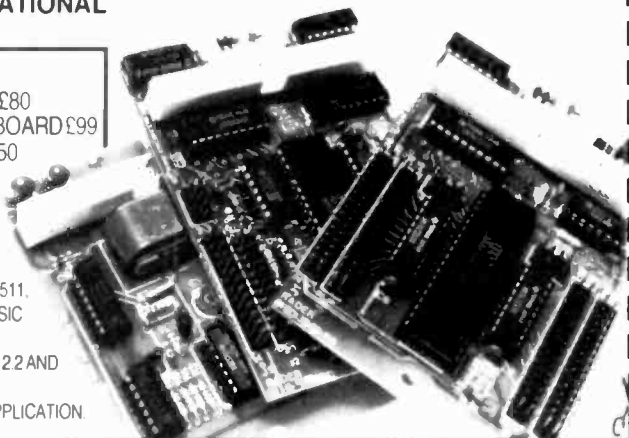ALSO AVAILABLE PIO, SIO, IEEE 488 PORT, REAL TIME CLOCK, PROTOTYPING BOARD, MATHS PROCESSOR USES AMD9511, A TO D CONVERTOR, STEREO SOUND MUSIC BOARD, 192K RAM BOARD, CASSETTE INTERFACE, HARD DISC INTERFACE, CPM 2.2 AND TURBODOS AVAILABLE INTERFACE KITS FOR ALL LEADING MICROS, PRICES ON APPLICATION.



PLEASE MAKE CHEQUES/POSTAL ORDERS PAYABLE TO RADE SYSTEMS LTD.

- R50 DIY SINGLE BOARD COMPUTER £215 ☐
- FLOPPY DISC CONTROLLER £80 ☐
- SPRITE COLOUR GRAPHICS BOARD £99 ☐
- R50 TECHNICAL MANUAL £6.50 ☐
- MORE INFORMATION ☐
- AMOUNT ENCLOSED £

NAME
ADDRESS
POST CODE

RADE SYSTEMS LTD.
290A HIGH ROAD,
WILLESDEN,
LONDON
NW10 2EU

RADE
DIY computer

9" MONITOR in attractive case. Non Standard Input With Info £25 each. Carr £7. Matching ASCII coded Query Keyboard with Numeric Keypad and 27 Function Keys £25 each P&P £5. The Pair £40. Carr £7.
12" MONITOR. Cased Non Standard Input With Info £20 each. Carr £7. With Matching ASCII coded Query Keyboard with Numeric Pad and 24 Function Keys £35 the Pair. Carr £7.
POWER UNIT. 240V Input Outputs +5V/15A, +24V/1.5A, -24V/3A £12 each.
INSTRUMENT CASE standard 19" width x 16" depth x 10" high £5 each. Carr £7.
FLOPPY DISK DRIVE 8 by MEMOREX Connection details £85 each P&P £5.
FOR FURTHER INFORMATION CONTACT DWAYNE STEWART

GEARED MOTOR 117/234 Volt Input 50HZ. 4" dia x 5 1/2" deep. 1" shaft. New £5 each P&P £4.
MOTOR 12V DC Input. 3" dia x 4 1/2" deep. 1" shaft. New £3.50 each P&P £2.
DC MOTOR 6-12 Volts. Mechanical Constant Speed Control 1 1/2" dia. £1 each.
MOTOR 12V DC with pulley & semi-conductor speed control. £1 each.
SYNCHRONOUS MOTOR 2 Phase 9 volt AC. 375 RPM. Good torque (needs 30 40 mfd capacitor Suitable for Robotics/Plotters etc. £1 each.

OTHER SYNCHRONOUS/STEPPING MOTORS AVAILABLE. PLEASE ENQUIRE

GEARED MOTOR 120V 50HZ 4 Watt 1 rpm. 2" dia x 1 1/2" deep. £1.50 each.
CENTAUR FANS 41". Brand new. 100V 20W. 2 speed. £2 each P&P £2.
CENTAUR FANS 41". 115V New. £4.50 each.
MUFFIN 115V 41". unused. £3 each P&P £2.
TRANSFORMERS - All brand new. all 240 volts input.
Sec 25.5V 2.5A. Size 3 1/2" x 2 1/2" £2.50 each.
Sec 115V 1A (auto) £1.20 each. Sec 6V 1.66A £1.50 each.
Sec 12V 100MA 50p each.
TRANSFORMER 127/220 Volt Input. Sec 12V 1A RMS £1.50 each.
TRANSFORMER 120 Volt Input. Sec 10-0-10V 1A 75p each.
Sub Min TRANSFORMER 0-120-240V Input. Sec 12-0-12V 4VA 75p each 10 off £8.
TOROIDAL TRANSFORMER 0-115-230V Input. Sec 13.5-0-13.5V 8VA. £1.50 each 10 off £12.
TOROIDAL TRANSFORMER 0-120-240V Input. Sec 0-12V. 0-12V 10VA per winding. Encapsulated. £4 each. 10 off £35.
Sub Min PULSE TRANSFORMER. Sec centre tapped. Suitable for Thyristor triggering 20p each. 10 off £1.80.
RAPID DISCHARGE CAPACITOR 8 mfd 4KV £5 each P&P £2.

TELEPHONES. 706 style black, blue, green, grey. £5.50 each. 10 off £45.
Discoloured £4 each. 10 off £30. 746 style black or grey £7.50 each. P&P £2 each. 4-10 units £7. Over 10 by arrangement.
TOKIN NOISE FILTER VG215FU. 250VAC 15A 50/60HZ. With fixing bracket. New £2 each.
VU METER. Scaled 0-5. size 1 1/2" x 7/8". 50p each 10 off £4.
I.T.T. LOUD SPEAKER. 3 1/2" dia. 50 ohm 0.2 Watt. New. 75p each. 10 off £5.50.
E.M.T. CABLE. Overall dia 5mm. 10p per metre. 100 metre drum £7.50 P&P £4.
Multi Colour RIBBON CABLE 10 way. 50p per metre. 10 metres £4. 14 way 75p per metre. 10 metres £5. 100 metres £40.
ILLUMINATED ROCKER SWITCH. 2 pole 250V 8 Amp. orange. 50p each. 10 off £4.
JOYSTICK SWITCH 4 directions. £3 each. P&P £2.
CATHODE RAY TUBES. Brand new. D14-121GM & D14-12GH £40 each. SE5/2A/P31 £25 each. Many others available. please enquire.
PCB KEYBOARD PAD. 19 push contacts. 0-9. A-F plus 3 optional. £1.50 each. 10 off £12.
KEYBOARD PAD. 12 Alma Reed Switches. push to make. 0-9. + & Blank. size 3 x 2 1/2" x 2" high. £4 each. 10 off £15. P&P £3.
EPROM 2716 Single rail. £1.50 each. 2564 £4 each.
SPECTRAL RELIANCE TEN TURN POT. 100 ohm ± 1%. Brand new. 75p each 10 off £8.
SLIDER POTENTIOMETER. Twin Gang. 200K or 1M. 35p each 10 off £3.
PANEL MOUNTING FUSE HOLDER for 1 1/2" fuse. 20p each. 10 off £1.50.
BELLING LEE CHASSIS MOUNTING FUSE HOLDER for 1 1/2" fuse. 15p each. 10 off £1.
I.E.C. MAINS LEAD. 2 metre length. heavy duty. 40p each. 10 off £5.
4 CORE CURLY WIRE extending to 2 metres. 20p each. 10 off £1.80.
MICROPHONE/EARPIECE INSERTS. Brand new. 75p each. 10 off £8.

EXECUTIVE TELEPHONE-PUSH BUTTON. Functions include 10 number memory. repeat dialing. internal Microphone & Speaker and separate handset etc. Will connect direct to British Telecom System. BRAND NEW. ONLY £25 ea. P&P £4.
PUSH BUTTON TELEPHONES for Internal Systems BRAND NEW. P&P £2 ea. 746 style Two Tone Grey £8 each. KRONE type FeTap 731 Beige £6 ea. Quantity discount - Please Enquire

Minimum Order of Goods £3. Minimum P&P £1.50. VAT at 15% MUST be added to TOTAL OF GOODS & PACKAGING.
Many more components and test equipment available. S.A.E. or telephone for lists.

FOR HI-FI & ELECTRONICS ENTHUSIASTS!

We are the specialists of electronic kits. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control (electronic touch switch, sound activated switch, light activated switch, infra-red remote control), music generators, battery fluorescent light and high quality black anodised amplifier cases... etc. with illustrative pictures now available at the cost of 60p including P + P, together with a 10% discount voucher for your first order.

EQUALIZER & REVERBERATION AMPLIFIER

Equaliser Built £73.50



Reverberator Built £79.50

All prices include VAT

HI-FI AMPLIFIER MODULES



TA-323A 30W + 30W stereo amplifier £18.95 Kit £23.95 Ass.
TA-280 60W + 60W stereo amplifier £27.50 Kit £33.50 Ass.
TA-920 70W + 70W stereo amplifier £36.50 Kit £42.50 Ass.

CONTROL MODULES



TY-7 Electronic touch switch £2.90 Kit £4.50 Ass.
TY-11 Light activated switch £2.20 Kit £3.50 Ass.
TY-18 Sound activated switch (Clap switch) £4.50 Kit £5.95 Ass.
TY-38 Sound activated switch (voice switch) £5.50 Kit £7.50 Ass.
TY-41 Infra-red remote control (receiver and transmitter) £17.20 Kit £21.95 Ass.

PROFESSIONAL RACK MOUNTING CABINET



Available Soon
● Wholly made of black anodised aluminium sheets ● Suitable for high quality amplifiers and many other purposes ● Top, bottom and rear cover removable for access ● Different sizes available ● Compatible price ● Front panel is of brushed aluminium finish

To: Concept Electronics Ltd., 51 Tollington Road, London N7 6PB
Mail orders only
Please send me the electronic kits catalogue & the 10% discount voucher for my first order. I enclose 60p in stamps/cheque/postal order. Make cheques payable to Concept Electronics Ltd.

Name
Address
Block caps please

STEWART of READING

110 WYKHAM ROAD, READING, BERKS. RG6 1PL

Tel: (0734 68041)

Callers welcome 9 am-5.30 pm Monday to Saturday inclusive



TYPE 161B DUAL POWER SUPPLY KIT

INCORPORATES A POSITIVE & A NEGATIVE REGULATED SUPPLY

BOTH ARE ISOLATED & ADJUSTABLE 1.3V TO 16V D.C.

Interconnect to give 2.6V to 32V or


- 1.3V/0 + 1.3V to - 16V/0 + 16V

Output current 1A at 16V to 0.35A at 1.3V

Ripple is less than 1mV

£25.99

inc. P & P and VAT

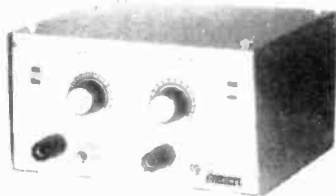

Built & Tested

£37.95 inc. P&P and VAT

Comprehensive design details with calculations

are included so that the kit is an exercise in power supply design. The kit, which uses quality components, is complete with instructions. Case punched and stove enamelled in attractive blue and grey with a printed front panel to give a professional finish.

Excellent for the beginner, the experienced amateur and as a tutorial for schools and colleges.

SEND CHEQUE OR P.O.

ALLOW 21 DAYS FOR DELIVERY

BRANIME MARKETING LTD DEPT. ETI
BALTHANE IND. EST., BALLASALLA, ISLE OF MAN

Branime
TEACHING KITS
BUILD YOUR KNOWLEDGE



BIG ELECTROLYTICS

from

EMOS



- * Computer grade
- * Made by Sprague or G.E.
- * Short shelf life

BARGAIN PRICES TO CLEAR

*** ONLY £2.50 EACH ***

any of the following values

300,000 @ 7V	100,000 @ 30V
185,000 @ 15V	71,000 @ 40V
120,000 @ 15V	60,000 @ 40V

IMMEDIATE DELIVERY

p&p	1 or 2 capacitors	£1.00
	3 to 6	£1.50
	6 +	£2.00

Dept. 5F, High March, Daventry, NN11 4HQ
Tel. 03272 5523

Please add 15% V.A.T.

Send large s.a.e. for catalogue giving details of our vast range of components. Walk round supermarket open Mon - Sat 9 - 4. Come and see our fantastic offers.

EMOS

Accurate Digital Multimeters at Exceptional Prices

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- * 10 amp AC/DC
- * Battery: Single 9V drycell. Life: 200 hrs
- * Dimensions: 170 x 89 x 38mm.
- * Weight: 400g inc. battery.
- * Mode Select: Push Button.
- * AC DC Current: 200µA to 10A
- * AC Voltage: 200mV to 750V
- * DC Voltage: 200mV to 1000V
- * Resistance: 200Ω to 2MΩ
- * Input Impedance: 10MΩ
- * Display: 3 1/2 Digit 13mm LCD
- * O/Load Protection: All ranges

OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010
-5% Accuracy
£29.95

7030
-1% Accuracy
£35.95

NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

NEW
HM102 BZ
£13.00

NEW HM 102 BZ SPECIFICATION

- * DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- * AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- * Decibels: -20 to +22dB
- * DC Current: 0-50, 500µA, 0-5, 50, 500mA
- * Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- * Power Supply: One 1.5V size 'A' battery (incl)
- * Size & Weight: 135 x 91 x 39mm, 280gr.



HM 101 POCKET SIZE MULTIMETER SPECIFICATION

- * DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- * Decibels: -10 to +22dB
- * DC Current: 0-100mA
- * Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- * Power Supply: One 1.5V size 'A' battery (incl)
- * Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- * Price: £5.50

Quantity discount for trade on application.

Add 15% to your order for VAT. P&P is free of charge. Payment by Cheque with Order.

ARMON ELECTRONICS LTD.

Access & Barclaycard accepted.



Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone 01-902 4321 (3 lines)

TELEX No 923985



LB ELECTRONICS

LIMITED STOCKS

Brand new havard H452, power supply and Nickel charger, output 13 volts at 0.7A (max 1 amp) 7" x 3" x 3 1/2" appx. Fully cased and boxed only £4.95p plp £1.70p.

SPECIAL OFFERS

(while stocks last)
Mullard 2" Red L.E.D.'s 0.06p, 7805 38p, 7805KC 5 Volt 1.5A 75p,
78H05 5V 3 AMP £3.50p, 5K 3/4" multiturn trim pots 14 for
£2.50p

DISC DRIVE BONANZA

PERTEC FD650 DSDD £199 + VAT
TEAC FD-55F 1/2 Height DSDD 80 track £288 + VAT
Cannon 2/3 drive SSDD Shugart Compatible £129 + VAT
40 Track

Apple controller card for two drives..... £40.00 + VAT p&p 50p
ASC11 coded qwerty Keyboard, manufactured by Alphanumeric
(Woking UK). Model 60K brand new plus data..... £19.95p p&p
£1.50

25 WAY 'D' Types, plugs £1.85, sockets £1.85 (solder tail) p&p
30p. Telephone for bulk prices.

8" Drive Cabinets complete with power supply (LINEAR) to take
two 8" Drives, Brand New £99.95p + VAT 5p (carriage cost)

Twin 5" Cabinets with power supply £30.00 + VAT (providing a
disc drive is purchased from us, if drives purchased elsewhere
£40.00 + VAT)

9" Green Phosphor Monitors Brand New and Cased Composite
Video Input 18mhz band width £78 + VAT each (carriage cost)

American
Express

LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON,
MIDDLESEX UB10 9 LS, ENGLAND
TEL: UXBRIDGE 55399



HAPPY MEMORIES

Part Type	1 off	25-99	100 up
4116 200ns	.90	.81	.78
4116 250ns	.70	.63	.60
4816 100ns For BBC comp	2.20	1.95	1.85
4164 200ns	3.99	3.56	3.42
2114 200ns Low power	1.15	1.00	.90
2114 450ns Low power	.95	.85	.80
4118 250ns	3.35	3.00	2.85
6116 150ns CMOS	3.35	3.00	2.85
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.35	2.10	2.02
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.50	3.15	3.00
2532 450ns Texas type	3.70	3.30	3.00
2764 250ns	4.90	4.35	4.20

Z80A-CPU £3.95	Z80A-PIO £2.99	Z90A-CTC £2.99
6522 PIA £3.70	7002 A-D £4.60	3691 £2.75
88LS120 £2.20	7805 reg .50	7812 reg .50

Low profile IC sockets: Pins 8 14 16 18 20 22 23 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSDD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
5 inch DSQD £26.35
8 inch SSDD £19.25 8 inch SSDD £23.65 8 inch DSDD £25.50

74LSLS series TTL, large stocks at low prices with DIY discounts
starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to
total. Access & Visa welcome. 24hr service on (054 422) 618
Government & Educational orders welcome, £15 minimum.
Trade accounts operated, 'phone or write for details.

Happy Memories (ETI),

Gladestry, Kington, Herefordshire. HR5 3NY.
Tel: (054 422) 618 or 628

EUROPA ELECTRONICS

Mail Order to 160 High Road, Willesden, London NW10 2PB

TEL: 01-907 1659

SEND FOR A FREE LIST OF OUR LARGE RANGE OF ITEMS ALL DEVICES ARE NEW, FULL SPEC AND GUARANTEED

Post & Packing: Add 30p to all orders under £5.

VAT: All UK orders add 15% to total cost including p. & p.

TTL SERIES		74LS14	75p	TTL	TRANSISTORS		4000 CMOS		LINEAR		
		74LS15	40p	7400							
74LS00	11p	74LS154	30p	7401	AD161	42p	4000	10p	741	14p	
74LS01	11p	74LS155	30p	7402	AD162	42p	4001	12p	748	80p	
74LS02	11p	74LS156	30p	7403	BC107	10p	4002	12p	CA3019	80p	
74LS03	12p	74LS157	25p	7404	BC108	12p	4006	50p	CA3048	70p	
74LS05	12p	74LS158	30p	7405	BC109	10p	4008	38p	CA3048	220p	
74LS06	12p	74LS160	30p	7406	BC109C	12p	4009	24p	CA3059	285p	
74LS07	12p	74LS161	36p	7407	BC177	14p	4010	24p	CA3060	285p	
74LS08	12p	74LS162	36p	7408	BC178	14p	4011	11p	CA3080E	72p	
74LS09	12p	74LS163	36p	7409	BC179	20p	4012	16p	CA3086	48p	
74LS10	12p	74LS164	40p	7410	BC179	20p	4013	20p	CA3130E	80p	
74LS11	13p	74LS165	50p	7411	BC182L	10p	4014	48p	CA3130T	110p	
74LS12	12p	74LS166	80p	7412	BC183L	10p	4015	40p	CA3140E	80p	
74LS13	15p	74LS168	85p	7413	BC184L	10p	4016	20p	CA3140E	80p	
74LS14	25p	74LS169	85p	7414	BC187	10p	4017	32p	CA3160E	100p	
74LS15	12p	74LS170	70p	7415	BC213L	10p	4018	45p	CA3181E	150p	
74LS20	12p	74LS173	50p	7427	BC214L	10p	4019	25p	CA3182E	450p	
74LS21	12p	74LS174	40p	7428	BC2547	12p	4020	48p	CA3189E	300p	
74LS22	12p	74LS175	40p	7430	BC2548	12p	4021	48p	CA3240E	110p	
74LS26	12p	74LS181	80p	7448	BC3549C	14p	4022	45p	CA3280G	200p	
74LS27	13p	74LS183	120p	7450	BC3556	15p	4023	13p	LF347	180p	
74LS28	14p	74LS190	30p	7474	BC3567	15p	4024	32p	LF351	80p	
74LS30	12p	74LS192	35p	7475	BC3568	15p	4025	13p	LF353	80p	
74LS32	13p	74LS193	35p	7476	BC3569	15p	4026	80p	LF355	80p	
74LS33	14p	74LS193	35p	7477	BC3570	15p	4027	20p	LF356	80p	
74LS37	14p	74LS194	35p	7485	BC3571	15p	4028	20p	LF357	110p	
74LS38	15p	74LS195	35p	7491	BC3572	15p	4029	40p	LM301A	25p	
74LS40	15p	74LS196	45p	7492	BC3573	15p	4030	15p	LM301 120p		
74LS42	15p	74LS201	45p	7493	BC3574	15p	4031	110p	LM311 70p		
74LS47	35p	74LS220	55p	7494	BC3575	15p	4032	40p	LM318 160p		
74LS48	35p	74LS221	55p	7495	BC3576	15p	4033	40p	LM319 216p		
74LS51	14p	74LS242	55p	7496	BC3577	15p	4034	40p	LM324 20p		
74LS54	14p	74LS245	55p	7497	BC3578	15p	4035	40p	LM334E 80p		
74LS55	14p	74LS243	55p	74107	BC3579	15p	4036	40p	LM335 100p		
74LS63	18p	74LS247	55p	74122	BC3580	15p	4037	40p	LM339 50p		
74LS73	18p	74LS245	70p	74123	BC3581	15p	4038	40p	LM348 85p		
74LS74	18p	74LS247	55p	74160	BC3582	15p	4039	40p	LM380 75p		
74LS75	18p	74LS248	55p	74161	BC3583	15p	4040	40p	LM381N 40p		
74LS76	17p	74LS249	55p	74162	BC3584	15p	4041	40p	LM382 110p		
74LS83	16p	74LS251	35p	74163	BC3585	15p	4042	40p	LM384 80p		
74LS85	16p	74LS253	35p	74164	BC3586	15p	4043	40p	LM386 80p		
74LS86	16p	74LS257	35p	74165	BC3587	15p	4044	40p	LM387 120p		
74LS90	22p	74LS258	35p	74166	BC3588	15p	4045	40p	LM389 80p		
74LS91	80p	74LS259	35p	74167	BC3589	15p	4046	40p	LM393 100p		
74LS92	80p	74LS260	35p	74190	BC3590	15p	4047	40p	LM3900 80p		
74LS95	40p	74LS261	138p	74191	BC3591	15p	4048	40p	LM3909N 120p		
74LS96	50p	74LS266	20p	74192	BC3592	15p	4049	40p	LM3914 120p		
74LS107	20p	74LS273	30p	74193	BC3593	15p	4050	40p	LM3915 280p		
74LS109	27p	74LS275	225p	74194	BC3594	15p	4051	40p	LM3916 280p		
74LS112	20p	74LS279	30p	74195	BC3595	15p	4052	40p	LM3918 280p		
74LS113	20p	74LS280	100p	74196	BC3596	15p	4053	40p	LM3919 280p		
74LS114	22p	74LS283	40p	74197	BC3597	15p	4054	40p	LM3920 280p		
74LS122	28p	74LS383	140p	74198	BC3598	15p	4055	40p	LM3921 280p		
74LS123	34p	74LS364	140p	74199	BC3599	15p	4056	40p	LM3922 280p		
74LS124	30p	74LS366	27p	74200	BC3600	15p	4057	40p	LM3923 280p		
74LS125	24p	74LS367	27p	74201	BC3601	15p	4058	40p	LM3924 280p		
74LS126	25p	74LS368	27p	74202	BC3602	15p	4059	40p	LM3925 280p		
74LS132	34p	74LS368	27p	74203	BC3603	15p	4060	40p	LM3926 280p		
74LS133	30p	74LS374	55p	74204	BC3604	15p	4061	40p	LM3927 280p		
74LS136	25p	74LS375	45p	74205	BC3605	15p	4062	40p	LM3928 280p		
74LS137	27p	74LS378	45p	74206	BC3606	15p	4063	40p	LM3929 280p		
74LS139	27p	74LS377	45p	74207	BC3607	15p	4064	40p	LM3930 280p		
74LS145	70p	74LS390	45p	74208	BC3608	15p	4065	40p	LM3931 280p		
74LS147	120p	74LS393	45p	74209	BC3609	15p	4066	40p	LM3932 280p		
				LEDS inclcd. clip							
				3mm 5mm							
				Red 11p 12p							
				Green 14p 14p							
				Yellow 14p 14p							

AUDIOPHILE

Stop press. Just in time for this issue, Vivian Capel supplied a report on the topical and apparently revolutionary Hugo Zuccarelli and Holophonic Head. Don't go away, it isn't a music hall act . . .

What caused hard-bitten cynical audio experts to gasp in amazement? What produces multi-directional sound from two channels; and still does so when one channel is switched off? What has put conventional stereo, and even quad, into the same class as the wind-up trumpet gramophone? What modern discovery has been clouded with more myths and confusion than The Ring? Who or what is Ringo?

The answer to all these questions lies in the new brain-child of 26-year old inventor Hugo Zuccarelli, the Argentine-born Italian now resident in London. The system is termed holophony after a claimed, though rather tenuous, comparison with holography.

It seems that Mr. Zuccarelli has been musing over the principles of holophony for a long time, since he was nine no less, but it wasn't until October 1981 that he filed a European Patent Application which describes his invention and gives patent protection in nine European countries.

Since then, particularly in January and February of this year, there have been press demonstrations and a TV programme in the 'Real World' series. The results of these have been impressive indeed, with audio experts and reviewers being converted from scepticism to astonished acceptance. Neurophysiologist Dr. Martin Rosenberg of London University has joined the redoubtable Angus Mackenzie (who is not given to extravagant praise) in acclaim with phrases such as "quite striking and novel," and "absolutely remarkable."

Sounds Interesting

So what was the cause of all the excitement? The demonstrations were conducted with recordings played through a pair of conventional stereo headphones, although a pair of stereo speakers suitably placed will give the same result. This immediately strikes a favourable note, as it means that potential users do not have to buy or change expensive hi-fi, or find room for extra speakers as with the defunct quad systems. Existing speakers can do the trick, with perhaps a move from the usual stereo front location to a side position. Another proviso we shall see later.

Some of the recorded material was played by digital recorder, but there were also recordings from an ordinary stereo cassette machine. There was no evidence of a special decoder (as needed with the quad systems): in fact there was little different from an ordinary stereo system — except the recordings.

These consisted of everyday sounds rather than music, and so were more readily comparable to normal experience; people moving about and talking, matches being struck, birdsong and jet aircraft. The remarkable thing was that in every case the exact location of the sounds could be pin-pointed. Not only in front, as is the case with normal good stereo, but at the sides and the back, and even overhead and below at floor level. There was a com-


plete sphere of locatable sound sources. This demonstrated the superiority over quad systems, which imperfectly create the illusion of 'surround sound' and fail to give a height dimension.

The degree of realism was so great as to produce descriptions such as 'terrifying' from the subjects — especially when the experience took place in a darkened room, and the eyes could not contradict the evidence of the ears. One auditioner spoke of withdrawing his feet instinctively as he heard someone walking directly in front of him, the sound of footsteps coming unmistakably from the floor, while another claimed to have felt the "heat" from a match that was struck in front of his face. Those listening in a normally lit room but with eyes closed as instructed, frequently had to open them to reassure themselves that it was only a recording.

Myths And Legends

There is then no doubt, that the system does work, and it works quite remarkably. The question (and it is a big one) is HOW does it work?

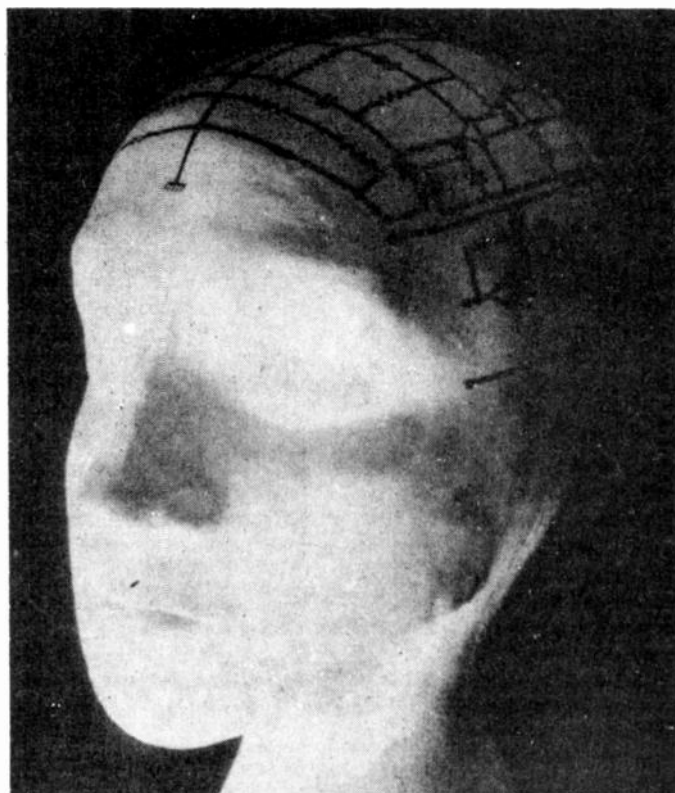Although protected by patent, Zuccarelli is more than normally protective in guarding the secret. Perhaps he has good reason to be, as imitators in the past have not found it impossible to get around patents. So, in addition to be-



ing vague in describing the principle of working, he has disseminated half-truths which have been interpreted in various ways by journalists, mostly with completely erroneous 'explanations'. Also statements have been made which are quite misleading.

The result, as readers who may have seen press reports in other magazines will have gathered, is confusion and conflicting theories. Some of these appear to be contrary to the known facts of physics and biology, and unfortunately have done little to raise the system's credence in the minds of doubters. It is a pity that what is undoubtedly a genuine breakthrough should be so surrounded by clouds of suspicion and scepticism.

Let us take a look at what has been already published. Firstly, the name holophony is meant to imply a similar mode of operation to that of holography. With this, a beam from a coherent light source such as a laser is split into two parts. One is the reference beam which is directed at a photographic plate or film. The other illuminates the object to be photographed from which reflections are also received at the plate. These are delayed by reason of the extra distance they have travelled, the delay thus being proportional to the depth of the object.

The object beam is now has a slightly different phase than the reference, and re-combining them at the photographic plate produces interference patterns. Where there are no reflections from the object such as from holes in its surface or beyond its boundaries, there are no patterns on the plate, only the reference beam.

Thus the plate carries two-dimensional information corresponding to the flat or frontal appearance, but in addition it has information regarding the depth as conveyed by phase differences and the resulting patterns. So the original image in depth can be reconstituted with the use of a laser.

Your Theory Is Crazy . . .

In an attempt to reconcile this principle with the claimed workings of holophony, writers have tried to identify the two components, the signal and reference, and have met with trouble, especially in the case of the latter. They report Zuccarelli as asserting that the ear is not a receiver but a transmitter. It actually radiates a sound which interacts with the incoming pressure waves and compares them to produce a resultant signal which somehow has spatial information.

A variant of this is that the reference is like 'pink' noise (the audio technician's term for noise in which each octave of random frequencies contains equal power, in contrast with 'white' noise where the power increases according to a square law for each rise in octave), and that we call this noise 'silence'. Incoming signals are alleged to mix with this and thereby become spatially identifiable.

There are two obstacles to this theory. One is that there seems to be nothing published in the medical and biological books as to the ear radiating sound — strange that such a phenomena has passed unnoticed before!

The second is that, even if true, in what way could the mixture of an internally generated signal and the external ones identify the location of the latter? Remember that with the hologram, the reference and object beams originate from the same source, and it is the displacement from the phase of the original that conveys the spatial information in the reflected one.

Mr Zuccarelli is also reported as saying that he communicates directly with the brain: "We actually record brain codes". As we shall see, spatial coding which the brain unravels as spatial information certainly does take place, but such a statement is rather misleading. It suggests

that sound and the ears are not involved at all, in which case one might expect to have electrodes implanted in the head in order to accept the recorded signals!

This mysterious non-auditory concept of the recorded signals is further heightened by Zuccarelli's reported emphatic denial that microphones are used at all in the recording process. In fact this is simply not true; two cardioid microphones with a minimum diaphragm diameter of 7 mm are employed as transducers in the recording device.

Allusions to 'encoding', the 'generator', and the comments that "if an electronics expert were to examine the latter it is unlikely he would understand it", all serve to enhance the aura of way-out complexity, and discourage too-close investigation. We are further told that Hugo would never sell the secret, and that "someone might find it in 10 or 20 years".

All highly intriguing stuff, but having blown away the chaff, let us see what remains.

Limitations Of Traditional Hearing Theory

The traditional explanation of how we distinguish the origin of sounds is that the pressure waves reach one ear slightly later than the other, thus giving rise to a phase difference. Furthermore, the amplitude is marginally greater at the nearer ear. The head casts an acoustic shadow, thus giving rise to these effects. The extent of the phase and amplitude differences depend on the sound location, allowing us to sense direction.

Zuccarelli correctly points out that this theory is inadequate to explain all the facts of spatial identification in hearing. For example, persons who are completely deaf in one ear can still identify sound-source locations, although to a limited extent. According to the theory they should have no spatial information at all.

You can check this for yourself by closing your eyes and plugging one ear, then getting someone to rattle a box of matches or some keys at various points around your head. You will find that the locations can be closely identified both laterally and vertically, especially around the hemisphere of the exposed ear.

Another fact is that two microphones placed on either side of a dummy head in the position of the ears will indeed give a spatial location to sounds coming from the front, this being the way binaural recordings are made. However, the effects are ambiguous: sounds from the rear have the same effect and there is no way they can be distinguished. Furthermore, there is no means of telling whether sources are high or low-height information is absent.

Now why should this be? We have only two auditory receptors on our heads, just like the microphones. We have no hearing organs on the top or at front or back, only at the sides. Yet these can identify sound sources in any direction, and for good measure, whether they are near or distant! How? Why?

Holophony

By asking questions such as these, Hugo Zuccarelli arrived at an explanation which seems to fit all the known facts. The spatial encoding takes place as the sound enters the ear. While the head plays a part in this, the major factor is the auricle or the external part of the ear. A pressure wave enters the ear canal directly and is conducted down to the eardrum, but a larger portion is collected by the auricle (due to its larger area) and is reflected around the whorl, to follow the direct wave slightly later. The delay is small, but it does produce a phase difference, especially at higher frequencies.

If the auricle was symmetrical, then such reflections would be similar irrespective of the direction of the wave

fronts. What is required is a reflector that is asymmetric in all directions. The human auricle fits this need perfectly, there being no two directions in which the reflective path is the same. Hence the delay and phase difference depends largely on the direction of the sound source. It is in this sense that the ear generates its own spatial code, by comparing these reflections with the direct sound originating from the same source.

Thus the similarity with holography can be more clearly appreciated and the term holophony justified.

Reflection of a sound pressure wave only occurs to any degree when the reflecting surface is a quarter-wavelength in size or larger. The spatial location facility would therefore be expected to be frequency-dependent. Frequencies above 3.4 kHz are well handled by the shortest auricle dimension, and down to 1.4 kHz by the longest. Below this, the head itself comes into play at frequencies down to 450 Hz, although with rather less precision.

It must be remembered, though, that there are few if any natural sounds that are pure fundamentals; nearly all consist of fundamental plus a varying number of harmonics. Thus a sound in the low frequency range could be spatially located by reason of its harmonics.

This is in accord with common experience; low frequency sounds with few harmonics are notoriously difficult to place. Have you ever tried to locate the source of a mains hum from several separate pieces of equipment? Or the direction of a distant explosion? Such low frequencies travel through the auditory system without modification and so without any spatial coding.

The theory also fits the phenomena of the retention of restricted locational ability with one ear only. One of the things that can be affected by hearing in mono is the facility for judging the distance of a sound. Each ear fixes the direction, and if the directions are notably different it must be because the sound source is near. Conversely a virtually similar direction means the source is distant.

All this information is fed to the brain which supplies an instantaneous fix on the location of any sound. Thus it serves as the decoder of the data encoded by the external ear and its orifice.

Recording

So now we come to the big question; how can audio signals be recorded and encoded to simulate our natural direction-finding mechanism? It doesn't take long to arrive at the conclusion that the best way is to copy nature. If an artificial head is constructed that contains an auditory system closely resembling that of the human head, but has microphones in the position of the ear drums, then the sounds picked up by them will have spatial coding just as those reaching the natural ear drums. The same phase displacements and diffractions are all present.

This is the basis of Zuccarelli's system; an artificial head called Ringo. Of course artificial heads have been used before for making realistic binaural recordings, but these have not duplicated the auditory system with any accuracy, and their main object is to simulate the acoustic shadow of the human head between the ears.

Ringo is quite different. The head is made of a plastic material such as polystyrene and rubber, and has two ears which faithfully copy the auricle of the human ear. These lead into cavities which again duplicate the ear orifice, and from there pass into the auditory canal. This is some 24 mm long, the first 8 mm of which is the same plastic material as the auricle, but the remaining 16 mm is lined with a more rigid plaster coating. This is to simulate the fibro-cartilaginous and bony portions of the human canal respectively. It is of elliptical cross-section which is twisted



Fig. 1. The received sound from a nearby source makes different angles at each ear. From a distant sound the angles are virtually the same. The brain interprets the directional differences between the ears in terms of distance.

through about a quarter turn, and has an abrupt dilation some half-way along. Thus the internal contour of the human channel is closely duplicated.

At the end of each canal is a cardioid microphone oriented in the same plane as the ear drum. Cardioid microphones are not pressure-operated but are exposed at the rear of the diaphragm, giving them the pressure-gradient or velocity mode of operation. The ear drum is also not enclosed at the rear but opens through a tube known as the Eustachian tube into the pharynx at the top of the throat. By means of this, air pressure is equalised on both sides of the ear drum.

In a similar manner, a tube runs from the back of each microphone diaphragm to a large cavity which corresponds to the human oral cavity. In this way, the acoustic properties of the Eustachian tubes and oral cavity (which influence the result although they may not be in the direct sound path) are duplicated. Microphone cables pass out through the oral orifice.

It was found in the development of the head that the identification of front and rear sounds was influenced by the presence of hair. In fact, it seems that men who are bald are less able to distinguish between certain front and rear originating sounds than those with normal hair (one wonders if a hat might improve the ability in such cases). Anyway, Ringo is also equipped with a wig, and so has all the features for accurate spatial sound identification demanded by the theory.

Reproduction

Recorded sounds are amplified in the usual way and fed to a pair headphones or loudspeakers. They are heard by listeners, but because they include the natural spatial coding, the brain interprets them as coming from some location relative to the listener corresponding to that of the original sound relative to the recording head.

So far so good, but in entering the listener's ear do not the reproduced sounds undergo a spatial coding again and so present the brain with a double coded signal? The short answer must be yes, and if the reproduced sounds were *actually* coming from various directions the brain would be much confused.

However, the *real* direction of the reproduced sounds is fixed; in the case of headphones, it is on an axis with the ear. The sounds are therefore unidirectional and no different spatial coding takes place in the ear. The recorded coding provided by the dummy head therefore takes over, and the brain responds. We can therefore regard the side position as a mean point or reference from which the apparent direction deviates according to the recorded coding.

However, as may be expected, the human auditory system consists of various air chambers producing resonances, and some frequencies are favoured at the expense of others. According to the International Standard Loudness Contours, peaks in human hearing occur at 400 Hz, 4 kHz, and 12 kHz, these being the average over a large number of subjects tested.

The dummy head also has resonances, although these are somewhat lower at 2.5 kHz and 7.5 kHz. Like the

human hearing system, the peaks are due to the fundamental and third harmonic.

If uncorrected, these peaks would appear in addition to those present in natural hearing and would result in a distorted frequency response. They play no part in the spatial coding, so can be ironed out without any detriment to the working of the system.

Correction can be done by means of acoustic boxes in the head near the microphone diaphragms, but more conveniently it is done by connecting an equaliser circuit somewhere in the recording chain.

It was also found in developing the system, that sounds coming from the front and rear differed in their frequency response from those facing the ear at the side. Front radiated sounds emphasize the high frequencies, while those from the rear accentuate the low. Furthermore, there is a displacement between the fundamental and harmonics caused by the auricle reflection, and these also differ according to the direction of propagation. All this adds to the spatial coding.

Earlier the point was made that holophonic recordings need no decoder other than the brain, and so can be played on any domestic playing equipment, disc or tape. This is true but there is one proviso: hi-fi speakers having two or more units fed by a crossover network may not be suitable. The reason is that these often introduce phase anomalies. Since it is the subtle phase differences that constitute the spatial codification, any other introduced by the speakers (or amplifiers, for that matter) would disrupt the code.

The best type of loudspeaker for holophonic material is a single wide-range driver. Alternatively a multi-driver speaker may be used providing it has been designed to give zero phase shift between the drivers. Some have been produced with this characteristic.

Future Prospects

As prospective users do not have to equip themselves with special players or decoders, and the results are so startlingly better than conventional stereo or quad, the future of holophony would appear to be bright. As one-channel reproduction gives results almost as good as twin-channel, even cheap mono player users could benefit.

The technique could be used in broadcasting and television to considerably enhance some of the existing dreary fare. All that is required is to convince the upper echelons of the BBC and ITA of the fact. Unfortunately, the confusion and mysticism surrounding the subject won't have improved its chances there.

On the recording front things are more hopeful, with discs being made and more on the way. So far (as might be expected) the recordings are of pop, but serious music lovers may well imagine the effect with a large-scale choral work. In live broadcasts, the coughs and programme rustling come from various points behind and would be less intrusive (as at an actual performance) than they usually are when broadcast. Imagine what could be done with broadcast drama with the constraints of the small television screen replaced by a wide stage stretching all round. The possibilities for creative use are almost without limit.

Hugo Zuccarelli and his associate Mike King have formed a company, Holcphonic Zuccarelli Laos Ltd, for the exploitation of holophony. Ringo is understood to be an active partner!

Postscript

Since preparing the above article, I have had the opportunity of a conversation with Hugo Zuccarelli. He blames the confusion surrounding holophony entirely on the journalists who have reported it and describes their efforts in rather strong terms that I would prefer not to repeat. Now it is true that non-technical reporters writing for the popular press often get the wrong end of the stick when reporting on technical matters, and many use their imagination to fill in the bits they don't know. However, the extent of the misinformation in this case points to a paucity of information at the source. I found this to be true myself; in response to my request for details and specific questions about the system, I received merely a montage of photocopied press-cuttings. These just underlined the confusion of the reporters who wrote them. Accordingly I had dig elsewhere and pursue other channels for the information.

Now this may be due to inexperience in PR and disseminating accurate information to the press — a fault not unknown in more established enterprises — or it could be attributable to the aforementioned caution over giving too much away to potential competitors.

In our conversation he maintained that holophony does not consist of recorded sound, and referred to the analogy of the hologram which is not a record of a picture as such but interference patterns. True, but a hologram is a recording of *light*, although in a different pattern from a normal photograph. Similarly holophony is a recording of *sound* which can be defined as vibrations in air that produce sensations of hearing, even though these contain spatial-encoded phase delay.

If this were not so, holophonic recordings could not be reproduced directly through headphones and loudspeakers.

It seems that Mr Zuccarelli restricts his definition of sound to the original propagations from the sound source, and this could well be responsible for the confusion and some of the more fanciful descriptions.

ETI

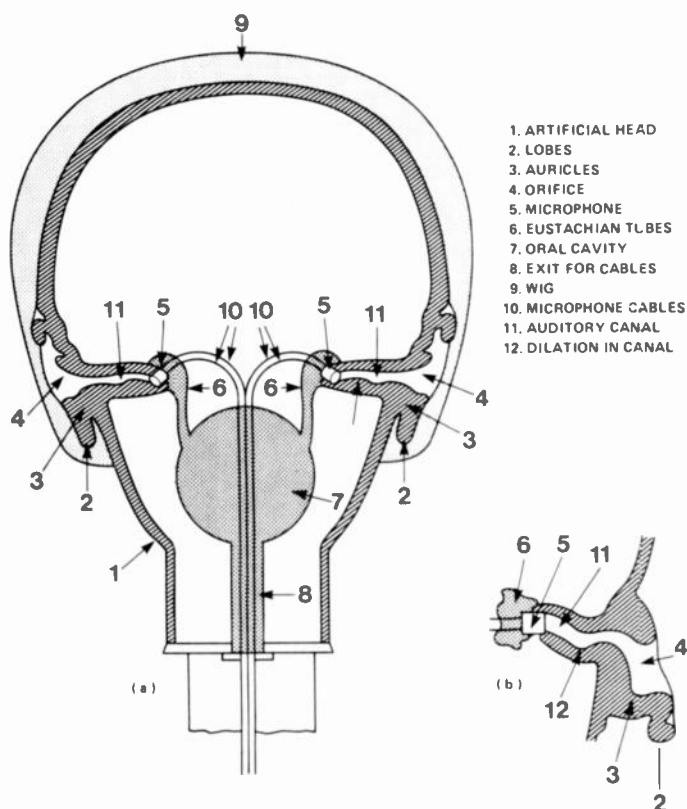


Fig. 2. The anatomy of Ringo.

All devices guaranteed Brand New and to full spec. Items ex stock despatched same day. Prices are EXCLUSIVE of VAT. Please add 60p to order to cover P&P BEFORE calculating VAT. Payment by cheque, Postal Order, Bankers Draft or Cash (PLEASE register) with order. Official orders from Govt. Depts and Educational Institutes Welcome. Trade Accounts opened subject to satisfactory status — send for details. We are pleased to receive overseas orders (please allow adequate postage — surplus refunded) which, unless accompanied by Bankers Draft in UK Currency may be subject to Bankers Commission and slight delay in despatch. Overseas trade enquiries welcome — send for full details. VAT not applicable to export orders. Price List detailing full range of components available — 30p refundable with first order. Please send SAE.

COMPARE OUR PRICES

LINEAR	CMOS	74LS	TANTALUM	1N5408
555CMOS 80	LM3909 70	ZN459 285	BEADS	ZENER DIODES
556CMOS 140	LM3911 120	ZN1034E 200	LS153 38	2V7-33V 500MW 7
709 25	LM3914 175	LOGIC ICs	LS155 29	5V1-75V 1.3W 14
741 14	LM13600 105	AY5-2376 590	LS156 39	BRIDGE RECTIFIERS
9400CJ 345	MC1496 68	MC1488 55	LS157 25	1A/100V 20
AY-3-1270 710	MC3340 120	MC1489 55	LS158 27	1A/200V 23
AY-3-8910 370	MF10CN 350	MM5303 625	LS160 30	1A/400V 25
AY-3-8912 540	ML924 195	MM5307 1250	LS161 35	1A/800V 38
CA3046 60	NE529 225	MM58174 700	LS162 35	2A/100V 36
CA3080 65	NE531 135	TMS6011 365	LS163 35	2A/200V 40
CA3089 190	NE544 180	ULN2003 75	LS164 40	2A/400V 40
CA3090AO 370	NE555 16	8T26 99	LS165 50	2A/800V 52
CA3130E 85	NE556 45	8T28 120	LS168 80	REGULATORS
CA3140E 36	NE565 110	8T95 90	LS170 70	78L05 30
CA3161E 100	NE566 140	8T97 90	LS173 47	78L12 30
CA3189 200	NE567 100	81LS95 80	LS175 36	78L15 30
CA3240E 110	NE570 370	81LS96 80	LS176 36	78L24 30
ICL7106 680	NE571 370	81LS97 80	LS181 87	78T05 36
ICL7611 95	RC4136 55	81LS98 85	LS183 105	78T12 36
ICL7621 180	RC4558 45	6522 310	LS190 35	78T15 36
ICL7622 180	SL490 250	6532 675	LS191 35	79L12 60
ICL8038 290	SL76477 380	6821 110	LS192 35	79L15 60
ICL8211A 150	SP8629 250	6845 650	LS193 36	79T05 42
ICM7224 775	TBA120S 70	6847 650	LS194 32	79T12 42
ICM7555 80	TBA800 75	6850 110	LS195 32	79T15 42
LF353 85	TBA810 95	6852 250	LS196 43	79T24 42
LF356 90	TBA820 70	6855 485	LS197 45	LM309K 130
LM10 325	TBA950 220	8155 350	LS200 50	LM317K 270
LM301A 24	TDA1008 310	8212 110	LS201 55	LM317T 120
LM311 70	TDA1022 480	8216 100	LS202 55	LM323K 350
LM318 120	TDA1024 115	8224 110	LS203 55	LM723 35
LM324 30	TL061 40	8226 220	LS204 55	Carbon Film, High Stab 5%
LM334Z 95	TL062 60	8228 220	LS205 55	1/4W 10Ω-1M
LM335Z 120	TL064 95	8243 270	LS206 55	1/4W 10Ω-10M
LM339 45	TL071 25	8250 865	LS207 55	2% Met. Film E24
LM348 60	TL072 45	8251 265	LS208 55	1% Met. Film E24
LM358 55	TL074 95	8253 400	LS209 55	
LM377 165	TL081 24	8255 225	LS210 55	
LM380 65	TL082 45	8257 400	LS211 55	
LM381 120	TL084 90	8259 395	LS212 55	
LM382 110	TL170 49	8279 385	LS213 55	
LM384 130	UA2240 115	8832 250	LS214 55	
LM386 65	ULN2003 75	9602 220	LS215 55	
LM387 120	ULN2004 75	Z80ACTC 260	LS216 55	
LM393 95	XR2206 295	Z80ADART 260	LS217 55	
LM711 60	ZN414 79	Z80ADMA 975	LS218 55	
LM725 325	ZN423 130	Z80AP10 270	LS219 55	
LM733 69	ZN424 130	ZN425E8 320	LS220 55	
LM747 60	ZN425E 340	ZN426E8 320	LS221 55	
LM1458 40	ZN426E 290	ZN427E8 575	LS222 55	
LM2917 185	ZN427E 575	ZN428E8 395	LS223 55	
LM3900 45	ZN428E 395		LS224 55	

COMMQUIP LTD.

HAMILTON HOUSE 11 WALKERN ROAD
STEVENAGE HERTS SG1 3QD
Telephone (0438) 729771 Telex 825378 G



Bigger and Better

the colourful Wilmslow Audio brochure
— the definitive loudspeaker catalogue!

Everything for the speaker constructor — kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue
(cheque, M.O. or stamps — or phone with your credit card number)

- ★ Access — Visa — American Express accepted ★
also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
£1.00 per hundred mixed (Min 10 per value)
£8.50 per thousand mixed (Min 50 per value)

Special stock pack 60 values. 10 off each £5.50

DIODES: 1N4148 3p each Min order quantity 15 items
£1.60 per hundred

CAPACITORS, REGULATORS, SWITCHES, I.C. TRANSISTORS, DIODES, etc., etc.
FULL LIST AVAILABLE — SEND S.A.E.

DIL SOCKETS: High quality, low profile sockets
8 pin — 10p. 14 pin — 11p. 16 pin — 12p. 18 pin — 19p. 20 pin — 21p.
22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 4 pin — 42p.


ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER — UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE



Visual Display Units
Burroughs MT686 VDUs
These versatile micro controlled programmable terminals have 3 RCA 1802 CPUs and 64K of memory. 12" Green screen (80 x 25) RS232. 106 key detached keyboard. Can also be used as quality video monitor. £149 + £15 carr. WHILE STOCKS LAST.

CENTRONICS 306 LINE PRINTERS

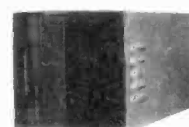professional fast compact line-printer. 80 columns, 120 char/sec. Parallel i/f. Quality at a silly price. Vertical format unit. To inc. operations manual. ONLY £149.00. Carriage (England) £17.50. Tech manual (230 pages) £10.00.



FLOPPY DISC DRIVES

Fantastic MEMOREX 550 8" discs mounted in attractive case with power supply and fan. Shugart standard 50 way interface. Space for second drive. £199 (carr. £9.50).

MAWSON ASSOCIATES

124 Lennard Rd, Beckenham, Kent BR3 1QP

WE ALSO BUY COMPUTERS AND COMPUTER PERIPHERALS

01-778 3600

Callers welcome by appointment
£/h items sold working but not g'teed

READ/WRITE

Letters for this page should be addressed to Read/Write at our Charing Cross Road address.

Dear Sir

I was most disappointed to see your article on FEVAs or Valves, in the April edition of ETI. I see enough stupidity in the world without reading it in electronics magazines.

I can do without that sort of rubbish. You have just lost one regular customer.

Yours sincerely,
K. J. Sparkes, BSc, AIEE,
ARCS,
Hemel Hempstead.

Dear ETI

Any prizes for spotting the April fool? Mind, the FEVAs nearly had me fooled — I read half the article like a lamb — then it clicked!

Nice try — ETI!
Margaret Hibbert,
Pontypridd.

Dear Sir

Please find enclosed a photo of a FEVA in my possession. It was found that Bakelite did not like high temperatures, and the pins were a little weak. An Edison screw was much more robust, and, as you can see, it is the No. 6 Valve.

*This one is brand new; the heater is low voltage for safety and runs very bright. Ideal for reading ETI by.
Name and address supplied.*

You can please some of the people some of the time

Dear ETI

Your RAM has had a power failure. Gareth Lee (Read/Write October 1982) wrote asking you about expander/compressor noise reduction circuits and you FORGOT even to MENTION your own — November 1977 —

"COMPANDER" based on the NE571. I built one and it did have some unsatisfactory features: the record/play switch and compression ratio switch introduced noise and made tape monitoring impossible, but a Mark II version using one NE570 per channel and based on the "100 Circuits" design works well and produces a major noise reduction. Mark III — using 4066s to control expansion/compression ratio — is now on the breadboard.

Howard B Broughton
Putney, London

We look forward to receiving a Tech Tip from Howard!

Dear Sir

I read with interest your article in the April 1983 ETI, using our MM58174AN (the Real Time Clock — Ed.) Unfortunately, the design breaks many of the design rules for using the part.

1. The diode derived supply will be typically 4.3 volts normally, well out of spec. This will cause read errors. It may also cause latch up if any pin is driven above 4.3 volts. This is usually destructive.

2. The write protect switch SW1 is a good idea, but will not prevent IC6 and IC5c producing glitches on power up/down, causing erroneous data to be written into the MM58174AN. This is a common but serious design fault, and typically stops the clock or corrupts data during power down.

3. Most 6502 based systems demand memory and peripherals with an access time of less than 1 microsecond. The MM58174AN does not meet this requirement, having an access time of 1.2 microseconds at 5 volts and 25 deg C. At 4.5 volts and 70 deg C, this increases to 1.9 microseconds. Clearly wait states must be introduced.

Typically some registers will be read correctly and others will not if this important parameter is ignored.

4. I commend your designer for fitting C5, many people fail to realise its importance. Ideally it should be 12 or 15 pF, but 10 pF will probably be OK.

5. You correctly state the importance of reading all required registers of the MM58174AN in 100 mS, which is tricky in BASIC, but make no mention of servicing the Interrupt, which is somewhat involved.

6. The PCB track to pin 15 (clock in) should be moved further away from the track to pin 12 (AD0), or noise may be coupled in causing the clock to run fast.

Quirky behaviour may be tolerable in some home constructed equipment, but I honestly believe that your readers will demand utter reliability from a real time clock if it is to have any practical value.

My fear is that many of your readers will waste their time building a real time clock card that doesn't work very well. They will probably blame the component and waste the manufacturer's time, craving advice and assistance. They will probably also



waste much of your time, by phoning and writing to ETI.

Sorry to sound super critical, but I have spent three years helping and persuading people to use the MM58174AN properly, and I think you have undone it all!

Yours sincerely

D.E.Brown,

Applications Manager,

National Semiconductor (UK) Ltd.

The author replies:

Taking National Semiconductor's points in order:

1. If a supply voltage of 4V3 is "well out of spec", then the data sheets contain wrong information. I have both an N.S. and an R.S. data sheet for the device, both of which quote a minimum supply voltage of 4V0.
2. Whereas in theory I accept that powering up/down could cause glitches on CS and NWDS hence corrupting data, I haven't found in practice that this happens. If the device is prone to this sort of problem, it is unfortunate that it is not mentioned in the data sheet which in actual fact suggests the contrary. The N.S. data sheet describes a typical microprocessor application in which the

circuit diagram includes a battery back up and is therefore intended for uses in which it will be powered up and down without resetting the MM58174AN.

This circuit contains no write protection facility at all, CS and NWDS being connected directly to the bus.

3. I was concerned whilst designing the RTC board that the access time on the MM58174AN was rather long for the 6502 processor. However, since an alternative method of interfacing would have greatly increased the complexity of the board, I was tempted to experiment with the configuration actually used. The circuit proved to be successful in practice and my choice of this configuration was confirmed when I encountered a similar circuit in another magazine (Shame! — Ed). I have more recently spoken to the author of this article who informed me that the circuit was closely based on applications information supplied by R.S. Components and that the circuit has also been manufactured on a commercial basis with no problems.
4. No comments.
5. I would imagine that no more than 5% of readers building this board would wish to use it in the interrupt mode. It was therefore my intention to make

mention of the fact that the board could also be used to generate interrupts without using a lot of space to describe something that would be of interest to a small minority. Obviously any reader intending to use interrupts may obtain all the relevant information from the data sheet.

6. I have noticed that the RTC does in fact run slightly fast. I had originally explained this as being due to the tolerance of the crystal, as the inaccuracy is no greater than that which I experience with my digital wrist watch which presumably uses a similar chip and crystal. I would imagine that the comment made by N.S. is a more likely explanation. It is a pity that if the circuit board geometry is so critical to the correct operation of this device that no mention of this requirement is made in the data sheet.

To summarise, I think that the following two points sum up my thoughts:

- A. The board does in fact work.
- B. All but one of the points above could not have been discovered by reading the data sheet. Perhaps there is a need here for a more accurate and more detailed data sheet.

Mike Bedford

ETI

THE VICTORY ORGAN

- * Exciting range of authentic voices
- * Preset sounds—Piano, Harpsichord, Hawaiian Guitar (with glide), Banjo (with repeat), Accordion
- * 16 modern rhythms with superb sounds including handclap
- * Full range of 'Easi-Play' features * Custom Programmed ROM
- * Walking Bass on Lower Manual and Pedals
- * Real wood veneer cabinet with American walnut finish
- * The only organ with update facilities for synthesizer and "add-a-chord" unit
- * Starter kit from £98.80 + VAT
- * Full kit £280.54 + VAT Carriage extra on kits



Send for a demonstration tape today only £1.95 inclusive. Hear the difference yourself.

Full details & specification on request

LEIGHTON ELECTRONIC SERVICES

17 BRIDGE STREET, LEIGHTON BUZZARD, BEDFORDSHIRE LU7 7AH

TELEPHONE (0525) 382504

POWER SUPPLY PART 2

Before powering up the complete supply it is better to check each of the control circuit functions separately. The first check should be the auxiliary power supply for the control IC. Connect an isolated 12 V power supply to V_A and check that the current is not greater than 200 mA. Verify that the collector waveforms of Q3, Q4 and the waveform at the gate of each HexFET is as shown in the photographs at the end of last month's article.

The next task is to set up the dead time. With a dual trace scope connected to pins 11 and 14 of IC1, adjust the preset PR3 so that the dead time measures 1.5 microseconds.

To set up the current limit circuit, disconnect R15 and apply a voltage of 550 mV in its place. With the scope connected to pin 11 of IC1, adjust

preset PR1 until the waveform disappears. The current limit is now set for about 5.5 amps.

To adjust the stabilisation circuitry, connect an auxiliary adjustable power supply across the output terminals (making sure you follow the polarity), and slowly increase the voltage from zero to 12 V. With the scope still connected to pin 11 of IC1, check that the frequency of operation changes from 40 kHz to 75 kHz as the voltage passes through 5 V. This confirms that the short circuit protection is working. When the voltage reaches 12 V, adjust the preset PR2 until the waveform present at pin 11 disappears.

Now the power supply is ready to be powered up. Connect the main line to the AC input through a variac, and connect a load to the output. Slowly increase the input voltage and verify that the supply begins to operate. With a nominal 220 V AC input adjust again, if necessary, PR1 and PR2. If everything is working correctly, remove the variac and plug the supply directly into the AC mains for normal operation.

Kindly Note . . .

The text for the switched mode power supply was originally written in Italian, and some errors have occurred in the translation. Please note the following corrections to the June article:

Page 36, column 2. The sentence should read "A 400 V HexFET allows a 15% margin in voltage and gives a lower loss during the conduction time than would a device with a higher voltage rating, because of its lower 'on' resistance".

Page 37, column 1. The statement before the first equation should be "— must be chosen higher than the critical value so that current circulation will *not* be stopped".

Page 37, column 2. The first paragraph should read "— the zener diodes ZD5 and ZD6 are connected in parallel with the transistors on the primaries of the transformers".

Page 37, column 3. The first paragraph should read "The width of this dead time is controlled by the value of the timing capacitor CT . . ."

Page 38, column 2. The figure referred to under DC Output Stabilisation should be Fig. 6, not Fig. 5.

In the specification, the sixth line is "100 Hz ripple", not "100 kHz ripple".

Additionally, not that the control circuit is 'grounded' to the positive rail

of the output, providing a -12 V supply rather than a +12 V supply. Also, the first photo was printed upside down.

PARTS LIST

Resistors (all $\frac{1}{4}W$, 5% except where stated)

R1,2	390k
R3,4,15	27R
R5,6	270R
R7,8	1k0
R9-12	430R
R13	2k2 3W
R14	0R1 3W
R16	2k2
R17	1M0
R18	10k
R19	12k
R20	1k5
R21	5k6
R22,25	510k
R23,24	5k1
R26	51k
R27,28	2k49 $\frac{1}{2}W$ metal oxide

Potentiometers

PR1	200R multiturn cermet
PR2	2k0 multiturn cermet
PR3	5k0 multiturn cermet

Capacitors

C1,2	10nF 630 V polyester
C3,4	220uF 250 V aluminium electrolytic (switching)
C5	2u2 63 V polycarbonate
C6,7	560pF 630 V ceramic
C8,14,16	1u0 polycarbonate
C9	470pF 630 V ceramic
C10	4n7 1000 V ceramic
C11	4u7 50 V polycarbonate
C12,19	1000uF 25 V aluminium electrolytic (switching)
C13	4n7 ceramic
C15	33uF 10 V tantalum
C17	100nF polycarbonate
C18	2n21 $\frac{1}{2}W$ polycarbonate

Semiconductors

IC1	SG3524
Q1,2	IRF720
Q3,4	BSX32
Q5	2N3502
Q6	2N1613
D1-4	1N5408
D5,6	1N3981
D7-9	BAV20
ZD1,4	15 V, 1W zener
ZD5,6	33 V, 1W zener
ZD7	10 V, 400 mW zener
ZD8	2V7, 400 mW zener

Miscellaneous

TH1	15R NTC thermistor
L1 (see Table); T1-3 (see Table); PCB (see Buylines); heatsinks for Q1,2 and rectifier diodes.	

TABLE 1

Output Inductor L1: Siemens pot cores 30 x 19 AL400, with 20 turns of 1.4 mm diameter enamelled copper wire in three layers (7 turns per layer). $L = 160 \mu H \pm 5\%$.

Power Transformer T1: Siemens pot cores 30 x 19 AL10500; Primary P1, 24 turns of 0.355 mm diameter enamelled copper wire in one layer;

Secondaries S1, S2, 6 + 6 turns of 0.95 mm diameter enamelled copper wire wound bifilar in one layer; Primary P2, 24 turns of 0.355 mm diameter enamelled copper wire in one layer; insulation suitable for 220 V should be wound between each primary and secondary layer; primaries and secondaries should be wound in the order listed.

Drive Transformers T2,3: Siemens pot cores 14 x 8 AL3300-5500; Primary is 60 turns of 0.2 mm enamelled copper wire; Secondary is 60 turns of 0.2 mm enamelled copper wire. Insulation suitable for 220 V should be wound between the primary and secondary layers.

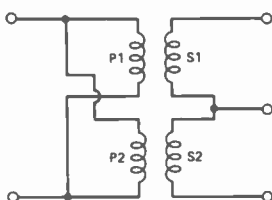


Fig. 1 How to connect the windings of T1.

BUYLINES

A complete kit of components for this project can be obtained from Electrovalue, 28E St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. The price is £51 plus VAT and does not include the double-sided, plated-through hole board which is available from our PCB Service for £14 plus postage and packing (see the ad on page 91).

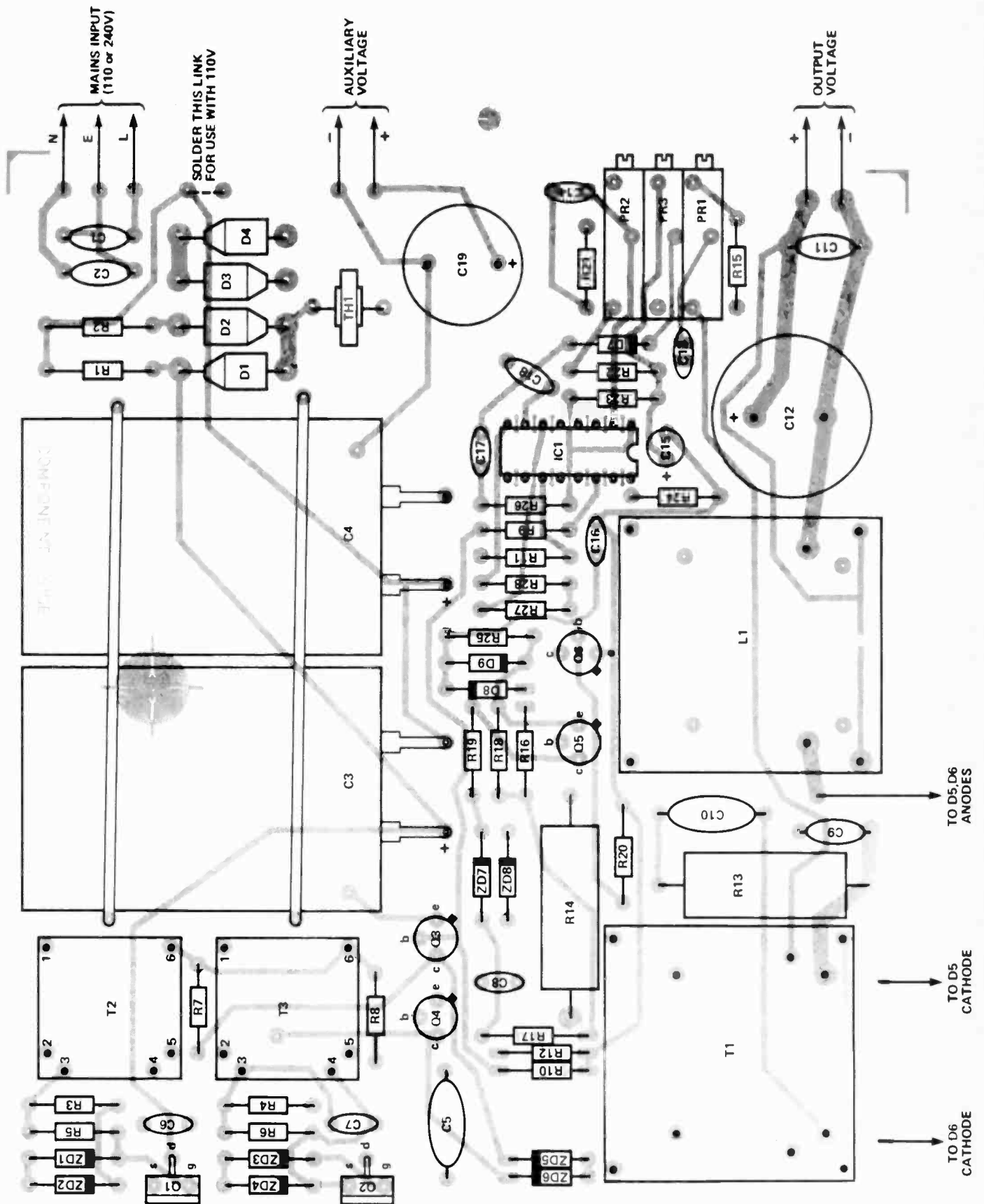


Fig. 2 Component overlay for the switched mode power supply. D5 and D6 are mounted off-board on a heatsink.

TALK TO THE WHOLE WORLD

Study now for the RADIO AMATEUR'S EXAMINATION

We have had 40 years successful experience
in training men and women for the
G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:—

British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

ETI/7/817 BLOCK CAPS PLEASE

Interak 1

THERE'S NO LIMIT TO WHAT A COMPUTER WITH NO CARDS CAN DO!

It's the oldest trick in the book to grab your attention with a stupid title, but in this case there's a grain of truth in the statement above.

The Interak 1 Computer System is a 4 MHz Z80A development system, one which you build yourself, perhaps for enthusiastic home use, or more often for industrial or educational purposes.

The fundamental structure is a 3U 19" rack which has space for 13 cards ("international" size, i.e. 4.5" x 8") on 1" pitch, with space for a power supply at one end of the rack. International size — rack mounting. Inter-rack Interak! 13 cards 4.5" by 8" gives a total potential board area of over 400 square inches, enough for a couple of hundred chips or more; there's no real limit on what that could do is there? (It would leave a few of today's marvels a bit in the shade eh?)

But don't be scared, you don't have to build a Frankenstein's monster until you're ready. The first few cards are pretty straightforward: First the VDU-K, which can be connected to your own TV (or monitor), then the Z80A-CPU card, the brains, then dynamic RAM, and finally the Keyboard inter face (to any standard parallel ASCII keyboard), and you've got a computer — with the ultimate resource: 9 empty slots for the future. (Perhaps use one of them for a 2400 baud tape interface or later floppy disks.)

Example prices (excluding VAT), everything is available separately and full after sales service in case you make a mistake: Z80A CPU card £10.95, Manual £1.50, Main Parts £13.41.

40 type-written pages of description, specification, price lists etc. are yours for the asking (a 25p stamp and/or SAE is a help, but not essential), or telephone if you prefer. You'll have to live with your computer for a long time, so make the effort and find out all about Interak now, a couple of minutes is all it takes to ask for a leaflet!

Greenbank

Greenbank Electronics (Dept. T7E), 92 New Chester Road,
New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391 (Dept T5E)

ALARMS



FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES
PHONE OR WRITE FOR YOUR COPY


051-523 8440

AD ELECTRONICS

217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



CALLING ALL THEATRE GROUPS & BANDS

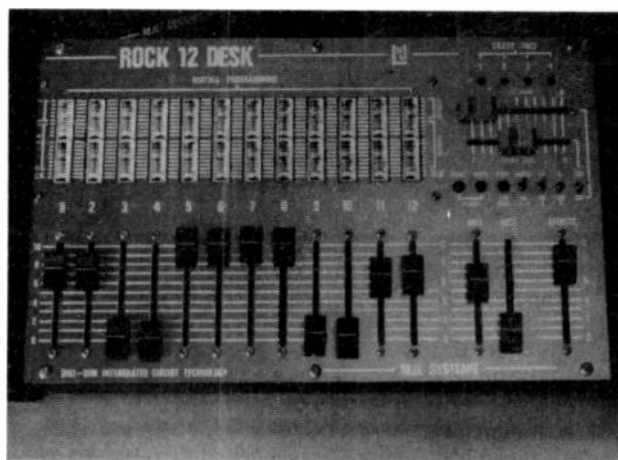

MJL manufacture a range of lighting desks and power packs for the entertainment industry, and whether your pro or amateur, you will find our prices attractive. It makes no sense to hire when you can own your own equipment, so why not drop us a line:

The Sales Manager
MJL Systems Ltd.
(power division)
45 Wortley Road, W. Croydon
Surrey CR0 3EB
or Phone 01-689 4138

MULTIMETERS

(UK C/P 65p)

RANGE DOUBLER 10A DC1
Special price.....£15.95

ETC 5000/5001 121 Ranges

50K/V Range Doubler 10A DC
.....£16.50

TMK 500 23 Ranges 30K/V 12A
DC Plus cont. buzzer.....£23.95

NH56R 20K/V 22 Range Pocket
.....£10.95

360TR 23 Range 100K/V. Large
scale 10A AC/DC plus Hfe.....£36.95

AT1 020 18 Range 20K/V. DeLux
plus Hfe Tester.....£17.50

ST303TR 21 Range 20K/V plus Hfe
Tester.....£16.95

SPEAKERS

(Hi-Fi, P.A., Disco, Bass Guitar)

12" 50W£14.95

12" 100W£19.95

15" 100W£29.95

18" 100W£39.95

Postage and Packaging £3

RETAIL • MAIL ORDER

EXPORT • INDUSTRIAL

EDUCATIONAL

Order by Post
with cheques.
Access Visa or
you can
telephone your
orders.

ALL PRICES

INCLUDE

VAT

FREE
CATALOGUE
SEND LARGE
SAE
(UK 20p)

MUSICRAFT 303 EDGWARE RD, LONDON W.2. TEL: 01-402 9729/2898

WHY WRITE TO LONDON

When you can walk to the Midlands largest
selection of DIY.

Plugs, sockets, connectors, cable, flex, leads,
boxes, Aerials, styli, components, elements,
semi-conductors, meters.

In fact the lot!

Spares and repairs for all electronic, electrical
and audio.

H. G. Electronics Co.

1350 Stratford Road, Hall Green,
Birmingham B28 9EH

Telephone: 021-777 2369



SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;

- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);

- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;

- **We will not reply to queries that are not accompanied by an SAE (or international reply coupon). We are not able to answer enquiries over the telephone.** We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.

- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:

UK: £13.15
Overseas: £16.95 Surface Mail
£36.95 Air Mail

Send your order and money to: ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Below we list the backnumbers that are available from our backnumbers department. Please note that this list will be out of date if you use an old copy of the magazine. Backnumbers cost £1.50 (UK or overseas by surface mail) and are available from: ETI Backnumbers Department, 513 London Road, Thornton Heath, Surrey CR4 6AR (cheques should be made payable to ASP Ltd).

Even if the copy of ETI you need is not listed, all may not be lost, because we run a photocopying service. For £1.50 (UK and overseas) we will photocopy an entire article (note that parts of a series of articles count as separate articles). Your request should clearly state what article you require and the month and year in which it appeared (the

index for 1980 and 1981 was published in January 1982, and the index for 1982 appeared in December 1982). Send your request to ETI Photocopies, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE (cheques should be made out to ASP Ltd).

November 78
November 79
April 80
September 80
October 80
November 80
December 80
January 81
February 81
March 81
April 81
May 81
June 81
November 81
December 81
March 82
May 82
June 82
July 82
August 82
September 82
October 82
December 82
February 83

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details.

We don't bother with the bureaucracy for Tech Tips — all you do is to send in your idea, stating clearly if you want an acknowledgement of receipt. If possible, please *type* your explanation of why the circuit is different, what it does and how it works, on a separate sheet from the circuit diagram; both sheets should carry your name, address and the circuit title. Unused Tech Tips will be returned.

OOPS!

We have in the past published small corrections to projects on the letters page, and major corrections separately. From now on corrections will appear on this page, and will be repeated for several months (just to increase our embarrassment). If a correction is too large to fit on here, we will publish it just once, but will note the fact that a correction does exist, and that copies of it can be obtained from us provided you send in an SAE.

Subscription Order Form

To: ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey, CR4 6AR, England.

Please commence my subscription to Electronics Today International. I enclose a cheque*/Postal Order*/International Money Order* for the appropriate fee*, made out to ASP Ltd.

Please debit my Access*/Barclaycard* account number*

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signature
(* delete as appropriate)

Please indicate subscription required and fee enclosed

UK & Rep of Ireland: UK £13.15 ☐

Overseas surface mail: £16.95 ☐

Overseas air mail: £36.95 ☐

Until further notice, each subscription includes a free binder (normal price £4.25)

PLEASE COMPLETE YOUR NAME AND ADDRESS IN BLOCK CAPITALS

Name

Address

PLEASE INCLUDE POSTAL CODE AS APPROPRIATE

Date of order.....
THIS COUPON IS VALID UNTIL: 31st AUGUST 1983.

Backnumber Order Form

To: ETI Backnumbers Department, 513 London Road, Thornton Heath, Surrey CR4 6AR, England.

Please supply me with the following backnumber(s) of ETI

Month Year

Month Year

Month Year

I enclose cheque*/Postal Order*/International Money Order* to the value of £1.50 per magazine ordered, made out to ASP Ltd (* delete as appropriate).

Total money enclosed £.....
PLEASE COMPLETE YOUR NAME AND ADDRESS IN BLOCK CAPITALS

Name

Address

PLEASE INCLUDE POSTAL CODE AS APPROPRIATE

Date of order.....
Note that the cost is the same for orders from overseas as for UK orders; overseas orders will be sent by surface mail.
PLEASE CHECK THAT THE BACKNUMBER YOU REQUIRE IS AVAILABLE BEFORE ORDERING.

THIS COUPON IS VALID UNTIL: 31st AUGUST 1983.

Binder Order Form

To: ETI Binders, 513 London Road, Thornton Heath, Surrey CR4 6AR, England.

Please send me.....binder(s) for ETI. I enclose a cheque*/Postal Order*/International Money Order* to the value of £4.25 per binder required, made out to ASP Ltd (* please delete as appropriate).

Total money enclosed £.....
PLEASE COMPLETE YOUR NAME AND ADDRESS IN BLOCK CAPITALS

Name

Address

PLEASE INCLUDE POSTAL CODE AS APPROPRIATE

Date of order.....
Note that binders cost the same for UK and overseas; overseas orders will be sent by surface mail.

THIS COUPON IS VALID UNTIL: 31st AUGUST 1983.

Photocopy Order Form

To: ETI Photocopies Department, 145 Charing Cross Road, London WC2H 0EE, England.

Please supply me with the following photocopies:

Month.....Year Article

.....Page No.....

Month.....Year Article

.....Page No.....

I enclose cheque*/Postal Order*/International Money Order to the value of £1.50 per photocopy ordered, made out to ASP Ltd (* delete as appropriate).

Total money enclosed £.....
PLEASE COMPLETE YOUR NAME AND ADDRESS IN BLOCK CAPITALS

Name


Address

PLEASE INCLUDE POSTAL CODE AS APPROPRIATE

Date of order.....
Note that the cost is the same for overseas orders as for UK orders; overseas orders will be sent by surface mail.
PLEASE REMEMBER TO INCLUDE MONTH AND YEAR WHEN ORDERING.

THIS COUPON IS VALID UNTIL: 31st AUGUST 1983.

BUILD A BETTER AMPLIFIER!

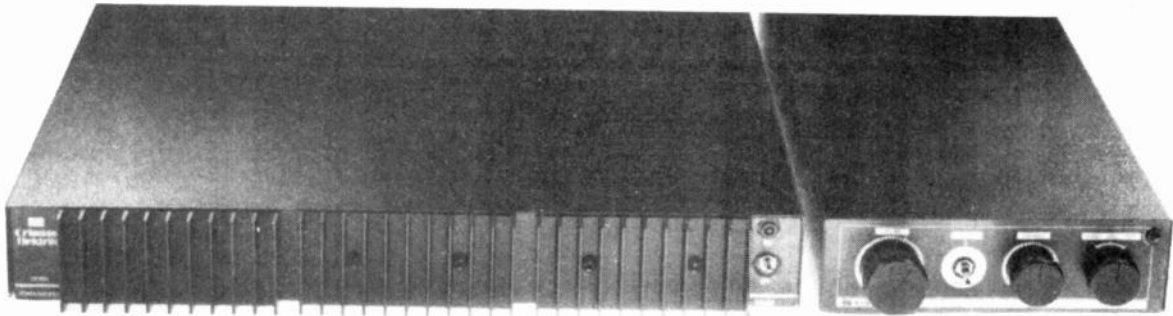

How can you own a top class HiFi amplifier, of comparable standard to Naims, Meridians, Quads etc., for an outlay of less than £250? — Simple! Build it yourself — with a Crimson kit.

It is not necessary to spend a small fortune to obtain true HiFi performance. Crimson Kits offer all the features and sound quality of the most esoteric amplifiers available and their ease of assembly ensures that they work first time and continue to do so. Not only do Crimson Kits offer outstanding value, but they also have the flexibility to adapt to any users needs. All the P.C.B.'s are ready assembled and tested (they are not "potted" as we believe disposable modules are rather extravagant!) therefore constructing a kit is pleasurable in itself and, once built, will give years of untroubled service. So, whether you use a simple record player or a compact disc, you can be sure to get the most from your system. E.T.I. said, in their review of the CK1010/1100: "I can say no more than that for £250 it is a bargain and one that will become the reference point for kit amplifiers from now on." Need we say more?

PRICES ★ Summer Special Offer: Buy a CK1010 and any CK power amplifier and get an MC2K board free!!* ★
 CK1010 — STEREO PRE-AMPLIFIER (moving magnet, tape, tuner input) takes power from any CK power amp or separate p.s.u. type P.S.K. **£92.00**
 CK1040 — STEREO POWER-AMPLIFIER 40 watts R.M.S./Chanel **£121.00**
 CK1080 — STEREO POWER-AMPLIFIER 80 watts R.M.S./Chanel **£134.00**
 CK1100 — STEREO POWER-AMPLIFIER 100 watts R.M.S./Chanel **£151.00**
 MC2K — Moving coil add on kit for CK1010 **£25.00**
 P.S.K. — power supply for CK1010 (if not used with a CK power amp) **£20.00**
 CRIMSON also supply power amp, pre amp and electronic crossover modules, power supplies and hardware — too much to list here — but on receipt of an S.A.E. we will be happy to supply full details.

TO ORDER Send C.W.O. or quote your access card no (phone orders accepted) Crimson Products are also available from Bradley Marshall Ltd, 325 Edgware Road, London.
 * Offer closes 31st July 1983 (Return this ad with your order)



CRIMSON ELEKTRIK STOKE

MANUFACTURERS OF PROFESSIONAL, DOMESTIC & INDUSTRIAL AMPLIFICATION

PHOENIX WORKS, 500 KING STREET, LONGTON, STOKE-ON-TRENT, STAFFORDSHIRE, ST2 1EZ ☎ 0782 330520

THE "INSTANT" PC BOARD



E-Z CIRCUIT "quick, easy & reliable" the best way to make one or two-of-a-kind PC boards! That's what "Doc" Savage (hobby editor, Radio Electronics magazine) says about E-Z CIRCUIT.

Why all the excitement?

Simple. E-Z CIRCUIT's exclusive 1 oz. pressure-sensitive copper tapes & patterns apply directly to the PC board, creating an actual current carrying circuit. Simply apply E-Z CIRCUIT's Copper Mounting Configurations to the board, solder your components into place, and you have a professional, production quality PC board instantly without artwork photography, screening or etching.

There's no need to worry about mistakes either. With E-Z CIRCUIT's special 2-layer adhesive, you can make corrections, modifications or improvements quickly & easily without damaging the performance or appearance of your PC board.

For building, prototyping or repairing PC boards instantly, E-Z CIRCUIT truly is the quick, easy, reliable way!

Prove it to yourself, send for your FREE copy of the E-Z CIRCUIT Copper Products Printed Circuit Technical Manual & Catalog E2-3001. See why "Doc" Savage & thousands of other users recommend E-Z CIRCUIT for instant PC boards.

Send for your FREE E-Z CIRCUIT Printed Circuit Copper Products Technical Manual & Catalog E2-3001

Engineering & Electronic Design Services Ltd.

Unit 7, Enterprise Centre, Childers Road, Limerick.
 IRELAND Tel: (061) 49366



HORIZON ELECTRONICS

(Midlands)
 Dept H/E Charlotte St. Rugby Tel: 78138
 Prime quality. TERRIFIC PRICES. Mail order only

REGULATORS (5/12/15V)			
100mA +ve	28p		
1 amp +ve	33p		
723 ver	28p		
ZENERS (3.3 to 30V)			
500mW	6p		
1.3 watt	12p		
DIODES			
IN 4001	3p		
4002	4p		
4004/6	5p		
IN 5401	12p		
5405	13p		
5406	14p		
BRIDGES			
1 amp 50v	20p		
2 amp 100v	30p		
2 amp 200v	35p		
2 amp 400v	38p		
6 amp 100v	45p		
6 amp 200v	65p		
6 amp 400v	75p		
THYRISTORS (plastic)			
4 amp 400v	35p		
8 amp 400v	60p		
TRIACS (plastic)			
24 amp 400v	50p		
8 amp 400v	60p		
TOGGLE SWITCHES			
Min. SP ST	57p		
Min. DP DT	70p		
S. Min. SP ST	48p		
S. Min. DP DT	62p		
TRANSISTORS			
BC107B	9p	TIP 31B	35p
BC108B	9p	TIP 32B	38p
BC109B	10p	BCV71	15p
BC 140	25p	BFY51	22p
BC 142	22p	BC182	7p
BC160	35p	BC212	7p
BCY70	15p	BC227	8p
BFY 50	20p	BC337	8p
BD139	32p	BD139	33p
BD149	32p	BD140	33p
LINEAR IC's			
741	50p		
748	33p		
ICM 7555	70p		
ICM 7556	130p		
LF 351	40p		
LF 353	70p		
LM 301A	24p		
LM 324	27p		
LM 380	80p		
LM 3809	80p		
NE 567v	85p		
TDA 202	180p		
TDA 2002	285p		
BOLDERING IRONS			
Antex C 15w	445p		
CK 15w	455p		
K25 25w	470p		
All bits			
LED's			
2" Red	7p		
2" Green	8p		
2" Yellow	8p		
D' (Mini) connectors			
15 way plug	80p		
Socket	120p		
Cover	90p		
25 way plug	120p		
Socket	180p		
Cover	90p		


ABOVE: Just a few examples Send S.A.E./List
 ADD 65p p&p to all orders under £5.00
 VAT add 15% VAT to total order value

SOUNDS AND MUSIC FOR ZX81 AND SPECTRUM


Music Board Project featured in ETI April/May '83
 COMPATIBLE WITH SINCLAIR 16K RAM PACK & ZX PRINTER
 On-board prom — wide range of sounds with 2 basic commands.
 Easy-to-use program to devise and use your own sound effects.
 Comprehensive music program with ordinary music notation A-G to copy or write music — over 800 three-note chords with 16K. Full piano range. Complete with detailed manual and software cassette only £24.95; built & tested £29.95; cased £39.90*.
 *State ZX81 or Spectrum — stereo or mono. Demo cassette 95p.

Pannon Electronics (Dept. ETI)
 Courtlands Road, Newton Abbot, Devon TQ12 2JA
 (0626) 62836


PCB FOIL PATTERNS

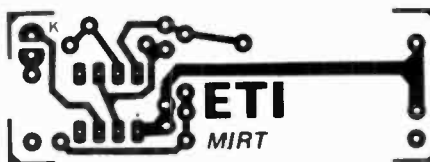


PCB for the Trigger Unit IR transmitter.

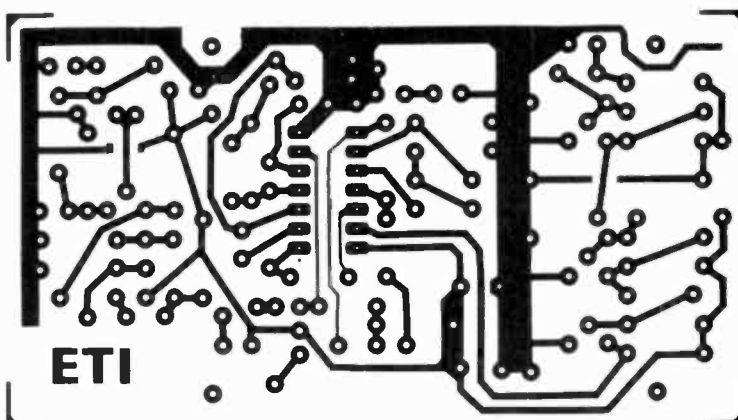

The Trigger Unit PCB.

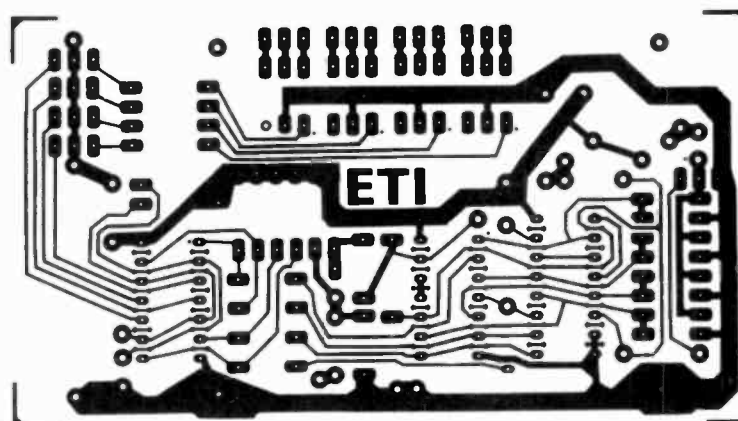

The Flash Sequencer PCB.

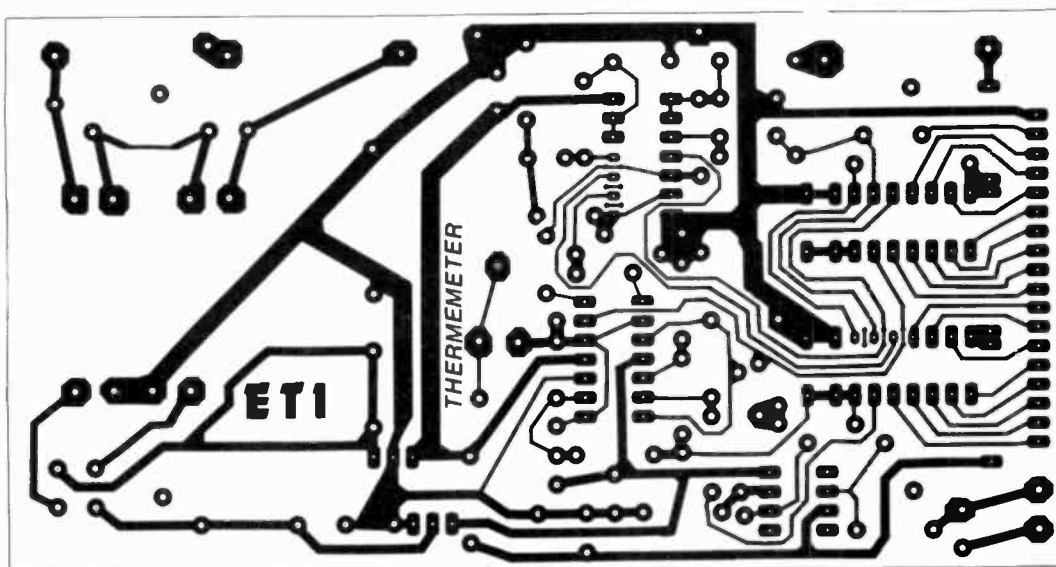

The correct version of the Thermometer (see page 29).

ETI

AITKEN BROS.

**ELECTRONIC COMPONENTS AND
TEST EQUIPMENT**
35, HIGH BRIDGE, NEWCASTLE
UPON TYNE NE1-1EW TEL: 0632 326729

MULTIMETERS

THANDAR TM351

● Bench/portable ● 3½-digit 0.5" LCD ● 0.1% basic accuracy ● 29 ranges ● Battery life typically 2000 hrs ● Complete with batteries & test leads. £113.85.
Accessories. Carrying case £6.84. Universal test lead set £12.65. Service Manual £3.00.

THANDAR TM353

● Bench/portable ● 3½-digit 0.5" LCD ● 0.25% basic accuracy ● 26 ranges ● Battery life typically 3000 hrs ● Complete with batteries & test leads £86.25. Accessories as TM351.

THANDAR TM354

● Pocket size ● 3½-digit 0.5" LCD ● 0.75% basic accuracy ● 14 ranges ● Battery life 200 hrs £45.94. Carrying case £3.45. Universal test lead set £12.65. Service Manual £3.00.

THANDAR TM451

● Bench/portable ● 4½-digit 0.4" LCD ● 0.03% basic accuracy ● Full auto-ranging or manual ● Sample hold ● Audible continuity test ● Complete with battery and leads £171.35.
AC Adaptor £7.99. Universal test leads £12.65. Service Manual £3.00.

OSCILLOSCOPE

THANDAR SC110A

● Bench/portable ● Low power ● 10 MHz bandwidth ● 10mV sensitivity £171.35. Carrying case £6.34. AC Adaptor £7.99. Rechargeable battery pack £12.65. X1 probe £8.05. X10 probe £8.20. X1 X10 Switched probe £10.93. Sprung hook trimmer pack £2.88. Manual £3.00.

GENERATORS

THANDAR TG100 Function 1 Hz to 100 KHz £90.85

TG102 Function 0.2 Hz to 2 MHz £166.75

TG105 Pulse 5 Hz to 5 MHz £97.75

FREQUENCY COUNTERS

THANDAR TF200 10Hz to 200 MHz

● Bench/portable ● 8-digit Liquid Crystal Display ● Frequency range 10 Hz - 200 MHz ● Resolution better than 1 ppm ● Sensitivity typically 10mVrms ● Time base accuracy 0.3 ppm ● Battery life 200 hours ● Frequency, time average period, totalize & reset, 2 ranges, 5 gate times; external clock facility ● Complete with batteries. £166.75.

THANDAR TFO40 10 Hz to 40 MHz

● Bench/portable ● 8-digit Liquid Crystal Display ● Frequency range 10 Hz - 40 MHz ● Resolution 1 Hz ● Sensitivity 40 mV rms ● Timebase accuracy 0.5 ppm ● Battery life 80 hours ● Frequency, totalize & reset: 2 gate times ● Complete with batteries. £126.50.

ACCESSORIES FOR TF200 & TFO40 AC

adaptor £7.99, Carrying case £6.48, X1 Probe £8.05, X10 Probe £9.20, Service manual £3.00. TP600 prescaler £51.75. TP1000 prescaler £74.75.


THANDAR PFM200A 20 Hz to 200 MHz

● Pocket size ● 8-digit LED display ● Frequency range 20 Hz - 200 MHz ● Resolution 0.1 Hz. Sensitivity typically 10 mV rms. Timebase accuracy 2 ppm ● Battery life 10 hours ● Frequency, 2 ranges, 4 gate times ● BNC input sockets £77.62. Accessories. Carrying case £3.45. AC adaptor £7.99, X1 probe £8.05, X10 probe £9.20, Service Manual £3.00.

Full spec available on all instruments, just phone or write:

Schools, colleges, universities supplied on official orders.

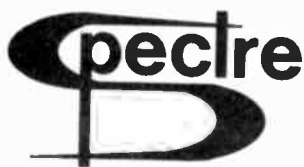Prices include VAT. Please add £1.00 postage to orders under £20.00.



48 K SPECTRUM

ELECTRONICS

£6.95

Ever built a digital electronic circuit that didn't work? Now you can draw your circuits on the T.V. screen using standard symbols. (57 defined graphics are used). Wires may be interconnected or crossed and individual components may be rotated as required. Addition of earth and power symbols allows the computer to activate your circuit to display voltage levels throughout. Design may be activated, modified, re-activated, printed or saved on tape.

NUMERIC

£6.95

Solves any equation with single unknown and/or plots its graph. This may be rotated through 90 degrees and the axes subsequently varied to suit. Solves right-angle triangles, simultaneous and quadratic equations. Produces standard deviation, arithmetic mean and coefficient of correlation of lists plus deviation curves. All displays can be sent to the printer.

SHARES

£6.95

Stores daily prices of up to 20 shares/investments for a year. Displays graphs of performance over last year, 200 days or 12 days plus written data such as holdings, original and latest prices, percentage variation and equivalent annual variation. Holdings can be manipulated, bought and sold at will.

NUTRION

£6.95

Far more than a diet book. Builds up a profile based on your physique and lifestyle then monitors your food intake. It will advise, not only on calorie intake and ideal weight, but your personal requirements and any tendency to become deficient in vitamins, minerals etc. Offers advice on foods to correct the balance. Detailed information on all foods held in memory can be accessed at will. Operates in metric and Imperial units.

These programs are exceptionally user friendly and have all been written in consultation with professionals in their respective fields. They all have comprehensive written instructions and are fully guaranteed. Dealer enquiries welcomed.

Please make cheques payable to SPECTRE.


2 MULL CLOSE, OAKLEY, BASINGSTOKE, HANTS.

PROBABLY THE MOST INEXPENSIVE QUALITY SIGNAL GENERATOR AVAILABLE TODAY

Audio Range: 10 Hz-100KHz, in four switched ranges.

Distortion
Extremely low.
(.0015% typical, @ 1 KHz).

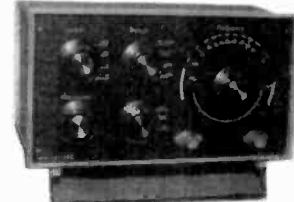Output
1v into 600Ω, with
Fixed and Variable Atten.
Sine and Square Wave.
Based on a Linsley Hood design.
Battery or Mains.



£36.00 (batty.)
Tax extra £5.40
P&P £2.00

TELERADIO ELECTRONICS

325 FORE STREET, EDMONTON, LONDON N9 0PE
01-807 3719 Closed Thursdays SAE for lists

E.T.I. KITS

Full kits inc. PCB's. Hardware. Cases, I.C. Sockets, etc (unless stated). Less batteries.
Project reprints 45p extra. Reprints supplied separately 45p each & 45p p&p

ZX ADC Jan 83	£34.88	WAH PHASE June 81. Less pedal	£14.79
DUAL LOGIC PROBE Sept 82	£14.80	LED JEWELLERY June 81. Cross	£2.88
AUTO VOLUME CONTROL Sept 82 £4.28 less case		Star £9.81 Spiral £7.88	
INSULATION TESTER May 82	£17.57	GUITAR NOTE EXPANDER April 81	£17.98
HIGH QUALITY PHONO AMPLIFIERS Feb 82.		DRUM MACHINE April 81	£85.97
Less case		ENGINEERS STETHOSCOPE Mar 81	£20.98
MOVING COIL STAGE	£19.75	SOUND PRESSURE LEVEL METER Feb 81	£243.88
MOVING MAGNET STAGE	£19.80	INFRA RED ALARM Feb 81	£38.98
PEST CONTROL Feb 82	£7.46	4 INPUT MIXER Dec 80	£21.74
GUITAR TUNER Jan 82	£21.87	MUSICAL DOORBELL Dec 80	£12.77
COMPONENT TESTER Dec 81	£3.78	METRONOME Nov 80	£5.58
CAR ALARM Nov 81	£19.77	ULTRASONIC BURGLAR ALARM Aug 80	£29.50
SOUND BENDER Oct 81	£22.84	CAPACITANCE METER Aug 80	£22.28
WATCHDOG SECURITY ALARM Aug 81	£47.88	CMOS LOGIC TESTER Aug 80	£11.98
RECHARGEABLE BATTERY extra	£19.88	CLICK ELIMINATOR April 79 £87.70 Or less case	£48.98
HANDCLAP SYNTHESIZER Aug 81	£32.98		

MAGENTA ELECTRONICS LTD
EF30, 135 Hunter St., Burton-on-Trent
Staffs., DE14 2ST. Mail Order Only
Add 45p p&p to all orders. Prices
include VAT. Access & Visa accepted by
phone or post.

Official orders welcome.
OVERSEAS:— Payment must be
in sterling. Add 10% to prices
except BFPO & Irish Republic.

ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

ALWAYS QUOTE THE PCB CODE WHEN ORDERING PLEASE

☐ 1979	☐ E/794-1 Guitar Effects Unit	2.64	☐ E/819-4 Laboratory PSU	4.53	☐ E/829-2 Dual Logic Probe	1.93
☐ E/794-2 Click Eliminator	6.64	☐ E/8110-1 Enlarger Timer	3.40	☐ E/8210-1 Message Panel (2 Boards)	10.70	
☐ E/796-1 Accented Beat Metronome	3.60	☐ E/8110-2 Sound Bender	2.65	☐ E/8211-4 Pulse Generator	5.29	
1980			☐ E/8111-1 Voice Over Unit	3.97	☐ E/8212-1 ELCB	2.41
☐ E/803-1 Signal Tracer	2.27	☐ E/8111-2 Car Alarm	2.81	☐ E/8212-2 Servo Interface (2 Boards)	5.87	
☐ E/808-1 CMOS Logic Tester	2.64	☐ E/8111-3 Phone Bell Shifter	2.96	☐ E/8212-4 Spectracolumn	4.82	
☐ E/808-3 Ultrasound Burglar Alarm .	2.87	☐ E/8112-1 Alcometer (2 boards)	5.21	1983		
☐ E/8010-1 Cassette Interface	2.93	☐ E/8112-3 Bodywork Checker	1.75	☐ E/831-1 Fuel Gauge	3.00	
☐ E/8010-2 Fuzz/Sustain Box	3.27	☐ E/8112-4 Component Tester	1.49	☐ E/831-2 ZX ADC	2.25	
☐ E/8011-5 RIAA Preamp	1.93	1982			☐ E/831-3 Programmable PSU	3.00
☐ E/8011-6 Audio Test Oscillator . . .	3.13	☐ E/821-1 Parking Timer	2.20	☐ E/833-1 Sound Board	11.16	
☐ E/8012-1 Musical Doorbell	2.80	☐ E/821-3 Guitar Tuner (2 boards)	5.55	☐ E/833-2 Alarm Module	3.15	
☐ E/8012-3 Four Input Mixer	2.64	☐ E/822-1 Ripple Monitor	1.92	☐ E/833-3 ZX81 User Graphics	0.93	
1981			☐ E/822-2 Allez Cat Pest Repeller	1.68	☐ E/833-4 Logic Probe	2.17
☐ E/811-1 LED Tacho	4.13	☐ E/822-5 Moving Magnet Stage	3.49	☐ E/834-1 Real Time Clock	7.60	
☐ E/811-2 Multi-Option Siren	3.20	☐ E/822-6 Moving Coil Stage	3.49	☐ E/834-2 Thermometer (2 Boards) . . .	8.47	
☐ E/813-1 Universal Timer	3.31	☐ E/823-4 Capacitance Meter (2 Bd) . . .	10.14	☐ E/834-4 Stage Lighting — Main	11.94	
☐ E/812-1 IR Alarm (4 boards)	6.64	☐ E/824-5 Voltage Monitor	1.86	☐ E/834-5 Stage Lighting — Display . . .	3.00	
☐ E/812-5 Pulse Generator	3.57	☐ E/825-1 DV Meg	2.72	☐ E/835-1 Compressor/Limiter	5.38	
☐ E/813-1 Engineer's Stethoscope	2.65	☐ E/825-2 Analogue PWM	3.06	☐ E/835-2 Single PSU	2.75	
☐ E/814-2 Drum Machine (2 boards) . . .	5.60	☐ E/825-3 Slot Car Controller	4.51	☐ E/835-3 Dual PSU	3.49	
☐ E/814-4 Guitar Note Expander	3.20	☐ E/826-1 Ion Generator (3 Bds)	8.00	☐ E/835-4 60 W NDFL Amp	4.70	
☐ E/816-8 Waa-Phase	1.53	☐ E/826-4 MOSFET Amp Modulæ	6.78	☐ E/835-5 Balanced Input Preamp	2.81	
☐ E/816-9 Alien Attack	3.48	☐ E/826-5 Logic Lock	3.06	☐ E/835-6 Stage Lighting — Autofade	5.38	
☐ E/817-1 System AS- Input (MM or MC) .	2.65	☐ E/826-6 Digital PWM	3.34	☐ E/835-7 Stage Lighting — Triac Board .	4.12	
☐ E/817-2 System A — Preamp	5.17	☐ E/826-7 Optical Sensor	1.74	☐ E/836-1 to 3 PseudoROM (3 Bds) . . .	3.15	
☐ E/817-3 Smart Battery Charger	1.97	☐ E/826-9 Oscilloscope (4 Boards)	11.60	☐ E/836-4 Immersible Heater	2.00	
☐ E/818-3 Hand Clap Synth	3.97	☐ E/827-7 TV Bargraph Main	4.56	☐ E/836-5 Atom Keypad	4.50	
☐ E/818-5 Watchdog Home Security (2 boards)	5.31	☐ E/827-3 TV Bargraph Channel	2.28	☐ E/837-1 Flash Sequencer	2.32	
☐ E/819-1 Mains Audio Link (3 boards) . . .	7.35	☐ E/827-4 Hotwire	2.63	☐ E/837-2 Trigger Unit Main Board	2.32	
		☐ E/827-5 Bridging Adaptor	2.38	☐ E/837-3 Trigger Unit Transmitter	1.44	
		☐ E/828-1 Playmate (3 Boards)	7.20	☐ E/837-4 Switched Mode PSU	14.00	
		☐ E/828-4 Kitchen Scales	1.84			
		☐ E/828-5 Sound Track	4.25			
		☐ E/829-1 Auto Volume Control	1.84			
				What The PCB Code Means		

What The PCB Code Means

The letter (E) signifies that the PCB is for an ETI project (as opposed to a Hobby or Ham Radio project). The first two numbers give the year in which the project was published. The next one or two numbers before the dash give the month in which the project was published; the number after the dash identifies the project within the month.

STRICTLY CASH WITH ORDER — OFFICIAL ORDERS ARE NOT ACCEPTED

Prices Quoted are valid until 1st October 1983

How to order: indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £

Add 45p p & p 0.45

Total enclosed £

**PLEASE ALLOW
28 DAYS FOR
DELIVERY**

Signed

Name

Address

CLEF ELECTRONIC MUSIC

MICROSYNTH


2½ Octave Music Synthesizer with two Oscillators, two Sub-Oct. Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth. Music & effects.

FULL KIT £137 Also available in 3 parts

PERCUSSION MICROSYNTH

Two Channel touch Sensitive unit plus variable angle L.F.O., phaser, internal and external triggering

FULL KIT £121

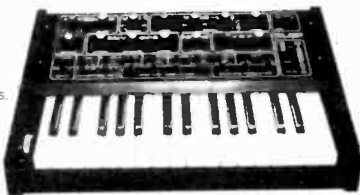

BAND-BOX PROGRAMMABLE BACKING TRIO

THREE PIECE BACKING BAND
Generates the sounds of three instrumentalists to back Soloists

DRUMS + BASS + KEYBOARDS

Over 3,000 chord changes (60 scores) on 132 different chords - extendable to 200 scores. Master Rhythm also required.

FULL KIT £235 EXTENSION £82



88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia



COMPONENT KITS

including Keyboard

88 NOTE £266

72 NOTE £234

The above may also be purchased in four parts.

DOMESTIC KITS

inc. Cabinet, P.A. & Spkr.


88 NOTE £442

72 NOTE £398

STAGE MODEL

inc. Cabinet & Stand

72 NOTE £383

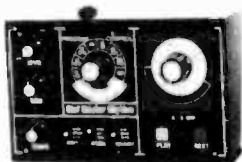

MASTER RHYTHM PROGRAMMABLE DRUMS

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.

COMPLETE KIT £79

STRING ENSEMBLE £198.50
ROTOR-CHORUS £98.00

SQUARE FRONT KEYBOARDS

88 NOTE £60 49 NOTE £29

73 NOTE £50 30 NOTE £19

KEYSWITCH ITEMS ALSO AVAILABLE

ALL PRICES INC. VAT, CARR. & TELEPHONE ADVICE
S.A.E. for full Specs & MANF. PRICES VISA-ACCESS

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept. ET1)
44A BRAMHALL LANE SOUTH BRAMHALL
STOCKPORT CHESHIRE SK7 1AH
TEL 061439 3297

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

TECHNICAL TRAINING IN ELECTRONICS, TELEVISION AND AUDIO

IN YOUR OWN HOME - AT YOUR PACE

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates

Radio Amateurs

Basic Electronic Engineering (Joint C&G/ICS)

Certificate Courses

TV and Audio Servicing
Radio & Amplifier Construction
Electronic Engineering* and Maintenance
Computer Engineering* and Programming
TV, Radio and Audio Engineering
Electrical Engineering,* Installation
and Contracting

*Quality for IET Associate Membership



Approved by CACC



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest _____

Name _____

Address _____



Post to: Dept J625
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ

01-622 9911
(All Hours)

NEW! MODULAR AUTOMATIC TELEPHONE SYSTEM

£24.50

+ £1 p&p

Each ready built module is a complete exchange providing up to ten extension lines

- ★ Simply connect 'phones and power supply
- ★ Only two wires to each telephone
- ★ Uses ordinary dial or push-button 'phones
- ★ Complete privacy for conversations
- ★ Range of several miles
- ★ Fully expandable system

Each module allows two 'phones to be used at one time, two modules allows four, etc.

RECONDITIONED TELEPHONES

Push Button Trimphones £15 + £1.80 p&p. 2 for £28 + £2.50

Push Button 746 £9.75 + £1.80. 2 for £18 + £2.50

Recent Style Dial Phones £4.75 + £1.80. 2 for £9 + £2.50. 5 for £20 + £5

Seconds (in good working order)

Class 1 £3.50 + £1.80. 5 for £15 + £5

Class 2 (discoloured) £2.25 + £1.80. 5 for £9 + £5

TEMPERATURE GAUGE 0-120 °C

Remote sensor on 38" capillary, panel mounting dial 55mm. dia. Only £2.50

16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point). Sensor on 22" capillary 2.30, including control knob

BUY ONE EACH OF ABOVE FOR £5.50

GEARED Synchronous motor, 8 r.p.m. 240V A.C. 3 Watt £2.

SOLENOID GAS VALVE, 240V A.C. 5 P.S.I. suitable for non-corrosive fluids. £2.20

UNISELECTORS. 50v. 4 Bank Homing Bank. 25 way £3.50

Desk-top Ten Way Manual Exchange (key & lamp unit) with instructions £8 + £1.80 P&P

BULGIN 3 pin free plug & panel socket. 2A 240V 50p

Send S.A.E. for free leaflet on telephone systems.

DIAL-OUT WITH YOUR COMPUTER. PCB's convert binary to dialing pulses and enable your computer to dial-out (with suitable interface). Ex-equipment. Tested. £12 with explanatory notes.



L.E.M. SERVICES
22 Emscote Road,
Warwick,
Warwickshire
Tel: 0926 490740

ADD 50p P&P
ORDERS OVER
£7.50 POST FREE
unless stated otherwise

ALL ITEMS - MONEY BACK IF NOT DELIGHTED

electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 146 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

BEGINNERS GUIDE

☐ Beginner's Guide to Basic Programming Stephenson	£5.35
☐ Beginner's Guide to Digital Electronics	£5.35
☐ Beginner's Guide to Electronics	£5.35
☐ Beginner's Guide to Integrated Circuits	£5.35
☐ Beginner's Guide to Computers	£5.35
☐ Beginner's Guide to Microprocessors	£5.35

COOKBOOKS

☐ Master IC Cookbook Hallmark	£10.15
☐ Microprocessor Cookbook M. Hordeski	£7.70
☐ IC Op Amp Cookbook Jung	£14.25
☐ PLL Synthesiser Cookbook H. Kinley	£7.70
☐ Active Filter Cookbook Lancaster	£13.40
☐ TV Typewriter Cookbook Lancaster	£11.15
☐ CMDS Cookbook Lancaster	£11.85
☐ TTL Cookbook Lancaster	£10.95
☐ Micro Cookbook Vol. 1 Lancaster	£15.30
☐ BASIC Cookbook K. Tracton	£6.00
☐ MC6809 Cookbook C. Warren	£7.25

ELECTRONICS

☐ Principles of Transistor Circuits Amos	£8.50
☐ Design of Active Filters with experiments Berlin	£11.30
☐ 49 Easy to Build Electronic Projects Brown	£6.00
☐ Electronic Devices & Circuit Theory Boylestad	£13.20
☐ How to build Electronic Kits Capel	£3.55
☐ How to Design and build electronic instrumentation Carr	£9.35
☐ Introduction to Microcomputers Dagles	£7.20
☐ Electronic Components and Systems Dennis	£15.00
☐ Principles of Electronic Instrumentation De Sa	£11.40
☐ Giant Handbook of Computer Software	£12.95
☐ Giant Handbook of Electronic Circuits	£17.35
☐ Giant Handbook of Electronic Projects	£11.75
☐ Electronic Logic Circuits Gibson	£5.35
☐ Analysis and Design of Analogue Integrated Circuits Gray	£30.25
☐ Basic Electronics Grob	£11.30
☐ Lasers - The Light Fantastic Hallmark	£7.70
☐ Introduction to Digital Electronics & Logic Joynton	£5.25
☐ Electronic Testing and Fault Diagnosis Loveday	£7.85
☐ Electronic Fault Diagnosis Loveday	£6.25
☐ Essential Electronics A-Z Guide Loveday	£7.50
☐ Microelectronics Digital & Analogue circuits and systems Millman	£12.70
☐ 103 Projects for Electronics Experimenters Minis	£8.30
☐ VLSI System Design Muroga	£34.10
☐ Power FETs and their application Oxner	£9.40
☐ Practical Solid State Circuit Design Olesky	£25.00
☐ Master Handbook of IC Circuits Powers	£12.85
☐ Electronic Drafting and Design Rashkoff	£22.15
☐ VDM - VTVM Handbook Risse	£8.50
☐ Video and Digital Electronic Displays Sherr	£28.85
☐ Understanding Electronic Components Sinclair	£7.50
☐ Electronic Fault Diagnosis Sinclair	£4.50
☐ Physics of Semiconductor Devices Sze	£17.35
☐ Digital Circuits and Microprocessors Taub	£32.00
☐ Active Filter Handbook	£7.60
☐ Designing with TTL Integrated Circuits Texas	£15.20
☐ Transistor Circuit Design Texas	£15.20
☐ Digital Systems: Principles and Applications Tocci	£12.95
☐ Master Handbook of Telephones Traister	£10.00
☐ How to build Metal/Treasure Locators Traister	£6.00
☐ 99 Fun to Make Electronic Projects Tymony	£8.50
☐ 33 Electronic Music Projects you can build Winston	£6.95

COMPUTERS & MICROCOMPUTERS

☐ BASIC Computer Games Ahl	£6.35
☐ From BASIC to PASCAL Anderson	£9.95
☐ Mastering Machine Code on your ZX81 T. Baker	£7.25
☐ UNIX - The Book Banaham	£8.75
☐ Z80 Microcomputer Handbook Barden	£10.95
☐ Microcomputer Maths Barden	£11.90
☐ Digital Computer Fundamentals Barter	£9.90
☐ Visicalc Book. APPLE Edition Bell	£15.55
☐ Visicalc Book. ATARI Edition Bell	£15.55
☐ Introduction to Microprocessors Brunner	£23.00
☐ Programming your APPLE II Computer Bryan	£9.25
☐ Microprocessor Interfacing Carr	£7.70
☐ Microcomputer Interfacing Handbook A/D & D/A Carr	£9.50
☐ Musical Applications of Microprocessors Chamberlain	£28.85
☐ 30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
☐ Microcomputers Dirksen	£9.30
☐ APPLE Personal Computer for Beginners Dunn	£9.50
☐ Microcomputers/Microcomputers - An Intro Giocone	£11.80

☐ Troubleshooting Microprocessors and Digital Logic Goodman	£9.25
☐ Getting Acquainted with your VIC 20 Hartnell	£8.50
☐ Getting Acquainted with your ZX81 Hartnell	£5.95
☐ Let your BBC Micro Teach you to program Hartnell	£7.90
☐ Programming your ZX Spectrum Hartnell	£8.50
☐ The ZX Spectrum Explored Hartnell	£6.95
☐ How to Design, Build and Program your own working Computer System Haviland	£9.30
☐ BASIC Principles and Practice of Microprocessors Heffer	£7.15
☐ Hints and Tips for the ZX81 Hewson	£5.25
☐ What to do when you get your hand on a Microcomputer Holtzman	£9.95
☐ 34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
☐ Microcomputer Builders' Bible Johnson	£12.40
☐ Digital Circuits and Microcomputers Johnson	£14.55
☐ PASCAL for Students Kemp	£7.20
☐ The C - Programming Language Kernighan	£18.20
☐ CDBOL Jackson	£9.25
☐ The ZX81 Companion Maunder	£9.50
☐ Guide to Good Programming Practice Meek	£6.40
☐ Principles of Interactive Computer Graphics Newman	£13.95
☐ Theory and Practice of Microprocessors Nicholas	£11.35
☐ Exploring the World of the Personal Computer Nilles	£12.95
☐ Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80

☐ Beginner's Guide to Microprocessors Parr	£5.35
☐ Microcomputer Based Design Peatman	£11.30
☐ Digital Hardware Design Peatman	£9.80
☐ BBC Micro Revealed Ruston	£9.45
☐ Handbook of Advanced Robotics Safford	£14.45
☐ 1001 Things to do with your own personal computer Sawusch	£8.50
☐ Easy Programming for the ZX Spectrum Stewart	£7.15
☐ Microprocessor Applications Handbook Stout	£34.40
☐ Handbook of Microprocessor Design and Applications Stout	£37.60
☐ Programming the PET/IBM West	£17.80
☐ An Introduction to Microcomputer Technology Williamson	£8.20
☐ Computer Peripherals that you can build Wolfe	£12.40
☐ Microprocessors and Microcomputers for Engineering Students and Technicians Woo and	£7.10

REFERENCE BOOKS

☐ Electronic Engineers' Handbook Fink	£56.45
☐ Electronic Designers' Handbook Giacoleto	£59.55
☐ Illustrated Dictionary of Microcomputer Technology Hordeski	£8.45
☐ Handbook for Electronic Engineering Technicians Kauffman	£27.50
☐ Handbook of Electronic Calculators Kauffman	£35.00
☐ Modern Electronic Circuit Reference Manual Marcus	£44.00
☐ International Transistor Selector Towers	£10.70
☐ International Microprocessor Selector Towers	£16.00
☐ International Digital IC Selector Towers	£10.95
☐ International Op Amp Linear IC Selector Towers	£8.50
☐ Illustrated Dictionary of Electronics Turner	£12.95

VIDEO

☐ Servicing Home Video Cassette Recorders Hobbs	£12.95
☐ Complete Handbook of Videocassette Recorders Kybett	£9.25
☐ Theory and Servicing of Videocassette Recorders McGinty	£12.95
☐ Beginner's Guide to Video Matthews	£5.35
☐ Video Recording: Theory and Practice Robinson	£14.40
☐ Video Handbook Van Wazer	£21.90
☐ Video Techniques White	£12.95

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed

Name

Address

ELECTROMART

**MONTHLY IN
ELECTRONICS TODAY —
YOUR OWN 'WHERE TO
BUY IT' GUIDE**

AVON

ANNLEY ELECTRO

190 Bedminster Down Road
Bedminster Down, Bristol
Tel: 0272 632622
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm

CHESHIRE



41 Winwick St., Warrington
Tel. 54174
Open: Mon-Fri 9.30-6
(closed Tues) Sat 9.30-5
Components, aerials & burglar alarm
specialists

DORSET

D.J. ELECTRONICS
64 Ensbury Park Road,
Bournemouth.
Tel: (0202) 515073.
Open: Mon-Sat 9am-6pm.

LANCASHIRE

ETESON ELECTRONICS
15B Lower Green,
E.E. Poulton-le-Fylde, Blackpool
Tel: (0253) 885107
Open 9.30am 12.30 1.30 5.30 Closed Wed & Sun
Electronic Component Specialists

MERSEYSIDE

MYCA ELECTRONICS

2 VICTORIA PL, SEACOMBE FERRY,
WALLASEY, L44 6NR.
Tel: 061 638 8847
Open Mon-Sat 10am-5.30pm
Mail Order price list 50p refundable

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
47 Whitechapel, Tel 051 236 5489
Liverpool 2
THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30



WYMCA Building, College St.,
St. Helens Tel. 50707
Open: Mon-Fri 9.30-5.30
(closed Thurs) Sat 9.30-5
Components, aerials & burglar alarm
specialists

W. MIDLANDS

H. G. ELECTRONICS CO

1350 Stratford Rd., Hall Green
Birmingham. Tel: 021-777 2369
Open: Mon-Sat 9-5.30 (Closed Weds)
Electrical accessories, plugs, skts, leads,
Electronic components, computers, audio,
video, tape, disco, hi-fi . . .

NORTHAMPTONSHIRE

- * A new company selling electronic components.
- * Mail order and walk-round supermarket.
- * Vast stocks and very competitive prices.

MOS High Merch. Daventry. NN11 4NQ.
Telephone 03272 5523. Telex 311245.
(Off A45 opposite John O'Gaunt.)

**FOR YOUR BUSINESS TO
BE INCLUDED, CALL
ELECTROMART ON
01-437-1002.**

S. WALES

STEVE'S ELECTRONIC SUPPLY CO. LTD.

45 Castle Arcade, Cardiff
TEL: 0222 41905
Open: Mon-Sat 9-5.30
For components to computers

WARWICKSHIRE



Charlotte St, Rugby. Tel: Rugby 78138
Open 5 Days 10-6 (closed Wed)
Wide range of components and R.S. stockists
1983 Mail Order Catalogue 75p

WORCS/W. MIDLANDS

WAVEBANDS

103 Coventry St., Kidderminster
Components, computers, car radios,
C.B.'s, amateur radio
and all electronic hobby equipment
Open: Mon-Sat 9-6, Sun 10-2
TEL: 0662 2179

YORKSHIRE



ACE MAILTRONIX LTD.
3A Commercial Street,
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)
Retail and wholesale

Please include my business details in the next available issue of **ELECTRONICS TODAY INTERNATIONAL**:

BUSINESS NAME:

ADDRESS:

TEL. NO.:

OPENING HOURS:

RETAIL ☐ WHOLESALE ☐ MAIL ORDER ☐ (Please tick)

CONTACT: (FOR OFFICE USE ONLY)



Lineage:

35p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£10.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 1002

EXT 204

Send your requirements to:

Julia Bates,

ASP Ltd.,

145 Charing Cross Road,

London WC2H 0EF

WANTED

WANTED: ELECTRONIC COMPONENTS and test equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley.

PLANS 'N DESIGN

AMAZING ELECTRONICS PLANS. Lasers, super-powered cutting rifle, pistol, light show, ultrasonic force fields, pocket defence weaponry, giant tesla, satellite TV pyrotechnics, 150 more projects. Catalogue £1 (refundable) from Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

BOOKS & PUBLICATIONS

PARAPHYSICS JOURNAL (Russian translation); psychotronics, kirlianography, heliaphonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

SOFTWARE APPLICATIONS

HIGH RESOLUTION GRAPHICS For Sinclair ZX81 1K without hardware! Tape and instructions only £3.99. P. Moody, 1, Benson Street, Camberley CB4 3QJ.

CORTEX SOFTWARE GRAPHICS SKETCHPAD. Easy design and modification of shapes and chars. Very useful tool for games animation. Cassette and user guide. £4.95. G. Alexander, Flat One, 26 Priory Road, Malvern, Worc.

NASCOM 1/2 speech using SP-0256 I.C. circuit details and software to drive PIO £3.50. R. W. Chandler, 15 Belvedere Mt, Leeds LS11 7ED.

EXHIBITIONS

SUSSEX MOBILE RALLY. A day by the sea with the family for £1. Brighton Raceground. 17th July. 10.30 am - 5.00 pm. Free car parking. Good catering under cover.

KITS

DIGITAL WATCH REPLACEMENT parts, batteries, displays, backlights etc. Also reports publications, charts. S.a.e. for full list Profords Conersdrive, Holmergreen Bucks. HP15 6SGD

PRINTED CIRCUITS Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

MINIATURE TRANSMITTER KIT. Complete with easy to follow instructions. Only £4.80. Ashley, 10 Stone Road, Coal Aston, Sheffield S18 6AH.

BUILD A HE-NE LASER. Plans and instructions £2.00. Includes lists of all components, (can be purchased separately). Lasertronics, 21 Grosvenor Road, Scarborough.

PUSH BUTTON TELEPHONE, 40 number memory. Build your own for around £16 using standard components. Full circuit, plans, and construction details, £3 (not BT approved). Ms M. J. Ellis, 1 Wells Drive, Heaton, Mersey, Stockport, Cheshire.

ADD ONS

TELETEXT (Oracle/Ceefax) add-on adaptors for any television. Only £147.50 plus £2.45 postage. Also Viewdata (Prestel). Access/Visa. Cytel (ETI). Freepost Bristol BS10 6BR. (0272) 502008 anytime.

FOR SALE

AMPEX 1" TAPE TRANSPORT MECHANISM. £350. Set 8-track heads £50 with circuit plans and construction details. 19" rack mounting cabinet, 6ft tall, free to purchaser. 061-998 7143.

TANGERINE MICROTAN COMPUTER. Professionally built V2.3 monitor, manual £40. Memotech 16K memory pack, brand new. Boxed £25. Tel: 01-455 0320.

FOR SALE

CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulkins, Reverb Trays, P & N Mic Stands, ASS Glasstire Horns, CELESTION POWER Speakers.

ADAM HALL SUPPLIES LTD

Send 30p cheque P.O. for illustrated catalogue. Adam Hall (ET Supplies), Unit B, Carlton Court, Grainger Road, Southend-on-Sea.

CONVERT ZX81 to Eprom programmer. ZP4000 unit £55 + VAT or SAE details Enterprise Technology Limited. P.O. Box 140, Wigan WN3 6LF.

ELECTRONIC ORGAN KEY-BOARDS and other parts being cleared out as special offer Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8 01-986 8455.

VERORACKS 19" BRAND NEW, beautifully made, will take card size 11.5 cms by 20.1 cms it has 40 card slides marked 1-20. Lockable front panels size 11.5 cms by 30.5 cms and 11.5 cms by 13 cms (PSU PANEL) PSU chassis included with plug and socket on back panel. 5 off "D" type cut outs on rack back panel, provision for fixing board sockets on rack. Only £30.00. Custom made fully enclosed case for the above, with carrying handles and back panel cut out for rack connections, colour Blue Only £25.00. RACK WITH CASE FOR £50.00 all prices have VAT and postage included in them. "Q" SERVICES, 29 LAWFORD CRESCENT, YATELEY (0252) 871048 CAMBERLEY, SURREY.

SHEETMETAL FOLDERS 18" x 18c Steel, 16G Aluminium bench or vice held. Hobby or Light industrial use. £33. 01-890-7838 Day/evening.

Whatever you are selling.

Do it quickly and cheaply

Phone ASP Classified 01-437 1002

ALARMS

A1

051-223 3483
INTRUDER ALARMS LTD
WHOLESALE SUPPLIES
MAIL ORDER DEPT

Bell Boxes	£6.00
Dummy Boxes	£4.50
Bell 6"	£7.50
SIRENS	
Minimite	£4.50
Electronic	£7.50
Cable (4 core)	£7.00
PRESSURE MATS	
Stair	£0.95
Standard	£1.50
CONTROL PANELS	
Battery T/E/E	£20.00
F S N 20/40	£36.00
CONTACTS	
Aluminium	£1.85
Surface	£0.75
Flush	£0.65
Quickfits	£0.75
BEAMS	
Infra Red	£31.50
Ultrasonic comp	£36.00
Rec Battery	£6.95

Discount on quantity - Please add 16% VAT
FOR ORDERS LESS THAN £30 P&P £2.00
OVER £30 P&P FREE
A1 ALARMS LTD
86 Derby Lane, Old Swan, Liverpool L3

CENTURION ALARMS

We manufacture, you save £ £ £'s

Send s.a.e. or phone for our Free list of professional D.I.Y. Burglar Alarm Equipment and accessories. Discount up to 20% off list prices, eg. Control Equipment from £15.98, Decoy Bell Boxes from £5.95 inc.

TRADE ENQUIRIES WELCOME

0484-21000

or 0484 35527 (24 hr ans.)
CENTURION ALARMS (ETI)

265 Wakefield Road, Huddersfield
HD5 9BE W. Yorkshire
Access by Visa
Orders Welcomed

BURGLAR Alarm Equipment. Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 308920.

BURGLAR ALARM EQUIPMENT: As used in the trade. JN Security Centre, 176 Sydenham Road, London SE26 5JZ. 01-778-1111. Showrooms open six days.

EQUIPMENT

U.V. LIGHT EXPOSER UNIT for use in prep. of photo-resist P.C.B's. Attractive wooden construction with exposer area of 250 x 150 mm. Case 350 x 250 x 95 mm. 240v operation. Only £37.00 p&p. Send cheque to V.E.P. Ltd. 5 Hewens Rd. Uxbridge UB10 0FR.

NEW 1983 EDMUND SCIENTIFIC CATALOGUE NOW AVAILABLE

72 pages of:
Solar Energy, Lab. Equipment, Photography, Magnifiers, Health, Astronomy, Motors, Magnets, Holography, Fibre Optics, Weather, And More!
Send for FREE copy to:
Dept ET10,
Rhenbergs Sciences Ltd,
Sovereign Way, Tonbridge,
Kent TN9 1RN
or phone 0732 357779

EASY MONEY. Installing electronic alarms in friends cars. Sounds if headlamps left on. Fitted 5 mins. Full details £1 + SAE. F. W. Kelly, 6 Rydal Close, Sacriston, Durham.

SHUGART SA400 5 1/4" SS/DD. Floppy Disc Drives £55 each. Fedranti VDU for spares/repair £60 ono. Orpington 71317.

HIGH POWER MERCURY ION LASER, emits green/red light. Easily built by the amateur constructor. Ideal school project, etc. Comprehensive kit of plans, including source of all materials, £5.25 + 25p P&P. Lasertech, 31 Mill Brow, Chadderton, Lancs.

COPPER CLAD Double Sided Fibreglass, 12" x 8". 10 sheets £6. 5 sheets £4. Davron, Box No. E.T.I. 202, ASP Ltd., 145 Charing Cross Road, London WC2.

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BLO 9AGH.



RCB's
Printed Circuit Boards
to your specification
from artwork through to
finished board.

**QUICK DELIVERY -
COMPETITIVE PRICES**

**EROFTON
ELECTRONICS
LIMITED**
35 Grosvenor Road,
Twickenham, Middlesex
TEL 01-891 1923/1513 Telex 295093

COMPONENTS

The Circuit Broker®

selects from twenty reliable,
economical P.C. suppliers.

The Circuit Broker, W.Q. Ltd.,
19, Storey's Way, Cambridge CB3 0DP
Tel: (0223) 311811

NEW COMPONENTS CHEAPEST PRICES

New full spec parts ex stock. Same day
despatch SAE or phone for full lists

Example prices: 10 uf. 35v radial
capacitors 5p each. 100 1/4w resis-
tors 75p (1K, 10K, 100K — other
values available) BC308B 10p each
25IN 4148 for only 45p

COLCHESTER COMPONENTS
Unit A2
Cowdry Centre, Colchester
(0206) 66345

**MAIDSTONE ELECTRONIC
COMPONENTS** shop. Thy-
ronics. Control Systems 8, Sand-
ling Road, Maidstone, Kent,
Maidstone 675354.

NOW OPEN IN NEWCASTLE,
Waterloo Street, "Marlborough
Electronic Components" for the
best in electronic components,
test equipments etc. Tel 618-
377.

**FOR ALL YOUR CLASSIFIED
REQUIREMENTS PHONE
ASP LTD.
01-437 1002**

CLASSIFIED ADVERTISEMENT — ORDER FORM

Advertise nationally in these columns to over 100,000 readers for only 35p per word (minimum charge 15 words).
Simply print your message in the coupon and send with your cheque or postal order made payable to

Argus Specialist Publications Ltd to:

CLASSIFIED DEPT., ELECTRONICS TODAY INTERNATIONAL
145 Charing Cross Rd., London WC2H 0EE. Telephone: 01-437 1002
Please indicate classification required.

Name

Address

.....

Tel. No. (Day)

WE TAKE ACCESS AND BARCLAYCARD

Please place my advert in E.T.I. for ☐ months. Please indicate number of insertions required.

TRAINEE ASSISTANT FILM RECORDISTS

Would you like to specialise in sound with the BBC TV's Film Department?

Trainee Assistant Film Recordists work initially in Sound Transfer and Dubbing areas operating sound recording equipment with the prospect of moving on to location Film Recording work in due course.

EXCELLENT TRAINING is given if you have ambitions to do this type of work but lack experience. You will need 'O' level standard of education or equivalent, preferably including Physics and/or Maths and a basic knowledge of electronics. Applicants should be able to demonstrate a practical interest in Sound Recording. Normal hearing and colour vision are essential and applicants must hold a current driving licence or be prepared to obtain one within a reasonable period.

Successful candidates will start their three year training period in January 1984 at a salary of £5,451 (currently under review). An additional allowance is paid for shift work (not nights). Based West London. Relocation expenses considered.

Contact us immediately for application form (quote ref. 1350/ETI and enclose s.a.e.): **BBC Appointments, London, W1A 1AA.**
Tel. 01-580 4468 Ext. 4619.

Completed application forms to be returned by Friday, 15th July 1983.

We are an Equal Opportunities employer



*For cost effective
results when you
need to recruit*

**Top Quality
Personnel**

**Phone
ETI Appointments
01 437 1002
extn 204**

METROPOLITAN POLICE

Are you interested in Security?

The Metropolitan Police Office has vacancies in south-east London for a number of

Telecommunications Technical Officers (Grade III)

to work on the maintenance and installation of intruder alarm systems.

The duties include planning detailed requirements and acting as team leader on the installation of systems, maintaining liaison with those responsible for the provision of services and preparing orders for equipment required, preparing documentation of the system including drawings and commissioning the alarm system when installation is complete. On-site training will be given as necessary.

Candidates must possess an ONC in Engineering or an equivalent City & Guilds/TEC qualification in a relevant discipline and at least 4 years' experience in electronics.

Salary (under review): £7,203 pa to £9,403 pa inclusive of inner London weighting.

Annual leave: 4 weeks 2 days rising to 6 weeks plus 10½ days public and privilege holidays.

There are good prospects for promotion.



For further details and an application form write to:
The Establishment Officer,
Room 213 (ETI/TTO(S))
105 Regency Street
LONDON SW1P 4AN

or ring 01-230 3122 (24 hour answering service)

Closing date for receipt of completed applications is
24th June 1983.



MONITORS

IT'S A BETTER BUY THAN MOST AT
LESS THAN £4 PER MHZ.

THE PRICE IS AS CRISP AS THE IMAGE.
ORDER TODAY - WE'LL SHIP RIGHT AWAY.
All major Credit Cards accepted.

Phone for details of cased and open
frame monitors.

CROFTON ELECTRONICS LTD.

35 GROSVENOR ROAD, TWICKENHAM, MIDDX. 01-891 1923/1513 Telex 295093

E.T.I. — JULY 83 ADVERTISERS INDEX

A.D. Electronics	90
Aitkin Bros.	90
Ambit Int.	16
Armon Electronics	74
Audio Electronics	51
Bi-pak	51
BK Electronics	14
Black Star	62
B.N.R.S.	67,85
Bradley Marshall	10
Branime Marketing	74
Circuit Board Components	51
Clef Products	92
Concept Electronics	73
Comcuip	80
Comtech Electronics	67
Cricklewood Electronics	8,9
Crimson Elektrik	88
Crofton Electronics	98
Display Electronics	18
Electronize Design	26
Electrovalue	50
Emos	74
Engineering and Electrical Design Services	88
Europa Electronics	75
Flight Electronics	27,39
Greenbank Electronics	85
G.S.C.	31
Happy Memories	75
H.G. Electronics	85
Horizon Electronics	88
ICS	92
ILP	40,41,62
Kelan Engineering	85
Kempston	25
LB Electronics	75
L&B Electronics	98
L.E.M. Services	92
Magenta Electronics	92
Maplin	OB
Mawson Assocs.	80
Memotech	54,55
Midwich	19
MJL Systems	61
Musicraft	85
Pantechnic	25
Parndon Electronics	80
Petron Electronics	88
Powertran	IFC,56,IBC
Rade Systems	73
Rapid Electronics	6
R.T.V.C.	61
Saffran Electronics	25
Scopex	39
Sinclair Research	32,33
Sparkrite	12
Spectre Electronics	90
Stuarts of Reading	73
Technomatic	68,69
Teleradio	90
Watford Electronics	4,5
Wilmslow Audio	80

POWER DIMMER MODULES

A range of electronic modular dimmers designed to
suit your custom channel and facility requirement

- Considerable saving over commercial equipment
- All the commercial facilities and more
- Compatible special effects
- Preset/remote master
- Easily installed and wired

SPC — Simple but effective 1000W controller	£15.70
SPU — Used in conjunction with RS units for Remote desks in 1000 and 2000W versions	£11.90 £23.90 (2K)
MC — Master dimmer for SPC/RS units	£7.90
RS — Remote controller for SPU/SPC Units	£9.40
SUP/REF — Supply/signals for up to 50 modules	£20.00

Discounts on above only (order £100 to £199 25% £200 to £299 £300 + 35%)


EFFECTS ACCESSORIES

MXSL — Four channel sound to light	£33.20
MXLS — Four Channel Sequencer	£21.40
MXLC-S Four Channel sound chaser	£24.00
MXECF — Dip/Dipless Electronic Crossfade	£28.70

3 CHANNEL SOUND/LIGHT

CHASER £35.70

LB31000SLC

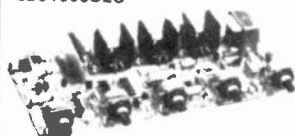

A high performance sound to light providing bass,
mid and treble separation employing active
filters. Automatic switching to chase in the
absence of a music signal 1000W chaser.

STEREO DISCO MIXER/PREAMP

LBPA3

M Magnetic
C Ceramic



Main supply £7.20
PFL supply £1.00

£36.70

All the requirements of a stereo disco preamp
on one board. Left and right deck mixers/tones
controls, misc. mixer tones, mic, auto, fade
over decks and P.F.L. The unit can be used with
virtually any power amp.

3 CHANNEL SOUND/LIGHT LB31000SL



£22.70

All the advantages
of the SLC without chase
Controls: bass/mid/treble/master sensitivity

AND MORE!

- * 4 CHAN S/L AUTO CHASER
- * 4 CHAN MULTI SOUND CHASER
- * 4 CHAN SEQUENCER
- * 4 CHAN SOUND CHASER
- * FASCIA PANELS

Active Crossovers £17.90 (supply £7.20)
(3-way 300Hz/3kHz)

Don't hesitate to write or phone for immediate information. All prices include VAT. Please include 75p
post except power dimmer (£2.75). Cheques P.O. COD. Access all welcome.
Tel: 01-640 6053 (Mon to Fri 9 to 4.30)

L & B ELECTRONIC 34 Oakwood Ave, Mitcham, Surrey CR4 3DP

Get moving with these new developments in UK Robotics

— advanced electrohydraulic designs for education, industry and now available to the home constructor.

Hebot II is a turtle-type robot which takes programming out of the two dimensional world of the VDU into the real three dimensional world. Given a DC supply of 9-15V it can perform a bewildering number of moves under computer control — forwards backwards, left and right — with each wheel independently controlled. It has blinking eyes, bleeps with a choice of two tones and has a solenoid operated pen to chart its progress. Touch sensors coupled to its shell return data about its environment, to the computer for it to calculate evasive or exploratory action. Hebot II connects directly to an I/O port or alternatively with the universal interface board to the expansion bus of a ZX81 or other computer.



HEBOTT II

Up to the nano-second hard, firm and software developments embodied in a complete system. 12 Mega Hertz 16 bit CPU; 64K upwardly compatible DRAM; separate 16K video DRAM and 24K TI Power Basic with overwrite. Supports up to four Disc drives of mixed type with 16 serial I/O ports. Programmable Baud rate and comprehensive E Bus interface designed to support real world applications.

Very high resolution graphics gives 3D simulation in 16 colours on 36 prioritised planes of user definable characters. Software FORTH coming includes this trendy language along with NOS C/PM.

Hardware components available separately with details in Nov, Dec, and Jan issues of ETI. Software features include; Real time clock, full renumber command, buffered I/O to free machine whilst

Top of the range is the Genesis P102 which has dual speed control, continuous servo operation and double acting cylinders for increased torque on the wrist and arm rotation joints. The microprocessor based control system has additional memory, position interrogation via the RS232C interface increasing the versatility of computer control and inputs are provided for machine tool interfacing.

6 axis system READY BUILT £1950.00
Powertran CORTEX 16 bit 64K computer Kit £295.00, READY BUILT £395.00
(Electronics Today International December issue on CORTEX)



GENESIS P102 PROCESSOR BOX, HAND-HELD CONTROLLER AND CORTEX COMPUTER

Robotic experience is becoming as essential a subject as computing. MICROGRASP provides the lowest cost means of acquiring that experience but despite its ultra low price the robot has considerable versatility. There are 5 axes each using a servo motor and there is feedback from each of the arm movements. Control is by any computer with an expansion bus — the ZX81 being particularly suitable. Servoing is achieved with hardware on the interface board to keep programming simple and the robot is operated under BASIC commands with no computer specific software required. The interface board's memory mapped using only 64 bytes at any of 1024 switch selectable locations.

MICROGRASP robot kit with power supply £145.00
Universal computer interface board kit £48.50
23 way edge connector £2.50
ZX81 peripheral RAM Pack splitter board £3.00



MICROGRASP, INTERFACE BOARD AND ZX81

printing, call to machine code routines, hexadecimal support and user-friendly textual error trapping messages.

If computers interest you then the Cortex will expand your understanding infinitely more than off the shelf machines. Use it in business, education, research or just play with the incredible graphics capability. At Powertran we are using these machines in conventional roles, in product control and R & D. We shall co-ordinate the Cortex user group and distribute software for the TMS 9995 CPU. Complete 16 bit 64K computer kit £295.00 + VAT. Complete 16 bit 64K computer ready built £395.00 + VAT.



Example prices and specifications

Genesis S101
Base 19.5" x 11" x 7.5"
Lifting capacity, 1500gm
Arm lift 66"
Weight 29Kg
4 axis model in kit form £425
5 axis model in kit form £475

Genesis P101
Base 19.5" x 11" x 7.5"
Lifting capacity 2000gm
Arm lengths between axes 14.0"
Weight 34Kg
4 axis model in kit form £675
6 axis model in kit form £595

Complete Systems as shown in Photograph above

Genesis S101
4 axis system in kit form £681.50
5 axis system in kit form £737.50
5 axis system Ready Built £1450
Genesis P101
6 axis system in kit form £945.00
6 axis system Ready Built £1650

All prices exclusive of VAT

With prices starting below £1 000 the Genesis range of general purpose robots provide a first rate introduction to robotics for both education and industry. Each has a self-contained hydraulic power source, which enables loads of several pounds to be smoothly handled. The system operated from a single phase 240 or 120V AC supply or a 12V Dc supply. The machine can be supplied with up to 6 axes each of which is fully independent but capable of simultaneous operation. Position control is achieved by means of a closed-loop feedback system based around a dedicated microprocessor. Movement sequences can be entered, stored and replayed by use of a hand-held controller, alternatively the systems can also be interfaced to an external computer via a standard RS 232C link.



GENESIS S101 AND GENESIS P101 WITH PROCESSOR BOXES AND HAND-HELD CONTROLLERS


WORLD LEADERS IN ELECTRONIC KIT DESIGN AND SUPPLY

(CYBERNETIC DIVISION) PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NN Phone Enquiries (0264) 64455
Export Enquiries Powertran International
Hollom Down Farm Lidscombe Salisbury
Wiltshire SP5 1BP
Tel: 0264 781545 TLX: 477407 ZENMON

Send now for an application form — then buy it with MAPCARD.

MAPCARD gives you real spending power — up to 24 times your monthly payments — instantly!

Maplin News

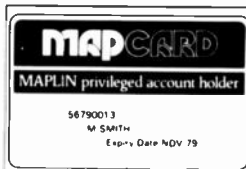

Sole UK Agents for Heathkit

NOW THE world-famous Heathkit range of superb electronic kits is available from Maplin — the newly appointed exclusive UK distributor. Kits range from a simple clock for beginners to a unique Robot (see pic) with which you can learn about robotics.

There is a range of training courses covering electronics and computing topics, many containing constructional projects. For full details, pick up a copy of the latest Maplin magazine or write for a free copy of our Heathkit catalogue. Order As XH62S.



GREAT PROJECTS FROM E&MM



OUR NEW book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. ORDER AS XH61R. PRICE £1.

Computer Shopping Arrives

AS FROM June 1st you can place orders directly with our computer from your personal computer. The computer shopping revolution has arrived! To communicate, you'll need a modem (our RS232 compatible modem kit is LW99H price £39.95) and an interface (our ZX81 interface LK08J price £24.95 is available already with many more for most popular micros coming soon).

Just dial us up on 0702 552941 and you'll be able to interrogate our stock file then place your order, type in your credit card number and a few minutes after you hang up your order will print out in our warehouse ready for packing. And all without saying a word.

Try out the future way of shopping now! You'll see immediately what stock we've got available and you'll discover how easy it is to ensure your order is exactly right. And you'll see precisely what the current price is for each item and what total amount will be charged to your credit card. It all helps to make buying easier. So give us a ring now!

Maplin's Fantastic Projects


FULL DETAILS in our project books. Price 70p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • Six Vero Projects.

In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W MOSFET Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

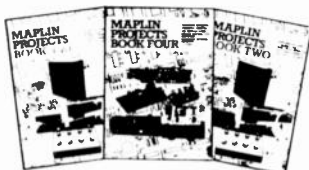In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to



600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard • 100W 240V AC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC 20 •

Module to Bridge two of our MOSFET Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) • Modem Interface for ZX81/VIC20 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • Minilab Power Supply • Electronic Lock • and others.

*Projects for Book 7 were in an advanced state at the time of writing, but contents may change prior to publication (due 14th May 1983).

25W Stereo MOSFET Amplifier



- Over 26W/channel into 8Ω at 1kHz both channels driven.
- Frequency response 20Hz to 40kHz $\pm$ 1dB.
- Low distortion, low noise and high reliability power MOSFET output stage.
- Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7

wires (plus toroidal transformer and mains lead terminations). • Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in Projects Book 3. Price 70p (XA03D). Complete kit only £55.20 incl. VAT and carriage (LW71N).

MATINEE ORGAN

EASY-TO-BUILD, superb specification. Comparable with organs selling for up to £1000.

Full construction details in our book (XH55K). Price £2.50. Complete kits available. Electronics (XY91Y) £299.95*. Cabinet (XY93B) £99.50*. Demo cassette (XX43W) £1.99.

*Carriage extra



Maplin's New 1983 Catalogue

Over 390 pages packed with data and pictures and all completely revised and including over 1000 new items.

On sale in all branches of WH SMITH. Price £1.25.



MAPLIN ELECTRONIC SUPPLIES LIMITED, P.O. Box 3, Rayleigh, Essex SS6 8LR. Telephone: Sales (0702) 552911 General (0702) 554155.

Shops at: 159 King St., Hammersmith, London W6. Tel: 01-748 0926. 284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000. Lynton Square, Perry Barr, Birmingham. Tel: (021) 356 7292.

Shops closed Mondays.

All prices include VAT & carriage. Please add 50p handling charge to orders under £5 total value.

POST THIS COUPON NOW!

Please send me a copy of your 1983 catalogue. I enclose £1.50 (inc. P&P). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.90 or 10 International Reply Coupons.

Name

Address

.....

.....

Post Code