

# electronics today

INTERNATIONAL

MARCH 1986

£1.20

## FREE PCB

AND PROJECTS GALORE TO USE IT FOR

## PLUS

▶ RS232 TO CENTRONICS CONVERSION

▶ DISPLAY TECHNOLOGY SHOWS ITS COLOURS

▶ EXPERIMENT WITH PROGRAMMABLE LOGIC

NAB EQUALISATION STAGE

CAPACITANCE METER MODULE

MEMO MINDER

NAB EQUALISATION STAGE

CAPACITANCE METER MODULE

RIAA EQUALISATION STAGE

RIAA EQUALISATION STAGE

MEMO MINDER

YOUR FREE PCB WORTH OVER £2

AUDI

MUSIC... RADIO... ROBOT

# OMP POWER AMPLIFIER MODULES

\* PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E. 28p STAMP FOR CURRENT LIST

## OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



**OMP100** Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max output 500mV at 10K, Size 355 x 115 x 65mm. PRICE £33.99 + £3.00 P&P.



**OMP/MF100** Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



**OMP/MF200** Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P.



**OMP/MF300** Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P.

NOTE: Mos Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) if required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.



**Vu METER** Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 - 50p P&P.

**LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S.** Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.



**POWER RANGE**  
**8" 50 WATT R.M.S. Hi-Fi/Disco.**  
 20 oz magnet, 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.  
**12" 100 WATT R.M.S. Hi-Fi/Disco**  
 50 oz magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.

**McKENZIE**  
**12" 85 WATT R.M.S. C1285GP** Lead guitar/key-board/Disco.  
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £28.76 + £3.00 P&P ea.  
**12" 85 WATT R.M.S. C1285TC P.A./Disco** 2" ally voice coil. Twin cone.  
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £29.80 + £3.00 P&P ea.  
**15" 150 WATT R.M.S. C15** Bass Guitar/Disco.  
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £54.99 + £4.00 P&P ea.  
**10" 60 WATT R.M.S. 1060GP** Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.  
 2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.15 + £2.00 P&P ea.  
**10" 200 WATT R.M.S. C10200GP** Guitar, Keyboard, Disco.  
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £51.00 + £3.00 P&P ea.  
**15" 200 WATT R.M.S. C15200** High Power Bass.  
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £59.45 + £4.00 P&P ea.  
**15" 400 WATT R.M.S. C15400** High Power Bass.  
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £85.00 + £4.00 P&P.

**WEM**  
**5" 70 WATT R.M.S. Multiple Array Disco** etc.  
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £19.99 + £1.50 P&P ea.  
**8" 150 WATT R.M.S. Multiple Array Disco** etc.  
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £29.49 + £1.50 P&P ea.  
**10" 300 WATT R.M.S. Disco/Sound re-enforcement** etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £33.49 + £2.00 P&P ea.  
**12" 300 WATT R.M.S. Disco/Sound re-enforcement** etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £41.49 + £3.00 P&P ea.

**SOUNDLAB (Full Range Twin Cone)**  
**5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco** etc.  
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.  
**6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco** etc.  
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.  
**8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco** etc.  
 1 1/4" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.  
**10" 60 WATT R.M.S. Hi-Fi/Disco** etc.  
 1 1/4" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P.

**PANTEC HOBBY KITS.** Proven designs including glass fibre printed circuit board and high quality components complete with instructions.



**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.  
**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.  
**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each, S.A.E. for complete list.

3 watt FM Transmitter

## BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units complete with inter-connection cable. FULLY GUARANTEED.

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



**Control Unit** - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.  
**Indoor Alarm** - Electronic swept freq. siren 104dB output.  
**Outdoor Alarm** - Electronic swept freq. siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

**SAVE £138.00** Usual Price £228.85  
**BKE's PRICE £89.99 + £4.00 P&P**  
 Why buy a collection of self assembly boards!



## OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models B ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R.M.S. per cabinet. Sensitivity 1W. 1mtr. dB.



**OMP 12-100 Watts 100dB. Price £149.99** per pair.  
**OMP 12-200 Watts 102dB. Price £199.99** per pair.  
 Delivery Securicor £8.00 per pair

## OMP 19" STEREO RACK AMPS



**Professional 19" cased Mos-Fet stereo amps.** Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. **Three models** (Ratings R.M.S. into 4ohms). Input Sensitivity 775mV  
**MF200** (100 + 100)W. £169.00 Securicor  
**MF400** (200 + 200)W. £228.85 Delivery  
**MF600** (300 + 300)W. £274.85 £10.00


## 1 K-WATT SLIDE DIMMER

- \* Control loads up to 1Kw
- \* Compact Size 4 1/2" x 1" x 2 1/2"
- \* Easy snap in fixing through panel cabinet cut out
- \* Insulated plastic case
- \* Full wave control using 8 amp triac
- \* Conforms to BS800

\* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.  
**PRICE £13.99 - 75p P&P**
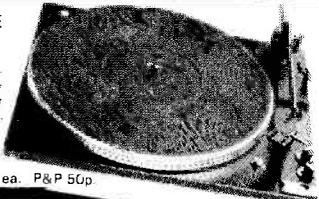
## BSR P295 ELECTRONIC TURNTABLE

\* Electronic speed control 45 & 33 1/3 r.p.m. \* Plus Minus variable pitch control \* Belt driven \* Aluminium platter with strobed rim \* Cue lever \* Anti-skate (bias device) \* Adjustable counter balance \* Manual arm \* Standard 1/2" cartridge fixings \* Supplied complete with cut out template \* D.C. Operation 9-14V D.C. 65mA  
 Price £36.99 - £3.00 P&P




ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p
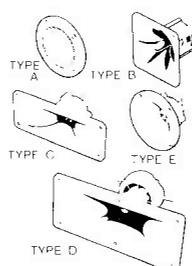
## PIEZO ELECTRIC TWEETERS MOTOROLA


Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P  
**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P  
**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P  
**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P  
**TYPE 'E' (KSN1038A)** 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P  
**LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P


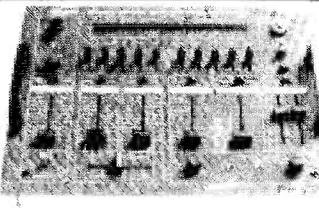
## STEREO DISCO MIXER

**STEREO DISCO MIXER** with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following - 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor, Pan Pot, L & R Master Output controls. Output 775mV. Size 360 x 280 x 90mm  
 Price £134.99 - £3.00 P&P




**B. K. ELECTRONICS** DEPT ETI  
 UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
 ESSEX, SS2 6TR TEL: 0702-527572

VISA POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED

# electronics today

INTERNATIONAL MARCH 1986 VOL 15 NO 2

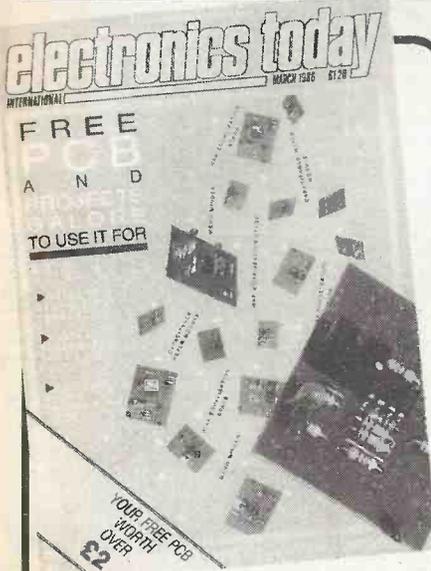

**Gary Herman:** Editor  
**Ian Pitt:** Assistant Editor  
**Paul Chappell:** Project Editor  
**Jerry Fowler:** Technical Illustrator  
**Paul Stanyer:** Ad. Manager  
**Stuart Taylor:**  
 Classified Sales Executive  
**Debra Barrie:** Copy Control  
**Dave Bradshaw:** Group Editor  
 - Electronics  
**Peter Welham:** Publishing Director

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 1 Golden Square, London W1R 3AB.  
**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)

**PRINTED BY:**  
 The Garden City Press Ltd.  
**COVERS DESIGNED BY:**  
 Argus Press Design.  
**COVERS PRINTED BY:**  
 Alabaster Passmore.



Member of the  
 Audit Bureau  
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1986 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK: £18.10. Overseas: £22.50. USA: \$29.50. Airmail: £49.50.

## EDITORIAL AND ADVERTISEMENT OFFICE


1 Golden Square, London W1R 3AB. Telephone 01-437 0626.  
 Telex 8811896.

## FEATURES

- DIGEST**..... 7  
 Not the Nine O'Clock News!
- READ/WRITE**..... 14  
 Letters now praise famous men.
- MICROEXPANSION**..... 18  
 If your micro is an eight-bit weakling, Mike Barwise shows you how to build its muscles.
- THE SHOW MUST GO ON** .... 22  
 Keith Brindley lights the way to the latest in display technology.
- BETTER BY DESIGN** ..... 27  
 Avoid simple design faults the Andy Armstrong way.
- RS232-CENTRONICS CONVERSION**..... 52  
 D. J. Virden provides a circuit solution for the serial-minded.
- TECH TIPS**..... 54  
 These tips are always pointed.
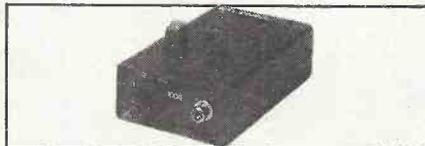
## PROJECTS

- FREE PCB PROJECTS** ..... 30  
 The first four free printed circuits won't board you — a Capacitance Meter module, the Memo Minder and RIAA and NAB Equalisation Stages. Three more next month, too.
- PROGRAMMABLE LOGIC EVALUATION BOARD**..... 37  
 Mike Bedford concludes his introduction to programmable logic with an experimenters' board.
- DIGITAL SOUND SAMPLER**.... 44  
 The analogue board performs all the conversions necessary for an eight-bit sampler.
- 6809 SINGLE-BOARD COMPUTER** ..... 47  
 Get the system up and running.
- DIGIBARO LISTING**..... 50  
 The ROM contents for last month's digital barometer project.



## ETCETERA

- CROSSWORD** ..... 61
- REVIEWS** ..... 61  
 A QLutch of QL books.
- OPEN CHANNEL**..... 63  
 Keith Brindley airs his views.
- PLAYBACK**..... 62  
 Vivian Capel Cs D emergence of digital audio tape.
- ALF'S PUZZLE**..... 63  
 Alf gets his buses in a knot.
- SCRATCHPAD** ..... 62

## INFORMATION

- NEXT MONTH'S ETI**..... 17
- COMPETITION** ..... 35
- FOIL PATTERNS**..... 56
- PCB SERVICE** ..... 59
- READER'S SERVICES** ..... 60
- CLASSIFIED ADS**..... 64
- AD INDEX**..... 66

# WATFORD ELECTRONICS

250 High Street, WATFORD, WD1 2AN, HERTS.  
 MAIL ORDER & RETAIL SHOP  
 Tel: (0923) 37774 Tlx. 8956095 WATFRD

ALL DEVICES BRAND NEW & FULLY GUARANTEED. SEND CHEQUES, P.O.s & BANK DRAFT OR ACCESS/MASTER CHARGE & VISA CARD NUMBER WITH ORDER. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS' OFFICIAL ORDERS ACCEPTED. P&P ADD 1% TO ALL CASH ORDERS. OVERSEAS ORDERS, POSTAGE CHARGED AT COST AIR/SURFACE. PRICES SUBJECT TO CHANGE WITHOUT NOTICE AND AVAILABLE ON REQUEST.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

**ELECTROLYTIC CAPACITORS:** (Values in  $\mu F$ ) 500V: 10 $\mu F$  52, 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 8p; 101 10p, 1.5, 2.2, 3.3, 15p; 47 12p; 68 20p; 100 19p; 220 26p; 1000 70p; 2200 90p; 50V: 68 20p; 100 17p; 220 24p; 400V: 22 9p; 33 12p; 330, 470 20p; 1000 48p; 2200 80p; 25V: 1.5, 4.7, 10, 22, 47 8p; 100 11p; 100 17p; 220 21p; 330 22p; 470 25p; 680, 1000 30p; 1500 42p; 2200 50p; 3300 70p; 4700 92p; 18V: 47, 68, 100 9p; 125 12p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 28p; 4700 72p.

**TAG-END CAPACITORS:** 63V: 2200 140p; 3300 145p; 4700 245p; 50V: 2200 95p; 3300 150p; 40V: 4700 160p; 25V: 2200 70p; 3300 85p; 4200 120p; 75p; 1500 250p; 1500 250p; 20V: 1200 250p; 3300 200p.

**POLYESTER CAPACITORS: Axial Lead Type**  
 400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 16n, 22n 12p; 33n, 47n, 68n 16p; 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 100p; 1500n 220n  
 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 100n 42p.

**POLYESTER RADIAL LEAD CAPACITORS: 250V**  
 10p; 15n, 22n 27p; 33n 47n; 68n, 100n 8p; 150n, 220n 10p; 330n, 470n 15p; 680n 19p; 1u5 40p; 2u2 48p.

**TANTALUM BEAD CAPACITORS:** 35V: 0.1 $\mu F$ , 0.22, 0.33 15p 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 20p; 15 22p; 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15, 36p; 2.2, 4.7, 10 15p; 100 95p; 10V: 1.5, 2.2, 3.3, 4.7 50p; 100 80p; 6V: 1.0 50p.

**MYLAR FILM CAPACITORS**  
 100V: 1nF, 2, 4, 4nF, 10 8p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 9p; 400V: 47nF 12p.

**CERAMIC CAPACITORS 50V:**  
 Range: 0.5pF to 10nF 4p  
 15nF, 22nF 33nF: 47nF 5p  
 100nF/20V 7p 200nF/5V 8p

**POLYESTER CAPACITORS:**  
 10pF to 1nF 8p; 1.5nF to 12nF 10p.

**SILVER MICA (Values in pF)**  
 2, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180p  
 200, 220, 250, 270, 300, 330, 360, 390, 470, 500, 600, 820, 1000, 1200, 1500, 2200, 3300, 4700pF

**MINIATURE TRIMMERS Capacitors**  
 2-6pF 2-10pF 22p  
 2-25pF, 5-65pF 30p  
 10-80pF 30p

**RESISTORS Carbon Film, miniature, Hi-Stab, 5%.**  
 RANGE Val 1-99 100+  
 0.25W 202 - 10M E24 3p 1p  
 0.5W 25W - 4M E12 3p 1p  
 1W 202 - 10M E24 6p 4p  
 2% Metal Film 512 - 1M E24 6p 4p  
 1% Metal Film 512 - 1M E24 5p 4p  
 100+ price applies to Resistors of each type not mixed.

**RESISTORS NETWORK S.I.L.**  
 7 Commoned (8 pins) 100n, 680n, 1K 2k2, 4k7, 10K, 47K 100K 18p  
 8 Commoned: (9 pins) 150n, 180n, 270n, 330n, 1K, 2K2, 4K7, 6K8, 10K, 22K, 47K & 100K 20p.

**DIODES BRIDGE RECTIFIERS 75 SERIES**

AA119 8 1A/50V 18 75I07/8 95  
 AA129 10 1A/100V 20 75I10/11 150  
 AA130 10 1A/400V 25 75I12/13 220  
 BA100 15 1A/50V 30 75L150 125  
 BY126 12 2A/50V 26 75L154 125  
 BY127 10 2A/200V 40 75L158 150  
 CR033 198 2A/400V 42 75L159 150  
 CA3 470 800 800 820 75L160 420  
 OA47 10 6A/100V 83 75L162 650  
 OA70 9 2A/500V 98 75L182 950  
 OA79 10 10A/200V 215 75L188/9 1000  
 OA81 10 10A/200V 298 75L192 1300  
 OA85 10 25A/200V 340 75L24 360  
 OA86 10 25A/600V 398 75L25 360  
 OA91 8 BY164 56 75L36/3 150  
 OA95 75L36 50  
 OA96 75L36 50  
 OA97 75L36 50  
 OA98 75L36 50  
 OA99 75L36 50  
 OA100 75L36 50  
 OA101 75L36 50  
 OA102 75L36 50  
 OA103 75L36 50  
 OA104 75L36 50  
 OA105 75L36 50  
 OA106 75L36 50  
 OA107 75L36 50  
 OA108 75L36 50  
 OA109 75L36 50  
 OA110 75L36 50  
 OA111 75L36 50  
 OA112 75L36 50  
 OA113 75L36 50  
 OA114 75L36 50  
 OA115 75L36 50  
 OA116 75L36 50  
 OA117 75L36 50  
 OA118 75L36 50  
 OA119 75L36 50  
 OA120 75L36 50

**ZENERS**

Range: 2V7 to 39V 400mW  
 AA148 4 8p each  
 NS4001 12 33V 8p each  
 NS1504 16 15p each  
 NS4006 19  
 IS44 9  
 IS921 9  
 BA1100V 40  
 BA4000V 50  
 BA8000V 60

**TRIACS**

3A200V 54  
 3A400V 56  
 6A200V 60  
 8A200V 60  
 8A400V 60  
 8A800V 115  
 12A100V 98  
 12A200V 98  
 12A400V 102  
 12A800V 126  
 16A100V 83  
 16A200V 106  
 16A400V 120  
 25V500V 220  
 25V600V 220  
 25V800V 220  
 25V1000V 220

**DIAC**

33V105B 40  
 33V106 40  
 25V60 125

**VARICAPS**

33V105B 40  
 33V106 40  
 25V60 125

**DIAC**

33V105B 40  
 33V106 40  
 25V60 125

33V105B 40  
 33V106 40  
 25V60 125

## TRANSISTORS

AC126/7	30	BC441/61	34	BF594/5	30	MPF5056	55	ZX302	16	2N3903/4	18	2SC2612	200
AC141/2	35	BC477	22	BF700	20	OC28	170	ZX303	25	2N3904	18	2SD234	74
AC187	25	BC517/8	30	BF701	20	OC28	220	ZX304	17	2N3906	17	2SK45	80
AC188	25	BC549C	12	BF702	20	OC35	50	ZX326	30	2N4037	60	2SK288	225
AC192/1	75	BC557/8	15	BF703	20	OC47	75	ZX451	23	2N4058	15	25R85	225
AC192/2	75	BC559/15	15	BF704	20	OC75	75	ZX500	14	2N4061/2	15	3N128	115
AD149	75	BC639/40	85	BF705	20	OC75/72	55	ZX501/2	15	2N4062	15	3N140	115
AD151	42	BC640C	12	BF706	20	OC75/72	55	ZX502	18	2N4063	15	3N142	115
AD162	42	BC658/59	36	BF707	20	OC81/82	35	ZX503	18	2N4064	15	3N145	90
AD156/8	60	BC707/18	18	BF708	20	OC85/84	70	ZX504	125	2N4065	15	3N146	90
AF134/26	60	BC708	18	BF709	20	OC85/84	70	ZX505	25	2N4066	15	3N147	90
AF139	40	BD114	190	BF710	20	OC92	75	ZX506	23	2N4067	15	3N148	90
AF178	75	BD121	95	BF711	20	OC92	75	ZX507	32	2N4068	15	3N149	90
AF286	70	BD124	115	BF712	20	OC92	75	ZX508	38	2N4069	15	3N150	90
AF233	55	BD131/32	55	BF713	20	OC92	75	ZX509	38	2N4070	15	3N151	90
BC107	12	BD135	45	BF714	20	OC92	75	ZX510	38	2N4071	15	3N152	90
BC108	12	BD136/37	35	BF715	20	OC92	75	ZX511	38	2N4072	15	3N153	90
BC108B	14	BD138/39	35	BF716	20	OC92	75	ZX512	38	2N4073	15	3N154	90
BC109	12	BD144/45/48	18	BF717	20	OC92	75	ZX513	38	2N4074	15	3N155	90
BC109B	14	BD158	68	BF718	20	OC92	75	ZX514	38	2N4075	15	3N156	90
BC109C	14	BD184	35	BF719	20	OC92	75	ZX515	38	2N4076	15	3N157	90
BC113	12	BD205/6	110	BF720	20	OC92	75	ZX516	38	2N4077	15	3N158	90
BC117/8	25	BF25	35	BF721	20	OC92	75	ZX517	38	2N4078	15	3N159	90
BC119	15	BF378	70	BF722	20	OC92	75	ZX518	38	2N4079	15	3N160	90
BC137/9	40	BD344	70	BF723	20	OC92	75	ZX519	38	2N4080	15	3N161	90
BC140	28	BD517	75	BF724	20	OC92	75	ZX520	38	2N4081	15	3N162	90
BC141/3	22	BF45	45	BF725	20	OC92	75	ZX521	38	2N4082	15	3N163	90
BC147	12	BD654	40	BF726	20	OC92	75	ZX522	38	2N4083	15	3N164	90
BC147B	15	BD696A	150	BF727	20	OC92	75	ZX523	38	2N4084	15	3N165	90
BC148	12	BF115	45	BF728	20	OC92	75	ZX524	38	2N4085	15	3N166	90
BC148B	15	BF154/8	30	BF729	20	OC92	75	ZX525	38	2N4086	15	3N167	90
BC149	12	BF149B	60	BF730	20	OC92	75	ZX526	38	2N4087	15	3N168	90
BC149C	15	BF173	35	BF731	20	OC92	75	ZX527	38	2N4088	15	3N169	90
BC182L	10	BF177	35	BF732	20	OC92	75	ZX528	38	2N4089	15	3N170	90
BC183L	10	BF178	35	BF733	20	OC92	75	ZX529	38	2N4090	15	3N171	90
BC184	10	BF179	35	BF734	20	OC92	75	ZX530	38	2N4091	15	3N172	90
BC186/7	28	BF184/5	12	BF735	20	OC92	75	ZX531	38	2N4092	15	3N173	90
BC212	10	BF198/9	18	BF736	20	OC92	75	ZX532	38	2N4093	15	3N174	90
BC212L	12	BF200	35	BF737	20	OC92	75	ZX533	38	2N4094	15	3N175	90
BC213	10	BF224A	40	BF738	20	OC92	75	ZX534	38	2N4095	15	3N176	90
BC213L	10	BF224B	40	BF739	20	OC92	75	ZX535	38	2N4096	15	3N177	90
BC214	10	BF245	38	BF740	20	OC92	75	ZX536	38	2N4097	15	3N178	90
BC214L	10	BF256A	45	BF741	20	OC92	75	ZX537	38	2N4098	15	3N179	90
BC237/8	10	BF266B	50	BF742	20	OC92	75	ZX538	38	2N4099	15	3N180	90
BC256B	35	BF269	30	BF743	20	OC92	75	ZX539	38	2N4100	15	3N181	90
BC307B	15	BF275	55	BF744	20	OC92	75	ZX540	38	2N4101	15	3N182	90
BC308	12	BF336/7	35	BF745	20	OC92	75	ZX541	38	2N4102	15	3N183	90
BC318	60	BF394	40	BF746	20	OC92	75	ZX542	38	2N4103	15	3N184	90
BC318B	60	BF415	40	BF747	20	OC92	75	ZX543	38	2N4104	15	3N185	90
BC337/8	12	BF494/5	40	BF748	20	OC92	75	ZX544	38	2N4105	15	3N186	90

**SIEMENS pcb Type Miniature Poly Capacitors**

250V	1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 18n, 22n, 27n, 33n, 39n, 56n, 82n, 100n, 110n, 150n, 180n, 220n, 270n, 330n, 390n, 470n, 560n, 680n, 820n, 1000n, 1500n, 2200n, 3300n, 4700n	7p, 8p, 10p, 12p, 15p, 18p, 20p, 22p, 25p, 27p, 30p, 33p, 36p, 39p, 42p, 45p, 48p, 51p, 54p, 57p, 60p, 63p, 66p, 69p, 72p, 75p, 78p, 81p, 8
------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------



# Rapid Electronics

Fast component distribution

Unit 1,  
Hill Farm Industrial Estate  
Boxted, Colchester  
Essex CO4 5RD

Telephone orders: 0206 36412  
Telex: 987756



LINEAR			
IC128	30	BC148	10
IC129	30	BC159C	10
IC176	25	BC171	10
IC187	25	BC175	16
IC188	25	BC179	18
BC107	10	BC182	12
BC108	12	BC183	10
BC109C	12	BC184	10
BC140	28	BC212	10
BC141	28	BC213	10
BC143	30	BC214	10
BC147	10	BC214	10

TRANSISTORS			
AC127	30	BC148	10
AC128	30	BC159C	10
AC176	25	BC171	10
AC187	25	BC175	16
AC188	25	BC179	18
BC107	10	BC182	12
BC108	12	BC183	10
BC109C	12	BC184	10
BC140	28	BC212	10
BC141	28	BC213	10
BC143	30	BC214	10
BC147	10	BC214	10

RESISTORS	
Carbon film	1+ 25+
1/4W 5% 4.7ohm-10M	2p 1p
1/2W 5% 4.7ohm-4M7	3p 2p
Metal film	
1/4W 1% 10ohm-1M	3p 3p
25+ price applies to 25+ per value	
SIL resistor networks	
8 resistor 9 pin type 20p	

**COMPONENT KITS**  
Our component kits offer a considerable saving when buying a complete range of components. Ideally suited for re-stocking etc

BRIDGE RECTIFIERS	
1A 50V	20
1A 200V	25
1A 400V	30
1A 800V	38

**0.25W Resistor kit.** Contains 1000 0.25W 5% resistors from 4.7ohms thru to 10M. Quantities depend upon popularity i.e. 10x10R, 30x470R, 30x10K, 25x470K. Just £7.90 each

**Ceramic capacitor kit.** Total of 240 miniature ceramic capacitors from 220pF thru to 0.1uF. Just £6.90 each

**Polyester capacitor kit.** Total of 110 miniature polyester capacitors from 0.1u to 0.47uF. Just £6.90 each

**Radial electrolytic kit.** Total of 93 miniature radial electrolytics from 1u 63V thru to 2200u 16V. Just £7.50 each

**Presets kit.** Total of 110 miniature, horizontal mounting presets from 100R thru to 1M. Just £6.90 each

CABLES	
20 metre pack single core connecting cable ten different colours.	75p
Speaker cable	10p/M
Standard screened	16p/M
Twin screened	24p/M
3 core 2.5A mains cable	23p/M
Four core screened	35p/M

REGULATORS	
78L05	30
78L12	30
78L15	30
7805	40
7812	45
7815	45
LM317K	230
LM317T	90
LM323K	420

RELAYS	
Ultraminiature SPDT relay rated 2A 6 or 12V	105
Ultraminiature DPDT relay rated 2A 6 or 12V	160
Miniature relay SPDT rated 10A 6 or 12V	160
Miniature relay DPDT rated 5A 6 or 12V	180

OPTO	
3 or 5mm red	8
3 or 5mm green	11
3 or 5mm yellow	11
3 or 5mm blue	3
5mm superbright	30
5mm red	30
5mm yellow	30
5mm green	30
5mm blue	30
5mm white	30
5mm clear	30
5mm black	30
5mm grey	30
5mm brown	30
5mm purple	30
5mm pink	30
5mm orange	30
5mm silver	30
5mm gold	30
5mm black	30
5mm clear	30
5mm white	30
5mm yellow	30
5mm green	30
5mm blue	30
5mm red	30
5mm purple	30
5mm pink	30
5mm orange	30
5mm silver	30
5mm gold	30
5mm black	30
5mm clear	30
5mm white	30
5mm yellow	30
5mm green	30
5mm blue	30
5mm red	30
5mm purple	30
5mm pink	30
5mm orange	30
5mm silver	30
5mm gold	30
5mm black	30
5mm clear	30
5mm white	30
5mm yellow	30
5mm green	30
5mm blue	30
5mm red	30
5mm purple	30
5mm pink	30
5mm orange	30
5mm silver	30
5mm gold	30
5mm black	30
5mm clear	30
5mm white	30
5mm yellow	30
5mm green	30
5mm blue	30
5mm red	30
5mm purple	30
5mm pink	30
5mm orange	30
5mm silver	30
5mm gold	30
5mm black	30
5mm clear	30
5mm white	30
5mm yellow	30
5mm green	3

# DIGEST

## Acorn Masters Some New Tricks

The continuing association between Acorn Computers Ltd and the BBC has been reinforced with the introduction of a new range of microcomputers called the Master Series.

Said to have been developed as a result of feedback from users of Acorn's BBC B microcomputer, the main machines in the new range are fully compatible with existing software and peripherals yet differ markedly from both the original BBC B and the recent B+ 128.

The foundation of the new range is the Master 128, an 8-bit, 65C12-based machine with 128K of RAM. It incorporates all the features of the BBC B plus a battery backed-up real time clock, improved graphics, and a suite of on-board software.

An internal expansion slot allows the Master 128 to be upgraded by the addition of a co-processor board. By adding a 65C102 processor board the 128 becomes the Master Turbo, an 8-bit machine which offers an extra 64K of memory and increased speed. Acorn say the Master Turbo beats all records for BASIC interpreting that they are aware of.

Adding an 80186 co-processor board to the Master 128 produces the Master 512, a sixteen bit machine with 512K of RAM which uses Digital Research's DOS-plus operating system to enable it to run MS-DOS software. This makes it compatible with a wide range of commercial

and professional software. It also comes complete with an Acorn mouse and Digital Research's GEM software including Gem Desk Top, Gem paint and Gem Write.

The top machine in the range is the Master Scientific which uses a 32016 co-processor board running at 8MHz. This provides 32-bit processing with 1Mbyte of RAM and hardware floating point support. It can handle a wide range of languages used in the engineering and scientific fields including Fortran 77, C, ISO Pascal and many others as well as BASIC.

The final member of the new range is the Master Econet Terminal, a modified version of the Master 128 which includes an Econet interface and the new Advanced Network Filing System. It excludes some of the features of the 128 which are not required on an Econet system and therefore costs about £100.00 less. Those who require full facilities plus Econet working can add an Econet upgrade board to the Master 128.

The external styling of the Master series is similar to that of the BBC B but the case is about 125mm (5") wider and is stepped so that the keyboard is lower than the rest of the case. The BBC B keyboard layout has been retained complete with ten function keys but a 20-key numeric pad has been added to the right of the main keyboard and the BREAK key incorporates a screw-



driver lock to prevent accidental operation.

Two sockets are provided which will accept Electron-style ROM cartridges of up to 256K and there are also three internal ROM expansion sockets, one of which takes 128K ROMS while the other two will accept 128K or 256K ROMs. In addition to the internal TUBE connection used for the upgrade boards there is also an external TUBE socket. This will allow the connection of second processors other than those on the upgrade boards, for example, one of the existing Z80 second processors. All of the other connections present on the BBC B and B+ are included and there is also a new audio output socket.

The suite of on-board software includes a VIEW-3 wordprocessor package, a VIEWSHEET spreadsheet and BASIC 4, an enhanced version of the BBC BASIC programming language. New graphics commands extend the range of facilities available on the BBC B to include colour mix-

ing and allow easier and faster graphics development and manipulation. 50 bytes of battery backed-up CMOS RAM is also provided, allowing power-up default conditions to be defined in a rather more comprehensive fashion than was possible using the keyboard links on the BBC B.

The Master 128 is available now and costs £499.00 including VAT. The Econet upgrade board for the 128 is also available now and costs £49.99 inclusive. The Master Econet Terminal should be available by the time you read this at a cost of £399.00 along with the Master Turbo upgrade board which will cost £125.00, both prices inclusive of VAT. The Master 512 upgrade board and the Master Scientific upgrade board will both become available during the second quarter of 1986 at prices which have yet to be announced.

Acorn Computers Ltd, Cambridge Technopark, 645 Newmarket Road, Cambridge CB5 8PD, tel 0223-214411.

## The Newrad Case

Those who have followed the saga of Newrad Instrument Cases Ltd will be interested to learn that the Sheriff of the High Court has taken walking possession of the company's assets.

Whilst this does not mean that the company has gone into liquidation it does imply that Newrad will not be able to fulfil orders or

make refunds in respect of orders already placed.

Under no circumstances should any further orders be placed with Newrad, nor should any money be sent to them for any other reason.

Unfortunately, it seems unlikely that those who have orders outstanding with Newrad will get either their goods or their money back. Readers who find themselves in this position are invited to contact us so that we can keep them informed should circumstances change.

Those who have ordered kits for the John Linsley Hood Audio Design amplifier from Newrad and have not received all of the parts may like to know that Hart Electronic Kits can supply the MOSFET transistors required. Their address is Penylan Mill, Oswestry, Shropshire SY10 9AF, tel 0691-652 894. None of the other components specified should prove difficult to obtain. The cases shown in the illustrations in the article were made by Newrad and are therefore no longer available, but cases with

similar dimensions can be obtained from a number of suppliers and should prove an acceptable alternative.

The printed circuit boards for the amplifiers have hitherto been available only from Newrad but we will shortly be able to supply them through our own PCB Service. We hope to include prices next month. Meanwhile, the complete series of articles has been reprinted in the Winter, 1985/6, issue of Electronics Digest and the boards can be obtained from them.

# COMPUTER WAREHOUSE

THE "ALLADIN'S" CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

1000's OF BARGAINS FOR CALLERS

## EX-STOCK INTEGRATED CIRCUITS

4164 200ns D RAMS 8 for £14.95 4116 300ns £1.50  
 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50  
 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95  
 27128 £5.50 6800 £2.50 6821 £1.00 68A09 £8.00  
 6B09 £10.00 8085 £5.50 8086 £15.00 8251 £7.00  
 8748 £15.00.

Thousands of IC's EX STOCK send SAE for list.

## RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa  
 A300 07191315 12v 3ah as RS 591-770 NEW £13.95  
 A300 07191312 6v 3ah as RS 591-360 NEW £9.95  
 A300 07191202 6.0-5v 1.8ah as RS 591-382 Ex Equip  
 £5.99 3.6v 100 mah PCB mount as RS 591-477 NEW £10.00

## DISK DRIVES

Japanese Half height, 80 track double sided disk drives by TEAC, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £125.00.  
 SUGART SA400 SS FH 35 TRK £55.00  
 SIEMANS FDD100 SS FH 40 TRK £75.00 carriage on 5 1/4" drives £5.50  
 Brand NEW metal cases with internal PSU etc for above drives, below cost!!!  
 DSKC 1 for 2 HH or 1 FH 5 1/4" drive £39.95 + pp £4.50 DSKC 2 for 1 HH or 1 FH 5 1/4" drive £29.95 + pp £4.50  
 8" Refurbished standard units.  
 SUGART 801 SS £175.00 + pp £8.50  
 SUGART 851 DS £250.00 + pp £8.50  
 DRE 7100 SS as seen £125.00  
 TWIN SUGART 851's in smart case, complete with PSU etc, £595.00  
 8" DRIVE PSU for 2 drive units £45.00

Hard Disk Drives  
 DRE/DIABLO Series 30 2.5 Mb front load, £525.00. Exchangeable version £295.00  
 ME3029 PSU for above £95.00  
 DIABLO 44/DRE4000A, B 5+5 Mb from £75.00  
 CDC HAWK 5+5 Mb £795.00  
 CDC 9782 80 Mb RM03 etc £2500.00  
 PERTEC D3422 5+5 Mb £495.00  
 RODIME 10MB ST506 Winchester NEW £299.00  
 BASF 6172 23Mb Winchester, as seen £199.00  
 Carriage on other drives £10.00.  
 Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

## MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets.  
 BRAND NEW State of the art products.  
 DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc £268.00  
 DACOM DSL2123AD Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer with flow control etc. £365.00  
 DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index buffer etc etc £498.00  
 SBBECK SB1212 V22 1200 baud FULL DUPLEX, sync or async, optional auto dial, £465.00  
 TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 £49.00

Ex. BRITISH TELECOM full spec, CCITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface.  
 DATED 2B 300 Baud Modem see SPECIAL OFFER.  
 MODEM 13A 300 baud unit, only 2" high fits under phone. CALL mode only £45.00  
 MODEM 20-1. 75-1200 baud. Compact unit for use as subscriber end to PRESTEL TELECOM GOLD, MICRONET etc £39.95 + pp £6.50  
 MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end. £65.00 + pp £6.50  
 DATED 2412 Made by SE labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc.  
 COST OVER £800 Our price ONLY £199 + pp £8.00  
 DATED 4800, RACAL MPS4800 baud modem, EX BT good working order, ONLY £295.00 + pp £8.00

SUMMER OFFER  
 MODEM TG2393. Ex BT, Up to 1200 baud, full duplex over 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR + pp £10.00

For more information CONTACT OUR SALES OFFICE

## HOT LINE DATA BASE



The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily.  
**ON LINE NOW.** CCITT, 8 bit word, no parity.  
 For 300 baud modems call 01-679 1888  
 For 1200-75 baud modems call 01-679 6183

## PRINTER / TERMINAL SCOOP

A MASSIVE purchase of these attractive stand alone terminal units enables a SUPER BARGAIN offer. Made by the US GENERAL ELECTRIC CORPORATION the GE MODEL 30 features a standard QWERTY 80 key electronic keyboard coupled to a quality built matrix printer with variable 3" to 9.5" forms tractor. The printer is capable of continuous duty printing, with up to 120 characters per line. Standard RS232 interface accepts ASCII data at 110, 150 or 300 baud. Ideal for Terminals, Data loggers, local label printing, or just as a printer! Sold TESTED with data ONLY £95.00. Also available with TWIN MAGTape CASSETTE unit for data capture, data preparation etc £150.00 Carriage £10.00.

## COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of COOLING FANS  
 ETRI 126L271 240v 5 blade equipment fan Dim. 80 x 80 x 38mm £9.95  
 ETRI 88XU01 Dim. 92 x 92 x 25mm 240v equipment fan, complete with finger guard NEW £9.95  
 GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240v operation. NEW £6.95.  
 BUHLER 69.11.22 8-16v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, also silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.  
 MUFFIN-CENTAUR standard 4" x 4" x 1.25" fans 110v OR 240v NEW at £10.50 or tested EX EQUIPMENT 240v £6.25 or 110v £4.95.  
 1000's of other fans Ex Stock.  
 Call for Details. Post & Packing on all fans £2.00.

## QWERTY KEYBOARDS

Manufacturer's BRAND NEW surplus.  
 ALPHAMERIC 7204/60 Full travel ASCII, 60 key with parallel output and strobe. £39.95  
 DEC LA34 Un-coded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc. £24.95  
 AMKEY MPNK-114 Super word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, Numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT!! ONLY £69.00 with data.



Carriage on all Keyboards £3.50

## PLESSEY VUTEL

Manufactured by PLESSEY Ltd this compact unit, only slightly larger than a telephone, features an all in one TELEPHONE, 24 x 40 character CRT screen, VIEWDATA - PRESTEL modem.  
 Keypad and electronics to run as a fully fledged PRESTEL terminal or telephone. Ready to plug direct into a BT 800 type jack socket and instantly connect you to PRESTEL etc. Many other features include Memory dialling, Recall button, Off line screen data storage, Picture expand, Standard Mullard LUCY chip set, Integral 5" JVC crt monitor, etc etc. Designed to sell to the EXECUTIVE at over £600!! But from DISPLAY, BRAND NEW AND BOXED at only £99.00 for DTMF tone dial or £140.00 for standard DIAL PULSE version. Carr. £8.00.

## COLOUR AND MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR made in the UK by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future monitor requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to the BBC and most other makes of micro computers and VCR's. An internal speaker and audio amplifier may be connected to your systems output or direct to a VCR machine, giving superior sound quality. Many other features included PIL tube, Matching BBC case colour, Major controls on front panel, Separate Contrast and Brightness - even in RGB mode, Two types of audio input, Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc etc.

This Must be ONE OF THE YEAR'S BEST BUYS  
 Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. SUPPLIED BELOW ACTUAL COST - ONLY £149.00

DECCA 80 16" COLOUR monitor. RGB input. Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of!! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the tried and tested DECCA 80 series TV chassis gives 80 column definition and picture quality found only on monitors costing 3 TIMES OUR PRICE. In fact, WE GUARANTEE you will be delighted with this product, the price for the price, has to be seen to be believed. Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, Modular construction, auto degaussing circuit, Attractive TEAK CASE, compact dimensions only 62cm W x 34 H x 24 D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition, ONLY £99.00 + Carr.

DECCA 80, 16" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.  
 REDIFFUSION MARK 3 20" Colour monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for shops, schools, clubs and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

## BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors.

All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for 80 column use on BBC micro etc. Even when MINOR screen burns exist - normal data displays are unaffected.  
 12" KGM 320-1 B/W high bandwidth input, will display up to 132 x 25 lines. £32.95  
 12" GREEN SCREEN version of KGM 320-1 Only £39.95  
 9" KGM 324 GREEN SCREEN fully cased very compact unit Only £55.00  
 9" HITACHI VM-906E/K Black and White screen £49.95  
 Carriage and insurance on all monitors £10.00

## D.C. POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 55a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £14.95  
 GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00  
 GREENDALE 19A-BOE Switch mode 60 watt open PCB with a fully regulated DC output of 5v @ 6 amps, and three semi regulated outputs of +12v, -12v +15v @ upto 1 amp. Dim only 11 cm x 20 cm x 5.5 cm. Similar to RS 591-994, 110 or 240v AC input. TESTED ex equipment. Only £24.95  
 ALL-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 110 or 240 V AC input. Dim 28 x 12.5 x 7 cm NEW £49.95.  
 Carriage on PSUs £3.00

## SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows US to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF ONLY £29.95. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

- 300 baud full duplex
- Full remote control
- CCITT tone standards
- Supplied with full data
- Modular construction
- Direct isolated connection
- CALL, ANSWER and AUTO modes
- Standard RS232 serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms. line

BT 600 Jack plug and cable £2.25 Carriage and Ins. £10.00

## VDU TERMINALS

Standard VDU data entry terminals at give away prices!  
 QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" green screen, 2 page RAM, TVI 925 emulation, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00  
 AJS150 - EX RENTAL 280 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00.  
 ADS 520 - Dumb terminal used, 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00  
 Carriage on terminals £10.00  
 100's of other terminals in stock, CALL for more details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please add £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF  
 Telephone 01-679 4414 Telex 894502 Data 01-679 1888



## GrunDig For Victory




As part of the efforts by the new Grundig management to revive the company's flagging fortunes, a new range of video products has been announced.

The VS380 hi-fi stereo video recorder has reached the market after some delay. Like its smaller sister, the mono VS310, the 380 is a VHS machine offering 40 channels and up to ten pre-programmable events. The usual advanced features are included, and the 380 also offers 'longplay' which doubles effective tape time to 8 hours. Both machines feature the new Auto Tape Time Select (ATTS) tape counter system

which measures the exit and entry angles of the tape from and to its cassette and uses a microprocessor to calculate and display tape time used and remaining.

As if to demonstrate their firm commitment to the VHS system, Grundig have also released their first VHS camcorder, the VS150, which uses standard cassettes and features autofocus, 6:1 motor zoom, electronic assemble editing and record review. The VS150 weighs 2.5kg, without its accumulator and sells for around £1350. The VS310 is priced at around £440 and the VS380 at around £650.

## Smooth Con Merchants

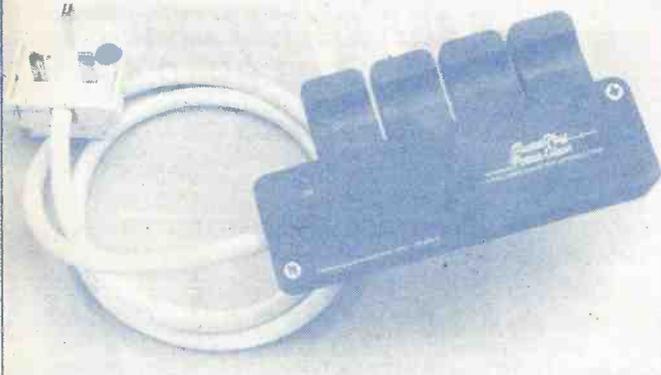

A Welsh company, Conblock Electrical, are supplying a four outlet, domestic mains filter for use with home computer systems. The unit plugs into a standard 13A socket and is rated at 6A maximum.

Attractively styled in grey moulded polycarbonate, the Smoothline costs no more than a couple of computer games,' say Conblock, 'and allows the enthusiasts to almost totally eliminate

system problems caused by interference transmitted via the mains supply.'

The unit is supplied complete with mains lead, mains plug and four miniature plugs for connections to a computer and various peripherals.

Contact: Conblock Electrical Ltd., Mochdre Industrial Estate, Newtown, Powys SY16 4LF (tel: 0686-27100).

## EPSON-Line

Purchasers of new Epson computers and printers will receive free membership of EpsomLink, an electronic mail service run on Telecom Gold. EpsomLink promises next-day delivery anywhere in the UK or USA and also allows users to transmit to any Telex terminal in the World without Telex equipment. The system also allows users to receive information from several databases not subscribed to directly. It is aimed particularly at the users of portable computers, which Epson specialise in.

## Not Disc-ontinued

Way back in our January 1986 issue (you know, the one that came out in December 1985) we offered a twin 3½in disc drive unit in conjunction with Watford Electronics at a special price.

Unfortunately, our February 1986 issue (which should come out in January but is printed in December to avoid the Christmas holidays) was distributed almost as soon as it was printed, appearing on some news-stands as early as the 19th December. As a result, the January issue (which comes out in December, remember) was on sale for less than two weeks and many people missed it (if all this sounds confusing to you, think how much worse it is for us as we sit here, in January, writing the March issue (which comes out in February) and planning the April issue).


Because so many people missed the January issue, we have decided to extend the period for which the Watford disc drive offer is available.

The unit consists of two 3½" 80 track, double-sided, double density disc drives in a steel case which is coloured and styled to match the BBC microcomputer. The disc drives will work with other machines, of course, but they are provided with leads ready for direct connection to a BBC and come with a free utility disc containing a game for the BBC. The capacity of the drives is two megabytes total unformatted which represents 327K per side formatted.

The cost of the twin disc drive unit is £140.00 plus VAT, a total of £161.00. Postage and packing is included in this price. Cheques should be made payable to Watford Electronics and sent to us at the address on the contents page. Please mark envelopes ETI(DD) to ensure prompt attention.
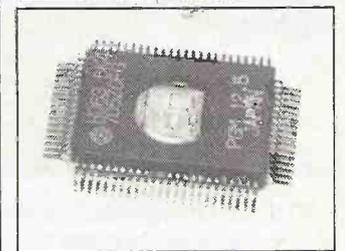
## Be A PAL

Copies of the latest edition of the Monolith Memories Programmable Logic Handbook are available free from MMI. The catalogue includes PAL and Programmable Logic Elements applications and data sheets and a number of technical articles that might be of interest. The catalogue can be obtained from Monolith Memories Ltd., Monolithic House, 1 Queens Road, Farnborough, Hants. GU14 6DJ (tel: 0252-517431).



## SeePROM

The latest addition to Hitachi's growing range of CMOS microcomputer chips is a single-chip device including an 8-bit microprocessor, 8k of EPROM and an 8 channel by 8-bit ADC on board. Hitachi say that the HD63705Z also features a serial communications interface, 8 parallel I/O lines and 8 interrupt lines. The chip is supplied in an 80-pin flat-pack for surface mounting and, in one version, includes a window for UV erasing.

Further details from Hitachi Electronic Components (UK) Ltd., Hitec House, 221-225 Station Road, Harrow, Middlesex HA1 2XL (tel: 01-861 1414).

- Caddis Systems have been appointed distributors for RETEX enclosures. The range includes a variety of styles and sizes including the ABOX (ABS enclosure with sloping anodised aluminium front panel, taking standard Euro-cards), the ELBOX (ABS with a steel sub-frame and slope-back feet) and SOLBOX-2 (steel enclosure with aluminium front panel, optional handled, louvred ventilation and slope-back feet). Caddis can be contacted at 5 Keats Close, Maldon, Essex, CM9 6DB (tel: 0621 55116).

- Marco Trading have produced a component catalogue for 1986 which includes a reasonable range of items, some at notably low price. The catalogue comes complete with a six page special offer list and a 50p credit note. It costs £1.00 from Marco Trading, The Maltings, High Street, Wem, Shropshire SY4 5EN (tel: 0939 32763).

# Cortex

**HARDWARE  
SOFTWARE**

**Operative Systems**

MDEX Professional Dev. System £95  
CORTX POWER-BASIC disc extensions: CDOS £43

**MDEX Extensions**

FORTH with Screen editor assembler £55  
- Graphic extensions £35  
PASCAL by Pre Brinch Hansen £85  
QBASIC Compatible with  
CPM CBASIC - only complied! £150  
WINDOW Full screen editor £150

**CORTX LISTINGS/CDOS DISCS**

PENGO, BLUE-BIRD, GOLF £13  
SPACE-BUGS, BREAKOUT, PONTOON, MICROPEDE £13  
CDOS WORD PROCESSOR (DISC ONLY) £13  
DRAWTECH (DISC ONLY) £43


**DISC DRIVES**

80 Track half height, double sided, double density IM £125  
40 Track half height, single sided, double density 256K £110

**E-Bus cards**

9995 Processor Board	Blank + PAL'S	£52
	Built	£175
64/128k RAM Card	Blank + PAL	£42
	Built	£145/245
Floppy/Winchester Interface Card	Blank	£32
	Built	£135
Joystick/Centromes/Timer Board	Blank	£13
	Part kit	£36
	Full kit	£43

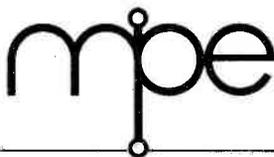**LIMITED OFFER ONLY: 9909's**  
STATE DISC FORMAT & ADD VAT TO ALL PRICES




**MicroProcessor Eng Ltd**  
21 Hanley Road · Shirley  
Southampton · SO1 5AP  
Tel: 0703 780084

Interak 1
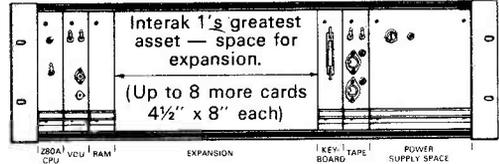
## A METAL Z80A COMPUTER

Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from £10.95 to £19.95 + VAT; manuals £1.15.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletter etc. No fears about this one going obsolete — now in its sixth successful year! Send us your name and address with 24p stamps and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work! Interak, Interak, Interak!

**Greenbank**

Greenbank Electronics (Dept. T3E), New Chester Road,  
New Ferry, Wirral, Merseyside L62 5AG  
Telephone: 051-645 3391

**BEST PRICE DEVICES**

ALL THE LATEST FASTEST DEVICES NOT TO BE CONFUSED WITH SLOWER OLD STOCK OFFERED ELSEWHERE

**DRAM**

5v NMOS 150ns  
4164 64k x 1 ..... £0.95  
41256 256k x 1 ..... £2.80  
4416 16k x 4 ..... £2.95  
41254 64k x 4 ..... £5.90

**SRAM**

5v CMOS 250ns + .....  
6116 2k x 8 ..... £1.49  
6264 8k x 8 ..... £3.19

**LINEAR**

BIFETS	Each	5 OFF
TL072CP	50p	£2.10
TL074CN	80p	£3.50
TL082CP	40p	£1.80
TL084CP	85p	£3.50

**EPROM**

5v NMOS 250ns  
2716 2k x 8 ..... £2.95  
2732 4k x 8 ..... £2.75  
2764 8k x 8 ..... £1.95  
27128 16k x 8 ..... £2.85  
27256 32k x 8 ..... £4.50  
5v CMOS 250ns  
27C64 8k x 8 ..... £8.50  
27C256 32k x 8 ..... £15.00

**OTHER LINEAR**

NE555	19p	£0.90
LM311P	39p	£1.80
LM324	39p	£1.80
LM348N	39p	£1.80
LM358	39p	£1.80
SN75154N	95p	£4.50
OP07CP	£1.20	£5.00

ORDERS OVER £25 DEDUCT 10% DISCOUNT ADD 15% V.A.T. POST FREE  
ORDERS UNDER £25 ADD 15% V.A.T. PLUS 50p P&P. Lists of other offers processors etc. sent DESPATCH BY RETURN TO C.W.O.

**MICROKIT LIMITED**  
MANOR PARK, RAUNDS,  
NORTHANTS NN9 6PD

### MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio and TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Electrical Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
<b>GCE</b> over 40 'O' and 'A' level subjects <input type="checkbox"/>	

**ICS** Name \_\_\_\_\_ P. Code \_\_\_\_\_  
Address \_\_\_\_\_  
International Correspondence Schools, Dept 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (24hrs).

**For KITS & COMPONENTS - Choose the easy way - with**



Send now -  
for our **FREE CATALOGUE**  
Or ring: 01-567 8910 for  
the keenest prices on -

- |        |                |          |
|--------|----------------|----------|
| CMOS   | TRANSFORMERS   | BOOKS    |
| TTL    | CONNECTORS     | TOOLS    |
| OPTO   | MICROPROCESSOR | BOXES    |
| TRIACS | HEATSINKS      | RELAYS   |
| HICADS | MULTIMETERS    | SWITCHES |

**AND LOTS LOTS MORE**

We also **STOCK** over 30 **KITS** for Timers, Remote Control, Disco Lights, Temperature Control, etc. **PLUS** a wide range of **VELLEMAN** and **PANTEC KITS**.

Any questions please ring **BART TREPAK** on 01-579 9794.

**TR ELECTRONICS**  
13 BOSTON RD  
LONDON W1 3SJ  
SEND 9" x 6" SAE OR CALL AT SHOP  
MON-FRI 9-5pm  
SATURDAY 10-4pm

**FREE P&P** on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P. Europe £2.75. Elsewhere £6.50. Giro No. 529314002. **SCHOOL OR LOCAL AUTHORITY ORDERS WELCOME.** Goods by return subject to availability.

## DIARY

### Electronics In Oil and Gas — February 4-6th

Barbican, London. See November '85 ETI or contact Cahners at the address below.

### Intellectual Property and Patents — February 18th

Institute of Physics, London. One-day meeting. For details and registration forms contact The Meetings officer of the IoP at the address below.

### Power UK '86 — March 4-6th

Kensington Exhibition Centre, London. Exhibition and conference devoted to power supplies and alternative power sources. Organised by the Power Supply Manufacturers Association. For details contact TCM Expositions Ltd, Exchange House, 33 Station Road, Liphook, Hampshire GU30 7DN, tel 0428-724 660.

### Electronic Production Efficiency Exposition — March 11-13th

Olympia, London. See November '85 ETI or contact Cahners at the address below.

### Electro-Optics/Laser International — March 18-20th

Metropole Convention Centre, Brighton. Exhibition and conference on optics and lasers which includes a special focus on fibre optics. For details contact Cahners at the address below.

### Low Energy Ion Beams — April 7-10th

University of Sussex, Falmer, Brighton. Conference on the production and use of ion beams, covering such areas as semiconductor processing and machining and material modification in metals and insulators. There will also be an exhibition of related equipment. For details contact the Meetings Officer of the IoP at the address below.

### Electrical Insulation Conference — May 19-22nd.

Brighton. International conference described by the organisers as the premier event in its field. For details contact the British Electrotechnical and Allied Manufacturers Association, Leicester House, 8 Leicester Street, London WC2H 7BN, tel 01-437 0678.

### Advanced Infrared Detectors And Systems — June 3-5th

Institution of Electrical Engineers, London. Conference which aims to cover the developments in infrared detectors, systems and techniques and their relationship to developments in the field of millimetre waves. For details contact the IEE, Savoy Place, London WC2R 0BL, tel 01-240 1871.

### Networks '86 — June 10-12th

Wembley Conference Centre, London. Exhibition and conference devoted to all aspects of data exchange networks. For details contact Online Conferences Ltd, Pinner Green House, Ash Hill Drive, Pinner, Middlesex HA5 2AE, tel 01-868 4466.

### Northern Computer Show — June 24-26th

G-MEX Exhibition Centre, Manchester. Exhibition aimed at professional computer users, from professionals in user departments to computing specialists. For details contact Reed Exhibitions, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ, tel 01-643 8040.

### KBS '86 — July 1-3rd

Wembley Conference Centre, London. Exhibition and conference devoted to knowledge based systems. Contact Online at the address below.

### Voice Processing — July 1-3rd


Tara Hotel, London. Conference. For details contact Online at the address below.

### Addresses:

Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham, Middlesex TW1 3SZ, tel 01-891 5051.

Institute of Physics, 47 Belgrave Square, London SW1X 8QZ, tel 01-255 6111.

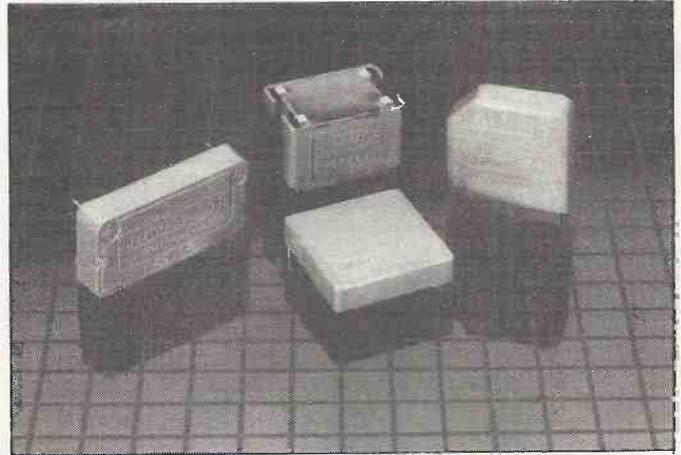Online Conferences Ltd, Pinner Green House, Ash Hill Drive, Pinner, Middlesex HA5 2AE, tel 01-868 4466.



## Getting Your Back Up

**B**attery backed-up memory is becoming increasingly important in microprocessor applications and can often be the most effective and efficient means of non-volatile data storage. Direct PCB mounting batteries are an attractive option where space is at a premium. A new range of batteries from the French company SAFT should meet most requirements.

The batteries are produced in upright or flat packs for either a small footprint or a low profile and the range includes rechargeable Ni-Cads and non-rechargeable lithium batteries with an operating life of up to 10 years.

The Ni-Cads are produced in versions with nominal voltages of 2.4 and 3.6 and capacities of either 40 mA/h or 100 mA/h. The smaller capacity batteries require a trickle-charging current of 2mA, while the larger capacity versions need 4mA. The upright Ni-Cads are only available at 3V6.

The SAFT lithium batteries are produced in both upright and low profile packages, but only in a 3V0, 200 mA/h version.

The range is supplied by MS Components Ltd., Zephyr House, Waring Street, West Norwood, London SE27 9LH (tel: 01-670 4466).

- Mullard have announced a SECAM to PAL converter which distinguishes between SECAM and PAL signals, passing PAL directly to the chroma output but converting SECAM signals into PAL standard before output. The transcoder, as it is called, contains all necessary circuitry on a single chip, the TDA3592A, and operates by demodulating the SECAM signal and remodulating it in PAL format. The output is, therefore, a true PAL signal and the chip can be used with any PAL decoders in monitors, VCRs and video cameras as well as televisions.

Contact: Mullard Ltd., Mullard House, Torrington Place, London WC1E 7HD (tel: 01-580 663).

- The new short form catalogue from British transistor manufacturers, Semelab, has been expanded to include devices distributed by the company as well as made by them. The catalogue also lists a range of USA replacement types and gives basic data and device characteristics. It is available free from Semelab Ltd., Coventry Road, Lutterworth, Leics. LE17 4JB (tel: 04555-56565).

- Pineapple Software have released a circuit-drawing program for the BBC micro. The program is called DIAGRAM and covers 39 screens in Mode 0 (high resolution). Individual screens operate as windows on this larger logical screen. The program supports printouts on most dot matrix printers in a variety of print sizes and can also be used to produce PCB layouts. DIAGRAM is supplied on 5¼ inch disc and costs £28.75 from Pineapple Software, 39 Brownlea Gardens, Seven Kings, Ilford, Essex IG3 9NL (tel: 01-599 1476).

- Halley's Comet disappears below the UK horizon on 31st March. Throughout March, it can be seen in Sagittarius having reappeared after its closest pass to the sun (perihelion) on 20th February before sunrise in the east at magnitude +3. Information from the European Space Research Unit, thanks to Oscar News, the magazine of AMSAT-UK, the Radio Amateur Satellite Organisation of the UK. Contact Ron Broadbent G3AAJ, 94 Herongate Road, Wanstead Park, London E12 5EQ (tel: 01-989 6741).

ETI

ETI



**74 SERIES** **LINEAR ICs** **COMPUTER COMPONENTS**

7400	30p	74181	340p	74LS162A	75p	74S08	50p	4063	85p
7401	30p	74182	140p	74LS163A	75p	74S10	50p	4066	85p
7402	30p	74183	180p	74LS164	75p	74S11	75p	4067	230p
7403	30p	74184	180p	74LS165A	110p	74S12	50p	4068	25p
7404	30p	74185	130p	74LS166A	130p	74S22	50p	4069	24p
7405	30p	74186	130p	74LS167	130p	74S30	50p	4070	24p
7406	30p	74187	110p	74LS168	100p	74S32	50p	4071	24p
7407	40p	74188	110p	74LS169	140p	74S37	60p	4072	24p
7408	40p	74189	110p	74LS170	100p	74S38	60p	4073	24p
7409	40p	74190	80p	74LS171A	75p	74S40	50p	4075	24p
7410	30p	74191	130p	74LS172	75p	74S51	45p	4076	65p
7411	30p	74192	130p	74LS173	200p	74S64	45p	4077	25p
7412	30p	74193	220p	74LS174	190p	74S74	70p	4078	25p
7413	30p	74194	110p	74LS175	75p	74S85	30p	4081	24p
7414	30p	74195	110p	74LS176	75p	74S86	100p	4082	25p
7415	30p	74196	100p	74LS177	80p	74S112	100p	4085	60p
7416	30p	74197	150p	74LS178	80p	74S113	120p	4086	75p
7417	30p	74198	300p	74LS179A	75p	74S114	120p	4089	120p
7418	30p	74199	200p	74LS180	75p	74S124	300p	4093	35p
7419	30p	74200	140p	74LS181	80p	74S132	100p	4094	90p
7420	30p	74201	170p	74LS182	80p	74S133	100p	4095	90p
7421	30p	74202	170p	74LS183	80p	74S138	180p	4096	90p
7422	30p	74203	170p	74LS184	80p	74S138	180p	4097	270p
7423	30p	74204	170p	74LS185	80p	74S139	180p	4098	75p
7424	30p	74205	170p	74LS186	80p	74S140	100p	4099	90p
7425	30p	74206	170p	74LS187	80p	74S151	150p	4501	36p
7426	30p	74207	170p	74LS188	80p	74S153	150p	4502	55p
7427	30p	74208	170p	74LS189	80p	74S157	200p	4503	95p
7428	30p	74209	170p	74LS190	80p	74S158	200p	4504	36p
7429	30p	74210	170p	74LS191	80p	74S183	300p	4505	360p
7430	30p	74211	170p	74LS192	80p	74S183	300p	4506	90p
7431	30p	74212	170p	74LS193	80p	74S175	320p	4507/4030	
7432	30p	74213	170p	74LS194	80p	74S175	320p		
7433	30p	74214	170p	74LS195	80p	74S188	180p	4508	120p
7434	30p	74215	170p	74LS196	80p	74S188	180p	4509	120p
7435	30p	74216	170p	74LS197	80p	74S194	300p	4510	55p
7436	30p	74217	170p	74LS198	80p	74S194	300p	4511	55p
7437	30p	74218	170p	74LS199	80p	74S196	300p	4512	55p
7438	30p	74219	170p	74LS200	80p	74S196	350p	4513	150p
7439	30p	74220	170p	74LS201	80p	74S201	350p	4514	110p
7440	30p	74221	170p	74LS202	80p	74S201	350p	4515	110p
7441	30p	74222	170p	74LS203	80p	74S201	350p	4516	55p
7442	30p	74223	170p	74LS204	80p	74S201	350p	4517	220p
7443	30p	74224	170p	74LS205	80p	74S201	350p	4518	48p
7444	30p	74225	170p	74LS206	80p	74S201	350p	4519	48p
7445	30p	74226	170p	74LS207	80p	74S201	350p	4520	60p
7446	30p	74227	170p	74LS208	80p	74S201	350p	4521	115p
7447	30p	74228	170p	74LS209	80p	74S201	350p	4522	70p
7448	30p	74229	170p	74LS210	80p	74S201	350p	4523	80p
7449	30p	74230	170p	74LS211	80p	74S201	350p	4524	80p
7450	30p	74231	170p	74LS212	80p	74S201	350p	4525	80p
7451	30p	74232	170p	74LS213	80p	74S201	350p	4526	80p
7452	30p	74233	170p	74LS214	80p	74S201	350p	4527	80p
7453	30p	74234	170p	74LS215	80p	74S201	350p	4528	80p
7454	30p	74235	170p	74LS216	80p	74S201	350p	4529	80p
7455	30p	74236	170p	74LS217	80p	74S201	350p	4530	80p
7456	30p	74237	170p	74LS218	80p	74S201	350p	4531	80p
7457	30p	74238	170p	74LS219	80p	74S201	350p	4532	80p
7458	30p	74239	170p	74LS220	80p	74S201	350p	4533	80p
7459	30p	74240	170p	74LS221	80p	74S201	350p	4534	80p
7460	30p	74241	170p	74LS222	80p	74S201	350p	4535	80p
7461	30p	74242	170p	74LS223	80p	74S201	350p	4536	80p
7462	30p	74243	170p	74LS224	80p	74S201	350p	4537	80p
7463	30p	74244	170p	74LS225	80p	74S201	350p	4538	80p
7464	30p	74245	170p	74LS226	80p	74S201	350p	4539	80p
7465	30p	74246	170p	74LS227	80p	74S201	350p	4540	80p
7466	30p	74247	170p	74LS228	80p	74S201	350p	4541	80p
7467	30p	74248	170p	74LS229	80p	74S201	350p	4542	80p
7468	30p	74249	170p	74LS230	80p	74S201	350p	4543	80p
7469	30p	74250	170p	74LS231	80p	74S201	350p	4544	80p
7470	30p	74251	170p	74LS232	80p	74S201	350p	4545	80p
7471	30p	74252	170p	74LS233	80p	74S201	350p	4546	80p
7472	30p	74253	170p	74LS234	80p	74S201	350p	4547	80p
7473	30p	74254	170p	74LS235	80p	74S201	350p	4548	80p
7474	30p	74255	170p	74LS236	80p	74S201	350p	4549	80p
7475	30p	74256	170p	74LS237	80p	74S201	350p	4550	80p
7476	30p	74257	170p	74LS238	80p	74S201	350p	4551	80p
7477	30p	74258	170p	74LS239	80p	74S201	350p	4552	80p
7478	30p	74259	170p	74LS240	80p	74S201	350p	4553	80p
7479	30p	74260	170p	74LS241	80p	74S201	350p	4554	80p
7480	30p	74261	170p	74LS242	80p	74S201	350p	4555	80p
7481	30p	74262	170p	74LS243	80p	74S201	350p	4556	80p
7482	30p	74263	170p	74LS244	80p	74S201	350p	4557	80p
7483	30p	74264	170p	74LS245	80p	74S201	350p	4558	80p
7484	30p	74265	170p	74LS246	80p	74S201	350p	4559	80p
7485	30p	74266	170p	74LS247	80p	74S201	350p	4560	80p
7486	30p	74267	170p	74LS248	80p	74S201	350p	4561	80p
7487	30p	74268	170p	74LS249	80p	74S201	350p	4562	80p
7488	30p	74269	170p	74LS250	80p	74S201	350p	4563	80p
7489	30p	74270	170p	74LS251	80p	74S201	350p	4564	80p
7490	30p	74271	170p	74LS252	80p	74S201	350p	4565	80p
7491	30p	74272	170p	74LS253	80p	74S201	350p	4566	80p
7492	30p	74273	170p	74LS254	80p	74S201	350p	4567	80p
7493	30p	74274	170p	74LS255	80p	74S201	350p	4568	80p
7494	30p	74275	170p	74LS256	80p	74S201	350p	4569	80p
7495	30p	74276	170p	74LS257	80p	74S201	350p	4570	80p
7496	30p	74277	170p	74LS258	80p	74S201	350p	4571	80p
7497	30p	74278	170p	74LS259	80p	74S201	350p	4572	80p
7498	30p	74279	170p	74LS260	80p	74S201	350p	4573	80p
7499	30p	74280	170p	74LS261	80p	74S201	350p	4574	80p
7500	30p	74281	170p	74LS262	80p	74S201	350p	4575	80p

A07561	£18	LM309	350p	TBA231	130p
ADC0808	1190p	LM309A	350p	TBA800	80p
AM7910DC	230p	LM710	48p	TBA810	50p
AN103	320p	LM711	100p	TBA820	50p
AV-1-5000	100p	LM723	100p	TBA820M	75p
AV-3-1800	300p	LM725CN	300p	TBA820	250p
AV-S-2010	100p	LM725	300p	TBA860	50p
AV-3-8812	80p	LM741	22p	TC109	500p
CA3019A	110p	LM747	70p	TC210	380p
CA3028A	110p	LM748	30p	TC220	380p
CA3045	110p	LM1011	100p	TC240	175p
CA3059	320p	LM1014	100p	TC240	175p
CA3090	80p	LM1801	300p	TD1A1022	250p
CA3090E	80p	LM1802	300p	TD1A1022	250p
CA3090E	80p	LM1803	300p	TD1A1022	250p
CA3090E	80p	LM1871	300p	TD1A1705	300p
CA3090E	80p	LM1872	300p	TD2A002	320p
CA3090E	80p	LM1886	550p	TD2A003	180p
CA3090E	80p	LM1888	480p	TD2A006	240p
CA3130T	130p	LM2917	100p	TD2A006	240p
CA3140E	48p	LM3302	300p	TD2A020	320p
CA3150	100p	LM3303	300p	TD2A020	320p
CA3161E	200p	LM3308	100p	TD2A293	800p
CA3162A	200p	LM3311	180p	TD2A310	750p
CA3240E	180p	LM3314	180p	TD2A700	380p
CA3290G	27p	LM3315	340p	TD1A1002	700p
D7002	27p	LM13610	150p	TL062	60p
DAC108-8	80p	LM1518L	48p	TL071	50p
DAC0800	300p	MS3712	200p	TL072	70p
DAC0800	300p	MC1310P	150p	TL074	110p
DG908	300p	MC14143	75p	TL081	35p
HA1368	190p	MC1458	48p	TL082	55p
ICL7106	67p	MC1465L	300p	TL083	75p
ICL7611	95p	MC1468	70p	TL094	250p
ICL7660	400p	MC1469	200p	TL104	250p
ICL7680	300p	MC3401	70p	TL170	50p
ICL8038	400p	MC3403	85p	UAA1003-3	50p
ICM7216B	22p	MF10CN	300p	UA759	300p
ICM7217	750p	MK52040	800p	UA240	120p
ICM7555	80p	MK50398	790p	UA170	7

# READ/WRITE

## Social Consequences

Dear Sir,

I feel I must reply to Joseph Michael's letter (ETI, January 1986) concerning the inclusion in ETI of articles with political aspects. If I understand Mr. Michael's rather garbled argument correctly, he is presenting an attitude which is, in my opinion, untenable. In the interests of brevity, and in order not to appear too didactic, I will make three simple points.

Firstly, those of us who are scientists or technicians of some description have a responsibility to pay heed to the social consequences of our work, a point which Alfred Nobel realised. How can we do this if we are not kept informed of how science and technology is (allegedly) being used?

Secondly, although as Mr. Michael says, 'Many hours of politics are screened on television each day' it is devoid of hard technical data, aimed as it is at an audience most of whom would not understand such details. What better forum for these details than a technical publication like ETI?

Thirdly, these articles do not pose a threat to the conventional contents of the magazine, as Mr. Michael seems to imply. The Greenham piece took up only half a page in an issue of sixty-six pages! Anyone who wished to ignore it could do so with ease.

In conclusion, I look forward to many thought-provoking future articles about the wider implications of electronics.

Yours faithfully,  
Malcolm Ray,  
London NW6

Dear Sir,

On return from a trip abroad I welcomed the opportunity to peruse Dec. and Jan. issues of the magazine. After reading of Greenham Common and your reply to the letter from Sgt. R. Hailstones I have informed my newsagent to cancel my subscription.

I have no wish to encourage you to monitor any aspect of one of our defence establishments.

Yours faithfully,  
C. H. Hargreaves,  
Manchester.

The idea that 'our defence establishments' are above monitoring, I find frankly appalling. They are, I believe, there to defend us and, what's more, they hold the power to destroy millions of us and millions of our fellow human beings. If any institutions should be monitored as a matter of course, surely it is them. Like it or not, ETI belongs to the family of the media and the responsible members of this family should represent the interests of concerned citizens. Electronics is a hobby or a career for just about all our readers, but it is also an instrument of warfare (or, if your prefer, defence). I think it absolutely right and proper that ETI and its readers should be aware of this. Incidentally, the abandonment of the dual-key policy with regard to cruise missiles means that the Greenham base can hardly be described as 'one of our defence establishments.' The decision to deploy the missiles sited there will, if that dreadful day ever comes, be entirely in the hands of the American Armed Forces. — Ed.

## Alf — A Bet!


Dear Alf

I spend a great deal of time doing puzzles of one sort or another, and enjoy yours very much. However, I think I've spotted a mistake in your solution in the January issue: the answer '(9R + 4R) // Alf' should read '9R + (4R // Alf)', with a similar amendment to the following line.

I wonder if you've ever come across the old favourite about the cube of one-ohm resistors? Twelve one-ohm resistors are wired together in the form of a cube and the problem is to determine the resistance between any two diagonally opposite corners; for

instance, between point A and G in Fig. 1. A solution by the usual series and parallel resistor calculations is possible, but there is a much easier way.

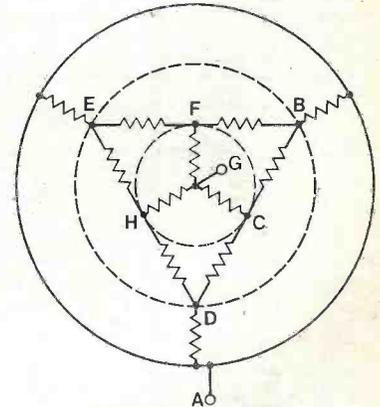
From the symmetry of the cube, it is easy to see that the voltages at points E, D and B will all be the same, no matter what signal may be applied to points A and G. A similar argument applies to the voltages at points H, F and C, which will also be equal to each other. If the symmetry is not obvious from Fig. 1, the same resistor network is shown rearranged in Fig. 2 to make it clearer.



If the voltages at any two points in a circuit are equal, it can make no difference at all to the operation of the circuit if the points are shorted together, since no current will flow through the link. Therefore, points E, D and B can be joined together, and so can points H, F and C, as shown by the dotted lines in Fig. 2. With these links in place, the resistance of the cube can easily be calculated: it is  $1/30\text{ohm} + 1/6\text{ohm} + 1/3\text{ohm} = 5/6\text{ohm}$ .

Yours sincerely,  
Chris Finn,  
Beverley.

Thank you for writing, it's not often I get a letter to myself, not being appreciated around here like I should. I can't speak about the brackets, not actually writing the puzzles myself, it's Auntie know-it-all Static to blame for that. She probably has a degree in brackets, I shouldn't be surprised. How would you like it if everytime you made a mistake, old smarty pants let the whole world know about it? The puzzles would be a darn sight better if I did write them, I could tell you a few things about

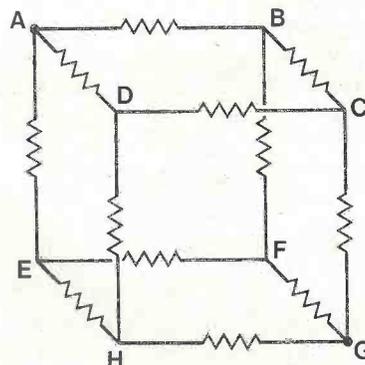

Auntie's rust spots and flea byte's wooden head. I hope they don't see this letter. Anyway, thanks again for the letter, and if you've got a puzzle that will really tie old smarty pants in knots, just send it along and then we'll see. — Alf.

P.S. Auntie Static writes: Any student of bracketology will realise that Chris is right. I blame the editor. — Auntie.

P.P.S. The Editor writes: That's enough about brackets (or parentheses, (for that matter)). — Ed.

## Scope For Improvement

Dear Sir,

I am interested in building the ETI Oscilloscope (May-July, 1982, and February, 1983) and as informed in the February 1983 issue, I sent a PO for £2 to obtain the pot core (ET30) from Neosid. This PO was sent in early August. Up to now, I have not received the pot core. Please clarify. I have not got any sort of acknowledgement from Neosid.

It was mentioned that other pot cores may not work because a large inductance factor is needed. What is the inductance factor — perhaps Siemens or others may have one suitable? Please advise.

Finally, please note, I have written many times on previous occasions and have got no replies. Please break your habit in this case!

Yours faithfully

K. G. Vergis,  
Malaysia.

Since the design was published, Neosid have become trade suppliers only. They will not supply individual orders for the ET30 but they should, of course, return your postal order. Unfortunately, we have no specifications for the pot core used in the design. All is not lost, however. We have received a number of queries like Mr. Vergis's and — as a result — the relevant parts of the circuit are being redesigned around a more readily available inductor. The revised design will be published towards the middle of this year. — Ed.

## 2001 Revisited

Dear Sir,

Reference ETI, September 1985, and the Cortex I/O article. Your circuit for the 74LS2001 has an error. Header pin 2 should be the output and pin 16 the input of IC2. By the way, if you have any info on the internals of the 74LS2001 or know where I can get info. on it, I would be grateful.

ETI MARCH 1986

I built the header circuit (modified as above) and it works okay. I built mine a bit more compact than that suggested in your article — on a 20 pin DIL header (soldering the board directly on to pins 11 to 20 of the header and mounting IC2 about IC1)

Yours,  
Mike Gallagher  
Rugby.

Thanks for the correction, which will go straight into OOPS! As for the 2001 we can only suggest you get in touch with Richard Roberts at Microprocessor Engineering, 21 Hanley Road, Shirley, Southampton SO1 5AP (0703 780084). — Ed.

## Cri De Constructor

Dear Mr. Editor, Sir!

I am writing to you in hope that you might be able to help me get some components for the Barry Porter Modular Preamplifier (ETI, December 1983, January and February, 1984). Your were able to help before when I was building the System A Power Amps — which are still going strong and love CDs.

I need two sets of parts for the disc amps (I received the PCs from you) and a friend in the UK has been unable to contact XL Audio Parts either by phone or letter. They may have moved again or folded. I would be grateful if you could help with an address.

Incidentally the headphone amp sounds great (with mods to PCB and using TIP41/42Cs).

If XL don't exist anymore, be so kind as to suggest someone else.

Thanks,  
John Alderton,  
Republic of South Africa

XL have proved to be elusive for a number of readers. NP Electronics, The Mill House, Watlington, Kings Lynn, Norfolk PE38 9DW (tel: 0553 — 810 096) have offered to supply kits of the non-polarised electrolytic capacitors and none of the other components should present many problems. By the way, 'Mr. Editor, Sir' strikes just about the right note. Keep it up. — Ed.

Dear Sir,

In your July and August, 1984, editions of your magazine you featured a printer buffer kit. In Zimbabwe we do not have ready suppliers of electronic components

and I would like to make up two of the above buffers, is there any supplier that you know of who could assist in making up the kits and at the same time give me some advice on connections, firstly to a Commodore which has only an RS232 interface and secondly to a Nascom 2. The printer in both cases has a Centronics interface. Will I require an additional adaptor for the Commodore to accept the Centronics interface?

Your assistance is appreciated.

Yours faithfully

P. Squair,  
Zimbabwe.

I presume you are talking about a Commodore 64, in which case the answer to that query is that you will definitely require a lead to connect the 64 user port to the printer Centronics input. You may also require some software, although most commercial programs include the routines as standard and, in any case, the routines are not complicated if you know how to handle the 64 user port. For further information and advice, contact the PCB and EPROM supplier, Tronik Designs, 68A Broomfield Avenue, Palmers Green, London N13 4JP. Cables and software for the 64 can be obtained from 64 Supplies Company, PO Box 19, Whitstable, Kent CT5 1TJ. — Ed.

Dear Sir or Madam,

I wish to construct a Digital Cassette Deck such as is described in your issue of ETI for September 1984, page 27, for computer use.

Could you please inform me where I can obtain the Tanashin Electric TN-3600 cassette deck required for this project.

As there is no mention of the renewal of your PCB service in your issue of ETI for this December I must assume it is not yet functioning. If you are not yet in a position to supply the PCB I require for this project, perhaps you would be so kind as to let me have a good foil pattern so that I can etch a board myself.

Yours sincerely  
D. Van Beirendonck  
Flint,  
Clwyd

The PCB Service is now back and raring to go. The Digital Cassette Deck PCB costs £10.25 and you will find details of how to order towards the end of the magazine. The deck itself is obtainable from Cirkit, Park Lane, Broxbourne, Herts. Stock number is 72-03600, price £43.95. — Ed.

ETI

## AUNTIE STATIC'S PROBLEM CORNER

Dear Auntie,

I have been following ETI's Sound Sampler project with great interest, but despite my degree in electronics I often find myself getting in deep water. For one thing, I have never heard of 'switched capacitor' filters. Will you please explain what they are and how they work? I am sure other readers would be interested.

W. Richards,  
Chatham,  
Kent.

A popular circuit for implementing standard filter configurations is the 'Universal State Variable' filter, shown in Fig. 1. The circuit gives high pass, band pass and low pass outputs, and with the addition of an extra op-amp will also give a band reject, or notch, output. In addition, with suitable choice of component values, the circuit can be made to conform to any of the classical

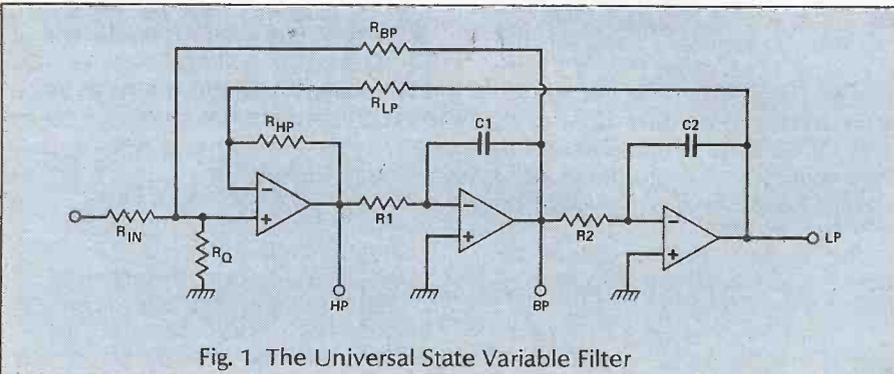


Fig. 1 The Universal State Variable Filter

filter responses: Bessel, Cauer, Chebyshev, Butterworth, and so on. You can't get much more universal than that!

Unfortunately, the circuit has a number of disadvantages, not the least of which is that the design equations are complicated enough to make you consider abandoning electronics and devoting your life to stamp collecting. Apart from that, if the response of the circuit is to be at all satisfactory, precision low-drift capacitors are needed. These tend to be rather expensive.

The switched capacitor filter offers all the advantages of the state variable filter with far fewer shortcomings. The design equations are simple, there are no external capacitors, and the turnover frequency is accurately determined by the frequency of the applied clock signal.

If you look again at Fig. 1, you will see that the filter consists, in essence, of

an op-amp followed by two integrators. The resonant frequency of the filter will be determined by the time constants of the two integrators,  $R_1 C_2$  and  $R_2 C_1$  (and also by the ratio of  $R_{HP}$  to  $R_{LP}$ , incidentally).

Using sampled data techniques, the resistor in each integrator can be replaced by a capacitor and two switches, as shown in Fig. 2. The two switches are closed alternately. With SW1 closed and SW2 open,  $C_1$  will charge up to  $V_{in}$ . With SW1 open and SW2 closed,  $C_1$  is discharged into the virtual earth at the inverting input of the op-amp. Each time SW2 closes, a charge of  $C_1 V_{in}$  is transferred, and if the switches are opened and closed by a clock of frequency,  $f$ , with one operation of both switches every clock cycle, the average current will be  $V_{in}/R$ , so the capacitor and switches have an 'equivalent resistance' of  $1/fC_1$ , and the time constant of the integrator will be  $C_2/fC_1$ .

Now, if the idea is to build a filter from discrete components, this has just compounded the problem. Instead of one precision capacitor for each integrator, we now need two! In the

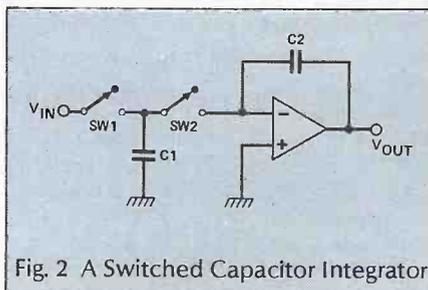



Fig. 2 A Switched Capacitor Integrator.

case of an IC, however, although it is still quite tricky to fabricate accurate capacitor values, it is relatively simple to maintain the ratio of two capacitors within very precise tolerances. For instance, if the IC designer intended  $C_1$  to be 10 pF and  $C_2$  to be 50 pF, variations in the production process may lead to their values being 10% higher than intended (say), but as both capacitors are subject to the same processes they will both be higher by 10%, and the ratio (11 pF to 55 pF) will still be 1:5.

The term involving time constants in the equation for the resonant frequency of the filter of Fig. 1 is  $1/\sqrt{T_1 T_2}$ , where  $T_1$  and  $T_2$  are the time constants for the two integrators. If all other component values are held constant, the frequency will be directly proportional to the value of this term. Using the time constant of  $1/kf$  for each switched capacitor integrator ( $k$  is  $C_1/C_2$  - a constant determined by the IC manufacturer, as already explained), this term becomes  $\sqrt{k^2 f^2}$ , or  $kf$ , so not only is the resonant frequency dependent on the clock frequency, it is directly proportional to it! In the case of the MF10 IC, circuit parameters have been chosen by the manufacturer to make the ratio between the clock frequency and turnover frequency 50:1 or 100:1 (selectable) so the calculation could hardly be easier!

The complete diagram of the MF10 is shown in Fig. 3. It has various additional facilities to make the circuit more versatile, but still consists essentially of an op-amp and two integrators. There are two identical second order filters in each IC, which makes the circuit look more complicated than it actually is.

Fig. 3 Block diagram of the MF10 switched capacitor filter (courtesy National Semiconductor).

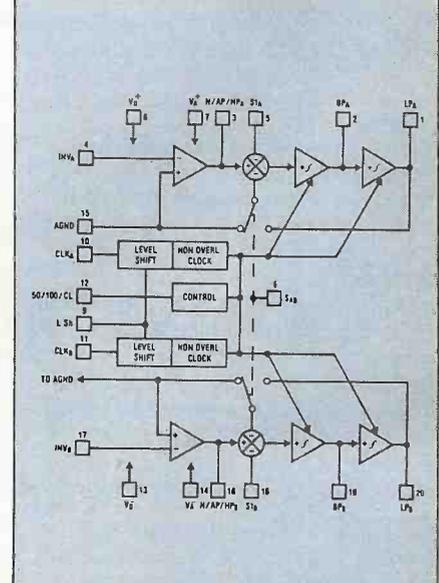

Other members of the MF10 family are: the MF4 - a fourth-order Butterworth low pass filter in an 8-pin package, needing no external components at all, the MF5, which is just half of the MF10, that is to say just a single second-order filter, and finally the MF6, a sixth-order Butterworth low pass filter which doesn't even need an external clock.

## Almost An Audio Special!

### 10 Gigawatt Amplifier On A Pinhead

Well, Almost. Actually, it isn't quite that powerful and it is a little bit bigger than a pinhead, but even so we think the ETI Matchbox Amplifier is going to be hard to . . . well, match. It's a good bit smaller than the average matchbox, delivers up to 50 watts RMS and uses a standard power-amp IC in either a single-ended or bridging configuration. Even with a power supply and generous heatsinking attached, it should still be possible to produce a strikingly small amplifier system using this board. Get your magnifying glasses ready now!

### Battery-Operated PA Amplifier

Continuing with the audio theme, we present a John Linsley Hood amplifier design which offers 50 watts of high quality audio and can be operated from a car battery or other 12V DC supply. Unlike some designs in

which the amplifier stages operate directly from the low-voltage supply, this project employs a switch-mode power supply which generates a 55V DC rail, reducing the need for compromises in the design of the amplifier itself. The first article describes the design and construction of the PSU, a self-contained unit which can be used with this and with other amplifier units or in any application where a 55V DC 2A supply must be obtained from a 12V DC input.

### Constant Current Sources



Graham Nalty takes a look at the various types of constant current generator circuits in use and discusses their strengths and the weaknesses and the uses to which they are put. Taking up the audio theme which runs through this issue, he considers the use of constant current sources in audio amplifiers and describes the effect of introducing modified constant current arrangements into a proprietary hi-fi amplifier, raising some potentially controversial issues in the process.

### Plus

Projects, features, Tech Tips, News Digest, Circuit Solutions, Read/Write, Reviews and a SPECIAL OFFER — a digital multimeter module which we are offering at a knock-down price, complete with some suggested circuits to help you make maximum use of it.
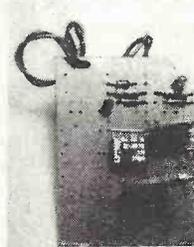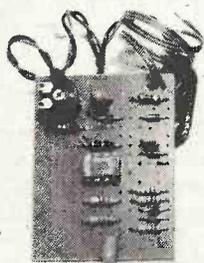
### AND . . .

Three more projects to build on your free PCB — a frequency meter module, a touch switch and a Coldbathwaterometer!



**THE AUDIBLY-SUPERIOR APRIL 1986 ISSUE  
OF ETI, ON SALE MARCH 7th. HAVE YOU  
HEARD HOW GOOD IT IS?**

Articles described here are at an advanced stage of preparation but circumstances beyond our control may dictate changes to the final list of contents.

# MICRO- EXPANSION

**Why upgrade when you can expand? Do you really need Megabyte power, or can your micro do the job with a little ingenuity and a home-built add-on? Mike Barwise cuts through the jargon jungle to rescue the good old 8-bit from the inflated claims of the supermicros.**

**T**he mushroom growth of the home computer industry has injected an almost maniacal sense of urgency into marketing strategy. No sooner is one model in the shops than the next is under development, in the hope that the public will buy and buy again.

This has had a significant influence on the design of the home micro. Short development times coupled with the need for obvious advantages in the next model has led the industry to provide micros which are in essence cut down versions of the previous generation of business computers. But design concepts which have validity in high performance business computer systems can easily degenerate into mere buzz words when pared down and applied to the design and marketing of the low cost home micro.

Emotive descriptions of processor power, speed and memory capacity capture the imagination, frequently clouding understanding of the concepts involved and their currency. These descriptions often prove to be no more than sales pitch, having little relevance to the real performance of the home micro.

## **Megabytes: Who Needs Them?**

As microchip design progresses it becomes possible to cram more and more microscopic hardware into a smaller and smaller space. Larger scale integration can run faster due to improvements in design, and costs less per function, since expenditure on die development is not directly proportional to gate count.

On the other hand, skilled technician time stays as expensive as always and various high level compilers are now almost universally used to speed up commercial software development. These produce bulky and slow code, but increase the productivity of software developers by up to 100 times, when compared to the output of programmers using assembler.

Faster and more highly integrated hardware systems running massive software at considerably less than maximum efficiency have become the order of the day in business computing. Since the tasks generally required for business applications are not excessively demanding, performance can be very high, but the high speed and enormous memory requirements of such implementations have created user expectations which are not really applicable to the 8-bit micro.

To keep the price down, the home micro uses much simpler hardware than its business brother, with an 8-bit data and a 16-bit address bus remaining the norm. The average business-oriented micro, with a 20-bit or 32-bit address bus, has an address map in excess of 1Mbyte, whereas the home micro usually has 64Kbytes maximum. Ironically, home micro users are likely to demand a much wider variety of applications of their less complex and slower hardware.

There is nothing, however, to prevent the expansion of almost any 8-bit home micro into quite an advanced, fast and complex system. The first step is to appreciate some of the most significant machine-level design principles.

## **Micro Memory**

The small micro address map may generally be divided into four more or less functionally distinct areas: systems, program and data memory, and I/O space. As most recent micros have almost every available space already dedicated, it is important to take the maximum advantage of any 'user area' available.

Systems memory is that portion allocated to the hidden 'housekeeping' tasks of the micro, including the I/O drivers, the system control code, the variable and pointer stacks and the scratchpad areas. Different systems make widely differing demands on memory, but in general, the higher 'level' the micro, the more systems memory it requires. As a user of a ready-built machine, you normally have little control over the allocation of systems memory.

Program memory is the area set aside for user applications software. Strictly speaking high level language interpreters and compilers are situated in the program memory as well, although some micros will not allow the user to access the areas set aside for them when they are absent.

The way in which applications software is written largely defines program memory usage, so it is reasonably easy to adapt and make use of extensions if you are writing your own software. However, few efficiently written 8-bit micro applications should require in excess of 28-32K of program memory, so you shouldn't go mad.

Data memory is the real crunch when it comes to the small address map of the home micro. It is often

1V=1n

not delineated from program memory, there being a tendency to store data in array structures appended to the program. This is not necessarily the best answer. Depending on your application, you may need anything from a few bytes to a Megabyte or more. When data memory is separate from program memory, it is the easiest of all memory areas to adapt. Various approaches to unmapped and semi-mapped storage can extend it theoretically almost without limit.

I/O space is the easiest area to start from when post-implementing expansion on your micro. Almost all adequate micros have one or more (usually small) undedicated 'user' expansion areas. The trick is to cram as much as possible into these spaces.

## Commercial Micro Expansion

Paged memory units, RAM-disk, files, second processors and buffers are optional add-ons available for an increasing number of home micros in an attempt to overcome capacity and speed restrictions. Unfortunately, it is rare to find add-ons from different sources which are compatible, and it is difficult to select the one which will perform best in a specific user-defined application. All of them have to be fairly general in their application, or else be dedicated to accompanying software packages, in order to cover an adequate market. The principles of these gizmos are nevertheless remarkably simple, and with a little ingenuity they may even be improved upon by the enthusiast.

## RAM Disk

RAM disk is really a misnomer. The system is actually a type of buffer ported to look at high level like a disk interface. Without the disk drive emulation software, a similar buffer concept can be used with

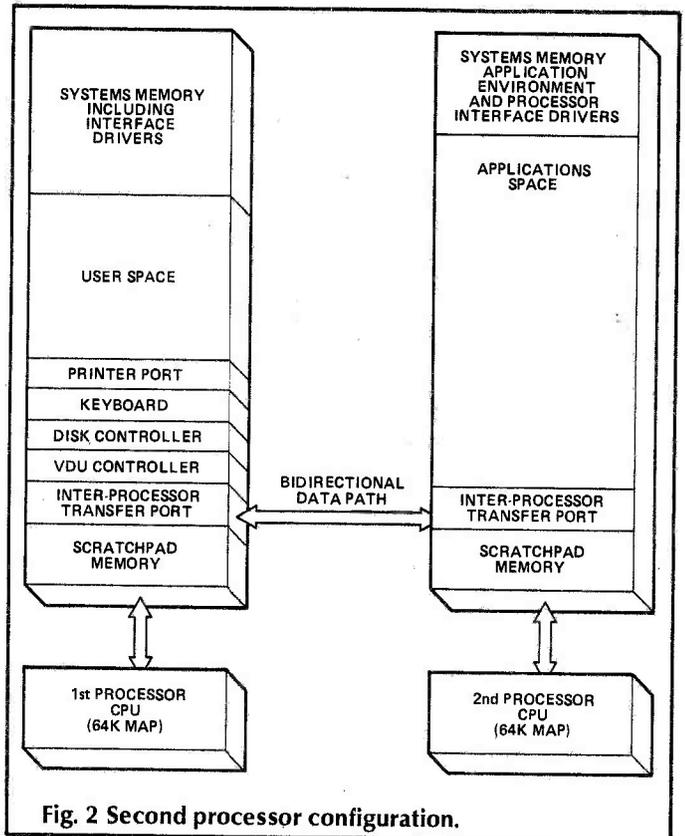


Fig. 2 Second processor configuration.

increased versatility, as long as the user keeps track of data structures. Such buffers are more suited to data than to program storage, but can also be used in interfaces to secondary or slave processors in multi-processor systems. The design of ported buffers will figure later in this series.

## Second Processors

The second processor (Fig. 2) is essentially a special case of the multi-processor concept. Its aim is twofold: to increase the effective program and/or data memory of a limited map CPU, and to allow the running of non-native applications code.

Either or both these aims may be fulfilled in any given installation. The principle is that the second processor takes over the running of the application, while the primary processor performs the relatively simple but time-consuming tasks associated with I/O: keyboard input, printer output, disk storage, and so on. This not only relieves the second processor of interruptions and delays, but in addition releases for other uses the memory areas that would otherwise have to contain the I/O drivers and associated housekeeping code. A good example of this is the running of CP/M on the Z80 second processor with the BBC micro.

The idea is not a bad one in principle, but it has a few drawbacks for post-implementation. In order to install a second processor of this type, the original host (primary) processor has to be working in a software environment which was created with a second processor in mind. Also, to write applications software which makes full use of the facilities available takes a great deal of systems knowledge. Both these cautions are due to the very general nature of the tasks being performed by both processors.

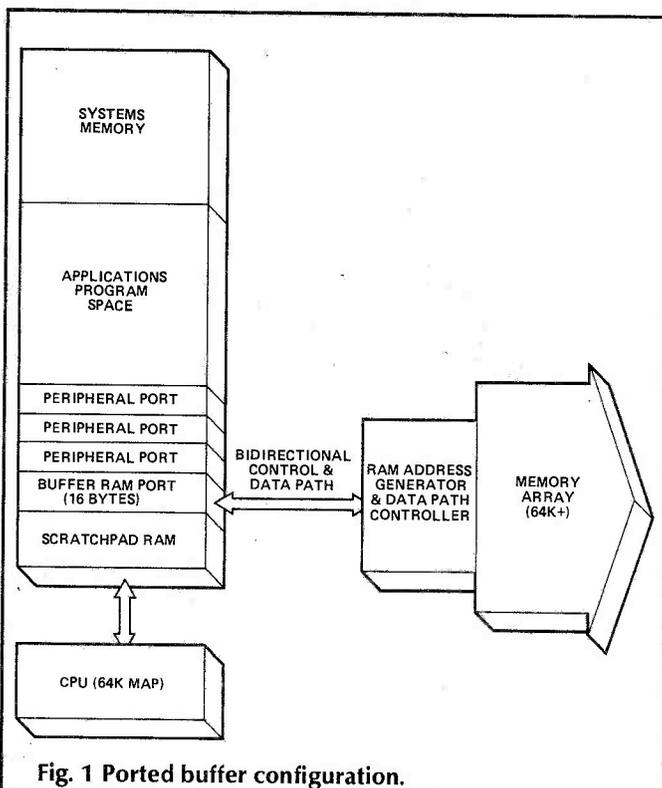


Fig. 1 Ported buffer configuration.

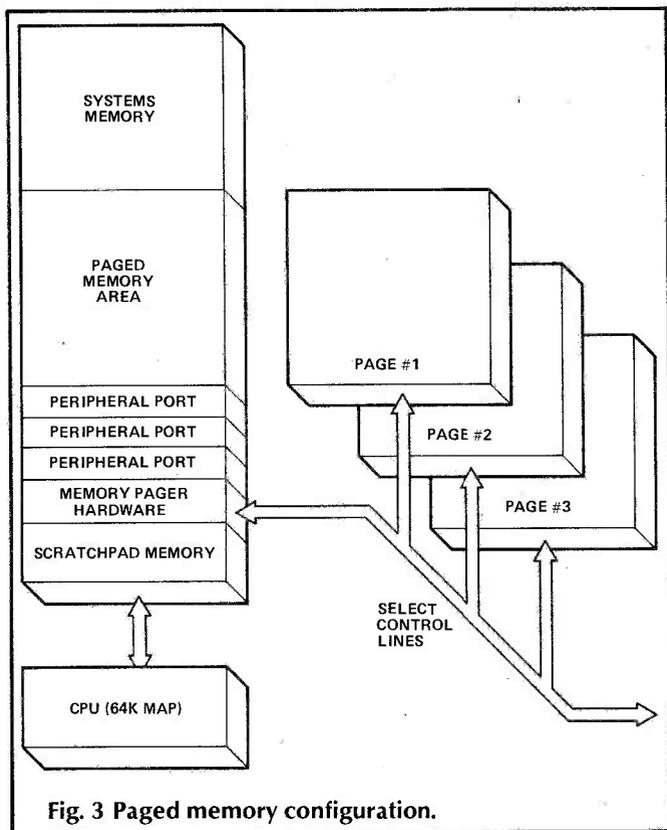


Fig. 3 Paged memory configuration.

As a generalised system, the second processor will not necessarily perform specific tasks at optimum efficiency compared with dedicated multi-processors, but on the whole it is probably a great deal better than nothing. Several DIY second processors have featured recently in ETI, and it is well worth a look back at the concepts embodied in them. (See, in particular, 'Second Processor For The Electron', June and July, 1985).

### Paged Memory

Paged memory (Fig. 3) allows whole large areas of the processor map to be replaced at will by others effectively wired in parallel. Whole or part applications can be rapidly exchanged for others during a program run. A high degree of consistency is required in the structure of software to be used in paged virtual memory systems, but the control overhead can be remarkably small. The BBC micro paged ROM system is an excellent example of the job done well. Commands included in different ROMs can be executed in succession, creating an effective program storage many times larger than the available real program memory.

### Multiprocessors

The aim of a multiprocessor system (Fig. 4) is to enhance overall system performance by allowing dedicated sub-systems to handle specialised tasks concurrently and independently.

Significant losses of system efficiency occur when data has to be transmitted to and from the real world. The majority of I/O is painfully slow by CPU standards, due to its reliance on mechanical devices, with all their attendant problems of inertia, wear and

tear and bits of carpet fluff. Some really complex maths problems can, if implemented in software, tie up the arithmetic logic unit and its associated areas for long periods, leaving the remainder of the system idle. It may also be necessary to acquire and/or transmit information asynchronously with a primary task, or in such volume that the memory constraints of the primary processor cannot accommodate it.

These problems can frequently be eliminated by the efficient linking together of single function subsys-

---

*There is nothing to prevent the expansion of almost any 8-bit home micro into . . . an advanced, fast and complex system . . .*

---

tems which can perform the time-wasting or otherwise impossible operations concurrently with, and independently of, other primary processor operations.

An excellent everyday example of this is the printer buffer (see ETI, July and August, 1985). The dedicated system emulates a printer port as far as the primary processor is concerned, but can accept data as fast as it can be sent, rather than at the mere 100 or so characters per second of the mechanical printer.

A floppy disk controller chip is also a single function sub-system, although this is less obvious at first sight. In this case it normally shares the primary processor memory (either by primary processor intervention or by direct memory access — DMA), but the principle is the same. Without the FDC, the micro's CPU would have to send all the drive head stepping pulses with their associated timing, load and unload the heads, test the index pulses and write protect signal, identify the track and sector ID references and compute the CRCs. Some additional means of parallel/serial conversion and back would also be needed. This is altogether a massive task, which would take a great deal of the primary CPU time to perform without an FDC.

### Multi-User and Multi-Tasking

These are two increasingly common buzz phrases, primarily of interest in the office environment, where they improve throughput and assist the efficient use of expensive peripherals such as Winchester disks and high speed printers. Either several workstations or terminals (multi-user) or several independent tasks on one micro (multi-tasking) are performed concurrently by multiplexing so that most of the hardware is active most of the time.

The principles are quite simple, but the adaptation of small systems to work in this way is probably too much effort for the return from a system not designed with multiplexed operation in mind.

Home micro users should consider enhancement of their systems primarily from the hardware standpoint. Adaptation of the operating system, apart from being frowned upon in the current contentious atmosphere surrounding the copyright situation, is really a very difficult job. The level of familiarity required to do it properly would enable the user to make a start on their own independent OS, and if you could do that, you would be unlikely to be reading this article!

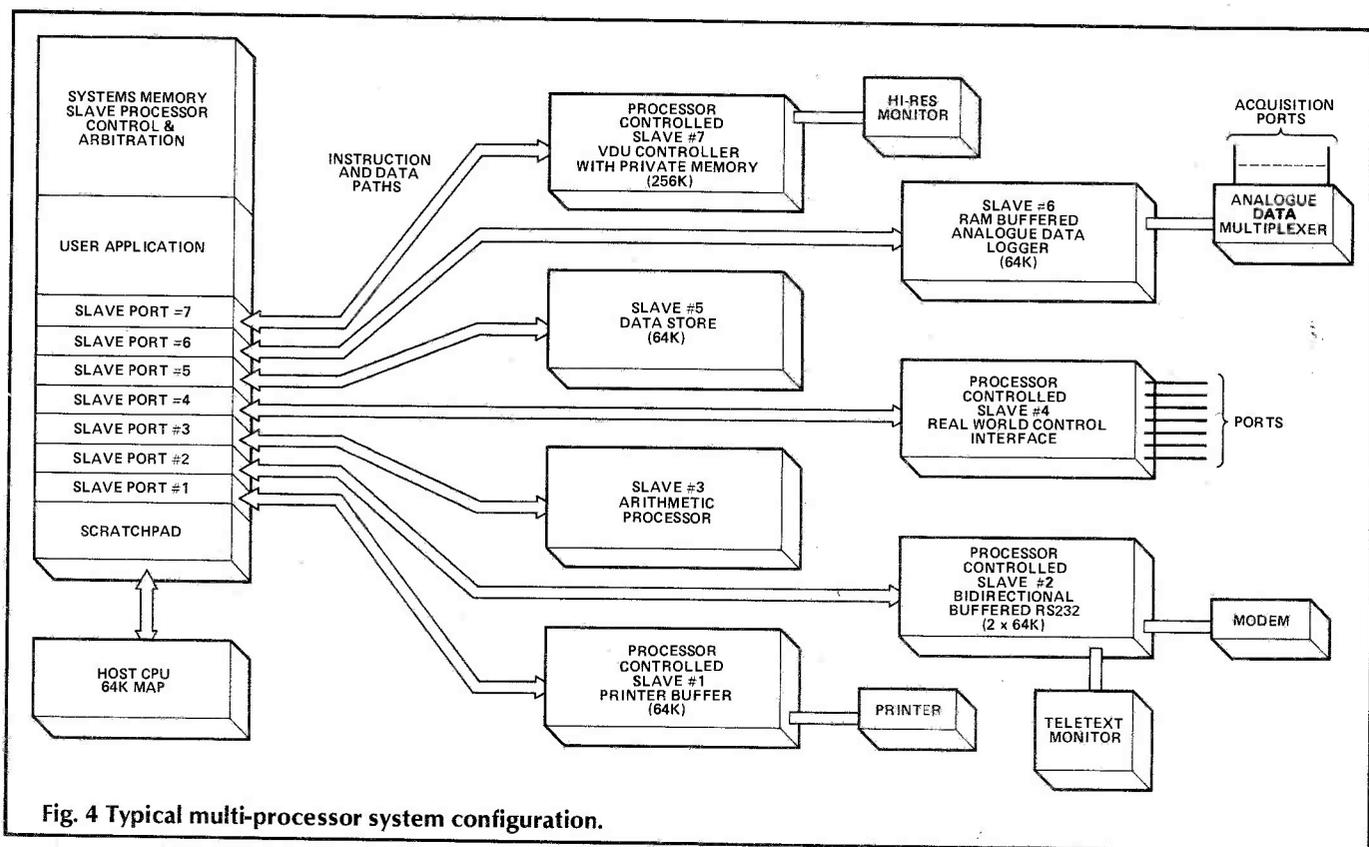


Fig. 4 Typical multi-processor system configuration.

The host (primary processor) software required to drive any extensions should be minimal, so we are really left with the addition of dedicated single function (possibly processor-controlled) sub-systems, allowing concurrency of independent tasks, controlled ideally by no more than short instruction sequences from the primary processor. Interdependent tasks performed in this way require more careful control in the time domain, but the problems are by no means insuperable.

## Key Functions

The key to optimisation is to identify those functions of the overall system which are invariable or could advantageously be operating concurrently with other tasks. These will normally include:

1. Data file I/O operations via mechanical devices which constrain the processor system to low fixed transfer rates, frequently asynchronous with the system timing.
2. Protracted arithmetic on volume data (for example, encryption/decryption) where long delays can occur between provision of data and obtaining a valid 'answer', and where hardware arithmetic can substantially improve throughput.
3. Real world data interfaces such as analogue data logging where data may be presented unexpectedly or at high asynchronous rates, and are lost if the interface is not serviced in time.
4. Control interfaces to motors and experimental rigs where the control consists of the sending of one or two mode instructions followed by long sequences of, say, serial pulse trains which could be readily generated by simple hardware.

In the forthcoming parts of this series I will be discussing ideas for systems building blocks suitable

for these and similar tasks. Design notes will cover inter-systems ports, buffer memory, hardware handshaking.

The 6500 series processor will be used as a model when specific details are called upon, as these processors are about the simplest in structure, but operate in a manner typical of the majority of 8-bit CPUs used in home micros.

Next month I will be concentrating on efficiency, reliability and dynamic investigation of microsystems, systems watchdogs and guidelines for a DIY logic analyser.

In the meantime, get out your micro technical manual and familiarise yourself with the address map.

*Home micro users should consider enhancement of their systems primarily from the hardware standpoint . . .*

Make notes first on the locations of designed-in 'user areas' dedicated to both RAM and I/O, and then on functions which you would like to see enhanced. For example, if you need a fast A-to-D interface (around 50kHz acquisition rate) it is worth considering exchanging it for the slow one built into your micro already.

Once you have a general idea of the address map which is free for post-expansion, the best approach can be defined. If your list is very short, the only answer is really to add intelligent peripherals, and finish up with a multi-processor system. Even if your list is quite long, this is, in my opinion, still the most exciting alternative.


# THE SHOW MUST GO ON

Display technology is such a fast moving field that we felt it worthwhile to get up to date with some very recent developments. Keith Brindley was at the latest trade show in the cause of further enlightenment.

It's only right that we should give priority to age, and the CRT is certainly getting on a bit. It has been around for a hundred years or so in one form or other, although only as a display device in televisions since about 1930.

The resolution of a CRT display is dependent primarily on the distance between the phosphor spots produced by the electron beam as it forms the picture. In a colour CRT, the resolution depends on the distance between triads of primary colour spots, which in turn is dependent on the accuracy of the shadow mask used to direct the three beams to their respective colour phosphors. CRTs with spot distances (known as pitch sizes) of as small as 0.2mm have been made, but typical television CRT displays have pitch sizes of about 0.6mm. In terms of resolution, the CRT has a way yet to develop, but we can expect television pictures of tremendous clarity from high resolution CRTs.

The problems associated with CRTs are not to do with picture clarity. They are large, ungainly and heavy; their depth is often as big as or greater than the screen size. They consume a lot of power — up to 200 watts or so. They are fairly easily damaged. None of this is any great disadvantage for mains-powered, fixed-site equipment, as long as you don't mind your television taking up all of the corner of the living room, or your computer taking up most of the room on your desk. If lightness, durability, and power consumption are important, then the conventional CRT will not do.

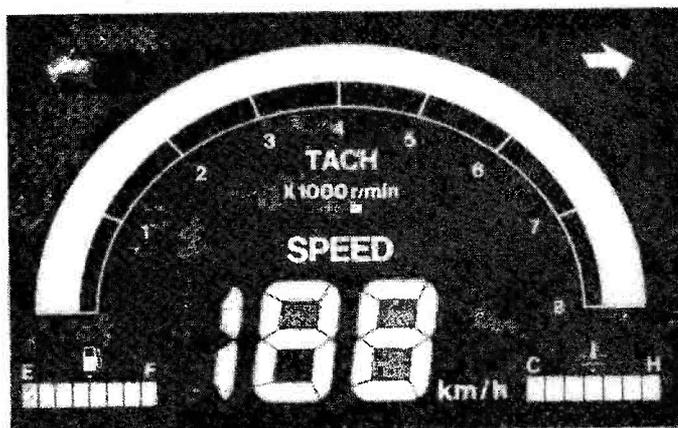

The latest from Epson — the high-contrast 'Black Shutter'.

Sinclair's flat-screen CRT is one development of a traditional technology. As it stands, however, the device — though ingenious — is monochrome, difficult to view and constrained by its very ingenuity to remain small. Philips is one company developing a flat-screen colour CRT. While similar to the Sinclair device in that the electron beam is side-projected, it is totally different in other respects (Fig. 1). The Sinclair tube uses a familiar electron gun bent through 90°. To engineer such a tube for the accuracy required of colour television would be very difficult. Philips use a single electron beam — like Sinclair but it scans at three times the normal rate, so it can cover all three spots in a colour triad. It also has an unusual approach to deflection. After reversal of the beam, frame plates bend it to the required spot on the screen. Before hitting the screen the beam passes through an electron multiplier, increasing the number of electrons and so making a brighter spot. ITT and Siemens are the other two companies working on the developments of flat-screen colour CRTs.

## The Liquid Crystal Ball

Apart from dabbling at new developments in CRTs (Sony's Trinitron CRT — a single electron beam device — and Toshiba's flatter, squarer tube) the Japanese appear to be leaving major CRT developments such as flat-screen devices well alone. Instead they are concentrating efforts towards flat-panel displays which do not use electron beam at all.

The main force of their work so far has been in the


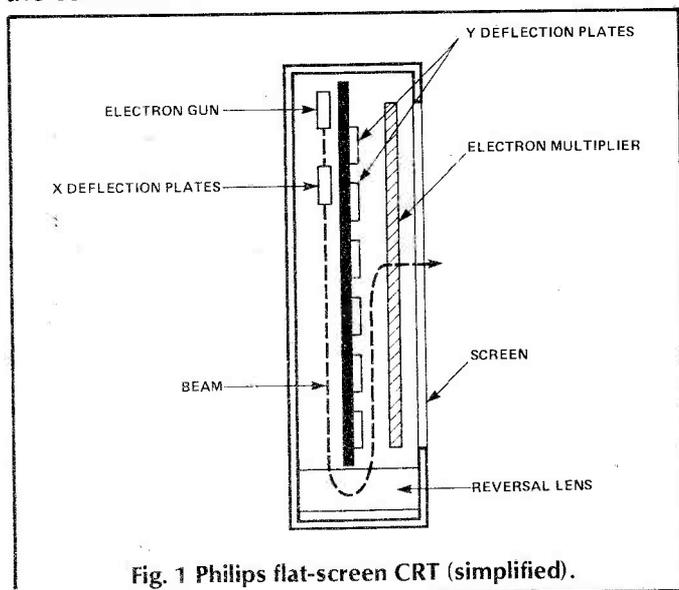


Fig. 1 Philips flat-screen CRT (simplified).


development of LCD devices, but other technologies will probably form the display devices of the future.

There are a number of types of LCDs, but the principle is the same in all of them (Fig. 2). A layer of liquid crystals is sandwiched between two transparent electrodes. The molecules of the liquid crystals are generally aligned in one direction and so light from behind the device can pass through. When a potential is applied across the electrodes, however, the molecules of the crystals all become polarised into another alignment, which prevents light from passing through the layer, making the layer appear dark.

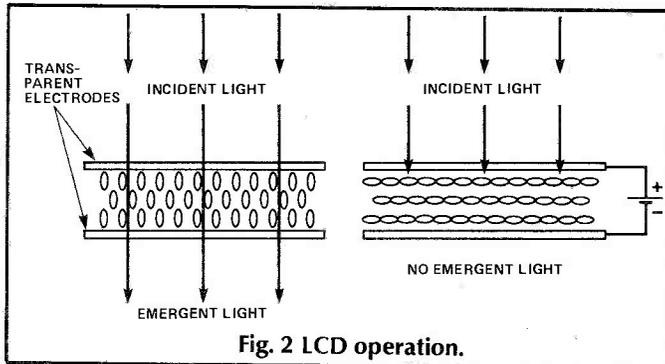


**Fig. 2 LCD operation.**

Three main varieties of liquid crystal are used to make LCDs: nematic, cholestric and smectic (Fig. 3). The major difference is in how the molecules are aligned, and this produces greatly different LCDs.

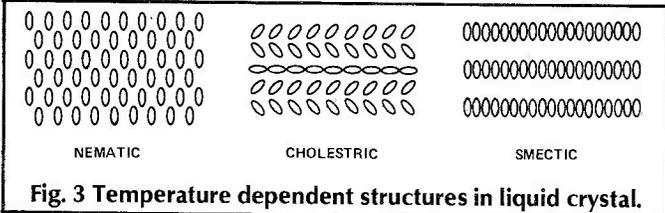

**Fig. 3 Temperature dependent structures in liquid crystal.**

Nematic liquid crystals are more commonly called 'twisted nematic' crystals, because the crystals sandwiched between the transparent electrodes are twisted through  $90^\circ$  between one electrode and the other when no potential is applied. Polarising sheets (at  $90^\circ$  to each other) are applied at the front and back of the device, so that light entering the LCD is polarised in one plane by the first polarising sheet, passes through the liquid crystal where it is twisted through  $90^\circ$  by the twisted nematic structure, then leaves the device through

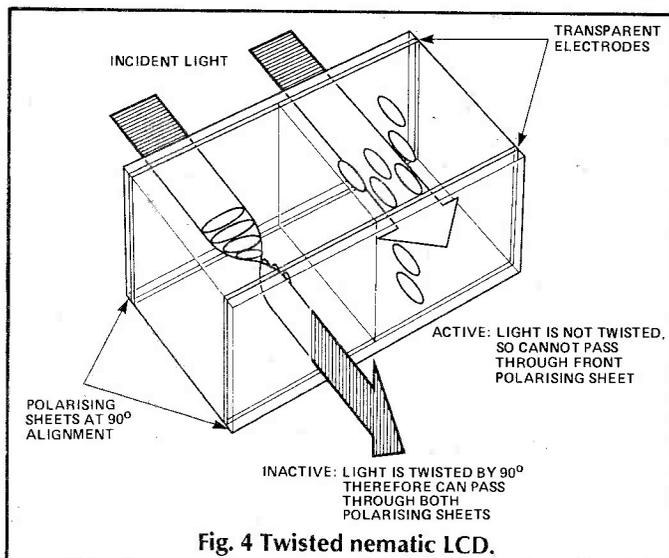


**Fig. 4 Twisted nematic LCD.**

the second polarising sheet (Fig. 4). Typically the LCD wouldn't normally be used like this, but a reflecting surface would direct the emergent light back through the set-up, so that an observer on the same side as the incident light would see a 'transparent' area.

When a potential is applied across the electrodes, the crystal becomes active, and the molecules are all aligned in one direction. The incident light, which is polarised by the first sheet, now passes through the liquid crystal without being twisted. It cannot pass through the rear polarising sheet, cannot be reflected, and therefore cannot be seen by the observer. An opaque area is produced.

Cholestric crystals do not need polarising sheets since a dye is added to the liquid crystal to absorb the incident light. LCDs using this principle are sometimes known as 'guest-host' devices. Dichroic dyes, which produce a different colour depending on which way their cells are aligned, are the 'guests' in the liquid crystal 'host'.

In an inactive state, incident light passing through the liquid crystal is polarised by the natural twist in the structure, and because of the dye the emergent light appears coloured (Fig. 5). As with twisted nematic LCDs, when the activating potential is removed the structure reverts back to its inactive, though this time coloured, state.

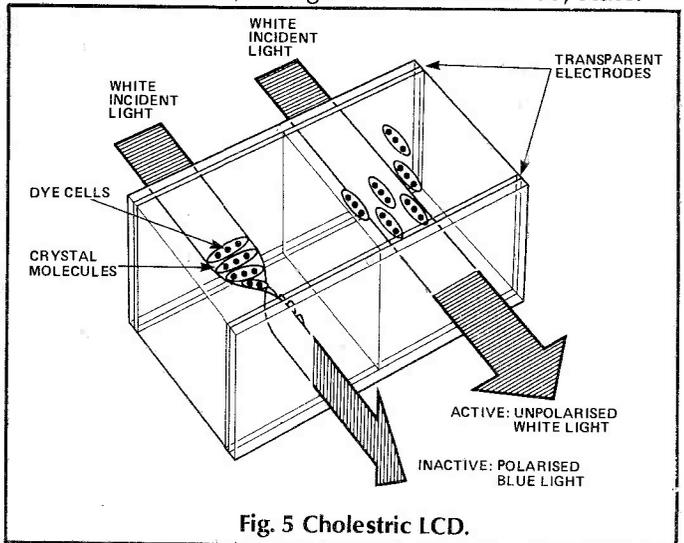

**Fig. 5 Cholestric LCD.**

## Heat Waves

All liquid crystals have several temperature dependent phases, in which the ordering properties of the molecules change. Three phases: isotropic, nematic and smectic are used in smectic liquid crystal devices to create a different type of LCD. Smectic LCDs rely on three phenomena to do their job:

1. In the smectic phase, the molecular arrangement of the liquid crystals cannot be changed by an applied electric field.
2. When liquid crystals are heated to the isotropic phase then cooled to the smectic phase with no applied electric field, they become strongly disordered.
3. When heated to nematic phase, then cooled with an applied electric field to the smectic phase, the orientation of the molecules will be as in the nematic phase.

To exploit these phenomena, smectic LCDs use a matrix of electrical lines so that each display element in the display can be addressed and heated electrically.

By heating the liquid crystals to the isotropic phase, then cooling them to the smectic phase, incident light is prevented from passing (Fig. 6). By heating the crystals to the nematic phase, applying an electric field to align the molecules, then cooling to the smectic phase, incident light is allowed to pass.

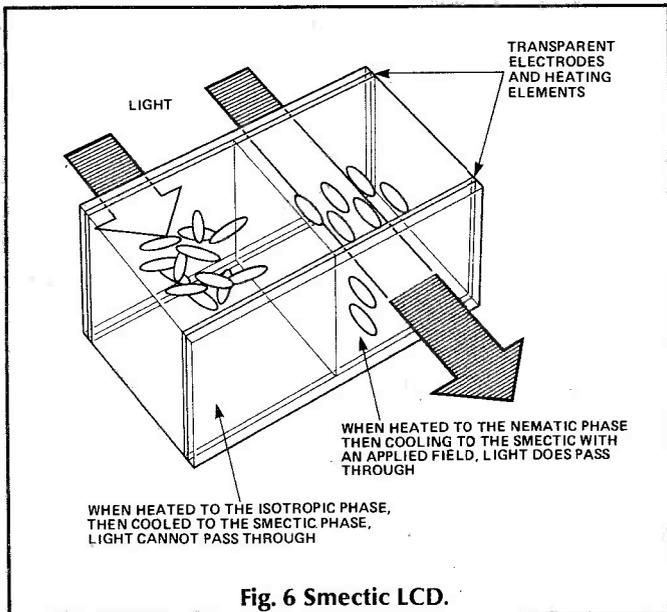


Fig. 6 Smectic LCD.

The really clever bit is that by maintaining the temperature so that the liquid crystal is held in the smectic phase after it has cooled from an isotropic or nematic phase the crystal molecule arrangement remains fixed at what it was, prior to cooling. Smectic LCDs have a memory facility so that removing the 'addressing' potential has no effect. To change the molecular arrangement requires a further addressing, heating, and cooling procedure.

Most of the work currently being undertaken into computer-type LCDs is along the smectic lines. One of the latest LCD developments is STL's smectic-A 760 x 420 pixel prototype display which, it is hoped, will be on the market soon.

### Colour LCDs

The LCD techniques we've looked at so far have been for dot-matrix displays — ideal for computers but not so good for televisions. There are three reasons for this. First, the displays are monochromatic — and who wants a black-and-white television? (Well, Sir Clive?) Second, the display type is dot-matrix — each dot can only be on or off, unlike CRT screen spots which are graduated in brightness. Most important is the response time of these devices (the time it takes for the device to switch between active and inactive states). Common response times are around 300ms — great for computer or alphanumeric displays, but certainly not fast enough for television where each spot on the CRT screen is addressed by the electron beam every 40ms.

Two of these problems, colour and response time, are being tackled by a number of Japanese manufacturers with LCD devices which use thin-film transistors (TFTs) mounted directly on the glass which forms the casing to contain the liquid crystal. The transistors are thus in direct contact with the crystal itself (Fig. 7).

The use of TFTs dramatically reduces the LCD response time, down to a level approaching that required to display television pictures. By making an LCD element so small that it can be considered as a spot,

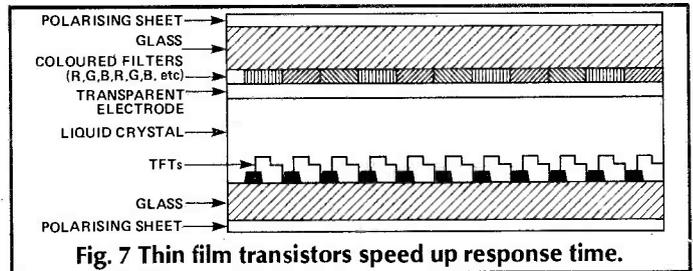


Fig. 7 Thin film transistors speed up response time.

and by grouping three spots into triads, coloured filters can be placed over the individual spots so that the triads can be addressed much like the triads of a conventional CRT. And, hey presto, we have an LCD colour television display device.

A number of Japanese manufacturers, notably Sanyo, Casio, and Citizen, have recently shown prototypes of colour television using this method. Sanyo's, the largest, is a 4 inch display. The Epson Elf, a colour television with a 2 inch display, was the first to be produced and has been on sale abroad for a year or so already.

The resolution of these displays is limited by the number of liquid crystal triads which can be produced in the device. At present the resolution doesn't even approach that of typical low-grade television CRTs, but it is only a matter of time — and research money.

Size is probably the colour LCD's greatest enemy. The quality of the colour display is limited by the constancy of the thickness of the layers in the device. The larger the device, the more difficult it becomes to maintain constant thickness. So, no wall-sized flat-panel television screens using LCDs yet, I'm afraid.

### Flat Contender

A contender in the race to beat the CRT as the only viable television display device is the electroluminescent (EL) flat-panel. Electroluminescence occurs when certain phosphorescent materials are influenced by an electric field.

Figure 8 shows a cross-section of an EL display, with criss-crossed electrodes allowing each point where two electrodes overlap to be addressed. The material sandwiched between the layers of electrodes is typically zinc sulphide, which emits a bright yellow-orange colour when an electric field is generated through it, but red, green and blue emitting materials have recently been isolated.

EL displays are of four main types: DC thick-film, AC thick-film, DC thin-film, AC thin-film. Thin-film varieties have proved to be the most successful so far, in terms of reliability and power requirements. In these, a layer of powder phosphor, typically around 30µm thick is deposited onto a sheet of transparent oxide which forms the front electrode. This layer is then covered by a vacuum evaporated aluminium rear electrode. After

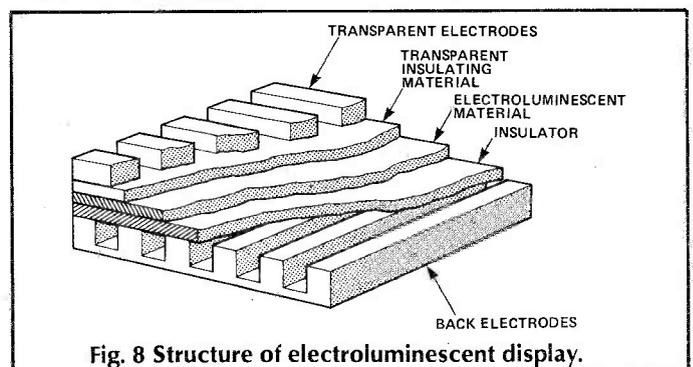


Fig. 8 Structure of electroluminescent display.

etching horizontal and vertical rows and columns into the front and rear electrodes, the device is more or less usable.

Such displays are of monochromatic dot-matrix form suitable for alphanumeric computer displays and graphics. By overlaying thin-films of red, blue and green emitting phosphide layers, there is hope that EL displays suitable for reproduction of coloured television pictures can be made. Their availability on a commercial basis is many years off yet.

EL displays generally need quite a high operating voltage (over 100V) and considerable current, so they are probably not the display to be used in portable equipment, but for flat-panel home or office use their potential is great.

## Plasma Gas Discharge

Plasma gas discharge of inert gases under a strong electric field is the basis of another type of flat-panel display — the plasma display panel (PDP). The gas breaks down into a plasma and gives off light. Neon indicators work in the same way.

The two main varieties of PDP differ in the applied voltages. In the DC plasma display the criss-crossed electrodes are in direct contact with the gas. In the AC plasma display, the electrodes are close to the gas but electrically isolated from it (Fig. 9).


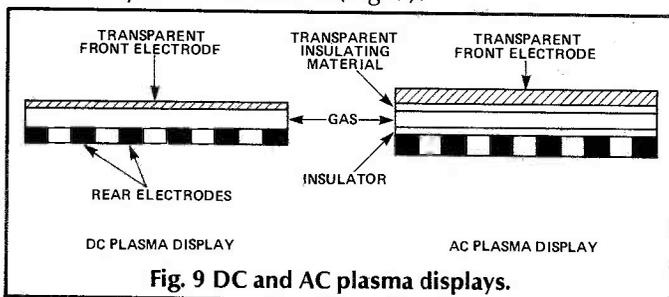


Fig. 9 DC and AC plasma displays.

Large sized PDPs have been developed, initially for military use, and now available on a commercial basis and used in many computers. Thomson-CSF, for example, has recently produced a 1024 x 1024 dot-matrix PDP display, whose resolution is not far short of a CRT.

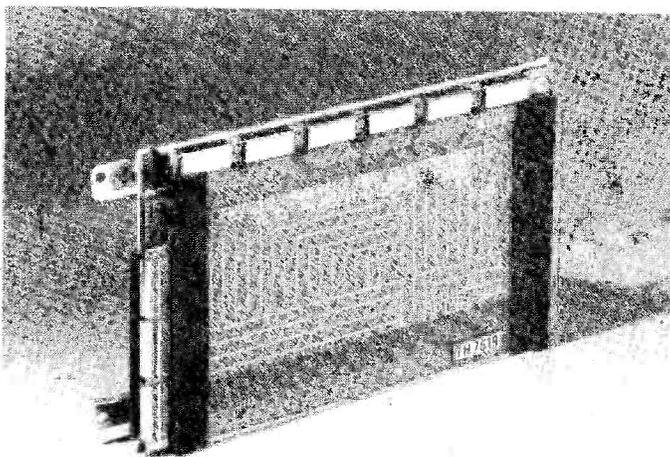PDP displays still have many disadvantages. Operating voltages are quite high (typically around 80V),




Thomson-CSF compact 96 x 200 dot graphic AC plasma display.

they're not solid-state devices and can't be as rugged as LCD or EL displays. Colour displays suitable for television use are going to be difficult, if not impossible, to make.
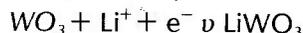
## ECDs

One new form of display device, just now reaching the market, looks as though it might topple the CRT in years to come. The electrochromic display (ECD) uses the fact that an electrochromic material changes its colour reversibly by redox reaction.

For example, amorphous tungsten trioxide ( $a\text{-WO}_3$ ) turns reversibly from transparent to blue by reacting with lithium ions in an electrolyte, following the formula:



A simple display is illustrated in Fig. 10.

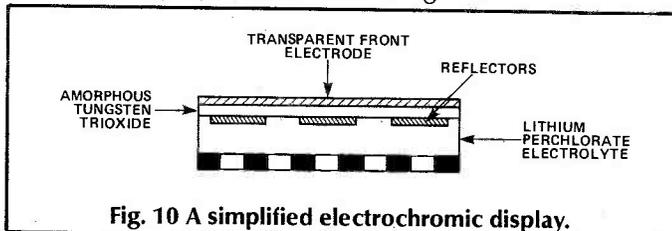


Fig. 10 A simplified electrochromic display.

This display is much simpler in operation than an LCD, and would be much cheaper to make. It does, however, have significant disadvantages, not the least of which is its response times (over half a second to change from white to blue, and over two seconds to change from blue to white!) Significant development work is underway, and it's probably true to say that ECDs are only at the stage which LCDs were at 15 years ago (nowhere). Given a few years and some hard research and development...

## Old And New

The problem for manufacturers is not just one of research and development because other factors, mainly financial, are also involved. CRTs are an old technology. They've been made for many, many years by experienced manufacturers. They are used mainly as a television display device, but they're also used in test equipment — oscilloscopes, spectrum analysers, logic analysers and frequency response analysers — as well as in computers. Because of the numbers involved and because of tried and tested manufacturing techniques, they are very cheap.

Flat-panel displays, on the other hand, are new. They're relatively difficult to make and therefore expensive. So, manufacturers are going to be very careful to analyse the situation before they decide on any one other display technology which they think can fit the bill. No one display technology is yet capable of being better than the CRT in *all* applications. LCDs use much less power, but they have a very restricted viewing angle, low contrast, and can't be viewed in the dark (they are a non-emissive technology); EL displays are much thinner and are an emissive technology, but their power requirements are not much less than those of the CRT. ECDs are thin, have a wide viewing angle and high contrast, but they still have an unacceptably long response time.

At present, CRTs are unbeatable because technology rides on the back of its own success. New developments such as flat-screen, low-powered, high resolution colour CRTs will be along soon. But time is the CRT's own worst enemy. Given a few years, easier manufacturing techniques and lower manufacturing costs, flat-panel displays must surely beat and CRT. The questions are: which flat-panel device will do it — and when?

# CRICKLEWOOD

ELECTRONICS LTD



## It's no secret...

... that there is a *real difference* at *Cricklewood Electronics*. That's why you should never be without the *FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE*, for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your *FREE* copy now (no SAE required). You have nothing to lose.

### CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977



ETI

You can depend on

# ELECTROVALUE

for your supplies of  
world famous  
QUALITY  
COMPONENTS  
by

# SIEMENS

and other  
leading  
names

52 PAGE  
FREE CATALOGUE

- Write, phone or call
- Priced & illustrated
- Over 8000 items
- Real discounts
- Prompt despatch

- I.C.s
- semi conductors
- capacitors
- inductors
- ferrites
- connectors

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475 North Branch, 680 Burnage Lane, Manchester M19 1NA Telephone 061 432 4945 Please mention this publication when replying

BRITAINS FOREMOST QUALITY COMPONENT SUPPLIERS

# TEST INSTRUMENTS

A wide range of high performance instruments that put professional test capability on your bench.

**COUNTERS** — TF600 5Hz to 600MHz; TF200 10Hz to 200MHz; TF040 10Hz to 40MHz; PFM200A 20Hz to 200MHz (hand-held model); TP600 prescales to 600MHz; TP1000 prescales to 1000MHz.

**MULTIMETERS** — TM351 0.1% 3½ digit LCD; TM356 0.25% 3½ digit LCD; TM355 0.25% 3½ digit LED; TM354 0.75% 3½ digit LCD (hand-held model); TM451 0.03% 4½ digit LCD with autoranging and sample hold; TM452 0.05% 4½ digit LCD with built-in frequency counter (hand-held model).

**OSCILLOSCOPE** — SC110A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions.

**THERMOMETERS** TH301 -50°C to +750°C, 1° resolution; TH302 -40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple.

**GENERATORS** — TG101 0.02Hz to 200kHz Function Generator; TG102 0.2Hz to 2MHz Function Generator; TG105 5Hz to 5MHz Pulse Generator; TG501 0.005Hz to 5MHz Function Generator; TG502 0.005Hz to 5MHz Sweep Function Generator; TG503 0.005Hz to 5MHz Pulse Function Generator.

**LOGIC ANALYSERS** — TA2080 8 channel 20MHz; TA2160 16 channel 20MHz.

**ACCESSORIES** — Bench rack, test leads, carrying cases, mains adaptors, probes, thermocouple probes, microprocessor disassembly options.

For further information contact:

Thandar Electronics Ltd, London Road, St Ives, Huntingdon, Cambs PE17 4HJ Telephone (0480) 64646 Telex: 32250

**thandar**  
ELECTRONICS LIMITED



# BETTER BY DESIGN

Even professionals make mistakes, and Andy Armstrong is not afraid to point out some of the commonest. If you're thinking of designing a circuit, the best place to start is here. . .

After inspecting many designs at the draft stage, it is clear that there are some misunderstandings and design errors which crop up again and again. Some aspects of circuit design, for reasons unknown, seem to be ignored or glossed over by even the most seasoned practitioners.

Most of the problems fall into the category of 'things which will work most of the time or work with certain samples of the components used'.

A typical example was faced by a friend of mine, in a vacation job after his second year at college, and involved unijunction transistors. Someone had designed (by dint of sheer building) a control unit, incorporating a unijunction, for an electric arc welder. The first production batch of welders worked very well, but none in the second batch worked at all.

It turned out that the circuit had been optimised, by trial and error, to work with a batch of unijunctions which were at the edge of the specification. The next batch purchased had more typical characteristics, and the circuit could not cope. The configuration of the circuit was not designed to take account of the tolerances of unijunctions but a change of component values centred the circuit on the typical operating parameters. Subsequently only one component value had to be changed if a batch of unijunctions was too far from typical.

## Design Posts

Nobody expects magazine projects to be designed to industrial standards, (although we prefer it if they are — Ed.). This would be uneconomic, because of the very large amount of time required to design even a simple circuit to production standard, and because of the need to make more than one prototype to double check a design. These limitations notwithstanding, a project design needs to be as close in standard to an industrial design as possible, and should, in particular, avoid problems connected with variations in the electrical and mechanical characteristics of components.

Of course, there are differences in emphasis. For example, a circuit may rely on a particular component characteristic, perhaps requiring that two diodes have a similar voltage drop at a certain current. The home constructor could happily select the components but, in an industrial design, the cost of paying someone to grade components would mean that the real price of a 5p diode would be a lot more than 5p!

On the other hand, if too much decision-making on the part of the constructor is necessary to make a project work, then some of the people who build it will simply never succeed.

## Family Characteristics

Many of the marginal designs I have encountered have used CMOS, so this is the place to start.

The 4000 range of CMOS is designed to work over a wide range of power supply voltages. Different manufacturers specify slightly different operating characteristics at different voltages, but here I shall refer to the Mullard/Signetics HEF4000B range. Some of the family specifications are reproduced here for reference.

## Logic

### CMOS: HEF4000B family

book 4 part 4

#### Family Specification

D.C. characteristics  $V_{in} = 0V$ ; for all devices unless otherwise specified

parameter	$V_{DD}$	symbol	$T_{amb}$ (°C)						unit	conditions
			-40		+25		+85			
			min.	max.	min.	max.	min.	max.		
Quiescent device current	5									
gates	10	$I_{DD}$	—	1.0	—	1.0	—	7.5	$\mu A$	
	15		—	2.0	—	2.0	—	15.0	$\mu A$	
			—	4.0	—	4.0	—	30.0	$\mu A$	
buffers, flip-flops	5									
	10	$I_{DD}$	—	4.0	—	4.0	—	30	$\mu A$	
	15		—	8.0	—	8.0	—	60	$\mu A$	
			—	16.0	—	16.0	—	120	$\mu A$	
MSI	5									
	10	$I_{DD}$	—	20	—	20	—	150	$\mu A$	
	15		—	40	—	40	—	300	$\mu A$	
			—	80	—	80	—	600	$\mu A$	
LSI	5									
	10	$I_{DD}$	—	50	—	50	—	375	$\mu A$	
	15		—	100	—	100	—	750	$\mu A$	
			—	200	—	200	—	1500	$\mu A$	
Output voltage LOW	5									
	10	$V_{OL}$	—	0.05	—	0.05	—	0.05	V	
	15		—	0.05	—	0.05	—	0.05	V	$V_i = V_{DD}$ or $V_{DD}$ (1)
			—	0.05	—	0.05	—	0.05	V	
Output voltage HIGH	5									
	10	$V_{OH}$	4.95	—	4.95	—	4.95	—	V	
	15		9.95	—	9.95	—	9.95	—	V	$V_i = V_{DD}$ or $V_{DD}$ (1)
			14.95	—	14.95	—	14.95	—	V	
Input voltage LOW (buffered stages only)	5									
	10	$V_{IL}$	—	1.5	—	1.5	—	1.5	V	$V_O = 0.5V$ or $4.5V$
	15		—	3.0	—	3.0	—	3.0	V	$V_O = 1.0V$ or $9.0V$
			—	4.0	—	4.0	—	4.0	V	$V_O = 1.5V$ or $13.5V$
Input voltage HIGH (buffered stages only)	5									
	10	$V_{IH}$	3.5	—	3.5	—	3.5	—	V	$V_O = 0.5V$ or $4.5V$
	15		7.0	—	7.0	—	7.0	—	V	$V_O = 1.0V$ or $9.0V$
			11.0	—	11.0	—	11.0	—	V	$V_O = 1.5V$ or $13.5V$
Input voltage LOW (unbuffered stages only)	5									
	10	$V_{IL}$	—	1	—	1	—	1	V	$V_O = 0.5V$ or $4.5V$
	15		—	2	—	2	—	2	V	$V_O = 1.0V$ or $9.0V$
			—	2.5	—	2.5	—	2.5	V	$V_O = 1.5V$ or $13.5V$
Input voltage HIGH (unbuffered stages only)	5									
	10	$V_{IH}$	4	—	4	—	4	—	V	$V_O = 0.5V$ or $4.5V$
	15		12.5	—	12.5	—	12.5	—	V	$V_O = 1.5V$ or $13.5V$
Output (sink) current LOW	5									
	10	$I_{OL}$	0.52	—	0.44	—	0.36	—	mA	$V_O = 0.4V, V_i = 0$ or $5V$
	15		1.3	—	1.1	—	0.9	—	mA	$V_O = 0.5V, V_i = 0$ or $10V$
			3.6	—	3.0	—	2.4	—	mA	$V_O = 1.5V, V_i = 0$ or $15V$
Output (source) current HIGH	5									
	10	$-I_{OH}$	0.52	—	0.44	—	0.36	—	mA	$V_O = 4.5V, V_i = 0$ or $5V$
	15		1.3	—	1.1	—	0.9	—	mA	$V_O = 9.5V, V_i = 0$ or $10V$
			3.6	—	3.0	—	2.4	—	mA	$V_O = 13.5V, V_i = 0$ or $15V$
Output (source) current LOW	5									
	10	$-I_{OL}$	1.7	—	1.4	—	1.1	—	mA	$V_O = 2.5V, V_i = 0$ or $5V$
	15	$\pm I_{LH}$	—	0.3	—	0.3	—	1.0	$\mu A$	$V_i = 0$ or $15V$
3-state output leakage current: HIGH	15									
		$I_{OZH}$	—	1.6	—	1.6	—	12.0	$\mu A$	output returned to $V_{DD}$
3-state output leakage current: LOW	15									
		$-I_{OLZ}$	—	1.6	—	1.6	—	12.0	$\mu A$	output returned to $V_{SS}$

Note: (1)  $I_{OL} < 1\mu A$

66

Family specification of HEF4000B devices (with thanks to Mullard).

A number of circuits use a CMOS gate output to switch a transistor, which is used to control a relay, lamp, etc. Normally, a small signal transistor such as a BC182 is used to drive the load and, in order to work well, the transistor must be switched on hard. This requires adequate base current — a rule of thumb is to use a base current of 0.1 times the required collector load current. This can exceed the current which the gate is guaranteed to supply, though in fact most gates manage well over the minimum specified current.

It is not a good idea to rely on your good fortune in selecting a gate. Back on the industrial front, I recently had to investigate a rash of mysterious board failures, and discovered that one of the CMOS gates was being asked to deliver about twice its guaranteed output current. After a while, most gates from one batch failed, though the design had been produced without problems for several years beforehand. Presumably this batch of gates was unable to exceed its specification without damage.

To avoid this sort of problem in home projects, a CMOS gate sourcing current should have a load resistance of at least 1k $\Omega$  per volt of power supply. If this means that the transistor it is feeding receives insufficient base drive to switch properly, then the answer is to use a Darlington transistor, or two transistors connected as a Darlington pair.

*Most of the problems fall into the category of 'things which will work most of the time or work with certain examples of components used'...*

Alternatively, you could use a power FET suitable for the desired load current. A power FET capable of switching several amps may be driven directly by a CMOS gate. The switching speed may be low, because of the limited rate at which the CMOS output can charge or discharge the FET gate capacitance. The heavy load presented to the CMOS gate output by this capacitance is of short enough duration not to risk damaging the CMOS chip unless a high frequency switching signal is used.

There is one exception to these stern warnings about overloading CMOS outputs. When powered from a 5V supply, most CMOS chips are designed to be 'short circuit proof'. The practice of driving an LED from the output of a CMOS gate should not be harmful at this supply voltage, though the output will not provide a proper logic level when used in this manner. My recommendation is that this practice be confined to 'novelty' circuits, such as the infamous Thing.

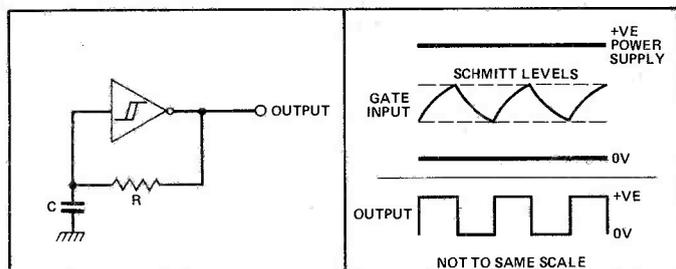


Fig. 1 Simple Schmitt oscillator. Fig. 2 Waveform diagram.

## Clock Oscillators

Many projects incorporate some sort of oscillator, which may be needed to clock a counter, or to generate an audible tone. Figure 1 illustrates a simple oscillator circuit, using a Schmitt trigger IC. As shown in the waveform diagram, Fig. 2, the capacitor charges through the feedback resistor until the voltage on it reaches the positive threshold of the Schmitt trigger gate. The output of the gate then switches to logic 0 and the capacitor starts to discharge until it reaches the lower Schmitt threshold.

There are two drawbacks to this circuit. The Schmitt levels may vary widely from batch to batch of the chip, and the output frequency of the circuit is directly dependent on these levels. Also, the threshold levels are not symmetrical with respect to the power supply (the characteristic of Schmitts known as hysteresis), so the mark-to-space ratio of the output wave is not unity. If the mark-to-space ratio is not important, the circuit may be made more acceptable by the addition of a potentiometer to fine tune frequency.

*Some aspects of circuit design seem to be ignored or glossed over by even the most seasoned practitioners...*

A more consistent circuit is shown in Fig. 3, and its waveform diagram in Fig. 4. The junction point of R2 and C1 alternately takes up voltages outside the power supply rails, and then charges or discharges to approximately half the power supply voltage. Because the voltage range over which the capacitor works is large, small differences in switching level between different samples of chip do not have much effect on the frequency or the mark-to-space ratio. The frequency is approximately  $1/(2.2 \times R2 \times C1)$ .

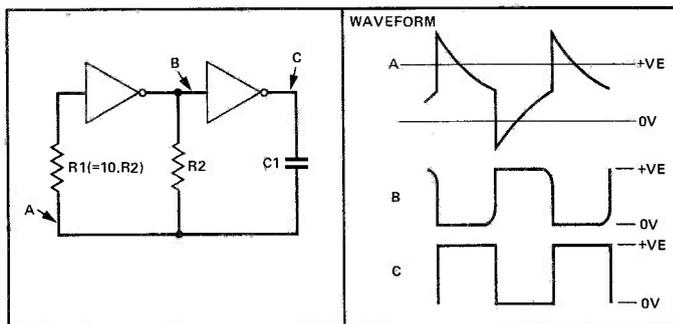


Fig. 3 Clock oscillator. Fig. 4 Waveform diagram.

Many project designers omit the resistor R1. If this component is omitted, then the junction of R2 and C1 is prevented from taking up a voltage outside the supply rails by the input protection diodes of the CMOS gate. The frequency is approximately three times the frequency given if R1 is included (and if R1 is, as specified, ten times R2). Variations in switching levels or gain between samples of chip now have a more significant effect, so the net effect is to decrease the predictability of the circuit's performance.

If very high value resistors are used in the circuit, then high frequency noise pickup on the input connected to R1 may be a problem. In this case, rather than lower R1 and make the operation less predictable, a capacitor of a few hundred picofarads may be added in parallel with R1. Practice has shown that this always solves the problem without any detectable effect on the correct operation of the circuit.

In some project designs, NOR or NAND gates are used instead of inverters. The 'spare' inputs may be used to gate the oscillator and turn it on or off in response to a logic signal. A logic 0 signal will stop a NAND gate oscillator, while a logic 1 will stop a NOR gate oscillator. If it is necessary to start to clock a counter immediately the oscillator is started, then the rest of the oscillator should be considered. For example, if the signal is generated by pressing a switch, the response should be immediate or the user may begin to wonder if it is working.

*Data books never claim that a circuit will work precisely as well under all circumstances. . .*

The circuit shown in Fig. 5 will generate a positive edge on its output immediately a logic 0 is applied to its control input. By its nature, the circuit in its inhibited state will always charge its capacitor in such a way that it ready to switch as soon as it is allowed to do so.

## Op-Amps

The correct use of op-amps is another area which seems to be difficult for some project designers. There are several aspects which cause problems.

First of all, some designers simply fail to take account of the input bias and offset current. If a bipolar op-amp is used, the bias resistors should be of a low enough value that the voltage drop in them is small. I recall seeing a reader's circuit in one electronics magazine, showing a 741 connected with all the bias current for the negative input flowing through a 4M $\Omega$  resistor.

A good rule is to make the bias resistors as low as the rest of the circuit design allows, and to make the total DC resistance connected to each input the same. In this way, the difference in voltage between the two inputs (the offset) is determined by the difference in bias current between the two inputs (the input offset current) rather than the total bias current. If the offset is still too large, then a FET input amplifier should be used.

The open loop gain of an op-amp also seems to confuse some people. The text of the reader's circuit mentioned above stated, 'the maximum gain of a 741 is quoted as 20,000, but in this circuit it is wired to provide a gain of 47,000'. This mistake arises from a misunderstanding about the way the op-amp's gain is determined. The gain is determined by the ratio of the two feedback resistors in the circuit. You can use any ratio you please, but you cannot make the op-amp give more than its maximum open loop gain.

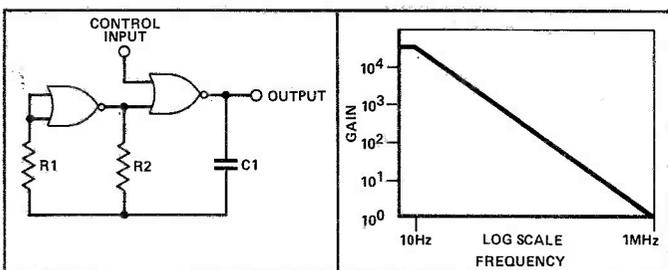


Fig. 5 An instant turn-on.

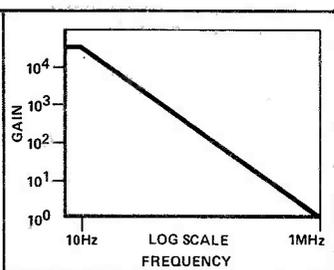


Fig. 6 Typical frequency response of an op-amp.

A typical op-amp frequency response is shown in Fig. 6. There are two relevant and related factors, the open loop gain and the gain-bandwidth product. The open

loop gain defines the maximum low frequency gain the op-amp can produce under any circumstances, and the gain-bandwidth product indicates the increase in gain with decreasing frequency.

An op-amp having a gain-bandwidth product of 1MHz, for example, will have an open loop gain of unity at a frequency of 1MHz. As the frequency is decreased, this gain will rise until the maximum open loop gain is reached, often at a frequency of about 10Hz.

## Totally Slewled

The effects of output slew rate limiting and of power supply variations on op-amp characteristics are clearly illustrated by a mistake of mine, made when 741s were the normal choice of op-amp for any task. In a car project, I used a 741 to clock a CMOS counter. According to the data books, the slew rate of the output of a 741 is inadequate to clock the CMOS counter reliably, but still the circuit seemed to work — at least some of the time. After a little experimenting, I found that the car battery voltage affected the circuit. It all worked well when the engine was running and the lights were turned off, but couldn't be relied on when the battery was being drained and its voltage dipped.

It seems that the op-amp's slew rate was slightly higher when the voltage was higher. This was just enough to make the counter clock on.

The moral of this is that the slew rate of the op-amp can be crucial, and that you should not assume that a characteristic which is specified to be just good enough with, say, +/- 15V power supplies will still be alright at lower voltages. This is true even though the op-amp may be specified to work at much lower voltages. Data books never claim that a circuit will work precisely as well under all circumstances.

## Passive Components

There are two common areas of misunderstanding which I have noticed in the use of passive components. The problem with resistors is very simple: ordinary quarter-Watt resistors have too low a voltage rating to be connected to the mains. Resistors rated 1/2 Watt and greater have a higher voltage rating and are therefore generally okay to connect to the mains. The voltage rating of a resistor can limit the maximum power that can be fed into it to less than its nominal wattage rating.

The other point of misunderstanding is in the use of non-polarised capacitors on AC, specifically when connected to the mains. Most people realise that a capacitor to be used on AC should have a DC rating equal to the peak of the AC waveform, but the problem does not stop there.

At any significant frequency, above a few Hertz, the voltage which the capacitor can withstand is reduced, because the chemical bonds in the dielectric material are stressed first one way then the other by an AC waveform, and in this process power is dissipated. Weak spots in the dielectric can become hot spots if subjected to AC waveforms, and can subsequently break down. Dielectric materials with higher levels of AC power dissipation suffer from this problem more severely. Generally, polypropylene capacitors are much better than polyester, while ceramics come in widely varying qualities.

One type of polyester capacitor, for example, is rated at 400VDC, 150VAC at 50Hz. A high quality polypropylene capacitor in the same catalogue is rated at 1000VDC, 350VAC at up to 5kHz. Some mica capacitors are rated to handle substantial RF signals. **ETI**

# CAPACITANCE METER MODULE

This free PCB project gives your multimeter extra capacity.

A multimeter is an essential item for anyone with an interest in electronics, but it has its limitations. Few will measure anything more than voltage, current and resistance, but there is no reason why this range should not be extended by the addition of a little extra circuitry. The module described in this project produces an output voltage proportional to the value of a capacitor connected to its terminals, and can be connected to a multimeter on a low voltage range to give direct capacitance readings. The accuracy is surprisingly good for such a simple circuit and you can have just as much confidence in the capacitance readings as you would in the meter's own resistance ranges.

## Methods

Two common methods of measuring capacitance are the bridge method, which you can read about in the RCL bridge project (ETI August, 1985), and the monostable method. The bridge method is notionally capable of great accuracy, since its readings are independent of the accuracy of the meter movement, but the full potential is rarely realised in any but the most expensive

instruments. Precision components must be used since the bridge effectively compares a known value and the unknown one at the terminals. The most awkward point, from a home construction point of view, is the need to construct an accurate scale for the balancing pot. If unlimited numbers of precision components are available, the scale can be calibrated directly. Otherwise the constructor is faced with the problem of trying to interpolate a highly non-linear scale between the readings that can be made. Unpredictable non-linearities in the pot itself make matters worse.

An attractive idea is to measure some circuit parameter which is related to capacitance, and thus derive a direct reading. A common method is shown in Fig. 1.

The monostable is triggered at regular intervals by a pulse from an oscillator. The monostable is designed to have a timing period proportional to the value of the timing capacitor, which is the unknown capacitor. Assuming the oscillator runs at a fixed frequency and the monostable output pulses are of constant amplitude, the mark-to-space ratio of the monostable output, and hence the average voltage across C1, will be

proportional to the value of the unknown capacitor. R1 and C1 are chosen to give a reasonable compromise between ripple and settling time.

This type of circuit can work well or not so well, according to the care taken over the design. One point to note, however, is that there are three circuit parameters which must be accurately controlled: the oscillator frequency, the output amplitude of the monostable, and the linear relationship between the unknown capacitor value and the monostable period. Drift in any of these will cause a proportional change in the output voltage. If the number of critical areas can be reduced, it seems reasonable to expect a corresponding improvement in the accuracy of the meter.

Without increasing circuit complexity, another arrangement is possible (Fig. 2a). The oscillator produces an output of constant frequency and amplitude which is applied via R1 to the unknown capacitor. When the oscillator output is low, Cx will discharge via D1. When the oscillator output rises, charge is transferred from Cx via D2 to C1. (R1 is just a current limiting resistor.) Assuming that the rise in voltage across C1 is negligible, the amount of charge transferred is easily calculated: it will be  $V.C_x$ , where V is the high output voltage of the oscillator. This charge transfer will take place  $f$  times a second, where  $f$  is the oscillator frequency, so the total charge transferred every second (in other words, the average current) will be  $f.V.C_x$  amps. The average voltage across R2 will therefore be  $R2.f.V.C_x$  volts. As R2, V and  $f$  are constant, the voltage across R2 will be proportional to  $C_x$ ... or will it?

The assumption I slipped in earlier on, that the rise in voltage across C1 should be negligible,

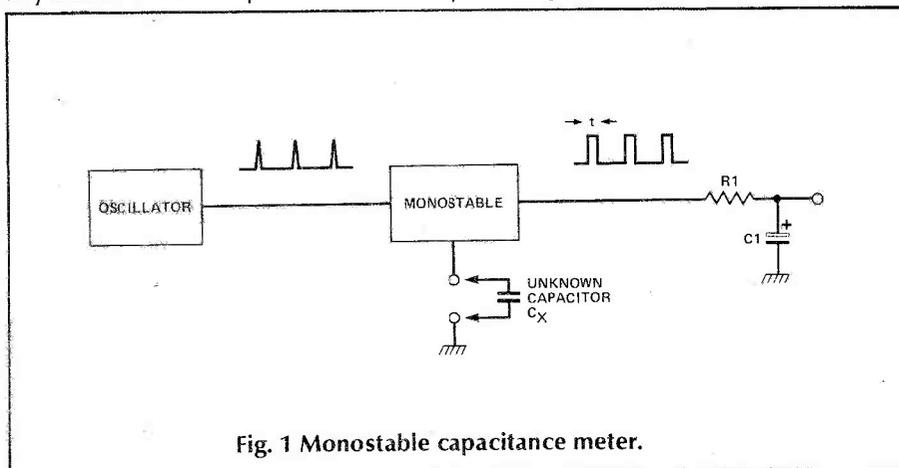


Fig. 1 Monostable capacitance meter.

Fig. 2a Charge pump capacitance meter.



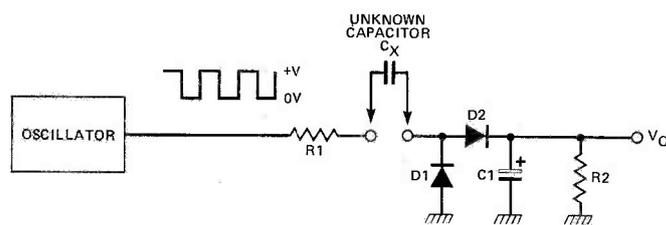


Fig. 2b Linear charge pump capacitance meter.

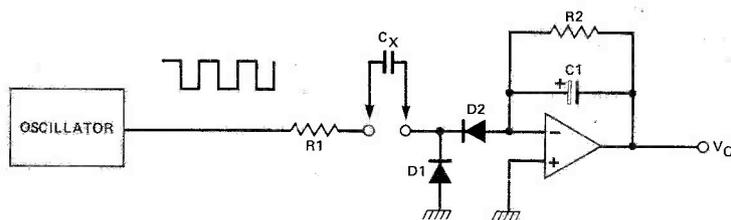

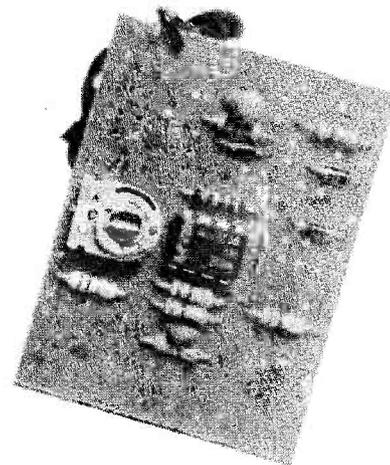of small capacitance values; RV1 is adjusted for an output of 1V per 100p, so on a 10V meter range you can make readings up to about 800p (remembering that the output voltage of the module is limited by the battery voltage) or readings of 0 to 100pF on a 1V meter range. As the output is linear, a reading of 2V2 would mean 220p, 4V7 will be 470p, and so on.



imposes an unfortunate restriction since this is the voltage used as an output. As it rises, it reduces the voltage available to pump charge through  $C_x$  and so, as the value of  $C_x$  rises, the corresponding increase in the output voltage gets progressively smaller. In other words, the relationship between capacitance and output voltage is not really linear at all. Reasonable results can be achieved by limiting the output to a low voltage (0 to 100mV, say) but to make the circuit truly linear  $C_x$  should transfer charge into a constant voltage.

In the diagram of Fig 2b, a virtual earth current to voltage converter has been added to provide a constant voltage point for the charge transfer, as in this project. The diodes have been

reversed so that an increase in capacitance will still give an increase in output voltage. As the average current flowing from the virtual earth via D2 will equal the average current through R2, the output voltage is still equal to  $R_2 \cdot i \cdot V \cdot C_x$ .  $C_1$  is chosen to give a reasonable settling time without excessive ripple and  $R_1$  is chosen so that  $R_1 \cdot C_x$  is very small in relation to the oscillator period for the largest value of  $C_x$  to be measured, while limiting the peak current to a value that the oscillator output can cope with.

### Circuit

The final circuit is shown in Fig. 3. IC1a forms the oscillator and IC1b the virtual earth current to voltage converter. The component values shown are for measurement

### HOW IT WORKS

IC1a and the components around it form an oscillator which produces a square wave output at about 8KHz, adjustable by RV1. One of the features of the LM358 is that its output is quite happy to go down to the negative supply rail without disturbing the operation of the feedback. Unfortunately, the IC won't pull the output down quite that far of its own accord — an external resistor ( $R_5$ ) is necessary.  $R_6$  performs two functions: it is the equivalent of  $R_1$  in Fig 2b, and it is also the ballast resistor for the zener, D1.

D1 clips the output of IC1a at about 5V, giving a square wave of fixed amplitude. D3 holds the 'right hand' plate of  $C_x$  at the negative supply voltage during high outputs from IC1a; D2 allows  $C_x$  to draw current from the virtual earth at IC1 pin 6 when IC1a output goes low.

The current to voltage converter around IC1b makes use of another useful characteristic of the LM358: it remains in linear mode when one or both of its inputs are at the negative supply voltage. This means that pin 5 can be taken directly to the negative supply, giving a circuit with very few passive components.

$R_7$  produces a voltage at the output of IC1b proportional to the current drawn from pin 6.  $C_2$  smoothes out the fluctuations so that the voltage across  $R_7$  is proportional to the average current.  $R_8$  is once again included to pull the output of IC1b to the negative supply so that the meter will give a zero reading when no capacitor is connected.

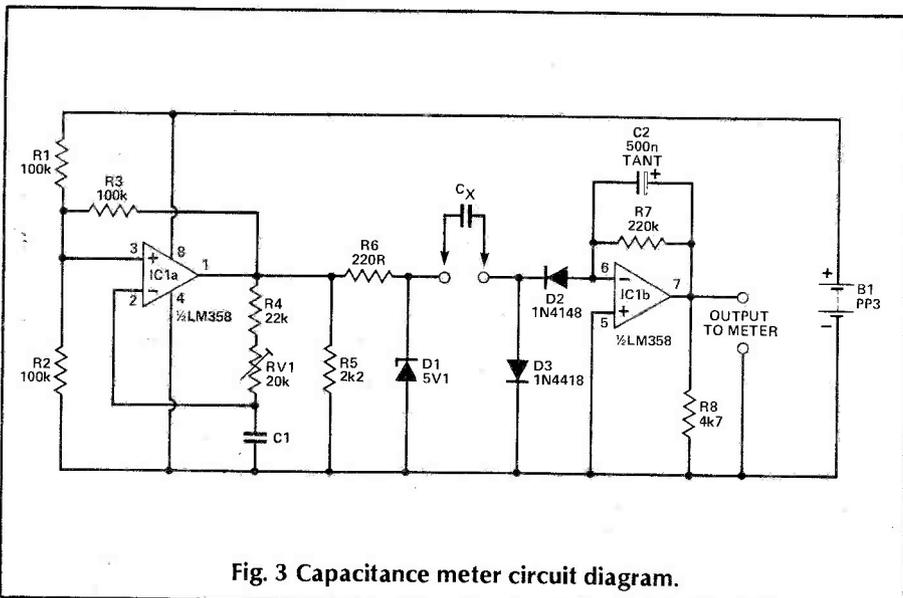


Fig. 3 Capacitance meter circuit diagram.

# PROJECT: Capacitance Meter


For different ranges, all that is necessary is to change the value of C1, as shown in Table 1. Although there is no room for the additional components on the PCB, the circuit can be adapted without difficulty to give a multi-range instrument, as shown in Fig. 4. The additional capacitors and presets could be mounted on a small piece of veroboard, or could even be soldered directly to the switch. The values from Table 1 should be followed, so C1a would be 1n (for the 1V per 100p range), C1b is 10n, and so on. To make the best use of the higher ranges, it would be a good idea to increase the value of C2 to 10 $\mu$ .

## Calibration

The component layout for the project is shown in Fig. 5. It is a good idea to check component positions carefully, since the locations are not all used and mistakes are easily made. To calibrate the instrument, you will need a 1% tolerance capacitor for each range. For best results, set your multi-meter to the 10V range and use a capacitor which will give a half-scale deflection. For instance, on the 1V per 100p range, use a 500p capacitor and adjust RV1 for a meter reading of 5V.

C1	1n	10n	100n	1 $\mu$	10 $\mu$
Range	1V=100p	1V=1n	1V=10n	1V=100n	1V=1 $\mu$

Table 1 Values of C1 required for various ranges.

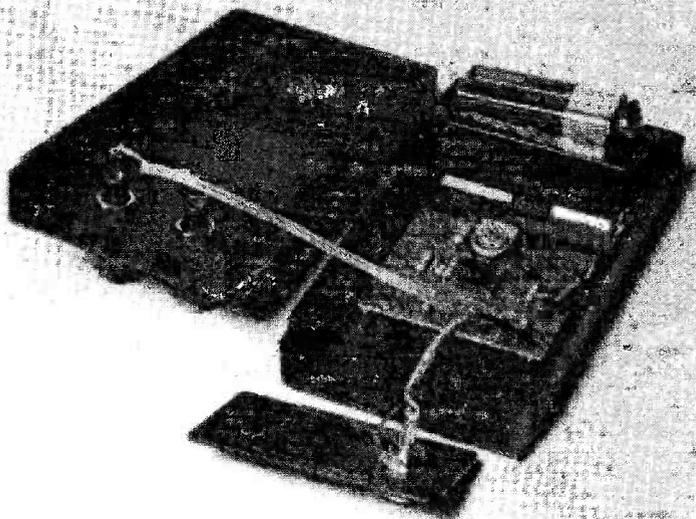

## PARTS LIST

### RESISTORS (all 1/4W 5%)

R1	100k
R2	100k
R3	100k
R4	22k
R5	2k2
R6	220R
R7	220k
R8	4k7
RV1	20k miniature horizontal preset

### CAPACITORS

C1	1n
C2	500n 10V tantalum

### SEMICONDUCTORS

IC1	LM358
D1	4V7 or 5V1 zener
D2, 3	1N4148

### MISCELLANEOUS

PP3 battery clip, PP3 battery, BC3 box with battery compartment.

## BUYLINES

None of the components used in this project should present the slightest difficulty. However, you may be interested to know that the LM358 ICs are available to ETI readers at the special price of 5 for £2, inclusive, from: Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent. A box with a PP3 battery compartment to house the project is available for £2.80 from the same address. Spare printed circuit boards can be obtained by sending £1 and a stamped, self-addressed envelope to: ASP Readers Services, PO Box 35, Wolsey Road, Hemel Hempstead, Herts. HP2 4SS.

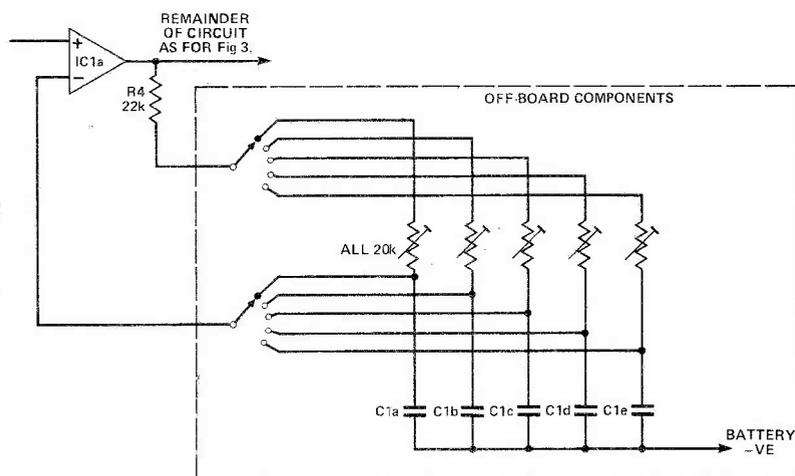


Fig. 4 Switching arrangement for a multi-range meter.

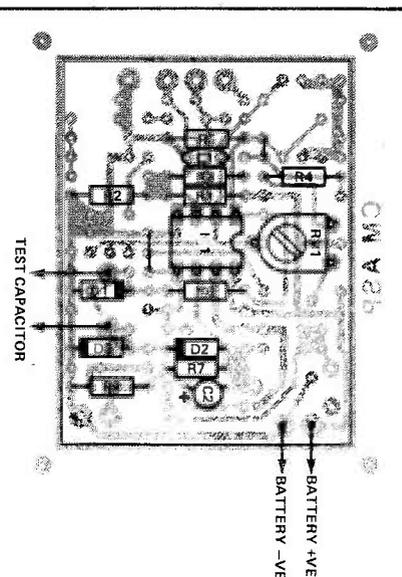


Fig. 5 Component overlay for capacitance meter.

ETI

# MEMO MINDER

In a phrase, a lighthouse on a board. Amazing, but true! ETI's free PCB shows that it's more than just a flash-in-the-pan. Not much . . .

'What ETI really needs,' ruminated Alf, absentmindedly syringing his ears with a solder sucker, 'is something completely different.' The wind howled around ETI Towers and rain lashed the windows of as Flea-byte drew his chair closer to the solitary candle which spluttered fitfully, as solitary candles will, in the centre of the floor. 'What did you have in mind?' he asked. 'Well, I can't remember the last time we had a project,' said Alf thoughtfully, 'to flash an LED.'

Flea-byte resisted the temptation to put the solder sucker to better use and Auntie Static reverted to her background program. This would be a bad winter for her diodes, she sensed it in her sprockets, and having to listen to Alf's blathering didn't help matters in the least.

Alf, realising that his genius would once again go unrecognised, stomped off to make adjustments to an oscillator. Outside, it was raining cats and dogs, speckled geese and the occasional marmoset. It was that kind of day. A lone police car, searching for a mate, wailed plaintively from the Soho wilderness. Suddenly, Auntie's photocells began to twinkle. A half forgotten mini-flopperama diskette, an unwise purchase from Carnaby Street in the late Sixties, had engaged in her disk drive and was infusing her with vital statistics. 'Gather round, my friends,' she said, 'I think I've got the answer.'

## The Auntie's Tale

Auntie quickly outlined the story of the two itinerant coal porters who had patented a device for minding buildings when the owners were away. Their invention was a light which would be illuminated as long as the building remained in place, but would go out if it was stolen, so that anyone could see at a glance whether the house was still there

or not. Theft of darkhouses, as they were called at the time, was rife, but since the invention of the 'houseminder' security light, very few of these seaside homes have been moved.

The next stage of development had to await the arrival of a child to the Kunn family, who had an astonishing degree of foresight in naming their offspring after the light he would one day invent. Belisha B. Kunn it was who adapted the lighthouse principle to produce a 'roadminder' to preserve small sanctuaries of whiteness on an otherwise black road surface. These areas are now great tourist attractions; indeed the more popular ones are so crowded that it is hard to stop and admire the handiwork of the artist who painted them on.

Further reference to the invention can be found in the diaries of Arthur Daley . . . 'And that,' concluded Auntie, 'is the story of the minder. Why don't we do a miniature version for looking after memos?'

'Sounds OK to me,' said Alf, 'but what are we going to write about it?' 'Oh, I think we could get away with just a Parts List and a "How It Works",' said Auntie. 'After all, nobody ever reads the rest of the article anyway.'

## HOW IT WORKS

IC1 contains an infra red LED and phototransistor. When the LED is illuminated the beam will normally fall on the phototransistor, allowing it to conduct and pull the inverting input of IC2a low. If the beam is interrupted by a memo being placed in the slot between the LED and detector, the phototransistor will cease to conduct and the inverting input of IC2a will go high. IC2b and the components around it form an oscillator to flash the LED once a second. When the output of IC2a is low, it has no effect on the oscillator since D1 will be reverse biased. If IC2a output goes high, the oscillator capacitor will be kept at full charge, since R5 is much smaller than R8; IC2b will cease to oscillate and the LED will be extinguished.

The result of all this is that when a memo is held in the slot of IC1, the LED will flash to attract attention to it.

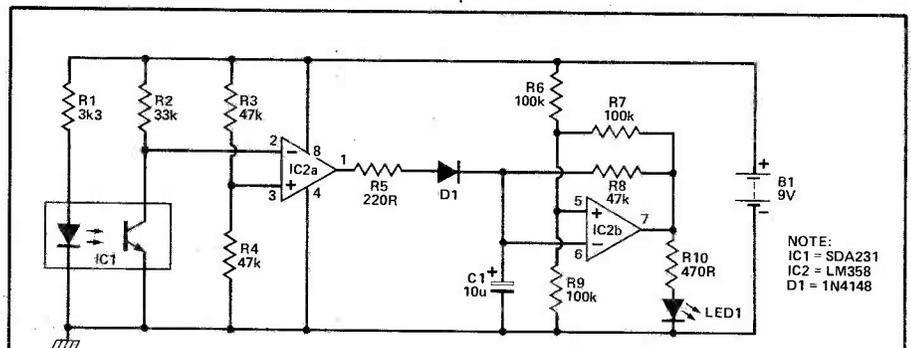


Fig. 1a Circuit of memo minder.

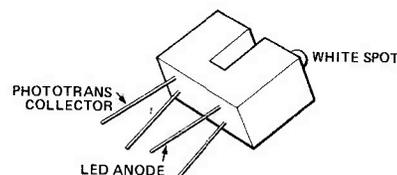


Fig 1b Pin-out of the SDA 231.

## PARTS LIST

### RESISTORS (all 1/4W 5%)

R1	3k3
R2	33k
R3	
R4	47k
R5	220R
R6	100k
R7	100k
R8	47k
R9	100k
R10	470R

### CAPACITORS

C1 10 $\mu$  10v tant.

### SEMICONDUCTORS

IC1 SDA231

IC2 LM358

D1 1N4148

LED1 3mm LED, the colour of your choice.

### MISCELLANEOUS

PP3 battery connector,  
PP3 battery.

## BUYLINES

The SDA 231 slotted opto switch is available from Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent. Price 80p. They will supply the LM358 ICs to ETI readers at the special price of 5 for £2. Extra printed circuit boards can be obtained by sending £1 and a stamped, self-addressed envelope to: ASP Readers Services, PO Box 35, Wolsey Road, Hemel Hempstead, Herts. HP2 4S.

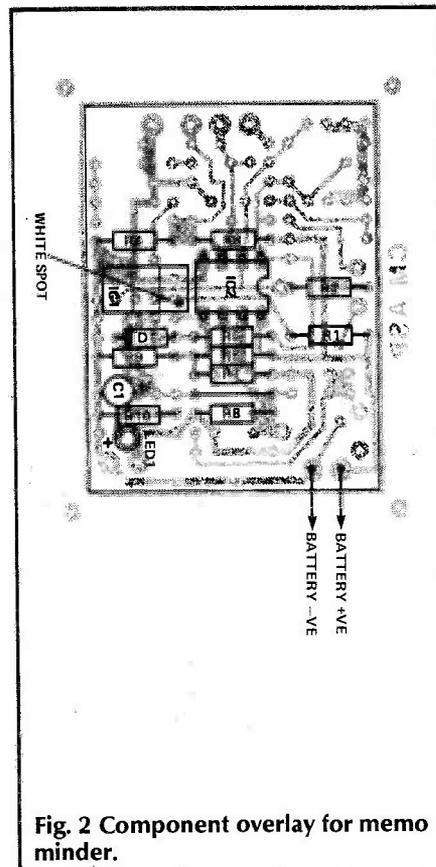
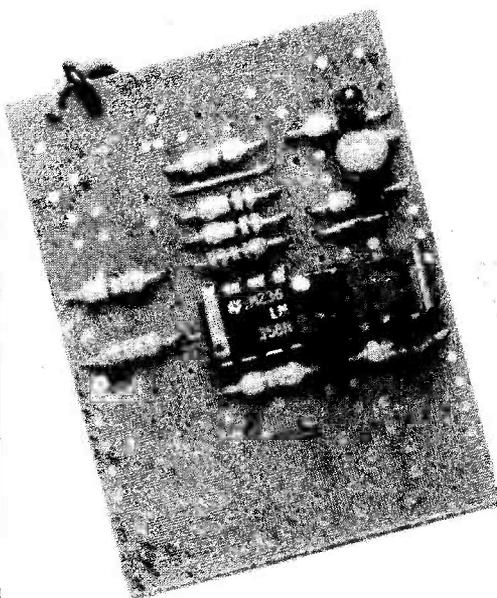


Fig. 2 Component overlay for memo minder.

ETI

ONLY  
£1.15

# Cirkit

Spring 1986

## Electronics Component Catalogue OUT NOW!

- ★ New kits include transverter and PA for the new 6m band.
- ★ Computer add-ons for the Amstrad CPC series.
- ★ Linear IC data with pin outs.
- ★ Plus the usual extensive range of components for all your construction needs.

The Spring catalogue is on sale now at your newsagent or direct from our sales counter at Broxbourne, Herts – Brentwood, Essex and Portsmouth, Hants.

### Cirkit Distribution

Park Lane, Broxbourne, Herts, EN10 7NQ Telephone (0992) 444111 Telex 22478

200 North Service Road,  
BRENTWOOD  
Essex CM14 4SG

53 Burrfields Road  
PORTSMOUTH  
Hampshire PO3 5EB

Park Lane  
BROXBOURNE  
Herts EN10 7NQ

# RIAA AND NAB EQUALISATION STAGES

The free PCB demonstrates that it has an ear for a good tune. Start here for the ultimate in low-cost stereo.

A stereo pre-amplifier which can give either RIAA magnetic pickup equalisation, or NAB standard tape equalisation, is the final offering

for this month. Used with the 'matchbox amplifier' to be featured next month, a low cost, powerful sound system can be assembled in no time!

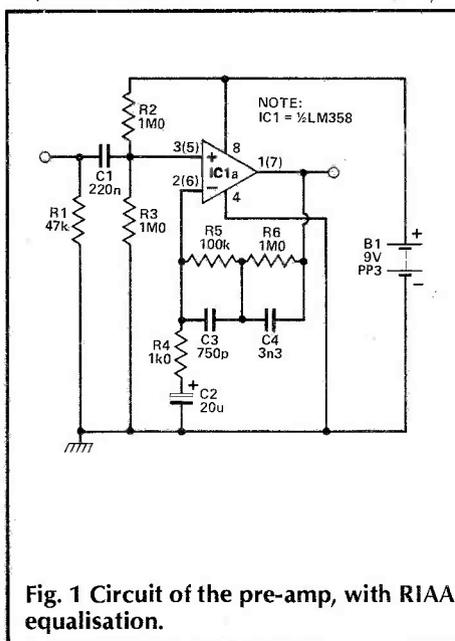


Fig. 2 Circuit of the pre-amp, with NAB equalisation

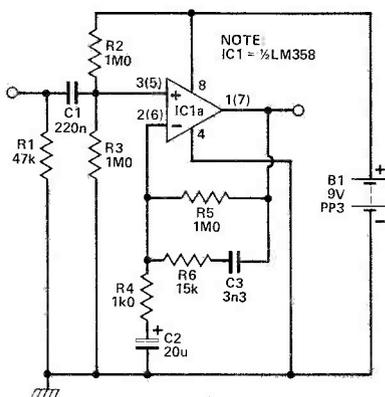


Fig. 1 Circuit of the pre-amp, with RIAA equalisation.

## HOW IT WORKS

The LM358 is connected as a shunt feedback amplifier with some additional components in the feedback network to tailor the frequency response. The NAB equalisation standard requires a roll-off of 6dB per octave to begin at 50Hz and continue to 3180Hz, at which point it levels off again. In Fig. 2, if the effect of C2 are ignored, the low frequency gain of the circuit will be determined by R5 and R4, and will be 1000. By 50Hz, the impedance of C3 has dropped sufficiently for it to have a significant effect on the gain of the circuit, which will be reduced by about 30% at this frequency, giving the first -3dB point.

The gain continues to drop until the impedance of C3 is comparable with the resistance of R6, at which point any further drop in its impedance will have less and less effect on the gain. At high frequencies, therefore, the gain levels out and is determined by R6 and R4. It will be about 15.

The RIAA circuit operates in a similar way, with the addition of another turnover point introduced by C4.

## BUYLINES

The LM358 ICs are available to ETI readers at the special price of 5 for £2 from: Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent. Extra printed circuit boards can be obtained by sending £1 and a stamped, self-addressed envelope to: ASP Readers Services, PO Box 35, Hemel Hempstead, Herts. HP2 4SS.

## COMPETITION

Why not use your own ingenuity to design a circuit for our free PCB? The sender of the winning entry will receive £40 and the two runners up will win £20 each. We will publish the winning circuits later in the year. The circuit should fit neatly onto the board, without components soldered to the back, and we will be looking for original, well presented and elegant designs.

Entries should include a circuit diagram, component layout, a

parts list and a description of the circuit (typed, please, and not more than 750 words in length.) If you are not the kind of person who has circuits published, have a go anyway. You may find out that you are!

Send your entries to: ETI (FP), 1 Golden Square, London W1R 3AB. Please enclose a stamped, self-addressed envelope if you want your entry returned and, please, no submissions after 2 May, 1986.

# PROJECT: Equalisation stages

## PARTS LIST

RIAA		C3, 103		750p		R4, 104		1k	
RESISTORS (all 1/4W, 5%)		C4, 104		3n3		R5, 105		1M	
R1, 101	47k	SEMICONDUCTORS		IC1		LM358		CAPACITORS	
R2, 102	1M	MISCELLANEOUS		PP3 battery connector,		PP3 battery.		C1, 101	220n
R3, 103	1M	RESISTORS (all 1/4W, 5%)		R1, 101		47k		C2, 102	20µ 10V tant.
R4, 104	1k	R2, 102		1M		R3, 103		1M	
R5, 105	100k	R3, 103		1M		SEMICONDUCTORS		IC1	
R6, 106	1M	CAPACITORS		C1, 101		220n		MISCELLANEOUS	
C1, 101		220n		C2, 102		20µ 10V tant.		PP3 battery connector,	
C2, 102		20µ 10V tant.		PP3 battery.					

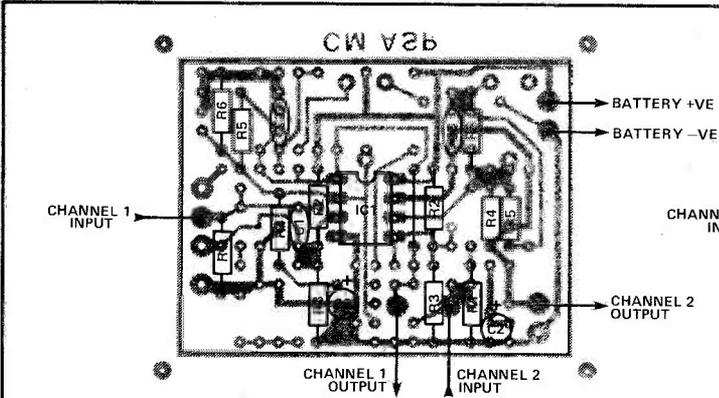


Fig. 3 Component overlay for the RIAA circuit — duplicated components are distinguished in Parts List.

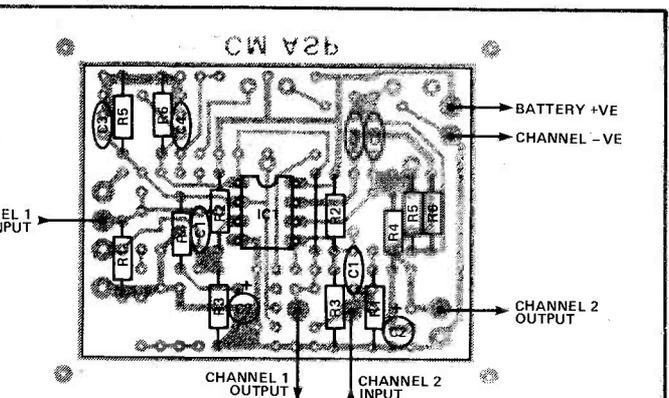


Fig. 4 Component overlay for the NAB circuit — duplicated components are distinguished in Parts List.

ETI

## Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.



## New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

**FREE! COLOUR BROCHURE** OR TELEPHONE US 062 67 6114 OR TELEX 22758 (24 HR SERVICE)

Please send your brochure without any obligation to

NAME \_\_\_\_\_ I am interested in

ADDRESS \_\_\_\_\_  ELECTRONICS

MICROPROCESSORS

RADIO AMATEUR LICENCE

CITY & GUILDS EXAMS

Other Subjects \_\_\_\_\_

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS

## Time Machine

### SOUND ENGINEERING of Devon

ANNOUNCE AN EXCITING NEW RANGE OF STUDIO QUALITY PROCESSORS, AMPLIFIERS AND ANCILLARIES, IN STACKABLE 8 1/2" CASES 1U HIGH.

**DI Compression Gate**  
Sophisticated signal conditioner combining the functions of NOISE GATE, COMPRESSOR & DIRECT INJECT BOX. Minimum of controls for maximum ease of operation. Musical performance and strappable for stereo operation. 4-LED display of gain reduction and tricolour indication of gate status.

**Activator**  
Psychoacoustic enhancer offers performance rivaling that of £400 units yet is easier to use, with sophisticated filtering, semi-automatic operation and an "intelligent" display.

**Microamp**  
Compact, stereo power amplifier with the reliability and superb performance of MOSFET technology. 30 Watts rms per channel into 8Ω or bridgeable for 60W mono. True clip indication and soft limiting.

**PSU**  
The tidy answer to power supply problems. Housed in a 13A plug, this supplies ±15V at 200mA per rail for powering TIME MACHINE processors. Supplied with a sensible 2 metre cable terminated in a 3-pin DIN plug (regulated voltage).


Coming soon: **LEVELLOR MULTIBAND COMPRESSOR**  
**TIME MACHINE ONE REVERB/DELAY/HARMONISER**

All TIME MACHINE products have attractively styled steel cases bristling with inputs and outputs, balanced and un-balanced, have knobs you can get your fingers between with metal shafts that don't break as soon as you look at them, offer remarkable specifications at affordable prices, are made in Britain and have manuals written in clear English. Need we say more? If so send a decent size SAE to:

Time Machine, (ETI), Abbotsford, Deer Park Avenue, Teignmouth, Devon, TQ14 9LJ. Tel: 06267 2353.

Cheques payable to 'TIME MACHINE'. Please allow 3 to 21 days for despatch. All prices include VAT, postage and packing.

# PROGRAMMABLE LOGIC EVALUATION BOARD

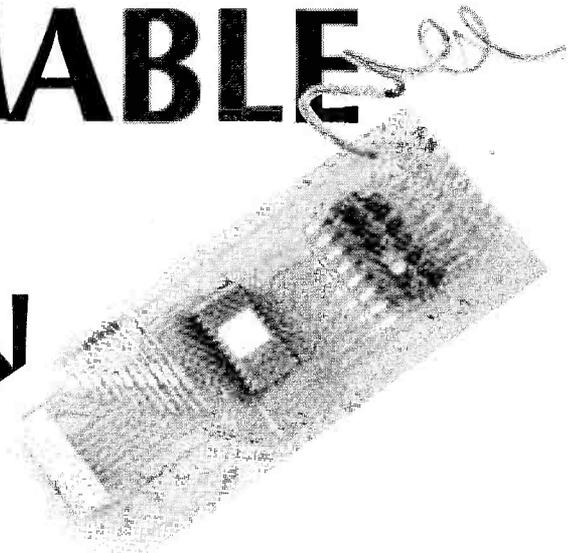

In a follow-up to his article on programmable logic in last month's issue, Mike Bedford describes a simple evaluation board which will allow readers to experiment for themselves.

In last month's Digital Superglue article, the whole realm of custom, semi-custom and programmable logic devices was investigated. It is quite out of the question for the amateur electronics enthusiast to make use of custom or semi-custom chip technology but the use of programmable logic, on the other hand is quite feasible.

It was shown that programmable logic devices are divided into three categories, namely PALs, FPLAs and PROMs. Of these, PALs and FPLAs are the most flexible but, for reasons mentioned in the article, are also the most difficult to program. It would not be impossible for the amateur to design and build a PAL programmer, but whilst this would prove interesting it would also be extremely ambitious.

PROMs, on the other hand, although less flexible are more easily programmed. EPROMs in particular would make an ideal programmable logic device for home electronics use since many people now have EPROM programmers operating in conjunction with home

## BUYLINES

The PCB is available as usual from the ETI PCB service. The other components are quite standard and should be easily obtainable from any other source. If a 12 way DIL switch proves to be a problem then two or more smaller DIL switches could be stacked end to end.

computers. The theory of using EPROMs in programmable logic arrangements is identical to the concept of using PROMs and was fully covered last month. The purpose of this article is to present both a BASIC program and an experimentation board to allow the amateur to investigate this technology in a practical way.

## Basic Program

To recap a little on what was said in the feature article, a PROM (or EPROM) is an example of an AND/OR array. This is an arrangement which allows any Boolean sum-of-products function to be implemented, dependent only on there being sufficient inputs and outputs. Since any Boolean transfer function may be expressed in this form, it follows that any such functions could be programmed into an EPROM. As in all custom, semi-custom and programmable chip design, computer assistance is required for all but the simplest of cases. The purpose of the BASIC program presented here is to convert Boolean equations entered by the user into a hex dump of the data required to program into the EPROM. Alternatively, the program will write the data to a block of memory where it may be accessed by an EPROM programmer.

The design software listing (Listing 1) is written in BASIC but not specifically for one machine.

Instead of using a particular dialect and hence special features which may only be applicable to one computer, the program has been written in standard Microsoft BASIC. It should prove a simple task to get it running on any machine. The only areas which may prove to be a problem on some computers are the long IF statements, such as that at line 490. If the version of BASIC in use does not support sufficient continuation lines, it will have to be split into a number of separate IF statements.

The following is a brief description of the way the program works. Lines 300-700 prompt the user for the number of inputs and outputs to be used followed by the Boolean equations, one for each output in use. Within this loop, lines 430-570 carry out syntax checking of the equations, print an error message, indicate the offending character and re-prompt where necessary. Also in this input loop, lines 500-690 add brackets to the equations in order to prioritise the operators such that ANDs are carried out before ORs. The main loop of the program, lines 710-1000, then executes for each memory location used within the EPROM which in turn is equal to 2 to the power of the number of inputs used. For each location the elements of D%() are set to the binary bits of the address. These values are then 'plugged in' to

```

100 REM *****
110 REM * PROGRAM : PROM
120 REM * AUTHOR : MIKE BEDFORD
130 REM * DATE : AUGUST 1985
140 REM *
150 REM * PURPOSE : TO GENERATE PROGRAMMING
160 REM * INFORMATION FOR A 2716
170 REM * EPROM TO ALLOW A SET OF
180 REM * BOULLEAN EQUATIONS TO BE
190 REM * IMPLEMENTED.
200 REM *
210 REM *
220 REM *****
230 DIM ARR$(2048),X$(16),E$(8),EON$(8),BAZ(20),IB$(20),NVZ(20),
    OP$(20),DX(11),ODZ(8),OVZ(8)
240 URZ = 32000% : REM *** SET TO HIGHEST AVAILABLE RAM ***
250 XX$="0123456789ABCDEF"
260 FOR NZ=0% TO 15%
270 X$(NZ)=MID$(XX$,NZ+1%,1%)
280 NEXT NZ
290 PRINT : PRINT "ETI BOULLEAN TO EPROM PROGRAM FOR 2716" : PRINT
300 INPUT "INPUTS, OUTPUTS USED";ITZ,OTZ
310 IF ITZ<1% OR ITZ<1
    THEN PRINT "INPUTS SHOULD BE IN RANGE 1-11" : GOTO 300
320 IF OTZ>8% OR OTZ<1
    THEN PRINT "OUTPUTS SHOULD BE IN RANGE 1-8" : GOTO 300
330 REM ... INPUT AND SYNTAX CHECK EQUATIONS - ONE PER OUTPUT USED
340 FOR NZ=0% TO OTZ-1%
350 PRINT "OUTPUT";NZ;"=";E$(NZ);
360 INPUT E$(NZ)
370 EON$(NZ) = ""
380 FOR IZ=1% TO LEN(E$(NZ))
390 C$=MID$(E$(NZ),IZ,1%)
400 IF C$=" " THEN 420
410 EON$(NZ) = EON$(NZ)+C$
420 NEXT IZ
430 IF LEN(EON$(NZ))=0% THEN 350
440 BCZ=0% : L$="( "
450 FOR IZ=1% TO LEN(EON$(NZ))
460 C$=MID$(EON$(NZ),IZ,1%)
470 IF C$=" " THEN 550
480 IF ((C$<"0" OR C$>"9") AND C$<"(" AND C$<")" AND C$<"/"
    AND C$<"A" AND C$<"+" AND C$<"*") THEN
    PRINT TAB(IZ+11%);"" : PRINT "INVALID CHARACTER" : GOTO 350
    OR (L$="( " AND (C$="*" OR C$="+" OR C$=")"))
    OR (L$=")" AND (C$="(" OR C$="/" OR (C$>"0" AND C$<="9")))
    OR (L$="/" AND C$<"(" AND (C$<"0" OR C$>"9"))
    OR ((L$="+" OR L$="*" AND (C$="+" OR C$="*" OR C$=")"))
    OR ((L$>"0" AND L$<="9")
    AND (C$="( " OR C$="/" OR (C$>"0" AND C$<="9")))
    THEN PRINT TAB(IZ+11%);"" : PRINT "SYNTAX ERROR" : GOTO 350
    IF (C$="A" AND ITZ<11%) OR
    ((C$>"0" AND C$<="9") AND C$>CHR$(48%+ITZ-1%)) THEN
    PRINT TAB(IZ+11%);"" : PRINT "UNUSED INPUT" : GOTO 350
    IF C$="( " THEN BCZ=BCZ+1%
490
500
510

```

```

800 FOR IZ=1% TO LEN(EON$(NZ))
810 C$=MID$(EON$(NZ),IZ,1%)
820 IF C$=" " THEN 940
830 IF C$="/" THEN NVZ(BCZ)=1% : GOTO 940
840 IF C$="(" THEN BCZ=BCZ+1% : OP$(BCZ)=" " : GOTO 940
850 IF C$=")" THEN XZ=BAZ(BCZ) : BCZ=BCZ-1% : GOTO 900
860 IF C$>"0" AND C$<="9" THEN XZ=0%(ASCII(C$)-48%)
870 IF C$="A" THEN XZ=DX(10%)
880 IF C$="+" THEN OP$(BCZ)="+" : GOTO 940
890 IF C$="*" THEN OP$(BCZ)="*" : GOTO 940
900 IF NVZ(BCZ)=1% THEN NVZ(BCZ)=0% : XZ=NOT XZ
910 IF OP$(BCZ)="+" THEN BAZ(BCZ)=BAZ(BCZ) OR XZ
920 IF OP$(BCZ)="*" THEN BAZ(BCZ)=BAZ(BCZ) AND XZ
930 IF OP$(BCZ)=" " THEN BAZ(BCZ)=XZ
940 NEXT IZ
950 IF BAZ(0%)<0% THEN ARR$(AZ)=ARR$(AZ) OR 2%*NZ
960 IF AZ=0% THEN OVZ(NZ)=BAZ(0%) : ODZ(NZ)=0%
970 IF BAZ(0%)<>OVZ(NZ) THEN ODZ(NZ)=-1%
980 OVZ(NZ)=BAZ(0%)
990 NEXT NZ
1000 NEXT AZ
1010 REM ... PRINT SUMMARY OF EQUATIONS AND HEX DUMP OF DATA
1020 PRINT : PRINT "BOULLEAN EQUATIONS" :
1030 PRINT
1040 FOR NZ=0% TO OTZ-1%
1050 PRINT "OUTPUT";NZ;"=";E$(NZ);
1060 IF ODZ(NZ)=-1% THEN PRINT : GOTO 1110
1070 PRINT " *** ALWAYS " ;
1080 IF OVZ(NZ)=0% THEN PRINT "LOW " ; GOTO 1100
1090 PRINT "HIGH " ;
1100 PRINT " *** "
1110 NEXT NZ
1120 PRINT : PRINT "EPROM MEMORY DUMP (HEX) : "
1130 CZ=0 : AZ=0%
1140 FOR NZ=0% TO 2*ITZ-1%
1150 IF CZ<0% THEN 1190
1160 PRINT
1170 HZ = INT(AZ/256%) : GOSUB 1600 : PRINT H$;
1180 HZ = AZ-256%*INT(AZ/256%) : GOSUB 1600 : PRINT H$;
1190 CZ=CZ+1 : AZ=AZ+1
1200 IF CZ=16% THEN CZ=0%
1210 HZ=ARR$(NZ)
1220 GOSUB 1600
1230 PRINT H$; " " ;
1240 NEXT NZ
1250 PRINT
1260 IF ITZ=11% THEN 1340
1270 PRINT : PRINT "REMAINING LOCATIONS UNPROGRAMMED"
1280 PRINT : PRINT "INPUT(S) " ;
1290 FOR NZ=ITZ+1 TO 11%
1300 PRINT X$(NZ)-1% ;
1310 IF NZ<>11% THEN PRINT " " ;
1320 NEXT NZ
1330 PRINT " SHOULD BE TIED TO 0V"
1340 PRINT
1350 REM ... WRITE TO MEMORY IF REQUIRED
1360 INPUT "WRITE TO MEMORY BLOCK FOR EPROM PROGRAMMER USE ";0$
1370 IF LEFT$(0$,1)="N" THEN 1650

```

```

520 IF C$="" THEN BCZ=BCZ-1%
530 IF BCZ<0% THEN PRINT TAB(IX+11%); " " ;
      PRINT "BRACKETS MISMATCH" ; GOTO 350
540 L$=C$
550 NEXT IX
560 IF BCZ<0% THEN PRINT TAB(IX+11%); " " ;
      PRINT "BRACKETS MISMATCH" ; GOTO 350
570 IF L$="/" OR L$="+" OR L$="*" THEN PRINT TAB(IX+11%); " " ;
      PRINT "SYNTAX ERROR" ; GOTO 350

580 REM ... INSERT BRACKETS TO GIVE 'AND' PRIORITY OVER 'OR'
590 REM ... NOT USING 'FOR' LOOP SINCE LIMIT CHANGES IN LOOP
600 IB$(0%)="" ; BCZ=0
610 IX=1%
620 C$=MID$(EON$(NZ), IX, 1%)
630 F$=MID$(EON$(NZ), IX+1%, 1%)
640 IF C$="( " THEN BCZ=BCZ+1 ; IB$(BCZ)=""
650 IF F$="*" AND C$<>"(" AND IB$(BCZ)="" THEN IB$(BCZ)="(" ;
      GOSUB 1560
660 IF (C$="+" OR C$=")") AND IB$(BCZ)="" THEN IB$(BCZ)=")" ;
      GOSUB 1560
670 IF C$=")" THEN BCZ=BCZ-1
680 IX=IX+1% ; IF IX<=LEN(EON$(NZ)) THEN G20
690 IF IB$(0%)="" THEN EON$(NZ)=EON$(NZ)+")"
700 NEXT NZ
710 REM ... GENERATE DATA FOR EACH REQUIRED MEMORY LOCATION
720 FOR AZ=0% TO 2%:ITZ=1%
730 FOR IZ=0% TO 11%
740 DZ(IZ)=0%
750 IF (AZ AND 2%:IZ)<>0% THEN DZ(IZ)=-1%
760 NEXT IZ
770 ARR$(AZ)=0%
780 FOR NZ=0% TO 07%-1%
790 BCZ=0% ; OP$(0%)="" ; NV$(BCZ)=0%

```

```

1380 IF LEFT$(0$, 1)<>"Y" THEN 1360
1390 INPUT "ENTER START ADDRESS (HEX) " ; 0$
1400 IF LEN(0$)<>4 THEN 1390
1410 HZ=0%
1420 FOR NZ=0% TO 3%
1430 H$=MID$(0$, NZ+1%, 1)
1440 FOR IZ=0% TO 15%
1450 IF H$=X$(IZ) THEN 1480
1460 NEXT IZ
1470 GOTO 1390
1480 HZ=HZ+1%*16%*(3%-NZ)
1490 NEXT NZ
1500 IF HZ+2%:ITZ-1% > URZ THEN PRINT "INSUFFICIENT MEMORY HERE" ;
      GOTO 1390
1510 FOR AZ=HZ TO HZ+2%:ITZ-1%
1520 POKE AZ, ARR$(AZ-HZ)
1530 NEXT AZ
1540 PRINT : PRINT "DONE"
1550 GOTO 1650

1560 REM ... INSERT IB$( ) IN EON$(NZ)
1570 EON$(NZ)=LEFT$(EON$(NZ), IZ-1)+IB$(BCZ)+
      RIGHT$(EON$(NZ), IZ)
1580 IZ=IZ+1%
1590 RETURN

1600 REM ... DECIMAL TO HEX
1610 HHZ=INT(HZ/16%)
1620 HZ=HZ-16%*HHZ
1630 H$=X$(HHZ)+X$(HZ)
1640 RETURN

1650 END

```

**Listing 1** The design software in BASIC.

each equation in turn, and the appropriate bit set in the byte for this location if the result is 1.

Within this loop a record is kept of any output bits which are always high or always low. After executing this loop, lines 1100-1540 print out the results. These results consist of a summary of the equations followed by a hex dump of the EPROM contents. In the equation summary, if a particular output is always either high or low, a warning message is printed to indicate that a logical error has probably been made. Once the dump has been printed, the user is given the option of writing the data to a RAM memory block for subsequent access by an EPROM programmer package.

Turning to the user of the program, the variable UR% must first be modified to the highest RAM memory available on the machine in use. The line in question is 240. Equations may be entered in equations may be entered in virtually any format consistent with a few basic rules. Inputs 0-10 are represented by the characters 0-9 and A respectively, the + sign is used to signify OR and the \* sign to signify AND. The / sign is used to indicate that the following term is negated and brackets may be used. The AND operator takes precedence over OR and spaces may be added to improve readability. The following

examples illustrate this notation:-

```

0 * 1 = Input 0 AND Input 1
2 + 3 = Input 2 OR Input 3
/A = NOT Input 10
0*1+2*3=(0AND1)OR(2AND3)
0*(1+2)*3=0AND(1OR2)AND3
/(2+13)=NOT(2OR3)

```

INVALID CHARACTER	A character other than 0-9, A, +, *, /, (, ) or space has been entered.
UNUSED INPUT	An unused input has been specified. For example the use of 5-A when 5 inputs (0-4) were specified.
SYNTAX ERROR	An invalid combination of characters was entered. For example two consecutive logic operators (*+).
MISMATCHED BRACKETS	The number of opening brackets is not equal to the number of closing brackets.

If a syntax error is detected, the line in error is printed out with an arrow pointing to the location of the offending character. The nature of the error is also printed in plain English. The following error messages are possible:

## PARTS LIST

**RESISTORS** (all 1/4W, 5%)  
 R1-11 10k  
 R12-19 100k  
 R20-27 180R

**SEMICONDUCTORS**  
 IC1 2716 EPROM  
 LED 1-8 Standard Red LEDs  
 Q1-16 BC184L

**MISCELLANEOUS**  
 SW1 12-Way DIL Switch  
 PCB; 24-Way DIL socket for IC1.

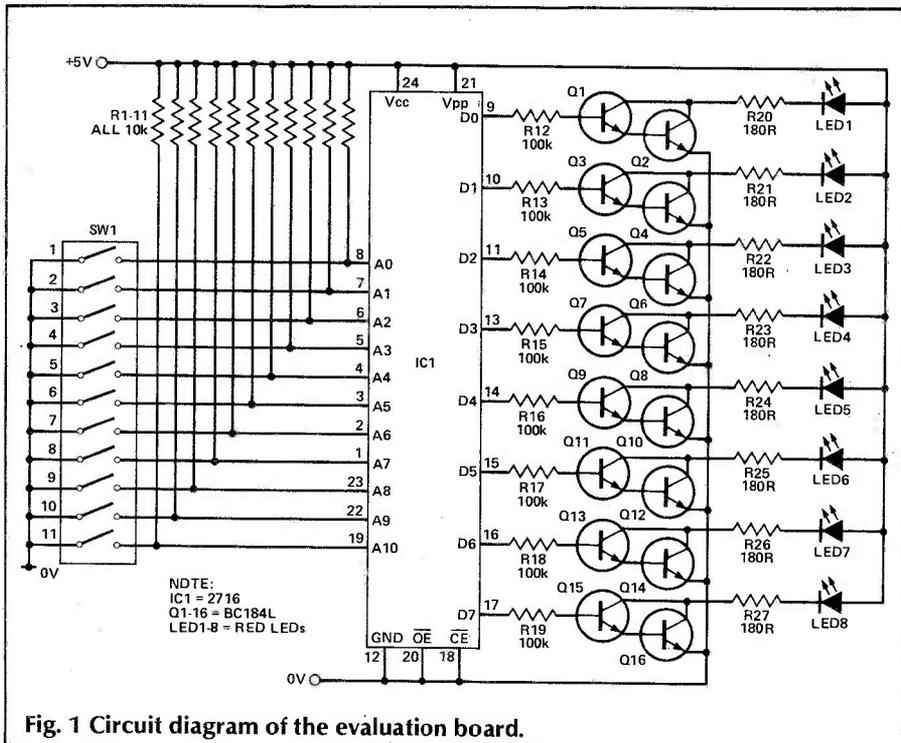


Fig. 1 Circuit diagram of the evaluation board.

Apart from these comments, the only other point which needs to be mentioned is that warning messages may be printed with the equation summary and hex dump. The following examples illustrate this:

OUTPUT 0 = 1 + /1  
 \*\*\* ALWAYS HIGH \*\*\*

OUTPUT 1 = 0 \* /0  
 \*\*\* ALWAYS LOW \*\*\*

In these cases it is quite obvious that 1 OR NOT 1 will always give a high result and that 0

AND NOT 0 will always give a low result. Cases can be much more obscure, however, and the messages indicate that a logic error has probably been made. If a constant high or constant low signal is really required it isn't necessary to use an EPROM output to generate one!


### The Evaluation Board

To fulfil the requirements of an experimentation/evaluation board, the inputs should be easily programmable between logic

levels and the state of the outputs should be displayed clearly. These requirements are provided by a row of DIL switches, one for each of the inputs (address lines) of the 2716 and a row of LEDs, one for each of the EPROM outputs (data lines). The 2716 EPROM was chosen purely because it is the least expensive yet still has 11 available inputs. The principles are clearly the same if a larger EPROM is used to give more inputs.

The circuit diagram is shown as Fig. 1. The board requires a low current 5V power supply or could be operated from a battery. The operation of the board is very simple and doesn't really justify a separate how it works section. The 11 address lines, which act as inputs, are held high by pull-up resistors R1-R11, logic lows being achieved, when required, by switching to 0V through the DIL switches SW1-SW11. The 8 data lines act as outputs and drive Darlington pairs Q1/Q2, Q3/Q4 etc and the LEDs are connected to these via current limiting resistors

Fig. 2 Component overlay for the evaluation board.

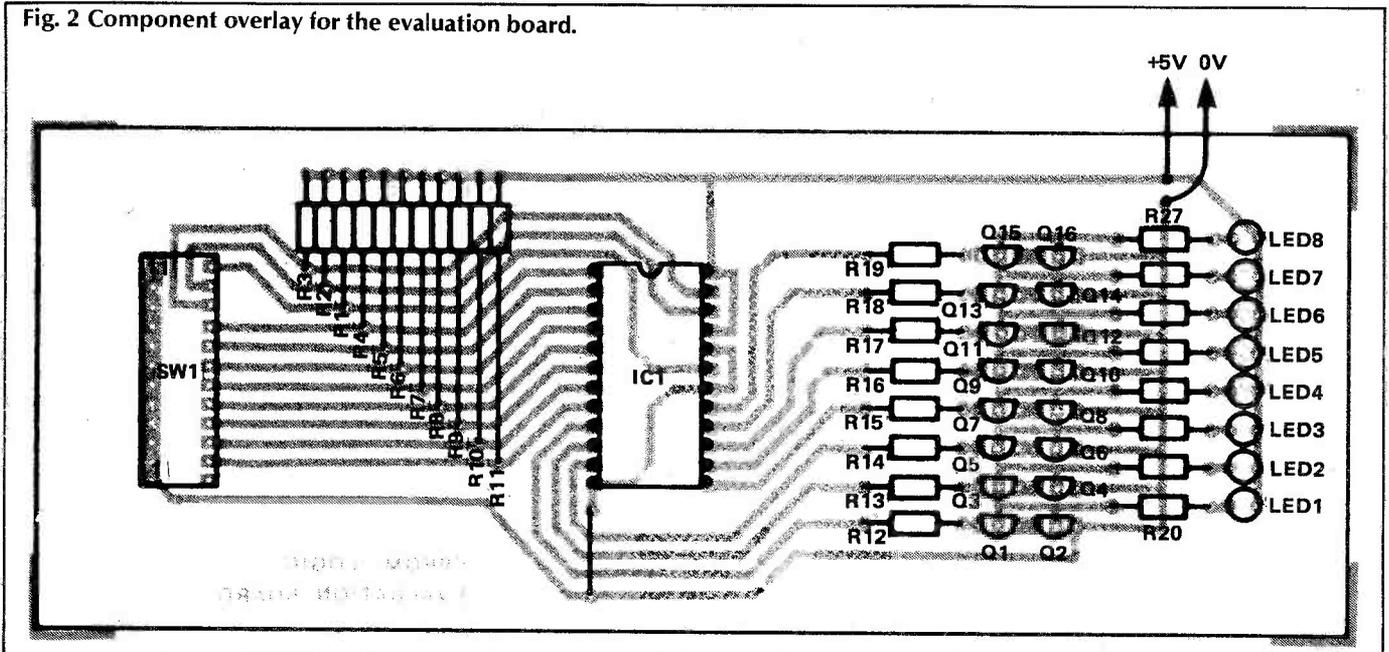

R20-27.  $\overline{CE}$  and  $\overline{OE}$  are held constantly low, ensuring that the outputs are always active and that any changes to the inputs will be reflected on the outputs immediately.

Construction of the board is quite straightforward and requires little comment. A socket must obviously be used for the EPROM, IC1, and care must be taken when installing the LEDs and transistors to ensure that they are the right way around. Some form of labelling will be required to identify the switch positions and LED numbering. On the prototype this was achieved simply by sticking down pieces of paper on which the required legends had been typed, but if you are after a really professional result you may prefer to use Indian ink or Letraset on the board and then apply a coat of clear lacquer for protection.

## Using The Program And Board

For the purposes of this example, let us assume that it is required to implement 8 different functions of 6 inputs. This means that 8 outputs and inputs are needed and this is the answer to the first question asked by the design program. The functions required are shown in Fig. 3 as a verbal description, a circuit diagram of the discrete logic implementation and the Boolean equations. These functions are entered into the software in the form of the final equations given in each part of Figure 3, and the program output is shown as Listing 2. It will be noticed that 64 values are listed (2 to the power of 6) and that inputs 6 — A should be tied low by closing the switches SW7-11. If a 2716 is programmed with this data, spending a few minutes with the evaluation board will confirm that the functions are correctly implemented.

## Other Function Types

Although all logic transfer functions can be expressed in terms of a set of Boolean equations, this is not always the most obvious way to describe a particular function. Cases where there is an easier way to describe the function include code conversions, for example binary to decimal, binary to BCD, BCD to 7 segment, etc. In these instances, it is perhaps not immediately obvious what the discrete logic

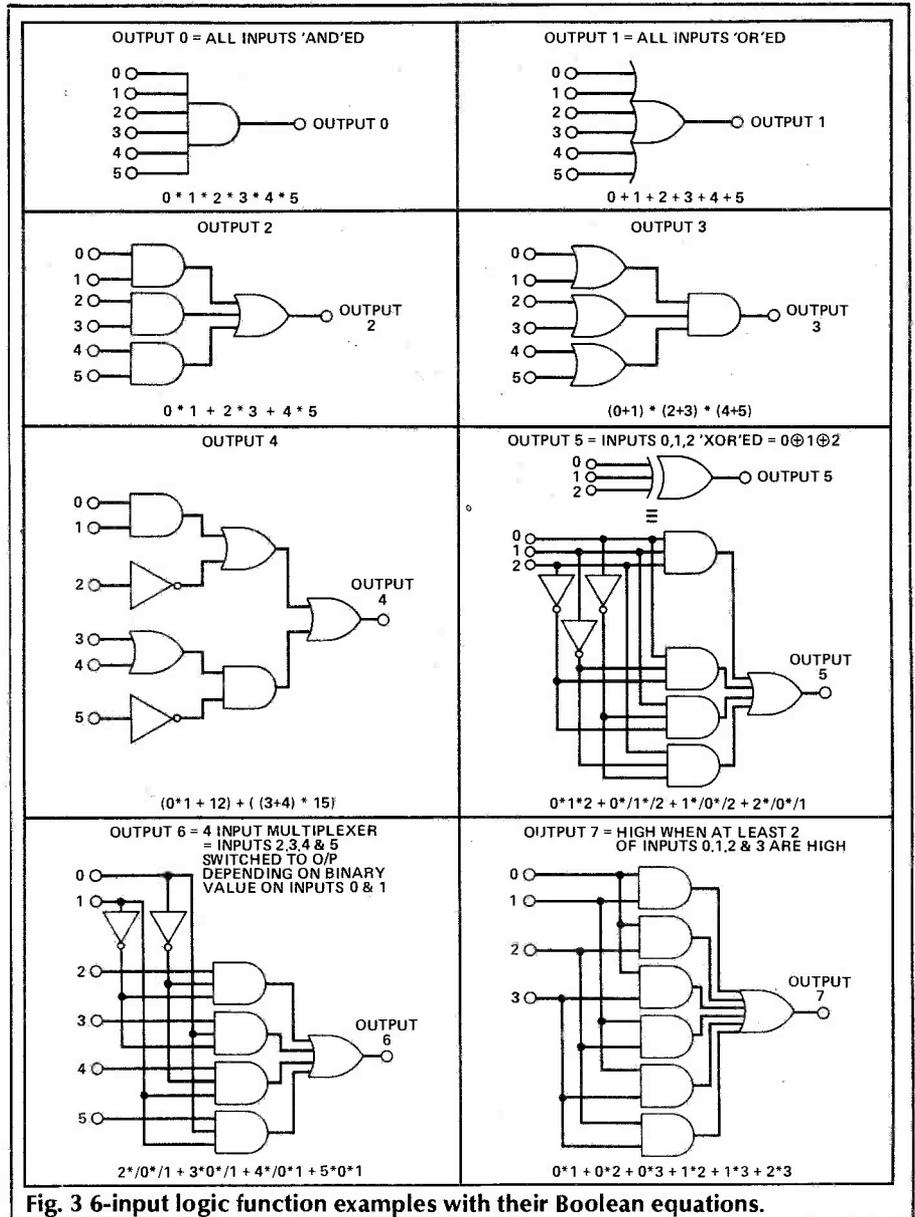


Fig. 3 6-input logic function examples with their Boolean equations.

### BOOLEAN EQUATIONS :

```

OUTPUT 0 = 0*1*2*3*4*5
OUTPUT 1 = 0+1+2+3+4+5
OUTPUT 2 = 0*1 + 2*3 + 4*5
OUTPUT 3 = (0+1) * (2+3) * (4+5)
OUTPUT 4 = (0*1+2) + ((3+4)*5)
OUTPUT 5 = 0*1*2 + 0*/1*/2 + 1*/0*/2 + 2*/0*/1
OUTPUT 6 = 2*/0*/1 + 3*0*/1 + 4*/0*1 + 5*0*1
OUTPUT 7 = 0*1 + 0*2 + 0*3 + 1*2 + 1*3 + 2*3
    
```

### EPROM MEMORY DUMP (HEX) :



```

0000  10 32 32 96 62 82 82 B6 12 F2 B2 96 F6 D6 96 B6
0010  12 32 72 96 72 9A DA BE 12 FA FA 9E F6 DE DE BE
0020  12 32 32 D6 62 8A 8A FE 12 FA BA DE E6 CE BE FE
0030  16 36 76 D6 66 8E CE FE 16 FE FE DE E6 CE CE FF
    
```

REMAINING LOCATIONS UNPROGRAMMED

INPUT(S) 6, 7, 8, 9, A SHOULD BE TIED TO 0V

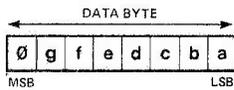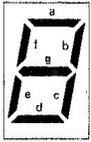Listing 2 The hex dump which results when the Boolean equations of Fig. 3 are entered into the BASIC program.



Display	Binary	Hex	Decimal
0	00111111	3F	63
1	00000110	06	6
2	01011011	58	91
3	01001111	4F	79
4	01100110	66	102
5	01101101	6D	109
6	01111101	7D	125
7	00000111	07	7
8	01111111	7F	127
9	01100111	67	103
A	01110111	77	119
B	01111100	3C	60
C	00111001	39	57
D	01011110	5E	94
E	01111001	79	121
F	01110001	71	113

Fig. 4 Working out a single-digit, seven-segment LED decoder program by hand.

implementation and hence Boolean equations would be. In cases like this it will often be found more convenient to write a dedicated BASIC program to calculate the EPROM contents.

The conversion of 6 bit binary to 2 digit BCD provides an ideal example of such a solution. This example could be worked out by hand without too much difficulty, but in the general case the software solution will be more effective in terms of effort expended. Listing 3 shows the main loop of a program to calculate EPROM contents for this function. Following this main loop, the hex dump and copying to RAM portions of the main program in Listing 1 could be added. The hex dump produced by such a program is shown as listing 4. Even without blowing an EPROM and plugging it into the evaluation board, it is quite clear just by studying this dump that the function is truly implemented. (Please note that, in spite of their appearance, the values in the dump are hexadecimal not decimal!)

A rather more interesting example of code conversion is that of binary to decimal or hexadecimal 7-segment code. The driving of a single digit 7-segment display is quite trivial, requiring only ten values for the decimal case or 16 for hexadecimal. The calculation of the EPROM contents required can be done by hand as shown in Fig. 4.

For a two digit display the requirements are considerably more involved. The initial problem is that two digits require 14 outputs to drive them, compared

```

300 REM *** THIS LOOP CALCULATES EPROM CONTENTS
310 REM *** FOR 6 BIT BINARY TO BCD CONVERSION

320 FOR A%=0% TO 63%
330 TENS%=INT(A%/10%)
340 UNITS%=A%-10%*TENS%
350 ARR%(A%)=TENS%*16%+UNITS%
360 NEXT A%

370 IT%=6 : REM *** THIS VALUE REQUIRED FOR HEX DUMP ETC

```

Listing 3 The main loop of a program which calculates the EPROM contents for a 6-digit binary to 2-digit BCD conversion.

EPROM MEMORY DUMP (HEX) :

0000	00	01	02	03	04	05	06	07	08	09	10	11	12	13	14	15
0010	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31
0020	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47
0030	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63

REMAINING LOCATIONS UNPROGRAMMED

INPUT(S) 6, 7, 8, 9, A SHOULD BE TIED TO 0V

Listing 4 The hex dump produced by the program given in Listing 3.

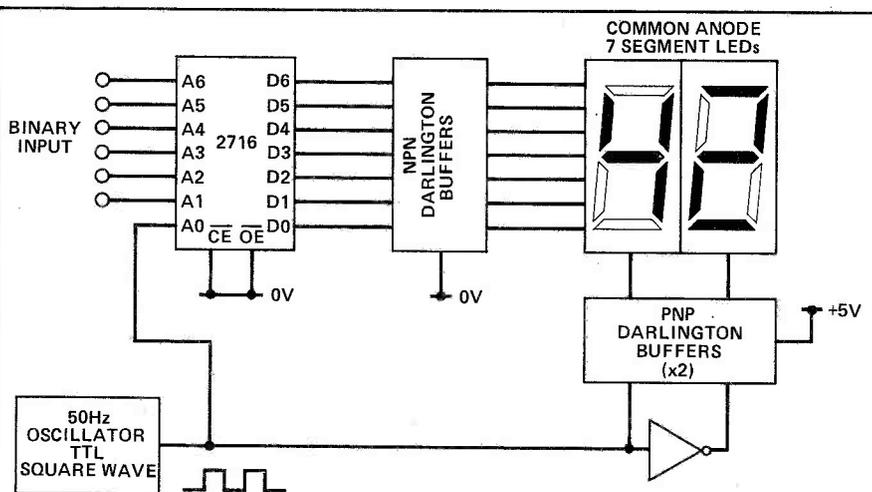


Fig. 5 Simplified circuit diagram of a 2-digit, seven-segment LED encoder using an EPROM.

```

300 REM *** PROGRAM PORTION TO CALCULATE EPROM CONTENTS FOR
310 REM *** 6 BIT BINARY TO TWO DIGIT DECIMAL 7-SEGMENT CODE

320 REM *** LOAD 1 DIGIT 7-SEGMENT DATA (OK FOR HEX TOO)
330 DIM SEG%(15)
340 DATA 63,6,91,79,102,109,125,7,127,103,119,60,57,94,121,113
350 FOR NX=0% TO 15%
360 READ SEG%(NX)
370 NEXT NX

380 REM *** MAIN LOOP
390 FOR A%=0% TO 126% STEP 2%
400 D%=INT(A%/2%)
410 TENS%=INT(D%/10%)
420 UNITS%=D%-10%*TENS%
430 ARR%(A%)=SEG%(UNITS%)
440 ARR%(A%+1%)=SEG%(TENS%)
450 NEXT A%

460 IT%=7% : REM *** REQUIRED FOR HEX DUMP ETC

```

Listing 5 The main portion of a program which calculates the EPROM contents for a binary to 2-digit, seven-segment display conversion.

with the 8 outputs available on the 2716 EPROM. The answer is to utilise the common LED driving technique of multiplexing the two digits. A simplified circuit diagram for such an arrangement is shown in Fig. 5. The common anode LED displays are both driven from the NPN Darlington which in turn are driven from the EPROM output data. The clock signal will drive the anodes of each LED in turn by means of Darlington drivers (in this case PNP) and an inverter. The clock frequency is high enough to ensure both LEDs appear to be constantly illuminated even though only one is actually on at a time. Since the clock signal is also used as an input to the EPROM, the resident program can be made to output the data for one of the two digits for a particular value of the other address bits, depending on the state of the clock input. This causes the correct data to be supplied to the currently illuminated digit.

The program to generate the required data is shown as listing 5. Once again the hex dump routines and so on will require appending to the end of this code. The

## EPROM MEMORY DUMP (HEX) :

```
0000 3F 3F 06 3F 5B 3F 4F 3F 66 3F 6D 3F 7D 3F 07 3F
0010 7F 3F 67 3F 3F 06 06 06 5B 06 4F 06 66 06 6D 06
0020 7D 06 07 06 7F 06 67 06 3F 5B 06 5B 5B 5B 4F 5B
0030 66 5B 6D 5B 7D 5B 07 5B 7F 5B 67 5B 3F 4F 06 4F
0040 5B 4F 4F 4F 66 4F 6D 4F 7D 4F 07 4F 7F 4F 67 4F
0050 3F 66 06 66 5B 66 4F 66 66 66 6D 66 7D 66 07 66
0060 7F 66 67 66 3F 6D 06 6D 5B 6D 4F 6D 66 6D 6D 6D
0070 7D 6D 07 6D 7F 6D 67 6D 3F 7D 06 7D 5B 7D 4F 7D
```

REMAINING LOCATIONS UNPROGRAMMED

INPUT(S) 7, 8, 9, A SHOULD BE TIED TO 0V

Listing 6 The hex dump produced by the program given in Listing 5.

program will obviously generate the two digits for each binary value in pairs of consecutive locations, with the units in the least significant byte of the pair. Listing 6 shows the output produced by this program.

## Conclusions


It is quite obvious that by the use of programmable logic in the form of an EPROM, it is possible to implement a wide range of logic functions varying from the very

simple to the quite sophisticated. The board and software presented here provide a means of verifying this and makes an interesting and educational experimental project. It is hoped that the board will also be used to aid the design of practical projects making use of programmable logic. By using the evaluation board it is possible to experiment with the programmable portion of such a project before incorporating it into the main design.

ETI

## caddis Systems


Presents Quality Boxes

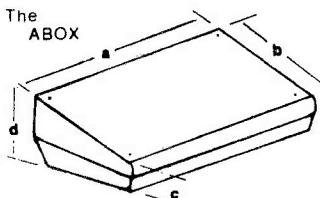

TYPE	a	b	c	d
RA.2	262	185	33	7
TYPE A <th>a</th> <th>b</th> <th>c</th> <th>d</th>	a	b	c	d
RA.2	262	185	33	78
RA.3	260	185	33	117
RA.4	400	230	35	85

\* not as shown see below

AND the ELBOX

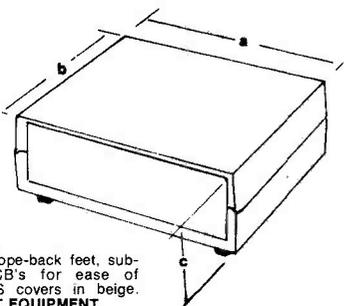

TYPE	a	b	c
RE.2	171	145	56
RE.3	231	181	77

Anodised front panel, slope-back feet, sub-frame to support PCB's for ease of construction, tough ABS covers in beige. IDEAL FOR BENCH TEST EQUIPMENT.

ABOX. An attractive two tone beige/brown ABS moulded box in two parts with sloping anodised front panel. The RA.3 is as RA.2 but has a dual slope front panel, giving two panels areas 100x248 (lower) and 50x248.

MANY MORE TYPES AVAILABLE send large size for brochure.

PRICES RA.2 £10.28 RA.3 £11.25 RA.4 £19.75  
RE.2 £8.00 RE.3 £12.00

All prices include VAT & postage and packing. Please allow 7-21 days delivery.

Trade enquiries welcome, good quantity discounts offered. Also full engineering service offered panel punching, engraving, painting etc.

Caddis Systems Ltd. 5 Keats Close,  
Maldon, Essex. CM9 6DB. 0621 55116

## OSCILLOSCOPES

TELEQUIPMENT D67. Dual Trace 50MHz. Delay Sweep with manual. £260  
COBSOR CDU 150. Dual Trace 35MHz Solid State. Portable. 8x10cm display. With manual. £200  
S.E. LABS 34W. Dual Trace 18MHz Solid State. Portable AC or External DC Operation. 8 x 10cm display. With manual. £150  
TEKTRONIX 547 Dual Trace 50MHz. Dual TB. Delay Sweep. With Manual. £140  
TELEQUIPMENT D43. Dual Trace 15MHz. With manual. £100  
EX-MINISTRY CT436. Dual Beam 6MHz. Size 10 x 10 x 16ins. With manual. £60

## PHILIPS DIGITAL MULTIMETERS

4 DIGIT. AUTO RANGING. Complete with batteries and leads (P&P £5)  
TYPE PM2517X (L.C.D.) £75

## MULTIMETERS

AVO 8 Mk3. Complete with batteries & Leads. £80  
AVO 8 Mk4. Complete with Batteries & Leads. £65  
AVO Model 7X Complete with batteries, leads & carrying case. £40  
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads. £18  
AVO 72 - Similar to above but no AC Current range. With Batteries & Leads £10

## STEPPING MOTORS

200 Steps per rev. 4 Phase (5wire) 12.24V Torque 25 oz inch (will run on 5V with reduced torque). Size 57mm dia x 57mm. 6mm shaft £15 ea. £12 Steps per rev. 3 Phase. 12-24V (will work on 5V). Size 44mm dia x 41mm shaft. £2 ea. 5 off £7.50.  
NORTH AMERICAN PHILIPS. 24 Steps per rev. 4 wire 5V 3.3Amps. 0.250rpm 0.200 P&P. Size 70mm dia x 41mm. £8 ea.  
200 Steps per rev. 120V (3 wire). Torque 25 oz inch. Size 60 x 57mm. 6mm shaft. £4 ea.

## PLEASE NOTE

From January 1st 1986 we will be closed Saturdays. Opening times:- Monday to Friday 9am - 5.30pm with late night Thursdays until 8pm.

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage. Please allow 21 days for delivery.

**STEWART OF READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: 0734 68041



Callers welcome 9am to 5.30pm Monday to Saturday inclusive

## NEW EQUIPMENT

HAMEG OSCILLOSCOPES 605. Dual Trace 60MHz Delay Sweep. Component Tester £515  
HAMEG OSCILLOSCOPE 203.5 Dual Trace 20MHz Component Tester £270  
All Other Models Available.

## BLACK STAR COUNTER TIMERS

Meteor 100-100MHz. Ratio/Period/Time Interval etc. £126  
APOLLO 10 - 100MHz. (As above - with more functions) £285  
BLACK STAR FREQUENCY COUNTERS. P&P £4

Meteor 100-100MHz £99  
Meteor 600-600MHz £126  
Meteor 1000-1GHz £175  
BLACK STAR JUPITER 500 FUNCTION GENERATOR Sine/Square/Triangle 0.1Hz - 500KHz P&P £4  
HUNG CHANG DMM 6010. 3½ digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. p&p £4 £33.50

OSCILLOSCOPES PROBES. Switched x1; x10 P&P £11

PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for REUTERS. Gives quality 80 x 24 line display! Composite Video In. Cased. Good Condition £110 each

5¼" FLOPPY DISK DRIVES  
TANDON ½ Height. Brand New Single Sided Double Density £45  
Double Sided Double Density £100  
MPI Double sided, Double Density 80 Track unused £100

DISK DRIVE PSU. 240V 1N; 5V 1.6A & 12V 1.5A out. Size: W125mm, H75mm, D180mm. Cased. Un-used. Only £10.00 p&p £2

QWERTY KEYBOARD (as in LYNX micro). Push to make. Cased. Only £5 each p&p £2

AVO TRANSISTOR TESTER TT169 Handheld. GO/NOGO for In-situ Testing. Complete with Batteries, leads & Instructions (P&P £3). NOW ONLY £12

# DIGITAL SOUND SAMPLER

Nothing could be simpler than building the analogue board. Paul Chappell shows the way.

The component layout for the analogue board is shown in Fig. 1. Construction should not present any difficulties. The main point to watch is that all the through-hole connections are made. It's easy to leave one out! Some through links are made via component leads, so be sure to solder these at the top whenever there is a pad for them.

Enclosed cermet trimmers are recommended for RV1 to RV6, although I have provided extra holes in the board to allow open cermet or carbon presets to be used (as a last resort). Good quality polystyrene capacitors should be used for the filters — the tighter the tolerance the better

— and you may wish to use 1% resistors around the MF10s. The connectors for the power supply, bus and control lines can be of any type — if you have any problem finding a 12-way connector for the control signals, use an 8-way and a 4-way connector side by side. If you decide to socket the expensive ICs — the AM6072s, CMP01 etc. — the extra few pennies for good quality gold plated sockets will be well repaid. Some ICs cannot be socketed because through connections are made on their leads.

To test the analogue board without the control board, the circuit must be made to drive itself. The on-board oscillator can

be used to drive the mobile filters and the ADCs can be made to sample continuously with a few temporary connections to the control lines. To test the signal path, proceed as follows.

- 1) Join FCLK(1) to FCLK(2) on the control line connector.
- 2) Wire IC7 pin r to FCLK(1),(2).
- 3) Connect OE to +5V.
- 4) Connect STM to 0V.
- 5) Connect SCS, SCC, SFM(1) and SFM(2) together.
- 6) Connect the keyboard trigger input to +5V.
- 7) Connect a signal source (microphone, signal generator, tape recorder output from hi-fi, etc.) to the signal input and an

## PARTS LIST

### RESISTORS (all 1/4 W 5% unless stated)

R1, 18, 22, 54, 69, 74	1k0
R2, 3	680R
R4, 5, 29, 30, 31, 46, 47, 48	12k
R6, 7, 19, 20, 32, 33, 49, 51, 52, 70, 73	10k
R8, 9, 11, 12, 13, 15, 34, 35, 37, 38, 39, 41	15k
R10	39k
R14	13k 1% metal film
R16, 17, 23, 56, 60, 71	100k
R21, 44, 45, 66	470R
R24, 25, 27, 28, 42, 43	2k4 1% metal film
R26, 55	3k9
R36	9k1 1% metal film
R40	7k5 1% metal film
R50, 59, 62, 67, 68	4k7

R53, 72	22k
R61	56k
R63	390R
R64	82k
R65	3k3
RV1	200k
RV2	500k
RV3	2k
RV4, 6	10k
RV5	20k
(all horiz. cermet trimmers)	

### CAPACITORS

C1	100µ 25V tantalum
C2, 4	47µ 25V tantalum
C3, 5, 12, 13, 15, 20, 23, 29 32-42	100n ceramic
C6, 7, 11, 14, 21, 22, 27, 31, 43-46	10µ 25V tantalum
C8, 9, 16, 17, 18, 24, 25, 26	1n0 polystyrene
C10	100p ceramic
C29	150p polystyrene
C30	4µ7 25V tantalum

### SEMICONDUCTORS

IC1	NE5534
IC2, 12, 15, 16, 17	LM318
IC3, 20, 21	741
IC4	LM311
IC45, 13	MF10
IC6	CMP01
IC7	74LS86
IC8	74LS74
IC9	Am2502
IC10, 14	Am6072
IC11	74LS541
IC18, 19	74LS374
IC22	ZN448
Q1	BF244A
Q2	BC212
D1-4, 7-9	IN914
D5, 6	9491
LED 1	Red panel mounting LED
LED 2	Green panel mounting LED

### MISCELLANEOUS

IC sockets (3x18-way, 1x8-way); Molex connectors (0.1" pitch 12-way plug and socket, 0.1" pitch 8-way plug and socket, 0.2" pitch 5-way plug and socket); PCB.

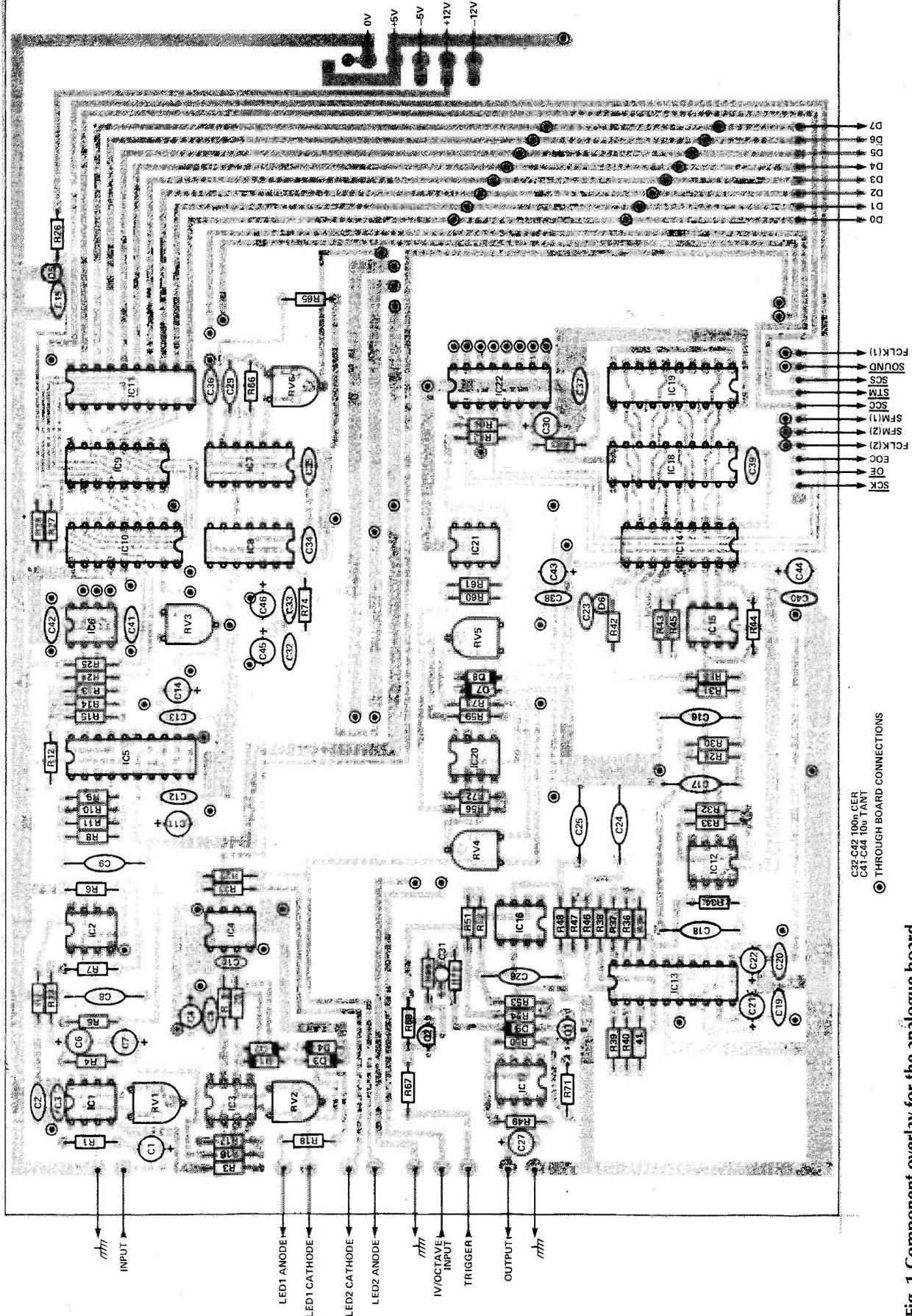


Fig. 1 Component overlay for the analogue board.

amplifier to the signal output of the board.

8) Set all presets to mid position.

If the board is now powered up, the A to D section of the circuit should sample continuously and the D to A section should take each generated code and translate it back into analogue form. A signal applied to the input should therefore follow the entire audio path and emerge at the output.

## Fault Finding

If there is no signal from the output, or if the sound is distorted, the following test procedure should identify the troublesome area.

First, check pin 6 of IC1 with a 'scope. The input signal should emerge from this pin considerably amplified and RV1 should control the gain. Next check pin 6 of IC2 to make sure the signal is present there too. Now proceed to pin 20 of IC5. If there is no signal, inspect pins 10 and 11 to make sure the clock signal — a square wave of about 1MHz — is present. No clock means that the circuit around IC7 c/d is not oscillating (or possibly a faulty connection, of course. You did remember steps 1 and 2, didn't you?).

To check the A to D conversion, the best way is to synchronise your 'scope to SCC — either by connecting the external sync. to this signal, or even better by viewing it on one channel of a dual beam 'scope.

The SCC signal should spend about 90% of its time at logic 1 and drop to logic 0 briefly about once every 10 $\mu$ s (assuming the clock is running at the nominal 1MHz rate. You can adjust the clock frequency with RV6). Check each data bit in turn (on the connector at the edge of the board) with the other 'scope channel. Each data bit should go to 1 at some time during every period when SCC is at logic 1, regardless of whether or not there is an input signal to the circuit (you are watching the trial setting of each bit by the successive approximation register). With an audio signal at the input to the circuit, you will see two traces on most of the data lines: one where the line drops back to zero again after about 1 $\mu$ s and one where it remains at logic 1 until SCC goes

low and high again. You will see both traces at once because both situations will occur during each cycle of the input wave.

If everything is functioning correctly up to this point, the A to D conversion is taking place. Now we've got to get the audio signal back again. Check pin 11 of IC18 and the same pin on IC19. They should both follow SCC, since you effectively connect them all together in step 5. Keeping the 'scope synchronised to SCC, check the data on pins 2 to 9 of IC14. The voltage on all these pins should remain constant while SCC is high, but may change on each low to high transition. Pin 9, the lowest order data bit, should certainly change, even with a very small audio input to the circuit. As the signal level increases, the higher order data lines will also change. On the data lines that do change, you will see both traces at once on the 'scope (one remaining at logic 0, one at logic 1) for the same reason as before.

From here the signal can be traced — back in analogue form — at pin 6 of IC15, pin 6 of IC12, pin 20 of IC13 (check the clock on pins 10 and 11 again if there is no signal from here), pin 6 of IC16 and finally at pin 6 of IC17. If the signal gets lost between IC16 and IC17, check the keyboard trigger circuit (Q1, Q2). If the keyboard trigger input is grounded, the audio output from the circuit should cease; taking it to +15V will allow the sound to emerge. There should be no 'click' when the trigger voltage is changed.

The circuit around IC3 and IC4 must generate a logic signal to inform the control circuit that a suitable audio signal to be sampled is present at the input. Connect your 'scope to SOUND on the control line connector. With a very small audio input to the circuit, the signal should remain at logic 1; as the input level increases, SOUND should begin

to oscillate between logic 1 and logic 0. The exact level at which this happens can be controlled by RV2. With the LEDs connected at the edge of the board, the green one (LED2) should begin to light, as soon as the input level is great enough to trip SOUND; the red LED (LED1) will light when the signal reaches a higher level still, giving a rough indication of the input signal level.

## Testing The Keyboard Interface

First of all, remove all the connections made in steps 1 to 8 for testing the audio circuit, then make the following links.

- 1) Connect 0E to 0V
- 2) Connect STM to +5V
- 3) Connect EOC to SCK via the transistor circuit shown in Fig. 2.
- 4) Connect a variable voltage source of 0 to +5V to the 1V/octave input. (A battery and a 1k $\Omega$  pot will do).

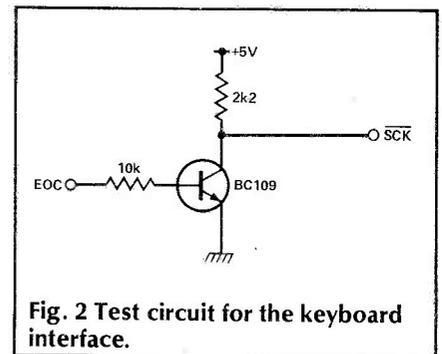


Fig. 2 Test circuit for the keyboard interface.

With the input at 0V, adjust RV4 until the voltage at the junction of D7 and D8 is also at 0V. Check that pin 6 of IC21 is at 0V too. Keeping the meter on IC21 pin 6, increase the input voltage. The voltage shown by the meter should also rise, and should be about half the input voltage. (You can make it exactly half by adjusting RV5, but don't bother too much at this stage.)

Finally, check the data lines. During the time that EOC is high the contents of the data lines will represent the voltage present at the input. If you have a steady hand on the input voltage control, you will see the data lines stepping through the normal binary sequence as the input rises from 0V. As the codes of interest occur when EOC is high — about 10% of the time — you will need a 'scope to see it.


This concludes the testing. Setting up the various presets for best results will be described in a later article.

## BUYLINES

The ICs and various other parts for the sampler are available from Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent. Please write for details. Metal film resistors can be obtained from Maplin Electronic Supplies Ltd., PO Box 3, Rayleigh, Essex, SS6 8LR (tel: 0702 554155). The PCBs will be available from our PCB Service.
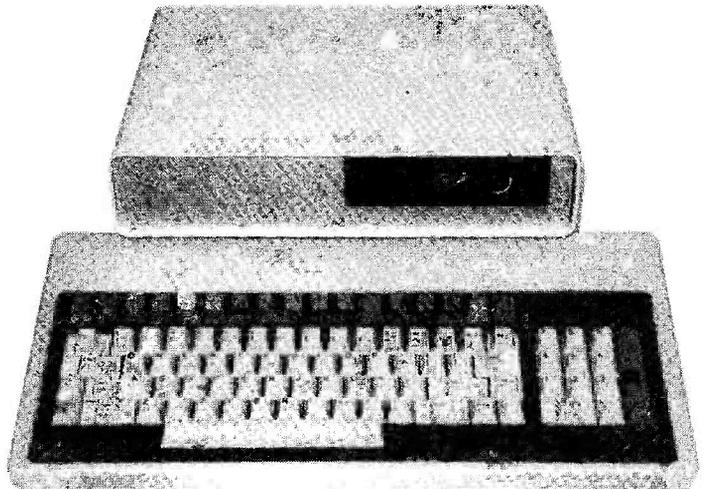
# 6809-BASED MICROCOMPUTER

Gary Mills discusses the choice of I/O devices and case to complete the system before going on to describe the testing and initial power-up procedures.



With assembly of the boards complete, the next step is to select and interface the appropriate input/output devices, attach a power supply, and install the complete system in a case or cases. Diagnostic test routines can then be run using the ROM monitor program.

The board can be used either with a separate keyboard and video monitor or with a serial terminal which includes both keyboard and VDU. Unless you already have such a terminal, you will probably wish to use separate devices. There is a wide range of suitable equipment to choose from.

The video monitor chosen may have either a composite video or a TTL interface. Using the composite video interface, any monitor that sinks 1 volt into 75 ohms will do. Since this is an almost universal standard, most composite video monitors can be used. Because the video resolution of the board is very high, the higher the resolution of the monitor, the better your display will look. 20MHz or over is a good figure to go for. Also, the picture will improve significantly if the video phosphor is a long persistence type, for example P39 or amber. Monitors that satisfy the requirements above include the Phillips Computer Monitor 80, No. BM7502/05 G (green) or A (amber), and the Kaga/Taxan KX1201, KX1202, and KX1203.

Pin No.	Signal
1.	Gnd
2.	TTLVID
3.	HSYNC
4.	VSYNC

**Table 1 Pin connections on the TTL-Video output socket, SK8. Pin 1 is the pin nearest the composite video output socket, SK9.**

Pin No.	Signal
1.	Gnd
2.	XMIT
3.	RCVE
4.	RTS
5.	CTS
7.	Gnd
11.	+5v
25.	-12v

**Table 2 Pin connections on the RS232 serial ports, SK3 and SK4.**

Pin No.	Inner row	Outer row
1, 2	DO	+5v
3, 4	D1	Gnd
5, 6	D2	Gnd
7, 8	D3	Gnd
9, 10	D4	Gnd
11, 12	D5	Gnd
13, 14	D6	Gnd
15, 16	nc	Gnd
17, 18	STROBE	Gnd
19, 20	RST	-12v

**Table 3 Pin connections on the parallel keyboard port, SK2.**

TTL video monitors can also be interfaced to the board. One of the commonest types is the IBM compatible monitor. There is a

slight problem here in that the signals required (HSYNC, VSYNC and TTLVIDEO) are active high while the signals coming from the board are active low. To get around this problem, inverting buffers can be connected to the TTL video output lines. This is not available as a modification from Micro Concepts, but those who require it should not have too much difficulty sorting it out for themselves.

## Keyboards

As with monitors, the 6809 board can be interfaced to a wide range of keyboards, including both parallel and TTL-serial types.

The WD2123 chip was expressly chosen because it can support serial TTL keyboards, and for greatest flexibility the RS-232 drivers were also provided. To interface a serial TTL device such as a keyboard, it is necessary to circumvent the drivers. Remove the 75189 receiver chip and replace it with a header, jumpered so that each input line connects directly to an output. When the port is required as an RS232 interface, swop back to the driver. Two serial TTL keyboards which would be suitable are the IBM Work-Alike from Diamond H Controls, Vulcan Road North, Norwich NR6 6AH, tel 0603-45291, and the GAT-0414

Pin No.	Signal
1	PA4
2	PA3
3	PA5
4	PA2
5	PA6
6	PA1
7	PA7
8	PA0
9	Gnd
10	PC7
11	PC6
12	PC5
13	PC4
14	PC0
15	+5v
16	PC1
17	PB7
18	PC2
19	PB6
20	PC3
21	PB5
22	PB0
23	PB4
24	PB1
25	PB3
26	PB2

**Table 4 Pin connections on the EPROM disc board connector, SK6.**

from Verospeed. Any serial keyboard used should be set to 9600 baud, eight data bits and no parity on start-up.

The second keyboard option is the parallel interface. Quite a few low cost parallel interface keyboards can be found, but caution must be exercised. Make sure that the keyboard is ASCII encoded, and that it has a full set of upper and lower case letters, numbers and punctuation marks. The keyboard must provide a negative going strobe of at least one millisecond width to the board with each character.

If you are going to use a serial terminal instead of a separate keyboard and monitor, it should be set to 9600 baud, 8 data bits and no parity. The board requires RTS/CTS handshaking. If this is not available from the terminal, link the two pins together.

### Power Supplies

The next piece of equipment is the power supply. There are two important considerations here, the dimensions of the power supply which must be determined in relation to the cabinet you are going to use, and the output current and number of voltage rails required. This in turn depends on whether you will also be powering your drive(s) with the same supply, whether you use the serial driver chips, and what the power requirements of your keyboard are.

The general requirements for the power supply are +5 volts at 2.5 amps, +12 volts at 2 amps, and -12 volts at 0.1 amps. This assumes that you will be powering two drives, and that you have a separate keyboard drawing a small amount of power. One supply which is suitable is the Model PRD 303 from Power Rail Electronics Ltd, tel 0582-600277. This unit is recommended for use with the Vero Total Access case used on the prototype because it fits easily within the limit the cabinet places on height.

### The Case

This board does not necessarily require a case. Indeed, as we mentioned in the last issue, a prototype can be found mounted to the wall of the designer's workroom. However, a case does protect things, and it can also help to collect and organize the cables, power supply and drives.

The case pictured is from Vero and is a Total Access case type 212-8154H. To use it you will also need a chassis plate type 212-27826K. Use of this case requires that you mount the disk controller cable socket and the buss extension socket vertically. The power supply should be the one mentioned above, or should conform to the dimensions of the case. There is sufficient room available inside it to mount one 5 1/4 or two 3 1/2 inch drives.

Further, a slot must be cut in the front of the cabinet to allow the EPROM disk to be installed. A connector cannot be taken out to the front of the case because the extension of the EPROM connector would create too high an impedance. Micro Concepts will substitute a reduced size EPROM board, in the kit if you specifically ask for it. This will fit fully within the cabinet but must be soldered on to the main board rather than socketed. In practice this only means you will have to replace EPROMs rather than replace the whole EPROM board.

The board should be mounted to the chassis plate with four standoffs. The fit is a bit snug, so make sure you mark the holes correctly before you drill.

The Total Access case is the only one we have tried using, but there is no shortage of other case designs for those who don't mind experimenting a little with mounting and connector

positioning. Vero sell several larger sizes of Total Access case which would allow more flexibility in the choice of power supply, number and type of disc drives and in the use of the EPROM disc board.

There are also a large number of other cases on the market which would no doubt be suitable. For those who want a really professional look, a number of manufacturers offer suites of matching cases to house processor, monitor, keyboard, disc drives and peripherals in several combinations of stacking and distributed units. One such packaging system from Vero was described briefly in a short item in last month's News Digest, and West Hyde Developments and OK Industries are among the other manufacturers who produce this type of case.

### Power-Up And Testing

Assuming that you have purchased your hardware, assembled the board, tested for continuity, inserted the ICs, and connected the peripherals, the next steps are as follows.

First set the switches on SW1 to match the peripherals you have connected. The appropriate settings are shown in Table 5. Now connect power to the board. If all

Hardware	Switch Settings			
	1	2	3	4
Parallel keyboard and video monitor	off	off	off	off
Serial keyboard on Port 1 and video monitor	on	off	off	off
Serial Terminal on 1	on	on	off	off

**Table 5 SW1 switch settings to select peripherals.**

Pin No.	Inner row	Outer row
1, 2	Gnd	nc
3, 4	Gnd	nc
5, 6	Gnd	nc
7, 8	Gnd	index
9, 10	Gnd	Select 0
11, 12	Gnd	Select 1
13, 14	Gnd	nc
15, 16	Gnd	Motor on
17, 18	Gnd	Direction
19, 20	Gnd	Step
21, 22	Gnd	Write data
23, 24	Gnd	Write gate
25, 26	Gnd	Track 0
27, 28	Gnd	Write prot
29, 30	Gnd	Read data
31, 32	Gnd	nc
33, 34	Gnd	nc

**Table 6 Pin connections on the floppy disc port, SK5.**

is well a header and a prompt will appear. The prompt should look like this

=>

Try typing a few characters. If they appear correctly on the screen, use the TM (test memory) command to test memory from 0000 to DE00. While the test is proceeding, tap the board gently. This will show up any bad solder joints.

Now switch off, disconnect all connections to the board and fit the NiCad battery. Be extremely careful not to short circuit it, as it can break open and foam over, damaging the board and making a mess. Momentarily short pin 22 of the clock chip to ground. This will cause it to load the default values into its RAM on power up.

### Memory

AD= ASCII dump of memory  
 HD= Hex dump of memory  
 ME= memory examine  
 PM= Poke memory with value  
 FM= Fill memory with value  
 SM= shift a block of memory  
 FI= find ASCII string in memory  
 TM= test memory  
 DR= display registers  
 CD= calculate displacement

### Input/Output

SI= Set keyboard input port  
 SO= set output port  
 SB= set baud rate  
 LK= load ASCII text from keyboard

### Real Time Clock

DC= display contents of RTC memory  
 MC= modify contents of RTC memory

### Disc

DF= format disk  
 TS= test stepping  
 TD= test drive  
 RS= read sector  
 WS= write sector


### Running Programs

JU= jump to program  
 CP= continue program after software interrupt  
 RP= run program

### Flex

BF= boot Flex from disk  
 BO= boot Flex from wherever it was last booted  
 JT= jump to Flex warm start

**Table 7** A list of monitor commands, arranged according to the area they serve.

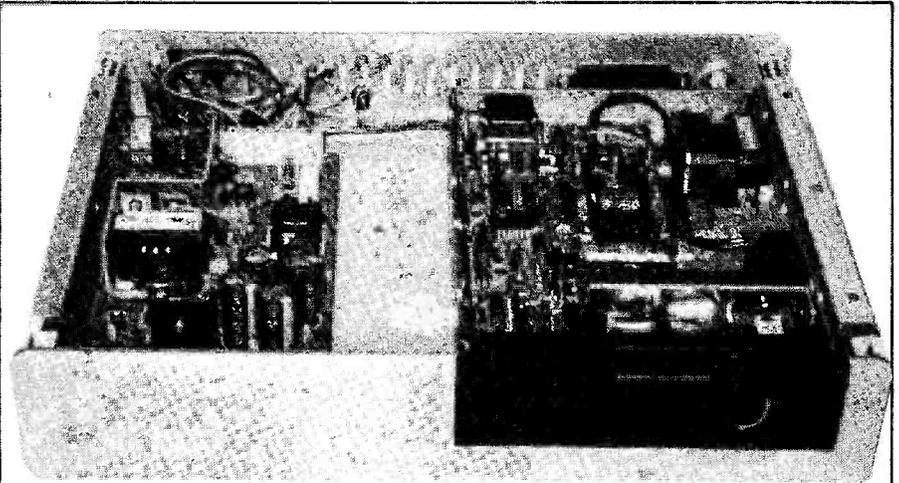

An internal view of the computer showing the power supply and disc drive installed below the chassis.

Reconnect the board. If you have drives, now is the time to hook them up. They should be set for head load with motor on and the drive selected.

A further suite of routines in the monitor which can be used for testing the disk drives is listed in Table 7.

If you have got this far and have Flex, you are ready to boot it. If you don't have Flex, you can still use some of the powerful monitor commands. A list of commands is given in Table 7, each with a short description.

If there are problems with the board here are some things you might check:

are the configuration switches set correctly?

are your serial devices connected correctly?

are any of the chips getting overly hot?

do any of the address or data lines look shorted?

is the 16MHz clock being generated?

are E and Q getting to the processor?

are the DRAMS getting the correct signals?

is the MONO9 EPROM getting the correct signals?

are there any spurious interrupts?

is there a video signal?

Pin No	Inner row	Outer row
1, 2	D6	Gnd
3, 4	D7	Gnd
5, 6	D4	Gnd
7, 8	D5	Gnd
9, 10	D2	Gnd
11, 12	D3	Gnd
13, 14	D0	Gnd
15, 16	D1	Gnd
17, 18	BUSY	Gnd
19, 20	STROBE	Gnd

**Table 8** Pin connections on the printer port, SK1.


Pin No	Inner row	Outer row
1, 2	+5v	+5v
3, 4	Gnd	Gnd
5, 6	BA0	IC19 pin 6
7, 8	BRTS	BA1
9, 10	BD1	BD0
11, 12	BD3	BD2
13, 14	BD5	BD4
15, 16	BD7	BD6
17, 18	BA2	BR/W
19, 20	BA4	BA3
21, 22	16MHz	BE
23, 24	WDS	Q
25, 26	RTC	LPEN
27, 28	I/O2	RDS
29, 30	I/O1	I/OBUFF
31, 32	NMI	RST
33, 34	FIRO	TRQ
35, 36	TTLVID	VSYNC
37, 38	Gnd	Gnd
39, 40	-12v	+12v

**Table 9** Pin connections on the expansion bus socket, SK10.

● Next month's concluding article will discuss applications and the use of the machine and will include a list of some of the Flex software available. A basic kit for this project is available from Micro Concepts, 2 St. Stephens Road, Cheltenham, Gloucestershire GL51 5AA, tel 0242-510525. **ETI**
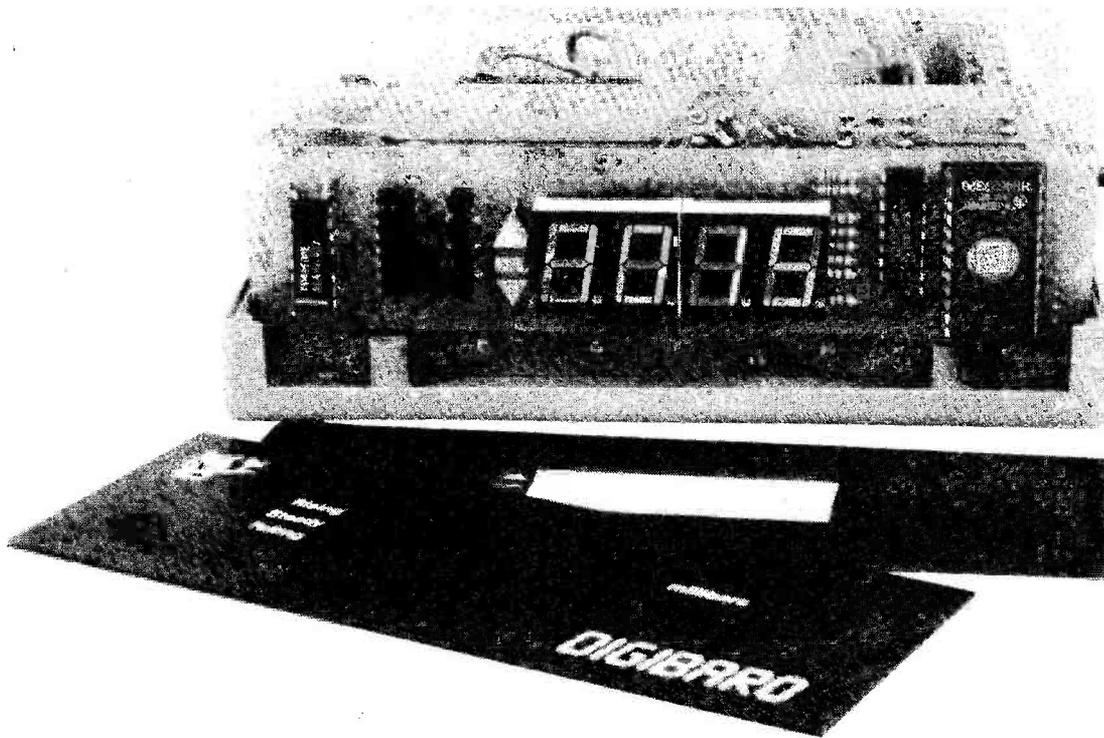
# THE DIGIBARO

Ken Wood supplies the EPROM listing to go with last month's digital barometer design.



```

0000 00 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0010 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0020 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0030 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0040 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0050 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0060 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0070 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0080 10 10 10 10 10 10 10 10 10 10 10 10 10 10
0090 10 10 10 10 10 10 10 10 10 10 10 34 34 34 34
00A0 34 34 34 34 34 34 34 34 34 34 34 34 34 34
00B0 34 34 34 34 34 34 34 34 34 34 34 34 34 34
00C0 34 34 34 34 34 34 34 34 34 34 34 34 34 34
00D0 34 34 34 34 34 34 34 34 34 34 34 34 34 34
00E0 34 34 34 34 34 34 34 34 34 34 34 34 34 34
00F0 34 34 34 34 34 34 34 34 34 34 34 34 34 00
0100 00 40 40 40 40 40 40 40 40 40 40 40 40 40
0110 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0120 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0130 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0140 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0150 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0160 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0170 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0180 40 40 40 40 40 40 40 40 40 40 40 40 40 40
0190 40 40 40 40 40 40 40 40 40 40 40 64 64 64 64
01A0 64 64 64 64 64 64 64 64 64 64 64 64 64 64
01B0 64 64 64 64 64 64 64 64 64 64 64 64 64 64
01C0 64 64 64 64 64 64 64 64 64 64 64 64 64 64
01D0 64 64 64 64 64 64 64 64 64 64 64 64 64 64
01E0 64 64 64 64 64 64 64 64 64 64 64 64 64 64
01F0 64 64 64 64 64 64 64 64 64 64 64 64 64 00
0200 00 80 80 80 80 80 80 80 80 80 80 80 80 80
0210 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0220 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0230 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0240 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0250 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0260 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0270 80 80 80 80 80 80 80 80 80 80 80 80 80 80

```

```

0280 80 80 80 80 80 80 80 80 80 80 80 80 80 80
0290 80 80 80 80 80 80 80 80 80 80 80 80 80 80
02A0 A4 A4
02B0 A4 A4
02C0 A4 A4
02D0 A4 A4
02E0 A4 A4
02F0 A4 00
0300 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0310 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0320 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0330 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0340 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0350 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0360 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0370 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0380 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0390 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03A0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03B0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03C0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03D0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03E0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
03F0 08 08 08 08 08 08 08 08 08 08 08 08 08 08
0400 49 E4 E4 E4 E4 E4 E4 D6 D6 D6 D6 D6 D6 D6
0410 D7 D7
0420 34 34 34 34 34 34 34 34 34 34 34 34 34 34
0430 F6 F6 F6 F6 F6 F6 F6 F6 B7 B7 B7 B7 B7 B7 B7
0440 B7 B7 24 24 24 24 24 24 24 24 24 24 24 24
0450 73 73 73 73 73 73 73 73 76 76 76 76 76 76
0460 E4 D6 D6 D6 D6
0470 D6 D6 D6 D6 D7 D7 D7 D7 D7 D7 D7 D7 34 34
0480 34 34 34 34 34 34 34 34 34 34 34 34 34 34
0490 F7 F7 F6 F6 F6 F6 F6 F6 F6 F6 F6 B7 B7 B7 B7
04A0 B7 B7 B7 B7 B7 B7 24 24 24 24 24 24 24 24
04B0 73 73 73 73 73 73 73 73 73 73 76 76 76 76
04C0 76 76 76 76 E4 E4 E4 E4 E4 E4 E4 E4 E4
04D0 D6 D6 D6 D6 D6 D6 D6 D7 D7 D7 D7 D7 D7 D7
04E0 D7 D7 34 34 34 34 34 34 34 34 34 34 34 34
04F0 F7 F7 F7 F7 F7 F7 F6 F6 F6 F6 F6 F6 F6 F6

```



# RS232-CENTRONICS CONVERSION

D.J. Virden has come to the rescue of numerous readers who want to convert an RS232 into a Centronics output.

If you have a computer equipped with a RS232 port, but your printer has a Centronics interface then you will have to beg, steal or build a serial-to-parallel converter, not a cheap bit of equipment by any means. RS232 printers also tend to be more expensive than their Centronics equivalent, but many portable and cheap micros sport only the RS232 output.

The RS232 interface was developed as a standard to ensure compatibility between equipment from different manufacturers. The output levels from the interface can be anywhere between +3V and +15V for an on state and -3V to -15V for an off state. The area between -3V and +3V gives some degree of noise immunity. The output data is asynchronous, using stop and start bits to achieve synchronisation. Fig. 1 shows the transmission sequence of a complete byte.

## The Circuit

The heart of the interface is the General Instruments AY-3-1015D UART (Universal Asynchronous Receiver/Transmitter), whose sole purpose in life is to convert serial data to parallel and vice versa. However, only the receiver section of the device is used in the circuit. The chip can also cope with parity and any number of data bits from five to eight. The number of stop bits can be one or two. The circuit is shown in Fig. 2.

Data from pin 2 (Tx) of the RS232 plug is fed to Q2 which converts the bipolar data signal to a TTL level. This TTL level is fed to the serial input of the UART. The UART strips the data byte of its sync bits, and presents the byte in parallel to the data lines RD1-RD8. Each time a data byte is received the DAV latch is set, signalling that data is available. This line is connected via a monostable (IC5) to the printer's data strobe. Data strobe is brought low and the byte is stored in the printer's buffer. While it is doing this the printer signals that it cannot accept more data by setting BUSY high. BUSY is connected via Q3 to CTS (pin 5). When the data byte has been stored, the

printer sets BUSY low and sends an acknowledged pulse which is used to reset the DAV latch, enabling another byte to be sent.

IC2 c and d and XTAL1 form an oscillator whose output is fed to the dividers, IC3 and IC4. The outputs from the dividers are used for the clock input of the UART. The clock rate is 16 times the desired baud rate. For example, the clock rate required for a receiver rate of 2400 baud is  $16 \times 2400 = 38.4 \text{ KHz}$ . The baud rate is selected by connecting wire link LK1 to the appropriate divider output, marked A, B, C and D.

If lower baud rates are required, replace the 7493 counter with a CMOS 4040 12 bit counter. This will allow speeds down to 75 baud. This should only be required when the equipment you are using to transmit the data is incapable of higher speeds, as the Centronics itself is capable of keeping up with all but the highest baud rates.

IC6 and IC7 are used to buffer the signals going to and from the printer. These are open collector as the printer inputs are all pulled up to 5V.

## In Use

A power supply for the unit is not given. It is worth examining the feasibility of using the printer's power supply. The Microline 80, for example, has a power pin at 10V DC, 150mA (P34), which could be used to derive the required TTL supply of 5V, and one at 23V AC, 50mA (P36), which could be the source for the bipolar swing required by the RS232 specification. Figure 3 shows the connections to this printer — other printers with Centronics inputs may differ slightly and you should check with the manual.

Pull-up resistors are not necessary with SW1 since all inputs to the 1015 are pulled-up internally. Table 1 shows the effect of each switch on the data transmission parameters.

After the unit is constructed select the transmission

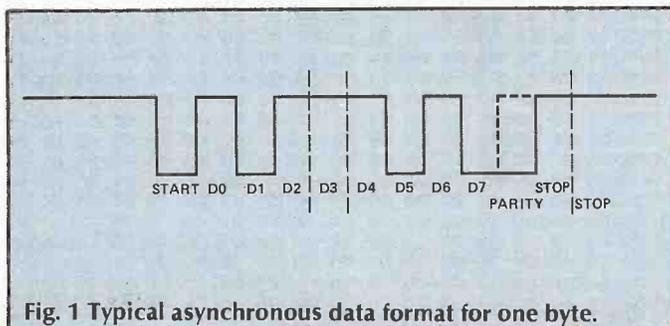


Fig. 1 Typical asynchronous data format for one byte.

SW1	a	b	DATA BITS	c	d	PARITY	e	STOP BITS
1	1	5*	X	0	off	1	1	
1	0	6	1	1	odd	0	2*	
0	1	7	0	1	even	—	—	
0	8	—	—	—	—	—	—	

(\* combination of two stop bits and five data bits gives 1½ stop bits.)

1=Switch closed. Use DIL switch unit or independent miniature toggles.

Table 1 Transmission parameter selection using SW1.

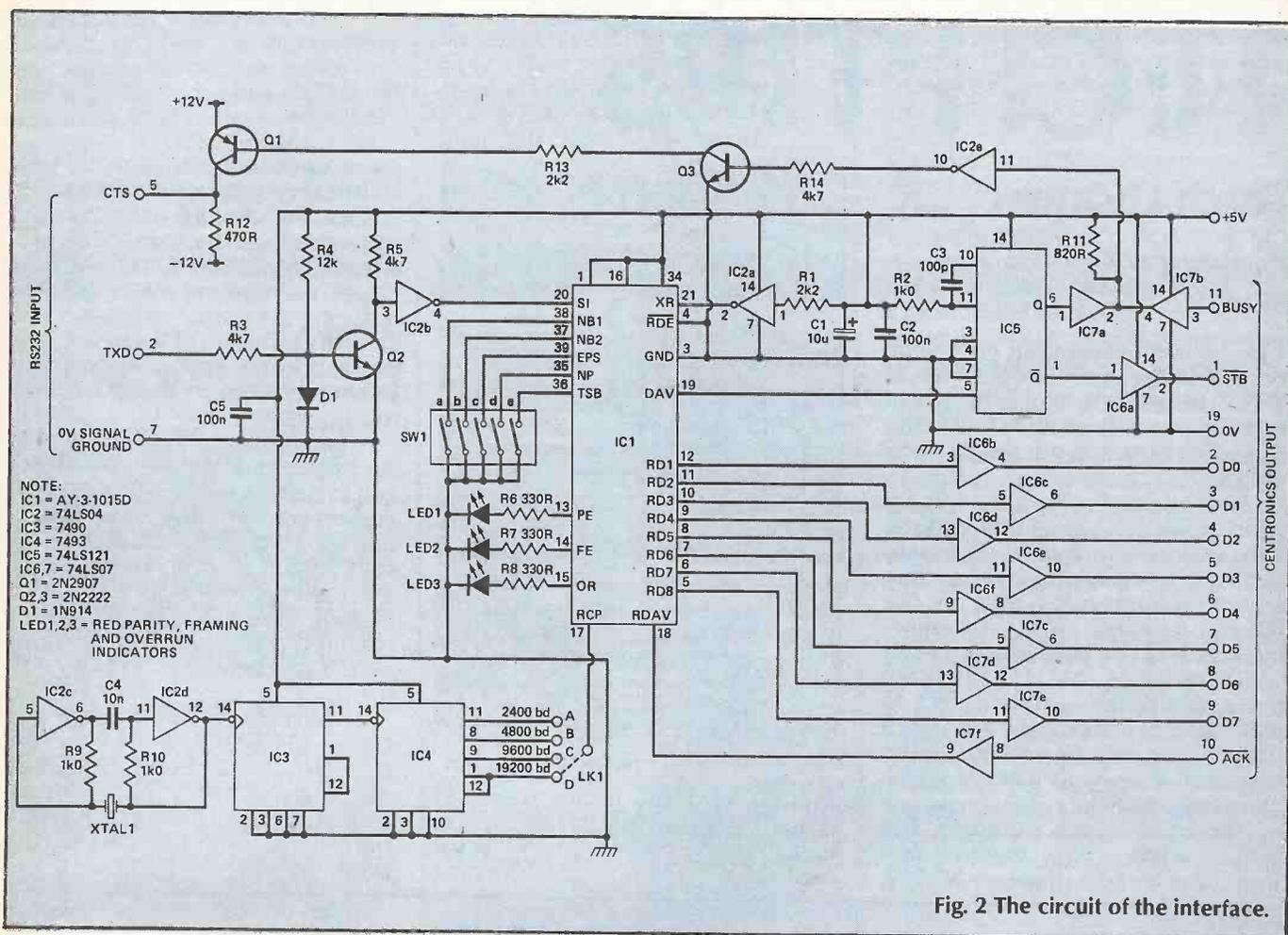


Fig. 2 The circuit of the interface.

parameters required — baud rate, parity and number of data and stop bits. Switch off the printer and computer while you connect up the leads. Test the unit is working by sending text to the printer. Refer to your users' manual on how to do this.

If the interface does not seem to work, check the error LEDs. If the frame error LED is on, you are either running the unit at the wrong baud rate or have the parity switch in the wrong position. The overrun LED indicates that a byte has not been read from the UART. If this occurs check the connections from the unit to the printer. The parity error LED indicates that the parity check has returned an incorrect value. You will probably need to confirm the settings on your printer and adjust SW1 accordingly.

The *CIRCUIT SOLUTION* section is designed to provide original design ideas and solutions more comprehensively than *TECH TIPS* but without the complexities of a full-scale project. Readers are invited to experiment and design their own stripboard or PCB layouts.

ETI


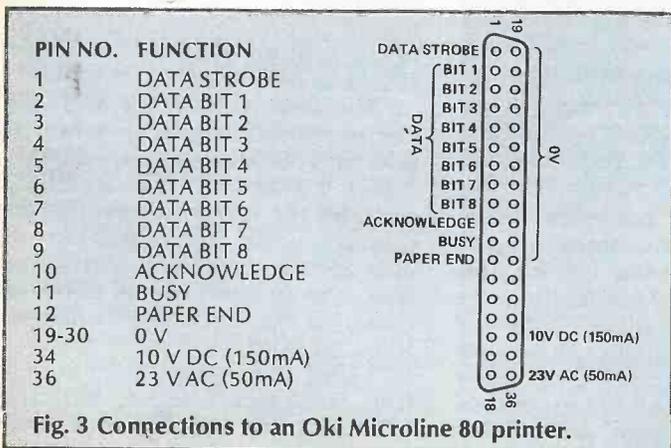


Fig. 3 Connections to an Oki Microline 80 printer.

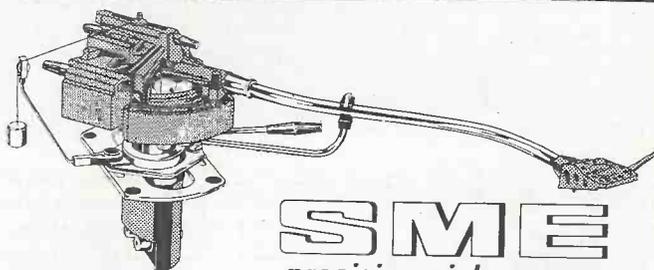

**SME**  
 precision pick-up arms

Please call or write:  
 SME Limited, Steyning, Sussex, BN4 3GY  
 Telephone: 0903 814321 Telex: 877808 G

# TECH TIPS


## Torch Locator

L.M. Loong  
Hong Kong

Having been caught out on several occasions by unexpected power cuts, I resolved to find a means of making my torch easier to find in the dark. This circuit is the result of my efforts.

It consists of a simple oscillator which will flash an LED on and off. The current drawn by the LED is quite small and using a flashing rather than a steady illumination reduces the current demand. A further refinement is an LDR light sensor circuit which switches the LED off when there is sufficient ambient light to make it unnecessary. As a result, a battery life of at least a month can be expected even with torches which use penlight cells.

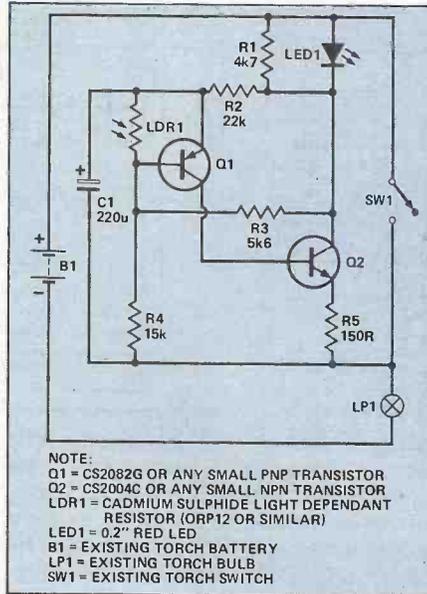For construction purposes, the best type of torch to convert is one using D size cells (HP2, MN1300,




R/LR20, etc.) and having plenty of space inside the case. It is also a good idea to get one with a lamp reflector made of silvered plastic, as the best

place to mount both the LED and LDR is on the silvered surface. This ensures that the LED flashes are projected well and that the LDR picks up all the light around the reflector and biases the flashing circuit off, thus reducing the current demand. With care, the intrusion of these two components has negligible effect on the beam produced by the torch in normal operation.

The component values given are for 3 volt operation and allow the circuit to work down to 2.5 volts. As the current consumption is minimal, the normal 3 volt torch bulb, although still in circuit, is not illuminated whilst the flashing circuit is operational. The flashing circuit is effectively short-circuited when the normal on/off switch is operated to switch on the torch.

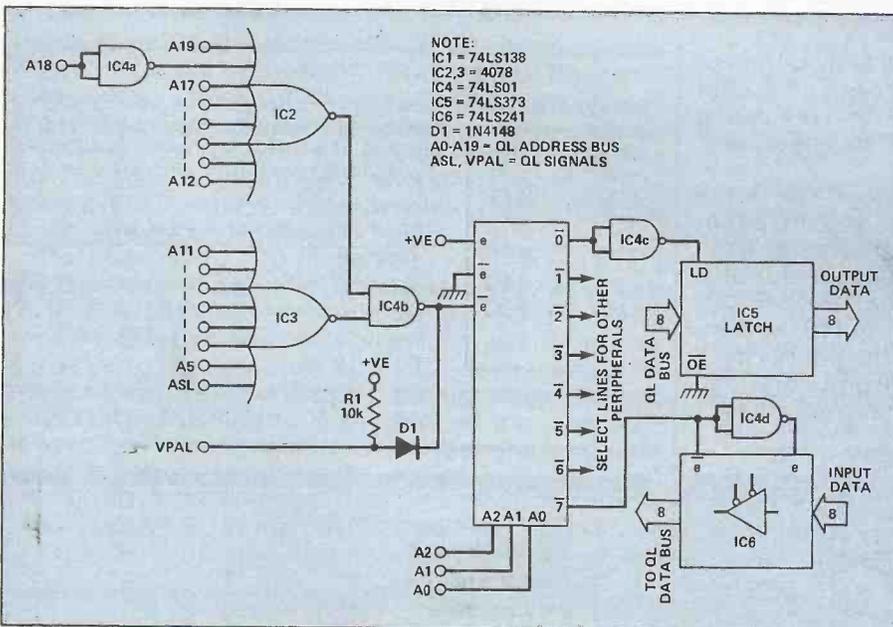Whilst the circuit diagram gives Q1 as a CS 2082G and Q2 as a CS2004C, these being Hong Kong made transistors I had to hand, almost any small plastic cased silicon transistors will function in their positions.



## Interfacing The QL

Greg Parker  
London N11

Now that the Sinclair QL costs only £200 or so it is within reach of the electronics experimenter. It may even replace the Spectrum as the computer workhorse for which most

interface projects are made. It is, however, a bit more complicated to interface than the old faithful Z80 with all its ideal I/O capabilities.

Looking at the edge connector pin-out (in the manual) it can be seen that various devices have been added to the basic 68008 to confuse matters. So I wrote to Sinclair Research for some explanation; they

replied that a book costing £15 would help — please send a cheque. Unwilling to spend £15 on a book, I decided to rely on common sense and designed this circuit.

The standard 68000 accesses a peripheral by setting up the address and data busses and asserting the Address Strobe (ASL) line. If the address is correct the peripheral replies with a Valid Peripheral Address (VPAL) signal. The 68000 then confirms this with a Valid Memory Address (VMAL) signal, inserting wait states to allow for slow peripherals. On the QL, the VMAL line is not brought to the edge connector so proper handshaking cannot be assured, but the circuit shown seems to work well.

The two NOR gates and IC4a decode the address bus — when the address 4000x(h) is accessed VPAL is pulled low and IC1 is enabled. IC1 decodes the low 3 address bits and outputs a SELECT signal to the appropriate peripheral. An output latch and an input 3-state buffer are shown as examples. The devices are selected from BASIC by PEEKing or POKEing the appropriate address (the addresses from 40000(h) to C0000(h) are specifically reserved for expansion I/O).

## Self-Activating Siren

Steve Brown,  
Woking

This simple analogue self-activating siren for an intruder alarm offers several functional advantages over its more usual digital rivals but uses only one 8-pin IC.

The main features are:


- virtually tamper proof
- fault protected
- automatic reset
- siren disable
- retriggerable while siren sounds
- uses 4-core cable — 2 signals, 2 power.

The siren is activated by a retriggerable monostable (for example, a 4047B or NE555) in the control unit which sends a 2s duration logic pulse to input B. The pulse length is kept short for security reasons but is long enough to fully charge C3 via D1 and R1 (C3 will be 95% fully charged in three R1C1 time constants or about 1.5s).

Op-amp IC1b compares the voltage across C3 with the threshold voltage  $V_{TH}$  which is set by the voltage divider R9, R10. For a +12V supply rail,  $V_{TH}$  is 365mV. When  $V_{TH}$  is exceeded at pin 5 of IC1b, its output saturates at +12V, Q2 turns hard on and the siren sounds.

As the siren sounds, C3 will exponentially discharge to 0V via R3. After a time  $t$  ( $=3.5 \times R3 \times C3s$ ), the threshold voltage begins to exceed C3 voltage and the siren switches off. In practice, this time may be double its theoretical values (Table 1).

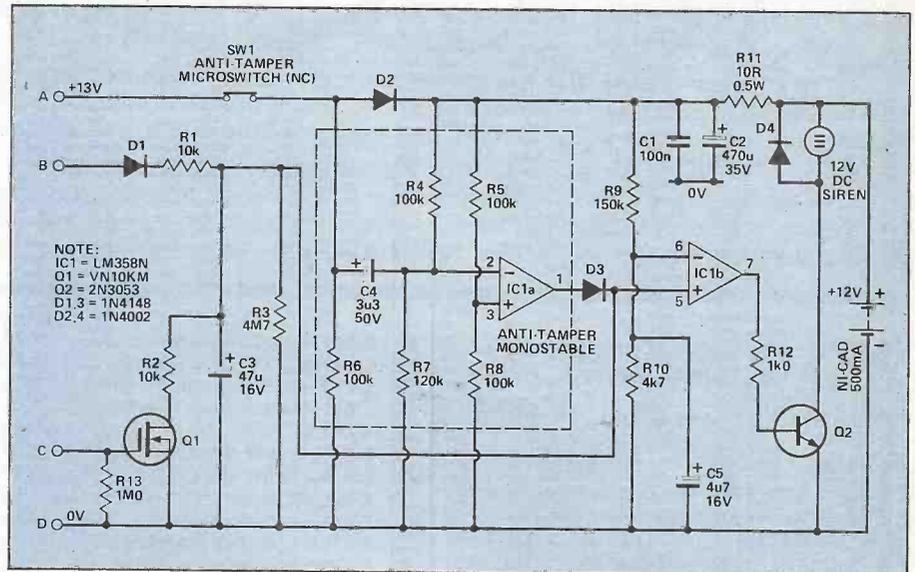A surprise result in Table 1 is the relatively poor performance of low-leakage tantalum bead capacitors against electrolytics. This may be



due to the fact that electrolytic capacitors usually have a high over-tolerance (up to +50%) and consequently offer better value for money. For longer on-times,  $V_{TH}$  can be reduced or R3 increased. However op-amp offset voltage and noise considerations will set a minimum  $V_{TH}$  while leakage currents through C3 will set a maximum on-time.

IC1a and its associated components form a classic op-amp monostable. When the +ve supply is interrupted a 1-2s logic pulse is transferred to C3 via D3 and the siren sounds as before.

Input C allows the siren to be

controlled from the control unit. When the alarm is armed, input C is latched low. In SIREN TEST mode, input B goes high for the test duration and input C is also latched high. C3 discharges via Q1 and R2 immediately input B goes low. Similarly, input C is latched high for SIREN DISABLE mode and the siren is switched off and held off.

The op-amp circuits are filtered from the siren switch-on transient by C1, C2 and R11. These components can be omitted if a low current drain electronic siren is used. C5 provides extra filtering for  $V_{TH}$  and prevents oscillations around IC1b as the input voltages approach one another.

IC1 was selected for the ability of both inputs and outputs to swing from +Vcc to ground, although in practice, most op-amps can be used.

D1 and D2 provide tamper and reverse polarity protection while D4 would be added if the siren is an inductive device.

ETI

R	theory	tant.	elect.
1M5	247	345	400
3M3	543	780	850
4M7	773	1005	1440
O.C.	—	1860	2700

Table 1

## KEF CONSTRUCTOR SERIES SPEAKER KITS

Based on the famous Kef Reference Series, these three DIY designs give the home constructor the opportunity to own an upmarket pair of loudspeakers at a very down-to-earth price!

With a Wilmslow Audio Total Kit it's so easy — no electronic or woodworking skill is necessary. Each kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly), speaker drive units, crossover networks, wadding, grille fabric, terminals, nuts, bolts etc.

Model CS1 is based on the Reference 101, CS3 is equivalent to the Ref. 103.2 and CS9 is based on the Reference 105.2 (but in a conventionally styled encl.).


CS1 £116 pair inc. VAT plus carr/ins £6

CS3 £138 pair inc. VAT plus carr/ins £10

CS9 £383 pair inc. VAT plus carr/ins £18

We also offer a kit (less cabinet) for Elector PL301

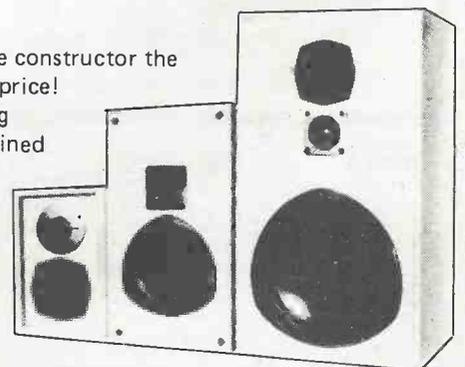Lightning service on telephoned credit card orders!



WIMSLow AUDIO LTD. 35/39 Church Street, Wilmslow, Cheshire SK9 1AS Tel: 0625 529599

Call and see us for a great deal on HiFi. (Closed all day Mondays)

DIY Speaker catalogue  
£1.50 post free (export \$6)

# ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third and fourth are the month and the number after the hyphen indicates the particular project.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until after we receive payment.

## 1981

- E/8107-1 System A disc input, MM/MC ..... 3.58
- E/8107-2 System A preamplifier ..... 7.10

## 1982

- E/8202-5 MM disc preamp ..... 4.13
- E/8207-1 Microphone switching unit ..... 3.36
- E/8208-1 Playmate practice amplifier ..... 7.45
- E/8209-1 Auto volume control ..... 3.59

## 1983

- E/8301-2 ZX81/Spectrum ADC ..... 3.87
- E/8305-1 Stereo compressor/limiter ..... 8.83
- E/8305-3 Hi-fi power supply ..... 4.48
- E/8305-4 NDFL power amplifier ..... 10.32
- E/8305-5 Balanced input preamp ..... 3.68
- E/8306-1 PseudoROM# ..... 3.77
- E/8307-1 Flash sequencer ..... 3.67
- E/8307-2 Flash Trigger ..... 3.67
- E/8307-3 Infra-red transmitter ..... 2.21
- E/8308-1 1/2 octave graphic equaliser ..... 11.59
- E/8309-1 NiCad charger/regenerator ..... 3.77
- E/8310-2 Car Alarm ..... 3.99
- E/8310-3 Typewriter interface ..... 4.11
- E/8311-1 Mini Drum Synth ..... 3.85
- E/8311-8 JLLM MC disc preamp ..... 3.85
- E/8312-3 Finesse light chaser ..... 12.48

## 1984

- E/8402-1 Speech Board Mini-Mynah ..... 11.47
- E/8402-2 MP (Modular Preamp) Disc input (mono) ..... 3.80
- E/8402-3 MP Output stage (stereo) ..... 3.80
- E/8402-4 MP Relay/PSU ..... 3.80
- E/8402-5 MP Tone, main (mono) ..... 3.80
- E/8402-6 MP Tone, filter (stereo) ..... 3.80
- E/8402-7 MP Balanced output (st) ..... 3.80
- E/8402-8 MP Headphone amp (st) ..... 3.80
- E/8402-9 MP Mother Board ..... 11.64
- E/8403-1 Power Meter, stereo ..... 6.93
- E/8403-2 Z80 DRAM ..... 10.24
- E/8404/2 Mains Borne RC rcvr ..... 3.80

- E/8405-1 Auto Light Switch ..... 4.11
- E/8405-2 ZX81 EPROM Prog ..... 11.00
- E/8405-3 Mains Borne RC xmtr ..... 5.70
- E/8405-4 Centronics Interface ..... 4.06
- E/8405-5 Vario ..... 7.95
- E/8405-6 Midi Drum Synth ..... 3.63
- E/8406-1 Oric EPROM Bd ..... 20.47
- E/8406-2 Spectrum Joystick ..... 3.52
- E/8407-1 Warlock Alarm ..... 9.45
- E/8408-1 Joystick Interface ..... 3.96
- E/8408-2 EPROM Emulator ..... 12.42
- E/8408-3 Infrared Transmitter ..... 3.96
- E/8408-4 Infrared Receiver ..... 3.96
- E/8409-1 EX42 Kybd Interface ..... 3.93
- E/8409-3 Dry Cell Charger ..... 2.82
- E/8410-1 Echo Unit ..... 3.95
- E/8410-2 Digital Cassette ..... 10.25
- E/8410-3 Disco/Party Strobe ..... 5.31
- E/8411-1 AM/FM Radio (4 bds) ..... 14.61
- E/8411-2 Control Port-control bd ..... 12.70
- E/8411-3 Control Port-I/O bd ..... 6.62
- E/8411-4 Capacitance Meter ..... 3.68
- E/8411-5 Video Vandal (3 bds) ..... 12.44
- E/8411-6 Temperature Controller ..... 3.02
- E/8411-7 Mains Failure Alarm ..... 2.63
- E/8411-8 Knite Light ..... 3.96
- E/8411-9 Stage Lighting Interface ..... 3.74
- E/8411-10 Perpetual Pendulum ..... 3.38
- E/8412-1 Spectrum Centronics ..... 3.57
- E/8412-2 Experimenter's DRAM ..... 14.72
- E/8412-3 Active-8: Motherboard ..... 12.22
- E/8412-4 Active-8: Protection Unit ..... 3.69
- E/8412-5 Active-8: Crossover ..... 3.69
- E/8412-6 Active-8: LF EQ ..... 3.69
- E/8412-7 Active-8: Equaliser ..... 3.69
- E/8412-8 Active-8: Delay Unit ..... 3.69

## 1985

- E/8501-1 Active Bass speaker ..... 2.82
- E/8501-2 DRAM Card Update ..... 3.61
- E/8501-3 Digital Delay (2 bds) ..... 27.18
- E/8502-1 Digital Delay Expander ..... 11.28
- E/8502-2 Data Logger ..... 6.21
- E/8503-1 Combo preamplifier ..... 4.74
- E/8503-2 THD meter mV & osc. bds ..... 7.41
- E/8503-3 THD meter mains PSU ..... 3.63
- E/8503-4 THD meter battery PSU ..... 1.59
- E/8503-5 ParaGraph Equaliser IP/MSP & OP/PSU bds ..... 10.42

- E/8503-6 ParaGraph Equaliser filter bd ..... 4.93
- E/8504-1 Framestore Memory ..... 12.05
- E/8504-2 Framestore ADC/DAC ..... 6.21
- E/8504-3 Framestore Control ..... 17.26
- E/8504-4 Buzby Meter ..... 3.56
- E/8504-5 CCD Delay ..... 3.82
- E/8505-1 6802 board ..... 8.22
- E/8505-2 EPROM prog. update ..... 5.28
- E/8505-3 Scoreboard controller, PSU and opto-isolator bds ..... POA
- E/8505-4 Scoreboard digital driver ..... 4.27
- E/8505-5 Stereo Simulator ..... 3.64
- E/8506-1 Audio mixer main bd ..... 6.40
- E/8506-2 Audio mixer PSU bd ..... 3.98
- E/8506-3 Audio mixer RIAA bd ..... 2.62
- E/8506-4 Audio mixer tone ctrl ..... 2.85
- E/8506-5 EPROM Prog MkII ..... 14.90
- E/8507-1 Noise Gate ..... 5.72
- E/8508-1 RCL Bridge ..... 12.25
- E/8508-2 EX42/BBC Interface ..... 3.25
- E/8508-3 EPROM Emulator ..... POA
- E/8509-2 Direct Injection Box ..... 2.90
- E/8509-1 SpectROM ..... POA
- E/8510-7 Sorcerer Boards ..... POA
- E/8510-9 Sunrise Light Brightener ..... 6.61
- E/8510-8 MTE Power Supply ..... 17.60
- E/8511-1 MTE Waveform Generator 4.83
- E/8511-2 Millifarodometer ..... 4.69
- E/8511-3 Cymbal Synth ..... 6.04
- E/8511-4 Memory Scope ..... 10.65
- E/8511-5 Chorus Effect ..... 5.16
- E/8511-6 Rhythm Chip ..... \*
- E/8511-7 Enlarger Exposure Meter ..... 3.86
- E/8511-8 Switching Regulator ..... 3.75
- E/8511-9 Second Line Of Defence ..... 9.94
- E/8512-1 Specdrum Connector ..... \*
- E/8512-2 MTE Pulse Generator ..... 6.62
- E/8512-3 Specdrum ..... \*
- E/8512-4 DI Compression Gate ..... \*

## 1986

- E/8601-1 Autowipe ..... \*
- E/8601-2 Walkmate ..... POA
- E/8601-3 MTE Counter/timer ..... POA
- E/8602-1 Digibarot ..... 11.80
- E/8603-1 Free PCB ..... \*
- E/8603-2 Programmable logic bd ..... 5.52
- E/8603-3 Sound Sampler Analogue bd ..... POA

\* PCB available from another source. See the original article for details.

‡ Several boards supplied as one. Purchaser must separate.

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ASP Readers' Services, PO Box 35, Wolsey House, Wolsey Road, Hemel Hempstead, Hertfordshire HP2 4SS, tel 0442-41221. Payment in sterling only please. Prices subject to change without notice.

Total for boards £ .....  
 Add 50p p&p 0.50  
 Total enclosed £ .....



**PLEASE ALLOW  
 28 DAYS FOR  
 DELIVERY**

Signed .....

Name .....


Address .....


# PCB FOIL PATTERNS

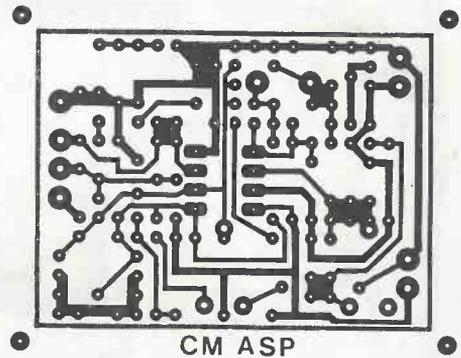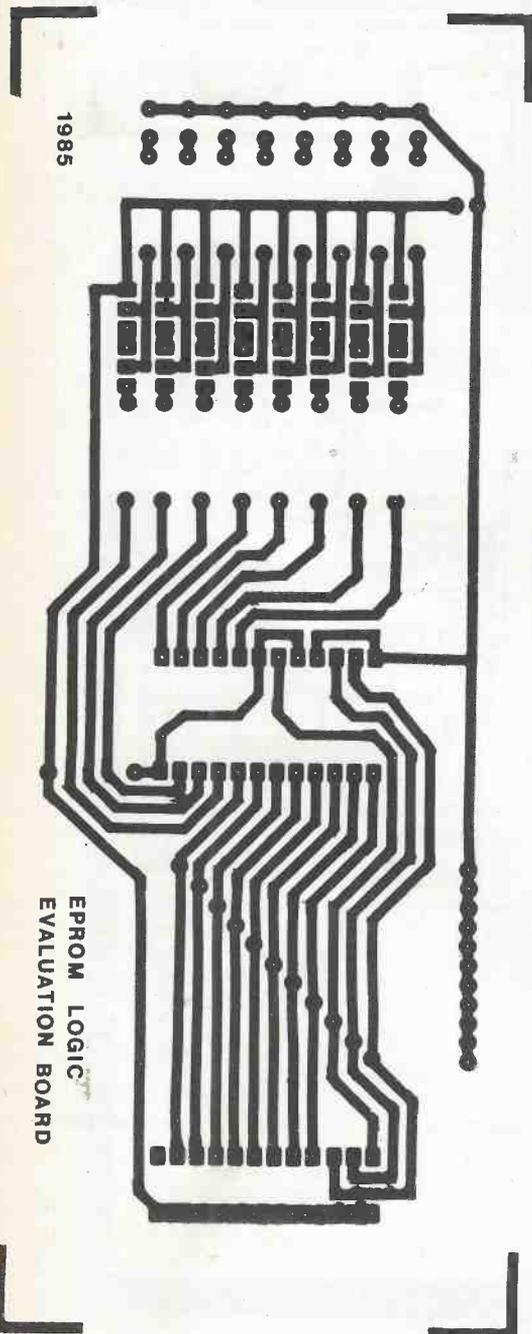

The foil pattern for the free PCB, just in case you want to make up some extra ones! The board will not be available through our PCB Service, but we have had a quantity made up and these will be available until stocks are exhausted from Argus Readers' Services at the address given on the PCB Service page. The cost will be £1.00 each and cheques, postal orders, etc should be made payable to ASP Limited. Please enclose a stamped, self-addressed envelope.

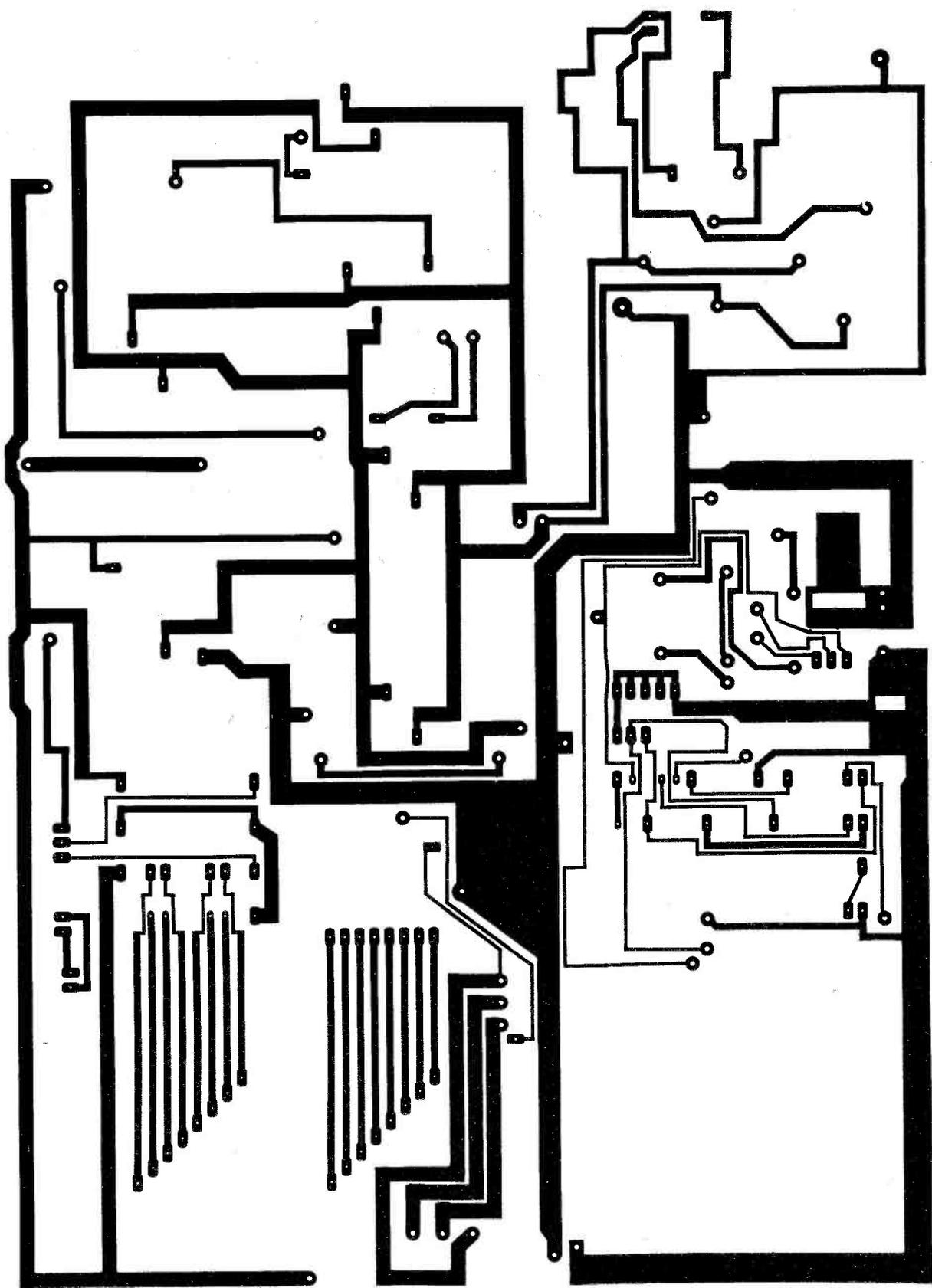The foil pattern for the programmable logic evaluation board.



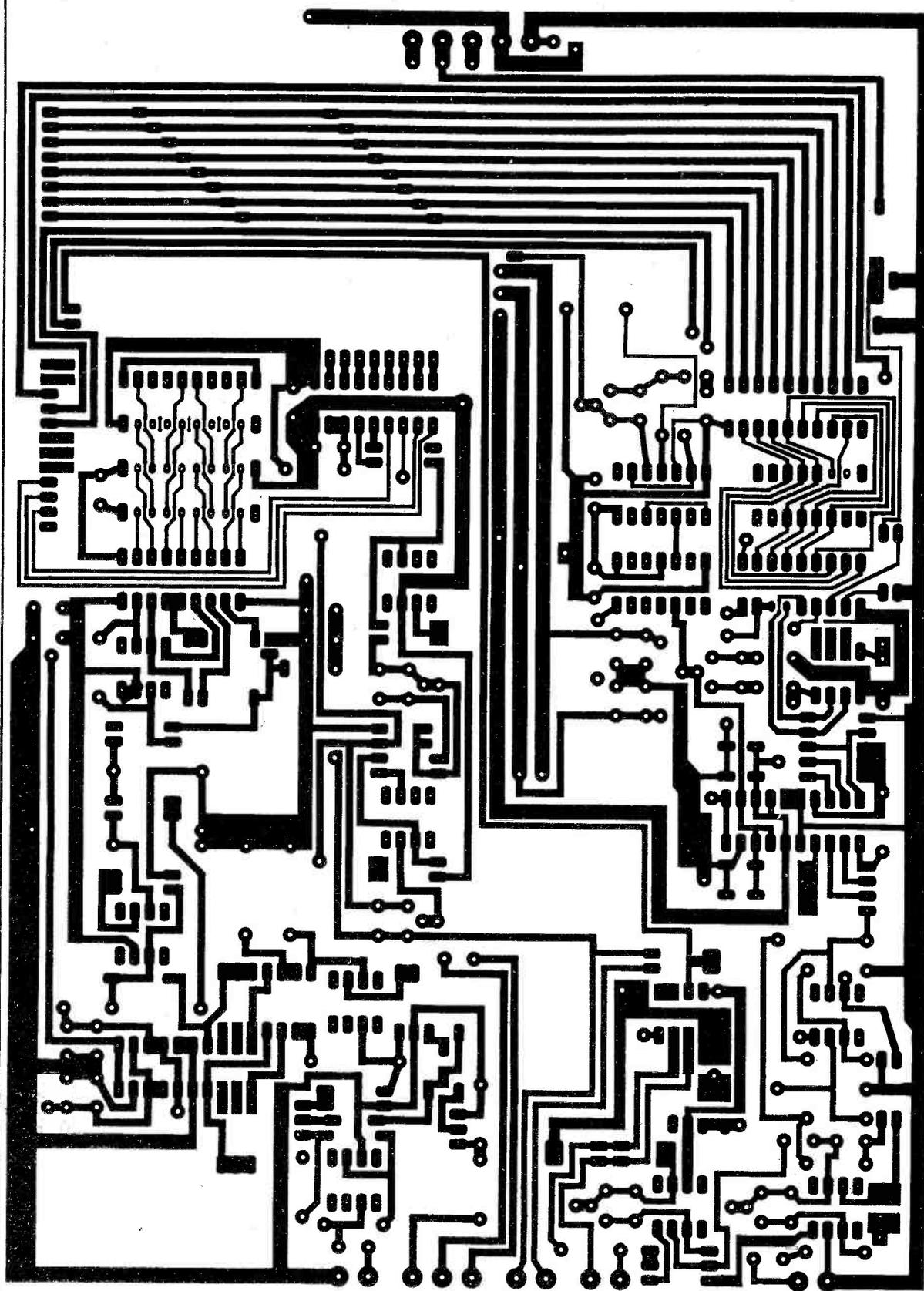

# SERVICE SHEET

## Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We receive a large number of letters asking if we have published projects for particular items of equipment. Whilst some of these can be answered simply and quickly, others would seem to demand the compiling of a long and detailed list of past projects. To help both you and us, we have made a full index of past ETI projects and features available (see under Backnumbers, below) and we trust that, wherever possible, readers will refer to this before getting in touch with us.
- **We will not reply to queries that are not accompanied by a stamped addressed envelope** (or international reply coupon). **We are not able to answer queries over the telephone.** We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

## Subscriptions

The prices of ETI subscriptions are as follows:  
UK: £18.10  
Overseas: £22.50 Surface Mail  
\$29.50 Surface Mail (USA)  
£49.50 Air Mail

Send your order and money to: ETI Subscriptions Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

## Backnumbers

Backnumbers of ETI are held for one year only from the date of issue. The cost of each is the current cover price of ETI plus 50p, and orders should be sent to: ETI Backnumbers Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire HP1 1BB. Cheques, postal orders, etc should be made payable to ASP Ltd. We suggest that you telephone first to make sure there are still stocks of the issue you require: the number is (0442) 48432. Please allow 28 days for delivery.

We would normally expect to have ample stocks of each of the last twelve issues, but obviously, we cannot guarantee this. Where a backnumber proves to be unavailable, or where the issue you require appeared more than a year ago, photocopies of

individual articles can be ordered instead. These cost £1.50 (UK or overseas surface mail), irrespective of article length, but note that where an article appeared in several parts each part will be charged as one article. Your request should state clearly the title of the article you require and the month and year in which it appeared. Where an article appeared in several parts you should list these individually. An index listing projects only from 1972 to September 1984 was published in the October 1984 issue and can be ordered in the same way as any other photocopy. If you are interested in features as well as projects you will have to order an index covering the period you require only. A full index for the period from 1972 to March 1977 was published in the April 1977 issue, an index for April 1977 through to the end of 1978 was published in the December 1978 issue, the index for 1979 was published in January 1980, the 1980/81 index in January 1982, the 1982 index in December 1982, the 1983 index in January 1984, the 1984 index in January 1985 and the 1985 index in December 1985. Photocopies should be ordered from: ETI Photocopies, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Cheques, postal orders, etc should be made payable to ASP Ltd.

## Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

## Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

## OOPS!

Corrections to projects are listed below and normally appear for several months. Large corrections are published just once, after which a note will be inserted to say that a correction exists and that copies can be obtained by sending in an SAE.

### Single Board Controller (March 1985)

There were a number of errors in the parts list. RP2 is listed as a 10k SIL pack but is actually four separate resistors, and the same applies to RP3. RP4 is also listed as a SIL pack but should consist of seven commoned resistors. R13 is always required, not just when a cassette interface is used as stated.

### The Real Components (May 1985)

In Fig. 1 on page 20, the connections for the Texas L and 2N transistors are incorrectly shown. They should read B, C and E from the top.

### Heat Pen (June 1985)

The instruction in the penultimate paragraph on page 49 should read "... adjust RV2 for 2.73V ...", not 2.37V as stated.

### Low Cost Audio Mixer (June 1985)

In Fig. 6 on page 39, the PCB foil pattern has been incorrectly shown as though from the copper side. The board is shown correctly from the copper side in the foil pattern pages. In Fig. 10 on page 40, the positive power rail at lower left should be shown connected to pin 8 of the TL072s, IC1-5).

### Noise About Noise (July 1985)

In Fig. 5 on page 24, no connection should be shown between the cathode of the diode and the negative side of the 470u capacitor.

### Printer Buffer (July 1985)

The case specified is actually larger than the one used for the prototype. It will, of course, work perfectly well, but if you want to a compact unit use a Verocase 202-21038H (180 x 120 x 65mm) rather than a Verocase 202-21035. The regulator IC17 should be bolted to the back of the case to provide heatsinking or, alternatively, fitted with a TO220 heatsink.

Please note that the designer, Nick Sawyer, has been in touch to inform us that the refresh problem we mentioned in September ETI is dealt with in the printer buffer software. In this case there is no need to replace the TMS 4416 dynamic RAMs, although as far as we know the replacement parts mentioned (Hitachi HM48416 DRAMs) will cause no problems. The full text of Nick Sawyer's letter will appear next month. Meanwhile, our apologies for any confusion caused.

### Cortex Parallel I/O (September 1985)

Pins 1 and 2 of IC2 have been swapped over on both the circuit diagram (Fig. 1) and the Veroboard overlay (Fig. 2). Pin 1 should connect to pin 16 on the header and pin 2 should connect to pin 2 on the header.

### Intel 8294 Data Encryption Unit (September 1985)

It should be apparent from the text, page 35, that an actual program has been omitted. This program is for use with the SDK 8085 kit only, and copies may be obtained from us on receipt of a stamped addressed envelope.

### Tech Tips — Novel Input Stage (October 1985)

The caption against the lower figure should read "Low noise output at *minimum* gain", not maximum gain.

### Chorus Unit (November 1985)

IC3 is shown on the circuit diagram on page 49 connected to the 9V supply. It should be connected to the 5V supply. The foil pattern connections to this IC are correct.

### Foil Patterns (November 1985)

The foil patterns for the Modular Test Equipment Waveform Generator and the Chorus Unit are shown from the component side rather than the copper side.

## REVIEWS — QL BOOKS

Introduction to SuperBASIC on the Sinclair QL  
Price: £6.95

Advanced Programming with the Sinclair QL  
Price: £6.95

Hutchinson and Co. Ltd., 17-21 Conway Street,  
London W1P 6JD

### QL COMPUTING

Ian Sinclair. Price £5.95

Granada Publishing Ltd., 8 Grafton Street, London  
W1X 3LA.

With the Sinclair QL now selling (or, maybe, attracting dust) at £199, it seems a good time to look at some of the titles available for that machine. Hutchinson — like a number of other more-or-less foolhardy publishers — are in the throes of a QL series. The latest two additions add texts on Sinclair 'SuperBASIC' and 'Advanced Programming' to a list already featuring an introduction to the computer and books on word-processing and desk-top computing.

The SuperBASIC title contains all the usual ingredients, with chapters on topics ranging from how to plug the QL in to all the

wonderful intricacies of procedure structuring and the like. Appendices deal with SuperBASIC keywords and computing terms.

#### All QLearn?

The layout is clear and the text fairly readable. Simple exercises are included at the ends of most chapters, but there isn't anything outstanding to merit recommendation over many other books in the same vein — especially since the manual — although bad in many ways — will probably serve for most would-be QL users.

'Advanced Programming ...'

should not be regarded as a sequel to the previous book. In fact, the contents aren't so much advanced when compared to that book as just different.

Aimed at those people whom the author euphemistically calls 'practical' users, the book reminds me very much of books published around a decade ago with such unassuming titles as 'Computer Programming Made Really Easy' which then proceed to be as stodgy as a bowl of cold custard. In this case, 'advanced' seems to be a synonym for monotonous.

On the credit side, the last chapter contains some simple business and statistical programs which may be of some interest.

'QL Computing' by the redoubtable Ian Sinclair is yet another beginners' guide to SuperBASIC in an already flooded market. Much of the book is the usual standard fare we have come to expect from Ian Sinclair's word-processor and is, as a result, no better than the manual. The main body of the book, however, departs from the manual style of presentation in which keyword functions are summarized in alphabetical order. It is arranged in a prosaic fashion, with

examples of usage and simple demonstrative programs to type in and experiment with. Consequently, the book has some degree of continuity and is more effective at teaching the rudiments of SuperBASIC than a manual style book, which may be useful for reference at a later stage.

#### In ConQLusion


All the QL's assets are dealt with in this relatively comprehensive publication, including micro-drives, effective graphics and the usually neglected sound producing capabilities of the QL. If you are bemused by BASIC or just confused by computer, you could do a lot worse than buy 'QL Computing'.

None of the books dealt with have anything significant to say about the 68008 MPU at the heart of the QL. For electronics buffs, the presence of a 68008 (a 68000-series device with an 8-bit rather than a 16-bit data bus) is the most interesting fact about the QL. Next month, I hope to look at some books dealing specifically with machine code programming and assembly for the QL and, by extension, for 68000-family devices as a whole.

Leigh Chappell

## CROSSWORD

No. 2 Solution next month

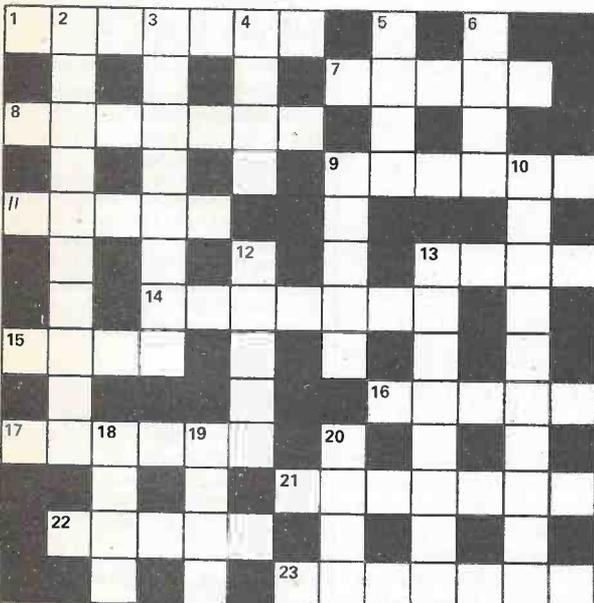

### ACROSS

- 1) ..... trigger, a circuit with hysteresis (7).
- 7) The smallest dot a micro can define on its monitor (5).
- 8) Another term for a monostable (3, 4)
- 9) Transducer found on an electric guitar or record player, for example (4, 2).
- 11) Bidirectional silicon controlled switch (5).
- 13) BASIC command, followed by a sequence of numbers or strings (4).
- 14) Something metals do in adverse conditions (7).
- 15) Type of aerial, based on a sphere with a focussed detector (4).
- 16) The opposite of cut (5).
- 17) ..... ratio, the ratio of the height of a display to its width (6).
- 21) Moving from channel to channel in a stereo image (7).
- 22) A soldered connection (5).
- 23) This is essential for radio transmission, according to the Department of Trade and Industry! (7).

### DOWN

- 2) The industry standard parallel printer connection (10).
- 3) Difference in impedance between an input and an output, leading to signal losses. (8).
- 4) Hand-held or other utensil such as a screwdriver, soldering iron, spanner, etc. (4).
- 5) Better quality audio equipment (2, 2)
- 6) BASIC command (4).
- 9) IBM's disc operating system (T, 1, 1, 1, 1).
- 10) Above the upper frequency limit of human hearing (10).
- 12) Movement away from a desired operating point, usually associated with temperature changes (5).
- 13) To remove contact oscillations from a switched line (8).
- 18) Non-reuseable, non-volatile memory (1, 1, 1, 1).
- 19) Central part of a loud-speaker on which the coil is mounted (4).
- 20) The most popular type of television aerial, comprising a half-wave dipole with parasitic directors in front and behind (4).

### Solution to Crossword No. 1.

#### Across:

- 1) ELSE
- 3) Transmit
- 8) Eject
- 10) Monitor
- 11) TDK
- 12) Integer

- 15) EPROMs
- 16) Decade
- 19) Sprites
- 20) DFM
- 22) Dropper
- 24) Drain
- 25) Electron
- 26) Bell

#### Down:

- 1) Electret
- 2) Speaker
- 4) Remote
- 5) NPN
- 6) Meter
- 7) Turn

- 9) Trimmer
- 13) Greased
- 14) Terminal
- 17) AND gate
- 18) stereo
- 19) 'Scope
- 21) Edge
- 23) Pot

## SCRATCHPAD

### by Flea-Byte

I suppose, with great regret, that 1986 will become the year of Star Wars. Regret for a number of reasons. The first is in some ways the most profound — and that is a deep disturbance at the way Hollywood fantasies can be and have been co-opted by the real power-brokers in Washington and Moscow.

The public image of the latest American mega-plan to keep the world safe for democracy, apple pie and Mickey Mouse comes straight out of James Bond movies and, of course, the Luke Skywalker saga. Actually, the Star Wars plan is known officially as the Strategic Defense Initiative (SDI), only I can't help but think that when an ageing Hollywood actor masquerading as President of the United States characterises a defence policy as though it was being produced by a special effects department, then things have got out of hand.

The core idea behind SDI is, of course, to use nuclear powered laser and pulse-beam weapons directed from earth-orbit at the missiles and missile installations of hostile foreign powers. That such weapons could just as easily be directed at civil nuclear installations, city centre skyscrapers, factories, schools and hospitals seems to have been overlooked by most commentators. Even fewer people seem to have taken the trouble to ask whether such weapons are feasible or, more importantly, whether the idea of controlling them with super intelligent computer systems via a super-fast and secure communications network is anything more than a script-writer's dream.

Everybody knows the diasters and mistakes that can and do plague quite simple exercises in satellite deployment and space transport. The space shuttle is routinely required to deal with rogue satellites, and the shuttle itself has very nearly come to grief on more than one occasion (most notably in its early days when heat deflecting panels kept falling off because of the glue used to attach them). And yet the advocates of Star Wars are preparing, so they say, to risk millions of lives to the protection of such imperfect technology.



The kind of thinking that suggests these people may be as far out to lunch as their satellites are out in space is best illustrated

by the now-classic tale of the quest for a zero-gravity writing instrument. The problem was that even the most sophisticated capillary action pens don't work in zero-gravity conditions. The ink blots, doesn't run freely or fails to adhere to the writing surface. NASA's best minds were put on to the job of coming up with a new kind of writing implement that would allow astronauts to take notes and jot down readings in space with 100% reliability. It took them months before they came up with the humble pencil.

The fact is that much of the time, the scientists and technologists live in a kind of fantasy world of gleaming machines and simple minds — well-ordered, well-behaved and well-intentioned. That's okay, because occasionally the machines do gleam and the minds are simple and then everything goes according to plan. The problems arise when dirty and complex reality intrudes.

Now, politicians are supposed to inhabit this real world. Politics, someone once said, is the art of the possible. So when politicians slip into improbable fantasies it's time to worry. None of this is to say that Star Wars couldn't work. It may do, but 'may' isn't good enough. The people who claim to protect us from megalomaniac excesses and totalitarian paranoia have slipped, with no apparent effort, into megalomania and paranoia. Surely that's what has happened when a film actor promotes a movie scenario as the policy of his government and heads of other governments across the world actually listen to him. The worst thing, of course, is that many ordinary citizens with no power at all find the Star Wars idea convincing — presumably because they've seen it at the movies or on their TV screens already.

### Kings Of The High Frontier

The Star Wars concept is a direct descendant of a notion called 'The High Frontier', developed in the seventies by a group of right-wing thinkers in the US who, I'm told, still operate today. The High Frontier is, of course, the modern equivalent of the old American frontier — the Wild West. By analogy, life in the High Frontier will be brutal and violent and any latter-day Indians who get in the way had better watch out.

The old frontier, in case you'd forgotten, was merely another way of talking about the expansion and conquests of the original Union — the 13 Eastern states who broke with British rule in

1776. The white settlers of these states moved westwards at the point of a gun, taking land from the American Indians and attempting genocide on the way. (In this attempt they were very nearly successful.) They didn't use lasers, of course, but they did use a revolver known as the Colt Peacemaker.

Perhaps the movie Ronald Reagan thinks he's in is not a science fiction epic at all, but an old-fashioned western.

### Resigned To Their Fate

I was interested to read of the resignation of Richard Ennals from his post as Alvey research manager at Imperial College. The Alvey project — under the auspices of which government funds are being distributed to academic and research institutions — is Britain's response to the Japanese programme to develop a 'fifth-generation computer'.

Ennals' resignation followed Margaret Thatcher's reply to a letter from Imperial College computer scientists asking her not to participate in SDI. Thatcher promptly declared her unswerving commitment to Ronald Reagan and all his works. The price of her commitment was high — a pat on the head, in return for which Britain will hand over to the US the results of all its research in areas related to SDI. Some crafty negotiating here!

Interestingly, the Imperial letter followed a visit to the college by executives from the American conglomerate, United Technologies (they own Mostek), who were interested in getting their mits on computing and AI work from the college for use in their SDI work. Ennals' comment was that the Imperial research 'ain't for sale'.

It would appear, however, that Ennals' feelings and those of his team do not count for much. Not only are we selling-off the family silver (as Lord Stockton put it), but we're selling off the family silicon, too.

Heriot-Watt University has eagerly exchanged its expertise in opto-electronics for what appears to be a mess of potage. Imperial itself, along with Manchester University, is engaged in the biggest single computer development project in Britain, in collaboration with Plessey and ICL and with funding from Alvey. The Flagship project is a three-year research programme aiming at developing a parallel-processing computer based on experimental machines already installed at Imperial and Manchester. Researchers at both institutions have sought a formal

agreement from Plessey and ICL that their work will not be put to military use. No such agreement has been forthcoming, and there is clearly consternation that Flagship is destined for a part in SDI.



So far, Richard Ennals' has been the only resignation stemming from worries over Britain's attitude to SDI. However, feeling against the military use of high tech research is very strong among many academics. Meanwhile, United Technologies — in the shape of their helicopter company, Sikorsky — are set to snap up Westland Helicopters, another piece in the British technological jigsaw. If they do so, it will — ironically — be in the face of determined opposition from former Defence Minister, Michael Heseltine, who now finds himself an uneasy bed-fellow in Richard Ennals, son of a former Labour minister.

It may be that Heseltine knows more about SDI and its impact on British high technology industry than he is saying at the moment. It is certainly the case that Reagan's defence policy is causing havoc among the very nations it is supposed to aid and assist. To paraphrase that national hero, the Duke of Wellington: I don't know if it frightens the Russians, but by God it frightens me!

## PLAYBACK

'CD or not CD, that is the question, whether 'tis nobler in the mind to suffer the slings and arrows of outrageous price-rises ...'. There can be no doubt now that the compact disc is firmly established as the hi-fi audio record format. The market for players trebled last year (1985) to 530 million, and forecasts for this year are at least as high. Thousands of titles are listed on CD, of all types of music.

Virtually noise- and crackle-free and with minimal distortion, the medium has caught on in a big way. So, the writing is on the wall for the familiar vinyl LP. Nimbus is ceasing to manufacture its own label LPs, while it installs a second CD pressing plant at Monmouth to increase its present capacity from six to 15 million discs. Undoubtedly, other LP manufacturers will follow suit before long.

This will be the fourth major format change in the history of the gramophone. First the original cylinders gave way to shellac 78s. Then came the mono LP from which we progressed to the stereo 45/45 grooved disc. And now to CD, the biggest change of them all. The stereo disc served us well for some thirty years, but few will bemoan the passing of scratches,

## OPEN CHANNEL

Historically, the PTTs (postal, telegraph and telephone companies) around the world were set up to ensure that a level of standardisation was maintained. Thus, any letter posted in one country, correctly addressed of course, would find its way to the addressee quickly and efficiently. Any telegraph written would be delivered to the receiver promptly. Any telephone call would be instantly received. The PTTs of each country were given a monopolising control of postal, telegraph and telephone services in the land to make sure they had the power to enforce standardisation. The GPO was the British PTT, with complete control over the services.

Knowledgeable authorities were set up, comprising representatives from member nations, designed to specify standards which the PTTs were advised to follow. So far as telecommunications is concerned, the CCITT (International Telegraph and Telephone Consultative Committee) was, and still is, the main standards approving and advising authority. In effect, however, as the PTTs were gener-

ally the only provider of the services in any one country (such is the power of a monopoly), what they wanted was most often granted or implemented without approval anyway.

With such large, cumbersome organisations as the PTTs, time was of little concern. They had more-or-less the sole right to supply and take away services to or from the user (that is, thee and me) and it was not uncommon to have to wait for months on end to have a telephone line installed after application. New grades of service and new standards usually took years to be implemented, if at all. After all, that's what a monopoly is for, isn't it?

In the days of yore, this was of little problem. Few new services or standards appeared, anyway. And if too many telephones were rented to users the whole system would have to be updated, so it's better that users don't have an efficient service, otherwise they'll all want a phone, eh what?

Times change, however! New services are desired by users. Some want data communication facilities; some want facsimile communication; some even want to be able to hold a conversation over the phone without having to shout over the crackles, hisses and pops (heaven forbid!). Eventually even the monopolising

PTTs realise they cannot cope with the increased demands of the user and regulations are altered to de-monopolise them. Hence, the birth of British Telecom. Now customers (note the use of the word customers and not users) can have a phone installed within just a few days, and, what's more, they can buy it too rather than having to rent. New digital services are being provided. Without the monopoly, other organisations may provide parallel services which rival or even better BT's. The PTTs now have to compete to stay in existence. This all sounds too good to be true.

It is. Without monopolies the whole telecommunications area is much improved. Standards are, without doubt, advised and instated more rapidly now than ever before. But new European services still take a long time to appear because the regulations governing them are still based around the PTT's monopolising stranglehold. It has been said that new European service providers face a regulatory burden 100 times greater than those in America.

The problem is that each European country has its own set of regulations which must be adhered to if services are to be sold in that country. Not only that, there are often a number of

bodies in each country (interested in such things as electrical safety and electromagnetic interference) which proffer their own sets of regulations. A service provider wishing to introduce, say, a new modem, must have it approved by the safety regulatory body, the telephone regulatory body, the electromagnetic regulatory body, etc, etc. In many cases the standards of each country's regulatory organisations are different, so the whole procedure must be gone through again, at each new country where the service is to be provided.

This situation must be changed. Yes, regulations must still be there, but they must be reduced to the minimum needed to protect the customer and the services, and they must be unified so that approval covers all countries. Preferably, one regulatory body in each country should maintain *all* regulations, be they of safety, interference, telephone standards, or other categories. Then the prospective provider of a new service would just need to apply to the regulatory body to have the service approved. Once approved the service may be marketed worldwide.

After all, this is surely the whole purpose of having worldwide standards — without this capability there is no point in having standards at all.

Keith Brindley

surface static, warps, chipped styli, arm balancing and all the other irritations that have accompanied it.

The compact disc is not confined to audio. Laser video discs are well-established and are being developed in some haste as the latest mass-storage medium for computing. Recently, two huge industrial giants, Philips and Du Pont, have gone into partnership in a new venture called Philips Du Pont Optical (PDO) to produce and market CD ROM discs for storing computer information. Philips, of course, introduced the laser video disc and (lest it be forgotten) the compact cassette.

### Pressing On

In manufacturing terms, CD ROMs and audio CDs are identical (like computer cassettes and music cassettes), only the software is different. PDO plans to set up a disc pressing plant sometime this year in North Carolina with a capacity of 50 million discs a year. The associated PolyGram factory in Europe is scheduled to increase production from 25 million to 50 million, and the field is wide open for growth.

One of the problems of disc manufacture is the time taken to apply the reflective aluminium coating to the plastic base. It must be done in a high vacuum. At present a small batch of discs are treated at a time in a vacuum

chamber which takes 40 minutes to completely evacuate. PolyGram have developed a technique whereby each disc is treated in its own tiny cell, the vacuum taking only four minutes to achieve. This will greatly accelerate disc production.

Nearer home, Thorn EMI is due to start pressing discs in Britain during March, the planned output being ten million discs a year. Another firm, Distec also has plans to start a plant this year.

The disc shortage caused by the world-wide boom is therefore likely to be soon turned into a surplus. But here's the rub, to

quote the bard once again. Disc player prices have been tumbling in spite of the complexity and minimal production savings of mass production. They have fallen by 50% in the space of two years. On the other hand, disc prices — which should have dived as a result of mass production — have climbed steeply, by up to 25% in some cases. Why? Steve Dowdie, Sony's hi-fi products manager, says, 'CD is already more profitable than LPs and cassettes.' So the manufacturers must be taking advantage of the boom to make quick profits. Existing owners are unlikely to abandon

the format because of escalating disc prices, so they are sitting ducks for the big rip off.

Take heart though. Think of all that over-production looming over the horizon. CD will continue to be upmarket for some time to come as player costs can't dip much more. We are unlikely to see a repeat of the 45-single, portable record player boom with CD — although a few over-priced CD portables have hit the streets. So, when those millions of excess discs hit the market, the tables will turn — and they won't be just those of the CD players!

Vivian Capel

## ALF'S PUZZLE

Alf is inclined to get so carried away with his projects that he often works late into the night, long after the rest of us have gone home. Although we admire his dedication, there are times when the mistakes he makes by working on circuits when he is tired cause enough problems to keep him working late for the next fortnight.

One evening last week, we left him hard at work taping a printed circuit board for a small micro-processor board. The board con-

tained an 8-bit micro and 64K of RAM. When we arrived at ETI Towers the next morning, there was the completed PCB master, all finished. Except that when we tested it, there were several mistakes. The address lines from the micro to the RAM section were all back to front so A<sub>15</sub> on the micro joined to A<sub>0</sub> of the RAM address, A<sub>14</sub> joined to A<sub>1</sub>, and so on. The data line connections were mostly correct, but D<sub>3</sub> and D<sub>4</sub> had somehow been swapped over on the way from the micro to the RAM.

We were cursing Alf loudly when Auntie Static walked in. We started to explain the problem to her, but she didn't seem at all

worried. 'There's no need to alter the address lines,' she said. 'It will work as it is.' And without offering any explanation she dashed off to an appointment with her hairspring-dresser. 'Well, if it will work with the address lines back to front, I don't suppose it matters about the data lines either,' said Alf. 'Let's build it and see.'

Now we all know that when Auntie is in working order she is never wrong, but could she have blown a diode? Alf, on the other hand, is almost always wrong since he makes wild guesses about anything he's not sure of. But could luck be with him this time? Did the board work?

ETI

01-437 0699 Ext 291

**Lineage:**

45p per word (minimum 15 words)

**Semi Display:** (minimum 2 cms)

£11.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



Send your requirements to:  
Stuart Taylor  
ASP Ltd.,  
1 Golden Square,  
London W1.

## COMPONENTS

### RS AND FARNELL COMPONENTS

All RS Components/Farnell Components available to order. Please write/phone stating requirements to:

TRIOLOGIC, 29 Holme Lane, Bradford BD4 0QA.  
Tel: 0274-685928.

### CHEAP, CHEAP!

Mail order only.

LS138	50p	4116	£1.20
LS244	75p	4164	£1.10
LS245	85p	41256	£5.50
LS373	85p	2764	£2.40
LS393	95p	27128	£5.50

Add £1 P&P. Send 20p + S.A.E. for price list.  
C. Bank, 9 Jubilee Rd., Porchester, Hants.

**NEW AND SURPLUS** components in stock. Spectrum Radio & Electronics Ltd, 36 Slater St, Liverpool L1 4BX. Tel. 051-709 4628.

**AIRLINK TRANSFORMERS** manufacturer of Torodial and standard transformers. Phone Mike Dornan, Newmarket 0638 662989 for details.

Humpty Dumpty sat on the wall. Humpty Dumpty had a great fall when he saw **MICROKIT'S** component prices. See their display advertisement **NOW** in this copy.

Humpty Dumpty sat on the wall. Humpty Dumpty had a great fall when he saw **MICROKIT'S** component prices. See their display advertisement **NOW** in this copy.

## WANTED

**TURN YOUR SURPLUS** transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

## PLANS 'N DESIGNS

**AMAZING ELECTRONIC** plans, lasers, gas, ruby, light shows, high voltage tester, van de graph surveillance devices ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Old String Works, Bye Street, Ledbury HR8 2AA.

## KITS

### J. Linsley Hood Designs

	£25.00	£1.00	P.P.
Distortion Analyser Kit.	£25.00	£1.00	
Millivoltmeter Kit.	£12.25	£0.75	
Case and Panel for above	£12.00	£1.00	
ETI Mosfet P.A. Kit.	£51.00	£1.50	
Audio Signal Gen. (.02%) Kit.	£28.50	£1.50	
Audio Signal Gen. (.002%) Made	£46.00	£2.00	
Fixed Freq. Sig/Gen. (.002%)	£14.00	£0.50	
Case and Panel for above	£9.50	£0.75	
Reg. P.S.U. 1.5/35 volts from	£12.80	£0.00	

S.A.E. for full information.  
TELERADIO ELECTRONICS  
325, Fore Street, London N9 0PE. Tel: 807 3719

**FM TRANSMITTERS.** Same day despatch. **MINIATURE MODEL** frequency 60-145 Mhz; range 1 mile. Glass fibre P.C.B. All components. Full instructions 9-12V operation, broadcast reception. Super sensitive microphone. Pick up on FM/VHS radio. £6.95 inc or ready built £8.95. Size 57 x 19 x 12mm. **HIGH POWER MODEL.** 3 watts 80-108 MHz. Professional broadcast performance. Low drift varicap controlled. Range up to 7 miles. 12V operation. Any input audio/microphone. All components P.C.B. diagrams and instructions. Size 103 x 30 x 29mm. Kit £13.99 inc or ready built: £18.99. **tone generator:** 3-selectable functions, PIP, Warble and pulse tone: All components, instructions & P.C.B.; feed into any audio input or transmitter; variable frequency and gating controls. 6-12V operation 53 x 38 x 14mm. £5.50 incl. **tone generator power amplifier.** All components, instructions and P.C.B. Turns tone generator into a high power siren for alarms: 18 watts max. At 12-57V. 62 x 38 x 14mm £7.00 inclusive. **ZENITH ELECTRONICS.** 21 Station Road Industrial Estate, Hailsham, E. Sussex BN27 2EW.

**ELECTRONIC ORGAN KEYBOARDS** and other parts being cleared out. Special Offer: Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8.

**ETI KITS** assembled and tested\* by electronic trainees under supervision within a purpose built electronic workshop for as little as £10\* (\* depending on type of kit and complexity). Contact:- A.J. Smith, Dept K.A. Electronics Workshop, Lincoln I.T.E.C. Dean Road, Lincoln LN2 4JZ. Tel. 0522 43532.

## FOR SALE

### NICADS

**AA/HP7 Rechargeable Cells**  
4 for £2.30 or 10 for only £5!  
(ex. equip. tested & quaranteed)  
**Universal Nicad Charger £8**  
with battery test facility and LED indicators for any combination PP3, AA, C&D cells  
Above prices inclusive of p&p — goods sent by return  
**Croydon Discount Electronics (E)**  
40 Lower Addiscombe Rd.  
Croydon CRO 6AA

**100W AMPLIFIER** — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms, etc., by using alternative output transistors and P.S.U. S.A.E. for full details to:- ESS Amplification, 269 Hessele Road, Hull.

**CORTEX** £140 ono RS232 E-Bus. Switchable Forth/Basic. All IC Bases. Perfect order. Deliver reasonable distance. 036 283 8110. (Norfolk).

**EVERYDAY ELECTRONICS,** Hobby, TV, electronics and radio magazines for sale. Very cheap. Ring after 7pm for details 01 853 0946.

**100 WATT FET' POWERAMPS** £10. Automatic relay protection — mirror input & delayed switch-on. Glass/PCB built. KIA, 8 Cunliffe Rd, Ilkley. Free slider/V.C.

**CORTEX BUILT** working £170 all chips for disc, RS232, E BUS except 74L 52001. Tel: 0935 72413 after 6pm.

**TEKTRONIC OSCILLOSCOPES.** 556 dual beam four trace 50MHz delay sweep £375. 546 dual trace 50MHz delay sweep £175. 551 dual beam eight trace 19MHz £165. 581A dual trace 85MHz £155. 545B dual trace 24MHz delay sweep £135. Storage oscilloscopes, semiconductor curve tracers, manuals, plug-ins, spares. Tel. (01) 868 4221.

## SERVICES

### JBA ELECTRONICS

Specialists in manufacture and design of:  
Microprocessor, Telemetry, and Audio-based systems.

UNIT 9,  
**BRECON INDUSTRIAL ESTATE,**  
BRECON, POWYS, S. WALES  
Tel: (0874) 2563

**FREE PROTOTYPE** of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited, Finsbury House, 31 Head St, Halstead, Essex CO9 2BX.

**TECHNICAL AUTHORS,** illustrators M.O.D. IC designers Software — Fortran Pascal, CNC (APT), European Languages (0903) 501 763.

## REPAIRS

**ZX SPECTRUM.** VIC20, C64, BBC, QL 15 40/41 Commodore computers, prints and floppy discs. Send faulty machine to: Trident Enterprises Ltd., Unit 7, Wentworth Industrial Court, Goodwin Road, Britwell, Slough. Tel: 0753 21391.

## TEST EQUIP.


**TOP PRICES PAID** for surplus electronic test equipment. Always a good selection of **BIG-GEN METERS** and **SCORES** for sale. Phone (0438) 353828.

## COMPUTER ADD-ONS

6809 CPU, 14, 32, & 128K RAM/EPROM cards. Disk/Real-time Clock, VIA & bleeper card, Flex O/S. All chips, cases, P/supplies, K/boards, etc from stock, build your own 6809 Flex system from scratch. See for details.  
**RALPH ALLEN ENGINEERING**  
Forncett End, Norwich NR16 1HT  
Tel: 095 389420

**ALARMS**

# ALARMS

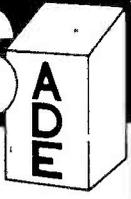

**FREE BOOKLET**  
on  
**BURGLAR ALARMS**  
with

**LOWEST U.K. DIY PUBLISHED PRICES**  
PHONE OR WRITE FOR YOUR COPY  
**051-523 8440**  
**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU

## SECURITY Alarm Systems

- FREE COMPREHENSIVE CATALOGUE!
- **LOWEST DISCOUNT PRICES**
  - **HIGHEST QUALITY EQUIPMENT**
  - **FREE DIY DESIGN GUIDE**
  - **FULLY ILLUSTRATED**
  - **MICROCHIP CIRCUITRY**
  - **QUICK DESPATCH SERVICE**
  - **FULL INSTRUCTIONS**
- SEND SAE OR PHONE  
CTEC SECURITY, Dept E1,  
Stephens Way, Goose Green,  
Wigan WN3 6PH  
Telephone (0942 42444)
- Trade Enquiries Welcome

**LOWEST PRICED TOP QUALITY** fire and intruder alarm equipment, etc. SAE for catalogue Security Services, 62 High St, Hythe, Kent CT21 5JR.

## COILS & CHOKES.

### MAXI-Q

COILS AND CHOKES  
PREVIOUSLY MADE BY DENCO  
S.A.E. PRICE LIST  
**8 BRUNEL UNITS, BRUNEL RD,  
GORSE LANE IND. ESTATE,  
CLACTON, ESSEX CO15 4LU.  
TEL: (0255) 424152**

## MISC.

**HEATHKIT U.K.** Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

## SOFTWARE.

**EX42 AND CP/M?** Simulate EPSON MX80 Operation. Also for other Printers/Systems. All Source/Manuals on Disk/Cassette. SAE to NCS Highhall Farm Nettlestead Suffolk IP8 4QT.

**SPECIAL OFFERS**

**CLEARANCE BARGAIN!! THOUSANDS** of components in stock. Led 7 Segment Display, Brand new 14 Pin Dill Red .43 inch, common anode display 049 with right and left decimal point. 9 pieces £1.50 (30p each), 10 pieces £2.50 (25p each); 50 pieces £10.00 (20p each); 100 pieces £15.00 (15p each); 1000 pieces £100.00 (10p each). TELEPHONE YOUR ORDER TO 0296 613816.

**FREE MEMBERSHIP** to a new national electronics club. For details and a free gift of components worth over £10 send only £1 p&p to **Woodside, Dowsett Lane, Ramsden Heath, Essex CM11 1JL.**

**BBC MICRO** analogue port plugs. 5 for only £3.75 10 for £7.00. P/P 30p x 15% VAT. Capital Delta, 8 Dunlin Close, Poynton, Cheshire.

## SWITCHES

**VOICE/SOUND ACTIVATED SWITCHES.** Easy to follow diagrams and uses only £1. Components and P.C.B.s available from **HERRINGTON, 63, Homefarm Road, Hanwell, London W7 1NL.** Tel: 01-578 6627.

**EQUIPMENT**

### Flanger/Chorus parts re E.T.I. Jan 84

Reverb Springs, Pedal Cases, Dummy Keyboards, Microphones, Audio leads and adaptors, clearance bass effects pedal and many more items.  
Send S.A.E. for free price list to:-  
**SOLAR SOUND LTD**  
18 Berton Way  
Croxtley Green  
Rickmansworth  
Herts WD3 3QA

**PRINTED CIRCUIT BOARDS** one-offs and small quantities supplied. Artwork carried out. Fennell Industrial Electronics, 54 Watling Street, Nuneaton, Warks CV11 6JL. Tel: 0203 382296.

**POWER SUPPLIES**

### NEW ADJUSTABLE 1 AMP DC PSU

3 to 9V or 9 to 15V current limited, battery circuit, high quality, built and tested, £14.50. Remote switching option £1.50, case £2.50. Please add 15% VAT.

**RYD DESIGN LTD**  
Railway Station  
Rye. E. Sussex TN31 7AB

**150W SWITCHMODE PSU.** +5V 8.4A; +12V 4.8A; +24V 1.7A; +12V 0.2A. Perfect working order, over £70 in Henries Radio £29 + Carr. 0245-59027 after 6.00pm.

**SCOPES**

### MENDASCOPE LTD.

REPAIR & RECALIBRATE  
OSCILLOSCOPES.  
ALL MAKES ALL MODELS.  
NATIONWIDE COLLECTION &  
DELIVERY  
**FREE ESTIMATES**  
Phone 069-172-597

**BOOKS & PUBS.**



**We use only 10% of our mental potentials**

Einstein  
These are the words of Albert Einstein, the greatest physicist of recent times.  
L. Ron Hubbard's discoveries in the field of the mind prove today that Einstein was right.  
In his book "DIANETICS: The Modern Science of Mental Health" L. Ron Hubbard takes one more giant step in this direction.  
He reveals how anyone can use his discoveries to isolate the exact barriers that have so far prevented people from using their mental potentials to the full.  
More and more people from all walks of life including technicians, artists, GPs, scientists, workers and managers alike use Dianetics technology today.  
The many written reports on their success are the best proof of the quality of this book.  
Find out for yourself. Order your copy of this remarkable book today.  
Price £3.95 paperback £17.50 hardback. Make cheques and POs payable to S.H.F. Send to Church of Scientology Saint Hill Foundation, FREEPOST (ETI 1) East Grinstead, Sussex RH19 4ZA (no stamp required).

**PARAPHYSICS JOURNAL** (Russian translation); psychotronics, kirlianography, heliphonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

## STATIC RAMS

**6116** (150 NS) industry standard. 16K static memory. New at only £1.80. Tel. 01 281 0633.

**KENT**

### ONE STOP ELECTRONICS

126a Maidstone Rd., Rochester ME1 3DT  
Tel: 0634 400179  
Open 7 days a week.  
Test equipment, telephones, two-way radios, repairs, cellular radio and components.  
Call and browse anytime except Wednesday afternoon.

**LANCASHIRE**

### ETESON ELECTRONICS

15B Lower Green,  
Poulton-le-Fylde, Blackpool  
Tel: (0253) 886107  
Open: 9.30am-12.30 1.30-5.30. Closed Wed & Sun.  
Electronic Component Specialists.

**LIVERPOOL**

### PROGRESSIVE RADIO

87/93 Dale Street. Tel 051 236 0154  
47 Whitechapel. Tel 051 236 5489  
Liverpool 2  
**'THE ELECTRONICS SPECIALISTS'**  
Open: Tues-Sat 9.30-5.30

**SCOTLAND**

### VISIT SCOTLAND'S NEWEST COMPONENT SHOP OMNI ELECTRONICS

174 Dalkieth Rd  
Edinburgh EH16 5DX  
Tel: 031 667 2611  
Send S.A.E. for catalogue.  
Open Mon-Sat 9am-6pm


E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T

E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T





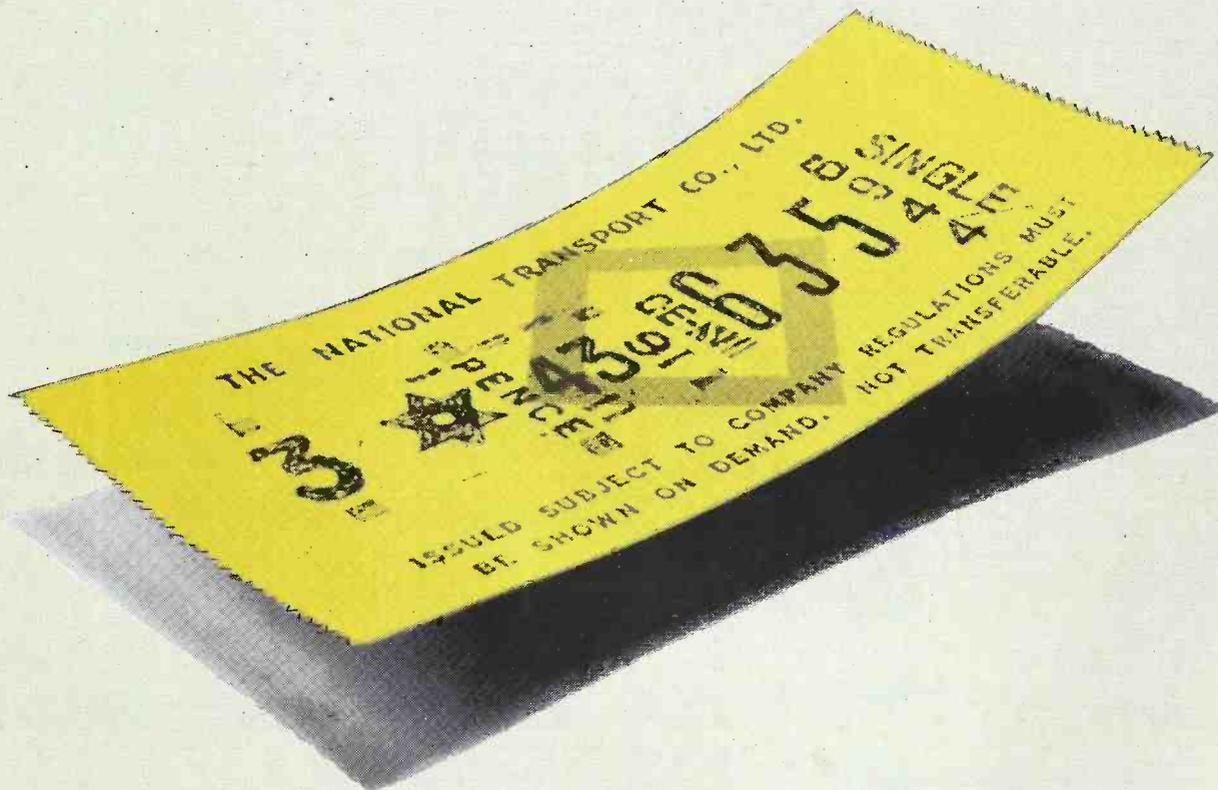**Lowest possible prices?  
Top quality components?  
Fast reliable service?  
Large range?**



**Maplin** ..... Just the ticket.

Pick up a copy of our new 1986 catalogue from any branch of W.H. Smith for just £1.45.

Or post this coupon now, to receive your copy by post for just £1.45 + 40p p & p. If you live outside the U.K. send £2.50 or 11 International Reply Coupons. I enclose £1.85.


Name .....

Address .....

.....

.....

ETI

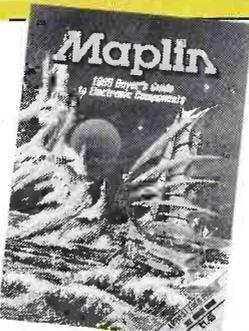

**MAPLIN ELECTRONIC SUPPLIES LTD.**

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 552911

**SHOPS**

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
- LONDON 159-161 King Street, Hammersmith, W6.  
Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 225831.
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex.  
Telephone: 0702-554000

*Shops closed all day Monday.*