

AN ARGUS SPECIALIST PUBLICATION


electronics today

INTERNATIONAL

MAY 1986

£1.20

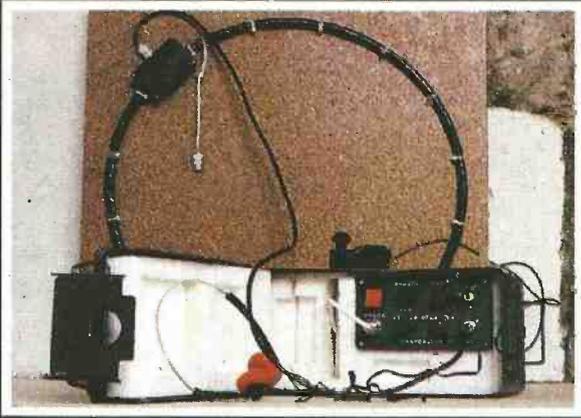COMMUNICATIONS... COMMUNICATIONS... COMMUNICATIONS...



THE TROGLOGRAPH

Talking through rock
with very low frequencies

EXPAND YOUR MODEM
WITH OUR
BAUD RATE
CONVERTER

HELMET INTERCOM

LEARN ABOUT LASERS

80 M DIRECT CONVERSION RECEIVER

Do-It-Yourself Automatic Testing


AUDIO... COMPUTING... MUSIC... RADIO... ROBOTICS...

OMP POWER AMPLIFIER MODULES

★ PRICES INCLUDE V.A.T. ★ PROMPT DELIVERIES ★ FRIENDLY SERVICE ★ LARGE S.A.E. 28p STAMP FOR CURRENT LIST

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**

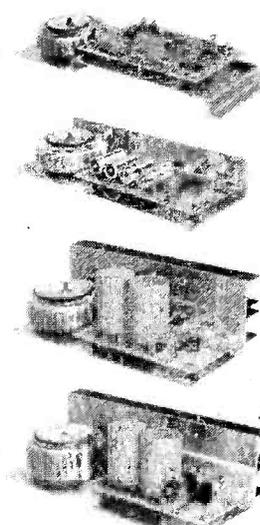


OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115 x 65mm. **PRICE £33.99 + £3.00 P&P.**

OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**

OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. **PRICE £62.99 + £3.50 P&P.**

OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. **PRICE £79.99 + £4.50 P&P.**

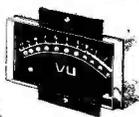NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 - 50p P&P.**

LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of **McKenzie Loudspeakers** available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco.
20 oz. magnet. 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99. Available with black grille £11.99. P&P £1.50 ea.
12" 100 WATT R.M.S. Hi-Fi/Disco.
50 oz. magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 - £3.00 P&P ea.

McKENZIE

12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.
2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £28.76 - £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £29.80 - £3.00 P&P ea.
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £54.99 - £4.00 P&P ea.
10" 60 WATT R.M.S. C1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.15 - £2.00 P&P.
10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.
2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £51.00 - £3.00 P&P.
15" 200 WATT R.M.S. C15200 High Power Bass.
Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £59.45 - £4.00 P&P.
15" 400 WATT R.M.S. C15400 High Power Bass.
Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £85.00 - £4.00 P&P.

WEM

5" 70 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £19.99 - £1.50 P&P ea.
8" 150 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £29.49 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £33.49 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £41.49 - £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)

5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 - £1.00 P&P ea.
6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 - £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 - £1.50 P&P ea.
10" 60 WATT R.M.S. Hi-Fi/Disco etc.
1 1/4" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) **Price: £8.62 + 75p P&P.**
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) **Price: £14.49 + 75p P&P.**
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). **Price: £17.82** Transmitter 80 x 50 x 15mm (9/12 volt). **Price: £11.29** P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

BURGLAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed 30 second exit and entry delay.
Indoor alarm - Electronic swept freq. siren. 104dB output.

Outdoor Alarm - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85

BKE's PRICE £89.99 + £4.00 P&P

? Why buy a collection of self-assembly boards?

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12" Watts R.M.S. per cabinet. Sensitivity 1W 1mtr dB

OMP 12-100 Watts 100dB. Price £149.99

per pair.

OMP 12-200 Watts 102dB. Price £199.99

per pair. Delivery. Securicor £8.00 per pair



OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. **Three models** (Ratings R.M.S. into 4ohms), Input Sensitivity 775mV

MF200 (100 + 100)W. £169.00

MF400 (200 + 200)W. £228.85

MF600 (300 + 300)W. £274.85

Securicor Delivery £10.00

1 K-WATT SLIDE DIMMER


- ★ Control loads up to 1Kw
- ★ Compact Size 4 1/2" x 1" x 2 1/2"
- ★ Easy snap in fixing through panel cabinet cut out
- ★ Insulated plastic case
- ★ Full wave control using 8 amp triac
- ★ Conforms to BS800

★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.

PRICE £13.99 - 75p P&P

BSR P295 ELECTRONIC TURNTABLE

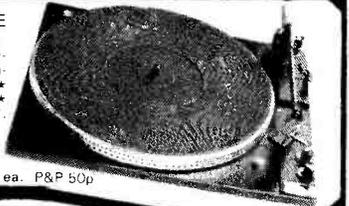
★ Electronic speed control 45 & 33 1/3 r.p.m. ★ Plus Minus variable pitch control ★ Belt driven ★ Aluminium platter with strobed rim ★ Cue lever ★ Anti-skate (bias device) ★ Adjustable counter balance ★ Manual arm ★ Standard 1" cartridge fixings ★ Supplied complete with cut out template ★ D.C. Operation 9-14V D.C. 65mA **Price £36.99 - £3.00 P&P.**



ADC Q4 mag. cartridge for above. **Price £4.99 ea. P&P 50p**

PIEZO ELECTRIC TWEETERS MOTOROLA

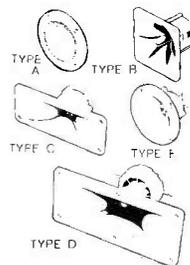Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. **Price £4.90 each - 40p P&P**

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £5.99 each - 40p P&P**

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. **Price £6.99 each - 40p P&P**


TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. **Price £9.99 each - 40p P&P**

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. **Price £5.99 each - 40p P&P**

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. **85 x 85 mm Price £3.99 + 40p P&P**

STEREO DISCO MIXER

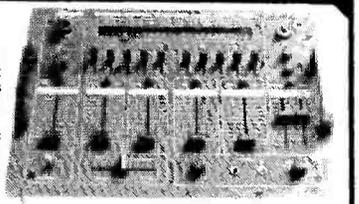STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following: 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor, Pan Pot, L & R Master Output controls. Output 775mV. Size 360 x 280 x 90mm. **Price £134.99 - £3.00 P&P**



B. K. ELECTRONICS DEPT ETI
UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
ESSEX, SS2 6TR TEL: 0702-527572




POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.



electronics today

INTERNATIONAL MAY 1986 VOL 15 NO 5

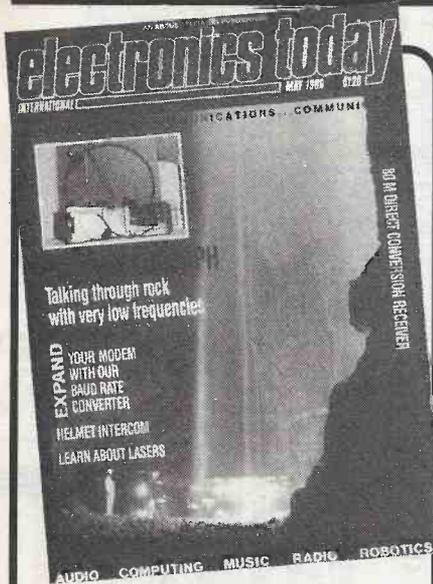

Gary Herman: Editor
Ian Pitt: Deputy Editor
Paul Chappell: Project Editor
Jerry Fowler: Technical Illustrator
Paul Stanyer: Ad. Manager
Stuart Taylor:
 Classified Sales Executive
Pam Smithson: Copy Control
Dave Bradshaw: Group Editor
 - Electronics
Peter Welham: Managing Director

PUBLISHED BY:
 Argus Specialist Publications Ltd.,
 1 Golden Square, London W1R 3AB.
DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd.,
 12-18 Paul Street, London EC2A 4JS
 (British Isles)

PRINTED BY:
 The Garden City Press Ltd.
COVERS DESIGNED BY:
 Argus Press Design.
COVERS PRINTED BY:
 Alabaster Passmore.



Member of the
 Audit Bureau
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1986 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK: £18.10. Overseas: £22.50. USA: \$29.50. Airmail: £49.50.

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
 Telex 8811896.

FEATURES

- DIGEST** 7
 The news chronicled.
- READ/WRITE** 18
 Letters leaves.
- FIBRE OPTICS AND LASERS**.... 21
 Electronic engineers are lighting-up. Roger Bond explains how and why.
- THE ETI TROGLOGRAPH** 24
 Deep in an English cave, Mike Bedford has been soak-testing his latest project — a VLF transmitter-receiver. Here, he explains why cavers, in particular, welcome very low frequencies.
- AUTOMATIC TESTING ON A HOME MICRO** 48
 This circuit solution by Alan Paton explains the hardware and software needed to test logic chips on almost any home micro.
- TECH TIPS**..... 56
 Ideas logically sound.

PROJECTS

- MICROLIGHT INTERCOM** 28
 Ian Coughlan gets into conversation in a noisy environment.
- BAUD RATE CONVERTER**..... 33
 Give your modem a new lease of life, expand your communications end-work and make your bits go faster or slower, courtesy of Ola Borrebaek.
- 80M DIRECT CONVERSION RECEIVER**..... 40
 S. Niewiadomski says that 80 metres is a good introduction to short-wave for the beginner and has designed a receiver to prove it.
- PORTABLE PA**..... 43
 John Linsley Hood's design for the power amp section of his portable, battery-operated PA.

ETCETERA

- REVIEWS** 61
 A Q'lection of books on the QL hardware.
- OPEN CHANNEL** 62
 More on long-distance communications.
- TRAINS OF THOUGHT** 62
 Roger Amos re-trains.
- PLAYBACK** 63
 What noise annoys Vivian Capel?
- ALF'S PUZZLE** 63
- CROSSWORD** 66

INFORMATION

- COUPONS**..... 14
NEXT MONTH'S ETI 55
PCB FOIL PATTERNS..... 58
READERS' SERVICES 60
AD INDEX 62
CLASSIFIED ADS 64

Due to continued illness, we very much regret that the promised part of the Digital Sound Sampler has had to be held over for yet another month. Our apologies to all readers interested in pursuing this project. We assure you that we will bring you the conclusion of this project as soon as possible.

WATFORD ELECTRONICS

250 High Street, WATFORD, WD1 2AN, HERTS.

MAIL ORDER & RETAIL SHOP

Tel: (0923) 37774 Tlx. 8956095 WATFRD

ALL DEVICES BRAND NEW & FULLY GUARANTEED. SEND CHEQUES, P.O.s & BANK DRAFT OR ACCESS/MASTER CHARGE & VISA CARD NUMBER WITH ORDER. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS' OFFICIAL ORDERS ACCEPTED. P&P ADD £1 TO ALL CASH ORDERS. OVERSEAS ORDERS, POSTAGE CHARGED AT COST AIR/SURFACE. PRICES SUBJECT TO CHANGE WITHOUT NOTICE AND AVAILABLE ON REQUEST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

ELECTROLYTIC CAPACITORS: (Values in uF) 500v, 10uF 52; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7 8p 10 10p; 15, 22 12p; 33 15p; 47 12p; 68 20p; 100 19p; 220 22p; 1000 70p; 2200 99p; 50V: 68 20p; 100 17p; 220 24p; 40V: 22 9p; 33 12p; 330, 470 32p; 1000 49p; 2200 90p; 25V: 1.5, 4.7, 10, 22, 47 6p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 1500 42p; 2200 50p; 3300 70p; 4700 92p; 16V: 47, 68, 100 9p; 125 12p; 330 16p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 28p; 4700 72p.

TAG-END CAPACITORS: 63V: 2200 120p; 3300 145p; 4700 245p; 50V: 2200 95p; 3300 155p; 40V: 4700 180p; 25V: 2200 70p; 3300 85p; 4000 170p; 1000 250p; 1500 270p; 16V: 2200 200p.

POLYESTER CAPACITORS: Axial Lead Type
400V: 1nF, 1.5n, 2n, 3n, 4n, 7n, 10n, 15n, 18n, 22n, 33n, 47n, 68n, 150n, 220n, 330n, 470n, 680n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 10000n, 15000n, 22000n, 33000n, 47000n, 68000n, 100000n, 150000n, 220000n, 330000n, 470000n, 680000n, 1000000n, 1500000n, 2200000n, 3300000n, 4700000n, 6800000n, 10000000n, 15000000n, 22000000n, 33000000n, 47000000n, 68000000n, 100000000n, 150000000n, 220000000n, 330000000n, 470000000n, 680000000n, 1000000000n, 1500000000n, 2200000000n, 3300000000n, 4700000000n, 6800000000n, 10000000000n, 15000000000n, 22000000000n, 33000000000n, 47000000000n, 68000000000n, 100000000000n, 150000000000n, 220000000000n, 330000000000n, 470000000000n, 680000000000n, 1000000000000n, 1500000000000n, 2200000000000n, 3300000000000n, 4700000000000n, 6800000000000n, 10000000000000n, 15000000000000n, 22000000000000n, 33000000000000n, 47000000000000n, 68000000000000n, 100000000000000n, 150000000000000n, 220000000000000n, 330000000000000n, 470000000000000n, 680000000000000n, 1000000000000000n, 1500000000000000n, 2200000000000000n, 3300000000000000n, 4700000000000000n, 6800000000000000n, 10000000000000000n, 15000000000000000n, 22000000000000000n, 33000000000000000n, 47000000000000000n, 68000000000000000n, 100000000000000000n, 150000000000000000n, 220000000000000000n, 330000000000000000n, 470000000000000000n, 680000000000000000n, 1000000000000000000n, 1500000000000000000n, 2200000000000000000n, 3300000000000000000n, 4700000000000000000n, 6800000000000000000n, 10000000000000000000n, 15000000000000000000n, 22000000000000000000n, 33000000000000000000n, 47000000000000000000n, 68000000000000000000n, 100000000000000000000n, 150000000000000000000n, 220000000000000000000n, 330000000000000000000n, 470000000000000000000n, 680000000000000000000n, 1000000000000000000000n, 1500000000000000000000n, 2200000000000000000000n, 3300000000000000000000n, 4700000000000000000000n, 6800000000000000000000n, 10000000000000000000000n, 15000000000000000000000n, 22000000000000000000000n, 33000000000000000000000n, 47000000000000000000000n, 68000000000000000000000n, 100000000000000000000000n, 150000000000000000000000n, 220000000000000000000000n, 330000000000000000000000n, 470000000000000000000000n, 680000000000000000000000n, 1000000000000000000000000n, 1500000000000000000000000n, 2200000000000000000000000n, 3300000000000000000000000n, 4700000000000000000000000n, 6800000000000000000000000n, 10000000000000000000000000n, 15000000000000000000000000n, 22000000000000000000000000n, 33000000000000000000000000n, 47000000000000000000000000n, 68000000000000000000000000n, 100000000000000000000000000n, 150000000000000000000000000n, 220000000000000000000000000n, 330000000000000000000000000n, 470000000000000000000000000n, 680000000000000000000000000n, 1000000000000000000000000000n, 1500000000000000000000000000n, 2200000000000000000000000000n, 3300000000000000000000000000n, 4700000000000000000000000000n, 6800000000000000000000000000n, 10000000000000000000000000000n, 15000000000000000000000000000n, 22000000000000000000000000000n, 33000000000000000000000000000n, 47000000000000000000000000000n, 68000000000000000000000000000n, 100000000000000000000000000000n, 150000000000000000000000000000n, 220000000000000000000000000000n, 330000000000000000000000000000n, 470000000000000000000000000000n, 680000000000000000000000000000n, 1000000000000000000000000000000n, 1500000000000000000000000000000n, 2200000000000000000000000000000n, 3300000000000000000000000000000n, 4700000000000000000000000000000n, 6800000000000000000000000000000n, 10000000000000000000000000000000n, 15000000000000000000000000000000n, 22000000000000000000000000000000n, 33000000000000000000000000000000n, 47000000000000000000000000000000n, 68000000000000000000000000000000n, 100000000000000000000000000000000n, 150000000000000000000000000000000n, 220000000000000000000000000000000n, 330000000000000000000000000000000n, 470000000000000000000000000000000n, 680000000000000000000000000000000n, 1000000000000000000000000000000000n, 1500000000000000000000000000000000n, 2200000000000000000000000000000000n, 3300000000000000000000000000000000n, 4700000000000000000000000000000000n, 6800000000000000000000000000000000n, 10000000000000000000000000000000000n, 15000000000000000000000000000000000n, 22000000000000000000000000000000000n, 33000000000000000000000000000000000n, 47000000000000000000000000000000000n, 68000000000000000000000000000000000n, 100000000000000000000000000000000000n, 150000000000000000000000000000000000n, 220000000000000000000000000000000000n, 330000000000000000000000000000000000n, 470000000000000000000000000000000000n, 680000000000000000000000000000000000n, 1000000000000000000000000000000000000n, 1500000000000000000000000000000000000n, 2200000000000000000000000000000000000n, 3300000000000000000000000000000000000n, 4700000000000000000000000000000000000n, 6800000000000000000000000000000000000n, 10000000000000000000000000000000000000n, 15000000000000000000000000000000000000n, 22000000000000000000000000000000000000n, 33000000000000000000000000000000000000n, 47000000000000000000000000000000000000n, 68000000000000000000000000000000000000n, 100000000000000000000000000000000000000n, 150000000000000000000000000000000000000n, 220000000000000000000000000000000000000n, 330000000000000000000000000000000000000n, 470000000000000000000000000000000000000n, 680000000000000000000000000000000000000n, 1000000000000000000000000000000000000000n, 1500000000000000000000000000000000000000n, 2200000000000000000000000000000000000000n, 3300000000000000000000000000000000000000n, 4700000000000000000000000000000000000000n, 6800000000000000000000000000000000000000n, 100n, 15000000000000000000000000000000000000000n, 22000000000000000000000000000000000000000n, 33000000000000000000000000000000000000000n, 47000000000000000000000000000000000000000n, 68000000000000000000000000000000000000000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 3300n, 4700n, 6800n, 100n, 15000n, 22000n, 33000n, 47000n, 68000n, 1000n, 1500n, 2200n, 33000

SWITCHES TOGGLE: 2A 250V SPST 35p DPDP 48p SUB-MIN TOGGLE SPST on/off 54p SPDT c/over 86p SPDT Centre off 85p SPDT based both ways 105p DPDT 6 lags 80p DPDT centre off 86p DPDT based both ways 145p DPDT 3 positions on/on/off 185p 4 pole 2 way 220p SLIOE 250V: DPDT 1A 14p DPDT 1A c/off 15p DPDT 1A 13p PUSHBUTTON 6A with 10mm Button SPDT latching 150p DPDT latching 200p DPDT moment 200p Mini Non Locking Push to Make 15p Push to Break 25p DIGITAST Switch Assorted Colours 75p each ULTRASONIC TRANSDUCERS 40 Khz 475p GAS/SMOKE DETECTORS TGS812 or TGS813 £8 each Holders for above 40p TRANSFORMERS 3-0-3V, 6-0-6V, 9-0-9V, 12-0-12V, 15-0-15V @ 100mA PCB mounting, Miniature, Split bobbin 3VA: 2x6V/0.25A, 2x9V/0.15A, 2x12V/0.2A, 2x15V/0.2A 6VA: 2x6V/0.5A, 2x9V/0.3A, 2x12V/0.25A, 2x15V/0.2A Standard Split Bobbin type 6VA: 2x6V/0.5A, 2x9V/0.4A, 2x12V/0.3A, 2x15V/0.25A 12VA: 2x4.5V/1A, 2x5V/1A, 2x9V/0.6A, 2x12V/0.5A, 2x15V/0.4A, 2x20V/0.3A, 3x5p (35p DP) 24VA: 2x6V/1.5A, 2x9V/1.2A, 2x12V/1A, 2x15V/0.8A, 2x20V/0.6A 50VA: 2x6V/4A, 2x9V/2.5A, 2x12V/2A, 2x15V/1.5A, 2x20V/1.2A, 2x25V/1A, 2x30V/0.8A, 520p (520p DP) 50VA: Outputs +5V/5A, +12V, +25V, -5V, -12V at 1A @ 820p (80p DP) 100VA: 2x12V/4A, 2x15V/3A, 2x20V/2.5A, 2x25V/2A, 2x30V/1.5A, 2x50V/1A, 955p (75p DP) P&P charge to be added over and above our normal postal charge	DIP SWITCHES (SPST) 4 way 85p; 6 way 80p; 8 way 85p; 10 way 125p (SPDT) 4 way 190p ROTARY SWITCHES (Adjustable Stop type) 1 pole/2 to 12 way; 2 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way 48p ROTARY: Mains DP 250V 4 Amp on/off 88p Make a multiway switch. Shuffling assembly has adjustable stop. Accommodates up to 5 wafers, max. 6 pole/12 way + DP switch. Mechanism only 90p WAFERS: (make before break) to fit the above switch mechanism: 1 pole/12 way, 2 pole/6 way, 3 pole/4 way, 4 pole/3 way, 5 pole/2 way 45p Mains DP 4A Switch to fit Spacers 4p. Screen 6p. ROCKER SWITCHES ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V SPST 38p ROCKER: 10A/250V DPDT c/off 95p ROCKER: 10A/250V DPST with neon 85p THUMBWHEEL Mini front mounting switches Decade Switch Module 275p B.C.D. Switch Module 275p Mounting Cheeks (per pair) 75p JUMPER LEADS (Ribbon Cable Assembly): Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header, Plug) Jumper 24 inches 145p 185p 240p 380p Double ended DIP (Header, Plug) Jumper 12 inches 198p 215p 315p 480p 24 inches 210p 235p 345p 540p 3ft 290p 370p 480p 525p 3ft Female Header Socket Jumper Leads 36 20pin 26 pin 34 pin 40 pin 180p 200p 240p 280p Double ended 290p 370p 480p 525p	VERO VERO BOARDS 0.1" 2% x 1 30p 2% x 3 1/4 95p 2% x 5 110p 3% x 5 110p 3% x 5 125p 3% x 7 420p 4% x 7 550p V9 Board 385p DIP Board 395p Vero Strip 95p VERO PINS per 100 Single Ended 55p Double ended 60p Wire Wrap S/E. 155p Wire Wrap D/E. 255p VERO TOOLS Spot face cutters 150p Fin insertion tool 85p COPPER CLAD BOARDS Fibreglass Single-Double-sided sided 8" x 12" 175p 225p 6" x 12" 175p 225p DIL SOCKETS Low Wire Turned Pin Prof Wrap Pin 8 8p 20p 18p 16 10p 23p 28p 16 10p 40p 28p 18 16p 40p 33p 20 20p 58p 37p 22 22p 60p 39p 24 25p 68p 42p 28 28p 78p 52p 40 30p 88p 72p ANTEX SOLDERING IRON C-15W 500p CS17W 3p G-18W 620p X255W 650p Spare tips, assorted size Spare elements 100p 245p Iron stand with sponge 195p SIL SOCKETS 0.1" pitch 20 way 80p 0.15" pitch 20 way 85p	IDC CONNECTORS PCB Plugs Female Female with latch Pins Header Card Strt Angle Pin Angle Pin Edge 10 way 65p 65p 65p 100p 16 way 75p 75p 80p 100p 20 way 80p 80p 95p 185p 28 way 105p 110p 115p 230p 34 way 115p 130p 135p 320p 40 way 140p 145p 150p 335p 50 way 165p 170p 175p 350p 80 way 195p 210p 220p 435p EURO CONNECTORS Gold Flashed Contacts Female Male Plug Pins Strt Pins Strt Angle Pin DIN41617 125p - - 175p DIN41612 200p - - 175p 185p 2 x 32 A + B 200p - - 175p 185p DIN41612 2 x 32 A + C 225p - - 185p 210p DIN41612 3 x 32 A + B + C 280p 290p 295p 300p RIBBON CABLE price per foot Grey Colour 10 way 15p 28p 16 way 25p 40p 20 way 30p 50p 24 way 40p 85p 28 way 55p 80p 34 way 60p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p 'D' CONNECTORS Male Solder lugs 55p 80p 120p 150p Angle pins 110p 175p 225p 300p PCB pins 100p 100p 180p 250p Female Solder lugs 90p 125p 180p 275p Angle pins 150p 200p 280p 390p PCB pins 100p 125p 195p 355p Covers 75p 70p 70p 85p IDC 25 way 'D' Plug 385p; Socket 450p 25 way 'D' CONNECTOR (RS232) Jumper Lead Cable Assembly 18" long, Single end, Male 475p 18" long, Single end, Female 510p 36" long, Double Ended, M/M 995p 36" long, Double Ended, F/F £10 36" long, Double Ended, M/F 995p	PANEL METERS FSD 60 x 46 x 35mm 0-50uA 0-100uA 0-500uA 0-1mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0-1A 0-2A 0-25V 0-50V 0-300V AC 520p CRYSTALS 32.768KHz 100 100KHz 400 200KHz 370 455KHz 370 1MHz 285 1.008M 275 1.28MHz 300 1.8MHz 200 1.8MHz 545 1.8432M 210 2.0MHz 225 2.4578M 140 3.12MHz 240 3.278M 195 3.5794M 95 3.686M 330 4.0MHz 190 4.032MHz 240 4.19430M 150 4.433619M 100 4.508MHz 200 4.80MHz 200 5.0MHz 150 5.185MHz 300 5.24289M 390 6.0MHz 175 6.144MHz 140 6.55366MHz 225 7.0MHz 150 7.328MHz 175 7.68MHz 200 8.0MHz 140 8.089333M 395 8.66723M 175 9.0MHz 200 10.0MHz 170 10.24MHz 200 10.5MHz 250 10.7MHz 150 12.0MHz 150 12.528M 300 14.31814M 170 15.0MHz 155 16.0MHz 200 18.0MHz 150 18.432M 150 19.3836M 150 20.0MHz 150 24.0MHz 150 24.9300MHz 325 26.89M 150 27.546M 170 27.145M 180 36.6667M 240 48.0MHz 240 100.0MHz 285	RELAYS Miniature, enclosed, PCB mount. SINGLE POLE Changeover RL-91 20SR Coil, 12V DC, (10V to 19.5V), 10A at 30V DC or 250V AC 195p DOUBLE POLE Changeover, 8A 30V DC or 250V AC RL-113 5SR Coil, 6V DC (5V to 9V), 190p RL-111 20SR Coil, 12V DC (10V to 19.5V) 195p RL-114 740R Coil, 24V DC (22V to 30V) 200p ASTEC UHF MODULATORS Standard 6MHz 375p Wideband 8MHz 550p BUZZERS miniature, solid-state 6V & 12V 70p PIEZO TRANSDUCERS PB2720 70p LOUDSPEAKERS Miniature, 0.3W @ 2in, 3W @ 2 1/2in, 3in 80p 2 1/2in 40in, 64in or 80in 80p 6" x 4" 8in 200p 7" x 5" 8in 225p 8" x 5" 8in 250p VIDEO MONITORS ● ZENITH - 12" Green, Hi-Resolution Popular £72 ● MICROVITEC 1431, Standard Res. Colour RGB input 14" incl cable £179 ● MICROVITEC 1451, 14" Medium resolution £229 ● KAGA 12", Med-res. RGB Colour. Has flicker-free characters. Ideal for BBC, Apple, VIC, etc £225 (car £7) ● KAGA 12", As above but Hi-Resolution £310 (car £7) ● Connecting Lead for KAGA £3 Carriage £7 Securicor
--	--	---	---	--	--

CMO 4000 20 4076 25 4543 65 4007 20 4077 25 4548 40 4001 20 4078 25 4553 210 4002 20 4081 20 4554 180 4006 70 4082 20 4555 50 4007 25 4085 60 4556 50 4008 60 4086 60 4557 250 4009 40 4089 120 4558 120 4010 20 4093 25 4559 140 4011 20 4394 70 4560 110 4012 20 4095 70 4561 104 4013 30 4096 100 4562 350 4014 50 4097 280 4563 180 4015 40 4098 70 4568 250 4016 25 4099 110 4569 175 4017 45 4160 95 4572 45 4018 55 4161 95 4580 255 4019 35 4162 96 4581 125 4020 50 4163 96 4582 99 4021 55 4174 96 4583 100 4022 80 4175 105 4584 40 4023 20 4194 105 4585 85 4024 35 4408 850 4597 330 4025 20 4409 850 4599 155 4026 80 4410 725 40085 90 4027 30 4411 750 40097 45 4028 40 4412 805 40098 42 4029 45 4415 590 40100 215 4030 20 4419 280 40101 130 4031 128 4422 770 40102 140 4032 85 4435 850 40103 412 4033 130 4440 900 40104 120 4034 145 4450 360 40105 220 4035 70 4451 350 40106 40 4036 250 4450 450 40107 58 4037 115 4500 395 40108 325 4038 75 4501 40 40109 100 4039 270 4502 90 40110 235 4040 45 4503 45 40114 240 4041 55 4504 100 40161 194 4042 45 4505 350 40163 75 4043 45 4506 100 40173 100 4044 50 4507 45 40174 75 4045 110 4508 130 40175 75 4046 60 4510 55 40181 220 4047 50 4511 55 40182 80 4048 50 4512 55 40192 95 4049 25 4513 150 40193 90 4050 25 4514 115 40194 70 4051 50 4515 115 40195 75 4052 50 4516 50 40244 198 4053 60 4517 275 40245 196 4054 70 4519 35 40225 250 4055 70 4519 35 40373 220 4056 85 4520 50 40374 220 4057 1000 4521 110 45106 588 4058 400 4522 125 45107 588 4059 500 4527 60 OCP71 120 4060 986 4528 45 ORP12 85 4063 80 4529 80 ORP61 88 4066 95 4531 120 BPW21 320 4067 230 4532 65 TL139 225 4068 20 4534 365 4069 20 4536 250 4071 20 4539 80 4072 20 4539 80 4073 20 4541 95	OPTO ELECTRONICS LEDs with clips TL209 10 TL211 GRN 14 TL212 Yel 14 TL220 2" Red 12 2" Green, Yellow or Amber 14 0.2" Bi colour 100 Red/Green 100 Green/Yellow 115p 0.2" Tri colour Red/Green/Yellow 85 Hi-Brightness Red 58 High-Bri Green or Yellow 68 Flashing red 100 0.2" red 55 Square LEDs, Red, Green, Yellow 30 Rectangle Stackable LEDs Red/Green or Yellow 18 Triangular LEDs Red 18 Green or yellow 22 Hi-Brightness Red 48 SFH205 Detector 118 TL32 Infra Red 52 TL78 Detector 55 TL38 50 TL100 50 BARGRAPH, Red 10 segments 200 ISOLATORS IL74 75 ILD74 145 ILQ74 275 TL111/214 70 ILCTE Darlington 135 TL117 125 4N33 Photo Darlington 136 7 Segment Displays TL312, 3" CA 120 TL313, 3" CC 120 TL321, 3" CA 140 TL322, 3" CC 140 TL729/730 140 DL704, 3" CA 125 DL707, 3" CA 125 FND557 Red 120 FND500 130 3" Green CA 150 3" Green CA 150 3" ± 1 Red CA 215 3" ± 1 Green CA 150 LCD 3 1/2 Digits 498 LCD 4 Digits 530 LCD 6 Digits 825 Reflective Switch 225 SLICED Optical Switch similar to RS Comp's 295
--	--

SPECIAL OFFER

ACCESS & VISA orders

Just phone your orders through, we do the rest.

Tel: 0923 50234

2764-250nS	195p	185p
27128-250nS	285p	285p
6116LP-3	195p	195p
6264LP-150nS	395p	385p

COMPUTER CORNER

- EPSON FX80 Printer £259
- EPSON FX100 Printer £249
- EPSON LX80 Printer £210
- CENTRONICS (NLI) Printer £195
- KAGA/TAXAN KP810 Printer £235
- KAGA/TAXAN KP910 Printer £315
- BROTHER HR15 Daisywheel £215

Cable for above printers to interface with BBC Micro £7

- TEX EPROM ERASER - Erases up to 25 Eproms. Has a built in safety switch. £30
- SPARE UV Lamp Bulb £8
- C12 Computer CASSETTES in Library cases £32p
- 8" & 9" Fan Fold paper (1000 sheets) £7 (Carr. 150p)

(Securicor/Carriage charge on printers is £7)

CALL IN AT OUR SHOP FOR A DEMONSTRATION ON ANY OF THE ABOVE ITEMS. BE SATISFIED BEFORE YOU BUY OR WRITE IN FOR OUR DESCRIPTIVE MICRO PERIPHERALS LEAFLET.

5 1/4" DRIVES for the BBC Micro

(All Drives are supplied cased with Power Supply and Utilities Disc)

- CS200 - Epson Single 200K, 40 track Double sided £89
- CS400S - Mitsubishi Single 400K, Double sided 40/80 track switchable £103
- CD400 - Epson dual 400K, 40 track Double sided £140
- CD800S - Mitsubishi dual 800K, Double sided 40/80 track switchable £186

- TWIN Disc drive case with Power supply and Cables to house your own drives £35
- All Single Drives with Power supply are supplied in a twin case for later inclusion of a second drive. (Securicor/Carriage on Drives £7)
- DISC INTERFACE KIT complete £59
- DFS Manual (comprehensive) (NO VAT) £7

SPDOS

The only professional Disc Interface for the Spectrum Micro.

SPECIAL OFFER THIS MONTH for ONLY £75

BBC MICRO WORDPROCESSING EXAMPLE PACKAGE

A complete wordprocessing package (which can be heavily modified to your requirements, maintaining large discount). We supply everything you need to get a BBC Micro running as a word-processor. Please call in for a demonstration.

Example Package:
 BBC Model B Plus, Watford DDFS+ upgrade, Wordwise Rom, Twin 800K Mitsubishi drives in beige, Zenith 12" Hi-res. monitor (Green), Brother HR15 daisywheel printer, Database & Spreadsheet software, 10 Discs, 500 sheets fan-fold paper, 4 way mains trailing sockets, manuals, leads & a carrying for the BBC.

Only: £999

BBC & MICROCOMPUTER & ACCESSORIES

BBC Model B PLUS £365

We stock the full range of BBC Micro peripherals, Hardware & Software like, Disc Drives (Top quality Epson & Mitsubishi), Diskettes, Printers, printer, Paper, Interface Cable, Dust Covers, Cassette Recorder & Cassettes, Monitors, Connectors (Ready made Cables, Plugs & Sockets), Plotter (Graphic Tablet) EPROM Programmer, Lightpen Kit, Joysticks, Sideways ROM Board, EPROM Eraser, Machinecode ROM. The highly sophisticated Watford's 16K BEEB DFS, WORDWISE, BEEB-CALC, Software (Educational Application & Games), BOOKS, etc, etc, Please send SAE for our descriptive leaflet.

Rapid Electronics

Fast component distribution

Unit 1,
Hill Farm Industrial Estate
Boxted, Colchester
Essex CO4 5RD

Telephone orders: 0206 36412
Telex: 987756



LINEAR										
555 CMOS	LM7555	55	LM386	85	LM924	290	SL486	240	TL084	90
709	LM339	30	LM387	90	ML925	290	SL490	280	TL170	50
741	LM301A	30	LM393	45	ML926	275	SN75477	380	TL170	50
748	LM311	35	LM710	48	ML927	275	SPO256AL2	425	ULN2003	80
AY-3-8910	LM318	110	LM721	48	ML928	275	Data on above	50	ULN2004	80
AY-3-8912	LM324	40	LM741	270	ML929	275	TB800	70	ULN2803	130
CA3046	LM332Z	85	LM747	60	NE551	135	TB810	65	XR2206	395
CA3080E	LM335Z	85	LM1458	35	NE552	20	TB820M	60	ZN414	75
CA3130E	LM339	40	LM1459	35	NE556	95	TCA940	65	ZN423	100
CA3140E	LM348	80	LM3915	190	NE566	95	TD41022	270	ZN424	70
CA3240E	LM355	40	LM3909	85	NE568	95	TL061	60	ZN425E	340
ICL7105	LM357	210	LM3914	190	NE568	95	TL082	65	ZN426E	200
ICL7611	LM380	80	LM3915	190	NE570	230	TL064	05	ZN427E	580
ICL8038	LM391	130	LM13600	100	NE571	195	TL071	32	ZN428E	435
ICL9211A	LM392	130	MC3302	75	NE532	160	TL072	55	ZN435E	360
			MC3340	190	NE534	135	TL074	105	ZN436E	525
			MF-10CN	300	RC4136	65	TL081	105	ZN459	190
			LM922	415	RC4558	45	TL922A	45	ZN1034E	190

BREADBOARDS

Protobloc breadboards are extremely useful for quick construction of electronic circuits without soldering. All sockets are on a 2.54mm pitch enabling DIL circuits and a wide range of components to be plugged in to the board. The contact pattern contains two separate contact groups each of rows of 5 interconnected contact sockets. Bus strips are provided for power use. All contact patterns are clearly marked on an alphanumeric grid. Supplied complete with approx. 20 layout sheets. Two sizes are available.



length	width	file points	rows	max no. 16 pin devices	prices
80mm	60mm	390	29	7	395p
172mm	65mm	840	64	7	695p

CAPACITORS

Mn polyester 63V DC type
1n, 2n2, 4n7, 10n, 22n, 5p, 47n, 100n, 6p, 220p, 9p, 470n, 13p.

Electrolytic. Radial lead type
1u, 2u2, 4u7, 4.7u, 6.3u, 10u, 22u, 22u, 25V 5p, 47u, 25V 7p, 100u, 25V 8p, 220u, 25V 13p, 470u, 16V 14p, 1000u, 16V 20p, 1000u, 25V 30p, 2200u, 16V 34p, 2200u, 25V 42p.

Tantalum bead
0.1u, 0.47u, 1u, 4.7u, 35V 6p, 2u2, 2.5V 6p, 4u7, 4.7u, 25V 6p, 10u, 4.7u, 25V 14p, 22u, 4.7u, 18V 18p, 47u, 4.7u, 40V, Ceramic disc 50V, 100p-10n 3p each, 100n 25V 6p

TRANSISTORS

AC127	30	BC148	10	BC237	6	BD132	40	MPF102	45	TIP42A	45	2N2904A	28
AC128	30	BC169C	10	BC238	5	BD138	35	TIP29A	35	TIP120	60	2N2905	28
AC175	25	BC171	10	BC239	6	BD140	35	TIP29C	35	TIP121	60	2N2905A	28
AC187	25	BC178	10	BC240	6	BF140	35	TIP30A	35	TIP122	60	2N2907	24
AC188	25	BC179	18	BC241	14	BF244B	35	TIP30C	35	TIP125	60	2N2907A	24
BC107	10	BC182	10	BC242	14	BF244B	35	TIP30A	35	TIP126	60	2N2907A	24
BC107B	12	BC182L	10	BC243	14	BF244B	35	TIP30C	35	TIP127	60	2N2907A	24
BC108	10	BC183	10	BC244	14	BF244B	35	TIP30C	35	TIP128	60	2N2907A	24
BC108C	12	BC183L	10	BC245	14	BF244B	35	TIP30C	35	TIP129	60	2N2907A	24
BC109	10	BC184	10	BC246	14	BF244B	35	TIP30C	35	TIP130	60	2N2907A	24
BC109C	12	BC184L	10	BC247	14	BF244B	35	TIP30C	35	TIP131	60	2N2907A	24
BC140	29	BC212	10	BC248	14	BF244B	35	TIP30C	35	TIP132	60	2N2907A	24
BC141	30	BC212L	10	BC249	14	BF244B	35	TIP30C	35	TIP133	60	2N2907A	24
BC142	28	BC213	10	BC250	14	BF244B	35	TIP30C	35	TIP134	60	2N2907A	24
BC143	30	BC213L	10	BC251	14	BF244B	35	TIP30C	35	TIP135	60	2N2907A	24
BC147	10	BC214	10	BC252	14	BF244B	35	TIP30C	35	TIP136	60	2N2907A	24

MICRO

2716	320	6116LP3	150	6800	200	6522	330
2532	430	6254LP15	320	6802	280	6532	520
2732 one time programmable	380	4156-15	160	6809	600	6551	540
2732	380	Z80A CPU	160	6810	140	8085A	320
2764-BBC	240	Z80A PIO	160	6811	140	8156	380
		Z80A DMA	520	6812	360	8251	350
		Z80A SO	520	6850	165	8253	370
		Z80A SO	520	6852	140	8255	320
		Z80A DMA	520	6875	500	8259	400
				6880	100	MC1488	60
				6502	370	MC1489	60

IDC CONNECTORS

PCB	PCB	PCB	Edge conn
16 way	80	85	90
20 way	90	95	90
26 way	110	110	105
34 way	120	130	130
40 way	140	150	145

RESISTORS

Carbon film 1+ 25+
1/4W 5% 4 70hm-10M 2p
1/2W 5% 4 70hm-4M7 3p
Metal film 3p
1/4W 1% 100hm-1M 3p
25+ price applies to 25+ per value
SIL resistor networks
8 resistor 9 pin type 20p

COMPONENT KITS

Our component kits offer a considerable saving when buying a complete range of components. Ideally suited for re-stocking etc.

0.25W Resistor kit. Contains 1000 0.25W 5% resistors from 4.7ohms thru to 10M. Quantities depend upon popularity i.e. 10x10r, 30x10r, 30x10k, 25x470k. **Just £7.90 each**

Ceramic capacitor kit. Total of 240 miniature ceramic capacitors from 22pF thru to 0.1uF. **Just £6.90 each**

Polyester capacitor kit. Total of 110 miniature polyester capacitors from 0.01u to 0.47uF. **Just £5.90 each**

Radial electrolytic kit. Total of 93 miniature radial electrolytics from 1u 63V thru to 2200u, 16V. **Just £7.50 each**

Preset kit. Total of 110 miniature horizontal mounting presets from 100R thru to 1M. **Just £6.90 each**

HARDWARE

PP3 battery clips 6
Red or black crocodile clips 36
Pan ultrasonic transducers 25
20mm panel fuseholder 25
6 or 12V electronic buzzer 65
6mm 8 ohm min. speaker 70
65mm 64 ohm min. speaker 75
12 way chocolate block 214
Red or amber panel neon 28

PCB EQUIPMENT

We offer a comprehensive range of equipment

Expo Helant 12V PCB drill 675
Expo Titan 12V PCB drill 1040
Drill stand to suit 1250
Variable speed power supply 1450
0.8, 1.0 or 1.4mm drills 50
Photo-etch PCB (Professional quality) single double
100 x 160mm 180 200
233 x 4 x 220 660 640
305 x 457mm 1160 1320

Pan fibre glass board double sided 75
100 x 160mm 160 175
233 x 4 x 220 160 175
203 x 95 80 90
203 x 306 200 220
Etch resist PCB 70p
Full range of PCB transfers also available - see catalogue

BRIDGE RECTIFIERS

1A 50V	20	2A 200V	40
1A 200V	25	2A 400V	45
1A 400V	30	6A 100V	80
1A 800V	38	6A 400V	85

REGULATORS

78L05	30	LM336K	680
78L12	30	LM712	40
78L15	30	79L05	50
7805	40	79L12	50
7812	45	79L15	50
7815	45	7905	45
LM317K	20	7912	45
LM317T	90	7915	45
LM323K	420	78H05	550

RELAYS

Ultraminiature SPDT relay rated 2A 6 or 12V 105
Ultraminiature DPDT relay rated 2A 6 or 12V 160
Miniature relay SPDT rated 10A 6 or 12V 180
Miniature relay DPDT rated 5A 6 or 12V 160

OPTO

3 or 5mm red 8
3 or 5mm green 11
3 or 5mm yellow 11
3 or 5mm clips 3
5mm superbright 30
5mm incoulor 30
ILD74 95
ILD74 185
MOC3020 180
Seven segment displays
0.3m common anode or cathode 95
0.5m common anode or cathode 100
0.5m common anode or cathode 105
10 bar DIL LED array (20pin DIL) 23p/m
High efficiency red 140

DIODES

BY127	12	1N4001	4
OA47	10	1N4002	7
OA90	8	1N4006	7
OA91	7	1N5401	12
OA200	8	1N5404	14
OA202	6	1N5405	15
1N914	4	400mV zeners	3
1N4148	3	1.3W zeners	13

AUDIO CONNECTORS

DIN	Plug	Skt	Jack	Plug	Skt
2 pin	8	8	2.5mm	10	9
3 pin	13	13	3.5mm	10	9
5 pin	14	13	2.5mm	17	20
Phono	10	14	Stereo	25	25

4mm plugs and sockets red or black
Plugs 12 Sockets 12
4mm terminals 36

TOOLS

Low cost side cutters 180
Both the above represent exceptional value. We have seen similar tools advertised at £30!
Bib wire stripper 180
Automatic wire stripper 590
Light duty cutters 380

VERO

Veroboard. Size 0.1in matrix
2.5 x 1 26 2.5 x 3.75 95
3.75 x 5 120 3.75 x 17 390
4.75 x 17 495 Vero board 190

Veropans per 100
single sided 55 double sided 65
Spot face cutter 150

RIBBON CABLE

Grey	per foot	100ft reel
10 way	14	650
16 way	25	1050
20 way	28	1310
26 way	35	1720
34 way	58	1950
40 way	68	2650
50 way	90	3320

DIN 41612

Gold flashed	Rt ang	wirewrap
64 way A+B	pin	socket
64 way A+B	150	175
64 way A+C	115	175
96 way A+B+C	150	245

CRYSTALS

1MHz	275	5.00MHz	100
1.00MHz	270	6.144MHz	110
1.8432MHz	180	8.0MHz	85
2.0MHz	180	10.0MHz	85
2.4576	85	12.0MHz	85
3.276	85	16.0MHz	85
4.0MHz	90	18.0MHz	100

SWITCHES

Low cost DIL switch
4 way 8 pin 70
6 way 12 pin 80
8 way 16 pin 90

Submin toggle switches
SPST 55 SPDT 60 DPDT 65

Miniature toggle
SPDT 50 DPDT centre off 65
DPDT 70 DPDT centre off 75

Standard toggle
SPST 35 DPDT 48

Miniature push to make
Miniature push to break 25

Side switches DPDT
Miniature 14 Standard 16

CONNECTORS

2X8 1/2 23 way edge connector	150
Spectrum 28 way edge conn	290
24 way IEEE male	350
36 way Centronix male	330

SOLDERING IRONS

High quality desolder tool 480
Antex CS 17W soldering iron 480
Iron stand to suit CS or XS 500
10 metres 22 swg solder 170
10 metres 22 swg solder 75
0.5Kg reel 22 swg solder 750

POTENTIOMETERS

Single pots 470ohms-2M2	38
Stero pots 1K-2M2	110
Switched pots 1K-2M2	105
Slider pots 5K-500K (60mm)	7
Min. no. presets 100-1M	30
Single turn cermet 100-1M	30
20 turn cermet 10ohms-500K	65

DIGEST

256K CMOS DRAM from Hitachi

Hitachi have introduced a 256K DRAM (dynamic random access memory) which uses CMOS technology.

The device offers the high capacity and high packing density of dynamic memories coupled with the low power requirements of CMOS, including the possibility of battery back-up.

The new DRAM is designated the HM51256 and is available in two versions, suffix P and suffix LP. The low power LP version draws between 40 and 60ma maximum in active mode (depending on access speed) and requires refreshing once every 32ms rather than once every 4ms as most conventional NMOS 256K DRAMs do. This reduces the average stand-by current from the 11mA required by NMOS devices to 300uA.

The access times available are 100, 120 and 150ns but a high speed page mode allows these devices to achieve access times of 55, 65 and 80ns respectively.

The HM51256P/LP is available in a plastic 16-pin DIL package and is pin-compatible with Hitachi's existing HM50256 256K DRAM.

Also new from Hitachi is a 32K x 8 pseudostatic RAM which they claim is much nearer in operation to true static RAMs than are existing pseudo-static types.

The HM65256BP requires minimal refresh control circuitry and can be interfaced directly with a microprocessor. It offers accesstimes of 60, 75 or 100ns, a power consumption of 175mW (typical) in active mode, and is expected to cost around one-fifth as much as a 256K static RAM. The device is available in a 28-pin DIL package, a skinny DIP or a SOP plastic package.

For further information on either of these products contact John Vickerton at Hitachi Electronic Components (UK) Ltd, Hitec House, 221-225 Station Road, Harrow, Middlesex HA1 2XL, tel 01-861 1414.



ETI PCB Service

Eye-eyed readers may have noticed that the PCB Service page is not included in this issue.

We will hasten to point out that this does not, we hope, mark a new round of problems with our suppliers, but rather reflects the popularity of the service. A considerable backlog of orders built up during the period for which the service was unavailable, and the number of orders received since the service restarted has exceeded all our expectations. The result is

that we are finding it difficult to meet the 28-day delivery deadline on orders, as some readers have already discovered to their cost.

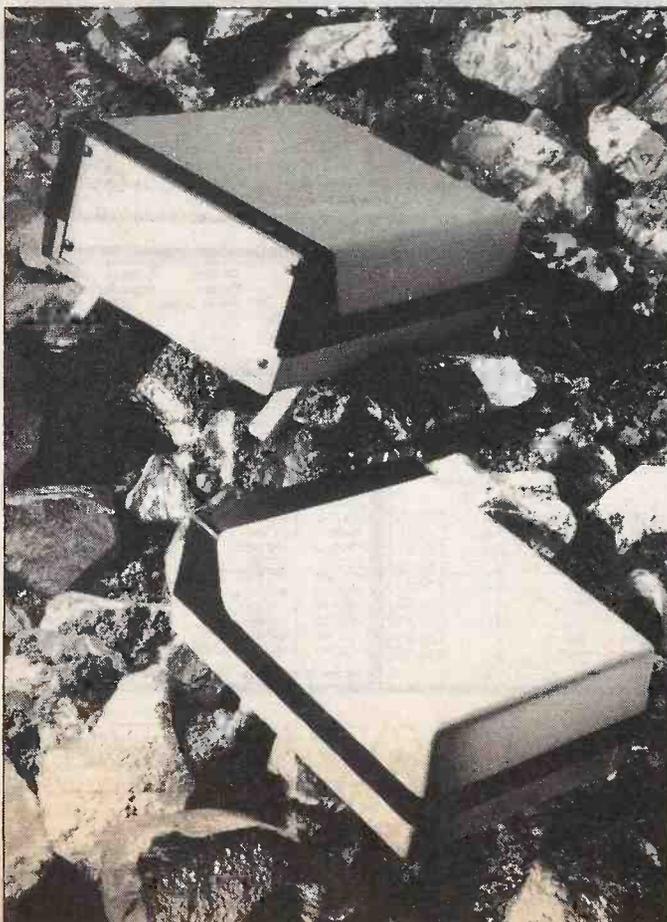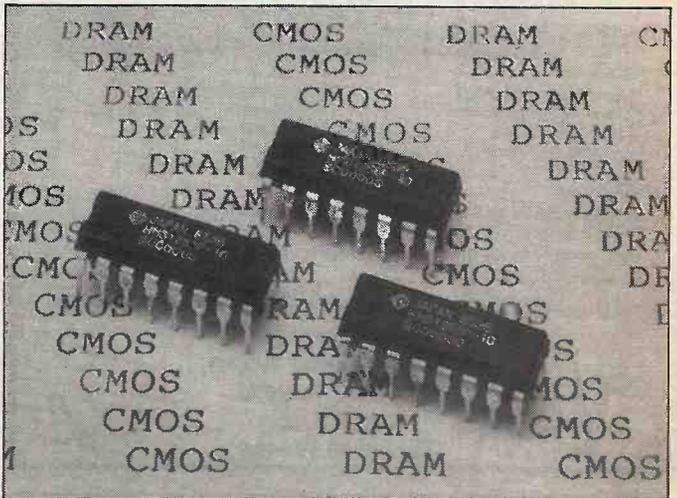Because of this, we have decided not to advertise the service this month in order to give our suppliers a chance to catch up a bit. We advise those readers who were thinking of ordering boards from us to hold on until things are straightened out, by which time we will be in a position to process their orders promptly.



Instrument Cases With Battery Compartments

The latest addition to BICC-Vero's line-up of instrument cases is a range of stylish, two-tone ABS enclosures which include an optional battery compartment.


Known as the Lux range, the cases are moulded in textured ABS and offer a choice of two-tone grey or two-tone brown colour schemes. One section of the three-part construction is designed to unclip from the outside and provide access to the optional battery compartment which can hold up to four AA cells.

The cases are designed to hold standard 100 x 160mm Eurocards and come in two sizes, 150 x 118 x 57mm and 190 x 148 x 67mm. The larger size will accept up to six Eurocards. The front panel is of aluminium and can either be fitted into a retaining slot in the case or screwed into place for greater security. The safe operating temperature of the Lux range is -20 to 90°C.

Also new from BICC-Vero is a development kit which contains ten blank front panels for Eurocards along with all the necessary handles, screws, etc. It is designed


to allow greater freedom in the siting of front panel controls on Eurocards, allowing the handle and other attachments to be placed in non-standard positions or even dispensed with entirely. The panel sizes available are 3U x 4, 5, 6 and 12HP widths and 6U x 4, 6 and 10HP widths.

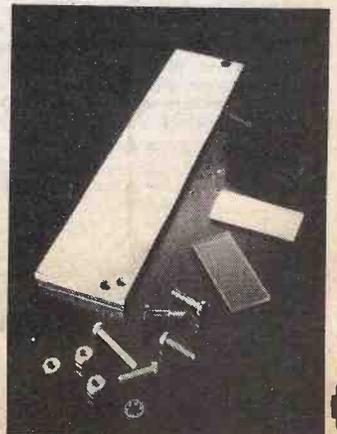BICC-Vero Electronics, Unit 5, Industrial Estate, Flanders Road, Hedge End, Southampton SO3 3LG, tel 04892 - 5824.



SPECTRUM OSCILLOSCOPE

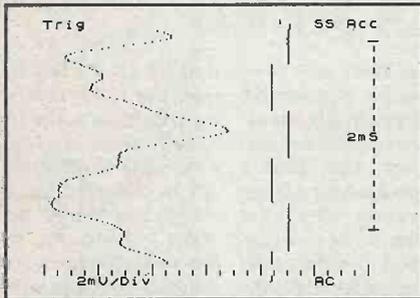YES! Your Spectrum Computer can do this:—



The AliDin Scope Module plugs into the ZX Spectrum expansion port and is completely controlled from the computer's keyboard, thus there are no knobs or dials and all settings are displayed on the screen, see above screen dump.

The waveform seen on the TV screen is a continuously updated waveform as seen on any normal digital oscilloscope, however it may be captured and held on the screen or in memory whilst displaying another signal for comparison.

The screen may also be printed out and this is useful for reports and handbooks.

- *Real-time or Storage
- *Trace Accumulation
- *Printing Option
- *AC and DC inputs

- *Single Shot feature
- *Settings displayed on screen
- *Further software under development
- *Comprehensive triggers

You need:—

- a) The Module at **£49.95** complete with signal input leads.
- b) The Scope software at **£24.95** complete with handbook.

Further software is under development to enable the module to be used as other test instruments.


Send your cheque or P.O. for **£74.95 + £1.00 P&P** or SAE for full details to:—

A/iDin
39 KINGSCLERE ROAD,
OVERTON, HANTS.
RG25 3JB.
TEL: 0256 770488

AFFORDABLE ACCURACY

Quality Multimeters from

Cirkit

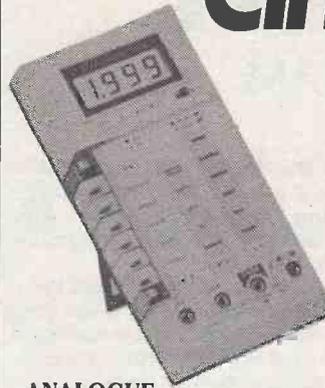

A comprehensive range of Analogue and (Pushbutton or Rotary Switched) Digital Models

ANALOGUE

HM-102BZ — 10ADC Range, 20k Ω /VDC, Buzzer, Battery Test Scale £12.50
 19 measuring ranges
HM-102R — Low end voltage & current ranges, Jack for Audio o/p voltages ... £11.00
 20 measuring ranges
HM-1015 — Rugged, Pocket sized meter, for general purpose use £7.50
 16 measuring ranges

Battery, Test Leads and Manual included with each model.

Please add 15% for VAT and 60p for p&p

DIGITAL

HC-7030
 0.1% Accuracy, Standard Model £39.50
HC-6010
 0.25% Accuracy, Standard Model £33.50
HC-5010
 0.25% Accuracy, TR Test Facility £39.50
DM-105
 0.5% Accuracy, Pocketable £21.50

All models have full functions and ranges and feature: 3 1/2 digit 0.5" LCD display — low battery indication — auto zero & auto polarity — ABS plastic casing — DC AC 10amp range (not DM-105) — Overload protection on all ranges — battery, spare fuse, test leads and manual


Full details and specification from:

Cirkit Distribution Ltd

Park Lane, Broxbourne, Herts, EN10 7NQ
 Telephone (0992) 444111 Telex 22478

TRADE ENQUIRIES WELCOME

ILP FROM JAYTEE

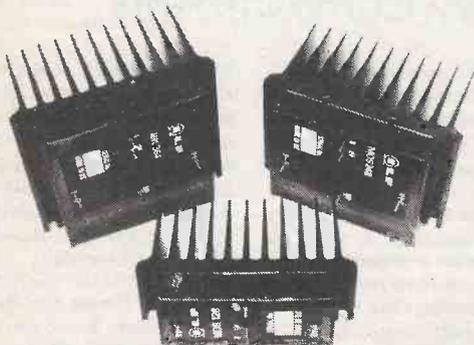

THE SPECIAL DISTRIBUTOR FOR SPECIAL AMPLIFIERS

ILP have long been recognised as manufacturers of top quality amplifiers.

All ILP products are built to extremely high specification for the ultimate in hi-fi performance. They're unique in being completely encapsulated with integral heatsinks, and can bolt straight onto the chassis. They're also extremely robust, ensuring high levels of reliability as well as performance.

ILP Amplifiers are now available through Jaytee. The UK Distributor with the availability and service to match the quality of the amplifiers.

POWER BOOSTER AMPLIFIERS

The C15 and C1515 are power booster amplifiers designed to increase the output of your existing car radio or cassette player to 15 watt rms.

C15 15 watts £10.65
 C1515 15 + 15 watts £19.78

ILP LOUDSPEAKER

power 350 watt rms
 size 12 inches
 impedance 8 ohms
 range 20 Hz to 5 KHz

NEW £78.61

FOR FREE DATA PACK PLEASE
 WRITE TO OUR SALES DEPT.

PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches, etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre-Amp	Full Hi Fi facilities	£8.45
HY66	Stereo Pre-Amp	Full Hi Fi facilities	£13.95
HY73	Guitar Pre-Amp	Two Guitars plus Microphone	£14.45
HY78	Stereo Pre-Amp	As HY66 less tone controls	£13.45
NEW! HY83 Guitar and Special Effects Pre-Amp as HY 73 Plus Overdrive and Reverb £18.95			

MOUNTING BOARDS: For ease of construction we recommend the B6 for HY6 £0.95. B66 for HY66-83 £1.45.

MOSFET MODULES

Ideal for Disco's, public address and applications with complex loads (line transformers etc). Integral Heatsink
 slew rate 20V/ μ s distortion less than 0.01%

Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4-8	£34.45
MOS248	120	4-8	£39.45
MOS364	180	4	£64.45

BIPOLAR MODULES

Ideal for Hi Fi, Full load protection
 integral Heatsink, slew rate 15V/ μ s

Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4-8	£10.45
HY60	30	4-8	£10.45
HY6060	30 + 30	4-8	£21.95
HY124	60	4	£17.45
HY128	60	8	£17.45
HY244	120	4	£22.45
HY248	120	8	£22.45
HY364	180	4	£33.45
HY368	180	8	£34.95

Distortion less than 0.01%

POWER SUPPLY UNIT

Type	For Use With	Price
PSU30	PRE AMP	£6.45
PSU212	1 or 2 HY30	£16.45
PSU412	1 or 2 HY60, 1 HY6060, 1 HY124	£18.45
PSU422	1 HY128	£20.45
PSU432	1 MOS128	£21.45
PSU512	2 HY128, 1 HY244	£22.45
PSU522	2 HY124	£22.45
PSU532	2 MOS128	£22.95
PSU542	1 HY248	£22.95
PSU552	1 MOS248	£24.95
PSU712	2 HY244	£26.45
PSU722	2 HY248	£27.45
PSU732	1 HY364	£27.45
PSU742	1 HY368	£29.45
PSU752	2 MOS248, MOS364	£29.45

All the above are for 240v operation



Jaytee Electronic Services, 143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL Telephone: (0227) 375254

All Prices include VAT, Post & Packing

Creditable Stereo

The idea of the 'credit card' radio has been around for a little while now and several companies have brought out AM and mono FM models in this style. Now Sony have gone a stage further and introduced a radio receiver which is no larger than any of the other models on sale but offers full FM stereo reception.

The SRF 201 has the outline dimensions of a standard credit card (around 3½" x 2¼") and is just 3mm (⅛") thick. Three tiny buttons on the top edge control power on/off, volume increase and volume decrease while tuning is achieved by means of a knob set into the front surface of the radio and projecting slightly at one side. The two padded earpieces are joined by thin, lightweight wire and are connected to the radio by means of a flat, moulded connector which slides onto one corner.

The radio has internal rechargeable batteries and a separate charger unit is included. This takes the form of a black plastic box about the size of a cigarette packet with a slot on the front into which the radio clips.

The radio can be used normally whilst charging is taking place and all of the controls remain accessible. The charger operates either from the mains by means of an adaptor (not supplied) or from four AA-size cells, allowing the radio to be carried about even when it is being charged.

Sony were happy to lend us an SRF 201 and the ETI staff were just as happy to try it out for a couple of weeks. The sound quality is quite excellent and the volume level obtainable is enough to satisfy all but the most diehard of aural masochists. The earpieces are very light and generally quite comfortable but a number of people had difficulty persuading them to stay in place. Not everyone, it seems, has ears which conform to the Sony model.

The sensitivity is pretty good but, as might be expected, it is often impossible to find a signal strong enough to ensure continuous stereo. As a result, when walking around with the radio on, the reception tends to change from stereo to mono and back again with each change in direction.



This problem is exacerbated a little by tuning difficulties. Because the tuning knob is quite small and has no reduction drive, it is not easy to set it accurately to give the best reception. It was generally felt that Sony might have done better to use a large knob which extended to both sides of the radio. It would then be possible to twiddle the knob

between thumb and index finger which would give much greater control.

These criticisms aside, the SRF 201 represents a considerable achievement and is undoubtedly well made and presented. However, at a recommended retail price of £69.95 we suspect it is destined to remain something of a novelty.

Bright Buoys

Many of the navigation buoys around Britain's coast will soon be powered by electricity derived from the action of the waves.

The lighthouse authority Trinity House have been conducting tests in the Harwich area using a device called the Whale Wave Activated Turbine Generator. They now plan to extend the test to cover the North West coast, the North Sea area and the Isle of Wight, after

which they hope to use the turbine to power about 100 of the 400 lighted buoys they are responsible for.

The generator is based upon a device known as the Wells turbine which is named after its inventor, Dr Alan Wells, a former professor at Queen's University, Belfast. It relies on a flow of air to drive it but, unlike other turbines, the blades always turn in the same direction regardless of the way the air flows.

This makes it ideal for use on buoys. The conventional navigation buoy has an open tube run-

ning right through it and extending some three metres or so into the water. The tube is designed to add stability. The turbine will be placed at the top of this tube, about two metres above the water level. Movement of the buoy causes the water column to rise and fall and so produces a flow of air which will drive the turbine.

Trinity House say they are sufficiently convinced of the turbine's reliability to allow it to be used to protect shipping. Buoys powered by batteries or gas cylinders have to be serviced at intervals of six months or less, and the

increasing use of radar beacons and other electrical equipment is reducing battery life still further. It is hoped that the wave-powered buoys will only need servicing every three years or so apart from routine checks on moorings.

The manufacturers of the turbine, Munster Simms Engineering Ltd of County Down, Ireland, say they have received enquiries from many lighthouse authorities around the world. They point out that the system has many possibilities including, eventually, the supply of electricity to mains grids.

Automatic Wire Stripper



We have featured so many wire strippers in these pages that it is hard to believe anyone still thinks the market is worth getting into, but Plasplugs are apparently undaunted. They have launched their new product with considerable publicity and sent several free samples to ETI.

The tool is designed to remove the insulation from single and multicore round cables in one action. The wire is inserted into the jaws to the desired length (graduations along the jaws act as a guide) and the handle then squeezed until the insulation is fully removed. A second aperture carries a blade which will cut cleanly through cables of up to 5/16" (8mm) diameter.

We found that the samples

supplied generally worked well and stripped away insulation on both stranded and solid-cored wire without visible damage to the insulation. However, whilst the tool worked well on cables of 0.5mm² and above (3A mains cable, 16/0.2 stranded wire, etc), it was less efficient with some of the thinner connecting wires often used in electronics. Because of this, it will probably be of more use to the DIY enthusiast involved with domestic mains wiring than to the electronics hobbyist.

The Plasplugs Automatic Wire Stripper will be available from DIY and hardware stores, etc, and the recommended retail price is £3.95.

OSCILLOSCOPES

TELEQUIPMENT D67 Dual Trace 50 MHz Delay Sweep with manual £250
 COSSOR CDU150 Dual Trace 35MHz Solid State. Portable 8 x 10cm display. With Manual £200
 S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8 x 10cm display. With Manual £150
 TELEQUIPMENT D43. Dual Trace 15MHz. With Manual £100
 TELEQUIPMENT S54A. Single Trace 10MHz Solid State. With Manual £110
 TELEQUIPMENT S43. Single Trace 25MHz. With Manual £75

PHILIPS DIGITAL MULTIMETERS
 4 digit. auto ranging. Complete with batteries and leads (p&p £5)
 TYPE PM2517X (LCD) £75

MULTIMETERS

AVO 8 Mk4 Complete with batteries & leads £60
 AVO 8 Mk2 Complete with batteries & leads £50
 AVO TEST SET No 1 (Military version of Avo 8). Complete with batteries, leads & carrying case £65
 AVO Model 7x. Complete with batteries, leads & carrying case £40
 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads. £18
 AVO 72 - Similar to above but no AC current range. With batteries & leads £10
 ELEMIC Multimeters. Un-used. Supplied with leads & batteries (p&p £2)
 EBM20 - 37 Ranges £10
 SUPER 50-57 Ranges (incl carrying case) £20
 Other models available.

STEPPING MOTORS

Type 1.200 Steps per rev. 4 Phase (5 wire) 12/24V. Torque 25oz inch (will run on 5V with reduced torque) £15 ea
 Type 2.6/12 Steps per rev. 3 Phase. 12/24V (will work on 5V) £2 ea, 5 off £7.50
 Type 3. NORTH AMERICAN PHILIPS 24 Steps per rev. 4 wire 5V 3.3Amps 0-250rpm 0-200 PPs £6 ea
 Type 4.200 Steps per rev. 120V (3 wire) Torque 25oz inch £4 ea
 Type 7. WARNER 24 Steps per rev. 3 Phase (6 wire). 28V. Holding Torque 45 oz inch £5 ea

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total Goods & Carriage.

STEWART OF READING Telephone: 0734 68041

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
 Callers welcome 9 a.m. to 5.30 p.m. Mon-Fri (until 8pm Thurs)

PROFESSIONAL 9" GREEN SCREEN MONITORS

Made by KGM for Reuters. Gives quality 80 column x 24 line display. Composite Video In. Cased. Good Condition. Now only £32 ea

5 1/4" FLOPPY DISK DRIVES

TANDON 1/2 Height. Single sided double density. Brand new £45 ea
 MP1 Double sided. Double density. 80 track. Un-used £100 ea

DISK DRIVE PSU. 240V in 5V 1.6A & 12V 1.5A Out. Size W125mm. H75mm. D180mm. Cased. Un-used. Only £10 ea (p&p £2)

QWERTY KEYBOARD (as in LYNX MICRO). Push to make. Cased Only £5 ea (p&p £2)
 LYNX MICRO - 128K. No power. Supply available. Therefore Only £50 ea (p&p £5)

AVO TRANSISTOR TESTER TT169

Handheld GO NOGO for in situ testing. Complete with batteries, leads & instructions. p&p £3 Now only £12

RACAL 32MHz Universal counter timer. Type 836 with manual Only £50 ea

NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester £515
 HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester £270

All other models available.

BLACK STAR COUNTER TIMERS (p&p £5)

APOLLO 10 - 100MHz Ratio/period/time interval etc £219

APOLLO 100 - 100MHz (As above - with more functions) £285

BLACK STAR FREQUENCY COUNTERS P&P £4

Meteor 100 - 100MHz £99

Meteor 600 - 600MHz £126

Meteor 1000 - 1GHz £175

BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110

HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 £33.50

OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 £11

Universal Semiconductor Devices Ltd.

17 Granville Court, Granville Road, Hornsey, London N4 4EP, England. Tel: 348 9420/9425* Tlx: 25157 usdco g




We offer one of the largest ranges of semiconductors at highly economical prices. The following semiconductor types are available from stock. If we don't stock what you need then we can get it fast from our facilities in West Germany and USA upon request.

TRANSISTORS - Bipolars - Germanium and Silicon


Small signal Power Darlington - all shapes and sizes VHF/UHF devices - all shapes and sizes

FETS - Power Mosfets Unijunctions

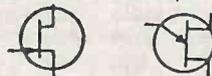

DIODES - Germanium and Silicon

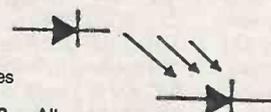Rectifiers and Bridges Opto-Electronic devices LEDs of all shapes and sizes



THYRISTORS and TRIACS - All shapes sizes ratings



INTEGRATED CIRCUITS: Consumer - Digital/Analogue Microprocessors and Peripherals IC Sockets

JAPANESE COMPONENTS - Vast range of discrete's and consumer IC's System A - All semiconductors available from USD. Amp - £75.00 incl. VAT & p&p. Pre-amp - £90.00 incl. VAT & p&p.

Mail order customers: Please send for our comprehensive price list, enclosing £1.00 in stamps. Cheque or postal order.

SYSTEM A AMP
 All semi-conductors available. Amp plus pre-amp £90, amp only £75

Catalogue sent free of charge, when requested on official letterhead (without refund), to OEM's, Schools, Colleges, Universities, Government Institutions, Computer Firms, Electronic Repair Firms and Distributors. Special discounts and payment terms are available to above institutions.

Please enquire for quantity discounts.

WE WELCOME TELEPHONE AND TELEX ENQUIRIES!

MICROBOX II THE 6809 SINGLE BOARD COMPUTER THAT YOU BUILD YOURSELF

VIDEO KEYBOARD PRINTER SERIAL PORT SERIAL PORT
 OUTPUTS PORT PORT

SYSTEM EXPANSION BUS
 BATTERY BACKED REAL-TIME CLOCK/CALENDAR

128KBYTES SHARED MEMORY RAMDISC
 HIGH SPEED SILICON DISC ACTS LIKE A STANDARD 'FLEX' DISC

ALPHANUMERIC DISPLAY
 108 x 24 CHARACTER FORMAT.
 USER DEFINABLE CHARACTERS.
 STANDARD VDU CONTROL FUNCTIONS

EXTREMELY FAST, VERY HIGH RESOLUTION GRAPHICS
 768 x 576 MONOCHROME DISPLAY
 HARDWARE VECTOR GENERATION BY ADVANCED NEC7220 DEVICE. LINE, POINT, ARC, PATTERN, TEXT, AREA FILL ETC.

POWERFUL 68B09E 8/16 BIT MICROPROCESSOR

SYSTEM SUPPORT MONITOR (8KBYTES) containing:
 DISC AND INPUT/OUTPUT DRIVERS
 GRAPHIC PRIMITIVES
 TERMINAL EMULATOR
 UTILITY AND DIAGNOSTICS
 "FLEX" BOOT AND CONFIGURE

60KBYTES USER MEMORY

FLOPPY DISC INTERFACE
 SUPPORTS SINGLE OR DUAL, 40/80 TRACK, SINGLE OR DOUBLE DENSITY DISC DRIVES

EPROM DISC (AND PROGRAMMER)
 HIGH SPEED READ ONLY SILICON DISC ACTS LIKE A STANDARD 'FLEX' DISC PROVIDES 'INSTANT' SOFTWARE

**BARE PCB's AND DOCUMENTATION
 + SYSTEM SUPPORT MONITOR
 + SYSTEM UTILITIES DISC - £95.00
 FLEX + EDITOR + ASSEMBLER £75.00**


Micro Concepts



Ex VAT

2 ST. STEPHEN'S ROAD · CHELTENHAM · GLOUCESTERSHIRE GL51 5AA
 Telephone: Cheltenham (0242) 510525

Low-Profile PCB Mounting Transformers

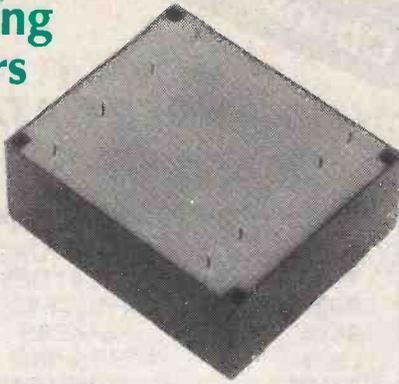

The latest additions to Avel-Lindberg's range are a series of 6 and 12VA PCB-mounting transformers which are less than one inch high.

Fully encapsulated in flat thermoplastic cases, the transformers conform to what is known as the 'American footprint' for pin spacing and feature four moulded holes which allow them to be screwed to the board for additional security.

The ZFL6 (6VA) and ZFL12 (12VA) ranges are available with either 110, 115 or 120 volt dual primary windings and 5, 6, 6.3, 8, 9, 10, 12, 15, 17 and 18 volt dual secondary windings. The construction uses separate, non-concentric bobbins to give low inter-winding capacitance and complete immersion in epoxy resin enables them to withstand a prof-

test at 5000V AC. The maximum operating temperature is +40°C, the insulation is to class E and both ranges conform to IEC 65 class 2, BS415 class 2 and VDE 0551 class 2.

The ZFL6 range have maximum dimensions of 22m (0.86") high x 53mm (2.09") x 44m (1.73"). Maximum dimensions for the ZFL12 range are 24mm (0.93") high x 68mm (2.67") x 57mm (2.24").

Also available from Avel Lindberg is a leaflet which describes their range of ultra-thin transformers in ratings from 0.8VA to 30VA. The 0.8VA type is claimed to be the thinnest transformer in the world and was featured in News Digest in ETI January 1984.

Avel-Lindberg Ltd, South Ockendon, Essex, England RM15 5TD, tel 0708 - 853 444.

● A group with the catch title of UK National Coordinating Committee on Satellites in Education has got together to, well, coordinate the use of satellites in education. They are stressing the possibilities offered by satellites not just in science and technology courses but also in geography and modern language teaching, and are keen to liaise with teachers and others who have ideas for projects or research. Their 40-page Guide For Teachers costs £3.50 inclusive from AMSAT (UK), 94 Herongate Road, Wanstead Park, London E12 5EQ (cheques payable to SEUK) and their strategy paper is available free-of-charge from Dr John Gilbert, Department of Educational Studies, University of Surrey, Guildford GU2 5XH.

● We have run out of the digital panel meters which were on special offer in last month's issue, but mensurative readers may be interested to hear that Electronics and Computer Workshop Ltd offer a 3-digit DPM kit for £17.90 inclusive. Known as the K2032, it will display readings

from -99mV to +999mV full scale, has positive and negative overflow indications and features a resolution of ±1mV and non-linearity of 0.1%. The input resistance is 100M and it requires a 5V DC supply at 250mA. ECW Ltd, 171 Broomfield Road, Chelmsford, Essex CM1 1RY, tel 0245 - 262 149.

● The Health and Safety Executive say that more accidents are caused by defective plugs, leads and sockets than by faults in the appliances to which they are connected. Because of this, they have issued a Guidance Note called Flexible Leads, Plugs, Sockets, Etc which gives practical advice on safe working procedures, repairs and sensible precautions. The note is designated GS37 and costs £2.25 from HMSO bookshops. Also available is a leaflet on health and safety requirements which is aimed at the self-employed and those running small businesses. Contact the Health and Safety Executive, Regina House, 259-269 Old Marylebone Road, London NW1 5RR, tel 01-723 3418.

Cortex

HARDWARE
SOFTWARE

Operative Systems

MDEX Professional Dev. System £95
CORTEX POWER-BASIC disc extensions: CDOS £43

MDEX Extensions

FORTH with Screen editor assembler £55
- Graphic extensions £35
PASCAL by Pre Brinch Hansen £85
QBASIC Compatible with
CPM CBASIC - only complied! £150
WINDOW Full screen editor £150

CORTEX LISTINGS/CDOS DISCS

PENGO, BLUE-BIRD, GOLF £13
SPACE-BUGS, BREAKOUT, PONTOON, MICROPEDE £13
CDOS WORD PROCESSOR (DISC ONLY) £13
DRAWTECH (DISC ONLY) £43


DISC DRIVES

80 Track half height, double sided, double density 1M £125
40 Track half height, single sided, double density 256K £110

E-Bus cards

9995 Processor Board	Blank + PAL'S	£52
	Built	£175
64/128k RAM Card	Blank + PAL	£42
	Built	£145/245
Floppy/Winchester Interface Card	Blank	£32
	Built	£135
Joystick/Centromes/Timer Board	Blank	£13
	Part kit	£36
LIMITED OFFER ONLY: 9909's	Full kit	£43

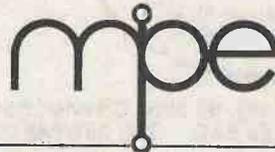STATE DISC FORMAT & ADD VAT TO ALL PRICES




MicroProcessor Eng Ltd
21 Hanley Road · Shirley
Southampton · SO1 5AP
Tel: 0703 780084

Master Electronics - Microprocessors - Now! The Practical Way!

● Electronics - Microprocessors

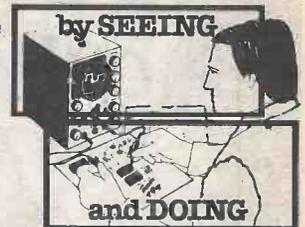- Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.



● Recognise and handle all current electronic components and 'chips'.

● Carry out full programme of experimental work on electronic computer circuits including modern digital technology.

● Build an oscilloscope and master circuit diagram.

● Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE

Please send your brochure without any obligation to

OR TELEPHONE US 062 67 6114
OR TELEX 22758 (24 HR SERVICE)



NAME _____

ADDRESS _____

IS
IT

I am interested in

ELECTRONICS

MICROPROCESSORS

RADIO AMATEUR LICENCE

CITY & GUILDS EXAMS

Other Subjects


British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS

Interak 1

AN EXPANDABLE DISK-BASED Z80A DEVELOPMENT SYSTEM YOU CAN BUILD YOURSELF!

Universities, Colleges, Industry, Enthusiasts:

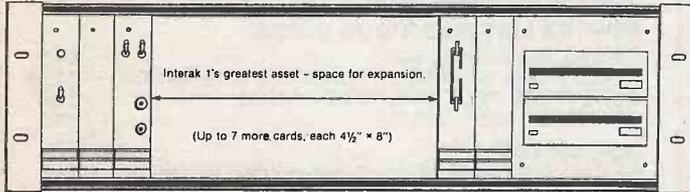Unlike home computers, development systems have entirely "open" architectures, use standard TTL etc. chips (ie no ULA's!), and are built in a proper engineering fashion. Usually these superior products carry a correspondingly superior price tag, but you can build Interak yourself board by board and thus afford a system which would normally be out of your reach and/or understanding.



The initial development system has 64K of RAM, a 4 MHz Z80A CPU, parallel ASCII keyboard interface, VDU Interface (TV set or monitor), and a floppy disk drive interface for up to 4 drives. Any size (including 8" double density) can be used, but our 1 Megabyte 3.5" drives are proving very popular because they can fit into the system rack, (and they only cost £87.00 each + VAT). CP/M 2.2 is available, giving access to thousands of "public domain" programs.

The system can be described as "future proof" because it uses plug in 4.5" x 8" cards in an industrial quality 19" 3U rack. We have been established since 1970, and this system was first made in 1977 so (unlike almost all other computers) it has stood the test of time.

Send two second class stamps, or telephone for a detailed descriptive leaflet, specification, prices, etc.

Greenbank

Greenbank Electronics (Dept T4E), 92 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG. Tel: 051-645 3391

For KITS & COMPONENTS - Choose the easy way - with

TK

SEND SAE NOW

for our **FREE CATALOGUE**
Or ring: 01-567 8910 for

the **LOWEST** prices on -

- | | | |
|--------|-----------------|----------|
| CMOS | CONNECTORS | BOOKS |
| TTL | REGULATORS | TOOLS |
| LINEAR | MICROPROCESSORS | PCBs |
| SCRs | SPEAKERS | CRYSTALS |
| LEDs | HEATSINKS | SWITCHES |
| NICADS | MULTIMETERS | RELAYS |

AND **LOTS LOTS** MORE

We also **STOCK** over 30 KITS for Timers, Remote Control, Disco Lights, Temperature Control, etc. **PLUS** a wide range of **VELLEMAN** and **PANTEC** KITS.


Z80A CPU **£2.19**
(5 for **£9.95**) + VAT

TK ELECTRONICS
13 BOSTON RD
LONDON W7 3SJ

SEND 9" x 6" SAE
OR CALL AT SHOP
MON-FRI 9-5pm
SATURDAY 10-4pm

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P. Europe £2.75. Elsewhere £6.50. Giro No. 529314002. **SCHOOL OR LOCAL AUTHORITY ORDERS WELCOME.** Goods by return subject to availability.

CRICKLEWOOD ELECTRONICS LTD

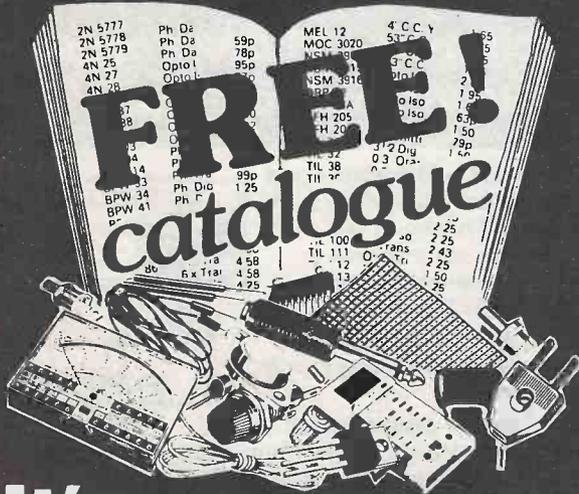

It's no secret...

...that there is a *real difference* at *Cricklewood Electronics*. That's why you should never be without the **FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE**, for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your **FREE** copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977



ETI

ELECTROVALUE

means...

reliability when you need it most
We've been the leading Mail order suppliers for over 20 years

I.C's
SEMI CONDUCTORS
TOOLS • COMPONENTS
ACCESSORIES

METERS
FREE POSTAGE • DISCOUNTS

52 PAGE CATALOGUE FREE ON REQUEST

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham,

Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475

North Branch, 680 Burnage Lane, Manchester M19 1NA

Phone 061 432 4945

Please mention this publication when replying

BBC Micro Computer System

BBC Master Series

AMB15 BBC MASTER Foundation computer 128K £435 (a)

AMB12 BBC MASTER Econet computer 128K (only ANFS) £348 (a)

AMC06 Turbo (65C102) Expansion Module £87 (b)

ADF13 Rom Cartridge £13 (d)

ADF10 Econet Module £49 (c)

ADJ22 Ref. Manual Part I £14.50 (c)

ADJ23 Ref. Manual Part II £14.50 (c)

ADJ24 Advanced Ref. Manual £19.50 (c)

ACORN COMPUTER SYSTEMS

BBC B PLUS with 128K £389 (a)

BBC B PLUS Econet & DFS £399 (a)

BBC Dust Cover £4.50 (d)

UPGRADE KITS

Econet Kit £55 (d)

1770 DFS Upgrade for Model B £43.50 (d)

1.2 OS ROM £7.50 (d)

DNFS ROM £17.50 (d)

ADFS Rom (for B with 1770 DFS & B Plus) £26 (d)

64K Upgrade Kit for B Plus £35 (d)

ECONET ACCESSORIES

Econet Starter Kit £85 (d)

Econet Socket Set £34 (c)

File Server Level 1 £75 (d)

File Server Level II £210 (d)

Printer Server Rom £41 (d)

10 Station Lead set £26 (c)

Adv. Econet User Guide £10 (d)

ACORN ADD-ON PRODUCTS

Z80 2nd Processor £329 (a)

6502 2nd Processor £169 (a)

Teltext Adaptor £125 (b)

IEEE Interface £278 (b)

COMMUNICATIONS ROMS

Terminator £25 (d)

Communicator £49 (d)

Commstar £28 (d)

DATABEEB £24 (d)

BBC FIRMWARE & SOFTWARE

Database Management Systems

Word Processors

Languages

Spreadsheets

Utilities

For full details on the wide range of above packages please write to us.

TORCH UNICORN products including the IBM Compatible GRADUATE in stock. For detailed specification or information on our comprehensive BBC range please write to us.

PRINTERS

EPSON

LX-80NLQ £195 (a)

FX85 (80col) NLQ 8K RAM £315 (a)

Optional Tractor Feed £20 (c)

FX105 (136col) £449 (a)

JX80 4 colour printer £435 (a)

LQ800 (80col) £595 (a)

LQ1500 (136col) 2K buffer £875 (a)

LQ1500 (136col) 32K buffer £950 (a)

PLOTTERS

Epson H180: A4 4 colour Plotter £345 (a)

Hitachi 672: A3 4 colour Plotter £465 (a)

TAXAN KAGA:

KP810 80 Col NLQ £195 (a)

KP910 156 Vol NLQ £339 (a)

JUKI 6100 Daisy Wheel £289 (a)

HR15LX (Serial) £295 (a)

HR15LX (Serial) £365 (a)

Paper:

2000 Sheets Fanfold:

9.5" x 11" £13 (b)

14.5" x 11" £18.50 (b)

Labels: (per 1000)

3.5" x 17/16" Single row £5.25 (d)

27/16" x 17/16" Triple row £5.00 (d)

ACCESSORIES

EPSON

FX plus sheet feeder £129.00 (b)

LX80 Sheet feeder £48.00 (b)

Paper Roll Holder £17.00 (d)

FX80 Tractor attachment £37.00 (c)

Interfaces: 8143 RS232 £28.00 (c)

8148 RS232 + 2K £57.00 (c)

8132 Apple II £60.00 (c)

8165 IEEE + cable £85.00 (c)

Serial & Parallel Interfaces with larger buffers available.

Ribbons: RX/FX/MX80 £5.00 (d)

RX/FX/MX100 £10.00 (d)

LX80 £8.00 (d)

Spare pens for H180 £7.50/set (d)

FX80 Tractor Attachment £37 (c)

KAGA TAXAN

RS232 Interface + 2K Buffer £85 (c)

Ribbon KP810/910 £8.00 (d)

JUKI:

RS232 Interface £85 (c)

Spare Daisy Wheel £14.00 (d)

Ribbon £2.50 (d)

Sheet Feeder £182 (a)

Tractor Feed Attachment £129 (a)

BROTHER HR15:

Sheet Feeder £189 (a)

Tractor Feeder £99 (a)

Ribbons Carbon or Nylon £4.50 (d)

Red Correction Ribbon £2.00 (d)

BBC Printer Lead:

Parallel (42") £7.00 (d)

Serial £7.00 (d)

Printer Leads can be supplied to any length.

DISC DRIVES

These are fully cased and wired drives with slim line high quality mechanisms. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. All 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

PD800P (2 x 400K/2 x 640K 40/80T DS) with built in monitor stand £279 (a)	3.5" DRIVES
PD800 (2 x 400K/2 x 640K 40/80T DS) £249 (a)	1 x 400K/1 x 640K 80T DS TS35 £109 (b)
TS400 1 x 400K/1 x 640K 40/80T DS £109 (b)	2 x 400K/1 x 640K 80T DS TD35 £199 (b)
PS400 with psu 1 x 400K/1 x 640K 40/80T DS £129 (b)	PS35 1 with psu £129 (b)
	PD35 2 with psu £209 (b)

3M FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

5 1/4" DISCS	3 1/2" DISCS
40 SS DD £12 (d)	80T SS DD £30 (d)
40T DS DD £16 (d)	80T DS DD £38 (d)
80T SS DD £21 (d)	

DISC ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives... 3 1/2" £16 (d), 5 1/4" £14.50 (d)

Single Disc Cable £8 (d)

10 Disc Library Case £1.80 (c)

40 Disc Lockable Box £14 (c)

Dual Disc Cable £8.50 (d)

30 Disc Case £8 (c)

100 Disc Lockable Box £19 (c)

MICROVITEC

All 14" monitors now available in plastic or metal cases, please specify your requirement.

14" RGB	14" RGB with PAL & Audio
1431 Std Res £179 (a)	1431 AP Std Res £205 (a)
1451 Med Res £235 (a)	1451 AP Med Res £275 (a)
1441 Hi Res £375 (a)	
Swivel Base for Plastic 14" Microvitec £20 (c)	
20" RGB with PAL & Audio	
2030CS Std Res £380 (a)	2040CS Hi Res £685 (a)

KAGA TAXAN 12" RGB

SUPERVISION III with amber/green option £345 (a)

MITSUBISHI XC1404 14" RGB Med Res IBM & BBC Compatible £249 (a)

MONOCHROME MONITORS:

SANYO DM8112CX Hi Res 12" Green Screen £95 (a)

KAGA KX1201G Hi Res 12" Etched Green Screen £99 (a)

KAGA KX1203A Hi Res 12" Etched Amber Screen £105 (a)

PHILIPS BM7502 12" Hi Res Green Screen £75 (a)

PHILIPS BM7522 12" Hi Res Amber Screen £79 (a)

Swivel Base for Kaga Monochrome fitted with Digital Clock £21 (c)

MODEMS

— All modems listed below are BT approved

MIRACLE 3000:

A new range of microprocessor based modems offering up to 2400 baud, full duplex. Features include 'HAYES' protocol compatibility, auto answer, auto dial, speed buffering, printer port, data security option etc. Mains powered.

WS3000 V2123 (V21 & V23) £295 (b)

WS3000 V22 (as above plus 1200 baud full duplex) £495 (b)

WS3000 V22bis2400 (as above plus 2400 baud full duplex) £650 (b)

MIRACLE 2000

A world standard modem covering V21, V23 (Bell 103/113/108 outside UK) and including 75, 300, 600, 1200 baud ratings. Optional Auto dial, auto answer cards, complete control from computer keyboard. WS2000 £125 (b)

Auto Dial Card £30 (d)

Auto Answer Card £30 (d)

SKI Software Control Kit £10 (d)

GEC DATACHAT 1223:

BABT approved modem complying with CCITT V23 standard. Supplied with software £86 (b)

Data Cables for above modems available for most computers.

Serial Test Cable

Serial Cable switchable at both ends allowing pin options to be re-routed or linked at either end using a 10 way switch making it possible to produce almost any cable configuration on site.

Available as M/M or M/F £24.75 (d)

SPECIAL OFFER

2764-25 £2.20

27128-25 £2.75

6264LP-15 £3.75

ATTENTION

All prices in this double page advertisement are subject to change without notice.

ALL PRICES EXCLUDE VAT

Please add carriage 50p unless indicated as follows:

(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

Serial Mini Patch Box

Allows an easy method to reconfigure pin functions without rewiring the cable assembly.

Jumpers can be used and reused. £22 (d)

Serial Mini Test

Monitors RS232C and CCITT V24 Transmissions, indicating status with dual colour LEDs on 7 most significant lines.

Connects in Line. £22.50 (d)

GANG OF EIGHT INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395 (b)

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface.

Softy II £195 (b)

Adaptor for 2764/2564. £25.00 (c)

UV ERASERS

All erasers with built in safety switch and mains indicator.

UV1 B erases up to 6 eproms at a time £47 (c)

UV1 T as above but with a timer £59 (c)

UV1 40 erases up to 14 eproms at a time £71 (b)

UV1 41 as above but with a timer £88 (b)

I.D. CONNECTORS

No of ways	(Speedblock Type)		Edge Conn.
	Header	Receptacle	
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No of Ways

9	15	25	37
---	----	----	----

MALE:

Ang.Pins 120 180 230 350

Solder 60 85 125 170

IDC 175 275 325 -

FEMALE:

St Pin 100 140 210 380

Ang.pins 160 210 275 440

Solder 90 130 195 290

IDC 195 325 375 -

St Hood 90 95 100 120

Screw 130 150 175 -

Lock

TEXT TOOL ZIF

SOCKETS

24-pin	£7.50
28-pin	£9.00
40-pin	£12

EDGE CONNECTORS

2 x 6-way (commodore)	0.1" 0.156"	300p
2 x 10-way	150p	—
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	220p
2 x 25-way	225p	220p
2 x 28-way (Spectrum)	200p	—
2 x 36-way	250p	—
1 x 43-way	280p	—
2 x 22-way	190p	—
2 x 43-way	385p	—
1 x 77-way	400p	500p
2 x 50-way (S100conn)	600p	—

EURO CONNECTORS

DIN 41612	Plug	Socket
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B	400p	—
IDC Skt A + C	400p	—

For 2 x 32 way please specify spacing (A + B, A + C).

MISC CONNS

21 pin Scart Connector: 200p

8 pin Video Connector: 200p

AMPHENOL CONNECTORS

36 way plug	500p	475p
36 way skt	550p	500p
24 way plug	—	—
IEEE	475p	475p
24 way skt	—	—
IEEE	500p	500p
PCB Mtg Skt Ang Pin	—	—
24 way 700p	36way	750p

GENDER CHANGERS

25 way D type

Male to Male £10

Male to Female £10

Female to Female £10

RS 232 JUMPERS

24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female Female	£10.00
24" Male Male	£9.50
24" Male Female	£9.50

RIBBON

(grey/metre)

10-way	40p	34-way	160p
16-way	60p	40-way	180p
20-way	85p	50-way	200p
26-way	120p	64-way	280p

DIL HEADERS

14 pin	40p	IDC	100p
16 pin	50p	—	110p
18 pin	60p	—	—
20 pin	75p	—	—
24 pin	100p	150p	—
28 pin	160p	200p	—
40 pin	200p	225p	—

TECHNOLINE VIEWDATA SYSTEM

Using 'Prestel' type protocols for information and orders phone 01-450 9764. 24 hour service, 7 days a week.

74 SERIES		74LS162A		74S08		4063		85p	
7400	30p	74181	340p	74S10	50p	4066	40p	85p	40p
7401	30p	74182	140p	74S11	50p	4067	230p	230p	230p
7402	30p	74183	180p	74S12	50p	4068	25p	25p	25p
7403	30p	74184	180p	74S13	50p	4069	24p	24p	24p
7404	30p	74185	180p	74S14	50p	4070	24p	24p	24p
7405	30p	74186	180p	74S15	50p	4071	24p	24p	24p
7489	30p	74270	180p	74S99	50p	4155	24p	24p	24p
7490	30p	74271	180p	74S00	24p	74S273	125p	74S273	125p
7491	30p	74272	180p	74S01	24p	74S274	125p	74S274	125p
7492	30p	74273	180p	74S02	24p	74S275	125p	74S275	125p
7493	30p	74274	180p	74S03	24p	74S276	125p	74S276	125p
7494	30p	74275	180p	74S04	24p	74S277	125p	74S277	125p
7495	30p	74276	180p	74S05	24p	74S278	125p	74S278	125p
7496	30p	74277	180p	74S06	24p	74S279	125p	74S279	125p
7497	30p	74278	180p	74S07	24p	74S280	125p	74S280	125p
7498	30p	74279	180p	74S08	24p	74S281	125p	74S281	125p
7499	30p	74280	180p	74S09	24p	74S282	125p	74S282	125p
7500	30p	74281	180p	74S10	24p	74S283	125p	74S283	125p

LINEAR ICs

COMPUTER COMPONENTS

CPU		EPROMs		CART CONTROLLER		SUPPORT DEVICES		INTERFACE ICs		ROMS/PROMS		DISC CONTROLLER ICs	
1802CE	650p	2516-5v	350p	CR2502	£18	2651	£12	AD5863	775p	2812	£12	DM8311	900p
2650A	1050p	2516-3v	350p	CR2507	£12	3242	800p	AD5864	775p	2816	£12	DM8312	900p
6502	450p	2516-1.5v	350p	CR2508	£12	3245	800p	AD5865	775p	2817	£12	DM8313	900p
6502A	450p	2516-5v	350p	CR2509	£12	6520	300p	AD5866	775p	2818	£12	DM8314	900p
6502B	800p	2516-3v	350p	CR2510	£12	6522	350p	AD5867	775p	2819	£12	DM8315	900p
6800	250p	2516-1.5v	350p	CR2511	£12	6524	480p	AD5868	775p	2820	£12	DM8316	900p
6800	300p	2516-5v	350p	CR2512	£12	6525	550p	AD5869	775p	2821	£12	DM8317	900p
6802	300p	2516-3v	350p	CR2513	£12	6526	650p	AD5870	775p	2822	£12	DM8318	900p
6803-2	£12	2516-1.5v	350p	CR2514	£12	6527	750p	AD5871	775p	2823	£12	DM8319	900p
6809	650p	2516-5v	350p	CR2515	£12	6528	850p	AD5872	775p	2824	£12	DM8320	900p
6809E	£12	2516-3v	350p	CR2516	£12	6529	950p	AD5873	775p	2825	£12	DM8321	900p
6809E	£12	2516-1.5v	350p	CR2517	£12	6530	1050p	AD5874	775p	2826	£12	DM8322	900p
6800-LB	£36	2516-5v	350p	CR2518	£12	6531	1150p	AD5875	775p	2827	£12	DM8323	900p
8035	350p	2516-3v	350p	CR2519	£12	6532	1250p	AD5876	775p	2828	£12	DM8324	900p
8039	420p	2516-1.5v	350p	CR2520	£12	6533	1350p	AD5877	775p	2829	£12	DM8325	900p
8039	700p	2516-5v	350p	CR2521	£12	6534	1450p	AD5878	775p	2830	£12	DM8326	900p
8080A	420p	2516-3v	350p	CR2522	£12	6535	1550p	AD5879	775p	2831	£12	DM8327	900p
8085A	750p	2516-1.5v	350p	CR2523	£12	6536	1650						

READ/WRITE

Pot Shop

Dear Sir,

With reference to K.G. Vergis' letter 'Scope for Improvement' (Read/Write, ETI March 1986).

Neosid Small Orders, PO Box 86, Welwyn Garden City, stopped trading in 1983. The PO Box number address was discontinued when further communications became a matter for the postal authorities to return to sender.

Whilst I sympathise with your correspondent's dilemma, I regret there is nothing I can do to assist at this stage as regards return of the postal order. However, if you will furnish K.G. Vergis' full address we will be pleased to send an ET30 pot core with our compliments.

Would-be purchasers should in the first instance write to me and I will arrange supplies.

M.J. Bass

Neosid Limited.

We were delighted to receive the above letter and have passed on K.G. Vergis' address as requested. We have also spoken to Neosid to confirm the offer made at the end of the letter. Mr Bass tells us that although his company no longer has a small orders department they will be happy to deal with individual orders for the ET30. Readers who require this pot core for the ETI Oscilloscope should telephone Neosid on 0707 - 325011 and ask for the sales desk. — Ed.

Hi-fi Praise

Dear Sir,

I'd like to react to all the complaints about the John Linsley Hood Audio Design Amplifier by saying 'Stick with it — it is well worth the effort.' I have built up the amplifier and preamplifier myself and have nothing but praise for the design.

Regarding the difficulty with components, the small signal MOSFET type VN1210M is manufactured by Siliconix. Readers outside the UK should try their agents (Electrolink in South Africa).

Finally, I wish to congratulate ETI. The audio design series was well presented, easy to follow, and had few errors.

I thank you.

Yours faithfully,
Hugh Hacking,
Johannesburg,
South Africa.

Simply Not Good Enough

Dear Sir,

I have been a regular reader of ETI since it first appeared in the early seventies. However, I feel that the quality of the projects over the past year leaves a lot to be desired. Many have either been esoteric projects at extortionate cost or re-hashes of past designs. I feel that some simpler projects and new ideas are sorely needed. To this end, I enclose a list of items I would like to see in the pages of ETI:

- 1) Digital recording of audio signals in the picture circuits of a VCR for high quality.
- 2) In car graphic equaliser/power booster/quadraphonic simulator.
- 3) Video enhancer and booster.
- 4) Car exhaust gas analyser.
- 5) Home computer based engine fault diagnostic aid.
- 6) Home computer to VCR Interface.
- 7) Extension to the above to allow control down a telephone line.
- 8) Use of a home computer for sub-titling on video recordings and for superimposition of messages and time on the picture.
- 9) Circuits to allow decoding of VCR composite Video to RGB to allow direct coupling to an RGB equipped TV.
- 10) Switch, amplifier and distribution centre for TV/VCR/aerials.
- 11) Interface circuits and software for widely available surplus hard disk drives.
- 12) Projects for the Amstrad computer range, for example, interfacing a standard 5¼" drive to the CPC6128.
- 13) Comprehensive central

heating controller, possibly using a ZX81.

14) Digital audio mixer/sound processor circuits.

15) Touch screen system for a home computer using a network of infra-red LEDs and diodes surrounding the screen.

F.R. Felgate,
Camberley,
Surrey.

Thank you for your suggestions for simple (?) projects. We will bear them in mind. — Ed.

PROMises, PROMises ...

Dear Sir,

Some time ago I constructed an EPROM programmer from a design published in the August and September 1984 issues of ETI. As it happened, I had to modify the front end to use it with my BBC micro. Much of the software had to be re-written, but after a lot of midnight oil it now all works.

I was highly delighted when in the May 1985 issue you published an upgrade to the board. I sent off and received the PC board and duly made up the modification. Then, in the July 1985 issue it was mentioned that a version for the BEEB was about to be produced, with the driving software in Sideways ROM. Since then I have seen nothing more on the subject. I have held off modifying my working board to include the update so as not to break down the programmer for a second time. Can you please let me know if this article will appear?

Yours faithfully,
M.D.J. Foreman,
Frenchay,
Bristol.

We are still expecting to publish a design for an EPROM programmer to use with the BBC computer, but at the moment it is not possible to say when it will appear. Our apologies to all frustrated BEEB owners but we can assure you that it will be worth waiting for. — Ed.


AUNTIE STATIC'S PROBLEM CORNER

Dear Auntie,

I have built a flashgun slave trigger unit, but I can't get the circuit to work. I have tested the circuit with my multi-meter, but the results are so spurious that I cannot pinpoint the error. I am now reaching desperation point over what should be such a simple project (this is my fourth attempt!) I have sent my circuit, so will you please have a look at it and tell me what I am doing wrong.

Yoursh faithfully,
Gerry Barlow B.Sc.,
Colwyn Bay,
Clwyd.

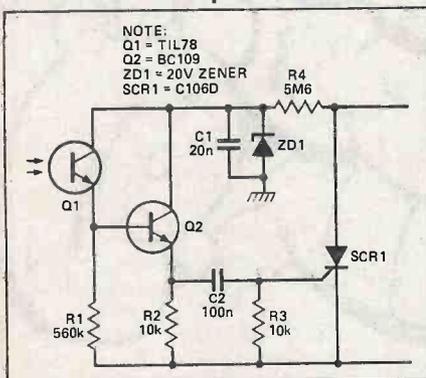Before I begin, I must point out that in general we do not encourage readers to send us circuits for modification or repair. If we started doing it regularly, we'd have no time to design any projects! We made an exception in Mr. Barlow's case, but this is not intended to set a precedent.



The circuit, as it arrived, is shown above. It derives its power supply from the trigger input of the flash gun — on the slave flash unit sent in by Mr. Barlow about 150V was present under open circuit conditions. This voltage comes from a very high source resistance and a load of 3M3 is enough to reduce the voltage to less than half and also to prevent the gun from triggering — hence the 5M6 resistor in the trigger circuit. The available current would not be enough to fire SCR1, which requires 200µA gate current, so C1 is included as a 'reservoir'. ZD1 prevents the voltage across C1 from rising above 20V. Q1 has a high resistance in darkness and a

low resistance in light, so the idea of the circuit is that the flash from the master gun is picked up by Q1, causing a sudden rise in voltage at the top of R1 which fires the SCR via Q2 and C2, in turn triggering the slave flash gun. This is the theory, anyway.

Naturally, Mr Barlow's first instinct was to get out his multi-meter and try to trace the fault. Unfortunately, a standard 20k per volt multi-meter on the 20V range will have a resistance of 400k. This resistance is quite low enough to discharge C1 to a greater or lesser extent whenever any readings are made on the circuit. The results will bear very little relation to the actual operating voltages, and will not be directly comparable with each other since C1 will discharge by varying amounts depending on where the readings are made. The way round this is to connect a temporary voltage supply of, say, 18V across C1. Not 20V, by the way, as the zener will then be on the point of conduction, with possibly disastrous results. You could, of course, use a supply of about 25V and a series resistor, but unless you suspect that ZD1 is not working, which is quite easy to test anyway, why bother? You will still have to take the meter resistance into account when measuring the voltage across R1, but at least the readings will now make some kind of sense.

With the 18V test supply connected, the voltage across R1 was checked with various light levels. Two things would make the value of R1 unsuitable: if it was too low, very intense lighting would be required to raise the voltage across it by an appreciable amount, and if it was too high, normal room lighting would take the voltage across it almost to the supply rail level and leave little margin for a voltage rise when the master flash goes off. In fact, the value of 560k is fine in both respects and was not changed.

Although the value of R2 was perfectly good with the 18V supply connected, it was too low for reliable operation when powered by the flash gun. As the slave flash

would not necessarily be used in pitch darkness, allowance must be made for the fact that there will be some voltage developed across R2 from background lighting falling on Q1. A quick calculation shows that a drop of about 250mV across R2 would be enough to sink all the current from R4, discharge C1, and prevent the circuit from working at all.

Are there any disadvantages in raising the value of R2? As its only purpose is to provide a discharge path for C2 after the trigger has operated, the main requirement is that the time constant of R2 + R3 and C2 should be small enough to allow a reasonably quick recovery. The value could be raised to several megohms from this point of view so there is no need to worry. The final value settled on was 100k, which is quite adequate to cure the discharge problem and leaves plenty of room for increasing the values of C2 and R3.

If you feel that R2 has some other function besides discharging C2 — perhaps you think in some vague way that emitter followers need emitter resistors — I suggest that you try removing R2 from the circuit. Make sure that the 'left hand' plate of C2 is discharged to ground, then try using the trigger. You'll find it will work perfectly well once but won't fire a second time. To make it work again, you will have to discharge C2 to ground (which is the function of R2, as I have said ...)

C1 must store enough charge to operate the circuit and maintain conduction in the SCR during the entire triggering period. The value of C1 was a little low to do this reliably and the value was raised to 100n. This still gives a charge time via R4 which is less than the time Mr Barlow's flash gun needs to recharge.

To test the values of C2 and R3 I simply attempted to trigger the flash, with the 18V supply in place, by shorting the collector and emitter of Q2. Once again, triggering was unreliable with the original values and the solution was to increase C2 and R3 to 470n and 100k respectively, bearing in mind the recovery time of C2 as already mentioned. R3 could have been replaced by a 200k preset as a 'sensitivity' control.

The final component values for the circuit were: R1 560k, R2 100k, R3 100k, R4 5M6, C1 100n, C2 470. — Auntie.

FIBRE OPTICS AND LASERS

In this, the first of a series of articles, Roger Bond takes a close look at the technologies that are set to revolutionise our communications systems.

Head the one about the Englishman, the American and the Japanese? They are all racing each other to get higher and higher bit rates down optical fibre.

In 1982 British Telecom engineers at Martlesham, near Ipswich, showed how an optical signal could be sent at 140 Mbit/s over a distance of 100 km without repeaters. A bit rate of 140 Mbit/s is sufficient to handle a 625 line television signal or 1920 telephone circuits. In spring 1983 the Japanese transmitted at 445 Mbit/s over 134 km without a repeater and with an error rate of only $1 \text{ in } 10^9$. Then in September 1983 the US Bell Laboratories transmitted at 420 Mbit/s over 161 km with an error rate of only $5 \text{ in } 10^9$. At these high information rates it is possible to transmit thirty volumes of the Encyclopedia Britannica in one second, and at the above error rates, one letter of the alphabet might be wrong for every five encyclopedia sets.

Why the sudden interest in optical communications? An optical ray has the advantage of wide bandwidth and immunity from electrical noise. For example, the maximum bandwidth obtained from operating on a carrier of 10 kHz is 10 kHz for each sideband. The maximum bandwidth obtainable from a carrier of 10^{14} Hz is 10^{14} Hz for each sideband, and it is in this frequency range (the infra red) that lasers operate.

Some Light On The Laser

Laser stands for light amplification by the stimulated emission of radiation. Light travels in discrete bundles or photons, and light falling on photosensitive materials will stimulate electrons. The opposite is also true. If electrons are sufficiently stimulated, light will be emitted.

Figure 2a shows an atom consisting of a positive nucleus and a negative electron circling the nucleus. If

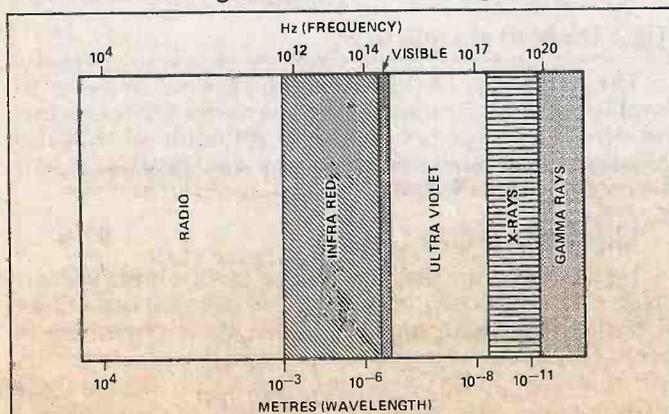


Fig. 1 A portion of the electromagnetic spectrum.

energy is supplied to the electron it will revolve around the nucleus at a greater distance from the centre. If the energy is sufficiently great, the electron could escape from the nucleus.

When atoms are close together as in a solid, the energy levels become energy bands (Fig. 2b). At absolute zero temperature, the valency band would be filled and there would be no electrons in the conduction band.

The valency band determines which group of the periodic table an element belongs to. Between the valency and conduction bands is a forbidden gap. Electrons cannot possess energies within this gap. Therefore, in giving up its energy and dropping across this gap, an electron causes light to be emitted of the same wavelength as the gap. For communications over optical fibre this wavelength is $0.85 \mu\text{m}$ or $1.3 \mu\text{m}$.

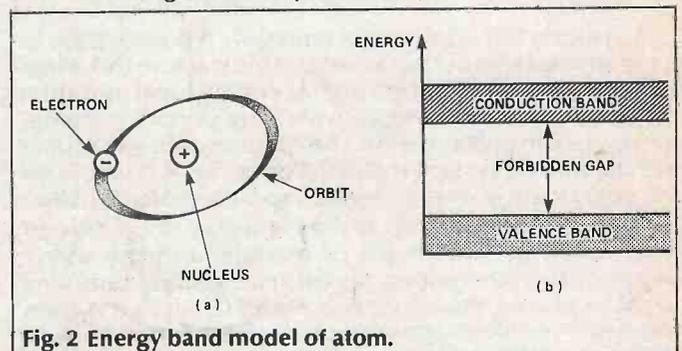


Fig. 2 Energy band model of atom.

In lasers, the stimulation is achieved by a process known as pumping, in which electrons are deliberately raised to higher energy levels. The normal distribution of electrons is shown in Fig. 3a, and it will be seen that there are fewer electrons in outer orbits than there are in inner orbits around an atom.

If such an atom is stimulated using an electromagnetic signal of suitable wavelength, electrons will

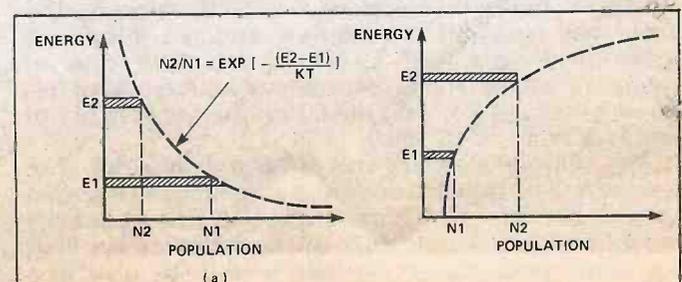


Fig. 3 Electron distribution, normally and after population inversion.

move to the outer orbits until there are more of them there than in the inner orbits, a situation known as a population inversion (Fig. 3b). The electrons will not be stable in this state and will fall back to their previous energy levels within a few nanoseconds producing a spontaneous emission of light. As a result, this system produces pulsed rather than continuous emission.

Although pulsed lasers have their applications, most of the useful lasers emit coherent light. Coherent light can be described as being of the same frequency and travelling in the same direction, parallel and in phase. That is why lasers can burn holes in metal.

As examples of incoherent radiation consider the sun or a light bulb. Various frequencies at random intervals are emitted. The power obtained from focusing the sun's rays is well known to anyone who has tried to burn a hole in paper using a magnifying glass. Not only is a laser prefocused (parallel) but it continues to remain so. For instance, a spot light may diverge by 2° whereas a laser diverges by only a few seconds of arc. That is one reason for using a laser to communicate with say, astronauts on the moon. Light from a spotlight would be completely dissipated over the distance.

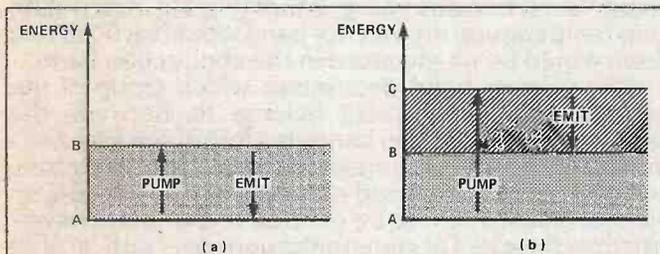


Fig. 4 Pulsed and metastable electron pumping.

To obtain this continuous emission, it is necessary to achieve what is known as a metastable state. In this, electrons are raised to a much higher energy level and then remain there for a comparatively long period, microseconds or even milliseconds. The difference between this and the pulsed system is illustrated in Fig. 4. If electrons will not remain at energy level C, spontaneous emission will take place as before. If they will stay at C (a factor determined by the choice of material and the wavelength of the stimulating signal), continuous pumping can take place between levels A and C. All that is then required to achieve continuous emission is to stimulate the atoms with another signal whose wavelength is equivalent to the gap between B and C. In this way, a continuous population inversion will be maintained between these two levels.

Masers

Before going on to look at the different types of lasers, we will consider briefly the device which preceded them, the maser.

Maser stands for microwave amplification by the stimulated emission of radiation, and the difference between masers and lasers is therefore one of frequency. While the former operate at microwave frequencies (about 10^{12} Hz) the latter operate at light frequencies (around 10^{14} Hz).

The ammonia maser was invented in 1954. The designers were trying to design an amplifier, but it ended up as an oscillator which worked at only one frequency and refused to be tuned even over a narrow range. That was when the designers decided it could be used as a clock.

The world's best clocks at that time accumulated errors of one second in ten years but the ammonia maser

accumulated an error of only one second over 10,000 years. Today, caesium and rubidium provide even more accurate clocks.

Masers were used in satellite communication and radio astronomy where a weak signal had to be detected in the presence of noise. The maser is ideal for this since it generates little noise itself compared to klystrons and travelling wave tubes. It saturates at power levels above 10^{-5} watts. In 1960 the Echo I satellite was used merely as a reflector to bounce the signal. 10kW was beamed up at it and only 10^{-14} was reflected back. Later, Telstar amplified the signal before transmitting it back to earth, but even then the received signal was only 10^{-13} watt.

Molecular vibration stops at absolute zero, so the maser is operated at 1.5°K (-271.5°C) by immersing it in a helium bath. The maser used at the satellite station in Cornwall was ruby with 0.05% chromium. This front end amplifier has largely been replaced by parametric amplifiers, but that is a different story.

Crystal Lasers

The ruby laser was the first to be operated successfully by Maiman in 1960. Ruby is aluminium oxide Al_2O_3 with some of the aluminium atoms replaced by 0.05% chromium for effective lasing.

The ruby crystal was a rod 10 cm long and 1 cm in diameter (Fig. 5). Pumping and hence population inversion was obtained by means of an xenon flash tube spiralled around the crystal. A few kilovolts was discharged through the tube from a bank of capacitors of around 100 microfarads.

This flash energy was in the green and blue end of the colour spectrum which is the absorption band for ruby. Provided sufficient energy was supplied, the ruby crystal emitted its characteristic red in the visible part of the colour spectrum, at a wavelength of 10^{-8} cm.

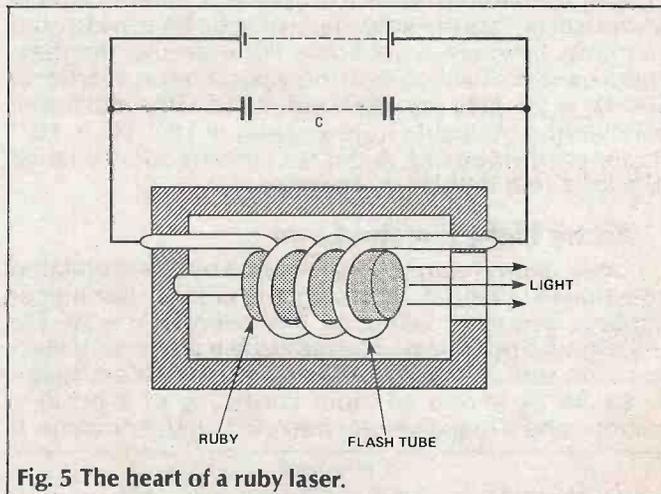


Fig. 5 The heart of a ruby laser.

The end faces of the rod were silvered in order to amplify the light. One end acted as a perfect reflector but the other end was only a partial reflector so that the radiation could burst through. Ruby was ideal because it is easy to cut and shape.

Liquid And Gas Lasers

Liquid lasers employ a group of compounds known as the rare earth chelates which give out vast quantities of fluorescent light. Unfortunately, their chemistry is rather complicated and quite outside the scope of this article, so we can do little more than acknowledge their existence and pass rapidly on to consider gas lasers.

The gas laser was invented in 1961 and the prototype

used a mixture of helium and neon in the ratio 5:1 (Fig. 6). Helium and neon were chosen because they have similar energy levels, and population inversion can be obtained by energy transfer from one to the other. The tube was 1 metre long and of 1.5 cm internal diameter. Mirrors were mounted on the inside ends and were capable of adjustment so that they were parallel to each other.

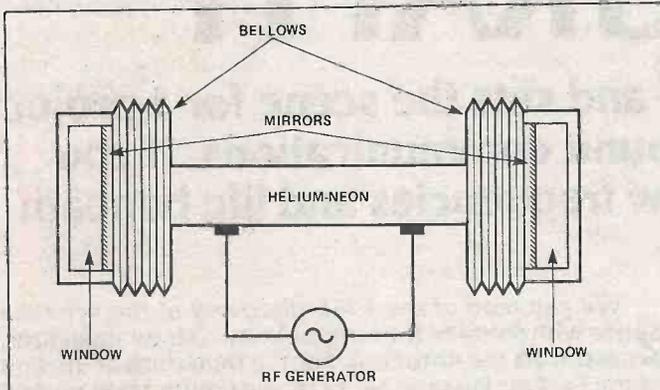


Fig. 6 Helium-neon laser.

The object of using mirrors is to amplify the light by bouncing it back and forth. Nothing could be simpler, it's all done with mirrors and since we are dealing with light it seems logical to use mirrors. However since the gas is at low pressure, the mirrors have to be adjusted in a virtual vacuum which is not easy. This is now overcome by using external spherical mirrors.

Carbon dioxide is also used in gas lasers and in general, gas lasers are more directional and monochromatic than solids like ruby. Monochromatic means approximating to a single frequency, and this is possible because gases do not have the physical imperfections of solids. Gas lasers can also emit a continuous beam at room temperatures without the need for cooling.

Semiconductor Lasers And LEDs

So far we have only dealt with laser light sources. In considering semiconductor lasers, however, it is convenient to look also at LEDs since they share the same technological base and have important applications in fibre optic communications.

The main difference between light emitting diodes and lasers is that LEDs emit spontaneously whereas lasers have to be stimulated. This can be seen in the characteristic curves of Fig. 7.

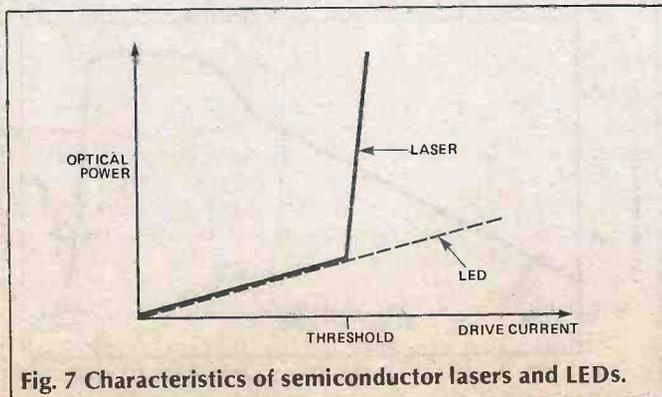


Fig. 7 Characteristics of semiconductor lasers and LEDs.

Stimulated emission is of higher fidelity than spontaneous emission because photons stimulate other photons of the same wavelength. Hence the linewidth of lasers is 1 nm (10^{-9} m) whereas the linewidth of LEDs is

about 20nm. This means that the useful bandwidth of LEDs is limited since sidebands are produced which overlap. For the widest possible bandwidth, a single pure frequency is required.

The output of a LED is linear and can therefore be used to transmit an analogue signal. The laser curve rises slowly until a breakpoint or threshold is reached, then the emission takes off. Because of the shape of the laser curve, it is more suitable for transmitting digital signals in which the light is switched on and off.

LEDs operate in the 0.85 μm to 0.95 μm range, the infra-red. Figure 8 shows a high radiance light emitting diode (HRLED), also called a Burrus diode. The difference between this and an ordinary LED is that a well is etched in the top. The well is usually 50 μm in diameter and a 50 μm optical fibre fits snugly into it, reducing coupling losses.

Edge light emitting diodes (ELEDs) are even more efficient than Burrus diodes. The Burrus diode uses a homojunction, a construction in which several layers of gallium arsenide (GaAs) with opposite charges are sandwiched together. ELEDs use heterojunctions, which have alternate layers of gallium arsenide and gallium aluminium arsenide. Figure 9 shows a double heterojunction.

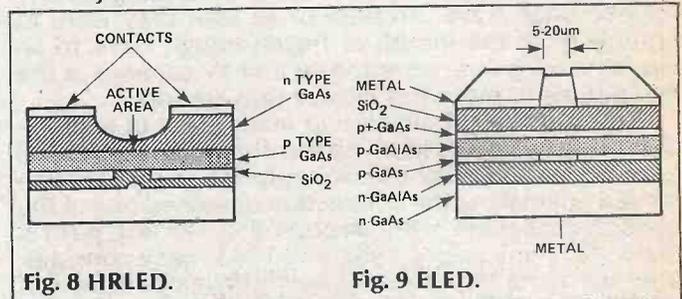


Fig. 8 HRLED.

Fig. 9 ELED.

The important feature is the stripe etched on the top which helps concentrate the emission from a very small area. The reflex index of the stripe needs to be uniform so that the output characteristic is a straight line.

The first semiconductor lasers were homojunctions, then heterojunctions were used and now double heterojunctions. The design is similar to that of ELEDs, but there is one big difference. The stripe in the ELED does not extend the whole length of the chip whereas it does in the laser.

The effect of having a stripe over the full length is to provide feedback and hence laser action. If the stripe does not extend to the end, the region without a stripe acts as an absorption region and light is absorbed here. Therefore there is no feedback and no lasing. The threshold current is the minimum current required to produce lasing and both the geometry of the stripe (5 to 20 μm) and the double heterojunctions help to reduce the required current.

The laser chips are around 400 μm square with perpendicular ends as near perfect as possible and silvered as with all lasers. When a photon is emitted it reflects off the mirrored surface and, if it meets an electron about to emit a photon, stimulated emission takes place releasing more photons.

The wavelength of the emission can be altered slightly by changing the concentration of aluminium. The active region is below the stripe and contains 5% aluminium. The other regions contain 35% aluminium and help the device to expand without cracking as heat is generated. The heat sinks are copper, soldered with indium. Typical outputs are around 5 mW and a laser's life at room temperature is about 10 years.

ETI

THE ETI TROGLOGRAPH

Mike Bedford gets down real low and sets the scene for a project using VLF for surface-to-underground communications. If you want to know more about very low frequencies and life beneath the Pennines, read on ...

A loud cheer rang through the night air as the long awaited words came over the Molephone — the connection had been made. It was Saturday 28th May 1983 and the words in question came from a group of potholers 300 feet below informing the surface party that they had made the link up between Gaping Gill and Ingleborough Cave. An hour or so later they were to emerge from the mouth of Ingleborough Cave to an overwhelming array of reporters and TV cameras as the first people to make this elusive through trip.

This was the culmination of many years of exploration in the two caves in which the distance between the known extremities of the two systems gradually diminished but making the connection remained one of the greatest challenges in British potholing. The final push at making the link during 1982 and 1983 made considerable use of the Molephone, a newly developed piece of equipment allowing voice communication and radio location through solid rock.

This historic through trip has been named Dr Mackin's Delivery by the Bradford Pothole Club in recognition of the assistance given by the developer of the Molephone, and without which the feat would have been virtually impossible.

Cave Law

Gaping Gill is situated on the lower slopes of Ingleborough in the Yorkshire Dales National Park and must be considered one of the most famous potholes in Britain. The first descent of this 340 foot shaft was made in 1895 by the Frenchman Edward Martel who reported that no obvious passages radiated from the huge cavern which he found.

Throughout this century the cave system has attracted numerous potholers who proved that in marked contrast to Martel's initial reports, the main chamber is the hub of a sizeable array of passages and chambers totalling 7½ miles in length (excluding Ingleborough Cave) and ranking among the largest systems in the country.

Gaping Gill features prominently in the annals of caving folklore, being a cave of superlatives — the deepest shaft in Britain, the tallest waterfall, the largest cave chamber and also the second largest in the vast Mud Hall. Tales abound of Eric Hensler's solo exploration of the hundreds of yards of 18-inch high passages which now bear his name. In 1953, crowds fearing for his sanity eagerly awaited the return of Geoff Workman after his 14-day lone encampment in Sand Cavern aimed at discovering the effects on the human body of such a period cut off from our natural clock, the sun.

We can read of the 1968 discovery of the Whitsun Series with some of the longest known straw stalactites, accessed via the notorious 'Font', a mud duck at the end of the Far East Passage. More recently numerous people have sampled the grandeur of the main chamber as public winch meets have been arranged at Spring and August Bank Holidays during which members of the public could be transported down the massive shaft in a bosun's chair.

A mile away in the wooded valley known as Trough Gill is the large mouth of Ingleborough Cave. Established as a show cave as long ago as 1838, it is a major tourist attraction, drawing many visitors each year. The cave also has much to interest the potholer in the areas beyond the limit of the show cave, these flooded passages being the domain of cave divers using aqualung equipment.

For many years it had been realised that the stream thundering down the 340-foot waterfall into Gaping Gill was the same one which emerged some time later out of the mouth of Ingleborough Cave. The fact that water could find a way through impelled the search for a link between the two caves through which a person could pass.

Later discoveries in Gaping Gill, the Far Country and Far Waters which were first explored during 1970, did appear to come very close to the Radaghost's Revenge area of Ingleborough Cave, discovered by diving in 1976. The way through would almost certainly require

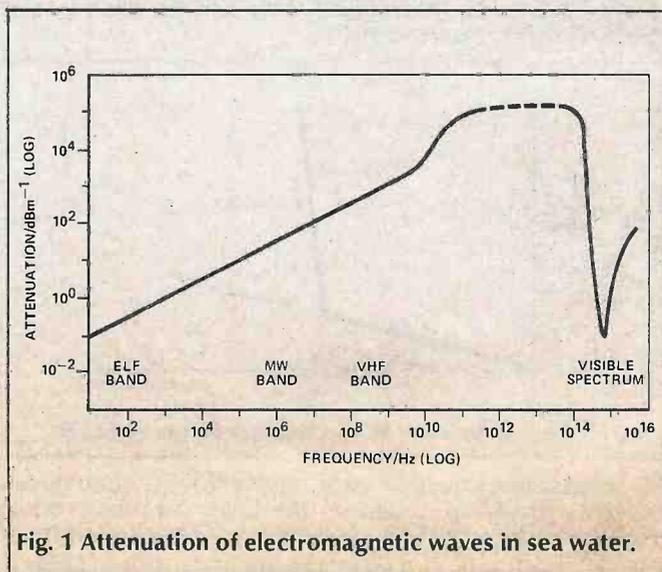


Fig. 1 Attenuation of electromagnetic waves in sea water.

digging and, although both caves were reasonably well surveyed, it was very difficult to tell exactly which points in the two systems were the areas to concentrate on.

Technology To The Rescue

In the early 1980s, the Molephone helped locate a point in Radaghast's Revenge that was found to be so close to the Far Waters of the Gaping Gill system that the surface team found it hard to believe that the link had not been made! The remaining few metres did not give up without a struggle, however.

Numerous digging parties made the long and laborious journey from Gaping Gill to the Far Waters passing through the so called Wallows in which the airspace was sometimes as little as one inch. By early 1983, sufficient progress had been made to start making plans for the through trip.

Planned with the precision of a military operation, the expedition involved a party on the surface, one entering Ingleborough Cave and another party entering Gaping Gill accompanied by a two man BBC film crew making a TV documentary on the link-up. Each party was in communication with the others by use of Molephones, the surface party tracking the Gaping Gill group across the moors and the Ingleborough Cave party being called into the cave once the other team were close to the connection area.

Even this final assault wasn't without its problems. The Gaping Gill party of thirteen took over 1½ hours to move themselves and their equipment through the final 20 feet from where Geoff Yeadon and Geoff Crossley were to dive through the sump pool into Ingleborough Cave.

Geoff's account of the through trip¹ notes that the conditions of the final dig were appalling — extremely wet, mud-logged, cold, tight and loose clay (you name it, the connection certainly seems to have it!). All the same,

Dr. Mackin's Delivery is now history.²

Way Down Low

It will come as no surprise to most people that electromagnetic radiation is greatly attenuated by solid rock. In actual fact, due to its greater conductivity, sea water is even more difficult to penetrate than rock, a fact which makes communication with submarines a significant problem. Since submarine communication is of military importance, a great deal of research has been carried out in this area and Fig. 1 shows a graph of attenuation through sea water against frequency.³


It will be noticed that the degree of attenuation increases with frequency except for a small band at the high frequency end which corresponds to the visible spectrum (light). To get some idea of the severe limitations imposed at normal radio frequencies, consider a frequency of 1MHz which falls in the medium wave band and accordingly wouldn't normally be considered a particularly high frequency.

The attenuation here is 30dB per metre — in other words, the power level is reduced by a factor of 1024 over this distance. After two metres at this degree of attenuation, the signal remaining from a high power 100kW broadcast station would be only a tenth of a watt. As a result of this situation, submarine communication has to take place in the ELF (30–300Hz) portion of the electromagnetic spectrum.

A concept often used in submarine/subsurface communications is that of skin depth, a measure of how far signals will penetrate below the surface. The skin depth is given by the formula:

$$\delta = (1/\pi f \sigma \mu)^{1/2}$$

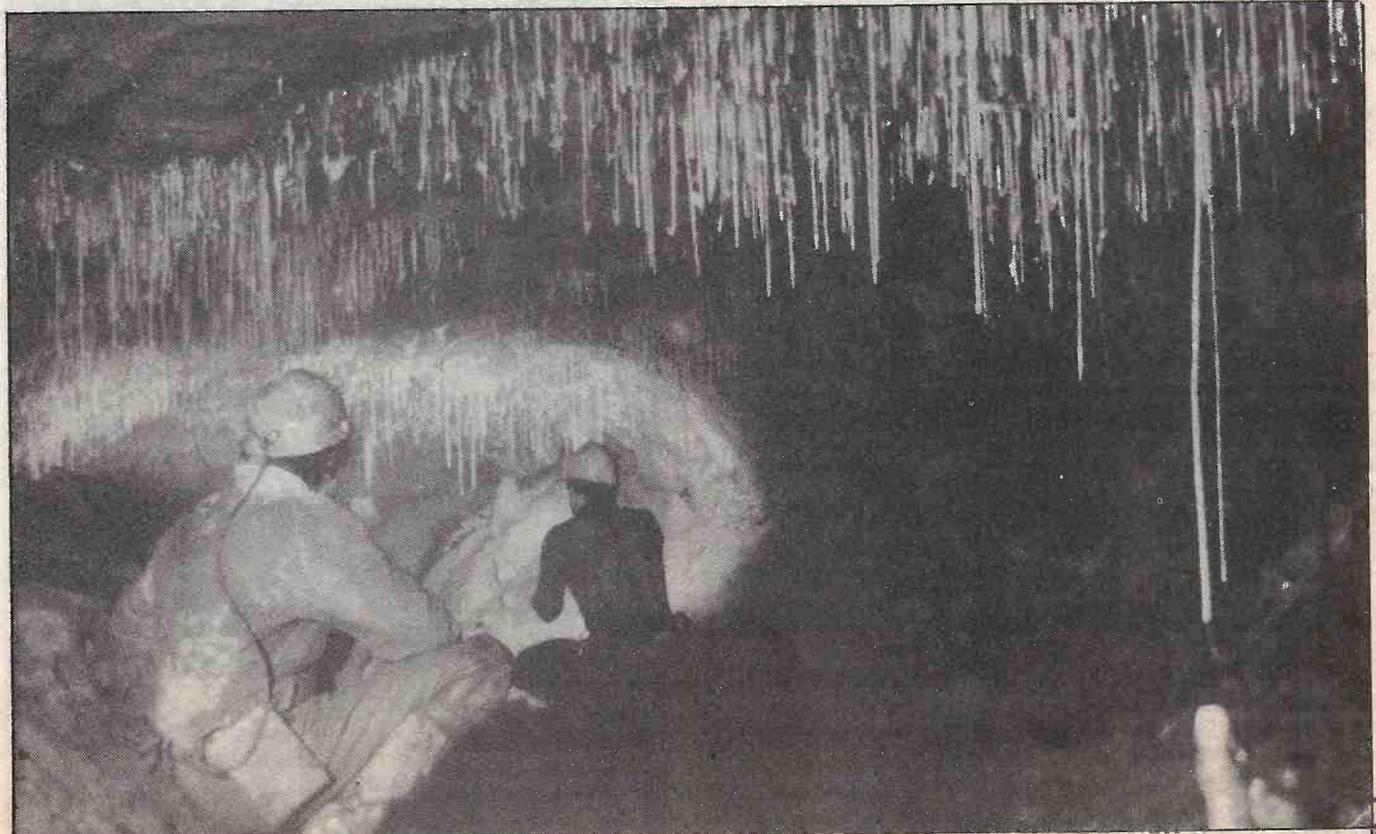where f is the frequency in Hertz, σ is the electrical conductivity of the medium in S/m and μ is the magnetic



Travelling by underground

permeability which is reasonably constant for media such as rock and sea water.

Since the conductivity of rock is generally in the region 10^{-1} to 10^{-3} S/m compared to about 4S/m for sea water it is easy to see that considerably greater ranges can be achieved through rock at the same frequency. Alternatively, acceptable distances can be obtained at a higher frequency than those used for submarines. Since the rate of data transmission is limited by the bandwidth and hence the carrier frequency it is clearly advisable to use the highest frequency possible.

For caving use, where depths of much more than 400 feet are rarely met in Britain and where the rock is limestone (not a particularly conductive substance) a frequency of about 3kHz is quite suitable for CW and direction finding and even an order of magnitude higher could be used if there was a requirement for speech communication.

Nevertheless, 3kHz is a very low frequency (the VLF band is officially designated as 3kHz to 30kHz) with a correspondingly long wavelength. The generally accepted standard aerial, against which the gains of more sophisticated aerials are measured, is the half-wave dipole — such an aerial would be 50km long for 3kHz and even a quarter wave aerial would be 25km or 16 miles in length.

Clearly such an aerial is not a feasible proposition in a cave! For submarine communications, aerials many miles in length are used but since even this length is small in terms of wavelengths, extremely high power levels are used to compensate for the inefficiency of the aerial.

Field Strength

Electromagnetic radiation consists of two elements — the electric field and the magnetic field. Normally, when we refer to radio waves, it is the electric field which we really mean and it is these waves which require aerials of the order of a quarter of half wavelength in order to propagate. A magnetic wave, on the other hand, can be radiated from much smaller aerials, a current carrying multi-turn loop being a classic example.

As is the case for electric waves, the magnetic field will also pass through conductive materials if the frequency of the radiation is sufficiently low. The disadvantage of communicating by magnetic waves is that field strength decreases with the cube of distance compared with the electric waves which diminish with the square of distance. This means that long distances are out of the question for magnetic wave communications and is the reason why only the electric waves are usually considered as radio.

For cave communication, long distances are not required and the inverse cube law does not present a great problem. Magnetic field communication is sometimes referred to as inductive communication as its operation can be compared to that of a transformer with a very large separation between the primary and secondary windings.

It will probably have been noticed that the frequencies mentioned are within the band normally referred to as audio. Before going any further, let's clear up any confusion which may be caused by this.

Even though we may use audio frequencies, it is not correct to assume that the communications could be heard by someone close to the aerial. This is because the human ear cannot receive electromagnetic radiation. The ear is sensitive to mechanical vibrations of the air (normally called sound) and audio frequencies occupy just the range over which the ear might respond to air vibrations. ELF and low end VLF communications could

therefore be said to use radio waves at audio frequencies.

Direction Finding

The Gaping Gill link-up made extensive use of the directional properties of magnetic waves to accurately map the appropriate areas of the caves both horizontally and vertically. Figure 2 shows the shape of the magnetic field generated by a current carrying loop.


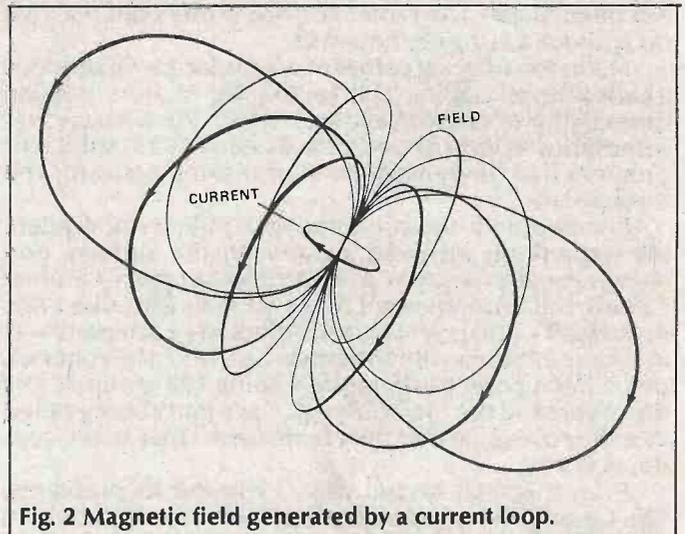


Fig. 2 Magnetic field generated by a current loop.

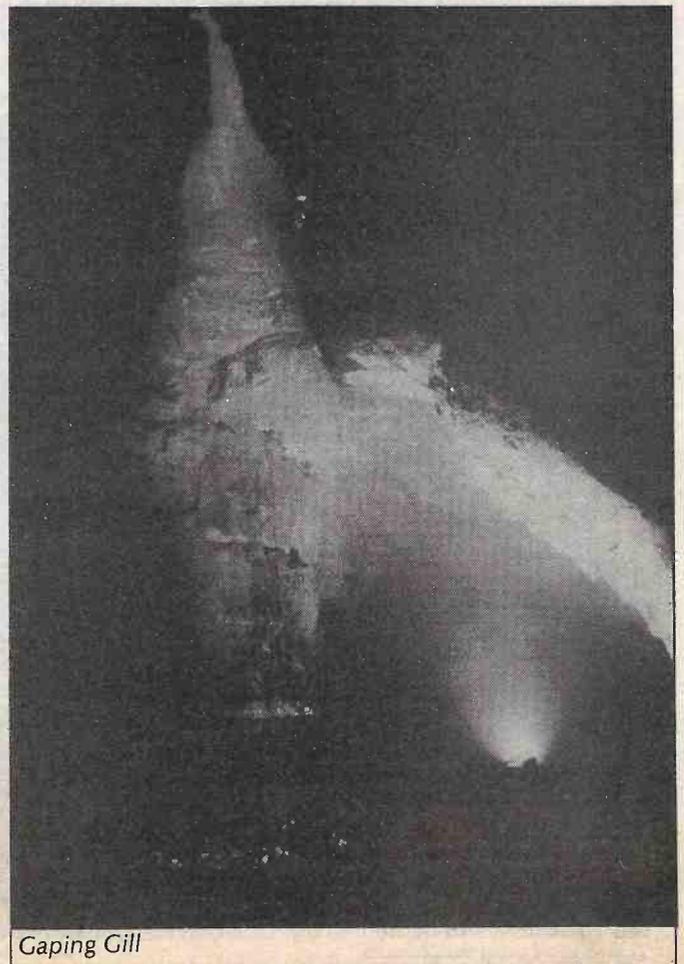In contrast to the electric field of normal radio communications, which radiates in straight lines from the aerial, the magnetic field is made up of closed elliptical



Gaping Gill



The author takes the Troglograph for a swim.

loops. As a result, direction finding is not as straightforward as the normal triangulation method used in radio location.

The method used in cave surveying involves taking a transmitter to the point of interest in the cave and switching on at a pre-determined time, having first ensured that the aerial coil is perfectly horizontal. The surface party on first receiving these signals will determine firstly the horizontal location and then the depth. If the field pattern illustrated in Fig. 2 were to be viewed from above (as will be the case with a transmitter in a cave), the lines of flux will appear to be straight lines radiating from the centre of the coil. This means that the

point immediately above the transmitter (referred to as ground zero) can readily be found by triangulation.

Maximum signal strength is received when the lines of flux pass through the plane of the receiving coil, but in practice it will be found to be easier to detect nulls than peaks. By obtaining three nulls, a first approximation of ground zero can be obtained, a more accurate result then being found by repeating the procedure closer to this first point. Having found ground zero, the depth can then be determined.

Figure 3 shows how the force lines from the cave transmitter will break through the surface. In order to calculate depth it is necessary to determine the vertical angle of the field at various known distances from ground zero. It won't be of interest to most people to go into the mathematics; but suffice to say the depth is given by the formula:

$$D = L (3/4 \cot A) + 1/4 \operatorname{cosec} A$$

where L is the distance to ground zero and A is the vertical angle. Clearly it is advantageous to have a programmable calculator in the field, a look up graph can be used. More practical details on locating can be found in references 4 and 5.

References

1. Bradford Pothole Club Bulletin. Vol. 6, No. 5, Winter 1984. 'Gaping Gill to Ingleborough Cave — The 150 Year Link Up'. G.W. Crossley.
2. 'Gaping Gill — 150 Years of Exploration'. Howard M. Beck. Robert Hale, 1984.
3. 'ELF Communications Antennas'. Michael L. Burrows. Peter Peregrins Ltd, 1978.
4. Bradford Pothole Club Bulletin, Vol. 6 No. 6, Spring 1985. 'Radio Location'. J. Rattray.
5. 73 Magazine, February 1984, p 42. 'Caveman Radio'. Frank S. Reid W9MKV.

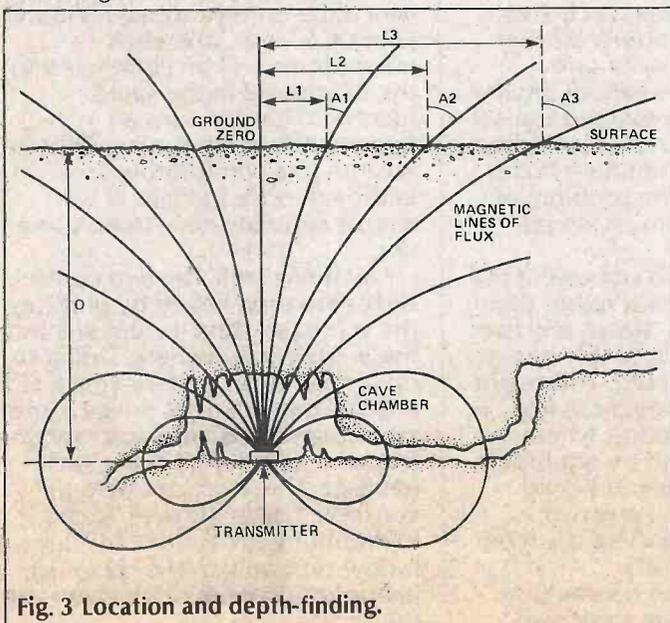


Fig. 3 Location and depth-finding.

MICROLIGHT INTERCOM


Ian Coughlan describes a high-performance intercom system which is designed for use in microlight aircraft but lends itself to any application which demands short-range, two-way communication in a noisy environment.

The pleasures of microlight flying can be greatly enhanced by taking along a passenger, but, thanks to the noise-level, talking to each other can be a pain in the neck in more ways than one.

This article describes a high-quality intercom system that was designed specifically for microlight aircraft but which has obvious applications in other areas, for example hang-gliding, motorcycling, and rallying. The system may be used either with headsets, or with modified crash-helmets.

The basic requirement of an intercom system is that it should provide a two-way communication link with sufficient audio quality and output to overcome background noise. Furthermore, it should be reliable and of rugged construction.

The system to be described boasts several advantages over commercially available intercoms, not least of which is the high output-power available. Each headset is served by its own 1.5 watt power amplifier, making very high sound pressure levels possible with the minimum of distortion. In addition, each microphone has its own automatic gain control device which reduces the dynamic range over which the headphone amplifiers have to operate, thereby reducing the possibility of the system being driven into overload. The overall performance of the system is excellent, and is certainly better than anything else that the author has tried. The prototype system has been up to 14,000 feet with nary a complaint from the pilot or his passenger!

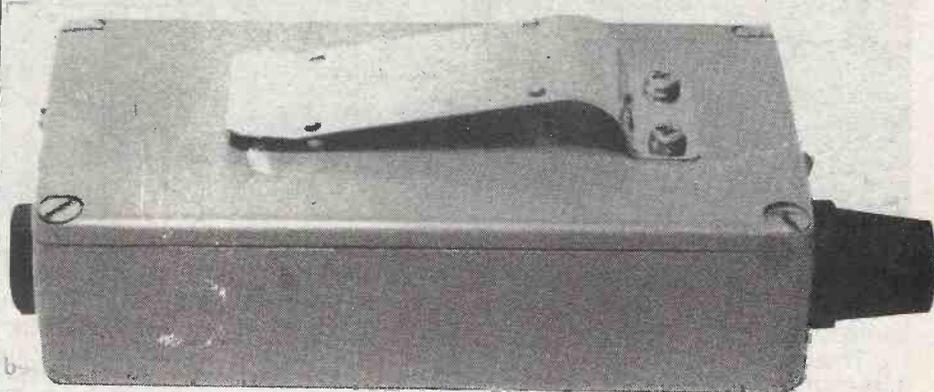

Of Mikes And Men

The system comprises two identical control-boxes, each of which contains a microphone pre-amplifier with AGC and a headphone amplifier. Each also contains its own battery, battery-check LED, and headphone volume control. The various internal components are protected against vibration by foam rubber padding and the diecast aluminium boxes help to minimise the problem of electrical noise from an aircraft engine.

Because the two stations of the intercom are identical rather than being 'master' and 'slave', any two control boxes made to this design can be interconnected. This might be of value to microlight flying clubs and other groups, where each member could be equipped with one control box. It would then be possible for any two members to establish an intercom link quickly and easily.

In use, each user connects a headset or helmet to their own

control-box by means of a latching DIN plug. This switches the control-box on, and provided the send-return link is not also connected the system will be in battery-check mode. The LED will light if the battery voltage is above about 6.5 Volts, and each microphone will be connected to the earphones in the same headset. This provides an opportunity to set the headphone volume to a comfortable level (although once in flight, it will almost certainly have to be turned up).

All being well, the two control-boxes are then linked by plugging the screened send-return link into the ¼-inch jack-sockets. Doing so disconnects the battery-check LED and the circuitry that drives it and also disconnects each microphone from the earphones in the same headset. These actions help to conserve battery power. Each microphone pre-amplifier's output is now sent only to the other user's headphone amplifier by means of the send-return link.

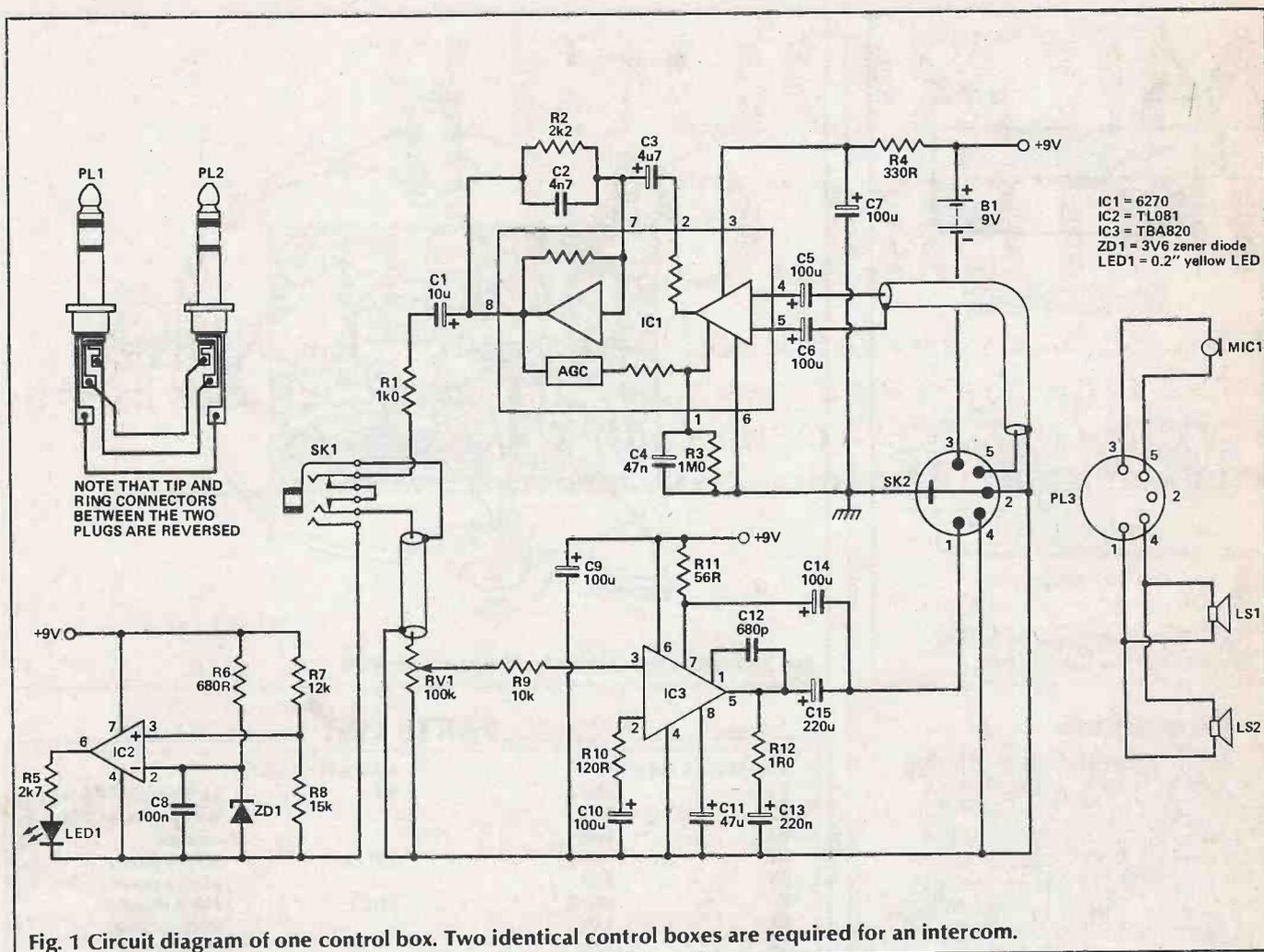


Fig. 1 Circuit diagram of one control box. Two identical control boxes are required for an intercom.

HOW IT WORKS

Each microphone is connected to an SL 6270 VOGAD integrated circuit. VOGAD stands for Voice Operated Gain Adjusting Device, and the device maintains an output of some 100mV RMS over a wide range of microphone levels, allowing either user to shout without overloading the system. The attack and decay times of the VOGAD are set by R3 and C4. With the values shown, the attack time (the time taken for the device to reduce its gain in response to a large input) is somewhat less than 20ms. The decay time, that is, the time taken for the device to return its gain to its former level when the large input is removed, is about 3 seconds.

R4 and C7 serve to decouple the sensitive microphone preamplifier from the supply line, which may be subject to surges caused by the headphone amplifier. It will be noticed that the microphone pre-amplifier and the headphone amplifier have separate 0V returns to the DIN socket; this is



because the headphone amplifier is capable of high output currents which would otherwise cause a voltage drop in the microphone pre-amplifier's 0V return, resulting in instability.

The output from the microphone pre-amplifier goes to the 'ring' contact of the send-return jack-socket. When nothing is plugged into this socket, the microphone output is routed to the volume control and hence to the associated headset; when the send-return link is plugged-in, the microphone output is routed to the volume control in the *other* control-box.

The wiper of the volume control goes to the input of the headphone amplifier, a TBA820. This device is capable of producing an output in excess of 1.5 Watts into 4 ohms with a good 9 volt battery, falling to some 750mw at 6 volts. The miniature loudspeakers used in the prototype have an impedance of 8 ohms, and are connected in parallel, giving 4 ohms. The

recommended microphone impedance is 300 ohms.

A FET-input op-amp and a 3.6 volt zener diode form the basis of the battery-check circuit. The op-amp is connected as a comparator with its output driving the LED. The inverting-input of the op-amp is connected to the 3.6 volt reference and the non-inverting-input is connected to a potential-divider between +9V and 0V. When the non-inverting-input exceeds 3.6V, as it will for all battery voltages above 6.5 Volts, the output of the op-amp will be high and the LED will light. As the battery voltage drops below 6.5 volts, the voltage on the non-inverting-input will drop below 3.6V and the op-amp output will go low, causing the LED to go out. This section of the circuitry is connected to 0V via one of the contacts on the send-return jack-socket, so it is disconnected when the jack-plug is inserted to reduce the drain on the battery.

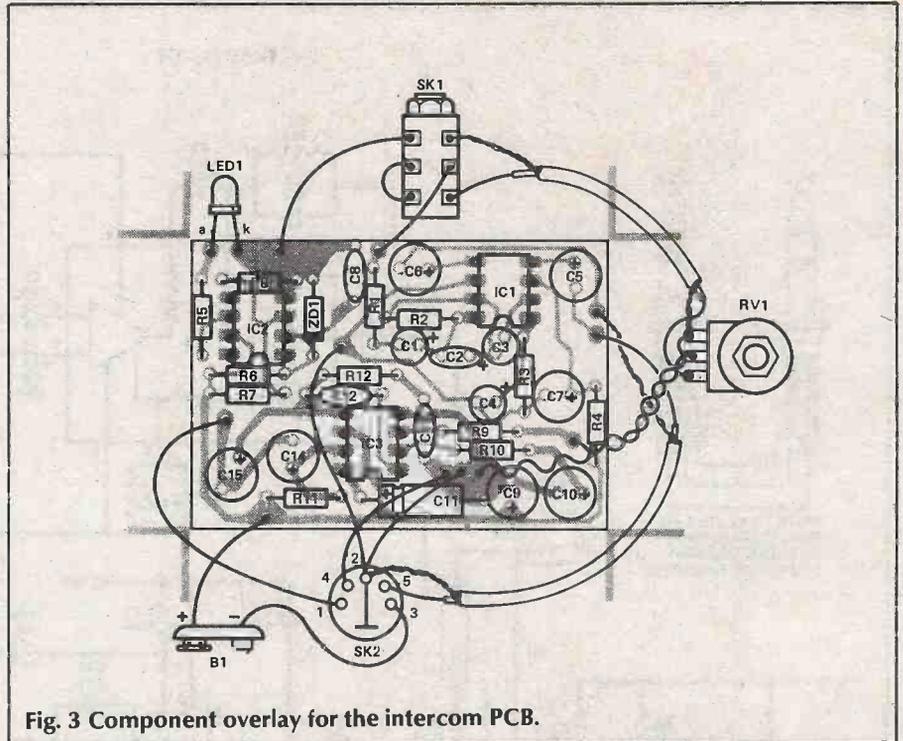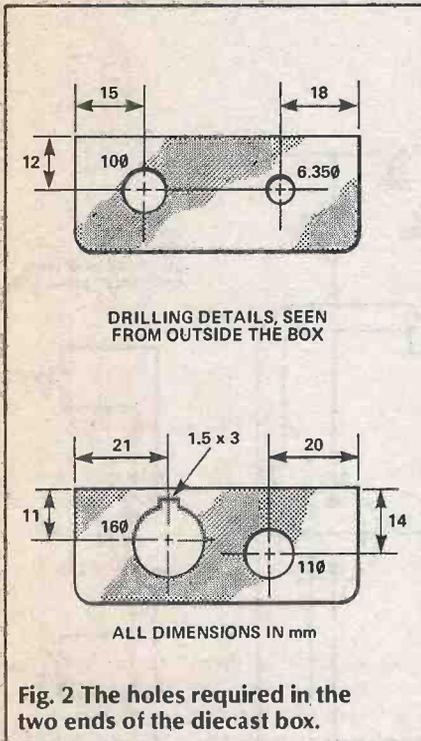

Construction

Begin construction by drilling the box as shown in Fig. 2, and don't forget to file the notch for the anti-rotation spigot on the DIN socket. Rub the box down with wet-and-dry paper, clean it, and apply a coat of primer. When this is dry, paint the box in your chosen colour, preferably by spraying (orange was used on the prototypes because it makes them easy to spot on a grass airstrip). Lettering can be applied when the paint is dry, and should be protected by a coat of Let-Fix or Letracote.

Before mounting anything on the PCB, check it for shorts. The Veropins should be gently tapped into position with a (small!) hammer from the underside of the PCB.

Mount the resistors onto the PCB, followed by the capacitors, and the DIL sockets. Crop leads tightly to the board before soldering to reduce the risk of short circuits to the die cast box. Attach 150mm lengths of insulated stranded wire to the Veropins and slide short pieces of 1mm diameter silicone rubber sleeving over them, right down to the PCB. Note that one of the wires comes from the battery connector. Connect the miniature screened cable in the same way.

Cut a piece of thin foam-rubber (56 x 58mm) and glue it to the inside of the box where the PCB

PARTS LIST

RESISTORS (all $\pm 5\%$)

R1	1k0
R2	2k2
R3	1M0
R4	330R
R5	2k7
R6	680R
R7	12k
R8	15k
R9	10k
R10	120R
R11	56R
R12	1R0
RV1	100k miniature logarithmic potentiometer

CAPACITORS

C1	10u 16V radial electrolytic
C2	4n7 polystyrene
C3	4u7 10V radial electrolytic
C4, 11	47u 10V radial electrolytic
C5, 6, 7, 9, 10, 14	100u 16V radial electrolytic
C8	100n miniature layer
C12	680p polystyrene
C13	220n miniature layer
C15	220u 16V radial electrolytic

SEMICONDUCTORS


IC1	6270
IC2	TLO81
IC3	TBA820
ZD1	3V6 400mW zener (BZY88C3V6 or equivalent)
LED1	yellow 0.2" LED

MISCELLANEOUS

B1	9V battery, PP3 or similar, preferably alkaline
LS1, 2	8R miniature loudspeakers
MIC1	300R dynamic microphone capsules (see Buylines)
PL1, 2	stereo 1/4" jack plugs*
PL3	5-pin 180° latching DIN plug
SK1	stereo 1/4" jack socket with three break contacts
SK2	5-pin 180° latching DIN socket

PCB; 8-pin DIL sockets, 3 off; panel-mounting bezel for LED1; diecast box, 113 x 163 x 28mm; PP3-type battery connector; knob; foam rubber; thin screened cable for internal wiring; sleeving; length of twin-core screened microphone cable for link between control boxes*; telephone-type four-core coiled leads for headsets; pocket clip for boxes; connecting wire, nuts, bolts, etc.

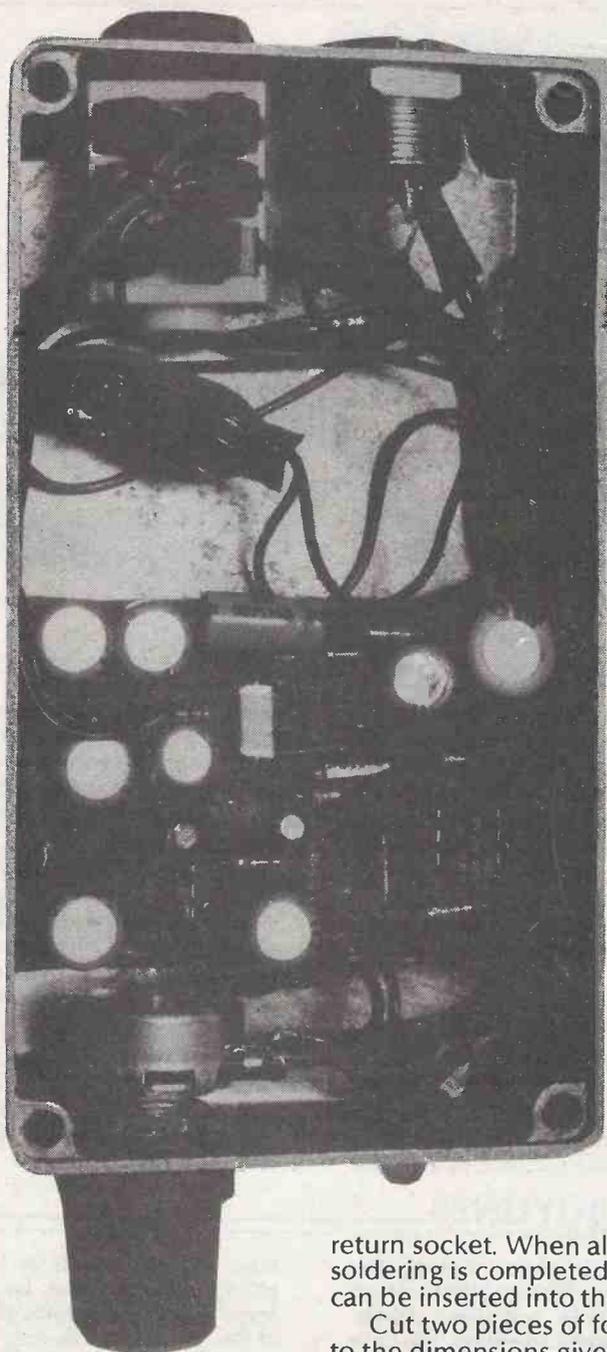*With the exception of PL1, PL2 and the length of cable which joins them, all of the parts listed are for one control box only and two of each will be required for a full system.





will sit. Mount the DIN socket, the jack-socket, the volume control pot and the LED clip. Place the PCB in the box on top of the foam-rubber, and connect the flying leads to the case-mounted components as shown in Fig. 3. Use silicone-rubber sleeving wherever possible. Note that the two wires connecting the potentiometer to the PCB should be twisted together and be careful to get the polarity of the LED correct.

The electronics are connected to the case at only one point, and that is at the DIN connector. Also, don't forget the link on the send-

return socket. When all the soldering is completed, the ICs can be inserted into their sockets.


Cut two pieces of foam-rubber to the dimensions given in Fig. 4. The narrower of the two mounts under the battery and the other goes over the PCB. These should be glued into place, but not until the unit has been tested.

The DIN plug wiring for the headsets is shown in Fig. 1. Telephone-type curly leads were used on the prototype system, but it is impossible to solder to the very flexible wire in these leads without losing the flexibility. It is recommended that the crimped-connectors on these leads are retained, and cut as shown in Fig. 5. After cleaning with a Stanley knife or similar, these connectors can readily be soldered and none of the lead's flexibility lost.

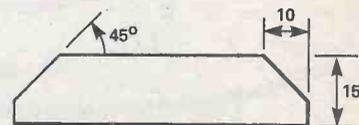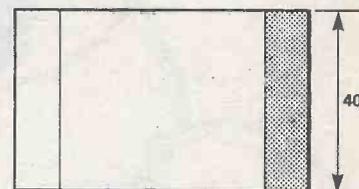

ALL DIMENSIONS IN mm

Fig. 4 Details of the foam rubber padding pieces. One of each size is required for each control box.

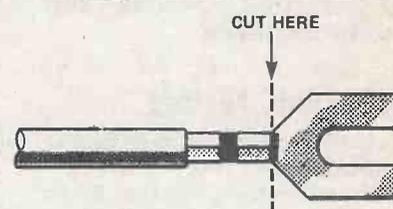


TURN TERMINAL OVER, SCRAPE-CLEAN THE UNDERSIDE, SOLDER TO THIS SURFACE



DO NOT LET SOLDER FLOW UP THE CONDUCTORS OF THE CABLE!

Fig. 5 Modifying the connectors on the telephone-style coiled headset leads.

If the microphones and earphones are to be installed in helmets, bear in mind that helmets are constructed to a very high standard, and, for motorcyclists at least, *must* comply with safety standards laid down by the British Standards Institute. Modifying a helmet in just about any way will probably mean it no longer complies with safety standards. To the best of the author's knowledge, such standards are not applicable to helmets worn while flying microlight aircraft. It is left to

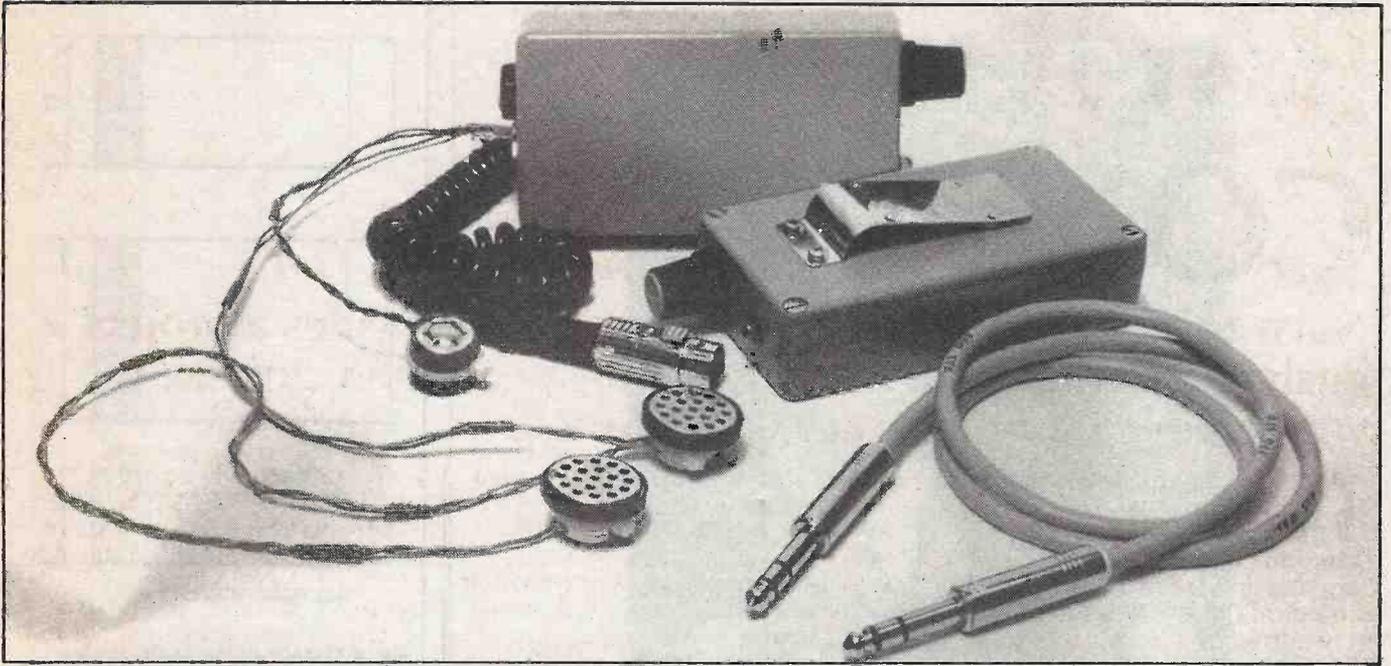

the individual constructor to decide whether such modifications are morally and legally defensible.

Testing, Testing

Have a quick look over the PCB to make sure there's nothing obviously wrong, such as an IC fitted the wrong way round. Connect a PP3 battery, and, if nothing catches fire, plug the headset or helmet into the DIN socket. The battery-check LED should light. If it doesn't, disconnect the battery and check everything again. Also, check the

DIN plug for the wire link. If satisfied that all is as it should be, reconnect the battery. If the LED still does not light, check the voltages around that part of the circuit. If the LED does light, turn the volume up and try speaking to yourself! You should be able to hear your own voice clearly. Check the other control-box in the same way.

When both control-boxes are working individually, they should be tested together. You'll need a partner for this. The send-return link is simply two stereo jack-plugs connected by one metre of twin-core screened cable. Choose the

most flexible cable you can get hold of, such as microphone cable. Note that the wires in this lead are reversed so that the 'tip' contact of one jack-plug goes to the 'ring' contact of the other.

With each user wearing a headset or helmet, plug in the send-return link. Both LEDs should go out. Neither user should be able to hear his own voice, but should, of course, be able to hear the other person's voice. If all is well, testing is complete and the pieces of foam mentioned above can be glued into place and the lids put on the boxes. The system is now ready for use.

BUYLINES

The resistors, capacitors and most of the semiconductors are widely available, the only exception being the 6270 which can be obtained from Cirkit or Watford (designated SL6270, SL6270CD, etc). Miniature loudspeakers are available from the author, whose address is given below. The low-impedance dynamic microphone capsules used in the prototype were taken from a pair of stick microphones of the type supplied with cheaper music centres and portable cassette machines. These are often sold as 'accessory packs' for a few pounds in radio and electrical shops. It may even be possible to obtain helmets with suitable transducers already in place — have a look through some of the motoring magazines which cover car rallying. If you require a headset rather than separate transducers to mount in a helmet, try the secondhand and surplus stores.

Failing that, a glance through the adverts in one of the magazines aimed at amateur radio enthusiasts should yield some useful addresses, but note that many amateur radio headsets use electret microphones (which require a separate power supply) and that they may not block out ambient noise. If all else fails, a DIY microphone boom-arm could be added to a pair of cheap, 'Walkman'-style headphones.

The only components likely to cause any problems are the pocket clips and the coiled leads. The clips used on the prototype came out of the junk-box and we do not know of anyone who supplies new ones. However, early pocket beepers appear frequently on the second-hand and surplus market and usually have a metal pocket clip attached by two rivets. These can be drilled out and the clip then attached to the intercom control box using nuts and bolts of a suitable size. The coiled

leads are not available as a new part either, but again can be found in second-hand and surplus shops. One of the companies who may be able to help with the above items is Henry's Audio Electronics, 301 Edgware Road, London W2, tel 01-724 3564.

One point to note is that Alkaline batteries (Duracell, Ever Ready Gold Seal etc) are recommended for use in the intercom. The battery drain can be quite considerable, especially if high volumes are being used to overcome wind noise in microlight flying, and ordinary zinc-carbon batteries may not last very long.

The PCB will be available from our PCB Service, but see the note in News Digest. The miniature loudspeakers cost £2.50 inclusive per pair and can be obtained from 17d Stuart House, Burns Road, Cumbernauld, Glasgow G67 2AP.

ETI

BAUD RATE CONVERTER

Norwegian correspondent Ola Borrebaek provides a project designed to make the most out of data communications. If you're pining for the bauds, start here ...

There are two basic ways in which personal computers and peripherals communicate with each other. The first, parallel communication, is the simpler of the two because data is transmitted as it is stored — in byte-wide chunks. Speed of transfer is controlled by the peripheral device, which acknowledges reception of each data word by pulsing a control line running parallel to the data. The main drawback is that multiway or ribbon cable is very expensive if you need enough of it to transfer data over a long distance. If you intend to use a telephone line for parallel data, you would need some very complex circuitry.

For computer-to-terminal applications, synchronous serial transmission is often used. The data is sent serially (one bit after another) but parallel to a clock signal on another line. Asynchronous serial transmission does away with the clock signal altogether. In these cases, the peripheral device does not control the rate of data transfer. Instead, computer and peripheral must operate at the same speed and the start and finish of a block of data is usually signalled by particular bits bracketing the block. Although serial transmission is increasing in popularity — especially through growing use of modems (modulators-demodulators) — many computers on the market have only limited capabilities, especially when it comes to bi-directional serial communications with different transmission rates in each direction.

Problems

PC serial ports are often far from flexible. Some require resoldering to allow for a change in baud rate (measured as the average number of bits

transmitted per second), although most are software programmable. In some cases, programmable baud rates won't themselves be sufficient. For example, the Sinclair QL has two serial communication ports, configured in such a way that the computer can act as an originating device (DTE or Data Terminal Equipment) and an answering device (DCE or Data Circuit-terminating Equipment) at the same time. Both ports operate in full-duplex mode — that is, both can transmit and receive simultaneously — but all operations on both ports are restricted to the same, albeit programmable, baud rate. You will have problems using a split rate modem — 1200/75 or 75/1200, for example — or using a modem on one port and a printer on the other operating at different bit transmission rates.

Principles

The kind of serial data dealt with in this article is called asynchronous because the transfer of a character does not need to occur in synchrony with a clock signal or, indeed, simultaneously with any particular event or events in time. The receiving part of an asynchronous serial connection will need to know when a character is being sent, so a start — low level — bit always precedes the data bits which comprise the transmitted character (Fig. 1).

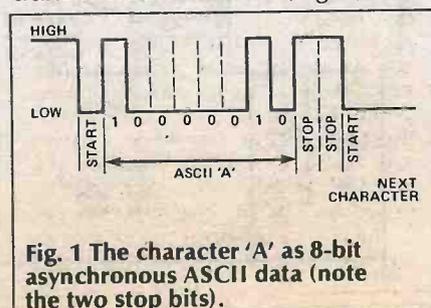


Fig. 1 The character 'A' as 8-bit asynchronous ASCII data (note the two stop bits).

There are typically between five and eight of these data bits, each one being a high or low state of equal duration to that of the start bit. The least significant bit is transmitted first.

One or two stop bits (high) signal the end of a character transfer. Note that with RS-232, the actual levels are inverted: a high being between $-3V$ and $-12V$ and a low being between $3V$ and $12V$. The RS-232 protocol is quite old now — RS-423 describing a more recent but largely compatible system.

In European literature, the equivalent specification is referred to as V.24. V.24 is actually a list of definitions for interfacing DTE with DCE. Commonly, these will be a computer and a modem, respectively. V.28 gives electrical characteristics, while plugs are defined by an international standard (ISO 2110). All these aspects are covered by the American RS-232 standard (current revision level, C). RS-232 is the closest we have to an internationally agreed data transmission standard. Despite a wide variety of practical implementations and the fact that it and V.24/V.28 were originally restricted to telephonic data transmission, it is the commonest serial communications specification in use today.

The number of stop bits specified for a particular port is the minimum number required. With asynchronous transmission, it is possible to insert as many high-level bits as you like between data words, but this would decrease the baud rate, whose definition takes no account of any distinction between start, data and stop bits.

Error Detection

ASCII (The American Standard Code for Information Interchange)

HOW IT WORKS

One UART (IC1) is used for converting data from your PC to the peripheral device while the other (IC2) converts from the device to the PC (Fig. 4b). A high-level on either the PARITY ERROR or FRAMING ERROR outputs of IC2 will charge C1 and provide the ERROR LED with current via Q1 and Q2. The PARITY ERROR Output of IC1 is used to toggle a D flip-flop (IC3a). The state of this flip-flop determines the type of parity used by both UARTs (of course, only when parity is enabled — parity may be enabled at one UART only if desired).

The following applies for both UARTS:

When a character has been received and transferred to the RECEIVER HOLDING REGISTER the DATA RECEIVER Output (pin 19) will go high and force the TRANSMITTER HOLDING REGISTER LOAD input (pin 23) low. After a slight delay in IC4b and c, the DATA RECEIVER RESET input (pin 18) is forced low to reset pin 19 to a low state. Since the received-data outputs are directly connected to the transmit-data inputs, the character has now been transferred from the transmitter to the receiver section of the UART. The conversion of bit durations is accomplished by using different receive and transmit clocks. The above process will repeat itself for every received character.

The TRANSMITTER HOLDING REGISTER EMPTY output from IC1 is used as a CTS output (it is ANDed with the CTS output from the peripheral device to provide CTS for the PC). When the THR is empty, the character previously occupying this space has been transferred to the TRANSMITTER SHIFT REGISTER and while it is being shifted out a new character may be shifted in at the RECEIVER SHIFT REGISTER. But as long as a character is waiting to be transferred to the TSR, no character should be sent by the PC. In such case THRE is low and CTS is kept inactive.

The 4060 oscillator and binary counter (IC7, Fig. 4a) has several clock outputs which are derived from the quartz crystal, XTAL1. They are given by 2.4576MHz divided by 2^n , where n is the number of IC7's Q output. The divider circuit consists of a programmable down-counter (IC8). It will count down from a value set by SW1. After each countdown a pulse is output on TC (ripple carry output, IC8 pin 1, which in turn reloads the value set by SW1. Before being fed to one of the UARTs, the pulse is squared (to achieve a 50% duty cycle) by IC3b which divides by two.

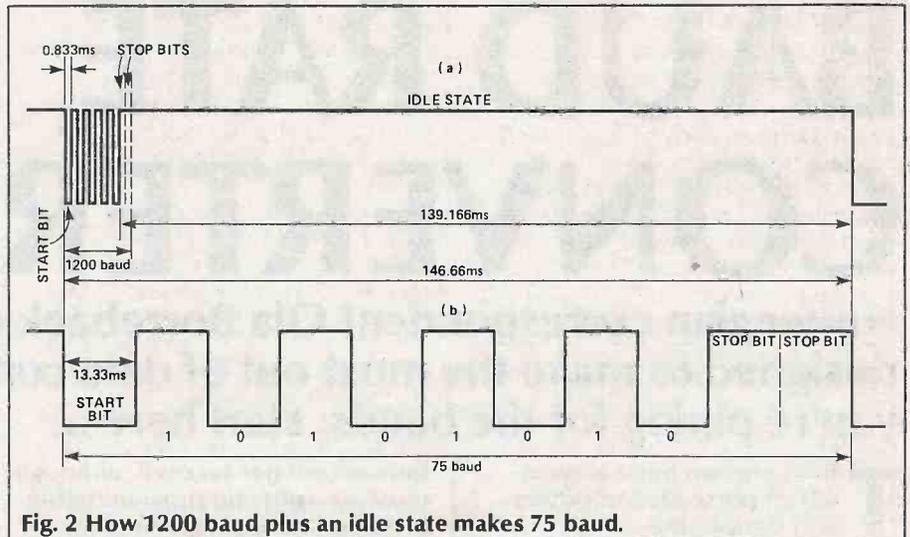


Fig. 2 How 1200 baud plus an idle state makes 75 baud.

uses seven bits of character information. Following these bits can be an eighth bit called the parity bit. This bit is set high or low by the transmitter so that there are always an even number of high levels (in even parity) or always an odd number of high levels (in odd parity), excluding the start and

stop bits transmitted (Table 1).

If the received parity doesn't match the transmitted parity, at least one bit has altered during the transfer. This comparison provides a basic error checking mechanism, which is only guaranteed to detect single-bit errors.


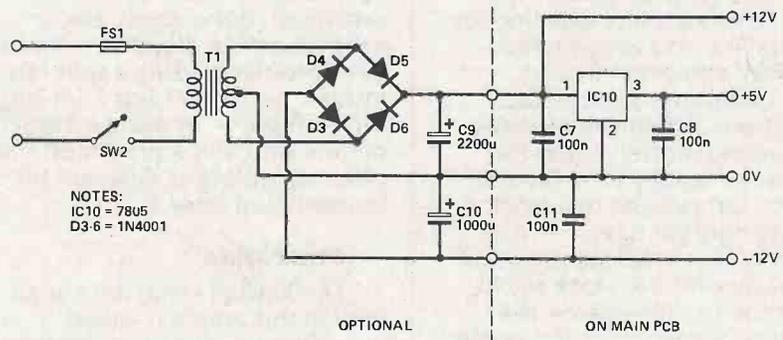


Fig. 3 Optional PSU — components to right of dotted line are on main board.

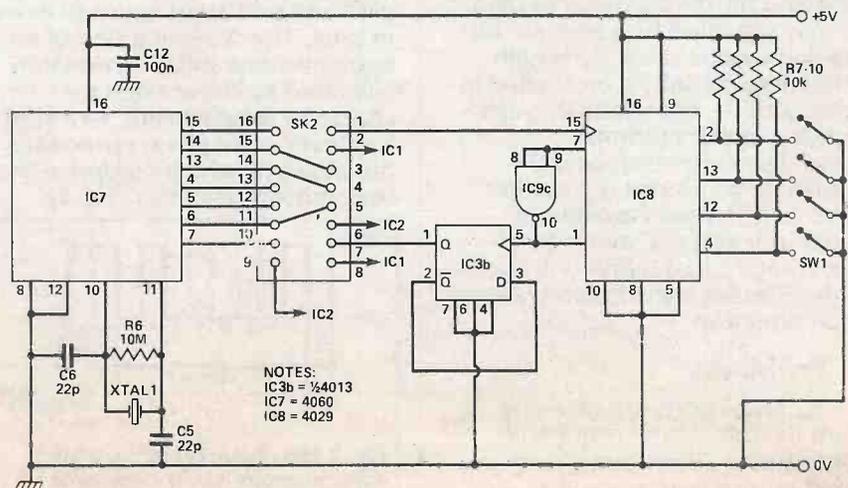

read the parallel holding registers, but this circuit makes no use of the parallel data-handling features of the UART. The rates for shifting data in and out of the UART are controlled by receive and transmit clocks.

The converter actually contains two UARTS — one to convert data going from the computer to the peripheral and one to handle data flowing in the reverse direction. An LED indicates if this latter UART issues a framing or parity error. Both UARTs automatically adjust to the same parity as that received by the first UART. Parity may be enabled or disabled and the UARTs can be programmed for the number of data and stop bits. The in-circuit clock may be configured for a large number of baud rates and all programming is undertaken by setting links on two 16-pin IC sockets and positions on a 4-way DIL switch.

Supply Demanded

The converter requires +12V at 200mA and -12V at 50mA as well as the more usual 5V supply. Modems will use these voltages for the generation of RS-232 levels, and they are often available at an RS-232 socket. The pins that may be used for these voltages vary (as, indeed, do RS-232 sockets), so the appropriate connecting points should be checked in your documentation. Alternatively, a separate PSU could be used. The circuit for a suitable PSU is described in Fig. 3. The +12V and -12V supplies are not regulated — they will only drive the line interface directly. A +5V supply is generated from the +12V supply via a 7805 regulator mounted on the main PCB. This will get hot, but a heatsink is not necessary.

Handshaking

The RS-232 specification allows data to be transferred in two directions simultaneously (full duplex). If the peripheral device needs time (in addition to the duration of the stop bits) to process the last received character, it will deactivate the Clear To Send (CTS) line. The computer will then deliver a high-level (commencing an idle state) until CTS is reactivated. CTS will be activated if the computer requests permission to send by activating the Request To Send (RTS) line.

The RTS output from the

computer is often held active. If the computer has no RTS output but an RTS input exists at the peripheral device, this input would have to be held active. Note that CTS and RTS have no effect on the data going from the peripheral device to the computer.

Common implementations of RS-232 use a Data Terminal Ready (DTR) line to enable the peripheral device. It is often held active inside the computer. A Data Set Ready (DSR) line may also be provided to inform the computer that data has been received by the modem and is ready to be transferred to the computer's serial port. This line is sometimes equal to the Carrier Detect (CDC) output from a modem. 'Data Set', incidentally, is American for 'modem'.

Construction

Before mounting the IC sockets (not used for IC10) be sure to solder the links, some of which run beneath the sockets. Not until all other components are mounted should the ICs be inserted into their sockets. For extra safety, you could also test that the regulator is working properly before inserting the ICs. This is done by connecting a 100R resistor between +5V and GND and connecting the +12V supply. As a current now runs through the regulator, its output should be within a few percent of five volts.

When using off-board switches for SK1, SK2 or SW1, remember to keep the wires short. They will not

require screening, but do not twist them together as this may result in cross-talk and noisy clock-signals. To avoid glitching, good quality switches should be used. If you want easy selection between several RTTY baud rates, off-board switches will have to be used for SW1 as well as SK2.

The link between pin 21 of ICs 2 and 1 should be made with insulated wire as it is rather long. When soldering in the crystal do not over-heat as this may destroy the quartz.

Normal precautions against static electricity should be taken when handling ICs. Inserting the ICs the wrong way round will probably destroy them, so note that IC7 is mounted the same way as SK2 — the opposite way to most of the ICs (Fig. 6).

The choice of cabinet is entirely up to the constructor but keep in mind that it may need to be large enough for both the main and the PSU PCBs (Figs. 5 and 6).

Two RS-232 connectors are used. SK3 connects to the computer and SK4 to the peripheral. These are not mounted on the PCB. The pin-outs given in the circuit diagram (Fig. 4b) are for standard main channel RS-232 25-pin D-connectors. Some modems may use separate pins for back channel signals and the constructor will have to deal with this. Alternative pinouts are: (from peripheral device) BRD pin 16, BCTS pin 13; (to peripheral device) BTD pin 14, BRTS pin 19. If the modem use these pins they


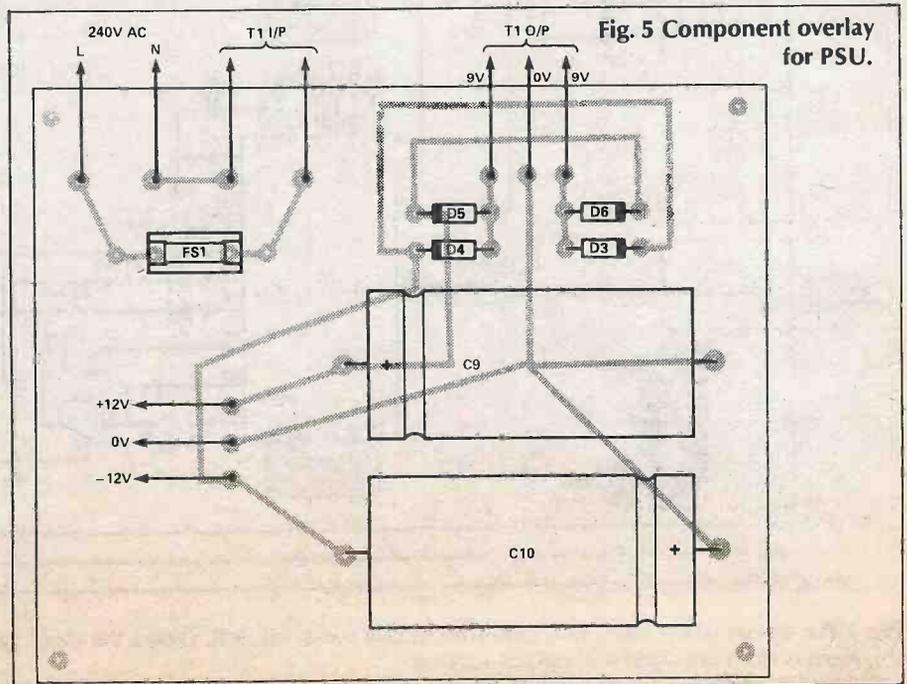


Fig. 5 Component overlay for PSU.

will have to be connected instead of pins 3, 5, 2 and 4 respectively. Pins 4, 6 and 20 of SK3 should be connected to the equipment pins on SK4. If a back channel configuration is used, connect pin 4 of SK3 to pin 19 of SK4 instead. Many devices use simpler, non-

standard connectors with only four or five pins. Appropriate connections should be obvious from a comparison of Fig. 4a and the wiring diagrams of these connectors to be found in the device documentation.

Fig. 6 Component overlay for main board.

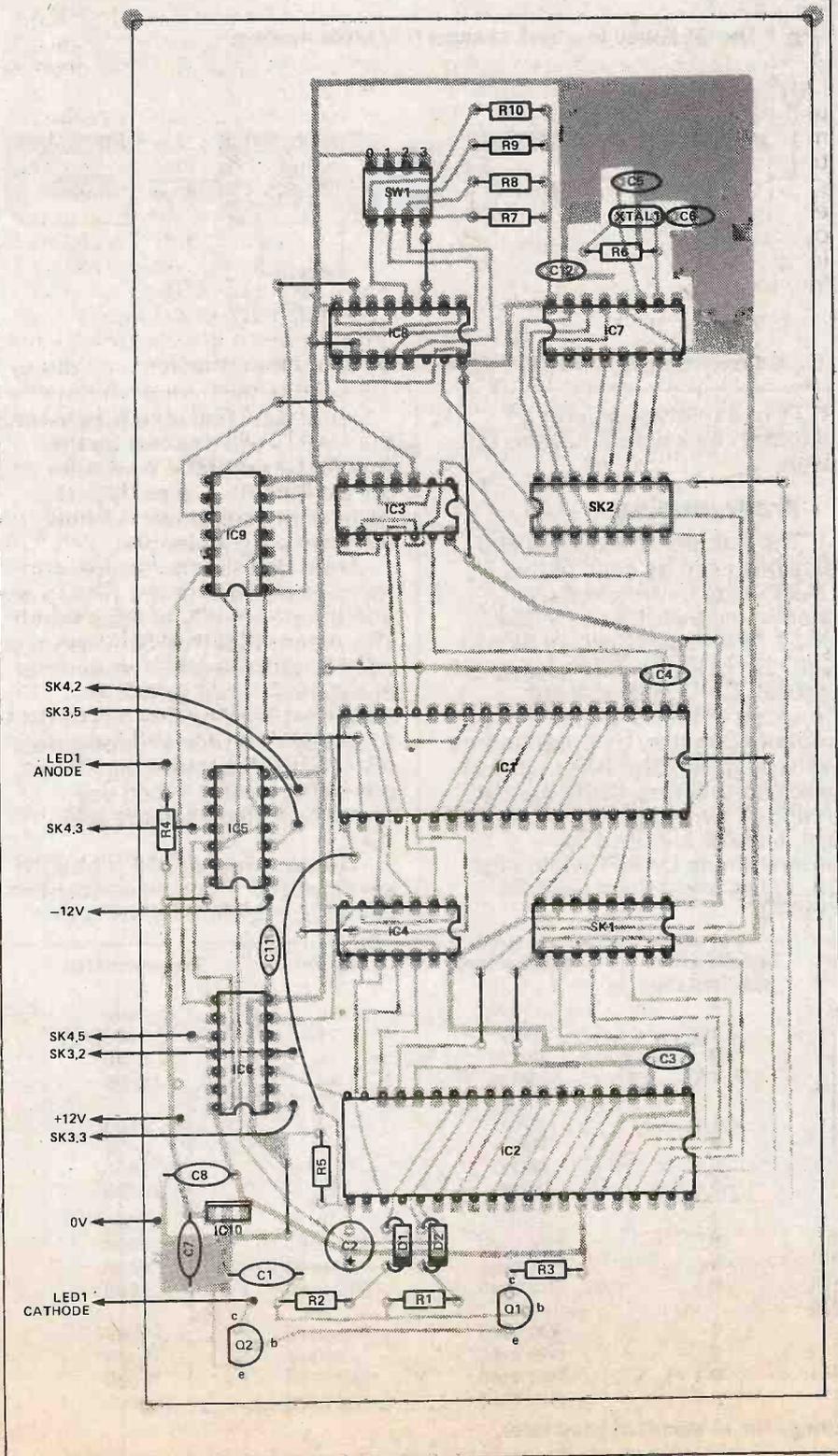

PARTS LIST

RESISTORS (all 1/4 W, 5%)

R1	4k7
R2	4k7
R3	22k
R4	1k0
R5	4k7
R6	10M
R7, 8, 9, 10	10k

CAPACITORS

C1	100n polyester
C2	10μ elect.
C3	100n ceramic
C4	100n ceramic
C5	22p ceramic
C6	22p ceramic
C7	100n ceramic
C8	100n ceramic
C9	2200 μ25V* elect.
C10	100 μ25V* elect.
C11	100n ceramic
C12	100n ceramic

SEMICONDUCTORS

IC1, IC2	TR1863
IC3	CD4013
IC4	CD4069
IC5	MC1488
IC6	MC1489A
IC7	CD4060
IC8	CD4029
IC9	CD4011
IC10	78M05
Q1, 2	BC247
D1, 2	1N4148
D3, 4, 5, 6	1N4001*
LED1	Red LED

MISCELLANEOUS

SW1	4-way DII-switch
SW2	Mains switch*
FS1	50mA fuse*
T1	9V-0.9V 200mA mains
SK1, 2	16-pin IC sockets with headers as required
SK3, 4	25-way female D-sockets
IC sockets	3 x 14 pin, 4 x 16 pin, 2 x 40 pin
XTAL1	2.4576 MHz parallel resonance crystal; PBC; case (*optional — PSU components).

BUYLINES

None of the components should provide particular problems. As mentioned in the text, Western Digital's TR1863 can be happily replaced by the CDP6402 (RCA), or General Instruments' AY3-1015. To be on the safe side, make sure you get a fast version, if different speed versions are available. The 78M05 is not absolutely necessary, an ordinary 7805 will do. Modems themselves are widely available, but particularly suitable models may be obtained (cheaply) from Cirkuit, Maplin and Computer Warehouse — all of whom advertise regularly in ETI.

Use

The converter was originally intended for connection of a back channel modem to the Sinclair QL. The setup in Fig. 7 not only allows separate rates to be used, it also makes sure that all data received by the QL are of correct parity and thereby prevents the QL from issuing a 'Xmit Error'. The Xmit Error interrupts any BASIC programme and is a real nuisance when trying to receive continuous text.

Switches could be connected to the serial converter so that the modem could operate on either 1200/75 or 300/300 without having to disconnect the converter and reprogram the computer.

Some PCs require re-soldering to change baud rates and here a switchable converter would add new prospects of multi-baud operation if the PC did support separate transmit and receive rates in the first place.

There are many other applications. Converting RTTY from an amateur receiver to a PC is an interesting possibility. Converting 50/300 is shown in Fig. 8. Here only UART2 is used and UART1 need not be mounted. For RTTY operation, every baud rate is available (Table 2). For modem operation, even a Bell (US) 5-band back channel is obtainable.

A useful application could be to interface your PC to an old 110 baud teletype printer. The serial converter could also be used as a clock generator for other circuitry — just don't mount the UARTS.

Since there is only one programmable divider on board, 50 and 110 baud cannot be used at the same time. For interfacing

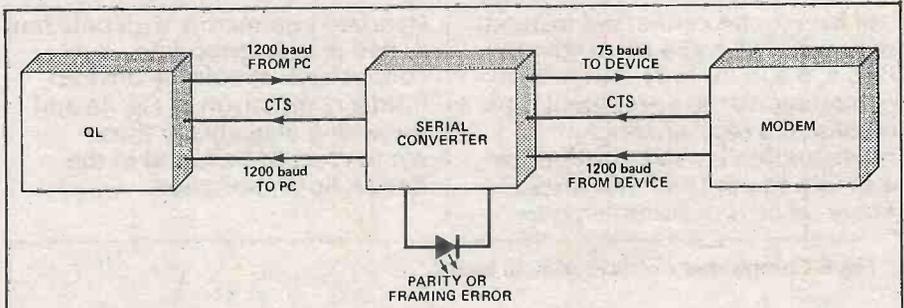


Fig. 7 The QL linked to a back channel (75/1200) modem.

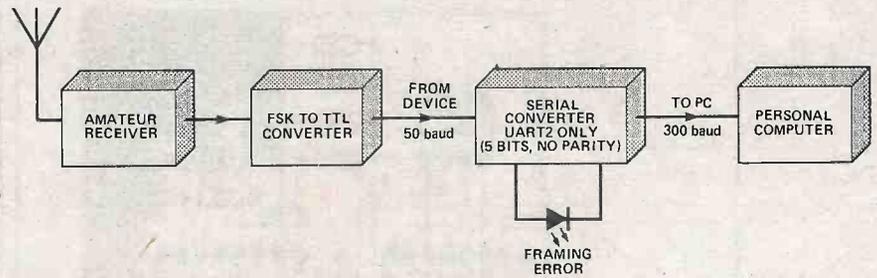


Fig. 8 Converting 50 baud RTTY signal to 300 baud for a computer.

RTTY to a teletype printer an external clock would have to be used.

Programming

The number of stop bits and data bits used by each of the UARTS may be selected by connecting the SBS and WLS1/WLS2 pins respectively of SK1 to GND or +5V (see Table 3, Figs. 4b and 9a). GND and +5V are provided at the socket so that any combination may be programmed without getting the wires crossed when hard-wiring. Parity may be inhibited by wiring PI to +5V. Pins 2, 4, 6 and 8 are used for programming UART1 while pins 10, 12, 14 and 16 are used for UART2.


How you choose to programme the UARTS will depend on the specifications of the computer and the peripheral — especially the latter as the computer is usually software programmable.

Note that the transmitter and receiver sections of the UARTS are not independently programmable. This means that true conversion of word length (altering the number of databits) is not possible. However, sending five bits of data to an eight bit receiving-port will result in the four most significant bits being set to 1 when up-converting, thanks to the idle state.

The alert reader will probably have noticed that true conversion could be achieved by using the

Standard baudrate	Used by converter	Deviation from standard (%)	Divider setting	Divisor	Frequency (Hz)
5.000	5.000	0	1111	30	2400
45.45	46.15	+1.5	1101	26	19200
50.00	50.00	0	0011	6	4800
56.92	54.55	-4.2	1011	22	19200
74.20	75.00	+1.1	0001	2	2400
75.00	75.00	0	0001	2	2400
100.0	100.0	0	0011	6	9600
110.0	109.1	-0.8	1011	22	38400
120.0	120.0	0	0101	10	19200
150.0	150.0	0	Not used	Not used	2400
300.0	300.0	0	Not used	Not used	4800
600.0	600.0	0	Not used	Not used	9600
1200	1200	0	Not used	Not used	19200
2400	2400	0	Not used	Not used	38400
4800	4800	0	Not used	Not used	76800
9600	9600	0	Not used	Not used	153600

Table 2 Source frequencies and divider settings for 16 standard baud rates.

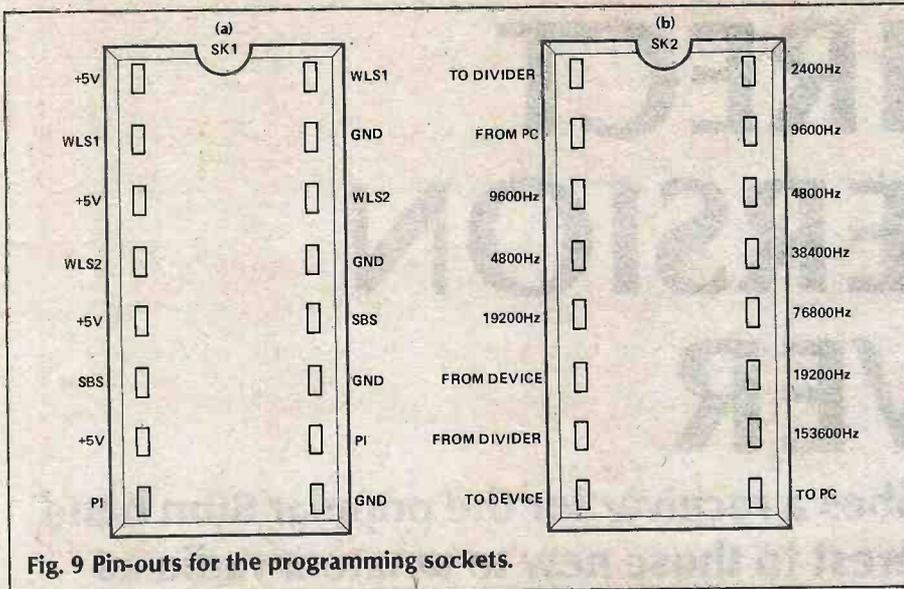

receiving section of one UART together with the transmitter of the other. This would introduce the need for a more expensive double-sided PCB and it would no longer be possible to use a different number of data bits in each direction. User-designed software is probably used when receiving RTTY (Baudot) code (with five bit data words) and including a mask instruction to clear the four ones should be easy.

SK2 and SW1 are used for programming the clock generator. Clock signals of 2^n multiples of 2400Hz are available at SK2 (Figs. 4a and 9b). These may be fed directly to the clock inputs of the UARTs, also available at SK2, or they may be fed through an on-board divider first.

Specifying number of stop bits:

SBS	No. of bits
0	1
1	2 (1.5 when using 5 databits)


Selecting number of databits:

WLS2	WLS1	No. of bits
0	0	5
0	1	6
1	0	7
1	1	8

+5V on PI inhibits parity generation and checking.

0 is GND
1 is +5V

Table 3 Programming the UARTS for number of stop bits (SBS) and word length (WLS).

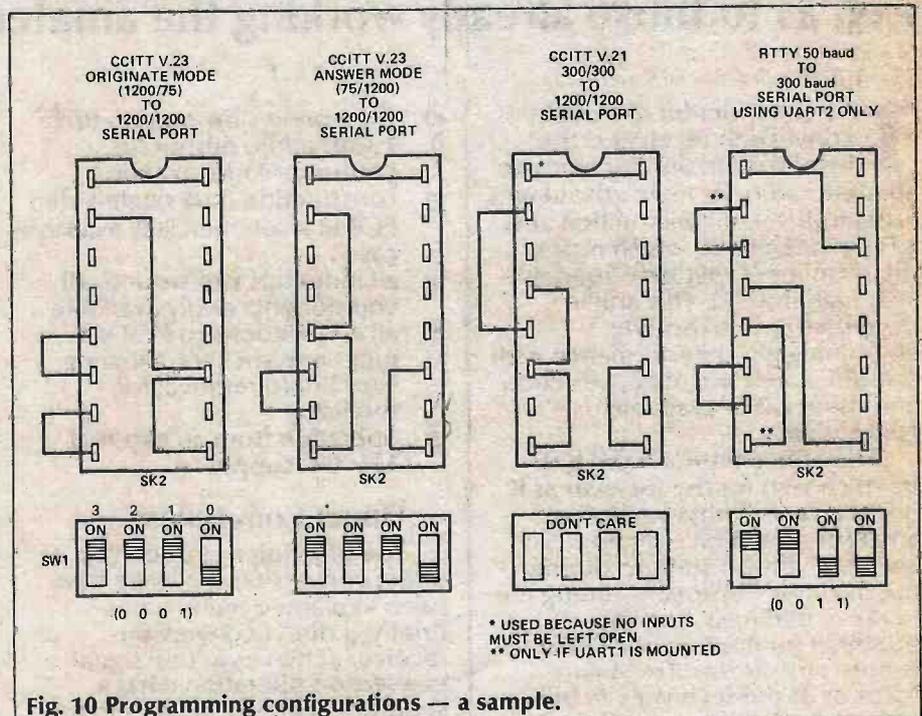

* USED BECAUSE NO INPUTS MUST BE LEFT OPEN
** ONLY IF UART1 IS MOUNTED

Fig. 10 Programming configurations — a sample.

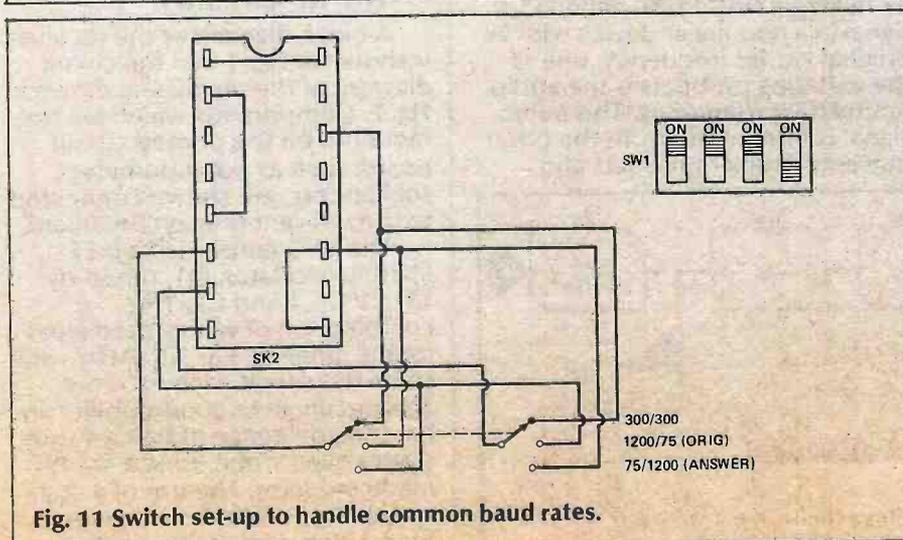


Fig. 11 Switch set-up to handle common baud rates.

The divider divides by two times the binary value set by SW1. Be careful not to connect any of the clock outputs together as this may destroy IC7. Note that the baud rate (maximum baud rate, to be precise) used by the UARTs is 1/16 of the clock frequency. The frequencies and the divider settings used for some standard baud rates are shown in Table 2. Some examples of hard-wiring the sockets are shown in Fig. 10. When connecting off-board switches, some ingenuity will be demanded from the constructor as to how to achieve the switch-action required. A set-up for use with a 1200/75+300/300 modem is also shown in Fig. 11.

80m DIRECT CONVERSION RECEIVER

S. Niewiadomski describes a receiver for the popular 80m band which should be of interest to those new to amateur radio as well as to those already working the amateur bands.

The construction of a direct conversion receiver is the first introduction for many to amateur radio. Its main advantages are simplicity of construction and ease of alignment, which makes the chances of first time success very high indeed. This article describes such a receiver, combining good performance with printed circuit board construction and using easily available components.

The 80m amateur band has been chosen for the receiver as it offers a varied cross-section of amateur operation — “rag-chewing” British stations during the daytime, Europeans during the hours of darkness, and the potential for more exotic DX at sunrise and sunset. The main features of the receiver can be summarised as:

- a) operation on the 80m amateur band
- b) audio AGC System
- c) high quality passive audio bandpass filter
- d) high stability VFO design

- e) two-speed slow motion drive
- f) 1 watt audio output for phones or loudspeaker
- g) construction on a single-sided PCB in a commercially available case
- h) all inductors pre-wound, all components easily available
- i) all connections to PCB via plugs and sockets, allowing easy board removal for servicing
- g) operation from an external 12V DC supply.

Direct Conversion

The principles of operation of direct conversion receivers have been explained many times. Briefly, a direct conversion receiver achieves in one signal conversion operation what a superhet achieves in two or more. By mixing a single side band (SSB) signal in a non-linear device with its original carrier frequency, one of the resulting products is the audio modulating frequency. This audio signal is filtered out from the other unwanted mixer products and

amplified, forming the audio output of the receiver. Since most amplification and filtering take place at audio frequencies, the performance of a direct conversion receiver depends on high audio amplification and a selective audio filter.

To recover the modulating frequency exactly, the oscillator used for detection must be at precisely the original carrier frequency. If not, the received audio will be shifted in frequency, and may be completely unintelligible. Shifts of a few tens of Hz for SSB are unimportant and when receiving a CW signal, the audio frequency can be set to whatever the listener finds easiest to read.

The RF Circuitry

A block diagram of the receiver is shown in Fig. 1 and the circuit diagram of the receiver is shown in Fig. 2. Components which are not mounted on the printed circuit board, such as potentiometers, sockets, etc. are shown connected to the relevant plug on the board.

The VFO consists of a JFET Hartley oscillator, Q1, tuned by T1, CV1, C1 and C2. The combination of values used gives a tuning range of 3.5–3.8 MHz, with some overlap at each extreme. This circuit gives good stability and has the advantage of being a sure-starter even when using a ready-made inductor. The use of a dual-speed slow motion drive gives both a slow tuning rate so that no

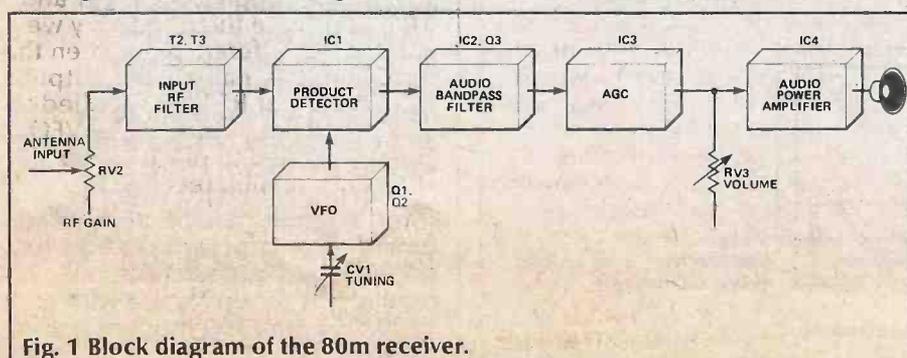


Fig. 1 Block diagram of the 80m receiver.

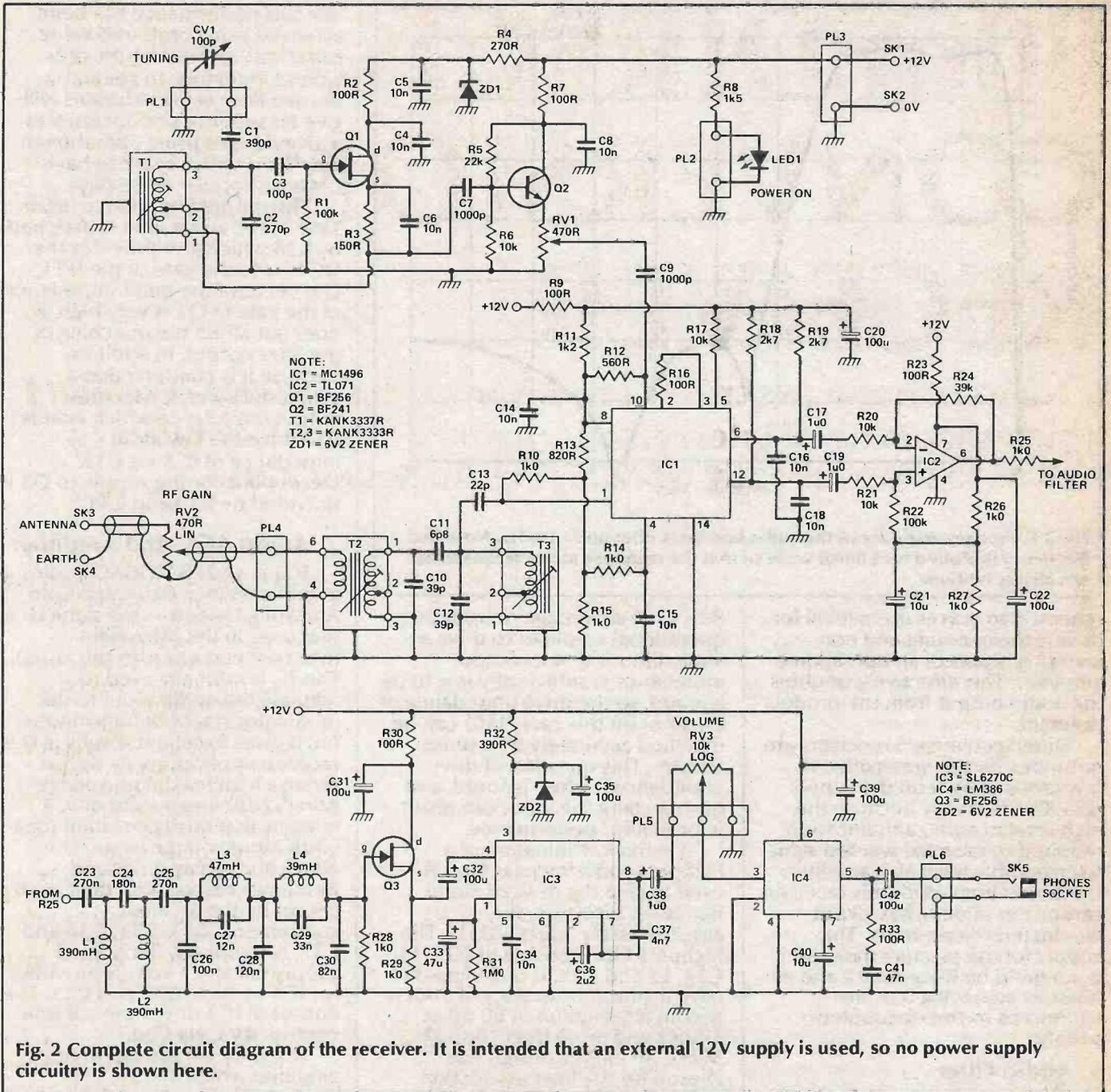


Fig. 2 Complete circuit diagram of the receiver. It is intended that an external 12V supply is used, so no power supply circuitry is shown here.

fine tuning control is needed and a faster rate for rapid frequency changes.

A stabilised 6.2 volt supply for the VFO JFET is derived from the 12 volt rail by R4 and ZD1, and decoupled by C5, R2 and C4. Q2 is configured as an emitter follower to give high input and low output impedance, and its output can be varied by adjusting the preset potentiometer RV1. A maximum output of 500mv peak-to-peak was available from RV1 on the prototype.

Although direct conversion receivers do not suffer from image reception problems in the same

way as superhets, an input RF filter is required to reduce the amount of unwanted RF energy reaching the product detector if intermodulation problems are to be avoided. The filter is formed by T2, C10, C11, C12 and T3 which can be set to cover the entire 80m band without the need for any tuning during operation. The amount of signal from the antenna reaching the input filter can be varied by RV2 and this prevents the product detector from being overloaded on strong signals.

IC1 (an MC or LM 496) is a double-balanced mixer biased for operation from a single 12 volt

supply rail. This IC produces the sums and differences of various multiples of the two input frequencies applied to pins 1 and 10. In this case the frequency we want is the difference between the fundamentals, namely the output from the input RF filter (applied to pin 1) and the output of the VFO buffer (applied to pin 10). In a direct conversion receiver the required output of the detector stage is at audio frequencies, so the outputs of IC1 (pins 6 and 12) are decoupled to RF by C16 and C18. Both outputs of IC1 are used in this application because the voltages are in anti-phase to each

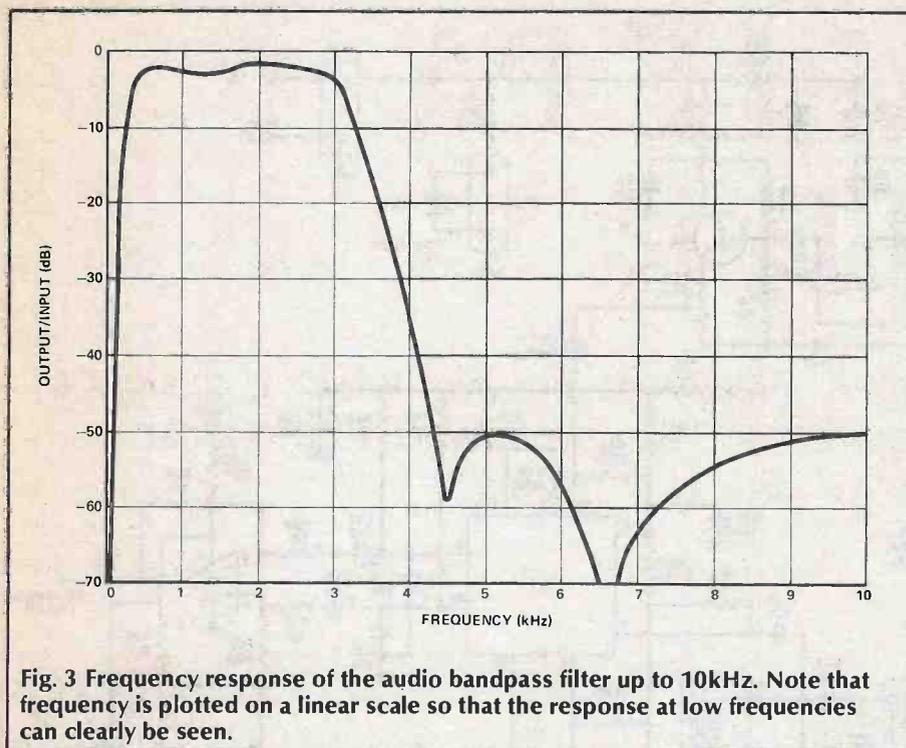


Fig. 3 Frequency response of the audio bandpass filter up to 10kHz. Note that frequency is plotted on a linear scale so that the response at low frequencies can clearly be seen.

other which makes them ideal for driving the inverting and non-inverting inputs of an operational amplifier. This effectively doubles the audio output from the product detector.

Direct conversion receivers are notorious for being sensitive to low levels of hum on the supply rails. This is mainly because the high level of audio amplification required to raise the wanted signal to an audible level also amplifies unwanted hum. With this receiver, careful decoupling has all but eliminated the problem. The supply for the product detector is decoupled by R9 and C20 and all resistors supplying IC1 are connected to this decoupled supply.

Audio Filter

IC2 is an operational amplifier whose gain is set at 3.9 by its input and feedback resistors. Because IC2 is operated from a single supply rail, its inputs (and therefore its output) are biased to mid-rail by R22 from potential divider network R26 and R27. A low noise amplifier, a TLO71, was used for IC2, but it is debatable whether it is really merited. Other ICs with the same pinout (such as the 741) can be substituted without much degradation in performance. A decoupled supply for IC2 is provided by R23 and C22.

The output of IC2 drives the audio filter via the 1k0 resistor,

R25. One advantage of using an operational amplifier to drive an audio filter is that its output impedance is sufficiently low to be ignored, so the drive impedance of the filter (in this case, 1k0) can be matched accurately by a series resistor. This question of drive impedance is often ignored, and mismatching the input can result in poor filter performance.

A series combination of a highpass and a lowpass filter is used to give the desired audio bandpass response of approximately 300Hz-3kHz. The highpass filter consists of C23, L1, C24, L2 and C25. It is designed to have a cut-off frequency of 300Hz and an attenuation of 60 dB at 100Hz and more than 70dB at 50Hz. An elliptic design was chosen for the lowpass section which consists of C26, L3, C27, C28, L4, C29 and C30. You can see that it is an elliptic filter by the tuned circuits (L3/C27 and L4/C29) which it contains. Elliptic filters give a very fast initial roll-off but the attenuation does not continue to rise in the stopband. It settles down to a more or less constant value, in this case approximately 50 dB.

Figure 3 shows the response of the complete filter. This is an excellent response for a direct conversion receiver whose main selectivity depends on the audio filter (and the ability of the human brain to concentrate on the desired signal, of course). Note

that this performance has been achieved using preferred value capacitors and miniature, pre-wound inductors. In general, a passive filter using inductors will give far superior performance to active designs using operational amplifiers which seem to have become popular these days.

The output impedance (again 1k0) of the audio filter is matched by R28 which also provides the DC bias to the gate of the JFET, Q3. Because the input impedance of the gate of Q3 is very high, it does not affect the matching of the filter output. In addition, because it is connected as a source-follower, it has a low output impedance which enables it to drive the low input impedance of IC3 via C32. Decoupling for the supply to Q3 is provided by R30 and C31.

Audio AGC And Amplifier

IC3 is a 6270 VOGAD audio amplifier (Voice Operated Gain Adjusting Device — the same IC as that used in the Microlight Intercom elsewhere in this issue). This IC is normally used to regulate the audio input to the modulator stages of transmitters, but it gives excellent results in this receiver application. As well as giving a high maximum voltage gain (52dB), the output of IC3 remains essentially constant for a 60dB input voltage range. The attack and decay times and frequency response of the circuit are set by the external components C33, R31, C36 and C37. A stabilised, decoupled supply rail at 6.2 volts is provided for IC3 by R32, ZD2 and C25. The output of IC3 drives the volume control, RV3, via C38.

IC4 is an LM386 audio power amplifier which in this configuration has a gain of approximately 20. This IC produces less output noise than the popular LM380, and is housed in a more compact 8 pin DIL package. A standard output-stabilising Zobel network is fitted, consisting of R33 and C41. IC4 drives the phones socket SK5 via capacitor C42. The supply to IC4 is decoupled by C39.

Details of the construction, testing and alignment of the receiver will appear next month, along with some notes on reception for those unfamiliar with SSB operation.

ETI

PORTABLE PA AMPLIFIER

John Linsley Hood describes a fifty watt amplifier which is designed for public address applications and can be powered from a car battery using last month's DC-DC converter.


As those who saw the article in last month's ETI will know, this design was evolved to meet the need for a cheap, fully-portable amplifier system which requires the minimum of ancillary equipment and can be operated out-of-doors and in other locations where a mains supply is not readily available.

To meet these requirements, it was decided that the amplifier should be able to operate from a 12V DC car battery supply. Rather than supply the amplifier directly at this low voltage, a DC-DC converter is employed which steps the 12V up to 55V. This simplifies the design of the amplifier stages considerably and reduces the need for compromises, allowing near 'hi-fi' levels of performance to be achieved at reasonable cost. This converter formed the subject of last month's article.

Amplifier Design Requirements

An output level of 50 watts was chosen as being a good compromise, providing reasonably high power without excessive battery drain. It was also decided that basic mixing facilities should be included so as to remove the need for an external mixer. The result is that a complete sound reinforcement system can be produced by adding a loudspeaker, a microphone and a car battery to the piece of equipment described here.

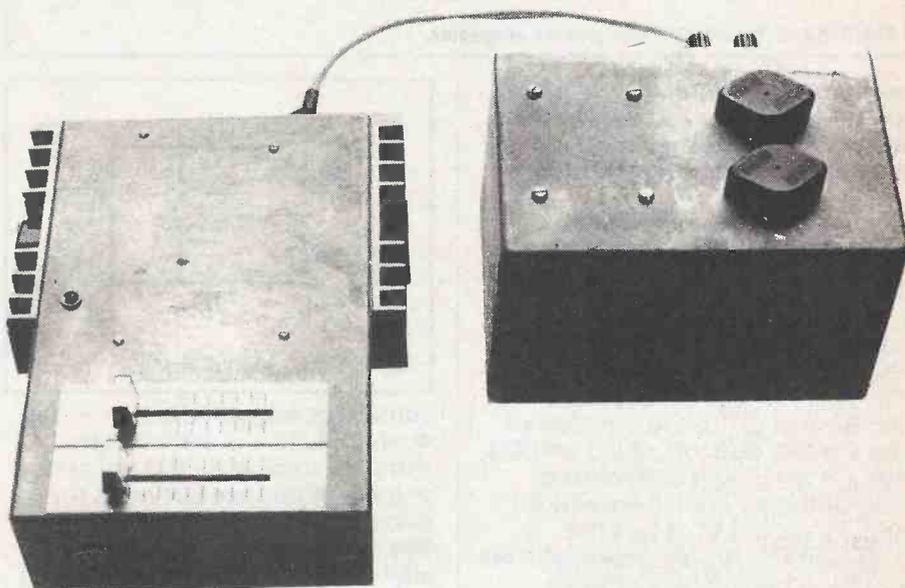I decided that the target THD value at 50W into 4 ohms should be 0.1% — not a very low distortion level by today's hi-fi standards, but entirely adequate for this purpose. In fact, if many of the PA systems I hear could get



down below 10% they would be much more pleasant to listen to. I also chose a fairly conventional bandwidth of 40Hz–20kHz. This allows the design of the amplifier to be both conventional and simple, which makes it easier to design and cheaper to build.

I used a single supply line system in the converter so that 12V of the 55V DC output could be provided directly by the battery, and also to simplify the

DC output voltage regulation circuitry. This means that the amplifier cannot be directly coupled, although this has advantages since a capacitor coupling the output to the loudspeaker will help protect both the 'speaker and the amplifier from inadvertent misuse.

A design feature which I feel is an absolute essential in such a PA system is an amplifier overload indicator. This is necessary because the operator and/or the person behind the microphone are, invariably, behind the loudspeakers and therefore have no idea of the sort of sounds reaching the audience. One of the more unpleasant of these is the sound of the PA amplifier being driven hard into clipping. A bit of forethought at the design stage allows this condition to be indicated, so that the operator can make remedial adjustments to the

OOPS!

In the parts list which accompanied last month's DC-DC converter article, SK3 was listed as a two or three way connector. Please note that, for use with the amplifier described here, SK3 will need to have three or more ways since it must carry a +12V supply as well as +55V and ground.

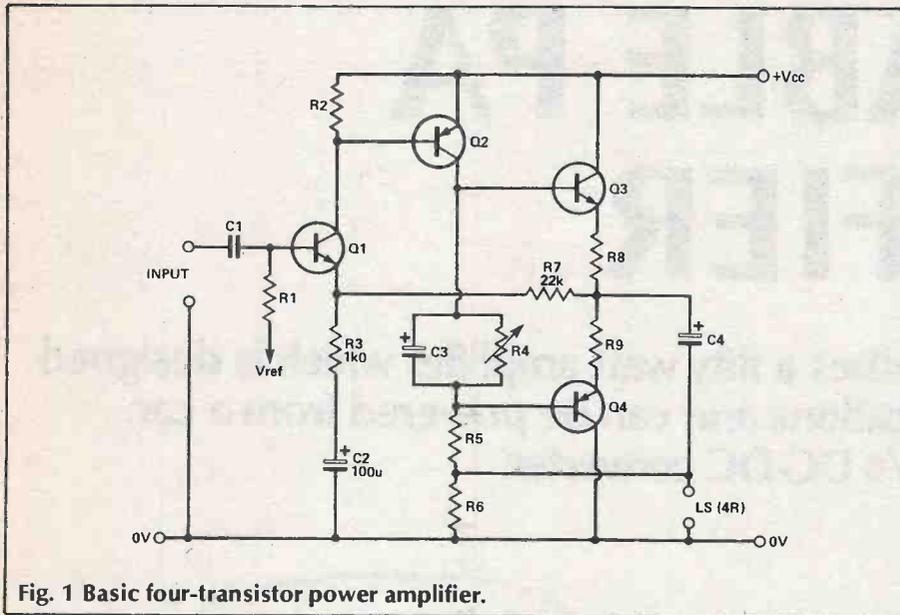


Fig. 1 Basic four-transistor power amplifier.

volume levels. After all, once an amplifier reaches its clipping level, no more volume can be obtained, only more noise and distortion.

The Power Amplifier Design

A simple audio power amplifier which is well suited to this sort of application is the four transistor design shown in Fig. 1. This is direct coupled from the base of Q1 to the junction of the emitter resistors of Q3 and Q4, and for maximum undistorted output the junction between R8 and R9 should sit at half the available DC supply potential. This can be achieved by a suitable choice of the reference DC potential to which Q1 base resistor is returned.

If the output transistors are power Darlington devices, quite high output power levels are possible. Also, because of the way it is laid out, the output capacitor, C4, can serve as a 'bootstrap' coupling capacitor to the bottom end of R5. This allows a high AC voltage swing to be obtained from Q2, which is the final class A voltage amplifier stage.

The overall AC gain of the amplifier is determined by the negative feedback resistors R7 and R3. With the values shown, the overall gain would be 23x. Since the output voltage swing for 50 watts into 4 ohms will be 14.14V RMS, the required input signal level for maximum output will be 615mV RMS.

To avoid excessive crossover-type distortion, the output transistors need to be biased

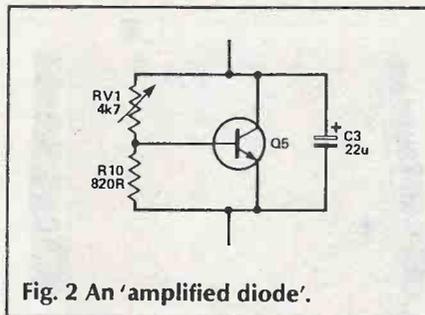


Fig. 2 An 'amplified diode'.

somewhat into conduction — say 40–60mA. This is achieved by using R4 to provide the necessary voltage difference between the two output transistor bases, and this could be made variable to allow for setting up to the desired value.

Circuit Improvements

One of the problems of this simple type of circuit is that the quiescent current through the output transistors is determined by the forward voltage drop of the base-emitter junctions of the output transistors, and the potential drop across R4. These are affected by operating temperature (the hotter the output devices become, the lower the Vb-e potential), and the supply voltage, which affects the current flow through the chain Q2, R4, R5 and R6//LS.

A considerable improvement to the output quiescent current stability is given if R4 is replaced by an 'amplified diode' layout of the kind shown in Fig. 2, particularly if Q5 is physically mounted on the heat sink of the output transistors.

The HF stability of the circuit is

also improved if an output Zobel network, typically 100n in series with 8.2 ohms, is connected from the output to the 0V line, effectively in parallel with the loudspeaker. This ensures also that the amplifier will still be stable with the loudspeaker disconnected.

The main HF stabilisation component is an internal HF roll-off capacitor, which can either be connected between the collector of Q2 and Q2 base, or, preferably, from the point of avoiding slew-rate limiting effects, between Q2 collector and Q1 emitter. I have always preferred the latter method.

Overload Indication

If a 'DC bootstrap' circuit (consisting of Q6 and R11 in Fig. 3) is interposed between Q1 and Q2, several advantages follow. The major one is that the gain of both Q1 and Q2 is substantially increased. This happens because the input impedance of the emitter follower in Fig. 1 (Q6) is higher than that provided by Q2, and this greatly increases the stage gain of Q1. In addition, the fact that Q2 is now driven from a very low impedance also increases its stage gain.

I originally introduced this circuit dodge in my '75 watt' amplifier of 1972, and it contributed greatly to the low distortion given by that design. However, a small phase-correcting capacitor, C5, is necessary to prevent the HF stability of the amplifier from being impaired. A further advantage offered by this circuit addition is that the collector current of Q6 (in Fig. 3) increases substantially if the amplifier is

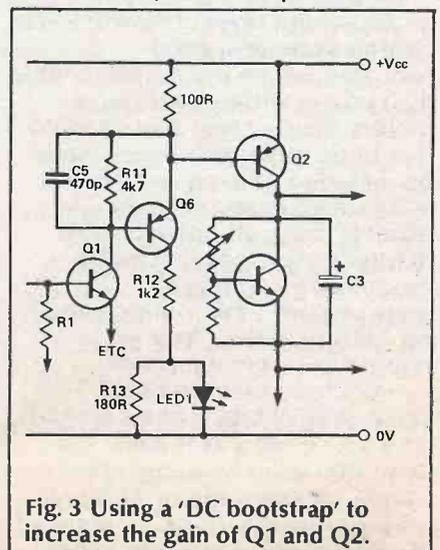


Fig. 3 Using a 'DC bootstrap' to increase the gain of Q1 and Q2.

driven into clipping, and this can be employed to give an indication, by way of LED1, that the amplifier is being over-driven.

The only other point requiring attention concerns the output stage. As it stands, the amplifier circuit of Fig. 1 suffers from a brief 'hang-up' when driven into clipping, which makes the audible effects even worse. This defect can be removed simply by putting a couple of resistors, R14 and R15, in the base leads of the output devices, as shown in Fig. 4. This leads to the final power amplifier circuit shown in Fig. 5.

Circuit Component Value Calculations

Most of these are either not very critical or very straightforward. For example, R1, R2 and R3 are chosen simply to give a base potential at Q1, which will

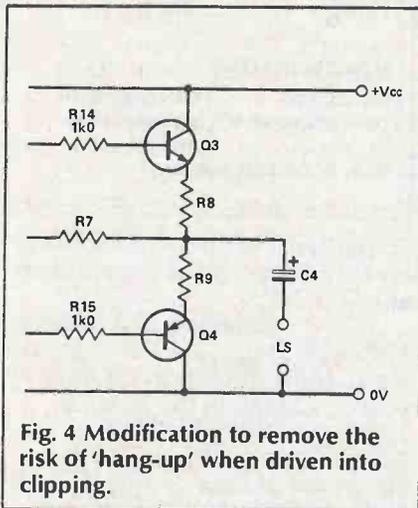


Fig. 4 Modification to remove the risk of 'hang-up' when driven into clipping.

give half the supply voltage at the top end of C7 after allowing for the voltage drops along R4 and R14. R12 is present to allow C7 to charge or discharge if the loudspeaker is not connected, and will prevent a bang sounding if this is connected up after the amplifier is switched on. It also allows the amplifier to work normally even without the LS load.

The value of R11 is chosen to give a DC current through Q3 which is a good bit greater than the likely 2mA peak base currents demanded by Q5 and Q6 at maximum output. The value chosen puts Q3 collector current at about 10mA, which is also high enough to ensure that the charging and discharging of the HF compensation capacitor C5 will not significantly affect the possible rate of change of voltage at Q3 collector, within the audio band.

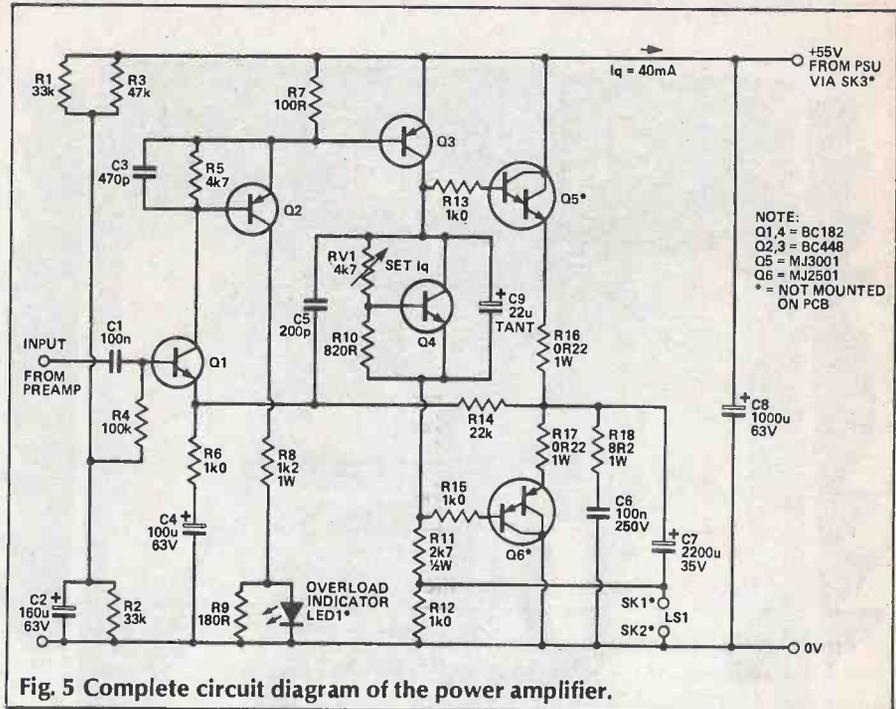


Fig. 5 Complete circuit diagram of the power amplifier.

This helps give a good sound quality. The transistor used for Q3 should be capable of supporting some 80V collector-emitter potential and have a permitted dissipation in excess of 550mW. Apart from this, the type used isn't particularly critical.

R8 and R9 are chosen so that the 5-6mA collector current which flows in Q2 under normal drive conditions will not light up to the LED. This current level would provide about 1V drop across R9. If, however, the amplifier is driven into clipping, Q2 will provide a progressively increased drive current to Q3 and the voltage drop across R9 will increase rapidly and light the LED. R8 is included to limit the worst case current flow to a peak value of 40mA, and also to prevent excessive dissipation in Q2.

At maximum output the amplifier THD is about 0.1% at 1kHz. This is mainly second harmonic, and decreases rapidly at levels below peak power output.

BUYLINES

We understand that some or all of the parts for this project will be available from Hart Electronic Kits Ltd, but we didn't have the time to sort out the details before going to press. We suggest contacting them directly at Penylan Mill, Oswestry, Shropshire SY10 9AF or on 0691-652 894. The boards will also be available from our PCB Service, but see the note in News Digest.


The acoustically objectionable crossover residues, 7th, 9th and 11th harmonics, are all below 0.01% total and so should not be significant.

The Preamp

Although there may be other possible input requirements, the likely signal sources from which the power amplifier will be driven are a music source, such as a battery operated cassette player, and a voice source from a microphone. It will often be more pleasing in effect if these can be present simultaneously, so that the background music can be faded down when the microphone is used, giving a 'voice over' effect.

This suggests that a simple mixer circuit with a couple of volume controls will be preferable to a simple selector switch. This is easy to arrange.

The power amplifier requires an input drive of some 620mV RMS for full output. A typical battery operated cassette recorder output into a high impedance load will be about 250-300mV. If the cassette recorder input circuit in the preamp is simply a unity gain impedance converter stage, included so that the volume control potentiometer doesn't directly load the cassette recorder output, a gain of 2.5x will be necessary between the input buffer and the power amplifier input. This can be given by a

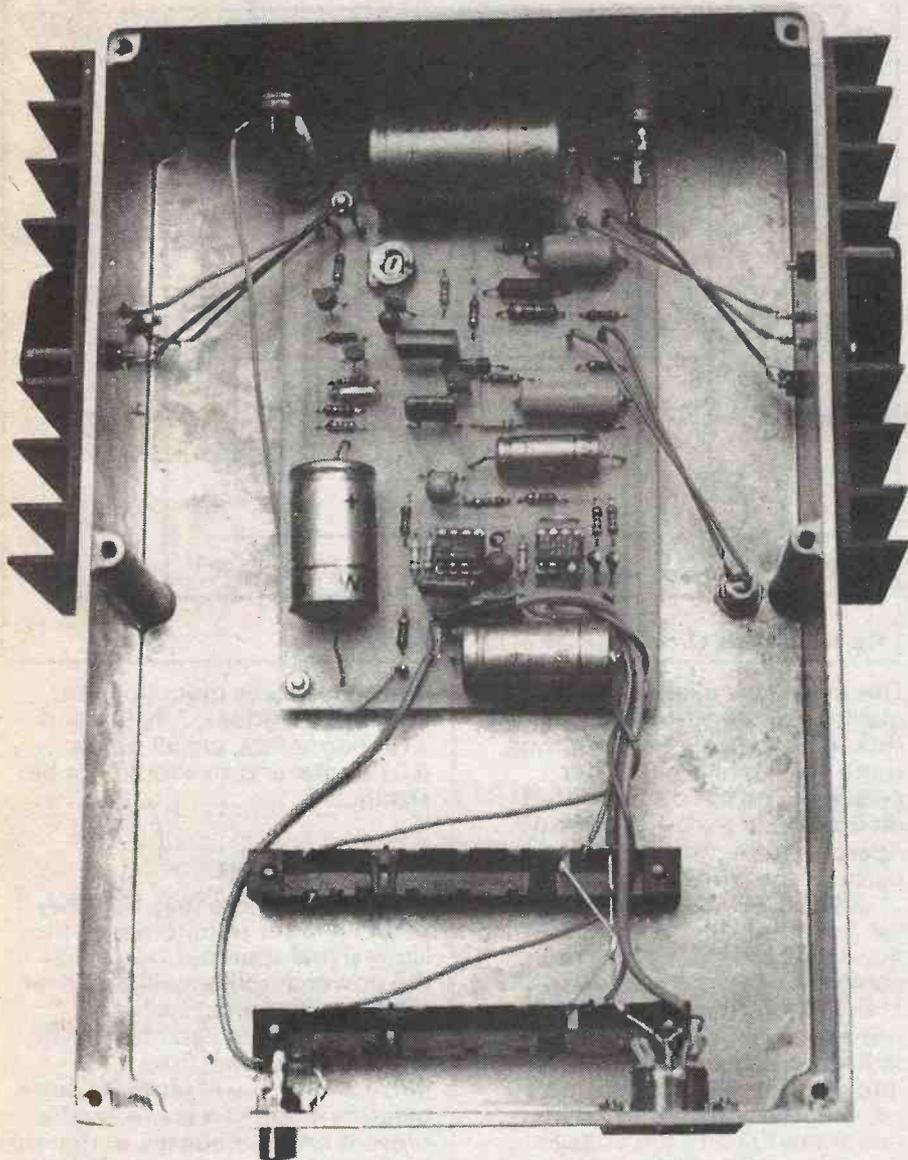

PARTS LIST — PREAMPLIFIER

RESISTORS (all 1/4W 5%)

R101-3	100k
R104	1k Ω
R105, 106	47k
R107	120k
R108	5k Ω
R109, 110	10k
R111	100R
RV101, 102	10k logarithmic slide potentiometer

CAPACITORS

C101, 102	100n
C103	47 μ 16V tantalum
C104-107	1 μ 0 16V tantalum
C108	100 μ 16V tantalum
C109	470 μ 16V axial electrolytic

SEMICONDUCTORS

IC101	TL072
IC102	TL071

MISCELLANEOUS

SK101, 102	DIN, pho or 1/4"
DIN, phono or 1/4"	jack socket as desired
PCB; IC sockets if desired	

virtual earth connected inverting op-amp stage, of the type shown as IC3 in Fig. 6.

IC2 is connected as a straight 100x gain stage for a microphone input. Most microphones have an output voltage in the range 2–10mV, and this will allow adequate gain without the likelihood of overloading IC2. The preamplifier is operated from a 12V DC supply obtained directly from the battery input, with some additional smoothing provided by R11 and C9 to remove any HF generator noise should the unit be operated from a car battery while the engine is running.

No voltage regulation is necessary since the ICs can accept up to 30V DC supply, and it is not possible for a 12V car battery to get much higher than 15.5V even under the worst conditions of overcharge.

On 12V DC, the op-amps can deliver some 3.5–4V RMS, which allows an adequate overload margin to the power amplifier. In practice, if the gain controls are used sensibly, the only op-amp which could overload is IC2, for which the maximum input signal is 40mV RMS.

Although I have only shown two input connections, the circuit

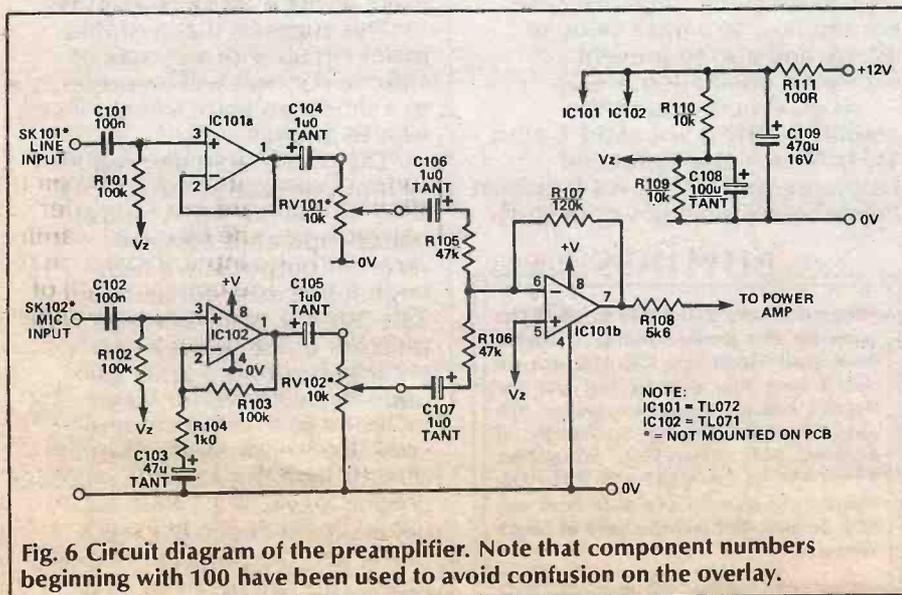


Fig. 6 Circuit diagram of the preamplifier. Note that component numbers beginning with 100 have been used to avoid confusion on the overlay.

PROJECT: PA Amplifier

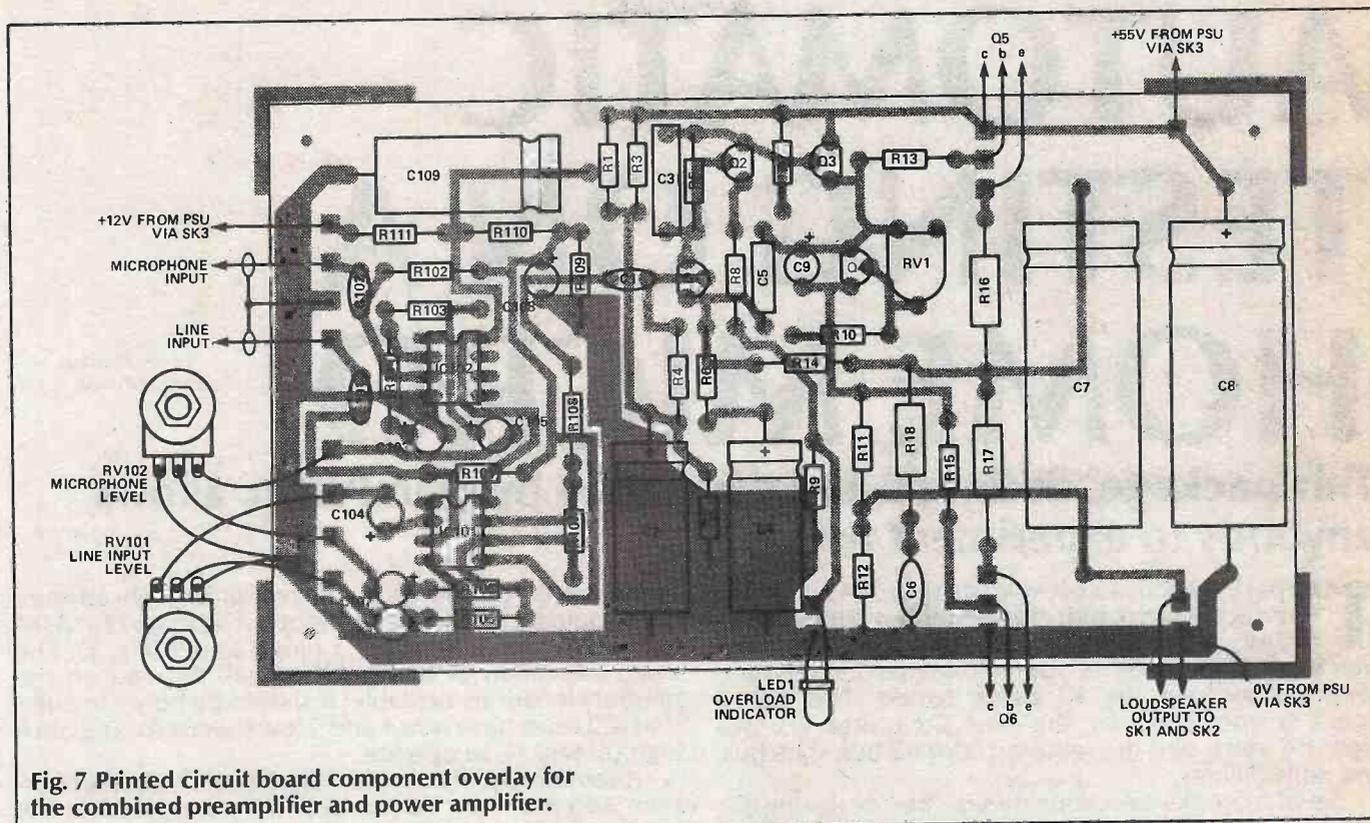


Fig. 7 Printed circuit board component overlay for the combined preamplifier and power amplifier.

PARTS LIST — POWER AMPLIFIER

RESISTORS (all 1/4W 5% unless otherwise stated)

R1, 2	33k
R3	47k
R4	100k
R5	4k7
R6, 12, 13, 15	1k0
R7	100R
R8	1k2 1W
R9	180R
R10	820R
R11	2k7 1/2W
R14	22k
R16, 17	OR22 1W
R18	8R2 1W
RV1	4k7 horizontal skeleton preset

CAPACITORS

C1, 6	100n
C2	150u 63V axial electrolytic
C3	470p
C4	100u 63V axial electrolytic
C5	200p
C7	2200u 35V axial electrolytic
C8	1000u 63V axial electrolytic
C9	22u 16V axial electrolytic

SEMICONDUCTORS

Q1, 4	BC182
-------	-------

Q2, 3	BC448
Q5	MJ3001
Q6	MJ2501
LED1	red LED

MISCELLANEOUS

SK1	red 4mm terminal
SK2	black 4mm terminal
SK3	3 pole chassis-mounting plug (Eg., Bulgin P429 and P646 or P430SE plug to suit)

PCB; heatsinks and insulating sets for Q5 and Q6; diecast metal box; panel-mounting bush for LED1; nuts, bolts, PCB-pillars, etc.

of IC1, RV1 and R7 can be replicated as many times as the user wishes to give additional inputs, the additional feed resistors (as R5 and R6) being taken to the inverting ('virtual earth') input of IC3.

Construction

The pre-amp/power amp combination is built in a 222 x 146mm diecast box. The two output transistors are separately mounted on either side of the box, as shown in the photograph. Individual heat sinks are used since calculations have shown

that, at full power, a dissipation of 50 watts (total) will occur.

Two 10k slider pots are mounted through the top of the box at the opposite end to the power transistor connections and are wired to the PCB using screened cable, as are the input phono/DIN connectors.

Due care should be taken in the layout of the input and output wiring to avoid possible feedback problems, bearing in mind that 2mV at the microphone input will become 14V at the output transistors and loudspeaker terminals at full gain.

No on-off switch is provided

on the PA since there is a power switch on the DC-DC converter unit. The only items present on the PA top panel are the two slider controls and the overload warning LED, with the input sockets on the side wall at the opposite end of the box to the LS output terminals and the power supply input socket.

The quiescent current in the output stage is adjusted by RV1, and this will be correct (although the actual value is not particularly critical) when the total HT current drain from the PA unit is about 40-50mA.

AUTOMATIC TESTING ON A HOME MICRO

This package, designed and developed by Alan Paton, allows anybody to experiment with ATE.

The package consists of two parts, the software and an interface which holds the integrated circuit being tested. The test interface consists of a circuit board which contains three or four integrated circuits and a socket to hold the IC being tested. The circuit board is controlled by the host computer via two eight-bit ports, plus the required address bus, data bus, and control lines.

Several circuits were considered when designing this interface, the main problem being that the two eight-bit ports had to be able to configure any of their bits for input or output in any combination. The data being sent to the IC under test had also to be latched while incoming data was read.

The final circuit, shown as a schematic diagram in Fig. 1, uses a Peripheral Interface adaptor (PIA) to do most of the work. The PIA provides all the facilities required and the chip count for the circuit is minimal.

Properly Addressed

Figure 2 shows the circuit for a Z80 system (in this case, a Spectrum), while a 6502 system configuration is shown in Fig. 3.

For Z80 systems the allocation of ports is decided by the output pin used at IC2. Each pin will select a group of four ports as shown in Table 1.

The port values are assigned at line 60 in the program (Listing 1) and the values are the first and third in the group. For example, if the program uses ports 90-95 (HEX) set A=90H and B=92H.

For 6502 systems, the PIA will have to be memory-mapped which means decoding all 16 address lines

instead of just the first eight. The remaining eight address lines could be taken to an 8-input NAND gate (74LS30) and the output taken to IC3 pins 4 and 5 (Fig. 3). The exact allocation of address lines will depend on the memory locations available. It should be borne in mind that IC2 must have pins 4 and 5 low (binary 0), and pin 6 high (binary 1), to operate.

Alternatively, the circuit of Fig. 3 could be used. Fourteen address lines (A2 to A15) are connected to the inputs of IC4 and IC5. The PIA (IC1) will be selected when all inputs to IC4 are at logic 1 and all inputs to IC5 are at logic 0.

Depending on the system or individual requirements the four consecutive addresses are decoded as follows.

From the combinations of the six 1s and eight 0s the lowest address block possible is 252 to 255 (or 00FCH to 00FFH) which is 0000 0000 111111XX in binary where A15 is the leftmost bit and A0 is the rightmost bit. The two Xs can be either 0 or 1 depending on which of the four locations are selected.

In this example address lines A15 to A8 would be connected to the inputs of IC5 and address lines A7 to A2 would be connected to the inputs of IC4. A0 and A1 are connected directly to the PIA at pins 35 and 36.

The highest address therefore is 64512 to 64515 which is 11111100000000XX in binary. Any location between these extremes may be used, which should cater for any computer system.

For example, a more useful location may be 25000; this converts to 01100001110010XX binary or 61A8H. Connect each address line to a 1 or 0 and the interface can be used at memory locations 25000 to 25003.


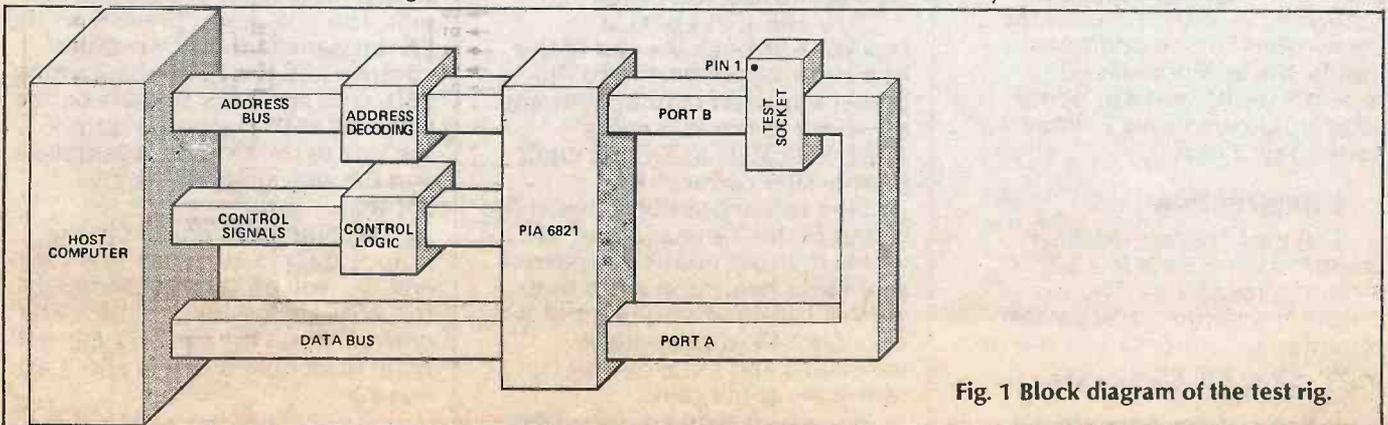


Fig. 1 Block diagram of the test rig.

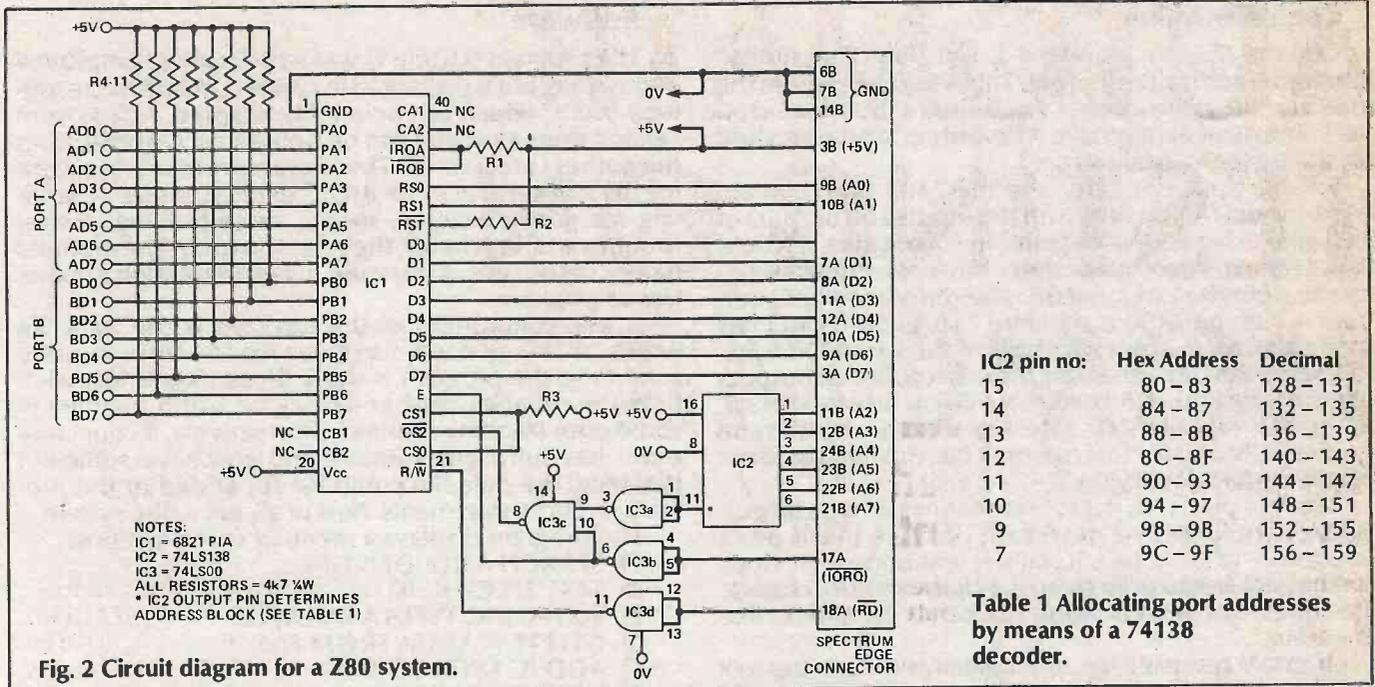

Method Of Testing

In order to test a logic gate for correct function, all possible combinations of logic level could be applied to its inputs while its output is monitored. This, in effect, produces a truth table for the particular function whose states are well known.


The rules of logic prove that the number of tests required to validate one gate is 2 to the power of the number of inputs. To completely test an 8-input NAND gate, for example, would require 256 tests. In practice, a far smaller number is sufficient to identify the device and to prove that it will function correctly. Of course, multiple gate chips can have their gates tested simultaneously.

Provided the tests are carefully considered, four tests for each IC should be sufficient to identify the device and to assess its function. This means that any device with a number of 2-pin input gates will be completely

tested while almost all other devices will be tested with reasonable accuracy.

Power Supply

As it stands, the project is designed to test TTL and TTL-compatible combinational logic chips only. This means that 74, 74LS, 74S, 74F, 74ALS, 74L, 74C, 74HC and 74HCT types are all catered for. The common J and N packages (that is, most of them in everyday use) have supply voltages on the highest number pin and the one diametrically opposite (5V on 14, 16 or 20 and 0V on 7, 8 or 10). Some TTL packages don't obey this convention, so be warned. Some chips are anomalous, the commonest being the 7473 and 7490, 92 and 93. These latter involve sequential logic and are not catered for by the project at present. Testing a chip with unconventional power supply pins will have no damaging effect on the chip or on the interface. The test results will, however, be meaningless.

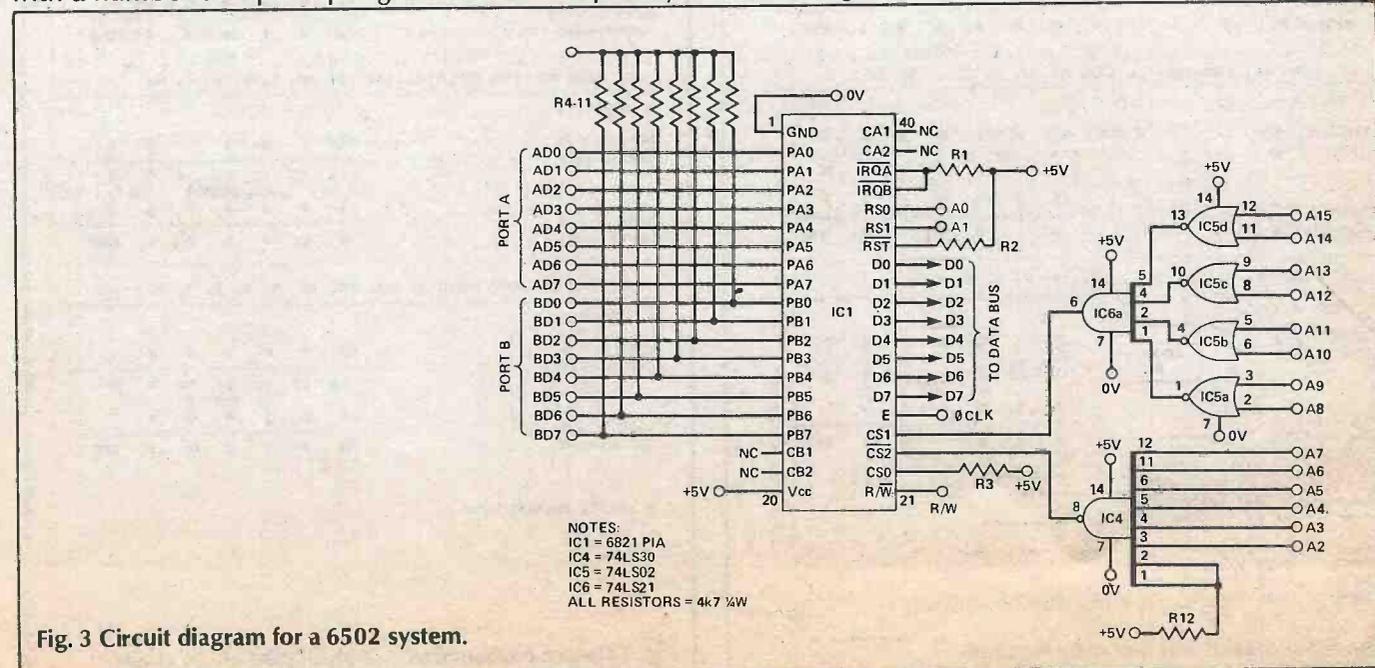

Logically Alike

Certain ICs, as mentioned, are 'logically similar' although electrically different. This is the case where the code number is the same — 7400 and 74LS00, for example. Some devices may have different code numbers and yet still be logically similar.

For example, the 7400 and the 7403 both contain four 2-input NAND gates with the inputs and outputs of each gate using equivalent pins. In some cases, it would be possible to interchange these devices without affecting the operation of a circuit. The difference between them is that the 7400 is standard TTL, but the 7403 has open collector outputs which allow the wired-OR function, achieved by connecting the open collector outputs together and adding an external pull-up resistor. In fact, the quad 2-input NAND gate is one of the most useful ICs available and for this reason it has the longest list of logically equivalent types.

Because of all this, it is sometimes extremely difficult precisely to identify a device. In practice this is not a problem — when a logic IC fails, it fails because it stops working, not because its electrical characteristics change. This does not always apply to other IC types, like amplifiers.

With this test package, any logically similar types will be printed with the result of the test, and since the vast majority of ICs have legible number codes on them, this can be checked against the test identification. The IC is first tested for correct function, then checked with test identification (one or more types) for characteristics.

```

I.C. PINS SET FOR INPUT...12, 11, 9, 8, 2, 3, 5, 6,
-----
[ TEST 1 ]
DATA A = 54          +5V 0 1 1 0 1 1
INP (A)=246
    14 13 12 11 10 9 8
    )      [ 7402 ]
    1 2 3 4 5 6 7
DATA B = 54
INP (B)=246
    0 1 1 0 1 1 GND

I.C. PINS SET FOR INPUT...12, 11, 9, 8, 2, 3, 5, 6,
-----
[ TEST 2 ]
DATA A = 36          +5V 0 0 1 0 0 1
INP (A)=228
    14 13 12 11 10 9 8
    )      [ 7402 ]
    1 2 3 4 5 6 7
DATA B = 36
INP (B)=228
    0 0 1 0 0 1 GND

I.C. PINS SET FOR INPUT...12, 11, 9, 8, 2, 3, 5, 6,
-----
[ TEST 3 ]
DATA A = 18          +5V 0 1 0 0 1 0
INP (A)=210
    14 13 12 11 10 9 8
    )      [ 7402 ]
    1 2 3 4 5 6 7
DATA B = 18
INP (B)=210
    0 1 0 0 1 0 GND

I.C. PINS SET FOR INPUT...12, 11, 9, 8, 2, 3, 5, 6,
-----
[ TEST 4 ]
DATA A = 0          +5V 1 0 0 1 0 0
INP (A)=201
    14 13 12 11 10 9 8
    )      [ 7402 ]
    1 2 3 4 5 6 7
DATA B = 0
INP (B)=201
    1 0 0 1 0 0 GND

Device is 100% Functional
Identified as... Quad 2-Input NOR

Logically similar to...
7402 Quad 2-Input NOR Gate
7428 Quad 2-Input NOR Buffer
7433 Quad 2-Input NOR Gate ( Open Collector )
    
```

Fig. 4 Successful test and identification.

Software

The program (Listing 1) was written for a home-brew Z80 system, but is presented in a fairly standard Microsoft-type BASIC which can be readily adapted. A Spectrum version does exist and can be bought, on cassette, from the author (see below). The biggest problems in adapting the software for other BASIC dialects will be in handling memory allocation, strings, cassette filing, printer routines and, inevitably, the screen display. The modular nature of the program should make adaptation as painless as possible.

A key component of the package is the data file which, as things stand, has to be loaded from cassette each time the program is used. Since data is lost each time the program crashes, it may be worth building in some error trapping routines. Alternatively, if your computer has sufficient memory and you have sufficient patience, the data file could be appended to the program as DATA statements. Best of all, get a disc system.

The program displays a menu of seven options:

- 1) SEARCH AND IDENTIFY
- 2) TEST SPECIFIC IC
- 3) LIST ALL IC TYPES AVAILABLE
- 4) DELETE IC DATA FROM FILE
- 5) ADD IC DATA TO FILE
- 6) LOAD DATA FILE
- 7) SAVE DATA FILE

Initially, there is no data present and only Options 5 or 6 will be accepted. Option 5 enables the user to build up a data file from scratch as well as add to an existing one,

```

I.C. PINS SET FOR INPUT...13, 12, 10, 9, 1, 2, 4, 5,
-----
[ TEST 1 ]
DATA A = 27          +5V 1 1 1 1 1 1
INP (A)=255
    14 13 12 11 10 9 8
    )      [ 7403 ]
    1 2 3 4 5 6 7
DATA B = 27
INP (B)=255
    1 1 1 1 1 1 GND

I.C. PINS SET FOR INPUT...13, 12, 10, 9, 1, 2, 4, 5,
-----
[ TEST 2 ]
DATA A = 18          +5V 0 1 1 0 1 1
INP (A)=246
    14 13 12 11 10 9 8
    )      [ 7403 ]
    1 2 3 4 5 6 7
DATA B = 18
INP (B)=246
    0 1 1 0 1 1 GND

I.C. PINS SET FOR INPUT...13, 12, 10, 9, 1, 2, 4, 5,
-----
[ TEST 3 ]
DATA A = 9           +5V 1 0 1 1 0 1
INP (A)=237
    14 13 12 11 10 9 8
    )      [ 7403 ]
    1 2 3 4 5 6 7
DATA B = 9
INP (B)=237
    1 0 1 1 0 1 GND

I.C. PINS SET FOR INPUT...13, 12, 10, 9, 1, 2, 4, 5,
-----
[ TEST 4 ]
DATA A = 0          +5V 0 0 1 0 0 1
INP (A)=228
    14 13 12 11 10 9 8
    )      [ 7403 ]
    1 2 3 4 5 6 7
DATA B = 0
INP (B)=228
    0 0 1 0 0 1 GND

( DEVICE MALFUNCTION )
    
```

Fig. 5 Device malfunction — output pins stuck at one.

CIRCUIT SOLUTION: Automatic Testing

1)	27	219	27	219	18	246	18	246	9	237	9	237	0	228	0	228	1
2)	54	246	54	246	36	228	36	228	18	210	18	210	0	201	0	201	3
3)	21	213	21	213	5	229	5	229	1	233	1	233	0	234	0	234	5
4)	27	255	27	255	18	210	18	210	9	201	9	201	0	192	0	192	9
5)	29	221	31	223	13	239	13	237	5	231	4	228	0	226	0	224	11
6)	27	223	27	223	18	246	18	246	9	237	9	237	0	228	0	228	19
7)	6	223	63	255	4	249	15	207	2	251	3	195	0	249	0	192	25
8)	27	255	27	255	18	246	18	246	9	237	9	237	0	192	0	192	26
9)	54	246	54	246	36	237	36	237	18	219	18	219	0	201	0	201	2
10)	29	255	29	255	17	209	17	209	21	213	21	213	1	1	1	1	-1
11)	29	255	31	255	17	209	4	196	21	213	22	214	0	192	0	192	12
12)	27	255	27	255	18	214	18	214	9	205	9	205	0	196	0	196	20
13)	27	219	27	219	18	246	18	246	9	237	9	237	0	192	0	192	31
14)	51	243	51	243	34	238	34	238	17	221	17	221	0	192	0	192	34
15)	29	221	31	223	21	213	22	214	8	198	9	199	0	226	0	224	23
16)	-1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
17)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
18)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
19)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
20)	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

Table 2 Contents of sub-file A.

while Option 6 loads a file from cassette.

Once loaded, you can select any of the seven options, returning to the Menu if you want by pressing 'M' on the keyboard.

Option 1 will, if possible, identify an IC, printing out its code number, function and logically equivalent types. Option 2 tests a specified IC, checking whether it is present in the data file or not, printing out the appropriate

identity if it is and the result of the tests (Figs. 4 and 5). Option 3 lists all devices held on file. Option 4 deletes specified devices. Option 5 asks for a device code-number, a functional specification, additional information such as 'open-collector outputs' and the appropriate test data in order to add the device to the file. If the device is already on file, its details will be displayed and the user will be given the chance to change all or some of them.

Option 6 loads the data file from tape. It comprises three 'sub-files' designated A, B and C which are loaded in that order — A containing numerical test data for each IC, B containing numerical device codes and pointers to other information and C containing alphanumeric information on logic functions (see Tables 2, 3 and 4). Option 7 will save a new or amended data file to tape.

Formulation Of Test Data

The IC being tested is held in a socket in the test interface. The connections to these sockets (14, 16 or 20 pins) are shown in Fig. 6. Port A of the test interface's 6821 PIA controls the high number pins and Port B controls the low number pins. Each IC requires 16 numbers as test data since there are four tests and each test uses four data numbers. Each group of four numbers (one test) consists of two codes to be sent to Ports A and B and two codes to be compared with the data received from Ports A and B.


	Device Code		Pointers		
1)	7400	1	1	0	1
2)	7402	1	1	3	9
3)	7402	2	1	0	2
4)	7403	1	1	3	1
5)	7404	3	0	0	3
6)	7405	3	3	0	3
7)	7406	9	3	4	3
8)	7407	9	3	4	3
9)	7408	4	1	0	4
10)	7409	4	1	3	4
11)	7410	5	1	0	5
12)	7411	10	1	0	11
13)	7412	5	1	3	5
14)	7413	6	5	0	6
15)	7414	11	5	0	3
16)	7415	10	1	3	11
17)	7416	9	3	4	3
18)	7417	9	3	4	3
19)	7420	6	1	0	6
20)	7421	12	1	0	12
21)	7422	6	1	3	6
22)	7426	1	1	4	1
23)	7427	13	1	0	15
24)	7428	2	2	0	2
25)	7430	7	1	0	7
26)	7432	8	1	0	8
27)	7433	2	3	0	2
28)	7437	1	2	0	1
29)	7438	1	2	3	1
30)	7440	6	2	0	6
31)	7486	14	1	0	13
32)	74132	1	5	0	1
33)	74136	14	1	3	13
34)	74266	14	1	3	14
35)	74386	14	1	0	14
36)	-1	-1	-1	-1	-1
37)	0	0	0	0	0
38)	0	0	0	0	0
39)	0	0	0	0	0
40)	0	0	0	0	0

Table 3 Contents of sub-file B.


	Array T\$
1)	Quad 2-Input NAND
2)	Quad 2-Input NOR
3)	Hex Inverter
4)	Quad 2-Input AND
5)	Triple 3-Input NAND
6)	Dual 4-Input NAND
7)	8-Input NAND
9)	Quad 2-Input OR
9)	Hex Buffer
10)	Triple 3-Input AND
11)	Hex
12)	Dual 4-Input AND
13)	Triple 3-Input NOR
14)	Quad 2-Input EX-OR
15)	EOF
16)	
17)	
18)	
19)	
20)	

Table 4 Contents of sub-file C and of array T\$.

Consider the 7400 (Fig. 7). The inputs to the four NAND gates are pins 1, 2, 4, 5, 9, 10, 12 and 13. It should be clear that to send a high to each of these pins involves taking PA0, PA1, PA3, PA4, PB0, PB1, PB3 and PB4 high. Taking binary weighting into account (PA_n and PB_n each correspond to 2ⁿ), this means sending a 27 to Port A and a 27 to Port B. This is done on the 6821 in a fairly round-about manner.

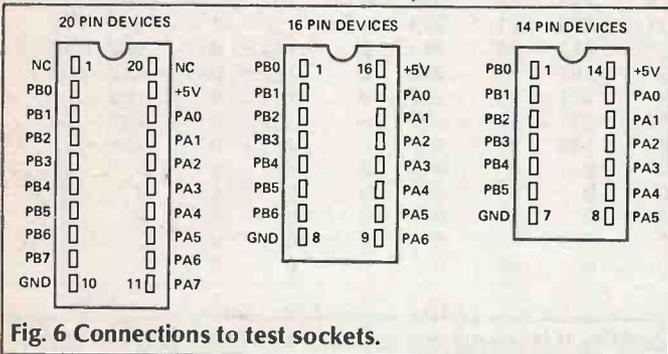

First, the data direction registers for Ports A and B must be set to receive data. This is achieved by setting bit 2 of the control registers for Ports A and B to 0. If Port A's address is 144 (as here) then its control register will be located at address 145. To write to Port A, bit 2 of location 145 must be set to zero. This is done in the program by the command OUT A+1,0 (line 680), where A equals 144 or 90H (line 60). Then the inputs to the chip under test must be set up by configuring them as outputs from the two ports. As far as Port A is concerned, this is done by means of the command OUT A,A(J,K) (line 690), where A is 144 again and A(J,K) is the test data — the number 27 we discussed above. This ensures that the right pins on the IC under test are connected to outputs from the 6821. All the port lines on the 6821 not configured as outputs will be treated as inputs and will be ignored by the 6821 when data is sent to the IC under test.

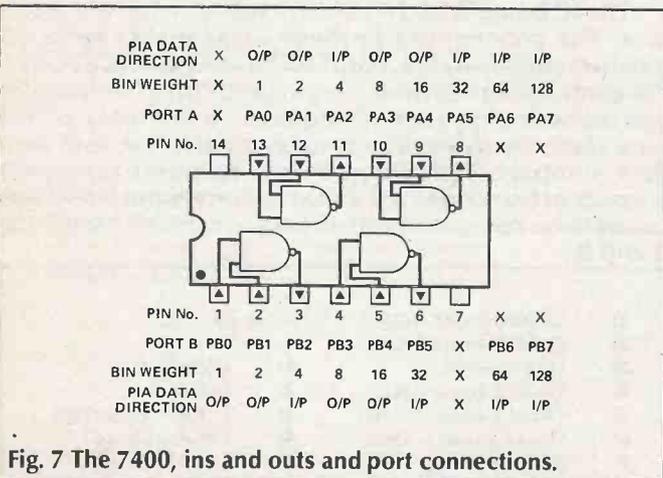

Line 700 in the program then resets bit 2 of the control registers by actually setting all bits high (OUT A+1,255). Now the program has access to the peripheral hanging off the ports and all the right lines have been set to outputs and inputs. In line 830 (and in line 390, for that matter), we find the command OUT A,A(J,K) again. Having sent 27, in the first instance, to Port A we now seem to be doing it again. The difference is that this time the command actually writes logical highs to the port lines which were defined as outputs the first time 27 was sent to Port A. In line 804, inputs from Port A and Port B appear in the guise of the functions INP(A) and INP(B). These read their respective ports and return numbers composed of

values from every line or bit of the ports. The value read from input lines will be determined by whatever is connected to those lines. The values read from the output lines will normally be whatever value was last written to those lines. (The only problem arising when Port A — and only Port A — is so heavily loaded that voltages on the data lines fall below 2V for a high or rise above 0.8V for a low).

Thus, if we send 27 to Port A and the 7400 is working properly, pins 11 and 8 and hence lines PA2 and PA5 will be low. The remaining data lines, PA6 and PA7, are held high by internal pull-up resistors (the Port B lines all have external pull-ups). The result will be that a read operation on Port A will return 27+64+128 — or binary 11011011 — or decimal 219. This number appears as the second (and fourth) item in data file A's entry for the 7400 and is, therefore, the value ascribed to A(J,K+1) (and A(J,K+3)). Line 840 (and line 400) of the program test that the value returned from read operations on Ports A and B does correspond to the proper data file entry. If there is any error, a device malfunction can be assumed under Option 2 of the program menu, or under Option 1, non-equivalence of the device under test and a library device follows.

The complete test data (held on sub-file A) for a 7400 quad 2-input NAND gate is:
 27 219 27 219 18 246 18 246 9 237 9 237 0 228 0 228.
 The format being 1) data out to Port A, 2) comparison data for Port A read operation, 3) data out to Port B, 4) comparison data for Port B read operation. The next group of four numbers form the second test, then come the third and fourth tests. Between them, they exhaust all possible input conditions for this IC.

A complete set of test data can be simply built-up by reference to a pin-out diagram and a functional specification of any device, bearing in mind the connections from the PIA ports to the test sockets. After entering a new device, the data can be verified by an actual test using a known functioning IC. Test data can be displayed and printed in order to help locate any mistakes in the test data or any malfunction of a device under test. The new data file should be saved to tape using Option 7. As it stands, the program includes too little in the way of error-checking and can crash quite easily. Each time it does, your data will be lost.

Program Structure And Operation

The program can be split into seventeen sections. It is menu driven with seven of the sections being the options already listed. These, in turn, call subroutines as required before returning to the menu.

The program was designed to be easily expandable and adaptable to other types of IC. For this reason, fixed length files are not used. During program execution, frequent checks are made when accessing files to ensure that the end of file has not been reached. This slows down the speed of execution but, in practice, the devices tested with the current data files appear to be identified immediately when data is available.

The arrays are dimensioned in line 50 of the program; this is a requirement of BASIC and if larger files were required for future use these dimensions would have to be changed and the new program copy saved. This also applies to array T\$ which is loaded from data at line 2740. If different data were required, items would have to be added or changed at this line.

The structure of the arrays has been designed to make as efficient use of memory as possible, and where data could be duplicated the use of pointers has avoided this.

CIRCUIT SOLUTION: Automatic Testing

Only 14 different sets of test data are used, but the package can test and identify 35 different IC types. Table 3 shows most clearly how pointers are used to maximize memory use.

Array Structure

Array A, which has been described during the formulation of test data, is two-dimensional with each row holding the 16 test numbers plus a pointer to an IC identified by this data. There may be more than one IC which could be identified from this data and, because of the design of the program, it does not matter which of the logically similar ones it is.

If the first element of a row, A(n,1), contains -1 this is the 'end of file' marker. The last element, A(n,17), of a row is -1 when test data has been erased.

Array B is two-dimensional with each row holding data as follows:

- B(n,1) Numerical device code. A -1 is the 'end of file' marker;
- B(n,2) Pointer to an element of array C\$ which describes the function of the device;
- B(n,3) Pointer to an element of array T\$ which describes the type of device;
- B(n,4) Also pointer to array T\$ if there is any further information (zero if none);
- B(n,5) Pointer to array A which contains the test data for device B(n,1). If this element contains -1 then the data has been erased.

C\$ is a one-dimensional alphanumeric array containing all the IC functions. It is referenced by B above during program execution. EOF is the 'end of file' marker.

Table 5 Program variables.

Variable	Function
C	Temporary counter
Q	Holds value of option chosen (1-7).
LD	Data file flag. If LD=0 file is empty. If LD=2 file contains data.
J, K, O	Temporary counters.
C1	Used to reference array B, as in B(C1,1).
L\$	String containing a row of dashes half of screen width.
Q\$	Holds single character from keyboard scan
A, B	Address of ports used for testing, 90H and 92H in this case.
T	Counts number of tests made for display of test process.
D	Decimal number to be converted to binary.
A\$	Binary number to be displayed alongside IC being tested, to show logic levels.
S\$	Holds single character from keyboard scan.
PN\$	Holds pin numbers used for input during display of test process.
P9	Temporary count, used when translating pin numbers from binary string A\$.
DN, DT	Holds device number and device type number.
A1	Temporary count, used in loop to display test data.
X	Free element of array B. Used when adding IC to data file.
CR	Change Record flag. If CR=0 then IC data already on file is being amended.
DF\$	Holds device function
D1	Temporary store for pointer. Used when deleting IC from file.
A(X,Y)	Two dimensional array, holds test data for all ICs on file, also the last element in each row holds a pointer to array B.
B(X,Y)	Two dimensional array, holds device codes and pointers to arrays A, C\$ and T\$.
C\$(X)	One dimensional array, holds IC functions.
T\$(X)	One dimensional array, holds further device information.

T\$ is a one-dimensional alphanumeric array containing further device information. It also is referenced by B above during program execution. EOF is the 'end of file' marker.

Doing it Yourself

The hardware requires very little effort to modify for your own system or to build. The author's original circuit was built on strip-board, looks fine and works well.

The program as it stands requires very little modification to work on an Amstrad, BBC or Commodore 64 computer, once you have sorted out the hardware addressing. The circuit given in Fig. 2 works with a Spectrum and Spectrum+ and the author will provide suitable software on cassette. The price is £2 inclusive of p&p from Alan Paton, 67 Bradford Road, Trowbridge, Wiltshire BA14 9AN. Please make cheques payable to Alan Paton.

Listing 1 The IC Functional Test Program.

```

10 REM *****
20 REM FUNCTIONAL TEST OF INTEGRATED CIRCUITS A.D.Paton.
30 REM *****
40 REM .... INITIALISATION
50 CLEAR 500: DIM A(20,17), B(40,5), C$(20), T$(10)
60 A=$90: B=$92: L$="-----";
70 C=0
80 C=C+1: READ T$(C)
90 IF T$(C) <> "EOF" THEN 80
100 A(1,1)=-1: B(1,1)=-1: C$(1)="EOF"
110 REM *****
120 REM ===== TITLE AND OPTIONS =====
130 REM *****
140 CLS : PRINT STRING$(64,42): PT=0: P=0: CR=0: Q$=""
150 PRINT : TAB(11) "INTEGRATED CIRCUIT FUNCTIONAL TEST PACKAGE"
160 PRINT : PRINT STRING$(64,42)
170 PRINT : PRINT TAB(14) "1) SEARCH AND IDENTIFY"
180 PRINT TAB(14) "2) TEST SPECIFIC I.C."
190 PRINT TAB(14) "3) LIST ALL I.C. TYPES AVAILABLE"
200 PRINT TAB(14) "4) DELETE I.C. DATA FROM FILE"
210 PRINT TAB(14) "5) ADD I.C. DATA TO FILE"
220 PRINT TAB(14) "6) LOAD DATA FILE"
230 PRINT TAB(14) "7) SAVE DATA FILE"
240 PRINT : PRINT TAB(18) "Select option (1 to 7)....";
250 GET Q: IF Q < 1 OR Q > 7 THEN 250
260 CLS : IF LD=2 OR Q=5 OR Q=6 THEN 280
270 GOSUB 1250: GOTO 110
280 ON Q GOSUB 330, 750, 970, 2350, 1540, 2610, 2680
290 GOTO 110
300 REM *****
310 REM ===== FUNCTIONAL TEST ROUTINE =====
320 REM *****
330 J=0
340 J=J+1
350 IF A(J,1) < 0 THEN GOSUB 630: RETURN
360 IF A(J,17) < 0 THEN 340
370 FOR K=1 TO 13 STEP 4
380 IF K=1 THEN GOSUB 600
390 OUT A, A(J,K): OUT B, A(J,K+2)
400 IF A(J,K+1) <> INP(A) OR A(J,K+3) <> INP(B) THEN 340
410 NEXT K
420 C1=A(J,17)
430 REM *****
440 REM ===== TEST O.K. ROUTINE =====
450 REM *****
460 PRINT : PRINT "Device is 100% Functional"
470 PRINT "Identified as... "; J=0
480 PRINT C$(B(C1,2)): PRINT : PRINT "Logically similar to..."
490 J=J+1: IF B(J,1) < 0 THEN 520
500 IF B(J,5)=B(C1,5) THEN PRINT B(J,1), C$(B(J,2)), T$(B(J,3)), T$(B(J,4))
510 GOTO 490
520 GOSUB 2780
530 PRINT L$: PRINT " D...Display Test Process P...Print Test Process M...MENU"
540 PRINT TAB(20) "Select Option (D,P or M)...": J=B(C1,5): PRINT L$:
550 GET Q$: IF Q$="" THEN 550
560 IF Q$="D" THEN CLS : GOSUB 1050: RETURN
570 IF Q$="P" THEN CLS : GOSUB 1040: RETURN
580 IF Q$="M" THEN RETURN
590 GOTO 550
600 REM *****
610 REM ===== TEST FAIL ROUTINE =====
620 REM *****
630 PRINT "Device malfunction or insufficient data."
640 GOSUB 1260: RETURN
650 REM *****
660 REM ===== Set up PIA for required input bits. =====
670 REM *****
680 OUT A+1,0: OUT B+1,0
690 OUT A, A(J,K): OUT B, A(J,K+2)
700 OUT A+1,255: OUT B+1,255
710 RETURN
    
```

CIRCUIT SOLUTION: Automatic Testing

```
720 REM *****
730 REM ===== TEST SPECIFIC TYPE =====
740 REM *****
750 PRINT "Enter No. of device to be tested (omit any letters)"
760 INPUT "...";DT:C=0:PRINT
770 C=C+1:IF B(C,1)<0 THEN THEN 800
780 IF B(C,5)=-1 THEN THEN 770
790 IF B(C,1)=DT THEN J=B(C,5) ELSE 770
800 C1=C:GOSUB 920
810 FOR K=1 TO 13 STEP 4
820 IF K=1 THEN GOSUB 680
830 OUT A,A(J,K):OUT B,A(J,K+2)
840 IF A(J,K+1)<INP(A) OR A(J,K+3)<INP(B) THEN 870
850 NEXT K
860 GOSUB 460:RETURN
870 PRINT:PRINT "( DEVICE MALFUNCTION )":GOSUB 520:RETURN
880 PRINT "No record of I.C. type "DT" on file.":PRINT:GOSUB 12
60:RETURN
890 REM *****
900 REM ===== PRINT I.C. No. and TYPE =====
910 REM *****
920 PRINT "Number ..... "B(C1,1)
930 PRINT "Type ..... "C$(B(C1,2));T$(B(C1,3));T$(B(C1,4))
:RETURN
940 REM *****
950 REM ===== LIST ALL I.C. TYPES =====
960 REM *****
970 C=0:PRINT
980 C=C+1:IF B(C,1)<0 THEN GOSUB 1260:RETURN
990 IF B(C,5)=-1 THEN 980
1000 PRINT B(C,1),C$(B(C,2));T$(B(C,3));T$(B(C,4)):GOTO 980
1010 REM *****
1020 REM ===== DISPLAY OR PRINT PROCESS =====
1030 REM *****
1040 GOSUB 2760
1050 T=0:FOR K=1 TO 13 STEP 4
1060 IF K=1 THEN GOSUB 680:GOSUB 1320
1070 OUT A,A(J,K):OUT B,A(J,K+2)
1080 PRINT "I.C. PINS SET FOR INPUT..."PN$:PRINT L$&L$
1090 A9=INP(A):B9=INP(B)
1100 T=T+1:PRINT "[ TEST "T" ]":PRINT
1110 D=A9:GOSUB 1440:PRINT "DATA A =":A(J,K)TAB(31)+5V "A$
1120 PRINT "INP(A)="+A9TAB(30)L$
1130 PRINT TAB(32)"14 13 12 11 10 9 8":PRINT TAB(30)"
[ "B(C1,1)" ]"
1140 PRINT TAB(32)"1 2 3 4 5 6 7"
1150 PRINT "DATA B =":A(J,K+2)TAB(30)L$
1160 D=B9:GOSUB 1440:PRINT "INP(B)="+B9:PRINT TAB(32)"A$GND"
1170 PRINT:PRINT "IF Q$="P" THEN NEXT K:GOSUB 810:RETURN
1180 PRINT:PRINT "Press M for MENU - any key to continue test"
1190 GET S$:IF S$="M" THEN 1190
1200 IF S$<>"M" THEN NEXT K
1210 RETURN
1220 REM *****
1230 REM ===== KEYBOARD SCAN =====
1240 REM *****
1250 PRINT "No data available .....Please LOAD DATA FILE"
1260 PRINT:PRINT "Press M to return to MENU";
1270 GET Q$:IF Q$<>"M" THEN 1270
1280 RETURN
1290 REM *****
1300 REM ===== LOCATE PIN NUMBERS =====
1310 REM *****
1320 PN$="":D=A(J,K):GOSUB 1440:P9=13
1330 FOR O=1 TO 24 STEP 4
1340 IF MID$(A$,O,1)="1" THEN PN$=PN$+STR$(P9)+", "
1350 P9=P9+1:NEXT O
1360 D=A(J,K+2):GOSUB 1440:P9=1
1370 P9=1:FOR O=1 TO 24 STEP 4
1380 IF MID$(A$,O,1)="1" THEN PN$=PN$+STR$(P9)+", "
1390 P9=P9+1:NEXT O
1400 RETURN
1410 REM *****
1420 REM ===== DECIMAL TO BINARY ROUTINE =====
1430 REM *****
1440 A$=""
1450 IF D=0 THEN A$="0 0 0 0 0 0 0 0":RETURN
1460 IF INT(D/2)=D/2 THEN A$=A$+"0 "":D=D/2:GOTO 1460
1470 A$=A$+"1 "":D=D-1:IF D=0 THEN D=D/2:GOTO 1460
1480 IF LEN(A$)>24 THEN A$=A$+"0 "":GOTO 1480
1490 IF LEN(A$)>24 THEN A$=LEFT$(A$,24)
1500 RETURN
1510 REM *****
1520 REM ===== ADD I.C. DATA TO FILE =====
1530 REM *****
1540 PRINT "* ADD I.C. DATA TO FILE"
1550 PRINT:INPUT "Enter Device No. (or -1 to return to MENU)...
":DN
1560 IF DN<0 THEN RETURN
1570 REM ...Is device on file ?
1580 J=0
1590 J=J+1:IF B(J,1)=-1 THEN 1680
1600 IF B(J,5)=-1 THEN 1590
1610 IF B(J,1)<>DN THEN 1590
1620 PRINT:PRINT "Device "DN" is on file with the following dat
a..."C1=J:GOSUB 920
1630 A1=B(J,5):PRINT:FOR K=1 TO 16:PRINT A(A1,K) "":NEXT K
1640 GOSUB 1980
1650 IF Q$="N" THEN RETURN
1660 IF Q$="Y" THEN X=J:CR=1:GOTO 1740
1670 REM ...Device not found - find free location in File B
result into X
1680 J=0
1690 J=J+1:IF B(J,1)=-1 THEN B(J+1,1)=-1:GOTO 1720
1700 IF B(J,5)=-1 THEN 1720
1710 GOTO 1690
1720 X=J:B(X,1)=DN
1730 REM ...Get device details for data file
1740 IF CR=1 THEN PRINT "Current function..."C$(B(X,2)):GOSUB 19
80
1750 IF Q$="N" THEN 1800
1760 PRINT "Enter Device Function"
1770 INPUT " (or L to list Functions on file)...":DF$
1780 IF DF$="L" THEN GOSUB 2290:PRINT:GOTO 1740
1790 IF CR=0 THEN GOSUB 2230 ELSE C$(B(X,2))=DF$
1800 IF CR=0 THEN 1830
1810 PRINT "Current further details are..."B(X,3);T$(B(X,3)),B(X
,4);T$(B(X,4))
1820 GOSUB 1980:IF Q$="N" THEN 1860
1830 PRINT "Enter further device details (No.1,No.2)"
1840 INPUT " (or 0,0 to list details available)...":B(X,3),B(X,4
)
1850 IF B(X,3)=0 AND B(X,4)=0 THEN GOSUB 2190:PRINT:GOTO 1800
1860 GOSUB 2030:IF CR=0 THEN 1880
1870 GOSUB 2150:GOSUB 1980:IF Q$="N" THEN 1960
1880 PRINT:PRINT "Enter test data (16 integer numbers)..."
1890 FOR K=1 TO 16:PRINT K"...":
1900 IF CR=1 THEN PRINT "Current test data..."A(B(X,5),K);
1910 INPUT "...":A(A1,K)
1920 IF A(A1,K)<0 OR A(A1,K)>INT(A(A1,K)) THEN PRINT "INCORRECT
DATA":K=K-1
1930 NEXT K
1940 A(A1,17)=X:B(X,5)=A1
1950 GOSUB 2080:GOTO 1580
1960 RETURN
1970 REM ...Get YES or NO response
1980 PRINT:PRINT "* Change data ? (Y or N) "
1990 GET Q$:IF Q$="Y" THEN 1990
2000 IF Q$<>"Y" AND Q$<>"N" THEN 1980
2010 RETURN
2020 REM ...Find free location in array A (result into A)
2030 J=0
2040 J=J+1:IF A(J,1)<0 THEN A1=J:A(J+1,1)=-1:RETURN
2050 IF A(J,17)<0 THEN A1=J:RETURN
2060 GOTO 2040
2070 REM ...Is same test data already in use ?
2080 J=0
2090 J=J+1:IF A(J,1)<0 THEN RETURN
2100 IF J=A1 THEN 2090
2110 FOR K=1 TO 16:IF A(J,K)<>A(A1,K) THEN 2090
2120 NEXT K
2130 B(X,5)=J:A(A1,17)=-1:RETURN
2140 REM ...Print test data from array A
2150 PRINT "Current test data is..."
2160 FOR K=1 TO 16:PRINT A(B(X,5),K) "":NEXT K
2170 RETURN
2180 REM ...Print contents of array T$
2190 J=0
2200 J=J+1:IF T$(J)="EOF" THEN RETURN
2210 PRINT J,T$(J):GOTO 2200
2220 REM ...Is Device Function (DF$) already in array C$ ?
2230 J=0
2240 J=J+1:IF C$(J)="EOF" THEN 2260
2250 IF C$(J)=DF$ THEN 2270 ELSE 2240
2260 C$(J)=DF$:C$(J+1)="EOF"
2270 B(X,2)=J:RETURN
2280 REM ...Print contents of array C$
2290 J=0
2300 J=J+1:IF C$(J)="EOF" THEN RETURN
2310 PRINT J,C$(J):GOTO 2300
2320 REM *****
2330 REM ===== DELETE I.C. FROM FILE =====
2340 REM *****
2350 PRINT "* DELETE I.C. FROM FILE"
2360 PRINT:INPUT "Enter Device No. (or -1 to return to MENU)...
":DN
2370 IF DN<0 THEN RETURN
2380 J=0
2390 J=J+1:IF B(J,1)=-1 THEN PRINT "Device No. "DN" not on file."
:GOTO 2360
2400 IF B(J,5)=-1 THEN 2390
2410 IF B(J,1)<>DN THEN 2390
2420 C1=J:PRINT "The following device to be deleted from file :-
":GOSUB 920
2430 PRINT:PRINT TAB(22)"Confirm or Reject ? (C or R)"
2440 GET Q$:IF Q$="C" THEN 2440
2450 IF Q$="R" THEN RETURN
2460 IF Q$<>"C" THEN 2360
2470 D1=B(C1,5)
2480 IF C1>A(D1,17) THEN B(C1,5)=-1:RETURN
2490 B(C1,5)=-1:J=0
2500 J=J+1:IF B(J,1)<0 THEN GOSUB 2540:RETURN
2510 IF B(J,5)=D1 THEN A(D1,17)=J:RETURN
2520 GOTO 2500
2530 REM ...Delete test data from FILE A
2540 K=0
2550 K=K+1:IF A(K,1)<0 THEN RETURN
2560 IF A(K,17)=C1 THEN A(K,17)=-1
2570 GOTO 2550
2580 REM *****
2590 REM ===== LOAD DATA FILES =====
2600 REM *****
2610 PRINT "* LOAD DATA FILES"
2620 INPUT "Start TAPE and press RETURN";Q$
2630 LOAD ("FILE A")@A:LOAD ("FILE B")@B:LOAD ("FILE C")@C$
2640 LD=2:RETURN
2650 REM *****
2660 REM ===== SAVE DATA FILES =====
2670 REM *****
2680 PRINT "* SAVE DATA FILES"
2690 INPUT "Start TAPE and press RETURN";Q$
2700 PRINT "FILE A":SAVE ("FILE A")@A
2710 PRINT "FILE B":SAVE ("FILE B")@B
2720 PRINT "FILE C":SAVE ("FILE C")@C$
2730 RETURN
2740 DATA "Gate","Buffer","( Open Collector )","( High Voltage )
","Schmitt Trigger","EOF"
2750 REM ...Switch on printer
2760 POKE $1401,$55:PRINT:RETURN
2770 REM ...Switch off printer
2780 POKE $1401,$AA:RETURN
```

NEXT
MONTH

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

COMING TO THESE PAGES SOON

Etienne Scrooge yawned, scratched himself and got up from his chair. 'June,' he said to himself, 'is busting out all over.' With that out of the way, he found himself with a little time on his hands. It was half an hour. He rushed to the window, seized with a sudden irrational fear. Luckily, the window was open and Etienne immediately proceeded to shake his hands vigorously in the air. The half an hour soared up and away. 'Time flies', Etienne muttered. He breathed a sigh of relief for the time had been weighing heavily.

Turning from the open window, Etienne was aghast to notice the other half of the hour on the floor by the chair he had only recently been occupying. It was very still and Etienne wondered whether it had been standing that way for long. It certainly didn't look longer than a few minutes, which — in fact — it wasn't. Etienne picked it up gingerly and with something more like auburn he tip-toed out of the room. 'I suppose you could call this "taking my time"', Etienne thought.

No sooner had he stepped outside into the hall when the first half of the hour burst through the front door and raced by. It was musical time, and it had the right key. The second half sprang into action and pursued its one-time partner all the way down the road to the shops. 'Time,' thought Etienne, 'waits for no man.' On his way to work, Etienne found a few minutes in the newsagents to pick up the latest copy of ETI. Curiously, there was almost nothing about time in it. 'That sounds like the cue for a song,' Etienne thought. But it wasn't.

The Upgradeable Amp

Easy for the beginner to build, yet equally easy to upgrade into a quality amp, this design represents one school of audio thought in practice. Designer Graham Nalty will explain exactly why each critical component has been used and how each stage of upgrading can be accomplished. The result is an amplifier which at the most basic level provides outstanding quality for the cost of building it and, when fully upgraded, quite simply provides outstanding quality.

RF Oscillators

In this general feature on radio frequency oscillators, design considerations and actual circuits are examined. These circuits are not only vital to communications devices, but can also be the basis of valuable test equipment and clock-controlled digital circuits.

MIDI to CV Converter

Music to the ears of all those readers with pre-digital synthesizers. This project by Robert Penfold will allow full digital control of these instruments using the MIDI protocol as an input and a 1V per octave control signal as an output.


PLUS

All our usual features. Tech Tips, News Digest, Read/Write, Circuit Solutions, Reviews, Open Channel, and much, much more.

THE JUNE ISSUE OF ETI ON SALE MAY 2nd
MAKE YOUR SUMMERTIME SPECIAL


Articles described here are at an advanced stage of preparation but circumstances beyond our control may dictate changes to the final list of contents.



PCB FOIL PATTERNS

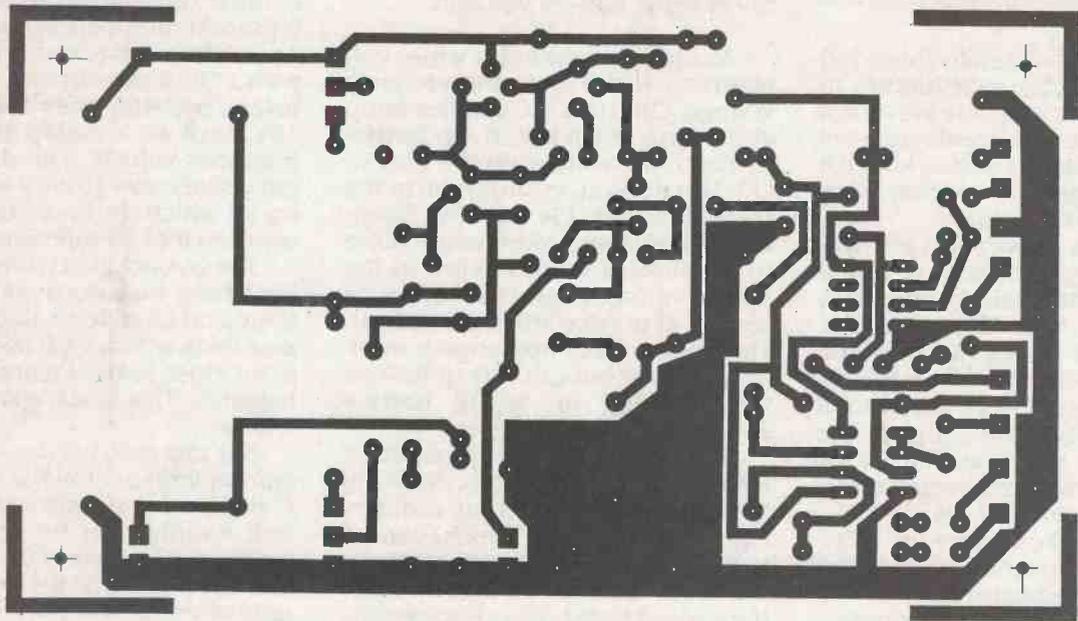

The foil pattern for the JLLH PA amplifier board.

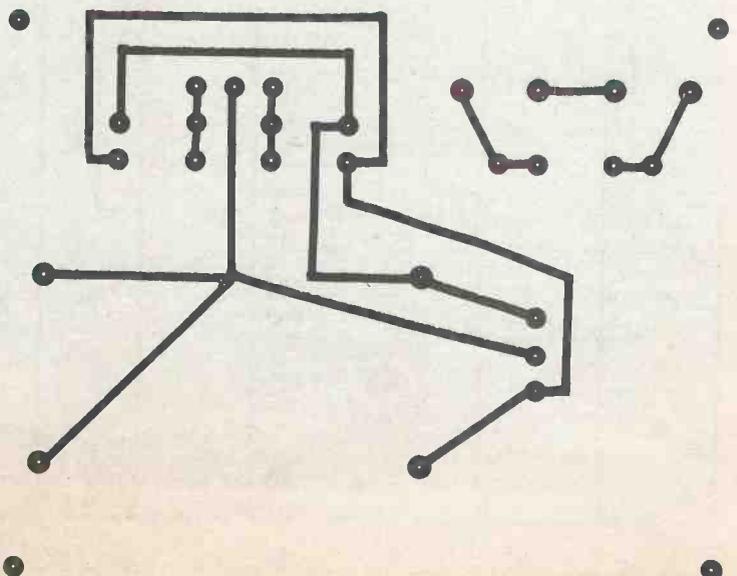The foil patterns for the Baud Rate Converter main board (opposite) and the optional PSU board (below).



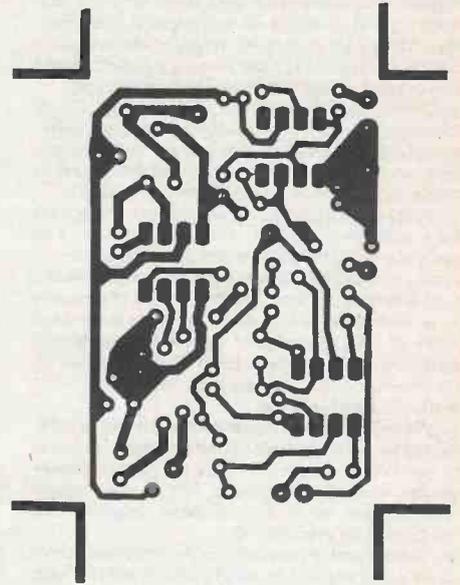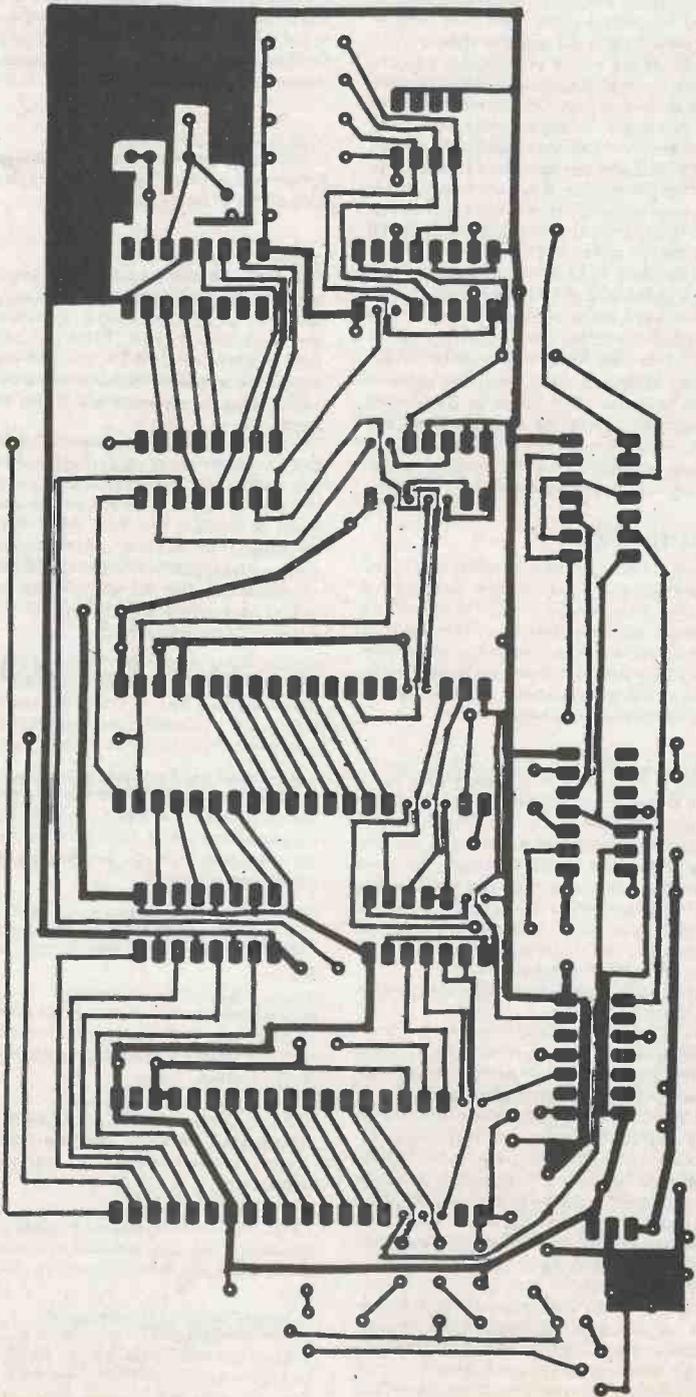

The pattern for the Microlight Intercom board.

SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We receive a large number of letters asking if we have published projects for particular items of equipment. Whilst some of these can be answered simply and quickly, others would seem to demand the compiling of a long and detailed list of past projects. To help both you and us, we have made a full index of past ETI projects and features available (see under Backnumbers, below) and we trust that, wherever possible, readers will refer to this before getting in touch with us.
- We will not reply to queries that are not accompanied by a stamped addressed envelope (or international reply coupon). We are not able to answer queries over the telephone. We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:
UK: £18.10
Overseas: £22.50 Surface Mail
£29.50 Surface Mail (USA)
£49.50 Air Mail

Send your order and money to: ETI Subscriptions Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Backnumbers of ETI are held for one year only from the date of issue. The cost of each is the current cover price of ETI plus 50p, and orders should be sent to: ETI Backnumbers Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire HP1 1BB. Cheques, postal orders, etc should be made payable to ASP Ltd. We suggest that you telephone first to make sure there are still stocks of the issue you require: the number is (0442) 48432. Please allow 28 days for delivery.

We would normally expect to have ample stocks of each of the last twelve issues, but obviously, we cannot guarantee this. Where a backnumber proved to be unavailable, or where the issue you require appeared more than a year ago, photocopies of

individual articles can be ordered instead. These cost £1.50 (UK or overseas surface mail), irrespective of article length, but note that where an article appeared in several parts each part will be charged as one article. Your request should state clearly the title of the article you require and the month and year in which it appeared. Where an article appeared in several parts you should list these individually. An index listing projects only from 1972 to September 1984 was published in the October 1984 issue and can be ordered in the same way as any other photocopy. If you are interested in features as well as projects you will have to order an index covering the period you require only. A full index for the period from 1972 to March 1977 was published in the April 1977 issue, an index for April 1977 through to the end of 1978 was published in the December 1978 issue, the index for 1979 was published in January 1980, the 1980/81 index in January 1982, the 1982 index in December 1982, the 1983 index in January 1984, the 1984 index in January 1985 and the 1985 index in December 1985. Photocopies should be ordered from: ETI Photocopies, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Cheques, postal orders, etc should be made payable to ASP Ltd.

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

OOPS!

Corrections to projects are listed below and normally appear for several months. Large corrections are published just once, after which a note will be inserted to say that a correction exists and that copies can be obtained by sending in an SAE.

Low Cost Audio Mixer (June 1985)

In Fig. 6 on page 39, the PCB foil pattern has been incorrectly shown as though from the copper side. The board is shown correctly from the copper side in the foil pattern pages. In Fig. 10 on page 40, the positive power rail at lower left should be shown connected to pin 8 of the TL072s, IC1-5).

Noise About Noise (July 1985)

In Fig. 5 on page 24, no connection should be shown between the cathode of the diode and the negative side of the 470uF capacitor.

Printer Buffer (July 1985)

The case specified is actually larger than the one used for the prototype. It will, of course, work perfectly well, but if you want to use a compact unit use a Verocase 202-21038H (180 x 120 x 65mm) rather than a Verocase 202-21035. The regulator IC17 should be bolted to the back of the case to provide heatsinking or, alternatively, fitted with a TO220 heatsink.

Please note that the designer, Nick Sawyer, has been in touch to inform us that the refresh problem we mentioned in September ETI is dealt with in the printer buffer software. In this case there is no need to replace the TMS 4416 dynamic RAMs, although as far as we know the replacement parts mentioned (Hitachi HM48416 DRAMs) will cause no problems. The full text of Nick Sawyer's letter will appear next month. Meanwhile, our apologies for any confusion caused.

Cortex Parallel I/O (September 1985)

Pins 1 and 2 of IC2 have been swapped over on both the circuit diagram (Fig. 1) and the Veroboard overlay (Fig. 2). Pin 1 should connect to pin 16 on the header and pin 2 should connect to pin 2 on the header.

Intel 8294 Data Encryption Unit (September 1985)

It should be apparent from the text, page 35, that an actual program has been omitted. This program is for use with the SDK 8085 kit only, and copies may be obtained from us on receipt of a stamped addressed envelope.

Tech Tips — Novel Input Stage (October 1985)

The caption against the lower figure should read "Low noise output at minimum gain", not maximum gain.

Chorus Unit (November 1985)

IC3 is shown on the circuit diagram on page 49 connected to the 9V supply. It should be connected to the 5V supply. The foil pattern connections to this IC are correct.

Foil Patterns (November 1985)

The foil patterns for the Modular Test Equipment Waveform Generator and the Chorus Unit are shown from the component side rather than the copper side.

The Rhyth-ROM (November 1985)

R2 has been omitted from the parts list on page 35. Its value is 39k, as given on the circuit diagram. Also in the parts list, R821 should, of course, read R8-21.

Cymbal Synth (November 1985)

R18 is labelled as R20 on the circuit diagram (page 59) and the real R20 is missing altogether. It should be shown connected between the base of Q3 and the +ve rail. The overlay diagram is correct in both cases.

Digibaro (February 1986)

Capacitors C1, C3, C5 and C7 should be 470uF 25V types as shown on the circuit diagram, not 47uF 25V types as stated in the parts list. We have also been told that one of the companies mentioned in Buylines, Hawke Electronics, no longer supply the MPX100a pressure transducer. The other company recommended, Macro Marketing, should still be able to help.

REVIEWS — BOOKS

68000 User Guide

Lionel Fleetwood. Price: £8.95
Sigma Press, 5 Alton Road, Wilmslow, Cheshire.

The Sinclair QDOS Companion

Andrew Pennell. Price: £6.95

Inside The Sinclair QL

Jeff Naylor and Diane Rogers Price: £6.95

Sunshine Books, 12-13 Little Newport St., London WC2H 7PP.

68000 Machine Code Programming

David Barrow. Price: £12.95
Collins, 8 Grafton Street, London W1X 3LA.

Having looked at some basic books for the QL (pun intended), we now move on to the heart of the matter — the 68008 and Sinclair's own operating system, coyly titled QDOS.

The growth in the number of relatively low cost computers using the 68000-series processors (not least, the QL) means that there will be a corresponding growth in the number of books to support the series. Most of them will pursue comprehensiveness, while some will hope to prepare new and established programmers for the '68000 Revolution'.

68000 Machine Code Programming

This is quite a large book by paperback standards and the price is correspondingly large. As the title suggests, the book is concerned with the 68000, the 68008, the 68010, and it also contains a large amount of information on the immensely powerful 68020.

It is a very comprehensive reference work, comprising all the essential information on the processors, and a whole lot more. Among other things, the book contains details of the internal architecture and data organisation of the chips, a summary of the addressing modes, exception handling, supervisor mode, assembler directives and 68020 emulation on the other 68000s.

Other interesting features of this family of ICs are discussed, for example, concurrent bus and CPU activity, pipelined decoding and cache memory.

Around 60% of the book is given over to appendices, which are dominated by two very large sections describing the 68000/8/10 and the 68020 instruction sets respectively.

If you have experience of machine code on other processors and want to move to the Motorolas then you will probably need to read another book before tackling this one. However, as a reference manual for a 68000 programmer or for someone moving from the smaller 68000 chips to the 68020, the book may prove invaluable.

68000 User Guide

Which can't be said for this one.

This book contains a 68000 overview and programming model, a brief look at some of the more universal assembler directives and conventions, a reasonable explanation of only the more frequently used op-codes and some general programming advice with unusual examples.

For a newcomer to machine code, the op-code chapter describes a subset of the instruction set quite well. Unfortunately, the examples given are usually in 'structured idea' form rather than ready for typing into an assembler.

In fact, the author has tried to include too many topics in this short book and, in doing so, has sacrificed useful detail. No one topic is covered very thoroughly and most seem, at times, confusing.

The style is generally lighthearted, with some very strange programming examples. The book is certainly not a complete 68000 user guide, treating some of the more powerful features of the processor all too briefly and some not at all, and is neither a proper user guide nor a preparatory tome for the coming revolution.

The 68000 may be old-hat to some, in the shape of the QL's 68008, a cut-down version of the

full machine featuring an 8-bit data bus for downward compatibility and an internal architecture like that of its big sister for upward compatibility. So let's prise open the QL box and take a look inside.

Inside The Sinclair QL

This book — another in Sunshine's growing QL library — purports to be our guide beneath the keyboard. It is divided into two parts.

The first deals with the fundamental principles of digital electronics, at a level suitable for people with very little or no knowledge of computer or any other sort of hardware. The text begins by attempting to describe the very nature of electricity, as we currently (!) theorise it. It then moves through logic gates (!) to show how TV pictures and sound are generated, ending up with a description of microprocessors and their associated systems.

The second section deals specifically with QL, and is more to do with software than hardware, or to be more precise, 68000 assembly language. With this switch, the book also changes for a considerable time from 'educational' to reference format. Actually, some useful hardware information about the QL is included.

The text keeps our interest while explaining various aspects of computer operation. This is a simplified description of a very complex piece of equipment and is suitable only as an introductory text for someone who would like to learn about the basics of computing electronics.

The Sinclair QDOS Companion

The professional programmer

will be more interested in this — especially since it aims to give real help.

One of the problems of writing commercial software for Sir Clive's micros is that he too often decides to release a slightly revised computer. As like as not, your machine code, instead of proving the ultimate in cheque book reconciliation, merely crashes. One way around this, of course, is to rewrite the whole program, making slight changes here and there.

A far better way — on the QL, at least — is to write your machine code in the first place using QDOS.

The aim of 'The QDOS Companion' is to enable you to do just that. Of course, using QDOS has other advantages. Why write a program to print a character to the screen for example, when such a routine already exists in the ROM and is easily accessible through QDOS?

The book is basically a list of all the QDOS calls that can be made, explaining the parameters needed to enter, the parameters returned from the routine, the function of the routine and so on. This comprehensive list can be divided into a number of sections: multi-tasking; the 8049 second processor (used for sound production and reading the keyboard); input and output (including microdrives); device drivers; exceptions; interrupts and the job scheduler; and QDOS utilities.

Other useful information includes how to add procedures to SuperBASIC, a complete list of the system variables and memory and microdrive maps.

This reference book will certainly be of value to anyone who owns a QL and understands 68000 assembly language.

Leigh Chappell



OPEN CHANNEL

As reported last month, big blue IBM declined to join the Corporation for Open Systems, the group set up by a number of American computer manufacturers to define and implement standards which would conform to open systems interconnection (OSI). The idea of OSI is that any computer conforming to it will be able to talk to any other similarly conforming computer.

Now, in a distinctly embarrassing about-face, IBM have decided that a unified opposition to their own systems network architecture (SNA) would be too much to compete with and have joined COS.

In a similarly eye-opening move here in the UK, IBM have managed to weasel their way into a Department of Trade and Industry sponsored project to develop software which will test whether computers conform to the OSI standard.

I'm sorry to be cynical but I'm

sure the only reason why IBM have conducted such turn-arounds is that there's gold in them thar hills. If IBM had thought for one minute that their SNA standard could win the day, they would have had no hesitation in maintaining it and making full use of patents, copyrights, royalties etc, in leasing the system to competitors. As the situation now stands, IBM will probably still be able to maintain their piece of the pie with SNA by using delaying tactics within the organisations they have decided to join — it will be many years before OSI finally takes off, remember. Oh well, if you can't beat 'em ...

Just Another Socket In The Wall

It looked, for a time, as if Oftel was getting to grips with British Telecom and was managing to gently persuade it to liberalise everything for the benefit of the customer. In a recent document, however, Oftel has suggested that, although domestic telephone extension wiring could be done by BT's competitors, wiring of the master socket (the first socket on the user's premises) would still be in BT's hands.

At first sight, this seems logical — it's BT's line and obviously they don't want any old Tom, Dick or Harry sticking an unauthorised connector on the end of it, wilfully or negligently committing damage. After all, BT will willingly come and install master and extension sockets for the user.

On the other hand, you have to consider what happens when you ask BT to do the job for you. First, it often takes a while for them to get their act together and send an engineer out to your house (the time span is better than it used to be, but we're still talking of up to a week or so). Second, you get a whopping great bill for a job that shouldn't cost even one fifth of the amount!

If BT maintains a monopoly on this condition, only BT benefits (that's what a monopoly is all about, isn't it?). The customer is overcharged and BT's competition is forced out of some essentially worthwhile work. After all, there is no reason why qualified private engineers couldn't do the conversions, and there is no reason why master sockets which the private engineers fit shouldn't be of a sufficiently high standard not to do damage (the other sockets which private contractors would

be allowed to fit presumably are). Come on, Oftel. Do the work you're supposed to do.

DBS

Finally, the Home Office has decreed that a non-British satellite may be used to broadcast British DBS television channels. This may seem like a small concession, but the previous insistence on all British systems is the main reason why we haven't already got the originally proposed DBS service. As it happens, the British satellite manufacturers up to now haven't been able to provide a satellite which will make an economic proposition of DBS television. Perhaps this change of heart by the Government will make them see the folly of their ways. If they can't reduce costs, then the programme providers will go elsewhere.

About the time you read this, an advertisement will probably appear in the national press requesting potential operators of the DBS service. Later this year the operator who gets the job will be announced. Then, in only another three years (yawn, yawn) we may, just may, have DBS.

Keith Brindley

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Argus Specialist Publications Ltd will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of this publication, summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent (up to a limit of £2,000 per annum for any one Advertiser so affected and up to £6,000 per annum in respect of all insolvent Advertisers. Claims may be paid for higher amounts, or when the above procedure has not been complied with, at the discretion of this publication but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties).

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements). Classified advertisements are excluded.


TRAINS OF THOUGHT

Watch television in the same house as an operating model railway and you will soon be well aware of the amount of electrical noise they generate. Turn the light off in the railway room leaving the trains running and you will see the multitude of spark-gap transmitters responsible, aided by their direct coupling to a most effective antenna system, the track! Some proprietary model locomotives incorporate so-called 'suppressors' — in practice just small capacitors in parallel with the motor — but they do little to alleviate the problem.

The problem is only a petty

irritation until you try to operate certain kinds of logic circuit close to the layout. Circuits using TTL flip-flops may prove so susceptible to spurious sets and resets as to be useless. The trouble is that TTL flip-flops can be tripped by pulses as low as 1V, and with 12V motors whizzing around on circuits all too prone to interruption, transients of 1V occur quite frequently.

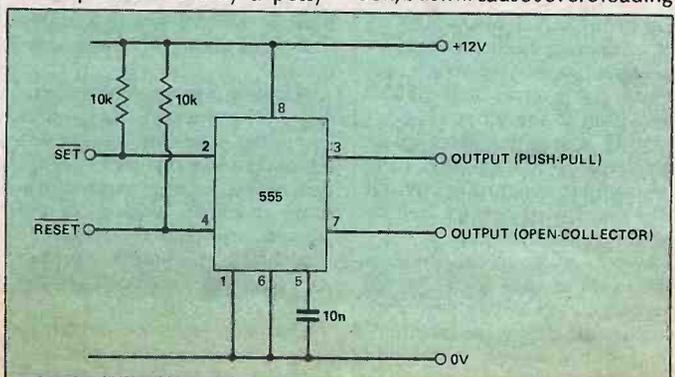So what can we do? Keeping the track, the locomotive wheels and power pick-ups scrupulously clean undoubtedly helps to reduce the amount of sparking but is most unlikely to eliminate all of it. Connecting 47R resistors in series with 100R capacitors between the rails at intervals of 2 ft (600 mm) will reduce the amount of electromagnetic radiation, but will cause severe loading



PLAYBACK

Question: *What sort of a noise annoys an oyster? An up-dated version of this old chestnut could be: what sort of a noise annoys an audiophile?* Noise has been one of the principal annoyances associated with sound reproduction from the earliest days. This is why noise specifications figure prominently in the specifications quoted for various items of equipment.

One of the chief sources of noise has been recording tape. Early examples had high noise levels, and wide tracks travelling at high speed were the only means of reducing noise at source whilst maintaining a reasonable high frequency response. The compact cassette would have been impossible with the tape then in use.

To 'B' Or...

To reduce tape noise various noise-reduction systems were introduced. The best-known of these is Dolby B which is found on the majority of tape decks. This functions by increasing the recording gain of sounds below a

certain level and within a particular frequency range, then reducing the same ones at playback. That restores the original proportion, but reduces anything that appeared between recording and playback, such as tape noise.

Though apparently an ideal solution, there are, as always, snags. Identical levels must be presented to the recording and playback processors or variations of frequency response will result. Level differences can result from various causes including using another brand of tape. There can be modulation of the noise, and also of frequencies occurring simultaneously that are outside of the processed band. Furthermore, as all circuits containing active components add distortion, the noise reduction circuitry can be no exception.

There are other noise-reduction systems such as Dolby C (which operates over a wider band), dbx, High Com, and ANRS, all of which have appeared on domestic recorders. These all have their good and bad points, but even the bad systems have been accepted as being preferable to the noise.

While all this has been going on, tape development has been steadily moving ahead. Numerous small improvements in particle shape, size, dispersion and other features have added up to significant improvements in performance, including a notable reduction in noise.

Noises Off

You can check this for yourself. Record about a minute of silence on a high-grade tape with the recording level control right back. Now replay it at normal setting of the volume control, turning up the control until noise can be heard. This is the combined effect of all noise sources. Next, depress the pause control. The noise you now hear is that mainly due to the pre-amp circuits, the difference being that contributed by the tape. In many cases, especially in 'medium-fi' equipment there is only a marginal difference between the two levels.

So, tape noise may now be only a small part of the total. This raises the question: are noise-reduction circuits with their inherent drawbacks any longer necessary? Have they outlived their usefulness? If you record BBC music concerts you will find another type of noise far more annoying — audience noise! Which brings us back to our opening question. The answer if you haven't heard it before is: A noisy noise annoys an oyster; and some audiences can be very noisy!

Roger Amos

Vivian Capel

ALF'S PUZZLE

Passing Alf's workbench one day, we all noticed an interesting looking circuit diagram on a scrap of paper. 'What is it, Alf?' we asked. Alf replied that it was something he had invented, but he couldn't remember what it did. A simplified version of the circuit is shown in Fig. 1. The coffee stains and half a fish-paste sandwich have been omitted for clarity. What do you think it could be?

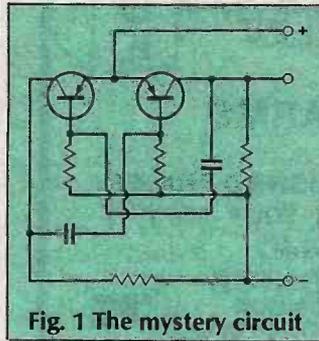


Fig. 1 The mystery circuit

When we first decided on a puzzle for the April issue, it was going to be slightly different from the one that actually appeared. It was going to begin with a capacitor charged up to 10V, which would then be connected with another capacitor of the same value. The text-book formulae would show that either some charge had been gained or some energy lost in the process.

The answer would have been that energy was lost because the first capacitor would be effectively short-circuited by the second, so losses would occur in the form of a spark, say, on heating of the capacitor leads.

At the last moment, Alf decided to confuse the issue further by using four capacitors. We thought that would make no difference to the answer. But when we came to look at the puzzle again, we found

that Alf had accidentally invented a new one! The odd effects that occur when you short one capacitor with another will do to explain the discrepancy in the puzzle as it was presented, but suppose that Alf had simply started off with the series-parallel arrangement of capacitors and compared them to a single capacitor (Fig. 2)?

The arrangement of capacitors in Fig. 2a should have the same value as the single capacitor in Fig. 2b. If we do a quick calculation of the total energy of Fig. 2a, it comes to $25\mu\text{J}$ for each capacitor, or $100\mu\text{J}$ total, the same as for the single $2\mu\text{F}$ capacitor. The charge, however, would appear to be $10\mu\text{C}$ for each capacitor in Fig. 2a, making a total of $40\mu\text{C}$, as opposed to $20\mu\text{C}$ for the single capacitor in Fig. 2b.

If the series parallel arrangement stores twice as much charge as the single capacitor, how can they be equivalent? Wouldn't it take twice as much current for a given time to charge Fig. 2a to 10V as it would for Fig. 2b? what is going on?

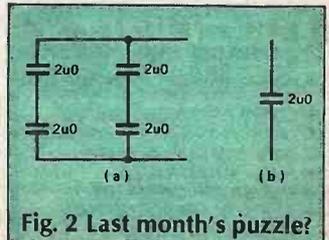


Fig. 2 Last month's puzzle?

As the rules of Alf's puzzle say that we only have to give one answer each month, we're not going to tell you. If anyone would like to write in with a solution to this little mystery, we will publish the best answer (it must be clear enough to be understood by a ten year old and convincing enough to persuade the most sceptical) and as an added incentive the author of the published reply will receive a prize of £10.

Please
mention
E.T.I.
when replying
to all
adverts

Lineage:
45p per word (minimum 15 words)
Semi Display: (minimum 2 cms)
£11.00 per single column centimetre
Ring for information on series bookings/discounts
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 291

Send your requirements to:
Stuart Taylor
ASP Ltd.,
1 Golden Square,
London W1.

ALARMS

ALARMS 

FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES
PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU

COMPONENTS

ROMNEY MARSH ELECTRONICS
(PROPRIETOR: D. J. HOOKER)

RESISTORS
METAL FILM RESISTORS 5% 1/4w 2p EACH 15p/10 80p/100 PER VALUE.
10 OF EACH VALUE 10R-1M E12 SERIES 610 TOTAL £6.75, 25 OF EACH VALUE £12.95.

CAPACITORS
ELECTROLYTIC (RADIAL 16v) 10u,22u,47u,-6p,100u,-7p,220u,-16p,470u,-18p,1000u,22p.
POLYSTYRENE (160v 5%) 10pF-1nF 9p, 1n5-12nF,11p.
POLYESTER (RADIAL PCB MTN 10%) 10n/100v,22n/100v,33n/63v,47n/63v,68n/63v,8p,100n/63v,9p,220n/63v,12p,470n/63v,22p.
MINIATURE 100v CERAMIC PLATE 1.2pF-1,000pF,6p,1,200pF-4,700pF,7p,10nF/63v,22nF/63v,8p.
CERAMIC DISC 50v 0.01uF,4p,0.1uF,8p.

SEMICONDUCTORS
DIODES 1N4001/2/3/4,4p;1N4005/6/7,6p;1N5404/6,12p;1N5408,16p;1N4148,2p,£1.00/100.
ZENERS 2v4 400mw,8p;2v7-39v 1.3w,12p. BRIDGE RECTIFIERS 1.5A 50v,18p;100v,20p.
TRANSISTORS BC107/8/9,10p;BC182/3/4L,8p;BC212/3/4L,8p;BFY50,20p;2N3055,40p.
ICS 741,18p;555,20p. REGULATORS 7805,7812,7815,7824,35p;7905,39p;78L05,78L12,78L15,28p;79L05,30p;723,28p.
LOW PROFILE D.I.L. I.C. SOCKETS 8PIN,5p;14PIN,8p;16PIN,9p;18PIN,10p;20PIN,11p;24PIN,12p;28PIN,14p;40PIN,19p. PLEASE ADD 60p POSTAGE & PACKING TO ORDER.
PENNYWOOD, CLARK ROAD, GREATSTONE, NEW ROMNEY, KENT TN28 8PB

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!
● **LOWEST DISCOUNT PRICES**
● **HIGHEST QUALITY EQUIPMENT**
● **FREE DIY DESIGN GUIDE**
● **FULLY ILLUSTRATED**
● **MICROCHIP CIRCUITRY**
● **QUICK DESPATCH SERVICE**
● **FULL INSTRUCTIONS**

SEND SAE OR PHONE
CTEC SECURITY, Dept. E1
Stephens Way, Goose Green,
Wigan WN3 6PH
Telephone (0942 42444)



COMPONENTS

ESR ELECTRONIC COMPONENTS

- Full range of components
- Capacitors, Vero-boards LED's
- Audio Connectors & Switches
- Amplifier Modules and Cases

Free Price List available

13A STATION ROAD
CULLERCOATS, NORTH SHIELDS
TYNE AND WEAR NE30 4PQ
091-251 4363

COILS & CHOKES.

MAXI-Q

COILS AND CHOKES
PREVIOUSLY MADE BY DENCO
S.A.E. PRICE LIST

8 BRUNEL UNITS, BRUNEL RD,
GORSE LANE IND. ESTATE,
CLACTON, ESSEX CO15 4LU.
TEL: (0255) 424152

SITUATIONS VACANT

WANT THE RIGHT PERSON FOR THE JOB? THEN WHY NOT ADVERTISE WITH E.T.I.

LOWEST PRICED TOP QUALITY fire and Intruder alarm equipment, etc. SAE for catalogue Security Services, 62 High St, Hythe, Kent CT21 5JR.

BOOKS & PUBS.


Einstein

We use only 10% of our mental potentials

These are the words of Albert Einstein, the greatest physicist of recent times.
L Ron Hubbard's discoveries in the field of the mind prove today that Einstein was right.
In his book "DIANETICS: The Modern Science of Mental Health" L Ron Hubbard takes one more giant step in this direction. He reveals how anyone can use his discoveries to isolate the exact barriers that have so far prevented people from using their mental potentials to the full.
More and more people from all walks of life use Dianetics technology today.
The many written reports on their success are the best proof of the quality of this book.
Find out for yourself. Order your copy of this remarkable book today.
Price £3.95 paperback £17.50 hardback. Make cheques and POs payable to S.H.F. Send to Church of Scientology, Saint Hill Foundation, FREEPOST (ETI), East Grinstead, Sussex RH19 4ZA (no stamp required).

COMPUTER ADD-ONS

AMSTRAD OUTPUT PORT.
Plugs into printer port and provides seven open-collector outputs. Easy to use from Basic or M/C. £14.95 inc. S.A.E. for details. NCJ Electronics, 13 Binfield Square, Ella Street, Hull HU5 3AP.

6809 CPU, 14, 32, & 128K RAM/EPROM cards. Disk/Real-time Clock, VIA & beeper card. Flex O/S. All chips, cases, P/supplies, K/boards, etc from stock, build your own 6809 Flex system from scratch. See for details:
RALPH ALLEN ENGINEERING
Fornett End, Norwich NR16 1HT
Tel: 095 389420

EQUIPMENT

PRINTED CIRCUIT BOARDS
one-offs and small quantities supplied. Artwork carried out. Fennell Industrial Electronics, 54 Watling Street, Nuneaton, Warks CV11 6JL. Tel: 0203 382296.

LANCASHIRE

ETESON ELECTRONICS
15B Lower Green,
E.E. Poulton-le-Fylde, Blackpool
Tel: (0253) 885107

Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

LIVERPOOL

PROGRESSIVE RADIO
87/93 Dale Street. Tel 051 236 0154
47 Whitechapel. Tel 051 236 5489
Liverpool 2
THE ELECTRONICS SPECIALISTS
Open: Tues-Sat 9.30-5.30

SCOTLAND

VISIT SCOTLAND'S
NEWEST
COMPONENT SHOP
OMNI ELECTRONICS
174 Dalkieth Rd
Edinburgh EH16 5DX
Tel: 031 667 2611
Send S.A.E. for catalogue.
Open Mon-Sat 9am-6pm

ELECTROMART

ELECTROMART

FOR SALE

STEREOAMPS 120watt £21 (inc.) (60 + 60) case stereo controls and din/sockets + magnetic pickup preamps and selector STAB/PSU 240 volt KIA, 8 Cunliffe Rd., Ilkley LS29 9DZ.

POWERTRAN D.D.L. Partially built £80. **LINSLEY HOOD 75W** deluxe amp built, needs testing £70. **TRANSCENDENT 2000** built, excellent condition £100. **T20 + 20** built £15. **DJ90 MIXER** partially built, 100W amp. **BSR TURNTABLE X2** in disco console. Never used £220 ono. **POLY-SYNTH + expander** (8 voice total) excellent condition £400 ono. (Cost £700). Tel: Weyhill (026477) 2763

MICROTAN/TANEX computer plus keypad. Fully assembled and working. Also keyboard. Offers? Tel: Stocksfield (0661) 843766.

KITS

ETI KITS assembled and tested* by electronic trainees under supervision within a purpose built electronic workshop for as little as £10* (* depending on type of kit and complexity). Contact:- A.J. Smith, Dept K.A. Electronics Workshop, Lincoln I.T.E.C. Dean Road, Lincoln LN2 4JZ. Tel. 0522 43532.

ELECTRONIC ORGAN KEYBOARDS and other parts being cleared out. Special Offer: Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8.

C.P.L. ELECTRONICS



RF. SPEECH PROCESSOR KIT PW MARCH '86	£54.20
RITTY/WORSE MODEM KIT PW JAN. '86	£36.55
50 MHz TRANSVERTER KIT (MEON) PW OCT. '85	£51.00
FET DIP OSCILLATOR KIT PW OCT. '85	£20.80

The above prices include P&P Do not Add VAT
All kits complete. Components new and to full spec.
Article reprints 60p if required. Cheques or P.O. to:

C. P. L. ELECTRONICS (ETI)
8 Southdean Close, Hemlington,
Middlesbrough TS8 9HE

Many other kits available, plus a wide range of components, etc. Components also supplied for E.T.I. projects. RS, Farnell and STC Components available.

FREE PRICELIST ON REQUEST

J. Linsley Hood Designs

	P.P.	
Distortion Analyser Kit.	£25.00	£1.00
Milivoltmeter Kit.	£12.25	£0.75
Case and Panel for above	£12.00	£1.00
ETI Mosfet P.A. Kit.	£51.00	£1.50
Audio Signal Gen. (.02%) Kit.	£28.50	£1.50
Audio Signal Gen. (.002%) Made	£48.00	£2.00
Fixed Freq. Sig./Gen. (.002%)	£14.00	£0.50
Case and Panel for above	£9.50	£0.75
Reg. P.S.U. 1.5/35 volts from	£12.80	£0.00

S.A.E. for full information.
TELERADIO ELECTRONICS
325, Fore Street, London N9 0PE. Tel: 807 3719

POWER SUPPLIES

150W SWITCHMODE PSU. +5V at 8.4A; +12V at 4.8A; +24V at 1.7A; -12V at 0.2A. Perfect working order, over £70 in Henries Radio £29 + Carr. 0245-50927 after 6.00pm.

KITS AND READY BUILT

FM TRANSMITTERS Same day despatch **MINIATURE MODEL** frequency 60-145 Mhz, range 1 mile. Glass fibre P.C.B. All components. Full instructions 9-12V operation, broadcast reception. Super sensitive microphone. Pick up on **FM/VHF** radio. £6.95 inc or ready built £8.95. Size 57 x 19 x 12mm. **HIGH POWER MODEL.** 3 watts 80-108 MHz. Professional broadcast performance. Low drift varicap controlled. Range up to 7 miles. 12V operation. Any input audio/microphone. All components P.C.B. diagrams and instructions. Size 103 x 39 x 29mm. Kit 13.99 inc or ready built £18.99 inc. **TONE GENERATOR** 3-selectable functions; PIP, Warble and pulse tone: All components, instructions & P.C.B., feed into any audio input or transmitter, variable frequency and gating controls. 6-12V operation 53 x 38 x 14mm. £5.50 incl. **TONE GENERATOR POWER AMPLIFIER.** All components, instructions and P.C.B. turnstone generator into a high power siren for alarms; 18 watts max. at 12-15V. 62 x 38 x 14mm £7.00 inclusive **DIGITAL CLOCK/TIMER MODULE.** 12/24 hour & seconds (0.7inch LED) display, 8-functions. Applications: uncommitted output transistor for switching on Tape-recorders: Lighting, Security, etc. External Loudspeaker Output. 84 x 38 x 16.25mm. Full instructions & Modular PCB £17.49 inclusive. **MAINS TRANSFORMER** for above if required: £5.24 incl. **DIGITAL CODE LOCK MODULE: 4 18V.DC** operation; 10,00 combination quality key pad; programmable code; low-power 3-outputs (0.2A); **3-LED** status indicators; All components, instructions & PCB. Applications: Alarms; garage doors; cars, etc. 39 x 62 x 9mm. Kit: £15.95 incl. Ready built; £19.95 incl **ZENITH ELECTRONICS.** 21 Station Road Indust. Estate, Hailsham, E. Sussex BN27 2EW. Tel: 04353 2647.

HEATHKIT U.K. Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

AMAZING ELECTRONIC plans, lasers, gas, ruby, light shows, high voltage tester, van de graph surveillance devices ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Old String Works, Bye Street, Ledbury HR8 2AA.

REPAIRS

ZX SPECTRUM. VIC20, C64, BBC, QL 15 40/41 Commodore computers, printers and floppy discs. Send faulty machine to: Trident Enterprises Ltd., Unit 7, Wentworth Industrial Court, Goodwin Road, Britwell, Slough. Tel: 0753 21391.

SERVICES

JBA ELECTRONICS

Specialists in manufacture and design of:
Microprocessor, Telemetry, and Audio-based systems.

UNIT 9,
BRECON INDUSTRIAL ESTATE,
BRECON, POWYS, S. WALES
Tel: (0874) 2563

FREE PROTOTYPE of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited, Finsbury House, 31 Head St, Halstead, Essex CO9 2BX.

VERSATILE Z80 BOARD complete with non-volatile S RAM, on board power supply, 7 sequential relay functions, outputting printer/displays. If required programmed to your specification. Fennell Industrial Electronics, 54 Watling Street, Nuneaton, Warwickshire CV11 6JL. 0203 382296.

DESIGN SERVICES, microprocessor, special interfaces, analogue, digital, signalling, alarm systems, PCB design and artwork. Prototype and small batch production. **ALAB ELECTRONICS.** Grantham (0476) 860089.

SCOPES

MENDASCOPE LTD.

REPAIR & RECALIBRATE
OSCILLOSCOPES.
ALL MAKES ALL MODELS.
NATIONWIDE COLLECTION &
DELIVERY
FREE ESTIMATES
Phone 069-172-597

TEKTRONIX OSCILLOSCOPES

547 Dual Trace 50MHz Delay Sweep £195. 545 B Dual Trace 24MHz Delay Sweep £135. 551 Dual Trace 24MHz £125. 556 Dual Beam Four Trace 50MHz Delay Sweep £345. 7 B 50A Time Base £295. 107 3n S Pulse Generator £45. Marconi TF868 LCR Bridge £85. Telequipment D83 Scope 50MHz Delay Sweep £445. Tel: 01-868 4221.

SOFTWARE.

EX42 AND CP/M? "PRT-SYS", Z80 program simulates EPSON MX80 Operation. Full source code/manuals disk copying most formats: CP/MMSDOS Amstrad... SAE NETCOM, Highall Farm, Nettlestead, Suffolk.

SPECIAL OFFERS

CLEARANCE BARGAIN!! Thousands of LED 7 Segment Display, brand new 14 pin DIL RED .43 inch common anode display 0-9 with right and left decimal point in stock. 10 pieces £2.50 (25p each) 50 pieces £10.00 (20p each) 100 pieces £15.00 (15p each) 1000 pieces £100.00 (10p each). Telephone your order to 0296 613816.

FREE MEMBERSHIP to a new national electronics club. For details and a free gift of components worth over £10 send only £1 p&p to **Woodside, Dowsett Lane, Ramsden Heath, Essex CM11 1JL.**

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES. Easy to follow diagrams and uses only £1. Components and P.C.B.s available from HERRINGTON, 63 Homefarm Rd., Hanwell, London W7 1NL. Tel: 01-578 6627.

TEST EQUIPMENT

TOP PRICES PAID for surplus electronic test equipment. Always a good selection of **SIG-GENS, METERS and SCOPES** for sale. Phone (0438) 353828.

WANTED

TURN YOUR SURPLUS transistors, IC's etc into cash. Contact Cole's Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

COURSES

TRAIN WITH BOC For A NEW CAREER IN COMPUTER OPERATING OR PROGRAMMING OR COMPUTER SERVICING

We will offer you FREE training and help in finding a job. Check if you qualify:
* Over 19? * Out of full-time Education for 2 years or over? * Eligible for MSC TOPS/JTS Sponsorship? (Check with local Job Centre)
If you live within commutable distance of London, post this coupon for your FREE Aptitude Test at our centre.

INTERESTED IN SERVICING PROGRAMMING OPERATING

NAME

ADDRESS

THE LONDON COMPUTER AND ELECTRONICS SCHOOL
GLENTHORNE HOUSE, HAMMERSMITH GROVE, LONDON W6 0ND

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE "ALLADINS' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HOT LINE DATA BASE

DISTEL

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily. ON LINE NOW. COITT, 8 bit word, no parity. For 300 baud modems call 01-679 1888 For 1200-75 baud modems call 01-679 6183

FREE

Your monitor from its computer!! For only £24.95 it becomes a SUPERB HIGH QUALITY * COLOUR * TV SET

The fabulous TELEBOX, an INVALUABLE MUST for the owner of ANY video monitor with a composite input, colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed!! The TELEBOX consists of a compact, stylish two tone charcoal moulded case, containing ALL electronics tuner, power supply etc. to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral Hi-Fi watt audio amplifier for driving an external speaker, PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include: Compact dimensions of only 15.75" w x 7.5" d x 3.5" h, latest technology, BRITISH manufacture, fully tuneable 7 channel push button tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240v AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £24.95 OR £19.95 if purchased with ANY of our video monitors. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.50 *When used with colour crt

COLOUR & MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR
Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs RGB and PAL, composite video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour, Major controls on front panel. Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc.

This is MUST BE ONE OF THE YEAR'S BEST BUYS. PC USER Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. ONLY £105.00 as above OR IBM PC Version £165.00 15 Day 'D' sct £1.00. BNC sct 75p BBC Interface cable £5.50

DECCA 80 16" COLOUR MONITOR. RGB Input.
Little or hardly used manufacturers surplus enables us to offer this special converted DECCA RGB Colour Video 16" monitor at a low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: Internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34" H x 24" D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage

DECCA 80, 16" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPS, DISCOS, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 - Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors.
All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for 18 to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected. 30 day guarantee.

12" KGM 320-1 B/W bandwidth input, will display up to 132 x 25 lines. £32.95
12" GREEN SCREEN version of KGM 320-1. Only £39.95
9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00

Carriage and insurance on all monitors £10.00

DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £16.95
GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00
AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.8 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm NEW £49.94
Carriage on all PSUs £3.00

KEYBOARDS

Manufacturer's BRAND NEW surplus. DEC L434 Un-coded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc. £24.95
AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT! Less than half price
Only £69.00 with data. Carriage on Keyboards £3.50



Double sided 40/80 track disk drives (1Mb per drive), PSU, 4K of memory mapped screen RAM, disk controller, RS232, CENTRONICS and system expansion ports, and if that's not enough a ready to plug into STANDARD B' DRIVE port for up to FOUR 8" disk drives, either in double density or IBM format. The ultra slim 92 kc, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti-glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request.

PC2000 System with CPM etc. COST OVER £1400

NOW only £399

DON'T MISS THE CPM Deal OF THE CENTURY

The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC, CPM system, recently on sale at OVER £1400, at a SCOOPE price just over the cost of the two internal disk drives!! Or less than the price of a dumb terminal!!!

Not a toy, the BIG BROTHER of the EINSTIEN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

The central processor plinth contains the 84K, Z80A processor, DUAL TEAC 55F5 1/4" PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

PC2000 Business System with CPM and 'Ready to Run' FAST Sales and Purchase Ledger, supports up to 9000 Accounts, VAT etc. COST OVER £1700

NOW only £499
Carriage & Insurance £12.00

PC2000 Wordprocessor System with CPM and TEC FP25 daisywheel printer

NOW only £799

MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets... BRAND NEW State of the art products.
DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc. £268.00
DACOM DSL2123AQ Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer with flow control etc. £365.00
DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc etc. £498.00
Stebeck SB1212 V22 1200 baud FULL DUPLEX sync or async, optional auto dial. £465.00
TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 interface. £49.00

Ex BRITISH TELECOM full spec. COITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface.
MODEM 13A 300 baud unit, only 2" high fits under phone. CALL mode only. £45.00
MODEM 20-1 7.5-1200 baud. Compact unit for use as subscriber end to PRESTEL, TELECOM GOLD, MICRONET etc. £39.95 +pp £6.50
MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end. £65.00 +pp £6.50
DATL 2412. Made by SE Labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc. COST OVER £800. Our price ONLY £199 +pp £6.00
DATL 4500, RACAL MP4800 2400 baud modem, EX BT good working order. ONLY £295.00 +pp £8.00

SPECIAL OFFER

MODEM TG2393. EX BT, up to 1200 baud, full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR +pp £10.00

For more information contact our Sales Office.

MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps bidirectional, full pin addressable graphics, 8 type fonts, up to 9.5" single sheet or tractor paper handling, RS232C and CENTRONICS parallel interface. Many other features. BRAND NEW and BOXED. COST £420. Our price ONLY £199.00

RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa.
A300 07191315 12v 3Ah NEW £13.95
A300 07191312 6v 3Ah NEW £9.95
A300 07191202 6-0-6v 1.8Ah TESTED Ex Equip £5.99

VDU TERMINALS

Standard VDU data entry terminals at give away prices!!
QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen; 2 page RAM, TVI 925, Hazeltine, ADMSA emulations, software setup, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00
AJ510 - EX RENTAL, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00
ADD5 200 - Dumb terminal, used, 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00. Carriage on terminals £10.00
100's of other terminals in stock, CALL for more details.

SURPLUS SPECIALS ON PRESTEL - VIEWDATA - TELEX

PLESSEY VUTEL, ultra compact unit, slightly larger than a telephone features a STANDARD DTMF TELEPHONE (tone dial) with 5" CRT monitor and integral modem etc. for direct connection to PRESTEL VIEWDATA etc. Designed to sell to the EXECUTIVE at over £600!! Our price BRAND NEW AND BOXED at only £99.00

DECCAFAX VP1 complete Professional PRESTEL system in slimline desk top unit containing Modem, Numeric keypad, CPU, PSU etc. Connects direct to standard RGB colour monitor. Many other features include: Printer output, Full keyboard input, Cassette port etc. BRAND NEW with DATA. A FRACTION OF COST only £65.00

ALPHATEL Very compact unit with integral FULL ALPHA NUMERIC keyboard. Just add a domestic TV receiver and you have a superb PRESTEL system and via PRESTEL the cheapest TELEX service to be found!! Many features: CENTRONICS Printer output, Memory dialling etc. Supplied complete with data and DIY mod for RGB or Composite video outputs. AS NEW only £125.00
Post and packing on all PRESTEL units £8.50

EX-STOCK INTEGRATED CIRCUITS

4164 200 ns D RAMS 9 for £11 4116 ns 1.50 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95 27128 £5.50 6800 £2.50 6821 £1 68A09 £8 68B09 £10 8085A £5.50 8086 £15 8088 £8 NEC765 £8 WD2793 £28 8202A £22 8251 £7 8748 £15 Z80A DART £6.50 Z80A CPU £2.00. Thousands of IC's in EX STOCK send SAE for list.

DISK DRIVES

Japanese 5 1/4" half height, 80 track double sided disk drives by TEAC, CANON, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £85.00
TEC FB-503 Double sided HH 40 TRK NEW £75.00
SUGART SA400 SS FH 35 TRK £55.00
SIEMENS FDD100 SS FH 40 TRK £65.00
carriage on 5 1/4" drives £5.50
Brand NEW metal 5 1/4" DISK CASES with internal PSU.
DSK1 for 2 HH or 1 FH drive £29.95 +pp £4.00
DSK2 for 1 HH drive £22.95 +pp £3.50
DKSC 3 As DSK1 LESS PSU £12.95 +pp £2.50
DKSC 4 As DSK2 LESS PSU £10.95 +pp £2.00
8" IBM format TESTED EX EQUIPMENT.

SHUGART 800/801 SS £175.00 +pp £8.50
SHUGART 851 DS £250.00 +pp £8.50
TWIN SHUGART 851's 2 Mb total capacity in smart case, complete with PSU etc. £585.00
MITSUBISHI M269-4-63 8" DS 1 Mb equiv. to SHUGART S801. BRAND NEW at £275.00 +pp £8.50
DYSAN B Alignment disk £29.00 +pp £1.00
Various disk drive PSUs in Ex Stock SEE PSU section.
HARD DISK DRIVES
DRE/DIABLO Series 30 2.5 Mb front load £525.00
Exchangeable version £295.00. ME3029 PSU £95.00
DIABLO 44/DRE4000A, B 5 +5 Mb from £750.00
CDC HAWK 5 +5 Mb £795.00. CDC 9762 80 Mb RMO3 etc. £2500.00.
PERTEC D3422 5 +5 Mb £495.00
RODIME 5 1/4" Winchester ex-stock from £150. CALL Clearance Items - Sold as seen - No guarantee.
ICL 2314 BRAND NEW 14" Mb Removable pack hard disk drive, cost over £2000 with data ONLY £99.00
BASF 6172 8" 23Mb Winchester £199.00
Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts, Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF

Telephone 01-679 4414 Telex 8924502 Data 01-679 1888



Makers and Sounders



Projects and

Elliptical Speakers

A range of high quality loudspeakers. All have high flux density



XENON FLASH TUBE DRIVER



CAR DIGITAL TACHOMETER

In these days of ever-higher motoring costs the driver to change gear at the most advantageous engine life. Anyone using a car to tow a trailer

Books

Capacitors

Solving Projects



Advanced PCB Interfacing

by John M. Holland
For anyone interested in robotics and computer control, here is a collection of design techniques and circuits that can be used in virtually any situation. Thoroughly covered are input and output design, serial communications, timing and timers, and D/A conversion, data acquisition and closed loop control. Though offering advanced solutions to rather complex and

Maplin
1986 Buyer's Guide to Electronic Components

LOWEST EVER PRICES SEE INSIDE NOW £1.45

1000V Disc Ceramic

1000V disc ceramic capacitor for general purposes

Photo-Electrical

RESPONSIVE CELLS

Cell MS4A



Photo-cell size 5.26 x 6.35mm
50V varnish to protect the junction
Short circuit current: 3mA into 100Ω at 3000 lux
Open circuit voltage at 3000 lux: 500mV. Typical short circuit current: 5mA per sq. ft. 5mA. Picture surface which is the negative.

Cell MS4A)

Transistor BPX25

ANTI-STATIC WORK MAT



flexible plastic mat which can be used to build-up of static charges on the floor. The mat has an anti-static surface which may be clamped to a suitable earth for a suitable time. The static charge on any item

Working voltage 500V DC

Connectors

Stereo Line Socket



3mm stereo line socket with plastic body and strain relief sleeve.

Part No. (Stereo Plas 3.5 Skt)

Shielded Line Socket



3mm mono jack line socket in metal barrel with strain relief sleeve.

Projects and Modules

BRIDGING MODULE MAKES 400V SOCKET AND

Increases output to 400V
Anti-thump at switch
Loudspeaker protection
Accommodates wide range of loads

Heathkit

Hero Jr. will stick by you

Hero Jr. is programmed to greet his companions with such phrases as "Hello, my friend," "I am your friend, companion and servant." In addition, an internal 100-year clock permits Hero Jr. to remind his owner of the week, date and time...and it even corrects itself twice a year for Time. Once familiar with all facets of Hero Jr.'s personality, the owner can advance to the level of "Robot Wizard" which permits Hero Jr. to identify by name and much more. Hero Jr. even uses his senses to seek out trouble while moving about. The robot's ability to locate humans can be enhanced.

No Catalogue ... No Component

Semiconductors

OPERATIONAL TRANSCONDUCTANCE AMPLIFIERS

Absolute max rating
Voltage supply range
Power dissipation



Miniature
chromium
end, 4
the other
68.57r
Order
FY36
natural
len-En

Pick up a copy of our new 1986 catalogue from any branch of W.H. Smith for just £1.45.
Or post this coupon now, to receive your copy by post for just £1.45 + 40p p & p. If you live outside the U.K. send £2.50 or 11 International Reply Coupons. I enclose £1.85.

Name

Address

ET15/86



ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 552911

SHOPS • BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
• LONDON 159-161 King Street, Hammersmith, W6. Telephone: 01-748 0926.
• MANCHESTER 8 Oxford Road, Tel: 061-236 0281. • SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 225831. • SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Telephone: 0702-554000
Shops closed all day Monday.