

# electronics today

INTERNATIONAL

February 1988 £1.40

## SPECTRUM CO-PROCESSOR



© The Walt Disney Company

TRANSISTOR TESTER

ELECTRIC FENCE

SATELLITE TV – 60 System Survey

AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS..

# GREAT NEWS FOR ALL PHOTOPLAY READERS!

STARTING WITH THE JANUARY 1988 ISSUE THE COVER PRICE  
WILL BE REDUCED TO **£1**


- \* **MORE COLOUR**  
of your favourite stars
- \* **MORE REVIEWS**  
by our top team of critics
- \* **CELEBRITY INTERVIEWS**  
with the top personalities
- \* **SCREEN CHAT**  
the latest news and gossip
- \* **VIDEO & TV**  
more coverage of the  
small screen

**MEET *ROBOCOP***  
**THE LATEST MOVIE  
SENSATION  
IN THE JANUARY ISSUE  
ON SALE THE FOURTH  
WEEK IN DECEMBER**

PHOTOPLAY'S BRIGHTER NEW  
LOOK TAKES A LIVELY,  
INFORMATIVE VIEW OF MOVIE,  
VIDEO AND TV SCREEN ENTERTAINMENT

**DON'T MISS OUT – BE IN THE PICTURE  
WITH BRITAIN'S BEST KNOWN  
SCREEN MAGAZINE!**


**★ NOW ONLY £1**

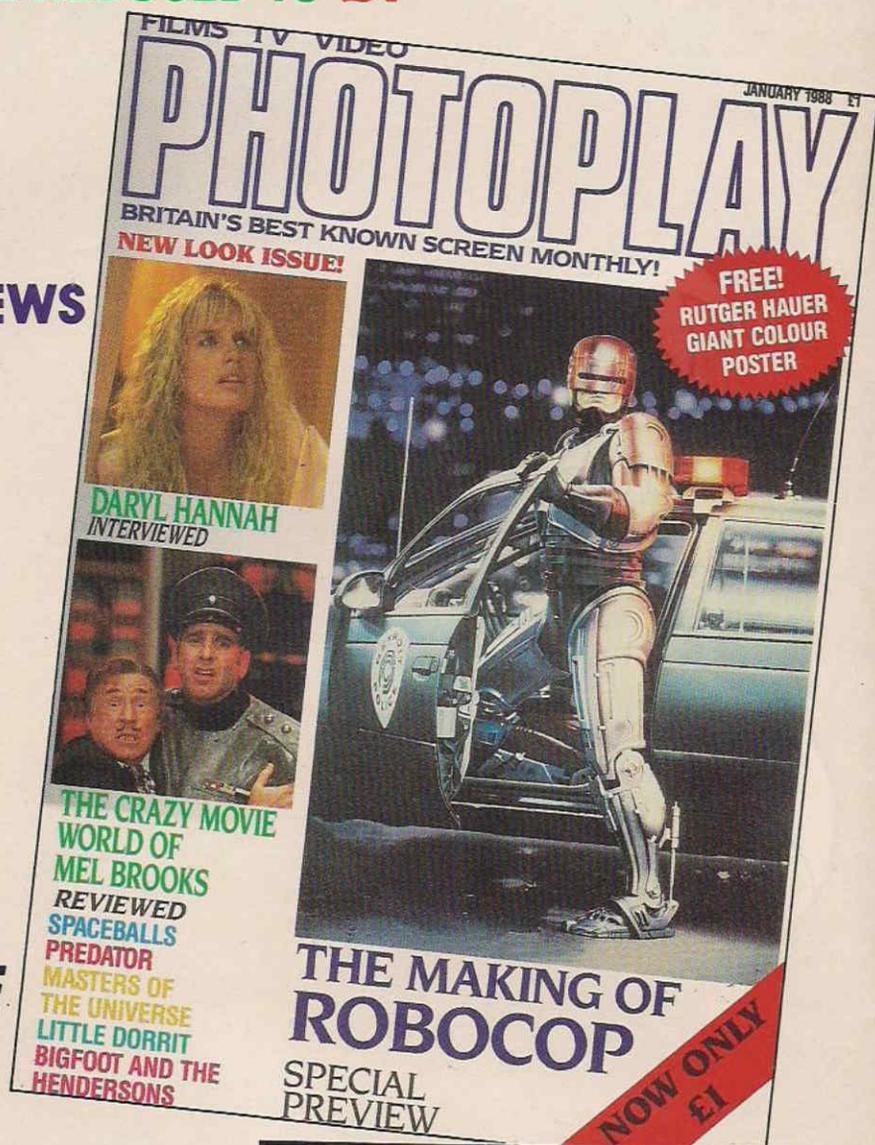

**GIANT RUTGER HAUER  
COLOUR POSTER FREE  
WITH THE BRIGHT NEW  
LOOK ISSUE!**

# electronics today

INTERNATIONAL FEB 1988 VOL 17 No. 2

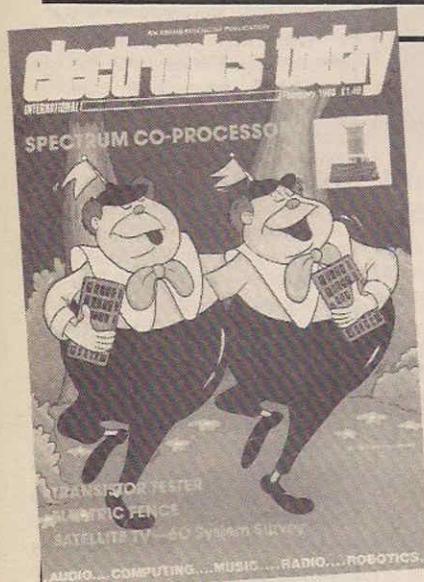

Editor: **Geoff Bains**  
 Assistant Editor: **Jez Ford**  
 Projects Editor: **Paul Chappell**  
 Illustrator: **Jerry Fowler**  
 Ad Manager: **Christopher Harris**  
 Classified Sales: **Julie Capstick**  
 Copy Control: **Andrew Selwood**  
 Group Editor: **Mark Webb**

- Published by Argus Specialist Publications Ltd., 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.
- UK newstrade distribution by SM Distribution Ltd., 16-18 Trinity Gardens, London SW9 8DX. Tel: 01-274 8611.
- Overseas and non-newstrade sales by Magazine Sales Department, 1 Golden Square, London W1R 3AB. Tel: 01-437 0626.
- Subscriptions by Infonet Ltd., 5 River Park Estate, Berkhamstead, Herts. HP4 1HL. Tel: (04427) 76661.
- Typesetting and origination by Multiform.
- Printed by Adlard & Son, The Garden City Press.
- Covers printed by Loxley Brothers Ltd.

ISSN  
0142-7229



Member of the  
Audit Bureau  
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1988 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisements nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

● Subscription rates: UK £16.80  
 Europe: £21.00 Middle East: £21.20 Far East: £22.80 Rest: £21.50 or US\$32.00.

1 Golden Square  
 London W1R 3AB  
 Tel: 01-437 0626  
 Telex: 01-881 1896

**ARGUS  
 PRESS  
 GROUP**

## FEATURES

- COMPETITION** ..... 11  
 Win one of the DCP Interfacing modules reviewed last month in this free competition.
- IMAGINARY TIMES** ..... 17  
 Paul Chappell continues his *Circuit Theory* investigation of complex numbers.
- DISH OF THE DAY** ..... 12  
 Keith Brindley looks at 60 satellite TV systems to wet your appetite for pictures from afar. All the info you need to deck out your back garden with tomorrow's technology.
- THE DIRECT APPROACH** ..... 20  
 Mike Barwise is looking at direct memory access for this month's *Chip In* and both integral and discrete designs come under scrutiny.

## PROJECTS

- SPECTRUM CO-PROCESSORS** ..... 24  
 Graeme Durant unveils his Spectrum's twin brother. At last the Spectrum comes of age.
- THAR' SHE BLOWS** ..... 31  
 Alan Wilcox's in-circuit transistor tester will help fathom those baffling failures.
- SMOOTH OPERATOR** ..... 36  
 Sick of the engaged tone? Phone yourself with this intercom for old phones from Henry Davies.
- THE ETI ELECTRIC FENCER** ..... 40  
 Zap your livestock and live in peace with your plot with this rural project from Paul Chappell.
- OPTO CIRCUITS** ..... 44  
 Robert Penfold makes light work of a few *Tech Tips* to brighten those dark winter evenings.

## REGULARS

- NEWS** ..... 4  
**PLAYBACK** ..... 54
- NEXT MONTH** ..... 6  
**OPEN CHANNEL** ..... 54
- SPECIAL OFFER** ..... 6  
**KEYNOTES** ..... 55
- DIARY** ..... 7  
**PCB SERVICE** ..... 56
- READ/WRITE** ..... 9  
**PCB FOILS** ..... 59
- SUBSCRIPTIONS** ..... 10, 51  
**READERS' FREE ADS** ..... 62
- TOKYO AUDIO FAIR REPORT** 53  
**CLASSIFIED ADS** ..... 63
- BOOK LOOK** ..... 53  
**AD INDEX** ..... 66

● Philips has come up with a CD decoding system that uses only two ICs and remarkably few other components. It originates from Holland and will be marketed in this country by Mullard Ltd (01-626 0394) who says that stocks should be available from March (ish).

The two chips are the SAA7310 and SAA7320. The SAA7310 is a third generation version of the SAA7210 providing demodulation, error correction and basic interpolation and in addition has modes for CD-ROM and CD-I.

The SAA7320 provides digital filtering, over-sampling and analogue post-filtering. The two chips together have a much lower power consumption (about 475mW) than the four chips previously required and can now handle temperatures from -40 to +85°C.

Mullard wasn't giving anything away when asked about prices. 'Competitive' was the word used. In Holland Philips estimate a price of about £11 for each chip but this is for large quantity orders only.


● A series of fine soldering irons are available from EES of Port Talbot. The smallest is an 11W iron weighing only 18.5g and having a maximum temperature of 340°C. All the irons can be supplied for various standard voltages and prices range from £7. Contact EES, Seaway Parade, Baglan Bay, Port Talbot SA12 7BR. Tel: (0639) 813663.

● Readers without the time to construct last month's Mains Cleaner may wish to investigate two protectors from Rendar. The Spikebloc, originally designed for use by BT, is intended for industry and provides an effective block to EM pulses and RF interference.

The Linebloc is for less sensitive equipment (home computers and hi-fi for instance).

Prices before VAT are £29.95 and £10.95 respectively. For more details contact Rendar, Durban Road, South Bersted, Bognor Regis PO22 9RL. Tel: (0243) 825811.

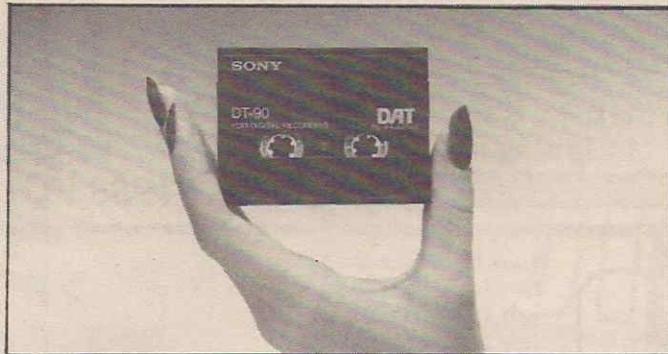● Blank audio cassettes will NOT have a levy imposed on their retail price as was originally proposed in the upcoming Copyright Bill. The furore surrounding this part of the Bill has obviously made its mark in the halls of Westminster but opponents of the tax claim that although not directly implementing the tax, the Bill still does not positively preclude its introduction in the future.



## If You Can't Beat Them — Buy Them


Digital Audio Tape merchant Sony has bought out its main opponent in the fight to get DAT onto the streets. CBS Records has cost Sony \$2 billion and even away from its parent group, the company is not cowering to the new owners. 'Sony is not about to go steamrolling through CBS' said Jonathon Morrish for CBS in London 'and the opposition of the CBS management to DAT is unchanged.'

That opposition requires a jammer on all DAT machines to

prevent direct digital recording from CD. Sony knows that such CD bootlegging is a major attraction of DAT to domestic users.

Sony has pledged not to interfere with the management of CBS but it is inconceivable that its enormous investment in DAT should be blocked by its own company.

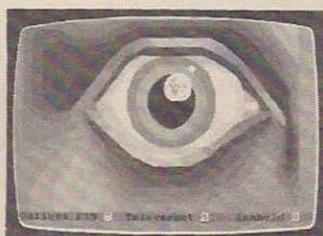The Sony view of DAT is based on profit motives, the CBS argument is based largely on ethics. It will be interesting to see who triumphs.



## The Scene Behind The Screen

Things are changing in the world of Teletext. Since the feature in the November ETI the BBC has purchased the new Signet system from Softel of Reading to replace the Logica system that has been running Ceefax since 1979.

The new system uses two micro PDP11/83s, three 11/53s and can link via modems to other systems such as Prestel and the Stock Exchange (not that you'll be able to dump those BP shares from the safety of your TV remote control but it should help get information onto the screens faster).

The BBC is also increasing the number of spare TV lines used to transmit Ceefax data. Up to now there have been six lines (numbered 13-18) but as of January 4th this will increase to eleven lines. The extra data will be only dummy information until March at the earliest and it seems likely that they will be used for the Datacast system run by BBC Enterprises, used by

such customers as Coral betting shops and Marks and Spencers (see November for details).

However, the BBC is hoping the extra line or two that will be devoted to Teletext will give a faster response time and more varied page-format. It is intended that 13 lines (numbered 8 to 20) will be used for both Teletext and Datacast combined.

Meanwhile, the Norwegians are raving about the 'almost complete' Concept 3 development from Lohja Comms Systems. This is an advanced teletext system with vastly improved graphics resolution and a palette of 4096 colours compared to the eight used in Oracle/Prestel (all CEPT 1 systems).

The snag is that existing teletext decoders are unable to understand it and Lohja have yet to design a unit that can update a CEPT 1 decoder to CEPT 3. So don't hold your breath...

## Integration For UK ICs

Plessey has bought Ferranti's semiconductor operations for £30 million.

The aim of the buyout is to develop growth in Europe and America.

With their combined sales this will put Plessey into the top ten ASIC (Application Specific Integrated Circuits) producing companies in the world, at a time when concern about the fragmentation of the British chip industry is high.

Plessey's first task will be to make cost savings that can bring Ferranti's operations up to the profitability Plessey achieves.

Ferranti is only projected to break even this year and speculation is that the loss-making discrete components business in Manchester may now be axed.

If Plessey now puts all its semiconductor eggs in the ASIC basket, it would do well to remember how Ferranti lost its leading role in the gate-array market to America and Japan back in the 70s.

As integration in ASIC gets more complex, access to micro-processor and memory technology will be essential. The Japanese and American giants would then be able to force prices to levels that Plessey would be unable to match.

## Heat From The Home Service

Budget Warmth is a scheme now available in seven of Britain's electricity boards thanks to the Electricity Council's award-winning Radio Teleswitch. Using the switch to alter tariff rates and selected supplies, the Electricity Board guarantees a constant temperature in one room of a customer's house for a fixed weekly charge — currently between £2.50 and £4. Tariff and load control commands are received by the teleswitch in the home from the carrier of Radio 4 (and yes, they are prepared for the frequency shift in February). Up to thirty commands per minute can be received plus a two second time code frame.

Please note that the Budget Warmth scheme is currently only being supplied to cases put forward by the social services (so put that phone down)...

## The Answer's EFTPOS At TSB

Customers of the TSB will soon be saved from the late-night search for those elusive TSB Cash Dispensers by a new £2.5m YESNET deal which will link their dispensers with the Nat West/Midland network.

The system (of which dispensers are but a tiny part) is from Plessey-Telenet and is based on a packet-switched data network (PDSN) enabling different computer systems within the TSB to communicate. At the heart of the system is the TP5/II which will allow monitoring and control to take place from a central location.

Other possibilities for the TSB include computer-linking Swan National (a TSB subsidiary) and getting involved with EFTPOS — a new card system projected for the late 1990s where the customer uses a plastic card to transfer money 'instantaneously' from his account to a retailer. Two intermediary services are already in service — Midland Transact (where credit cards are handled without hand-written receipts) and Barclays 'Connect' which is treated as a normal credit card but takes money from a current account.

With a complete EFTPOS system the retailer would receive VDU confirmation of the customer's ability to pay and the transfer of money would take place on the spot.

## Maxwell To Take Over The World

Well not quite, but it seems that not a day passes when Cap'n Bob doesn't buy up another publishing house or football team. Now the Maxwell Communications Corporation is acquiring Nimbus Records, the only CD manufacturers in the UK. The money from the sale (£24m) will be used mainly for expansion into CD-related areas such as electronic publishing. The development of CD-ROM will presumably be significantly boosted by Moneybags' loot and we must hope that it is Nimbus' Monmouth plant rather than MCC's American factory that sees the R&D funds from the acquisition.



## Twinkle Twinkle Little LED

Do you absentmindedly build up stocks of components that you never get around to using? If you've managed to collect 360,000 LEDs then you could knock them together into a little airship advertising sign like the one Airship Industries is flying over Tokyo.

The UK built skysign can display TV pictures (live or recorded) or graphics generated

on board the airship. The image is refreshed up to 25 times a second across the 5x19m screen.

We're so inspired by the idea here at ETI that we were preparing to light the whole side of our Golden Square offices with live broadcasts from our editorial department. Unfortunately we're having trouble getting planning permission...



## New Arrival At Euston Station

The biggest LCD in the world now hangs above the forecourt of Euston station providing train information for the 25 million passengers a year that will gaze upon its splendour.

The display is 75 feet long, 9 feet high and consists of 8000 60mm high characters, each a 12 x 6 dot matrix.

Although at present it is arranged as a standard train indicator with each train allocated 20 lines of 19 characters, it is completely modular and can be formatted in any manner desired.

Racal made the display and already has contracts for similar boards in other major London stations and in Ayr.

Driving the signboard is a Compaq 386 micro with 20Mb of memory. The central processor has two auxiliary processors — one for details of normal train movements and the other to show departures from that normality.

Train departures are displayed in chronological order (unlike mechanical boards) and as trains depart each set of information shifts across to the left. The characters are bright yellow and easy to read except if drunk when they appear as spectacular blurs of golden starlight. Probably best to ask an inspector...

If you want to ask Racal, the number is (0734) 782158.

●CK (the toolmakers) has brought out a range of delightful little screwdrivers with colour coded buttonheads. Specifically designed for electronics, TV and radio use, the colour code refers to screw type (slotted, Philips or Torx) and range from slot sizes of 0.8mm to 1.8mm, Philips sizes 000, 00 and 0, and Torx sizes from 06 to 09. All drivers are 85mm from tip to button. Prices start at £4 per driver. They are available in shops or contact the Sales Dept of CK on (0758) 612254.

●Temperature and humidity are measured simultaneously in a new handy sized module from Solex. Readings are displayed by LCD and the unit also features a high/low alarm, a min/max memory and is °C/°F selectable. Probes can be used but are an optional extra. The module measures about 3½ x 1½in and costs £46. Contact: Solex International, 44 Main Street, Broughton Ashley, Leics LE9 6RD.



●A de luxe version of the Octopus work holder is now available. The Super Octopus has a heavy base block and four flexible goose neck arms equipped with two clips, a magnet and a 2½in magnifying lens. The Super Octopus costs £13.17 including VAT and postage from Electronic and Computer Workshop, Unit 1 Cromwell Centre, Stepfield, Witham CM8 3TH. Tel: (0376) 517 413.

●The latest 'new standard' in interface communications is the RS485 which takes over from the RS422, while most people are still using RS232s anyway. The advantage of the RS485 is in its high-speed multimessaging since 32 driver-receivers can be put on a common data bus (the RS422 could have only 1). It also has a wider common mode voltage range, now +12 to -7V.

More information can be obtained from Texas Instruments, Manton Lane, Bedford MK41 7PA. Tel: (0234) 63211.

**NEXT  
MONTH**

# electronics today

INTERNATIONAL

## **GAS ALARM**

Nothing to do with warning of the after effects of Sunday lunch. This professional quality project protects your home from the rather more serious after effects of a gas leak.

## **BBC MICRO OSCILLOSCOPE**

Turn your BBC micro into a piece of test gear with this useful add-on to build. All the hardware and software to give you four input channels and up to 91kHz sampling rate.

## **SEQUEL IV**

There's more on Satellite TV (we'll convince you yet!) and the second part of the Spectrum Co-processor project — the 256K RAM board. Complex numbers finally find a use in electronics in our *Circuit Theory* series and *Chip In* takes a look at programmable counters.

In case that's not enough for you, the March ETI will also be packed to the gills with the usual assortment of News and Reviews, facts and opinions, practice and theory. Don't miss it!

*The March ETI - on the shelves on 5th February*

All these articles are in preparation but circumstances may prevent publication.

# BUILD YOUR ETI DREAM MACHINE IN STYLE

**WITH THIS SPECIAL OFFER PACK OF PARTS FROM ETI READERS SERVICES 'EXPANSION' OR 'FULL' KIT**

Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might head for the sound of soft rain, sea surf, or perhaps the wind through distant trees. Almost hypnotic, the sound draws you irresistibly into a peaceful, refreshing sleep.

For many, the prospect of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are some strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!

The ETI expansion parts set contains all you need to turn the basic Dream Machine into a very special project. The parts set contains:

- **PRESTIGE CASE** ● **MAINS POWER SUPPLY COMPONENTS** (transformer, rectifiers, capacitors, regulator) ● **HIGH QUALITY EXPANSION COMPONENTS** (TBA820 IC, resistors, capacitors, transistors, preset, loudspeakers) ● **ALL CONTROLS AND ACCESSORIES** (pots, switches, knobs, neon lamp, fuse holder, fuse, mains cable, etc.) ● **FULL INSTRUCTIONS** (Copies of the November and December ETI articles describing construction, testing and all kinds of dream experiments!)

**The expansion set costs only £19.95 incl. postage and VAT**  
(You will need the free components and PCB from the November and December issues to complete this project).

**The complete parts set (including PCB and all components) is yours for only £20.95 incl. postage and VAT.**

To A.S.P. Readers Services, 9 Hall Road, Maylands Wood Estate, Hemel Hempstead, Herts HP2 7BH. Please supply  
..... expansion sets ROET 8 @ £19.95 .....  
..... complete sets ROET 9 @ £20.95

I enclose my cheque/P.O. payable to A.S.P. Ltd. Please debit my Access/Barclaycard A/c No. ....

Signature .....  
Name .....  
Address .....  
.....

Please allow 28 days for delivery. This offer is available to readers in U.K. only. Overseas enquiries in writing to the above address.

## Total AV From Sony's CD-Interactive

Sony has been showing off its latest achievements with CD-I (Compact Disc Interactive). CP-I has a designated Real Time Operating System and associated CPU (68000 series) and blends audio functions with computing, text, graphics, animation and still pictures.

Each disc contains a spiral track arranged into sectors for ease of data management, although two forms of subdivision exist depending on the priorities of the end user.

Form 1 is designed for text-based applications. Form 2 has space (2324 bytes) for user-data

such as audio and video. Audio signals can be degraded from the normal 16-bit CD audio (44.1kHz) to rough 'n' ready 4-bit (18.9kHz) to boost the storage capacity.

In Japan Sony has just shown its latest prototype CD-I along with a disc featuring all the options above and music from the group Casiopea. The machine is heavily supported by peripheral hardware but the disc mechanism itself is comparable to that of a large CD player.

High quality moving video is limited to only 10% of the screen area (a full screen takes two-thirds of a second to update).

The area to be changed can be increased by enlarging the pixel size and reducing the resolution and Sony disguised some of the limitations of the system by scrolling, zooming, image mixing, fading and wiping.

With room for between 150000 and 200000 pages of text on each disc, CD-I will undoubtedly elbow its way into the education/training and entertainments markets. Nevertheless it is likely to be next Christmas before the first self-sufficient pre-production units are displayed and even longer before CD-I becomes a commercial reality.

## February Freebies

Those of you who like to have something other than Readers' Digest subscription forms through your door might want to send off for some of the latest catalogues that are free for the taking.

Universal Instruments' Test and Measurement Catalogue has 76 pages covering test gear from the classic Avometer to the latest digital stuff. For your copy just phone (0756) 69737.

ECC Electronics has a 28 page catalogue of capacitors, crystals and relays, mainly Japanese, available from Online on (0234) 217915.

RR Electronics has produced a 48 page engineers' guide to Ferranti ICs with block diagrams and text descriptions. Contact John Perks, RR Electronics, St Martins Way, Bedford MK42 0LF (0234) 47211.

Flight Electronics has released the sixth annual catalogue. The first half lists their lab testing gear and the rest is devoted to 'educational products' including a bread-boarding system that interfaces with an IBM PC. Telephone (0703) 227721 and ask for Suzanne Kittow.

Lambda Photometrics has a 6-page brochure with full details of single and dual phase lock-in amplifiers. It's available from: Lambda House, Batford Mill, Harpenden, Herts AL5 5BZ.



A profusion of new multi-meters is appearing on the market at the moment. Alpha Electronics has two digital meters - a 3-digit display for £35.95 (+VAT) and a 4½-digit for £79.95 (+VAT). The latter measures capacitance and frequency as well as the more standard circuit tests. Details from Alpha Electronics, Unit 5, Linstock Trading Estate, Atherton M29 0QA (0942 873434).

TMK is hedging its bets with a smart digital meter and the 500TU-B, a new version of a previous analogue multitester. The digital G60 has only basic functions (but looks lovely) and costs £47.00 (+VAT). The 500 TU-B is £49.75 (+VAT). Both are available from Harris Electronics, 138 Grays Inn Road, London WC1X 8AX. Tel: 01-837 7937.

## Remote Possibilities

Infra-red remote control of four separate receiver outputs is offered by a new kit from Electronic & Computer Workshop.

The transmitter (K2547) and receiver (K2548) cost £26.27 and £35.04 respectively (inclusive of VAT and postage).

Also new from ECW is a stroboscope kit with a light output of 11 watt-seconds at a frequency variable from 2 to 20Hz. The kit (K2601) costs £16.51 inclusive. Replacement tubes are also available.

Contact ECW, Unit 1, Cromwell Centre, Stepfield, Witham, Essex CM8 3TH. Tel: (0376) 517413.

## DIARY... DIARY... DIARY... DIARY... DIARY...

### Mathematical Modelling Of Semiconductor Devices — January 7-8th

University Of Technology, Loughborough. Contact IEE on 01-240 1871 or The Institute of Mathematics and its Applications on (0702) 612177.

### Early Days Of Electric Lighting — January 11th

IEE, London. Lecture by C. N. Brown of the Science Museum. Contact IEE on 01-240 1871.

### Corporate Computer Security '88 — January 12-14th

Metropole Exhibition Centre, Brighton. Contact PLF Communications on (0733) 60535.

### Gallium Arsenide: A New Generation Of Devices — January 14th

IEE, London. Lecture by Prof. D. V. Morgan (UWIST). Contact IEE on 01-240 1871.

### The Illusion Of Colour — January 14th

Lecture by M. B. Halstead (Thorn EMI) at the Gonville Hotel, Gonville Place, Cambridge. Contact Eastern Region IEEIE on (0603) 628321.

### British Engineering Supplies & Technology — January 18-21st

Olympia, London. Contact Mack-Brooks Exhibitions on (07072) 75641.

### The Which Computer Show — January 22nd

NEC, Birmingham. Contact Cahners Exhibitions on 01-891 5051.

### Office Update — January 19-22nd

NEC, Birmingham. Contact Cahners Exhibitions on 01-891 5051.

### E-Beam Testing Of VLSI Circuits — January 27th

Newport Faculty of Technology. One day seminar. Contact David Jones on (0633) 51525.

### Role Of Highly Elliptical Orbits In Satellite Communications — January 28th

IEE, London. Lecture by G. Beretta of the European Space Agency. Contact IEE on 01-240 1871.

Electromagnetic Compatibility And Micro-processor Based Systems — February 2nd  
Heathrow Penta Hotel, London. Contact ERA Seminars and Exhibitions on (0372) 374151.

Smartex '88 — February 9-11th  
Barbican Exhibition Centre. Surface mount technology exhibition.

### European Seminar On Neural Computing — February 8-9th

Royal Garden Hotel, London. Contact IBC Technical Services on 01-236 4080.

### Energy '88 — February 10-12th

Harrogate Exhibition Centre. Contact Emap Maclaren Exhibitions on 01-686 9200.

### Cable And Satellite '88 — February 25-28th

Wembley Exhibition and Conference Centre, London. Contact Montbuild Exhibitions on 01-486 1951.

### E-Beam Testing OF VLSI Circuits — March (date to be finalised)

Cavendish Conference Centre, London. One day seminar. Contact ERA Seminars and Exhibitions on (0372) 374151.

# COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

## THE "ALLADINS" CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HOT LINE DATA BASE

### ★ DISTEL ★

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell, 1000's of stock items, spares and one off bargains. Updated daily.  
**ON LINE NOW.** CCITT, 8 bit word, no parity.  
 For 300 baud modems call 01-679 1888  
 For 1200-75 baud modems call 01-679 6183

### FREE

Your monitor from its computer!! For only £29.95 it becomes a SUPERB HIGH QUALITY COLOUR TV SET

The fabulous TELEBOX, an INVALUABLE MUST for the owner of ANY video monitor with a composite input, colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed!! The TELEBOX consists of a compact, stylish two tone charcoal moulded case, containing ALL electronics tuner, power supply etc to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family!! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral 4 watt audio amplifier for driving an external speaker, PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include: Compact dimensions of only 15.75" w x 7.5" d x 3.5" h, latest technology, BRITISH manufacture, fully tuneable 7 channel push button tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240v AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £29.95 OR £24.94 if purchased with ANY of our VIDEO MONITORS. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.50 \*When used with colour crt.

### COLOUR & MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR  
 Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's, including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour, Major controls on front panel, Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc.

This Must Be ONE OF THE YEAR'S BEST BUYS. PC USER Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. ONLY £159.00 as above OR IBM PC Version £165.00 15 Day 'D' sct £1.00, BNC sct 75p BBC interface cable £5.50

DECCA 80 16" COLOUR monitor. RGB input. Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of!! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed!! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34 H x 24 D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage.

DECCA 80, 16" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPDS, DISCOS, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

BUDGET RANGE EXE EQUIPMENT MONOCHROME video monitors. All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for up to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected 30 day guarantee.  
 12" KGM 320-1 B/W bandwidth input, will display up to 132 x 25 lines. £32.95  
 12" GREEN SCREEN version of KGM 320-1. Only £39.95  
 9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00  
 Carriage and insurance on all monitors £10.00

### DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £16.95  
 GOULD G6-40A 5v-40 amp switch mode supply NEW £130.00  
 AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm NEW £49.94  
 Carriage on all PSUs £3.00

### KEYBOARDS

Manufacturer's BRAND NEW surplus DEC L434 Un-coded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc £24.95  
 AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board MICRO, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT!! Less than half price  
 Only £69.00 with data. Carriage on Keyboards £3.50



### DON'T MISS THE CPM Deal OF THE CENTURY

#### The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC, CPM system, recently on sale at OVER £1400, at a SCOOP price just over the cost of two internal disk drives!! Or less than the price of a dumb terminal!!  
 Not a toy, the BIG BROTHER of the EINSTIEN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

Double sided 40/80 track disk drives (1Mb per drive), PSU, 4K of memory mapped screen RAM, disk controller, RS232, CENTRONICS and system expansion ports, and if that's not enough a ready to plug into STANDARDS 'DRIVE port for up to FOUR 8" disk drives, either in double density or IBM format. The ultra slim 92 key, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti-glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request.

The central processor plinth contains the 84K, Z80A processor, DUAL TEAC 55F 5 1/4" PC2000 System with CPM Etc. COST OVER £1400  
 PC2000 Business System with CPM and 'Ready to Run' FAST Sales and Purchase ledger, supports up to 9000 Accounts, VAT etc. COST OVER £1700  
 PC2000 Wordprocessor System with CPM and TEC FP25 daisywheel printer

**NOW only £399**

**NOW only £499**  
 Carriage & Insurance £12.00

**NOW only £799**

### MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets -  
 BRAND NEW State of the art products.  
 DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc. £268.00  
 DACOM DSL2123AQ Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer £385.00  
 DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc. £498.00  
 Steebek SB1212 V22 1200 baud FULL DUPLEX sync or async optional auto dial £485.00  
 TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 interface £49.00

Ex BRITISH TELECOM full spec, COITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface.  
 MODEM 13A 300 baud unit, only 2" high fits under phone. CALL mode only £45.00  
 MODEM 20-1, 75-1200 baud. Compact unit for use as subscriber end to PRESTEL. TELECOM GOLD, MICRONET etc. £39.95 +pp £6.50  
 MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end £65.00 +pp £6.50  
 DATEL 2412. Made by SE Labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc. COST OVER £800. Our price ONLY £199 +pp £8.00  
 DATEL 4800, RACAL MP54800 baud modem, EX BT good working order. ONLY £295.00 +pp £8.00

### SPECIAL OFFER

MODEM TG2393. EX BT, up to 1200 baud, full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR +pp £10.00

For more information contact our Sales Office.

### MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps bidirectional, full pin addressable graphics, 6 type fonts, up to 9.5" single sheet or tractor paper handling, RS232 and CENTRONICS parallel interface. Many other features. BRAND NEW and BOXED. COST £420. Our price ONLY £199.00

### RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa  
 A300 07191315 12v 3Ah NEW £13.95  
 A300 07191312 6v 3Ah NEW £9.95  
 A300 07191202 6v-0.6v 1.8Ah TESTED Ex Equip £5.99

### VDU TERMINALS

Standard VDU data entry terminals at give away prices!!  
 QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen, 2 page RAM, TVI 925, Hazeltine, ADMSA emulations, software setup, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00  
 AJS10 - EX RENTAL, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00  
 ADDS 520 - Dumb terminal, used, 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00. Carriage on terminals £10.00  
 100's of other terminals in stock, CALL for more details.

### SURPLUS SPECIALS ON PRESTEL - VIEWDATA - TELEX

PLESSEY VUTEL, ultra compact unit, slightly larger than a telephone features A STANDARD DTMF TELEPHONE (tone dial) with 5" CRT monitor and integral modem etc. for direct connection to PRESTEL VIEWDATA etc. Designed to sell to the EXECUTIVE at over £600.00. Our price BRAND NEW AND BOXED at only £99.00

DECCAFAX VP1 complete Professional PRESTEL system in slimline desk top unit containing Modem, Numeric keypad, CPU, PSU etc. Connects direct to standard RGB colour monitor. Many other features include: Printer output, Full keyboard input, Cassette port etc. BRAND NEW with DATA, A FRACTION OF COST only £55.00

ALPHATHANAL. Very compact unit with integral FULL ALPHA NUMERIC keyboard. Just add a domestic TV receiver and you have a superb PRESTEL system and via PRESTEL the cheapest TELEX service to be found!! Many features: CENTRONICS Printer output, Memory dialling etc. Supplied complete with data and DIY mod for RGB or Composite video outputs. AS NEW only £125.00  
 Post and packing on all PRESTEL units £8.50

### EX-STOCK INTEGRATED CIRCUITS

4164 200 ns D RAMS 9 for £11 4116 ns £1.50 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95 27128 £5.50 8800 £2.50 8821 £1.68A09 £8 68B09 £10 8085A £5.50 8086 £15 8088 £8 NEC765 £8 WD2793 £28 8202A £22 8251 £7 8748 £15 Z80A DART £6.50 Z80A GPU £2.00. Thousands of IC's EX STOCK send SAE for list.

### DISK DRIVES

Japanese 5 1/4" half height, 80 track double sided disk drives by TEAC, CANON, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £85.00  
 TEC FB-503 Double sided HH 40 TRK NEW £75.00  
 SHUGART SA400 SS FH 35 TRK £55.00  
 SIEMENS FDD100 SS FH 40 TRK £65.00  
 carriage on 5 1/4" drives £5.50  
 Brand NEW metal 5 1/4" DISK CASES with internal PSU.  
 DSKC1 for 2 HH or 1 FH drive £29.95 +pp £4.00  
 DSKC 2 for 1 HH drive £22.95 +pp £3.50  
 DK9C 3 As DSK1 LESS PSU £12.95 +pp £2.50  
 DSKC 4 As DSK2 LESS PSU £10.95 +pp £2.00 etc.  
 8" IBM format TESTED EXE EQUIPMENT.  
 SHUGART 800/801 SS £175.00 +pp £8.50  
 SHUGART 851 DS £250.00 +pp £8.50  
 TWIN SHUGART 851's 2 Mb total capacity in smart case, complete with PSU etc. £595.00  
 MITSUBISHI M2894-83 8" DS 1 Mb equiv. to SHUGART SA850R. BRAND NEW at £275.00 +pp £8.50  
 DYSAN 8" Alignment disk £29.00 +pp £1.00  
 Various disk drive PSU's Ex Stock SEE PSU section.

HARD DISK DRIVES  
 DRE/DIABLO Series 30 2.5 Mb front load £525.00  
 Exchangeable version £295.00. ME3029 PSU £95.00  
 DIABLO 44/DRE4000A, B 5+5 Mb from £750.00  
 CDC HAWK 5+5 Mb £795.00. CDC 9762 80 Mb RM03 etc. £2500.00. £495.00  
 PERTEC D3422 5+5 Mb £495.00  
 RODIME 5 1/4" Winchester's ex-stock from £150 CALL  
 Clearance items - Sold as seen - No guarantee.  
 ICL 2314 BRAND NEW 14" Mb Removable pack hard disk drive, cost over £2000 with data ONLY £99.00  
 BASF 6172 8" 23Mb Winchester's £199.00  
 Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

**32 Biggin Way, Upper Norwood, London SE19 3XF**  
 Telephone 01-679 4414 Telex 894502 Data 01-679 1888

# Display ELECTRONICS

# READ/WRITE

## Decline And Fall?

In all honesty, do you really feel that your current issue can by any stretch of the imagination justify a price tag of £1.40?

As a loyal reader of ETI since it was first published in 1972 I feel more than qualified to complain at the way your publication is plodding drearily downhill.

In 1972 ETI cost 20p and had 88 pages. Now it costs £1.40 and has 68 pages. That is a 700% increase on the price and almost 25% less reading material.

Of the 68 pages on offer, your December issue has:

- 1 page contents
- 3 pages news and diary
- 3 pages foil patterns
- 2 pages PCB service
- 3 pages written by Messrs Brindley, Tame, Pitt and Armstrong
- 2 pages index
- 18½ pages commercial advertising

Less the front cover this leaves only 34½ pages of actual informative or constructional material. Most of this is well spaced and gobbles up page after page.

Of the remaining 35½ pages, 7½ were given over to your 'feature' on test equipment which was padding almost all the way. For goodness sake get it back together again.

Bob Collins  
St. Peter Port, Guernsey.

The size and price of ETI has indeed fluctuated quite wildly over the course of the 15 years it has been published. Although 700% seems to be a horrific increase, this is in line with other standard price comparisons such as a gallon of petrol or a pint of beer.

The size of ETI is dependant on the number of advertisements we carry. It is the ads which largely pay for the magazine. The more we carry, the bigger ETI can be. At its peak in 1981 ETI was regularly over 110 pages. How-

ever, things really were spaced out then!

Today ETI is slowly but surely increasing its circulation (and ad revenue) and so we can look forward to larger issues in the future.

Meanwhile, I think you are a little unfair on the contents. The very first ETI which apparently won your loyalty contained a much higher proportion of the 'padding' you now object to. There were six pages of news in that issue, two pages of book reviews and four pages of record reviews!

We do aim the magazine at a wider audience than simply project constructors although we are indeed increasing the number of small projects published. The majority of the letters we receive tend to confirm that the more general interest articles are appreciated by the majority. However, we do need to be told! If you feel strongly about how you think ETI should change, drop us a line and make your case.

## Frequently Wrong

Your news story in the December issue incorrectly stated that Radio Four's frequency was changing from 198kHz to 200kHz. In fact the old frequency is 200kHz and the new frequency is 198kHz (1515m).

Tony Carrington  
General Systems Engineer  
BBC, Bristol

Yes, sorry about that one. Not only that but we said the transmissions maintained a stability of one part in 10<sup>11</sup>. This should have read one part in 10<sup>11</sup>.

## Meltdown

I read the useful tip from Mr Startin in Read/Write in the December 1987 issue of ETI about reproducing printed PCB artworks using a photocopier.

I find this a great idea but, as an office equipment engineer, I have come across the situation many times where photocopiers use not only compression to fix the toner but also heat.

Can you imagine what an A4 sheet of transparent film looks like oozing out of the fuser rollers? Not a pleasant sight I assure you!

Please read any manual you have for your particular copier before trying this tip. Otherwise there may be some big engineers wearing very big boots knocking at your door!

G. Harrison  
Seaford, Liverpool

Good point, that. Thanks for warning us of a sticky situation.

## Washout

Last year I built your Ecolight ultrasonic activated light switch. The unit was working quite happily as the landing light but has recently been moved outside as a yard light.

All went well until it rained. Yes that's right, the rain activates the switch.


The unit was mounted out of the rain about 4ft off the ground with no bushes or trees within range.

Any bright ideas from ETI or any readers?

Andrew Jenkins  
44 Tudor Terrace, Gadlys,  
Aberdare, CF44 8EB

Tricky one, this. We can only suggest you mount the sensors horizontally so the rain (falling downwards!) moves at 90° to the sensor and therefore cannot trigger it (in theory). If that doesn't work, use the passive infra-red alarm circuit from last month instead!

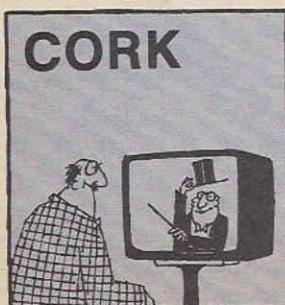Mr Jenkins would be pleased to hear from any readers who can help him on this one.



Mostly criticism this month. Still, we did ask for it. ETI is always happy to receive readers' comments and opinions, whether favourable or otherwise. Don't keep your thoughts to yourself. Write in to:

Electronics Today International  
1 Golden Square  
London W1R 3AB

# SUBSCRIPTIONS SENSATIONS!

## AT COVER PRICE ONLY!

Any of the magazines from the list below can be delivered to your door  
with :                      NO handling charge                      NO postage costs

A&B Computing	£18.00
Aeromodeller	£22.20
Citizens Band	£16.20
Clocks	£27.00
Commodore Disk User	£15.00
Disk User	£17.70
Electronics Digest	£11.00
Electronics Today International	£16.80
Ham Radio Today	£15.60
Military Modelling	£15.60
Model Boats	£15.60
Model Engineer	£26.40
Photography	£15.00
Photoplay	£12.00
Popular Crafts	£16.20
Radio Control Model Cars	£16.20
Radio Control Boat Modeller	£7.50
RCM&E	£14.40
Radio Control Scale Aircraft Quarterly	£9.00
Radio Modeller	£14.40
Sea Classic International	£11.70
Scale Models International	£15.00
Video Today	£15.00
Which Video?	£15.00
Woodworker	£15.60
Your Commodore	£14.40
Model Railways	£13.20
Practical Wargamer	£7.80

**The Above Prices Refer to U.K. Subscriptions Only**

This offer is also open to existing U.K. subscribers who  
may wish to extend their current subscriptions.

Please commence my subscription(s) To..... with the..... Issue  
I enclose my cheque/money order for £..... made payable to Argus Specialist Publications Ltd.  
or debit £..... from my Access/Barclaycard No.

valid from..... to..... Signature.....  
Name.....  
Address.....



Send this form with your remittance to:  
INFONET LTD. (N.R.S. 88) 5 River Park Estate,  
Berkhamsted, Herts. HP4 1HL.



# COMPETITION

Yes folks — yet again the generous folks at ETI are giving away valuable pieces of technologically advanced stuff for you to cuddle up with in your own homes.

The new *Interpack* range of interfacing modules are hot on the streets from DCP Microdevelopments in Norwich. The *Interpacks* link up to your micro using the appropriate DCP *Inter-card* and from there on the application possibilities are endless!

There's a detailed review of the three new DCP *Interpacks* in last month's issue so you can see just what these babies can do.

But what could **you** do? How clever could you be if you had your own *Interpack* and *Inter-card*?

Now's your chance to find out. We're giving them away! We want you to come up with an original and stunningly innovative application for one of the three *Interpack* types. You don't have to do a full-blown design, just explain what your 'Thing with an *Interpack*' would do and outline roughly how it would work. The winner gets the *Interpack* that they used and the *Inter-card* of their choice.

It's so easy! I've entered twice myself already.



So bung your 150-300 words on an enormous postcard and send it along with Your name  
Your address  
Your choice of Inter-card

to 'Thing with an Interpack' Competition  
ETI  
1 Golden Square  
London W1R 3AB

## The Interpacks

- INTERPACK 1:**  
8-bit I/O ports for TTL  
4-bit switch input port  
4 relay-isolated outputs 24V 1A  
8-channel ADC
- INTERPACK 2:**  
8 switch inputs  
6 relay outputs 24V 1A
- INTERPACK 3:**  
stepper motor driver, separate control of 3 motors available

## Pick A Card

ZX, BBC micro, Commodore 64, Apple II, Amstrad CPC, IBM PC, Scorpion.  
Also: DCP Bus Inter-card, Powerbus Card, Invertabus Card.

DCP Microdevelopments, 2 Station Close, Lingwood, Norwich NR13 4AX. Tel: (0480) 830997.

**Closing date: 1st February 1988**

ETI NEEDS YOU!

This copy of ETI is your magazine — in more ways than one. You bought it (and thank you for that!) but it is most of the contents.

Staff and regular contributors fill some ETI pages but we still have a constant need for good features, projects and circuits. We'll even pay you for them!

If, like most ETI readers, you build electronic devices of your own design we want to hear from you. You may have just finished the hi-est of hi amplifier, or a microprocessor-controlled Sellotape dispenser, or just a great gadget to impress your friends.

Whatever your project, if it will appeal to other readers it can earn you fame and fortune in ETI into

If you don't want to take your idea to a working prototype, novel circuits and improvements to existing ETI projects are always welcome for the ever-popular Tech Tips pages.

From experts in their fields we want features ETI has a reputation for presenting interesting, informative and wide-ranging features. If you know something the rest of us don't, tell us all through the pages of ETI.

Whatever you can contribute to ETI we want to hear from you soon. Write in with a brief description of your idea. Include a circuit diagram for projects and a brief synopsis of features.

Write to: **The Editor**  
**Electronics Today International,**  
**1 Golden Square,**  
**W1R 3AB.**

---

---

# DISH OF THE DAY

---

## Keith Brindley continues his overview of Satellite TV with a look at 60 systems currently available

---

**F**irst off, we should point out that the systems included in this ETI survey aren't the only systems — not by a long chalk! We had to stop somewhere and so our choice of the systems included here is purely arbitrary, based on the information we have been able to obtain from suppliers before going to press.

### The Gen

The table shows short-form information about satellite reception systems which has been made available to ETI by various manufacturers and suppliers.

Some suppliers sell the equipment as a complete system, in which case there is no problem in showing the systems' main features in tabular form.

On the other hand, some suppliers only supply individual parts of systems, it being left to the user (with some guidance from the supplier of course) to choose what is required. In such instances it is a bit more difficult to specify features and so readers are always advised to consult suppliers for final details of a chosen system.

Whatever the case, it is impossible to compare like for like because each system tends to have individual features (if not gimmicks!) which are unique to it. Also, most suppliers are willing to sell all parts (receivers, actuators, antennae, antenna mounts, LNBS) separately so it is perfectly possible for readers to build their own systems from different sources. You really need to know what you're doing though, to make sure all parts match.

We've limited the survey purely to STV systems suppliers for the good reason that most of the larger suppliers (NEC, Rediffusion and so on) see the future of STV in terms of systems sales only — not individual parts. STV isn't like hi-fi where users can choose individual kits (a tuner here, cassette deck and amplifier there) and know that a first-class system will result. STV systems are a bit more delicate than audio systems because they are dealing with microwaves.

One supplier made the point to ETI that setting up a microwave system is something like DIY plumbing. A good analogy — you don't know whether it's going to work until you've turned it on, and by then it's too late. Water, water everywhere!

The information detailed here, then, refers only to complete systems supplied from single sources and can only cover the main range of features common to all systems.

You'll see that suppliers in this ETI survey supply a range of systems from simple, fixed position antenna (for single satellite reception) through to complex multi-satellite reception systems.

Prices of systems are shown but are only included as a guideline — some suppliers specify price exactly but as most rely on smaller sales outlets like your local television shop, prices can vary. The moral is to shop around. Prices generally do not include installation so £150 to £250 should be added to the basic system price

to cover this — unless you're going to do it yourself.

However, most suppliers do not advise a DIY approach, saying that only qualified personnel can do the job properly. Presumably, many ETI readers will be up to the job and we'll leave the choice to you. Details of DIY system set-up are outside the scope of this article but may be covered in a future issue of ETI if demand sees fit.

Neither do prices include cost of programme reception. At the time of writing only two channels are encrypted (Filmnet and Skychannel) — although Premiere intends to encrypt on the 5th of January). Until the user has paid for a decoder and subscriptions, these cannot be legally received. Even some un-encrypted channels require payment of subscription, although the channels would be the first to admit that not every viewer has paid the dues.

Most channels, however, are considering encryption shortly, so all users must bear in mind that future cost. Details of encryption, decoding and subscriptions are available from: The Satellite Programme Clearing House, The Quadrangle, 180 Wardour Street, London, W1V 4AE.

### Antenna


The Antenna size you require depends very much on where you live. In the south of England, some suppliers say that a 0.9m antenna is suitable for current transmissions — personally, I'd ask to see this in operation before I paid out my money. A dish size of 1.2m is probably a safer bet to achieve good reception in London. Further north the antenna needs to be bigger — up to 1.8m or bigger in Scotland. Again, though, always ask to see operation first.

Whatever sized dish you end up with, you can at least be assured that any future television channels received by satellite, either DBS or from the intermediate Astra will be more than adequately picked up.

On the subject of antennae, it might be worth considering when televisions themselves were first being installed (before my time!) their aerials were considered part of the system and installation costs were a necessary evil. Once fitted, however, any television receiver bought at a later date can be used with the same aerial.

That's much the same as the situation now with satellite reception systems — the antenna you buy with your system, if chosen carefully, could be with you for a long time. It should certainly see out your chosen system's receiver and be used with whatever receiver you buy in the future. At the price you'll pay, it can't really be considered a disposable item!

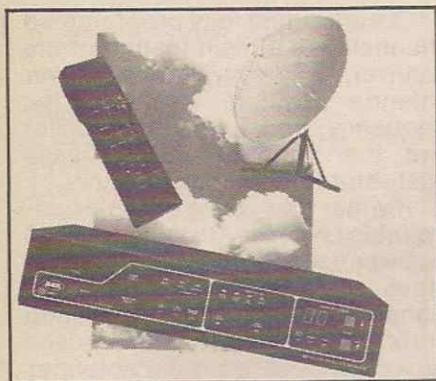It only remains to look at each supplier's range of systems individually. Further specifications and details of any system can be sought from the supplier's address given with each listing and suppliers will be able to provide readers with details of local outlets and installers.



**BEL-Tronics (UK) Ltd**  
**Cherry Orchard North**  
**Kembrey Park**  
**Swindon**  
**Wilts SN2 6BL**

BEL-Tronics (UK) is the British subsidiary of Bel-Tronics of Canada. All the company's TVRO equipment is manufactured there having been on sale in Canada for many years. This has the advantage that it is tried and tested before finding its way to the British market place. A Bel system is certainly not the cheapest but in most respects it's one of the best.


The systems offered are based around the Micro Eye receiver. The customer merely has to choose the required size of antenna to suit and decide whether reception is to be from a single satellite or many.

The Micro Eye is quite a classy receiver and is one of the best looking around. Technically speaking, it's one of the most advanced too, with all features being remotely controlled. Over 60 channels can be fully programmed into the receiver and from there on merely calling up a program invokes the necessary adjustments to antenna position, LNB polarity and internal electronics to select the required satellite, transmission polarity, frequency and audio sub-carrier.

A free site survey is included and a maintenance contract offered after the initial guarantee period.

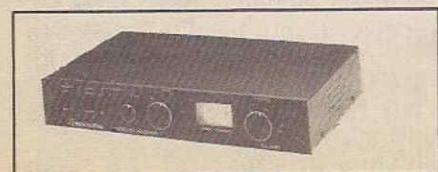**Technical Specification**

- receiver (input level: -60dBm to -20dBm. Noise figure: 6dB. Audio sub-carrier tuning: 5-8.5MHz)
- LNB (noise figure: 2.1dB. Gain: 50dB min)
- antenna in sizes of 1.2, 1.5, 1.8m (gain 41, 42.5; 44.5dB. 3dB beam width 1.5°, 1.25°, 1°)



Make	Model	No of prog	Main features	Diam	Type	Price
BEL-Tronics	Micro Eye	>60	P, POL, R, St	1.2	B	1325
BEL-Tronics	Micro Eye	>60	P, POL, R, St	1.5	B	1440
BEL-Tronics	Micro Eye	>60	P, POL, R, St	1.8	B	1550
BEL-Tronics	Micro Eye	>60	P, POL, POS, R, St	1.2	B	2000
BEL-Tronics	Micro Eye	>60	P, POL, POS, R, St	1.5	B	2120
BEL-Tronics	Micro Eye	>60	P, POL, POS, R, St	1.8	B	2250
Champ	WR-516		P, POL, R	1.2		850
Champ	WR-516		P, POL, POS, R	1.8		1500
Connexions	CX1260B	n/a	M, POL	1.2	O	695
Connexions	CX1860B	n/a	M, POL	1.8	*	845
Connexions	CX1260D	32	P, POL, POS, R	1.2	O	995
Connexions	CX1860D	32	P, POL, POS, R	1.8	*	1145
Connexions	CX8012		P, POL, POS, R, St	1.2	O	1195
Connexions	CX8018		P, POL, POS, R, St	1.8	*	1275
Eledyne	00	n/a	M, POL	1.2/1.5	B	770
Eledyne	01	n/a	M, POL, POS (by hand)	1.2/1.5	B	850
Eledyne	02	n/a	M, POL, POS	1.2/1.5	B	1075
Eledyne	03	32	P, POL, POS, R	1.2/1.5	B	1140
Eledyne	04	36	P, POL, POS, R	1.2/1.5	B	1350
Ferguson	ES03	149	P, POL, R	1.2	B	1245
Ferguson	ES01	149	P, POL, R	1.5	B	1345
Ferguson	ES03	149	P, POL, POS, R	1.2	B	1545
Ferguson	ES01	149	P, POL, POS, R	1.5	B	1645
Ferguson	ES02	149	P, POL, R	1.8	*	1645
Ferguson	ES02	149	P, POL, POS, R	1.8	*	1945
Grundig	STR200	29	P, POL, R	1.5	B	1700
Luxor	Mark 2-1	24	P, POL, R, St	1.25	B	916
Luxor	Mark 2-2	24	P, POL, R, St	1.6	B	980
Luxor	Mark 2-3	24	P, POL, R, St	1.8	B	1111
Luxor	Mark 2-4	24	P, POL, POS, R, St	1.25	B	1330
Luxor	Mark 2-5	24	P, POL, POS, R, St	1.6	B	1390
Luxor	Mark 2-6	24	P, POL, POS, R, St	1.8	B	1520
Megasat	XX3R	n/a	M, POL	1.2	O	850
Megasat	XX3RI	99	P, POL, POS, R	1.2	O	1250
Megasat	XX3G	576	P, POL, POS, R, St	1.2	O	1500
NEC	Nesat 2000	50	P, POL, R	1.5	B	1100
NEC	Nesat 2000	50	P, POL, R	1.8	*	1200
NEC	Nesat 2000	50	P, POL, POS, R	1.5	B	1500
NEC	Nesat 2000	50	P, POL, POS, R	1.8	*	1600
Rediffusion	RSR30	30	P, R	1.2	B	800
Rediffusion	RSR30P	30	P, POL, R	1.2	B	970
Rediffusion	RSR50	50	P, POL, POS, R	1.25	B	1350
Rediffusion	RSR50	50	P, POL, POS, R	1.5	B	1430
Rediffusion	RSR50	50	P, POL, POS, R	1.7	B	1450
Salora	SRV1150-1	32	R	0.9	B	549
Salora	SRV1150-2	32	P, R	0.9	B	669
Salora	SRV1150-3	32	P, POL, R	1.25	B	880
Salora	SRV1150-4	32	P, POL, R	1.6	B	950
Salora	SRV1150-5	32	P, POL, R	1.8	B	1070
Salora	SRV1150-6	32	P, POL, POS, R	1.25	B	1290
Salora	SRV1150-7	32	P, POL, POS, R	1.6	B	1360
Salora	SRV1150-8	32	P, POL, POS, R	1.8	B	1480
Skyscan	K1	24	P, POL, POS, R	1.5	O	1299
STS	312	n/a	M	1.2	O	799
STS	314	n/a	M, POL	1.2	O	899
STS	316	n/a	M, POL, POS (by hand)	1.2	O	999
STS	318	n/a	M, POL, POS	1.2	O	1199
STS	322	72	P, POL, POS, R	1.2	O	1299
STS	324	72	P, POL, POS, R	1.2	O	1399
SVT	GS-1	99	P, POL, POS, R			1600

Prices are quoted in most cases as approximate retail price including VAT. Installation is generally extra. Check all prices with your local sales outlet.

**Main features: tuning (P=preset, M=manual). LNB (POL=polarisation control). Antenna (POS=antenna positioning). Receiver (R=remote control, St=stereo)**

**Antenna: diameters are quoted in metres. Type (B=basic, O=offset, \*=petalised)**

**Connexions (UK) Plc**  
**Unit 3,**  
**South Mimms Distribution Centre**  
**Huggins Lane**  
**Welham Green**  
**Herts AL9 7LE**

Like Bel-Tronics' Micro-Eye, Connexions TVRO systems have been around for a few years which means that equipment is tried and tested and the company has a large foot in the marketplace door. Also like Bel-Tronics, the company originated from abroad — unlike

Bel-Tronics, however, the originating company is from Taiwan where the equipment is manufactured.

Systems range from cheap single satellite reception to a multi-satellite programmed reception. New systems are being introduced regularly. Rather than using a single receiver the company has opted to produce different receivers, depending on customer requirement. In this way users requiring simple systems don't have to pay for unused refinements.

For example, the bottom of range systems use a rotary tuning knob while higher up models feature digital readout of channels. Further, medium range systems use a separate antenna positioning control unit from the receiver, while the top of range receiver uses internal electronics to do the job.

Only two antenna sizes are offered: 1.2m and 1.8m but there is a range of LNBs to suit individual applications.

#### Technical specification

- CX2460 receiver (input level: -45dBm to -30dBm. Audio sub-carrier tuning: 4.5-8MHz)
- CX1321 LNB (noise figure: 1.8dB. Gain: 50dB)
- antenna in sizes 1.2, 1.8m (gain: 43.5, 44.7dB. 3dB beam width: 1.2°, 1°)

**Eledyne Ltd**  
Isaac Newton Way  
Alma Park  
Grantham  
Lincs NG31 9RT

Eledyne is part of a much larger group which has supplied control equipment for 17 years. The company's satellite reception equipment is imported from the east and a great deal of testing and re-tuning is apparently undertaken before customers see it.

Equipment ranges from a cheap and cheerful single satellite receiver system to a full spec multi-satellite remote control system.


Only 1.2 and 1.5m antennae are shown (system prices are the same for both sizes) but smaller (90cm) and larger (up to 2.4m) are available so check your local outlet for prices and details. Prices listed are for GRP antennae. Spun aluminium antennae are available at a surcharge of about £20.

#### Technical Specification

- receiver (input level: -55dBm to -20dBm. Noise figure: 2dB. Audio sub-carrier tuning: 4.8-8.2MHz)
- LNB (noise figure: 2dB. Gain: 50dB min)
- antenna in sizes 1.2, 1.5 metre (gain: 40.5, 43.5dB. 3dB beam-width: 1.5°, 1.25°)

**Ferguson**  
(Thorn EMI Ferguson Ltd)  
Cambridge House  
270 Great Cambridge Road  
Enfield  
Middlesex EN1 1UL

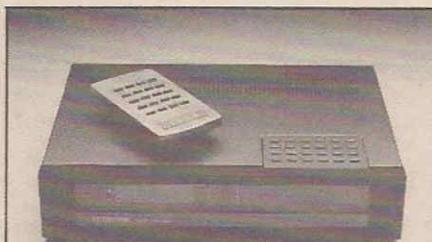To our knowledge, Ferguson was the first big name in British electronics to put a toe in the water and test the satellite reception system market. According to reports the



water must have been pretty cold and there seemed to be a number of problems in use with the SMO1 receiver.

However, the original system has been updated to help heat the water and Ferguson has now gone in at the deep end with a full range of systems based around a new receiver, the SM02.

The SMO2 features a 149 channel memory with remote control. Its memory can only be classed as 'semi-programmable' as only transmission frequency is remembered. Antenna position and LNB polarisation have to be done separately.

All-in-all, the prices for the various systems offered seem pretty high but the potential user has to bear in mind the Ferguson name bought with them.

#### Technical Specification

- receiver (input level: -55dBm to -25dBm. Noise figure: 12dB)
- LNB (noise figure: 2.3dB. Gain: 53dBm)
- antenna in sizes 1.2, 1.5, 1.8m (gain: 42, 43, 44.5dB)

**Grundig International Ltd**  
Mill Road  
Rugby  
Warwickshire CV21 1PR

Another of the 'big boys' who has recently entered the satellite arena, Grundig offers a single system with a good specification, albeit fairly pricey for what it is. The Grundig name, however, may be the enticement to persuade potential buyers.



Twenty-nine fully programmed channels are a main feature of the receiver, allowing control over antenna position, LNB polarity, frequency and audio sub-carrier and the remote control means push-button choice of channel.


Rather than using a single controllable LNB, the Grundig STR500 receiver used in the system has two input sockets corresponding to signals from two LNBs (receiving horizontal and vertical polarised signals) mounted on the antenna.

#### Technical Specification

- receiver (no specification available)
- LNB (noise figure: <2.2dB)
- antenna (gain: 43dB. 3dB beam width: 1.25°)

**Luxor Satellite**  
Bridgemoor Close  
Westmead  
Swindon SN5 7YG

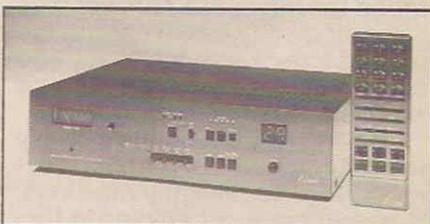Luxor is a subsidiary of Salora, which also produces satellite reception systems and although a comparatively new name in British television it is part of the Nokia Group of Finland originating way



back in 1926. The two companies operate under separate identities.

Luxor satellite reception systems are all based around the Luxor Mark 2 receiver which has some impressive features including Dolby stereo, a signal strength meter and 24 programmable channels.

Use of a single channel receiver to cover all options means a user can upgrade fairly easily and cheaply but it does mean that lower spec systems can be quite pricey because the user has to pay for some unused features.

A separate antenna control unit is used in the multi-satellite system but is controllable directly from the receiver's hand-held remote control unit. Three sizes of antenna are offered.


#### Technical Specification

- receiver (input level: -70dBm) to -30dBm. Audio sub-carrier tuning: 5-8MHz)
- LNB (noise figure: 1.9dB. Gain: 50dB min)
- antenna in sizes 1.25, 1.6, 1.8m

(gain: 41.7, 43.8, 45dB. 3dB beam width: 1.5°, 1.2°, 1°)

**Megasat Ltd**  
**5 St Pancras Commercial Centre**  
**Pratt Street**  
**London EC4A 3JB**

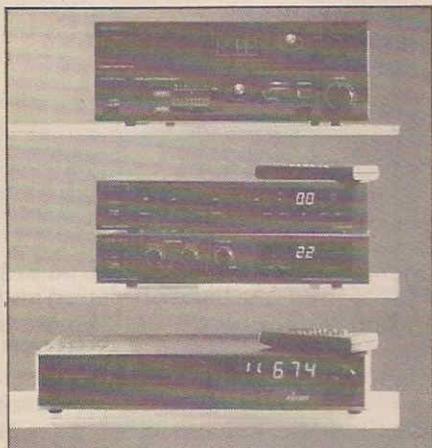Megasat has been around in satellite television reception systems for a while and has considerable experience in its marketing.



The company doesn't manufacture (or badge manufacture) receivers as such, merely buying in receivers from outside and combining them with other required hardware to form complete systems. Most manufacturers' hardware can be supplied by Megasat.

Megasat's XX3 range includes Rockdale receivers (XX3R and XX3RI) and the well-known Gensat receiver (XX36). New systems to be released shortly after the time of writing include Drake receivers and the Rediffusion RSR50 receiver. These systems will be available by publication date.

With the release of the latest systems Megasat is also launching the 'Compact Dish' — a 90cm antenna which appears to have extremely good characteristics — and a new LNB with noise figure claimed to be as low as 1.2dB.

Technical specifications and prices for the new systems were unavailable at the time of writing. Interested readers should contact Megasat direct.

**NEC Business Systems (Europe) Ltd**  
**35 Oval Road**  
**London NW1 7EA**

NEC first entered the TVRO market a year or so ago although its commitment to satellite television reception is far older and far wider. NEC was one of the world's leading

manufacturers of satellite reception equipment.

The present NEC TVRO systems are based around the Model 2022 receiver which is a good-looking programmable device offering a number of features such as on-screen graphics, last-channel memory and MAC output (so you can add necessary decoders to receive future signals).

Indeed the only real drawback foreseen with the receiver is that it is not *fully* programmable. Antenna position needs to be set with a separate instruction to the channel number so changing channels on different satellites is not just done by pressing one button. It's really only a small niggle but one which many customers may regard as important — we're not all computer/electronics whizzkids! Other receivers, notably the Rediffusion RSR50, achieve channel *and* satellite changeover with more simple operations.

The same receiver services all systems in the range, purely because the antenna actuating



device is classed as optional and there is a choice of two antenna sizes. An electronic polariser is used — a nice finishing touch to a well thought out range.

#### Technical Specification

- receiver (input level: -60dB to -30dB. Audio sub-carrier tuning: 5.5-8MHz)
- LNB (no data forwarded)
- antenna in sizes 1.5, 1.8m (no data available)

**Rediffusion Radio Systems Ltd**  
**Satellite Systems Division**  
**Unit 9 Mole Business Park**  
**Randalls Road**  
**Leatherhead**  
**Surrey KT22 7BA**

It was only a matter of time until one of the big British names produced a system capable of doing everything at a reasonable price. It



just happened to be Rediffusion. This type of approach is likely to herald the way forward because most customers don't want to fiddle with dozens of knobs and buttons to change channels — they want a single push button, just as they change channels on their existing television set.

Systems are based around two main receivers, the RSR30 and the RSR50. The RSR30 is nothing to write home about. In fact, in its basic form the receiver doesn't even allow control over LNB polarisation. The RSR30P, a derivative of the basic receiver, does. Also available is a dish position control unit for these receivers.

It is the RSR50 receiver-based systems which are of note. They feature *full* programmability of 50 channels — all channel details (frequency, antenna position, LNB polarity, audio sub-carrier and so on) are stored and you need only to press the channel number to change satellite channels and pick up a new programme.


Three antennae are available with RSR50 systems although only one is specifically for RSR30 systems.

#### Technical Specification

- RSR30 and RSR50 receivers (input level: -60dBm to -25dBm. Noise figure: 12dB. Audio sub-carrier tuning: 5-8.5MHz)
- LNB (noise figure: 2.2dB. Gain: 55dB)
- antenna in sizes 1.2, 1.25, 1.5, 1.7m (gain: 40, 41, 43.5, 44.5dB)

**Salora (UK) Ltd**  
**Bridgemoor Close**  
**Westmead**  
**Swindon SN5 7YG**

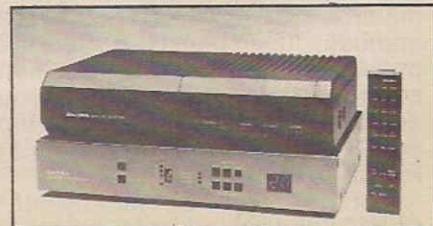Salora is the parent company of Luxor and like Luxor it manufactures complete satellite reception systems and sells products individually. Although a relative newcomer to the British television



scene, the company is part of the Nokia Group of Finland and has been around since 1926. The company claims to have over 700 dealerships throughout the UK which must make it one of the biggest satellite reception system suppliers.

Salora satellite reception systems are based around the Salora SRV1150 receiver and systems differ only in the extra lines which are bought with the receiver.

The SRV1150 is one of the nicest looking receivers available. It has a 32 channel memory which together with a separate antenna control unit (part of the multi-satellite systems) allows fully programmable control over channel choice.

A selection of four antenna sizes complements the range of systems, including a recently introduced 90cm dish.

#### Technical Specification

- receiver (input level: -60dBm to -30dBm. Noise figure: 6dB. Audio sub-carrier tuning: 5.5-8.5MHz)
- LNB (noise figure: 2dB. Gain: 50dB min)
- antenna in sizes 1.25, 1.6, 1.8m (gain: 41.7, 43.8, 45dB. 3dB beam width: 1.5° 1.2° 1°)

#### Satellite Technology Systems Ltd Satellite House Blackswarth Road Bristol BS5 8AU

Although a comparative newcomer to the television scene, STS has concentrated on SMATV for a while and has recently entered the TVRO market where its SMATV experience stands it in good stead. The company also offers good training for its dealers in installation techniques.



Systems are based around two main receivers — a simple to operate but basic STS300M and the more complex and programmable STS320R. The STS300M is a manually tuned beast but offers the possibility of antenna position control via hand-cranking or (if you don't like the idea of having to nip outside to turn your antenna) motor drive.

The STS320R is remotely controlled, and allows the facility of

programmability, using a separate remotely controlled dish actuator.


All systems are based on use of a 1.2m antenna but a 1.8m antenna option is available for around an extra £250.

#### Technical Specification

- STS300M and STS320R receivers (input level: -55dBm to -20dBm. Audio sub-carrier tuning: 4.8-8.2MHz)
- LNB (no data available)
- antenna (no data available)
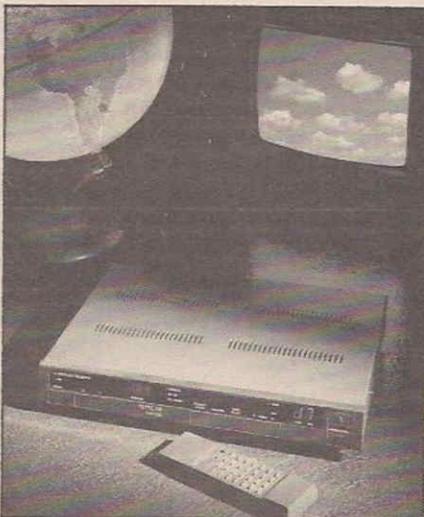
#### Skyscan Satellite Television Unit 2, Priors Way Maidenhead Berkshire SL6 2HP

Another well established company in the satellite receiving systems arena is Skyscan. The K1 system has been around for a little while, proving to be reliable and versatile. Notably, Skyscan is the only company to have issued an exact retail price — all other companies only state approximate retail prices which depend on local suppliers' mark-up and so forth.



Satellite channels can only be described as 'semi-programmable' because the user has to first tell the receiver a code for the satellite and then change the channel. The receiver alters antenna position and adjusts polarity and the audio sub-carrier to suit.

One clever feature which Skyscan is rightly proud of is the fact the antenna steering mechanism is set up to always approach the final antenna position from the same direction, helping to eliminate possible hysteresis effects in the mechanics which may occur with wear through time.

Only one system is offered with just one receiver, one LNB, and one antenna. It really couldn't be simpler. This no doubt helps the

company to maintain the system's low price.

#### Technical Specification

- receiver (input level: -55dBm to -15dBm. Audio sub-carrier tuning: 5-8.5MHz)
- LNB (noise figure: 2dB. Gain: 55dB)
- antenna (gain: 44dB)

#### SVT Video Systems Ltd Heybridge Industrial Estate Holloway Road Maldon Essex CM9 7XS



A newcomer to the TVRO marketplace, SVT has been operating for a while in more general areas of television equipment and SMATV television distribution systems.

The SVT system is based around the Palcom GS-1 satellite receiver which in itself offers high flexibility with ease of use. Up to 99 channels can be fully programmed into the receiver which takes care of antenna positioning, LNB polarity, frequency and audio sub-carrier. Useful is an analogue signal strength meter for tuning by scan mode.

Notably, SVT is one of the few companies whose system price includes installation (subject to site survey).

#### Technical Specification

- receiver (input level): <-60dBm. Noise figure: <dB. Audio sub-carrier tuning 5-8MHz)
- LNB (no data available)
- antenna (no data available) **ETI**



# IMAGINARY TIMES

Paul Chappell continues to delve the depths of the complex plane

In introducing complex numbers last month, I went to some trouble to avoid using the terms 'real' and 'imaginary' which are a hangover from Victorian uncertainty about the status of  $\sqrt{-1}$ . Sadly, the terms are still in common use so I must now submit to convention and start using the horrible things myself.

For a number like  $2+j3$ , it is usual to refer to the 2 as the *real* part and the 3 (not  $j3$ ) as the *imaginary* part. There, I've said it. Now I'll go and wash my mouth out.

Complex numbers can be visualised as points on a plane. Figure 1 shows the general idea. The correspondence between the numbers and their representation is obvious, so I'll let the diagram speak for itself.

The plane where complex numbers live is called, naturally enough, the complex plane. It is sometimes referred to as the *z*-plane since it is conventional to use the symbol *z* to denote an arbitrary complex number, just as *x* might stand for any old real number.

Addition of complex numbers is best demonstrated by putting a few arrows into the diagram. Figure 2a represents  $2+j0$ , Fig. 2b shows  $3+j0$ , Fig. 2c shows their sum which is  $5+j0$ . The arrows add nose to tail. When the imaginary part is zero, it is often left out altogether, so this sum might be written:  $2+3=5$ . Revolutionary stuff, eh?

Figures 2d, e and f represent  $(2+j3)+(4+j1)$ ,  $(2+j3)+(-4+j1)$  and  $(2+j3)+(-4-j1)$  respectively. When a complex number arrow begins at the origin, it is said to be *bound*. The arrow, or vector, representing  $2+j3$  is bound in Fig. 2d, e and f. If the vector is moved to a

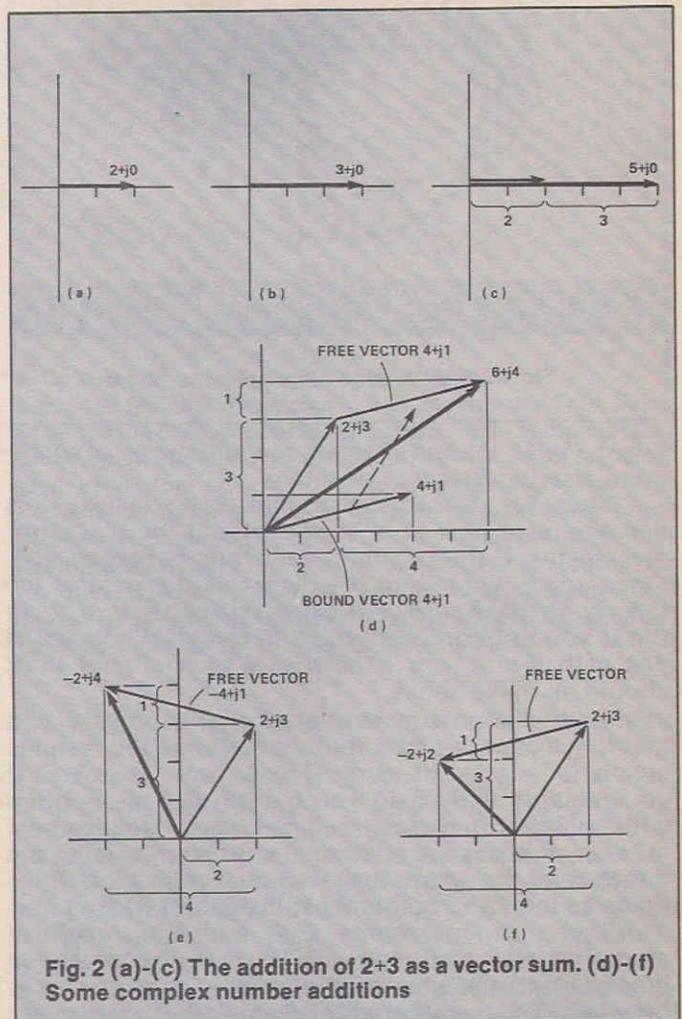


Fig. 2 (a)-(c) The addition of  $2+3$  as a vector sum. (d)-(f) Some complex number additions

different position, it is said to be *free*. The rule for shunting vectors about is demonstrated in Fig. 2d. They keep the same length and direction at all times.

Without the diagrams and arrows, you simply add the real and imaginary parts individually, so  $(2+j3)+(-4-j1) = (-2+j2)$ . If you remember that we're allowing *j* the status of a real number and that you'd be quite happy to write  $(2+3\pi)+(-4-\pi)$  as  $(-2+2\pi)$ , the reason for adding in this way becomes evident. With 'pi-numbers,' you add the good parts and the pi-parts individually, right?

Returning to the arrows, subtracting one complex number from another is simply a matter of reversing the arrow for the one to be subtracted. Figure 2d represents  $(2+j3)+(4+j1)$  whereas Fig. 2f (where the free vector points in the opposite direction) represents

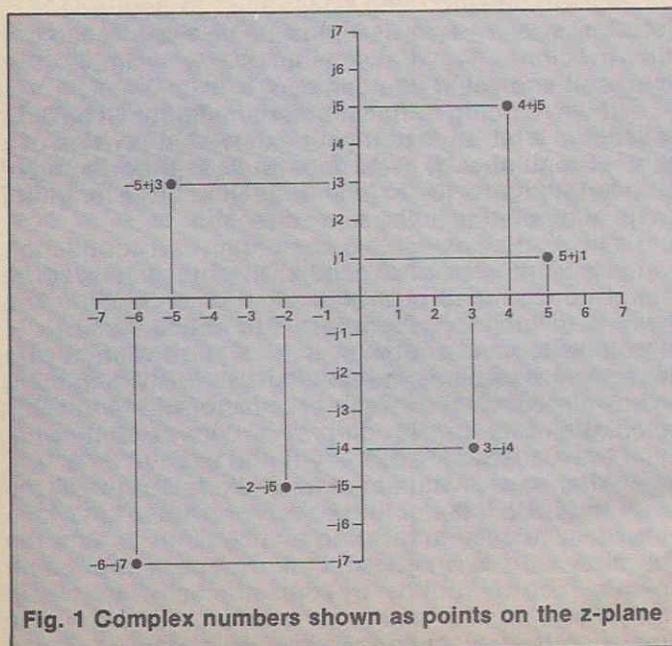


Fig. 1 Complex numbers shown as points on the *z*-plane


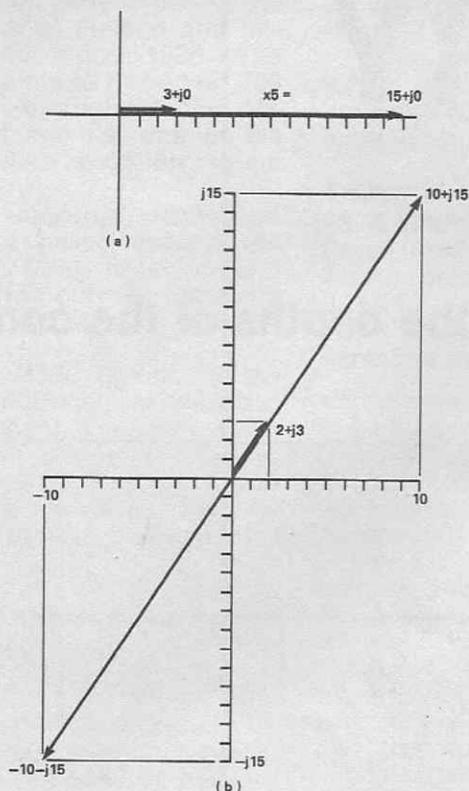
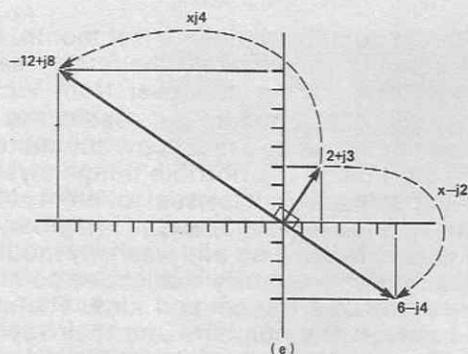


Fig. 3 Multiplication of complex numbers

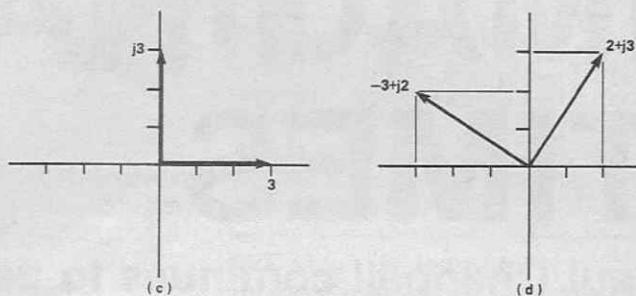

$(2+j3)-(4+j1)$ . (I hope all this is reminding you of something else you've seen recently!)

Since Fig. 2f also represents  $(2+j3)+(-4-j1)$ , this demonstrates how to subtract without the diagrams: reverse the signs of the second number, then add. Once again, I'm letting the diagrams do most of the talking, so make sure you've got it sussed before going on! If you get confused, think in terms of how you'd deal with pi-numbers (if there were such a thing) and it should all make sense.

Multiplication is more interesting. First of all, if you multiply a complex number by a real one, the result is simply to increase its length. Fig. 3a represents  $3+j0$ . If you multiply it by  $5+j0$  you get  $15+j0$ . This is often written  $3 \times 5 = 15$ . If you multiply by a negative real number, this has the additional effect of reversing the direction of the arrow:  $3+j0 \times -5 = -15+j0$ , which is five times as long and points West instead of East.

Figure 3b represents  $2+j3$  and the result of multiplying this by 5 and by -5. The arrow becomes five times as long and when multiplied by -5 it also reverses direction. The results are  $10+j15$  and  $-10-j15$ , which are simply the results of multiplying the real and imaginary parts individually by 5 or -5. You can think of pi-numbers again here but they are about to outlive their usefulness.

Now, what happens if we multiply by  $j$ ? If 3 is multiplied by  $j$ , the result is obviously  $j3$ . Figure 3c shows the before-and-after picture.

The arrow has the same length but is now pointing in a different direction. How about  $(2+j3) \times j$ ? The result is  $j2+j^23$  and since  $j^2 = -1$  (because  $j = \sqrt{-1}$ , right?) this can be written  $-3+j2$ . In Figs. 3c and 3d, multiplying by  $j$  leaves the length of the arrow unchanged but rotates it anti-clockwise by  $90^\circ$ . This is no coincidence!

Multiplying by  $j4$  rotates anti-clockwise by  $90^\circ$  and stretches the arrow by a factor of 4. Multiplying by  $-j2$  doubles the length and rotates clockwise by  $90^\circ$ . The graphical results are shown in Fig. 3e. You can do the

arithmetic for yourself!

Now to multiply a complete complex number by another. Let's try  $(2+j3) \times (5+j4)$ . Graphically this is a matter of multiplying  $(2+j3)$  by 5 (Fig. 3b), then  $(2+j3)$  by  $j4$  (Fig. 3e), then adding the results. This time you can draw the diagram for yourself!

Remembering that the vectors add nose-to-tail, you should end up at  $-2+j23$ . As a long-hand calculation, it looks like this:

$$\begin{array}{r} 2+j3 \\ 5+j4 \\ \hline 10+j15 \\ \quad j8-12 \\ \hline 10+j23-12 \\ \hline = -2+j23 \end{array}$$

The pattern here is not quite so easy to see but there is one. Try drawing out a few examples for yourself and see if you can spot it.

If we're going to finish before midnight I'll have to speed up a bit, so fasten your safety belt! Division of a complex number by a real one results in a shortening of the length so  $(a+jb)/2 = (a/2+jb/2)$  — half the length of  $a+jb$  and pointing in the same direction.

Dividing by a negative number gives a contraction and also a reversal of direction. Dividing by  $j$  leaves the length unchanged but rotates clockwise by  $90^\circ$ . The way to divide by  $j$  in symbols is to notice that  $1/j = -j$  (multiply top and bottom by  $j$ , right?) so dividing by  $j$  is exactly the same as multiplying by  $-j$ . Dividing by  $jn$  gives a reduction in length by a factor of  $n$  and a  $90^\circ$  clockwise rotation. Dividing by  $-jn$  does exactly what you have guessed it will. Try it and see!

When faced with something like  $(a+jb)/(c+jd)$  the way to tackle it is not immediately obvious. Let's take the idea we used in dividing by  $j$ . We'll try to turn the division into a multiplication. Suppose we could multiply top and bottom by some number which would give a real number as the denominator. Dividing by a real number is something we can already do so it

# CIRCUIT THEORY: Complex Numbers

should crack the problem. Let's try an example and see what happens. Try  $(2+j3)/(4+j5)$ , for instance. First of all, what can we multiply  $4+j5$  by to turn it into a real number? We begin a long-hand multiplication to see:

$$\begin{array}{r} 4+j5 \\ 2+j? \\ \hline 8+j10 \\ j \dots \end{array}$$

How do I know the number we want is  $2+j$  something? I don't know. I chose the 2 at random to see what would happen. If the imaginary parts are going to cancel out, then ? must clearly be  $-2\frac{1}{2}$ , so let's continue:

$$\begin{array}{r} 4+j5 \\ 2-j2.5 \\ \hline 8+j10 \\ -j10 +12.5 \\ \hline 8 +12.5 = 20.5 \end{array}$$

So the original division problem can be transformed into:

$$\frac{2+j3}{4+j5} = \frac{(2+j3) \times (2-j2.5)}{20.5}$$

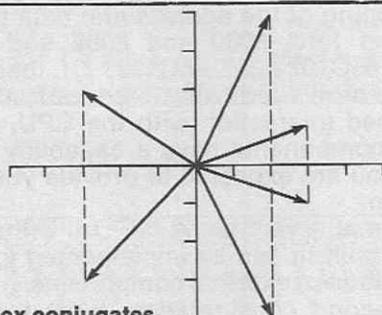


Fig. 4 Complex conjugates

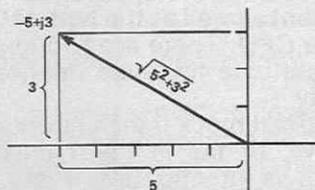


Fig. 5 The modulus of a complex number

which we can do! I'll leave you to work out the answer.

The idea of multiplying one complex number by another to give a real number answer is a very useful one. If you have a complex number  $a+jb$ , multiplying it by  $a-jb$  will give the answer  $a^2+b^2$ , which is a real number — not a  $j$  in sight!

The numbers  $a+jb$  and  $a-jb$  are *complex conjugates* of each other. To find the conjugate of any number, just reverse the sign of the imaginary part. If you want to refer to the complex conjugate of a number, it is usual to put a bar over the top, like the negation sign in logic (although the meaning is entirely different) so  $\overline{a+jb} = a-jb$ .

Some pairs of conjugates are shown in Fig. 4. They are 'reflections' of each other in the real axis. Bearing in mind that the result of multiplying any pair together will give an answer on the positive real axis, this might give you another clue about the interpretation of multiplying complex numbers, if you haven't already sussed it.

If  $z$  is a complex number and  $\overline{z}$  its conjugate then anything of the form  $kz\overline{z}$ , where  $k$  is real, will give a real number as the result. The number we hit on by experiment in the earlier division would give  $k$  the value 0.5 (because  $2-j2.5$  is half of  $4-j5$ , which is the conjugate of  $4+j5$ , right?)

Throughout the article I have spoken loosely about



Girolamo Cardano  
1501-1576

Cardano is credited with cubic equations. being the first mathematician His morals may not have to derive the basic properties equalled his mathematical of complex numbers — an skills — his book of dice idea well before its time. games contained extensive Cardano was a professor advice on cheating and of medicine, astrologer and rumour has it that his keen gambler. Apart from his remarkable cubic equation controversial horoscope of formula was actually the Jesus, he is best known for invention of Tartaglia. deriving a method for solving Cardano stole it!

the length of a complex number. In formal terms, this is known as its *modulus* and can be calculated from Pythagoras' theorem (Fig. 5). If  $z=a+jb$  then the modulus of  $z$  (written  $|z|$ ) will be  $\sqrt{a^2+b^2}$ . This gives the distance of the number from the origin, or the 'length of its arrow.' The modulus of  $-4+j0$ , for instance, will be  $\sqrt{16+0} = 4$ , often written  $|-4| = 4$ . The modulus of  $3-j4$  will be  $\sqrt{9+16} = 5$ .

An alternative way of identifying a complex number is to specify its distance from the origin and the angle its arrow makes with the positive real axis. By convention, the angles are measured in an anti-clockwise direction. The distance from the origin is the modulus. The angle is referred to by the quaint old term 'argument'. You can't argue with that.

One thing I hope you picked up from this article is that the arithmetic of complex numbers doesn't conflict with the arithmetic of ordinary numbers. (It would cause a lot of problems if it did!) If you apply complex number arithmetic to the set of complex numbers where the imaginary part is zero, it churns out the ordinary number arithmetic that you learned at your mother's knee.

I hope you're also beginning to feel a certain sense of *déjà vu* over some of the results. Looks a lot like phasors, doesn't it? Next month I'll be digging a lot deeper into complex numbers and beginning to tie them in to the behaviour of electronic circuits.

ETI

# THE DIRECT APPROACH

## Mike Barwise unravels the mysteries of direct memory access

**D**irect memory access (DMA) was one of the business computer buzz words of the late 1970s. It is really a very simple concept. Any technique of transferring data between peripheral ports and memory without the intervention of a microprocessor can be termed DMA. There are, however, some standard DMA scenarios which form a more common restricted definition of the term.

A typical DMA configuration is that used in the IBM PC. The 8088 microprocessor and the 8257 DMA controller work together to allow double density (MFM) disk transfers, although the processor is not capable of handling the data at the required speed by itself. This highlights the main purpose of DMA — increasing system throughput.

The PC, however, only uses the very simplest implementation of DMA. Some more sophisticated alternatives can do a whole lot more than save you time. I will look briefly at some of these alternatives in due course but first let us consider the time-saving use of a basic DMA controller.

A DMA controller (Fig. 1) consists in principle of an address generator, a data holding register and a control bus via which the controller communicates with the microprocessor.

During normal system operation, the microprocessor puts out addresses onto the address bus and captures the data released by the program ROM. The data is interpreted, causing new addresses to be put out together with output or capture of data. So, the sequence of operations required to move one byte from a port into memory goes something like this:

- 1) put out next address
- 2) when address stable, put out read strobe
- 3) interpret incoming data (read port op code & parms)
- 4) put out address of port
- 5) when address stable, put out read strobe
- 6) put out write address
- 7) when address stable, put out write strobe
- 8) put out next address

This is a narrative of the 8086 MOV instruction which performs a read/write byte transfer in one operation. Other processors (6502 and so forth) need another op-code fetch between stages 5 and 6 as the read and write operations are separate. This means you have to duplicate 1-3 between 5 and 6 making an 11-stage sequence.

The minimum requirement for reading and writing memory is actually much simpler than this. All you really need is:

- set up read address
- output read strobe
- set up write address
- output write strobe.

When you consider that the microprocessor will normally take one clock cycle per stage and that the clock cycle is usually about four times as long as the

minimum memory read or write time, it becomes clear that a great deal of time can be saved by a method of data transfer that bypasses the microprocessor.

### The DMA Process

To perform DMA, the controller has to take over the address, data and control buses normally driven by the microprocessor. There are two considerations here:

- how control is transferred
- what the microprocessor does during a DMA cycle.

The first depends on the microprocessor. Certain CPUs have a built-in DMA capability by means of tri-state switching of the address and data buses. These include the Intel 8080 and 8086 and the newish Rockwell 65C102 and 65C112. Of these, the Intel processors have a dedicated DMA controller which has a specialised interaction with the CPU, whereas the Rockwell components have a capability and control bus, but you are expected to provide your own DMA mechanism.

Note that even early CPUs without a DMA capability built-in can be implemented to allow DMA by the addition of external components.

The second consideration, what the CPU does during a DMA cycle, depends very much on what result you want as well as the type of DMA interface available on the CPU. There are two main protocols for DMA:

- single byte transfers interleaved with normal CPU activity
- ultra-fast block transfers while the CPU is either held inactive, or (as in the Transputers) while the CPU directs its attention elsewhere.

We will now look at DMA applications, which will demonstrate the pros and cons of the different protocols for various jobs.

### The Uses Of DMA


The simplest case, mentioned earlier, is the use of DMA to perform data transfers between memory and peripherals which are too fast for the CPU to handle. The usual given example is disk data transfer.

The original IBM PC used an 8088 processor running at 4.77MHz. This roughly equates to a 1MHz 6502 in throughput. The double density (MFM) data transfer rate is one byte every 32µs and, given the length of code needed to transfer the data as required by MS-DOS (which includes the termination of transfer *immediately* the last wanted byte has been handled) the CPU is just too slow for the job.

However, we are not worried about the actual time the data transfer takes so we just halt the CPU, pass the bus to the DMA controller and transfer a complete disk sector before returning control to the CPU.

The other uses of DMA which follow are all a little hypothetical but they are worthy of mention.

The first provides the ability to run programs of enormous size in small memory maps. It has actually been implemented on the Transputers. Here the task consists of repetitive overlaying of routines into either

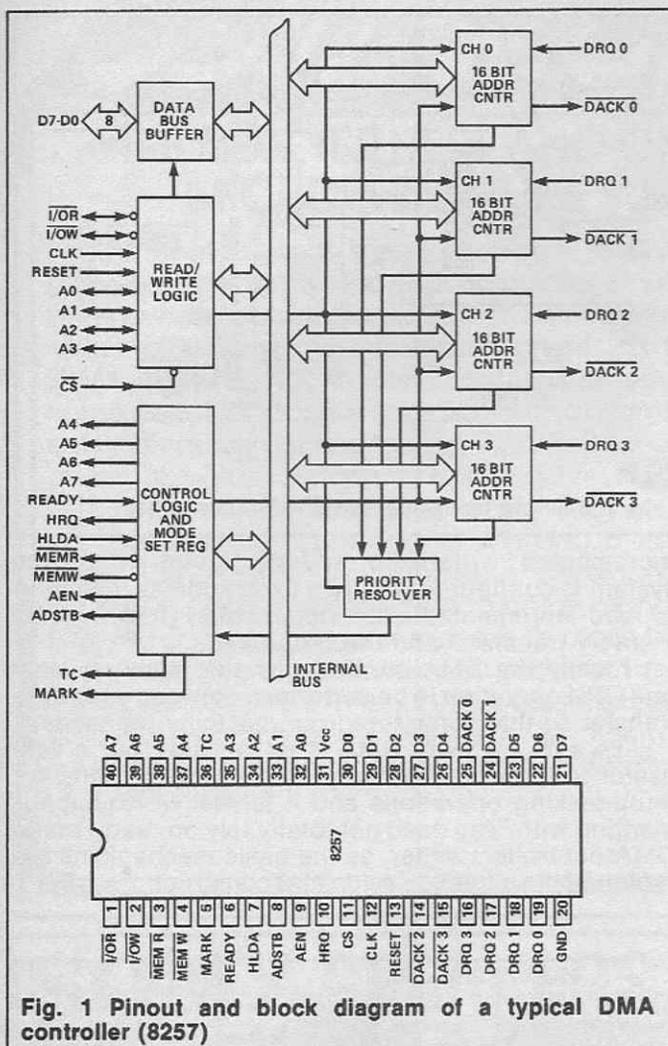

**Fig. 1 Pinout and block diagram of a typical DMA controller (8257)**

buffer. Let's take the slow case. Let us suppose it takes about two seconds to capture the required data (typical of, for example, a heating or cooling curve derived by a thermocouple sensor). Let us also suppose we need a spectrum analysis of the data. We put the data through a fast fourier transform which, being highly iterative, takes about a couple of seconds to run. The simplest case would be to run an acquisition sequence (2s) then enter the FFT routine (another 2s) resulting in a system which can update once every four seconds.

However, we can be crafty and double the throughput by taking advantage of the ADC-FIFO DMA. If we cause (by hardware design) the FIFO to be loaded every acquisition by the end-of-conversion signal from the ADC until the FIFO is full and cause the FIFO to generate a maskable interrupt as soon as it is full, we have the required hardware so long as the interrupt remains active until acknowledged by the CPU.

The system software will need a null wait loop at the end of its run (after it has done the FFT and display handling), an instruction to start the acquisition system hardware running and control over the interrupt mask.

The operation will go something like this:

- first time round, there is no data to work on, so the software starts the acquisition system, unmask the interrupt and enters the null wait loop.
- on interrupt, the software unloads the FIFO into mapped memory, masks the interrupt, restarts the acquisition hardware then continues with the FFT and display.
- as soon as the FFT and display are done, the software unmask the interrupt and enters the null wait loop.

If you follow this through, you will find the system is a self-prioritising truly concurrent dual process. That means both operations (calculation and data capture) are going on simultaneously and whichever finishes first waits for the other. Let's prove it:

Suppose the data capture finishes before calculation and display (C&D) software. The interrupt is generated but the interrupt mask is active, so the interrupt is postponed until the mask is cleared — as soon as the C&D finishes.

Now suppose the C&D finishes before the data capture. The interrupt mask is cleared and the C&D enters the null wait loop. Some time later, the interrupt is generated and is immediately acted upon as the mask is already clear.

## The Hardware For DMA

As previously mentioned, many modern microprocessors have inbuilt capacity for DMA either by dedicated DMA controller or by a control bus for independent implementation. Even the humble 6502 can be configured for DMA. Here is what you do . . .

The only realistic action the 6502 can take during a DMA cycle is . . . nothing. Due to the pipelined architecture of the 6502, the bus is active during most processor cycles. There are therefore practically no 'bus idle' cycles to steal.

The 6502 can be stopped during any READ cycle by assertion of the RDY line. However, this could cause the processor to stop during the execution of an operation, as all operations take several clock cycles. The saving grace is an output from the 6502 called SYNC. This signal is high (logic 1) during the whole clock cycle in which an op-code is being fetched from memory. Assertion of RDY while SYNC is active causes the processor to stop with the address bus pointing to the op-code to be fetched until RDY is released, when it commences the fetch and continues. No status, flags or parameters are lost by the process.

a buffer or an execution area, concurrently with ongoing execution.

There will obviously be some execution speed degradation due to the DMA unless some execution space is 'privatised' but the software will appear to run continuously, rather than in bursts (as occurs when overlaying and execution are alternated).

In the case of the Transputer there is just such a 'private' memory. There is a RAM between the processor and the expansion bus. This bus is the point at which the transfer of control takes place when entering DMA so during DMA to memory beyond the bus interface, processor execution can continue on the 'internal' RAM.

This is the most efficient format. Unless the execution time of the code in the internal memory is shorter than the DMA transfer time, the DMA is invisible. If you want to perform additional overlays, the code transferred under DMA will have to be copied into the private memory, which will waste time. However, supposing the DMA is transferring data for use by a highly iterative *math* routine, the system becomes very efficient indeed.

The next case is that of a data acquisition system. DMA is still DMA even where no microprocessor has direct access to the memory. A typical example is that of a very *slow* data capture system (or an extremely *fast* one) where, for example, an analogue to digital converter generates a stream of bytes and puts them directly into one of our hardware FIFO memories.

There is no direct bus link between the ADC and the CPU bus but the data can get through via the FIFO

If the address, data and control buses are passed through buffers such as 74LS244 (74LS541 is a newer and more convenient alternative) and the DMA controller controls them and RDY and monitors SYNC and READ/WRITE, the DMA controller can at any time halt the processor and take over the bus, along with all memory and peripherals attached to it.

The newer Rockwell 65C102 and 65112 have the buffers built in and also have a couple of minor differences. First, both read and write cycles can be held by RDY and secondly, there is an additional output called ML or memory lock which goes active during the modify and write cycles of read-modify-write operations such as INCREMENT, ROTATE and SHIFT. This means you can hold and DMA at any time except during an RMW instruction, rather than waiting for the next op-code fetch.

As to the DMA controller itself, it typically consists of a counter as large as the memory map (a 16-bit counter for a 64K map) which increments at a rate suitable to the speed of the memory after a start trigger, a comparator to stop the counter when the end of the block has been reached, one or two fixed address registers for device addresses, a read/write data register and some control signals and flags. These consist of a minimum of: write strobe, read strobe and end of block flag although there may be others as well depending on the implementation. These are all fitted together as in Fig. 2.

The counter is loaded with the start address of the block to be transferred, the comparator is loaded with the end of block, the controller is programmed to read-fixed write-incremented address or to read-

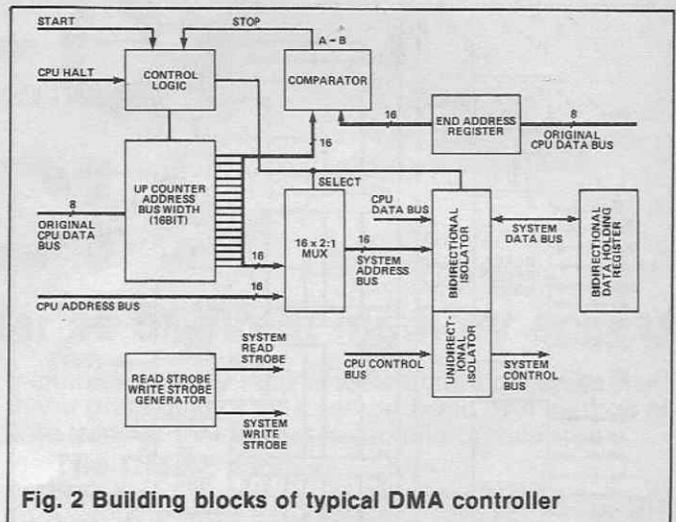


Fig. 2 Building blocks of typical DMA controller

incremented write-fixed address mode or (if the system is configured with two fixed address registers) to read-incremented write-incremented (for memory-memory transfers) and then triggered.

Ideally the DMA controller should allow at least one CPU operation to be performed between each byte transfer so that some foreground activity proceeds.

To sum up then, DMA is no mystery but a very useful tool for improving system throughput and for multi-tasking operations and it is well worth experimenting with. You need not totally rely on ready-made DMA controllers either, as the basic mechanisms are remarkably simple to design and construct. **ETI**

## CRICKLEWOOD ELECTRONICS LTD

WRITE OR PHONE NOW FOR OUR FREE, 1987/1988

PINK COMPONENTS CATALOGUE



HUNDREDS OF LOWER PRICES  
HUNDREDS OF NEW DEVICES

from the U.K.'s number one 100% components shop - no gimmicks, no gadgets, no computers, just millions of components, all easily available by mail order, calling at shop, or credit card telephone orders. Just pick up, or a pen, to get the catalogue (no SAE required) - posted FREE to any country on the globe.

**CRICKLEWOOD ELECTRONICS LIMITED**  
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET  
Tel: 01 450 0995 & 01 452 0161 Telex: 914977



### OSCILLOSCOPES

TELEQUIPMENT DB3 Dual Trace 50MHz Delay Sweep Large Tube £350  
S.E. LABS SM111 Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display with Manual £150  
TELEQUIPMENT 061 Dual Trace 10MHz with Manual £150  
TELEQUIPMENT S54A Single Trace 10MHz Solid State with Manual £90  
GOULD/ADVANCE OS255 Dual Trace 15MHz £225 with Manual  
HAMEG 207 Single Trace 8MHz. With Manual... £50

### MULTIMETERS

AVO 8 Complete with Batteries & Leads from £45  
AVO 8 MVV Complete with batteries Leads & Case £90  
AVO TEST SET No. 1 (Military version of AVO 8) Complete with Batteries Leads & case £85  
TEST LEADS suitable for AVO METERS Red & Black with 2 croc-clips & 2 prods (p&p £2) £5  
AVO Model 7x Complete with Batteries. Leads & carrying case £40  
AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads £18  
AVO - 72 Similar to above but no AC current range. With batteries & leads £10  
ANALOGUE POCKET MULTIMETERS Philips & Taylor etc. With Batteries & Leads from £10

### COMMUNICATION RECEIVERS

RACAL RA17 500MHz with Manual only £150  
LABGEAR Colour Bar Generator KG1. 8 Test Patterns. (P&P £4) ONLY £40 each

### AVO TRANSISTOR TESTER TT169

Handheld GO/NOGO for in-situ Testing. Complete with Batteries Leads & instructions (P&P £3) unused £12 each

### ISOLATING TRANSFORMERS 240V INPUT

240V Out 500VA £15 (p&p £5) 100VA £6 (p&p £2)  
24V Out 500VA £6 (p&p £5) 200VA £4 (p&p £4)

### STEPPING MOTORS

Type 1 200 Steps per rev. 4 Phase (5 wire) 12 24V Torque 25oz inch will run on 5V with reduced torque £15.00  
Type 2 6/12 Steps per rev. 3 Phase. 12/24V (will work on 5V) £2 each 5 off £7.50  
Type 3 NORTH AMERICAN PHILIPS 24. Steps per rev. 4 wire 5V 3.3Amps 0.250rpm 0.200 PPs £6 each  
Type 4 200 Steps per rev. 120V (3 wire) Torque 25oz inch £4 each  
Type 7 WARNER 24 Steps per rev. 3 Phase (6 wire) 28V. Holding Torque 45oz. inch £5 each

Used equipment - with 30 days guarantee. Manuals supplied if possible.  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone or Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.



**STEWART OF READING**

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041 Callers welcome 9am - 5.30 pm Mon - Fri. (until 8 pm Thurs.)

### SPECIAL OFFERS

COSSOR OSCILLOSCOPE CDU150. Dual Trace 35MHz Delay Sweep. Dual State Portable 8x10cm Display With Manual NOW ONLY £180 each  
Optional Front Protection Cover. Containing 2 Probes & Viewing Hood £10  
SOLARTRON OSCILLOSCOPE CD1400 Dual Beam 15MHz With Manual ONLY £85 each  
AVO VALVE TESTER CT160 Suitcase style. 22 Bases ONLY £25 each (p&p £7)  
DISK DRIVE PSU 240V 1N-5V 1.6A & 12V 1.5A out Size W125mm. H75mm. D180mm. Cased Un-used only £10 p&p £27  
QUERTY KEYBOARD (as in LYNX MICRO) just to make Cased £5 each (p&p £2)  
SWITCHED MODE PSU +/-12V 0.25A-5V 15A etc. £12 each (p&p £3)  
OTHER SWITCHED MODE PSU available. Please enquire.  
DISK DRIVES 5¼" - Double Sided. Double Density. 80 track From £50  
MARCONI AF Power Meter TF893A 20Hz-35KHz. 20uW-10W. With Manual (p&p £7) only £35  
MARCONI RF Power Meter TF1152A/1 DC-500MHz. 0.5 to 25 watts 50ohm. With Manual (p&p £7) only £45  
MARCONI AM/FM Sig Gen TF1066B 10-470MHz £250  
MARCONI AM/FM Sig Gen. TF995 range from £150  
FARNELL SINE/SQUARE type LFM2 1Hz-1MHz Compact £80  
ADVANCE SG628 AM 150KHz-220MHz £80

### NEW EQUIPMENT


HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester £583  
HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester & 2 Probes £314  
All Other Models Available.

BLACK STAR FREQUENCY COUNTERS P&P £4  
Meteor 100-100MHz £99  
Meteor 500-800MHz £126  
Meteor 1000-1GHz £175  
BLACK STAR JUPITOR 500 FUNCTION GENERATOR Sine/Square/Triangle 0.1Hz-500KHz. P&P £4 £110  
BLACK STAR ORION. PAL TV/VIDEO COLOUR PATTERN GENERATOR £199  
HUNG CHANG DMM 7030. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with batteries & leads. P&P £4 £39.50  
As above OMM 6010. 0.25% £33.50  
OSCILLOSCOPES PROBES. Switched x1: x10 P&P £2 £11

# SURFACE MOUNT
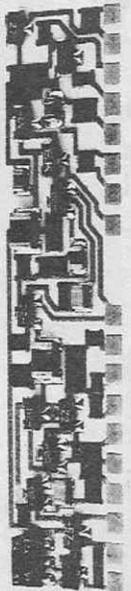
## IT'S NEW, IT'S HERE AND ONLY AVAILABLE THROUGH ETI MICRO MINIATURE SURFACE MOUNT PROJECTS

You've heard about them, probably seen and marvelled at them inside your calculator or watch and now you can begin using them with the latest range of surface mounted component kits from **SUMA DESIGNS**. All the kits are of well proven, in-house design and come complete with all components individually packed for easy identification, high quality fibreglass, surface mount, solder resist P.C.B., full assembly and circuit instructions. All you need is a pair of tweezers, a fine-tipped iron and a steady hand. Using assembly techniques developed to cope with our own prototype and batch manufacture you can be assured of success. To make things even easier we have developed a custom made component jig which although not essential greatly simplifies assembly and is well worth the investment. A full range of SM components are also stocked for your own projects.



- SM20: SOUND TRIGGERED SWITCH: Triggers from slightest sound, L.E.D. indication, variable sensitivity. £13.95
- SM21: DIGITAL DICE: Touch control, roll down speed SM L.E.D. readout. £15.95
- SM22: VHF FM TRANSMITTER: Complete with mic, tuneable over 88-108 band. £12.95
- SM23: LIVE WIRE DETECTOR: Non-contact indication of live wires, blown fuses etc. £9.95
- SM24: VHF FM BLEEPER: Transmits constant beep to nearby FM radio, tuneable. £13.95
- CHJ22: Custom designed assembly jig for speedy and accurate assembly. £6.96

Send 9 x 4 S.A.E. for full details of these and other kits plus all components available. All prices are inclusive but please add £1.50 per order to cover post & packing.



The Workshops  
95, Main Road, Baxterley,  
Near Atherstone,  
Warwickshire, CV9 2LE  
Telephone: 0827-714476

## SONY SPEAKERS

MODEL  
Z-3000  
20 WATT  
2-WAY

made in UK


Size 41.5 x 25 x 17cm approx.  
Impedance 6 ohm nominal.  
Finished in simulated black teak with matching grille.



**£20.95**  
per pair + p&p £3.95

JUST OUT  
1988  
CATALOGUE

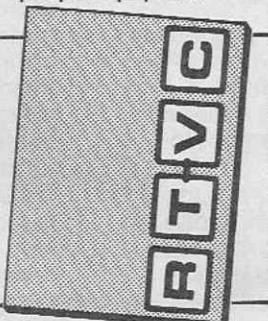Send 50p (cheque or P.O.) and 230 x 325mm s.a.e.



All mail to RTVC, 21 HIGH STREET, ACTON W3 6NG. Callers to Acton or 323 Edgware Rd, London W2. Please allow 14 days delivery.

Payments to RTVC Ltd. Order by Access - tel: 01-992 8430.

### Xen-Electronics

0983  
292847

<p><b>I.C.s</b></p> <p>10V 4w .06 11V 4W .08</p> <p>4001UB .12 4011UB .12 4011 .12 4017 .31 4050 .20 4040 .38 4053 .37 4066 .19 4081 .12 2208CPU 1.85 2208AFIO 1.60 7217PI 4.00 6402PL 7.30 555 .41 558 3.50 741 .25</p> <p>LM339N 1.87 TDA3810 5.96 TL074CP .51 SG3525N 3.69 SG3526J 4.92 SL485DP 2.50 SL485DP 2.13 ML825DP 3.04</p> <p>LM4001 .05 LM4003 .05 LM4005 .05 LM4007 .06 IN5401 .12</p> <p>2N7 4W .05 5V1 4W .06 7Y5 4W .06 5V1 4W .06</p>	<p>BC182 .05 BC212 .05 BC546B .04 BC568A .04 BD243 .42 BF251 .54 BF259 .58 BSR50 .49 IRF520 1.61 IRF840 4.10 J112 .57 MTP2810 1.44 TIP121 .34 TIP126 .34 TIP31C .30 TIP34C .30 2N2846 1.18 2N3055 .47</p> <p>+5V 1A .36 +5V 1.5A .68 +12V 1.5A .38 +15V 1A .36 +24V 1A .60 -5V 1A .38 -12V 1A 2.10 -15V 1A .38 -24V 1A .39 +5V 0.1A .28 +8V 0.1A .28 +12V 0.1A .28 +15V 0.1A .36 -5V 0.1A .30 -12V 0.1A .30 -15V 0.1A .30</p> <p>BC107 .16 BC108 .21 BC109C .19</p>	<p>20 Way .40 22 Way .44 24 Way .48 28 Way .56 40 Way .80</p> <p>Connectors D-Type solder 9 W Sht .43 9 W Plug .38 9 W Cover .58 15 W Sht .60 15 W Plug .53 15 W cover 1.07 25 W Sht .20 25 W Plug .53 25 W cover 1.18</p> <p>I.C. Sockets Low Cost 6 Way .05 8 Way .07 14 Way .11 16 Way .12 18 Way .15 20 Way .16 22 Way .18 24 Way .20 28 Way .23 40 Way .33</p> <p>Turned Pin 6 Way .12 8 Way .16 14 Way .28 16 Way .32 18 Way .36</p>	<p>100,F 16V .06 100,F 25V .07 100,F 35V .08 100,F 50V .19 100,F 63V .21 220,F 10V .06 330,F 16V .19 470,F 16V .25 470,F 50V .40 470,F 63V .63 1000,F 10V .23 1000,F 15V .22 2200,F 16V .46</p> <p>330,F 16V .19 470,F 16V .25 470,F 50V .40 470,F 63V .63 1000,F 10V .23 1000,F 15V .22 47,F 25V .10 100,F 25V .18 470,F 10V .22 1000,F 10V .31</p> <p>15 W Sht 1.02 15 W Plug .39 25 W Plug 2.15</p> <p>Capacitors Radial Lead 3.3nF 400V .08 0.01,F 100V .08 0.022,F 63V .08 0.047,F 100V .08 0.1,F 63V .08 0.15,F 63V .17 0.33,F 63V .33 0.47,F 63V .17 47,F 35V .08 47,F 63V .08 47,F 100V .11 10,F 63V .06 10,F 63V .06 0.25 Watt 5% 1/2 to 10MΩ Each .02</p>	<p>0.5 Watt 5% 100 to 10 MΩ Each .04</p> <p>Terminator Resist (NTC)</p> <p>GM42ZW (4.7KΩ) 1.95</p> <p>Potentiometers PCB Mount Cermet Top Adj</p> <p>100Ω 0.30 1KΩ .30 5KΩ .30 10KΩ .50 20KΩ .50 200KΩ .50</p> <p>Project Kits RS232 to Centronics Converter</p> <p>Kit Only 18.40 200 Based Controller Board, 4MHz Kit Only 20.45</p> <p>Ultrasonic Time-measure Display Module (Extra)</p> <p>Kit Only 23.52 Four Digit LCD-Module for above Kit Only 14.30</p>
--	---	--	---	---

**WHO SAYS WE NEVER GIVE ANYTHING AWAY?**  
AN OFFER WHICH CAN ONLY LAST UNTIL STOCKS ARE EXHAUSTED.

THE ELECTRONIC INDUSTRY TELEPHONE CODE BOOK AND DIARY 1988

Yours absolutely FREE when you next place an order worth £25 or more. Alternatively, you can order the diary on its own at a price of £7.25 zero rated.

**ORDER NOW AND DON'T BE CAUGHT WITHOUT IT!**

Mail or Telephone Orders Only Please To:  
**DEPT 14, SAMUEL WHITES ESTATE,  
BRIDGE ROAD, COWES, ISLE OF WIGHT, PO31 7LP**

Please add £1 for 1st class post and packing, and 15% VAT to total. Stock listing available soon, please send SAE to be put on the mail list

# SPECTRUM CO-PROCESSOR

Graeme Durant describes the first part of a twin Z80 system to boost your Spectrum or just use on its own

**T**he term multiprocessing is a much bandied expression these days. It usually refers to the operation of a number of separate processors working together towards a common goal.

The idea is similar to the old maths problem of how long it takes for different numbers of men to dig a hole. The more men you use, the less time it takes.

In simple computer terms, the time taken to complete a given problem can be reduced by using either a faster machine (the sledgehammer approach) or by using lots of slower machines all working simultaneously on the problem (the 'lots of slower machines all working simultaneously' approach!).

As fast machines are so expensive, the multiprocessing system is a good solution to many problems. Its main disadvantage is the need for communication between the individual processors.


Lots of people working together to write a single book with no communication between them would not produce a well structured novel when the individual parts are put together. The same is true of multiprocessing.

However, communication itself takes time and so the advantage of having more than one processor is best applied to problems where the processing itself can be easily partitioned and movement of data between the processes is not a frequent requirement.
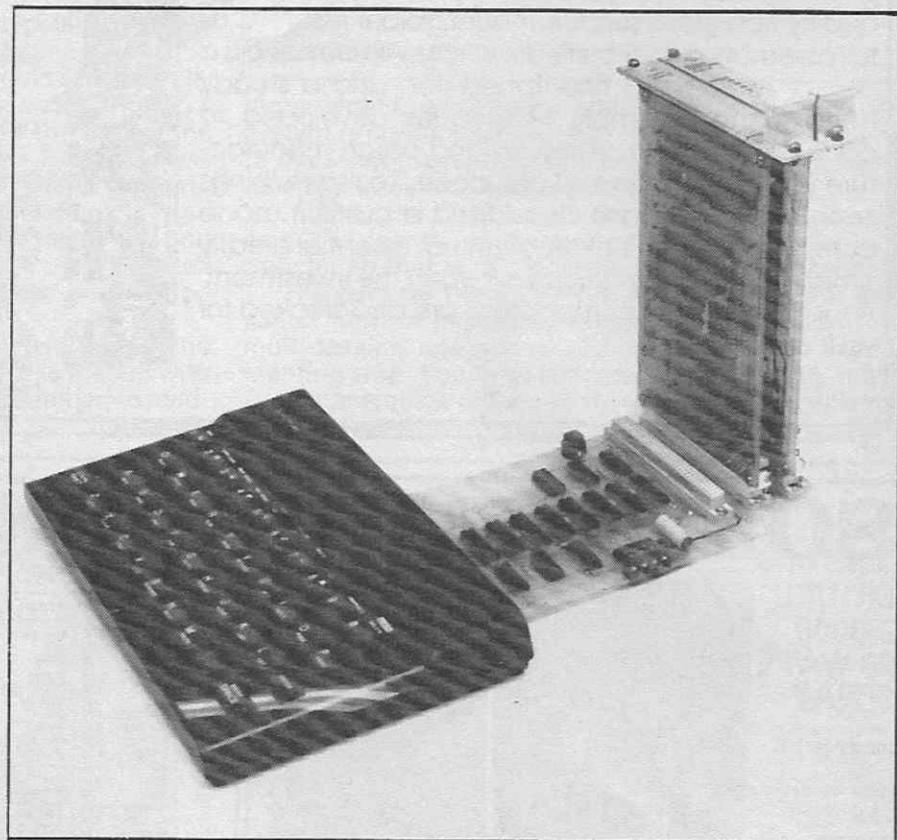
## Co-processing

Co-processing is just one form of multiprocessing. The co-processor itself is just a specialised processor optimised towards some particular task.

A co-processor is designed to be fed information and commands from a master processor (the 'host') and then to go away and get



on with what it is best at while the host does something else. When the co-processor has finished its current task, it will tap the host on the shoulder and the host will exchange data and supply the next command.

On its own, the co-processor can do very little but with a suitable host and sensible allocation of tasks, the result can be a dramatic improvement in overall throughput.

An increasingly common example of co-processing can be seen in the maths co-processor chips, now available to work alongside today's popular microprocessor devices.

These maths chips are designed to perform high-accuracy arithmetic functions very quickly, taking the strain off the

general-purpose microprocessor itself, when number crunching is the order of the day.

Since the maths chip is designed specifically to work alongside a particular microprocessor, interfacing and communication are very straightforward. The main disadvantage of maths co-processors is cost — this usually being well over the hundred pounds mark!

Obviously, such cost cannot be justified when simple machines such as the ZX Spectrum are designed. So most basic home computers do not have the facility to add on a maths co-processor, despite the possible rewards.

Of course, co-processors need not be as dedicated to one function as these maths chips.

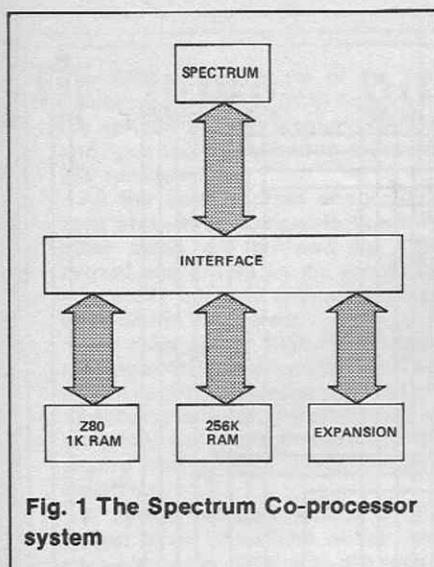


Fig. 1 The Spectrum Co-processor system

Acorn provided the famous 'Tube' interface on the BBC micro designed specifically for communication with a co-processor.

The Acorn co-processors are based on ordinary micro-processors such as the 6502 and the Z80. Jobs usually done solely by the internal processor are shared with the co-processor to speed things up. The result is indeed a speed increase, transparent to the user, but this depends on the machine having been designed from the start with co-processing in mind.

The ridiculously popular ZX Spectrum has been mostly left out of all this co-processing fun. This is mainly because it was never designed for serious expandability and so the designer of a suitable co-processor is forced to start from nothing.


However, there are a great many Spectrums out there — some feeling very lonely and dejected, wanting nothing more than a little companionship. So, here comes the ETI Spectrum Co-processor to the rescue!

### The System

The design to be described here consists of three circuits which together form a fully expandable co-processor (Fig. 1). The heart of the system is a general purpose Z80A based CPU card running at 4MHz with its own operating system software in EPROM.

The second card in the system is a general purpose 256K paged dynamic RAM board. This offers the co-processor a large store area for data or programs.

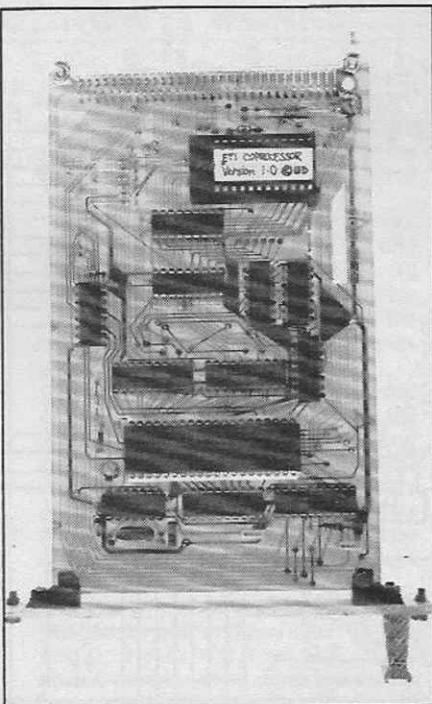The third board in the system is the interface card to the



Spectrum. This consists of a connector for the Spectrum's expansion port, the bi-directional communication circuits and a three position mini-backplane for the co-processor CPU, DRAM and any other circuits the user may wish to add later such as analogue input or output or serial/parallel interfacing to the outside world.

It must be stressed that the CPU card and the DRAM are completely general purpose

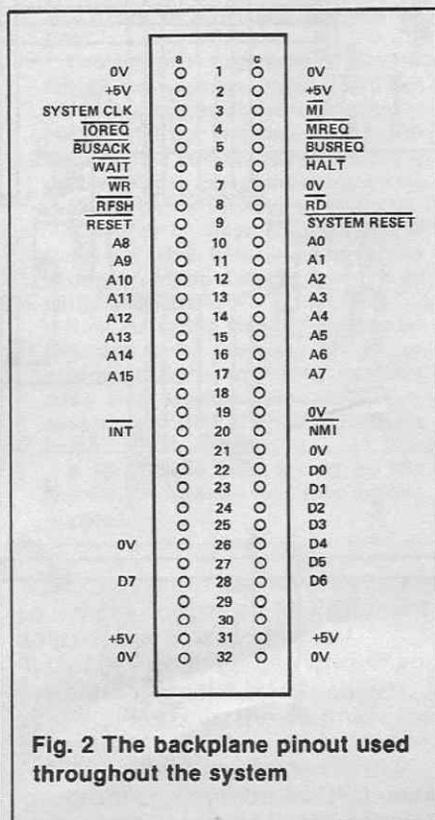


Fig. 2 The backplane pinout used throughout the system

circuits and can equally well be applied individually or together to any Z80 based system.

This co-processor design is simply one possible application for their use.

### Software

These days, a chunk of hardware, no matter how sophisticated, is useless without its associated software. The Spectrum co-processor is no exception.

The CPU card has provision for a 4K EPROM and in this application the machine code residing there provides the basic functions required to make the co-processor operate.

The co-processor can respond to five different commands when controlled by the Spectrum. Code or data may be moved from the Spectrum and into the co-processor memory (block write), code or data may be moved from the co-processor memory and into the Spectrum (block read) and user code may be executed in the co-processor (code execute).

Executing code may be stopped by the Spectrum (break), and finally, the co-processor can be commanded to run a self test routine which reports on how much DRAM is present and the state of the EPROM and RAM on the CPU card.

There is also the facility to extend the number of commands to include new user defined functions but that must wait until later.

### Why Co-process?

So what advantages are gained by spending all your hard earned cash on a companion to your neglected old Spectrum?

First the bad news. Since the venerable Spectrum was never intended for such serious expansion, there are major limitations on the performance improvements possible. However, put to appropriate use, this co-processor will offer enhanced processing speed over the Spectrum alone.


The Spectrum also provides a superb low-cost base for experimentation and, coupled with this project, offers a great way to learn first hand about multiprocessing environments.

Over and above the obvious speed advantages, there are also a number of important things to be gained by having a pool of processing power detached from the Spectrum, yet under its

BACKPLANE PCB  
CONNECTOR SKT

20c NMI  
20a INT  
6c HALT  
6a WAIT  
5c BUSREQ  
31b,e +5V  
32a,c GND

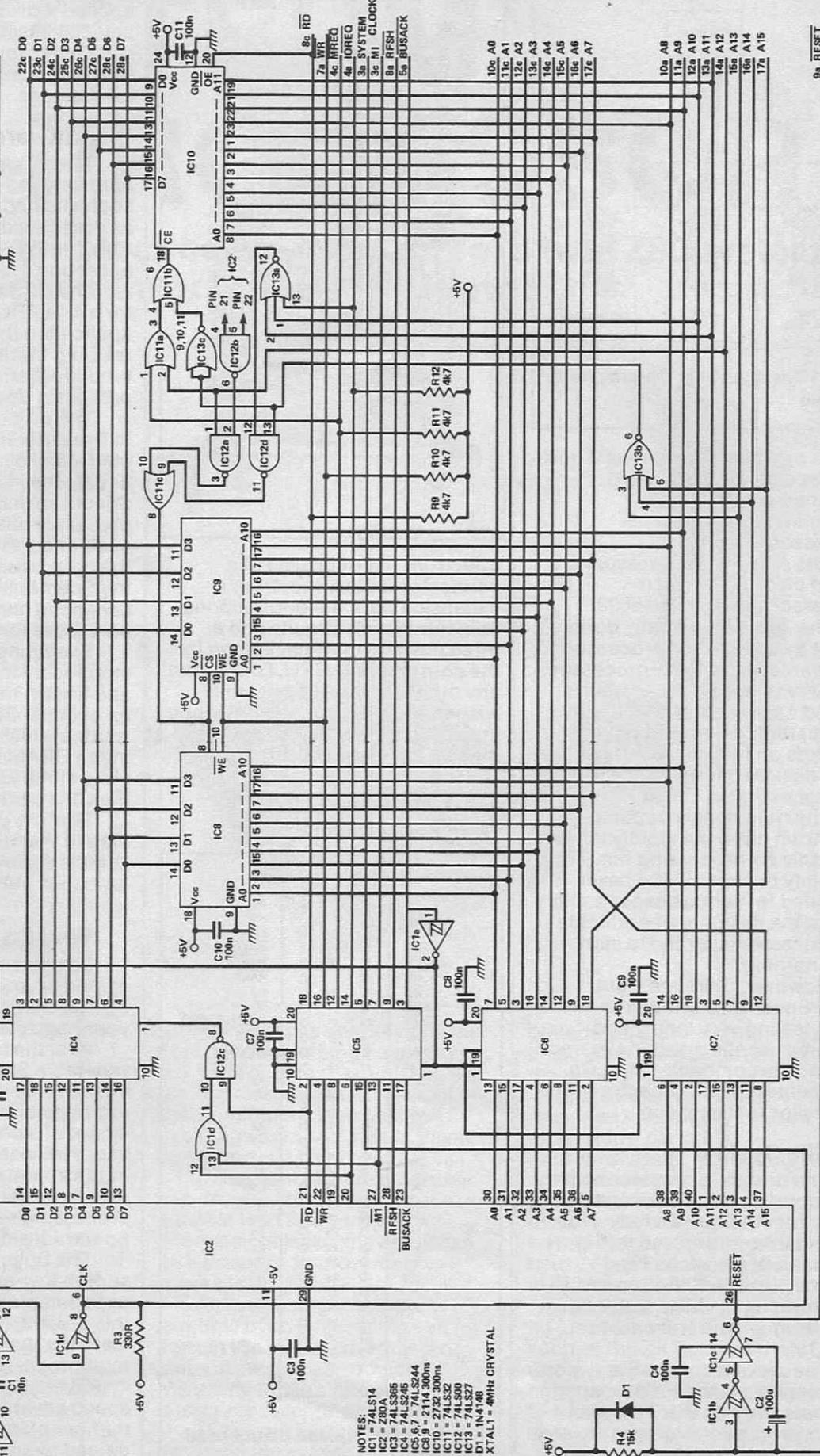+5V O  
TO CIRCUIT  
C14 100n  
C13 100n  
C12 100u



9a RESET  
9c SYSTEM  
RESET

NOTES:  
IC1 = 74LS14  
IC2 = 280A  
IC3 = 74LS245  
IC4 = 74LS245  
IC5,6,7 = 74LS244  
IC8,9 = 2114 300ns  
IC10 = 2732 300ns  
IC11 = 74LS32  
IC12 = 74LS20  
IC13 = 74LS27  
D1 = 1N4148  
XTAL1 = 4MHz CRYSTAL

Fig. 3 The circuit diagram of the co-processor CPU board

# PROJECT: Spectrum Co-processor

## HOW IT WORKS

The CPU card consists of the Z80 microprocessor itself (IC2) along with the various buffers, memory devices and 'glue logic' required to make the Z80 run software.

All the data, address and control lines which allow communication with other cards are buffered by high current line drivers so the processor may easily interface with many other cards within the system.

The main system high-speed clock running at 4MHz is generated by a TTL crystal oscillator based around IC1e,f. After being buffered, this drives pin 6 of the Z80A, with pull-up resistor R3 to ensure the correct clock voltage transitions.

A further buffered version of the system clock is available at the card edge-connector (SK1) with IC5 acting as the bus driver. This signal is available at all times, since other devices in the system may require the clock signal even when the Z80 itself is disabled.

Two more inverters from IC1 are used to generate the Z80 reset signal. A brief power-up reset pulse is generated by C2 and R4, which acts on IC2 pin 26 via IC1b,c. Diode D1 ensures a reliable reset occurs even when the power is only briefly removed. Alternatively, a reset operation may be initiated by an external device by it pulling low the SYSTEM RESET line on the card connector.

IC3 and IC5 buffer control signals to and from the card connector. IC4 is a bidirectional buffer used to drive the system data bus from the Z80. IC6 and IC7 are unidirectional buffers which drive the address bus from the Z80.

IC4, IC6, IC7 and half of IC5 have their output enable controls wired together and driven by an inverter IC1a. This in turn is driven by the BUSACK signal from the Z80. This disables the data bus, address bus and some of the control lines when an external bus request is granted.

For example, if another processor or a DMA controller sharing the same buses requires use of these buses, it sends an active low signal on the BUSREQ line to the Z80. When ready to release its buses to the requester, the Z80 sends a BUSACK strobe and tristates its own buses. So the buffers must do the same, via IC1a.

When the external bus user has completed its operations, it releases BUSREQ and the Z80 removes BUSACK in response. The buses are then re-enabled and the Z80 can resume its own operations.

In addition to those signals which must be tristated during external bus activity, there are several control signals which need not, and in some cases must not, be disabled at such times.

The system clock, M1, RFSH, BUSACK, NMI, INT, HALT, WAIT and BUSREQ are all left active, even during DMA cycles. So, the buffers which pass these particular signals, IC3 and the other half of IC5, have their outputs permanently enabled.

Pull-up resistors R5-8 are provided on the four signals which enter the processor card via IC3. These four inputs, NMI, INT, WAIT and BUSREQ require such treatment to ensure reliable operation if no signals drive these lines from outside or in the case of a 'wired-OR' connection from more than one peripheral.

Similarly, pull-up resistors R9-12 are fitted to the output signal lines RD, WR, MREQ and IOREQ from IC5. These ensure no erroneous active low pulses can occur as the buffer is disabled via IC1a, during DMA operation.

IC4, the bi-directional buffer which controls the system data bus, must receive a signal pin 1 to determine the direction of data flow — either into or out of the card.

This signal, generated by IC11d and IC12c, depends on two conditions. First and most important, the active RD strobe from the Z80 pulls IC4 pin 1 high via IC12c allowing data flow into the Z80 during read cycles. Second, when the Z80 IOREQ strobe (pin 20) and the Z80 M1 signal (pin 27) go low simultaneously, again the direction control pin of IC4 is pulled high, via both IC11d and IC12d, to allow data flow into the Z80.

This happens only when a Z80 interrupt acknowledge cycle occurs and allows the external interrupt source to put an interrupt response vector onto the Z80 data bus if required. For more details refer to one of the many books available on the operation of the Z80.

If neither of these conditions is in force, IC4 drives data out of the card to allow for wiring data to memory or peripherals.

Now, on to the memory devices on this card: When reset, the Z80 microprocessor starts executing program code from address zero (the processor's operating program must begin here).

A 4K EPROM, IC10, is mapped into the first 4K address locations for this purpose.

The next 1K locations up from the EPROM are inhabited by static RAM, intended for use as a general scratch-pad workspace. This is shown on the circuit as IC8 and IC9, each 1K x 4-bit device covering half of the data word width.

Both the EPROM and the static RAM are available at all times to the processor. The mapping of these memories is performed by the logic gates in IC11-13 driving the chip select pins of IC8 and IC9 (pin 8) and of IC10 (pin 18).

These signals are active low when the Z80 addresses a location within the device's allocated range. The write enable inputs of the RAM chips, pin 10 of IC8 and IC9, are driven directly by the Z80 WR strobe. Similarly, the output enable pin of IC10, pin 20, is driven from the Z80 RD strobe. The result is that reading an address between zero and 4K will access the EPROM and reading or writing to an address between 4K and 5K will access the scratchpad RAM.

Any further memory in the system (such as the 256K dynamic RAM card) should be mapped into the rest of the Z80's available address space, this being between addresses of 5K and 64K to avoid contention with the on-board memories.

It is worthwhile noting that the data and address lines to the static RAM devices are not connected here in the same order as described in the manufacturer's data sheet.

This serves to ease the printed circuit layout and does not make any difference to circuit operation so long as a data signal goes to a data pin and an address signal goes to an address pin on the RAM chips. Every unique address location in the RAM is the same and data can be stored there regardless of its value.

The same is not true of the EPROM, which is programmed externally by sticking to the standard manufacturer's pin allocations, so these same pin designations must be (and are) used here.

Finally, a note about supply decoupling. Low value decoupling capacitors are liberally scattered about the circuit to avoid problems with supply and ground noise. A high value electrolytic capacitor (C12) is placed very close to the backplane power connections to provide bulk energy storage and helps to avoid the problems associated with remotely controlled power supplies.

control.

For example, if an application has very critical timing associated with it — say, audio sampling — then the various interrupts already present in the Spectrum can upset operation. Using the co-processor can avoid this problem.

Furthermore, a co-processor offers a great opportunity for the

user to develop low-level software in a more controlled environment than on the Spectrum itself. Assembly code can be written and assembled on the co-processor, downloaded into the co-processor memory and then executed there.

Input data can be fed to the program and output data examined. If some kind of endless

loop is entered then execution can be stopped by the Spectrum.

Every time user code stops execution, either naturally or via a Break command, all the co-processor Z80 registers are copied into a reserved area in its memory and these can be subsequently examined to aid de-bugging.

Although the co-processor's

operating software in EPROM is completely usable in any desired application, this idea of a 'software development system' seemed so attractive that this project will finish with a complete listing, in ZX Basic, for a menu-driven program to implement such a tool.

This fully commented listing will also serve to illustrate clearly, the ways of passing data to and from the co-processor and how to control its actions afterwards so that any required co-processing application may be realised by the reader.

### The CPU Card

Let's take a closer look at the heart of the co-processor — the CPU card. This card is built on a standard 160 x 100mm Eurocard-sized double-sided PCB and consists of the Z80A CPU itself, 4K EPROM for the operating software, 1K static 'scratchpad' RAM and full buffering for all the control, data and address lines going in and out.

Connections to the other boards are made via DIN41612 connectors and the pinout used throughout this project is shown in Fig. 2.

As stated earlier, this CPU card is strictly general purpose and there is absolutely no reason why it should not be used in any application you care to devise, indeed, the co-processor system could be used to develop software for some final target system which in turn would use the same Z80 card at its heart.

### Construction

The construction of the Z80 processor card is relatively straightforward, particularly if the suggested PCB design is used.

This PCB is double-sided but is not through-hole plated. So, connections between the layers must be added by wire links or by the component leads themselves.

Where a through connection is marked on the PCB layout diagram (Fig. 4) a short length of tinned copper wire should be pushed through the hole and carefully soldered on both sides before cropping to length.

Where a copper pad encircles a passive component lead on the topside of the board, this lead should be used to form a through connection. The lead should be soldered in place from the underside as normal and then soldered on the topside, being careful not to use too much solder.

A large number of through

connections are made via the pins of the ICs themselves (again, a copper pad encircles the IC pin on the topside).

Before the ICs can be fitted, however, there are a small number of through PCB connections and miniature decoupling capacitors which, due to circuit layout constraints, are sited underneath ICs themselves. These must be fitted first. Once these are present, the ICs can be soldered in.

It is strongly recommended that DIL sockets are used for all the ICs on this PCB. Apart from the ease of future repair, sockets rather neatly raise the ICs off the board surface making space for the decoupling capacitors underneath.

The chosen DIL sockets must be capable of being soldered in from the topside as well as from underneath, to form the through connections. This is not as big a problem as might be thought since most 'turned pin' IC sockets leave the base of their pins accessible on the topside of the PCB.

Standard 'sprung contact' DIL sockets rarely offer this feature and so turned pin style sockets are to be preferred.

The trick is to first solder the socket into the PCB from underneath as normal. Then, by heating each pin in turn from underneath with the soldering iron, it will be possible to form a solder joint on the topside by simply dabbing the solder onto the base of the pin. It is advantageous to use fine solder for this operation.

This technique is necessary as the exposed pin bases on the topside are usually too recessed to get a soldering iron to them and you risk melting the plastic socket

frame if you try!

If you envisage writing new code for this processor yourself, it is a good idea to use a zero insertion force (ZIF) socket for the EPROM (IC10). This will reduce the risk of damage to EPROMs with repeated insertion and extraction.

The PCB was designed for a ZIF socket for IC10. The construction of ZIF sockets is such that they rarely provide access to their pins on the topside of the PCB. So, the through connections which would normally be made via the pins of IC10 are made conventionally by separate wire links through the board. This means that any type of 24-pin DIL socket can be used to hold the EPROM — including most available ZIF sockets.

After making all the through PCB connections and fitting the IC sockets, the rest of the components can be added. Note that resistors R1 and R2 should be soldered in on end.


It is suggested that for extra strength, SK1 is bolted to the PCB using short M2.5 bolts and matching nuts.

Finally, after all the components have been fitted, it is a good idea to check for solder splashes which may form short circuits, especially across the closely spaced bus lines.


After this it is always nice to complete the job by removing any remaining traces of flux from the board, using methylated spirits and a stiff brush.
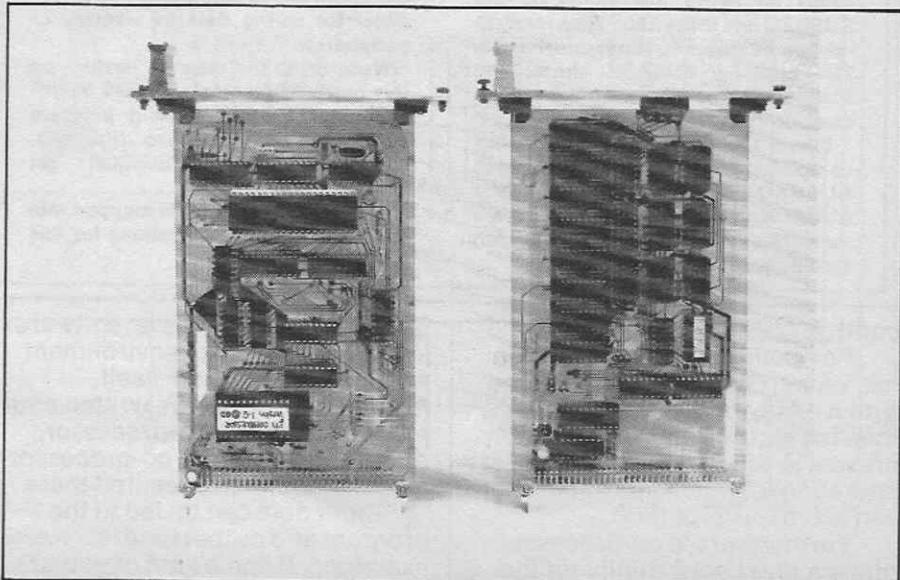
### Testing

Testing the completed CPU card is not easy at this stage. If you intend to build the whole co-processor system, the methods for



# PROJECT: Spectrum Co-processor

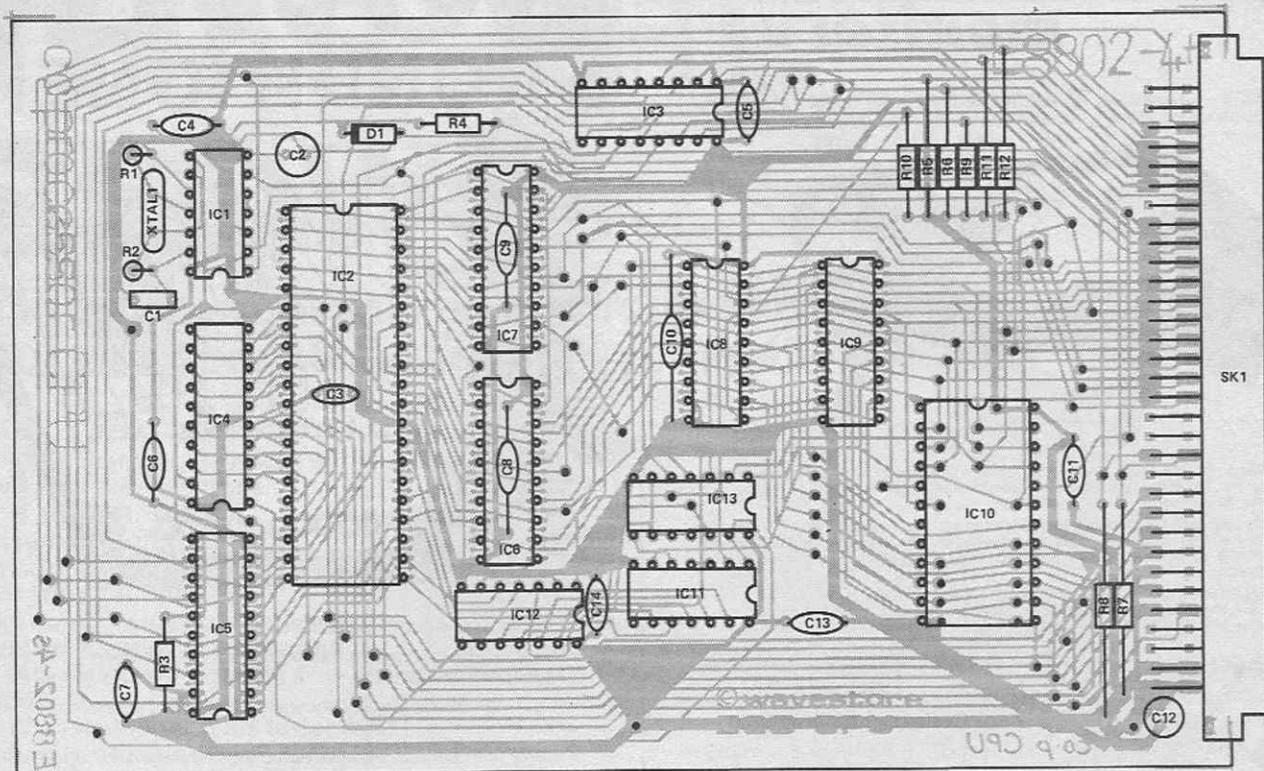

• - THROUGH CONNECTIONS

Fig. 4 The component overlay for the CPU board

## PARTS LIST

### RESISTORS (all 1/4W 5% unless otherwise stated)

R1, 2 1kΩ  
R3 330R  
R4 15k  
R5-12 4k7

### CAPACITORS

C1 10n polyester  
C2, 12 100µ 6V ultramin radial electrolytic  
C3-11, 13, 14 100n monolithic axial ceramic

### SEMICONDUCTORS

IC1 74LS14  
IC2 280A  
IC3 74LS365  
IC4 74LS245  
IC5, 6, 7 74LS244  
IC8, 9 2114 350ns  
IC10 2732 350ns (see Buylines)  
IC11 74LS32  
IC12 74LS00  
IC13 74LS27  
D1 1N4148

### MISCELLANEOUS

SK1 DIN41612C 64-pin right angle PCB mounting plug  
XTAL1 4MHz crystal  
PCB; IC sockets; tinned copper wire for through connections; M2.5 nuts and bolts for DIN connector.

testing all the hardware together will be described later in the series.

However, if the card is destined for your own application then testing must consist of powering up the card, with a suitably programmed EPROM present and simply checking the program runs as expected. If it does not (and there are no dramatic blue flashes) then try running a tight program loop such as a line of code repeatedly jumping to itself and test for activity on the clock, data, address, control and EPROM chip enable lines with a scope.

If all seems fine, try a program

which accesses RAM and look at the signals driving the RAM chips.

Fault finding in complex logic circuitry is at best very tricky and without the correct equipment, almost impossible. Think very carefully about what is going on in the circuit and try to narrow down the fault to an area of the circuitry.

Beyond this, consider investing in a Logic Analyser!

Next month we shall move on to look at the design and construction of the general purpose 256K paged dynamic RAM card which provides the co-processor with storage for large programs and databases. Don't miss it!

ETI

## BUYLINES

Most of the components used on the CPU card are readily available from your usual supplier. The miniature axial ceramic capacitors used throughout this project are available from Vero-speed as order code 92-50952H. Vero-speed can be contacted at Stansted Road, Boyatt Wood, Eastleigh, Hants SO5 4ZY. Tel: (0703) 644555.


The ultramin 100µ radial electrolytic capacitors were obtained from Maplin (order code RK50E) as is the DIN41612 backplane connector (FJ51F). The turned pin IC sockets suitable for use with this PCB are supplied by most component stockists but try Maplin's range if uncertain.

For readers set on typing reams of hex into a programmer, a hex dump of the co-processor operating system EPROM will be printed later in the series. Otherwise, an EPROM pre-programmed with this code, is available from the author, price £10 inclusive of postage. A comprehensively commented assembly listing for this code is also available for £3.50. Please send cheques or postal orders, made payable to the author, to 52 Bishops Court, Trumpington, Cambridge CB2 2NN and allow 28 days for delivery.

Finally, as ever, the printed circuit board is available from our PCB service.
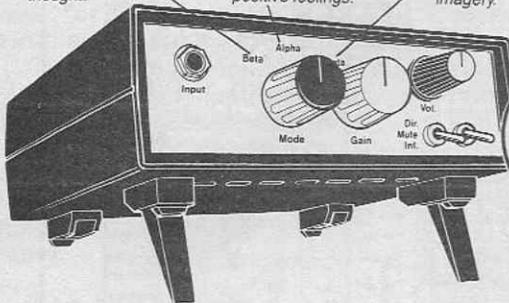
# Brainwave monitor

**B BETA** - Concentration, problem solving, active thought.  
**A ALPHA** - Relaxation, pleasure, tranquility, positive feelings.  
**THETA** - Imagination, creativity, hypnagogic imagery.



**BRAINWAVE MONITOR PARTS SET ONLY**  
**£36.90**  
 + VAT

This unique project will allow you to hear your own brainwaves! Through a simple training program you can learn to control them and achieve peak performance in all situations. It will revolutionise your life!

The approved parts set contains: two PCBs; all components, including three PMI precision amplifiers; shielded box for screening the bio-amplifier; attractive instrument case with tilting feet; controls, switches, knobs, plugs, sockets; leads and brass electrodes; full instructions for assembly and use.

Parts are available separately. We also have a range of accessories, professional electrodes, books, etc. Please send a stamped, self-addressed envelope if you just want the lists. Otherwise, an SAE + £2 will bring you lists, construction details and further information.



## THE ALPHA PLAN

Can you really train your mind to think more effectively? Can you really excel at things you're 'no good at'? The Alpha Plan has all the answers!  
**£2.50** (no VAT)




## SILVER SOLUTION

Just wipe on with a cloth to plate PCB tracks, connectors, wire, component leads, coins or household ornaments with a layer of pure silver. It must be magic!  
**LARGE BOTTLE (150ml) SILVER SOLUTION £11.20 + VAT!**
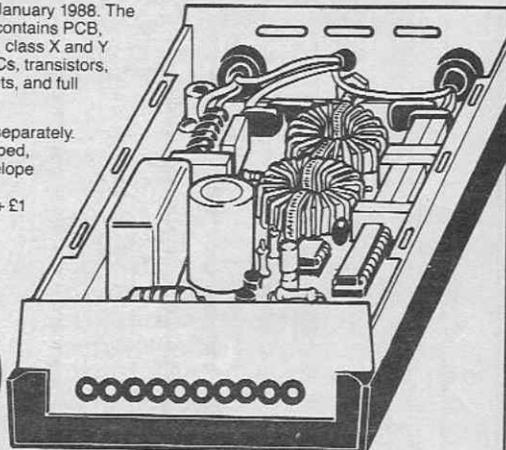
# DOWER CONDITIONER

As featured in ETI, January 1988. The approved parts set contains PCB, case, toroidal cores, class X and Y capacitors, VDRs, ICs, transistors, LEDs, all components, and full instructions.

Parts are available separately. Please send a stamped, self-addressed envelope if you want the lists. Otherwise, an SAE + £1 will bring you lists, construction details and further information.



**POWER CONDITIONER PARTS SET ONLY**  
**£28.50**  
 + VAT

- For those who will only be satisfied with the best
- Use with Hi-Fi, computers, radios, TV sets to eliminate mains-borne interference
- 10 LED logarithmic display shows the amount of interference removed
- Massive filter section with thirteen capacitors and two current-balanced inductors
- Bank of six VDRs to remove transients and spikes
- Suppresses common mode and differential mode interference

# Complete Parts Sets for ETI Projects

## MAINS CONTROLLER

FEATURED IN ETI, JANUARY 1987


Have you ever wondered what people do with all those computer interfaces? Put your computer in control, say the ads. The Spectraebs has eight TTL outputs. What on earth can you control with a TTL output? A torch bulb?

The ETI Mains Controller is a logic to mains interface which allows you to control loads of up to 500W from your computer or logic circuits. An opto-coupler gives isolation of at least 2,500V, so the controller can be connected to experimental circuits, computers and control projects in complete safety. Follow your computer interface with a mains controller and you're really in business with automatic control!

The mains controller connects directly to most TTL families without external components, and can be driven by CMOS with the addition of a transistor and two resistors (supplied).

Your mains controller parts set contains: high quality roller tinned PCB, MOC3021 opto-coupler; power triac with heatsink, mounting hardware and heatsink compound; all components, including snubber components for switching inductive loads; transistor and resistors for CMOS interface; full instructions.

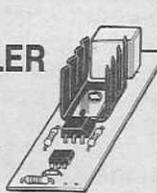**MAINS CONTROLLER PARTS SET £6.20 + VAT!**



## KNIGHT RAIDER

FEATURED IN ETI, JULY 1987

The ultimate in lighting effects for your Lamborghini, Mercedes, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bar, bouncing backwards and forwards along the row. Press again and by one of the other six patterns. An LED display on the control box lets you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent toy) or bicycle into a spectacular TV age toy!

The control box parts set consists of case, switches, LEDs, PCB components, hardware and instructions. The sequence board includes PCB, ICs, power FETs, components, hardware and instructions.

**KNIGHT RAIDER CONTROL BOX ONLY £6.90 + VAT!**

**KNIGHT RAIDER SEQUENCE BOARD ONLY £13.90 + VAT!**

## MATCHBOX AMPLIFIER


FEATURED IN ETI, APRIL 1986

No ordinary amplifiers, these. When our first customers took an interest, it was for the diminutive size (both modules will fit in a matchbox!), the total disregard for power supplies and speaker impedances, and the impressive power output from these little amplifiers. When they re-ordered, it was for the sound quality.

Two amplifier modules were described, both based on the powerful L165V IC. The single IC version will deliver over 20 Watts with a suitable speaker and power supply. The bridge version can provide up to 50W! Although the specified supply voltage and speaker impedance must be used to achieve maximum power, both modules are quite happy to work from any voltage between 12V and 32V, and will accommodate any type of speaker. The bridge version is ideal for giving a boost to car Hi-Fi systems, driving two 4 Ohm speakers in parallel on each channel for best effect.

Both designer-approved parts sets consist of a roller tinned printed circuit board and all components. The L165V ICs are also available individually, with a free mini data sheet giving specifications and suggested circuits.

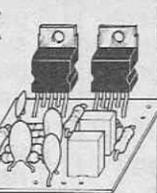**SINGLE IC MATCHBOX AMPLIFIER SET (20W into 4 Ohms) £6.50 + VAT**  
**BRIDGE AMPLIFIER SET (50W into 8 Ohms) £8.90 + VAT**  
**L165V IC, with data, £3.90 + VAT**



## POWERFUL AIR IONISER

FEATURED IN ETI, JULY 1986

Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build... and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs 'about a third of the price of the individual components. What more can we say?'

**DIRECT ION PARTS SET WITH BLACK CASE £11.50 + VAT**  
**WITH WHITE CASE £11.80 + VAT**



## SPECIAL OFFERS

AD7541 Precision 12-bit multiplying DAC £1.20 + VAT  
 LM3524 Switch-mode regulator IC £0.80 + VAT  
 CF585 Calculator IC £1.00 + VAT  
 LM339 Quad comparator IC 3 for £1.00 + VAT  
 MC1458 Dual op-amp 3 for £1.00 + VAT

All ICs supplied with FREE DATA. Prices apply only while stocks last.

## LM2917 EXPERIMENTER SET


Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

**LM2917 Experimenter Set £5.80 + VAT**

## RUGGED PLASTIC CASE

suitable for mains conditioner and mains controller.

**ONLY £1.65 + VAT**

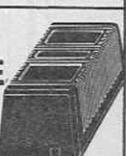

## LEDs


Green rectangular LEDs for bar-graph displays.

50 for £3.50 500 for £25

100 for £6 1000 for £45

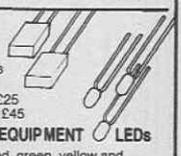**DIGITAL AND AUDIO EQUIPMENT LEDs**

Assorted 3mm LEDs: red, green, yellow and orange. 25 of each (100 LEDs) for **£6.80**



Prices shown are exclusive of VAT, so please add 15% to the order total. UK postage is 70p on any order. Carriage and insurance for overseas orders £4.50. Please allow up to 14 days for delivery.

Specialist SEMICONDUCTORS LIMITED

SALES DEPT  
 ROOM 107  
 FOUNDERS HOUSE  
 REDBROOK  
 MONMOUTH  
 GWENT

# THAR' SHE BLOWS!

Alan Wilcox presents an in-circuit transistor tester that will test your components rather than your patience

**H**ow many hours have you spent testing transistor after transistor in a ponderous search for that monstrous component which has blackened your golden PCB? How often do you wish for a device that could tell a good 'un from a bad 'un with a single prod from a probe?

Wish no longer. This tester will confirm in a single measurement if a diode, transistor or thyristor is OK as well as showing its polarity (PNP/NPN for a transistor and PN/NP for a diode). It is tolerant of in-circuit resistance of the order of 40R across the junctions so you can flit from component to component without once reaching for your soldering iron. There is even a buzzer which sounds whenever a healthy piece of semiconductor is tested.


## The Test

To test a transistor, a 5Hz square wave is applied to the collector-emitter terminals of the device being examined (see Fig. 1). Forward bias is supplied to the base, again with a 5Hz square wave.

The low saturation voltage of a good transistor is taken as the indication of a good device but is differentiated from a short circuit by checking that conduction occurs in one direction only.

If conduction occurs on the positive half-cycle (relative to the emitter) this is interpreted as being a good NPN transistor. Conduction on the other half-cycle would be due to a good PNP device.

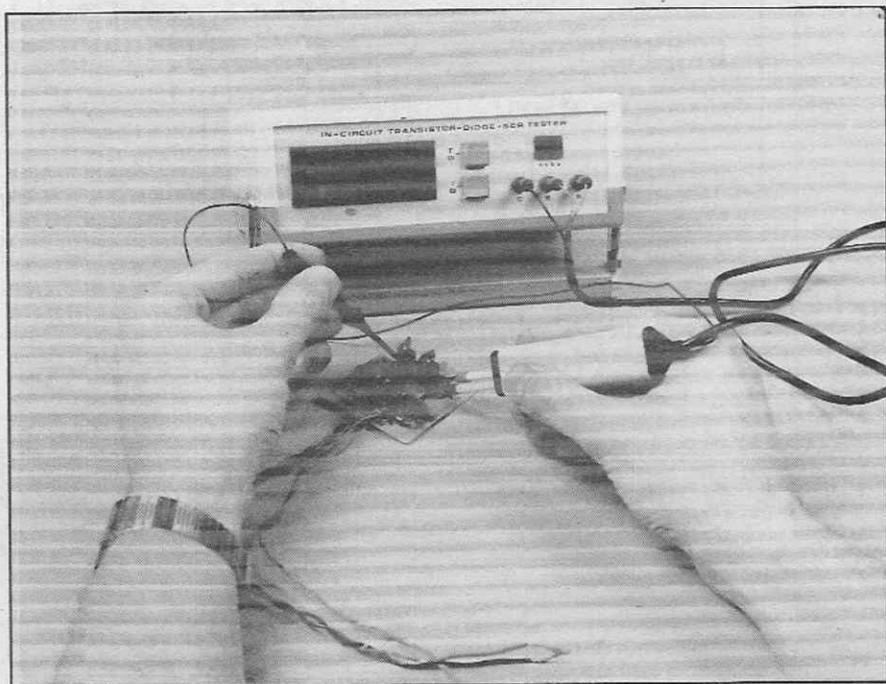The design criterium here is that the collector-emitter voltage must fall below 500mV for a good indication to be given. This ensures the tester ignores any diodes that may be in circuit. This is particularly important in order to detect a collector-base short



which would act as a diode, conducting on one half-cycle only and erroneously indicating a good device.

Diodes, thyristors and Darlington transistors have a forward voltage drop between 500mV and 1V so to test these a separate range is provided. On this range the threshold for a good indication is increased to approximately 1V.

## The Display

A 4-digit LCD is used to show the status of the device under test. The first three 'digits' can show either an **n** or a **p**, and indicate the device type. The first digit is blanked when testing diodes.

The fourth digit shows either a **t** or a **d** to indicate transistor or diode range. It also serves as an 'on' indicator.

Failed devices will give a display of **nnn** on the LCD if the test terminals are short circuited. If they are open circuit, the first three letters of the LCD are blank.


## Construction

The component overlay for the main PCB is shown in Fig. 2. All ICs are CMOS and so the usual precautions against static should be taken. Note that they all face the same way on the board.

All odd numbered transistors are PNP and even numbered are NPN. The presets RV1, RV2 may be replaced by 4M7 fixed resistors with just a small increase in the response time resulting.

Avoid any stress on the LCD display, taking care not to overtighten any fixing nuts. The mounting bezel specified comes complete with two socket strips on a board. These were removed and used on the display PCB (Fig. 3). Take care to observe the polarity of the ribbon cable when connecting the main PCB to the display PCB.

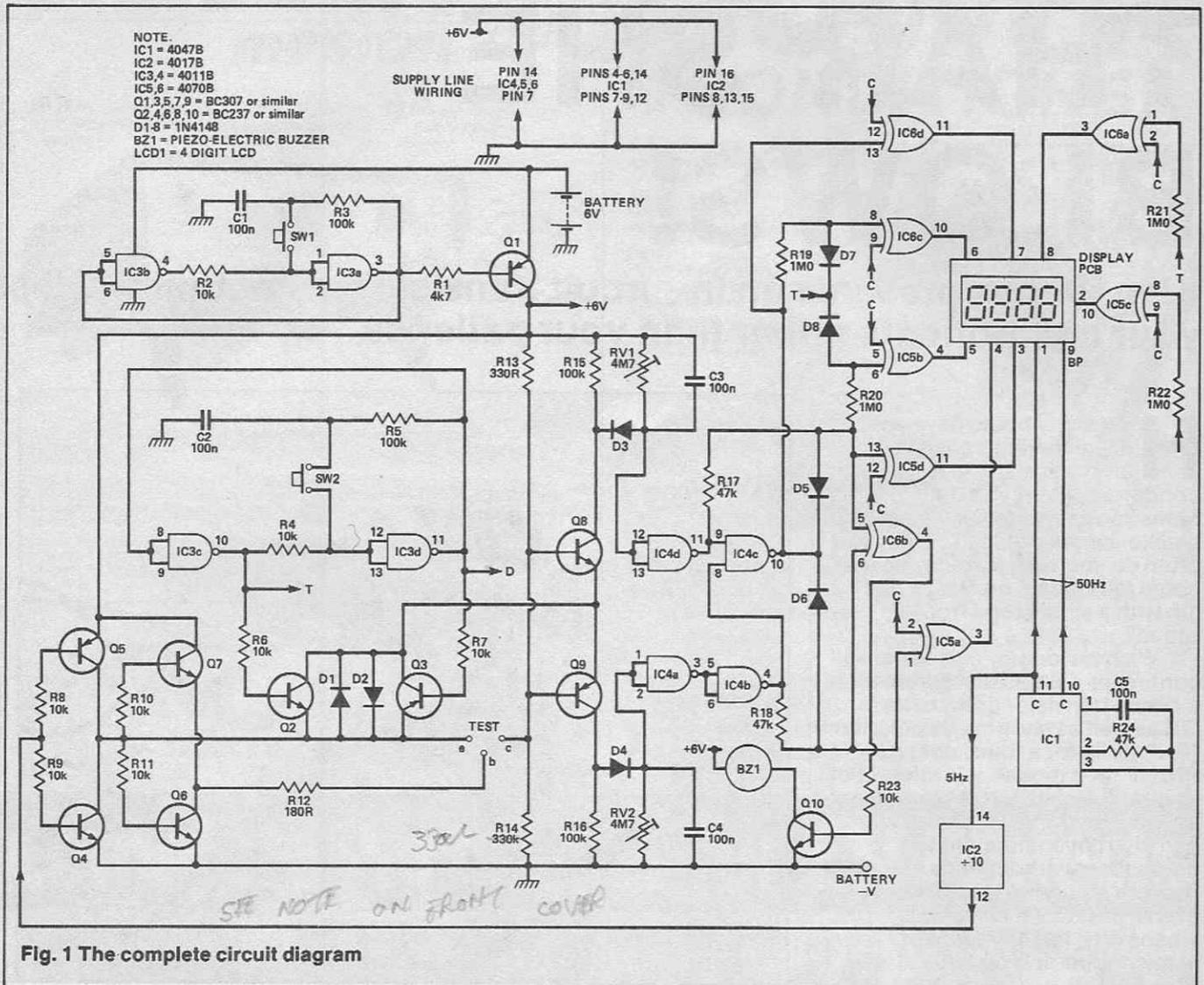Note that the two switches are momentary push to make, similar to a keyboard type. The ones used on the prototype were from the junk box.



### Shock, Horror, Probe


Testing a transistor involves connecting into the circuit at three separate points. Manipulating three individual probes with only two individual hands can be a practical problem. To overcome this, a special collector-emitter test probe was constructed using a small Eveready torch case into which were fitted two short lengths of curtain wire to form the probes. Dart points were filed down to fit tightly into these. The result can be seen in the photograph.

The probe used for the base connection is one commercially available.

In addition to sockets for the circuit probes, a transistor socket was fitted to the front panel of the case to ease the testing of devices out of circuit.
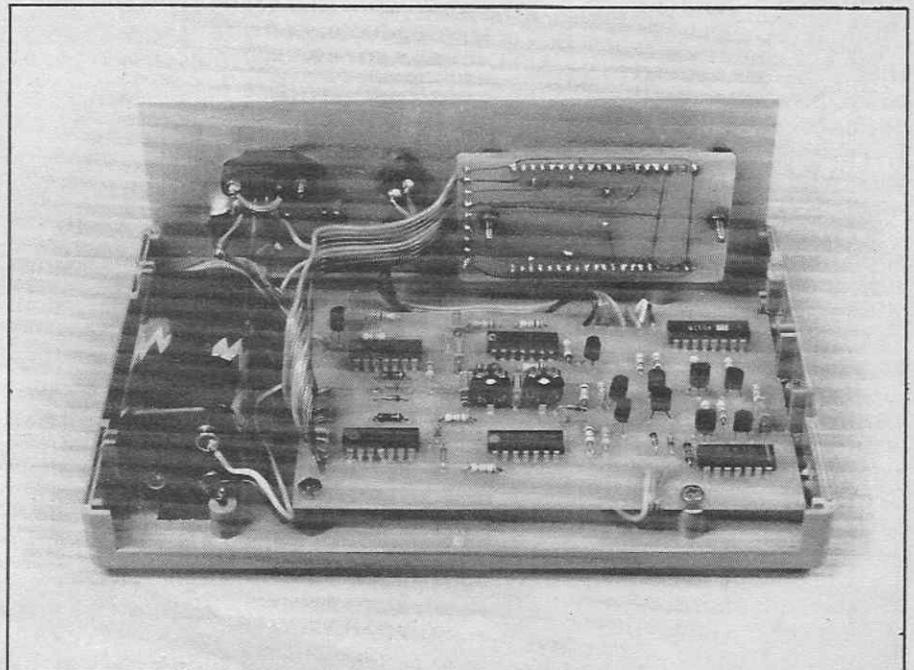
### Testing And Setting Up

If the presets (RV1,2) are fitted, turn both anticlockwise and connect up the batteries. When on,



the display should blank apart from the mode indication which should be a d or t. This should alternate each time SW2 is

operated.

Now select the diode mode and advance a preset until the display starts to flash, then back

# PROJECT: Transistor Tester

## HOW IT WORKS

Gates a and b in IC3 are wired as a bistable that changes state each time the on/off switch SW1 is pressed. When pin 3 is low, Q1 is turned on through R1 and power is supplied to the rest of the circuit.

Gates c and d are also connected as a bistable, this time changing state when the transistor/diode switch SW2 is pressed. In the transistor test mode, Q2 and Q3 are biased on, effectively shorting out diodes D1,2. (Some features of the display are also controlled by this bistable).

These diodes come into effect in the diode test mode, raising the threshold voltage for testing as mentioned above.

IC1 is connected in the astable mode having a frequency set at 50Hz by R24 and C5. This provides the waveform to drive the display and is divided by IC2 to give the 5Hz square wave used to drive the bridge circuit formed by Q4-7. The result of this is that the collectors of Q4,5 have a 5Hz square wave that is the inverse of that on the collectors of Q6,7. A 12V peak-to-peak waveform is thus generated, providing an AC supply to the test terminals.

The potential to the collector-emitter terminals is limited to 600mV in each direction by the base-emitter junctions of Q8,9 across these terminals in the transistor test mode. In this mode, Q2 and Q3 are always on as the Q4 and Q5 collectors switch between the supply lines because IC3 pin 10 is high whilst pin 11 is low.

Assuming no device is connected to the test terminals, Q8 and Q9 will conduct alternately, again at 5Hz. When the common emitter line is low Q8 is biased on through R13 and when it is high, Q9 receives its bias via R14. It is the conduction or otherwise of Q8 and Q9 that is monitored by IC4 to provide information on the device being tested.

Q8 charges C3 each time it conducts, and the time constant C3-RV1 is such that the input to gate IC4d remains below its switching threshold, thus holding the output pin 11 high. Conduc-

tion through Q9 on the other hand charges C4 so the input to gate a stays just above the switching threshold, keeping output pin 3 low.

The collector-emitter junction of a transistor being tested is effectively across the base-emitter junctions of Q8 and Q9 so if, say, a good NPN transistor is in circuit the bias to Q8 is diverted and it will switch off. Forward bias to the test transistor at this time is through Q7 and R12.

Similarly Q9 will be turned off by the application of a PNP device, this time biased by Q6 and R12. A short circuit across the collector-emitter connection will of course turn off both Q8 and Q9.

A diode across these connections will draw some current but this will be insufficient to effect conduction of Q8 and Q9. This ensures a transistor with a base-emitter or base-collector short will register.

In the diode test mode, the bistable IC changes state, reverse biasing Q2,3. D1 and D2 are effectively in series with the bias feed to Q8 and Q9. A diode connected across the collector-emitter terminals will be able to turn off either Q8 or Q9 depending on which way around it is connected.

The time constant RV1-C3 and RV2-C4 is dictated by the choice of 5Hz as the rate at which the supply to the test terminals is reversed. This in turn is a trade off between the response time of the instrument and reasonable immunity to the effect of any large value electrolytic capacitor that may be in circuit across a junction.

Good immunity to in-circuit resistance is achieved because the resistance across the junction must fall below one tenth of the value of R13,14 in the case of the collector-emitter connection and one tenth of R12 in the case of the base-emitter connection before the conduction of Q8,9 or the transistor being tested is affected.

In-circuit resistance below this will reduce the bias in each case to under the 600mV required for conduction.

off until the display just blanks. Repeat this procedure with the other preset.

To test the unit connect a diode across the collector-emitter terminals. The display should show **pn** when the diode anode is connected to the collector terminal and **np** when the diode is reversed. There should be no response from the connection of the diode when the unit is in the transistor test mode.

Check the transistor mode using a good transistor of each type. The display should remain blank until the base connection is made. Now short the collector-emitter probes together and check the display shows **nnn**.

Note that the buzzer will sound continuously whilst a good device of any type is connected. This is useful for rapid testing of components on a board when there is no regard for polarity.

Thyristors should be tested on the diode range due to their higher saturation voltage. The collector, emitter and base terminals become anode, cathode and gate respectively.

A good device will show **pn** (it does of course act as a diode) but *only when the gate connection is made*. Confirm that point otherwise it is faulty.

If the thyristor has an internal diode then it will show **np** before the application of the gate

A conventional 4-digit LCD is used to indicate the status of the device being tested. The display is driven by a perfect square wave from the bistable output of IC1. The individual segments required to represent the desired letters are driven by the exclusive-OR gates of IC5 and IC6.

The clock output from pin 10 of IC1 is connected to one input of each EX-OR gate and also to the backplate of the LCD. If the second input to any gate goes high, a square wave will then turn on any segments connected to the output of that gate.

Open circuit across the test connections blanks the first three letters of the LCD since both inputs to IC4 from Q8 and Q9 are high, forcing a low on pin 10 and the five control inputs of the relevant gates.

If a good NPN transistor is tested, Q8 turns off, sending the output of IC4d low and IC4c high, displaying **nnn** and releasing control of the lines through R17 and R18. Since Q9 is on, IC4b is high and the display **npn** is completed.

With a PNP transistor, the output of IC4b goes low as Q9 turns off, leaving **n** showing on the second digit. A **p** is completed each side from IC5b and IC5d, since the output of IC4d is high.

In short circuit, both Q8 and Q9 are off, sending the lines through R17 and R18 low. This leaves a display of **nnn** from the high output of IC4c.

In the diode mode, the first digit of the LCD is blanked by sending the control inputs of IC5b and IC6c low through D7 and D8. The bistable IC3 turns off Q2 and Q3 placing diodes D1 and D2 in series with the bias path to Q8 and Q9. The voltage across the collector-emitter test connections is now about 1.2V and the application of a diode will cause the cut-off of either Q8 or Q9 depending on its direction. This displays either **pn** or **np** as described above.

The buzzer sounds if the inputs of gate IC6b are different, which only occurs when a good device is in circuit.

connection due to the conduction of the internal diode.

Once the gate connection is made in this case, the display will show **nn** (which would normally indicate a short circuit) due to a legitimate conduction in both directions.

The display will similarly show **nn** when testing two diodes which are connected 'back to back'. A check can be made that this is due to conduction through two good diodes rather than a short circuit by switching to the transistor range and checking the display blanks off.

Darlington transistors also have a high saturation voltage and can be tested in the same way on

## PARTS LIST

### RESISTORS (all 1/4W, 5%)

R1	4k7
R2,4,6-11,23	10k
R3,5,15,16	100k
R12	180R
R13,14	330R
R17,18,24	47k
R19,20,21,22	1M0
RV1,2	4M7 horiz.

### CAPACITORS

C1,2,3,4,5	100n
------------	------

### SEMICONDUCTORS

IC1	4047B
IC2	4017B
IC3,4	4011B
IC5,6	4070B
Q1,3,5,7,9	BC307 or equiv.
Q2,4,6,8,10	BC237 or equiv.

### MISCELLANEOUS

BZ1	piezo-electric direct drive, 4-digit LCD
LCD1	2mm sockets (3) and/or 4-way Minicon Latch connector
SK1	push-to-make

PCB; case; type AA batteries (4); battery holder; LCD mounting bezel; nuts and bolts.

## BUYLINES

All components are readily available from component suppliers. The LCD and mounting bezel used in the prototype were from Electromail (Tel: (0536) 204555 stock numbers 588-588 and 587-282 respectively.

The case used was a 180 x 120 x 65mm Verobox.

Note that buzzer BZ1 is a piezo-electric sounder that contains its own electronics and is polarity conscious.

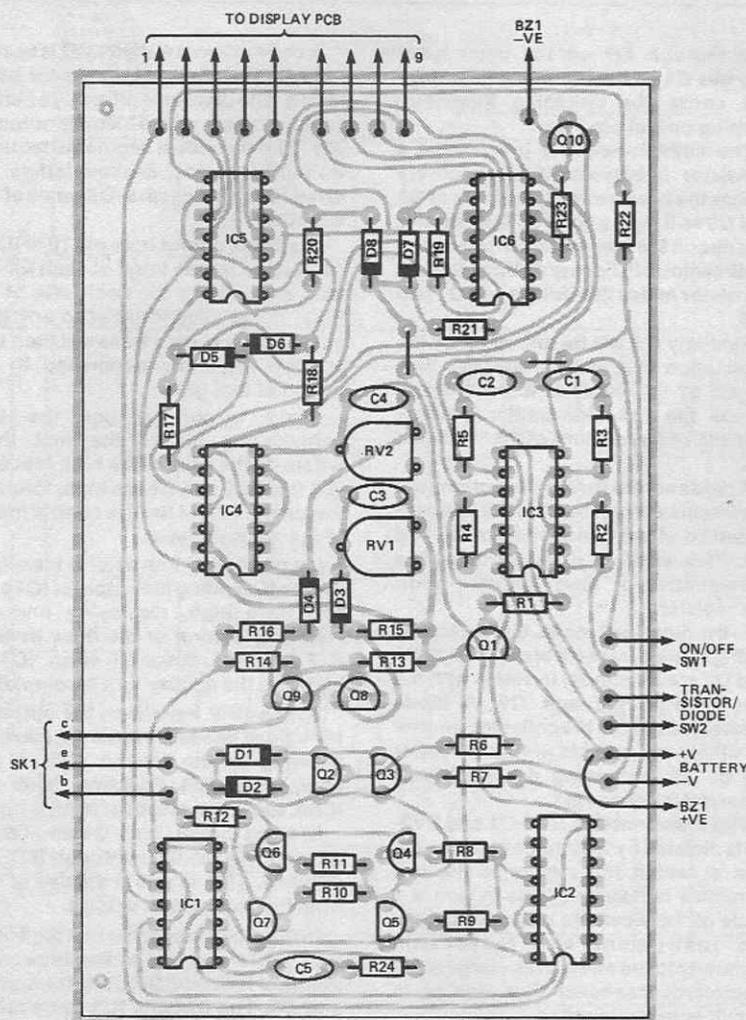


Fig. 2 Component overlay for the main PCB



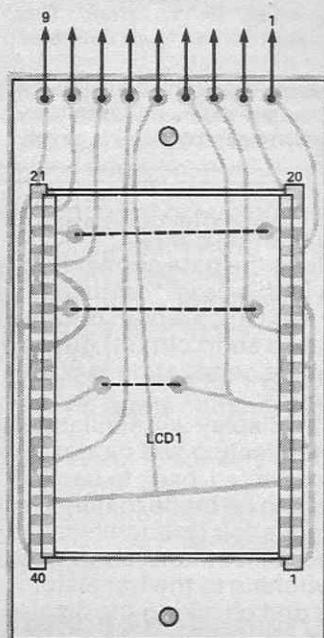


Fig. 3 Component overlay for the display PCB

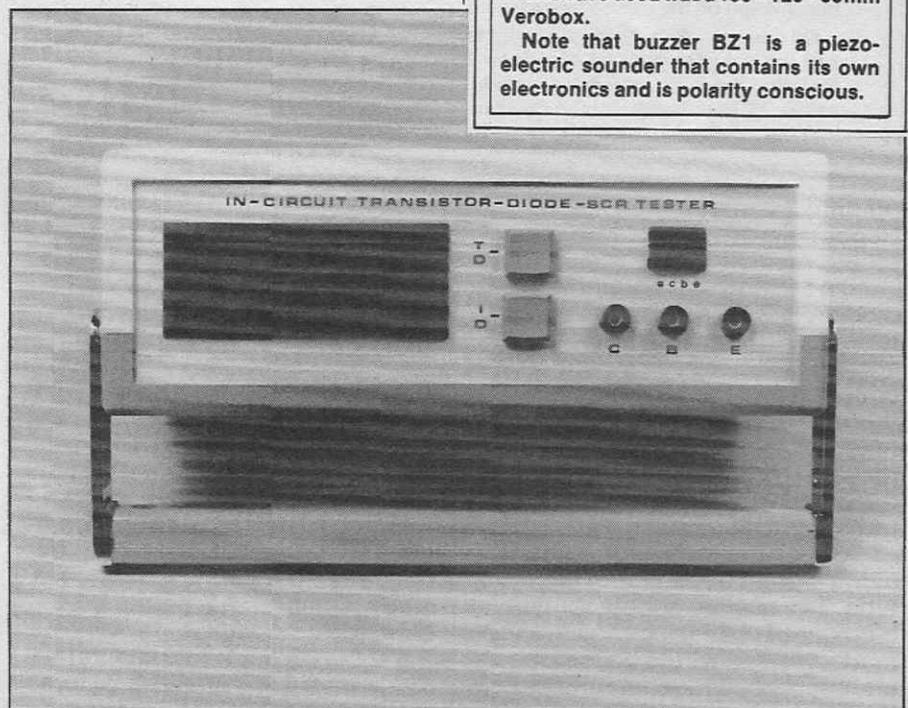

# PROJECT: Transistor Tester

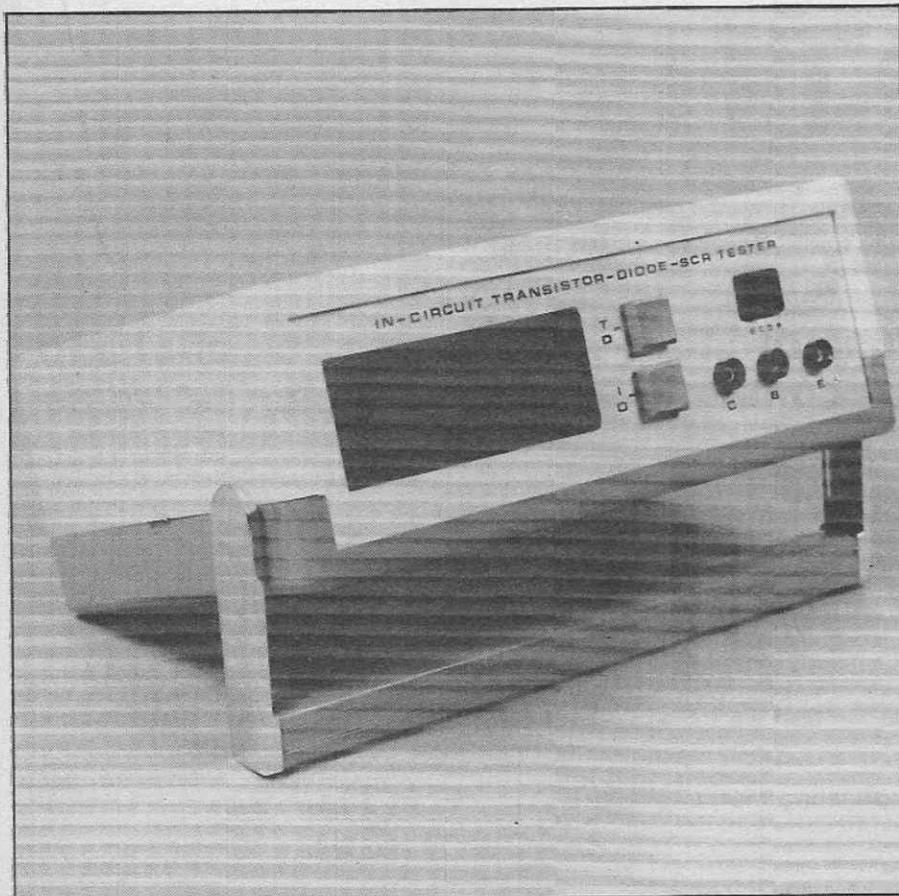

the diode range. Darlington's with internal diodes mean that an NPN device for example will display **np** due to an internal diode which updates to **nn** upon application of the base connection, again due to valid conduction in both directions.

A flashing display at any time should normally be interpreted as being a good device of the type indicated but with the presence of a large value electrolytic capacitor across a junction. The presence of such a component in circuit will give some conduction in the opposite direction to the semiconductor being tested and cause this effect.

As a result, this unit is not really suitable for checking mains supply rectifiers. Because of the low resistance of the supply transformer winding, the reservoir capacitor is effectively across the diode as far as the tester is concerned. If the capacitive reactance is below 40R or so at 5Hz, a short circuit indication will result even though the rectifier may well be OK.


A low battery will first show up as the display flashing at all times.

ETI

## 19" RACK CASES

\* Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish \* New improved construction and finish \* Black anodised aluminium front panels \* Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure \* Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles \* With ventilation slits and plastic feet \* Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package spare front panels available.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight	Price £
1U-10	19 x 1.75	17 x 1.5 x 10	2.4kg	23.50
2U-10	19 x 3.5	17 x 3.0 x 10	2.9kg	24.50
3U-10	19 x 6.25	17 x 5.0 x 10	3.5kg	26.50
2U-12	19 x 3.5	17 x 3.0 x 12	3.3kg	25.50
3U-12	19 x 5.25	17 x 5.0 x 12	4.0kg	27.50
4U-12	19 x 7.0	17 x 6.5 x 12	4.6kg	29.95

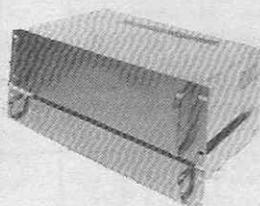

Please add £3.00 P&P for the first item and £1.50 for each additional item. No VAT to be added to the price.

## TEST EQUIPMENTS



C83A Digital Power Supply/Voltmeter (0/35 Volts 1.5 A)	£44.95
C83B Digital Power Supply (0/30 Volts 1 A)	£38.95
C89A Function Generator (2 Hz to 200 KHz)	£39.95
C86A 60 MHz Counter/Timer	£47.95
C87A Autoranging Capacitance Meter (0.1 pF to 99.9 mF)	£47.95
MV338 Metal-mains detector	£4.99

A new range of quality test equipment at the lowest possible price. The C89A (£34.95) and C86A (£39.95) are also available in kit form with full construction details. Please add £3.00 p/p per item (£1.00 for MV338).

To order send cheque/postal order — please allow up to 7 days despatch for cheque clearance. Quantity discount available. Customers who require further information please send S.A.E. Trade and overseas orders welcome. Mail order only.

**T.J.A. DEVELOPMENTS**  
Dept. ETI, 53 Hartington Road,  
London E17 8AS.

## Zenith Electronics<sup>®</sup>

### Kits — Modules — Hardware

#### EXTENDED OFFER

10-Channel variable speed running light kit, drives LED's or Mains lamps - plus 2-FREE LED display boards and LED lamps.

SPECIAL PRICE  
£14.97

- The following are examples of our proven product designs
- \* High quality touch dimmer 500W R/Built..... £12.99
  - \* Selectable tone generator 9-12v operation..... £5.50
  - \* 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit..... £9.83
  - \* Miniature FM Transmitter; 60-145MHz. Kit..... £6.95
  - R/Built..... £8.95
  - \* 3 Watt FM Transmitter, 80-108MHz. Kit..... £13.99
  - R/Built..... £18.99
  - \* 300 Watt Light Dimmer unit for 240 volt mains lights. Kit..... £6.95
  - \* 4 Code Digital Code unit plus Key Pad - select own code; 9 volt. Kit..... £15.95
  - \* 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit..... £11.11
  - \* VU Meter 10 LED indicator; -5 to +12dB range. Kit. £12.59
  - \* Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £28.08
  - \* Mains Wiring and Metal Detector. R/Built..... £11.00
  - \* Zenith Speech Processor P-202 R/Built..... £25.00
  - \* 18-Watt Car/Home Power Amp. 12-V. Kit..... £13.23
  - \* Amplifier Power Meter; 10 LED indicator from 0.25-100 Watt Input - 9 volt operation. Kit..... £9.52
  - \* Light sensitive relay unit; variable sensitivity trigger control; senses light or dark - selectable. Kit..... £8.45

ALL KITS CONTAIN FULL INSTRUCTIONS: P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.

OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.

S.A.E. For  
FREE  
Data Pack

Zenith Electronics, 14 Cortlandt Business Centre,  
Hailsham, E. Sussex, U.K. BN27 1AE.  
Tel: 0323 847973 Telex: 878334

# SMOOTH OPERATOR

Henry Davies makes use of the recent abundance of cheap telephones to design a complete system for home or office

Since the liberalisation of the telephone network, inexpensive telephones have become widely available. Obsolescent BT models such as the Trimphone and the once-standard 8746 can be picked up from surplus dealers very cheaply.

Using a little ingenuity and a soldering iron these phones can be linked together to create an intercom system or, if expanded, an entire house telephone system.

Figure 1 shows a complete two phone intercom system with all the necessary signalling, ringing and transmission functions. The switching and signalling take place automatically and are initiated by taking a telephone off-hook in the usual manner.

The familiar 'burr-burr' ringing cadence is generated by an economical circuit shown in Fig. 2 and examined in detail later.

## Operation

Each telephone requires a loop detector (indicated by a dotted line in Fig. 1). The internal workings of the telephones themselves are described in the panel but basically when the handset switch of the phone is lifted, current will flow through the diodes of the relevant loop detector and the associated relay will operate.

Assuming both telephones are on-hook, neither loop detector is activated and the relays assume their normally closed positions. The contacts have been interconnected such that if both are in the normally open position or both are in the normally closed position, the result is an open circuit and the ringer is not enabled.

If one relay is energised while the other is not, however, then

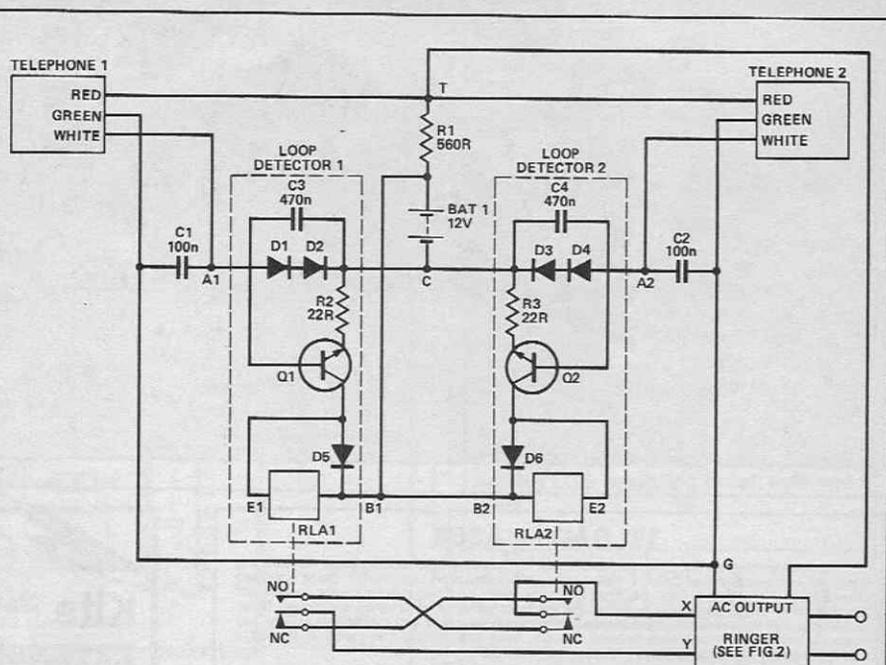


Fig. 1 Circuit diagram for a two phone intercom

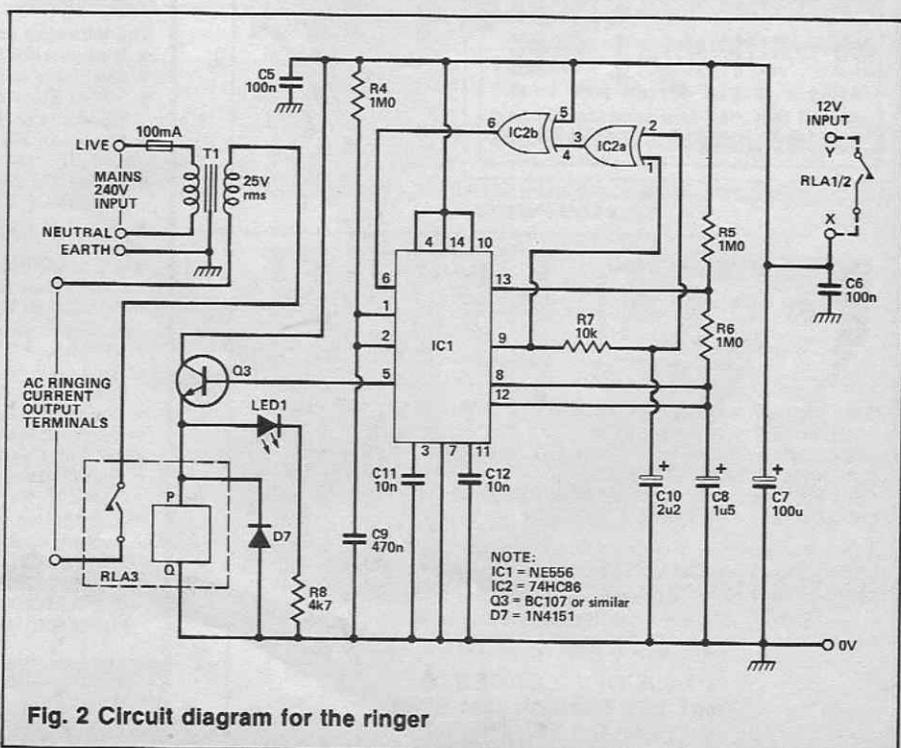


Fig. 2 Circuit diagram for the ringer



the ringer is enabled (it is a form of hard-wired exclusive-OR gate).

In practice this means that ringing current is switched on when the handset of either telephone is lifted and is

switched off again when the second handset is lifted (call answered) or when the first handset is replaced (call unanswered).

The ringing current generator

cadences the ringing current to produce the familiar UK ringing pattern and the internal configuration of the telephone ensures that only the bell in the on-hook instrument can ring. The capacitors C1,C2 allow a small amount of ringing current into the speech circuit thereby providing a ringing tone to the calling party.

## HOW IT WORKS

The loop detector circuits LD1 and LD2 are indicated by the dotted lines in Fig. 1. The circuit is basically a common emitter amplifier with DC negative feedback (developed across R2 and R3). When current flows from A to C, the two diodes in this path are biased on and about 1.4V is dropped across them.

This voltage is used to switch on the transistor and energise the relay. The reverse biased diode across the relay coil is present to protect the transistor from back EMF. The relay can be any nominal 12V type with a set of change-over contacts so long as the coil requires no more than about 30mA for operation.

The cadencing in the ringer is

achieved by a single 556 (dual timer) package (IC2) with two EX-OR gates functioning as an edge detector as shown in Fig. 2. The 556 is used in a conventional configuration with one half acting as an astable and the other as a monostable multivibrator.

The edges of the astable output are processed by the EX-OR gates and each edge is used to trigger the monostable section. By choosing a suitable mark-to-space ratio for the astable, the desired cadencing is achieved — pairs of on periods repeating after a suitable off period. The timing waveforms are shown in Fig. 3.

The LED (optional) will glow in sympathy with the ringing cadence.

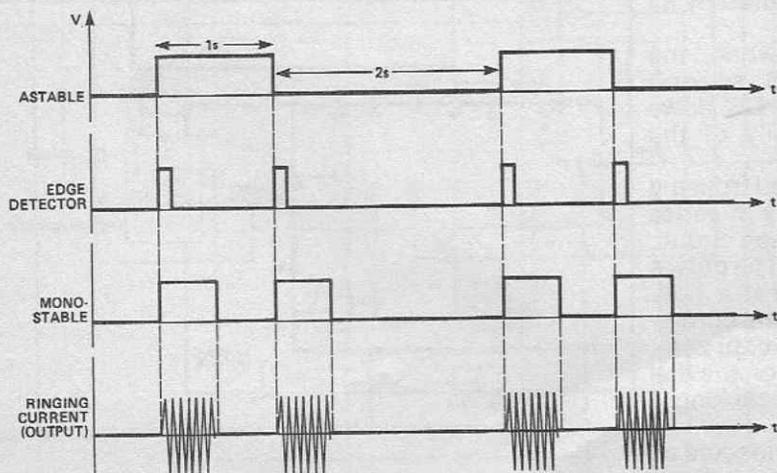


Fig. 3 Ringing generator waveforms and timing diagram

## Central Battery

The loop current established by the central 12V battery supplies the power for the carbon or electret microphones as well as operating the loop detector relays. The speech signals are developed across R1 and can therefore be heard by both parties. The loop detectors are designed to amplify the loop current to a sufficient extent to ensure the relays operate.

The ringer circuit is shown in Fig. 2. UK telephone bells and warbling tone ringers (or 'ringing detectors' as they are generically termed in the British Standards) are designed to operate from 25Hz AC at 80V RMS. However, this allows for considerable voltage loss in the line between the exchange and the installation and a lower voltage will be found perfectly adequate (and considerably safer!) in this application.

The experimenter may choose a ringing voltage to suit the range of transformers he or she already possesses. I used a voltage of 25V RMS.

Experiment reveals that the bells can be made to ring satisfactorily from a 50Hz stimulation and this of course

considerably simplifies its generation as little more than a mains transformer is required. Note that there is no easy way of converting 50Hz to 25Hz. Half-wave rectification, for example, produces harmonics of 50Hz but the period of the resulting waveform is still 20ms — a means of extending the period to 40ms needs to be employed if a 25Hz fundamental is to be generated. It is fortunate, therefore, that the bells and tone ringers respond to 50Hz!

### Construction

The PCB design is laid out for a two station system (see Fig. 4). Note the wire link between pins 10 and 14 of IC1.

The mains transformer and relays are mounted off the circuit board to allow freedom of choice

in the types used and flexibility from the point of view of layout within the enclosure. However, some spare space has been left on the board to allow the loop detector relays to be mounted there if desired.

Fit the components to the board ensuring that the diodes and electrolytic capacitors are oriented with the correct polarity. Check the location of pin 1 when installing the ICs. Use of IC sockets is recommended to avoid soldering the IC and for ease of replacement in case of failure. Refer to the wiring diagram (Fig. 5) to complete the connections.

Observe safe practices in terminating the mains cord securely and shielding the live terminals from contact. Ensure that a 100mA fuse is fitted in series with the mains live.

### Testing

Taking both telephones off-hook should allow speech to be conveyed. This can be tested without the ringer switched on in the first instance. If no DC is present (blow in the microphone to check) suspect a wiring error. Check the polarity of the loop detectors.

With the supply to the ringer switched on, the ringer should be found to operate following a short delay when one but not both of the telephones is off-hook. If the ringing pattern is incorrect, check the components around IC1.

If no ringing current is generated at all, check the wiring to the transformer and relays, and the condition of the fuse. Shorting terminals X and Y together should cause the

## Internal Telephone Configuration

The old BT telephones such as the 8746 and Trimphone contain numbered screw terminals and a system of links with spade-type cut-outs. The essential circuit details of these telephones are shown in Fig. A.

In normal use, the red and white wires are connected to the two wires of the telephone line. Green is connected to white in the junction box external to the telephone. A link is usually fitted across the handset switch A in series with the telephone bell. The remaining contacts of the handset switch B in series with the speech circuits control whether or not the instrument draws DC from the telephone line. This switch is open-circuit when the handset is on-hook but becomes short-circuit when the handset is lifted to initiate or answer a call. The exchange central battery acts as a source of 50V DC.

Note that DC is prevented from flowing in the bell circuit by a  $1\mu 8$  capacitor. Therefore, the presence or absence of a DC path enables the exchange to detect the state of the handset. The telephone bell is rung when the instrument is on-hook by supplying AC ringing current to the line, flowing through the capacitor and energising the bell or tone caller. Incidentally, it is this capacitor which is now fitted in the master socket of the new style connection arrangement (defined by BS6305) being shared by all the telephones plugged into the system.

The capacitor also plays a role when the instrument is off-hook, coupling AC speech waveforms to the telephone receiver. The DC flows through the microphone which is typically of the carbon or, more recently, electret type.

The dial pulse contacts have been omitted from the diagram for clarity but these are essentially in series with the handset switch contacts in the speech circuit. They interrupt the DC in the off-hook state. The pulses are counted at the exchange and registered as a digit. Each digit on the dial (or keypad) generates the corresponding number of current break pulses except zero, which generates ten pulses. Other contacts on the dial assembly short out the earpiece so that loud clicking is not heard during dialling.

You should make sure your phone is connected as in Fig. A. Remove the case of the telephone by unscrewing the rear retaining screw (or in old designs

the two screws adjacent to the handset switch buttons). The red, green and white wires of the telephone lead (when not fitted with the new style plug) should already be connected as in Fig. A. Be careful to distinguish between the wires of the telephone lead and those of the curly lead to the handset which uses the same colours.

Check that the links are correctly located. If a link is fitted between terminals T5 and T6, remove it. If you omit to do this, the bell of the calling station will ring in addition to that of the called station during the set up of a call — a somewhat confusing situation. This is because the method of applying ringing current to be used here differs from the BT network arrangement.

If the telephones you obtain are fitted with the new style line jack plugs, you will find that the green wire needs to be connected to the bell as shown in the figure and it will be necessary to transfer the wire to the appropriate terminal. The link between T7 and T6 must be fitted. The blue wire in the telephone lead is not required and may be connected to a spare terminal.

You will usually find some spare links inside the telephone, connected to unused terminals.

The numbering of the terminals within the Trimphone agrees with that of the 8746 so the above instructions apply equally to either instrument.

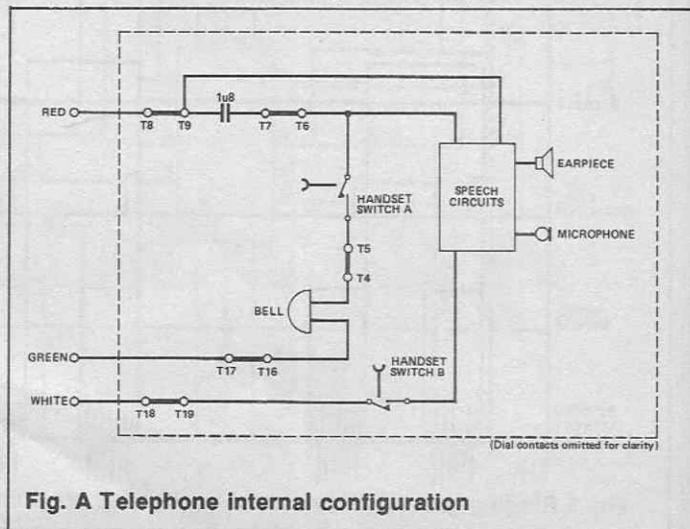


Fig. A Telephone internal configuration

# PROJECT: Telephone System

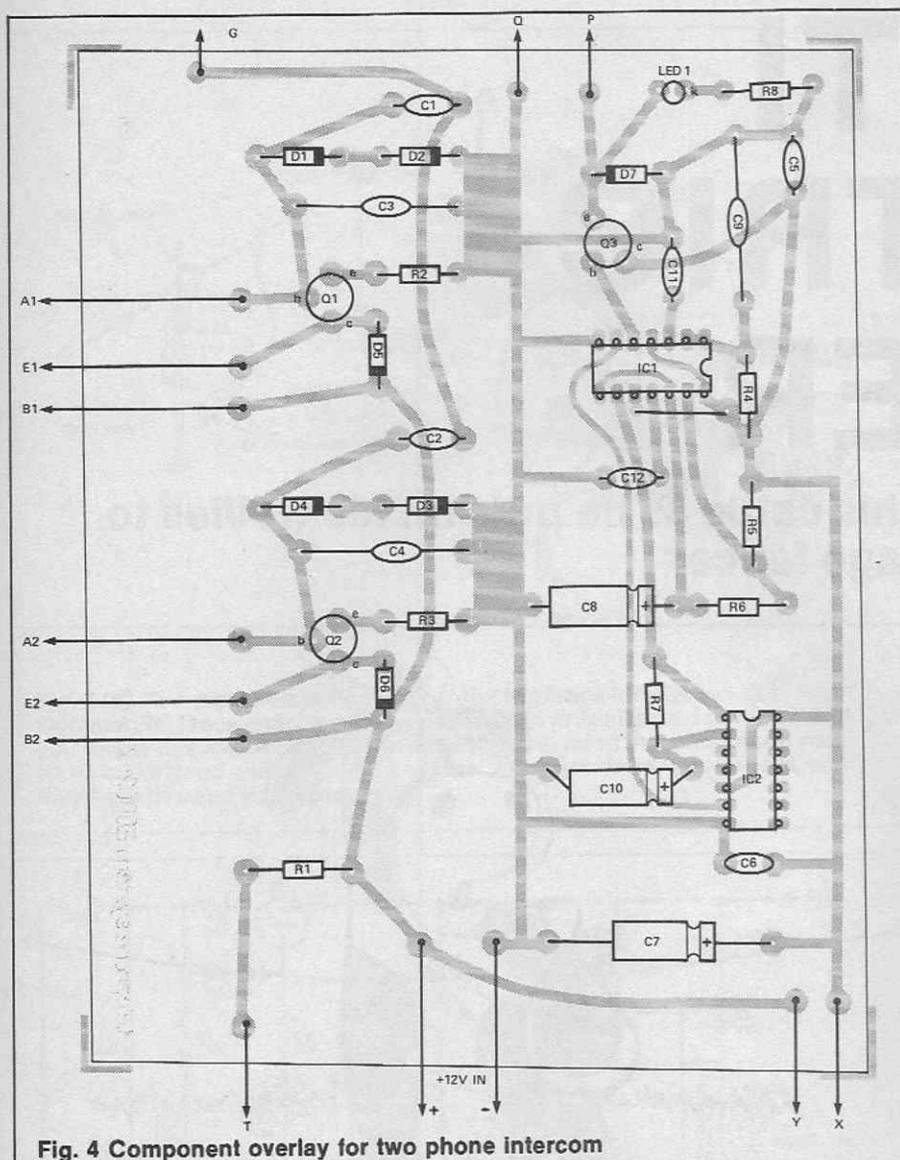


Fig. 4 Component overlay for two phone intercom

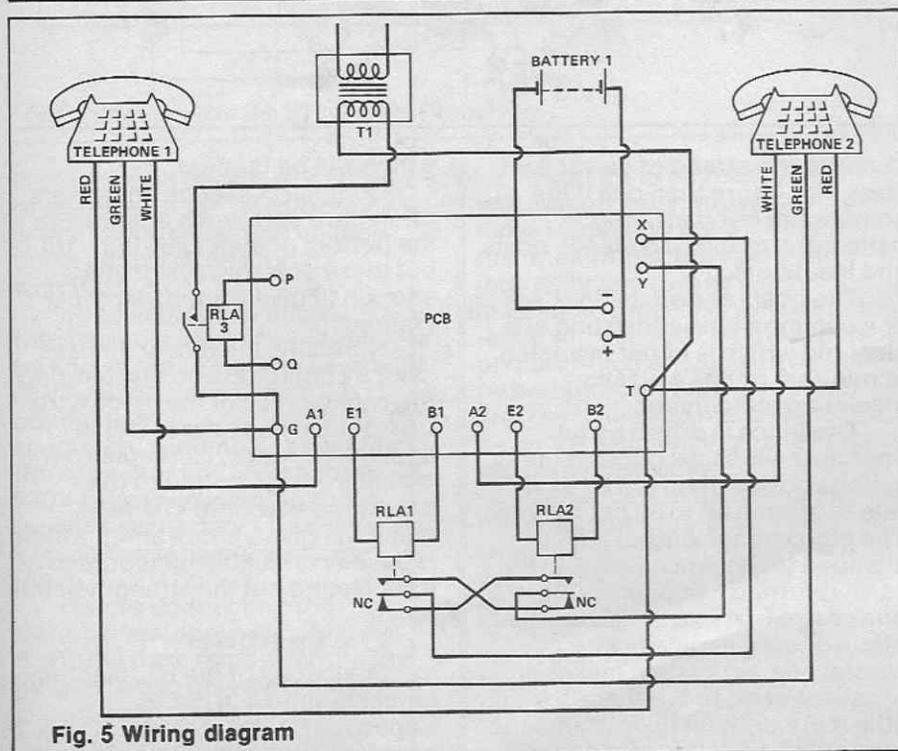


Fig. 5 Wiring diagram

## PARTS LIST

### RESISTORS (all 1/4W 5% unless specified)

R1	560R 1/2W
R2,3	22R
R4,5,6	1MO
R7	10k
R8	4k7

### CAPACITORS

C1,2,5,6	100n polyester
C3,4,9	470n polyester
C7	100µ 25V electrolytic
C8	1.5µ tantalum
C10	2.2µ 25V electrolytic
C11,12	10n ceramic

### SEMICONDUCTORS

IC1	NE556
IC2	74HC86
Q1,2,3	BC107 or equiv.
D1,2,3,4,5,6,7	1N4151
LED1	LP301

### MISCELLANEOUS

BAT1	12V accumulator or dry cells
RLA1,2	12V relays with change-over contacts (SPCO)
RLA3	12V relay with a normally open contact (SPST)
T1	Mains transformer approx 25V AC, 250mA
PCB	100mA fuse (20mm) and fuseholder; case; wire; nuts and bolts; ex-BT telephones.

## BUYLINES

All components are easily available from the usual sources. The transformer used in the prototype was the Greenweld XO57 transformer. The SPCO relays were National RS12 sub-miniature SPCO relays. The PCB is available from the PCB Service as detailed in the back of this issue.

ringing generator to operate irrespective of the loop detectors so that LED1 if fitted will start to flash after a short delay and the ringing relay should be heard to operate.

### Expansion

Further telephones can be added to the system by including additional loop detectors for each one and inter-connecting the relay contacts as necessary. The basic building blocks presented here could be developed to form a more complex system if desired. I leave it to the experimenter to develop an automatic dialling facility for a multi-station version!

ETI

# THE ETI ELECTRIC FENCER

**Paul Chappell rattles his cattle as he puts on his wellies to present this high-voltage fencer**

**T**he image of returning to a simpler, slower-paced way of life is one which must have crossed the mind of many a tired and frustrated city worker caught in yet another traffic jam or having the breath squeezed out of him on a well stuffed tube train.

A few acres of good, fertile land, a cow for milk, a few hens to lay eggs for the family breakfast, a vegetable garden, the kids playing in fresh country air and learning the names of trees and flowers ... a blissful dream.


For many people this dream has become a reality. Probably not in the way they first thought when they set off for the country, heads crammed with TV images of wacky subsistence farming in a Surbiton garden, or the nonsense spouted by early proselytes of the 'back to the land' movement. A good life all the same.

One of the problems of taking on a smallholding is that the fences are likely to be in poor condition. This is by no means the only problem but it's one that ETI can help with! An electric fence can be set up in hours, rather than the weeks it may take to put up a conventional fence, so you can get everything moving without delay.
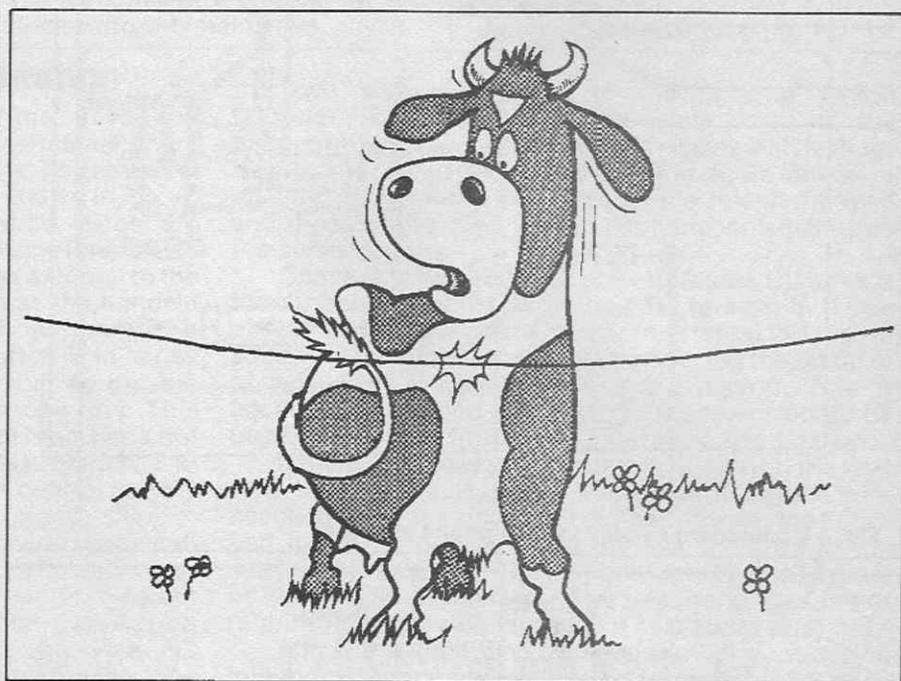
## Electric Fencing

The attractions of electric fencing are in its very low cost and in the ease with which it can be set up or moved. Since it doesn't rely on physical strength for its effectiveness, the posts and wire can be much lighter and cheaper than for conventional fencing methods.

The main components of an electric fence installation are shown in Fig. 1. The fence itself



consists of a strand of galvanised steel wire (more than one if the animals are good at limbo dancing) supported by fence posts and insulators.

The posts shown in Fig. 1 are of a common type consisting of a steel rod which is either insulated at one end, or has a plastic insulating attachment.

The fence is driven by an energiser which produces high voltage pulses of up to 4kV at a rate of around 40 to 60 per minute. The high voltage output lead is clamped to the fence wire and the earth return to a copper rod sunk one or two feet into the ground. An offcut of copper pipe from a central heating system makes an excellent earth rod, although it's a little more difficult to drive into the ground than a purpose made rod,

which will be tapered.

Commercial fence energisers often have earth rods attached to the bottom of their case (Fig. 1b) but these don't always go deep enough to give a good electrical connection.

Normally, the fencer amuses itself by charging and discharging the capacitance of the fence wire. If an animal happens to brush against the fence, it completes the circuit from HT output to the ground connection. The next pulse will give a sharp sting, which is usually enough to discourage it from testing out the strength of the fence.

## The Energiser

The circuit of the ETI electric fencer is shown in Fig. 2. Capacitor C1 charges at a constant current through Q1 and

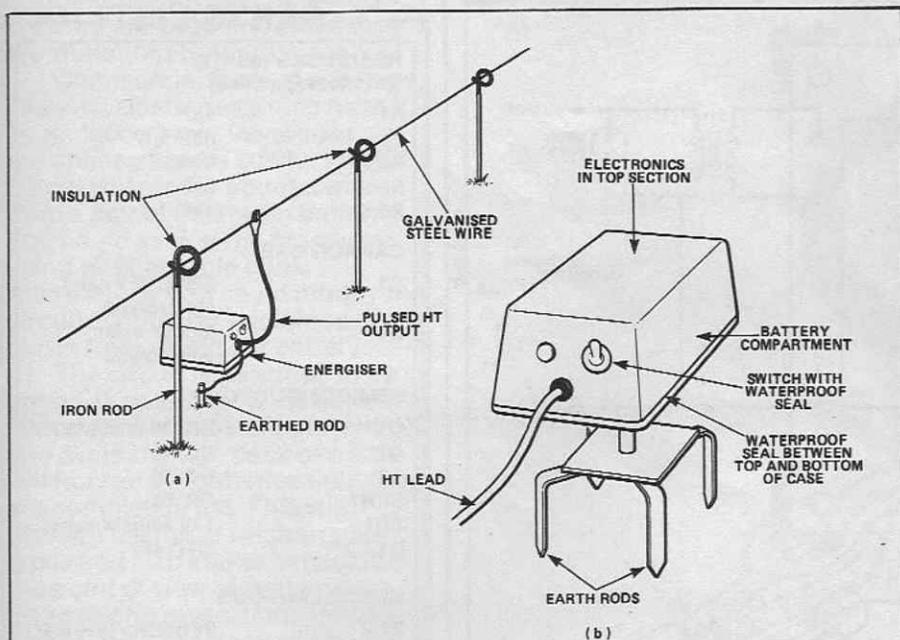


Fig. 1 (a) The main components of an electric fence installation. (b) Commercial fence energisers often have earth rods attached to the case. If you follow this idea for your own fencer, bear in mind that short earth rods won't make good contact in dry weather. When you water your plants, you may have to water your fencer too!

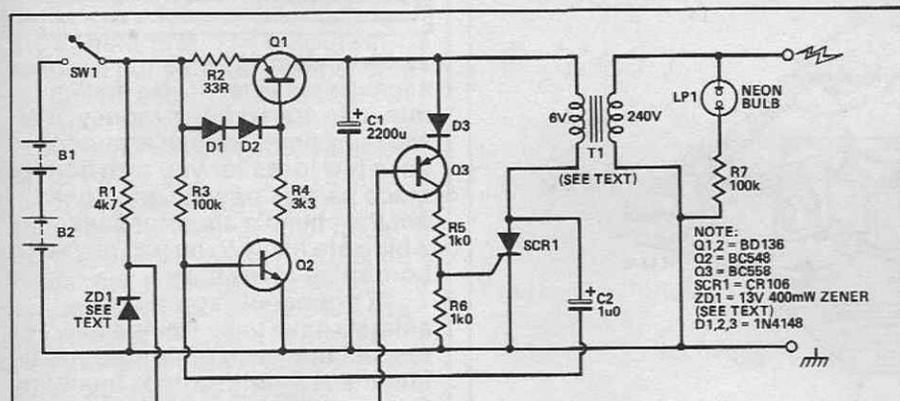


Fig. 2 The circuit of the ETI Electric Fencer

is discharged once every second or so through the transformer T1 which produces a high voltage pulse across its secondary windings.

Special purpose pulse transformers are not easy to come by and so the prototype used a 6V 25VA mains transformer connected 'back to front' — its 6V secondary winding connected to the capacitor and SCR and its 240V primary becoming the fencer's secondary and delivering the high voltage pulses to the fence.

Before connecting the transformer, about two thirds of the turns were removed from the 6V winding to give a greater open circuit output voltage — about 1.5kV on the prototype which should be enough for anybody!

If you try to increase the voltage too much (by removing more turns from the 6V winding) the transformer will spark internally and ruin its own insulation. Since the voltage of the fence will depend to a great extent on how much energy can be pulsed through the transformer and removing too many turns will lower the efficiency, your efforts will be wasted anyway.

Construction of the PCB poses no particular problems. The overlay is shown in Fig. 3 and if you follow it carefully, the circuit should work first time. Q1 and SCR1 do not need heatsinks.

It's worth giving some thought to the case for the project, bearing in mind that it will be outside in all weathers and won't last long if it's not properly protected.

By far the best solution is to use a weather-proof plastic case. West Hyde do a range of cases with a sealing gasket between the base and lid. If you can find anything similar in the home constructor catalogues, this will be ideal. Be prepared to pay about £8-£10 for a good one.

A low cost alternative is to use a die-cast box of suitable size (see Buylines) and to use it upside down with the PCB and transformer suspended from the top and the batteries on a stand of some sort (two lengths of wood baton will do) to keep them clear of any puddles that might form by ingress of rain or by condensation (Fig. 4). Drill drainage holes in the base and stand the fencer on some bricks when in use to prevent the holes from becoming blocked with mud (or build a stand if you want to make a professional looking job of it).

A low cost insulator for dry weather can be made from a humble plastic cotton reel. A nail through the centre into a wooden post, a groove or notch to hold the fence wire away from the post, wind the wire once around the reel and you're done. It can be quite effective.

## HOW IT WORKS

Capacitor C1 is charged at a constant current through transistor Q1. The base of Q3 is held at 13V by ZD1 so the transistor will begin to conduct via D3 when the capacitor has charged to about 14.3V.

Conduction in Q3 supplies the gate trigger to SCR1 which discharges C1 through the primary (the modified 6V winding) of the transformer. This produces a high voltage pulse at the output of the circuit, which is connected to the fence.

The discharge of C1 removes the gate drive from the SCR which is then free to turn off as soon as the current sinks to zero. Diode D3 prevents excessive current flowing in the base-emitter junction of Q3 if reverse breakdown should occur. The current is limited to the diode's reverse leakage current so the transistor will come to no harm.

Under open-circuit conditions, the SCR will turn off without help since the transformer will ring slightly and will divert Q1's current from the SCR to C1. When the circuit is loaded, there's no guarantee that this will happen, so to ensure reliable turn-off of the SCR, the current from Q1 is briefly cut off by C2 and Q2 until the SCR has had time to recover.

The resistor and neon bulb serve to give an indication that the fencer is working without the need to touch the output terminals (rather you than me!) The lamp flashes on each pulse of the fencer.

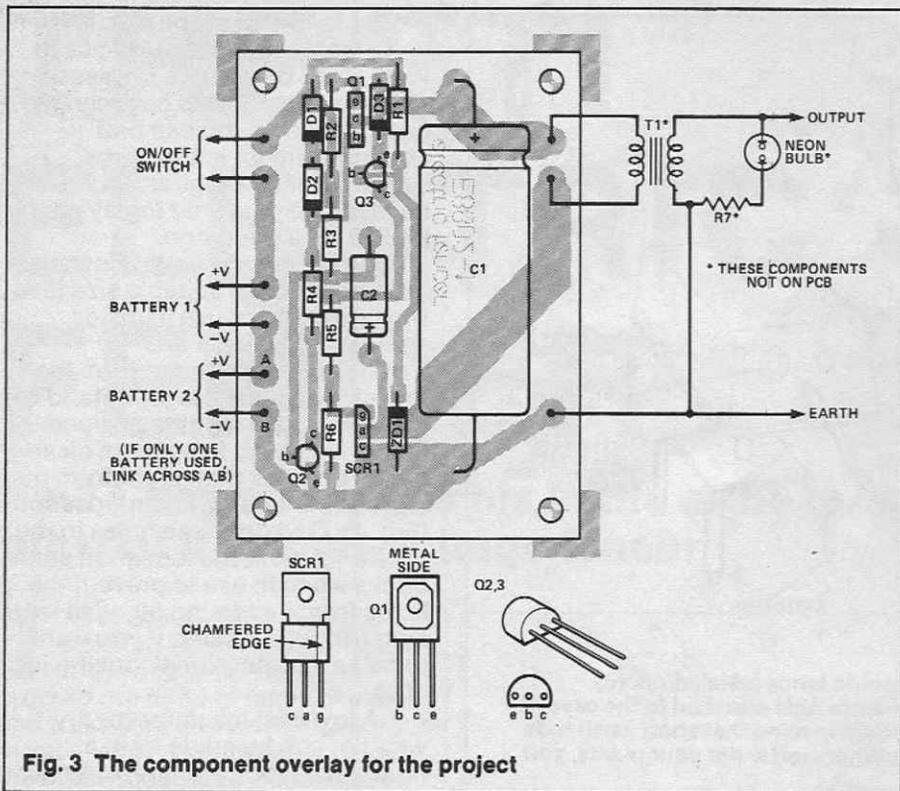


Fig. 3 The component overlay for the project

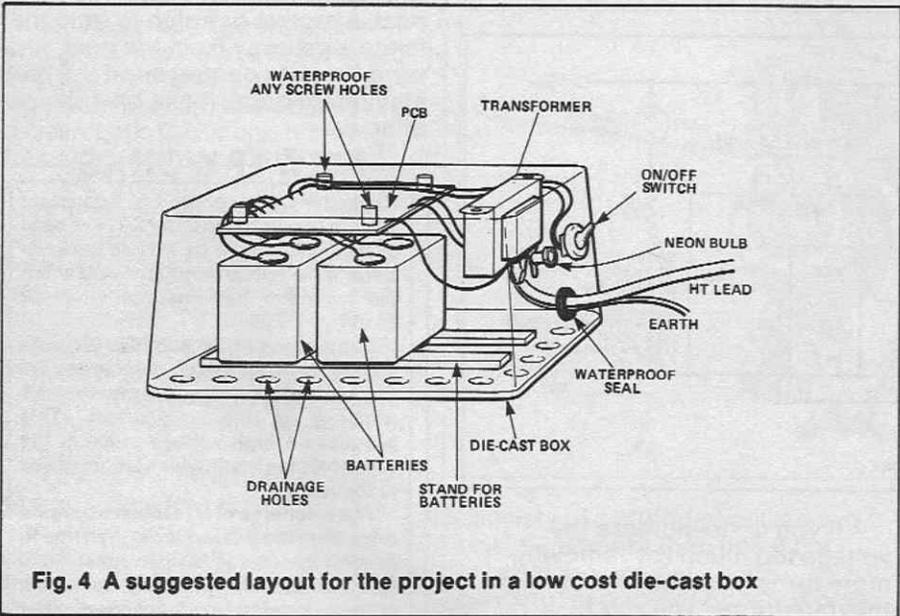


Fig. 4 A suggested layout for the project in a low cost die-cast box

Electricity can also leak away from the fence by corona discharge, ionisation and surface tracking. The first two are prevented by not using an excessively high voltage and avoiding frayed fence wire with sharp points. Surface tracking can be cut down by using insulators with a long surface path to the nearest conducting material — some are better than others in this respect.

The end of the fence is usually held by an insulator in the form of a twisted figure eight (like the old ceramic 'egg' insulators) which should be in compression (Fig. 5a)

and not in tension (Fig. 5b) when it will be likely to break. The ceramic ones are best avoided, by the way, since the glaze cracks easily and this reduces their effectiveness considerably.

Weather proofing is the order of the day for any equipment to be used outdoors. Use a good strong clamp to connect the ground wire to the earth rod and another to connect the HT wire to the fence. Croc clips will rust faster than you can say 'where are my sheep?' and will not make good contact once the spring has failed.

Most agricultural merchants (look in Yellow Pages!) will have a

## PARTS LIST

### RESISTORS (all 1/4W 5% unless specified)

R1	4k7
R2	33R 1/2W
R3,7	100k
R4	3k3
R5,6	1k0

### CAPACITORS

C1	2200µ 25V axial electrolytic
C2	1µ 25V axial electrolytic

### SEMICONDUCTORS

Q1	BD136 or similar
Q2	BC548
Q3	BC558
SCR1	CR106
ZD1	13V 400mW zener
D1,2,3	1N4148

### MISCELLANEOUS

B1,2	9V battery (see text)
LP1	neon bulb
SW1	SPST switch
T1	modified 6V mains transformer (see text)

PCB; case (see text); battery connectors; connecting wire; EHT wire for output lead; clips for fence and earth wires.

stock of electric fence accessories. Even if you don't intend to spend much money, it's worth having a mooch around to get a few ideas for your own home-made parts. Copy the good ones, not the cheap'n'cheerful ones, which are likely to be just on the borderline of usability.

It's generally agreed that animals have to be trained to respect the fence otherwise you'll find the slow witted ones bumbling their way through before they realise what's happening. Introduce them to the fence under controlled conditions and they'll soon learn to avoid it.

## Safety

It goes without saying, I hope, that the fence must *not* be powered from the mains or any kind of battery eliminator. Batteries only. If the fence is placed where members of the general public might come into contact with it — around the boundaries of your land, for instance — you are required to put up warning signs. You can get little tags to hang on the fence wire itself.

Any holes drilled for the PCB and transformer supports must be sealed and a good coating of waterproof lacquer over the electronics and transformer wouldn't go amiss.

# PROJECT: Electric Fencer

Batteries for electric fences are always a problem, since they are quite thirsty for current.

Commercial fencers use large, expensive batteries which have to be replaced every few weeks, so the upkeep can be costly. The ETI fencer will run for about a week from a pair of PP9 radio batteries. You could save some money by using re-chargable ones. Alternatively you could modify the circuit slightly (as explained later) to run from an old car battery.

The circuit is designed to be as gentle as possible on the batteries, taking a fairly constant current and avoiding high peak currents. It will not run the batteries until they are completely flat. This will prolong the life of re-chargable types and also makes sense from the point of view of sustaining a good strong pulse. If the fence just tickles, your livestock will trample it down in no time!

## Modifications

To run the fencer from a car battery, all that is needed is to reduce the value of ZD1 to 7V5 and to remove a few more turns from the transformer. The output will be reduced but you can compensate for this by using a higher value of capacitor for C1 (4700 $\mu$  instead of 2200 $\mu$ ) and reducing the value of R2 to 15R.

If you are determined to squeeze every last drop of juice from your batteries, at the risk of ineffective pulses, this can be achieved by replacing ZD1 with a 12k resistor. With the zener, the pulse strength will remain constant until the circuit eventually ceases to fire. With the resistor, the pulses will get weaker as the batteries run down.

You may like to experiment with different kinds of transformer for T1. You can try large TV line output transformers or car ignition coils, for example. The transformer must have a large enough core to transmit the burst of energy from primary to secondary without undue loss. Miniature transformers are no good at all.

As it stands, the fencer will energise several hundred yards of fence. If this is not enough, the output can be increased by stepping up the value of C1. Choose a capacitor with a high peak current rating or use several smaller capacitors in parallel. The value of R2 should be decreased to maintain the pulse rate. Keep an eye on the temperature of Q1 and R2 — use a 1W resistor and a heat

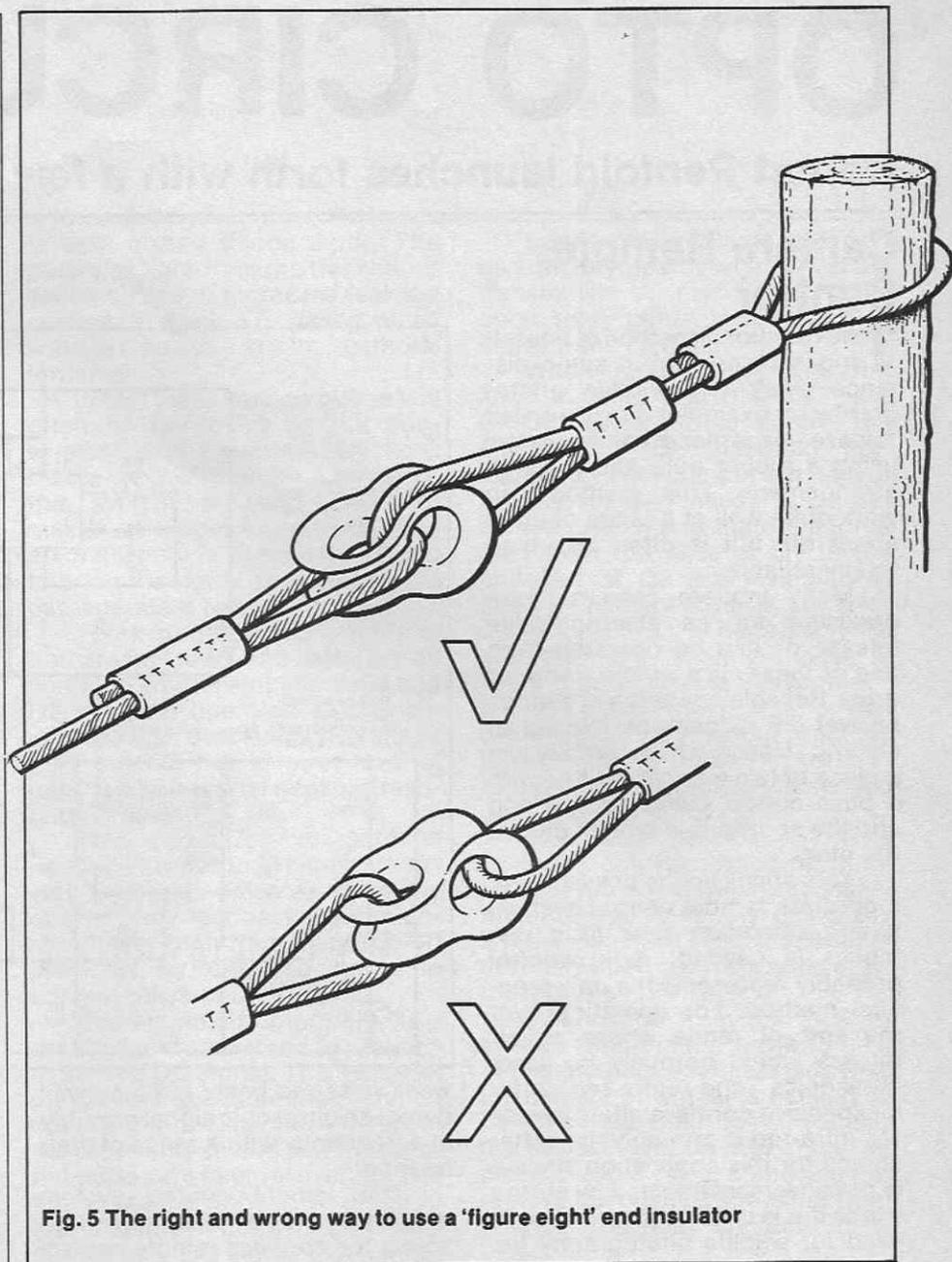


Fig. 5 The right and wrong way to use a 'figure eight' end insulator

## BUYLINES

A die-cast box for the project can be obtained from: Cirkit, Park Lane, Broxbourne, Herts. EN10 7NQ. Tel: (0992) 444111. The size you need will depend on whether or not you want to fit batteries inside it, so perhaps the best thing to do is to send for a catalogue and choose your own. None of the components should cause any problems.

The PCB is available from the PCB Service.

If you'd like to know more about small-scale farming and the profit opportunities from keeping special breeds of livestock, a year's subscription to *Home Farm* magazine will cost £9.00 inclusive from Broad Leys Publishing, Widdington, Saffron Walden, Essex. Tel: (0799) 40922.

sink on the transistor if necessary. Use a larger transformer (50 or 100VA) and batteries that are man enough for the job.

## Using the Fencer

Very often, using an electric fencer for the first time means learning the facts about high

voltage electricity the hard way. Materials which are OK as insulators for low voltages (wood, for instance) may be hopeless at high voltages. When a wooden post is sodden with rain, it may as well be a direct short to ground. Even when bone dry it's none too good. It's essential to use insulators.

ETI

# OPTO CIRCUITS

Robert Penfold launches forth with a few Tech Tips.


## Camera Remote Control

The traditional method of operating a camera from some distance away (for wildlife photography for example) is to use an 'air release' — a rather primitive system using a rubber bulb and a piston arrangement. This method can work quite well at a range of up to about 6m but is often less than totally reliable.

Many modern cameras have provision for an electric cable release or can be operated from one of these via a winder or motor drive. Reliable operation at a range of over 6m is then possible via an electric release, which is really just a piece of two way cable fitted with a push-button switch at one end and the appropriate type of plug at the other.

This opens up the possibility of a cordless remote control system. Where operation over long distances is needed, radio control probably represents the only practical method. For operation over the sort of range where an air release would normally be used, ultrasonics and infra-red offer inexpensive cordless alternatives.

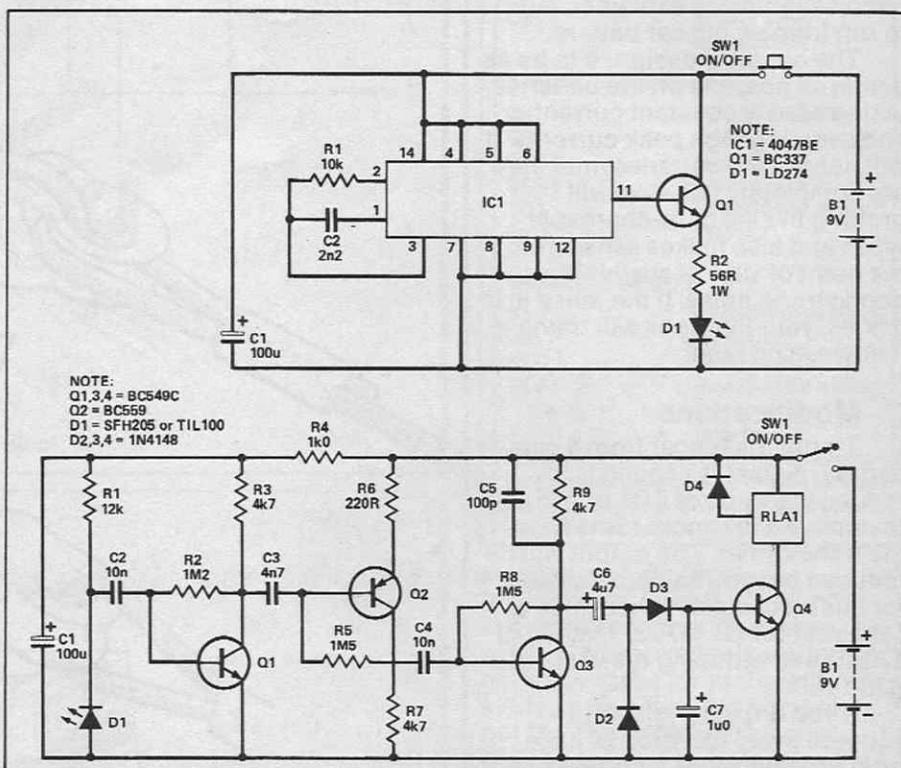Infra-red is probably the better choice for this application since it is not adversely affected by strong winds if it is used outdoors. Also, if used for wildlife photography the animals are unlikely to react to a



weak infra-red beam but may well detect an ultrasonic signal possibly at a frequency within range of their hearing!

The remote control system described here was designed solely for cordless remote control of a camera and will work over a

presence sensing.

IC1 is the passive infra-red detector. This is a special *pyro* sensor which is specifically designed for this application. Infra-red photo-diodes and other common types of infra-red sensor are totally unsuitable for use in passive detector circuits.

It is quite long infra-red wavelengths which must be detected whereas most infra-red devices are only sensitive in the part of the infra-red spectrum close to visible red wavelengths. IC1 has a special ceramic sensor plus a built-in source follower buffer amplifier.

Other *pyro* sensors can be used in the circuit, but most alternatives (including the SRA02) require a discrete 47k load resistor from the source terminal to the

range of about 8m or so. It is a simple on/off type controller and as such it probably has many potential uses in other fields of interest. Of course, it is only a practical proposition if you have a camera or winder that permits electrical operation of the shutter,

negative supply rail.

The output from IC1 is a weak AC signal at a frequency of between about 0.3Hz and 3Hz. This is amplified by a high gain common emitter amplifier based on Q1 and then by a non-inverting operational amplifier circuit built around IC2. These provide a total gain of around 70dB which gives an output signal of a few volts peak-to-peak when the unit is activated. Lowpass filtering is provided by C3 and C5 and this helps to minimise problems with noise.

IC3 is an operational amplifier which is connected to act as a voltage comparator. RV1 is adjusted so that it provides a reference voltage that is higher than the maximum quiescent output potential from IC3. So, under

## Passive IR Sensor

Passive infra-red alarms operate by detecting body heat and are generally accepted as being amongst the most reliable (and false-alarm free) of alarms. In fact their use is not limited to burglar alarms and they can be used as general purpose presence detectors. Possible applications include energy saving (automatic) lighting and automatic doors.

Passive infra-red detectors can be quite simple and although an optical system is required to obtain optimum performance, where only short range is required this can be dispensed with. This design is simple and cheap and suitable for

of if you build a simple actuator to drive a mechanical cable release from this unit.

Adequate performance can be obtained without having to resort to any exotic circuitry and the system can be built for quite a modest cost. The transmitter circuit is built around a CMOS 4047BE astable/monostable device. In this circuit it is connected in the free running astable (oscillator) mode with timing components R1 and C2 setting the operating frequency at around 10kHz.

The infra-red LED (LED1) is driven from an output of IC1 via an emitter follower buffer stage based on Q1. The latter is needed as IC1 is unable to provide the 100mA required to fully drive LED1. Of course, LED1 is fed with a square-wave signal and it is therefore switched off for 50% of the time. This gives an average control consumption of about 50mA.

The LD274 LED specified gives quite a narrow beam of light (about 20°). However, the beam is not so narrow as to make aiming the unit excessively critical and by concentrating the infra-red energy into a tighter beam a significantly improved range is obtained.

The receiver circuit uses a large area photo-diode as the sensor (D1). This is operated in the reverse bias mode, where it normally passes the low levels of leakage current associated with a

reverse biased silicon diode. The pulses of light from the transmitter cause pulses of increased leakage current through D1 giving small voltage pulses at its cathode terminal.

In fact these voltage pulses will often be bordering on the non-existent, with a peak-to-peak level that will be way under 1mV when the system is used close to maximum range. A vast amount of amplification is therefore needed to bring the signal up to a level that can operate a relay.

Three stages of AC amplification are included, and these are all common emitter amplifiers. Q1 and Q3 are both operated at full gain and provide over 40dB of voltage gain but Q2 has a lower level of gain due to the local negative feedback provided by R6.

This reduction in gain is needed in order to avoid problems with excessive noise or instability due to stray feedback. The minor amount of high frequency roll-off provided by C5 also helps to combat noise and instability.


The amplified output signal is rectified and smoothed to produce a positive DC signal. This switches on Q4 and activates the relay. Of course, this only happens if SW1 at the receiver is closed and the infra-red pulses are being transmitted. In their absence only noise is fed to the rectifier circuit and this generates a DC signal that cannot switch on Q4.

So the relay contacts switch on and off in sympathy with SW1 at the transmitter. A pair of normally open relay contacts are used to activate the camera.

When constructing the unit keep in mind that the 4047 is a CMOS device and so requires the standard CMOS handling precautions. The component layout for the receiver needs to be designed carefully as there is a lot of gain from the base of Q1 to the collector of Q3 and instability is likely if there are any easy paths for stray feedback. If necessary, R6 can be made slightly higher in value in order to ease this problem. On the other hand, with a well designed layout it would probably be possible to make R6 lower in value, which would give increased gain and operating range.

The relay can be any type having a coil resistance of about 180R or more that will work reliably on a nominal 9V supply. Obviously it must also have at least one set of normally open contacts rated at 2A (or more) at 12V DC.

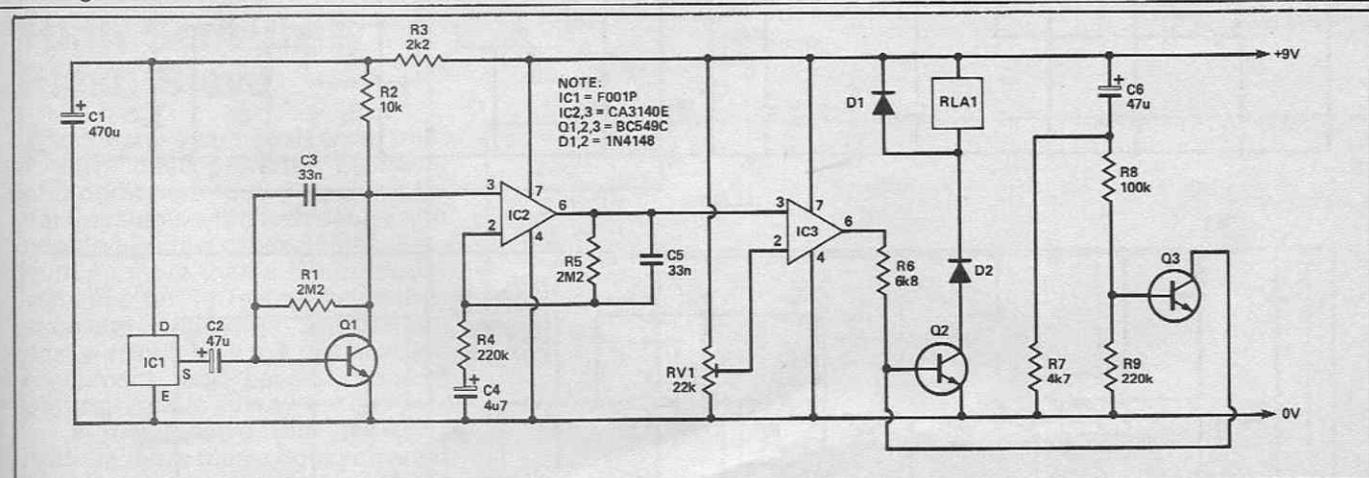Connection from the receiver to the camera might prove to be a little difficult as a suitable plug to fit the camera or winder is unlikely to be an off-the-shelf item. Probably the easiest solution is to obtain an electric cable release and then to remove the push button switch and connect the relay contacts in its place.



stand-by conditions the output of IC3 is in the low state and both Q2 and the relay are switched off.

When the unit is activated, the

output voltage of IC2 swings well outside its normal limits and on positive excursions it goes above the reference voltage. IC3's output

then goes high, Q2 is switched on and the relay is activated.

As the circuit stands it does not incorporate latching. If this feature

is required it is merely a matter of connecting a spare set of normally open relay contacts across the collector and emitter terminals of TR2.

One slight problem with the basic circuit is that it takes a few seconds for the capacitors to settle down to their normal working charges after switch-on. During a substantial proportion of this time the relay will be activated. In some applications this might be no more than a minor inconvenience, but in others it could make the unit virtually impossible.

To overcome this problem a simple timer circuit based on Q3 is

used to short circuit the base of Q2 to the negative supply rail for about 20 seconds after switch-on, so that the initial triggering of the relay is avoided.

Construction is in most respects quite easy but IC1 does provide a slight problem. It has quite a wide angle of view, and it will only respond to changes in the detected infra-red level. This gives rather poor sensitivity to anything moving across its field of view at anything less than about 60mph!

Much improved results are obtained by adding a special lens or a grating in front of it, so as to give alternative blind spots and

areas of high sensitivity. As someone crosses in front of the unit they move continuously from sensitive zones to blind spots and back again, generating a strong output from the sensor.

A simple grating made by cutting a few slits in a piece of cardboard is sufficient to give a range of up to about 3 metres, which is adequate for many purposes.

The relay can be any type that has a coil resistance of about 200R or more, will operate reliably from a nominal 9V supply and has sufficient contacts of adequate rating for the application.

## Fibre Optic Link

Fibre optics is one of those technical innovations that seems to be forever about to revolutionise the world but never quite makes it! The years of development do now seem to be paying dividends and fibre optic communications links are a reality at last. Fibre optic cables and components are available to the home constructor at reasonable prices and represent an interesting line of experimentation.

The main appeal of an audio link based on this technology is its novelty value but there are advantages to an optical link. There is no radiation of electrical


signals from the connecting cable and there is complete immunity to electrical pick up in the cable. A lack of problems with earth loops is also helpful but the potential ultra-wide bandwidth is obviously of little value in a simple audio link.

Although extremely simple, this audio link offers quite reasonable performance with low levels of noise and distortion. It has only been tried with a cable 6m long but good results over a somewhat longer range should be possible. However, even good quality fibre optic cable has relatively high losses and a system of this type is

unsuitable for communication over long distances.

Good results can be obtained using a simple amplitude modulation (AM) circuit but some form of pulsed system is needed for optimum results. Any lack of linearity through the photocells is then rendered irrelevant and has no effect whatever on the linearity of the system. This is determined primarily by the linearity of the modulator and demodulator circuits.

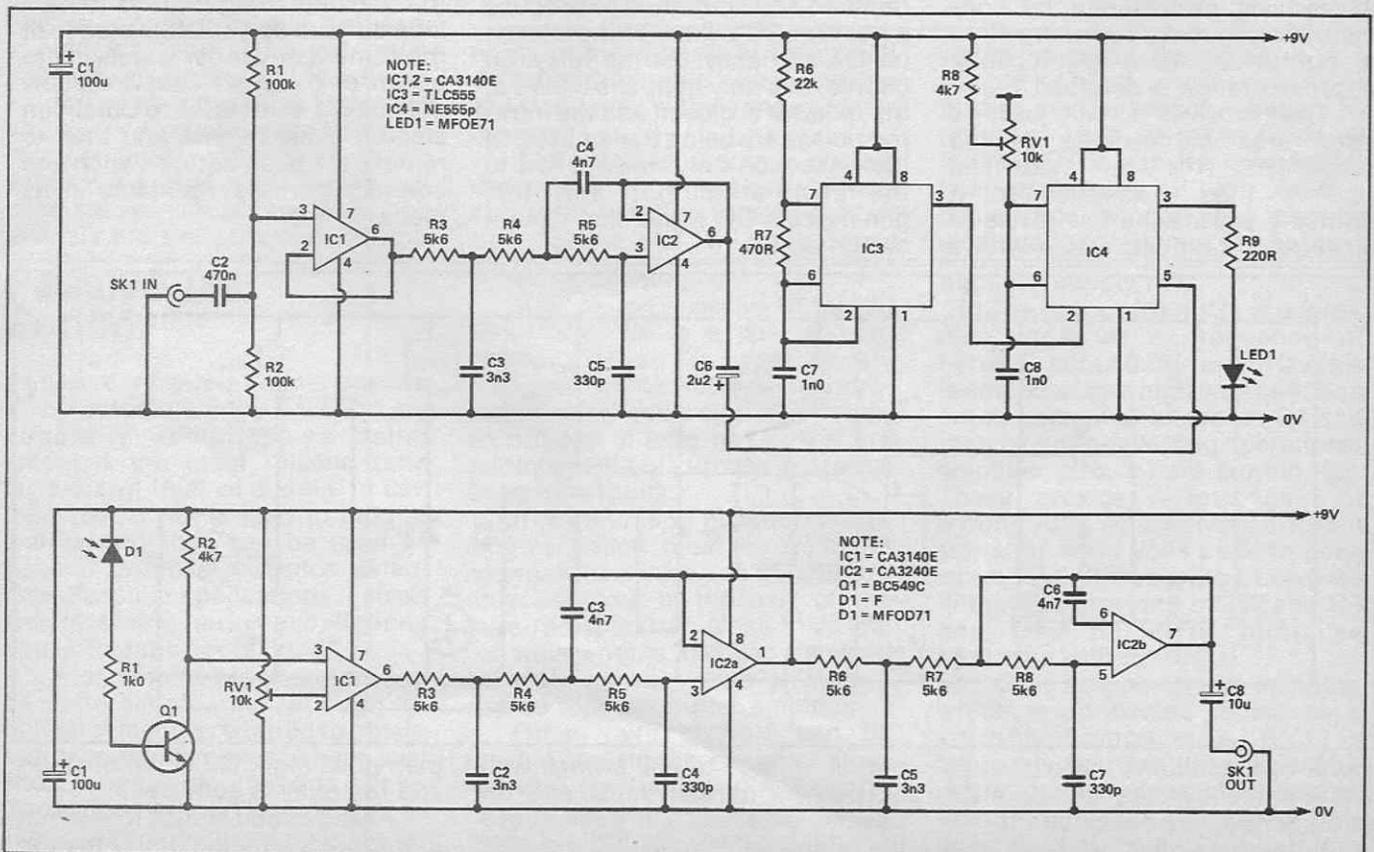Both frequency modulation (FM) and pulse width modulation (PWM) can be used to good effect



in this application and this system utilises PWM.

The transmitter is based on two 555s, with one (IC3) acting as a clock oscillator and the other (IC4) operating in the monostable mode. The 555 works well in PWM circuits and this is actually one of the tasks for which it is was originally designed. However, this seems to be a facet of the device which is little used in practical published designs.

The clock oscillator must operate at a frequency well above the maximum input frequency and in this case an operating frequency of around 50kHz is used.

In order to trigger IC4 a series of short negative pulses are required and a suitable output waveform is obtained by making R7 very low in comparison to the value of R6. RV1 is adjusted so that with no output signal there is a 1:1 mark:space ratio on the output signal from IC4. This gives an average output voltage.

By modulating the voltage at pin 5 of the device the mark:space ratio (and hence the average output voltage) can be varied. There is a linear relationship between the input and average output voltages.

The output signal drives an LED but the suggested type is one which is specifically designed for fibre optic applications. It is quite ordinary from the electronic point of view but physically it is designed to efficiently couple its light output into a narrow optical fibre, and it has a built-in connector which can be used to lock a standard 1mm fibre optic cable in position.

At the input of the unit there is a buffer amplifier based on IC1

which gives the unit an input impedance of about 50k. This is followed by a third order lowpass filter having a cutoff frequency at just under 20kHz. This removes any high frequency signals on the input which could otherwise cause heterodyne whistles or other problems if they were to reach the modulator stage.

The receiver must first recover the PWM signal with the mark:space ratio intact and then some lowpass filtering is all that is required to produce a properly demodulated output signal. Remember that the average voltage of the signal is proportional to the input voltage. Lowpass filtering integrates the output pulses to give a voltage equal to the average level of the signal.

D1 is the receiving photocell and this is the complementary device to the LED used in the transmitter. Like this LED, it couples efficiently to the fibre optic cable and includes a sort of screw gland coupling arrangement which holds the cable firmly in place. Normally it passes an insignificant current but the pulses of light from the cable cause pulses of increased leakage current to flow through the device.

These pulses are amplified by common emitter amplifier Q1 but the signal at its collector is not an accurate replica of the transmitter's output signal. However, a simple trigger circuit based on IC1 is all that is needed in order to restore the original wave shape. RV1 is adjusted to give a 1:1 mark:space ratio from the unit under quiescent conditions.

The low pass filter consists of two third-order filters connected in

series, giving a total attenuation rate of 36dB per octave. This gives an output having a reasonably low carrier content but a third filter block can be added if a really low ripple level on the output signal is essential.

Construction of the two units is mainly quite straightforward, but bear in mind that the CA3140E and CA3240E devices are both MOS input types. They consequently require the standard anti-static handling precautions to be observed.

The only unusual aspect of construction is dealing with the fibre optic cable. Avoid bending the cable through a tight radius as this can damage the filament and reduce light transmission.


The end of the cable must be prepared by first cutting the ends at right angles using a sharp modelling knife. Provided each cut is made in a single movement this should give surfaces that efficiently transmit and receive light, without any polishing being required. Next a few millimetres of the cladding are carefully removed from each end of the cable, again using a sharp modelling knife. To fix the cable to one of the opto devices, slacken off the screw terminal, push the end of the cable fully into the aperture, and then tighten the screw terminal. Do not tighten the terminal any more than is really necessary in order to securely hold the cable in place.

The system is designed to handle high level signals of around 3V peak-to-peak. Using a much lower level will give a reduced signal to noise ratio, while going much beyond this level will result in severe distortion.
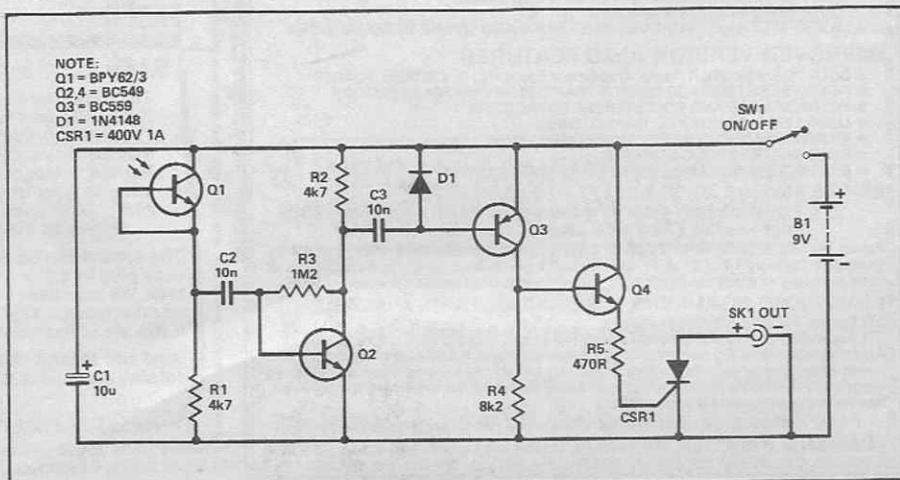
## High Sensitivity Flash Slave

For many years flash slave units have been preferred by many photographers to wiring up multi-flash systems with flash cables and adapters. A few cables might seem nothing more than a minor inconvenience but in reality they act as excellent trip-wires which can easily result in a lot of damaged equipment (and possibly injured photographers as well!)

A flash slave unit is really nothing more than a light activated switch. It senses the pulse of light from the main flashgun (normally on or near the camera) and triggers a second flashgun. If more than two flashguns are needed, it is



merely necessary to have a slave unit for each secondary flashgun.

In this way it is possible to have quite complex flash lighting arrangements that are completely devoid of any connecting cables.

Although a flash slave unit is just a light activated switch, to work well it must have suitable characteristics. In particular, it must operate very fast. With the shutter set to the fastest flash synchronisation speed and a powerful gun in use, the shutter may not stay fully open for much longer than the flash duration. A reasonably fast form of photocell must be used and a solid state switching device at the output is definitely preferable to a relay.

To work well the unit should also have high sensitivity and operate over a wide range of ambient light levels.

This circuit uses a photo-transistor as the detector together with a thyristor as the output device and these ensure a fast response time. Some flash slave units avoid the need for a battery by either using a photosensitive thyristor, or extracting power from the flashgun. This circuit was designed

primarily with high performance and reliability in mind and it was decided to opt for a battery supply rather than to compromise with a so-called 'self-powered' circuit.

The higher than average sensitivity is obtained by using a comparatively large gain in the circuit but with AC coupling to minimise any problems with the unit saturating under bright conditions.

Q1 is the photo-transistor and it is connected in the emitter follower mode. Its base is tied to its emitter, which gives lower sensitivity than if it was to be given a small forward bias or just left unconnected. However, the overall sensitivity of the circuit is still excellent and the relatively low sensitivity of Q1 itself gives good immunity to the unit being saturated in high ambient light levels.

When Q1 detects a pulse of light from the primary flashgun, this causes a small increase in its leakage current. This in turn results in an increase in its emitter voltage and this signal is coupled by C2 to the input of a common emitter amplifier based on Q2. Here it is substantially amplified and the

strong negative pulse this produces is coupled by C3 to the base of Q3 which is switched on, supplying a trigger current to CSR1 via emitter follower buffer stage Q4 and current limiting resistor R5.


The thyristor is driven with a gate current of nearly 20 milliamps and even inexpensive, insensitive types should work well in this circuit (R5 can be reduced in value if necessary).

The unit will only work properly if the flashgun is connected to CSR1 with the polarity shown in the circuit diagram. The 'suck it and see' method can be used to find the correct polarity if you do not have a multimeter (note that the voltage on the flashlead is quite high — 175V).

If a miniature coaxial socket for SK1 cannot be obtained, a socket and short length of cable cut from a flash extension lead can be used here. The unit is very sensitive but there must still be a reasonably effective path for the light from the main gun to reach Q1. Aiming Q1 straight at the main flashgun is not usually necessary, reflected light is generally sufficient to give reliable operation.

**ETI**

## AUDIOKITS PRECISION COMPONENTS

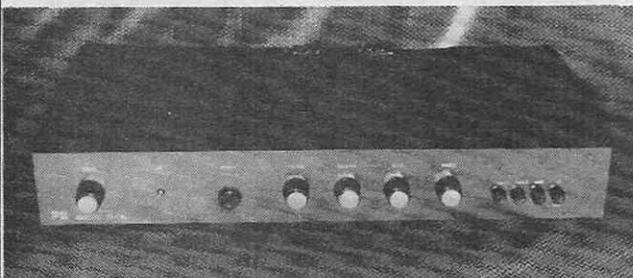

### THE 30+30 INTEGRATED AMPLIFIER

- ★ DESIGNED FOR OUTSTANDING SOUND QUALITY
- ★ VERY HIGH QUALITY COMPONENTS SUPPLIED
- ★ LOW TEMPERATURE GENERATED DISTORTION
- ★ ULTRA LOW NOISE MC STAGE
- ★ STAR EARTHING - MAPPED ON PCB TRACKS
- ★ CLEAN SOUND RIGHT UP TO FULL OUTPUT
- ★ 7 SEPARATELY RECTIFIED POWER SUPPLIES GIVES OUTSTANDING STEREO IMAGERY
- ★ LATEST KITS HAVE IMPROVED HEAT SINKS AND LOWER RESIDUAL NOISE

### IMPROVED VERSION ALSO FEATURES

- ★ BULK FOIL RESISTOR (Temp. Coefficient 5ppm/°C) IN CRITICAL PLACES
- ★ HOLCO RESISTORS FOR OUTPUT TRANSISTOR EMITTER RESISTORS
- ★ POLYPROPYLENE AND POLYSTYRENE CAPACITORS
- ★ LONG LIFE ELECTROLYTIC CAPACITORS
- ★ KIMBER CABLE FOR INTERVAL WIRING
- ★ GOLD PLATED PHONO SOCKETS
- ★ EXTRA OUTPUT TRANSISTORS FOR 40 WATT OUTPUT

**PRICES** Standard 30+30 kit £172 + £6 p&p = £178  
Standard with extra o/p transistors £185 + £6 p&p = £191  
Improved kit £380 + £6 p&p = £386

Export version to order with 110V or 220V primary transformers. P&P charges by quotation. Delivery 14 to 21 days, but can be longer as lead times for manufacture of case or supply of some top quality parts used in improved version is much greater.

**ETI VIRTUOSO PREAMP KITS, PCB'S AND ALL PARTS AVAILABLE.**

ETI System A Preamp & Power Amp  
ETI Audio Design Preamp & Power Amp

Amazing how many ETI readers are still building system A and Audio Design pre and power amps, many years later. Most are using higher grade parts recommended and supplied by Audio Kits and enjoying much better sound quality than the original design. Special parts list available on request.

For details of Audio Kits components and kits, please send SAE (9" x 4") (overseas 3 IRCs) to:


**AUDIOKITS, 6 Mill Close, Borrowash, Derby DE7 3GU. Tel: 0332 674929**

## Interak 1
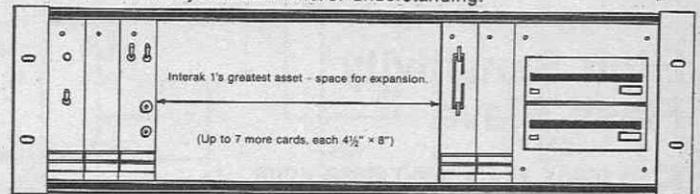
### AN EXPANDABLE DISK-BASED Z80A DEVELOPMENT SYSTEM YOU CAN BUILD YOURSELF!

Universities, Colleges, Industry, Enthusiasts:

Unlike home computers, development systems have entirely "open" architectures, use standard TTL etc. chips (ie no ULA's!), and are built in a proper engineering fashion. Usually these superior products carry a correspondingly superior price tag, but you can build Interak yourself board by board and thus afford a system which would normally be out of your reach and/or understanding.



64K CPU | 64K DRAM | 64 x 24 | 100" | YOUR OWN EXPANSION (EG. SPEECH, SOUND, EPROM, PRINTER, MODEM, TAPE, RELAY, CONTROL, INTERFACING, ETC. ETC.) | ASCII ASCII | ASCII ASCII | 2 x 1 MBYTE 3 1/2" DISKS (EXAMPLE)

The initial development system has 64K of RAM, a 4 MHz Z80A CPU, parallel ASCII keyboard interface, VDU Interface (TV set or monitor), and a floppy disk drive interface for up to 4 drives. Any size (including 8" double density) can be used, but our 1 Megabyte 3.5" drives are proving very popular because they can fit into the system rack, (and they only cost £94.00 each + VAT). CP/M Plus is available, giving access to thousands of "public domain" programs.

The system can be described as "future proof" because it uses plug in 4.5" x 8" cards in an industrial quality 19" 3U rack. We have been established since 1970, and this system was first made in 1977 so (unlike almost all other computers) it has stood the test of time.

Send two second class stamps, or telephone for a detailed descriptive leaflet, specification, prices, etc.

### Greenbank

Greenbank Electronics (Dept. T2E), 460 New Chester Road, Rock Ferry, Birkenhead, Merseyside L42 2AE.

Tel: 051-645 3391

# SPECIAL OFFER...

## ALTAI DIGITAL MULTIMETER £49.95 plus V.A.T.

- ★ Full 3½ digit multimeter—0.25% basic accuracy, 10A a.c./d.c.
- ★ Temperature measurement
- ★ Capacitance measurement—up to 20µF.
- ★ Transistor gain measurement

THE Altai HC-5010EC digital multimeter features a 0.5 inch 3½ digit l.c.d. display with polarity, low battery and overrange indication. The meter gives 200 hours typical battery life with a 9V alkaline battery.

The meter has a tilt stand built in, measures just 170 x 87 x 42mm and weighs 382gms. It is provided with an operator's manual, test leads, with extra screw-on insulated crock clip connectors, and a plug-in thermocouple for temperature measurement.



CONDUCTANCE	RESOLUTION	ACCURACY
200nS	0.1nS	±(1.5% rdg+10d)
CAPACITANCE	RESOLUTION	ACCURACY
2000pF	1pF	±(1.5 % F.S.+5d)
2µF	0.001µF	±(2 % F.S.+5d)
20µF	0.01 µF	±(2 % F.S.+5d)

hFE TEST Test condition: 10µA 2.8V. hFE gain 0-1000 (npn. pnp).

Post to: Meter Offer, B.K. Electronics,  
Unit 5, Comet Way, Southend-on-Sea,  
Essex SS2 6TR. Tel: 0702 527572

D.C. VOLTAGE	RESOLUTION	ACCURACY
200mV	100µV	±(0.25% of reading + 1 digit)
2V	1mV	
20V	10mV	
200V	100mV	
1000V	1V	

Input Impedance: 10M on all ranges. Overload Protection: 1000V d.c. or peak on all ranges.

D.C. CURRENT	RESOLUTION	ACCURACY	MAX. F.S. VOLTAGE DROP
200µA	100nA	±(0.5 % rdg+1d)	0.25V
2mA	1µA	±(0.5 % rdg+1d)	0.25V
20mA	10µA	±(0.5 % rdg+1d)	0.25V
200mA	100µA	±(0.75% rdg+1d)	0.25V
2000mA	1mA	±(2 % rdg+5d)	0.75V
10A	10mA	±(2 % rdg+5d)	0.30V

Overload Protection: mA Input: 2A/250V fuse. 10A Input: Unfused up to 15A for 15 seconds.

A.C. VOLTAGE	RESOLUTION	ACCURACY	FREQ RANGE
200mV	100µV	±(0.5% rdg+5d) on all ranges	45Hz-500Hz on all ranges
2V	1mV		
20V	10mV		
200V	100mV		
750V	1V		

Conversion: Calibrated for rms of sine wave. Input Impedance: 10M shunted by 100pF on all ranges except 200mV range. Overload Protection: 1000V d.c. or 750V r.m.s. a.c. continuous, except 15 sec max above 300V on 200mV range.

A.C. CURRENT	RESOLUTION	ACCURACY	MAX. F.S. VOLTAGE DROP
200µA	100nA	±(0.75% rdg+5d)	0.25V rms
2mA	1µA	±(0.75% rdg+5d)	0.25V rms
20mA	10µA	±(0.75% rdg+5d)	0.25V rms
200mA	100µA	±(0.75% rdg+5d)	0.25V rms
2000mA	1mA	±(2 % rdg+5d)	0.75V rms
10A	10mA	±(2 % rdg+5d)	0.30V rms

Overload Protection: mA Input: 2A/250V fuse. 10A Input: Unfused up to 15A for 15 seconds.

RESISTANCE	RESOLUTION	ACCURACY	MAX. OPEN CIRCUIT V
200Ω	100mΩ	±(0.5 % rdg+3d)	2.8V
2KΩ	1Ω	±(0.3 % rdg+1d)	2.8V
20KΩ	10Ω	±(0.3 % rdg+3d)	500mV
200KΩ	100Ω	±(0.3 % rdg+3d)	500mV
2MΩ	1KΩ	±(0.75% rdg+5d)	500mV
20MΩ	10KΩ	±(3 % rdg+5d)	500mV

Max allowable input: 500V d.c. or rms.

### CONTINUITY TEST

Resistance range: Buzzer sounds at approximately less than 200Ω.

### DIODE TEST

Test voltage: 2.8 Volts. Maximum test current: 3mA.

TEMPERATURE	RESOLUTION	ACCURACY
-20°C to 1370°C	1°C	±(3+1d) up to 150°C ±3% of rdg over 150°C

Sensor: Type K (NiCr-NiAl).

Please complete the coupon in BLOCK CAPITALS

Please supply

Quantity	Item	Value
	Altai Digital Multimeters at £57.44 each (including VAT and postage)	£
<b>Total</b>		£

Visa/Access or Cheque No. ....  
 Signature.....  
 Name.....  
 Address.....  
 .....  
 .....  
 .....

**WE CAN ACCEPT VISA AND ACCESS ORDER BY TELEPHONE**

**Post to: Meter Offer, B.K. Electronics,  
 Unit 5, Comet Way, Southend-on-Sea,  
 Essex SS2 6TR. Tel: 0702 527572**

# BACK NUMBERS

- Missed part one of your favourite project?
- Lost that all-important article on circuit design?
- Desperately need that Tech Tip to get your latest masterpiece going?
- Pining for that one issue to complete your valuable collection?

**ETI Backnumbers Department  
to the rescue!**

Please note that backnumbers are only held for 12 months. Articles published previous to this must be obtained through our photocopy service.

# PHOTO-COPIES

ETI has been published for over 15 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 months issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

Please supply the following backnumbers of ETI.  
Note: Backnumbers are held for 12 months only  
(complete in block capitals)

Month ..... Year ..... Month ..... Year .....

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.90 per issue ordered.

Total remittance £ ..... Date .....

Name .....

Address .....

..... Postcode .....

Send the completed form and your remittance to:

**ETI Backnumbers Department  
Infonet Ltd.  
5 River Park Estate  
Berkhamsted  
Herts HP4 1HL**



Please supply photocopies of the following articles from ETI (complete in block capitals):

Month ..... Year ..... Page (if known) .....

Title .....

Month ..... Year ..... Page (if known) .....

Title .....

Month ..... Year ..... Page (if known) .....

Title .....

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ ..... Date .....

Name .....

Address .....

..... Postcode .....

Send the completed form and your remittance to:

**ETI Photocopy Service  
ASP Readers' Service  
9 Hall Road  
Hemel Hempstead HP2 7BH**



# 2 issues FREE

When you take out a subscription to any of these magazines

	EUROPE	MIDDLE EAST	FAR EAST	REST OF THE WORLD
A&B Computing	£27.30	£27.60	£31.10	£28.30
Aeromodeller	£27.00	£27.20	£29.00	£27.50
Citizens Band	£20.10	£20.30	£21.80	£20.50
Clocks	£32.40	£32.60	£34.70	£33.00
Commodore Disk User	£18.00	£18.20	£19.30	£18.40
Disk User	£21.60	£21.70	£23.20	£22.00
Electronics Digest	£12.90	£13.00	£13.70	£13.10
Electronics Today International	£21.00	£21.20	£22.80	£21.50
Ham Radio Today	£20.10	£20.30	£22.00	£20.60
Military Modelling	£22.40	£22.60	£25.20	£23.10
Model Boats	£20.00	£20.10	£21.80	£20.40
Model Engineer	£35.40	£35.70	£39.00	£36.30
Photography	£22.00	£22.30	£25.00	£22.80
Photoplay	£16.70	£16.90	£18.70	£17.20
Popular Crafts	£21.40	£21.60	£23.60	£22.00
Radio Control Model Cars	£21.10	£21.30	£23.10	£21.60
Radio Control Boat Modeller	£10.00	£10.20	£11.10	£10.30
RCM&E	£20.40	£20.60	£22.90	£21.00
Radio Control Scale Aircraft Quarterly	£11.10	£11.20	£12.00	£11.30
Radio Modeller	£20.00	£20.20	£22.40	£20.60
Sea Classic International	£10.70	£10.80	£12.00	£11.00
Scale Models International	£19.60	£19.80	£21.50	£20.10
Video Today	£20.20	£20.40	£22.30	£20.70
Which Video?	£19.40	£19.50	£21.20	£19.80
Woodworker	£22.80	£23.00	£25.70	£23.50
Your Commodore	£22.00	£22.30	£25.20	£22.80
Model Railways	£19.10	£19.30	£21.50	£19.70
Practical Wargamer	£7.10	£7.20	£8.00	£7.40

## The Above Offer Applies to Overseas Subscriptions Only

This offer is also open to existing subscribers who may wish to extend their current subscriptions.

Please commence my subscription(s) To..... with the..... Issue  
 I enclose my cheque/money order for £..... made payable to Argus Specialist Publications Ltd.  
 or debit £..... from my Access/Barclaycard No.   
 valid from..... to..... Signature.....  
 Name.....  
 Address.....



Send this form with your remittance to:

INFONET LTD. (S.O. 88) 5 River Park Estate,  
 Berkhamsted, Herts. HP4 1HL.



**For KITS & COMPONENTS -**  
**Choose the easy way - with**

**Send 50p\* & SAE for CATALOGUE (AUTUMN 1987)**

\*refundable with first order

**ORDERS: RING (01) 567 8910 - 24 HRS.**



**NEW ELECTRONIC GUARD DOG KIT**



One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains supply, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.

**KK125 Complete kit of parts £21.95**

**DISCO LIGHTING KITS**

**DL1000K** - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel.....**£17.50**

**DLZ1000K** - A lower cost uni-directional version of the above. Zero switching to reduce interference.....**£9.95**

**DLA/1** (for DL & DLZ1000K) Optional opto input allowing audio 'beat' /light response.....**70p**  
**DL3000K** - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel**£14.25**

The **DL8000K** is an 8-way sequencer kit built with in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80! different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED timing lamps and sound to light LED and a 300 W output per channel.

And the best thing about it is the price.

**ONLY £28.50**



**TEN EXCITING PROJECTS FOR BEGINNERS**

This Kit has been specially designed for the beginner and contains a **SOLDERLESS BREADBOARD, COMPONENTS**, and a **BOOKLET** with instructions to enable the absolute novice to build TEN fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

**ORDER NO XK118 £13.75**

**MICROPROCESSOR TIMER KIT**

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box, 18 time settings.



**CT6000K**.....**£42.90**  
**KK114** Relay kit for CT6000, includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts. **£4.30**  
**701 115** Additional relays.....**£1.80**

**VERSATILE REMOTE CONTROL KIT**



This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the **MK18** which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - **MK9** (4-way) and **MK10** (16-way), depending on the number of outputs to be used.

**MK12** IR Receiver (incl. transformer) **£14.85**  
**MK18** Transmitter.....**£7.50**  
**MK9** 4-Way Keyboard.....**£2.00**  
**MK10** 16-Way Keyboard.....**£5.95**  
**601 133** Box for Transmitter.....**£2.60**

**HOME LIGHTING KITS**

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.

**TDR300K** Remote Control Dimmer **£16.45**  
**MK6** Transmitter for above **£4.95**  
**TD300K** Touchdimmer **£8.50**  
**TS300K** Touchswitch **£8.50**  
**TDE/K** Extension kit for 2-way switching for TD300K **£2.70**  
**LD 300K** Light Dimmer **£4.35**

**NEW POWER STROBE KIT**

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Ws strobe tube and full assembly instructions. Supply: 240V ac. Size: 80 x 50 x 45.

**NEW POWER STROBE KIT £12.50**  
**DVM/ULTRA SENSITIVE THERMOMETER KIT**

Based on the ICL 7126 and a 3/4 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches required - details supplied) or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP3) **£17.00**

**KK113 MW RADIO KIT**  
 Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. **IDEAL FOR BEGINNERS £6.00**

**PROPORTIONAL TEMPERATURE CONTROLLER KIT**

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max. load 3kw (240V ac) Temp. range up to 90°C. Size: 7x4x2.5cms. **MK4 £7.10**

**BARGAIN COMPONENT PACKS**  
 Refill those empty component drawers at a fraction of the normal price and don't be caught without that odd resistor or capacitor to complete your project. All components supplied are to full spec. and are not seconds or surplus stock.

**Pack A:** 650 x .25 watt resistor 47R-10M **£4.25**  
**Pack B:** 60 x Radial electrolytics 1uf - 1000uf **£3.25**  
**Pack C:** 30 x Polyester capacitors a or 0.01 uf - 1uf **£4.50**  
**Pack D:** 35 x horizontal presets 1k-1M **£3.00**  
**Pack E:** 30 x IC sockets 8, 14, 16 pin **£2.00**  
**Pack F:** 25 x Red 5mm LEDs **£1.75**  
**Pack G:** 25 x Green 5mm LEDs **£2.00**  
**Pack H:** 30 x 5mm LEDs 10 Red, 10 Green, 10 Yellow **£2.50**  
**Pack J:** 50 x 1n 4148 silicon diodes **£1.00**  
**Pack K:** 40 x npn/ppn transistors BC/182/212 General Purpose **£2.25**

Free Solderless Breadboard (verobloc type). When you buy all ten packs. Prices exclude VAT (15%).

**TOOLS ★ TOOLS ★ TOOLS**

Good quality tools selected to offer outstanding value for money.

**650 004** 6in mini. Snipe Nose Pliers. Serrated jaws and return spring. **£2.10**  
**650 005** 6in lap jointed side cutters. Insulated handles and return spring. **£2.10**  
**650 006** Light duty cutters. Cutting capacity 0.22-1.2mm copper wire. **£1.80**

**TOOL KIT** - Contains: side cutters, snipe nose pliers, wire strippers, flat blade screwdriver, Phillips screwdriver in black textured, reinforced and padded case which when opened out measures 240x205mm **£6.80**

**650 007** Self-adjustable automatic wire stripper with built-in cable cutter. **£3.95**  
**650 012** Watchmakers Screwdriver Set. 1.0/1.4/2.0/2.4/3.0/3.8mm **£1.75**  
**650 019** Set of 4 Stainless Steel Tweezers. Straight nosed, straight nosed-reverse action, bent nosed, flat nosed. 110mm long. **£3.85**  
**650 502** Reliant 9-12V dc Drill. **£6.90**  
**650 500** Titan 12V dc Drill. **£10.25**  
**650 570** Saturn Mains Drill. **£16.50**

**WE ALSO STOCK ANTEX IRONS AND ACCESSORIES**

**NOT JUST A MULTIMETER**

A professional quality 3 1/2 digit multimeter with 34 ranges. As well as the usual current, voltage & resistance this meter features transistor and diode test, continuity AND CAPACITANCE and TEMPERATURE ranges. Basic accuracy is 0.25%. Size: 170x87x42mm. Includes test leads, thermocouple and full instruction & recalibration manual.

AC Volts .....200m-2-20-200-750  
 DC Volts .....20m-2-20-200-1KV  
 AC Current .....200u-2m-20m-200m-2A-10A  
 DC Current:200u-2m-20m-200m-2A-10A  
 Resistance .....200-2K-20K-200K-2M-20M  
 Capacitance .....2000p-2uF-20uF  
 Temperature .....-10° to 1370° C  
 Conductance .....200nS  
 hFE .....0-1000 (NPN & PNP)  
 Continuity Buzzer .....less than 200 ohms (405208) **£55.00**

**LOGIC PROBE**

A MUST for working with TTL & CMOS devices. Displays logic levels and pulses down to 25nS with LEDs and sound. Comprehensive instruction booklet supplied.

Working voltage 4-16V dc  
 Input Impedance 1M  
 Max. i/p frequency 20MHz

**ONLY £9.50**

**RECHARGEABLE SOLDERING IRON**

Powerful cordless iron complete with table-top/wall-mounting charging bracket. Reaches soldering temperature in 10 seconds. Includes lamp which lights when soldering. Comes with mains charging unit and 12V car battery adaptor. **Special Offer £15.95**

**ELECTRONIC WEIGHING SCALES**

This kit contains a Single Chip Microprocessor, PCB, displays and all electronics to produce a digital readout of weight in Kgs, or Sts, and Lbs. In normal use a toothed wheel (pattern provided) is made to rotate when a weight is placed onto the scales, interrupting two infra-red beams. The processor counts the number of teeth passing the sensor (up or down, depending on which beam is broken first) and shows the reading on the LED display in Sts, & Lbs., Lbs. or Kgs. A PCB link selects the scale for bathroom or two types of Kitchen Scales. A linear version of the toothed wheel could also be used. Other uses include up/down counters. A low cost digital ruler could be made by using a wheel with the correct tooth to diameter ratio. **£5.50**

**SECURITY PRODUCTS**

Install your own burglar alarm and save pounds. All parts available separately.

- 950 120 Stair Pressure Mat **1.70**
  - 950 125 Floor Mat 29x16 ins. **2.60**
  - 950 130 External bell box - an ideal deterrent on its own! **10.00**
  - 950 130 Xenon Beacon (12v) **10.50**
  - 950 140 Flush door/window contacts **1.22**
  - 950 143 Surface mounting contacts **1.05**
  - 960 160 Alarm Control Unit **4737**
  - 950 162 Alarm Control Unit
- This unit incorporates all the features required to form the basis of a complete security system for the home or business. Operating off a 240v AC supply with facility to charge a 12v lead acid standby battery. The unit is housed in a white steel box 225x225x80mm. Full instructions supplied to connect normally open and closed sensors, bells, personal alarms etc. Separate entry and exit alarm delays. 2 zone operation complies with BS price **£39.95**
- 950170 DOOR PHONE**  
 An attractively styled 2 station mains powered handset type door phone. Allowing conversation with visitors without opening the door. Free standing or wall mounted, connections to a 9volt battery for standby. Electric doorlock release button which may be used with our 701150 lock release mechanism. Ivory and Fawn body 210x100x70mm. **£27.95**

**TR ELECTRONICS**  
**13 BOSTON RD**  
**LONDON W7 3SJ**  
**Tel: 01-567 8910**




**SEND 9"x6" S.A.E. & 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5pm SATURDAY 10-4pm**

**ORDERING INFORMATION: ALL PRICES EXCLUDE VAT**

**FREE P&P** on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

**LOCAL AUTHORITY AND EXPORT ORDERS WELCOME GOODS BY RETURN SUBJECT TO AVAILABILITY**

# TOKYO AUDIO FAIR

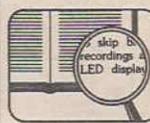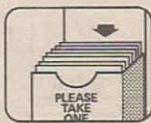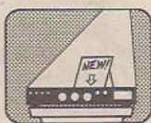

At about the same time Ian Pitt was exercising his sexual frustrations at the Heathrow Penta Show in the UK, several disgruntled journalists had just arrived at Narita Airport to learn that their luggage had been left in the good old USSR.

Perhaps we had got out of the wrong side of the plane but this was not the most impressive introduction to the hectic delights of Japan. Later that afternoon we engaged in a running battle with a myriad of oriental shop assistants in a vain attempt to procure clean shirts, underwear and the like — despite the raving gesticulations of our party, they simply failed to understand that it really did not matter if the shirts were too small.

This accomplished, we struggled out of our hotel in ill-fitting garb to descend upon the Japanese equivalent of Pizzaland only to pass our luggage going the other way. Having broken down much of our party's resilience we were finally reunited with our cases just in time to change for an assault on the dreaded Tokyo Audio Fair.


This annual event is actually housed in two extremely large venues which looked for all the world like a couple of disused aircraft hangers. Nevertheless, the bustling hordes seemed more interested in the vast quantities of gadgetry than the dubious acoustics presented by this man-made cavern.

Although there were peripheral exhibitions of 'tweaky' high-end audio gear, it has to be said that the bulk of the show was concerned with the latest in digital and video technology — CD, CDV, high-definition VCR's and DAT machines of every description filled the arena. The contrast with Heathrow's Penta Show could not have been greater.

Our hosts, Sony, were demonstrating their DTC-1000ES DAT player by allowing groups of visitors to actually make their own recordings of a live music session. Meanwhile on the stand proper they were displaying an entirely new range of ESD CD players. In this country we are still oggling over their first-generation ES players such as the CDP-555ES whereas their home market is now enjoying the CDP-557ESD, 337ESD and 227ESD machines.

The top player is one of the new breed employing 'hi-Bit' DAC's offering the resolution and noise performance of 18-Bits — the price in Japan was about £750.

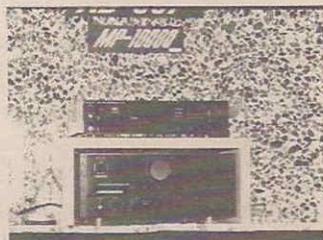Other '18-Bit' CD-players included the huge Onkyo Integra C-2001 (£1300), Technics SL-P990 and SL-P770 and Hitachi DA-703D, although how long it will be before they are competing with Yamaha in this country is anyone's guess.



Yamaha themselves were busily showing off their millionaire-budget 100000 series which includes CD-player and exotic amplification.

The latest DSP-3000 'Natural Sound' digital sound field processor was also exhibited, now including some 20 artificially replicated acoustic environments.

Technics showed their SV-D1000 home DAT player in addition to a portable unit called the RQ-MD1 and in-car player, the CQ-DT1D. The portable would still set you back £1300 in Japan.

Many more companies appeared to be dabbling with external digital to analogue converter units, either included in chunky integrated amplifiers or manufactured as add-on accessories. Accuphase (a company last seen over here with the AC-2 moving-coil cartridge displayed their DD80 CD player and optically-coupled DC81 converter. Luxman boasted a similar level of OTT construction with their 'Limited Edition' series of digital hardware and back-breaking pre/power amplifiers.

Technics revealed a pair of rather frightening planar loudspeakers with a scary price-tag to match. Costing some £10,000, the 320kg SB-AFP1000's utilised garishly blue, flat rectangular drive units to create a wall of sound — they sounded so overwhelmingly bright that I was forced to exit soon after clapping eyes (and ears) on them!



The daftest loudspeaker award must go to Sasaki Acoustics who were seriously marketing a range of single and dual-concentric loudspeaker systems based around glass-crystal spheres. They were duly christened the 'eyeball' speakers. Apparently designed for non-military purposes, Bose were demonstrating two huge drainpipes under the guise of an 'Acoustic Wave Cannon System.' The low frequency extension was considerable (25Hz) but domestic applicability was not their strong point.

Likewise for the monstrous Diatone bass drive unit that must have had a diameter of around 2m!



Any visitor who managed to frequent both the London and Tokyo shows could not have failed to experience the vast contrast between events — both cultural and electronic.

At Penta, analogue replay equipment and 'old-technology' valve gear was still reigning supreme while in Japan only Ortofon were daring to represent the black disc.

Whether the tide will turn so strongly against the revered turntable in our own marketplace is uncertain at present. However I rue the day that this ever happens — regardless of all the technological arguments I cannot help but feel detached from the antiseptic precision engendered by this new age of digital audio.

Paul Miller

# BOOKS

More and more projects in METI and other electronics magazines are (when stripped of a few external frills) little more than a microcomputer with input and output interfacing.

Although projects go some way to teaching you all there is to know about bolting bits onto microprocessors, a solid foundation in theory is also a good idea and what this month's tome provides.

**Practical Microprocessor Interfacing by S. A. Money (Collins) £20.**

The 'practical' of the title does not mean you will find ready to make projects nestling in these pages. There are no PCB designs nor even full circuits.

It is only an introduction to the subject and many ETI readers will have already passed on to greater things. Nevertheless, it is a reasonably thorough and eminently readable grounding.

The book starts with a look at CPUs and bus systems. At once the spread afforded by this book is shown. This chapter doesn't just concentrate on one processor, not even one family. All the processors you are likely to meet are here — 6802, 6809, 6502, 8085, Z80, 68000, 8086.

In a classic Von Neumann manner, memories are next. How they work and what you do with them are both covered in reasonable detail and a friendly style. Then it's theory of parallel interfacing, practical parallel interfacing, theory of serial interfacing, practical serial interfacing, counting, timing, analogue input and output and finally, a short discourse on interrupts.


The whole work is spattered with small, easily digestible part-circuit diagrams showing the relevant section of a whole system. Every aspect seems to be covered — both the fundamentals and the use of specialised chips to perform all the interfacing tasks.

The biggest lack is anything in the way of examples. It would be nice to see some 'case studies,' even of the most trivial nature.

The price is certainly over the top. Twenty quid for book (even a well produced hardback) is steep. It's a shame that the price will put off a great many potential readers no matter how much I recommend it. Catch it in your local library instead.

Malcolm Brown

## PLAYBACK

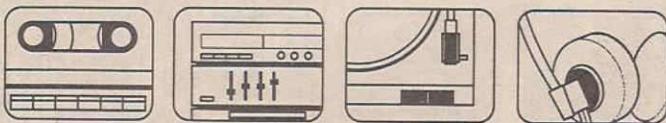

Regardless of the quality of modern electronics, a cassette recorder cannot function well unless it is mechanically sound.

The purpose of the mechanics is to move the tape in a stable, straight path past the heads at an absolutely even speed, with a moderate, even tension and at exactly 90° to the head gap.

One obvious necessary condition for all this is that every part of the mechanism should be stably positioned relative to every other part. Flimsy bits of metal supporting the tape heads and pinch wheel(s) won't do.

### Drive In

Let's start with the drive mechanism. This must use a capstan with a substantial flywheel to pull the tape through the system at an even speed and must employ precise motor control to ensure the speed is accurate.

The motor speed control system cannot control short term speed fluctuations (which is why a flywheel is essential) but it should respond rapidly to changes in average loading to cope with the varying pull from an unevenly wound tape.

If two capstans are used, they must be driven in such a way as to maintain an even tension on the tape and not either stretch it or build up a loop around the heads. This can become a serious problem.

On an old Tandberg machine, I found that if the capstans were not cleaned frequently enough, the buildup of tape oxide and dirt (faster on the first capstan than the second) increased the effective diameter of the first capstan enough to build up a self-destructive loop of tape. This machine worked well clean but it illustrates the point that a good single capstan is better than a poor dual capstan machine.

Going to the other extreme my present machine (a Nakamichi) uses two capstans of different sizes so that any resonance due to imbalance of the flywheels is at a different frequency for each capstan. This avoids low frequency beat effects which would be audible as wow and flutter. The first capstan is driven so as to pull the tape through the system a fraction of a per cent slower than the second one which provides an accurately

calculated tape tension.

While we are on the subject of the capstan drive, it should be noted that the humble pinch-wheel plays a vital role. In order that the tape shall move in a straight line, the axis of rotation of the pinch wheel must be exactly parallel to the axis of rotation of the capstan. This will avoid driving the tape to one side or another.

An easy way to find out if this is happening is to record white noise such as the interstation hiss on an FM tuner and then replay the recording with the amplifier set to mono.

If the tape is wandering (or if the head angle itself is unstable) then the timing of the signal from left and right channels will vary and this will produce phasing effects on the sound. If the sound replayed in mono is the same as that in stereo, then the mechanism is accurate and stable, which is a big step in the right direction.

### Into Reverse

Some machines boast an auto reverse facility and in some cases this involves the record/replay head turning through 180° when the tape is reversed. This can work well but the quality of the turning mechanics must be very high in order to return the head to the same position accurately.

If we assume a stereo recording takes up 40% of the total width of the tape and that to obtain good response the maximum error over this width must not exceed, say, a quarter wavelength of 15kHz, then the maximum angular error of the tape head is approximately 1½ minutes of arc.

The take up spool must also work smoothly. The tape tension must be enough to wind on the tape even if the take up reel is sticking slightly. However it must do this without stretching or dragging the tape.

If a separate motor is used for this purpose, it must provide even tension without 'cogging' and its speed must be limited so that, should it be required to take up a loop, it does not run away and snap the tape.

Critical examination of these factors will rule out many machines, leaving a choice between fewer better quality models.

Andrew Armstrong

## OPEN CHANNEL



A couple of recent happenings make it prudent to take a look to the future of telecommunications services, both here in Britain and around the world — or at least in Europe.

First, PTTs (Postal, Telephone and Telegraph) companies from some of the major European countries have started talking about the sorts of service wanted when digital telephone networks become the norm. An integrated services digital network (ISDN) can obviously be of benefit within a country. However, international ISDNs could have even greater benefits — not the least of which would be common standards. Cheaper equipment should result.

PTTs in Germany, France, Italy and Britain (BT) are beginning to combine resources with this European network aim. Eventually, any service available in one country will be available throughout all.

Second, GEC has been seen playing around with Iris!

You'll be pleased to know that Iris is the codename of a new videophone for use on digital networks. It will be available, as far as I am aware, as you read this column.

A while ago (February 1987), I reported in these very pages of research into videophone techniques, specifically about ways to reduce required bandwidth of a videophone to a low enough level to allow transmission down single digital telephone lines. It appears the research also being conducted on behalf of GEC at BT's Martlesham labs has found a way to do it. Iris allows connection to a single 64Kbit/s digital line such as will be available when ISDNs get off the ground.

### X Marks The Spot

Talking of GEC, Plessey has negotiated a significant order of System X exchanges, sold to China Railways. This follows other worldwide orders of the exchanges recently and according to Plessey it won't be the last.

However, it will probably be the last as a single company. Plessey of course is in the process of being united with GEC in a new company, GEC Plessey Telecommunications Holdings, with the aim of unifying both companies' interests.

Some 26 exchanges and con-

centrators are to be delivered by Plessey to the railway in China by 1989 — a fact which will perhaps help to allay fears that System X is a duff 'un.

China is a massive and as yet untapped potential market so even greater sales may result. Maybe the London Business School would like to reconsider its earlier muck-spreading report which criticised System X and its development by BT.

### DBS and Chips

Within a matter of weeks several announcements about chip sets for DBS receivers should be made.

RCA had announced it was in the process of producing chips at the time of writing and a joint Plessey/Philips agreement was to have chips ready by ETI's current publication date. Chip designs for both RCA and Plessey/Philips have been originally developed by Nordit, a Norwegian manufacturer, and are to be compatible with all proposed European DBS broadcasts.

All DBS broadcasts will follow the multiplexed analogue component (MAC) format but there the similarity ends. DMAC is to be used in the British DBS service, while D2MAC is to be used in German and French systems.


ITT is about to produce D2MAC-only chips which of course will not be usable for the British market. This means that European manufacturers such as Grundig, Thomson and so forth will not have a product to sell in Britain if they choose to use ITT chips. Philips, however, will!

I suspect that ITT's preliminary drive will be to produce an initial batch of chips for D2MAC purposes — giving European manufacturers what they need to make receivers for the home markets. Then ITT will turn its attention rapidly to multi-format compatible chips, so that the same manufacturers can sell into Britain.

In turn, this implies that Grundig et al will beat Philips to the European home markets but later Philips et al will beat them to the British market with a multi-format product which will undercut previous ones.

Keith Brindley

# KEYNOTES

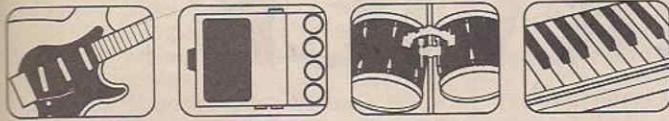

Hot gossip at the moment is that IBM and Yamaha are putting their heads together to produce an FM synth/MIDI interface plug-in card for IBM PCs, to be known as the IBM Music Feature.

IBM is keen to trample all over clone makers and will therefore be leaning hard on Yamaha to make the board as uncopiable as possible.

It is certainly becoming difficult for the home constructor to emulate the performance of the modern digital synthesiser. The problem is compounded by a heavy reliance on custom or semi-custom ICs.

Not only is it usually impossible to get hold of these proprietary ICs but it is difficult to even figure out what they do, let alone how they do it. Secrets are being hidden from us under a heavy silicon mattress.

Ensoniq was the first to break the ice by selling their Q chips to Apple Computer. Ensoniq is nevertheless reluctant to make them more generally available (I tried).

Quite surprisingly, Yamaha is now prepared to sell FM chips to all and sundry - with a catch. These sales will be discretionary, the intention being to protect their right to refuse supplying competitors they don't like or don't trust. The main difficulty at the moment is that of getting hold of small quantities and data, so I will have to report back on this in a future issue of *Keynotes*.

Yamaha is offering four main devices, all intended for use under microprocessor control: YM2149, YM2163, Y8950 and YM2203. Taking these in turn, the NMOS YM2149 is pin-compatible with General Instruments' AY-3-9810 (available from Maplin) but with enhanced features. Output resolution is a whopping five bits and no FM is provided.

The YM2163 is a similar non-FM NMOS sound chip with 24 pins and 7-bit output.

The Y8950 is what Yamaha used in their ill-fated commercial failure, the MSX computer. This is a complex 64-pin CMOS device which can do FM, sing, dance and make coffee but requires a fair amount of external hardware to do so.

Top of my list comes the 40 pin NMOS YM2203, which is

software compatible with the AY-3-9810 but more importantly offers three channels of FM sound, each comprising four operators.

Output is in a serial floating point format with ten bits of mantissa and three bits of exponent. This is a good technique for keeping signal to noise ratio high when outputting signals of low amplitude but means you are compelled to use the matching YM3014 DAC which costs extra.

So far as I know, the YM2203 is not actually used in any Yamaha machines. Since data on the device has already been made commercially available, it is unlikely that IBM would agree to its use as the mainstay of their Music Feature card. So in the near future we can at least hope to see some FM chips becoming available in small quantities through distributors.

There is some more good news on the chip front. Curtis Electromusic Specialities (CES) have launched no less than ten new devices. CES did (and still do) the CEM33xx series of ICs, as used extensively by Digisound, Sequential Circuits, Moog, Roland and Simmons, back in the days when the analogue grass was greener than the digital grass.

CES is now prudently straddling the analogue/digital fence with a wide variety of DAC multiplexer, anti-aliasing filter and VCA combinations.

Also on offer is a cheap current in/out dual VCA with a claimed 100dB S/N and 0.1% distortion. What is really clever about these is that they come in eight pin packages. Normally a VCA operating from dual supply rails requires an earth connection, if the control voltage is to be referenced to zero volts but unfortunately this takes the pin count up to nine.

CES wanted to use a VCA output as the 0V reference, given that it feeds a virtual earth supplied by an external opamp in the inverting amplifier configuration. However, this is easier said than done as an unwanted instability-causing feedback loop is created and it was two years' work before the problem was solved.

CES are intending to make available a data/applications handbook early in the new year.

Bruno Hewitt

# TEST INSTRUMENTS

UK's LARGEST IN-STOCK RANGE

## DIGITAL MULTIMETERS

- KT305 (\*) 26 range plus Hie test 10A AC/DC 20meg buzz 0.5% (R) £33.50
- KT110 (\*) 31 range incl. 5 range CAP 10A AC/DC 20meg buzz 0.5% (R) £33.00
- KT5005 (\*) 4 1/2 digit 26 range plus Hie 10A AC/DC 20meg 0.07% (PB) £83.00
- KD5008 (\*) 15 range AC/DC volts 0.2A DC 2 meg (S) £34.50
- KD578 (\*) 20 range 10A AC/DC auto range display hold 0.8% (R) £33.50
- 6010 (\*) 28 range 10A AC/DC 20 meg 0.25% (PB) £39.50
- 7030 (\*) 0.1% version of 6010 £52.13
- 5010EC (\*) 34 range incl. CAP Hie temp etc 0.25% (R) £35.00
- M3530 (\*) 28 range incl. 5 range CAP plus Hie 10A AC/DC 0.5 (R) £35.00
- M3800 (\*) 30 range plus Hie 20A AC/DC 20 meg 0.5% (R) £57.00
- M3650 (\*) 30 range incl. Hie CAP freq. count. 20A AC/DC 0.3% (R) £35.00
- M3800 (\*) 30 range - CAP - Hie - Databold 20A AC/DC 20meg 0.05% (R) £77.00
- M4630 (\*) 30 Range - CAP - Hie - Databold 20A AC/DC 20meg 0.05% (R) £36.50
- HC5010 (\*) 31 Range 10A AC/DC 20meg 0.25% (R) £41.00
- HC779 (\*) 20 Range 10A AC/DC Auto range - Hie - mem/hold 0.5% (R) £14.95
- 6511 (\*) Wallet auto range £21.50
- DM205 (\*) 14 range 10A DC Hie test display hold 0.5% (R)


All 3 1/2 Digit LCD.  
Case £2.17  
4 1/2 Digit.  
With Case.  
(R = Rotary  
Pb = Push Button  
S = Slide)


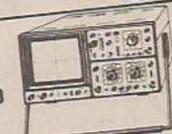
## SCOPES (\*with probes)

- HAMEG - all with component testers £314.00
- \*203/6 Dual 20MHz £698.00
- \*806 Dual 80MHz, 3 chan delay etc £527.00
- \*205/2 Dual 20MHz - digital store £575.00
- \*604 Dual 60MHz - sweep delay
- THANDAR SC110A Batt 10MHz £195.00
- Portable
- CROTECH 3031 20MHz Single track + comp. £199.00

- GENERAL OST5M 5MHz Bench portable £146.00
- HITACHI V212 Dual 20MHz £330.00
- HUNG CHANG 615 Dual 15MHz Batt/Mains £399.00



## POCKET INSTRUMENTS

- \*KT905 8 Range Digital Cap Meter £34.74
- 555 20KHz to 150KHz Audio Generator £47.50
- 2030ET 27 Range multimeter 10A AC/DC - Hie + Cap £37.90
- 5050E-41 Range FET meter 0.1 uA, 1000 meg etc £28.65
- 102BZ 18 Range Meter 20K/V, 10A DC Buzzer £10.39
- 07 20 MHz Logic Probe, TTL, CMOS £9.52
- 625 50 MHz Logic Probe - Logic Pulse 0.5/400Hz £22.95
- X1/X10 Scope/Inst. Probe 250 MHz with access £11.50
- Pfm 200a 200MHz LED 8 digit Freq counter £75.00
- K0m6 1.5MHz to 250MHz TR Dipmeter £43.04
- \*ST300 0/300 AMPS AC 5 range 0/600V AC 4 ranges £32.83
- 10K Ohm Res clamp meter £65.00
- \*S01 Electronic insulation tester 500V DC 100 meg 10A AC/DC volts LCD £63.04
- \*6060 Digital power meter 2KW/4KW tru power £59.50
- 10A AC/DC volts LCD £14.17
- \*TH301 Digital temperature meter with probe LCD
- \*HC201 19 range, analogue meter, 12A AC/DC



## BENCH DIGITAL MULTIMETERS

- 3 1/2 digit LCD 100 uV AC/DC 100mA 100m OHM con buzzer battery operated 20A AC/DC £89.00
- 3225 0.25% basic £119.00
- 3210 True RMS Version 0.1% £85.00
- Tm355 3 1/2 digit LED 10A AC/DC 0.25% (Batt operated) £85.00
- Tm351 LCD 0.1% £115.00; Tm 356 LCD 0.25% £95.00
- 8035 LED 20A AC/DC 0.1% £179.00
- 8035T LED 20A AC/DC True RMS £179.00
- 8145 4 1/2 digit LED 20A AC/DC 0.05% £169.00

## DC POWER SUPPLIES

- 240V AC input. Stabilised variable output voltages. Direct meter reading volts and amps. £50.39
- 243 0/24 volts 0/3 amps DC £64.50
- 245 0/24 volts 0/5 amps DC £36.50
- 154 5/15 volts 0/4 amps DC £66.00
- 0/30V 0/3A DC twin meter
- THURLEY, GW. THANDAR DIGITAL PSU's AVAILABLE

## SIGNAL SOURCES

- AC220/240 V operations
- FUNCTION SINE/SQ/TRIANGLE/TTL £110.00
- Jupiter 500 0.1Hz to 500KHz £110.00
- TG101 0.02Hz to 200KHz £160.00
- TG102 0.2Hz to 2MHz £149.00
- Jupiter 2000 0.2Hz to 2MHz

## COUNTERS & TIMERS

- ALL BENCH MODELS
- FREQUENCY COUNTERS
- MET100 220/240V AC 8 digit £99.00
- MET600 LED 0.1Hz £126.00
- MET1000 RESOLUTION £175.00
- MET1500 5mv min Sensitivity £199.00
- TF200 8 digit LCD batt 200 MHz £175.00
- COUNTER/TIMERS 8 DIGIT LED
- APPOLLO 10 STANDARD MODEL £219.00
- APPOLLO 100 PLUS DISPLAY HOLD RPM STOP WATCH ETC. £285.00



## TV-VIDEO

- PAL VHF/UHF 5.5/6/6.5MHz Fm SOUND RGB 2 SYN a/p/s Colour - B/W etc. £199.00
- DIGITAL DISPLAY (0.2Hz - 2MHz)
- 2D 4 digit 0.2Hz - 2MHz Function £165.00
- 80160 6 digit 0.2Hz - 2MHz Function £215.00
- 8019 5 digit AM/FM Function £250.00
- SWEEP FUNCTION (0.2Hz - 2MHz)
- 8016S FM mod 6 types of wave-form £190.00
- 8019 5 digit 0.2MHz - 2MHz AM/FM Function £250.00

PLEASE ADD VAT (UK ONLY)  
CATALOGUES WITH DISCOUNT VOUCHERS Send 12" x 19" SAE (£1 Stamp UK)  
TRADE ■ EDUCATION ■ EXPORT SUPPLIED

ORDER BY POST OR PHONE • OPEN 6 DAYS A WEEK FOR CALLERS  
**HENRY'S**  
404 EDGWARE ROAD  
LONDON W2 1ED  
Tel: 01-724 0323  
Account Enquiries 01-258 1831. Telex 298102 Trans G  
Also at 301 Edgware Road, W2. Tel: 01-724 3564

# ETI PCB SERVICE

Build your projects in style with a properly designed PCB.

Use the form below (or a photocopy) for your order. Please fill in all parts of the form.

The board reference number tells you when the PCB foil was published. The first two numbers are the year and the next two the month. The number after the dash indicates the particular project in that issue.

The terms are strictly cash with order. Make cheques payable to ASP Ltd. We cannot accept official orders but we can supply a pro-forma invoice if required. Such an order will not be processed until payment is received.

Orders can also be made by telephone on (0442) 41221 for Access and Visa card holders.

Please allow 28 days for delivery.

Price Code	Price (inc VAT) £
C	1.80
D	2.50
E	3.23
F	4.00
G	4.75
H	5.50
J	6.62
K	7.20
L	8.80
M	10.60
N	13.10
O	15.80
P	17.90
Q	21.80
R	23.90
S	25.90
T	29.00
U	32.20
V	35.80
W	37.90
X	40.70

TO: ETI READERS' SERVICES DEPARTMENT  
Argus Specialist Publications Ltd,  
9 Hall Road, Hemel Hempstead,  
Herts HP2 7BH

Please supply:

No. required per type	Board reference number	Price letter	Price each £	Total for board type £
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p

POSTAGE & PACKING £ 0.75p

TOTAL ENCLOSED £ . p

ORDER TO BE SENT TO: (BLOCK CAPS PLEASE)

Name .....

Address .....

Postcode .....

(Make cheques payable to ASP Ltd)

ACCESS and VISA credit card orders can be taken on (0442) 41221 (office hours only).

- E8107-1 System A Disc Input bd MC-MM..... F
- E8107-2 System A Preamp Main ... K
- E8108-1 System A Power Amp ..... L
- E8109-2 System A PSU ..... F
- E8201-2 Infant Guard ..... C
- E8202-5 MM Stage Disc Preamp (Tilsbrook) ..... G
- E8206-5 Logic Lock ..... F
- E8208-1 Playmate Practice Amp 3bds SA1 ..... K
- E8212-1 ELCB ..... F
- E8301-2 Analogue to digital conv (ZX81/Spectrum) ..... E
- E8305-3 Dual Audio Power Supply, Linsley Hood ..... G
- E8305-5 Balanced Input Preamplifier ..... F
- E8307-2 Flash Trigger-sound or FR ..... F
- E8308-1 Graphic Equaliser 1/2 Oct/Chnl ..... M
- E8308-2 Servo Fail-safe ..... C
- E8309-1 NICAD Charger/Regenerator ..... F
- E8310-3 Typewriter Interface - EX42 ... F
- E8311-1 Mini Drum Synth ..... F
- E8311-8 Moving Coil Pre-Preamp ..... F
- E8312-3 Light Chaser EPROM Controlled (2 Boards) ..... K
- E8402-1 Speech Board ..... M
- E8402-2 Modular Pre-amp Disc Input Mono ..... F
- E8402-3 Modular Pre-amp Stereo Output ..... F
- E8402-4 Modular Pre-amp Relay, PSU ..... F
- E8402-5 Modular Pre-amp Tone Main Mono ..... F
- E8402-6 Modular Pre-amp Tone Filter, Stereo ..... F
- E8402-7 Modular Pre-amp Balanced Output ..... F
- E8402-8 Modular Pre-amp Headphone Amp ..... F
- E8404-2 Mains Remote control Receiver ..... F
- E8405-1 Auto Light Switch ..... F
- E8405-2 ZX81 EPROM Programmer ... N
- E8405-3 Mains Remote Control Transmitter ..... H
- E8405-4 Centronics Interface ..... F
- E8405-6 Drum Synth ..... F
- E8406-1 Oric EPROM Board ..... O
- E8406-2 Spectrum Joystick ..... E
- E8406-3 Audio Design RIAA Stage .... G
- E8406-4 AD Buffer/Filter/Tone ..... H
- E8406-5 AD Headphone Amp ..... F
- E8406-6 AD Preamp PSU ..... K
- E8406-7 AD Power Amp ..... H
- E8406-8 AD Power Amp PSU ..... J
- E8406-9 AD Stereo Power Meter ..... F
- E8406-10 AD Input Clamp ..... C
- E8407-1 Warlock Alarm ..... M
- E8408-2 EPROM Emulator ..... N
- E8408-3 Infrared Alarm Transmitter ... E
- E8408-4 Infrared Alarm Receiver ..... F
- E8409-1 EX42 Keyboard Interface ..... F
- E8409-2 Banshee Siren Unit ..... F
- E8410-1 Echo Unit ..... F



E8410-2 Digital Cassette Deck ..... N  
 E8410-3 Disco Party Strobe ..... H  
 E8411-5 Video Vandal (3boards) ..... N  
 E8411-6 Temperature Controller ..... D  
 E8411-7 Mains Failure Alarm ..... D  
 E8411-8 Knife Light ..... D  
 E8411-9 Stage Lighting Interface ..... F  
 E8411-10 Perpetual Pendulum ..... E  
 E8412-1 Spectrum Centronics Interface  
 ..... F  
 E8412-4 Active- 8 Protection Unit ..... F  
 E8412-5 Active- 8 Crossover ..... F  
 E8412-6 Active- 8 LF EQ ..... F  
 E8412-7 Active- 8 Equaliser ..... F  
 E8501-3 Digital Delay (2 boards) ..... T  
 E8502-1 Digital Delay Expander ..... N  
 E8502-2 Data Logger ..... J  
 E8503-1 Combo Preamplifier ..... F  
 E8503-2 THD Meter mV & oscillator  
 bds (2 boards) ..... K  
 E8503-3 THD Meter Mains PSU ..... F  
 E8504-1 Framestore Memory ..... M  
 E8504-3 Framestore Control ..... N  
 E8504-4 Buzby Meter ..... E  
 E8504-5 CCD Delay ..... F  
 E8505-5 Stereo Simulator ..... F  
 E8506-1 Audio Mixer Main ..... J  
 E8506-2 Audio Mixer PSU ..... F  
 E8506-3 Audio Mixer RIAA ..... D  
 E8506-4 Audio Mixer Tone Control ..... D  
 E8506-5 EPROM Prog MKII ..... O  
 E8508-1 RCL Bridge ..... N  
 E8508-2 EX42/BBC Interface ..... E  
 E8508-3 EPROM Emulator ..... L  
 E8509-1 Spectrum ..... F  
 E8509-2 Direct Injection Box ..... E  
 E8510-9 Sunrise Light Brightener ..... K  
 E8511-1 MTE Waveform Generator ..... H  
 E8511-2 Millifaradometer ..... H  
 E8511-3 Cymbal Synth ..... J  
 E8511-5 Chorus Effect ..... H  
 E8511-7 Enlarger Exposure Meter ..... F  
 E8511-8 Switching Regulator ..... E  
 E8511-9 Second Line of Defence ..... M  
 E8512-1 Specdrum connector ..... F  
 E8512-2 MTE Pulse Generator ..... H  
 E8511-3 Specdrum ..... L  
 E8601-2 Walkmate ..... L  
 E8601-3 MTE Counter-timer ..... M  
 E8602-1 Digibaro ..... O  
 E8603-2 Programmable Logic Evaluation  
 Board ..... H  
 E8603-3 Sound Sampler Analogue  
 Board ..... R  
 E8604-1 JLLH PA PSU ..... H  
 E8604-2 Matchbox Amplifier ..... C  
 E8604-3 Matchbox Amp Bridging  
 Version ..... C  
 E8604-4 MTE Analogue/Digital  
 Probe ..... M  
 E8605-1 Microlight Intercom ..... E  
 E8605-2 Baud Rate Converter ..... M  
 E8605-3 Baud Rate Converter  
 PSU Board ..... G  
 E8605-4 Portable PA ..... H  
 E8606-1 Midi-CV Converter Board ..... H  
 E8606-2 Midi-CV Converter PSU ..... D  
 E8606-3 Troglograph ..... F  
 E8606-4 80m Receiver ..... H  
 E8606-5 Sound Sampler ..... R  
 E8607-1 Direction ..... E  
 E8607-2 Upgradeable Amp, MC stage  
 (Stereo) ..... G  
 E8607-3 BBC Motor Controller ..... F  
 E8608-1 Digital Panel Meter ..... G  
 E8608-2 Upgradeable Amp, MM stage  
 (mono) ..... H  
 E8609-1 Mains Conditioner ..... E  
 E8609-2 Experimental preamp ..... F  
 E8609-3 Upgradeable amp, Tone board  
 (mono) ..... H

E8609-4 Upgradeable amp, Output  
 board (mono) ..... F  
 E8610-1 Audio Analyser Filter  
 Board ..... L  
 E8610-2 Audio Analyser Display  
 Driver ..... K  
 E8610-3 Audio Analyser Display ..... H  
 E8610-4 Audio Analyser Power  
 Supply ..... F  
 E8611-1 Audio Switcher (2 bds) ..... H  
 E8611-2 PLL Frequency meter (4 bds) ... Q  
 E8611-3 Upgradeable Amp PSU ..... J  
 E8611-4 Call meter, main bd. .... O  
 E8611-5 Call meter, interface bd. .... N  
 E8612-1 Bongo Box ..... J  
 E8612-2 Biofeedback monitor  
 (Free PCB) ..... E  
 E8701-1 RGB Converter ..... F  
 E8701-2 Mains Controller ..... D  
 E8701-3 Flanger ..... H  
 E8701-4 Audio Selector main board ... M  
 E8701-5 Audio Selector PSU ..... H  
 E8701-6 Tacho-Dwell ..... F  
 E8702-1 Ratemeter main board ..... K  
 E8702-2 Ratemeter ranging board ..... F  
 E8702-3 Photo Process Controller  
 (3bds) ..... O  
 E8702-4 LEDline display board  
 (2 off) ..... K  
 E8702-5 LEDline PSU and controller  
 (2 bds) ..... G  
 E8703-1 Capacitometer ..... F  
 E8703-2 Geiger Counter ..... L  
 E8703-3 Credit Card Casino ..... E  
 E8704-1 BBC micro MIDI interface ... L  
 E8704-2 ETIFaker patch box ..... H  
 E8704-3 24Hr. Sundial ..... E  
 E8705-3 MIDI Keyboard keyswitch  
 boards (3 boards) ..... W  
 E8705-4 Batlite ..... C  
 E8705-5 Budget Power Meter ..... E  
 E8706-1 Hi-fi Power Meter ..... N  
 E8706-2 MIDI Keyboard CPU ..... U  
 E8706-3 MIDI Keyboard Front Panel ... O  
 E8706-4 Flame Simulator ..... G  
 E8707-1 MIDI Keyboard PSU ..... H  
 E8707-2 Telephone Alarm ..... J  
 E8707-3 Nuclear Strategy Simulator ... J  
 E8708-1 Remindalite ..... F  
 E8708-2 Rear Wiper Alarm ..... G  
 E8708-3 Rev Counter ..... F  
 E8708-4 Car alarm ..... F  
 E8708-5 Knight Raider ..... J  
 E8709-1 Boiler Controller ..... G  
 E8709-2 Amstrad Sampler (2 bds) ..... P  
 E8709-3 Portable PA ..... G  
 E8709-4 EEG Monitor (2 bds) ..... L  
 E8710-1 Concept CPU board ..... N  
 E8710-2 Concept Power board ..... K  
 E8710-3 Concept display board ..... G  
 E8710-4 Hyper-Fuzz ..... F  
 E8710-5 Big Digits digit board ..... N  
 E8710-6 Big Digits minute board ..... F  
 E8710-7 Big Digits battery board ..... G  
 E8711-1 Quiz Controller ..... E  
 E8711-2 256K Printer Buffer ..... N  
 E8712-1 Heating Management System ... O  
 E8712-2 SWR Meter ..... H  
 E8712-3 Dream Machine (free PCB) ... D  
 E8801-1 Smart Talker ..... L  
 E8801-2 Passive IR Alarm ..... H  
 E8801-3 Mains Cleaner ..... G  
 E8801-4 RGB Dissolve ..... L  
 E8802-1 Electric Fencer ..... E  
 E8802-2 Telephone Intercom ..... L  
 E8802-3 Transistor Tester (2 bds) ..... L  
 E8802-4 Spectrum Co-processor CPU .. N



**Flat Alarm** (June 1987)  
 In the circuit diagram Q2 is shown as an NPN transistor. It should be a PNP device as given in the parts list. IC4 is given in Fig. 2 as a 74LS260 and C5 as 470n. They should be 74LS132 and 4µ7 as in the parts list. R13 is incorrectly given as 280R in the parts list instead of 270R.

**Nuclear Strategy Simulator** (July 1987)  
 The bridge rectifier (BR1) on the overlay diagram has no polarity markings. It should be positioned with the positive at bottom left, connected to the track which connects to IC8 IN and C4 positive.

**Telephone Alarm** (July 1987)  
 In the component overlay (Fig.2) IC1 and IC2 should be swapped. The capacitor to the right of IC1,2 is C1 and the inductor between them is L1. The unmarked resistor to the left of L1 should be a wire link. In the circuit diagram (Fig.1b) IC4a,b should be AND gates. IC5 should be NAND gates. The parts list is correct.

**Kappellmeisters** (July 1987)  
 The position of the speaker port in the front panel was omitted from Fig.2. This should be a 7¼x4½in ellipse centred across the panel with its top edge 2½in below the panel top.

**Knight Raider** (August 1987)  
 In Fig.1(a) pins 4 and 5 of IC1 are swapped. IC2-3 show the correct pin-out.

**Car Alarm** (August 1987)  
 In Fig. 1 Q7 is not numbered and its emitter is shown unconnected. This connects to earth. The transistors in the parts list went a little awry. Q2-6 are BC237 and Q7 is a TIP31.

**Boiler Controller** (September 1987)  
 In Fig. 2 (a) the primary of T2 is shown connected to Earth. This should be neutral. In Fig. 2(b) one of the bridge rectifier diodes, D6-9, is shown the wrong way around. This is correctly shown in Fig. 5.

**EEG Monitor** (September 1987)  
 In Fig.3a the pins of IC1 connected to the power rails are shown swapped around. In Fig.4a R7 is unlabelled and is between C3 and C6. In Fig.5 C20 should be £10 and R18 is unlabelled. It lies between R17 and R19.

**ETI Concept** (October 1987)  
 The Power Board parts list wrongly lists R6 as 270R. This should be 270k. Also, note that the power board's 0V rail must *not* be connected to Earth or the 0V rail of the CPU board.

**Printer Buffer** (November 1987)  
 The software for the EPROM had three errors listed. The byte at 039A should read 20, at 039B 14 and at 0492 30. All numbers are in Hex.

**Dream Machine** (December 1987)  
 The transistors used in this project are ST1702. BC108s can be substituted.



# Electro Mech Industries Limited

More Transistors, Thyristors, Triacs, Diodes, 74s, Switch Mode PSUs etc. etc. All at competitive prices. Details on request. ACCESS or VISA welcome. Just phone your order through, we do the rest. 24hr answerphone. Tel: 0933 75827 Fax: 0933 76605

Unit 2, Wessex Industrial Estate, Station Lane, Witney, Oxfordshire. Telephone (0993) 75827 or 76605

## IBM COMPATIBLES x VA

Superb quality at sensational prices by Beltron Computer Systems Inc.

EX VAT P&P	
XT COMPATIBLE	790.00 10.00
AT COMPATIBLE	1245.00 10.00
TURBO/AT VGA SYSTEM	1840.00 10.00
Full technical specs available. Ranged options/peripherals available	
At incredibly low prices.	
Demonstrations can be arranged by appointment. Write/phone for brochure & price list.	

## MEMOTECH

MTX512 80K RAM	60.00 5.00
MTX512 Series 2 256K RAM	87.00 5.00
MCL 3.5" CP/M Disc Drive Upgrade	225.00 5.00

**SPECIAL OFFERS**

3.5" CP/M Disc Drive Upgrade, MTX512 Series 2 Computer, 12" Hi-Res Monitor, Comprehensive Software Package, Detailed Manuals, 10 x 3.5" Disquettes

All this for £399.95 inc. VAT, Delivery at £10.00 extra. Various Expansions Available.

## BBC

Master 128	395.00 7.00
Compact Entry System	360.00 7.00
Compact Colour System	545.00 7.00
Archimedes Basic 305 System	799.00 7.00
Archimedes Basic 310 System	875.00 7.00

Full range of accessories - Send for price list.

## EMI DISC DRIVE RANGE

### BBC DISC DRIVES

All supplied with Leads, Manual & Utilities Disc

Single 200K drive, 40 Track D/S	£95.00
Single 400K drive, 40/80 Switchable	£112.00
Dual 400K drive, 40 Track D/S	£183.00
Dual 400K drive, 40/80 Switchable	£214.00

### 5.25" DRIVES, WITH POWER SUPPLY

Single 200K drive, 40 Track D/S	£108.00
Single 400K drive, 40/80 Switchable	£125.00
Dual 400K drive, 40 Track D/S	£196.00
Dual 400K drive, 40/80 Switchable	£235.00

horizontally mounted in monitor stand (Master Version) £265.00

### 3.50" DRIVES, WITHOUT POWER SUPPLY

Single 400K drive, supplied in dual case, with blanking plate, to allow easy upgrade to dual drive.	£95.00
Dual 400K drive	£165.00

### 3.50" DRIVES, WITH POWER SUPPLY

Single 400K drive, as above	£110.00
Dual 400K drive, as above	£180.00

NB: Please add £3.00 P and P per Single Drive, and £5.00 P and P per Dual Drive  
Please add £7.00 delivery on Monitors, £3.00 on Modems

## SPECIAL OFFER

5 1/4" 500K DS/DD MITSUBISHI DISC DRIVE £75.00  
5 1/4" 1MB DS/DD MITSUBISHI DISC DRIVE £80.00  
PHILIPS 8833 COLOUR MONITOR with BBC lead £225.00

D type CONNECTORS	RIBBON CABLE	IDC CONNECTORS	MODULATORS
PLUGS	way 9 15 25 37	PCB R/A/EDGE	UM1286 2.00
SOLDER	0.45 0.60 0.90 1.25	SKT Plug Plug	UM1233 3.00
PCB	.65 75 1.05 .	10 way 0.61 0.65 0.65	
PCB R/A	.95 1.50 2.05 .	16 way 0.70 0.85 0.85	
SOCKETS		20 way 0.80 1.30	
SOLDER	.65 .90 1.25 2.00	20 way 0.88 1.10 1.10	
PCB	1.75 1.10 1.75 .	26 way 0.98 1.20 1.20	
PCB R/A	.70 1.00 2.60 .	34 way 1.12 1.50 1.50 3.20	
COVERS		40 way 1.35 1.65 1.65	
IDC PLUG	3.15 3.75 5.80 .80	50 way 1.65 2.50 2.50	
SOCKET	3.40 3.90 3.00		


## 74LS & 74F

74LS175	0.50	74LS368	0.35	74F74	0.40	7430	0.30	7446	0.85	7486	0.60
74LS181	1.80	74LS373	0.18	74F85	1.85	7436	0.75	7448	1.40	7492A	0.50
74LS182	2.00	74LS374	0.65	74F125	1.05	7438	0.35	7450	0.25	7491	0.60
74LS183	1.50	74LS378	0.75	74F138	1.05	7440	0.30	7470	0.90	7492	0.30
74LS184	0.85	74LS380	0.18	74F151	2.95	7441	0.60	7474	0.36	7493	0.50
74LS185	0.85	74LS390	0.55	74F161	0.62	7442	0.62	7475	0.45	7494	0.85
74LS186	0.65	74LS393	0.45	74F163	0.90	7476	0.85	7485	0.74	7496	0.60
74LS187	0.65	74LS395A	0.40								
74LS188	0.55	74LS40	0.18								
74LS189	0.55	74LS42	0.60	7400	0.22	AC128	0.30	BP200	0.35	MPSA55	0.25
74LS190	0.30	74LS44	0.40	7401	0.22	AC142	0.33	BP244	0.35	MPSA05	0.25
74LS191	0.18	74LS46	0.90	7402	0.22	AC176	0.25	BP268	0.45	TIIP29A	0.32
74LS192	0.18	74LS48	0.90	7403	0.22	AC187/B	0.25	BP257/B	0.45	TIIP29C	0.32
74LS193	0.18	74LS50	0.18	7404	0.22	AD149	0.75	BP259	0.30	TIIP295	0.50
74LS194	0.18	74LS52	0.18	7405	0.22	AD151	0.40	BP324	0.25	TIIP300	0.32
74LS195	0.18	74LS54	0.18	7406	0.22	AD152	0.40	BP336	0.30	TIIP303	0.35
74LS196	0.18	74LS56	0.18	7407	0.22	AF124-127	0.50	BP337	0.30	TIIP305	0.50
74LS197	0.18	74LS58	0.18	7408	0.22	AF139	0.38	BP421-423	0.22	TIIP310A	0.45
74LS198	0.18	74LS60	0.18	7409	0.22	AF238	0.50	BP469-472	0.40	TIIP31C	0.40
74LS199	0.18	74LS62	0.18	7410	0.22	BC107B-110	0.10	BP470-872	0.30	TIIP32A	0.40
74LS200	0.18	74LS64	0.18	7411	0.22	BC114	0.25	BP471	0.22	TIIP32C	0.40
74LS201	0.18	74LS66	0.18	7412	0.22	BC140	0.30	BP472	0.22	TIIP33C	0.40
74LS202	0.18	74LS68	0.18	7413	0.22	BC147-159B	0.12	BP490	0.60	TIIP33A	0.90
74LS203	0.18	74LS70	0.18	7414	0.22	BC170	0.30	BP491	0.75	TIIP34C	0.30
74LS204	0.18	74LS72	0.18	7415	0.22	BC182-238C	0.09	BP494	0.88	TIIP34P	1.20
74LS205	0.18	74LS74	0.18	7416	0.22	BC256A	0.30	BP498	0.88	TIIP34S	0.30
74LS206	0.18	74LS76	0.18	7417	0.22	BC307B-338	0.30	BP499	0.88	TIIP34T	0.30
74LS207	0.18	74LS78	0.18	7418	0.22	BC441-461	0.33	BP495	0.45	TIIP42A	0.50
74LS208	0.18	74LS80	0.18	7419	0.22	BC477	0.20	BP497/88	0.45	TIIP42B	0.50
74LS209	0.18	74LS82	0.18	7420	0.22	BC516	0.30	BP498	0.30	TIIP42C	0.50
74LS210	0.18	74LS84	0.18	7421	0.22	BC517	0.30	BP499	0.30	TIIP390	0.20
74LS211	0.18	74LS86	0.18	7422	0.22	BC547B-559	0.50	BP499	0.30	TIIP395	0.20
74LS212	0.18	74LS88	0.18	7423	0.22	BD124P	0.11	BP499	0.30	TIIP390	0.20
74LS213	0.18	74LS90	0.18	7424	0.22	BD131	0.50	BP499	0.30	TIIP390	0.20
74LS214	0.18	74LS92	0.18	7425	0.22	BD132	0.50	BP499	0.30	TIIP390	0.20
74LS215	0.18	74LS94	0.18	7426	0.22	BD133	0.48	BP499	0.30	TIIP390	0.20
74LS216	0.18	74LS96	0.18	7427	0.22	BD135	0.48	BP499	0.30	TIIP390	0.20
74LS217	0.18	74LS98	0.18	7428	0.22	BD136-140	1.55	BP499	0.30	TIIP390	0.20
74LS218	0.18	74LS100	0.18	7429	0.22	BD177	0.80	BP499	0.30	TIIP390	0.20
74LS219	0.18	74LS102	0.18	7430	0.22	BD178	0.35	MJE3055	1.60	2N3055	1.60
74LS220	0.18	74LS104	0.18	7431	0.22	BD179	1.05	BP499	0.30	2N3819	0.35
74LS221	0.18	74LS106	0.18	7432	0.22	BD184	2.00	BP499	0.30	MJE3055	1.60
74LS222	0.18	74LS108	0.18	7433	0.22	BD185	0.80	BP499	0.30	MJE3055	1.60
74LS223	0.18	74LS110	0.18	7434	0.22	BD186	1.55	BP499	0.30	MJE3055	1.60
74LS224	0.18	74LS112	0.18	7435	0.22	BD187	2.10	BP499	0.30	MJE3055	1.60
74LS225	0.18	74LS114	0.18	7436	0.22	BD188	1.05	BP499	0.30	MJE3055	1.60
74LS226	0.18	74LS116	0.18	7437	0.22	BD189	2.00	BP499	0.30	MJE3055	1.60
74LS227	0.18	74LS118	0.18	7438	0.22	BD190	1.20	BP499	0.30	MJE3055	1.60
74LS228	0.18	74LS120	0.18	7439	0.22	BD191	0.30	BP499	0.30	MJE3055	1.60
74LS229	0.18	74LS122	0.18	7440	0.22	BD192	0.30	BP499	0.30	MJE3055	1.60
74LS230	0.18	74LS124	0.18	7441	0.22	BD193	0.30	BP499	0.30	MJE3055	1.60
74LS231	0.18	74LS126	0.18	7442	0.22	BD194	0.30	BP499	0.30	MJE3055	1.60
74LS232	0.18	74LS128	0.18	7443	0.22	BD195	0.30	BP499	0.30	MJE3055	1.60
74LS233	0.18	74LS130	0.18	7444	0.22	BD196	0.30	BP499	0.30	MJE3055	1.60
74LS234	0.18	74LS132	0.18	7445	0.22	BD197	0.30	BP499	0.30	MJE3055	1.60
74LS235	0.18	74LS134	0.18	7446	0.22	BD198	0.30	BP499	0.30	MJE3055	1.60
74LS236	0.18	74LS136	0.18	7447	0.22	BD199	0.30	BP499	0.30	MJE3055	1.60
74LS237	0.18	74LS138	0.18	7448	0.22	BD200	0.30	BP499	0.30	MJE3055	1.60
74LS238	0.18	74LS140	0.18	7449	0.22	BD201	0.30	BP499	0.30	MJE3055	1.60
74LS239	0.18	74LS142	0.18	7450	0.22	BD202	0.30	BP499	0.30	MJE3055	1.60
74LS240	0.18	74LS144	0.18	7451	0.22	BD203	0.30	BP499	0.30	MJE3055	1.60
74LS241	0.18	74LS146	0.18	7452	0.22	BD204	0.30	BP499	0.30	MJE3055	1.60
74LS242	0.18	74LS148	0.18	7453	0.22	BD205	0.30	BP499	0.30	MJE3055	1.60
74LS243	0.18	74LS150	0.18	7454	0.22	BD206	0.30	BP499	0.30	MJE3055	1.60
74LS244	0.18	74LS152	0.18	7455	0.22	BD207	0.30	BP499	0.30	MJE3055	1.60
74LS245	0.18	74LS154	0.18	7456	0.22	BD208	0.30	BP499	0.30	MJE3055	1.60
74LS246	0.18	74LS156	0.18	7457	0.22	BD209	0.30	BP499	0.30	MJE3055	1.60
74LS247	0.18	74LS158	0.18	7458	0.22	BD210	0.30	BP499	0.30	MJE3055	1.60
74LS248	0.18	74LS160	0.18	7459	0.22	BD211	0.30	BP499	0.30	MJE3055	1.60
74LS249	0.18	74LS162	0.18	7460	0.22	BD212					


---

---


# PCB FOIL PATTERNS

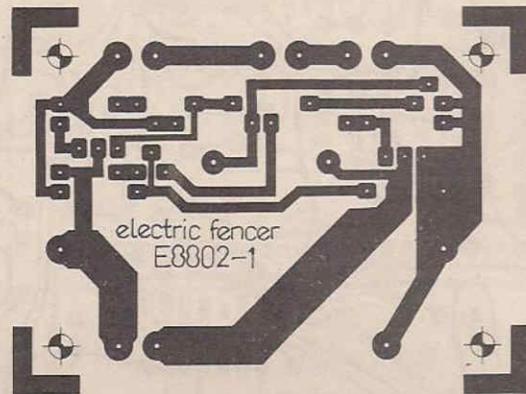


The Electric Fence PCB

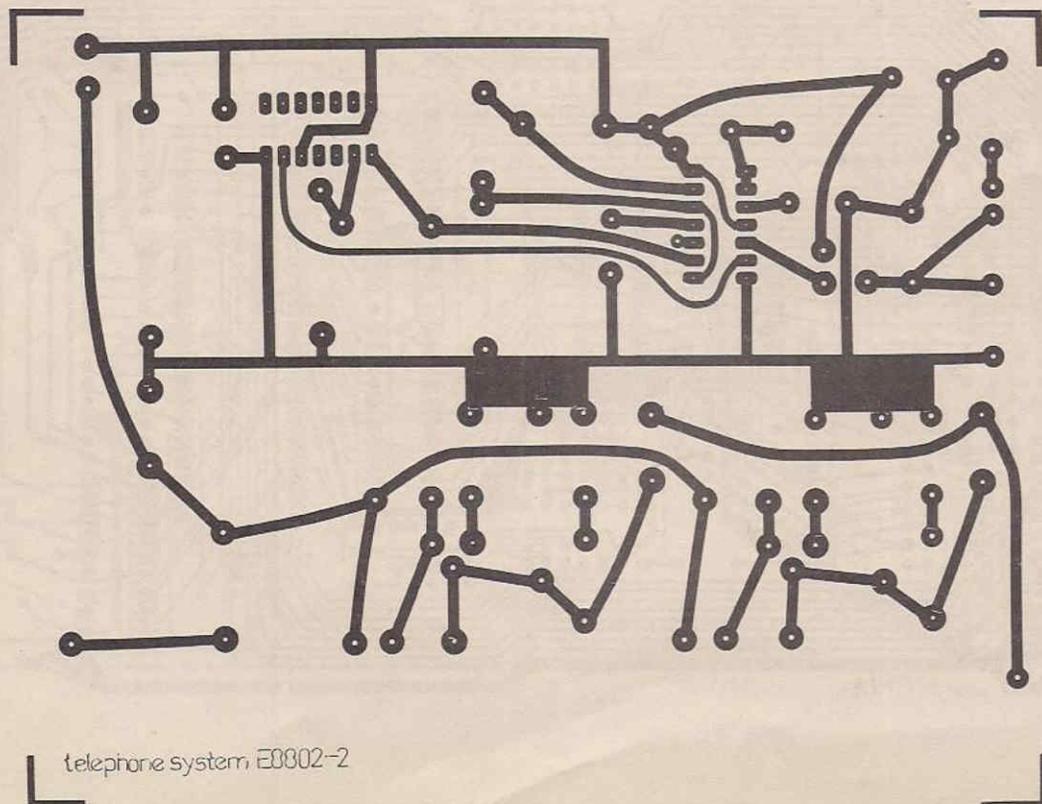


The Telephone Intercom foil pattern

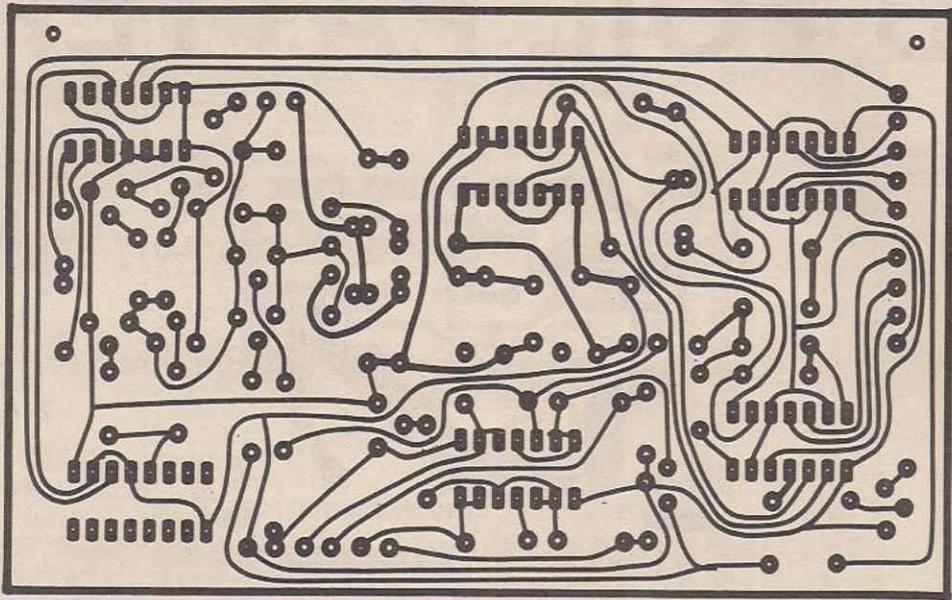


The Transistor Tester main board

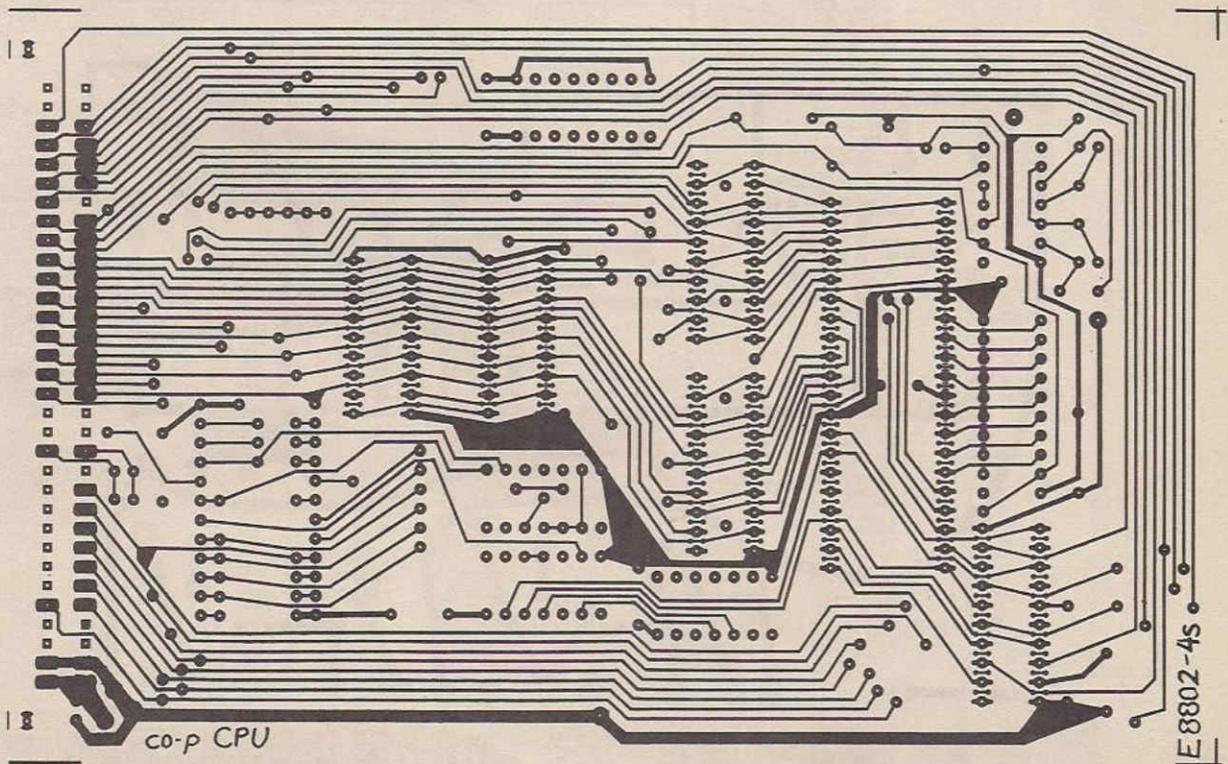

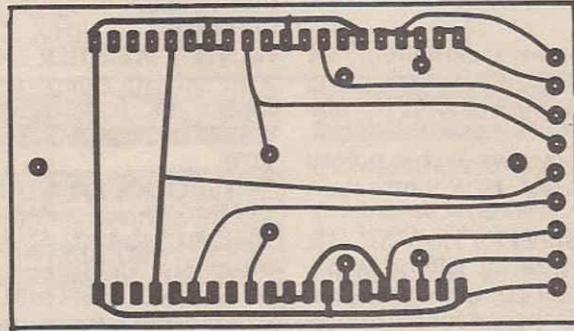The Co-processor CPU board solderside foil



The Transistor Tester display board

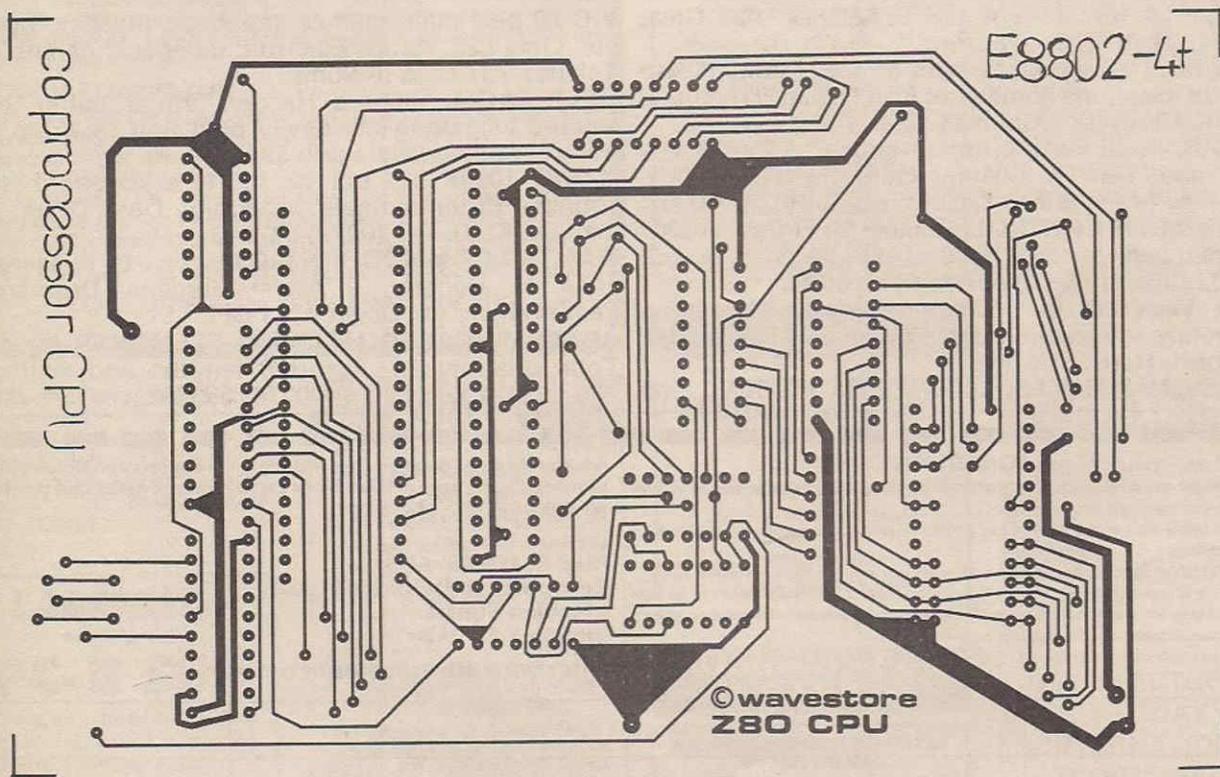

The Co-processor CPU board topside foil

# FREE READERS' ADS

Buy, sell or exchange through our free service to readers

**OSCILLOSCOPE.** Gould OS300 dual with case, probes, manual. Condition as new. £250. Tel: (0324) 713037.

**WANTED: DIGITAL MULTIMETER.** Any make in good working order with test leads. Paul Brown, 48 Lanndale Lawns, Tallaght, Dublin 24, Eire.

**LINSLEY HOOD** Audio Design power amplifier. 75% complete. Quality components, needs hardware, transformer and smoothing capacitors. £60 ONO. Tel: Clyde 01-639-5036.

**SPECTRUM MIDI** Projects Fanzine owners of commercial or electronics enthusiasts. Contact J. H. Robinson, 34 Kingston Road, RM1 3NB.

**WANTED** circuit diagram/service sheet for HMV MCH12 music-centre. P. Lewin, 21 Bretney, Jurby, Isle of Man.

**WANTED:** EPROM for Z80 controller computer, project. ETI August 1983. Will pay cash or exchange for hardware. Tel: (0656) 58203, after 730pm.

**WANTED ALL DISCO EQUIPMENT.** Amps deck, lighting, effects, etc. Will buy or swop for allsorts. Let me know what you've got. Alan 01-890 3304 Heathrow area.

**COMMODORE 64,** many games, joystick, books, mags, etc. All for £150 ONO. Phone 01-368 0934.

**FOR SALE:** Hart electronics DGS001 digital control tape cassette mechanism. Brand r.e.w. Unwanted gift. £35. Call Paul (0274) 593242.

**MAGAZINES:** Personal Computer World. May 1980 to April 1982. Any offers? Tel: 01-524 5350.

**OSCILLOSCOPE** with LED screen (unmade kit) £29.99. Also case kit £9.99 and scope lead, £3.95. J. E. Ellis, The Flat, 18, Butter Hill, Wallington, SM6 2JD.

**WANTED:** Ready built, complete working model, ETI's Knight Raider. Mr K. Rana, 145 Station Street East, Coventry CV6 5FR.

**GUITAR EFFECTS:** Especially bass. Info, circuits, etc. Wanted. ETI or own designs. Yaxi, 63 Keswick Road, Great Bookham, Leatherhead, Surrey.

**HELP!** I need advice on 'System A' power amp. Please write with telephone number to: Alan Phelan, 9 Lomunda Crescent, Clonsilla, Dublin 15, Eire.

**EX. GOVT.** Royal Electric Inc. inverter CLA-2500VA P/N X3516-1. Input: 275 VDC 150Amps. Output: 1PH115V. 400CY. 2500VA 0.90PF MFR SER No8220. Offers! Tel: (0274) 593382.

**VIDEO REMOTE CONTROL.** Suitable for Grundig V2000 2x4 Super. Full function handset plus receiver. Boxed. Unused. £10 and P&P. Tyneside 091-2630714.

**VALVES WANTED** by radio enthusiast. Also valve manufacture information and equipment. PO Box 23, Letchworth, Herts. SG6 1PF.

**EAGLE SIGNAL TIMERS** HZ-40A6, £200. HZ-170A6, £200

ONO. Pulse encoder model No. G70DSL D B1/2500-120-12, £600 ONO. Tachometer 5PY59JY27, £75. Tel: (0625) 72506.

**WANTED:** Circuit to interface teletext decoder panel to printer (parallel input). C. Savage, 9 Cook Road, Millom, Cumbria. LA18 4JH.

**WANTED WEATHER SATELLITE RECEIVER.** Full system required. Timestep or any system considered. Could collect. Phone Mr Day, Sheffield 46724.

**WANTED: ZAB1 PRINTER** plus paper. Ring Mike on (0727) 50799.

**COMMODORE 128** computer with disk drive and tape recorder. Three computers in one. Compatible with C64. Manuals included. Price £380. The Well House, Frittenden, Cranbrook, Kent.

**PE STRING ENSEMBLE** four octave keyboard fully working. Pitch transpose, strings, brass, woodwind, split keyboard, £125 ONO. Phone Dave evenings (0624) 73634, Isle of Man.

**WANTED: CIRCUIT DIAGRAMS** for the Pet 8032 business computer. Ring Anderson 051-256 9157 evenings.

**WANTED PHILIPS OSCILLOSCOPE PM3234** or PM3240 or PM3244 or PM3262. Mr Alnoor, 85 Swinderby Road, Wembley, Middlesex, HAO4SE.

**BBC B PERIPHERALS:** 128K SWR, £30. Opus DDOS, £30. OS1.2, £5. Basic 2, £5. Keyboard, £10. Various software, ionizers. Tel: 01-309 7921.

**GEMINI MULTIBOARD IVC** £40. 64K RAM, £35 or offers. Also Nascom assortment. Ring Steve on Wensleydale 23459 for a full technicolor list!

**WANTED:** Parallel phone to tape circuit, also transmitter. D. Thomas, 68 Bishopton Road, Stockton, Teesside.

**YAESU FR50B Rx, FL50B Tx, SSM Europa-B 2M TCVR,** hand mic, SWR meter. £150 ONO the lot. Phone Derby (0332) 792136.

**VIC 20** plus many games, tapedeck, joystick, books, etc. Only £25. Acorn Electron, tapedeck, games £30. Tel: 061-737 4015 (6-9pm).

**HELP E&CM,** Richard Harvey, printer buffer. Help wanted in getting my newly built unit to work! Tel: Stuart Winsor, Kenilworth 59491.

**CASIO 1000P** five octave, full size keyboard, 1000 sounds. Programmable arpeggio. Dust cover and manual, £120. Tel: (0272) 512550.

**WANTED COMMODORE VIC20** for parts. Reasonable price. H. Doherty, 9 Assisi Gardens, Drumaroad, Castlewellan, Co. Down BT31 9PE.

**BRASS ENCASED HEATING ELEMENTS** for sale. Total quantity 18. Assorted lengths and wattages: 170-1150W. Offers! Tel: (0274) 593382.

## CONDITIONS

- These ads are only for ETI readers not engaged in buying or selling the same items or services on a commercial basis.
- Ads will be inserted as and when space permits. Insertion in a specific issue cannot be guaranteed.
- ETI reserves the right to alter or refuse ads whenever this is judged necessary.
- All ads are accepted in good faith. Neither the magazine nor its publishers can be held responsible for any errors in the reproduction of ads, nor for untruths or misrepresentations, nor for the activities of advertisers or respondents.
- Advertisers submitting ads for this section shall be deemed to have accepted these conditions.

Ads should be 20 words or less including the address and/or telephone number. Please write in black block capitals or type in the grid provided on this form or a photocopy.

Send the form to:  
**FREE READERS' ADS**  
Electronics Today International  
1 Golden Square  
London W1R 3AB

Enter your advertisement below




# ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

## Lineage:

44p (VAT excl) per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£12.20 per single column centimetre + VAT

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 292

Send your requirements to:  
**Julie Capstick**  
ETI Class. Dept.,  
ASP Ltd.,  
1 Golden Square,  
London W1.

## FOR SALE

### LYTHALL COMMUNICATIONS

49a LINDEN WAY, HADDENHAM, ELY,  
CAMBS, CB6 3UG. TEL (0353) 740664

#### CORDLESS TELEPHONE

Range 700 feet, re-dial, call, mute etc. 240v AC power (BABT approved). £89.95p inc P&P.

#### ANSAFONE

240v AC power, complete, (BABT approved) £89.95 inc P&P.

#### MODEMS(all RS232 to micro)

1. V23 (1200/75 baud) such as used by PRESTEL and XMODEM type protocols. Autoanswer/originate. Duplex. Inc COMSTAR II ROM comms software for BBC micro series. £149.99p inc P&P.
2. V21 (300/300 baud) + V23(1200/75 baud). Call progress mon speaker, processor controlled, Autodial (pulse/DTMF) with 32 number store, Autoanswer, Duplex, Hayes Compatible so requires no special software. £199.95p inc P&P.
3. V21 (300/300) + V23(1200/75). Autodial (pulse/DTMF) with 64 number store, Autoanswer (V25 protocols), Duplex, Speed buffering, Hayes command set, Parallel printer port, date and time stamp, BABT approved. £399.00p inc P&P.

#### COMPUTER SWITCH (patent pending)

Enables your computer to switch external low power circuits (eg Buzzers, Radio's, Alarms, Indicators etc) on and off under software control. Compatible with most computers eg APPLE, ATARI, BBC, EINSTEIN, SINCLAIR. Powered by internal PP3 battery (supplied). Supplied with detailed instructions and example programmes (including morse-trainer+clock/timer) £34.99p inc P&P. Sample programmes available on 5.25" disk for Apple ][, add £4.95p

#### MODEM ELIMINATOR

Enables you to get programmes over wires to another computer of the same type. Internally powered from PP3 battery (supplied). Not suitable for use with other modem. Supplied with detailed instructions. £26.95p inc P&P.

Morse Trainer for Tatung Einstein on disk, (using internal speaker) £5.95p inc P&P. Other software for Einstein SAE. Send SAE for further details of any item, or send Cheque to:

**LYTHALL COMMUNICATIONS**, 49 LINDEN WAY, HADDENHAM, ELY, CAMBS, CB6 3UG.

## SPECIAL OFFERS

**CASSETTE MOTORS** large and small 2 for £1.00. Mono and stereo cassette tape heads. 2 for £1.00. Microphone small for cass. tel. etc. 2 for £1.00. Telephone buzzers at £2.50 each. Please add 75p p&p no VAT. Access card accepted. Golden Orange Supplies, Brockholms Road, Woodside, Bream, Lydney, Glos. Tel: 0594 563009.

#### FREE MEMBERSHIP to a new NATIONAL ELECTRONICS CLUB.

For details and a free gift of components worth over £10 send only £1.00 p&p to  
**Woodside, Dowsett Lane,  
Ramsden Heath,  
Essex CM11 1JL.**

## WANTED

#### IDEAS/INVENTIONS wanted.

Call I.S.C. 01 434 1272 or write, Dept ASP 99 Regent St, London W1.

Turn your surplus transistors, IC's etc., into cash. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. Contact:

**COLES HARDING & CO.**  
103 South Brink  
Wisbech, Cambs.  
ESTABLISHED OVER 10 YEARS  
Tel: 0945 584188  
Fax Number: 0945 588844

## SCOPES

### MENDASCOPE LTD.

REPAIR & RECALIBRATE  
OSCILLOSCOPES.  
ALL MAKES ALL MODELS.  
NATIONWIDE COLLECTION &  
DELIVERY  
FREE ESTIMATES  
Phone 069-172-597

## BUSINESS FOR SALE

#### ELECTRONIC COMPONENT DISTRIBUTION BUSINESS FOR SALE

A mail order business with an existing current customer base of over 350. Ideal business for expansion or part time operation. Two and a half years trading record, a turnover in excess of £15,000 and high percentage profits. All mailing lists and existing customers, over 2000 in total, £2500 worth of stock. Sources of supply and trading records supplied. Must sell due to other business commitments. Quick sale required hence any reasonable offer considered.  
Phone The Countryside Group on (0268) 725111

## SURVEILLANCE

### ESKAN ELECTRONICS

(MANUFACTURERS AND SUPPLIERS OF SURVEILLANCE AND AUDIO EQUIPMENT)

#### MICRO BUG

SK1 Miniature Transmitter 20mm x 47mm x 20mm, extremely sensitive. Operates from 1.5v battery, elegant metal box included.

Ready built + tested only **£29.50**  
Kit Form ..... **£24.90**

#### EXTRA MINIATURE TRANSMITTER

EK2 25mm x 30mm x 9mm  
Ready built + tested ..... **£49.00**  
Kit Form ..... **£37.95**

#### HIGH POWER FM RADIO TRANSMITTER

EK65, 65W adjustable frequency Mains operated. **£650 + £35 p&p** (Operation in the UK illegal without licence).

#### AUTOMATIC TELEPHONE MONITOR

SK19 ready built + tested **£34.50**  
Kit Form ..... **£29.95**

Many other surveillance equipment available. Send large S.A.E. for catalogue.

#### SOUND TO LIGHT UNIT

SK72 separate sensitivity, bass, treble and mid-range frequency controls, designed and manufactured to highest professional standard.

Ready Built..... **£39.95 p&p £3.50**  
Kit Form ..... **£21.95**  
Casing ..... **£11.95**  
SK70 sound to light control unit  
Kit Form ..... **£14.95**

Send Cheque or P.O. payable to:

### ESKAN ELECTRONICS

172 Caledonian Road,  
London N1 0SG.

Tel: 01 278 1768



Trade and Export Enquiries Welcome

**PANEL METERS**, Multimeters, Microphones, Transformers, Computer Leads, Ni-Cad Batteries. Send £1.00 for illustrated colour catalogue. M. Dziubas, 158 Bradshawgate, Bolton, Lancs.

### LABCENTER electronics

## PC-B £80

At last, an affordable PCB design tool for your Amstrad PC. Plotting service available.

Send SAE for further details, or £2 for demo disk.

**Labcenter Electronics**  
14 Marriner's Drive,  
Bradford, BD9 4JT.  
Tel: 0274 542868

## SITUATIONS VACANT

### Shalom Employment Action Centre ELECTRONICS SUPERVISOR

Supervisor wanted to provide basic training in electronics. Applicants should have skills in Hi-Fi/Audio and T.V., project design & development, and the ability to pass on skills to a variety of users, including women and people with disabilities.  
33 hours per week  
Scale: 6.27, £10,335 (6.28, £10,656 after 1 year)

Closing date: 29 January 1988  
Details and application forms from: Shalom EAC Appointments Group, 395 High St. North, London E12. Tel: 01-472 3571  
**EQUAL OPPORTUNITIES EMPLOYER**

USE ETI TO FILL YOUR JOB VACANCY.  
RING 01-437 0626 FOR DETAILS.

## SWITCHES

**VOICE/SOUND ACTIVATED SWITCHES** easy to follow diagrams and uses only £1.00. Components and P.C.B's available: **Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.**

USE 'ELECTRONICS TODAY INTERNATIONAL' TO BUY, SELL & EXCHANGE ALL YOUR PRODUCTS & SERVICES

## ELECTRONIC COMPONENTS

# TRADE LIST

## BRYANT ACOUSTIX

5 BELLE VUE TERRACE  
GILES GATE MOOR,  
DURHAM, DH1 2HR.  
Tel: (091) 3864500

### SEMICONDUCTORS

#### LINEAR

DEVICE	50+	100+
CA555CE	0.130	0.120
CA741CE	0.138	0.123
CA3130E	0.620	0.580
CA3140E	0.260	0.225
LF351	0.380	0.340
LM324	0.286	0.230
NE556	0.400	0.385
TBA820M	0.680	0.590
UA747	0.300	0.255

#### CMOS

DEVICE	100+
4000B	0.119
4001UB	0.119
4002B	0.132
4008B	0.160
4011B	0.120
4012B	0.120
4016B	0.265
4017B	0.220
4018B	0.225
4022B	0.245
4028B	0.190
4029B	0.250
4042B	0.185
4046B	0.320
4049UB	0.165
4050B	0.133
4071B	0.130
4081B	0.130
40106B	0.300

#### Mixed Quantity Pricing

#### V-REGS

DEVICE	10+	25+
7806 1 AMP	0.450	0.240
7812 1 AMP	0.450	0.240
7815 1 AMP	0.450	0.240
7805 1 AMP	0.500	0.380
LM317T	0.740	0.675

#### TRANSISTORS

DEVICE	50+	100+
BC108C	0.125	0.123
BC109C	0.125	0.121
BC182L	0.080	0.060
BC184L	0.080	0.060
BC212L	0.065	0.060
BC214L	0.065	0.068
BC547L	0.055	0.045
BC548C	0.055	0.045
BC549C	0.050	0.045
BC558C	0.050	0.045
BD131	0.420	0.410
BFY51	0.223	0.212
BFY51	0.223	0.212
TP41C	0.220	0.190
2N3055	0.440	0.420

#### LED'S 5mm

COLOUR	50+	100+
RED	0.070	0.064
YELLOW	0.080	0.070
GREEN	0.080	0.070

#### LSTTL

DEVICE	100+
74LS00	0.130
74LS01	0.150
74LS02	0.130
74LS04	0.130
74LS08	0.135
74LS10	0.130
74LS11	0.130
74LS14	0.210
74LS22	0.155
74LS42	0.245
74LS47	0.410
74LS48	0.550
74LS51	0.135
74LS86	0.150

#### DIODES

TYPE	50+	100+
1N4148	0.020	0.016
82Y88C5V1	0.045	0.034
W005	0.200	0.192
W04	0.215	0.210

### RESISTORS

¼ WATT CARBON 5% V24 RANGE  
MIXED VALUE PRICING  
100+ 0.008  
1K+ 0.006  
5K+ 0.005  
10K+ 0.0045

### POTENTIOMETERS

LIN OR LOG STANDARD SIZE  
MIXED VALUE PRICING  
50+ 0.32  
100+ 0.30

### PRESETS

HORIZONTAL OR VERTICAL  
MIXED VALUE PRICING  
MINIATURE 50+ 0.095  
100+ 0.090  
STANDARD 50+ 0.095  
100+ 0.090

ALL PRICES ARE PRICE EACH, PER QUANTITY UNLESS OTHERWISE STATED.

ALL TRADE PRICES EXCLUDE VAT.

PRICES SUBJECT TO CHANGE

PRICES OPEN TO NEGOTIATION ON SMALLER QUANTITIES TO MSC CENTRES ETC.

PLEASE ADD £1.00 CARRIAGE TO ALL ORDERS.

LARGER QUANTITIES P.O.A.

ALSO STOCKED: ACCESSORIES, BOOKS, CABLES, CAPACITORS, LEADS, TEST GEAR ETC. SAE FOR CATALOGUE/LISTS.

## COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on

REF: ETI/2/88

06267 79398

NAME \_\_\_\_\_

- City & Guilds Exam 271
- Radio Amateur Licence
- Micro-processor
- Introduction to Television

Radio & Telecommunications Correspondence School, 12, Moor View Drive, Teignmouth, Devon. TQ14 9UN.

## KITS AND READY BUILT

**ELECTRONIC KITS**—For those Winter evenings. SAE for details: COVE ELECTRONICS, 7 St. Anne's Avenue, Southbourne, Bournemouth, Dorset BH6 3JR.

## ELECTRONICS TECHNICIANS

Updating Courses  
London Electronics College,  
(Dept ET1), 20 Penywern Road,  
London SW5 9SU. 01-373 8721.

## PCB'S

**PRINTED CIRCUIT BOARDS**  
Need 100 off...or just one? You can send the Artwork (1:1 single sided) for your boards or let me work, at little extra cost, from your own drawings. Enquiries: Watling Wire PCB Production, 52 Watling Street, Nuneaton, Warwickshire, CV11 6JL or telephone (0203) 382296.

# Sonolux

PCBs from your own artwork from as little as £4.00 + p&p (excluding VAT) Send SAE or telephone for details:

**SONOLUX LTD**  
29-31, Corporation Street,  
Lincoln. LN2 1HL  
Telephone: (0522) 510013

## KITS

**AMAZING KITS: BUG-87** matchbox sized surveillance transmitter with super sensitive microphone can be received by any FM/VHS radio, £4.95 inc. **ROBO-VOX** instantly transforms your voice into Dalek/Robot type also amazing feedback/Sound effects possible, £11.95 inc. **ROBOT CIRCULAR** unique radio controlled robot can also be converted to control via computer £16.95 inc. **EDU-SCOPE** Build your own Oscilloscope with flat LED screen complete kit of parts excluding case £39.99 inc. All enquiries send SAE. **IMAGINA-TRONICS**, Aberdeen House, The Street, Charlwood, Surrey RH6 0DS.

**MICRO TRANSMITTER KIT**, 500m Range, tunable 88-115MHz, sensitive microphone, £3.95. Cheques/PO's to Quantek Ltd., (ETI), 267 Rednal Road, Kings Norton, Birmingham B38 8EB.

## MISCELLANEOUS

**HEATHKIT U.K.** Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

## SATELLITE

# LSC

SEE IT LIVE AT OUR SHOWROOM  
EVERYTHING FROM KITS  
TO DELUXE SYSTEMS  
SURVEY • INSTALLATION • SERVICES  
LONDON SATELLITE CORPORATION LTD.  
DEPT. ET, 17 REGINA ROAD, SOUTHWALL,  
MIDDX. UB2 5PL. TEL: 01-571 9605  
Open: 10 a.m.-7 p.m.

## BOOKS

**PARAPHYSICS** Journal (Russian Translation); Psychotronics; Kirlianography, Heliphonic Music, Telekinetics. Computer Software. S.A.E. 4" x 9", Paralab, Downton, Wiltshire.

## PLANS & DESIGNS



Design and build your own electronic dashboard.  
Plans, instructions, circuits, parts lists  
£4.95 inc p&p

**BURLINGTON MOTOR CO. LTD.**  
(G8) ARCH 39M, BATH PLACE,  
LEAMINGTON SPA, CY3 3AQ.


## EQUIPMENT

WOULD YOU BUY A CAR  
WITHOUT A TEST DRIVE?  
THEN WHY BUY A MIXER  
WITHOUT A TEST DRIVE?

Thinking about a new project — from a small Mixer to a large studio complex — come and talk over ideas with the people who offer manufacturing and user experience at our new premises:

Unit D, 318 High Road,  
Bentley, Essex SS7 5HB  
TO TAKE THAT TEST DRIVE —  
PHONE 0268-793381

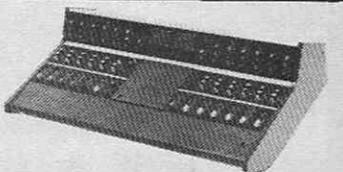(Weekend Committee visits  
welcome by prior arrangement)



# PARTRIDGE ELECTRONICS

Head Office, 56 Fleet Road, Bentley, Essex SS7 5JN  
Telephone 0268-793255

**RING 01-437 0699  
FOR ADVERTISING  
DETAILS**

**MAKE SOME SPECTRUM CeNce**  
Simple Computer Controller for Machinery and Models using your Sinclair Spectrum.

A little black box which plugs into the expansion socket of any Spectrum and enables you to drive two small to medium stepper motors (up to 2AMPS per phase) or up to 8 DC motors, relays, lamps or any other DC device.

Simple to Program and built by an engineering firm for its own use. You can use it for CNC turning, milling or coordinate drilling.

Reliable. Prototype still running after three years use. We provide interface, instructions, software, hints and examples. Price: £125 inc carriage and VAT. Power supplies and Stepper Motors available. We will be pleased to quote for larger units.

**P.R. PRODUCTS, PARK MILL, HOBSON STREET, MACCLESFIELD, CHESHIRE SK11 8BE Tel: (0625) 22800.**

## ALARMS

# ALARMS

FREE BOOKLET

on  
**BURGLAR ALARMS**

with  
**LOWEST U.K. DIY PUBLISHED PRICES**

PHONE OR WRITE FOR YOUR COPY

051-523 8440

**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU



## RETAIL OUTLETS

### LIVERPOOL

#### PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154  
47 Whitechapel. Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'

Open: Tues-Sat 9.30-5.30

### LONDON

#### CRICKLEWOOD

FOR COMPONENTS  
LOTS OF NEW DEVICES  
LOTS OF LOWER PRICES  
Phone for our catalogue:  
01 452 0161/450 0895 Telex: 914 977  
40 Cricklewood Broadway,  
London NW2 3ET.

### TYNE AND WEAR

ELECTRONIC COMPONENTS AND KITS



STATION ROAD, CULLERCOATS,  
NORTH SHIELDS, TYNE & WEAR NE30 4PQ  
091 251 4363

New 1988 Catalogue now available £1.85 incl p&p. MON-SAT 9.30 to 5.30  
CLOSED THURS.

ELECTROMART

ELECTROMART

LEAP INTO 1988 WITH ETI.  
CALL JULIE CAPSTICK ON 01-437 0699  
FOR ADVERTISING DETAILS

## COMPONENTS

# T-systems Ltd

COMPUTER SYSTEMS AND COMPONENTS

3" CF2 Maxell disks .....	£1.90
3.5" unbranded DS disks .....	£0.90
5.25" unbranded disks, DS96, TPI .....	£0.35
Bulk storage, 5.25"/50 .....	£6.90
Bulk storage, 3.5"/80 .....	£8.00
Epson MX/FX80 ribbon .....	£2.75
Epson MX/FX100 ribbon .....	£3.10
Epson LX80/86 ribbon .....	£2.50
M/Tally MT80 ribbon .....	£2.90
Printer cable, PC1512/IBM .....	£7.95

All prices inc. P&P, please add VAT at 15%.

T-STYSTEMS LTD.

The Signal Cabin, 61 High Street, Orpington, Kent BR6 0JF.  
Access card accepted. Tel: 0689 22196

### PROMS - EPROMS - PALs ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

Typical prices (excluding VAT)  
(Data Entry P&P extra)

2716 £4.20 ..... 2732 £3.85  
2764 £2.85 ..... 27128 £4.40

**BIPOLAR PROMS from £1.35**

e.g. 82S123, 18S030, 74S288

**PALs, PLDs etc. from £3.26**

e.g. 82S153, 16L8, EP310

Full design and prototyping service.

Any quantity programmed - SAE or

phone for details.

P.L.S., 80 Central Road,

Worcester Park, Surrey, KT4 8HU

Phone: 01-330 6540

### FREE DELIVERY

12" 8Ω 150W MONACOR  
PA POWER SPEAKER £25

Just send your name &  
address with number

required, to:  
**STRACHAN ELECTRONICS**

9 Croall Place, Edinburgh EH7 4LT  
Pay Postman on delivery.

S.H. COMPONENTS presents  
18 pages of very competitively  
priced semi-conductors,  
switches, Opto Electronics, etc.  
Send 50p to: 17 Beeley Road,  
Grimsby, S. Humberside.

**COPY DEADLINE  
FOR APRIL ISSUE  
= 26 JANUARY**

Carbon Film Resistors 1/4W E24 series 0.51R to  
10MΩ - 1p 100 off per value-75p 1000 off in even  
hundreds per value-£7 Metal Film 1/4W 10R0 to 1MΩ  
5% E12 series-7p 1% E24 series-3p 1/2Watt  
metal/carbon film E24 series 1R0 to 10MΩ-1p 1  
Watt metal/carbon film E12 series 4R7 to 10MΩ-5p  
BC107/18-12p BC547/18-9-9p BC182L 184L-10p  
BFY50/51/52-20p 2N3055-50p TIP31A, 32A-25p  
TIP41, 42-40p

Tantalum head subminiature electrolytics (Mids/Volts)  
0.1/35, 0.22/35, 0.47/35, 3.3/16-14p 4.7/35-15p  
2.2/35, 4.7/25, 10/5-15p 4.7/35, 6/8/16-16p  
10/16-22/6-20p 22/16-30p 33/10-30p 47/10-35p  
100/6-40p

Aluminium Electrolytics (Mids/Volts)  
1/50, 2.2/50, 4.7/25, 4.7/50, 10/16, 10/25, 10/50-  
5p 22/16, 22/25-8p 22/50, 47/16, 47/25, 47/50-8p  
100/16, 100/25-7p 100/50-12p 100/100-14p  
220/16-18p 220/25, 220/50-10p 470/16, 470/25-  
11p 1000/25-18p 1000/35, 220/25-22p 4700/25-70p

Miniature Polyester Capacitors 250V Wkg. Vertical  
Mounting.  
01, 015, 022, 033, 047, 068-4p 0.1-5p 0.15, 22-  
6p 0.47-8p

Mylar Capacitors 100V Wkg. Vertical Mounting E12  
Series.  
1000p to 8200p-3p 01 to 068-4p 0.15p 0.15, 0.22-6p

Subminiature Ceramic Plate 100V Wkg. E12 Series  
Vertical Mounting.  
2%, 1% 158 to 47F-3p 56P to 330P-4p 10% 390P to  
4700P-4p Ceramic plate/disc E6 Series 50V 22P to  
047-2p

Polystyrene Capacitors 63V Wkg. E12 Series Axial  
Mounting.  
10P to 820P-3p 1000P to 10,000-4p 12,000P-5p  
1N4148-2p 1N4002-4p 1N5404-14p W01 bridge-25p  
0A91-6p AA143-8p W005-20p 1N4006-6p Zener  
diodes E24 series 3V3 to 33V 400mW-8p 1 watt-12p  
L.E.D's Red, Green & Yellow 3mm & 5mm-10p 8mm-  
35p 20mm fuse 0.1A to 5A quick blow-5p Anti Surge-  
8p High Speed drills 0.8mm, 1.0mm, 1.3mm, 1.5mm,  
2mm-25p Expo Reliant drilling machines 12V d.c. with  
improved 3-jaw chuck-6.50 Nicas AA-80p HP11-12  
PP3-E4.20 Universal Chargers-£6.50 Glass reed  
switches single pole make contacts-8p Magnets-12p

VAT inclusive. Return postage 20p (free over £5). Lists  
free.

THE C.R. SUPPLY CO., (DEPT ETI),  
127 Chesterfield Road,  
Sheffield S8 0RN. Tel. 557771

## CLASSIFIED COUPON

ELECTRONICS TODAY INTERNATIONAL, CLASSIFIED ADVERTISEMENT  
DEPT, No. 1 GOLDEN SQUARE, LONDON W1R 3AB.

PLEASE DEBIT MY ACCESS/BARCLAYCARD NO. EXPIRY DATE -

FOR SALE   
  COMPONENTS   
  WANTED   
  KITS   
  PCB'S   
  OTHERWISE STATE


Rates: Lineage 51p per word (VAT inclusive) minimum £7.65  
semi-display £12.20 per single column cm. No reimbursements  
for cancellations. All ads must be pre-paid.

Name .....

Address .....


Daytime Tel. No: .....

Signature ..... Date .....

# HART

**HART ELECTRONICS** are specialist producers of kits for designs by **JOHN LINSLEY-HOOD**. All kits are **APPROVED** by the designer.
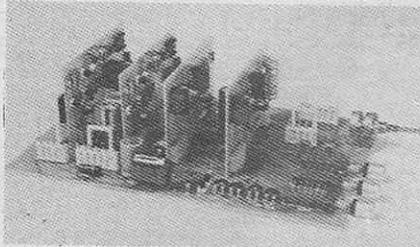
### LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit ..... **£33.70**  
 VU Meters to suit ..... **£2.30 each**  
 Reprints of original Articles ..... **75p no VAT**  
 860X Stereo Mic Amplifier ..... **£8.70**

### LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hoods articles in 'HiFi News'. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35. 35 Watt. Discount price for Complete Kit ..... **£98.79**  
 K300-45. 45 Watt. Discount price for Complete Kit ..... **£102.36**  
 RLH4&5. Reprints of Original Articles from 'Hi-Fi News' ..... **£1.05 no VAT**

### LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchrodyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains easy to build. The Synchrodyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of it's sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

### STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.

K900W Stereo Kit with Wound Coils and Twin Meter Drive ..... **£65.67**  
 RSJ1 Reprints of Original Articles ..... **£1.30 no VAT**

### HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

**HC20 Permalloy Stereo Head.** This is the standard head fitted as original equipment on most decks ..... **£7.66**  
**HS16 Sendust Alloy Super Head.** The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response ..... **£14.86**  
**HO551 4-Track Head** for auto-reverse or quadrophonic use. Full specification record and playback head ..... **£14.60**  
**HX100 Stereo Permalloy R/P head.** Special Offer **£2.49**  
**MA481 2/2 Language Lab R/P head.** ..... **£13.35**  
**SM166 2/2 Erase Head.** Standard mounting. AC type ..... **£8.85**  
**SM150 2/2 Erase Head.** DC Type ..... **£3.60**  
**HQ751E 4/4 Erase Head** for Portastudio etc. .... **£46.80**  
 Full specifications of these and other special purpose heads in our lists.

### HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only **£4.66** plus VAT and 50p postage.

**Tape Head De-magnetiser.** Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback ..... **£4.54**  
 Curved Pole Type for inaccessible heads ..... **£4.85**

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

**INLAND**  
 Orders up to £10 - 50p  
 Orders £10 to £49 - 1£  
 Orders over £50 - £1.50

**OVERSEAS**  
 Please send sufficient to cover Surface or Air Post as required.

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE  
 (0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED

**HART**  
 HART ELECTRONIC KITS LTD  
 4 PENYLAN MILL  
 OSWESTRY, SHROPSHIRE  
 SY10 9AF

### 19" RACK MOUNTING EQUIPMENT CASES

This new range of 19" rack equipment cases have been designed with economy and versatility as their objective. These cases are supplied as a flat pack kit with assembly instructions. The equipment cases feature a black powder coat 1/4" (3mm) aluminium frontpanel with the rest of the case constructed from 7mm or 9mm 'Stelvetite' PVC coated steel. All kits include front panel handles and rubber feet.

They are available in the following popular sizes with all the units having a standard front panel width of 19", and an enclosure width of 17 1/2" (433mm) by a depth of 10" (254mm).

ORDER CODE	HEIGHT	PRICE
U1	1 3/4" (44mm)	16.00
U2	3 1/2" (88mm)	18.00
U3	5 1/2" (133mm)	20.00
U4	7" (178mm)	22.00
M6U Sloped mixer console		£25.50


All prices Exclude V.A.T.  
 Please include £2.50 + VAT. Per Item  
 For Post & Packing.  
 Flat pack size = 500 x 260 x 32  
 Maximum weight = 1.5Kgs.

Blanking Panels, Racking Consoles and Rack Cabinets also available.

Please send S.A.E. for further details  
 \* TRADE ENQUIRIES WELCOME \*

Tel. 0275 823983 for Access/Visa card sales for immediate despatch or send cheque with order to:

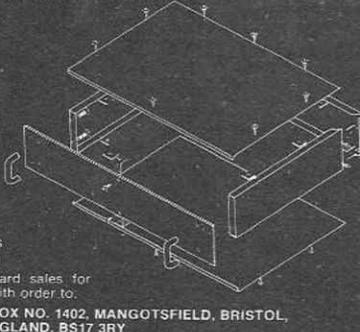RACKZ PRODUCTS PO, BOX NO. 1402, MANGOTSFIELD, BRISTOL, ENGLAND, BS17 3RY



### ADVERTISERS' INDEX

Audiokits .....	48	Photoplay .....	IFC
BK Electronics .....	49, IBC	Rackz Mounting Products .....	66
Cricklewood Electronics ..	22	R.T.V.C. ....	23
Display Electronics .....	8	Specialist Semicon Devices ..	30
Electromech Industries .....	58	Stewarts of Reading .....	22
Greenbank Electronics .....	48	Subscriptions .....	10, 51
Hart Electronics .....	66	Suma Designs .....	23
Henry's Audio Electronics ..	55	TK Electronics .....	52
Maplin Electronics .....		TJA Development .....	35
Supplies .....	OBC	XEN Electronics .....	23
Microkits .....	66	Zenith Electronics .....	35
Omni Electronics .....	66		

### microkit LTD 0536 744664 24 hr 7 days/week

74TTL LS HC 00 20 25 02 20 25 04 20 25 06 20 25 10 20 25 11 20 25 14 20 29 20 20 29 21 20 29 27 20 29 42 49 51 20 25 74 20 39 85 59 86 20 49 123 60 55 132 49 138 40 49 139 40 49 153 45 59	157 40 55 158 40 55 161 55 55 164 55 55 165 60 75 166 60 60 WD2797 19.00 WD1797 19.00 WD9216 14.26 7812 30 78M12 30 75154 90 ADC0808 9.90 LM311 40 LM324 40 LM337 1.20 LM340 55 LM358 45	LM5900 40 OP07CP 65 NE555 18 TL074 90 TL072 50 TL082 45 TL084 45 ULN2004 70	MEMORIES DRAM 5V NMOS 4164 64k x 1 £0.88 41256 256K x 1 £2.39 4416 16K x 1 £3.30 41464 64K x 1 £3.30 SRAM 5V NMOS 2114LP 1K x 8 £1.50 2128LP 2K x 8 £2.50 SRAM 5V CMOS 6116LP 2K x 8 £1.10 6264LP 8K x 8 £2.40 62256LP 32K x 8 £14.50 EPROM 5V NMOS 2716 2K x 8 £2.70 2732 4K x 8 £2.65 2764 8K x 8 £2.45 27128A 16K x 8 £2.70 27256 32K x 8 £3.75 27512 512K x 8 £9.70
--	---	--	--

ADD VAT 15% ORDERS UNDER £25 ADD £1 P&P OVER £25 POSTAGE FREE  
 ORDERS DISPATCHED SAME DAY BEFORE 3.30PM  
 DEPT (E7) 18 KOLDERMEADOW A, CORBY NORTHANTS NN18 9AJ

### OMNI ELECTRONICS

for a comprehensive range of components aimed at the enthusiast:

1N4148	4p	1.5A 100V bridge	36p
1N4001	5p	5mm red leds	13p
LM741	25p	5mm green leds	14p
7805	50p	400mW zeners	10p
OA90/OA91	13p	1.3W zeners	17p
Skeleton presets	11p	Red/black phono plugs	14p
UM 1286 modulator	7.95	Quality panel meters	5.98
98mm cable ties	2.00/100	Velleman kits/Babani books	

The above is a sample of our range and includes VAT. P&P 60p. Send for catalogue 20p + 18p or 13p stamp. Shop open: Monday-Friday 9am-6pm, Saturday 9am-5pm.

174 Dalkeith Road  
 EDINBURGH EH16 5DX  
 031-667 2611

# OMP POWER AMPLIFIER MODULES

## OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof


Supplied ready built and tested.




**OMP100 Mk II Bi-Polar** Output power 110 watts R.M.S. into 4 ohms. Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. -118dB. Sens for Max. output 500mV at 10K. Size 355 x 115 x 65mm. **PRICE £33.99 + £3.00 P&P.**



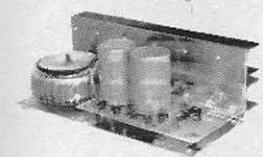**OMP/MF100 Mos-Fet** Output power 110 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 80. Slew Rate 45V/uS, T.H.D. Typical 0.002%. Input Sensitivity 500mV, S.N.R. -125dB. Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**




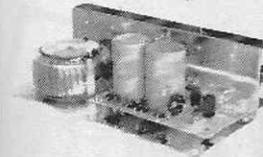**OMP/MF200 Mos-Fet** Output power 200 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 250. Slew Rate 50V/uS, T.H.D. Typical 0.001%. Input Sensitivity 500mV, S.N.R. -130dB. Size 300 x 150 x 100mm. **PRICE £62.99 + £3.50 P&P.**



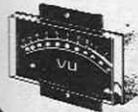**OMP/MF300 Mos-Fet** Output power 300 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz - 3dB, Damping Factor 350. Slew Rate 60V/uS, T.H.D. Typical 0.0008%. Input Sensitivity 500mV, S.N.R. -130dB. Size 330 x 147 x 102mm. **PRICE £79.99 + £4.50 P&P.**

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order Standard or P.A.



**Vu METER** Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

**LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S.** Cabinet Fixing in stock. Huge selection of **McKenzie Loudspeakers** available including Cabinet Plans. Large S.A.E. (28p) for free details.



**POWER RANGE**  
 8" 50 WATT R.M.S. Hi-Fi/Disco.  
 20 oz magnet 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz Freq Resp to 6KHz Sens. 92dB PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.  
 12" 100 WATT R.M.S. Hi-Fi/Disco  
 50 oz magnet 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq 25Hz Freq Resp to 4KHz Sens. 95dB PRICE £28.60 + £3.00 P&P ea

**McKENZIE**  
 12" 85 WATT R.M.S. C1285GP Lead Guitar/Keyboard/Disco.  
 2" ally voice coil. Ally centre dome. Red. Freq. 45Hz. Freq. Resp. to 6-5KHz. Sens. 98dB. PRICE £34.57 + £3.00 P&P ea.  
 12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone. Res. Freq. 45Hz Freq. Resp. to 14KHz. PRICE £35.35 + £3.00 P&P ea.  
 15" 150 WATT R.M.S. C15 Bass Guitar/Disco.  
 3" ally voice coil. Die cast chassis. Res. Freq. 40Hz Freq. Resp. to 4KHz. PRICE £66.39 + £4.00 P&P ea.  
 10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.  
 2" voice coil. Res. Freq. 75Hz Freq. Resp. to 7.5KHz Sens. 98dB. PRICE £23.72 + £2.00 P&P.  
 10" 200 WATT R.M.S. C10200GP Guitar/Keyboard/Disco  
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £47.49 + £3.00 P&P.  
 15" 200 WATT R.M.S. C15200 High Power Bass.  
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £73.26 + £4.00 P&P.  
 15" 400 WATT R.M.S. C15400 High Power Bass.  
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £94.12 + £4.00 P&P.

**WEM**  
 5" 70 WATT R.M.S. Multiple Array Disco etc.  
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £22.00 + £1.50 P&P. ea.  
 8" 150 WATT R.M.S. Multiple Array Disco etc.  
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £32.00 + £1.50 P&P. ea.  
 10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £36.00 + £2.00 P&P. ea.  
 12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £47.00 + £3.00 P&P. ea.

**SOUNDLAB (Full Range Twin Cone)**  
 5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
 1" voice coil. Res. Freq. 63Hz Freq. Resp. to 20KHz Sens. 86dB PRICE £9.99 + £1.00 P&P ea  
 6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
 1" voice coil. Res. Freq. 56Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £10.99 + £1.50 P&P ea  
 8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
 1 1/2" voice coil. Res. Freq. 38Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £12.99 + £1.50 P&P ea.  
 10" 60 WATT R.M.S. Hi-Fi/Disco etc.  
 1 1/2" voice coil. Res. Freq. 35Hz Freq. Resp. to 15KHz Sens. 89dB PRICE £16.49 + £2.00 P&P

**PANTEC HOBBY KITS.** Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 44mm (9 volt) **Price: £8.62 + 75p P&P.**  
**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) **Price: £14.49 + 75p P&P.**  
**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). **Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.**



3 watt FM Transmitter

PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E. 28p STAMP FOR CURRENT LIST

## BURGLAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units, complete with interconnection cable **FULLY GUARANTEED.**

**Control Unit** - Houses microwave radar unit, range up to 15 metres, adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed, 30 second exit and entry delay.

**Indoor alarm** - Electronic swept freq. siren. 104dB output.

**Outdoor Alarm** - Electronic swept freq. siren. 98dB output. Housed in a tamper proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

**SAVE £138.00** Usual Price £228.85  
**BKE's PRICE £89.99 + £4.00 P&P**  
 Why buy a collection of self assembly boards!

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



## OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R.M.S. per cabinet. Sensitivity 1W. 1mtr. dB.

**OMP 12-100 Watts 100dB. Price £149.99 per pair.**

**OMP 12-200 Watts 102dB. Price £199.99 per pair.** Delivery: Securicor £8.00 per pair



## OMP 19" STEREO RACK AMPS



**Professional 19" cased Mos-Fet stereo amps.** Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. **Three models (Ratings R.M.S. into 4ohms). Input Sensitivity 775mV**

**MF200 (100 + 100)W. £171.35 Securicor**  
**MF400 (200 + 200)W. £228.85 Delivery**  
**MF600 (300 + 300)W. £322.00 £10.00**

## 1 K-WATT SLIDE DIMMER

- \* Control loads up to 1Kw
- \* Compact Size. 4 1/2" x 1" x 2 1/2"
- \* Easy snap in fixing through panel/cabinet cut out
- \* Insulated plastic case
- \* Full wave control using 8 amp triac
- \* Conforms to BS800


\* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.

**PRICE £13.99 + 75p P&P**
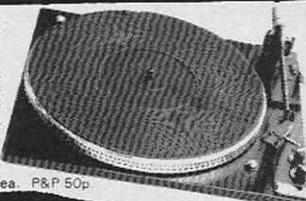
## BSR P295 ELECTRONIC TURNTABLE

- \* Electronic speed control 45 & 33 1/3 r.p.m.
- \* Plus Minus variable pitch control
- \* Belt driven
- \* Aluminium platter with strobed rim
- \* Cue lever
- \* Anti-skate (bias device)
- \* Adjustable counter balance
- \* Manual arm
- \* Standard 1/2" cartridge fixings

Supplied complete with cut out template \* D.C. Operation 9.14v D.C. 65mA  
**Price £36.99 - £3.00 P&P.**



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p.


## PIEZO ELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

- TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. **Price £4.90 each + 40p P&P.**
  - TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £5.99 each + 40p P&P.**
  - TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. **Price £6.99 each + 40p P&P.**
  - TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz) Suitable for high quality Hi-Fi systems and quality discos. **Price £9.99 each + 40p P&P.**
  - TYPE 'E' (KSN1038A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. **Price £5.99 each + 40p P&P.**
- LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm **Price £3.99 + 40p P&P.**
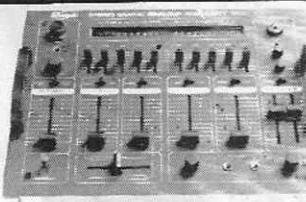
## STEREO DISCO MIXER

**STEREO DISCO MIXER** with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following:—  
 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot. L & R. Master Output controls. Output 775mV. Size 360 x 280 x 90mm.  
**Price £134.99 - £3.00 P&P**



# B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED



1988 BUYER'S GUIDE TO ELECTRONIC COMPONENTS

# Maplin



**UNIQUE**



Make your own  
**DIGITAL WATCH KIT**  
1/2 PRICE OFFER  
**ONLY £1**  
SEE INSIDE COVER.  
NO SOLDERING.  
SUITABLE FOR  
AGES 10+

**NEW! RADIO CONTROL MODELS  
+ 100'S OF NEW PRODUCTS  
AT LOW, LOW PRICES  
£1.60**

**VISIT OUR NEW  
SHOP IN BRISTOL  
NOW OPEN AT  
302 GLOUCESTER ROAD  
Tel: (0272) 232014**

**GET YOUR COPY OF THE NEW MAPLIN CATALOGUE ON SALE NOW**

**AVAILABLE NOW IN ALL W.H. SMITH STORES GET YOUR COPY NOW!**

Pick up a copy from any W.H. Smith for just £1.60 or post this coupon now to receive your copy by post for just £1.60 + 40p p & p. If you live outside the UK, send £2.75 or 12 International Reply Coupons. (enclose £2.00)

Name

Address

Post Code

Essex SS6 8LR

Send to Maplin Electronic Supplies Ltd., P.O. Box 3, Rayleigh, Essex, SS6 8LR