




ELECTRONICS
TODAY INTERNATIONAL

OCTOBER 1993 £1.95

ELECTRONIC PICTURE



A moving LED display

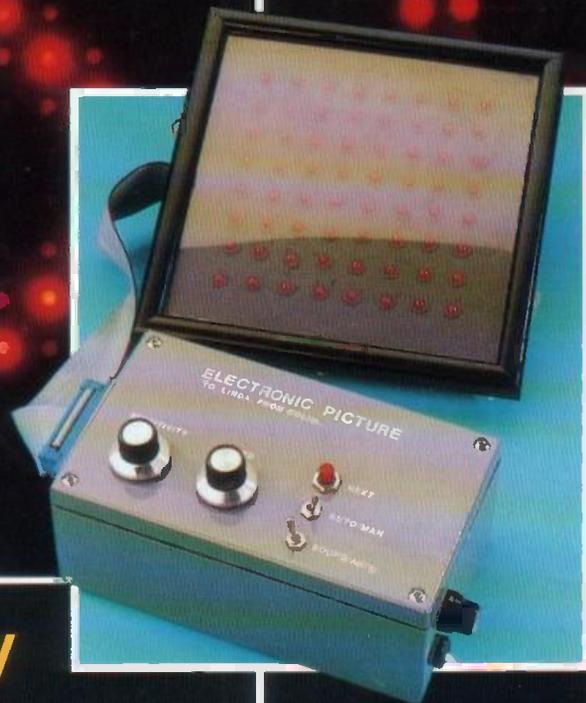

HOT WIRE CUTTER
TRANSISTOR POWER AMP
SEGA BOX

CONTINUITY TESTER

Use the PCB to check out circuits

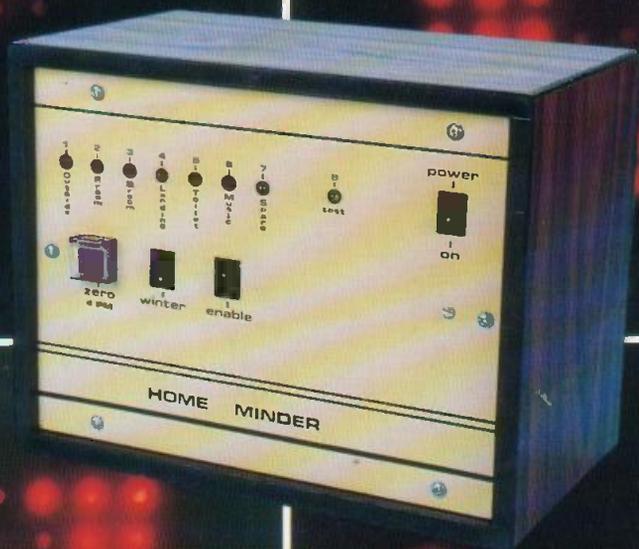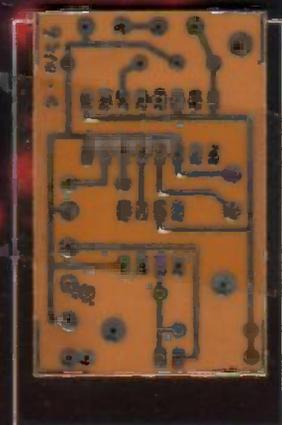

HOME MONITOR

A Minder to keep the burglars away

10

9 770142 722023

Argus SPECIALIST PUBLICATION **BEST VALUE**

At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...

... call now for details.

Board Capture

Schematic Capture Design Tool

£395

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back-annotation from BoardMaker2

Board Maker

BoardMaker1 - Entry level


£95

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

BoardMaker2 - Advanced level

£295

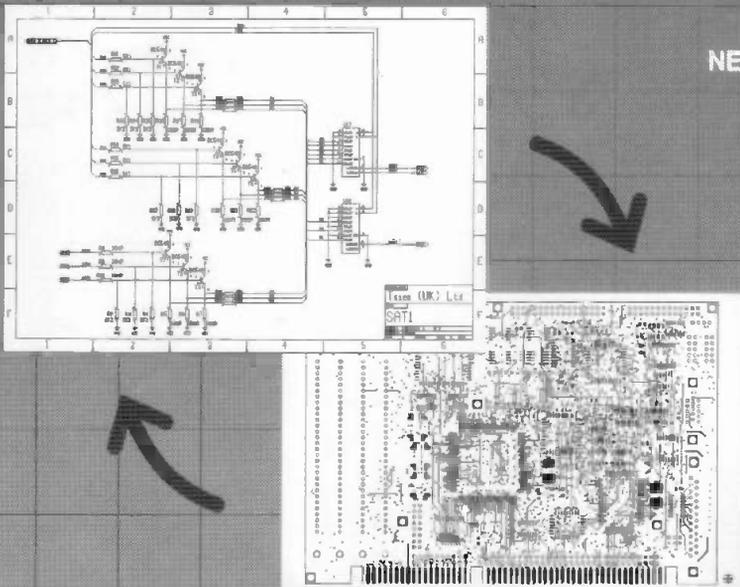- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC



NEW

Board Router

Gridless re-entrant autorouter

£200


- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

Call, write or fax for more information or a free evaluation kit :

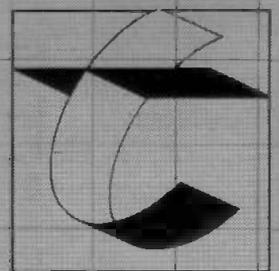Tsien (UK) Limited
Cambridge Research Labs
181A Huntingdon Road
Cambridge CB3 0DJ
Phone : (0223) 277 777
Fax : (0223) 277 747




tsien



Features & Projects



Volume 22 No.10
October 1993

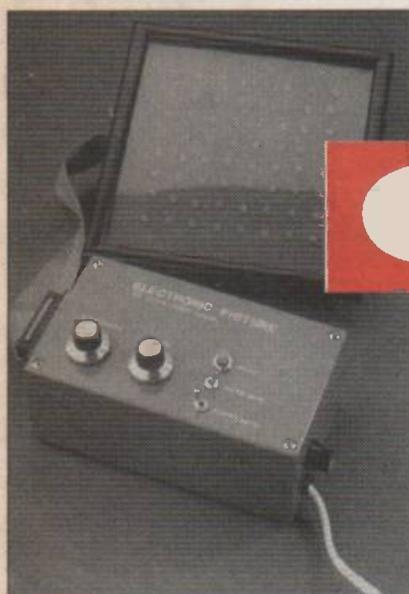

Page 18

Hot Wire Cutter	12
Colin Meikle has come up with a temperature controlled cutter to tackle intricate carving of plastics.	
Electronic Picture	18
Whether it is for visual amusement or as part of a bigger message display system this project should enlighten you to the simple usage of EPROMs. Colin Meikle reports.	
AutoMate Mixer	26
This month Mike Meechan looks at 'Pots and Pans' and their connection with routing.	
Continuity Tester	30
Continuing with our 'test-gear' series, Robert Penfold builds a continuity tester using our cover PCB.	
Sega Box	37
Keep your kids happy and save your fingers from plug pulling with this handy little box. A quick project from David Silvester.	
Transistor Amplifier	38
Back to the good old days of transistor amplifier design with this contribution from L Boullart.	
Home Minder	47
You could put your mind at rest and the burglar on guard by using this 'magic box'. It switches on various lights and appliances throughout the house at various times. Bob Noyes provides the details.	

Contents

Regulars

Open Channel	4
News	5
News Stateside	8
Read/Write	16
PCB Service	60
PCB Foils	61

Editorial

by Paul Freeman


SUBSCRIPTION
& BACK ISSUES
HOTLINE
0737 768611

It is that time of year again when we issue our Reader Survey. We like to know your comments regarding the magazine in order to steer it in the direction you want it to go. So please fill in the pages and return it to us (postage paid) as soon as you can. Those who reply early will be sent the new Maplin catalogue in return for your efforts.

A time for security?

Home security is very much on our minds these days as a result of rising crime. From this you'd expect the home security business to be a growth area of consumer electronics, and you'd be right.

Providing your own home security can prove an intriguing challenge and also cheap at half the price. This is of course assuming high security is required. Also intriguing is what deterrents could be produced without falling foul of the law. Alternatively you could build this issue's Home Minder to provide a psychological deterrent to any intruder, by making them think someone is in the building.

And finally, it's a pleasure to see a transistor amp project in this issue after all the hype we have seen and heard about valves. Thank you for taking the time to read ETI.

All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors in the contents of this magazine or for any loss however arising from such errors, including loss resulting from the negligence of our staff. Reliance placed upon the contents of this magazine is at readers own risk.

OPEN CHANNEL



There's a whole lot going on in the world of personal telecommunications these days. For a start, I use the term personal telecommunications rather than the synonymous term, mobile telecommunications.

CB started the personal telecommunications revolution because once users felt the benefits of being able to communicate from the wheel, they began to question why this couldn't apply to other situations. Its great being able to chat with others in the immediate area - but wouldn't it be so much better if it could be as a connection into, say, the public telephone system. Then a mobile user could call up (or receive calls from) anyone else in the world who has a telephone or a similar mobile communications device.

Cellular telephony allows this and various systems have been set up in the UK (Cellnet and Vodafone) as well as in Europe and around the world. They all share the same basic philosophy of having literally hundreds of small local base transceivers picking up signals and retransmitting them to and from other base transceivers or users.

Another mobile phone service known as CT2 (Cordless Telephone type 2) has started up recently in the guise of telepoint, with the only surviving telepoint system known as Rabbit, operated by Hutchison Telecom. However, Rabbit handsets can't receive calls, and outgoing calls can only be made within a strictly limited range (within 200 metres) of a base station. Handsets and calls are, however, much less expensive than those of existing cellular systems.

Cellphones, in their original state, were generally mobile devices, simply because power requirements in the old days meant that a high-current 12V supply was needed for the output power. Over the last year, low-current low-voltage cellphones have become commonplace, giving users access to totally portable and pocket-sized cellular telephones.

Around 80% of cellphones currently sold are of this hand-held category, which signifies a general move from mobile telecommunications to those of a more personal nature. In the UK both Cellnet and Vodafone are tremendously successful. Vodafone is expecting to sign up its millionth customer at the beginning of next year. With user-numbers like this, it's important for us all to see that personal telecommunications - with the accent on personal - is a big thing, and not just a flash in the marketing departments pan. When the landline telephone was invented there were probably people who said it would never catch on, too. Like it or not, personal telecommunications is here and is set to stay in no small way. If you haven't got a personal handset yet, you will have!

Cellular systems in this current category are of an analogue nature and analogue electronic devices are generally destined for the scrapyard. Sooner or later digital devices will take their place, with higher quality and less expense. Cellular systems have their limitations though. For a start, they are fast approaching their maximum numbers of users. Each communication channel has quite a large bandwidth requirement which means only a limited number of channels can be allocated within any given frequency slot. Secondly, analogue systems are prone to interference and speech

quality problems. Thirdly, they are still expensive with only businessmen and well-to-do consumers able to afford them.

Already starting operation are the latest forms of personal telecommunications, operating on the cellular basis of small local base transceivers but in a digital manner. Being digital, communications between users are less liable to interference and with high-quality audio. Eventually the hand-held or mobile will be cheaper than their analogue counterparts.

The digital networks involved in these cellular systems are of two types. First is the global system for mobiles (GSM) network in which all connected users are able to access any phone or cellular user world-wide with high digital quality. Not only can this be done in the country where the unit was purchased, but in any country which also has a GSM network. Such inter-country usage is called roaming and current analogue cellular systems don't properly allow it. Greater numbers of users can be connected, too, sufficient for every current telephone user to have at least one. Vodafone has the first GSM in the UK, called EuroDigital.

The second type of digital cellular system to start is the personal communications network (PCN). First off the ground here are Mercury's One-2-One and Vodafone's MetroDigital. A third, operated by Hutchison Telecom, will start next year and others may be allocated the following year.

There are several similarities between PCNs and GSM, apart from the obvious that they are both digital. However, it's their differences which are most important. PCNs are envisaged more as local networks, aimed at the mass consumer market, while GSM networks are considered to be for the more business-oriented user who travels internationally.

Interestingly, it looks like handsets used on GSM and PCN networks will be interchangeable, with premium charges, on GSM networks. Pricing, as it happens, is an important consideration. PCNs are set to be considerably cheaper than current cellular systems, while GSM networks should eventually end up at around the same as current systems. Its the price which will make or break the systems, after all. Cheap enough and consumers and business users alike will be falling over themselves to get a handset connected to the respective networks. Too pricey (or no cheaper than current cellular prices) and what's the point? Its going to take a year or two until the PCN and GSM networks are fully up-and-running, so customers might stick with analogue systems for a while too, to avoid confusion.

Over the last year, current analogue networks have already begun the two-tier strategy with a cheaper connection arrangement (alongside higher call charges) for consumer users - Cellnet's Lifetime, and Vodafone's LowCall. Now the two-tier pricing has been introduced and is understood by users, PCNs and GSM networks should widen the differential even more. Business users can have their world-wide telephone conferences at one price and consumers in the mass market at another, a lower price. And all of this can be achieved without recourse to an existing landline telephone.

Keith Brindley



SONY ANNOUNCES TWO NEW DAT BASED INSTRUMENTATION RECORDERS

Sony has launched two new instrumentation Data Recorders, the 4 channel PC-204A and 8 channel PC-208A. These models offer better features over their predecessors the PC-204 and PC-208, but are available at the same price.

The PC-204A and PC-208A offer Double Bandwidth recording and playback at 80kHz, which can be split into four 20kHz or eight 10kHz channels. A wide 'dynamic range of over 80dB al-

lows the capture of signals in noise-critical environments such as acoustic noise measurement.

The employment of DAT technology makes the equipment suitable for high density storage as it offers more than ten times the capacity of standard audio cassettes.

In addition to the four or eight available channels there is a digital I/O channel which uses the LSB (Least Significant Bit) of each data word. This allows for

the recording of binary signals such as rotational and stimulus pulses as well as timing or reference signals.

The PC204A and PC208A can also be used as serial digital recorders with input and output capabilities of up to 3.072 Mbits/sec. A high speed parallel digital output enables 16-bit transfer of data to computer platforms.

Another feature of the Sony

Data recorders is the use of PCM (pulse code modulation), a measurement technique which guarantees the accuracy of logged data. By converting the analog signal levels into numeric values and recording them digitally, it avoids the risk of corruption by magnetic tape or tape transport mechanisms.

COMMUNICATION GAP IS HOLDING BACK INDUSTRY

Research released at the Computers in Manufacturing Show (CIM '93) reveals a communication gap between Information Technology suppliers and manufacturers that is holding back UK industry, according to John Puttick, Director of Manufacturing Europe for PA Consulting.

The research undertaken on behalf of CIM '93 by Benchmark Research shows that manufacturers remain unconvinced, and distrustful, of the benefits of IT and revert to manual methods during critical production runs. 33% of managers from large and medium sized manufacturing plants revert to manual methods when scheduling rush jobs, 43% still believe manual methods are more suited to control shopfloor processes and 21% are convinced that manual methods are better for scheduling production.


However, users universally accepted that computers were able to manage accounts, sales orders, purchase orders and stock control better than traditional manual methods. Another 51% admitted they did not actively measure the success of computer investments unless a problem emerged.

John Puttick from PA Con-

sulting Group commented: "Manufacturers are so caught up in the chaotic world of the factory floor that they're unable to define their problems adequately, let alone explain them to anybody else. While, IT suppliers do not understand the complexities of manufacturing and are unaware of the limitations of the technology. The result is that IT suppliers can 'over-sell' the capabilities of the technology and some manufacturers can become disappointed and disillusioned with IT and its suppliers.

"This gap is holding back technological development within UK manufacturing. Our manufacturing industry is based on the production of capital goods, such as aerospace components, luxury cars and gas turbines. These goods require constant modifications, testing and manufacturing. What is needed is a system that can 'think' in a flexible way, while coping with complex tasks. The UK has the opportunity to do for capital goods what the Japanese have done for high-volume products, but the adoption of IT is critical.

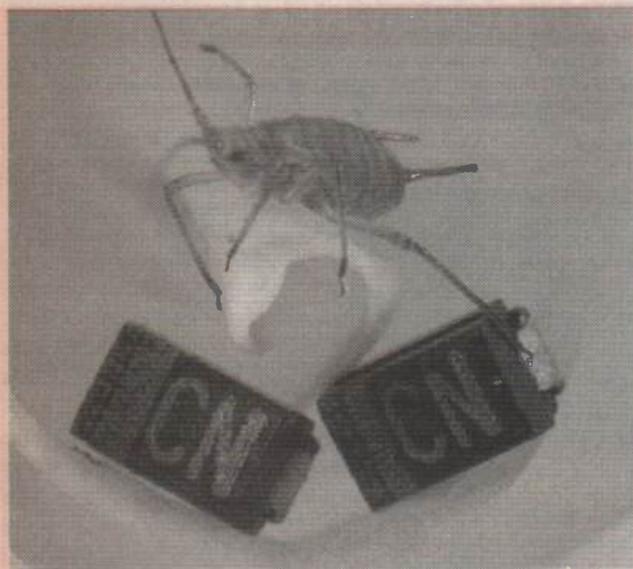Alec Cassells, Systems Consultant for IBM Industrial Con-



SMALLEST CHIP CAPACITORS

NEC Electronics' new range of ultra-miniature tantalum chip capacitors are claimed to be the smallest available for their capacitance value range.

The SVS series, which ranges from 0.33uF to 2.2uF with voltage ratings of 2.5 volts to 16 volt DC, have outline dimensions of only 2.00mm x 1.20mm x 1.25mm - half the size of the EIA standard A case.

These new products complement NEC's existing R-series tan-

talum chip capacitors which range in value from 0.047uF to 330uF with voltage ratings of up to 50 volts DC.

All of the SVS series of products operate over the -55°C to +125°C temperature range with a tolerance of 20%. Leakage current is 0.5uA maximum with a dissipation factor of 0.1 max. The capacitors are available in tape reel format and pricing is £0.12 in 1,000 piece quantities.

sultancy agreed that there were problems to be solved, but sees this as an opportunity for customers and supplier alike.

"The fact that most of the users only measure the success of

their computer systems when a problem emerges demonstrates that they don't have an accurate idea about the successes they are achieving," Cassells said.

The Computers in Manufac-

turing Show 1993 (CIM '93) is now commissioning a greater study into the attitudes held by manufacturers, IT suppliers, management consultants and the me-

dia, to look at ways of overcoming this communication problem.

CIM '93 will be held at the National Exhibition Centre in Birmingham from October 19-21.

NICAD UNIVERSAL CHARGER

MAPLIN Electronics can now supply a NICAD UNIVERSAL CHARGER priced at £9.95 (incl VAT). The Nickel-Cadmium battery charger is capable of charging AAA, AA, C, D, PP3 and rechargeable button cells singly or simultaneously in varying combinations. There are two charge sockets for PP3 batteries and either one or two may be charged together. There are two positions where AA, C or D cells may be charged. In addition there are two positions for rechargeable button cells, diameters 16mm, 11.6mm or 8mm. (Note: It is very dangerous to attempt to recharge

mercuric oxide, zinc-air or silver oxide cells). All ten charge positions may be used simultaneously or in any combination. Each of the eight main charge positions (ie. not the button cells) has an LED associated with it which lights when charging is in progress. In addition, three test positions are provided, one for AAA and AA, one for C and D cells and one for PP3 batteries. When the charging switch is off, depressing the test button for the test position in use allows the meter to show if the battery is flat. The unit has 1.7m mains lead. Overall size: 185 x 155 x 56mm.



SPECIALLY COATED MONITOR SCREENS

Philips Components latest screen coating for monitor screens has given the company the leading edge in information display applications.

The anti reflection/anti static screen coating (ARAS) which cuts light reflections on monitors to just 0.5% - a mass twentyfold drop compared with uncoated screens.

The anti-reflection/anti-static screen coating (ARAS) cuts light reflections on monitors to just 0.5% - a twentyfold drop compared with uncoated screens.

The special coating is made of a multi-layer structure of transparent dielectric material that



suppresses specular reflections by broad band interference effects at

the screen surface. The anti-static properties are provided by a sin-

gle conductive layer within the multi-layer structure.

Philips Components has recently won a major contract to supply Amsterdam's Schiphol airport with these specially coated monitor screens which cut light reflections by 90%.

Schiphol has just ordered 400 coated screens and plans to equip each of its 2000 flight information displays with the coated monitors by the end of 1994.

ARAS coating is available as an option on 66cm (28 inch) Flat-ter, Squarer Monitor Tubes type M66EEU418X and 16:9 ratio displays.

MD DATA STANDARDS FOR COMPUTER DATA STORAGE

Sony has announced the development of standards for MD DATA, the new compact data storage medium offering high data storage capacity for personal computer applications.

The MD DATA standard has been developed to meet the computer industry's growing need for storage media capable of handling large amounts of data. The standard is based on specifications recently established for MiniDisc personal audio system, which Sony introduced in No-

vember 1992. Sony will offer the new MD DATA standard to computer and other manufacturers to generate industry support.

Typically, floppydisks have been the medium of choice to fit the everyday data storage needs of personal computers because of the disks compact size and cost effectiveness. However, the need to add graphic as well as audio information to documents created on a PC led to the demand for a removable data storage medium capable of handling larger

amounts of data. While magneto optical (MO) discs are currently being used to meet these needs for workstations, Sony believes that factors, such as system size cost and ease-of-use will make MD DATA products widely accepted by consumers seeking portable computing applications.

MD DATA is expected to evolve into the next generation in data storage technology. Offering the cost-effectiveness and user-friendliness of floppydisks, MD DATA will also provide sev-

eral special features including, a small portable size, 140MB memory capacity, 2,000 frames of still color images on one MD DATA disc;

It also allows a data transfer rate of 150kB per second, enabling

CD full motion video;

Importantly, a new file system, which determines how information is encoded on the disc, has been developed as part of the MD DATA standard to facilitate compatibility between computers

based on different operating systems (OS).

Computers using different CPUs and/or OSs employ file systems unique to their standard. These file systems determine file structure and the manner in which data is written onto the disk. As a result, it is difficult to interchange floppy disks between com-


puters of different platforms.

The MD DATA's file system will circumvent this problem. Once MD DATA system software is installed onto the computer, information written onto MD DATA discs can be retrieved and modified regardless of differences in the CPU and/or OS of the computers being used.

Specifications:

*Recording Capacity:	140 MB (maximum)
*Sector Size:	2,048 bytes
*Data Units	64 kB
*Data Transfer Rate	150 kB/sec
*Cartridge Dimensions	68 mm x 72 mm x 5 mm
*Disc Diameter	64 mm
*Disc Thickness	1.2 mm
*Track Pitch	1.6
*Laser Wavelength	780 nm
*Numerical Aperture	0.45
*Recording Method	Magnetic Modulation Overwrite System
*Linear Velocity	1.2 m/sec-1.4 m/sec
*Modulation System	EFM
*Error Correction System	Adaptive Cross Interleave Reed Solomon Code (ACIRC)

VERY LOW POWER SRAMS

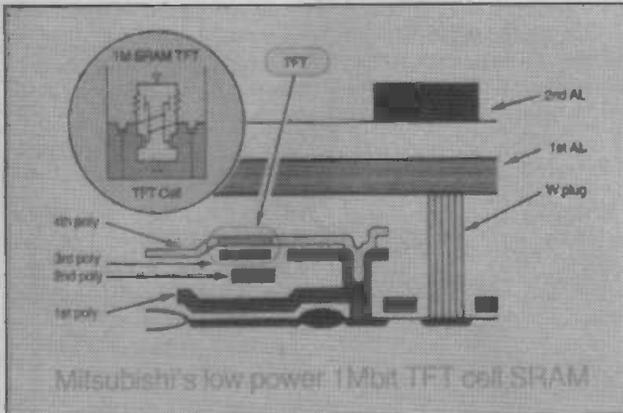

Mitsubishi's low power 1Mbit TFT cell SRAM

Mitsubishi has announced the expansion of its second generation 1Mbit, low power SRAM product family. A new TFT (thin film transistor) cell version of the

1Mbit SRAM has been produced using 4Mbit technology to achieve superior power saving performance. Indeed, the new TFT device is the lowest power 1Mbit SRAM

currently available.

The 1Mbit TFT cell SRAMs, like the other 1Mbit SRAM products, operate at 3V (2.7 to 5V range) giving increased battery life. The SRAMs are useful in portable applications ranging from computers and dataloggers to mobile communications equipment. The low power devices are also ideal for memory card type applications where battery backup is used to give portable, non-volatile mass data storage.

The new TFT devices can be used in a 2Mbyte memory card, providing a ten year life from a single 3V standard lithium cell.

The 1Mbit TFT series SRAMs typically consume 0.05µA on standby from a 3V supply com-

pared to 0.3µA from current HR cell devices. The new TFT cell device is downward compatible with previous HR cell 1Mbit SRAMs and is organised as 128k x 8bit.

MORE NEWS NEXT MONTH

Hesing Technology

Cromwell Chambers, 8 St. Johns Street,
Huntingdon, Cambs. PE18 6DD

Tel: (0480) 433156
Fax: (0480) 413357

TEST EQUIPMENT SYSTEM CONSULTANCY


Supply
Maintenance
Commissioning

Replacement Parts
Supply of Service &
Operators Manuals
Components

Distributors for:
WAUGH INSTRUMENTS, RAMTEST LTD, KRENZ ELECTRONICS, PANTHER

AFFORDABLE DATA ACQUISITION

For PC's + Compatibles

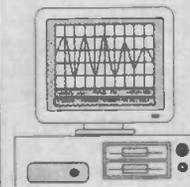

AD8 **£29.95**

AD8-6 **£54.95**

- 1 channel 8-bit A to D
- Plugs into printer port
- Up to 25 KHz sampling
- 0 to 5 Volt input range
- Software drivers in C and BASIC
- Voltmeter and Scope software + source
- 6 channel 8-bit A to D
- Plugs into printer port
- Up to 4 KHz sampling/ch
- 0 to 5 Volt input range
- Software drivers in C and BASIC
- Data Logger software (requires egavga)

Prices include P+P
Software supplied on 3.5"
Disk unless 5.25" specified.

C.P. Technology

Red Lion Yard, Market Place, Blandford, Dorset DT11 7EB.

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

- The supplier to use if you're looking for —
- ★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST ★
 - ★ COMPETITIVE VAT INCLUSIVE PRICES ★
 - ★ MAIL ORDER - generally by RETURN OF POST ★
 - ★ FRIENDLY SERVICE ★



Open: Monday-Thursday 9.15-6.00
Friday 9.15-5.00 Saturday 9.30-5.00



EQ LTD STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

- Do you have a requirement for any of the following services:
- PCB Assembly (Conventional and Surface Mount)
 - Wave & Hand Soldering
 - Complete Equipment Manufacture
 - Device Programming from hand written sheets or PC 3 1/2" disc
 - Cable Harness Assembly /loom Manufacture
 - Card Cage and Module Wiring
 - Full Inspection
 - Product Design/Consultation
 - Full Procurement Service
 - PCB Test & "Burn in" Facilities
 - Enclosure Design & Manufacture
 - PCB Artwork Manufacture
 - Circuits Drawn Professionally
 - Kit Procurement & Supply
 - Component Sales
 - Refurbishment a speciality
 - Top Quality Work at Reasonable Rates

Phone Tracey on (0438) 310066 or Fax details of your requirements to us on (0438) 315829
EQ LTD, BTC, Bessemer Drive, STEVENAGE, HERTS, SG1 2DX

...Stateside...

Volume holographic storage

Although still in the research stage, volume holographic storage for computer software has recently required its own data compression technique, called fractal space multiplexing.

The technique was tried recently at Northrop Corp.'s Electronic Systems Division, where a demonstration project stored a

Protecting gas furnaces from power cuts

During a sustained power cut, even people with gas furnaces may be without heat because electricity is needed to operate the blower. Petrol and kerosene-powered generators may be used for backup power, but they must be watched and maintained and mean that potentially dangerous fuel must be kept around the house.

Rochester Gas and Electric, of Rochester, New York, has sought help from the GE Research and Development Centre in Schenectady to solve this problem. The GE centre has now demonstrated the viability of a continuous gas furnace, which converts gas heat into electricity to power the blower and accessories. The key is a small thermoelectric generator that could be incorporated in new furnace designs. The generator exploits the Seebeck effect, where a circuit made of different materials (a thermocouple) will generate electromotive force (voltage) when its two junctions are kept at different

temperatures.

The prototype furnace, a small, 70lb unit burning diesel fuel, produced 7.2kW or 25,000 BTU/hr of heat, about one-quarter the output of a typical home heating system. In tests, the unit also produced 160W of electricity, approximately 60W of which were needed to run the heating system. This left 100W of auxiliary power. A full-sized gas system could produce around 600W of energy without reducing heat efficiency. However, economics dictate a production system with fewer thermocouples, which would produce 100W to 300W of electricity.

record 5,000 holograms in a lithium niobate crystal. Without the fractal geometry, the crystal could only support 500 holograms with reasonable resolution.

Holographic techniques already perform a kind of data compression. A two-dimensional array of pixels can be represented as a one-dimensional array of ref-

erence beams. The two-dimensional image is reconstructed from a wave interference pattern, generating the reference beams.

That fractal geometry multiplexing would save space seems to be paradoxical at first, since it requires several one-dimensional reference-beam arrays that would therefore take up more

information storage space in the crystal. A large gain in storage occurs on read out, however, since the added information greatly reduces the optical crosstalk between stored images. The reduction in noise results in the ability to store 10 times as much information in the same space.

New microprocessor speeds pose problem

Now microprocessor speeds are moving above 100MHz, problems normally associated with radio-frequency design are beginning to intrude into digital systems. Several projects aimed at solving system communication bottlenecks with optical methods have converged on a little-known area of organic chemistry - long-chain polymers, to which optically active molecules known as chromophores are attached.

Researchers believe the polymer materials may not only be the key to uncorking future bottlenecks but could also lower the

cost per bit of information transmitted by orders of magnitude.

At cycling rates above 100MHz, electromagnetic interference, terminal echo and ground bounce start to disrupt the simple capacitance model of interconnecting wires. While those unwanted effects complicate current designs, they threaten to become an insurmountable obstacle at the inter-chip level.

Polymer-based materials are attractive because they solve a crucial materials-compatibility problem that has plagued other electro-optic approaches.

Compound semiconductors such as gallium arsenide or indium phosphide are star performers, but crystalline mismatch with silicon has effectively blocked attempts at integration. The same is true of ceramic E-O materials. Lithium Niobate, for example, is preferred for its strong electro-optic performance but, as a crystal, is similarly difficult to integrate with other crystalline materials.

GE research has turned up a new candidate - dimethyl amino stylybazolium tosylate (DAST) - which the project is targeting for

use as a thin-film interconnect technology for multi-chip modules. DAST has an unusually strong electro-optic coefficient, which makes it ideal for shrinking the size of devices.

In general, organic polymers tend to have weaker E-O coefficients than crystalline materials, and they also suffer from stability problems.

The new material discovered at GE has an unusually high E-O coefficient, but keeping that value stable over wide temperature ranges and long operational periods is proving difficult.

High temperature superconductor

Superconductor Technologies Inc., of Santa Barbara, California, has constructed what it believes is the first high-temperature superconductor delay line longer than 100 nanoseconds.

Made of a thallium-based HTS, the line is drawn in a module that measures only 3.8 x 3.8 x 0.5in. It would replace 70ft of RG-141 stainless steel coaxial cable in instrumentation and electronic warfare-delay applications.

Compared with the coax line, the HTS delay line improves insertion loss by a factor of 5, which

enables a system designer to reduce the number of amplifiers needed to recover a signal, improving signal integrity.

The choice of 100 nanoseconds was more or less arbitrary, though within a certain window. The company thinks there is a competitive advantage with superconductors with delays between 25 and 500, before optical systems become more optimal.

The delay line could be useful for storing signals in channelised receivers while a superheterodyne is being tuned.

Simulated Annealing

Exatech Software of Colorado Springs, has announced an add-on that applies simulated annealing, a neural-like learning method, to spreadsheets.

It can quickly locate minima or maxima in problems involving too many simultaneous equations or unaccelerated PCs.

Called XSolver, the programme has been designed for use with Microsoft's Excel spreadsheet. It communicates directly with Excel via Windows' dynamic data exchange method.

Simulated annealing simulates the way that the temperature is repeatedly raised and lowered on an annealing furnace. For micro-

chips, annealing helps form a perfect crystal lattice.

XSolver's user interface presents the user with the control panel on an annealing furnace while the spreadsheet data undergoes the annealing. The model, must first be expressed as a spreadsheet, with the user declaring the spreadsheet cells that contain adjustable parameters and the value in the single cell, which is a function of those parameters, to be minimised.

The user can choose whether thermal changes alter the values of individual cells or a swap in values between random pairs of cells.

OUT NOW!!

**HENRY'S
NEW
1994
COLOUR
CATALOGUE**

**TRADE • EDUCATION
RETAIL • MAIL ORDER
EXPORT**



Open 6
days a
week -
CALLERS
WELCOME

HENRY'S
404 Edgware Road,
London W2 1ED

Components
Telephone: 071-723 1008

Security - Communications
Telephone: 071-724 0323

Audio and Test Instruments
Telephone: 071-724 3564

Trade/Quantity
Telephone: 071-258 1831
Fax: 071 724 0322

RETAIL - MAIL ORDER VERSION

With price lists, special offers and purchase vouchers. Send PO/Cheque £4.00 (UK) £6.00 (EC) £10.00 (Non EC) Callers £2.00.

Education, trade, quantity purchasers Post or fax letterhead for **FREE** copy with trade/quantity price list (UK). Overseas prices as above.

**PLASTIC
BOXES**




A RANGE OF SMALL PLASTIC BOXES, CASES AND POTTING BOXES AVAILABLE IN ANY QUANTITY.

SEND FOR FREE CATALOGUE

SLM (MODEL) ENGINEERS
CHILTERN ROAD, PRESTBURY,
CHELTENHAM, GLOS GL52 5JQ
FAX: 0242 226288

**READY
NOW**

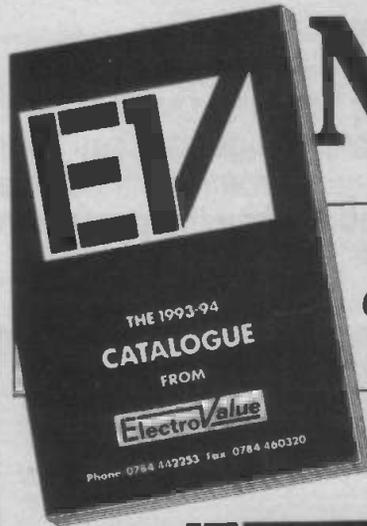

**Every keen
constructor
needs it**

THE 1993-94

**ElectroValue
CATALOGUE**

Profusely illustrated, this 140+ page A4 size catalogue packs a wealth of information on items from the highly sophisticated to modest but essential screws, washers and wire, etc. With 28 years in personal mail order service we know how much you rely on quality of goods above everything plus back-up service from the supplier i.e. Electrovalue. We've got the catalogue you want and we deliver the goods!

TO GET YOUR CATALOGUE

Send your cheque or postal order for £1.50 to address on coupon or phone your Credit Card No. & its expiry date. Catalogue comes with two £1. vouchers, each for spending with orders value £10. or more.

***SHOPS AT:**

Egham, Surrey
28 St. Jude's Road, Englefield Green.
Tel. 0784 434757

Burnage, Manchester
680 Burnage Lane
061 432 4945

*PERSONAL SHOPPERS, NOT MAIL ORDER

DISTRIBUTOR
FOR
SIEMENS
PROFESSIONAL
ELECTRONIC
PRODUCTS
SEMICONDUCTORS
OPTO-ELECTRONICS
FERRITES
CONNECTORS
SWITCHES
CAPACITORS
INDUCTORS
etc

**ELECTROVALUE LTD., UNIT 3. CENTRAL
TRADING ESTATE, STAINES TW18 4UX**

Phone 0784 442253 Fax 0784 460320

Your 1993/94 Catalogue please, to:

Name

Address

Block letters please, and POST CODE

I enclose cheque/postal order for £ TE.2

If not using coupon please quote this journal when writing.

We'll pay for every issue of **ETI** to be posted to you*

A one year subscription guarantees every issue of 'Electronics Today International' is delivered to you on publication and we pay the postage anywhere in the U.K.!



Go for our *Direct Delivery Service* - you can't lose!

Electronics Today International
 1 Year Subscription Rates:
 U.K: £23.40
 Europe & Eire: £29.50
 Sterling O/Seas: £31
 US Dollars: \$56
 *U.K. only



Post me today! PLEASE COMPLETE IN BLOCK CAPITALS

Yes, I would like to subscribe to **ETI Magazine** for 1 year. (Quote subscription number if renewing/extending.....) Commence my subscription from the issue.

I enclose my cheque /M.O. for £ made payable to ASP or debit my Access/Visa account:

.....

SIGNATURE..... EXPIRY.....

TODAYS DATE:..... NAME.....

ADDRESS.....

..... POST CODE.....

Please send this coupon to: The Subscription Dept., Argus Subscription Services, Queensway House, 2 Queensway, Redhill, Surrey, RH1 1QS
 Or Call our Hotline: 0737 768611

You may receive further information about offers and services which may be of interest to you. Offer close :8/8/93. (ETI120)

4 great christmas ideas

FROM ARGUS BOOKS



- Aviation Enthusiast's Handbook ISBN 185486 0542 £9.95
 - ETI Book of Electronics ISBN 185469 282 £10.95
 - Scanners 2 International ISBN 085242 924x £10.95
 - Scanners 3rd Edition ISBN 185486 0062 £8.95
- p&p + 10% minimum £1. Telephone orders 0679 66905
- I enclose my remittance of..... Please make cheque payable to Bailey Distribution and send to the address below. Please charge my Mastercard/Visa
-



Expiry Date:..... Signature:.....

Name.....

Address.....

..... Post code.....

Complete details and return to Bailey Distribution Ltd, Units 1a/1b Learoyd Road, Mountfield Road Estate, New Romney, Kent. TN28 8XU.


Please ensure that all cheques are made payable to Bailey Distribution.

NEW VERSION 2
NOW SHIPPING

SCHEMATIC DRAWING FOR WINDOWS

NEW
LOW PRICES

ISIS ILLUSTRATOR combines the high functionality of our DOS based ISIS products with the graphics capabilities of Windows 3. The result is the ability to create presentation quality schematics like you see in the magazines. ILLUSTRATOR gives you full control of line widths, fill styles, fonts, colours and much more. When the drawing is complete, transferring it your WP or DTP program is simply a matter of cutting and pasting through the Windows Clipboard.

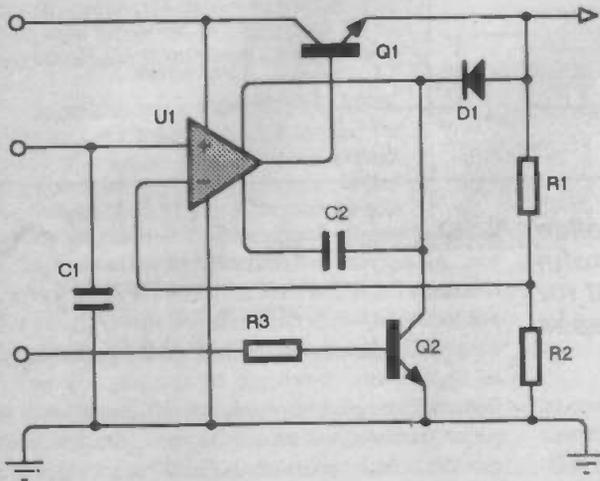

Features

- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Curved or angular wire corners.
- Automatic wire routing and dot placement.
- Fully automatic annotator
- Comes complete with component libraries.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Output to Windows printer devices including POSTSCRIPT and colour printers.
- ILLUSTRATOR+ adds netlist generation, bill of materials etc. and is compatible with most popular CAD software for DOS & Windows.

From
£99

CADPAK - Two Programs for the Price of One.

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

Only
£79

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.

PCB II

High performance manual PCB layout package for DOS. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Graphical User Interface with intuitive "point and do" operation gives unparalleled ease of use.

ISIS and ARES for DOS - The Professional's Choice

ISIS

from £275

ISIS DESIGNER+ forms the ideal front end of your CAD system, providing schematic capture, netlisting, bill of materials and electrical rules checks. Advanced features include automatic annotation, hierarchical design and an ASCII data import facility. Put simply, DESIGNER+ is one of the easiest to learn and most powerful schematics packages available for the PC.


ARES

from £275

The ARES range of advanced PCB design products links with ISIS (DOS or Windows) and other schematics programs. Working from a netlist, ARES helps you get it right first time with each connection automatically verified against the schematic.

ARES AUTOROUTE adds multi-strategy autorouting, whilst for the ultimate in performance, ARES 386 goes up to 400% faster with unlimited design capacity.

labcenter
E l e c t r o n i c s

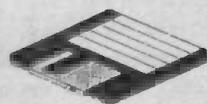

Call us today on 0274 542868 or
fax 0274 481078 for a demo pack.
Combination, multi-copy and
educational discounts available.

14 Mariner's Drive, Bradford, BD9 4JT.

Hot Wire Cutter

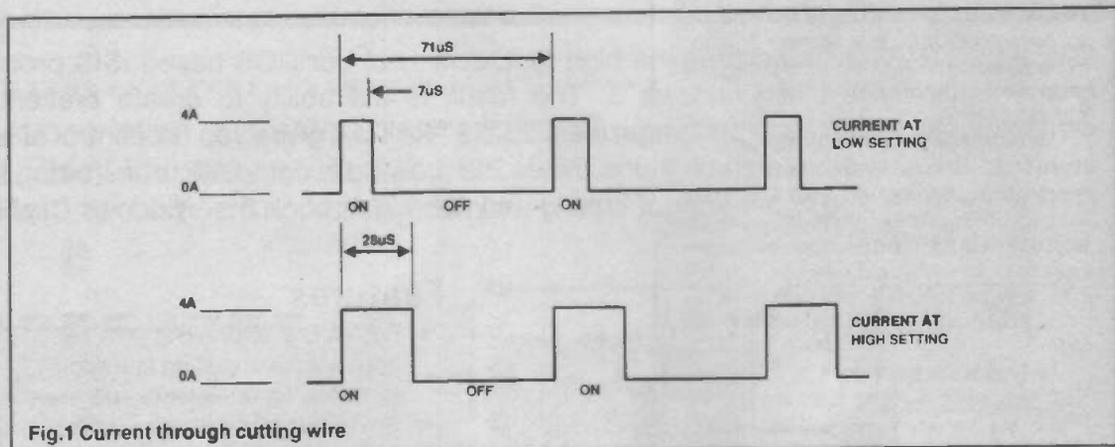


Fig.1 Current through cutting wire

Colin Meikle describes a useful instrument for cutting shapes

This piece of equipment will easily find a home on the work bench. Anyone who builds electronic projects has undoubtedly spent many hours drilling, sawing and filing boxes to accommodate meters, connectors, displays, etc.. This piece of equipment is a controllable hot wire, which can be used to cut detailed shapes out of plastic enclosures (or can be used anywhere plastic or even polystyrene requires cutting). The equipment consists of three separate parts, a Power Supply, the control electronics and a 'U' shaped handle which has the cutting wire. The circuit incorporates a temperature control, which is essential to be able to cleanly cut different thicknesses and cut at different speeds. A Tricoloured LED gives an indication of the cutting wires temperature (green = cool, orange = warm and red = hot). Touch strips are incorporated in the handle of the cutting arm, so that the hot cutting wire is only turned on when the handle is being held (this helps avoid the inevitable burnt fingers). The circuit as described has been designed to operate from a 12V PSU, such as the power supply for a PCB drill (see the section on Power Supply).

There are a number of ways of controlling the power to the hot wire and hence the temperature of the wire. The method employed in this circuit is Pulse Width Modulation, which is a very efficient method. The power to the hot wire is pulsed on and off and by varying the on/off period, the temperature of the wire can be controlled. Figure 1 shows the output waveform to the hot wire. The current through the wire when it is on is approximately 4A and, from Figure 1, it can be seen that the duty cycle is between 10% and 40%. A bulk capacitor supplies the peak current and hence the current which is drawn from the supply is between 0.35A and 1.5A. Since the wire is either on or off, the losses in the circuit are very small. A MOSFET was chosen for the output transistor due to its very small on resistance (0.18R), hence it can operate without a heatsink. The circuit's operating frequency is not

critical, although a few factors must be taken into consideration. As the wire is continually pulsed on and off, it is constantly heated and cooled. This causes the wire to expand and contract which in turn causes the wire to vibrate a small amount. This vibration at low frequencies manifests itself as an audible hum, which can be annoying. At very high frequencies the circuit becomes less efficient, as losses in the output transistor will start to increase. Another factor to consider at high frequencies is Electromagnetic Emissions. At high frequencies, with large switching currents the emissions from the circuit could easily interfere with other electronic equipment. With the components specified the operating frequency is between 13-15kHz.

Component Selection

The most important component is the cutting wire itself. The wire used was salvaged from the heating element of an old hair dryer, one element will give years of supply. (I have used the wire from two different elements, both had a resistance of approximately 3 ohms per 10cm). It is not critical that the wire has the same resistance, as the duty cycle of the circuit can be altered to compensate for different wires, but wire with a significantly lower resistance should not be used.

The MOSFET specified can be substituted for any Power MOSFET which has a low On resistance (less than 0.25R). Any device which has a higher On resistance may require a heatsink - if alternative devices are used, check the pin out.

Resistor 9 is not strictly required, but it does allow the current through the circuit to be easily monitored, thereby allowing you to check that your PSU is not over-loaded (current = $4 \times$ Voltage across R9). The wire used between the control unit and the handle should be the 'Extra Flex' type, to allow free movement of the handle. Ensure the connectors used to connect the wires the handle are capable of handling over 4A.

Power Supply

The circuit has been designed to work from any 12V power supply that can supply 2A or more. Standard batteries are not a suitable source for the supply, due the high current

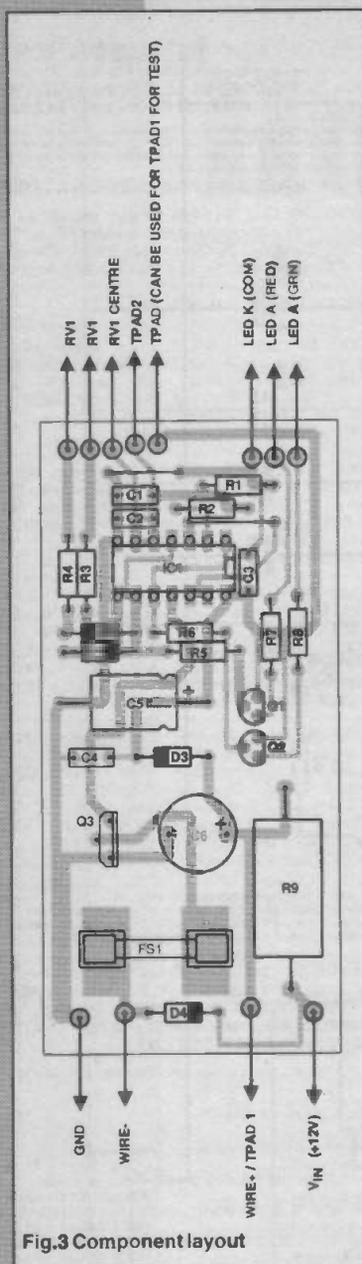


Fig.3 Component layout

This gives a simple, quick method of connecting and disconnecting the wire. A small spring is used to keep the cutting wire taut, but still allows some flexibility.

The touch strips on the handle can be any type of metal rod or strip. The two strips should be positioned apart, so that when the handle is held your hand covers both. The connecting wires should be connected as shown in Figure 3/4. Note that the WIRE+ wire connects to one touch strip and one end of the cutting wire.

Setting Up

The circuit should first be tested without the cutting wire. Connect the power supply to the circuit and connect a 12V bulb or an LED via a 1k resistor to the output terminals. With the touch pad connections open, turn the power on. The tricoloured LED should light and when the pot is altered, the colour should change from mainly green to mainly red. If it does not, check that D1 and D2 are the correct way round. Turn the pot until the LED goes green, then connect the touch pad wire to the positive supply (the test point can be used for this). The test LED or bulb should glow dimly, as the pot is altered the intensity should increase. If the bulb glows most brightly when the LED is green, swap the green/red connections to the tricoloured LED.

Assuming all is OK turn off, leaving the pot set with the LED at green and replace the test bulb with a piece of the Cutting Wire (the same length

as to be used in the handle). Take care that the ends cannot be shorted out and that the wire is away from anything it may burn. When the power is applied to the circuit, the wire should warm up (this may not be visible at the cool setting) and as the pot is slowly altered, the wire should get hotter. When the other end stop of the pot is reached (the LED will be mainly red) the wire should be visibly glowing.

If the wire gets visibly hot before the end of the pot or does not get hot enough, a few adjustments will be required.

If the wire gets too hot at the maximum setting, increase the value of R4. If the wire does not get hot enough decrease R4. If the wire is too hot at the minimum setting, decrease R3 and if it's too cool increase R3. If the values of R3 and/or R4 are altered the tricoloured LED may appear too red or too green. The colour can be easily altered by changing R7 for the red content and R8 for the green (increasing the value decreases the intensity of the corresponding colour).

In Use

When using the cutting wire, you will find the wire will cool locally around the cutting point. To obtain the best results, the wire should be moved gently up and down as you cut, so that the local cooling has less of an effect. You may also find it helpful to build different sized handles, which can be swapped as required, to suit different situations.

PARTS LIST

RESISTORS

All 0.25W, 5% Carbon Film, except where stated

R1	5M6
R2	100k
R3	12k
R4	56k
R5,6	10k
R7	330R
R8	1k2
R9	0R25 (3W W/Wound)
RV1	47k Potentiometer

CAPACITORS


C1	10n
C2	1n
C3	100n
C4	100n polyester (5mm pitch)
C5	100µ16V Elect
C6	1000µ16V Elect

SEMICONDUCTORS

D1,2	1N4148
D3,4	1N4001
Q1,2	BC327
Q3	BUZ11 Power MOSFET
IC1	4093 CMOS Schmitt NAND Gate

MISCELLANEOUS

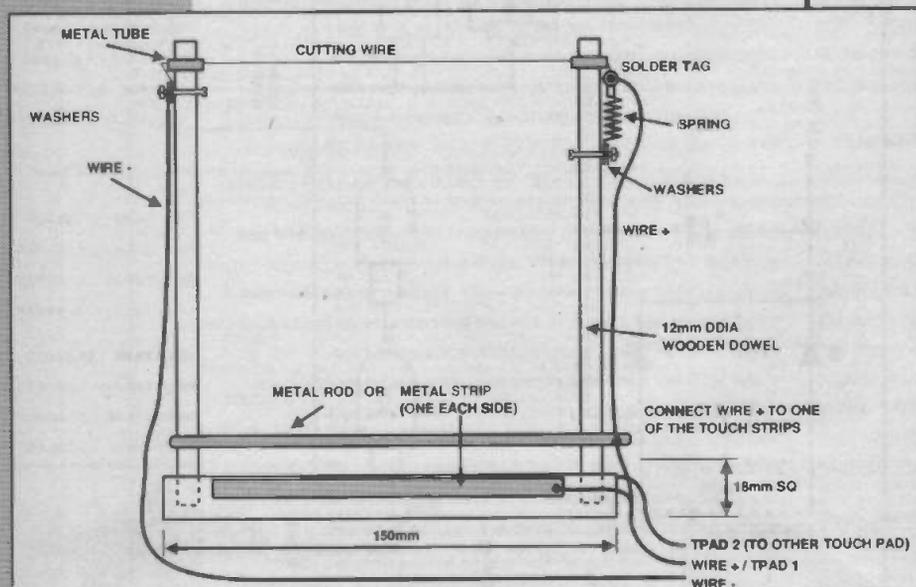4A Slow Blow Fuse and PCB clips.
Tricoloured 5mm LED and clip.
Suitable 'cutting wire', approx. 3 ohms per 10cm, e.g. wire from the heating element from a hair dryer.
Extra-Flex wire to connect the handle to the control box.
Plugs and sockets, e.g. 'Wander' type
Suitable plastic box to house the circuit (e.g. 125 x 60 x 40)



NOTE: EITHER METAL ROD OR STRIPS CAN BE USED FOR THE TOUCH PADS

Fig.4 Cutting arm

POWER AMPLIFIER MODULES-TURNTABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

PRICES INCLUDE V.A.T. • PROMPT DELIVERIES • FRIENDLY SERVICE • LARGE (A4) S.A.E. 60p STAMPED FOR CATALOGUE

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W) ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3 1/2" (2U)x D11"
MXF400 W19"xH5 1/2" (3U)x D12"
MXF600 W19"xH5 1/2" (3U)x D13"
MXF900 W19"xH5 1/2" (3U)x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls, bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalizers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs: 3 turntables (mag), 3 mics, 6 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN1038A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2"x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2"x6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

ibi FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
ibi FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £8.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS
Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.M.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 100D Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.M.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

MINIANCE- INSTRUMENTS, P.A. DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE
6" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB. PRICE £32.71 + £2.00 P&P
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB. PRICE £35.74 + £2.50 P&P
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB/D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 95dB. PRICE £43.47 + £2.50 P&P
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. RES. FREQ. 49Hz, FREQ. RESP. TO 8KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB. PRICE £46.71 + £3.50 P&P
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB. PRICE £70.19 + £3.50 P&P
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £50.72 + £4.00 P&P
16" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB. PRICE £73.34 + £4.00 P&P

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.05 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS
3W TRANSMITTER 88-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 120mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P
FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 58 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P

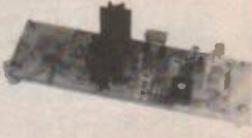


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.
Tel.: 0702-527572 Fax.: 0702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.


READ/WRITE **ETI** Letters

Supplies Supplies

I would like to congratulate you on one of the most interesting issues of ETI that I have read in a long time. It was nice to see the article on transformerless power supplies but hopefully your contributors will be able to design these safely in the future, and I won't have to write to complain. Contrary to what you seemed to infer from my letter, I have nothing against the transformerless power supply - I design circuits using them on a regular basis, but as I design them commercially, electrical safety is paramount and compliance to the relevant standards is mandatory.

Andrew Armstrong makes no mention of how to calculate R1 in

Figure 4 (the surge limiting resistor). In practice, the larger the better. Not only does R1 limit the surge, it is the only limit to high frequency interference, where the capacitor reactance is negligible. I choose a 2W component for R1 and select its value such that $I_{ac}^2 R1 = 1W$ approx.. Class X capacitors are available up to 1μ ,

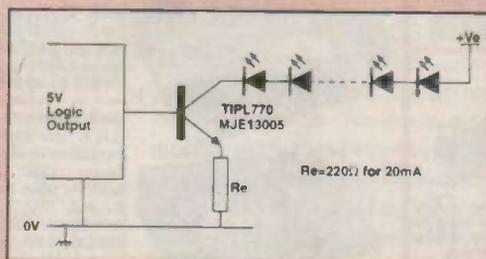

which gives a respectable current. If a 400V polyester is substituted it will blow up sooner rather than later, a 630V component will last a bit longer. D1 can be the Zener and D3 can be omitted to reduce component count giving

an output voltage 0.6V less than the Zener voltage. The waveform at the junction of D1 and D2 is a very useful 50Hz square wave, but unfortunately it is in quadrature with the mains, not in phase.

I was very interested in Mr Binga's clock and I have used the circuit below instead of Figure 3 very successfully. For 5V logic, the current is $4.4V/R_e$ and is independent of supply voltage fluctuations and number of LEDs in the chain. I have used +VE as rectified mains with next to no smoothing, but the transistor needs a heatsink. The TIP1770 or MJE13005

has a gain of at least 30, so the logic has to supply less than $660\mu A$ for 20mA in the LEDs.

If the clock has a 7-segment display, would fluorescent tubes be a possibility? Starting them would be interesting, I'll leave

that design for someone else to do! Arranging to turn the heaters on a few seconds before voltage is applied to light the tube would be a possibility or, alternatively, running them cold-cathode from a leakage-reactance transformer.

On a final note regarding making PCBs, photocopying onto overhead projector film does not usually give enough density, but making two copies and fixing them together, one on top of the other usually produces excellent results, provided that the copier produces two copies of identical size.

Ian Benton
Ilkeston
Derby

Andrew Armstrong replies:
For a low power design, R1 would be in the region of 0.6-1W. The minimum value of R1 with $V_{pk} = 360V$ and $I = 2.5A$ would be 144R (nearest preferred value of 150R). If 50mA is drawn, you would need a 10W version of R1 (150R).

Power Down Problem

I am currently attempting to design a circuit incorporating CMOS Static RAM and I would be very grateful if you could offer some advice.

The circuit is designed to download and store data from a computer's serial port using two CMOS Static RAMs, (6264 8K x 8bit and 62256 32K x 8bit). Both devices share a common address bus in my circuit design, but are individually selected to store data by switching logic. It is vital that data is retained after switching off the main 5V supply to the circuit.

It is simple enough to connect a battery backup to the RAMs using diodes to maintain power to the chips when the main 5V supply is switched off. One possible problem, however, is the fact that the logic circuitry controlling the RAM chips may set the READ, WRITE and CHIP SELECT lines to an undesirable state as they

power-down. The effects of this would be possible corruption of data in one or more RAM chips.

It seems that a voltage monitoring circuit is required to disable writing to both RAM chips during switching on and switching off the main 5V supply. The CHIP SELECT lines of both RAMs must be available for use by the rest of the circuit when the main 5V supply is present.

Any suggestions for such a circuit would be gratefully received and I'm sure would interest other readers.

G A Haddon
Birmingham

Your request is being dealt with and will appear as a Blueprint. - Ed.

InterCard 1 Update News

Here's an update on developments concerning the InterCard 1 Universal Interface Card for the IBM PC:

1) The software disk for the project has been revised to version 1.1. Improvements to the disk are mainly to do with the format and structure of the files, with a few extra sound samples. No new programs yet.

2) Distribution of the software disk is now being handled by:

The Public Domain
Software Library
Winscombe House
Beacon Roall
Crowborough
Sussex
TN6 1UL
United Kingdom
Tel: (0892) 663298

The volume number of the InterCard 1 software is 3861 - this

should be quoted when placing an order. The current cost for one disk in the UK is £6-00, with free postage. Due to other commitments I will no longer be able to honour requests for the software disk. All future orders should be sent to the PDSL at the above address. Those readers who originally acquired the high-density version of the disk from the author and found two extra directories of programs - namely SCOPTRAX and MODPLAY - should note that the disk from the PDSL does not contain these programs (they can be found on disks 3676 and 3554 respectively) Further details/catalogue available from the above address.

Neil Johnson

PROFESSIONAL SERVICES

We offer a full R.F. DESIGN SERVICE from design and development to prototype. Our extensively equipped laboratory with screened room is available for EMC PRE-TESTING to ensure products comply with the EC Directive on emissions and susceptibility.

R. N. Electronics EMC
1 ARNOLDS COURT, ARNOLDS FARM LANE, MOUNTNESSING
ESSEX CM13 1UT. Tel: 0277 352219 Fax: 0277 352968


Low cost data acquisition for IBM PCs & compatibles...

A unique range of low cost data acquisition products for IBM PCs and compatibles. Installed in seconds they simply plug directly into either the serial or parallel port. They are completely self contained, require no external power supply and take up no expansion slots.

Each device comes with an easy to use software package (PicoScope, PicoLog or both). C, Pascal, and Basic drivers are supplied for those who want to develop their own software, as is a manual giving full details of the hardware and software. All software supplied on 3.5" disk.


PICO TECHNOLOGY

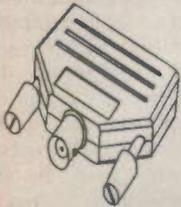ADC-10 Up to 24kHz sampling rate from a 386/33MHz machine
0-5V Input range
BNC input connector allows use of standard scope probes
30V overload protection
Parallel port connection
Includes PicoScope software




Single Channel 8 bit ADC **£49**

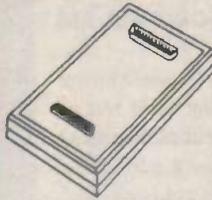ADC-16 Software selectable single ended or differential inputs
Resolution programmable between 8 and 16 bits + sign
 $\pm 2.5V$ input range
5V reference output
Connects to serial port
Includes PicoLog software




8 Channel 16 bit + sign ADC **£99**

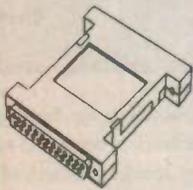ADC-11 15K samples per second
0-2.5V Input range
Digital output
D25 input connector
30V overload protection
Parallel port connection
Includes both PicoScope and PicoLog software



11 Channel 10 bit ADC **£75**

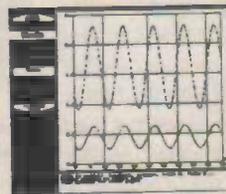PicoScope 'Virtual instrument' software package for the ADC-10, ADC-11 and ADC-12.



Scope, voltmeter, spectrum analyser

Storage oscilloscope with trigger and timebase. Traces can be printed and saved. Multiple meters on screen. Real time spectrum analysis.

ADC-12 Up to 18kHz sampling rate
0-5V Input range
BNC input connector allows use of standard scope probes
30V overload protection
Parallel port connection
Includes both PicoScope and PicoLog software



Single Channel 12 bit ADC **£85**

PicoLog Collect samples from 1 permsto one per day. Scale samples linearly, by equation or by table look-up. Graphical (against time or XY) and text reports can be displayed, printed or exported.



Advanced data logging software

Picolog is also available for the ADC-10: call for details.

Typical application	ADC-10	ADC-11	ADC-12	ADC-16
Oscilloscope	●	●	●	
Voltmeter	●	●	●	●
Spectrum analyser	●	●	●	
Audio sampling	●		●	
Chart recorder emulation		●		●
Temperature measurement	●	●	●	●
Pressure measurement	●	●	●	●
Chromatography				●
Automotive monitoring		●		●
Medical research		●	●	●
Education	●	●	●	●

PICO BENEFITS

- 30 day no quibble money back policy
- Full 1 year guarantee
- 1 year's free software upgrades
- Free technical support
- Free user newsletter
- Same day dispatch



Pico Technology Ltd. Broadway House, 149-151 St Neots Road, Hardwick, Cambridge. CB3 7QJ.

TEL: 0954-211716 FAX: 0954-211880



Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT.

Electronic Picture

*A moving LED display
by Colin Melkle*

I designed this project as a novel present for my girlfriend. I intended building some sort of display that could show a series of short messages and the original intention was to build a large display that would show several words at a time, although I soon discarded this idea. The circuit would be too complex and even the size of the display would be impractical for my girlfriend's bedroom. I therefore decided on a small LED display that would display one character at a time. This had several advantages, the display could be built into a small picture frame and the electronics to drive the display could be kept very simple. I soon realised that in addition to text, interesting patterns could be displayed. As development progressed, I thought the patterns would be more interesting if they responded to surrounding sound, particularly music, so a sound activated circuit was included.

The Electronic Picture itself is made up of an 8 × 8 array of LEDs, mounted in a small picture frame. The picture can display short text messages, or various types of patterns to form visual effects. It is similar to the LED type displays found in Post Offices and shops, but on a smaller scale. The circuit allows the messages or patterns to be displayed at a fixed rate. In addition, the circuit has a built in microphone, which allows the display to respond to surrounding sounds.



This feature is of little use for text messages but very good visual effects can be created. Both modes of operation have controls that allow the sensitivity or speed to be altered. A switch allows either sound or automatic mode to be selected. The circuit can store 16 different sequences, which can be individually selected (a push button allows you to cycle through the sequences), or all the sequences can be displayed in turn after a set number of repetitions.

The patterns or messages are stored in an EPROM. Programming the EPROM is a time consuming task (although not as difficult as you may first think), but this is a compromise to keep the circuit simple. The circuit can be powered from the mains or via a small external PSU.


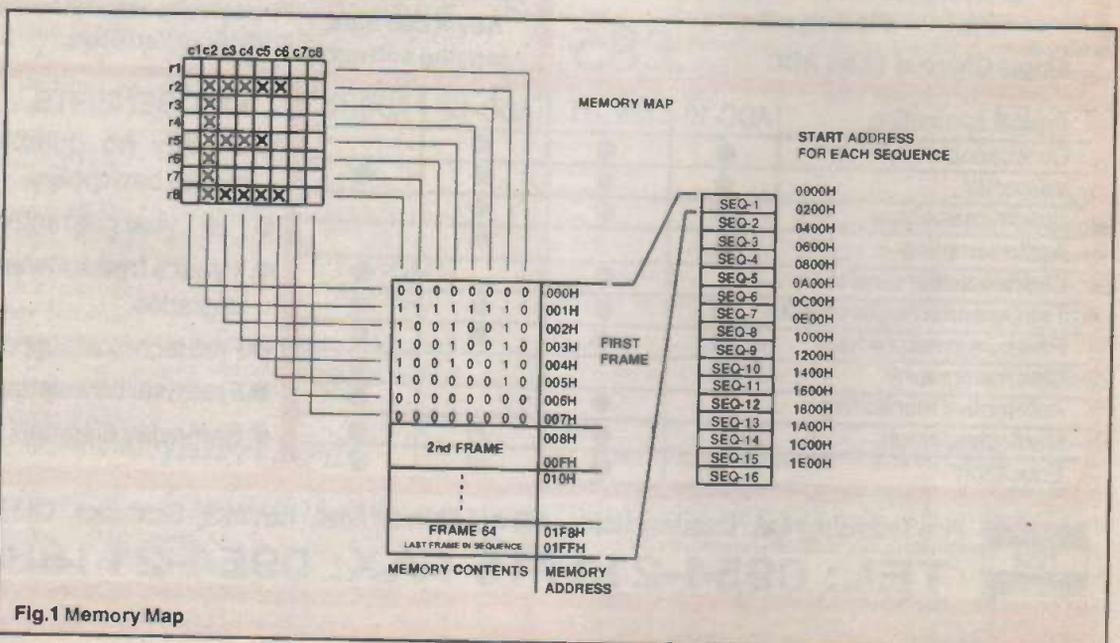


Fig.1 Memory Map

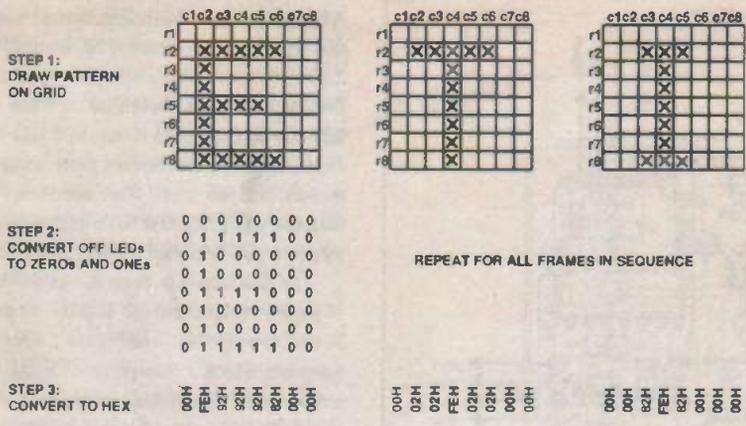

EXAMPLE 1A: DATA FOR THE CHARACTERS 'ETI'

0000	00	00	00	00	00	00	00	00
0008	00	00	00	00	00	00	00	00
0010	00	00	00	00	00	00	00	FE
0018	00	00	00	00	00	00	00	FE 10
0020	00	00	00	00	00	00	FE 10 10	
0028	00	00	00	00	FE 10 10 10			
0030	00	00	00	FE 10 10 10 FE				
0038	00	00	FE 10 10 10 FE 00					
0040	00	FE 10 10 10 FE 00 00						
0048	FE 10 10 10 FE 00 00 82							
0050	10 10 10 FE 00 00 82 FE							
0058	10 10 FE 00 00 82 FE 82							
0060	10 FE 00 00 82 FE 82 00							
0068	FE 00 00 82 FE 82 00 00							
0070	00 00 82 FE 82 00 00 00							

FIRST 15 FRAMES OF A SEQUENCE

EXAMPLE 1B: EXAMPLE OF SCROLLING TEXT
THIS EXAMPLE SCROLLS 'HI' ACROSS THE DISPLAY
NOTE THAT IT TAKES 15 FRAMES TO SCROLL TWO LETTERS

0000	10	10	10	10	10	10	10	00
0008	02	04	08	10	20	40	80	00
0010	00	00	00	FE	00	00	00	00
0018	80	40	20	10	08	04	02	00


EXAMPLE 1C: 'SPINNING *' PATTERN
THIS SEQUENCE STARTS WITH A '-', FOLLOWED BY ' / \ / \ / \ / \'
THIS GIVES THE EFFECT OF A SPINNING STAR
(THE STAR SPINS IN TIME WITH THE MUSIC)

Fig.2 Examples for creating patterns

In Operation

It is important to understand the memory organisation and the way in which patterns are displayed if you are to create your own display sequences. Figure 1 shows how the memory is organised and how it relates to the LED display.

The EPROM is an 8K x 8bits device. Each byte in the EPROM corresponds to a column on the LED display. Each of the 8 bits within the byte control a LED within that column (setting a bit to a 1 turns the LED on). The memory is firstly organised into 8 byte blocks and each block corresponds to one complete picture 'frame' (one byte for each of the 8 columns). By repeatedly displaying the 8 byte block, with each column displayed in quick succession, it appears that all 8 columns are being displayed at the same time, although there is only one on at any one time. Referring to Figure 1, memory location 0000 corresponds to the first column C1, the data in this location is 00H, thus all the LEDs on this column would be off. Location 0001 corresponds to the second column C2, this contains FEH, where all the LEDs in column C2, apart from the top LED R1, would be on. If you complete this for the complete block (i.e. 0000 to 0008) you will find the character 'E' would be displayed. Each of these 8 byte blocks are displayed for a period of time, e.g. 1 second,

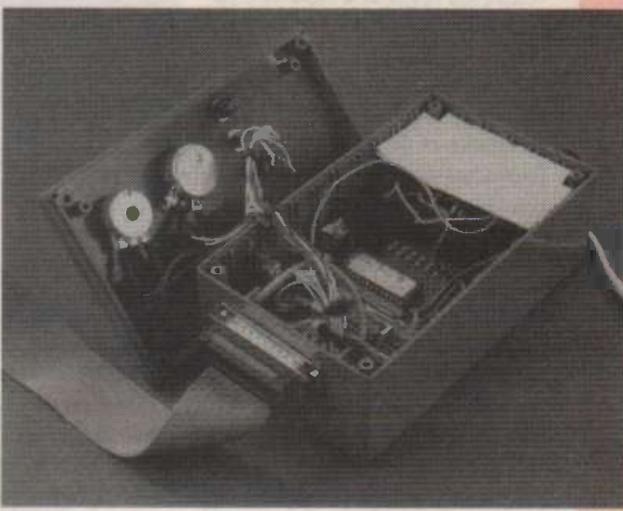

then the next 8 byte block is displayed. This next block would contain, the next character in the message or the next part of the picture sequence. Thus, each 8 byte block defines a picture frame. 64 of these blocks are displayed in sequence for a set period of time, to create a complete message or

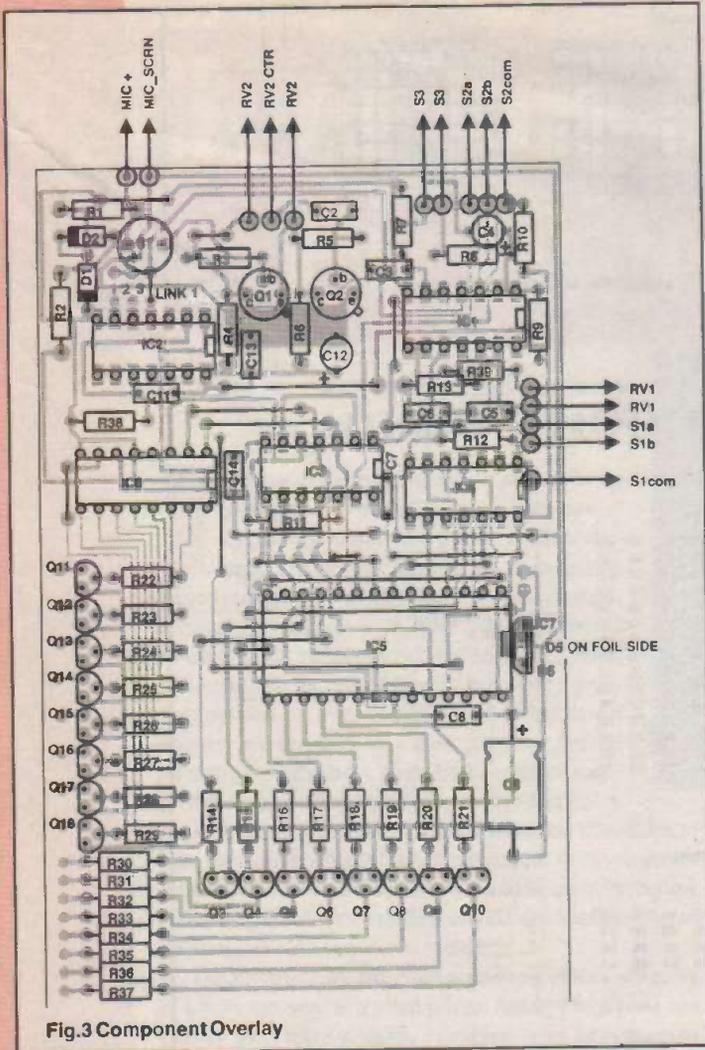


Fig. 3 Component Overlay

effect. Since there are 64 frames in any complete message or effect, the maximum length of a message is 64 characters. At the end of each message or effect, the circuit loops back to the first frame in the sequence and the sequence is repeated. If the period between each frame is shortened, the individual frames can be run together to create moving pictures or scrolling text.

If the circuit is operating in sound mode, the period between frames depends upon the music or surrounding sounds, (as a result text is difficult to read in this mode, but it results in interesting patterns). The total memory used for one complete message or picture sequence is 0.5K, therefore 16 individual messages or sequences can be stored in 8K of memory (8 columns \times 64 frames \times 16 sequences = 8K of memory).

Creating Patterns In The EPROM

Messages can be displayed in a number of different ways. The most memory efficient way is to display one character at a time (note only one full character can fit in the 8 \times 8 array

of LEDs). This method makes long messages difficult to read. A better way is to scroll characters across the display, although this uses a greater amount of memory and the length of the message that can be displayed is greatly reduced. You may find the 64 frames a limitation when creating messages but this can be expanded if required (see the section on further expansion). When creating patterns or visual effects, the 64 frames will be more than adequate. To create your own patterns you first must have access to an EPROM programmer and you will find a good text editor invaluable.

The first step is to draw out an 8 \times 8 grid on a blank piece of paper, to represent the display. Number the columns (C1-8) and rows (R7-0), see Figure 2. This can now be used as a template. Place a thin piece of blank paper on top of your template and lightly draw on the grid, the character or pattern you wish to display. Put a X in all the boxes where a LED should be On. Note that if only displaying text, a 5 \times 7 array should be marked out (as most text can fit into this array), that is, don't use C1, C7, C8 and row R1.

The next step is to convert the Xs into a Hexadecimal number. This can be done in two steps, convert the Xs to 1s and the blank spaces to 0s (remember to include all the blank columns). Reading each of the columns, convert the 8 digit binary number into a hex number (note the bottom, R7 is the MSB). This can be seen in Figure 2, example 1. This process is simply repeated for all the different picture frames you require for your sequence. Remember, you need 64 frames to complete one sequence. If your sequence is, say only 16 frames it can simply be repeated 4 times to fill the 64 frames, blank frames (i.e. all 0s) or repetitions of frames can be used to pad sequences out.

Displaying moving (i.e. scrolling) text, is equally simple. For example, to scroll the letter 'E' across the display. Draw the 'E' on the grid, as previously described, move the top sheet of paper so that the 'E' is just to the right of the grid, so that the grid is blank. The blank grid is the first frame.



Move the top sheet one box width to the left, the first part of the 'E' should now be on the grid, (i.e. a vertical line in C8 from R7 through R1) - this is the second frame. This is simply repeated until the 'E' is shifted fully into the display, the next character can be shifted in from the right as the 'E' is shifted out to the left.

Although this may seem a very long process, after a bit of practice it becomes very easy, and drawing each pattern becomes unnecessary.

A small problem will arise when displaying individual characters and moving text or patterns. To display individual characters, you require the frames be displayed at a much slower rate than for moving sequences (e.g. Characters have to be displayed for >1 second, but moving sequences require frames to be displayed for <0.25 sec). This can be overcome by setting the frame speed to the faster setting (e.g. 0.25s). When individual characters are to be displayed they can be repeated a number of times, so in effect they are displayed for a long enough period of time. This avoids having to alter the frame speed between sequences.

Figure 2 gives a few more examples for frames and sequences. When you have collected all the data for your picture sequences you must generate a valid fuse map. Figure 1 shows the start and end addresses for each sequence. If you wish to generate your fuse map in INTEL HEX format, which is accepted by most EPROM programmers, the format is given below.

```
:Byte Count|Address|Block Type|Data Bytes|Checksum
Byte Count : No. of data of bytes E.G 08 (2 Characters)
Address : 4 ASCII hex characters E.G. 0008
Block Type: 2 characters. 00 data, 01 end of file
Data Bytes : Data, No. of bytes specified by byte count
Checksum : Two's Complement of the sum of all the bytes in the line.
```

```
e.g. :0800000000FE929292820000FDC2 'E'
:08000800000202FE02020000FFEA 'T'
:08001000000082FE82000000FFE6 'I'
:00000001FF END OF FILE
(last line, always the same)
```

Note: Ensure there are no extra characters after the checksum.

Construction

Construction of the PCB is fairly straight forward and Figure 3 shows the component overlay. The main thing to be careful about is the placement of the numerous links. These must be put in place first, as some of them go under IC5. Also make sure that all the links are insulated, as some are close together. Next, solder in place all the resistors and diodes, followed by the ICs and transistors. All the ICs can be mounted in sockets if desired, but IC5 (the EPROM) must be, as it will probably need to be removed several times. The regulator, IC7, requires mounting on a small heatsink, which can be directly mounted to the regulator with some heatsink compound. If the heatsink is close to any of the component leads, use an insulator and mounting kit to isolate it. Do not mount the regulator too close to the board or the heatsink will foul against IC5 (if it does, bend back or cut off the bottom fin of the heatsink). D5 is soldered on the reverse of the PCB across the regulator's input and output terminals.

Figure 4 shows connections to the switches and potentiometers. When connecting the microphone, check the connections with the microphone you have bought. The PSU components, i.e. transformer, C10 D3 and D4, are not mounted on the PCB and all connections to these should be suitably sleeved. Take care that all the usual mains precautions are observed when mounting the components in its enclosure. Alternatively, the circuit can be powered from an external 9V DC supply that can supply greater than 300mA. Simply connect the supply to the +ve and 0V inputs on the PCB. This method may be preferred if the circuit is to be operated by children - it removes the mains hazard and

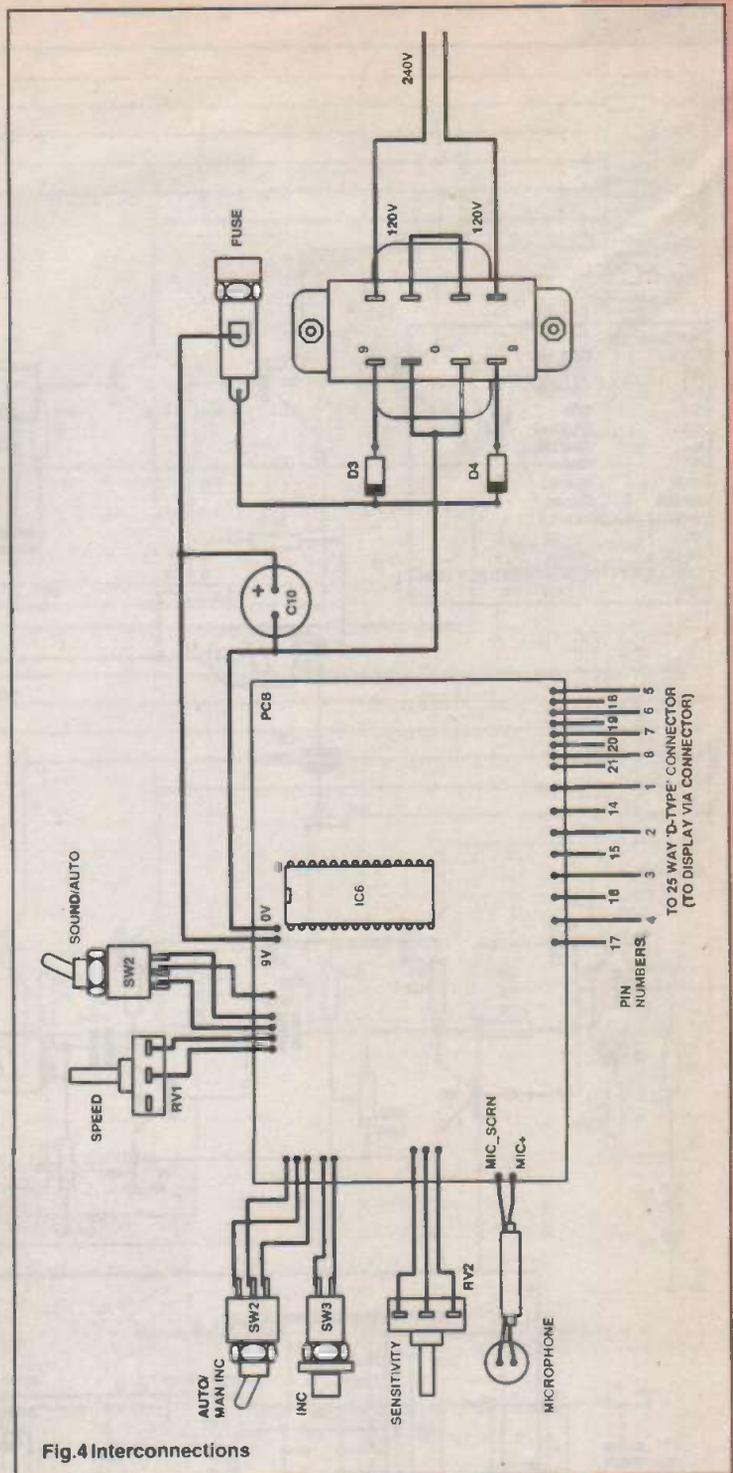


Fig.4 Interconnections

reduces the size of the control box.

Figure 4 also shows the connections to a 25 way D Type connector. Obviously any pins on the connector can be used as long as the rows and columns match up on the control box and on the display. You may even wish to omit the connector and take a ribbon cable directly to the display, although the connector is recommended.

Display

The 64 LEDs are mounted on a thick piece of black card, within a small picture frame as shown in Figure 5. Any picture framing shop will make the frame for you. A plastic face will give more room for the LEDs than would glass. The card should be cut to size, to fit the frame and then the

NOTE:

IC1	4093
IC2	4024
IC3	74HC393
IC4	4024
IC5	27C64-15
IC6	74HC138
IC7	7805
Q1,2	BC109C
Q3-Q10	2N3706
Q11-Q18	BC327
D1,2	1N4148
D3-D5	1N4002
LED1-LED64	5mm DIFFUSED RED LEDs
FS1	1A 125V FUSE


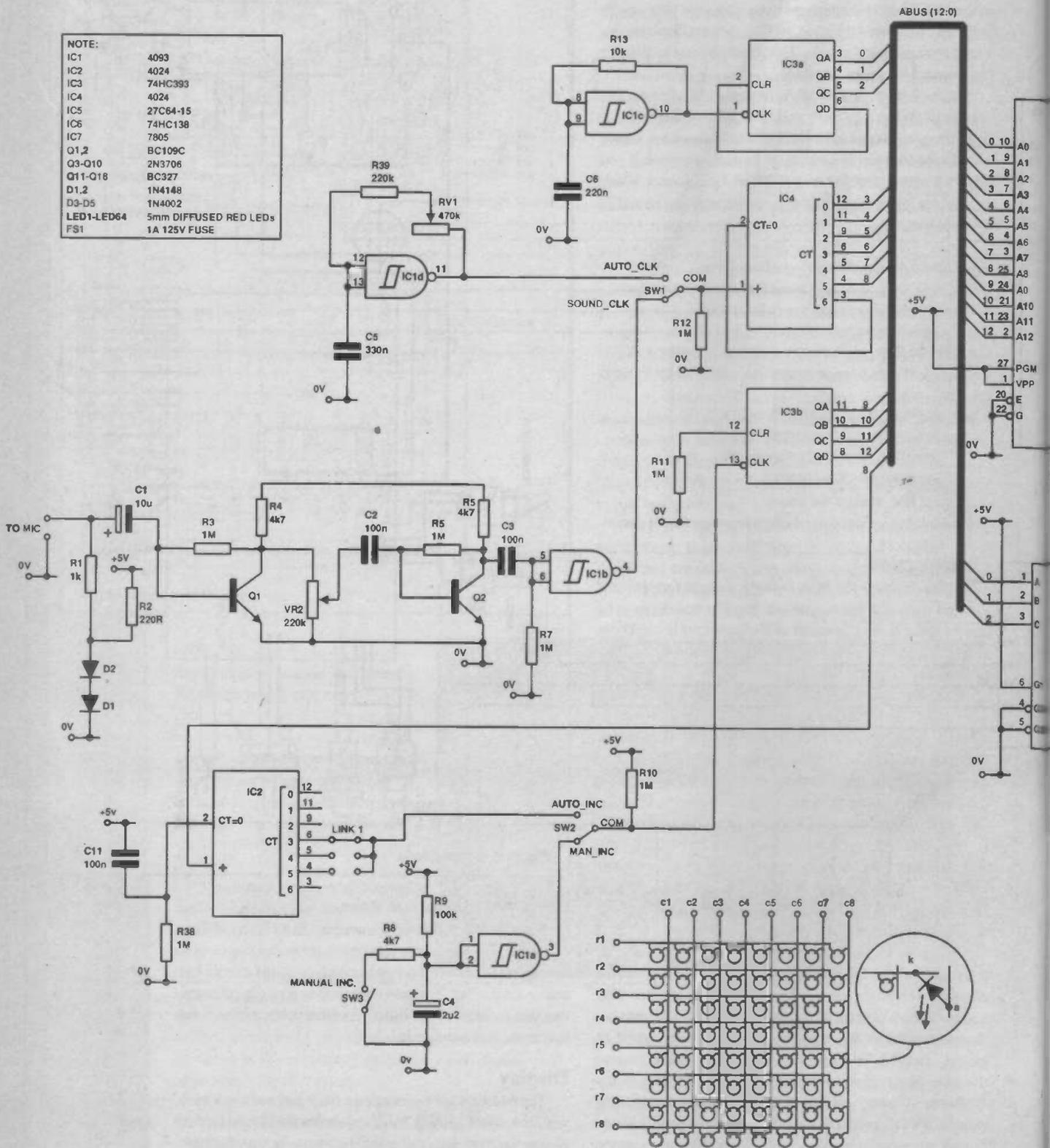


Fig.6 Circuit diagram

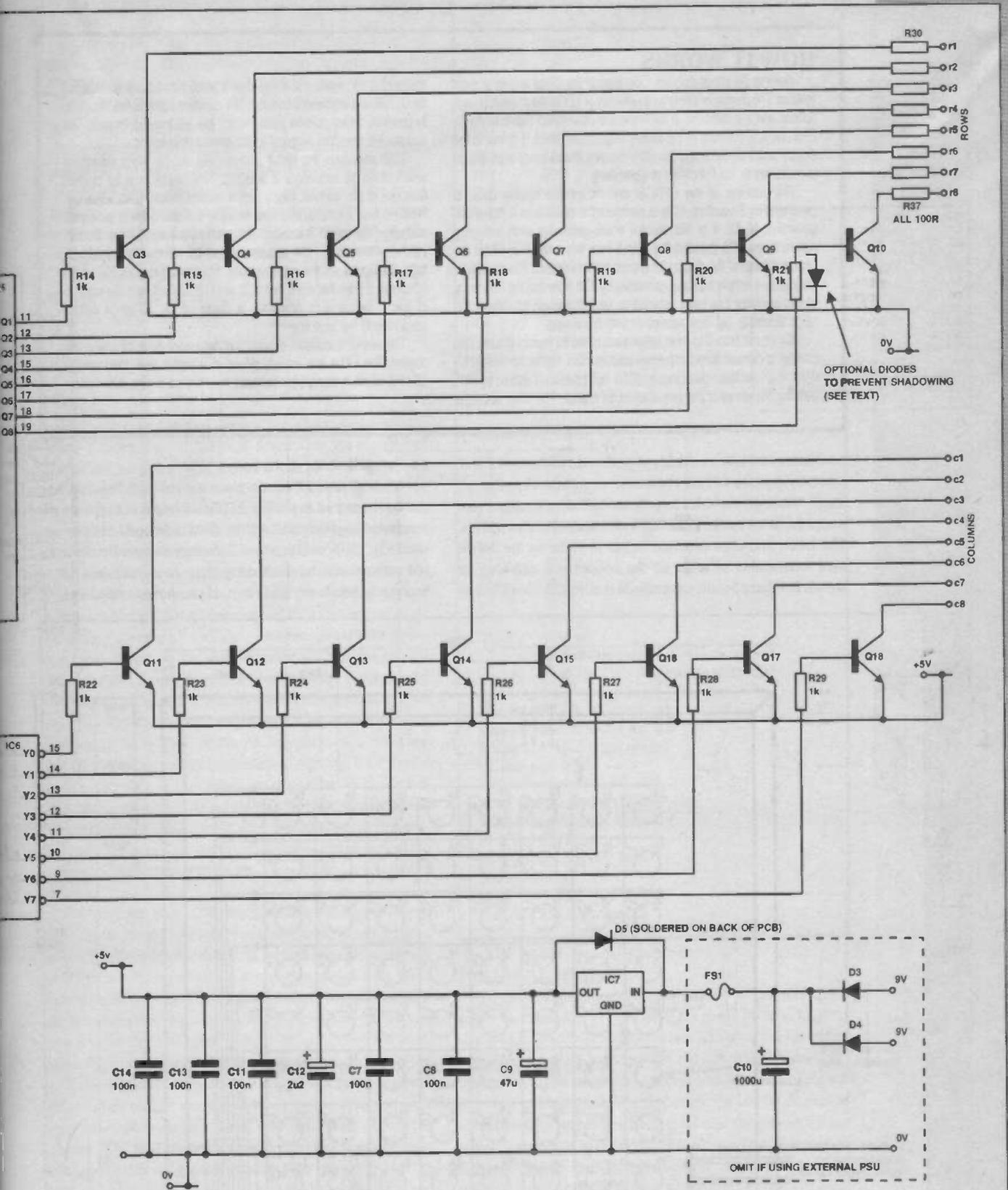

HOW IT WORKS

Refer to the circuit diagram. Operation of the circuit is quite straight forward. The display is simply an 8 × 8 array of LEDs, the anodes in each column and the cathodes in each row are commoned together. An 8k EPROM, IC5, contains all the display information, which is output to the display under the control of the other circuitry (the memory organisation is explained in the Principles of Operation).

The address of the EPROM and hence the display data, is generated by 3 counters. IC3a is configured to count from 0 to 8 which generates A0-A2. It is this counter which generates each individual picture frame. IC6 decodes the output from this counter to select the correct column of the display for any particular address. The counter is clocked by a simple oscillator generated by IC3. Note that the frequency of this oscillator has been selected to be fast enough to prevent the LEDs flickering, but slow enough to limit shadowing.

IC4 counts from 0 to 64 to select each of the 64 frames in turn. This counter is clocked from one of two sources. The first is the 'auto_clk', which is an oscillator generated by IC1d. Its frequency is altered by RV1 allowing the speed of the sequence to be altered. The other source is

the 'sound_clk'. Here, the signal from a small microphone is amplified by Q1, Q2 and associated circuitry. The resultant signal is fed into IC1b, to generate better defined pulses which are fed into the counter. The counter will therefore respond to the surrounding sound.

IC3b generates the last 4 address bits, A9-12, which determine which of the 16 sequences is selected. This counter, can be clocked from one of two sources. Firstly from a manual switch, SW3. IC1a, C4, R8 & R9 form a simple debounce circuit so that one pulse is generated each time the switch is pressed (this works because IC1 has Schmitt inputs). Alternatively, the sequences can be incremented automatically. A8 toggles once every sequence, this is used to clock IC2 which effectively divides this down by 16, 32 or 64 dependent upon the position of link_1, hence each sequence is displayed 16, 32 or 64 before advancing to the next one.

The output transistors provide the necessary drive to power the display. The LEDs are actually driven at a higher level than normal (30mA), which is acceptable because they are on a 12% duty cycle.

positions of the holes marked out on the rear of the card. Next, carefully drill the 64 holes (diameter to suit the clips that are used). When all the holes have been drilled, any ragged card round the holes can be tidied up with a scalpel or sharp knife. The LEDs and clips can then be put in place on the drilled card - remember to align all the anodes and cathodes, as shown in Figure 5 (note the cathode is normally identified by

the flat on the side of the body).

When all the LEDs are in place and correctly lined up they can be connected as shown. All the cathodes in each row are connected together and all the anodes in each column are similarly, connected together. Take care that neither the rows nor columns can be shorted together. Also, take care not to weaken or break any LED legs, if you have to bend any.

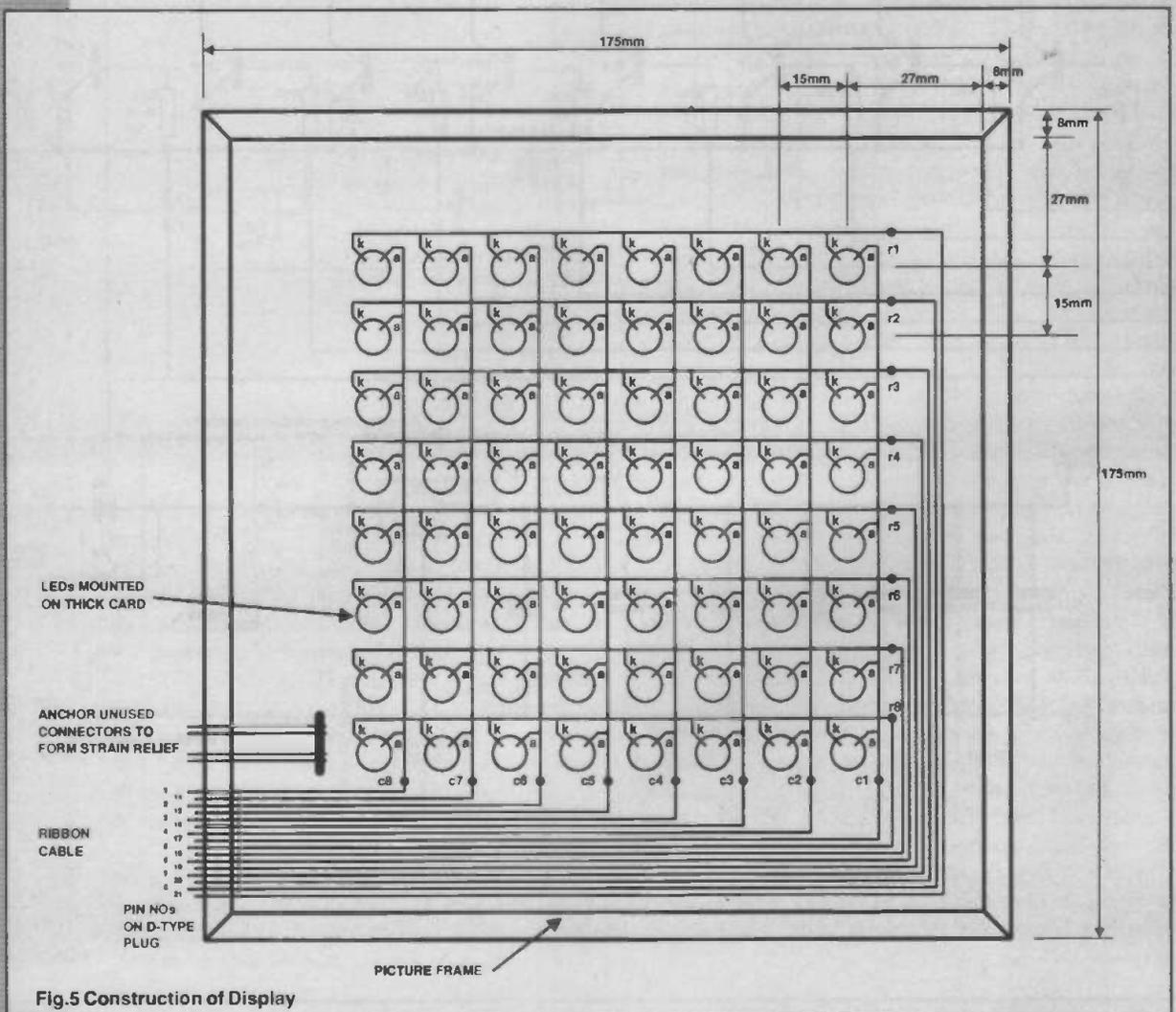


Fig.5 Construction of Display

When the circuit has been tested and found to be correctly working, the back of the 'picture' can be coated in silicon rubber (the clear type used to seal sinks, windows, etc. works well). This will help to hold all the LEDs in place and will also stop accidental shorts.

Note that the LEDs used should all be of the same type. The best way to get LEDs of matched brightness and colour, is to buy all the LEDs from the same supplier at the same time. Beware of bargain packs as they may contain different types. It is also best to use bright diffused LEDs with a wide viewing angle.

The suggested connector is a 25 way D Type. Using an IDC type simplifies the connections required. Although only 16 conductors of the ribbon cable are needed, the other 9 conductors can be glued to the back of the picture to prevent straining the other wires.

Testing

Before testing can start there is one option which should be set. The position of LINK_1 determines the number of times each sequence will repeat when in auto increment mode. In position 1, each sequence will repeat 16 times, in position 2, 32 times and 64 times in position 3. The link should be soldered in whichever position you wish (initially, for testing, it does not matter).

To test the circuit, connect the PCB up to an external 9V PSU (so you can poke about without worrying about the mains voltages). With a programmed EPROM in place and the display connected, turn the power on. Hopefully something will appear on the display, with SW2 in the manual position. Press SW3 a few times to advance the sequences (if you have not filled your EPROM this may be necessary, until you find a valid sequence). Assuming you have something on the display, with SW1 in the AUTO position, a valid sequence of pictures should be displayed. Altering RV1 should change the speed at which they are displayed. With SW1 in the sound position, any sound close to the microphone should alter the display. RV2 should alter the sensitivity. If everything appears to be OK, the internal supply can be connected (if used) and the circuit can be put into its box and suitably secured.

If everything is not OK, there are a few things to check. First check for the obvious - solder shorts, missing links, correct component orientation. If parts of the display do not appear to be working check the orientation of the LEDs. If the pattern on the display does not make sense, check the row and column wires have been connected correctly and ensure you have a valid EPROM. If the sound circuitry does not work check the connections to the mic. are correct.

A small amount of shadowing on the display may be seen under certain circumstances. This was not found to be a great problem on the prototype, but if you wish, there is a simple solution. The problem is caused because the output transistors cannot turn off quickly enough (Q3-10 seem to be the main culprits). A small diode (1N4148) should be soldered across the base resistors (R14- 21), the anode towards the transistors and cathode (stripe) towards IC5. This will cause the transistors to be turned off much more quickly.

You may wish to alter the frame speed, i.e. the time between successive frames, although RV1 gives a large amount of control. This can be done by altering C5 - increasing it's value will slow the frame speed.

PARTS LIST

RESISTORS

R1, 14-29	1k
R2	220R
R3,5,7,10	1M
R11,12,38	1M
R4,6,8	4k7
R9	100k
R13	10k
R30-37	100R
R39	220k
RV1	470k
RV2	220k

CAPACITORS

C1	10µ16V elect
C2,3	100n ceramic
C4,12	2µ2 tant
C5	330n min. poly
C6	220n min. poly
C7,8,11,13,14	100n miniature poly or ceramic
C9	47µ16V elect
C10	1000µ16V elect

SEMICONDUCTORS

IC1	4093
IC2	4024
IC3	74HC393
IC4	4024
IC5	27C64-15 8K ∞8 CMOS EPROM
IC6	74HC138
Q1,2	BC109C
Q3-10	2N3706
Q11-18	BC327
D1,2	1N4148
D3,4,5	1N4002
IC7	7805 5V 1A
LED1-64	5mm Red LEDs (high intensity preferred)

MISCELLANEOUS

2 terminal miniature electret mic
2 x miniature SPDT toggle switches
Miniature push switch
TR1 Transformer 6VA 0-9, 0-9V o/p. (or 9V external PSU >300mA o/p).
1A fuse and panel mount fuse holder
25 WAY D type socket
25 WAY D type plug (IDE Type)
64 Low profile LED clips
Small TO220 heatsink (21°C/W)
Box (150 x 90 x 60mm Approx.)

Further Expansion

If you wish to experiment, the amount of memory could easily be expanded. A 16K EPROM could be used in place of the 8K, the additional address line A13 would come out on pin 26. If the track between IC4 pin 2 & 3 is cut and pin 3 connected to the additional address line, the length of each sequence could be doubled, although the last 64 frames of each sequence would be offset by 8K (i.e. the first 64 frames of seq 0 would be at 0000 to 01FF and the last 64 would go from 2000H to 2FFF). Alternatively, the number of sequences could be doubled by connecting A13 to the common pin of a SPDT switch with the other two pins connected to 0V and +5V. The switch would allow the upper or lower 16 sequences to be selected.

There are also 4 unused pads on the PCB. These are connected from A9 to A12. This allows the current sequence number to be decoded and displayed on a 7 segment display (with a little decoding). None of the above suggestions have, however, been tested.

Anniversary AutoMate Mixer

This month, Mike Meechan looks at Pots and Pans and just what they have to do with Routing

It is a belief widely held by engineers and designers alike that on a desk, there can never be too few Aux Mixes (or FX Sends, or a Foldback Mixes as they are sometimes known). Some might go so far as to say that the number (or lack) of facilities in this particular region determines just how flexible (or inflexible, as the case may be) the whole of the desk is.

The Aux Mix section is an area of the desk which lends itself readily to some form of AutoMation. The requirement for automation has arisen because of the pressing need, in the interests of space, convenience, and more importantly, economy, to share FX units between tracks. The engineer may mixdown each vocal track separately and during each of these operations, he may wish to add reverb, so the reverb unit might be connected to Aux Mix 1 output socket. Any channel requiring access to the reverb during mixdown would have its signal routed to the mix bus via the associated Aux Mix 1 Level pot - and perhaps an Aux Mix 1 Mute/Unmute pushbutton - at the appropriate time. Perhaps, once a collage of almost-completed sounds had been built up, the FX might only be required for brief intervals, or perhaps on different channels in quick succession. Such an operation lends itself readily to implementation by the console automation system, which itself may be under the direction of some kind of automatic time reference control (timecode), or manual time reference.

On a fully equipped Aux Mix module, there are a total of 12 accessible buses. Aux.'s 1 - 4 are switchable Pre or Post Fade. These are also stereo FX sends, with each Aux Mix able to be panned across the pair of busses associated with the control. In effect, a stereo signal fed to an external FX unit can have the same spatial positioning as the channel, or a different one, for special effects. Within this particular group of Aux Mixes, number 1 is the most capable of the four. Not only is it able to be switched pre or post fader, but the output from the panpot is able to be routed not to Aux 1 Mix bus, but rather to the multitrack group routing matrix. The normal source assigned to the Group Routing Matrix (the Channel panpot) is disconnected in this instance, although routing to the main stereo mix busses is uninterrupted and available, as always, via the Mix pushbutton. In effect, this means access to a further possible 32 busses, with all of the attendant operational advantages, especially during those occasions where a lot of different foldback or monitor mixes are required (PA work, perhaps).

Aux.'s 5-8 are post fade stereo pairs, able to access the 5/6 pair, or the 7/8 pair, or another pair - 9/10 in the instance of 5/6, and 11/12 in the instance of 7/8. Each of the six pairs of Aux Mixes on the AutoMate channel architecture can be muted or unmuted by the console AutoMation system (if this is fitted). AutoMated control can be overridden manually with local, strip-mounted pushbuttons. Even on a non-

automated console, it is still possible to properly mute any of the twelve Aux Mixes as a pair.

Although proper muting and turning the rotary level control to zero would seem to be doing the same thing (i.e. reducing the channel's contribution to that Aux Mix bus to zero), they are completely different in their electrical operation and subsequent effect. Muting in the correct sense of the word means physically disconnecting the bus driving resistor from the mix bus, whereas moving the level control to zero merely attenuates the channel contribution.

Ah, you may say, but surely this has the same subjective effect, in that each method removes the unwanted signal (associated with that channel) from the bus. This is partially true, but it misses the point of most importance, and unfortunately, it is a common misconception shared by engineers and designers alike. Insofar as the channel signal is concerned, both are similar, but with the mix bus, the two most definitely do not achieve the same effect.

To understand the basic electrical differences between muting and attenuation, we need to refer to something said way back in the past (Part 4). Consider Figure 1a. On the face of it, the first two achieve the same electrical effect - isolation of signal input from mix bus - with Figure 1b scoring in the added convenience stakes by providing the facility - a switch - to turn the signal send on and off from the mix bus at any desired level. Many mixers use this technique in so-called muting circuits, so what is wrong with it?

Consider Figure 1a once more, since it is a not untypical arrangement, with 36 or so channel inputs all able to contribute to a particular Aux Mix bus (which we'll call Aux 1, for arguments sake). We've also just recently bought two thousand quids worth of all singin', all dancin' digital FX gizmo which, quite naturally, we want to use on many parts of the final mix. We connect its input to FX Send 1 (Aux 1 Output), connect its output to the FX Return, turn Channel 1 Aux Mix 1 Level control up and start the tape machine, with Track 1 replaying through Channel 1 - it's an in-line desk. The vocal ends and we suddenly think, "Wait a minute, where's that hiss coming from." We check the FX manufacturer's spec. sheet which quotes noise and distortion as being -90 down on 0dBu. We know from experience that the hiss isn't -90dBu - more like -60dBu. We mute (or turn down) Aux Mix 1 on all of the channels and the hiss is still there, so it can't be coming from the channels. Hey presto, unplugging the FX unit from the FX Return socket causes the noise to disappear. QED. Must be a noisy FX unit, or a manufacturer quoting some distinctly unrealistic figures in the spec. sheets - ad-man's euphemism for lying - or both? Not necessarily...

Pause to consider the mix bus at this time. We have 36 paralleled Rs's and one Rf. All resistors are equal in value, so it's unity gain for each of the individual contributions to the mix bus, and a gain of 36 for any composite signals


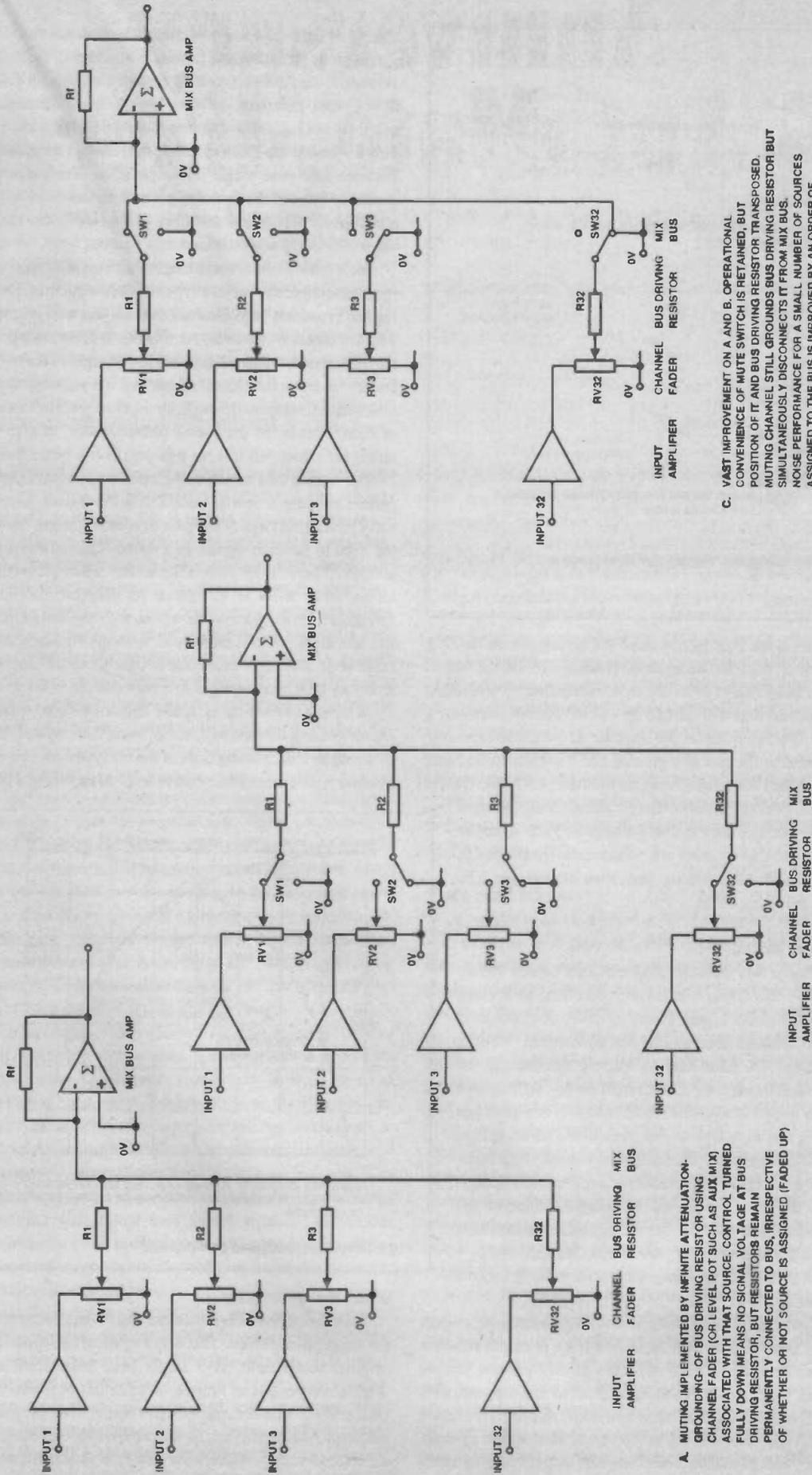


Fig.1 Typical Aux mix muting arrangements


A. MUTING IMPLEMENTED BY INFINITE ATTENUATION.
 GROUNDING OF BUS DRIVING RESISTOR USING CHANNEL FADER (OR LEVEL POT SUCH AS AUX MIX) ASSOCIATED WITH THAT SOURCE. CONTROL TURNED FULLY DOWN MEANS NO SIGNAL VOLTAGE AT BUS DRIVING RESISTOR, BUT RESISTORS REMAIN PERMANENTLY CONNECTED TO BUS. (RESPECTIVE OF WHETHER OR NOT SOURCE IS ASSIGNED (PAID UP))

B. OPERATIONAL IMPROVEMENT ON A BUT NO MORE. SOURCES ARE ABLE TO BE ASSIGNED TO BUS A LEVEL DETERMINED BEFOREHAND BY THE CHANNEL FADER (OR LEVEL POT). CAN NOW BE 'MUTED' WITHOUT DISTURBING SETTING OF LEVEL CONTROL. HOWEVER, BUS DRIVING RESISTORS ARE STILL EFFECTIVELY CONNECTED TO THE MIX BUS REGARDLESS OF THE SETTING - MUTE OR ON - OF THE MUTE SWITCH. NOISE GAIN IS STILL $R_{bus} \times 32/R1$ FOR ALL POSSIBLE SOURCE ASSIGNMENTS. IN SUMMARY, A NON-ECONOMICAL, ALMOST WORTHLESS USE OF SWITCHES AS FAR AS IMPROVED NOISE PERFORMANCE IS CONCERNED.

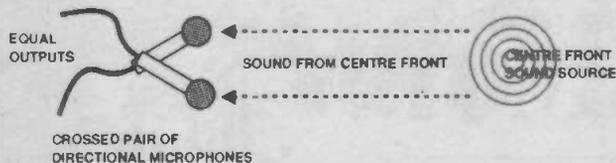C. VAST IMPROVEMENT ON A AND B. OPERATIONAL CONVENIENCE OF MUTE SWITCH IS RETAINED, BUT POSITION OF IT AND BUS DRIVING RESISTOR TRANSPOSED. MUTING CHANNEL STILL GROUNDING BUS DRIVING RESISTOR BUT SIMULTANEOUSLY DISCONNECTS IT FROM MIX BUS. NOISE PERFORMANCE FOR A SMALL NUMBER OF SOURCES ASSIGNED TO THE BUS IS IMPROVED BY AN ORDER OF MAGNITUDE - AROUND 25 - 30 dB FOR A 32 INPUT BUS. DRIVING RESISTORS ARE CONNECTED TO THE BUS WHEN NEEDED. WITH A LARGE NUMBER CONNECTED, NOISE PERFORMANCE IS NO WORSE THAN A OR B.



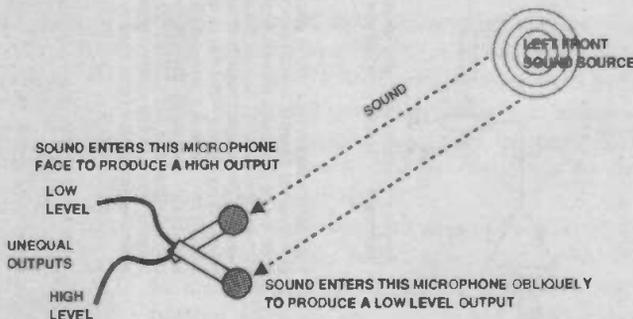A. CROSSED MICROPHONE RECORDING - IDENTICAL SIGNALS REACH BOTH MICROPHONES AND GIVE EQUAL OUTPUTS



B. CROSSED MICROPHONE RECORDING - THE OFF-CENTRE RECORDING CAUSES UNEQUAL OUTPUTS

Fig.2 Crossed mic. recording

present on the bus. Surely there are no signals on the bus, since everything has been turned down or off? On the face of it, this would seem to be the case. Nevertheless, something is there and it gets amplified up - from -100dBu, say - by a factor dependent upon the number of paralleled resistors presented to the bus at a given time. It is then stuffed out, through the FX unit and back into the mixer at -70dBu (where it's audible) - regardless of the excellent specification of the FX unit. In our case, it will always be 31dB since the 36 bus driving resistors are permanently connected to the bus and the summing amp must always see 1/36 times the value of Rs.

Art of noise

What is this phantom plague of mix busses. Noise. Consider this scenario next time you blame an FX unit for excess noise. Figure 1c shows a way of eliminating this unfortunate noise amplifying phenomena. Turning a channel FX Send Off completely disconnects the associated bus driving resistor from the bus, so it doesn't appear as part of a parallel combination of any other bus driving resistors. Unless that particular channel is contributing to the bus, potentially noise-amplifying resistors are not connected. Furthermore, the noise needn't come from any, or all, of the sources. Noise on the ground or earth reference for the mix bus is just as likely a culprit, and contingency measures - outlined in Part 5 - must be taken to prevent ground noise ruining console performance.

This is the principle behind the AutoMate muting system and is employed on every mix bus. It's a principle which is applicable where the virtual earth mixing process is concerned. Here, gain for each signal input to mix-amp output is unity, regardless of how many individual resistors are present as a parallel combination at the virtual earth of the op-amp. It does not, extend to every mix bus in existence in every console, so if your console suffers in this aspect, it's not just

a simple matter of a few two-minute modifications.

As far as the AutoMate muting is concerned, the manual version of the Aux Mix routing system does this by disconnecting the bus driving resistors from the bus via a mechanical, level pot backstop-operated switch. Similarly, the automated versions use FETs to isolate the resistors from the bus. Because four pole single throw switches aren't generally available fitted to the backs of potentiometers (which, from a cost point of view, is probably just as well), the manual version features non-balanced mix busses.

We've discussed at some length the many diverse routing requirements of the various types of desk - monitor, recording and broadcast - and illustrated the subject with examples. The one aspect which every routing has in common has been the centralised theme of the last few months - the switch. Before we leave the subject of routing, it's probably wise to look at one final area, although, strangely, there isn't a switch in sight. This is the panoramic potentiometer, to give it its rather grandiose full title, or pan-pot, as it's better known.

The routing of a signal, using a pan-pot, comes under the general heading of Spatial Localisation Processing. Since the early pioneering days of the stereo recording, there has been the need to position signals in a sound-stage of one sort or another. There is no such requirement when recording in mono, since there is no spatial localisation information available from this format. However, with modern stereo and the so-called multi-dimensional systems the engineer is capable of placing a particular source of sound anywhere along an imaginary straight line between the two speakers.

Where a recording is made direct-to-stereo (that is, captured using a stereo pair, either coincident, M and S, XY, or whatever), the placing both of the microphones and of the musicians determines the relative level of each sound source

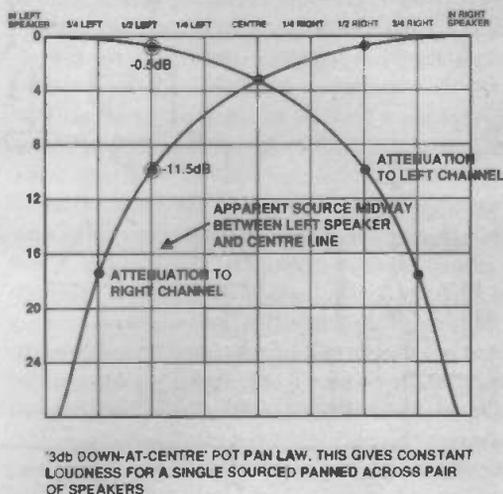


Fig.3 Constant loudness pan pot law

across the stereo image.

Two sound channels are the minimum required to achieve the stereophonic effect. This is not an accurate replica of the original sound field, as it might have been heard at the original venue, but an illusion or sensation of spatial distribution which enhances the apparent reality of the programme material. Although it might seem impossible to achieve an acceptable stereo effect with just two channels and two loudspeakers, since the ear can hear sounds coming from all

directions, our ears, using level and phase information, are deceived sufficiently by pure level distances between the left and right paths of a stereo pair into perceiving changing image position. From this, we are able to determine where within this image a particular source lies.

Stereo information is derived and captured using this technique shown in Figure 2. It is referred to as the coincident pair, or Blumlein pair, and modern examples use a pair of identical directional microphones placed as nearly as possible in the same point in space. There is minimum time-of-arrival difference at the two capsules and the whole of the directional (stereo) information relies on the controlled difference between the two mic. outputs.

In essence, this is the only genuine stereo recording, with all of the instrument placements captured on tape exactly as they were live.


Synthesising Sound Placement using Level

Intuitively, the design of a control to position an image anywhere across the stereo field might seem like a fairly trivial task. In practise, this is seldom the case. The primary reason is mono compatibility. Although mono has traditionally been associated with old recordings and out-of-date, low-technology equipment, for many listeners, mono still forms the backbone of their enjoyment of recorded music. Mono radios are still in abundance and just because a track has been mastered using state-of-the-art digital mixing desks and recorders, doesn't necessarily mean that it won't end up as part of a programme which is then broadcast on short-wave to one of the far-flung corners of the globe. Mono compatibility is of primary importance in every aspect of recording and broadcasting.

Consequently, the pan-pot must achieve a respectable stereo effect whilst leaving the mono signal untouched, or relatively untouched. Since potentiometers play an integral part in the system, it is not surprising that the curve which describes the characteristic of the pan-pot is known as the 'law'. Two basic laws are constant power and constant voltage, and they describe the way in which the control, across its travel, acts in dividing the mono input signal between the two output channels, and whether or not the sum of the two is constant across this travel.

A relationship was established between the proportion of signal level fed to two loud speakers and the apparent position of the sound source (see Figure 3). If the levels to right and left are controlled according to these curves, the power outputs from the two speakers will remain constant. In this way, a source panned from one channel to the other will not cause any apparent change in the level of loudness. This relationship equates to a sine/cosine law and, when desks were fitted with rotary stud faders et al, a double stud potentiometer (with precision resistors connected, as far as was practicable, to each of the studs), was commonly used to reproduce the desired law.

This '3dB-down-at-centre' law, as it is known, whilst causing a constant acoustic level from a pair of loudspeakers, causes some strange effects if the two identical -3dB signals are summed further down the signal chain. The resultant mono output voltage will be doubled, with the ultimate mono output from the system some 3dB higher with the pan-pot central than with it routing the signal to one side. A stereo signal summed to mono in a playback system suffers from the

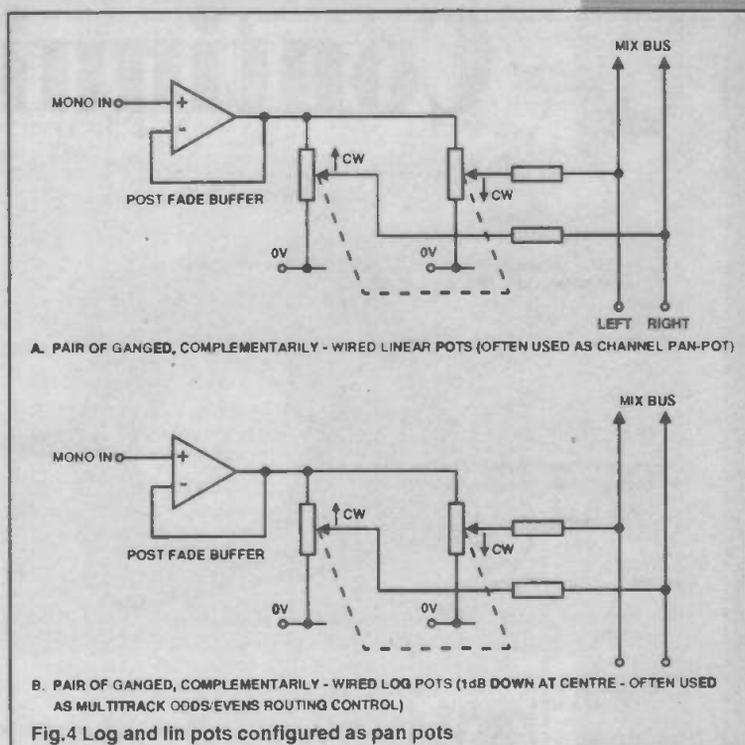


same problem. Incorporating a 6dB loss at the mid-point would correct this, at the expense of an apparent dip in level in the centre when on stereo. Somewhere between these two extremes lies a theoretical happy medium. Here, the signal will keep an even subjective level panning across the image plane. The amount of loss has been the subject of debate and controversy for many years, with proponents of the values 2, 3, 4 or 4.5 all arguing the case. Mono is most important in a broadcasting environment and here a compromise value of 4.5dB is often used.

Pots and Pans

An example of what is probably the simplest of all pan-pots is shown in Figure 4a. Here, a ganged pair of linear potentiometers have complementary connections made to their tracks, such that as the output level from one increases, that from the other decreases. This type doesn't suffer from the drawback outlined above, since re-mono-ing the signals yields an output which remains at constant amplitude, regardless of pan-pot setting. However the subjective effect is one of too much loudness at the extremes of pot travel and diminished output in the middle.

Figure 4b shows a derivation of the simple type, with the linear law pots replaced by a pair of log/anti-log types, again ganged and complementarily wired. Panning right achieves a steady decrease in the level of the left output, with the right output remaining fairly constant in level. When the control is central, both outputs are attenuated only slightly with respect to original mono input. Subjectively, the image seems louder in the middle than it does at the extremes of settings, which is the opposite of the effect when linear pots are used. This kind of circuit is often implemented as a multitrack routing pan-pot, or as an offset control. Tracking between both halves of the pot is often not too good - certainly not as good as with a linear pot - because it is much harder both to manufacture the log law to accurate tolerances and to retain relatively low cost.

Continuity Tester

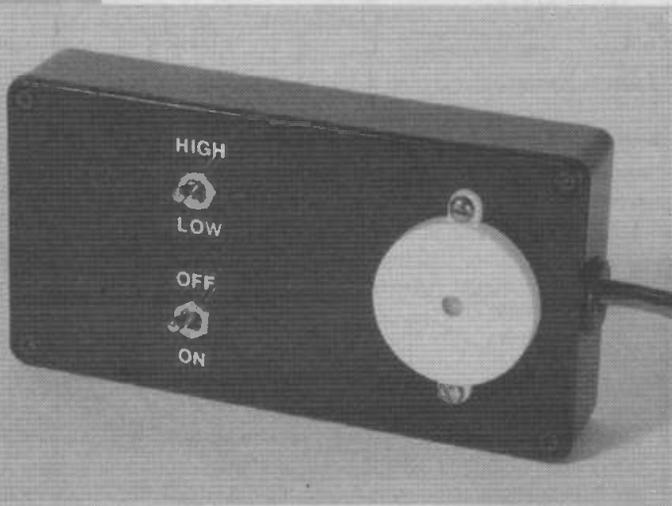

A piece of test gear that no experimenter should be without. A design by Robert Penfold

is used here as a voltage comparator. If the non-inverting (+) input is at a higher voltage than the inverting (-) input, the output will go high. If the inverting input is at the higher voltage, the output will go low. The output of the comparator controls a gated audio oscillator which drives a small loud-speaker. Strictly speaking, the oscillator is a complement gated type and it is therefore switched on when the control signal is low, and switched off when a high control level is received.

R2 and R3 form a potential divider across the supply rails. Their function is to provide a reference voltage to the inverting input of the comparator. R1 takes the non-inverting input to the full supply voltage under standby conditions, which in turn sends the output of the comparator high. Thus the audio oscillator is gated off under standby conditions.

Connecting a true short circuit across the test prods results in the non-inverting input being taken to 0V and it is then at a lower potential than the inverting input. This results in the comparator's output going low and the audio oscillator being activated. Of course, it is not essential to have zero

There are two common problems with continuity tester designs. One is simply that many testers indicate continuity when there is actually a significant resistance across the test prods. What is supposedly continuity can sometimes be resistances of up to a few hundred ohms. Also, many designs are 'fooled' by diode junctions. Such junctions are not just present in diodes, but also exist in transistors and integrated circuits. In fact modern circuits are liberally scattered with hidden semiconductor junctions that will give misleading results with any continuity tester that is not designed to ignore them.

The second problem is that of high currents flowing through the test circuit. Most continuity testers consist of an audio oscillator driving a loudspeaker, with the test prods connected in series with the battery supply. The full supply current of the continuity checker therefore flows through the test circuit. This is fine if the circuit is designed to consume no more than a few milliamps, but could cause damage to delicate integrated circuits if currents of 50mA or more are allowed to flow.

The continuity tester featured here avoids both problems. It has two sensitivities, one which requires a test resistance of less than 10 ohms before the audio tone is activated, and one which requires a test resistance of just a fraction of an ohm. This second mode is useful when testing circuits which contain very low value resistors and (or) small inductors which exhibit low resistances. When set to either sensitivity, diode junctions will not 'fool' the unit into producing false indications of continuity. The current flow through the circuit under test is a mere 4mA or so, which is too low to damage any normal components.

System Operation

This continuity tester uses the basic arrangement shown in the block diagram of Figure 1. The operational amplifier

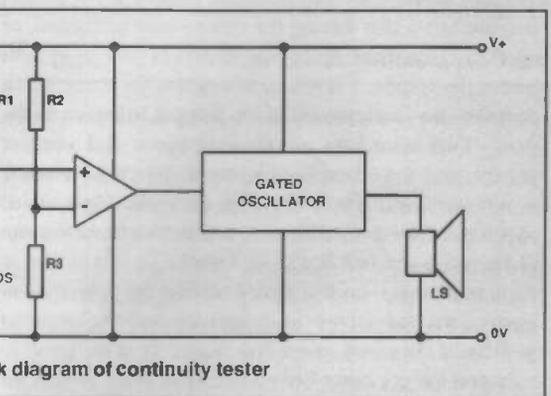


Fig. 1 Block diagram of continuity tester

resistance across the test prods in order to activate the unit. The resistance here merely has to be low enough to take the potential at the non-inverting input below that at the inverting input. Just what constitutes a low enough resistance to achieve this depends on the values of R1 to R3.

Unlike many continuity testers, this one does consume power when the test prods are open circuit, so on/off switch SW2 is therefore needed. Under standby conditions, the circuit has a current consumption of only about 3mA, but the consumption rises to about 8mA when the unit is activated. A PP3 size battery is adequate as the power source.

Construction

The component overlay for the printed circuit board, plus the small amount of hard wiring, is shown in Figure 3. Both

ETI
Cover PCB
Project

PROJECT

the integrated circuits are MOS types and, accordingly, they require the normal anti-static procedures to be observed. The most important of these is to use holders for the two integrated circuits. They should only be fitted into their holders once the unit has been completed in all other respects. Both devices should be left in the anti-static packaging until then.

In other respects, construction of the board is extremely simple. Single-sided solder pins are fitted to the board at the points where connections will eventually be made to off-board components such as LS1 and SW1. The tops of the pins should be tinned with a generous amount of solder. Unusually for modern components, some solder pins seem to be reluctant to take a proper coating of solder. If this should occur, clean the pins by scraping them with the blade of a penknife, prior to tinning them.

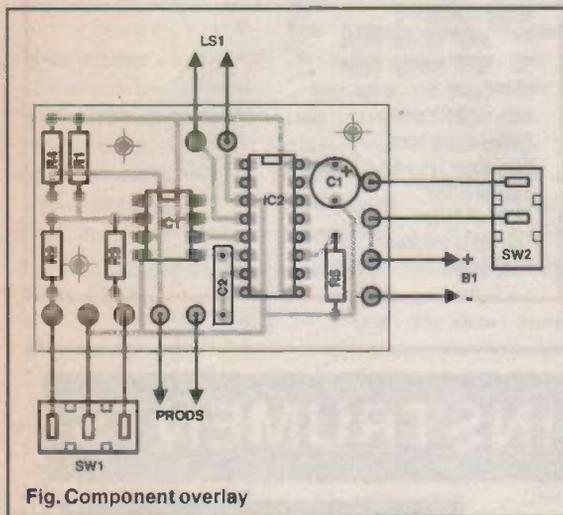


Fig. Component overlay

The case for the prototype is a small plastic box, which has approximate outside dimensions of 110 x 56 x 20mm. It is unlikely that the unit could be fitted into a case which is significantly smaller than this in any dimension. The printed circuit board is mounted on the rear panel, well towards one end of the case, using 6BA or metric M3 fixings. The battery fits into the space at the opposite end of the case, leaving room for SW1 and SW2 in the middle section of the case. The switches are mounted on the front panel/lid of the case.

LS1 must be a cased ceramic resonator which is intended for screw fixing to a case (not an uncased element or a cased type intended for printed circuit mounting). Most require two small (M2 or 8BA) fixing screws. A third small hole is needed in the case to accommodate the resonator's two flying leads. LS1 is mounted towards the right hand end of the front panel, in front of the circuit board. The resonator itself can be used as a template when marking the positions of these three holes. Note that LS1 must be a ceramic resonator and that this circuit can not drive a moving coil loudspeaker. The test prods could be connected to the circuit board via a pair of plugs and sockets, but it is advisable to use direct connection to the circuit board. This ensures that the prods will be in really good electrical contact with the circuit board, which is essential if the unit is to operate properly in the low resistance mode. An entrance hole for the test leads is drilled in the centre of the right hand end panel of the case.

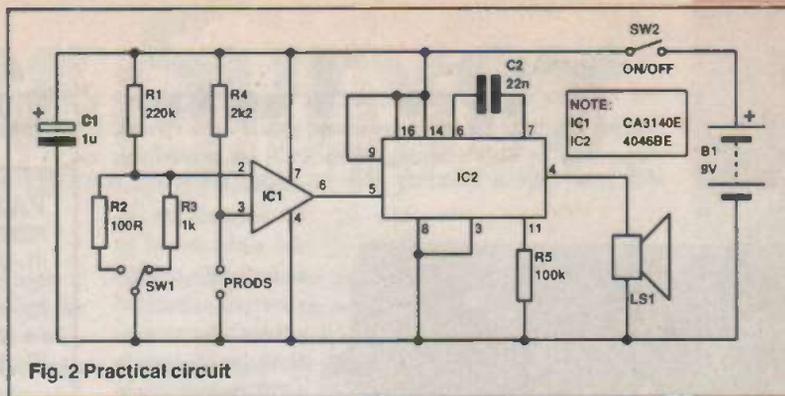


Fig. 2 Practical circuit

HOW IT WORKS

In the practical continuity tester circuit of Fig.2, IC1 is the comparator. The reference voltage to the inverting input of IC1 is provided by R1 and either R2 or R3, depending on the setting of SW1. For the moment, assume that R3 has been selected, which places the unit in its high resistance mode. This gives a reference voltage that is only about 1/220th of the supply voltage, approximately 40mV. R4 biases the non-inverting input to the positive supply rail and the important point to note here is that its value is only 1/100th of R1's value. Therefore, the resistance across the test prods must be 1/100th the value of R3 (10 ohms) in order to balance the input voltages to IC1. The resistance across the prods must be fractionally lower than this in order to activate the audio oscillator.

For general purpose testing, this gives good results. Few circuits contain many resistances that are below 10 ohms, so there should be few false alarms. On the other hand, if dirty printed circuit tracks, or something of this nature, should produce some less than perfect electrical contacts with the test prods, this should not be sufficient to prevent the device from being activated properly. Silicon diode junctions will not produce misleading results either. Less than about 40mV must be present across the test prods in order to activate the alarm. The voltage drop across a silicon diode is over ten times this figure. There is no danger of the unit producing high currents which would damage the circuit under test. R4 limits the current flowing through the test prods to a safe level of about 4mA.

The circuit operates in much the same way in the low resistance mode. SW1 is then set to select R2. This reduces the reference voltage at the inverting input by a factor of around ten times, since R2 has a resistance which is only 1/10th of R3's resistance. The main practical consequence of this is that the resistance across the test prods must now be less than 1 ohm (i.e. 1/100th of R2's value) in order to activate the tone generator. If desired, the value of R2 could be made lower, in order to make the maximum acceptable test resistance lower as well.

In practice, it is probably best not to use a value of much less than 100R. Firstly, bear in mind that there will be a certain amount of resistance through the test leads. If the unit is made too discriminating, this could be sufficient to prevent it from operating properly. Also, bear in mind that it might sometimes be difficult to get really good electrical contacts between the test prods and the printed circuit tracks, etc., in the test circuit. Even with R2 at 100R, bad contacts could easily result in misleading results unless adequate care is exercised when using the unit. The audio oscillator is a simple voltage controlled oscillator (VCO) based on IC2, a CMOS 4046BE. In this case it is used at a fixed frequency with the control input at pin 9 simply wired to the positive supply rail. The operating frequency is around 700Hz, which is too low to give peak efficiency from LS1. This component is a cased ceramic resonator. In this application a tone of moderate volume is all that is required and it would be undesirable to use a higher frequency that would give a powerful tone from LS1.

Complete the unit by adding the small amount of point-to-point wiring. This is very straightforward and should present no difficulties. Although most ceramic resonators have one red lead and one black lead, LS1 can in fact be connected either way round.

Testing And Use

With the unit switched on and the two test prods connected together, the audio generator should be activated, regardless of SW1's setting. With SW1 set to the high



resistance mode (i.e. R3 selected), the audio alarm should be activated if a 4R7 resistor is connected across the prods. However, changing to a 22R resistor should not give a response from the unit. With the tester set to the low resistance mode (i.e. R2 selected), connecting the 4R7 or 22R test resistors across the test prods should fail to activate the audio tone generator. Using a 0R47

resistor should result in the tone generator being activated.

In normal use it is probably best to use the high resistance mode. The unit is not easily 'fooled' when in this mode, and something less than really good connections to the test circuit will give satisfactory results. The low resistance mode is better when the circuit under test is known to contain a lot of

low value resistors, small inductors, RF transformers, etc.. However, when using this mode it is essential to ensure that the test prods make good contact with the test circuit.

PARTS LIST

RESISTORS (0.25W carbon film)

R1 220k
R2 100
R3 1k
R4 2k2
R5 100k

CAPACITORS

C1 1 μ 63V radial elect
C2 22n polyester

SEMICONDUCTORS

IC1 CA3140E
IC2 4046BE

MISCELLANEOUS

S1 SPDT sub-min toggle
S2 SPST sub-min toggle
LS1 Cased ceramic resonator
B1 9V (PP3 size)
Printed circuit board
Case about 111 ∞ 57 ∞ 22mm
8 pin dil holder
14 pin dil holder
Test prods and leads
Wire, solder

TEST and MEASURING INSTRUMENTS



Multimeters

183, 3.5 digit LCD; DC V, AC V, DC A, AC A, Res. Cont. Hold, Basic acc. 0.5% £39.50

185, 3.5 digit as 183 plus Bar graph, Temp. Freq. Max/Min, Edit Basic Acc. 0.3% £74.50

187, As 185 but Auto Range £99.50

285, As 185 plus 4.5 digit True, RMs £109.50

Oscilloscopes

CO 1305, DC to 5MHz Single channel £169.00

CS 4025, 20MHz Dual trace full featured £330.00

CS 5170, 100MHz Dual, Cursor readout £1159.00

CS 6040 150MHz, 4 Chan. Full Featured £2049.00



SP-1000 £299.00

Eprom Programmer/Emulator

Stand alone or PC hosted.
Fast programming/downloading.
Manufacture specified algorithms.
Large device support.
Easy to drive.

SP-1000 Programmer/Emulator £299.00
4M Bit option £149.00
PC Software package £29.00

Counters, Generators Oscilloscopes, Power Supplies, Multimeters, Clamp Meters, L.C.R. Meters
Programmers/Emulators, Multi-Instrument, Video and Audio Test, Probes and Accessories.

For further information
please contact:

SAJE
ELECTRONICS

SAJE Electronics
117 Lovell Road, Cambridge, CB4 2QW
Tel: (0223) 425440 Fax: (0223) 424711

Reader Survey

It's survey time again and your chance to win one of 40 prizes supplied by Maplin Electronics.

Although some of the questions here may not seem to relate directly to the magazine, please complete the whole questionnaire. Your answers not only help us to steer the editorial content of the magazine in the direction you want but they also help us to build up an overall profile of readers to present to advertisers who require such data to select

suitable magazines for their products.

No names and addresses will be disclosed to any third party and all information will be treated in the strictest confidence.

As an incentive for your hard work, all entries received by 11th October will be entered in the draw for the 40 prizes given by Maplin Electronics.

1. If you could make one improvement to ETI, what would it be?

2. Please indicate what you think of the following aspects of ETI's coverage:

	Poor	Average	Good	Excellent
Product News	<input type="checkbox"/> 001	<input type="checkbox"/> 002	<input type="checkbox"/> 003	<input type="checkbox"/> 004
Industry Technology News	<input type="checkbox"/> 005	<input type="checkbox"/> 006	<input type="checkbox"/> 007	<input type="checkbox"/> 008
Advanced Projects	<input type="checkbox"/> 009	<input type="checkbox"/> 010	<input type="checkbox"/> 011	<input type="checkbox"/> 012
Basic Projects	<input type="checkbox"/> 013	<input type="checkbox"/> 014	<input type="checkbox"/> 015	<input type="checkbox"/> 016
General Features	<input type="checkbox"/> 017	<input type="checkbox"/> 018	<input type="checkbox"/> 019	<input type="checkbox"/> 020
Tutorial Features	<input type="checkbox"/> 021	<input type="checkbox"/> 022	<input type="checkbox"/> 023	<input type="checkbox"/> 024
Product Reviews	<input type="checkbox"/> 025	<input type="checkbox"/> 026	<input type="checkbox"/> 027	<input type="checkbox"/> 028

3. Would you like to see a greater or lesser proportion of ETI devoted to the following:

	Less	The same	More
Beginners' Projects	<input type="checkbox"/> 029	<input type="checkbox"/> 030	<input type="checkbox"/> 031
Advanced Projects	<input type="checkbox"/> 032	<input type="checkbox"/> 033	<input type="checkbox"/> 034
Computer Projects	<input type="checkbox"/> 035	<input type="checkbox"/> 036	<input type="checkbox"/> 037
Audio Projects	<input type="checkbox"/> 038	<input type="checkbox"/> 039	<input type="checkbox"/> 040
Music Projects	<input type="checkbox"/> 041	<input type="checkbox"/> 042	<input type="checkbox"/> 043
Radio Projects	<input type="checkbox"/> 044	<input type="checkbox"/> 045	<input type="checkbox"/> 046
Home Improvement Projects	<input type="checkbox"/> 047	<input type="checkbox"/> 048	<input type="checkbox"/> 049
Bio-electronics/Health Projects	<input type="checkbox"/> 050	<input type="checkbox"/> 051	<input type="checkbox"/> 052
Test Equipment Projects	<input type="checkbox"/> 053	<input type="checkbox"/> 054	<input type="checkbox"/> 055
Security/Alarm Projects	<input type="checkbox"/> 056	<input type="checkbox"/> 057	<input type="checkbox"/> 058
Car Electronics Projects	<input type="checkbox"/> 059	<input type="checkbox"/> 060	<input type="checkbox"/> 061
Robotics Projects	<input type="checkbox"/> 062	<input type="checkbox"/> 063	<input type="checkbox"/> 064
Photographics	<input type="checkbox"/> 065	<input type="checkbox"/> 066	<input type="checkbox"/> 067
Novelty/Gimmick Projects	<input type="checkbox"/> 068	<input type="checkbox"/> 069	<input type="checkbox"/> 070
Basic Elementary Theory	<input type="checkbox"/> 071	<input type="checkbox"/> 072	<input type="checkbox"/> 073
Advanced Electronic Theory	<input type="checkbox"/> 074	<input type="checkbox"/> 075	<input type="checkbox"/> 076
General Science/Technology	<input type="checkbox"/> 077	<input type="checkbox"/> 078	<input type="checkbox"/> 079
News	<input type="checkbox"/> 080	<input type="checkbox"/> 081	<input type="checkbox"/> 082
Product Reviews	<input type="checkbox"/> 083	<input type="checkbox"/> 084	<input type="checkbox"/> 085
Letters	<input type="checkbox"/> 086	<input type="checkbox"/> 087	<input type="checkbox"/> 088
Open Channel/etc	<input type="checkbox"/> 089	<input type="checkbox"/> 090	<input type="checkbox"/> 091
Design/Circuit ideas	<input type="checkbox"/> 092	<input type="checkbox"/> 093	<input type="checkbox"/> 094
Competitions	<input type="checkbox"/> 095	<input type="checkbox"/> 096	<input type="checkbox"/> 097
Others (please specify)	<input type="checkbox"/> 098	<input type="checkbox"/> 099	<input type="checkbox"/> 100

4. Indicate which of the following equipment you use:

	Own	Don't own but regularly use
Home Computer	<input type="checkbox"/> 101	<input type="checkbox"/> 102
Professional Computer	<input type="checkbox"/> 103	<input type="checkbox"/> 104
Hi-fi	<input type="checkbox"/> 105	<input type="checkbox"/> 106
Electronic Musical Instrument	<input type="checkbox"/> 107	<input type="checkbox"/> 108
MIDI Equipment	<input type="checkbox"/> 109	<input type="checkbox"/> 110
PA/Recording equipment	<input type="checkbox"/> 111	<input type="checkbox"/> 112

Photographic/Darkroom Equipment	<input type="checkbox"/> 113	<input type="checkbox"/> 114
Ham Radio/CB	<input type="checkbox"/> 115	<input type="checkbox"/> 116
Satellite TV	<input type="checkbox"/> 117	<input type="checkbox"/> 118
Video Camera	<input type="checkbox"/> 119	<input type="checkbox"/> 120
Security/Alarm System	<input type="checkbox"/> 121	<input type="checkbox"/> 122
Oscilloscope	<input type="checkbox"/> 123	<input type="checkbox"/> 124
Multimeter	<input type="checkbox"/> 125	<input type="checkbox"/> 126
Other test gear	<input type="checkbox"/> 127	<input type="checkbox"/> 128

5. Do you buy ETI for:

Projects only	Features only	Both
<input type="checkbox"/> 501	<input type="checkbox"/> 502	<input type="checkbox"/> 503

6. Do you read any of the following magazines:

	Never	Occasionally	Regularly
Everyday with Practical Electronics	<input type="checkbox"/> 129	<input type="checkbox"/> 130	<input type="checkbox"/> 131
Elektor Electronics	<input type="checkbox"/> 132	<input type="checkbox"/> 133	<input type="checkbox"/> 134
Maplin Magazines	<input type="checkbox"/> 135	<input type="checkbox"/> 136	<input type="checkbox"/> 137
Electronics & Wireless World	<input type="checkbox"/> 138	<input type="checkbox"/> 139	<input type="checkbox"/> 140
Music Technology	<input type="checkbox"/> 141	<input type="checkbox"/> 142	<input type="checkbox"/> 143
Home & Studio Recording	<input type="checkbox"/> 144	<input type="checkbox"/> 145	<input type="checkbox"/> 146
Hi-fi News & Record Review	<input type="checkbox"/> 147	<input type="checkbox"/> 148	<input type="checkbox"/> 149
New Scientist	<input type="checkbox"/> 150	<input type="checkbox"/> 151	<input type="checkbox"/> 152
Scientific American	<input type="checkbox"/> 153	<input type="checkbox"/> 154	<input type="checkbox"/> 155
Practical Wireless	<input type="checkbox"/> 156	<input type="checkbox"/> 157	<input type="checkbox"/> 158
Ham Radio Today	<input type="checkbox"/> 159	<input type="checkbox"/> 160	<input type="checkbox"/> 161
Electronics Product News/ Electronics Equipment			
News/New Electronics/ Electronic Product Review	<input type="checkbox"/> 162	<input type="checkbox"/> 163	<input type="checkbox"/> 164

7. If read, please indicate what you think of the following magazines.

	Not as good as ETI	As good as ETI	Better than ETI
Elektor Electronics	<input type="checkbox"/> 165	<input type="checkbox"/> 166	<input type="checkbox"/> 167
Everyday with Practical Electronics	<input type="checkbox"/> 168	<input type="checkbox"/> 169	<input type="checkbox"/> 170
Maplin Magazine	<input type="checkbox"/> 171	<input type="checkbox"/> 172	<input type="checkbox"/> 173

8. Which of the following do you buy and how frequently?

	Never	Sometimes	Regularly
Electronic Components	<input type="checkbox"/> 174	<input type="checkbox"/> 175	<input type="checkbox"/> 176
Complete Electronic Kits	<input type="checkbox"/> 177	<input type="checkbox"/> 178	<input type="checkbox"/> 179
ETI PCBs	<input type="checkbox"/> 180	<input type="checkbox"/> 181	<input type="checkbox"/> 182
Stripboard/Wirewrap Etc	<input type="checkbox"/> 183	<input type="checkbox"/> 184	<input type="checkbox"/> 185
Cases/Case Materials	<input type="checkbox"/> 186	<input type="checkbox"/> 187	<input type="checkbox"/> 188
Tools	<input type="checkbox"/> 189	<input type="checkbox"/> 190	<input type="checkbox"/> 191
PCB making Equipment/Materials	<input type="checkbox"/> 192	<input type="checkbox"/> 193	<input type="checkbox"/> 194
Pre-programmed ROMs	<input type="checkbox"/> 195	<input type="checkbox"/> 196	<input type="checkbox"/> 197
Computer Software	<input type="checkbox"/> 198	<input type="checkbox"/> 199	<input type="checkbox"/> 200

- Floppy Disks 201 202 203
 Electronic Books 204 205 206
 Data Books 207 208 209
 Second Hand Equipment 210 211 212

9. Please indicate what you think of the services offered:

- | | Poor | Average | Good |
|-------------------|------------------------------|------------------------------|------------------------------|
| PCB Service | <input type="checkbox"/> 213 | <input type="checkbox"/> 214 | <input type="checkbox"/> 215 |
| Photocopy Service | <input type="checkbox"/> 216 | <input type="checkbox"/> 217 | <input type="checkbox"/> 218 |
| Foil Patterns | <input type="checkbox"/> 219 | <input type="checkbox"/> 220 | <input type="checkbox"/> 221 |
| Buylines | <input type="checkbox"/> 222 | <input type="checkbox"/> 223 | <input type="checkbox"/> 224 |
| Subscriptions | <input type="checkbox"/> 225 | <input type="checkbox"/> 226 | <input type="checkbox"/> 237 |
| Back numbers | <input type="checkbox"/> 228 | <input type="checkbox"/> 229 | <input type="checkbox"/> 230 |

10. Have you used:

- | | Yes | No |
|-------------------|------------------------------|------------------------------|
| Our PCB service | <input type="checkbox"/> 231 | <input type="checkbox"/> 232 |
| Photocopy service | <input type="checkbox"/> 233 | <input type="checkbox"/> 234 |

11. If you own or regularly use a computer, please indicate which it is:

- Spectrum 235
 BBC Micro/Master/Electron 236
 Commodore 64/128 237
 Amstrad CPC 238
 Amstrad PCW 239
 IBM PC Compatible 240
 Atari ST 241
 Amiga 242
 Archimedes 243
 Apple Mac 244
 Other (please specify) 245

12. How many ETI projects have you built in the past 12 months?

- None 246
 1-3 247
 4-6 248
 7-12 249
 More than 12 250

13. Do you find ETI projects

- | | Yes | No |
|----------------------------|------------------------------|------------------------------|
| Reliable | <input type="checkbox"/> 251 | <input type="checkbox"/> 252 |
| Easy to build | <input type="checkbox"/> 253 | <input type="checkbox"/> 254 |
| Useful | <input type="checkbox"/> 255 | <input type="checkbox"/> 256 |
| Instructive | <input type="checkbox"/> 257 | <input type="checkbox"/> 258 |
| Technically understandable | <input type="checkbox"/> 259 | <input type="checkbox"/> 260 |
| Work first time | <input type="checkbox"/> 261 | <input type="checkbox"/> 262 |

14. Do you modify ETI project designs?

- Not At All 263
 A Few Mods 264
 Many Mods 265

15. Do you prefer to build ETI projects from complete kits when they are available?

- Yes 266 No 267

16. Do you make your own PCBs?

- Never 268
 Sometimes 269
 Always 270

17. Have you used our cover PCB to construct a project?

- Once 271 Sometimes 272
 Always 273 Never 274

18. What type of projects would you like to see using our cover PCB?

-

19. Do you primarily build electronics projects

- To save money on commercial goods 275
 As a satisfying pastime 276
 As an instructional exercise 277

20. As far as electronics design and construction is concerned, do you consider yourself:

- Novice 278
 Proficient 279
 Accomplished 280
 Expert 281

21. Estimate the value of your electronics test gear and construction equipment as new:

- Under £25 282
 £25-£100 283
 £101-200 284
 £201-£500 285
 £501-£1000 286
 £1000-£2000 287
 £2000-£4000 288
 over £4000 289

22. How much do you estimate you have spent on equipment and components during the past 12 months?

- Nothing 290
 Under £25 291
 £25-£50 292
 £51-100 293
 £101-£200 294
 £201-£500 295
 £501-£1000 296
 over £1000 297

23. Are you responsible for recommending/specifying electronic equipment in your job?

- Yes 298 No 299

24. How long do you keep your copies of ETI for:

- Less than one month 300
 One month 301
 Three months 302
 Six months 303
 A year or more 304

25. If kept, how often do you refer back to issues of ETI?

- Once a week or more 305
 About once a month 306
 Once every three months 307
 Less often 308
 Never 309

26. How long do you spend reading your copy of ETI?

- Over 2 hours 310
 1½-2 hours 311
 1-1½ hours 312
 ½-1 hour 313
 Less than ½ hour 314

27. How long have you been an ETI reader?

- Less than three months 315
 3-6 months 316
 7-12 months 317
 1-2 years 318
 2-5 years 319
 Over 5 years 320

28. How often do you buy ETI?

- Occasional issues 321
 Most issues 322
 Every issue 323

29. How much of ETI do you read?

- Read only some articles 324

- Read most articles 325
 Read all articles 326
30. With regard to the advertisers in ETI do you?
- Read or look through most or nearly all the ads 327
 Read or look through some of the ads 328
 Just read or look through the occasional ad 329
 Very rarely/never look at the ads 330

31. Thinking specifically about the advertising content, would you please rate the two main types of advertisement:

- | | Display | Classifieds |
|-----------------|------------------------------|------------------------------|
| Very useful | <input type="checkbox"/> 331 | <input type="checkbox"/> 332 |
| Useful | <input type="checkbox"/> 333 | <input type="checkbox"/> 334 |
| Not very useful | <input type="checkbox"/> 335 | <input type="checkbox"/> 336 |

32. Which of the following would you most like to see featured with the magazine? (one box only).

- Cover mounted gifts 337
 Additional supplements 338
 Competitions 339
 Money saving offers 340
 Other (please specify) 341

33. Does anyone else read your copy of ETI?

- No only myself 342
 One or two other people 343
 Three or four other people 344
 More than four other people 345

34. If your copy of ETI is read by other people, please give details of their age and sex:

- | | Person 1 | Person 2 | Person 3 |
|-------------|------------------------------|------------------------------|------------------------------|
| Age: | | | |
| 9-14 yrs | <input type="checkbox"/> 346 | <input type="checkbox"/> 347 | <input type="checkbox"/> 348 |
| 15-24 yrs | <input type="checkbox"/> 349 | <input type="checkbox"/> 350 | <input type="checkbox"/> 351 |
| 25-34 yrs | <input type="checkbox"/> 352 | <input type="checkbox"/> 353 | <input type="checkbox"/> 354 |
| 35-44 yrs | <input type="checkbox"/> 355 | <input type="checkbox"/> 356 | <input type="checkbox"/> 357 |
| 45-54 yrs | <input type="checkbox"/> 358 | <input type="checkbox"/> 359 | <input type="checkbox"/> 360 |
| 55-64 yrs | <input type="checkbox"/> 361 | <input type="checkbox"/> 362 | <input type="checkbox"/> 363 |
| Over 64 yrs | <input type="checkbox"/> 364 | <input type="checkbox"/> 365 | <input type="checkbox"/> 366 |
| Sex: | | | |
| Male | <input type="checkbox"/> 367 | <input type="checkbox"/> 368 | <input type="checkbox"/> 369 |
| Female | <input type="checkbox"/> 370 | <input type="checkbox"/> 371 | <input type="checkbox"/> 372 |

35. Are you aware of the scheduled publication date of ETI?

- Yes 373 No 374

36. If the answer to the last question is YES, do you normally attempt to purchase the magazine on that day?

- Yes 375 No 376

37. How do you normally obtain your copy?

- Chance purchase 377
 Newsagent shop collection 378
 Newsagent home delivery 379
 Subscription by post 380
 Passed on copy 381

38. If you are a subscriber, on which date did you receive this issue?

/ /

39. If you are a subscriber, how long have you subscribed to this magazine?

- 1-6 months 382
 7-12 months 383
 1-2 years 384
 3-5 years 385
 6-10 years 386
 Over 10 years 387

40. Are you aware that to subscribe to this magazine in the UK costs the same as purchasing it in a shop?

- Yes 388 No 389

41. Would you like to receive details of our latest subscription offer?

- Yes 390 No 391

42. If you do not subscribe, from which type of newsagent do you most often obtain your copy?

- High Street Shop 392
 Estate shop 393
 Corner shop 394
 Other (please specify) 395

43. Please tick any hobby/interests you may have besides Electronics:

- Model Railways: 396
 Model Engineering: 397
 Model Cars: 398
 Model Boats: 399
 Model Aircraft: 400
 Steam Locomotives: 401
 Radio/CB: 402
 Computers: 403
 Woodworking: 404
 Handcrafts: 405

44. Please tick the box which represents the annual total of your gross income:

- Under £6,500 406
 £6,501-£8,000 407
 £8,001-£10,000 408
 £10,001-£12,500 409
 £12,501-£15,000 410
 £15,001-£19,000 411
 £19,001-£25,000 412
 Over £25,000 413

45. What is your age?

- Under 15 yrs 414
 15-18 yrs 415
 19-21 yrs 416
 22-24 yrs 417
 25-34 yrs 418
 35-44 yrs 419
 45-54 yrs 420
 55-64 yrs 421
 Over 64 yrs 422

46. Which of the following newspapers do you read?

- The Times 423
 The Daily Telegraph 424
 The Financial Times 425
 The Guardian 426
 The Independent 427
 The Daily Express 428
 The Daily Mail 429
 The Daily Mirror 430
 The Sun 431
 Today 432
 None of the above 433

47. Which of the following Sunday newspapers do you read?

- The Sunday Times 434
 The Observer 435
 The Sunday Telegraph 436
 The Sunday Express 437
 The Mail on Sunday 438
 The Sunday Mirror 439
 The People 440
 The News of The World 441

News on Sunday 442
 Today 443
 None of the above 444

48. What is your marital status?
 Married 445
 Single 446
 Divorced 447

49. Sex:
 Male 448
 Female 449

50. Are you a member of a book club?
 Yes 450
 No 451

51. Are you a member of a record club?
 Yes 452
 No 453

52. Are you:
 In full time employment 454
 In part time employment 455
 Not employed at present 456
 Retired 457
 Student - full-time 458
 Student - part-time 459

53. If in full-time employment, please state your occupation:

54. If a student what subjects do you study?

55. If you have children, please indicate their age given in the ranges:

	First	Second	Third	Fourth
Age: 1-3 yrs	<input type="checkbox"/> 460	<input type="checkbox"/> 461	<input type="checkbox"/> 462	<input type="checkbox"/> 463
4-8 yrs	<input type="checkbox"/> 464	<input type="checkbox"/> 465	<input type="checkbox"/> 466	<input type="checkbox"/> 467
9-12 yrs	<input type="checkbox"/> 468	<input type="checkbox"/> 469	<input type="checkbox"/> 470	<input type="checkbox"/> 471
13-16 yrs	<input type="checkbox"/> 472	<input type="checkbox"/> 473	<input type="checkbox"/> 474	<input type="checkbox"/> 475
Over 16 yrs	<input type="checkbox"/> 476	<input type="checkbox"/> 477	<input type="checkbox"/> 478	<input type="checkbox"/> 479
Male	<input type="checkbox"/> 480	<input type="checkbox"/> 481	<input type="checkbox"/> 482	<input type="checkbox"/> 483
Female	<input type="checkbox"/> 484	<input type="checkbox"/> 485	<input type="checkbox"/> 486	<input type="checkbox"/> 487

Thank you for completing the ETI readers' survey. To qualify for entry in the free draw for one of 40 prizes from Maplin Electronics you must fill in your name and address below, pull out the centre pages, fold as shown and post to arrive not later than 11th October 1993

Name

Address

..... Postcode

To post, fold on the dotted line A. Fold again at B and C and tuck B into the flap formed by C.

A

Postage will be paid by licensee

Do not affix Postage Stamps if posted in Great Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
 Licence No. HM37

ETI
 Reader Survey,
 Argus Specialist Publications,
 Argus House, Boundary Way,
 Hemel Hempstead
 Herts HP2 4BR

2

C

B

Sega Switchbox

An easy to construct switcher for the kids, by David Silvester.

Father Christmas was rather generous to my sons last year, as we acquired a Sega Megadrive games system - along, I suspect, with a rather large proportion families. For most games, the joypads supplied with the unit are fine but for those of us who find that after a while you get thumb ache, or when playing flight simulator games, a joystick or touch sensitive joypad is better. Fine you say, just plug in the one you want, which is all very well, but in a short time the sockets will wear and you will get problems.

However, all is not lost. Luckily, the Sega system appears to use a standard 9 pin D connector for the joypads. The answer is to use a switchboard to select the joypad or joystick as required. The problem is that no-one makes one. Centronics parallel and 25 way RS232 switchboxes, yes, but 9 pin D type connectors - no way, well not at a sensible price anyway. At this point I started to consider whether such a simple item really constituted a project, but it was my wife who said "If you can't buy it, then it will be of interest". In addition, the switchbox suggested here is suitable for use with a standard 9 pin RS232 output as found on most IBM compatible personal computers.

Construction

Unlike most of the projects in ETI, there is no How it Works section, as the use of a 10 way change-over switch to change over 9 signal lines is just too simple. With the D connectors, the outside pair must be of the same type (either male or female), while the centre one is of the opposite type.

Initially open the case and check that the PCB will fit on the small support studs. The PCB is a tight fit, it will nearly touch both the front and back aluminium panels in the box and it is easier to check at an early stage. If there is a problem, the PCB will need to be filed until it fits, but be careful not to damage any of the tracks. Next, check the position of the six small supports and mark the PCB where the mounting holes have to go, then drill the holes. There are six screws supplied with the box that fit the supports.

Figure 1 shows the PCB layout. To save cost, the PCB is single sided and uses link wires on the component side for the other connections. Fit the bracket to the switch and add the push button. Following Figure 1, mount the switch, the 9 pin D connectors (remember - outside pair the same type) and the link wires.

The box chosen is symmetrical top and bottom except that the bottom has holes for the securing screws. Take the top of the box and insert the front and rear panels back to front, i.e. with the surface that does not have the protective coating on the outside. Then leave it upside down. Fit the completed PCB into the box bottom. Since the two box halves are the

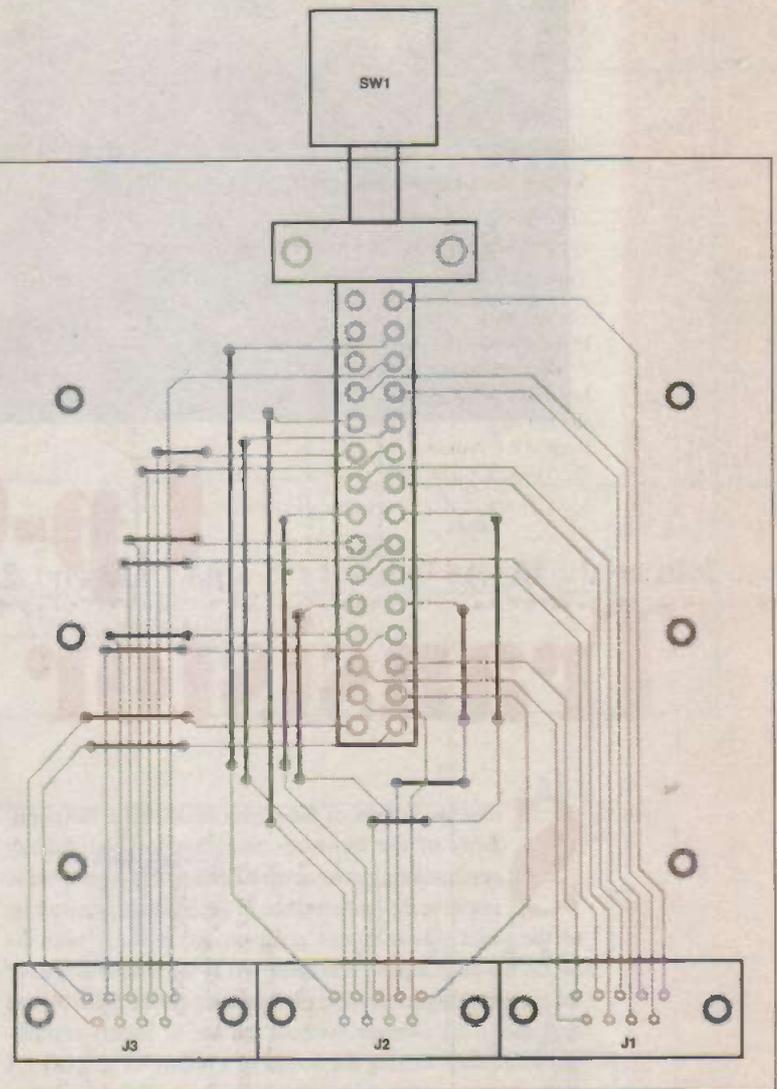


Fig.1 Component overlay

same size, by placing the top and bottom together on a flat surface it is easy to mark the front and rear panels where the switch button and D connector holes should go. Drill a small hole then use an abrafile or a holesaw to cut out the correct size holes. Remove the PCB from the lower box section, place the holes cut out over the switch and the D connectors and, if all is well, then the PCB can be refitted into the lower box half with the panels fitting into their slots. It may be necessary to ease open some of the holes with a file to make everything fit correctly. Lastly, mark the position of the mounting screw holes for the D connectors, dismantle, drill the holes and reassemble with filing screws.

Conclusions

I think you will agree that the box is a simple but useful connecting box and it was certainly worth the effort in our case. I hope you think so too!

PARTS LIST

10 pole switch	Cirkit Code 53-77010
Switch bracket	Cirkit Code 53-75100
Switch button	Cirkit Code 53-11509
ABS Case	Cirkit Code 21-15992
D female	Cirkit Code 10-62247,
D male	Cirkit Code 10-62248
Screws for D connectors	

BUYLINES

When ordering the D connectors you will need two of one type and one of another. Since they are low cost items it is possibly easier to buy two of each rather than find you have made a mistake when the parts arrive. The saving in postal charges makes it worthwhile.



Up-Grading a Transistor Amplifier

by L. Boullart

Since the advent of the power MOSFETs, the popularity of the transistor amplifier for high-fidelity applications has somewhat declined. Is it possible to improve the performance of the bipolar transistor up to the point where it can compete successfully with its MOSFET counterpart? Not quite, but as the specifications of the present design show, the performance can be lifted a good deal above the average, without the use of unduly complicated circuitry. During the design of a MOSFET amplifier, I made some inquiries into the behaviour of the high-frequency response and distortion with respect to phase-frequency-compensation networks. The results, presented here, were highly interesting:

1. Any kind of phase-frequency compensation, in order to ensure unconditional stability in a feedback amplifier, will increase harmonic distortion in the upper frequency range.

2. Increasing the gain of the pre-amplifying stages will give a higher feedback ratio, but the expected reduction of harmonic distortion will be lost again, owing to the need for heavier compensation. Besides, it will become more and more difficult to avoid random oscillations.

3. It follows, therefore, that unconditional stability in a feedback amplifier should depend essentially on the inherent properties of the circuit. This implies that stability must be guaranteed at all signal levels and frequencies, with all kinds of waveforms and with inductive loads.

SPECIFICATIONS

Nominal power output:	50 Watt
Sensitivity:	600mV
Signal/noise ratio:	-106dB (90µV)
Feedback factor:	60dB +/-2dB
Harmonic distortion:	
10 Watt:	1kHz :0.006% (hum and noise included)
	10kHz :0.03% (2.9mV)
50 Watt:	1kHz :0.016% (3.2mV)
	10kHz :0.033% (6.6 mV)
Efficiency (50W)	58%

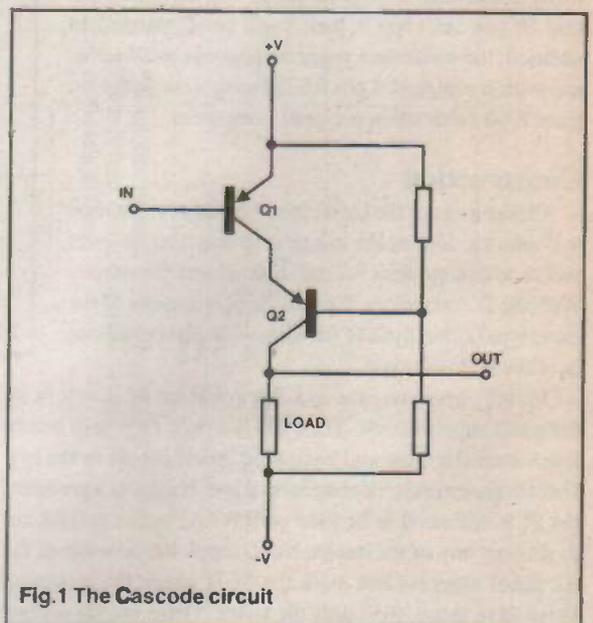


Fig.1 The Cascode circuit

The Case For The Preamp

The requirements for a preamp may be summarised as follows:

- a) High amplification factor
- b) Linear response within the audio-frequency range
- c) Low harmonic distortion.

Feeding the input stage and the driver from a current source and using current mirrors as load resistances, it is possible to obtain amplification factors up to 150,000. Unfortunately, there will be a considerable loss of high frequencies and an unfavourable degree of phase-shift, which will make stability a major problem. Several compensation networks

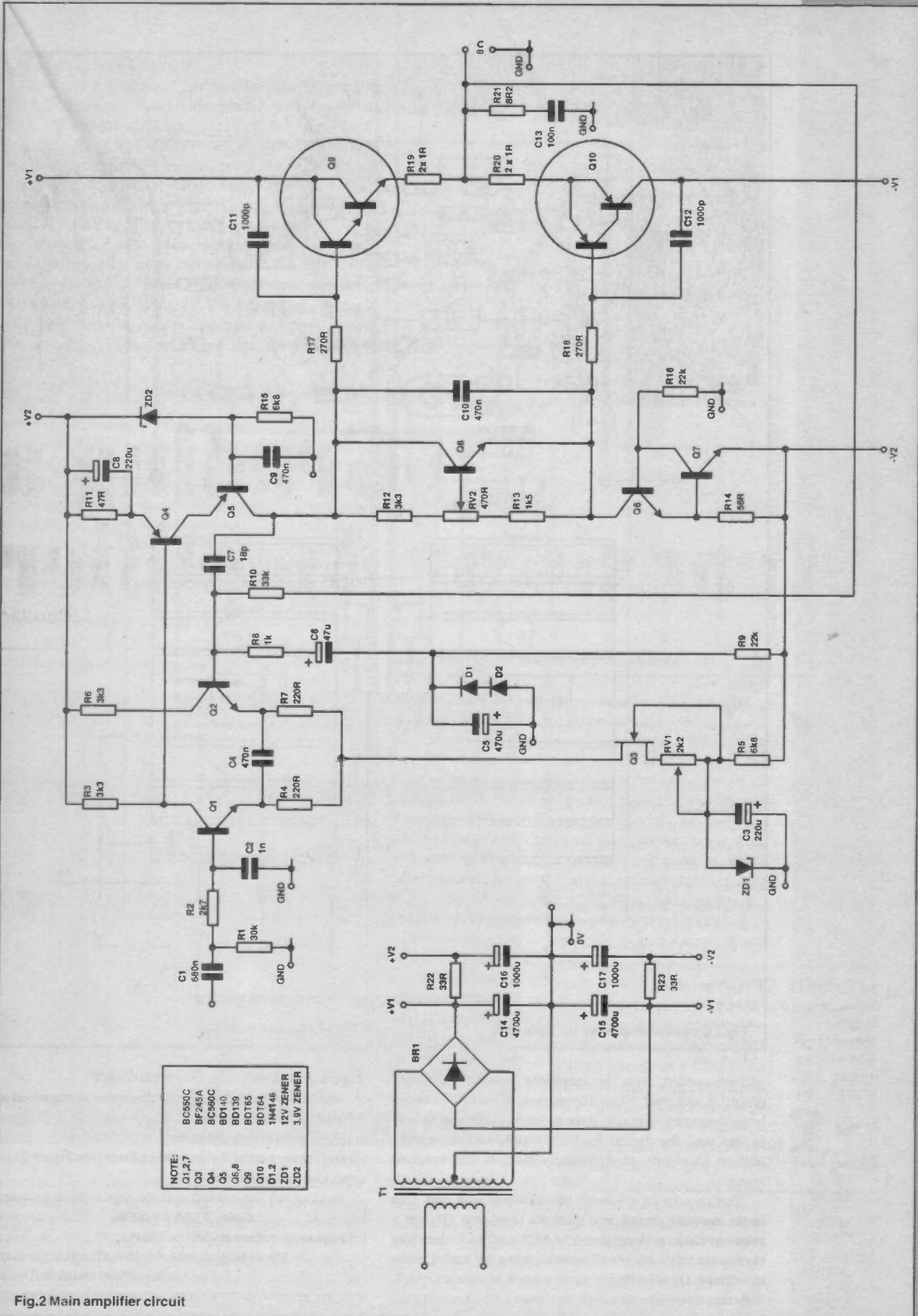


Fig.2 Main amplifier circuit

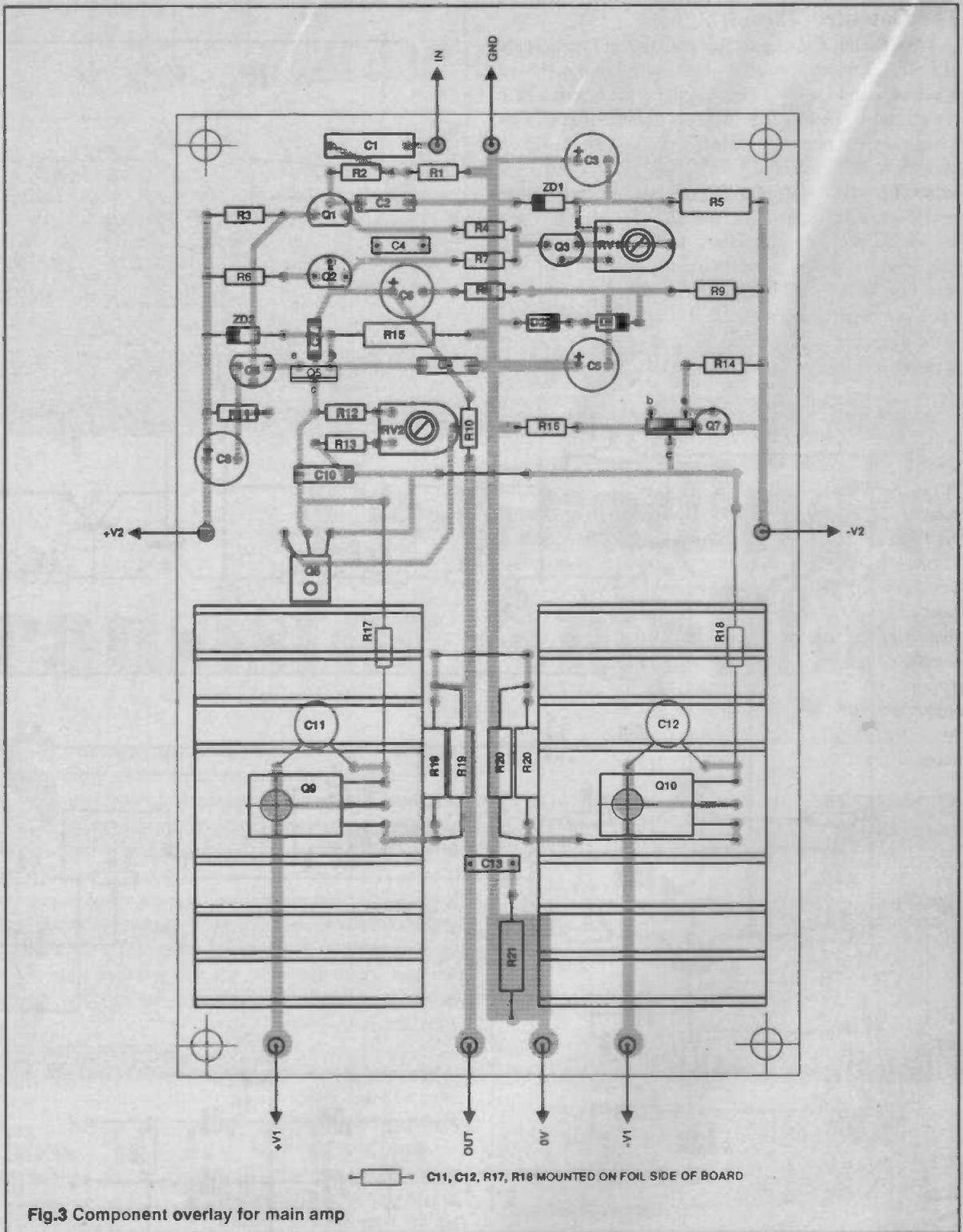


Fig.3 Component overlay for main amp

will be needed, with the inevitable result of increased distortion and poor transient response. With less gain and better frequency response, these problems can be overcome. In this way, the overall feedback ratio could be reduced without ill effects on harmonic distortion and transient response.

There is a device which will help us to reach our goal. This is the cascode circuit in Figure 1. Transistor Q1 has a common base configuration. The Miller effect is therefore eliminated and a high load resistance can be used. On the other hand, Q1 is loaded by the low input impedance of Q2. Together they make up a high gain stage with excellent high

frequency response.

Another important feature is the low distortion level, owing to the complementary characteristics of Q1 (common emitter) and Q2 (common base). The test results of the preamplifying part of the complete circuit (see Figure 2) are approximately as follows:

Gain	91dB (36000x)
Frequency response	-3dB at 18kHz
Distortion	0.15% for 20Veff at 1kHz 0.35% for 20Veff at 10kHz

The Complete Circuit

From the input, the signal first goes through the lowpass filter R2, C2, which attenuates supersonic frequencies above 60kHz. Q1 and Q2 are a long-tailed pair, fed from a FET current sink Q3. A FET transistor is an excellent current sink because in the pinch-off region, drain current is almost completely independent of drain voltage. Q3 works a -12V tension by means of Zener diode ZD1; the trimpot RV1 is used to equalise the collector currents of Q1 and Q2. For a perfect balance, both transistors should have equal base resistance, hence the somewhat unusual value for R1. Total resistance for R1 + R2 is 32k7, which will allow the use of a non-polarised capacitor for C1. But for C6 - which is also in the signal path - we have to choose an electrolytic; so we have included a polarisation network consisting of R9, C5, D1, D2.

At first sight, the driver stage (Q4...Q7) looks like a symmetrical design. This is not the case: the upper part with Q4, Q5 is the cascode, whereas the lower half (Q6, Q7) is in fact a stabilised current source. Resistor R14 is used to polarise Q7. Because V_{be} for Q7 is approximately 620mV, the fixed current of the complete stage is $620\text{mV}/56\text{R} = 11\text{mA}$, which will be more than adequate to provide the driving current for the output transistors. The voltage at the base of Q5 is stabilised by ZD2, R15, C9. Feedback is applied to the base of Q2 through R10. The gain of the complete amplifier is then determined by the ratio R10/R8 (approx. 34). Since the initial gain (without feedback) is approximately 36,000, we have a feedback factor of $36,000/34 \approx 1000$ or 60dB. With this heavy feedback it becomes necessary to apply a small amount of phase/frequency com-


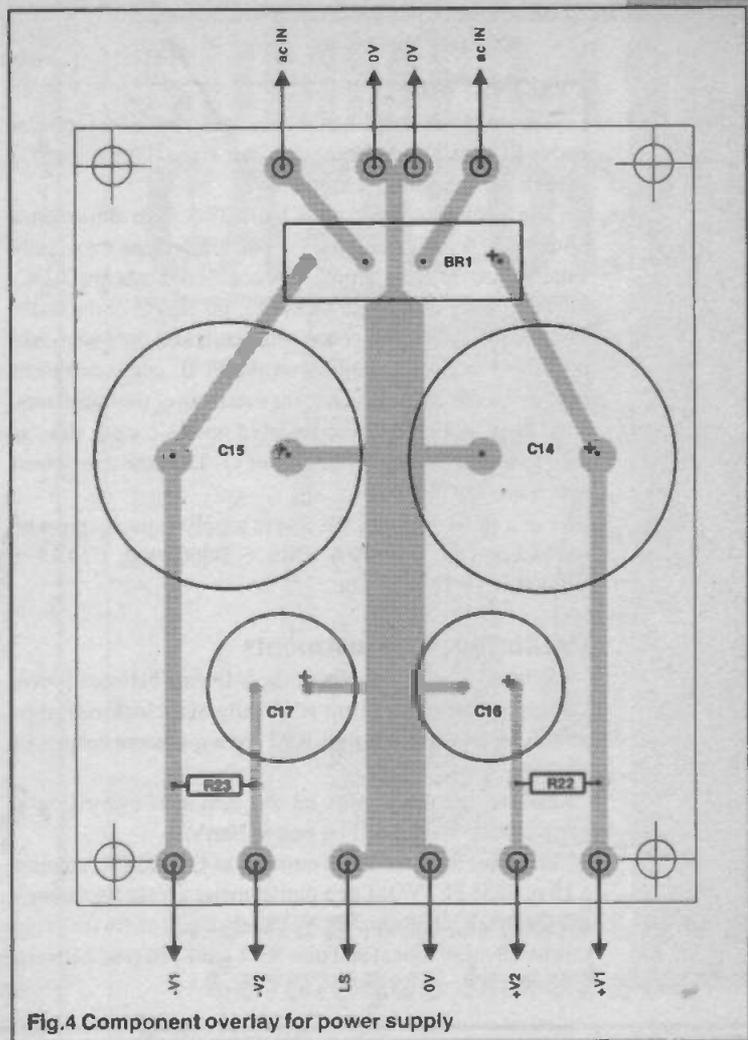


Fig.4 Component overlay for power supply

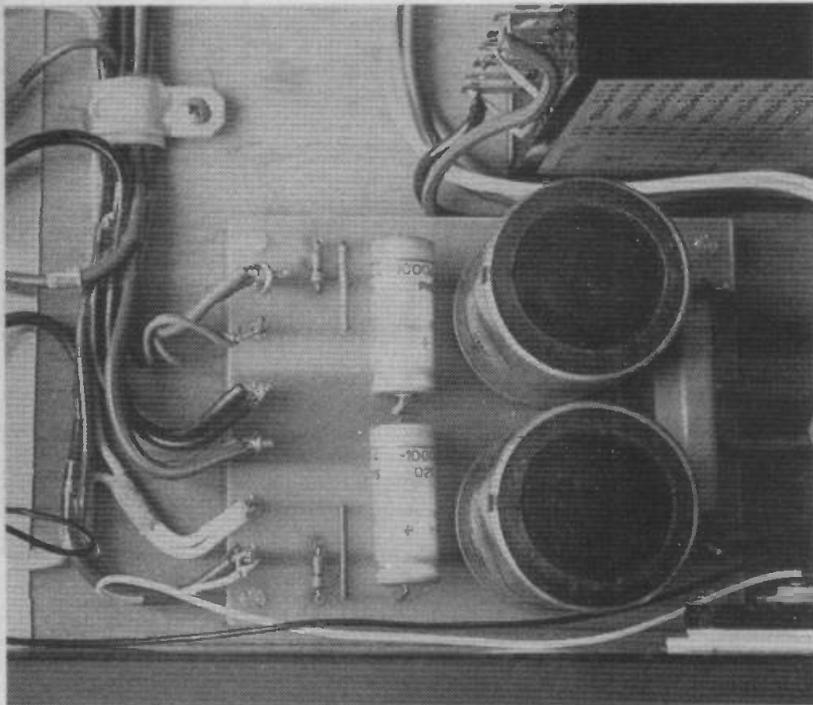

pensation. This is taken care of by C7, from the collector of Q5 to the base of Q2. Values between 5 and 33p are suitable, depending upon individual parameters of the transistors involved, but 18p is a good compromise. The effect of C7 on audio frequencies is negligible, but its presence will ensure absolute stability. Power supply for the preamplifying stages is applied through R22, C16 and R23, C17 on the power

supply PCB. The use of separate decoupling networks gives a better signal to noise ratio as well as a small increase of music-power output.

Q9 and Q10 as complementary Darlington emitter followers with a gain of less than 1; even so they are responsible for the major part of the distortion contents, hence the need for heavy feedback. Quiescent current for Q9 and Q10 is adjusted to 60mA by means of RV2 together with transistor Q8. Power output is limited to 50W - still an awful lot of noise in the ordinary living room. Medium sized heatsinks for the power transistors can be used and mounted directly on the PC board without separate wire connections and without insulating accessories. Thermal stability is accomplished by screwing Q8 (BD139) firmly to the heatsink for Q9. Beware: the

metal part of Q8 must be insulated from the heatsink with a mica washer! R17, C11 and R18, C12 are used to avoid self-oscillation. They should be mounted on the copper side of the board, as near as possible to the base of Q9, Q10. R19 and R20 consist of 2 x 1R at 1W each. Do not use wire-wound resistors here. The usual Zobel network across the output consists of R21 and C13.

Practical hints

The complete amplifier is mounted on a Eurocard-size epoxy PCB (100 x 160mm), half this size (100 x 80mm) is needed for the power supply unit.

The heatsinks are type KL107/37.5 with dimensions 70mm x 37.5 W. Other types for T0220 envelope are equally suitable, provided the temperature coefficient is below 3.2°C/W. Of course, with larger heatsinks, the length of the board must be increased. The power transistors and their heatsinks must be fixed very carefully on the PCB; apply sufficient heat-conducting compound to the metal tab of the transistors.

R17,18 and C11,12 are soldered on the copper side, as well as a wire link for the emitter of Q10. On the component side there are two links.

For a stereo version, the power supply capacity must be increased. TR1 = 225VA, BR1 = B80C8000, C14,15 = 10000µ, C16,17 = 2200µ

Preliminary Adjustments

a) Insert a milliammeter in the V1+ line between power supply and amplifier. Turn RV2 fully anti-clockwise, then switch on power and adjust RV2 for a quiescent current of 60mA.

b) Measure the voltage on the output. If everything is correct, this voltage will be below 20mV.

c) Adjust RV1 for equal currents in Q1 and Q2: connect a 10 or 20M FETVOM or a digital meter across R6 through a 10k resistor, connected to the collector end of R6 (to avoid unwanted oscillations) and turn RV1 until you read between 1.3 and 1.4V.

PARTS LIST

Resistors (0.3W 1%)

R1	30k
R2	2k7
R3,6,12	3k3
R4,7	220R
R8	1k
R9,16	22k
R10	33k
R11	47R
R13	1k5
R14	56R
R17,18	270R
R22,23	33R
RV1	2k2
RV2	470R

Capacitors (ceramic)

C7	18p
C11,12	1000p
C3,8	2200µ16V
C5	470µ6V
C6	47µ6V (low leakage or tantalum)
C14,15	4700µ50V
C16,17	1000µ50V

Semiconductors

D1,2	1N4148
ZD1	12V Zener
ZD2	3V9 Zener
Q1,2,7	BC550C
Q3	BF245A
Q4	BC560C
Q5	BD140
Q6,8	BD139
Q9	BDT65
Q10	BDT64

Resistors (1W 5%)

R5,15	6k8
R19,20	2 x 1R each
R21	8R2

Capacitors (MKM)

C1	680n
C2	1n
C4,9,10	470n
C13	100n

Miscellaneous

TR1	Transformer 120VA 2 x 30V
BR1	Bridge rectifier 80V, 5A
2 PCBs	
2 heatsinks	3.2°C/W or less (KL 107/37.5 or similar)

d) A final remark: the amplifier has been designed for an 8R load. Higher loads will give less power output, but lower loads may cause damage to the amplifier, due to overheating of the output transistors, in case of continuous full power operation.

PCB DESIGN SOFTWARE

RANGER 1 XT/AT PC Circuit — PCB

From Circuit Design
Through to Artwork
In One Package!

£100

Fully Integrated
AutoRouter

£50

Exchange your easy PC
For a free AutoRouter

RANGER 2 XT/AT + 386 PC

It has all the features you will ever need
at an outstanding price. But now with a new 2
layer 386 Ripup & Retry AutoRouter

£599

Option Pack 100% Router
Simultaneous 6 layer Ripup & Retry
AutoRouter with via Minimisation.
Autocad DXF in & out. GERBER in.

£350



Call us for details & demo disk on 0705 591037

SEETRA




Seetra CAB, Hinton Daubney House, Broadway, Lyndean, Hants. PO8 0SG

Tel: 0705 591037 Fax: 0705 599036



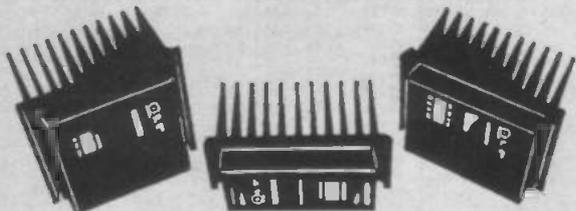**UK Distributor for the
complete ILP Audio Range**



BIPOLAR AMPLIFIER MODULES

Encapsulated amplifiers with integral heatsink.

HY30P	15W Bipolar amp	£9.95
HY60	30W Bipolar amp	£12.62
HY6060	30W Stereo Bipolar amp	£26.46
HY124	60W Bipolar amp (4 ohm)	£20.69
HY128	60W Bipolar amp (8 ohm)	£20.69
HY244	120W Bipolar amp (4 ohm)	£27.38
HY248	120W Bipolar amp (8 ohm)	£27.38
HY364	180W Bipolar amp (4 ohm)	£42.86
HY368	180W Bipolar amp (8 ohm)	£42.86

MOSFET AMPLIFIER MODULES

Encapsulated amplifiers with integral heatsink.

SMOS60	30W Mosfet amp	£23.15
SMOS6060	30W Stereo Mosfet amp	£39.95
SMOS128	60W Mosfet amp	£30.95
SMOS248	120W Mosfet amp	£42.50

CLASS A AMPLIFIER MODULE

Encapsulated Class A amplifier with integral heatsink

HCA40	20W Class A amp	£36.60
-------	-----------------	--------

POWER SUPPLIES

Full range of transformers and DC boards available for the above amplifiers.

100 VOLT LINE TRANSFORMERS

Full range of speech and music types for amplifiers from 30 watt to 180 watt

PREAMPLIFIER MODULE

General purpose preamplifier for a wide range of applications.

Prices include VAT and carriage



Quantity prices available on request

Write, phone or fax for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254 Fax: 0227 365104

SUMMER 1993 CATALOGUE



The new enlarged Cirkit Catalogue is out now!

- ▶ 32 more pages
- ▶ New range of Kenwood 'scopes
- ▶ The latest scanning receivers and accessories
- ▶ New section of low cost security products
- ▶ Extended range of Velleman kits including: 250W 12Vdc to 220Vac inverter, in-car amplifier power supply, 200 and 400W amplifiers, suppressed lamp dimmer, halogen lamp dimmer, day/night thermostat and telephone remote control unit
- ▶ New test equipment, includes: 2.3GHz bench frequency counter, EPROM emulator/programmer, portable 'scopes and bench function generators
- ▶ Host of new components, including: compression trimmers, variable capacitors, connectors, fuses, and fuseholders, potentiometers, IC's, soldering irons and lead free solder
- ▶ Published 27th May 1993
- ▶ Available from most large newsagents or directly from Cirkit
- ▶ **Send for your copy today!**

£1.90
+ 30p p&p

Cirkit



CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone (0992) 444111 · Fax (0992) 464457

EXPRESS COMPONENTS

74LS SERIES		74LS273		4511		LM335Z		2.2UF 25V		TNC 50R PLUG		BD138		2N2907		74HC243	
74LS00	0.10	74LS279	0.32	4512	0.28	LM339	0.30	3.3UF 25V	0.14	TNC CHIS SOC	0.65	BD159	0.19	2N2907A	0.19	74HC244	0.34
74LS01	0.10	74LS280	0.86	4514	0.72	LM348	0.32	4.7UF 25V	0.18	PL259 PLUG	0.55	BD140	0.23	2N2926	0.14	74HC245	0.49
74LS02	0.10	74LS283	0.49	4515	0.77	LF351	0.35	6.8UF 25V	0.20	REDUCER (PL259)	0.16	BF180	0.30	2N3053	0.26	74HC251	0.28
74LS03	0.10	74LS290	0.24	4516	0.30	LF353	0.35	10UF 25V	0.22	PL259 SOCKET	0.55	BF182	0.30	2N3054	0.85	74HC253	0.28
74LS04	0.10	74LS293	0.24	4518	0.26	LF356	0.79	15UF 25V	0.28	COAX PLUG	0.18	BF185	0.30	2N3055	0.56	74HC257	0.28
74LS05	0.10	74LS295	0.58	4520	0.25	LM358	0.26	22UF 16V	0.28	COAX LINE SOC	0.38	BF194	0.18	2N3442	1.34	74HC259	0.34
74LS06	0.39	74LS298	0.63	4521	0.62	LM380	1.10	33UF 16V	0.50	SCART PLUG	0.65	BF195	0.18	2N3702	0.09	74HC266	0.25
74LS07	0.39	74LS299	1.18	4526	0.39	LM381	2.60	47UF 16V	0.62	IEC CHIS PLUG	0.49	BF196	0.19	2N3703	0.09	74HC273	0.34
74LS08	0.10	74LS322	1.58	4527	0.38	LM386	0.46	68UF 6V	0.72	IEC LINE SOCKET 1.70	1.70	BF197	0.19	2N3704	0.09	74HC280	0.36
74LS09	0.12	74LS323	1.78	4528	0.39	LM393	0.27	100UF 10V	1.40	IEC 2M LEAD	1.80	BF198	0.19	2N3705	0.09	74HC299	0.59
74LS10	0.10	74LS347	0.90	4529	0.43	ZN414Z	0.99	100UF 16V	1.70	IEC 2M LEAD	1.80	BF199	0.19	2N3706	0.09	74HC354	0.42
74LS11	0.10	74LS348	1.18	4532	0.20	ZN416E	1.59			1M MONO PLUG 0.18		BF202	0.32	2N3773	1.78	74HC356	0.44
74LS12	0.10	74LS349	0.78	4534	0.31	ZN423	1.45			1/4" STEREO PLUG 0.29		BF258	0.35	2N3866	1.18	74HC365	0.44
74LS13	0.18	74LS353	0.88	4536	0.99	ZN424P	1.20			2.5 MONO PLUG 0.12		BF259	0.32	2N3903	0.09	74HC366	0.32
74LS14	0.22	74LS353	1.38	4538	0.36	ZN425E	4.90			3.5 MONO PLUG 0.12		BF259	0.35	2N3904	0.09	74HC367	0.25
74LS15	0.22	74LS364	1.38	4541	0.30	ZN426E	2.90			3.5 STEREO PLUG 0.20		BF259	0.38	2N3905	0.09	74HC368	0.25
74LS20	0.12	74LS365	0.24	4543	0.45	ZN427E	9.40					BF259	0.38	2N3906	0.09	74HC373	0.34
74LS21	0.12	74LS366	0.28	4555	0.34	ZN428E	7.90					BF259	0.38	2N4062	0.16	74HC374	0.34
74LS22	0.12	74LS367	0.28	4556	0.33	ZN435E	6.25					BF259	0.38			74HC390	0.44
74LS24	0.33	74LS368	0.28	4560	1.17	ZN448E	9.20					BF259	0.38			74HC393	0.32
74LS26	0.12	74LS373	0.32	4566	1.95	SL486	2.70					BF259	0.38			74HC423	0.36
74LS27	0.12	74LS374	0.32	4572	0.24	SL486	2.35					BF259	0.38			74HC424	0.42
74LS28	0.12	74LS375	0.34	4584	0.23	NE531	1.54					BF259	0.38			74HC425	0.42
74LS30	0.12	74LS377	0.32	4585	0.32	NE544	2.75					BF259	0.38			74HC426	0.46
74LS32	0.13	74LS378	0.62	4724	0.69	NE555	0.19					BF259	0.38			74HC427	0.46
74LS33	0.13	74LS379	0.62	40106	0.30	7555	0.41					BF259	0.38			74HC428	0.42
74LS37	0.14	74LS385	2.22	40109	0.49	NE556	0.34					BF259	0.38			74HC429	0.42
74LS38	0.13	74LS386	0.46	40163	0.45	NE556	1.09					BF259	0.38			74HC430	0.60
74LS40	0.23	74LS390	0.25	40174	0.33	NE566	1.10					BF259	0.38			74HC431	0.72
74LS42	0.13	74LS393	0.24	40175	0.35	NE567	0.35					BF259	0.38			74HC432	1.10
74LS44	1.62	74LS395	0.34	40193	0.59	NE570	2.35					BF259	0.38			74HC434	1.10
74LS47	0.60	74LS396	1.68			NE571	1.98					BF259	0.38			74HC436	1.10
74LS48	0.46	74LS398	1.22			LM710	0.80					BF259	0.38			74HC438	1.10
74LS49	0.62	74LS399	0.62			LM711	0.80					BF259	0.38			74HC440	1.10
74LS51	0.11	74LS445	1.30			LM725	4.80					BF259	0.38			74HC441	1.10
74LS54	0.11	74LS490	0.90			LM725	4.80					BF259	0.38			74HC442	1.10
74LS55	0.13					741	0.17					BF259	0.38			74HC443	1.10
74LS73	0.20					LM747	0.37					BF259	0.38			74HC444	1.10
74LS73A	0.26					LM748	0.30					BF259	0.38			74HC445	1.10
74LS74	0.16					TBA810	0.67					BF259	0.38			74HC446	1.10
74LS74A	0.18					TBA820	0.38					BF259	0.38			74HC447	1.10
74LS75	0.21					ML924	4.65					BF259	0.38			74HC448	1.10
74LS76	0.22					ML926	4.25					BF259	0.38			74HC449	1.10
74LS76A	0.24					ML927	4.25					BF259	0.38			74HC450	1.10
74LS77	0.42					TDAL024	1.80					BF259	0.38			74HC451	1.10
74LS83	0.34					SAA1027	3.20					BF259	0.38			74HC452	1.10
74LS85	0.34					ZN1044E	3.20					BF259	0.38			74HC453	1.10
74LS86	0.22					LM1458	0.30					BF259	0.38			74HC454	1.10
74LS90	0.24					ULN2003	0.39					BF259	0.38			74HC455	1.10
74LS91	0.20					ULN2004	0.42					BF259	0.38			74HC456	1.10
74LS92	0.29					TDA2004	1.75					BF259	0.38			74HC457	1.10
74LS93	0.24					TDA2030	1.18					BF259	0.38			74HC458	1.10
74LS95	0.38					ULN2064	1.20					BF259	0.38			74HC459	1.10
74LS96	0.46					ULN2065	1.20					BF259	0.38			74HC460	1.10
74LS107	0.25					ULN2068	1.20					BF259	0.38			74HC461	1.10
74LS109	0.25					XR2205	4.20					BF259	0.38			74HC462	1.10
74LS112	0.25					UA2240	2.60					BF259	0.38			74HC463	1.10
74LS113	0.25					ULN2803	0.64					BF259	0.38			74HC464	1.10
74LS114	0.25					LM2917N8	2.60					BF259	0.38			74HC465	1.10
74LS122	0.33					CA3045	0.35					BF259	0.38			74HC466	1.10
74LS123	0.33					CA3080E	0.71					BF259	0.38			74HC467	1.10
74LS123	0.33					CA3130E	0.97					BF259	0.38			74HC468	1.10
74LS126	0.28					CA3140E	0.55					BF259	0.38			74HC469	1.10
74LS132	0.28					CA3240E	1.20					BF259	0.38			74HC470	1.10
74LS133	0.28					MC3302	0.60					BF259	0.38			74HC471	1.10
74LS136	0.31					MC3340	1.75					BF259	0.38			74HC472	1.10
74LS137	0.62					LM3900	0.70					BF259	0.38			74HC473	1.10
74LS138	0.24					LM3909	1.45					BF259	0.38			74HC474	1.10
74LS139	0.26					LM3911	2.20					BF259	0.38			74HC475	1.10
74LS145	0.58					LM3914	2.65					BF259	0.38			74HC476	1.10
74LS147	0.96					RC4558	0.36					BF259	0.38			74HC477	1.10
74LS148	0.86					NE5532	0.79					BF259	0.38			74HC478	1.10
74LS151	0.25					NE5534	0.80					BF259	0.38			74HC479	1.10
74LS153	0.28					ICL7106	5.80					BF259	0.38			74HC480	1.10
74LS154	0.28					ICM7555	0.45					BF259	0.38			74HC481	1.10
74LS155	0.25					ICM7556	1.20					BF259	0.38			74HC482	1.10
74LS156	0.25					ICL8038	4.90					BF259	0.38			74HC483	1.10
74LS157	0.20					LM13600	1.10					BF259	0.38			74HC484	1.10
74LS158	0.25											BF259	0.38			74HC485	1.10
74LS160	0.32											BF259	0.38			74HC486	1.10
74LS161	0.32											BF259	0.38			74HC487	1.10
74LS162	0.32											BF259	0.38			74HC488	1.10
74LS163	0.33																

MICROWAVE CONTROL PANEL. Man operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P151. Good experimenters board.

FIBRE OPTIC CABLE. Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R or £2 a metre.

12V SOLAR CELL. 200mA output ideal for trickle charging etc. 300mm square. Our price £15.00 ref 15P42R. Gives up to 15v.

PASSIVE INFRA-RED MOTION SENSOR. Complete with daylight sensor, adjustable lights on timer (8 secs -15 mins), 50° range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R

VIDEO SENDER UNIT. Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12v DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P191R. Turn your camcorder into a cordless cameral

FM TRANSMITTER Housed in a standard working 13A adapter (bug is mains driven). £26.00 ref 26P2R. Good range

MINIATURE RADIO TRANSCIEVERS. A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases and earpieces. £30.00 ref 30P12R

FM CORDLESS MICROPHONE. Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 battery. Tuneable to any FM receiver. Our price £15 ref 15P42AR.

12 BAND COMMUNICATIONS RECEIVER. 9 short bands. FM, AM and LW DX/local switch, tuning 'eye' mains or battery. Complete with shoulder strap and mains lead. £19 ref 19P14R. Ideal for listening all over the world

CAR STEREO AND FM RADIO. Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db, wow and flutter less than .35%. Neg earth. £19.00 ref 19P30

LOW COST WALKIE TALKIES. Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R. Ideal for garden use or as an educational toy.

7 CHANNEL GRAPHIC EQUALIZER plus a 60 watt power amp! 20-21KHZ 4-8R 12-14v DC negative earth. Cased. £25 ref 25P14R.

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P4R. 2 x Cs £4.00 ref 4P73R. 4 x D's £9.00 ref 9P12R. 1 x PP3 £6.00 ref 6P35R Pack of 10 AAA's £4.00 ref 4P92R.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalents book. New ed. £20.00 ref 20P32R.

GEIGER COUNTER KIT. Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158R. 35mm square.

FM BUG Built and tested superior 9v operation £14.00 ref 14P3R

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R

SINCLAIR C5 MOTORS. 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £22.00 ref 20P22R. Limited stocks.

ELECTRONIC SPEED CONTROL KIT. for C5 motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R. Potentiometer control.

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased. £6.00 ref 6P3R. 2x C cell model £6.00.

ACORN DATA RECORDER ALF503. Made for BBC computer but suitable for others. Includes mains adaptor, leads and book. £15.00 ref 15P43R

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 10 tapes New low price £15.00 ref J15P4

PHILIPS LASER 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £22.00 REF 22P33R READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

12 TO 220V INVERTER KIT. As supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R.

WIND UP SOLAR POWERED RADIO! FM/AM Radio takes rechargeable batteries. Complete with hand charger and solar panel. £14.00 REF 14P200RA

BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10 £4.00 REF 4P92R, PACK OF 100 £30.00 REF 30P16R

FRESNEL MAGNIFYING LENS. 83 x 52mm £1.00 ref BD827R.

12V 19A TRANSFORMER Ex equipment £20 but OK

POWER SUPPLIES Made for the Spectrum plus 2 give +5 @ 2A, +12 @ 700mA & -12 @ 50mA. £8 ref QBP3

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R.

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3,4,5,6,7,8,9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R.

QUICK CUPPA? 12v immersion heater with lead and cigar lighter plug £3.00 ref 3P92R. Ideal for tea on the move!

LED PACK. 50 red, 50 green, 50 yellow all 5mm £8.00 ref 8P52

360K 5.25" DISK DRIVE. Industry standard, ideal replacement or second drive for most computers. £9.00 EACH ref. X9P1.

PPC PSU 13.8V 1.9A (not plug in). £10.00 EACH REF: X10P1.

MINIMUM GOODS ORDER £5.00 *TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILLINGLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

THIS MONTHS SPECIAL OFFERS

SOLAR CELLS

10 WATT SOLAR CELL (3" x 1") 14.5v/700mA

Now available by mail order

Coated with exceptionally efficient amorphous silicon these glass solar cells have an almost timeless lifespan and will not suffer with discolouration. There are possibly hundreds of uses for these cells, a few of which could be: for Car Battery Charging, for use on Boats or on Caravans, in fact anywhere a portable 12V supply is required. Several of our overseas Mediterranean customers with homes in remote hilly sites, use these solar cells as a daytime power source to backup generators. The solar cells can be connected in series or parallel to give higher voltages or larger current capacity. REF: ET34P1

PRICED at only £33.95. PLUS an additional £2.00 special packaging charge on this item in addition to £3.00 PP charge.

OTHER SOLAR PANELS:

12V 200mA GLASS SOLAR PANEL. 12" x 12" in dimension £15.00 EACH ref: 15P42.

.45V 700mA SOLAR CELL. silicon plastic encapsulated. 95 x 65 x 7.5mm in dims. £3.00 EACH ref: 3P42.

.45V 400mA SOLAR CELL. silicon plastic encapsulated. 75 x 45 x 7.5mm in dims. £2.00 EACH ref: 2P199.

.45V 100mA SOLAR CELL. silicon plastic encapsulated. 45 x 26 x 7.5mm in dims. £1.00 EACH ref: BD631.

SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL
250 PORTLAND ROAD HOVE SUSSEX BN3 5QT
MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £2.00 POST PLUS VAT.
PLEASE ALLOW 7-10 DAYS FOR DELIVERY
TELEPHONE ORDERS WELCOME
TEL: 0173 263500
FAX: 0173 323677

INDUCTIVE AMPS £5.00

Made for amplifying a telephone handset for the hard of hearing. However if you hold one against a piece of wire carrying a telephone conversation you can hear both sides of the conversation! It can also be used for tracing live wires in a wall or detecting cables carrying mains etc. Fully cased complete with battery and fixing strap. Approx 2.5" diameter 1" thick.
Our Price :£5.00 Our Ref :ET5P11



CTM644 COLOUR MONITOR £79.00

Refurbished monitor suitable for many home computers standard RGB input.
Our Price :£79.00 Our Ref :ET79P11

ARCHEMEDIES A3000 PSU £10.00

A compact switch mode PSU with on/off switch, selectable voltage input 110/240. NEW O/P via fly leads. GOOD STOCKS AVAILABLE.
Our Price :£10.00 Our Ref :ET10P11

ANSWERPHONES from only £18.00

Yes its true BT approved push button dialling. These are customer returned units and have two faults. We will supply you with a chip to cure one fault then you have to sort out the other problem! NON RETURNABLE.
Prices:
£18.00 each. REF: ET18P21
£60.00 PKT 4. REF: ET60P21

PORTABLE ALARM SYSTEM £17.00

'PAL' Portable Multi Beam Scanning System. Lockable Stand-alone PIR unit with removable keys (3 supplied). This unit uses a PP3 battery and when activated emits a piercing SHRILL! The unit scans the room and memorises the layout. Should this change, the alarm is triggered. There is a 60 second exit delay.
Our Price :£17.00 Our Ref :ET17P11

PIR MOVEMENT DETECTOR £15.00

Once again we have aquired stocks of this popular line and are able to offer you a very high quality and professional detector at only **£15**. Range: 20m with a 90. arc. Day and Night Mode Dims: 15cm x 9cm x 11cm. New and boxed, complete with installation guide.
Our Price :£15.00 Our Ref :ET15P21

MANY MORE SPECIAL OFFERS IN OUR REGULAR NEWSLETTERS

- WE HAVE HUNDREDS AND HUNDREDS MORE STOCK LINES - TOO MANY TO LIST IN ONE ADVERT ! CHOOSE FROM**
- | | |
|--------------------------|--------------------------|
| AERIAL AMPLIFIERS | FANS |
| AEROSOLS | FUSES |
| ALARMS | GLUE GUN AND GLUE |
| AMPLIFIED SPEAKERS | HEADPHONES |
| ANALOGUE MULTIMETERS | HEATSHRINK SLEEVEING |
| APPLIANCE LEADS | HI FI SPEAKERS |
| BATTERIES AND HOLDERS | IONISERS |
| BATTERY CHARGERS | LED's |
| BOOKS | LASERS AND LASER PSU's |
| BOXES AND CASES | LOGIC PROBES |
| CAMCORDER BITS | LOUD AND MARINE SPKRS |
| CAPACITORS | MICROPHONES |
| CAR AMPS, RADIOS & SPKRS | PIR LIGHTS AND DETECTORS |
| CB SPEAKERS AND PSU's | POWERS SUPPLIES |
| COMPUTER BITS | POWER AMPLIFIERS |
| CONNECTORS | RADIOS |
| DESOLDER PUMP | SERVICE AIDS |
| DIGITAL MULTIMETERS | SOLDERING EQUIPMENT |
| DISCO LIGHTING | STEAM ENGINES |
| DISPLAYS | TRANSCEIVERS |
| DUBBING KIT | TRANSFORMERS |
| DRILLS | WIRELESS MICROPHONES |

IN SUSSEX? CALL IN AND SEE US!!

TURN YOUR SURPLUS STOCK INTO CASH IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

MUCH MUCH MORE IN OUR 1993 CATALOGUE. PLEASE SEND 41P, A4 SIZED SAE FOR YOUR FREE COPY.


VOLT HOME STUDIO MONITOR

Designed specifically for studio use, this design also gives excellent results when used for conventional HiFi reproduction. The HSM kit is remarkable value - you would have to spend many times its cost to achieve comparable results from a ready-made speaker. The HSM will produce high undistorted sound pressure levels & has massive power handling capability (full unclipped output of 200 watts). Split circuitry crossover is used to enable biwiring to be employed without any modifications.

... all in all, highly recommended"

Paul White, Home & Studio Recording magazine.

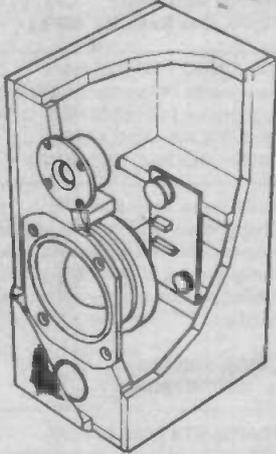The kit includes bass and treble units, flat pack cabinets (accurately machined from smooth MDF for easy assembly), acoustilux, assembled crossovers, reflex ports, binding posts, grille fabric etc...



Dimensions:
508 x 267 x 343mm
Response:
30 HZ - 20 KHZ
Sensitivity:
90db/1w/1m
AMP Suitability: 20-200w
£379.00 per pair inc VAT
carriage/ins. £18.00

Wilmslow Audio

Dept. ET1, Wellington Close,
Parkgate Trading Estate
Knutsford, Cheshire
WA16 8DX
Tel: (0565) 650605
Fax: (0565) 650080

DIY Speaker catalogue £2.00
post free (export £3.50)




Telephone credit card
orders welcome



Open Tuesday to Saturday, 4 demonstration rooms available.

NEW

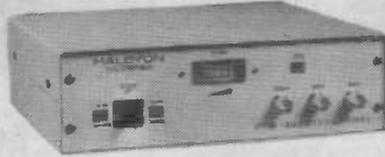THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Only
£195 + VAT
carriage extra

- ★ Provides 10MHz, 5MHz & 1MHz
- ★ Use it for calibrating equipment that relies on quartz crystals, TCXOs, VCXOs, oven crystals.
- ★ Phase locks to DROT/WICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP - French eq to NPL)
- ★ British designed and British manufactured

Output frequencies -
10MHz, 5MHz, 1MHz -
Short term stability -
better than 2x10⁻⁸ (1 sec)
Typical - 4x10⁻⁹ (1 sec)
Long term - tends to
2x10⁻⁹ (100sec)

ECG MONITOR SEM430 WITH SEM4202	£75	PHILIPS PM6456 FM STEREO GENERATOR	£195
TV PATT GENERATORS PAL 825/425	FROM £20	MARCONI TF2333 M/F OSC LEVEL METER	£35
EDDYSTONE EP15 PAN ADAPTOR	POA	7SEG 12V & 9" DISPLAYS DIGITEX SIGNALX	£15 & £10
QUAD TUNER & Z2 CONTROL UNIT	POA	VALVE TESTERS AVO MK 1,2,3,4	FROM £49 TO £149
TEKTRONIX 2215 60MHZ 2 TRACE DEL T/B	£450	FEEDBACK FG600 FUNC GEN SIN/SQ/TRI	£125
TEKTRONIX 453A 50MHZ 2 TRACE DEL T/B	£249	TIME 2003S VOLTAGE CALIBRATOR	£195
TELEQUIPMENT S62 SINGLE TRACE 5MHZ SCOPE	£35	100V 1:10 MULTIPPLIER FOR ABOVE	£35
H.P. 8405A VECTOR V/METER 1GHZ	£595	MARCONI TF2300 FM/AM MODULATION METER	£195
PHILIPS PM3226 15MHZ DUAL TRACE	£195	NASCOM/GEMINI CARDS, VARIOUS	POA
LEADER LB0522 20MHZ DUAL TRACE	£225	CASELLA TEMP RECORDER 7 DAY	£99
TELEQUIPMENT DS1A 10MHZ DUAL TRACE	£149	McKENZIE 7 DAY TEMP/HUMIDITY RCORDR	£95
SE LABS SM111 18MHZ DUAL TRACE	£129	19" RACK CASE 20U x 31" DEEP	£99
TER 468B 100MHZ DUAL TRACE DEL T/B	£475	FEEDBACK SS0603 1MHz SINE/SQ OSC	£125
TEKTRONIX 520 521A PAL VSCOPES	£395 & £895	KAYE DEE. PNEUMO UV EXP UNIT 390x260mm	£175
TELEQUIPMENT D67A 25MHZ 2T, DEL T/B	£215	FARNELL E350 0-350v 100mA, 2 x 6.3V	£49 to £59
H.P. 1700A 35MHZ DUAL TRACE	£249	FARNELL FG1 FUNC GEN 2-2.2MHz	£129
HITACHI VC 6015 10MHZ DIGITAL STORAGE	£345	COMMUNICATIONS RECEIVERS, VARIOUS	POA
H.P. 1340A X-Y DISPLAYS	£149	LCR MARCONI TF1313 0.25%	£35
TEK 545/585 SERIES PLUG-INS	From £10	LCR COMPONENT COMPARATOR AVO C2457/S	£35
WANDEL/GOLTERMANN SPM-2 LEVEL METER	£169	LEVEL TM68 MICRO V-METER 450MHZ	£35
WANDEL/GOLTERMANN SPM-3 LEVEL METER	£189	LEVEL TM38 MICRO V-METER 3MHZ	£35
WANDEL/GOLTERMANN PS-3 SIGNAL GEN	£169	CERTLING V20 SINGLE PAN BALANCES 200GM	£35
MARCONI TF2304 AM/FM MOD METER PRTBLE	£249	ANALYTICAL BALANCES WITH WEIGHTS 250GM	£99
MARCONI TF2330 WAVE ANALYSER 20Hz-50kHz	£149	VACUUM PUMPS 1.5 & 2.8 CU.MM/R	£125 & £149
H.P. S315A 1GHz F/CTR, OPTS 1, 2 & 3	£750	TOPAZ 91007-117.5KVA 120/240-120/240 ISOL	£175
CONSTANT VOLTAGE TRANSFORMS 150VA-2KVA	POA	KINGSHILL NLS1540 15V 40A PSUs CASED, AS NEW	£195

LIST AVAILABLE BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS ALL PRICES EXC. OF P&P AND VAT
QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED



HALCYON ELECTRONICS



423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340

JUST LOOK AT WHAT'S AVAILABLE FROM BONEX

Balance Mixers Batteries

Button Cells, Ni-cads,
Battery Holders,
Battery Eliminators,
Ni-cad Chargers,

Boxes

ABS Plastic, Die-cast,
Hand-Held Enclosures,
Bridge Rectifiers

Bulbs

Audio, BBC, Camcorder,
Cassette/Calculator, Mains,
Computer, IBM PC/AT,

Serial, Monitor Extension,
Parallel, Patch/Video Leads,
Scart Cables, Serial Printer,
Video/Audio Dubbing Kit,

Cable Ties

Capacitors
Ceramic Discs
Ceramic Feedthroughs,
Chip, Electrolytics,
Monolithic, Mylar,
Polycarbonates,
Polystyrenes, Polyesters,
Tantalum Beads,

Capacitors Variable

Film Dielectric Trimmers,
Ceramic Trimmers,

CMOS Devices Computer Accessories

Adaptors 9W to 25W,
Data Switch Boxes,
Gender Changers,
RS232 - Patch Boxes, Null
Modems, Plug in Testers,
Surge Protectors,
Surge Protector Plugs,

Connectors

Audio Adaptor/Plugs,
Banana Connectors,
Blinding Posts BNCs,
Centronics, D,
D High Density,
DC Power, DIL IC,
DINs, IDCs, Edge, F,
Jack 2.5mm, 3.5mm, 5.3mm,
Mains, Microphones,
Molex, N-Type, Phono,
PL259, RF Adaptors,
Scart, TNC, Terminal
Strips, TV, XLR,
Crocodile Clips

Crystals

Desolder Pumps
Diodes
Plastic IN4000 / IN5400,
Toko Varicaps
Signal Diodes,
Zener, BZYs and BZXs,

Drills

Bits and Burrs,
Expo,
Pin Chucks,
Power Supplis,
Saws and Slicing Discs,

Fans

Feet, Rubber

Ferrites

Filters
FM Ceramics, Mechanical
IFs, Ceramic Resonators,
Crystal, Helicals, NTSC/
PAL, Pilot Tone, Quadrature
Detector, Satellite TV, Video,

Fuses

Grommets
Howes Kits
Heatsinks
Inductors Fixed
Inductors Moulded
Inductors Surface Mount
Inductors Variable
Infra-red Source Sensor
Insulating Tape
Integrated Circuits

CMOS,

Eproms,
Linears,
Memory,
TTL,

Kits and Modules

L.E.D.s, 3mm and 5mm
Light Dep Resistors
Loudspeakers
Microphone Inserts

Multimeters

Neon Indicators
Nuts and Bolts
Opto Switches
Optoisolators

P.C.B.s

Copper Clad, Etch Resist
Transfers, Photo Resist,
Plns, Proto-type,
Polishing Mops
Potentiometers
Control Pots, 16mm, 24mm,
Pre-sets, Horizontal/Vertical
Trimmer Pots,
Power Supplies

Relays

Resistors
Carbon Film, Metal Oxide,
Wirewound,
Screening Cans
Semi's Mount Kits
Solder
Soldering Irons
Switches
DIL, Key, Microswitches,
Push, Rotary, Slide, Toggles,

Test Leads

Test Probes
Tools
Crimping, Cutters,
Files, Insertion,
Reamers,
Screwdrivers,
Strip Board, Trimtools,
Toroid Cores
Thyristors
Transformers, Mains
Transistors
Audio Power,
Darlingtons, F.E.T.s
GaAsFETs,
Low Power RF,
Microwave,
MosFETs,
Power RF,
Small Signal,
VMOS,
Triacs

TTL

Video Modulators
Voltage Regulators
Wire
Enamelled Copper,
Tin Plated,
Silver Plated,
Zero Insert Force
Sockets



12 Elder way
Langley Business Park
Slough
Berkshire SL3 6EP. Telephone : 0753 549502 Fax : 0753 543812

CATALOGUE AVAILABLE

SPECIAL OFFER
SBL-1 BALANCE MIXERS £3.75


Home Minder

Bob Noyes deters the burglars with his house minder

Reducing the risk of break-ins was a topic raised at a Neighbourhood Watch talk which I attended recently. A lot of house break-ins are of an opportunistic nature, where someone walks around in the evening passing the same houses several times, looking for those either in total darkness or with a landing or hall light on only.

Such houses are singled out as potential targets because their owners are almost certainly out. Although a burglar alarm can be fitted and is expected to be set off when the house is broken into, there is always the feeling that someone has been in your home and may well have done major damage during entry. Far better to discourage burglars from attempting to break in in the first place, by making your home appear to be buzzing with activity.

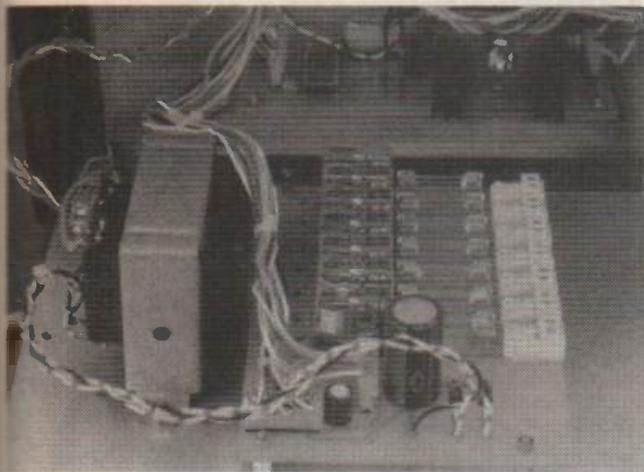All this seemed pretty obvious and what was needed was something that would switch lights on and off in a controlled



fashion, suggesting to the casual passer by that the house was occupied. Single channel timed light switches are readily available, but on the whole these turn on and off once per 24 hours - not really giving the appearance of normality. Several of these could be used in different rooms to give a more realistic effect, but all require suitable table or standard lamps and all the clocks require setting up. This means leaving maybe four or five time clocks running all day and all night and even then they would all have to have their lights activated when required - altogether an impracticable solution when you're in a hurry to go out.

What was needed was a custom designed unit that only



required one switch to be activated once installed and set up. It would need to be crystal controlled for long term accuracy and have battery back up for accurate time keeping, even in a power cut, because if the clock stopped and restarted, the lights would come on late depending on the length of the power cut. It must have a summer and winter set of commands because lights are switched on earlier in the winter and stay on longer in the mornings than in the summer. The 'program' would have to be able to be tailor made to the type of building and family it served. In all quite a tall order, but Home Minder achieves all this - and for a very affordable price, considering the peace of mind given when either going out for the evening or away on holiday for a couple of weeks.

Unfortunately, no guarantees can ever be given, no matter what security measures are undertaken, that a break-in will not occur but I can say quite confidently that with Home Minder installed and working, a break-in is far less likely when the house is unattended. With the music channel on as well, even in the early evening before lighting up time, the house would have the feeling of being occupied.

How It Is

The principle of operation is basically a crystal controlled clock that gives a pulse every minute. This is fed to a counter that recycles every 24 hours or 1440 minutes. From between 4pm and 9am, every minute can be individually programmed to switch up to seven different electrical circuits in any combination and in any order, the object being to switch lights on and off in a controlled manner to give the impression of someone being in. Here's the idea. The outside light comes on just before dusk, followed later by the front room light. Music can be switched on and off during the evening as can the bedroom and toilet lights. The music and front room lights are turned off first and the bedroom and toilet lights are turned on at bedtime. These are then turned off in due course imitating the normal routine of the house. These instructions as to which lights are on or off and when they are turned on and off are held in a program of an EPROM. The one used here is a 2716 - although small in capacity in modern terms of Megabits, its 2048 bytes are capable of storing two programs, one for winter, the other for summer, selected on a switch Summer/Winter.

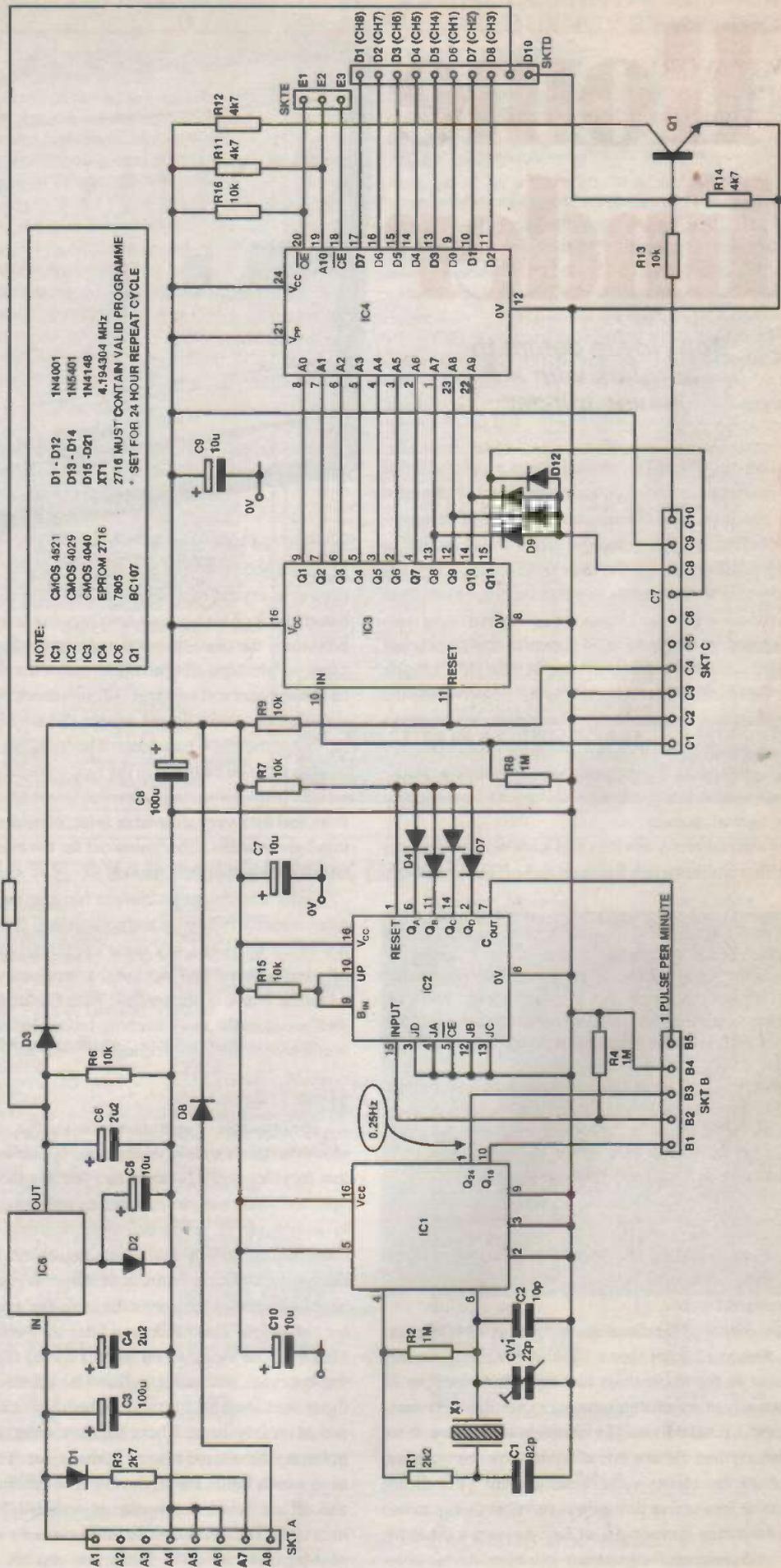


Fig.1 Main control board circuit

HOW IT WORKS

A crystal oscillator of 4.194304MHz is built around IC1, a CMOS 4521. This IC contains most of the oscillator circuit and the dividers necessary to produce a 0.25Hz output at pin 1, i.e. 4.194304MHz divided by 2 twenty-four times gives a frequency of 0.25Hz. Also Q18, a 16Hz signal is taken from pin 10 - this is used to test the program in fast mode (see later in the text). The 0.25Hz is normally connected to a divide by 15 circuit built around IC2, a CMOS 4029. The 4029 counts in binary and would normally reset at 16, but by the addition of D4, D5, D6, D7 and R7 it now resets at 15. The effect of a 0.25Hz signal divided by 15 is to produce a pulse every minute. This is taken from the carry out pin 7. None of the jam inputs are required so they are all grounded. The carry in pin 5 is always enabled so is grounded. A '1' on pin 10 causes it to count up, while a '1' on pin 9 makes the 4029 count in binary.

The pulse every minute is counted by IC3, a CMOS 4040, a 12 bit binary counter. Normally, this would count to 4096 before starting again from zero, but with the addition of D9, D10, D11, D12 and R9 it resets after 1440, the number of minutes in a day: $60 \times 24 = 1440$. This is done by taking

Q6	32 count	Pin 2
Q8	128 count	Pin 13
Q9	256 count	Pin 12
Q11	1024 count	Pin 15
=	1440 count	

and forming an AND gate, so when Q6, Q8, Q9, Q11 are all high, the reset goes high, via the pull up R9. The switch that connects the common point of the diodes to the reset should be of the normally closed type. In order to synchronise and zero at 4pm, the 'zero' switch is normally pressed at 4pm. Then, assuming the Home Minder is not turned off, the counter will recycle and zero at 4pm every day automatically - even if the outputs are disabled.

If the mains fails, the crystal oscillator and counters remain working via the battery back up. When the mains fails, the -15V stops causing the regulator to be starved of power. The 5V +0.7 due to D2 no longer appears at the output of the regulator. D8 now becomes forward biased allowing the battery supply 4.8 nominal voltage - 0.7 across D8 to supply the board and being CMOS, this is enough to maintain correct operation of the circuit. For the duration of the power failure, the EPROM is disabled via Q1 causing CE chip enable to be pulled high by R12, normally the 5.7V supply is used via R5, R13 to turn on Q1 keeping CE low and hence the EPROM working. Removing CE considerably reduces the power consumption while on battery back up, allowing for even the longest power cut not to affect the overall timing (of course the outputs will not operate, but with no mains the lights would not work anyway).

When a circuit containing a battery back up system is switched off deliberately, it must be remembered that not only the mains must be switched off, but the battery line must also be switched or all that will happen is that the batteries will take over and eventually run down because they are no longer being trickle charged.

The 2716 EPROM only has 2048 memory addresses and, as stated there are 1440 minutes in a day and two programs would normally require $1440 \times 2 = 2880$ addresses. This problem is overcome by not connecting A10 on the EPROM to the counter Q11, but to a 'Winter/Summer' switch. This means that addresses 0 - 1023 are used for the winter program and 1024 - 2047 for the summer program. The Q11 (1024) output from the counter IC3 is connected to the OE output enable of the EPROM. This means that from count 1024 to 1440, the outputs from the EPROM are disabled but as this happens at 9.04am, no lights would normally be on in either winter or summer, so this has no detrimental effect and allows a 2716 EPROM to be used. These are regarded as old hat nowadays and hence are inexpensive and quicker to program. A 2732 could have been used as it has 4096 addresses or memory locations, but the programs would have been twice as long, and for those people without an automatic EPROM programmer, it is a lot of switches to activate to make the program normally (4096×12 address $\times 8$ data combinations), as all the addresses should be programmed even if they are not used in the actual program.

When the Home Minder is not required on a day to day basis, the CE chip enable is used to disable the outputs but the counter and oscillator are kept running. To activate Home Minder, assuming it has been left on - i.e. zeroed at 4pm and left powered up, but disabled by the 'activate/deactivate' switch - just flick the switch to 'activate' and it's as simple as that. The outputs from the EPROM are now fed to the Darlington drivers in IC5 on the relay board between (4pm and 9am) which in turn switch the various circuits according to the program. The 'activate' switch can be switched on or off at any time, day or night. It has possibly crossed your mind as to why Home Minder is zeroed at 4pm. Well each of the two programs are 1023 minutes, long or 17 hours 3 minutes. In order to cover the evening, night and early morning for full winter coverage within this 17 hour band, all lights should be off by 9am so working back 17 hours comes to 4pm. In order to start the winter and summer programs at the same time, 4pm was chosen.

Channel 8 is used as a test signal, which flashes on for one minute every hour. If it comes on, on the hour you could never be sure which hour it was set to, because having a full clock display showing the time would have added to the complexity and cost when normally it is out of sight anyway. So, the test signal appears four minutes past four five minutes past five, six minutes past six and so on. so a simple check can be made that it is in step with the correct time. This test light does not work during 9am - 4pm because it works off Channel 8 which is disabled by OE after a count of 1024, but it is present between 4.04pm and 8.08am.

When 'Home Minder' has been on for several days it may be noticed that it is gaining or losing a few seconds a day. this can be confirmed by timing the test light from one day to the next using a good digital watch with a seconds display. Trimmer T1 on the oscillator can be adjusted to improve the accuracy. To start with, the trimmer is set to half way, at around 10p. This in parallel with the 10p C2 is the optimum value for the oscillator but a slight tweak may be necessary to improve matters.

Up to seven channels are programmable but without Channel 8 being used as the time test, this could be increased to 8. An extra relay is required and is connected like the others on the output of the Darlington driver pin 11. Diodes have been connected across the coils of the relays although this is not strictly needed because the Darlington drivers have built in diodes but too many precautions are better than too few.

In practice we have found six channels quite enough to simulate the average family house - with too many lights flashing it more resembles a Christmas tree than a house.

Relays were chosen as the output switching devices as these can switch any voltage AC or DC. Fuses are fitted as standard on all channels for safety.

Opto triacs controlling power triacs could have been used instead of relays, but this would require a different PCB. The

triacs should be fitted with small heatsinks. Isolated tab triacs should always be used as this reduces the amount of live metalwork, since the tab of a normal triac is connected to the output pin. Great care must be taken as they remain live at all times because power to them is brought in from the circuit being switched and not that supplied by the Home Minder via its mains supply. Fuses should still be used for ultimate safety on each channel, as for the relays.

Great care should also be taken when connecting up the outputs of the relays to the house lighting circuit. A diagram of a conventional lighting circuit is shown. This is a simple one switch circuit, the relay contacts are wired in parallel with the wall switch. Never get at the wires via the wall switch, always make the connections well out of the reach of everyone. Don't be surprised if the mains return is the side

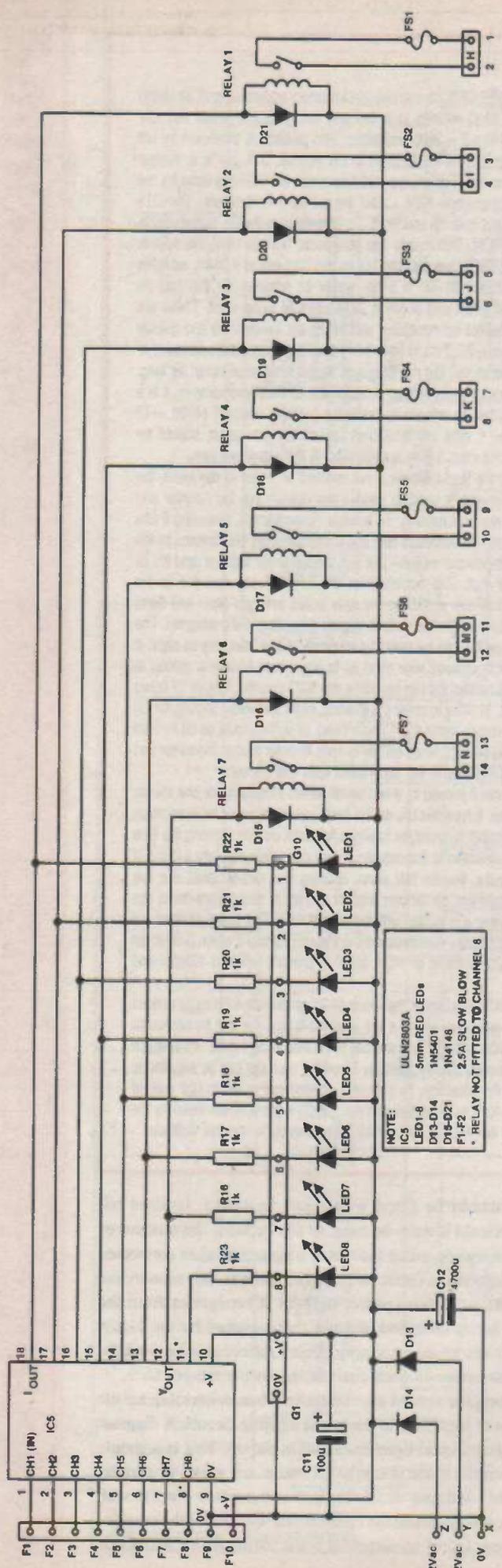


Fig.2 Relay Driver board circuit

that is switched. This is why a common live is not used in the circuit, but each output is completely independent of any of the others.

Again, it must be stressed that once connected the relay terminals and fuses remain live even if the Home Minder is unplugged from its mains supply, because the power is supplied all the time to the live side of the wall switch, or in our case, relay contacts. To connect into the lighting circuit, the mains master switch should be switched off - do not just remove the lighting fuse.

The relay contacts are intended to bypass the normal on/off switch on the wall to the light. They should not be used for two switch circuits normally found in halls/landings where the light can be turned on or off by either switch. There is no easy, safe way of connecting the relay contacts into this type of circuit (see diagram). In such cases another light should be wired up and run independently from the original light (as shown in the diagram). If you are in any doubt, contact a qualified electrician.

In our case, most of the wires were easily located in the loft for the upstairs and the front room was wired through a new cable to a wall socket which was activated by the relay, causing a standard lamp to come on.

Home Minder is mounted on the top shelf of the wardrobe and the wires connected up into the loft and on to the various lighting circuits. Each one was wired inside a covered 5A connector box - this means that there are no live wires exposed or odd pieces of connector block lying around in the loft. The connections that plug into the relay board are female types, so there are never live, unprotected pins. The pins are on the relay board (unpowered side) and even then, they are covered. Safety is vital in all aspects of mains wiring and no short cuts or economies with safety should ever be taken - if in any doubt at all seek expert advice.

When using Home Minder, neighbours and close trusted friends should be informed of its use if you're out or away, as they may call the Police thinking you have squatters - the effect is that real.

A full program listing is available for the running order to see if the program is suitable - even if it is not used in its entirety, at least it shows what is possible. The channels chosen - and their functions - can be changed to suit so long as the program is made accordingly. The music channel in our case switches a battery operated transistor radio tuned to Radio 2. It is not advisable to leave a television set running unattended and I would strongly dissuade anyone from doing so, although a mains radio would be OK.

A Test For Speed

From the interconnections diagram it can be seen that Q18 from the 4521 is brought out to a switch, 'Test/Normal'. This function allows the program to be run roughly sixty times faster than normal. The complete program can be run in this mode to test that everything is OK. It will show up things like all the channels coming on together because one location has not been programmed or if the EPROM is faulty. Although at this speed it still takes nearly half an hour to run a program, running it any faster it is hard to equate quite what is happening at any particular time. The Test/Normal switch can be mounted inside the Home Minder so that it's not accidentally switched during normal use. Once tested and proved OK, the zero button will still need to be pressed at 4pm because the counter will be out of step after running at

* SET TRIMMER CV1 TO MIDDLE TO START
THEN ADJUST TO CALIBRATE 24 HR CYCLE

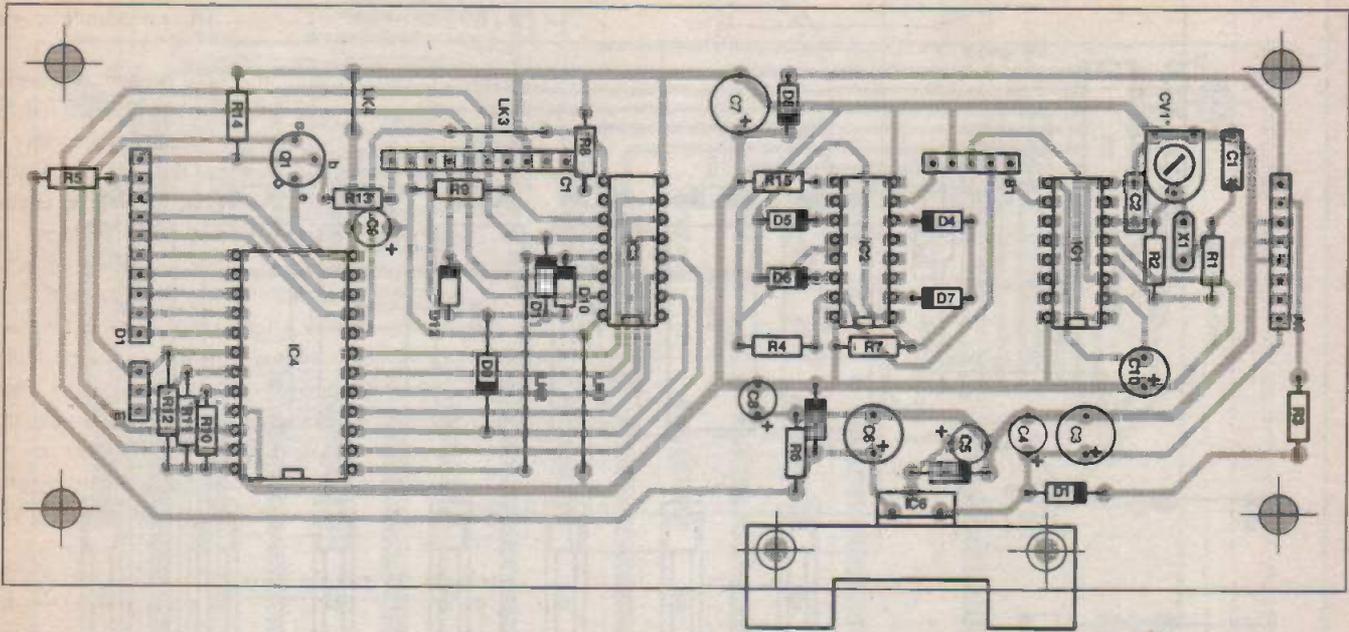


Fig.3 Component overlay for Main control board

the higher speed. The battery back up power switch can also be mounted inside the box so that it's not accidentally turned off.

Casing The Joints

Because of the physical size of this project, buying a suitable case to mount it in could cost a small fortune, so a home-made box was used instead. This was made out of 10-12 mm MDF (medium density fibreboard). It is a very easy material to work with as it has no grain or knots. Four pieces should be cut as per the drawing, although their exact sizes are not critical so long as they are compatible with each other and everything fits inside, leaving enough room for the wiring.

The front and back panels are made out of 16 swg aluminium sheet cut to size to fit inside the box, indented by 10mm to give a pleasing effect. They are mounted on a ledge of 12mm wide MDF - this, as well as forming a ledge front and back for mounting the panels, also adds to the strength of the box. All the MDF parts are glued using Evostik W resin glue rather than screws. This saves a lot of work filling over screw heads when finishing off. The front and back aluminium panels are drilled - a suggested front panel layout is given but this is not critical. The switch holes must suit the type of switches used, so only their centres are shown in the layout. Round hole mounted switches are a lot easier than oblong ones, unless you happen to have an oblong drill!

The panels can then be assembled and wired. A small bracket can be made to take the two internal switches ('Battery' and 'Fast/Normal') and should be mounted well away from the relay board so that the live mains on the fuses don't prove a problem if these switches are activated. It must be remembered that both the front and back panel must be earthed, as must the chassis of the mains transformer.

The PCBs are mounted on stand-off pillars. The main control board is screwed onto these pillars to lift the trackside of the board off the base of the case. Check that these screws


are not too long and don't come out through the bottom of the case. The transformer is screwed down - a small piece of MDF can be glued to the base of the box inside to mount the transformer, which will enable longer screws to be used for holding it down.

The relay board is bolted to the rear panel, again on stand-off pillars. These should be at least 10mm long to keep the live connections of the track side of the relay board well away

	Channel 8	Channel 7	Channel 6	Channel 5	Channel 4	Channel 3	Channel 2	Channel 1
EPROM Out function	D7	D6	D5	D4	D3	D2	D1	D0
EPROM Pin	17	16	15	14	13	11	10	9
Control Output Pin	D1	D2	D3	D4	D5	D6	D7	D8
Relay board Input pin	F8	F7	F6	F5	F4	F3	F2	F1
Relay No.	No Relay	7	6	5	4	3	2	1
Function	Time Test	Not used	Music	Toilet	Landing	Bedroom	Front room	Outside
Output pins		13 14	11 12	9 10	7 8	5 6	3 4	1 2
Darlington	8 11	7 12	5 13	5 14	4 15	3 16	2 17	1 18
LED Monitor	G3	G10	G9	G8	G7	G6	G5	G4

from the rear panel.

The PCBs should have been fully tested before they are mounted - so a final check can be made that the relays and LEDs come on as expected. Before the lighting connections are made, the master mains switch should be turned off. The cables that come in through the back panel should do so through grommets to protect them from the sharp metal edges of the rear panel. As each of the lighting wires is added, it should be clearly marked with a label. A drawing should also be made as to which fuse and relay switch is which. This is helpful in years to come if a fault should occur or modifications are made to the wiring of the house. So often, something that seems obvious at the time seems anything but much later. The unit is then left on for a few hours and tests made to check there is no heat build up. It is now ready to be zeroed

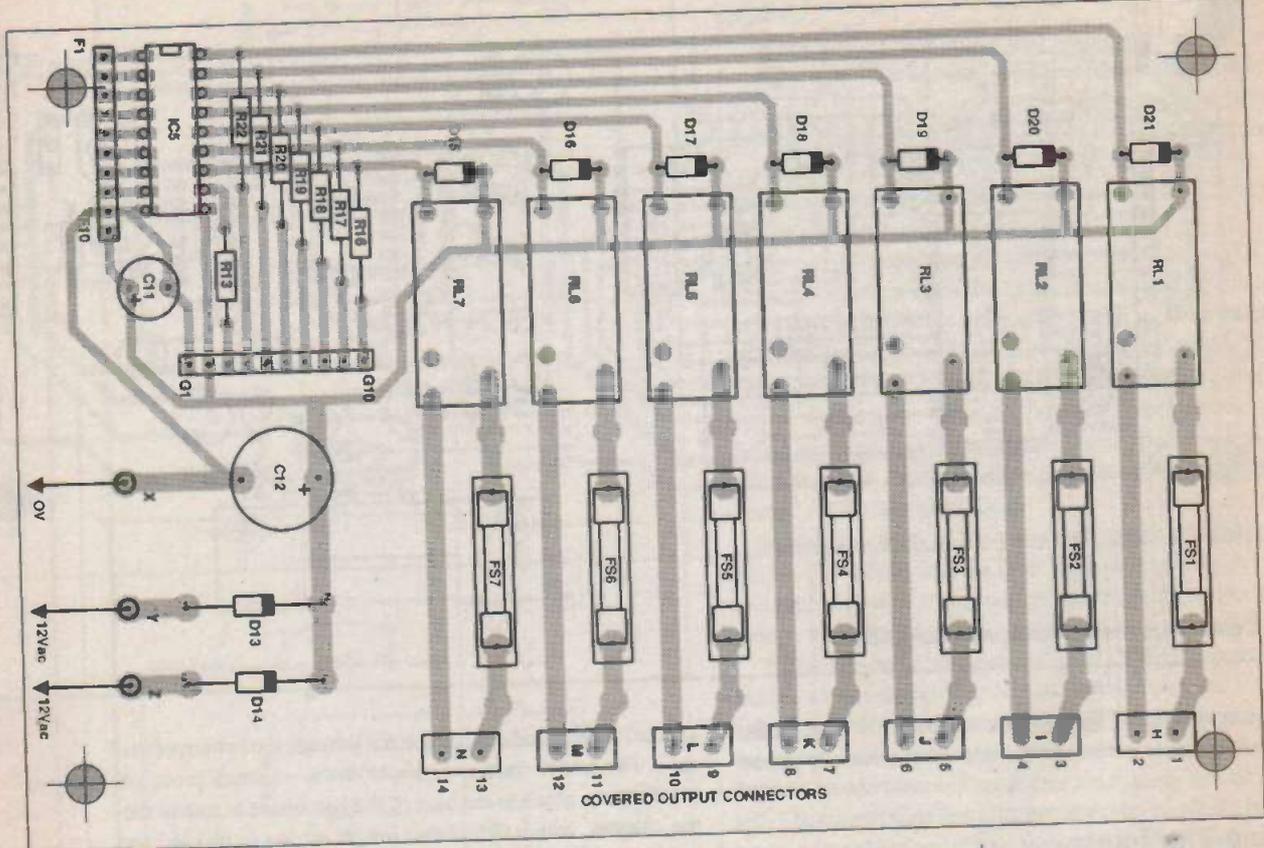

3.5mm FOR M3 MOUNTING BOLT

Fig.4 Component overlay for Relay board

	TIME TEST	NOT USED	MUSIC	TOILET	LANDING	BEDROOM	FRONT ROOM	OUTSIDE LIGHT	
EPROM FUNCTION	D7	D6	D5	D4	D3	D2	D1	D0	DATA CODE
CHANNEL	8	7	6	5	4	3	2	1	
BINARY No.	D	C	B	A	D	C	B	A	
	0	0	1	0	0	0	0	1	21
	0	1	0	1		1	1	1	57
	1	0	0	1	1	0	1	0	9A
	0	0	0	0	1	0	1	1	0B
	0	1	0	0	1	1	0	0	4C
	1	0	0	0	1	1	0	1	8D
	0	0	1	1	1	1	1	0	3E
	0	1	1	0	1	1	1	1	5F

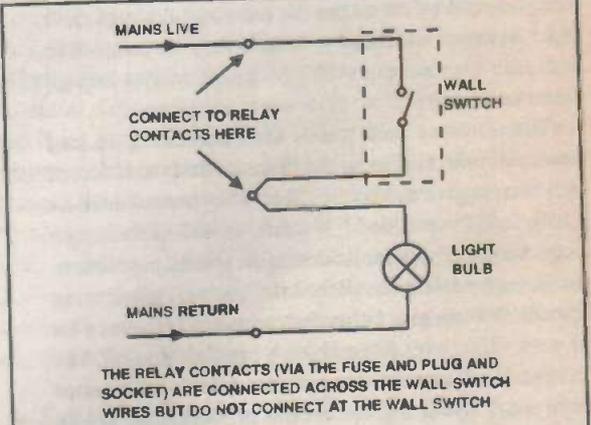


Fig.5 Mains lighting circuits

at 4pm and started using the 'Activate/Deactivate' switch.
Other Ideas


1. By connecting A10 of the EPROM to Q11 of the counter IC3 and disconnecting the connection from Q11 on the counter IC3 to the EPROM OE and grounding OE on the EPROM, one full 24 hour program can be run which recycles every 1440 minutes or 24 hours. This has been used in a toy shop window display, to switch on and off various electrical toys, including 3 electric trains in every combination. The zero button can be pressed at various times so that different parts of the program are played at different times during the day and evening when people are passing.

2. Another idea put forward but not tried is that the unit is used in fast speed, the Test rather than the Normal is

selected, and a robotic type toy can be programmed to move in time segments, i.e. 4 seconds forward, 2 seconds right, 7 left and so on. Here, the 16Hz divided by 15 gives slightly longer than one second time intervals, but by removing D4, D5, D6, D7, R7 and grounding pin 1 of IC2, IC2 now divides by 16. 16Hz from IC1 pin 10 divided by 16 in IC2 should produce a 1Hz pulse to the counter, advancing the program one step every second. The relay contacts are then used to switch the motors on the model causing it to follow the program.

By bringing out the major control signals to sockets, any number of options are available. Obviously, for both of these off shoot ideas, the program listing given will not be suitable.


PROJECT

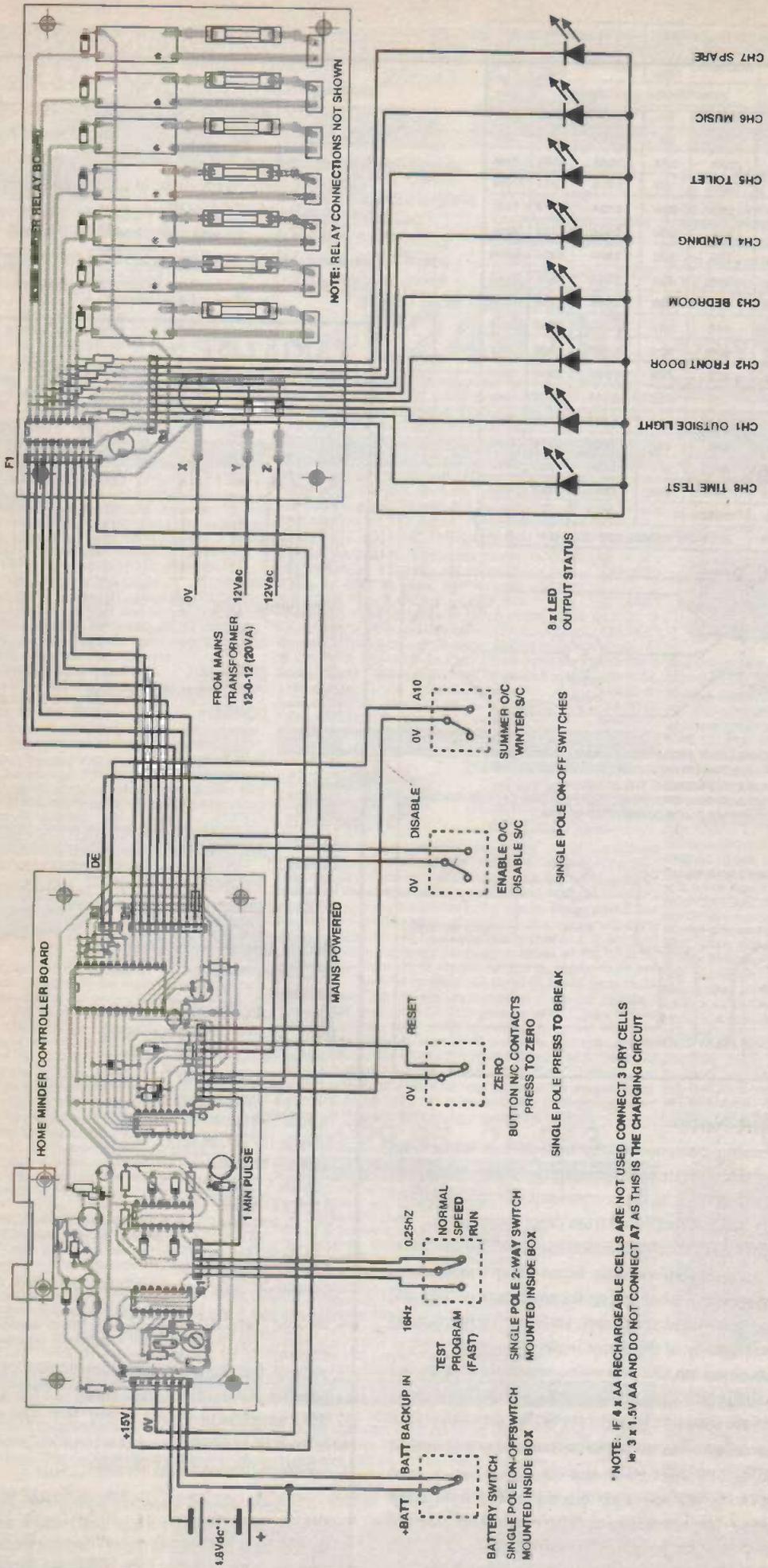

*NOTE: IF 4 x AA RECHARGEABLE CELLS ARE NOT USED CONNECT 3 DRY CELLS IN 3 x 1.5V AA AND DO NOT CONNECT A7 AS THIS IS THE CHARGING CIRCUIT

Fig.5 Board Interconnections

WINTER PROGRAM			SUMMER PROGRAM		
TIME	ADDRESS	TEST TIME	ADDRESS	TEST TIME	TIME
4pm	ZERO WINTER AND SUMMER				4pm
4pm	0	04	1024	1028	4pm
5pm	60	65	1084	1089	5pm
6pm	120	126	1144	1150	6pm
7pm	180	187	1204	1211	7pm
8pm	240	248	1264	1272	8pm
9pm	300	309	1324	1333	9pm
10pm	360	370	1384	1394	10pm
11pm	420	431	1444	1455	11pm
12pm	480	492	1504	1516	12pm
1am	540	541	1564	1565	1am
2am	600	602	1624	1626	2am
3am	660	663	1684	1687	3am
4am	720	724	1744	1748	4am
5am	780	785	1804	1809	5am
6am	840	848	1864	1870	6am
7am	900	907	1924	1931	7am
8am	960	968	1984	1992	8am
9am	1020	*	2044	*	9am
9.04	OUTPUTS TURNED OFF TILL 4AM				9.04

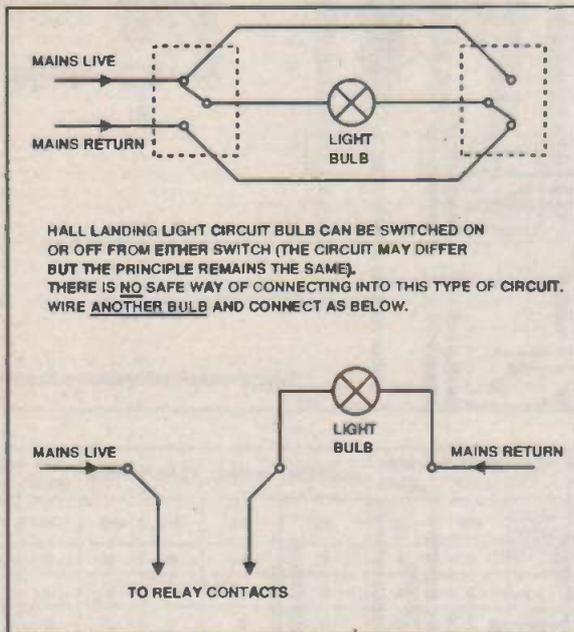

Important Note

When buying components for this project it must be remembered that this circuit may well be switched on and left on for a very long time, so the components used should be of good quality and not reclaimed from other projects.

The mains transformer and smoothing capacitor should be new and from a reputable source. Some cheap transformers can get extremely hot when left on for any length of time and these should be avoided at all costs. Only use known dealers and suppliers for any of the major items.

The relays used are 12V coil with contacts that can switch 10A with a single pole change over contacts from Electromail. If any others are used it will pay to check that they fit the PCB before buying them. Several look the same but closer inspection shows their pin outs differ slightly.

The value of the fuses depends upon the circuit being switched, but 2.5A slow blow 1-1/4in should be sufficient in most cases. A slow blow type is recommended as there is an initial current surge when a light bulb is illuminated.

I can supply pre-recorded 2716 EPROMs with the sum-

mer and winter programs for £17.50 including postage and packing, but payment must be with order and in the form of a postal order or cheque made payable to Bob Noyes at the address below. Custom programs can be made, but their cost depends upon complexity, so write giving the listings and I can quote a price. Write to me at 13 Bowfell Close, Tilehurst, Reading, Berks. RG3 6QR.

A list of programming Hex codes for Summer and Winter are available by sending an SAE to the editor at the ETI offices.

PARTS LIST

RESISTORS

R1 2k2
R2 1M8
R3 2k7
R4,8 1M
R5,11,12,14 4k7
R6,7,9 10k
R10,13,15 10k
R16,17,18,19 1k
R20,21,22,23 1k

CAPACITORS

C1 82p
C2 10p
C3,8,11 100µ25V
C4,6 2µ2/25V
C5,7,9,10 10µ25V
C12 4700µ25V

SEMICONDUCTORS

IC1 4521
IC2 4029
IC3 4040
IC4 2716 Programmed EPROM
IC5 2803A
Q1 BC107
REG1 7805
D1,2,3,8 1N4001
D4,5,6,7,9 10,11,12 15,16,17 18,19,20,21 1N4148
D13,14 1N5401
8 0.2in Red LEDs

MISCELLANEOUS

7 PCB straight headers 0.1in 10 way
7 Housings for above
1 pack of crimps for housings
Mains connector plugs on relay board
7 Horizontal PCB headers - 2 way
7 plugs for above - 2 way
7 Fuses 1 1/4in 2.5A slow blow
14 Fuse PCB holders (one each end)
7 Relays 12V DC coil SPCD
1 22p min trimmer
1 crystal 4.194304MHz
1 18 pin IC holder
1 16 pin IC holder
1 24 pin holder
1 Box to suit application
3 Single pole on/off switches, style to suit
1 Single pole 2 way switches, style to suit
1 Press button N/C contacts, style to suit
1 12-0-12V 20 VA transformer
2 PCB 1 x Main board, 1 x Relay board
4 1.2V AA rechargeable Ni cad batteries
1 4AA battery holder
1 Connector for above
8 Stand-off pillars to suit, 10 mm long

Enclosed electrical connectors (lighting style), number to suit
Wire, mains plug, cable to suit application Heatsink, see layout. Size unimportant as 7805 does not get hot - used as a precaution - but the larger the better so long as it can be mounted securely.


Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

LOW COST PC SPECIALISTS - ALL EXPANDABLE - ALL PC COMPATIBLE

8088 XT - PC99

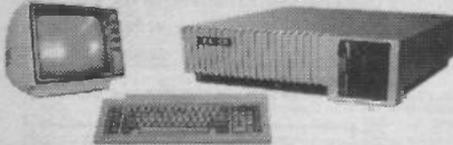

- 256k RAM - expandable to 640k
- 4.7 Mhz speed
- 360k 5-1/4" floppy
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Factory burnt-in
- Standard 84 key keyboard
- 12" green screen included
- In good used condition

Optional FITTED extras: 640K RAM £39. 12" CGA colour monitor with card £39. 2nd 5-1/4" 360K floppy £29.95. 20 mbyte MFM hard drive £99.

Only **£99.00** (F)

286 AT - PC286



- 640k RAM expandable with standard SIMMS
- 12 Mhz Landmark speed
- 20 meg hard disk
- 1.2 meg 5-1/4" floppy
- 1.4 meg 3-1/2" floppy
- EGA driver on board
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 key keyboard
- Clock & calendar with battery back up

BRAND NEW AND BOXED!

Only **£249.00** (F)

The Philips 9CM073 is suggested for the PC286 and the CMB873 for the PC386. Either may use the SVGA MTS-9600 if a suitable card is installed. We can fit this at a cost of £49.00 for the PC286 and £39.00 for the PC386.

386 AT - PC386




- 2 meg RAM expanded by slots
- 20 Mhz with 32k cache. Expandable to 64k
- 40 meg hard disk
- 1.2 meg 5-1/4" floppy
- VGA card installed
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 keyboard
- Kwik Disk Accelerator Software - FREE

BRAND NEW AND BOXED!

Only **£425.00** (F)

MONITORS

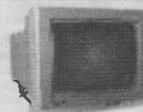

14" Forefront Model MTS-9600 SVGA multisync with resolution of 1024 x 768. 0.28 pitch. "Text" switch for word processing etc. Overscan switch included. Ideal for the PC-386 or PC-286 with SVGA card added. Also compatible with BBC, Amiga, Atari (including the monochrome high resolution mode), Archimedes etc. In good used condition (possible minor screen burns). 90 day guarantee. 15" x 14" x 12". Only **£159(E)**



14" Philips Model CM8873 VGA multisync with 640 x 480 resolution. CGA, EGA or VGA, digital/analog, switch selectable. Special "Text" switch for word processing, spreadsheets and the like. Compatible with IBM PCs, Amiga, Atari (excluding the monochrome high resolution mode), BBC, Archimedes etc. Good used condition (possible minor screen burns) 90 day guarantee. 15" x 14" x 12". Only **£139(E)**

Philips 9CM073 similar (not identical) to above for EGA/CGA PC and compats. 640 x 350 resolution. With Text switch with amber or green screen selection. 14" x 12" x 13-1/2". **£99(E)**

KME 10" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acom Archimedes & BBC. Measures only 13.5" x 12" x 11". Also works as quality TV with our HiB Telebox. Good used condition. 90 day guarantee. Only **£125 (E)**

KME as above for PC EGA standard **£145 (E)**
Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only **£129 (E)**

NEC CGA 12" IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. The front cosmetic bezel has been removed for contractual **£69 (E)** reasons. Only **£129 (E)**

20", 22" and 26" AV SPECIALS
Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee. 20"....**£135** 22"....**£155** 26"....**£185 (F)**

CALL FOR PRICING ON NTSC VERSIONS!

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart!

Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2" H x 32-1/2" D x 22" W. Order as:

Rack 1 Complete with removable side panels....**£275.00 (G)**

Rack 2 Less side panels **£145.00 (G)**

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. **£85.00 (B)**

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A ± 12v @ 1.5A. Switch mode. New. **£59.95(B)**

Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New **£22.95(B)**

Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cm. **£24.95(C)**

Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cm. New. **£49.95(C)**

Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a. +12v @ 2.5a. -12v @ 0.5a. -5v @ 0.5a. **£29.95(B)**

Farnell G6/40A. Switch mode. 5v @ 40a. Encased **£95.00(C)**

Farnell G24/5S. As above but 24v @ 5a. **£65.00(C)**

BBC Model B APM Board

WIN £100 CASH!

£100 CASH FOR THE MOST NOVEL DEMONSTRABLE APPLICATION!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board!! It is supplied complete with a connector panel which brings all the I/O to "D" and BNC type connectors - all you have to do is provide +5 and +12 v DC. The APM consists of a single PCB with most major ic's socketed. The ic's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only **£29.95** or 2 for **£53 (B)**

SPECIAL INTEREST

Trio 0-18 vdc bench PSU. 30 amps. New **£ 470**

Fujitsu M3041 600 LPM band printer **£2950**

DEC LS/02 CPU board **£ 150**

Rhode & Schwarz SBUF TV test transmitter **£6500**

25-100mhz. Complete with SBT/P2 Modulator **£ 650**

Calcomp 1036 large drum 3 pen plotter **£ 375**

Thurby LA 160B logic analyser **£ 950**

1.5kw 115v 60hz power source **POA**

Anton Pillar 400 Hz 3 phase frequency converter 75Kw **POA**

Newton Derby 400 Hz 70 Kw converter **POA**

Nikon PL-2 Projection lens meter/scope **£750**

Sekonic SD 150H 18 channel H/V recorder **£2000**

HP 7580A A1 8 pen high speed drum plotter **£1850**

Kenwood DA-3501 CD tester, laser pickup simulator **£ 350**

BRAND NEW PRINTERS

Microline 183. NLQ 17x17 dot matrix. Full width. **£139 (D)**

Hyundai HDP-920. NLQ 24x18 dot matrix full width. **£149 (D)**

Qume LetterPro 20 daisy. Qume QS-3 interface. **£39.95 (D)**

Centronics 152-2 9 x 7 dot matrix. Full width. **£149 (D)**

Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width **£ 99 (D)**

FLOPPY DISK DRIVES

5 1/4" from **£22.95** - 3 1/2" from **£21.95!**

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

3.5" Panasonic JU363/4 720K or equivalent **£29.95(B)**

3.5" Mitsubishi MF355C-L. 1.4 Meg. Laptops only **£29.95(B)**

3.5" Mitsubishi MF355C-D. 1.4 Meg. Non laptop **£29.95(B)**

5.25" EXTRA SPECIAL BRAND NEW Mitsubishi MF501B **£22.95(B)**

360K. Absolutely standard fits most computers **£22.95(B)**

* Data cable included in price.

Shugart 800/801 SS refurbished & tested **£175.00(E)**

Shugart 851 double sided refurbished & tested **£275.00(E)**

Mitsubishi M2894-63 double sided switchable hard or soft sectors. BRAND NEW **£250.00(E)**

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! **£499.00(F)**

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra high speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only **£299(E)**

THE AMAZING TELEBOX!

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

Telebox ST for composite video input monitors **£32.95**

Telebox STL as ST but with integral speaker **£36.50**

Telebox MB as ST with Multiband tuner VHF-UHF-Cable, & hyperband For overseas PAL versions state 5.5 or 6mhz sound specification. **£69.95**

Telebox RGB for analogue RGB monitors (15khz) **£69.95**

Shipping code on all Teleboxes is (B)

RGB Telebox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM/NTSC not available.

No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBB is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals. MUK....**£249 (F)** MUD....**£525 (G)**

1992 Winter Issue of Display News now available - send large SAE - PACKED with bargains!

DISPLAY

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET.32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP
Open Mon-Sat 9-5.30
Thursday till 9.00pm
215 Whitehorse Lane,
South Norwood,
London. SE25.

DISTEL © The Original
Free dial-up database!
1000's of items+info on line
V21. V22 & V22 bis
081-679-1888

ALL ENQUIRIES
081-679-4414
Fax: 081-679-1927



-ELECTRONICS-

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome-minimum account order £30. Carriage charges (A)=£2.00, (A1)=£3.75, (B)=£5.50, (C)=£8.50, (D)=£11.50, (E)=£14.00, (F)=£18.00 (G)=Call. Scotland surcharge: call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.

LEDs 3mm or 5mm red or green 6p each, yellow 11p each. High intensity red, green or yellow, 5mm 30p each.
 Cable ties 1p each. £8.95 per 1000, £49.50 per 10,000.
 Stepping motor 4 phase 12V 7.5' step
 50 ohms £8.95
 SAA1027 stepping motor driver chip £8.95
 FM Transmitter kit, good quality sound £8.80

High quality photo resist copper clad epoxy glass boards

Dimensions	single sided	double sided
3x4 inches	£0.95	£1.07
4x6 inches	£2.40	£2.48
6x12 inches	£8.37	
12x12 inches	£10.86	

Rechargeable Batteries

AA (HP7) 500mAh £0.99
 AA 700mAh £1.95
 C 2Ah with solder tags £3.80
 D 4Ah with solder tags £4.95
 1/2AA with solder tags £1.85
 AAA (HP16) 180mAh £1.75
 AA 500mAh with solder tags £1.55
 C (HP11) 1.8Ah £2.20
 D (HP2) 1.2Ah £2.60
 PP3 8.4V 110mAh £4.95
 1/3 C with solder tags £2.50
 1/3 AA with tags (Philips CTV) £1.95

Standard charger, charges 4 AA cells in 5 hours or 4 Cs or 4 Ds in 12-14 hours + 1x PP3 (1, 2, 3 or 4 cells may be charged at a time) £6.95

High power charger, as above but charges the Cs and Ds in 5 hours. AAs, Cs and Ds must be charged in 2s or 4s. £10.95

Special offers - please check for availability

F cells 32dia x 87mm £3.95
 F cell with solder tags 1.2V £4.30
 42mm x 16mm dia 1.2V £1.45
 Stick of 4 171mm x 16mm dia, with red & black leads 4.8V £5.95
 4 cell battery 94mm x 25mm dia (1/2C cells) £3.50

Computer grade capacitors with screw terminals.
 3800uF 20V £2.60; 87000uF 10V £1.95;
 68000uF 15V £2.95; 10000uF 16V £1.50

7 segment common anode led display, 12mm £0.45
 LM2931 AT 5.0 low drop out 5V regulator TO220 package £0.85
 7812 and 7912 1A regulators £20.00 per 100
 LM337E TO3 case variable regulator £1.60
 100+ £1.10
 BS256 P channel mosfet 45p, BC559 transistor per 100 £3.95
 74LS05 hex inverter £10.00 per 100
 Used 8748 Microcontroller £3.50
 SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet £1.95
 AN27502 £1.28 each, 90c 100+
 CD4067 US 10p 100+ 3p 1000+
 TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.95
 box of 50 £19.95

DC-DC converter, Reliability model, V12PS, 12V in 5V 200mA out, 300V input to output, isolation with data, £4.95 each or pack of 10 - £39.50
 Hour counter using 7 digit 240V ac 50Hz... £1.45
 Resistor pack 2500 resistors 1/8-2W 50 different values £8.95

Resistor jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be mainly in boxes or rolls of 1000, 2000 and 5000 of one type. £25.00
 Qwerty keyboard 58 key good quality switches new £8.00
 Qwerty keyboard with serial output, no data (used) £6.00

Polyester capacitors, box type, 22 5mm lead pitch 1uF 250V dc 20p each, 15p 100+ , 10p 1000+ 2.2uF 250V dc 30p each, 20p 100+ , 15p 1000+ 3.3uF 100V dc 30p each, 20p 100+ , 15p 1000+ 1uF 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000+ 0.22uF 250V polyester axial leads, 15p each, 100+ 7.5p each, 33uF 10V & 2.2uF 40V 40p each, 25p 100+ Multilayer AVX ceramic capacitors, all 5mm pitch 100V 100pF, 150pF, 220pF, 10,000pF (10n) 10p each, 5p 100+ , 3.5p 1000+ Welwyn W23 9W 120 ohm 35p each, 20p 100+ 880 ohm 2W metal film resistor, 4p 100+ , 2p 1000+ Solid carbon resistors, very low inductance, ideal for RF circuits, 27ohm 2W, 68ohm 2W 25p each, 15p each 100+ , we have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list

Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package, Siemens type DLRT1414 £2.50 each, £2.00 30+ data sheets £1.00

AMD 27256-3 Eproms £2.00 each, £1.25 100+ DIP switch 3PCD 12 pin (ERG SDC-3-023) 60p each, 40p 100+

Disk Drive Boxes for 5.25 disk drive with room for a power supply light grey plastic 87x268x247mm £7.95 or £49.50 for 10

Hand Held Ultrasonic remote control £3.95

Computer grade 5800uF 60V capacitors with screw terminals £4.95

CY 2488 gas relay 30mm x 10mm dia with 3 wire terminals will also work as a neon light 20p each £7.50 per 100

A23 12v car alarm remote control and lighter battery 75p each £50.00 100+ 40 of 370vac motor start capacitor (dielectric type containing no PCBs) £5.95 each £49.50 for 10.

All products advertised are new and unused unless otherwise stated.

Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc. always in stock

Please add 96p towards P&P VAT included in all prices

JPG ELECTRONICS
 276-278 Chatsworth Road
 Chesterfield S40 2BH
 Access Visa Orders.
 (0246) 211202
 Callers welcome

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES Dual Trace Plug-in with TB from £200 Many Plug-in options available. 4 Trace Differential etc.
 PLUC-INS SOLD SEPARATELY

PHILIPS 3065 2 - 1 Channels 100 MHz Delay Sweep £700
 KIKUSUI COS6100M 3 Channel CH4/CH5 Trig View 100 MHz Delay Sweep £600
 TEKTRONIX 475 Dual Trace 200 MHz Delay Sweep £550
 H.P. 1715A Dual Trace 200 MHz Delay Sweep £500
 H.P. 1740A Dual Trace 100 MHz Delay Sweep £450
 HITACHI V625 Dual Trace 50 MHz CAT Readout/Cursors £475
 PHILIPS PM327 Dual Trace 50 MHz Delay Sweep £400
 HITACHI V422 Dual Trace 40 MHz £325
 GOULD OS30000A Dual Trace 40 MHz Delay Sweep £200
 KIKUSUI 5530 Dual Trace 35 MHz £180
 GOULD OS1100 Dual Trace 30 MHz £160
 GOULD OS300 Dual Trace 20 MHz £130
 GOULD OS2500 Dual Trace 15 MHz £125

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

PHILIPS PM5193 Programmable synthesizer/Function Generator 0.1MHz - 50MHz IEEE-488. As new £1500

MARCONI 2019 Synthesized AM/FM Sig Gen 80KHz-100MHz £2000
 MARCONI 2022 AM/FM Sig Gen 10KHz-1GHz £1200
 MARCONI 2018 Synthesized AM/FM Sig Gen 80KHz-500MHz £950
 RACAL 5081 Synthesized AM/FM Sig Gen 1.5 - 520 MHz £600
 FARNELL PS6520H Synthesized AM/FM Sig Gen 100KHz - 520 MHz £600

LEADER LSG216 AM/FM Sig Gen 2 ranges 0.1 - 3.0MHz & 75 - 115 MHz £400
 MARCONI TF2015 AM/FM Sig Gen 10 - 520 MHz £200
 MARCONI TF2016 AM/FM Sig Gen 10 KHz - 120 MHz £175
 MARCONI TF2016 with Synchronizer TF2173 (Lock box) £300
 RACAL 9001A True RMS Millivoltmeter 10KHz-1GHz £300
 KIKUSUI AVM23 AC Voltmeter Dual Channel 10Hz-500KHz, 300V-100V £100
 LEADER LMV181A AC Millivoltmeter
 5Hz-1MHz, 100V-300V £75
 MARCONI TF2600 AC Millivoltmeter 10Hz-10MHz 1mV-300V FSD £80
 H.P. 8008A Pulse Gen 10Hz - 200MHz Variable Rep rate
 H.P. 8011A Pulse Gen 0.1Hz - 20 MHz Pos/Neg/Sym output £200
 LYONS 2PFG3N Pulse Gen PRF 1Hz - 20MHz £150

SPECTRUM ANALYSERS

HP 141T with 8554A & IF plug-in 10MHz - 18GHz £1800
 HP 141T with 8554B & 8552B 500KHz - 1250MHz £1300
 HP 140T with 8554A & 8552A 500KHz - 1250MHz £1000
 HP 141T with 8556A & 8552B 20Hz - 300KHz £1000
 HP 140T with 8553B & 8552A 180KHz - 110MHz £800
 MARCONI TF2370 - 110MHz £1500
 HP 182c with 8558 100KHz - 1500MHz £1500
 HP 3582A 0.02Hz - 25 KHz £2000

DATRON 1081A - Multimeter £1250
 8 1/2 digit True RMS AC/Current £1500
 DATRON 1085 - Multimeter 5 1/2 digit AC/DC/Ohms IEEE 488 HEWLETT PACKARD 3490A Bench Multimeter 5 1/2 digit AC/DC/Ohms £200
 PHILIPS PM2534 Multifunction DMM 8 1/2 digit GPB/IEEE £450
 MARCONI Digital Frequency Meter 2430 10Hz-100MHz £125
 MARCONI Digital Frequency Meter 2431A 10Hz-200MHz £150
 MARCONI Universal Counter Timer 2437 DC-100MHz £175
 MARCONI Universal Counter Timer 2438 DC-520MHz £225
 HP 3311A Function Generator 0.1Hz-1MHz Sine/Sq/Tri £125
 BLACK STAR Jupiter 500 Sine/Sq/Tri 0.1Hz - 500KHz £70
 FEEDBACK FG8000 Sine/Sq/Tri 0.1Hz - 100KHz £160
 MULTIMETER HAND HELD ME585-32 ranges AC/DC 10 Amps Diode/Transistor Tester, Func counter £32.50

FARNELL ELECTRONIC LOAD R81030-35
 1KW 30Amp 35 Volt £600

HP 8608 Sweep Osc with 66974 Plug-in, 26.5-40GHz £300
 RACAL/DANA RF Power Meter P140 £400
 RACAL/DANA 3341 Calibrator, Automatic LCR, 8.0 £350
 WAYNE KERR 8905 Automatic Precision Bridge 0.05% £800
 WAYNE KERR 8505 Automatic Component Bridge 0.1% £350
 WAYNE KERR 8424 Digital Component Tester LCR £125
 FARNELL PSU TV5700M2 0-70V 5A; 0-30V 10A £300
 FARNELL PSU H8025 0-60V; 0-25Amps Metered £600
 FARNELL PSU L30E 0-30V; 0-5Amps Metered £280
 FARNELL B3010 0-30V, 20Amps £250
 FARNELL B3010 0-30V, 10Amps £200
 H.P. 6255A 0-40V; 0-1.5Amps Terica £130
 H.P. 6205B 0-320V; 0.0-1Amps Metered £125
 FARNELL TF2700 Universal LCR Bridge, Battery from £150
 AVO Value Characteristic Meter VCM163 £300
 FARNELL LA500 RF Power Amp, 1.5-520MHz 300mW £175
 RACAL 9100 Absorption Wattmeter 1MHz-1GHz, 3W £100

FARNELL ISOLATING TRANSFORMERS
 GU500 240V 500VA un-used £50

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM 1005 Triple Trace 100MHz Delay Timebase £847
 HAMEG OSCILLOSCOPE HM 604 Dual Trace 80MHz Delay Sweep £853
 HAMEG OSCILLOSCOPE HM203 7 Dual Trace 20MHz Component Tester £382
 HAMEG OSCILLOSCOPE HM205 8 Dual Trace 20MHz Digital Storage £863
 All other models available - all oscilloscopes supplied with 2 probes

BLACK STAR EQUIPMENT (pAp all units £5)

APOLLO 10-100MHz Counter Timer Ratio/Period/Time interval etc £222
 APOLLO 100 - 100MHz (As above with more functions) £325
 METEOR 100 FREQUENCY COUNTER 100MHz £109
 METEOR 600 FREQUENCY COUNTER 600MHz £135
 METEOR 1000 FREQUENCY COUNTER 1GHz £179
 JUPITOR 500 FUNCTION GENERATOR 0.1Hz-500Hz Sine/Sq/Tri £110
 ORION COLOUR BAR GENERATOR PAL/TV/Video £220
 All other Black Star Equipment available

OSCILLOSCOPE PROBES Switchable x1: x10 (P&P £5)

Used Equipment - Guaranteed. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIA GE all units £18. VAT to be added to total of Goods and Carriage.

STEWART OF READING
 110 WYKHAM ROAD, READING, BERKS RG6 1PL
 Tel: (0734) 268041 Fax: (0734) 351606. Callers welcome 9am-5.30pm Mon-Fri (until 6pm Thurs).

READER OFFER

Needle Files


10 assorted *English made Needle Files in a variety of useful shapes.

The ideal tools for putting those finishing touches to a wide range of materials.

Telephone orders 0442 66551 (24 HRS)

*assorted not always as shown on photograph.

Only £6.50 inc p&p

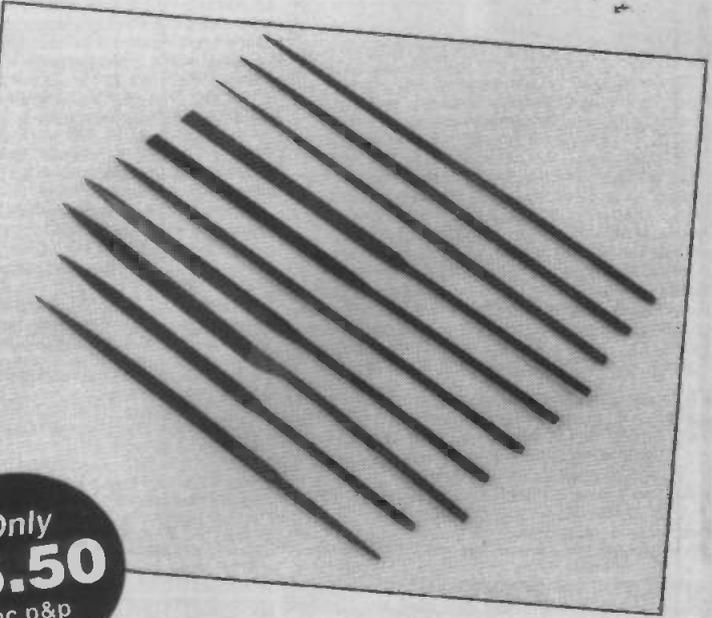

Please supply.....ROET/29 @ £6.50

I enclose my cheque / P.O. for £.....payable to ASP or please debit my Access / Visa

Signature.....Expiry.....

Name.....

Address.....

Post Code:.....

Please allow 28 days for delivery U.K. only. Overseas upon request. Coupon to: ASP Reader Offers, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST. Please note the above information may be used for marketing purposes.

Don't miss the
**NATIONAL
WOODWORKER
SHOW**

**SANDOWN
EXHIBITION CENTRE**
**23rd - 26th
SEPTEMBER 1993**

EASY TO FIND!

**SANDOWN EXHIBITION
CENTRE, ESHER SURREY**

- Free car parking ● Easy access
- Within easy reach of London
- Well sign posted for motorists

By car; Sandown is just 15 minutes from the M25 (junction 10) and national motorway network, 35 minutes from central London and 30 minutes from Heathrow or Gatwick.

By rail; British Rail's Esher station from Waterloo is in the immediate vicinity. Trains journey time just 21 minutes - run at least every half hour, more frequently at peak times.

Bus services run regularly from central London and neighbouring towns of Guildford and Kingston-upon-Thames.

**Come one, come all -
to the National
Woodworker Show!**

You'll be amazed at the artistry - the craftsmanship - the labour of love represented by the wide range of exhibits on show at Sandown this year. There will be competitions, demonstrations, displays by colleges, trade stands - and much, much more. Sandown Exhibition Centre is easy to get to - and car parking is free! Come early - stay late!



Admission prices

Adults: £5
Senior citizens: £3.50
Children: 5-16 years £2.

Opening times

10am-6pm daily except Sun. 26th, 10am-5pm

Further information from Argus Specialist Exhibitions,
Argus House, Boundary Way, Hemel Hempstead,
Herts HP2 7ST Tel: 0442 66551

ADVANCE TICKET DISCOUNT

Use this coupon to save money when you buy tickets in advance!

	Standard Entrance	Advance Discount	No. of tickets
Adults	£5	£4.50
Senior Citizens	£3.50	£3
Children (5-16 years)	£2	£1.50

Cheque enclosed for £..... made payable to Argus Specialist Exhibitions

NAME.....

ADDRESS.....

POST CODE.....

Complete coupon and return to Argus Specialist Exhibitions (AT),
Argus House, Boundary Way, Hemel Hempstead, HERTS HP2 7ST
There is no limit to the number of tickets you may order. Special rates for coach parties available on request. Hurry! Offer closes on Tuesday 1st September.

Competition entry form

If woodworking is your skill, why not enter an exhibit in the National Woodworker Show competition? Complete this coupon to receive details and entry form (one per exhibit) and send to Argus Specialist Exhibitions at the address shown in advance tickets coupon on left.

NAME.....

ADDRESS.....

POST CODE.....

Closing dates for entry: 5th July for show catalogue entry.
FINAL CLOSING DATE 30th August

ESR ELECTRONIC COMPONENTS

Station Road, Cullercoats,

Tyne & Wear NE30 4PQ


Tel. 091 251 4363

Fax. 091 252 2296


74LS Series		4000 Series		TRANSISTORS				LINEAR ICs				SOLDERING IRONS				RF CONNECTORS			
74LS00	£0.14	4000	£0.17	2N1613	£0.31	BC186	£0.33	BD534	£0.47	CA311E	£0.28	Antex Soldering Irons				BNC Solder Plug 50R			
74LS01	£0.14	4001	£0.17	2N1711	£1.28	BC204C	£0.72	BD536	£0.48	CA324	£0.23	M 12 Watt	£0.18	BC Solder Plug 75R	£0.96	BNC Crimp Plug 50R			
74LS02	£0.14	4002	£0.17	2N1893	£0.28	BC208B	£0.72	BD536	£0.65	CA355	£0.22	C 15Watt	£7.87	BNC Solder Plug 75R	£0.68	BNC Crimp Plug 75R			
74LS03	£0.14	4006	£0.32	2N2218A	£0.28	BC207C	£0.72	BD648	£0.52	CA741CE	£0.18	G 18Watt	£8.41	BNC Crimp Plug 50R	£0.88	BNC Solder Skt			
74LS04	£0.14	4007	£0.17	2N2219A	£0.25	BC208	£0.72	BD648	£0.52	CA747CE	£0.39	CS 17Watt	£8.31	BNC Solder Skt	£1.06	BNC Chassis Skt			
74LS05	£0.14	4008	£0.31	2N2222A	£0.18	BC209A	£0.72	BD650	£0.53	CA3046	£0.37	XS 26Watt	£8.41	BNC Chassis Skt	£0.80	PL259 5.2mm			
74LS08	£0.14	4009	£0.19	2N2646	£0.80	BC212	£0.08	BD707	£0.42	CA3080	£0.72	ST4 Stand	£2.97	BNC Solder Skt	£0.68	PL259 11mm			
74LS09	£0.14	4010	£0.23	2N2904A	£0.25	BC212L	£0.98	BD907	£0.80	CA3130	£0.98	35Watt Gas Iron	£11.56	RND UHF socket	£0.82	SQR UHF socket			
74LS10	£0.14	4011	£0.16	2N2905A	£0.23	BC212BL	£0.08	BD932	£1.78	CA3130E	£0.98	Gasert Gas Iron	£15.26	RND UHF socket	£0.62	F Plug RGB			
74LS107	£0.23	4012	£0.16	2N2907	£0.20	BC213	£0.08	BD932C	£0.49	CA3140	£0.56	Low Cost 15 Watt Iron	£3.93	F Plug RGB	£1.60	N Socket RGB			
74LS109	£0.21	4013	£0.17	2N2926	£0.16	BC213CL	£0.08	BD933C	£0.50	CA3240	£1.20	Desolder Pump	£3.00	N Socket RGB	£1.40	BNC Crimp Pliers			
74LS11	£0.17	4014	£0.30	2N3053	£0.27	BC214	£0.08	BD933C	£0.47	ICL7621	£1.27	Antistatic Pump	£4.30	BNC Crimp Pliers	£15.50				
74LS112	£0.21	4015	£0.31	2N3064	£0.30	BC214L	£0.08	BD954C	£0.50	ICM7555	£0.43	22SWG 0.5kg Solder	£7.40						
74LS113	£0.21	4016	£0.19	2N3055	£0.42	BC237B	£0.09	BF180	£0.31	ICM7556	£0.96	18SWG 0.5kg Solder	£6.80						
74LS114	£0.21	4017	£0.27	2N3440	£0.50	BC238C	£0.09	BF182	£0.31	LM4301A	£0.25	1mm 3 yds Solder	£0.82						
74LS12	£0.14	4018	£0.27	2N3702	£0.09	BC239C	£0.10	BF185	£0.31	LM348N	£0.31	Desolder Braid	£0.87						
74LS122	£0.31	4019	£0.19	2N3703	£0.10	BC251	£0.13	BF194	£0.19	LF351N	£0.36								
74LS123	£0.31	4020	£0.31	2N3704	£0.10	BC252	£0.13	BF195	£0.19	LF353	£0.41								
74LS125	£0.21	4021	£0.31	2N3705	£0.10	BC281B	£0.24	BF244	£0.35	LM358N	£0.27								
74LS126	£0.21	4022	£0.32	2N3904	£0.10	BC282B	£0.24	BF257	£0.33	LM377	£2.57								
74LS13	£0.14	4023	£0.16	2N3771	£1.44	BC287B	£0.09	BF258	£0.33	LM380N	£1.12								
74LS131	£0.14	4024	£0.21	2N3772	£1.51	BC308	£0.10	BF337	£0.38	LM381	£2.70								
74LS132	£0.21	4025	£0.15	2N3773	£1.79	BC309	£0.10	BF355	£0.38	LM386	£0.48								
74LS133	£0.14	4026	£0.16	2N3819	£0.40	BC327	£0.10	BF423	£0.13	LM387	£1.40								
74LS138	£0.24	4027	£0.18	2N3820	£0.66	BC328	£0.10	BF451	£0.19	LM392N	£0.79								
74LS139	£0.26	4028	£0.22	2N3905	£0.10	BC338	£0.10	BF459	£0.29	LM393N	£0.28								
74LS14	£0.26	4029	£0.27	2N3906	£0.10	BC414C	£0.13	BFX29	£0.29	LM1458	£0.28								
74LS145	£0.56	4031	£0.20	2N4038	£0.31	BC441	£0.40	BFX64	£0.31	LM3900	£0.72								
74LS147	£1.28	4033	£0.56	2N5296	£0.57	BC461	£0.40	BFX85	£0.32	LM3914	£2.70								
74LS148	£0.70	4034	£1.24	2N5321	£0.67	BC463	£0.29	BFX85	£0.29	LM3915	£2.70								
74LS15	£0.14	4035	£0.31	2N6107	£0.60	BC478	£0.32	BFY51	£0.28	MC3340	£1.60								
74LS161	£0.25	4040	£0.29	AC127	£0.30	BC479	£0.32	BFY52	£0.28	MC4658	£0.36								
74LS153	£0.25	4041	£0.31	AC128	£0.30	BC490	£0.24	BS107	£0.21	NE531	£1.64								
74LS154	£0.70	4042	£0.31	AC128	£0.28	BC516	£0.22	BS170	£0.21	NE556N	£0.36								
74LS155	£0.25	4043	£0.28	AC187	£0.45	BC517	£0.20	BS176	£1.35	NE567N	£0.47								
74LS156	£0.25	4044	£0.35	AC188	£0.37	BC527	£0.20	BU126	£1.70	NE5632	£0.80								
74LS157	£0.25	4046	£0.31	AC188	£0.37	BC528	£0.20	BU205	£1.82	NE5534	£0.66								
74LS158	£0.25	4047	£0.25	AD149	£1.67	BC537	£0.20	BU208A	£1.73	TBA1205	£0.80								
74LS159	£0.25	4048	£0.31	AD161	£0.92	BC546C	£0.08	BU256A	£1.81	TBA1205	£0.80								
74LS161	£0.32	4048	£0.31	AD162	£0.92	BC547C	£0.09	BU500	£2.32	TBA2105	£0.80								
74LS162	£0.32	4050	£0.20	BC107	£0.14	BC548C	£0.08	BU508A	£1.78	TDA2030	£1.35								
74LS163	£0.32	4051	£0.25	BC107B	£0.15	BC549C	£0.10	BU526	£2.24	TLO61	£0.35								
74LS164	£0.26	4052	£0.25	BC108A	£0.13	BC550C	£0.08	BU806	£1.36	TLO62	£0.42								
74LS165	£0.48	4053	£0.25	BC108B	£0.14	BC557C	£0.08	IRF540	£0.76	TLO64	£0.46								
74LS170	£0.30	4054	£0.56	BC109	£0.17	BC558C	£0.08	IRF740	£1.63	TLO72CP	£0.38								
74LS173	£0.24	4055	£0.34	BC109C	£0.15	BC559C	£0.08	MJ11015	£2.11	TLO74CN	£0.44								
74LS174	£0.24	4056	£0.31	BC114	£0.41	BC560B	£0.09	MJ11016	£2.11	TLO81	£0.33								
74LS175	£0.24	4063	£0.29	BC115	£0.41	BC587	£0.21	MJ2501	£1.80	TLO82CP	£0.34								
74LS190	£0.26	4066	£0.18	BC116	£0.41	BC588	£0.21	MJ3001	£1.82	TLO84CN	£0.46								
74LS191	£0.24	4067	£1.91	BC118	£0.41	BC639	£0.21	ME340	£0.42	UA3	£0.64								
74LS192	£0.24	4068	£1.91	BC132	£0.38	BC640	£0.21	ME350	£0.40	ULN2004	£0.40								
74LS193	£0.24	4069	£0.20	BC134	£0.36	BCV70	£0.21	MPSA12	£0.12	ZN414Z	£1.04								
74LS195	£0.24	4070	£0.17	BC135	£0.36	BCV71	£0.20	MPSA43	£0.17	ZN425E	£4.68								
74LS196	£0.24	4071	£0.20	BC140	£0.25	BCV72	£0.20	MRF475	£7.28	ZN426E	£2.81								
74LS197	£0.24	4072	£0.17	BC141	£0.25	BCV73	£0.20	MRP21	£0.35	ZN427E	£8.82								
74LS20	£0.16	4073	£0.17	BC142	£0.31	BD136	£0.21	TP122	£0.21	ZN428E	£2.81								
74LS21	£0.14	4075	£0.17	BC143	£0.34	BD137	£0.22	TP125	£0.37	ZN435E	£5.31								
74LS22	£0.14	4076	£0.30	BC148	£0.12	BD138	£0.22	TP127	£0.37	ZN448E	£7.92								
74LS221	£0.40	4077	£0.17	BC154	£0.32	BD139	£0.23	TP132	£0.46										
74LS240	£0.32	4081	£0.14	BC157	£0.12	BD140	£0.24	TP137	£0.48										
74LS241	£0.32	4082	£0.17	BC159	£0.12	BD150C	£0.82	TP142	£1.06										
74LS242	£0.32	4085	£0.28	BC160	£0.28	BD165	£0.42	TP147	£1.12										
74LS243	£0.32	4086	£0.26	BC170	£0.16	BD166	£0.35	TP2955	£0.63										
74LS244	£0.32	4089	£0.55	BC170B	£0.18	BD187	£0.39	TP29C	£0.31										
74LS245	£0.33	4093	£0.18	BC171	£0.11	BD201	£0.40	TP3055	£0.63										
74LS247	£0.32	4094	£0.31	BC171B	£0.16	BD202	£0.40	TP30C	£0.31										
74LS251	£0.24	4097	£0.20	BC172B	£0.13	BD203	£0.40	TP32C	£0.32										
74LS252	£0.24	4098	£0.31	BC177	£0.18	BD222	£0.40	TP33C	£0.72										
74LS253	£0.24	4099	£0.38	BC178	£0.18	BD225	£0.42	TP41A	£0.36										
74LS26	£0.14	4502	£0.38	BC179	£0.17	BD232	£0.38	TP42C	£0.38										
74LS266	£0.14	4503	£0.31	BC182	£0.08	BD237	£0.32	TP47	£0.48										
74LS273	£0.32	4508	£0.90	BC182L	£0.08	BD240B	£0.37	TP50	£0.82										
74LS279	£0.25	4510	£0.32	BC183	£0.08	BD243B	£0.50	VN10KM	£0.44										
74LS30	£0.14	4512	£0.32	BC183L	£0.08	BD244A	£0.53	VN66AF	£1.60										
74LS32	£0.21	4514	£0.73	BC183BL	£0.08	BD246	£1.06	ZTX300	£0.16										
74LS365	£0.21	4515	£0.98	BC184	£0.08	BD441	£0.41	ZTX500	£0.16										
74LS367	£0.21	4516	£0.31	BC184L	£0.08	BD442	£0.41												
74LS368	£0.21	4518	£0.27	TRIACS				THYRISTORS											
74LS37	£0.14	4520	£0.28	20105DA	£0.42	PO102AA	£0.30												
74LS373	£0.32	4521	£0.62	TIC206D	£0.65	TIC106D	£0.40												
74LS374	£0.32	4526	£0.40	TIC226D	£0.73	TIC116D	£0.66												
74LS375	£0.34	4527	£0.39	BT408-600B	£0.84	TIC126D	£0.77												
74LS377	£0.32	4528	£0.40	TIC236D	£0.86														
74LS378	£0.62	4529	£0.44	DIAC	£0.20														
74LS38	£0.19	4532	£0.32					HARDWARE											
74LS390	£0.25	4532	£0.30					T2 Box 75 x 56 x 25mm £0.82											
74LS393	£0.24	4536	£1.00					T3 Box 75 x 51 x 25mm £0.82											
74LS395	£0.26	4538	£0.37					T4 Box 111 x 57 x 22mm £0.96											
74LS399	£0.82	4541	£0.33					M1 Box 79 x 61 x 40mm £1.44											
74LS																			

PCB Foils

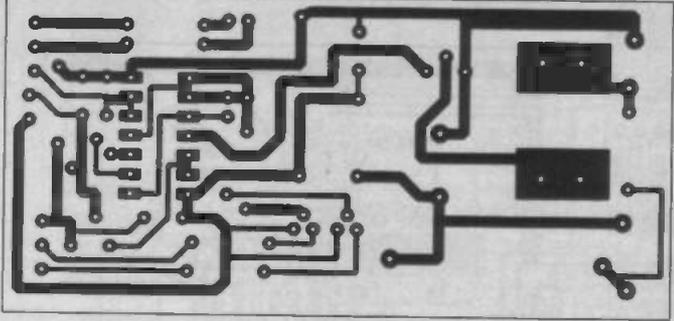
The PCB foil patterns presented here are intended as a guide only. They can be used as a template when using tape and transfer for the creation of a foil.




Hot Wire Cutter

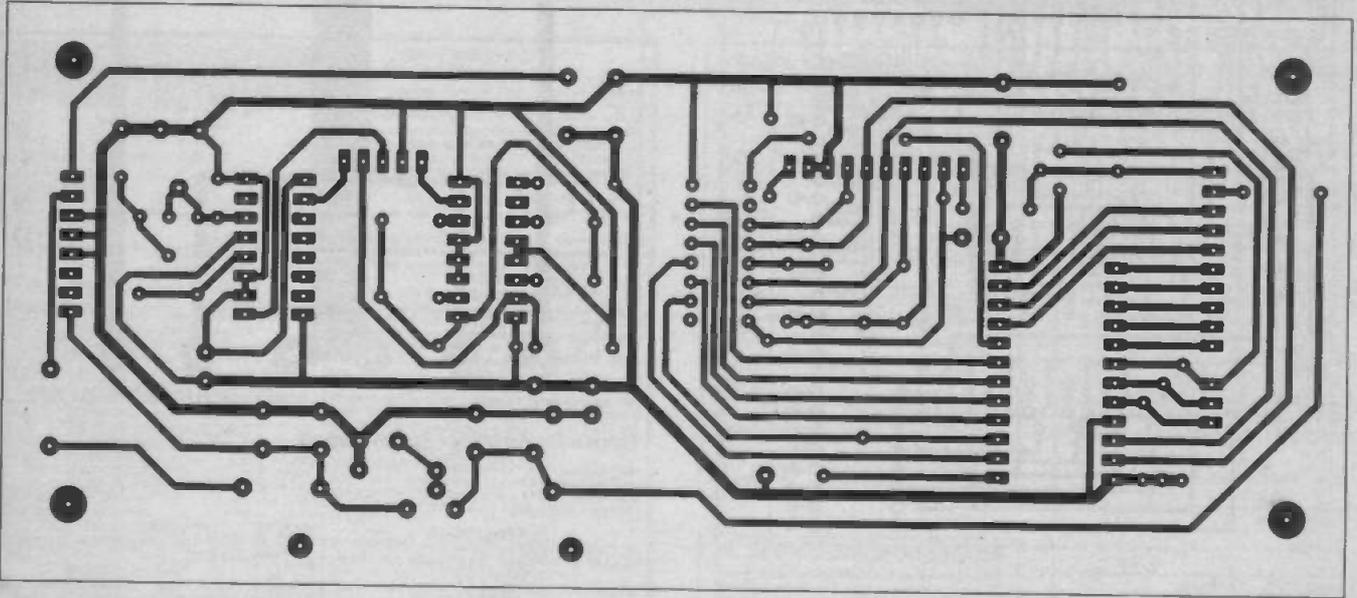


Home Minder

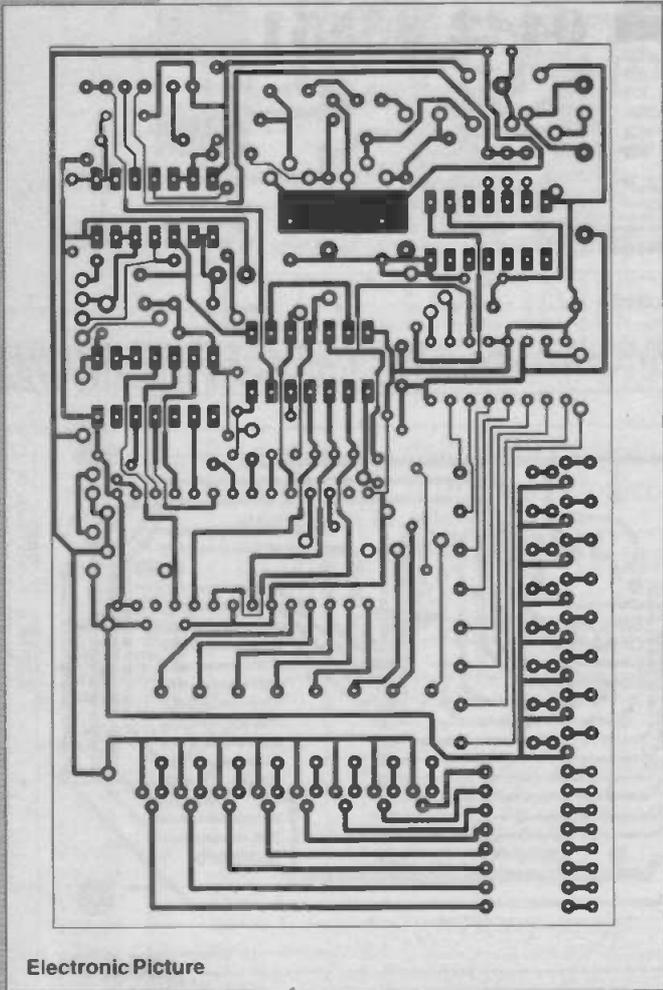

Electronic Picture

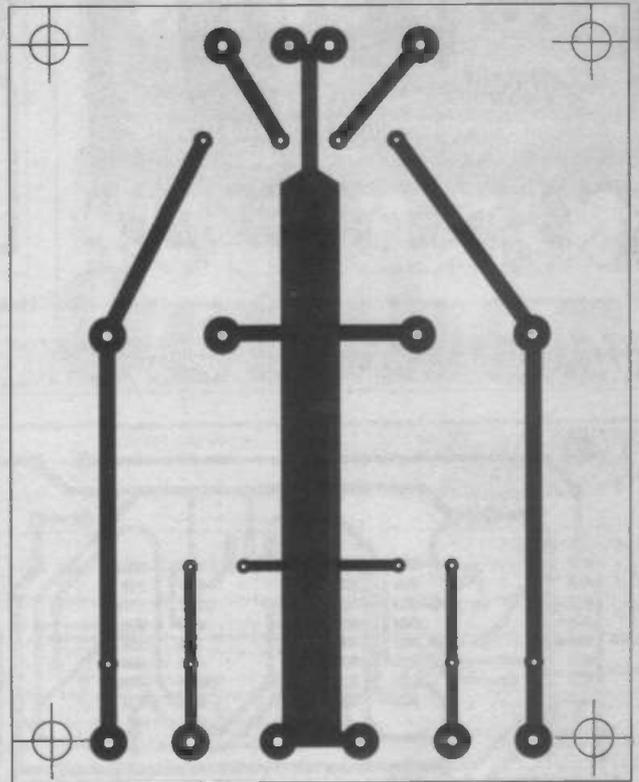

Transistor Amplifier Power Supply

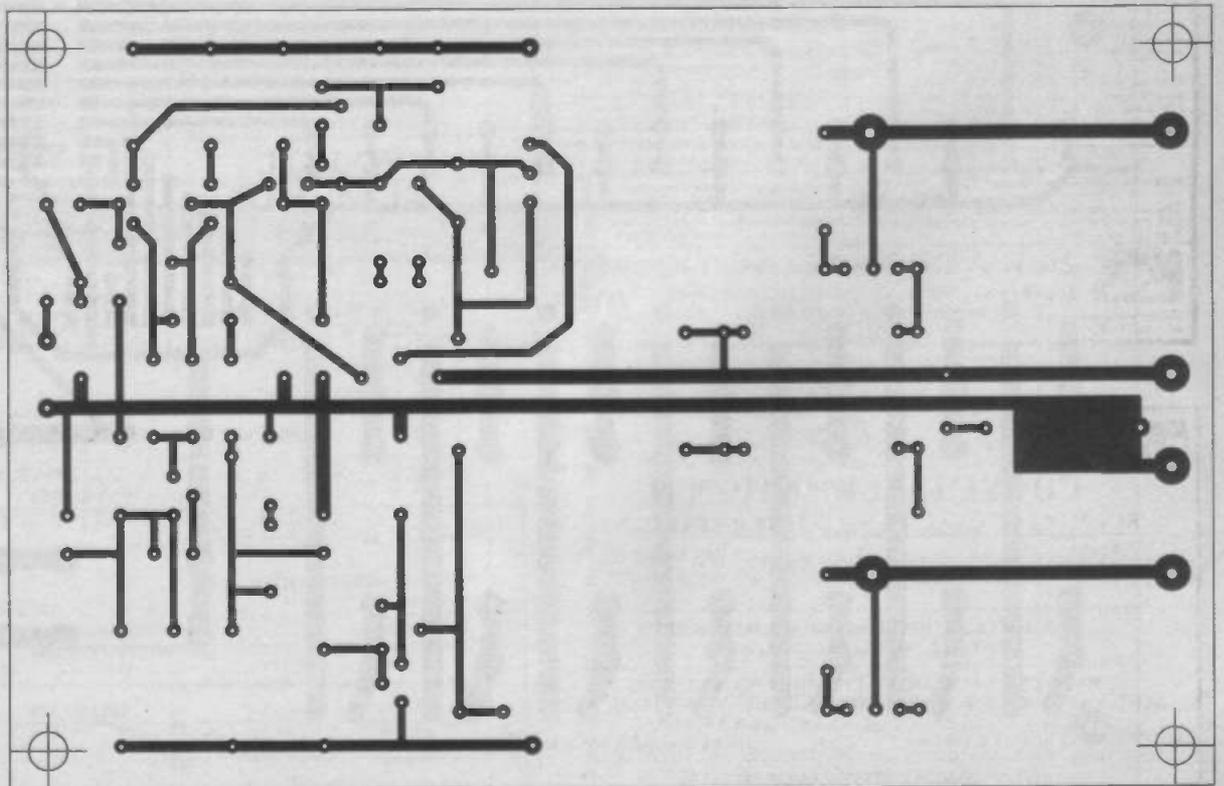

Transistor Amplifier

FOILS

Classified



James Gale
0442 66551

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 60p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£8.00 + VAT per single column centimetre } Per
Electromart £24.00 (+ VAT) } Insertion



Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60	OUTPUT 0-260V	Price	P&P
0.5KVA 2.5 amp max		£29.00	£4.65
		(£39.54 inc VAT)	
1KVA 5 amp max		£37.40	£6.25
		(£51.29 inc VAT)	
2KVA 10 amp max		£54.00	£7.80
		(£72.62 inc VAT)	
3KVA 15 amp max		£71.50	£7.80
		(£93.19 inc VAT)	
5KVA 25 amp max		£126.50	

(Plus Carriage)
Buy direct from the Importers. Keenest prices in the country.
COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries
ULTRA VIOLET BLACK LIGHT FLOURESCENT TUBES

4ft 40 watt	£12.00 (callers only)	(£14.10 inc VAT)
2ft 20 watt	£7.44 + £1.25 p&p	(£10.21 inc VAT)
12in 8 watt	£4.80 + 75p p&p	(£6.52 inc VAT)
9in 6 watt	£3.98 + 50p p&p	(£5.24 inc VAT)
6in 4 watt	£3.98 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT
For either 8in, 9in or 12in tubes. £6.05 + £1.40 p&p (£8.75 incl)

400 WATT UV LAMP
Only £34.00 + £2.50 p&p (£42.89 inc VAT)

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB
Available with BC or ES fitting price inc VAT & p&p and VAT £25.55



"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (letter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad AA cells back-up L.C.D. Digital read-out 17mm high with legends. Audible warning.

These are sold for the dismantling of the exceptional quality components. Register no Circuits available. Ridiculously low price: £16.00 + £4.00 p&p (£23.50 incl VAT)

12V D.C. GEARED MOTOR
Reversible precision-built Motor Output speeds no load approx. 12V-26 rpm; 9V-20 rpm; 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L 40mm W 29 mm H 39mm. Shaft: 3mm dia x 10mm long. Price £8.00 + 50p p&p (£10.00 inc VAT)

TORIN CENTRIFUGAL BLOWER
230V AC, 2.800 RPM, 0.9 amp, 130mm diameter impeller outlet 63 x 37mm, overall size 195 x 160 x 150mm. long. Price £17.50 + £2.50 p&p (£23.50 inc VAT)

SOLID STATE RELAY
7 amp + 240V, A.C. when mounted on suitable Heat-sink. Can be driven from T.T.L. or Computer output between 3-10V D.C. Size: 24mm x 17mm x 15mm high. Fixing centres 30mm (T0-3). Price: £3.00 + 40p p&p (£4.00 inc VAT)

GEARED MOTORS
71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £23.50.

SOLID STATE EHT UNIT
Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics. eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

SAVE POUNDS!!!
Build your own forged bolt note detector. Can detect counterfeiters amongst a quantity of notes. Complete kit of parts less case. 240V a.c. including 5" vV black light tube, starter and holder, a pair of pin tube holders. Total price including p&p & VAT only £13.99

WASHING MACHINE WATER PUMP
Brand new 240V AC, fan cooled. Can be used for a variety of purposes. Inlet 1/2" in. outlet 1" in. dia. Price includes p&p & VAT £11.20 each or 2 for £20.50 inclusive

MICROSWITCH
Pye 15 amp changeover lever microswitch, type S171. Brand new price 5 for £7.05 inc VAT & p&p

CATALOGUE £1.00 + 25p P&P

LEDs 3mm or 5mm red or green each yellow 1ip each
High intensity red, green or yellow 5mm 30p each
Cable ties 1p each £5.95 per 1000 49.50 per 10,000
Shipping motor & phase 12v 7.5 step, 50 ohms £3.95
SAA1027 sleeping motor driver die £3.95
FM Transmitter xl good quality sound £8.80
High quality photo resist copper clad epoxy glass boards
Dimensions single sided double sided
34 inches £1.07 £1.07
4 1/2 inches £2.40 £2.98
5 1/2 inches £3.37
12x12 inches £10.88
Special Offers
Computer grade capacitors with screw terminals 38000u/20v £2.80
87000u/10v £1.95, 88000u/10v £2.85, 10000u/10v £1.50
7 segment common anode led display 12mm £9.45
LM2917ATS 0 low drop out 5v regulator TO220 package £0.95
BS250 P channel mosfet £0.45, BC559 transistor £3.95 per 100
74LS255 has tri-state £16.00 per 100, used 8748 microcontroller £3.50
TV Mains switch 4A double pole with momentary contacts for remote control push all 10 £3.95 box of 60 £19.95
DC-DC converter Reliability model V12P5 12v to 5v 200ma out 300v input 8v output isolation with case £4.95 each or pack of 10 £38.50
Hour counter used 7 digit 240v ac 50Hz £1.45
Resistor pack 2500 resistors 1/8-2W 50 different values £8.00
QUERTY keyboard 58 key good quality switches new £8.80
QUERTY keyboard with serial output for data (used) £3.00
Wide range of CMOS TTL 74HC 74F Linear Transistors etc.
rechargeable batteries capacitors tools etc always in stock. Please add 95p towards P&P vat included

JPG ELECTRONICS
278-278 Chateworth Road Chesterfield S40 2BH
Access Visa Orders (0246) 211282 callers welcome

!!! ON OFFER THIS MONTH !!!

Red Super Led 5mm	15p	Crystal IR Receiver	20p	Earphone Neon Bulb	65p
0.1uF X rated	5p	0.1uF Pol	5p	250AC	15p
33uF 16v RAD	10p	BD332 PNP Darl	40p		
47uF 35v RAD	10p	BC639 100V 1A	30p		
47uF 16v RAD	10p	LM337 VREG	45p		
22uF Non Pol	30p	LM7924 VREG	45p		
250uF 16v RAD	10p	2718 Eprom	£1.00		
2700pF 9v Tol	10p	2732 Eprom	£1.65		
Contact Cleaner	£1.25	Contact			
Flux-Off	£1.25	Restorer	£1.25		
2p-20pF	65p	2p-10pF Trim	40p		
IM401	8p	Tilt Switch	£1.00		
47uF 350V DC	45p	4Way Tilt SW	£2.95		
74HC75	30p	5 Watt 300 OHM	10p		
Crystal 45Mhz	40p	200uF 300V DC	85p		

STRIP OF ASSORTED COMPONENTS 1M LENGTH £1.
WIDE RANGE OF ELECTRONIC COMPONENTS ALWAYS IN STOCK RING FOR DETAILS
- FM TRANSMITTERS ALSO IN STOCK

ELEY ELECTRONIC LTD
100-104 BEATRICE ROAD, LEICESTER, LE3 9FF
TEL: 0533 515944
PAY BY: VISA/ACCESS
OPEN 10-6 MON-SAT

PC TECHNICAL SHAREWARE

Would you like to see the best range of low cost technical and scientific public domain & shareware for IBM PC in the UK? HUGE RANGE includes: PACKET, FAX, RX, TX control, PCB design, Circuit and ANTENNA analysis, OSO logging, CAD ELECTRONIC & MECH engineering, SCIENTIFIC, MATHS & STATS, MEDICAL, PROGRAMMING, SOURCE CODE, DATA, EDUCATIONAL, WINDOWS, BUSINESS and lots more
Write, phone or fax today for your free £24 page printed catalogue

The Public Domain Software Library
Walscombe House, Beacon Road,
Crawleydown, Sizers TN6 1UL
Tel 0892 663393, Fax 0892 667473

FOR ALL DETAILS OF RATES TELEPHONE JAMES GALE 0442 66551

Falcon DIY SPEAKERS
Send for our FREE price list PL21: All we ask for is a large S.A.E. (34p stamp) or \$2 bill (A/R) overseas. (Europe - 3 International reply coupons) SYSTEM DESIGNS (Total Kits)
Focal, KEF Constructor, Seas, etc. DRIVE UNITS FOCAL, KEF, Audax, Coles. Peerless, Seas, Siare, Etac Metal Dome, Scanpeak, etc
Also Group/Disco Units CROSSOVER NETWORKS - Active & Passive Components, Accessories, Polypropylene Caps. AUDIO AMATEUR PUBLICATIONS BACK ISSUES:
Speaker Builder, Audio Amateur & Glass Audio, L/S Cookbook + books
Full details from FALCON ELECTRONICS (Dept E.T.I.), Tabor House, Mulbarton, Norfolk NR14 8JT (0508) 78272 (Proprietors: Falcon Acoustics Ltd.)

SERVICE TRADING CO
57 BRIDGMAN ROAD, CHISWICK, LONDON W4 6BB
FAX 081 995 0549 081-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10
Showroom open Monday/Friday
Ample Parking Space

COOKE INTERNATIONAL
SUPPLIER OF QUALITY USED TEST INSTRUMENTS
ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS, ETC ALWAYS AVAILABLE
ORIGINAL SERVICE MANUALS FOR SALE COPY SERVICE ALSO AVAILABLE
EXPORT, TRADE AND U.K. ENQUIRIES WELCOME SEND LARGE S.A.E. FOR LISTS OF EQUIPMENT AND MANUALS ALL PRICES EXCLUDE VAT AND CARRIAGE DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED
OPEN MONDAY TO FRIDAY 9AM - 5PM
COOKE INTERNATIONAL
ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex, PO22 0EB Tel (+ 44) 0243 545111/2 Fax + 44) 0243 542457

BREWER ELECTRONICS
BRYNAWELON, CROESLAN, LLANDYSUL, DYFED, WALES. SA44 5SH.
TELEPHONE:- 0239 851669
WRITE OR PHONE FOR FREE CATALOGUE
A small selection from our catalogue of full spec. branded products:-
E24 5% 1/4W Carbon Film Resistors (10 Pack) 7p (1p each)
E24 2% 1/4W Metal Film Resistors (10 Pack) 14p (2p each)
(Also available - 1%, 1/2W, 2.5W Sil. Dis Networks)
10mm Carbon Presses 100R - 4M7 Vertical and Horizontal 10p each
1uF/50V, 2u2/50V Radial 5p 100uF/25V, 220uF/16V Axial 12p each
2,200uF/50V Snap-in 90p Out/150V, Out/150V Polyester 4p each
IN4148 (10 pack) 12p IN4001-2-3 2p IN4004-7 5p IN5400-1-2-3 8p
1/2W Zeners 2V4 - 5V1 4p 1.3W Zeners 2V7 - 5V1 12p
(0.1A) 78L05-06-08-10-12-15-20-24 Regulator 18p LM317L(0.1A/1.2-37V) 35p
(0.1A) 79L05-06-08-10-12-15-20-24 Regulator 20p LM317T(1.5A/1.2-37V) 45p
(1.0A) 7805-06-09-10-12-15-20-24 Regulator 20p
(1.0A) 7905-06-09-10-12-15-20-24 Regulator 25p
BC182, BC183, BC184, BC212, BC213, BC214 4p
8D131, BD132, BD437, BD438 25p 2N3055 80p
3mm, 5mm - RED, YELLOW, GREEN LEADS 10p
12x12mm PCB Tactile Switches 20p
4000 Series, 74HC Series plus much more all in our catalogue. Please add £1.00 towards p&p all prices include VAT.

For KITS & COMPONENTS
Choose the easy way with

Send £2.00
for CATALOGUE

ORDERS: RING 081-579-9794 - 24 HRS.



MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and preset times over a 7-day cycle.



LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box, 18 time settings.
CT6000K£85.95
XK114: Relay kit for CT6000, includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts£10.50
701 312 Additional relays£1.60

COMPUTERS



COMPUTERS
LOW COST SYSTEMS
286's FROM £449
386's FROM £489
486's FROM £545

All low cost systems include: Mono VGA Monitor, 1MB RAM, 42 MB Hard Drive Mini Tower or Desktop Case, 3.5 Inch 1.44MB Floppy Disk Drive, 2 Serial, 1 Parallel, 1 Games, 102 Enhanced Keyboard, Three Year Warranty (first year parts & labour, then labour only).

SECURITY EQUIPMENT



TK ELECTRONICS HOME SECURITY
CALL US NOW FOR YOUR FREE ESTIMATE

HIGH.TEC

EEPROM CARDS
NOW AVAILABLE

COMMUNICATIONS

PRIVATE MOBILE RADIOS AND ACCESSORIES

HOME CONTROL CENTRE

XK128 SUPER-SENSITIVE FM MICROBUG



FM transmitter measuring only 46x26x16mm, including built-in microphone. Frequency 88-93MHz enabling reception on a standard domestic FM radio. Range approximately 300m, depending on terrain. Powered by 9V PP3 (7mA). Its small size and highly sensitive electret microphone makes it ideal for surveillance, baby alarm, etc.
.....£10.25

DISCO LIGHTING KITS


XK141: SEQUENCER. four channel chaser with 32 different sequence patterns£29.95
XK 130: STROBOSCOPE designed to produce a high intensity light pulse. Built In Audio Trigger£21.85
XK153: Extra - Highpower strobe. as above but more powerful.....£25.85
DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone 1kW per channel £24.95

8 WAY SEQUENCER KIT

DON'T CHASE AROUND FOR ANOTHER SEQUENCER

The DL8000K is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY-YES 80 different sequences including standard flashing and chase routines. The kit includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300W output per channel. And the best thing about it is the price:

ONLY £49.95

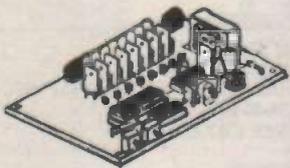

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformers) to make a sensitive IR receiver with 16 logic output (0,15V) which with suitable interface circuitry (relays, tricas, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2cms. The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of out-puts to be used.
MK12 IR Receiver (incl. transformer)£24.95
MK18 Transmitter£12.75
MK9 4-Way Keyboard£8.35
MK10 16-Way Keyboard£12.75
601 133 Box for Transmitter£3.10

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting.
See XK132 300W touch dimmer - IR remote control
XK136 300w touch dimmer just touch to switch on/off & dim
XK135 IR transmitter for XK132
TDE/K Extension kit for XK132/XK136 to enable 2 way switching£4.95



WANTED

SURPLUS COMPONENTS WANTED

- ★ COMPLETE CLEARANCE
- ★ BEST PRICES PAID
- ★ PCB BOARDS POPULATED

CONTACT
D.T.S. SERVICES
Tel: (0602) 208955
or Fax: (0602) 484530

TURN YOUR SURPLUS TRANSISTORS, ICS ETC INTO CASH immediate settlement.
We also welcome the opportunity to quote for complete factory clearance.

Contact:
COLES-HARDING & CO.
Sandall Road, Wilsbech,
Cams PE13 2PS
BUYERS OF SURPLUS INVENTORY
ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax: 0945 475216

WANTED

Receivers, Transmitters, Test Equipment, Components, Cable and Electronic, Scrap. Boxes, PCB's, Plugs and Sockets, Computers, Computer Scrap, Edge Connectors.

TOP PRICES PAID FOR ALL TYPES OF ELECTRONIC EQUIPMENT.

A.R. Sinclair Electronics,
Stockholders, 2 Normans Lane,
Rabley Heath, Welwyn, Herts AL6 9TQ.
Telephone: 0438 812 193.
Mobile: 0860 214302. Fax: 0438 812 387

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

WIND POWER, DESCRIPTIVE GUIDE including list of manufacturers and equipment. Plus descriptive price list of 25 plans, wind, solar, water, petrol and welding generators, inverters, controllers, books and guides only £2.50.

JEMMETT ENGINEERING, 8 Hallam Gardens, Pinner, Middlesex HA5 4PR.

KITS

NEW VHF MICROTRANSMITTER KIT tuneable 70-115MHz, 500 metre range, sensitive electret microphone, high quality PCB, **SPECIAL OFFER** complete kit **ONLY £5.95** assembled and ready to use £9.95 inclusive P&P. 3 Watt FM transmitter kit £15.95 Credit card orders telephone 021 486 3092 Cheques/PO's to: Quantek Electronics, (DEPT ET1) 3 Houldry Rd, Birmingham, B31 3HL. Send 2 x 1st Class stamps for details of these and other kits.

COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on 0626 779398 ET1 10/93

Name _____

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Micro-processor
- Introduction to Television

Radio & Telecommunications Correspondence School
12 Moor View Drive, Telgmouth, Devon TQ14 9UN



ELECTRONICS
13 BOSTON RD.
LONDON W7 3SJ
TEL. 081 579 9794
FAX: 081 840 6519

ORDERING INFORMATION:

P&P:- UK £1.25 Europe & Eire £3.60. Elsewhere £10.00 (unless otherwise notified)
Barclaycard/Access No. with order.

SEND £2.00 FOR CATALOGUE OR CALL AT SHOP Mon-Sat 9.30-6.00



LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY



EDITORIAL

Editor *Paul Freeman*
Sub Editor *Jim Bluck*

CREATIVE

Art Editor *Peter Kirby*
Designer *Iain Houston*
Technical Illustration *John Puczynski*
Photography *Manny Cefai*

ADVERTISEMENT SALES

Display Sales
Tony Hill
Advertisement Copy Control
Marie Quilter
Classified Sales
James Gale

MANAGEMENT

Managing Director
Terry Pattison
Circulation & Promotions Manager
Debra Stuppel
Production Manager
Tony Dowdeswell
Group Editor
Stuart Cooke
Group Advertisement Manager
Claire Jenkinson



ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and reproduction requires the prior written consent of the company ©1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

● Subscription rates...UK £23.40 Europe £29.50 Sterling Overseas £31.00 US Dollars Overseas \$56.00

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Telephone (0442) 66551. UK newstrade distribution by SM Distribution Ltd, 6 Leigham Court Road, London SW16 2PG. Telephone 081-667 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Telephone (0442) 66551. Subscriptions by Argus Subscription Services, ETI, Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6258 Fax (310) 375 0548. Pacific Time: 9am-9pm Weekdays. 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (0442) 66551 Fax (0442) 66998

Next Month

Ever wondered how to find those stray radio frequencies that seem to lurk around in your amplifier and cause small amounts of noise and distortion? OK, so the ETI RF Hound, featured next month, can sniff out where those mysterious little oscillations are coming from.

For any of you worried about car theft, we have another car alarm to tax the mind of the burglar. We also have a MIDI program change pedal for our music fans and a fast charger for your batteries if you are one of those people that have not got all day to wait.

All this, plus a feature article on computer interfacing for the PC, are the regular features you have come to expect from ETI.

The November edition of ETI is available from your newsagents on 1st October.

The above articles are in preparation but circumstances may prevent publication

Last Month

Our August issue featured:

- Flashing Beacon for R/C models
- 4 Range Capacitance Meter
- RF Signal Generator
- Tech Tips
- MIDI Analyser
- AutoMate
- Metronome
- Digital Television News


Back issues can be obtained from Argus Subscription Services. Address in column to left.

ADVERTISERS' INDEX

BK ELECTRONICS	15	JPG	56
BONEX	46	LABCENTER	11
CIRKIT	43	MAPLIN ELECTRONICS	OBC
CHELMER VALVE Co.	57	NUMBER ONE SYSTEMS	IBC
CP TECHNOLOGY	7	OMNI ELECTRONICS	7
DISPLAY ELECTRONICS	30	PICO TECHNOLOGY	17
ELECTROVALUE	9	RN ELECTRONICS	16
EQT	7	SAJE ELECTRONICS	32
HALCYON ELECTRONICS	46	SEETRAX	42
HESING TECHNOLOGY	7	SLM	9
HENRYS AUDIO	9	STEWARTS OF READING	56
J&N BULL	44,45	TSIEN (UK) Ltd.	IFC
JAY TEE ELECTRONICS	43	WILMSLOW AUDIO	46

EASY-PC, SCHEMATIC and PCB CAD

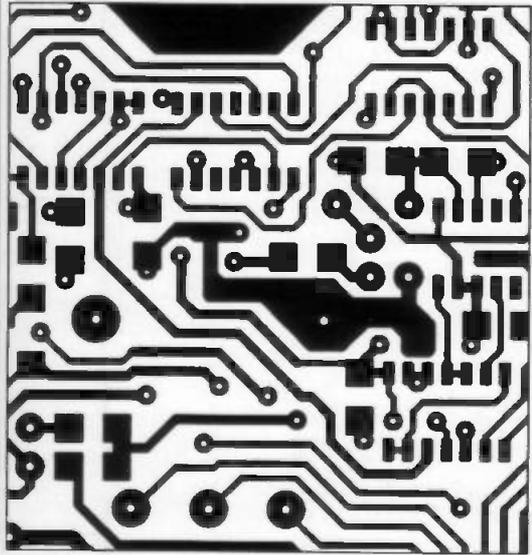
Over 17,000 Installations
in 70 Countries World-wide!



- Runs on:- PC/XT/AT/ 286/ 386/ 486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.

Still Only £98.00!
Plus P&P+VAT

BRITISH DESIGN AWARD 1989


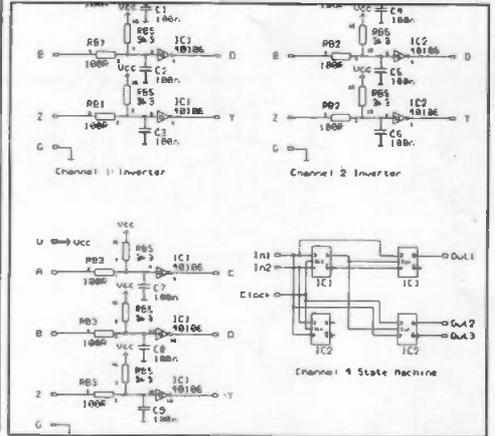


Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?

Ask for our fully functional Integrated Demo

Integrated Electronics CAD

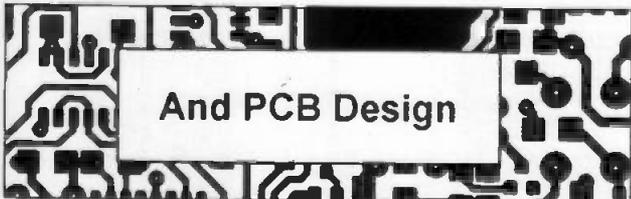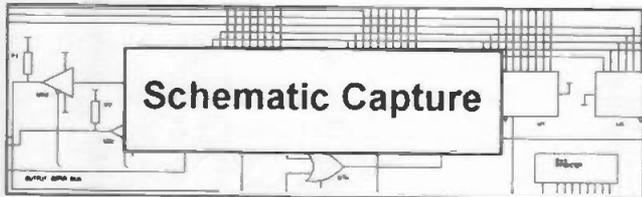

For Less than £400/\$775!

Affordable Electronics CAD

EASY-PC: Low cost, entry level PCB and Schematic CAD.	\$195.00	£98.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III and PULSAR.	\$375.00	£195.00
PULSAR: Low cost Digital Circuit Simulator ~ 1500 gate capacity.	\$195.00	£98.00
PULSAR Professional: Digital Circuit Simulator ~ 50,000 gate capacity.	\$375.00	£195.00
ANALYSER III: Low cost Linear Analogue Circuit Simulator ~ 130 node capability	\$195.00	£98.00
ANALYSER III Professional: Linear Analogue Circuit Simulator ~ 750 node capability.	\$375.00	£195.00
Z-MATCH II: Smith Chart program for RF Engineers - direct Import from ANALYSER III.	\$375.00	£195.00
<i>We operate a no penalty upgrade policy. You can upgrade at any time to the professional version of a program just for the difference in price.</i>	<i>US\$ prices include Post and Packing.</i>	<i>Sterling £ prices exclude P&P and VAT</i>

For full information, Write, Phone or Fax:-

Number One Systems Ltd.

REF: ETI, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 461778 (7 lines) Fax: 0480 494042

International: +44 -480-461778, Fax:+44-480-494042



- TECHNICAL SUPPORT FREE FOR LIFE!
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

ACCESS, AMEX, MASTERCARD, VISA Welcome.


NEW

FULL COLOUR GUIDE TO ELECTRONIC PRODUCTS

Maplin



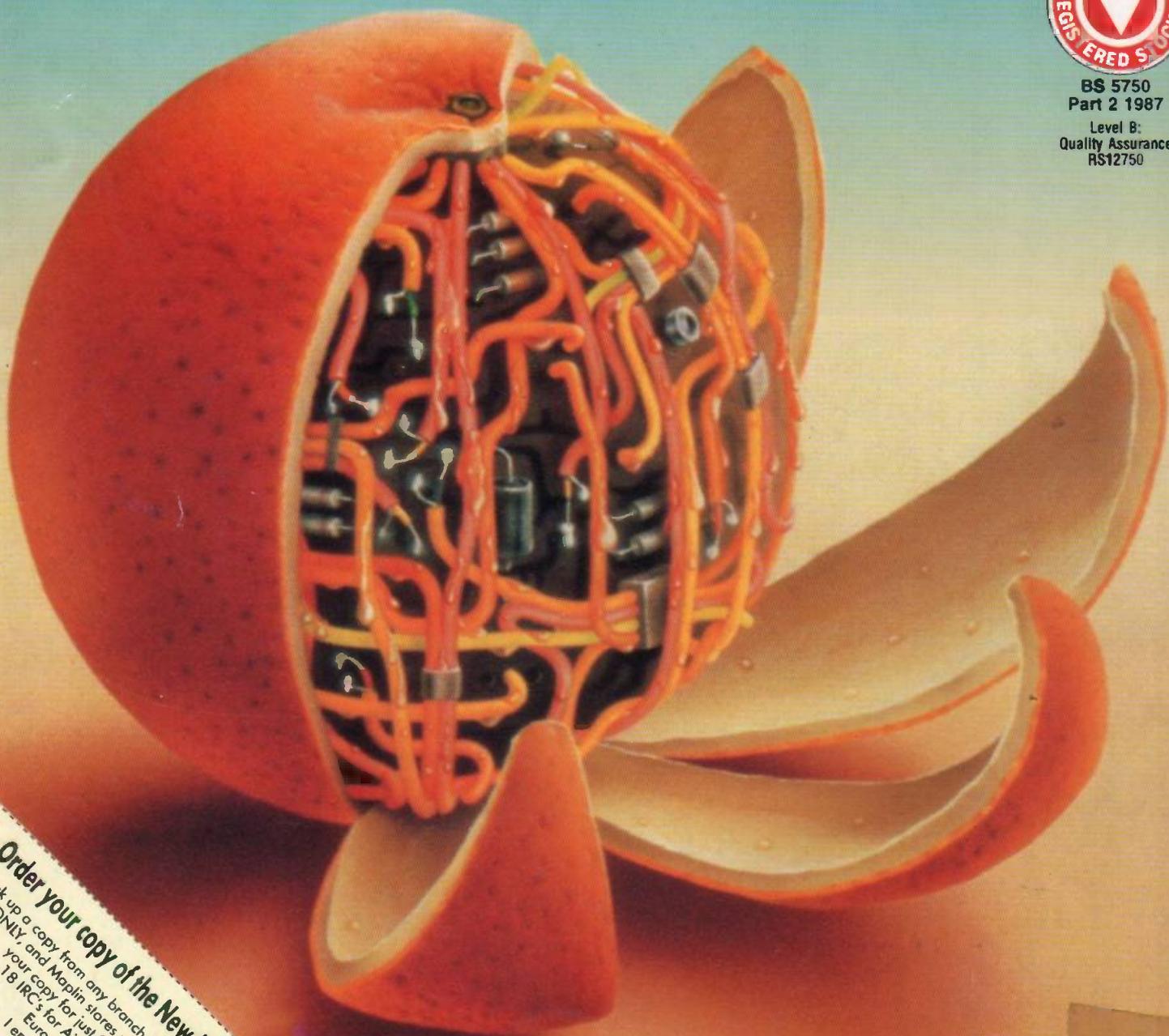BS 5750
Part 2 1987
Level B:
Quality Assurance
RS12750



Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any branch of WHSMITH, selected branches of RSM^{COLL} in Scotland ONLY, and Maplin stores nationwide for just £2.95 or post this coupon now to receive your copy for just £3.45 inc. p&dp. If you live outside the U.K. send £6.80 or 18 IRC's for Airmail in Europe/£5.20 or 13 IRC's for surface mail outside Europe; or £11.50 or 30 IRC's for Airmail outside Europe. I enclose £3.45/£6.80/£5.20/£11.50 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England
SS6 8LR.
ET194

Over 700 colour packed pages with hundreds of brand New Products at Super Low Prices, on sale now, only £2.95.

Available from all branches of WHSMITH, selected branches of RSM^{COLL} in Scotland ONLY, and Maplin stores nationwide. The Maplin Electronics 1994 Catalogue - UNIQUELY DIFFERENT!