

An exciting hobby.... for everyone

everyday electronics

MAY 72

15p


FREE! INSIDE ▶

... A POCKET GUIDE TO
CONSTRUCTIONAL
ELECTRONICS


Presented free
with the
May 1972 issue of
Everyday Electronics



CONSTRUCTORS COMPANION

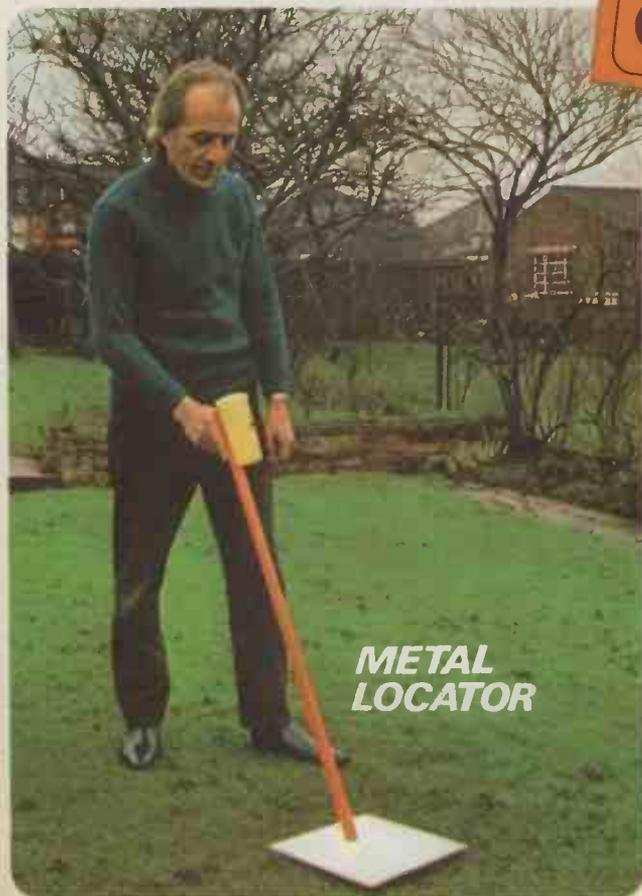

METAL
LOCATOR

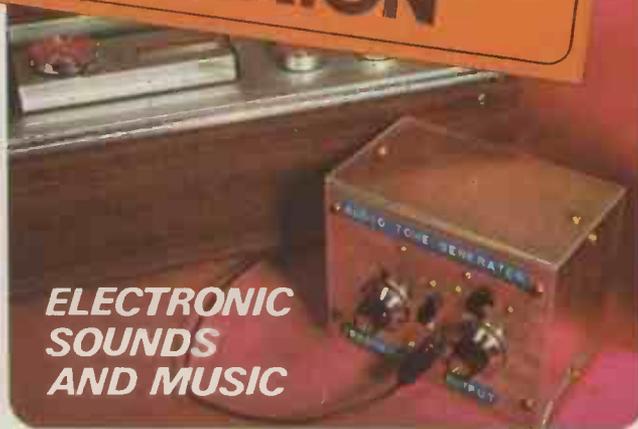

ELECTRONIC
SOUNDS
AND MUSIC



BEE
COUNTER

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits

(illustrated) available

COPPER

B 38 $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{8}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. Y), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

SAFEBLOC

of robust construction

Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.



If ordering by post, send cash with order.

PRICE £2.60+10p P.&P. EACH

Special bulk order wholesale and industrial rates on application



RENDAR®

Rendar Instruments Ltd., Victoria Road, Burgess Hill, Sussex. Tel. Burgess Hill 2642

BARGAIN PRINTED CIRCUIT OFFER

Circuit Board with all holes drilled, 7 1/4" x 5 1/4" inc. central hole 1 1/2" for speaker magnet and cut out for PP9 batt.; Rocker w/change switch and mounting bracket; 2 gang tuning capac.; 3 L.F.S.; Osc. Coil, Ferrite rod with coils and holder, Potentiometer and knob; Circuit Booklet showing component values and positions. All for £1.75 (25p Post). Worth £5.

BATTERY CHARGER

5 1/2" x 3" x 3" with firing feet; 12V 2Amp. On-off Indicator, 2 yds. Mains and 2 yds. Battery Leads; Battery Clips. £1.50 (25p. Post).
PANEL METERS—70mm square. Minus 10A. to Plus 20A. D.C. £1 (15p Post); DITto 0-25V. A.C. and D.C. £1 (15p. Post); 2 1/2" dia. 0-40V. D.C. 50p (15p Post); ELECTROSTATIC VOLTMETER 3 1/2" dia. 0-1000V. £2 (15p Post).

STEREO AMPLIFIER Type SHV—2 x 3 watts

Fully built. Separate vol., bass and treble controls each channel; 12 x 4 1/2" x 6 1/2" high, EZ80, ECC83, 2 x ECL86 valves. O.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal magnet cartridge, tuner, etc. 200-250V. A.C. mains. £7. 50p P. & P.



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med.-short, Gram., 200-250V. A.C. Ferrite aerial. Chassis 13 x 7 x 5 1/2 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81, EF89, EBC81, EL84, EZ80. Price £10.63. (37p P. & P.) Output trans. for 3-ohm speaker. Some slightly tarnished at £10 carr. pd.



MAINS TRANSFORMERS (240-250V Input)


Postage in brackets. 6-3V at 2 1/2A. 40p (15p)
280-280V 60mA, 6-3V 2 1/2A, 6-3V 700mA £1 (27p)
250V at 50mA and 6-3V at 1 1/2A. 50p (20p)
22V at 1A, 6-3V at 2A and 250V at 50mA. 75p (25p)
90V at 20mA and 1-4V at 250mA. 50p (15p)
Deduct 10 per cent from total bill for more than one transformer.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, HANTS.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240. CLOSED WEDNESDAY. S.A.E. for enquiries please.

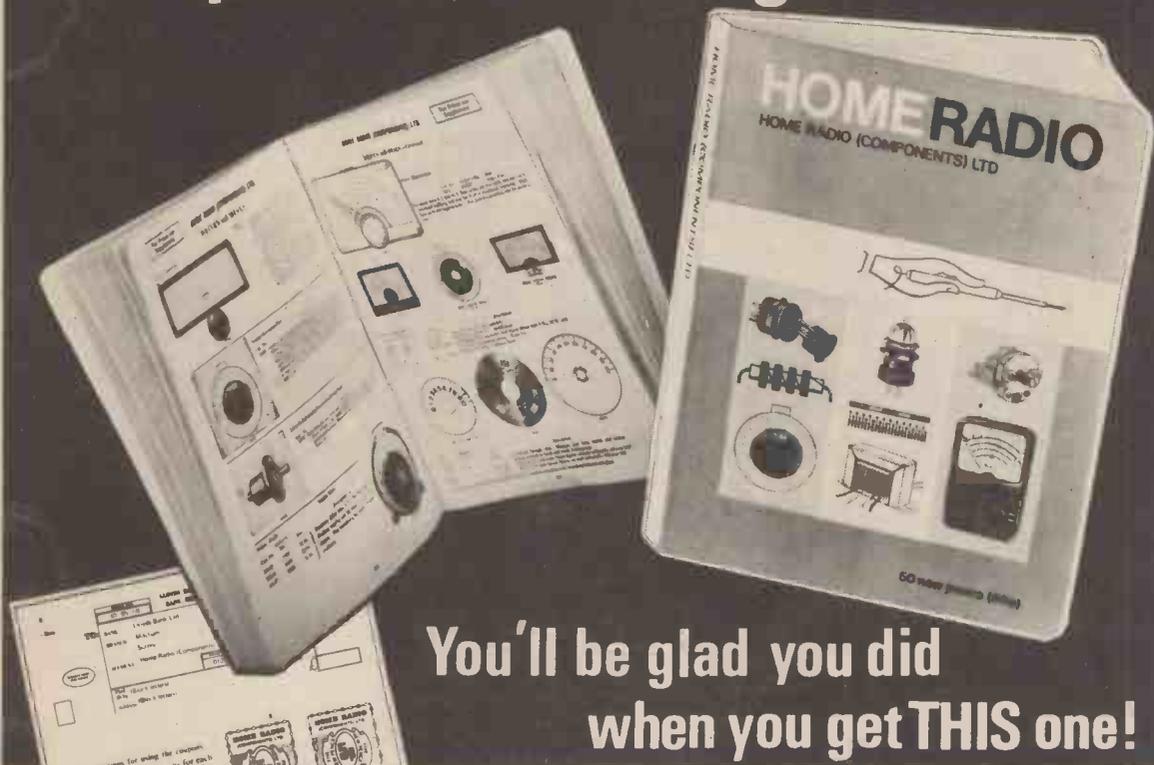Would YOU pay 50 pence for a components catalogue?



You'll be glad you did
when you get THIS one!

A components catalogue is so vital to any keen constructor that it simply does not pay to make do with less than the best. True, the best may cost a little more . . . but it's the cheapest in the end. So invest in a *Home Radio Components Catalogue*, listing over 8,000 items, more than 1,500 of them illustrated. If you call at our shop the catalogue is yours for just 50 pence. If you order by post—70 pence, including postage and packing. You also get 10 Vouchers, each worth 5 pence when used as instructed—so you can get the cost of the catalogue back in any case!

Ask for details of our Credit Account Service.

24-hour Phone Service. Ring 01-648 8422

POST THIS COUPON with your cheque or postal order for 70p



Please write your Name and Address in block capitals

NAME

ADDRESS



The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

HOME RADIO (COMPONENTS) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD.

Viscount III

See Stereo Amplifier

R T V C



The Specification sounds fine the System sounds great

Viscount III Audio Suite complete £49

14 + 14W per channel 40Hz to 40kHz \pm 3dB Total distortion at 10 watts at 1kHz —0.1%.

This is real value for money! We have designed 3 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet, it is available in 2 versions — R100 for ceramic cartridges, and R101 for magnetic and ceramic. FET's (field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For all systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with teak finished plinth and perspex cover.

The exclusive 'Duo loudspeaker' systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES

SYSTEM 1	
Viscount III R101 amplifier	£22.00+£90 p&p
2 x Duo Type II speakers	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00+£1.50 p&p
Total	£59.00

Available complete for only £52+£3.50 p&p

SYSTEM 2	
Viscount R101 amplifier	£22.00+£90 p&p
2 x Duo Type II speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23.00+£1.50 p&p
Total	£77.00

Available complete for only £69+£4 p&p


SYSTEM 3	
Viscount III Amplifier R100	£17.00+£90 p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover	£21.00+£1.50 p&p
Total	£52.00

Available complete for only £49+£3.50 p&p

SPEAKERS Duo Type II
Size approx. 17" x 10 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. £14 pair+£2 p&p.

Duo Type III. Size approx. 23 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ". Drive unit 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair+£3 p&p.

SPECIFICATION R101
14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2 —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

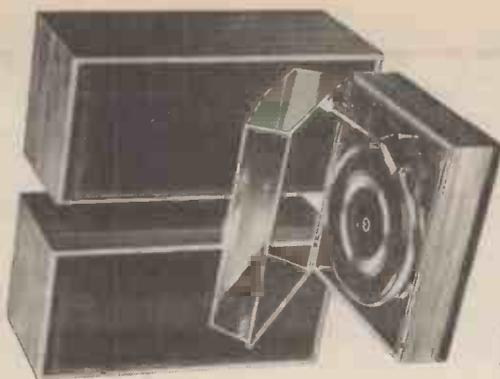

Goods not despatched outside U.K.

R T V C

Radio and TV Components (Acton) Ltd.,
21c High Street, Acton, London W3 6NG,
323 Edgware Road, London, W2. Mail orders
to Acton. Terms C.W.O. All enquiries S.A.E.

**FOR
RAPID
SERVICE**

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

TRANSISTORS

AC127	17p	BFX29	38p
AC128	18p	BFX84	25p
AC176	22p	BFX88	30p
AC187	28p	BFY50	21p
AC188	27p	BFY51	21p
ACY19	23p	BFY52	22p
AD149	47p	MAT100	
AD161/162	72p	MAT101	29p
ADT140	62p	MAT120	25p
AF118	45p	MAT121	29p
AF124	22p	OC28	58p
AF125	19p	OC35	48p
AF126	20p	OC44	12p
AF127	19p	OC45	12p
AF178	67p	OC71	11p
AF179	66p	OC72	12p
AF180	45p	OC75	20p
AF239	32p	OC200	27p
BC107	11p	OC201	38p
BC108	11p	OC271	60p
BC109	11p	ST140	15p
BC147	12p	ST141	23p
BC148	12p	UT46	35p
BC149	12p	2N696	15p
BC157	15p	2N706A	12p
BC158	14p	2N2926G	14p
BC159	14p	2N2926Y	13p
BD131	75p	2N2926O	12p
BD132	75p	2N3053	25p
BD155	25p	2N3054	60p
BF178	32p	2N3055	72p
BF179*	32p	2N3702	15p
BF180	32p	2N3703	14p
BF181	32p	2N3704	15p
BF184	30p	2N3705	14p
BF185	32p	2N3706	14p
BF194	14p	2N3711	14p
BF195	14p	2N3819	35p
BF196	28p	2N4058	14p
BF197	15p	2N4058	17p
BFW10	70p	2N5459	60p

DIODES

AA119	11p	OA202	10p
OA47	71p	BY100	15p
OA90	71p	BY127	22½p
OA91	6p	BYZ12	22½p

ZENER DIODES

From 2 to 33 volts,
400mW, 15p; 1.5W, 22½p

SILICON BRIDGE RECTIFIERS

40 P.I.V., 1.5A
200 P.I.V., 2.0A **50p**

FUSES AND HOLDERS

1in glass—2½p
60, 100, 150, 250, 500, 750mA; 1, 1.25, 1.5, 2, 2.5, 3, 5, 7.5, 10, 15 amp.
1in glass—2½p
100, 250, 500mA; 1, 2.5 amp.
Anti-surge 1½in—8p
250, 500, 750, 850mA; 1, 1.5, 2, 3 amp.
Anti-surge 20mm—5p
80, 125, 200, 315, 400, 500, 630, 800mA; 1, 2 amp.

PANEL FUSEHOLDERS

For 1½in fuses 18p
For 20mm fuses 15p

CONTROLS, Log. or Lin.

Single, less switch, 15p
Single, D.P. switch, 24p
Tandem, less switch, 40p
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ,
250kΩ, 500kΩ, 1MΩ, 2MΩ

RESISTORS

Carbon
All 5%, high-stability, E12 values.
¼W, 1½p; 1W, 4p; 2W, 6p
Wire-wound
5W, 10p; 10W, 12p

ELECTROLYTICS

1µF	450V	19p	1,000µF	25V	27p
2µF	500V	20p	1,000µF	50V	39p
4µF	350V	14p	2,000µF	25V	36p
8µF	450V	16p	2,000µF	50V	53p
16µF	450V	17p	2,500µF	50V	45p
25µF	50V	9p	2,500µF	50V	60p
32µF	450V	24p	3,000µF	25V	48p
50µF	50V	10p	5,000µF	25V	55p
100µF	25V	10p	5,000µF	50V	98p
100µF	50V	10p	8-8µF	450V	18p
250µF	25V	12p	8-16µF	450V	20p
250µF	50V	17p	16-16µF	450V	37p
500µF	25V	18p	16-32µF	450V	63p
500µF	50V	25p	32-32µF	450V	49p
			50-50µF	350V	38p

MINIATURE ELECTROLYTICS

1µF	25V	10µF	64V
2.5µF	64V	16µF	40V
4µF	40V	25µF	25V
5µF	64V	30µF	15V
8µF	15V	50µF	15V
8µF	40V	100µF	15V
10µF	15V		

ALUMINIUM BOXES with lids and screws

Type	Length	Width	Depth	Price
GB7*	2½in	5½in	1½in	38p
GB8*	4in	4in	1½in	38p
GB9*	4in	2½in	1½in	38p
GB10*	4in	5½in	1½in	44p
GB11	4in	2½in	2in	38p
GB12	3in	2in	1in	33p
GB13	6in	4in	2in	52p
GB14	7in	5in	2½in	63p
GB15	8in	6in	3in	81p
GB16	10in	7in	3in	92p

* These sizes fit standard Verobords

VEROBOARD

Size	0.1 matrix	0.15 matrix
2½in x 3½in	22p	16p
2½in x 5in	24p	15p
3½in x 3½in	24p	25p
3½in x 5in	27p	37p
17in x 2½in	75p	75p
17in x 3½in	£1	75p

Pins—both sizes: packet of 36, 18p

VARIABLE POWER SUPPLY

Input: 240V, a.c.
Output: Switched 3, 4.5, 6, 7.5, **£4-20**
9, 12 volts d.c. at 500mA

CASSETTE OWNERS!

For Philips and similar cassette recorders.
PU12 Power unit for connection to 12V + or -
E car electrical systems. **£3-25**
giving 7½V, stabilised output.

PP75 Mains power supply, output **£1-95**
7½V d.c.
Both units are complete with cable
and 5 pin D.I.N. plug

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The
ideal lining for speaker enclosures. 25p per
yard

MISCELLANEOUS ITEMS

B9A valve bases, 2p
5kΩ edge control, fits most small,
imported radios, 7p
20Ω volume control for 3Ω speakers, 20p
Antex CN240, 15W miniature soldering iron,
£1-70
Valve and Transistor Data book, 9th edition,
75p
Transistor equivalent book, BPI, 40p

LOW-OHM RESISTORS

2½ watt wire-wound, 10,
1.8Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω, **11p**
5.6Ω, 6.8Ω, 8.2Ω

CAPACITORS

2-2pF	500V	S/M	7½p	0.0027µF	500V	S/M	15p
3-3pF	500V	S/M	7½p	0.0031µF	500V	Cer.	5p
5pF	500V	S/M	7½p	0.0033µF	125V	P.S.	6p
10pF	125V	P.S.	5p	0.0033µF	500V	Poly.	6p
10pF	500V	S/M	7½p	0.0033µF	1,000V	MDC	6p
15pF	125V	P.S.	5p	0.0036µF	500V	S/M	15p
15pF	500V	S/M	7½p	0.0047µF	125V	P.S.	9p
15pF	500V	Cer.	4p	0.0047µF	500V	S/M	20p
18pF	500V	S/M	7½p	0.0047µF	1,000V	MDC	6p
22pF	125V	P.S.	5p	0.0051µF	1,000V	Mylar	3p
22pF	500V	S/M	7½p	0.0051µF	500V	Cer.	5p
25pF	500V	S/M	7½p	0.0068µF	125V	P.S.	10½p
27pF	500V	Cer.	4p	0.0068µF	500V	S/M	30p
33pF	125V	P.S.	5p	0.0068µF	500V	Poly.	6p
33pF	500V	S/M	7½p	0.0082µF	125V	P.S.	10½p
39pF	500V	S/M	7½p	0.0082µF	500V	S/M	30p
47pF	125V	P.S.	5p	0.01µF	12V	Disc	4p
47pF	500V	Cer.	4p	0.01µF	125V	P.S.	10½p
50pF	500V	S/M	7½p	0.01µF	160V	Poly.	4p
56pF	500V	S/M	7½p	0.01µF	250V	M.F.	3p
68pF	125V	P.S.	5p	0.01µF	400V	M.F.	3p
68pF	500V	S/M	7½p	0.01µF	500V	Cer.	5p
75pF	500V	S/M	7½p	0.01µF	500V	S/M	30p
82pF	500V	S/M	7½p	0.01µF	600V	MDC	7p
100pF	125V	P.S.	5p	0.01µF	1,000V	MDC	9p
100pF	500V	S/M	7½p	0.015µF	160V	Poly.	3p
100pF	500V	Cer.	4p	0.015µF	400V	Poly.	3p
120pF	500V	S/M	7½p	0.02µF	100V	Mylar	3p
150pF	125V	P.S.	5p	0.022µF	18V	Disc	5p
150pF	500V	S/M	7½p	0.022µF	250V	M.F.	3p
150pF	500V	Cer.	5p	0.022µF	400V	Poly.	3p
180pF	500V	S/M	7½p	0.022µF	600V	MDC	7½p
200pF	500V	S/M	7½p	0.022µF	1,000V	MDC	9p
100pF	125V	P.S.	5p	0.033µF	250V	M.F.	4p
220pF	500V	Cer.	5p	0.033µF	400V	Poly.	4p
250pF	500V	S/M	8p	0.047µF	12V	Disc	6p
270pF	500V	Cer.	5p	0.047µF	160V	Poly.	3p
300pF	500V	S/M	8p	0.047µF	250V	M.F.	3p
330pF	125V	P.S.	5p	0.047µF	400V	Poly.	4p
330pF	500V	S/M	8p	0.047µF	600V	MDC	8p
390pF	500V	S/M	8p	0.047µF	1,000V	MDC	10p
470pF	125V	P.S.	5p	0.1µF	300V	Disc	4p
470pF	750V	Disc	5p	0.1µF	250V	M.F.	6p
500pF	500V	S/M	8p	0.1µF	400V	Poly.	5p
560pF	500V	S/M	8p	0.1µF	600V	MDC	10p
680pF	125V	P.S.	6p	0.1µF	1,000V	MDC	13p
680pF	500V	S/M	8p	0.15µF	250V	M.F.	5p
820pF	500V	S/M	8p	0.22µF	160V	Poly.	6p
0.001µF	100V	Mylar	8p	0.22µF	250V	M.F.	5p
0.001µF	125V	P.S.	6p	0.22µF	400V	Foil	10p
0.001µF	400V	Poly.	10p	0.22µF	1,000V	MDC	15p
0.001µF	500V	S/M	10p	0.33µF	250V	M.F.	8p
0.001µF	500V	Cer.	5p	0.47µF	250V	Foil	8p
0.001µF	1,000V	MDC	6p	0.47µF	400V	Foil	15p
0.0015µF	400V	Poly.	3p	0.47µF	1,000V	MDC	20p
0.0015µF	500V	S/M	10p	1.0µF	250V	M.F.	15p
0.0015µF	500V	Cer.	5p				
0.0018µF	500V	S/M	10p				
0.002µF	100V	Mylar	3p				
0.002µF	500V	Cer.	5p				
0.0022µF	125V	P.S.	6p				
0.0022µF	500V	S/M	10p				
0.0022µF	1,000V	MDC	6p				

Note:
S/M = silver mica 1% tol.
P.S. = polystyrene 2½% tol.
MDC = a.c. rating = 300V.
M.F. = Milspec min. foil.
Cer. = ceramic.

PLUGS

Car aerial
Co-axial
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 4 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
D.I.N. 6 pin
Jack, 2½mm unscreened
Jack, 2½mm screened
Jack, 3½mm unscreened
Jack, 3½mm screened
Jack, ½in unscreened
Jack, ½in screened
Jack, stereo, unscreened
Jack, stereo, screened
Phono, plastic top
Phono, plated metal
Phono, fitted 4 ft lead
Wander, red or black
Banana 4mm, red or black



SOCKETS

Car aerial
Co-axial, surface
Co-axial, flush
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
Jack, 2½mm
Jack, 3½mm
Jack, ½in unscreened
Jack, ½in switched
Jack, stereo, switched
Phono, single
Phono, 2 on a strip
Phono, 3 on a strip
Phono, 4 on a strip
Wander, single, red or black
Wander, twin strip
Banana 4mm red, or black

LINE SOCKETS

Car aerial
Co-axial
D.I.N. 2 pin (speaker)
D.I.N. 3 pin
D.I.N. 5 pin, 180°
D.I.N. 5 pin, 240°
Jack, 3½mm
Jack, ½in screened
Jack, stereo, screened
Phono, plated metal

MAIL ORDERS: C.W.O. only. Please include
10p P. & P. (Air mail extra). S.A.E. with all
enquiries please. Telephone 01-692 4412

THIS FANTASTIC OFFER ONLY FROM US!

SAVE £20.25 NOW!

fabulous BRAND NEW **SOLID STATE**

BATTERY/MAINS AC/DC

This equipment gets EVERYTHING!

Combined **V.H.F AM/FM RADIO** and **CASSETTE TAPE RECORDER & PLAYER**



RECOMMENDED RETAIL PRICE £44

OUR PRICE **£23.75** CARR. ETC. 35p

WITH REMOTE CONTROL MICROPHONE

Latest sensation in the world of sound! First-class makers. Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder and Player combined, AND runs off standard batteries or mains (plug in the 220/240v. AC line cord). Record, play back anything, anywhere! Even tape direct from Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44. WE OFFER AT ALMOST HALF PRICE!** Wonderful features:

- * Press button Keyboard Control panel!
- * New "pop up" Cassette ejection system!
- * "MAGIC EYE" Visual Battery check/recording level indicator or built in automatic leveller.
- * Separate ON/OFF, HI-LO volume controls!
- * Heavy duty built-in speaker!
- * Earphone (for personal listening or "monitoring") and extension speaker socket!
- * Remote control microphone!
- * Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case, size 11 1/2in. x 9 1/2in. 3 1/2in. overall approx., with carry handle. Designs vary slightly. Takes standard 30, 60, 90 or 120-minute Philips Cassette Tapes obtainable everywhere. The amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC, National VHF. Picks up dozens of foreign stations. Also fabulous! In car! You could pay ££££'s mere for a Car Radio or Car Cassette player ALONE! £23.75, CARR. 35p. Simple instructions, remote control microphone with on/off switch and microphone stand. BONUS—Standard Batteries and Cassette Tape 25p extra if required.

COMMERCIAL TRAVELLERS Please note: Merchandising office at our Holborn Store. (PERSONAL SHOPPERS WELCOME AT BOTH STORES).

SHOPERTUNITIES LTD. SL

ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!

BRAND NEW RUSSIAN WORLD BEATER!

6 WAVEBAND WORLD WIDE RECEPTION 10 TRANSISTOR PORTABLE RADIO

£9.97 BOX POST ETC. 43p

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

THE VERY LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS:—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! Instant refund if you are not astounded! Purrr and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even messages from all over the world. Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in length. It's also a fabulous CAR RADIO—any speed requires no additional aerial. **UNIQUE!** Elegant Black, White and Chrome finished case, SIZE 10 1/2in. x 8in. x 3 1/2in. overall approx. Magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

*COMPARE ITS PERFORMANCE with **£34 RADIOS!**

Dept. EE 7, 164 UXBRIDGE ROAD, LONDON W12 8AQ (facing Shepherds Bush Green) (THURSDAY I, FRIDAY 7). Also at 37/39 High Holborn, LONDON, W.C.1 (Thurs. 7). Both stores open from MONDAY-SATURDAY 9 a.m.-6 p.m.

ERSIN Multicore for fast, easy reliable soldering

5 CORE SOLDER

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME CONSTRUCTORS

EASY-TO-USE DISPENSERS



Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

Size 5 (Savbit) 18swg, 18p (illustrated)

Size 19A (60/40 alloy) 18swg. 18p

Size 15 (60/40 alloy) 22swg. 22p

BIB WIRE STRIPPER AND CUTTER



NEW!

Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4 & 6 BA spanner ends, ground cutting edges. Price 32p. Also available, de luxe Model 8. Price 58p.

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

KASPEX

16 SEYMOUR ROAD TILBURY . ESSEX RM18 7AP

Would you believe it, some people still house their constructed projects in 'tatty' looking cases 'bashed out' from aluminium, tin plate, etc., or get involved in complicated carpentry.

No need for this any more!!!

We can supply cases in kit form to house most of your Everyday Electronics projects which will give them a touch of professionalism and a modern appearance with a mirror-like finish. Our cases, which are fabricated from Perspex, Orglass and Acrylic sheet (both in dense and transparent bright colours), are supplied in kit form, their construction being quick and easy and involving the minimum amount of work. Included with the kits are comprehensive assembly details and diagrams. Take the hard work out of making your cases and go MODERN with KASPEX.

ASTRON	£1.40	SOIL MOISTURE METER	£1.00*
DARKROOM TIMER	£1.30	REMOTE TEMP. COMP.	£1.30*
RAIN ALARM	£0.90	BABY ALARM	(pair) £1.50

* State diameter of meter cut-out required when ordering.

All prices include post and packing.

Mail Order only—Cash with order.

SERIOUS AMATEUR CONSTRUCTORS

need components of professional quality. Our Catalogue shows practically the entire range marketed by R.S. Components Ltd. All of these components, used extensively by industry, are now made readily available to amateur constructors.

CATALOGUE, by return of post—only 25p, post free

Some popular examples from our range:

15A. Miniature mains transformer, 2 x 12 volt secondaries	£1.10 each
15C. Hygrade filament transformer, 0-245 volt primary, 2 x 6-3 volt, 1.8 amp secondaries	£1.95 each
39B. Capacitors, paper and polyester 1000 volt 0-001, 0-0022, 0-0033, 0-0047uF	all at 5p each
61B. Small perforated phenolic resin boards, 172 x 133 x 1.57mm, punched 6.35mm grid	22p each
61C. Small turret tags, to suit above boards, 144 per box	95p per box
85C. Plastic cable wrap spiral, 1/4in to secure up to 1/4in cable bunches. Per 5 metre coils	24p each
86D. Insulated 4mm socket terminals, in colours Black, Red, Green, Blue, White, Yellow	14p each
86E. Banana plugs to fit above terminals. Colours as above	6p each

All prices Post Free. Minimum Order 50p. Mail Order only from

CELETRON-E

MAIL ORDER ELECTRONIC COMPONENTS

P.O. BOX No. 1, LLANTWIT MAJOR, GLAMORGAN CF6 9YN



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**


CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83**.



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety; fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**

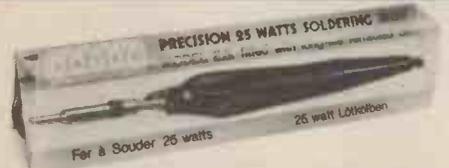CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.


Price **£2.75**



SK. 2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40.**

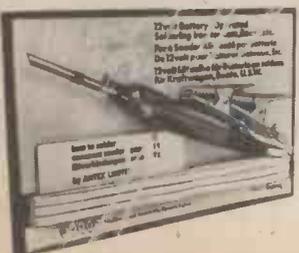

MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95.**

sign here

to answer all
your soldering
problems

I enclose cheque/P.O./Cash
(Giro No. 2581000)


Name _____

Address _____

E.E.5

Please send the Antex
colour catalogue.

Please send the following:

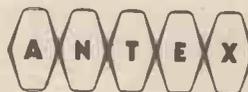

from electrical, radio or car accessory
shops or from Antex Ltd., Freepost
(no stamp required) Plymouth
PL1 1BR Telephone 0752 67377/8

NATION WIDE SERVICE + ATTRACTIVE DISCOUNTS

ELECTROVALUE—an independent company since its establishment in 1965

ELECTROVALUE

Electronic Component Specialists

SEMI-CONDUCTORS

Brand new, guaranteed to spec. No seconds or surplus.

1B40K10	175p	2N2925	22p	2N6163	25p	AD142	50p	BC149	10p	BF167	18p	NKT212	25p
1N914	5p	2N2926	11p	2N5172	18p	AD149	58p	BC163	19p	BF173	19p	NKT213	23p
1N316	10p	2N3053	27p	2N5192	125p	AD160	50p	BC154	20p	BF177	25p	NKT214	23p
1N1783A	24p	2N3054	50p	2N5195	147p	AD161	33p	BC157	12p	BF178	31p	NKT217	50p
1N3784	20p	2N3055	60p	2N5487	49p	AD162	38p	BC168	11p	BF194	14p	NKT261	21p
1N5399	21p	2N3225	53p	2N5489	49p	AD161/162	60p	BC169	12p	BF195	15p	NKT271	18p
1N5402	28p	2N3405	60p	40250	71p	AF114	24p	BC167	11p	BF244	30p	NKT274	18p
1N6407	45p	2N3663	52p	40261	89p	AF115	24p	BC168	10p	BF254	14p	NKT275	23p
1844	9p	2N3702	13p	40361	55p	AF116	22p	BC169	11p	BF255	15p	NKT403	61p
18940	5p	2N3703	13p	40362	68p	AF117	22p	BC177	14p	BFX18	90p	NKT404	61p
2N696	17p	2N3704	13p	40406	75p	AF118	82p	BC178	18p	BFX29	31p	NKT405	79p
2N697	15p	2N3705	13p	40408	70p	AF124	24p	BC179	14p	BFX84	25p	NKT603F	30p
2N706	12p	2N3706	13p	40412	87p	AF125	24p	BC182L	14p	BFX85	32p	NKT613F	30p
2N930	21p	2N3707	13p	40430	140p	AF126	22p	BC1838	10p	BFX87	29p	NKT674F	24p
2N1131	20p	2N3708	10p	40432	185p	AF127	22p	BC184L	11p	BFX88	28p	NKT677F	24p
2N1132	20p	2N3709	11p	40512	195p	AF129	33p	BC185	42p	BFX50	23p	NKT713	30p
2N1302	10p	2N3710	13p	40602	52p	AF239	36p	BC212L	16p	BFY51	20p	NKT773	25p
2N1303	19p	2N3711	13p	40669	140p	AL192	77p	BC213L	16p	BFY52	23p	OA47	8p
2N1304	20p	2N3731	13p	AC107	48p	AS226	27p	BC214L	16p	BFY90	104p	OA90	8p
2N1305	28p	2N3794	15p	AC126	20p	AS227	36p	BC25	6p	BSX20	16p	OA91	5p
2N1306	33p	2N3819	23p	AC127	20p	AS228	27p	BC258	8p	BF164	45p	OA95	6p
2N1307	33p	2N3820	23p	AC128	20p	AS229	36p	BC259	8p	BF259	18p	OA200	8p
2N1308	36p	2N3904	35p	AC141H	34p	AU111	87p	BC267	17p	BXX38-300	38p	OA202	10p
2N1309	36p	2N3906	35p	AC141HK	37p	B30C250	24p	BC268	15p	BXX38-300R	38p	OC19	50p
2N1396	100p	2N4036	55p	AC142H	25p	B30C550/300	34p	BC269	17p	C407	17p	OC25	42p
2N1599	12p	2N4058	13p	AC142HK	29p	B1912	82p	BC300	48p	CF62	19p	OC28	70p
2N1613	23p	2N4059	10p	AC153K	23p	B5041	72p	BC301	37p	CL142	102p	OC29	78p
2N1711	28p	2N4060	11p	AC176	16p	BA102	25p	BC303	60p	CE2512	184p	OC35	60p
2N1893	54p	2N4061	11p	AC176K	17p	BA130	28p	BCY30	60p	EA403	10p	OC36	65p
2N2147	95p	2N4062	12p	AC187K	17p	BA145	27p	BCY31	75p	EB383	10p	OC41	42p
2N2218	34p	2N4124	18p	AC188K	23p	BA155	15p	BCY70	18p	EC401	18p	OC42	48p
2N2218A	44p	2N4125	27p	*AC187K/188K	48p	BA159	13p	BCY71	35p	EC402	17p	OC44	38p
2N2219	58p	2N4284	24p	40	40p	BA1X13	13p	BCY72	18p	ER900	64p	OC45	42p
2N2219A	53p	2N4286	15p	ACY17	31p	BB103/B	18p	BD121	105p	MC140	25p	OC70	28p
2N2270	62p	2N4289	15p	ACY18	19p	BB103/G	18p	BD123	105p	MJ481	120p	OC71	38p
2N260A	19p	2N4291	15p	ACY19	23p	BC107	12p	BD124	105p	MJ491	135p	OC72	38p
2N2483	35p	2N4292	15p	ACY20	20p	BC108	11p	BD130	50p	MJ371	108p	OC75	40p
2N2484	42p	2N4410	24p	ACY21	21p	BC109	12p	BD131	79p	MJ E21	92p	OC81	25p
2N2484	42p	2N4410	24p	ACY21	21p	BC109	12p	BD132	86p	MJ E2055	165p	OC81D	25p
2N2484	42p	2N4443	11p	ACY22	21p	BC122	22p	BD132	86p	MJ E2055	165p	OC81D	25p
2N2904	38p	2N4906	305p	ACY39	63p	BC125	15p	BD135	38p	MJ E3055	82p	OC83	25p
2N2904A	42p	2N4915	215p	ACY40	17p	BC126	22p	BD136	44p	MPF102	37p	OC84	25p
2N2905	44p	2N4911	62p	ACY41	18p	BC140	30p	BD141	22p	MPS6531	35p	P346A	26p
2N2905A	47p	2N5082	61p	ACY44	31p	BC147	10p	BDY20	22p	MP86534	30p	82CN1	10p
2N2924	20p	2N5088	38p	AD140	63p	BC148	9p	BF115	23p	NKT211	25p	* Matched pair	

1972 ELECTROVALUE CATALOGUE

Biggest and best edition yet—packed with hundreds of items at keen prices, valuable information and diagrams post free 10p

COMPONENT DISCOUNTS

allowed on all items other than those at NET prices.

10% on orders for £5 or more 15% on orders for £2.00 or more. Please add 10p if under.

Overseas orders welcomed. Prices subject to alteration without prior notice.

Terms of business—C.W.O. as in catalogue

We are now approved distributors for

ELREMCO SOLDERSTAT SOLDERING IRONS

A popular and beautifully made lightweight example from a wide and versatile range of soldering irons of exceptional quality. Type HMS for 16 or 24 watts, A.C. mains. £1.70

Minitron DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available. In 16 lead dil case £2.00

Suitable BCD decoder driver type £1.35

DL1121T £1.35
Fill Socket: 16 lead 30p. No. 3015G showing + or - and fig. 1 and decimal point £2.00.

CAPACITORS

SIEMENS 5% POLYCARBONATES

250V up to 0.1mf; 100V 0.1mf and above
0.01, 0.012, 0.015, 0.018, 0.022, 0.025, 0.03, 0.033, 0.039, 0.045, 0.056, 0.068, 0.082, ... 5p
0.01, 0.012, 0.015, 0.018, 0.022 ... 6p
0.27, 7p; 0.33, 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p, 1.00 13p

MULLARD polyester C280 series

250V 20%; 0.01, 0.022, 0.33, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p, 10%; 0.33, 7p; 0.47, 8p; 0.68, 11p; 1.0, 14p; 1.5, 17p, 21p; 2.2, 24p, 24p.

MULLARD SUB-MIN ELECTROLYTICS

C26 range, axial lead ... 6p each
Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/10; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 152/4; 125/10; 125/16; 150/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91.

Simple to Build, Astonishingly Good

10W/15Ω BAXENDALL SPEAKER

As originally designed, by P. J. Baxendall and described in *Wireless World*, 10 watt/15 ohm loudspeaker with equaliser network speaker unit and specially designed cabinet in kit form. Size when built approx. 18" x 12" x 10". Price inc. carriage paid in U.K. Nett £13.90.

HANDBOOK OF TRANSISTOR EQUIVALENTS.

40p. HANDBOOK OF TESTED TRANSISTOR CIRCUITS (H. Ness), 40p. RADIO & ELECTRONICS. Colour codes & data wall chart, 15p

ENGINEERS REFERENCE CATALOGUE

Handbook & Tables 20p. (Add 3p. for postage on each of above if bought separately.)

CARBON TRACK POTENTIOMETERS, long spindles.

Double wipers
SINGLE GANG linear 100Ω to 2.2MΩ, 12p; Single gang log 4.7KΩ to 2.2MΩ, 11p; Dual gang linear 4.7KΩ to 2.2MΩ, 42p; Dual gang log, 4.7KΩ to 2.2MΩ, 42p; Log/antilog, 10K/47K, 1MΩ only 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 & 47 available in ranges quoted.
DUAL CONCENTRIC in any combination of above values, 60p; with switch, 72p.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

ZENER DIODES 5% full range E24 values: 400mW: 2.7V to 36V, 15p each; 1W, 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each.
Clip to increase 1.5W rating to 3 watts (type 266F), 4p.

RESISTORS—10%, 6%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	9	8-0	7
C	1/8W	5%	4.7 Ω-470K Ω	E24	1	0-8	0-7
C	1/4W	10%	4.7 Ω-10M Ω	E12	1	0-8	0-7
C	1/2W	5%	4.7 Ω-10M Ω	E24	1-2	1	0-9
C	1W	10%	4.7 Ω-10M Ω	E12	2-5	2-5	1-8
MO	1/2W	2%	10 Ω-10 Ω	E12	7	7	6
WW	1W	10% ± 1/20 Ω	0.22 Ω-3.9 Ω	E12	7	7	6
WW	3W	5%	12 Ω-10K Ω	E12	7	7	6
WW	7W	5%	12 Ω-10K Ω	E12	9	9	8

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, ElectroSil TR5, ultra low noise.
WW = wire wound, Plessey.
Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

30W BAILEY AMP. PARTS

Transistors and PCB for one channel, £6.46. Rs Kit for one channel, £1.95. Power Supply Kit (Unreg.).

MAIN LINE AMPLIFIER KITS

70 watt power amp. module kit, £12.60 nett. Power supply kit, £6.00 nett. Matching pre-amp kit, £3.30 nett. (Above prices for mono.) Stereo Kit, 2 power amps, pre-amp kit, power supply kit and matched controls for building into your own cabinet, £38.40 nett.
S-DeC, £1.44; Four pack, £5.10. DeCSTOR pack, £2.88, T-Dec, may be temperature cycled (208 points), £2.88. µDecA £3.18. µDecB, £5.94. Also integrated circuit carriers.

TERMINATORS

VAI039, VAI040, VAI055, VAI066, VAI077, VAI088, K151-K, VAI100, 15p. R24, R53, R54, £1.35.

INSULATED SCREW TERMINALS

In range of seven colours, each 12p. Matching plugs: 2mm, each 5p; 4mm, each 7p. Sockets, hardware, Veroboard, edge connectors, switches, etc., in stock at keen prices.

ELECTROVALUE

DEPT. EE572, 28 St. Judes Road, Englefield Green, Egham, Surrey. TW20 0HB
Hours: 9-5.30, 1.0 p.m. Saturdays. Phone: Egham 5533 and 4757 (STD 0784-3)
Telex 264475

BUDGET HIGH-FIDELITY STEREO SYSTEMS



ONLY
£40-95
carr. £1-75

FREE
LEADS
AND PLUGS
SUPPLIED
WITH ALL
SYSTEMS

PREMIER STEREO SYSTEM "ONE" Consists of the new Premier 800 all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 400 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Mono/Stereo switch. Stereo Headphone socket. Black leatherette cabinet with aluminium front panel. Size: 12 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ". (Amplifier available separately if required £16-25. Carr. 50p).

PREMIER STEREO SYSTEM "TWO", as above but with Garrard 8P25 MK III and magnetic cartridge. **ONLY £48.** Carr. £1-75.

METER BARGAINS



MODEL GT-800 MULTIMETER
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. **RANGES**—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltages: 10, 50, 250, 1,000V (1,000opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibels: -10 +22db (at AC 10V range) £2-47. P. & P. 25p.



MULTIMETER 20,000 O.P.V.
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size 4 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1". **RANGES**—DC Voltages: 0-5-25-50-250-500-2500V. A.C. Voltages: 0-12-50-100-500-1000V. D.C. Current: 0-50µA-2-5mA-250mA. Resistance: 0-6000 ohms-0-6 megohms (300 ohms and 30 Kohms, at centre scale). Capacity: 10µF to .001µF, .001µF to .1µF. Decibels = 20 to +22dB. £4-90. P. & P. 25p.



MODEL CT-62 MULTITESTER
RANGES—DC Voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50µA, 0, 5, 50, 500mA. Resistance: 0, 5k, 500k, 5M, 50M ohms. Decibels: -20 db to +62 db in 5 ranges. £5 62. P. & P. 25p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. £3-95. P. & P. 50p



"Marksman" Soldering Iron. Lightweight $\frac{1}{2}$ " pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1-50 P. & P. 15p

VERITAS V-313 TAPE HEAD DEFLUXER



A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. £1-72 P. & P. 15p.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250'	P.V.C.	25p	LP8 5 $\frac{1}{2}$ " 1200'	P.V.C.	75p
TT3 3" 450'	POLYESTER	37p	DT8 5 $\frac{1}{2}$ " 1800'	POLYESTER	£1-12
DT3 3 $\frac{1}{2}$ " 600'	POLYESTER	57p	TT8 5 $\frac{1}{2}$ " 2400'	POLYESTER	£1-87
SP5 5" 600'	P.V.C.	42p	SP7 7" 1200'	P.V.C.	62p
LP5 5" 900'	P.V.C.	50p	LP7 7" 1800'	P.V.C.	75p
DT5 5" 1200'	POLYESTER	75p	DT7 7" 2400'	POLYESTER	£1-25
			TT7 7" 3600'	POLYESTER	£2-50

TAPE SPOOLS 3" 5p, 5", 5 $\frac{1}{2}$ ", 7" 9p.
Post and Packing 3" 5p, 5", 5 $\frac{1}{2}$ ", 7" 10p (3 reels and over Post Free).



PREMIER HI-FI OFFERS

- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52-50) **£38-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**
- Metrosound ST20E Stereo Amplifier in teak case (List £39-50) **£28-50**
- Thorens TD150A/II turntable with arm **£31-00**
- Garrard SP25 III with Goldring G800 cartridge (List £28-35) **£15-50**

SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK PLINTH WITH COVER. Total list price over £34.

PREMIER PRICE
£18-90
P. & P. 50p.

Garrard AP76 with G800, ready wired to 5 pin Din in plinth with cover **£29-95**


Garrard AP76 less cartridge **£19-50**

Garrard 401 Transcription Unit List £40-15) **£28-00**

Garrard 2025 T/C with Stereo Ceramic Cartridge **£9-97**
Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover **£12-45**

Carriage and Insurance 60p extra any item.

PREMIER 800 STEREO AMPLIFIER

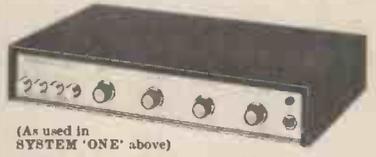

(As used in SYSTEM "ONE" above)
A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ ".

ONLY £16-25 Carr. 50p.

HI-FI STEREO HEADPHONES



Designed to the highest possible standard. Fitted 2 $\frac{1}{2}$ in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug. **£2-47** P. & P. 25p.

STEREO STETHOSCOPE SET Low Imp. £1-25 P.&P. 10p
MONO STETHOSCOPE SET Low Imp. 52p. P. & P. 10p

E.M.I. 13x8in. HI-FI SPEAKERS



Fitted two 2 $\frac{1}{2}$ in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new. **£3-47** P. & P. 40p

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case.



MONO MODEL **£3** STEREO MODEL **£3.47** P. & P. 15p

TAPE CASSETTES

- | | | |
|-----------------|-----|-------------|
| C60 (60 min.) | 37p | 3 for £1-05 |
| C90 (90 min.) | 62p | 3 for £1-80 |
| C120 (120 min.) | 87p | 3 for £2-55 |
- P. & P. 5p.

FREE Cassette Head Cleaner with every 10 cassettes
All cassettes can be supplied with library cases at 3p. extra each



PREMIER RADIO | OXFORD ST | 23 TOTTENHAM COURT RD | DOMINION
23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451

DISCOUNTS UP TO 30% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

Garrard SP25 Mk. III SPECIAL £18
Goldring G800H OFFER
Teak plinth and tinted cover. Ready wired for immediate use.
Please add £1.25 for P & P.

TURNABLES
Please add 75p for P. & P.
Garrard SP25 Mk. III £9.95
Garrard AP76 £19.95
Garrard SL65B £13.25
Garrard 401 £27.00
Garrard Zero 100 (Auto) £39.95
Garrard Zero 100 (Single) £37.25
Garrard SL72B £24.00
Garrard SL75B £26.00
Garrard SL95B £35.00
BSR MP60 £10.00
Goldring GL72 £27.50
Goldring GL75P £29.25
Goldring GL75 £27.50
Goldring GL75/P £35.50
Wharfedale Linton & cart. £27.75
Thorens TD125 £57.75
Thorens TD125AB £90.00
Thorens TD150 Mk. II £28.00
Thorens TD150A Mk. II £33.75

AMPLIFIERS
Please add 75p P. & P.
Amstrad 8000 Mk. II £16.95
Amstrad IC2000 £27.90
Armstrong 521 (teak cased) £43.95
Alpha Highgate 212 £25.00
Alpha Highgate FA300 £27.95
Alpha Highgate FA400 £31.95
Cambridge P100 £116.00
Cambridge P40 £65.95
Cambridge P50 £71.00
Ferrograph F307 Mk. II (Wood cased) £47.50
Ferrograph F307 Mk. II (Metal cased) £45.00
Leak Delta 30 £48.00
Leak Delta 70 £56.00
Metrosound ST20E £24.75
Metrosound ST60 £47.25
Pioneer SA600 £58.00
Pioneer SA700 £66.50
Pioneer SA800 £73.95
Pioneer SA900 £92.00
Pioneer SA1000 £94.00
Rogers R/brook (Chassis) £35.00
Rogers R/brook (Cased) £37.00
Rogers R/bourne (Chassis) £41.50
Rogers R/bourne (Cased) £46.50
Sinclair PRO60 2 x Z30/PZ5 £15.25
Sinclair PRO60 2 x Z30/PZ6 £17.50
Sinclair PRO60 2 x Z50/PZ8/Trans £21.75
Sinclair AFU (Filter Unit) £41.50
Sinclair 605 £18.75
Sinclair 2000 Mk. II £21.75
Sinclair 3000 Mk. II £29.75
Sugden A21/11 £51.50
Sugden AS1/CS1 £102.00
Wharfedale Linton £39.95
Goodmans Max Amp £37.95
Teleton SAQ206B £21.50
Teleton SAQ306B £22.95
Europion 10 + 10 £16.95

TUNERS
Please add 75p P. & P.
Armstrong 253 £39.50
Armstrong 524 £31.00
Rogers Ravensbrook FET4 (Chassis) £31.00
Rogers Ravensbrook FET4 (Cased) £35.00
Rogers Ravenbourne FET4 (Chassis) £43.00
Rogers Ravensbrook FET4 (Cased) £48.00
Sinclair PRO60 (Module) £18.50
Sinclair Cased Tuner £34.00
Phillips RH690 £33.00
Leak Delta FM (Cased) £55.50
Leak Delta AM/FM (Cased) £66.50

TUNER/AMPLIFIERS
Please add 75p for P. & P.
Alpha Highgate 150 £44.95
Alpha Highgate R500 £64.50
Armstrong 525 (Teak cased) £68.50
Armstrong 526 AM/FM £78.50
(Teak cased)
Leak Delta 75 £130.95
Phillips RH781 £50.00
Phillips RH 882 (+cass head) £72.00
Phillips RH702 £82.50
Teleton 2100 £29.95
Goodmans One Ten £105.00
Rogers R/brook (Teak) £80.00
Rogers R/brook (Chassis) £74.50

SPEAKERS
Please add £1.25 P. & P. per pair
Amstrad I38 £20.00
Wharfedale Denton 2 £29.00
Wharfedale Linton 2 £37.00
Wharfedale Helton 2 £47.95
Wharfedale Doveedale 3 £61.50
Celestion Ditton 120 £39.00
Celestion Ditton 15 £55.00
Celestion Ditton 25 £89.00
Goodmans Double Maxim £48.50
Goodmans Mezzo 3 £45.75
Goodmans Magister £78.25
Sinclair Q16 £12.50

£3.20* 
Plus 35p p. & p.
Finished in teak veneer with tinted dust cover fully assembled. For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 55p P. & P.
Also finished in walnut to match Japanese equipment—at no extra.
CARTRIDGES
Please add 10p for P. & P.
Goldring G850 £3.65
Goldring G800 £6.25
Goldring G800E £10.35
Goldring G800 Super E £15.75
Shure M3D £4.50
Shure M44E £6.25
Shure M55E £6.75
Shure M75E Type 2 £12.25
Sonotone 9TAHC £1.85

TRANSISTORS & DIODES

A Selection From Our Wide Range

AC107	30p	BF163	35p	MPP102	42p	OC201	60p	2N1307	84p
AC126	20p	BF167	18p	MPP103	35p	OC202	75p	2N1308	30p
AC127	25p	BF173	19p	MPP104	37p	OC203	40p	2N1309	30p
AC128	20p	BF177	25p	MPP105	40p	OC204	40p	2N1507	23p
AC131	15p	BF178	31p	NKT112	30p	OC205	75p	2N1613	15p
AC152	15p	BF180	35p	NKT125	40p	OC206	90p	2N1711	15p
AC153	10p	BF181	35p	NKT126	37p	OC207	75p	2N2147	75p
AO176	25p	BF184	20p	NKT128	25p	OC217/M	42p	2N2148	60p
AO187	25p	BF185	25p	NKT211	25p	ORP12	60p	2N2160	67p
AO188	25p	BF194	17p	NKT212	25p	ORP60	40p	2N2388	17p
ACY117	27p	BF195	15p	NKT213	25p	ORP61	40p	2N2389	17p
ACY118	27p	BF196	15p	NKT216	46p	P346A	19p	2N2389A	19p
ACY19	20p	BF200	35p	NKT217	50p	SL403D	£1.50	2N2644	47p
ACY20	20p	BFX13	25p	NKT218	25p	SL140	15p	2N2904	44p
ACY21	18p	BFX29	25p	NKT219	25p	SL141	20p	2N2904A	48p
ACY22	10p	BFX84	25p	NKT223	27p	TIP31A	82p	2N2906	65p
ACY40	15p	BFX85	34p	NKT271	18p	TIP32A	74p	2N2909A	76p
AD140	15p	BFX86	25p	NKT272	17p	TI888A	45p	2N2906	44p
AD149	50p	BFX87	30p	NKT274	18p	UL900	40p	2N2906A	54p
AD149	50p	BFX88	24p	NKT275	20p	UL914	40p	2N2926 all	
AD161	36p	BFY50	22p	NKT278A	12p	UL923	40p	coloura	10p
AD162	38p	BFY51	18p	NKT281	29p	V405A	46p	2N3053	20p
AF106	24p	BFY52	20p	NKT403	65p	ZTX108	11p	2N3064	60p
AF114	25p	BFY53	17p	NKT404	60p	ZTX309	15p	2N3055	60p
AF115	25p	BFY54	67p	NKT461	58p	ZTX302	18p	2N3072	10p
AF116	25p	BSX19	18p	NKT452	54p	ZTX303	15p	2N3703	10p
AF117	26p	BSX20	16p	NKT713	20p	ZTX304	27p	2N3704	11p
AF118	44p	BSX21	20p	OA5	20p	ZTX314	11p	2N3705	10p
AF124	25p	BSY27	20p	OA10	25p	ZTX320	30p	2N3706	9p
AF126	17p	BSY28	25p	OA47	8p	ZTX330	18p	2N3707	11p
AF139	30p	BSY55A	12p	OA70	8p	ZTX309	15p	2N3708	7p
AF186	40p	BY100	15p	OA73	8p	ZTX501	16p	2N3709	9p
AF239	36p	BY127	15p	OA79	8p	ZTX502	20p	2N3710	9p
AF279	47p	BY210	85p	OA81	8p	ZTX503	17p	2N3711	9p
ASV26	25p	BYZ12	30p	OA85	8p	ZTX504	40p	2N3819	35p
ASV27	30p	BYZ13	20p	OA90	8p	IN914	7p	2N3820	60p
ASV28	22p	BZY78	18p	OA91	8p	IN4001	7p	2N3826	30p
ASV29	30p	CV3	15p	OA95	8p	IN4002	7p	2N4058	15p
ASZ21	37p	CV6	15p	OA200	10p	IN4003	10p	2N4060	12p
BC107	10p	CV9	15p	OA202	10p	IN4004	10p	2N4061	12p
BC108	10p	CAV3	15p	OC19	37p	IN4005	12p	2N4062	12p
BC109	10p	CAV7	15p	OC20	97p	IN4006	16p	2N4289	15p
BC147	10p	CV1	15p	OC22	47p	IN5756	98p	2N4871	40p
BC148	8p	CV6	15p	OC23	60p	IN4007	20p	2N5245	45p
BC149	10p	CV2	15p	OC24	60p	IN4148	7p	40250	55p
BC158	11p	CV8	15p	OC25	37p	2G302	15p	40309	33p
BC167	11p	CV5	15p	OC26	33p	2G371	15p	40310	45p
BC168	10p	CV2	15p	OC28	60p	2G374	25p	40312	48p
BC169	11p	CV1	15p	OC29	60p	2N174	80p	40320	47p
BC189C	15p	C10	15p	OC35	50p	2N385A	50p	40360	43p
BC182	10p	C11	15p	OC36	63p	2N388A	50p	40361	47p
BC182L	10p	C12	15p	OC41	25p	2N404	25p	40362	65p
BC183	9p	C13	15p	OC42	30p	2N696	15p	40406	58p
BC183L	10p	C15	15p	OC44	15p	2N697	17p	40407	39p
BC184	18p	C16	16p	OC45	12p	2N698	30p	40408	61p
BC184L	12p	C18	15p	OC71	12p	2N706	10p	40409	54p
BC192	12p	C20	15p	OC72	12p	2N708A	12p	40410	62p
BC192L	12p	C22	15p	OC75	23p	2N708	16p	40468A	58p
BCY30	26p	C24	15p	OC76	25p	2N711	37p	40600	35p
BCY31	48p	C27	15p	OC77	40p	2N711A	37p	40601	65p
BCY32	50p	C30	15p	OC81	20p	2N911	50p	40602	40p
BCY33	20p	CR1/061C	40p	OC81D	20p	2N914	20p	40603	49p
BCY34	25p	CR1401C	60p	OC81Z	55p	2N918	45p	40486	95p
BCY38	30p	CRS305AF	£1.08	OC82	25p	2N1090	30p	40430	97p
BCY70	15p	CR8/305AF	£1.08	OC82D	15p	2N1091	35p	40432	£1.37
BCY71	30p	CR83/40AF	£1.08	OC83	23p	2N1131	30p	40512	£1.45
BCY72	16p	D1	£1.53	OC84	25p	2N1132	30p	40576	£1.70
BD124	75p	DI3T1	£1.53	OC139	25p	2N1302	17p		
BD131	75p	MJ520	50p	OC140	35p	2N1303	17p		
BD132	75p	MJ480	97p	OC170	25p	2N1304	25p		
BDY20	£1.05	MJ481	£1.25	OC171	30p	2N1305	25p		
BF115	23p	MJ491	£1.35	OC200	40p	2N1306	24p		

TERMS: Retail Mail order subject to 50p minimum order. Cash with order only.

Postage: 10p inland; 25p Europe; elsewhere—send plenty, will refund.

Guarantee: All goods carry Manufacturers' warranty. Counter sales: Same address—open weekdays and Saturdays.

LST ELECTRONIC COMPONENTS LTD

Mail Order Dept. (EE)

7 COPTFOLD ROAD, BRENTWOOD, ESSEX.



All prices correct at time of press E. & O.E.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE7) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.
MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that credits can only be accepted together with cheque cards (not Barclay Card).
2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS



TYPESW.100
100 x 80 mm.

500μA	...	23-80
50-0-500μA	...	23-45
100μA	...	23-20
100-0-100μA	...	23-45
500μA	...	23-85
1mA	...	23-10
20V. D.C.	...	23-10
50V. D.C.	...	23-10
300V. D.C.	...	23-10
1 amp. D.C.	...	23-10
5 amp. D.C.	...	23-10
300V. A.C.	...	23-10
VU Meter	...	23-75

TYPE S-80
80 mm.
square fronts

50μA	...	23-80
50-0-50μA	...	23-10
100μA	...	22-75
100-0-100μA	...	23-10
500μA	...	23-00
1mA	...	22-80
20V. D.C.	...	22-80
50V. D.C.	...	22-80
300V. D.C.	...	22-80
1 amp. D.C.	...	22-80
5 amp. D.C.	...	22-80
300V. A.C.	...	22-80
VU Meter	...	23-37

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts.



50μA	...	23-80
50-0-50μA	...	23-10
100μA	...	23-10
100-0-100μA	...	23-10
500μA	...	22-80
500-0-500μA	...	22-80
1mA	...	22-80
1-0-1mA	...	22-80
5mA	...	22-80
10mA	...	22-80
10V. D.C.	...	22-80
50V. D.C.	...	22-80
300V. D.C.	...	22-80
15V. A.C.	...	22-80
300V. A.C.	...	22-80
8 Meter 1mA	...	22-87
VU Meter	...	23-60
1 amp. A.C.*	...	22-80
5 amp. A.C.*	...	22-80
10 amp. A.C.*	...	22-80
20 amp. A.C.*	...	22-80
30 amp. A.C.*	...	22-80

Type MR.35P. 1 21/32 in. square fronts.



50μA	...	22-10
50-0-50μA	...	21-80
100μA	...	21-80
100-0-100μA	...	21-75
200μA	...	21-75
500μA	...	21-85
500-0-500μA	...	21-80
1mA	...	21-80
1-0-1mA	...	21-80
2mA	...	21-80
5mA	...	21-80
10mA	...	21-80
20mA	...	21-80
50mA	...	21-80
100mA	...	21-80
150mA	...	21-80
5 amp.	...	21-70
10V. D.C.	...	21-80
20V. D.C.	...	21-80
50V. D.C.	...	21-80
300V. D.C.	...	21-80
30V. D.C.	...	21-80
15V. A.C.	...	21-70
15V. A.C.	...	21-70
30V. A.C.	...	21-70
150V. A.C.	...	21-70
300V. A.C.	...	21-70
8 Meter 1mA	...	21-70
VU Meter	...	22-10

Type MR.45P. 2 in. square fronts.

50μA	...	22-25
50-0-50μA	...	22-10
100μA	...	22-10
100-0-100μA	...	21-87
200μA	...	21-87
500μA	...	21-75
500-0-500μA	...	21-70
1mA	...	21-70
5mA	...	21-70
10mA	...	21-70
20mA	...	21-70
50mA	...	21-70
100mA	...	21-70
500mA	...	21-70
1 amp.	...	21-70
5 amp.	...	21-70
10V. D.C.	...	21-80
20V. D.C.	...	21-80
50V. D.C.	...	21-80
300V. D.C.	...	21-80
30V. D.C.	...	21-80
15V. A.C.	...	21-80
15V. A.C.	...	21-80
30V. A.C.	...	21-80
150V. A.C.	...	21-80
300V. A.C.	...	21-80
8 Meter 1mA	...	21-85
VU Meter	...	22-25

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/4 in. square fronts.

50μA	...	23-50
50-0-50μA	...	22-75
100μA	...	22-35
100-0-100μA	...	22-25
500μA	...	22-20
1mA	...	21-95
1-0-1mA	...	21-95
5mA	...	21-95
10mA	...	21-95
50mA	...	21-95
100mA	...	21-95
500mA	...	21-95
1 amp.	...	21-95
5 amp.	...	21-95
10V. D.C.	...	21-95
20V. D.C.	...	21-95
50V. D.C.	...	21-95
300V. D.C.	...	21-95
30V. A.C.*	...	21-85
150V. A.C.*	...	21-85
300V. A.C.*	...	21-85
500mA A.C.*	...	21-95
1 amp. A.C.*	...	21-95
5 amp. A.C.*	...	21-95
10 amp. A.C.*	...	21-95
20 amp. A.C.*	...	21-95
30 amp. A.C.*	...	21-95
50 amp. A.C.*	...	21-95
VU Meter	...	23-10

EDGEWISE METERS

Type PE.70. 3 1/2" x 1 1/2" x 2 1/2" in. deep.	50μA	...	23-10
	50-0-50μA	...	23-00
	100μA	...	23-00
	100-0-100μA	...	22-90
	200μA	...	22-90
	500μA	...	22-75
	1mA	...	22-45
	300V. A.C.	...	22-45
	VU Meter	...	23-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

***MOVING IRON—ALLOTTHERS MOVING COIL**
Please add postage

SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments. Ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is demonstrably internal working. Available in the following ranges:

50μA	...	24-40
100μA	...	24-40
1mA	...	24-40
50-0-50μA	...	24-40
1-0-1mA	...	24-40
5A d.c.	...	24-40
1A d.c.	...	24-40
5V/50V d.c.	...	24-65
20V d.c.	...	24-40
50V d.c.	...	24-40
300V d.c.	...	24-40
20V d.c.	...	24-40
50V d.c.	...	24-40
300V d.c.	...	24-40
500mA/5A d.c.	...	24-65
5V/50V d.c.	...	24-65
10V d.c.	...	24-40

MULTIMETERS for EVERY purpose!



MODEL LT.101 1000 O.P.V.
0/10/50/250/1000 V. D.C.
0/10/50/250/1000 V. A.C.
0/1/100 M.A. 0/150 K ohms.
£1.97. P. & P. 15p.



MODEL PL436
20k Ω/Volt D.C.
8k Ω/Volt A.C.
Mirror scale.
0/3/12/30/120/600V
D.C. 3/30/120/600V
A.C. 50/600/60/600
600 mA. 10/100K/1
1 Meg/10 Meg Ω
120V. A.C.
-20 to +46db. 28-971. P. & P. 121p.



MODEL 5025 57 Ranges,
Giant 5 1/2 in. Meter. Polarity Reverse Switch.
Sensitivity: 50k/Volt D.C.
5K/Volt A.C. D.C. Volt: -125, -25, -1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V.
A.C. Volt: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V.
D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp.
Resistor: 2K, 10K, 100K 1MEG, 10MEG. Decibels: -20 to +85 dB. £12.50. P. & P. 174p.



HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale.
3/6-1/2-1/5/3/6/12/30/60/120/300/600/1200VDC
1.5/3/6/12/30/60/150/300/600/1200 V. A.C.
15/30mA/3/6/30/60/150/300 mA
6/12 AMP. DC. 2K/20K/2 Meg/20 Meg ohm -20 to +63 db. £13.50. P. & P. 20p.

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68



Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 ohm p.v. Resistance 0/500K ohms. ONLY £1.97 P. & P. 13p

TMK MODEL 117 P.E.T. ELECTRONIC VOLT METER



Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0-3-1200V. AC VOLTS 3-300V RMS. 8-0-800V P-P. DC CURRENT 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51 db. Complete with leads/instructions. £17.50. P. & P. 20p.

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 Kcfs-500 Mcfs on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. X1 socket for calibration. 220/240V. A.C. Brand new with instructions. 215. Carr. 374p. Size 140 x 215 x 170 mm.

TE22 SINE SQUARE WAVE AUDIO GENERATORS




Sine: 20cps to 200 Kcfs on 4 bands. Square: 20cps to 30 Kcfs. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £17.50. Carr. 374p.

TE-20RF SIGNAL GENERATOR




Accurate wide range signal generator covering 120 Kcfs-260 Mcfs on 6 bands. Directly calibrated variable R.F. attenuator. Operation 0/20/240V. A.C. Brand new with instruction. 215. P. & P. 374p. S.A.E. for details.

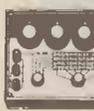
TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



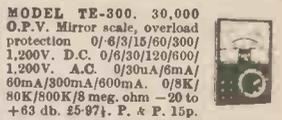
A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 meg Ω. 6 Ranges ± 1%. L. 1 μH - 111 μH. H. 100Ω-1100Ω. P.D. 5 Ranges ± 2%. TURNS RATIO 1:1/100:1. 1:1/100. 5 Ranges ± 1%. Bridge voltage at 1,000 ops. Operated from 9 volts. 100μA Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2. £20. P. & P. 35p



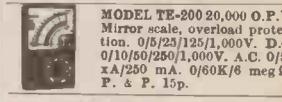MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection 0/6/3/15/60/300/1,200V. D.C. 0/6/3/12/60/1,200V. A.C. 0/30μA/6mA/60mA/300mA/600mA. 0/8K/80K/500K/8 Meg. ohm -20 to +63 db. 25-971. P. & P. 15p.



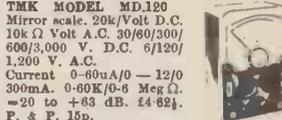MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50 μA/5/60/600/600K/6 Meg. Ω/6 Meg Ω. P. & P. 15p.



TMK MODEL MD.120 Mirror scale. 20k/Volt D.C. 10k Ω Volt A.C. 50/60/300/1,200/3,000 V. D.C. 6/120/1,200 V. A.C. Current -0.60μA/0 -12/30 mA. 0-60K/0-6 Meg Ω. -20 to +63 dB. £4.624. P. & P. 15p.



MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/5/25/10/25/100/250/500/1,000 V. D.C. 0/2.5/10/25/100/250/500/500μA/5/60/600/600K/6 Meg Ω/6 Meg Ω. £8.74. Post paid.



TMK LAB TESTER. 100,000 O.P.V. 6 1/2 in. Scale. Buckner Short Circuit Checker. Sensitivity: 100,000 O.P.V. D.C. 5K/Volt A.C. D.C. Volt: -5, -2.5, 10, 50, 250, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG Ω. Decibels: -10 to +49 db. Plastic case with Carrying Handle. Size: 7 1/4 in. x 6 1/2 in. x 3 1/4 in. £18.90. P. & P. 25p.

V4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 657 O.P.V. 0/3/1.5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/3/1.5/7.5/30/60/150/300/600/900 VAC. 0/300mA/1.5/6/60/150/300mA/1.5/6 AMP. D.C. 0/1.5/15/150/150/600mA/1.5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%, AC 1.5%. Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £8-50 plus P. & P. 25p.

RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 μA/1/10/100mA/1A. Resistance 300 ohm/300/30K/300K Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5-97 P. & P. 25p.

HOEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. ADJUSTMENT: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 1/2 in. x 3 1/2 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. £48.974. Carr. 50p.

G. W. SMITH & CO (RADIO) LTD.
Also see next two pages

SEMICONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors				Integrated Circuits				VALVES									
2G301	20p	2N3416	37p	2N3417	37p	2N3418	37p	FJH111	70p	SN7430	20p	OA2	38p	2524	30p	EL95	35p
2G302	20p	2N3439	130p	2N3440	97p	2N3441	97p	FJH121	25p	SN7440	20p	OZ2	45p	2525	42p	EM80	45p
2G303	20p	2N3440	97p	2N3441	97p	2N3442	97p	CA3005	180p	FJH151	25p	OB4	30p	2526	65p	EM81	60p
2G306	42p	2N3564	17p	2N3565	17p	2N3566	17p	CA3007	282p	FJH161	70p	IL4	20p	30C15	80p	EM84	30p
2G308	30p	2N3565	17p	2N3566	17p	2N3567	17p	CA3011	175p	FJH171	25p	IL5	40p	30C16	80p	EM85	£1.00
2G309	30p	2N3567	17p	2N3568	17p	2N3569	17p	CA3012	175p	FJH181	25p	IL6	30p	30C18	80p	EM87	30p
2G371	15p	2N3568	25p	2N3569	25p	2N3570	25p	CA3013	105p	FJH221	25p	IT4	25p	30F5	85p	EY41	40p
2G374	20p	2N3569	25p	2N3570	25p	2N3571	25p	CA3014	124p	FJH231	25p	IU4	30p	30FL1	75p	EY46	40p
2G381	22p	2N3570	25p	2N3571	25p	2N3572	25p	CA3018	84p	FJH241	25p	IU6	60p	30FL12	120p	EY47	42p
2N388A	40p	2N3572	97p	2N3573	97p	2N3574	97p	CA3018A	84p	FJH251	25p	2D21	35p	30FL14	96p	EZ40	55p
2N404	20p	2N3605	27p	2N3606	27p	2N3607	27p	CA3020	110p	FJH261	25p	3Q4	35p	30FL15	85p	EZ41	50p
2N406	15p	2N3606	27p	2N3607	27p	2N3608	27p	CA3029	84p	FJH111	60p	3S4	35p	30L17	80p	EZ88	27p
2N407	15p	2N3607	27p	2N3608	27p	2N3609	27p	CA3030	120p	FJH121	60p	3V4	45p	30P12	80p	EZ81	29p
2N408	15p	2N3608	27p	2N3609	27p	2N3610	27p	CA3030A	120p	FJH131	60p	5R4	75p	30P19	85p	GZ32	45p
2N409	15p	2N3609	27p	2N3610	27p	2N3611	27p	CA3032	160p	FJH141	125p	5U4	35p	30P17	75p	GZ34	60p
2N410	15p	2N3610	27p	2N3611	27p	2N3612	27p	CA3032A	160p	FJH151	125p	5V4	45p	30P13	93p	KT86	£2.00
2N411	15p	2N3611	27p	2N3612	27p	2N3613	27p	CA3032B	160p	FJH161	125p	5Y3	40p	30P14	90p	KT88	£2.00
2N412	15p	2N3612	27p	2N3613	27p	2N3614	27p	CA3032C	160p	FJH171	125p	5Z4G	40p	35L6	50p	MU14	75p
2N413	15p	2N3613	27p	2N3614	27p	2N3615	27p	CA3032D	160p	FJH181	125p	6J00L2	80p	35W4	35p	PAC80	40p
2N414	15p	2N3614	27p	2N3615	27p	2N3616	27p	CA3032E	160p	FJH191	125p	6A5	40p	35Z4	35p	PC86	60p
2N415	15p	2N3615	27p	2N3616	27p	2N3617	27p	CA3032F	160p	FJH201	125p	6AG7	40p	35Z5	50p	PC88	60p
2N416	15p	2N3616	27p	2N3617	27p	2N3618	27p	CA3032G	160p	FJH211	125p	6AK5	35p	50B5	50p	PC97	45p
2N417	15p	2N3617	27p	2N3618	27p	2N3619	27p	CA3032H	160p	FJH221	125p	6AK6	60p	50C5	50p	PC00	48p
2N418	15p	2N3618	27p	2N3619	27p	2N3620	27p	CA3032I	160p	FJH231	125p	6AL5	20p	80	55p	PC08A	40p
2N419	15p	2N3619	27p	2N3620	27p	2N3621	27p	CA3032J	160p	FJH241	125p	6AM6	60p	8E2	40p	PC08B	40p
2N420	15p	2N3620	27p	2N3621	27p	2N3622	27p	CA3032K	160p	FJH251	125p	6AQ6	35p	8E3	40p	PC08C	40p
2N421	15p	2N3621	27p	2N3622	27p	2N3623	27p	CA3032L	160p	FJH261	125p	6A86	40p	16Z5	50p	PC08D	50p
2N422	15p	2N3622	27p	2N3623	27p	2N3624	27p	CA3032M	160p	FJH271	125p	6AT6	35p	5768	70p	PC189	55p
2N423	15p	2N3623	27p	2N3624	27p	2N3625	27p	CA3032N	160p	FJH281	125p	6AU6	25p	6146	100p	PC180	30p
2N424	15p	2N3624	27p	2N3625	27p	2N3626	27p	CA3032O	160p	FJH291	125p	6AV6	30p	AZ31	55p	PCF82	34p
2N425	15p	2N3625	27p	2N3626	27p	2N3627	27p	CA3032P	160p	FJH301	125p	6BA6	25p	CV31	35p	PCF84	60p
2N426	15p	2N3626	27p	2N3627	27p	2N3628	27p	CA3032Q	160p	FJH311	125p	6BE6	35p	EA92	30p	PCF86	60p
2N427	15p	2N3627	27p	2N3628	27p	2N3629	27p	CA3032R	160p	FJH321	125p	6BH6	75p	DFP6	60p	PCF80	60p
2N428	15p	2N3628	27p	2N3629	27p	2N3630	27p	CA3032S	160p	FJH331	125p	6BJ6	50p	DF91	25p	PCF801	50p
2N429	15p	2N3629	27p	2N3630	27p	2N3631	27p	CA3032T	160p	FJH341	125p	6BQ7A	40p	DF96	45p	PCF802	50p
2N430	15p	2N3630	27p	2N3631	27p	2N3632	27p	CA3032U	160p	FJH351	125p	6BR7	90p	DK91	40p	PCF805	80p
2N431	15p	2N3631	27p	2N3632	27p	2N3633	27p	CA3032V	160p	FJH361	125p	6BR8	70p	DK92	55p	PCF806	70p
2N432	15p	2N3632	27p	2N3633	27p	2N3634	27p	CA3032W	160p	FJH371	125p	6BW6	85p	DK96	60p	PCF807	75p
2N433	15p	2N3633	27p	2N3634	27p	2N3635	27p	CA3032X	160p	FJH381	125p	6C4	35p	EL8F	100p	PL81	50p
2N434	15p	2N3634	27p	2N3635	27p	2N3636	27p	CA3032Y	160p	FJH391	125p	6CZ4	40p	DL4	40p	PL84	45p
2N435	15p	2N3635	27p	2N3636	27p	2N3637	27p	CA3032Z	160p	FJH401	125p	6C4	35p	DL96	45p	PL85	45p
2N436	15p	2N3636	27p	2N3637	27p	2N3638	27p	CA3032AA	160p	FJH411	125p	6CD6	125p	DM70	40p	PL86	45p
2N437	15p	2N3637	27p	2N3638	27p	2N3639	27p	CA3032AB	160p	FJH421	125p	6CL6	50p	DY88	32p	PL86	45p
2N438	15p	2N3638	27p	2N3639	27p	2N3640	27p	CA3032AC	160p	FJH431	125p	6CW4	65p	DY87	33p	PL200	65p
2N439	15p	2N3639	27p	2N3640	27p	2N3641	27p	CA3032AD	160p	FJH441	125p	6E1	62p	E88C	100p	PL39	55p
2N440	15p	2N3640	27p	2N3641	27p	2N3642	27p	CA3032AE	160p	FJH451	125p	6F6	45p	EC34	30p	PL60	40p
2N441	15p	2N3641	27p	2N3642	27p	2N3643	27p	CA3032AF	160p	FJH461	125p	6F6G	35p	EAB	30p	PL82	45p
2N442	15p	2N3642	27p	2N3643	27p	2N3644	27p	CA3032AG	160p	FJH471	125p	6F13	45p	EABCB	35p	PL82	45p
2N443	15p	2N3643	27p	2N3644	27p	2N3645	27p	CA3032AH	160p	FJH481	125p	6F14	70p	EAF42	35p	PL83	45p
2N444	15p	2N3644	27p	2N3645	27p	2N3646	27p	CA3032AJ	160p	FJH491	125p	6F15	65p	EB91	20p	PL84	40p
2N445	15p	2N3645	27p	2N3646	27p	2N3647	27p	CA3032AK	160p	FJH501	125p	6F18	50p	EB41	55p	PL500	75p
2N446	15p	2N3646	27p	2N3647	27p	2N3648	27p	CA3032AL	160p	FJH511	125p	6F23	85p	EB08	30p	PL504	80p
2N447	15p	2N3647	27p	2N3648	27p	2N3649	27p	CA3032AM	160p	FJH521	125p	6G1	17p	EBF80	40p	PL59	55p
2N448	15p	2N3648	27p	2N3649	27p	2N3650	27p	CA3032AN	160p	FJH531	125p	6J4	50p	E8F	100p	PL81	50p
2N449	15p	2N3649	27p	2N3650	27p	2N3651	27p	CA3032AO	160p	FJH541	125p	6J5	25p	EBP29	30p	PL80	40p
2N450	15p	2N3650	27p	2N3651	27p	2N3652	27p	CA3032AP	160p	FJH551	125p	6J5GT	30p	EBL21	60p	PL81	50p
2N451	15p	2N3651	27p	2N3652	27p	2N3653	27p	CA3032AQ	160p	FJH561	125p	6J6	20p	EC86	60p	PL82	35p
2N452	15p	2N3652	27p	2N3653	27p	2N3654	27p	CA3032AR	160p	FJH571	125p	6J7	45p	EC88	80p	PL83	35p
2N453	15p	2N3653	27p	2N3654	27p	2N3655	27p	CA3032AS	160p	FJH581	125p	6K8G	40p	EC40	65p	PL88	40p
2N454	15p	2N3654	27p	2N3655	27p	2N3656	27p	CA3032AT	160p	FJH591	125p	6L6GT	40p	EC43	30p	PL90	40p
2N455	15p	2N3655	27p	2N3656	27p	2N3657	27p	CA3032AU	160p	FJH601	125p	6L92D	50p	EC85	40p	PL901	50p
2N456	15p	2N3656	27p	2N3657	27p	2N3658	27p	CA3032AV	160p	FJH611	125p	6Q7	40p	EC88A	40p	U25	80p
2N457	15p	2N3657	27p	2N3658	27p	2N3659	27p	CA3032AW	160p	FJH621	125p	68A7	40p	EC80	35p	U26	80p
2N458	15p	2N3658	27p	2N3659	27p	2N3660	27p	CA3032AX	160p	FJH631	125p	68J7	40p	EC82	35p	U50	40p
2N459	15p	2N3659	27p	2N3660	27p	2N3661	27p	CA3032AY	160p	FJH641	125p	68K7	40p	EC86	65p	U52	35p
2N460	15p	2N3660	27p	2N3661	27p	2N3662	27p	CA3032AZ	160p	FJH651	125p	68L7	40p	EC88	100p	PL81	75p
2N461	15p	2N3661	27p	2N3662	27p	2N3663	27p	CA3032BA	160p	FJH661	125p	68M7	35p	EC85	100p	U81	40p
2N462	15p	2N3662	27p	2N3663	27p	2N3664	27p	CA3032BB	160p	FJH671	125p	68N7	35p	EC84	75p	U82	40p
2N463	15p	2N3663	27p	2N3664	27p	2N3665	27p	CA3032BC	160p	FJH681	125p	68Q7	40p	EC81	30p	U01	40p
2N464	15p	2N3664	27p	2N3665	27p	2N3666	27p	CA3032BD	160p	FJH691	125p	6U4	65p				

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!

RECORD DECKS

BSR	UAG50 Mono†	£4-97	ZERO 100A	£41-65
C129†		£6-30	ZERO 100B	£40-70
MP90		£10-40	GOLDDRING	
610		£14-07	GL72	£18-97
510		£11-50	GL69/2P	£24-20
310		£29-40	GL72	£22-25
810		£33-45	GL72P	£29-05
MP60 TPD1	£17-12		GL75P	£29-05
MP50 TPD2	£16-40		LD175	£23-83
610 TPD1	£22-35		GL72	£23-85
510 TPD1	£18-20		Q99	£19-30
210 Package*	£9-55		GL85	£46-30
HT 70	£14-99		GL85P	£54-50
HT 70 Package	£21-60		LD185	£4-80
			G101	£21-95
GARRARD			PIOWEER	
2025 T/C*	£8-50		PL12AC	£25-15
40B*	£9-25		PL15C	£25-25
5-300*	£9-50		PLA25	£62-85
SP25 III	£10-50		THORENS	
SL65B	£13-45		TD125	£57-65
AF78	£18-85		TD125AB	£91-15
AF78 with	£16-40		TX25	£27-40
G800*	£22-50		TD150	£27-90
SL72B	£23-25		TD150A II	£33-20
SL75B	£26-00		TD150AB II	£37-80
SL95B	£32-50		TD150 Plinth	£34-47
401	£26-60		TXII	£36-65

† Mono * Stereo Cartridge
All other models less Cartridge
Carriage 50p extra incl. model.

RECORD DECK PACKAGES

Decks supplied with cartridge ready wired in trunk veneered plinth with cover.

Garrard 2025T/C9TAHCD	£12-95
Garrard SP25 III/9TAHCD	£18-95
Garrard SP25 III/G800	£18-50
Garrard SP25 III/M75E	£20-35
Garrard SP25 III/M44-7	£20-35
Garrard SP25 III/M55-E	£22-30
Garrard SP25 III/G800 (Play on Plinth and Cover)	£19-75
Garrard AF78/G800	£29-50
Garrard AF78/M75-E	£32-50
Garrard AF78/M55-E	£33-95
Garrard AF78/M75EJ	£34-90
BBR McDonald MP60/AT55	£18-25
Golding GL72/G800	£34-50
Golding GL75/G800	£39-70
Golding GL75/G800E	£44-15

Carriage 50p any item.

★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. 812E ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £8-37¹/₂. P. & P. 12p. Stereo multiplex adapters £4-97¹/₂.

NS-1600W STEREO AMPLIFIER

Exceptional budget price amplifier. All silicon transistor. Handsome Walnut case. Switched input selector, separate balance, volume, treble, bass controls. Output 2x6W RMS. Inputs Mag. Tape. Xtal. Tuner, Tape Out. £14-75. Carr. 37p.

LATEST CATALOGUE

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS

VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW

ONLY 37¹/₂ p P & P 10p



TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. OUR PRICE £18-50 Carr. 37p.

TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Car. phono inputs. AFC/Built-in MPX. List £51. OUR PRICE £28-75. Carr. 50p.

● SUGGESTED SYSTEM ●

F.2000, Garrard 2025T/C Changer fitted stereo cartridge, with plinth and cover and pair of G.W.S. Speakers. Total Rec. Price £97-73¹/₂. OUR PRICE £62-95. Carr. £1.

HA 10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50MW. £9-97. P. & P. 15p.

SINCLAIR EQUIPMENT



Project 60. Package offers. 2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. £18-95 Carr. 37p. Or with PZ8 power supply £18-00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-25. Carr. 37p. Transformer for PZ8. £2-97¹/₂ extra. Add to any of the above £4-45 for active filter unit and £18-90 for pair of Q16 speakers. Project 60 FM Tuner £18-95. Carr. 37p. All other Sinclair products in stock. 2000 Amp £23-50 Carr. 37p.; 3000 Amp £30-95 Carr. 37p.; Neoteric Amp £49-95 Carr. 37p. IC12 £1-80 Post 10p NEW PROJECT 605 — £20-97. Carr. 37p.

BH.001 HEAD-SET AND BOOM MICROPHONE

Moving coil. Ideal for language teaching, communications. Headphone Imp. 16 ohms. Microphone Imp. 200 ohms. £4-62. P. & P. 15p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 240) Quantities available.

E.H.T. TESTER 0-30KV.



Completely self-contained with built-in voltmeter. Easy to read, very accurate, robust construction. An essential for colour television servicing, etc. Size 360mm, long. 50mm. dia. £8-95. P. & P. 25p.

SPECIAL OFFER! SINCLAIR PROJECT 60 STEREO FM TUNER



The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 67.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2uV. AFC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 26-30V. D.C. Size: 93 x 40 x 207 mm. REC. LIST PRICE £25. OUR PRICE £16-95 P. & P. 25p

Unrepeatable offer—buy now and save over £8

Model S-100TE MULTI-METER/TRANSISTOR TESTER 100,000 o.p.v. MIRROR SCALE/OVERLOAD PROTECTION

0/12 — 6/3/12/30/120/600 V/DC — 0/130/120/600 V. AC. 0/12/600uA/12/300MA/12 Amp. DC. 0/10K/1 MEG/100 MEG. —20 to +30 db. 0-01 — -2 mfd. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50. PIP 25p.

MCA. 220 AUTO-MATIC VOLTAGE STABILISER

Input 88-125 VAC or 176-250VAC. Output 120VAC or 240VAC. 300VA rating. £11-97. Carr. 50p.

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

50 Hz — 50,000 Hz. Square 18 — 200,000 Hz. Output max. +10 dB. (10 K ohms). Operation internal batteries. Attractive 2-ton case 7 1/2" x 5" x 3 1/2". Price £17-50. Carr. 17p.

TE-16A Transistorised Signal Generator, 5 ranges 400KHz — 30MHz.

An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 3 1/2 x 3 1/2 in. Complete with instructions and leads. £7-97¹/₂. P. & P. 20p.

TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ohm range (0.1 Ohm x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (—3dB). Accuracy: 0.05dB. +Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ohm load resistance with internal/external switch. Brand new. £27-50. P. & P. 25p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/2in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, £1-05 P. & P. 7p. 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms, £1-37¹/₂ P. & P. 7p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

S-260 General Purpose Bench Mounting	1 Amp £7-00	S-280B Panel Mounting	1 Amp £7-00
2.5 Amp £8-05	2.5 Amp £8-05	2.5 Amp £8-05	2.5 Amp £8-05
5 Amp £11-75	5 Amp £11-75	5 Amp £11-75	5 Amp £11-75
8 Amp £15-90	8 Amp £15-90	8 Amp £15-90	8 Amp £15-90
10 Amp £22-50	10 Amp £22-50	10 Amp £22-50	10 Amp £22-50
12 Amp £23-60	12 Amp £23-60	12 Amp £23-60	12 Amp £23-60
20 Amp £49-00	20 Amp £49-00	20 Amp £49-00	20 Amp £49-00

Special discounts for quantity

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 100mm. £8-97 P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". £11-97. P. & P. 25p.

UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control, 220/240V. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end, 2 mech. filters, product detector, variable B.F.O. noise limiter. 8. Meter, Bandspread, RF Gain, 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12v. C Brand new with instructions. £50. Carr. 50p.

B.C. 221 FREQUENCY METERS

Latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. 50p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 220/240V. A.C. Output continuously variable from 20V-230V. Model MR 2305 5 amp. 68 x 46 x 43mm. £8-37¹/₂. Model MR 2310 10 amp. 90 x 48 x 60mm. £11-97¹/₂. Postage 12p.

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80 W	£2-10	P. & P. 18p
150 W	£2-70	P. & P. 18p
300 W	£3-60	P. & P. 23p
500 W	£4-25	P. & P. 33p
1000 W	£7-50	P. & P. 38p
1500 W	£10-20	P. & P. 43p
2250 W	£17-25	P. & P. 50p
3000 W	£36-00	P. & P. 41

G.W. SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-5 MONDAY TO SATURDAY

everyday electronics

PROJECTS...
THEORY....

FOR ALL SEASONS

Our cover this month has quite an outdoor touch. Of course, you don't have to be an apiarist to sense that things are beginning to buzz in the outside world. Spring is now well advanced and thoughts are likely to be turning towards all kinds of pastimes and occupations for the coming summer months.

It is an appropriate time to point out that do-it-yourself electronics has no closed season. Outdoor activities like gardening, touring, camping, sporting events, and so on, present many unique opportunities for putting electronics to effective use. So we advise, take stock *now*, anticipate your needs and start building to remedy any deficiencies in this respect.

GOOD COMPANION

The *Constructors Companion* given free with every copy of this month's EVERYDAY ELECTRONICS is small and compact. It has been designed for your pocket, so that wherever you go you can have essential facts constantly at hand. Compiled with the beginner particularly in mind, this booklet will prove a valuable *aide-memoire* for the more experienced constructor as well.

Those still feeling their feet will be glad of the technical back-up they can instantly call upon

when confronted with a choice of allegedly alternative or equivalent parts when shopping personally for components.

READY ACCESS

Our regular readers will already appreciate the amount of important and useful information they are accumulating, as the months go by. True, not everyone will have an immediate need for every project described. But a word of advice: do not discard back numbers. You never know when circumstances may arise that create a definite need which some previously described project would satisfy exactly.

This leads us on to another common problem: how to store numerous copies of a magazine so that ready access may be made at any time to one particular article. The only really satisfactory solution is to keep copies of the magazine in the binder specially designed to hold 12 issues of EVERYDAY ELECTRONICS and which is now available.

Fred Bennett

Our June issue will be published on Friday, May 19

EDITOR F. E. BENNETT • M. KENWARD • B. W. TERRELL B.Sc.
ART EDITOR J. D. POUNTNEY • P. A. LOATES • S. W. R. LLOYD
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.35.

Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.



...EASY TO CONSTRUCT
...SIMPLY EXPLAINED

VOL. 1 NO. 7

MAY 1972

CONSTRUCTIONAL PROJECTS

AUDIO TONE GENERATOR Suitable for making electronic music by F. C. Judd	358
BEE COUNTER An electronic eye for the hive by G. A. Cozens	376
METAL LOCATOR Detects and locates metal objects underground by D. Bollen	382

GENERAL FEATURES

EDITORIAL	356
SHOP TALK New products and this month's constructionals by Mike Kenward	362
MAKING ELECTRONIC SOUNDS AND MUSIC Using the Audio Tone Generator by F. C. Judd	363
PLEASE TAKE NOTE	367
THEY MADE THEIR MARK No. 1—Introduction By J. E. Gregory	368
TEACH-IN Part 7—Semiconductors: Transistors by Mike Hughes	369
RUMINATIONS by Sensor	374
TEACH-IN HALF TERM TEST ANSWERS See how well you did	389
READERS LETTERS Your news and views	390, 393

EE binders...


Your copies of Everyday Electronics deserve a permanent Home!

An Easi-Binder is now available handsomely finished in orange de luxe Balacron with black lettering on the spine. It holds 12 issues of Everyday Electronics.

Order your binder from Binding Dept., IPC Magazines Ltd., Carlton House, 68, Great Queen Street, London W.C.2.

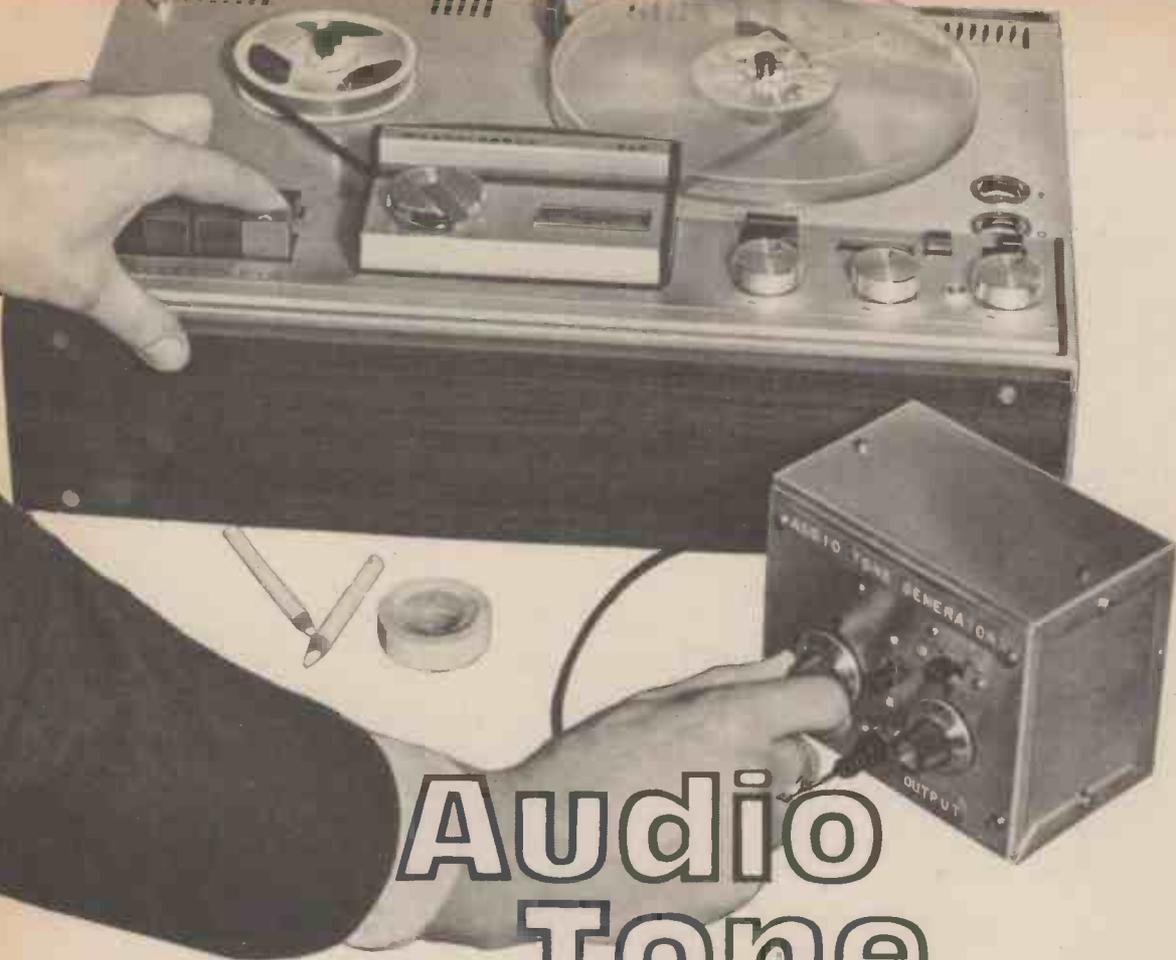The price is 88p, including postage and packing.





Audio Tone Generator

BY FRED JUDD

This simple tone generator covers the audio range from 50 to 2,000 Hz and has been specifically designed for use with a tape recorder to make electronic music.

THE multivibrator is one of the most commonly used electronic oscillator circuits and generates an almost square waveform. It can be made to cover a wide frequency range without the need for switching in different values of components and moreover will produce a high output signal level for a relatively small supply voltage. As a primary signal generator it has many uses as a test instrument in audio as well as electronic applications.

The generator described in this article is used as a tone source for the creation of electronic music and "science fiction" sound effects in conjunction with a tape recorder. The feature *Electronic Sounds and Music* on page 363 deals with the use of the tone generator in detail.

GENERATOR CIRCUIT

The circuit diagram is given in Fig. 1 and employs three *pnp* transistors, two of which form the multivibrator (TR1 and TR2), the remaining one, TR3, being used as a squaring amplifier.

The operating frequency and mark to space ratio (see Fig. 2) of the multivibrator are set by the time taken for C2 and C3 to charge up enough to switch transistors TR2 and TR1 respectively. This "charging time" is determined by the value of the capacitor and the value of the resistor through which it is charged.

Providing the time taken for each capacitor to charge is similar then the mark to space

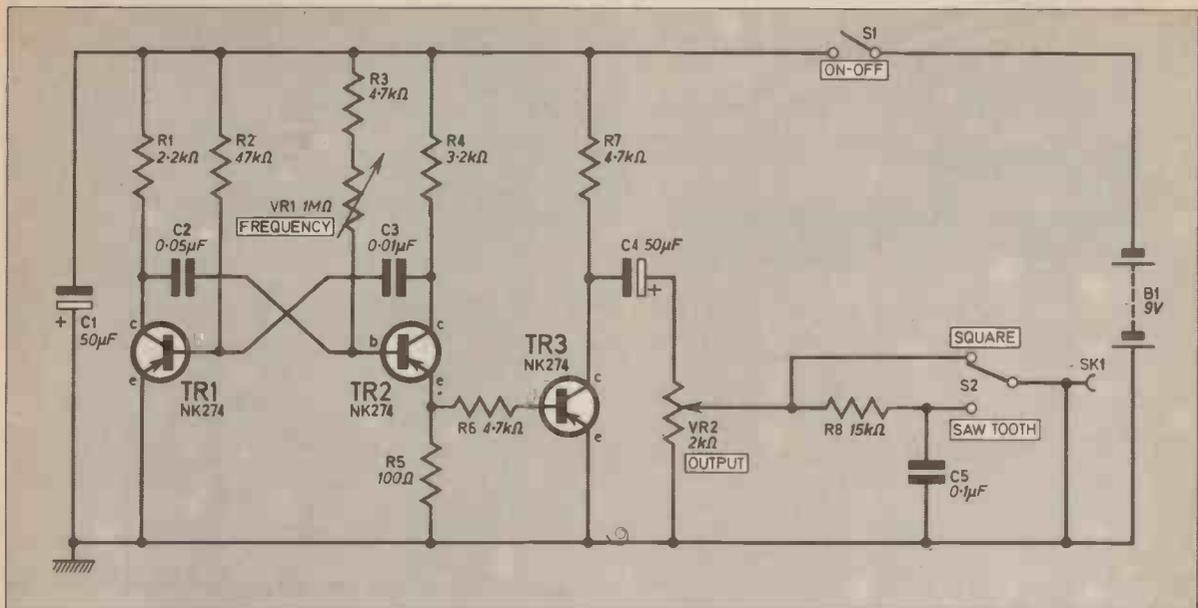


Fig. 1. Complete circuit diagram of the Audio Tone Generator.

ratio will be 1 to 1 or the mark and space will be of similar duration (Fig. 2). If we now change one of the controlling values—in this case VR1—both the frequency and mark to space ratio will be altered.

If we increase the value of VR1 the frequency will decrease as C2 will take longer to charge, and the mark to space ratio will alter for the same reason (see Fig. 3). Thus frequency control is achieved by VR2 and the total frequency range is approximately 50 to 2,000Hz.

The waveform has a mark to space ratio of 1 to 1 at approximately 1,500Hz at all lower frequencies the mark to space ratio increases becoming about 1 to 20 at the lowest frequency (Fig. 3).

The output from the multivibrator is taken from the emitter of TR2, through R6 to the base of TR3. Transistor TR3 is switched hard on and off by the output from TR2 and thus ensures a completely square output at its collector. The output level from TR3 is continuously variable from 0 to approximately 7 volts by VR2.

SAWTOOTH OUTPUT

The square wave output from TR3 can also be switched via S2 through an integrating network, C5 and R8, to provide an approximately sawtooth waveform (Fig. 4) of about 1 volt peak-to-peak maximum output, instead of the square-wave.

One of the major differences between a square wave and a sawtooth wave is the harmonic content and hence the tonal quality, when either are made audible via an amplifier and loudspeaker. The square wave contains only odd harmonics, in addition to its fundamental,

whereas a sawtooth wave consists of both odd and even harmonics plus the fundamental.

Audibly the square wave has a sound rather like that produced by a clarinet particularly in the region of middle C (261Hz approx.). The sawtooth wave has a sound rather more like a

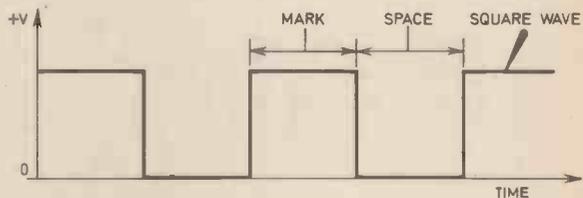


Fig. 2. A square wave with a 1 to 1 mark to space ratio.

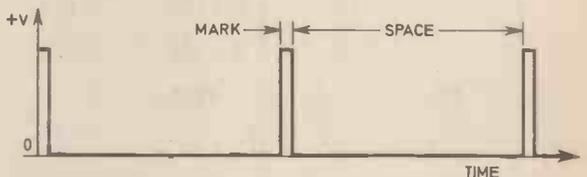


Fig. 3. A square wave with a 1 to 20 mark to space ratio.

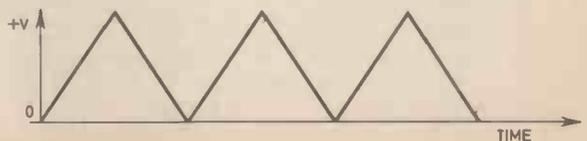


Fig. 4. A sawtooth waveform.

Audio Tone Generator


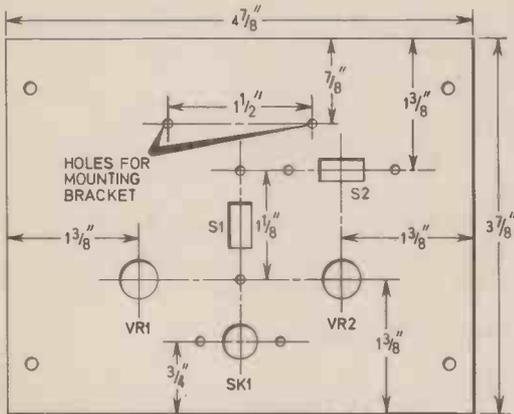
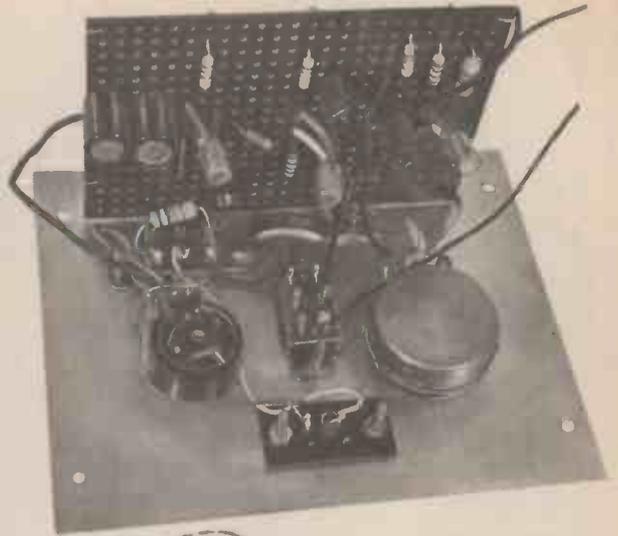


Fig. 5. Front panel drilling details.

Approximate cost of components...
£ 2.60 plus case

Fig. 7. Wiring of the final unit. The tinted area is the component mounting board as shown in Fig. 6.

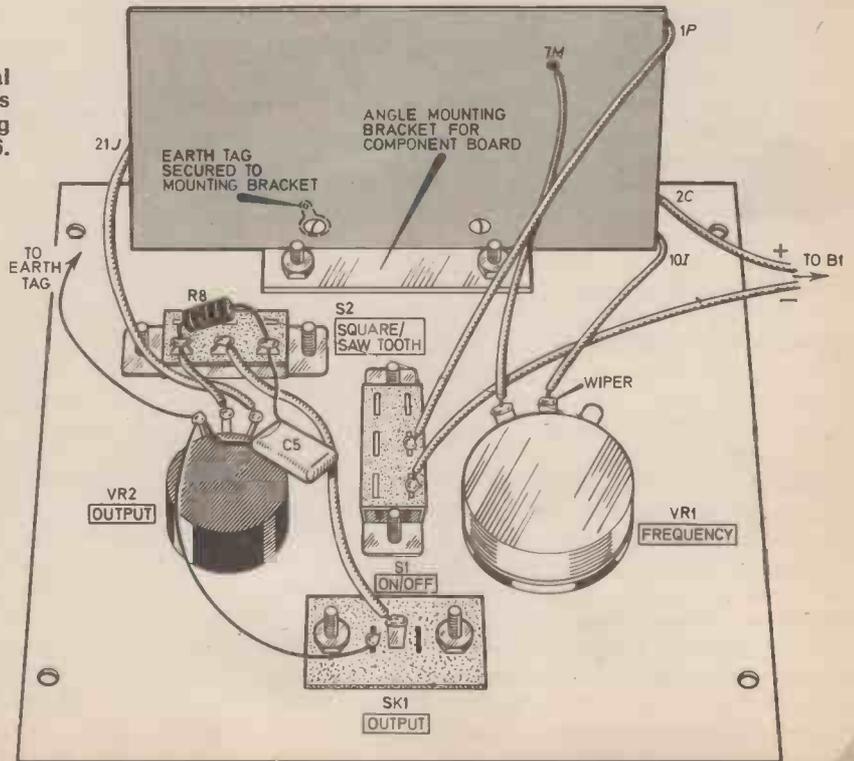

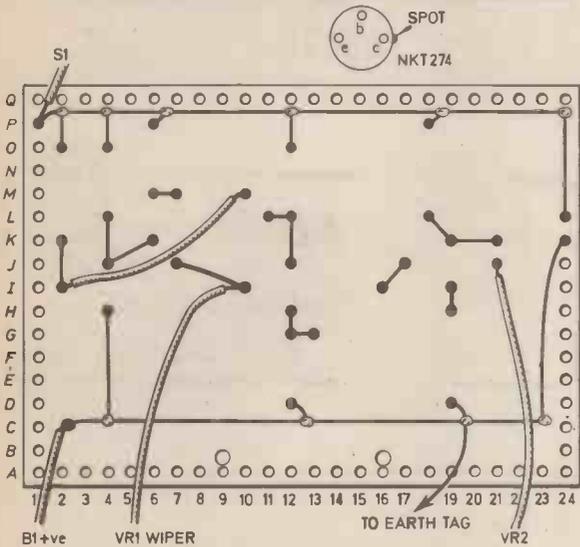
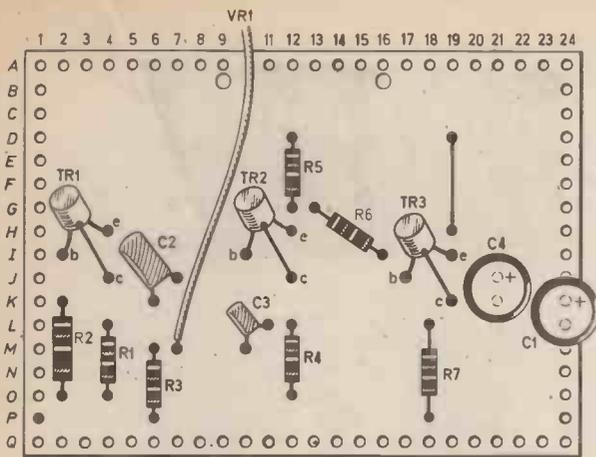


Fig. 6. Top and underside views of the component board. The transistor connections between the two diagrams are viewed from the underside.

flute. Both waveforms are used extensively in electronic organ voicing and for electronic music.

CONSTRUCTION

The prototype unit was housed in a box made from universal chassis parts. The pieces used assemble into a box measuring 5 by 4 by 3 inches. The sides and top and bottom can be assembled leaving one plate for the front panel and one for the rear. The plate used for the front panel is drilled as shown in Fig. 5 and is used to mount all the components.

If the layout and assembly of the generator is as shown there is just room in the case for a PP9 9 volt battery. Even if you spread the layout a little there should still be room for a slightly smaller 9 volt battery. The circuit board is 0.15 inch matrix plain perforated veroboard and is mounted on a 2 inch length of $\frac{3}{8}$ by $\frac{3}{8}$ inch aluminium angle.

Components....

Resistors

- R1 2.2k Ω
 - R2 47k Ω
 - R3 4.7k Ω
 - R4 3.2k Ω
 - R5 100 Ω
 - R6 4.7k Ω
 - R7 4.7k Ω
 - R8 15k Ω
- All $\frac{1}{4}$ W $\pm 10\%$ carbon

Capacitors

- C1 50 μ F elect. 12V
- C2 0.05 μ F
- C3 0.01 μ F
- C4 50 μ F elect. 12V
- C5 0.1 μ F

Transistors

- TR1 NKT 274 germanium *pn*p
- TR2 NKT 274 germanium *pn*p
- TR3 NKT 274 germanium *pn*p

Potentiometers

- VR1 1M Ω log carbon
- VR2 2k Ω lin carbon

Switches

- S1 S.P.S.T. slide
- S2 S.P.D.T. slide

Miscellaneous

- SK1 Phono socket
- B1 PP9 9V battery
- Control knobs (2 off) Eagle type F10, case 5 x 4 x 3in made from universal chassis panels or a similar size case, battery connector, aluminium angle 2 x $\frac{3}{8}$ x $\frac{3}{8}$ in. Veroboard 5 x 4 x 0.15in matrix plain perforated, earth tag, connecting wire, 4BA fixings.


Commence wiring of the component board by inserting all components except the transistors, and the wire link on the top of the board as shown in Fig. 6. Turn the board over and connect up the two supply lines along the two sides of the board using 18 or 22 s.w.g. tinned copper wire. Next connect up the remaining components using the component leads where possible and connect the flying leads.

Finally insert the transistors checking carefully the lead connections with the underside view shown in Fig. 6, and solder them to the other components using a heat shunt on each lead as it is soldered. After checking the circuit board mount the board on the aluminium angle bracket and mount this on the front panel together with the remaining components.

Wire up all the components to the circuit board as shown in Fig. 7 and check the completed unit carefully before connecting the battery and switching on.

Continued on page 386

SEE
**SHOP
TALK**

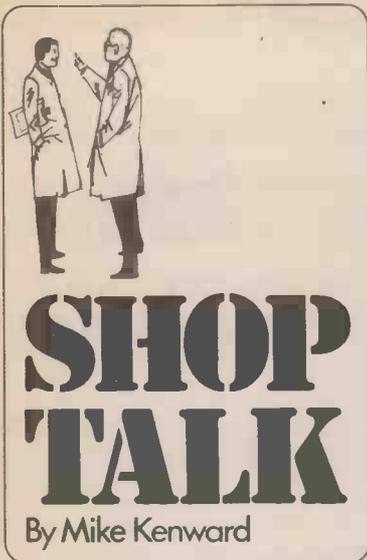

THIS month we have one item which many readers will probably wish to construct but which is not given in the form of a constructional project. It is the simple passive mixer that is described and drawn up in the *Making Electronic Sounds and Music* feature.

Since this is really a bonus that will be useful to those following the article we have not given full constructional details or a components list. All the component values are given on the circuit diagram and the wiring diagram shows how they are put together. The three sockets can be any type suitable for use with your particular tape recorder—the types we have shown are phono sockets.

The complete unit can be mounted in any small case. No battery or power supply is necessary. We would like to emphasise that this is a simple passive mixer and will not be able to cope with all inputs.

A more advanced type of mixer may form the subject of a future article. However this simple mixer should be suitable for use with the *Audio Tone Generator* that is also described in this issue.

Audio Tone Generator

There should be very few buying problems for the *Audio Tone Generator*. As described above the sockets could be changed to any suitable type if your equipment does not use phono sockets or if you already

have other types. Once again the case for this project can be any type that is available in a suitable size.

Bee Counter

We find it difficult to comment on the availability of cedar wood—not after-shave—but apparently this wood must be used or the bees will not accept it!

As far as the remaining components for the *Bee Counter* go make sure that the resistors you buy are of adequate wattage. The lamp and holder should be of the miniature type so that they can be accommodated in the wooden base panel. Since the current drawn by this circuit is fairly large the section in the article concerning the battery should be noted.

There are a number of Post Office type counters available so make sure you get the right one—4.2 ohms coil resistance is the important thing.

Metal Locator

The *Metal Locator* is a project which we are sure will create great interest but please remember that this is a simple one-transistor design and cannot be expected to out-perform a £30 unit. The use of Perspex or Paxolin is recommended for the locator head as these materials are not affected by damp or water.

All remaining components for the locator should be readily available. The use of a subminiature switch is recommended since only a small hole then needs to be cut in the plastic beaker. Any 50 μ A moving coil meter could be used in the locator provided it will fit the beaker lid. The one specified is probably the cheapest.

Finally do not forget the operating licence and don't say we did not tell you!

New Products

Two products from one go-ahead firm have been introduced this month. Both in the audio field, possibly the most outstanding is the Unisound 505 as Radio and T.V. Components call their do-it-yourself £25 stereo system. This competitively priced unit comes as a complete kit and only needs two screwdrivers to put together. All the electronics are in module form and are supplied

with wiring looms that only need connecting up using a screwdriver supplied with the kit.

The large EMI speakers are housed in attractive cabinets again put together with only a screwdriver. It is said that anyone who can wire up a mains plug can put the system together in one evening. The system utilises modified Mullard Unilex modules, has an output of 3.7 watts continuous sine wave r.m.s. per channel; and frequency response of 40Hz to 20kHz at the 3dB down points. It would be very difficult to buy the individual components—including Garrard 2025TC deck, cartridge, plinth and cover and build a unit to match this one for £25, excluding the two speakers and cabinets.



The second unit from RT-VC is a £7 push button car radio kit, slightly more difficult to construct but any reader who has some experience of soldering should be able to build a working unit.

The kit is of good quality and uses the same push button tuning unit as radios costing three or four times the price. These features ensures good sensitivity and the pre-aligned i.f. (intermediate frequency) module and tuner avoid complicated alignment.

The kit is suitable for 12V positive or negative earth operation and readers may like to note that an after sales service—to repair any item not functioning correctly—is operated by RT-VC for all their kits; cost about £2 depending on the fault.





Making Electronic Sounds and Music

BY FRED JUDD

Simple experiments with a tape recorder

THE term "electronic music" almost defies explanation because it is not the music that is electronic but the equipment and methods of creating it.

Its origin goes back many years, in fact to the invention of the thermionic valve and even as early as 1921 a "concert" of electronic music was performed in Paris by an Italian, Luigi Russolo, who used what was then called electrical sound generating and reproducing equipment.

Electronic music was difficult to perform directly from sound generators, etc., because composition required arranging the sounds in a given order and even changing the order, and sometimes the sounds, at a later time.

MODERN METHODS

Magnetic tape recording finally provided the ideal medium for composition. The sounds required could be recorded and rearranged afterwards by simply cutting out the pieces of tape containing them and splicing these together again in the order required. This technique paved the way for composers who, with both electronics and magnetic tape at their disposal, could produce new kinds of music with tonal qualities never before possible.

More recently of course the music synthesizer has taken over the task of tone generation, etc., and electronic music composers can now programme a synthesizer, couple it to a tape recorder and produce "instant" electronic music.

Nevertheless there is much that can be accomplished by the amateur with an ordinary domestic tape recorder, an audio tone generator (like the one described on page 358) and some splicing tape. The techniques are simple and you can get a good deal of fun out of experimental electronic music and "science fiction" sounds.

Your efforts need not be wasted either because you can enter them for the experimental music and sounds section of the annual British Tape Recording Contest (details later).

EQUIPMENT

An ordinary spool to spool tape recorder is the main requirement and if you have a stereo recorder with provision for recording independently on either track or you can get together with a friend and use two tape recorders, so much the better. A tape recorder with track-to-track or duoplay facility is also advantageous especially if it permits echo effects.

It is not possible to lay down procedures for specific makes and types of tape recorder but you will find that most of the techniques described can be applied.

Note that cassette or cartridge tape recorders are of limited use for creative recording of this nature which requires fairly extensive tape cutting and splicing.

Most modern spool to spool tape recorders are designed for stereo operation employing half or quarter track on standard quarter inch wide tape. If the tape recorder has a track-to-track recording facility it will have separate recording and replay heads, thus allowing a recording on one track to be copied on to another together with other signals.

Some stereo recorders may only have a common record/replay head which will not normally allow track-to-track copying but may have a facility for making separate recordings on each of two tracks. Information concerning such facilities should be given in the tape recorder instruction book. If in doubt, you should contact your dealer or the manufacturer for such information.

AUDIO TONE GENERATOR

An audio tone generator is not absolutely essential but is most advantageous. The simple *Audio Tone Generator* described on page 358 is quite suitable as it covers a wide enough frequency range and will deliver a square-wave or a nearly sawtooth-wave output signal, thus providing two basic sounds.

Sounds picked up by a microphone can also be used because these can be reshaped by tape cutting and splicing and by certain recording techniques. Magnetic tape will be required of course and for initial experimental work low priced brands will suffice.

Some splicing tape and blank leader tape will also be required. Do not use ordinary plastic sticky tape, such as Sellotape, for splicing as

this may damage the tape and will not give a long lasting joint. Small kits of coloured leader and proper splicing tape are readily available. A small tape splicer is also a very useful, though not essential, tool.

FIRST EXERCISES

It is important to know the extent to which your tape recorder can be used. If it has two or three speeds, as most of them do, record some musical sounds, whistling will do, at all three speeds and then play them back at one speed only, say the highest.

The sounds recorded at the lower speed(s) will be raised in pitch, by one or two octaves, depending on the speed. If the replay speed is double that of the recording speed the pitch is raised one octave and the sounds will occur faster but if the replay speed is half the recording speed, the pitch will be reduced by one octave and the sounds will occur slower. This is one of the most simple but most used techniques.

REVERSE REPLAY

Now, if your recorder is a stereo machine try turning the tape over (reverse the spools) and see if you can obtain replay on another track in reverse, i.e., the sounds will be going backwards. This technique is also commonly used for electronic music because it alters the nature of the sound completely by placing what was the beginning of the sound, i.e., its attack, at the end as illustrated in Fig. 1 in which (a) is the sound as recorded and (b) as played in reverse.

If you cannot play sounds in reverse try this exercise; connect a tone generator, or if this is not available record whistles through a micro-

Fig. 1. (a) Original waveform of the recorded sound (b) The sound recorded and shown in (a) played in reverse.


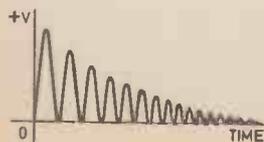


Fig. 2. Waveform of a sound which starts instantly and slowly dies away.

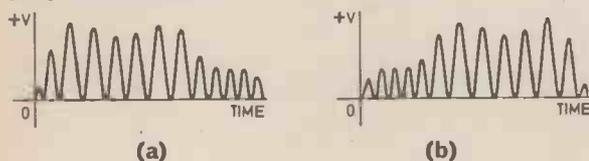Photograph showing the use of a tape splicer to join up a number of sounds.





Recording various sounds, using the microphone, to form a composition.

phone. Start with the recording level control at the maximum, set the tape running to record the sound but then almost simultaneously slowly turn the record level control to zero.

On replay you will have a sound that starts instantly and then slowly dies away as in Fig. 2. With a little practice you will be able to get various dying away or decay times depending on the speed at which the recording level control is turned off. Now try the reverse procedure; gradually increase the sound whilst recording and then quickly stop it.

TAPE CUTTING EXERCISES

Now try some tape cutting; first use the highest tape speed and record a few sounds of different pitch, i.e., from a tone generator, or whistles via the microphone, each one lasting two or three seconds.

Locate the beginning of each sound on the tape by carefully feeding the tape across the head and then cut the tape about two inches in front of the sound. Run off the remainder until you reach the beginning of the next sound; cut the tape here and splice to the end of the piece containing the first sound. Cut and join pieces of the remainder of the sounds.

On replay you will have a series of short sounds each rapidly following the other. Now try a similar exercise but this time insert pieces of blank leader tape between each sound.

MUSIQUE CONCRÈTE

Finally a variation of the two previous exercises. Record a few sounds each at a different tape speed. These should preferably be musical sounds, such as whistles or tones, or sounds produced by tapping a wine glass for example. Cut one or two pieces of each from the tape and assemble them at random with pieces of blank leader between groups. The pieces may be long or short.

Try replaying the assembled tape at different speeds and note the effect. You are well on the way to a form of composition known as "musique concrète" which is the creation of abstract forms of music out of real sounds. The same technique can, however, be used for abstract forms of electronic music in which the main sound source is an audio tone generator.

USING A TONE GENERATOR

The exercises outlined above demonstrate how almost any recorded sound can be altered by tape cutting and by recording and replay at different tape speeds. Electronic music does not normally include natural sounds recorded via a microphone and therefore the sound sources are electronic, i.e., from tone generators of one kind or another. The recording and tape cutting techniques, however, remain the same.

If you have a full range audio signal generator then tones can be recorded at the pitch required. The simple generator described on page 358 has a frequency range of approximately 50 to 2000Hz.

If frequencies outside the range of the generator are required it is simply a case of recording and replaying at different tape speeds for example; if a frequency of around 4000Hz is required, record the highest pitch of the generator (approximately 2000Hz) at a tape speed of $3\frac{3}{4}$ in/sec (inches per second) and replay at $7\frac{1}{2}$ in/sec.

If a very low pulsing sound is required at say 20 to 25Hz record a square-wave signal from the generator at its lowest pitch and then replay the recording at half the speed. Some experiment in this direction will soon reveal the tonal and pitch ranges that can be obtained simply by recording and replaying at various tape speeds.

Once this has been done, further experiment with the audio tone generator can be carried out in order to discover the type of sounds that can be produced. Start by recording a continuous note and while recording this vary the frequency and output controls on the generator, try this for both the square and sawtooth outputs (note that the output in the sawtooth position is much lower than in the square wave position).

Try cutting and reversing the sounds recorded to obtain various effects. You can also try making recordings at a distorted level by turning up the record level control, this will distort the original sound and produce yet another effect. Try switching from one output waveform to the other whilst recording—you can vary frequency and output at the same time—and also try switching the generator on and off while recording, again you can vary the output and frequency whilst turning on and off.

Edit the sounds produced by cutting and splicing and experiment fully with all possible

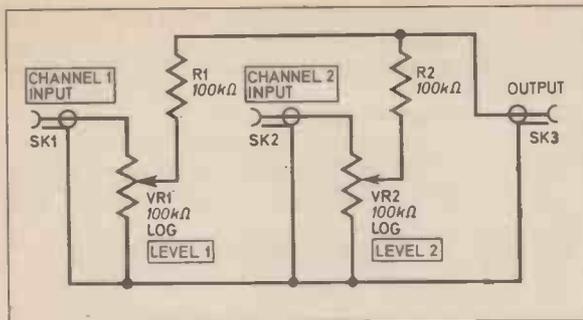


Fig. 3. Circuit diagram of a passive mixer that can be used for making electronic music.

effects. Once you have done this and feel fully conversant with the various effects that the generator is able to produce you can start to add one effect to another.

SIGNAL MIXING

Recording from track-to-track or using two separate tape recorders may necessitate mixing signals that are to be recorded and re-recorded i.e., signals from a recording already made to be mixed with signals from another source such as the tone generator.

Some recorders have built-in mixing facilities whilst others may permit a form of mixing by using the track-to-track recording facility or by superimposing one sound on another previously recorded. Again the tape recorder instruction book will provide information of this nature.

However, it is possible to build a very simple mixing circuit as shown in Fig. 3; Fig. 4 shows the construction. This is known as a passive mixing network, but will allow two signal sources to be mixed at different levels and coupled to a common input on a tape recorder (Fig. 5).

TAPE LOOPS

Another interesting technique widely used for electronic music is the tape loop. This is the use of a small endless loop of tape containing recordings which are played continuously to produce repeating rhythm patterns.

Record a few natural sounds, or low pitched tones from an audio generator, of quite short duration, one immediately after the other. Cut a piece of the tape containing the sounds, about 18 inches long, and splice the ends together so as to form a complete loop. Place the loop in the recorder so that it runs past the tape heads when the machine is set to replay. You can hold the loop under tension by one of the methods shown in the photographs. Try running the loop at different speeds and, if possible, reverse the direction.

Record some percussion sounds, e.g., sounds produced by knocking together empty boxes, etc. Cut out pieces and make up a loop consisting of the various sounds and blank leader tape.

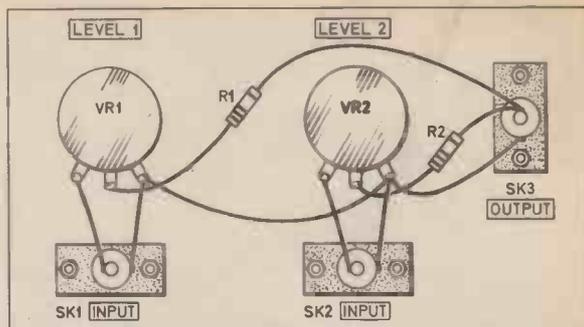


Fig. 4. Constructional details of the circuit shown in Fig. 3. Shop Talk refers to this figure.

For the first attempt use only two or three sounds and two or three pieces of leader.

You can make up an almost endless variety of fascinating rhythm patterns by this method and if you use two tape recorders the rhythm loop can be copied from one to the other whilst other sounds are added.


MULTIPLE RECORDING


If you have a tape recorder with a track-to-track recording facility the scope is much wider as sounds may be recorded on one track and then re-recorded on to another track whilst adding more sounds. If your tape recorder can produce the echo effect this too can be used in various ways to produce those echoing science fiction sounds. Try allowing the echo to build up into a crashing roar and see if you can play it in reverse.

Now that you have discovered the variety of sounds and rhythms available using the facilities you have it is up to you to put these together to form an interesting "musical" passage. It may take some time before you achieve the required effect.

By combining even a few of the techniques outlined the number of permutations possible are fantastic. Instructions on composition cannot be given because no rules exist. Your ideas must come solely from imagination and experiment.

Fig. 5. Using the passive mixer to combine two signals for recording purposes.

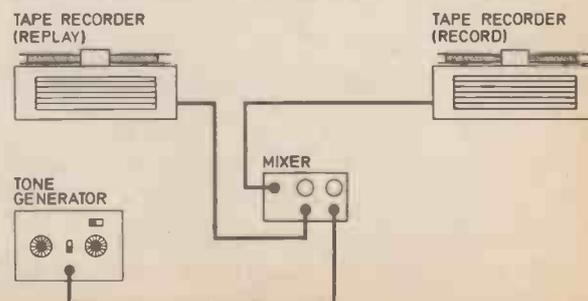

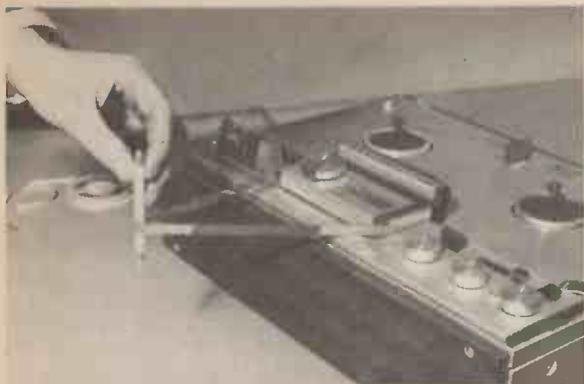

The three photographs on the left illustrate various methods of using a tape loop. The top photograph shows a reversed loop held under tension by passing it around a pencil; this is only suitable for short periods.

The centre photograph shows a reversed loop held under tension by a small spool hanging over a table edge; this is only suitable for fairly large loops.

The lower photograph shows a system that can be used for any size loops by routing the tape around suitable objects—batteries are shown. This photograph also shows a cardboard tape holder used to keep recorded sections of tape in the order required.



COMPETITION

Finally, why not try an entry for the "technical experiment class" of the annual British Tape Recording Contest. It is open to anyone and the closing date for the 1972 contest is not until June 30. The Technical Experiment class allows for tapes of up to 4 minutes duration and includes; sound composition, electronic music, musique concrète, multi-track music and experimental sound recordings. The prizes are worthwhile and you can get an entry form free by writing to The Secretary, British Amateur Tape Recording Contest, 33 Fairlawnes, Maldon Road, Wallington, Surrey, and enclosing a stamped addressed envelope. You may also be interested to know that the special "Tape of the Year" award for 1971 was for an experimental class entry.

Every tape entered is carefully assessed by the expert judges and their comments are passed to the contestant concerned when the tape is returned. Thus you will know how to make an even better tape next time. □



PLEASE TAKE NOTE

The approximate cost of components given in the Simple Calculator article last month was incorrectly shown as £1.20. This should have been £2.20.

The probe flying lead in the Signal Injector article (March issue) should be soldered to Y3 not Y2 as stated in the text.

The Normatest 2,000 multi-range test meter mentioned in Shop Talk last month is available from: Croydon Precision Instrument Company, Hampton Road, Croydon, CR9 2RU.



THEY MADE THEIR MARK

No 1 Introduction By J. E. Gregory

ELECTRONICS is an internationally uniform world of symbols. Look at any advertisement or study the simplest circuit diagram in EVERYDAY ELECTRONICS and you will be confronted with strange symbols of every shape. Magical signs used to signify basic units of physical quantity; Table 1 lists some of them.

Although electronics is regarded as a modern science and hobby many of these units are named after pioneers, scattered throughout the world, whose accumulated research spans hundreds of years.

This series sets out to explain the symbol, and perhaps more important something of the man who gave his name to it. But let's begin our potted history of electronics at the beginning.

THE GREEKS HAD A WORD FOR IT

Take the word electronics itself, for that we must go back in time to ancient Greece. To the ladies of Greece passing time by decorating their spinning wheels with amber, found on shores in the far north. They observed that the amber when contacting the threads would draw the threads to itself as they separated from the wool, and then push them away in a frictional force. The

Greek word for amber was *elektron*, from the verb *elkein* to attract. Although this phenomenon was observed and noted by several of the great Greek philosophers we have to jump two thousand years to the early 1600's and to the reign of Good Queen Bess, who was persuaded by her physician William Gilbert, to attend a demonstration of a frictional electric machine based upon the power of amber to attract. This power he called electricity.

It was soon realised that the crackling and sparking of Gilbert's electric machine were the same phenomena on a minute scale, as thunder and lightning, but how to prove it?

THE KITE FLYER

One of the first to try was the fifteenth child of an English immigrant; born in Boston Massachusetts in the year 1706, this was the well known American statesman and philosopher Benjamin Franklin (see illustration above).

His historic but dangerous

experiment trying to capture electricity from the sky occurred during a thunderstorm in the summer of 1752, when accompanied by his small son, he flew a kite with an iron door key. During the storm, he saw that sparks sprang from the key to his wrist, what he didn't realise of course was that if the lightning had actually struck the kite he would have been killed.

The study of natural phenomena had to take second place to his other activities, but he came to the conclusion that thunderstorms were simply the levelling of opposed electrical potentials, between one cloud and another or between a cloud and earth.

It was Franklin who introduced the positive and negative signs for electric charges, realising there are two kinds which neutralise each other.

Next month we move from America to 18th Century Italy and a scientist, Alessandro Volta, after whom the Volt, the measurement of electrical potential is named.

Photograph; Science Museum, London.

Table 1 FUNDAMENTAL UNITS

unit symbol	name of unit	physical quantity
A	Ampere	Electric Current
V	Volt	Electric Potential
F	Farad	Electric Capacitance
Ω	Ohm	Electric Resistance
W	Watt	Power
Hz	Hertz	Frequency
H	Henry	Inductance

These basic units are often inconveniently large or small and the units are prefixed with the following symbols:

p	pico	\div 1,000,000 million
n	nano	\div 1,000 million
μ	micro	\div 1 million
m	milli	\div 1,000
k	kilo	\times 1,000
M	mega	\times 1 million
G	giga	\times 1,000 million

Hence $5kV = 5,000$ Volts ; or $5mV = 0.005$ Volt





TEACH-IN

... FOR BEGINNERS

By Mike Hughes M.A.

7 SEMICONDUCTORS: Transistors

THIS year sees the twentieth birthday of the component most responsible for bringing electronics within the scope of do-it-yourself enthusiasts; it has greatly simplified design and construction and has also brought about terrific reductions in costs. It is the "transistor".

As a replacement for the valve, it allows us to use low voltages and removes the arduous task of having to assemble valve bases and massive transformers on tank like chassis. Connections to a transistor are few and the basic way it operates in a circuit is quite easy to understand.

PNP—NPN

The transistor is a member of the semiconductor family and is basically a sandwich of different types of either silicon or germanium. The "filling" of the sandwich can either be *p*- or *n*-type material; we can clad a *p*-type filling with *n*-type material giving what we call an *npn* transistor. Alternatively a *pnp* device is made by filling a *p*-type material with an *n*-type.

One encounters both types in practice but nowadays *npn* devices made from silicon predominate, the reason being that they are easier to make and hence cheaper!

Fig. 1(a) shows a diagrammatic cross-section of both types of transistor, *pnp* and *npn*. One end is heavily doped and is called the "emitter"; the other end is lightly doped and called the "collector".

The filling material is very thin in practice (usually one or two microns; 1 micron is a

millionth of a metre) and is called the "base". In its simplest form you can think of an *npn* device as two diodes connected together by their anodes (back-to-back), and facing each other in a *pnp* device, Fig. 1(b).

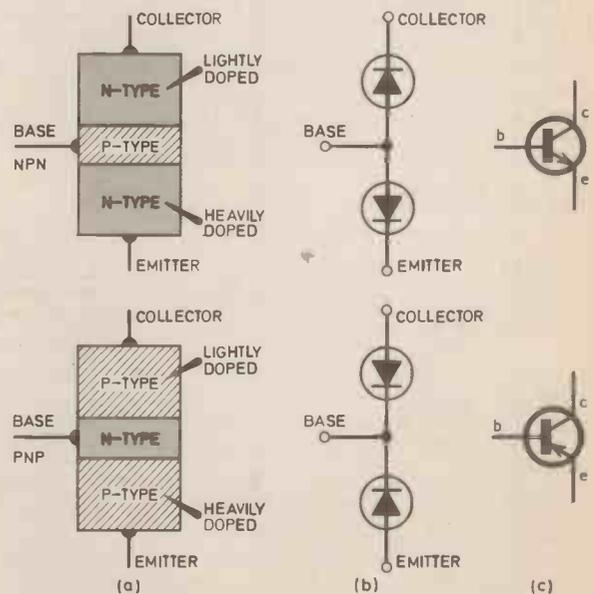


Fig. 1. (a) Schematic diagram of the internal make-up (b) equivalent representation and (c) circuit symbol for (top) *npn* transistor and (bottom) *pnp* transistor.

BASE CONNECTIONS

All the transistors you will come across have connections brought out from the emitter, base and collector. A very common silicon *npn* device is the BC108 and we shall be referring to this frequently in this series.

Fig. 2 shows what it looks like. If you have one handy see if you can identify which lead is which.

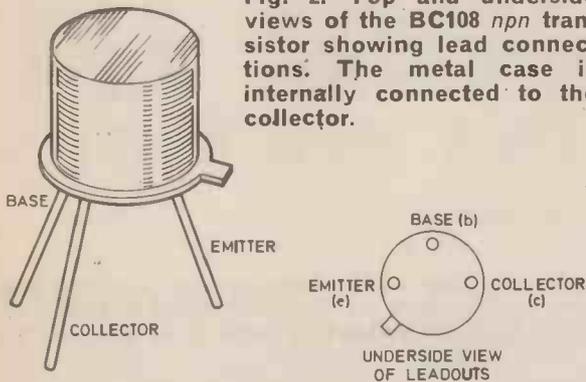


Fig. 2. Top and underside views of the BC108 *npn* transistor showing lead connections. The metal case is internally connected to the collector.

The emitter is the one closest to the spigot on the side of the can, the collector is diametrically opposite, and the base is between the two but set off to one side. This is a metal can transistor and the can is electrically "live"—in actual fact it is connected to the collector as well as the lead out wire.

Different types of transistor may have different shaped cans and some are in plastic encapsulations. Always make sure you know which lead is which before you start using a transistor.

Most constructional projects in **EVERYDAY ELECTRONICS** give you lead designations for the transistors specified, but if you want to experiment with alternative types make sure you know the correct base lead connections.

SIMPLE TEST

Use the BC108 *npn* transistor to identify the effect of the two diodes connected back-to-back. First of all make an ohmmeter on the Demo Deck. Use a 4.5V battery (not 9V) in series with a 2.2 kilohm resistor and VR2 (5 kilohm). Complete the circuit and set VR2 to give zero ohms at full scale deflection and then connect the leads of your ohmmeter between the base and emitter connections of the transistor—to do this it is best to solder the transistor on to three adjacent pins of the Demo Deck and use crocodile clips on the leads from the meter.

If you connect the meter so that the lead coming directly from the negative terminal of the battery goes to the emitter, the meter needle will move to almost full scale showing there is little resistance in the transistor. Now reverse the leads so that the base is more negative than the emitter—you should see that no current

flows (indicated by meter needle not moving). Thus the base-emitter junction is a diode and follows the same rule that we saw last month.

Now leave the lead on the base and transfer the one from the emitter to the collector—again no current flows but reverse the leads and current flows between the base and collector.

If you connect the leads between the collector and the emitter no current should flow whichever way you have them because in both connections, the current would have to pass through a reverse biased diode.

This simple experiment can be used as a rough and ready test to check if a transistor is likely to be in working order, and provided you remember the rule "make p stand for positive for current to flow" you can use it to identify *npn* and *pnp* transistors.


REVERSE VOLTAGE LIMITS

Like all diodes, the junctions of a transistor have reverse voltage limits. These are usually specified with abbreviations. For the BC108 the reverse emitter-base voltage (V_{eb0}) is 5V—i.e. you must never make the base more than 5 volts negative with respect to the emitter (this is why we had to use 4.5V for our ohmmeter instead of the 9V we have been used to). Likewise the reverse base/collector voltage (V_{cb0}) is 30V. You might expect the reverse voltage between the emitter and the collector to be equal to the highest of the other two but this is not the case—it is lower—for the BC108 V_{ceo} is 20V.

The "O" in the suffixes of the reverse voltage characteristics indicates that the third terminal is "open circuit" i.e. not connected.

HOW THE TRANSISTOR WORKS

Let's see what a transistor actually does by using the circuit of Fig. 3(a). Now that we are using the transistor in a real circuit it is important to note the polarity of the supply voltage—for an *npn* transistor the collector must always be kept more positive than the emitter (the converse applies to *pnp* devices). We are going to make the transistor work like a tap and control the amount of current flowing through R1. You can see this happening if you follow the details through on the Demo Deck.

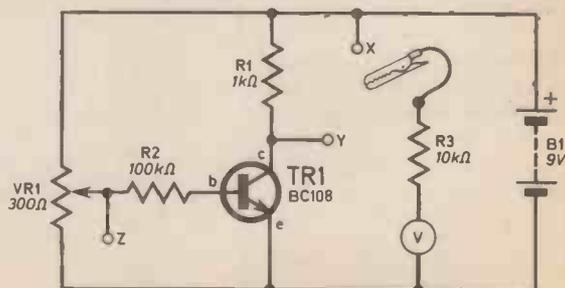

VR1 is a 300 ohm potentiometer working as a potential divider giving us a variable supply at its wiper.

Wire up the circuit of Fig. 3(a) on the Demo Deck as shown in Fig. 3(b), but do not connect R2 to the base of the transistor just yet.

Resistor R3 and the 1mA meter makes a 10V range voltmeter in the usual way. Connect the negative lead to the emitter of the transistor. All voltages we measure will be relative to that of the emitter.

First measure the power rail at point X—it should, of course, be +9V; now measure the potential at the collector of the transistor (point Y) it should be +8.2V. This is what is expected because no current can flow through the back-to-back diodes of the transistor, but the meter will draw some! If you had a high sensitivity meter (say 20 kilohm per volt) this current would be negligible and you would see +9V at both points, X and Y.

Now set VR1 so that the potential on its wiper is zero (with respect to the emitter) and connect R2 to the base of the transistor. VR1 potential is measured by attaching the crocodile clip from the meter to point Z. Again measure the potential at the collector—it should not have changed.

We shall now see what happens if we increase the potential at the wiper of VR1. Do this in 0.5V increments (use crocodile clip at point Z) and for each setting measure the collector potential. You should see that once the potential of the wiper exceeds 600mV, the potential at the collector falls, and continues to fall towards zero as the controlling voltage is increased. Once the collector potential reaches almost zero no more

control can be effected. We say that the transistor is now fully conducting between collector and emitter. This state is called "saturation."

Record your results and plot a graph of collector voltage versus voltage at the wiper. A graph should be obtained similar to that of Fig. 4.

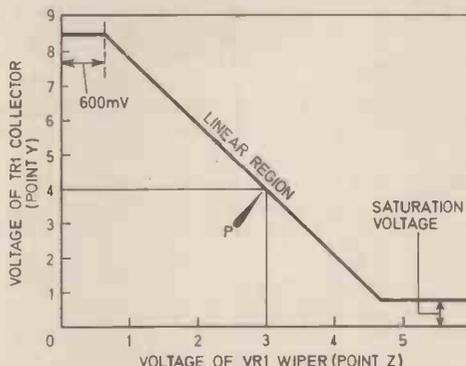



Fig. 4. The graph obtained by plotting the recorded results of experiment using circuit of Fig. 3(a), i.e. voltage at point Y versus voltage at point Z.

Control of the collector/emitter current is brought about by passing a current through the forward biased base/emitter junction. The more current we pass into the base in this way, the more current we can control between the collector and the emitter. The controlling current is called "base current," (I_b) and the controlled current "collector current," (I_c).

Base current is set by the potential difference between the wiper of VR1 and the emitter of the transistor, acting through the resistance R2

Fig. 3(a) (left). The circuit diagram used for investigating some of the properties of a BC108 transistor.

Fig. 3(b) right. The circuit of Fig. 3(a) wired up on the Demo Deck.

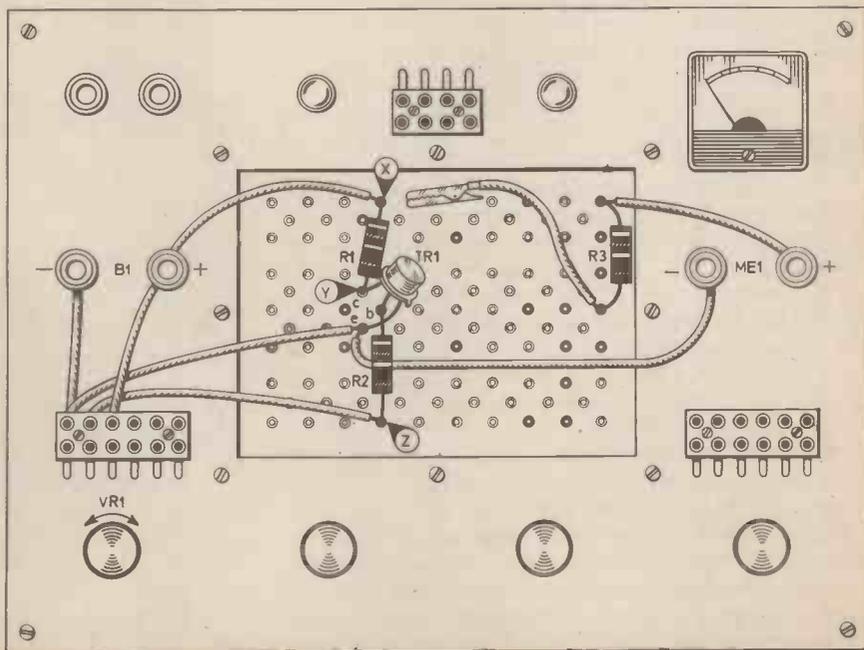

and any internal resistance between base and emitter. The latter is small and can be neglected at this stage. We must, remember, however, that the base must be made at least 600mV positive with respect to the emitter before any current can flow (this is the usual forward voltage drop for any silicon junction).

We can thus calculate the current flowing into the base by measuring the potential at the wiper of VR1, subtracting the base emitter forward voltage drop (600mV) and dividing by the value of R2.

GAIN

If you do this for your experiment you will find that the base current ranges from 0 to 0.084mA. The range of collector current we are controlling was from 0 to 9mA. It can be seen that the transistor enables us to use a very small current to control a larger one. We call this effect "current amplification." The factor that governs the ratio between I_b and I_c is called "gain" and although it increases with I_c it is pretty well constant for any given transistor. It can, however, vary widely between different types of transistor and even between devices having the same type number! Provided you take a combination of base and collector currents within the controllable region (this is called "linear region") you can calculate the gain of the transistor you are using.

It would be best to increase the potential at VR1 until the collector potential is approximately 4V. This reduces the shunting effect of our voltmeter.

Use the precise values of voltage measured to calculate the current through R2 and R1 then use the ratio of these values to calculate the gain.

$$\begin{aligned} \text{gain} &= \text{collector current} \div \text{base current} \\ &= I_c \div I_b \end{aligned}$$

For the BC108 transistor it should be approximately 200, but as we have said, will vary from device to device.

Example To calculate the gain from your plotted curve (similar to the one of Fig. 4) select a convenient point on the linear region such as point P of Fig. 4.

The base current, I_b is given by the voltage difference between the base and emitter divided by the base resistor.

$$\text{i.e. } \frac{3 - 0.6}{100.000} = 0.024\text{mA}$$

Now the voltage drop across the collector resistor R1 is $(9 - 4)\text{V} = 5\text{V}$. Therefore, collector current I_c is $(5 \div 1000) = 5\text{mA}$.

Substituting these values for I_c and I_b in equation (1) gives the gain $= (5 \div 0.024) = 208$.

There are various ways of describing current gain for a transistor so we shall define that measured above a little more precisely—it was the d.c. current gain. This is sometimes abbrevi-

ated to the designations β (beta) or h_{FE} . The latter is rather a strange type of designation but is one of a range of what are called "h" parameters—we need not worry ourselves about these in this series except for the term h_{FE} which is usually used in manufacturer's data sheets. Do not confuse h_{FE} with h_{ie} , the latter is called the small signal current gain and we shall not be dealing with this until later.

The gain equation above can be rewritten:
 $I_c = h_{FE} \times I_b$

Remember that the experiment we have just done has been using a silicon *nnp* device. We could have used one made from germanium having *nnp* structure and obtained a similar effect—except that the base/emitter forward voltage drop would have been only about 200mV and h_{FE} , in general, would have been lower.

We could also have used a silicon or germanium *pnnp* device but would have had to reverse the battery connections so that the collector was negative with respect to the emitter. The same rules would have applied and we could have still calculated a value for h_{FE} .

If you are a little confused by the difference between *nnp* and *pnnp* devices do not worry too much as this stage—most of the early experiments in Teach-In will use *nnp* devices and when you have got used to these you will find it quite straightforward to switch over to *pnnp* devices when necessary. The most important thing to remember is the polarity of battery voltage when using one type or the other. An aid to remembering what the polarity ought to be is to bear in mind the direction of conventional current flow;

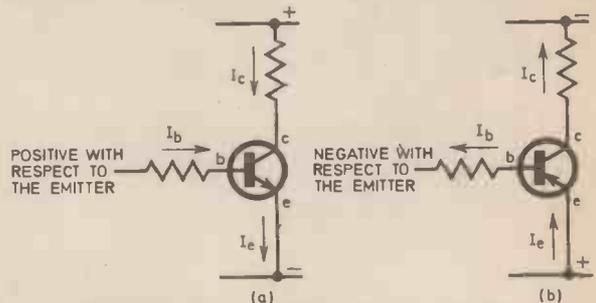


Fig. 5. Circuits showing major current flow directions for (a) *nnp* and (b) *pnnp* transistor. I_b —base current, I_c —collector current, I_e —emitter current.

the arrow on the emitter of the symbol points in the direction of current flow, i.e. it points away from positive and towards negative. See Fig. 5.

Whether using *nnp* or *pnnp* devices an aid to remembering how to turn collector/emitter current "on", is to make the potential at the end of the resistor connected to the base tend towards the same polarity voltage as applied to the collector; the more you move towards this voltage, the more I_b increases, and I_c will increase in direct proportion.

When the potential feeding the base rises towards the supply voltage the voltage at the collector falls towards the emitter voltage. This is called "inversion."

In Fig. 3 R1 is called the "collector load." The limit of I_c control is set by the value of this resistor; if it has a high value then it does not matter how much base current you apply, you cannot control more collector current than that given by the collector supply voltage divided by the value of collector load. On the other hand, if the load is too low you might find yourself trying to force more collector current than the construction of the transistor can handle. Thus one of the specifications of a transistor is the maximum collector current it can handle without "blowing". This is called I_{cmax} and for the BC108 is 100mA.

A final parameter we must deal with is the power rating of a transistor. As current is passing through it a certain amount of heat is dissipated. We already know that too much heat can spoil the properties of a semiconductor so it must be limited. The limit is set by the maximum power dissipation parameter, P_{cmax} . It is easy to calculate what the power dissipation is likely to be; it is the dissipation you would get if you replaced the transistor in the circuit with a resistor having the same ohmic value as the collector load.


Table 1 gives you some typical values of parameters for some common transistors of varying types, powers and polarities.

Table 1: THE MORE IMPORTANT CHARACTERISTICS OF SOME COMMON TRANSISTORS

Type	Polarity	P_{cmax}	V_{cbo}	V_{ceo}	V_{ebo}	I_{cmax}	h_{FE}
BC108	npn	300mW	30V	20V	5V	100mA	240
2N2926	npn	200mW	18V	18V	5V	100mA	150
BFY51	npn	800mW	60V	60V	6V	1A	70
BFX13	pnp	300mW	-20V	-15V	-5V	100mA	120
2N3702	pnp	360mW	-40V	-25V	-5V	200mA	60
AC126	pnp	500mW	-32V	-32V	-10V	100mA	100
OC72	pnp	125mW	-16V	-16V	-3V	125mA	50
OC26	pnp	12W	-16V	-16V	-10V	3.5A	50
OC36	pnp	30W	-80V	-32V	-40V	10A	70

Fig. 6(a) (below). The circuit diagram of the "Electronic Candle" which illustrates positive feedback.

Fig. 6(b) (right). The circuit of Fig. 6(a) wired up on the Demo Deck. Ensure that PCC1 is close to LP1.

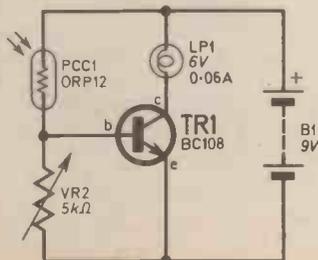

ELECTRONIC CANDLE EXPERIMENT


We shall now make a simple working circuit using the circuit diagram of Fig. 6(a). This is wired up on the Demo Deck as shown in Fig. 6(b). Connect the ORP12 (light dependent resistor) very close to the LP1 on the Demo Deck as shown below. Set VR2 to zero ohms. The potential at the base of TR1 will be zero, therefore no current will flow between collector and emitter. Now, in a reasonably lit room, increase the value of VR2. At a certain point the potential at the base will reach 0.6V (set by the potential dividing effect of PCC1 and VR2) and the transistor will start to conduct (the bulb will glow dimly).

Continue to increase the resistance of VR2; the current flowing through PCC1 will now pass into the base/emitter circuit of the transistor in preference to the higher resistance path through VR2. This base current will cause TR1 to pass more collector current until the bulb is fully illuminated.

When you reach this point (the minimum value of VR2 that will give full illumination) try casting a shadow over PCC1, the lamp will go dim and ultimately go out altogether as I_b reduces due to the resistance of PCC1. We did a similar sort of thing in Teach-In Part 4.

The difference is that we now have a circuit that is much more sensitive to small changes in light level which is brought about by the transistor amplifying the current from the photo resistive cell.

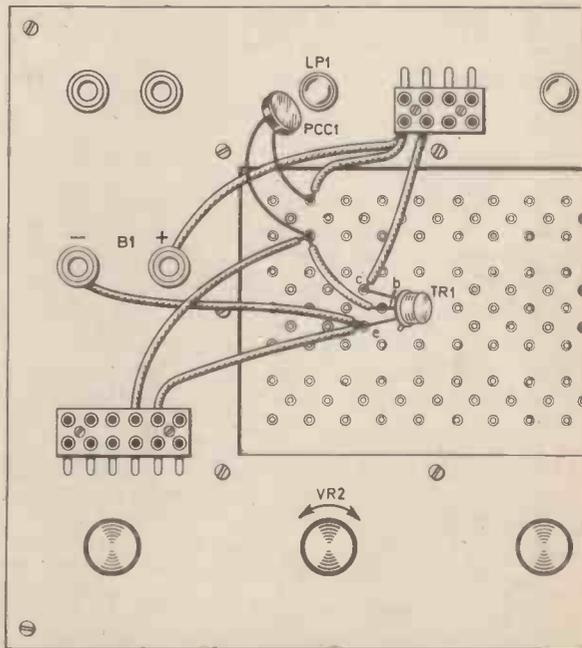If you place the cell very close to the bulb in a dimly lit room you can set the value of VR2 so that the ambient lighting does not turn the transistor on, but the light from the bulb will.



Break the light path between the bulb and the cell and the bulb goes out and stays out. Now use a match or lighter to provide a stimulus of light. Bring it close to the bulb/cell assembly and the bulb lights up; you can now remove the match and the bulb will stay on because its own light output is holding the transistor on. This is called "positive feedback" and in this circuit will provide an amusing party trick—especially if assembled to look like a candle.

A bit of practice at "snuffing" the candle with the fingers (actually you are breaking the light path between the bulb and the cell) will make the effect even more astounding.

Photograph of the Demo Deck set up for the Electronic Candle Experiment showing the lamp being "lit" by the light emitted from the lighter.



TEACH-IN PART 6—ERRATA

Fig. 4(b) last month shows a lead connected wrongly. The lead from the junction of R3 and the negative meter terminal should go to the negative end of VR1 (not the wiper as shown) i.e. the one connected to the battery negative.



Next month: Multivibrators. The components needed for next month in addition to those already acquired are: resistors 22 kilohm (2 off), 100 ohm (1 off); capacitors 0.1 μ F polyester (2 off), 500 μ F elect. 12V (1 off); transistors BC108 (1 off); diodes OA91 (1 off).

Ruminations By Sensor

Not so Clever

The coal miners' strike has shown how dependent we are, in this age of high technology, on the efforts of men who work in damp, dirty and often dangerous conditions.

I find it difficult to comprehend that on one hand the semiconductor industry owes its existence to the ability to obtain and to process materials with an impurity content of less than ten parts in a thousand million, and to operate with tolerances down to one millionth of a metre, while on the other hand men have still to dig fossil trees out of the earth (albeit with mechanical assistance) so that these fossilised remains can be burnt to boil water in order to raise steam

and to generate electricity! Without coal and electricity there would be no semiconductor industry; truly our idol has feet of clay!

Let There be Light

Have you heard about the old lady who telephoned the C.E.G.B. to complain that, during the power cut, the buses were passing her house with all their lights on? She also said that she could manage to get along quite well without the electricity, except for the little light in the hall, and could they please leave that one switched on.

Many people must have been irritated, in the early days of the strike, to see street lights blazing all day and switched off at night, due to their electric clock switch mechanisms getting umpteen hours behind. To the electronics man the answer to this problem is so simple—a light operated switch, either using discrete components or in integrated form.

A recently introduced inte-

grated circuit provides the necessary photo cell, level sensor and time delay all on one tiny chip of silicon and complete with lens. It could operate a relay or, better still, work into a switching transistor controlling the street lamp directly.

Some years ago, I was shown around a large generating station, where, tucked away in a dusty corner there was a cast iron box about the size of a domestic cooker. This apparatus was installed at the station about twenty five years ago and its purpose was to switch on all the electric street lamps in the town.

When switched on it produced a ripple which was superimposed on the mains. Sections of street lighting were grouped together under the control of master switches, spread throughout the town, which were operated by switching on the ripple equipment. The system had been in use but for some reason, unknown to my guide, had been discontinued. It would have been a blessing during February 1972.

Everyday Electronics, May 1972


Watch for these features in the

JUNE



Wash 'n Wipe

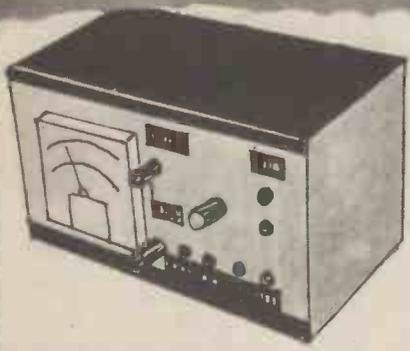We have produced one very popular car wiper accessory now we are going to describe another. This unit starts the wipers automatically when the washers are used, keeps the wipers going for a pre-determined time, and then turns them off. For all 6 and 12V cars fitted with washers and self parking wipers. Extremely useful with the Windscreen Wiper Control or just on its own.



Multimeter

Probably the most useful of all test equipment is a multimeter and next month we show you how to build a fairly simple one that will meet the needs of most constructors.

Light to Sound Converter

A project for those who like to experiment. This unit produces an audio tone, the frequency of which is dependent on the light level sensed by a photocell.


Also...

A new feature for all beginners and constructors... GUIDE TO CIRCUIT SYMBOLS

A new feature for all beginners and constructors; Guide To Circuit Symbols. We explain the symbols and show you what the components look like. Starting next month.


On sale Friday, May 19

Everyday Electronics, May 1972

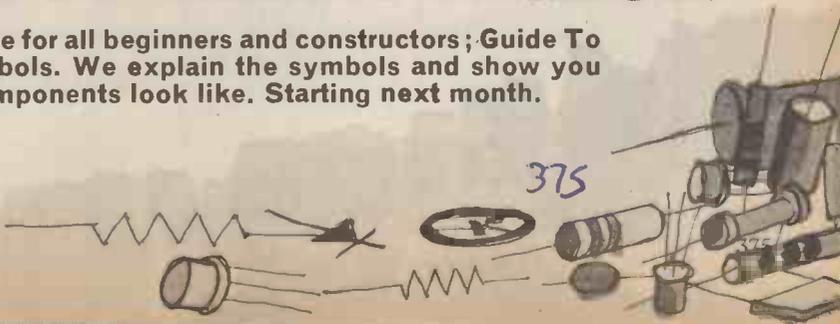

Use this 'electronic eye'
to monitor the busyness
of your bee-hives

By
G.A.Cozens

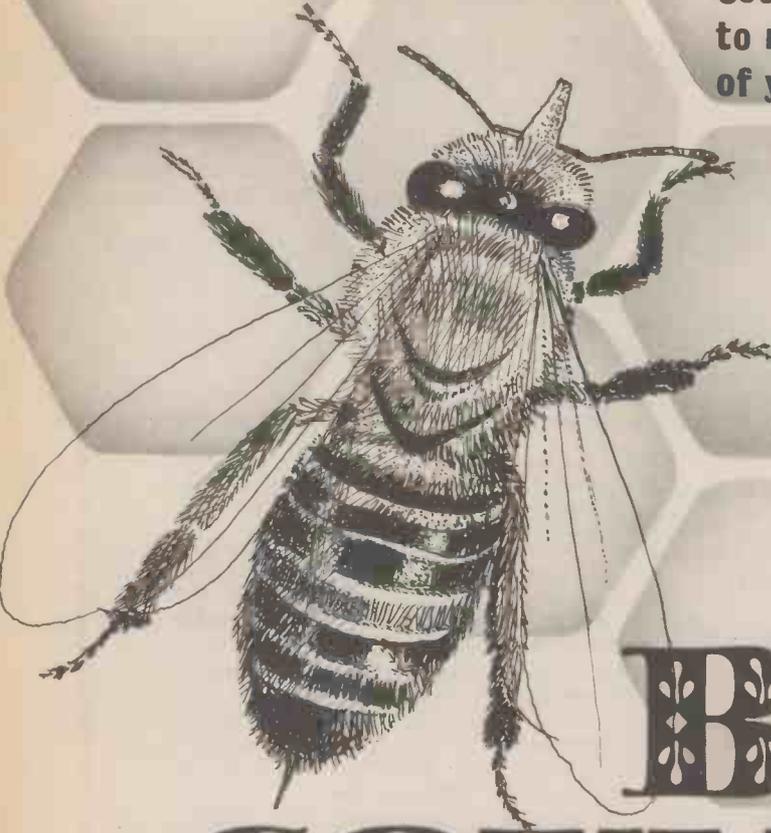

BEE COUNTER

MODERN research calls for accurate measurement and comparisons, and with this in mind this device was designed to help the bee-keeper assess the performance of his beehives more definitely, and to compare the different strains of bees under the same working conditions and so help to breed a strain which will produce the most honey under all the difficulties encountered in our changing climate without the rather nasty habit of the English bee, of attacking the bee-keeper as soon as he appears anywhere near the hive.

The Bee Counter is an instrument which records the number of bees entering the hive, and used in conjunction with other devices such as a wind speed indicator, a wind direction indicator, an air temperature thermometer, a maximum/minimum thermometer, a rain gauge and a sunshine recorder, then some degree of assessment can be made, and some basis established for the bee-breeder to work upon his main goal—lots of honey from a reasonably good tempered, busier bee.

The Bee Counter makes use of the fact that bees are highly organised in their habits, and utilises the bees sense of sight and smell. These bee "characteristics" are used in the design of the cabinet housing all the circuitry which is described later in full detail.

THE CIRCUIT

The complete circuit diagram of the counter is shown in Fig. 1 and is basically an amplifier which works as follows.

The lamp LPI, which is always "alight" when



Approximate
cost of
components...
£ 2.20 plus case

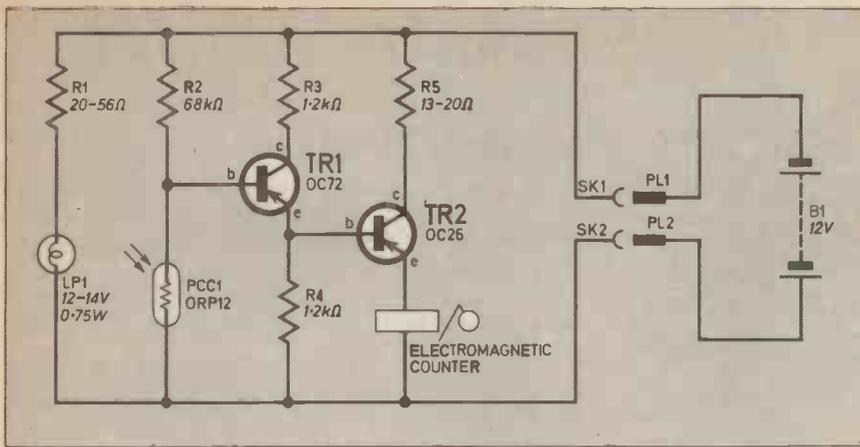


Fig. 1. The complete circuit diagram of the Bee Counter.

the unit is switched on, illuminates the light dependent resistor, PCC1, and causes its resistance to be at a low value, about 100 ohms.

The l.d.r. and R2 form a potential divider circuit and under "illuminated conditions" of the l.d.r., a positive voltage with respect to the emitter, is applied to the base of TR1 causing it to be in a conducting state.

With TR1 conducting, a negative voltage is applied to TR2 base with respect to the emitter and consequently TR2 is "off" (not conducting).

When the light path between LP1 and PCC1 is broken, the resistance of PCC1 increases considerably (to about 100 kilohm for complete "blackout"). This causes the potential at TR1 base to go negative and turns it "off". This state of TR1 causes the voltage applied to the base of TR2 to go more positive and causes it to switch "on" i.e. conduct—current flows through TR2.

When current flows through the emitter leg of TR2 containing the relay coil in the counter, the relay is energised.

When the light to PCC1 is restored, TR2 switches "off" and the counter is de-energised and springs back to its off position and in doing so mechanically adds "one" to the counter readout.

The arrangement of LP1 and PCC1 in the case is so devised that the bee, on entering the hive, breaks the light path between these devices and its entry is thus recorded.

The 13-20 ohm 3 watt resistor, R5, in the collector circuit of the power transistor, TR2, is to prevent damage to the counter or the transistor if the entrance passage to the hive should become blocked, as once happened in the prototype when a drone got stuck in the narrow part.

A heavy duty battery is required to operate the Bee Counter since current drain is substantial—250 mA when TR2 is "off" and 400 mA when TR2 is "on" at 12V. A car battery is therefore recommended to supply the power. The cost of this battery is not included in approximate cost.

The voltage is fairly critical as it must be sufficient to operate the counter, but not high

Components....

Resistors

- R1 20-56Ω 3 watt
- R2 68kΩ
- R3 1.2kΩ
- R4 1.2kΩ
- R5 13-20Ω 3 watt

All ½ watt carbon ± 10% unless otherwise stated

Transistors

- TR1 OC72 (or similar) germanium pnp
- TR2 OC26 germanium pnp

Light Dependent Resistor

- PCC1 ORP12


Micellaneous

- LP1 12-14V 0.75W bulb and holder
- PL1, PL2 Wander plugs, 1 red 1 black (2 off)
- SK1, SK2 Sockets to suit plugs PL1, PL2
- B1 12V battery—heavy duty rechargeable type (Not accounted for in cost box.)
- Counter: Post Office type 14C 4.2Ω 4 figure readout. Cedar wood, Perspex and adhesive, Paxolin, wood screws, 4 B.A. nut and bolt, wood glue.

SEE
**SHOP
TALK**

enough to cause overheating of TR2 or the counter coil in the event of the passage being blocked for long.

If the apparatus is disconnected every night the battery will last at least a week on one charge.

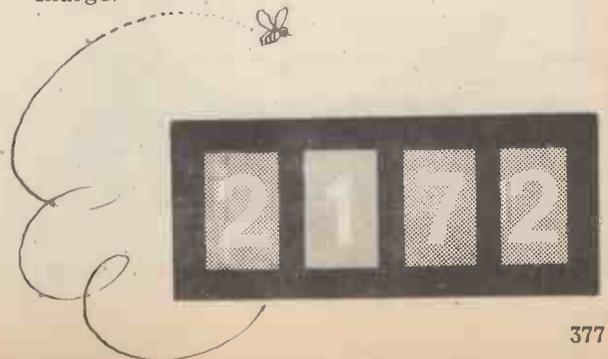

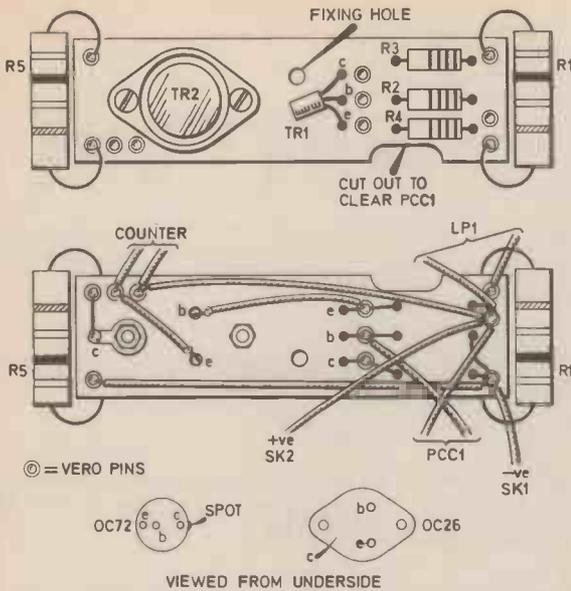


Fig. 2. The layout of the components on both sides of the Paxolin board. Veropins are used for attachment.

Variations in performance can be dealt with in several ways. The lamp should be bright enough to turn off the amplifier, but not any brighter than necessary. This is best adjusted by altering the series resistor R1, which may be increased to as high as 56 ohms.

Also, the size of the light hole can be varied, or a part of the l.d.r. painted over so that it has less area exposed, until the instrument is sufficiently sensitive, but positive in its action.


THE COUNTER

The electromagnetic counter used is a Post Office type. It has a four digit readout and can thus count up to 9,999. The maximum count rate is ten per second.

COMPONENT WIRING

Most of the components of Fig. 1 are mounted on a piece of Paxolin size $4\frac{1}{2} \times 1\frac{1}{4}$ inches with a cut-out as shown along one side to accommodate the light dependent resistor, PCC1.

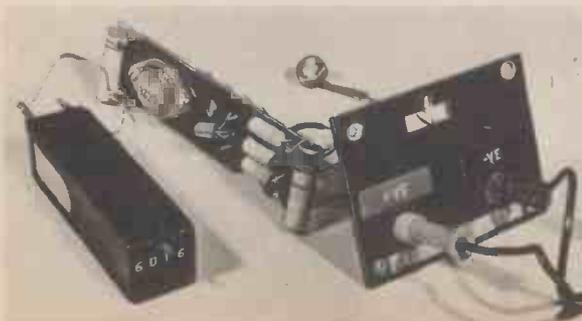Both sides of the board containing the components are shown in Fig. 2.



Veropins are used for mounting the components in position and small holes should be drilled where indicated to accommodate these pins.

Three more small holes of the same size should be drilled to take the leads of TR1 as shown.

Drill the component board fixing hole and the four holes for transistor TR2; (see reverse side of component board Fig. 2); $\frac{1}{8}$ in. diameter holes will do for all five holes.

Begin assembly by pushing in all the Veropins and then attach TR2 to the board using two small nuts and bolts.

The connection to the collector of TR2 is via its casing, so a solder tag should be attached to one of the securing bolts to enable this connection.

Attach and solder all the components, link wires and flying leads as detailed in Fig. 2 making sure a heat shunt is used when soldering in TR1, which incidentally should be the last component connected.



The l.d.r. should be attached to the board via 6in. long flexible leads.

The flying leads to the counter should be about 4in. long.

The two wander sockets used for battery connection to the counter, are attached to the end of the case which is made from a piece of Paxolin, dimensions are given in Fig. 3.

The connection wires from the wander sockets to the component board should be about 4in. long.

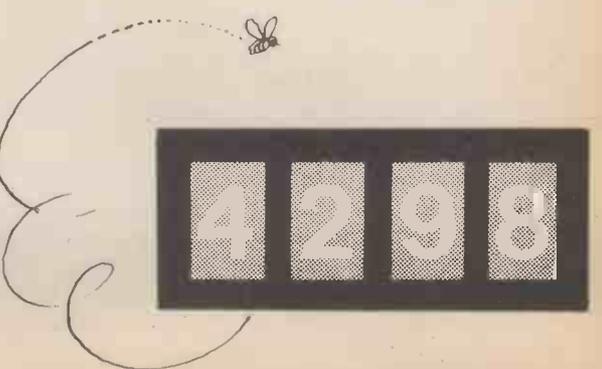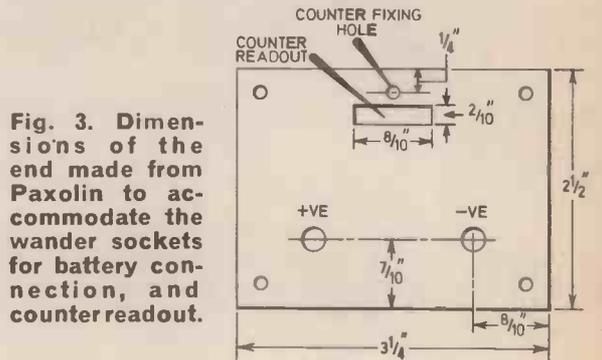Connection to the battery is made via two wander plugs and a length of twin flex.



BEE COUNTER


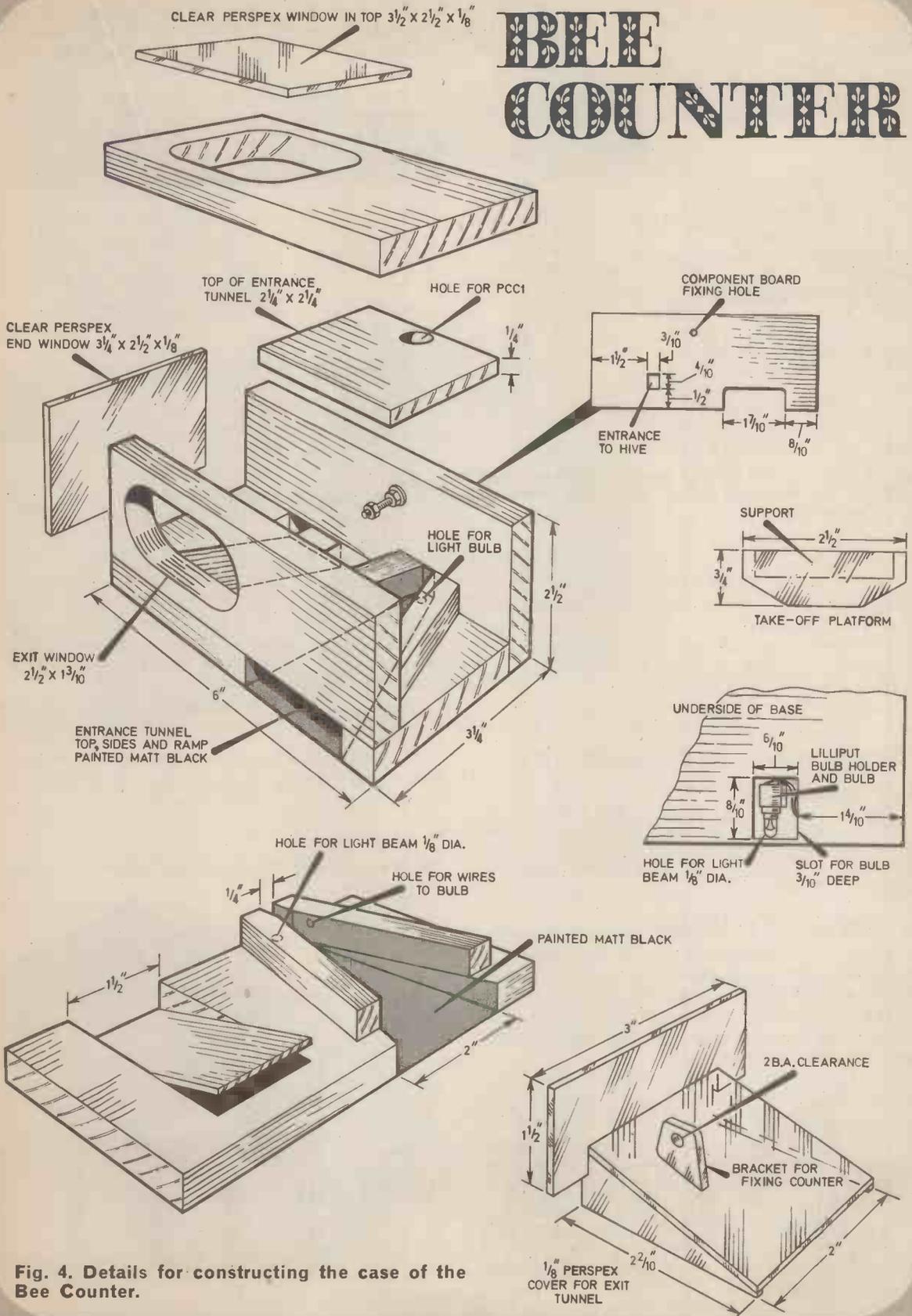


Fig. 4. Details for constructing the case of the Bee Counter.

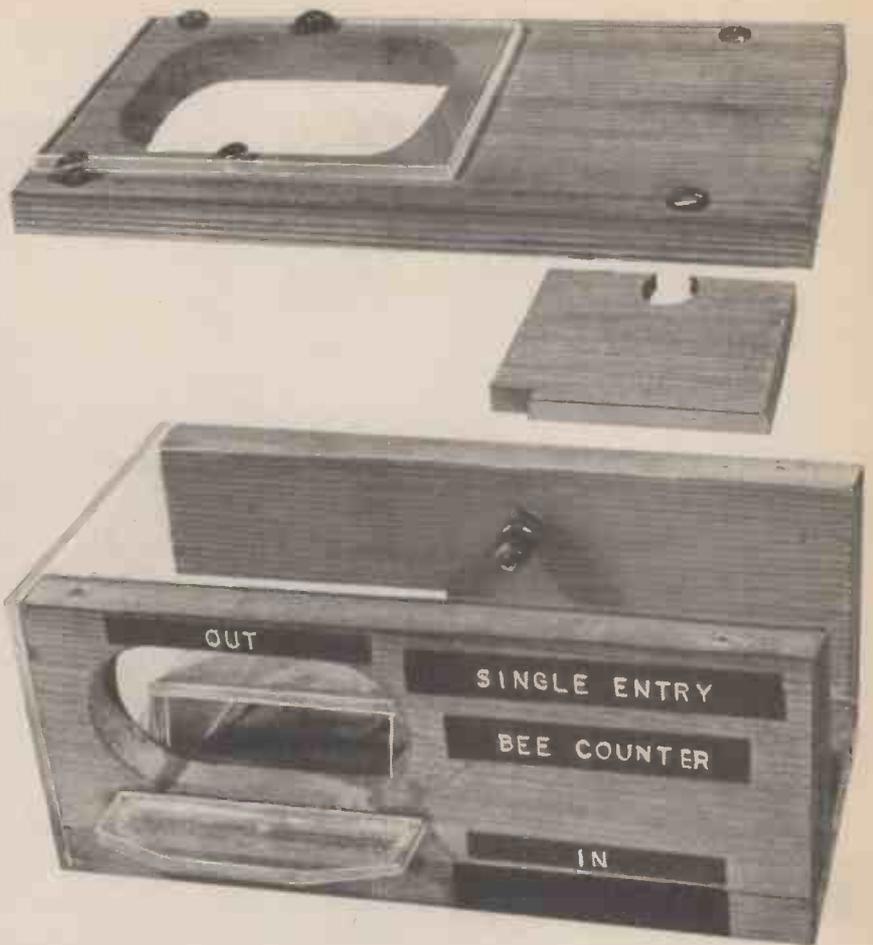A photograph of the prototype with top and tunnel lid (which holds PCC1 in position) removed. The photograph clearly shows the entrance and exit tunnels (labelled IN and OUT respectively). The take-off platform, made from Perspex, is located just beneath the exit cut-out, and is glued in position with Perspex adhesive.



EXIT AND ENTRANCE GEOMETRY

As said before, this device and its design utilises the bees' senses of smell and sight. From inside the hive, the exit from the hive appears as a bright opening to the outside world and so the exit path through the instrument must be a tunnel with transparent sides and top to allow this condition to be fulfilled.

In the instrument this tunnel slopes upwards so that when the bee emerges, it finds itself on a platform of Perspex, about $\frac{3}{4}$ in. wide, situated above the hive base, and flies away.

When it returns, it will land on the hive base (landing/alighting board) and walk towards the hive.

The entrance to the hive is now through the Bee Counter which is a tunnel painted matt black; when the bee walks along the front of the instrument and reaches this tunnel it will enter.


On entering, the tunnel becomes narrower and at the same time slopes upwards until it is just wide enough for a single bee to pass.


There is a lamp under the narrow part, with a hole in the floor of the tunnel, made up to the level of the floor with Perspex cement so that light can shine up through it.

The light dependent resistor is situated in the

roof of the tunnel and as the bee walks between this and the lamp, the light beam is cut and the circuit activated.

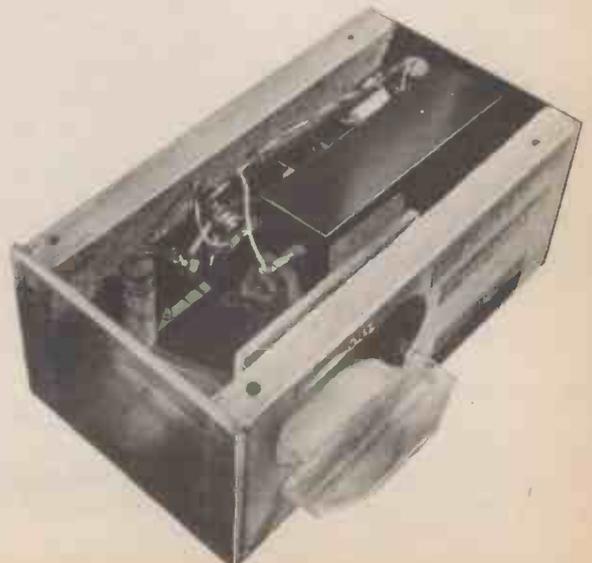Positions of the "electronics" within the case.



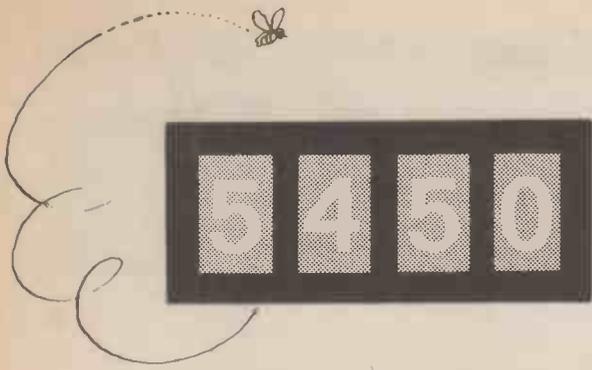

CONSTRUCTION OF CASE

Cedar wood should be used to construct the case as this material will be readily acceptable to the bees.

Cedar wood will also withstand the weather without the need for painting but it is well to remember that if the counter is to be used in exposed outdoor conditions, weather protection becomes an important consideration, whereas in laboratory conditions it is not so.

The best compromise for an outdoor installation is a shelter which will keep off the rain.

First of all make all the wooden parts of the case as detailed in Fig. 4.

Now solder the two thin flexible covered wires to the bulb holder tags and screw in the bulb. These wires are led out through the top of the base and the bulb assembly is glued in position.

It is not likely that the bulb will need replacement because it is "under run" and there is a 20 ohm resistor (R1) in series with the bulb which reduces the light and heat dissipated in the bulb.

When the glue has set, fill up the light hole with Perspex cement so that it comes flush with the passage floor.

Glue down the two sides of the tunnel so that the width of the narrowest region is $\frac{1}{4}$ in. Paint the tunnel top, bottom and sides a matt black.

The light dependent resistor should be a push fit into a hole in the tunnel roof.

Glue and screw the front and back to the base and glue the exit ramp in position. Drop the tunnel roof into position indicated. The other parts of the case are made from Perspex and their dimensions are given in Fig. 4.

With these made we can proceed with the assembly.

ASSEMBLY

Begin by screwing the Perspex side and top windows in position as indicated. Glue the Perspex platform to the front and place the Perspex exit guide in position.

Now solder the two wires from the bulb holder to the component board as detailed in

Fig. 2, push the l.d.r. in position and then attach the board to the back of the case by means of a 4 B.A. nut and bolt. This bolt should be countersunk into the back so the back is flush with the front of the hive. If there is a gap here, the bees will try to go in or out through the smallest crevice.

Attach the wander sockets to the Paxolin side and solder to the appropriate flying leads from the component board. Next screw the Paxolin side to the case.

When the flying leads to the counter have been connected, fit the counter into its locating holes, (one end in the Paxolin and the other in the bracket on top of the Perspex exit guide) and secure with nuts. The counter digits should be visible through the slot in the Paxolin side.

Screw the top on and the unit is complete.

CAPACITY AND POSITION OF CASE

The single entry counter (as this is) is only suitable for a three or four frame hive, since with a full scale hive the returning bees would sometimes overload the tunnel capacity.

The maximum a single entry counter can handle is about 60 per minute.

For a full scale hive a three entry counter is necessary. This means the entry tunnel is divided into three passages, each with its own light beam arrangement, amplifier and counter.

Whereas the single entry model is only $6\frac{1}{4}$ in. wide, which is about right for most observation hives, it is better to make the three entry model $16\frac{1}{2}$ in. wide so that it takes up the whole width of a Standard National hive.

When the counter is put in front of the hive the hive should be moved back by a distance equal to the depth of the Bee Counter, in this case $3\frac{1}{4}$ in. so that the point of entry is exactly as it was without the counter.


When this is done the bees will soon get used to the new conditions and will be using the exit and entry passages without any confusion. □



METAL

A simple, easy to construct self-contained locator giving a meter indication of buried metal.

By D. Bollen

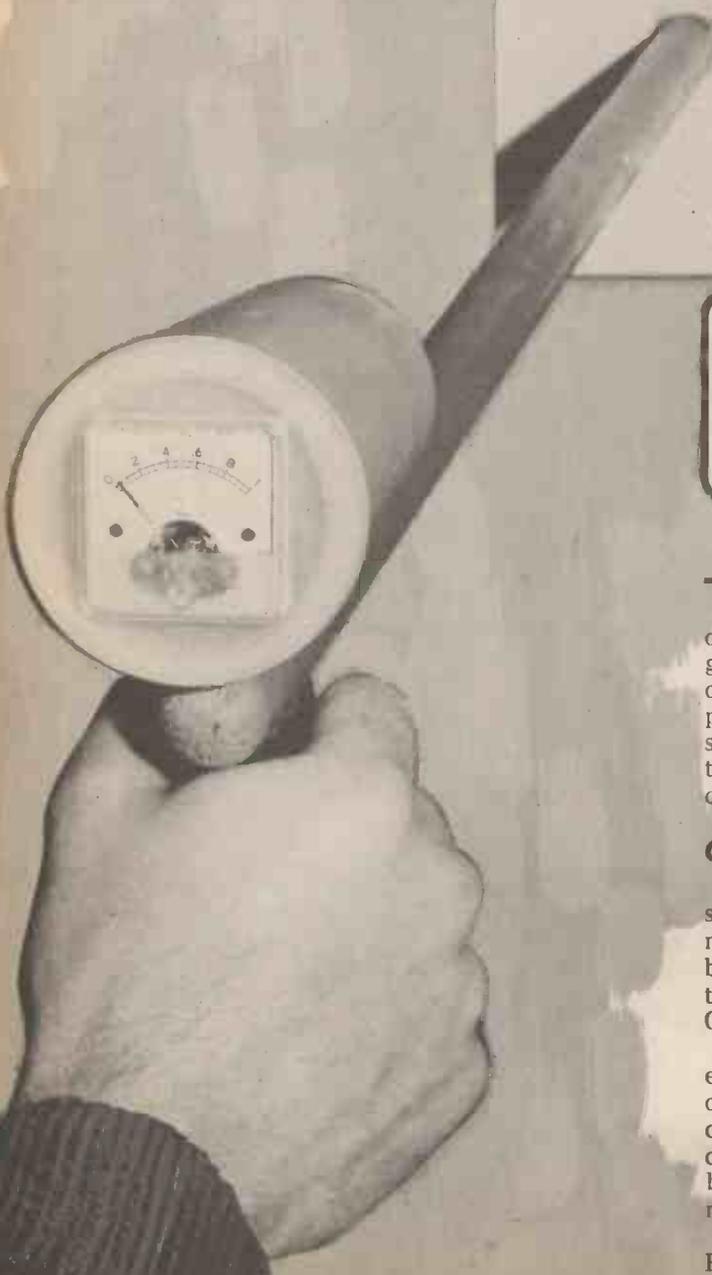

**Approximate
cost of
components...**
£ 4.00 plus case

THE metal locator described in this article was designed for simplicity and ease of operation. A single transistor circuit is used to give a clear meter indication of the presence of buried metal without the need for headphones or a nearby portable radio as used by some locators. Under typical operating conditions the instrument will detect a 2p coin at a depth of about 1 inch.

CIRCUIT OPERATION

The complete circuit of the metal locator is shown in Fig. 1. Transistor TR1 acts as a common base oscillator with positive feedback between collector and emitter controlled by trimmer C4. Search coil inductor L1 is tuned by C2 to give an oscillation frequency of 100kHz.

When the circuit is functioning, L1 will induce eddy currents in nearby metal and this transfer of energy causes an increase of TR1 emitter current. Although small, the accompanying change of d.c. voltage across R3 can be detected by a sensitive null (or zero registering) voltmeter.

In Fig. 1 the d.c. null voltmeter consists of R3, R4, R5, R6 and ME1. Capacitor C5 is included

LOCATOR

to remove unwanted a.c. from the voltmeter input, and diodes D1 and D2 protect the meter movement against overload.

At a certain setting of C4, the d.c. voltage at TR1 emitter will equal the voltage at the junction of R5 and R6 so that no current flows through ME1; this can be taken as the normal operating point for the circuit. If metal is brought close to L1, the emitter voltage of TR1 will rise by several millivolts in relation to the voltage at the junction of R5 and R6, and the meter will read.

Full scale sensitivity of the null voltmeter is around 150 millivolts. Metal Locator response is shown in Fig. 2, where meter reading is plotted against depth for three weights of metal.

CONSTRUCTION

Commence construction by cutting a piece of 0.1 inch matrix plain perforated circuit board to a size of 3.1 by 1.4 inches, and drill holes to take C4, VR1, and S1 (see Fig. 3).

Cut two brackets from a length of 1/2 inch aluminium angle and drill to accept the meter terminal screws and 6B.A. circuit board mounting screws.

Bolt the brackets to the circuit board, complete with solder tags, and insert all terminal pins in the positions shown in Fig. 3.

With C4, VR1, and S1 in place on the circuit board, proceed to mount and solder the remaining components in the following order; resistors, capacitors, wire links and leads, diodes and the transistor, using a heat shunt to protect the diodes and transistors while soldering them.

Obtain a plastic beaker with lid (of minimum dimensions 5 inches high by 2 1/2 inches diameter) and cut away the centre of the lid to accept the meter ME1. Next, drill holes in the beaker for L1 leads, woodscrews, and to allow access to the circuit board controls, see Fig. 4.

When following the step-by-step instructions in Fig. 5, for making up the search coil L1, ensure that the pile windings can slide easily off the 5 inch diameter former. Short strips of insulating tape, placed sticky side out around the former, will hold the turns together and facilitate removal of the coil. Do not use Sello-tape for this purpose as it is likely to damage the wire.

The metal locator frame (Fig. 4 and 6) consists of a chipboard or plywood handle, a 5/8 inch diameter dowel pole, and two s.r.b.p. or Perspex sheets for the search head. Screw and glue the handle to the pole and then glue the other end of the pole to the search head top board, this assembly can then be painted.

To complete the construction, screw the

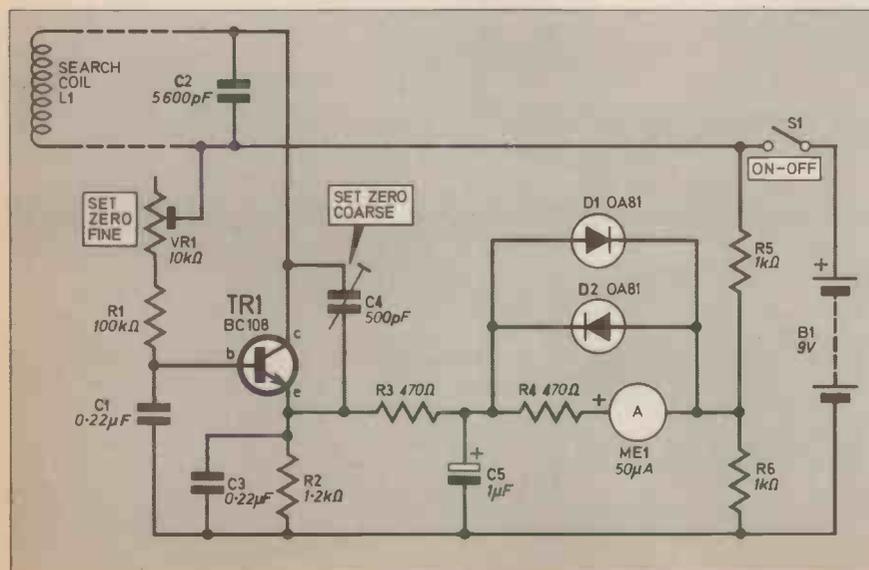


Fig. 1. Circuit diagram of the Metal Locator. The search coil L1 is mounted in the locator head and the dotted lines are the connecting wires to the circuitry.

OPERATING LICENCE

The *Metal Locator* described in this article is designed to operate in the frequency band specified by the Ministry of Post and Telecommunications (16 to 150kHz). The circuit design of the locator should not be altered in any way that may affect the operating frequency.

A licence must be obtained before using the locator; this costs 75p for 5 years. An application form for a licence is obtainable from the Ministry of Post and Telecommunications, Waterloo Bridge House, Waterloo Road, London, S.E.1.

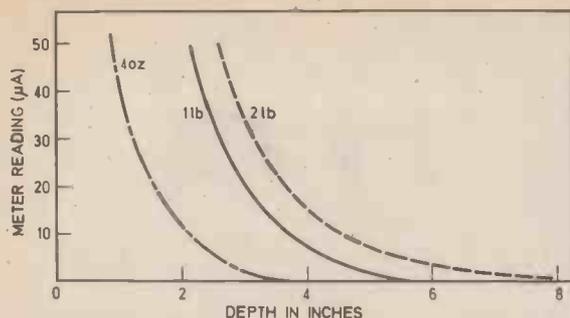


Fig. 2. Response curves of the Metal Locator.

plastic beaker to the pole opposite the handle, securely clamp the search coil between the boards, run twin leads from L1 to the beaker, and position the battery.

In the prototype, the battery was held in place behind the meter with a rubber band, as shown in the photograph, but it could equally well be fixed inside the beaker with a small clip or elastic band.

SETTING UP

Adjust VR1 to mid track, C4 to minimum capacitance (unscrewed), and switch on. The meter pointer should go beyond full scale. With the search coil well away from metal objects, screw in C4 until the meter reads somewhere between zero and full scale. Trim for a zero reading with VR1.

If the meter fails to read, or no response is obtained from adjustment of C4, check for wiring errors.

A certain amount of drift will be evident immediately after the locator has been switched on, therefore allow the circuit to settle down and then readjust C4 and VR1. Locator response can then be checked with metal weights and compared with Fig. 2.

Increased sensitivity can be achieved by reducing the value of C3 to 0.15µF, but this will enhance circuit drift to the point where frequent adjustment of VR1 is necessary. Conversely, drift and sensitivity will be reduced if C3 is increased in value.

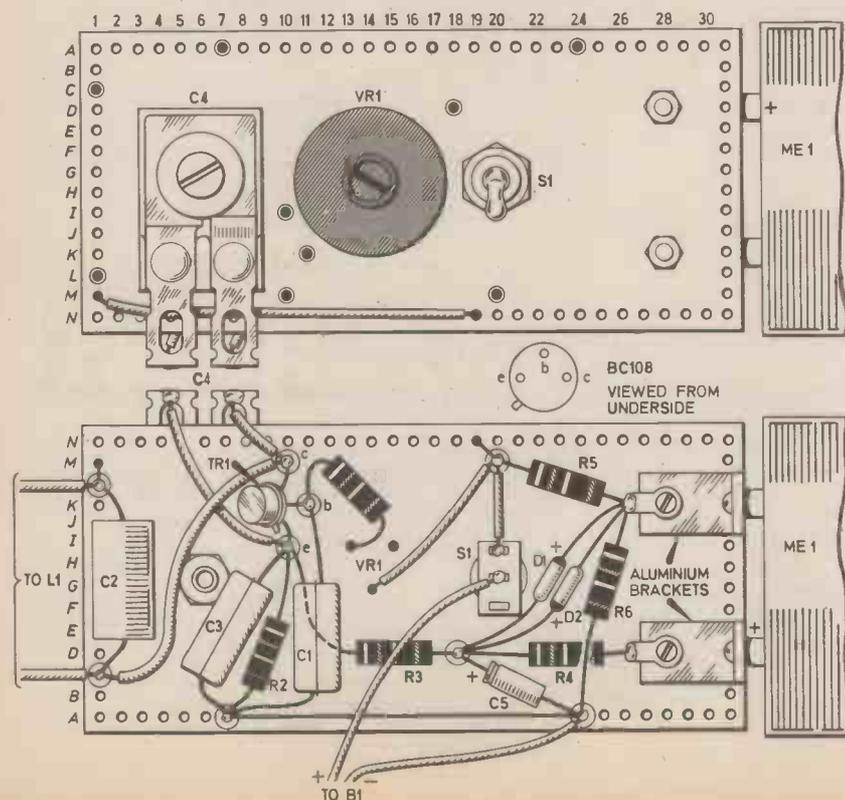


Fig. 3. Top and underside views of the circuit board and meter assembly. The circled connections represent the terminal pins used in the construction of this item. These pins are clearly indicated in the top diagram.

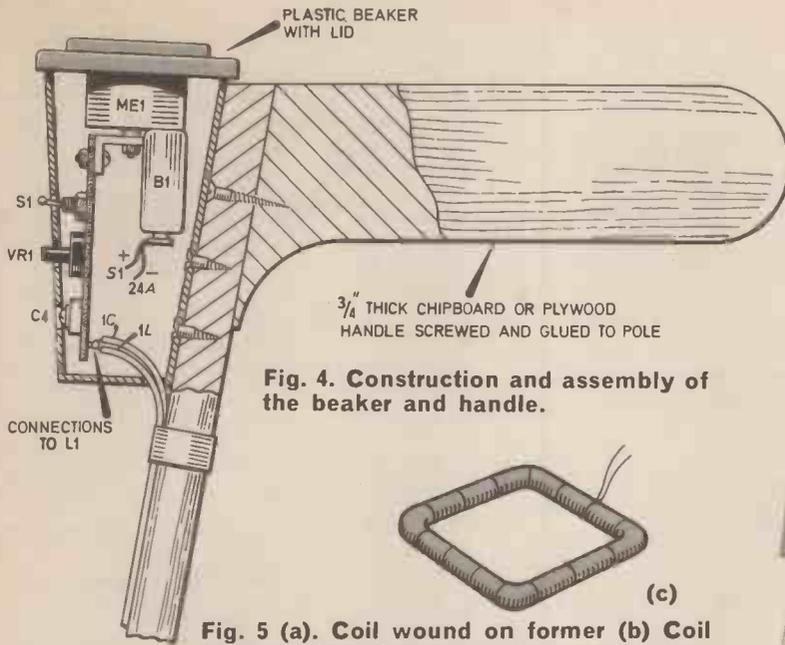


Fig. 4. Construction and assembly of the beaker and handle.


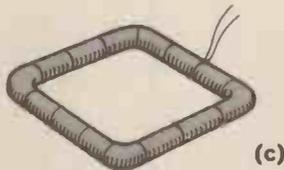
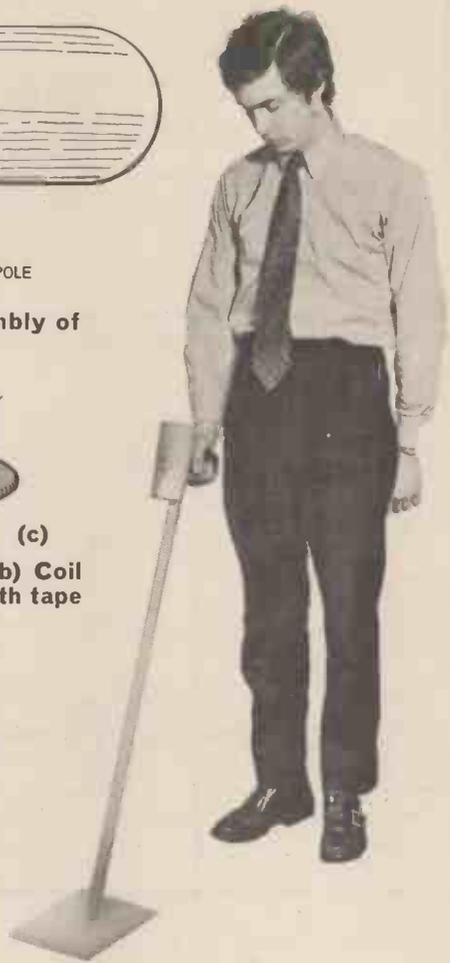
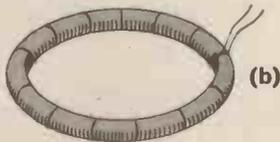


Fig. 5 (a). Coil wound on former (b) Coil removed from former and bound with tape (c) Shaped coil.

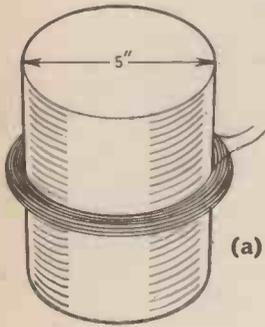

METAL LOCATOR


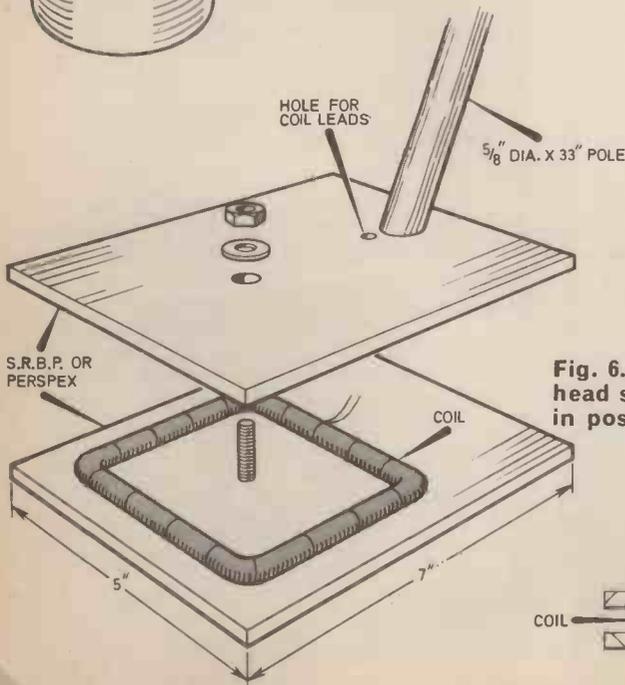


Fig. 6. Construction of the locator head showing how the coil is held in position.

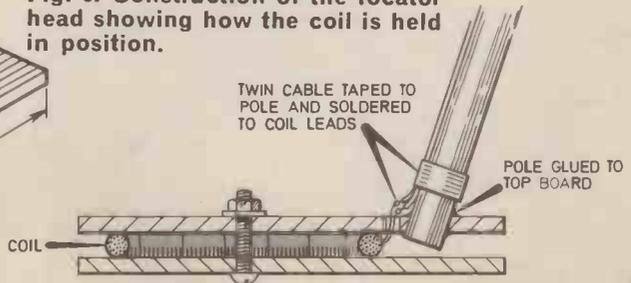

Components

Resistors

- R1 100k Ω
- R2 1.2k Ω
- R3 470 Ω
- R4 470 Ω
- R5 1k Ω
- R6 1k Ω
- All $\pm 10\%$ $\frac{1}{2}$ watt carbon.

SEE
**SHOP
TALK**

Capacitors

- C1 0.22 μ F polyester 250V
- C2 5,600pF polystyrene
- C3 0.22 μ F polyester 250V
- C4 500pF mica compression trimmer
- C5 1 μ F elect. 12V

Semiconductors

- TR1 BC108 silicon npn
- D1 OA81
- D2 OA81

Meter

- ME1 50 μ A f.s.d. moving coil. SEW type MR 38P

Switch

- S1 S.P.S.T. sub-miniature toggle


Miscellaneous

- VR1 10k Ω miniature carbon T.V. type preset
- B1 PP3 battery. Circuit board 3.1 inch by 1.4 inch plain, perforated 0.1 inch matrix Veroboard and Veropins. 26 s.w.g. cotton covered or enamelled copper wire, plastic beaker (see text), connecting wire, wood and screws for assembly, $\frac{1}{2}$ in aluminium angle for brackets.

USE

The locator is now ready for use and can be used for beachcombing or searching the back garden or waste ground. The locator may be subjected to damp and the pole, in particular, should be painted for protection if nothing else. ▣

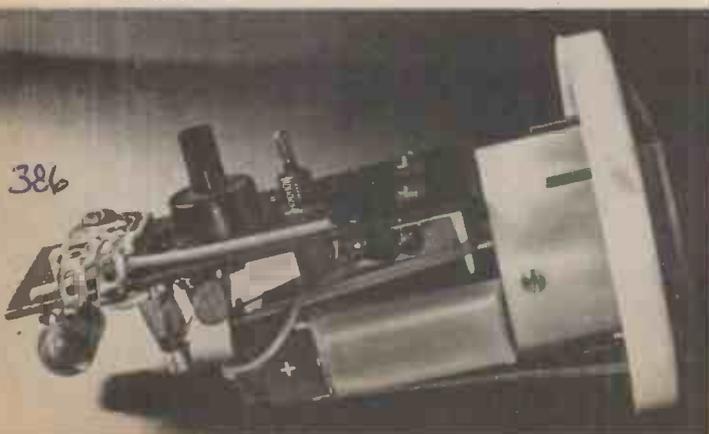Photograph showing the construction of the circuit board and meter mounted on the beaker lid.



Continued from page 361

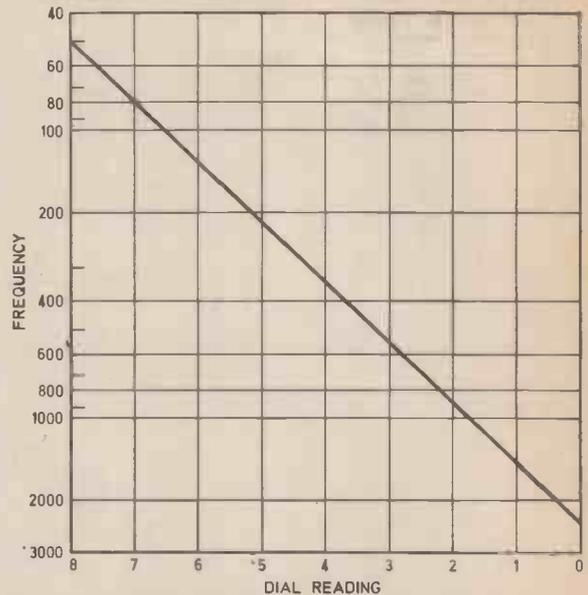


Fig. 8. Approximate output frequency for various control settings.

FINAL ASSEMBLY

Final assembly amounts to attaching the front panel to the box frame with self tapping screws, fitting the battery inside and fitting rear panel.

The generator can be connected to the input of any amplifier but the signal output level should be adjusted in accordance with that required by the amplifier input. To comply with the calibration chart given in Fig. 8 turn VR1 fully anti-clockwise and fix the frequency control knob to read zero. The output control knob is fixed in the same way i.e., to read zero with VR2 fully anti-clockwise.

The Audio Tone Generator is now ready for use and can be tried out in conjunction with a tape recorder. ▣



**BRAND NEW
GUARANTEED**

**LARGEST SELECTION OF SEMICONDUCTORS
COMPONENTS**

**RETURN OF POST
SERVICE**

TRANSISTORS

2G301	20p	2N3404	32p	40310	45p	BC121L	13p	BSX28	32p	NKT281	27p
2G302	20p	2N3405	45p	40311	45p	BCY30	27p	BSX60	82p	NKT401	87p
2G303	20p	2N3414	22p	40312	47p	BCY31	30p	BSX61	82p	NKT402	90p
2G306	42p	2N3415	22p	40314	37p	BCY32	50p	BSX76	22p	NKT403	75p
2G308	30p	2N3416	37p	40315	45p	BCY33	25p	BSX77	22p	NKT404	62p
2G309	30p	2N3417	37p	40323	32p	BCY34	30p	BSX78	27p	NKT405	75p
2G371	15p	2N3470	11.25	40324	47p	BCY38	40p	BSY10	27p	NKT406	62p
2G374	20p	2N3572	97p	40326	30p	BCY39	60p	BSY11	27p	NKT451	62p
2G381	22p	2N3605	27p	40329	30p	BCY40	50p	BSY24	15p	NKT452	62p
2N404	22p	2N3606	27p	40344	27p	BCY42	15p	BSY25	15p	NKT453	47p
2N406	20p	2N3607	22p	40347	47p	BCY43	15p	BSY26	17p	NKT454	32p
2N487	17p	2N3702	11p	40348	55p	BCY54	32p	BSY27	17p	NKT455	32p
2N494	25p	2N3703	10p	40360	42p	BCY58	22p	BSY28	17p	NKT474	30p
2N706	12p	2N3704	11p	40361	47p	BCY59	22p	BSY29	17p	NKT477	30p
2N705A	12p	2N3705	10p	40362	50p	BCY60	87p	BSY32	25p	NKT4713	25p
2N708	15p	2N3706	09p	40370	32p	BCY70	20p	BSY36	25p	NKT781	30p
2N709	62p	2N3707	11p	40406	57p	BCY71	25p	BSY37	25p	NKT10419	30p
2N716	25p	2N3708	07p	40407	40p	BCY72	17p	BSY38	22p	NKT10439	37p
2N726	30p	2N3709	09p	40408	52p	BCZ10	27p	BSY39	22p	NKT10519	37p
2N727	30p	2N3710	09p	40410	62p	BCZ11	42p	BSY40	32p	NKT10519	37p
2N914	17p	2N3711	12p	40467A	57p	BD116	11.12	BSY51	32p	NKT20329	47p
2N916	17p	2N3715	11.25	40468A	55p	BD121	65p	BSY52	32p	NKT20334	47p
2N918	30p	2N3716	11.30	40690	57p	BD123	82p	BSY53	37p	NKT20334	47p
2N929	22p	2N3791	22.06	AC107	12p	BD124	60p	BSY54	40p	NKT20334	47p
2N930	27p	2N3812	25p	AC109	31p	BD125	75p	BSY55	30p	NKT20334	47p
2N1090	22p	2N3823	97p	AC127	25p	BD132	85p	BSY78	47p	NKT80111	37p
2N1091	22p	2N3864	27p	AC128	20p	BDY10	11.37	BSY79	45p	NKT80112	87p
2N1131	25p	2N3854A	27p	AC154	22p	BDY11	11.62	BSY82	52p	NKT80113	87p
2N1132	25p	2N3855	27p	AC176	25p	BDY17	11.50	BSY90	57p	NKT80212	92p
2N1302	17p	2N3856A	30p	AC187	62p	BDY18	11.75	BSY96A	12p	NKT80213	92p
2N1303	17p	2N3857	30p	AC188	35p	BDY19	11.97	BSY97	12p	NKT80214	92p
2N1304	22p	2N3856A	35p	ACY17	27p	BDY20	11.12	BSW70	27p	NKT80215	92p
2N1305	22p	2N3858	25p	ACY18	25p	BDY38	97p	C111	75p	NKT80216	92p
2N1306	25p	2N3858A	20p	ACY19	25p	BDY60	11.25	C424	27p	NKT80213	92p
2N1307	25p	2N3859	27p	ACY20	25p	BDY61	11.25	C425	55p	NKT80214	92p
2N1308	30p	2N3859A	32p	ACY21	20p	BE162	11.00	C426	40p	NKT80215	92p
2N1309	30p	2N3860	30p	ACY22	20p	BF115	25p	C428	37p	NKT80216	92p
2N1310	17p	2N3862	11.50	ACY28	20p	BF117	47p	C614	30p	NKT80216	92p
2N1613	25p	2N3877	40p	ACY40	20p	BF163	37p	D16P1	37p	NKT80216	92p
2N1631	35p	2N3877A	40p	ACY41	25p	BF167	18p	D16P2	40p	NKT80216	92p
2N1632	30p	2N3900	37p	ACY44	40p	BF173	18p	D16P3	37p	NKT80216	92p
2N1638	27p	2N3900A	40p	AD140	52p	BF177	30p	D16P4	40p	NKT80216	92p
2N1639	27p	2N3901	97p	AD149	57p	BF178	30p	GE102	30p	NKT80216	92p
2N1716	25p	2N3902	30p	AD150	92p	BF179	30p	GE103	30p	NKT80216	92p
2N1717	25p	2N3904	35p	AD161	37p	BF180	35p	GE114	20p	NKT80216	92p
2N1889	32p	2N3905	37p	AD162	37p	BF181	32p	GE118	20p	NKT80216	92p
2N1893	37p	2N3906	37p	AF106	42p	BF184	25p	GE119	20p	NKT80216	92p
2N2147	82p	2N4058	17p	AF114	25p	BF185	42p	GE120	52p	NKT80216	92p
2N2148	57p	2N4069	10p	AF115	25p	BF194	17p	GE128	27p	NKT80216	92p
2N2160	57p	2N4060	12p	AF116	25p	BF195	15p	GE180	30p	NKT80216	92p
2N2190	40p	2N4061	12p	AF117	25p	BF196	42p	GE182	92p	NKT80216	92p
2N2193A	42p	2N4062	12p	AF118	62p	BF197	42p	GE189	22p	NKT80216	92p
2N2194A	30p	2N4244	47p	AF119	20p	BF198	42p	GE189	22p	NKT80216	92p
2N2217	27p	2N4285	17p	AF124	22p	BP200	52p	GE196	22p	NKT80216	92p
2N2218	23p	2N4286	17p	AF125	20p	BP224	14p	GE197	22p	NKT80216	92p
2N2219	23p	2N4287	17p	AF126	20p	BP225	18p	GE198	22p	NKT80216	92p
2N2220	25p	2N4288	17p	AF127	17p	BP227	17p	MJ400	11.07A	NKT80216	92p
2N2221	25p	2N4289	17p	AF139	37p	BP238	23p	MJ420	11.12	NKT80216	92p
2N2222	30p	2N4290	17p	AF178	42p	BP244	23p	MJ421	11.12	NKT80216	92p
2N2270	47p	2N4291	17p	AF179	72p	BPW61	47p	MJ430	11.02	NKT80216	92p
2N2297	30p	2N4292	12p	AF180	52p	BPX12	22p	MJ440	95p	NKT80216	92p
2N2368	17p	2N4303	47p	AF181	42p	BPX13	22p	MJ480	97p	NKT80216	92p
2N2369	17p	2N5027	52p	AF198	42p	BPX29	30p	MJ481	11.25	NKT80216	92p
2N2369A	17p	2N5028	52p	AF199	42p	BPX30	30p	MJ490	90p	NKT80216	92p
2N2410	42p	2N5029	47p	AF280	62p	BPX42	37p	MJ491	11.37	NKT80216	92p
2N2483	37p	2N5030	42p	AF211	35p	BPX44	37p	MJ180	12.17	NKT80216	92p
2N2484	32p	2N5172	12p	ASY26	25p	BPX68	87p	MJE340	82p	NKT80216	92p
2N5539	22p	2N5174	52p	ASY27	37p	BPX84	25p	MJE520	60p	NKT80216	92p
2N5540	22p	2N5175	52p	ASY28	27p	BPX85	32p	MJE521	73p	NKT80216	92p
2N5541	35p	2N5176	52p	ASY29	27p	BPX86	25p	MJE522	73p	NKT80216	92p
2N5614	30p	2N5232A	30p	ASY35	25p	BPX87	27p	MPF103	37p	NKT80216	92p
2N5646	52p	2N5245	45p	ASY36	25p	BPX88	25p	MPF104	37p	NKT80216	92p
2N5696	38p	2N5246	42p	ASY51	32p	BPX89	62p	MPF105	37p	NKT80216	92p
2N7211	25p	2N5249	67p	ASY54	25p	BPX93A	70p	MPS3638	32p	NKT80216	92p
2N7212	25p	2N5265	23.25	ASY68	32p	BFY10	32p	NKT0013	47p	NKT80216	92p
2N7213	27p	2N5266	22.75	AU103	11.25	BFY11	43p	NKT124	42p	NKT80216	92p
2N7214	30p	2N5267	22.02	ASZ21	42p	BFY17	22p	NKT125	27p	NKT80216	92p
2N2865	62p	2N5305	37p	BC107	10p	BFY18	32p	NKT126	27p	NKT80216	92p
2N2904	30p	2N5306	40p	BC108	10p	BFY19	32p	NKT128	27p	NKT80216	92p
2N2904A	32p	2N5307	37p	BC109	10p	BFY20	11.60	NKT135	27p	NKT80216	92p
2N2905	37p	2N5308	37p	BC113	15p	BFY21	42p	NKT137	32p	NKT80216	92p
2N2905A	40p	2N5309	62p	BC115	15p	BFY24	45p	NKT139	30p	NKT80216	92p
2N2906	25p	2N5310	42p	BC116A	15p	BFY25	25p	NKT211	30p	NKT80216	92p
2N2906A	27p	2N5354	27p	BC118	10p	BFY26	20p	NKT212	30p	NKT80216	92p
2N2907	30p	2N5355	27p	BC121	20p	BFY29	50p	NKT213	30p	NKT80216	92p
2N2923	15p	2N5356	32p	BC122	20p	BFY30	50p	NKT214	22p	NKT80216	92p
2N2924	15p	2N5357	32p	BC123	20p	BFY41	50p	NKT215	22p	NKT80216	92p
2N2925	15p	2N5368	35p	BC126	20p	BFY43	62p	NKT216	22p	NKT80216	92p
2N2926	15p	2N5369	35p	BC127	20p	BFY45	23p	NKT217	42p	NKT80216	92p
Green	14p	2N5457	37p	BC140	37p	BFY50	20p	NKT219	30p	NKT80216	92p
Yellow	12p	2N6005	75p	BC147	10p	BFY52	23p	NKT223	87p	NKT80216	92p
Orange	12p	2N6020	82.00	BC149	12p	BFY53	17p	NKT224	25p	NKT80216	92p
2N3011	32p	2N6122	50p	BC152	17p	BFY66A	57p	NKT225	22p	NKT80216	92p
2N3012	32p	2N6103	27p	BC153	17p	BFY76	30p	NKT226	27p	NKT80216	92p
2N3053	18p	2N6104	25p	BC158	11p	BFY76	42p	NKT237	35p	NKT80216	92p
2N3054	46p	2N6101	32p	BC159	12p	BFY77	57p	NKT238	35p	NKT80216	92p
2N3055	62p	2N6102	35p	BC160	62p	BFY90	67p	NKT240	27p	NKT80216	92p
2N3133	30p	2N6103	27p	BC167	11p	BFY68	27p	NKT241	27p	NKT80216	92p
2N3134	30p	2N6104	27p	BC168B	10p	BFY69	25p	NKT242	27p	NKT80216	92p
2N3135	25p	2N6105	70p	BC169	11p	BFY70	25p	NKT243	27p	NKT80216	92p
2N3136	25p	2N6140	77p	BC169B	11p	BPX25	11.85	NKT244	17p	NKT80216	92p
2N3390	25p	2N141	72p	BC169C	12p	BPX29	11.80	NKT245	20p	NKT80216	92p
2N3391	20p	2N142	55p	BC170	12p	BPY10	11.45	NKT261	20p	NKT80216	92p
2N3391A	30p	2N143	87p	BC171	15p	BRY39	37p	NKT262	30p	NKT80216	92p
2N3392	17p	2N152	87p	BC172	15p	BRX19	17p</				

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book, B.I.E.T. has successfully trained *thousands* of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast—makes learning easier and something you look forward to. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths,
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.
C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero
A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.
WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

Free! Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY Dept B31, Aldermaston Court, Reading RG7 4PF

POST THIS COUPON NOW

To: B.I.E.T. Dept. B31 Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age
BLOCK CAPITALS PLEASE

Address

Accredited by the Council for the Accreditation of Correspondence Colleges.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



B.H. COMPONENT FACTORS LTD.

For Eagle, Sinclair, Data Books and Components—
1w 5% resistors 1p, or 50p/100. Electrolytic C426 4/40,
3/40, 10/18, 32/10, 25/25, 100/6.4, all 4p. IN914 6p, 100v
1A Bridge 50p. Panel neon 15p. Mains Transformers
32-0-32 @ 150 mA 50p, 150v @ 250mA and 8v @ 650mA
75p. Electrolytic 100/50 10p, 500/50 12p, 1000/12 12p.
1000/25 25p, 1000/50 35p. UL914 30p, 7400/01/10/30 15p.
Free list, C.W.O. p.p. U.K. 10p. Discount £10-10%.
Money back guarantee. Brand new to spec.

P.O. BOX 18, LUTON, BEDS, LU1 1SU

NEW

15 watt Hi-Fi AMPLIFIERS
£3.75 plus 25p postage & packing

7 TRANSISTORS - GUARANTEED PRINTED CIRCUIT - TESTED DESIGN BUILT - INSTRUCTIONS

A great new 15 watt HiFi amplifier is now available at the low cost of £3.75. Just look at the specification—Power 15 Watts E.M.S., frequency response 15-cs 19000 cs. Signal to noise ratio better than 70 db, Harmonic distortion 0.1%, Input sensitivity 760mv into 2k. These factors make the H Electronics HiFi amplifier the best at its price—order now.

H ELECTRONICS.
105, Grange Road, London . S.E.25

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 36 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

709C OPERATIONAL AMPLIFIER TO5
8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS 62p
‡ and † watt.

150 MIXED HI STABS 62p
‡, † and 1 watt 5% and better.

QUARTZ HALOGEN BULBS
With long leads. 12V 55W for car spot lights, projectors, etc. 50p each, P. & P. 5p.

GPO EXTENSION TELEPHONES
with dial but without bell. 95p each, P. & P. 30p, £1.75 for 2, P. & P. 50p.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 50V. 2.5k Ω coil. 8 for 50p, P. & P. 5p.


KEYTRONICS mail order only

44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

TEACH-IN

Half term test

ANSWERS

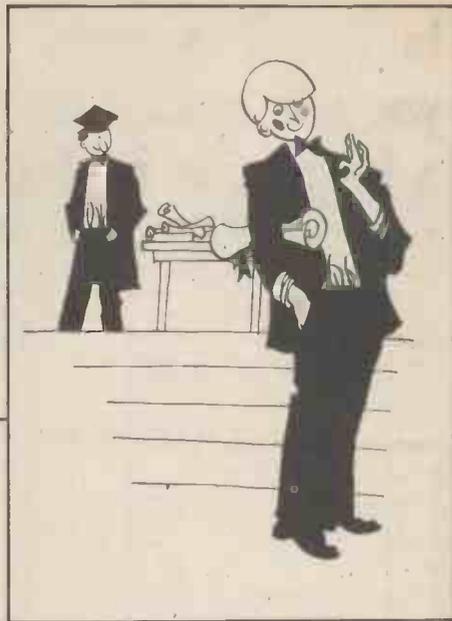

Last month we posed some problems under the heading *Teach in Half-Term Test*. We will now answer those problems and try to show how we arrived at the answers. If you have got some of them wrong do not worry, just try and follow our explanation and see where you went wrong.

(1) They flow from negative to positive in reality. Although we assume that conventional current flows from positive to negative the actual electrons flow from negative to positive.

(2) (b) μA (microamps), (e) A (amps)

(3) 22 volts. $V = IR$ hence $V = 0.01 \times 2.2 \times 1,000 = 22\text{V}$

(4) It does not matter. All the resistor does is to limit the current; this can be done at any point around the circuit.

(5) 2.8mA. Total resistance is $2.2\text{k}\Omega + 1\text{k}\Omega = 3.2\text{k}\Omega$.

$$\text{Current flow } I = \frac{V}{R} = \frac{9}{3.2 \times 1,000} = 2.8 \div 1,000 \text{A} = 2.8\text{mA}$$

(6) R1 and R3 $\frac{1}{2}\text{W}$, R2 1W. Total circuit resistance

$$R_T = R_1 + \frac{R_2 \times R_3}{R_2 + R_3} = 10 + 33.3 = 43.3\Omega.$$

$$\text{Total current } I = \frac{V}{R} = \frac{9}{43.3} = 0.21\text{A}$$

Dissipation of R1 = $I^2R = 0.21 \times 0.21 \times 10 = 0.44\text{W}$. The nearest commercial rating is $\frac{1}{2}\text{W}$. Next calculate the voltage drop across R2 and R3 together $V = IR = 0.21 \times 33.3 = 7\text{V}$.

We know that $W = I^2R$, but $I = \frac{V}{R}$ therefore

$$W = \frac{V}{R} \times \frac{V}{R} \times R \text{ and, cancelling } W = \frac{V^2}{R}$$

$$\text{Dissipation in R2} = \frac{V^2}{R} = \frac{7 \times 7}{50} = \frac{49}{50} = 0.98\text{W}$$

$$\text{Dissipation in R3} = \frac{V^2}{R} = \frac{49}{100} = 0.49\text{W}$$

(7) 0.4W or 400mW. Maximum dissipation occurs when the value of VR1 equals that of R1 i.e. 50Ω . When both resistors are of equal value the voltage drop across each is half the voltage drop across both, therefore, maximum dissipation in VR1

$$= \frac{V^2}{R} = \frac{4.5 \times 4.5}{50} = \frac{20.25}{50} = 0.405\text{W}$$

(8) (a) $4.7\text{k}\Omega \pm 10\%$

(b) $22\text{k}\Omega \pm 5\%$

(c) $100\text{k}\Omega \pm 10\%$

(9) (b) $20\mu\text{F}$ 40V. In most applications using electrolytic capacitors the capacitance must be greater than a certain value; the tolerance of a normal $16\mu\text{F}$ would encompass $20\mu\text{F}$. The important thing is that the working voltage is the same or greater.

(10) Reject it politely. He has given you a $120,000\text{pF}$ or $0.12\mu\text{F}$ capacitor. Check to see if he has the precise value and, if he does not, you may as well take this one, since it should be near enough to use as a substitute.

(11) C1 will charge up the fastest as it has the lowest value and is being charged through the lowest value resistor.

(12) C2 will take the longest time to charge, as it has the highest value and is being charged through the highest value resistor.

(13) Forward biased. The conventional current flows from positive to negative and can thus flow through the diode in the direction of the arrow.

(14) 100V and 100mA. Peak reverse breakdown voltage will be the battery voltage. Since in the reversed biased condition there is negligible current flowing R1 will not drop any voltage and the full supply voltage will appear across D1. In the forward biased condition the diode can be assumed to be a short circuit thus only R1 can limit the current flowing hence

$$I = \frac{V}{R} = \frac{100}{1 \times 1,000} = 0.1\text{A or } 100\text{mA}$$

(15) (d) 100V, 150mA. Both ratings given are minimum ratings, $0.1\text{A} = 100\text{mA}$.

(16) (b) 0.6V. As the diode is forward biased the voltage would be 0.6V. There is always a voltage drop of approximately 600mV across silicon diodes due to the "knee" in the characteristic.

Well, how did you fare? If you got them all right that is excellent, if you did not the important thing is that you understand where you had difficulties. We suggest that you re-read the relevant sections of the *Teach-In* series.

We hope that you found the questions a challenge and at the same time they have opened your eyes to some calculation methods—particularly the calculation of dissipation. If you used $W = I^2R$ instead of deriving $W = \frac{V^2}{R}$ this does not matter but it may pay to look for an easier way next time.

REMEMBER
TO USE THE
POSTCODE



Readers Letters

Bias Value

Having been a subscriber to P.E. and P.W. "off and on" for about 10 years I came across the January issue of EVERYDAY ELECTRONICS, which had my instant approval and now joins the rank of my other magazine's culminating in an endless and very informative pile on top the piano.

I find it is a magazine not only of theoretical enthusiasm but of great practical interest to the "everyday handyman" and certain to be a book for beginners, especially the very helpful facts "projected" by Mike Hughes, M.A.

I would hope in the future that perhaps Mr. Hughes could give reference to finding values of bias resistors, etc., needed for the satisfactory operation of different transistor parameters, and also relevant circuit operation of thyristors, unijunction and field effect transistors and other very useful flexible types of semiconductors.

Noticing other readers' troubles referring to the *Electro Laugh*, I also constructed this article and it worked first time owing to the way I adopt when working on, or constructing any project, I always check the finished article with the actual circuit diagram thus finding our little friend Q7 and P7.

Unfortunately the only earphone I had was a high impedance crystal type, but by connecting a resistor in the region of 250 ohms in parallel with it, it brought the overall impedance down to a satisfactory level with a slight reduction in volume.

J. Mason
S. Wales

We doubt if Teach-In will be able to meet all your needs as it will finish after 12 months. However we will be publishing further series that should help.

Another Bug

Naturally, I was quite flattered to discover that you had found my letter sufficiently interesting for inclusion in *Readers Letters* (March issue), however, I must admit that my pleasure was mixed with large helpings of disappointment and frustration due to your editing of the letter.

I am not complaining at all about the amount of space allocated to my comments—I realise you have the right to include only that which in your wisdom you decide is worthy of publication.

My complaint is that you have entirely neglected to make even a brief reference to what was after all the main point of my letter—the difficulty of obtaining items advertised in your magazine. By omitting any reference to this frustrating situation, my letter as printed is sailing under false colours—the few minor constructional queries were in fact, sorted out by trial and error once I got going. The real reason for being unable to get cracking was not so much mounting components, as actually getting hold of them!

The fact that you completely ignored my comments regarding suppliers leads me to two conclusions:

(One) That you accepted my comments to be an exaggeration of a somewhat hysterical nature, and were not a true picture of the real situation, or

(Two) That you accepted my statements as correct, but did not wish to offend your advertisers whose business you must obviously wish to retain.

With regard to the former, I feel I must now justify my remarks by quoting a few of the more deplorable examples of SERVICE, and leave you to form your own conclusions. These examples are on a separate sheet herewith enclosed.

Regarding (Two), whilst I

realise that you are not to be held responsible for goods or services advertised in your columns, you do, however, have a moral responsibility to your readers. After all, it is you that place these offers before us, the readers, and if for example, I had not seen a certain item offered in your magazine, then I would have been saved the trouble and frustration that followed when the item failed to arrive, and all attempts to obtain satisfaction are largely ignored.

However, I have now found a couple of very good suppliers whose friendly, courteous, and extremely efficient service have allowed me to obtain some of the pleasure that I had hoped would be derived from my new hobby (Galleon Trading Co. and Radio Exchange Co.).

To date I have completed several very efficient radios, some from kits; also the *Astron*, a general purpose amplifier, and one or two other gadgets, and success rate so far is quite satisfactory, so the situation is not too black after all.

J. G. Richards
Sale, Cheshire

The above correspondent supplied us with details of orders placed with four different advertisers, none of which had been expediently dealt with, at the time of writing.

We have investigated all of these cases on behalf of our reader. The delays, regrettable as they are, seem to be unavoidable and can be largely attributed to the phenomenal success of this magazine's declared intention to popularise the hobby of electronics!

As a consequence, our advertisers are sometimes overwhelmed by a flood of orders, and delays do therefore sometimes arise. But we know all our advertisers make determined efforts to clear their back-log of orders as quickly as possible.

We, on our part, will always investigate any serious and reasonable complaints, on behalf of our readers.

Cell Life

I have just read the March issue of EVERYDAY ELECTRONICS and thoroughly appreciated the *Ruminations* by Sensor where he mentioned the tin saw and how much damage could result to a

MULTI-SPEED MOTOR

81x speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 & 15,500 r.p.m. shaft is 1/2 in. diameter 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 88p plus 23p postage and insurance.



RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckon your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprise: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 88p, plus 20p postage.

MICRO SWITCH

5 amp. changeover contacts, 9p each. 1/2 doz. 15 amp. Model 10p each or £1-05 doz.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2 plus 38p post and ins.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



THERMOSTAT

Continuously variable 30°-90° C. Has sensor bulb connected by 33in. of flexible tubing. On operation a 15 amp 250 volt switch is opened and in addition a plunger moves through approx 1/2 in. This could be used to open valve on ventilator etc. £1-50 plus 23p p. & ins.



5A 3-PIN SWITCHED SOCKETS

An excellent opportunity to make that bench dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Heraft) bakelite flush mounting shuttered switch sockets for only 50p plus 18p post and insurance. (20 boxes post free).




MAINS OPERATED SOLENOIDS

Model 778—small but powerful 1" pull—approx. size 1 1/2" x 1 1/2" x 1 1/2". 60p. Model 400/1 1/2" pull. Size 2 1/2" x 2 1/2" x 2 1/2". 75p. Model TT10 1 1/2" pull. Size 3" x 2 1/2" x 2 1/2". £1-80 plus 20p post and insurance.




TELESCOPIC AERIAL

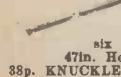for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 38p. KNUCKLED MODEL FOR P.M. 50p.



3 STAGE PERMEABILITY TUNER

This Tuner is precision instrument made by the famous 'Clydon' Company for the equally famous Radiomobile Car Radio. It is a medium wave tuner (but set of longwave coils available 25p) with a frequency coverage 1820 Kc/s to 900 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2" x 2 1/2" x 1 1/2") with reduction gear for fine tuning. Snip price this month 50p, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post free.

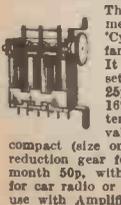

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient. We offer kit of parts as P.W. circuit £5 95 plus 20p p. & p. De-luxer model with prepared circuit board £8-95. When ordering please state whether for positive or negative systems.

ELECTRONIC IGNITION

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £3—twin set instead of earpiece 75p extra post and ins. 20p.



STANDARD WAFER SWITCHES

Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 1/2" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	70p	70p						
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1-20	£1-20
5 poles	40p	40p	70p	70p	95p	95p	95p	£1-45	£1-45
6 poles	40p	70p	70p	70p	95p	95p	95p	£1-70	£1-70
7 poles	70p	70p	70p	95p	£1-20	£1-20	£1-20	£1-95	£1-95
8 poles	70p	70p	70p	95p	£1-20	£1-20	£1-20	£2-20	£2-20
9 poles	70p	70p	95p	95p	£1-45	£1-45	£1-45	£2-45	£2-45
10 poles	70p	70p	95p	£1-20	£1-45	£1-45	£1-45	£2-70	£2-70
11 poles	70p	95p	95p	£1-20	£1-70	£1-70	£1-70	£2-95	£2-95
12 poles	70p	95p	95p	£1-20	£1-70	£1-70	£1-70	£3-20	£3-20

THYRISTOR LIGHT DIMMER

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £1-99 plus 20p post and insurance.



THIS MONTHS SNIP



1 HOUR MINUTE TIMER. Made by Smiths complete with control knob and calibrated dial. This month's special bargain at 50p. Useful in the Kitchen, Office and Dark-room etc.

MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohms speakers. Input suitable for crystal mic. or pick-up. 9 volt battery operated. Size 2" long x 1 1/2" wide x 1" high. SPECIAL SNIP PRICE 60p each. 10 for £5.



POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car electric. Test polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied), 80p or 2 for 50p. Post paid.



METAL LOCATOR AUDIO TONE GENERATOR BEE COUNTER

To receive details on these kits send s.a.c. for parts list.

MULLARD I.F. MODULE

This is a fully screened intermediate frequency module for amplification and detection of I.m. signals at 10-7MHz and a.m. signals at 470KHz. The first stage is used as an i.f. amplifier for I.m. and a self oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 75p each. 10 for £6-75. 100 for £62-50. With connection dia.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2-25 plus 23p P. & I



BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace" "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £1-75 plus 20p postage.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

Thermostat with Probe. Made by the famous Ranco Thermostat Co. Covers the range from approx. 0°-200°C. variable by a control spindle, handles currents up to 16 amps. Length of capillary and sensor tube approx. 3' 6". These are ideal for ovens and as a general purpose thermostat. Price 50p each or 10 for £4-50. Small Tunix Condenser as fitted to many imported Japanese and Hong Kong radios. 2" x 2" about 200PF per gang. Size approx. 1" x 1" with a 1/2" diameter spindle with dust cover. 25p each or 10 for £2-25.

Heat Sink. Small type as used with OC81 etc. Price 6p each or 10 for 49p. Spectacle Frames. (No lenses) with built-in hearing aids. The amplifier and battery being housed in the arms. Although these are complete hearing aids we are selling them purely for the sub miniature components they contain. We give 30 guarantee that they are in working order also these may be secondhand. Price £2-50 each. Foot Switch. Twin levers each of which operates a 10 amp QMB changeover switch. Price 90p each. Programmers. 5 Revs per minute. Made by Magnetic Devices Ltd. The contacts may be set to trigger anywhere around the shaft. Ideal for motivated lighting displays, sequential switching etc. Drive motors are 800/1400/50Hz. Model A has 5 change over contacts. Price £1-50. Model B has 11 change over contacts. Price £3.

Radiant Cooker Bings. As fitted to Tricity and many other popular cookers. We have two types. These are copper clad 1/2" tubular construction. Both models having an external diameter of 6 1/2" and the elements have been slightly flattened to increase radiation. Backer Model 7D1 MHIH again 2000 watts rated but 230-240v, has no cover over element ends. Price 65p each or 10 for £2-85. Slide Switch. 2 pole change over panel mounting by two 6 BA screws. Size approx. 1" x 1/2" rated 250v lamp. 6p each. 10 for £5-10. 100 for £5-10. 500 for £24.

As above but for printed circuit 5p each, 10 for 45p, 100 for £4-25. Sub Miniature Slide Switch. DPDT 19mm (1/2" approx.) between fixing centres. 12p each or 10 for £1-08.



KITS FOR PREVIOUS PROJECTS

Unless otherwise stated, kits contain electronic parts only. The case and special items can be obtained locally. Also batteries are not included. Kits may be returned for refund if construction has not been started. We reserve the right to substitute components should deliveries be protracted so as to avoid undue delay.

HOME SENTINEL INTRUDER ALARM Electronic Components with suitable case £3-75

SNAP INDICATOR 75p

WINDSCREEN WIPER CONTROL Components including metal for chassis £2

RECORD FLAYER. All components, but not case, loudspeaker, record deck or pick-up £5-50

DEMO DECK £6-75 POST PAID

FUZZ BOX £1-85

PHOTOGRAPHIC COLOUR TEMPERATURE METER £2-85

ASTRON RADIO £3

REMOTE TEMPERATURE COMPARATOR £4-25

ELECTRO LAUGH £2

TRANSISTOR MICROPHONE £1-70

AUTO ALERT All electronic parts and metal bracket £2-50

BATH WARNING ALARM All electronic parts and chassis £1-80

WA-WA PEDAL £2-90

DARKROOM TIMER £4-50

SIGNAL INJECTOR 50p

SOIL MOISTURE METER £3-00

SIMPLE CALCULATOR £2-20

D.C. POWER SUPPLY £5-00

BABY ALARM £4-00

Mains Transformer. Primary 240v, tapped 220v. Secondary 20v. ± amp. Price 60p each or 10 for £5-40.

Dial Thermometer—reading from 200-525F used on Tricity and other cookers. This has a fuse and can be mounted through a 1 1/2" hole or alternatively it can just be rested on the object whose temperature it is required to measure. Size 2" x 1/2" overall diameter. Depth 1 1/2" below and 1/2" above mounting panel. Price 80p each or 10 for £7-20p.



24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £2 post and ins. 23p. Additional time contacts 50p pair.

J. BULL (ELECTRICAL) LTD.
(Dept. E.E.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

TRANSISTORS

A SELECTION FROM OUR LIST

AA4730	10p	BD115	75p	OC18	50p	2N1303	18p
AA4742	15p	BD123	85p	OC20	85p	2N1304	22p
AAZ13	10p	BD124	80p	OC22	50p	2N1306	22p
A4Z15	10p	BD131	75p	OC23	60p	2N1306	25p
AC127	10p	BD182	80p	OC24	60p	2N1306	25p
AC107	35p	BDY11		OC25	40p	2N1307	25p
AC126	30p		£1.50	OC26	25p	2N1308	25p
AC127	25p	BDY17		OC28	60p	2N1309	25p
AC127Z	50p		£1.50	OC29	60p	2N1613	20p
AC128	20p	BDY38	65p	OC35	50p	2N1477	75p
AC176	20p	BDY60		OC36	60p	2N1610	60p
AC187	25p			OC42	40p	2N2217	25p
AC188	25p			OC43	50p	2N2218	20p
ACY17	30p	BF115	25p	OC44	15p	2N2218A	
ACY18	25p	BF154	20p	OC45	12p		25p
ACY19	25p	BF168	15p	OC70	12p	2N2219	20p
ACY20	25p	BF159	35p	OC71	12p	2N2219A	
ACY21	20p	BF180		OC72	20p		25p
ACY23	10p	BF194	15p	OC75	25p	2N2220	25p
ACY39	65p	BF195	15p	OC76	25p	2N2221	20p
ACY40	20p	BF196	15p	OC77	40p	2N2221A	
ACY41	15p	BF197	15p	OC81	20p		25p
ACY44	25p	BFX13	25p	OC81D	20p	2N2222	20p
AD140	50p	BFX29	25p	OC81Z	40p	2N2222A	
AD149	50p	BFX30	25p	OC82	20p		25p
AD161	35p	BFX84	25p	OC84	25p	2N2369	15p
AD162	35p	BFX85	30p	OC139	25p	2N2369A	
AF114	25p	BFX86	25p	OC140	40p		15p
AF116	25p	BFX87	25p	OC141	60p	2N2644	40p
AF116	25p	BFX88	20p	OC170	25p	2N2904	20p
AF117	20p	BF189	25p	OC71	12p	2N2904A	
AF118	60p	BFY50	20p	OC200	40p		25p
AF124	25p	BFY51	20p	OC201	75p	2N2905	25p
AF125	20p	BFY52	20p	OC202	80p	2N2905A	
AF126	20p	BFY53	18p	OC206	95p		25p
AF127	20p	BFY90	65p	OC271	97p	2N2906	20p
AF139	20p	BSX20	15p	ORF12	50p	2N2906A	
AF180	50p	BFY126	25p	OC71	12p		25p
AF181	45p	BFY27	15p	ST140	15p	2N2907	23p
AF185	50p	BHT95A	12p	ST141	20p	2N2907A	
AF186	40p	BSY95	12p	TIP29A	60p		25p
AF239	40p	BU105	£2.25	TIP30A	60p	2N2925	15p
AS926	25p	BY100	15p	TIP31A	60p	2N2926	10p
AS927	30p	BY126	25p	TIP32A	70p		25p
AS928	25p	BY124	15p	TIP33A	20p	2N3053	20p
AS929	30p	BY182	90p		£1.00	2N3054	50p
ASZ21	50p	BY210	85p	TIP34A	20p	2N3056	75p
BA100	15p	BYZ1	30p		£1.50	2N3252	
BA102	30p	BYZ12	30p	TI843	40p		£1.00
BA110	25p	BYZ13	25p	TI850	12p	2N3614	55p
BA115	7p	BZ7821	10p	TI851	10p	2N3702	10p
BAK13	5p	GET102	35p	TI852	10p	2N3703	10p
BAK16	7p	GET103	25p	TI860	18p	2N3704	12p
BAY31	7p	GET111	45p	TI861	20p	2N3705	10p
BAY38	15p	GET113	25p	TI862	25p	2N3707	12p
BC107	10p	GET114	20p	V406A	25p	2N3708	10p
BC108	10p	GET115	30p	VR25	35p		
BC109	10p	GET116	25p	W01	30p	2N3714	£2.00
BC109C	12p	GET180	45p	W06	45p		£2.00
BC113	10p	GET182	30p	ZTX107	15p		£2.20
BC114	20p	GEX66		ZTX108	12p		£2.30
BC115	20p		£1.50	ZTX109	15p		£2.85
BC116	20p	GM375A	55p	ZTX300	12p		
BC116A	25p	MAT191	25p	ZTX301	15p		£2.00
BC117	20p	MAT191	25p	ZTX302	20p		£2.00
BC118	20p	MCT24F	60p	ZTX303	20p		£2.05
BC119	30p	MJ420	80p	ZTX304	25p		£2.373
BC134	30p	MJ421	80p	ZTX500	15p		£2.35
BC135	15p	MJ2801		ZTX501	15p		£2.791
BC136	20p		£1.10	ZTX502	20p		£2.75
BC137	20p	MJ901		ZTX503	17p		
BC138	20p		£1.50	ZTX504	40p		
BC147	12p	MJE340	50p	ZTX531	26p		
BC148	10p	MJE370	20p	IN914	7p		
BC149	12p	MJE371	80p	IN916	10p		
BC153	20p	MJE375	75p	IN918	7p		
BC154	20p	MJE521	70p	IB44	7p		
BC167	15p	MJ2295		IS921	7p		
BC169	12p		£1.10	IS922	8p		
BC169C	15p	MJE3055		G3001	25p		
BC177	20p		75p	G3002	30p		
BC178	20p	MPSA60	25p	G3003	35p		
BC179	20p	MPSA62	20p	G3004	20p		
BC182L	10p	MPSA70	15p	G2696	15p		
BC183L	10p	MPSU06	50p	G2697	15p		
BC184L	12p	MPSU06	55p	G2698	30p		
BC212L	12p	NK7214	20p	N7608	10p		
BC213L	12p	NK7216	35p	N7609A	12p		
BC214L	15p	NK7403	75p	N7608	12p		
BCY30	30p	NKT404	55p	N7630	20p		
BCY31	40p	OA5	25p	N2987	40p		
BCY32	60p	OA10	25p	N21121	25p		
BCY33	30p	OA47	10p	N21132	25p		
BCY34	35p	OA70	10p	N21302	18p		
BCY35	45p	OA79	10p				
BCY39	40p	OA80	8p				
BCY40	50p	OA91	7p				
BCY70	15p	OA95	7p				
BCY71	20p	OA290	7p				
BCY72	15p	OA292	10p				

Full transistor list available—send for your free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES BRANDED FAIRCHILD, I.T.T. AND TEXAS

DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quad 2-input NAND gates	20p	18p	14p	14p	12p
7401	Quad 2-input NOR gates	20p	18p	14p	14p	12p
7402	Quad 2-input open collector NAND gates	20p	18p	14p	14p	12p
7403	Quad 2-input open collector NOR gates	20p	18p	14p	14p	12p
7404	Hex inverter	20p	18p	14p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	14p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	14p	14p	12p
7413	Dual 4-input Schmitt triggers	20p	18p	14p	14p	12p
7420	Dual 4-input NAND gates	20p	18p	14p	14p	12p
7430	Single 8-input NAND gates	20p	18p	14p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	14p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	72p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7443	Excess 3-Decimal decoder TTL outputs	£1.00	95p	90p	80p	75p
7447	BCD-Decimal 7 seg. decoder/indicator driver	£1.75	£1.45	£1.45	£1.10	£1.15
7448	BCD-Decimal 7 seg. decoder/indicator TTL O/P	£1.75	£1.40	£1.45	£1.30	£1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	14p	14p	12p
7454	4-wide 3-input AND-OR-INVERT gates	20p	18p	14p	14p	12p
7460	Dual 4-input expanders	20p	18p	14p	14p	12p
7470	Single J-K flip-flop (gated inputs)	20p	18p	14p	14p	12p
7472	Single J-K flip-flop (gated inputs)	20p	18p	14p	14p	12p
7473	Dual J-K flip-flop	40p	37p	35p	33p	30p
7474	Dual D flip-flop	40p	37p	35p	33p	30p
7475	Quad 2-input bistable latch	45p	42p	40p	38p	35p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	34p	31p	28p
7480	Gated Full Adder	80p	72p	67p	59p	55p
7481	16-bit read/write memory	£1.25	£1.15	£1.10	£1.00	90p
7482	2-bit binary full adder	80p	75p	70p	65p	60p
7483	4-bit binary Full Adder	£1.00	90p	85p	80p	73p
7484	16-bit RAM with gated write inputs	90p	85p	80p	75p	71p
7486	Quad 2-input Exclusive OR gates	45p	41p	38p	35p	33p
7480	BCD decade counter	75p	70p	65p	60p	55p
7481	8-bit shift register	£1.00	85p	80p	75p	70p
7482	Divide by two counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	80p	75p	70p	65p	60p
7494	Dual 2-line 4-bit shift register	80p	75p	70p	65p	60p
7495	4-bit up-down shift register	80p	75p	70p	65p	60p
7496	5-bit parallel/serial/in/out shift register	£1.00	97p	90p	85p	80p
74100	8-bit bistable latch	£2.50	£2.30	£2.00	£1.75	£1.50
74113	Hextable Set-Reset latches	£1.00	85p	80p	75p	70p
74121	Monostable multivibrators	£1.00	85p	80p	75p	70p
74141	BCD-Decimal decoder/Nixie driver	£1.00	95p	90p	80p	70p
74145	BCD-Decimal decoder (1-4-line) TTL O/P	£1.50	£1.40	£1.30	£1.10	£1.00
74150	16-bit data selector/multiplexer	£3.35	£3.20	£2.95	£2.15	£2.05
74151	8-bit data selector/multiplexer	£1.10	95p	90p	80p	70p
74153	Dual 4-line to 1-line data selector/multiplexer	£1.35	£1.27	£1.20	£1.15	£1.10
74154	16-bit decoder/demultiplexer	£2.00	£1.75	£1.55	£1.30	£1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	£1.55	£1.47	£1.35	£1.10	£1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	£1.55	£1.47	£1.35	£1.10	£1.05
74190	Sync decade up-down counter, 1-line mode	£1.95	£1.85	£1.75	£1.60	£1.50
74191	Sync 4-bit up-down counter, 1-line mode	£1.95	£1.85	£1.75	£1.60	£1.50
74192	Sync decade up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.65	£1.55
74193	Sync 4-bit up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.60	£1.40
74198	Asynchronous presetable decade counter	£1.50	£1.40	£1.30	£1.10	£1.00
74197	Asynchronous presetable 4-bit binary counter	£1.50	£1.40	£1.30	£1.10	£1.00

Complete data on the above in booklet 20 pages, Ref. 29, Issue 2 at 15p post paid.
 Texas I.C. Handbook. Complete information on 100 types. 40p. Post 10p.
 Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

INTEGRATED CIRCUITS

MPC4001F	55p
MPC4010F	60p
LC12	£2.50
PA246	£1.50
TAD100	£1.50
TAD110	£1.50
MCT24F	50p
702C (T05)	75p
709C (T05)	45p
709C (D.I.L.)	45p
723C(T05)	£1.00
741C(T05)	80p
MC1303F	£2.00
MC1304F	£2.25
8L403D	2N5404
741C(D.I.L.)	75p
914(T05)	40p
923(T05)	40p

FLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier 8L403D

Complete with 8-page booklet, circuits and data
£1.50 ea.

ZENER DIODES

1	25	100	500	1000
24	+	+	+	+

400mW

beginner's enthusiasm.

When I read about the *Signal Injector* by Alan Jardine I was reminded of the poor beginner.

Following the instruction to solder the leads direct on to the cell will result in heating up the electrolyte and a very short life for the cell.

Perhaps this is not important as the choice of a push-on/push-off switch allows no easy means of knowing if the thing is on or off. Very few beginners will remember to test each time, and cell life will be short it is expected. A push button perhaps?

The blind cannot be expected to lead the blind, and beginners are usually short of experience.

R. Quorn
Sussex

Of your two points concerning the Signal Injector, the first is a bit exaggerated. It is true that the cell life will be reduced by applying heat (from soldering iron) to the battery terminals but this is only negligible for the time required to execute the connection.

To install a holder to suit this type of battery would increase the cost by about 40 per cent.

We agree that it will be difficult to tell if the unit is on or off when not in use, but it can be determined; when the unit is "on" the push button will feel "loose" but in the "off" position this looseness disappears.

If this proves unsatisfactory a push-to-make release off type can be substituted.

More Accurate Timer

May I thank you for publishing another article combining the hobbies of electronics and photography (ref. *Darkroom Timer*, March issue).

Although of excellent design, I feel it must be stated that a timer with only a 5 second timing intervals is not nearly accurate enough for the demands of the high quality black and white or well balanced colour prints that are required. However, with a small modification, I have found that the timer may be converted to an accurate piece of equipment having a timing range of 5 to 45 seconds in one second steps.

The modification requires four extra components, which are a 5 position two-pole switch (S4), VR5, VR6 and VR7 which are

skeleton presets of the values, 5 kilohm, 10 kilohm and 20 kilohm respectively.

These components form an additional timing circuit which is connected in series with the original (R₁).

Position 1 of the switch has no further resistance and acts as a short circuit; position 2 connects VR5 into circuit, whilst position 3 connects VR6; position 4 connects VR5 and VR6 and position 5 connects VR7 into circuit.

Each position of the new switch is to represent a further one second delay.

Position 1 of course, has no further delay, position 2 however, will give a one second delay, position 3 two seconds etc. when the presets are set as they were in the original timing circuit.

Now, any time, in one second steps may be selected from 5 to 45 seconds by selecting the required 5 second range, plus the required extra time (if any) on the new switch.

D. G. Smith
Emsworth, Hants.

Components

Let me say first of all how much I enjoy your magazine and as a newcomer to electronics I find your *Teach-In* articles very interesting and also *Shop Talk*, etc. However, I wonder if I may make a suggestion?

I constructed your *Demo-Deck* and find that in following this series for a month or so there is a list of the more minor components used in the experiments and I wondered if it would be at all possible, either, preferably, if you could publish the list of all the components that would be required for the rest of this series in one complete list or if possible broken up into the individual months during which they will be required.

The reason I say this is, that I,

like many of your other readers no doubt, have no local supplier of components in my immediate vicinity and it usually means a trip to Edinburgh or Glasgow to purchase these components.

However, if I could have a full list this would make things much easier for me. It would also make it much easier to send off a full list by post to a mail order firm rather than asking for two or three small components every month or so. I wonder if this could be done.

I am very grateful to you and wish you every success for your future publications.

R. L. Grant
Scotland

It was our intention to publish an advanced list and in future we shall be publishing, at the end of each Teach-In every month, a list of components additional to those you have already acquired.

Calling Gloucester

Now that I'm receiving your magazine on regular order and greatly enjoying it, I feel that I ought to go a stage further in order to get any lasting benefit from your guidance.

Can I please find out through your pages how many people in the Gloucester area are willing to ask for, and attend, an evening class on useful, basic "everyday electronics"?

Should anyone be interested, could they please write to me at the address given, then provided enough wish it, our local Education Authority can be approached with evidence that the need for such a class does exist.

Many thanks for giving me a chance to ask for these people through your very sensible magazine.

E. L. Payn
82 Innsworth Lane,
Longlevens,
Gloucester
GL2 0DE

If you write to us for advice, and wish to have a personal reply you must include a s.a.e. Unfortunately, we cannot prepare special designs, circuits or wiring diagrams, to meet individual requirements nor can we answer queries concerning commercial equipment, or subjects or designs not published by us.

For all technical and editorial matters, write to: The Editor, *Everyday Electronics*, Fleetway House, Farringdon Street, London, E.C.4. Phone 01-634 4452.

For all enquiries concerning advertisements or advertisers write to: The Advertisement Manager, *Everyday Electronics*, at the above address. Phone 01-634 4202.

BI-PRE-PAK



TELEPHONE DIALS
Standard Post Office type.
Guaranteed in working order.
ONLY 50p

COMPLETE TELEPHONES
EX-G.P.O. NORMAL HOUSEHOLD TYPE



95p
EACH
P. & P.
35p
each.

NEW TESTED AND GUARANTEED PAKS

H2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, Approx. quantity, counted by weights	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes codded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mV. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1/2 watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

5p		6p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
AC177	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF186	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-20	2N1306-7	0-20
BC107	0-10	2N1308-9	0-22
BC108	0-10	2N3819FET	0-45
BC109	0-10		
BF194	0-15	Power Transistors	
BF274	0-20	OC20	0-50
BFY50	0-15	OC23	0-30
BSY25	0-13	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-10	AD149	0-30
OC44	0-15	AUY10	1-25
OC45	0-10	2S034	0-25
OC71	0-10	2N3055	0-50
OC72	0-10	Diodes	
OC81	0-13	AA442	0-10
OC81D	0-13	OA95	0-09
OC83	0-18	OA79	0-09
OC139	0-13	CA81	0-09
OC140	0-15	IN9114	0-07

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp., 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	10p	9p	8p
J. K. Flip-Flops, Factory, Marked and Tested by A.E.I.	20p	18p	15p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 1/2 P/Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes;** This includes many thousands of British U.S.A., European and C.V. equivalents. **The Hi-Fi Radio Valve & Transistor Data Book 9th Edition;** Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

F.E.T. PRICE

BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BS126-29, BS195A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc. £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 3p each; 1,000+ at 4p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

Please send me the FREE BI-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. E 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same — there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative — Project 605.


In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one — Masterlink — which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together — the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

Guarantee If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

sinclair

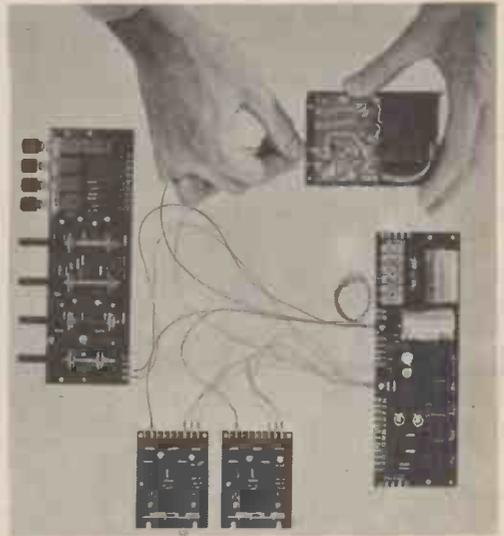Sinclair Radionics Ltd., London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Telephone: St. Ives (04806) 4311



Specifications

Output — 30 watts music power (10 watts per channel R.M.S. into 3 Ω).

Inputs — Mag. P.U. — 3mV correct to R.I.A.A. curve 20–25,000 Hz ± 1dB. Ceramic pick-up — 50mV. Radio — 50 to 150mV. Aux. adjustable between 3mV. and 3V.

Signal to noise ratio — Better than 70dB.

Distortion — better than 0.2% under all conditions.

Controls — Press buttons for on-off, P.U., radio and aux. Treble +15 to -15 dB at 10 kHz. Bass +15 to -15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel — brushed aluminium with black knobs.

Project 605 comprises Stereo 60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

£29.95

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE17 4HJ

Please send Project 605 post free Details and list of stockists

Name

Address

for which I enclose £29.95 cheque/money order/cash. E.E.7B

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records.
Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 1 3/4 x 1 1/2 in.
Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL £8-75 Post 25p.
MONO-COMPATIBLE
Plays all records £7-75 Post 25p.



RCS 3 WATT AMPLIFIER. Ready made tested. 2-stage triode valve UCL32. 3 watts output. Tone and volume controls. Rectifier valve UY85. Knobs. With high performance Loudspeaker.
Response 50-12,000 cps. Sensitivity 200mV. Post 25p £4

R.C.S. PORTABLE PLAYER CABINET

£4

Post 25p.

Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 x 15 x 8 in. Metal fittings. Carrying handle. Popular colours. Two-tone bezel covered.

GARRARD SINGLE PLAY TA MK II Complete with stereo/mono plug in head. Ideal Discotheque or Hi-Fi. £10

GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER £4-50
Turntable, 4-speed motor and separate pick-up

EMI PICK-UP ARM with mono stylus £1.25.
HI-FI PICK-UP CARTRIDGES: Diamond LP/Stereo Stereo/Mono 9TA £2.50; GP94 £2.50; GP93 £2.00; Sapphire Mono GP91 £1.50; Power-point LP/78. 60p.

E.M.I. WOOFER AND TWEETER KIT £5-75 Post 25p

Comprising a fine example of a Woofers 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines.
Impedance Standard 8 ohms
Maximum Power 12 watts
Useful Response 35 to 18,000 cps
Base Resonance 45 cps
SUITABLE ENCLOSURE 20 x 13 x 9 in, £9 POST 25p



WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial... 72p	Spare Cores 3p
O.C. P50/LAC 33p	Driver Trans. LPD74 58p
I.F. P50/CC 470 kc/s. 38p	Printed Circuit, PCA1 58p
3rd I.F. P50/3CC 38p	J.B. Tuning Gang 65p
P51/1 or P51/2 38p	Weyrad Booklet 10p
P50/7 38p	OPTI 58p
Mullard Ferrite Rod 8 x 1/2 in. 20p, 6 x 1/2 in. 20p.	

VOLUME CONTROLS
Long splines, Midget Size 5 K ohms to 2 Meg. LOG or LIN. 1/8 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K. S.P. Translator 25p

80ohm COAX 4p. yd.
BRITISH AERIALITE
AERIAL-AIR SPACED
40 yd. £1.40; 60 yd. £2.
FRINGE LOW LOSS 10p yd.
Ideal 625 and colour.

8in ELAC HI-FI SPEAKERS

Dual cone plasticized roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power. £4-80



BLANK ALUMINIUM CHASSIS 18 a.w.g. 2in. sides. 7 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 3in. 50p; 16 x 10in. 51p.
ALUMINIUM PANELS 18 a.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 3in. 18p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 28p; 16 x 6in. 28p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 60p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p.
2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.
TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

"THE INSTANT" BULK TAP ERASER & HEAD DEMAGNETISER 200/250v. A.C. £2-35 Post Leadet S.A.E. 15p

HI-FI STOCKISTS RADIO COMPONENT SPECIALISTS

Radio Books & Component Lists 5p. Written guarantee. (Export: Remit cash and extra postage.)

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifier and Double Wound Mains Transformer input 200/240v. A.O. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less.
PLEASE STATE VOLTAGE REQUIRED. £2 POST
Details S.A.E. Size 3 1/4 x 1 1/4 x 1 1/4 in. FREE

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 3/4". Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Post Full instructions supplied. Details S.A.E. 90p 10p

NEW TUBULAR ELECTROLYTICS	GAN TYPES
2/350V .. 14p	250/25V .. 14p
4/350V .. 14p	500/25V .. 20p
8/450V .. 14p	1000/25V .. 35p
16/450V 14p	1000/50V .. 47p
32/450V 20p	8+8/450V 18p
25/25V 10p	8+16/450V 20p
50/50V .. 10p	18+16/450V 25p
100/25V .. 10p	32+32/350V 25p
LOW VOLTAGE ELECTROLYTICS	1. 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.	1000mF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.	2500mF. 50V. 62p; 3000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.	

CERAMIC 1pF to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p. 0.5 13p; 1mF 15p; 2mF 15V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 500-2.200 pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01, mid 80p; each. TWIN GANG. "0-0" 208pF + 178pF. 65p; Slow motion drive 365+365 with 25+25pF. 56p 500pF slow motion, standard 45p; small 3-gang 500pF £1-60.

SHORT WAVE. SINGLE. 10pF 20p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1/4 w. 20% 1p; 2 w. 5p 10 ohms to 10 meg HIGH STABILITY. 1/4 w. 2% 10 ohms to 1 meg. 10p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 8 watt, 10 watt, 15 watt 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p

DECCA DECADEC GARRARD MOTOR UNIT MKII
Single play Stereo Mono Deram transcription head and arm Four speeds. 10 1/2 in. turntable. Anti-rumble filter Bias compensation. Laboratory motor.



SPECIAL PRICE £18-50 Post 25p

METAL PLINTH & PLASTIC COVER £5-50 Post 25p

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 7 1/2 in. ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6-3 v. 4 amp.	£1-50
250-0-250 80 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a.	£2-50
350-0-350 80 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a.	£3-00
300-0-300 v. 120 mA. 6-3 v. 4 a. C.T.; 6-3 v. 2 a.	£3-25
MINIATURE 200 v. 20 mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA. 6-3 v. 2 a. 4 1/2 x 2 1/2 in.	90p
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in.	90p
HEATER TRANS. 8-3v. 3 a.	60p
Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6-3 v. 1 1/2 amp.	80p
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 16, 18, 24 and 30 v. £2-25	
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £2-25	
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £3-25	
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60. £8-75	
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 160w. £2-25; 500w. £3-25; 750w. 100; 1000w. £14.	
CHARGER TRANSFORMERS. Input 200/250v. for 6 or 12v. 1 1/2 amp. £1-50; 2 amp. £1-60; 4 amp. £2-50.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p	
LUGAS 2DS500 Bridge 70V 5 amp. 11.	

E.M.I. 1 1/2 x 8in. LOUSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 15p £4-25

With fixed tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. Post 15p £2-75

State 3 or 8 or 15 ohm. Post 15p £5

Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

ALL MODELS "BAKER SPEAKERS" IN STOCK BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell's. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-GROUP" SPEAKERS
'Group 25' 12 inch £7 25 watt 3 or 8 or 15 ohm
'Group 35' 12 inch £9 35 watt 3 or 8 or 15 ohm
'Group 50' 15 inch £19 50 watt 8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20x12x9in. £9. Post 25p For 13x8in. or 8in. speaker 16x10x9in. £5. Post 25p For 10x6in. or 6in. speaker 16x8x6in. £4. Post 25p LOUSPEAKER CABINET WADDING 18in. wide, 15p ft.

GOODMANS 6 1/2 in. HI-FI WOOFER 8 ohm, 10 watt. Large ceramic magnet. Special Cambrie cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. HI-FI Enclosures Systems, etc. £4

ELAC CONE TWEETER
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1-90 Post 10p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16kc/s., 10W 8 ohm or 15 ohm £1-60. De Luxe Horn Tweeters 2-18 Kc/s, 15W 15 ohm £3-20. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 30 ohm 2 1/2 in.; 2 1/2 in.; 35 ohm. 2in.; 3in 25 ohm. 2 1/2 in.; 3in dia.; 6 x 4 in.; 8 x 6 in. £1 EACH TYPE 3 ohm. 2 1/2 in. 5 x 3 in. LOUSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 in. £1-50; 8 x 5 in. £1-60; 8 x 9 in. £1-75; 10 x 8 in. £1-90. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50-1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER
4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. £39 Post Free Guaranteed. Details S.A.E.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4-50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4-50.

BARGAIN FM TUNER 88-108 Mc/s. 8 Pin Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12-50

BARGAIN FM TUNER as above less cabinet £8-85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50

COAXIAL PLUG 8p. PANEL SOCKETS 6p. LINE 18p. OUTPUT BOXES, SURFACE OR FLUSH 5p. BALANCED TWIN FEEDERS 5p yd. 80 ohm or 300 ohms. JACK SOCKET 3id. open-circuit 15p. closed circuit 25p. Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS'S Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 8p; CERAMIC 8p; CANS 5p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. A.C. 1.200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1-25 Size 3 1/2 x 2 1/2 x 2 1/2 in. (Illustrated). BALFOUR GRAM MOTORS 120v. or 240v. A.C. 1.200 r.p.m. 4 pole 50mA. Spindle 1 x 3/20. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p 85p

CUSTOMERS FREE CAR PARK CALLERS WELCOME 337 WHITEHORSE ROAD, CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-3 p.m.) Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665

Everyday Electronics Classified Advertisements

RATES: 7p per word (minimum 12 words). Box No. 7p. extra. Semi-display—£4.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

EDUCATIONAL

TECHNICAL TRAINING in Radio, TV & Electronics through world-famous ICS. For details of proven home-study courses write: ICS (Dept. 566), Inter-text House, London, SW8 4UJ.

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, G22 Oxford House, 9-15 Oxford Street, London, W.1.

FREE

TO ENGINEERS

Whatever your age or experience you must read **New Opportunities**. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.



Send for your copy today—FREE!
B.I.E.T. B125, Aldermaston Court,
Reading, RG7 4PF

Accredited by the Council for the
Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SERVICE SHEETS

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

RECEIVERS and COMPONENTS

Send now for our
**ILLUSTRATED COMPONENT
EQUIPMENT CATALOGUE
SLIDE AND ROTARY LAMP
DIMMER CATALOGUE**

10p each—post free

YOUNG ELECTRONICS
54 Lawford Rd., London, NW5 2LN
01-267-0201

COMPUTER PANELS 5BC108, diodes, 4-50p post 10p. **PANELS WITH SILICON AND GERM/TRANS.** at least 50, 6—£1.00 post 15p. **UNIT WITH 4AL POT CORES+11 2% CAPS** 50p post 15p. **ICs 7400 SERIES ON PANEL(S)** 10—75p post 10p. **FALLOUTS 5—13p.** ORP12 on panel ex equipt. 35p cp. **BANK 20 WIRE ENDED NEONS** 50p post 8p. **SEND LARGE S.A.E. FOR LIST OF PANELS ETC.**
7LB ASSORTED COMPONENTS £1.30 cp.

J.W.B. RADIO
75 HAYFIELD ROAD SALFORD 6 LANCAS
MAIL ORDER ONLY

FOR SALE

ELECTRONIC COMPONENTS for sale, cheap, clearing laboratory, write for details. G. Smith, 3 Hart Road, Old Harlow, Essex.

MISCELLANEOUS

BEFORE BUYING Hi-Fi equipment; buy Audio Supply's new 105 page photographically illustrated catalogue (60p). Fair cash terms and service. Our associates manufacture records from customers' tapes. Specify requirements to Sound News, 18 Blenheim Road, London W4 1ES.

AUDIBLE CONTINUITY AND VOLTAGE TESTERS

Type D65. Suitable for Circuits up to 2.5 ohms. £2.50 each.
Type D67. Suitable for Circuits up to 10k ohms. £3.50 each.
Type D71. from 10k-5m ohms. £4.55 each.
All plus 10p Packing and Postage.

Coventry Controls Limited,
49, Allesley Old Road,
COVENTRY. CV5 8BU.

UNIMIXER 4S mono/stereo mixing unit £52. Recent reviews, specs, from manufacturers; Soundex Ltd., 18 Blenheim Road, London W4 1ES.

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3-30** post paid
or in kit form **£2-90**

Easy to construct
SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire Large S.A.E. for lists

ARE YOU BUILDING THE NIPPIBOARD

BABY ALARM
in April Everyday Electronics
or the **DARKROOM TIMER** IN MARCH.
Make these on easy-to-use type 2A ^{only 28p}
NIPPIBOARD ^{WIRING LAYOUTS SUPPLIED}

See our advert last month for other projects on this multi-purpose printed wiring board.
SL403D i.c. REDUCED to £1-20

NIP ELECTRONICS
DEPT. NB/EE, P.O. BOX 11, ST. ALBANS, HERTS

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8-90. **WAA-WAA Pedal** kit of all parts, incl. all mechanics & instr. Only £2-95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrots etc. costs £18-00 in modules. **SYNTHESIZER MODULES** and other miracles. Send 15p for illust. list.
D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually **SECRET** since they won't be heard by conventional means. Actually it's **TWO KITS IN ONE** because you get all the printed-circuit boards and components for both the transmitter **AND** receiver. You're going to find this project **REALLY FUN-TO-BUILD** with the **EASY-TO-FOLLOW** Instructions. An extremely flexible design with quite an **AMAZING RANGE**—has obvious applications for **SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.**

GET YOURS! SEND £5-50 NOW
S.A.E. for details

TO: BOFFIN PROJECTS'
DEPT. KEE.
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY

FLICKDIM SWITCH. Dim up to 500 watts at a flick. A must for TV, children's bedrooms, etc. White unit easily replaces lighting switch. Only 70p with money back guarantee. 5p postage. E. Griffiths, 6 Stanway Close, Alkington, Middleton, Manchester.

**PLEASE BE SURE
TO
MENTION**

EVERYDAY ELECTRONICS

when replying to
advertisements

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. **CROWBOROUGH ELECTRONICS (E.E.)**, Eridge Road, Crowborough, Sussex.


**SOUND SUPPLIES
(LOUGHTON) CO. LTD.**

for
Eagle International and International Rectifier Products
TOA P.A. Equipment and Mikes.
Capacitors, Resistors, Plugs, Sockets, Cables, Audio Leads, Remiconductors, Valves, Vero Board, etc., for the constructor.

ELECTRONICS DEPT. Tel. 01-508-2715
12 Smarta Lane, Loughton, Essex.

Hours: 9.30 a.m.-1 p.m., 2-6 p.m. Mon., Tues. Wed. and Fri.; 9.30 a.m.-1 p.m., 2-5.30 p.m. Sat. Closed all day Thursday.

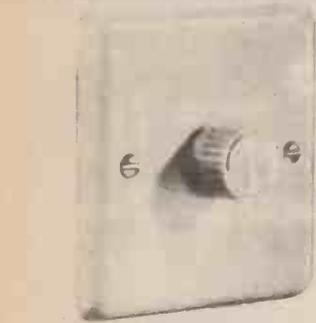Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70
300 Watt—£2.70. Kit Form £2.20

All plus 10p post and packing.
Please send C.W.O. to:—

DEXTER & COMPANY
5 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH Tel: 0244-25883,
As supplied to H.M. Government Departments.

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

MAIL ORDER ONLY.
S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ

BODINE TYPE N.C.I. GEARED MOTOR



(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle, 0.38 amp (Type 2) 28 r.p.m. Torque 20lb inch. Reversible. 1/80th h.p. 50 cycle, 0.28 amp. "As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.50 plus 35p P. & P. or less transformer £2.25 plus 27p P. & P.

12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of approx. 125 RPM. Size 4 1/4" x 2 1/4" dia. Price 95p Inc. post.



230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.

1 R.P.M. cw	1 R.P.H. A/cw	10 R.P.H. A/cw
2 R.P.H. cw	2 R.P.H. A/cw	15 R.P.H. A/cw
60 R.P.M. cw	3 R.P.H. A/cw	20 R.P.H. A/cw
6 R.P.H. cw	6 R.P.H. cw	30 R.P.H. cw

cw=Clockwise.
A/cw=Anti-clockwise rotation.
Fraction of maker's price. All at 75p incl. P. & P.

CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing. 2,750 r.p.m. Length 2 1/8". Dia. 1/2". Shaft length 1/2". Shaft dia. 3/32". No load 40 mA. Normal load 350 mA. Ideal for portable recorders, etc. etc. Price £1.25 p & p 10p



PROGRAMME TIMERS

(Mfr. by 'Magnetic Devices Ltd.')

240V A.C. 5 r.p.m. 'Crouzet' motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW PRICE: £5.75. P. & P. 25p.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1.75 incl. post.

VENNER Electric Time Switch

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk. OFF dawn. Price as above.

D.C. AMMETERS NEW!

1A, 5A, 15A, 20A, £1.75.

0-300V a.c., £1.90, incl. P. & P.

"HONEYWELL" LEVER OPERATED MICRO SWITCH

15 amps. 250 volt A.C. c/o contacts. NEW in maker's Carton. Price: 10 for £1.90 Incl. P. & P.



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT

VARIABLE 0.260V

All Types (and Spares) from 1/2 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7.00 2.5 amp, £8.05

5 amp, £11.75

10 amp, £22.50 20 amp, £49.00

15 amp, £25.00 25 amp, £58.00

37.5 amp, £82.00 50 amp, £98.00

OPEN TYPE (Panel Mounting) 1/2 amp, £4.75.

1 amp, £7.00 2 1/2 amp, £8.05. All types carriage paid.



Superior Quality Precision-Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 5 kΩ, 1.40 mA. Diameter 3 1/2 in. Shaft length 1/2 in. dia. 1/4 in. All at £1.63 each. P. & P. 7p.

50 WATT. 1/15/10/25/50/100/250/500/1/1-1/2-5/5kΩ. All at £1.15 each. P. & P. 7p.

25 WATT. 10/25/50/100/250/500/1/1-1/2-5/3-5/5kΩ. All at 90p each. P. & P. 7p.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT

Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard 5.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

HY-LYGT STROBE MK III

This strobe has been designed and produced for use in large rooms, halls and the photographic field and utilises a silicone plug-in tube for longer life expectancy.

Printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00. P. & P. 50p.

SPECIALLY DESIGNED. FULLY VENTILATED METAL CASE. Including reflector. £4.00 P. & P. 45p

Post paid with kit.

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Reactor control circuit producing an intense white light.

The brilliant light output of the 'SUPER' HY-LYGT gives fabulous effects with colour filter.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including reflector £7.00 P. & P. 45p.

7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price £3p, P. & P. 13p or post paid with kits.

RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1		2		3		4	
1	2	3	4	1	2	3	4
52	3-6	2 c/o	63p*	700	22-30	6 c/o	75p*
410	10-18	4 c/o	73p*	700	15-35	2 c/o HD	73p*
600	12-24	4 c/o	78p*	700	16-24	6M	65p*
600	18-32	4 c/o	78p*	1,250	24-36	4 c/o	63p*
700	16-24	4M 2B	63p*	2,500	36-45	6M	63p*
700	16-24	4 c/o	78p*	2,400	30-48	4 c/o	50p*
700	12-24	2 c/o	63p*	9,000	40-70	2 c/o	50p*
700	6-12	1 c/o HD	80p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.e. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid.

*Including Base.

12 VOLT D.C. RELAY

Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS (UNUSED)

Three sets c/o contacts rated at 5 amps. Price: 50p P. & P. 10p. (100 lots £40.00 incl. P. & P.)

'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P. & P. 5p. (100 lots £32.00 incl. P. & P.)

230 VOLT A.C. SOLENOID OPERATED FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/2" b.s.p. inlet/outlet. Precision made, British mfg. Price £1.75. P. & P. 20p. Special quotation for quantity.



SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. E.E. 57 BRIDGMAN ROAD, LONDON, W4 5BB
Phone 01-795 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.
9 LITTLE NEWPORT ST.
LONDON WC2H 7JJ 01-437 0579

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

MIDGET FLEX CONNECTOR
Approx. 2 amp rating.
Two-pin non-reversible midget flex connector. Approx. size: 2in. x 1/2in. Ideal for loudspeaker connections, etc. 8p plus 2p P. & P.

MAINS TRANSFORMER
Fused Primary 240V. Secondary 220V @ 50M/A. 6.3V.
@ 1A. This transformer is made to a very high standard and is a small size: 2in. x 2 1/2in. x 2 1/2in. 63p plus 15p P. & P.

BRIDGE RECTIFIER
Plastic encapsulated. Texas Type No 1B40. K05 50v at 4 amp. Our Price 55p + 5p P. & P.

HIGH QUALITY IMPORTED HEADPHONES
1,000 Ω per phone ... 80p
2,000 Ω per phone ... 88p
Plus 10p P. & P. per pair.

COMPONENT CORNER each
Veroboard Offcuts - 2in. 3 1/4" x 5 1/4" ... 17p
Plain Veroboard - 1in. 3" x 3" ... 8p
Standard Toggle Switch, DPDT 18p
D.P.D.T. Slide Switch ... 13p

Experimental Transistor Holders, 3-pin and 4-pin 7p
I.C. Holders for 14 or 16 pin 20p
Please include 5p p. & p. per 3 items

10,000MFD @ 16V CAPACITOR
A few only at this price. 3 1/2" long. 1 1/2" diameter. Screw Terminals. 40p each. Please include 5p p. & p.

2W3055
POPULAR POWER TRANSISTOR
Now at our Low Price 50p each
Please include 5p P. & P.

BARGAIN S.C.E.
TESTED THYRISTOR
400 volt. 3 amp.
45p each 5 for £2.00
Please include 5p P. & P.

POWER TRANSISTOR HEAT SINKS
Extruded aluminium. Approx. size: 6" x 4 1/2" x 1 1/2". A few only at this low price - 40p each + 5p P. & P.

SINGLE EARPIECES
Crystal or Magnetic 3.5mm or 2.5mm (please state which type you require. Complete with lead. 20p plus 3p p. & p.

LOUDSPEAKER BARGAINS
E.M.I. 450 set 3.8. 15 ohm 23-25 plus 38p. P. & P.
E.M.I. 350 set 8 ohm. 27-00 plus 38p. P. & P.

MINI LOUDSPEAKERS
2 1/2" 8 ohm 38p 2 1/2" 40 ohm 38p
3" 8 ohm 40p 2 1/2" 25 ohm 38p
Plus 3p. P. & P. on each Mini Speaker.

TRI-VOLT BATTERY ELIMINATOR
Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require - 6v, 7 1/2v or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2 1/2" x 2 1/2" x 3 1/2". OUR PRICE - £2.75p + 10p. P. & P. Same model suitably wired for the Philips Cassette - £3.00 + 10p. P. & P.

ALUMINIUM CHASSIS
Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.
6 x 3 - 41p 12 x 3 - 53p 14 x 3 - 84p
6 x 4 - 45p 12 x 4 - 81p 16 x 6 - 86p
8 x 6 - 53p 12 x 8 - 88p 16 x 10 - 1.08p
10 x 7 - 63p 14 x 3 - 60p
Please send 10p per chassis P. & P.

CAPACITORS
Mini Electrolytics all values up to 100MFD @ 15V - 7p each
Small PP Capacitors only in packs of 10 but you can mix values - 25p for 10.
250MFD @ 25V - 15p
500MFD @ 25V - 21p
1000MFD @ 25V - 27p
2000MFD @ 25V - 34p
3000MFD @ 25V - 45p
5000MFD @ 25V - 53p
Please inc. 10p. P. & P. with orders under £2 value.

PRINTED CIRCUIT KIT
Everything for producing your own printed circuits. £1.40p plus 10p. P. & P.

PRINTED CIRCUIT BOARD
8 x 10 - 10p 10 x 8 - 15p
9 x 5 - 10p 12 x 12 - 20p
Please inc. 3p. per board P. & P.

EA1000 3 WATT AUDIO AMPLIFIER MODULE
An Audio Amplifier designed around the TAA821 Linear I.C. -
Supply Voltage ... 9-24V
Speaker Imp. ... 8-16 ohm
Frequency ... 50Hz-25kHz
Overall Size ... 2in x 3in x 1 1/2in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at

BULGIN OCTAL PLUG
Ideal for all those multi-way connections. This plug couples with a standard 8-pin valve holder. Plug ... 12p Socket ... 8p
Please include 4p p. & p.

POTENTIOMETERS
All types 1" and less diameter. SINGLES DUAL
5K Log or 10K
10K Lin Less 10K
25K Switch 25K Less
50K Switch 50K Switch
100K 17p ea. 100K 45p.
250K Double 250K
800K Pole 300K each
1M 1M
2M Switch 2M
2M 2M
Up to 3 Pots. Please add 5p. P. & P.

RESISTORS
We stock all recognised values of resistors all at 10% or closer tolerance. We regret we can only mail them in lots of ten. You can send for mixed values.
All midget types.
1 watt lots of 10 - 13p
1/2 watt lots of 10 - 15p
1 watt lots of 10 - 25p
Please include 3p P. & P. for each 10 resistors.

£2-63 + 5p P. & P.

YOURS FREE FOR 7 DAYS



The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

To The SELRAY BOOK CO., 60 MAYES HILL, MAYES, BROMLEY, KENT BR2 7HP
Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. BASIC ELECTRONICS £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

WHAT READERS SAY

"A MATHEMATICAL IDIOT"
They have an easy approach to learning that a mathematical idiot like myself can easily understand. K.L.Y., Ashton-u-Lyme.

"WAS AMAZED"
I was amazed how easy it was to read and learn. L.Y.C., Addington.

"FIRMEST RECOMMENDATION"
You have my firmest recommendation in favour of this method of Self Teaching. B.W., Blackburn.

Tick Set required (Only one set allowed on free trial)
BASIC ELECTRICITY BASIC ELECTRONICS
Prices include Postage and Packing.
Signature _____
(If under 21 signature required of parent or guardian)
NAME _____
BLOCK LETTERS
FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER !!

A TECH-PRESS PUBLICATION
400

Build yourself a TRANSISTOR RADIO



NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 8" x 2 1/2" Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)

ROAMER EIGHT Mk I




NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 8" x 2 1/2" Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9" x 7" x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P.P. & Ins. 41p. (Overseas P. & P. £1)


ROAMER SEVEN MK IV

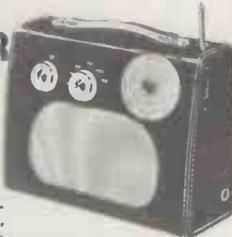

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 8" x 2 1/2" speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9" x 7" x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs **£5-98** P.P. & Ins. 41p. (Overseas P. & P. £1)

ROAMER SIX

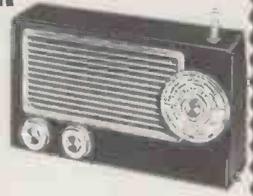

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9" x 6 1/2" x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P.P. & Ins. 22p. (Overseas P. & P. £1)

POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P.P. & Ins. 21p. (Overseas P. & P. 63p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2" x 4 1/2" x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P.P. & Ins. 22p. (Overseas P. & P. 63p)

TRANS EIGHT

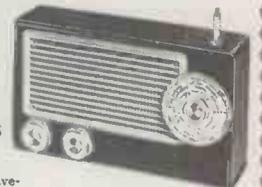

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9" x 5 1/2" x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P.P. & Ins. 31p. (Overseas P. & P. £1)

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for

Name

Address

(Dept. E.E.7.)

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4"x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: Diodes: Resistors: Capacitors: Three 1/2" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including **£5-50** P.P. & Ins. 31p. (Overseas P. & P. £1)



FULL AFTER SALES SERVICE

- Callers side entrance Barratts Shoe Shop
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

HENRY'S RADIO LIMITED



ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · ELECTRONIC COMPONENTS · TEST · P.A. · DISCOTHEQUE · LIGHTING · MAIL ORDER

TEXAN



20 + 20 WATT I.C. STEREO AMPLIFIER

(As featured by "Practical Wireless" May/June 1972)

DEVELOPED BY "TEXAS" ENGINEERS FOR PERFORMANCE, RELIABILITY AND POWER

FEATURES INCLUDE: Low profile with specially designed Gardners Transformer, 6—I.C.'s, 10 Transistors, 4 Diodes, 2 Zeners, Fibre glass P.C. panel, Multi protection, Stabilised supply, DIN input/output. Complete chassis work.

FUNCTIONS: Separate Treble/Bass/Volume/Balance controls, Input selector, Mag. pu, Radio, Tape in and out, Headphone socket, Scratch and rumble filters, Mono/Stereo switch.


SLIM DESIGN WITH SILVER TRIM—Chassis size overall 14 1/2" x 6" x 2" max.

TOTAL COST TO BUILD £28.50. Post 45p. (Optional Teak sleeve available July/August)

Henry's are sole U.K. trade and retail suppliers of the Texan—enquiries invited

TEXAS—HENRY'S VALUE & PERFORMANCE

LATEST EDITION CATALOGUE

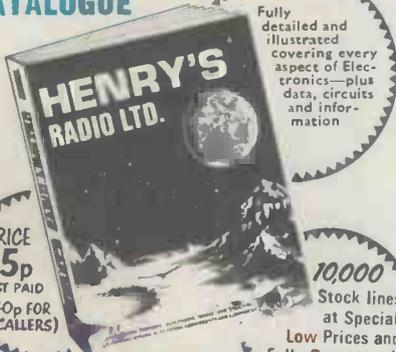

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE 55p POST PAID (40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. EE), 3 Albemarle Way, London, E.C.1.—for catalogue by post only.

All other mail and callers to "303", see below

PUBLIC ADDRESS, LIGHTING & DISCOTHEQUE EQUIPMENT

- DJ105S 30 watt rms Amplifier, 4 inputs, master tone and volume controls etc. 8 ohm output. Cased portable. £33.50. Post 40p.
- DJ70S 70 watt rms version. Cased portable. £49.75. Post 40p.
- DISCOAMP 100 watt rms to 8 ohms. 4 inputs, separate bass and treble controls, PFL, etc. Cased for cabinet or rack mounting £67.50. Post 40p.
- McDONALD MP60 fitted to plinth with cover, SC5MD cartridge to match above amplifiers. £17.25. Post 70p.
- DJ30L11 3 channel light control unit for above amplifiers. 3 x 1 K Watt, Treble, Bass and Mid range. £28.50. Post 35p.
- DJ40L as 30L plus mike £37.50
- EFFECTS PROJECTORS—Coloured rotating light patterns.
- DISCO-COLT 150w Tungsten £23.50
- LQ1 50—50 watt Q.I. £32.50
- LQ1 150—150 watt Q.I. £50.00



SPECIAL! Anti-Feedback Microphone designed and made for Henry's for all PA/Disco Equipment. £11.50

LIGHT GUIDE 64 fibres sheathed £1 per yd. Mono (0-01") £1.50 per 25 metre reel.

Call, write or phone for details and lists.

HI-FI—LARGEST RANGE IN STOCK—BIGGEST DISCOUNTS.

FREE 12 Page STOCK LIST Ref 16/17

Complete range of Disco PA/ Lighting on display at "303"

TEST EQUIPMENT

Huge range in stock—too much to list here. It's all in the latest catalogue—prices—specifications etc. Also Panel Meters and Edge Meters.



GARRARD McDONALD GOLDRING TURNTABLES

- CHASSIS (Post 50p)
- SP25 £10.50 HT70 £15.00
 - MP60 £10.40 MP610 £14.15
 - AP76 £18.85 Zero 100S £40.75

With PLINTH/COVER (Post 70p)

- MP60 PC £17.20
- HL75 PC £35.25
- HT70 PC £21.60
- GL75 £29.24

CART/PLINTH/COVER (Post 70p)

- GL72PC/G800 £34.50
- (HL)AP76/G800 £29.95
- HT70 PC/G800 £27.00
- MP60 PC/SC5M £17.25
- (HL)SP25/3/G800H £18.95
- (HL)2025 TC/9TAHCD £13.50

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.

PRICE PAIR £5.90 Post 10p

POWER INTEGRATED CIRCUITS

- SL403D—3 watt with 8 page data, layouts & circuits £1.50
- P.C. Board 60p; Heat Sink 14p
- IC12—6 watt with data and circuits £1.80
- TH9013P—20 watt Power Amp Module £4.57
- TH9014P—IC Preampifier £1.50

Data / Circuits Book for above No. 42 10p

TEXAS PUBLICATIONS

- 1-100 watt Amplifiers and PreAmp. Layouts and data £1.25 (Price list No. 49A FREE)
- 700 page IC Data Book (No. 2) (All TTL IC's) 60p
- 420 page Transistor Data (No. 3) 60p
- 340 page Transistor Data (No. 4) 60p

(Post etc. 20p each.)

7 SEG & NIXIE TUBES (Post 15p per 1 to 6)

- XN3, XN13, GN6 0-9. Side view with data 85p.
- GNP-7, GNP-8 0-9. Side view with decimal points and data 95p
- 3015F 7-Segment £7 per 4 with data. New Digital Clocks Circuits, Nixie and 7 segment. Ref 31 15p

SEE EARLIER PAGE FOR TRANSISTORS & DIODES, etc. FREE LIST No. 36 ON REQUEST

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.


- TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
- TYPE 150 TC Twin cone version £2.75. Post 22p.
- TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
- TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.

POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.

HIGH POWER AMPLIFIER MODULES



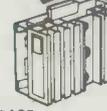Quality transformerless low noise amplifiers suitable for all Audio, PA and HI-FI use. Modern compact designs, PA25 and PA50 supplied with plug harness for use with MU442 Power Supply.



- MPA12/3 18v. 0-8A. 12W. 3-4 ohm. £4.50
- MPA12/15 30v. 0-5A. 12W. 12-16 ohm. £5.25
- MU24/40 Mains unit for 1 or 2 MPA12/3 or 15. £4.50
- PA25 22-0-22v. 1A. 25W. 8 ohm. £7.50
- PA50 22-0-22v. 2A. 50W. 3-4 ohm. £9.50
- MU442 Mains unit for 1 or 2 PA25 or 1 only PA50. £6.00

PA25 Post 20p per unit

ALL SILICON-FET PREAMPLIFIER AND MIXER SELF POWERED



All inputs. Adjustable input and output. DIN sockets. Tape in and out. Microphone mixing. Suitable up to 4-PA25 or 2-PA50.

300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled STR Amplifier. Size 5 1/2" x 1 1/2" x 3/4". 1-10mV adjustable sensitivity. Output 3-8 ohms; Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost.

Price £1.75, p.p. 15p (or 2 for £3.25, p.p. 15p)



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO

A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.

TOTAL £6.97, p.p. 20p. Decoder Kit £5.97.

Tuning meter unit £1.75

Mains unit (optional) Model PS900 £2.47. Post 20p

Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p



SINCLAIR PROJECT 60 MODULES—SAVE POUNDS!

- Z30 £3.57 Z50 £4.37
- STEREO PZ5 £3.97
- 60 £7.97 PZ8 £4.77
- PZ6 £6.37



Transformer for PZ8 £2.95

- Active Filter Unit £4.45
- Stereo FM Tuner £16.95

IC12 £1.80; Q16's £15 p.p.

Post etc. 20p per item

ALSO IN STOCK

- 2000 £23.50; 3000 £30.95
- Post 50p each

PACKAGE DEALS

- 2 x Z30, Stereo 60, PZ5 £15.95
- 2 x Z30, Stereo 60, PZ6 £18.00
- 2 x Z50, Stereo 60, PZ8 £20.25

Post 25p extra on above items

Transformer for PZ8 £2.95 Post 20p

NEW PROJECT 605 KIT £20.95 Post 25p

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module, Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tunings, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.

TOTAL COST TO BUILD £7.98.

p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2.

771 MEDIUM AND LONG WAVE PORTABLE (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

SLIDER CONTROLS. Top quality 60mm stroke singles and ganged. With knobs. (Post 1-3 15p; 6 or more 20p)

- 5K, 10K, 25K, 50K, 100K, 500K, 1 Meg. Log and Lin 45p each
- 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S

Electronic Components, Audio and Test Gear Centre
356 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 5854

P.A., Disco & Lighting Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Orders. Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/9

"309", "354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY