

Easy to build projects for everyone

Everyday ELECTRONICS

KIOSKS KIOSKS
McCloud

MAY 79
45p


free

DUAL
PURPOSE
TOOL




FOR
YOUR
TOOL
KIT

INTRUDER ALARM

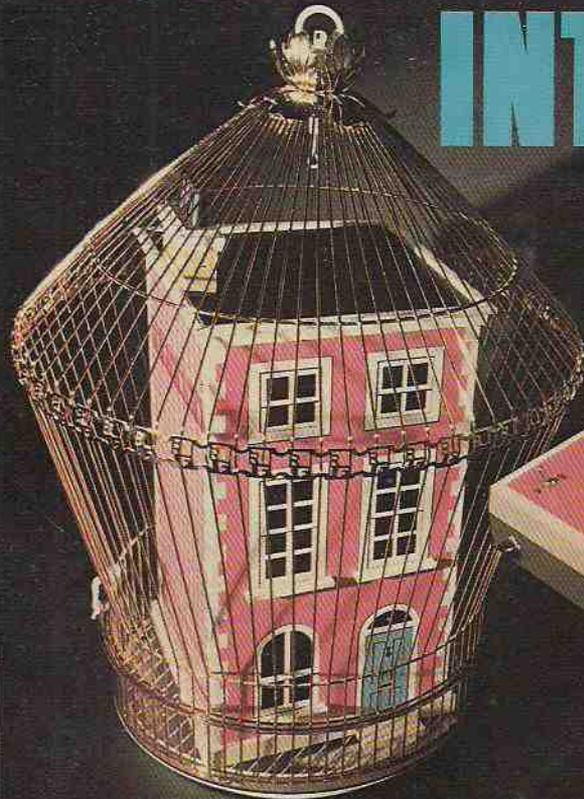


WIRE
UP
FOR
ALL
ROUND
PROTECTION

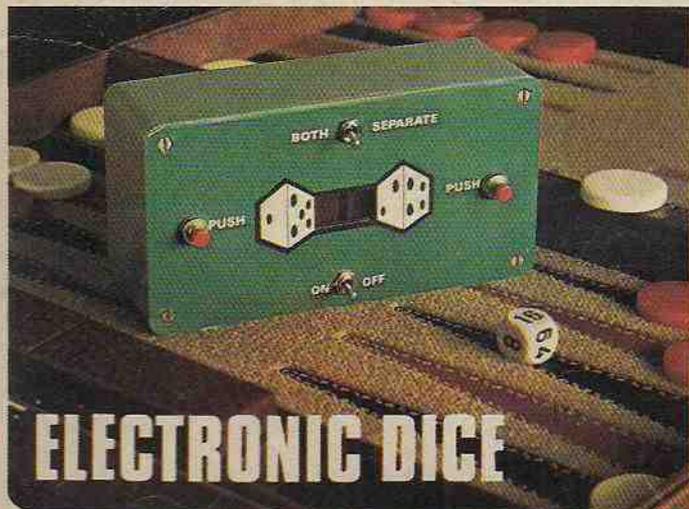

ELECTRONIC DICE

THERMOSTAT

FOR
PHOTOGRAPHIC
SOLUTIONS

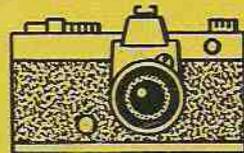

S.W. CONVERTER

FOR USE WITH M.W. RECEIVERS

QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.

Very slim, only 6mm thick.



M1

QUARTZ LCD 7 Function

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9 65

Guaranteed same day despatch.

Very slim, only 6mm thick.



M2

QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Metac Price:

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

QUARTZ LCD ALARM 6 Function

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65



M4

QUARTZ LCD ALARM 7 Function

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

£18.65



M5

QUARTZ LCD Alarm Chronograph with Dual Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£24.65



M6

QUARTZ LCD Alarm Chrono with front alarm

Dual time. Ten function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light.

£27.65



M7

QUARTZ LCD Alarm Chrono

Ten function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION

£22.65



M8

SOLAR QUARTZ LCD Chronograph

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£14.95



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00

METAC PRICE

£105.00



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

£68.00



M11

SOLAR QUARTZ LCD 5 Function

Genuine Solar Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.


£ 9.95

Guaranteed same day despatch.



M12

HANIMEX Electronic LED Alarm Clock

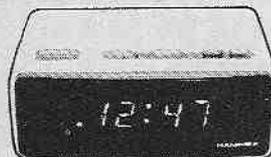

Features and Specification:

Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.16" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

£8.65

Guaranteed same day despatch.

M13

QUARTZ LCD Ladies Slim Bracelet

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold.

State preference.

£15.95

Guaranteed same day despatch.



M14

QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.


£9.95

Guaranteed same day despatch.



M15

DIGITAL LED CLOCK

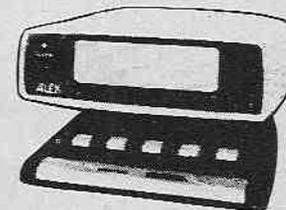

Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED OVERSHEDES
DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/
P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL
INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY
WELCOME. P&P Add 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS
POSTAGE AT COST. AIR/SURFACE. Send 50p (plus 25p p&p) for our catalogue.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise,
all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add
12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football
Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to
Saturday 9.00 am-6.00 pm. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in μF)
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 11p;
0.047, 0.068 14p; 0.10 17p; 0.15, 0.22 24p; 0.33, 0.47 41p; 0.68 48p;
160V: 0.033, 0.15, 0.22, 1p; 0.33, 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 4.7 48p.
DUBILIER: 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 25p; 0.1 38p; 0.47 48p; 1.0 175p.

POLYESTER RADIAL LEAD (Values in μF) 250V:
0.01, 0.015, 0.022, 0.027 9p; 0.033, 0.047, 0.068, 0.1 7p; 0.15 12p;
0.22, 0.33 13p; 0.47 17p; 0.68 19p; 1.0 24p; 1.5 31p; 2.2 34p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in SF) 500V: 10 40p; 47 68p;
250V: 100 65p; 65V 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 5.6, 10, 15, 22 8p; 47, 30 50 15p; 63, 100 22p;
50, 50, 100, 220 25p; 470 32p; 1000 50p; 40V: 22, 33, 9p; 100 12p; 2200 89p; 3300 82p; 4700 85p;
35V: 10, 33 7p; 330, 470 32p; 1000 49p; 25V: 10, 22, 47 6p; 80, 100, 160 8p; 220, 250 13p; 470, 640
35p; 1000 27p; 1500 30p; 2200 45p; 3300 68p; 4700 85p; 16V: 10, 40, 47, 68 7p; 100, 125 9p; 220,
330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 10V: 1.0 10p; 100 8p; 640 12p; 1000 14p.

TAG-END TYPE: 70V: 2000 89p; 4700 135p; 50V: 10,000 255p; 49V: 2500 85p; 3300, 4700 70p;
15,000 45p; 25V: 4700 2200 48p; 325V: 200+100+50+100 196p; 32+32 175p.

TANTALUM BEAD CAPACITORS 35V-0.1 μF : 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 22p; 3.3, 4.7, 5.6 25p;
1.5, 10 20V: 1.5 15p; 10 13p each 47, 100, 40p; 22 μF : 22 μF , 33 20p 6p;
47, 68, 100, 30p 3p; 68, 100 10p 7p.

MYLAR FILM CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01 μF 8p
0.015, 0.02, 0.04, 0.05, 0.056 μF 7p
0.1 μF , 0.2 9p 50V: 0.47 12p

MINIATURE TYPE TRIMMERS
2.5-90F, 3-10pF, 10-40pF 22p
2-25pF, 5-45pF, 50pF, 85pF 30p

COMPRESSION TRIMMERS
3-40pF, 10-80pF 30p; 25-190pF 33p
100-500pF 45p; 1250pF 60p

POLYSTYRENE CAPACITORS
10pF to 1nF 9p; 1.5nF to 10nF 11p

SILVER MICA (Values in pF): 3.3, 4.7, 5.6, 10, 12, 18, 22, 33, 47, 50, 68,
75, 82, 85, 100, 120, 150, 220 5p each
250, 300, 330, 360, 390, 450, 500, 560, 620 10p each
1000, 1200, 1500, 2000 20p each

CERAMIC TRIMMER CAPACITORS
2-7pF, 4-15pF, 8-25pF, 8-30pF 20p

SOLDERING PINS*
100 50p; 300 20p


JACK PLUGS Screened chrome 13p; Plastic body 10p; open metal 8p; moulded with break contacts 8p; S-DEC 250p; T-DEC 480p; U-DEC 38p; U-DEC 38p 89p*

SOCKETS 2-Pin 13p; 3-Pin 13p; 4-Pin 13p; 858-Pin 13p; 859-P

KITS FOR SOUND EFFECTS AND OTHER PROJECTS

PHONOSONICS

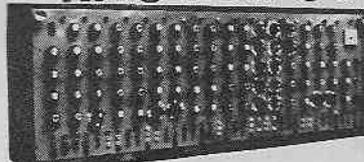MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.



GUITAR EFFECTS PEDAL (P.E. July 75)

Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit. Component set with special foot operated switches £7.69
Alternative component set with panel switches £5.05
Printed circuit board £1.43

GUITAR FREQUENCY DOUBLER

(P.E. Aug. 77)
A modified and extended version of the circuit published. Component set and PCB £4.52

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)

Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments. Component set using dual rotary pot £6.89
Printed circuit board £1.62

GUITAR SUSTAIN (P.E. Oct. 77)

Maintains the natural attack whilst extending note duration. Component set, PCB and foot switches £5.13
Component set, PCB and panel switches £3.71

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds. Component set (incl. PCB) £4.26

COMPONENTS SETS include all necessary resistors, capacitors, semi-conductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately

10% DISCOUNT VOUCHER (E94)

TERMS: Goods in current adverts & lists over £50 goods value (incl. P & P & V.A.T.). Correctly coded. C.W.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of E.E.

ADD: POST & HANDLING
U.K. orders—Keyboards add £2.00 each plus VAT. Other goods: under £15 add 25p plus VAT, over £15 add 50p plus VAT. Recommended: optional insurance against postal mishaps, add 50p for cover up to £50, £1.00 for £100 cover, etc. pro-rata.
N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

VOICE OPERATED FADER (P.E. Dec. 73)
For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows. Component set (incl. PCB) £3.97

PHASING UNIT (P.E. Sept. 73)
A simple but effective manually controlled unit for introducing the phasing sound into live or recorded music. Component set (incl. PCB) £3.20

PHASING CONTROL UNIT (P.E. Oct. 74)
For use with the above Phasing Unit to automatically control the rate of phasing. Component set (incl. PCB) £4.74

TREMOLO UNIT
Based upon P.E. Sound Design circuit. Component set (incl. PCB) £2.94

TREBLE BOOST UNIT (P.E. Apr. 76)
Gives a much shriller quality to audio signals fed through it. The depth of boost is manually adjustable. Component set (incl. PCB) £2.51

WAH-WAH UNIT (P.E. Apr. 76)
The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller. Component set (incl. PCB) £3.63

AUTOWAH UNIT (P.E. Mar. 77)
Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played. Component set, PCB, special foot switches £7.67
Component set and PCB, with panel switches £4.63

PHOTOCOPIES of texts for most of the kits are available—prices in our lists.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

ADD 12½% VAT (or current rate if changed). Must be added to full total of goods. Discount, post & handling, on all U.K. orders. Does not apply to Exports.

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list—Europe send 20p, other countries send 50p.

PRICES ARE CORRECT AT TIME OF PRESS.
E.O.E. DELIVERY SUBJECT TO AVAILABILITY.

TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT
(TEL: 01-302 6184)

PHONOSONICS · DEPT. EE94 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success: knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept G268 Intertext House, London SW8 4UJ or telephone 622 9911

Subject of Interest
Name
Address
Tel: Agc:

S. & R. BREWSTER LIMITED

WHY PAY MORE?

for Miniature Soldering Irons & Accessories		PRICE EACH	P & P Extra EACH
 18 watt Soldering Iron available in 12, 110 & 240 Volts fitted with No. 20 bit		£3.78	+ 22p
SPARE BITS	No. 19 size 1.5mm or No. 20 size 3mm or No. 21 size 4.5mm or No. 22 size 6mm		44p
	No. 78. I.C. Desoldering Bit		88p + 9p
	No. 1920L Long Life Bit		95p
SAFETY STAND		£3.25	+ 65p
SOLDER	Savbit 20'		52p + 9p
	Savbit 10'		26p + 4p
	Lowmelt 10'		65p + 9p

INDUSTRIAL/RETAIL ENQUIRIES WELCOME FOR THE ABOVE

We also Offer & Recommend for Mail Order & Personal Callers Only

	PRICES EACH including V.A.T. and P & P
Oryx 50 Temperature Controlled Soldering Iron	£10.50
Spare tips for above	£1.10
Isotip quick charge rechargeable Soldering Iron	£20.40
Spare tips for above	£2.60
Cable 7/0.2 11 Colours 100 meter reel	£2.25
0.1 Veroboard 3" x 11"	£1.90
0.1 Veroboard 4" x 18"	£4.25
Copper Clad board single sided	70p
Watchmakers Side Cutters	£4.75
Watchmakers Pliers	£4.25
Transformer 100VA 2 x 12V 4.1A	£10.50

OTHER ITEMS ALSO AVAILABLE ASK FOR LIST S.A.E.

MAIL ORDER DEPT.
86-88 Union Street, Plymouth
PL1 3HG Tel:(0752) 65011

Please Quote your Number when ordering.




SOLDERING IRONS
THE MIGHTY MIDGETS

The latest kit innovation!

from **Sparkrite**

Sparkrite was featured by Shaw Taylor in "DRIVE IN"

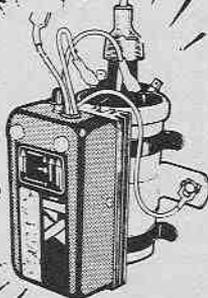the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronics Design Associates, Dept. EE 5
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791 (U.K. only)

Electronics Design Associates, Dept. EE 5
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791


Name
Address

Phone your order with Access or Barclaycard
Inc. VAT and P.P. (U.K. only.) QUANTITY REQ'D. Send SAE if brochure only required.

X4 KIT	£16.65	I enclose cheque/PO's for £ Cheque No. _____
TACHO PULSE SLAVE UNIT	£3.85	

PLEASE STATE POLARITY POS OR NEG EARTH.
Access or Barclaycard No. _____

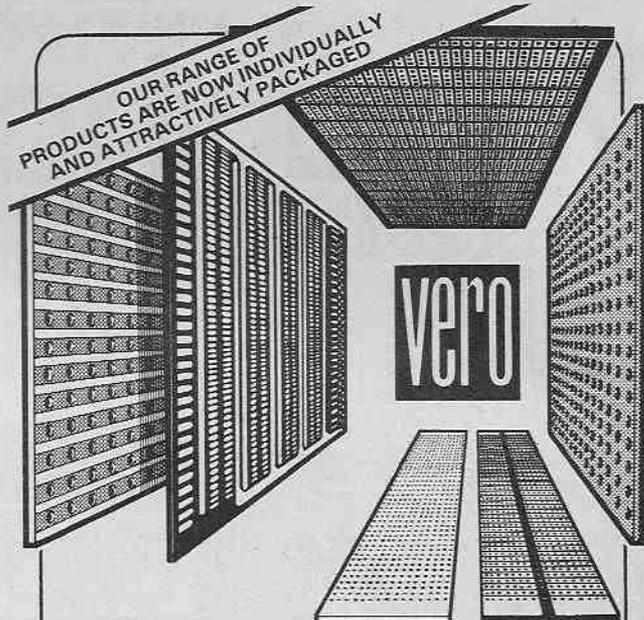OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new catalogue lists circuit boards for all your projects, from good old Veroboard through to specialised boards for ICs. And we've got accessories, module systems, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

MAIL ORDER DEPT.

CRESCENT RADIO LTD.

1, ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22. 45J.
PHONE 01-888 3206



"FLIP"
Push button heads or tails.
Complete kit and full instructions supplied.
A pocket game.
Easy to build and great to play.
Kit price—£5.25 + 8% VAT. Post free.

4 OHM DOOR MOUNTING CAR LOUSPEAKERS



High performance, door mounting. 5 1/2 inch units with smart front grill. 10 oz magnet, 12 watts, 4 ohms. In attractive see-through carton. £12.60 + 12 1/2% VAT. per pair.

HEAVY DUTY XOVER 2 WAY 8 OHM

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100 watt. Fitted with screw terminals for input and a three position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB. ONLY £3.00 + 8% VAT

A CRESCENT 'SUPERBUY'
Goodmans 5" 8 ohm long throw H/D loudspeaker.
Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/2" (diagonally). ONLY £5.00 + 12 1/2% VAT



'P&P' ORDERS UP TO £5. Add 30p
ORDERS £5-£10. Add 50p
All orders over £10 post free!
Please add VAT as shown.
S.A.E. with all enquiries please



Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N13.
ALSO: 13 SOUTH MALL, EDMONTON GREEN, EDMONTON.

LOUDSPEAKERS + 12 1/2% V.A.T.
2 1/2" (57mm) 8 or 75 ohm 90p
(please state impedance req'd)



MORSE KEY CR.38
All metal, cast base, professional high speed key. Fine adjustment. Mounted on bakelite base.
Dimensions: (Base) 120 x 75mm
£3.90 + 8% VAT

CR 4110 DESOLDERING PUMP



ONLY £6 + 8% VAT
High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000W lighting per channel, max. This 3 channel sound to light unit is housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions supplied. S.A.E. for spec. sheet. ONLY £20.00 + 8% VAT

CR LV1 12v DRILL



£12.00 + 8% VAT
BRITISH MADE "Versadrill", 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:— 150 x 50mm (dia.)

LOOK!

Here's how you master electronics.

.... the **practical** way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

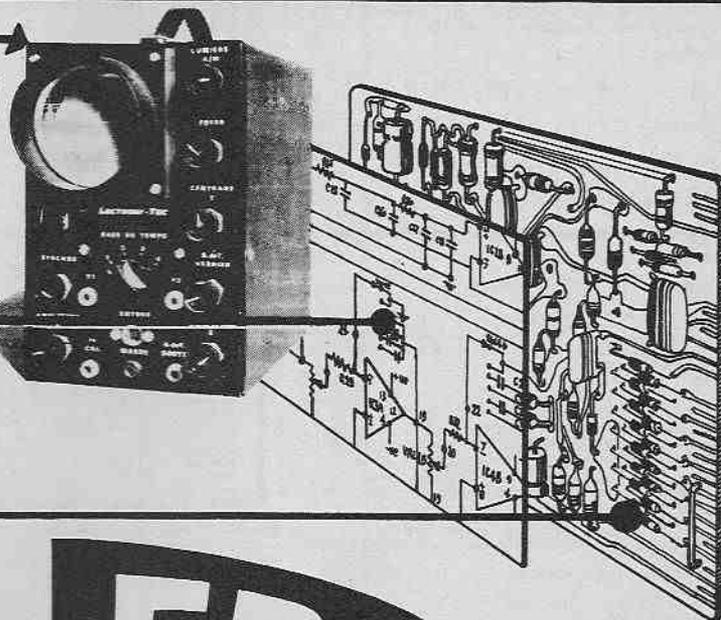1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2. Read, draw and understand circuit diagrams.


In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

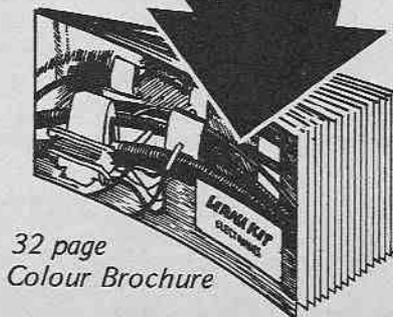4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



32 page
Colour Brochure

Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

EEB5/79

Block caps please

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS

Electrolytic Axial Leads

-10% to +50% Tol

µF	V d.c.	16	25	40	63
1.0					8
1.5					8
2.2					8
3.3					8
4.7					8
6.8					9
10					9
15		7	7		9
22					10
33					10
47		7	7		10
68					12
100		8	8		12
150		8	9		12
220					24
330					28
470					34
680					36
1000					36
1500					55
2200					39

Electrolytic Can Type

High Ripple, IEC Grade 1, Low E.S.R.
Supplied complete with Vertical Fixing Clip

Cap	HR	µF	Volts	
2200	16V	1.4A @ 85°C	1.4A @ 50°C	166
4700	16V	2.8A	3.6A	184
10000	16V	5.8A	5.1A	172
22000	16V	9.0A	12.7A	246
2200	25V	1.3A	1.5A	175
4700	25V	4.8A	6.4A	201
10000	25V	8.0A	11.2A	264
22000	25V	12.8A	17.9A	428
1000	40V	0.8A	1.2A	168
2200	40V	2.4A	3.2A	188
4700	40V	5.6A	7.8A	231
10000	40V	9.2A	12.8A	367
1000	70V	1.8A	2.5A	190
2200	70V	4.8A	5.6A	235
4700	70V	7.5A	10.5A	376
1000	100V	4.0A	5.6A	222
2200	100V	7.8A	10.9A	346

Miniature Low Value

Polystyrene, Axial, -1% Tol, > 63V D.C. Wkg
Ceramic Plate, Low K, 1.8pF-8.2pF, > 25pF Tol, 10 to 33pF -2% Tol, 100V D.C. Wkg
Ceramic Plate, Radial, Med K, > 10% Tol, 100V D.C. Wkg
Ceramic Plate, Radial, High K, > 20% to +50% Tol, 63V D.C. Wkg

Order Code	Cap 424	Cap 632	Cap 630	Cap 629	Cap 424	Cap 632	Cap 630	Cap 629	Cap 424	Cap 632	Cap 630	Cap 629
100	16	6	5	5	10	16	6	5	10	16	6	5
120	18	8	8	8	12	18	8	8	12	18	8	8
150	18	8	8	8	15	18	8	8	15	18	8	8
180	18	8	8	8	18	18	8	8	18	18	8	8
220	18	8	8	8	22	18	8	8	22	18	8	8
270	18	8	8	8	27	18	8	8	27	18	8	8
330	18	8	8	8	33	18	8	8	33	18	8	8
390	18	8	8	8	39	18	8	8	39	18	8	8
470	18	8	8	8	47	18	8	8	47	18	8	8
56	10	5	5	5	56	10	5	5	56	10	5	5
68	10	5	5	5	68	10	5	5	68	10	5	5
82	10	5	5	5	82	10	5	5	82	10	5	5
100	10	5	5	5	100	10	5	5	100	10	5	5
120	10	5	5	5	120	10	5	5	120	10	5	5
150	10	5	5	5	150	10	5	5	150	10	5	5
180	10	5	5	5	180	10	5	5	180	10	5	5
220	10	5	5	5	220	10	5	5	220	10	5	5
270	10	5	5	5	270	10	5	5	270	10	5	5
330	10	5	5	5	330	10	5	5	330	10	5	5
390	10	5	5	5	390	10	5	5	390	10	5	5
470	10	5	5	5	470	10	5	5	470	10	5	5
56	10	5	5	5	56	10	5	5	56	10	5	5
68	10	5	5	5	68	10	5	5	68	10	5	5
82	10	5	5	5	82	10	5	5	82	10	5	5
100	10	5	5	5	100	10	5	5	100	10	5	5
120	10	5	5	5	120	10	5	5	120	10	5	5
150	10	5	5	5	150	10	5	5	150	10	5	5
180	10	5	5	5	180	10	5	5	180	10	5	5
220	10	5	5	5	220	10	5	5	220	10	5	5
270	10	5	5	5	270	10	5	5	270	10	5	5
330	10	5	5	5	330	10	5	5	330	10	5	5
390	10	5	5	5	390	10	5	5	390	10	5	5
470	10	5	5	5	470	10	5	5	470	10	5	5
560	10	5	5	5	560	10	5	5	560	10	5	5
680	10	5	5	5	680	10	5	5	680	10	5	5
820	10	5	5	5	820	10	5	5	820	10	5	5
1000	10	5	5	5	1000	10	5	5	1000	10	5	5
1200	10	5	5	5	1200	10	5	5	1200	10	5	5
1500	10	5	5	5	1500	10	5	5	1500	10	5	5
1800	10	5	5	5	1800	10	5	5	1800	10	5	5
2200	10	5	5	5	2200	10	5	5	2200	10	5	5
2700	10	5	5	5	2700	10	5	5	2700	10	5	5
3300	10	5	5	5	3300	10	5	5	3300	10	5	5
3900	10	5	5	5	3900	10	5	5	3900	10	5	5
4700	10	5	5	5	4700	10	5	5	4700	10	5	5
5600	10	5	5	5	5600	10	5	5	5600	10	5	5
6800	10	5	5	5	6800	10	5	5	6800	10	5	5
8200	10	5	5	5	8200	10	5	5	8200	10	5	5

Tantalum Bead

20% Tol

µF	V d.c.	3.15	6.3	10	18	25	36
0.1							9
0.15							9
0.22							9
0.33							9
0.47							9
0.68							9
1							10
1.5							10
2.2							11
3.3							11
4.7							14
6.8							15
10							16
15							20
22							20
33							20
47							20
68							20
100							20

Electrolytic Radial Leads

-10% to +50% Tol

µF	V d.c.	6.3	10	18	25	36	40	50	63
0.1									6
0.15									6
0.22									6
0.33									6
0.47									6
0.68									6
1									6
1.5									6
2.2									6
3.3									6
4.7									6
6.8									6
10									6
15									6
22									6
33									6
47									6
68									6
100									6
150									6
220									6

Polyester Radial Leads

Dipped Type, -20% Tol, > 250V D.C. Wkg, C280/352 Style
Moulded Type, -10% Tol, > 100V D.C. Wkg, 10.2mm Pitch Centres
Moulded Type, -10% Tol, > 100V D.C. Wkg, 7.6mm Pitch Centres

µF	352	360	PHE280	µF	352	360	PHE280
.001	5	6	6	1	6	8	9
.0015	5	6	6	1.5	7	9	9
.0022	5	6	6	2.2	8	10	10
.0033	5	6	6	3.3	10	10	10
.0047	5	6	6	4.7	12	12	12
.0068	5	6	6	6.8	15	15	15
.01	5	6	6	10	15	15	15
.015	5	6	6	15	15	15	15
.022	5	6	6	2.2	32	32	32
.033	5	6	6	3.3	32	32	32
.047	5	6	6	4.7	32	32	32
.068	5	6	6	6.8	32	32	32
.1	5	6	6	10	32	32	32
.15	5	6	6	15	32	32	32
.22	5	6	6	2.2	32	32	32
.33	5	6	6	3.3	32	32	32
.47	5	6	6	4.7	32	32	32
.68	5	6	6	6.8	32	32	32
1	5	6	6	10	32	32	32

Trimmers

250V D.C. Wkg, Film Dielectric, Miniature

Order Code	500V D.C. Wkg, C004 EA Tubular Type
1.4 - 1.0pF	19
2 - 8pF	19
2 - 20pF	21
5.5 - 50pF	29
Cap 808 A	8 - 3.8pF
Cap 808 B	8 - 6.8pF
Cap 808 C	1 - 13pF
Cap 808 D	1.7 - 19.7
Cap 802 A	46
Cap 802 B	48
Cap 802 C	61
Cap 802 D	62

CASES

Small Desk Console - Boss Industrial Mouldings

Slope Front Console, Recessed Top
ABS Base, C/W Brass Bushes, In Orange
1mm Aluminium Top Panel Finished Grey

Order Code	Case BIM1005 OR	Case BIM1006 OR
W161 D96 H39 (57)	185	
W215 D130 H47 (73)	268	

Plastic Boxes - Boss Industrial Mouldings

Moulded Box and Close Fitting Flanged Lid
ABS Box, C/W Brass Bushes, and Lid In Orange

Order Code	Case BIM2005 OR	Case BIM2006 OR
L112 W82 D31	87	
L150 W80 D50	115	
L190 W110 D80	195	

VERO ELECTRONICS PRODUCTS

2.5" x 5" 1" pitch Veroboard	59	VERO 21069J
3.75" x 6" 1" pitch Veroboard	66	VERO 21072D
2.5" x 11" 1" pitch Veroboard (S)	70/Pack	VERO 21076C
3.75" x 9" 1" pitch Plain Board	66	VERO 21078E
3.82" x 2.9" 1" pitch V-Q-DIP Board	111	VERO 21084E
Spot Face Cutter	59	VERO 21019A
Pin Insertion Tool for .040 type pin	122	VERO 21015F
D5 Pins, D40 (100)	38/Pack	VERO 21087G
SS Pins, D40 (100)	38/Pack	VERO 21017H
6mm Board Standoff (100)	181/Pack	VERO 21321K
15mm Board Standoff (100)	215/Pack	VERO 21322G
19mm Board Standoff (100)	226/Pack	VERO 21323D
Verovis Kit (1 open, 2 wire, 25 comb)	375/Kit	VERO 21341D
Verovis Comb (100)	407/Pack	VERO 21339F
Verovis Wire (4)	728/Pack	VERO 21340G
Flip Top Box, Small, Black	192	VERO 21317D
Flip Top Box, Large, Black	250	VERO 21319J

HARDWARE

D.I.L. Sockets

Order Code	D.I.L. Sockets
8 Pin Low Profile Socket Tin	11
1	

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

GMT ELECTRONICS
Freepost
Birmingham B19 1BR
 TEL ORDERS WELCOME

DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed

5-15V 'B' Series, Up to 20MHz

7400 T.T.L.

HEF4000	14	HEF4048	100	HEF4514	250	N7400N	9	N7444N	83	N74122N	39	N74193N	80	N74LS28N	32	N74LS138N	85	N74LS263N	105
HEF4001	14	HEF4047	87	HEF4515	299	N7401N	11	N7445N	85	N74123N	37	N74194N	80	N74LS29N	16	N74LS139N	85	N74LS264N	104
HEF4002	14	HEF4049	28	HEF4516	90	N7402N	11	N7446AN	62	N74125N	32	N74195N	79	N74LS30N	24	N74LS140N	76	N74LS265N	107
HEF4006	95	HEF4050	28	HEF4517	382	N7403N	11	N7447AN	51	N74126N	32	N74196N	100	N74LS31N	32	N74LS141N	122	N74LS266N	106
HEF4007	14	HEF4061	60	HEF4518	69	N7404N	12	N7448AN	44	N74128N	44	N74199N	139	N74LS32N	24	N74LS142N	300	N74LS267N	100
HEF4008	80	HEF4062	72	HEF4519	85	N7405N	12	N7449N	13	N74132N	46	N74201N	160	N74LS33N	24	N74LS143N	80	N74LS268N	100
HEF4011	14	HEF4063	72	HEF4520	65	N7406N	12	N7450N	15	N74134N	46	N74202N	160	N74LS34N	24	N74LS144N	120	N74LS269N	100
HEF4012	14	HEF4066	37	HEF4521	168	N7407N	25	N7451N	13	N74135N	46	N74203N	160	N74LS35N	24	N74LS145N	80	N74LS270N	100
HEF4013	32	HEF4067	380	HEF4522	90	N7408N	13	N7452N	13	N74136N	46	N74204N	160	N74LS36N	24	N74LS146N	80	N74LS271N	100
HEF4014	84	HEF4068	14	HEF4523	120	N7409N	13	N7453N	13	N74137N	46	N74205N	160	N74LS37N	24	N74LS147N	80	N74LS272N	100
HEF4015	60	HEF4069	14	HEF4524	510	N7410N	11	N7454N	13	N74138N	46	N74206N	160	N74LS38N	24	N74LS148N	80	N74LS273N	100
HEF4016	35	HEF4070	14	HEF4525	110	N7411N	18	N7455N	13	N74139N	46	N74207N	160	N74LS39N	24	N74LS149N	80	N74LS274N	100
HEF4017	35	HEF4071	14	HEF4526	155	N7412N	17	N7456N	13	N74140N	83	N74208N	160	N74LS40N	24	N74LS150N	80	N74LS275N	100
HEF4018	65	HEF4072	16	HEF4527	78	N7413N	22	N7457N	23	N74141N	83	N74209N	160	N74LS41N	24	N74LS151N	80	N74LS276N	100
HEF4019	65	HEF4073	16	HEF4528	78	N7414N	22	N7458N	23	N74142N	83	N74210N	160	N74LS42N	24	N74LS152N	80	N74LS277N	100
HEF4020	88	HEF4075	16	HEF4529	380	N7415N	22	N7459N	23	N74143N	83	N74211N	160	N74LS43N	24	N74LS153N	80	N74LS278N	100
HEF4021	39	HEF4076	85	HEF4530	97	N7416N	22	N7460N	23	N74144N	83	N74212N	160	N74LS44N	24	N74LS154N	80	N74LS279N	100
HEF4022	82	HEF4077	14	HEF4531	119	N7417N	22	N7461N	23	N74145N	83	N74213N	160	N74LS45N	24	N74LS155N	80	N74LS280N	100
HEF4023	14	HEF4078	16	HEF4532	90	N7418N	26	N7462N	23	N74146N	83	N74214N	160	N74LS46N	24	N74LS156N	80	N74LS281N	100
HEF4024	45	HEF4081	16	HEF4533	73	N7419N	27	N7463N	23	N74147N	83	N74215N	160	N74LS47N	24	N74LS157N	80	N74LS282N	100
HEF4025	14	HEF4082	16	HEF4534	62	N7420N	22	N7464N	23	N74148N	83	N74216N	160	N74LS48N	24	N74LS158N	80	N74LS283N	100
HEF4027	32	HEF4085	64	HEF4535	64	N7421N	22	N7465N	23	N74149N	83	N74217N	160	N74LS49N	24	N74LS159N	80	N74LS284N	100
HEF4028	52	HEF4086	64	HEF4536	119	N7422N	22	N7466N	23	N74150N	83	N74218N	160	N74LS50N	24	N74LS160N	80	N74LS285N	100
HEF4029	80	HEF4093	50	HEF4537	119	N7423N	21	N7467N	23	N74151N	83	N74219N	160	N74LS51N	24	N74LS161N	80	N74LS286N	100
HEF4030	68	HEF4094	175	HEF4538	119	N7424N	21	N7468N	24	N74152N	83	N74220N	160	N74LS52N	24	N74LS162N	80	N74LS287N	100
HEF4031	26	HEF4104	166	HEF4539	119	N7425N	21	N7469N	24	N74153N	83	N74221N	160	N74LS53N	24	N74LS163N	80	N74LS288N	100
HEF4035	110	HEF4502	166	HEF4540	119	N7426N	22	N7470N	24	N74154N	83	N74222N	160	N74LS54N	24	N74LS164N	80	N74LS289N	100
HEF4040	68	HEF4505	57	HEF4541	119	N7427N	22	N7471N	24	N74155N	83	N74223N	160	N74LS55N	24	N74LS165N	80	N74LS290N	100
HEF4041	75	HEF4506	161	HEF4542	119	N7428N	22	N7472N	24	N74156N	83	N74224N	160	N74LS56N	24	N74LS166N	80	N74LS291N	100
HEF4042	54	HEF4510	70	HEF4543	119	N7429N	22	N7473N	24	N74157N	83	N74225N	160	N74LS57N	24	N74LS167N	80	N74LS292N	100
HEF4043	74	HEF4511	110	HEF4544	119	N7430N	21	N7474N	24	N74158N	83	N74226N	160	N74LS58N	24	N74LS168N	80	N74LS293N	100
HEF4044	84	HEF4512	98	HEF4545	117	N7431N	21	N7475N	24	N74159N	83	N74227N	160	N74LS59N	24	N74LS169N	80	N74LS294N	100
						N7432N	21	N7476N	24	N74160N	83	N74228N	160	N74LS60N	24	N74LS170N	80	N74LS295N	100
						N7433N	21	N7477N	24	N74161N	83	N74229N	160	N74LS61N	24	N74LS171N	80	N74LS296N	100
						N7434N	21	N7478N	24	N74162N	83	N74230N	160	N74LS62N	24	N74LS172N	80	N74LS297N	100
						N7435N	21	N7479N	24	N74163N	83	N74231N	160	N74LS63N	24	N74LS173N	80	N74LS298N	100
						N7436N	21	N7480N	24	N74164N	83	N74232N	160	N74LS64N	24	N74LS174N	80	N74LS299N	100
						N7437N	21	N7481N	24	N74165N	83	N74233N	160	N74LS65N	24	N74LS175N	80	N74LS300N	100
						N7438N	21	N7482N	24	N74166N	83	N74234N	160	N74LS66N	24	N74LS176N	80	N74LS301N	100
						N7439N	21	N7483N	24	N74167N	83	N74235N	160	N74LS67N	24	N74LS177N	80	N74LS302N	100
						N7440N	21	N7484N	24	N74168N	83	N74236N	160	N74LS68N	24	N74LS178N	80	N74LS303N	100
						N7441N	21	N7485N	24	N74169N	83	N74237N	160	N74LS69N	24	N74LS179N	80	N74LS304N	100
						N7442N	21	N7486N	24	N74170N	83	N74238N	160	N74LS70N	24	N74LS180N	80	N74LS305N	100
						N7443N	21	N7487N	24	N74171N	83	N74239N	160	N74LS71N	24	N74LS181N	80	N74LS306N	100
						N7444N	21	N7488N	24	N74172N	83	N74240N	160	N74LS72N	24	N74LS182N	80	N74LS307N	100
						N7445N	21	N7489N	24	N74173N	83	N74241N	160	N74LS73N	24	N74LS183N	80	N74LS308N	100
						N7446N	21	N7490N	24	N74174N	83	N74242N	160	N74LS74N	24	N74LS184N	80	N74LS309N	100
						N7447N	21	N7491N	24	N74175N	83	N74243N	160	N74LS75N	24	N74LS185N	80	N74LS310N	100
						N7448N	21	N7492N	24	N74176N	83	N74244N	160	N74LS76N	24	N74LS186N	80	N74LS311N	100
						N7449N	21	N7493N	24	N74177N	83	N74245N	160	N74LS77N	24	N74LS187N	80	N74LS312N	100
						N7450N	21	N7494N	24	N74178N	83	N74246N	160	N74LS78N	24	N74LS188N	80	N74LS313N	100
						N7451N	21	N7495N	24	N74179N	83	N74247N	160	N74LS79N	24	N74LS189N	80	N74LS314N	100
						N7452N	21	N7496N	24	N74180N	83	N74248N	160	N74LS80N	24	N74LS190N	80	N74LS315N	100
						N7453N	21	N7497N	24	N74181N	83	N74249N	160	N74LS81N	24	N74LS191N	80	N74LS316N	100
						N7454N	21	N7498N	24	N74182N	83	N74250N	160	N74LS82N	24	N74LS192N	80	N74LS317N	100
						N7455N	21	N7499N	24	N74183N	83	N74251N	160	N74LS83N	24	N74LS193N	80	N74LS318N	100
						N7456N	21	N7500N	24	N74184N	83	N74252N	160	N74LS84N	24	N74LS194N	80	N74LS319N	100
						N7457N	21	N7501N	24	N74185N	83	N74253N	160	N74LS85N	24	N74LS195N	80	N74LS320N	100
						N7458N	21	N7502N	24	N74186N	83	N74254N	160	N74LS86N	24	N74LS196N	80	N74LS321N	100
						N7459N	21	N7503N	24	N74187N	83	N74255N	160	N74LS87N	24	N74LS197N	80	N74LS322N	100
						N7460N	21	N7504N	24	N74188N	83	N74256N	160	N74LS88N	24	N74LS198N	80	N74LS323N	100
						N7461N	21	N7505N	24	N74189N	83	N74257N	160	N74LS89N	24	N74LS199N	80	N74LS324N	100
						N7462N	21	N7506N	24	N74190N	83	N74258N	160	N74LS90N	24	N74LS200N	80	N74LS325N	100
						N7463N	21	N7507N	24	N74191N	83	N74259N	160	N74LS91N	24	N74LS201N	80	N74LS326N	100
						N7464N	21	N7508N	24	N74192N	83	N74260N	160	N74LS92N	24	N74LS202N	80	N74LS327N	100
						N7465N	21	N7509N	24	N74193N	83	N74261N	160	N74LS93N	24	N74LS203N	80	N74LS328N	100
						N7466N	21	N7510N	24	N74194N	83	N74262N	160	N74LS94N	24	N74LS204N	80	N74LS329N	100
						N7467N	21	N7511N	24	N74195N	83	N74263N	160	N74LS95N	24	N74LS205N	80	N74LS330N	100
						N7468N	21												

EDITOR

F. E. BENNETT

ASSISTANT EDITOR

B. W. TERRELL B.Sc.

PRODUCTION EDITOR

D. G. BARRINGTON

TECHNICAL SUB-EDITOR

T. J. JOHNSON G8MGS

ART EDITOR

R. F. PALMER

ASSISTANT ART EDITOR

P. A. LOATES

TECHNICAL ILLUSTRATOR

D. J. GOODING

EDITORIAL OFFICES

Kings Reach Tower,
Stamford Street,
London SE1 9LS
Phone: 01-261 6873

ADVERTISEMENT MANAGER

V. PIERI
Phone: 01-261 6727

REPRESENTATIVE

N. BELLWOOD
Phone: 01-261 6727

CLASSIFIED MANAGER

C. R. BROWN
Phone: 01-261 5762

MAKE-UP AND COPY DEPARTMENT

Phone 01-261 6618

ADVERTISEMENT OFFICES

Kings Reach Tower
Stamford Street,
London SE1 9LS

Projects... Theory...

and Popular Features ...

Remember the boy who cried "Wolf"? Burglar alarms ring continuously in the High Street and passers by go about their business without turning a head. Frequent false alarms due to malfunctioning of the equipment have conditioned people to disregard all alarms they hear. Despite this they serve a purpose since in the case of a genuine alarm the initial sounding-off must have caused the would-be intruders to beat a hasty retreat.

There are of course other more subtle and sometimes more effective ways of deploying electrics and electronics to safeguard premises and homes than through the triggering of a strident externally-sited bell or siren. The arrangements possible for detecting a break-in are pretty well unlimited. So anyone can have an intruder detection system tailored to suit his own needs and circumstances. The degree of complexity of design and/or of devices used can vary considerably: the whole gamut of the electronic armoury can be brought into play if money is no object.


On a more practical and reasonable level, very effective intruder alarm systems can be built and installed by any handyman, using standard components and without excessive cost. Such an example is presented in this issue.

Most importantly, our *Intruder Alarm* is immune from power failures, and allows the alarm device (sound or visual as desired) to be situated wherever required.

It is a sad reflection upon the times, that this project could be the most important and urgent undertaking for today's householder.

An apology to disco fans and others. Unfortunately it has not proved possible to include the Xenon Strobe in this issue, as announced last month.

That most widely used of all tools, the humble screwdriver, is in its time applied to many a purpose entirely unconnected with screw heads. But there is no doubt about the *intended* dual purpose of our Free Gift to readers this month, for it is a useful pocket screwdriver with the bonus of a built-in wire stripper. This straight away gives it a head start on other screwdrivers for electronics constructors.

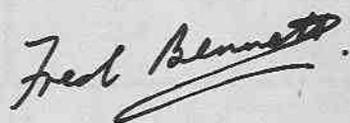

Our June issue will be published on Friday, May 18. See page 275 for details.


Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

Telephone enquiries should be limited to those requiring only a brief reply. We cannot undertake to engage in discussions on the telephone, technical or otherwise.

Component Supplies

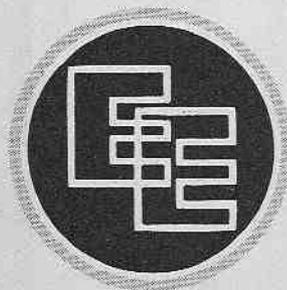Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.



Everyday ELECTRONICS

VOL. 8 NO. 5

MAY 1979

CONSTRUCTIONALS

INTRUDER ALARM	<i>Adds extra security to your home by F. G. Rayer</i>	266
ELECTRONIC DICE	<i>For games requiring one or two dice by P. Leah</i>	272
EE LABCENTRE	<i>Part 3: Interwiring and component drawer construction by R. W. Coles and B. Cullen</i>	280
SHORT WAVE CONVERTER	<i>Open up a new world of listening on your m.w. radio by R. A. Penfold</i>	288
THERMOSTAT for PHOTOGRAPHIC SOLUTIONS	<i>For consistent prints by R. A. Penfold</i>	294
EE2020 TUNER AMPLIFIER	<i>Part 6: Concluding article—Alignment and testing by E. A. Rule</i>	306

GENERAL FEATURES


EDITORIAL		264
BOOK REVIEWS	<i>A selection of recent releases</i>	270
FOR YOUR ENTERTAINMENT	<i>The art of audio reviewing by Adrian Hope</i>	271
DOING IT DIGITALLY	<i>Part 8: Timing systems with the 555 i.c. by O. N. Bishop</i>	276
JACK PLUG AND FAMILY	<i>Cartoon by Doug Baker</i>	279
COUNTER INTELLIGENCE	<i>A retailer comments by Paul Young</i>	282
SQUARE ONE	<i>Beginners page. The Transistor</i>	283
MICROPROCESSOR BASICS	<i>Part 3: ROMS, PROMS, EPROMS, and RAMS by R. W. Coles</i>	284
SHOP TALK	<i>Guidance on component buying by Dave Barrington</i>	287
CROSSWORD No. 15	<i>by D. P. Newton</i>	287
EVERYDAY NEWS	<i>What's happening in the world of electronics</i>	292
PROFESSOR ERNEST EVERSURE	<i>The Extraordinary Experiments of. by Anthony J. Bassett</i>	302
RUMMAGING AROUND	<i>Money-saving ideas for the constructor by Keith Cadbury</i>	310
RADIO WORLD	<i>A commentary by Pat Hawker</i>	312


Back issues of EVERYDAY ELECTRONICS June 1977 onwards (October to December 1977, January to March 1978 NOT available) are available worldwide at a cost of 60p per copy inclusive of postage and packing. Orders and remittance should be sent to: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

Binders for Volumes 1 to 8 (state which) are available from the above address for £2.85 inclusive of postage and packing. Subscriptions (for one year)—UK: £8.50. Overseas: £9.50.


© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.

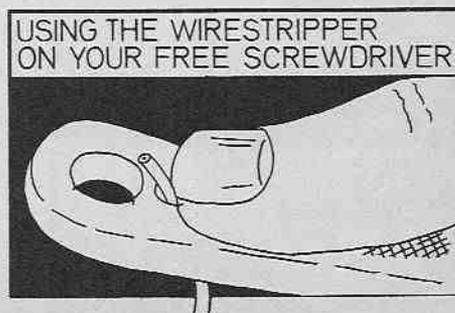All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



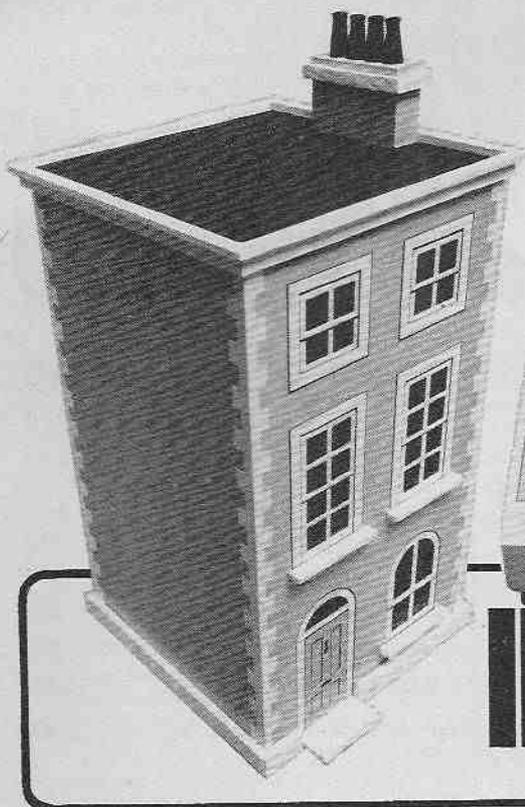

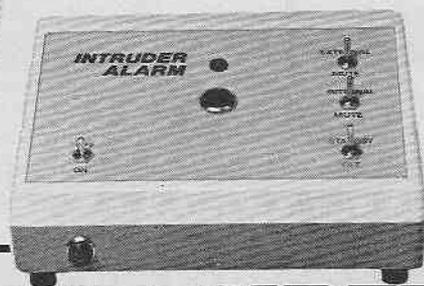**A RELIABLE SYSTEM FOR THE HOME
— MAINS OPERATED WITH AUTOMATIC
BATTERY BACK-UP**



INTRUDER ALARM

By F. G. Rayer

ANYONE who has had the unfortunate experience of being burgled will certainly appreciate the usefulness of the Intruder Alarm described here.

When all entrances into the house e.g. doors, windows, fanlights etc. are connected via switches into one or both of the "loops" in this system, the alarm will be activated and alert you instantly if any of these entrances are opened. Closing the door or window afterwards will not cause the alarm to be turned off. This can only be done at the unit.

The Intruder Alarm is powered by a mains derived supply that automatically switches over to an internal battery should the mains supply fail or be interrupted. A remote alarm facility is included that can be muted by a switch on the front panel.

COMPONENTS
approximate
COST £13 excluding
loop switches

CIRCUIT DESCRIPTION

The circuit diagram of the Intruder Alarm is shown in Fig. 1.

Mains voltage enters the unit via FS1 and S1 and is placed across the primary winding of T1; 12 volts a.c. is produced across the central-tapped secondary. Full-wave rectification is achieved by diodes D1 and D2 producing a d.c. level of approximately 7.8 volts across smoothing capacitor C1.

Under normal conditions, all the switches in the parallel loop are open, and all those in the series loop closed. The voltage on the gate of CSR1 is thus very low, being equal to the voltage drop across R4 (100 ohms) in series with D4, R2 and R1. Thus the gate voltage is insufficient to turn on CSR1.

If now any of the switches in the series loop are opened, the gate voltage rises and causes CSR1 to turn on bringing the anode down to almost 0V. With S3 and S4 closed, the full supply voltage is placed across WD1 and RLA operating both; also D4 is illuminated. If S3 is opened the internal alarm is muted; S4 takes the relay out of circuit, its contacts open and mute the external alarm, WD2 and/or LP2.

Consider all the series loop switches closed. If now a switch in the parallel loop is closed, the voltage at CSR1 gate is equal to about 1.2 volts [$V_{supply} \times R3 / (R4 + R30)$] which is high enough for CSR1 to turn on and sound the alarms as before.

Once the thyristor has turned on, it cannot be turned off again by closing (or opening) the loop switches. It can only be turned off at the unit by setting both S1 and S2 to OFF.

POWER SUPPLIES

When operating on the mains derived power supply there is no drain on B1 with S2 in the STANDBY position since D3 is reverse biased (7.8 volts on cathode and 6 volts on anode).

Power for the external bell WD2 and/or lamp LP2 is obtained through relay contacts RLA1 when the relay coil is energised.

If a high power external alarm is required, the relay contacts should be disconnected from the circuit and taken to sockets on the back panel for connection to the external alarm and its own power

Front Cover: Birdcage by courtesy of Harrods of Knightsbridge.

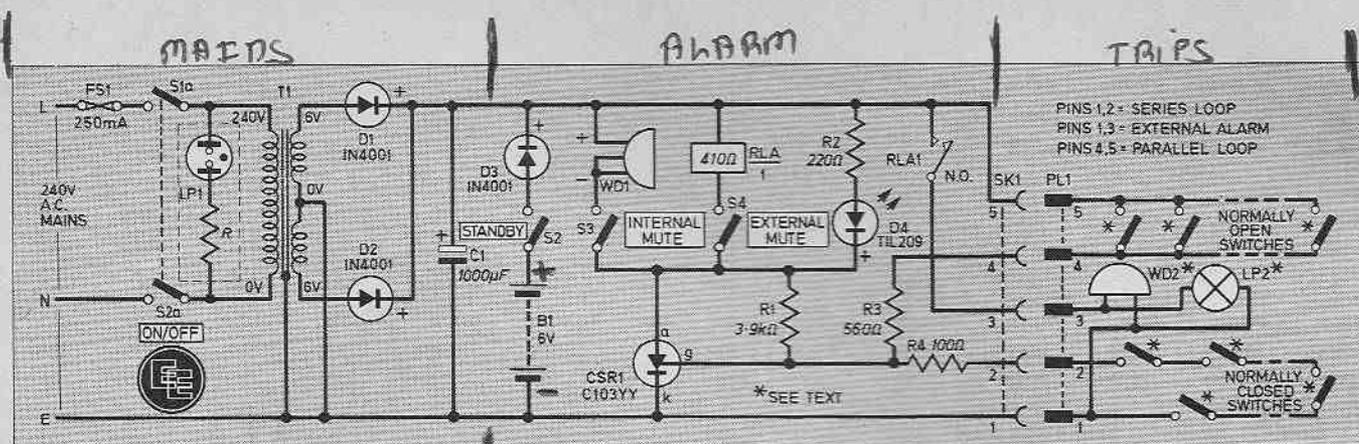


Fig. 1. The complete circuit diagram of the Intruder Alarm.

supply which may be mains or battery operated. With the relay specified, the contacts can handle mains voltages at currents up to 5A and d.c. power up to 150 watts.

Under "no alarm" conditions D4 will be off (completely dark) when S4 is closed. With S4 open, D4 will be lit very dimly, warning the user that the external alarm has been muted.

The inclusion of the MUTE switches allows the silent detection of an intruder by means of the l.e.d. and are useful when setting up.

Removal of PL1 from SK1, accidentally or deliberately will activate the internal alarm since the series loop will have been broken.

LOOP SWITCHES

The switches connected in the parallel loop must be normally open push-to-break, release-to-make types if used in the closed position and push-to-make, release-to-break in the open position. Various types can be used such as push-button, microswitch, reed/magnet and pressure mats that close when stepped on. See Fig. 2.

The latter are preferred when "fitting" is to be kept to a minimum. These are to be placed at strategic points around the house such as below windows, close to external doors, foot of stairways. In all cases it is recommended they should be sited below carpets/rugs for security reasons.

OPERATING DEVICES

Home made switches can be devised from strips of metal with touch contact screws depressed by weight or by opening of windows of the sash variety.

Switches in the series loop must be of the normally closed type and could be push-button, microswitches, reed/magnet, foil conductors on a door or window which will be fractured if the glass is broken.


Fine gauge wire can also be used. This is most suitable and cheap for windows that are seldom opened and can be fitted across windows/frames so as to break the wire when the window is opened.

Pressure mats can also be obtained that have four leads. Here two form a continuous circuit

which can be wired in the series loop and activate the alarm if cut.

Microswitches are particularly suitable due to their small size; most are of the changeover type allowing them to be fitted in the series or parallel loops.

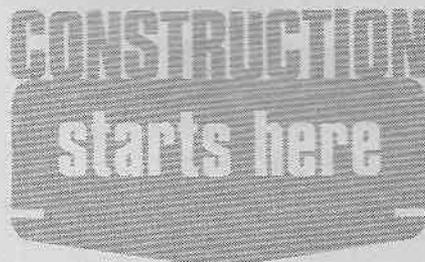If the alarm is required to "protect" an empty house (e.g. owners on holiday) a keyswitch wired in parallel with the series switch at door of exit is required. In the unlocked position the keyswitch should short-circuit the loop switch. The remote alarm should of course be sited outside the house.



The prototype was constructed in a Verobox type 75-1798K which has a sloping top panel producing an attractive unit.

Some of the components are mounted on a piece of 0.1 inch

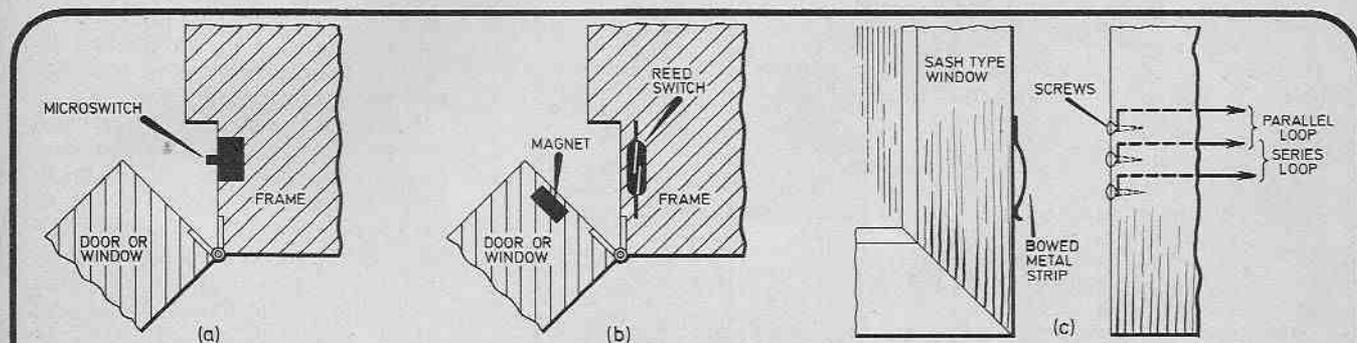


Fig. 2. Fitting of loop switches to doors and windows: (a) the microswitch is positioned so that it is operated when the door opens/closes; (b) using a reed switch and magnet. When the door closes the magnet causes the switch to close (suitable for series loop); (c) a home-made switch constructed from brass plate and screws. A dual type is shown for connection in both parallel and series loops.


matrix stripboard size 27 strips x 32 holes. The layout of the components on the topside is shown in Fig. 3. There are only two breaks to be made on the underside at locations C13 and C18. If board fixings other than those specified are used, isolation breaks may be necessary around the fixing holes.

Assemble and solder all the components to the board paying attention to polarities of C1, D1, D2 and D3. Solder all flying leads to the board, of sufficient length to reach the other components in their final positions.

POWER SUPPLY

The transformer, neon, fuseholder and mains cable entry are accommodated in the lower section of the case. Drill and fix these components in position and wire up. Also connect S1 and check that the power supply is functioning; approximately 12 volts a.c. should be measured across T1 secondary. With one test probe connected to the earthing solder tag, 6 volts a.c. should be measured when the other probe is connected in turn to each "6V" tag of T1 secondary.

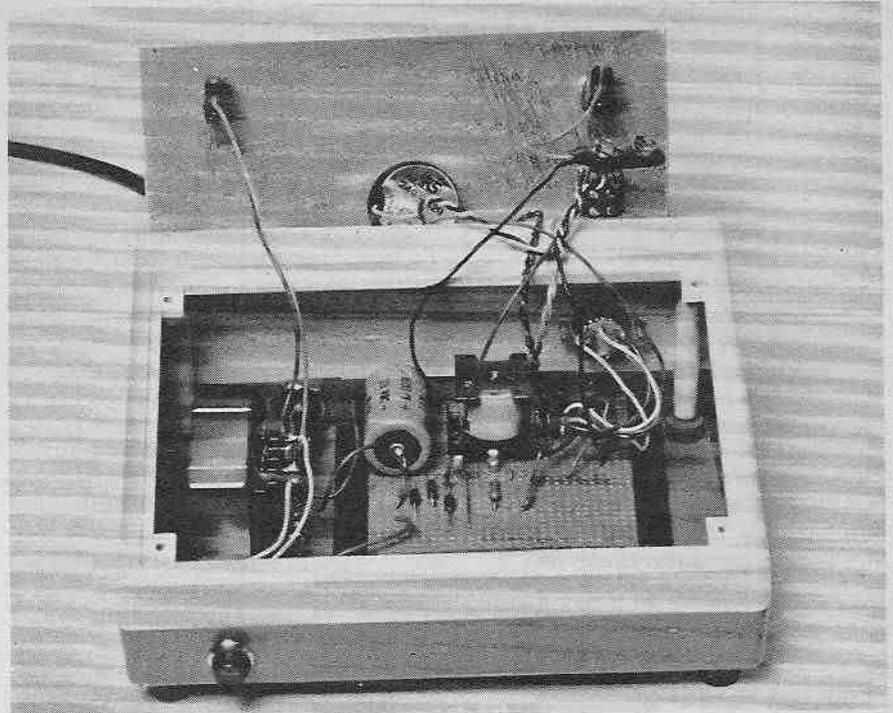Fit the self adhesive board mounts, push the board in place and then wire up according to Fig. 3.



The complete prototype with lid removed.

Next the top panel and upper half of case should be prepared to accept the switches, socket etc. Fit SK1 and secure the top half of case to its other section and wire to SK1.

Connect the switches, WD1 and D4 to the appropriate flying leads, wire in the battery connector and finally secure to the top panel. The unit is now ready for testing.

A multi-way terminal block is a suitable connector for interconnecting unit to its loops and external alarm and allows other loops to be readily added. The DIN plug/socket arrangement allows instant removal of the unit from the system should this prove necessary.

Six-cored cable is required for PL1 to terminal block, see Fig. 4. The length of this cable is determined by the siting of the concealed terminal block.

COMPONENTS

Resistors

R1 3.9k Ω
R2 220 Ω
R3 560 Ω
R4 100 Ω

All $\frac{1}{4}$ watt carbon $\pm 10\%$

Capacitor

C1 1000 μ F 10V elect.

Semiconductors

D1 to D3 1N4001 or similar silicon diode (3 off)
D4 TIL209 red l.e.d. with bush
CSR1 C103YY or similar thyristor

Miscellaneous

T1 mains primary/6.0-6V 250mA secondary
S1 to S4 miniature on/off toggle switches (4 off)
FS1 250mA 20mm including panel fuseholder
LP1 mains panel mounting neon
LP2 6V 100mA lamp (optional)
SK1 5-pin DIN socket chassis mounting
PL1 5-pin DIN plug to suit SK1
RLA miniature open relay, 410 ohm coil resistance with one set normally open contacts
WD1 miniature solid-state buzzer or similar
WD2 low voltage bell or other alarm (optional)
B1 9V type PP6
Stripboard: 0.1 inch matrix 27 strips x 32 holes; Verobox type 75-1798K self adhesive board mounts; sleeved grommet; mains cable; 4BA fixings; bell wire and switches for loops; PP6 battery connector; terminal block; six-cored cable.

See
**Shop
Talk**


page 287

TESTING

Thoroughly check out your wiring and when completely satisfied proceed as follows. Set S3 and S4 to MUTE and S2 to STANDBY. The l.e.d. should light brightly. Switch S4. The relay should be heard to pull in. Switch S3 and the internal buzzer should emit a tone. Set S2 to OFF. The buzzer should be quiet and the l.e.d. extinguish.

Now plug into the mains and switch on at S1. The internal buzzer should sound and the l.e.d. light along with LP1. Set S2 to STANDBY and switch off at S1. The only difference to be noticed is that LP1 goes out, WD1 pitch is slightly reduced and D4 is less bright. Set S2 to OFF.

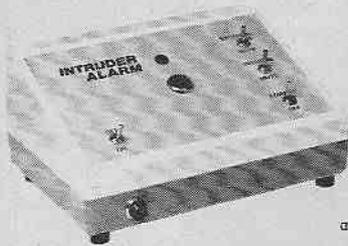Insert PL1 in SK1 and put a shorting link between 1 and 2 on terminal block and set S2 to STANDBY. The alarm should not



INTRUDER ALARM

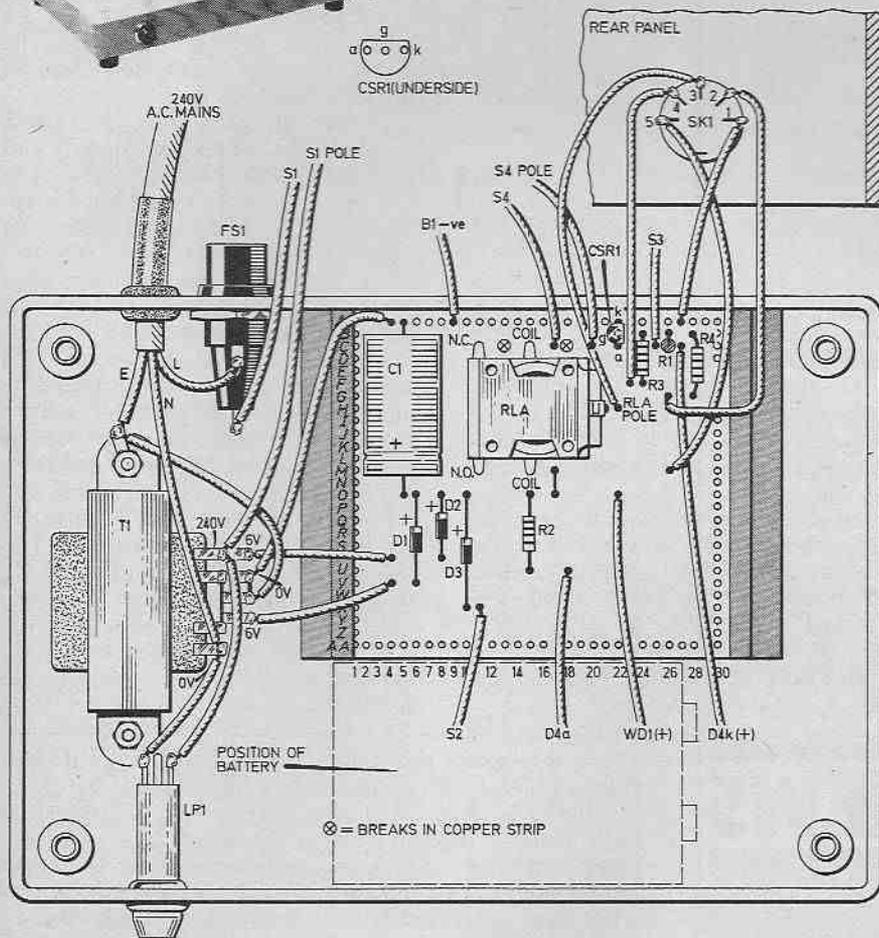


Fig. 3. Layout of the components on the stripboard and wiring-up details. Below shows positions of top-panel controls and wiring information. Note that the copper strip on the board underside is to be broken at two points, C13 and C18.


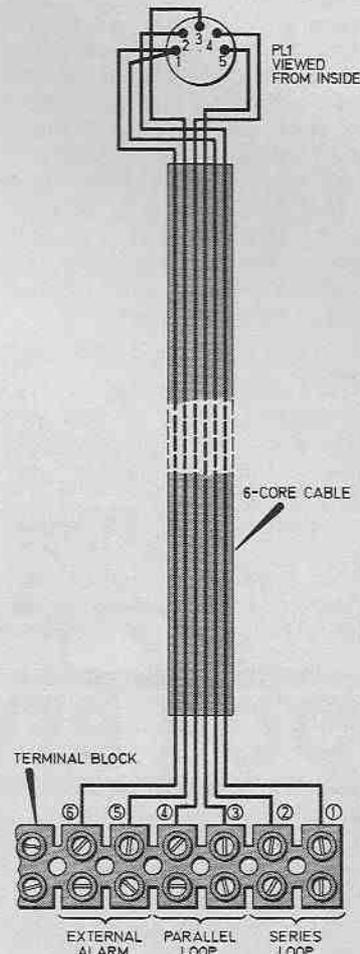
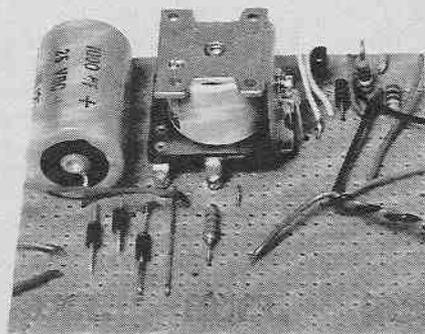


Fig. 4. Wiring up a terminal block to a 5-pin DIN socket.

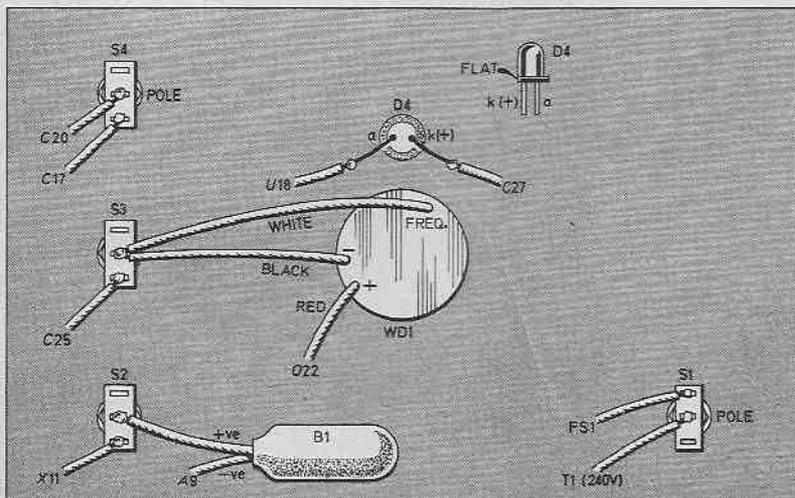

The prototype component board shown in close-up.

sound. With S4 in the MUTE position the l.e.d. may glow dimly (not important). In its other position, the l.e.d. should be dark.

Connect the remote bell (or lamp) to positions 5 and 6 on the terminal block. Instantaneously short positions 3 and 4 on the terminal block. Both alarms should sound and the l.e.d. be on. Test EXTERNAL MUTE. Switch S2 to OFF and then return to STANDBY. The alarms and l.e.d. will turn off. Remove the shorting link between 1 and 2. Both alarms should sound and the l.e.d. light. Set S2 to OFF.

If all the above results have been obtained, the unit is complete and ready for use. It only remains to lay the two loops, remote alarm wiring and connect this to the terminal block.

IN USE

The final position of the unit will be a matter of individual preference but the bedside may be the favourite choice.

The application of the remote alarm will also vary. In some instances it would be used to alert everybody in the household including the intruder with the intention

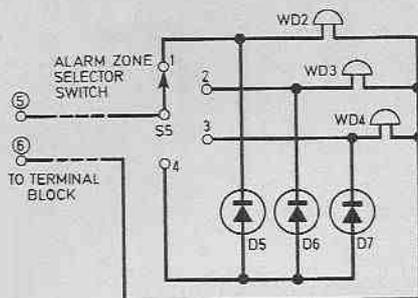


Fig. 5. Circuit for choice of remote alarm.

of scaring him away. Alternatively a local "soft" alarm may be employed so as to be inaudible to the intruder.

Also, the sounding of the external alarm can be left to the user by leaving S4 in the MUTE position and operating this if required after the internal buzzer has sounded. During daytime, S4 would be in the non-MUTE position so then the external alarm is the primary means of warning.

In larger premises, it may be advisable to fit several remote alarms in parallel (current output of power supply may need up-rating) or be able to switch any one of several depending on the room occupied at the time e.g. TV room, bathroom, kitchen, Fig. 5.

The rotary switch and diode arrangement allows a choice of remote alarm, any one at a time or all three at once. Suitable diodes are 1N4001.

It is advisable for reasons of security and tidiness, that wires from and forming the loops be hidden e.g. below floorboards or under carpets. Twin bell wire is suitable for both loops.

If only the parallel loop is used, the terminal block position 3 and 4 must be shorted by means of a link wire. This can quickly be removed should a series loop be added at a later stage.

Double-pole type switches may be used to produce series and parallel loops protection at certain places around the house. This would help confuse the intruder if he was on the lookout for wiring to switches with the intention of cutting parallel loops and bridging series connected switches.

Finally, the Intruder Alarm is not intended to be a substitute for locks, bolts, catches etc., but to act as a back-up for these conventional fittings. If these do not prevent the intruder's entrance, the alarm will tell you of his presence. □

BOOK REVIEWS

TELEVISION INTERFERENCE MANUAL

Author B. Priestley

Price £1.35

Size 210 x 150mm

Publisher Radio Society of Great Britain

ISBN 0 900612 45 2

THIS book, intended mainly for the radio amateur gives much valuable information on the often ticklish problem of TV interference.

It is a sad fact, that because the TV viewer might suffer from a brief burst of interference, the total blame is put upon the innocent local amateur down the road. But as the reader will discover after reading this book, this is not always the case. Indeed, it could well be, and nearly always is, due to a fault in the TV set, rather than the amateur station.

QUESTIONS & ANSWERS RADIO REPAIR

Author Les Lawry-Johns

Price £1.50

Size 165 x 110mm

Publisher The Butterworth Group

ISBN 0 408 003 677

THERE have been many books in the *Question and Answer* series, and no doubt there will be many more of these highly popular books. The essential

aim is to present the reader with a question, and then follow this up with an answer of great detail.

The book is divided into a number of chapters, each leading logically on to the next. For example: power supplies, i.f. stages, audio amplifiers. Thus the reader is taken from first principles (it even tells you what tools are required!) to complex fault finding.

One chapter is devoted exclusively to car radios and gives much essential information on their repair. One aspect of repair which is often overlooked by the beginner is the trick of heating and/or cooling a component to find an intermittent fault.

ELECTRONIC PROJECTS IN THE HOME

Author: Owen Bishop

Price £2.25 Paperback

Size 215 x 135mm 88pages


Publisher Newnes Technical Books

ISBN 0 408 00346 4

A RECIPE for yoghurt is an unexpected "find" in this book of useful electronic projects. The Yoghurt Maker, by the way, is quite ingenious and uses the heat produced by the control circuit components to maintain the interior of the container at the required 35 degrees C.

A Flashing Messenger and a Decorative Star for the Christmas Tree are two unusual and novel ideas that add further interest to this collection of simple circuits. The remaining ten projects have a more familiar ring about them: moisture detector, temperature-operated alarm, light-operated switch and so on.

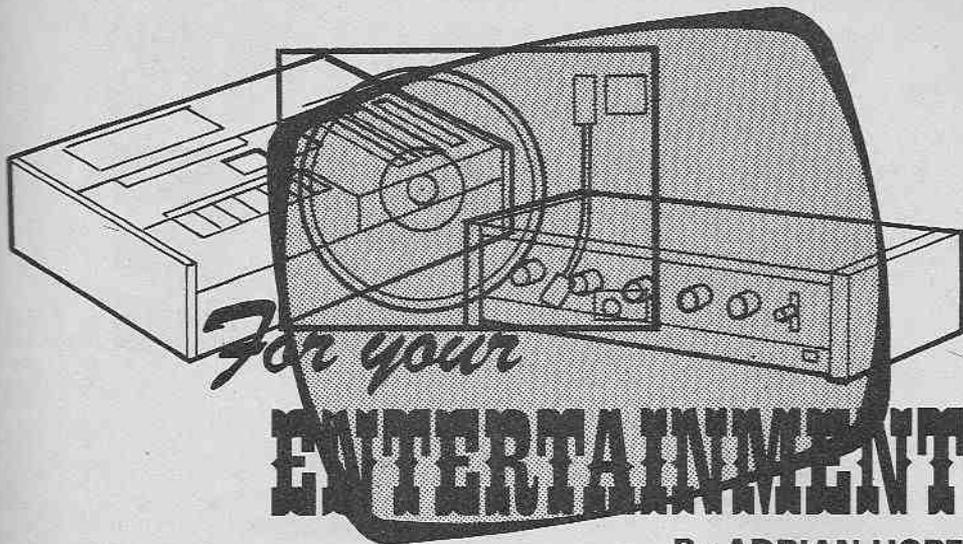Each project is well described, with a component list and stripboard layout. An excellent handy reference source for the constructor by the author of the highly acclaimed series "Doing It Digitally".



By ADRIAN HOPE

Audio Reporting

The audio industry and press is currently engaged in publicly tearing itself apart in an effort to agree on who should review equipment and how. So the main bones of contention are now well known, even if there are as yet no answers.

Should sophisticated electronic equipment be reviewed by measurement or by ear—or by both? Is it reasonable for a lone reviewer to appraise the performance of a product developed and produced by a large company using money-no-object test techniques? Should reviewers test a carefully checked sample provided by the manufacturer and thus perhaps not representative of what appears in the shops? Or should the reviewer risk condemning a product on the strength of one faulty sample that has reached the open market and been bought for review unbeknown to the manufacturer?

Dubious Practice

And so it goes on, and on, and on. Meanwhile, these pages, being out of the mainstream of audio and hi fi, seem an ideal place to mention a couple of dubious practices that have crept into audio journalism over recent years.

Very reasonably reviewers have objected to the use of their review comments in advertising material produced by the manufacturer, either because it is lifted out of context in the manner of a film or theatre review "so funny it's pathetic" in a theatre critic's review becomes "so funny" in the theatre's advertising) or because lengthy reviews are reproduced in their entirety without the original writer's permission. Understandably reviewers have clamped down on this practice, attaching tight strings to

permission to reproduce and asking an additional reproduction fee.

There is no evidence that anyone has deliberately praised a product simply to better their chances of selling a quote for subsequent reproduction, but some remarkably bland reviews have appeared. I even noticed excerpts of one review quoted in an advertisement that appeared in the *same* issue of the monthly hi fi magazine that carried the review. Doubtless there was nothing whatsoever dishonest about this coincidence, but it hardly engenders the confidence of thinking people in the independency of the reviewer.

Consult or Review

Although some reviewers somehow manage to finance a respectable laboratory almost entirely on the strength of reviews commissioned for magazine publication (usually by working very hard, very long hours) many find it necessary also to work on a consultancy basis for the manufacturers. Viewed from a distance, and in pure consumer terms, this may seem undesirable. But it is now, for better or for worse, an integral, and possibly essential part of audio reviewing.

The fee paid by the firms, either on a retainer or occasional consultancy basis, can be fat compared to those which magazines can afford to offer most contributors. Consultancy fees can thus go to subsidise the purchase of laboratory equipment which then enables the reviewer to conduct a more thorough appraisal of equipment for the magazines.

Unwritten rules over the years have emerged. First and foremost has been the tacit assumption that it is undesirable for one and the same person to both consult on a product and then review it in print.

Consultancy on a product can take many forms, from helping out a small manufacturer who is short on skill or equipment in one particular area to advising the importer of equipment from a vast Japanese company on the likely sales potential of a product, *vis à vis* the competition. But either way the reviewer is accepting hard cash from the manufacturer to advise.

Until recently no-one has suggested that it is ethically acceptable for anyone to act as a paid adviser on a product, then remove his consultant's hat, don his reviewers hat and appraise the same product for the benefit of the trade and consumer. *But this is now exactly what is happening, due largely to the move over recent years towards comparative reviewing.*

New Technology

There is also the additional problem that in some areas of technology the number of reviewers that are sufficiently skilled to appraise new products fairly is limited because to become skilled in any one area of fast moving technology may now be an almost full time job.

It is also argued that pure measurement consultancy will in no way prejudice a future review and that a volt is a volt, whether you measure it as a consultant or a reviewer. But the question then becomes, which volt to measure, how and when?

As hi fi technology becomes increasingly sophisticated, parameter compromises become essential and opinions diverge on the best and worse compromises to adopt. For instance product price may be no object or it may be taken into consideration.

Conflict of Interest


The issue here is not so much whether the public is at risk. There is no evidence that anyone functioning both as a reviewer and consultant has ever knowingly misled anyone. But no mortal is infallible.

What matters most of all is that the trade and public should recognise the situation for what it is and form their own opinion on its desirability or otherwise. This necessitates a clear, bold and unambiguous declaration of interest on the part of any reviewer appraising a product on which he has also consulted.

Surely if a conflict of interest is innocuous there is nothing to be lost, and everything to be gained, from an open acknowledgement of the fact? You can't, as they say, have your cake and eat it.

ELECTRONIC DICE

By P. Leah

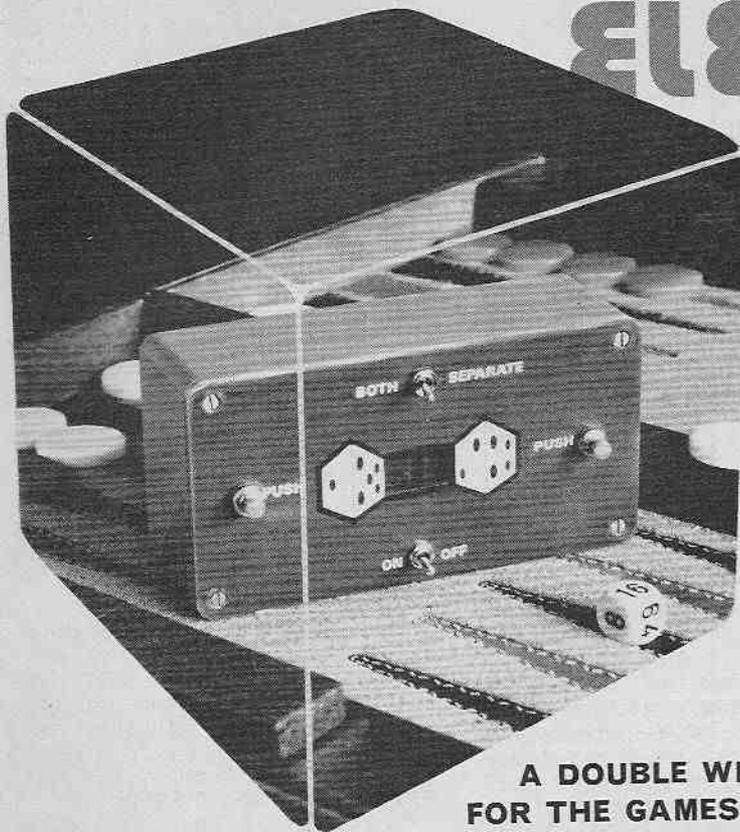

A DOUBLE WINNER FOR THE GAMES PERSON

THE Electronic Dice to be described here has two independent counters and displays which can be operated separately or together. This makes it ideal for games such as Monopoly and Backgammon which require two dice as well as games that require only one dice such as Snakes and Ladders and Ludo.

This particular design is ingenious in so far as it uses only a single four-bit binary up-down counter to directly interface to a BCD/seven-segment display decoder/driver without the need for complex gating.

TRUTH TABLE

The truth table of the complete counting sequence of the binary counter, and the required sequence to drive a display decoder over the range of numbers 1 to 6 is shown in Table 1.

It can be seen that the counting sequence over the range 9 to 14 is identical to the range 1 to 6 if we ignore the most significant digit, and replace this logical 1 with a logical 0.

If we continually preset the counter to 9 after it has counted up to 14, the counter will count

continuously over the range 9 to 14, which, when decoded, provides a display over the range 1 to 6.

CIRCUIT DESCRIPTION

The circuit diagram of the Electronic Dice is shown in Fig. 1.

The circuit can be split directly into the two identical circuits each comprising an oscillator made from two 2-input NOR gates (IC5), a 74C193 counter a 4511 decoder-driver and a seven-segment minitron display.

The Minitron display was chosen in preference to a l.e.d. display as each segment of the Minitron has

Table 1: Truth table for four digit binary counter

Decimal	Binary outputs			
	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

a resistance of about 600 ohms and hence can be driven directly from the 4511 decoder-driver without the need for current limiting resistors.

The 74C193 binary counter provides a carry output which appears as a logical 1 as soon as the counter has reached 15. This carry output is used to preset the counters to 9. Hence the counter will continuously count over the range 9 to 14 when a clock pulse train is connected, without the need for additional gates.

OSCILLATORS

The oscillators are connected in a feedback loop as shown with the values of R1 (or R4) and C2 (or C3) controlling the frequency of the oscillators. The oscillators will oscillate when pin 13 or pin 5 is connected to ground (0V). This is achieved by depressing switches S3 or S4.

Switch S2 ensures that the earth from either S3 or S4 is connected to both oscillators when switched on so that the oscillators operate together (BOTH) or only one of the oscillators operate while S2 is switched off when the oscillators will operate by only S3 or S4 (SEPARATE).

The oscillator outputs are connected directly to the count-up inputs of the two binary counters (IC1 and IC4 pin 5) which count over the range 9 to 14 when the oscillators are enabled. The carry output, pin 11 of each counter is connected back to their respective "load" outputs to ensure that the counters are preset to 9 on every carry output pulse.

Two capacitors C1 and C4 are necessary to extend the duration of the preset pulse and hence ensure that the counters have sufficient time to preset correctly. The three

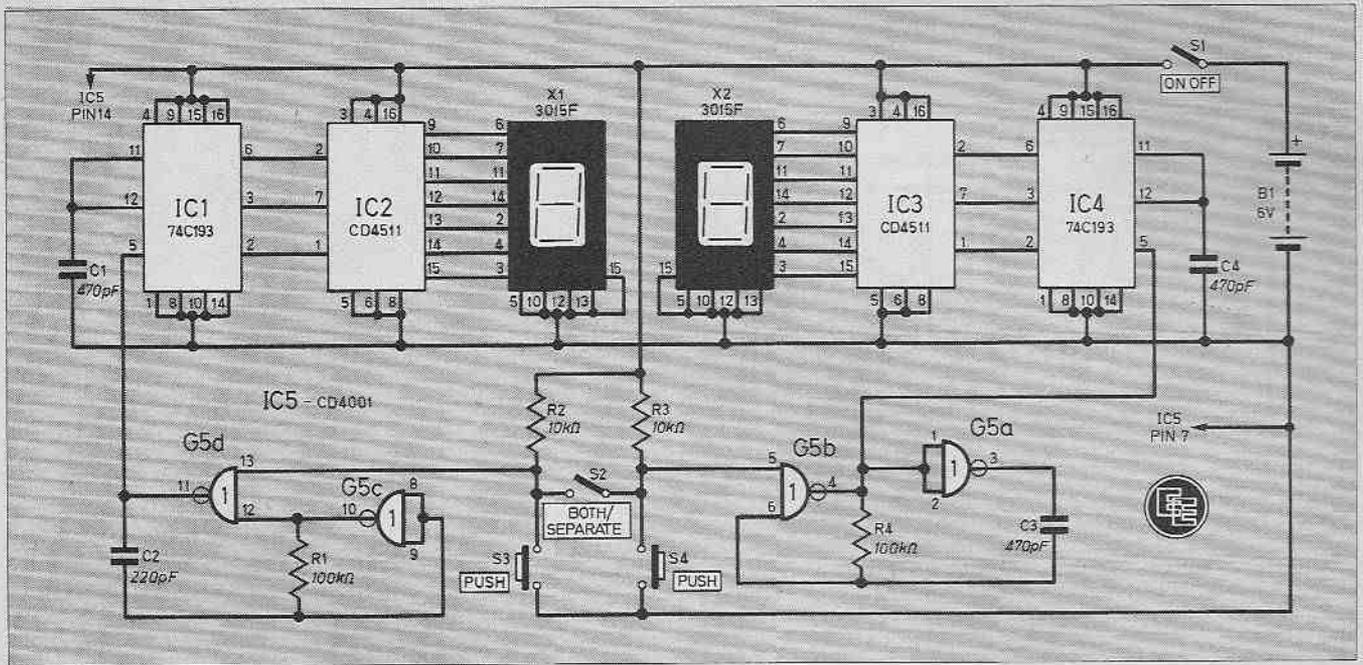


Fig. 1. The complete circuit diagram of the Electronic Dice.

least significant digits from the counters (pins 2, 3 and 6) are directly connected to the A, B, and C inputs of the decoder-drivers IC2 and IC3, while the D input (pin 6) is held at 0V. Hence the input to the decoder-drivers will be binary coded numbers 1 to 6. The decoder-driver outputs are directly connected to the Minitrons X1 and X2.

When the push buttons S3 and S4 are depressed, the display will appear to show number 8 because the display is changing so fast the eye cannot detect the changes. Only when the buttons are released will a number between 1 and 6 become clearly visible; S1 is the on-off switch which connects the battery to the circuit.

CLOCK SPEED

The random count is dependent on the length of time the push-button switches are depressed which connect the two clocks to the counters. The clocks count independently of each other at frequencies of 10kHz and 20kHz, so there is no possibility of cheating by depressing the push-buttons for a set period of time, since no-one could depress the switches for a time within an accuracy of one ten thousandth of a second!

The power consumption is very low, the majority of the load being the display. When segments of both digits are operating, this is

approximately 60mA, and therefore operated from four HP11 (1.5 volt) batteries. Hence the whole assembly is completely portable, enabling it to be mounted in a small plastic instrument case.



The author's unit uses a printed circuit board. A full-size master of this is shown in Fig. 2. This is viewed from the copper side. The black regions are the areas of copper to remain after etching.


The layout is not critical and if desired can be constructed on stripboard.

The p.c.b. is specially shaped along its two longer sides to accommodate the switches and allow the unit to comfortably fit inside a small case. This arrangement at the same time provides space for the four batteries to sit below the board in the specified case.

Prepare the printed circuit board in the usual way. The design is not too complicated and can easily be laid out using transfers and ink resist pen.

The layout of the components on the topside of the board is also shown in Fig. 2.

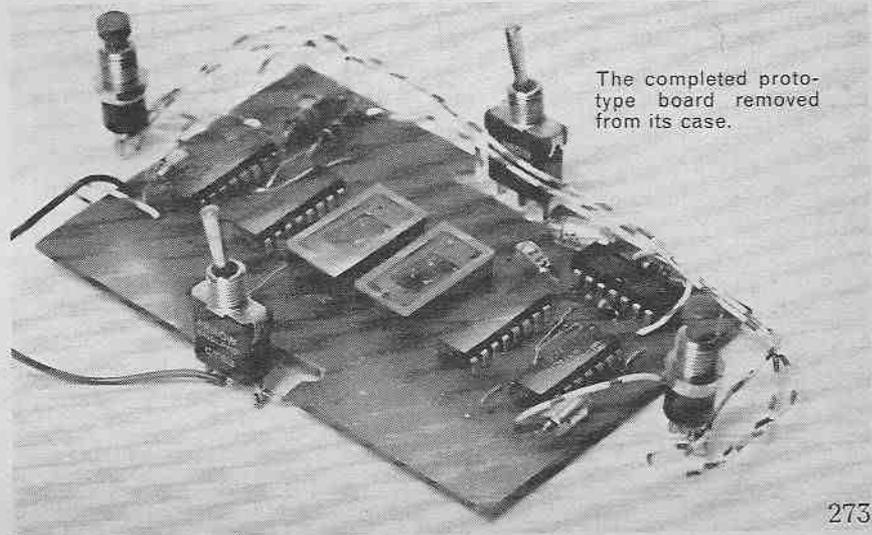Begin assembly by soldering the link wires in place followed by the resistors and capacitors. I.C. sockets



The completed prototype board removed from its case.

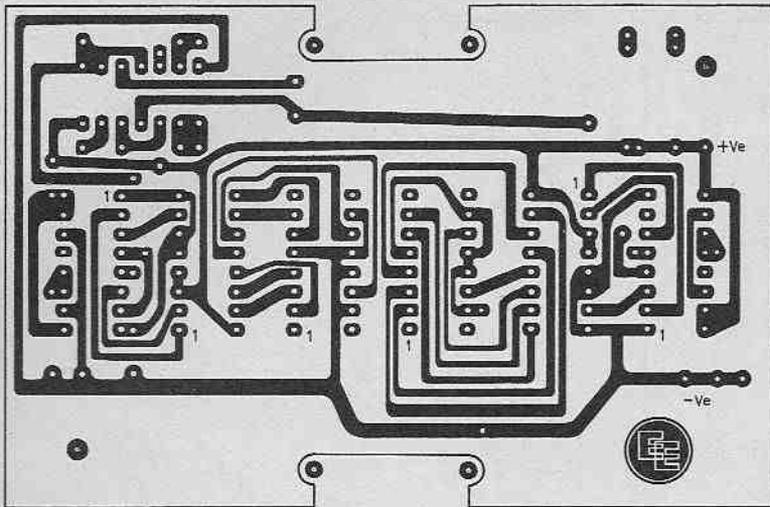


Fig. 2. Full size printed circuit board master pattern. The black areas are the regions of copper to remain after etching.

COMPONENTS



See
**Shop
Talk**

page 287

Resistors

R1 100k Ω
R2, 3, 4 10k Ω (3 off)
All $\frac{1}{4}$ W carbon $\pm 10\%$

Capacitors

C1,3,4 470pF polystyrene or ceramic (3 off)
C2 220pF polystyrene or ceramic

Semiconductors

IC1, 4 74193 TTL 4-bit binary up-down counter (2 off)
IC2, 3 CD4511 CMOS BCD to 7-segment latch decoder/driver (2 off)
IC5 CD4001 CMOS Quad 2-input NOR gate
X1, 2 Minitron 3015F filament 7-segment display (2 off)

Miscellaneous

S1, 2 miniature on/off toggle (2 off)
S3, S4 miniature push-to-make, release-to-break types (2 off)
B1 6 volt (HP11—4 off)
Printed circuit board, single sided 100mm \times 66mm; Bimbox type BIM 5000/14; size approximately 145 \times 75 \times 50mm; battery holder; red Perspex 30 \times 20mm; connecting wire.

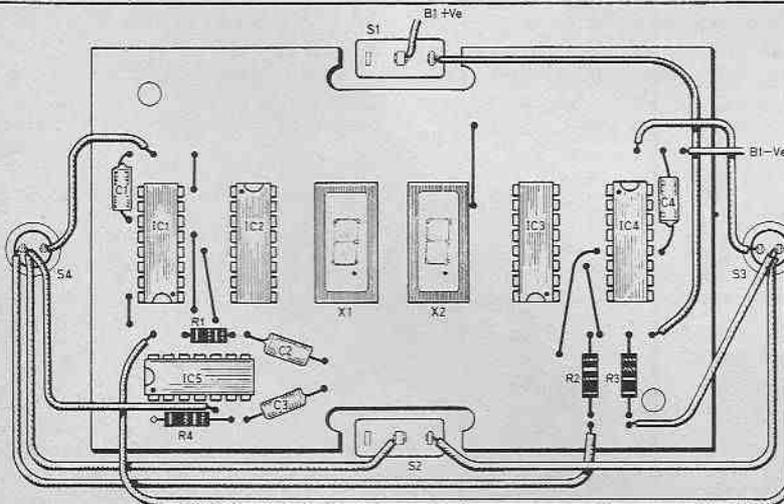


Fig. 3. Layout of the components on the topside of the board and wiring-up details.

COMPONENTS
approximate
cost **£12**

were not used in the prototype but room exists between the board and top panel for the low-profile type of socket. Position and solder the i.c. sockets and displays.


The switches in Fig. 2 are shown inverted for clarity. These should next be wired up to the board. Connect the leads to the battery connector and finally insert or solder the i.c.s. in position paying attention to polarity. An indented marker appears between the first and last pin numbers as shown in Fig. 2.

ASSEMBLY

The p.c.b. is secured to the lid of the plastic case by means of two countersunk bolts. This enables the whole assembly to be easily removed and provides easy access to the batteries. A fascia glued to the lid will mask the board fixing screws.

The lid should next be prepared to accept the switches and a 25 \times 13mm rectangular slot cut in the centre to enable the displays to show through. The hole is backed with a small piece of red Perspex which helps to emphasise the digits. The Perspex is glued to the underside of the lid. Araldite is suitable.

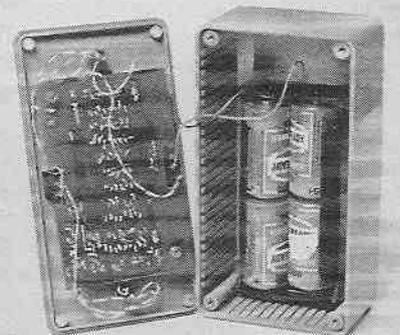The battery holder can either be glued or screwed to the base of the case to retain it. Fit the switches and board to the lid, attach the fascia and the dice are ready to be rolled. \square




Board mounted on the lid of the case and housing of the batteries.

BARGAIN HUNTERS...

YOUR SEARCH IS OVER

LOW COST METAL LOCATOR

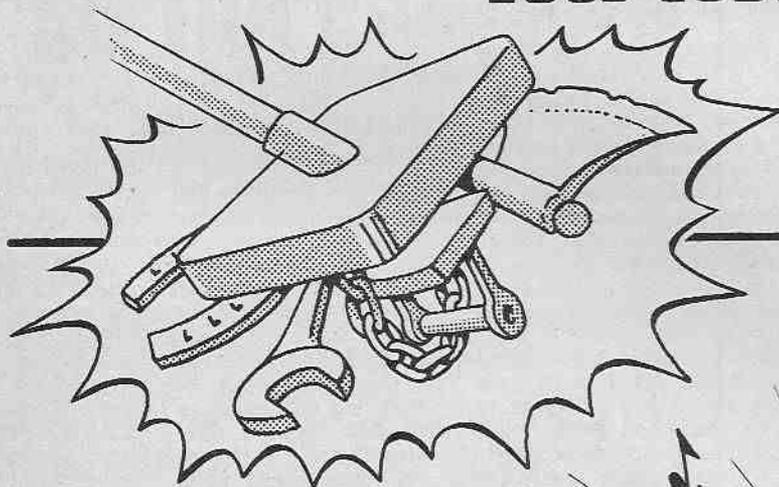A simple but effective instrument based on a beat frequency oscillator circuit. Crystal earpiece provides sound indication of the presence of metal.



QUADRAPHONIC SIMULATOR

A simple modification to any stereo reproducer which gives impressive results. Includes headphones control unit.


TREMOLO UNIT

An add-on effects unit for the guitar or organ. Provides amplitude modulation at variable speeds indicated by flashing l.e.d.

**INEXPENSIVE PROJECTS
FOR ALL IN NEXT MONTHS ISSUE**

ELECTRONIC CANARY

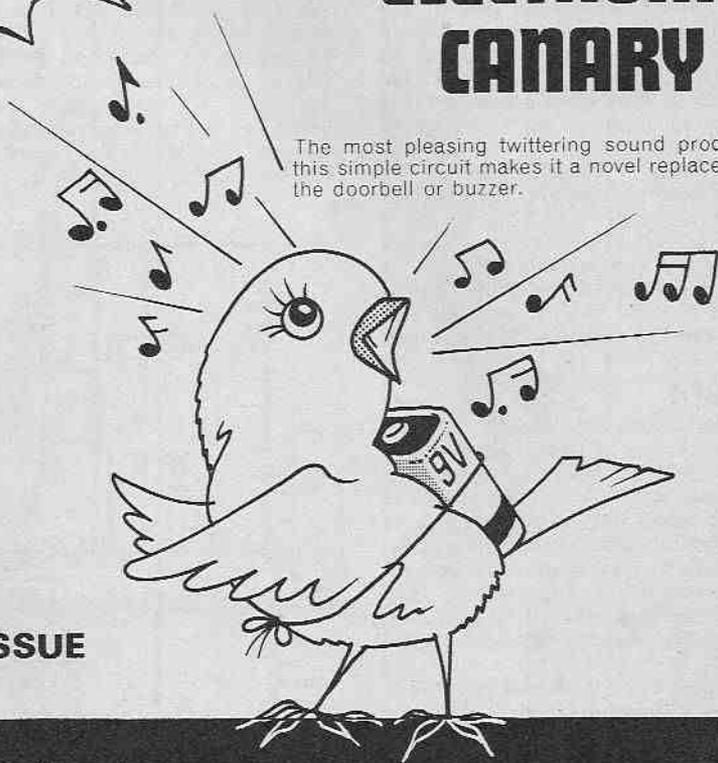
The most pleasing twittering sound produced by this simple circuit makes it a novel replacement for the doorbell or buzzer.



Everyday ELECTRONICS

JUNE
ISSUE ON SALE
FRIDAY, MAY 18
Price 45p

DOING IT DIGITALLY

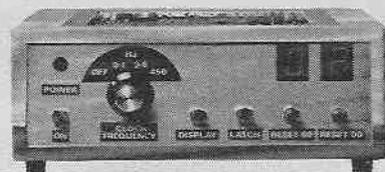

By O. N. Bishop

PART 8

A PULSE generator, sometimes called a clock, is at the heart of all timing systems. The TTL Electronic Test-Bed has its own built-in clock which can be very useful for simple timing projects and for designing and testing more elaborate projects being built up on the Test-Bed.

Unfortunately the built-in clock is not reliable enough for precision timing. Its frequency depends upon the supply voltage and, since the in-built voltage regulator is only a simple one, V_{CC} can vary by as much as 10 per cent, depending on the load connected to it. This gives a timing error of up to six minutes per hour, which is clearly unacceptable for many timing purposes.

If we need greater accuracy we can use the 555 timer i.c. This is not a TTL device, but it has a digital output that is fully compatible with TTL. It can be driven by any supply voltage between 3V and 15V, so we can run it from the V_{CC} supply of the Test-bed.

555 TIMER

The 555 timer i.c. can be used in many ways, one of which is shown in Fig. 8.1(a). Here it is being used as a *monostable multivibrator*. Its output is normally low, but goes high for a single period when the i.c. is triggered. This circuit is shown wired up on the Test-Bed in Fig. 8.1(b). Try various combinations of the timing capacitor C1 and the timing resistor R1.

With the values indicated the length of the high pulse is about 10 seconds.

Triggering is achieved by applying a negative-going pulse to the trigger input. This is obtained by grounding point A.

Another way is to connect a TTL gate output directly to pin 2; R2 will not then be needed. You could use the output of the NOR gate of IC3. Its input should be connected to ground; this applies a "high" to the trigger pin of the 555 i.c. If you next make the input of the NOR gate high, its

output goes low, triggering the timer.

The input to the NOR gate need go high only for a fraction of a second, yet the timer output will go high for a considerably longer period, if we choose the appropriate values for C1 and R1. In this way the 555 can be used as a *pulse-stretcher*, giving out a long pulse whenever it is fed with a short one.

One way of delivering a short, low pulse is to touch pin 2 with your finger. Normally this is sufficient to trigger the i.c. This effect can be made use of in the construction of touch-switches, but can cause confusion when you are building or testing other circuits, for accidental touching can produce spurious triggering.

CHARGE/DISCHARGE

The action of the 555 i.c. depends upon the charging and discharging of C1. When the i.c. is in its quiescent state, C1 is charged to one-third of V_{CC} and the output of the i.c. is low. Although current flows through R2 it is diverted into the i.c. through pin 7 and the charge on C1 does not increase.

Upon triggering, the output goes high and current is no longer allowed to flow through pin 7; C1 charges steadily, at a rate depending upon its capacitance and upon the value of R1. The higher the capacitance and the higher the resistance, the more slowly the charge on C1 increases.

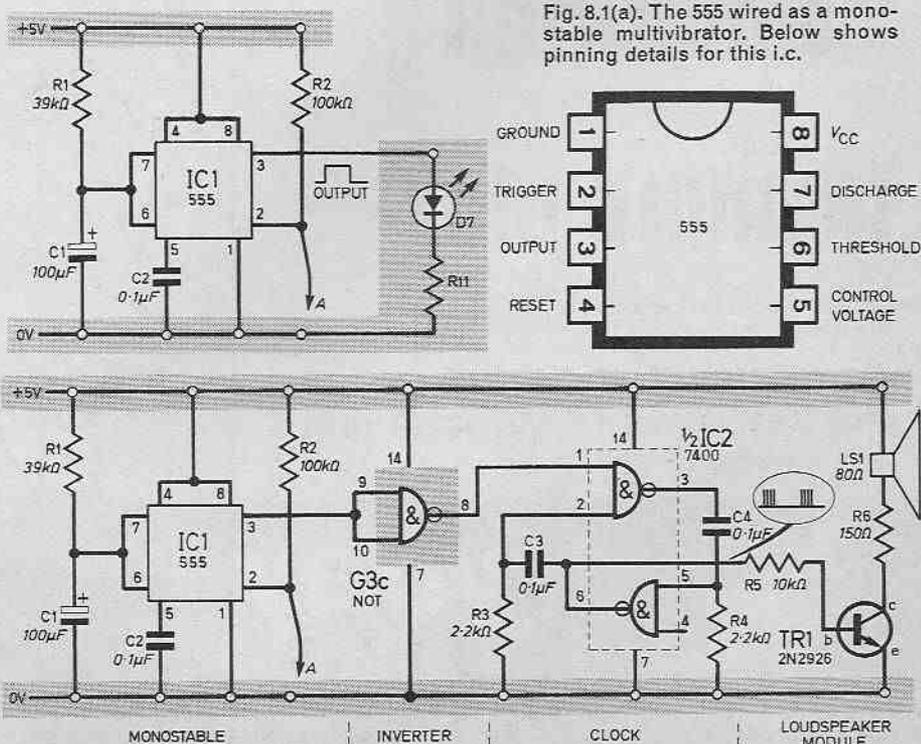


Fig. 8.1(a). The 555 wired as a monostable multivibrator. Below shows pinning details for this i.c.

Fig. 8.2(a). An audible alarm is produced at a preset time after grounding point A.

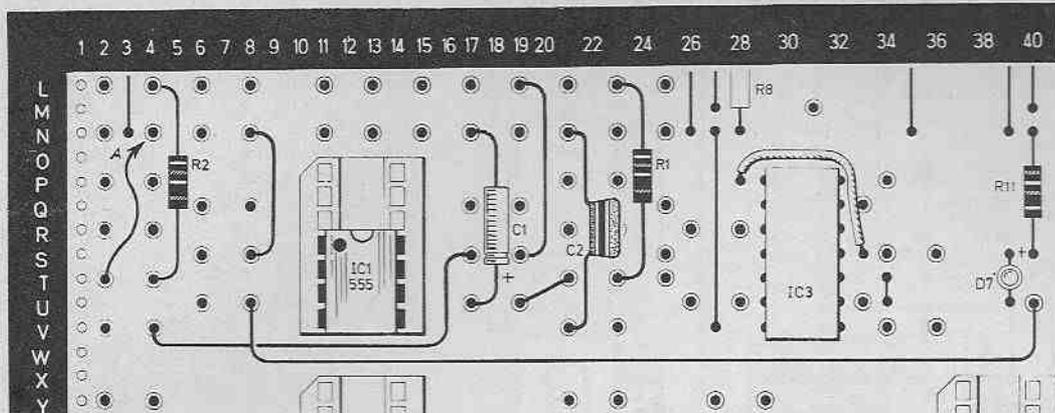


Fig. 8.1(b). The circuit of Fig. 8.1(a) wired up on the Test-Bed. Try different combinations of values for C1 and R1 and observe the high pulse length.

Eventually the charge reaches two thirds of V_{CC} ; circuitry connected to pin 6 detects that the value $2/3V_{CC}$ has been reached, causes output to go low again, and begins the rapid discharge of C1 through pin 7.

When the voltage across C1 has once again fallen to $1/3V_{CC}$ discharge


ceases and the i.c. is ready to be triggered again.

Because the action of the i.c. depends upon certain fractions of V_{CC} , but not upon the actual value of V_{CC} , the time intervals are independent of the value of V_{CC} .

Once the i.c. has been triggered, it

goes through the sequence described above and is not affected if a second triggering pulse is applied during this time. If, while its output is high, a negative-going pulse is applied to the reset pin (pin 4), the output immediately goes low, and C1 is rapidly discharged to $1/3V_{CC}$.

Fig. 8.2(b). The circuit of Fig. 8.2(a) wired up on the Test-Bed.

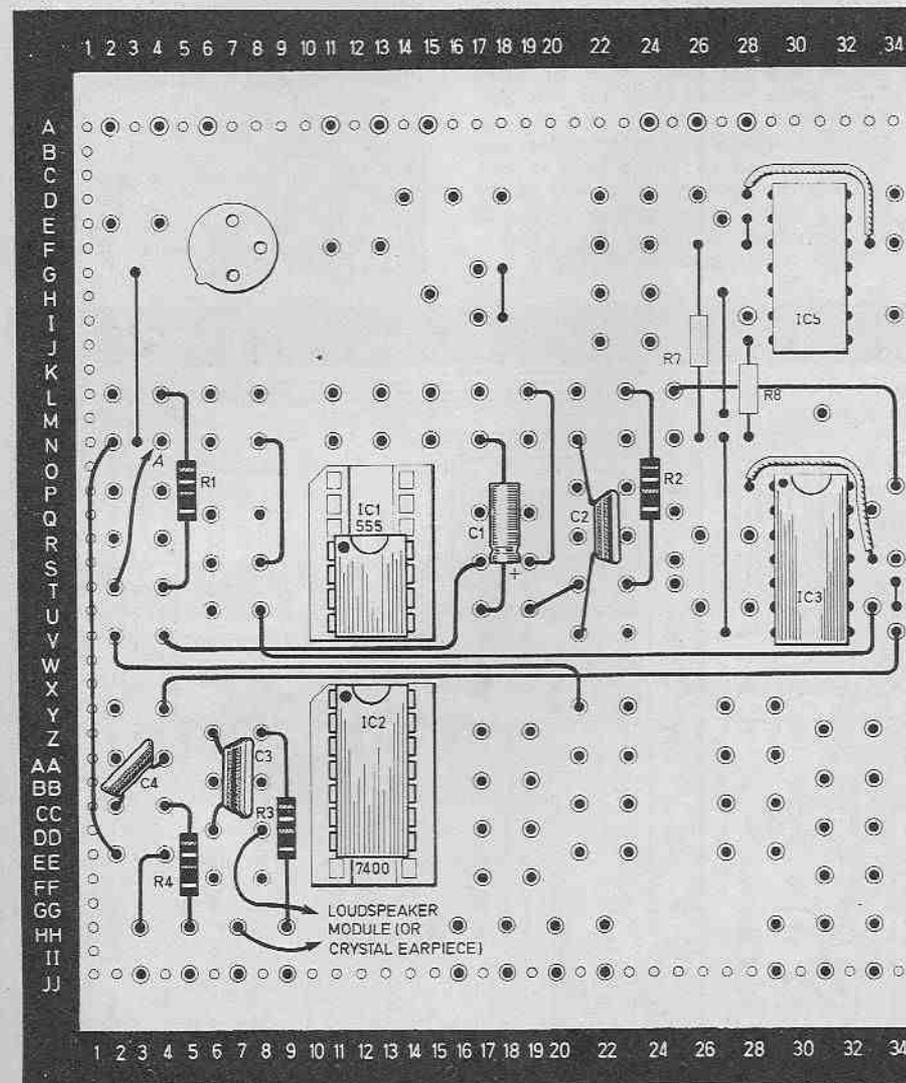

EGG TIMER

The circuit of Fig. 8.1(a) is the basis of a simple egg-timer. If C1 is a $100\mu\text{F}$ capacitor and R1 has a resistance of 1 megohm, the high pulse lasts 4 or 5 minutes, depending upon the exact values of the timing components. Electrolytic capacitors have high tolerance (can be as high as -50 to $+100$ per cent) so you may need to select C1 from a number of capacitors having the same nominal value. Alternatively, a variable preset resistor in series with R1 will allow you to adjust the length of pulse to the correct time for cooking your egg to perfection.

So far, we have a timer that lights an l.e.d. for the prescribed period; when the lamp goes out the egg is ready for eating. This simple circuit can be improved upon to sound an alarm at the end of the time period. We need only use circuit elements that have already been described in this series, see Fig. 8.2(a). When the 555 is triggered, its high output pulse is inverted to a low pulse by the nor gate. This low state inhibits the action of the astable multivibrator (this is the same circuit as the in-built clock, with capacitors chosen to give an audio-frequency output).

As soon as the timing period is over, the astable multivibrator begins to oscillate; since its output is connected to the loudspeaker module, an alarm note is heard. Thus the circuit emits a note as soon as it is switched on. This is silenced by pressing the trigger switch, and it remains silent until the set period has elapsed.

This circuit would be very suitable for building up into permanent form after you have worked out all the details on the Test-Bed. A single 7400

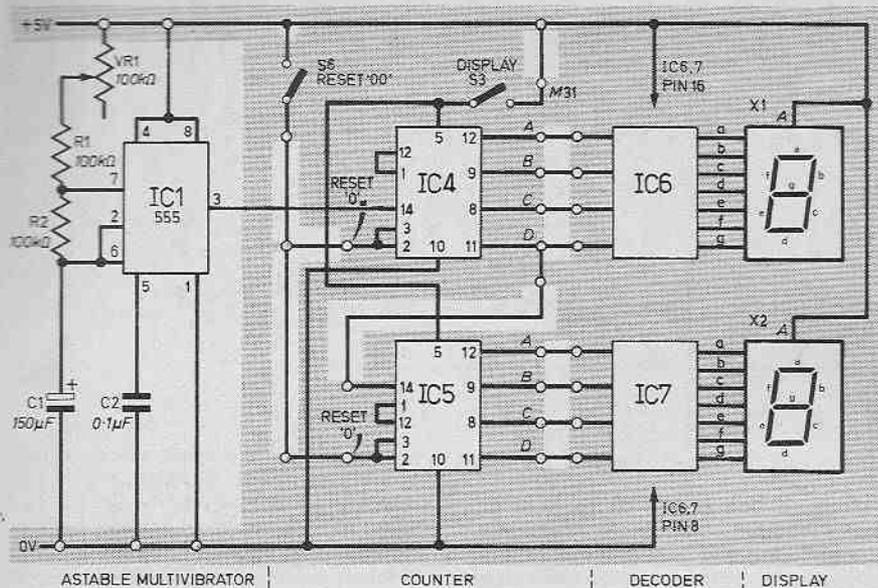


Fig. 8.3(a). The 555 wired as an astable multivibrator in an event timer up to 99 minutes in steps of one minute.

i.c. provides the necessary gates. See Fig. 8.2(b). As a refinement you could arrange a rotary switch to switch in a range of resistors, each in series with a preset resistor to allow fine adjustment. This would replace R1 and allow you to select one of a number of preset periods (say, 3, 4 and 5 minutes).

PARKING METER TIMER

The egg timer operates for a preset period, and is suitable for timing

eggs or timing moves in games such as chess or Scrabble, but it does not tell you how much time has passed and how much remains before the period will be over. Now we shall build some timers that tell you how much time has elapsed since the circuit was triggered and so allow you to work out how much time is left. Circuits of this type make use of the 555 i.c. operating in another mode, as an *astable multivibrator*, Fig. 8.3(a).

Since the trigger pin (pin 2) is con-

nected to pin 6, this circuit is self-triggering. Once started it produces a continuous train of pulses.

The timing capacitor, C1, charges through VR1, R1 and R2, but discharges only through R2, so the high pulses are longer than the low intervals between them.

The values shown in Fig. 8.3(a) cause the 555 to run at 1 cycle per minute (0.017Hz) when VR1 is suitably adjusted. If you next connect the output of the 555 to the built-in display system of the Test-Bed, the display changes once every minute, details in Fig. 8.3(b).

The RESET 00 button is used to set the display to zero at the beginning of a period that you wish to time. Thereafter the display counts from zero to 99. In short, this system can be used for timing events up to 99 minutes in length.

There is one small inaccuracy in this system. The operation of the 555 is not synchronised with your action in resetting the counter. This means that the first display change (from zero to "1") could occur at *any time* during the first minute.

This error (half a minute, on average) could be serious if you are timing relatively short periods, but is unimportant if you are using this circuit for purposes such as a parking meter reminder. Ingenious readers may like to discover a way of applying a low pulse to the reset of the 555 at the same time as the display reset button is pressed. The timer will then be fully accurate.


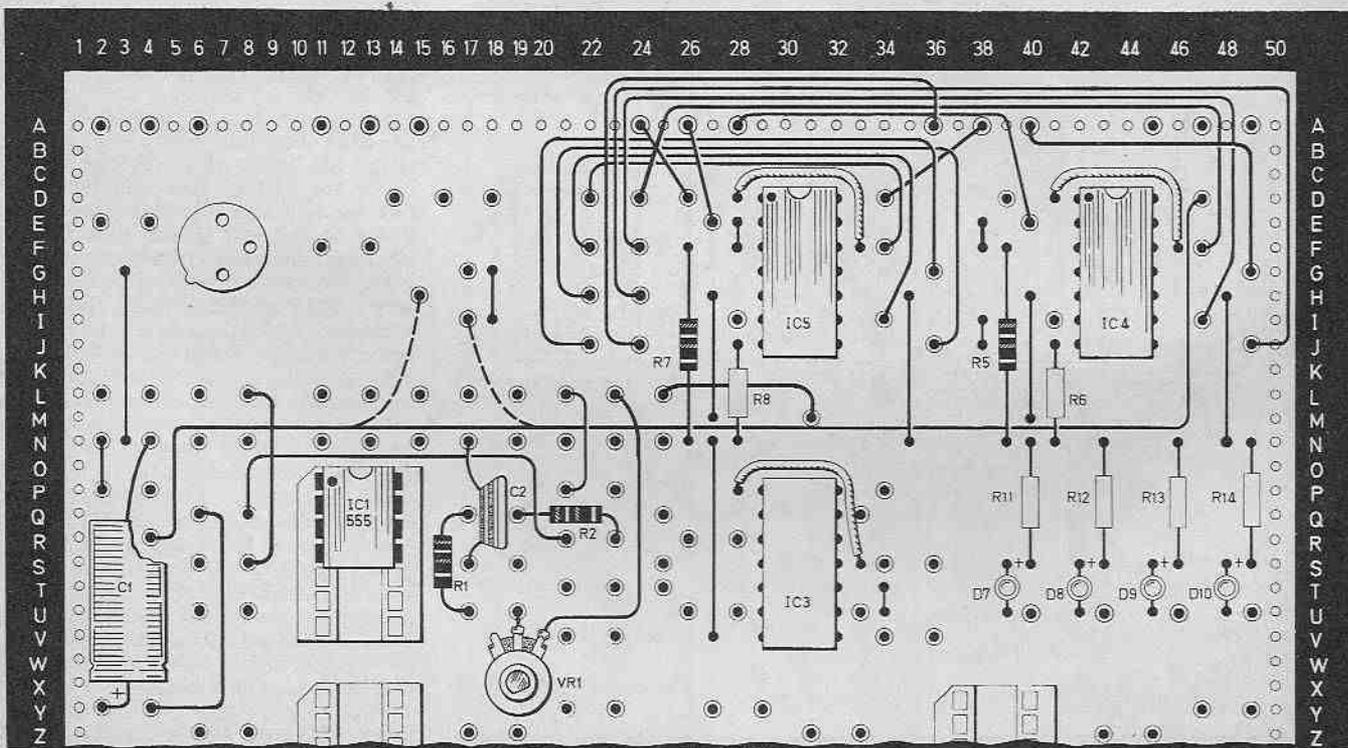


Fig. 8.3(b). The circuit of Fig. 8.3(a) wired up on the Test-Bed; S4 must be switched on.

LAB CENTRE

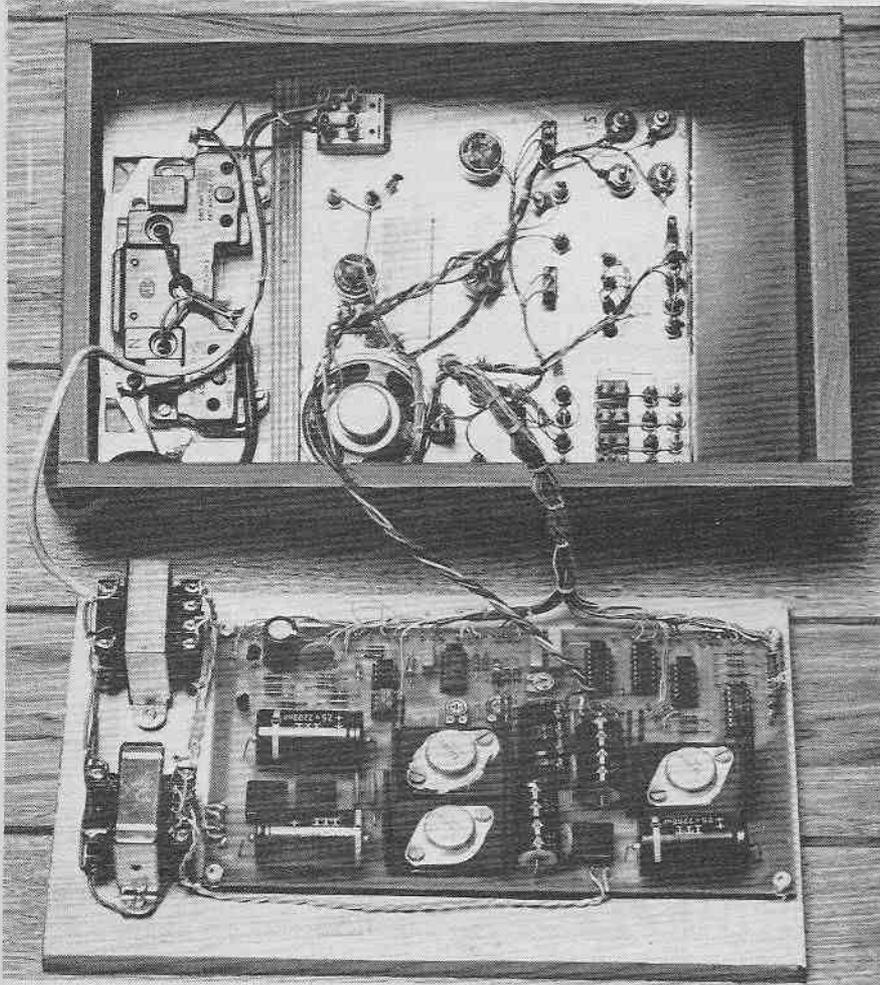

PART 3

By R. W. Coles
and B. Cullen

THIS month completes the construction of the Labcentre.

Dimensions and bending details of the component drawer incorporated in the console are shown in Fig. 3.1.

FRONT PANEL FINISH

On the prototype the front panel and the console frame were both finished using aerosol cellulose paints. At least three coats should be used, with sanding down between each coat,

until a uniform and pleasing finish is obtained. Frame and front panel colours are of course the choice of the individual constructor but you are advised not to use a front panel colour which is too dark because black lettering and marking inks are easier to obtain than white!

To make Labcentre easy to use, its separate functions are clearly indicated on the front panel, using words, outline boxes, and where necessary,

circuit schematics, see photographs. The lettering is applied using Letra-set, and the symbols and outlines can be drawn using a dense drawing ink. It is of course this stage of the job which makes or breaks the finished unit as far as appearance is concerned, and we recommend a slow and careful approach to get the best results.

When lettering is complete, the front panel should be given several coats of clear polyurethane varnish to provide a lasting and durable, high gloss finish.

OVERALL ASSEMBLY

With the front panel completed, the controls and other front panel hardware can be fitted as shown in the underside view of the panel in Fig. 3.2. Note the fitting of larger solder tags under same socket fixing nuts.

Next carry out the interwiring between panel mounted components and soldertags. With the console base removed from the sides, mount the p.c.b. and the mains transformers with reference to the photographs and Fig. 3.3.

Nuts and bolts (4BA), rather than woodscrews, should be used to attach these components to the base, and this will necessitate drilling and countersinking to leave the bolt heads flush with the base lower face. The circuit board should be mounted after the transformers, and should be spaced above the base by means of a couple of nuts or spacers. Washers should be used wherever appropriate. Remember, a sturdy construction will pay dividends when you decide to take advantage of the portability of your Labcentre!

WIRING UP

The transformer wiring shown in Fig. 3.3 should be tackled next, using a solid or flexible p.v.c. wire rated at 2A or more. Next, with the base panel sited adjacent to the inverted frame fitted with the front panel, connect the wiring between the 13A sockets, the rocker switch, and the mains transformers with due regard to the lethal voltages which will be preset on these wires. Good quality well insulated flexible wire of 2A rating or greater is essential.

The wiring between the circuit board terminal pins 6, 7, 8 and 9 and the front panel power supply SK1, 2, 3 and 4 terminals can now be carried out using the same flexible p.v.c. insulated wire as was used for the transformer wiring. At this point it is a good idea to check that all is well with the mains wiring and the power supply circuitry. This can be done by applying the mains supply via a fused 13A plug, and checking that the required 5V, plus 15V and minus 15V

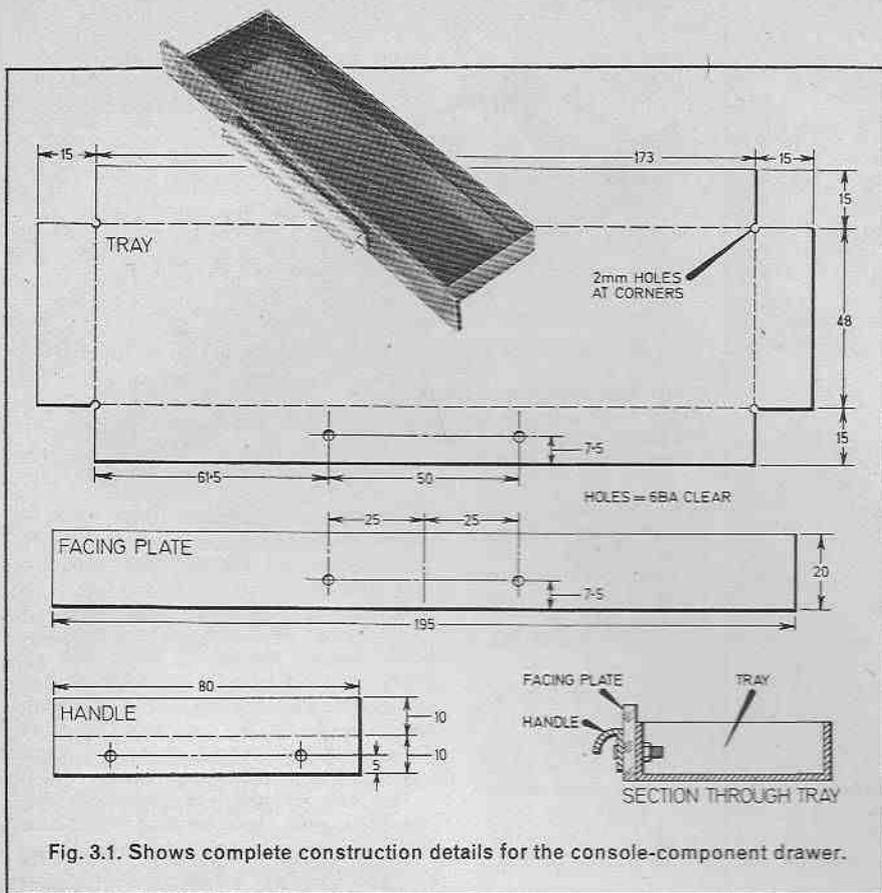


Fig. 3.1. Shows complete construction details for the console-component drawer.



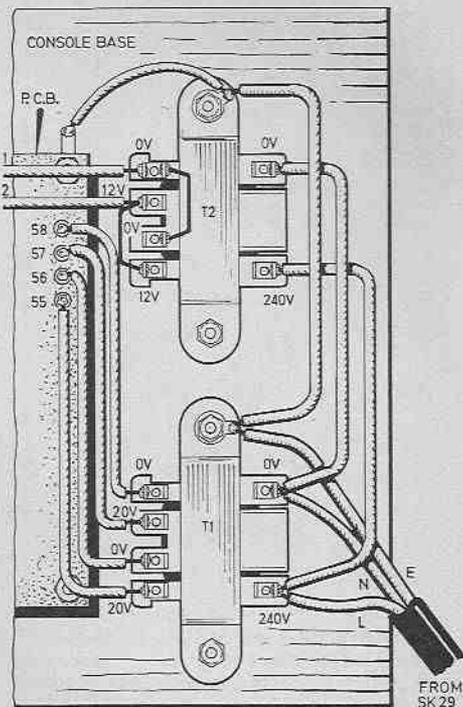


Fig. 3.3. Shows position of the transformer alongside the p.c.b. and wiring details. Note the use of solder tags for earthing purposes, particularly the one at the p.c.b. fixing. This must be in good contact with the earth plane on the board underside.

Fig. 3.2. Underside view of the top panel showing positions of components, interwiring and wiring to the p.c.b. Encircled numbers refer to terminal pin numbers on p.c.b., see Fig. 2.2.

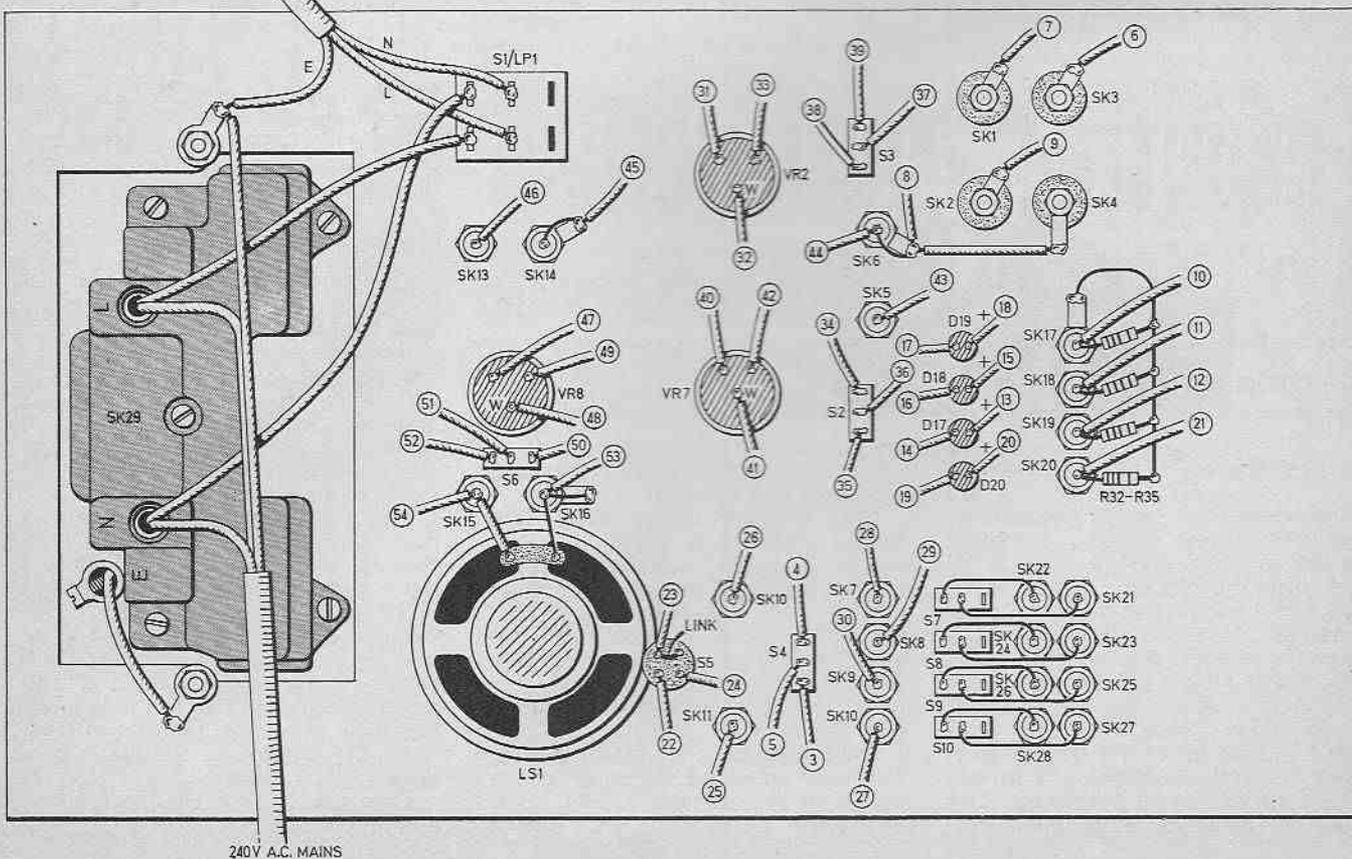

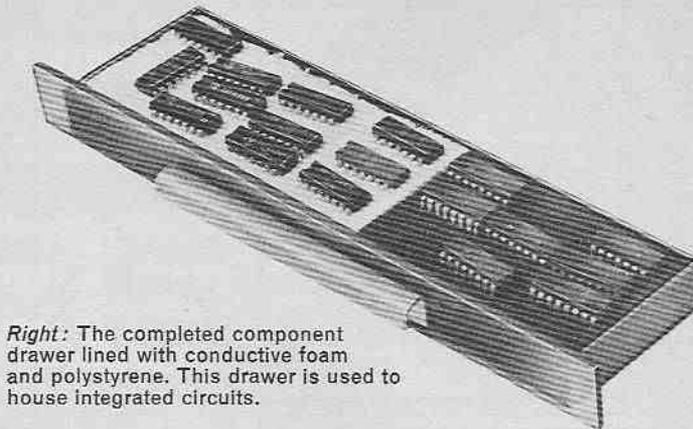

Right: The completed component drawer lined with conductive foam and polystyrene. This drawer is used to house integrated circuits.

Left: Completed console showing the front panel layout. The lettering is applied using Letraset, and symbols and outlines added with artists ink.

supplies are all available on the front panel terminals.

Unplug from the mains before proceeding.

The next task is to wire the front panel controls etc, to the p.c.b. terminal pins.

There are 48 connections remaining to be made from components on the rear of the front panel to terminal pins 3 to 5 and 10 to 54 inclusive.

As can be seen from the photographs these wires are in four separate wiring looms (pins 3 to 5, 10 to 24, 25 to 30 and 31 to 54) which run into a single large loom. Deal with each sub-loom in turn and record the connections as they are made by crossing the appropriate terminal pin in Fig. 2.2.

All wiring should be kept as short as possible, consistent with accessi-

bility and a tidy loom. Extra care is recommended during this phase to ensure that all connections are correctly made.

A flexible p.v.c. insulated wire of finer gauge than that used for the other wiring should be used for all loom connections to prevent undue strain on the soldered joints. Remember to make up the looms so that they do not impede front panel replacement or removal.

The unit is complete and ready for checking and then testing after the 48th connection has been made.

ERRATUM: In Fig. 2-2 diode D4 should be renumbered D13.

Next month: Testing and fitting out.



Burnt Offering

I suppose I am always advocating that if someone designs a better mousetrap let's change over to it and drop the old one; if not, let's keep what we have already got. For example consider the ordinary domestic toaster. Just after the War they were simple affairs but they produced nice evenly toasted bread. Then came the "pop up" which shot it up to the ceiling and gave you a choice of black or white. I have very recently purchased the latest in toasters. It is much the

same, except it shoots the toast out sideways and hits you in the ear.

Here are the design faults. The timer, which is a simple bi-metal strip, is never constant. Surely today one might reasonably expect that it was replaced by a timing chip? The other fault is this. The toast is always burnt at the top. Don't toaster designers know that heat rises and they must compensate for this?

On the early post war toasters, this was achieved by spacing the wiring of the element further apart at the top. Looking at the element

on my toaster I see it is equally spaced all the way up. It seems pathetic that a generation that can put men on the moon can not produce a satisfactory toaster.

Question Time

One of my greatest delights was the discovery that I have so many well informed readers. If I ask them a question in the electronic field I can be sure that a number of them will write to me with detailed answers. A question I have been pondering on lately is this. Has static electricity ever been made to perform any useful functions?

The first question to decide was how different is it from the type that is produced by a dynamo. I have put this question to one or two quite knowledgeable colleagues in a slightly different form, namely "What is the difference between static electricity and the ordinary sort and I do not mean just the way they are produced?" To date the question has only produced blank stares.


Can any of my brainy readers enlighten me?

SQUARE one

FOR BEGINNERS

PRESENT day electronics owes everything to a three-legged device (in discrete form) called a *transistor*. The business part occupies only a tiny fraction of the volume, the remainder being protective encapsulation.

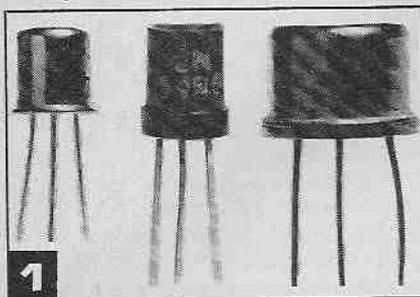
There are a huge number of different encapsulation and case geometries to suit particular mechanical and operating requirements. Three small-signal type transistors of different casings are shown in Fig. 1.




Transistors are made from "treated" wafers (or chips) of silicon or germanium—the latter being used less and less due to inferior performance compared to silicon devices.

Depending on the "arrangement" of the treated sections a transistor is either a *pnp* or an *nnp* device which determines its operating polarity. There are three distinct sections and these are called the *base*, *collector* and *emitter*. The three legs are connected to these sections.

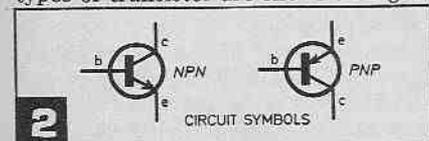The circuit symbols for these two types of transistor are shown in Fig. 2.



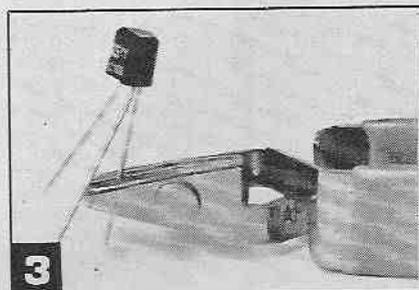Transistors are sensitive to over-voltage and current and are easily destroyed. So extra care should be taken when positioning them on circuit boards. They are also sensitive to heat so swift soldering or the use of a heatshunt on the leads when soldering is recommended. Pliers can be used for this but a spring-loaded heatshunt is more convenient, Fig. 3.



Quite a selection of transistor types are used in constructional projects in EE, but in most cases each can be changed for other type numbers you may have in stock that have similar electrical characteristics, without affecting circuit operation. They may even have different pin-out arrangements and case styles, but the leads can easily be re-formed to suit.

TRANSISTOR CHARACTERISTICS

What characteristics are to be taken into account when deciding on a substitute is a question often asked.

The most important ones are voltage and current ratings. Manufacturers quote a parameter I_{Cmax} . This is the maximum collector current that may pass before the transistor starts to suffer damage. A

knowledge of currents flowing in the circuit would be useful in deciding on a replacement type, but if this is not known, select one with at least the maximum rating of the recommended type.

Transistor data sheets contain three voltage parameters: V_{CEmax} is the maximum voltage that is allowed across the collector/emitter under dynamic (operating) conditions before breakdown occurs; V_{CB} is the maximum voltage that can exist between collector and base before breakdown; V_{EB} is a much overlooked parameter, the maximum reverse voltage allowed across the emitter/base. In germanium transistors this can be quite high, but in silicon devices this is low being approximately 5 to 6 volts.

A transistor has two gains, h_{fe} and h_{FE} ; h_{fe} is small signal current gain and h_{FE} large signal current gain. Due to production spreads you will find that a device gain is quoted either by its minimum and maximum gain (20-100) or by its minimum value only. The gain is defined as the ratio of collector current (I_c)/base current (I_b).

For low power devices, the base current is adjusted to obtain a collector current of 2mA when measuring gain.

A very important parameter is P_{TOT} , the maximum permissible power dissipation that can be tolerated before the internal "semiconductor junctions" overheat and destruct. This is equal to the product of the voltage between collector and emitter V_{ce} when collector current I_c flows.

This parameter is usually quoted for an ambient temperature of 25°C or, for power devices, case temperature maintained at 25°C.

Last but not least is f_T , the frequency at which the current gain drops to unity. This is particularly important for high frequency circuits when considering replacements.

Characteristics for some commonly used transistors, case styles and lead-outs are listed in Table 1.

TABLE 1: Some common transistor types and their characteristics.

Type No.	Polarity	I_{Cmax} (mA)	V_{CE} (V)	V_{CB} (V)	V_{EB} (V)	h_{FE} *	P_{TOT} (mW)	f_T (MHz)	Case
BC107	nnp	100	45	50	6	110	300	150	TO-18
BC108	nnp	100	20	30	5	120	300	150	TO-18
BC109	nnp	100	20	30	5	180	300	150	TO-18
BC182L	nnp	200	50	60	5	240	300	120	TO-92
BC194L	nnp	200	30	45	5	240	300	150	TO-92
BC212L	pnp	200	50	60	5	50	300	200	TO-92
BC214L	pnp	200	30	45	5	125	300	200	TO-92
BFY51	nnp	1000	30	60	6	40	800	50	TO-5
2N2926/g	nnp	100	25	25	5	235	200	100	TO-98
2N3702	pnp	200	25	40	5	60	360	100	TO-92
2N3704	nnp	800	30	50	5	300	360	100	TO-92
ZTX300	nnp	500	25	25	5	50/300	300	150	E-Line

All silicon devices

* Minimum values only with exception of ZTX300

MICROPROCESSOR BASICS

By R. W. Coles

3

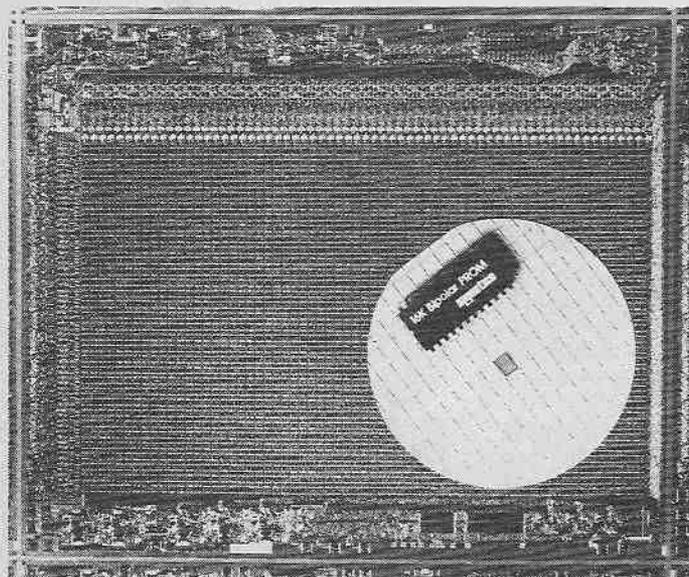


Photo micrograph of the Signetics (Mullard) 16K Programmable ROM (see Fig. 3.2) with inset photo's of one silicon slice which contains around 100 individual chips and an encapsulated chip—the final device.

LAST month we had a look at microprocessor systems, and went on to consider the microprocessor chip itself. We saw how the microprocessor could send out an address from the program counter, and how this address was used to "point" to the next instruction word stored in program memory. The instruction word is "fetched" by the microprocessor and then "executed" by appropriate use of resources such as the Arithmetic and Logic Unit and the internal registers.

We also saw that other registers, apart from the program counter, could be gated on to the address bus to access not instructions, but data during the "execution" part of a cycle.

Program memory and data memory are usually external to the microprocessor chip itself, and other essential external components are the so-called input/output "ports" which allow the microprocessor to communicate with its environment. It is now time for us to consider these important elements of a microprocessor system in more detail.

NON-VOLATILE MEMORY

Many microprocessor systems perform "dedicated" functions. Control of a traffic light system or a washing machine, for example. Well, obviously for jobs like these we do not want to have the policeman or housewife loading a paper or magnetic tape based program into the system every time the power is turned on!

For controller jobs such as these we need the program to be an integral and unalterable part of the system, and so we put it in a Read Only Memory or ROM. Once the program is entombed in a ROM, it will stay there for as long as we like, whether the power is on or off. ROM storage is therefore "Non-Volatile" and ideal for fixed program storage.

Some data may also need the same treatment. Consider the washing machine controller. Its program may need access to data which describes the temperatures or washing times for different fabrics, and once again these must not be lost when power is removed and so a ROM is used.

READ/WRITE MEMORY

Data stored in a ROM must be constant data, but of course most systems also need to handle variable data also and these will need to be kept in alterable memory so that the current value of a variable can be stored and retrieved whenever necessary. An obvious variable for the traffic light system would be "time", but the system may also need to store data on the number of cars arriving in a particular direction, the current light status and so on. Washing machine variables could be the weight of the current load, actual temperature of the water in the drum, and also elapsed time.

Variable data is stored in Read/Write memory, and this is usually referred to as RAM. RAM actually stands for Random Access Memory, which is unfortunate because ROMs are also accessed in a random (rather than sequential) fashion. All you can do about this confusing situation is to mentally translate RAM into Read Write Memory, after that, it's easy!

Read/Write Memory can be thought of as a very large array of flip-flops or bistables, each of which can "remember" one binary bit. A microprocessor system needs to access the data on a word-by-word rather than a bit-by-bit basis, and so microprocessor Read/Write Memory is organised as an array of words, each word being separately addressable.

As anyone who has tinkered with TTL or CMOS flip-flops will know, when the power is turned off, the previous state of the flip-flop is lost. This "amnesia" also occurs with microprocessor RAM, making it unsuitable for the storage of system constants or fixed programs. Variable data on the other hand is generated anew when power is applied, and also has to be changed from time to time. For variables therefore, RAM is ideal.

PROGRAM R.A.M.

If RAM was only needed to store variables, most systems would not require very much of it, some would even be able to make do with only their internal registers, and yet some microprocessor systems are advertised as having "32K bytes of RAM" or more. Why is this?

Well, our traffic lights and washing machine can certainly make do with very little RAM, but some systems need to be able to change their programs, either for development purposes or because they are general purpose systems which need frequent program changes. In these systems RAM is used to hold programs as well as data, and so a lot of RAM is necessary.

To most microprocessors, RAM and ROM appear identical, so they can have any appropriate mixture depending on the job they have to perform. Only the programmer needs to know where in the address range of the microprocessor the two types of memory can be found.

To sum up then, programs can be stored in ROM (for dedicated applications) or RAM (for general purpose use). Data can be stored in ROM (for constants) or RAM (for variables).

READ ONLY MEMORIES

ROMs are an essential part of most microprocessor systems, and they are available in a wide variety of sizes and types. Like microprocessors, ROMs are complex integrated circuits and they are currently available in sizes of up to 64K bits each.

The 64K device is the largest ROM presently available, and you can see that a very large program can be stored in this chip when you consider that the 64K is organised as 8,192 eight-bit words. (Most microprocessor instructions consist of one, two or three eight-bit words.) All of this is packaged in a 28-pin dual-in-line package with thirteen address pins, eight data-out pins, three chip-select pins and two power supply pins. Fig. 3.1.)

The cheapest way to get your program into a ROM is to let the ROM manufacturer build it in when he makes the silicon chip. This is called "mask programming" because the final photographic mask used in the chip fabrication process is made up to your program's

requirements. There is one small snag. It will be necessary to purchase over one thousand of the resulting ROMs to take advantage of this low cost method! For hobby use this isn't on of course, and so back to the drawing board!

P.R.O.M.S.

To overcome the need for mass production, the chip manufacturers have designed ROMs which arrive at your door unprogrammed. Using these chips, the final programming step can be carried out in the comfort of your own home or workshop. These ROMs are referred to as PROMs (the P stands for programmable) and there are many varieties available.

There's still a snag I'm afraid. To program these devices you will need a "PROM programmer" unit. This applies the correct voltages and timing pulses to the chip to persuade it to accept your program. Programmers are not cheap,

although it is possible to build your own which can act as an accessory to a simple microprocessor system. This possibility is getting more practical as the semiconductor manufacturers make their PROMs easier to program.

One of the most common PROM technologies is called "Fusible link." In this case the PROM is manufactured with a logic one in each bit cell, the state being programmed by means of a shorting link made of metal alloy or silicon. To program the logic zeroes where you need them, the trick is to apply accurately timed high-current pulses which have the rather dramatic effect of destroying the appropriate links—just like fuses. (Fig. 3.2.) Another PROM family relies not on blowing links, but growing them by means of a technology called "Avalanche Induced Migration."

As you may have guessed, a big problem with PROMs is that if you

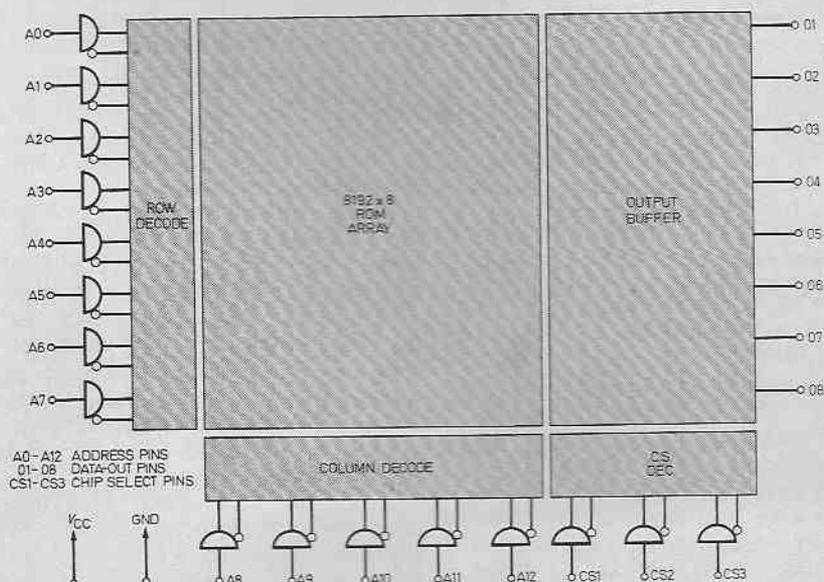


Fig. 3.1. The National Semiconductor MM5235 Read Only Memory. An example of the largest ROM currently available.

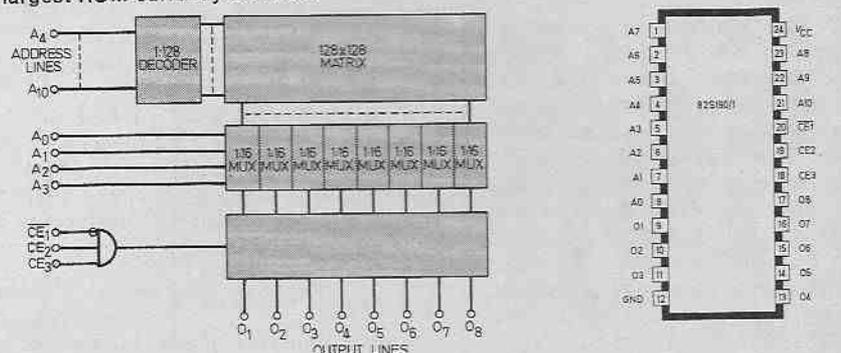


Fig. 3.2. The Signetics (Mullard) 82S190 16K Programmable ROM. An example of a fusible-link device, for field programming.

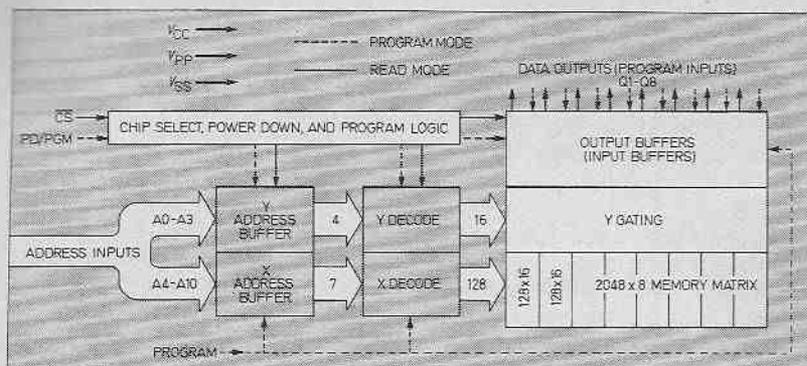


Fig. 3.3. (above and left). The Texas Instruments TMS 2516 16K EPROM. This ultraviolet light erasable electrically programmable read-only memory is ideal for use in microprocessor systems.


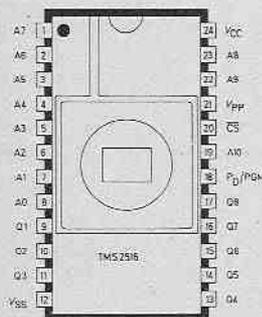


Fig. 3.4 (right). The Texas Instruments TMS 4164 65,536-bit Dynamic Random Access Memory. "Refreshing" is required to prevent data loss.

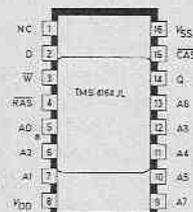

make mistakes during programming, you can't erase the mistake and start again—blowing fuses is for keeps! This disadvantage makes this type of ROM less than ideal for microprocessor work where a program will probably evolve through many stages before it can finally be called "finished."

E.P.R.O.M.s

To solve the problem of wasted PROMS, semiconductor manufacturers have developed a radically different technology which allows you to erase mistakes and old programs over and over again. These memory components are called Erasable, Programmable, Read Only Memories, or EPROMS, and it is this type of ROM chip which is best for hobby use.

You still need a programmer, but some of the new EPROMS such as the 2516 from Texas (Fig. 3.3) are so easy to program that your microprocessor can be used to do the job. The only other necessary facility is a 25 volt supply, and that's only needed during programming, the chip normally runs from a five volt supply.

But if these chips are erasable, you may wonder, how can we be sure our program will be safe? The answer is that the erasure operation requires the application of

high intensity short-wave ultraviolet light for some tens of minutes, a combination never likely to occur in normal operation, even in direct sunlight.

To use these devices you will need an erase light system to go with your programming facility, but once again these are easy to put together, and require only the purchase of a special UV lamp and some wood or metal bashing! A word of warning though, short wave UV light can be harmful to people, so the lamp must be used inside a light-tight box.

If all this talk about programmers and erasers is putting you off micro's, remember that you don't have to have these facilities because programs can be stored in RAM, an ideal form of storage while you are learning about hardware and software, and all you may ever need if programming becomes your source of enjoyment.

Finally, if you want to find out how a ROM or PROM actually works, and how address selection operates in both ROM and RAM read next month's panel feature "Build your own ROM."

R.A.M.

RAM if you remember, is synonymous with Read/Write memory, and like ROM, it comes in all sorts

of varieties and sizes. There are two main types, Static and Dynamic, and a quick look at the differences will help to avoid costly purchasing mistakes!

Static RAM uses storage cells for each bit which are based on cross coupled latches, just like the TTL or CMOS flip-flops you may have used in the past.

Dynamic memory is quite different and relies on the storage of a voltage representing a logic one or zero by means of a small capacitor in each cell. The advantage of the dynamic design is that it needs fewer transistors per cell and is therefore smaller, faster and cheaper. In effect you get more memory for your money.

Before you rush out and buy any dynamic chips, though, let me tell you about a small problem! The dynamic memory cell forgets. In fact it can only remember things for 2 milliseconds or so! This rather unfortunate behaviour stems from the use of a leaky old capacitor for storage, and memory systems using this type of chip have to go round to each cell at least every 2 milliseconds to re-write the data and hence prevent data loss.

This all sounds pretty horrible but in fact for large memories the dynamic devices are very cost effective because the extra hardware needed to carry out the "Refresh" operation as it is called, can be shared among all the chips in the system.

To see why dynamic memory is attractive despite its problems, have a look at the new Texas device which crams no less than 65,536 bits, all individually addressable, into a tiny 16-pin package! (Fig. 3.4.)

NOT RECOMMENDED

Having demonstrated that dynamic RAM is a good idea for some purposes, I think it only fair to say that I can't really recommend it for hobby use unless it comes as part of a fully designed memory board, for a home computer say.

For most hobby purposes memory sizes are small, and static RAM is therefore ideal, being easy to use and more tolerant in its power supply and timing requirements.

To be continued



By Dave Barrington

Catalogue

When Maplin Electronic Supplies first introduced their now famous components catalogue in 1973 it immediately jumped to the UK number one spot in popularity amongst readers, and also set the standards for other component suppliers to maintain. This position would seem to be strengthened with the introduction of their latest catalogue and must make them strong contenders for the number one spot in Europe, including the UK.

The new edition has been increased in size to 280 pages and includes 30 pages in full colour. We did not think it possible for Maplin to add many more products to their range but they have listed over 450 new items. This does not include new semiconductor devices and the expanding area of microprocessors which brings the grand total of new lines to well over 1000.

Over 50 pages are devoted to

the Semiconductor/Microprocessor sections. For the constructor there are 14 pages of project kits, with circuit diagrams, ranging from a 150W power amplifier to a model train controller.

The 1979/80 Maplin components catalogue is a good investment for 75p (£1 overseas) and they also back up the catalogue with a bi-monthly newsletter which contains the current prices and lists special offers. All prices quoted in the newsletter are guaranteed until a new issue is published.

The newsletter/price list is available on a subscription basis and cost 30p for six issues. For overseas customers the price is as follows: Europe 60p; non-European countries 60p surface mail and £1.20 airmail.

To help recover the cost of the catalogue and save on components vouchers are issued with most orders over £2. Also, each issue of the newsletter carries a 5p voucher.

Further details and copies of the 1979/80 catalogue can be obtained from Maplin Electronic Supplies Ltd, see back cover.

Power Supply

Further feedback from readers on the *General Purpose Power Supply* shows that readers are still having difficulty in obtaining the CA3085 voltage regulator.

We understand that Magenta Electronics are supplying a d.i.l. version together with an i.c. socket (with long connecting leads) for mounting on the Veroboard. The i.c. costs £1.15 and the socket 21p. A minimum order charge of 25p must be added.

The equivalent LM305H is also available from ACE Mailtronix Ltd, Dept EE, Tootal Street, Wakefield, Yorks WF1 5JR at an inclusive cost of £1.

Shaver Inverter

Please note that Davian Electronics, are NOT supplying parts for the *Shaver Inverter*. They were mentioned in last month's Shop Talk due to an editorial misunderstanding, and we apologise to Davian Electronics and to readers for any inconvenience this error may have caused.

Ace Mailtronix, Wakefield and other advertisers should be able to supply complete kits or individual parts for the *Shaver Inverter*.

Constructional Projects

Just a couple of pointers regarding the availability of components for this month's constructional projects need further comment.

Thermostat for Photographic Solutions

New to this magazine is the LM3911N temperature controller/thermometer i.c. called for in the *Thermostat for Photographic Solutions*. Being a rather unusual device this may prove difficult to obtain, but we have found that your local Tandy store, Maplin and Watford Electronics stock this item.

Electronic Dice

The Minitron displays specified for the *Electronic Dice* may be obtained from Electrovalue. Cost for both displays including VAT and postage is £5.13.

Intruder Alarm

When constructing the *Intruder Alarm* the space within the specified case is critical and it is advisable to use the miniature toggle switches called for in the article. The audible warning device in the prototype was rather expensive and we suggest one of the many alternative buzzers be used.

EE CROSSWORD No 15

BY D. P. NEWTON

ACROSS


- 1 One who follows electrical paths, often through carbon deposits.
- 4 The flasher's aftermath?
- 7 Prejudiced towards a personal potential (4,4).
- 9 Loudspeaker screen.
- 10 Characters not to be trusted.
- 12 Drinking partner for tiffin.
- 13 Dodge.
- 15 Would such a circuit keep our feet under cover?
- 17 Fittings suitable for the attachment of components.
- 19 Switch to original state.
- 21 Nervous twitch.
- 22 Low person having a shared circuit.
- 24 Badge of sorts.
- 25 A hi fi fanatic must be one of these.
- 27 Leaving points.
- 28 A slow loss of charge.

DOWN

- 1 To start a horse's pulse?
- 2 Wired.
- 3 A soporific wave transporter.
- 4 Quavering.
- 5 Rapid vibrations in their initial state.
- 6 Charge carriers with nowhere to go.
- 8 Mischievous current?
- 11 Nearly a close relative in the transistor.
- 14 Core it for arousing display (Anag.).
- 15 Computers do it all in military style, like this (2,7).
- 16 Cement for emergency jobs (5,3).
- 17 Characteristically full of loosely bound electrons.
- 18 To render minute.
- 20 To begin a journey in an ark?
- 23 Circuit connector in body.

- 26 Electromotive force will shortly indicate the initial parts of this once-flighty animal.

Solution on page 305

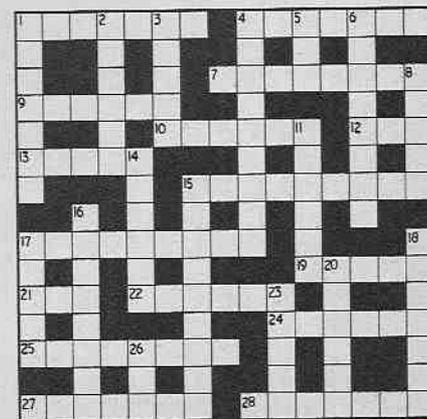

Short Wave



CONVERTER

By R. A. Penfold

WHEN MOST people become interested in short wave reception they choose to build their own receiver, this usually being of the t.r.f. variety.

While this type of receiver is capable of excellent performance and is relatively simple and inexpensive to construct, it does have disadvantages in terms of performance and convenience of use when compared to a superheterodyne receiver. Unfortunately, the complexities of a superhet make this type of set beyond the capability of most newcomers to electronics.

CONVERTER

There is another, and perhaps less common approach to commencing s.w. reception, and this is to use an ordinary medium wave superhet receiver in conjunction with a s.w. converter. Here an aerial is connected to a unit which can be tuned across the s.w. bands, with the received signals being converted to a frequency on the m.w. band. These signals are then picked up by a m.w. receiver which is tuned to the output frequency of the converter. Thus, in effect, a m.w. receiver is converted to a s.w. one.

This type of set up is not ideally suited to amateur bands reception

due to the widespread use of s.s.b. and c.w. on these bands (an ordinary m.w. set cannot resolve these types of transmission without modification), but the author has obtained really excellent results on the s.w. broadcast bands using such a combination.

The subject of this article is a simple two transistor converter which covers a frequency range of approximately 4.5 to 15MHz, and has an output frequency of about 1.6MHz at the high frequency end of the m.w. band. Included in the converter's coverage are most of the popular s.w. broadcast bands, namely the 19, 25, 31, 41, and 49 metre bands.

Use of a long aerial is not essential and quite good results can be obtained using an indoor aerial. No direct connection is made to the m.w. receiver, and there is no need to modify the set in any way whatsoever.

OPERATING PRINCIPLE

Operation of the converter is based on the *heterodyne* principle and the unit is rather like the initial stages of a superhet receiver. Whereas in a normal receiver the output of the mixer would be fed to the i.f. stages of the set, here the output of the mixer is coupled to a m.w. receiver

which provides the necessary amplification, detection, etc.

The block diagram in Fig.1 illustrates the operation of the device.

The aerial signal is fed to a tuned circuit which accepts signals at or close to the required reception frequency but rejects all others. The output from the tuned circuit is fed to one input of a mixer, and the output from an oscillator is fed to the other input.

In the mixer the two signals are "heterodyned" to produce two new frequencies at the output, in addition to the two original ones. The new signals are the *sum* and *difference* frequencies. In this case it is the difference signal that is of interest.

The oscillator frequency is always 1.6MHz above the input frequency, so that a difference signal of 1.6MHz is always produced at the output. In this way the s.w. input signal is converted to a frequency of 1.6MHz.

MIXING

A simple mathematical example is given in Fig.1. Here it is assumed that a 10MHz signal is being picked up.

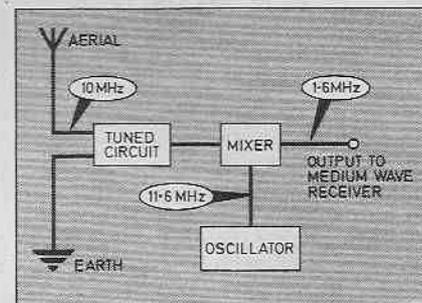


Fig. 1. Block diagram showing the various stages of the converter and the principle of operation.

The oscillator is at 11.6MHz and this produces output frequencies of 1.6MHz (11.6-10), 21.6 (11.6+10), 10MHz, and 11.6MHz. A m.w. receiver tuned to 1.6MHz will obviously only respond to the 1.6MHz signal and the other output signals are of no significance.

The oscillator could be adjusted so that it is always 1.6MHz *below* the input frequency (10-8.4=1.6), but it is conventional to have the oscillator frequency above the reception frequency. The input tuned circuit is an essential part of the design, as without it the unit would be simultaneously receiving

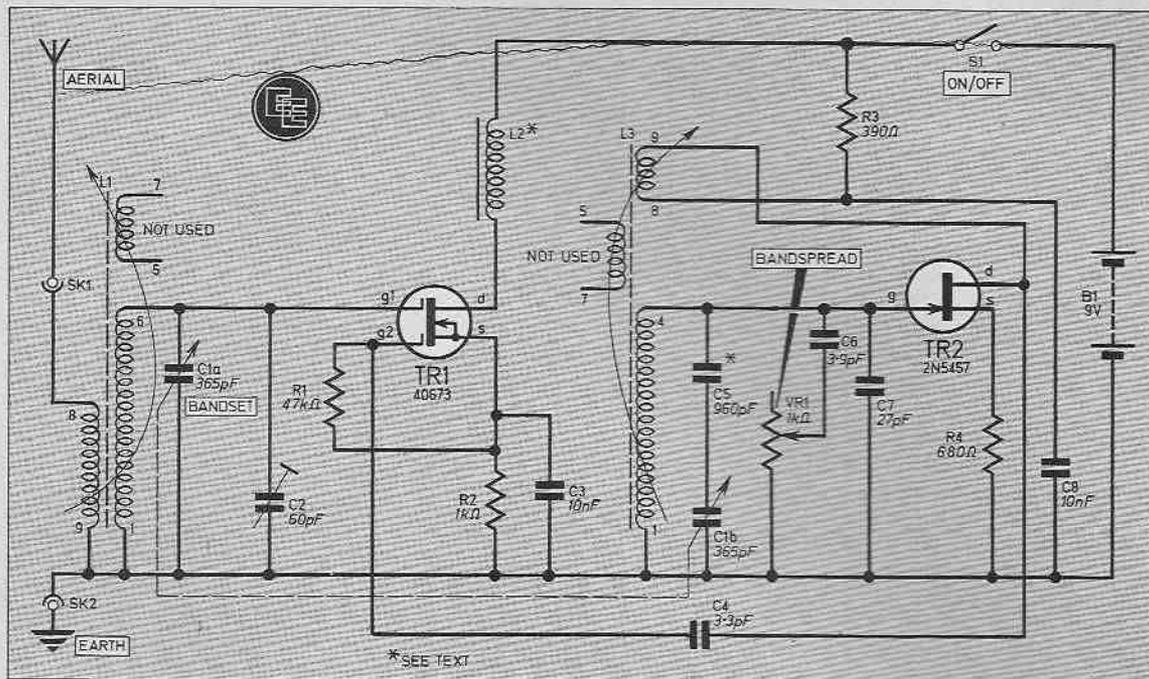


Fig. 2. Complete circuit diagram of the Short Wave Converter.

on two frequencies ($11.6 - 10 = 1.6$ and $13.2 - 11.6 = 1.6$). The tuned circuit is required in order to reject the higher reception frequency, or "image signal" as it is termed.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Short Wave Converter appears in Fig.2. Transistor, TR1 is the heart of the design and this is a dual gate mosfet which is used as a mixer.

The aerial signal is coupled to the tuned circuit via the primary winding of L1. The mosfet has a very high input impedance at its g1 terminal and the tuned circuit can be coupled direct to this. The coil normally has a base coupling winding, but as a f.e.t. is used this winding becomes redundant.

Resistor R2 is the usual source bias resistor and C3 is its bypass capacitor. Capacitor C1a is the tuning capacitor for the input tuned circuit and C2 is an alignment trimmer. The gain of TR1 at its g1 terminal can be varied by altering the voltage at its g2 terminal. The g2 terminal is biased about 1V positive of chassis by being connected to the source terminal by R1.

The oscillator output is connected to the g2 terminal of TR1, and so the gain of TR1 varies in sympathy with the oscillator sig-

nal. The oscillator thus modulates the aerial signal and produces the necessary mixing action.

The resultant output is developed across L2 which is a homemade choke. The output signal is radiated in the vicinity of L2 and if this is placed near the ferrite aerial of a m.w. receiver, this receiver will pick up the s.w. input signal. This provides about the simplest possible "interface" between the converter and the receiver.

OSCILLATOR

The oscillator is a simple design using a jugfet TR2. Positive feedback is provided between TR2 drain and gate by L3. The second half of the variable capacitor, C1b is the oscillator tuning capacitor. Capacitor C5 is a padder capacitor and is needed to ensure correct tracking between the oscillator and aerial tuned circuits. In order to obtain the correct frequency coverage a small amount of fixed capacitance must be added across the tuned winding of L3. This is provided by C7.

The variable control, VR1 and C6 form a bandspread "capacitor" and can be used to adjust the oscillator frequency slightly either side of its nominal frequency. It thus acts as a fine tuning capacitor, and this is a very useful feature as tuning over the very crowded

s.w. bands can be very difficult using C1 alone. When a bandspread control is fitted to a receiver or converter, the tuning control is usually termed a "bandset" control.

Resistor R4 is the source bias resistor for TR2, and adequate gain is obtained without bypassing this component. In fact performance suffers if this resistor is bypassed, as this produces higher harmonic signal levels at the output of the oscillator, and this gives the converter increased spurious responses.

The small capacitor C4 couples the oscillator to the mixer and also provides d.c. blocking. Resistor R3 and C8 are a supply decoupling network, and S1 the on/off switch.

Note that L3 is not designed for use in this particular oscillator configuration, and has a third winding which is not used in this application. The coil manufacturer recommends a padder capacitor value of 960pF. As far as the author is aware, no such value is available to the amateur. It is therefore necessary to use two or more capacitors in parallel to make up the required value. The author used two 470pF components in parallel (940pF) and this seemed to be near enough.

The unit has a current consumption of only about 3mA from a 9V (PP3) battery, and is therefore very economical to run.

Short Wave CONVERTER


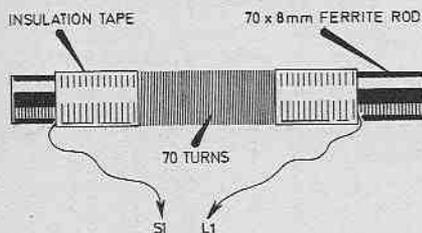


Fig. 3. Construction of the coupling coil L2. The coil is a single layer using 32 s.w.g. copper wire.

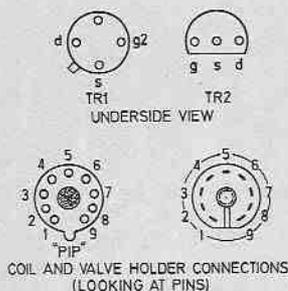

COMPONENTS

Resistors

- R1 47k Ω
- R2 1k Ω
- R3 390 Ω
- R4 680 Ω
- All carbon $\frac{1}{4}$ W \pm 10%

Potentiometer

- VR1 1k Ω lin. carbon

Capacitors

- C1a,b 365 + 365pF air spaced variable (Jackson type 00)
- C2 60pF plastic dielectric trimmer
- C3 10nF plastic
- C4 3.3pF miniature ceramic
- C5 960pF (see text)
- C6 3.9pF miniature ceramic
- C7 27pF ceramic plate
- C8 10nF plastic

Semiconductors

- TR1 40673 n-type mosfet
- TR2 2N5457 n-channel f.e.t.

Miscellaneous

- L1 Denco Range 4T Yellow or Blue coil for transistor usage
- L2 Coupling coil (choke—see text)
- L3 Denco Range 4T White coil for transistor usage
- SK1, 2.4mm sockets (two off)
- S1 single pole toggle switch
- B1 9V PP3 battery
- Small plastic case 150 x 100 x 50mm or similar; two B9A valveholders; battery connector to suit B1; two small control knobs; ferrite rod, 70 x 8mm; 32 s.w.g. enamelled copper wire; small container for L2; connecting wire.


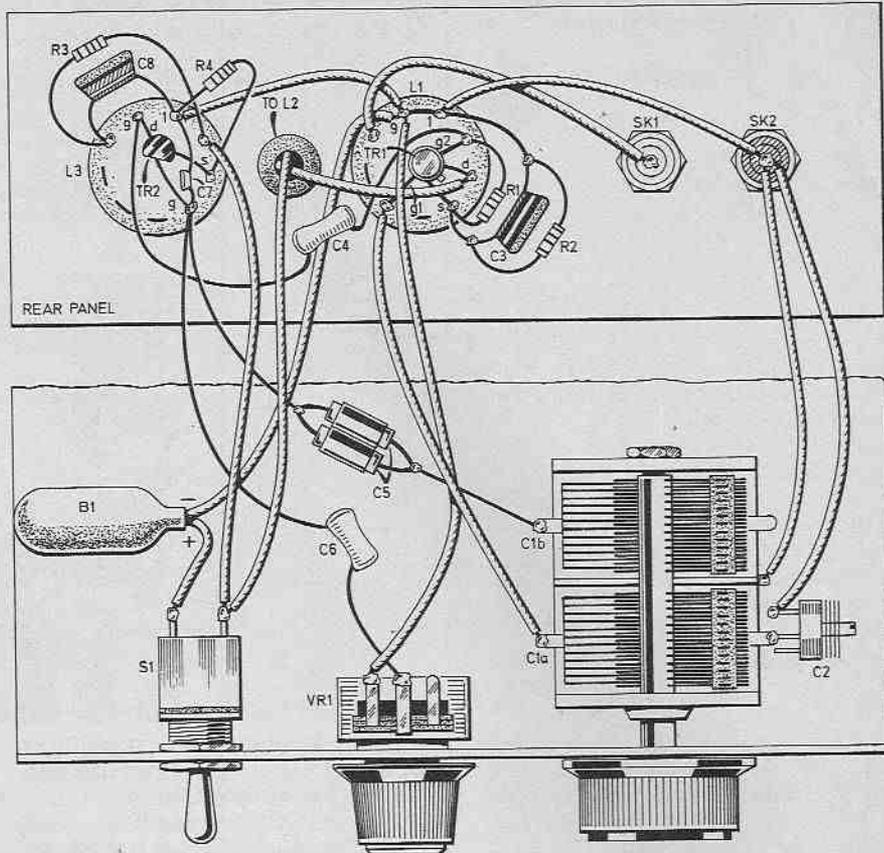


Fig. 4. Complete wiring details for the converter. Most of the components are mounted on the coils directly. When soldering TR1 be sure to leave the shorting clip in place, otherwise the device will be destroyed. Remember however, to remove it before switching on!

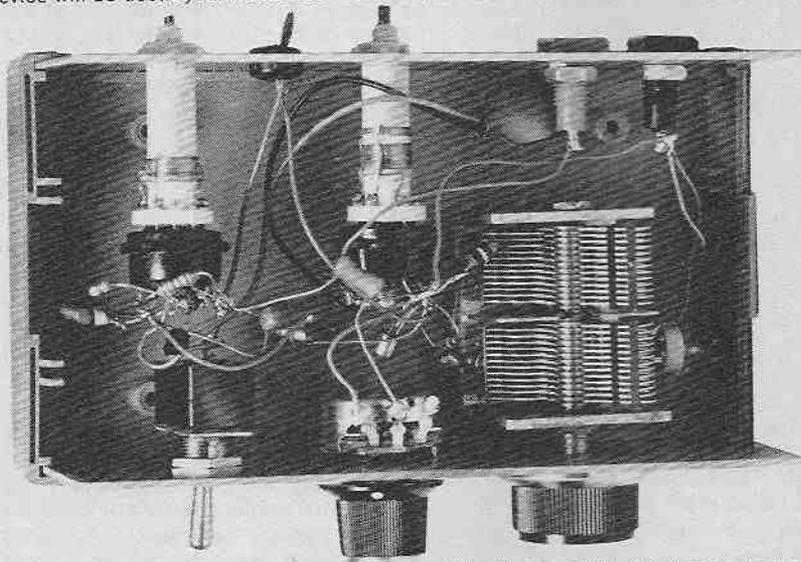

COMPONENTS
approximate
cost **£7**
excluding case

CONSTRUCTION starts here

CHOKE

The choke L2, is home-made and is wound on a 70×8mm length of ferrite rod. It has 70 turns in a single layer with the ends of the winding secured to the rod by bands of insulation tape. Either 32 s.w.g. enamelled or d.c.c. wire is used depending on what is already available, and details of the choke are given in Fig. 3.

This is not a tuned winding and is not critical with regard to size of rod, wire thickness, or even the precise number of turns. Many constructors will probably be able to make a suitable unit using items from their junk box.

CASE

The unit can be constructed in any case measuring about 150×100×50mm, but the case must not be much smaller than this. Components S1, VR1 and C1 are mounted in a line along the front panel. The bandset capacitor is not actually fastened to the front panel, but is secured to the base of the case by two 4BA bolts. These pass through holes drilled in the bottom of the case and into threaded holes in the bottom of C1.

Spacers or washers are used to hold the component at the right height, and to prevent the screws from penetrating too far into it and fouling one of the sets of plates.

The two coils and the aerial and earth sockets are mounted on the rear panel. This general arrangement can be seen from the accompanying photographs. A hole is drilled in the rear panel between the two coils and this takes the output leads to L2.

This is mounted in a small box by itself, and it is simply glued in position inside this.

WIRING

A point to point wiring system is used, and details of this are shown in Fig.4. It is not a good

idea to solder direct to the pins of the coils as this will cause the plastic coil formers to melt. Instead, a B9A valveholder is pushed onto each coil base, and the connections are made to the holder.

Some components are mounted solely on one or other of the coil holders, and it is advisable to solder these into position prior to fitting the coil holders onto the coils. Then the other wiring is completed.

Tin with solder the ends of component leadout wires and tags, and good soldered joints should be obtained.

AERIAL AND EARTH

A suitable aerial for the converter is a length of wire which is as long as possible and placed as high as possible. Ideally an outdoor aerial 15 metres or more long should be used, but an indoor aerial consisting of say, 6 metres of wire in the loft, will provide good results.

An earth can consist of a metal pipe buried at any convenient spot with a lead connecting it to SK2. An earth is by no means essential though.

(A suitable installation was given on page 149 of the March issue.)

ALIGNMENT AND USE

The coupling coil L2, must be placed fairly close to the m.w. coil of the receiver if an efficient signal transfer is to be obtained. Usually the ferrite rod is situated towards the top of a receiver, and it is merely necessary to place the box containing L2 on top of the set at the appropriate point. If it should be necessary to place the coil at some other spot on the receiver, double sided tape can be used to hold it in place.

As supplied, the cores of L1 and L3 are screwed right into the former. Initially these are unscrewed so that about 10mm of

metal screwthread protrudes from the top of each coil.

Turn the receiver on and tune it to the extreme high frequency end of the m.w. band. Try to find a tuning point that is free from stations, and remember that a ferrite aerial is directional, and the set can be turned to null a station if necessary.

Connect an aerial, and if required an earth to the converter and switch the unit on. Set the bandspread control at a central position and then try to tune a few stations using C1. When a station is picked up, adjust the core of L1 to peak this. It should then be possible to tune many stations.

Tune to one at the h.f. end of the band (C1 vanes unmeshed) and then adjust C2 to peak this signal. Tune to one at the other end of the tuning range and adjust the core of L1 to peak this station. Go back to the h.f. end of the range and repeat this whole cycle a few times until no further improvement in overall performance can be obtained.

NO SIGNAL


If no signals at all are received, then this is probably due to the oscillator not working. Slight adjustment of the core of L3, while tuning as normal with C1, should remedy this.

This completes the alignment and the unit is ready to use.

The m.w. receiver must always be tuned to the same frequency when it is used with the converter. If a significantly different one is used it will be necessary to realign the converter to suit the new output frequency.

Provided the m.w. receiver used has a reasonable performance, excellent results should be obtained and worldwide reception is possible. ☐

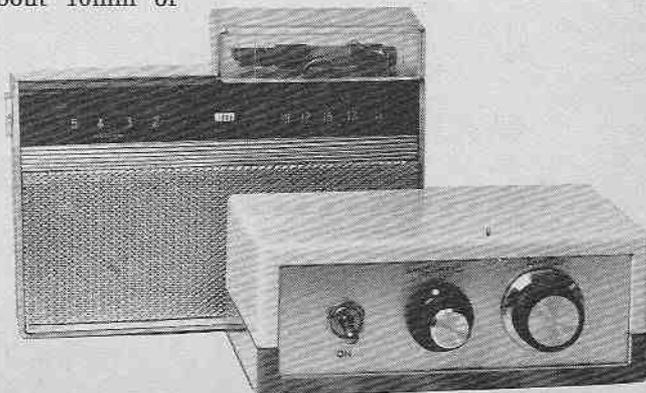How to use the Converter with a transistor radio. Note the position of the coupling coil. This is near the internal ferrite rod, and *in line* with it.



Everyday News



THE ALL-ELECTRONICS SHOW 1979

JAM-PACKED, that just about describes the three days of the "All-Electronics Show" this year at the Grosvenor House Hotel in London from February 27 to March 1. With attendances topping 19,000 this is 50 per cent up on last year according to show organisers, a physical impossibility it seemed at the time!

Exhibitors numbered around 215 with a heavy bias on component manufacture. It was good to be able to fiddle with many components that one can only normally see in catalogues. RS Components had over 400 new items on show, introduced since last year's show.

Gould Instruments decided to launch its new Alpha IV DMM at a press reception in the show. This 3 $\frac{1}{2}$ -digit meter has 25 ranges for just over £100, the l.c.d. readout giving long battery life. Gould's OS5300B scope might be a bit expensive but could prove invaluable to the TV service engineer, being able to analyse line-by-line as well as digital signals exemplified by the teletext services.

Old-established Wayne Kerr still produce a wide range of r.f. and a.f. bridges but featured this year was the B605 automatic component bridge for L, C, R, D and Q functions using, needless to say, a microprocessor. Meter makers Bach-Simpson highlighted its model 463 DMM with 3 $\frac{1}{2}$ -digit $\frac{1}{2}$ in high l.c.d. readout with 200 hour continuous operation capability from internal 9V alkaline battery. B-S's 710 Compact frequency counter covers 10Hz to 60MHz with 1Hz resolution from a 6-digit l.e.d.



display, and weighs only 12oz. An ac adaptor is supplied and several optional extras are available.

Tools and suchlike were not neglected, with Tele-Production showing its mains-operated and low voltage soldering irons including thermostatically controlled versions adjustable to predetermined temperatures.

Lektrokit exhibited wire-wrapping tools and all the associated bits and pieces while OK Machine and Tool had a selection of pliers, cutters and the like which every DIY electronic enthusiast would love to have in his workshop.

Microprocessors were to be seen everywhere including the Fairchild 16-bit 9440 with a demo of its Spark 16 single board microcomputer. AMI Microsystems featured its S2000A single chip microcomputer designed to operate a vacuum fluorescent display. Siliconix displayed the latest in VMOS power FET's including high voltage devices such as the 350V VN35JA and 450V VN45JA in TO3 packages, both rated at 4A.

IIT Meridian was all lit up with "the brightest devices available", in the form of the new range of Stanley l.e.d.s. Four colours are in production in various configurations. Germanium Power Devices Inc attracted a lot of attention now that it is producing germanium devices for replacement purposes, mainly by using plants that have already been written off by other manufacturers.

Potential visitors to next year's Show may like to note the later dates of April 29 to May 1.

MATTER OF DEGREE

The Institute of Electronic and Radio Engineers is resisting pressure from the Council of Engineering Institutions to make an honorary degree mandatory for corporate membership as a chartered engineer.

The IERE would like to retain the ability to grant corporate membership to those with proven engineering aptitude and achievement, arguing that there is no invariable connection between academic qualifications and ultimate engineering achievement.

Getting the message

The UK's first computer-controlled telex gateway exchange is now in service handling autotelex calls between the UK and more than 100 other countries. The system is supplied by Plessey Controls.

The two earlier non-computerised telex gateways give users access to a million teleprinters in 205 countries. Telex usage is growing at 10 per cent per annum in Europe and 15 per cent beyond Europe.



ANALYSIS

THE ELECTRONIC TELEPHONE

If asked which country is likely to have the first national all-electronic telephone system in the world most people would probably say the United States. Other choices might be Japan, W. Germany, France, even Britain. In fact the answer is Saudi-Arabia who will go all-electronic by 1981.

All very well, you might say, for an oil-rich Arab State to indulge in such luxuries. What other country with a population only that of Greater London could afford to spend £1,500 million on a technological up-date?

Well, money is an important factor, of course, but it is not the only one. Paradoxically, the most advanced nations are handicapped in implementing new innovations while the "backward" nations, because of their former backwardness, can start with almost a clean slate. Countries with well-developed and long established telephone systems like the United States and Britain have enormous problems of interfacing the most modern equipment into their existing networks.

The electronic exchange is now fully established as a reliable successor to the electro-mechanical system which has served so well for the past few decades. It is smaller, less costly, not so much in first cost but in maintenance costs over its service life, and can provide many more facilities for the user.

Up till now the BPO has been concentrating on electronics at their own telephone exchanges and only at the larger of the thousands of private automatic branch exchanges (PABXs). Now the small business will be able to have MPU-controlled PABX systems with the phased introduction of BPO's Customer Digital Switching System No. 1 (CDSS1). It is a modular system expandable to 20 exchange lines and 100 extensions now being manufactured by GEC and Plessey. It replaces the existing PABX systems first introduced in 1952 and of which 40,000 are in service.

The CDSS1 has a touch-sensitive panel instead of keys for the operator and includes a visual display unit. Because it is electronic all sorts of tricks can be played on it and users can program it to suit their own requirements. The equipment will come into service first in London and Scotland, then in other areas over a period of years.

On a smaller scale but important to every telephone user is the prospect of an electronic replacement for the present carbon granule microphone, unaltered in operational principle for over 100 years. Here again, there is the problem of compatibility, the new unit having to meet the requirement that it must be a direct replacement unit demanding no modification to the telephone handset. The electronic replacement will, however, give better quality speech over a considerably longer period.

But with well over 20 million private telephones in service in the UK it will be many years before you get your new electronic microphone. You can't expect to change everything overnight.

Brian G. Peck

Wakey—Wakey

Subscribers to Paris telephone exchange are now able to get early morning wake-up calls by computer. The service operates by dialling a special "wake-up" number and then dialling your own number and the time you need the call in standard 24-hour clock format (e.g. 0630 for 6.30 a.m.).

Heavy sleepers who don't respond are called a second

time after an interval of 10 minutes. The computerised system guarantees the call within one minute of the requested time and can currently handle 10,000 wake-up calls daily.



Some 45,000 different integrated circuits are listed in the 1979 edition of "The IC Master" published in the USA.

TREASURE HUNTING BOOM

Amateur treasure hunting with the aid of metal detectors will continue to boom for the next seven years in Europe according to market researchers. Savo Electronics of Inverness, Scotland, a manufacturer in this specialised field is planning to treble work-force and turnover in the next three years to meet the demand.



Bubble memories are expected to have a market of some £250 million a year by 1985 according to a Rockwell International spokesman. Rockwell recently launched a 256k bubble memory in Europe and is expected to market a million-bit unit this year.



NEW MEMBER

Former US Secretary of State Henry Kissinger is acting as a consultant to the board of Britain's GEC group of companies. The appointment coincides with GEC's increased involvement in business in the USA through acquisition of US companies such as A. B. Dick and joint ventures such as GEC-Fairchild.

LINK-UP

What is thought to be the first-ever marriage by computerised data link is reported from Las Vegas. Bride and groom had met through a business network.

The happy couple stood before a VDU terminal with the presiding Minister some 2,000 miles away. Questions and responses were keyed in at each end of the networks.

The young couple are said to have conducted their courtship via terminals and became engaged before even seeing each other.



Food-chain Sainsbury is to try out computer-linked electronic checkout systems at two branches this year. An IBM system is to be fitted at Crawley in June and an NCR system at Chippenham in September.

NEWS FROM SPACE

Solar power

A solar power panel with an output of over 1A at 14.4V has been developed by Ferranti Electronics Ltd. Designated the MST 300, it is said to be suitable for industrial, professional or domestic use and is competitive with imported units. It uses 36 silicon cells, each 3 inches in diameter connected in series.

On a larger scale Ferranti is building a 2kW output system under a contract awarded by the EEC. It will use 160 solar panels, the d.c. output of which will be stored in a battery bank which, in turn, powers an inverter developing 240V 50Hz as a continuous mains supply. This is virtually a feasibility study to determine the effectiveness of solar power generation in northern latitudes.


Amateur satellite

The UK's first amateur scientific satellite is to be built at the University of Surrey. It will be launched into polar orbit at a height of 900km in early 1981 if all goes well and will allow radio amateurs throughout the world to study propagation conditions.

Industry support for the £150,000 project is promised from British Aerospace, Ferranti, Marconi, MEL, Philips and Racal.

We have been informed that an Orbital Predications Calendar for Oscar 7 and 8 and both Russian Satellites, RS1 and 2, are now available in a single book form, price £2.15 (including postage). Readers with a "Pet" computer can also obtain a Predications Programme Tape for any satellite for £2.15 including postage.

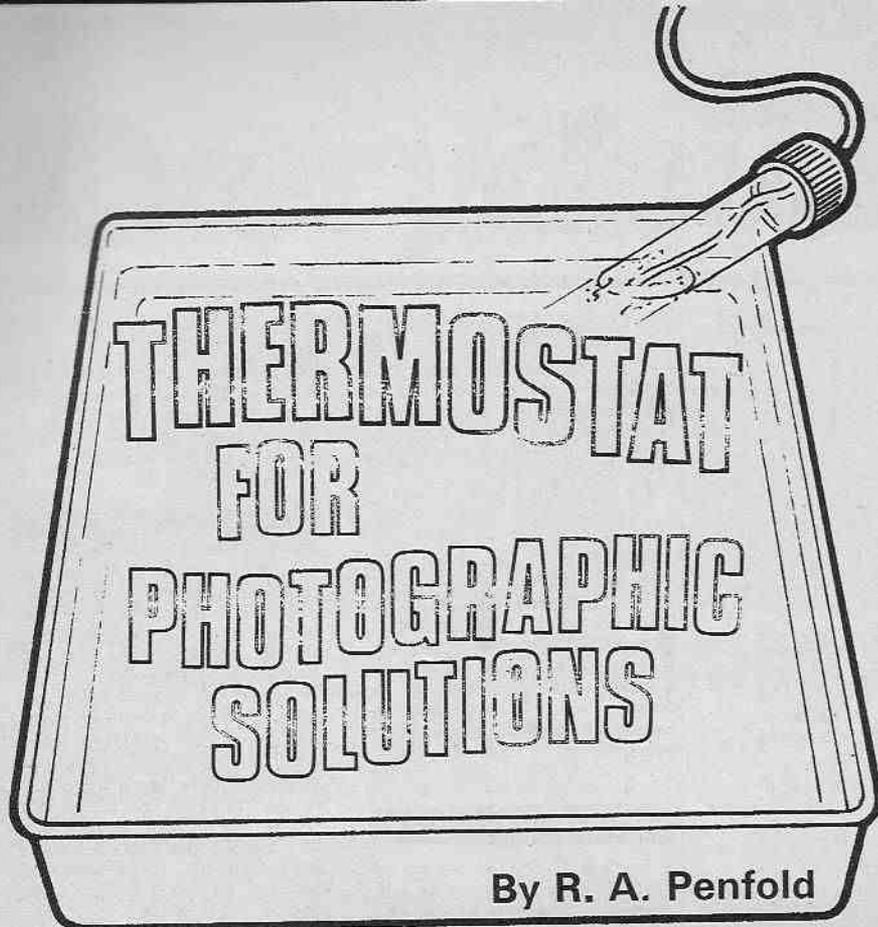Orders and other enquiries should be sent to: Honorary Secretary, AMSAT-UK, 94, Herongate Road, Wanstead Park, London E12 5EQ.



SENSOR

An LM3911N temperature controller/thermometer i.c. is employed as the basis of the project. This has an internal circuit arrangement as detailed in the block diagram of Fig.1a.

The temperature sensor relies on the fact that the voltage produced across a forward biased silicon diode varies with applied temperature. It actually varies by about 2 or 3mV per degree centigrade, with increased temperature causing decreased voltage, and *vice versa*.

The sensor is actually quite a sophisticated circuit which uses two transistor base/emitter junctions as sensing diodes, and these have different operating currents. A differential amplifier multiplies the difference in the output voltages of the two sensing transistor junctions, and produces an output voltage which varies by 10mV per degree centigrade. This gives a highly linear relationship between output voltage and applied temperature, which enables the device to be used as the basis of an accurate thermometer, but is admittedly of minor importance in the present application.

THIS DEVICE is primarily intended for precisely controlling and maintaining the temperature of photographic solutions.

It is important that the solutions should be maintained at a constant temperature during the printing process when dealing with colour or black and white, but colour printing is by far the more critical of the two. Thus a highly accurate thermostat of this type is of particular value when undertaking colour work.

The usual method of controlling the temperature of photographic solutions is to use a thermostatically controlled dish warmer. This system often lacks extreme accuracy as dish warmers are usually fitted with a mechanical thermostat of comparatively low sensitivity, and it is the temperature of the warmer rather than the solution that is actually controlled.

ACCURACY

A high degree of accuracy is obtained here by using an extremely sensitive integrated circuit temperature sensor which is fitted in a probe which is then immersed in the photographic solution. This enables small tempera-

ture changes to be quickly detected, and the warmer to be switched on or off, as appropriate, in order to compensate for this.

The unit will maintain the temperature of the solution to within a fraction of one degree centigrade, but the exact level of performance obtained will vary slightly from one unit to another, and is also affected by other parts of the overall set-up.

The circuit has four preset temperature settings which can be set to any desired levels from below zero to more than 60 degrees centigrade (32 to 140 degrees fahrenheit). Therefore, the unit can be used in many applications other than photography.

OUTPUT VOLTAGE

The voltage to the sensor circuit must be well stabilised, otherwise the sensor output voltage would vary considerably with changes in supply potential. A high quality 6.8V Zener diode is therefore incorporated in the device.

The output from the sensor is coupled to the non-inverting (+) input of an operational amplifier. The diode and the 50 kilohm resistor form the load for the *npn* output transistor of the amplifier,

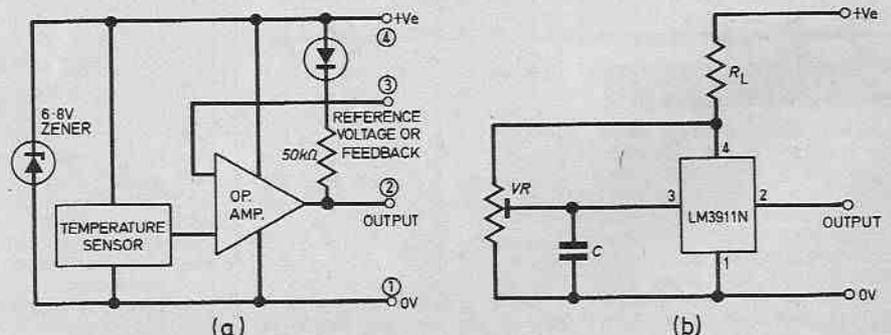


Fig. 1a. Block diagram of the circuit inside the LM3911N temperature controller i.c. (b) Illustrating the method of using the i.c. as a switching type thermostat.

COMPONENTS
approximate
cost £8.50
excluding case

but a higher output current drive can be obtained by connecting a discrete resistor between pin 2 and the unregulated positive supply line.

THERMOSTAT

When the i.c. is used as a temperature controller the inverting (-) input of the operational amplifier is connected to a reference voltage, and the amplifier is actually used as a comparator. The diagram of Fig.1b illustrates the basic method of using the LM3911N as a thermostat.

If the unit is required to produce a controlled temperature of, say, 25 degrees, then VR would be adjusted to provide a voltage at pin 3 of the i.c. which was identical to that generated by the sensor when at a temperature of 25 degrees. Capacitor C is merely required to decouple any hum or noise which would otherwise be picked up at pin 3 of the i.c.

The output potential depends on the capacitive levels of the two input voltages to the comparator. If the non-inverting input is at a higher voltage than the inverting one, the output voltage will be equal to the positive supply rail

potential. If the states are reversed, the output voltage will fall to little more than zero. In practice the circuit is arranged so that the heating element is switched on when the output is high, and switched off when it is low.

OPERATING LIMITS

Thus, if the sensor is below 25 degrees it produces a voltage which is more than that at pin 3 of the i.c. and the heater is turned on. When the sensor rises above 25 degrees it produces a voltage which is lower than that at pin 3 of the i.c., and so the heater is turned off. The sensor voltage has to change by only an extremely small amount in order to change the output state of the comparator, and so the temperature of the sensor is only allowed to drift between extremely narrow limits.


The operating temperature of the circuit can be adjusted over very wide limits by varying the setting of VR, and the LM3911N has an operating temperature range of at least -25 to +85 degrees centigrade.

Resistor R_L is the current limiting resistor for the Zener diode, and it is essential to include this to protect the Zener against an excessive current flow.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Photographic Thermostat is given in Fig.2.

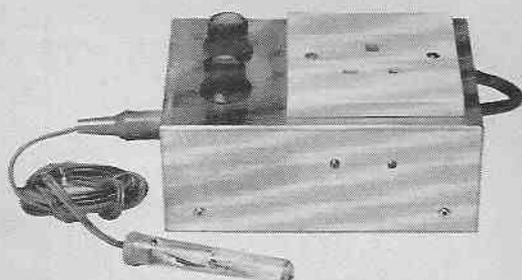A nominal supply voltage of about 11 volts is provided by the simple mains power supply which is comprised of T1, D1, D2 and C1, S1 is the on/off switch.




The reference voltage for the i.c. is produced by R3, R4, and whichever one of the four presets (VR1 to VR4) is switched into circuit by S2. The latter is the temperature selector, and the presets are adjusted to produce the four thermostat temperatures that are required, C3 is the decoupling capacitor.


Resistor R2 is the current limiting resistor for the Zener diode and C2 provides additional smoothing of the stabilised supply.

Transistor TR1 is driven from the output of IC1 and will be switched on when the output is high, or cut off if it is low, R1 is used to increase the drive capability of IC1.

When TR1 is turned on, it activates the relay coil which forms its collector load. A pair of normally open relay contacts are connected in the mains supply to the heating element, and switch the element on when TR1 and the relay are activated. Diode, D3 is a protective diode which quenches the high reverse voltage which would otherwise be produced across the relay coil at it deactivated. Unless suppressed this voltage could easily damage TR1 and IC1.

Fig. 2. Complete circuit diagram of the Photographic Thermostat.

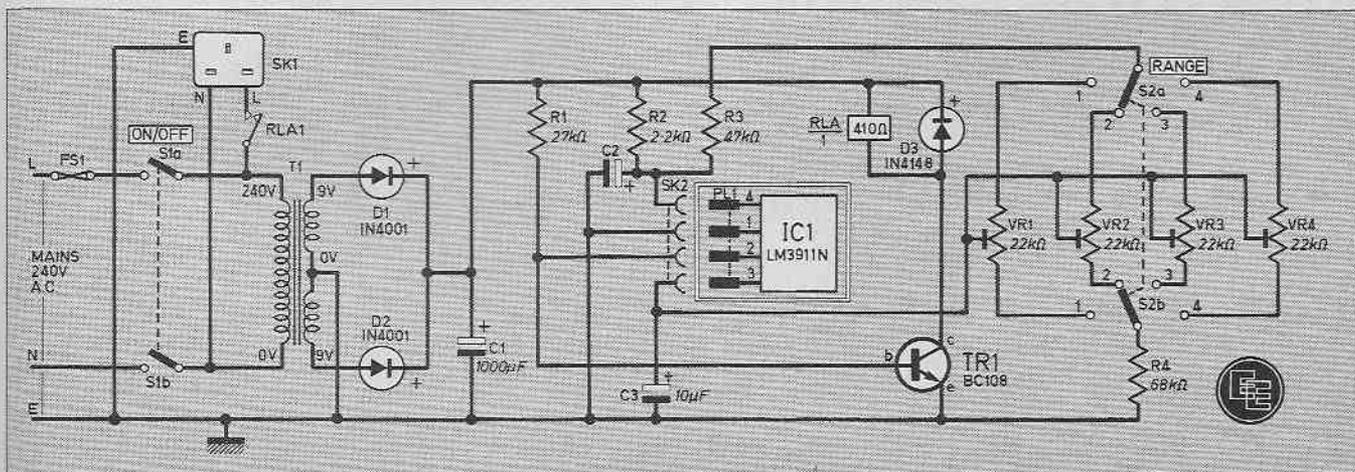

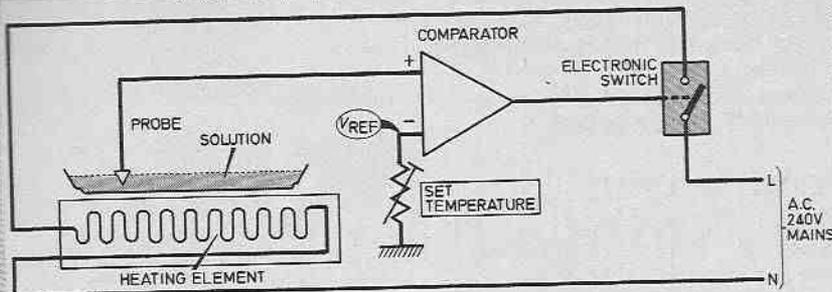

HOW IT WORKS

A special PROBE produces a voltage which decreases with an increase in temperature, (or *vice versa*). This voltage is fed to one input of a comparator, while a variable reference voltage is fed to the other input. If the probe produces a voltage which is higher than the reference voltage, the comparator switches on an ELECTRONIC SWITCH. This in turn switches on the heating element. This action causes the heating element to heat up the solution until such time the temperature causes the voltage from the probe to fall below that of the reference voltage. The comparator then switches off the ELECTRONIC SWITCH and thus the heating element. Because the heating is removed, the temperature of the solution starts to fall, the probe detects this drop, its voltage falls below that of the reference voltage, and the heating element is turned on once again. In this way the temperature of the solution is maintained within very fine limits.

probably be necessary to fabricate a mounting bracket of some kind. An Open P.C. relay having a 6 volt 410 ohm coil was used in the prototype, but any relay having a nominal 6 volt coil resistance of about 185 ohms or more should be equally suitable, but make sure the contacts are of the right type and of suitable current rating.

A piece of 0.1 inch plain matrix board having 14 by 16 holes is used as the mounting bracket for the relay on the prototype, and this has five of the holes enlarged slightly (to about 2mm dia.) to take the lugs on the relay. These are bent over at right angles on the underside of the panel to secure the relay to the panel. The panel is then bolted to the case, and spacers are used to hold the panel a little way clear of the case.

The mains transformer, T1 is mounted on the rear plate of the case, near to S1, using two short 4BA bolts and mounting nuts.

CONSTRUCTION
starts here

the left hand side panel of the case and the probe plugs into this, which is more convenient than wiring it direct to the rest of the unit. This socket requires a main 15mm diameter mounting hole as well as two 3.2mm diameter holes for the 6BA mounting bolts.

The relay is mounted on the front plate of the case, and it will

STRIPBOARD

All the other components are assembled on a 0.1 inch pitch stripboard which has 19 strips by 28 holes. Details of this panel are given in Fig.3 which also shows the remaining wiring.

First cut out a board of the correct size using a hacksaw and then make the six breaks in the copper

A suitable case for the unit can consist of a 152×102×64mm (6×4×2½inch) 18 s.w.g. aluminium chassis and baseplate. The base is fixed to the corner pieces of the chassis using four 6BA self-tapping screws, and four cabinet feet are fitted to the baseplate. A mains socket is mounted on top of the box on the right hand side, and this requires two 6BA mounting nuts and bolts. It also requires quite a large cut-out to be made in the case, and this can be achieved using a fretsaw or a needle file.

A solder tag is mounted on one of the fixing bolts for the mains socket to provide a chassis connection.

RELAY MOUNTING

Switches S1 and S2 are mounted to the left of the mains socket, and both these components require a 10mm diameter mounting hole. A five pin DIN socket is mounted on

COMPONENTS

Resistors

- R1 27kΩ
- R2 2.2kΩ
- R3 47kΩ
- R4 68kΩ
- All ¼W carbon ± 5%

Capacitors

- C1 1000µF 16V elect.
- C2 10µF 16V elect.
- C3 10µF 16V elect.

Miscellaneous

- SK1 mains outlet socket (MK type)
- SK2 5 pin DIN socket
- PL1 5 pin DIN plug
- S1 d.p.d.t. rotary mains switch
- S2 2 pole 4 way rotary switch
- RLA 6V 410 ohm coil with one set of mains rated normally open contacts
- FS1 1A fuse, with panel mounting holder
- T1 9.0-9V at 67mA mains transformer

Stripboard 0.1 inch matrix, 19 strips by 28 holes; plain matrix board, 0.1 inch 14 by 16 holes; aluminium chassis with baseplate 152 × 102 × 64mm; small glass tube or similar for probe (see text); silicon grease; twin screened cable or other four way cable; two round control knobs; length of three core mains lead; connecting wire; standard mains plug.

Potentiometers

- VR1 to 4 22kΩ subminiature horizontal presets (4 off)

Semiconductors

- TR1 BC108 silicon npn
- IC1 LM3911N temperature controller
- D1 1N4001 silicon
- D2 1N4001 silicon
- D3 1N4148 silicon

See
**Shop
Talk**
page 287

MAGENTA ELECTRONICS LTD

EC4, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS DE13 0UL
PHONE 02 83 65435. 9 a.m.-12.2 p.m.-5. MON.-FRI. Callers by appointment.

ALL PRICES INCLUDE VAT AND
FIRST CLASS POST. ADD 25p TO
ORDERS UNDER £5.



E.E. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Appropriate hardware—nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply—You construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. *PROJECT INSTRUCTIONS ONLY SUPPLIED AS EXTRA 39p EACH*.

- ONE TRANSISTOR RADIO. Mar. 79. with Amplifier & Headset. Less case. £5.84.
- TIME DELAY INDICATOR. Mar. 79. £4.08.
- VERSATILE POWER SUPPLY. Mar. 79. £7.36.
- CHOKE WARNING DEVICE. Apr. 79. £5.05 case 71p.
- AUDIO MODULATOR. Feb. 79. £1.44 less case and pins.
- LW CONVERTER. Feb. 79. £3.98. case £1.49.
- THYRISTOR TESTER. Feb. 79. £2.98.
- ADJUSTABLE PSU. Feb. 79. £21.54. Case (horizontal layout) £3.54 extra.
- I'M FIRST. Jan. 79. £3.06 less case.
- LIGHTS REMINDER. Jan. 79. £4.16 less case.
- CONTINUITY TESTER. Jan. 79. £2.91 less case.
- FUZZ BOX. Dec. 78. £4.36.
- VEHICLE IMMOBILISER. Inc. PCB. Dec. 78. £3.77 case extra 71p.
- WATER LEVEL ALERT. Nov. 78. £4.82.
- "HOT LINE" GAME. Nov. 78. £4.23 less case & rod.
- AUDIO EFFECTS OSCILLATOR. Nov. 78. £2.75 inc. board.
- SUBSCRIBERS TELE TEL METER. Nov. 78. £15.55 case extra £3.75.
- FUSE CHECKER. Oct. 78. £1.51.
- C.MOS RADIO. Oct. 78. £7.79.
- TREASURE HUNTER. Oct. 78. £14.44 less handle & coil former.
- GUITAR TONE BOOSTER. Sept. 78. £4.13 inc. p.c.b.
- SHAVER INVERTER. April 79. £10.99.
- TRANSISTOR TESTER. April 79. £3.18.
- TOUCH BLEEPER. April 79. £2.98.
- SOUND TO LIGHT. Sept. 78. £5.99 FILTER. £1.25.
- SLAVE FLASH. Aug. 78. £2.66 less SK1.
- LOGIC PROBE. July 78. £2.29.
- IN SITU TRANSISTOR TESTER. June 78. £4.23.
- VISUAL CONTINUITY CHECKER. June 78. £2.96 inc. probes.
- FLASHMETER. May 78. £11.29. less calc and diffuser.
- POCKET TIMER. April 78. £2.82.
- WEIRD SOUND EFFECTS GENERATOR. Mar. 78. £3.64.
- CHASER LIGHT DISPLAY. Feb. 78. £19.78. inc. p.c.b. case extra £3.54.
- AUDIO VISUAL METRONOME. Jan. 78. £4.22.
- RAPID DIODE CHECK. Jan. 78. £1.97.
- AUTOMATIC PHASE BOX. Dec. 77. £9.45 inc. p.c.b.
- VHF RADIO. Nov. 77. £11.46.
- ULTRASONIC REMOTE CONTROL. Nov./Dec. 77. £13.75.
- TREASURE LOCATOR. Oct. 77. £3.77 case extra. £2.32. Less handle, etc.
- ELECTRONIC DICE. March 77. £4.20.
- SOIL MOISTURE INDICATOR. June 77. £3.09 inc. probe.
- PHONE/DOORBELL REPEATER. July 77. £5.27.
- SHORT WAVE RECEIVER. Aug. 77. £10.98 case extra £1.49.
- CAR BATTERY STATE INDICATOR. Sept. 78. £1.54 less case inc. PCB.
- R.F. SIGNAL GENERATOR. Sept. 78. £15.20 less case.
- TRANSISTOR TESTER. Oct. 77. £6.34 case extra £3.55.
- ELECTRONIC TOUCH SWITCH. Jan. 78. £1.44.
- ADD-ON CAPACITANCE UNIT. Sept. 77. £4.46.

TEACH - IN - 78 COMPLETE KIT £14.98

INCLUDES FREE COMPONENT IDENTIFICATION CHART. TEACH-IN REPRINTS EXTRA 39p. EACH PART. ALL 12 PARTS AVAILABLE.

1979 ELECTRONICS CONSTRUCTORS CATALOGUE

HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS. PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS. FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS CATALOGUES. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!
WRITE TODAY ENCLOSING 4 x 9p STAMPS.

- BUZZER. 6V 74p. 12V 77p.
- F.M. INDOOR AERIAL. 49p.
- TELEPHONE PICK-UP COIL. 65p.
- SPEAKERS. Miniature 8 ohm 79p. 64 ohm 89p. 80 ohm £1.15.
- EARPIECES. Crystal 38p. Magnetic 15p.
- STETHOSCOPE ATTACHMENT fits our earpieces 58p.
- HEADPHONES. MONO. 2K Padded Superior Sensitive. £2.98.
- HEADPHONES. STEREO. 8 ohm. £3.85.
- INTERCOM. 2 STATION. £6.45.
- MICROPHONE DYNAMIC 600 OHM CASSETTE TYPE with 3.5mm jack plug and plastic desk stand. £1.25.
- MULTIMETER TYPE 1. 1,000 o.p.v. with probes 2" x 3/4" x 1" £5.95.
- MULTIMETER TYPE 2. 20,000 o.p.v. with case and probes 5" x 3/4" x 1 1/2" £12.45.
- ANTEX X25 SOLDERING IRON 25W. Ideal for electronics £3.95.
- SOLDERING IRON STAND. ANTEX ST3 £1.84.
- DESOLDER BRAID. 82p.
- HEAT SINK TWEEZERS. 13p.
- DESOLDER PUMP. Easy to use £5.98.
- SIGNAL INJECTOR. £4.98.
- DENTISTS MIRROR. Adjustable £2.15.
- JEWELLERS EYEGLASS. 93p.
- TRIPLE MAGNIFIER. £1.48.
- SPRINGS—SMALL 100 Assd. 98p.
- CROC CLIP TEST LEAD SET 10 leads with 20 clips 96p.

DOING IT DIGITALLY

New Series—complete kit or separate parts IN STOCK NOW for FAST DELIVERY by FIRST CLASS POST. All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE TTL and COMPONENT IDENTIFICATION CHART. Follow this educational series—start today—and learn about digital electronics. SEND £22.95 for the TTL TEST BED. £3.75 for ADDITIONAL COMPONENTS (6 months).

New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself—computers, oscilloscopes, transceivers etc.... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.

Soldering Iron offer FREE



New Heathkit CI 1265 Digital Tach/Speedometer.


Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.

To: Heath (Gloucester) Limited, Dept. EE 5 79 Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name _____
Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

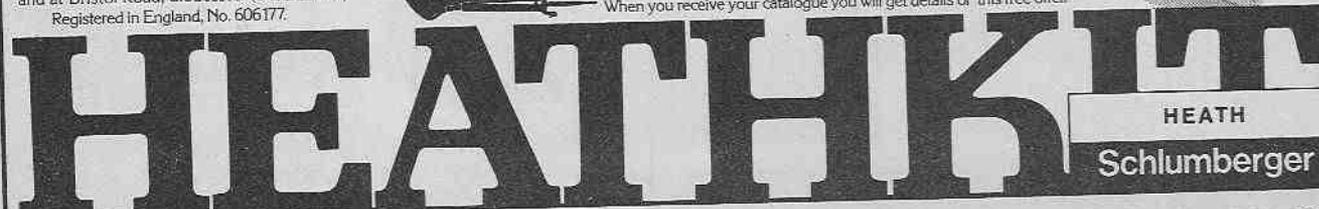When you receive your catalogue you will get details of this free offer.



THERMOSTAT for PHOTOGRAPHIC SOLUTIONS


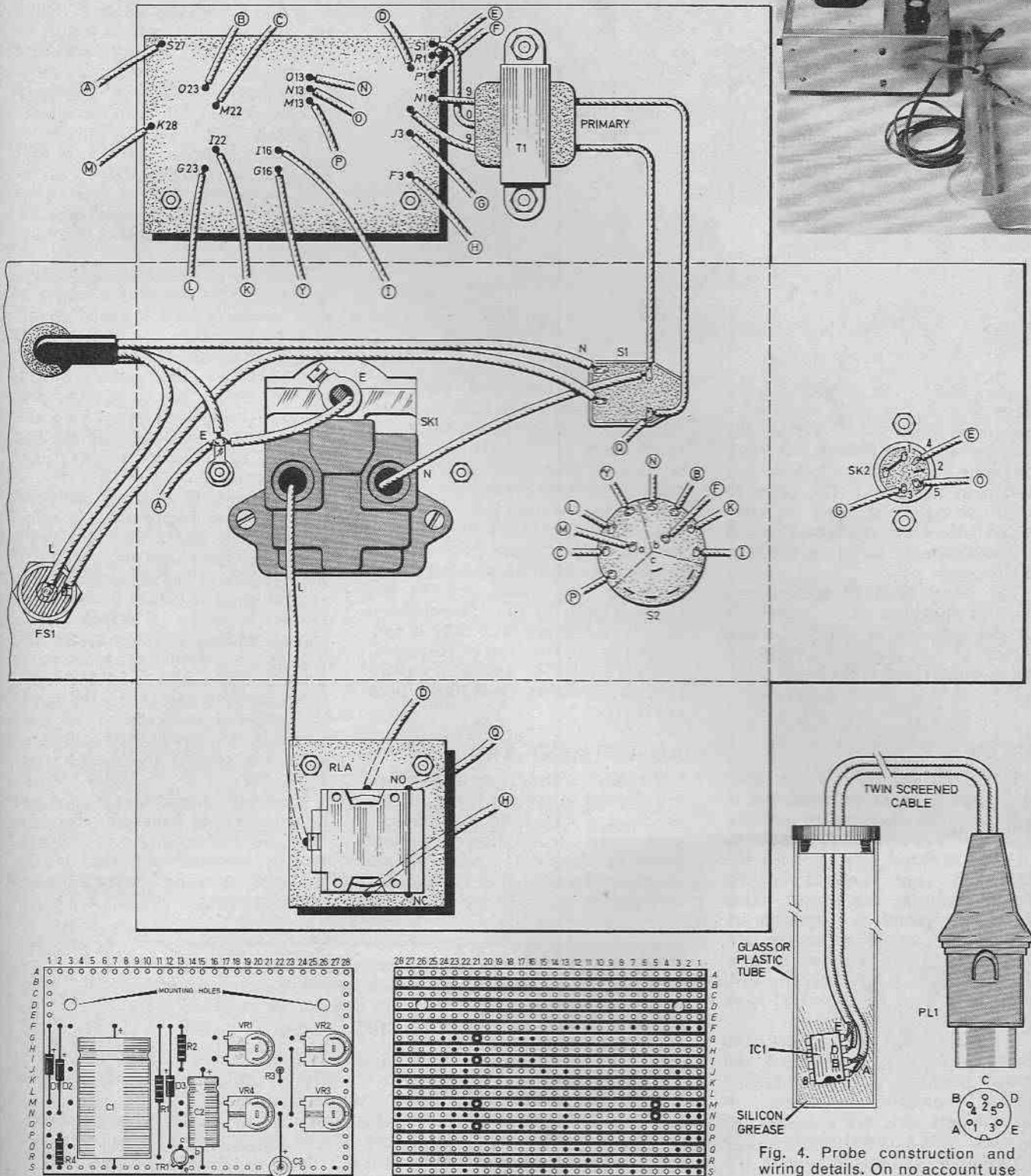


Fig. 3. Complete wiring details for the unit, showing the stripboard layout and other wiring. There is nothing critical about the layout and could be varied as required. When wiring up the mains socket, use mains rated connecting wire and insure that all connections are well insulated. The probe socket, SK2 needs particular care when wiring otherwise an incorrect connection will damage the i.c. The socket is shown looking at the tags. Note the earth tag connection.

Fig. 4. Probe construction and wiring details. On no account use a socket for this i.c.—it would rather defeat the whole object of the unit. Providing you are quick when soldering, no damage should occur to the i.c. A convenient length for the lead would be about four feet.

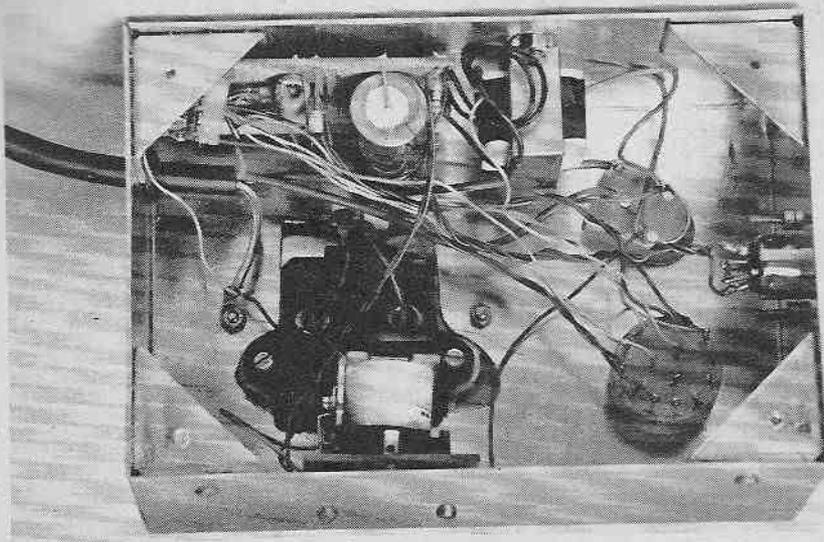

strips. Next the various components and the single link wire are soldered into position on the board, and the two 3.2mm diameter mounting holes are drilled in the board. The point to point wiring must then be completed before the component panel is mounted next to T1 on the rear of the case.

The panel must be spaced well clear of the case so that there is no risk of any of the underside wiring of the board short circuiting through the metal casing.

PROBE

If the i.c. sensor is to be used in liquids it must be mounted in a waterproof housing to provide electrical insulation, but it must be in good thermal contact with the liquid. A poor thermal contact would result in the sensor being slow to respond to temperature changes and would reduce the performance of the set up. A poor thermal contact between the dish warmer and the solution will have the same effect.

A suggested form of construction for the probe is shown in Fig.4, and this is based on a small tube-like plastic container (such as that cake decorations are supplied in) or a test tube and cork stopper.

Begin by drilling a hole in the stopper to take the connecting cable. Twin individually screened cable was used by the author, but any four way cable not necessarily screened should be suitable. A short length of cable is threaded

through the hole and then the cable is connected to IC1.

Some silicon grease is forced to the bottom of the tube and some of this is also spread over IC1. The i.c. is then pushed down into the bottom of the test tube, and the silicon grease will ensure a good thermal contact between the outside of the tube and pins 5 to 8 of the i.c. (which provide the thermal path to the silicon chip). Finally, a five pin DIN plug is connected to the free end of the cable, and care must be taken to ensure that all the connections to the plug are correct.

ADJUSTMENT AND USE

The dish warmer, or other heating device) is merely plugged into the mains socket on the thermostat, any temperature control fitted to the heater must be set to maximum so that it is rendered ineffective.

Probably the easiest way of adjusting the presets is to use the following procedure. Start with all four presets adjusted fully clockwise and S2 set to position 1. Allow the dish warmer to heat a dish of water to the lowest required thermostat temperature, and then slowly adjust VR1 in an anti-clockwise direction until the heater is switched off.

It is essential that it is not adjusted any further than is necessary to switch off the heater, as this would cause a significant reduction in the thermostat temperature.

Next S2 is switched to position 2, the dish of water is allowed to rise to the second lowest thermostat temperature, and then VR2 is adjusted just far enough in an anti-clockwise direction to switch off the heater. The same basic procedure is then used to set VR3 and VR4 to the second highest and highest thermostat temperatures respectively.

Of course, if all four temperatures are not required, it is quite in order to use a switch having fewer positions and omit some of the presets. If more temperatures are required it would probably be better to wire a 22k Ω linear potentiometer in place of S2 and VR1 to VR4, rather than use more presets and a switch having more positions. The potentiometer would be mounted in place of S2, and would have a simple dial calibrated with the desired thermostat temperatures.

In some applications it might be necessary to have the relay contacts close when a rise in temperature is detected, and this can be achieved by using normally closed relay contacts. □

RECORD REVIEW

TITLE Long Live Short Wave!
LABEL Trans—Island Productions Ltd.
PRICE LP £3.50 Cassette £3.50 inc. p & p
PLAYING TIME Approx 55 minutes

THIS, our first-ever LP for review, is an attempt to introduce the listener to the fascinating hobby of DX'ing and short wave listening.

The first side contains an introduction as spoken by the BBC's World Service most respected and famous presenter, who also by chance happens to be a radio amateur of long standing; Henry Hatch. It continues with such interesting topics as; identifying different modes of transmissions, the aerial and how to operate a short wave receiver, the QSL card and reporting, and an explanation of the different frequency bands, etc. PO Box 24, Douglas, Isle of Man.

15-240 Watts!

HY5

Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input impedance 4-7k Ω at 1kHz.


OUTPUTS: Tape 100mV; Main output 300mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0.1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.

Price £6 27 + 78p VAT P&P free.

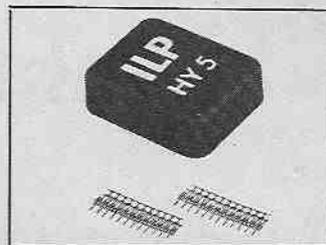

HY30

15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator


SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0.1% at 1-5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price £6 27 + 78p VAT P&P free.

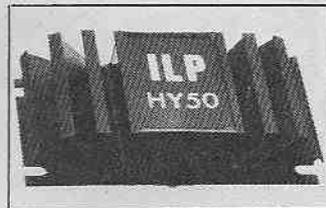

HY50

25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: **INPUT SENSITIVITY** 500mV

OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 25W

at 1kHz. **SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm

Price £8 18 + £1 02 VAT P&P free

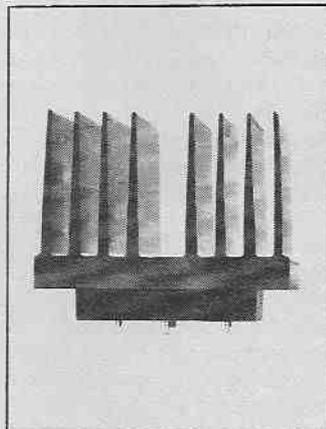

HY120

60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS:

INPUT SENSITIVITY 500mV.


OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 60W

at 1kHz. **SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 25V

SIZE 114 50 85mm

Price £19 01 + £1 52 VAT P&P free.

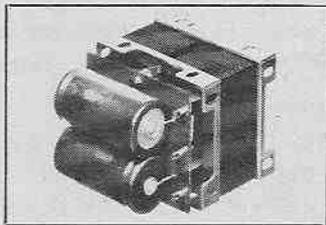

HY200

120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS:

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.05% at 100W

at 1kHz. **SIGNAL/NOISE RATIO** 96dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

SIZE 114 50 85mm

Price £27 99 + £2 24 VAT P&P free.

HY400

240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.1% at 240W

at 1kHz. **SIGNAL/NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

INPUT SENSITIVITY 500mV **SIZE** 114 100 85mm

Price £38 61 + £3 09 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £6 44 plus 81p VAT. P/P free.

PSU60 suitable for two HY50's £14 58 plus £1 02 VAT. P/P free.

PSU70 suitable for two HY120's £14 58 plus £1 17 VAT. P/P free.

PSU90 suitable for one HY200 £15 19 plus £1 21 VAT. P/P free.

PSU180 £25 42 + £2 03 VAT.

B1 £20 48 + £2 06 VAT.

P. & P. FREE U.K. ONLY

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,

**GRAHAM BELL HOUSE,
ROPER CLOSE, CANTERBURY,
KENT, CT2 7EP. Tel: (0227) 54778.**

Please Supply _____

Total Purchase Price _____

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number _____


Name and Address _____

Signature _____

Regd No. 1032630.

The Extraordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

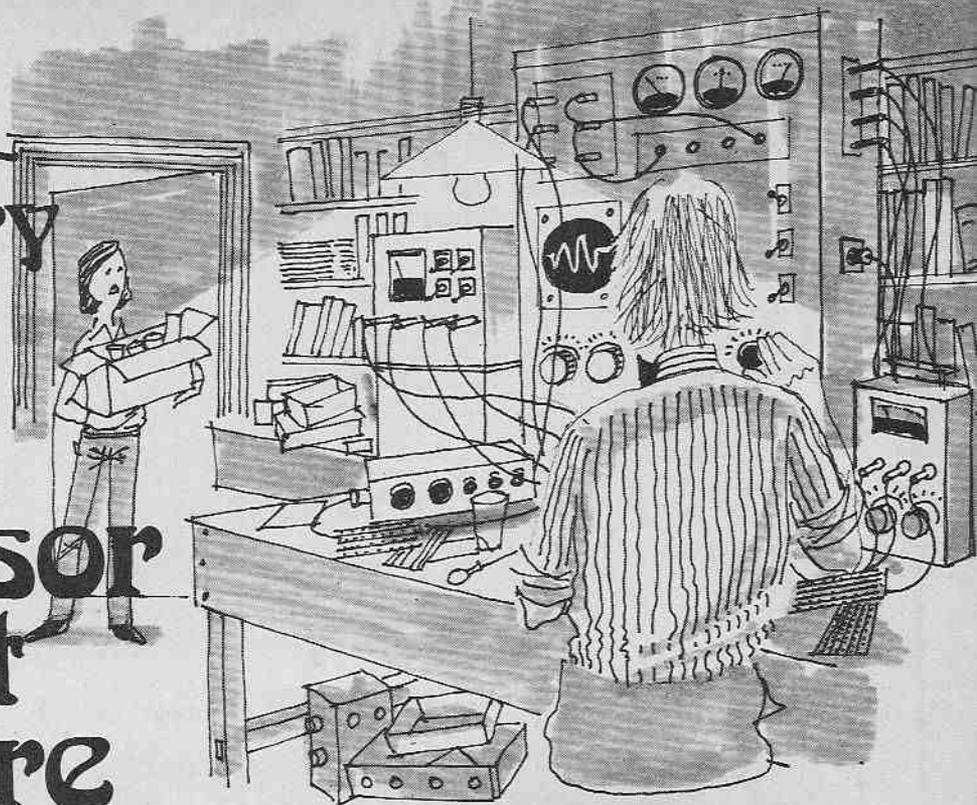

A TEAM of the Prof.'s experimental robots have constructed an enormous vacuum chamber. It is so big that, by wearing special suits similar to space-suits, Bob and the Prof. can go inside and carry out experiments in a simulated space environment.

From outside the capsule Bob watched as the robots used electronically controlled energy, laser and electron beams and other vacuum techniques to fabricate his space suit under vacuum conditions to avoid atmospheric contamination of the welded joints. He was eager to learn more about lasers and energy beams and could hardly wait to put on his space suit and enter the vacuum chamber.

AIR-LOCK

At last, after a series of careful tests, the suit was ready and the Prof. brought it out through the air-lock and instructed Bob on how to put it on, to check against leakage and other safety precautions such as a check on the oxygen reserves and power supply.

"An interesting technical point about these suits," the Prof. told Bob, "concerns the 'constructed volume joints'. Each of the joints is so constructed that movement

does not result in change in the volume of the suit. This is a precaution which should be taken in construction of all suits where there is an appreciable pressure differential between the interior and the exterior, and naturally this applies even more to diving suits where the pressure differential can be much greater than for a space suit. At last, you're ready", The Prof. showed Bob how to operate the air-lock and conducted him into the vacuum chamber.

LIGHTER THAN AIR

"That's strange, Prof." Bob remarked once they were inside, "I feel lighter inside the vacuum chamber than outside it, and I was expecting the opposite. Lacking the natural buoyancy provided by normal air pressure I should seem to be a little heavier if anything, but even with the space suit, oxygen bottles, power supply unit, radio intercom, all these things I'm carrying, yet I still seem to be lighter than I was before I put the space suit on! How can this be so?"

"I wondered when you'd notice that, Bob. It is the result of my experimental weight-control device which is operating within the vacuum chamber to compensate

for the extra weight of the space suit and life-support system."

NEGATIVE WEIGHT

He showed Bob a control knob set on one of the control panels of the internal control console of the vacuum chamber. As the Prof. turned the knob, Bob began to feel very heavy, then light again. He noticed that the calibrations on the weight control went all the way down to zero, then beyond that were some "negative" calibrations, but a small piece of metal set into the panel prevented the control from going into the "negative" region.

"Can the control be turned beyond the metal stop to give negative weight, Prof.?"

The Prof. used a small key and the metal stop retracted inside the panel, but before Bob could indulge any thought of turning the control to give a negative weight, the stop popped up again as the Prof. took away the key.

"By using this key it can be done, whenever I wish to," the Prof. told Bob, "but the stop prevents the control from being set to a negative value by accident." Bob was fascinated by this new control. "Before you learn about



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE


correct at 28.3.79
TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. or quote
Access/Barclaycard No. and post to TUAC LTD. 121
Charlmont Road, London SW17 9AB. We accept phone numbers
from Access/Barclaycard Holders, Phone 01-672 9080.

NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS


Featuring
Electronic Short Open & Thermal Overload Protection.

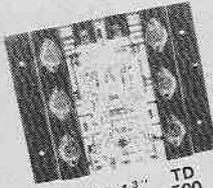Brief Spec.
Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25 K Ohms
Frequency Response 20 Hz-20 KHz
Hum & Noise - 100 dB Relative full output



7" x 9" x 1 1/2" TD 500


T.H.D. at full power 0.1%	
T.D. 500 300W into 2 Ohms	
220W into 4 Ohms	
140W into 8 Ohms	£45.00
Power supply P.S. 300	£30.00
T.D. 150 150W into 4 Ohms	
100W into 8 Ohms	£26.25
Power supply P.S. 150	£18.50
T.D. 150. 60 Version 60W into 8 Ohms	
40W into 15 Ohms.	£17.75
Power supply P.S. 60	£15.50
Note P.S. 300 will drive 2 T.D. 150 amplifiers	

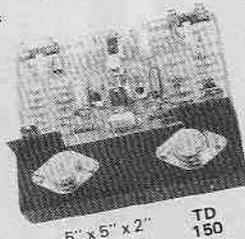

5" x 5" x 2" TD 150

All output ratings are R.M.S. continuous sine wave output.

AMPLIFIER MODULES

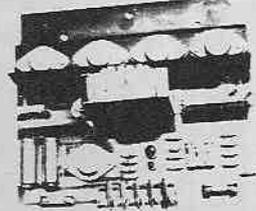

SPEC. INPUT
SENSITIVITY 60 mV
for full output
Frequency response
20 Hz-20 KHz
HUM & NOISE - 70 dB

TL30 5" x 5" x 2"	£13.25
* 35 watt 10 amp output transistors	
TL60 5" x 5" x 3"	£18.50
* 60 watt R.M.S. continuous sine wave output.	
* 2 R.C.A. 110 watt 15 amp output transistors	
TL100 5" x 5" x 3"	£21.50
* 100 watt R.M.S. continuous sine wave output	
* 2 R.C.A. 150 watt 15 amp output transistors	
TP125 7" x 6 1/2" x 3"	£27.50
* 125 watt R.M.S. continuous sine wave output	
* 4 R.C.A. 150 watt 15 amp output transistors	


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSM1

- Full wave control
- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as above without sound triggering

£14.00

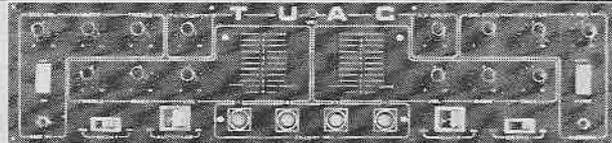

STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R.I.A. comp.) Flat 50mV at 1kHz. Bass controls ± 18 dB at 60Hz. Treble controls ± 18 dB at 15kHz.

OUTPUT: Up to 3 volts (± 12 dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz \pm dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions. Size: 25in long x 6in high x 3in deep

Mono Disco Mixer with autofade £49.00

£149.00

3 CHANNEL LIGHT MODULATOR SILMB


- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W
- Full wave control

£20.75

Single Channel Version 1500 Watts

£9.75

POWER SUPPLIES

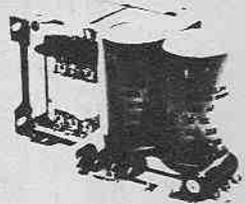

Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply.


PS250 for supplying 2 TP125s	£30.00
PS200 for supplying to TL100s	£30.00
PS60/60 for supplying 2 TL60s	£30.00
PS125 ± 45 volts for TP125	£18.50
PS100 ± 43 volts for TL100	£17.00
PS60 ± 38 volts for TL60	£15.50
PS30 ± 25 volts for TL30	£11.75
PSU 2 for supplying disco mixer	£7.50

STOCKISTS - CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061-236 0340)
Geo. Mathews, 85/87, Hurst St., Birmingham (Tel 021-622 1941)
Soccodi, 9, The Friars (Tel. Canterbury 60948)
Cookies Disco Centre, 126/128, West Street (Tel Crewe 4739)
Garland Bros. Ltd., Deptford Broadway, London 01-682 4412
Luton Disco Centre, 89, Wellington Street, Luton (Tel Luton 411733)
Session Music, 163, Mitcham Road, Tooling (Tel 01-672 3413).
Mon-Sat 10am to 6pm. Closed Wed.
Electrocare Ltd., Four St., Exeter. Tel. 56687.
Salcoolen Ltd., 43 Borough Rd., Cleveland, Middlesbrough.
(Tel. 242851).
Menhouse Ltd., 82, St. Mary St., Southampton. (Tel 28028)
Electra Centre, 58 Lancaster Road, Preston (Tel. Preston 58488)

TRADE & EXPORT ENQUIRIES 01-672 3137

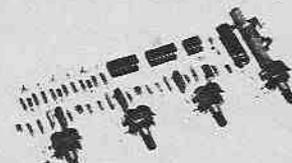ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel

3SDMI £15.25

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
as illustrated



For SILMB £7.25
Size 8" x 4 1/2"



4LSM1 £6.00
Size 6 1/2" x 4 1/2"



FUZZ LIGHTS
Red, Green, Blue,
Amber. £24.50



SILMB £8.25
Combined with 3SDM1
Size 9" x 4 1/2"

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

ELECTRONI-KIT

"EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"

(AUDIO magazine)



THIS IS A POWERFUL RADIO RECEIVER!

The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits, Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, Bird, Metronome, Cds cell light & sound control, Photogun, Light Oscillator, Light Switch, Light and Sound Morse Code, Field Strength Meter, Hygrometer, Sphygometer, Etc., Etc.

Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer, Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator Etc., Etc.

The above is just a selection of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

ALL KITS ARE FULLY GUARANTEED. Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.

150 PROJECT KIT £39.75 60 PROJECT KIT £25.75
120 PROJECT KIT £33.75 30 PROJECT KIT £18.95
100 PROJECT KIT £29.25 15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT, p & p (in the U.K.). Free introduction to the British Amateur Electronics Club. Free list of low price electronics books.

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. EE.


SEE US AT "BREADBOARD", BINGLEY HALL, BIRMINGHAM, 23-26 MAY

ELECTRONI-KIT LTD.

20 BRIDE LANE, LUDGATE CIRCUS,
LONDON EC4Y 8DX (01-353 6430)

BUILD A SYNTHESISER!

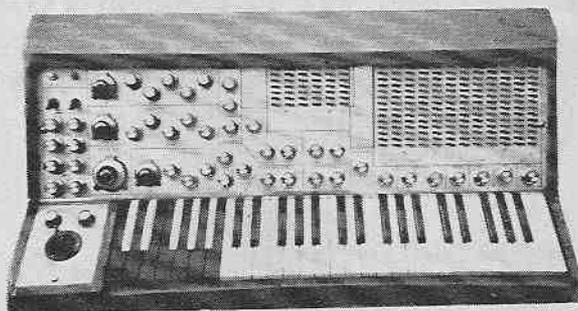**NO SPECIAL SKILLS REQUIRED
SPECIAL EQUIPMENT**



Using **Dewtron** (Reg'd)
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR

ELECTROVALUE

All the many types of components we supply are BRAND NEW and guaranteed and only from manufacturers direct or approved suppliers. No surplus, no seconds

ICS - TTL 7400 series			
7400 13p	7413 22p	7451 14p	7483 58p
7401 13p	7414 60p	7453 14p	7485 74p
7402 13p	7420 14p	7454 14p	7486 27p
7403 13p	7430 14p	7460 14p	7490 40p
7404 18p	7440 14p	7470 24p	7491 71p
7405 14p	7442 58p	7472 24p	7492 48p
7407 22p	7443 60p	7473 23p	7493 40p
7408 18p	7444 60p	7474 23p	7494 66p
7409 18p	7447 70p	7475 45p	7495 57p
7410 14p	7450 14p	7476 32p	7496 63p
		7480 41p	74100 73p
		7482 61p	74104 40p

OUR COMPUTER TAKES GOOD CARE OF YOUR ORDERS

SIEMENS CAPACITORS*

World famous for quality and dependability -
PCB TYPES - 7.5mm PCM 0.001 to 0.015
6p each; 0.015 to 0.047 7p each.
5mm PCM 0.068 8p, 0.1 9p, 0.22 12p.
CERAMIC 2.5mm PCM 0.01 5p, 0.022,
0.033, 0.047 5p, 0.068 6p, 0.1 6p.
ELECTROLYTICS - 1/100, 10/25, 10/63,
100/25, etc. For full range see our current lists.

RESISTORS

1/2, 1/4 watts* 2p each*; metal film, metal
oxide and 1 watt carbon 5p ea*; good quantity
discounts. Magnetic field dependent
from £1.60. Hall Effect from £1.23.

SIEMENS TRANSISTORS

Silicon npn and pnp from 8p ea; LEDs, red
19p; yellow or green from 23p (3 or 5mm).
Photo transistors from 46p.

KEEN PRICES ★ GOOD SERVICE ★ WIDE RANGES

DISCOUNTS

5% if list value of order
over £10
10% if list value of order
over £25. Discounts available
where cash (P.O. or cheque)
is sent with order.

V.A.T. - Add 8% to value of order or
12% with items marked*
(No V.A.T. on overseas orders)
Goods sent post free on C.W.O. orders in
U.K. over £5 list value. If under, add 27p
per order.

Latest 120 page
catalogue on request.

Cash with order (P.O. or cheque payable to Electrovalue Ltd) or your Access or Barclaycard number
TRADE AND INDUSTRIAL ENQUIRIES INVITED

For all round satisfaction - be safe - buy it from ELECTROVALUE

ELECTROVALUE LTD

Dept. EES, 28 St Judes Rd, Englefield Green, Egham, Surrey TW20 0HB.
Phone Egham 3603; Telex 264475.
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage,
Manchester M19 1NA. Phone (061) 432 4945.

'anti-gravity', Bob, you need to learn more about normal gravitational properties. Be careful how you move, I'm setting it to $\frac{1}{6}$ G which is approximately the same as the weight you would experience on the surface of the moon. Under these conditions a little effort can take you a long way.

DIELECTRIC HEATING

"Now some more knowledge of lasers, energy and particle beams will help you go deeper into gravitational theories. We will take advantage of this 'lunar' gravity to move the heavy power supplies of the lasers and electron beams into better positions."

"Prof., why did the robots use several different kinds of energy in fabrication of my space suit? I noticed that they used lasers, electron beams, dielectric heating and other equipment besides. Why not do all of the cutting and welding which is involved by just one of these methods, and save the complication of having the apparatus and power-supplies for each of them?"

"Each method has its own advantages and disadvantages, Bob. For instance, the electron beam can be used for both cutting and for welding."

ELECTRON GUN

The Prof. set a piece of thin sheet metal, and a piece of sheet plastic side by side in the bench vice, and scribed a line on each. Picking up the electron gun, he set it to give a high beam current suitable for cutting or welding, aimed it at the metal sheet and sliced it neatly along the marked line.

"Now don't you think the plastic should be easier to cut than the metal? Try it!" The Prof. handed the electron gun to Bob, who pointed it steadily towards the plastic and switched on. However, instead of the neat, easy cut which he had expected, Bob saw the plastic crumple and deform even in places at which he wasn't aiming the beam. Yet when Bob turned the electron-beam onto the remainder of the metal sheet, he found that he could cut it easily and neatly as the Prof. had shown him.

"This is because the plastic, being a good insulator, does not

conduct away the electrons from the beam, and these tend to accumulate at the surface. The surface of the plastic quickly acquires a strong negative charge and deflects the beam, which is then forced to 'wobble' away from the point at which it is being aimed. This problem does not occur with the metal, as it is earthed and conducts away the charge instantly."

EARTH PROBLEM

"Prof, if this type of equipment were being used in space, where it could not be connected to earth, wouldn't there be a problem even with metal cutting? If the metal could not be earthed, wouldn't it become electrically charged like the plastic and repel the beam and wouldn't the electron-gun also become positively charged?"

"Yes, Bob, this could easily happen. The equipment operator would need to connect a wire from the workpiece to the electron-gun in order to provide a return path for the beam current. If he did not take care to do this properly, a number of problems could easily arise, and it might even be dangerous.

"By touching the apparatus, the operator could himself acquire an electric charge, and this could cause him to produce dangerous discharges upon touching other objects, or to pick up small unwanted objects by electrostatic attraction. Sharp objects such as nails and razor blades could easily be picked up under low-gravity conditions, and could do a lot of damage when the person moved around.

"An interesting way of demonstrating deflection of an electron-beam is to make the beam become visible, and this is something which we can easily do in this chamber."

EXCITING ELECTRONS

The Prof. unsealed a small container and held it near to the beam from the electron gun. The beam glowed a greenish-blue colour as it passed near the container.

"I am releasing a small amount of mercury vapour from the liquid mercury in this container. As the electron-beam passes through the mercury vapour, it excites the electrons which are orbiting around the mercury atoms in the vapour.

"These orbiting electrons absorb energy from the electrons of the beam, then re-emit this energy on wavelengths which are characteristic of the mercury atom, causing the characteristic spectral colours of mercury to appear along the path of the electron beam".

VAPOUR TRAIL

The Prof. released a number of different gases, and vapours of elements and volatile compounds, each of which caused the electron beam to show its path in brilliant colours.


"It's amazing Prof., really great! But I would have thought that these vapours would have caused the electrons in the electron beam to scatter as they collided with the vapour molecules, and cause the beam to spread and diverge from its path. Yet I can see that the electron beam keeps to a narrow path all the way across the vacuum chamber. Why is this, Prof?"

"That is a very keen observation, Bob," The Prof. remarked, "It almost seems as if the presence of the vapour assists in keeping the electron beam to a narrow path, rather than scattering the beam as might be expected. This property has been made use of extensively in radar equipment, and the explanation is quite interesting."

Can readers find out the reason for this useful but unexpected behaviour of an electron-beam in the presence of a vapour, before the Prof. reveals all next month? One clue is the behaviour of the beam when Bob tried to use it for cutting plastic.


To be continued

Crossword No. 15—Solution

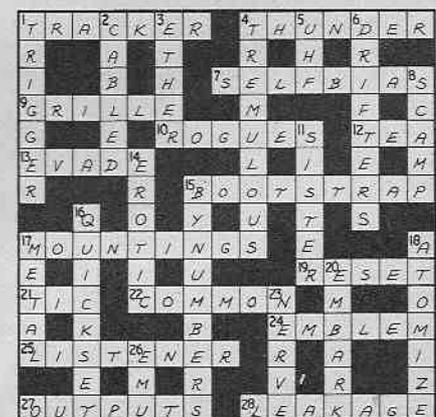

TUNER AMPLIFIER

HI-FI SERIES

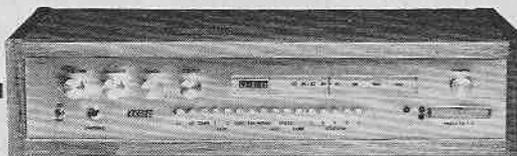

PART 6

WHEN all the work described in the previous article has been completed, the tuner amplifier must be thoroughly checked out in accordance with the detailed procedures given under **Initial Tests** and **Final Testing and Setting Up**. A voltmeter and milliammeter (multimeter) is the only test equipment required.

An additional (and optional) more advanced procedure is also given. This is for the benefit of those with the appropriate test equipment.

Comprehensive voltage tables are included, together with advice on Fault Finding.

This final article in the 2020 Series concludes with some notes concerning operation of the tuner amplifier and constructional details of a simple wooden case to house the chassis.

INITIAL TESTS

1. Mains switch off.
2. Remove 1 amp fuses from holders FS2, FS3.

3. Set all presets to the mid-way position.
4. Turn volume control to minimum. All other controls to mid-way.
5. Connect 8 ohm dummy loads (wirewound resistors 15W rating) across each loudspeaker output.
6. All pushbuttons out except AUX 1 and manual tuning.
7. Connect mains supply.
8. Switch on.
9. Connect a voltmeter -ve to chassis and +ve to TE3. The reading should be 52 volts.
10. Transfer meter to 25-volt line (pin TE5) and adjust VR17 for 25 volts on meter.
11. Transfer meter to pin TE9. This should read 14.5 volts.
12. Switch off. If all the above checks are correct proceed as follows; if not, recheck all wiring etc.
13. Connect a 30 ohm wirewound (5W) resistor across each fuseholder

14. Switch on and recheck voltage on TE3. This should still be the same as before. If correct measure the voltage on pins TD12a and TD12b. The voltage on these should be approximately 50 per cent of the voltages on pins TD10a and TD10b, which should be at almost the full supply voltage.


NOTE. If either or both of the voltages on TD10a, b are very low it may be that VR16a or VR16b are set for a high quiescent current which would cause a voltage drop across the 30 ohm wirewound resistor fitted to the fuseholders. To check, carefully adjust each VR16 (one on each channel); the voltage on pins TD10 should rise and fall. Set VR16 for highest voltage reading. Recheck that TD12a, b voltages are still approx 50 per cent of respective TD10 voltage.

The voltage on TD10a, b should be about 2 volts less than the full supply voltage. A larger drop in voltage may indicate a fault in the power amplifier, in which case the voltage to pin TD12 would also normally be wrong. This fault (if one exists) must be found and cleared before removing the 30 ohm wirewound resistor, otherwise the transistors could be damaged.

The purpose of the 30 ohm resistors is to limit the current to a safe value in the event of a fault condition.

Assuming the above check is correct proceed with the remaining tests.

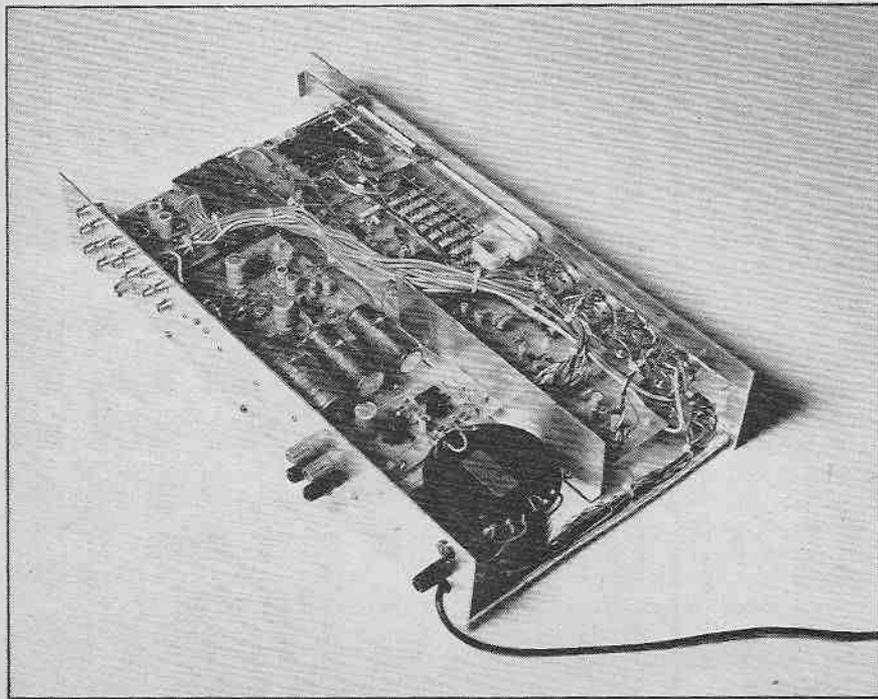15. Switch off.
16. Remove 30 ohm wirewound resistors and connect a milliammeter in place of the fuses -ve to TD10 and +ve to TE3 (set to highest range to start). Check each channel in turn and switch off when changing over meter from one channel to the other.
17. Switch on, adjust VR16 on metered channel for a reading of between 40mA and 50mA.
18. Switch off. Remove meter and fit 1 amp "quick blow" fuses.



19. Switch on. Measure voltages at each point shown in Table 6-2 and adjust presets where instructed.

TABLE 6-1

Terminal Pin	Voltage	Adjust
TE5	25	VR17
TE9	14.5	
TB2	25	
TC3	14.5	
TA7	14.5	
TA17	3.2	VR10
TD13 a, b (Loud-speaker Outputs)	ZERO*	

* VERY IMPORTANT NO VOLTAGE PRESENT

20. Switch off.

This completes the Initial Tests and it should now be safe to proceed with the Final Testing and Setting Up.

FINAL TESTING AND SETTING-UP

Radio

- Remove 8 ohm dummy loads and connect loudspeakers.
- Switch to FM and switch on. A "thump" may be heard from the speakers, but this should not be very loud. It is caused by capacitors in the loudspeaker circuit charging up.
- Tune to 100MHz approximately on manual tuning. Advance volume control; a "hissing" should be heard from the loudspeakers.
- Adjust L2 tuning slug carefully until meter reads centre-scale. Switch a.f.c. on (by pressing AFC button) and adjust VR1 until meter just reads to left-hand side of scale. Release AFC button.
- Connect f.m. aerial and tune to approximately 89MHz. The BBC Radio 2 programme should be heard. Tune for centre-reading on meter. Adjust tuning cursor to the correct frequency for your Radio 2 programme.
- Check Radio Times for actual frequency. At the same time check if a stereo transmission. If it is, adjust VR2 until stereo beacon lights up. Set final position of VR2 to mid-point of the two positions where the lamp comes on and goes out.
- Check frequencies of other stations and also select preset stations and adjust preset tuning potentiometers as described in Part 1. (p. 875) (Anticlockwise for l.f.)
- Switch back to manual tune and press MUTE button. Receiver should mute either with no signal and when de-tuning.
- Release MUTE button. Tune to a spot around 100MHz where there

is no signal. Listen to hiss while pressing H.F. or L.F. filters. A change in the general sound should be heard. The H.F. filter should cut the higher frequencies and the L.F. filter the lower. It may be difficult to detect the change on the L.F. filter, depending on how good the loudspeakers are.

Audio inputs

Connect a pick-up to the DISC input and a tape recorder to AUX 1, then AUX 2, and finally TAPE. Select the correct input and check that each input is working correctly. Test BASS and TREBLE controls.

That completes the Final Testing and Setting Up procedure.

MORE DETAILED PROCEDURE

Anyone who has access to test equipment would (normally) also know how to use it for checking a full specification, therefore only the f.m. i.f. alignment procedure will be given here. Once this has been carried out a full check of the performance can then be made against the Specification given in Part 1.

Radio I.F. Alignment

Having completed all the Initial Tests and the Final Testing and Setting Up satisfactorily, the next stage is to correctly align the f.m. i.f. section. This requires a f.m. signal generator with stereo modulation, an output meter, and a frequency counter.

- Disable a.f.c. by shorting out switch S2c (front tags next to front panel—see Fig. 5-5 and *Erratum* below). Press AFC switch in. Inject f.m. generator to pins TAI and earth at approximately 10.7MHz. Increase input until meter reads, then tune generator until meter shows maximum tuning point. The generator frequency is now set to the centre of the ceramic filter pass band.
- Release AFC button and remove short from S2c. Do not alter generator. Adjust L2 for a centre reading. Discriminator is now correctly tuned to the ceramic filters.
- Remove generator. Transfer to AERIAL input and inject a frequency of 88MHz. Tune receiver to the signal, adjust cursor to 88MHz on dial.
- Check other frequencies. Very slight adjustment of VR10 may be needed, but this is normally set for 3.2 volts on TA17.
- Connect frequency counter to pin TA8 and earth. Remove generator. Adjust VR2 for a frequency of 19kHz \pm 2Hz.

**TABLE 6.2
CIRCUIT VOLTAGES**

No signal applied. Volume control at minimum. AVO 8 meter used.

BOARD A

Terminal Pin	Voltage
TA1	0
TA2	0
TA3	14.5
TA4	0.3
TA5	7
TA6	5.6
TA7	14.6
TA8	1.7
TA9	0
TA10	0
TA11	0
TA12	3 or 12†
TA13	13.2
TA14	3.2-12*
TA15	12
TA16	10.5
TA17	3.2
TA18	5.7

† Depending on preset hi-lo l.e.d.s.
* Depending on tuning. 88-102MHz.

BOARD B

Terminal Pin	Voltage
TB1	21.4
TB2	25
TB3a,b	0
TB4	0
TB5a,b	0
TB6a,b	0
TB7a,b	0
TB8a,b	0
TB9a,b	0
TB10a,b	0

BOARD C

Terminal Pin	Voltage
TC1a,b	0
TC2	0
TC3	14.5
TC4a,b	0

BOARD D

Terminal Pin	Voltage
TD1a,b	0
TD2	0
TD3	0
TD4a,b	0.5
TD5a,b	25.5
TD6a,b	0
TD7a,b	54.5
TD8a,b	25.5
TD9a,b	55.2
TD10a,b	55.2
TD11	0
TD12a,b	25.5

BOARD E

Terminal Pin	Voltage
TE1	55.4
TE2	0
TE3	55.4
TE4	0
TE5	25
TE6	} Secondary of T1
TE7	
TE8	0
TE9	14.5

6. Disconnect frequency counter and reconnect signal generator. Switch to stereo and check separation using the output meter connected to the loudspeaker terminals together with 8 ohm dummy loads. Separation at 1kHz should be a minimum of 30dB. Slight readjustment of VR2 may be needed for optimum separation.

7. With oscilloscope connected to output, adjust VR15 for symmetrical clipping on full sine wave drive.

NOTE: If oscilloscope not available, set VR15 to mid-way position.

Frequency Response

When testing for frequency response, some tone controls may not indicate a "flat" response when in their mid setting. If necessary small fixed resistors can be shunted across one half of each control to correct this. The actual value and section of control will have to be found by trial. Resistor values between 82k ohms and 180k ohms should prove satisfactory.

OPERATION OF THE 2020 TUNER AMPLIFIER

Most controls are self explanatory, but for completeness a few comments are in order.

Phones socket (SK9). This is wired directly to the power amplifier output and it may be necessary to use an attenuator to protect the headphones (and your ears) from excessive power at high volume levels.

An attenuator could not be fitted internally as a switched jack socket of suitable type was not readily available. In most cases a resistor of 100 to 270 ohms in series with each channel will prove satisfactory.

Tuning Meter (ME1). With AFC off, the meter shows the correct tuning point when set to the centre of its scale. With AFC on, it indicates the strength of the incoming signals over a range approximately 1 microvolt to 100 millivolts.

Pre-set tuning adjustment. This is fully described in Part 1 under

Varicap Tuning and L.E.D. Tuning Indicator.

Mute. When detuning, the output is muted before the station goes out of tune and distorts. It stays muted until another station is correctly tuned in.

Mono. Not often used, but can be useful on weak stereo transmissions to give a mono reception with less background hiss. Sometimes also used for older records.

All other control functions are described in Part 1.

Preamp Out/Power Amplifier In. These sockets (SK7, SK8) are internally linked and are provided so that at a later date a quadrasonic decoder or other unit may be added simply by removing the internal link and plugging a suitable unit into these sockets.

Earth Terminal. Any ancillary equipment, such as a tape recorder or record player must be earthed to this terminal and NOT to the mains earth if hum loops are to be avoided. Note: on some record players the pick-up



**TABLE 6.3
TRANSISTOR VOLTAGES**

Transistor	Emitter	Base	Collector
BOARD A			
TR1	5.1	4.5	1.5
TR2	0.9	1.5	12
TR3a,b	6.3	6.8	14
TR4a,b	14.5	14	12
BOARD B			
TR5a,b	4.3	5.4	20.7
TR6a,b	21.5	20	11
TR7a,b	9.6	10.2	20.7
TR8a,b	21.5	20.7	9.6
TR9a,b	0	0.6	12.7
TR10a,b	12	12.7	21.4
BOARD C			
TR11a,b	4.5	5.0	12.1
TR12a,b	4.5	5.0	6.5
TR13a,b	12.7	12.1	5.8
BOARD D			
TR14a,b	11.8	12.3	38.4
TR15a,b	11.8	12.5	18.9
TR16a,b	50.6	49.9	26.3
TR17a,b	25	25.7	26.3
TR18a,b	50.6	51.3	55.5
TR19a,b	25.8	25.0	0.6
TR20a,b	0	0.6	25.8
TR21a,b	25.6	26.3	54.8
TR22a,b	55.5	54.8	25.6
BOARD E			
TR23	12.8	13.3	25.7
TR24	25	25.7	35
TR25	14.9	15.4	25

**TABLE 6.4
INTEGRATED CIRCUIT VOLTAGES**

IC1, 2 and 3 are on Board A, see Fig. 2.2.
IC4 is on Board E, see Fig. 2.6.

Pin	IC1	IC2	IC3	IC4
1	2	14.7	*	0
2	1.9	3	*	14.9
3	1.9	5.2	—	14.7
4	0	10.8	0	7.3
5	0	10.8	*	7.3
6	5.6	13.2	*	7.3
7	5.5	0	*	0
8	5.6	2.3	—	0
9	5.6	2.3	—	8.9
10	5.6	1.7	*	15.4
11	10.7	2.3	—	25
12	2.8	2.3	3 or 12	25
13	0.4	2.3	14.5	0
14	0	3.3	—	0
15	7.9	—	—	—
16	0.4	—	—	—

* 3-12 volts (depends on tuning).

PRESET AND VARIABLE POTENTIOMETERS

Ref.	Function	Board Location
VR1	—	A } Fig.2.2
VR2	—	A } Fig.2.2
VR3	Manual Tune	— Fig.5.3
VR4	Station 1	A } Fig.2.2
VR5	Station 2	A } Fig.2.2
VR6	Station 3	A } Fig.2.2
VR7	Station 4	A } Fig.2.2
VR8	Station 5	A } Fig.2.2
VR9	—	A } Fig.2.2
VR10	—	A } Fig.2.2
VR11a,b	Bass	} Front Panel
VR12a,b	Treble	
VR13	Balance	
VR14a,b	Volume	
VR15a,b	—	D } Fig.3.2
VR16a,b	—	D } Fig.3.2
VR17	—	E Fig.2.6

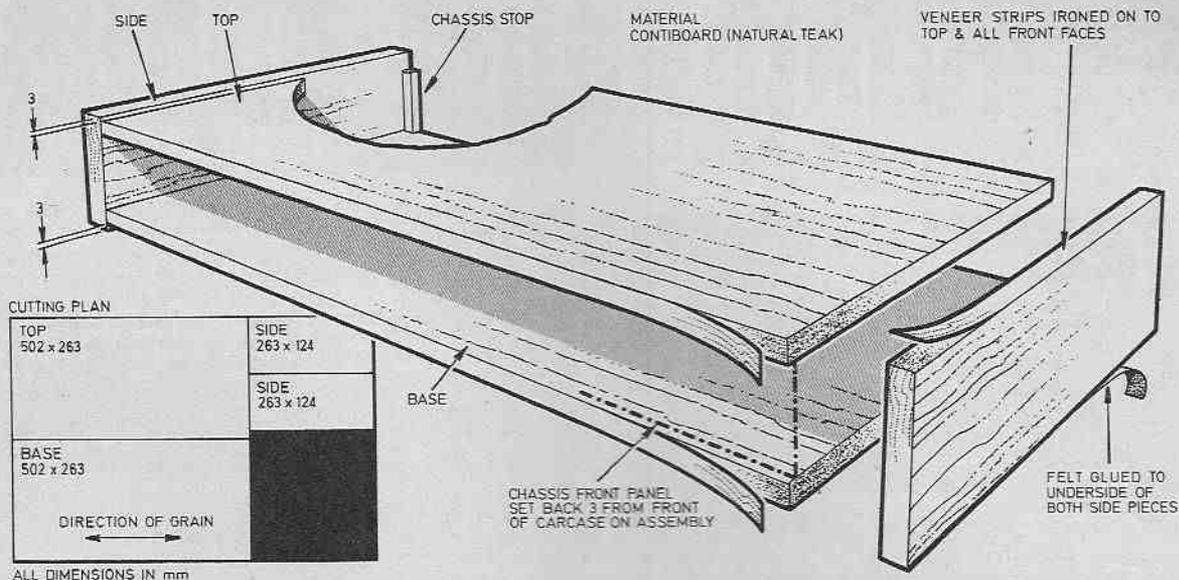


Fig. 6-1. A wooden case for housing the 2020 Tuner Amplifier.

earth return is also connected to the turntable metal chassis. These must be isolated and the turntable chassis connected directly to the tuner amplifier earth terminal; that is, the pick-up is earthed via the audio leads, but not the turntable chassis.

The tuner amplifier is earthed via its mains lead.

FAULT FINDING

All significant voltages are given in Tables 6-2, 6-3 and 6-4 and should prove helpful. Remember to check both channels were applicable.

When investigating suspected power amplifier faults, always fit the 30 ohm 5W resistors in place of the fuses (to limit the current) until the fault has been cleared. As the power amplifier is d.c. coupled a voltage check will not help as all voltages will be wrong. The best method is to switch the tuner amplifier off and check each transistor in turn.

If only one channel is faulty, compare the resistance reading from each part of the circuit when measured either to earth or H.T. line. (Remove fuses and 30 ohm resistors for this test.)

Most power amplifier faults (assuming the unit had been working) in the Author's experience have been due to faulty or blown transistors.

Erratum

In Fig. 5-5 the switch S2 is incorrectly marked. The "c" and the "d" should be transposed. (S2d is not used.)

WOODEN CASE

Details of a suitable case are given in Fig. 6-1. It is suggested that a wooden sleeve type of case as indicated be constructed, so that when the chassis is inserted into the sleeve from

the front, the chassis front panel overlaps the front edges of the sleeve. The 2020 front panel has been made larger than the chassis so that it overlaps enough on all edges for mounting in a case of this type.

All parts were cut to the sizes stated, care being taken to ensure that the grain runs in the direction indicated on the cutting plan.

These parts were then assembled with the aid of panel pins and Resin W adhesive.


VENEER

Conti-strip veneer was ironed on to all top and front raw edges which were exposed during the cutting stage.

The carcass was given two coats of Contipol, and rubbed down with glass-paper between coats.

Stereo Decoder IC2

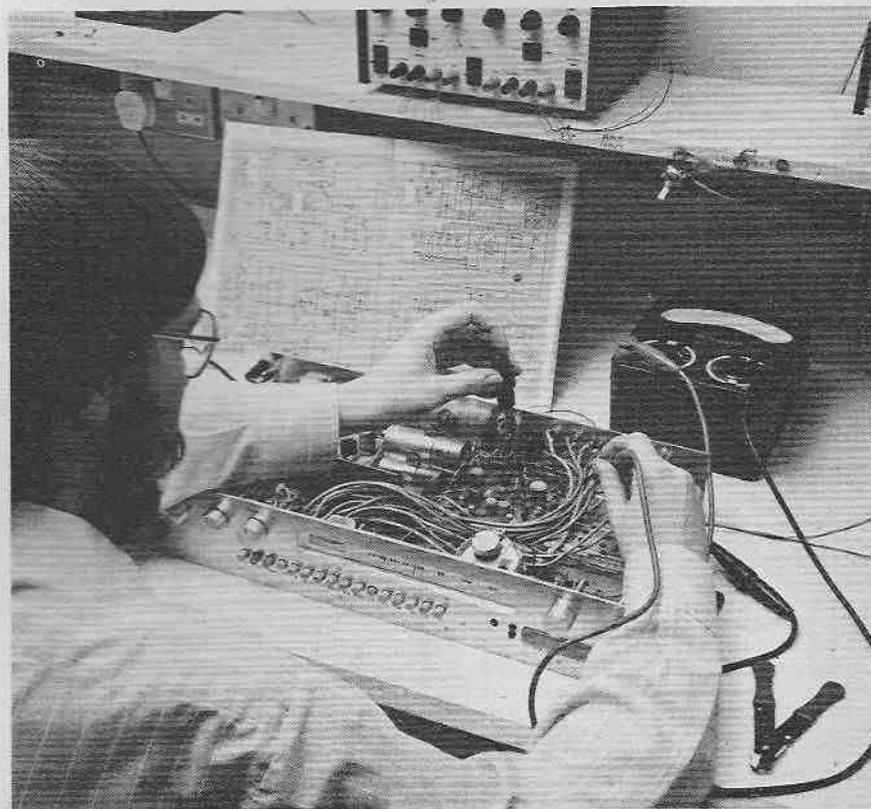Please note that MC1310 (Motorola) is a pin-for-pin replacement for the type specified, and may be more readily available.





RUMMAGING AROUND

with Keith Cadbury

DEAR READER as you might well have guessed this column will be concerned with short-cuts and cheap ways of producing some projects, obtaining bargains in components and apparatus, and improvising in all constructional aspects of our hobby. The important consideration with all my ramblings will be that of *cost*. I cannot really be the only electronics aficionado who is unable to spend significant amounts on parts for projects, so I shall pass on as many tips for buying cheaply as I can.

HOW I GOT HOOKED

Before going further, it might be a good idea to tell how I got into electronics.

Less than two years ago I picked up a Philips cassette recorder in a junk shop for a fiver. Working away from home and with time on my hands, I determined to "dramatize" tapes for friends and relatives, by way of a change from my indecipherable letters.

Having long been an admirer of Kenny Everett's radio technique, I sat down after work one day to "do" a cassette for a friend in Canada, complete with background music, effects and lots of funny voices.

With no mixing facilities, no direct connection between record player and recorder, and next-door's howling dog complaining at being locked-out, the result of that first tape was poor, to say the least. I was going to need a mixer, sound-proofing, script, and rehearsals.

Sound-proofing proved unnecessary, when the mic was pointed away from the closed and curtained window; scripting meant learning to read my awful writing; taping "rehearsals" often resulted in successful "takes" first time.

It was because I needed a mixer that I took up electronics.

A visit to the local library revealed a number of books about elementary electronics that proved to be adequate introduction to transistors, capacitors, resistors and suchlike. A week later I went to the local shop to purchase components. I stayed up all

night building the simplest of two-channel mixers from a 741 i.c., a couple of rotary pots and half-a-dozen other bits and pieces, and fitted the whole thing in a plastic box about 80mm by 70mm by 35mm that had housed an Ingersol wristwatch.

It worked!

I was hooked.

That first C60 tape for my old school-friend in Canada was enthusiastically received—he rang me at 5 a.m. my time to tell me he had just played it. So in the first week of taking up electronics as a hobby, I had lost-out on sleep three nights already (the other time was when I had stayed up very late, recording the cassette).

FAILURES

A lot of the ideas I tried didn't work—I have a two-litre ice-cream carton-full of failures, but I can't say that I learned from all of them. Some *should* have worked, and I still can't fathom out why they *don't* work. One of these days I'll go over them again and see if extra knowledge, gained since they were thrown in the box, enables me to work out what is wrong with them.

Still a "beginner," still an electronics hobbyist, still not understanding all of the basic rules, I continue to read everything I can get my hands on that has anything to do with your, and my, exciting pastime.

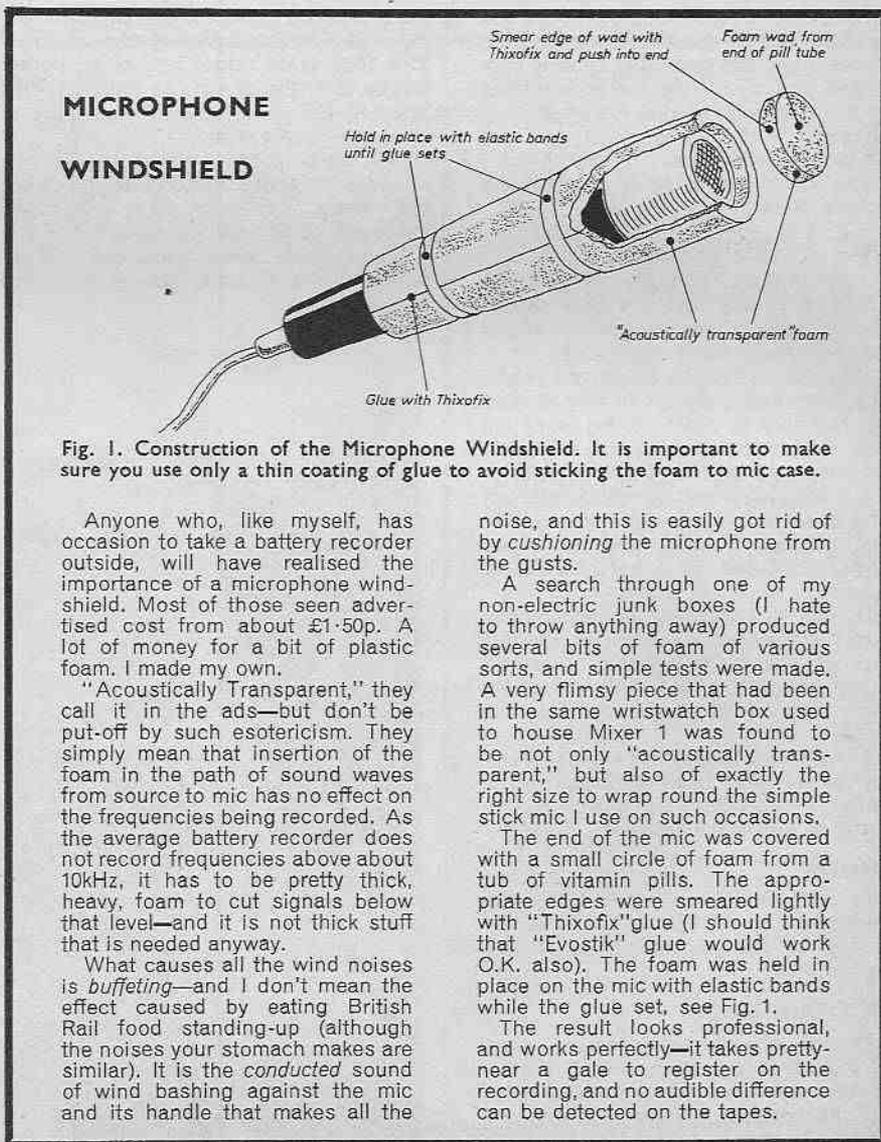


Fig. 1. Construction of the Microphone Windshield. It is important to make sure you use only a thin coating of glue to avoid sticking the foam to mic case.

Anyone who, like myself, has occasion to take a battery recorder outside, will have realised the importance of a microphone windshield. Most of those seen advertised cost from about £1.50p. A lot of money for a bit of plastic foam. I made my own.

"Acoustically Transparent," they call it in the ads—but don't be put-off by such esotericism. They simply mean that insertion of the foam in the path of sound waves from source to mic has no effect on the frequencies being recorded. As the average battery recorder does not record frequencies above about 10kHz, it has to be pretty thick, heavy, foam to cut signals below that level—and it is not thick stuff that is needed anyway.

What causes all the wind noises is *buffeting*—and I don't mean the effect caused by eating British Rail food standing-up (although the noises your stomach makes are similar). It is the *conducted* sound of wind bashing against the mic and its handle that makes all the

noise, and this is easily got rid of by *cushioning* the microphone from the gusts.

A search through one of my non-electric junk boxes (I hate to throw anything away) produced several bits of foam of various sorts, and simple tests were made. A very flimsy piece that had been in the same wristwatch box used to house Mixer 1 was found to be not only "acoustically transparent," but also of exactly the right size to wrap round the simple stick mic I use on such occasions.

The end of the mic was covered with a small circle of foam from a tub of vitamin pills. The appropriate edges were smeared lightly with "Thixofix" glue (I should think that "Evostik" glue would work O.K. also). The foam was held in place on the mic with elastic bands while the glue set, see Fig. 1.

The result looks professional, and works perfectly—it takes pretty-near a gale to register on the recording, and no audible difference can be detected on the tapes.


THE NEW

EUROSOLDERSUCKER

This 195mm long, all metal, high suction desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

THE UNIQUE

EUROBREADBOARD

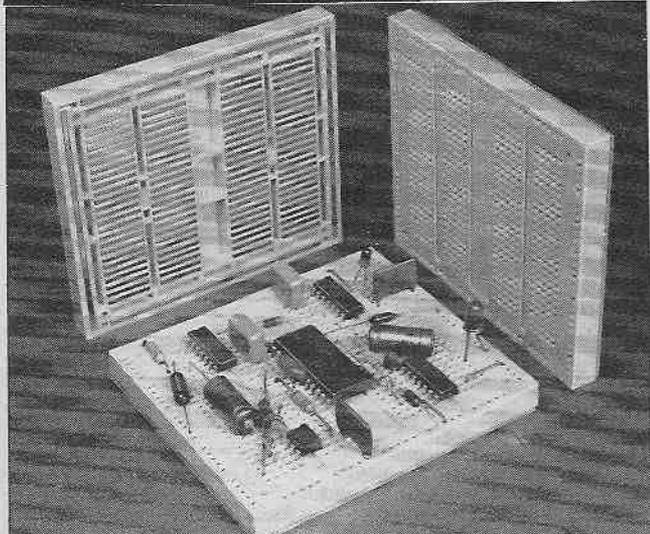

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

EE 5179

Please send me 1 EuroSolderSucker @ £6.80 Please
 or 1 EuroBreadBoard @ £5.80 Tick
 or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name. _____

Company. _____

Address. _____


Tel. No. _____

Please make cheque/P.O.'s payable to David George Sales

MICRO CHIMES

FROM THE INVENTORS
OF MICROPROCESSOR
MUSICAL CHIMES

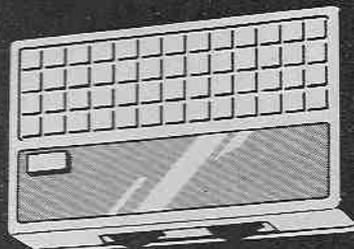**A COMPLETE
KIT FOR THE
EE
MICRO
CHIME**



This easy to build kit includes:

- * TMS1000 Custom MPU Chip
- * Special purpose designed case
- * Fully drilled and legended PCB
- * All transistors, Resistors and Capacitors
- * Full set of mechanical parts
- * Smart fascia labels
- * IC Socket and Loudspeaker
- * Really Low Price!

only **£8.95 + 55p p&p**

TMS 1000N - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.

New low price only **£4.95** inc. p&p

(Only present 24 tune repertoire currently available.)

New price for the original
CHROMA-CHIME 24 tune model!

Due to the fantastic success of this product right across the World we are able to offer it at

only **£9.95 + 75p p&p**

Comes complete with:

- * TMS1000 Micro
- * Superb cabinet
- * All R's & C's
- * Switches & pots
- * Fully prepared PCB
- * All semiconductors
- * Loudspeaker
- * Socket & Hardware
- * Fully detailed kit manual

ALL CHROMATRONICS PRODUCTS
SUPPLIED WITH MONEY BACK REFUND

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX. UK.

NAME _____

ADDRESS _____

EE3

I enclose cheque/PO value £ _____

or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

RADIO WORLD

By Pat Hawker, G3VA

Losing the lead?

BRITISH television has a long-established tradition as a pioneer of new technology, stretching right back to the development of the original 405-line system by the EMI team in the mid-1930s and more recently to the setting up of a nationwide, "four-channel" u.h.f. transmitter network (seldom recognised as the technically audacious scheme that it was when planned over a decade ago).

Yet undoubtedly in some respects we are at the moment falling behind North America. One such area is the successful implementation there of satellite distribution systems, such as the Canadian *Anik* satellites that carry television to remote Arctic communities or those used by "Subscription TV" cable operators in the USA and the Public Broadcasting System (PBS).

Unlike so many technical innovations distribution satellites have really brought costs tumbling down and made coast-to-coast distribution relatively cheap. The smaller geographical area of the UK makes such systems less essential here, but there also seems to be less "get up and go" about the whole European approach to satellites.

Another, even more pertinent area in which the UK is treading water is the thorny subject of "electronic news gathering" (ENG). Almost everybody in television recognises that it must come here, as it has in America, yet for months the expensive experimental BBC unit (insured for some £90,000) has been figuratively in mothballs and the whole topic of "new technology" is almost as hairy in TV circles as it is in Fleet Street.

In 1976 I visited the CBS News Centre in Chicago just as it was being converted from film to electronic cameras and U-matic portable recorders. Since then one has waited for a similar revolution in the UK . . . waited and waited and waited.

Not so easy

There is a view of amateur radio h.f. operation that makes it look all too easy. If it really were just a matter of buying and installing a modern s.s.b./s.w. transceiver and then immediately being able to

work at will all over the world, the hobby would in fact be altogether less challenging and less interesting than it is in practice, with the opportunity for gradual improvement as experience is gained.

It is true that with a transceiver and modest aerial, a newly licensed amateur can contact other amateurs in all parts of the world; but usually only when band conditions are just right, at the right time of the day, on the right band, in the right season. The urban amateur has to contend with high levels of electrical interference, may still encounter tricky problems of television or "audio" interference and, if he operates on s.s.b., has to get used to listening to amateurs who may be speaking with heavy accents under "frequency-shifted" conditions due to receiver or transmitter frequency drift or inexpert tuning.

If he uses simpler and more effective "cw" (Morse telegraphy) he finds there is a good deal of difference between scraping through a 12-words-per-minute Morse test and actual two-way working with weak, fading signals often under heavy interference. His aerial may often be at limited height, located near to power-absorbing objects such as trees, fences and metal drainpipes and guttering—or even slung up in a roof space.

Making contact

It thus remains true, as it always has been, that many amateurs, even when working on the long-distance (DX) bands such as 14, 21 and 28 MHz make contact most frequently with stations located a "single hop" away (under say 2000 miles). The really long-distance contacts thus come as a bonus, especially when using simple wire aerials.

At the moment, as we head towards the sunspot peak (expected late 1979 or early 1980 but possibly not until later) it is much easier to work long distances from poor locations. A high "maximum usable frequency" (muf) and low D-layer attenuation make even poor aeri-als suddenly seem as good as a beam, and logs are filling up with American, Japanese, Australian and other call signs that are rare in sunspot minimum years.

Even so, it is still not possible just to switch on the rig at any time of the day or night and be sure of making contacts with stations many thousands of miles away. That is part of the attraction, and why the hobby is genuinely a form of "self training".

One of the high spots this year has been the reception in the UK of American amateurs working on the 50MHz band (not available to amateurs in the UK). Two-way contacts have been made with these stations by using the 28MHz band but there is the possibility of 50/70MHz cross-band contacts in the period October 1979 to March 1980.

If 70MHz signals can reach North America along an East/West path, there is an even greater possibility of their being heard in southern Africa or South America since the "muf" always tends to be higher for north/south than for east/west paths.

Working the stars


In the March 1979 issue, I reported the suggestion by Japanese scientists that we should listen on precisely 4829.659MHz for interstellar communications. Now a Russian, N. S. Kardashev of the Space Research Institute, Moscow, has come up with his favoured frequency for CETI (communication with extraterrestrial intelligence).

It is the very high frequency of 203.385GHz (wavelength about 1.5mm) which corresponds to splitting of the ground state of the lightest atom: positronium. Such a frequency corresponds roughly with minimum background radiation noise although not exactly a part of the radio spectrum covered by many existing sensitive receivers!



"Personally, I think it is a computer with a warped sense of humour!"

BUSH "PARTY AMP"

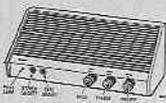

This very attractive unit is a complete mono amplifier originally designed as the second channel BUSH record players. All solid state, the case houses good quality speaker, power supply, pre-amp and controls. Standard DIN socket input accepts ceramic cartridge input. 240v operation. Brand new and boxed complete and screened DIN to DIN connection lead and instruction leaflet. Many uses include baby alarm, guitar practice amp, booster amp for transistor radios, etc. etc.


Two types available:
Type 1 2-3 watts output with volume and tone control £7.50
Type 2 2-5 watts output with separate bass, treble, volume controls and tape output £8.50 + 50p, PP £1

*NOTE For use as baby alarm and guitar practice amp it may be necessary to use our phono preamplifier module (BM).



6 DIGIT COUNTER

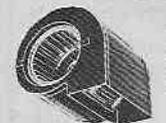one pulse at mains voltage moves 1 digit—not resettable—real bargain @ 87p.



MAINS BLOWER

The Torrin—quiet but powerful outlet size 2 1/2 x 1 1/2 for cooling equipment etc. will extract output is blowing outwards price £2.50. Other models from £2.00.

PP3/PP9 REPLACEMENT

Japanese made in plastic container with leads size 2in. x 1 1/2in. x 1 1/2in., this is ideal to power a calculator or radio. It has a full wave rectifier and smoothed output of 9V suitable for loading of up to 100mA. £2.53.



MICRO SWITCH BARGAINS

Rated at 5 amps 250V. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 (two types) for £1.25.



INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT 1/2 stack 1 1/2 spindle £2.25, 1 stack model £1.75. 1 stack £2.75, 1 1/2 stack £3.25.



MOTORIZED DISCO SWITCH


With 10 amp change-over switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating 8 switch model £5.25, 10 switch model £5.75, 12 switch model £6.75.



25A ELECTRIC PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to.

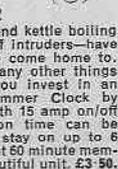All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch on time can be set anywhere to stay on up to 8 hours independent 60 minute memory jogger. A beautiful unit. £3.50.




SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.



CAR STARTER CHARGER

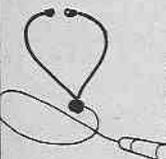Our own kit this has proved a godsend to many motorists contains 20 amp transformer and bridge rectifier switch HD resistor and full instruction £9.95.



RADIO STETHOSCOPE

Easiest way to fault find, traces, signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £9.95.


MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opv—mirrored scale. 11 instant ranges measure:—DC volts 10, 50, 250, 1000. AC volts 10, 50, 150, 1000. DC amps 0-1 mA and 0-100 mA. Continuity and resistance 0-150K Ohms. Complete with insulated probes, leads, battery, circuit diagram and instructions. Unbelievable value only £6.50+50p post and insurance.

FREE Amps ranges kit enables you to read DC current for 0-10 amps directly on the 0-10 scale. Its free if you purchase quickly but if you already own a mini tester and you would like one sent £1.50.

MULLARD UNILEX

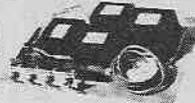A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in an easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.



ELECTRONIC VOLTMETER/SENSITIVE RELAY

Consists of a large, extremely readable, 4 1/2" square drop through panel volt meter, 0/0-1 fsd. Built into the front of the meter are two screw adjusters which move two separate pointers, one red and one green, up and down the scale, the purpose being to set a minimum and maximum level so that when the needle falls below or rises above the preset levels a unique 'under' and 'over' circuit inside the meter operates one of two reed relays to bring an 'under' or 'over' circuit into action. The scale plate is detachable via two screws to be calibrated to your own individual requirements. The 10 transistor 'under' and 'over' circuit is completely separate from the meter movement so does not have to be connected to use this as a standard 0-1 meter. Many uses including level controls, light controls, auto battery chargers, alarm units, etc. etc. Manufacturers list price of over £120 each. An unbelievable snip at £7.75 + 82p, p & p. 80p. (Less than value of the meter alone). Circuit diagram included.

G.P.O. HIGH GAIN AMP/SIGNAL TRACER

In case measures 5 1/2 x 3 1/2 x 1 1/2 extremely high gain (70 DB) solid state amplifier designed for use as a signal tracer on GPO cables etc. Functions very well as a signal tracer for fault finding in radios etc. etc. By connecting a simple coil to the input it becomes a useful mains cable tracer. Uses standard 4 1/2v battery and has input, output sockets and on-off volume control mounted flush on the top. Many other uses include general purpose amp, casing amp, etc. etc. An absolute bargain at only £2.25. Suitable 80 ohm earpiece 60p + 5p.

PLUG IN MODULES



MODULES Neat 'plug-in' size approximately 2" long x 2 1/2" wide x 1 1/2" high. Japanese made, 6v operation, solid state, eight different types to perform various functions as follows—

FIRE-ALARM MODULE (BM 71) Used with thermostatic switch or switches and 6v battery this will drive a speaker and give audible alarm. Note: Ceiling type, white, fire operated thermal switches available £2.50 + 10p ea.

ELECTRONIC ORGAN MODULE (BM 81) This is a tone oscillator especially designed for an electric organ. Requires an external 10k resistor miniature variable type to provide various notes.

RAIN ALARM MODULE (BM 61) Intended to detect rain or moisture and will operate a loud speaker with a high frequency sound which will vary in intensity to a degree which depends on the amount of moisture collected. A grid type pick up is recommended with a spacing about 1/16" between grids (the raindrops short the grids).

PHONO PREAMPLIFIER (BM 1) Will amplify the output of a magnetic cartridge, tape head, timer etc., up to about 1 volt, and give a reasonably flat response curve, should suit most amplifiers.

DUAL LAMP FLASHER (BM 100) An electronic switch designed to flash two miniature bulbs alternatively at 1 sec. intervals with any 6v, 1 to 3 amp bulb. Ideal for flasher of model car, model plant and boat, warning of railroad crossing of HO gauge; display attention getter, car emergency warning, etc.

MORSE CODE OSCILLATOR (BM 42) Miniature transmitter, it transmits a modulated signal (400-3000hz) which can be picked up with normal AM radio receiver. Also ideal for a signal source on test bench for tracing troubles in AM radios.

METRONOME MODULE (BM 32) Designed to vary the tempo from approximately 40 to 208 beats per minute a complete solid state electronic timer only a speaker, a potentiometer and a 6v DC supply are required to complete. Cost easily be tucked away into our £4 extension speaker to make a nice looking instrument.

BURGLAR ALARM MODULE (BM 70) This module enables connection to as many trigger mats, window switches, micros etc. as you require, and when the circuit is closed will emit a horn type sound from the speaker. No power is consumed in the nonalarm condition, therefore giving long battery life. PRICES any module £1.95, bases optional 56p.

TERMS: Prices include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1833.

BARCLAYCARD & ACCESS ACCEPTED

J. BULL (ELECTRICAL) LTD

(Dept. E. E.), 103 TAMWORTH RD.,

CRUYDON CR8 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

COMPUTER EQUIPMENT We are stocking a wide range of computer equipment including:

MEMOREX 8" floppy disc drives, as new, £180.56 + £14.44

TELETYPES ASR33 from £295. KSR33 from £175

SPERRY UNIVAC Display Keyboard with VDU Uniscope 300 from £60.00

5V 2.5-6 AMP P.S.U. With Circuit £6.74 + 54p, pp £1.75

CLO RACAL Supergrade cassettes with library cases 2 for £1.10 for £5.00

A range of TTL and other components is now stocked at the Shop.

OSCILLOSCOPES We now have a good range of scopes ex stock at the shop, prices range from £40—£275 for example:

Double Beam Scope—working order £45

Philips Single Beam—working order £35

CT430 Double Beam DC-6mhz, as soon £75

Marconi TF 2200 Double Beam DC-22mhz special order £225

Tektronix 545A Double DC-24mhz £175

Scopes sell very fast we strongly advise a visit to the shop where personal callers can snap up bargains! Mail customers please telephone—working order.

Constant Voltage Auto-Transformers made for operating American made computer equipment of standard 230-240v mains. Input voltage can be plus or minus 20%, output voltage would be a steady 115v. They are beautifully made regardless of cost. We have two models, one 500w price £49.50 + 750w price £75. Carriage depending on distance.

Telephone Headset and Mouthpiece As used by switch-board operators, made for the GPO so obviously best quality. Very lightweight so not uncomfortable to wear. £3.75.

Telephone Plug Short GPO 4 pole type, reference number 420, as currently used with plug-in telephones, ex equipment but unused. 92p.

Telephone Socket Panel mounted, 4 pole, will take the 420 plus. 75p + 6p.

Strong Metal Box just the right size to hold in your hand approx. 5" x 3" x 1 1/2", removable lid and top punched to take controls. This has dozens of uses, particularly suitable for making rugged portable test systems. £1.30.

1000 Watt Heat and Light Lamp Mullard, tubular, suitable high speed drying, or for quick heat especially where localised heating is required in workshops are warehouses where general heating is impossible costwise. Supplied complete with holder and mounting clips. £4.00.

Making a Convector Heater? We can offer a bank of four 1kw metal clad elements all mounted on a 3" square iron plate. By comparatively simple switching 8 heat outputs ranging from approximately 250 watt to 4000 watt can be achieved. The elements, which are in the form of loops with push on tag connectors, extend to a length of approx. 17" from the plate, so a relatively compact simple convector heater could be made using this; if a blower is also fitted the element size can be kept relatively small. Suitable blowers are available price £2 each. Price of the element £3.50 plus 28p, pp £1.25.

Waterproof Heating Element Many uses include, winding round water pipes to prevent freezing, under seed boxes to assist germination in gloves or boot leathers, etc. etc. 13 yard length gives approximately 30 watts at 230 volts, has self regulating temperature control. Price 85p + 7p.

0-40 amp AC Panel Meter This is a surface mounted meter 2 1/2" dia, calibrated at 50hz being moving iron it should also be suitable for DC. Reasonably linear scale gives very clear readings at 1 amp intervals up to 40 amps. No external shunts necessary. £2.20.

Dual Range Panel Meter Scale calibrated 0-10v and 0-500v. 2 1/2" flush mounting this has internal resistor for the 10v range but would require external resistor for the 500v range. A very sensitive 20k per volt movement. First class British Manufacturer. £3.24.

SUPER VALUE HARDWARE PACK Ever been stuck for the right nut, bolt, giant hardware pack, contents include nuts, bolts, screws, washers, spacers etc. Mixed in BA, whitworth and metric threads, contents are in brass, bronze, steel, etc. 2lb per bag, average contents 400-600 pieces. £2.50.

900 WATT TRANSFORMER 110v 8 amps centre tapped. The winding however is extra heavy gauge so this will carry up to 16 amps at 115 volts. Made by Foster this is impregnated and varnished with very substantial clamps and punched for base mounting, also has a terminal platform with screw down terminals—weight approximately 30lbs. Has many applications including welding. £17.28 carriage £3 (mainland only). Order transformer ref. TM53.

TELEPHONE CABLE Made for the GPO to very rigid specification, circular PVC overall, 15 core colour coded 40p per metre. 10 colour coded cores 30p per metre. 6 colour coded cores 25p per metre. 4 colour coded cores 22p per metre. 2 core, but made of extra strong wire for straining across open yards etc. 30p per metre. Please add 25% to the price to cover cost of postage and packing and VAT.

TELESCOPIC AERIAL 5 sections 21" when extended. Nickel plated superior make, one nut fixing, fold over for FM. 97p.

HALF PRICE OFFERS. 1. Cassette player recorder not second hand but because of a small technical defect or case blemish or something similar we are not asking the recommended retail price of £19.50. Our price is £12.15. Don't miss this bargain.

2. 6 Transistor Radios again new but slightly faulty, 10 for £11.25. 12" GONG ALARM BELL Mains operated for fixing outside. Metal case and gong are made from heavy cast iron, this is a real quality product suitable for factory, warehouse, home, club of flats etc. £25.00 + carriage £3. Mainland only.

3. **CONTINENTAL RELAYS** Plug in standard bases or can have wires soldered directly to tags—Ref. Rel C1 700 ohm (18-24v) coil C/O 54p. Ref C2 180 ohm (6-12v) coil C/O £1.08.

4. **BLEEPER** Makes a sound very similar to the Black & Decker smoke alarm. 6-12ac or 12-24v ac. Ideal for fire and smoke alarm, anti-mugging device, car or boat alarm. American made, compact about the size of an egg. £1.35. Order Delta Bleeper. A large quantity in stock so we will be glad to quote special price for quantity user.


5. **8 TRACK CASSETTE PLAYER** 12 volt Japanese make stereo amplifier for in car sound entertainment. Perfect order £7.98. Speakers in sloping cases only £2.40 per pair if ordered with player.

6. **VARIABLE INDUCTANCE CHOKE** A choke will oppose the flow of AC depending on how much its core is saturated, therefore, if the choke is built with a separate coil for deliberately saturating the core, a small variable dc current will act as a voltage regulator for lamp dimming and a multitude of other purposes. We offer such a choke of 8 amps AC rating requiring 75mA DC control current at bargain price of £24.34. Carriage £5.00 + 40p. This choke weighs approx. 60lbs.

7. **PANEL METER** 0-1mA Japanese made full vision perspex front, flush mounting. Price £3.24.

8. **PHOTO MULTIPLIER TUBE** American RCA, their type no. 4555. Have a gain of a million or more, regular price over £20 but we offer these brand new at £4.80 + 36p.

it's WAR!!

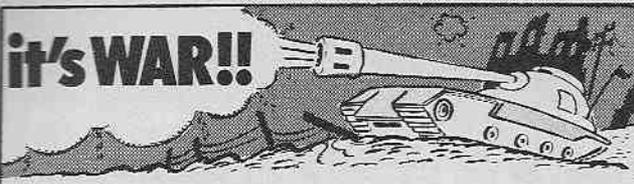

ANOTHER WAR!!!

Yes once again we have stock coming out of our ears! Arrow have purchased the entire stock of a prominent mail order company & must clear space in our warehouse.

Cut out & mail whole coupon:

Insert no. of packs required in box

1. Quarter Kilo weight mixed resistors, may incl. 1/4 to 2 watt/Wirewounds great variety **£1.00**
2. 100 Assorted Capacitors, may incl. Discs, Electrolytic/MyIars/Polys. etc. **£1.00**
3. Thyristor pack—3 mixed S.C.R.'s may incl. 1/2 to 10 Amp @ 50 to 400 volt **£1.00**
4. Zener pack. 15 assorted Zener diodes/regulators may inc. 250mw to 5 watt many voltages **£1.00**
5. Trimmer Capacitors, Unique pack may incl. Variables, presets, UHF/VHF/TV types 15 pcs **£1.00**
6. 20 Transistors, may incl. Germanium, silicon, NPN & PNP, Power etc. **£1.00**
7. 20 Diodes, may incl. Signal, planar, gold bonded, rectifiers etc. **£1.00**
8. Linear Integrated Circuits 9 pcs, may incl. 741s, 709s, 301s, DIL & T099. Great value **£1.00**
9. COSMOS pack, 4011 plastic/ceramic DILs 8 pieces for just **£1.00**
10. 10 PCS Presets/Pots/Rectilinears all sorts **£1.00**

FREE ORDER ALL 10 PACKS, GET A JUMBO SURPRISE PACK ABSOLUTELY FREE

OFFER IS LIMITED TO U.K. MAINLAND CUSTOMERS ONLY. PRICE INCLUDES V.A.T. no more to pay except—POSTAGE 30p BUT **FREE** if you order over 5 packs.

(Your name & address)

To:

.....

.....

.....

.....

Please print clearly: Please give your postcode.

ARROW ELECTRONICS LIMITED
LEADER HOUSE
COPTFOLD ROAD
BRENTWOOD
ESSEX CM14 4BN



If you wish you may collect at our shop.

OUR 1979 PRICE LIST SUPPLEMENT IS NOW AVAILABLE SEND LARGE STAMPED SELF ADDRESSED ENVELOPE.

or if you are ordering packs tick box


LINEAR		LM380	90p	SN76227N	150p	TBA810	100p
AY38500	450p	LM391	180p	SN76228N	180p	TBA820	100p
CA3009	70p	LM555	25p	SN76660N	75p	TBA920Q	280p
CA3046	60p	LM709C	40p	TAA300	100p	TCA270Q	220p
CA3060	225p	LM710T05	60p	TAA350	190p	TCA270S	220p
CA3065	200p	LM710DIL	65p	TAA550	35p	TCA760	300p
CA3076	230p	LM722T05	40p	TAA570	220p	TCA4500A	450p
CA3080	75p	LM720DIL	40p	TAA651B	140p	TD1009	350p
CA3084	250p	LM733	120p	TAA700	350p	TD1034	450p
CA3085	85p	LM741	20p	TAA790	350p	TDA2002	300p
CA3086	60p	LM748	40p	TAD100	150p	TDA2020	300p
CA3088	190p	LM1303N	100p	TAD110	130p	TL084	120p
CA3089	160p	LM1458	100p	TBA120S	80p	XR320	250p
CA3090AQ	360p	LM3080	75p	TBA122T	85p	XR2206	450p
CA3123E	130p	LM3800	55p	TBA480Q	200p	XR2207	450p
CA3130	100p	LM3909N	65p	TBA520Q	200p	XR2208	600p
CA3140	80p	MC1310P	140p	TBA530Q	200p	XR2216	650p
LF355	80p	MC1312P	150p	TBA540	200p	XR2567	250p
LF357	80p	MC1314P	190p	TBA550Q	250p	XR4136	150p
LM211H	250p	MC1315P	230p	TBA560C	250p	XR4202	150p
LM300TRS	170p	MK5038S	650p	TBA641A12	250p	XR4212	150p
LM301AN	30p	MM5314	380p	TBA700	180p	XR4739	150p
LM304	200p	MM5316	480p	TBA720Q	225p	ZN414	100p
LM307N	65p	NE529K	150p	TBA750Q	200p	95H90	700p
LM308T05	100p	NE555	25p				
LM308DIL	100p	NE556	30p				
LM309K	100p	NE562B	400p				
LH310T05	150p	SAD1024	1500p				
LM311T05	150p	SL917B	650p				
LM317K	325p	SN76003N	150p				
LM324	70p	SN76013N	110p				
LM339	60p	SN76013ND	125p				
LM348N	90p	SN76023N	110p				
LM380	60p	SN76023ND	125p				
LM381N	90p	SN76033N	150p				

In 4148 diodes by I.T.T./Texas 100 for £1.50
 Static Ram 2102 1024 x 1 bit 450 nanosec £1.00 each
 £112 256 x 4 bit 450 nano sec £2.50
 Murata ultrasonic transducers 40kHz £2.00 each or £3.50 pair
ALL PRICES INCLUDE POST AND VAT

7400	10p	7433	28p	7484	70p	74131	90p	74157	45p	74182	50p
7401	10p	7437	20p	7485	60p	74132	45p	74160	55p	74184	120p
7402	10p	7438	20p	7486	25p	74135	90p	74161	55p	74185	100p
7403	10p	7440	12p	7489	130p	74136	80p	74182	55p	74188	320p
7404	12p	7441	45p	7490	25p	74137	90p	74183	55p	74190	70p
7405	12p	7442	40p	7491	40p	74138	100p	74184	60p	74191	70p
7406	25p	7443	60p	7492	35p	74141	50p	74185	60p	74192	80p
7407	25p	7444	60p	7493	30p	74142	180p	74186	75p	74193	60p
7408	12p	7445	65p	7494	70p	74143	270p	74167	160p	74194	55p
7409	12p	7446	50p	7495	45p	74144	270p	74170	100p	74195	50p
7410	12p	7447	50p	7496	45p	74145	55p	74173	80p	74196	50p
7411	15p	7448	50p	7497	120p	74147	100p	74174	80p	74197	50p
7412	15p	7450	12p	74100	80p	74148	90p	74175	60p	74198	100p
7413	25p	7451	12p	74104	40p	74150	85p	74176	50p	74199	100p
7414	45p	7453	12p	74105	40p	74151	45p	74177	50p	74293	90p
7416	25p	7454	12p	74107	25p	74153	45p	74178	75p	741500	180p
7417	25p	7460	12p	74108	100p	74154	70p	74179	120p	745112	80p
7420	12p	7470	25p	74109	25p	74155	45p	74180	90p		
7421	20p	7472	20p	74118	75p	74156	45p	74181	130p		
7422	15p	7473	25p	74120	80p						
7423	20p	7474	25p	74121	25p						
7425	20p	7475	25p	74122	35p						
7426	22p	7476	25p	74123	40p						
7427	22p	7480	40p	74125	35p						
7428	25p	7481	85p	74126	35p						
7430	12p	7482	75p	74128	60p						
7432	20p	7483	75p	74130	120p						

T. POWELL

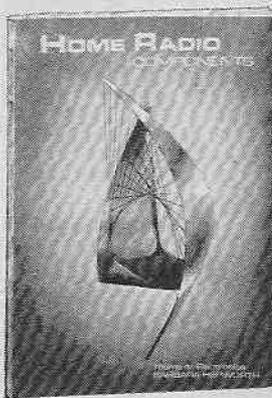306 St Paul's Road London N1
 Telephone 01-226 1489
 Barclay/Access credit cards accepted



EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

HOME RADIO COMPONENTS LTD.
 Dept. EE, 234 London Road
 Mitcham, Surrey CR4 3HD

FREE—Recharge Batteries—FREE

Use **PHOTO VOLTAIC ENERGY**

- Build your own power source from easy to assemble kits
- Use indoors and outdoors
- 3v and 6v kits available NOW
- Self regulating
- No mains electricity needed

Please send me the following Photo Voltaic Battery Charger Kit(s)


No. of KITS	COST
3 Volt Model	£
£7.95 per kit plus 95p p + p	:
6 Volt Model	£
£11.95 per kit plus 95p p + p	:
I enclose Cheque/P.O. for	£

Mrs/Miss/Mr _____
 Address _____
SOLAR-TEK, Post Code _____
 P.O. Box No. 123, Beckenham, Kent, BR3 3SC
 74 Manor Way, Beckenham, Kent

VARIABLE CAPACITOR 3 GANG 25+25+25pf @ 75p each.
50 PLASTIC BC 107-5-9 TRANSISTORS Assorted untested @ 57p.
50 PLASTIC NPN-PNP TRANSISTORS Mixed untested @ 57p.
VENITRON 10.7 MHz FILTERS @ 50p each. 3 for £1.
MULLARD STRIPLINE NPN TRANSISTOR BF 362 @ 25p.
COIL FORMERS 3/16" dia. with core at 6 for 25p.
VHF TUBULAR TRIMMERS 6pf at 10p each.
50 PIV 2 1/2 Amp WIRE ENDED DIODES @ 7p, 6 for 25p.
LARGE 6-2" RED LEDS at 10 for £1.
ELECTRET MICROPHONE INSERTS with FET PRE-AMP @ £1.85.
SUB-MIN TANTALUM CAPACITORS 4-7uf 10v.w. 5p, 6 for 25p.
DISC CERAMICS .01uf 50v.w., 1000pf 500v.w., both 20p doz.
10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.
3 PIN PLUG AND SOCKET LIKE RS EUROPEAN 2M. OF CABLE @ 75p pair.
50 ASSORTED 2 WATT ZENERS Untested @ 57p.
MINIATURE 1 1/2" 8 ohm LOUDSPEAKERS @ 75p.
MAINS TRANSFORMERS 240 volt input. Type 1. 24 volt tapped at 14 volt @ £1.30 (p&p 25p). Type 2. 22-0-22 volt 500mA @ £1.60 (p&p 25p). Type 3. 45 volt 6 amp @ £4.50 (p&p 35p). Type 4. 20 volt 1 amp twice. 10 volt 1 amp twice @ £4.50 (p&p 35p). Type 5. 45 volt 2 amp. 45 volt 500mA @ £3.50 (p&p 35p). Type 6. 16 volt 2 amp @ £1.60 (p&p 25p). Type 7. 24 volt 1.75 amp @ £1.16 (p&p 25p). Type 8. 30 volt 1 amp @ £1.60 (p&p 25p). Type 12. 22 volt 1 amp 7.5 volt 500mA, 6 volt 1 amp @ £1.60 (p&p 25p).
THYRISTORS 10 amp Type 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
MINIATURE POLYSTYRENE CAPACITORS 12, 15, 20, 25, 30, 56, 100, 120, 150, 1000pf. All 20p doz.
400mW ZENERS unmarked good. 3-6v, 6-8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 38 volt. All at 10 for 40p.
WIRE ENDED ELECTROLYTICS 100uf 100v.w. @ 10p, 6 for 25p.
MULLARD C 281 .1uf 250v.w., CAPACITORS @ 20p doz.
LM 380 AUDIO I.C. with various circuits @ 80p.
MULLARD TRANSISTORS BC 549 @ 10p each. 8 for 50p.
20 PHOTO TRANSISTORS AND DARLINGTONS Assorted untested @ £1.
200 ASSORTED 1/2 watt RESISTORS for 75p.
VARIABLE CAPACITORS Direct drive. 5pf @ 75p, 10pf @ 75p, 30pf @ 85p, 125+125pf @ 55p, 100+200pf @ 55p.
CRYSTAL PACKS 30 assorted 10X @ £1.10, 20 assorted 10XJ @ £1.10, 20 assorted FT 243 @ £1.50, 20 assorted FT 241A @ £1.10.
AUDIO AMP I.C.'s TCA 940 @ £1, TBA 820 @ 55p, TBA 810 @ £1, TBA 800 @ 85p, SN 76001N @ 60p.
50 1 Amp S.C.R.'s THYRISTORS untested for £1.
25. 5 AMP STUD MOUNTING THYRISTORS untested for 75p.

Please add 20p for post and packing on U.K. orders under £2. Overseas orders at cost.

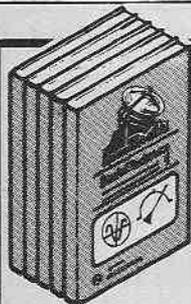J. BIRKETT
RADIO COMPONENT SUPPLIERS
 25 The Strait, Lincoln LN2 1JF Tel. 20767



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.
 Bound in stiff linen. Cover size 8 1/2 in x 5 in.
 Price £7.50 per set (we pay the postage).

Book 1. Introducing Electronics Book 4. Meters/Voltage-dividers
 Book 2. Resistors/Capacitors Book 5. Transistor Project Circuitry
 Book 3. Inductors/Diodes

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm.

Order now:
 Selray Book Company
 60 Hayes Hill
 Bromley
 BR2 7HP

OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name:

Address:

EE16

GREENWELD

443D Millbrook Road, Southampton
 SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

THE NEW 1978-9 GREENWELD

CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE 30p + 15p POST

KITS OF BITS FOR THIS MONTH'S EE PROJECTS

MAY 1979
 ELECTRONIC DICE
 XENON STROBE
 S.W. CONVERTER
 INTRUDER ALARM

APRIL 1979
 SHAVER INVERTER
 TOUCH BLEEPER
 TRANSISTOR TESTER
 TOUCH BLEEPER

MARCH 1979
 LABCENTRE
 A portable "instant" electronic workshop with tools, power supplies and test equipment for design work in logic (TTL and CMOS), audio, r.f. etc.

CAR DIRECTION
 INDICATOR
 ONE-TRANSISTOR
 RADIO

Prices not available at time of going to press. Please send S.A.E. for full details.

E.E. 20+20 TUNER
 AMPLIFIER

We can supply all parts required except the components for the RF unit for approx. £40. Send SAE for detailed list.

NOTE: A more detailed list of parts supplied in these and other kits is available on receipt of a SAE.

"DOING IT DIGITALLY"

This new series which started October 1978 is bound to be a big success. We supply a complete set of parts (as we did for last year's Teach-in series) for just £19.75 + £1 post for the Electronic Test Bed, and £2.75 for additional parts required for first 6 parts.

The GREENWELD
 Amplifier Kit

Ideal for the beginner to make, this kit is complete right down to the last screw!! Easily constructed on the PCB provided, the 4 transistor circuit will give 2W output from a crystal cartridge. Battery version £1.75, or with transformer for mains operation £3.95

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.25

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW. MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210. £3.35
K002 Extended range. 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.058, 0.1, 0.15, 0.22, 0.33, 0.47µF, 110 altogether for £4.75
K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for £12.30
K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.58, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for £14.20

K007 Electrolytic capacitors 25V working small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 170 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M. E12 series. Total 610 resistors, £6.50

K022 Extended range, total 850 resistors from 1R to 10M £8.30

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 38V. E24 series. Total 280 for £15.30

K042 As above but 5 of each value £8.70

TRANSFORMERS

All mains primary: 12-0-12V 50mA 85p; 100mA 85p; 1A £2.50, 6-0-6V 100mA 85p; 1 1/2A £2.40, 9-0-9V 75mA 85p; 1A £2.10, Multitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.80; 20V 21A £3.80; 25V 1 1/2A £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50; 12V @ 250mA twice £2.00

RELAYS

W847 Low profile PC mntg 10x33x20mm 6V coil, SP CO 3A contacts, 85p
W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A, 85p
W839 50V ac (24V DC) coil, 11 pin plug in type, 3 pole c/o 10A contacts. Only 85p
W846 Open construction mains relay, 3 sets 10A c/o contacts, £1.20
W877 675R 12-27V. DPCO 23 x 20 x 10mm sealed can 85p.
W880 230V a/c DPCO 10A contacts, enclosed case £1.30
W850 200R 5-12V DPCO, 23 x 20 x 10mm, sealed can 88p.
 Send SAE for our relay list—84 types listed and illustrated.

HEAT SINK OFFER


Copper TOS sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

POLYTHENE SHEET

Size 36 x 18" 200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £19

Newnes

constructors projects

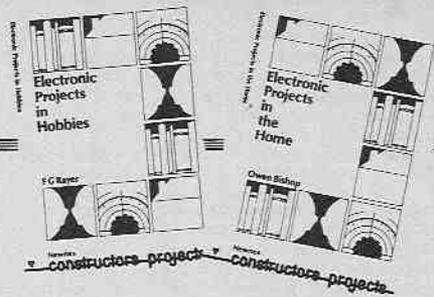

☆ This new series has been specially compiled for the electronics enthusiast.

Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify circuit operation, and circuit board layouts are suggested. Shopping lists of components are drawn up for each project.

☆ The first four titles are available now at £2.25 each (US \$5.25)

Electronic Projects in Audio R. A. Penfold
Electronic Projects in Hobbies F.G. Rayer

Electronic Projects in the Home Owen Bishop
Projects in Radio and Electronics Ian R. Sinclair

☆ Also available six Constructors Guides:

Electronic Diagrams £1.80 US \$4.25
Electronic Components £1.80 US \$4.25
Simple Circuit Building £1.90 US \$4.50

Printed Circuit Assembly £1.80 US \$4.25
Project Planning and Building £1.90 US \$4.50
Practical Electronic Project Building £1.90 US \$4.50

Write for a free colour brochure about all our hobby books to

Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH



TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

Courses in
C & G Elect. Technicians
C & G Elect. Installations
Telecomms. Technicians Exams
Television Servicing
Radio Maint. & Repairs (BIET)
Pract. Radio & Electronics
Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE43 Reading RG7 4PF.

NAME (Block capitals please) _____


ADDRESS _____

POSTCODE _____

Other Subjects _____ AGE _____

Accredited by CACC Member of ABCC

Clef Kits

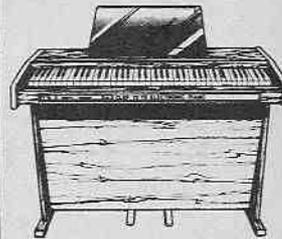

Designer approved quality kits for Electronic Musical Instrument Construction.

JOANNA 72 & 88 PIANOS

Six and 7½ Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia—a feature not available in any other design. A new physical layout has been adopted to simplify construction.

P.E. STRING ENSEMBLE

The only kit available to the proven A. J. Boothman Design for this versatile String Machine.


Sent S.A.E. to:

Clef Products (Dept E.E.)

16 Mayfield Road, Bramhall, Cheshire SK7 1JU.

PRECISION HAND TOOLS

PLIERS



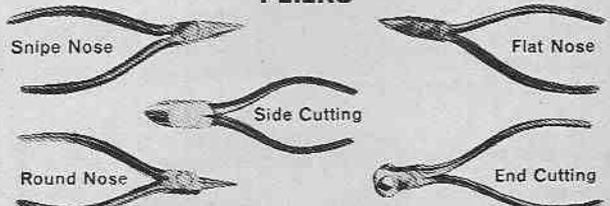


SIZES: WATCHMAKERS 4 inch; INSTRUMENT MAKERS 4½ inch
British-made precision box-jointed hand tools with insulated handles, each tool packed in an attractive pvc wallet.

Only £3.85 each OR any 3 tools FOR ONLY £10.80 inc P&P

C.W.O. to **QUINTON TOOL SUPPLIES**, Dept. E.E.,
52 Grayswood Park Road, Birmingham B32 1HE

+ BATTERY FLUORESCENT LIGHTING —

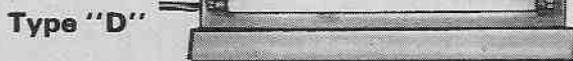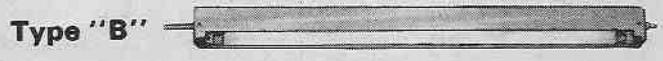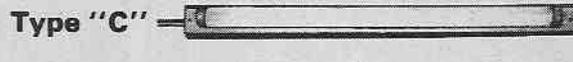

White Enamel cases as shown above, including lampholders. Type "A" or "B" £1.50. Case only, £1.00. Plastic Lampholders to suit 50p pair. Ceramic (adaptable) 40p pair. Tubes to fit (21 in.) £1.00. (These can only be supplied when cases are ordered due to risk of postal damage.) Case type "C" (18 in.) or Case type "D" (12 in.) including lampholders £1.25.

INVERTER TRANSFORMERS, special design for maximum efficiency £1.00 each
 Transistor, Heat Sink, Circuit board cut to size, Resistor, Capacitors etc £1.00 pack
 21 in. Fittings built and tested £4.95
 12 in. ditto (Batten type) £3.95

THIS IS ABOUT HALF THE PRICE THAT A SIMILAR FITTING WOULD COST YOU ELSEWHERE!!!!
 WHY NOT DO AS MANY OTHERS ARE DOING. BUILD THEM AND SELL THEM TO YOUR CAMPING FRIENDS?

PRINTED CIRCUITS. WHY NOT MAKE YOUR OWN WITH FOTOLAK POSITIVE LIGHT SENSITIVE LACQUER

Now you can produce perfect printed circuits in minutes! Method: Spray cleaned board lightly with lacquer. When dry, place positive master of required circuit on now sensitised surface. Expose to daylight. Develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK Aerosol	£1.50	Plain Copper-clad Fibre-glass	Single-sided	Double
Developer	30	Approx. 3.18mm thick sq. ft.	£1.25	£1.50
Ferric Chloride	40	Approx. 2.00mm thick sq. ft.	£2.00	£2.25
Clear Acetate Sheet	12	Approx. 1.00mm thick sq. ft.	£1.50	£1.75
Daylo Pens	98	Approx. .75mm thick sq. ft.	£1.25	
		Single-sided Copper-clad paxolin		
		Pack of 10 sheets each 245mm x 150mm	£2.50	

Giant packs of unused mixed components! Weight 4lbs., these contain an assortment of resistors (carbon and wire-wound); capacitors, (electrolytic, paper, silver-mica, polyester and polystyrene); transistors, diodes, volume and pre-set controls and hosts of other 'bits and pieces'. No two bags are the same, but all contain a jolly good mixture of parts. Ideal for the odds and ends box!!! Per bag £3.00


Brand new printed circuit boards containing I.C.'s, transistors, diodes, resistors, capacitors etc. etc. It is quite impossible to list these so we are selling by weight at £1.00 per lb. This could include upwards of 100 integrated circuits! Send as many £1's as you wish, we will weigh as varied a parcel as possible and refund your change!

SPECIAL OFFER! Few only 3-channel (each 750 watts) Sound-to-light units. Fantastic value for money! Plug into any loudspeaker socket and create your own disco-type light show! Any mains lamps may be used . . . £17.95

PLEASE NOTE: All lighting and printed-circuit materials plus 8% VAT. Other goods 12½%. No VAT on overseas orders. Postage **INLAND** 65p per order. Overseas include extra to cover. We will refund any excess paid. Any enquiries for further details **MUST** include stamped addressed envelope!

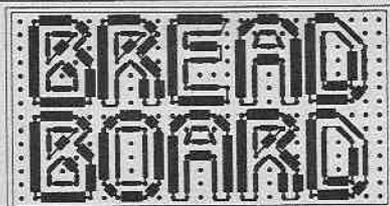G. F. MILWARD (ELECTRONIC COMPONENTS LTD.), 369 Alum Rock Road, B'Ham B8 3DR. 021-327 2339

The action-packed show for the electronics enthusiast now includes the Midlands among its venues. If hobby electronics is your interest or your business, then Midlands Breadboard is tailor-made for you.



Crammed with the gear that constructors need. Circuit boards, components, audio kits, d.i.y. computer systems, electronic musical instruments — you'll find it all here. And you can buy it on the spot — or browse at your leisure. Demonstrations and competitions (exciting prizes!) keep the show humming with activity.

P.S. There's a London Breadboard too, December 4-8th, Royal Horticultural Halls — come to both!

- I want to visit the show. Send me more details nearer the date.
- Please send me details now of exhibition space.

Name

Position

Company

Address

Telephone Telex

Bingley Hall, Birmingham,
23-26 May, 10 am - 6pm
Admission: £1 Adults
75p Students

Return to: Trident International Exhibitions Limited
 Abbey Mead House, 23a Plymouth Road,
 Tavistock, Devon. PL19 8AU

Telephone: 0822 4671 Telex: 45412 TRITAV

LOWER PRICES !!

SUPERIOR CASIO WATCHES

All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100ft. (except Sports watches and 50QS-17B-66 feet).

DOWN 46CS-27B PRICE REDUCED

Almost certainly the slimmest and most sophisticated ALARM CHRONOGRAPH available today.

- LC Display of hours, minutes, seconds, day; and with day, date, month and year.
- Optional 12 hour with am/pm or 24 hour clock display.
- 24 hour alarm setting.
- Optional hourly chimes.
- Chrono measures from 1/10 second to 6 hours.
- Net, lap, 1st and 2nd place.
- 7.8mm Stainless steel case
- Mineral glass face
- Water resistant to 100 feet
- Less than + 10 seconds/month



Only £39.95

SPORTS WATCHES



DOWN
F-100
Left: 9.45mm
Was £29.95
£19.95

52QS-14B
Right: 8mm
Was £44.95
£22.95

Up to 25 functions. Net, lap and first and second place times to 1/100th sec. F-100 Resin case, strap 52QS-14B 5/5 encased version and bracelet.

DOWN CHRONOGRAPH AND ALARM



45CS-22B
Left: Chrono
Was £69.95
£34.95

25CR-16B
Right: Alarm
Was £69.95
£24.95

CHRONOGRAPH. Displays hours, minutes, seconds and day of week; and day, date, month and year calendar. Selectable 12 hour (with am/pm) or 24 hour clock. With stopwatch measuring net, lap and 1st and 2nd place times from 1/200 sec to 6 hrs. Dual time facility.

ALARM. Displays hours, minutes, seconds (or date) day, am/pm. Perpetual calendar. 24 hour alarm. Not illustrated.

50QS-17B	4 digits Square	£19.95
51QR-20B	4 digits Round	£19.95
51QR-19B	6 digits Round	£22.95
51QR-18B	6 digits Round	£22.95
54QS-16B	6 digits Square	£24.95
54QS-15B	6 digits Square	£24.95
60QR-22B	6 digits Round Chronograph	£29.95
60QS-20B	6 digits Square Chronograph	£34.95
25CS-16B	6 digits Square Alarm	£34.95

NEW THE AMAZING MELODY 80 Musical Calculating Diary Watch

ADVANCE SPECIFICATION: Two separate Alarm Tunes. Calculator with keys 18 playing individual notes—a mini synthesizer! Complete Calendar. Watch. Stopwatch measuring net and lap times to 1/20 second. Alarm Timer and Calculator with $\sqrt{\quad}$, % full memory. Date calculations. RRP £30.95

£25.95

NEW THE INCREDIBLE AQ2000 Universal calendar watch

LC Display of hours, minutes, seconds, am/pm, full calendar display of day, date & every Sunday. Also digital date, month, year, with day, Sundays. Three date memories. Two independent alarms with hold and recall. Countdown alarm timer or Time Memory (24hr), or 1/10th second stopwatch. Will display any monthly calendar from 1901 to 2099. Memorises and displays three optional important dates. Calculator with full memory. %, K, $\sqrt{\quad}$. Battery life approx. 1 year. 1 x 2 1/2 x 4 1/2 ins. Leatherette wallet. RRP £29.95 An incredible £24.95



MOST CASIO products in stock. Send 25p for brochures. Prices include VAT. P. & P. Send cheque. P.O. or phone your Access or Barclaycard to:

TIMETRON

Dept. EE, Beaumont Suite, 164-167 East Road, Cambridge CB1 1DB. Telephone 0223 67503
Callers welcome by appointment.

SMALL ADS

The prepaid rate for classified advertisements is 16 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £4.40 per single column centimetre. All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

DISCOVER ELECTRONICS. Build forty easy projects including: Metal Detector; Wireless Transmitter; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1.29 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-25 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-50 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5 each plus 25p P. & P.

LOTS MORE! Send 25p for lists. Prices include VAT.

BOFFIN PROJECTS

4 CUNLIFF ROAD, STONELEIGH
EWELL, SURREY. (E.E.)

NEW SHOP IN EAST KENT. Vast range of electronic components, equipment, hardware. Technocraft, 143 Tankerton Road, Whitstable. 265097. Open Tuesday to Saturday. Easy parking.

ELECTRONIC COMPONENTS and E.E. project kits 1973-now. Catalogue SAE, plus 30p. Jadebond Ltd. Middridge Drift Ind. Est., Middridge, Shildon, Co. Durham. Tel: Shildon (038 884) 3845.

7lb ASSORTED COMPONENTS £5.60, 3 1/2 lb £2.10. Small Audio Amplifiers. 3 Transistors equivalent to AC128, OC72, with circuit, 3 for £1. 300 small components, Transistors, Diodes £1.50. Wire ended Neon's, 20 for £1. Panel with 40 74 series ICs, £1.50. No postage. List 15p, Refundable insurance add 15p. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

GUARANTEED ICs. 7400/10p 7447/55p 7473/24p 74121/24p 4000/15p 4011/15p 4017/15p 4027/32p 709/22p 741/22p 7805/60p NE555/25p. Many more! SAE full list CP ICs 22 Oakfield Road, Croydon, Surrey.

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.

2. The publishers reserve the right to refuse or withdraw any advertisement.

3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO Electronics, Grenfell Place, Maidenhead, Berks.

COMPONENT IDENTIFICATION, data service, also numerous components available. Details from B. Grundy, 16 Park Lane, Waddingborough, Lincoln.

PARCELS. Caps, Res, Trans, Diodes, items. Over 100 parts, £2-25, 200, £3-50. List s.a.e. Sole, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

Books and Publications

ALL SERVICE SHEETS and manuals supplied—enquiries welcome—SAE please. Repair any TV easily, full, individual instructions any set for £5 (circuit £1 extra). Send details of set to TIS (EE), 76 Church Street, Larkhall, Lanarks ML9 1HE.

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated Manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the Manual covers in 13 Chapters, where to obtain all the work you need, materials required, all instructions rewind charts and how to take data, etc. A goldmine of information. How to set up your home workshop and how to cost each job to your customer. £4.00 plus 30p P. & P. U.K. CWO to:

INDUSTRIAL SUPPLIES

102 PARRSWOOD ROAD, WITHINGTON,
MANCHESTER 20, DEPT. EE

Service Sheets

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

For Sale

NEW BACK ISSUES of "EVERYDAY ELECTRONICS". Available 60p each Post Free, open PO/Cheque returned if not in stock. BELL'S TELEVISION SERVICES 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

E.E. BACK COPIES, Volumes one to six complete. Offers? 01-828 4744.

Record Accessories

STYLI, CARTRIDGES FOR MUSIC CENTRES etc. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. FELSTEAD ELECTRONICS (EE), LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.

Educational

HOLIDAY FOR BOYS, 14-16 years, August 1979. Tuition and Practical Work in Engineering (Karting), Electronics, Radio Production and Tape Recording and Photography. 10 days in Oxfordshire, £38. Write for free brochure. Inter School Christian Fellowship, c/o Ashcroft, Old Bolingbroke, nr. Spilsby, Lincs.

Miscellaneous

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4.
Reg. Office, 22 Coningsby Gardens.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10-19	2-65	1-45	0-75	0-60
20-29	2-85	1-65	0-90	0-70
30-34	3-05	1-75	1-00	0-75
35-40	3-40	1-95	1-15	0-84
41-43	4-55	2-55	1-95	1-30
44-46	5-05	3-05	2-15	1-70
47	8-00	5-00	3-00	1-80
48	15-00	9-00	6-00	3-30

SILVER PLATED COPPER WIRE

14, 16, 18	4-50	2-25	1-44	0-90
20 & 22	5-00	2-85	1-74	1-06
24 & 26	5-70	3-31	2-00	1-22
28 & 30	6-67	3-86	2-35	1-44

Prices include P & P and VAT.
SAE brings list of copper & resistance wires.
Dealer enquiries invited.

TUNBRIDGE WELLS COMPONENTS,
BALLARD'S, 108 Camden Road, Tunbridge
Wells, Phone 31803. No lists, enquiries S.A.E.

AERIAL BOOSTERS improve weak VHF radio and television reception, price £5. SAE for leaflets, Electronic Mailorder Ltd., Ramsbottom, Bury, Lancashire, BL6 5AG.

PRINTED CIRCUIT BOARDS FOR EE2020 TUNER-AMP DESIGNER APPROVED

- ★ Professional boards in Fibreglass, roller tinned and drilled.
- ★ COMPLETE SET OF FIVE BOARDS ONLY £10.95 incl. p/pkg.
- ★ ALSO AVAILABLE INDIVIDUALLY:
 - ★ BOARD A £3.67
 - ★ BOARD B £3.27
 - ★ BOARD C £1.10
 - ★ BOARD D £2.14
 - ★ BOARD E £1.15

Add 25p p/pkg. on orders under £10.
SAE for list of other p.c.b.s.

PROTO DESIGN 14 DOWNHAM ROAD, RAMSDEN HEATH, BILLERICA, ESSEX CM11 1PU

Resistors 1/4W 5% 2R2-2M2 (E12). 10 each or more of each value 90p/100. 100 assorted, our mixture 75p/100. C60 cassettes in library cases 30p each. Miniature relays 17 x 30 x 28mm 600Ω coil 4 sets change over contacts 50p each. Prices include V.A.T. Add 10% postage.


SALOP ELECTRONICS
23 Wyle Cop, Shrewsbury

INDEX TO ADVERTISERS

Arrow Electronics	...	314
Bi-Pak	...	297
Birkett J.	...	315
B.N.R.E.S.	...	261
Boffin Projects	...	318
Brewster S. & R.	...	258
Bull J.	...	313
Charcroft Electronics	...	319
Chromatronics	...	311
Clef Projects	...	316
Collier McMillan (B.I.E.T.)	...	316
Crescent Radio	...	260
Dewtron	...	304
E.D.A.	...	260
Electroni-Kit	...	304
Electrovalue	...	304
George Sales, David	...	311
G.M.T. Electronics	...	262, 263
Greenweld	...	315
Heath-Kit	...	298
Home Radio	...	314
ILP Electronics	...	301
Industrial Supplies	...	318
Intertext (ICS)	...	258
Magenta Electronics	...	298
Maplin Electronics Supplies Ltd.	...	cover iv
Marshall A.	...	259
Metac	...	Cover II
Milward G. F.	...	317
Newnes-Butterworth	...	316
Phonosonic	...	258
Powell T.	...	314
Proto Design	...	319
Quinton Tool Supplies	...	316
Radio & TV Components	...	Cover III
Salop Electronics	...	319
Scientific Wire Co.	...	319
Selray Book Co.	...	315
Solar-Tek	...	314
Swanley Electronics	...	319
Tamtronik	...	320
Terminal Display Systems	...	320
Timetron	...	318
Trident Exhibitions	...	317
TUAC	...	303
Vero Electronics	...	260
Watford Electronics	...	257

wonderboard
patents pending

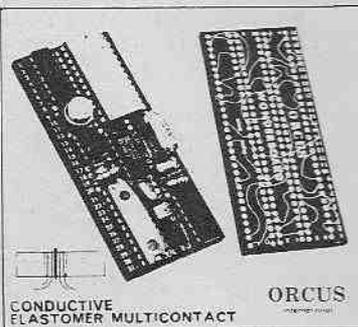SOLDERLESS CIRCUIT BOARDS
"One for each circuit"



CONDUCTIVE ELASTOMER MULTICONTACT

ORCUS

Build
Your Circuits
Just Once
In Minutes...

It's crazy to build, unbuild, construct and destruct your circuits on expensive "Breadboards". Now very economically on WONDERBOARD, you plug your components into one side of the board, the wires into the other, and you install the finished circuit in your equipment. They're like PC boards, but no soldering (which is enemy No. 1 of prototypes). Change any wire or component any time without disturbing others. Up to six interconnecting wires and one component lead into one multicontact. WONDERBOARDS accept all IC's from 4 to 60 pins and discrete components too.

Reliable? They conform to applicable sections of USA Military Standard MIL-A-46146 and are used by the US Navy. You can't ask for better. WONDERBOARDS the universal board for equivalents of single-sided, double-sided, plated-thru' hole, and multilayer printed circuits.

"Small Wonder"
12 IC DIL-14 capacity
(Equiv. No. tie-points 1302)

£2.80

"Big Wonder"
48 IC DIL-14 capacity
(Equiv. No. tie-points 5208)

£11.20

All prices include VAT and P&P. Send cheque or postal order to:-

CHARCROFT ELECTRONICS LIMITED
Charcroft House, Sturmer, Haverhill, Suffolk CB9 7XR
Telephone: Haverhill (0440) 5700 Telex: 817574

Please mention
EVERYDAY
ELECTRONICS
when replying to
advertisements

SINCLAIR PRODUCTS microvision tv world model £147.95, UK model £89.95, mains adaptor £6.75. PDM35 £28.95, mains adaptor £3.19, case £3.19. DM350 £68.95, DM450 £97.95, DM235 £49.45, rechargeable battery £7.50, mains adaptor £3.70, case £8.45. Enterprise prog. calculator with accessories £22.95. Cambridge prog. calculator £12.13, prog. library £4.45, mains adaptor £3.20.
CSC MAX100 freq. meter £75.40.
CALSCOPE oscilloscopes send see for data or see the Calscope advert in this magazine. Super 6 £174. Super 10 £236.
COMPUTER GAMES chess challenger £167. Chess challenger 7 £79. Checker challenger 4 £84. Checker challenger 2 £30. Atari videocomputer £198. Cartridges £13.45.
COMPONENTS send see for full list. 1N4148 1-4p. 1N4002 2-8p. 741 15p. bc182b, bc183b, bc184b, bc212b, bc213b, bc124c 4-3p. Resistors 1W 5% E12 10R to 10M 1p, 0-8p for 50+ of one value. 16V electrolytics. 5/12/5/10/22uf 5p, 100uf 6p, 100uf 6p, 1000uf 16p. 1 lb FeCl £1.05. Dale pen 79p. 60 sq ins pcb 5p.
BATTERY ELIMINATORS 3-way type 6/7/9v 300 ma £2.55. 100ma radio type with press-studs 9v £3.35. 9v + 9v £4.50. Car converter 12v input, output 4 1/2/6/7 1/2/9v 800ma £2.50.

TRANSFORMERS 6-0-6v 100ma 74p, 1 1/2 £2.35, 6-3v 1 1/2 £1.89, 9-0-9v 75ma 74p, 1a £2, 2a £2.60, 12-0-12v 100ma 99p, 1a £2.49.
IC AUDIO AMPS with pcb. JC12 6W £1.60. JC20 10W £2.95. Send see for data. **TV GAMES** send see for data. AY-38500 + kit £8.95. Rifle kit £4.95. AY-38500 + kit £12.50. Stunt cycle chip + kit £10.90. Tank battle chip + kit £13.65 (in stock).
BATTERY ELIMINATOR KITS send see for data. 100ma radio types with press-studs 4 1/2 £1.40, 6v £1.40, 9v £1.40, 4 1/2 + 4 1/2 £1.80, 6 + 6v £1.80, 9 + 9v £1.80. Stabilized 9-way types 3/4 1/2/7 1/2/9/12/15/18v 100ma £2.80. 1Amp £6.40. Stabilized power kits 2-18v 100ma £3.60, 2-30v 1A £6.95, 2-30v 2a £10.95. 12v car converter 6/7/9v 1a £1.35.
T-DEC AND CSC BREADBOARDS s-dec £3.17, l-dec £4.02, u-dec £4.40, u-dec £5.73, exp300 £9.21, exp350 £3.40, exp325 £1.73, exp45 £2.48.
BI-PAK AUDIO MODULES s450 £23.51, AL80 £4.86, pa100 £16.95, spm80 £4.47, bmt80 £5.95, stereo 30 £20.12. AL30 £3.95, PA12 £7.60, PS12 £1.39. MA30 £35.44.
SWANLEY ELECTRONICS (Dept. EE)
32 Golds Rd., Swanley, Kent
Post 30p extra. Prices include VAT.
Official and overseas orders welcome.

TAMTRONIK LTD (DEPT EE)

217, Toll End Road, TIPTON, West Midlands DY4 0HW TEL: 021-557-9144

Printed Circuit Boards & KITS for EE projects

Mag issue	PROJECT	Ref	P.C.B.	KIT	KIT CONTENTS (see key)	
1978 Jan	Audio Visual Metronome	E001	+ 65	5-50	B.E.H.L.	
	Touch Switch	E002	+ 74	1-80	B.E.	
	Rapid Diode Check	E004	+ 52	2-23	B.E.H.L.	
Feb	Car Alarm	E005	+ 80	5-48	B.E.G.J.L.	
	Lead Tester	E006	51	4-17	B.E.H.L.	
	Chaser Light Display	E007	+ 75	20-32	B.E.H.L.	
	A.C. Meter Converter	E008	+ 60	5-37	B.E.H.L.	
Mar	Audio Test (2 Pcb's)	E009	+1-74	14-96	B.F.G.J.	
	C.R. Substitution Box	E010	+ 94	8-45	E.H.L.	
	Catch-a-Light	E011	+ 82	8-35	B.E.H.L.	
	Weird Sours	E012	+ 62	5-29	B.E.H.L.	
Apr	Roof Rack Alarm	E013	+ 60	—	—	
	Mains Delay Switch	E014	+ 84	12-48	B.E.J.L.	
	Pocket Timer	E015	+ 60	3-48	B.E.H.L.	
May	Flash Meter	E016	+ 75	11-09	B.E.H.L.	
	Mains Tester	E017	+ 54	1-35	B.E.H.	
	Teach In—Power Amp	E018	+ 74	1-55	B.E.H.L.	
	Power Pack	E019	+ 70	5-71	B.E.H.L.	
Jun	Tele-Bell	E020	+1 000	10-89	B.E.H.L.	
	Insitu—Transistor Tester	E021	+ 65	5-10	B.E.G.H.L.	
	Teach In—S.W. Receiver	E022	—	2-61	E.	
	Power Slave	E023	- 1-75	—	—	
	Visual Continuity Tester	E024	—	4-09	E.H.L.	
Jul	Auto Night Light	E025	+ 85	9-39	B.E.G.H.L.	
	Short Wave Radio	E026	—	7-86	E.J.	
	Quagmire	E027	+1-40	7-39	B.E.G.H.	
	Logic Probe	E028	+ 50	2-76	B.E.G.H.L.	
	Slave Flask	E029	+ 55	2-72	B.E.	
Aug	M.W. Mini Radio	E030	50	4-78	B.E.J.L.	
	Audio Freq. Signal Generator	E031	+ 85	12-41	B.E.J.L.	
	CHRONOSTOP	E032	+2-50	29-20	C.G.K.M.P.	
	R.F. Signal Generator	E033	—	15-82	E.H.	
Sep	Sound to Light Unit	E034	—	5-14	E.H.L.	
	Guitar Tone Booster	E035	75	4-06	B.E.H.L.	
	Car Battery State Indicator	E036	65	1-82	B.E.	
	C.M.O.S. Radio	E037	+1-45	10-76	B.E.G.H.L.	
Oct	Fuse Checker	E038	—	1-60	E.H.L.	
	Treasure Hunter	E039	1-25	15-95	B.E.G.H.L.	
	DOING-IT-DIGITALLY—TTL TEST BED	E040	—	20-65	N.	
	DOING-IT-DIGITALLY—1st 6 PARTS	E041	—	3-60	N. (inc. add. comps.)	
	Audio Effects Oscillator	E042	—	2-40	E.H.L.	
	Water Level Alert	E043	+ 70	3-98	B.E.G.J.L.	
	SUBSCRIBERS TELE-TELL METER	E044	+2-80	19-90	C.E.G.K.M.P.	
Components to add 3rd digit to kit E044	E044A	—	3-00	E.		
Nov	Combination Lock (2 x PCB's)	E045	+2-55	19-80	B.E.H.L.	
	Hotline Game	E046	+ 75	4-57	B.E.H.	
	Mini-Module—Passive Mixer	E047	—	2-47	B.E.H.	
	Audible Flasher	E048	—	1-21	E.H.	
Dec	Fuzz Box	E049	+ 75	5-20	B.E.H.L.	
	Vehicle Immobiliser	E050	1-00	4-56	B.E.H.L.	
	Mini-Module—Microphone Amp	E051	—	2-45	D.E.H.	
1979 Jan	Mini Module—Continuity Tester	E052	+ 80	3-75	B.E.H.	
	Lights Reminder	E053	+ 80	6-02	B.E.G.H.L.	
	1st First	E054	—	1-58	E.H.	
	Roulette inc. colour printed wheel (2 x PCB's)	E055	+3-40	17-90	B.E.H.	
	Headphone Enhancer	E056	—	2-06	E.H.L.	
DEC	EE 2020 Tuner Amp—Board A inc. RF unit	E057	3-65	54-44	B.E.G.H.	
	EE 2020 Tuner Amp—Board B	E058	3-40	22-38	B.E.H.	
	EE 2020 Tuner Amp—Board C	E059	1-45	4-30	B.E.H.	
	EE 2020 Tuner Amp—Board D	E060	2-20	16-53	B.E.H.	
TO	EE 2020 Tuner Amp—Board E Hardware & wire	E061	1-40	22-28	B.E.G.H.	
	EE 2020	E062	—	11-95	K.	
FEB	EE 2020	E063	10-50	123-00	C.E.G.K.	
	Longwave Converter	E064	95p*	6-20	B.E.H.L.	
	Mini Module Audio Modulator	E065	—	1-53	E.H.	
	Power Supplies	E066	80p*	22-12	B.E.H.	
	Thyristor Tester	E067	55p*	3-92	B.E.H.L.	
	Sound Adaptor Treasure Hunter	E068	90p*	5-99	B.F.H.	
	+ P.c.b.'s designed by Tamtronik to EE circuit specifications					

KEY TO KIT CONTENTS

A Vero-board(s)
 B Printed Circuit Board(s)
 C With screen printed component layout
 D Tag strip
 E ALL Resistors, potentiometers, capacitors, Semi-conductors
 F As E but with exclusions—Please ask for details
 G Diode and/or transistor sockets and/or soldercon pins
 H Hardware includes Switches, Knobs, Lamps & Holders, Fuses & Holders, Plugs & Sockets, Microphones, Transformers, Speakers, Meters, Relays, Terminal Blocks, Battery Connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, Batteries and special miscellaneous items.
 J As H but with exclusions—Please ask for details
 K As H but including connecting wire
 L Suitable Case(s)
 M Suitable Case with Screen printed fascia
 N Full kit to magazine specification standards
 P Kit with professional finish incorporating all prime features including screen printed PCB and case where appropriate

Doing-it-Digitally

TTL ELECTRONIC TEST BED

Complete kit E040
£20.65

Components for first 6 parts E041 **£3.60** (including additional components)
BOTH KITS (special price) £24.00

BARGAIN CORNER

100 x 1/4w 1k carbon resistors 30p
 10 x 1w 5% 1k5 resistors 10p
 10 x 1w 5% 7k5 resistors 10p
 10 x 1w 5% 100R resistors 12p
 10 x 6w 5% 390R wirewound 50p
 10 x 47u 10v Axial Elec. Caps 25p
 4 x NE55 Timer **£1.00**

Plug in mains PSU
 3v/6v/9v/12v DC
 300mA suitable for calculators & T.V. Games **£2.99**

TELE-TEL

Nov. 78 Ref. E044

Subscribers phone call charge meter
 A kit with a professional finish CASE with screen printed fascia similar to magazine photograph but includes provision for 3rd digit.
 An aluminium sub-facia panel is also provided with screen printed hole centres to allow access to preset potentiometers.
 PCB designed to incorporate 3rd digit facility and is screen printed for ease of assembly.
 Basic kit (2 digits) **£19.90**
 (3 digits) **£22.90**

CHRONOSTOP

Aug. 78 Ref. E032

SPLIT 6 TAYLOR lap timing modes plus normal start/stop operation.
 A kit with a professional finish including CASE with screen printed fascia
 PCB with screen printed component layout
 Full Assembly Instructions
PRICE INC. VAT £29.20

SOLDERING IRONS & ACCESSORIES

SRB 18 watt Iron inc. No. 20 Bit **£3.78**
 Stand **£3.25**
 Solder-Savbit 20 inch 52p

Bit sizes No. 90 (1.5mm) " " " 20 (3mm) " " " 21 (4.5mm) " " " 22 (6mm)
 Ideal for Home Constructor

Tamtronik Ltd. reserves the right to change kit content without notice, where necessary to incorporate current modifications or to make valid substitution for temporarily unavailable components. The majority of the kits we advertise can be supplied from stock or compiled at short notice from component stocks held, but when ordering you should be prepared to allow at least ten days, and up to one month, for us to complete your order. Upon receipt of your order, acknowledgement will be made by return post within 48 hours detailing our control number for that transaction. In case of any enquiry please quote this number.

Kits can be supplied excluding P.C.B.'s and/or case. Send SAE for details naming kit and kit reference and free catalogue.
TRADE & EDUCATIONAL ENQUIRIES WELCOME
PRICES INCLUDE VAT P & P 30p

VISIT OUR SHOP AT Telephone or Letter
32 Market Place,
Great Bridge, Tipton,
West Midlands.

Buy it with Access **BARCLAYCARD VISA**

a digitizer adds another dimension

The Bit Pad computer digitizer converts graphic information into digital form for direct entry into a computer. By touching a pen like stylus or a cursor, to any position on a drawing, diagram, photograph, or other graphic presentation, the position co-ordinates are converted to digital equivalents.

- Bit Pad interfaces with almost any micro computer.
- Bit Pad consists of a 15" sq. digitizer tablet (11" sq. active area), a stylus, and a controller cabinet.
- Bit Pad costs only £450 (excluding VAT). Fill in the coupon and we will send you full information and details.

Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate, Blackburn BB1 5SM, Lancs, England


Send to: Department CPED, Terminal Display Systems Ltd., Hillside, Whitebirk Industrial Estate, Blackburn BB1 5SM, Lancs, England.

Name

Address



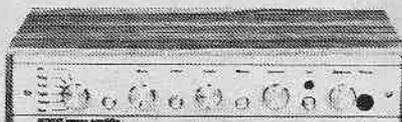Microscopic Network Architecture
 Structural Geology
 Correlation
 Exam marking
 Teaching
 Mensural research
 Measurement
 Menu Market research
 Cartographic Archeological
 Orthodontics Design Geology
 Radiology Microscopy Art
 Structural Civil Mil
 Process Control Gra
 Teaching Games
 Measuring Biology
 Menu Market research
 Archeological App
 Design Geology



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90
£2.50 p&p

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4 15 ohms speakers.

£29.00 + p&p
£2.50

SPECIAL OFFER

30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 GOODMAN compact 12" bass woofers with cropped size 14.000 Gauss magnet, 30 watts RMS handling, plus 2 3" approx. tweeters and cross overs to suit.

£49.00

+ p&p £4.00

BUILT AND READY TO PLAY

30x30 Viscount Available fully built and tested.

39.00

+ p&p £2.50

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95

Per stereo pair + £3.40 p&p.

BSR P200

Belt drive chassis turntable unit semi automatic, cueing device.

£24.95

p&p £2.55

A.D.C. OLM 30 Mk III Magnetic Cartridge to suit.

£7.75



BSR Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle and approx. ideally suited from home or disco use. p&p

OUR PRICE £10.95

£7.55

GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95

p&p £2.00

Size 12" x 8 1/2"

SANYO Nic/cad battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/2" x 1 1/4" x 2" approx.

£7.50

p&p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE WITH DECODER

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz. (150mV/100K) deviation FM signal Frequency Range (Audio) 50Hz to 17KHz within ±1dB Radio FM sensitivity for 3dB below limiting better than 10 uV AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre Size approx length 16" x height 2 1/2" x depth 4 1/4"

240 Volts AC Complete with tuning dial Circuit diagram.

£19.95 p&p
£2.25

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE £25 AT OVER PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE £4.95 p+p £1.00

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2. Stereo pre amp for magnetic, ceramic and auxiliary inputs. OUR PRICE £7.45 p+p £1.00

illus. £7.45

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

p&p £2.05 £11.95

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish £5.95

LED 5 function men's digital watch stainless steel finish £6.95

LED 8 Function CHRONOGRAPH men's digital watch, stainless steel finish £12.95

POCKET CALCULATOR. With LED display, memory and percentage key £2.95

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer £11.95

125 Watt Power Amp Module £13.95

Mains power supply for above unit. £3.50

MULLARD Built power supply £1.50

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers £20.00

VIDEOMASTER Super Score TV Game with pistol mains operation £14.95

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation £41.95


VIDEOMASTER COLOUR SHOT TV GAME Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED. OPPORTUNITY AT £9.95 ONLY



323 EDGWARE ROAD, LONDON W2
21A HIGH STREET, ACTON W3 6NG
ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 12.3.79 and subject to change without notice. EEB5/79

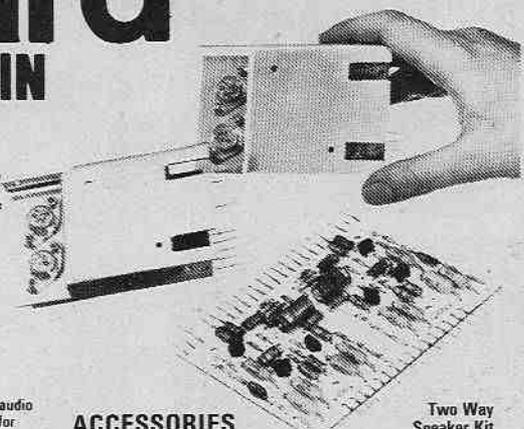ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.



ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.


£2.90 plus £1.50 p & p

Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors.

£3.95 per stereo pair plus £1.50 p & p

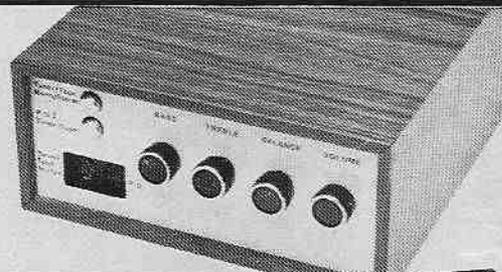Available also to purchasers of the 10 + 10 Amplifier Kit.



50 WATT MONO DISCO AMP

£29.95
P&P £2.50

Size approx. 13 3/4" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls.

Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before loading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

70 watt £57
140 watt peak p&p £4.00
100 watt £65

For personal shoppers only

DUO II SPEAKERS

Attractive teak finish modern design incorporating 2 speaker units — 6 1/2" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz. Impedance 8 ohms. Power 15 watts RMS. 20 watts max. Per stereo pair £17.00

FOR PERSONAL SHOPPERS ONLY

TANNOY 15" Lancaster corner cabinets, traditional design. £20.95 each

NOTE DUE TO INDUSTRIAL UNREST, PLEASE ALLOW EXTRA TIME FOR YOUR ORDER TO REACH YOU.



A quality range of British made electrical accessories plus a 'How to...' book. Do your own home electrical work with complete confidence. See cat. pages 129 to 134.



This superb organ—build the first working section for just over £100. Full specification in our catalogue.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.



A pulse-width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road,
Westcliff-on-Sea, Essex.
(Closed on Monday).

Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £13.98 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages, some in full colour—it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.

Post this coupon now for your copy of our 1979-80 catalogue price 75p.
Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____
ADDRESS _____