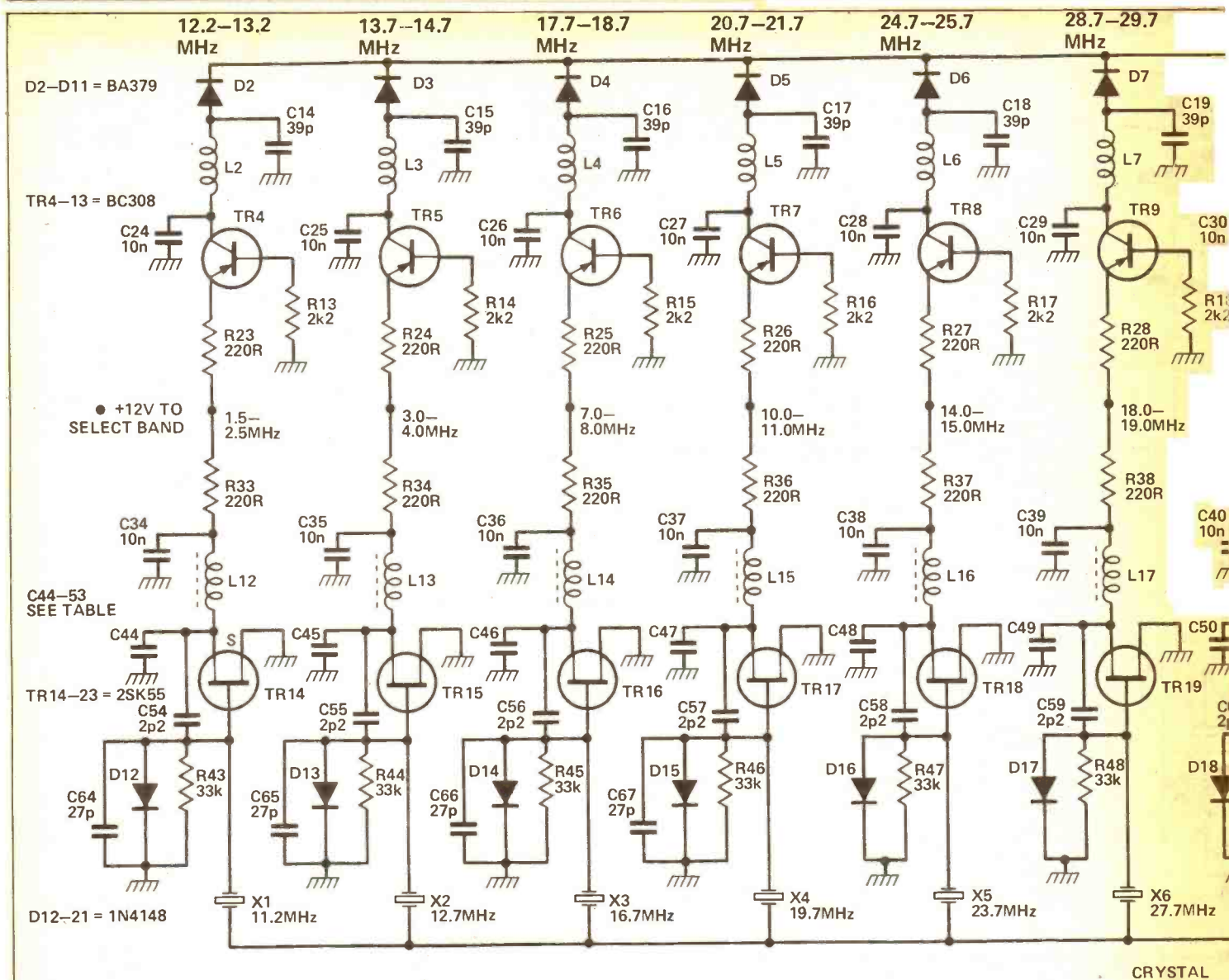
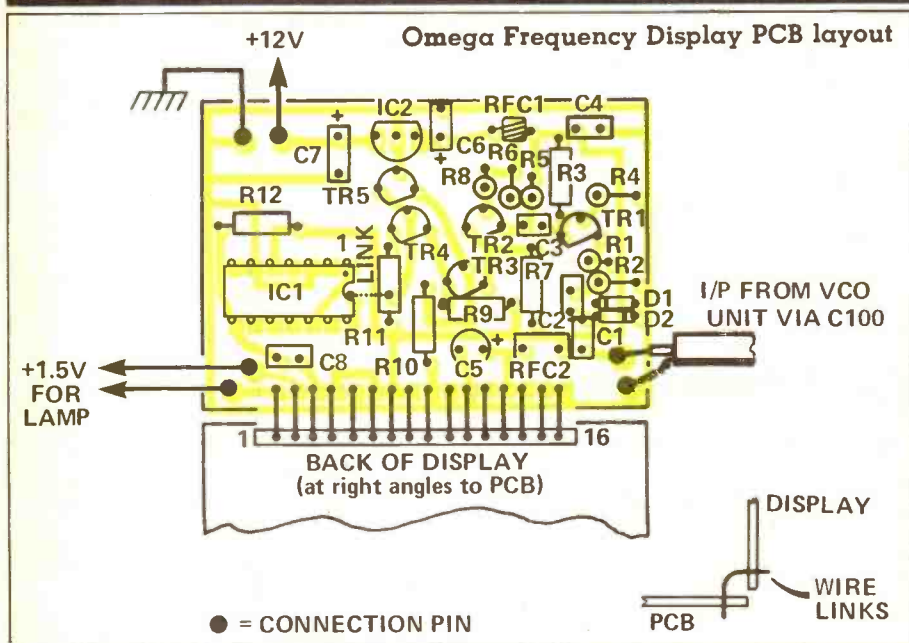




Circuit diagram of crystal oscillator and VCO inductor bank



Component Listing —

- R1, 53
- R2, 12
- R3, 5, 77, 78, 82, 90
- R4, 11, 43 — 52
- R6, 13 — 22
- R7
- R8
- R9
- R10, 74, 89
- R23 — 42, 62, 73
- R54, 58, 61
- R55, 56, 71, 72, 84, 85
- R57, 63, 86, 87, 88
- R59
- R60, 76, 79, 80, 83
- R64, 75
- R65
- R66, 67
- R68