

# Addendum

## Go Foxhunting!

HRT, October


The diagrams below, giving constructional data for the tuned circuit of the simple DF receiver, were omitted from the original article due to lack of space.

## Licence Conditions and the RAE

HRT November

Please note that all references to the Secretary of State for the Home Department should now read the Sec-

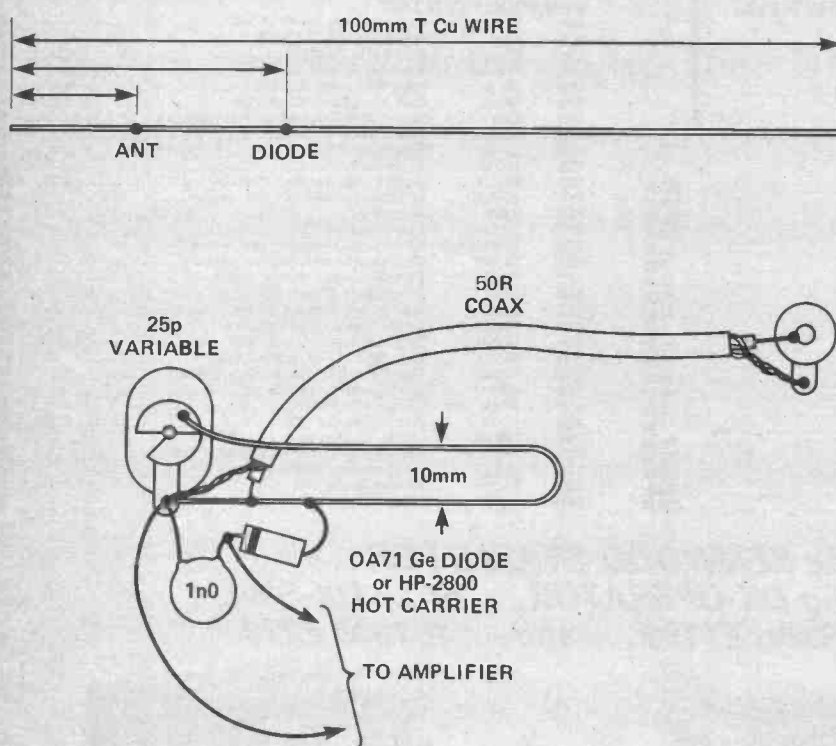retary of State for the Department of Trade and Industry. Also, the term GMT has now been superseded for log. keeping purposes by UCT (Universal Co-ordinated Time).



## Auto Antena Switch

HRT November

The component listing and the overlay diagram were held over from last month due to lack of space. They are given below.

## COMPONENT LISTING

### RELAY DRIVER PCB

R1	1k5 ½W
D1-D7	1N4148
Q1	BFY51
IC1	ULN2803A
JO1	13-pin Yaesu PCB socket
JO2	2-pin socket
JO3	10-pin angled socket

### RELAY BOX

PO1, PO2, PO3	To suit sockets
RL1-RL5	2-pole power relay, 12V (both poles wired in parallel)

### MISCELLANEOUS

15-pin plug and socket; 15-way multi-core cable; box, 222 by 146 by 55mm

### NOTES

IC1 is RS part no. 303-422  
Box is RS part no. 509-254  
JO1 is obtainable from SMC Ltd — see their advertisement for the address.

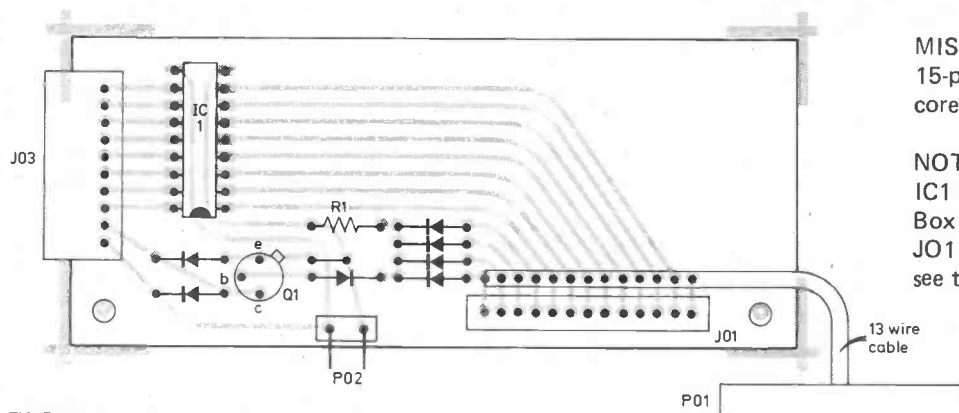


FIG. 7. PCB component location.