D.I.Y. PROJECTS TV/FM Aerial Amplifier Noiseless Fuzz Box Sound Switch

040 00

Home-Brev

0

Made Easy

01

Special Offer-Special Offer-Special Offer-Special Offer No-Mess PCB Etching Kit, including Resist-Pen, PCB Cleaner and TWO Blank Printed Circuit Boards!

ACAF

FEBRUARY 82

MOIN

10.0

Down-To-Earth Approach To Electro

65p

HOW TO SUCCEED IN THE ELECTRONICS BUSINESS:



INVEST 60p AND MAKE £2.40 net profit

Buy Ambit's new concise component catalogue and get £1 vouchers. Use them for a £1 discount per £10 spent. But even without this, you will still find WR&E offers the low prices, fast service and technical support facility second to none.

Here are some examples from the current issue:

Processors Processors CONCLISE PARTS CATALLOVA Processors Processors Processors Processors Processors 1000 11 477 0.18 478 175 100 MHz 2.00 110 MHz 2.00 1001 13 477 0.18 478 0.10 110 MHz 2.00 110 MHz 2.00 1001 13 477 0.18 477 100 MHz 2.00 110 MHz 2.00 1001 13 477 10 11 100 MHz 2.00 110 MHz 2.00 1001 4077 0.18 477 400 14 141549 157 100 MHz 2.00 1001 13 4077 10 14 141549 100 141549 100 MHz 2.00 110 MHz 2.00				L.C. S A rar low p for b types brom: 8 x 14 x 16 x 18 x 20 x 20 x 3 7 8 7 8 7 8 7 8 7 8 7 8 7 8 7 8 7 8 7	SOCKETS ige of high qualit profile DL socke oth the OEM and if eature doubles ze contacts, tim-p act resistance. 0.3" 12p 2 0.3" 12p 2 0.3" 13p 2 0.3" 13p 2 0.3" 13p 2 0.3" 13p 2 0.3" 13p 4 OLTAGE REGUI XX1A TO-220 n G 1A TO-220 ad G 1A TO-23 adj p H5A TO-3 Sv po	y, low cost, ts ideally suited t hobbyist. All sided phospher ilated for low 22 x 0.3" 20p 22 x 0.4" 20p 44 x 0.6" 22p 88 x 0.6" 22p 88 x 0.6" 25p 00 x 0.6" 35p 12 x 0.6" 35p 12 x 0.6" 35p LATORS os 0.58 eg 0.60 j pos 1.10 os 3.95 s 4.25	DISCRET BC237 BC238 BC238 BC239 BC307 BC308 BC309 BC413 BC414 BC415 BC416 BC546 XTALS 1MHz 3.2768MHz 4.194MHz 4.194MHz 4.33MHz	ES E 8p E 8p E 8p E 8p E 8p 2 8p 2 8p 2 10p 2 11p 2 10p 2 11p 2 3.000 1.70 1.70 1.25	C556 C550 C660 C6639 C6640 SC1775 SSD6664 SSD6664 SSD66684 SSD66684 SSB648A SS	12p 12p 12p 22p 23p A 22p 30p 30p 30p 30p 40p 38p 28p shown excl irr order (UI LAYCARD in or telephotails on app	2SK 16 J310 40823 3SK 45 3SK 66 3SK 86 BF96 BF96 BF96 BF96 Wde VA (), ACC 0 may b one ord plication	38 35p 69p 65p 65p 65p 5 49p 1 54p 0 58p 8 99p 380 75p 0 99p 3 99p VT. Postage 2ESS/ e used with ers - official n, and a a
CMOS 4077 0.18 4705 4.24 7447N 0.62 7415N 0.55 7415N		CONCISE PA	RTS CATALOG	78 78 78 79 79 79 10 10 10 10 10 10 10 10 10 10 10 10 10	H5A TO-3 12v p HG5A TO-3 adj HG5A TO-3 adj i M317.5A adj pos M337.5A adj neg S401.5A adj pos	os 5.45 pos 7.45 neg 7.45 1.30 1.75 sw reg 1.20	6.5536MHz 7MHz 8MHz 9MHz 10MHz 11MHz	2.00 2.00 2.00 2.00 2.00 2.00 2.00	ads car crystal buy - j attach	refully - a fi filter with ust clip out it to your -	every C t the par order. E	8MHz CPU IC you ragraph and E&OE.
	CIMOS 4000 0.13 4001 0.13 4002 0.13 4002 0.15 4008 0.70 4008 0.70 4008 0.80 4009 0.30 4010 0.30 4011 AC 0.24 4011 0.15 4011 AC 0.24 4011 0.15 4013 0.32 4015 0.64 4017 0.45 4016 0.30 4017 0.45 4016 0.30 4017 0.45 4020 0.58 4021 0.68 4022 0.64 4022 0.56 4022 0.50 4028 0.50 4028 0.50 4028 0.50 4028 0.50 4028 0.50 4028 0.50 4028 0.50 4035 0.15 4040 0.68 4042 0.58 4042 0.58 4042 0.58 4043 0.65 4043 0.65 4044 0.68 4044 0.68 4044 0.68 4044 0.68 4045 1.30 4055 1.30 4056 1.30 4055 1.30 4056 1.30 4056 1.30 4056 1.30 4056 1.30 4056 1.30 4056 1.30 4055 1.30 4056 1.30 4056 1.30 4056 1.30 4055 1.30 4056 1.30 4056 1.30 4055 1.30 4056 1.30 4055 1.30 4055 1.30 4055 1.30 4056 1.30 4055 1.30 4055 1.30 4055 1.30 4055 1.30 4055 1.30 4056 1.30 4056 1.30 4055 1.30 4056 1.30 4055 1.30 4056 1.30	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	4705 4.24 4706 4.50 4720 4.00 4723 0.95 4724 0.95 4725 2.24 40014 0.54 40085 0.99 40088 0.54 40161 0.69 40161 0.69 40162 0.69 40175 0.69 40192 0.75 40193 0.75 40193 0.69 40195 0.69 40194 0.69 40195 0.69 7401N 0.10 7402N 0.10 7403N 0.11 7404N 0.12 7406N 0.22 7407N 0.22 7407N 0.12 7406N 0.27 7411N 0.18 7412N 0.19 7413N 0.27 7414N 0.51 7409N 0.15	7447N 0.62 7447N 0.56 7450 0.14 7451N 0.14 7453N 0.14 7453N 0.14 7453N 0.14 7453N 0.28 7472N 0.28 7472N 0.28 7473N 0.28 7474N 0.28 7475N 0.30 7476N 0.30 7480N 0.26 7481N 0.20 7480N 0.75 7485N 0.75 7485N 0.75 7490N 0.30 7491N 0.55 7492N 0.35 7493N 0.40 7494N 0.55 7492N 0.35 7493N 1.00 7494N 0.40 74104 0.62 74105 0.60 74106 0.82 74110N 0.54 74120N 0.40 <	74153N 0.55 74154N 0.55 74154N 0.55 74154N 0.55 74155N 0.55 74155N 0.55 74157N 0.55 74157N 0.55 74161N 0.55 74161N 0.55 74163N 0.55 74163N 0.55 74164N 0.55 74164N 0.55 74166N 0.55 74166N 0.55 74166N 0.55 74166N 0.55 74170N 1.25 74170N 1.25 74170N 0.55 74170N 0.55 74190N	74366N 0.85 74367N 0.85 74368N 0.85 741500N 0.11 74L501N 0.11 74L502N 0.12 74L508N 0.14 74L508N 0.14 74L508N 0.14 74L508N 0.14 74L508N 0.14 74L508N 0.14 74L518N 0.13 74L52N 0.15 74L52N 0.16 74L532N <td>74L S109N 0.25 74L S112N 0.25 74L S112N 0.25 74L S12N 0.40 74L S12N 0.80 74L S13N 0.30 74L S13N 0.30 74L S151N 0.35 74L S153N 0.36 74L S155N 0.38 74L S155N 0.38 74L S155N 0.33 74L S164N 0.40 74L S164N 0.40</td> <td>74L S248N 74L S248N 74L S251N 74L S250N 74L S250N 74L S250N 74L S253N 74L S36N 74L S36N 74L S36N 74L S36N 74L S36N 74L S36N 74L S37N 74L S36N 74L S37N 74L S37N</td> <td>1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 2.05 1.50 1.15 1.199 1.105 1.255 1.105 1.255 1.105 1.159 1.125 1.250 1.25</td> <td>74CXX 74C00 74C02 74C04 74C08 74C10 74C14 74C20 74C32 74C42 74C42 74C42 74C48 74C73 74C74 74C76 74C85 74C86 74C89 74C90 74C90 74C151 74C151 74C151 74C157 74C161 74C157 74C161 74C165 74C163 74C165 74C164 74C173 74C164 74C165 74C164 74C165 74C165 74C160 74C165 74C164 74C165 74C174 74C165 74C166 74C195 74C195 74C195 74C195 74C195 74C290 74C290 74C906 74C906 74C906 74C906 74C906 74C907 74C906 74C907 74C910 74C910 74C910 74C910 74C910 74C927 81T G</td> <td> ↓ 0.20 0.48 0.98 0.26 0.80 0</td> <td>Processors B080 series B080AFC/2 311 B212 1.70 B214 350 B224 1.85 B255 3.97 6800/6809 68000 4.25 68000 4.25 68000 4.25 68000 4.25 68000 4.25 6800 4.25 6800 1.75 6801 0.204 6801 2.04 6802 1.95 6821 2.34 6801 2.04 6802 1.95 6821 2.34 6804 4.75 68840 4.75 68850 2.17 68850 2.17 68850 2.17 68850 2.275 68848 5.25 Z80 series Z80 series Z80 series Z80API 4.99 280ADRT 7.50 290API0 4.10 280ASI0.7 14.00 280ASI0.7 14.00 280ASI0.7 4.55 28001 65.00 PROM 2706 2.00 2716 3.55 2532 8.50 2732 8.50 285</td>	74L S109N 0.25 74L S112N 0.25 74L S112N 0.25 74L S12N 0.40 74L S12N 0.80 74L S13N 0.30 74L S13N 0.30 74L S151N 0.35 74L S153N 0.36 74L S155N 0.38 74L S155N 0.38 74L S155N 0.33 74L S164N 0.40 74L S164N 0.40	74L S248N 74L S248N 74L S251N 74L S250N 74L S250N 74L S250N 74L S253N 74L S36N 74L S36N 74L S36N 74L S36N 74L S36N 74L S36N 74L S37N 74L S36N 74L S37N 74L S37N	1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 1.35 2.05 1.50 1.15 1.199 1.105 1.255 1.105 1.255 1.105 1.159 1.125 1.250 1.25	74CXX 74C00 74C02 74C04 74C08 74C10 74C14 74C20 74C32 74C42 74C42 74C42 74C48 74C73 74C74 74C76 74C85 74C86 74C89 74C90 74C90 74C151 74C151 74C151 74C157 74C161 74C157 74C161 74C165 74C163 74C165 74C164 74C173 74C164 74C165 74C164 74C165 74C165 74C160 74C165 74C164 74C165 74C174 74C165 74C166 74C195 74C195 74C195 74C195 74C195 74C290 74C290 74C906 74C906 74C906 74C906 74C906 74C907 74C906 74C907 74C910 74C910 74C910 74C910 74C910 74C927 81T G	 ↓ 0.20 0.48 0.98 0.26 0.80 0	Processors B080 series B080AFC/2 311 B212 1.70 B214 350 B224 1.85 B255 3.97 6800/6809 68000 4.25 68000 4.25 68000 4.25 68000 4.25 68000 4.25 6800 4.25 6800 1.75 6801 0.204 6801 2.04 6802 1.95 6821 2.34 6801 2.04 6802 1.95 6821 2.34 6804 4.75 68840 4.75 68850 2.17 68850 2.17 68850 2.17 68850 2.275 68848 5.25 Z80 series Z80 series Z80 series Z80API 4.99 280ADRT 7.50 290API0 4.10 280ASI0.7 14.00 280ASI0.7 14.00 280ASI0.7 4.55 28001 65.00 PROM 2706 2.00 2716 3.55 2532 8.50 2732 8.50 285



★ UNIVERSAL RELAY DRIVER A project with 101 uses.																			18
* TV/FM MASTHEAD AMPLIFIER	•	•							•	•	•	•	•	•		•	•	•	26
Give your TV a boost where it helps.		•	•			•		•	•	•	•	•	•	•	•	•	•		42
Sound Switch	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		•		64

FEATURES

MAKIN' TRACKS All you need to know to make printed of \$ SCALING THE HIFI HEIGHTS	:ir	CI	ui	tŁ	00	aı	d	s								11
Part Two considers Arms and the Man											•	•				37
Meet Lee De Forest on page	•							•	•					,	. •	45
Part 7 introduces transistors	•	•					•	•		•	•	•	•	•	. •	46

SPECIALS

READER OFFER	
A Special kit to get started making PCBs at home	2
A GOOD JOINT IS HARD TO FIND	
A comprehensive special feature on soldering techniques 53	3

REGULARS

Monitor																		6
Your Letters																		. 23
Errata																		.23
Clever Dick .																		. 30
Bookshelf																		. 50
PCB Service																	•	. 63
Index to Adve	ər	ti	se	rs	5													. 65
Classified																		.66

Editor: Ron Keeley Editorial Assistants:Paul Coster BSc Tina Boylan Senior Art Editor: Andrew Sawyer Layout: Enzo Grando Advertisement Manager: Esmé Dansiger Managing Editor: Ron Harris BSc Managing Director: T.J. Connell







Hobby Electronics is normally published on the second Friday of the month prior to the cover date. Hobby Electronics, 145 Charing Cross Road, London WC2H OEE, 01 437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd, Distributed by Argus Press Sales & Distribution Ltd, 12-18 Paul St, London EC2A 4JS. Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore. Copyright: All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing of kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Argus Specialist Publications Ltd, cannot be held responsible for it legally. © Copyright 1981 Argus Specialist Publications Ltd Circulation. **Right first**

Portable VOM

If you've never built a kit before, Heathkit have some very pleasant surprises for you. Their kits are easy to build. Simple, but detailed

Rechargeable Light instructions take you through every stage. Everything is included. Even the solder you need is there.

Follow the steps and you'll end up with a hand-crafted, well designed piece of equipment. Much better than shop bought, massproduced. Because you built it yourself.

.



There's a great range of kits to start you off. From a buzzer alarm to a digital electronic clock, or a portable rechargeable

fluorescent light to a portable VOM. With all this going for you, you can count yourself very lucky you started off with Heathkit. Because all first time kit builders will get a free soldering iron and 10% discount off ten selected kits HEATHKE

Constants

10

Buzzer Alarm

To: Heath Electronics (UK) Limited, Dept (HE2), Bristol Road, Gloucester GL2 6EE.

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name

Address



E PROJECT KI

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to contruct H.E. projects. Kits include ALL the electronics and hardware needed. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original anticle, we even include nuts, screws and I.C. sockets, PRICES INCLUDE ASES unless otherwise stated. BATTERIES ARE NOT INCLUDED, COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p

DRUM SYNTHESIZER Dec 81. Full kit £21.17 GUITAR HEADPHONE AMPLIFIER Dec 81 £3.48 IN CAR CASSETTE POWER SUPPLY Dec 81 £4.46 Stereo £8.40 LED VU METER Nov 81 less case £4.56 SIMPLE STYLUS ORGAN Nov 81 less case £4.74 METRONOME Nov 81 £11.88 TELEPHONE BELL REPEATER Oct 81 £12.78 Med Linking wire extra 14p metre COMBINATION LOCK Oct 81 less solenoid £17.43 DOOR INTERCOM Oct 81 (less solenoid) £22 39 BABY ALARM Oct 81 £8.14, Fig 8 linking wire 7p metre TOUCH LAMP Oct 81. Bulb version £4.51, Mains version £7.16 'DIANA' METAL LOCATOR Sept 81 £33.85 C33.85 LOWER POWER PILOT LIGHT Sept 81, less case £1.30 LIGHT/WATER ALARM Sept 81 £5.98 CAR LIGHTS DELAY Sept 81 £5.99 POWER PACK Sept 81 £9.58 SHORT WAVE RADIO Sept 81 £23.98, EXTA: MONo headphones £2.98 REACTION TESTER GAME Sept 81 E11.99 THERMOMETER Aug 81 £12.98 R.P.M. METER Aug 81, inc. probe £15.48 VARIABLE BENCH POWER SUPPLY Aug 81 £25.35 ULTRASOUND BURGLAR ALARM July 81 £18.67 ELECTRONIC DOOR BUZZER July 81 E5.65 ELECTRONIC METRONOME July 81 E4.67 TREBLE BOOST July 81 £10.93 CONTINUITY CHECKER June 81 £5.34 ENVELOPE GENERATOR June 81 £16.85 AUDIO MIXER June 81 £4.99 VOICE OPERATED SWITCH May 81 £10.37, Microphone extra £1.41 SUPER SIREN April 81 £19.52 DOORBELL MONITOR April 81 £3.28 WINDSCREEN WASHED ALA PENA april £4.67 WINDSCREEN WASHER ALARM april 81 £5.78 81 £5.78 PUBLIC ADDRESS AMPLIFIER March 81 £18.21, Extras — horn speakers £6.83 each. PA MIC £4.40 each, PA MIC £4:40 FUZZBOX March 81 £10.35 WINDSCREEN WIPER CONTROLLER March 81 £7.67 STEAM LOCO WHISTLE March 81 £12.26 PHOTOGRAPHIC TIMER March 81 £3.28

HEARTBEAT MONITOR Feb 81 £23 40 HIGH IMPEDANCE VOLTMETER Feb 81 £9.87 AUDIO SIGNAL GENERATOR Feb 81 £18.93

TWO-TONE TRAIN HORN Feb 81 £5.24 MEDIUM WAVE RADIO Feb 81 67 67

LADDER OF LIGHT (Sound Into Light)

Jan 81 £29.98 BENCH AMP Jan 81 £10.10 NICARD CHARGER Jan 81 £7.67 CHUFFER Jan 81, less case £7.04 MODEL TRAIN CONTROLLER Dec 80 BATTERY CHARGE MONITOR Dec 80

£5.40 STEREO POWER METER Dec 80 £20.87

MEMORY BANK – MINI SYNTH-ESISER Nov & Dec 80 £26.61 PARTY GRENADE Nov 81 £8.77 TRANSISTOR TESTER Nov 81 £6.12 inc

test leads

Test leads DOUBLE DICE Nov 80 £15.18 GUITAR PRE-AMP Nov 80 £5.65 case (diecast) extra £2.99 NOBELL DOORBELL Oct 80 £11.98

INTRUDER ALARM Oct 80 £19.61 FREEZER ALARM Oct 80 with probe £10 36

TUG O'WAR Oct 80 £17.57 KITCHEN TIMER Oct 80 (2% resistors)

E7.98 MICROMIX Sept 80 £8.60 AUTO PROBE Sept 80 £3.99 less case TOUCH SWITCH Sept 80 £2.57 less case & contacts GUITAR PHASER Sept 80 £15.22

GUITAR PHASER Sept 80 £15.22 BENCH PSU Sept 80 £31.35 OP AMP CHECKER Aug 80 £4.99 MOVEMENT ALARM Aug 80 £6.24 PASS THE LOOP GAME Aug 80 £15.37 SOUND OPERATED FLASH TRIGGER July 80 no skt £4.99 FOG HORN June 80 £6.21 SPEED CONTROLLER FOR R/C April 80 £16.41 (lies case)

E16.41 (less case) DIGITAL FREQUENCY METER April 80 £39.35

ELECTRONIC IGNITION (CD) April 80

DIGI-DICE Jan 80 £10.97 BARGRAPH CAR VOLTMETER Dec 79

£7.98 less case RING MODULATOR Dec 79 £14.24 GUITAR TUNER Nov 79 £11.99

ANALOGUE FREQUENCY METER Oct 79 616 98

MULTI-OPTION SIREN Oct 79 £17.57 HOME SECURITY UNIT Aug 79 £31.41

less siren SIREN £5.59 less case SINEN E5.59 less case LED TACHOMETER Aug 79 £19.77 INJECTOR TRACER Aug 79 £4.77 LINEAR SCALE OHMMETER July 79 £17.57 GSR MONITOR June 79 £10.59 WHITE NOISE EFFECTS UNIT May 79 £19.51 CAR AL ADM Ech 70 £10.07

CAR ALARM Feb 79 (12 07

PUSH-BUTTON DICE Dec 78 £7.67

MEMORY BANK SYNTHESISER

Miniature synthesiser feat uring vibrato, envelope, tempo, volume + pitch controls. Uses 24 push button switches in a keyboard style layout. Based on a custom designed L.c. The accessible memory stores a 32 beat length sequence of notes + spaces. Can be played live'. Fitted with an internal speaker. Jack socket allows the use of an external amplifier if wished.

Memory Bank Synthesizer £26.61



I.C.s T001 S CASES RESISTORS TRANSISTORS KITS CAPACITORS

MAGENTA ELECTRONICS LTD.

$\begin{array}{cccccccccccccccccccccccccccccccccccc$	CMOS 20p LM386N 92p 4001 20p LM387 €1.10 4011 32p LM387 €1.10 4013 32p LM387 €1.10 4017 62p LM387 €1.10 4017 62p LM387 €1.98 4020 65p LM390 82p 4024 60p LM3814 £2.99 4026 20p LM3915 £3.95 4081 20p MC3340 £2.15 4093 38p NE570N £4.84 4522 £1.25 OM335 £8.85 555 25p SN6477 £2.59 556 79p TL064 £1.84 741 22p TL071 470 CA3130E 88p TL082 740 CA3138 £3.20 TL084 €1.52 MA1388 £3.20 TL084 €1.52
JW CARBON FILM RESISTORS E12 SERIES. 1R-10M MIN. HORIZ, PRESETS. 100R-4M7. 12p each MIDGET POTS. LINEAR. 470R-4M7. 12p each LOG. 4K7-2M3 SWITCHED POTS. 4K7-1M. LIN. 75p. LOG 76p POLYESTER. (C28) CAPACITORS, 250V 100F 10F 20F 30F 47E TO OVER 5455	ICM7555 99p UZ376 €1.69 LF351N 56p UZ378 €2.20 LF353N 99p ULN2283 €1.67 LF356 €1.14 2.4414 98p LF356 €1.15 2.4416 22p LM301A 36p 7400 22p LM317X £320 7447 €1.14 LM325 €1.16 2.4470 €1.64 LM317X £320 7447 €1.96 LM317A £320 7447 €1.96 LM317A £320 7447 €1.96 LM317A £320 7447 €1.96 LM317A £320 7447 €1.96 LM380N 89p 7496 56p
100nF \$p. 150nF; 220nF 12p. 330nF 15n, 470nF 20p. 683nF 28p. 1µF 33p. 1 5µF 49p. 2 2µF 65p. SUB MINIATURE PLATE CERAMICS, 63V Values in pF; 2 2; 3 3; 4 7; 5 6; 6 8; 8 2; 10; 15; 22; 33; 47 Å 55pF 7p each. 68pF; 100pF 7p each. 150pF; 220pF; 330pF 11p each. 330pF, 470pF 100pF 5p each. 2200pF 6p each. 3300pF, 4700pF 7p each. 10nF 13p. 100nF 22p. 41nF 14p.	OPTO BPX25 .22.24 2N5777 .50p ORP12 .99p TIL32 .51p TIL78 .74p LEDS WITH CLIPS .74p LEDS WITH CLIPS .3mm.Red 15p. Green 28p. Yellow 20p
ELECTROLYTIC CAPACITORS AXIAL Leads: $1\mu F/16V$ 11p; $1\mu F/63V$, $1\mu F/100V$ 12p; $22\mu F/63V$, $32\mu F/63V$, $4^{-1}\mu F/63V$ 12p; $10\mu F/$ 16V 11p; $10\mu F/25V$, $10\mu F/63V$ 12p; $22\mu F/63V$ 12p; $22\mu F/63V$ 15p; $32\mu F/63V$ 15p; $32\mu F/64V$ 12p; $4^{-1}\mu F/40V$ 15p; $47\mu F/63V$ 15p; $100\mu F/65V$ 12p; $220\mu F/10V$ 15p; $102\mu F/4VV$ 18p; $100\mu F/63V$ 22p; $220\mu F/10V$ 15p; $102\mu F/4VV$ 19p; $470\mu F/16V$ 28p; $220\mu F/10V$ 15p; $100\mu F/64V$ 19p; $470\mu F/16V$ 28p; $470\mu F/12V$ 36p; $100\mu F/16V$ 35p; $1002\mu F/16V$ 32p; $1003\mu F/10V$ 36p; $1000\mu F/16V$ 33p; $1000\mu F/12V$ 48p; $1003\mu F/10V$ 36p; $1000\mu F/16V$ 33p; $2200\mu F/10V$ 39p; $2200\mu F/25V$ 64p; $2200\mu F/33V$ 19p; $2200\mu F/10V$ 39p;	290. FLASHING LED
SWITCHES MIN. TOGGLE spet 59p; spdt 69p; dpdt 79p. MIN. PUSH ON. 13p. PUSH OFF. 22p. FOOTS WITCH & ALT. ACTION spco £1-39; dpco £1+8t. ROTARY SWITCHES. 1p 12 way, 2p 6w, 3p 4w, 4p 3w. 69p each 12V 185R DPCO RELAY £2 98	JACKSON £2:36 500pF dilecon £2:36 500pF dilecon £2:92 C804 Ver. Capac.; 10pF £2:28, 25pF £2:46. 50pF £2:48, 100pF £2:83, 150pF £3:48, '02'365pF, £4:49 '02' 208 + 176pF £3:98.
SPÉAKERS. Ministure. 8 ohm 87p MIN. E 64-75 ohm 83p 12V. 63 75 MAGE CRYSTAL EARPIECE 65p MAGE 70 MAGE MONO MEADPHONES £2.96 STERI 74. 74. PHONE PICK-UP COIL 72p F.M. A	UZZERS. 6V. 50p. 9V. £1 10. TIC EARPIECE
PANEL METERS. 60 - 45mm. 504A, 1004A, 1mA, VEROBOARD 61" COPPER. 10 Strips, 24 holes. 24S 37M. 74D. 24S 50M. 89p. 36S 37M. 89p. T 3RMINAL PINS PIN INSERTION TOOL £1-69 SPOT	LIPS 11p 1A. 25V £4-99 each 1A. 25V £1-20 per 5 36S 50H. 99p. 48p/100 FACE CUTTER £1-23
PCB ETCHING KIT £4 98 PLASTIC TWEEZERS 590 EUROBREADBOARD £6 20 JEWELLERS EYE BIMBOARD 1 £6 48 HAND MAGNIFIE 5. DEC £3 98 ILLUMINATED M VEROBLOC	ECTION MIRROR. £2.85 GLASS £1 50 R.3" £2.99 AGNIFIER. 1; £1.14.3". £3.19
MULTIMETER TYPE 1. 1,000 opv with probes MULTIMETER TYPE 2. 20,000 opv with transistor to CROC CLIP TEST LEAD SET. 10 leads with 20 clip CONNECTING WIRE PACK. 5 Syd colls RESISTOR COLOUR CODE CALCULATOR AM-IM sircraft band porable radio 21 tation desh intercom Plug in power supply, 4 5V, 6V, 5V, 300mW Dimmer switch PVC table - 3 reels	د دور دور دور دور دور دور دور دور دور دو

SOLDERING

ANTEX X5 SOLDERING IRON 25W £5-48 SOLDERING IRON STAND

£2.40 £2:40 SPARE BiTS. Small standard, large. 55 peach. For X5+X25. SOLDER. Hand, size 99p. HOW TO SOLDER LEAFLET 120

DESOLDER BRAID 690 HEAT SINK TWEEZERS 29p SOLDER CARTON £1-84 LOW COST CUTTERS £1-69 LOW COST LONG NO PLIERS £1-68 NOSE WIRE STRIPPERS & CUTTERS £2 -89



DRUM SYNTHESISER

PROPENDENCE STATE Projects Device States and See also H.E. Projects Dec 81 - another Drum Synthesiser

SOUND BENDER

From ETI Oct 81. A very effective 'Ring Modulator' sound effects unit. This design incorporates its own variable frequency oscillator with sine or traingular waveform, and a 4 quadrant multipler circuit. A mix control allows the modulated signal to be mixed with the straight through signal. Ideal for outer space, voice and music effects. Just connect a signal source and a power amplifier and seeaker.

ound Bender Kit £20.76, less case £15,78.

GUITAR NOTE EXPANDER

HAND CLAP SYNTHESISER

STRIFFESTIGATION OF THE STREET Hand (23.58

Reprints of the Above 45p each

BOOKS . BOOKS . BOOKS

SEMICONDUCTOR DATA BOOK - NewDes CE an
MICROPROCESSORS FOR HOBBYISTS - R. Coles
PRACTICAL ELECTRONIC PROJECT BUILDING Analie & Conwell
CONSTRUCTOR'S PROJECT BOOKS
ELECTRONIC GAME PROJECTS Rayer 53 36
ELECTRONIC PROJECTS FOR HOME SECURITY Bishop 63.35
ELECTRONIC PROJECTS IN AUDIO Penfold F3 35
ELECTRONIC PROJECTS IN MUSIC Flind
ELECTRONIC PROJECTS IN PHOTOGRAPHY Penfold. (3.36
ELECTRONIC PROJECTS IN THE CAR George
PROJECTS IN AMATEUR RADIO & SHORT WAVE LISTENING Rayer. E3.35
PROJECTS IN RADIO AND ELECTRONICS Sinclair
ELECTRONIC PROJECTS IN HOBBIES Rayer
ELECTRONIC PROJECTS I THE HOME Bishop
ELECTRONIC PRDJECTS IN THE WORKSHOP Penfold
ELECTNONIC TEST EQUIPMENT PROJECTS Ainslie
MORE ELECTHONIC PROJECTS IN THE HOME Flind. (3.35
ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR Marston
COST REFECTIVE PROJECTS - PAPERMAC
PROJECTS CARD THE HOME Watsen
AUDIO CIRCUITS AND BROUSSING A
TEST CEAR ON INCOME AND PROJECTS BISNOP
ELECTRONIC DRO MODEL BALLWARD ELECTRONIC CONTRACTOR ELECTRONIC
ELECTRONIC PROJECTS FOR MODEL RAILWAYS Babani
Solid State Short WAVE RECEIVERS FOR BEGINNERS Pentoid
ELECTRONIC AND CONTAINED AND CONTAINED AND A CONTAINED AND C
LC 55 DRO IE CTO BOL AND CREATIVE TAPE RECORDING Berry
EASIC ELECTRONICE DOOKS to £1.90
Super set of books covering theory and practice Educational Suite and Annual Annual (1)
circuite build a construct build on an E. Des burdhead
Sold as a set of 5 books Plag on
2 AND BE B BOL AL B BOOKS \$ 11 98

ADVENTURES WITH by Tom Duncan MICROELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering. Uses a Bimboard 1 breadboard, gives clear instruc-tions with lots of pictures. 11 projects based on integrated circuits —includes dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard 1 breadooard and all the components for the projects. Adventures with Microelectronics £2.55. Component pack £29.64 less battery.

ADVENTURES WITH ELECTRONICS by Tom

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2-40. Component pack £17-98 less battery

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification, We give personal service & quality products to all our customers—MAVE YOU TRIED US?

MAGENTA	ELECTA	RONICS	LTD.
DE14 257. 0283 65435. M	51., BURIU 10NFRI. 9-5	MAIL ORDER	STAFFS.
ADD 40p P. & P. TO ALL PRICES INCLUDE 15%	LL ORDERS.	OFFICIAL ORDERS	WELCOME

IRISH REPUBLIC & B.F.P.O. EUROPE: Deduct 10% from prices shown Payment, must be in Sturling. MUST be In Storling. ACCESS and BARCI AYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SAE ALL ENQUIRES.

MONITOR

Multitudes of Meters

Electronics enthusiasts are now able to get their hands on the Sanwa range of high quality multimeters through Toolmail Ltd's mail order service. Prices start at $\pounds 20$ for multimeters which feature a wide range of performance specifications.

Sanwa boasts the widest range of multimeters anywhere in the world, with many of its products regularly specified for use in industry and government in several countries.

For a full colour brochure and details of selected models, contact Toolmail Ltd, Parkwood Industrial Estate, Sutton Road, Maidstone, Kent ME15 9LZ Tel: Maidstone (0622) 672736. The catalogue also contains many useful tools of interest to the electronics hobbyist.





The Case of the In-Car Cassette

To make tape cassette storage easier, more organised — and therefore safer — Cambrasound Ltd offer the Tapemate, the incar tape holder.

Tapemate is made of impactresistant material and is easily attached to the dashboard, behind the visor, or to the door of the car by means of velcro and self-adhesive strips (supplied). Tapes stay secure in the holder thanks to a locking device which eliminates the problem of discovering your favourite tape on the floor, mutilated beyond recognition.

For details write to Cambrasound Ltd, Foreden House, 4/10 North Road, Islington, London N7 9HN or phone (01) 607 8141.

Holy Holography!

Light Fantastic, Britain's first gallery of holography, was opened by Sir Hugh Casson, President of the Royal Academy, on the 3rd December 1981. The inaugural display featured forty holographs (three dimensional images created by laser beams) which showed a cross-section of hologrophy from works of art to engineering and promotional holographs, as well as a display of 'laser writing' advertising.

The gallery is located at the centre of Covent Garden at No. 48 South Row (opposite Southampton Street), and features the most comprehensive exhibit of holography in Britain since the successful Light Fantastic exhibitions in 1977 and 1978.

Light Fantastic will be Britain's premier showcase of holography showing the best of holography in terms of technical achievement, creative interpretation and pure fascination.

The gallery is open to the public from 10 am to 8 pm each day (except Monday) with an entrance fee of £1 for adults and 60p for children. Holographs are on sale at the gallery (from £5 to \pounds 9001) along with a wide selection of literature on the subject of holography.

Modular Modes

ILP Electronics of Canterbury, designers and manufacturers of encapsulated audio modules, have announced the addition of four new stereo modules to their family.

The first of the new units is the HY74 stereo mixer, which offers sophisticated five-intoone mixing facilities on each of the two channels. Used in combination with an appropriate preamp and power amp, it is possible to create a quality mixer-amplifier at a reasonable price. The cost of the HY74 itself is £11.45 plus VAT.

An alternative is the new

HY75 stereo pre-amp with builtin mixer for two signals on each of two channels. The HY75 offers separate bass, mid range and treble controls and costs £10.75 plus VAT.

The other new modules are the HY76, a four-way stereo switch matrix, and the HY77, a combined VU meter drive/LED overload driver module with programmeable gain.

For the future, ILP are promising new products for the new legal CB market.

Contact ILP, Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP. Tel: (0227) 54778 for details.



New 'Scope

MONITOR

The Hitachi V-202 is a low cost dual trace oscilloscope with a full range bandwidth of 20 MHz. Both vertical channels have a maximum sensitivity of 1mV/ division, and variable controls allow intermediate sensitivity between attenuator steps.

The vertical deflection system provides sweep speeds up to 20 nsec/div with X10 magnification, a comprehensive triggering system with bright line auto mode and an active sync separator for video signals.

The 5¼ inch rectangular CRT has an internal (parallax free) graticule with variable scale illumination, and automatic focus compensation eliminates the need to reset the focus control when altering the brightness.

The cost is £260, plus VAT, from the distributor, Reltech Instruments, Coach Mews, St. Ives, Huntingdon, Cambs. PE17 4BN, Tel: (0480) 63570.

Robot Invasion (continued)...

Systems Control Company and Acorn Computers have designed and developed a small "army" of eight robots, for use in education, research, and light industry. Appropriately called'Smart-Arms', they are similar to a human arm, with a gripping hand, wrist, shoulder and elbow movements.

The 'baby' of the range is the 4E (Educational) model, which has elbow, shoulder rotation and grip movements and is suited for experimental projects; the more sophisticated 6E and 6ES, have a lifting capacity of 200g and a maximum reach of 300 mm. Top of the range are the 6R and 6I series; the 6R robot is designed for research use while the 6I is a lower-priced, industrial version.

The robots are completely programmable — the software is in BASIC. Time delays and jumps between points in a sequence of movements can be programmed, and complete sequences may be stored on cassette.

With prices starting at £430 (for the 4E), the Smart Arms will be of great interest to keen students of rototics. For all the details contact Systems Control 30 Thirsk Road, Northallerton, North Yorkshire, DL6 1PH, Tel: (0609) 70643, or Acorn Computers, Tel: Cambridge (0223) 245 200.

The perfect present for the

Soft Competition

Here's a contest for computer buffs who know the BASICs – Sinclair Research Ltd is sponsoring a special award scheme to help meet the need for more ZX81 educational software. The prizes are six ZX Printers, for the best programs accepted by the end of March 1982 for the Mini and Micro Computer Users in Secondary Education (MUSE) software library.

MUSE is a national organisation which co-ordinates educational computer activities in primary and secondary schools, teacher training institutions and colleges. MUSE and the Educational ZX80/81 Users Group (EZUG) will administer the scheme and, in collaboration with Sinclair, judge submissions in the categories at primary maths and science, other primary, secondary maths, science and computing, other secondary and special education.

Sinclair's sponsorship of this competition is the result of their interest in supporting, wherever possible, the development of educational software. The company has already sold ZX81s to more than 2300 secondary schools under its subsidised purchase scheme.

Entries or inquiries should be sent to Eric Deeson, EZUG Organiser, Highgate School, Birmingham B12 9DS. Closing date is February 27th, so you'll have to be quick!

On the Groove

Seeing is believing, so they say . . . and pictures don't lie, but if you can't believe your eyes, you'll have to trust your ears when you hear the Record Runner motoring across your favourite album. Yes, it does look like a micro Volkswagen Minibus, but it contains a speaker built into the roof and a stylus where the exhaust should be ... and it plays records without the help of any stereo equipment whatsoever. Just place it on the vinyl and the Record Runner will motor around the disc, making music as it does.

man who has everything else? See it and believe it, at The Video Palace, 62/64 Kensington High Street, W8.

MONITOR

Spare Hands

Serious HE project builders will be familiar with the traditional problem of the Third Hand: how to hold a printed circuit board, a sensitive component, a heat sinking clamp, solder and the soldering iron with only the regulation two hands. This outstanding problem for the electronic constructor has been solved by a British manufacturer, Carlton Nichol & Co. Ltd. who have released two new printed circuit board holders. Both models are made from aluminium and plated steel, and allow easy rotation through 360 degrees with positive locking at any angle. The boards are firmly held in any convenient position, leaving both hands free

The CNC 6 will take boards of up to $10^{\prime\prime} \times 7^{\prime\prime}$, held in position by spring-loaded clamps, while the larger CNC 9 will hold boards as big as $8^{\prime\prime} \times 8^{\prime\prime}$ in sliding vee clamps which minimise damage to the surfaces but allow maximum ease of access.

An optional anti-static foam pad allows the insertion of a number of sensitive components before the board is flipped for



soldering. The pad is on a backing plate and clips onto the rotating arms of the PCB holder. The listed prices including VAT, of these handy holders are £13.80 for the CNC 6, £15.95 for the CNC 9, and the pad is £9.20 — but just think of the savings on burn ointment, and the goodwill you will gain when it is no longer necessary to ask someone to "... just hold this a moment, please ..." as you wave a hot iron within millimetres of their trembling fingers! The PCB holders are available direct from the manufacturers — Carlton Nichol & Co. Ltd., Goldkey Industrial Estate, Kelvedon, Essex.

Disabled Aid

Undergraduate apprentices at British Aerospace Dynamics Group, Bristol Division, have built a robot arm and a tone operated telephone in a training exercise. Both, with further development, could be used by the disabled.

The arm is electro-mechanical, lifts up to half a kilogramme, can be programmed to repeat simple functions, move in three dimensions, and rotate through 360 degrees.

The tone operated telephone is remotely controlled by three separate whistles which can be positioned away from the telephone. The whistle tones enable the desired number to be obtained, displayed and electronically fed into the telephone. A directional microphone enables the telephone to be answered from a distance.

These projects were the result of the collaboration of seven apprentices who were given abudget of £200 for each project and a set of specifications.

For further information contact T. C. Bickerton, Public Relations Manager, British Aerospace Dynamics Group, Bristol Division, PO Box 5, Filton Bristol BS12 7QW. Tel: Bristol 693831.

Jogging Time

Jogging may be hazardous to your health yet, despite this, masochists everywhere persist in pounding the path, risking shin splints, pulled muscles, ankleeating dogs and asthma, in their quest for fitness.

Riding high on the myths ofprosperity through pacing, new products are constantly creeping into the market; now Casio Electronics has made the running with one of their multimode watches.

mode watches. The model J100 features what Casio calls "a novel 'pacer' mode," designed to help runners get the most from their tortuous activity. Before donning jogging togs, you simply feed the watch information about your length of stride and preferred running rate. The stride length is set digitally and is measured in either feet and inches or in meters. Running rate is expressed by audible pips on an adjustable 69-step scale, and is also shown on the display.

Provided a jogger keeps pace with the pips and holds the set stride length, the watch will show target speed, elapsed time, distance traveled, and the number of strides made. Of course the J100 gives the time, day and date, and also includes a 1/100th second stopwatch and an eight-digit, four-function calculator, a daily alarm, and an hourly time signal. Whew! Does anyone make watches that simply tell time?

Joggers can huff and puff down to the shop and pick up this new watch for £22.95, although Cesio products are often available below this recommended price. For more information contact Casio, 28 Scrutton St, London, EC2A 4TY, Tel: 01-377 9087. But don't say you heven't been warned!

And Now for Something Similar . . .

The new model 3T from Centemp is a battery opereted, hand held, 3¼ digit liquid crystal display digitel multimeterwith push-button control over six functions in 16 ranges. It measures DC voltege, AC voltage, DC current, resistance, Diode/continuous check and also has a transistor gain measurement facility.

The model 3T can be yours for £43.50 plus VAT.

Contect Centemp, 62 Curtis Road, Whitton, Hounslow, Middx. TW4 5PT. Tel: 01-894 2723.



WATFORD ELE 35 CARDIFF ROAD, WATFOR MAIL ORDER. CALLERS WELCO	CTRON D, HERTS., EN ME. Tel. Worth	NICS	7400 TTL 7400 11 7401 11 7402 11 7403 14 7403 14 7405 18	74126 4 74128 4 74132 4 74136 3 74141 7 74142 19 74143 25 74145 25	LS48 80 LS55 30 LS63 150 LS73 25 LS74 25 LS75 26 LS75 26 LS76 20 LS76 20	4015 66 4016 32 4017 48 4018 68 4019 42 4020 61 4021 70	4412 800 4415 480 4419 280 4422 770 4433 770 4435 850 4440 999	LF351 48 LF355 75 LF356 90 LM300H 170 LM301A 26 LM308 95
ALL DEVICES BRAND NEW, FULL SPEC. AND F PATCHED BY RETURN OF POST. TERMS P.O. OR BANKERS DRAFT WITH ORDER. GOVEF TUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE P&P ADD 50p TO ALL ORDERS UNDER £10 NET COST. AIR/SURFACE. ACCESS ORDERS WELCON VAT	ILLY GUARANTEE OF BUSINESS: NMENT AND EDUC AND EXPORT INCI OVERSEAS ORDER E. AT to the total coat Incl.	D. ORDERS DES CASH/CHEQUE/ CATIONAL INSTI- UIRY WELCOME. RS POSTAGE AT POP.	7406 20 7407 20 7409 16 7409 16 7410 14 7411 20 7413 24 7416 25 7420 16 7420 16 7420 16 7423 20 7420 16 7423 20 7423 20	/4145 7 74145 7 74148 7 74150 8 74151 4 74153 4 74154 7 74155 4 74156 7 74157 4 74156 7 74157 9 74160 6 74161 6 74162 6 74163 6	1 LS83 50 1 LS85 70 5 LS86 36 1 LS90 35 5 LS92 36 5 LS95 45 5 LS96 120 6 LS107 43 7 LS113 40 1 LS113 40 1 LS113 56 4 LS122 44 LS123 55	4022 66 4023 20 4024 45 4025 19 4025 130 4027 38 4028 58 4029 77 4030 50 4031 170 4032 125 4033 165 4033 165 4035 95 4035 97	4450 350 4451 350 4390 350 4500 675 4502 90 4503 50 4504 105 4505 50 4506 85 4507 40 4508 265 4510 68 4511 68 4512 75	Lm318 200 LM324 45 LM339 66 LM339 65 LM349 11 LM349 11 LM349 11 LM358 75 LM381 145 LM381 215 LM384 99 LM387 120 LM387 120 LM387 120
POLYESTER CAPACITORS: Axial Lood Type 400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 18n, 22n 1 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 64p; 2µ2 82p; 4µ7 9 160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 420n 30p; 1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 4	p; 33n, 47n, 68n 18p; 1) p. 580n, 38p; 1µF 42p; 1µ 8p; 100n 50p; 470n 99p	100n, 150n 20 p; 220n 5 45 p; 2µ2 48p . 9	7425 28 7426 30 7427 27 7428 28 7430 16 7432 26	74165 6 74166 6 74167 18 74170 16 74172 29 74173 6	Z LS124 105 5 LS125 30 5 LS126 30 8 LS132 45 0 LS133 35 4 LS136 20	4037 115 4038 110 4039 290 4040 59 4041 78 4042 60	ICs 2114L-3 88 2706 195 2716 210 4116 86 6502 450	LM3900 60 LM3909N 70 LM3911 125 LM3914 220 LM3915 220 LM3916 240
POLYESTER RADIAL LEAD CAPACITORS: 250V: 10-F, 15-n, 22-n, 27-n 6p; 33-n, 47-n, 58-n, 100-n 7p; 150-n, 22 330-n, 470-n 13-p; 680-n 13p; 1// F.23p; 1// 5.40p; 2// 2.46p; 4/ ELECTROLYTIC CAPACITORS: (Values are in µ/F) 500V: 10 1.5, 2.2, 2.5, 3.3 8p; 4.7 9p; 6.8, 10 10p; 15, 22, 12p; 33 15p; 20p; 20 24p; 470 32p; 220 30p; 40V: 4.7, 15, 22 9p; 33002 5p; 47.6p; 130-11p; 150 12p; 220. 15p; 330 22p; 470 25p;	10p. 10p. 10p. 20p. 47 78p; 250V: 100 10p. 4700, 120p; 25V: 100 10p. 4700, 120p; 25V: 1 100, 34p; 2200, 5	HC TRANSDUCER6 /pr 0 65p; 83V: 0.47, 1.0, 70p, 50V: 47 12p; 68 1.5, 6.8, 10, 22 8p; 33 0p; 3300, 78p; 4700	7433 27 7437 27 7438 27 7440 17 7441 68 7442 39 7443 90 7444 90 7445 65	74174 7. 74175 7. 74176 55 74177 7. 74178 99 74180 66 74181 144 74182 7. 74184 97	2 LS138 35 2 LS139 38 5 LS145 75 5 LS147 199 5 LS147 99 5 LS147 99 5 LS151 39 0 LS153 39 5 LS155 39 6 LS155 39 6 LS157 35 5 LS156 35 5 LS157 35 5 LS1	4043 70 4044 65 4045 170 4046 75 4047 75 4048 55 4048 55 4049 30 4050 30 4051 78	6522 350 6800 375 709C 8 pin 35 710 48 733 100 741 8 pin 14 747C 76 749C 36 753 150	LS7220 280 M252 625 M253AA 1150 MC1304P 260 MC1310 150 MC1455 150 MC1458 45 MC1488 62 MC1489 62
32p; 18V: 40, 47, 100 9p; 125, 12p; 220 13p; 470, 20p; 680 74p; 7400 73p; TAG: END TYPE: 70V: 4700, 245p; 64V: 3300 198p; 2200 13 160p; 25V: 10,000 320p; 15,000 244p; TANTALUM BEAD CAPACITORS 3VV: 0.1µF, 0.22, 0.33 15p; 0.47, 0.68 10µF, 15, 15p; 22, 33 15p; 47, 68 22p; 10µF 26p; 18V; 2.2, 33 16p; 4/µF, 6.8. 10 18p; 15, 38p; 22 30p; 33, 47 35p; 100 55p; eV: 100 42p; 5%Q: 2%p; 33, 47 35p; 100 55p; eV: 100 42p;	34p; 1000 27p; 1500, 3 hp; 50V: 3300 154p; 22 18: Rotary, Carbon, 0 5W Lin (Linear only) Single 28p ng 27p 28p ng 27p 88p 88p	31p; 2200 36p; 3300 200 110p; 40V: 4700 OPTO ELECTRONICS LEDs with Clips TIL209 Red 13 TIL211 Grn. 18 TIL212 Yel. 19 Z" Red 14	7446 55 7447 50 7448 50 7450 16 7451 16 7453 16 7453 16 7453 16 7454 16 7460 16 7470 35 7472 30 7473 30 7474 25	74188 99 74188 29 74190 7/ 74191 7/ 74192 7/ 74193 6/ 74195 6/ 74195 6/ 74196 6/ 74196 9/ 74197 6/ 74198 9/ 74221 8/	LS186 36 LS160 41 LS161 41 LS162 41 LS163 41 LS165 44 LS165 48 LS166 85 LS166 85 LS173 72 LS173 58 LS173 58 LS173 58	4052 70 4053 70 4054 125 4055 125 4056 120 4057 1915 4059 480 4061 1225 4062 995 4066 36 4067 399	810 159 81L596 90 81L596 90 81L597 90 9400C.J 350 AY-1-1313A 660 AY-1-1320 225 AY-1-5051 160 AY-3-8500 390 AY-3-8500 390 AY-3-8510 720 AY-3-8910 720	MC1494 894 MC1495 350 MC1496 92 MC1648 230 MC1710 79 MC3302 160 MC3340P 120 MC3401 52 MC3401 52 MC3403 110 MFC6040 9
MINIA CLAR FLIM CLARACTIONS SLIDER POTENTI 100Y: 1nF, 2. 4, 4n7, 10 8p; 15nF, 203, 30n, 40, 47 7p; 56 100n, 200 9p; 370n/50V 12p. SLIDER POTENTI 470n/50V 12p. MINIATURE TYPE TRIMMERS 24pF, 2-10nF, 2-25pF, 556F 30p. PRESET POTENT COMPRESSON TRIMMERS 3-40pF, 10-80pF 20p; 20 250pF 24p; 00-5500 1-33 200 580pF 24p; 20 250pF 24p; 00-5500 1-33 0-25W 100-33	METERS ar values 60mm gang 70p jang 110p id Bezel 40p DMETERS kniature 7p 40 horu. 10p	.2" Yell or Grn 18 Square LEDs 29 ORP12 86 2N5777 45 LD271 46 SFH205 98 TIL32 52 TIL78 54 YIL78 54 YIL38 65 YIL100 50 7 Segment Displays	7476 30 7480 48 7481 120 7482 70 7483 50 7485 95 7486 26 7486 26 7489 205	74247 154 74248 154 74LS00 12 LS01 13 LS02 14 LS03 14 LS04 19 LS05 19	LS191 58 LS192 58 LS193 65 LS195 40 LS196 58 LS197 85 LS221 60 LS240 96 LS241 96 LS242 85 LS243 85	4068 22 4069 20 4070 26 4071 20 4073 20 4075 20 4076 60 4077 26 4078 26 4078 26	236 AY-5-1230 450 (CA3011 110) CA3018 68 CA3020 186 CA3023 191 CA3028A 120 CA3035 235 CA3045 365 CA3045 214	MK50398 635 MK503 635 NM5307 1275 NE529 225 NE543 210 NE544 185 NE556 16 NE556 55 NE560 325 NE561 398 NE562 410
POLYSTYNENE CAPACITORS: RESISTORS 10pf to 1nf 8p; 1.5nf to 10nf 10p RSISTORS SLVER MICA (Values in pF) 2, 3.3, 47 Toferance 5%. 6.8, 8.2, 10, 15, 18, 22, 72, 3.3, 94, 7 Toferance 5%. 180pf 15p ech; RANGE 200, 220, 250, 270, 300, 330, 360, 390, 470, 600, 800 210 peach Toferance 5%. 3300, 4700p ech; Toferance 5%.	arbon Film High loise. Miniature VAL 1-99 100+ E24 2p 1p E12 2p 1p E12 2p 4p 1M 6p 4p 1M 6p 6p 1M 6p 6p	TIL321.5 CA 115 TIL322.5 CC 115 DL704.3 CCth 99 J.Green CA 120 DL747.6 CA 180 FND357 120 MAN3640 175 10 Seg Bargraph LCD 3 ¹ /2 Digits 550	7.492 30 7.493 30 7.493 30 7.495 50 7.496 45 7.496 45 7.4100 85 7.4107 32 7.4109 35 7.4109 35	LS08 19 LS09 19 LS10 19 LS11 19 LS12 10 LS12 10 LS14 42 LS15 19 LS20 19 LS21 19 LS22 19 LS22 19 LS22 19	LS244 80 LS245 118 LS247 400 LS248 65 LS249 68 LS251 40 LS253 40 LS257 48 CMOS 4000 14 4001 14	4082 21 4082 21 4085 65 4086 70 4089 140 4093 43 4095 90 4097 320 4098 88 4099 95 4096 95	CA3059 196 CA3075 213 CA3080E 65 CA3080E 190 LA3085 95 CA30896 215 CA30890AQ 375 CA3122E 150 CA3123E 150 CA3130 90 CA3140 48 CA3189 295	NE564 420 NE566 120 NE566 150 NE571 150 NE571 420 RC4136 69 S566B 245 SAB3210 275 SAB3210 275 SAB3271 455 SAB3271 455
CERAMIC CAPACITORS BOY: 0-5pf Value not image to 10nF 4p: 22n to 47n 5p. 100n 7p. Gas and Sm TGS 812 VOLTAGE REGULATORS Ta T03 1A T03 VP 5V 7805 145p 12V 7812 145p 15V 7815 145p 18V 7815 145p	A Batectors ad B13 575p stock most of the s for the Projects in this magazine ACCESS	TOGGLE: 2A 250V- SPST 33 OPDT 44 4 Pole on / off 54 SUB-MIN TOGGLE SP changeover 60 SPST on / off 54 DPDT 6 dags 75 DPDT cf 76	74111 55 74112 170 74116 88 74118 80 74119 90 74120 75 74121 30 74122 45 74123 50 74125 42	LS27 15 LS28 20 LS30 16 LS32 15 LS33 16 LS37 16 LS36 16 LS40 16 LS40 16 LS42 35 LS47 40	4002 14 4006 66 4007 18 4008 62 4009 35 4010 40 4011 15 4012 18 4013 34 4014 75	4161 99 4162 99 4163 99 4174 99 4175 105 4194 105 4408 790 4400 790 4410 725 4411 695	ICL0703 975 ICL0038CC 340 ICM7205 1150 ICM7216A 1950 ICM7217A 790 ICM7555 80 ICM7555 80 ICM75555 80 ICM75555 80 ICM755555	TAA621 250 TAA205A 225 TAD100 159 TBA120 70 TBA641 275 TBA800 80 IBA810 95 TBA820 70 TCA365 120 TDA1004 230
1A TO 200 Plastic Casing 500 55p 100	phone your order gh. Wo deal with set (but min. £10 please). TCHES Minister Non-L to Make 15 KERA SPST on / off 10A KERA SPST on / off 10A KER	DPDT Briesed 145 BLIDE 250Y: 1A DPOT 14 1A DP c/off 15 9A OPDT 13 Locking Push Break 20 /250V 26home bezel, lights 85 STOPJ 1 pole/2-12 av, 4p/2-3 wey 45 4 Amp 52	AC125 36 AC126/7 35 AC128 30 AC116/87 30 AC111/2 30 AC1176/87 30 AC1176/87 30 AC197/87 30 AC198 30 AC197/718 70 AC192 60 AD140 120 AD140 120 AD149 79 AD161/2 42 AF115 60	BC477 BC516/7 BC547/8 BC556/7 BC556/7 BC556/9 BCY70 BCY71 BCY71 BCY71 BCY72 BD133 BD135 BD136/7	E421 MJ2955 40 MJE340 MJE370 14 MJE370 14 MJE371 15 MJE2955 15 MJE2955 15 MJE3055 16 MPF102 18 MPF103 0 MPF104 48 MPF106 60 MPF106 40 MPSA05/0	250 TIS44 54 TIS90 100 TIS91 100 TIS91 100 VK1010 95 VN10KM 99 VN46AF 64 VN86AF 64 VN86AF 65 ZTX107/8 65 ZTX107/8 66 ZTX301/2 25 ZTX301/2 25 ZTX303	45 2N3252 4 50 2N3563 21 32 2N3568 21 32 2N3563 21 32 2N3563 12 32 2N3702/3 11 45 2N3702/3 11 45 2N3706/7 11 78 2N3706/7 11 94 2N3706/7 11 11 2N3713 14 12 2N3771 17 13 2N3771 27 14 2N3773 27 15 2N3819 27 15 2N3819 27 15 2N3819 27 17 2N38	TDA1000 375 TDA1022 575 TDA1024 105 TDA1024 102 TDA1024 102 TDA1024 102 TDA1024 102 TL061 40 TL061 40 TL061 90 TL074 100 TL081 26 TL081 26 TL083 75 TL084 95 TL084 95 UAA1/0 170
LM 300H 170p LM325N 240p T8A5258 75p DIL LM305H 140p LM325N 240p T8A5258 75p DIL LM305N 135p LM327 270p 78H05 560p Pp JACKSONS VARIABLE CAPACITORS DIODES Dielectric 0.2 365p with slow 8v126 500p 220p motion Drive 495p 8v127 270b 78H05 560p Di 106/300-F 220p motion Drive 495p 8v127 300/47 30/47	SOCKETS: 8-pin 8p; 18-pin 16p; 20-pin 2; 8p; 40-pin 30p. 12 12 12 12 12 12 12 12 12 12	14-pin 10p; 16-pin 2p; 24-pin 25p; 28- SCRs Thyristors 1A400V 50 5A7400V 40 5A7400V 40 5A760V 45 8A300V 65 12A7400V 95	AF139 400 AF178 75 AF180/6 70 AF239 78 BC107/8 10 BC1081 12 BC109 10 BC1091 12 BC1092 12 BC1193 12 BC119 38 BC137 40 BC147/8 30 BC140/3 30 BC1447/8 9 BC149 9	BD138/9 BD140 BD695A BD695A BDY69 BDY60 BDY61 BF115 BF115 BF173 BF177 BF178 BF179 BF178 BF179 BF194/5 BF196/7	40 MPSA55 40 MPSA56 85 MPSU06 85 MPSU06 85 MPSU06 86 OC35 86 OC35 86 OC35 90 C44 27 OC45/70 25 OC71/2 30 OC44 30 OC76 35 OC81/2 38 OC83/4 12 OC170/1 12 TIP29	30 21X314 30 21X316 5 2TX326 5 2TX341 60 2TX500 10 2TX501/2 120 2TX504 120 2TX504 120 2TX504 120 2TX550 40 2N696 50 2N697 50 2N698 40 2N6998 40 2N6998 41 2N918	25 21382/3 6 21382/3 6 213866 213903/4 1 15 213903/4 1 15 213903/4 1 15 213903/4 1 15 213903/6 1 18 214037 5 21406/3 2 18 21406/3 2 18 21406/3 2 21406/3 2 2	xR2206 300 xR2211 -575 zB0ACPU 395 zB0ACPC 320 zB0ACPC 320 zB0ACPC 320 zB0ACPC 320 zB0ACPC 320 zB0CPC 300 zB0ACPC 326 zB0ACPC
DENCO COILS RFC 5 chokes OA95 DENCO COILS RFC 5 chokes OA95 DF VALVE TYPE 140p IN916 Range 1 to 5 BL. RFC 7 (19mH) IN916 RD, 11 Wht. 122p 160p IN4001/2 7 B-Y-R 110p 13; 14; 15; 16; 17 IN4001/2 15 Green 150p 18/1.6 125p PSA Valwe Holder TOC1 124p IN4006/7 RDT2 145p MW/LWSFR 154p IN4006/7 VEROBOARD COPPER IN4006 IN4006/7 Q1 = 11ch 13p 15/16 IN4006/7 29h 3/h 73p<52p	Bridge 15 BRIDGE RECTIFIEF (plastic case) 14/50V 14/50V 14/50V 14/400V 122/400V 122/400V 122/400V 122/400V 64/400V 64/400V 1004/200V 1004/200V 25 1004/200V	12A/800V 188 BT106 BT106 BT106 C106D 1111 1111 1111 1111 1111 1111 1111 1111 1111 <	BC153/4 27 BC157/8 10 BC157/8 10 BC157/8 10 BC157/8 10 BC1650 15 BC167/1 15 BC179 20 BC183/L 10 BC183/L 10 BC184 10 BC184 10 BC187 26 BC212 10 BC213 10	BF198 BF200 BF224A BF256 BF256 BF259 BF534/5 BFR39/40 BFR47/8 BFX81 BFX81 BFX84 BFX87/8 BFX87/8 BFX87/8 BFX87/8 BFX52 BFX52 BFX52 BFX39	16 TIP29C 0 TIP30 25 TIP30A 25 TIP30C 35 TIP31A 35 TIP31A 35 TIP32A 0 TIP32C 23 TIP33C 25 TIP34A 25 TIP34C 26 TIP35C 28 TIP36C 23 TIP36C 23 TIP44A 24 TIP42A 20 TIP42A 20 TIP42A	60 2005 84 2005 85 201305 85 201305 85 201305 85 201305 86 2015 86 2015 86 2015 87 205 87 20	20 20/5305 2 20 20/5305 2 64 20/5457/8 3 65 20/5459 3 66 20/5459 3 65 20/5459 3 65 20/5477 4 62 20/5477 4 62 20/5477 4 62 20/5477 4 62 20/5477 4 62 20/5477 4 62 20/5477 4 62 25/5477 4 62 25/5477 4 62 25/5477 4 62 25/5477 4 63 25/5477 12 7 25 25/5476 12 7 25 25/5477 12 8 25/5477 12 12 10 25/5477 12 12 25/5477 25/5477 25/5477 25/5477	ZN1040E 775 5 3N140 112 5 40313 130 2 40313 130 2 40313 130 0 40324 100 5 40327 70 4 40348 120 5 40327 70 4 40348 120 5 40327 50 4 40348 120 5 40327 50 4 40348 120 5 40361/2 50 5 40361/2 50 5 40407 50 4 40407 50 6 40407 50 5 5 5 40407 50 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5 5
3% = 5 95p 79p 6×12" 150p 3% = 71 326p 211p S R B P We stoc 4% = 17 426p 9 8 95p wide sete 5pot face currer 118p Ferric Chloride 05 ks ar Negazine Pin insertion tool 182p Ferric Chloride Magazine	254/200V 2 254/600V 3 BY164 VM18 DIAC ST2	12A000V 82 12A800V 136 56 16A100V 16A500V 115 25A800V 20 25A1000V 25 28 7280000 120 120	BC214 10 BC214L 10 BC307B 14 BC328 96 BC338 15 BC441 34 BC461 34	BSY65 BSY95A BU105 BU205 BU208 E113 E176	35 TIP120 25 TIP121/2 70 TIP142 90 TIP147 00 TIP2955 45 TIP3055 50 TIS43	90 2N2926G 99 2N3053 120 2N3054 120 2N3055 60 2N3121 60 2N3133 32 2N3135	25C2028 8 10 25C2029 18 26 25C2078 15 58 25C2091 8 30 25C2166 16 45 25C2167 19 30 3N128 11	0 40467 1.40 0 40468 B5 5 40594 105 5 40595 110 .5 40603 110 .5 40673 95 2 2 5

Rapid	Tel: 0322 863494 Hillcroft House Station Road Eynsford, Kent DA4 0EJ
7413 24 7442 40 7480 45 74107 30 74155 60 74177 75 7400 11 7414 35 7444 85 7482 70 74107 32 74156 60 74177 75 7400 11 7416 25 7446 60 7483 60 74121 28 74156 60 74179 65 7401 11 7417 26 7447 48 7483 50 74121 24 5 74160 60 74181 135 7402 12 240 15 7448 50 7486 25 74124 45 74166 60 74181 70 7403 14 7421 20 7450 16 7489 28 74126 40 74184 60 74182 70 7404 17 7423 14 7423 40 74184 6	VERO Size 0.1 matrix 2,5 x 1" 25p perienced constructor to obtain a wide range of components at reduced prices. 37p WW 65s Resistor Kit. Contains 10 of each value from 4.7Ω to 1M 480p (650 resistors) 480p Cepsein Capacitor Kit. Contains 5 of each value from 22p to 0.01 370p (135 caps.) 370p Polyester Capacitor Kit. Contains 5 of each value from 100Ω to 1M 576p each Preset Kit. Contains 5 of each hor. value from 100Ω to 1M CABLES CABLES 425p
LSTTL LS20 15 LS75 27 LS12 42 LS18 36 LS196 60 LS23 45 LS00 13 LS21 15 LS76 20 LS123 55 LS160 42 LS196 60 LS283 45 LS00 13 LS26 18 LS76 20 LS125 30 LS161 42 LS217 60 LS366 38 LS01 14 LS27 15 LS36 50 LS132 45 LS163 42 LS241 80 LS367 38 LS01 14 LS27 16 LS86 20 LS132 45 LS164 50 LS243 85 LS378 80 LS378 80 LS374 80 LS377 80 LS374 80 LS374 80 LS374 80 LS375 60 LS374 80 LS377 90 LS06 16 LS42 38 LS161 <th>Nut and Boit Kit. Total 300 items. 140p 25 6BA %" bolts 25 4BA %" bolts 26 6BA washers 50 4BA washers 50 6BA nuts 50 4BA nuts TRANSFORMERS 100p each Miniature mains. 65p/m 2064, 0-5V @ 10, 5A; 0-9, 0-9V @ 0, 4A; 0-12, 0-12V @ 220p aech 0.3A 220p aech 12VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 0, 1-2A; 0-12V @ 0.5A 24VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 0, 1-2A; 0-12V @ 0, 5A; 50-4 6 x 35mm. 24VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 1-2A; 0-12V @ 15A 50-4 6 x 35mm. 24VA 0-15, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-20, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-15, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-15, 0-15V @ 0, 0-4A 320p each 250 bach 320 bach (plus 60p carriage]. 24VA 0-15, 0-15V @ 0.8A 330p each (plus 60p carriage]. 24VA 0-15, 0-15V @ 0.6A 330p each (plus 60p carriage]. 24VA 0-15, 0-</th>	Nut and Boit Kit. Total 300 items. 140p 25 6BA %" bolts 25 4BA %" bolts 26 6BA washers 50 4BA washers 50 6BA nuts 50 4BA nuts TRANSFORMERS 100p each Miniature mains. 65p/m 2064, 0-5V @ 10, 5A; 0-9, 0-9V @ 0, 4A; 0-12, 0-12V @ 220p aech 0.3A 220p aech 12VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 0, 1-2A; 0-12V @ 0.5A 24VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 0, 1-2A; 0-12V @ 0, 5A; 50-4 6 x 35mm. 24VA 0-6, 0-6V @ 1-5A; 0-9, 0-9V @ 1-2A; 0-12V @ 15A 50-4 6 x 35mm. 24VA 0-15, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-20, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-15, 0-15V @ 0.8A 330p each [plus 60p carriage]. 24VA 0-15, 0-15V @ 0, 0-4A 320p each 250 bach 320 bach (plus 60p carriage]. 24VA 0-15, 0-15V @ 0.8A 330p each (plus 60p carriage]. 24VA 0-15, 0-15V @ 0.6A 330p each (plus 60p carriage]. 24VA 0-15, 0-
CMOS *4017 43 4036 286 4055 115 4082 20 4502 70 4523 150 4000 14 4019 35 4040 55 4066 65 4603 50 4503 50 4532 95 4000 12 *4019 35 4040 55 4060 65 4607 38 4534 495 *4001 12 *4020 56 4041 75 4068 90 4608 65 4607 38 4538 110 4002 14 4021 65 4042 55 4066 35 *4093 33 4510 65 4543 110 4005 68 4024 40 4068 15 4096 18 4097 30 4511 150 4554 450 4006 70 4068 18 4097 30 4516 76 455 455 </th <th>Diopy A D-30, 0-30 v D-50 ma D-25 v 100y A D-30, 0-30 v gt Sob D-50 ma D-25 v Please add carriage charges to our normal postage charges. D-100 ma D-30 v DC SOLDER(ING IRONS 420p BY127 12p *1N4001 3p 1N914 4p Summ and 4.7mm bits to suit 55p OA50 Bp TN4001 3p *1N4148 2p Antex CX 17W Soldering iron 440p OA50 Bp TN4007 7p *1N4007 7p *1N4007 7p *1N4007 7p *1N4007 7p *100mW zer. 6p 0A200 Bp 1N5404 15p *40mW zer. 6p 6p</th>	Diopy A D-30, 0-30 v D-50 ma D-25 v 100y A D-30, 0-30 v gt Sob D-50 ma D-25 v Please add carriage charges to our normal postage charges. D-100 ma D-30 v DC SOLDER(ING IRONS 420p BY127 12p *1N4001 3p 1N914 4p Summ and 4.7mm bits to suit 55p OA50 Bp TN4001 3p *1N4148 2p Antex CX 17W Soldering iron 440p OA50 Bp TN4007 7p *1N4007 7p *1N4007 7p *1N4007 7p *1N4007 7p *100mW zer. 6p 0A200 Bp 1N5404 15p *40mW zer. 6p
LINEAR CA3160 100 LM358 50 LM2917 200 NE565 150 TDA1022 560 '706 25 CA3162E 450 LM377 160 LM3900 50 'NE567 100 TDA1022 560 '706 25 CA3162E 450 LM377 160 LM3900 50 'NE567 100 TDA1024 125 '741 14 CL7106 790 'LM381 100 LM3814 200 RC4136 90 TL072 75 288 51 CL0808 320 LM3816 200 SN76013 170 'TL081 30 AY-1.0212 680 ICM7565 80 'LM386 65 LM13600 120 SN76013 170 'TL081 30 AY-3.1270 640 LF353 85 LM383 100 MC3302 160 TBA641811 250 'XR2206 300 AY-3.8912 625 LM710 39 LM7	SOCKETS *8 pin 7p 22 pin 20 pin *16 pin 10p 20 pin 22pin *16 pin 10p 20 pin 22pin *20 pin 15pin 15pin 15pin *20 pin 15pin 16pin 16pin *20 pin 15pin 16pin 16pin *20 pin 15pin 16pin 16pin *20 pin 15pin 16pin 10pin *20 pin 15pin 15pin 10pin *20 pin 15pin 15pin 10pin *20 pin 15pin 15pin
HARNSISTURS BL23/ BL23/ AC125 6 BC141 30 BC238 14 BC238 BF195 BF194 22 BL23 ML2366 BC142 6 BC142 30 BC142 30 BC143 30 BC143 30 BC143 30 BC143 30 BC147 30 BC	LM309K 120p 'LM323K Trimmers. Mullard 808 series. Speart 'LM317T 350p 2-10pF 22p. 2-22pF 30p. 5.5-65pF 35p. RESISTORS 120p LM723 40p 120p LM723 40p 120p Carbon film E12 series 14.50v 22p 4.400v 95p 35c 5.5-65pF 35p. 5.5-65pF 35p. RESISTORS BRIDGE RECTIFIERS Carbon film E12 series 14.50v 22p 4.400v 95p Carbon film 600 varies TRIACS + SCRS %W 5% Carbon film E12 series 14.50v 22p 64.00v 95p 4.00v 48p 400v 48 60p 400v 48 A 400v 48 A 400v 40v 48 A
AF196 70 BC172 8 BCY72 19 BFR90 25 T1228 40 27.2302 16 27.3302 16 AF239 75 BC177 18 BD111 56 BFR90 25 T1228 40 27.2302 16 27.3302 16 27.3302 16 27.3373 210 BC107 10 BC178 18 BD131 35 BFX92 25 T1228 65 ZTX304 17 27.33173 210 BC108 8 BC182 0 BD135 50 BFX86 25 T1290 40 ZTX500 16 27.3320 16 27.3320 40 87.332 65 66 60 ZTX500 15 27.8320 40 86.10 15 26 BFX87 25 T1290 40 27.4330 10 35 BFY50 22 T1791A 46 ZTX502 15 27.8203 10 35 BFY50 22	"Smm red 7p "Smm red 8p "Smm green 12p "Smm green 12p "Greet angular TIL32 42p 42p green 17p TIL11 62p Peric Chorn, ande 000 500 Corn, cathode Corn, ande 00p 100p DL704 0.3in 55p FIL312 0.5' 115p TIL32 0.5' 115p TIL32 0.5' 115p TIL31 0.5' 115p TIL32N 05' SwttrCHES Dual colour LED 65p Svbmin, toggle SPDT 60p 'DPDT 50p Miniature toggle SPDT centre off 100p 15M SPDT 80p SPDT centre off 100p Verobice Solderless Breadboard as used in
Submin reley, SPC 012V 170p Gárm 64 ohms min. speaker 70p BOXES Dimensions in Inches. Aluminium. Plug Socket Jack Plug Socket 3 x 2 x 1 70p 6 x 4 x 2 120p 12p 10p 35mm 10p 8p 4 x 3 x 1/h 85p 6 x 4 x 3 150p 13p 11p 51tic 16p 20p 1 mm 13p 12p 12p 5tic 16p 20p 4 x 3 x 2 100p 8 x 6 x 3 190p 13p 13p 13p 14p 15p The Randid Garantee Garantee Garantee 14p 13p	Standard toggle DPDT 48p any IC. 350p SPST 35p DPDT 48p 12p Miniature DPDT Side 12p Push to break 22p Push to break 22p Rotary type adjustable stop Push to break 22p DIL switches all SPST 4 SPST 80p STR day despatch 8 SPST 100p

Hobby Electronics, February 1982



Makin' Tracks

One of the neatest ways of building up a circuit is on printed circuit board. In this special feature, guest writer Don Keighley shows what a printed circuit board is and how to make your own

PRINTED CIRCUIT BOARDS - PCBs - are used extensively because they provide a neat and reliable way of holding components and of making the necessary connections between them. In the days before PCBs, circuits were built up underneath a large metal chassis with the components strung between connection points - tag strips, they were called - in a seemingly haphazard manner. You only have to look inside an old valve radio or TV to get the point. All electronics manufacturers must have breathed a sigh of relief when PCBs were invented.

PCBs aren't used only in industrial equipment - they are equally suitable for the hobbyist. The difference between commercial/industrial PCBs and those we make at home is really only in the techniques used.

Figure 1 shows the PCB of the Intelligent NiCad Charger project from last month's issue, with the components drawn in to show where they go; Figure 2 shows the same PCB viewed from the bottom. It is quite easy to make a board such as this at home - and shortly, we will explain how it's done.

Board Stiff

Now that you know why a PCB is used, let's backtrack a little and see just exactly what it is. Any PCB starts life as copperclad board - a thin base-board (about 2 mm) of insulating material (such as fibre-glass or resin-bonded paper) with an even thinner (about 0.25 mm) copper coating on one side. Figure 3 shows a cross-section of a piece of copper-clad board. Some highly specialised circuits may be built on boards with copper on both sides - called, naturally, double-sided PCBs.

To turn this copper-clad board into a PCB we have to remove all excess areas of copper, leaving behind only those areas (which make up the foil pattern) that we want. After this it's a simple job to drill the holes and to insert and solder components in their places.

By this time you'll be wondering, no doubt, how you 'remove' the areas of copper which aren't wanted - do you need a laser gun to blast them off the face of the earth? Or perhaps Superman might fly along to save the situation and burn them away with his infra-red vision?

The answer is nothing quite as sci-fi as that I'm afraid; in fact it's all down to pure, old-fashioned school chemistry. You see, copper is a metal and metals are dissolved by acids. So all we have to do is place the board into acid and the areas of unwanted copper will be rapidly dissolved (etched) away. But now we have another problem - surely the acid will etch away the wanted areas as well? Well, it will if we let it. But, if we cover up the wanted copper, in the shape of the required foil pattern (as shown in Fig. 4), with acid-resisting material before putting the board into the acid, then those areas will remain un-etched when the rest has disappeared (see Fig. 5).

Down To The Nitty-Gritty

By now, you'll have realised that the production of any PCB goes through three stages:

- design of the PCB foil pattern to suit the circuit
- application of resist in the shape of that foil pattern
- etching of the PCB until unwanted copper areas are removed, subsequent removal of etch-resist and drilling of the component holes prior to circuit make-up.

I'm now going to unravel the mysteries of each stage and show you how to set about designing and making your own PCBs.





Figure 5. After etching, the unwanted copper is etched away and those areas in the shape of the foil pattern (with acid-resisting material) remain.

Designing Your PCB Foil Pattern

The only things you'll need at this stage are: pencils, a rubber, some paper (plain, graph and tracing) and either: a selection of one of each type of component used — ie one resistor, one transistor, one IC, etc — or their physical dimensions. This is because you need to know how big each component is so that, when you begin the layout of the board, you know what distance to leave between component lead holes. If you attempt more than just a couple of PCB foil pattern designs you'll begin to remember the sizes of the more common components and you will only need to measure the unusual ones.



1) Begin by displaying the circuit diagram in front of you, along with a sheet of plain paper. Make sure all components in the diagram are numbered so that as you lay out the foil pattern design on paper you can mark each component's location with its number. Imagine that the sheet of paper is your PCB. All of the components fit into the 'board' from the top, therefore the 'foil pattern' is underneath and you can't see it directly.



2) Choosing a central component, say an IC, pencil in its approximate shape and mark where its connection leads enter into the paper 'board'. Now, draw another component which is connected to the first component.



3) When you have drawn a few components on the paper, you can begin to connect them by pencilling-in 'tracks' on the paper, between holes. Don't worry if you get stuck, or even make a mistake; that's why you have the rubber! Rub-out the error and start again.

Don't be afraid to position components close together: a spacing of 2 mm between components is ideal.



4) Remember that the finished PCB will have its foil pattern on the other side to its components, so tracks can actually pass underneath components. There is no reason why two; or even three tracks cannot pass underneath a component, as long as the tracks don't touch either each other, or the component lead holes.

Draw the remainder of the circuit components on the paper and draw in the remaining tracks to complete your foil pattern.



5) Place a sheet of tracing-paper over a sheet of graph paper and tape the two together along the edges. Now, using the grid of the graph paper to help align components, redraw the layout on the tracing paper. Draw component shapes in one colour of pencil (say, red) and tracks in another colour (say, black). In this way you can instantly tell which is the 'top' and which is the 'bottom' of the board. Check, as you redraw the foil pattern, that it is correct with regard to the circuit diagram.



6) The tracing-paper copy of your PCB foil pattern is now your reference. Cut, or pull off, the tape holding it to the graph paper Turn over the tracing-paper, so that you can see the 'underside' of the board — the black connection pattern corresponds to the actual foil pattern layout required on the copper surface of the copper-clad board.

Transferring Your Foil Pattern On To PCB

Now that you have the foil pattern, you need to transfer it on to the copper-clad board using etch-resistant materials (resist). This resist can take many forms: the simplest can be ordinary household enamel or gloss paint, applied with a fine brush (messy); the most complex is photograhic resist, developed on the circuit board much like your summer holiday snapshots are developed on film. The one you use will depend on how much you're prepared to pay. You can expect to pay about (gulp) £60 for a basic photographic system: this will let you make firstclass PCBs, but it won't do your pocket a lot of good — it's the system which is likely to be used by schools and colleges where large numbers of one-off PCBs are needed.

The poor electronics hobbyist doesn't normally have that sort of money to spend on his pastime, so a cheaper way of doing the job is preferable — but it must also produce boards of good quality. One of the best resists for hobby use (the method is not too expensive and can produce excellent quality boards) comes in the form of rub-down transfer sheets. All the shapes you need, ie holes, IC pads, transistor pads, straight and curved track, are available and a number of companies produce their own versions. Most electronics hobby shops will stock at least one variety. An outlay of about a fiver should get you all of the shapes you need to let you make a number of PCBs.

Putting the foil pattern on the copper board is easy:



1) Lay the pattern on the copper surface of the board and, with a sharp-pointed instrument (a scriber or the point of a pair of compasses), prick through the pattern in to the copper at every component hole location. The foil pattern can be your own design or one taken from HE.



2) At every prick-mark in the copper, rub down a transfer circular hole.

Feature



3) Following your foil pattern, interconnect the holes with transfer tracks until the resist on the copper has the same overall shape and connections as your foil pattern drawing. Be careful as you do this job, because any small cracks or breaks in the resist will mean that a corresponding crack or break will occur in the copper when the board is etched. If you make any mistakes at this stage, they can be removed with the corner of a small piece of sticky tape — but once you have etched the board your mistakes are permanent.

When you finish this task your board is ready to be etched.

Etching Your PCB

The etchant used to etch PCBs is not actually an acid — it's ferric chloride a horrible messy fluid — but it does its job well. Most local component stockists will sell it bagged as crystals or granules and you simply mix water with them to give an etchant solution.

The etching process takes place more rapidly when the ferric chloride solution is warm and you can buy specially built containers or 'baths' to hold the ferric chloride. These baths may be fitted with heaters to maintain a high temperature, with agitators to keep the solution moving (vital to stop the build-up of copper oxide on the surface of the copper, which prevents further etching). They are, however (you guessed it!) expensive.

At the other end of the scale, a plastic photographic-type dish can be used as a bath to hold the ferric chloride during etching, but this method is fraught with hazards — ferric chloride is a *very* dangerous fluid and a strong solution of it will merrily eat its way through your clothes, the carpet, or even the stainless steel kitchen sink (try explaining *that* to the missus!).

Until recently there was no real alternative to the these two methods but a new, low-cost, etching system seems to be the answer to the hobbyist's dreams. It's the subject of an HE Reader Offer, on page 51 and I think you'll agree that it offers excellent value for money.

The HE Reader Offer PCB Etching System is supplied in an expanded polystyrene box which is internally formed to hold the various bits before and after water has been added to the etchant granules. This polystyrene box, therefore, lets you store the system safely and tidily between use. Enough granules supplied to allow a number of PCBs to be etched. Most readers will find they use it only once or twice a month, so this way of storing it will be very convenient. All etching is done within a polythene bag and no mess is involved when making a PCB.

The way to use this system to etch a printed circuit board is illustrated in the following pictures. Start by unpacking the bag from its leak-proof box and making sure everything you need is to hand before commencing.



1). Holding the bag flat, make sure that the bottom clip is in place.



2). Remove the top clip and add 250 ml of warm water. If you have not got a measuring jug, use the polythene bag supplied. It will hold 250 ml when full to within an inch of the top.



3) Re-seal the top of the bag. Remove the bottom clip, mixing the water and the granules. Rock the bag backwards and forwards to dissolve the granules.



4) Seal the solution in the bottom of the bag. Unseal the top and insert the PCB then reseal the top.



5) Release the bottom clip then, holding the bag flat, rock it so that the etching solution flows evenly across all parts of the board. Check every few minutes to see if the etching process is complete.



6) Hold the bag by the bottom and turn it upside-down; holding onto the PCB, turn the bag right way up and squeeze any remaining solution down into the bottom of the bag.



7) Seal off the solution in the bottom of the bag, then remove the top clip. Leaving the PCB inside the bag, rinse off with cold running water.



9) All that's left to do is to clean the etch-resist off the copper tracks and to drill the holes for the component leads. One of the many 12 V hand-held drills is suitable for the job, or a hand drill can be used if one of the powered variety is not available. The best sized drill bit is 1 mm.



10) The completed PCBI The board is now ready for the components to be inserted and soldered in place. Provided the PCB layout (and all the components) are correct, there is now very little that could – or should – go wrong!





All prices include VAT @ 15% - just add 40p post

AMAZING! COMPUTER GAMES

PCBs FOR PEANUTS!!

A bulk purchase of PCBs from several well known computer games including Battle ships, Simon, Logic 5 and Starbird enable us to offer these at incredible low prices

STARBIRD

STANDINU Gives realistic engine sounds and flashing laser blasts – accelerating engine noise when module down, Press contact to see flash and hear blast of lasers shoofing. PCB tested and working complete with speaker and batt clip. (needs PP3). PCB size 130 x 60mm. Only £2,95

COMPUTER BATTLESHIPS

Currier UTER BALLLESHIPS Probably one of the most popular electronic games on the market. Unfortunately the design makes in impractia to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value: SN76477 sound IC; TMS1000 u processor; batr clips, Ris, C's etc. Size 80 x 140m. Only £1.50 Instruction book and circuit 30p extra

LOGIC 5

LUGIL 5 The object is to find the number held in the memory with as few entries as possible. PCB contains u-processor chip and 10 leds, and is linked to a membrare type keyboard. Overlay for keys and instruction provided. PCB sizes: 95 x 80 85 x 70mm. Supplied tested and working – PP3 required. Only E2.60

MICROVISION CARTRIDGES

inese are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag Is, we don't have any consoles! However, they can be used as an oscillator with 4 different freq, outputs simply by connecting a battery and speaker. Tested and working (as an osc) with pin out data. PCB size 72 + x 60m ONLY 25n acch¹¹



ELECTRO-DIAL

ELEC I HU-UIRAL Electrical combination lock — for maximum security — pick proof. 1 million combinations!! Diali is turried to the right to one number, loth one second number, then tight again to a third number. Only when this has been completed in the corract sequence will the electrical contacts close these can be used to operate a relay or solenoid. Overalt dia. 65 x 50mm deep Only 19.95

DEVELOPMENT PACKS

DEVELOPMENT PACKS These pack designed new rop quality compo-nomplete range so the right value attructor a complete range so the right value attructor a whenever raquired. They also give a substan-tial seving over buying nutricular parts. K001.50V ceremic plate capacitors, 5%, 10 of each value 22 for 10.000 F, total 210. C4.80. K002 Extended range 22pF to 0.1. Values over value 22 27 33 39 47 56 68 82 100 120 150 180 220 270 330 390 470 560 680 820 1000 1500 2200 2300 4700 6800.01.015 022.033.047.1. PRICE: 67.68. K003 C280 or similar Polyester capacitors, 10 each of the following: 01, 015, 022.033. 047, 068, 1, 15.22, 33 and 47µF. PRICE: 65.40.

each of the following: .01, .015, .022, .033, .047, .068, .1, .15, .22, .33 and .47bF PRRCE: E3.40, .047, .068, .1, .15, .22, .33 and .47bF PRRCE: E3.40, .011, .0012, .0015, .0018, .0022, .0027, .0033, .0039, .0047, .0056, .0068, .0062, .01, .010, .0103, .0047, .0056, .0068, .0062, .01, .0104,

25 65 Kohl Zener diodes 400mW 5% 10 of each of all the values from 2V7 to 36V Total 280 zen-ners PRICE 15 55. Kohl LEDs - pack of 60, comprising 10 each red, green and vallow mm and 5mm, to-gether with clips. PRICE: 28.95,

CAPACITOR BARGAINS

LAF Aufi Vui Daniburro 2200uF 100V cans 77 x 35mm dia. 75p; 10/05 50. 220uF 10/05 aział 5p; 100 62.30; 1000 616. 400 + 1000F 275V 102 x 44mm dia. 75p; 10 65 56. 200uF 350V, 100 + 100 + 50uF 300V can. 75 x 44mm dia. 40p; 10/52; 100/220. 100uF 25V axial 100/223.

1N4002 OIODES

Lowest ever price¹¹ full spec by Motorola Pre-formed leads for horiz mntg., 10mm pitch 100V 1A rating 100 £1.75; 500 £7.50. 1k £14.5k £65

TOROIOAL TRANSFORMER

110mm dia x 40mm deep 110/240V pri, sec 18V 4A 6 3V 1A, 240V 0 3A ideal for scopes monitors, VDUs etc. Reduced to £5.95

1,000 RESISTORS, £2.50 We ver just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same priceIII KS23 1.000 mixed ¼ and 12½ 5% carbon film resistors, preformed for PCB mntg Enormous range of preferred values 1.000 for E2.05, 5:000 E102; 20k E36.

200 ELECTROLYTICS, £4

K524 Large variety of values/voltages, mostly cropped leads for PCB mntg. 1-1000uF, 10-63V. All new full spec, components, not chuck-outs¹¹ 200 E4; 1,000 E17.50.

CHEAP CHIPS

76477 Sound IC											£1	.25
2102A RAM 8 for												£3
MK4027 shift reg. 8	fc	×										66
uA78MG + volt reg											£1	.00
uA79MG - volt reg											62	.00

FILAMENT DISPLAYS

2653 7 seg display 12.5mm high, Ideal for i operation, taking 5V 8mA per seg. Std 14 package. Only [1 each, 4 for £3.00. Data suppl RELAY

OPTO/REGS/OP-AMPS

UP LU/KELS/UP-AMPS FNA5220 2 digit 1/2 '7.seg. display on PCB, CC With data, £1.50 7.seg. displays: FND360, 367, 501, all 50p; 530, 847, 850, all £1.50. 100p, 7912 100p, 782E 320p, Others on B/L 13 Op Amps: uA4136 130p; uA776 145p; uA777 300p; uA318 245p. Isolators: FCD831, IL15, TIL118, all 60p. TL311 Hexadecumal display with decoder, 0.9-and A.F. With data, £3-50.

COMPONENT PACKS

COMPUNENT FREEDS K503 150 wirewound resistors from 1W to 12W, with a good range of values K505 20 assorted potentiometers, all types including single ganged, rotary and slider (1.70

K511 200 small value poly, mica, eeramic caps from a few pF to. 024F Excellent variety £1.20 K514 100 silver mica caps from 5pF to a few thousend pF Tolerances from 1% to 10%. £2 K520 Switch Pack, 20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2, K521 Heatshrink Pack, 5 different sizes each 200nm, 500

PANELS

C2521 Panel with 16236 (2N3442) on small heatsink, 2N2223 dual transistor, 2 BC108, diodes, caps, resistors, etc. 60p 2482 Potted Oscillator Module works from 1 20V, can be used as LED flasher (3V min.). Supplied with connection data, suitable R, C & I FIN £1

LED E1 Z527 Reed relay panel contains 2 x 6V reeds, 6 x 2S030 or 2S230, 6 x 400V rects • Rs S0p

50p 2529 Pack of ex-computer panels containing 74 series ICs. Lots of different gates and com-plex logic AII ICs are marked with type no. or code for which an identification sheet is supplied.2016s £1:100.ICs £4.100.ICs 4504 Black case 50 x 50 x 78mm with octal base. PCB inside has 24V reed relay. 2007 7A 5CR, 4 x 5A 200V rects, etc. 60p

RELAY/TRIAC PANEL

2537 PCB 100 × 75mm containing a wealth of

components: 2x12v DPCO min. relays, 2x47uf 16v tants, SC146E 10A 500v triac, C112d 8A 400v SCR, 555 timer, 10x1N400 indices, 2N5061, 2x 3mm leds 3x2N3704 jatso R s and Cs. Amazing valuell – if bought separately parts would cost around CBII – Price for the panel just £2.00.

1W AMP PANELS

A011 Competit audio amp intended for record player on panel 95-65mm including vol control and switch, complete with knobs Apart from amp circuitry built around LM380N or TBA820M, there is a speed control crucit using 5 transistors 9V operation, connection data supplied ONLY £1,50.

VU METERS

V006. Very attractive 55 × 48mm scaled 20 to · 5dB 250uA movement. Only £1 75 or £3 pr VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocs can be joined together Bus strips on X & Y axis total 360 connexion points for just £4.15.

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0 28V & 20mA-2A. Board contains all compu-nents except pots and transformer. Only 87.75. Suitable transformer and pots **£6**. Send SAE for fuller details.



Get maximum power at minimum price, yet still with hi-fi specifications and a wide choice of outputs. ILP Bipolar power mps, now with or without heatsinks are unbeatable value for domestic hi-fi - but for disco, guitar amplifiers and PA choose the new range of heavy duty power amps, again with or without heatsinks, with protection against permanent short circuit added safety for the disco or group user. Connection in all cases — via 5 pins. Every item has a 5 year no quibble guarantee and is simple -

includes full connection data. So send your order FREEPOST today.

Load impedance, all models, 4 ohm - infinity. Input impedance, all models 100K ohm. Input sensitivity, all models. 500 mV Frequency response, all models 15Hz-50kHz-3db. BIPOLAR Standard, with heatslinks

Model No	Output power Watts rms	DIST THD Typ at1kHz	ORTION IMD 50Hz/7kHz 4.1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
HY 30	15w/4 812	0 015%	<0.006%	±18±20	76×68×40	240	£8 28	£7 29
HY 60	30w/4-80	0 015%	<0 006%	±25±30	76×68×40	240	£9 58	£8 33
HY 120	60w/4-8Ω	0 01%	<0 006%	±35±40	120 × 78 × 40	410	£20 10	£17 48
HY 200	120w/4-892	0 01%	<0.006%	±45±50	120 × 78 × 50	515	£24 39	£21.21
HY 400	240w/452	0 01%	<0 006%	±45±50	120×78×100	1025	£36 60	£31 83

BIPOLAR Standard, without heatsinks

HY 120P	60w/4-852	0 01%	<0 006%	±35±40	120 × 26 × 40	215	£17 83	£15 50
HY 200P	120w/4-852	0.01%	<0 006 %	±45±50	120 × 26 × 40	215	£21 23	£18.46
HY 400P	240w/412	0 01%	<0 006%	±45±50	120 × 26 × 70	375	£32.58	£28 33

 $\begin{array}{l} \label{eq:protection: Load line.momentary short circuit (typically 10 sec) Slew rate 15V/\mus Rise time: \\ 5\mu s. S/N ratio 100db. Frequency response (-3dB):15Hz-50kHz. Input sensitivity 500mV rms. Input impedance 100k\Omega. Damping factor (8\Omega/100Hz)>400. \end{array}$

HEAVY DUTY with heatsinks

Model No	Output power Watts rms	DIST T H D Typ at 1kHz	ORTION I M D 50Hz/7kHz 4_1	Supply voltage Typ/Max	Sizemni	Wt	Price inc VAT	Price ex VAT
HD 120	60w/4-802	0 01%	<0 006%	* 35* 40	120 × 78 × 50	515	£25 85	\$22 48
HD 200	120w/4-802	0 01%	<0 006%	±45±50	120 × 78 × 60	620	£31 49	£27 38
HD 400	240w/412	0 01%	<0 006%	±45±50	120 × 78 × 100	1025	£44 42	£38 63

HEAVY DUTY without heatsinks

	Pro Pro	tection:	Load	line.	PERMAN	ENT SHO	RT CIR	CUIT	(ide	al	tor
HD 400P	240w/4\$2	0 01%	<0 0	06%	±45±50	120 × 26 ×	70 375	239	42 E	34 1	28
H D 200P	120w / 4:8Ω	0 01%	<0 (06%	±45±50	120 × 26 ×	50 265	£27	17 8	23.0	6 3
HD 120P	60w 4-812	0 01%	<00	06%	±35±40	120 × 26 ×	50 265	£22 l	82 E	19 8	34
		v						7		_	_



ET 2/2

disco/group use should evidence of short circuit not be immediately apparent) The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs as for standard types.

Int. Money Order

How to order Freepost: Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C 0.0 — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order

Please send me the following ILP modules Total purchase price Postal Orders I enclose Cheque Please debit my Access/Barclaycard No Name Address Signature

Post to: ILP Electronics Ltd, Freepost 2: Graham Bell House, Roper Close, Canterbury C12 7EP: Kent: England Telephone (0227) 54778: Technical (0227) 64723: Telex 965780



UNIVERSAL RELAY DRIVER

Operating a relay to switch heavy current or mains voltages is a common application. This project permits a relay to be switched in a variety of ways, from a variety of inputs.

THIS VERSATILE relay driver unit is intended to be used with projects or devices not normally providing a switched relay output. In addition, power for external circuitry can be obtained from the board.

The unit has three groups of 'logic' inputs and a direct input. The relay itself is driven by two transistors, Q1 and Q2, and the direct input goes to the base of Q1 via a resistor (R7). Linking this input to the unit's O V rails — via a switch, a transistor which is turned on by a signal (open-collector logic) or a logic gate output — will operate the relay.

The logic circuitry on the board can be implemented by installing Link 1, which connects the output of the logic circuitry to the direct input. There are two 'logic high to operate' inputs (pins 1 and 2). A logic high level - ie a voltage level above about 2 V - on either of these inputs will operate the relay. There are also two 'logic low to operate' inputs (pins 7 and 8). Pulling either of these inputs below logic low about OV5 — will operate the relay. Note that these input pairs are ORed with diodes and can be linked so that one input inhibits the other. In addition there are two 'latch' inputs, pins 3 and 5. Pin 4 is the output of the latch circuitry and latch operation is implemented by linking this pin to one of the other inputs. All the logic inputs are high impedance and can be driven from CMOS circuitry.

The unit is powered from a 12 to 15 V AC source such as a battery or 5 VA transformer. Supply for IC1 (and perhaps any off-board circuitry) is obtained from a simple zener regulator circuit. This can be chosen to suit individual requirements. We used a BZX61C/8V2 zener to provide an 8V2 rail for IC1, and a 220 ohm, 1 W resistor for R5. You can use any convenient zener from 5V1 to 15 V but no higher, and we recommend 1 W types run at around 50-60 mA current. You will have to work out the value of R5 according to your choice of zener. For a 15 V zener, R5 could be 47 ohms, for a 5V1 zener, 270 ohms, or for a 12 V zener, say 100 ohms. There's plenty of latitude and these values are only given as a guide.

The logic circuitry (ie IC1) can be supplied from an off-board source if you wish. To do so, remove R5 and use a 15 V zener for ZD1 to prevent spikes on the external supply line causing

П

Г

T

damage to IC1. Note also that the logic levels on inputs 1, 2, 3 and 5 should also be no higher than $15 V_{\rm c}$

The accompanying drawings illustrate how the unit is used in its four basic modes of operation.

Construction

Construction is very straightforward. The components may be mounted in any order but you will probably find it easiest to leave the relay and C1 until last. Watch the polarity of all the diodes, the transistor and the IC. However, leave out Link 1 at this stage.

Önce you've got it together and have checked everything, apply 12 V AC to the AC input and check various modes of operation as follows:

(1) Bridge the free end of R7 to ground. The relay should operate.

(2) Install Link 1, then bridge pin 7 to ground. The relay should operate. Likewise for pin 8.

(3) Bridge pin 1 to the cathode of the zener. The relay should operate. Likewise for pin 2.

(4) Connect pin 4 to pin 1 or 2. The relay may operate. Apply a pulse to pin 3 or 5 and see that it latches on. A pulse on the other input will drop it out again.

If all is well, you unit is ready for installation!





How It Works_

The best place to start is right in the middle of the circuit — because that's the 'business' end!

Transistor Q2 has relay RLA 1 as its collector load. Diode D5 provides protection for Q2 when the coil current is cut off whenever Q2 is turned off. The base of Q2 is driven by the collector of Q1 via R8 and R9. Base bias for Q1 is obtained from the resistor network of R6 and R7. The 'free' end of R7 can be linked to onboard logic circuitry (IC1) or driven by an external source.

If the free end of R7 is connected to 0 V then base current will flow in Q1 which will turn on. This will turn on Q2 and the relay will operate. In fact, all that is required to turn Q1 on is to 'pull' the free end of R7 about 1 V below the positive supply rail to overcome the OV6 base-emitter turnon voltage of Q1.

Effectively, a 'low' level on the free end of R7 will operate the relay.

Two groups of logic circuitry built around IC1 are included to provide a variety of operating 'modes'. IC1 is a quad NOR gate package. One gate, IC1d, is arranged to provide a 'logic high to operate' mode. Two diodes connected as simple OR gate have their cathodes connected to pin 1 of IC1d. The output of another gate, IC1c, drives the other input, pin 2, of IC1d. IC1c has one input (pin 6) connected to 0 V, which is thus held at logic low. Pin 5 IC1c is held at logic high by R3 and thus its output, pin 4, will be low. As this drives pin 2 IC1d, its output (pin 3) will be high. With Link 1 fitted, Q1 will normally be off and the relay not operated.

When a high logic level is applied to either input pin 1 or 2, or both, the diode(s) will conduct driving pin 1 IC1d high. The output, pin 3, will go low and the relay will operate. The relay will remain operated only while the input remains high.

Two diodes (D6, D7) are connected as a simple OR gate with their anodes connected to pin 5 IC1c. A logic low on either input pin 7 or 8 ('logic low to operate') or both will pull pin 5 IC1c low and its output, pin 4, will go high. Pin 2 IC1d will go high and thus pin 3 IC1d will go low and the relay will operate. The relay will remain operated only while the input remains high.

The remaining two gates from IC1 are connected as a set-reset (SR) flipflop. Pin 4 on the printed circuit board provides an output which may be coupled to the other inputs. Assume the SR flip output is initially low. A pulse applied to input pin 5 will cause pin 4 (pins 9, 11 or IC1a, b) to 'latch' high. A pulse then applied to the opposite input pin will cause the output to go low again and remain low.

This part of the circuit can be used as a 'switch debouncer' as illustrated.

Power is derived from an off-board 9 V AC or 12 V AC source. This drives a bridge rectifier, diodes D1 to D4, smoothing being provided by C1. A zener diode, ZD1, is used to provide a regulated supply to the logic circuitry (IC1).



There should be no problems with any of the components used in this project they are all easy-to-obtain types. The PCB-mounting relay is type RL111 from Watford Electronics, whose address can be found elsewhere in this issue.





LATCH OPERATION

Pin 4, the output of the set-reset (SR) flipflop, must be linked to either pin 1 or pin 2, or pins 7 or 8. A positive-going pulse on pin 3 or pin 5 will cause the relay to latch. A positive-going pulse on the opposite latch input will then cause the relay to unlatch.



SWITCH DEBOUNCING The SR flip-flop (IC1a and b) is not electrically connected to the rest of the circuit and may be used in external circuitry – for example, as a switch debouncing circuit.



DIRECT INPUT

The relay will operate when the input is low (ie 0 V) or 'pulled' about 1 V lower than the positive supply rall. Only those components shown are necessary for this mode of operation.

_Parts List

RESIST R1,2,9 R3,4 R5 R6 R7 R8	ORS (all ½ W, 5% unless noted) 1k0 10k 220R, 1W (see text) 4k7 12k 2k2
CAPAC	TORS
C1	1000 u, 25 V electrolytic (PCB mounting)
SEMIC	ONDUCTORS
IC1	4001B
Q1	BC557
Q2	BC547
D1-D5	1N4001, 1N4002 etc
D6-D9	1N914, 1N4148 etc
201	400 mw or 1 w zener, see text

MISCELLANEOUS

PCB; RLA1 - relay (type RL111).





Figure 2. Bottom view of the PCB - make it yourself (see page 11).





Because ILP MOSFET power amps give you ultra-fi performance without costing big money. Performance you thought you couldn't afford at a price you know you can

All II P modules are compatible with each other — you'll find many more in other ILP ads in this magazine. Choose ILP MOSFET power amps when you need the fastest possible slew rate, low distortion at high frequencies, better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Connection is simple - via 5 pins. With other ILP modules you can create almost any audio system, whatever your age or experience



or experience. ILP MOSFET power amps are now available with integral heatsink (no extra heatsink required), or ready for mounting on to your own heatsink or chassis. Full dissipation detail on data sheet, available on request. Each carries a 5 year no quibble guarantee and comes with full connection data

Send your order FREEPOST today on the coupon at the foot of this ad



models, 4 ohm - infinity Input impedance, all models 100K ohm Input sensitivity, all models, 500 mV Frequency response, all models 15Hz-50kHz-3db

MOSFET Ultra-Fi, with heatsinks

Model No	Output power Watts rms	DISTI T H D Typ at 1kHz	ORTION IMD 50Hz/7kHz 4 1	Supply voltage Typ/Max	Size nim	Wt gms	Price inc VAT	Price ex VAT
M0S 120	60w/4-8Ω	<0 005%	<0 006%	+45±50	120 × 78 × 40	420	£29 76	£25 88
M0S 200	120w/4-80	<0 005%	<0 006%	±55±60	120 × 78 × 80	850	£38 48	£33 46
MOS 400	240w/4Ω	<0 005%	<0 006%	*55 ±60	120 × 78 × 100	1025	£52 20	£45 39

MOSEET Litra-Fi without heatsinks

	10.0	or nearenne			_		_
MOS 120P	60w/4-8\$2	< 0 005% < 0 0	06% ±45±50	120 × 26 × 40	215	£26 82	£23 32
MOS 200P	120w/4-852	< 0 005% < 0 0	06% +55±60	120 × 26 × 80	420	£32 B1	£28 53
MOS 400P	240w /452	< 0 005% < 0 0	06% ±55±60	120 × 26 × 100	525	£44 75	£38 91
Protection:							

Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice)

Siew rate 20V μ s. Rise time3 μ s. S/N ratio 100db. Frequency response (-3dB) 15Hz-100kHz. Input sensitivity 500mVrms. Input impedance 100k. Damping factor (8 Ω /100Hz)>400

How to order Freepost:

Huw to order Precipus: Use this coupon, or a separate sheet of paper, to order these products, or any products from other LP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C. 0.D. — add £1 to total order value. Access and Barclaycard welcome All UK orders sent post free within 7 days of receipt of order

Total purchase price		
l enclose Cheque 📃	Postal Orders	Int. MoneyOrder
Please debit my Access/	Barclaycard No.	
Name		
Address		
Signature		
ET 3/2	Post to: ILP Electronics Ltd, Freepost Canterbury CT2 7EP, Kent, England Telephone (0227) 54778, Technical (I	2 Graham Bell House, Roper Close 0227) 64723 Telex 965780
		HE 3/2
	All and a sead	

HE Special Offer

Seno GS PCB Etching Kit Etch Resist Pen Polyfix cleaning block Two Single Sided boards £9.50

HE Sp







PCB Etching Kit

No mess, no fuss.

Most important, no dangerous chemicals splashing about the kitchen or the bathroom.

The Seno GS printed circuit board etching system provides a high level of safety, convenience and efficiency for making one-off PCBs at home or at school. It is unique in allowing the etching process to be carried out in a sealed bag, eliminating the danger and mess associated with open tanks or baths.

Between use and disposal, the highly corrosive etchant solution is stored, in it's bag, in a leak-proof box. When the solution is finally expended (enough chemical is supplied to etch 248 square inches of copper — that's more than 12 average 6" x 4" single-sided printed circuit boards), the addition of a simple, safe neutraliser converts the remaining etchant into a harmless, solid lump!

The **Seno GS** kit consists of a sealable etching bag, granulated etch chemicals, leak-proof box and neutraliser. As a special bonus, this offer (available only through Hobby Electronics) includes an etch-resist pen that allows you to draw foil patterns directly onto the copper surface; a polyfix block for cleaning the copper both before and after etching; and, to get you started quickly and with minimum bother, two 6" x 4" single-sided copper-clad boards.

Make the most of the projects in Hobby Electronics by making your own printed circuit boards!

Price includes VAT and postage and packaging; please allow 28 days for delivery.





The Editor answers a selection of your letters

Printed Circuit Boards

Dear Sir,

Can you help, please? You sometimes state that matrix board (strip board) should not be used and that we must use PCBs. Why? Is this due to stray capacitance?

I built your Kitchen Timer, albeit modified so that the output, instead of going straight to the buzzer, goes through a circuit repeating the alarm at one minute intervals. Simple enough. It works, except for the calibration. One can calibrate out of the steel case but as soon as it is assembled in the case the calibration goes awry. Is this also due to stray capacitance, due to either the veroboard or the metal case? I would appreciate an explaination.

In any case I would like to make PCBs but have read articles for and against the standard method. I would prefer the photographic method for accuracy and perhaps time. I presume there is no method for doing the reverse, ie depositing a conductor in the appropriate place rather than etching the copper away.

Once again, your help would be appreciated.

E. Strang,

Krugersdorp, South Africa.

A very timely letter, this. The main reason for using PCBs is that they are neater, safer and allow less probability for error — always assuming that the circuit and the foil pattern itself is correct. And they do minimise stray capacitance which can be critical, particularly with circuits operating at high frequencies. I can see no obvious reason why the Kitchen Timer is behaving as you describe, but the effect does seem to be due to stray capacitance and putting the ciruit onto a PCB would certainly help. More simply, you should ensure that all the wiring is neat and external leads kept as short as practicable.

You will note that we are definitely FOR printed circuit boards and the article commencing on page 11 describes, step by step, one procerdure for making PCBs. It is not a photographic method but, if proper care is taken, it will produce virtually the same quality result.

Finally, there are methods for depositing metal in ''appropriate places'' but they are feasible only in industrial applications. In fact, transistors and ICs are made by a combination of etching and depositing different semiconductors and metals.

Problem Pages

Dear Sir,

I have been buying Hobby Electronics for a number of months. I know that, on occasion, gremlins get into circuits in the magazine. The gremlins have now migrated to the publishing mac hine. On obtaining my copy of December '81 HE recently I was surprised to find that what should have been page 3 was, in fact, page 15. Continuing, I reached page 30 and on turning to page 31 I found I was back at 15I This time I managed to reach page 62 without mishap, only to find that page 63 was actually page 47. I had double vision without touching a drop! R. Dunlop,

Blairmore, Argyll.

We apologise to our readers who struck these somewhat odd copies. The gremlins had (have?) migrated to our printers, causing considerable amazement to readers scattered throughout the country. Hopefully these annoying beasties have now been exorcised.

PCB Prints

Dear Sir,

Such a build-up to your Guitar Graphic Equaliser which, I am sure is a well designed project. But, with a capital 'B', what happened to the PCB pattern? Your 'underground map of printed circuit boards' appears to be of the wrong area! G. Lloyd, Wolverhampton.

Wherever and whenever possible, we publish the PCB foil pattern for projects in Hobby Electronics. Unfortunately, three of the projects in the December issue — the Equaliser, the Doorchime and the Drum Synthesizer, all highly popular projects, too — were designed for us by contributors who wished to retain the copyright on the PCB. For this reason we were unable to publish them. In general, the un-published PCB is the exception, certainly not the rule.

Errata and Back Numbers Dear Sir,

Firstly, a question. In the January '82 isue of Hobby Electronics you describe the construction of a NiCad battery charger. In the circuit diagram on page 27 I noticed that the collector of transistor Q1 is left un-connected. If, as explained in the text, Q1 and Q2 form a Darlingtopn pair, shouldn't the collectors of these two transistors be connected?

Secondly, a request. Some time ago I sent two separate cheques to your back issues department to cover the cost of a January '81 and a March '81. I've received the January issue but not the other. Would you check this for me, please?

Finally, a comment. I've been teaching myself electronics for about six months. During that time HE has provided a great deal of interesting and instructive reading. For me, HE is much more comprehensible than other magazines on the market. R. Berrisford, Thorpe, Derbyshire.

Working backwards through Mr. Berrisfords comments and queries, it is first of all gratifying that he chooses exactly those words we like to use for Hobby Electronics. We try to please but also to inform — and we work very

hard to ensure that we are

'comprehensible'. The matter of the missing issue has been taken up with the Reader Services department and an answer will be forwarded in due course. In principle, back numbers are available for all previous issues of HE but in practice certain popular issues have 'sold out' and can no longer be obtained, even by the editorial staff.

Then there's the gremlins (again) in the project. We're sure you know the line about 'The best laid plans . . . ''. As you say, the collectors of Q1 and Q2 should be connected. Try as we might to eradicate errors they still manage to creep in, like mice. Here's some more from the January '82 issue.

In the circuit of the Volume Expander (page 55) the unmarked transistor is, of course, Q2, the BF244B FET.

In the component layout of the Intruder Confuser (Figure 2, page 39) IC1 is shown up-side down. The notch dhould appear at the top, ie pin 1 is at the top left.



Hobby Electronics, February 1982





Suddenly, instead of two LP encapsuated pre-amps, there are eight — everything from the simple mono pre-amp (HY6), through mixing mono pre-amps (HY12 and HY69), to a dual stereo preamp (HY71). Plus a new guitar pre-amp (HY73). Each gives the very best reproduction from your equipment that your money can buy, and all are protected against short circuit and wrong polarity. All UP modules are compatible with

an ILP modules are compatible with each other — combine them to create almost any audio system. Every item carries a 5 year no quibble guarantee and includes full connection data.

So send your order today - the Freepost coupon needs no stamp.

PRE-AMPS

Model No.	Module	What it does	Current required	Price Inc. VAT	Price ex. VAT
HY 6	Mono pre-amp	Provides inputs for mic/mag_cartridge/tuner/ tape/auxiliary, with volume/bass/treble controls.	10 mA	£7.41	£6.44
HY 9	Stereo pre-amp	Two channels, mag. cartridge, mic + volume control	10 mA	£7.71	£6.70
HY 12	Mono pre-amp	Mixes two signals into one, with bass/mid- range/treble controls.	10 mA	£7.71	£6.70
HY 66	Stereo pre-amp	Two channels, with inputs for mic/mag, cartridge/tape/funer/auxiliary, with volume/ bass/treble/balance.	20 mA	£14.02	£12 19
HY 69	Mono pre-amp	Two input channels, mag. cartridge mic, with mixing and volume/treble/bass controls.	20 mA	£12 02	£10.45
HY 71	Dual stereo pre-amp	Provides four channels for mag. cartridge/mic with volume control.	20 mA	£12.36	£10.75
HY 73	Guitar pre-amp	Provides for two guitars (bass + lead) and mic with separate volume/bass/treble and mixing.	20 mA	£14.09	£12 25
HY 75	Stereo pre-amp	Two channels, each mixing two signals into one with bass/mid-range/treble controls.	20 mA	£12 36	£10.75



Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C 0.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Total purchase price		
l enclose Cheque	Postal Orders	Int Money Order
Please debit my Access / Barc	laycard No	
Name		
Address		
Signature		
ET 4/2	Post to TLP Electronics Ltd Freepost Canterbury CT2 7EP Kent England Telephone (0227) 54778 Technical (2 Graham Bell House Roper Close. 0227) 64723 Telex 965780
	P. P	
	ELECTRO	
TAYAH	AD STAY	WITH
	I enclose Cheque	I enclose Cheque Postal Orders Please debit my Access / Barclaycard No Name Address Signature ET 4/2 Post to ILP Electronics Ltd Freepost Canterbury CT2 7EP Kent England Telephone (0227) 54778 Technical (ELECTROP TAYAHEAD STAY

Project

NOISELESS FUZZBOX

No buzz, just fuzz!

THERE HAS BEEN no shortage of FuzzBox designs over the past few years and while most of them gave a good fuzz effect, many unfortunately also made quite good noise generators as well! The increase in noise has been due to he way in which the fuzz effect is produced; the two most common methods used are a high gain amplifier driving a clipping circuit (which generates the distortion and causes the effect), or a high gain amplifier with a built-in clipping circuit. The fuzz circuit itself is often followed by an attenuator which reduces the output to a level comparable to that produced by the guitar pick-up. This will also reduce the noise output of the unit proportionally, but there will still be a significant degradation in the overall signal-to-noise ratio of the system because the noise is actually being produced by the high gain amplifier.

A simple way of improving the *apparent* signal-to-noise ratio in situations such as this is to use a noise gate; a circuit that enables a signal to pass normally if it is above a certain level, but provides a fairly high level of attenuation (usually around 20 to 40 dB) if the signal is below the threshold level or is absent altogether. This system relies on the fact that when a reasonably strong signal is present it masks the noise. When such a signal is not present the noise gate provides attenuation which reduces the noise to an unnoticeable level. Thus the signal-



to-noise ratio is apparently increased, although the *true* signal-to-noise ratio remains unaltered.

This fuzz unit has a form of noise gate action built in so that it does not give any significant increase in the apparent signal-to-noise ratio. It produces conventional clipping-type fuzz, is battery powered and connects between the guitar and the amplifier in the usual way. A foot-operated switch enables the fuzz effect to be switched out if required.

Construction

We used an aluminium case measuring about $133 \times 102 \times 38$ mm to house this project, but any plastic or metal

case having similar dimensions should be OK. The two sockets are fitted at one end of the case and SW2 is mounted on the lid towards the other end. As SW2 is foot-operated switch it is obviously a good idea to use a reasonably strong case, but it is likely that any ready-made plasic or metal case of the appropriate size will be more than tough enough. Otherwise, tread carefully!

Fit the small components on a 0.1" matrix stripboard having 36 holes by 15 copper strips using the component layout (and wiring) shown in Figure 2. Make the breaks in the copper strips, drill the two 6BA clearance mounting holes using a 3.2 mm diameter drill and then solder the components and link wires into place.



Figure 1. The noiseless circuit.

Project



Figure 2. Component overlay and bottom view of stripboard.

Bolt the finished board to the base panel of the case between the sockets and SW2, using spacers to keep the underside of the board clear of the case, if it is metal. Of course, the point-topoint wiring must be finished before finally fitting the component panel in place. SK1 has double-pole, double throw (DPDT) contacts but these are used as an single-pole, single throw (SPST) switch in this circuit, with four of the switch tags left unused. If a separate on/off switch is preferred, there is ample space for this to be fitted alongside SK1 and SK2; SK1 can then be a straightforward ¼″ jack socket.

In use, the unit is simply connected between the guitar and the amplifier using screened jack leads. Assuming a switched socket is used for SK1, the unit will automatically be switched on when the guitar is plugged in, and switched off again when it is unplugged — so don't forget to unplug it! PR1 is adjusted, by trial and error, to a setting that gives no significant change in volume when SW2 is used to switch the unit in and out of the signal path.



Project

The input signal is fed to the output via a high gain amplifier which clips the signal to give the familiar distortion of the fuzz effect. The output signal virtually a square wave. To give the circuit a low noise level in the absence of a signal, the gain of the amplifier is normally quite low and is only switched to a high level when a suitable input signal is present. This is achieved by taking some of the input signal to another high gain amplifier, rectifying and smoothing the output to give a DC signal and then using this signal to control a switching transistor in the negative feedback circuit of the clipping amplifier. With no input present, there is no DC signal produced, the switching transistor is turned off and the clipping amplifier has a low gain (and so a low noise output). With an input signal applied to the unit, a DC signal is produced and switches on the transistor. The negative feedback of the clipping amplifier is thus reduced and its gain is boosted by a factor of more than 20. This produces clipping and although the noise level is greatly increased, it is not apparent as the noise is masked by the guitar signal.

The full circuit diagram of the fuzz unit shows that it is basically a conventional op-amp clipping circuit based on IC1. A low noise BIFET opamp is used so that the quiescent and operational noise levels of the unit are kept as low as possible.

How It Works

Normally IC1 has a voltage gain of about four and the gain is set at this level by the negative feedback network which consists of R5, R6 and R9. The voltage gain is actually equal to the sum of these resistances divided by the resistance of R5 and R6. If Q3 is switched on, its collectoremitter impedance becomes very low and effectively short-circuits R5. The gain of the circuit then becomes equal to R6 plus R9 divided by R6, or just over 100 (40 dB), with the specified values.

At this higher gain the output from any normal guitar pick-up will be sufficient to produce an output voltage swing of at least $\pm 0V6$ from IC1; this causes D3 to conduct on positive peaks and D4 to conduct on negative peaks. When either D3 or D4, are conducting, then, they shunt R9 and effectively reduces the value of the feedback resistances. In fact the reduction in gain produced by the two diodes is so great that the output does not change significantly while one or the other of them is biased into conduction, giving the required clipping action. C6 couples the output of IC1 to a simple variable attenuator using PR1 as a volume control. With many pick-ups, the output from IC1 will be much higher than the direct output of the pick-up and PR1 is adjusted to reduce amplified output to match the 'straight' guitar signal. SW2 is a foot-operated switch which can be used to bypass the unit when

the fuzz effect is not required and, provided PR1 is adjusted properly, there will be no obvious change in signal level when SW2 is operated.

R7 and R8 are used to bias the noninverting input of IC1 and, as this device is used in the non-inverting mode, the input signal is coupled to this input by C5. R7 and R8 are also used to bias Q1, which is used as an emitter follower buffer stage. The output of Q1 is coupled by C1 to the input of a high gain common emitter amplifier, Q2, and this stage provides about 40 dB of gain. With a reasonably strong input signal, Q2 supplies a large output signal which is rectified and smoothed by D1, D2, and C3. The resultant positive DC bias is used to drive Q3 by way of R4.

The switching circuit has a fast attack time so that Q3 is switched on almost immediately when an input signal is present. The decay time is also quite short, so that if the input signal suddenly ceases, the noise level also drops. If the input signals fades out quite slowly, then Q3 will switch off quite slowly too; a desirable feature as it masks the action of the noise gate circuit.

SW1 is the on/off switch and is actually a make contact on SK1 so that the unit is automatically switched on when the guitar is plugged into the input socket. A separate on/off switch can be used if preferred. The current consumption of the circuit is about 4.5 mA.



RECHARGEABLE BATTER ES AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SEND SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call:

> * NEW SEALED LEAD RANGE AVAILABLE *

SANDWELL PLANT LTD. 2 Union Drive, Boldmere Sutton Coldfield, West Midlands 021-354 9764

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advant-age of the many opportunities open to the trained man. You study in your own home. In your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful

City & Guilds Certificates

Telecommunications Technicians **Radio Amateurs Electrical Installation Work**

Certificate Courses

Colour TV Servicing Electronic Engineering and Maintenance Computer Engineering and Programming Radio, TV, Audio Engineering and Servicing Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

T	o: International correspondence
2	Chools
	Dept 262R, Intertext House, London SW84UJ or telephone 622 9911
Su	bject of Interest
N	ame
A	dress

Tel

MDXERS FADERS

Just some of the 28 new amazingly compact modules from ILP Electronics, Britain's leader in electronics modules - you'll find more new products in the amps and pre-amps advertisements

All ILP modules are compatible with each other-you can combine them to create almost any audio system. Together they form the most exciting and versatile modular assembly system for constructors of all ages and experience.

Every item from ILP carries a 5 year no quibble guarantee and includes full connection data. So send your order on the Freepost coupon below today!

Model No	Module	What it does	Current required	Price inc. VAT	Price ex. VAT
HY 7	Mono mixer	Moxes eight signals into one	10 mA	£5.92	£5.15
HY 8	Stereo mover	Two channels each mixing five signals into one.	10 mA	£7 19	£6.25
HY 11	Mono mixer	Mores five signals into one — with base/treble controls	10 mA	£8 11	£7.50
HY 68	Stereo mixer	Two channels, each mixing ten signals into one.	20 mA	٤9 14	£7.95
HY 74	Sterec mover	Two channels, each mixing five signals into one — with treble and bass controls.	20 mA	£13.17	£11.45

AND OTHER EXCITING NEW MODULES

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 13	Mono VU meter	Programmable gain / LED overload driver.	10 mA	£6.84	£5.95
HY 67*	Stereo head- phone driver	Will drive stereo headphones in the 4 ohm- 2K ohm range.	80 mA	£14 20	£12.35
HY 72	Voice operated stereo fader	Provides depth/delay effects	20 mA	£15.07	£13.10
HY 73	Guitar pre-amp	Handles two guitars (bass and lead) and mic with separate volume/bass/treble and mix.	20 mA	£14.09	£12.25
HY 76	Stereo switch matrix	Provides two channels, each switching one of four signals into one	20 mA	To be an	nounced
HY 77	Stereo VU meter driver	Programmable gain/LED overload driver	20 mA	£10 64	£9.25

For easy mounting we recommend: B 6 mounting board for modules HY6 -HY13 £0.90 mc VAT (0.78 ex VAT) B 66 mounting board for modules HY66-HY77 £1 12 inc. VAT. (0.99 ex VAT.) All modules are encapsulated and include clip-on edge connectors. All operate from ±15V minimum to ±30V maximum, needing dropper resistors for higher voltages. HY67 can be used only with the PSU 30 power supply unit. Modules HY6 to HY13 measure 45 × 20 × 40mm. HY66 to HY77 measure 90 × 20 × 40mm.

FP 480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by ILP for use with any two power amplifiers of the same type to double the power output obtained and will function with any ILP power supply. In totally sealed case, size 45 \times 50 \times 20mm with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8 Ω . Contributory distortion less than 0.005%. Price: £5.51 inc. VAT. VAT £4.79.)

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.O. - add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order

Postal Orders	Int, MoneyOrder
irclaycard No.	
Post to ILP Electronics Ltd, Freepost Canterbury CT2 7EP, Kent, England Telephone (0227) 54778 Technical (0	2. Graham Bell House. Roper Clos 0227) 64723 Telex 965780
	HE 5/2
	Postal Orders

والبين بتثبي جديد بت



Accept no substitute!

The heading this month is another of our Editor's attempts at wit — that's what he calls it and who am I to argue? It was inspired (if that's the word) by a number of letters, this month, offering alternative designs for the Substitution box project from the November '81 issue.

Dear CD,

I was looking at the substitution boxes in the November issue. I saw that the heart of the project — the resistors were only 2p each but the switches were 65p each, so I have re-designed the circuit. Mine has 96 resistances instead of 24 and it doesn't need a changeover switch.

If you need a capacitor substitution box you only need one rotary switch and one changeover switch. Yours Sincerely, Nicholas Bradley, Havant, Hants.

PS Can I have a binder, please?

My advice, Nicholas, is to stick to electronics, and leave economics well alone!

Offers of assistance abound this month (enough, stop, cease and desist etcetera), and this gentleman then had to nerve to ask for help!

Dear CD,

... Now if you could help me, where can I get thyristor C103 used in the Reaction Tester (September '81)? Also, could you give me a supplier for Tescus Instruments TO3 transistor R1039? It comes from the line sequesncer of a television. I. Scholey, Edenbridge, Kent.

The first question is easy; try RS Components. The second is more difficult - sounds more like a supermarket than a transistor manufacturer - but I think you mean Texas Instruments, don't you? In either case, I can't help you; I have no record of a TI transistor with that number. Very often the parts used in commercial equipment are specially made and have non-standard designations and this is why I am usually unable to help with enquiries relating to commercial equipment! I do like to help, you know, but sometimes you just have to help yourselves, if you see what I mean (no, I don't mean the binders)...

Dear CD

As part of my 'O' level technology project I am building your Six Watt Siren (March 1980), but the photograph does not make the component layout very clear. Could you please send me a diagram?

I've been reading HE since November 1978 so how about a binder to put by HEs in, or even my technology project? K. McDermott, Colchester, Essex.

It wasn't my project, I assure you - I had nothing to do with it, nothing but you're quite right; it's not very clear, is it? However, here is a letter followed by a genuine helpful reply; keep it and treasure it forever.

Dear Clever Dick,

I have a problem that you may be able to solve for me. I have been given a new car stereo radio/cassette. The instructions clearly say 'negative ground only' but I have an old car and its electrical system is positive ground. Is there any way I can install the new hifi in my old car? I would be grateful for any assistance you could offer. A.M. Lawrence, Chessington, Surrey.

Trade in your old car? If that's not practical (it isn't? Oh!) then you must be sure to insulate the chasis of the hifi from the car body. A piece of wood is as good as anything else; fix the wood to the car and the stereo to the wood, then connect the power leads normally — that is, negative to negative, positive to positive (the car chassis, in your case). Happy motoring!

Yes, CD administers assistance with a smile — and those ingrates who call it a smug sneer have written themselves permanently off the free binder list.

Dear Clever Dick,

I would appreciaste it if you could help me. I have not been able to obtain a U267B bargraph driver IC (LED VU Meter, November '81). Would I be able to order it from Britain?

Please could you send a binder to a regular reader of your fantastic magazine in South Africa? *A. Visagie, Bloemfontein, South Africa. Would you, could you? Of course. According to the Buyline for that project, the U267B is supplied by Ambit International. Their UK address is 200 North Service Road, Brentwood, Essex CM14 4SG, but if they really are International you might find them in South Africal

Old HEs never die, it seems - they just disappear!

Dear CD,

Looking through my copies of HE the other day, I found that I have missed some of the earlier issues. If you could publish my letter, any fellow readers who have any of the issues, and do not want them, could write to you for my address. I would be so grateful as not to ask for a binder to put them in. The following are the issues that I need: November and December, 1978; January and November, 1979. Naturally, I would be happy to pay for them. I. Spearman,

Ongar, Essex

Now before anyone gets bright ideas about cashing in their precious backissues, this is not some kind of lonely hearts club for lost copies! However, I could, if you wish, publish your full address so that anyone with spare copies can contact you directly. Over to you, Mr. Spearman.





ANDREW MAWSON, ARE YOU THERE, ANDREW MAWSON? Our super-efficient filing system has managed to 'eat' your address. Your binder awaits you.

Here we have a letter from a worried man — or perhaps the rest of us should be worried???

Dear CD,

When are you going to publish a circuit for a pocket radiation monitor? In the June issue you said you would — or did I blink and miss it? The world is waiting — what say you? Any new game projects coming up soon, please? Keith Williams, Basingstoke, Hants. PS Great mag, keep it up. PPS How's about a binder?

Did I say that . . . well, so I did. Don't know what happened to it, but I'll investigate, how's that? Why do you want a radiation monitor, anyway? Are you planning to start World War Three?

No brilliant ideas for games projects at the moment — maybe you'd like to suggest one or two? That's the cheapest grovel I've seen in ages, so the answer to your last question is . . . you guessed it.

Now here's a name that sounds familiar . . . if only I could remember . . .

Dear Clever Dick, If you look at page 32 You will notice something new. On page 50 there are ads. Not a charger for nicads. If this charger then you need You had better now take heed. It is on page 25, That's where battery freaks get there kicks. Now I've written to you in rhyme, I think that it is about time That you could get a bit kinder And send me a Hobby Electronics binder. Yours Sincerely, Nicholas Bradley. Havant, Hants.

Polite, isn't he? Not much of a poet, but polite with it, though. It appears that Nicholas, and many others throughout the country, has been the victim of an error by our printers who, moving in ways more mysterious than ever before, managed to do strange and wondrous things with the January issue.

Persistance is its own reward, Nicholas, but you can have a binder as well.

IT LIVES AN

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics – It's Easy**. Originally a long-running series in Electronics Today International, **Electronics – It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenominally successful publication is available again, in its third reprint. **Electronics – It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy by mail** order using the coupon below. Make cheques or postal orders payable to ASP Ltd; alternatively you may pay by Access or Barclaycard.





THE NEW 1982 CASIC WORLD BEATERS.

WE WILL BEAT ANY LOWER ADVERTISED PRICE BY 5% providing the advertiser has stocks

AVAILABLE SOON – THE SENSATION OF THE JAPANESE MUSIC SHOW

Designed by a genius, controlled by computer, programmed by a laser. Played by amateurs professionally and by professionals superbly. **THE NEW CASIOTONE 701**



The complete programmable polyphonic keyboard for around £500 Price and delivery on application. (Available very early 1982)

- specification Input an entire piece of music, specially scored in bar code and read by a light pen attached *
- to the instrument. Alternatively, program your own melodies, chords and timing into the extensive memory, (up to 5 minutes or more) with full editing. 46
- 3-WAY PLAYBACK 1/Auto playback of the entire piece; melody, chord, bass and rhythm with arpeggio; following the music via lamps above the keys.
- following the music via lamps above the keys. 2/Auto accompaniment only, with manual melody playing guided by the keyboard lamps which light up to indicate the next note to be played. 3/ONE KEY PLAY facility: allows the melody line to be played, simply by stroking one key to produce the next note. The 5 octave polyphonic keyboard can be split into 2 and 3 octaves and a different voice
- ä
- can be used for the accompaniment. 20 breasthtaking, clear and bright pre-set instruments and voices. Easy play Casio Auto Chord with chords and auto bass. Major, minor, 7th or minor 7th chords fingered or auto memory facility. 16 superb rhythm accompaniments with fill-in variation by touch sensitive strip and 2 different percussion effect buttons. 46

 NEW MT-31. 3 octaves, 22 instruments and voices. (RRP £79)
 ONLY £89

 NEW MT-40. As MT-31 plus rhythms and auto chords/bess. (£125)
 £19

 Other Casiotones: CT-101 £225. CT-202 £275. CT-403 £275. VL-1 £35.95.
 £19

NEW CASIO FP-10 PRINTER



(RRP £49.95) **AN INCREDIBLE £44.95**

Compatible with the FX-501P, FX-502P, FX-601P, FX-602P and FX-702P Manual and program results printout. Memory and program listing.

Manual and program results printout. Memory and program Hating. FP-10 electric discharge mini printer. A remarkably clear 5 × 7 dot matrix printout of 20 characters per line. Up to 30 characters store/printout over 1 ½ lines, with overload symbol. Fast 2 lines/second print speed. Aluminised paper rolls are approx 2,500 lines/30 feet long. Connect directly to the calculator, or via FA-2 cassette interface. Four AA batteries will print approx. 6,000-9,800 lines. Rechargeable pack NP-4M, 13,000 lines. (£6:90) AC adaptor AD-4150 will recharge NP-4M, in situ. (£5). Printer rolls 22:50 per pack of five. Dims: 43.5H × 157.5W × 82:50 [1%'' × 6%'' × 3%'') weight 372g (13.1oz). FX-602P. 512 program steps. With FREE MICROL PP (£9.95)

. £74.95

DISCOUNTS ON SOFTWARE WHEN YOU BUY YOUR HARDWARE FROM US MOST OTHER CASIO CALCULATORS - LOWEST UK PRICES

CASIO'S INCREDIBLE BOXING GAME ONLY £16.95

BG-15 Calculating Alarm Clock Display.

> 15 - 5 3 - 30 ELECTRONIC BOXING CLOCK &

Fight up to 100 challengers of 10 different weights and increasing speed and technique. All Fight up to four challengers of to unnegers weights and increasing speed and technique. All the realism of the ring with eight 30-second rounds per bout, with points scoring. You must win every bout on points or by KO to continue the game — scores are incremental. Raise or lower your guard in defence and attack, sway back to avoid a blow, or forward for maximum power. Throw stamina sapping combination punches (with digital display of stamina rating), high scoring counterpunches, knock-down and knock-out blows and lucky punches. You can even be saved by the bell Digital display of hours, minutes and seconds. 24 hour alarm function. B digits calculates with full memory. We and since change the share puice battarine function. For the served by the beam of gifter tagsary of hours, immutes and seconds. 2# imputes any second second



NEW SPACE INTERCEPTOR WATCH GM-10 Alarm Chronograph (RRP £22.95) £19.95

LCD readout of hours, minutes and seconds, with continuous display of Space Interceptor graphics. Automatic day, date and month calendar function. Daily alarm mode, with hourly time signal option. 1/100 second stopwatch measuring net, lap and 1st and 2nd place times to 1 hour.

INTERCEPTOR GAME

INTERCEPTOR GAME The UFO beams, travelling from left to right, have to be intercepted by changing the altitude of your defences and firing an interceptor slong the beam. A number will light up in the zone of the hit and when 4 zones are lit up a high bonus game starts. Shoot down 16 UFOs without losing 3 missiles and the next, speeded up, round starts. Sound effects are incorporated.

One lithium battery lasts approx 15 months. Black resin case/strap. Metal bezel, Mineral glass face.

World's Most Versatile Alarm Chronograph Watch AX-210

10 Alternative displays: over 60 functions. LCD ANALOG display of time, plus: DIGITAL display of: Time (12 or 24 hour); Calendar; Full month calendar (this month and next month); Dual time (12 or 24 hour); Alarm time; Professional 1/100 second stopwatch with laps, etc. Hourly time signal. Alarm — electronic buzzer or 3 selectable; melodies. Rapid forward/backward setting. 9.4 × 36.4 × 38mm.

(RRP £34.95) ONLY £29.95





Displays hours, minutes and seconds (12 or 24 hours system), day and Displays hours, minutes and seconds (12 or 24 hours system), day and date. Auto calendar; calculator; professional 1/100 second stopwatch measuring net, laps and 1st and 2nd place times; Pacer mode. Can be used as a metronome to pace your running, or any other event. Input data: Length of stride. Pacer signals, from 394 pips per minute to 63 pips per minute. Output data: Elapsed time, up to 24 hours. Distance covered, number of strides, and speed.

ONLY £19.95

OTHER CASIO WATCHES

(RRP £22.95)

F-82 £10.95 A-851 £14.95 W-200 £17.95 W-100 £19.95 CA-90 £19.95 W150C £21.95 W-51 £22.95 W150 £24.95 AN-8GL £24.96 CA-901 £29.95

SHORT FORM CATALOGUE of latest calculators, key-boards and watches available on request. 14p stamp appreciated.

PRICE includes VAT and P&P. Send your company order, cheque, PO or phone your Access or Barclaycard.

DELIVERY NORMALLY BY RETURN OF POST.



LEADING CASIO SPECIALISTS Telephone: 0223 312866





Send for my CATALOGUE ONLY 75p (plus 25p post/packing)

My VAT and post/packing inclusive prices are the lowest. All below normal trade price - some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS ... ELECTROLYTIC: CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS, 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS. TRIMMERS, PRESETS, POTS . . . SINGLE, OUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTORY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLI, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARD WARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED TRADE COMPONENTS **ESTABLISHED 24 YEARS** 161 St. Johns Hill, Battersea, London SW11 1TQ Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 5016



All models incorporate ILP toroidal transformers except PSU 30 and PSU 36 which include our own laminated transformers.

1 or 2 MOS 200/MOS 200P/1 × MOS 400

How to order Freepost:

1 × MOS 400P

PSU 185

Use this coupon, or a separate sheet of paper, to order these modules, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd: cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order

Please send me the follo ILP modules	owing	
Total purchase price		
I enclose Cheque	Postal Orders	Int Money Order
Please debit my Access/	Barclaycard No.	
Name		
Address		
Signature		
ET.6/2	Post to ILP Electronics Ltd. Freepost Canterbury CT2 7EP, Kent, England Telephone (0227) 54778 Technical (0	2 Graham Bell House Roper Close. 0227) 64723 Telex 965780
		HE 6/2
	ELECTRON	VICS LTD

£24 68 £21 46

Sinclair ZX81 Personal Compute the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under \pounds 100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just \pounds 69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



Every ZX81 comes with a comprehensive, specially- written manual – a complete course in BASIC programming, from first principles to complex programs

Kit: £49.⁹⁵

Higher specification, lower price - how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

 Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.

• Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.

• Unique syntax-check and report codes identify programming errors immediately.

• Full range of mathematical and scientific functions accurate to eight decimal places.

• Graph-drawing and animateddisplay facilities.

 Multi-dimensional string and numerical arrays.

 Up to 26 FOR/NEXT loops.
 Randomise function – useful for games as well as serious applications.
 Cassette LOAD and SAVE with named programs.

1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
Able to drive the new Sinclair printer.

• Advanced 4-chip design: microprocessor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

Built: £69.⁹⁵

Kit or built - it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.





ZX IGK RAM

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.



6 Kings Parade, Cambridge, Cambs., CB2 1SN. Tel: (0276) 66104 & 21282.

Available nowthe ZX Printer for only £49.⁹⁵

22

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further intructions.

At last you can have a hard copy of your program listings - particularly

How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stampneeded coupon below. You can pay useful when writing or editing programs.

10 20

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

by cheque, postal order, Access, Barclaycard or Trustcard. EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

Qty	Item	Code	Item price	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95
] Ple 'l enc 'Plea	ease tick if you require a VAT receipt close a cheque/postal order payable to Sinclair Rese se charge to my Access/Barclaycard/Trustcard acco	arch Ltd bunt no.	TOTAL £	
Please	e delete/complete as applicable	11	. i . i	L Please print
Vame	e: Mr/Mrs/Miss	•	1 1	÷ +
Addre	ess:	· · · · · · · · · · · · · · · · · · ·	1	
1				1 1
_				



SCALING the Hi-Fi HEIGHTS Part 2: Record Decks

LAST MONTH WE chose the amplifier that will form the heart of our proposed system and went through the specs necessary to make that choice a logical one. This month we move on to the record player for the system and consider what factors are important to its operation.

FROM A SYSTEM POINT OF VIEW the record source and the amplifier must be chosen to compliment each other electrically. The player has to provide the correct level of signal, from the cartridge, to match the amplifier input and it must have the correct balance to suit your tastes and produce a smooth overall result from the system as a whole.

SONY

Follow the guidelines and keep in mind possible upgrades; changing the cartridge is often the first of these. Make sure, therefore, that the arm will accommodate any future ambitions you may harbour. If you're quite sure that you have none, an integrated player (combining turntable and arm) will probably suffice, but for those with aspirations to higher-fi, separates are the most economical course in the long run.

The basic aim of a record playing system is identical whether it is an integrated arm/cartridge/deck bought complete, or is assembled from separate components. Whatever the method, the end result is that of extracting as much of the mechanical information from the LP as possible and converting it into an electrical signal which can, after amplification, induce the loudspeaker to re-create the original sound.

For this process three things are necessary: a turntable to rotate the LP at the correct speed, a signal producer (cartridge) to track, or follow, the recording groove and a means of holding that cartridge in exactly the right position above the record to enable it to do this accurately — the pickup arm.

The cartridge is the transducer, the device which converts one form of energy into another; it takes the vibrations from the stylus and produces an electrical output corresponding to that vibration. Figure 1 illustrates the method of operation.

Getting Turned

There are two main types of turntable on the market; direct-drive and belt-drive (Fig. 2), as well as two kinds of pickup arm (Fig. 3) and two leading cartridge varieties (Fig. 4). Thus it is better to ignore the myriad 'one-offs' such as moving iron cartridges and idler-drive turntables. As we are concerned here with choosing and using a first system, I think this is permissable.

To a large extent the operating method is irrelevant, much as it was with amplifiers, but because the disc-player is a considerably *less* refined product than the amp, differences between units is considerably *more* marked. Moving coil cartridges offer — in general — a more detailed and 'open' sounding result but at the cost of less secure tracking and looser bass (at the low end of the market, anyway). As with most things, differences become less general as the price goes up! Moving coils are more expensive to make superbly but the best is something truly wonderful! At up to around £100 a unit, it remains totally a matter of taste as to which type you will prefer.

If you read some of the hi-fi mags every month you will get the decided impression that there exists only one unit worthy of turning records around under a cartridge, but there are literally dozens of useful turntables available — all of which do the job very well indeed. Naturally some do it better than others, but cost and value for money vary enormously.

First Off

You'll probably be well advised to stick to an integrated deck at the beginning. A separate deck with added arm and cartridge *can* offer performance advantage, but will require setting up both initially and later on. If this thought induces spasms of panic — or even a moment's indecision — either find a friendly dealer or forget it for now. There is always time later, when upgrading after building up some 'hands-on' experience.

So to specs and interpreting them. We'll take it one component at a time so that the information can be applied equally to both the integrated deck and to separates. As with amplifiers, if we haven't mentioned it below, it's irrelevant to sound quality and can be ignored!

Turntables

Quartz-locked: Direct-drive turntables need some form of speed stabilisation and early models compared the rotation with the ultra-stable mains frequency of 50 Hz to judge how accurately the unit was maintaining its speed. Later designs nearly all employ a crystal oscillator, like those used in watches for example, at around 2 MHz. This ensures a much higher degree of accuracy. Another advantage of this system is the provision of 'variable speed' or *Pitch Control* where the nominal 33 ½ RPM can be varied by a set percentage to allow correction of recording faults.

Feature



- Wow And Flutter: As the turntable's main job is to rotate the LP at the correct velocity, any variations from that velocity can be considered as a form of distortion — it will render impossible the accurate replay of the source material on the record. There are two types of speed variation; (i) a sort of slow oscillation back and forth about the nominal value — noticeable on piano music in particular (wow); (ii) a short term variation, very rapid in nature (flutter) the speed of which can vary downward from a very fast unsettling waver in musical notes. Both are well under control in modern designs and figures of less than 0.5% are easily achieved. The best direct-drive designs can notch up less than 0.05%. Look for anything under 0.2%.
- Rumble: A common feature of all turntable types is the bearing on which the platter (or record support) rests. Any sort of mechanical rotating system will vibrate to some degree or other and a turntable bearing is no exception. As the stylus is picking up mechanical information from the record, if the latter is vibrating unduly due to the bearing, this will be passed on to the amplifier and appear from the loudspeakers as a very low frequency growl — rumble.

Usually specified as a signal-to-noise ratio in decibels (dB), rumble should be only a minor problem on new units — but watch out for it on second-hand components! Look for figures over -45 dB unweighted, or -65 dB weighted.

- Platter Mass: Simply the weight of the turntable upon which the record rests! More important on belt-drive units, where the mass is used like a flywheel to iron out minor variations in speed with sheer inertia. The best belt-drive units use somewhere around 6 lbs upwards. More important than actual weight is that the platter offers proper support to the LP. Mistrust any turntable mat that is not totally flat!
- **Damping/Insulation:** It is obviously important to isolate the turntable from all outside vibration as much as possible in order that only the record groove causes the stylus to move. With direct-drive decks, where the motor is fixed to the plinth, this is more important than with the better belt-drive units, where the entire drive systems 'float' on isolating springs.



Pickup Arms

- Effective Mass: This is the mass that the stylus will have to pull behind it when following the record groove. This parameter is particularly important in matching the arm and cartridge. Cartridges with a high compliance (a large degree of flexibility) are best matched to arms with a low effective mass. However, some of the modern (particularly moving-coil) units have a low compliance and will give of their best in medium to high mass arms. This is because the arm and cartridge together form a mechanical 'tuned circuit' which will behave in much the same way as a capacitor-inductor electrical circuit does and will exhibit a resonant frequency - a particular frequency at which it is easier to move than any other. Thus the frequency response will not be linear but will show a preference for this resonant frequency. The range of resonant frequencies for most arm/cartridge assemblies lies between 5 Hz and 25 Hz. In order that audible frequencies are effected as little as possible, it is advisable to choose components which have a combined resonance below 20 Hz, but above 75 Hz, the frequency around which record warps usually occur. Table One gives you a range of effective masses and cartridge compliances and lists their resonant frequencies. Choose the arm/cartridge in your system to have a resonant frequency of between 10 Hz and 15 Hz and all will be well.
- Bearing Friction: Usually quoted in two forms; lateral and vertical. As most pickup arms rely on two sets of bearings, one aligned in the same direction as the record surface and the other prependicular to it, both figures are important. They tell you the amount of 'drag' imposed by the arm when the cartridge tries to move it! Figures should be given in milligrams and are quoted as the force required to move the arm in a given direction (laterally across the record or vertical to it) when applied to the stylus. Look for something under 30 mg as good and don't use cartridges with a compliance of over 25 mg in an arm with any more than 30 mg friction!
- Tracking (or Downforce) Range: Tells you what range of tracking weight can be applied to a cartridge fitted into the arm. Sounds simple enough, but also watch out that the actual weight of the cartridge you buy can be accomodated by the arm. Somewhere in the spec there will be a 'maximum weight' figure for matching cartridges. It is unwise to come close to this as your available tracking force will be limited.
- Bias Compensation: Every arm should have some! Any object moving in a circle feels a force acting on it, trying to throw it away from the centre of the circle and a pickup cartridge is no exception. As the job of the arm is to keep the cartridge free of outside influences, by definition, it must counter this force. All a bias compensator does — usually with a hanging weight is to pull the arm in the opposite direction to the force, theoretically by an exactly equal and opposite amount; this is determined by experimenting with a test disc. As long as the arm has a bias compensator — don't worry about it! Some integrated decks use springs or magnetic plates and possess a dial to add or subtract bias while the cartridge is playing a record. Nice, but unnecessary.
- Lead Capacitance: Exactly what it says. The amount of capacitance added to the electrical load imposed upon the cartridge by the wiring from headshell to amplifier. Most car-



tridges are sensitive to this figure to some degree as the capacitance is like a mild frequency filter and 'rolls-off' the response. Unless you're making an expensive start to your hifi career by buying a system well up the price scale, it is generally safe to ignore this effect as it is very minor and not liable to effect the music on any but a very few units.

- **Tracking Error:** As nearly all pickup arms are of the type where they pivot at a single point behind the turntable, it will be impossible for them to follow the path taken by the record cutting head used to produce the LP, as this is driven across in a straight line. However, with correct setting-up, the difference in the paths at any point on the record will be small — less than 2° in fact. On integral decks there is little the buyer has to worry about, things will have been worked out for him (hopefully) during manufacture. If you are assembling a deck from components, use the provided protractors — as outlined in our installation article — and all should be well. In reading reviews etc, look for a figure less than $\pm 2^\circ$.
- Adjustments: Take all you can get! The ability of a pickup system to operate at maximum efficiency depends upon its mechanical accuracy and alignment. A deck which allows you more freedom to 'tinker' probably also offers more chance to set it up correctly and thus earn a better sound quality!

Cartridges

Compliance: A measure of the 'springiness' of the cantilever assembly that holds the stylus, ie how easily it bends! This is a good thing as far as following the record groove goes, but a bad thing when it comes to moving the weight of arm and cartridge along behind it. Thus there is no right or wrong value. High compliance means 'easily bent' and should be used only with low-mass arms. Compliance is measured in 'cu' (compliance units). Anything above 30 cu is high and anything under 15 cu is low. Shure moving-magnet pickups average 30-40 cu and the best moving-coils under 10 cul A high arm mass is anything over 15 grams, with anything less than 10 grams being considered low mass. Read back over the section on effective mass and take a look at Table One, which illustrates the interaction between these two parameters.

- Tip-Mass: Is the weight of the actual stylus as seen by the groove walls! This will determine record wear — and how well the stylus can stay in the groove at high frequencies, since there will be a second resonance here somewhere above 15 kHz. The higher this resonance (lower tip mass) the better, to some degree — suspect any figure less than 20 kHz!
- Output Level: There is no figure current for how much voltage a cartridge should generate; it will depend on the amp it is to feed. Figures are generally quoted in terms of millivolts output at 5 cm/sec recorded velocity. An average moving-magnet design will develop around 3 mV at 1kHz and a moving-coil substantially less. Look to match the quoted figure with the amplifier input sensitivity and you won't go far wrong!
- Frequency Response: As with amplifiers, a measure of 'flatness' or freedom from uneven treatment of an input. The cartridge should replay any frequencies between 20 Hz-20 kHz at an equal level. The limits (in dB) quoted with the figure — ignore it if there *are* no limits — show how close the unit comes to



The three most common stylus profiles and their relative parameters. Note that whilst the elliptical offers a greater ability, its area of contact will generate increased record wear.

Features



meeting this requirement. Look for ± 2 dB maximum across 20 Hz-20 kHz.

Distortion Figure: As the cartride is a transducer, it will impart some distortion to the signal during its transformation. Figures generally quoted are for Intermodulation Distortion — how much one note will effect another when replayed simultaneously — and Total Harmonic Distortion, which is the degree to which a pure sine wave going in is less than pure coming out! Look to better 2% on all distortions figures.

Cash Considerations

With an integral deck, assign 30 percent of your budget to the record player and cartridge. As separates will initially be more expensive, assign 35 percent of the total if you choose this option. The extra comes from the speaker allowance, on the grounds that, as you are in the upgrading game anyway, you will wish to improve them later on. The extra cash will make more audible difference at the source, initially.

Arms And The Man

Integrated decks offer the advantage that they require little, if any, setting up. Generally speaking, there is little the user can adjust, except the cartridge alignment in the headshell. If you have decided on such a machine then read carefully through the adverts in the hi-fi press from the larger dealers. Many of them run package deals, at very attractive prices, which comprise either an integrated deck with a good cartridge or even separate turntable/arm/cartridge set-ups, pre-assembled and prechosen to make things easy!

In just about every case, a Far Eastern machine will arrive with a pre-fitted cartridge. Throw it out! (or, at best, save it for a spare). Such offerings are usually of little value compared to the deck itself and are one reason why many dealers offer the aforementioned deals. Choose your own cartridge following the dealer's advice as to compatibility with the selected deck. If in doubt, ring up the manufacturer of the turntable and ask them whether your proposed cartridge is compatible. You'll be surprised at how helpful hi-fi companies can be! Separate disc-playing components are more trouble to choose, but offer much greater flexibility — and quality — later on. The problem is made irrelevant to some extent by the scarcity of good quality turntables, without an arm, at anything less than a king's ransom. No matter what the advertising may tell you, spending £400 on a turntable in a £600 system is sheer lunacy. It makes sense only if you're selling turntables! Given the level of other components in the system it would be impossible to distinguish, say, the Oracle at £680 from the TD 160 BC at £110. Keep a sense of proportion.

It is absolutely essential that you hear the cartridge you want together with your proposed loudspeakers. These two components are the ones most likely to possess a strong 'character', or sound of their own.

For example, a number of budget loudspeakers can sound a trifle dull and lifeless, while still being good value for the money. Partnering these with a bright sounding cartridge can produce an overall result which is pleasing and more accurate.

It doesn't matter which you fix on first, speaker or cartridge, but choose them together. You may, for instance, decide that because space in the home is limited, you need compact enclosures of below a certain size. Once more, make up a shortlist and audition a few with the same cartridge. Then get the cartridge changed. After a few minutes the combination which appeals to you most will become apparent.

Pick Up Pickups

With the advent of the new generation of moving-coil cartridges and their higher outputs, it is feasible to use such a device in a first system. However, don't be tempted to buy a cartridge simply because it is a moving-coil unit. The mode of operation is totally irrelevant; it is the sound that matters and if you prefer some other type of unit, go buy it.

By all means consider specification seriously, especially with regard to matching up units, but don't let one single line of ad copy or formulae decide which hi-fi you buy. Let your ears do the choosing for you! This is especially important when it comes to loudspeakers, as we shall see next month.

Ŕ

7400 7401 7402	11p 11p	74367 5 74368 5 74390 10	5p 401 5p 401 0p 401	4 60 5 60 6 30	P LINEAR I.C P AN103 P AY1-0212	s 200p 600p	MB3712 MC1310P MC1458	250p 150p 40p	CO	MP	UTER	co	мро	NEN	TS	CONNECT	OR SYSTEMS
7403 7404 7405 7406	12p 12p 18p 25p	- 74490 12 74LS SERIES 74LS00 1 74LS01 1	0p 401 401 2p 402	8 60 9 32 0 60 1 65	P AY1 1313 P AY1 1320 P AY1 5050 P AY3 8910 P AY3 8912	320p 140p 600p	MC1495L MC1496 MC3340P MC3403 MC3403	350p 70p 120p 120p	CPUs 1802CE	700p	6847 9365	E10 INT	ERFACE IC	wD1691 WD2143	£15 550p	Single end Double end	le with Headers 14pin 16pin 24pin 40pin 145p 165p 240p 380p 210p 230p 345p 540p with Sockata
7407 7408 7409 7410	25p 14p 15p 15p	74LS02 1 74LS03 1 74LS04 1 74LS05 1	4p 402 4p 402 5p 402 5p 402	2 70 3 20 4 40 5 20	P AY5 1224A P AY5 1315 P AY5 4007D P CA3028A	240p 600p 520p 120p	ML920 MM57160 MN6221A NE531	800p 620p £6 150p	6300 6502A 6300 6802	450p 600p : 370p ! 426p	2101A 40 2102 2L 12 21078 50 2111A 30	AD: 0p AM 0p AM 0p AM	561J E14 25\$10 350p 26L\$31 160p 26L\$32 190p 290 E20	22,768KH 100KHa	ALS 2 180p 300p	Single and (24") Double and (18")	20pin 26pin 34pin 40pin 160p 210p 270p 300p 290p 385p 490p 540p
7411 7412 7413 7414 7416 7417	20p 20p 22p 35p 25p 25p	74LS08 1 74LS09 1 74LS10 1 74LS11 1 74LS13 2 74LS14 4	6p 402 5p 402 5p 402 5p 402 5p 402 5p 403 0p 403	5 130 7 32 8 60 9 75 9 40 1 170	P CA3019 P CA3046 P CA3048 P CA3069 P CA3069 P CA30806 P CA3086	80p 70p 225p 300p 72p 48p	NE555 NE556 NE564 NE565 NE566 NE566 NE567	20p 50p 420p 130p 155p 146p	6809 6809£ 8035 8039 8080A 8085A IN\$8060	£10 £15 750p 850p 350p 550p £11	2112 A 30 2114 2L 16 2114 4L 13 2147 45 4027 3 30 4044 45 45	0p DM 0p DP8 0p DS8 0p DS8 0p DS8 0p DS8	8131 375p 1304 450p 1302 250p 1832 250p 1833 225p 1836 150p 1838 225p	200K Hz 1 0MHz 1 008MH 1 8432M 2 00MHz 2 45760N 3.276MH	300p 320p 12 350p H2 250p 250p AMz250p 2 150p	IDC CO 1 Header plug Receptacle	NNECTORS 0 26 34 40 Way Way Way Way 90p 200p 240p 270p 90p 200p 240p 270p
7420 7421 7422 7423 7425	30p 20p 22p 28p	74LS20 1 74LS21 1 74LS22 1 74LS26 1 74LS26 1	5p 403 5p 403 6p 403 6p 403 6p 403	5 295 295 295 5 55	CA3089 CA3090AQ CA3130E CA3140	225p 375p 90p 50p	NE570 NE571 NE5534A PLL02A	425p 425p 250p 500p	TM \$9980 280 280A 8088	220 370p 450p £19	4116-15 20 4116-20 200 4118-3 500 4118-4 450 4164-2 1		1488 55p 1489 55p 3418 950p 3446 300p	3.5795MH 3.686MH; 4.00MHz 4.194MH; 4.43MHz	12 100p 2 300p 150p 2 200p 150p	EUROC	ONNECTORS Plug Skt Way 300p 350p
7426 7427 7428 7430	30p 25p 30p 15p	74LS30 1 74LS32 1 74LS37 1 74LS38 1	5p 404 5p 404 5p 404 5p 404	70; 55; 60; 70;	CA3160E CA3161E CA3162 CA3189E CA3240	100p 140p 450p 300p 120p	RC4136 RC4151 S5668 SAD1024A SFF96364	200p 260p 1250p 800p	SUPPO DEVICE 3242 3245	B00p 450p	6116P 3 654 6514-45 6610 200 7489 210 7489 210	p MC Dp MC Dp MC Dp MC p MC	3480 850p 3486 500p 4024 325p 4044 325p 14411 700p	5 00MHz 6 0MHz 6 144MH 7 0MHz 7 168MH	175p 150p 2 250p 150p 2 175p	Angled 2 x 32 Wi DIN 41617 31 Wa (for 2 x 32 Way A	ay - 400p ly 200p 200p please specify A + B or + C type)
7432 7433 7437 7438 7440 7441	25p 27p 30p 17p 70p	74LS42 9 74LS47 4 74LS51 19 74LS55 34 74LS73 29 74LS74 19	5p 4040 5p 4040 5p 4045 5p 4050 5p 4050 5p 4051	75p 55p 27p 27p 60p	CA3280G DAC1408 8 HA1366 HA1388 ICL7106	200p 200p 300p 270p 850p	SL490 SN76477 SP8515 TA7120 TA7204 TA7205	350p 175p 200p 250p 250p	6522 6532 6821 6851 6821 6845	500p 775p 160p 650p 160p £10	745201 350 745289 325 ROMs/PRON	MC MV ULP ULP AS 750	4044 325p 158174 f12 12003A 100p 12004A 100p 17 160p 10 160p	8 00MHz 8 86MHz 10 00MH 10 7MHz 16 00MH 18 00MH 18 432	175p 175p 2 250p 150p 2 250p 2 200p 150p	DIL HEA 1 Solder type IDC type	DER PLUGS 4pin 16pin 24pin 40pin 50p 60p 100p 275p 130p 140p 200p 285p
7442A 7443 7445 7446A 7448	36p 90p 60p 93p 45p	74LS75 24 74LS76 20 74LS83 40 74LS85 69 74LS85 69	4052 0p 4053 5p 4054 5n 4055 0p 4056	80p 60p 130p 125p 120p	ICM7555	80p 400p 400p 160p	TA7222 TA7310 TA621 TBA651	200p 200p 275p 200p	0847 3850 1052 1875 3154	£10 160p 250p 600p 950p	74S188 325; 74S287 308; 74S288 226; 74S387 325; 74S387 325; 74S471 650;	p 751 p 751 p 751 p 751 p 751	12 160p 14 160p 15 160p 50P 140p 54 140p	19 968MI 26 690MI 27 145MI 38 6667N 48 0MHz	Hz 150p Hz 150p Hz 200p Hz 200p 1Hz 175p 175p	MINIATURE	D-CONNECTORS Male Fe
7450 7451 7453 7454	17p 17p 17p 17p	74LS90 21 74LS92 44 74LS93 30 74LS95 4	8p 4059 0p 4060 0p 4063 5p 4066	500p 90p 100p 35p	LF351 LF353 LF356P LF357	48p 100p 95p 120p	TBA800 TBA810 TBA820 TBA950 TCA220	90p 100p 90p 300p 350p	8205 8212 8216 8224	220p 160p 160p 250p	745473 850 745474 650 745570 650 745571 650 745573 950	P 751 P 753 P 753 P 753 P 753 P 753	82 230p 24 375p 51 150p 53 150p 55 150p	55.5MHz 116.0MH	400p 300p	Solder Bucket Solder Pin Solder Pin (angle Top entry/side e	200p 245p 215p 265p ed) 265p 310p
7460 7470 7472 7473 7474	36p 30p 30p 20p	74LA96 10 74LS107 4 74LS109 3 74LS112 34 74LS112 34	0p 4067 5p 4068 0p 4069 1p 4070 4071	400p 18p 18p 18p	LM301A LM310 LM318 LM319	425p 27p 120p 200p	TCA940 TDA1004A TDA1008 TDA1010	175p 300p 320p 225p	8228 8243 8250 8251	250p 450p 850p 350p	EPROMs 1702A 500 2708 300	754 754 754 P 8T2 P 8T2	51 2 72p 53 4 72p 91 2 70p 6 120p 18 120p	ENCOL AY 6 237 74C922	0ER 16 700p 500p	hood Locking lever & Counterpart	100p 100p
7475 7476 7480 7481	30p 30p 50p 100p	74LS114 30 74LS122 42 74LS123 50 74LS124 120	p 4072 p 4073 p 4075 p 4076	18p 20p 20p 60p	LM324 LM335Z LM339 LM348	45p 140p 65p 75p	TDA 1022 TDA 1024 TDA 10348 TDA 10348 TDA 1170	600p 120p 250p 300p	8255 8255 8257 8259 8259	800p 350p 800p 800p 950p	2716 (+ 5V) 300 2564 (3 2516 (+ 5V) 300 2532 600 2732 600	p 819 6 819 P 81L P 81L P 81L	5 120p 7 120p \$95 90p \$96 120p \$97 90p	MOOUL 6MHz UH 8MHz UH	ATORS F 375p F 450p	DiL SWITCH 4 way 90p 8 way 1 1M6402 450p TR1602 350p	20p 24 pin £6 28 pin £7 40 pin £11
7482 7483A 7484 7485 7485	70p 45p 100p 90p 20p	74LS125 30 74LS126 30 74LS132 45 74LS133 30 74LS133 30	p 4081 p 4082 p 4086 p 4086 p 4089 p 4089	16p 20p 72p 150p	LM358P LM377 LM380 LM381AN	75p 175p 75p 180p	TDA2020 TL071/81 TL072/82 TL074	320p 320p 45p 75p 130p	2804P10 2804P10 280CTC 280ACTC 280ADART	300p 350p 300p 350p 800p	UARTSs AY 3-1015P 300 AY 5-1013P 300 IM6402 450	963 9 2N4 9 2N4	S98 120p 2 220p 7AP 160p 125E 8 350p 126E 8 350p	BAUD R GENER/	ATE	EDGE C	ONNECTORS 0.1" 0 156" - 150p 310p 170p
7489 7490A 7491 7492A	210p 25p 60p 30p	74LS138 34 74LS138 34 74LS139 36 74LS145 75 74LS147 160	4094 4095 4026 4026 4097	150p 95p 95p 340p	LM386 LM387 LM389 LM393	95p 120p 95p 120p 95p	TL084 TL094 TL170 TL430C	110p 200p 50p 70p	ZBOS 101 CRT CONTROL		CHARACTER		127E 8 650p 128E 8 500p	MC 14411	E7 KT ICs	2 × 23 Way 2 × 25 Way 1 × 43 Way 2 × 43 Way	335p 210p 200p 260p 350p
7493A 7494 7495A 7496	30p 50p 45p	74LS148 90 74LS151 70 74LS153 60 74LS154 90	p 4098 p 4099 p 4008 p 4009 p 4009	90p 120p 90p £120p	LM394 LM709 LM710 LM711	350p 36p 50p 70p	UA2240 UDN6118 UDN6184 ULN2003	300p 320p 320p	COM5037 SF96364 TMS9927 6845	£18	GENERATOR RO 3 2513UC 750 RO 3 2513LC 700 SN74S262AN £1	5 DISC 9 FD17 9 FD17	71 £2 91 £3	0 SAA5030 SAA5040 O SAA5050	1 £16 £9	ACOR	
74100 74107 74109 74116 74118	85p 22p 40p 90p 75p	74LS155 40 74LS156 40 74LS157 35 74LS158 36 74LS160 40 74LS161 40	p 4010 p 4010 p 4010 p 4010 p 4010 p 4016	180p 180p 45p 100p	LM733 LM741 LM747 LM748 LM2917 LM3302	100p 18p 70p 35p 200p 140p	UPC575 UPC592H UPC1156H XR2206 XR2207 XR2211	400p 200p 300p 300p 400p	LOW PROF 8 pin 9p 14 pin 10p 16 pin 11p	18 pi 20 pi 22 pi	SOCKETS BY TEX n 16p 24 pin 2 n 18p 28 pin 2 n 22p 40 pin 3	AS WIRE 4p Bpi 6p 14 pi 0p 16 pi	WRAP SOCI n 25p 18p n 35p 20p n 40p 22p	(ETS BY TEX in 50p 24 in 60p 28 in 65p 40	AS pin 70p pin 80p pin 100p	Basic 2K + 8K Kit Fully Expanded 12 P8 P.S.U. £1 ACORN SDFT	£120, Built £150 2K + 12K £198 P £3.00 0.20 P&P £1.00 WARE AVAILABLE
74119 74120 74121 74122 74123	90p 70p 25p 45p	74LS162 40 74LS163 40 74LS164 48 74LS165 100 74LS166 90	p 4017 p 40174 p 40175 p 40193 p 40257	120p 90p 100p 120p 160p	LM3900 LM3909 LM3911 LM3914	55p 95p 130p 210p	XR2216 ZN414 ZN419C ZN423E	675p 90p 225p 150p	TRANSIS AD161/2 BC107/8 BC109	45p 13p 14p	8FX84 5 40p BFX86 7 30p BFX88 30p BFX89 180p	TIP33 TIP33 TIP34 TIP34 TIP34	A 90p C 114p A 115p C 160p	2N3054 2N3055 2N3442 2N3553	65p 48p 140p 240p	3N140 120p 3N141 110p 3N201 110p 3N204 120p	ZENERS 2.7V-33V 400mW 9p 1W 15p
74125 74126 74128 74132	40p 40p 40p 45p	74LS170 120 74LS173 70 74LS174 45 74LS175 50	P 4502 4503 4507 P 4508	70p 50p 40p 200p	LM3915 LM3916 LM13600 M51513L	225p 225p 125p 300p	2N424E ZN425E ZN427E ZN1034E	135p 350p 625p 200p	BC147 8 BC149 BC157 8 BC159 BC159	20p 9p 10p 10p 11p	8FY50 24p 8FY51 2 24p 8FY56 33p 8FY56 30p 8FY90 80p 8RY39 45p	TIP35 TIP36 TIP36 TIP41	C 290p A 270p C 340p A 65p	2N3584 2N3643 4 2N3702 3 2N3704 5 2N3706 7	250p 48p 12p 12p 14p	40290 2000 40361 2 75p 40408 90p 40409 100p 40410 100p	TRIACS PLASTIC 3A 400V 60p 6A 400V 70p
74136 74141 74142 74145 74145	32p 65p 200p 70p	74LS181 140 74LS190 50 74LS191 50 74LS192 50 74LS192 48	p 4510 p 4511 p 4512 p 4514 p 4515	50p 65p 150p 150p	VOL	FIXED PL	GULATORS ASTIC	700p	BC172 BC177 R BC179 BC182/3 BC184	12p 12p 12n 18p 10p 11p	BU104 2256 BU105 1906 BU108 2500 BU108 2500 BU109 2250	TIP42 TIP42 TIP54 TIP54 TIP12	A 70p C 82p 160p 0 75p	2N 3708 9 2N 3773 2N 3819 2N 3820 2N 3823	12p 300p 25p 50p 70p	40594 120p 40595 120p 40673 75p 40871 2 100p	6A 500V 88p 8A 400V 75p 8A 500V 95p 12A 400V 85p 12A 500V 105p
74148 74150 74151A 74153	75p 80p 45p 45p	74LS194 40 74LS195 48 74LS195 60 74LS196 60 74LS197 65	P 4516 P 4518 P 4520 P 4521 P 4521	75p 45p 70p 150p	5V 1A 12V 1A 15V 1A 18V 1A	7805 7812 7815 7818 7818	50p 7905 50p 7912 55p 7915 55p 7918	55p 60p 60p	BC187 BC212 3 BC214 BC237 BC327	30p 11p 12p 15p	BU125 150p BU180A 120p BU205 200p BU208 200p BU208 145p	TiP12 TiP14 TiP14 TiP14 TiP29	2 80p 2 130p 7 130p 56 78p	2N 3866 2N 3902 2N 3903 4 2N 3905 6 2N 4037	90p 700p 18p 20p 65p	DIODES BY127 12p BYX36 300 20p	16A 400V 110p 16A 500V 130p T2800D 130p
74154 74155 74156 74157 74157 74159	70p 50p 50p 50p	74LS221 60 74LS240 70 74LS241 70 74LS242 80	p 4526 p 4527 p 4528 p 4532 p 4534	75p 90p 75p 90p 500p	5V 100mA 12V 100mA 15V 100mA	78L05 78L12 78L15	30p 79L05 30p 79L12 30p 79L15	65p 70p 70p	BC337 BC338 BC461 BC477 8 BC477 8	16p 16p 25p 30p	BUX80 Lt BUY69C 350p E310 50p MJ802 (4 MJ2501 225p	TIS93	20 70p 30p 08 12p 00 13p 52 45p	2N4123 4 2N4125 6 2N4401 3 2N4427 2N4871	27p 27p 27p 90p 60p	OA90 91 9p OA95 9p OA200 9p OA202 10p	3A 400V 100p 8A 600V 140p 12A 400V 160p 16A 100V 180p
74160 74161 74162 74163	60p 60p 60p 60p	74LS244 65 74LS245 90 74LS251 40 74LS253 40	P 4536 P 4538 P 4539 P 4543 P 4543	300p 120p 110p 100p	LM309K 1A 5V LM317K LM317T 1A Ad LM337T	ATORS 135p 325p 200p 225p	78HGKC 78H05KC 78MGT2C 78GUUC	600p 550p 140p	BC5478 BC548C BC549C BC557B BC559C	16p 9p 18p 18p	MJ2955 90F MJ3001 225F MJ4502 E4 MJE340 60F MJE2955 100F	ZTX5 ZTX5 ZTX5 ZTX5 ZTX6	02 16p 04 30p 52 55p 52 60p	2N5087 2N5089 2N5172 2N5191 2N5194	27p 27p 27p 90p 90p	1N916 7p 1N4148 4p 1N4001 2 5p 1N4003 4 6p 1N4005 6p	10A 400V 1800 BT106 110p C106D 45p MCR101 36p T1C44 27p
74164 74165 74166 74170 74172	50p 55p 70p 140p 300p	74LS257 45 74LS258 45 74LS259 90 74LS260 100 74LS266 25	p 4555 p 4556 p 4560 p 4568	50p 60p 180p 300p	LM323K 3A 5V LM723 150mA TL494 78540	500p Adj 37p 400p 300p	79GUIC 79HGKC TL497 LM305AH	225p 700p 300p 250p	BCY70 BCY71 2 BD131 2 BD135 6 BD139	18p 22p 50p 40p	MDE3025 700 MPF102 406 MPF103/4 406 MPF105 306 MPSA06 306	VN66 VN10 VN66 2N69	80p KM 60p 80p 7 25p	2N5245 2N5298 2N5401 2N5457 8 2N5459	40p 65p 60p 40p	1N4006-7 7p 1N5401 3 14p 1N5404 7 19p 1S920 9p	2N3525 130p 2N4444 140p 2N5060 34p 2N5064 40p
74173 74174 74175 74175	65p 60p 60p 50p	74LS273 75 74LS279 451 74LS283 451 74LS298 1601	p 4569 p 4572 p 4683 p 4684	180p 30p 90p 45p	OPTO ELECTR 2N5777 OCP71 ORP12	ONICS 45p 180p 120p	ORP60 ORP61 TIL78	120p 120p 55p	BD140 BD189 BD232 BD233 BD235	40p 60p 95p 75p	MPSA12 50p MPSA13 50p MPSA20 50p MPSA42 50p MPSA43 50p	2N69 2N70 2N70 2N91 2N93	8 45p 6A 30p 8 30p 8 45p 0 18p	2N5460 2N5485 2N5875 2N6027 2N6052	44p 250p 48p 300p	BRIDGE	MOUNTING RELAYS 6 or 12V DC coil SPDT 2A 24V DC
74178 74178 74180 74181 74182	100p 50p 160p 90p	74LS323 250 74LS324 150 74LS348 150 74LS352 100 74LS353 100	14495 745 S	400p	ILD74 MCT26 MCS2400 ILQ74	0RS 130p 100p 190p 240p	TIL111 TIL112 TIL113 TIL116	90p 90p 90p 90p	BD241 BD242 BD677 BF244B BF256B	70p 70p 40p 35p 70p	MPSA56 32p MPSA70 50p MPSA33 40p MSPU06 63p MPSU07 60p	2N11 2N16 2N17 2N21 2N21	31 2 36p 13 25p 11 25p 02 70p 60 350p	2N6059 2N6107 2N6247 2N6254 2N6290	325p 65p 190p 130p 65p	1A 100V 20p 1A 400V 25p 1A 600V 30p 2A 50V 30p 2A 50V 30p	6 or 12V DC cori DPDT 5A 24V DC/240V AC 200p 6 or 12V DC Cori SPDT 10A 20V
74184A 74185 74186 74188	90p 120p 500p 325p	74LS363 1600 74LS364 1600 74LS365 360 74LS367 360	74500 74504 74508 74532 74532	60p 60p 75p 90p 90p	LEDS 0.125 TIL32 TIL209 Red	55p 11p	0.2 TIL220 Red TIL222 Gr TIL228 Yel	12p 15p 22p	BF257 8 BF337 BFR39 BFR40 1 BFR40 1	32n 30p 25p 25p	MPSU45 90 MPSU65 78 TIP29A 40 TIP29C 55 TIP30A 48	P 2N22 P 2N22 P 2N23 P 2N24 P 2N24 P 2N26	19A 25p 22A 25p 89A 25p 84 30p 46 45p	2SC1172 2SC1306 2SC1307 2SC1957 2SC1969	150p 150p 90p 195p	2A 400V 45c 3A 200V 60p 3A 600V 72p 4A 100V 95p	DC/240V AC 2250
74190 74191 74192 74193 74194	50p 50p 50p 12p	74LS268 36p 74LS373 70p 74LS374 70p 74LS375 50p 74LS377 90p	74585 74586 74512 74513	300p 180p 300p 160p	TIL211 Gr TIL212 Ye TIL216 Red	16p 18p 18p	Rectangular LEDs (R, G, Y) NSB5881 TIL311 TH 212/2	30p 570p 600p 110p	BFR90/1 BFR96 BFX29 BFX30	25p 180p 40p 30p	TIP30C 60 TIP31A 58 TIP31C 62 TIP32A 68 TIP32C 62	2N29 2N29 2N29 2N29 2N29 2N30	04/5 30p 06A 30p 07A 30p 26 9p 53 30p	25C2028 25C2029 25C2029 25C2078 25C2335 25C2612 3N128	250p 250p 250p 120p	6A 50V 80p 6A 100V 100p 6A 400V 120p 10A 400V 200p 25A 400V 400p	Size 2 ¹ /2" 64R 80p 2 ¹ /2" 8R 80p 2" 8R 90p
74195 74196 74197 74198 74199	12p 14p 14p 14p	74LS378 70p 74LS390 55p 74LS393 50p 74LS393 200p	74513 74513 74513 74515 74516	225p 225p 250p 300p	3015F DL704 DL707 Red FND357	200p 140p 140p 120p	TIL321/2 TIL321/2 TIL330 7750/60 DRIVERS	130p 140µ 200p				* AD	D SOUNO '	TO YOUR 2	X80/81	*	11/2 8R 100p
74221 74251 74273 74278	14p 70p 75p	74LS540 135p 74LS541 135p 74LS670 170p 4000 SERIES 4000 12	745174 745175 745194 745241	250p 320p 350p 450p	FND500 FND507 MAN3640 MAN4640	90p 90p 175p 200p	9368 9370 UDN6118 UDN6184	250p 300p 340p 320p	Port mo from sw	dule pi	ugs directly into photocells, joy	(As ZC80 or a sticks, e	published in X81 to provide and con	PCW Oct/ ide 8 input trol of up t	Nov 81) and 8 out o 8 relays	out lines. These a . Also 7-segmen	llow input of data t LED displays or
74279 74283 74284 74285	80p 75p 200p 200p	4001 140 4002 150 4006 650 4007 160	211	* SP	PECIAL 1-24	OF 25	FER #	0+	LED lam	nps ma 81 owi boardl	y be used and so output may be ners, we provide	olid-state e produce e <i>an exte</i>	buzzers man d. Ready bu ender card t	y be directly iilt & tested o accept th	End RAM p	ed to the port. Va P&P 70p + VA1 back so no need leprints of PCW a	for an expensive articles 75p + SAE
74290 74293 74298 74365 74366	100p 100p 100p 55p 55p	4008 60 4009 35 4010 40 4011 14 4012 16	271	6	2.25 4.50	24	.95 (.10 2 .00 3	2.00 3.75	The mo	10	*	(As pu	DPROCE	SSOR 1	RAINE Id Jan 811	R *	
TF	C	4013 35		-200n			.75 (0.70	PIA, 6 di as deskt dedicate	lgit dis op con d conti	play and up to 8 hputer and a sol of or calculator a	monitor ftware de applicatio	commands. velopment	Though de tool. The s	signed as	a trainer Nandco OM space allows	modification for
MAIL O	RDE	RS TO: 17 17 BURNL	BURNI EY RO	LEY RO	AD, LONI	DON N V10	W10 1ED		NR HRCI.	dil COI	PLEASE	ADD	40p P&P	8 15%	VAT (E	xport no VA	T)
	(3	(Tel: 01-45 805, EDGE	2 1500, WARE	01-450 ROAD	6597. Tele	x: 9220 W2 T	300 el: 01-723	0233			Govern	ISA &	ACCES	S, etc. O	S ACC	EPTED	-

Projects

MASTHEAD AMPLIFIER

A special project for campers or caravanners who like to watch their portable TV when away on holiday trips, but find that it's sometimes difficult to get good TVreception

WE APPRECIATE that it's not always possible to pick up a good TV signal from a set-top TV aerial because so much depends on distance from the nearest TV transmitter and the local terrain. If you find, when you're on holiday trips, that your TV picture often suffers from a weak signal then you may be interested by this project.

Given the right conditions, the HE Aerial Preamplifier can increase the size of the signal picked up by your aerial and thus improve the signal-to-noise ratio, allowing a good picture to be displayed. Of course, if the aerial signal is *too* small, no amount of amplification will do the job. However, the improvements which our project offers will certainly help you to maintain good reception in all but the poorest areas.

As you can see from the description in How It Works, the OM335 has a bandwidth which extends down to VHF frequencies. Consequently this preamplifier may also be of interest to people who have problems with FM radio reception.

Any voltage within the range of 10 V to 24 V will power the preamplifier, so a car battery - the same one used to run the TV - is ideal. We haven't given a circuit diagram of the project, because the circuit is so simple: a single ICI All the components which make up the circuits - the capacitors, resistors and transistors - are contained within the IC's body. The IC is what's known as a hybrid IC (the term 'hybrid' tells us that it is made up of individual discrete components), and no other components are required to build up the project. Figure 1 shows the pin configurations of the IC.



Figure 1. Pin configuration of the OM355 IC, with a cross-section through the board showing pins 2, 3, 5 and 6 soldered both sides.



Make sure the body of the IC fits as close to the board's surface as you can get if before soldering it in and DON'T OVERHEAT THE DEVICE! Solder one pin at a time, then let it cool for a few minutes before soldering the next. Figure 2 shows the PCB overlay. The PCB is double-sided (ie, there is a copper foil pattern on both surfaces) so make certain you insert the IC in to the correct surface.

The upper copper surface (the ground plane) should be at 0 V, which is achieved by soldering pins 2,3,5 and 6 on both sides of the board. Use good quality 75R co-axial cable to connect between the board and the co-axial sockets. Solder a short length (about 2") of cable to each end of the board — screen to the outside earth, as shown in **Figure 2** and the signal or centre lead of the cable to the centre connection of the Solder bridges across tracks.

Now wire up the power lead from the board to the switch and out of the box. Make sure you get the leads the right way round.

Construction

Mark and drill the die-cast box to fit the switch, the grommet, the two co-axial sockets and the PCB mounting bolts.

Use the PCB exactly as shown and follow the instructions carefully. This is important because high-gain, highfrequency amplifiers can cause interfering oscillations if they aren't correctly mounted. The PCB foil pattern is specially designed to prevent oscillation and *must* be used — and don't forget the ground plane connections on the component side of the board!

Mount the complete, wired PCB into the case and onto the mounting bolts.

Solder the two co-axial leads to their corresponding sockets, bolt on the bottom of the box and you're ready to go.

Figure 2. Component overlay.



How It Works

Integrated circuit IC1 is a wideband amplifier, the gain of which is about 18 times. Any signal picked up by the aerial within the frequency range of 50-900 MHz is amplified by the IC - thus all standard British 625-line TV transmissions are covered.

The actual theory behind the operation of a TV preamplifier is complex, but can be simplified in general terms. In effect, any amplifier is only as good as the input signal if the signal is noisy then the amplifier output will also be noisy, only bigger.

In the case of an amplifier fed by a long input lead (which adds noise), the output signal is a combination of equally amplified signal plus noise. If, however, the amplifier is at the other end of the lead (ie, before the noise occurs) then the signal is amplified but not the noise. This means that the signal is proportionally larger than the noise and we can say that the signal-to-noise ratio has increased.

Connecting The Preamplifier

Figure 3 shows the example of how the preamplifier may be connected if the TV has an existing set-top aerial.

If your portable TV aerial is mastmounted (as is sometimes the case in fixed caravan sites), Figure 4 shows suitable connection details.



Best-possible performance will be obtained when the preamplifier is mounted as close to the aerial as you can get it. Therefore, if you do have a mast-mounted aerial, it is advisable to mount the preamplifier at the top of the mast as well. For outside use the box should be mounted upside down and the edges sealed with waterproof sealant.

Incidentally, if you live in a poor TVreception area and the aerial on your roof isn't able to pick up strong enough signals to allow a good TV picture, then you may find this project can help. Mast-mounting the preamplifier (or perhaps putting it in your attic) as close as possible to the aerial and powering it from a mains-to-DC supply could give you a much improved picture signal.

Parts List

OM335 wideband amplifier

single-pole, single-throw

toggle switch





Figure 5. Top (upper diagram)and bottom (lower) PCB foil patterns, viwed from the top and bottom, respectively.

	THE	-								_
ľ	THIS MONTH	SNE	vv	KI	15	-		-		
	For the musically int Drum Synthesiser Mixer/Pre Amp Stylus Organ	lined								£29.50 £16.00 £4.95
	For the Service Engi Micro Volt Multiplie Sign Wave Generator Linear Power Output	neer r t Mete								£3.95 £5.75 £11.50
	For the Ham or CB Aerial Rotator Aerial Direction Ind	Enthus	iast							£24.50 £5.90
	For the Motorist Electronic Ignition	Kit .								£19.50
	For all of you Electric Jigsaw Puza Blow Heater Kit	te .								£5.30 £6.45
	And if you are havin High-Pass Filter Low-Pass Filter	ng TV I	Inti	erte:	reni	ce P	rot	larr	15	£1.95 £3.45

UNIVAC KEYBOARD BARGAIN

Ideal for use with ZX80/81. Has 50 keys and many other part for your sparse box. Probably cost in excess of £100. In very good used condition - £13:50 + £2.00 post. Diagram showing how to connect to ZX80/81 - £2.00 extra. other parts

COMPUTER DESK .



Size approx, 4'x 2' x 2'6'' high. These were made for hard work, the top being formica covered. Suitable for housing instruments or for use as office desks. Beautifully made, these cost over £100 each, our price only £11.50 each, however, you must arrange to collect.

EXTRACTOR FANS

- Mains operated ex. Computer 5" Woods extractor £5.75 Post £1.00 6"
- Woods extractor £8.90 Post £1.25 6" Plannair extractor £7.50 Post £1.00 4" x 4" Muffin 115v, £4.50 Post 50p, 4" x 4" Muffin 230v, £5.75 Post 50p.

INTERRUPTEO BEAM

IN LENKUPIED BEAM This is tenables you to make a switch that will trigger wh steady beam of infra red or ordinary light is broken. Mair ponents – relay, photo transistor, reistors and caps, etc. Circuit diagram but no case. Price £2.30 when a Main com

INSTRUMENT BOX WITH KEY

Very strongly made (ply-wood sides with hard hoard top and bottom). This is black grained effect, why! covered, very-pleasing appearance. Internal dimensions (2%) long, 4%' wide, 6' deep. Ideal for carrying your multi range meter and small tools and for keeping them in a safe place. £2,30. Post paid if ordered with other goods, otherwise £1.00.

ROPE LIGHT

A sets of coloured lamps in translucent plastic tube arranged to give the appearance of a running or travelling light. With variable speed control box, ideal for disco or shop window display. Complete, make up, ready to plug into mains. £36.00 + £2 post.

COMPUTER KEY SWITCHES (make your own keyboard)



fincluding tops

OUR CAR STARTER ANO CHARGER KIT has no doubt saved OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from meharrassment in an emergency ou can star-car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or teave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post. you can start the shelf in the

GPO HIGH GAIN AMP/SIGNAL TRACER. In case measuring only 5% in x 3% in x 1% in is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, With a radio it functions very well as a signal tracer. By connect a simple coil to the input socket a useful mains cable tracer can made. Runs on standard 4% battery and has input, output sock and on-off volume control, mounted flush on the top. Many oth uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80ohm earpiece 69p. he ut sockets



3 CHANNEL SOUND TO LIGHT KIT



3 CHANNEL SOUND TO LIGHT KIT Complete kit of parts for a three-channel unit controll-ing over 2000 watts of light-ing over 2000 watts of light-ing due this a thome if you wish but if is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metai case and has controls for each channel, and a master on/off. The audio input and output are by 4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connect-ing lamps. Special snip price is £14.95 in kit form or £25.00

MULLARD UNILEX

MOLLARD UNILLS A mains operated 4 + 4 stereo system, Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy to assemble modular form this should sell at about £30 - but due to a special bulk buy and as an in-centive for you to buy this month we offer the sys-tem complete at only £16.75 including VAT and post. FREE GIFT - buy this month and you will receive a Goodman's eliptical B"x 5" speakers to match this amp onth and you will receive a pa

THIS MONTH'S SNIP



With it you can quickly test diodes, rectifiers, transist-ors, capacitors, check wiring and p.c. boards for open circuits, find the anode and cathode of a diocle or rectifier and whether a transistor is PNP or NPN, which are the base collector and emitter connections. Con-denses, if bad, give a continuous signal, but if good, give intermittent signals of varying length depending on their value. The test current is very low (2uA) and the voltage only 1.4v, so it is also possible to check MOS devices, as well as sensitive transitors without fear of damaging them. The unit is supplied complete with internal battery, which should last many months. Price £3.45p

THERMOSTAT ASSORTMENT

THERMOSTAT ASSORTMENT 10 different thermostats. 7 is metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses, appliance stats, one for high temp-eratures, others adjustable over a range of temperatures which could include 0 – 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an te stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15,00 – however, you can have the parcel for £2.50.

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 85p. High resistance headphones (gives best results) £3.75. Kit incluries chassis and from but not case.

TRANSMITTER SURVEILLANCE

nable conversation to be picked Tiny, easily hidden but which will enable conversation up with FM radio. Can be made in a matchbox all el parts and circuit. £2.30. (Not licenceable in the U.K.). all electronic RADIO MIKE

IN UT UNINE Ideal for discos and garden parties, allows complete freedom of movement, Play through FM radio or tuner amp. £6.90 comp. kit. (Not licenceable in the U.K.)

RAOIO STETHOSCOPE

Easy to fault find — start at the aerial and work towards the speak — when signal stops you have found the fault. Complete kit £4.95

MUGGER OETERRENT A high-note bleeper, push latching switch, plastic case and bath connector. Will scare away any villain and bring help. £2.50 cor plete kit.

POPULAR SNIP - STILL AVAILABLE

And it still carries a free gift of a desoldaring pump, which we are currently selling at 68.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least 6500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensors, multi-turn pots, recifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only **28.50**, which when you deduct the value of the desoldering pump, works out to just a little over 40 per panel. Surely this is a bargain you should not misl ould not miss! een ordering please add £2.50 post and £1.27 VAT





BURGLAR ALARM CONTROL PANEL

Contains labelled connection block, latching relay, test switch and removable key control switch. Simplifies the whole installation, all you have to do is to take wires to pressure pads and to alarm bell. Price £7.95, with complete diagram.

MINI MONO AMP on p.c.b., size 4"x 2

approx. Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be Included with the amplifier. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



Mains operated — defay can be accurately set with pointers knob for periods of up to 2%hrs. 2 contacts suitable to switch 10 amps - second contact opens a few min utes after 1st contact. £1.95.



TIME SWITCH BARGAIN

time aWITCH BARGAIN Large clear mains frequency controlled clock, which will always show you the correct time & start and stop switch-es with dials, Complete with knobs. £2.50.

LEVEL METER

Size approximately %" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 u.A. 75p.

WATERPROOF HEATING WIRE 60 ohms per vard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses — around water pipes, under grow boxes in gloves and socks.

TANGENTIAL BLOW HEATER

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as



istrated, 2.5 Kw ment, control switch and data all for £4.95. post £1.50

12V SUBMERSIBLE PUMP

Let gouint Englisher of the second se



VENNER TIME SWITCH VENNER TIME SWITCH Mans operated with 20 amp switch, one on and one off per 24 hrs, repeats daily automatically correcting for the lengthen-ing or shortening day. An expensive time switch but you can have it for only £2.95. These are with window £2.95. Also available is adaptor kit to convert this into a normal 24hr7 time switch but with the added advantage of up to 12 onf-olfs per 24hrs. This makes an ideal con-oller for the immersion heater. Price of the kit is £3.0. Post any or all items £1. adaptor kit is £2.30. Post any or all items £1.

12V FLUORESCENT LIGHTING

camping - car repairing - emergeny lighting is 12v battery you can't beat fluorescent ing. It will offer plenty of well TAR OF

lighting. It will off distributed light and is omical. W offer an inverter for 21" 13 watt miniature fluore cent tube. £3.45 dl

FIVE UNUSUAL SWITCHES

FIVE UNUSUAL SWITCHES For inventor, experimenters, service engineers, students or in fact anyone interested in making electrical gadgets. The parcel contains: – delay switch – motor drivers inwitch – two-way and off switch – polarity changing switch – and humidity switch. Our regular price for these switches bought separately is over £10, but this month you can have the 5 for £2,50.

SPIT MOTORS 0.4

These are powerful mains operated induction motors with gear box attached. The final shaft is a '%' rod with square hole, so you have alterna-ative couplingmethods – final speed is approx. Free/min, price £5.50. Similar motors with final speeds of 80, 100, 160 & 200r.p.m. same price.

COMPONENT BOARD **Ref. WO998**

Ref. WO998 This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 Jamp 400v types (made up in a bridge) B transistors type BC 107 and 2 type BFY 51 electrolytic condensers. SCR ref 2N 5062, 25 Out 100v OC and 100uf 25w DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

HAYWARDS HEATH, SUSSEX RH16 3QU. Stablished

BULL(Electrical) Ltd.

6 WAVEBAND SHORTWAVE RADIO KIT Bandspread covering 13.5 to 32 matres. Baved on circuit which appeared in a recent issue of Radio Constructor. Complete kit in-cludes case materials, six transistors and diodes, condensers, resist-ors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

MEDIUM & 2 SHORT WAVE CRYSTAL RADIO





MASTER ELECTRONICS NOW! The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a selfemployed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

- You will do the following:
- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type
 - of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



NewJob?NewCareer?NewHobby?Get into Electronics Now

OUR BROCHURE NAME

ADDRESS

COURSE IN ELECTRONICS IN INCLUENCE RADIO AMATE UR LICENCE MICROFROCESSORS LOGIC COLRSE

LICENCE OTHER SUBJECTS

British National Radio & Electronics School Reading, Berks. RG17BR.



This might show you a thing or two about how to recognise the good, the bad and the indifferent among soldered joints.

SOLDERING IS somewhat of an art and is essential to the successful construction of electronic circuits. The beginner particularly *must* learn to solder correctly to achieve success and avoid frustration.

Components are supported by a variety of methods and connections rely on the soldered joint. The solder is not meant to provide mechanical support.

Solder

Solder is an alloy of tin and lead that melts at fairly low temperatures. A joint

is made using solder as a filler and bonding agent. Soldering creates a continuous intimate contact between the solder and the metal surfaces by the mechanical interlocking of the solder with the irregular surface texture of the metals. This process is called 'wetting', as the solder flows onto and into the metal surfaces. The wetting of the metal surface by the solder is important in making a joint electrically and mechanically sound.

All metals oxidise, or tarnish, on the surface as a result of being exposed to air. This prevents the solder from wetting the metal surface, resulting in a poor joint; 'flux' is used to remove tarnish. For electronic work this is composed of resin (sometimes spelt rosin), which is obtained from the sap of pine trees plus additives called 'activators'. At soldering temperatures, the activators decompose, liberating an acid that dissolves the tarnish faster than pure resin. Other fluxes are also made for non-electronic uses, usually sheet-metal work, copper and brassware manufacture. These fluxes are usually highly corrosive (such as hydrochloric acid) and must *never* be

Features



Fig. 1. How the melting temperature and plastic range are affected by the relative percentages of lead and tin in a solder alloy. At the 'eutectic point', an alloy of 63% tin and 37% lead goes from the liquid to the solid state at 183°C without going through a plastic phase. This makes it very brittle, and different contraction rates of the parts of the joint cause the solder to fracture. A small plastic range, such as for 60/40 solder, prevents this.

used for electronics work as even minute amounts rapidly corrode component leads and printed circuit board tracks.

Solder for electronics work is made as different gauge wires. Most have a resin core along their length, some have up to five separate cores.

The resin core melts before the solder and flows onto the joint, wetting both the joint and the solder, excluding the air. At the same time the activators dissolve the tarnish on the surface, allowing the solder to flow freely and properly wet the joint. When the solder melts, the increase in temperature deactivates the flux, limiting the possibility of corrosion. It is important to thoroughly heat activated resin during soldering to ensure the complete decomposition of the activators, otherwise they remain corrosive at normal temperatures.



Fig. 2. Construction of a 5-core multicore solder. The flux cores are located near the surface so that they melt faster, giving rapid fluxing action.

Resin-cored solder is obtainable in a variety of wire gauges. For general and heavy work, such as on sockets, chassis, switch contacts, etc, 16 gauge is suitable. For fine work on printed circuit boards, miniature components, etc, 20 or 22 gauge is best. It pays to have several different gauges handy. Experience will show which is the best under different circumstances.

As already mentioned, solder is an alloy of tin and lead. Tin melts at 327°C and is plastic down to 283°C. Lead melts at 232°C and is plastic from 183°C to 232°C. Either by itself

is unsuitable as any movement of the joint while the soldering metal is in its plastic state will result in a faulty joint. An alloy of appropriate proportions has a plastic state temperature range that is much smaller, and a lower melting point (see Fig. 1). With a composition of 63% tin and 37% lead, the alloy has no plastic region. It goes from solid to liquid at exactly 183°C. This is undesirable as a small region of plasticity reduces brittleness under practical circumstances. The most common composition of solder for electronics work is therefore 60% tin 40% lead, often called 60/40 solder. It melts at a temperature of 188°C and has a plastic range of about 5°C. It combines optimum strength with lowest electrical resistance. Another type of solder used in electronics work includes about 1.5% copper and is known under the trade name of Savbit. Soldering irons with copper tips corrode rapidly when used with straight 60/40 solder as some of the copper is absorbed into the molten solder. Savbit solder prevents this and can extend the life of copper bit soldering irons by up to ten times. Some soldering tools have iron-plated tips to reduce this sort of wear and the use of Savbit is not necessary with these irons.

Ordinary solders, such as 60/40 solder, are also referred to as 'soft solder'. Joints that have to withstand high temperatures, or that need greater mechanical strength than obtained with 60/40 solder, are joined with 'hard' solders that melt at higher temperatures. Hard solder contains either 30/70 or 20/80 tin-lead and melts at 255°C and 275°C respectively.

'Silver' solder, containing 5% tin/93.5% lead/1.5% silver, melts at about 300°C and is mostly used in fabricating brass or copper chassis, etc. Silver solder is usually melted with a gas-burning torch. A special flux is also used.

Low-temperature solder is also

obtainable and is used where components may be damaged or where it is necessary to solder onto a joint that is already soldered without melting the existing joint. This has most applications in special servicing jobs. It consists of 50% tin/33% lead/17% cadmium and melts at 145°C. It requires care in soldering as it tends to fracture the instant it solidifies.

Soldering Irons

It is important to select a suitable soldering iron — after all, it will probably be the tool you use the most! A bewildering variety of types and sizes are available.

Continuous Heat Irons

These are probably the most widely used despite a few drawbacks. They are heated by a wire resistance element located in the barrel just behind the tip. The most suitable rating for electronics work is between 15 and 30 watts. Tools below this rating generally do not have sufficient heat capacity, while those above have high tip temperatures -that can result in damaged components and poor joints. Irons of the continuous heat type that have ratings above 80 watts are best for sheet metal work. Irons advertised as 'universal' (mostly having a rating of 40 or 50 watts) should be avoided as they are usually too bulky for electronics work, particularly on printed circuit boards, and have too much heat capacity and high tip temperatures with the likelihood of component damage. The handle also usually gets too hot for comfort.

Choose an iron which is comfortable to hold. As well as being light, the iron should preferably have a lightweight power cord to reduce drag on your wrist when moving the iron around. The length of the cord should be adequate — about 1.5 m to 2 m is a good length.

Continuous heat irons are slow to heat to soldering temperatures — they are usually left running continuously. This causes tip oxidisation which therefore requires constant maintenance and fairly frequent replacement. These are minor drawbacks, however, if you cannot afford a more expensive iron.

Some irons of this type are obtainable with a temperature select switch in the handle. This usually doubles the power when needed to provide sufficient heat to make the occasional heavy joint. They are normally used on the lower power position for routine soldering.

Quick Heat Irons

These irons operate from a low voltage at a high current, usually supplied from a transformer, and take only a few seconds to reach soldering temperature. They take only a few more seconds to reach red heat if the operating button is held on too long!

Quick heat irons are made in two basic styles — the soldering gun and the low-voltage iron. HEATING ELEMENT

Fig. 3. A bettery-operated soldering 'gun' (this one is by Scope, too). Construction is similar to the Mini Scope. Such irons are useful where power is unavailable.

Soldering guns have a transformer mounted in the handle that passes about 50 amps at 0.5 volts through a short length of heavy copper wire the bit — thus heating it rapidly to high temperatures. Some irons of this type include a reel of solder which is automatically fed to the tip each time the trigger is pressed — but for good joints that's not where you want the solder; it needs to be applied to the joint.

Low-voltage irons have a push-ring or lever on the handle which pushes a carbon contact against the rear of the tip, passing a current of about 30 amps at 3 volts. The contact, having a higher resistance than the rest of the circuit, rapidly heats up, passing its heat to the tip, which reaches soldering temperature in a few seconds. An external transformer supply is the necessary power.

Quick heat irons are suitable for intermittent handyman use or applications requiring their large heating capacity. They are not recommended for general electronics use, particularly on printed circuit boards. They require some skill to control the heat so as not to damage components by overheating. Some do not have an electrostatic screen on the transformer, and ICs and some transistor (particularly MOSFETs) can be damaged by leakage currents.

Despite their limitations, quick heat irons can be useful in an electronics workshop. If you contemplate purchasing one make sure the transformer has an electrostatic screen.

Soldering guns have the disadvantage that the transformer in the handle tends to make them a little unwieldy, especially for prolonged use.

Battery-operated soldering irons have become widely available, and these find application where power is unavailable or inconvenient to supply. These irons can be used where components sensitive to leakage currents (ie MOS devices, CMOS ICs, etc.) are employed. Rechargeable batteries, usually contained in the handle, supply the current. They are not suitable for prolonged use.

Temperature-Controlled Irons

Temperature-controlled irons are made specifically for electronics work. They are unsurpassed for good soldering, convenience and minimum possible damage to components. They are more expensive than the other types but get one if you can afford it.

There are several ways of controlling the tip temperature. One method (used in the Weller iron) is illustrated in Fig. 4. A spring-loaded switch within the handle is operated by a magnet and temperature-sensitive sensor assembly located in the barrel. The temperature-sensing element consists of a ferro-magnetic material, which at a certain temperature (called the Curie point temperature), loses all magnetic properties. The actual Curie point temperature depends on the composition of the ferromagnetic material. The Curie point for iron is typically 1000°K, 633°K for nickel and 1393°K for cobalt. An alloy of these and other ferromagnetic materials can be selected to produce any temperature required.

When the tip is cold the magnet is attracted to the sensor, which actuates the switch, applies power to the element, and heats the tip. When the tip reaches the Curie point temperature the sensor releases the magnet, opening the switch and removing power from the heating element. When the tip cools slightly, the magnet is again attracted to the sensor and the whole cycle is repeated, maintaining the tip within a few degrees of the selected temperature. The iron can be heard to emit a small click as the magnet goes through its attract-release cycle.

The tips are removable and sensors having different Curie point temperatures are available. One can select tip temperatures in the range 260°C to 430°C. A variety of shapes is also available to suit different applications. The Weller irons operate from a 24 volt transformer which is moulded into the stand supplied.

TWIN 1.2 VOLT

NICKEL CADMIUM

4 AMP/HR BATTERIES

Another type of controlledtemperature iron has circuitry in the stand supplied with it which monitors the tip temperature and controls the supply to the heating element, thus maintaining a constant tip temperature. In this type, a control knob is provided in the stand which allows the operator to set the desired tip temperature (Fig. 7).

Where 60/40 solder is used for construction work, a tip temperature of 250°C (500°F) is recommended. This is sufficiently above the melting point of 215°C to allow for heat conducted away by the joint and still melt the solder. If using Savbit solder, it melts at a slightly higher temperature and a tip rated at 275°C (550°F) is recommended.

For desoldering, such as in servicing work, a tip temperature of 315°C (600°F) or more is necessary; up to 370°C (700°F) is recommended where large connections are involved.

Soldering Bits

The soldering iron bit conducts heat from the iron's element to the joint. A typical bit is shown in Fig. 6. The tip temperature and the amount



Fig. 4. Temperature control system that exploits the 'Curie point temperature' of a magnet to turn the power on end off to the heating element. The magnet is attracted to the rear of the tip, closing the switch. The element heats the tip and when the temperature reaches the Curie point of the magnet, the magnet loses its magnetism and the spring opens the switch. When the temperature drops below the Curie point, the cycle is repeated. Some models of the Weller soldering irons employ this technique of temperature control.

Features



Fig. 5. This iron, Weller's model EC2000D, employs a temperature sensor in the tip and electronic control of the power to the heating element to maintain the tip temperature within very close limits. The desired temperature is set by a knob and displayed in the threedigit readout.

of heat it stores are important factors in obtaining a good soldered joint. The tip temperature will drop when making a joint due to heat being conducted away by the parts of the joint. Just how much the temperature drops and how fast depends on the capacity of the bit to store heat and the mass of the parts being joined. The larger the bit, the more heat it will store and transfer to a joint, and the les will be the temperature drop. Temperaturecontrolled irons minimise these problems to a large extent.



Fig. 6. A typical replaceable soldering iron bit. This one screws onto the end of the iron barrel, and the cylindrical tip has a 'flat' on the end at an angle of about 60° to the axis.

For an adequately rated iron, the correct bit for the job will remain above soldering temperature (without burning the joint) and cause the solder to flow properly. If the tip is too small, too much heat will be conducted away, and the solder, while it may melt a little initially, will not melt and flow properly and a poor joint results. The effect of proper bit size is shown in Fig. 7.

Bits are usually made of copper, copper alloy or iron-plated copper. A plated bit is shown in Fig. 8.

Unplated bits transfer heat more effectively but oxidise rapidly, reducing their efficiency. Their life is much shorter than plated bits and they require more frequent maintenance.

The area of the tip face determines the rate of heat transferred to the joint. A small area will have a higher temperature but less heat reserve (or



Fig. 7. The bit should be large brough for the job, otherwise too much heat is conducted away from it by the joint and the solder will not flow properly. The bit on the left is OK, that on the right is too small.

capacity) than a large tip. Generally, the more heat the work is likely to absorb, the larger the tip area should be. However, the area should not be so large that it obscures the work or damages adjacent parts.



Fig. 8. Plated bits last longer because they do not oxidise as rapidly as unplated bits. They are usually iron-plated.

The distance the bit protrudes from the barrel of the iron is also important. The shorter this distance, the higher the tip temperature. Usually, it is best to select a bit length as short as practicable to reduce the heat path from the element to the tip, and to minimise wobble and bending of the bit. It should not be so short that the barrel touches or radiates onto nearby components or that the tip temperature becomes too high. One way of reducing the temperature of a smalldiameter bit is to increase the length beyond that used for the larger-sized bit — or vice versa. Bent bits can be used in awkward places where a straight bit cannot reach.

Maintaining The Iron And Bit

For maximum efficiency and consistently good joints, the soldering iron and bit require frequent but simple maintenance. Heating produces oxidisation of the barrel and bit, the oxide forming a scale on the parts. This reduces heat transfer as the scale is an insulator. Continuous heat irons are particularly affected. Excessive scaling is produced by high operating temperatures and by prolonged use without descaling.

To remove scale, remove the bit and tap both the barrel and bit firmly on the bench top. This should be done regularly. Only remove a plated bit from the barrel of an iron when it is quite cold.

For efficient transfer of heat from the bit to the work, the face of the bit should be smooth and coated with a shiny layer of resin-free solder. A bit in this condition is said to be 'tinned'. A clean, new bit is tinned by heating it to soldering temperature (test it by lightly touching solder on the face of the bit) and applying a small amount of solder to the face and letting it flow freely to cover the face. Any excess should be removed by wiping it on a lightly damped sponge or cloth.



Fig. 9. Bits can be obtained in a variety of shapes to suit the job, such as conical, wedge, bevel, chisel, etc. The most common bit shapes are the wedge (or chisel) and the bevel. They can be different diameters and lengths, giving different heat capacities.

With use, the face of the bit becomes pitted and the solder layer takes on a dull grey appearance. During soldering, some of the copper from the face is absorbed into the solder and with repeated use the surface becomes uneen. There is less absorption with plated tips. Copper bits in good condition and in bad condition are illustrated in Fig. 10. The 'pitting' can be removed by filing. Only file off as much as necessary to produce a smooth face again. Excessive filing reduces the heat capacity and increases the bit temperature. Remove any scaling as well. When a clean tip is obtained, re-tin the face. Do not pull the tip further out from the barrel to compensate for reduced length as this overheats that section of the heating element not in contact with the bit, producing excessive scaling and eventually causing the element to fail.



Fig. 10. The tip should be in good condition, as at left, for good soldering, not worn, pitted or oxidised as at right.

Small surface irregularities on plated tips should be repaired with fine emery cloth when the tip is cold. Take care not to remove the plating. After cleaning, heat the bit and re-tin the face. Relatively large pitting on a plated bit means that some plating has come off. Attempts to remedy the situation usually result in more plating being removed. In such cases, replace the bit.

During normal soldering with a plated bit, the molten solder on the face should be replenished regularly while the tip is hot. The face can be cleaned by wiping it on a damp, finetextured sponge (these are usually supplied with controlled temperature irons). Do not overdo it or you will remove all the molten solder. Wait a few seconds after wiping the bit to allow it to recover heat and then lightly re-tin the face. Plated bits should have a small amount of excess solder on the face while not being used.

With either plated or unplated bits, regular cleaning during use is a good practice, making soldering easier and ensuring good joints. A damp sponge pad is good for either type of bit. A fine textured wire brush may also be useful with copper bits. (Fig. 11.)

Soon after learning soldering, most people will use one of two methods to remove excess solder from the bit: viz: flicking or wiping. Wiping is the recommended method. Flicking causes blobs of molten solder to splatter on to all sorts of awkward places. If you're a flicker, don't wear shorts! Apart from ruining the carpet and prompting sudden leaps into the air, molten blobs of solder have a nasty habit of getting into equipment and causing short circuits - which may be disastrous. For habitual flickers, either cure yourself of the habit or screw a low, open-topped container to the bench top and aim in there from close guarters. It is even possible to recycle the solder thus collected - but not in your project.

Basic Soldering

Before use, the soldering iron should be turned on for long enough to allow the bit to reach soldering temperature. Irons vary quite a bit in this; some take quite a few minutes to warm up, whereas others are much quicker. The parts to be joined should be bright and clean; if not they should first be tinned (see 'Preparing Leads and Components').

When the parts to be joined are prepared, and with the iron at the correct temperature, apply the face of the bit to that part of the joint having the greatest mass (providing it isn't the most heat sensitive). Allow the joint to heat for a few seconds to raise it to soldering temperature, and then apply a little solder. If the parts are clean, the solder will flow freely as it melts, wetting the joint properly and making a smooth, shiny joint. Remember that the solder must be applied to the joint and *not* to the iron.

Figure 12 shows how to solder a component lead to a tag. Apply the iron to the tag as the tag has the greatest mass. To improve heat transfer and reduce soldering time, first apply a little solder to the iron at the junction of the bit and the tag. Just a touch is sufficient. The flux removes any tarnish from the tag and the hot solder



Fig. 13. When soldering a component lead to a printed circuit board, apply the iron to the lead with the tip touching the copper track as wall.

tarnish that forms on the face of the bit, allowing rapid heating of a small area. The molten solder improves the thermal contact by wetting both surfaces and filling the minute air spaces between them. Next apply the solder to the tag. The solder will only melt if the tag is at the correct temperature, thus ensuring proper wetting.

Soldering components to a printed circuit board is shown in Fig. 13. Always take care not to overheat printed circuit boards as the copper track may lift, damaging the board and making subsequent connections difficult.

Always hold the iron on the joint for a second longer after sufficient solder has been applied. This ensures that all the solder is melted and that the flux has been de-activated. Allow the solder to cool naturally. Don't blow on it to cool it. Don't move the joint while the solder is solidifying — a poor joint may result.

Take care not to apply too much solder as it may conceal a poor joint. On printed circuit boards, too much solder may cause 'solder bridges' to form between tracks.

How much is the right amount of solder, and what does a good joint look like?



Fig. 11. The tip should be cleaned regularly during use. A moist sponge pad (left) is good for frequent wiping, while for unplated tips an occasional scrub on a wire brush keeps the tip in good condition.



Fig. 12. When soldering a component to a tag, apply the iron to the tag *and* the lead to heat them up. After a few seconds, touch the solder on the iron *briefly* and then apply the solder to the join.

Features

The size of the solder 'fillet' should be large enough to fill the area of the joint and the contours of the parts should be plainly visible. The surface of the solder should be smooth and bright and meet the parts of the joints at a tangent. This 'feathering' indicates good wetting. The characteristics of a good joint are shown in **Fig. 14**.



Fig. 14. A good joint will be covered by a small fillet of solder which meets the parts of the joint at a tangent. The solder should be smooth and bright.

There must be sufficient solder filling the spaces of the joint to ensure a good mechanical bond. Insufficient solder results in a mechanically weak joint. The joint is likely to go open circuit or intermittent under slight mechanical stress (such as due to vibration or expansion and contraction with temperature changes). Joints having insufficient solder are shown in Fig. 15.



Fig. 15. Insufficient solder leads to a week joint which may become faulty.

The Problem Of Plated-Through Holes

Double-sided PCBs with plated-through holes are becoming increasingly common. It is important that the correct technique be used to solder components to the board as well as when desoldering component leads.

In general, one can solder component leads from the *component* side of the board. The usual rules, as described here, about applying the iron to the lead and the track apply. Likewise with the appearance of the joint. Component leads should not be crimped or clinched as it is unnecessary. A properly made joint is illustrated in Fig. 16. The application of too little solder will result in a joint as illustrated in Fig. 17.

When desoldering leads from a through-plated hole, as much solder should be removed from the joint as

possible. Vacuum-operated desoldering tools are best for this purpose. However, the lead should be removed while the iron is still applied to the joint and the solder is molten. Otherwise, you may damage the through-plating in the hole. The iron should not be pressed hard onto the pad as this too can result in damage to the throughplating. With ICs and/or IC sockets where a number of joints have to be desoldered simultaneously, special desoldering tool bits can be obtained, or else the pins of the package must be cut, destroying it.







Fig. 17 Too little soldar results in weak joint that may fracture and become intermittent or unreliable. When desoldering, a little solder will always adhere to the joint inside the hole in the positions shown, so the lead must be withdrawn while the solder is molten.

Bad Joints And How To Cure Them

In some instances, the solder may not wet the joint evenly. The solder surface is not smooth and continuous, having irregular, round, non-wetted areas exposed. The solder may meet one surface abruptly in places. This condition is illustrated in Fig. 19. It can often be remedied by reheating, although desoldering and cleaning may be necessary in some cases.

When a joint is not wetted at all, usually due to tarnish, the solder will not completely cover the surface and appears as droplets or balls (Fig. 20). This is a bad joint mechanically and electrically and should be taken apart and properly prepared.



Fig. 18. Too much solder can hide poorly wetted surfaces (top left), which results in a poor joint. On PCBs with close conductor spacing too much solder leads to 'bridging' (bottom).



Fig. 19. When poor watting occurs, the solder meats one surface at an abrupt angle and the solder flows irregularly.



Fig. 20. Tarnished surfaces prevent wetting altogether. Ball of solder sit on the surface.

Sometimes during soldering, the molten solder will run along the metal and then withdraw towards the fillet when the iron is removed (Fig. 21).



SOLDER SPOTS LIKE WATER ON WAXED PAPER

Fig. 21. Dewatting. The solder appears to flow properly, then withdraws when the iron is removed from the joint.

This 'dewetting' is another problem caused by tarnish that the flux is unable to remove. The joint has to be desoldered and thoroughly cleaned before resoldering. Applying more heat and excess solder may make the joint look all right but it may conceal a bad joint.

A 'cold' or 'dry' joint is usually caused by movement of the parts during soldering or as the solder is solidifying. It is also caused by the solder running onto surfaces cooler than the soldering temperature. A cold joint has a frosty appearance, as shown in Fig. 22, but may otherwise look like a good joint. The trap with cold joints is that they may perform quite well for a considerable period and then suddenly become intermittent or go open circuit. They are repaired quite simply by reapplying heat or desoldering the joint and then resoldering.



Fig. 22. A 'cold' joint. The solder surface has a frosty appearance but looks good otherwise.

If insufficient heat is applied to a joint, the solder solidifies before adequate wetting occurs, causing the angle of contact between the solder and the parts to be very large. The flux is not properly activated and the joint may tarnish. The solder can usually be pried loose. The surface of the solder may be smooth and continuous but it is not attached to the parts of the joint (Fig. 23). Reheat the joint if tarnishing is not evident, otherwise desolder and clean before soldering.



Fig. 23. Too little heat. The solder forms a large contact angle with the surface and can be prised loose.

In some cases, a resin bond is formed between the parts of a joint. In this case, the angle of contact of the solder is usually large and a layer of solidified resin forms the bond, as shown in Fig. 24. There may be no electrical contact at all, the joint has little strength and may be prised apart. It may be caused by excess flux or solder running onto surfaces cooler than soldering temperature but hot enough to melt the flux. It is usually cured by reheating the joint, making



Fig. 24. A resin bond. There may be no electrical contact at all. it can be cured by reheating the joint.

sure that all parts are brought up to soldering temperature.

When soldering multi-strand hookup wire, excess solder or long soldering

time can cause solder to run along the strands. This is called 'wicking' (Fig. 25) and can be reduced by soldering faster or by using a heatsink on the wire. Wicking makes the wire brittle and liable to break when it is moved.

Fig. 25. 'Wicking' is caused by solder running back up multistrand hookup wire. This makes the wire brittle at the joint and movement may break it.

When the soldering iron is withdrawn from a joint a spike of solder, called an 'icicle', is sometimes left behind, usually pointing in the direction in which the iron was removed (see Fig. 26). Icicles may be caused by a variety of problems, including tarnished joints, too short soldering time, low soldering temperature or excess solder on the iron. Reapplication of the soldering iron usually remedies the problem, but make sure that there is not some other problem with the joint. If the joint is otherwise sound, small icicles are nothing to worry about.



Fig. 26. 'Icicles' sometimes form on a joint when you remove the iron. Reheat the joint with a clean tip to get rid of them.

Preparing Leads And Components

Most modern components have leads which are tin-plated to aid soldering. The tin is readily absorbed into the solder, allowing rapid wetting and reducing soldering time. The plating will tarnish with time and handling. Unplated leads and unprotected printed circuit boards are particularly affected as oxidisation is quite rapid.

It is always a good practice to tin the parts of a joint before puttig them together. Component leads can be tinned by simply heating them with the iron and then applying a little solder. Only tin that part of the lead that is actually going to make the joint as component leads are usually trimmed after the joint is made. If the lead is tarnished, it can be cleaned by pulling it through a doubled-over piece of emery cloth or plain steel wool. Printed circuit board tracks do not need tinning. If the tracks are tarnished, clean the board with an abrasive powder cleanser (such as Ajax) and a moist cloth. Wash the

board in clean water after cleaning and dry with a tissue or paper towel.

Stranded hookup wire is best prepared in the following manner. Strip away about 6-7 mm of insulation from each end. Twist the strands together, apply the hot iron for about one second and then a touch of solder. Don't overheat or apply too much solder. Solid hookup wire is prepared the same way as component leads.

Tarnished tags are best cleaned by rubbing with emery cloth or lightly scraping them with a penknife. Thoroughly heat the tag with the iron before applying a little solder to tin it.

Enamelled coil wire can be prepared by stripping the end back about 6-10 mm using a penknife, cutting blade, emery cloth or steel wool until the bright copper wire shows. Tin it quickly. Some modern coil winding wire is coated with an enamel that, although very tough, melts at soldering temperatures ('Bicalex' and 'Lewmex' are several trade names). A hot soldering iron is applied to the end to heat it first. Apply some solder to the face of the iron then to form a molten blob to cover the wire. Shortly, the insulation will smoke and burn off, allowing the wire to be tinned. A good hot tip is necessary for this operation.

Mounting Components On Terminals

There are good and bad ways of attaching component leads to terminals before soldering. The correct method of attachment depends on the type of terminal. Pins are generally meant to have the lead bent around them, other terminals have holes through which the component lead is inserted. The main principle to keep in mind is that the lead must always be easy to remove if subsequent servicing or modification is necessary. Also, the solder should not provide all the mechanical support for the component.

Terminal Pins are often used with matrix board, being inserted into the holes at convenient positions. The component lead should be bent around the pin, making an angle of approximately 135°, as shown in Fig. 27 (left). If the angle is too small, the connection is mechanically weak — it depends too much on the solder. If the



Fig. 27. How to attach a component lead to a terminal pin before soldering.

lead is wrapped right around the terminal it is difficult to remove (**Fig. 27, right**).

Features

When mounting a component between two terminal pins, first bend each lead at the point corresponding to the position of the terminal, leaving sufficient slack in each lead for a little movement in the component. Tension each lead against the terminal during soldering (Fig. 28).



Fig. 28. When mounting a component between terminal pins leave a little slack in the leads.

Solder Tags and Terminals with Holes are found on tagstrips, potentiometers, switches, etc. The best methods of connecting leads to them are shown in Fig. 29a. In each case, there is adequate contact between the lead and terminal and the lead can be easily removed if necessary later. Do not wrap the component lead right around the terminal as this makes subsequent removal difficult and messy, but if the lead is not bent around the terminal at all too much dependence is placed on the solder for both mechanical and electrical connection. The wrong ways are illustrated in Fig. 29b.

The way a component is mounted between two terminals of this type depends on the orientation of the terminals. Where the holes are approximately parallel, bend each lead at right angles at the point corresponding to the position of the terminal hole. The lead is inserted without further bending (Fig. 30). Leave a little slack in the leads for movement. Hold the lead firmly when soldering.

Where the terminal holes are in line (ie coaxial), bend one lead around one terminals as illustrated in Fig. 29 and pass the other lead through the other terminal without bending it. Solder the bent lead first. Tension it against the terminal while soldering. Arrange a little slack in the leads before soldering the remaining lead (Fig. 31a). If the terminals are at a slight angle to one another, form one lead to pass along the side of the terminal closest to the body of the component before entering the hole. Don't bend it further. Pass the other lead through the other terminal hole without bending it either. Solder the bent lead first, tensioning it against the terminal to prevent movement. Again arrange a little slack in the leads before soldering the remaining lead. (Fig. 31b).



Fig. 29. The best way to attach component leads to tags and terminals (left).



Fig. 30. Mounting a component between tags with parallel holes.



Fig. 31. Mounting component leads where the tag holes line up, or nearly so. Bend the leads to provide some slack.

To mount a component between a terminal pin and a solder tag, bend the leads around each terminal according to the principles outlined above.

When terminating several leads on one terminal, each lead should be connected separately, regardless of the type of terminal. This allows any single component to be easily removed. Don't twist the leads together as this prevents subsequent removal. Figure 32 illustrates the correct and incorrect methods of terminating several leads to one terminal.

When interconnecting two terminals use a length of wire between them. Don't use component leads.

Mounting Components On Printed Circuit Boards

Components should always be mounted on the *non-copper* side of a printed circuit board, unless especially noted otherwise. The component leads should be inserted in the correct holes and may be formed in a variety of ways





WRONG

Fig. 32. When several component leads go to one terminal, attach each lead separately.

before soldering. The leads may be splayed, as shown in Fig. 33, to hold the components in position before soldering. This method allows all the components to be mounted before soldering. See Fig. 34.

Another method is to mount the components one at a time, cutting the



Fig. 33. When mounting components to a printed circuit board, the leads may be splayed, before soldering, to hold them in position.

leads close to the board before soldering, as in Fig. 35. However, this necessitates holding the component steady whilst soldering.

For a neat appearance, do not leave excessive lead length on the components; place them against the board and align them parallel to an edge. Generally, printed circuit boards are laid out so that the components will lie parallel to an edge when correctly inserted. It is a good idea to position the components so that their value and voltage rating or type number can be seen. This greatly facilitates checking and later servicing.



Fig. 34. The leads may be cut off and bent to le flat along the track on the board and then soldered.



Fig. 35. Alternatively, the leads may be cut so that they protrude a short way, and then soldered. They may be cut off after soldering if you wish.

Sometimes components are mounted vertically. It is best to splay or clinch the leads in this case and allow a small clearance between the end of the component closest to the board and the board. Vertically mounted components are illustrated in Fig. 36.

Many capacitors, ceramic capacitors particularly, have their coating material extending a little way down the leads.



Fig. 36. Whilst axial lead components (ie resistors) are generally mounted horizontally on a PCB, they are sometimes mounted vertically. Leave a millimetre or so clearance between the bottom end and the board.

This should not be removed beyond the point where the leads enter the component body. The coating should not enter the hole in the printed circuit board. Where double-sided board is used, allow a clearance of 2 mm or so between the circuit pad and the coating on the lead.

Components with metal bodies that are mounted on the copper side of a board, or on double-sided board, or that cross a track or jumper lead should be sleeved or otherwise insulated to prevent a short circuit.

Precautions With Semiconductors

Most semiconductors are damaged by overheating. Always solder or desolder semiconductors quickly and cleanly. Make sure all parts to be joined are clean and/or tinned beforehand. If you don't feel confident about making the joint quickly, use a heat shunt (eg a pair of pliers) between the end of the lead being soldered and the transistor body to divert the heat. Special heatsink tools are obtainable for this purpose.

Integrated circuits require particular care when being soldered into printed circuit boards. If too much solder is applied, a 'solder bridge' may form between adjacent pins (see Fig. 18). This necessitates removing the solder, with the risk of damaging both the board and the component.

Transistors and integrated circuits of the MOS or CMOS type are easily damaged by electrostatic charges or leakage currents from the soldering iron. These devices are normally supplied with their pins inserted into a conductive material, usually a black foam. Leave them in this until they are to be used. Avoid touching the pins, as even small static discharges from the body (caused by clothing) can cause damage.

Always fit MOS or CMOS components last. Insert the device into place quickly. Solder the power supply pins first. The devices are built so that this activates built-in protective circuitry. The remaining pins may then be soldered with little chance of damage. Sockets for ICs are worth using as they remove the necessity of soldering directly to the IC pins, thus reducing the possibility of damage.

To reduce leakage currents produced by a soldering iron, connect a flexible lead from the metallic part of the iron (make sure it connects to the tip) to an alligator clip that can be attched to the equipment earth (O V rail). Soldering irons that use a stepdown transformer should have an earthed electrostatic shield between the windings. It is wise to check this when buying. Alternatively with an iron that has sufficient heat capacity, disconnect the iron when soldering components that are sensitive to leakage currents.

Desoldering

Where joints have to be desoldered there are two basic methods that can be used to effectively remove the solder — 'soaking' it up and sucking it up.

It is possible to remove leads while the solder is molten by just heating the joint. However, this is not the best



Fig. 37. A precaution to take when using mains-operated or unprotected low-voltage irons on MOS components is to connect the metallic part of the iron to the O V rail of the equipment with a clip lead.

method, as a component may be damaged by the amount of heat produced. Also, flexing the leads whilst trying to remove the component may damage the lead or the lead-body seal. A terminal or printed circuit can also be damaged by heat or attempts to prise the component loose while the solder is molten. It is much better to use a desoldering aid.

Desoldering 'wick' can be used to soak up molten solder from a joint. This consists of a copper braid impregnated with resin. When applied to a joint and heated with a soldering iron, molten solder from the joint flows into the fluxed braid by capillary attraction, effectively clearing the joint of solder. Figure 38 shows how it's done.

You lay the wick over the area to be desoldered. The iron is applied to the wick and some pressure applied. As the wick heats up it activates the flux in it, which flows onto the joint, and as the solder on the joint melts it replaces the flux in the wick, flowing into the braid quite quickly. The 'used' wick is cut off afterwards. A tip running at a higher temperature and having more heat capacity than generally used for soldering is recommended. Desoldering wick is excellent for general use and on joints having a large area.

Sucking up the solder with a suitable tool is a very effective method. Hand-



Fig. 38. How to use desoldering wick. Lay it over the joint and apply the iron tip to the braid, using a little pressure. When the solder is drawn into the braid, remove the iron and the braid.

Features

held 'solder suckers' are inexpensive and popular but a variety of desoldering irons with suction devices incorporated are also available.

Solder suckers have a spring-loaded plunger in a barrel with a thumboperated release mechanism. A heatresistant nozzle at one end is applied to the joint, which is heated with an ordinary soldering iron. When the plunger is released, molten solder from the joint is drawn into the barrel. Figure 39 shows how it's done. They are excellent for general use with PCBs. boards.

That's the general technique, and it's fine for equipment using bipolar



Fig. 40. This Hakko 'Vac Ace' desoldering tool from G.E.S. employes a small vacuum pump to draw molten solder from the joint into the glass barrel atop the gun handle. A steel wool wad absorbs the solder. This tool is particularly effective on through-hole plated PCBs.



Fig. 39. Using a hand-held solder sucker. The nozzle is made of Teflon (PTFE), a heatresistant plastic, and is replaceable. To use it, load the plunger in the tool. Heat the joint until the solder melts, apply the sucker's nozzle to the joint and release the plunger.

devices, but it can be extremely dangerous for MOS devices. A US maker of solder suckers, Anderson Effects, points out that standard plastic solder suckers have been found to produce a static surge of 5 kV to 10 kV at the tip. This is invariably in contact with the device's leads when the surge occurs and may damage or destroy the device. To obviate the problem staticfree metallised plastic nozzles may be obtained. Otherwise, use desoldering wick or a vacuum-operated desoldering

iron.

A variety of desoldering irons having a hollow tip through which the molten solder is drawn by a vacuum pump are available. These are particularly useful for servicing work. An example is HE shown in Fig. 40.

(Material for preparing this article was derived from Australian Post Office technical training publication ETP 0276, 1972, and The Art of Soldering, ETI April 1975. Additional material and photographs were kindly supplied by Royston Electronics, Multicore Solders Pty Ltd, The Cooper Tool Group Ltd, Scope Laboratories and General Electronic Services 1 Electronic Services.)



Ready made PCBs For Readers! PRINTED CIRCUIT BOARDS (PCBs) for HE projects have often represented an obstacle for our readers. Some of you, no doubt, make your own but our PCB Service saves you the trouble.

E PCB SERV

NOW you can buy your PCBs direct from HE. All (non-copyright) PCBs will be available automatically from the HE PCB Service. Each board is produced from the same master as that used for the published design and so each will be a true copy, finished to a high standard.

Apart from the PCBs for this month's projects, we are making available some of the popular designs from earlier issues. See below for details. Please note that only boards for projects listed below are available: if it isn't listed we can't supply it.

£2.20	September 80 Auto Probe	£1.25	May 81 Voice Operated Switch	£1.25
£1.98	Development Timer Bench PSU	£1.35 £2.20	June 81	20.40
f1 95	October 80 Nobell Doorbell Intruder Alarm	£1.98 £1.88	Envelope Generator Organ 2	£1.40 £1.90
£1.98	Tug O' War	£1.99	July 81 Organ 3	£4.50
£1.60 £2.95	November 80 Memory Bank Synth: Mainboard PCB	£2.48	Ultrasound Burglar Alarm	£1.90
£3.98 £2.98	Reyboard PCB Party Grenade (set of three) Double Dice	£2.60 £2.20	RPM Meter Thermometer	£1.33 £1.25
£3.50	December 80 Stereo Power Meter Digital Speedo (set of two)	£2.12 £3.50	September 81 Power Pack Reaction Tester Game	£1.27 £1.28
£1.40 £1.58	January 81 Car Rev Counter	£2.24	'Diana' Metal Detector October 81	£2.48
	Heartbeat Monitor Audio Signal Generator	£1.90 £1.85	November 81 Sound Torch (Set of Two)	£3.98
£1.20	March 81 Steam Loco Whistle	£1.99	December 81 Redalboard Organ	F4 48
£1.79 £1.98	April 81 Super Siren Russian Roulette Game	£1.48 £1.20	January 82 Intelligent NiCad Charger	£2.28
	£2.20 £1.98 £1.95 £1.98 £1.60 £2.95 £3.98 £2.98 £3.50 £1.40 £1.58 £1.20 £1.20 £1.79 £1.98	September 80£2.20Auto Probe Guitar Phaser Development Timer£1.98Bench PSUOctober 80 Nobell Doorbell£1.95Intruder Alarm Tug O' War£1.98Tug O' WarNovember 80£1.60Memory Bank Synth: Keyboard PCB£3.98Party Grenade (set of three)£2.95Double DiceDecember 80£3.50Stereo Power Meter Digital Speedo (set of two)£1.40January 81 Heartbeat Monitor Audio Signal Generator£1.20March 81 Steam Loco Whistle£1.79April 81 Super Siren Russian Roulette Game	September 80£2.20Auto Probe£1.25Guitar Phaser£1.48Development Timer£1.35£1.98Bench PSU£2.20October 80K2.20Nobell Doorbell£1.98£1.95Intruder Alarm£1.88£1.98Tug O' War£1.99November 80Keyboard PCB£2.48£2.95Mainboard PCB£2.70£3.98Party Grenade (set of three)£2.60£2.98Double Dice£2.20December 80£3.50£1.40January 81£1.58Car Rev Counter£2.24February 81Keyboard fitter£1.58Stereo Power Meter£2.12Digital Speedo (set of two)£3.50£1.40January 81£1.79April 81£1.79Super Siren£1.48£1.98Russian Roulette Game£1.20	September 80May 81£2.20Auto Probe£1.25Voice Operated SwitchGuitar Phaser£1.48Organ 1£1.98Bench PSU£2.20June 81Envelope GeneratorOrgan 2Envelope GeneratorOctober 80Nobell Doorbell£1.98July 81£1.95Intruder Alarm£1.88July 81£1.98Tug O' War£1.99Organ 3Movember 80Organ 4Ultrasound Burglar Alarm£1.60Memory Bank Synth:Ultrasound Burglar Alarm£2.95Mainboard PCB£2.48Keyboard PCB£2.20Thermometer£3.98Party Grenade (set of three)£2.60Party Grenade (set of three)£2.60RPM Meter£3.50Stereo Power Meter£2.12Digital Speedo (set of two)£3.50£1.40January 81£1.58Car Rev Counter£1.58Car Rev Counter£1.20March 81Steam Loco Whistle£1.99£1.79April 81Super Siren£1.48£1.79April 81£1.98Super Siren£1.79April 81£1.98Super Siren£1.79April 81£1.98Super Siren£1.79April 81£1.98Super Siren£1.20March 81Super Siren£1.48Lintelligent NiCad Charger

PLACE an order for your PCBs using the form below (or a piece of plain paper if you prefer not to cut the magazine), then simply wait for your PCBs to drop through your letterbox, protected by a Jiffy bag.

or the amount shown below	Boards Required	Price
wish to pay by Barclaycard. Please charge to my account number		
DR VISA		
wish to pay by Access. Please charge to my account number		
IGNATURE		
NAME		
DORESS		
	Add 40p p & p	0.40
	Total Enclosed £	

0 0 D SWITC SOUND ACTIVATED swit-ches lend themselves to applications such as baby alarms, voice activated tape recorders, burglar alarms and the like. A circuit for all reasons This simple design will operate from a voice of average SW1 ON/OFF volume at a range of about twometers or so using a high +9V R5 470R impedance microphone, or a NOTE RLA 01,2 ARE BC109C 03 IS VN10KM D1,2 ARE 0A91 D3 🛣 little less than this using a low (COIL RLA1 120R) **R**4 R2 10k impedance microphone or 5 5 5k6 C4 33p + C1 100u D3 IS 1N4001 with a high impedance 03 as the ► D2 C5 1u0 R1 3M3 from the microphone will be at a very R3 2M2 low level and must be greatly C3 1u0 amplified in order to operate a 100 02 01 T D1 switching device of some kind (a relay in this case). The microphone signals are C6 10u < MIC1 therefore coupled, by C2, to a high gain common emitter ov amplifier using Q1, collector load resistor R2 and base bias 0 resistor R1. The signal level at A the collector of Q1 is still in-00 adequate, so a further and vir-B 0 0 tually identical stage of C1 С **R4** 0 0 **R**2 **R5** amplification is used to boost it +9V VIA D • 0 R3 0 (•) further. The second stage is SW1 based on Q2, with C4 to at-Ε 0 (• 0 D3 tenuate the high frequency E lacksquarePR1 0 response of the amplifier and RLA (1) G D2 C5 d 0 h Ó C6 Q3 C5 couples the output of 1 0 н C3 Q2 Q2 to D1 and D2 which rectify 01 C2 +() g k R6 . I **D1** the signal to give a series of e 0 0 00 0 0 00 0 0V positive pulses. These are smoothed by C6 to give a positive DC bias. In the 0 0 0 0 0 MIC1 absence of an input signal 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 1 2 3 4 there will, of course, be no significant drive, and VMOS 0 0 . . switching transistor Q3 will be 0000 . 0 cut off. The drive will be of the Т order of a couple of volts or so • • • • • • 0 0000 0 0 • • 0 0 0 0 0 0 0 0 н when the unit is activated, 0 • 0 0 0 0 • 0 • 0 0 0 • 0 $\circ \circ \circ \bullet \circ \circ \bullet \bullet$ G switching on Q3 and the relay 0 • • • 0 0 0 0 • 0 0 0 0 • 0 0 0 • 0 0 • • F 0 which forms its collector load. A pair of normally open relay • • • • • • • • 0 0 0 0 0 ٠ 0 0 0 • 00 0000 0 Ε contacts then operate the ex-0000000000000000000000000 D 0 000000000 0000 0 0 00000 0 0 0 С 0 R6 is included so that the bias decays about two B 0 0(00000000000000 00000000 0 0 seconds after the input signal 0 ۵ has ceased and the unit reverts to the 'off' state. Without R6 the unit would tend to latch 'on', since the input resistance of Q3, unlike an ordinary bipolar transistor, is extremely SEMICONDUCTORS Parts List high. The attack time of the BC109C Q1,2 unit is very short and it swit-VN10KM Q3 RESISTORS (all ¼W 5%) ches on rapidly at the start of a D1,2 0A91 **R1** 3M3 1N4001 D3 The 0.1" matrix stripboard **R2** 10k layout for the Sound Switch is 2M2 **R3** MISCELLANEOUS straight-forward. Q3 requires **R4** 5k6 SW1 SPST toggle switch 470R no special handling precau-**R5** MIC1 microphone or high tions as it has an integral zener impedance loudspeaker (see diode which protects it from CAPACITORS text) high static charges. D1 and D2 RLA relay 6/12 V coil 185 ohms or more

C1	100u 10 V axial electrolytic
C2,3,5	1u0 25 V axial electrolytic
C4	33p ceramic plate
C6	10u 10 V axial electrolytic

0.1

64

necting them.

signal.

are germanium devices and

care should be taken to avoid

overheating these when con-

loudspeaker

Signals

thus aid stability.

ternal equipment.

microphone.

Hobby Electronics, February 1982

HE

matrix board, PP9 or similar

battery, battery clips, etc.





HIGH QUALITY COMPONENTS: Low profile sockets 24 pin 22p, 40 pin 30p. Resistors ½ W 5% 100 mixed 90p. Cermet potentiometers 10 mixed £1.95. P&P 40p. Large SAE for lists. T. Milner, 203 Goodman Park, Slough, Berkshire.

CLOSE ENCOUNTERS GROUP. Personal introductions/dances, parties, talks, social events. Meet interesting, attractive people. All areas. – Tel. (Liverpool) 051-931 2844 (24 hours).

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac 'light-sensitive lacquer – now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55b. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

CENTURION BURGLAR ALARM EQUIPMENT Send sae for free list or a cheque/po for £11.50 for our special offer of a full sized signwritten bell cover, to Centurion Dept HE, 265 Wakefield Rd, Huddersfield, W. Yorkshire. Access & Barclaycard. Telephone orders on 0484-35527

20% OFF CASES, SWITCHES, RELAYS, DIODES, IRONS, ETC. lists 28p, Industrial and Trade enquiries welcome. RELAY-A-QUIP, Moat Lodge, Stock Chase, Maldon CM9 7AA. 24 hr phone: 0621 58686.

BURGLAR ALARM equipment. Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium. C.W.A.S. Ltd.

CORDLESS TELEPHONES Build your own simple and inexpensive units. Send £3.00 for plans to: J.F. Ashley, Birley Grange Cottage Farm, Baslow road, Cutthorpe, Derbyshire.

AMAZING ELECTRONICS PLANS. Lasers; Super-powered Cutting Rifle, Pistol, Light Show. Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Cata-logue 95p. — From Plancentre, 16 Mill Grove, Bibbrook, Codsall, Wolverhampton.



PRIVATE OR TRADE ENQUIRIES WELCOME FULL RANGE AVAILABLE. S.A.E. FOR LISTS, £1.45 for Booklet. "Nickel Cadmium Power" plus Catalogue. "New range of sealed lead now available". Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COL-DFIELD, WEST MIDLANDS. 021-354 9764.



100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50; 60 watt £44; 200 watt £86; 100 watt twin channel sep. treble/bass per channel £85; 60 watt £52; 200 watt £78; 100 watt four-channel sep. treble/bass per channel £75; 200 watt £94; alevas 100 watt £34; 200 watt £12; bass fuzz £12.90; overdriver fuzz with treble and bass boosters, £22; 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £98; twin channel, £115; bass combo £118; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £16; microphone shure unidyn B £25; 3-channel sound/light £26.

Send cheque/P.O. to: WILLIAMSON AMPLIFICATION 52 Theracliffe Avenue, pukinfield, Cheshire. Tel. 051-300 2054

ZX81 FLICKER-FREE GAMES. 6 super games, each 1K, plus Free menu, all on cassette, plus Free listing, £3. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

ELECTRONIC CLEARANCE PACKS HUGE SCOOP PURCHASE

Containing Transistors, capacitors, resistors, pots, switches, radio and audio items, connectors, relays and many electronic devices. Must be worth over £20 per pack. Our price £5 car £1.75. JUMBO PACK Must be worth over £50. Our price £10. Car £2.50. Money back if

not delighted

HAVE YOU SEEN THE GREEN CAT?

1000s of components, Audio, radio, and electronic. Almost everything electronic at unbeleivably low prices. Something for everyone. Send 35p P.O. or cheque and receive FREE RECORD SPEED INDICATOR

MYERS Dept HE 12 Harper Street, Leeds LS2 7EA Tel, 452045

IONISER KIT (MAINS OPERATED)

 This Negative Ion Generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasent breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

 All parts, PCB and full instructions
 £12.50

 A suitable case including front panel, neon switch, etc
 Price includes Post & VAT

 Berclaycard/Access welcome
 £10.50

T. POWELL ADVANCE WORKS 44 WALLACE ROAD, LONDON N.1.

TEL: 01-226 1489 Hours: Mon-Fri 9-5 p.m. Sat 9-4.30 p.m.

ELECTRIFY YOUR SALES! . CLASSIFIED ADVERTISEMENT

 1
 2
 3

 4
 5
 6

 7
 8
 9

 10
 11
 12

 13
 14
 15

Please place my advert in: Electronics Today International (Delete as applicable) Hobby Electronics Advertise nationally in Electronics Today International/Hobby Electronics. Simply print your advertisement in the coupon here (left), indicating which magazine you require. Or telephone for more information.

				Ì										1	1		1	1		1		1	'	•	•	•	•	1		•	*	•	1		•	•	•	.*	•	53
A	l	C	1	d	r	8	5	5	2			ł			•	•	•		•	•		•	•	•		•	•	•			•	•		•				•	•	
•		•	×						•									•	•	•	•	•	•	•	•	•	•	•	•	•		•	•	•	•	•	•	•	•	
•		•	•	•	•	•	•	•	•	•		•		•		•	•	•	•	•	ł		•	•		•	•		•	•	•	•	•		•			•		
T	6	3	t.	1	N	c	١.	(C) 8	31)																											

Send, together with your cheque to: Jenny Naraine, ETI/HE, 145 Charing Cross Rd., London WC2H 0EE. Tel: 01-437 1002 Ext. 50.



APPROVED APPROVED ON B.K. ELECTRONICS the APPROVED the STOCKIST A SOUND CHOICE APPROVED STOCKIS

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY

STEREO CASSETTE TAPE DECK MODULE Comprising of a top panel and tape mechan ism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or

The second distribution of the second distribution distribution distribution of the second distribution distress distribution distribution distribut outputs are via individual screened leads all terminated with phono plugs (phono sockets provided) Dimensions Top panel 5, in x 11° in Clearance required under top panel 2° in Supplied complete with circuit dia gram and connecting diagram Attractive black and sliver finish

Price £26 70 + £2.50 postage and packing Supplementary parts for 18V D C power supply transformer bridge rectifier and smoothing capacitor) £3.50

NEW RANGE QUALITY POWER LOUD

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15), 12, and 8). These baspeakers are dea for both hit and or scolapplications. Both the 12, and 15 ard in uminium contrection es. All three and sist ave white speaker corres and, the fitted with anthractive cast is an num-group diffusitive registration of Specification and Price.

00

15. 100 watt R.M.S. in pedance- Bohm 59 oz. magnet 2. jelan nam volen col Reson ent Frequency 20Hz Frequency Respin se to 2.9KHz Sensitivity. 97dB Price £32 each ±2.50 Packing and Car

12 100 watt R.M.S. in pedancin 8 ohn = 50 op in agnet 2 , al an in im volunico L. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 35dB. Price £23.70 each 12.50 Packing and Carriage each.

8 50 watt R.M.S. Impedance 8 or n. 20 oz. n.a.piet 1. - ilumin um vol. e. o. Reson est Frequency. 4042, Frequency. Response to inkHz. Sensitivity. 92(B. Also av Flable with black come and black protect (a. graft. Price £8.90 each. F1.75 Plack ing and Carriage each.

Type A

Type C

2

L

PIEZO ELECTRIC TWEETERS MOTOROLA Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.

3

Туре В

Type 'D'

Type 'A' 3in round with removable wire mesh Ideal for bookshelf hi fi speakers Price (Type 'A') £3.45 each.

Type 'B' 3', in super horn. For gen eral purpose speakers disco and PA systems, etc. Price £4.35 each. Type 'C' 2in x 5in wide dispersion horn. For hi fi systems and quality disco etc. Price £5.45 each.

Jype 'D' 2in x 6in wide dispersion from Frequency response ex tending down to mid range (2000 c s) suitable for hi fi systems and quality disco Price £6.90 each.

U.K. post free (or SAE for Piezo leaflets).

Piezo Level Control Loudspeaker Terminals Con risk two string a leg objective tent roles in wound potentimeter and resister relevors insound on a smart brushed alum hum plate ts neatly through a 3 k 3 cut out on real of heaver cab net Price (20)

1K.WATT SLIDE DIMMER



. Suitable for both resistance and inductive loads Innumerable applications in ndustry, the home and discos

theatres etc. Price: £11.70 each + 50p P&P (Any quantity)

BSR P200 TURNTABLE

BSR P2UV I UNIVI I ABLC P200 Turnballe chassis © S shaped tone arm Belt driven © Precision calibrated counter talance © Anti skate thiasi device © Dampred cueng liver © 240 volt AC operation (50Hz) ©ut out template supplied Price £27.00 - £2.50 P&P





Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms Build a quality 60 watt R M S system

- 🛨 10 Woofer
- 🛨 3 Tweeter
- 🛨 5 Mid Range

🛨 3 way crossover

Ether with attentive list aluminum for opes in teams and most protection calls which en-encouble enabling calls grant occorditable ef-strong Cambia mouthed dients, on the baffs with on with out on vertice also executed that is A move protection or provide Cossistent attents in the other than simple and Cossistent on the segment in the nudspeaker form in us not on associate of the other provide Price £22.00 per kit + £2.50 postage and pack ng Alin dikisepenteli periosi

12 80 watt R M.S. loudspeaker

A superbigeneral purpose twin cone our speaker 50 oz magnet 2 aluminium volce coil Rolled surround Resonant fre quency 25Hz Frequency response to 13KHz Sensitivity 95dB impedance 80hm Attractive blue cone with aluminium centre dome Price ±16:49 ea + ±2:50 P&P

GENERAL PURPOSE 41/2" MINI SPEAKER

General purpose full range loudspeaker i deal for mini systems etc. Rolled fabric surround • Twin cone • 86hm impedance • 15 wart RMS • 1. voice col • 13oz magnet • Frequency range 50. 15000Hz

Price: £6.90 each + 75p P&P



100 AND 150 WATTS R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink Supplied as one complete built and tested unit Can be fitted in minutes Auxiliary stabilised supply and drive circuit incorporated to power an LED V u mitter available as an SPECIFICATION

SPECIFICATION Max output power 100 watts R M S (OMP100) 150 watts R M S (OMP150) Loads (Open and short circuit proof1.4.16 ohms Frequency Response20Hz 25KHz + 3dB Sensitivity for 100 watts 500mV at 10K 150 watts 500mV at 10K T H D Size 360 + 115 + 80mm Prices OMP 100W **£29.99** OMP 150W **£39.99** 00.1% P&P £39.99 £6.50 f2 00 V II Mutu





VISA

B.K. ELECTRONICS 37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists ★ Official orders welcome ★ All prices include VAT ★ Mail order only ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572





