

BUILD THE "POCKET MONEY" AMPLIFIER


# Popular Wireless

Every Thursday  
PRICE  
3d.

No. 304. Vol. VIII.

INCORPORATING "WIRELESS"

March 31st, 1928.

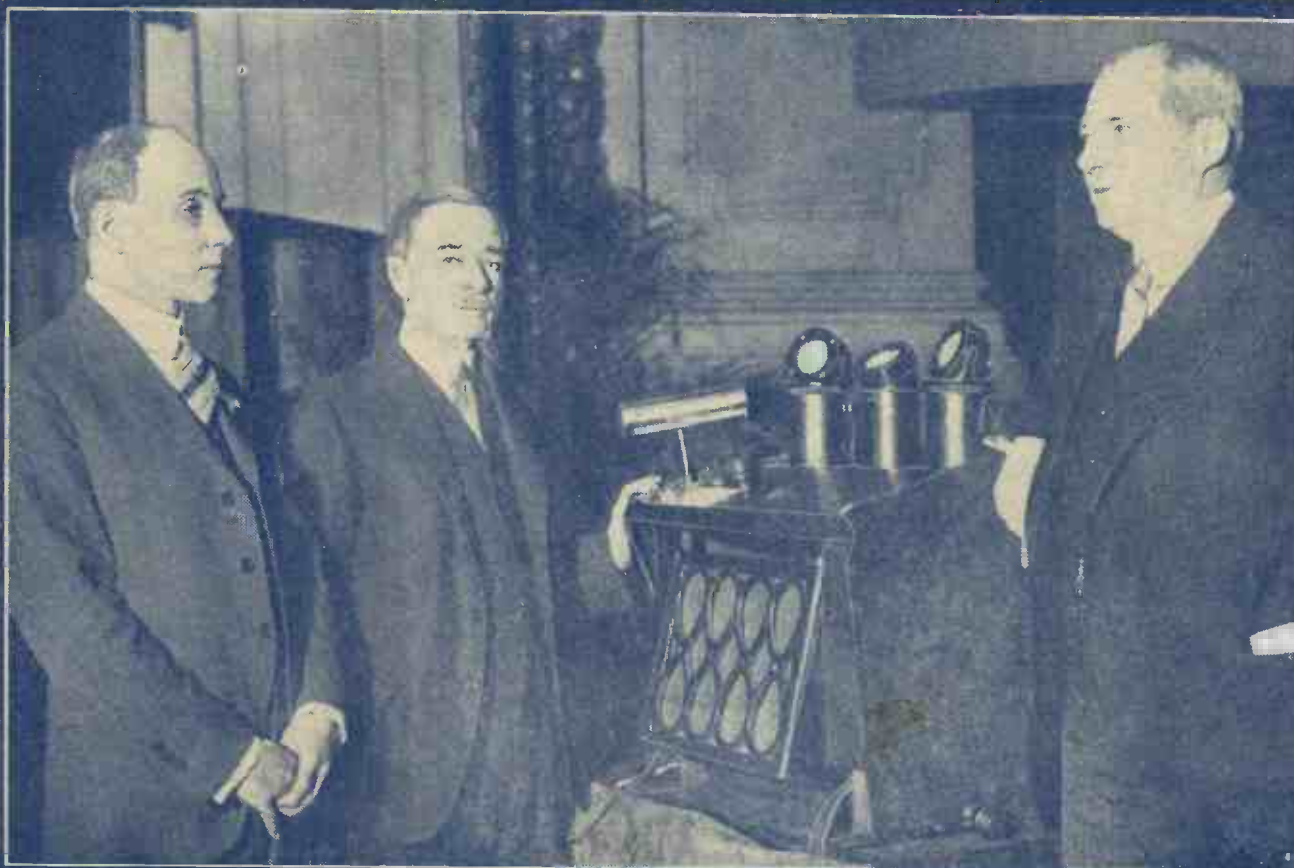

## *SPECIAL FEATURES IN THIS ISSUE*

**Ganging Your Own Condensers. "Pick-Up" Programmes  
A Disturbing Fault. "Secret Forces" and Television.**

**THE "HARTLEY" ONE-VALVER**

**Frame Aerial Reception. Is Selectivity Worth While?**

**Hints for the Handy Man, etc., etc.,**

Radio-telephony linked the two sections of a recent meeting of electrical engineers in such a way that speakers in either section—one in London and the other in New York—could address the whole meeting by means of microphones and loud speakers. The above photograph shows some of the speakers at the American end.

# THE WINNER!



New construction—  
new prices—but still  
**EVER READY.**  
The new "WIN-  
NER" gives splen-  
did service at the  
lowest possible cost  
per hour. Look for  
the Ever Ready  
"WINNER" in its  
improved red con-  
tainer.

**60 VOLTS 7/-**  
**66 VOLTS 7/6**

Obtainable from all  
Wireless Stores and  
Electricians.  
WRITE for com-  
plete Battery Cata-  
logue, free and post  
free, from THE  
EVER READY  
CO. (Gt. Britain)  
LTD., Hercules  
Place, Holloway,  
N.7.

**99 VOLTS 11/6**  
**9 V. GRID 1/3**

## EVER READY BATTERIES

**BRITAIN'S BEST**



**"Elementary, dear Watson"**



**Marconi  
H.L.210  
General  
Purpose  
Valve  
for  
2-volt Accumulators.**

As a detector, the Marconi Valve Type H.L.210 is a regular Sherlock Holmes. The faintest of signals are clapped heartily upon the shoulder and persuaded to say their piece with surety and volume.

And the H.L.210 makes no comments of its own. It detects without distortion and adds no adenoids to what the announcer has to say.

If your accumulator is a 2-volt one, and if you believe in making the amps. give as many hours as possible, try out the H.L.210 as a high frequency amplifier, as a detector, or in any L.F. stage except the last, then see how much more you get out for what you put in.

If you fill up the coupon below, we will send you a copy free and post free, of a helpful book, "500 Marconi Valve Combinations."

Suitable for the following purposes:—

- (1) For High Frequency Amplifiers in circuits where some form of stabilising or damping is employed.
- (2) As a Detector Valve.
- (3) In Transformer or Choke-coupled Low Frequency Amplifiers, except in the last stage where a D.E.P. 215 or D.E.P. 240 power valve should be used.

Filament Volts - 2.0 max.  
Filament Current 0.1 amp.  
Anode Volts - 150 max.  
Amplification Factor - 15  
Impedance - 25,000 ohms.

**Price 10/6 each**

**FREE ADVICE**

Our Engineers will furnish free advice as to the best possible combination of valves for your set, if details of the circuit and any valves at present in use are stated. "P.W." White mentioned in "P.W." to The Marconiphone Co. Ltd., 210/212, Tottenham Court Road, London, W.1.




**MARCONI VALVES**  
**-do everything that a valve should do**

Dept. P, The Marconiphone Company Ltd.,  
210/212, Tottenham Court Rd., London, W.1.  
Please send me "500 Marconi Valve Combinations" and other Marconi Valve literature.

Name.....

Address.....

P.W. 16.

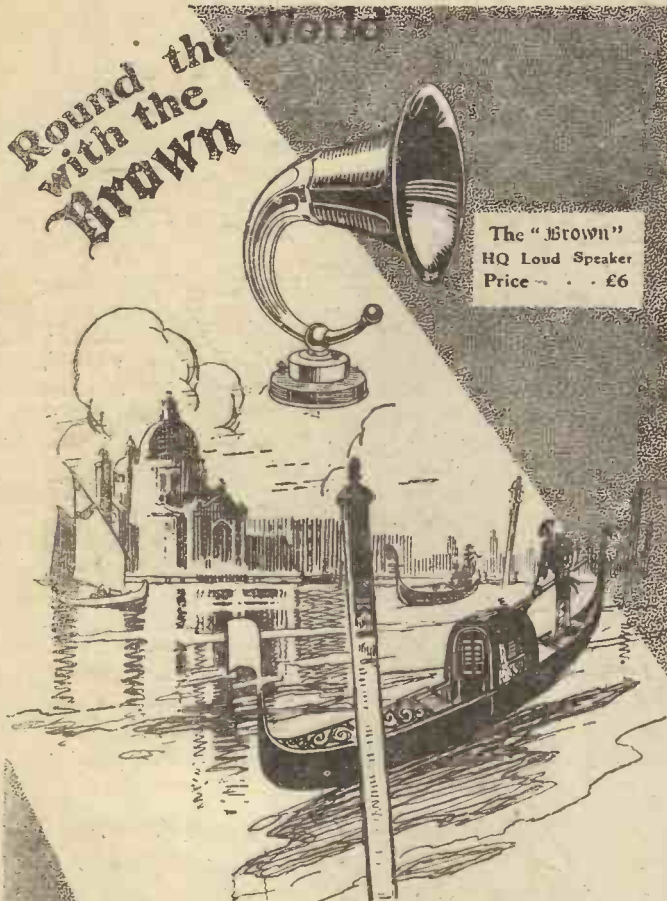

Round the World  
with the  
**Brown**

The "Brown"  
HQ Loud Speaker  
Price . . . £6

### In the City of Waterways (VENICE)

SHEER from the waters of the canal, stately palaces' false spire and turret into the waning sunlight. Smoothly the gondola glides and through the stillness comes the sound of music, ringing true and clear across the waters. It is the "Brown" Loud speaker, reproducing with its own inimitable realism.

All over the world, the perfect realism of the "Brown" Loud Speaker is enjoyed by those who enjoy good reception. All over the world the standard of Loud Speaker reproduction is set and maintained by the "Brown."

they listen to the

# Brown

The Loud Speaker on which the sun  
never sets

Adm. S. G. Brown, Ltd., Western Ave., N. Acton, W. 3.

What ever kind of set you have, or hope to have, you must not miss the April issue of

## MODERN WIRELESS

It is a wonderful double number, covering every fascinating phase of radio. For instance, if you have a

"MELODY MAKER"

a

"MASTER THREE"

or an

"R.C. THREESOME"

you will be delighted with the details of how to make your gramophone work the loud speaker, with wonderful clarity and volume.

Or perhaps you want to "reach-out" further? Details are given on an easily-made H.F. Amplifier to work in conjunction with your present receiver.

And finally there is a

## SPECIAL SOLODYNE SUPPLEMENT

containing full details of a

### THREE-VALVE SOLODYNE

(of which three versions are given) to enable you to use your own components. This special supplement also tells "How to Modernise the 1926 Solodyne," "Notes on the 1928 Model," etc., etc.

Be Sure to Order Your Copy Now.

## MODERN WIRELESS

APRIL DOUBLE NUMBER

Price 1/6 - - On Sale MARCH 30th



# "THE VALVE OF THE FUTURE"

No Dry Batteries

No Accumulators



"Cosmos-Met-Vick" A.C. Valves, Green Spot and Red Spot, are the result of investigation and experiment by one of the finest Research organisations in this Country.

They provide the complete solution for, and, in conjunction with the use of Met-Vick Eliminators, overcome all the difficulties of direct operation from the Electric Light Supply.

"Met-Vick-Cosmos" A.C. Valves not only provide the solution of the complete operation of wireless sets for the Electric Light Mains, but they also provide great volume and extreme selectivity free from distortion. By their use you can switch on your set like electric light, and yet lose nothing in effect. In fact a mains operated set with Met-Vick-Cosmos A.C. Valves is a much better set.

See what Mr. A. P. Castellain says in the "Wireless World" for March 7th:—

## "Remarkably High Mutual Conductance—

For the AC/G valve the mutual conductance is enormous when judged by ordinary valve standards—about 2 milliamperes per volt for an amplification factor of 36—and the heater current is only 1 ampere at 4 volts. The latter figures are quite comparable with valves of the 4½ volt 0.8 ampere L.S. class. For the AC/R valve the amplification factor is about 10, and the mutual conductance 4 milliamperes per volt, giving an A.C. resistance of about 2,500 ohms."

The writer continues by comparing the Cosmos AC/R Valve, very advantageously with other makes of valves for similar duties.

Note also what Mr. G. A. Exeter, the London Area Manager of the Radio Society of Great Britain says about the "Cosmos-Met-Vick" A.C. Valve:—

"..... in view of the results I have obtained upon trial, under decidedly adverse conditions, I now think you are indeed to be congratulated upon producing a great improvement in the technique of radio. Undoubtedly this is the valve of the future."

The power handling capacity of the AC/R Valve is as great as that necessary for Public Address Service and is sufficient for operating "moving coil" Loud Speakers to the greatest advantage

By using the ingenious "Cosmos" Disc Adaptors, these five-pin valves can be used in a set wired for accumulator valves, without altering the wiring.


# MET-VICK

## VALVES · COMPONENTS · & SETS


**Metro-Vick Supplies, Ltd., 155 Charing Cross Road, London, W.C.2**



TYPE No. 372.

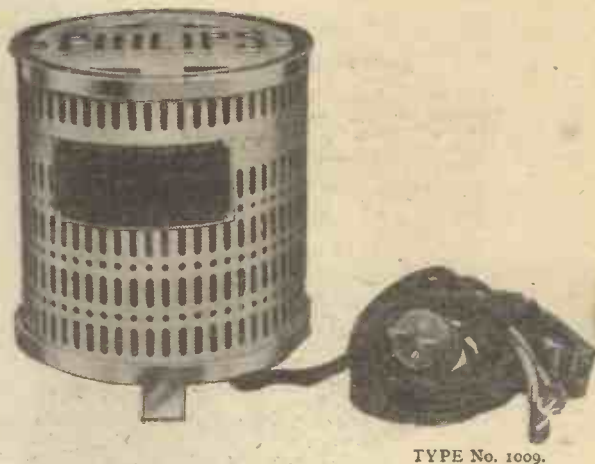

TYPE No. 1009.

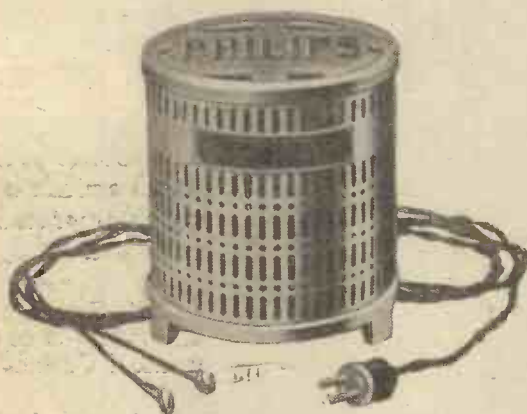

TYPE No. 327.



TYPE No. 450.

Beautifully designed and faultlessly constructed, these Units uphold Philips reputation for excellency. They are completely reliable.

Type No. 372.—A High Tension Supply Unit A.C. Mains.

Price complete, £7 10s. 0d.

Type No. 508.—A High Tension Supply Unit for D.C. Mains.

Price complete, £3 17s. 6d.

Type No. 1009.—The Dual Battery Charger for charging High and Low Tension Batteries from A.C. Mains.

Price complete, £6 10s. 0d.

Type No. 1001.—A High Tension Accumulator Charger for A.C. Mains.

Price complete, £4 0s. 0d.

Type No. 450.—A Battery Charger for Low Tension Accumulators from A.C. Mains, charging 2-6 volts at 1.3 amps.

Price complete, £4 0s. 0d.

Type No. 327.—Is a Low Tension Battery Charger similar to Type No. 450, but charging 2-12 volts.

Price complete, £4 15s. 0d.



TYPE No. 503.



TYPE No. 1001.

Follow Philips—developments are coming rapidly. Watch for future announcements, keep Philips in your mind and remember always



TYPE No. 366.

# PHILIPS

## *for Radio*






**The Valves which made possible  
Radio Concerts from Seven Countries  
through the wonderful Cossor "Melody Maker"  
USE THEM IN YOUR SET**



# Popular Wireless

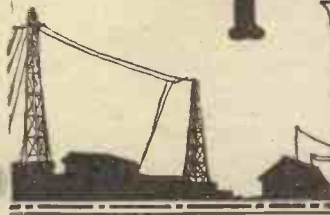

Scientific Adviser:  
Sir OLIVER LODGE, F.R.S.

Editor:

NORMAN EDWARDS, M.Inst.R.E., M.R.S.L., F.R.G.S.

Technical Editor: G. V. DOWDING, Grad.I.E.E.

Assistant Technical Editors: K. D. ROGERS, P. R. BIRD,  
G. P. KENDALL, B.Sc., A. JOHNSON RANDALL.



## RADIO NOTES AND NEWS.

### The Continental Relays—Regional Wireless—Have You Heard Harbin?—Eiffel Tower's Wave-length—Opportunity Knocks—The "Progressive" Four—A New Idea.

The World in A.D. 2000.

THE issue of the "Daily Mail" for January 1st, 2000, which I have obtained from the "Ideal Home" Exhibition, presents a somewhat nerve-racking picture of what the life and times of the human race may be then. Aircraft, radio and television bulk largely in the letterpress, which includes a "fill-up" to the effect that a crystal set dated 1923 has been placed in the British Museum, and an account of the murder by a woman of her husband, whom she shot at Tiflis "by a beam fired from some place unknown."

#### Our Chemical Lesson.

THE fact that a man was injured recently by the explosion of an accumulator, near which he had held a naked flame, renders it worth while to remind readers that a "gassing" accumulator is evolving an explosive mixture of gases. The "Manchester Evening News," I observe, informs the public that, when on charge, a battery develops sulphur dioxide gas, which is highly combustible. Except that it is not sulphur dioxide and that sulphur dioxide is not combustible in air, but will, in fact, put a light out, the "M.E.N.'s" chemistry is correct.

#### What "Gassing" Is.

WHEN an accumulator is fully charged, the chemical reactions between the electrolyte and "the plates" are completed. If the charging current is maintained after this stage is reached, it splits up the water of the electrolyte, so that the cell discharges a mixture of hydrogen and oxygen. Hydrogen by itself will burn but not explode; but when mixed with air, as it would be at the vent-holes of the battery, it will explode violently if a flame be applied to it. Moreover, a mixture of H and O also is explosive. But there is no danger at all unless a naked light or glowing body is very near the battery.

#### The Continental Relays.

THE line relays from Liège and Cologne were a great success, especially the Cologne job, and it looks as though for this particular work the line and submarine cable are more reliable and effective than the wireless relay. As a radio man, I

am chilled to the marrow at this, but as a "listener" I rejoice to think that the road seems clear to the extension of the B.B.C.'s programmes to the genius of capitals of Europe. Barcelona has one of the finest opera-houses in Europe. What about it, B.B.C.?

#### Tragedy of Imagination.

THERE was a young sailor of Bristol,  
Who thought he heard Mars on a crystal.  
But his friends wouldn't "bite,"  
So he shot himself right  
Through the head with a loud-speaking  
pistol.

#### More Listeners—or More Payers?

THE latest figures I have seen in regard to P.O. licences are little short of amazing. At the end of February the number of licence-holders in Great Britain was 2,451,051, an increase of about 33,000 over the January total. I read that the B.B.C. attributes this to the founding of new homes by marriages and the improvement of its programmes. But I am wondering whether it may not be partially

due to the prosecution by the P.O. of listeners who have sets without licences. Anyway, it looks as though the B.B.C. finances are on velvet—which is good for all of us. Or ought to be.

#### Radio and Employment.

LOOKING at that total of licence-holders, I cannot help smiling when I recollect that in 1922 a newspaper telephoned to me and asked whether I thought that the (then) proposed wireless telephone broadcasts would affect the unemployment problem. I said that I thought it would not affect it noticeably (which has proved correct), but that it would require the services of "hundreds of people." Well, I suppose I ought to have said hundreds of thousands. But at that time neither Sir J. Reith nor Captain P. P. Eckersley was appointed; in fact, there was no B.B.C.

#### More Sceptics.

MR. ELSTON'S letter in our number of March 10th, has caused a lot more sceptics to bob up. In a very piquant letter, T. M. (Tylorstown) suggests that the alleged loud-speaker results reported in respect of distant and numerous stations are nothing more than noises, because of distortion and "threshold" effect. I am afraid I must agree that there is a tendency to over strain reaction and amplification in order to get distant stations in the log, but so long as the signals are fairly recognisable I think reception may be claimed.

#### Limits of O-v-2.

T. M. says that with O-v-2 it is impossible to get pure full loud-speaker volume at more than 100 miles from Daventry or 25 miles from a local station, using a full P.M.G. aerial. I have not tried that, and will wait to learn readers' opinions. I will, however, say that my last set was a

(Continued on next page.)

### THEREMIN IN NEW YORK.



Prof. Theremin, whose "music from the air" recently created much amusement, some speculation, and a fair amount of controversy in this country, is now in New York, where he is busy endeavouring to mystify the Americans with his "magic box" (seen above). It is, of course, in essentials, an oscillating radio set, the "music" being controlled by a sort of hand-capacity effect.



## NOTES AND NEWS.

(Continued from previous page.)

straight det. with reaction and one L.F. stage, and on this 5 X X always came in at comfortable loud-speaker strength and only a little weaker than 2 L O; also, it was sufficiently pure in tone for domestic listening. Distance to 2 L O about 12 miles and to 5 X X about 90 miles.

## Regional Wireless.

I UNDERSTAND that there is to be a grouping of the northern English stations and that a choice will be given to the listeners of a "national" or a "regional" programme. The B.B.C. is no doubt working out its problems as well as it can, and I do not wish to obtrude premature criticism, but frankly I do not see the necessity for either of those kinds of programme. The average person, I am convinced, wants just a good programme, let it be as cosmopolitan as you please.

## The Right Idea.

TALKING of programmes, I recall that I have often said that the entertainment side of broadcasting ought to be run by people who have had successful experience in public entertainment. Hence, I note with subdued pleasure that this fact has been recognised and acted upon in America, where a Radio Programme Corporation was formed three years ago, run by men who have been brought up to cater for popular amusement. Cables and wireless are gradually joining forces! Why not broadcasting, music halls and theatres?

## Have You Heard Harbin?

REPORT says that C O H B (Harbin, China) has been broadcasting since January 1st on 445 metres. Has anyone here heard it? A pretty far cry, I admit, for such a long wave, but it is not an impossible performance. No doubt it can be recognised by the words "Chu Chin Chow," or by jokes about bobbed pigtails.

## Eiffel Tower's Wave-length.

DUE to the decision of the Washington Conference that the band for long-wave stations shall be 1,340 to 1,875 metres, the wave-length of the Eiffel Tower station, now 2,650 metres, is to be altered to 1,400 metres this year. It is probable that the power will be raised to 100 kw.

## Meat for Sceptics.

SINCE commenting upon Mr. Elston's letter, I have seen a report about Mr. W. R. Pierce, Junr., of Rhode Island, U.S.A. This gentleman is 17 years old, and claims to have logged 694 stations in 41 different countries, on a two-valve set. He says that the loudest European station is E A J 22, Salamanca. Yes, it would be. Well, gentlemen, let us pull up our socks and listen some more. Maybe we have missed one or two stations.

## Radio in America.

THE STOCK EXCHANGE gambling in shares of the Radio Corporation of America has attracted so much notice in the English Press that I have had a look at the R.C.A. balance sheet for 1927; it is sensational. Net income, \$11,799,659. After reserving for amortisation of patents,

income tax, foreign investments, pension fund and general reserve, the surplus is \$8,478,319. Machinery and tools are written down to \$1, and the patent account by \$1,000,000. After paying dividends of 7 per cent on Preferred Stock and placing \$4,500,000 to reserve for plant, the surplus is \$7,029,621, or something over £1,400,000. Wow!

## Opportunity Knocks.

K EEN radio amateurs are wanted by the Royal Corps of Signals, Territorial Army. You understand, no doubt, a good deal about radio in general, but here is a chance for you to get free instruction in its theory and practice and to be paid for it. Why not turn yourself from an amateur into a competent radio man.

## SHORT WAVES.

A loud speaker, with a radius of over four miles, has been constructed. This should give an added impetus to attempts to establish a new high-flying record.—"Humorist."

The only difference between electricity and wireless is that an electric installation often fuses and a radio refuses.

Many are grateful for the B.B.C.'s S.O.S.—pity.—"Daily Mirror."

Teacher: Can you name to me something that talks, sings and plays that wasn't in existence a hundred years ago?

Bright Pupil: Yes, me.—"News of the World."

In Athens there is a monument to Adam. But in every place where there is a loud speaker there is a monument to Eve.

## PERSONAL.

Young man with one pair headphones, five valves, two condensers, two tuning coils wishes to meet a young lady with some H.T. and L.T. batteries, two transformers, some busbar wire and a panel. Object: matrimony and a complete set.—"Radio News."

Uneasy lies the head that wears a crown. But uneasier lies the head that has fallen asleep with the headphones on.

Some critics of the B.B.C.  
Don't want these serious talks at all;  
They think the programmes ought to be  
Quite frivolous, or musical.

Time thus devoted is just rot,  
They say with frank hostility;  
And for the present they are not  
Devoted to the B.B.C.!

—"Bulletin and Scots Pictorial."

You never know when you may be glad of your knowledge and skill.

## Answer the Knock!

YOUR obligations are simply that you agree to present yourself for instruction for a certain number of hours per year; you can put in as much extra time as you like. You will receive expert instruction in radio and knowledge of the latest Army equipment, and a free fortnight's holiday at the annual camp in the summer, being, in addition, paid for every day at the camp. Call any day, 10 a.m. to 2 p.m. at 56th (1st London) Divisional Signals Headquarters, 51, Calthorpe St., London, W.C.1.

## A Real Beginner.

MR. J. R. ARMSTRONG KELLY, Donnybrook Estate, Box 180, Salisbury, S. Rhodesia, who is growing baccy and amusing himself with chess and one newspaper a week, got hold of a copy of "P.W.", the first radio paper he had

ever seen, and is now filled with a divine discontent. He wants to build a set, and wonders whether a "P.W." reader will advise him how to go about it. As this may be the nucleus of a "P.W." colony, I propose to spend another paragraph on Mr. Kelly.

## Which Shall He Build?

OUR friend wants to be able to receive J B, 500 miles away, besides England, America and Continentals, if possible. Moreover, situated as he is, he requires data as to all the necessary parts and their prices, delivery free by parcel post via Beira, for cash with order. Here's a chance for some kindly reader, or a club, to use experience in the cause of radio and work out a complete specification; but for the learner's sake I recommend that a set be chosen for which a "P.W." back number can be supplied.

## The "Progressive" Four.

I MENTION that because there is no doubt that "P.W.", "M.W." and "Constructor" articles have made construction as simple as A B C. As proof of this witness a letter from E. B. (Barnham) to Mr. P. W. Harris. E. B. says that he has no less than 25 youngsters making up the "Progressive" Four, only one of whom has made an error. Our Mr. Dowding, designer of the set in question, is having his hats made to measure now. E. B. hopes that Mr. Harris is keeping in the best of spirits, and Mr. Harris, authorises me to say that he is very "well preserved" indeed.

## Transmitting Note.

WILL all who are interested in observing amateur transmissions note that Mr. C. A. Webb, 38, Oakhill Road, Putney, S.W.15, has been allotted the call sign 5 W B, and transmits on 90 metres and 150-200 metres. He would be glad to have reports about the signals from all and sundry, either in this country or any other.

## Readers' Results.

AN analysis of the letters on hand shows that the most popular "P.W." circuit published this year is the "Sydney" Two, and the results obtained with it prove that it can do what was claimed for it. Most of the writers succeeded in getting Australia, though the rest got a number of American stations and are no less enthusiastic in their comments.

## A New Idea.

A THREE-MILE swim in the river Yarra was the cause, earlier this month, of a lot of public interest in Australia, and 3 L O broadcast an account of the race from start to finish. Now why not apply the same idea to Channel-swimming, so that there shall be no more dubious hoaxes. We could go to bed knowing that the swimmer was half-way across and catching buns as cleverly as a seal catches fish, and wake to learn that he or she is in sight of Dover Harbour but involved in a school of mackerel which is tickling him or her and impeding progress with laughter, etc., etc.

ARIEL.



**I**F you possess a two or three-valve set using a detector valve and one or two low-frequency stages (in all probability you do, because this is the most popular type of set in this country), and if you have an old gramophone or some apology for a gramophone, you can very simply arrange your own programmes, just how and when you want them, and with very little expense.

You have all heard of the gramophone pick-up, that little device which is fitted on the tone-arm of a gramophone in place of the usual sound-box, and which when connected up to an amplifier, enables you to reproduce the record placed on the gramophone *via your loud speaker*, the reproduction being, in most cases, very much better than that obtainable with an ordinary gramophone.

#### Not Expensive.

When you are using a pick-up, you do not use the gramophone at all, the only portion of the instrument that you employ is the tone-arm and the turn-table, which of course means the motor as well. So you see you may have a hopeless gramophone, when considered from a gramophone point of view, but as long as the turn-table and motor are all right and capable of running at constant speed, and as long as there is a tone-arm (which by the way you can purchase for about five or six shillings if the one you have is badly battered), you have all the elements of a gramophone as required for pick-up work.

If you have not such a gramophone, have no motor or turn-table, you can very easily buy one for about thirty shillings, a really reliable one, and this, mounted on a box with a suitable tone-arm and a pick-up, will provide you with all the pleasure you could get from a thirty or forty guinea gramophone, provided, of course, that your set is reasonably pure in reproduction, and that you have a reasonably good loud speaker. A pick-up, such as the Lissen, can be obtained for 15s. only.

#### No Set Alterations.

Now what do you have to do to make that pick-up work with your set? As I said before, all that has to be done is to fix it on to your gramophone tone-arm and then set the motor going with the record, place a needle in the pick-up, and lay it on to the record, and that is that end of the business. The other end consists in connecting the two ends of the pick-up, which by the way should be of the high resistance variety, to your valve receiver.

No alteration in this latter is necessary. All you need is a little adaptor which you can plug into the detector valve holder of the set, the valve being placed on the top of the adaptor, which has special sockets for it. The adaptor is connected to the two ends of the pick-up.

Suitable plug-in adaptors are available for practically any pick-up at varying prices from about 3s. 6d. upwards. There

## "PICK-UP" PROGRAMMES



Why not "broadcast" your own musical items? This is easily done, as this article shows.

By K. D. ROGERS.

may be slight alterations necessary in the set if you use a four-pin adaptor, because the original grid circuit of the set should really be broken.

But if you use an adaptor that only has three pins, or if you are supplied with an adaptor with four pins and you cut off the grid pin of the adaptor, leaving the socket,



A neat little pick-up that is marketed for the modest sum of 15s.

then your set will be absolutely fool-proof as regards the pick-up. All you have to do is to connect the pick-up between the grid socket of your adaptor, which will of course, have a little terminal, and one filament pin, the filament pin, making contact with its socket.

#### Collecting the "Pick-up."

Now you must choose that filament pin so that it plugs into the filament socket of your detector valve holder in the set which goes to L.T. negative. If you connect it to the one which plugs into L.T. positive you will find that you get distortion, because the valve will be operating at the wrong end of its curve, and you will be running into grid current.

So all you have to watch for is that the adaptor on your pick-up plugs into your valve detector sockets in such a way that the filament pin which is connected on the adaptor to the pick-up, plugs into the filament socket on the valve holder which is connected to low-tension negative. Whether it goes to L.T. negative through a rheostat

or not does not matter.

The plate pin, of course, will go into the plate socket and the grid pin is already cut off, so that the grid of the adaptor only makes contact with your pick-up and the valve, and does not plug into the grid socket of the original valve holder in the set.

#### Simple Volume Control.

The valve is inserted in the adaptor, which itself is inserted into the valve holder on the set. The set is switched on, the pick-up laid on the record, and there you are. The music comes out of the loud speaker. Nothing in the set has to be altered at all, neither H.T. nor grid bias.

It is useful in pick-ups to have a volume control. This usually consists of a 500,000-ohm potentiometer, which is connected right across the pick-up, and the slider of the potentiometer is then taken to the grid socket of the adaptor, instead of the end of the pick-up being taken there, so that you have the pick-up across the volume control, the slider of the volume control going to the grid socket of the adaptor, and then the filament pin and the volume control going to the other end of the pick-up.

I hope I have made this reasonably clear. It is rather difficult to make it quite clear in a short article, but the few points you have to watch when fitting a pick-up to a set are just those mentioned, and the rest entails no alteration or particular care whatsoever.

#### Further Details.

A detector with one stage of note magnification is quite enough for most records, but if you have two stages of note magnification so much the better. Should you have an H.F. valve in front of the detector, it should be switched off. It need not be disconnected, just the filament turned out, or the valve removed while the pick-up is in action. For pick-up work you use just the detector and the note magnifying stages.

For those who are more interested in pick-ups and gramophone work in conjunction with their sets I would draw their attention to the special gramophone section in "Modern Wireless" every month. This section goes into the matter far more deeply and gives details concerning the use of pick-ups with various sets, discusses records suitable for pick-up work, different types of pick-ups, hints and tips and so on. You will find it worth while to try your set as a gramophone reproducer and once tried I do not think you will regret the initial outlay and trouble.



# "SECRET FORCES" & TELEVISION.

By THE EDITOR.

WHAT is the secret behind all the conflicting statements about television? is a question Mr. William J. Brittain asked during his lecture on "My Television Journey" to the Hull Literary and Philosophical Society. Mr. Brittain pointed out that Mr. Baird has been able to announce that he has flashed a face across the Atlantic and enabled a sweetheart in London and her lover in mid-ocean to meet.

The Bell Telephone Company in America has achieved a demonstration of television in the home, and television sets are now on sale in London, and books and periodicals concerning television seem to be taking up the subject with great gusto.

"But," said Mr. Brittain, "against these amazing evidences of progress have been put up a series of statements by eminent scientists suggesting that television is years away, and culminating in a £1,000 challenge to Mr. Baird to give a television demonstration of five simple objects."

## "Ducks and Drakes."

Mr. Brittain suggested that there was a secret behind these two "opposing tornadoes" which nullified each other, and left the ordinary man wondering what way, if any, the television wind was blowing.

Mr. Brittain then proceeded to make a statement which calls for explanation. "It is necessary," he said, "for the public to know of these two secret and powerful groups which are playing ducks and drakes with the fortunes of television."

Exactly what Mr. Brittain means by that statement we are at a loss to know. But in the course of his lecture he went on to say that television has been achieved by Baird and by two large Companies in America, and other workers such as Jenkins in America, Dieckman and Mihaly in Germany, and Belin and Holweck in Paris, all of whom are doing excellent work.

## "Crude Toys."

"It must be realised, however," continued Mr. Brittain, "that only a face and shoulders of a person have been televised. It must be remembered, too, that television across the Atlantic is an achievement of little more difficulty than televising from one room to another. A scene at a theatre or a horse race cannot be attempted. And the sets now on sale are but crude toys which would not receive television if it were being broadcast. Machines equally advanced were made last century.

"In trying to realise what is the exact position of television," said Mr. Brittain, "the public must know of the two opposed forces, take the statements of both sides, and find the truth between the two."

In making statements like this, Mr. Brittain—no doubt quite legitimately in his rôle of popular lecturer—suggests that there is some "secret force" at work, and the innuendo is undoubtedly that POPULAR WIRELESS is one of these forces. But we would again point out that there is nothing secret in our desire to clarify the position with regard to television, and there is certainly nothing secret in our attempt to

warn amateurs that they must take a very large pinch of salt when they read in the daily newspapers the exaggerated and sensational statements in connection with television.

Make sure of your copy of the  
April double number of

## MODERN WIRELESS

which contains a

## SPECIAL SOLODYNE SUPPLEMENT

showing several versions of the incomparable "Solodyne" set. With these details you can make a Solodyne using components already on hand.

Don't miss this magnificent radio magazine.

APRIL DOUBLE NUMBER

## MODERN WIRELESS

ON SALE MARCH 30th. Price 1/6

Adverse criticism of a new branch of wireless science like television is undoubtedly not going to be popular. We have risked earning unpopularity among a large section of our readers in being so



A novel test for a tuning coil is to make it light a Neon lamp by power picked up from a local oscillator.

candid with regard to television, but we have done so because we feel that in the long run if we were to follow in the footsteps of those hysterical people who, on the strength of certain crude experiments which eminent scientists regard as the limit certain systems are capable of achieving, and attempt to convince the public that television in the home is very nearly an

accomplished fact, and that before very long a real television service will be started, we should be far more unpopular!

We have yet to find, as we have already stated, any scientist of repute who will substantiate fantastic television theories; just as we have yet to find a scientist of repute who will be so dogmatic as to state that true television will never be possible.

We again reiterate that our views, concisely expressed, are these: That by the known systems of television, especially the mechanical systems, the optimistic forecasts of television critics will never be realised. And we again reiterate that not until System X (which is the unknown system) has been discovered will it be possible for moving pictures, in any reasonable detail, to be televised by wireless.

Mr. Brittain, we suggest, should carefully read the articles we have published in connection with television in this journal and in "Modern Wireless," and in particular we would draw his attention to the details of the challenge which we issued to Mr. Baird, which, by the way, he has not yet accepted.

Mr. Brittain is undoubtedly a journalist who has devoted considerable time and attention to the various television systems being experimented with in various parts of the world and, with certain limitations, we have a respect for his opinions. But when he suggests that there are secrets behind television, and when he talks about two opposing forces, he is allowing his journalistic imagination to run away with him.

As far as we are concerned, our challenge to Mr. Baird was made in all friendliness, and only because Mr. Baird has so many good friends that they are inclined to put him on a pedestal and to acclaim his pioneer work as the final achievement of a genius who has solved the television problem and made it possible for amateurs to build their own sets at home, and so ultimately receive moving pictures by wireless from broadcast television stations.

## P.M.G. and Television.

That such a contingency is not likely at the moment, and indeed, not until some really reliable system has been invented, is borne out by the fact that the Postmaster-General stated recently in the House of Commons that wireless licences covering experiments in television have been issued to a number of persons, and he understood that tests had been carried out; but his technical advisers considered that the matter had not yet advanced beyond the experimental stage.

We can only repeat that we thoroughly agree with the scientists whom we have consulted on the problem of television and whose general attitude may be summed up in the concluding words written by Sir Oliver Lodge in our issue for March 17th. We venture to close this article by repeating the conclusion to Sir Oliver Lodge's article on "The Problem of Television":

"No one can say that anything is finally impossible; but it is fairly safe to say that a given development has not yet been achieved. As far as I know about the attitude of other scientific men I think I am in agreement with them. I shall rejoice if the labours of Mr. Baird and other workers in this country, and in America, are able to falsify this caution within what remains of my own life-time."



THIS little unit has been designed to meet the demand for an amplifier that is capable of giving a consistently good degree of amplification without distortion, whatever the set used in conjunction with it, and provided one does not try to work off a super-regenerative or a really fierce reflex set, it fulfils this condition admirably.

It has other advantages in its compactness, simplicity, and low cost; and provision is made for the use of a gramophone pick-up without interfering in any way with the receiver in general use.

The circuit employed is shown on another page and it will be seen that the first valve is coupled to the set with which it is to be used by means of an L.F. transformer, the coupling between the first and second valves being through a standard R.C. unit. The transformer stage is placed first to render the amplifier more adaptable, as it would be impossible to use a resistance-capacity coupled stage immediately after a reflex set such as the Hale or Trinadyne, for which a valve having a low amplification factor is essential.

#### Connecting a Pick-up.


The jack which breaks the connections between the secondary of the L.F. transformer and the grid-grid-bias circuit is to

#### LIST OF COMPONENTS.

- Panel, 8 in.  $\times$  6 in.  $\times$   $\frac{1}{4}$  in. (any good branded material, Becol, Ebonart, Radion, Red Seal, etc.).
- Cabinet to fit, 6 $\frac{1}{2}$  in. deep (original is by Peto-Scott).
- L.F. transformer (Lissen in original amplifier).
- R.C. Unit (Dubilier in original. Any good make, Lissen, etc.).
- 2 Sprung valve holders (Benjamin, Bowyer-Lowe, B.T.H., Burndept, Burne-Jones, I granio Lotus, Marconiphone, Pye, W.B., etc.).
- 2 Fixed resistors (Burne-Jones in original. Any similar type, such as Cyldon, Dubilier, etc.).
- L.T. switch.
- Double circuit jack and plug (Lotus in original. Any good make, Bowyer-Lowe, Igranio, etc.).
- Terminal strip, 5 in.  $\times$  2 in.  $\times$   $\frac{1}{4}$  in.
- 8 Terminals.
- Wire, screws, etc.

facilitate the connection of a gramophone pick-up of the high resistance magnetic type. It is not always possible to plug an adapter into the detector valve holder, as it may happen that there is no detector valve; the amplifier may be intended for use with a crystal set, or with a set employing a crystal detector, and in this case the pick-up is connected to the plug, which, when inserted in the jack, cuts out the

## The "Pocket Money" Amplifier

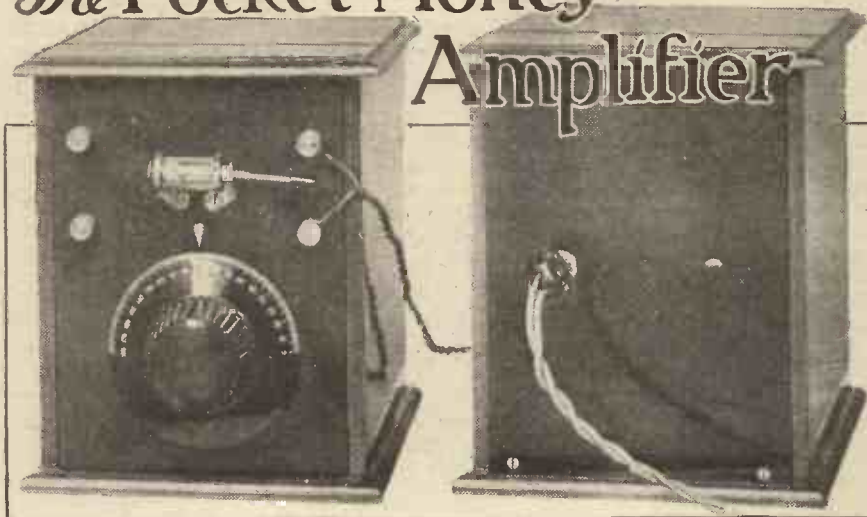

You can use this instrument with practically any set or with a gramophone pick-up. It gives extraordinarily good results although it is, as its name suggests, inexpensive and easy to build.

By the "P.W." Technical Staff.

secondary of the transformer and brings the pick-up into circuit instead.

The instructions given by the makers of the various pick-ups on the market state that the leads on the adapter should be changed over to find which connection gives the better results. This is to ensure that the pick-up is connected across the grid and grid return leads; with the amplifier this is unnecessary, as the jack contacts are already connected in the correct manner.

#### Very Simple.

Can see at a glance the simplicity of the lay-out, and the few holes which have to be drilled, the largest of which is  $\frac{3}{8}$  in. in diameter, and which is to accommodate the double-circuit jack. The hole for the L.T. switch is only  $\frac{1}{8}$  in. diameter, and those for the wood screws  $\frac{1}{4}$  in. counter-sunk to take the heads of  $\frac{3}{8}$  in. No. 3 wood screws.

The terminal strip should then be drilled according to the diagram provided, and the panel and strip may be fitted to the

base board. When fitting the terminals to the strip it is as well to cut off the projecting shanks and fit soldering tags under the nuts.

This will be found of great assistance when wiring, as the bottom row of terminals will be rather difficult to reach otherwise. The other components may now be secured to the baseboard as shown in the wiring diagram, and here are one or two points worthy of consideration.


The L.F. transformer and R.C. unit should be kept as close to the panel as possible, to allow the valve holders to be

kept away from the terminal strip, and before fitting the fixed resistors to the baseboard, turn the soldering tags round so that instead of being at right angles to the resistor, they are in line with it. They may then be placed quite close together, and the wiring will be simplified.

#### The Wiring.

This latter operation needs a little more care than is usually required, and it is essential that insulated wire should be used. The original amplifier was wired with Glazito

(Continued on next page.)

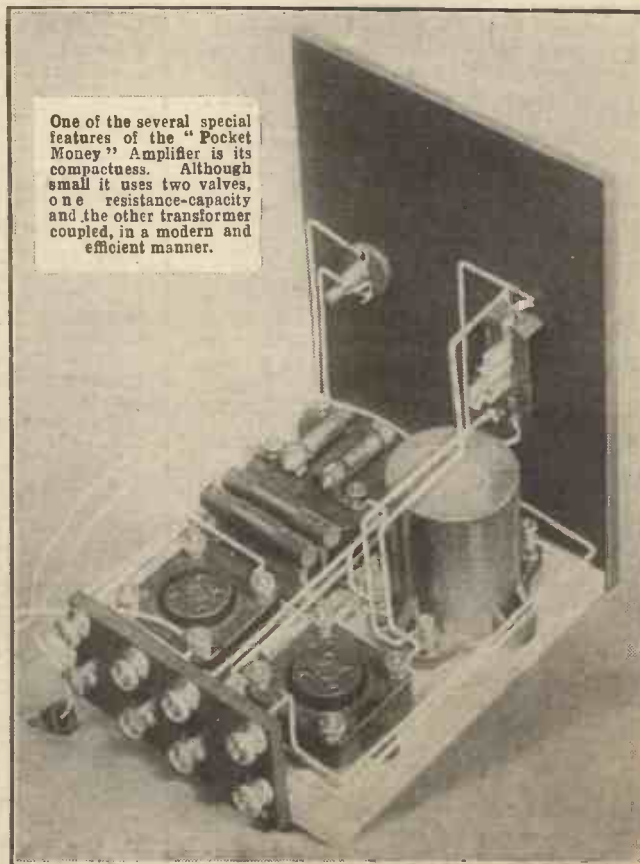



## THE "POCKET MONEY" AMPLIFIER.

(Continued from previous page.)

which, besides giving a neat appearance, is a perfect safeguard against short-circuits.

The query which always seems to crop up with this sort of wire concerns the best means of removing the insulation, at the same time leaving a clean end. The most satisfactory method, I find, is to cut it off with a sharp penknife by making a cut round the wire, and sliding the end off. Naturally, the cut must be right through the

tags a lot of bother will be avoided, and this part of the work greatly facilitated.

The only flex leads in the assembly are those to the grid-bias battery, which is fitted in the back of the cabinet. The battery actually used was one made by Siemens, and this is provided with a cardboard flap which can be fixed to the cabinet by drawing pins. This, of course, is the 9-volt type, which is quite sufficient in the ordinary way, but should it be desired to use a super-power valve in the second stage, or at least, one which requires more than 9 volts grid bias, the battery will have to be placed outside the cabinet, and the leads extended.

### Operating the Amplifier.

A few notes on the operation will not be out of place, and it may be mentioned that with standard R.C. and power valves the results obtained were really most satisfactory. Using a P.M.1 in the first stage and a P.M.2 in the second, the amplifier was tested in conjunction with a crystal set, a straight single-valver, and a single-valve reflex.


A B.T.H. B4 was used in the two single-valvers, and

with each of them a most satisfactory degree of amplification was obtained. A gramophone pick-up was tested at the same time, and the volume delivered from the loud speaker was more than sufficient for any ordinary room. With the crystal sets the results were equally gratifying, but it was, of course, necessary to earth the L.T. negative terminal. This should also be done if a pick-up only is connected to the amplifier.

### With Super-Power Valve.

To ascertain the performance of the amplifier under really strenuous conditions, it was again connected to the straight single-valve set, and the P.M.2 replaced by a P.M.252. The pick-up was refitted to the

(Continued on next page.)

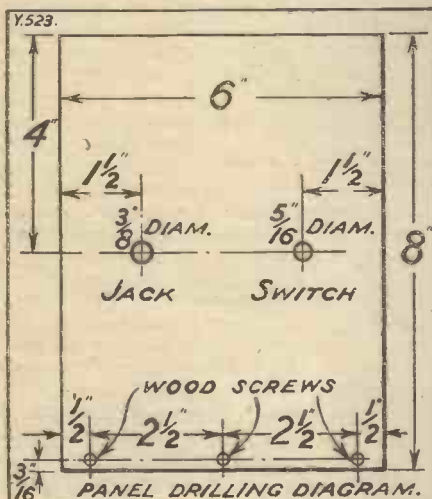


insulation, and must go right round the wire, but after a few attempts one acquires the knack of peeling it off as neatly as could be wished.

As the valve holders and, in fact, all the components except the resistors, switch, and jack have both terminals and soldering tags, one can carry out the wiring—which is not complicated—in the manner to which one is most accustomed.
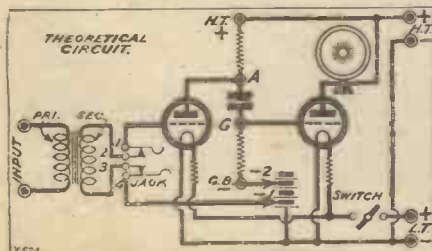
### Grid Bias.

The wiring itself, although needing care, is quite simple and there should be no difficulty experienced in carrying out this operation quite satisfactorily; the leads to the terminal strip being those which may prove a little tricky. To try to use a very



large soldering iron for these joints is hopeless, as there is not a great deal of room between the valve holders and the terminal strip, and to accomplish the soldering of the various leads to the terminals with any degree of success, a half-pound iron will be found essential. By cutting off the surplus terminal shanks, as suggested at the beginning of this article, and fitting soldering

### POINT-TO-POINT CONNECTIONS.

Input terminals to OP and IP terminals of L.F. transformer. L.T.—terminal to H.T.—terminal, G.B. positive, and to one filament terminal of each valve holder. L.T. positive to one side of L.T. switch; other side of switch to one side of each fixed resistor; other side of each resistor to remaining filament terminal of corresponding valve holder.

Grid terminal of 1st valve holder to No. 1 contact of jack.

No. 2 contact to OS terminal of L.F. transformer.

No. 3 contact to IS terminal of L.F. transformer.

No. 4 contact to G.B. — 1.

NOTE.—Nos. 1 and 4 contacts are the two longest, and are the outer spring contacts.


Plate terminal of 1st valve holder to "A" terminal of R.C. unit.

"H.T." terminal of unit to H.T. positive terminal, and to one L.S. terminal.

"G" terminal of unit to grid terminal of 2nd valve holder.

"G.B. —" terminal of unit to G.B. — 2.

Plate terminal of 2nd valve holder to remaining L.S. terminal.

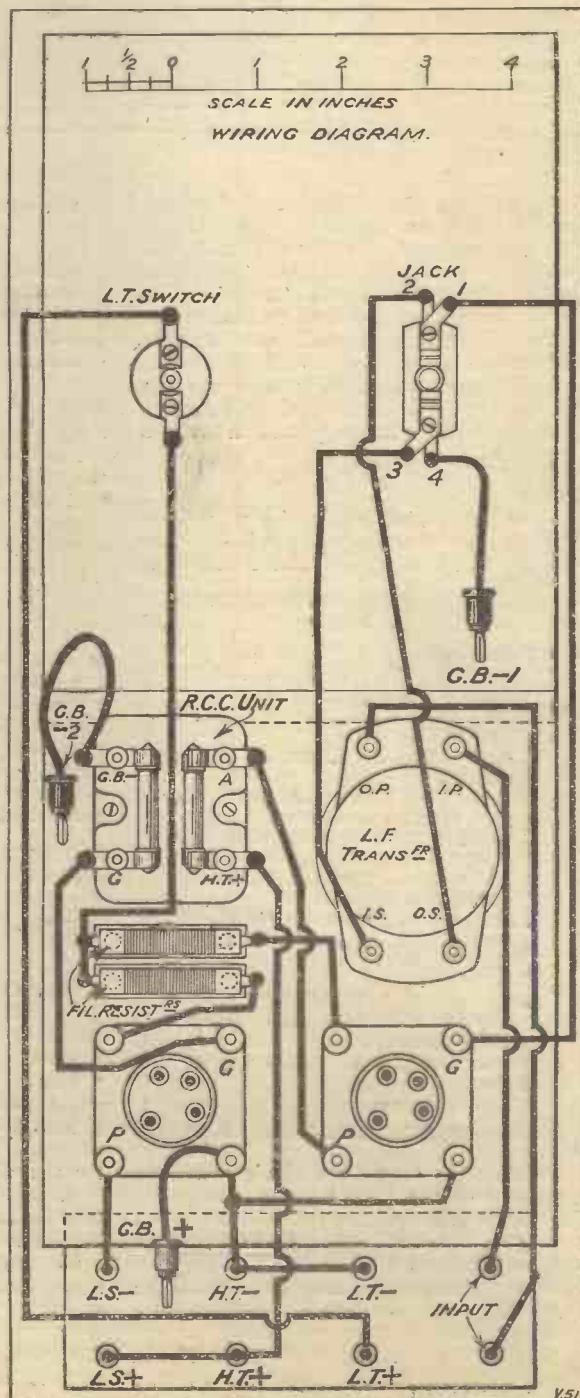



## SOME PRACTICAL POINTS.

Generally speaking, the *higher* the aerial the better.

The use of a large shell insulator instead of a metal pulley will avoid the jamming of halyards at the mast head.

It is unsafe to use rope as a stay for masts, but the seven-strand galvanised wire sold for clothes lines is both cheap and effective.

If your earth is a buried one it is a good plan to drive a length of metal piping in the ground, and occasionally to pour water down this so as to moisten the soil around the earth plate.

If two equal resistances are connected in *series* with each other the total resistance is *twice* that of the resistance.

If two equal resistances are connected in *parallel* with each other the total resistance in the arrangement is *half* that of one of the resistances.

The permanent magnets of telephones or loud speakers are injured by mechanical shocks, so that the efficiency is lowered every time they are dropped or knocked over.

## THE "POCKET MONEY" AMPLIFIER.

(Continued from previous page.)

4-pin adapter, and plugged into the valve holder of the single-valver; the detector valve was replaced. Unfortunately a large loud speaker was not available, and the one in use began to chatter when a fairly loud record was played, but on broadcasting the results were excellent.

The whole amplifier may be constructed for less than £2.

## SOME HINTS FOR THE CONSTRUCTOR.

How wireless receivers should be built.

By W. W. D.

**W**IRELESS-SET building these days has become more or less of a strenuous business, the amateur being so filled with all sorts of designs, blue prints, etc., gratis, that he finds that he really does not know exactly which type of set to build.

Not knowing much, and perhaps nothing about wireless, he looks at all and sundry and decides upon a particular set which appears so very simple to build. So off he goes, and this is where the advice part of this article comes in.

First of all, if you have decided upon the set you intend to build, **BUILD IT**. That is to say, get on with it and do not attempt to alter it half way through just because Jack Jones has another type that works so well, etc.

### Follow the Directions.

Yours will work equally as well, perhaps better, so do not be misled. Remember the people who have written up the article on the set you are going to build **KNOW** something about it; and perhaps Jack Jones doesn't, and he may be the means of making your set a failure.

Immediately you begin you will find heaps of pals who have built sets galore, and rest assured you will **NEVER** build the **RIGHT** set; they all know better what you **SHOULD** have done.

Carry on is the advice, and be careful to carry out the instructions, and you may then rest assured you will get a **SET** all right.

Another piece of advice is this, that when you get going nicely **DO NOT** experiment with it. Remember that the people who wrote the article have already done all the experimenting necessary, but leave the set alone; and if you are then enthusiastic, try and get some more parts and do your experimenting. Then, when you feel that you want a change, try to make a deal with the first set.


### Buy British.

The great point is this, that if you bought a piano or a gramophone you would never dream of tampering with it, so why tamper with a wireless design?

Don't be in a hurry; do all the work **WELL** and do not buy the very cheapest goods you can; it will not pay, and if you really take care and do as suggested by the article you will assuredly get a set that will be a pleasure and not a source of trouble.

Remember this and, if you like, call it a maxim. **ANYTHING** will **NOT** do for wireless, and that there is **NOTHING** **TOO GOOD** for wireless. Get the best you can afford, and by doing this you will save yourself no end of trouble later on, if not at the start.

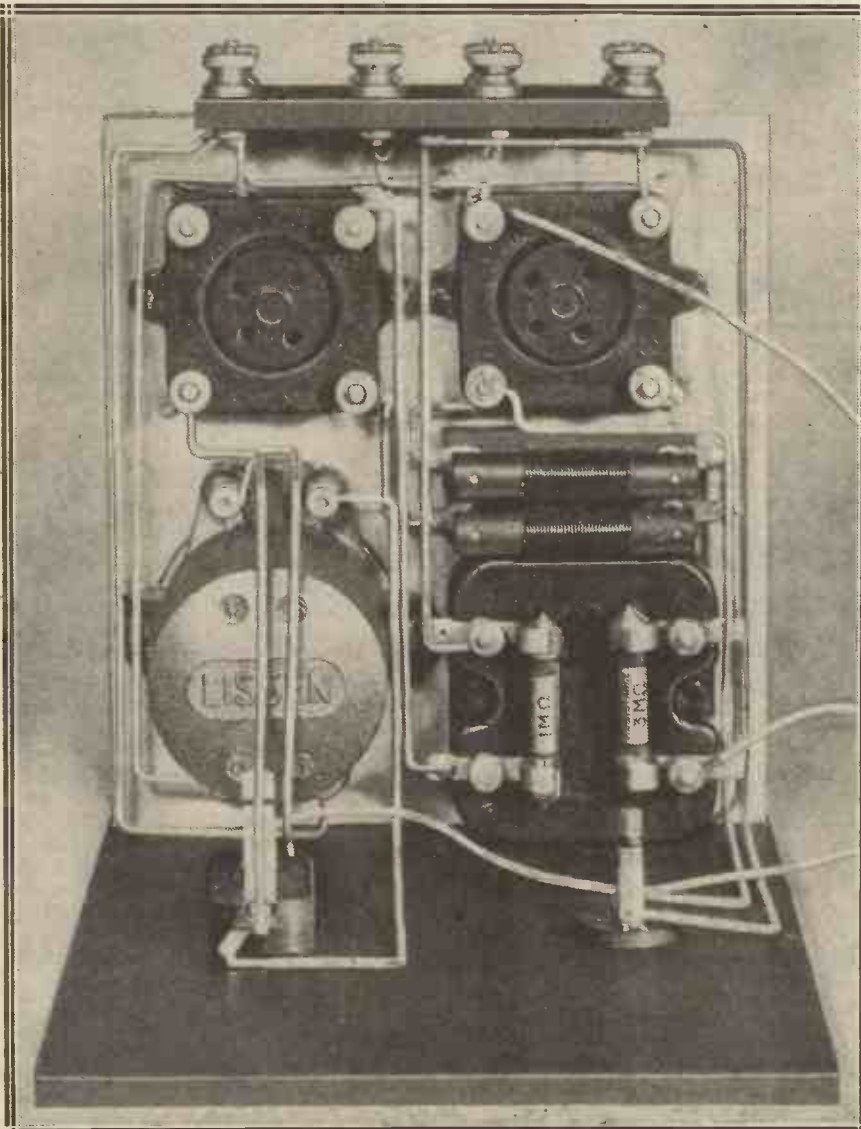As a last word, do not buy unknown valves, etc.; be British and **BUY** British goods. **THEY ARE THE BEST.**



On the left can be seen the connections to the jack of the amplifier, while on the right is the L.T. switch. Note the symmetrical and compactly grouped lay-out of components. The wiring is quite straightforward and is facilitated by this design.



## TECHNICAL NOTES.

By Dr. J. H. T. ROBERTS, F.Inst.P.

**A NOVEL ACCUMULATOR**

Kw. AS MEASURE OF POPULARITY—AN INTERESTING LECTURE.

## A Novel Accumulator.

READERS will remember that I mentioned, a short time back, an invention which had been sent to me in connection with accumulators and liquid rectifiers. This invention being for the purpose of igniting the mixed hydrogen and oxygen evolved during the working of the cell and converting back to water so as to avoid the necessity for topping up.

Several readers have written to me to point out that the ignition of these gases would probably fracture the containing vessel.

This, of course, is the first thing that occurs to one's mind, but you will remember that I remarked, at the time, that the case of the accumulator or rectifier should be made stronger than usual. At the same time those who have written to me may have perhaps an exaggerated idea of the instantaneous pressure developed when the mixed gases are ignited. If the ignition spark occurs sufficiently frequently the pressure developed may be comparatively small. In any case I understand that this invention has been fully tried out and that it is about to be adopted in the United States, so I suppose any possible snags of the kind which immediately suggest themselves have either proved to be of no serious account or else have been overcome.

## Kw. as Measure of Popularity.

It has often been suggested that a useful addition to the multitude of meters and indicating systems employed by a broadcast transmitting station would be one which indicated the popularity of the programme or particular item which was being transmitted at the moment. Such a meter would, for instance, "go up" when any of the various types of popular item was being broadcast, but would certainly "go down" wherever a talk came on. Its indication would be equivalent to a sort of instantaneous referendum from the listening public as to the acceptability or otherwise of the item in question. Suggestions have, in fact, been seriously put forward that a kind of "absorption meter" might be provided, indicating the amount of the radiation from the transmitting station which was being absorbed by wireless aërials.

The above-mentioned idea forms excellent material for the humorist and the wag but, curiously enough, a meter has been found which, in a sense, gives an indication of the amount of listening-in. It proves to be none other than the load meter (or set of such meters) at the New York Edison Company's power station, and it might be said that the kilowatt hour has provided a "measuring stick" to determine the relative popularity of broadcast features. According to Mr. Arthur Williams, the Vice-President of the New York Edison Company, there was about 6,000 dollars' worth

of extra electricity consumed on the night of the Tunney-Dempsey fight, which was attributed to people staying up late to listen to the description of the fight and to read the newspaper accounts that appeared in special editions shortly afterwards. The extra load carried by the company's generators did not fall off until about three o'clock in the morning.

## An Interesting Lecture.

Those of you who are interested in the development of short-wave work and particularly of the Beam system, will find a very valuable paper in a recent issue of the Proceedings of the Institute of Radio Engineers (Volume 16, No. 1). The paper in question is by Senatore Marconi, and is very long and comprehensive, covering over 40 pages. It is a most useful and interesting history of the development of radio communication in general and, of course, deals specially with the experiments leading to the Beam system with which Senatore Marconi has been particularly associated. The paper is one which, in any case, cannot fail to prove extremely interesting to all wireless experimenters whether they specialise in short-waves or not.

(Continued on page 208.)

## TRACKING THIEVES TELEGRAPHICALLY.



By means of the latest apparatus for transmitting photos, it is now possible to send very full descriptions of suspected or "wanted" malefactors either by radio or by land-line. Above is a "warrant," complete with finger print, received by the Berlin police by the Lorenz-Korn system. It is not television, for the process demands some minutes to "get over" just the one picture, but the result is remarkably successful.

## NEWS FROM SAVOY HILL.

## FROM OUR OWN CORRESPONDENTS.

**PROGRAMME PLANS FOR EASTER**

NEWCASTLE'S SCANDINAVIAN PROGRAMME—LIVERPOOL FEATURES.

## Programme Plans for Easter

IN accordance with the practice of the B.B.C., the programmes on Good Friday, April 6th, will be in keeping with the solemnity of the occasion, the hours of transmission being restricted to those of an ordinary Sunday, except that there will be no break between the afternoon and evening programmes. The afternoon concert from London will be given by the Casano Octet, following which, at 5.15 p.m., a Children's Service, conducted by the Rev. A. R. Brown Wilkinson, M.C., of St. Christopher's College, will be relayed from Bournemouth.

At 6 o'clock Masfield's play "Good Friday" will be taken from Glasgow, and at 7 o'clock a service will be heard from St. Anne's Church, Manchester. The evening concert will take the form of a National Symphony Concert, conducted by Sir Henry Wood, and relayed from the Queen's Hall, the music from which will consist of excerpts from Wagner's "Parsifal." The interval

will be made between 8.50 and 9.10 p.m. for the news bulletin and local announcements.

The programmes from 5 G B consist of a performance of the St. Matthew Passion by Bach, the great sacred music drama which was first performed at Leipzig on Good Friday, 1729, since when it has become firmly established as one of the finest sacred musical works of all time. Later there will be a concert of chamber music followed by a religious service from Manchester, and then a concert of vocal and instrumental works provided from London.

Easter Sunday will be marked by the broadcasting at 10.30 a.m. of Matins from York Minister with an address by the Archbishop of York. This service will be heard from London and 5 G B, as well as other stations. The afternoon programme from London is to be provided by the Wireless Military Band, while the evening service

(Continued on page 205.)




A VERY popular receiver has three valves. The first is a detector, that also provides reaction, which is resistance-capacity coupled to the second valve. The second valve is transformer-coupled to the third or output valve.

Such a receiver may be connected as in Fig. 1. Here  $R_1$  is the anode resistance joined to the detector valve,  $C$  the coupling condenser, and  $R_2$  the grid leak;  $T$  is the transformer that is used to couple the second and third valves. You will notice that a common high tension is applied to all three anode circuits, and that a bypass condenser,  $C_1$ , of 2 microfarads is connected across the high-tension battery.
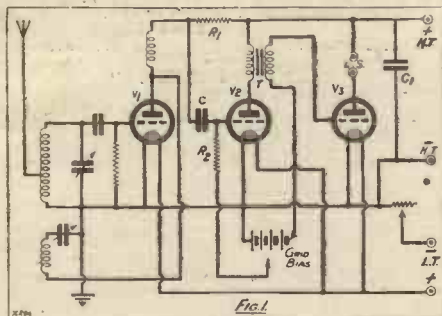
#### "Common" Batteries.

A common grid-bias battery is also used, but only a small part of it is applied to the grid of valve  $V_2$  through the grid leak  $R_2$ . The point we wish to bring out is that the receiver has one battery for the high-tension circuits, one for the filaments, and one for the grid circuits. It therefore follows that if either of these batteries have resistance the valves have a common coupling. This is undesirable.

We can ignore the filament circuit and for the moment the grid circuit. We will confine ourselves to the high-tension supply.



and the anode circuits of the valves. The internal resistance of a new battery is generally negligibly small, but after it has been used for a length of time, depending on its capacity and the construction of the battery, its resistance increases to such a value that the behaviour of the circuit is modified.


When the high-tension circuit has a negligibly low resistance it is quite fair to assume that the amplification-frequency characteristics of the receiver are exactly what one would expect them to be from a knowledge of the characteristics of the individual stages. We can, in fact, look upon the circuit as though it had separate high-tension batteries for each valve. But when the high-tension supply has an appreciable resistance the individual anode circuits are no longer isolated. They are united through a resistance common to them all.

#### Cause of "Howling."

This greatly modifies the performance of the receiver. Distortion may be produced, "motor-boating" may occur, and, in some cases, a howl may be emitted by the loud speaker.

You will see, that the behaviour of the

## MAKING YOUR SET STABLE

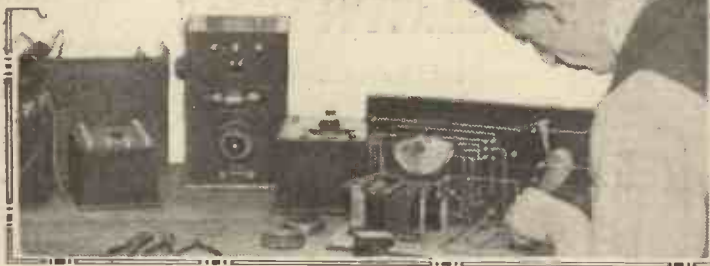

How, in an inexpensive and simple manner, you can eliminate howls and other noises due to battery coupling and, incidentally, make your H.T. batteries last longer.

By W. JAMES.

receiver must change when resistance is present in the high-tension supply, if you consider what happens when a signal is applied to the last valve. The anode current of this valve rises and falls according to the signal voltage applied to the grid. This varying current flows through the loud speaker, and, of course, actuates it, but it also flows through the high-tension supply. Voltages corresponding to the signal are, therefore, produced across the high-tension supply. But the same high tension is applied to all three valves. Therefore, the varying voltage is applied to all the valves. This is passed through the amplifier and tends to increase or decrease the fluctuating currents.

#### Preventing the Trouble.

In back cases the coupling produces a howl which shows that self oscillation has set in. The problem is, therefore, how best can one arrange the circuit that the evil effects of the resistance of the high-tension supply are minimised.

The first thing to be done is to reverse the primary or the secondary winding of the intervalve transformer  $T$ . Notice that only one of the windings has to be reversed, and it does not matter much whether it is the primary or the secondary.

As a rule it is the OP terminal of the primary that goes to the anode of the valve, and the OS terminal of the secondary that goes to the grid. The effect should be tried of joining the IP terminal to the plate, or the IS terminal to the grid.

The effect of changing over one of the windings as suggested is to help stabilise the receiver. The effect produced on the quality of reproduction is as a rule quite negligible.

The next change that should be made to the circuit will be understood by referring to Fig. 2. In this drawing we show the first and second valves only of the receiver, but we have modified the anode circuit of the detector. We have added a further resistance,  $R_3$ , to the anode circuit and a bypass condenser,  $C_2$ .

The value of  $R_3$  may be approximately the same as that of  $R_1$ , and condenser  $C_2$  should be of 2 microfarads.

I have found that a receiver having the


transformer arranged as described, and with this additional anode resistance and bypass condenser, gives very good quality and does not howl or "motor-boat." For this reason it would be a good thing to include the stabilising device  $R_3$ ,  $C_2$  in a receiver.

Dry batteries soon develop a high internal resistance. This does not mean that their terminal voltage is much less than their rated voltage, and, in fact, the harmful effects of the battery's resistance may be

very noticeable long before the battery is discharged. The expense of the stabilising resistance and condenser is saved because a battery can be used for a longer period. It is a common experience that the battery may develop such a resistance that the receiver "motor-boats" long before its voltage has fallen to a point which would warrant it being replaced. The stabiliser helps prevent this.
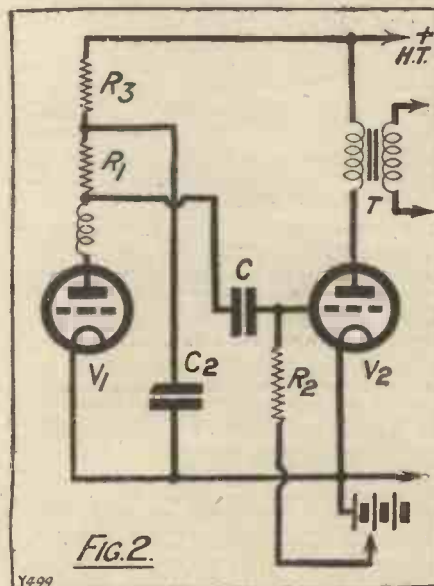
#### The "Stabiliser" in Use.

If the stabiliser is added to an existing receiver the working of the reaction circuit may be altered. A little more capacity will have to be put in to make the circuit oscillate, or if the circuit was one which only oscillated when reaction condenser was all in it will be necessary to add a few more turns



to the reaction coil. The correct number can soon be found by trial. Even when a battery eliminator is used there is an advantage in modifying the receiver as described. Certain high-tension eliminators have a circuit for the detector which includes a high resistance and a bypass condenser, but even so, the extra filtering provided by the resistance and condenser is worth having.

If you are already having trouble with your receiver, and it is exhibiting any of the above-mentioned symptoms, it is very probable that "battery-coupling" is the cause, as it is a frequent source of such faults. But it may happen that an error in design or connections is at the bottom of it—the "stabiliser" is not a "cure-all"!



## FROM SIR OLIVER LODGE.

The Editor, POPULAR WIRELESS.

Dear Sir—Near the end of my last article on "Television" I made reference to the use of cathode rays, or moving electrons, as the only things likely to be sufficiently docile and controllable to be used as the agents for television. No material things are likely to be able to move quick enough; but electrons respond so instantaneously that if devices can be invented for utilising them, the theoretical difficulties connected with the required rapidity of motion would begin to disappear, both from the sender and receiver, especially as photo-electric response is almost infinitely rapid.

When I wrote my article I had entirely forgotten that a suggestion to the same effect was made long ago by Mr. A. A. Campbell Swinton, F.R.S. on several occasions, and I think it will be a convenience to your readers if I give references to his utterances, so that they may look them up. They are as follows:

A letter to "Nature," June 18th, 1908 p. 151, entitled "Distant Electric Vision."

Presidential Address to the Röntgen Society, on November 7th, 1911, reported in "Nature" of December 7th, 1911, p. 191, "Scientific Progress and Prospects."

A Paper read before the Radio Society of Great Britain on March 26th, 1924, on "The Possibilities of Television."

I am, Sir,

Yours faithfully,  
OLIVER LODGE.

## OUR £1,000 TELEVISION CHALLENGE.

The Editor, POPULAR WIRELESS.

Dear Sir,—I would just like to say that I am heartily in accordance with your challenge to Mr. Baird, and I also think that your terms set down in the challenge are extremely lenient, especially if the present television claims are true.

If you will permit me, I would like to suggest that in the event of Mr. Baird declining your challenge, you still keep the offer of £1,000 open to any inventor who can come forward and perform the feat according to your terms.\*

A prize of £1,000 would greatly stimulate invention in this direction and may bring forth many valuable discoveries. I, for one, would perfect my own ideas, which I think will greatly improve the present apparatus. Of course, less than £1,000 could be offered, that is your part of the business. I just suggest offering a prize.

Yours truly,

London, E.C.1.

RONALD L. MANSE.

[\*This suggestion is under consideration.—The Editor.]

The Editor, POPULAR WIRELESS.

Dear Sir,—I have read with interest your article and that of Sir Oliver Lodge on Television. I gather that in your view Mr. Baird has encountered a cul-de-sac, as it were, in his line of television experimenting, and his refusal to accept your challenge and the opportunity indicate that he is conscious of his limitations.

What I am curious to know is—assuming the Press account of the "Berenaria" incident is true—how is it he cannot accept your challenge?

Yours,

New Malden, Surrey.

THOS. J. COE.

The Editor, POPULAR WIRELESS.

Dear Sir,—The attitude adopted by "P.W." with regard to Television rather surprised me. But having read the issue for March 10th, 1928, and the challenge to Mr. Baird, I have been convinced that "P.W." is in earnest, and have therefore changed my opinion.

Every new thing seems to be deprecated—it was always so. From telescopes to the Atlantic cable, from gunpowder to aeroplanes—all have been deprecated. Why do not the "velvet-edged" pessimists learn a lesson, with all the preceding failures of pessimists to make pessimistic predictions before them?

If the science of electricity had had as much publicity two or three hundred years ago, as television and ordinary wireless are having to-day both wireless and television would have been beyond their infancy a hundred years ago. Present systems of television seem to lead to dead ends. So did the first methods employed in wireless, until Marconi showed the way. The difficulties always get solved.

The chief difficulty with regard to television seems to be the light-sensitive device.

Probably the television sets of the future will not employ a large screen, but two small ones, viewed through eyepieces—like the stereoscope. This, to some extent, will solve the problem of bright light at the receiving end. The variation of intensity of the light is another problem. A clue might be found to this in experiments relating to the Interference of Light, and Fresnel's Mirror Experiment.

The challenge made to Mr. Baird interests me very much. The conditions seem to be very reasonable, all things considered, and I am sure all readers of "P.W." and others as well will follow developments with interest.

P. S. ROBSON.

Barras Bridge, Newcastle-upon-Tyne.

The Editor, POPULAR WIRELESS.

Dear Sir,—Your challenge to Mr. Baird, as published in your issue of March 10th, is distinctly interesting, and because progress in this intriguing quest is much to be desired, I hope to hear that Mr. Baird has accepted it.

It might not be necessary to jump to the conclusion that no progress has been made in the Baird system, even if Mr. Baird should not take up the challenge,

## CORRESPONDENCE.

OUR £1,000  
TELEVISION  
CHALLENGE"REGIONAL" TWO ON SHORT WAVES  
—"THAT RADIO SCEPTIC."

Letters from readers discussing interesting and topical wireless events, or recording unusual experiences, are always welcomed; but it must be clearly understood that the publication of such does in no way indicate that we associate ourselves with the views expressed by our correspondents, and we cannot accept any responsibility for information given.—EDITOR.

but if he is really ready to demonstrate in the positive way you have suggested, the demonstration would immensely quicken the practical interest and give direction to the research of many who already believe in the possibility of television, but are in doubt as to the line of experiment by which it may most hopefully be sought.

Yours faithfully,

J. S. MOULD

(Sales Manager),

Igranic Electric Co., Ltd.,

147, Queen Victoria Street, London.

The Editor, POPULAR WIRELESS.

Dear Sir,—The controversy regarding Television has undoubtedly reached the stage when it becomes highly desirable to raise the veil of mystery surrounding its possibilities and limitations. If, as we understand, the £1,000 challenge is designed to prove whether or no television in its present state of development can fulfil the expectations which have been aroused in the public mind, then we congratulate you in performing a public service. In the interest of all concerned, including the inventors, we sincerely hope that the challenge will be accepted, and the present possibilities and limitations of Television made widely known.—Yours faithfully,

D. BURNE-JONES

(Managing Director),

Burne-Jones &amp; Co., Ltd.


288, Borough High Street, S.E.1.

"TELEVISION," "PHOTO-RADIO," AND  
"FACSIMILE."

The Editor, POPULAR WIRELESS.

Dear Sir,—In a paragraph which recently appeared in a number of newspapers dealing with an advertisement—concerning the Province of Buenos Aires Loan—transmitted by wireless from New York to London, the process by which this advertisement was transmitted was described as Television, and the heading put up "Advertisements by Television." This is not correct.

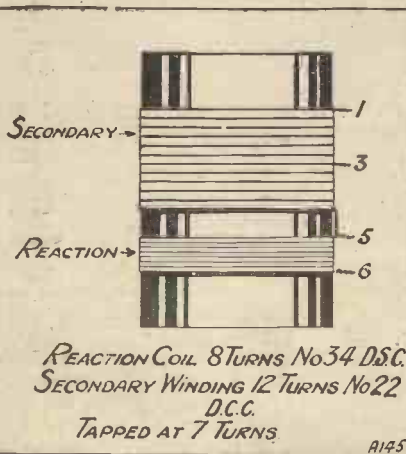Seeing that Television is now frequently mentioned in the newspapers, we think it might not be out of place if we draw your attention to the fact that there is a distinct difference between Television and Photo-radio or Facsimile transmission. Television is essentially the reproduction at a distance of things that



are actually happening at the moment. This has not yet been put into practice commercially.

Photo-radio or Facsimile transmission is, on the other hand, the transmission by electrical means of still pictures and of documents and diagrams of various kinds which are received in the exact form in which they are transmitted. This system has been in commercial use between the Radio Corporation of America's station in New York and the Marconi Company's station in London, since May, 1926.

As references to these different processes are likely to be frequent in the near future, you might find it useful to draw the attention of your sub-editors to this fundamental distinction between these methods.

Yours faithfully,

W. G. RICHARDS,

Chief of Publicity Department,

Marconi's Wireless Telegraph Co., Ltd.,

[NOTE.—The confusion referred to above chiefly concerns the daily Press. We have not noticed errors of this nature in "P.W." or in our technical contemporaries.—Editor.]

## "REGIONAL" TWO ON SHORT WAVES.

The Editor, POPULAR WIRELESS.

Dear Sir,—I recently built the "Regional" Two, as described in "P.W." No. 286. It gave excellent results on the medium and long waves, bringing in 44 stations on the 'phones and several at loud-speaker strength. I decided to wind a coil and try for K D K A on 62.5 metres. This station came through at excellent strength from 11.15 p.m. ('phones). Quality was good and a very slight, quick fading was experienced, but this gave no trouble. I gave a diagram of the coil in case any reader should be interested. A small condenser, such as that used in the "Sydney" Two, must be connected in series with the aerial lead. I am going to build a smaller coil and try for 2 X A F and P C J J in the near future.

Yours sincerely,

Hornchurch, Essex.

K. D. H. SELF.

## THE "VARIATOR."

The Editor, POPULAR WIRELESS.

Dear Sir,—Re the "Variator Two," published in your issue of January 7th, I made up the one-valve part from a collection of odds and ends, and, with two small alterations, I find it the handiest and best one-valve I have ever tried. With little trouble I can get from ten to twelve stations including Madrid, Toulouse and the big German stations. I found that with the loading coil at back of baseboard sufficient reaction could not be obtained. Arguing that if the variometer reached to one side it ought equally to reach to the other, I placed the loading coil to opposite side of variometer and was surprised at the improvement. Then, to save pulling out big coil when altering a broadcast wave-length, I fitted a home-made two-way switch, so that I could cut out large coil completely. This, with two separate aerial terminals, makes the handiest set anyone could wish for. I have tried it on four different aials including an indoor aerial, and with a P.M.I. for detector—it is the goods! Thanking you for such circuits as this,

Yours truly,

Great Yarmouth.

W. SMITH.

## "THAT RADIO SCEPTIC!"

The Editor, POPULAR WIRELESS.

Dear Sir,—After reading Mr. Elston's letter in to-day's "P.W.," I feel I must reply to it. I have been a reader of "P.W." practically from its first issue, and have got a great deal of useful information from it. I constructed a three-valve receiver (Det. and 2 L.F.) from details given in "P.W." which will tune from 60 to 3,000 metres, using home-made honeycomb coils, and will bring in fifteen stations on the loud speaker and a great number on the 'phones, which I think speaks very well for "P.W." circuits. I might add that my aerial is rather badly screened by buildings, and is not very high, being eighteen feet at the lead-in end, and thirty-five feet the other.

Wishing your paper every success.

Yours faithfully,

Ware, Herts.

E. J. WALKER.

The Editor, POPULAR WIRELESS.

Dear Sir,—I should like to say a few candid words to Mr. B. Elston. On the nights of March 2nd and 3rd, I received 49 low-wave European stations (details enclosed for Editor's perusal) on a cone speaker. In the early morning of March 4th I logged 18 U.S.A. stations on headphones (I await confirmation from "World Radio"). On March 5th I picked up W G Y at 11.25 p.m. At 12.15 a.m. I transferred him to loud speaker, which he worked at weak strength. While reception conditions may have been exceptional, I rarely have any trouble in picking up plenty of stations. A passage from Mr. Dowding's excellent article reads: "My practised hand was soon able to rope them in from all over the continent." Here is the crux of the whole matter. Other essentials I find are good layout, components, and detector valve. These results were obtained with a modified 0-v-2 placed on the market by a popular valve maker.

Yours faithfully,

Cornwall.

W. A. E. ROWETT.

## THOSE "ROLLING-IN" STATIONS.

The Editor, POPULAR WIRELESS.


Dear Sir,—I greatly enjoyed reading the letter of "A Radio Sceptic," as I think some of the performances of the amateurs must make even Mr. Marconi gasp. Witness E.C.'s letter from Co. Wicklow, on February 18th last, describing his "Q. and A." Set, a straight two. I will quote his words: "The stations rolled in one after another, altogether between 35 and 40."

Now, I have made quite a few in the last three years, but if this reader can do this on two, I shall give my three away, and buy a gramophone.

Yours sincerely,

"OLD TIMER."



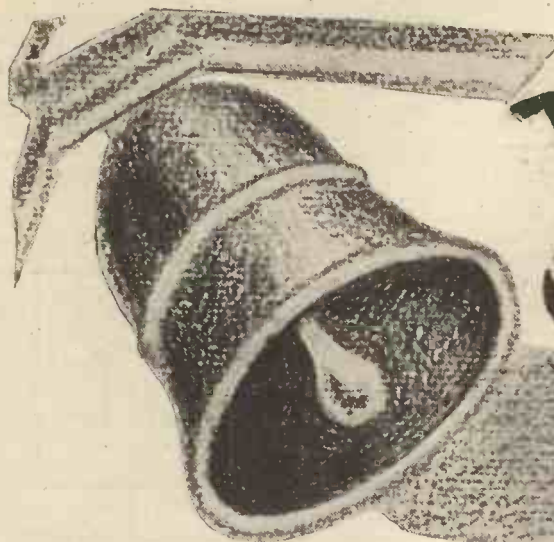

**THE BOOM  
OF BIG BEN**

Through a background  
of utter silence you  
hear it with startling  
clarity to its last  
reverberation

AS THE LAST notes of the Savoy Bands die away Big Ben's giant gong strikes out the midnight hour, and if you have a LISSEN Transformer in your set the notes sound so clear and true that you might be standing upon the silent forecourt of the Abbey. For the LISSEN Transformer fully amplifies every note, every tone, every harmonic, every overtone in a background of silence.

**TEST IT FREE FOR 7 DAYS!**


No matter what other Transformer may be specified, buy LISSEN L.F. Transformers when set building; test them in your chosen circuit for seven days—then if you are not satisfied take them back to the shop where you bought them and the dealer will refund your money.

This is a guarantee which only LISSEN gives—for the LISSEN Transformer may be used in every set and every circuit, no matter what else may be specified, and 10,000 radio dealers sell it under the unconditional guarantee given above.

**LISSEN L.F.  
TRANSFORMER**

LISSEN LIMITED, 8-16, FRIARS LANE,  
RICHMOND, SURREY.

Managing Director: Thomas N. Cole.

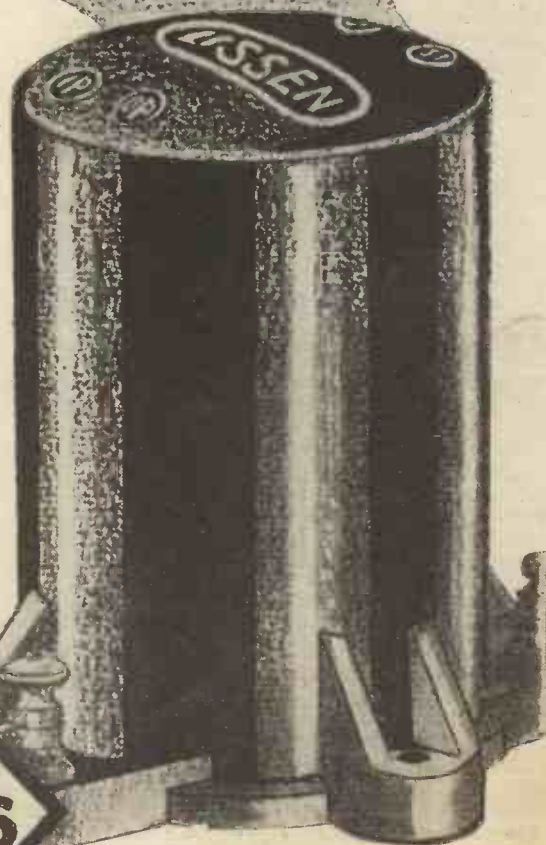

**8/6**

## A DISTURBING FAULT.

Possibly your set might not have developed this trouble,  
but you never know—

By H. J. B. C.

**METAL** panels for use in wireless receiving sets are no doubt proving very popular in many quarters, and deservedly so, for not only are they cheap and of pleasing appearance, but in a set designed specially for employing a metal panel the amount of wiring can be reduced by taking advantage of the metallic connection provided by the panel itself.


### A Recent Experience.

Particular care must be exercised, however, to ensure that the incorporation of this particular arrangement does not lead to a personification of the phrase concerning "a good servant but a bad master." This was brought home to me very forcibly just recently through the location of rather

The set was accordingly taken from its cabinet, the L.T. switch examined, and the fault at once revealed. A metal panel was in use, and the switch had been packed at the back with washers and one side of the switch was joined to the top washer by a short lead, see Fig. 1 (b).

This particular washer had a segment cut away to prevent it touching the other switch contact, but, unfortunately, during the process of mounting, or as the result of a loose nut, it had slipped from the position shown in Fig. 1 (a).

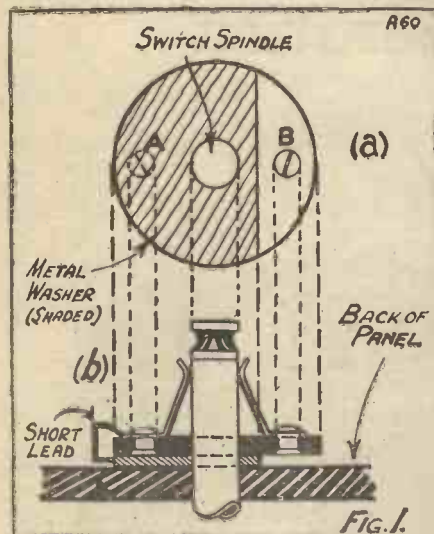Now the screw holding contact B in place projected slightly at the back, with the result that the washer was shorting contacts A and B, and hence the valve filaments were switched on all the time irrespective of the position of the push-pull switch.



an unusual fault in a two-valve receiver I had cause to examine.

The set was situated in one room of the house, with a loud-speaker jack in the drawing-room, and it appears that the procedure always adopted was to switch on the set, then retire to the drawing-room and insert the loud-speaker plug into the jack for the evening's entertainment. When the programme was finished the plug was withdrawn and then one of the family was deputed to go and switch off the set.

Always "On."

It transpired that the accumulators (two being kept in alternate use to prevent any break in the use of the set) only lasted for about a sixth of their expected time, while the H.T. battery ran down in a relatively short period. Further questioning elicited the information that the average nightly use was for four hours—i.e. one sixth of a day.

The similarity between these two proportions caused me to suggest that the set had not been properly switched off, and in consequence the valves were consuming current day and night.

## OVERCOMING RESISTANCE.

**T**HE picnic party was forced to remain on one side of the river owing to the sudden rising of the floods. Galvan Ometer, a huge Pole, volunteered to swim for aid, but they knew that the resistance of the swift current would amperé him.

"We shall have to get ohm by the bridge," said one gentleman with a large joule. But when they reached this, they found that it was sagging in the middle. "I am positive I can volt that gap," said Galvan Ometer. There were cries in the negative, but "Watts that to me!" he cried, determined to risk it and cell his life for his friends. He laid his switch down, and bundled himself up into a coil. After a series of swings, he let go, and describing an arc, landed safely on the other side. Examining the broken part, he exclaimed: "It's only these two ions which have snapped—that's the key to the whole thing. I'll soon fix them so that you can come across on these two parallel beams."

They cheered; and Mr. A. M. Meter said: "Anode 'e could do it, lad, yet I would have been filled with re-Morse if he had perished. Yes, he is a brave fellow."

E. W. H.


## FLEXIBILITY WITH THE "HARTLEY."

**T**HE increase in selectivity of the Hartley over the more common circuits of a detector valve is due to two causes: (a) the reduction of damping caused by the valve itself, and (b) the reduction of damping caused by the aerial.

The Hartley circuit is indicated in Fig. 1, where A.C. is the combined tuning and


reaction coil. The coil is generally tapped at the mid-point B—the part A B is in series with the aerial, and also connected across grid and filament of the valve; the other part of the coil is used for reaction.

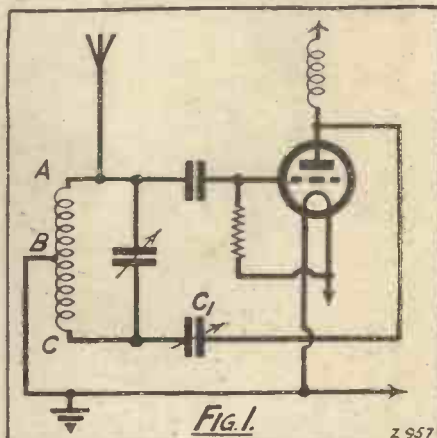If our coil is not centre-tapped, but tapped say at one-quarter way down from one end, in Figs. 2 and 3 we can alter the selectivity




by interchanging the connections at A and C. To change from Fig. 2 to Fig. 3 it is only necessary to reverse the coil in its holder, which can easily be arranged for in any home-made coil.

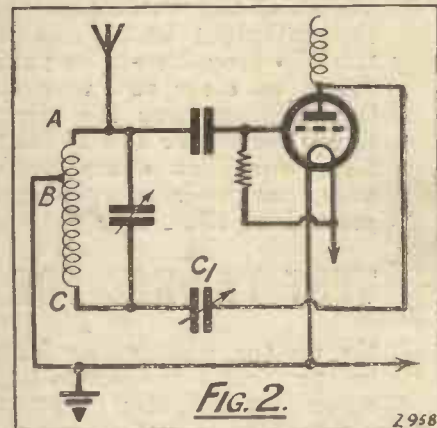If a multi-tapped coil is available the selectivity may be varied in steps. Simply by altering the position of the tap B, and



no dead ends are formed at any tapping. Incidentally, variation of the tapping point gives a rough control over reaction which may be very useful, particularly if a small capacity is used at C1, and the set is required to cover a large range of wavelength.

P. G. B.

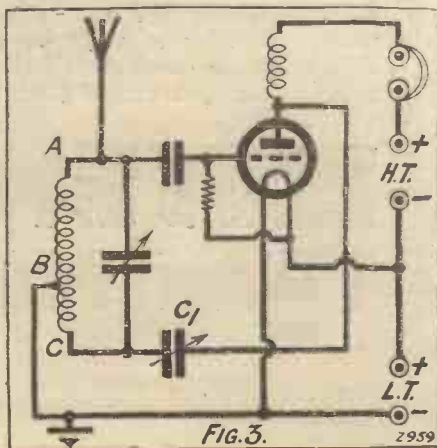



# Get this feast of real music

with a  
**LISSEN  
BATTERY**  
in your set

You need the pure power of the Lissen Battery in your set if you want to hear glorious opera at its best. Not only is there long life in the Lissen Battery but it gives a sustained power through many hundreds of programmes. With its large cells, low internal resistance, with a new combination of chemicals embodied in a new process known only to Lissen the cells of the Lissen Battery generate abundant energy and the current flows always so noiselessly, so smoothly, that every instrument of an orchestra and every note of music, every word of song, is clear and distinct.

If you want your loud speaker utterance to remain natural and true throughout the longest programme, use only the Lissen Battery.

Obtainable at 10,000 radio dealers. Ask for it in a way that shows you mean to have a Lissen and will take no other.


60 volt (reads	<b>7/11</b>
66 v.) - -	
100 volt (reads 108 v.)	<b>12/11</b>
60 volt Super Power	<b>13/6</b>



**LISSEN LIMITED** (Managing Director: THOS. N. COLE), 8-16, FRIARS LANE, RICHMOND, SURREY

# KILOCYCLE TUNING

## for greater selectivity!

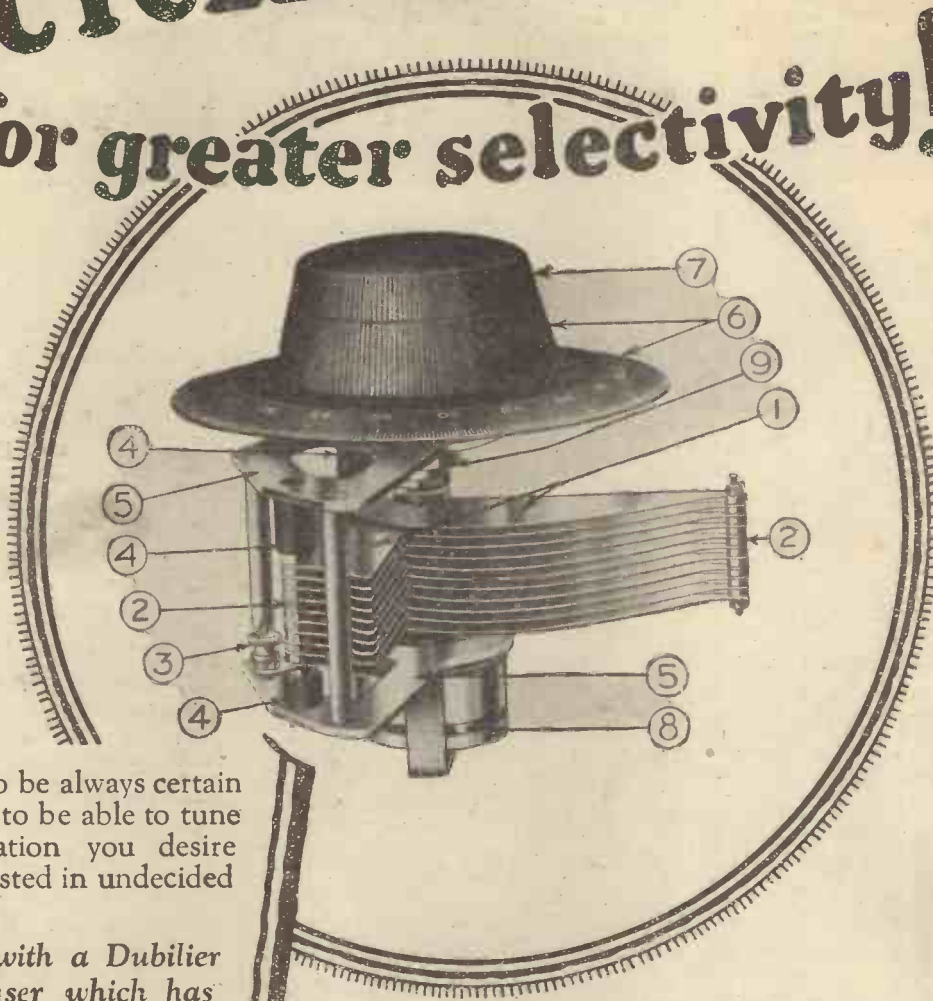

How delightful to be always certain of your station—to be able to tune in whatever station you desire with no time wasted in undecided searching.

Fit your set with a Dubilier K.C. Condenser which has been specially designed to render true kilocycle tuning. With no other type of condenser are the stations so adequately distributed round the dial.

In design and workmanship, the Dubilier K.C. Condenser maintains the recognised standard of Dubilier efficiency and, like all Dubilier products, is unsurpassed in performance.

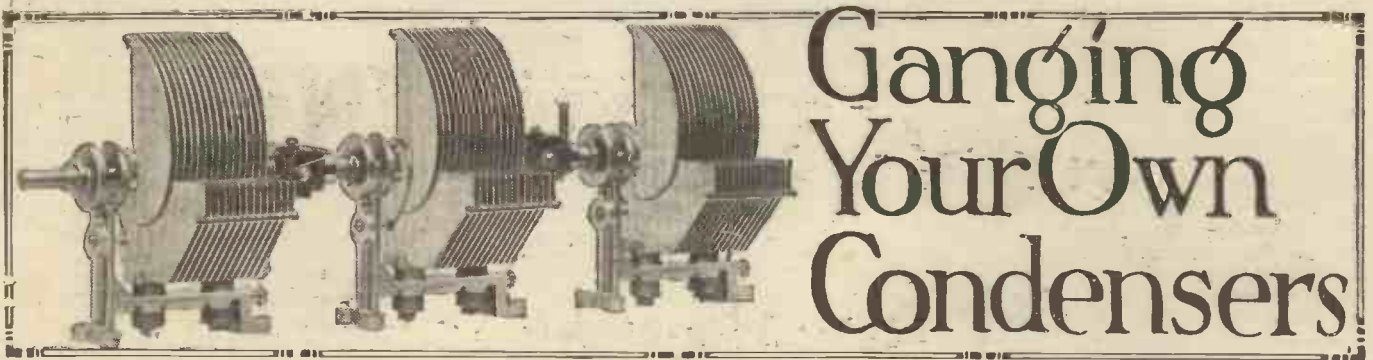
1. VANES of stout brass sheet. 2. SPACERS, between which vanes are firmly clamped, ensuring rigidity and eliminating possible resistance through loose connections. Consistent spacing assured by the extreme accuracy to which spacers are turned. 3. TERMINALS—one giving direct connection with the frame and rotary vanes and the other with the fixed vanes. 4. INSULATORS of high quality moulding material under compression, forming an effective insulation of the stator flutes, and eliminating dielectric losses. 5. END PLATES of the skeleton type, ensuring rigidity and lightness. 6. KNOB AND DIAL of finest finish and engraved in 180 single degrees. Diameter 4 ins. Main knob rotates moving vanes direct. 7. SMALL KNOB. This moves independently of the main knob and works a slow-motion drive. 8. SLOW-MOTION DRIVE. Approximate reduction ratio of 200:1 enabling precise tuning adjustments to be easily secured. 9. BALL RACE, giving a velvet-smooth movement whether the direct or slow-motion drive is used, and with entire absence of backlash in either case. One Hole Fixing— $\frac{1}{2}$  in. clearance. A large nut is provided for mounting on panel. Maximum Capacity 0005. Price (including knob and dial), 12/-.



©139

Advt. of the Dubilier Condenser Co. (1925), Ltd., Ducon Works, Victoria Road, North Acton, W.3.





# Ganging Your Own Condensers

THE tuning of a receiver which has one or more tuned H.F. stages is greatly simplified by the use of gang-controlled condensers. The tuning coils must, of course, be matched, or nearly so, and it is then vastly simpler to rotate the variable condensers together, with one knob, than to adjust separate dials to the correct readings.

The condensers now obtainable in ganged form are coupled together by means of their spindles. This method of coupling is not easy with existing single condensers, and it is a job which is hardly possible in most amateur workshops. There is one type

Details of a simple method of making your own "gang" condensers.


By A. V. D. Hort, B.A.

easy to construct, but it does not permit of much adjustment of one of the condensers independently of the other. A slight difference in the settings of the vanes can be obtained by slacking the nuts at one end of the coupling, turning the ebonite strip

of the coupling, sliding the bolt along the slot in the required direction and tightening the terminal head again. If you need a wider range of adjustment, make the slotted ebonite strip and the strip opposite to it longer. The slot should be wide enough to allow free play for the 4 B.A. bolt, as the latter has to move through an arc of a circle in making the adjustment.
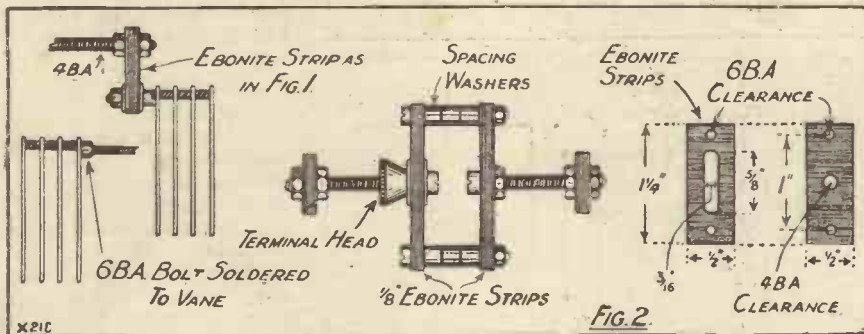
## The Friction Adjustments.

The friction adjustment of the condensers is important. The front one should be normal. Slack the spindle of the rear one until the vanes will fall back of themselves when they are lifted. There will then be no risk of straining the coupling or the vanes. The front condenser is mounted on the panel in the usual way. The rear one is supported by a metal bracket standing on an ebonite base, or on a vertical strip of ebonite fixed to the baseboard with brackets or against a block of wood as in the photograph. Be specially careful to align the condensers as exactly as possible. If they are out of line, they will not turn smoothly.



of condenser, however, which lends itself to ganging by another method. An example of a two-gang condenser constructed in this way is shown in one of the diagrams. The components to use are S.L.F. condensers with long moving vanes held together at their outer ends with some form of clip or bolt.

## Easy to Construct.


The coupling shown in Fig. 1 is the simplest. Here the moving vanes are held at their ends by a bolt. To make the coupling, take out this bolt and put in a slightly longer one. Clamp on this an ebonite strip

through a small angle and tightening up.
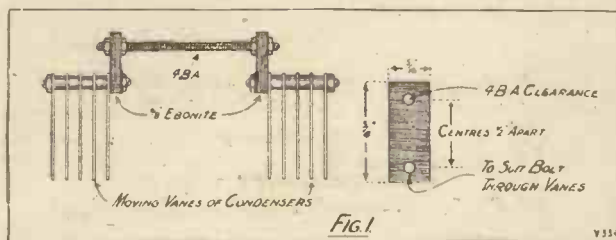
## More Satisfactory Type.

This, of course, throws the 4 B.A. rod out of line and tends to twist the moving vanes, but provided that the difference between the two condensers is not too great, no harm will be done.


In Fig. 2 are given details of a much more satisfactory type of coupling. It is a bit more troublesome to make, but it gives a fine adjustment without throwing the coupling out of line. A pair of condensers fitted with this coupling are, shown in the photograph, which illustrates also the method of mounting them. In these condensers a bolt through the ends of the vanes would cause a short-circuit with the fixed vanes, since the moving vanes do not overhang the fixed ones. A fibre strip is, therefore, fitted to the ends of the moving vanes. The coupling is fixed to the con-



of the dimensions given, and fix a 4 B.A. rod of the required length at the other end of the strip. The second condenser is fastened to the other end of the rod in a similar manner. This form of coupling is

condensers by means of cheeseheaded 6 B.A. bolts soldered to the outside moving vanes.

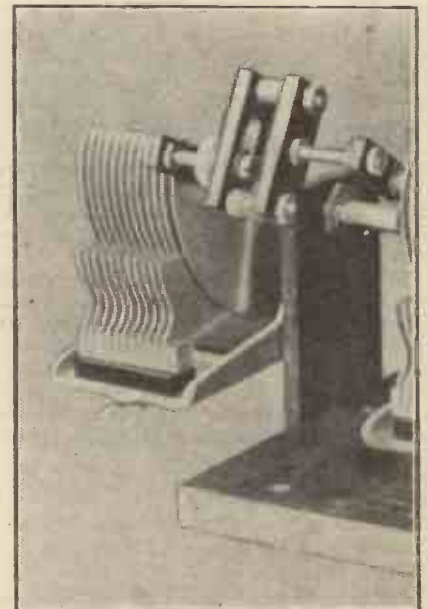Independent adjustment of one condenser relative to the other is effected by slackening the terminal head on one side



The two condensers connected together by the method explained above.

You will not have the vernier balancing adjustments provided on commercial models, but it is very easy to employ what is known as a "trimming condenser." This is a small "vernier" condenser of say .0001 mfd. connected across one of the sections of your home-made gang for balancing.



THE frame aerial is perhaps one of the most neglected of wireless devices. Presumably everybody knows what a frame aerial is, but most amateurs fight shy of using one. It is quite a common belief that a frame aerial is very inefficient, and apart from self-contained portable sets one rarely sees a frame aerial in use unless it is with a super-heterodyne receiver.

This general belief that frame aerials are too inefficient to be worth while probably arises from using too small a frame and using it incorrectly. Frame aerials for successful use with a modest receiver require careful consideration; properly used they are then far from inefficient and possess important advantages over the outside aerial.

Ignoring for the moment the degree of efficiency, the case for the frame aerial is quite a strong one. It is compact and easily transportable, it is cheaply and easily constructed, it is free from the dangers of lightning and minimises atmospheric and interference. Above all it increases selectivity, and has the well-known property of directional reception. A long list of merits you may say, but useless without some degree of efficiency as an aerial. This I hope to show is far higher than is generally believed. A modest receiver, such as a detector and one or two L.F. stages is ample for DX work.


#### Constructional Details.

The frame aerial should have a side of at least 3 ft.; but more than 3 ft. 6 in. is unnecessary. The construction of the former upon which the frame is wound should be rigid, using the least material possible. The frame winding must be well insulated, space wound, using for preference stranded wire, of which there are several kinds specially manufactured for this purpose. For a wave-length range of approximately 200 to 550 metres using a .0003 mfd. tuning condenser, 14 turns are required. Three of these comprise the reaction winding as described below.

The receiver attached to the frame aerial requires to be simple, straightforward and efficient. A regenerative detector must be used for fullest sensitivity and upon the manner of applying and controlling reaction hinges the whole success of frame aerial reception. Maximum signal strength depends upon delicate tuning at the stage prior to oscillation.
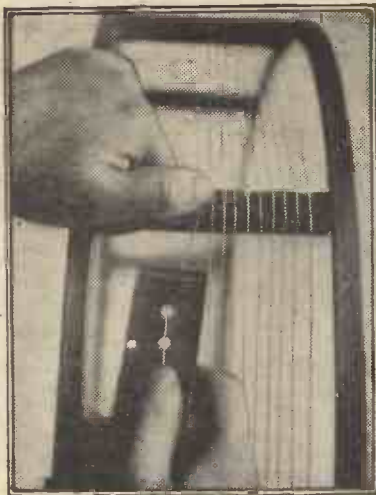
#### Smooth Reaction Control.

Undoubtedly the best method is to react straight into the frame, as shown in the theoretical diagram on this page. The usual form of capacity control is used and, with proper adjustments of H.T. and filament voltages, a very smooth reaction control is possible. Given this super-smooth control, plus a slow-motion tuning condenser, it is surprising how far one can reach out with a receiver like this. Careful tuning is necessary for the best results, but modern condensers simplify the operation greatly. Of course, the receiver will not give loud-speaker results on any station other than



## FRAME AERIAL RECEPTION

Some practical notes on the subject.

By  
J. ENGLISH.

the local, but during both summer and winter months, I have toured Europe on the phones on many evenings, stations a thousand miles away coming in with extraordinary clarity. Atmospherics have always been considerably less than with outside aerial and fading not so marked.

When searching for distant signals the frame is rotated until one position gives the strongest heterodyne note, the receiver

being in a state of gentle oscillation. Reaction is then carefully slackened off until the receiver is in the pre-oscillation state, the tuning condenser being moved at the same time to keep in tune. A final adjustment of this condenser then produces maximum signal strength.


The peculiar effect is noticed of a sudden jump in signal strength when the tuning condenser is exactly in tune, with the set just off oscillation. Although signals may be coming in well and the set appear to be in tune, there is just one critical setting where maximum signals are heard. Without the modern slow-motion devices it is difficult to obtain this fine tuning. Hand capacity effects, however, although they can be troublesome, can be largely avoided by careful design and construction.

#### Short-Wave Possibilities.

It is well known that the efficiency of the frame aerial increases as the wave-length decreases. This opens up possibilities for short-wave reception where the efficiency of the frame may approach that of the ordinary small aerial. As a basis of experiment the frame should have 3 to 4 turns, with a variable tapping for the filament lead. Alternatively a modified Hartley circuit can be used.

One of the essentials for satisfactory results on all wave-lengths is the elimination of receiver noises. When there is a perfectly quiet "background" weak signals are naturally more easily readable.

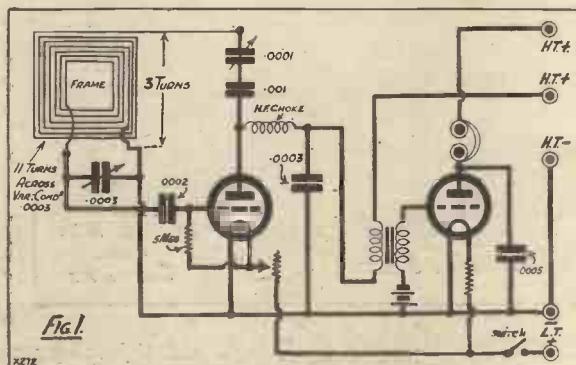The desired state of affairs can be secured by using reasonably fresh H.T. and grid-bias batteries, a reliable grid leak and condenser, and a transformer free from leakage.



A simple but efficient frame aerial circuit.

## RADIO JOTTINGS.

A record for amateur telephony in daylight was recently established by G 5 H S, of London, and U 6 Z A T, of Los Angeles, California.

The musical instruments used by one of the bands whose dance music is broadcast regularly by W J Z, New York, are valued at over £2,000.

Radio on railway trains is becoming increasingly popular on the Continent, and successful experiments have recently been carried out on the Warsaw railway.

An enterprising New York newspaper, "The Evening Telegram," has announced that its radio department is investigating the possibilities of transmission on a wave-length of only three-quarters of a metre.

Owing to the interruptions caused by storm and floods to the ordinary tele-

graphic and telephonic communication, the Government of Ceylon have been experimenting with a portable wireless receiving and transmitting set capable of communicating over a range of 300 miles.

It has been officially computed that the world contains no less than 18,000,000 radio receiving sets.


The first direct wireless messages between England and Australia were transmitted from Carnarvon on September 22nd, 1918, and were picked up in Sydney, New South Wales.

Four thousand metres is the longest wave-length used in Europe for broadcasting, this being one of the wave-lengths of the Berlin Koenigswusterhausen station.

The Belfast Station was opened on November 4th, 1923.

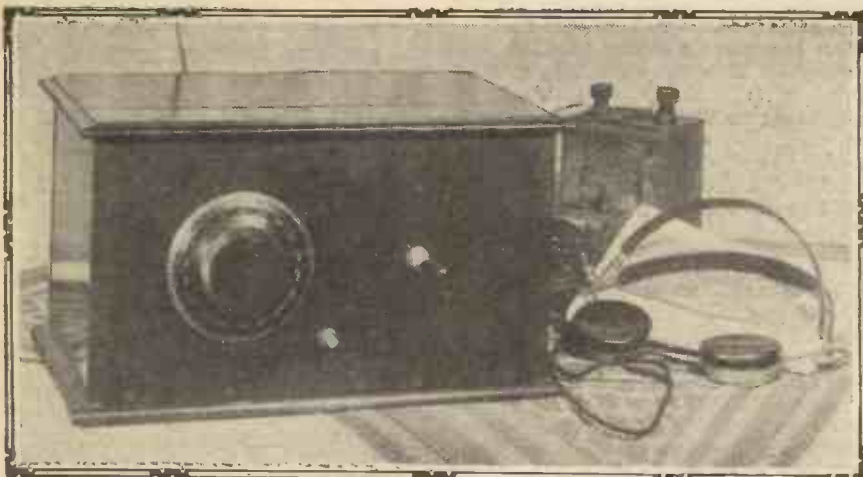The crystal as a wireless detector was discovered by an American, General Dunwoody, in 1906.





# The HARTLEY ONE- VALVER

Here is a fascinatingly simple and efficient little set—just the one to give you real DX results. It is a special design of the "P.W." Research Department, and has been given exhaustive tests.

Described by  
G. P. KENDALL, B.Sc.

IT always seems to me rather a curious thing that one of the most efficient and fascinating forms of the single-valve reaction circuit, namely the Hartley, should also be one of the most neglected. Probably this is due to some extent to the fact that one form or another of the popular

of cost, and it must not be forgotten that the Reinartz requires two variable condensers, although one of these may be of the relatively cheap type of .0001 mfd. developed for reaction purposes. Again it must not be assumed that the Reinartz necessarily gives the loudest possible signals that can be obtained with a detector valve.

## Tricky Circuits.

As a matter of fact, there are a number of special circuits which, when working at their best, will beat the average Reinartz for signal strength, although, of course, it does not follow that they have quite all the other advantages of the Reinartz. Many of these circuits are admittedly a little difficult to operate, troublesome to adjust so that reaction is smooth, and so

on. Many of them possess some slight drawback or other which is not present in the Reinartz, but nevertheless they form a very fascinating field for those who have acquired a little skill in handling wireless receivers, and can appreciate the very good results obtainable by the expenditure of just a little time in practising their operation.

The Hartley forms a very good example of a circuit of this kind, giving the possibility, as it does, of particularly good

(Continued on next page.)


## COMPONENTS REQUIRED.

- 1 Panel, 12 in.  $\times$  7 in.  $\times$   $\frac{1}{8}$  in. or  $\frac{3}{16}$  in. (any good branded material).
  - 1 Cabinet to fit, with baseboard 9 in. deep (Artercraft, Bond, Camco, Makerimport, Pickett, Raymond, etc.).
  - 1 .0005 mfd. variable condenser with slow-motion or vernier dial (Ripault in original. Any good make).
  - 1 On-and-off switch (Benjamin, Bowyer-Lowe, Igranic, Lissen, Lotus, etc.).
  - 1 Panel-mounting neudrodyne condenser (Peto-Scott in original. Any standard make).
  - 2 Board-mounting coil sockets (L. & P., Lotus, Magnum, Peto-Scott, etc.).
  - 1 .0003 mfd. fixed condenser (Clarke, Dubilier, Goltone, Lissen, Mullard, T.C.C., etc.).
  - 1 2-megohm grid leak with holder or other mounting (Dubilier, Igranic, Lissen, Mullard, etc.).
  - 1 Sprung valve socket (Benjamin, Burne-Jones, Burne-Jones, B.T.H., Cosmos, Igranic, Lotus, Marconiphone, Precision, Pye, W.B., etc.).
  - 1 Baseboard filament rheostat (Igranic, Lissen, or similar type).
  - 1 H.F. choke (Bowyer-Lowe, Burne-Jones, Cosmos, Lissen, Igranic, R.I. & Varley, etc.).
  - 1 Terminal strip, 8 in.  $\times$   $1\frac{1}{2}$  in.  $\times$   $\frac{1}{8}$  in.
  - 8 Terminals (plain type, or engraved, such as Belling & Lee, Eelex, Igranic, etc.).
- Wire, screws, short piece of flex, etc.

Reinartz has now become almost standard practice for the detector circuit, and so experimenters are ceasing to pay much attention to other arrangements.
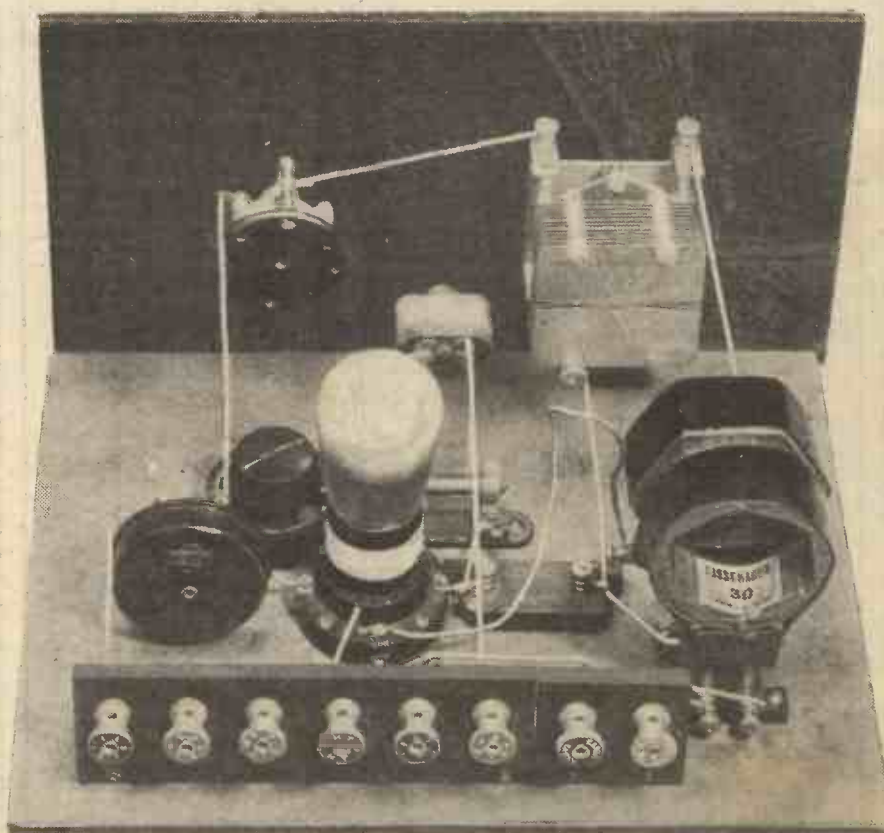
## Why the Reinartz?

No doubt the Reinartz circuit has a number of very solid advantages, such as the possibility of obtaining beautifully smooth reaction control, reasonably good selectivity, ease of control, and so on, but it does not follow necessarily that it is the best possible arrangement for a detector valve. For example, there is the question



You will gain a good idea of the simplicity of the receiver from this back-of-panel photograph. Note the two plug-in coils which are used and the small reaction control condenser.







# YOU GET MORE FROM MARCONIPHONE L.T. ACCUMULATORS



Why are Marconiphone Accumulators so extraordinarily long-lived? What is the secret behind their marked superiority? It lies in the plates—the heart of every accumulator. For only in Marconiphone can you obtain plates built from the new formulæ especially to resist acid attack. Remember, too, that all parts of Marconiphone Accumulators are protected against sulphuric acid fumes; the separators are made from the finest ebonite; the substantial celluloid container allows easy inspection of acid level, and a host of other features ensure unfailing service under all conditions.

Write now for full particulars. Marconiphone Accumulators are sold by most Wireless Dealers.

										Without crates.			Complete with crates.		
										£	s.	d.	£	s.	d.
2 volt, 20 amp. hours	..	..	..	..	..	..	..	..	..	11	3	..	..	15	3
2 volt, 30 amp. hours	..	..	..	..	..	..	..	..	..	13	6	..	..	18	6
2 volt, 40 amp. hours	..	..	..	..	..	..	..	..	..	16	0	..	..	1	1 0
4 volt, 20 amp. hours	..	..	..	..	..	..	..	..	..	1	2	6	..	1	7 0
4 volt, 30 amp. hours	..	..	..	..	..	..	..	..	..	1	7	0	..	1	13 0
4 volt, 40 amp. hours	..	..	..	..	..	..	..	..	..	1	12	0	..	1	18 0
6 volt, 20 amp. hours	..	..	..	..	..	..	..	..	..	1	13	9	..	1	19 3
6 volt, 30 amp. hours	..	..	..	..	..	..	..	..	..	2	0	6	..	2	7 0
6 volt, 40 amp. hours	..	..	..	..	..	..	..	..	..	2	8	0	..	2	14 6

THE MARCONIPHONE COMPANY LTD. (Dept. P.), 210-212, Tottenham Court Road, LONDON, W.1.

Pleasing  
Player's

TOM NEWMAN




Player's  
Please


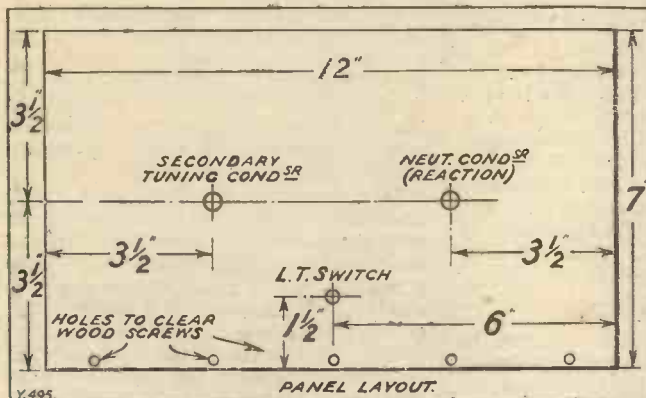
## THE "HARTLEY" ONE-VALVER.

(Continued from page 188.)

Coupled to this aerial coil is a secondary which is tuned by a variable condenser connected across its two ends in the ordinary manner, and this will be a No. 60 for the ordinary broadcast band, or a No. 250 for the 5 X X range. This coil, it will be noted, is of the centre-tapped variety, and in the circuit diagram you will see that this



centre tap is connected to the filament and to earth.

One side of the tuned circuit goes to the grid of the detector valve via the grid condenser, and the other end is taken to one side of the little reaction condenser, and through this to the anode of the valve. The anode circuit, of course, contains the usual H.F. choke and the telephones. At this point you will see what is meant by saying that neither side of the tuning condenser is at earth potential in this circuit.

### Efficient on Short Waves.

It is interesting to note in passing that one of the advantages of this circuit is that it is also quite useful on the short waves, and one can pick up the short-wave transmissions such as K D K A, 2 X A F, A F C, and so on, with the use of suitable short-wave coils, sets of which can now be obtained from a number of manufacturers, among others Messrs. Clarke and Igranic.

When using these coils, of course, the lead from the filament which normally goes to the centre tap of the coil (a terminal on the broadcast and long-wave sizes) will need to be furnished with a tapping clip, so that you can make connection on one of the turns of the bare wire coils used for the shorter waves.

### Easy to Build.

The construction of this little set is really so simple that little can be said about it, since if you use single-hole fixing components there are only three holes to be drilled in the panel, and you will merely have to screw the panel to the baseboard, mount the coil sockets, grid condenser, leak, valve socket, rheostat and H.F. choke upon the baseboard with the terminal strip, and you can then carry out the wiring-up operation.


Wiring again is extremely simple, as you will see from the photographs and wiring diagram, and there is nothing critical about it. If you follow the lay-out fairly closely,

you will find that the wiring automatically becomes very simple and there is little need to take any great pains in spacing out.

You will see in the photographs that the original wiring was done on the straight point-to-point system, running wires by practically the shortest paths possible from one terminal or soldering tag to the next. This makes quite an efficient arrangement but, of course, you can if you like try the right angle method, which no doubt looks very much neater although there may be some slight theoretical sacrifice of efficiency (probably not measurable with so simple a set). The wiring can naturally be carried out with practically any material the constructor chooses, such as bare wire covered with Systoflex, bare wire without covering, covered wire such as Glazite, a special material such as Junit, and so on.

One final point before leaving the details of construction. The particular variable condenser used in this set was the Ripault, which has two terminals connected to the moving plates. You will see that three wires go to the variable

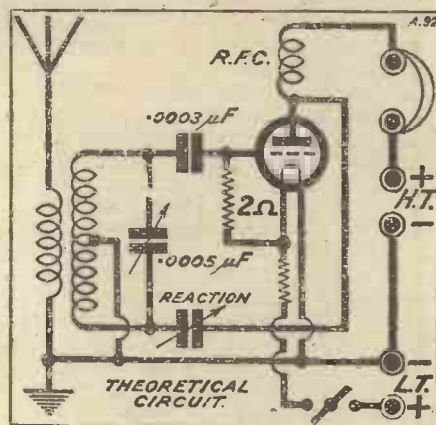
condenser, although two of these are both connected to the moving plates by the two terminals just referred to, and if you choose some other make of condenser these two wires will naturally be placed under the same terminal, namely that for the moving plates.



On the original set we did not actually fit a slow-motion dial, because the set would naturally be handled for its tests by skilled operators, but I would strongly advise that a very good vernier dial, with a knob placed at some little distance from the main body of the condenser, should be chosen by any constructor who desires to follow out this design.

Turning to operating details, the first important point to be considered is that of the kind of valve to use. Very good results have been obtained on test with a valve of the H.F. type, or even the R.C.C. type, namely, high impedance, high amplification factor, and good results will be obtained if either 2- or 6-volt types are used. Naturally, you will expect to obtain slightly better results with a 6-volt valve in most cases but, of course, the economy of the 2-volter is a very attractive feature.

(Continued on page 207.)

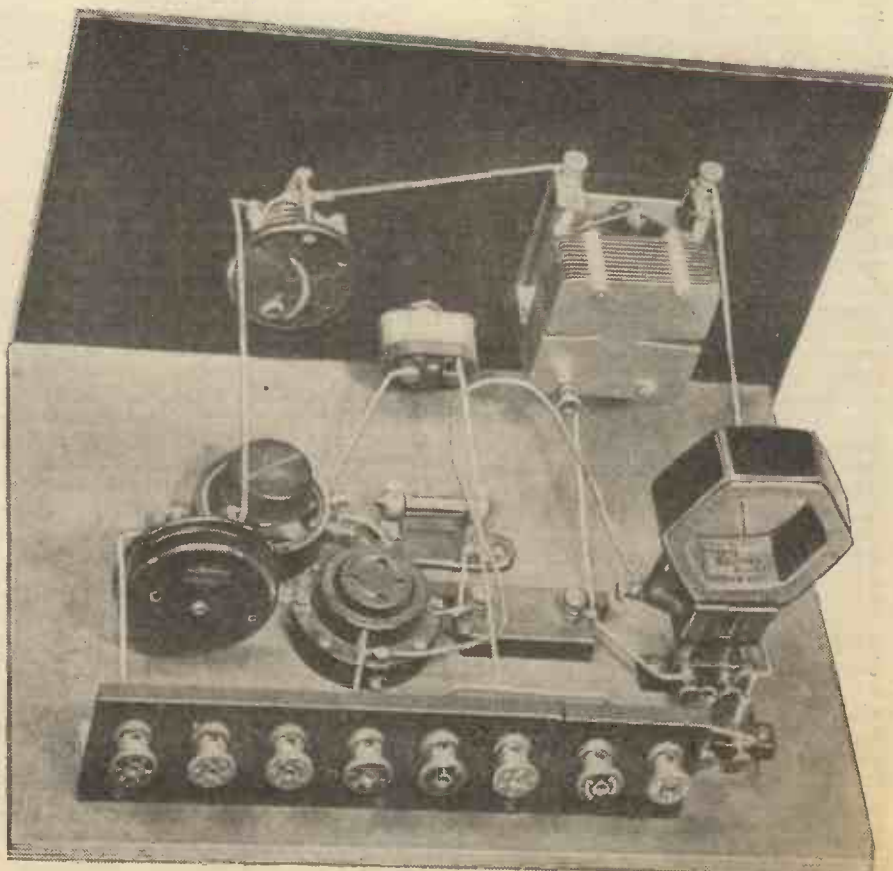


The terminals from left to right are: 'Phones minus, 'Phones plus, H.T. plus, H.T. minus, L.T. minus, L.T. plus, Earth and Aerial.


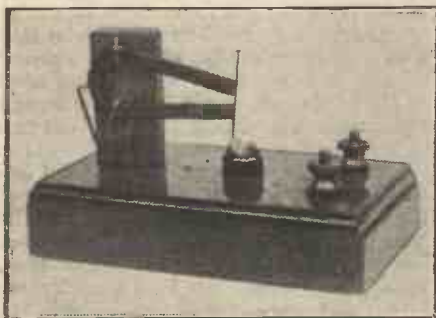
### A Magnet Detector.

A CRYSTAL detector constructed on the principle of the article depicted in the photo, can prove to be a very useful device for the crystal enthusiast. The illustration is self-explanatory, and therefore little need be said about the actual construction of the detector. It will be seen, however, that the magnet holding the pin which makes contact with the crystal is attached by means of two metal staples to an upright post which is screwed down to a baseboard. The latter screw should not be too tightly driven home, nor should the staples holding the magnet be too firmly driven into the wood. The magnet will then be free to be pushed slightly backwards and forwards through the staples, and also slightly from side to side by rotating the wooden post on its supporting screw.



Quite a simple idea, but it works well.

The great advantage of a detector of this nature, which, of course, can be constructed in many different patterns, is that the pin contact to the crystal is held securely and firmly, and also that it is entirely vibration-proof. By moving the magnet backwards or forwards, or from side to side slightly, almost the whole area of the crystal will be capable of being explored for sensitive spots.

Connections are taken from the underside of the crystal cup to a suitable terminal, and also from the magnet itself to another terminal.

Care should be taken to solder the wire connection to the magnet with the absolute minimum of heat. For this purpose, Wood's metal is best used. A little of the red enamel should be scraped off the end of the magnet, and the end of the wire, previously cleaned and tinned with ordinary solder, should be secured as rapidly as possible to the bared end of the magnet with the aid of a few blobs of Wood's metal. As there will be no strain on this joint, its actual strength is a matter of little consequence.

Finally, when the detector is not in use, the pin should always be allowed to adhere to the poles of the magnet in order to act as a "keeper," and thus to conserve the strength of the magnet.

### Aerial and Earth Leads.

Here is a good idea for aerial and earth leads. Equip the end of each lead with a spade terminal in the usual manner. To the spade terminal of each lead secure a Clix plug also, by simply placing the spade between the insulated bush and the nut of the plug. The idea is simple enough, but its advantages lie in its many useful adaptations.

For instance, when connecting the lines to a set equipped with terminals, the spade

## HINTS FOR THE HANDY MAN.

A selection of short and practical articles from various contributors.

ends are used. Connecting to a set equipped with sockets, the plugs are used. Finally, to earth the aerial, one socket is just plugged into the other. The plugs are easily attached to or taken off the spade terminals with the fingers.

### Dusty Panels.

It does not seem to be realised by some wireless enthusiasts that a dusty panel is by no means desirable. In sets of the old type, where panels are arranged in a sloping position with external valve holders, the dust is in the habit of getting round the legs, etc., thus causing faulty insulation. In any case, it cannot be over emphasised that dust is an undesirable commodity. Panels should therefore be periodically dusted with a camel-hair brush and kept scrupulously clean.

### Leatherette Radio Cabinets.

American cloth or leatherette may be put to a number of uses by the wireless constructor, especially by those who are accustomed to making their own cabinets. Where the constructor is not particularly good at cabinet work, or has no time to give such work a first-class finish, a rough cabinet may be knocked up from even unplanned deal and an extremely pleasing finish applied by giving it a complete covering of American cloth or leatherette of any desired tint, black usually presenting the neatest appearance. Owing to the cheapness of this material a considerable amount of expenditure may be saved in the direction of cabinets.

### Wood Filling.

Where cabinets are put together by amateur constructors with screws, a good wood filling is essential. All screw heads should be countersunk below the surface of the wood. When the work has been sandpapered the dust obtained in this operation should be carefully collected. If this is mixed with seccotine, or pure gum arabic and water, an excellent natural wood filling may be obtained.

This is carefully worked into all cracks and crevices, and screw head or nail punch recesses, and left till hard and dry. A final sandpaper will render all defects absolutely invisible, the filling used being the actual colour of the wood from which the cabinet is constructed.

### Sheet Fibre.

There are numerous uses to which sheet fibre can be put. This material may be obtained in two colours, black and brick red, and in varying thicknesses. The thin fibre lends itself admirably to such purposes as shaped loud-speaker flares, where the sides are of flat-shaped pieces of wood, the fibre being used for the curved sections.

Washers of any size or description can be quickly made from this material, and spacers also. Cone loud speakers of extremely rigid and good tone-producing types are easy to construct. Templates which are often extremely useful things to

have, such as valve or panel-drilling templates of any kind, if made from fibre, will stand a considerable amount of wear and tear, in addition to acting as extremely true guides for work of this nature.

Old panels may be utilised over again by placing over them a sheet of fibre, the panel terminals, etc., acting as ample security. Where wood panels are used an ebonite appearance may be given in a similar manner.

### Retaining Accurate Coil Adjustment.

In some forms of coil-holders, and particularly after such articles have been subjected to a good deal of wear, it often becomes rather a tricky task to retain a fine degree of close coupling between the two coils, the larger and weightier of the coils tending, under these conditions, to fall back slightly.

Naturally, the true remedy for a trouble like this is to disassemble the coil holder, and to take up any wear by means of washers of one form or another.

In times of emergency, however, the trouble may be cured by adopting the very simple mode of procedure illustrated in the accompanying photograph. Procure a not too tightly fitting rubber band, and slip this over the coil sockets in the manner shown. Of course, if the tension of the rubber band is too great, both coils will be pulled together. On the other hand, provided a rubber band which is not too tight has been employed, it will not influence the limited movements of the coils, but will merely serve to check any slight falling-back movement of the heavier coil. In most cases an accurate and stable coupling will thus readily be obtained.

### Interesting Facts.

Continuous fiddling with the adjustment of a crystal receiver is not only unnecessary, but is often responsible for corresponding clicks in the receivers of your neighbours.

Reaction is a good servant but a bad master.

If you are nervous of lightning use an outdoor earth arrester, which is very cheap and can easily be fitted.



The rubber band is shown here slipped over a coil holder.





# To PORTABLE SET USERS!

## A NEW AND BETTER VALVE

In neutralised and stabilised High Frequency Amplifiers the new H.L. 210 OSRAM VALVE gives a more sensitive response to weak signals from distant stations. The ideal valve for Portable Sets where only a small frame aerial is used. Gives maximum volume with minimum number of valves.

Its characteristics allow it to be used as a grid leak detector for sensitivity, or as an anode bend detector for highest quality reproduction.

Also used in the first stage of low frequency amplification, and ideal for choke coupled amplifiers. Write for full particulars.

**Made in England**



### Characteristics

Filament volts 20  
max.  
Filament current 0.1  
amps.  
Amplification Fac-  
tor 15.  
Impedance 25,000  
ohms.

**PRICE  
10/6**

# Osram Valves





EFFICIENT DETECTORS—  
THE "BROWN BUDGET"—  
A "CELESTION" LOUD  
SPEAKER—AN EX-  
CELLENT L.F.  
TRANSFORMER.

\* \*

Traders and manufacturers are invited to submit wireless sets and components to the "P.W." Technical Department for test. All tests are carried out with strict impartiality in the "P.W." testing-room, under the supervision of the Technical Editor, and the general reader is asked to note that this weekly article is also intended to provide a reliable and unbiased guide as to what to buy and what to avoid.—EDITOR.

#### EFFICIENT DETECTORS.

**M**ESSRS. N. M. C. DETECTORS, of Princes Parade, Finchley, London, N.3, recently sent us a range of their new crystal detectors. There are three varieties which sell at 6d., 1s., and 1s. 6d. They can be obtained, post free, at these prices. The detectors are of the semi-permanent variety and can be used with good effects in such circuits as the Hale, and other reflexes. Iron Pyrites is the crystal employed, and the specimens sent us are the best that we

have come across. The 1s. 6d. detector, which is known as the Azure label, comprises a practically perfect piece of the crystal.

#### THE "BROWN BUDGET."

This is the name of Messrs. S. G. Brown's monthly journal. It is mainly concerned with the activities of this go-ahead and interesting firm, but it makes absorbing reading, and we would like to take this opportunity of extending our appreciation and thanks for the copies regularly sent us.

#### A "CELESTION" LOUD SPEAKER.

No doubt a very large number of our readers would consider £7 5s. too much to pay for a loud speaker; this is the price of the "Celestion" model C.12 in oak. In mahogany it is £7 10s. It is admittedly a lot of money, but we think that if efficiency and appearance are taken into consideration it is very well worth it. It is always worth while buying the best of anything that one can afford, and nowadays, in radio, like in most other things, price is a pretty fair guide to quality. We know of one or two exceptions, but the rule is a fairly safe one.

To obtain a better speaker than this model C.12 Celestion one would have to pay very much more money. As a matter of fact a move up into the moving-coil class would, in our opinion, be necessary. The C.12 is a cabinet cone and its construction and finish are so good that one stamps it "de luxe" at a glance. A point in its favour is that it is not particularly large, being only 6 in. in depth, and 14 in. x 14 in.

It has a splendid projection, every vibration coming cleanly away from the cone, and we know of but one or two other cones which have less coloration. Speech is decidedly of moving-coil quality. There is no appreciable resonance and both bass and high notes are faithfully dealt with. The speaker is rather more sensitive than the majority, but it is capable of handling heavy inputs. We found it perfectly satisfactory on each of the several sets with which it was tested, ranging from two valves to a multi-valver of the super kind.

(Continued on page 196.)

## Recognised leaders in the design of

FOR THE 1928 SOLODYNE



B.B.C. Coils:

Aerial Circuit	1 Ref. LAA 5	} £2-5-0 Per Set including bases
H.F. Transformer	2 Ref. LAT 5	
5-pin Bases	3 Ref. LB	

Daventry Coils: (No. 285,723)

Aerial Circuit	1 Ref. LAA 20	} £2-5-0 Per Set without bases
H.F. Transformer	2 Ref. LAT 20	
Additional Bases	Ref. LB. . . . .	



1 Lewcos Wavetrap . . . . . 13/6

## Solodyne Coils

As manufacturers of the special coils used in the original 1926 Solodyne, Lewcos established a leadership which is still unchallenged. New developments necessitate many alterations in the design of coils for the 1928 Solodyne. But again LEWCOS will give you that extra selectivity and efficiency that constructors have learnt to expect from all Lewcos Coils.

The demand for these new coils and wave-trap will be heavy; place your order now and ensure early delivery. Obtainable through all good radio dealers.

The LONDON ELECTRIC WIRE CO. & SMITHS Ltd.,  
Playhouse Yard, Golden Lane, London, E.C.1.

# LEWCOS

(Regd. Trade Mark)

## COILS and WAVETRAP for the 1928 SOLODYNE



## MAKE YOUR OWN CONE SPEAKER

The New Wonder "Nightingale"

### CONE UNIT

Exactly as fitted to our Cabinet Cone Speaker. Guaranteed to give results equal to the most expensive Loud Speakers yet made.

Full constructional details with each Unit.

### GRAMOPHONE ATTACHMENT

Reduced from 32/6 to 15/- solely as an advertisement for the famous Bullphone Nightingale Loud Speakers. Cobalt Magnet guaranteed for all time.

With 4-inch Diaphragm.

Instantly converts your own Gramophone into a full power Loud Speaker, giving a wealth of pure undistorted volume which must be heard to be believed.

**BUY ON EASY TERMS**

**5/- Secures this Speaker**

The Nightingale "DE LUXE"

**57/6** cash, or 5/- deposit and 12 monthly payments of 5/-.

21 ins. high, with 14-inch Bell Mahogany finished with plated arm and stand.

**10/- Secures this Speaker**



**BAKELITE SOUND CONDUIT & TONE ARM**  
**NIGHTINGALE CONCERT SUPREME**

Guaranteed free from metallic resonance.

**63/-** cash, or **EASY TERMS**, 10/- deposit and 12 monthly payments of 5/-.

**Send Deposit NOW!**

Obtainable from your Local Dealer or direct from:—


**BULLPHONE LIMITED**

**38, HOLYWELL LANE, LONDON**

E.C.2.

**NIGHTINGALE SPEAKERS**

## For LONG LIFE

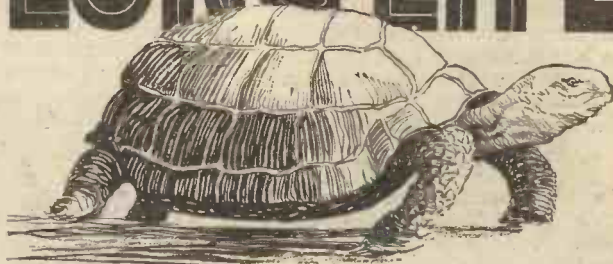

USE

## SIEMENS RADIO BATTERIES

NOT only do they enjoy a reputation for exceptionally LONG LIFE, but in addition possess all those qualities which are essential for the clear and powerful reproduction of Broadcast Programmes. Only in a SIEMENS Battery will you find all these good qualities. Insist on Siemens.


For all sets employing a Power Valve we recommend our

**LARGE CAPACITY (POWER) TYPE**

**SIEMENS "POWER 60" volts 15/-**  
(as illustrated)

**SIEMENS "POWER 100" volts 25/-**

At your Dealers.

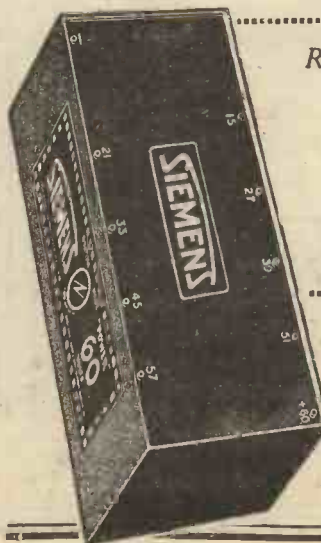

Recommended exclusively by the designers of the

**COSSOR MELODY MAKER**

For 120 volts connect two 60-volt batteries in series.

BRITISH MADE THROUGHOUT

**SIEMENS BROTHERS & Co., Ltd.,**  
WOOLWICH, S.E.18.



## APPARATUS TESTED

(Continued from page 194.)

It is some time since we have experienced so much pleasure during a loud-speaker test, and we have no hesitation in saying that we consider this "Celestion" a long way ahead of its class. Those of our readers who have the opportunity should endeavour to hear it in operation. We are sure they will agree with us when we say it is a revelation in what sound design and construction mean to such an instrument.

### A CORRECTION.

An advertisement concerning the well-known H.T. Eliminators produced by Messrs. E. K. Cole, Ltd., appeared in page 118 of our March 17th issue. Unfortunately, in connection with the address of that firm, the word "EKCO" was incorrectly spelt. The correct and full address is as follows: E. K. Cole, Ltd., Dept. A, "EKCO" Works, London Road, Leigh-on-Sea.

### AN EXCELLENT L.F. TRANSFORMER.

In the usual way the size and weight of an L.F. transformer are, to a certain extent, indications of its efficiency. They may mean that either there is a large amount of iron in the magnetic circuit or that there are ample windings, or both. And in the past we have advised constructors to be wary of transformers of very light construction for these reasons.

But it seems that we shall now have to

revise our ideas in this connection, for the new Mullard L.F. Transformer is both small and light, and yet it is extremely efficient. It is not much larger or heavier than the average R.C.C. coupler.


Of course, its internal structure is far from conventional, new things must be done to achieve such a revolutionary design. The transformer is called the "Permacore," because it incorporates a special iron having this name. This special metal has an exceedingly high permeability so that it allows a high flux density to be used in an iron circuit of very small dimensions. It can

therefore handle heavy currents without reaching "saturation."

The primary is wound with silver and the secondary with nickel wire. The former provides the advantages of good conductivity and capability of resisting deterioration, and the latter introduces excellent magnetic properties and a high resistance just where they are required. And as the makers claim, the use of these special windings provides permanent and robust construction apart from decidedly improved electrical characteristics. We also agree with their claim that "The amplification

of the Mullard transformer is large, smooth and uniform from 250 cycles upward, and below this limit gives a large percentage of its amplification even at 50 cycles. All the bass notes that are wanted are given and there is no shrillness whatever."

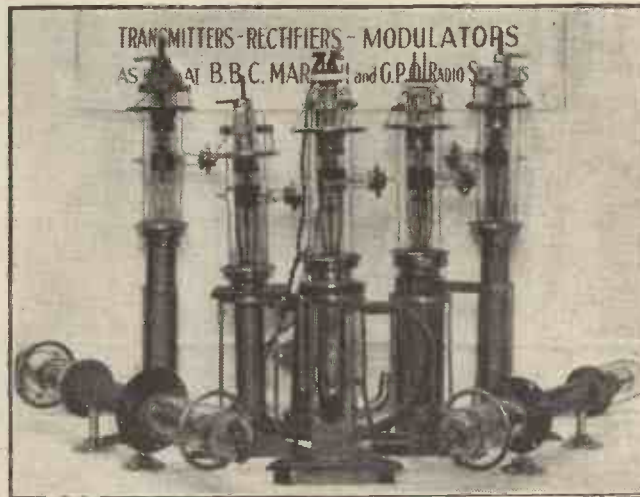In short, it is a very excellent transformer, indeed, and having the additional advantage of extreme compactness and lightness it is certain to achieve wide popularity among discriminating constructors. And as a transformer for portable sets it is absolutely ideal and has no rivals.



"At a recent London exhibition the M.O. Valve Co. displayed a range of water-cooled "Osram" transmitting valves. One, as can be seen above, has its anode cut away to show the glowing filament, a glass water-jacket being substituted for the usual metal casing to reveal the circulating water.

## THE NEW "AUTOGRAM" DOUBLE ELECTRIC GRAMOPHONE

Fitted with two Tone Arms, two Celestion Pick-Ups, two 12-inch Turntables, Automatic Stopping Device for Motors, two Universal Motors, suitable for any voltage from 110 to 240 volts A.C. or D.C., Speed Regulators, Pilot Lamps, &c., fitted in Substantial Leatherette Covered Mahogany Cabinet. Price, Complete £36. Quotations given for every type of design and outfit.

Send For Full Particulars.

MOVING COIL LOUD SPEAKER.—Send now for List of Parts and Special Reference Work by C. P. Allinson, A.M.I.R.E., at the specially REDUCED PRICE of 1/6.

OUR INTERNATIONAL RADIO CATALOGUE (3rd edition) will be sent to all enthusiasts sending 6d. to cover cost of postage and packing

## WILL DAY, LTD.

(The Best in the West)

19, Lisle Street, Leicester Square, London, W.C. 2

Telephone (2 lines):  
Regent 0921 and 0922.

Telegrams:  
Titles, Westrand, London.

**LOEWE RADIO**  
The Famous  
**LOEWE**  
**LOEWE**  
High Vacuum Resistances and High Vacuum Block Condensers



Should be installed in every wireless receiving set.

They are

Free from atmospheric influences.  
Moisture and dust proof.  
Free from losses.  
Fully guaranteed.

Stocked by all reputable dealers.  
Ask for illustrated leaflet.

**LOEWE RADIO COMPANY LIMITED,**

4, Fountayne Road,  
Tottenham, London, N.15.

Telephone: Tottenham 2076.





# HOBBIES THREE

## The Set.

The layout is neat and straightforward. The base-board plan shows component positions and tabulated wires (ready turned with loops) are supplied for the numbered circuit chart.

## The Cabinet.

Can be made by any amateur from the planed boards supplied cut ready for fitting. In good quality mahogany, with moulding and illustrated instructions, for 9/- complete.

## The Speaker.

A handsome cone cabinet complete for 23/1. Can be cut with a fretsaw from planed mahogany boards supplied. Gives results equal to any ordinary instrument.

## As simple as falling out of bed

Those who have never previously built a set will be able to undertake the Hobbies Three. It is a splendid circuit yielding wonderful results. Easy to build and simple to operate. Specially planned for the novice.

**Get your copy of this week's Hobbies to-day from any newsagent or Hobbies' branch—2d.**


If your newsagent has sold out send three penny stamps to Hobbies (Dept. 69), Dereham, Norfolk, for one.

# DIFFERENT

SOMETHING different from all the others because any amateur constructor can make the whole outfit for himself—set, cabinet and cone speaker—quite cheaply and in two or three evenings. The three valve set covers a range from 250 to 2,000 metres on a single tuner. No soldering, no technicalities. The cost is reasonable, and the results startling. An amateur who handled one for the first time logged 32 stations in one evening.
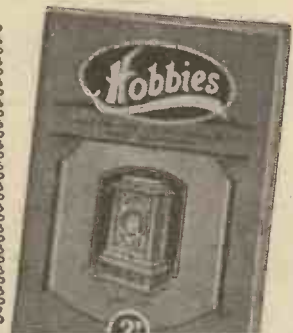
## FREE

WITH THIS WEEK'S HOBBIES IS GIVEN FREE A LARGE SHEET SHOWING COMPONENTS, POSITION, AND WIRING OF THIS SET. WITH AN ILLUSTRATED WRITE-UP ON HOW TO CONSTRUCT IT. INTERESTING TO ALL WIRELESS ENTHUSIASTS. MANY OTHER SUBJECTS OF GENERAL USEFULNESS IN THE SAME ISSUE.



## MURDER! MURDER!!

### Build the "SWEENEY TODD THREE" and MURDER that interfering Local Station.

Sweeney Todd, the Demon Barber of Fleet Street, trapped and murdered his victims ere robbing them. YOU CAN "SWEENEY TODD" YOUR LOCAL station that has been "kyboshing" your DX work and get all stations within range at FULL LOUD SPEAKER STRENGTH. Note the surging power of stations 500 miles away. Note the round melodious tone of music from stations you have never heard before. Note how your "local" can be cut dead out with no "messing about." Simple inexpensive parts. Simple "no soldering" wiring system. Your own "Baby" coils. No stunts. An entirely new and unconventional circuit described fully with full-size blue print in P.P.V. RADIO PLAN No. 30. PRICE 3/- POST FREE.

FREE with each circuit, the P.P.V. 25/- low-wave circuit receiving Sydney (Australia) direct. Also 20 pages of wireless information, some other circuits according to stock and wireless literature. If you cannot send for SWEENEY TODD (price 3/-) send for price lists of P.P.V. circuits.

**PRESS EXCLUSIVES, Wireless Publishers,**  
29, Paternoster Row, London, E.C.4.

## NOW ON SALE

# WIRELESS CONSTRUCTOR ENVELOPES

Envelope No. 1.—THE "RADIANO" THREE. A famous loud-speaker set which you can build in an hour or two—no soldering and a wide range of components to choose from.

Envelope No. 2.—THE "CONCERT" FOUR. Made of standard parts, all easily obtainable, this is a highly-sensitive long-distance set, giving powerful reproduction of wonderful quality on 3 or 4 valves.

In these envelopes you will find every detail of the set simply explained, photographic reproductions and diagrams are included, as well as a full-size Blue Print.

**AT ALL BOOKSTALLS Price 1/6**

By post, 1/9, from the Amalgamated Press, Ltd., Bear Alley, Farringdon Street, London, E.C.4.

**FORMO**  
A MONUMENT IN THE MARCH OF PROGRESS.  
The Formo Shrouded Transformer is the universal favourite.

**10'6** Ratios 1-3 and 1-5  
Send for Catalogue.  
**THE FORMO COMPANY,**  
CROWN WORKS, CRICKLEWOOD  
N.W.2. Phone: Hamp. 1797.





All Editorial Communications to be addressed to The Editor, POPULAR WIRELESS, The Fleetway House, Farringdon Street, London, E.C.4.

The Editor will be pleased to consider articles and photographs dealing with all subjects appertaining to wireless work. The Editor cannot accept responsibility for manuscripts and photos. Every care will be taken to return MSS. not accepted for publication. A stamped and addressed envelope must be sent with every article. All inquiries concerning advertising rates, etc., to be addressed to the Sole Agents, Messrs. John H. Lile, Ltd., 4, Ludgate Circus, London, E.C.4.

The constructional articles which appear from time to time in this journal are the outcome of research and experimental work, carried out with a view to improving the technique of wireless receivers. As much of the information given in the columns of this paper concerns the most recent developments in the radio world, some of the arrangements and specialities described may be the subject of Letters Patent, and the amateur and the trader would be well advised to obtain permission of the patentees to use the patents before doing so.

## QUESTIONS AND ANSWERS.

### MAKING THE FILADYNE OSCILLATE.

F. E. L. (Motherwell, Scotland).—"I have got a Filadyne going and, although I can pick up Glasgow very well, I feel I am not getting the best out of the set, because it will not oscillate properly. Perhaps it is my own fault, because I am using a cheap foreign valve, but as a matter of fact a friend of mine has used one of the same kind in a rather different circuit

and got excellent results; and it was this which persuaded me to try it. Is there anything I can do to make the set oscillate properly? If it will do this I feel sure I shall be able to get plenty of foreign stations on it like my friend."

With such an unusual circuit as the Filadyne it is customary to find that certain changes in the lay-out or components have a great effect upon the operation of the circuit. If, for instance, you have omitted to place a condenser across the telephones this would be quite sufficient to prevent the set from oscillating, and slight variations of coupling or of tapping points will very often overcome the difficulty.

One ingenious Scottish reader has hit upon a method of making the set oscillate which you might like to try, as it is very simple. He simply connects a 35-turn coil in series with the lead which goes from plate to potentiometer and couples this coil to that to which the aerial is connected. He found when using a cheap foreign valve that this made all the difference between faulty operation and good easy oscillation, so that we should certainly try the method, particularly as it is an interesting circuit to experiment with, the results frequently being phenomenal for one valve.

### VOLUME CONTROL WITHOUT DISTORTION.

W. P. (Newbury, Berks).—"In order to get distortionless reception the set must have resistance coupling throughout, but I am a bit puzzled about the volume control.

"The loud speaker is of the moving-coil type, and I understand it will not be very easy to overload this, but all the same I do not want to keep the neighbours awake at night when I am listening in, and I should like to have some method of cutting down the volume if necessary. But the important point is that it is essential that this must not interfere with the quality of reception. Quality is everything, in my opinion. What can you recommend as being the least likely to introduce distortion?"

We think that the most satisfactory method in your case would be to use a high-resistance potentiometer operating on the grid of the first low-frequency valve. Suitable resistances are now being marketed,

(Continued on page 200.)

## REFUSE IMITATIONS!



Standard Size panels supplied in three finishes, Black polished, Black Mat, and Grain polished, carefully packed in attractive cartons. Every panel and piece of ebonite guaranteed and made by British hands.

Apply for particulars of our new foot-proof 4 and 6 contact Former with bases ready for winding, directions and fully illustrated booklet, Price 6d.

ORIGINAL PRIZE-WINNING "BECOL" LOW LOSS FORMER, No. 5. 3 inch diam. overall.

Insist on a Becol Low Loss Former, the Former "with a reputation," incorporated in sets that have taken four first prizes and gold medal, a proof of their superiority. Supplied in cut lengths, 3 in., 4 in., 6 in., packed in cartons, and standard lengths of 3 ft.

Specify

**BECOL**

Registered Trade Mark.

products



THE BRITISH EBONITE COMPANY LIMITED, HANWELL LONDON W.7

*Powerful-Loud Speaker-Reception from a Crystal Set!*

Without Accumulators or Valves. Earth and Aerial Connections only are needed. Tunable to all wave-lengths.

**The CRYSTO-BAR**

Wireless Receiver — an epoch-making New Wilson achievement—is an up-to-date Crystal Set combined with the Microphone Bar Amplifier.

**50/-**  
POST FREE

It will make wireless cheaper and better for you. Only one or two inexpensive dry cells of 1½ required to give loud speaker results equal to a two-valve set.

Write for our fully descriptive and illustrated list POST FREE.

Sole Manufacturers and Patentees:


**NEW WILSON ELECTRICAL MANUFACTURING Co. Ltd.**

18, Fitzroy Street, Euston Road, W.1.

Phone: Museum 8974.





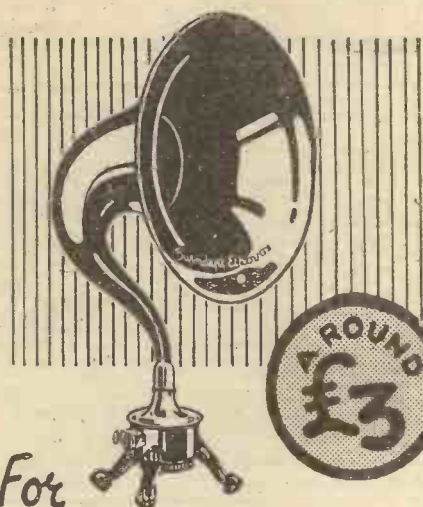

## For Natural Tone the Ethovox

Test the Ethovox Loud Speaker in *any* way you please and it will please you in *every* way! Its natural tone is full and mellow and it gives life to broadcast speech and music. The Ethovox is capable of considerable volume without any trace of distortion. Many thousands of this famous make have been sold and it has never been found necessary to modify the design in principle—because the Ethovox has *always* given good results. Hear this speaker—try one on your set.



## Burndept Condensers for easier Tuning

Having a spindle and end-plates of insulating material and a metal earth shield, the new Burndept Condenser is absolutely free from hand-capacity and gives increased signal strength. Experts acknowledge this Burndept product to be an important improvement in condenser design. There are two types: LOG-LAW (for H.F. circuits), .0003 mfd., 15/-; .0005 mfd., 15/6. SQUARE-LAW (for capacity reaction and short-wave circuits), .00007 or .0001 mfd., 13/6. The Log-Law Condensers are easily ganged and are supplied with printed scales for 150–3,000 metres (1/6 per set). Use these Condensers in your next set.

# BURNDEPT

Offices: Blackheath, London, S.E.3.  
London Showrooms: 15, Bedford St., Strand, W.C.2.




B.T.H. Nickel Filament Valves have a higher emission than other 2 volt valves of corresponding types, and they retain this emission for a longer period. In other words they give better reception and have longer useful lives.

You want to have and to maintain the best results of which your set is capable. B.T.H. Nickel Filament Valves alone will enable you to do this. Get some today and enjoy better radio from now on.

B. 210H	B. 210L	B. 215P
R.C. and H.F.	General Purpose	Power
Fil. Volts . . . 2	Fil. Volts . . . 2	Fil. Volts . . . 2
Fil. Amps. . . 0.10	Fil. Amps. . . 0.10	Fil. Amps. . . 0.15
Max. H.T. V. . 150	Max. H.T.V. . 120	Max. H.T.V. . 120
10s. 6d.	10s. 6d.	12s. 6d.

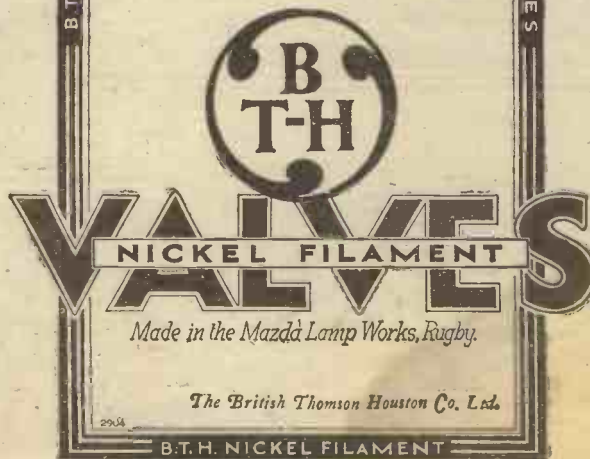
The above prices are applicable in Great Britain and Northern Ireland only.









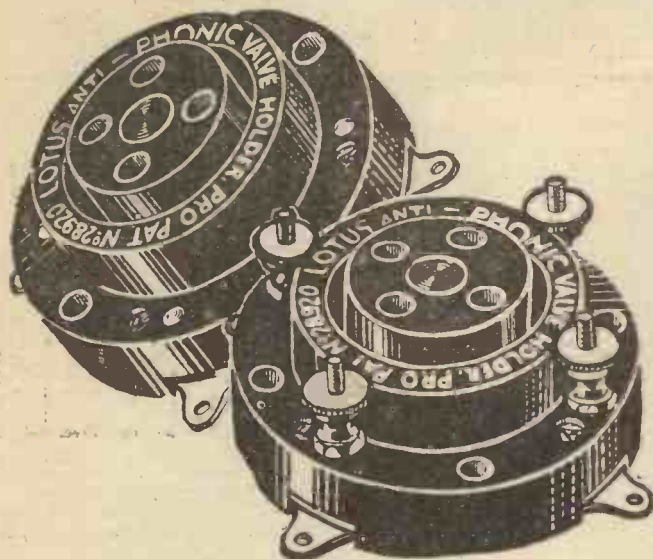

## CUT OUT MICROPHONIC NOISES!

Lotus Valve Holders cut out all microphonic noises. They produce pure, clear reception, absorb shocks and protect the valves.

\* If your set is prone to microphonic noises, look to your valve holders. A cheap, shoddy valve holder quickly spoils reception. Change to Lotus and you will get best possible results.

Without terminals - 1/6  
With terminals - 1/9

From all radio dealers



Made by the makers of the famous Lotus Remote Controls, Lotus Vernier Coil Holder, and Lotus Jacks, Switches and Plugs.

Garnett, Whiteley and Company, Limited,  
Lotus Works, Broadgreen Road, Liverpool.



## BRAINS!

RADIO Valves are the brains of your Wireless Receiver.

When you buy a new set look to the Valves. In nine cases out of ten you will find that they are Six-Sixty Valves—first-class Valves that are fitted as standard by Britain's leading set manufacturers.

Fit a new set of Six-Sixty's in your existing set. We need not tell you to notice the difference; it will be obvious at once.


Six-Sixty Valves are non-microphonic, are matched valve with valve, and give perfect electrical balance.

There is no Radio Valve like Six-Sixty, and no other Radio Valve is as good.

We publish a booklet that will plainly tell you why. Ask for a copy at the nearest radio shop, or write direct to us

All types and voltages,  
from 10/6.

USE ONLY

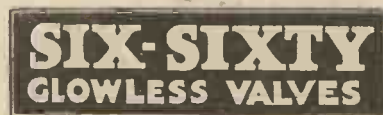


THE ELECTRON CO., LTD.

122-124, Charing Cross Road, London, W.C.2

Telephone: Regent 5336.

NO VALVE LIKE IT

# Economise in floor space

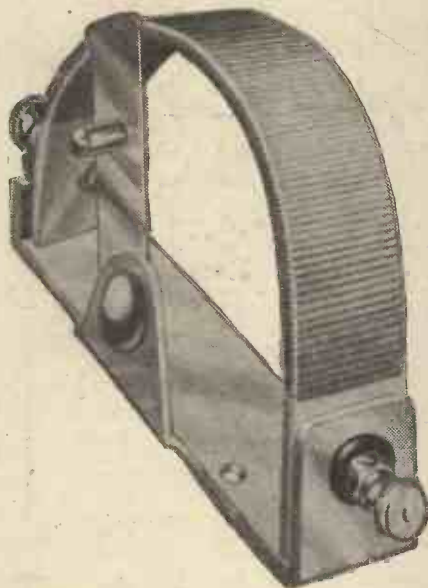

The "PEERLESS" VARISTOR stands up on the baseboard, taking only a fraction of the usual space. It can be fitted on an already crowded panel. The adjustable phosphor-bronze arm is easily accessible. The windings are of best-quality resistance wire, wound tightly on insulating fibre. Terminals are fitted in the most convenient position. You can buy 5 types—3, 6, 10, 15 and 20 ohms. The "Peerless" Varistor is fine for the Cossor "Melody Maker."

From all good dealers or direct:—

## PEERLESS VARISTOR

BEDFORD ELECTRICAL &  
RADIO CO., LTD.  
22, Campbell Road, Bedford.  
LONDON: 21, Bartlett's Bldgs., Holborn  
Circus, E.C.1  
GLASGOW: 115, St. Vincent St., 2.2

1/3

## RADIOTORIAL QUESTIONS AND ANSWERS

(Continued from page 200.)

aerial coil of any value in the position allocated to one in the original lay-out."

"The reason of this achievement under these strange conditions may be quite simple to an expert, but I have a lot to learn about wireless, and I wondered whether I had in my experimenting unconsciously stumbled across something which may be interesting?"

What was happening in this case was that you were in effect cutting out the first valve and receiving the short waves directly on the detector portion of the set. It is a peculiarity of short-wave signals that they hop across space in a most amazing way, so that even if the aerial lead is only brought quite close to the coil they pass across the intervening space, which forms a kind of natural condenser, and find their way to the grid circuit. As your 9-turn coil was tuned to K D K A, the signals were impressed upon the grid of the detector valve and thus operated your telephones in the ordinary way.

When the leads from the aerial were joined to the .0002 mfd. fixed condenser at the point where this is tapped to the grid coil you were in effect switching out the H.F. valve, but when you plugged the coil in the centre-tapped aerial holder the aerial was connected through this coil to earth and most of the signals choose this path instead of the alternative path via the short-wave coil in the detector.

## "P.W." TECHNICAL QUERY DEPARTMENT

### Is Your Set "Going Good" ?

Perhaps some mysterious noise has appeared and is spoiling your radio reception?—Or one of the batteries seems to run down much faster than formerly?—Or you want a Blue Print?

Whatever your radio problem may be, remember that the Technical Query Department is thoroughly equipped to assist our readers, and offers an unrivalled service.

Full details, including a revised scale of charges, can be obtained direct from the Technical Query Dept., "Popular Wireless," Fleetway House, Farringdon Street, London, E.C.4.

A postcard will do: On receipt of this an Application Form will be sent to you free and post free, immediately. This application will place you under no obligation whatever, but having the form you will know exactly what information we require to have before us in order to solve your problems.

Your experience constitutes an interesting instance of how powerful is the penetration of the short wave, even where the aerial system is anything but conventional, and similar instances of short-wave peculiarities are coming to light daily. As this is your first three-valve set we should like to take this opportunity of congratulating you

### THE POSITION OF THE LOUD SPEAKER.

"OLD STAGER," (Merstham, Surrey).—"We have been happily married for more years than I care to remember, but now we are falling out about the position of the loud speaker! Both my wife and myself are musical enthusiasts, and there is not much played at 2 L O that one of us does not listen to, one way or another. But whereas I like the loud speaker placed on the table in the middle of the room (loudest), my wife insists that it sounds better when it is placed near the window. I cannot convince her that the position of the loud speaker has no effect upon the reproduction. (Possibly you know what women are?) So that if you would write to me I can assure her that her idea is all nonsense, and I should be able to have the

(Continued on page 204.)

## FREE 5-DAY TEST SEND NO MONEY

We will send you without obligation up to 3 Valves for test in your own set, to be paid for or returned at the end of trial.

## OCTOPUS VALVES.

British Made. Fully Guaranteed.  
Low Consumption.  
Maximum Power and Distance.

Not to be confused with cheap valves of similar characteristics.

HOME CONSTRUCTORS of any make of set should take advantage of FREE TEST.

H.F., Det.,  
L.F., R.C.  
5/6  
Post Free.

2 or  
4 Volt.

Power  
3/-  
Post Free.

Type	Imp.	Amp. Fac.
H.F. 206	35,000	15
Det. 206	25,000	12
L.F. 206	18,000	8
R.C. 206	120,000	40
H.F. 215	40,000	20
Det. 215	30,000	15
L.F. 215	12,000	6
H.F. 406	23,000	15
Det. 406	19,000	9.5
L.F. 406	11,000	6
R.C. 406	120,000	40
P. 220	6,000	6
P. 415	4,000	4

WENBANS, 74, New Oxford St., W.C.1.



When your set gets out of hand take the one step that ensures the perfect balance necessary to secure harmonious, distortionless reception—fit a Sifam Meter and tune with your eyes on the dial FREE leaflet "Distortion" from (Dept. P), S.I.F.A.M., 10a, Page Street, Westminster, S.W.1

PLEASE be sure to mention  
"POPULAR WIRELESS"  
when communicating with  
Advertisers. THANKS!

MOVING COIL SPEAKERS AND GRAMOPHONE PICK-UPS. Demonstrations Daily. Call and Listen. It is worth your while. Blue Spot Balanced Armature Cone Unit, 25/-; Magnavox Ditto, 63/-; Balanced Armature Type Cone Unit, 10/6. Moving Coil Milliameters, 17/- and 17/6.

Telephone: Museum 0241. Send or call for our 136-page Catalogue FREE.  
**ELECTRIC (GRAFTON) COMPANY**  
Dept. P.W.  
24, Grafton Street, Tottenham Court Road, W.1.


## ADVERTISEMENTS

As far as possible all advertisements appearing in "P.W." are subjected to careful scrutiny before publication, but should any reader experience delay or difficulty in getting orders fulfilled or should the goods supplied not be as advertised, information should be sent to the Advertisement Manager, "Popular Wireless," 4, Ludgate Circus, London, E.C.4.




*Satisfaction  
Guaranteed  
or money  
refunded*

# RIDLEY for RADIO

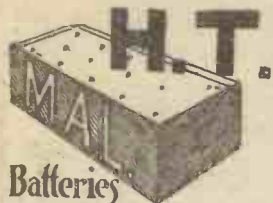

Batteries  
for your Wireless!  
**RIDLEY'S**  
price **4/11**  
60 volts

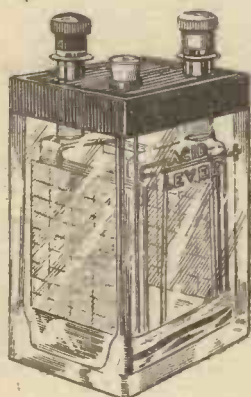The finest value in H.T. Batteries,  
having long life and giving con-  
stant output. 100-volt size, 8/6.  
Add 6d. postage.



2-volt Accumulators, 20 amps.  
hour capacity, well made, good  
large plates well insu-  
lated, in glass case, each **3/6**  
Carriage 6d. extra.



Ridley Head-  
phones, finest  
value on the  
market, guar-  
anteed.

Per pair,  
**4/11**  
Add 4d.  
postage.

## CABINETS SPECIAL OFFER

21 x 7 Cabinet Oak  
**16/-**  
18 x 7 Cabinet Oak  
**16/-**

ILLUSTRATED CATALOGUE POST FREE ON REQUEST

# CECIL RIDLEY

"RADIO HOUSE," MIDDLESBROUGH

'Phone 1368.

Here is a fine list of Radio  
Bargains you will be interested  
in. I purchased for quick clear-  
ance and offer at bargain prices.

72-yd. COILS RED AND BLACK FLEX,  
usually 10/6. My Price, 6/9.

Devicon Variable Condensers, .001,  
2/- each.

Miniature Ebonite Switches, 9d. each.

44-volt Flash Lamp Batteries, 3/6 per  
doz.

Neutron Crystals, 11d. each.

Hertzite Crystals, 6d. each.

.0002 Devicon Variable Condensers, 3/6.

4-volt Frelat Valves, 3/- each.

4-volt Frelat Power Valves, 3/- each.

Murray Valve-holders, 6d. each.

Valve-holders, 1/- each. Baseboard type.

Antimicrophonic Valve-holders, 10d.  
each.



Ebony Anti-  
microphonic  
VALVE-  
HOLDER,  
cheapest on  
the market,  
considering  
quality.  
Base-board  
mounting, 1/9

Single Circuit Plugs and Jacks com-  
bined, 2/6.

H.T. Voltmeters, 0-130, 4/3 each.

2- and 4-volt Electra Valves, 2/6.

30-ohm Rheostats, 9d. each.

Mans. Fixed Condensers, .5, 6d. each.

Mans. Fixed Condensers, .25, 6d. each.

## JACKS AND PLUGS

Single Circuit Jack, open, 1/3  
Double Circuit Jack, closed,  
1/6.

Filament Jack, Single, 1/9.

Filament Jack, Double, 2/3

Plugs, 1/6, 2/-, and 2/9 each

S.P.D.T. Switches, 6d.

D.P.D.T. Switches, 9d.

.0005 S.L.F. Condensers, 3/6

Push-pull Switches, 9d.

Baseboard Rheostats, 11d.

6-in. Panel Brackets, 6d.

2-way Coil-holder, geared, 2/6 each.

Valve Windows, 6d. each.

Transfers, per packet, 3d.

9-volt Grid Bias Batteries 1/- each.

Hydrometers, 2/- each.

Grid Leaks, 6d. each.

"Sovereign" Coil-holders, 9d. each.

Basket Coil-holders, 9d. each.

Porcelain Valve-holders, 3d. each.

.0003 Condenser and Grid Leak, 2/-  
each.

Scrap. Ebonite, 8 square inches a 1d.  
(in 5/- parcels only).

.001 Finstone Condensers, 6d. each.

Croix Transformers, 3/6 each.

Forward Transformers 3/- each.

Dundas Loud Speakers, full-size horn,  
25/-.

6-pin Coils, 3/6 each.

Brass Vaned Var. Condensers, .0005,  
3/10 each.

2-mfd. Condensers, 2/3 each.

2-volt Power Valves, 3/- each.

Complete Parts for Coscor Melody  
Maker, 25s.

Complete Parts for Mullard Master  
Three, 25 15s. 0d.

(Write for details.)

## The KABINET-KONE-KIT!

This beautiful  
**CABINET  
SPEAKER**

is only **52/6** complete  
in oak or 55/- mahogany

**INCOMPARABLE RESULTS!**



Incorporating the famous

**BLUE SPOT**


Four-pole, Balanced Armature

**CONE UNIT**

(as illustrated)

and the scientifically pro-  
duced "Six-Sixty" Cone.

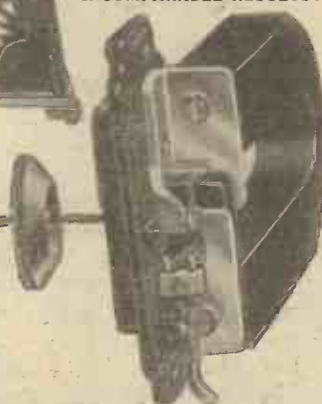Sold as a complete construc-  
tional outfit you can put it  
together in a few minutes  
by the aid of our illustrated  
booklet issued with each kit.



**ASK YOUR DEALER TO DEMONSTRATE IT AGAINST  
THE MOST EXPENSIVE MODELS AVAILABLE.  
THE RESULTS WILL ASTOUND YOU!**

If unable to obtain from your dealer, write direct to either:—  
**F. A. HUGHES & Co., Ltd.** **WALKER BROS. (Guildford) Ltd.**  
204/6, Gt. Portland Street, W.1 or St. Joseph's Works, Bramley, Guildford



**SAVE  
MUCH  
SPENDING**

**BY  
TIMELY  
MENDING  
WITH**



# FLUXITE

it simplifies soldering

All Hardware and Ironmon-  
gery Stores sell **FLUXITE**  
in tins, price 8d., 1/4 and 2/8.  
Another use for Fluxite—  
Hardening tools and Case  
Hardening. Ask for leaflets  
on improved methods.


**FLUXITE  
SOLDERING  
SET—complete**

**7/6**

or LAMP only

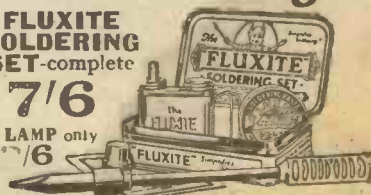**7/6**

**FLUXITE LTD.**  
Dept. 324, Rotherhithe,  
S.E.16





## What constitutes an excellent Loud-Speaker?



MODEL C12.

### Even response.

Not only on the low, but on the middle and the high frequencies.

### Extreme sensitivity.

Sensitive to the output from the weakest set.

### Adjustment.

Ability to produce weak as well as very heavy signals without readjustment.

### Improves with age.

Improves and *not deteriorates* with the passing of the years.

### Distinctive appearance.

An excellent loud speaker breathes craftsmanship in appearance, so careful and capable is the workmanship wrought upon it. And it must be British.

Let your dealer convince you that "CELESTION," most excellent of loud speakers, passes all these tests readily.

Write now to Dept. B for the "Celestion" illustrated folder and also for our new Gramophone Pick-up leaflet.

# CELESTION

THE VERY SOUL OF MUSIC

Write to Dept. B,  
THE CELESTION RADIO CO.,  
Hampton Wick, Kingston-on-Thames.

Showrooms: 33/35, VILLIERS ST., W.C.2. French Agents: CONSTABLE & CO. PARIS.

## RADIOTORIAL QUESTIONS AND ANSWERS

(Continued from page 202.)

loud speaker as near to me as she has it to her, and peace will thus be restored in our once happy home."

In a great many instances the position of the loud speaker *does* alter the "tone" of the reproduction. This is on account of the fact that the sound waves set up by the loud speaker are reflected by neighbouring surfaces. And the character of this reflected wave will obviously be different if the sounds reflect from a perfectly flat surface, such as a wall, than when the surface is a broken one such as perhaps a heavy curtain or other soft furnishing material. It is therefore quite probable that in your case there is a scientific explanation for the difference noted by your wife.

(We do not go so far as to say, however, that there is any need to draw your wife's attention to this fact. We do know what women are!)

### THE BARGAIN HUNTER.

E. K. (Canonbury, London, N.).—"The boy is very keen on wireless, but the other Saturday he spent a shilling on a big choke (apparently ex-Government) which he picked up on a stall in the Farringdon Road. The man who sold it to him said he could 'protect his loud speaker with it,' whatever that means, but although he told the boy some story about connecting it in the place of the loud speaker we have not so far succeeded in making any use of it. It is marked 50H, and it appears to be O.K. because you can hear clicks from it when a battery is connected across it with the telephones. Is there any use to which we could put it on the set?"

Apparently you have got a bargain, for if it is a good choke it is certainly exceedingly cheap at a shilling, and it *can* be used to protect the loud-speaker windings as stated. In a great many sets the H.T. current passes from the battery through the loud-speaker windings to the plate of the valve. This main current does not operate the loud speaker, but is, from the loud speaker's point of view, so much waste.

### Output Filter Connections.

What causes the sound is the *variation* in this current, and by means of the L.F. choke we have a method of operating the loud speaker by the variations without the necessity to pass a heavy, steady current through the windings. Thus the loud speaker is relieved of a comparatively heavy load, and if long leads are used the danger of leakage across these leads is entirely obviated. In fact, there are several distinct advantages about the method, which is called "filtering" the loud-speaker output.

In addition to the choke, however, you require a large fixed condenser of one or two, or more, mfd.s., and then all you have to do to get the advantages of the filter is to connect up as follows:

Disconnect the loud speaker from its terminals and join the choke across these. Now join one side of the large fixed condenser to that side of the choke which is connected to the plate of the last valve. Join the remaining terminal of the large condenser to one side of the loud speaker. The remaining side of the loud speaker is now joined to any point of the set connected to the filament of the last valve, probably H.T. negative or L.T. plus, or earth.

If you draw a sketch of this arrangement you will find that the steady H.T. current now passes through the windings of the choke direct to the plate of the valve. There is an alternative path to the plate from H.T. negative via the fixed condenser and the loud speaker, but the fixed condenser is an effective barrier to any direct current getting through this way. Steady current passes easily through the choke, but the varying current caused by the speech frequencies has great difficulty in overcoming the impedance of the choke, and therefore such variations in current find a much easier path through the alternative route consisting of the fixed condenser and the loud speaker. In this journey they operate the loud speaker just as well as if it were connected in the plate circuit of the valve. If you try the method we feel convinced that you will be delighted with the results.


### BACK NUMBERS OF "P.W."

J. W. F. (Hounslow).—"Where can I get back numbers of POPULAR WIRELESS?"

Application for back numbers should be made to The Amalgamated Press, Ltd. (Back Number Dept.), Bear Alley, Farringdon Street, E.C.4.

Price 4d. per copy.

## It will pay you to insist on Columbia

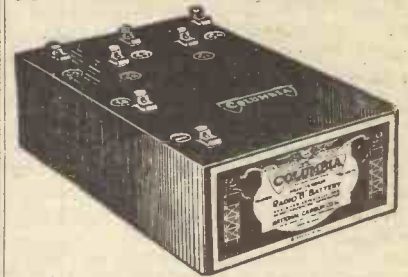

### Columbia

No. 4780, 60 volts type, 22/6.

Figures speak louder than words, and figures prove conclusively that Columbia High Capacity Batteries combine Efficiency with Economy to a far greater degree than any other H.T. Battery obtainable. The greater the weight of an H.T. Battery the greater its recuperative powers, and as the Columbia 60-volts type weighs 13 lb., as compared with 5 lb. of other batteries, the inference is obvious. In fact, the Columbia Battery commences its life containing nearly three times the amount of electricity-producing material contained in the smaller batteries.

And every Columbia Battery sold carries the full guarantee of the manufacturers, The National Carbon Company, the world's largest battery manufacturers Economise by using Columbia.

Price of 60-volts type—22/6.

Ask your dealer for descriptive literature.

J. R. MORRIS,  
15, Kingsway, London, W.C.2  
Scotland: J. T. CARTWRIGHT,  
3, Cadogan Street, Glasgow.

## CONDENSERS of QUALITY!

No mass production methods are employed in the manufacture of Camden Condensers. Every Condenser is stamped with a Serial No., and accompanied with a guarantee of 6 months' real service. Telegrams: KAMELCO, Telephone: Runcorn 109.

Send for list and prices to Camden Electrical Co., Stanley Chambers, Runcorn.



### WET H.T. BATTERIES

Solve all H.T. Troubles.

SELF-CHARGING, SILENT, ECONOMICAL. JARS (waxed) 2 1/2" x 1 1/2" sq. 1/3 doz. ZINCS, new type 1 1/2 doz. SACs 1/2 doz. Sample doz. (18 volts), complete with bands and electrolyte, 4/3, post 9d. Sample unit 6d. 16-page booklet free.

Bargain list free.

AMPLIFIERS 1-VALVE 19/-, 2-VALVE 32/-, 2-VALVE ALL-STATION SETS 4/-  
P. TAYLOR, 57, Sudley Road, STOCKWELL LONDON

PLEASE be sure to mention "POPULAR WIRELESS" when communicating with Advertisers. THANKS!

Make your loud speaker live

FIX A "TONER"

across the terminals and your loud speaker will reveal a clarity of reproduction equalled only in the broadcasting studio itself. This wonderful device removes all distortion and undesirable noises from any loud speaker or phones. The result of a long scientific research made applications invited

Send to day to

The JUNCTION ENGINEERING CO.  
(Dept. 13) 149a, JUNCTION RD.  
LONDON, N.19

26 POST FREE



## NEWS FROM SAVOY HILL.

(Continued from page 178.)

at 8 p.m. will be relayed from Carlisle Cathedral. 5 G B listeners will hear a symphony concert during the afternoon, and Bach's Cantata for Easter Day, followed at 6.30 by a service from Birmingham Cathedral. The evening concert will consist of music by the Wireless String Orchestra for London, and a programme by the Birmingham Police Band for 5 G B.

An attraction from London on Bank Holiday, Easter Monday, will be a burlesque pantomime by Mabel Constanduros filling the first part of the evening programme, after which the Wireless Military Band, under Mr. Walton O'Donnell, will give a programme of popular music, and there will, of course, be dance music until midnight. The alternative from 5 G B consists of a concert of chamber music and a play until 10 p.m., when there will be dance music until 11.15.

### Newcastle's Scandinavian Programme.

The many Scandinavian interests on Tyneside have induced the Newcastle station to arrange a special Scandinavian Programme on Tuesday, April 10th. Mr. Edgar L. Bainton, of the Conservatoire of Music, Newcastle, is to be the conductor, and the artistes include the distinguished Norwegian pianist, Madame Johanne Stockmarr, and Miss Gundrun Nordraak, both of whom will be making their first appearance in the local studio. Madame Stockmarr will include among her items Grieg's Concerto and pieces by Sibelius. Svendsen, Sinding and other Scandinavian composers.

### Liverpool Features.

Merseyside listeners have their own special programme from the Liverpool Station in the last part of the evening transmission on Monday, April 16th, when a pianoforte recital will be given by Norman Henderson, the brilliant young Liverpool pianist, who has already achieved fame both in this country and on the Continent. There will also be two short plays, "The Family Group," a farcical comedy, the scene of which is set in a photographer's studio, and "Witch-Wife," which is a play of terror, the action taking place in a Devonshire farm-house in the year 1697.

The first of these plays is by Mabel Constanduros, while the other play was written by her in collaboration with Michael Hogan. Songs will also be sung by Constance Astington (soprano), and some violin solos played by John P. Sheridan, who will be using an instrument made by Stradivarius.

### Music from Leamington.

The first concert of the season from Jephson Gardens, Leamington Spa, will be broadcast from 5 G B on Tuesday, April 10th, when a programme of music will be given by the Band of H.M. Royal Artillery (Mounted), conducted by Mr. T. J. Hillier. Their items will include a suite of Three Light Pieces (Fletcher), the Overture to "The Sicilian Vespers," and a selection of "Songs of the Fair" (Easthope Martin). Songs will also be sung by Walter Glynne (tenor), and other items given by Myra B. Johnson (entertainer). A permanent line has been installed between the Birmingham studio and Leamington Spa.



THE new Mullard "Permacore" Transformer is based upon absolutely revolutionary principles which give these outstanding features. Small in size; great in amplification. High flux density without saturation. No resonant peaks to give unnatural reproduction.

All shrillness eliminated.

Gives all the bass notes required.

Silver primary, nickel secondary; windings that will not deteriorate.

Silver for the primary has the advantage of good conductivity and no deterioration. Nickel for the secondary has the advantage of high resistance and magnetic properties.

The iron in the Mullard Transformer is a specially treated and scientifically prepared material with a high permeability that allows the use of a high flux density in an iron circuit of exceedingly small dimensions.

This new wonder Mullard Transformer opens new possibilities for the constructor. It is the finest L.F. Transformer ever produced.

Obtainable from all radio dealers.

25/-


# Mullard

## MASTER · RADIO



# KEYSTONE COMPONENTS MEAN CARE-FREE RADIO

## KEYSTONE "MIDGET" REACTION CONDENSER

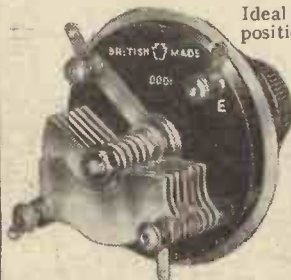

Ideal for the many positions where a small capacity condenser is required. An aluminium shield prevents hand-capacity effects, and a special taper bearing gives a beautifully

smooth movement. Accurately designed and rigidly constructed, this Keystone condenser is backed by the usual Keystone guarantee of efficiency. Capacity .0001 mfd. Price 5/6. '00005 5/-.

## KEYSTONE ALUMINIUM BRACKETS

Keystone Brackets are made from high-grade aluminium. The slots are a special Keystone feature, and the finish is of that standard which has made Keystone components the choice of thousands of radio enthusiasts.

2/-  
PER PAIR

NOTE THE  
SLOTS—A  
KEYSTONE  
FEATURE



WAVE-  
TRAP  
Standard  
Model

15/-

## SIX - PIN COIL BASE

Standard spacing with terminals arranged for easy accessibility. For use where the standard 6-pin coils are utilised without the actual screen. Price 2/9



**PETO-SCOTT Co., Ltd.,**  
77, City Road, and  
62, High Holborn, London  
Also 4, Manchester Street, Liverpool.

## SHORT-WAVE NOTES.

By W. L. S.

THE use of H.F. amplification for short-wave receivers seems to be achieving a considerable measure of popularity among those who are enthusiastic enough to take the necessary trouble.

True, it necessitates one or more extra tuning controls, which make really quick searching rather difficult, but there is a great deal of "certainty" in the performance which such a set will put up.

One may always argue that all the signals which are available will make themselves heard on an ordinary oscillating detector, but with a set incorporating H.F. stages greater selectivity can be obtained, and signals which would be smothered in mush on the average two-valver may be cleared of all such noise and received intelligibly. The short-waver with one or two stages of H.F. is the ideal set for those who wish to receive short-wave broadcast with something more than ordinary regularity.

It is surprising now to reflect that it is only a matter of about a year since it was believed impracticable to obtain any high-frequency amplification of signals below about 150 metres! This is the more surprising in view of the fact that perfectly ordinary circuits will now do the work; as a matter of fact, the straight circuit has been found considerably more successful for this purpose than any of the freak or unusual circuits that have yet been tried.

### Effect of Locality.

Different localities have greater effects upon short-wave work than upon ordinary broadcast reception. I have recently moved from a rather low and screened situation to a locality which, while not particularly high, is at the same time comparatively open and free from screening. The difference in reception is amazing.

On the whole, distant stations do not seem to be received at better strengths than before, but quite a different set of stations is heard. Several of the old familiars are now inaudible, and stations that were often eagerly listened for, but never heard, at the old station now come through with great vigour.

Transmission, strangely enough, does not seem to have been affected to such a great extent. The same directional properties seem to persist; the aerial still runs due east and west. Strong reports are still received from the same stations as before.

However, as the apparatus has only been installed for a matter of three weeks, it is probably somewhat premature to try to sum up the conditions.


I am of the general opinion that a good earth is preferable to a counterpoise for short-wave work. By a good earth is meant a large, buried plate or mat, not a water-pipe connection, and a short lead is certainly desirable.

For those who are not in a position to instal this arrangement, I certainly recommend a counterpoise, but it is well worth one's while to try an earth in comparison with the other before making a final decision.

## PANEL PLATE TUNER

Prov. Pat.

Regd. Design

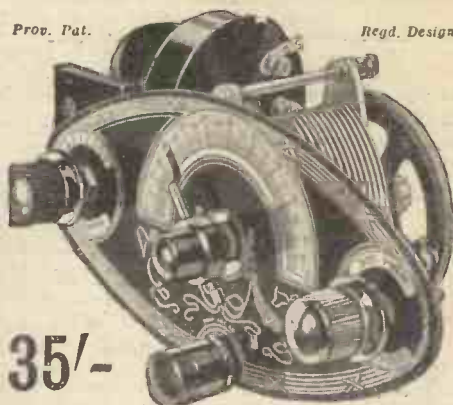

Great as is the popularity of our numerous high-grade Components and Receivers, the success achieved by this Unit has beaten all records. Amateur constructors in all parts of the country realize the immense assistance this unique assembly of parts affords them in the building of an efficient set which has the appearance of a professional product.

Above illustration clearly shows details of various parts mounted on richly engraved panel in black and gold or silver. No ebonite panel required, no coils to change, and diagrams for building 2 or 3-valver supplied.

35/-

## LAMPLUGH BRITAIN'S BEST RADIO

"LAMP-LOO"

S. A. LAMPLUGH, LTD.  
KING'S ROAD, TYSELEY, BIRMINGHAM.  
Representatives for London and Southern Counties:—  
G. O. Shore & Co., 28, Newman St., Oxford St., W.1.

TRADE MARK RD40 .2/-  
RED DIAMOND

REGD. A RADIO EXPERT writes:—

"I have now thoroughly tested your RD40 Detector, both on crystal and reflex sets. I have found it very satisfactory in every way, it is very efficient."

THE RECOGNISED DETECTOR FOR ALL CIRCUITS USING CRYSTAL RECTIFICATION. By Insured Post 2/3 or 2/9 with shield. Can be mounted on brackets or through panel. Once set always ready. Not affected by vibration. Each one is tested on broadcast before despatch, and is perfect. Of all high-class Radio Dealers or Sole Makers:—  
**JEWELL PEN CO., LTD.**  
(Radio Dept. 46)  
21-22 Gt. Sutton St., LONDON, E.C.1.

Shield for same 6d.  
"RED DIAMOND"

THE RELIABILITY GUIDE No. 999

0-6 VOLT METER  
Reliable Instrument 3/6.  
Double Scale Type 0-6 v., and 0/120 v., 5/6

S.O.S. BATTERY TESTER  
3-Head Type  
Tells immediately full or empty. Only 3/6. Vent Plug Type, 1/6

**J. H. TAYLOR & CO.**  
4, RADIO HOUSE,  
MACAULAY ST., HUDDERSFIELD.

THE LITTLE CELLS THAT SATISFY.  
Eton Primary H.T. Battery P.I. Porous Pot Cells, S1 and S2 Sac Cells. All complete.

	1-cell	6-cell	12-cell	30-cell
P.1	6d.	3/3	5/9	14/-
S.1	6d.	3/-	5/3	12/-
S.2	4d.	2/6	3/10	9/6

Send 12d. stamp for booklet giving full particulars to:—  
**THE ETON GLASS BATTERY CO.**  
46, St. Mary's Road, LEYTON, E.10

PLEASE be sure to mention  
**'POPULAR WIRELESS'**  
when communicating with  
Advertisers. **THANKS!**



## THE "HARTLEY" ONE-VALVER.

(Continued from page 191.)

The success of a little circuit like this depends very largely upon proper adjustment of the valve, and you must be prepared to spend a little time securing just the right combination of high-tension voltage and filament current for the best signals and smoothest reaction control. You are likely to find with most valves that a somewhat higher value of H.T. will be necessary than is usually the case with reaction circuits, smooth control being usually obtained with something like 60 to 65 volts on the average.

### Tuning Without Interfering.

Searching with a set of this type requires just a little practice to get the hang of running over the scale of the tuning condenser without actually oscillating, yet keeping the set on the very edge of oscillation, so that it is in its most sensitive condition. It is worth while to obtain this knack, and once acquired you will find that there is considerable satisfaction in feeling that you have learnt the method employed by all skilful operators, and one moreover which ensures your picking up any station within the limits of the set, yet causing no possible interference with anybody.

Finally, just a word as to the results which you will get. On test, this little set proved to be very good and noticeably above the average of single-valve reaction circuits, and quite a long string of foreign stations were logged with it.

### Regarding Results Reports.

Now, I always think that it is very misleading to give a string like this without comment, and to leave the constructor to imagine that he will be able to duplicate these results immediately. It must be remembered that on test the set is handled by a very skilled operator, who usually has at his disposal a highly accurate wave-meter for identifying stations quickly so that in a very short time he can make a really wonderful "catch."

As a matter of fact, to give such a report without a really definite warning is rather misleading, and I propose to try and give the reader some idea of what he is likely to do under his own conditions and without too great a degree of skill in operation.

Well, with a reasonably efficient outdoor aerial, it should be quite easy to hear at least a dozen foreign stations at clear 'phone strength provided that you do not live in a particularly bad locality, either with regard to reception conditions or with regard to bad jamming from a very nearby local station. On the longer wavelengths there should be something like a good and clear headphone strength, so that you may quite well expect something like twenty stations in the course of time as you gain skill in manipulating the controls.

### NEXT WEEK.

Full details will be given of

### THE "INDUCTO-CRYS,"

something new and highly efficient in the way of crystal sets.

ORDER YOUR COPY NOW.

# LONG LIFE

The Battery that lasts longest is the SURE-A-LITE—a fact your radio dealer will confirm.

No other battery can claim such recuperative powers or give such smooth and silent service, because no other battery is made just like a SURE-A-LITE. The cells in a SURE-A-LITE are larger than any other and, we definitely state, better designed and constructed. Each SURE-A-LITE is supplied in a sealed, dust-proof cover. That seal is your guarantee of perfect condition.

**GRID BIAS.** Each 66 volt battery tapped every 1½ volts up to 6 volts. Each 108 volt battery tapped every 1½ volts up to 9 volts.

## SURE-A-LITE

BRINGS MOST IN — GIVES MOST OUT  
REGISTERED TRADE MARK

"Supra"  
66 volts  
7/11  
108 volts  
14/3

"Giant"  
66 volts  
10/6  
108 volts  
17/6

THE BATTERY COMPANY,  
92, Hurst Street, Birmingham.



THE  
BETTER  
BATTERY

## STARTLING REDUCTION IN WIRELESS VALVES

BEST BRITISH MADE VALVES FOR 3/6 OLD PRICE 8/6

L.F., H.F., R.C., AND DETECTOR IN 2 and 4 VOLTS. P.R. SUPER VALVES are the latest product of one of the finest equipped Wireless Research Factories in Great Britain. They must not be confused with Bankrupt or Foreign stocks of old and rubbishy valves. The P.R. SUPER VALVE FILLS EVERY WIRELESS NEED, and has enormous TONAL STRENGTH, PURITY, and SELECTIVITY.

Type	Fil. Vts.	Fil. Amp.	Imp. Ohms.	Amp. Fac.	M/C	
PR 1	2	0.05	35,000	15	4	H.F.
PR 2	2	0.06	25,000	12	4.3	Det.
PR 3	2	0.06	18,000	8	4.4	L.F.
PR 4	2	0.06	120,000	40	3.3	R.C. MATCHED
PR 5	2	0.15	40,000	20	5	H.F. VALVES for the intermediate stages
PR 6	2	0.15	30,000	15	5	Det.
PR 7	2	0.15	12,000	6	5	L.F.
PR 8	4	0.06	23,000	15	6.5	H.F. of Super-
PR 9	4	0.06	19,000	9.5	5	hets specially selected for 1/- per set ex.
PR10	4	0.06	11,000	6	5.5	L.F.
PR11	4	0.06	120,000	40	3.3	R.C.
Power Valves	2V.	0.20	6,000	5	8.2	P.
	4V.	0.15	4,000	4	10	P.

Tell us what your circuit is. We can help you select the right valves. H.F. MATCHED VALVES for the intermediate stages of Super-hets specially selected for 1/- per set ex.

P.R. VALVES Dept. 35 (Opp. Post Office Tube) 17, PATERNOSTER SQ., Newgate St., London, E.C.4

"TROMBA" 72 volt, 15/2. THE WET H.T. Components supplied. NO EXTRAS, CARR. PAID. Postage extra. All Voltages stocked. Send 1d. stamp for booklet; 6d. a cell; or 1/- for full range of samples. TROMBA ELECTRICAL CO. (Dept. W.), 13, High Rd., Kilburn, N.W.8. Phone: Maiden Lane 1669

### REPAIRS

Any make of L.F. Transformer, Loudspeaker or headphones repaired and despatched within 48 HOURS—TWELVE MONTHS' GUARANTEE with each repair. 4/- Post free.

Terms to Trade.

TRANSFORMER REPAIR CO., "Repairs" Dept.

214, High Street, Colliers Wood, London, S.W.19.



'Phone-order: City 3788. Pay the Postman C.O.D.

Sets of Valves made up to any requirements.

NOW ONLY  
3/6

Post 4d.

2 Valves for 6/3 Post 6d.  
3 Valves for 10/- Post 6d.  
4 Valves for 13/- Post 9d.

All valves despatched by return of post under guarantee of Money back in Full if not satisfied. All valves are carefully packed and breakages replaced. Callers invited.

TRADERS GET YOUR COM- CABINETS AT THE RIGHT PRICES. Send for illustrated list. Dept. P.W., PERSEUS RADIO, Burton-on-Trent

EVERYTHING RADIO ON

EASY TERMS  
WOOLDRIDGE RADIO CO. LIMITED. 72-74 LILIE STREET. LEICESTER SQ. LONDON, W.C.

ALL APPLICATIONS FOR ADVERTISING SPACE IN "POPULAR WIRELESS" MUST BE MADE TO THE SOLE ADVERTISING AGENTS. JOHN H. LILE, LTD., 4, LUDGATE CIRCUS, LONDON, E.C.4.



## THE ROLLS-ROYCE OF RADIO IS THE

### DIX-ONEMETER

THE HIGH GRADE RADIO TESTER.

Low price. High Value. Worth £10.

INSTRUMENT, 55/- MULTIPLIERS, 6/6 each.  
Radio Test Booklet. All Radio Users need one.



The ACONEMETER. Model VAC.3. In Case.  
Is a new Model measuring Alternating Current,  
a 3-range instrument reading 0-150 v., 0-300 v.,  
and 0-600 v. Price, inclusive of case, 75/-.  
1,500 volt Multipliers, 44/- extra.

Capacity Meters, £8. Wheatstone Recorders, £12.  
Multi-Micro Galvos, 60/- Res. Boxes, 17/6.  
Hydrometers, 1/6. Relays, 6/6, and Remote  
Switches, 15/-. Transmitting Sets and Wave-  
meters, from £2. Loewe Triple Valves, 38/-.  
Cabinet Violina Speakers, 25/. Hear Easy Phone  
Pads, 3d. pair. Skinner Micro Buttons, 2/-.

GRAMO PICK-UPS. Magnetic Earpiece Units for  
making your own 40/- reproducer. Adapted with  
a little work, 1/2 each. Sullivan's are the smallest  
and have aluminium case, 1/6 each. Adapted  
Brown A Pick-ups, 17/6. Electradix 25/- Complete  
outfit, £5 10s.


TABLE ELECTRIC PROJECTORS. For Photo  
Slide or Home Television experiments. 4 Magnif.  
and focus lenses, swivel stand. Socket cord and  
plug for supply mains or battery. Sale 25/- Gun  
Telescopes, as used on Warships. 21 x 24 in. long,  
12/6, 15/-, & 17/6, in case. Selenium Cells, 10/-.  
A.C./D.C. Chargers for 2, 4 or 6 volt Batteries up  
to 6 amp. at half List Price, 50/-.

Get our New 72-Page Catalogue.

**ELECTRADIX RADIOS,**  
218, Upper Thames St., E.C.4

St. Paul's and Blackfriars Stations. Phone City 0191

## FREE A.0005 LOGARITH- MIC CONDENSER.

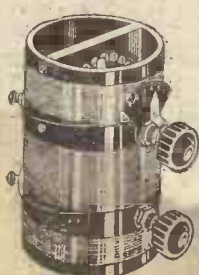

To all purchasers of our  
"All-Wave" Ebonite  
Tuner, wave-length 180-  
2,000 metres. Combines  
a six-point switch with a  
variable reaction wound  
with silk-covered wire,  
brass parts nickel-plated,  
size 4 1/2 x 3 1/2, two-hole  
fixing. The smallest,  
neatest and most efficient  
tuner on the market.  
Satisfaction guaranteed or  
money returned. Price  
only 15/-, post free. Cash  
with order, or C.O.D. Send  
now direct to the maker:-

S. W. SCOTT, 57, Camberwell New Road,  
LONDON, S.E.5.

ALL APPLICATIONS for ADVERTISING SPACE  
in "POPULAR WIRELESS" must be made to the  
Sole Advertising Agents, JOHN H. LILE, LTD.,  
4 LUDGATE CIRCUS LONDON, E.C.4. ::

## TECHNICAL NOTES.

(Continued from page 178.)

### Aerial Overhaul.

After a receiver has been in operation for some time it will generally be found that reception can be much improved by overhauling the aerial system. This is specially true in the winter when, owing to the usually damp conditions and the prevalence of fogs, the insulators are liable to be covered with a more or less conducting film of soot and other dirt. In most cases, it will be found that merely wiping the insulators with a dry cloth will bring about a noticeable improvement in reception. Various cleaners may be used for the insulators, the commonly recommended ones being alcohol (methylated spirit), benzene, and carbon tetra-chloride (separately, of course—not mixed together). When the aerial is lowered for the cleaning of the insulators, the aerial wire itself should be carefully examined to make sure that it has not become rotten at any part, otherwise there may be a breakage when it is again hoisted, and it may be inconvenient to get certain parts down again. Most listeners are apt to neglect their aerials, imagining that once installed an aerial should last and function efficiently for ever. As a matter of fact, the aerial ought to have more attention than some of the other parts of the set, as it is exposed to all kinds of destructive influences. An aerial overhaul is a job which is commonly shirked and put off till some other day, but as a matter of fact, it is well worth while, not only for the improvement in the loudness of local stations which may thereby be obtained, but for the great increase in sensitivity if you go in for distant reception.

### Winding Wire.

Talking about wire, you know how annoying it is when winding a coil, or one of the windings of a transformer, to come across an awkward joint in the wire which upsets the evenness of the layers (in the case of a transformer winding) and leaves you with a horrible suspicion that the covering may be chafed and that trouble may be in store.

It would certainly be a great advantage to be able to obtain an absolutely continuous length on a reel without any joint and also, in the case of enamelled wire, to be sure that the enamel was really pliable and not liable to crack.

The "KEW" enamel copper wire made by Kent Bros. Electric Wire Company and E. H. Phillips, Ltd., is guaranteed to be in continuous lengths per reel without any joints and the copper wire to be absolutely dead-to-gauge.

The enamel covering is claimed to be entirely free from liability to crack or peel and the thickness of the covering does not vary throughout the entire length of a reel of wire. Moreover—and this is a very important point—the enamel covering is free from pinholes: you will appreciate the value of this when using enamel wire for fairly high voltages.

### A Useful Dodge.

A reader in the Isle of Wight, referring to my recent note about holding short lengths of busbar by means of a pair of pliers, has kindly sent me a draughtsman's ruling pen which he says he finds very

useful in place of the pliers. When you want to solder a short piece of busbar in position in some more or less inaccessible place, you simply insert the length of wire at a suitable angle in the jaws of the draughtsman's pen, tightening up the screw and then holding in position whilst the soldering is done.

My correspondent states that the idea is not new, but that he has himself found it very useful. As a matter of fact, I believe I mentioned this idea in this journal some considerable time ago, and I know that the dodge is one which is often used by experimenters and constructors. At the same time I am, of course, very much obliged to my correspondent for his letter and to all the numerous readers who, from week to week, send me useful suggestions. In fact, many of the most useful ideas which I am able to pass on this way come originally from readers who are kind enough to write and send them to me.

### Sound and Sight.

One of the most remarkable things about radio is the immense stimulus which it has given to developments in all kinds of related sciences. I am thinking particularly, at the moment, of the developments in the recording of sound by means of light and the simultaneous reproduction of cinematograph pictures and sound.

The recording of the sound is done by means of a "light" process on a part of the film and the reproduction is effected by means of a beam of light projected through the film and varying in intensity as the different parts of the film pass through the machine. The light, of course, falls upon a photo-electric device by means of which variations in an electric current are set up these being amplified in the usual way.

**PANELS**

7x 6, 1/3	9x 6, 1/7
8x 6, 1/4	11x 8, 2/3
10x 8, 2/1	12x 8, 2/6
10x 9, 2/4	12x 9, 2/13
12x 10, 3/2	14x 10, 3/5
14x 12, 4/1	16x 9, 3/6
14x 7, 2/7	21x 7, 3/7
16x 8, 3/2	24x 7, 4/1
8x 5, 1/2	Post Free.

**RADIO**

Money back guarantee that each and all Panels are free from surface leakage. Megger test infinity. CROSSONIA CO., 10, South St., Moorgate, E.C.2

Phone: Clerkenwell 7853  
Agents: John Henry Smith, 139, Anlaby Rd., Hull.  
L. H. Helyar, 82, Chamberlin Rd., Norwich.  
A. Stredwick & Co., 27, The Market, Chatham.  
Boynton & Co. Ltd., 34, Bradford St., Birmingham

**HEADPHONES REPAIRED 4/-**  
Transformers 5/-. Loudspeakers 4/-. All repairs remanufactured free. Tested, guaranteed and ready for delivery in 24 hours.  
Discount for Trade. Clerkenwell 1795.  
MASON & CO., 44, East Rd., City Rd., N.1.

**D-XELLENT!**

**DX IN PLUG-IN COILS**

From No. 25 1/- to No. 500 4/-

**DX SHORT-WAVE SET**  
4 Coils Nos. 3, 5, 7, 9 .. 7/6

"P.W." Test Report, March 10:—"The fact that one of the first stations tuned in was 3 L O of Australia is ample proof that the coils are efficient."

If unable to obtain send P.O. 7/6.

**DX COILS LTD LONDON E8**



# The MASTER VALVE



The valve with the wonderful Mullard P.M. Filament, which is so essential to consistent service, length of life and purity of radio reproduction.

You buy Master products when you buy Mullard P.M. Valves.

*Obtainable from all Radio Dealers.*

# Mullard

**THE MASTER VALVE**

# New Eliminator Components



## SMOOTHING CHOKE.

The problem of producing efficient smoothing chokes to carry a heavy load without an appreciable fall of inductance has occupied the close attention of our Research Department for some considerable time. We have now solved this problem to an extent hitherto even unapproached. The new Smoothing Chokes which we have just marketed can carry the enormous current of 100 milliamperes without saturation, whilst the size, and therefore the price, has been kept within reasonable limits.

The extensive use of high power output valves calls for an eliminator capable of dealing with the necessary heavy anode current. Such current needs to be adequately smoothed, and the public have now available for the first time smoothing chokes which fulfil the necessary requirements, and which, owing to the special manner in which they are made, are procurable at a very reasonable price.

Price 21/-



## SUPER POWER RESISTANCE.

The series resistance method of adjusting the voltage in eliminators has proved so popular that we have specially designed a new form of resistance for this particular purpose.

These resistances are able to carry a heavy anode current without overheating, special care having been taken in their design to deal adequately with any slight heat generated.

There are many other uses for these super power resistances which will appeal to the discerning amateur and professional radio engineer.

These resistances are made up as follows: 500 ohms to carry 50 milliamperes; 1,000, 1,500, 2,000, 2,500 and 3,000 ohms each to carry 30 milliamperes.

Price 12/9 each.



## THE MARK OF BETTER RADIO

Kingsway House, 103, Kingsway, London, W.C.2

Telephone: Holborn 5303.