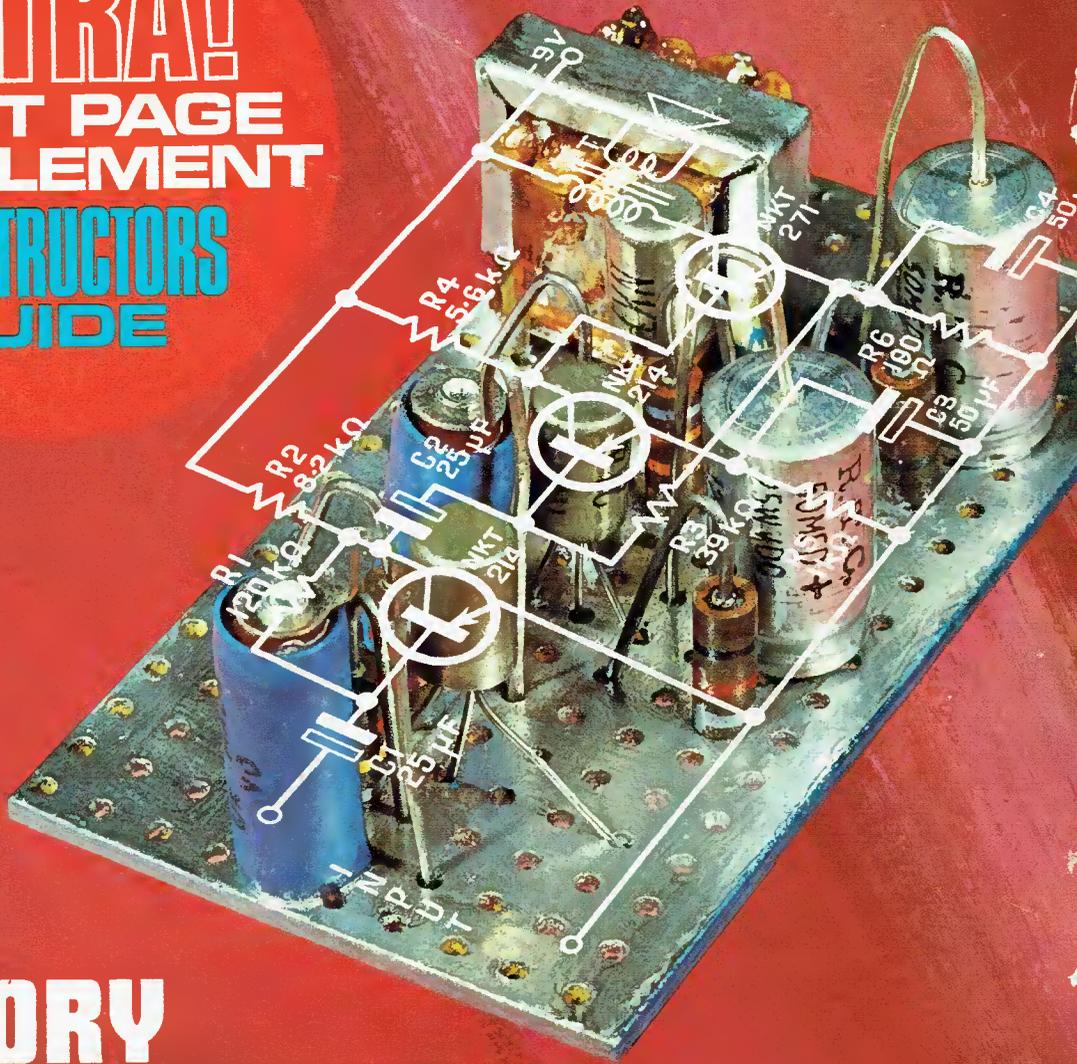


PRACTICAL ELECTRONICS

APRIL 1969

THREE SHILLINGS

EXTRA!
EIGHT PAGE
SUPPLEMENT
**CONSTRUCTORS
GUIDE**



**THEORY
into PRACTICE**

ALSO


New Design- **MICROPHONE MIXER**



ADCOLA

PRODUCTS LIMITED
(Regd Trade Mark)

Soldering Instruments

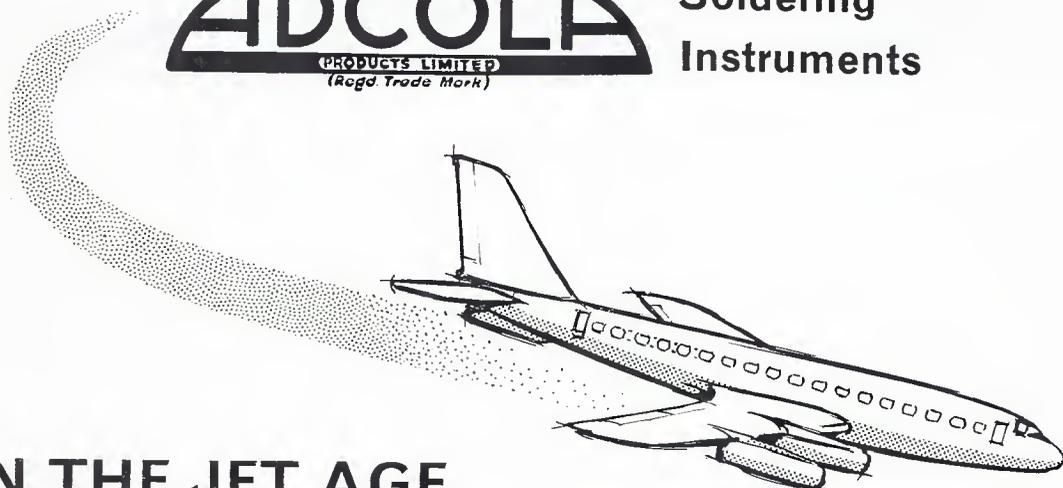

IN THE JET AGE

**EFFICIENCY AND RELIABILITY,
AND CONSISTANT, SUSTAINED PERFORMANCE
ARE BASIC REQUIREMENTS.**

**ADCOLA SOLDERING INSTRUMENTS MEET THESE NEEDS
AND GO ON MEETING THEM, DAY AFTER DAY, YEAR AFTER YEAR,
WITH UNFAILING REGULARITY.**

**LEADING MANUFACTURERS THROUGHOUT THE WORLD LIKE THIS,
THEY ALSO LIKE THE QUICK SERVICE WHEN REPLACEMENTS
DO BECOME NECESSARY. SO THEY SPECIFY ADCOLA.**

WHY DON'T YOU!

**AVAILABLE FROM SHOPS EVERYWHERE
OR DIRECT FROM**

**SALES & SERVICE DIVISION,
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4.**

TELEPHONE 01-622 0291

**SEND COUPON
FOR LATEST LEAFLET**

NAME	_____
ADDRESS	_____

P.E.167	

Lasky's Radio

LASKY'S RADIO ESTABLISHED OVER
36
YEARS

TCC G-1120

HEADPHONE/BOOM MICROPHONE SET

This lightweight headphone and boom microphone assembly is especially suitable for TV camera crews, communications equipment, language labs, recording studios, etc. The fully adjustable headset is extremely comfortable to wear for long periods. Low impedance microphone allows long cables to be used without any signal loss. Used with a Tape Recorder this assembly will provide constant monitoring. High quality specification and superb finish at a price you can afford.

Headset spec.: Dynamic impedance 16 ohms. Frequency res. 20-14-1000Hz. Input 200mV. Cord length 69in with jack plug fitted. Mic. spec.: Impedance dynamic 200 ohms. Frequency res. 200-8000Hz, sensitivity 75dB. Cord length 69in complete with jack plug.



LASKY'S PRICE **£6.5.0**

Post 2/6

FANTAVOX 500

12 WATT STEREO AMPLIFIER


This outstanding amplifier incorporates all the features expected of an expensive unit but at a budget price. The amplifier has separate tone and volume controls for both channels plus stereo mono switch and tuner output socket. Finished in an attractive walnut grained metal cabinet with anodised pale gold metal front panel. Brief spec: 12 transistors, 2 silicon diodes. Output, Peak power 12 watts (6 watts per channel). Freq. Response: 40-20,000 Hz, Output impedance 4-16 ohms. Input sensitivity. Phono/Tuner 250mV. Size: 9½ x 3½ x 6½in.



LASKY'S PRICE **£12.10.0**

Post 6/-

SPECIALIST RELAYS

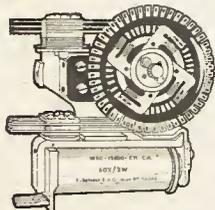

SCHRACK 4 POLE 12 WAY

This stepping relay inches one step per pulse of the coil, contacts are provided for continuous stepping and 2 pole changeover at position "6". Uses include programming Christmas tree lights, selection of stations on multiway intercom systems (using standard 2 way intercoms), Servo steering of radio control models. Automatic operation of model railways, etc.


Type RT 318900 60V - 2W coil OR Type RT 318120 12V - 2W coil

LASKY'S PRICE **59/6** each

Post 2/6

NEW TTC Model A-1008 BUDGET FM TUNER

For size, quality and price we feel sure the Model A-1008 FM Tuner is unbeatable. Probably the world's most compact FM tuner with 6 transistor and 3 diode printed circuit, self powered—operating from any 9V D.C. source. Slow motion tuning drive. Housed in beautifully finished walnut cabinet with classic silver trim. Clear horizontal tuning scale covering the entire FM band 38-108 Mc/s. Complete with FM aerial. Brief Spec: aerial imp. 75 ohms. Sensitivity better than 10uV (at 100% modulation for 20dB S/W). Size 7½ x 5 x 3½in.

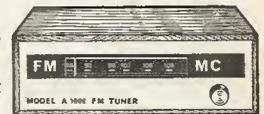

LASKY'S PRICE **£9.19.6**

Post 3/6

ADD MULTIPLEX TO THE MODEL A-1008

You can enjoy stereo sound with the Model A-1008 FM Tuner above by adding the TTC Model A-1005M Multiplex Adaptor. Brief Specification: MPX input sensitivity 100mV. Output 150mV. Self powered by a 9V battery. 4 transistor and 6 diode circuit. Size 5½ x 2 x 4½in. Also suitable for use with other FM tuners with MPX input.

LASKY'S PRICE **99/6**

Post 3/6

NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE at RECORD LOW PRICES

3in. Message tape, 150ft.	2 6	5½in. Standard play, 850ft. PVC . . .	11 6
3in. Message tape, 225ft.	3 8	5½in. Long play, 1200ft. Mylar . . .	15 0
3in. Message tape, 300ft.	7 6	5½in. Triple play, 2400ft. Mylar . . .	45 0
3½in. Triple play, 600ft. Mylar . . .	0 7	7in. Standard play, 1200ft. Acetate . . .	12 6
5in. Double play, 1200ft. Mylar . . .	15 0	7in. Standard play, 1200ft. Mylar . . .	12 6
5in. Long play, 900ft. Acetate . . .	10 0	7in. Long play, 1800ft. Mylar . . .	19 6
5in. Standard play, 600ft. PVC . . .	8 6	7in. Double play, 2400ft. Mylar . . .	25 0
5in. Triple play, 1800ft. Mylar . . .	35 0	7in. Long play, 1800ft. Acetate . . .	15 0
5½in. Double play, 1800ft. Mylar . . .	22 6	7in. Triple play, 3600ft. Mylar . . .	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free. Special quotes for quantities.

BUDGET PRICED CASSETTES

OVERTURE High quality cassettes from the U.S.A. C.60—10/6 C.90—15/- C.120—20/-

Post 1/- each. 4 and over Post Free. Special quotes for quantities.

THORN PYGMY PLUG-IN RELAY



A miniature 9 pin plug-in relay with 10A double changeover configuration. Mains operated coil switched for internal powered remote mains switching, using one contact as a latch to hold the relay in until the external circuit is broken. Coil resistance 82K/ohms, 200-240V AC/DC operation.

LASKY'S PRICE **12/6**

Post 2/6

AEI MINIATURE RELAY



A miniature shrouded 3 pole "make" relay of the chassis mounting type. DC coil resistance 900Ω 24V operation. Useful for remote Audio switching circuits, control systems, using low voltage and current, controlling small D.C. motors and pilot lights, etc., and any application switching three circuits from one switch.

LASKY'S PRICE **8/6**

Post 1/6

AD-76K MOVING MAGNET CARTRIDGE

New high compliance moving magnet stereo cartridge that really breaks the quality/price barrier. SPECIFICATION: Diamond Stereo LP stylus. Compliance 10 x 10⁻⁶cm/dyne. Frequency response 20-20,000c/s. Channel separation 20dB. Output 5mV. Tracking pressure 2 grammes. Standard ¾in mounting. Replacement Diamond stylus available. Fully guaranteed.

LASKY'S PRICE **90/-**

Post 2/-

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271

Open all day, 9 a.m.—6 p.m. Monday to Saturday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573


Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

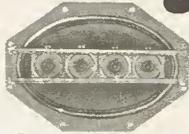How do you measure the extra quality of EMI speakers?



Listen!



EMISOUND

EMI are famous throughout the world for High Quality sound reproduction. Now our audio design engineers have developed loudspeaker systems suitable for home use.

These EMI Loudspeaker Systems, specially matched, produce every detail of the original sound over the full audio spectrum, at high and low listening levels.

They have many exclusive features. The range includes the unique 950 system with a 19 inches x 14 inches bass unit, power output 50 watts R.M.S.

Send for literature and price lists to:



EMI SOUND PRODUCTS LTD., HAYES, MIDD. TEL: 01-573-3888 EXT. 667

SEMICONDUCTORS BRAND NEW AND FULLY GUARANTEED

IN914	1/6	2N2696	6/6	AD161	7/6	BFV57	7/6	BYZ10	9/-
IN916	1/6	2N2904	8/-	AD162	7/6	BFV58	7/6	BYZ11	7/6
IS010	3/-	2N2904A	8/-	AF114	5/-	BFV59	6/6	BYZ12	6/-
IS020	3/6	2N2905	8/-	AF116	5/-	BFV60	6/6	BYZ13	5/-
IS021	4/-	2N2906	8/-	AF117	5/-	BFV61	5/6	GET103	5/-
IS025	5/-	2N2906	8/-	AF118	12/6	BFX12	5/6	MPF102	4/-
IS113	3/-	2N2906A	8/-	AF124	5/-	BFX29	12/6	MPF106	8/6
IS120	2/6	2N2907	8/-	AF127	5/-	BFX30	15/-	MPF103	7/6
IS121	2/6	2N2907A	8/-	AF181	6/6	BFX35	19/6	MPF104	7/6
IS130	2/6	2N2923	5/-	AF186	11/-	BFX43	8/6	MPF105	8/-
IS131	2/6	2N2924	5/-	AF199	5/6	BFX68	13/6	NKT117	10/6
IS132	2/6	2N2925	5/6	AFZ12	5/6	BFX92A	12/6	NKT121	8/6
IS44	2/-	2N2926	6/6	ASY26	4/6	BFX84	8/-	NKT261	4/6
2G301	4/-	Green	3/6	ASY27	8/6	BFX85	10/-	NKT262	4/6
2G302	4/-	Yellow	3/3	ASY28	6/6	BFX86	8/-	NKT264	4/6
2G303	4/-	Orange	3/-	ASY29	4/6	BFX87	10/-	NKT271	4/6
2G371	3/-	Brown	2/6	AXZ21	4/6	BFX88	5/-	NKT272	4/6
2N696	5/-	2N3005	15/-	BAX16	2/9	BFX93A	15/-	NKT274	4/6
2N697	5/-	2N3011	5/-	BAY31	2/6	BFY10	4/6	NKT281	5/6
2N698	4/6	2N3053	6/6	BAY38	3/6	BFY11	4/6	NKT403	15/-
2N706	3/-	2N3055	15/-	BC107	3/6	BFY17	4/6	NKT405	15/-
2N706A	4/-	2N3077	19/6	BC108	3/6	BFY18	4/6	NKT613	6/6
2N708	4/-	2N3078	4/-	BC109	3/6	BFY19	3/6	NKT674	5/6
2N929	5/6	2N3702	4/6	BC113	6/6	BFY41	10/-	NKT677	5/6
2N930	6/6	2N3703	4/6	BC118	6/6	BFY43	13/6	NKT713	5/6
2NI090	6/6	2N3704	5/6	BC125	13/6	BFY50	4/6	NKT781	6/-
2NI091	6/6	2N3705	4/6	BC147	5/-	BFY51	4/6	NKT8011	15/6
2NI131	9/6	2N3706	4/6	BC148	4/6	BFY52	4/6	NKT8012	19/6
2NI132	9/6	2N3707	4/6	BC149	4/6	BFY56A	11/6	NKT8013	22/6
2NI302	4/6	2N3708	4/6	BC182	4/6	BFY76	9/6	OAS	2/6
2NI303	4/6	2N3709	4/6	BC184	4/6	BFY77	11/6	OAS	2/6
2NI304	5/6	2N3710	4/6	BC184	4/6	BSX19	12/6	OAS	2/6
2NI305	5/6	2N3711	4/6	BCY30	7/6	BSX20	5/6	OAS	2/6
2NI306	6/6	2N3819	9/-	BCY31	4/6	BSX21	8/-	OAS	2/6
2NI307	6/6	2N3820	13/6	BCY32	6/6	BSX22	10/6	OAS	2/6
2NI308	8/-	2N3821	17/6	BCY33	5/6	BSX23	10/6	OAS	2/6
2NI309	8/-	2N4058	6/6	BCY34	4/6	BSX24	10/6	OAS	2/6
2NI507	5/6	2N4059	5/-	BCY38	5/6	BSX25	10/6	OAS	2/6
2NI613	6/6	2N4060	5/-	BCY39	6/6	BSX26	10/6	OAS	2/6
2NI771	6/6	2N4061	5/-	BCY40	6/6	BSX27	10/6	OAS	2/6
2NI889	8/-	2N4254	6/6	BCY42	5/-	BSX28	8/6	OAS	2/6
2NI893	8/-	2N4254	6/6	BCY43	6/6	BSX29	10/6	OAS	2/6
2NI102	13/6	2N4255	8/6	BCY43	6/6	BSX30	10/6	OAS	2/6
2NI147	17/6	AAZ13	2/-	BCY54	7/6	BSX31	12/6	OAS	2/6
2NI2148	12/6	AAZ15	3/6	BCY70	5/6	BSX32	8/6	OAS	2/6
2NI2160	14/6	AAZ17	3/6	BCY71	9/6	BSX33	8/6	OAS	2/6
2NI2193	5/6	AC107	8/6	BCY72	5/6	BSX34	8/6	OAS	2/6
2NI2193A	5/6	AC126	4/6	BCY10	4/6	BSX35	5/6	OAS	2/6
2NI2194A	5/6	AC127	3/-	BCZ11	4/6	BSY26	4/6	OAS	2/6
2NI2217	9/6	AC128	4/6	BD121	19/6	BSY27	4/6	OAS	2/6
2NI2218	10/6	AC176	5/6	BD123	23/6	BSY28	4/6	OAS	2/6
2NI2219	10/6	AC187	12/-	BD124	12/-	BSY29	4/6	OAS	2/6
2NI2220	5/-	AC198	12/-	BF115	4/6	BSY38	4/6	OAS	2/6
2NI2221	5/-	ACY17	5/6	BF117	10/6	BSY39	4/6	OAS	2/6
2NI2221	5/-	ACY18	5/6	BF167	6/6	BSY40	5/6	OAS	2/6
2NI2722	5/-	ACY19	5/6	BF173	7/6	BSY51	10/6	OAS	2/6
2NI2368	6/6	ACY20	4/6	BF180	8/6	BSY52	10/6	OAS	2/6
2NI2369	7/6	ACY21	5/6	BF181	8/6	BSY53	9/6	OAS	2/6
2NI2369A	5/6	ACY22	4/6	BF224	6/6	BSY54	10/6	OAS	2/6
2NI2539	4/6	ACY28	4/6	BF225	6/6	BSY95A	3/6	OAS	2/6
2NI2540	4/6	AD140	8/-	BF237	6/6	BY100	4/6	OAS	2/6
2NI2646	11/6	AD149	8/-	BF238	6/6	BYX10	5/6	OAS	2/6

THYRISTORS

1 AMP: 50V 8/-, 100V 5/6, 200V 7/-, 400V 9/6.
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/-.
Equivalent BYT 9/100R 15/- each
ZENERS. 1 1/2 WATT 2.7-33V 4/6
1/2 WATT 2.0-16V 3/-

RECORDING

TAPES

Fully Guaranteed

7" STD	1,200'	7/3
7" L/P	1,800'	12/3
7" D/P	2,400'	19/6
5 1/2" STD	900'	6/6
5 1/2" L/P	1,200'	9/-
5 1/2" D/P	1,800'	14/9
5" STD	600'	5/3
5" L/P	900'	7/3
5" D/P	1,200'	10/9
3" D/P	185'	2/3
3" L/P	225'	3/-
3" D/P	300'	4/-

7" D/P Concorde	1	18	1/6	16	450	3/3	100	15	1/6		
Spools:	3,000'	33/6	1	40	1/9	25	6.4	1/6	100	25	1/6
2/6, 5 1/2"	6/3, 7"	2	15	1/6	25	10	1/6	100	50	2/6	
4" 2 1/2", 3 1/2"	2/3, 5" 2/3,	2.5	16	1/9	25	5	1/6	125	4	1/6	
2 1/4" 1/10.	1/9, 3" 9d,	4	15	1/6	32	15	1/6	250	25	2/9	
		4	40	4/9	32	40	1/6	250	50	3/9	
		4	350	2/3	32	450	1/6	320	10	1/6	
		6.4	15	1/6	40	6.4	1/6	400	16	2/9	
		8	18	1/6	50	12	1/6	500	6	2/6	
		8	40	1/6	50	15	1/6	500	50	4/9	
		8	450	3/6	50	25	1/6	640	16	3/6	
		10	15	1/6	50	50	2/-	1000	12	3/9	
		10	25	1/6	64	25	1/6	1000	16	4/9	
		12.5	25	1/9	80	6.4	1/6	1000	25	5/9	
		16	10	1/9	80	16	1/6	1000	50	9/9	
		16	18	1/6	100	12	1/6				

CASSETTE TAPES

C-60 13/6, C-90 18/6

Post and Packing up to 3 reels 2/9, otherwise 4/6.

SPEAKERS (3 ohm)

10" x 6"	37/6,
9" x 4"	23/6,
7" x 5"	19/6,
7" x 4"	15/6,
5" x 3"	12/6,
3" 9/6, 5"	14/6,
8" 27/6, 12"	39/6.

Post and Packing 1/6

INTEGRATED CIRCUITS

R.C.A.				
CA3005, 3013, 3014, 3018	30/-			
CA3019, 3020	27/6			
CA3011, 3036	20/-			
CA3021, 42/6	CA3023	32/6	CA3012	25/-
FAIRCHILD				
L900, 914	11/-	L923	14/-	
DATA SHEETS FOR RCA DEVICES	2/- per type			

Presets std., horiz. or vert.

Potentiometers, Log/Lin

MFD V Price MFD V Price MFD V Price

1	18	1/6	16	450	3/3	100	15	1/6
1	40	1/9	25	6.4	1/6	100	25	1/6
2	15	1/6	25	10	1/6	100	50	2/6
2.5	16	1/9	25	5	1/6	125	4	1/6
4	15	1/6	32	15	1/6	250	25	2/9
4	40	4/9	32	40	1/6	250	50	3/9
4	350	2/3	32	450	1/6	320	10	1/6
6.4	15	1/6	40	6.4	1/6	400	16	2/9
8	18	1/6	50	12	1/6	500	6	2/6
8	40	1/6	50	15	1/6	500	50	4/9
8	450	3/6	50	25	1/6	640	16	3/6
10	15	1/6	50	50	2/-	1000	12	3/9
10	25	1/6	64	25	1/6	1000	16	4/9
12.5	25	1/9	80	6.4	1/6	1000	25	5/9
16	10	1/9	80	16	1/6	1000	50	9/9
16	18	1/6	100	12	1/6			

VEROBOARD

3 1/2" x 2 1/2" 3/6
3 1/2" x 3 1/2" 4/3
Cutter 9/-
3 1/2" x 5" 5/6
17" x 3 1/2" 16/-
5" x 2 1/2" 4/3

RESISTORS

1/2 watt 10%, 4d.
1/2 watt 5%, 8d.
1/2 and 1 watt, 6d.
3 watt, 1/6
5 watt 2/-

SEND 6d. STAMP FOR CATALOGUE

P.P. for Components 1/6 per order

A. MARSHALL & SON

28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

01-452 0161/2/3 CALLERS WELCOME


Sinclair

Z.12 - for all you want from any amplifier

The Z.12 is a most versatile integrated amplifier and pre-amp in which power, compactness and true high-fidelity standards are combined within a unit of very modest price. The most widely used unit of its kind in the world, the Z.12 has an output of 12W R.M.S. continuous sine wave (24W peak) or 15W music power (30W. speak). It has Class B ultralinear output which can be fed into any loud-speaker from 3 to 15 ohms. (Two 3 ohm speakers can be used in parallel.) Frequency response—15 to 50,000Hz, ±1dB; input sensitivity—2mV into 2 K/ohms. The Z.12 will operate from any power source between 6 and 20V d.c. As such,

a car battery or the PZ.4 are eminently suitable, giving much wider than usual scope in the applications to which the Z.12 may be put. As well as hi-fi, these include systems for P.A., electronic guitars, organs, intercom systems, laboratory, education or industry. You will find the Z.12 in use in such instances again and again. The Sinclair Z.12 is supplied ready built, tested and guaranteed, complete with manual of circuits and instructions for matching it to your precise requirements. Two may be used in stereo when, with the Stereo 25 and PZ.4 together with two Q.14s, you will have an ideal high fidelity assembly.

89/6

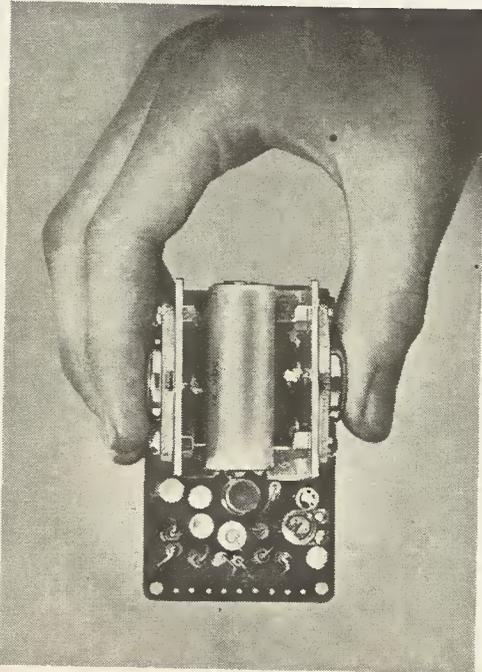


Q.14 - the unique loudspeaker

New materials and original design techniques have been used to produce speaker of fantastic quality at a most attractive price. Experts and reviewers have enthusiastically endorsed its performance. The shape and size of the Q.14 make it far more adaptable to its environment than is the case with conventionally styled speakers so that it is much easier to position this speaker in the room in which it is to be heard. The Sinclair Q.14 has a substantially flat frequency

response from 60 to 16,000Hz and outstandingly good transient response. It will comfortably handle up to 14W loading and is positively brilliant in stereo. Measuring 9 $\frac{1}{2}$ in square by 4 $\frac{1}{2}$ in deep, this loud-speaker is finished in matt black with solid aluminium bar trim. Try the Q.14 in your own home without delay. If you are not delighted with it, your money including cost of return postage to Sinclair will be refunded immediately.

£7.19.6

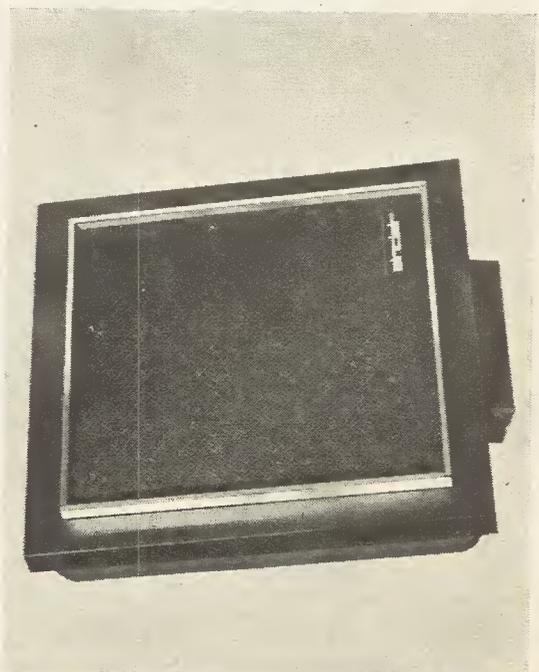

Stereo 25 de-luxe pre-amp/control unit

This is a very elegantly styled unit, which, although designed basically for use with the Z.12, is readily adaptable for use with any high quality power amplifier system. The switched input selector allows for Pick-up, Radio and Auxiliary and there are controls for bass cut and lift, treble cut and lift, volume and stereo balance. P.U. input is equalised to R.I.A.A. curve from 50 to 20,000Hz ± 1 dB and the

instructions manual provided gives matching details for pick-ups, shows how to connect up, etc. The front panel of the Stereo 25 is finished in brushed and polished aluminium embellished in black. The control knobs are in solid aluminium to match. Size $6\frac{1}{2} \times 2\frac{1}{4} \times 2\frac{1}{4}$ in plus knobs. Supplied built, tested and guaranteed.

£9.19.6

PZ.4 - stabilised power supply unit

Designed specially to meet the power requirements for an assembly of two Z.12s and the Stereo 25, this heavy duty transistorized power supply unit has stabilised output of 18V d.c. at up to 1.5A. It is for a.c. mains operation 200/250V.

99/6

Supplied built, tested and guaranteed.

SINCLAIR MICROMATIC

Whether you buy your Micromatic in kit form or built ready for use, you must not deny yourself the thrill of owning this fantastically small British receiver. Smaller than a matchbox, it has power, range and selectivity that must be experienced to be believed. The high quality magnetic earpiece supplied with the set ensures excellent reproduction indoors and out. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact you will find this set performing in some cases where other sets cannot be heard at all. The Micromatic is housed in a neat black case given an elegantly modern appearance by the attractive aluminium front panel and matching tuning control.

YOUR SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question.

FULL SERVICE FACILITIES AVAILABLE TO ALL PURCHASERS.

Goods sent post free in U.K. and overseas by surface mail. Air-freight charged at cost.

Kit in fitted pack with magnetic earpiece, instructions and free solder

49/6

Built, tested and guaranteed, inc. magnetic earpiece

59/6

Mallor Mercury Cell type RM.675 (2 required) 2/9 each

Please send **POST FREE**

NAME.....



ADDRESS.....

For which I enclose cash/cheque/
money order

PE.469

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

OCA3-52731

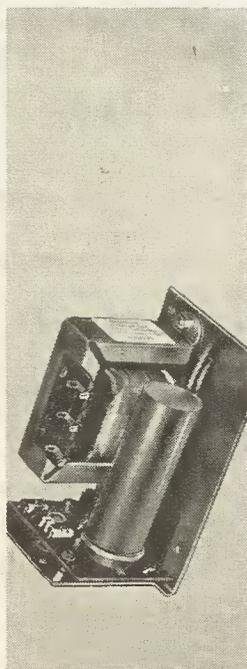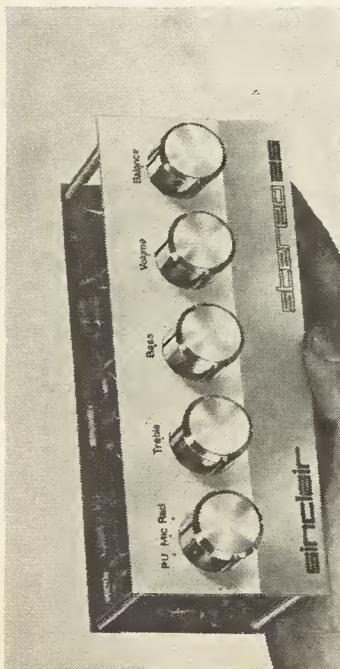

The world's smallest personal radio

Sinclair

Bargain—Car Radios. Our Price 9 gns. Negative or positive earth, (switched) fully transistorised (12V) medium and long waves. Speaker and fitting kit supplied at no extra cost. P/P 5/-.

Sonotone 9TA and 9TA/HC. Diamond Cartridge brand new, boxed in manufacturers' carton 49/6 plus 2/6 p/p. Acos GP 91-1 and GP 91-3 stereo compatible cartridges, new in sealed manufacturers' cartons 22/6 plus 2/6 p/p.

BASF TAPE 25% OFF

5in 600ft. 14/- 900ft. 19/- 1200ft. 30/-
5½in 900ft. 19/- 1200ft. 24/- 1800ft. 39/-
7in 1200ft. 24/- 1800ft. 35/- 2400ft. 57/-

P/P 2/- per reel—over £5 FREE

HI-FI SPEAKER

K12TC—12in 12 watt

Offers an exceptionally smooth and extended response, with very low level of distortion from the specially designed twin diaphragms.

Frequency Response: 30-16,000Hz.

Impedance: 15-160Hm

OUR SPECIAL PRICE 97/6

PLUS P/P 6/6

● **BARGAIN — Speakers, Hi-Fi —** The Baker Selhurst Stalwart. 12in round, 15 watt rating, 12,000 lines gauss, 15 ohms, response 45-13,000c/s. Bass resonance 40-50c/s, solid aluminium chassis. Our price £59.6. p/p 6/6

DULCI HI-FI UNITS

The Dulci range of tuners and amplifiers offer exceptional quality at a sensible price.

Amplifiers: 207 and 207M. **Tuners:** FMT7 and FMT7s.

SEND NOW FOR FULL DETAILS

TRIO Stereo Moving Magnet Cartridge Model AD76K. Diamond Stereo LP Stylus. Frequency response 20-20,000c/s output. 7mV tracking pressure 2 grammes ± 0.5 grm. Fully guaranteed. Price 85/- p/p free.

● **Bargain—Changer decks at lowest prices ever**

Beautiful teak and plinth and perspex cover to suit these units	GARRARD 1025	£8.00
Free	2025	£8.10.6
	AT60 Mk. 11	£12.19.6
	SP25 Mk. 11	£12.00
5 Gns. P/P		
	3500 with Son 9TA, HC diam. cart.	£10.19.6

Add 10/- p/p for each Garrard unit

SPEAKER ENCLOSURES

Type: INFINITE BAFFLE

Model 8: 8in plus 3in tweeter

Model 138: 13in × 8in EMI

Both £4.19.6 each

Model 1012: 10in or 12in, plus 4in tweeter


£7.19.6

All enclosures are in oiled teak, fully built.

Please add 8/- p/p on each enclosure

● **BARGAIN — Speakers, Hi-Fi —**

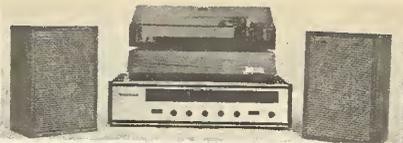The Baker Selhurst Guitar Group 25, 12in round, 25 watt rating, 12,000 gauss, 15 ohms, response 30-10,000c/s, solid aluminium chassis, heavy duty cone. Our price £59.6. p/p 6/6



The greatest Hi-Fi Budget system today — can't be beaten—price or quality anywhere — look at these great features—then compare.

Telefon F2000 tuner amp. AM-FM with multiplex decoder and A.F.C.—2 x 5W channels R.M.S. Bass Volume Treble Balance controls, a truly outstanding unit

£	s.	d.
43	1	0

Garrard SP 25 Mk II Transcription deck

15	11	11
----	----	----

Telefon SA 1003 matching speaker enclosures

9	5	0
---	---	---

Sonotone 9 TA Diamond Cartridge

4	2	0
---	---	---

Plinth and Perspex cover

7	0	0
---	---	---

£78 19 11

Exclusively offered by **WALDON** at the remarkably low price of **63 gns.**

E.M.I. HI-FI SPEAKERS

SET 450: 13 × 8 with two built-in tweeters and cross-over unit. Our Price 69/6. 3 or 15 ohm, 10W, 40-13,000Hz.

SET 850: 6½in bass plus 3½in tweeter and cross-over unit. 8 ohm, 10W, 65-20,000Hz. 79/6.

SET 250: 5in heavy duty bass plus 3in tweeter and cross-over unit. 8 ohm, 6W, 80-20,000Hz. 65/-

Add 5/6 p/p for each speaker set

WALDON ELECTRONICS, Atlas House, Chorley Old Rd., Bolton. Bolton 45628

YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful **NEW PICTORIAL METHOD**—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the **PICTORIAL APPROACH** to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT



The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"I am highly delighted with the books; I didn't know a complicated subject could be so easily presented."

J. K., Earlsfield.

"I am pleased to say how understandable your books are. I have now quite a sound knowledge of Electronics."

P. S., Southgate.

"I know your Manuals will prove invaluable for my training and career as a technician."

J. L., S. Shields.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me **WITHOUT OBLIGATION TO PURCHASE**, one of the above sets on **7 DAYS FREE TRIAL**, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY 75/-**. Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. **BASIC ELECTRONICS 90/-**. Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 20/- each. This offer applies to **UNITED KINGDOM ONLY**. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY

BASIC ELECTRONICS

Prices include Postage and Packing.

Signature

(If under 21 signature required of parent or guardian)

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS.....

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

L.S.T. ELECTRONIC COMPONENTS LTD.

1N914	2/-	25024	25/-	BF167	6/4	OA2246	3/6
1N113	3/-	25034	15/-	BF173	7/6	OA2269	3/6
1N120	2/4	AC126	14/6	BF180	7/6	OA2270	3/6
1N130	2/4	AC126	6/4	BF187	7/6	OA2271	3/4
1N131	2/4	AC127	6/4	BF195	7/6	OC19	5/-
1N132	2/4	AC128	6/4	BF200	7/6	OC20	5/-
2N301	4/-	AC176	7/6	BFV40	4/0	OC22	13/6
2N302	3/9	AC187	12/-	BFX13	4/8	OC23	15/6
2N339A	5/-	AC191	12/-	BFZ29	4/0	OC24	10/-
2G374	5/-	AC177	5/-	BFY50	4/0	OC35	6/8
2G38	5/-	AC178	3/4	BFY51	4/0	OC26	12/-
2G371	3/-	AC179	4/4	BFY52	4/0	OC28	12/-
2N385A	15/-	AC210	3/8	BFY53	4/0	OC29	15/-
2N496	6/-	AC222	2/4	BSX21	8/0	OC35	9/6
2N497	6/-	AD140	15/-	BSY27	4/0	OC36	13/6
2N498	4/4	AD149	11/8	BYX39/600	120/0	OC41	10/-
2N706	3/-	AD161	6/4	BSY95A	3/4	OC42	4/0
2N706A	6/4	AD162	6/4	BU111	15/0	OC44	3/0
2N708	4/0	AD170	12/6	BU100	5/0	OC45	3/0
2N711	7/6	AF102	18/0	BYX10	4/9	OC71	3/0
2N711A	7/6	AF114	9/4	BY210	9/0	OC73	4/6
2N929	5/4	AF115	4/4	BY212	6/0	OC73	3/0
2N930	6/4	AF116	4/4	BY213	5/0	OC75	5/0
2N1131	9/4	AF117	9/4	GET102	4/0	OC76	2/6
2N1132	7/6	AF118	16/6	GET103	4/6	OC77	8/8
2N1302	4/4	AF124	6/4	GET113	5/0	OC81D	3/0
2N1303	4/4	AF127	6/4	GET123	7/4	OC82	4/4
2N1304	3/4	AF139	15/0	GHO378B	6/0	OC83	3/0
2N1305	5/4	AF140	12/6	MAT100	5/0	OC83	4/4
2N1306	4/4	AF186	11/-	MAT101	5/4	OC84	4/4
2N1307	6/4	AF212	11/9	MAT120	5/1	OC123	7/0
2N1308	8/0	AF226	5/8	MAT100	5/4	OC139	2/0
2N1309	8/0	AS727	5/8	MPF102	9/0	OC140	12/0
2N1613	6/4	AS728	4/4	MPF103	9/0	OC169	4/0
2N2167	17/4	AS729	6/4	MPF104	9/4	OC170	6/0
2N2148	12/6	AS211	11/-	MPF105	9/0	OC171	6/0
2N2160	14/-	BA110	3/9	NKT216	10/0	OC200	6/0
2N2346	6/4	BAL15	2/8	NKT217	10/0	OC201	6/0
2N2369	6/4	BA130	3/0	NKT261	4/3	OC202	16/6
2N2369A	7/6	BA131	3/0	NKT262	4/3	OC203	16/6
2N2444	10/4	BA238	3/0	NKT264	4/3	OC204	16/6
2N2496	8/0	BC107	2/9	NKT271	4/3	OC205	8/0
2N2524	5/4	BC108	2/9	NKT272	4/3	OC206	16/6
2N2925	5/4	BC109	2/9	NKT274	4/3	OC207	7/4
2N2926	5/4	BC110	2/9	NKT275	4/3	OC207	7/4
Green	2/-	BC114	18/6	NKT276	2/6	ORP60	18/3
Yellow	2/-	BC115	13/6	NKT281	5/4	ORP61	8/0
Orange	2/-	BC118	5/4	NKT282	18/6	OC208	13/3
Red	2/-	BC125	14/0	NKT405	15/0	SX631	7/4
2N3053	8/0	BC126	14/0	NKT713	5/4	SX636	16/8
2N3054	15/0	BC134	5/4	NKT712	5/4	SX638	12/0
2N3055	15/0	BC147	6/4	NKT774	5/4	SZ20C	15/4
2N3702	4/0	BC148	4/0	OA447	3/8	SVCI	17/4
2N3703	4/0	BC149	4/0	OA447	3/8	SVCI	17/4
2N3704	4/0	BC154	12/0	OA70	1/4	P346A	9/3
2N3705	4/0	BC155	12/0	OA71	1/4	P346A	9/3
2N3706	3/0	BC131	9/0	OA79	1/4	EC901	9/0
2N3707	4/0	BC132	16/0	OA81	1/4	EC902	4/8
2N3708	4/0	BC133	16/0	OA82	1/4	EC911	9/0
2N3709	3/4	BC134	6/4	OA90	1/4	EC900	9/0
2N3710	3/4	BC135	3/0	OA91	1/4	EC911	45/9
2N3711	4/0	BC439	27/4	OA95	1/4	EA403	3/4
2N3819	8/0	BCY90	13/4	OA200	2/0	EA403	3/4
2N3820	22/6	BCY54	15/6	OA201	3/0	EA403	3/4
2N4058	7/0	BCY78	4/0	OA210	6/4	EA491	30/3
2N4059	6/4	BCY71	8/8	OA220	3/4	M1461	20/7
2N4060	6/4	BCY72	8/8	OA221	3/4	M1461	20/7
2N4061	6/4	BCY87	8/8	OA226	3/4	40362	16/3
2N4062	6/4	BCY88	8/8	OA227	3/4	ST140	3/0
2N4254	9/4	BD121	19/6	OA224	3/4	ST141	5/0
2N4255	8/4	BD122	17/4	OA223	3/4	OC243	6/0
25018	8/4	BF152	12/6	OA224	3/4	OC243	6/0

CHEAPEST EVER SOLID-STATE SALE

BEST VALUE IN BRITAIN

40 Silicon Planar Transistors. TO-18 case. NPN and PNP mixed. Similar V405A, P346A, etc. Not tested or coded. Guaranteed minimum 50% good. 10/-

40 Silicon Planar Transistors. TO-18 case. NPN type similar 2N706, BS195A, etc. Not tested or coded. Guaranteed minimum 50% good. 10/-

15 Silicon Medium Power Transistors similar to BFY51 range. TESTED. Not coded. 10/-

30 Silicon Planar Transistors. TO-18 case. NPN type similar BC107/8/9 range. Not tested or coded. Guaranteed minimum 50% good. 10/-

3 Silicon Power Transistors similar to BU111. TO-3 case. Not tested or coded. Gold plated cases. 10/-

100 Germanium PNP Transistors. TO-18 case. Type similar NKT74/6, etc. Not tested or coded. Minimum 50% usable. 10/-

20 Germanium Transistors 2G371B. Case 50-2. Fully tested to makers specifications PNP. Equal to OC71 range. Not coded. 10/-

30 Micro alloy diffused Transistors. (MAT type) Not tested or coded. PNP. 10/-

25 Silicon NPN VHF Transistors. TO-18 case. Similar to BSY27, etc. Not tested or coded. 10/-

20 Silicon Planar Transistors. Plastic type. NPN. Similar to 2N3707/7 range. Not tested or coded. Guaranteed minimum 50% good. 10/-

20 Silicon Planar Transistors. Plastic type. PNP. Similar to 2N3702. Not tested or coded. Guaranteed minimum 50% good. 10/-

16 Silicon Rectifiers. Top-Hat case. 750mA + @ 100-1,000 piv. Guaranteed minimum 80% good. 10/-

12 Silicon Avalanche Rectifiers. Top-Hat case 1 1/2 amp @ up to 1,200 piv. Guaranteed minimum 80% good. 10/-

15 Silicon Epitaxial Planar Diode. Sub-miniature. Type SD19 Plessey. Exact substitute for 1N914, etc. 100% perfect. Not coded. 10/-

30 Part made Top-Hat Rectifiers (no connection broken, but plenty room to solder) 750mA up to 800 piv. Guaranteed minimum 80% good. 10/-

2G371B and SD19 are Manufacturers' tested devices. Other un-coded stocks are given type numbers as a guide only. Money refunded if not satisfied.

All above packs post free in UK. EXPORT SPECIAL. 10% of the above SALE goods are reserved for export until August 1969.



S-DeCs Single "DeC" with accessories and project manual..... 29/6
 "2-DeC" kit contains two "DeCs", component trays, accessories, instructive book, all packed in protective plastic box 69/6
 "4-DeC" kit contains four "DeCs", accessories, manual, etc. 117/6

BOOKS FROM STOCK
 "General Electric Transistor Manual", 660 pages of data and circuits 29/6
 "RCA Transistor Manual", 554 pages includes SCR circuits 28/-
 "Designers Guide to British Transistors". Excellent data book lists over 1,000 common types plus computer selected substitution chart 25/-
 (ADD 2/6 POST & PACKING FOR ALL BOOKS)

NEONS
 Signal neons for many types of circuit type "N"
 Price 1/6 each or 14/- dozen
HEATSINKS. Suitable for 2 x OC35, etc. As used in commercial equipment. Type 100 6/-
ALUMINIUM CHASSIS
 6 x 4 x 2 1/2 in with reinforced corners 6/9 each (P. & P. 1/6). Allly panel to fit, 1/6. Paxolin panel to fit, 2/-. Many other sizes in stock up to 12 x 8 x 2 1/2 in (see catalogue)

X-LINE MODULES YOU CAN OPEN!

X-161	2 Watt Amplifier	35/-
X-461	Stem	35/-
X-461	Burglar Alarm	35/-
X-461	Mosquito	30/-
X-261	Motor Oscillator	30/-
X-461	Lamp Flasher (Double)	30/-
X-261	Mic. FM Transmitter	35/-
X-261	Telephone Transmitter	35/-
X-261	A Player Transmitter	35/-
X-261	Guitar Transmitter	35/-
X-261	Wireless Sanyo	35/-

Generous discounts to retailers on all "X" line products. Send for details now.

SILICON RECTIFIERS

PIV	20mA	750mA	2 Amp	10 Amp
50	6d	1/1	2/3	5/0
100	9d	1/6	2/3	4/6
200	1/3	2/-	2/9	5/-
400	2/-	2/6	4/-	9/-
600	3/-	4/6	6/6	14/-
800	3/6	3/9	5/-	11/3
1000	—	6/-	6/6	14/-

THYRISTORS - SCRs

PIV	1A	3A	10A	30A	100A
50	7/6	9/-	7/4	—	20/-
100	—	10/-	10/-	—	22/-
200	8/6	—	12/6	42/-	35/-
300	—	11/-	—	—	—
400	9/6	12/6	15/-	40/-	45/-
600	—	—	20/-	84/-	130/-
800	—	—	—	—	—

ZENER DIODES

Watt	10% Tolerance	12 All.
3-0	4-7	7-5
3-3	5-1	8-2
3-6	5-6	9-1
3-9	6-2	10
4-3	6-8	11
4-7	—	12

See IR Panel for 1 watt types. Full range 5 watt also in stock.

BC107/8/9 NPN 2/9

2N3819 TEXAS FET 8/-

2N2646 UNI-JUNCTION 10/-

T1S43A UNIJUNCTION SIMILAR 2N2646 T1S43 BEK 3000, ETC. 6/9

CRS3/404F 40V 3AMP SCR 12/6

TD716 DIODE 12/-

D13T1 PROGRAMMABLE UNIJUNCTION TRANSISTOR 10/-

2N3055 115 WATT POWER SILICON NPN 15/-

2N2926 POPULAR PLANAR NPN 2/-

AD161/2 PAIR 10/-

NPN PNP POWER PAIR BERMANIAN

LOGIC

UL900 1-6 7-11 12+
 UL900 11/- 9/6 8/4
 UL914 11/- 9/6 8/4
 5 page Data and Circuits article 2/6
 Larger quantity prices (100+ and 1,000+ on application)

LINEAR AMP. IC'S

CA3020 1/2 watt output 9 volt supply 30/6
 (price includes free circuit for Guitar/PA Amplifier!)

TAA263 Tiny Mullard linear only 17/6—data on request

CA3012 Wide band with built in regulation 27/6

CA3014 3 stage amp. with Darlington output 32/6

SL701 Plessey lin. amp. for PE circuits 18/-

ULTRASONIC TRANSDUCERS

Operate at 40kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.
 FREE: With each pair our complete transmitter and receiver circuit.
 PRICE £5.18.0 Pair (sold only in pairs)

IOR

SOLAR CELLS
 B2H 0.2-0.4 volts @ 2mA Selenium type 12/6
 B3H 0.2-0.4 volts @ 1-2mA Selenium type 15/-
 C1H 0.3-0.4 volts @ 10-15mA Silicon 19/-
 S4H 0.3-0.4 volts @ 25-40mA Silicon 33/6

SOLAR DRIVE MOTOR

EP50A Run from sunlight activity on S4H cells (above) 39/6

PHOTOCONDUCTIVE CELL

CS120 20V 0.4 watt dark Res 110kohms Min. R @ 10FC = 7.2k @ 100FC = 800 ohms 19/8

SOLAR CELL KITS

DD190 Contains 4 Selenium photocells and free 24 page handbook 9/11
 K-421 Super assortment of 7 cells, 3 Selenium, 2 Silicon and 2 Cadmium Sulphide plus 24 page manual 58/6

TRANSISTOR KITS

DD170 Contains 2 audio and 1 RF transistor plus free manual 11/4
 DD184 Contains audio, RF, and power transistors, Silicon solar cell and germanium diode. With FREE manual 33/6

SILICON RECTIFIER KITS

DD175 Contains 4 100 piv + amp diodes 9/11
 DD176 Contains 2 200 piv + amp diodes 5/11
 DD177 Contains 2 400 piv + amp diodes 9/11

ZENER DIODES

Available in the following voltages with a dissipation of 1 Watt and tolerance on 10%. All supplied with free manual describing many interesting projects.
 3.9V, 4.7V, 5.6V, 6.8V, 8.2V, 10V, 12V, 15V, 18V, 22V, 27V.
 ALL ONE PRICE: 7/11

ZENER KIT

DD170 Bargain pack—contains 5 popular 1 watt diodes plus free project manual 19/6

TRANSISTOR SUBSTITUTION

Our TROI-C to TROI-C range are universal replacements for over 700 JEDEC (2N—) types. Prices in our FREE Catalogue. FULL SEMICONDUCTOR CENTRE LISTINGS, DOZENS OF INTERESTING DEVICES IN OUR CATALOGUE.

COMPONENTS

RESISTORS ± OR ± WATT 5% LOW NOISE CARBON FILM
 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 ohms and decades (x 10, x 100, x 1,000, x 10,000) 1/2 Wgt. etc. to 82 Megohms (100% tolerance) PRICES: 1-25, 4d, 26-99, 3d, 100-—, 3d (your selection ± and/or ± watt mixed)

SKELETON PRESET POTS. 20% Tol. Linear. Low noise. Available in sub-miniature sizes: 10k, 25k, 50k, 100k, 200k, vertical. 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 200k, 500k, 1 Meg, 2.5 Meg, 5 Meg. NEW PRICE: 1/- each or any selection of 2 pieces 10/-

ELECTROLYTIC CAPACITORS (Mullard)—10% to +50% Tol.
 Subminiature (all values in µF)
 4V 4 4 32 64 125 250 400
 6.4V 4 4 25 50 100 200 320
 10V 4 4 16 32 64 125 200
 16V 2.5 10 20 40 80 125
 25V 1.6 4 8 12.5 25 50 80
 40V 1 4 8 16 32 50
 64V 0.64 2.5 5 10 20 32
 Price 1/4 1/3 1/2 1/1 1/1 1/2
 MIN. POLYESTER CAPACITORS. Printed circuit type 250V d.c. working. 0.01, 0.025, 0.05, 0.1, 0.2, 0.47, 0.68, 0.82, 0.91, 0.94, 0.97, 0.98, 0.99, 1.0, 1.1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1000, 1200, 1500, 1800, 2200, 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10000, 12000, 15000, 18000, 22000, 27000, 33000, 39000, 47000, 56000, 68000, 82000, 100000, 120000, 150000, 180000, 220000, 270000, 330000, 390000, 470

Step up your EARNINGS

with this complete Library of *Electrical know-how and practice*

Practical Electrical Engineering

IT TELLS YOU ALL ABOUT
—Installing domestic wiring, regulations, equipment, testing, cables and faults, meters and switchgear, lighting, water heating, space heating, cookers, refrigeration, public address equipment . . . in fact everything you need to add to your income, to really advance in your work.

You can have this handsomely-bound library of facts, figures, vital theory and day-to-day practices sent to your home to examine free of charge. It will help you understand the many branches of the vast electrical industry from installation work of all kinds, Equipment, Instruments, Motors and Machines, Repair work, Maintenance and Operation right through to the Generation and Distribution of electricity. And, to make the 2,350 pages of absorbing text crystal clear there are over 2,000 "action" photos and explanatory drawings. In addition you receive a slip-case of 36 large Blueprint charts and sheets of handy data. Plus fascinating colour booklet of transparent pages which peel away to reveal how a Nuclear Power Station is operated.

LEADING EXPERTS EXPLAIN IN DETAIL
Written by 87 experts, this PRACTICAL library is planned to give you the knowledge which would normally take a lifetime to acquire. Send for your free trial set now—no obligation to purchase.

YOU RECEIVE 4 VOLUMES strongly bound in Grey Morocco, 9 1/2 in. x 6 1/2 in. containing 2,352 Pages of instructive information on latest practice;
2,100 Photographs, Diagrams, Working Drawings, many showing actual operations in works and plants.

24 Data Sheets in colour.
12 Quick-reference Blueprint Charts, each in the large size of 16 1/2 in. x 11 1/2 in.
NUCLEAR POWER STATIONS BOOKLET

FREE GIFT
Newnes Electrical Pocket Book
Nearly 400 pages with 258 illustrations, diagrams, tables.
(Value 10/6d)



Sent to you by post on **7 DAYS FREE TRIAL**

To: Buckingham Press Ltd., 18-19 Warren Street, London, W.1
Please send PRACTICAL ELECTRICAL ENGINEERING without obligation to buy if you accept my application. I will return the books in 8 days or post—

Tick (✓) here Full cash price of £16, or
 16/- dep. & 16 monthly payments of 20/-.
If you are under 21 your father must fill up the coupon

Full Name.....
(Block letters)

Address.....

County.....

Occupation.....

Signature.....

(Credit price £16.16s.)

Please tick (✓) here

The address on left is

My/our property

Rented

unfurnished

Furnished accom.

Temporary address

If none of the above please answer here


Mr.
Mrs.
Miss

PEE/3953

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminated Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

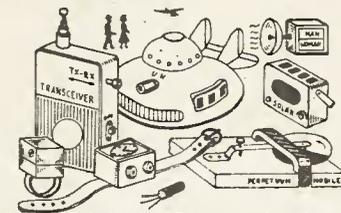

EXPERIMENTER'S PRINTED CIRCUIT KIT

8/6

Postage & Pack. 1/6 (UK)


Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-

Australia, New Zealand,
South Africa, Canada.

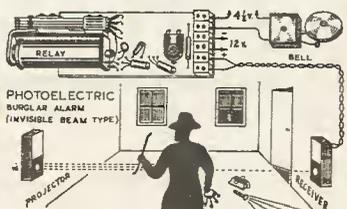(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. (10) 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (11) Postage Stamp Radio. Size only 1-62" x 0-95" x 0-25". (12) Wristwatch Radio 1-15" x 0-80" x 0-55". (13) Ring Radio 0-70" x 0-70" x 0-55". (14) Bacteria-powered Radio. Runs on sugar or bread. (15) Radio Control Tone Receiver. (16) Transistor P/P Amplifier. (17) Intercom. (18) 1-volts Amplifier. (19) Reliable Burglar Alarm. (20) Light-seeking Animal, Guided Missile. (21) Perpetual Motion Machine. (22) Metal Detector. (23) Transistor Tester. (24) Human Body Radiation Detector. (25) Man/Woman Discriminator. (26) Signal Injector. (27) Pocket Transceiver (Licence required). (28) Constant Volume Intercom. (29) Remote Control of Models by Induction. (30) Inductive-Less Transmitter. (31) Pocket Triple Reflex Radio. (32) Wristwatch Transmitter/Wire-less Microphone. (33) Wire-less Door Bell. (34) Ultrasonic Switch/Alarm. (35) Stereo Pre-amplifier. (36) Quality Stereo Push-Pull Amplifier. (37) Light-Beam Telephone "Phonephone". (38) Light-Beam Transmitter. (39) Silent TV Sound Adaptor. (40) Ultra-sonic Transmitter. (41) Thyristor Drill Speed Controller.

PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Flegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT 39/6

Postage and Pack. 2/6 (UK)

Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0

Australia, New Zealand
S. Africa, Canada and U.S.A.

Also Essential Data Circuits and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Project Lamp Stabiliser. (8) Electronic Project Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

JUNIOR PHOTOELECTRIC KIT

Versatile invisible-beam, Relay-less, Steady-Light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc. for the Experimenter.

CONTENTS: Infra-Red Sensitive Photo-transistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

PHOTOELECTRIC PARKING LAMP SWITCH

Automatically turns parking lamp on at dusk, off at dawn. Protects your car. Saves the battery. Miniature construction. Simply insert in parking lamp lead. Price: 27/6. Post and Packing 2/6 (U.K.).

THYRISTOR LIGHT DIMMER

Add a touch of luxury to your home. Adjust the light at parties, while watching TV, etc. Ideal for Children's bedroom. (100 watts max.) Replaces on-off switch. Price: 58/6. Post and Packing 2/6 (U.K.).

YORK ELECTRICS


333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 82 Radio, Electronic and Photoelectric Projects Assembled.

EXCLUSIVE PURCHASE!

PORTABLE AMPLIFIER UNIT

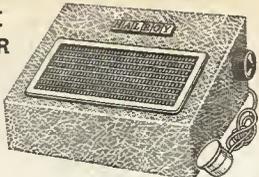By well known British Maker.
A luxury unit at a bargain price. Only 35/- P. & P.



Designed as a Telephone Amplifier but can be used in many different ways - a booster amplifier for transistor radios, a baby alarm, intercom, paging system, etc., etc. High gain four transistor amplifier unit housed in attractive leathercloth covered wooden cabinet with upward facing 3" high flux P.M., speaker covered by neat plastic grille. Fitted 3.5 mm jack socket and volume/control control. Size 7 1/2" x 4 1/2" x 3 1/2" high. Operates on standard PP6 or VT6 battery. Supplied complete with telephone pick-up induction coil fitted suction pad, lead and 3.5 mm jack plug.

Our Special price 35/- P. & P.

Or as above with 3.5 mm plug and DLR5 unit for use as sensitive microphone for baby alarms, communication systems, etc. Will operate over distances of up to 200ft or more when connected with twin flex or bell wire.

PRICE 40/- P. & P.
4/6
(Batteries and flex not included)

BRAND NEW 3 OHM LOUSPEAKERS
5in.14/-; 6in.18/8; 8in.27/-; 7 x 4in.18/8; 10 x 6in. 27/8.
E.M.I. 8 x 5in. with high flux magnet 21/-, E.M.I. 13 1/2 x 8in. with high flux ceramic magnet 42/- (15 ohm 45/-).
E.M.I. 13 x 8in. with two inbuilt tweeters and crossover network, 3 or 15 ohms 4 gns. P. & P. 5in. 2/-, 6 1/2 x 8in. 2/6, 10 x 12in. 3/6 per speaker.
BRAND NEW 12in. 15W H/D Speakers. 3 or 15 ohms. By well-known British maker. Now with Hi Flux ceramic ferrobar magnet assembly. 25.10.0. P. & P. 5/-. Guitar Models: 25w. 28/-, 35w. 28/-.
E.M.I. 3 1/2in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.
12in. "RA" TWIN COIL LOUSPEAKER. 10 watts peak handling. 3 or 15 ohm 25/- P. & P. 3/6.
3 1/2in. 12/8; 7 x 4in. 21/- P. & P. 2/- per speaker.

VYVAIN AND REXINE SPEAKERS AND CABINET FABRICS app. 54in. wide. Usually 35/- yd., our price 13/6 yd. length. P. & P. 2/6 (min. 1 yd.). S.A.E. for samples.

LATEST COLLARO MAGNAVOX 363 STEREO TAPE DECK. Three speeds 4 track, takes up to 7in. spools. 215.0.0. Carr. 10/-.
QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6.
Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 35/- P. & P. 3/-.

AGOS CRYSTAL MIKES. High Imp. for desk or hand use. High sensitivity. 15/6. P. & P. 7/6.
AGOS HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6.
CARBON MIKE INSERTS. Brand New. 2 1/2in. dia. 5/- P. & P. 1/6.

NEW S.T.C. TYPE 25 MINIATURE RELAYS— 12 volt. 4 s/p, c/o contacts. 1 amp rating. Coil resistance 185 ohms. Size approx. 1 1/4 x 1 1/4 in. high. 10/- each. P. & P. 1/6.
Also some similar, 4s above but coil resistance 5,800 ohms 48 volt operation. 8/- each. P. & P. 1/6.

SPECIAL OFFER! PLESSEY TYPE 99 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 x 1 1/4 in. Only 8/6. P. & P. 2/6.

TRANSFORMER BARGAINS

MAINS TRANSFORMER. Primary 200-240V two separate 1/2 wave secondaries giving approx. 16V at 1 amp and 20V at 1.2 amp; secs. can be connected in series for 36V at 1.5 amp. Ideal for transistor power supplies. Drop through mounting. Stack size 2 1/2 x 3 1/2 in. 15/- P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 11/- P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6.

MATCHED PAIR OF 2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

7-10 watt OUTPUT TRANSFORMERS to match pair of ECL86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.

BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240V AC. Sec. 240V at 50mA and 6.3V at 1.5 amp. Stack size 2 1/2 x 3 1/2 in. 10/6. P. & P. 3/6. (Special quotations for quantities).

HIGH GRADE COPPER LAMINATE BOARDS 8 x 6 in. FIVE for 10/- P. & P. 2/6.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Kit-board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response 1-30B. 20-20,000c/s. Bass boost approx. to +12dB. Treble cut approx. to -10dB. Negative feedback 18dB over main amp. Power requirements 25V at 0.6 amp.

PRICES: AMPLIFIER KIT 210.10.0; POWER PACK KIT 23.0.0; CABINET 23.0.0. All Post Free.
Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).



SPECIAL PURCHASE!

E.M.I. 4-SPEED PLAYER
Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 V shaded motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. LIMITED NUMBER ONLY 63/- P. & P. 6/6.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **E.M.I. MODEL 999 Single Player** with unit mounted pick-up arm and mono cartridge. 55.5.0
B.S.R. UA25 with latest mono compatible cart. 28.19.6
All plus Carriage and Packing 6/6.

LATEST GARRARD MODELS. All types available 1000 SP25, 3000, AT60 etc. Send S.A.E. for Bargain Prices!
FLUENT UNITS cut out for Garrard Model 1000, 1025, 2000, 3000. A.C.S. spec. With eight perspex cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

SONOTONE P1AHC compatible Stereo Cartridge with diamond stylus 50/- P. & P. 2/-
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. 32/6. P. & P. 2/-
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. 30/- P. & P. 2/-


FEW ONLY ACOS GP69/1. For EP and LP 10/- P. & P. 2/-
QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC85, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3d. x 6h. Ready built and tested. PRICE 75/- P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MK II
Uncut motor board size 14 1/2 in. clearance 2 in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 16 x 8 in. PRICE 79/6. P. & P. 9/6.

FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dormer & Wadsworth Ltd. Supplied ready fitted with twin -0005 tuning condenser for AM connection. Fresaligned FM section covers 88-102Mc/s. I.F. output 10-7Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/8 each. P. & P. 3/-.
GORLER F.M. TUNER HEAD 88-100 Mc/s, 10-7 Mc/s. I.F. 15/- plus 2/6 P. & P. (ECC85 valves, 8/6 extra).

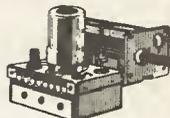

3-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 45 watts. Front panel can be detached and be extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.5.0. P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 8/-; AF117 7/6.

Set of Mullard 6 transistors OC44, 2-OC45, AC128D, matched pair AC28 25/-; Mullard LFH3 Audio Transistor Pack AC128D and matched pair AC128 12/6; ORP12 Cadmium Sulphide Cell 10/6. All post free.

SPECIAL OFFER!

A great opportunity to purchase a first class GENERAL PURPOSE HIGH GAIN, HIGH SENSITIVITY, PORTABLE AMPLIFIER. Completely self contained and can be used for a variety of purposes, i.e. Intercom, Baby Alarm, Booster unit for transistor radios etc., also ideal for classroom unit etc. Works perfectly with our special ACOS Stick Microphone (21/-). Output 1000mW. Uses standard 9 volt battery. Smart two tone carrying case size 12 x 4 x 9in. fitted standard input jack socket, volume controls, 7 x 4in. speaker. Completely built and tested, brand new with full maker's guarantee.




Only 79/6 POST FREE

STEREO AMPLIFIER

Incorporating 2 ECL86's and 1 E280, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete. Output impedance 3 ohms


ONLY 95.96

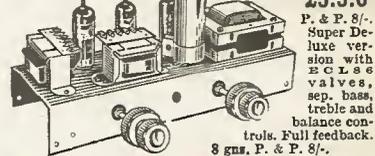

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

- Peak output in excess of 11 watts.
- All standard British components.
- Built on printed circuit panel size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GCT114 or 81 Mullard AC128D and matched pair of AC128 e/p).
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with KIT). All parts sold separately. SPECIAL PRICE 45/- P. & P. 3/-.

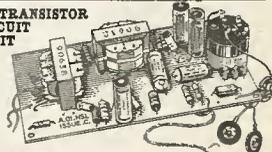Also ready built and tested, 52/6. P. & P. 3/-.




HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-8 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. LIMITED NUMBER.

OUR ROCK BOTTOM BARGAIN PRICE 49/6 P. & P. 6/-

10/16 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF85 and 2Z80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately, ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0. P. & P. 9/6.

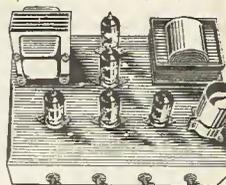

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.


BUILD YOURSELF A QUALITY TRANSISTOR RADIO—FULL AFTER SALES SERVICE!



THE MAGNIFICENT ROAMER 7

SEVEN WAVEBAND PORTABLE

7 FULLY TUNABLE WAVE BANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium-waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 × 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 × 7 × 4in approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. **Total building costs £5.19.6 P. & P. 7/6** (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

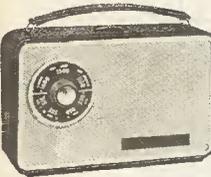

"NEW LOOK" MELODY SIX MED. AND LONG WAVEBAND WITH SPEAKER AND EARPIECE
6 transistors and 2 diodes. Push-pull output, tuning condenser, high "Q" ferrite rod aerial, 8in speaker, and personal earpiece with switched socket for private listening, 6½ × 4 × 2in. Total Building Costs 69/6. P. & P. 4/3. Plans and parts list 2/- (free with parts).



TRANSION FIVE MED. AND LONG AND TRAWLER BAND TO approx. 50 metres WITH SPEAKER AND EARPIECE 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, moving coil speaker. 6½ × 4½ × 1½in. Total Building Costs 47/6. P. & P. 3/9. Plans and Parts list 1/6 (free with parts).



POCKET FIVE MED. AND LONG WAVES AND TRAWLER BAND TO approx. 50 metres. WITH SPEAKER AND EARPIECE 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, moving coil speaker, etc. 5½ × 1½ × 3½in. Total Building Costs 44/6. P. & P. 3/6. Plans and Parts list 1/6 (free with parts).



SUPER SEVEN MED. LONG AND TRAWLER BAND 7 transistors and 2 diodes. 3in speaker, 2 R.F. stages, push-pull output, etc. 7½ × 5½ × 1½in. Total Building Costs 69/6. P. & P. 4/6. Plans and parts list 2/- (free with parts). Personal Earpiece with switched socket for private listening, 5/- extra.



ROAMER SIX 6 WAVEBANDS—MW1, MW2, SW1, SW2, LW AND TRAWLER BAND. 6 transistors and 2 diodes. Ferrite rod and telescopic aerials. 3in speaker. Top grade components. Size 7½ × 5½ × 1½in. Total Building Costs 79/6. P. & P. 4/9. Plans and parts list 2/- (free with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

RADIO EXCHANGE Ltd

DEPT. PE4, 61a HIGH STREET, BEDFORD. 0234 52367

Callers side entrance Style Shoe Shop. Open 10-1, 2.30-4.30 Monday - Friday 9-12.30 Saturday

LINEAR INTEGRATED CIRCUITS

- G.E. Type PA234 1 WATT AUDIO AMPLIFIER 23/-
Requires single supply between 9 and 24 Volts, drives 22 ohm loads, also compatible with 8 and 16 ohm loads. Dual-in-line package
 - G.E. Type PA280 LOW LEVEL AMPLIFIER 21/-
With single supply ideal as audio pre-amp. With two supply lines becomes economical operational amplifier. Dual-in-line package
 - RCA Type CA3080 WIDE-BAND POWER AMPLIFIER 32/-
Very popular 1 Watt, single supply line amplifier. DC to video. Suitable for motor control, Linear mixers, switches, etc.
 - RCA Type CA3085 ULTRA HIGH GAIN AMPLIFIER 30/-
3 amplifiers in one TO-5 (multilead) package, overall voltage gain well over 1,000,000 times. Can be used as 3 separate amplifiers
 - G.E. 2N5806 DARLINGTON PAIR 11/6
2 transistors in one package connected as Darlington Pair. Min. $\beta = 7,000$ at $I_C = 2mA$ (i.e. base current less than 290 Nanamps!). Ideal as low level, low noise input stage for pre-amps. Also $f_T = 60MHz$ min.
- Lead spreaders free with RCA types. Add 1/- for data sheets if required. Data sheets only 1/6 each, post free

TEXAS SELECT TRANSISTORS (SILICON)

- NPN Fast switches
 - TIS44 20V 50mA $\beta = 20$ (min) 1/9
 - TIS49 15V 200mA $\beta = 40-120$ 2/6
 - NPN Low level, low noise
 - 2N3707 30V 30mA $\beta = 100-400$ 4/-
 - 2N3708 30V 30mA $\beta = 45-600$ 2/5
 - BC182L 50V 200mA $\beta = 100-450$ 3/3
 - BC183L 30V 200mA $\beta = 100-850$ 2/5
 - BC184L 30V 200mA $\beta = 250$ (min) 3/2
 - NPN Medium power
 - 2N3704 30V 800mA $\beta = 100-300$ 3/3
 - 2N3705 30V 800mA $\beta = 50-150$ 3/4
 - PNP Fast switch
 - TIS50 12V 200mA $\beta = 40-150$ 3/8
 - NPN Low level, low noise
 - 2N4058 30V 30mA $\beta = 100-400$ 4/-
 - 2N4059 30V 30mA $\beta = 45-600$ 3/5
 - BC212L 50V 100mA $\beta = 90-300$ 3/3
 - BC213L 30V 100mA $\beta = 90-400$ 3/3
 - BC214L 30V 100mA $\beta = 140-400$ 4/-
 - PNP Medium power
 - 2N3702 25V 200mA $\beta = 60-300$ 3/8
 - 2N3703 30V 200mA $\beta = 30-150$ 3/8
 - N Channel FET
 - 2N3819 25V 10mA 9m - 2-6mA/V 9/-
 - P Channel FET
 - 2N3820 20V 10mA 9m - 0.8-5mA/V 18/9
- PORT & PACKING 1/6 CASH WITH ORDER PLEASE

KINVER ELECTRONICS LIMITED
STONE LANE, KINVER, STOURBRIDGE, WORCS.

HIGH SPEED MAGNETIC COUNTERS (4 × 1 × 1in). 4 digit. 12/24/48V (state which) 6/6 each. P. & P. 1/-.

COPPER LAMINATE BOARD (8½ × 5½ × ¼in). 2/6 each. 5 for 10/-.

RE-SETTABLE HIGH SPEED COUNTER (3 × 1 × ¼in). 3 digit. 12/24/48V (state which) 32/6 each.

BULK COMPONENT OFFERS

- 100 Capacitors 50pF to 0.5µF.
 - 250 Carbon Resistors ¼ & ½W (Transistor types).
 - 250 Carbon Resistors ¼ & 1W.
 - 100 Ceramic Capacitors 2-1,000pF.
 - 25 Vitreous W/W Resistors (5%).
 - 12 Precision Resistors (0.1% several standard values included)
 - 25 Close Tolerance Caps. (2%).
 - 10 Silicon Diodes 500 p.i.v. 750 mva.
 - 4 Silicon Rects. 400 p.i.v. 3 amp.
 - 8 Silicon Rects. 100 p.i.v. 3 amp.
 - 50 Silicon Trans. (2N706/708, BSY23/29, BCY41/42 types). Unmarked, Untested.
- ANY ITEM 12/6. ANY 5 ITEMS £2.10.0.

- S.C.s. (Thyristors) CRS1/20 5/6; CRS1/40 7/8; CRS3/10 7/8; CRS3/30 8/6; CRS3/40 10/-; CRS3/50 12/6 each.
- '3000' TYPE RELAYS (ex. new equip.) 10 for 25/- (our choice) P. & P. 5/-.
- VENNER LIGHTWEIGHT ACCUMULATORS (1oz 1½ × 1½ × ½in). 1.5 Ahr 12/6 each.
- COMPUTER LOGIC BOARDS containing: 14 BCZ11, 2 trippots, diodes, etc., 20/- each.
- LIGHT DIMMER/SPEED CONTROL MODULES: 200 watt, 35/-; 500 watt, 45/-; 1,000 watt, 60/-.
- RECORD LEVEL METERS (By Smiths). 1½ × ½in, 15/- each. P. & P. 2/6.
- MINIATURE RELAYS (1oz, ½ × ½ × ½in), 24V 1 c/o, 7/6 each. 12V. 10/- each.
- P. C. CONNECTORS (13 way in-line), 4/6 pair.
- LARGE CAPACITY ELECTROLYTICS: 100 + 400µF, 275V; 1,000µF, 50V; 2,500µF, 70V; 3,200µF, 16V; 5,000µF, 15V, 4/- each. 4,000µF, 90V; 5,000µF, 25V, 7/6 each. 5,000µF, 50V; 6,300µF, 63V; 10,000µF, 30V; 16,000µF, 15V; 25,000µF, 15V, 10/- each.
- SPEAKER BARGAINS (E.M.I. 13 × 8in.) With two Tweeters and x/over, 16 ohm, 65/-; with Dual Cone, 15 ohm, 62/6; Single Cone, 3 or 15 ohm, 45/- P. & P. 3/-.
- FAME, 12in, 20watt (Dual Cone), 95/- P. & P. 5/-.
- TWEETER (E.M.I. 3in), 15 ohm, 12/6.
- CAR RADIO (3/5 ohm), 7 × 4in, 15/-; 8 × 5in, 17/6.
- L.T. TRANSFORMERS. Prim 240V. SEC. 10/20/25V. and 3.5 amp, 20/- P. & P. 5/- 5 amp, model 25/- P. & P. 5/-.

PATTRICK & KINNIE
81 PARK LANE, HORNCHURCH, ESSEX
ROMford 44473

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/4	OC171	4/-
AC127	2/4	OC200	3/6
AC128	2/4	OC201	7/-
ACY17	3/-	2G301	2/6
AF114	4/-	2G303	2/6
AF115	3/6	2N711	10/-
AF116	3/6	2N1302-3	4/-
AF117	3/6	2N1304-5	5/-
AF118	3/6	2N1306-7	6/-
AF119	3/6	2N1308-9	8/-
AF186	10/-	2N3844A	5/-
AF139	10/-		
BFY50	4/-	Power Transistors	
BSY25	3/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	1/11	AD149	10/-
OC45	1/9	AUY10	30/-
OC71	2/6	Diodes	
OC72	2/6	AAY42	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/-	OA81	1/9
OC139	2/6	OA73	2/-
OC140	3/6	IN914	1/6

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

TRY OUR X PAKS FOR UNEQUALLED VALUE

XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000

XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706a, BSY27/29, BSY95A.

PRICE £5.50 PER 500
PRICE £10 PER 1000

XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £5 PER 1000

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

P/P 2/6 PER PACK (U.K.)

PRE-PAKS

Selection from our lists

No.	Description	Price
B1	50 Unmarked Trans. Untested	- 10/-
B2	4 Photo Cells Inc. Book of Instructions	- 10/-
B6	17 Red Spot AF Transistors	- 10/-
B6A	17 White Spot RF Transistors	- 10/-
B9	1 ORP 12 Light Sensitive Cell	- 9/-
B53	25 Sil. Trans. 400 Mc/s	Brand New - 10/-
B54	40 " " NPN To 5	Trans Voltage - 10/-
B55	40 " " NPN To 18	& Gain Fallouts 10/-
B56	40 " " NPN/PNP	All Tested - 10/-
B68	10 Top Hat Recs. 750 M/A	100-800 PIV - 10/-
B69	20 Diodes. Gld-Bnd. Germ Sil. Planar	- 10/-
B74	5 Gld-Bnd. Diodes. 2-OA9, 3-OA5	- 10/-
B75	3 Comp. Sec. 2G371, 2G381, 2G339A	- 10/-
C2	1 Unijunction Transistor 2N2160	- 15/-
B77	2 Comp. Pair AD161-AD162	- 10/-
C35	3 Unijunction Transistors = to 2N2160	- 15/-
A1	7 Silicon Rectifiers BY100 Type	- 20/-
A3	25 Mixed Marked and Tested Transistors	- 20/-
A21	5 Power Transistors 1-AD149/1-OC26 and 3 others	- 20/-

AND MANY MORE

JUST INTRODUCED !!! 2 BRAND NEW ITEMS !!!

PAK B.78

INTEGRATED CIRCUITS, MIXED UNTESTED, TYPES INCLUDE:- MIC 930, 932, 936, 944, 945, 946, 948, 950, 951, & 952. These are STC Type Numbers. Data and Circuits Supplied with Orders.

12 10/-

PAK B.79

GENUINE I.T.T. FULLY TESTED AND MARKED DIODES. 1N4007, 1 AMP. 1000 VOLT.

4 10/-

TRANSISTORS ONLY 1/- EACH

SILICON • PLANAR • N.P.N. • P.N.P.

All these types available

2N929	2N706	2S131	2S103	2N696	2N1613	2S733	BFY10
2S501	2N706A	2S512	2S104	2N697	2N1711	2N726	2S731
BC108	2N3011	2S102	2N2220	2N1507	2N1893	2N2484	2S732

All tested and guaranteed for gain and leakage—unmarked. Manufacturers' fall outs from the new PRE-PAK range.

SPECIAL OFFER

Stock clearance of Manufacturers' Rejects. Limited Number.

UHF/VHF Tuner Units. Consisting of: 2 AF186, 2 AF178, Tuning Condensers, Coils and Comps etc.

Price 10/- each.
Post & packing U.K. 2/6d.

NEW UNMARKED UNTESTED PAKS

25	BSY95A NPN Silicon	TRANSISTORS 10/-
10	OC45-OC81 Multi. Glass Type	TRANSISTORS 10/-
25	BSY26-27 NPN Silicon	TRANSISTORS 10/-
10	10 Watt Silicon All Voltages	ZENERS 10/-
25	BFY50-1-2 NPN Silicon	TRANSISTORS 10/-
10	4 amp. Stud. Silicon	RECTIFIERS 10/-
25	BC107-8-9 NPN Silicon	TRANSISTORS 10/-
40	1N914-6 OA200/202 Sub. Min. Silicon	DIODES 10/-
150	Min. Germ. High Quality	DIODES 10/-
25	2N706 A NPN Silicon	TRANSISTORS 10/-

PRE-PAK. N.605 POWER TRANSISTOR EQUIVALENT TO NKT301-2-3-4

5/- each

COMPLIMENTARY SET NPN/PNP GERM. TRANS.

2/6 pair

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. State 4 or 6 cylinder. **20/-each**

FREE CATALOGUE AND LISTS for:-

**ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

THERE IS ONLY ONE
BI-PRE-PAK LTD
BEWARE OF IMITATIONS

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

VALVES/SEMI-CONDUCTORS

BRAND NEW & GUARANTEED

O42	6/-	GJ4	9/-	30FL1	15/-	ECF85	7/6	GZ32	11/6	PY801	8/-
O82	6/-	GJ6	3/6	30L15	15/6	ECF85	11/-	PZ34	11/6	U25	15/-
1R5	6/-	6K8	4/-	30P19	14/-	ECM42	11/-	MU14	8/-	U26	15/-
1R5	4/6	6L6	9/6	30PL1	15/-	ECR81	6/3	PBC80	7/6	U191	14/-
1T4	3/-	6T7	8/3	30CL15	18/-	ECR83	8/6	PCB84	6/8	U281	13/-
1U4	4/-	6S7	6/-	32L8	8/6	ECR87	7/9	PC301	8/8	U301	11/-
1U5	7/-	6S7J	7/-	3524	3/6	ECR87	11/6	PC88	11/6	U801	22/6
2D21	5/-	6SL7	6/-	35W4	5/3	ECL83	10/6	PC88	11/6	UAC80	6/6
3A5	10/-	6SM7	5/6	50B5	6/6	ECL86	9/6	PC8189	12/6	UAF42	10/-
3Q4	7/-	6U7	7/-	50C5	8/6	EF37A	8/-	PC86	11/-	UBC41	8/-
3R5	6/-	6V6	4/3	6X1	7/-	EF37	7/-	PC86	11/-	UBF80	7/-
3V4	6/-	6X4	4/3	AZ31	10/-	EF41	9/6	PC87	8/8	UBF89	7/-
5R4	9/-	6X5	5/-	DAF91	4/6	EF42	10/6	PC90	9/8	UC84	10/-
5U4	6/-	7B7	7/-	DAF96	7/6	EF80	5/6	PCF80	7/8	UC85	7/-
5V4	5/6	7C6	6/6	DF91	3/-	EF85	6/6	PCF82	7/-	UCF80	9/6
5Y3	5/6	7Y4	8/6	DF96	7/6	EF86	6/6	PCF84	9/-	UCH42	10/-
6Z4	6/6	8V6	15/-	DK91	6/6	EF89	6/3	PCF86	6/6	UCM81	7/-
6/30L2	12/8	10F1	9/-	DK92	8/6	EF91	4/-	PCF80015/-	7/8	UCM82	8/6
6AC7	4/-	10P13	15/-	DK96	8/6	EF92	4/-	PCF80110/-	7/8	UCM83	8/6
6A67	6/-	10P14	16/-	DL92	5/-	EF183	7/-	PCF80210/-	7/8	UF41	10/-
6AK5	5/-	12A76	5/6	DL94	6/6	EF184	7/-	PCF80514/-	7/8	UF40	7/-
6AL5	3/-	12A77	4/-	DL96	8/6	EL83	17/6	PCL82	7/6	UF85	7/6
6AM6	4/-	12A77	5/-	EL96	6/6	EL84	11/6	PCL83	7/6	UF89	7/6
6AQ5	6/-	12A77	6/-	EL96	12/6	EL41	9/9	PCL84	7/-	UL41	10/-
6AS6	6/-	12BA6	6/3	EABC80	7/6	EL42	11/-	PCL85	9/6	UL84	7/-
6AT6	5/-	12BE6	6/3	E180F	15/-	EL81	9/-	PCL86	9/6	UY41	7/6
6AU6	5/9	12BH7	6/3	EAF42	9/6	EL84	5/6	PFL20012/8	8/6	UY85	6/6
6BA6	4/9	12Q7	6/6	EB91	3/6	EL86	8/6	PL105/30	5/6	VR105/30	5/6
6BE6	5/3	12SQ7	7/6	EB401	9/6	EL91	4/6	PL81	7/6	VR160/30	5/6
6BH6	8/-	12X36	6/6	EB96	6/6	EL96	5/6	PL82	7/6		
6BJ6	8/-	20F2	14/-	EBF80	7/6	EM80	7/6	PL83	7/6		
6BR7	11/-	20L1	13/-	EBF83	9/6	EM81	8/-	PL84	6/9		
6BZ6	7/-	20P1	12/-	EBF89	7/6	EM84	7/6	PL600	14/8		
6C4	3/8	20P3	12/-	ECC40	11/6	EM87	7/6	PY33	9/9		
6C6	4/-	20P4	22/6	ECC81	4/6	EY61	7/6	PY80	5/6		
6CD6	20/-	20L6	6/6	EC815	6/6	EY86	7/6	PY81	6/-		
6CH6	6/-	25Z4	4/6	EC828	6/-	EZ40	8/6	PY82	6/-		
6CL6	10/-	30C15	13/6	EC834	6/-	EZ41	8/6	PY83	6/-		
6D6	3/-	30C18	14/-	EC835	5/6	EZ80	5/6	PY88	7/6		
6E5	8/-	30F5	14/-	ECF80	7/6	EZ81	5/6	PY800	8/6		

TRANSISTORS

2N696	5/-	AF114	6/6	BSY53	8/3	OC70	3/-
2N697	5/-	AF116	4/6	BSY54	9/6	OC71	3/-
2N706	3/-	AF116	4/6	BSY55	15/9	OC72	4/-
2N708	4/-	AF117	4/6	BSY56	17/2	OC73	5/-
2N743	4/-	AF198	12/-	BSY65	4/6	OC74	5/-
2N744	4/-	AS228	6/6	BSY79	7/6	OC75	4/6
2N753	4/8	BC107	4/6	BUY10	12/6	OC78	5/6
2N914	4/8	BC108	2/6	GET113	5/6	OC81	2/6
2N916	4/8	BC109	4/6	GET131	4/6	OC81M	2/6
2N929	4/8	BC170	3/6	GET133	4/6	OC82	2/6
2N930	5/-	BC172	3/3	GE874	4/6	OC83DM	2/6
2N1613	6/-	BC173	3/6	MAT100	7/9	OC82	4/6
2N1711	6/8	BCY31	4/8	MAT120	7/9	OC83	5/6
2N1893	8/-	BCY34	4/8	MAT121	8/6	OC139	7/6
2N2160	14/11	BCY39	4/6	NK1211	5/6	OC140	9/6
2N2147	17/8	BCY43	5/-	NK1212	4/6	OC149	9/6
2N2869	5/6	BCY70	6/6	NK1213	5/6	OC170	8/6
2N2846	13/6	BCY71	10/6	NK1214	3/9	OC171	4/6
2N2926	3/-	BCY72	6/6	NK1215	3/9	OC202	6/6
2N3053	7/6	BF116	4/6	NK1216	9/6	OC203	6/-
2N3055	16/6	BF118	6/6	NK1217	5/6	OC204	6/-
2N3705	5/-	BF113	4/6	NK1219	4/6	SI140	4/6
2S102	6/6	BFY10	4/6	NK1223	5/-	SI141	6/-
2S103	6/6	BFY11	4/6	NK1224	3/9	XA104	4/6
2S104	6/6	BFY17	4/6	NK1225	3/9	XA124	4/6
AC107	4/6	BFY18	4/6	NK1226	5/-	XA125	4/6
AC108	4/6	BFY19	4/6	NK1227	4/6	XA126	4/6
AC127	4/6	BFY20	4/6	NK1261	4/3	XK141	7/-
AC128	4/6	BFY51	4/-	NK1405			
AC165	4/-	BFY52	4/6		14/3		
AC167	4/6	BFY90	12/6	NKT403			
AC176	5/6	BSX19	5/6		15/6		
AC199	4/6	BSX20	4/6	NKT1043			
ACY20	4/6	BSX40	13/9				
ACY21	4/6	BSX41	17/-	OC19	7/6		
ACY22	4/6	BSY10	5/-	OC23	8/6		
ACY28	5/-	BSY11	5/-	OC25	7/6		
ACY40	4/3	BSY26	4/6	OC28	8/6		
ACY41	4/6	BSY27	4/6	OC28	8/6		
AD140	8/-	BSY28	4/6	OC35	8/6		
AD149	16/-	BSY29	4/6	OC36	8/6		
AD161	8/-	BSY38	4/6	OC41	5/-		
AD162	8/-	BSY39	4/6	OC42	5/-		
ADT140	15/-	BSY51	7/8	OC44	4/-		
		BSY52	8/9	OC45	8/-		

SILICON

60 P.I.V.	6 AMP	5/6		
290 MA	400 P.I.V.	8 AMP	7/6	
	8 AMP	7/6		
70 P.I.V.	700 P.I.V.	100 AMP	35/-	
1 AMP	100 AMP	500MA	3/6	
140 P.I.V.	800 P.I.V.	800 P.I.V.	5 AMP	7/6
165MA	150 P.I.V.	5 AMP	7/6	
25AMP	200 P.I.V.	1000 P.I.V.	6 AMP	7/6
200 P.I.V.	400 P.I.V.	1000 P.I.V.	6 AMP	7/6
500MA	400 P.I.V.	650MA	6/6	

THYRISTORS SILICON CONTROL RECTIFIERS

400 P.I.V.	200 P.I.V.
3 AMP 7/6	7 AMP 15/6
400 P.I.V.	400 P.I.V.
7 AMP 13/6	7 AMP 15/6


ZENER DIODES

OAZ20012/-	OAZ208 6/6
OAZ210/-	OAZ209 6/6
OAZ205 8/6	OAZ210 6/6
OAZ208 8/6	OAZ211 6/6
OAZ204 8/6	OAZ212 6/6
OAZ205 8/6	OAZ213 6/6
OAZ206 8/6	OAZ227 8/6
OAZ207 9/6	

STC. 1 WATT SERIES 5%
 2.4/2.7/3.9/4.3/13/16/18/
 20/30/33 volt. 8/- each.
 7 series. All voltages from
 3.9-50 volt. 250mW, 2/6 ea.
 1.5w 4/- ea. 7w 5/- each.

PLEASE ADD POSTAGE

AVO CT.38 ELECTRONIC MULTIMETERS

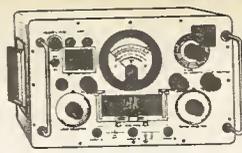

High quality 97 range instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power output. Ranges d.c. volts 250mV-10,000V. (10megΩ-110megΩ input). D.c. current 10μA 25 amps. Ohms: 0-1,000mΩ. A.c. volt 100mV-250V (with RF measuring head up to 250Mc/s). A.c. current 10μA-25 amps. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V. C. Supplied in perfect condition complete with circuit lead and RF probe £25. Carr. 15/-.

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B scope. T.B. 2c/s-750 kc/s. Bandwidth 0-5 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110/200/250V a.c. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, Hd, etc. £25. Carriage 30/-.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airmeec. Frequency coverage 20-80Mc/s. AM/C.W./F.M. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12x8x9in. Supplied in brand new condition complete with all connectors fully tested. £25. Carr. 20/-.

ADMIRALTY B.40 RECEIVERS



Just released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650kc/s - 30Mc/s, 1/1F 500kc/s. Incorporates 2 R.F. and 3 I.F. stages, band-pass filter, noise limiter, crystal controlled B.F.O., calibrator 1/F, output, etc. Built-in speaker, output for phones. Operation 150/230V a.c. Size 19 1/2 x 13 1/2 x 16in. Weight 114lb. Offered in good working condition. £22.10.0. Carr. 30/-.



AVOMETERS

Supplied in excellent condition, fully tested and checked. Complete with prods, leads and instructions. Model 7 £13.10.0. P. & P. 7/6.

TE-16A TRANSISTORISED SIGNAL GENERATOR



5 Ranges 400 KHZ-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 KHZ modulation. 3 1/2" x 5 1/2" Complete with instructions and leads. £7.19.6. P. & P. 4/-.


CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-8Mc/s. Operation on 6 volts d.c. Ideal for amateur use. Available in good used condition £5.19.6. Carr. 7/6. Or brand new with accessories £7.19.6. Carr. 7/6.

MARCONI TEST EQUIPMENT EX-MILITARY RECONDITIONED.

TF 1446 STANDARD SIGNAL GENERATORS, 85Kc/s-25Mc/s, £25, carr. 30/-, TF 885, VIDEO OSCILLATOR, 0-5Mc/s, £45, Carr. 30/-, T.F. 195M, BEAT FREQUENCY OSCILLATOR 0-40Kc/s, 200/250V a.c. £20, carr. 30/-, TF 142E, Distortion Factor Meter, £20, carr. 30/-, All above offered in excellent condition fully tested and checked. TF 1100 VALVE VOLTMETER, Brand New, £50, T.F. 1287 TRANS-MISSION TEST SET, Brand New £75, TF.1371. Wide Band Millivolt Meter, £50.

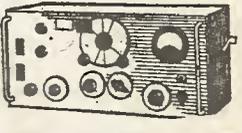

Variable Voltage TRANSFORMERS



Brand new, guaranteed and carriage paid. High quality construction. Input 50-60 cycles. Output full variable from 0-250V. Bulk quantities available. 1 amp - £5.10.0; 2 amp - £6.15.0; 5 amp - £8.15.0; 8 amp - £11.10.0; 10 amp - £13.10.0; 12 amp - £21; 20 amp - £37.

ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons
VM76. VALVE VOLTMETER
 R.F. measurements in excess of 100Mc/s and d.c. measurements up to 1,000V with accuracy of ±2%. D.c. range 300mV to 1kV. A.c. range 300mV to 300V RMS. Resistance 0.02-500MΩ. Price £72.
VM78. A.C. MILLIVOLT METER
 Transistorised. 1mV to 300V. Frequency 1c/s to 1Mc/s. Price £55.
VM79. RF MILLIVOLT METER
 Transistorised A.c. range 10mV to 3V. D.c. current range 0.01 μA to 0.3mA. Resistance 1 ohm to 10 megohms. £125.
HIB. AUDIO SIGNAL GENERATOR
 15c/s to 50kc/s, sine or square wave. Price £30.
JIB. AUDIO SIGNAL GENERATOR
 15c/s to 50kc/s. Price £30.
122B. AUDIO SIGNAL GENERATOR
 As per JIB except fitted with output meter. £35.
TT15. TRANSISTOR TESTER
 £37.10.0. Carriage 10/- per item.

TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 20c/s to 200kc/s on 4 bands. Square: 20c/s to 30kc/s. Output impedance 5,000 ohms, 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads, £15. Carr. 7/6.

RECORDING HEADS

Reuter j-track. As fitted to Collaro Mk. IV and Studio Decks. High imp. record playback, low imp. erase. Brand new. 19/3 pair. MINIFLUX j-track record 12/8. COSMOCORD j track heads. High imp. record/playback 65/-, Low imp. erase 20/-, MARRIOTT j track heads. High imp. record/playback 65/-, Low imp. erase 20/-, Post extra.

"SEW" CLEAR PLASTIC METERS



First grade quality Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR 38F, 1 1/2 in. square fronts.
 100-0-100μA 25/- 200μA 25/-
 500-0-500μA 25/- 300mA 25/-
 1-0-1mA 25/- 500mA 25/-
 1mA 25/- 750mA 25/-
 2mA 25/- 1A d.c. 25/-
 5mA 25/- 2A d.c. 25/-
 3mA 25/- 3V d.c. 25/-

MULTIMETERS for EVERY purpose!

LAFAYETTE DE-LUXE 100 KΩ/VOLT



"LAB TESTER"
Giant 6 1/2 in. scale.
Built-in meter protection. 0/0.5/10/50/250/500/1,000V a.c. 0/3/10/50/250/500/1,000V a.c. 0/10/100/500/100μA/10/100/500MA/2.5/10A. 0/1K/10K/100K/10M/100MΩ. —10 to 49.4dB ±15.13.0.P. & P. 5/.

10MΩ. —10 to 49.4dB ±15.13.0.P. & P. 5/.

LAFAYETTE
57 Range Super
50,000 O.P.V.
Multimeter. D.c.
Volts 125V-1,000V
A.c. Volts 1.5V-
1,000V D.c. Current
25μA-10 Amp.
Ohms. 0-15 MegΩ
dB.—20 to +81dB.
Overload Protection. \$12.10.0. Carr. 3/6.



NEW MODEL 550.30,000
O.P.V. with overload
protection. Mirror scale.
0/0.5/2.5/10/25/100/
250/500/1,000V d.c.
0/2.5/10/25/100/
250/500/1,000V a.c.
0/50μA/5/50/500mA.
12 amp. d.c. 0/60/1K6.
Meg. /60megohm \$9.17.6.
Post paid.



MODEL TE-30. 50,000
O.P.V. MIRROR SCALE
OVERLOAD PROTECTION
0/3/12/60/300/600/1,200V
d.c. 0/6/30/120/300/1,200V
d.c. 0-03/8/60/600MA d.c.
16KΩ / 160KΩ / 1/616MΩ.
—20 to +63dB. \$7.10.0.
P. & P. 9/.

MODEL TE12. 20,000
O.P.V. 0/0.6/30/120/600/
1,200/3,000/6,000V d.c.
1/6/30/120/600/1,200V a.c.
0/60μA/6/60/600MA.
0/15/600K/6meg. /60.
Megohm 50PF. 2 MFD
\$5.19.6. P. & P. 3/6.




MODEL TE 80. 80,000
O.P.V. 0/10/50/100/500/
1,000V. a.c. 0/5/25/50/
250/500/1,000V d.c.
0.5μA/5/50/500mA.
0/6K/60K/600K/6 Meg.
\$4.17.6. P. & P. 3/.



MODEL PT-34. 1,000 O.P.V. 0/10/50/
250/500/1,000V. a.c. 0/10/
100/1,000V d.c. 0/100/500/
1,000KΩ 30/8. P. & P. 1/6.



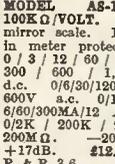TE-300 20,000 O.VOLT
GIANT
MULTIMETER
6 1/2 in. full view meter. 2
colour scale, overload
protection. 0/2.5/10/
250/1,000/5,000V a.c.
0/2.5/12.5/10/50/
250/1,000/5,000V
d.c. 0/50μA/110/
100/500MA 10A
d.c. 20K/200K/20
MΩ. \$15. P. & P. 5/.




MODEL AS-100D.
100KΩ/VOLT. 6 1/2 in.
mirror scale. Built-in
meter protection.
0/3/12/60/120/
200/600/1,200V
d.c. 0/6/30/120/300/
600V a.c. 0/10μA/
6/60/300MA/12 Amp.
0/2K/200K/2M/
200MΩ. —20 to
+17dB. \$12.10.0.
P. & P. 3/6.



PROFESSIONAL 80,000 O.P.V.
LAB. TESTER
Automatic
overload pro-
tection, mir-
ror scale.
Ranges: 1/10/
50/250/500/
1,000 volts, d.c. and a.c. 0-600μA,
10mA, 250mA. Current: 0/20K, 200K.
2 megohm. Decibels: —20 to +22dB.
\$5.19.6. P. & P. 2/6.



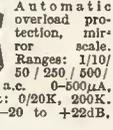MODEL TE-70. 30,000
O.P.V. 0/3/15/60/300/
600/1,200V d.c. 0/6/
30/150/300/1,200V
a.c. 0/30μA/3/30/
300MA. 0/16K/160K/
1.6M/16megohm.
\$5.10.0. P. & P. 3/.



MODEL TE-10A. 20KΩ/
Volt, 5/25/50/250/500/1,000V
d.c. 10/50/100/500/
1,000V. a.c. 0/50μA/2.5
mA/250mA. d.c. 0/6K/6
megohm. —20 to +22dB.
10-0, 100 mfd. 0.0-100-0-1
mfd. 69/6. P. & P. 2/6.




MODEL ZOM TRANSISTOR CHECKER
It has the fullest capacity for
checking on A, B and Ico.
Equally adaptable for
checking diodes, etc. Spec
A: 0-7-0-9987. B: 6-200.
Ico: 7-0-50 microamps
0-5mA. Resistance for
diode 200Ω-1MΩ.
Supplied complete with
Instructions, battery and
leads. \$5.19.6. P. & P. 2/6.



NEW CATALOGUE

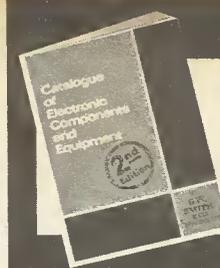Nearly 200 pages giving full details of a comprehensive range of COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT. Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-.



SEND NOW—ONLY 7/6 PER 1/-



UNR-30. 4-BAND COMMUNICATION RECEIVER

Covering 550Kc/s—30Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. a.c. Supplied brand new guaranteed with instructions. Carr. 7/6. 13 GNS.

TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550Kc/s to 30Mc/s. continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack 88B-CW • ANL • Variable BFO • 8 meter • Sep. band spread dial • IF 445Kc/s • Audio output 1.5W. • Variable RF and AF gain controls. 115/200V. a.c. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. \$35.15.0. Carr. Paid.



TRIO Communication Type Headphones. Normally \$5.19.6. OUR PRICE \$3.19.0 purchased with above receiver.

NEW LAFAYETTE SOLID STATE HA600 RECEIVER




5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE. 150Kc/s TO 400Kc/s AND 650Kc/s TO 80Mc/s. F.E.T. front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise Limiter • 8 Meter • 24in. Bandspeed • 230V a.c./12V d.c. neg. earth operation • RF gain control. Size 15in x 9 1/2in x 8 1/2in. Wt. 18 lb.

EXCEPTIONAL VALUE \$45. Carr. 10/- S.A.E. for full details.

LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

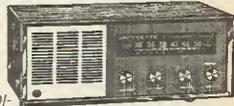A completely new transistorised receiver covering 152-174Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75Ω aerial input. Headphone jack. Operation 230V a.c./12V d.c. Neg. earth. \$37.10.0. Carr. 10/-



LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



19 transistors, 8 diodes, 1HF music power, 30W at 8Ω. Response 30-20,000 ±2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16Ω. Separate L and R. volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complimentary metal case. Size 10 1/2 x 8 3/4 x 7 1/2 in. Operation 115/230V. A.V. \$29. Carr. 7/6.

NEW STAR SR-200 SSB AMATEUR RECEIVER



An exciting new receiver covering 6 amateur bands 160/80/40/20/15/10 metres. Illuminated slide rule dial. 8 meter. Crystal calibrator. Product detector. Automatic noise limiter. RF tuning and gain controls. Speaker or phone outputs. 8 valves, 2 transistors, 2 diodes. 220/240V a.c. Supplied brand new and guaranteed. \$40.0.0. Carr. 10/-.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. 2 Y amp. Bandwidth 2 CPS-1 MHz. Input Imp. 2 megΩ 25 P.F. Illuminated scale. 2in tube. 115 x 180 x 230mm. Weighs 8lb. 220/240V a.c. Supplied brand new with handbook \$22.10.0. Carr. 10/-.



TELL DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced T. and Bridge T. Impedance 600Ω range (0-1dB x 10) + (1dB x 10) +10 +20 +30 +40dB. Frequency: d.c. to 200KHz. Accuracy: 0-05dB. + indication dB x 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new \$27.10.0. P. & P. 5/.



R209 MK. II COMMUNICATION RECEIVER



11 valve high grade communication receiver suitable for tropical use. 1-20Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, BFO. Aerial trimmer, internal speaker and 12V d.c. internal power supply. Supplied in excellent condition, fully tested and checked. \$15. Carr. 20/-.

T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -01/-003/-1/-3/-1/3/10/30/100/300V. R.M.S. 4c/s. 1.2Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. \$17.10.0. Carr. 5/.



GARRARD

FULL CURRENT RANGE OFFERED. BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS



SRP22 Mono	£8.10.0
SRP22 Stereo	£8.19.6
*1025 Mono	£7.10.0
*1025 Stereo	£7.19.6
*2025 Stereo	£8. 8.0
*3025T/C Mono/Stereo	£8.17.6
*3000 Stereo	£9.19.6
*3P25 MKII	£11.19.6
*SL55	£11.19.6
A70 MKII	£12.10.0
*AT60 MKII	£13.10.0
*SL65	£14.14.0
AF75	£19. 0.0
401	£23. 7.6
SL75	£29. 0.0
SL95	£35. 0.0

Carriage/insurance 7/6 extra any model. WB4 bases \$3.19.6. Perspex cover \$3.10.0. Carr. extra. *Special offer base and cover available for those models at \$4.15.0. Carr. 5/-. Full range of Garrard accessories available.

E.M.I. SINGLE PLAYERS

4 speed with separate arm and cartridge 52/6. Carr. 3/6.

FIELD TELEPHONES TYPE L

Generator ringing, metal cases. Operates from two 1.5v. batteries (not supplied). Excellent condition. \$4.10.0. per pair. Carr. 10/-.

GW. SMITH & CO (RADIO) LIMITED


Phone GERRARD 8204 9153
Cables SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W C 2

OPEN
9 a.m. to
6 p.m. every
day Mon. to
Sat. Trade
supplied.

Mullard DATA BOOK for 1969

Get up-to-date with the latest Mullard Data Book—just published. It contains details of current Mullard valves, picture tubes, semiconductors and components for Radio, TV, Audio and HiFi applications. Each section, colour coded for quick reference, includes comparables and equivalents information plus details of the latest devices in the replacement market.

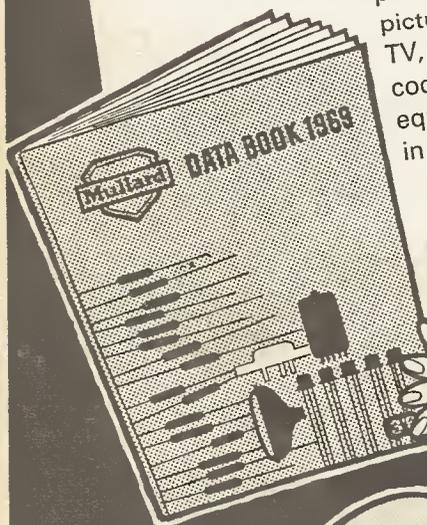Quick! Buy your copy from your local TV retailer or send 3/6 plus 9d for postage and packing direct to Mullard Ltd.



Mullard

Mullard Limited, Distributor Sales Division, Mullard House, Torrington Place, London WC1.

CED72

BROWSERS AND BEGINNERS

NOT all readers of this magazine are doers. Many are armchair constructors—though, let us hasten to add, they are just as welcome as the most zealous manipulators of soldering irons and pliers. That they do at anyrate *read* about electronics is a distinct mark in their favour! But we always try to coax the browsers from their armchairs into productive activity.

The varied range of projects described in these pages provide a strong incentive for action. At one stage or another some of our passive readers become enthused by the possibilities of certain projects and the plunge is taken. But others still hesitate on the brink, as enquiries we receive concerning the possibility of purchasing made-up projects testify.

Knowledge and practical skill are not obtained without effort. As with all specialised interests, electronics demands study of fundamentals and then practice.

Articles aimed at helping the beginner in the first steps of constructional work appear frequently in these pages. This month we are giving extra special attention to the needs of beginners—whether they be new readers or chair-bound regulars. The Constructors Guide included as a supplement in this issue should dispel any remaining qualms in the mind of the most hesitant reader. This guide will familiarise him with the principal features of components and enable him to translate the theoretical circuit diagram into a practical model. The most popular methods of construction are described; the tools and materials required and the techniques employed are concisely but clearly explained.

Having digested this basic information, the first steps in construction can be taken with confidence. Obviously simple projects should be tackled at the start, but with regular practice skills will be acquired and increased familiarity with components gained. A whole range of exciting projects will then come within reach.

But even when a state of high proficiency is reached, there will always be something new to read about: new components and new circuit techniques are constantly being evolved. Things are always happening—that's one reason for the great fascination of electronics. Just *reading* about the subject is only part of the story however; making practical use of these new developments is even more rewarding.

F. E. Bennett—*Editor*

THIS MONTH

CONSTRUCTIONAL PROJECTS

MICROPHONE MIXER	259
PHASE SPLITTER— FREQUENCY DOUBLER	267
POCKET RADIATION MONITOR	270
ELECTRONIC MIME MOBILE ANIMAL—EMMA	275
INTERRUPTED SCREENWIPER CONTROL	281

SPECIAL SERIES

BIONICS—6	294
-----------	-----

GENERAL FEATURES

THEORY INTO PRACTICE	256
LOUDSPEAKERS	286

NEWS AND COMMENT

EDITORIAL	255
NEWS BRIEFS	258, 291, 305
ELECTRONORAMA	284
MARKET PLACE	292
SPACEWATCH	306
READOUT	309

SUPPLEMENT

CONSTRUCTORS GUIDE

*Our May issue will be published on
Monday, April 14*

All correspondence intended for the Editor should be addressed to: The Editor, PRACTICAL ELECTRONICS, IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Advertisement Offices: PRACTICAL ELECTRONICS, IPC Magazines Ltd., 15/17 Long Acre, London, W.C.2. Phone: 01-836 4363. Subscription Rates including postage for one year, to any part of the world, 42s. © IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is specially reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

TRANSISTOR CIRCUITS INTO

Transistor circuits lend themselves readily to several simple forms of layout and construction, due to the facilities of direct transistor connection without the need for plug-in holders. Some of these methods are briefly outlined in this month's extra supplement *Constructors' Guide* in the centre of this issue.

The following article shows just how easy it is to make a constructional layout when given a circuit diagram only. It is based on a three-transistor class A amplifier, which does not boast a hi fi specification, but can be useful as a monitor in sound recording or as a booster for crystal tuners or pick-ups.

ONE of the problems faced by the amateur constructor, using laminated plastics and copper wiring boards, is the translation of a theoretical circuit to a practical layout.

This can be done quite easily by using a piece of squared paper to represent the hole matrix of the board. The horizontal rows of holes, those which lie along the length of the copper strips, are given a letter A-Z, and the vertical rows are given a number 1-26 or more.

These letters and numbers give a set of co-ordinates to work from. The size of the board to be used is determined after a rough layout has been drawn on the squared paper, showing the physical size of the components that are under consideration.

If space is not a major consideration, the components can be laid out flat on the board; for a more compact layout the resistors and capacitors can be stood up on end as shown in the example. If components are laid flat on the board, one has to determine the amount of space to be occupied, governed mainly by component length.

To give an example for guidance, a $\frac{1}{2}$ watt resistor occupies a minimum length of five holes on a matrix pitch of 0.15in.


SQUARED PAPER LAYOUT

When preparing the layout of the circuit on the board, take a piece of square paper, and mark it out as near as possible according to the circuit layout in the theoretical diagram. Take as an example for this exercise a simple general purpose linear amplifier (see Fig. 1).

Make a start with the transformer and, after taking a measurement of its size and finding the number of holes required, place this at the top right hand corner of the paper. Position it so that the secondary winding is nearest to the right hand end (Fig. 2). Two rows of holes are left clear of the transformer for the connection wires to the loudspeaker. The holes required are marked on the paper with large dots, for example, 17B and 17D (secondary), 13B and 13D (primary). Enter these references down in a table with the component reference number by the side of it. The copper strips are cut at 15B and 15D so that primary and secondary windings are not shorted.

The components can be drawn on the squared paper in block form and marked with reference numbers. The values can be placed on the position chart if required. The next components to be located will be TR3. The collector is marked out for the hole 12D, the base at

Fig. 1. Theoretical circuit. This example is a class A amplifier. Junction positions for the component board are shown

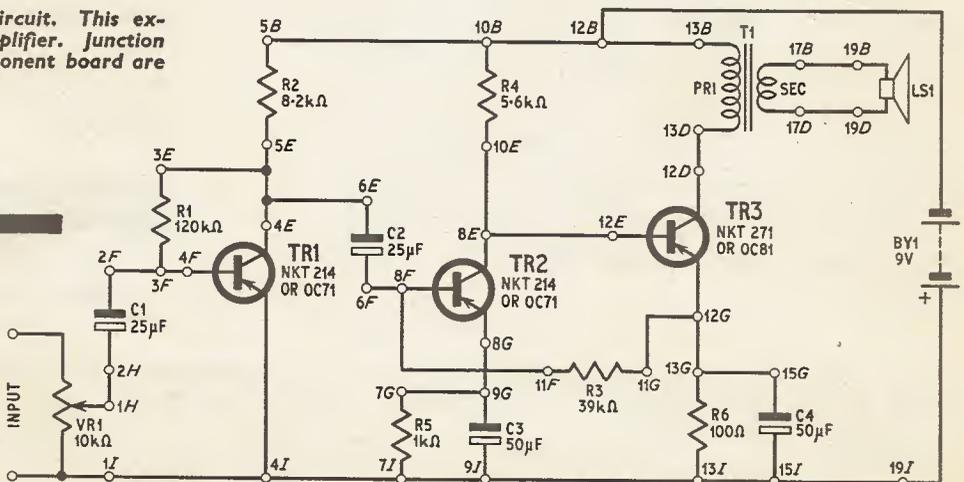

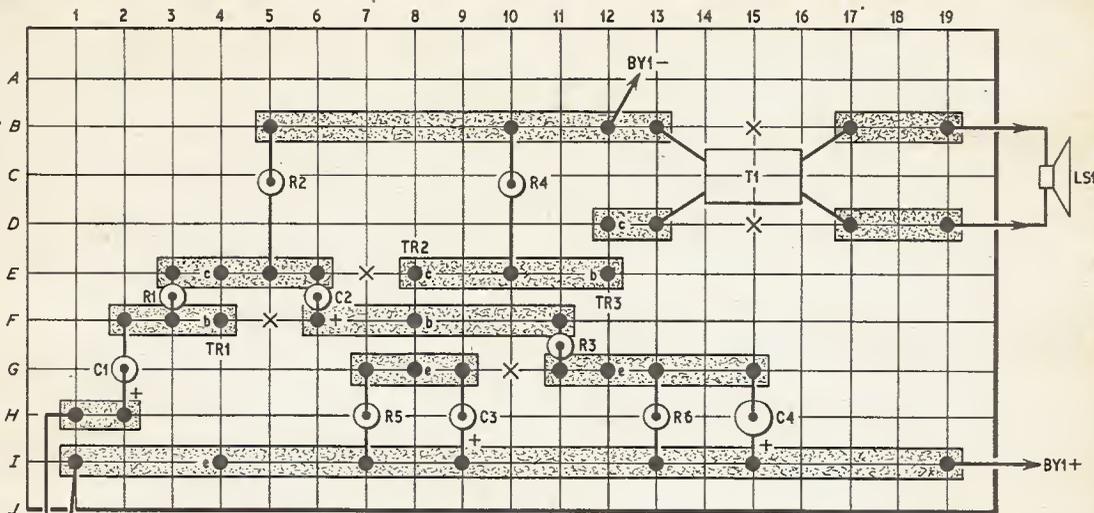


Fig. 2. Use squared paper to draw plan of component layout based on layout of circuit. External components VR1, LSI, and BY1 are connected by flying leads to the board. Collector is wire nearest spot; base is centre wire on all transistors



COMPONENTS . . .

Resistors

R1 120k Ω (3E-3F)	R4 5.6k Ω (10B-10E)
R2 8.2k Ω (5B-5E)	R5 1k Ω (7G-7I)
R3 39k Ω (11F-11G)	R6 100 Ω (13G-13I)

Potentiometer

VR1 10k Ω log (Wiper to 1H, Common to 1I)

Capacitors

C1 25 μ F elect. 15V (2F-2H)
C2 25 μ F elect. 15V (6E-6F)
C3 50 μ F elect. 15V (9G-9I)
C4 50 μ F elect. 15V (15G-15I)

Loudspeaker

LSI 3 ohms (19B-19D)

Transformer

T1 9.2:1 output transformer (Radiospares type T/T4) (Primary to 13B-13D; Secondary to 17B-17D)

Transistors

- TR1 NKT214 or OC71 (collector to 4E, base 4F, emitter 4I)
- TR2 NKT214 or OC71 (collector to 8E, base 8F, emitter 8G)
- TR3 MKT271 or OC81 (collector to 12D, base 12E, emitter 12G)

Battery

BY1 9 volts (negative to 12B, positive to 19I)

Component Board


Printed wiring board, can be either Veroboard (see Fig. 2) or plain s.r.b.p. with Cir-Kit copper strip

12E and emitter 12G. Next, R6 is marked at 13G and 13I. Following the general form of the theoretical circuit, C4 will be next and is connected to the emitter via hole 15G and 15I.

Resistor R3 is also connected to the emitter of TR3 and the base of TR2. Its position is marked on the paper at holes 11G and 11F. Mark in the conductor strips that are required by drawing parallel lines on the paper for each strip (see Fig. 2) between the points of entry of the components wires to be joined, e.g. between 15G and 11G.

TR2 base is connected to R3 through hole 8F. The collector is direct coupled to the base of TR3 through 8E. The emitter of this transistor is connected through 8G to R5 and C3 negative which are inserted at 7G and 9G respectively. The other end of these two components are inserted at 7I and 9I for direct connection to the positive supply line. It should be an easy matter to follow the layout of the first stage now. The rest of the components are marked out in a similar fashion.

continued on next page

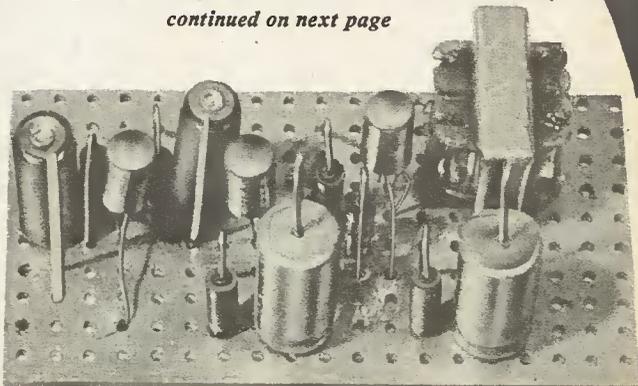

TRANSFER TO COMPONENT BOARD

When the last component has been drawn the size of the piece of board can be determined, which in this case will be given by the line *J* and row *19*.

Before placing any components on the piece of board all necessary copper strip breaks must be made. These must be indicated on the paper with crosses.

The drilling of holes is best carried out by clamping the board on a piece of wood, copper side up; this avoids tearing the copper foil. Where a copper strip has to be cut, a $\frac{3}{16}$ in drill will do this by putting the point of the drill in the holes and twisting it until the copper is removed. Be careful or the copper strip may be lifted.

The components are placed in their respective positions on the plain side of the board and all soldering is done on the copper side. The finished article should look like that in the photograph. With practice quite a compact layout can be achieved, and if the stand up method of fixing is used, a very small layout can be obtained.


When soldering on this type of wiring board a hot, clean iron must be used, and done quickly, otherwise prolonged heat may raise the copper foil from the base board.

Transformers, tags and pins or flying leads are either connected with insulated wire or soldered direct to the copper strip. If volume controls (potentiometers) are to be mounted direct on the printed wiring board, a hole must be carefully drilled in the board to accept the threaded fixing ($\frac{3}{16}$ in). The copper strip must be cleared away from the locking nut with a sharp knife to prevent short circuits. The potentiometer tags are connected to the board by insulated link wires soldered to the appropriate copper strips.

60mW AMPLIFIER

The circuit used in this example is a simple general purpose amplifier suitable for coupling to a crystal set tuner or gramophone crystal pick-up. In this latter application a 100 kilohm resistor should be connected in series with the input to VR1 to avoid mismatch to the amplifier.

TR1 is a small signal amplifier stage providing sufficient drive for the direct coupled power amplifier. The bias current for TR1 is derived through R1 to maintain stable d.c. operating conditions. The bias current for TR3 is taken directly through R4, whilst R3 feeds bias for TR2 from the potential divider formed by T1, TR3 emitter, and R6. With any increase in current through TR2, the base-emitter voltage of TR3 is reduced. This causes less current to flow through TR3. Consequently, the voltage across R6 is reduced, causing a simultaneous reduction in supply to TR2 base. The operating conditions of TR2 and TR3 are heavily dependent on R3 for stable working without over-running TR3. The power output fed to a 3 ohm loudspeaker is about 60mW, which is adequate for personal listening. ★

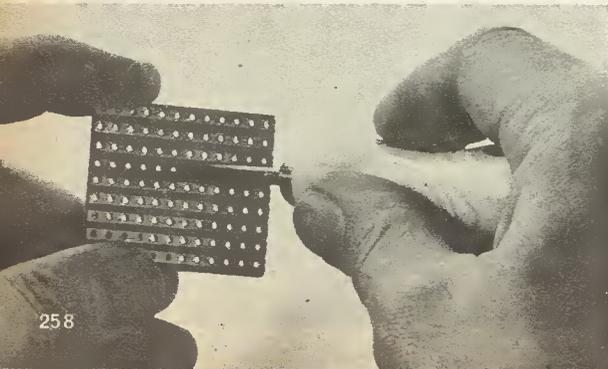

NEWS BRIEFS

Inflated Dome for Radar Stations

SEVERAL of the long range radar stations provided and operated by the National Air Traffic Control Service of the Board of Trade are sited on exposed positions and are therefore exposed to the most adverse weather conditions. At the Clee Hill Radar Station this problem has been overcome by enveloping the complete aerial system in a 40ft diameter inflated dome made of hypalon coated terylene. A blower system designed and developed by Premier Precision Ltd., inflates the dome with clean dry air, the pressure being controlled at 0.1 p.s.i. greater than the pressure imposed on the outer surface of the dome by the wind. Pressure control instrumentation was supplied by Thorn Automation and the dome was supplied and erected by the Frankenstein Group.

Computers for Hospitals

THE Department of Health and Social Security have ordered six small on-line computers, from Elliot Automation System Ltd., for automating bio-chemical analysis in hospitals.

The analysis of bio-chemical samples is carried out by hospital pathology laboratories for diagnostic reasons. By linking mechanical analysers directly to an on-line computer, skilled technicians will be relieved of the repetitive and time consuming clerical work involved in making the manual calculations which are otherwise necessary when producing data sheets.

Solid State Traffic Controller

THE first British designed and manufactured solid state traffic controller to be installed in the UK is now in operation at the Bishopsgate-Middlesex Street intersection in the City of London. The design is based on a set of interchangeable modules from which a controller can be assembled and programmed to cater for any intersection. The most complex intersections can be controlled by one equipment and additional modules enable the controller to cope with any increase or change in traffic demands.

The controller is used in conjunction with an inductive vehicle detector which uses a loop of cable buried under the road surface. Two versions of the detector are available—presence and passage detectors—both of which are used in the City of London installation (see photograph below). The presence detector gives an output to indicate queueing vehicles and the passage detector, which is sensitive even to bicycles, is arranged to ignore parked vehicles.



By F. C. JUDD



MICROPHONE MIXER

If you make high quality tape recordings that require mixing microphones and high level radio tuner inputs, this five channel audio mixer might be just the companion piece for your tape recorder.

Designed around two of the amplifier circuits that appeared in last month's article *Modern Audio Circuits*, this mixer has the added advantage that the constructor need not be limited to the two microphones and three high level signal inputs provided in the prototype as the amplifier circuits can be duplicated so providing more channels if required.

LOW Z MICROPHONES

The mixer can be constructed to cater for low impedance microphones such as ribbon or moving coil types where the microphone transformers are built-in.

Otherwise the microphone inputs have a nominal impedance of 120 kilohms which is suitable for low impedance microphones having their own matching transformers to provide a medium to high output impedance.

SPECIFICATION . . .

Sensitivity at mic inputs

3mV-10mV max. for 1 volt r.m.s. output

Sensitivity at line (high level) inputs

200mV-500mV max. for 1 volt r.m.s. output

Distortion for these inputs—Mic: Less than 0.75%
Line: Less than 0.15%

Microphone input impedance (without transformers)—120 kilohms

HIGH LEVEL INPUTS

The high level inputs are suitable for the output from other pre-amplifiers, radio tuners, and tape recorder high level outputs, that is, signals from audio outputs of between 600 ohms (line) and up to 500 kilohms at between 100 to 500mV. Adjustment can be made so that the input signals to both the microphone and high level inputs can be increased without introducing distortion.

NOT FOR CRYSTAL MICROPHONES

While the microphone pre-amplifiers have sufficient gain for use with crystal microphones, the input impedance of 120 kilohms would considerably reduce the bass response. This follows from the fact that crystal microphones have a high source impedance and also high internal capacitance.

Although the high level inputs have an impedance of 500 kilohms, these are equally unsuitable as a high signal voltage is required which the crystal microphone does not produce.

Line (high level) input impedance—500 kilohms

Output impedance—Nominal 600 ohms

Signal to noise ratio

Mic inputs—60dB below 1 volt at output

Line input—66dB below 1 volt at output

Frequency response—Mic: 40Hz to 15kHz \pm 2dB

Line: 30Hz to 20kHz \pm 2dB

Total current consumption—12mA

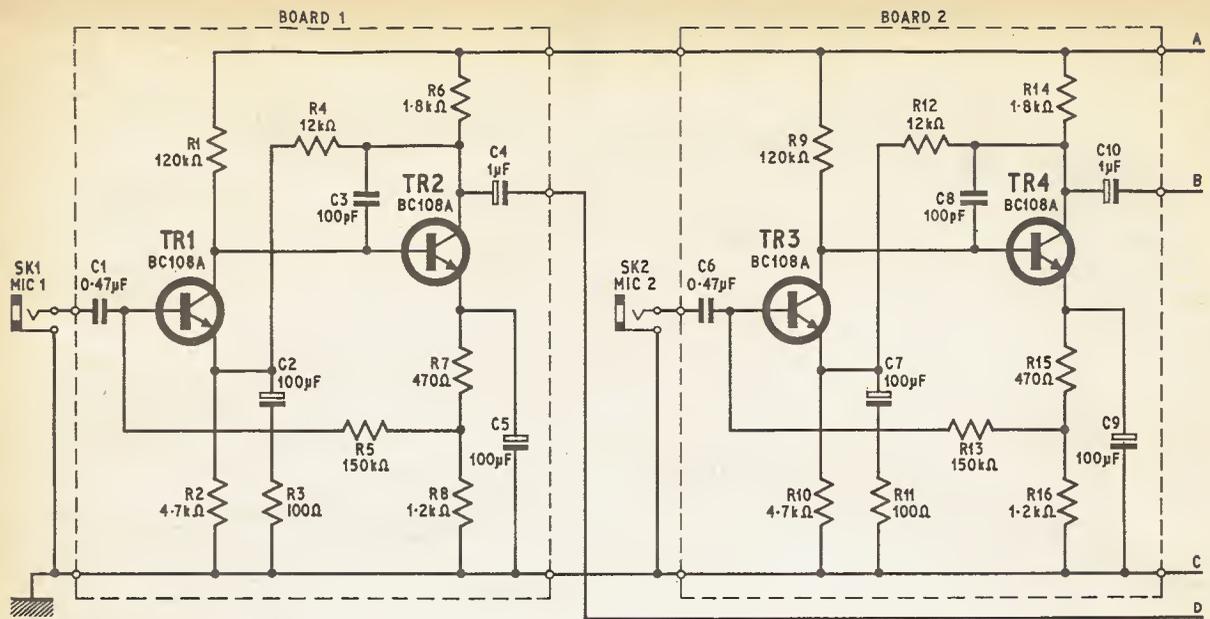


Fig. 1. Circuit diagram of mixer unit. Amplifier sub-assemblies are contained within the dashed lines

CIRCUIT DETAILS

The basic amplifier given in Fig. 1 consists of TR1 and TR2 microphone 1 pre-amplifier; TR3 and TR4 microphone 2 pre-amplifier, and TR5 and TR6 the mixing amplifier.

Common to all of the stages is the use of d.c. feedback loops to achieve stabilisation against temperature variations.

The gain of each microphone pre-amplifier is fixed at approximately 40dB for a distortion level of less than 0.75 per cent. The gain of the mixing amplifier is adjustable between approximately 13 and 30dB but, for the overall performance as per the specification, is adjusted to around 15dB. This more than compensates for the insertion losses of the passive network of mixing amplifier input potentiometers and associated series resistors.

A nominal 600 ohm output allows for a long screened connecting lead to a tape recorder without loss of treble response and will provide more than sufficient signal for tape recorder line or high level inputs at impedances between 600 ohms and 500 kilohms or greater.

FEEDBACK CONTROL

The pre-set control VR6 in the emitter circuit of TR5 controls the amount of feedback between the collector of TR6 and the emitter of TR5 and therefore the overall gain of this stage. With VR6 at maximum resistance the gain will be at a minimum but the circuit will accept much larger input signals. At the same time the gain from the microphone pre-amplifiers will be decreased but they will also accept larger input signals.

It follows that the microphone inputs could therefore be used for electric guitar pick-ups with a medium impedance but fairly high signal output, say 50mV or so.


For this application VR6 must be pre-set to its maximum value of 10 kilohms. Otherwise VR6 is adjusted as described later, to provide the performance given in the specification.


POWER SUPPLIES

The mixer operates from an 18V supply, consisting of two 9V batteries in series, at a total current consumption of 12mA. It would undoubtedly operate quite efficiently from a mains power unit, but this could lead to problems with mains hum pick-up by the microphone transformers if these are built into the mixer.

In view of the fairly low current consumption and the fact that a mixer is rarely run for so long and so frequently as most other kinds of audio equipment, it would hardly be worthwhile providing it with a mains supply.

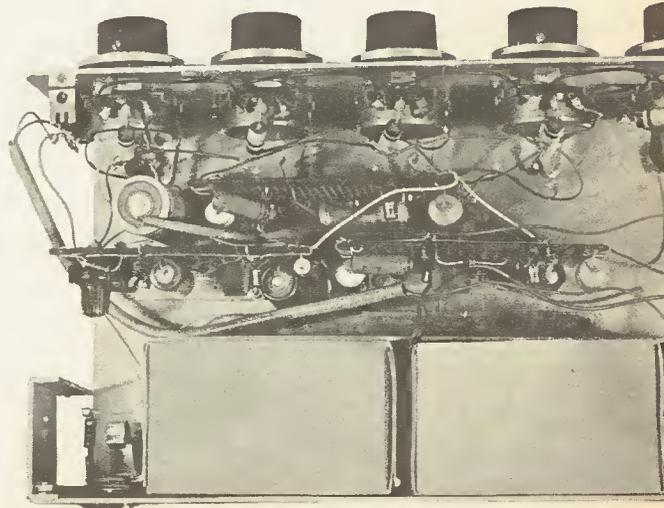Battery operation has the advantage of making the mixer completely portable and quite independent of mains supplies.



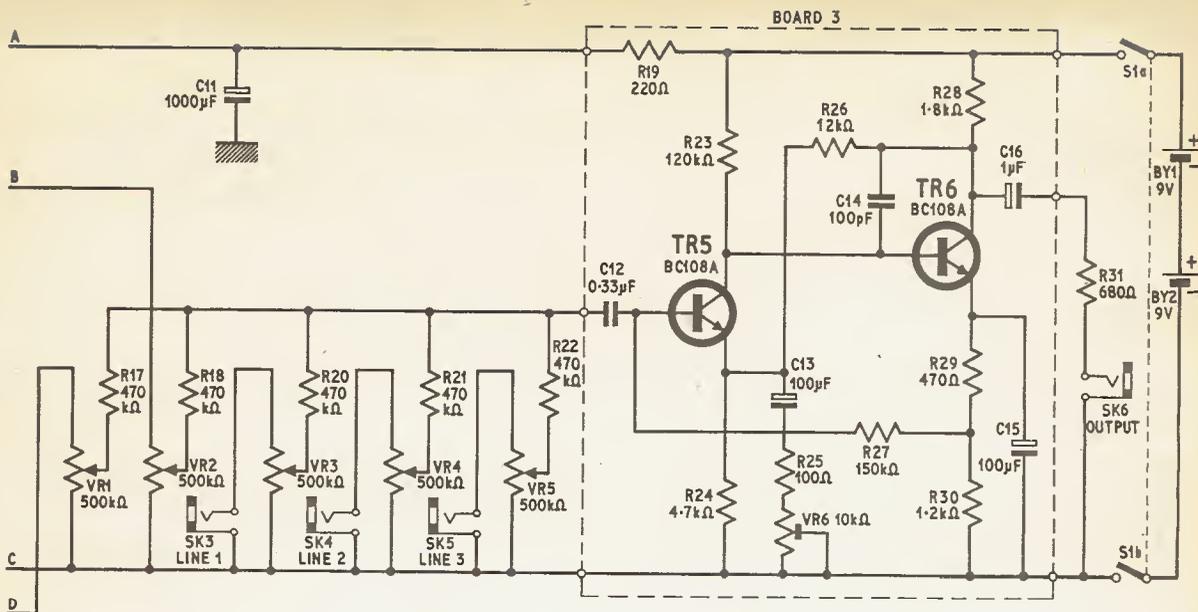

COMPONENTS . . .

Resistors

R1	120k Ω	R17	470k Ω
R2	4.7k Ω	R18	470k Ω
R3	100 Ω	R19	220 Ω
R4	12k Ω	R20	470k Ω
R5	150k Ω	R21	470k Ω
R6	1.8k Ω	R22	470k Ω
R7	470 Ω	R23	120k Ω
R8	1.2k Ω	R24	4.7k Ω
R9	120k Ω	R25	100 Ω
R10	4.7k Ω	R26	12k Ω
R11	100 Ω	R27	150k Ω
R12	12k Ω	R28	1.8k Ω
R13	150k Ω	R29	470 Ω
R14	1.8k Ω	R30	1.2k Ω
R15	470 Ω	R31	680 Ω
R16	1.2k Ω		

All $\frac{1}{4}$ watt $\pm 10\%$ carbon

Capacitors

C1	0.47 μ F tubular paper
C2	100 μ F elect. 25V
C3	100pF silvered mica
C4	1 μ F elect. 25V
C5	100 μ F elect. 25V
C6	0.47 μ F tubular paper
C7	100 μ F elect. 25V
C8	100pF silvered mica
C9	100 μ F elect. 25V
C10	1 μ F elect. 25V
C11	1,000 μ F elect. 25V
C12	0.33 μ F tubular paper
C13	100 μ F elect. 25V
C14	100pF silvered mica
C15	100 μ F elect. 25V
C16	1 μ F elect. 25V

Transistors

TR1-6 BC108A (6 off)—LST Components,
7 Coptfold Road,
Brentwood,
Essex.

Potentiometers

VR1-5 500k carbon log. (5 off)
VR6 10k carbon lin preset—Electroniques type
MPC

Sockets

SK1-6 Standard type jack sockets (6 off)

Switch

S1 Double pole on/off switch

Batteries

BY1, BY2 Ever Ready PP9, 9 volts

Miscellaneous

Aluminium case—Electroniques type, series 222

Calibrated control knobs—Electroniques type NK2

Perforated s.r.b.p. (0.15in matrix) $3\frac{1}{4}$ in \times $2\frac{1}{2}$ in
(3 off)

Microphone transformers (if used)—Electroniques/
Parmeko type 2549 for 25 ohm microphones, or
type 2570 for 100-600 ohm microphones

P.V.C. covered wire. Battery connectors (4 off)

CIRCUIT BOARD WIRING

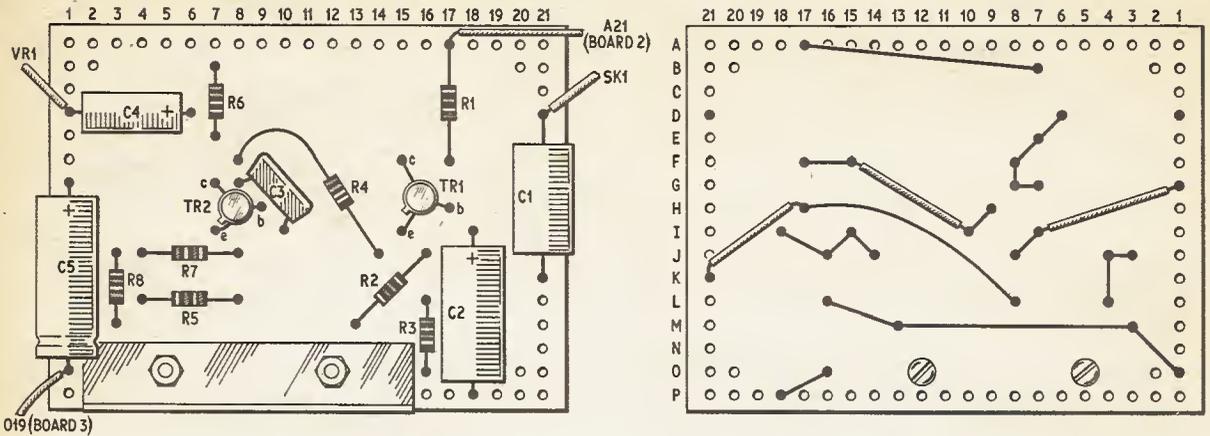


Fig. 2. Component layout and wiring for Board 1, comprising the pre-amplifier for Microphone 1

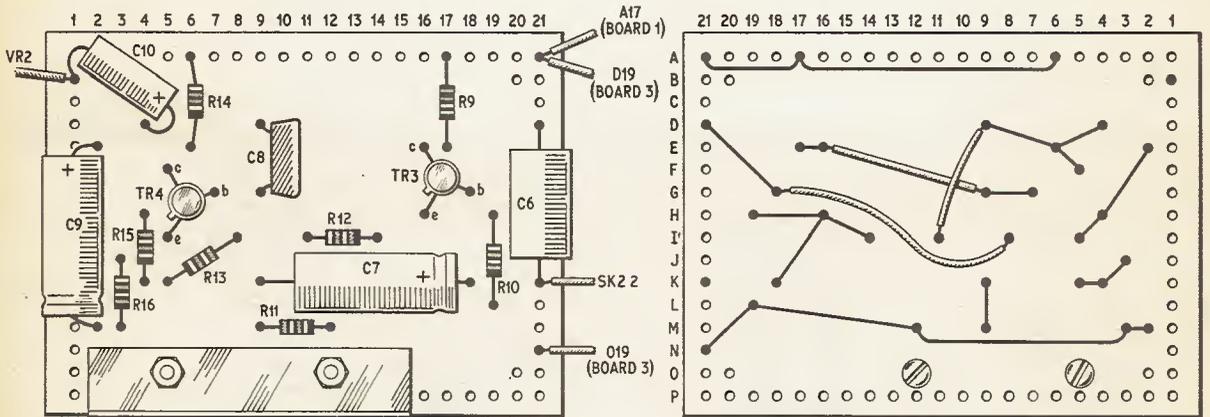


Fig. 3. Component layout and wiring for Board 2, comprising the pre-amplifier for Microphone 2

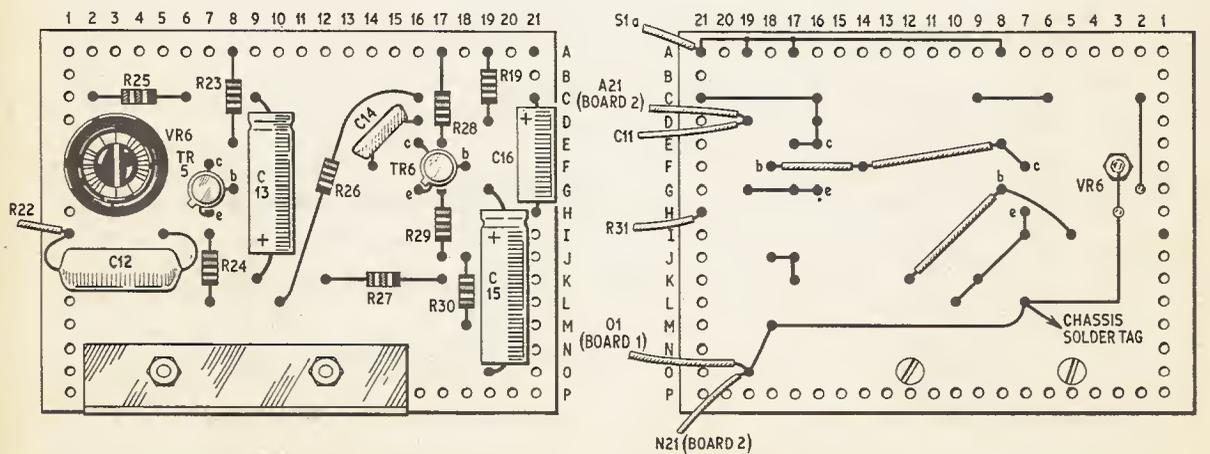


Fig. 4. Component layout and wiring for Board 3, comprising the mixing amplifier

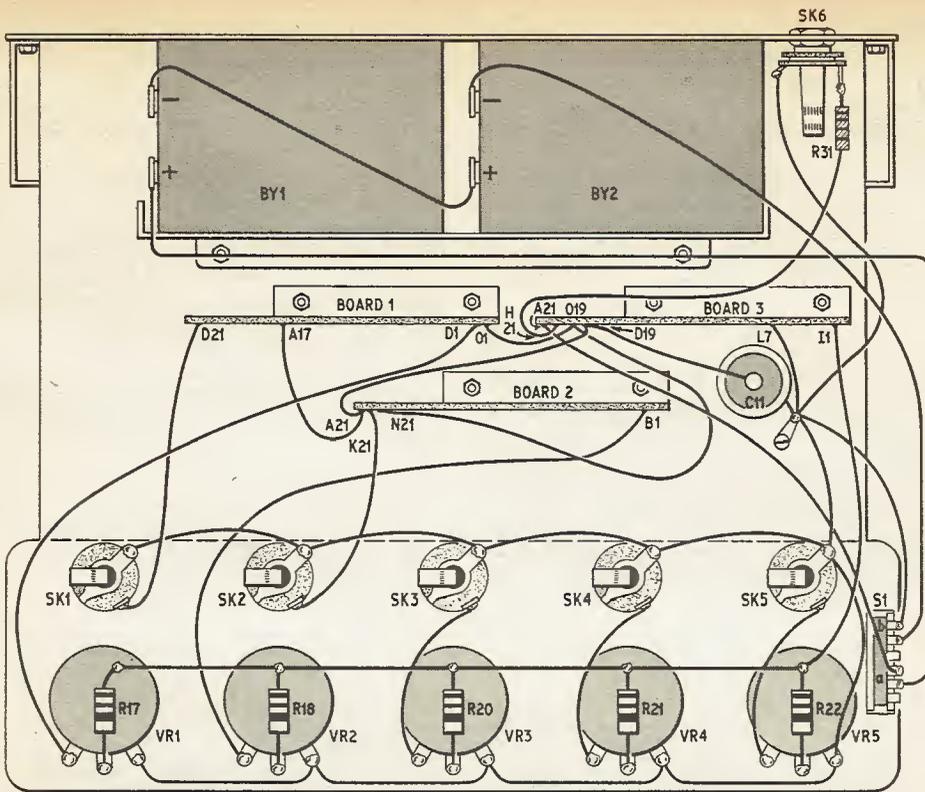


Fig. 8. Wiring of microphone mixer unit

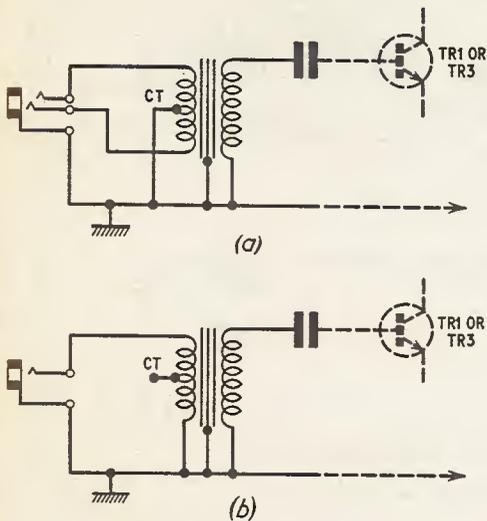


Fig. 9. Microphone transformer connections for (a) balanced input; (b) unbalanced input

The Electronics type P.2549 is a 40:1 ratio transformer for 25 to 30 ohm microphones. The type P.2570 is suitable for 400 to 600 ohm microphones and has a ratio of 10:1.

Connections for balanced or unbalanced inputs with these transformers are shown in Fig. 9. Balanced inputs will require three way, sleeve ring and tip, jack sockets.

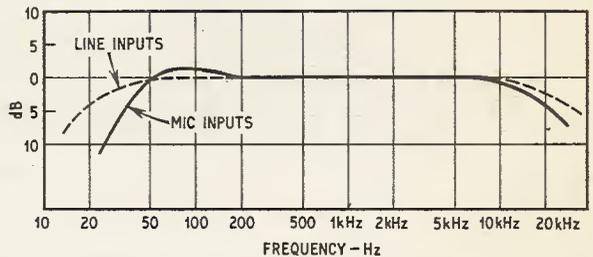


Fig. 10. Frequency response for microphone and line inputs

PERFORMANCE CHECKS

Frequency response and gain checks, etc. should be carried out with an audio signal generator and valve voltmeter.

With approximately 200mV of sine wave signal fed into either of the line inputs and with the gain control set to maximum, adjust the feedback control VR6 until the signal level at the output is approximately 1 volt r.m.s.

With this setting a 2 to 3mV signal fed into the microphone inputs should similarly produce this output of 1 volt.

The overall frequency response for these input and output signal settings is shown in Fig. 10.

If no test instruments are available VR6 must be pre-set by trial.

To perform as in the specification, around 2 kilohms of VR6 will need to be in circuit.

With all the preset resistance in circuit giving maximum negative feedback, the input signals to the high level sockets can be increased to around 1 volt and that to the microphone inputs around 50mV. ★



K. J. ENTERPRISES

BRITAIN'S PREMIER MAIL-ORDER AUDIO SPECIALISTS

Immediate despatch on Advertised Lines.

Send Cash with Order.

DISCOUNT BARGAINS * VAST STOCKS OF TAPE & EQUIPMENT * REFUND GUARANTEE.

BRANDED TAPES

20% OFF!

**BASF - EMI - GRUNDIG
PHILIPS - SCOTCH - AGFA**

Brand new, Fully Guaranteed and in normal manufacturer's pack

STANDARD PLAY	List Price	Our Price	DOUBLE PLAY	List Price	Our Price
5" 600' }	22/2	18/-	3" 300' Not Scotch	14/3	11/6
5 1/2" 900' } Except Agfa	29/5	24/-	3" 400' Scotch only	16/7	13/3
7" 1200' }	36/7	29/6	4" 600' }	26/-	21/-
LONG PLAY			4 1/2" 900' Agfa, BASF only	31/-	25/-
3" 210' Not Scotch	9/3	7/6	5" 1200' }	43/2	34/9
3" 300' Scotch only	9/7	7/9	*5 1/2" 1800' }	56/11	46/-
4" 450' }	14/9	12/-	*7" 2400' }	79/-	63/6
4 1/2" 600' BASF, Agfa only	22/-	18/-	10" 4600' Agfa, only	140/9	112/9
*5" 900' }	29/2	23/6	TRIPLE PLAY		
*5 1/2" 1200' }	36/5	29/6	3" 450' Not Scotch	22/3	18/-
*7" 1800' }	51/7	41/6	3" 600' Scotch only	24/10	19/9
8 1/2" 2400' BASF, Scotch	74/-	58/9	4" 900' }	40/-	32/3
10" 3280' Agfa only	85/9	68/9	*4 1/2" 1200' Agfa, BASF only	50/-	40/3
10" 3600' BASF only	96/6	77/6	5" 1800' Not Scotch	67/2	54/-
10 1/2" 4200' Agfa, BASF only	113/6	89/3	5 1/2" 2400' Agfa, BASF only	91/4	73/6
SCOTCH DYNARANGE (L/P)			7" 3600' }-only	116/6	93/6
5" 900' }	32/8	26/3	QUADRUPLE PLAY		
*5 1/2" 1200' }	41/-	33/-	3" 600' }	37/-	29/6
7" 1800' }	58/1	46/6	3 1/2" 800' } Kodak only	46/3	37/-
8 1/2" 2400' (Metal Reel)	84/3	67/6	4" 1200' }	64/6	51/6

GRUNDIG TAPE AVAILABLE ONLY WHERE MARKED WITH ASTERISK

Postage and packing 2/6. Orders over £3 post free

AMPEX TAPE - SAVE 30%

A special offer of top quality, premium grade, mylar (Polyester) base tape with Full Leader and Stop Foil. Boxed and Fully guaranteed.

Type	Description	List Price	One	Three	Six
541-12	1150' on 5 1/2" reel Long Play	35/-	24/6	71/-	137/-
551-12	1200' on 5" reel Double Play	42/-	29/6	86/-	166/-
551-16	1650' on 5 1/2" reel Double Play	55/-	33/6	97/6	189/-
551-24	2400' on 7" reel Double Play	77/6	49/6	145/6	285/-

POST & PACKING 2/6. ORDERS OVER £3 POST FREE.



COMPACT CASSETTES UP TO HALF PRICE!

Compact Cassettes with 60 and 90 minutes playing time. Brand New and packed in normal plastic library box. Available at this exceptional price.

MC.60	MC.90
1 for 10/6	1 for 14/-
3 for 30/-	3 for 40/6
6 for 55/6	6 for 78/-
12 for 105/-	12 for 150/-

Standard pattern to fit Philips, Stella, Elizabethan, Dansette, Sanyo, etc.

Post and Packing 2/6. Orders over £3 Post Free

K. J. ENTERPRISES (Dept) 17 THE BRIDGE, WEALDSTONE, MIDDLESEX (Opposite Harrow and Wealdstone Station). 01-427 7758. Showroom hours: 9.30a.m. - 5.30p.m. Closed Lunch 12.30 - 1.30p.m. Close 1p.m. Saturday.

ILFORD - ZONAL TAPE

40% OFF!



NEW KJ SPECTACULAR

From the Motion Picture and Magnetic Products Division of ILFORD LTD. we are proud to present a New Stupendous BARGAIN OFFER!! Never before have you been offered such a breathtaking opportunity. ILFORD-ZONAL premium grade magnetic tape (extensively used by the B.B.C.) at a terrific reduction of 40% Brand New, Boxed, Fully Guaranteed and complete with leaders, trailers and stop foil. **UNIQUE TO KJ**

Description	List Price	One	Three	Six
900' on 5" reel Long play P.V.C.	29/1	17/6	50/6	96/6
1200' on 5" reel Long play P.V.C.	36/1	22/6	65/-	125/-
1800' on 7" Long play P.V.C.	51/4	29/6	86/-	165/-
1200' on 5" reel Double Play (Polyester)	43/1	27/9	81/-	157/6
1800' on 5 1/2" reel Double Play (Polyester)	56/1	36/-	105/-	204/-
2400' on 7" reel Double Play (Polyester)	78/10	49/6	145/6	285/-

Post and Packing 2/6

Orders over £3 post free

SPECIALISTS in PHILIPS, GRUNDIG, FERGUSON, SANYO and EAGLE EQUIPMENT

BARGAIN OF THE MONTH

**PHILIPS 4-TRACK
TAPE RECORDER**
SAVE £7.15.0!



LIST PRICE £48.12.0 OUR PRICE £40.17.0

CARRIAGE 10/-

MODEL N4307

Superb reproduction, beautifully designed, simple operation.

The N4307 PHILIPS Tape Recorder incorporates all the famous Philips features.



SPECIFICATION

Freq. Range 60-14,000Hz. Signal to noise 45dB. Wow and Flutter ±0.25%. Output Power 2 watts. Inputs Mic. 2mV, Radio/Diode 2mV, Gram. 100mV. Power Supply Mains voltage 110/250V. Dimensions 16 1/2" x 11 1/2" x 5 1/2".

● Mono recording and playback at 3 1/2 i.p.s. ● Takes 7" spools. ● Provision for mono playback of two parallel tracks. ● Monitoring facilities. ● Position indicator. ● Tone control. ● Socket for direct recording from Mic./Record player. ● Ext. speaker socket. ● Stylishly housed in wooden cabinet. ● Complete with microphone, tape and spool.

FREE

Our New 100 page illustrated catalogue sent entirely FREE on request. Britain's most specialised comprehensive range of recording tape, Accessories and Audio equipment. 20,000 reels of tape always in stock with reductions ranging up to 50%

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm): Body: $\frac{1}{2}W \times 8 \times 2.8$
 $\frac{1}{2}W \times 10 \times 4.3$
 Leads: 35mm

Prices—per Ohmic value		each	10 off	25 off	100 off
$\frac{1}{2}W$	10%	2d	1/6	3/3	10/4
$\frac{1}{2}W$	5%	2½d	1/9	3/8	11/8
$\frac{1}{2}W$	10%	2½d	1/9	3/8	11/7
$\frac{1}{2}W$	5%	2½d	2/-	4/-	12/10

(10% ranges available in E12 renard series. 5% ranges available in E24 renard series.)

ELECTROLYTIC CAPACITORS (Mullard). —10% to +50%.

Subminiature (all values in μF)	4V	6.4V	10V	16V	25V	40V	64V	Price
8	6.4	4	2.5	1.6	1	0.64	1/6	1/3
32	25	16	10	6.4	4	2.5	1/2	1/1
64	50	32	20	12.5	8	5	1/2	1/1
125	100	64	40	25	16	10	1/2	1/1
250	200	125	80	50	32	20	1/2	1/1
400	320	200	125	80	50	32	1/2	1/1

POLYESTER CAPACITORS (Mullard)

Tubular, 10%, 160V: 0.01, 0.015, 0.022 μF , 7d. 0.033, 0.047 μF , 8d. 0.068, 0.1 μF , 9d. 0.15 μF , 11d. 0.22 μF , 1/- 0.33 μF , 1/3. 0.47 μF , 1/6. 0.68 μF , 2/3. 1 μF , 2/8.
 400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0.01, 0.015, 0.022 μF , 7d. 0.033 μF , 8d. 0.047 μF , 9d. 0.068, 0.1 μF , 11d. 0.15 μF , 1/2. 0.22 μF , 1/6. 0.33 μF , 2/3. 0.47 μF , 2/8.
Modular, Subminiature, Epoxy encapsulation, Polyester film, P.C. mounting. 10%, 100V: 0.001, 0.002, 0.005, 0.01, 0.02 μF , 6d. 0.05 μF , 8d. 0.1 μF , 10d. 0.2 μF , 1/1, 0.5 μF , 2/-.

POLYSTYRENE CAPACITORS: 5%, 160V (unencapsulated): 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 5d. 1,000, 1,500, 2,200pF, 6d. 3,300, 4,700, 5,600pF, 7d. 6,800, 8,200, 10,000pF, 8d. 15,000, 22,000pF, 9d. 19,000, 100V (encapsulated): 100, 120, 150, 180, 220, 270, 330, 390, 470, 500, 550, 630, 820pF, 1/3. 1,000, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 4,700, 5,000, 5,600, 6,800, 8,200, 10,000, 12,000, 15,000pF, 1/6. 18,000, 22,000, 27,000, 33,000, 39,000pF, 2/- 0.047, 5,000, 0.056 μF , 2/3. 0.068, 0.032, 0.1 μF , 2/9. 0.12 μF , 3/3. 0.15, 0.18 μF , 3/9. 0.22 μF , 4/9. 0.27, 0.33 μF , 5/- 0.33 μF , 6/6. 0.47, 0.5 μF , 7/6.

JACK PLUGS (Screened): Heavily chromed, $\frac{1}{2}$ in Standard: 2/9 each. Side-entry: 3/3 each. Standard (Unscreened): 2/3 each.

JACK SOCKETS ($\frac{1}{2}$ in Plug): With chrome insert, 2/9 each. Available with: Break/Break, Make/Break, Break/Make, Make/Make contacts.

POTENTIOMETERS (Carbon): Long life, low noise, $\frac{1}{2}$ W at 70°C. $\pm 20\% \leq \pm M$, $\pm 30\% > \pm M$. Body dia., $\frac{1}{2}$ in. Spindle, $\frac{1}{16}$ in. 2/3 each. Linear: 100, 250, 500 ohms, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

SKELETON PRE-SET POTENTIOMETERS (Carbon): Linear: 100, 250, 500 ohms, etc., per decade to 5M.

Miniature: 0.3W at 70°C. $\pm 20\% \leq \pm M$, $\pm 30\% > \pm M$. Horizontal (0.7in \times 0.4in P.C.M.) or Vertical (0.4in \times 0.2in P.C.M.) mounting, 1/- each. Submin. 0.1W at 70°C. $\pm 20\% \leq \pm M$, $\pm 30\% > \pm M$. Horizontal (0.4in \times 0.2in P.C.M.) or Vertical (0.2in \times 0.1in P.C.M.) mounting, 10d each.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/- OC70, OC28, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/- OC139, 5/3. OC25, 7/- OC35, 8/- OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/- 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/- (0.75A): 200 P.I.V., 1/6. 400 P.I.V., 2/- 800 P.I.V., 3/3. (6A): 200 P.I.V., 3/- 400 P.I.V., 4/- 600 P.I.V., 5/- 800 P.I.V., 6/-

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off 5/-. Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/-. DP/ST, 4/6. DP/DT, 5/-

PRINTED CIRCUIT BOARD (Vero). 0.15in Matrix: 3 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 3/3. 5 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 3/11. 3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in, 3/11. 5in \times 3 $\frac{1}{2}$ in, 5/6. 0.1in Matrix: 3 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in, 4/-. 5in \times 2 $\frac{1}{2}$ in, 4/6. 3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in, 4/6. 5in \times 3 $\frac{1}{2}$ in, 5/3.

Send S.A.E. for January, 1969 Catalogue

DUXFORD ELECTRONICS (PE)


97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale & Retail Premises)

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/6

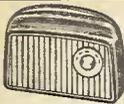

THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques make this simple to build. Sizes: 12" \times 8" \times 3"

MAINS POWER PACK KIT: 9/6 extra.

Price £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.


THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.


Circuit 2/6 FREE WITH PARTS.

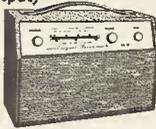

50 WATT AMPLIFIER A.C. MAINS 200-250V

An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls.

Price 27 gns. plus 20/- p. & p.

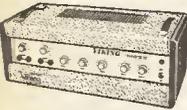

POCKET MULTI-METER

Size 3 $\frac{1}{2}$ \times 2 $\frac{1}{2}$ \times 1 $\frac{1}{2}$ in. Meter size 2 $\frac{1}{2}$ \times 1 $\frac{1}{2}$ in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-160, 0-1000 D.C. current 0-160mA. Resistance 0-100k Ω . Complete with test leads, batteries and full instructions, 49/8. P. & P. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

OUR PRICE
12 for 30/-
Postage 4/6 extra

12 for
21/-
Postage 4/6 extra

G.E.C. 13 amp surface mounting switched sockets in brown. Listed at 6/6.

W. & D. 13 amp flush sockets in green.

CYLDON 4 TRANSISTOR U.H.F. TUNER. BRAND NEW. COMPLETE WITH CIRCUIT DIAGRAM

£2.10.0 + 1/- p. & p.

THE CLASSIC

Controls: Selector switch. Tape speed equalisation switch (3 $\frac{1}{2}$ and 7 $\frac{1}{2}$ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.




Specification: Sensitivity for 10 watt output at 1KHz. Tape head: 5mV (at 3 $\frac{1}{2}$ i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80mV. Radio: 100mV. Aux.: 100mV. Tape/Rec. output: 100mV. Equalisation for each input is correct to within ± 2 dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ± 18 dB at 60Hz, Treble ± 14 dB at 16KHz. Total distortion: (for 10 watt output) $< 1.5\%$. Signal noise: < -60 dB. A.C. mains 200-250V. Size 12 $\frac{1}{2}$ " long, 4 $\frac{1}{2}$ " deep, 2 $\frac{1}{2}$ " high. Teak finished case. Price 8 gns. p. & p. 7/6.

THE RELIANT 10W SOLID STATE HIGH QUALITY AMPLIFIER

Specifications: Output: 10 watts R.M.S. Output impedance: 3 to 4 ohms. Inputs: 1. Xtal mic 10mV; 2. Gram/radio 250mV. Tone controls: Treble control range ± 12 dB at 10KHz; Bass control range ± 18 dB at 100Hz. Frequency response (with tone controls): Minus 3dB points are 20Hz and 40KHz. Signal to noise ratio: better than -60 dB. Transistors: 4 silicon Planar type and 3 Germanium type. Mains input: 220-240V a.c. Size of chassis: 10" \times 3 $\frac{1}{2}$ " \times 2". A.C. Mains, 200-240V. For use with Sd. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested. 8" \times 5" speaker to suit: Price 14/6 plus 1/6 p. & p. Crystal mike to suit: 12/6 plus 1/6 p. & p. PRICE £5.5.0 plus 8/- p. & p. RELIANT MARK II 6 gns + 7/6 p. & p. In teak finished case

THE VIACOUNT

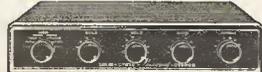Integrated High Fidelity
Transient Stereo Amplifier



SPECIFICATIONS: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner, Tape and Tape Rec. Sensitivity: All inputs 100mV into 1.5M ohm. Frequency response: 40Hz-20KHz ± 2 dB. Tone controls: Tone controls flat (Baxandall type), separate bass and treble controls. Treble 18dB lift and cut at 16KHz. Bass 18dB lift and 25dB cut at 60Hz. Volume controls: Separate for each channel. A.C. Mains input: 200-240V. 50-60Hz. Size 12 $\frac{1}{2}$ \times 6 \times 2 $\frac{1}{2}$ in. in teak finished case. Built and tested.

PRICE 13 $\frac{1}{2}$ gns. Postage & Packing 7/6 extra.

B.S.R. TD2 TAPE DECK

This tape deck takes 5 $\frac{1}{2}$ " spools complete with two-track heads. Size 13 $\frac{1}{2}$ " long by 8 $\frac{1}{2}$ " wide.

£8.19.6 plus 7/6 p. & p.

THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross-over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60c/s. Frequency range 60c/s to 20kc/s. Size 13 $\frac{1}{2}$ " \times 8 $\frac{1}{2}$ " \times 4 $\frac{1}{2}$ ". By famous manufacturer. List price £7. Our price 6/9 plus 5/- p. & p. Similar speaker to the above minus tweeters in 3 & 15 ohms 3/6 + 5/- p. & p.

Goods not despatched outside U.K. Terms C.W.O. All enquiries S.A.E.

RADIO & TV COMPONENTS (ACTON) LTD.

21d High Street · Acton · London W.3

323 Edgware Road · London W.2

ORDERS BY POST TO OUR ACTON ADDRESS PLEASE

THIS circuit is intended for use as the phase splitting stage in high quality push-pull amplifiers and oscilloscopes, or in any application where two equal signals, in anti-phase with each other, are required from a single input signal. The unit is particularly useful in applications where two output signals are required to vary about similar or identical mean d.c. levels. By suitably arranging the output connections of the unit, it may be used to act as an amplifier with a single output, variable in voltage gain between approximately +1 and -1, or it may be used as a frequency doubler for all a.f. and low r.f. signals.

Before delving into the details of this particular circuit, it is necessary to mention briefly some of the more conventional methods of phase-splitting, and the relative merits (or otherwise) of these alternative systems.

BALANCED INVERTER

Fig. 1 shows a single-transistor phase splitter, sometimes known as a balanced inverter. The circuit has equal loads in the emitter and collector lines (R3 and R4), and an output is taken from across each load. Since the currents flowing in the emitter and collector lines are nearly equal, the signals appearing across the two loads will also be nearly equal in amplitude, but opposite in phase. Apart from its simplicity, the circuit has the great advantage that the balance of the two output signals is virtually unaffected by variations in the transistor characteristics, since any change (in frequency response, etc.) will affect both output signals by an equal amount. The major snag of the circuit is that the two outputs are at very different impedance levels, so that severe unbalance may result when the outputs are terminated. Other minor snags are that the two outputs are at totally different mean d.c. levels, that the overall voltage gain between each output and the input is slightly less than unity (as in the case of the emitter follower) and, since the emitter and collector currents are not quite identical, the two outputs are not perfectly balanced.

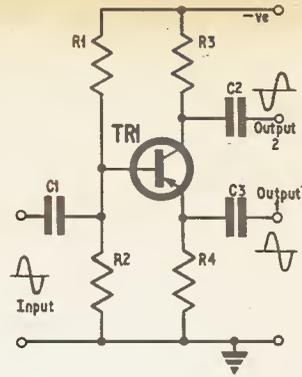


Fig. 1. The balanced inverter phase splitter


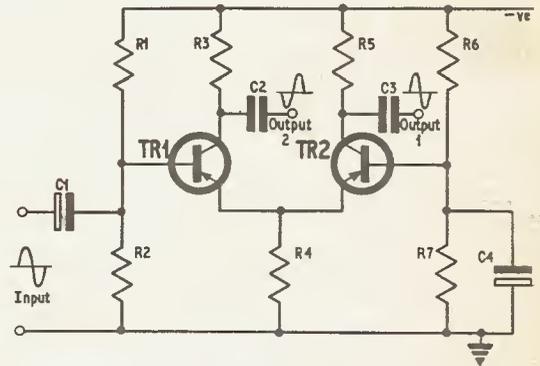


Fig. 2. Long-tailed pair phase splitter

PHASE SPLITTER - FREQUENCY DOUBLER

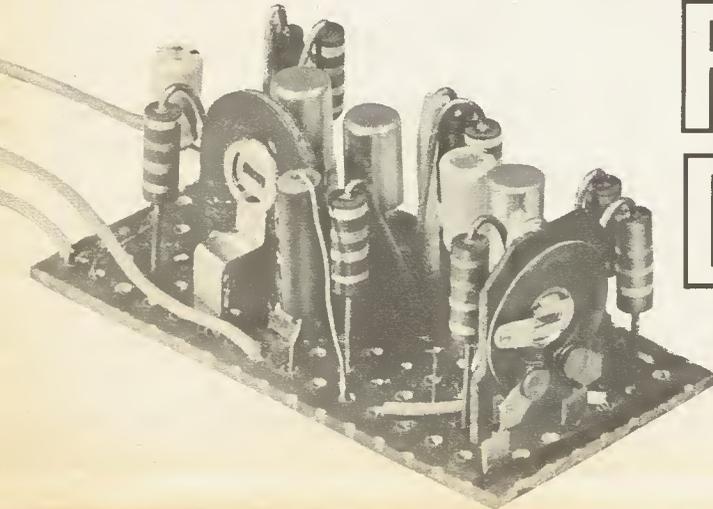

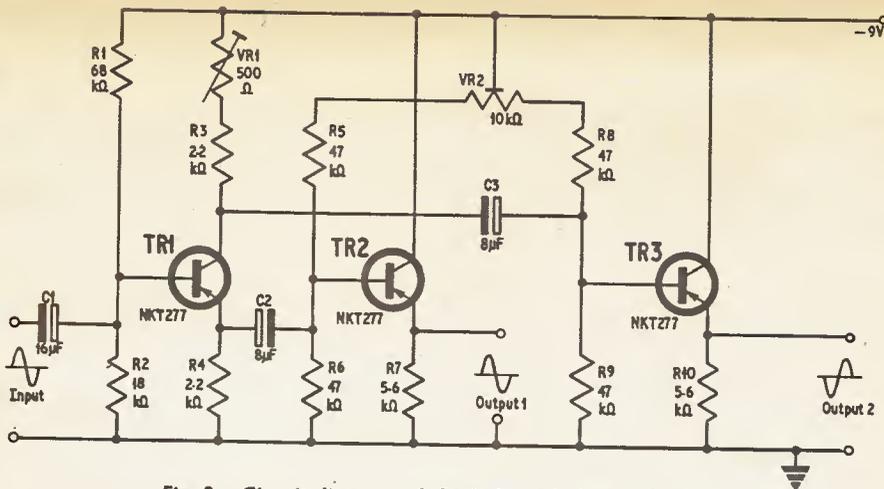


Fig. 3. Circuit diagram of the balanced phase splitter

LONG-TAILED PAIR

Fig. 2 shows an alternative phase-splitter circuit, known as the long-tailed pair or paraphase amplifier, which is widely used. Here, two transistors are used, each of which is wired as a common emitter amplifier, but sharing a common emitter resistor (R4). This common resistor introduces negative feedback to both transistors, with the result that, when an input is fed to TR1 base, both transistors are affected by the signal, and, if TR1 collector becomes more negative TR2 collector will become more positive; the circuit thus acts as a phase-splitter. Theoretically the greater the value of the common emitter resistor (R4), the larger will be the negative feedback and the more nearly balanced will be the two output signals.

This circuit offers two particular advantages: both output signals are at the same impedance, and, if components are suitably selected, both outputs are available at the same mean d.c. level.

The circuit also has the following disadvantages: perfect balance of the output signals is obtained (in theory) only when the emitter resistor is infinitely large,

in which case the voltage gain of the circuit falls to zero. When practical values of emitter resistance are used, voltage gain is obtained and the two outputs may be nearly balanced, but this balance is upset by any difference in the characteristics of the two transistors (such as gain, frequency response, etc.).

BALANCED PHASE SPLITTER

It can be seen that both the above circuits give rather doubtful results. However the circuit shown in Fig. 3, offers a performance superior to either of these alternative circuits. Here, TR1 is wired as a balanced inverter, but the load in the collector circuit is made variable and slightly greater than that in the emitter circuit. Thus, the two output signals can be made *exactly* equal in magnitude by suitably adjusting VR1, the balance condition then being unaffected by the transistor characteristics. The output from TR1 emitter is fed, via C2, to the base of TR2, which is wired as an emitter follower, and the output from TR1 collector is fed, via C3, to the base of TR3, which is also wired as an emitter follower.

COMPONENTS . . .

Resistors

R1	68kΩ	R6	47kΩ
R2	18kΩ	R7	5.6kΩ
R3	2.2kΩ	R8	47kΩ
R4	2.2kΩ	R9	47kΩ
R5	47kΩ	R10	5.6kΩ

All 10%, ¼W carbon

Potentiometers

VR1 500Ω skeleton preset
VR2 10kΩ skeleton preset

Capacitors

C1 16μF elect. 15V C3 8μF elect. 15V
C2 8μF elect. 15V

Transistors

TR1 NKT277 TR2 NKT277 TR3 NKT277

Miscellaneous

Veroboard
Plastic covered wire
Battery terminals
9V battery

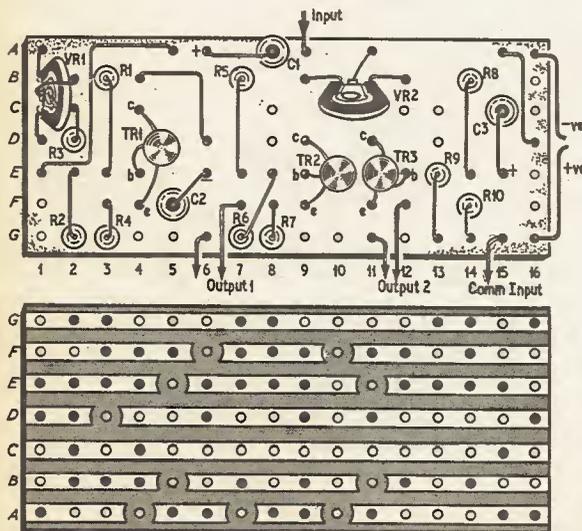


Fig. 4. Layout and wiring of components on the Veroboard

The emitter follower circuit has a high input impedance, a low output impedance, and gives a voltage gain of near unity. In Fig. 3 a pre-set variable resistor, VR2, is made common to the base-bias circuits of each emitter follower, making it possible to set both emitters at exactly the same d.c. level, or to set any required degree of difference in d.c. levels that may be needed.

The two balanced outputs of the unit are at low impedance, output 1 being in phase with the input, and output 2 being in anti-phase.

CONSTRUCTIONAL DETAILS

The unit is very easy to build, and all the details for wiring using Veroboard are shown in Fig. 4. The breaks in the circuit board are made first and then the components and fly-leads are wired in. All components are mounted vertically on the Veroboard panel; layout is in no way critical.

FREQUENCY DOUBLER

The principle by which the unit is made to act as a frequency doubler is best understood with the aid of Fig. 5. Here, it can be seen that a conventional centre-tapped mains transformer and full-wave rectifier are made to act as a frequency doubler, the transformer acting as a phase splitter, while the rectifiers chop off one half of each secondary signal and add the two remaining signals together.

Exactly the same general principle is employed when the phase splitter of Fig. 3 is used as a frequency doubler, this being accomplished by simply shorting the emitters of TR2 and TR3 together after first setting VR2 to give an exact d.c. balance between these two points. In this case, TR1 is used as the phase splitter (in place of the transformer of Fig. 5), TR2 and TR3 act as diodes (in place of the rectifiers), and frequency doubling is obtained. It should be noted, however, that although TR2 and TR3 are used as diodes, they can not be replaced by conventional diodes as correct biasing is essential to circuit operation. Similarly, if the balance of TR2 and TR3 emitters is not correctly set by VR2 before the emitters are shorted together, unbalanced rectification will result.

If the unit is to be built purely as a frequency doubler, the break at "10F" on the Veroboard may be omitted and R7 and R10 replaced by a single 2.7 kilohm resistor. The setting of VR2 for balanced rectification is obtained with the aid of an oscilloscope. It should be noted that, if balanced rectification is to be obtained, the input signal to the unit should be symmetrical, and preferably of sine form.

SINGLE VARIABLE OUTPUT

The unit of Fig. 3 may be adapted to give a single output, the amplitude of which can be varied between approximately +1 and -1. This is done by connecting a 10 kilohm variable resistor across the two output connections, and taking the output of the unit from the moving arm of this variable resistor. It should be noted that this modification does not give an output that is fully variable in phase, but an output that is either in phase or anti-phase with the input, but is variable in amplitude.

SETTING UP PROCEDURE

Before the unit is used, it must be correctly set up. An audio generator and an oscilloscope or a.c. valve voltmeter are necessary for this operation. Connect the generator to the input of the unit, and measure

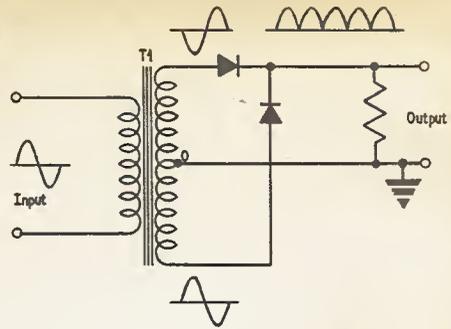


Fig. 5. Principle of the frequency doubler

"output 1" on the oscilloscope or voltmeter, noting the amplitude of the signal. The frequency of the generator is not particularly important, but the input signal should be approximately 1 volt peak to peak in amplitude. Now connect "output 2" to the oscilloscope or voltmeter and adjust VR1 until the amplitude is the same as that of "output 1". Disconnect the generator and the oscilloscope or voltmeter, and connect a d.c. voltmeter between outputs 1 and 2, and adjust VR2 until a null is obtained. The unit is now ready for use.

APPLICATIONS OF THE PHASE SPLITTER

Using the phase-splitter described here in a high quality amplifier, gives perfectly balanced drive and the necessary bias for any following transistors can be obtained by suitably adjusting VR2. Thus, although this circuit uses three transistors and gives unity voltage gain, it virtually eliminates the need for heavy negative feedback (to overcome distortion) in a complete amplifier system, thus enabling higher gain to be used elsewhere.

Similarly, the unit may be used in the amplifier stages of an oscilloscope, to give push-pull X or Y deflection, or, if used in an early part of the amplifier, to enable the trace to be displayed either in phase or in anti-phase with the input signal.


APPLICATIONS OF THE FREQUENCY DOUBLER

As a frequency doubler, the unit may be used, in conjunction with suitable filters, to form the basis of a high quality signal generator. Many generators employ only one oscillator range, additional ranges being added by selecting and filtering harmonics of the fundamental range. This system has the advantage that very pure waveforms can be obtained, and has only one tuning scale requiring calibration, all other scales being multiples of this basic range.

The frequency doubler may also be used to obtain special recording effects, although additional circuitry may be required. "Pinky and Perky" effects can be obtained, for example, by feeding normal voice signals into the input of the unit, and feeding the output to an amplifier or tape recorder via a filter circuit. To cover the full range of voice levels, however, a speech compressor should be used in front of the frequency doubler, and a matched speech expander should be used after the doubler.

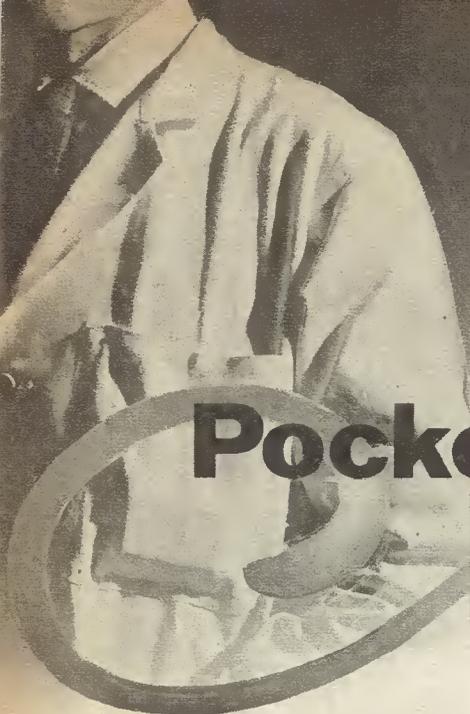Many other uses will, no doubt, occur to the reader.





Pocket RADIATION MONITOR

By D.M. BUSSELL

PERSONAL ALARM FOR WORKERS CLOSELY INVOLVED WITH RADIATION SOURCES

NOVEL COMPACT DESIGN USING MINIATURE GEIGER MULLER TUBE

THIS radioactivity monitor was evolved as a warning device for persons working near units which emit X-rays such as medical X-ray or cobalt units used in hospitals, thickness gauges in industry, or wherever radioactive isotopes are used. It was designed as a personal alarm and not as an accurate measure of beta, gamma or X-ray radiation.

The author has built a small number of these monitors which are giving good service in X-ray and radiotherapy departments of two large General Hospitals. Full cost of this unit will be between £8 10s 0d and £10 maximum, depending on availability of parts. The miniature G.M. tube accounts for £5-£7 of this amount. It may seem an expensive device, however in situations where the need is to be aware of radiation sources it can prove to be a life saver.

The radiation monitor circuit consists basically of four sections: monostable, blocking oscillator, h.t. voltage doubler circuit, and the G.M. tube. See Fig. 2.

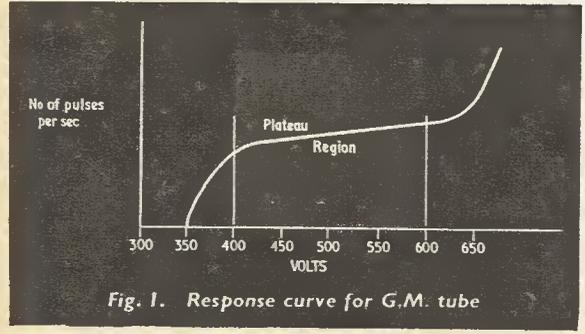


Fig. 1. Response curve for G.M. tube

THE GEIGER MULLER TUBE

An MX151 Geiger Muller tube is employed as the radiation detector; see Fig. 1 as a guide to operating point. The tube becomes sensitive to particles or radiation at around 350 volts, and its normal operating voltage is where the curve tends to flatten; this portion is referred to as the *plateau*. With the tube biased between 400 and 600 volts there is a little change in its sensitivity, i.e. number of discharges per volt applied. It is not advisable to apply a higher voltage than indicated in Fig. 1 as the tube may be destroyed by the discharge which follows the application of voltages above the plateau region.

When a particle of radiation enters the G.M. tube with the correct voltage applied, a controlled, short discharge through the gas in the tube is triggered off, resulting in a negative pulse being produced at the tube anode. This pulse is used to switch on the circuitry, thus producing an audible bleep, a visible neon tube flash and—through the action of the blocking oscillator—replacement or restoration of the h.t. voltage level.

THE MONOSTABLE

The monostable circuitry is in the form of an all-off, complementary transistor circuit. TR1 being a *pn*p transistor is switched on by the negative pulse from the G.M. tube. TR1 when on will also turn on TR2; the latter is an *n*pn transistor and part of its negative going collector voltage is fed back via R3 and C2 to TR1 base, so holding the monostable in the on condition, until the charge has leaked away from C2 via the input circuitry. The negative square wave on TR2 collector is used to supply the base current for the TR3 blocking oscillator circuit, which is then turned on.

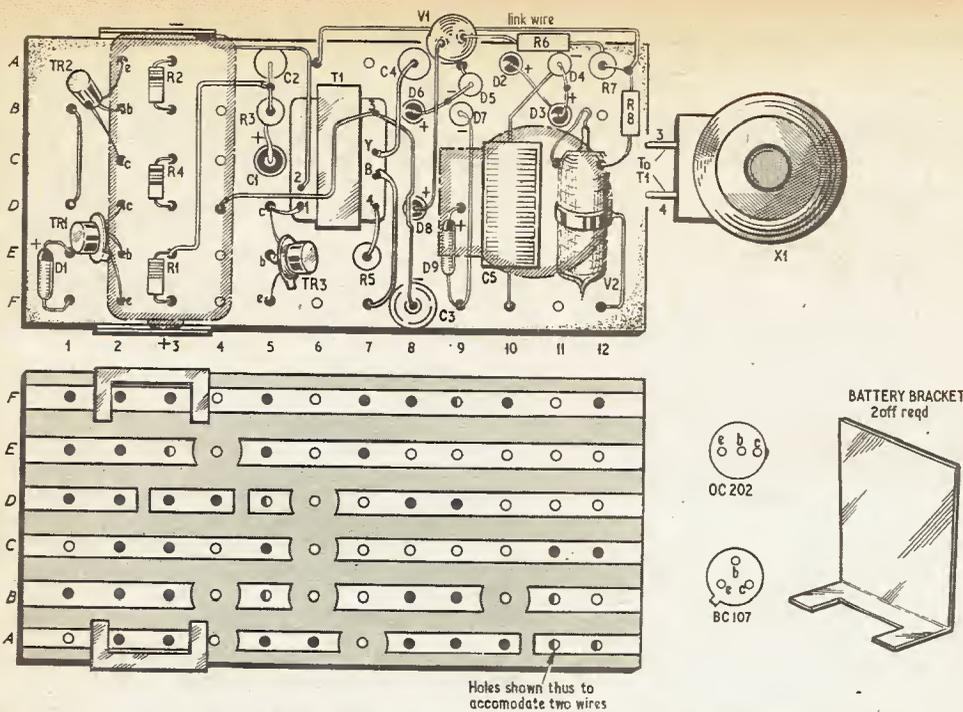


Fig. 3. Layout and wiring of the board. The battery and microphone are positioned as indicated by the dotted lines, see text. The battery clips are made from strips of brass or similar material

COMPONENTS . . .

Resistors

R1 1M Ω	R4 2.2k Ω	R7 4.7M Ω
R2 47k Ω	R5 390 Ω	R8 10M Ω
R3 47k Ω	R6 1M Ω	
All $\pm 10\%$, $\frac{1}{4}$ W carbon		

Capacitors

C1 2 μ F elect. 6V
C2 1,000pF paper 1kV*
C3 25 μ F elect. 6V
C4 0.01 μ F paper 400V
C5 0.047 μ F paper 630V*

* Wima (C.E.S. Ltd., P.O. Box 11, Cambridge)

Diodes

D1 EC401 (Fairchild)
D2, 3, 4 EC401 (3 off)
D5, 6, 7 EC401 (3 off)
D8, 9 EC401 (2 off)

Transistors

TR1 OC202 (pnp silicon)
TR2 BC107 (nnp silicon)
TR3 OC202 (pnp silicon)

Miscellaneous

V1 Neon, wire-ended (Radiospares)
V2 G.M. tube MX151 (Mullard)
T1 Transformer: primary 6V; secondary 400V (Parmeko L1321/4)
X1 Earpiece 30-100 Ω , miniature magnetic
BY1 5.3V battery. (Mallory TR114); or (Deac 225DK) (3 off)
Veroboard $1\frac{1}{2}$ in \times $2\frac{1}{8}$ in. Plastics box $1\frac{7}{8}$ in \times $2\frac{3}{8}$ in \times $1\frac{1}{4}$ in
Sponge rubber pad. Material for battery clips

centre anode pin or overheat the tube; use the anode clip supplied and only solder the clip into the circuit with the tube unplugged.

TESTING THE MONITOR

On completion of construction very carefully check the wiring with the circuit diagram. Check also the polarity of C1, C3, and the diodes. The h.t. should be monitored with an electrostatic voltmeter—but if this is not available the flashing of the neon will indicate voltages of over 600 or over.

The monitor may be made operative by connecting and disconnecting the 5 volt supply until "tweets" are heard in the earpiece and the neon flashes. Alternatively, a 10 kilohm resistor may temporary be connected between terminal 2 and 4 of T1. The unit is now ready for a radiation test. The most handy source is a luminous watch dial which will usually give tweets every two or three seconds when the dial is held as near as possible to the tube.

The neon visual indicator should light only for the duration of the audible "tweet". If it stays lit longer and there is no radiation response, the D8 and D9 EC401 diodes may have too low a reverse breakdown voltage and a third series diode should be tried. The neon may not light if D8 and D9 have too high a reverse breakdown; in this case one or both diodes should be substituted. (In the author's experience this condition only arose in about one in ten diodes, and as their current price is near 3s it is not a bad risk.)

No battery decoupling is used and when the battery is nearing the end of its life the tweet becomes much shorter with a clucking sound. This indicates a change is soon required.



SOLDER ON WITH



CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 32/6**

If you want the best in soldering, Antex irons are for you. Pin point precision, fingertip control, interchangeable bits that slide over the elements and do not stick, sharp heat at the tip, reliable elements and full availability of spares. World-wide users, both enthusiasts and professionals solder with Antex. It's time you joined them.

Antex soldering irons are stocked by quality electrical dealers, or order direct from Antex by sending Cash. A free colour catalogue will be supplied on request.



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon
Telephone: Plymouth 67377/8. Telex 45296. Giro No.258 1000



Model CN 240/2
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

31/-

Complete precision soldering kit



This kit—in a rigid plastic "tool-box" — contains everything you need for precision soldering.

- Model CN 15 watts miniature iron, fitted 3/16" bit.
- Interchangeable spare bits 3/32", 1/8", 3/16".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron
- Space for stowage of lead and plug

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash to Antex. **49/6**



G 18 watts. Ideal for miniature work on production lines. Interchangeable spare bits, 3/32", 1/8", 3/16", and 1/4". For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16". For 240, 220, 110 or 24 volts. from 35/-



ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4". Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. from 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" Very high temperature iron. Available for 240, 220, 110, 24 or 20 volts. from 42/6 Spare bits and elements for all models and voltages immediately available from stock.

- Please send me the Antex colour catalogue
 Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....
.....

To: Antex, Mayflower House, Plymouth, Devon

I enclose cheque/P.O./cash value

NAME

ADDRESS

P.E.4 Telephone:

A.P.T. STABILISED P.S.U. MODEL 515/3

will regulate from 0-500 v. at 500 mA also current regulated from 10 mA to 350 mA in 17 ranges, these units are in as new condition and perfect working order, save pounds, on this one price, P.P. 20/-, £45.00

HIGH QUALITY SWITCHING RELAYS

Ericsson miniature single pole changeover type for high speed operation, 720 ohms 6-9V, current drain at 6V 8MA, "hermetically sealed," normal price over 60/- OUR PRICE 17/6 ea. p.p. 1/6

MINIATURE RELAY of good quality. Suitable for many applications, model control circuits, alarm systems, etc. 6-9V 300 ohms 2 pole C/O + I MAKE. Contained in grey enamel case, weight only 30g—price 9/6 as above but 36-50V. 1500 ohms coil 4 C/O 8/6 ea. p.p. 6d.

LUCAS HORN AND OVERDRIVE RELAYS

Suitable for many applications for 12V operation. Note our price only 7/6 ea. p.p. 6d.

MINIATURE RECHARGEABLE L.A. BATTERIES

Ideally suitable for model boats, portable T.V.'s, etc., these batteries are of the non-spillable type rated at 12V 4 A.H. Size only 4in square fully sealed but not dry charged, complete with instructions, brand new and guaranteed only 45/- ea. p.p. 2/6

BECKMAN PRECISION POTENTIOMETERS "TEN TURN"

Value	Tol.	Model	Price
2K ohms	0.5 LIN	SA1101	45/- post free
10K ohms	0.05 LIN	"A" S	50/- post free
50K ohms	0.1 LIN	A	45/- post free
30K ohms	0.5	A	45/- post free
100K + 100K		A	60/- post free

The above HELICALS have 1/2in shaft and are rated at 10 watts.

MINIATURE HELICALS—TEN TURN

25K ohms	0.5 LIN	SA1327	30/- post free
5K ohms	0.5 LIN	500	35/- post free

LEDEX ROTARY SOLENOID SWITCHES

Suitable for all types of remote circuit selection and a variety of switching operations—brand new stocks—no waiting—off-the-shelf deliveries of the following types:

- (1) Miniature type—1 pole 7 positions 5 banks 1 1/2in dia. wafers for flange mounting. Operating voltage, 12V d.c. 50/-
- (2) Standard type as above, 1 pole 2 positions with long shaft to enable user to build up wafers to suit requirements. Voltage 48 d.c. 40/-


A.E.I. HIGHLY STABILISED P.S.U.

3-30V d.c. at 2A. Type R2240, this power supply is ideally suitable for semiconductor work, the unit has a very high specification and is fully transistorised and infinitely variable throughout its range. Supplied brand new boxed. List price £73. OUR PRICE £22.10.0 P. & P. 15/-



"DALE PRODUCTS INC." HEAT SINK RESISTORS

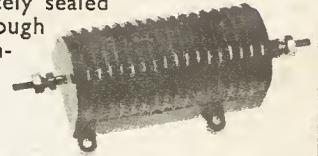These high grade resistors are completely sealed against moisture and will withstand rough treatment without failure, this non-inductive resistor lends itself to many applications and is ideal for dummy loads in power amplifiers, etc. in the following values:



15 ohms, 250 W, 45/-; 810 ohms, 200 W, 45/-; 200 ohms, 50 W, 7/6


DOUBLE BEAM OSCILLOSCOPE TYPE 13A

Bandwidth 2c/s—5Mc/s. The above scope has excellent specifications and is ideally suitable for radio and T.V. engineers. This well-known scope has sealed "C" core transformers and is renowned for reliability. Supplied in first class condition with leads, graticule, instructions and in guaranteed working order.

EXCELLENT VALUE AT £22.10.0 P. & P. 25/-

COSSOR DOUBLE BEAM OSCILLOSCOPE TYPE 1049 MK. III

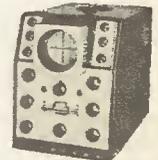This well-known scope is suitable for all D.C. applications, medical work, servo systems, amplifiers, etc. Supplied in excellent guaranteed condition. List price over £140. Our price £35 P. & P. 30/-



B40 "WORLD WIDE" COMMUNICATIONS RECEIVER

Manufactured by Murphy Ltd. for the British Navy, these high quality receivers have been carefully checked and serviced, and EF91 valves fitted in RF section. Specification: 10 Valve, 5 BAND, covers from 650Kc/s—30mc/s continuously. IF frequency 500kc/s 2RF stages. 3IF stages band pass filter, Xtal calibrator, B.F.O. Monitor Spk. 2 phone outlets and many other facilities, size 19 x 16 x 13ins. Weight 83lbs. OUR PRICE £27.10.0 carriage 30/-

★ STAR OFFERS — BRAND NEW AT SURPLUS PRICES ★

★ PORTABLE WHEATSTONE BRIDGE MODEL 7009

Calibrated in 5 ranges from 0.05 to 50K ohms. Miniature Galvanometer scale 10.0-10.0. Slidewire 0.5 to 5.0. Case moulded plastic. All ranges are switched, internal source 4V battery supplied brand new at


★ £9.19.6 P. & P. 4/6



★ HIGH QUALITY DECADE CAPACITANCE BOX TYPE R7004

4 individual ranges from 0.00002µF to 1µF in 0.00002µF steps. Accuracy 0.05%. Frequency range 40c/s to 10kc/s. Supplied brand new in hammer finish stove enamel at the much reduced price of


★ £22.10.10 P. & P. 7/6

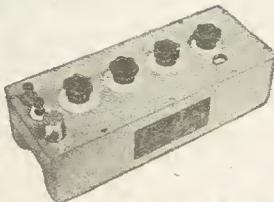

★ HIGH VALUE RESISTANCE BOX TYPE 7003

Range 0.01 to 11.10 Megohm. Accuracy 0.05%. Power rating 0.1 watt per step. Case hammer finish stove enamel.

★ Price £22.10.0

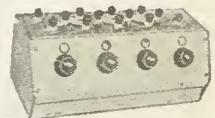

★ PORTABLE MULTIRANGE METER TYPE R7020

20K ohms. per volt. D.C. current 0—Micro Amps through to 12 Amps in 6 ranges.


D.C. Volts 0-6000V in 5 ranges.

A.C. current 0-1.2 fully switched.

A.C. volts 0-6000V. Resistance 0-3 Megohms.

These are very robust high quality meters with an easy-read scale. Supplied with 2 voltage dividers, spare rectifiers, and all leads contained in hinged lid at only


★ £12.19.6 BRAND NEW and GUARANTEED

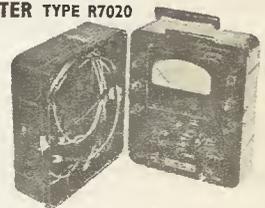

P. F. RALFE RADIO

10 CHAPEL ST., LONDON, N.W.1

Tel. 01-723 8753

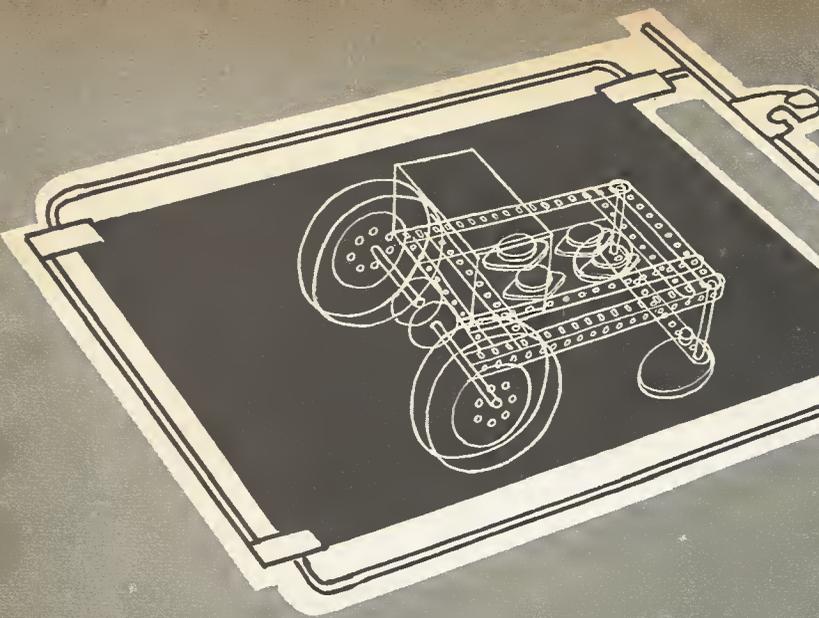

EMMA

ELECTRONIC MIME MOBILE ANIMAL

By G.C.BROWN
M.S.H.A.A. A.M.R.S.H.

PART one of EMMA detailed the theory and wiring of the complete reflex functions board. This month we describe the "muscle" control and load monitoring circuit and board, the power supply wiring and the mechanical details of EMMA's "skeleton". The block diagram for the electronic parts was shown in Fig. 1 (last month), enclosed by a separate broken line, designated "Board No. 2".

"MUSCLE" CONTROL

The "muscle" (motor) control circuits (Fig. 5) consist of two channels providing power switching for the port and starboard motors. Each channel comprises a pair of OC35 power transistors driven by a complementary input arrangement. Due to their inexpensiveness, common types of power transistors have been used as an alternative to more exotic miniature devices connected in full complementary format. Although larger, the cheaper versions have the advantage that with the small current demands made upon them additional heat sinks are not required.

The motor in each channel is connected between the centre-point of its associated power transistors and, via R67, the common point. With either input Mc1 or Mc2 at ground level the input transistors will be effectively non-conducting and the motors will be switched-off. A positive level on Mc1, however, will turn-on TR26 causing TR28 to conduct and hence drive the starboard motor forward. Taking Mc1, negative will turn off TR26 and switch on TR25 thus causing TR27 to conduct and the motor to drive in the opposite direction. The channel controlling the port motor is operated in an identical fashion.

Despite the employment of separate power supplies, some interference resulting from motor "hash" inevitably reaches the reflex functions board. In an attempt to minimise this complaint and make the motor control system a little more sanitary, two 0.1 μ F capacitors (C17 and C18) are wired in parallel with the motors.

LOAD SENSING CIRCUIT

During forward motion of EMMA, the joint current demands made by the two motors are monitored by transistor TR33 (Fig. 5) which under no-load conditions

is arranged to be just cut-off. Any mechanical load applied to either or both motors will increase the current drawn through R67 and therefore take the emitter of TR33 more positive causing the transistor to conduct. The collector level of TR33 under these conditions will thus tend to go more and more positive with increasing loads and be an indication of the degree of loading. Potentiometer VR3 sets the level for no-load conditions and controls the sensitivity of the circuit.

Resistor R67 can be fabricated from easily obtainable electric-fuse element wire. A few turns of this should be cut off and preferably measured on an ohmmeter for correct value. When the resistance is the correct value, the wire ends should be filed clean to facilitate soldering. R67 must obviously be kept low in value because the motors themselves only have a resistance of about 3 ohms.

CIRCUIT BOARD DETAILS

Illustrations of the "muscle" control board are given in Figs. 6a and b. The board should be drilled as indicated to accommodate the four power transistors. No heat sinks are required because the transistors are not called upon to dissipate any over-large currents.

The reflex functions board, which was detailed last month, is firmly mounted by way of 18 s.w.g. wire soldered between its four corners and the corners of the "muscle" control board. Such an arrangement lends itself well to instant modification and occasional "surgery", additional boards being freely accommodated in minutes.

POWER SUPPLIES

The "animal" requires two power supplies, termed "A" and "B". Two sources of supply are used in preference to one because of the demand for large de-coupling capacitors with a single supply. In fact the additional supply takes up less space than would the capacitors. Supply "A" feeds the whole of the reflex circuitry and consists of a pair of type 1289 batteries.

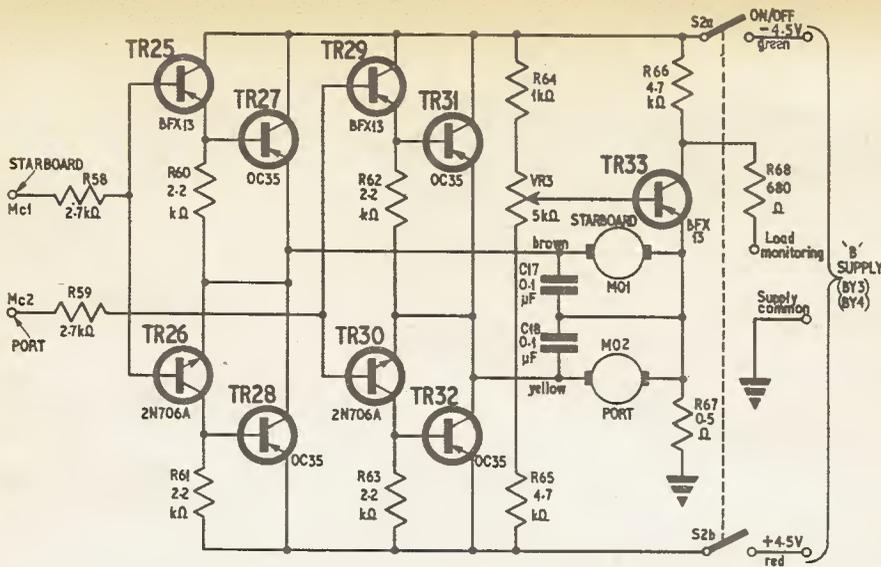


Fig. 5. Electronic mime mobile animal "EMMA". Circuit diagram of the motor control and load sensing circuits


Supply "B" feeds the motor control circuit and comprises a type 126 battery for forward drive (a heavy duty battery is used here because EMMA is more frequently in this mode) and a type 1289 battery for reverse drive. In both cases the supplies are connected so as to form 4.5V—0—4.5V sources (see Fig. 7), the zero point being common to "A" and "B".

CHASSIS DETAILS

In order to make the construction problem minimal, Meccano components were chosen for the model. The chassis which is of extremely simple construction is shown in Figs. 8, 9 and 10 and essentially comprises a rigid skeleton plinth, formed from two main

longitudinal angle girders connected together by five cross members. The cross members in addition to lending strength to the chassis also carry the motors, motor control board, and override switches S1 and S2, the switches being mounted between two chassis members and thereby dispensing with the need for drilling.

Downward extensions at the front and rear of the plinth support the castors and axles respectively. At the rear of EMMA this is constituted by four double-angle strips bolted between the plinth and a tie-strip. The frontal (anterior) end comprises a pair of screwed rods running between the plinth and a lower cross member. This member and the plinth are separated by

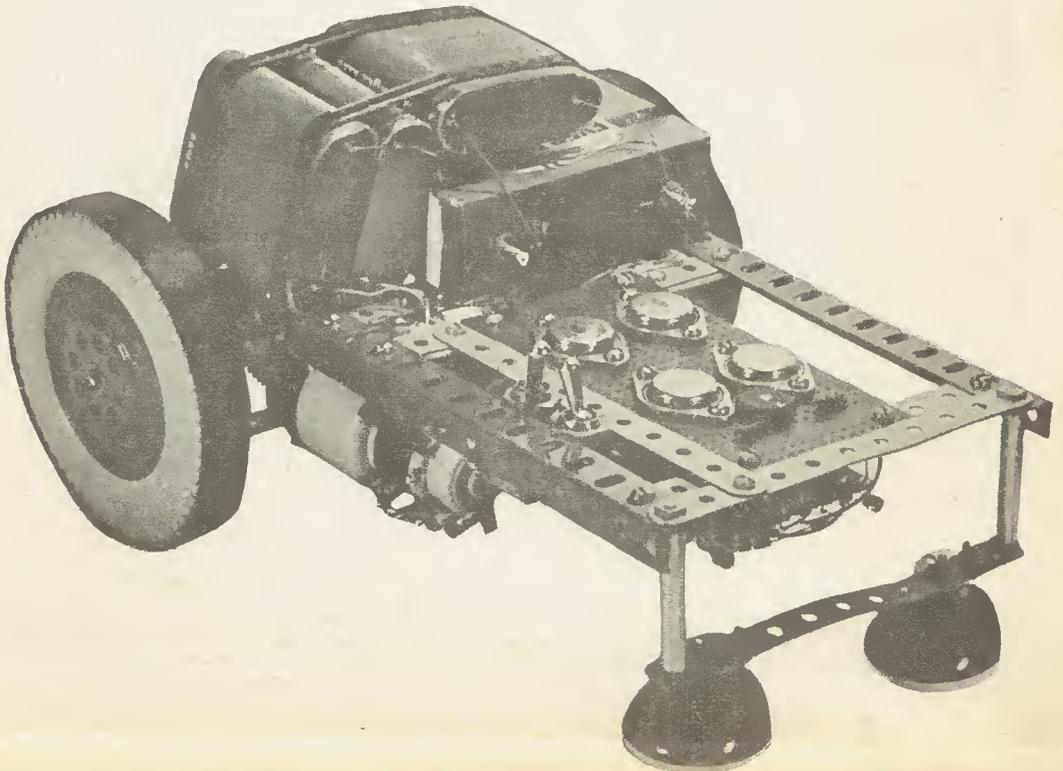

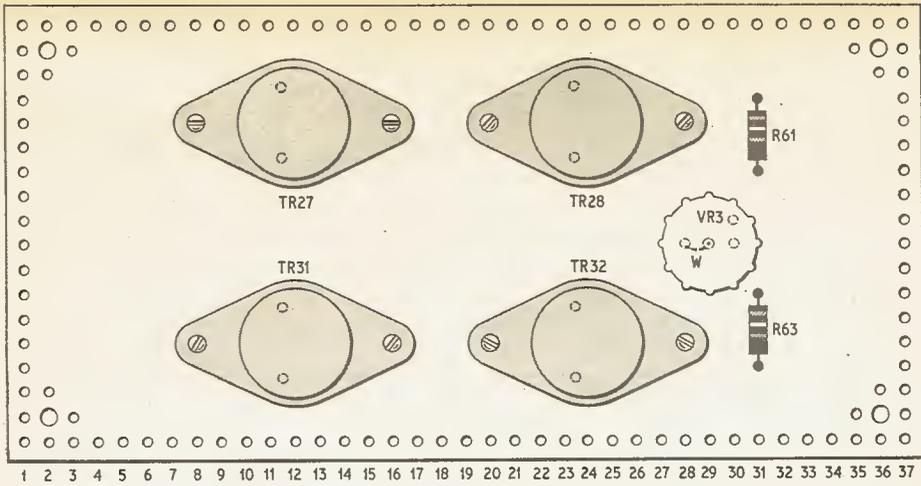


Fig. 6a. Top view of the motor control board. The board should be drilled to accommodate the OC35 mounting screws and the base and emitter pins. Mounting holes for the board are made at each corner to line up with the Meccano mounting strips

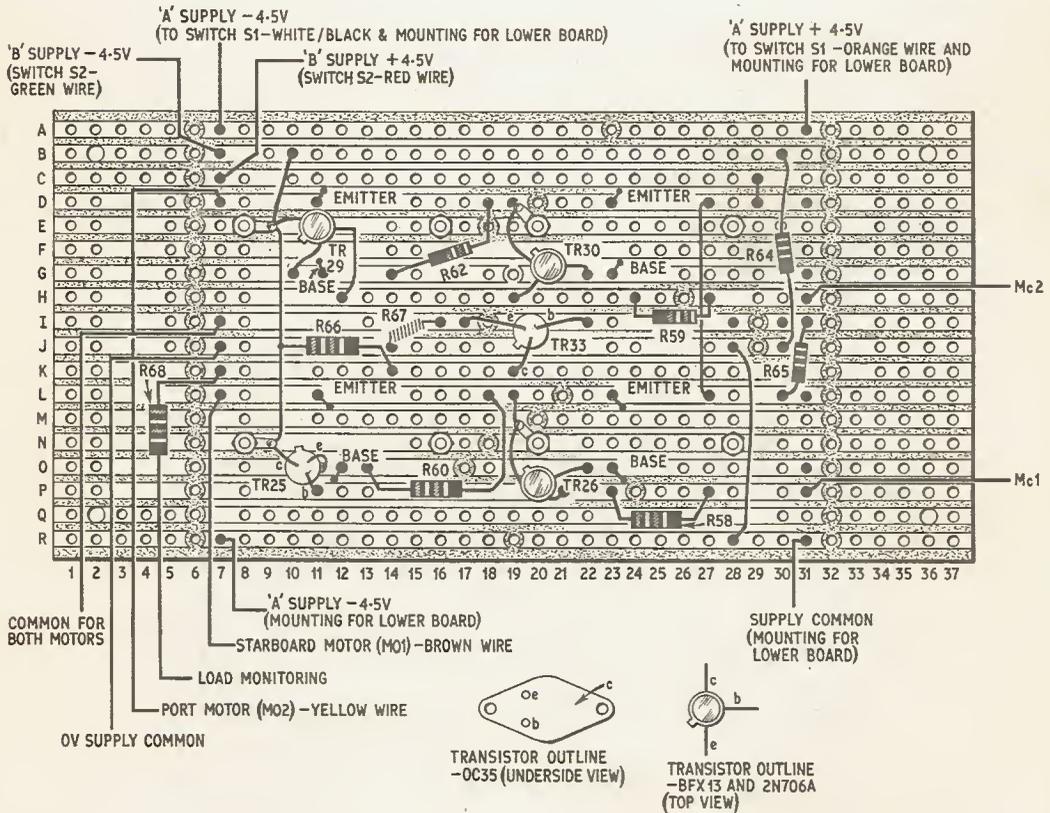


Fig. 6b. Underside view of the Veroboard showing component wiring and breaks in the circuit strips. Care should be taken that the emitter and base leads from the OC35's do not short with adjacent copper strips. All link wires should be of the plastic covered type. Transistors TR25 and TR33, which are mounted upside down, should be kept well clear of the copper strips

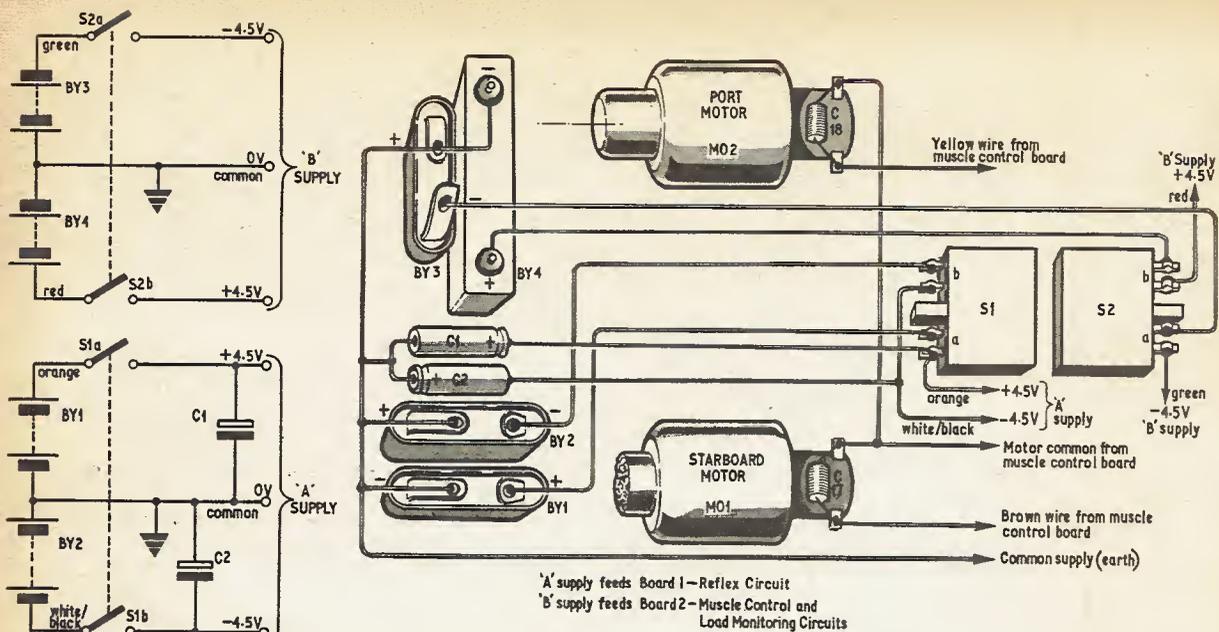


Fig. 7. Circuit and wiring of the two power supplies and motors. Capacitors C1 and C2 were shown in the main circuit diagram (Fig. 2) last month

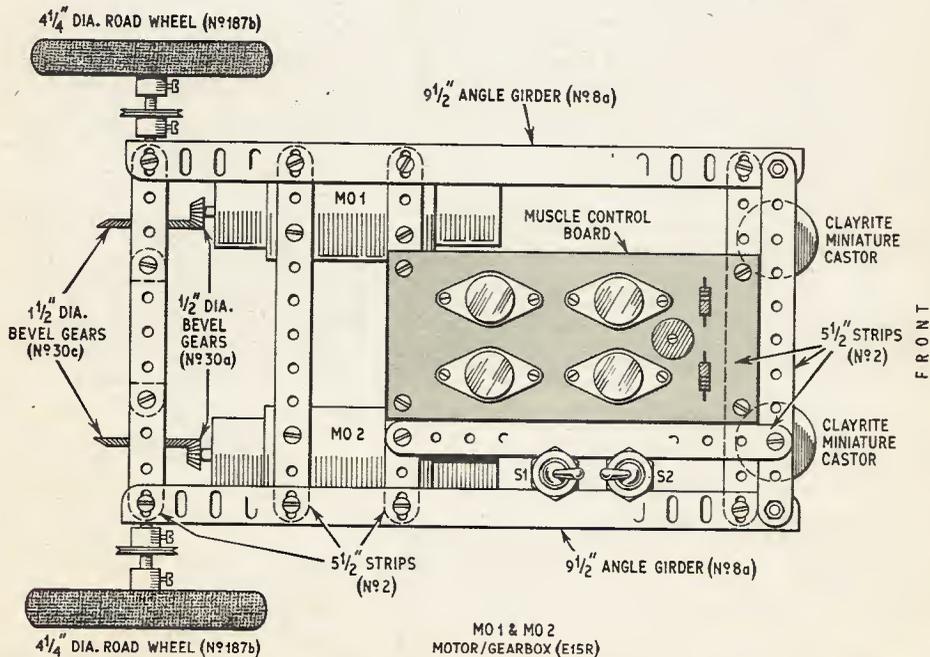


Fig. 8. Top view of EMMA's skeleton showing chassis construction and component mounting positions. Batteries BY1, 2, 3 and 4 occupy the rear end of the skeleton, above the motors (see photos)

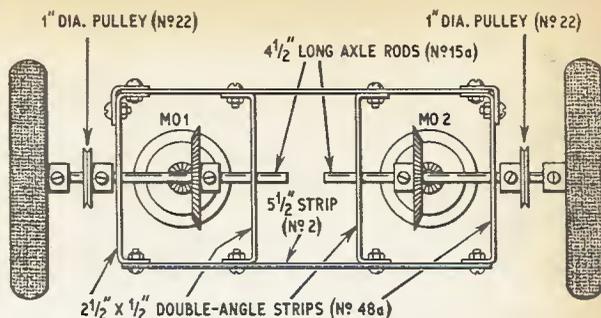
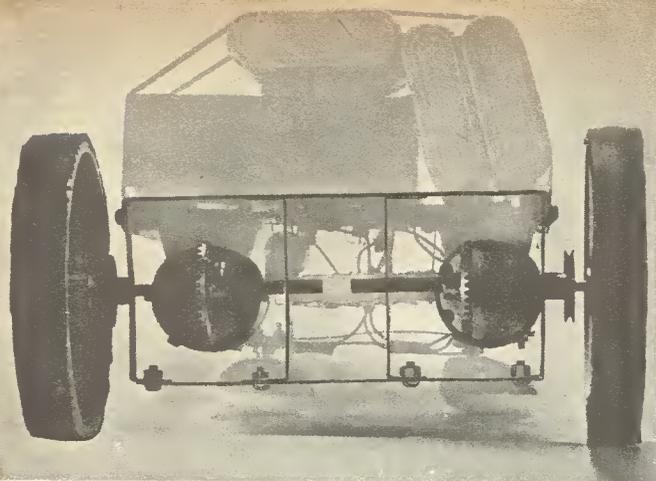


Fig. 9. Rear view of the chassis showing the drive arrangements

tubular pillars which slide over the screwed rods.

Space for the batteries is provided above and just rear of the motor mounting position. For easy access the batteries can be secured in place by way of elastic bands or plastics strips attached to either side of the chassis.

FINAL-DRIVE ARRANGEMENT

EMMA's motive power is derived from a pair of Meccano "Power Drive" motor/gearbox units; these are located port and starboard on the chassis and each is secured in position by four 4B.A. nuts and bolts. The gearboxes, which are of the epicyclic type, have provision for the selection of several gear ratios; in the model the lowest (60:1) is used. Output from the gearboxes is taken via bevel gears which provide a further 3:1 reduction, thus giving an overall figure of 180:1 between the motors and road wheels.

The final-drive axles which run through the centre holes of the double-angle strips each carry a road wheel, a large bevel gear, and a pulley. The pulley, properly adjusted, serves the purpose of reducing end-float and ensures correct meshing of the gears.

INTERCONNECTION WIRING

Wiring between the boards, switches, motors and power supplies is shown in Fig. 7. It must be emphasised that motor leads should be kept as short as possible and maintained clear of the reflex functions board and its wiring. The "A" and "B" power supply leads should not run in the same cableform and must have quite separate routes to avoid coupling motor "hash" into the reflex functions circuits.

SYSTEMS CHECK-OUT

When the circuit boards have been completed they should be carefully examined to ensure that components are correctly connected and no dry joints exist. Check too that there are no accidental solder bridge-overs between adjacent conductors.

Prior to check-out of the complete system, the inputs to the motor control board (Mc1 and Mc2) should be temporarily disconnected. At this time the "animal" is best raised off its wheels so that they are free to turn during the checks which follow.

MOTOR CONTROL AND LOAD SENSING

Connect both supplies and switch S2 on. Temporarily connect inputs Mc1 and Mc2 together and take this common input to zero (ground); under these

conditions neither motor should run. Reconnect the common input to the positive supply rail; both motors should now run in the forward direction—if this is not the case, reverse the connections to the offending motor(s). Now disconnect the common input from positive and connect to the negative rail, ensuring both motors now run in reverse.

COMPONENTS . . .

MOTOR CONTROL

Resistors

R58	2.7k Ω	R64	1k Ω
R59	2.7k Ω	R65	4.7k Ω
R60	2.2k Ω	R66	4.7k Ω
R61	2.2k Ω	R67	0.5 Ω (see text)
R62	2.2k Ω	R68	680 Ω
R63	2.2k Ω		

Capacitors

C17, C18 0.1 μ F polyester 150V

Transistors

TR25	BFX13 or BFX12	TR30	2N706A
TR26	2N706A	TR31	OC35
TR27	OC35	TR32	OC35
TR28	OC35	TR33	BFX13 or BFX12
TR29	BFX13 or BFX12		

Miscellaneous

VR1 5k Ω min
 MO1 Meccano "Power Drive" motor/gearbox
 MO2 Meccano "Power Drive" motor/gearbox
 S2 double pole on/off toggle switch
 BY1, 2, 3 type 1289, 4.5V batteries
 BY4 type 126, 4.5V battery
 Veroboard 5 $\frac{3}{4}$ in \times 2 $\frac{3}{4}$ in (0.15in pitch)
 22 s.w.g. plastic covered wire

MECHANICAL

Chassis Components

No. 2 strips (8 off)
 No. 8a angle girders (2 off)
 No. 37a nuts (4 off)
 No. 48a double angle strips (4 off)
 No. 80 screwed rods (2 off)
 2in \times $\frac{1}{4}$ in dia. dural pillars (2 off)
 4B.A. and 6B.A. fixings

Drive Components

No. 15a axle rods (2 off)
 No. 22 pulleys (2 off)
 No. 30a bevel gears (2 off)
 No. 30c bevel gears (2 off)
 No. 187b road wheels (2 off)
 Miniature slipper castors (Clayrite, 2 off)

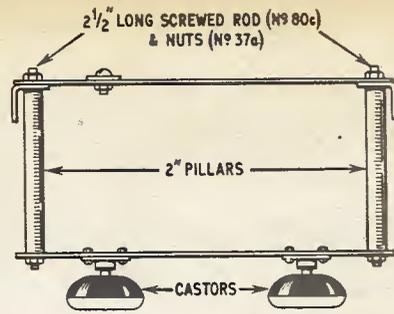
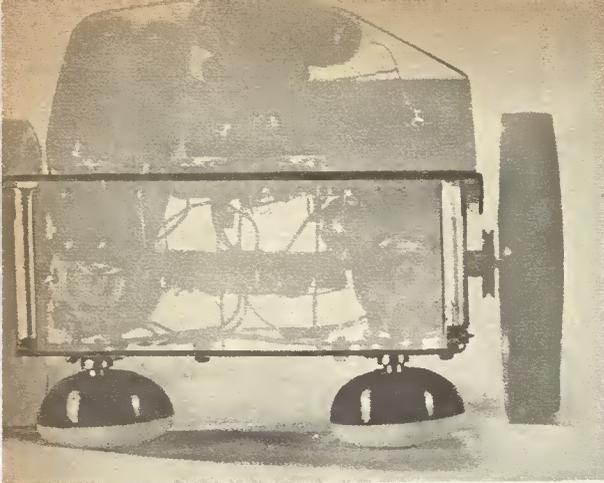


Fig. 10. View from the front of EMMA, with circuit boards removed, showing the castor mountings

Reconnect the common input (Mc1 and Mc2) to the positive rail and connect a voltmeter between the negative supply point and the collector of TR33. Adjust VR3 for zero indication under no-load conditions. Now gently load both motors, by slowing the road wheels, and ensure that the indicated voltage increases with increasing load. Disconnect the common input, separate Mc1 and Mc2 and return them to their normal connections with the reflex functions board. Switch S1 on.

LOAD THRESHOLD AND AVOIDANCE SYSTEM

Connect the voltmeter between the negative rail and the collector of TR18. Adjust VR2 so that the Schmitt fires at a point consistent with moderate loading; the circuit will fire after a short delay due to the transient damping.


During the load threshold checks one can simultaneously establish that the avoidance system is functioning correctly—i.e. that with application of loads exceeding the set threshold the motors reverse their direction of rotation and that one or other continues to reverse for a further period prior to resumption of the normal forward mode. Remember that there should be obvious randomness as to which motor runs-on in reverse. If not, adjust VR1 a fraction until some degree of randomness is present.

STEERING SELECTION AND FINAL CHECKS

Place EMMA on the floor and ensure that the random function also manifests itself in the forward mode of operation. EMMA should quite unpredictably stop, start and turn right or left. During encounters with various obstacles, EMMA should back and turn to commence a new, more favourable course. Finally,

shine a light onto EMMA's photo-sensors to ensure that she turns away and then resumes her previous mode.

Although crude compared with some of the most simple living animals, EMMA demonstrates in a quite striking way that electronics can be used to model a few of the basic reflexes. In a later article EMMA will "fill-out" her structure with a learning faculty; in the meantime however the constructor will have his hands full with a "pet" running around the house that requires little exercise and lives a lifetime—provided the battery manufacturers stay in business! ★

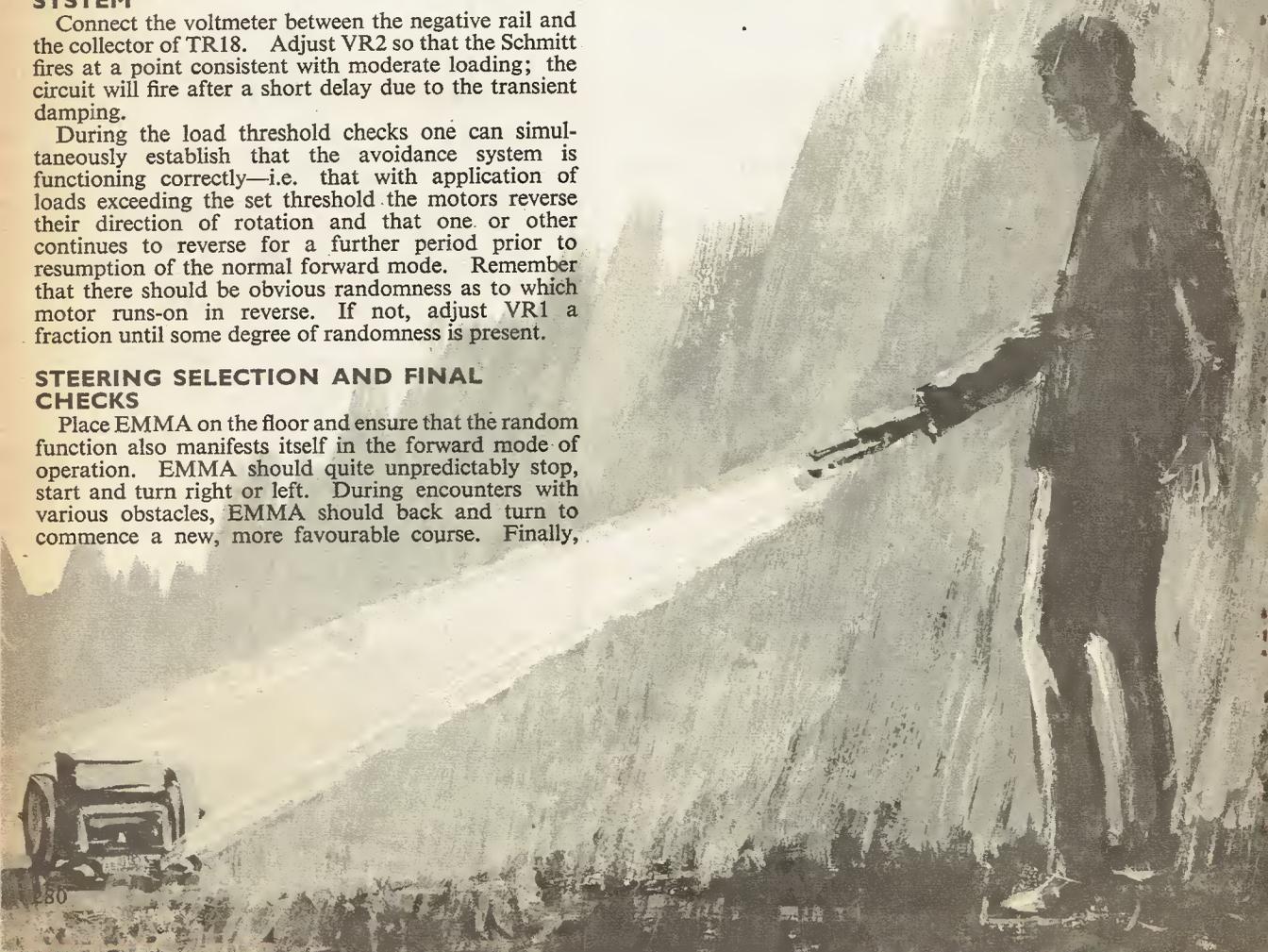

A unijunction circuit for modern cars fitted with permanent magnet wiper motors

INTERRUPTED SCREENWIPER CONTROL

By C.J. MILLS

In our October issue we published a "Vari Windscreen Wiper" control; this control was designed for use on any car having self parking wipers. We have since discovered that many modern cars are now fitted with permanent magnet wiper motors which have to be shorted to stop them. The circuit diagram of the latest wipers is shown in Fig. 1; in this case the parking switch is a change over type which disconnects the supply and short circuits the permanent magnet motor to stop it in the parking position; the "Vari Wiper" (October issue) cannot be used with these motors.

This article describes a circuit which is designed for the modern permanent magnet type of wiper and provides power to the motor to move it from the parking position; the motor will then continue to run until the wipers return to the parking position. After a controllable time interval another pulse is applied to the motor and the cycle repeats itself.

CIRCUIT DESCRIPTION

The circuit shown in Fig. 2 uses a unijunction, a transistor and a relay instead of the thyristor used in our previous article. The circuit works as follows: when the delay unit is switched on the 80 μ F capacitor (C1) charges up through diode D1 and control resistance R2 and VR1 until the unijunction trigger voltage is reached. When the unijunction is triggered its voltage drops, reverse biasing the diode and producing a square wave voltage output at the unijunction base B1. The duration of this square wave is controlled by the discharge time of capacitor C1 through the 5.6 kilohm resistor (R1). The voltage at B1 switches on the transistor and turns the relay on long enough to start the motor and drive it beyond the parking position. The parking switch now completes the motor circuit and breaks the control circuit allowing capacitor C1 to discharge through R1 until the parking position is again reached when the cycle repeats.

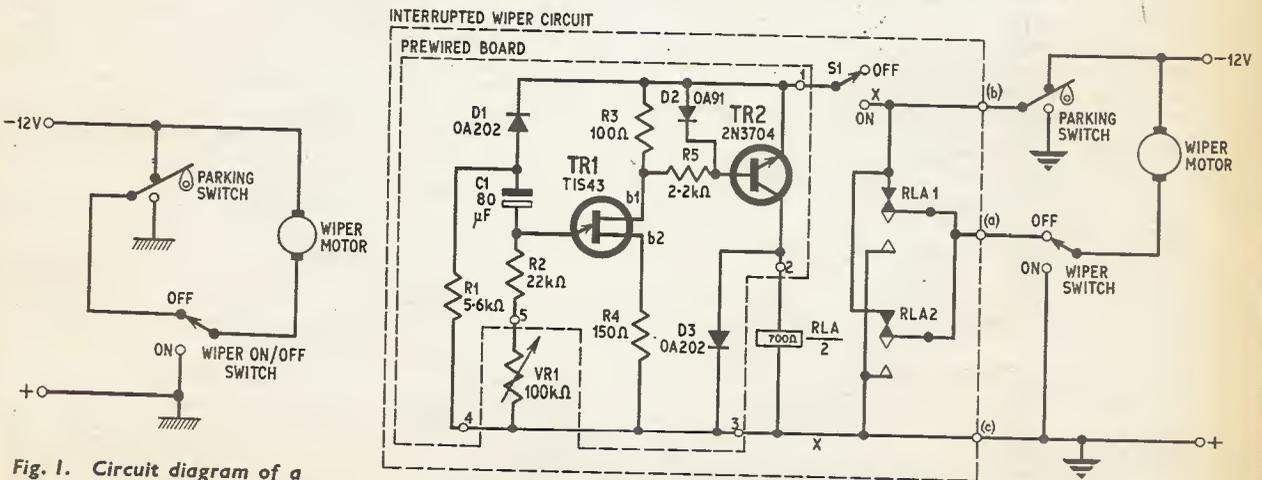


Fig. 1. Circuit diagram of a modern screenwiper using a permanent magnet motor

Fig. 2. Circuit diagram of the interrupted screenwiper control. Points a, b and c show connections to the car wiring

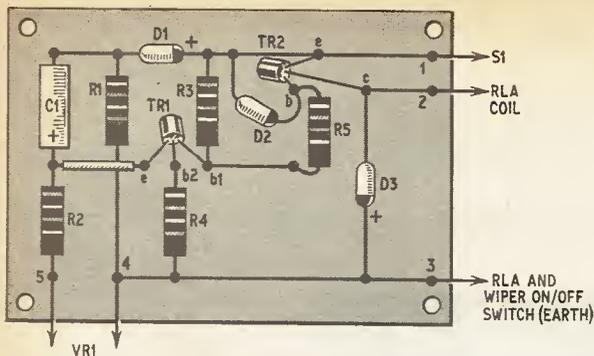


Fig. 3. Wiring diagram of the component-board

COMPONENTS . . .

Resistors

R1 5.6k Ω	R3 100 Ω	R5 2.2k Ω
R2 22k Ω	R4 150 Ω	
All $\pm 10\%$, $\frac{1}{4}$ W carbon		

Potentiometer

VR1 100k Ω carbon linear

Capacitor

C1 80 μ F elect. 16V

Semiconductors

TR1 TIS43 (unijunction) D1, D3 OA202
TR2 2N3704 D2 OA91

Miscellaneous

RLA 12V 700 Ω 2 pole change-over relay (Key-switch type MH2)
S1 single pole on-off toggle switch
Perforated s.r.b.p. (3in \times 2 $\frac{1}{2}$ in) and solder pins
Die cast box (see text)
Control knob; 3 core 5A lead; 6B.A. fixings

PRACTICAL POINTS

The delay time is controlled by the 100 kilohm variable resistor (VR1) in series with the fixed 22 kilohm resistor (R2). If a shorter delay is required the value of C1 should be reduced since resistor R2 is a minimum value for this circuit. Alternative types of unijunction may require different combinations of R and C but if the time constant (RC) is kept the same the delay time will not be affected. Any adequately rated npn switching transistor can be used with a base resistor to limit the base current—the relay given in the components list requires a current of only 17mA. It is a 12V type with two pole change over contacts connected together in parallel. As the inductive motor circuit is broken by the parking switch a 2 amp rating for the relay contacts is adequate and permits a smaller relay to be used.

Note: connections at points "X" in Fig. 2 must be reversed for use with negative earth systems.

CONSTRUCTIONAL DETAILS

The unit can be conveniently built into a small die cast box, although any suitable container may be used. The front of the box is drilled to take the control potentiometer (VR1) and the on/off switch S1. The remainder of the components, except the relay, are mounted on a piece of perforated s.r.b.p. which is

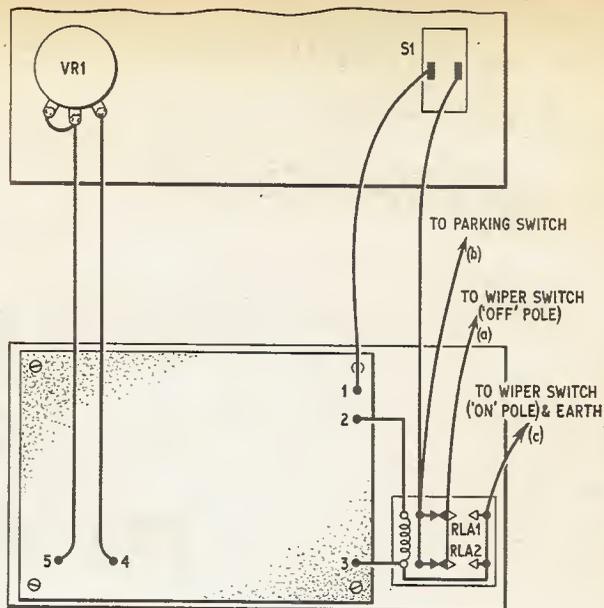


Fig. 4. Layout and wiring of the components mounted in the diecast case; all interconnections should be made using plastic covered wire. S1 and VR1 are positioned to avoid contact with the relay and component board when the front of the case is screwed down

trimmed to fit in the box behind the switch and potentiometer. If a small relay is used, the components can be mounted in a box with internal dimensions 4 $\frac{1}{2}$ in \times 2 $\frac{1}{2}$ in \times $\frac{7}{8}$ in. The relay is screwed to the box at one end and wired up using flexible plastics covered wire. The rest of the components are mounted on the board as shown in Fig. 3. Layout is not critical but an arrangement which is similar to the circuit diagram makes wiring and checking easier. Taper pins are used to anchor the component leads and the insulated wire connections from the rest of the circuit.

The prewired board is held in position by four 6B.A. screws (Fig. 4) and the three control leads from the relay are brought out through a grommeted hole. A control knob and a numerical scale complete with unit.

FITTING DETAILS

The die cast box was attached with a suitable bracket to the underside of the parcel shelf. A short 3 core 5 amp lead is required to reach the rear of the wiper on/off switch and the connections are as follows:

- (a) Attach a flat female connector to the common relay contact lead and plug it on to the back of the wiper on/off switch in place of the lead which goes to the parking switch.
- (b) Attach a flat male connector to the negative and normally closed relay contact lead and plug it into the lead disconnected in (a).
- (c) Connect the positive and normally open contact lead to the earth lead on the wiper switch—routing the positive lead via the case and mounting is not recommended.

Double check these connections and then turn on the wiper control at S1. The wiper blades should remain stationary for a short period and then execute one complete sweep and stop for another short period. This process will repeat *ad infinitum*, the length of the pause being varied by VR1.



In next month's **PRACTICAL ELECTRONICS**



PRACTICAL ELECTRONICS ORGAN

Thrill to the sound of a complete family of organ tone colours in your own home. Delight in a frequency range that encompasses keyboard music from 'classics' to 'pop.' Next month **PRACTICAL ELECTRONICS** gives you the first of a series of articles on how to build a professional class instrument which you will be proud to own for years to come. Designed by an acknowledged authority on organs, it is all solid state using up-to-the-minute silicon planar transistor techniques.

Voiced to produce the sound of an authentic theatre organ, it has two full 61-note manuals, 30 pedals and 19 stops, with the unusual feature of separate expression pedal for both the solo and accompaniment manuals to permit greater flexibility and tonal range. Separate two-unit speaker enclosure. Optional Leslie tremulant to manuals.

Simple unit construction enables you to complete the organ section by section so forestalling any initial large capital outlay. The total cost would be of the order of £200 — the completed job comparable with a commercial organ costing £600 upwards. This is the only home organ in existence with a complete 2ft top octave providing a host of exciting new tonal combinations.

INFRA-RED BURGLAR ALARM

An improved design of alarm based on a modulated infra-red beam.

**RELIABLE
SENSITIVE
FAIL-SAFE ACTION
TAMPER PROOF**

**PRACTICAL
ELECTRONICS**

3/- May issue — on sale Monday,
April 14

ORDER YOUR COPY NOW!

Goonhilly 2



In January of this year the G.P.O. opened its new Goonhilly 2 global communications system. The new installation will maintain for the Post Office a leading role as an Earth station owner in the expanding system of global communications via Intelsat III satellites. These satellites have facilities which provide flexible interconnections between a multiplicity of Earth stations, each satellite can carry a total of 1,000 telephony conversations and relay one colour television programme simultaneously. The now outdated Early Bird satellite has facilities to link only two Earth stations, with 240 telephone conversations or one television programme.

The new installation at Goonhilly was built to a Post Office specification, which meets the technical requirements of the International Telecommunications Satellite Consortium (INTELSAT), at a total cost (including roads, buildings, etc.) of approximately £2m.

The 90ft diameter aerial was built by Marconi who were the main contractors, threshold extension demodulators and certain other equipment have been supplied and installed by GEC-AEI (Electronics) Ltd.


The new aerial follows the pattern established


by the first Goonhilly installation of dispensing with a radome. This practice has since been followed by most other Earth station designers. The aerial makes use of a Cassegrain configuration with a spinning horn at the apex of the main reflector. The spinning feed-horn introduces a conical scan of the aerial beam only at the frequency of the satellite beacon signal. Thus it avoids unwanted amplitude modulation of the communication carriers or significant degradation of aerial efficiency for either direction of transmission. By this means auto-tracking can be achieved either by servo control of the main reflector mounting or, within a range of about 40 minutes of arc, by deflection of the sub-reflector. Provision has also been made for control of the aerial manually and for the addition of tape control facilities later, if required.

The very weak signals from the satellite in the 4GHz band are amplified by a three-stage parametric amplifier, cooled to 16°K in a closed-circuit, gaseous-helium refrigeration system, followed by a tunnel-diode amplifier. The four stages have an overall gain of 40dB over the 500MHz frequency band assigned for the down path from the satellite.

The aerial and telecommunications equipment are controlled and monitored from a suite of consoles in the

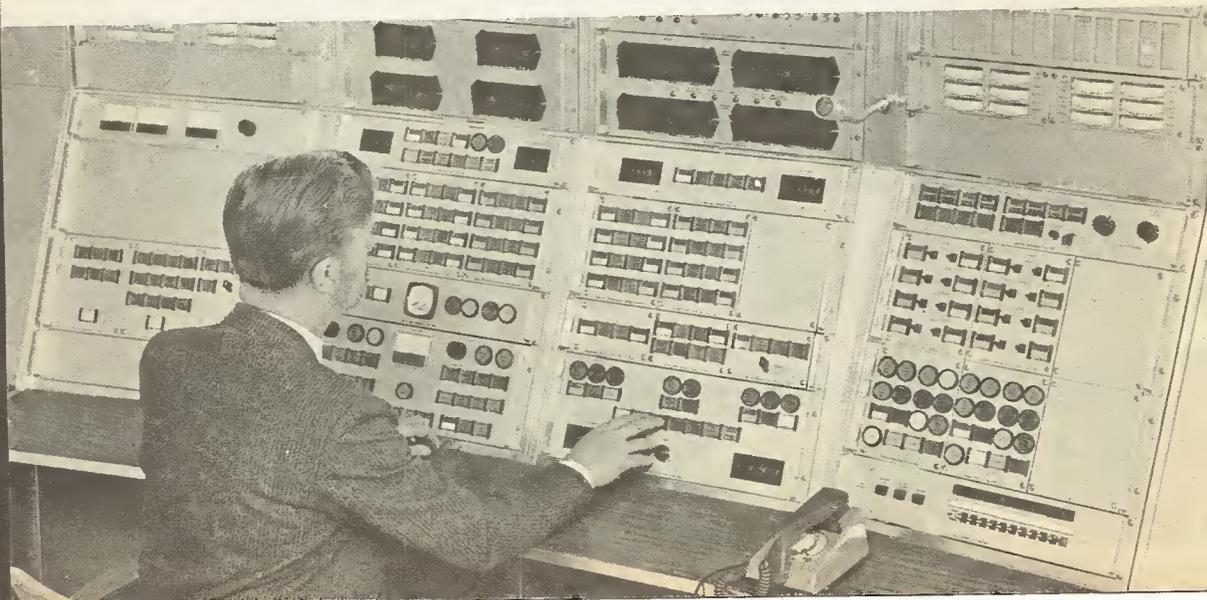
The remote control console in the main Goonhilly station building, full control of all components of the Goonhilly 2 space terminal is provided at this position



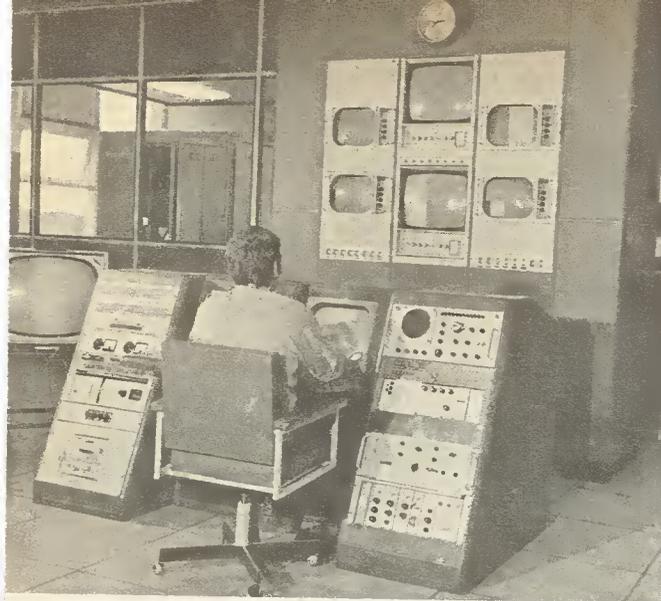

Comprehensive testing and monitoring facilities for both colour and black and white television signals is provided at this control console

central building. Each carrier, which may transmit up to 132 telephony channels, is monitored separately and reserve equipment is switched into use automatically if a disabling fault condition arises. Faults which cause degradation of the service but do not interrupt it can be located and eliminated by manual switching of their component sub-systems without interference with traffic. A separate console enables the television service to be monitored and tested. The extensive use of duplicated equipment and monitoring facilities ensures a reliability of

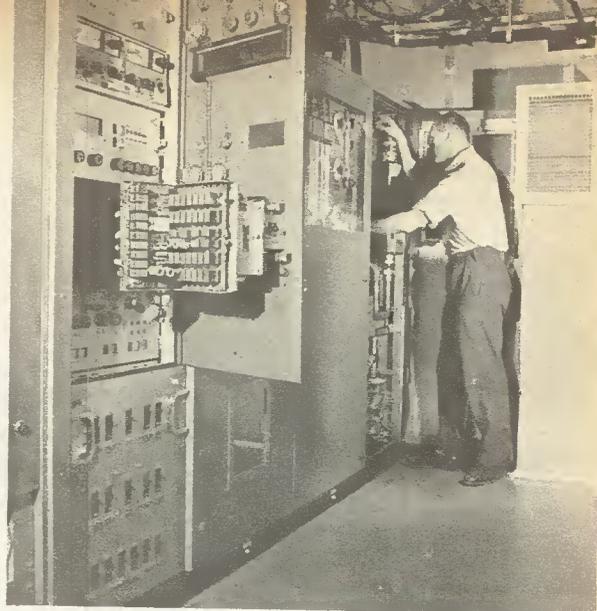

Part of the transmitter cabin with an operator adjusting the coolant supply for the output travelling wave tube of one of the transmitters. The local control panel in the foreground is open to show the controls for setting up the drive unit

99.9 per cent for the complete system, which is less than 9 hours per year out of service.

Initially Goonhilly will operate telephony circuits to only the USA and Canada but as more Earth stations become operational the system will expand until by 1971, Goonhilly is expected to be working to 20 countries. Goonhilly 1 aerial is now being refurbished to communicate with countries to the East and will be back in service as soon as an Intelsat III satellite is available over the Indian Ocean.



Faster TV Tubes

PRODUCTION of television picture tubes at the Mullard tube plant at Simonstone, Nr. Burnley has been speeded up with the introduction of a new machine shown below. The machine was developed and built by the Department of Production Engineering and Production Management of Nottingham University and is designed to assemble part of the electron gun automatically.

The electron gun is a precision sub-assembly comprising a large number of small components requiring the use of highly-skilled female labour for assembly; this machine automatically assembles three of the components. The

component parts are fed by vibrating feeders to "pick-and-place" units which place the components on mandrels at welding stations, an electronically controlled sequence then takes over and the parts are assembled and eight welds are made to produce the (grid 3) assembly.

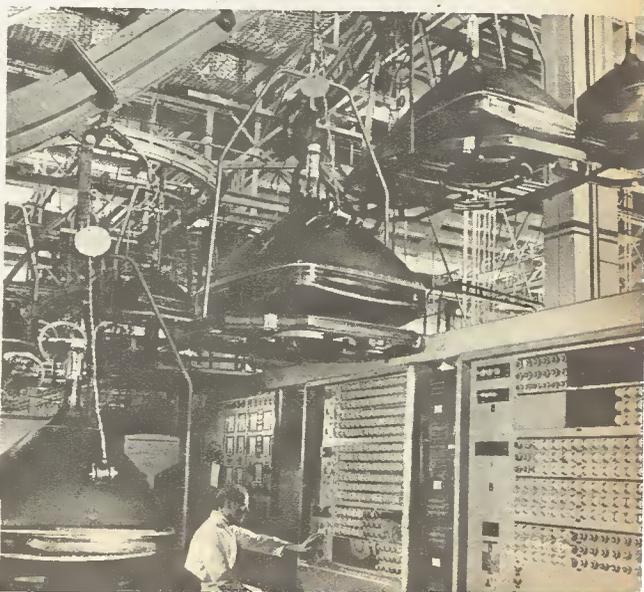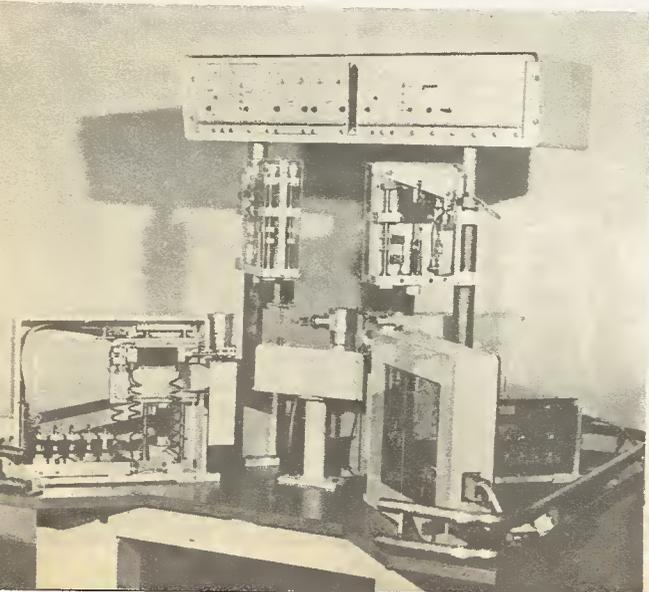On completion of the picture tubes an "ageing" process has to be carried out before the tubes are dispatched. This process is carried out at the Mullard plant whilst the tubes are moving around the factory on a conveyor. The still photograph below is from the film "Mullardability" and shows the conveyor carrying the picture tubes.





LOUDSPEAKERS

by P.T. Harrison

THERE is more to achieving high fidelity reproduction from a loudspeaker system than just matching its electrical impedance characteristic to that of the amplifier. Apart from electro-acoustic efficiency, mechanical loading of the moving element is a significant factor in obtaining an acceptable aural response free from distortion and disturbing resonances.

The loudspeaker can be likened to a transmitting aerial but with polar response related to audio frequencies. Horns or baffles act as deflectors to obtain certain directional properties and avoid frequency cancellation effects. Acoustic impedance matching is another factor to be considered.

This article traces the history of development of electro-acoustic receiving transducers, then goes into the main features of the moving coil loudspeaker with particular emphasis on solving some of these problems.

HORN LOADED LOUDSPEAKERS

The earliest type of electro-acoustic receiver was that using an electromagnet with moving metallic diaphragm, still in use in principle today in telephones and headphones. The efficiency is poor due to the difference in mechanical impedance between the diaphragm and the air. See Fig. 1a.

Attempts were made to match these impedances by attaching a conical horn to electro-magnetic receiver (Fig. 1a), the horn acting as an acoustic transformer between the low impedance of the air and the high impedance of the stiff diaphragm of the telephone type of receiver. It was soon discovered that an exponentially shaped horn gave better results, especially in the low frequency range. Sound waves propagated along the axis of an exponential horn are not distorted, as reflections from the wall of the horn are in phase with the propagated waves. Fig. 1c illustrates an example of such a unit.

The efficiency of the horn loaded loudspeaker was limited at the lower frequencies by the size of the horn.

Increases in the overall efficiency were achieved by arranging for the resonance of the diaphragm to be in the frequency range over which the unit was used.

The Brown loudspeaker (Fig. 1b) dispensed with the telephone receiver and used instead a spun aluminium diaphragm driven by an electro-magnetically motivated reed. The reed was fixed at one end (Fig. 2), whilst the remaining end was free to move under the influence of a magnetic field produced by a coil. The apex of the diaphragm was secured to the reed, which acted as a "mechanical transformer".

The response of this unit showed a marked improvement upon the response of the units which used a telephone type receiver, but was in many ways inferior to the response of the direct radiator loudspeakers that were to follow.

A further drive mechanism, which when horn loaded gave favourable results, was incorporated in the ribbon loudspeaker. A corrugated aluminium foil ribbon was suspended in the gap between the poles of a powerful magnet.

An electric current was caused to flow through the ribbon, thus giving rise to a magnetic field which interacted with the field produced by the permanent magnet and consequently caused the ribbon to move. The movements of the air surrounding the ribbon were coupled, via an exponential horn, to the outside air. This form of unit is still produced, but is used mainly as a tweeter to reproduce frequencies above 2,000Hz.

The low mass and low impedance, in conjunction with a high value of Young's Modulus for aluminium, make the speaker particularly suitable for the reproduction of high frequencies. (The value of Young's Modulus for a given material, determines the degree of stress that the material will withstand before fracture, i.e. Young's Modulus equals the ratio of longitudinal stress to longitudinal strain.) A powerful magnet is required to produce a high magnetic field strength across the gap in which the ribbon is situated.

ELECTROSTATIC LOUDSPEAKERS

The simplest form of electrostatic loudspeaker comprises two large flat metal plates mounted closely together. A potential difference developed across the plates causes a force to be exerted between the plates. A d.c. polarising voltage is usually required, in addition to the alternating voltage signal provided from the audio amplifier.

In its earlier development stages, it was difficult to obtain a wide frequency response compatible with low distortion; sensitivity was relatively low. However, some commercial concerns have in recent years applied specialised techniques to these shortcomings to provide effective and sometimes competitive results over a wide frequency range.

DIRECT RADIATOR LOUDSPEAKERS

The direct radiator loudspeaker superseded the large exponential horn, the diaphragm being coupled directly to the air. Various systems were used to drive the diaphragm, including a reed as in the Brown loudspeaker. Unless the mechanical arrangements of the reed mechanism is critically controlled, severe amplitude distortion could result.

One method of reducing this distortion is to use a balanced armature system (as in the modern lightweight telephone receiver), in which the reed is pivoted at its centre and attached, via a rod, to a cone. The reed moves under the influence of the magnetic field produced by two coils. An example of this form of loudspeaker is illustrated in Fig. 3.

The most popular form of direct radiator loudspeaker is the moving-coil loudspeaker, early examples of which were produced by Magnavox and Rice Kellogg.

The main functional components of the moving-coil loudspeaker are an electrical conductor in the form of a coil, suspended in a strong magnetic field produced by a powerful magnet (Fig. 4), and attached to a large diaphragm (cone), which is free to move under the influence of the forces exerted upon the coil as a result of the current through it.

Early types of moving-coil loudspeaker employed an electromagnetic field usually powered from the h.t. line, but this was later replaced by a permanent magnet.

Fig. 2. Simplified illustration of the reed drive mechanism

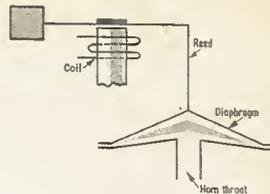


Fig. 3. Celestion Loudspeaker; early direct radiator loudspeaker

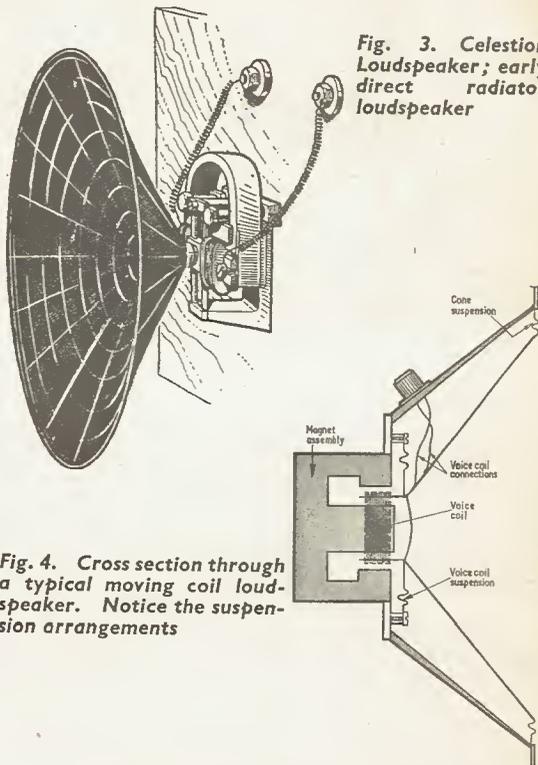


Fig. 4. Cross section through a typical moving coil loudspeaker. Notice the suspension arrangements

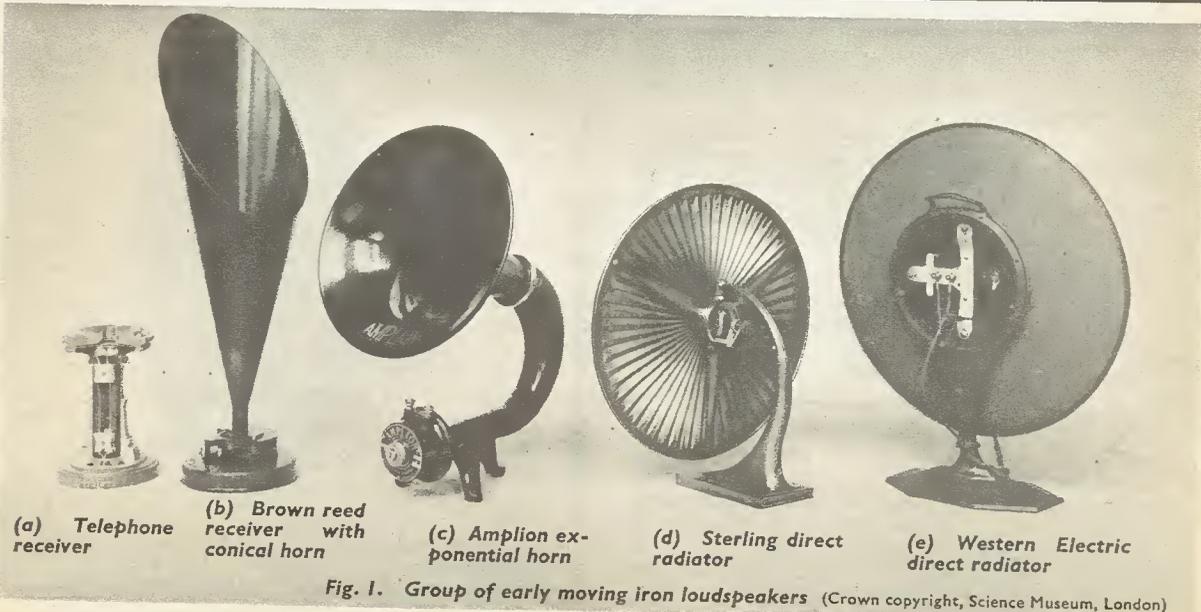


Fig. 1. Group of early moving iron loudspeakers (Crown copyright, Science Museum, London)

Unlike the loudspeaker shown in Fig. 4 all the early moving-coil loudspeakers were fitted with a front "spider" suspension system attached to the magnet for centring the coil in the air gap. The efficiency of a loudspeaker fitted with a front spider tends to be reduced at low frequencies, whilst at higher frequencies severe peaks in the response become prominent. The overall aural effect is rather harsh. Present-day types (Fig. 4) employ a corrugated foil or fabric suspension system behind the cone.

The popularity of the moving-coil loudspeaker is due, in the main, to the ease of construction and use, smaller space requirements, and the much improved frequency response; the latter is limited mainly by the dynamic characteristics in relation to the air mass which the cone has to move, and the side effects of wave propagation between front and rear. Fig. 5 illustrates an example of a modern moving-coil loudspeaker.

The main problems in any ideal audio system are concerned with the prevention of unwanted distortion and the maintenance of a reasonably flat frequency response throughout the audio frequency range. The loudspeaker is probably the most difficult part of the reproducing chain in which to achieve anything approaching perfection. Let us now look at the problems involved and see if they can be sorted out.

FREQUENCY RESPONSE

The response of a loudspeaker should not be confused with its efficiency. The efficiency of a loudspeaker is determined by the ratio of the sound power output to the electrical power input. The frequency response of a loudspeaker is a measure of the sound pressure produced at a specific position in the surrounding medium (usually in line with the axis of the cone) due to a known electrical input at a given frequency. The acoustic conditions, under which the test is performed, should also be specified. If the loudspeaker were non-directional there would be no differentiation between the efficiency characteristic and the frequency response characteristic.

A reasonably flat average response over a frequency range can be achieved with a direct radiator, moving-coil loudspeaker. (The term average is used because the speaker should respond to transients, see later.) The main problems are concerned with maintaining the response at both ends of the audio frequency range and reducing peaks in the response which occur at both low and high frequencies.

The mass of the vibrating system of a moving-coil loudspeaker, at low frequencies, may be regarded as equal to the sum of the mass of the voice coil and the mass of the cone; the compliance of the system may be considered as being the resultant of the compliance of the supports of the coil and cone.

The mass of a mechanical system is analogous to the inductance of an electrical system, whereas the compliance of a mechanical system is analogous to the capacitance of an electrical system. Consequently, as in an electrical system, the inherent mass and compliance of a mechanical system produce a fundamental resonance based on these two factors.

RESONANCE

The fundamental bass resonance of a moving-coil loudspeaker is an important factor. For a typical 12in diameter loudspeaker this bass resonance can occur around 30Hz, whereas for an 8in diameter loudspeaker the resonant frequency can be 60Hz or higher.

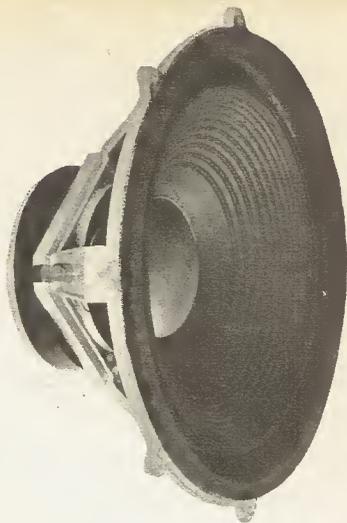


Fig. 5. Modern form of moving-coil loudspeaker manufactured by Wharfedale

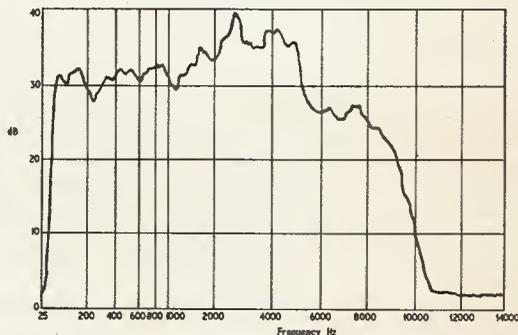


Fig. 6. Frequency response to be expected with a typical 10in moving coil loudspeaker mounted on an infinite baffle



Fig. 7. Dual-cone loudspeaker manufactured by Wharfedale

Fig. 6 shows the frequency response curve for a typical 10in diameter loudspeaker. The fall-off in response of the moving-coil loudspeaker at low frequencies is due, in part, to the inability to match the output of the loudspeaker to the surrounding air. This problem can be partially overcome in a variety of ways. Mounting the loudspeaker in a reflex cabinet (mentioned later in this article), tends to improve the low frequency response, whilst an exponential horn may be used as an "acoustic transformer", as described previously. Of course, the same result can be achieved by using a moving-coil loudspeaker with a larger cone.

The fundamental bass resonance is important in the determination of low frequency response. Below this resonant frequency the response of a loudspeaker falls off rapidly. Furthermore, unwanted harmonics are produced at and around the resonant frequency. It would appear that the aim should be to reduce, as far as possible, the frequency at which bass resonance occurs.

In practice, however, lowering this resonant frequency, by the use of a suspension with a greater deal of freedom can give rise to certain problems. The manufacture of such a loudspeaker tends to be very difficult and also results in a unit whose robustness leaves much to be desired. The centring of the voice coil would be unstable and could be easily affected by small mechanical shocks.

It is worth noting, that although the efficiency of a moving-coil loudspeaker rises at the bass resonant frequency, the actual increases in the response are normally not as great. This is due to the high damping factor of modern amplifiers, which incorporate negative feedback. It is therefore apparent that the effects of variations in the design, which influence the behaviour of a moving-coil loudspeaker, are more readily observed when the loudspeaker is driven by an amplifier without negative feedback.

EFFECTIVE WORKING RADIUS

At low frequencies, the time taken for a displacement of the cone, at its centre, to travel to the rim, is small compared with the period of the signals reproduced, and consequently may be neglected. The cone can thus be considered to behave as a rigid surface, similar to a vibrating piston.

However, at higher frequencies the cone no longer vibrates as a whole; the amplitude of vibration of the cone becomes smaller nearer its rim, hence causing the effective working radius of the cone to be reduced. The overall effect is an increase in the efficiency of the loudspeaker at frequencies in the order of 1,000 to 2,000Hz.

Sharpening of the directional pattern of a moving-coil loudspeaker is lessened by the reduction of effective cone radius which accompanies the increase in frequency.

It can be seen that the reduction of effective radius at higher frequencies is a desirable feature; it may be enhanced by employing a loudspeaker which has circular corrugations formed in its cone.

VOICE COIL

Another point to be considered with regard to the high frequency response of a moving-coil loudspeaker, is the electrical impedance of the voice coil. This impedance increases with frequency, consequently causing a fall-off in the high frequency response. Increases in voice coil impedance, with a constant applied voltage, result in a reduction of the current

through the coil, which in turn causes the driving force to be reduced. To maintain the response at higher frequencies requires a reduction in the mass of the voice coil; this can be achieved by using a coil wound with aluminium instead of copper.

Apart from utilisation of various forms of cabinet (mentioned later), a flat frequency response over a wide range can be achieved by using several loudspeakers, each using a filter to reproduce a section of the audio frequency band. The size of loudspeaker cone has a bearing on the frequency range which that loudspeaker can reproduce well; consequently, larger sizes are employed for low frequencies and smaller sizes for high frequencies.

Instead of using more than one loudspeaker it is possible to incorporate two cones in one loudspeaker (Fig. 7), a mechanical arrangement being used to couple the two cones. At low frequencies the entire system vibrates as a whole, both cones radiating together. At high frequencies the small cone vibrates, without damping interference from the large cone. This system is generally termed dual concentric. In some cases the two cones are energised from two separate voice coils, so that each can be suitably tailored for best response within its range.

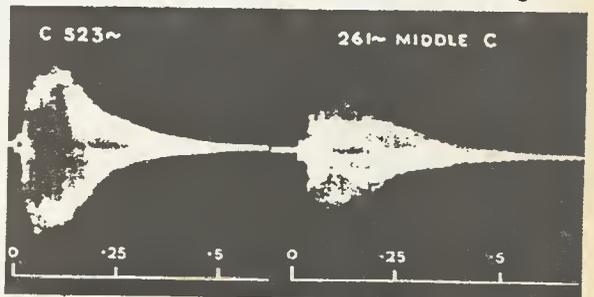


Fig. 8. An oscillogram showing the wave-envelope of a piano tone

TRANSIENT RESPONSE

A point often overlooked when considering the sound quality of a moving-coil loudspeaker, is its transient response. The transient response determines the ability of a loudspeaker to follow very rapid changes in the amplitude of the applied signal. The normal frequency response curve only illustrates the ability of a loudspeaker to respond to a constant sinusoidal signal irrespective of time.

In practice a loudspeaker is rarely used to reproduce pure sine waves of constant amplitude, but has to be able to handle signals, the waveforms of which can be of the form shown in Fig. 8. (Notice in this illustration the wave envelope of a piano tone, with its percussive attack and exponential decay.)

The source impedance of the amplifier used to drive the loudspeaker, and the flux density of the magnet used in the loudspeaker, both determine the transient response of the loudspeaker, in addition to the fundamental bass resonance previously discussed. High flux density in the magnet and reductions in the source impedance, by the use of negative feedback in the amplifier, tend to improve the transient response of a moving-coil loudspeaker.

POWER HANDLING


Another important property of a loudspeaker, is its power handling capacity. The output of a moving-coil loudspeaker is limited by the maximum permissible

axial displacement of its cone. The greatest displacements occur at low frequencies, while high frequencies are damped to some degree as mentioned above.

The loudspeaker should be designed to handle the lowest frequency (about 16 or 32Hz for organ music) without the risk of cone tearing or voice coil former being damaged. An unpleasant rasping sound at low frequencies is a sign to employ a larger loudspeaker. Similarly distortion and vibration at medium frequencies could also point to the need for a larger loudspeaker, but not always.

DISTORTION

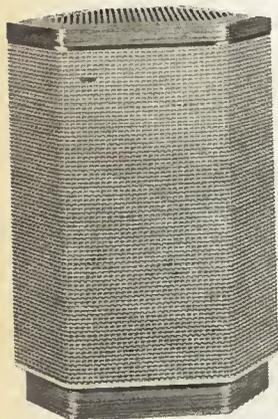Most of the distortion produced by a moving-coil loudspeaker is due to non-linearity of the cone suspension system. This non-linearity results in the production of harmonics and subharmonics. The harmonic distortion as stated earlier, is predominant



The "Airedale" hexagonal enclosure for corners designed by Wharfedale. Three loudspeakers are housed inside with a half-section three-way crossover separator unit. Dimensions are $38\frac{1}{2}$ in \times $27\frac{1}{4}$ in \times 14in

around the fundamental bass resonant frequency, whereas the production of subharmonics due to the cone suspension system occurs at very low frequencies and is not usually noticeable. The troubles associated with the production of subharmonics, are apparent in the mid-frequencies where non-linearity of the cone itself occurs.

Another source of distortion in the moving-coil loudspeaker is non-uniformity of the magnetic field in which the voice coil moves. This can be overcome by employing a voice coil winding, longer than the air gap in which the coil is positioned, thus ensuring that the whole of the voice coil winding remains in the air gap, even during maximum excursions of the coil.

The sources of distortion so far described also give rise to another form of distortion, known as intermodulation distortion. Intermodulation distortion occurs when the simultaneous reproduction of any two frequencies results in the production of another frequency. This form of distortion is reduced by ensuring that the cone suspension system behaves, as far as possible, in a linear manner, and that non-uniformity of the magnetic field is eliminated, in the manner already described.


BAFFLE

The sound energy radiated from the back of the cone of a moving-coil loudspeaker is 180 degrees out of phase with the sound energy radiated from the front. If, therefore, a loudspeaker is not mounted on a baffle board, or in a cabinet of some form, the sound energy radiated from the back of the cone will interfere with the sound energy from the front of the cone, thus

resulting in a reduction of acoustic perception at the listening position. This can be overcome by mounting the loudspeaker on a flat baffle of suitable dimensions with frontal aperture.

The choice of dimensions is governed by the size of loudspeaker and required low frequency response; the lower the frequencies to be reproduced, the larger must be the baffle. However, the baffle need only be made large enough to ensure satisfactory response down to the bass resonant frequency of the loudspeaker. Beyond that frequency, no matter how large the baffle is made, the response of the loudspeaker will fall off rapidly.

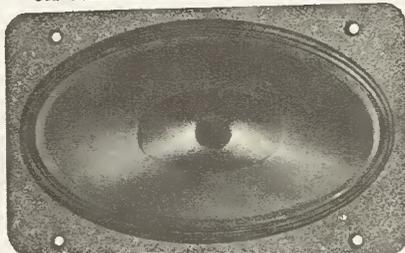The use of a small baffle can also produce a dip in the frequency response at higher frequencies. This is more pronounced when using small loudspeakers. It may be significantly decreased by mounting the loudspeaker off-centre on the baffle.



E.M.I. elliptical woofer and high flux tweeters with crossover unit, suitable for a 1.5 cu ft enclosure



The size of a flat baffle necessary to ensure satisfactory response is not generally practical and one must accept a compromise by using a smaller baffle with a poorer low frequency response.

TOTALLY ENCLOSED CABINET

A more satisfactory arrangement is often achieved by mounting the loudspeaker in a totally enclosed cabinet (infinite baffle cabinet). The sound energy radiated into the surrounding air then emanates from the front of the loudspeaker cone only, as with an infinite baffle.

The main objection to this form of cabinet is the increase in the frequency of bass resonance of the loudspeaker, as a result of the additional stiffness contributed by the mass of air confined within the cabinet. This causes the response at low frequencies to begin falling off at a higher frequency than if the loudspeaker were mounted on an infinite baffle.

This may be partially overcome in one of two ways; by increasing the volume of the cabinet, thus reducing the additional stiffness, or by using a loudspeaker with a lower bass resonant frequency (i.e. a loudspeaker suspension with greater freedom).

The sound energy radiated from the back of the cone still produces undesirable effects, in this instance causing, at certain frequencies, standing waves to be set up within the cabinet. This results in unwanted dips and peaks in the frequency response, but can be significantly reduced by lining the interior surfaces of the cabinet with a layer of sound absorbent material (e.g. fibre glass, cotton wool, etc.). This reduces the magnitude of the standing waves and also decreases the peak in the response at the bass resonant frequency.

OPEN-BACKED CABINET

One of the simplest ways of mounting a loudspeaker, is in an open-backed cabinet. This is a suitable way of applying a "folded" baffle where space is limited. Here once again, sound energy radiated from the back of the loudspeaker cone combines with sound energy radiated from the front of the cone to produce a rapid fall-off in the response below the fundamental resonant frequency of the cabinet.

The cabinet resonance, is in itself troublesome, as it introduces an unwanted peak in the frequency response. However, by arranging for the bass resonant frequency of the loudspeaker to be lower than that for the cabinet, a smooth and extended low frequency response may be achieved. Standing waves are not a problem due to the air pressure flexibility at the rear.

REFLEX CABINET

The use of a reflex cabinet enables the sound energy radiated from the back of the cone of a loudspeaker to be added, in phase, with the sound energy radiated from the front, thereby increasing the output at lower frequencies.

The reflex cabinet comprises essentially, an enclosed cabinet with a vent aperture situated below the loudspeaker aperture. At high frequencies the vent has no significant effect and the cabinet behaves as a totally enclosed cabinet. The interior of the cabinet must therefore be lined with a sound absorbent material to avoid the presence of standing waves.

At low frequencies, sound energy, radiated from the back of the cone, after undergoing a phase shift of 180 degrees, emanates from the vent, thereby reinforcing the sound energy, radiated into the surrounding air, from the front of the cone.

At frequencies below the resonant frequency of the cabinet, however, this phase shift rapidly decreases, and the air in the vent tends to move in phase with that at the back of the cone. The resultant response due to radiation from the vent and from the front of the cone produces the poor low frequency response associated with a small baffle at frequencies below cabinet resonance.

CONSTRUCTION OF LOUDSPEAKER CABINETS

In the preceding paragraphs the walls of the cabinet have been assumed to provide a definite boundary for the sound waves. In practice, careful attention has to be paid to the choice of cabinet wall dimensions to avoid vibrations of the cabinet itself. This is more important for totally enclosed and reflex cabinets, where high pressures may be set up with the cabinet.


Additional rigidity of the cabinet walls can be achieved by using cavity walls filled with sand. These are constructed by spacing two stout wooden sheets, say $\frac{1}{2}$ in to 1 in apart, and filling the cavity with dry sand; even better results can be achieved by constructing the cabinet of concrete or bricks.

More precise details of cabinet dimensions are not given here because they should be matched where possible to the loudspeaker to be used. Manufacturers' literature should be consulted or alternatively some text books may offer guidance.

ACKNOWLEDGEMENTS

The author wishes to acknowledge Rank Wharfedale Ltd. and Sir Isaac Pitman & Sons Ltd. for assistance in compiling this article. ★

NEWS BRIEFS

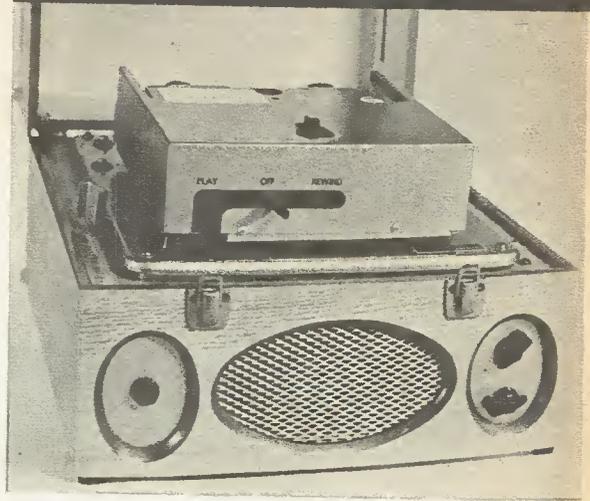

Talking Books Conversion for New Cassette

THE British Talking Book Service for the Blind, administered by the R.N.I.B. is now rapidly expanding due to the development of the Mark IV type tape cassette. This cassette, which is very much smaller than has hitherto been used, contains up to 13 hours of recording time, playing at $\frac{1}{8}$ in per second on a $\frac{1}{4}$ in tape. New features of the MkIV have brought about the development of a small portable machine (shown below) that has largely superseded the larger MkI version. Transistors are employed to amplify the tape signal and, in the case of the students' library, to give audible signals at high speed for fast chapter location.

Whilst there are still large quantities of MkI machines which are expected to offer another 10 years of service, they must be made capable of replaying both MkI and MkIV cassettes.

A special adaptor has been developed to enable the MkIV cassette to be played on the MkI machine, after minor modifications to the machine as shown above.

Due to the rapid expansion of the Talking Book Service (some 250 titles and 6,000 new members each year) the problem of voluntary installation and service mechanics is becoming acute in many parts of the United Kingdom. Persons who are willing to give occasional help on a voluntary basis to enable blind people to use the Talking Book machine and assist with repairs would be gratefully acknowledged. Further information and offers should be addressed to The Manager, British Talking Book Service for the Blind, Mount Pleasant, Alperton, Wembley, Middlesex.



BETTER RECEPTION

Now that colour television programmes are in full swing and more people are taking delivery of colour television receivers, **Belling-Lee Ltd.**, decided to develop a pre-amplifier which would improve colour, black and white, and stereo f.m. radio reception. The result of these developments is the Concord pre-amplifier which is claimed to give a signal amplification of approximately four times.

Designed to operate on all television channels and f.m. radio band, the Concord is an ultra broad band pre-amplifier which boosts the incoming signal giving better picture quality, sharpening contrast, reducing "snowstorm" noise effects, and, on colour sets, gives better colour quality.

The pre-amplifier is ideally suited for fringe areas and is easily installed by simply hooking the moulded grey case, measuring 5in x 3½in x 2¼in, onto the rear of the television or radio receiver. Plugging the aerial lead into the input socket, inserting a screened link lead between the pre-amplifier output socket and receiver aerial input socket, and connecting the mains lead to the supplies completes the installation.

Power consumption is very small, approximately the same as an electric clock, and the recommended selling price is £7 7s.

Once installed, it is claimed no further adjustments are necessary.

LOGIC KIT

To meet the needs of electronic project work in schools amongst students of all ages, **Geatronic Ltd.**, have developed the Norkit range of electronic kits.

The basic building brick is a NOR logic module which, together with the other components supplied, enables the rapid assembly of a sequential control system for any automatic device.

There are three Norkit ranges at the moment: the junior, price

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.



Belling-Lee ultra broad band pre-amplifier

£8 16s; the senior, price £17 12s; and the advanced kit, price £26 8s.

The junior kit contains seven NOR logic circuits, two output units, diodes, lampholders and lamps, push buttons, reed switch and magnet, capacitors and resistors and all necessary inter-connecting wires and solder.

The senior kit contains 12 NOR logic units, three bistable circuits, three output units, microswitch, and a larger selection of all components supplied with the junior version.

The advanced kit introduces components associated with automation equipment, and contains power driver units, photo cells, Zener diodes, thyristors, unijunction transistors, etc.

Handbooks supplied with the kits clearly outline the fundamentals of logic and automation and give a good introduction to computer work.

Most items can be purchased separately and further details can be obtained from, **Geatronic Ltd.**, 28, Redstock Road, Southend-on-Sea, Essex.

Another product aimed at education is the Pidam range of teaching modules from **West Hyde Developments Ltd.**

These modules are digital and analogue plug-in devices which can be used to make up demonstration models, and can be used to construct teaching machines which can be loaded with questions and answers in elementary physics.


Further details can be obtained from, **West Hyde Developments Ltd.**, 30 High Street, Northwood, Middlesex.

SOLDER

A handy size dispenser for solder has just been introduced by **Multicore Solders Ltd.**, Hemel Hempstead, Hertfordshire. The new, pen size pack contains 21ft of 60/40 Ersin 5-core solder and is ideal for the tool box, and for use when soldering small components, fine wires and printed circuit work.

The dispenser is known as size 15, costs 3s and is claimed to be designed so that the solder cannot fall back inside the container. If the reader only requires enough solder for the odd repair, then possibly the size 2 pack will suffice. This is a larger gauge 5-core solder contained in an envelope with full soldering instructions printed on the back. The size 2 pack costs 6d and contains enough solder for 80 average joints.

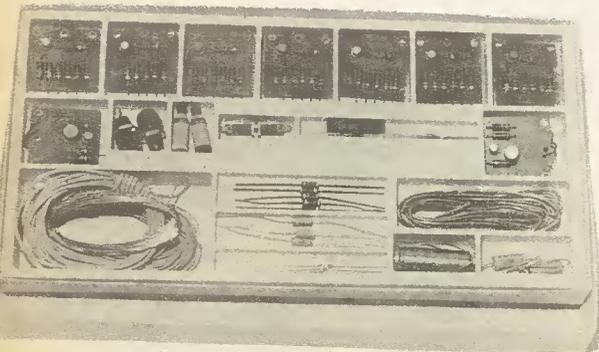Junior logic kit manufactured by Geatronic



Solder dispenser from Multicore Solders



Pidam logic modules produced by West Hyde Developments



CRYSTAL HOLDERS

Constructors may be interested in the range of Augat crystal holders marketed by Electrosil Ltd., Pallion Trading Estate, Sunderland, Co. Durham and available from some retail stockists.

Crystals may be easily inserted or removed without any adjustments to latches or screws, and once inserted it is claimed that the crystal will not shake loose under severe vibrations.

Developed to take crystal sizes HC-6/U, HC-13/U and sub-miniature type HC-25/U, the holders are easily bolted onto any chassis, and the solder terminals are completely insulated.

A 5-pin TO5 outline relay socket is also available from Electrosil Ltd., and can be supplied for printed circuit board or chassis mounting.

FINGER TOOLS

The items in our photograph (bottom right) are not stick-on claws to even up the sexes but finger tools useful for miniature electronic assembly work.

Known as Deli-Cut tools they consist of miniature cutters, tweezers and positioners. The tools are attached to the finger tips by a self-adhesive band and worked by the thumb. A different tool can be carried on each finger, if necessary.

Marketed by Henri Picard and Frere Ltd., 34 Furnival Street, London, E.C.4., the tools are steel hardened and vary in shapes and cutting angles.

IC CARD

A printed board designed specially to accept integrated circuits is now available from A.P.T. Electronic Industries Ltd., Chertsey Road, Byfleet, Surrey.

Designated Cardic 24 (part number LK-3121), 24 dual in-line (14 or 16 leads) integrated circuits can be mounted on one card. Printed power supply copper tracks run to each i.c. and a 24-way input/output edge connector provides plug-in facilities.

The cards are designed specifically to achieve simplicity of i.c. insertion and removal without undue damage to the wiring or device.

These cards are also supplied as part of a kit assembly, Lektrokit No. 10, which includes the components for a complete rack mounting framework with 12 sockets and guides for £23 10s.

PHOTO CELL

A new range of CdS photoconductive cells are now being distributed by Hird-Brown Ltd. Complimenting the existing $\frac{1}{2}$ in and $\frac{1}{4}$ in diameter devices these additional cells are packaged in TO5 outline encapsulations.

Described as types NSL481 to NS484 and NSL487, they offer twice the power ratings and values cover

2.5 kilohms to 160 kilohms, measured at one foot candle.

Spectral response covers the normal CdS range peaking at 0.55 microns, similar to that of the human eye.

All devices have a power rating of 200 milliwatts at 25 degrees centigrade. Maximum peak voltage is rated at 250V a.c. or d.c.

Any further information can be obtained from Hird-Brown Ltd., Lever Street, Bolton, Lancashire.

LITERATURE

Colleges and evening institutes may be interested in a booklet published by Mullard Educational Service describing an aid for teaching counting systems and logic functions.

Entitled *A Digital Integrated Circuit Training Aid* (DICTA), the booklet describes a system using integrated circuits and indicator lamps that can be easily arranged to make 100 different types of counter and shift register.

This is achieved by rearranging simple patching links made with copper-plated split pins. The equipment can also be used to demonstrate the logic functions of various types of gate and combination of gates as found in adders and decoders.

Copies of the booklet can be obtained free, from Mullard Educational Service, Mullard House, Torrington Place, London, W.C.1.

Readers of *Hi Fi News* will know just what to expect in their Audio Annual 1969—the fourth edition to be published by Link House Publications. It looks very much like a fat edition of the above journal with layout and presentation in the same style.

All this is by the way—most audiophiles will be looking for the usual run-down of audio equipment test reports and reviews that have appeared over the last year. For those about to embark on a spending spree and want to know more about what has come onto the market during this period, this Annual could be 7s 6d well spent.

A regular group of consultant contributors have provided some light hearted and serious articles on the general aspects of hi fi, including a survey of progress over the past 50 years.


This annual contains 132 pages including 50 pages of advertisements for current equipment. It is available from most large newsagents.

Available from distributors of International Rectifier components are a range of charts giving detailed operating characteristics for thyristors, triacs and unijunctions; low power and Zener diodes; voltage surge protectors, high power diodes and rectifier assemblies.



Further details of nearest IR distributors can be obtained from International Rectifier Co. Ltd., Hurst Green, Oxted, Surrey.



NSL 481 photocell from Hird-Brown

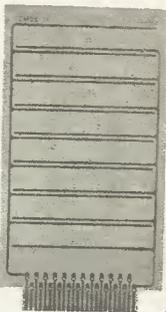

Lektrokit Cardic 24 i.c. mounting board by A.P.T. Electronic Industries

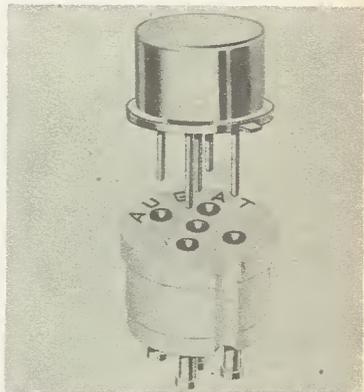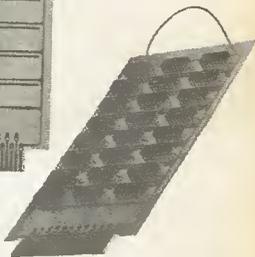

Augat 5-pin TO5 relay socket from Electrosil



Deli-Cut tools marketed by Henri Picard and Frere

PROPERTY DETECTORS

PATTERN RECOGNITION

BIONICS

BY G.C. BROWN

M.S.H.A.A., A.M.R.S.H.

ACTUAL hardware versions of the edge and bug property detectors mentioned in our last discussion really "eat up" photo-cells in the number required to do the job. Such devices additionally demand well matched and sensitive receptors; so even if we had decided upon using, say, ORP12's the total cost could have been extremely high. Unfortunately too, most cheap photo transistors are inappropriate in that they are light sensitive only from the side of the glass envelope—the requirements being that a group of receptors be mounted together so that they may be exposed to illumination end-on.

We will therefore "keep our expensive ideas to ourselves" and look at some equally interesting property detectors which require fewer receptor elements. (While in the meantime we can only hope that manufacturers will make an attempt to equalise the scandalous price differential between their transistors and photo-sensitive devices).

Unlike some of the previous examples which were based more upon inductions from physiological data, the property detectors we shall consider now will tend to be of the invented kind. The first is shown in Fig. 6.1.

A CRUDE FORM OF SIMULATION

The notion we have here is one which, although fundamentally simple, could prove to be quite advantageous if utilised in certain automata. One aspect of a higher animal's abilities is that which permits it to judge the speed of objects moving in relation to itself. Just how this is performed in the biological brain is a matter for further research and contemplation. However, in the diagram we see the basis for a method of obtaining a form of crude simulation. The basic scheme includes just one mono-

stable plus a NAND gate. Its operation is most easily seen if we install a pair of eyes (photo-cells) in the device, so that it can "observe".

For the sake of example we may assume that the monostable as shown in Fig. 6.1 has a period of 0.7 seconds. Now if a moving light, or even a bright object, passes photo-cell X1 the monostable will be triggered. If during the time the monostable is in this quasi-stable condition the moving object passes X2, the output from the gate will change from 1 to 0 permitting this output to appear up to the time that the monostable reverts to its stable state. On the other hand, if X2 receives the stimulus *after* the monostable has "switched back", or indeed if it never gets stimulated, the output will remain unchanged.

Such a device, though crude, could be used to classify "fast" and "slow" moving objects. How "slow" and how "fast" we of course do not know, except that the speed of movement was either above or below 0.7 seconds. We cannot be certain either that the stimulus at X2 was caused by the same object! Nevertheless, it is possible to improve the scheme a great deal by employing more classifiers.

MORE ADVANCED DETECTOR

In Fig. 6.2 the scheme is a little more ambitious, for not only does it break the classifications into "fast", "medium", and "slow"; but also permits observation of objects from either direction and additionally tells us the direction. (Fig. 6.1 was strictly "one-way only".)

This improved property detector operates in much the same way as the previous example, except that now we have three monostables in each side. Now each monostable in a group has a different period; so if, as before, X1 "saw" the approaching object first, then all the monostables in the associated group would turn on.

The design and construction of electronic "animals" or machines with artificial intelligence

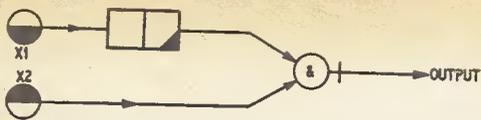


Fig. 6.1. A crude form of property detector for judging speed of moving objects

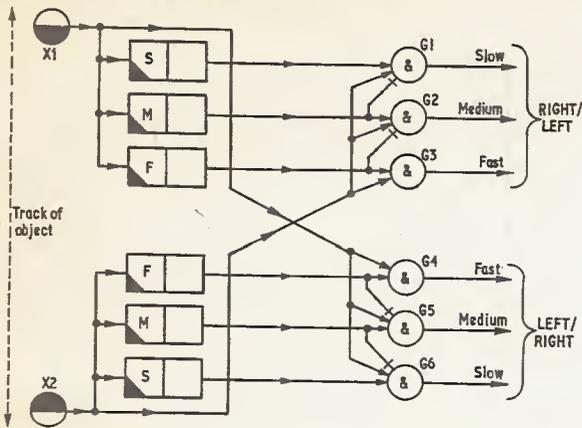


Fig. 6.2. Property detector for judging direction and speed of passing objects

We can arrange to do this by mutually inhibiting each group of monostables with the output from the opposite "slow" element. The machine will now be incapable of looking at anything else until the sampling time is over. Unfortunately, there is no easy way of overcoming this fault of "working backwards" once the sampling period is finished, unless we decide when it is going to "take a look".

COMPLETE CIRCUIT

The constructor might well like to try out the device in Fig. 6.1 for himself, and so in Fig. 6.3 we see the circuit. The monostable used here is fairly conventional and is triggered if X1 (an ORP12) is illuminated. This triggering arrangement, like so many we have used before, is unlikely to require its being preceded by a Schmitt, because generally there is a sufficiently abrupt change in illumination at the photo sensor as to make the inclusion of a threshold element unnecessary.

Following the firing of the monostable, TR2 collector will be at almost ground potential and therefore one half of the gate, TR3, will be enabled. Hence if X2 becomes illuminated at any time during this period, TR4 will be released with the result that the gate output will go negative (the "O" state); thus indicating that the

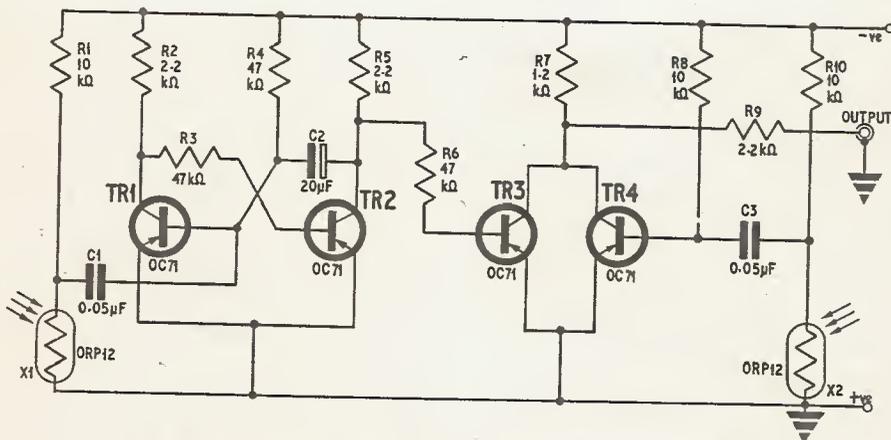


Fig. 6.3. Circuit diagram for property detector outlined in Fig. 6.1

(Notice that the gates at the outputs of the "slow" and "medium" speed monostables have inhibitory connections taken from the next shorter period element.) If the moving object passes X2 before the "fast" monostable has reverted to its stable condition, then a "1" will appear at the output of G3. Without the inhibition at gates G1 and G2 a "1" would occur at their outputs too. Assuming the object was moving less quickly, the "medium" or perhaps "slow" speed monostable would probably "catch it", with the result that G2 or G1 would show a "1".

As with all our schemes this one is not without its gremlins either, because when the object passes the second receptor all the monostables on the opposite side will fire too! Thus, it is only necessary for a further object to enter the machine's purview from the same direction to elicit a false response from G4, G5 or G6. This problem can, to a large extent, be overcome by "playing a waiting game" with the "slow" or longest period monostables.

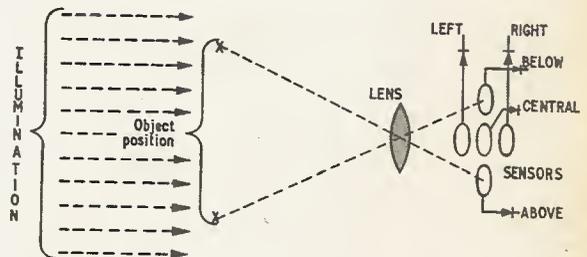


Fig. 6.4. Position detector employing a number of photo receptors. Each sensor delivers an output "1" if the source of illumination is obscured by an object

lighted object passing across the field of view was travelling at a rate faster than the period of the monostable. So far as the machine is concerned, the "apparent" rate of the object will depend on the distance between the sensors.

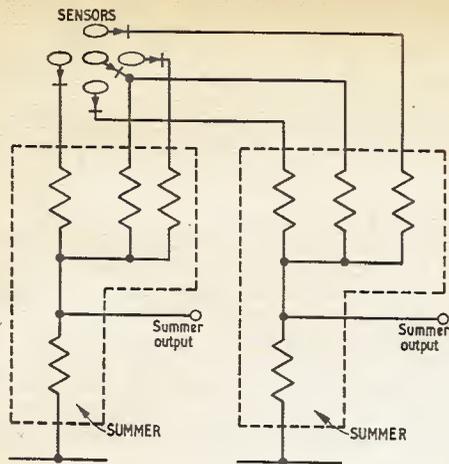


Fig. 6.5. Device for determining length of passing object

POSITION DETECTOR

In addition to establishing the rates of moving objects, there are other factors of which the machine could be made aware without involving a great deal of difficulty. Assuming an object moved into the field of view then it would be distinctly advantageous if its spatial position could be determined. To achieve this the minimum number of photo receptors required is likely to be about five, see Fig. 6.4. However, these five receptor elements are certain to be called upon to perform other functions as well, so the initially somewhat large number would be justified.

The device in Fig. 6.4 has a number of drawbacks, one in particular being the existence of blind spots between receptors. This effect can be reduced by either decreasing the size of the central receptor, so bringing the remaining elements closer together, or alternatively increasing the overall number of receptors. Nevertheless in view of the relative crudeness of the device certain disadvantages must be expected.

DETERMINING LENGTH

Up till now we have assumed that the object within the machine's purview has been "seen" only by one receptor at a time; suppose though that two, or perhaps three, elements become stimulated. This information could (depending upon the distance of the object) be used to obtain a rough idea of the object's length. To overcome the distance problem, and because the blessing of stereoscopic vision is not being considered, we must cheat just a little by standardising the distance at which objects pass the machine.

If all the passing objects now have this standard distance, we could arrange a device like that in Fig. 6.5. This utilises Kirchhoff resistive summing networks driven from the receptors. When an object stimulates just one receptor a certain voltage will appear at the output from the summer; but if more than one receptor is active then the output level will increase accordingly. Depending then on the length of the object, the summer will return either a greater or a smaller output.

Generally, when we think of a particular length (it might be one inch), if asked to describe it or perhaps draw a line of about the same length, we have little difficulty. We do not possess "odd inches" or "yards" of some fictitious stuff in our heads, but the ability to convert realistically none-the-less exists.

Just as we perform these transformations, the machine discussed is in principle doing the same sort of thing: it however converts length to voltage. These voltages although already quantised into relatively discrete "bits" by virtue of the all-or-nothing characteristic of each sensor, need to be referred to some standard value if meaningful information is to be obtained. This can be achieved quite simply by taking each summer output to a circuit like that in Fig. 6.6.

STANDARDISATION CIRCUIT

Consider the case where the image of an object measuring an inch just activates two receptors, and we require to set this as our standard. The summer output at this time may also be causing the standardisation circuit to return an output as well, so this level must be backed-off at VR1 until it is reduced to zero. Then for lesser or greater outputs from a summer, there will be corresponding positive or negative levels appearing at the output of the standardisation unit. It will thereby give an approximation to the size of an object in relation to some definite dimension.

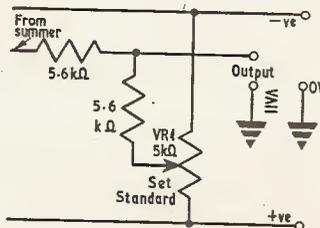


Fig. 6.6 Standardisation circuit for use in conjunction with the device shown in Fig. 6.5

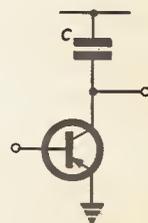


Fig. 6.7. A basic summation circuit

Apart from physical length, property detectors can be designed which determine the duration of an event—or perhaps the length of one event in relation to another. The number of devices which can accomplish this are manifold; the simplest though usually rely upon the necessary summation being performed by linearly charging a capacitor. An arrangement allied to this (though not strictly linear), was seen in the "learning" circuit discussed in the third article of this series.

SUMMATION DEVICE

A basic example of a device which will linearly sum the duration of input events is shown in Fig. 6.7. An "event" of course will constitute the length of time a current flows into the base of the transistor. Now providing this current remains substantially constant, the capacitor will charge linearly towards earth potential. The actual charge that it finally acquires will largely depend upon its capacity and the duration of the charging current. Thus the voltage E appearing across the capacitor will be equal to I_t/C ; where I is the charging current, t the time taken to reach this voltage, and C the value of the capacitor.

It should be remembered that in reading-out the level across the capacitor, only a very high impedance must be applied. Without this precaution the accuracy of any data would be seriously impaired. To meet this need the output is generally fed into an emitter follower, or better still, a Darlington "triplet". Once the information has been read, the capacitor can be discharged and so made available for further use.


HEATHKIT for a Hobby that's Fun and Fascinating

Building Heathkit models is so easy. THE CONSTRUCTION MANUAL SHOWS YOU HOW!



Easy to understand instructions and large, clear pictorials illustrate clearly the step-by-step procedure for enjoying a fascinating hobby that takes you away from the 'workaday' routine. There's also the thrill when you switch on and experience that exhilarating sense of self accomplishment, knowing that you've done something you doubted you could ever do.

FOR EXAMPLE

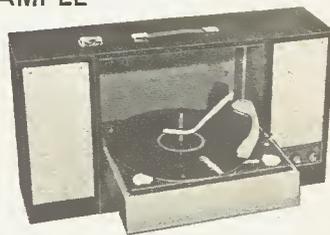


**This
STEREO RECORD PLAYER
IS SO EASY TO BUILD**

- ★ Completely assembled and finished cabinet—no gluing or covering required.
- ★ Completely assembled Record Changer deck. Simply drop in and connect a few wires.
- ★ Only a few components to mount on one printed-circuit board.
- ★ Two 8" x 5" speakers, easily mounted.
- ★ Takes only a few hours to build.
- ★ Suitcase portability.

ALL FOR ONLY **£28.6.0** KIT SRP-1
P. & P. 10/6

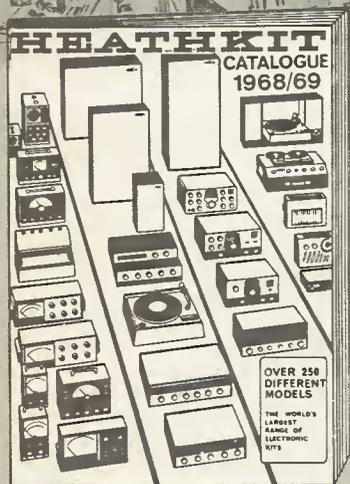Choice of blue/grey or red/grey colour scheme.
(Please state preference)



Up to 50%
savings
over
factory-built
equipment

Send for the FREE CATALOGUE

AND MAKE YOUR SELECTION FROM A WIDE RANGE

The latest Heathkit 36-page full colour catalogue contains details of models for the Hi-Fi and Audio Enthusiast, the Music Lover, the Tape Recordist and the Hobbyist, models for Communication, Test and Servicing, Amateur Radio and Short Wave Listening models for Educational Establishments and Industry. No matter what your vocation, there is something for you in this catalogue.

FREE FACTORY CONSULTATION SERVICE

Heathkit maintain a staff of skilled technical correspondents to advise, help, and answer any questions about selection, construction and use of your model. This service is free. A speedy factory repair service is also at your command should you ever need it.



DAYSTROM LTD.
Dept. PE.4, GLOUCESTER GL2 6EE

Please send me FREE Heathkit Catalogue

NAME.....

ADDRESS.....

SHOWROOMS: LONDON, 233 Tottenham Court Road

BIRMINGHAM, St. Martin's House

GLOUCESTER, Factory

In order to compare (as suggested earlier) the duration of one event with another, the outputs from two summation devices can be fed via suitable buffer amplifiers to a differential circuit. This will then give an indication of the degree of parity existing between the two inputs.

PATTERN RECOGNITION

The next natural step from property detectors is of course pattern recognition devices, and ultimately machines capable of reading the printed word. Research which has been aimed at discovering ways and means for achieving machine recognition (essentially of alpha-numeric, i.e. letters and figures) has been conducted for something like the last 20 years. The fruits of such labours have however been singularly modest; this to a very large extent being the result of inadequate information concerning the recognition processes employed by animals, particularly humans.

Although various forms of automatic character recognition are an actuality today, they nearly all suffer from disadvantages of one kind or another. Typically their abilities seem limited to recognising typefaces in some standard font and size, so that process by which scansion of the characters is performed may be maintained substantially simple and economic.

An example of a scanning process still currently used in some recognition systems is shown in Fig. 6.8. Here is seen the result of scanning the letter "T". The output pulses from the machine are produced by moving the character past a number of receptors; in this way a series of bits (binary digits) can be generated which, following suitable translation, uniquely categorise the letter.

The process of readout from the receptors is essentially in serial/parallel form, although some schemes utilise a single photo-cell which is made to scan each character several times to provide a wholly serial output. This of course is much like the method employed for interrogating the images projected on to



Fig. 6.8. A scanning process used in some character recognition systems

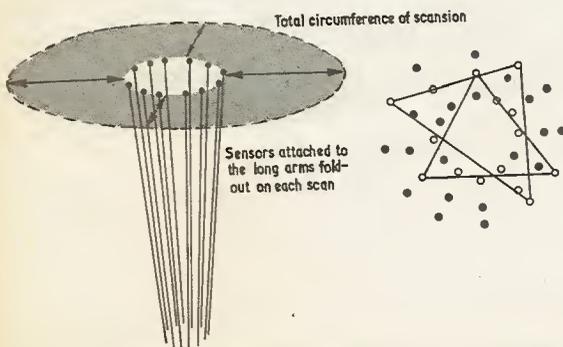


Fig. 6.9. A circular scan system used by one type of machine designed to recognise line drawings (left) pulse pattern when scanning a triangle

the mosaic of a Vidicon camera tube. Indeed, with the remarkable resolution which Vidicons display, it is hardly surprising that they too are now finding extensive use in this application.

MACHINES LIMITATIONS

Despite the severe limitations imposed by current recognition devices, a greater degree of versatility has been achieved by endowing them with memories for several forms of typeface. Nevertheless this form of recognition still falls very short of human capabilities in this field. With consummate ease we can decipher sloppy handwriting, and letters either lost in a background of irrelevant "splodges" or with such a lack of contrast, that one almost doubts if machines could ever approach this standard. To add insult to injury, we also remain perfectly able to read characters in just about any size, configuration, or position. The machine has many problems indeed!

Our considerable feats versus the few merits displayed by some machines do not however constitute a "checkmate". On the contrary, the people involved in this work are unruffled, and treat this more as a challenge than a vain hope.

BASED ON LOGIC

The argument, if argument there is, for the feasibility of really sophisticated pattern classifiers, stems from the fact that every pattern whether a geometrical figure or the written word is equivalent to some logical function in the field of input data. Hence any example of a particular pattern could have a logical value of "1", and any other input would constitute a "0". In simpler terms this means that any visual image either is or is not a square, a circle, an ellipse, a figure "4" or whatever. Thus for any pattern there must exist a unique set of rules for determining what it is.

However, for a machine to recognise, it must needs be capable of generalising to a certain extent. This is essential since, for example, no two B's or even "cows" are necessarily alike. Nevertheless, a "B" is always a "B" regardless of the way it may be written, and a "cow" is a "cow" for all that! Each particular pattern therefore has quite definite invariants by virtue of which it can generally be recognised.

Exceptions to this hypothesis are such figures as squares, which if rotated 45 degrees become diamonds, and with moderate distortion can take on the form of rectangles or even parallelograms. Another difficult figure of course is the "x". This can be taken to mean the letter "x" or a "times" sign; or, if rotated 45 degrees, it becomes a sign for "sum".


Problems of this kind can often be minimised by inspecting such characters in context with others. Hence if a machine is reading across a row of input patterns and it sees, say, a square, there is very little chance that this could be taken to imply a diamond because to make such a mistake the sensors would require to be moving diagonally to their normally accepted direction of travel.

CIRCULAR SCAN SYSTEM

A machine, built in the U.S.A. some years ago, which recognises simple line drawings is certainly worthy of mention here. This is a system which can account to an extent for size, lateral displacement, and rotation of a pattern, yet remain able to recognise it. The machine's ability to perform in this way is largely dependent on the method of scansion and the placement of its receptors during this process, see Fig. 6.9.

RADIO STETHOSCOPE

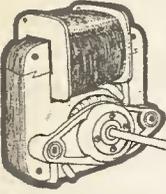Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stethos instead of ear-piece 11/- extra—post and ins. 2/9.




MAINS MOTOR
Precision made as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.



ROTISSERIE MOTOR

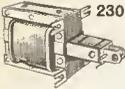Very powerful 7 r.p.m. operates from standard AC Mains. 29/6, plus 3/6 P. & P.



230 VOLT SOLENOID
1in. stroke, size 2 1/2in. x 2in. x 1 1/2in. 14/6, postage 2/9.





SNIPERSCOPE

Famous war-time "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. A golden opportunity for some interesting experiments. 7/6 each, post 2/6. Data will be supplied with cells, if requested.

MAINS TRANSFORMER SNIP

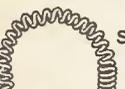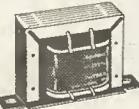Making a power pack for amplifier or other equipment? These transformers have normal mains primaries (230/40v) and isolated secondaries in two types (1) 12v. 500mA. at 8/6; (2) 15v. 500mA. at 8/6.



SPRING COIL LEADS


as fitted to telephones, 4 core 2/6 each, 3 core 2/- each.



PP3 ELIMINATOR. Play your pocket radio from the mains save 5s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions, only 6/6 plus 1/- post.

AC FAN

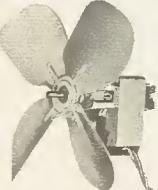Small but very powerful mains motor with 6in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts on back or front with 4BA screws.




TRANSISTOR SET CASE

Very modern cream cabinet, size 6 1/2 x 3 x 1 1/2in. with chrome handle, tuning knob and scale. Price 4/6 plus 2/- postage.



Soil Warming element, 30yds., heavy P.V.C. covering 12/6.

ELECTRIC TIME SWITCH

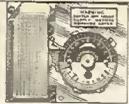

Made by Smiths these are a.c. mains operated, NOT CLOCKWORK ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. 59/8, post and ins. 4/6. Additional time contacts 10/- pair.

VARYLITE

Will dim fluorescent or incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob 23.19.8.




NICAD RECHARGEABLE BATTERY



3-6V-500mA hr.—size 1 1/2 x 1 1/2in. really powerful will deliver 1 amp for 3 hours. Regular price 32/6 each—our price 00/0 each. New and guaranteed. Other voltages available. Single cell 1-2V 6/8. 5 cell 6V 29/6.

ELECTRIC CLOCK WITH 20AMP SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another timer or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—new and unused only 45/- less than the value of the clock alone—post and ins. 2/9.

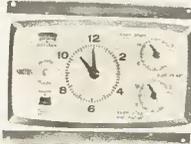

THIS MONTH'S SNIP

CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer a British made £31 outfit for only 20.19.8, brilliantly designed for speed and efficiency—cassette takes normal spools/drops in and out for easy loading—all formal functions—accessories include: stethoscopic earpiece—crystal microphone has on/off switch—telephone pick-up—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY, 24.19.8 plus 7/6 post and insurance. Footswitch 18/6 extra. Spare Cassettes at 4/6 each, three for 10/-.



HI-FI BARGAIN

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi Lead and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S.—Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1 1/2in. diam.—Overall height 5 1/2in. A 65 speaker offered for only 23.9.8 plus 7/6 p. & p. 15in. 30W 27.19.8 plus 7/6 post and ins. Don't miss this offer.



DRILL CONTROLLER



Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/8 plus 2/6 post and insurance. Or available made up 29/8, plus 2/6 post.



PROCESS TIME CONTROLLER



Made by Smiths, motorised and mains driven, enables 15A circuit to be started up to 18 hours in advance and to stay on for a period from 15 minutes to 3 hours. Totally enclosed in metal box with glass front and chrome surround. 49/6, plus 4/6 post and ins.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

REED SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass in cased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- a dozen. Suitable magnets are 1/- each.

When postage is not stated then orders over £3 are post free. Below £3 add 2/6. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

Multi Purpose Neon Test Unit. Robust, useful and instructive, tests insulation, capacity, continuity, resistor, volume controls, also acts as signal injector, and L.T. fault finder, kit comprises neon indicator, 4-way water switch, ebomite tubes, resistors-condensers, terminals, etc., with diagram, only 9/8, plus 2/- post and insurance.

Tuning Condenser. Solid dielectric, .0005 mfd, variable 2/6 ea. 24/- doz.

A.E.I. Fractional H.P. Motor. 200/250V 50/60c/s enclosed, continuous rating 1/40 h.p., ex. equip. Perfect order, 19/8, plus 4/6.

Experimenting with ultra violet? Philips U.V. lamp, 16/8; holder and control gear 19/8.

G.E.C. Black Light Tube for experiments and special lighting effects—40 watt 2ft. tubes only, 14/6 each; holders and control gear, 19/8, plus 4/6 post.

Clock Motor. 230V 50c/s synchronous—self-starting, 6/6.

Pentode Output Transformer. Standard size, 40-1, ex-equipment but OK, 4/3 each, 45/- doz. Post paid.

E.H.T. Condenser. 0-1 mfd. 5kV, 8/6 each.

Neon Mains Tester. 1/3 each, 12/- doz.

Flood Lamp Control. Our dim and full switch is resistor condenser, terminal flood lamp; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pairs or where circuit can be split exactly in half. Technically the switch is known as a double-pole change over with off. Our price 4/6.

Sub-Miniature Silicon Diodes. General purpose type with gold-plated leads, 1/- each or 7/6 per dozen.

Message Tapes. 225ft. Tape on 3in. spools, normally 4/6 each, we offer 4 tapes for 12/6.

White Circular Flex. Ideal for lighting drops, twin made by BICC. Usually 8d. yd. 100yd coil for 30/-, plus 6/- postage.

Edgewise Control. Morganite, as fitted many transistor radios, 2K or 5K with switch, 2/6 each or 24/- per dozen.

12V Inverter. Full transistorised for operating a 20-watt fluorescent tube, size 6in. long x 1 1/2 x 1 1/2. 23.10.0. Post and insurance 3/-.

Silicon Rectifier. Equiv. BY100 750mA 400V, 10 for 20/-.

Miniature Pickup for 7in. records made by Comco—crystal cartridge made with sapphire stylus only 10/0 or 36/- dozen.

Headphones. Ex W.D. unused and perfect, low resistance. Single with headband 4/6. Double with headband 8/6.

Midget Neons for mains indicators, etc., 1/3 each or 12/- dozen.

Compression Trimmers. Twin 100pF, 1/- each; 9/- per dozen.

3in. PM Loudspeaker. 8 ohm, 12/6; 80 ohm, 18/6

Rotary Cam Operated Switch. 12 positions each of which close a separate pair of contacts except the last which leaves them all open. Contacts rated at 250V 15 amps, 15/- each.

Rotary Cam Operated Switch. 4 positions: 1st position all contacts open; 2nd contact 1 closed; 3rd contacts 1 and 2 closed; 4th contacts 1, 2 and 3 closed. Contact rated 250V 16 amps, 8/6 each.

Breat Microphones. Fine American made dynamic type, suitable or breast plate with neck straps, 7/6, post 4/6.

Circular Fluorescent. 22 watt, 9in. diam. tube complete with choke, starter, holders and chrome clips, 29/6, post, etc., 4/6.

Midget Relay twin 250 ohm coils, size approx. 1 1/2in. x 1in. x 1in. 4 pairs changeover contacts, 7/6 each.

Pocket Test Meter, measures a.c. volts (3 ranges), d.c. volts (3 ranges), ohms, milliamps, ideal to carry around. Complete with instructions and test leads. 39/6, plus 2/6 p. & p.

Printed Circuit Board Edge Connector, solder terminations. 32 contacts, standard spacing for veroboard, etc. 6in. long but easily cut. 7/8 each, 80/- doz.

1,000V Fire Spiral, replacement for most fires. 1/3 each, 12/- doz.

50 ohm 50 watt Wire Wound Pot-meters, 2/6 each. 1 Meg Miniature. Pot-meter Morganite standard 1in. spindle 1/- each; 9/- per dozen.

ELECTRONICS (CROYDON) LTD.
Dept. PE, 266 London Road, Croydon CRO-2TH
Also 102/3 Tamworth Road, Croydon

NEW 1969 EDITION WORLD RADIO-TV HANDBOOK

35/- Postage 1/-

RADIO COMMUNICATION HANDBOOK, by R.S.G.B. 63/-. Postage 4/-.

LASERS WORK LIKE THIS, by Egon Larsen. 16/-. Postage 1/-.

COLOUR TELEVISION, PAL SYSTEM, by G. N. Patchett. 40/-. Postage 1/-.

RADIO COMMUNICATION, by J. H. & P. J. Reyner. 45/-. Postage 2/-.

TRANSISTOR & ELECTRONIC ORGANS FOR THE AMATEUR, by Alan Douglas. 18/-. Postage 1/-.

ELECTRONICS POCKET BOOK, edited by J. P. Hawker & J. A. Reddihough. 21/-. Postage 1/-.

THE ELECTRONIC MUSICAL INSTRUMENT MANUAL, by Alan Douglas. 55/-. Postage 1/6.

TAPE RECORDER SERVICING MANUAL, by H. W. Hellyer. 63/-. Postage 3/6.

NEW CATALOGUE. 2/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET

LONDON, W.2

Phone: PAddington 4185

Closed Saturday 1 p.m.

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 37/6. 11 element, 45/-. 14 element, 52/6. 18 element, 60/-. **Wall Mounting with Cranked Arm**, 7 element, 60/-. 11 element, 67/-. 14 element, 75/-. 18 element, 82/6. **Mast Mounting with 2in. clamp**, 7 element, 42/6; 11 element, 55/-. 14 element, 62/-. 18 element, 70/-. **Chimney Mounting Arrays**, Complete, 7 element, 72/6; 11 element, 80/-. 14 element, 87/6; 18 element, 95/-. Complete assembly instructions with every unit. **Low Loss Cable**, 1/6 yd. U.H.F. Pre-amps from 75/-. State clearly channel number required on all orders.

BBC • ITV AERIALS



BBC (Band 1), Telescopic loft, 25/-. External S/D, 30/-. "H", 22.15.0.

ITV (Band 3), 3 element loft array, 30/-. 5 element, 40/-. 7 element, 50/-. Wall mounting, 3 element, 47/6. 5 element, 52/6.

Combined BBC/ITV, Loft 1+3, 40/-. 1+5, 50/-. 1+7, 60/-. Wall mounting 1+3, 57/6; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.
VHF transistor pre-amps, 75/-.
COMBINED BBC1-ITV-BBC2 AERIALS 1+3+9, 70/-. 1+5+9, 80/-. 1+5+14, 90/-. 1+7+14, 100/-. Loft mounting only. Special leader available.

F.M. (Band 2), Loft S/D, 45/-. "H", 32/6. 3 element, 55/-. External units available. Co-ax. cable, 8d. yd. Co-ax. plugs, 1/4. Outer boxes, 3/-. Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 6/-. Send 6d. stamps for illustrated lists.

CALLERS WELCOME

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)

40-41 Monarch Parade
London Road, Mitcham, Surrey
01-448 4884

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 9/6 extra.

INTERCOM/BABY ALARM



65/-

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/3)
189 KENSINGTON HIGH STREET, LONDON, W.8

THE ELECTRONIC COMPONENTS CATALOGUE THAT SETS THE STANDARD

Used and
acclaimed by:—

**SCIENTISTS
ENGINEERS
TECHNICIANS
TEACHERS &
STUDENTS**

This edition of the Home Radio Catalogue is the result of eleven years of careful selecting, compiling and indexing.

It is the finest, most comprehensive we have ever produced—it has 300 pages, over 8,000 items listed and over 1,500 illustrations. It is a must for anyone interested in radio and electronics. With each catalogue we supply a Book Mark giving Electronic Abbreviations, an Order Form, an addressed envelope, and 6 vouchers each worth 1/- when used as directed. All this for only 8/6 plus 3/6 post, packing and insurance. Send the attached coupon today, with your cheque or P.O. for 12/-.

Please write Name and Address in block capitals

NAME

ADDRESS

Home Radio (Mitcham) Ltd., Dept. PE, 187 London Rd.,
Mitcham, CR4 2YQ

Of course no catalogue is ever really finalised. As soon as we have one edition off the press, our researchers get busy finding out what is the latest in the world of Radio and Electronics—ready for the next printing.

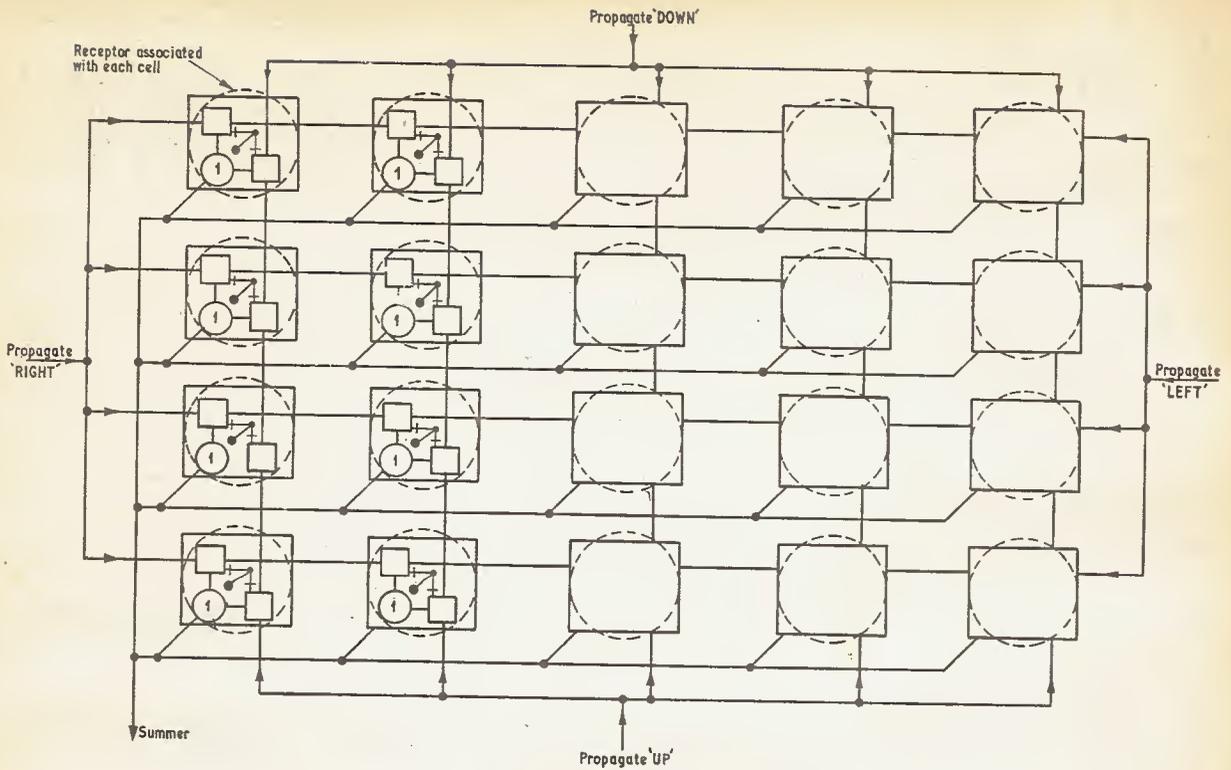


Fig. 6.10a. Basic principles of the fixed matrix system. Note: separate hold, trigger, and reset lines not shown

The receptors which form a circle are mounted at the ends of long scanning arms controlled by a motor-driven "iris-like" device. Thus as the motor runs, the iris progressively opens and the arms fan outwards. In this way the receptors are caused to describe a circular scan, and optically interrogate any illuminated pattern presented before them.

It will be seen that if during the scanning process the output from the receptors is sampled, the result will essentially consist of a series of "off" pulses. Furthermore, in the case of a triangle for example, the pattern of signals will almost invariably consist of a "wave" of three separate groups of pulses. Substantially this will hold true despite variations in orientation—the degree of spacing between the signals will in fact afford a measure of information about the shape of the triangle too. Actual identification of a pattern can of course only come following suitable processing.

FIXED MATRIX SYSTEM

Since the inception of this last type of machine, others possessing even more sophisticated modes of operation have come into being. A particularly exotic device was one which appeared (in experimental form) during 1965. This, instead of utilising a scanning system of moving sensors, relies upon a whole matrix of stationary elements upon which the image of the character to be recognised can be mapped. An understanding of the basic operating principles of the machine is best gained by initially referring to Fig. 6.10a.

In the illustration only an extremely small matrix is considered: in practice, a matrix containing an array of something like 30×30 elements would be used. Each

sensor in the matrix is connected so as to inhibit the output of a cell containing essentially a pair of bistable elements and an OR gate, every gate output passing along common lines to a summing network.

Assuming initially that no image is mapped upon the cells, then none of them will be inhibited; thus as we apply a pulse to any one of the "propagate" inputs, each one of the bistables in the rows or columns will switch successively until this wave of activity ends at the edge of the matrix when they will all be turned "on". Hence all the associated OR gates will present an output, resulting in the summer returning a maximum level. So far, so good!

Facilities (not shown in Fig. 6.10a) do exist for resetting the bistables, and we will accept now that they have all been reset. We might now consider the case where an image has been mapped upon the sensors. For the sake of simplicity we will assume that the machine is expected to recognise any character in a three letter alphabet; this will comprise the letters U, T and H.

RIGHT AND LEFT PROPAGATION

Now depending on the character being interrogated, there will result a corresponding image on the sensors, causing the associated cells to be inhibited. (At this stage it is important to realise that once the cells have been switched or inhibited they will, unless reset, act as barriers to propagation. A propagation can hence continue along every row/column until it encounters either a "barrier" or one of the edges of the matrix.)

Referring to Fig. 6.10b it will be seen that if we propagate "right" then "left", a different result will



1 Initial mapping for the various characters



2 State of the matrix following right/left propagation



3 Matrix state after propagation down

NOTE: Cross hatching indicates degree of summation for the various characters following each operation

Fig. 6.10b. Images formed on sensors as characters are interrogated



1 Initial mapping



2 Matrix state following usual right/left and down propagations



3 State of matrix after holding of unexposed area resetting the remainder and triggering the held segment



4 Final propagation right and left to reduce the character mapped on the matrix

Fig. 6.10c. Modified operation to deal with difficult characters

exist for each character. Thus if, following this operation, we inspect the summer output and discover this to be at maximum, then it can be concluded that the letter T is present. Conversely, if the summer does not return such a result, we can assume that the character must be either a U or an H.

If we continue the operation by propagation "down" the matrix, then check the summer level again, we can now be certain about the identity of the character. A maximum output will thus correspond with the letter U, and a lower output with an H. In practice the summer is generally fed into a number of Schmitt triggers set to fire at the different thresholds corresponding to various patterns.

TRICKY CHARACTERS

The capabilities of the machine are now however limited to just U, T and H. Consider the result of "throwing a spanner in the works" by presenting the machine with an M (Fig. 6.10c).

The same routine as described before can be applied, but when we come to the decision "is the character an H or an M?", the operation must obviously be modified. The procedure adopted is then to "hold" the unexposed area of cells whilst removing the image and resetting the remainder; following this (and by applicable gating arrangements) the "held" area is then inhibited.

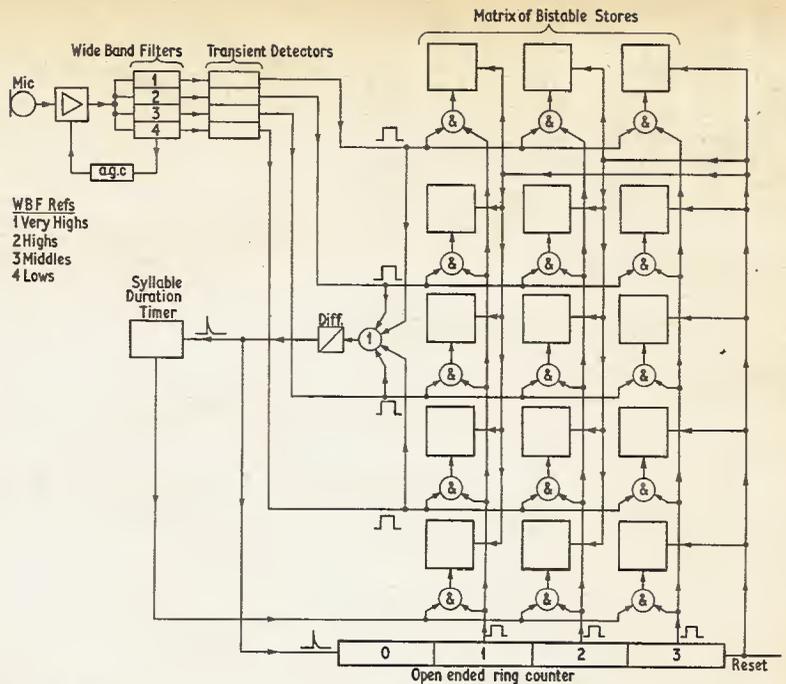


Fig. 6.11. A possible system designed for simple word recognition

If we again propagate "right" and "left", the summer will return a maximum level for the letter H, and (by virtue of a partly unexposed area) a lower level in the case of an M. By similar "artful dodges" this type of machine can be extended to not only the task of recognising the whole of the alphabet (a real one that is!), but also to "reading" characters in different sizes and fonts.

SPEECH RECOGNITION

Yet other devices have been "dreamt up" for recognition of the spoken word; most of these machines are however even more complex than the last! Nonetheless, one relatively simple example of this form of machine will be given now.

Such a machine might be of the adaptive kind; that is to say it could be *taught* to recognise a certain vocabulary of input words. The actual number of words to be "understood" by the device would be restricted according to the application.

Let us then, for convenience, choose a vocabulary comprising ten words; these might be the numbers zero through to nine. Several avenues for achieving an initial segregation of these input sounds are open to us; we however are only interested in ten basic types, and so the encoding method can be kept relatively uncomplex.

Referring to Fig. 6.11 we see a rather interesting example of a machine that could be built for simple word recognition. The input sounds are first passed to an audio amplifier which, possessing a measure of a.g.c., maintains signal amplitudes within reasonable limits. The amplifier output is then fed via a bank of four wideband filters to separate transient detectors which indicate either the presence or absence of a particular group of frequencies. In this way the various speech

LOOK!

PRACTICAL!

VISUAL!


EXCITING!



a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .


1 ▶ **OWN and HANDLE a**

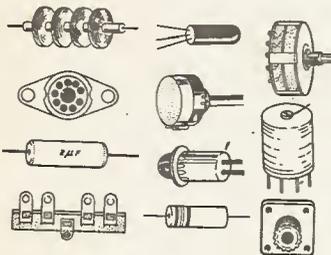complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ **BUILD and USE**

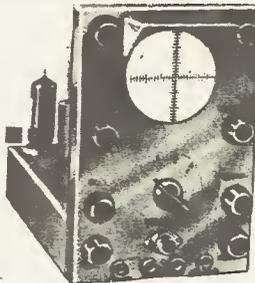a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ **READ and DRAW and**

UNDERSTAND CIRCUIT DIAGRAMS

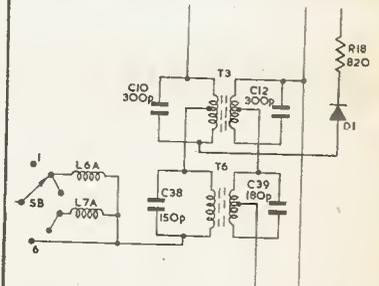

4 ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... **BLOCK CAPS**

ADDRESS..... **PLEASE PE 4**

GEATRONIX LIMITED


EDUCATIONAL ELECTRONIC EQUIPMENT

MANUFACTURERS OF

NORKIT

A new HOBBY for the automation age

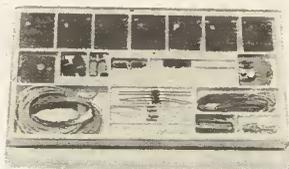- ★ Simple building bricks to build your own ELECTRONIC BRAINS.
- ★ Easy to understand handbooks to guide you.
- ★ Learn about LOGIC, BINARY arithmetic and BOOLEAN algebra.
- ★ Modules are rapidly assembled and dismantled to use again.
- ★ Make machines that play games, control model railways, etc. and control automatic machines of any description.




NORKIT JUNIOR £8.16.0
(as shown)

NORKIT SENIOR £17.12.0
Handbooks supplied for each kit or available separately 6/- each

LOGIC DEMONSTRATION UNIT TYPE LDU.1

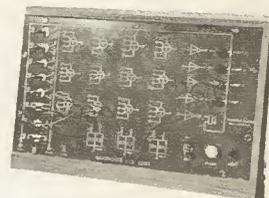A new teaching aid for rapidly setting up and demonstrating logic circuits. Stackable patching leads are used to interconnect logic symbols on a mimic diagram. The symbols are connected to appropriate components inside the unit. Switches and pushbuttons are provided to simulate input conditions and outputs are indicated by lamps and an audible alarm.



£68.0.0

Telephone: SOUTHEND 62521

GEATRONIX LTD., 28 REDSTOCK RD., SOUTHEND-ON-SEA, ESSEX

DIOTRAN SALES

P.O. BOX 5
WARE, HERTS
TEL.: WARE 3442

Nowhere in the world can you buy semiconductors cheaper than from us. We are the largest purchasers of manufacturers' surplus stocks, and can fulfill any requirements at competitive prices. S.A.E. for full lists.

Post and Packing costs are continually rising. Please add 1/- towards same. **CASH WITH ORDER PLEASE**

OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD

1/- each	TESTED TRANSISTORS ONE PRICE ONLY PNP. NPN. SILICON PLANAR 1/- EACH	1/- each
BC108	2N696 2N1132 2N2220 2S733	
BC109	2N697 2N1613 2N3707 2N3391	
BFY50	2N708 2N1711 2N3711 T1S44	
BFY51	2N708 2N2904 2S102 2N2906	
BFX84	2N929 2N2905 2S103 2N2907	
BFX86	2N930 2N2924 2S104 2N2696	
BFX88	2N1131 2N2926 2S732 2N3702 2N3703	

From Manufacturers' Over-runs—Unmarked Plastic and Metal cases.

GERM. PNP AND NPN TRANSISTORS FULLY TESTED, UNMARKED 1/6 EACH	1/6 each
AC125 ACY22 ACY36 NKT677 OC81 2G381	
AC126 ACY27 NKT141 NKT713 OC82 2G382	
AC127 ACY28 NKT142 NKT773 2G301 2G399A	
AC128 ACY29 NKT212 OC44 2G302	
AC130 ACY30 NKT213 OC45 2G303	
ACY19 ACY31 NKT214 OC71 2G308	1/6
ACY20 ACY34 NKT215 OC72 2G371	
ACY21 ACY35 NKT271 OC75 2G374	each

POWER TRANSISTORS	5/- each
OC25 OC35 NKT403 ASZ17	
OC26 AD130 NKT404 T13027	
OC28 AD140 NKT405 T13028	
OC29 AD149 NKT452 T13029	

Manufacturers' Surplus Germ. A.F.

TEXAS SILICON ALLOY TRANSISTORS
2S302 Eqr. OC200 VcB40 Hfe 15-50 1-49 off 3/6 each
2S303 " OC201 VcB25 Hfe 25-75 5-99 off 3/- each
2S304 " OC202 VcB15 Hfe 45-120 100 off 2/6 each
ALL BRAND NEW, FULLY GUARANTEED AND MARKED.

HIGH QUALITY SILICON PLANAR DIODES.
SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, 1S130, 1S940. 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD.

MIXED SILICON PLANAR TRANSISTORS NPN TO-18 CASE. Transistors to fill a number of requirements like 2N706, 2N708, BSY27, BSY95A, etc. 500 off, £5; 1,000 off £8.10.

THYRISTORS (S.C.R.'s), FULLY TESTED, BRAND NEW AND CODED: TO-5 CASE

Type No.	PIV	Amp	Each
2N1595	50	1	7/6
2N1596	100	1	8/-
2N1597	200	1	10/6
2N1598	300	1	14/-
2N1599	400	1	15/-
BTX30-500	500	1	22/6
BTX30-600	600	1	25/-

TO-46 CASE (STUD)

Type No.	PIV	Amp	Each
2N1771	50	4-7	9/-
2N1772	100	4-7	9/6
2N1774	200	4-7	12/6
2N1776	300	4-7	16/6
2N1778	500	4-7	19/-
2N2619	600	4-7	30/-
BTY79-150	150	4-7	12/-
BTY79-250	250	4-7	14/-
BTY79-400	400	4-7	20/-

TO-48 CASE (STUD)

Type No.	PIV	Amp	Each
2N682	50	16	12/-
2N683	100	16	12/-
2N685	200	16	19/6
2N687	300	16	25/6
2N688	400	16	32/6
2N689	500	16	47/6
2N690	600	16	50/-
2N691	700	16	55/-
2N692	800	16	62/-

BRAND NEW FULLY TESTED EPOXY CASE UNIJUNCTION TRANSISTORS. Type T1S43 and BEN 3000 and replacement for 2N2646. Full data available. **LOWEST PRICE AVAILABLE ANYWHERE.** 100 off 4/- each = £20; 500 off 3/6 each = £87.10; 1,000 off 3/- each = £150. Sample devices 7/- each on request.

SILICON PLANAR PLASTIC TRANSISTORS. 2N3708A VcB30 Hfe 20-60. All marked, fully tested and guaranteed. 1 off 1/6 each; 100 off 10d. each; 500 off 9d. each; 1,000 off 7½d. each.

TO-18 METAL CAN SILICON PLANAR TRANSISTORS. VERY HIGH QUALITY 99% good. Type 2N706 BSY27 £7.10 per 500 pieces; £12.10 per 1,000 pieces.

PRINTED CIRCUIT BOARDS with usable length leads on both Transistors and diodes. All Mullard devices with the exception of the 2G371 which are Texas.

EACH PANEL CONSISTS OF THE FOLLOWING:—

"A" 8 × OC43, 24 × OA81	12/- per Panel
"B" 64 × OA81	20/- per Panel
"C" 8 × 2G371	5/- per Panel
"D" 16 × OC84	15/- per Panel
"E" 8 × GET875, 24 × OA81	10/- per Panel
"F" 8 × GET114, 20 × OA81	8/6 per Panel
"G" 8 × 2G371, 12 × OA81	7/6 per Panel
"H" 8 × GET114, 12 × OA81	8/6 per Panel
"I" 8 × OC84	9/- per Panel
"J" 4 × OC28, 4 × FST1/0	15/- per Panel
"K" 4 × OC35, 4 × FST1/0	12/- per Panel
"L" 32 × OA81	3/- per Panel
"M" 4 × GET875, 2 × OA81	3/- per Panel

TRANSISTOR EQVT. BOOK

2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Exclusively distributed by DIOTRAN SALES. 15/- EACH.

Vast mixed lot of subminiature glass diodes. Comprising of silicon germ. point contact and gold bonded types plus some zeners. 500,000 available at Lowest of Low Price.

1,000 pieces £3.0.0. 5,000 pieces £13.10.0. 10,000 pieces £23.

Type No.	PIV	Each
IN4001	50	1/3
IN4002	100	1/6
IN4003	200	2/-
IN4004	400	2/9
IN4005	600	3/3
IN4006	800	3/9
IN4007	1,000	4/9

sounds (i.e. vowels, through to the dentally generated fricatives like "S" and "F") can be broken down into their respective components.

Now the utterance of every syllable in a word can be reckoned to have a duration of some average time. So if we settle on a value for this the signals can be encoded into two further categories, i.e. those within such a duration, and those whose length exceeds this.

Following the breakdown of a word into these discrete bits, it is necessary to store this data in order that the machine can be taught to assign a particular meaning. Storage of the information may be performed in a series-parallel fashion, by sequentially gating the signals into the columns of a bistable matrix.

RING COUNTER

This function is achieved by utilising the leading edge produced by any one of the signals to step-up an "open-ended" ring counter controlling the input gating to the matrix. Hence, the presence of components in the first three syllables of a word will be successively represented as a binary number in any of the first few rows of the matrix. The fifth row in the matrix is reserved for syllable duration information: this is derived from a timer (also triggered by the start of any signal) which generates a pulse only if a syllable exceeds some previous duration. No output pulse will appear from the timer if the next syllable occurs prior to the completion of this period—in fact the timer will be reset for the next duration.

LEARNING ABILITY

Having placed all this data into a memory, facilities must now exist which permit the machine to learn. This can be performed by first feeding the matrix outputs into an even larger matrix and, by so doing, expanding the original pattern to show it up in greater detail. The data stored in this expansion matrix can then be passed to a number of binary "weighted" decision devices corresponding with the various positions in the matrix. Combinations of outputs from the decision devices can then be used to drive a particular lamp relating to the spoken number at the input to the machine.

If the incorrect lamp comes on, the machine must be trained to give the right answer by manually adjusting the "weights" in its decision devices until it becomes successful. Once the machine has been trained for one word, further inputs may then be given—however as this process continues it may require re-training for some of the original words.

IN CONCLUSION

Throughout the present *Bionics* series, we have tried to capture just a mere glimpse of those aspects of electronics which hitherto only a few of us are likely to have come in contact. For various reasons much has been omitted; however it can be expected that further articles on this subject will appear in due course. Some of these, it is anticipated, will take the form of actual constructional projects: for example, one will be concerned with the fabrication of chemical memory devices, while another is likely to deal with a more sophisticated version of the "animal" *EMMA* described elsewhere in this month's issue.

In the meantime, it is the author's hope that he might have widened (just a little) the scope of amateur electronics, and simultaneously portrayed the folly in believing that living animals are essentially uncomplicated things. ★

NEWS BRIEFS


Solar Storm Probe

THE first launch by the European Space Research Organisation of a fully stabilised sounding rocket payload, from the Salto di Quirra range in Sardinia, carried an experiment designed to probe solar storms and assess the amount of X-ray radiation emitted from them. Such research is important because of the health hazard presented to astronauts and passengers in supersonic airliners by hard radiation. An understanding of such storms may also enable short wave blackouts to be predicted. The payload was aligned with the sun's centre to an accuracy of one three-hundredth of a degree by an attitude control unit supplied by Elliott Space and Weapon Automation Ltd.

Concorde Engines Simulator

A CONCORDE engines simulator, for training airline pilots and ground crew, has been ordered from Hawker Siddeley Dynamics by Rolls-Royce. The trainer (see picture) will be installed this Autumn in the Patchway (Bristol) Training School, of the Bristol Engine Division, pioneers in propulsion system trainers. It will simulate the Rolls-Royce Bristol/SNECMA Olympus engines of the Concorde supersonic airliner in all flight phases. Faults can be injected by the instructor at any stage of the training programme.

In addition, the trainer can simulate engine ground running, without noise, and can be used in conjunction with airline checkout and engine test equipment for ground crew training. Engine instrumentation in the trainer's Concorde flight deck mock-up is represented by realistic, inexpensive simulated instruments which receive information direct from a digital computer. The trainer is easy to maintain and programming is simple and flexible; no specialised computer training is required.

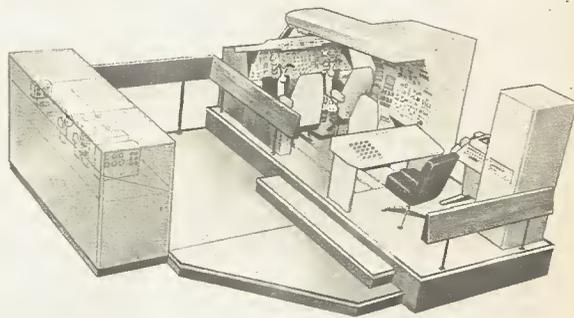

British Amateur Electronics Club

THE BRITISH Amateur Electronics Club now boast twenty overseas members, and is increasing all the time.

Two members serving in the British Forces in Germany have arranged an announcement to be made on their local radio programme about the activities of the club, and hope this will encourage other members of the overseas Forces to join.

The club issues a regular Newsletter to all its members containing much technical information and details of constructional projects as well as club activities and future functions. Newsletter No. 11 contains details for a Noughts and Crosses Computer and an Electronic Roulette (inspired by an article in P.E.).

ORBITING OBSERVATORY

One of the astronauts speaking of the *Apollo 8* flight made the point that although the situation in the sky, so far as the Earth and moon were concerned, took on an entirely new aspect when viewed from the spaceship, the stars were completely unchanged except in respect of clarity. This emphasises the fact that the galaxy and all that lies beyond needs instruments for exploration.

The advantages of being free from the Earth's atmosphere makes near space and the moon itself an obvious place for such instruments. Space platforms are already one evolving method. Here a team of observers will be able to operate sophisticated apparatus with direct control. The cost of such space laboratories will be high but inevitable.

SPACEWATCH

By Frank W. Hyde

In the meantime a half-way house is afforded by the Orbiting Astronomical Observatory. Launched at the beginning of December 1968, America's OAO is engaged on the most extensive mapping of the heavens ever undertaken. It is the heaviest unmanned satellite that has been put into orbit by the USA. It weighs some 2 tonnes and carries 11 telescopes. Its expected lifetime is six months but it may last longer. If it should last a year it will be able to chart some 100,000 stars and should it be fortunate that it lasts for two years then the whole sky will be mapped. OAO is in a circular orbit 474 miles above the Earth.

The mapping programme will be carried out by a battery of four telescopes. They were built by the Smithsonian Astrophysical Observatory under the direction of Dr F. L. Whipple. The heart of the system is a special television tube which is sensitive to ultra-violet light. The telescopes will lock onto a star and study the wave emission bands in the ultra-violet spectrum before moving on to the next star.

The other seven telescopes were built by the University of Wisconsin under the direction of Dr A. D. Coope. This unit is for the study of a limited number of stars each day. The programme is to be concentrated on "young stars" and also interstellar dust from which new stars are brought into being. A young star is one which is of the order of 100,000 years old and too faint to be seen by Earth based telescopes.

The telescope packages are fitted at either end of the satellite which is 10ft long. They will share the

observing time working a week at a time in turn.

The satellite is fitted with a special stabilising system designed so that even at its orbital speed of 16,000 miles per hour the telescopes can be pointed with an accuracy sufficient to lock on to the stars chosen. As a comparison it is about equal to being able to distinguish between two marbles at a distance of about 150ft.

Power supply is obtained from solar cells in panels which extend about 21ft.

Information is stored on tape and disc and on each orbit the storage systems transmit the information to the ground stations. The Smithsonian unit can be used in "real time", that is, it can directly relay its observations on command. Six ground stations receive the transmission as the satellite orbits the Earth. A computer aboard the satellite can store 256 commands, more than for any previous satellite.

Until now the observations planned in this orbiting observatory have been accomplished only on a few occasions with sounding rockets and balloons. Now there will be a continuous observation, with this and other craft to be launched later, in the gamma-ray, X-ray, and ultra-violet spectrum. It is thought by Dr H. Friedman, an astrophysicist, that X-ray stars may be more numerous than ordinary stars and if this is so new light may be thrown on the origin of the universe.

MARS MISSIONS

It is three years since the first space probe sent back pictures of Mars on its close fly-past. This year there are to be two more such missions.

In 1965 when the spacecraft took 21 pictures from a distance of 6,000 miles they showed that the surface of the planet was marked with craters like the moon. The new spacecraft will be able to approach within about 2,000 miles and there will be a more sophisticated two camera system on board which will

take some 66 pictures, some of them with a resolution of the order of 300 yards (as seen by the naked eye).

One spacecraft is to fly by the south polar cap and the other by the equator. At the time of closest approach to the planet the two vehicles will be about 62 million miles from the earth. The two camera system which will have wide angle and narrow angle facilities will take pictures of the whole disc and close-ups of specified areas. The spacecraft will carry other scientific equipment to provide information about the martian atmosphere and surface.

The weight of the craft has increased to 900lbs each as compared with 575lbs on the previous mission. The radio transmitter power is increased from 10 to 20 watts. The power is supplied by banks of solar cells incorporated in the four "sails" and a high gain dish antenna is used for maintaining contact with Earth.


RADIO CAMERA

A new radio camera device is being developed which will enable the reflection of radio waves to be used to produce pictures with the aid of a special emulsion and laser light. The camera has been developed to make use of the fact that when radio waves are directed at a target a small amount of heat is generated.

The back scatter of waves from a reflecting source, such as a ship for example, is directed on to a plate which has a special assembly. A sandwich of heat sensitive cholesterol backed by mylar plastic to pick up the reflected radio waves, and coated with a thin film of crystals suitable for the production of an image when bathed in laser light. The plate is processed as a negative and contains all the information as a refractory pattern. A laser beam played on the pattern produces a hologram with three dimensional image.

There are many applications for such a camera leading to safety measures for ships and aircraft, examining plastics, even to discover if unborn babies are single or twins.

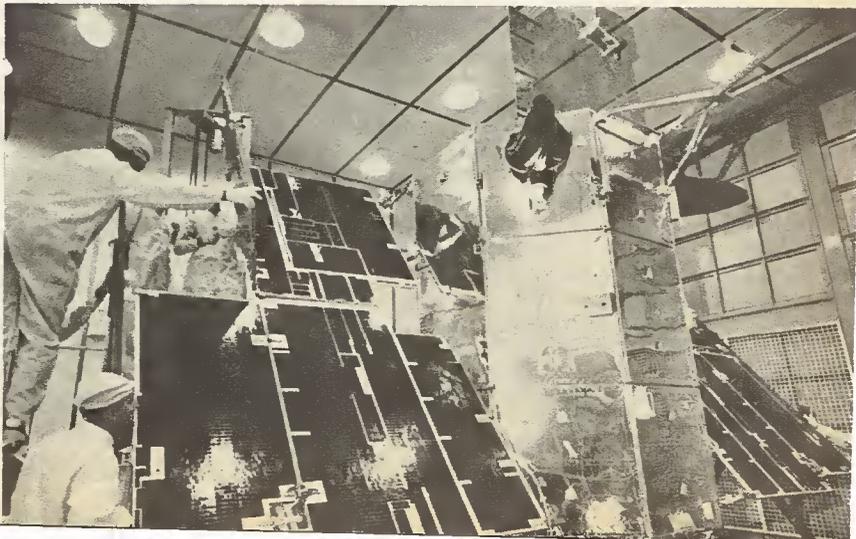The Orbiting Astronomical Observatory (OAO-2) undergoes final tests



BI-PAK



"KING SIZE"

BI-PAK SEMICONDUCTORS

SALE

500 Chesham House
150 Regent Street
London, W.1

**BARGAIN'S
GALORE**

**20% OFF THESE KING
SIZE TESTED PAKS. NORMAL
PRICE 10/-. SALE PRICE 8/-**

Pak No.	Description	Price
A14	4 npr Germ. Switching Trans., assorted	8/-
A15	20 Red Spot A.F. Trans., pnp tested	8/-
A16	16 White Spot R.F. Trans., pnp tested	8/-
A17	4 OC77 type Trans.=ACY24, OC309	8/-
A18	4 High Current Germ. Switching Trans., eqvt. OC42, CV7042	8/-
A20	3 200Mc/s Sil. Planar Trans., npr BSY27	8/-
A22	5 2G417 Trans., eqvt. AF117=AF137	8/-
A23	3 npr Germ. Trans., NKT773=AC130	8/-
A25	2 Drip Trans., 2N1225, RCA=AF118	8/-
A26	6 A.F./R.F. Trans., OC44/45/81/81D plus 1 Diode	8/-
A37	4 OC75 Trans. Type=NKT213, AC125	8/-
A39	2 OC139 npr Germ. Switching Trans.	8/-
A40	2 Low Noise Trans. Sil., npr 2N2925=BC107	8/-
A42	5 CT41/45 Germ. Trans. pnp=OC71	8/-
A43	2 GT31 L.F. Low Noise Germ. Trans., pnp	8/-
A46	3 Mullard OC76 Trans.=NKT212, AC151	8/-
A49	4 OC72 Type Trans. NKT212, AC128	8/-
A58	2 2N708 Sil. Trans. 300Mc/s npr=BSV63	8/-
A66	4 AC128 Trans. pnp High Gain=OC82	8/-
A67	4 AC126 Germ. Trans. pnp=AC163	8/-
A68	2 OC73 Mullard Trans.=NKT214, AC126	8/-
A69	7 OC81 Type Trans. British Made	8/-
A73	7 OC71 Type Trans. British Made	8/-
A81	6 TK220 Germ. Switching Trans.	8/-
A82	3 2N1307 pnp Switching Trans. ASY27	8/-
A83	3 OC170 H.F. Trans. Type=NKT612, AF124	8/-
A84	3 AF116 Type Trans.=AF126, AF127	8/-
A88	3 AF117 Trans. Type=NKT677, AF127	8/-
A89	3 OC171 L.F. Trans. Type=AF124	8/-
A90	3 AC107 Germ. Trans. TO-1 Case Low Noise	8/-
A94	5 2N2926 Silicon Epoxy Trans. npr	8/-
A95	2 GET880 Low Noise Germ. Trans.	8/-
A97	1 AF139 pnp High Freq. Trans. 700Mc/s	8/-
A98	3 npr Trans. 1 ST141 & 2 ST140	8/-
A99	4 MAT10 & 2 MAT106 & 2 MAT120 pnp	8/-
A100	3 MAT12 & 2 MAT101 & 1 MAT121 pnp	8/-
A101	4 OC44 Germ. Trans. A.F.	8/-
A102	3 AC127 npr Germ. Trans.	8/-
A104	5 Sil. Alloy Trans., like OC200, 2S302, TO-5 pnp	8/-
A106	3 OC84 Mullard Trans. 1 Amp pnp	8/-
B14	4 Silicon Rectifiers 400 PIV 500mA BY101	8/-
B18	4 Top Hat Silicon Rectifiers 100 PIV 740mA	8/-
B44	4 3Amp Silicon Rectifiers 100-400 PIV	8/-
B46	2 10Amp Silicon Rectifiers 100 PIV	8/-
C3	10 Ass. Gold Bonded Diodes all marked	8/-
C4	20 General Purpose Germ. Diodes unmarked	8/-
C6	7 CG628 Germ. Diodes=OA91	8/-
C10	3 OA10 Diodes Mullard 30 PIV 1Amp	8/-
C14	6 IN914 Silicon Diodes 75 PIV 75mA	8/-
C15	8 OA95 Germ. Diodes Sub-min.=IN69	8/-
C16	10 OA202 Sil. Diodes Sub-Min.	8/-
C17	8 OA81 Diodes=AA117, SD84	8/-
C18	5 OA47 Gold Bonded Diodes=OA180	8/-
C19	4 OA5 Gold Bonded diodes=IN270, IN276	8/-
C21	12 OA200 Sil. Diodes Sub-Min.	8/-
C22	3 IS113 Sil. Rects. 400 PIV 400mA Sub-Min.	8/-
C23	20 IS130 Sil. Diodes 60 PIV Sub-Min.	8/-
C24	4 BY126 Sil. Rects. Plastic	8/-
C25	3 BY127 Sil. Rects. Plastic	8/-
C45	12 Assorted Germ. Diodes all marked	8/-
DO2	3 12V Zeners. 400mW 5% tol.	8/-
DO4	4 Zener Diodes 250mW, 3/12V mixed, 5%	8/-

250 DIODES Sub. Min. Glass **10/-**
Sil. Germ and Zeners Identification Chart Free. Pak No. XB200.

150 TRANS. Mixed AF/RF **10/-**
XA100

100 SIL. DIODES **10/-**
DO-7 SIM OA200—OA202. Pak No. XB100
The above devices are untested

25 GERM. TRANS. 20/-
ALL KNOWN TYPES
EQVT. LIST INCLUDED
PAK No. T12

20 SIL. ALLOY TRANS.
eqvt. OC200-205
TO-5 2S301-304 **20/-**
pnp Pak No. T13

20 SIL. PLANAR TRANS.
BC108, 2N706, 2N697 **20/-**
npr Pak No. T14

30 GERM. DIODES CG62 **10/-**
eqvt. OA70-79-81
Pak No. T15

20 GERM. GOLD BONDED **10/-**
eqvt. OA47
Pak No. T17

10 OA182 GOLD BONDED **10/-**
DIODES. eqvt. OA5
Pak No. T16

PLASTIC UNIUNCTION TRANS.
eqvt. 2N2646 UT46 TIS43
2 FOR 10/- Pak No. T18

BULK TRANSISTOR BUYS

New BI-PAK untested — uncoded

PAK NO.	Description	Price
X1	50 A.F. TO-5 ACY17-20 series	10/-
X2	50 A.F. TO-1 NKT281-AC128 type	10/-
X3	30 V.H.F. TO-1 AF117-NKT667 type	10/-
X4	35 A.F. SO-2 2G371-OC71-75 type	10/-
X5	50 R.F. TO-5 NKT126, OC45 type	10/-
X6	40 A.F./R.F. STC ACY27-30, etc	10/-
X7	40 R.F. TO-1 NKT1412-OC44/45	10/-
X8	30 V.H.F. TO-5 2G401 Texas AF118	10/-
X9	30 npr TO-1 AC127 NKT773 type	10/-
X10	40 Sil. TO-5 pnp OC200, 2S302 type	10/-
X11	30 R.F. npr 2G339, 2N1302	10/-
X12	50 npr Sil. Planar mixed 2N706 type	10/-

DEDUCT 10% OFF THESE PRICES

NEW SILICON RECTIFIERS TESTED				SCR's			
PIV	400mA	750mA	1-5A	3A	10A	30A	LOWEST PRICE LARGEST RANGE
50	10d	1/-	1/6	2/9	4/3	9/6	PIV 1A 7A 16A 30A
100	1/3	1/8	2/6	3/3	4/6	15/-	25 7/8 30/-
200	1/3	1/8	2/6	4/-	4/9	20/-	50 7/8 8/8 10/8 35/-
300	2/-	2/6	3/9	4/6	6/6	22/-	100 8/8 10/- 15/- 45/-
400	2/-	2/6	4/-	5/6	7/6	25/-	200 12/8 15/- 20/- 55/-
500	—	3/-	—	6/-	8/6	30/-	300 15/- 20/- 35/- 80/-
600	2/9	3/3	4/3	6/9	9/-	37/-	400 17/8 25/- 35/- 85/-
800	—	3/6	4/9	7/6	11/-	40/-	500 30/- 40/- 45/- 85/-
1,000	—	5/-	6/-	9/3	12/6	50/-	600 — 40/- 50/-
1,200	—	6/6	7/6	11/8	15/-	—	—

10% = 2/- in £1. 1/- in 10/-. 6d in 5/-. etc.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

PAK No.	Description	Price
T1	8 2G371A eqvt.	10/-
T2	8 2G374 eqvt.	10/-
T3	8 2G374A eqvt.	10/-
T4	8 2G381A eqvt.	10/-
T5	8 2G382A eqvt.	10/-
T6	8 2G344A eqvt.	10/-
T7	8 2G345A eqvt.	10/-
T8	8 2G378 eqvt.	10/-
T9	8 2G339A eqvt.	10/-
T10	8 2G417 eqvt.	10/-
OC71	OC71	10/-
OC75	OC75	10/-
OC81D	OC81D	10/-
OC81	OC81	10/-
OC82	OC82	10/-
OC44	OC44	10/-
OC45	OC45	10/-
OC78	OC78	10/-
2N1302	2N1302	10/-
AF117	AF117	10/-

20AMP (RMS) SCR's Flying Leads TO-48 Stud **FULLY TESTED**
100 PIV 10/- 400 PIV 25/-
200 PIV 15/- 600 PIV 35/-

1 1/2 AMP SCR's TO-5 **FULLY TESTED**
100 PIV 5/- 400 PIV 8/6
200 PIV 7/- 600 PIV 12/6

**ALL
PRICES
SLASHED
GENUINE
REDUCTIONS**

"IMPORTANT NOTICE"
PLEASE USE PAK NO'S WHEN ORDERING, PLUS DESCRIPTION TO AVOID MISTAKES. PLEASE SEND ALL ORDERS DIRECT TO OUR WAREHOUSE and DESPATCH DEPT. P.O. BOX 6, WARE, HERTS. PLEASE ADD 1/- TOWARDS POST and PACKING. OVERSEAS ADD EXTRA FOR AIRMAIL.

BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

EXCEL

in

ELECTRONICS

Through this ICS 3-way Training Method:

MASTER THE THEORETICAL SIDE

1 From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

MASTER THE PRACTICAL SIDE

2 ICS show you how to develop your practical abilities in electronic engineering—*alongside* your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

MASTER THE MATHEMATICAL SIDE

3 To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:

Radio/TV Engineering and Servicing, Closed Circuit TV, Electronics, Electronic Maintenance, Servomechanisms, Computer Engineering, Numerical Control Electronics, etc.

EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS
CITY AND GUILDS ELECTRONIC SERVICING
R.T.E.B. RADIO/TV SERVICING CERTIFICATE
RADIO AMATEURS' EXAMINATION
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

Build your own radio, transistor portable, and professional-type test instruments with an ICS Practical Radio and Electronics Course. Everything simply explained and easy to handle. All components and tools supplied. For details post coupon below.

Member of the Association of British Correspondence Colleges

FOR **FREE** HANDBOOK POST THIS COUPON TODAY

I.C.S., Dept. 151, INTERTEXT HOUSE,
PARKGATE ROAD, LONDON, S.W.11

NAME

ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS

MAKE YOUR MONEY GO FURTHER with STUDENT ELECTRONIC SERVICES

RESISTORS: All brand new, Hi-Stab, low noise, 5% tol., carbon film; $\frac{1}{2}$ W E12 series 4.7-10M, 2d. each or 15/- per 100 of one value; $\frac{1}{2}$ W E24 series 4.7-10M, 2d. each or 15/- per 100 of one value; 1W E12 series 10-10M (10% tol.), 3d. each; 3W wirewound 0.5-12 (5% tol.), 1/6 each; 3W wirewound 15-8k2 (5% tol.), 1/9 each.
S.E.S. Pre-Pack gives you 5 off each 5% resistors from 4.7 to 1M, $\frac{1}{2}$ or $\frac{1}{2}$ W—65 different values (E12)—**ONLY £2.12.6.**

PRE-SETS: Min. skeleton carbon track, low noise with good stability; Values—Lin: 1k, 2k5, 5k, etc., to 5M; Log: 5k, 10k, 25k, etc., to 1M, only 10d. each; Sub-Min skeleton Lin. track—1k, 2k5, 5k, etc., to 5M, 9d. each; Slider presets wirewound $\frac{1}{2}$ W rating Lin. tracks 10 to 5k, 2/3; 3W wirewound fully insulated Lin. tracks 10 to 30k, 3/9.

POTENTIOMETERS: Min. enclosed, carbon track and wiper contact only 2/6; Values—Lin: 1k, 2k5, 5k, etc., to 10M; Log: 5k, 10k, 25k, etc., to 5M; Min. with double pole switch, insulated spindles only 5/6; Values—Lin: 25k, 50k, 100k; Log: 3k, 5k, 10k, 250k, 500k, 1M, 2M; 3W wirewound Lin. track 50 to 100k., 7/4 each.

CAPACITORS: New genuine Mullard Electrolytics

		(Min.)				(Small)						
6.4V	..	6.4	25	50	100	200	320	640	1,000	1,600	2,500	
10V	..	4	16	32	64	125	200	400	640	1,000	1,600	
16V	..	2.5	10	20	40	80	125	250	400	640	1,000	
25V	..	1.6	6.4	12.5	25	50	80	160	250	400	640	
40V	..	1	4	8	16	32	50	100	160	250	400	
64V	..	0.64	2.5	5	10	20	32	64	100	160	250	
Prices:		1/-	each			10d.	each		1/3	1/6	1/9	2/6

		(Large)				
25V	..	800	1,250	2,000	4,000	6,400
40V	..	500	800	1,250	2,500	4,000
64V	..	320	500	800	1,600	2,500
Prices:		3/-	6/6	8/-	12/6	15/-

All values in μ F

Mullard Miniature Metallised Polyester 250v.w. 0.01, 0.015, 0.022, 0.033, 0.047, 0.068—6d. each; 0.1, 0.15, 0.22 μ F—7d. each.
Mullard Polyester Film and Foil 400v.w. 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, etc., to 0.033 μ F 6d. each; 0.047 to 0.1 μ F 8d. each. 0.15 10d., 0.22 μ F 1/-, 0.33 μ F 1/6, 0.47 μ F, 1/9.
Disc Ceramics (Erie) 500v.w. 1,000, 4,700pF only 5d. each; Silver Mica 1% tol. 500v.w. 2.2 to 820pF 1/- each; Polystyrene 10% tol. 160v.w. 100 to 1,000pF only 5d. each.

SEMICONDUCTORS: ALL GENUINE MULLARD NEW AND UNUSED.

0A5 4/6, 0A81 3/4, 0A202 2/3, 0C71 4/-, 0C72 4/6, 0C44 7/9, 0C45 6/-, BC107, BC109 3/9 each, BC108 3/6, BFY51 4/6, F.E.T.—MPF 105 9/6, Silicon Rectifiers—(0.5A) 400piv 2/9, 800piv 3/-, 1,500piv 3/6 (1.2A) 400piv 6/0, 800piv 7/-, 1,500piv 7/6. (2.5A) 400piv 6/6, 800piv 7/6, 1,500piv 10/6 (1.2A and 2.5A types are stud mounted).

SWITCHES: Vast range of toggle, push button and rocker switches with or without centre position S.P.S.T., S.P.D.T., D.P.S.T., D.P.D.T. Very high quality. Toggles priced as low as 2/8 for S.P.S.T. Push-to-make or Push-to-break 3/11 each (push button available in white, black, red or green. Heavy duty toggle D.P.D.T. with centre position rated 10A 110V 9/7. Miniature "Maka-Switch" also available—shafts 5/4.

Stocks also include a wide range of plugs and sockets including Jacks and mains; a range of hardware and accessories which is increasing daily to supply you the customer with wire, pilot lights, insulating tape, and almost anything else needed when building a circuit of your choice. We even stock soldering irons by A.N.T.E.X. and solder by Multicore.

You will find all details of our stocks in our catalogue—a 120 page handbook divided into easy reference sections by the use of different coloured pages. The final section of the catalogue contains complete details of the LEKTROKIT chassis construction system including hints on assembly. A copy of this catalogue can be yours for just 3/6 and then you will see that Student Electronic Services are YOUR complete supplier. (For general data sheet send a 6d. stamp.)

Please include C.W.O. 1/- P. & P. on orders of components under £1
Orders of Lektrokkit: 2/- handling charge on orders under £1
5/- " " " " " £5

Send, with name and address to:

STUDENT ELECTRONIC SERVICES
196 Regent Road, Salford 5, Lancs.
Visit us at above address or call 061-872 5187

Readout —

A SELECTION FROM OUR POSTBAG

Arsenide Diodes

Sir—I and some fellow members of my school science society would be interested in carrying out some experiments in "Optical Communication using Laser Diodes" as published in the February issue of PRACTICAL ELECTRONICS.

We would be very grateful if you could indicate a supplier of the gallium arsenide diodes used for this project.

J. Martin,
Lymington,
Hants.

This is one of many similar enquiries we have received on this subject. GAL 1 and GAL 2 devices can be obtained from S.D.S. (Portsmouth) Ltd., Hillsea Industrial Estate, Portsmouth, Hants. at a cost of £4 and £8 respectively. Unfortunately the price of these devices is rather high; however we understand that Proops Bros. of 52 Tottenham Court Road, London, W.C.1 have offered "surplus" gallium arsenide diodes at low price, in the region of 28s each.

We can only hope that in the course of time these devices will become readily available to the amateur at a lower price—Ed.

Post Office Bill

Sir—Restrictions on the radiation of electromagnetic energy of any frequency is fair enough, following the activities of pirates and industrial spies. Legitimate users are already familiar with radio licensing, and presumably the Post Office will be prepared to grant licences to laser operators on a fairly free basis. However, if the term electro-mechanical does not refer to sound then the pirates have an immediate loophole. If they are prepared to go to the trouble of using short range light communication then they can equally well communicate by super-sonic carrier over similar distances, by radiating from a multiple transducer array.

Electric, magnetic, and electro-magnetic energy has been subject to restrictions for some time, and the

Bill merely seeks to tie up a few loose ends, but what are the obscure intentions and implications behind the term electro-chemical and electro-mechanical energy? To what do they apply and for what reasons? It might well be that the new restrictions are more far reaching than they at first appear to be!

D. Bollen,
Beaworthy,
Devon.

Make Light The Way

Sir—Regarding "Post office privilege", as I understood it, all those proud experimenters, building, and then giving the knowledge—via the various radio magazines—to others, of the use of light rays to pass any form of intelligence from one point to another, are controlled by the same regulations as "Hams"; those with licence to use normal radio methods.

It is quite clear, internal use will be just as one would make use of a signal generator, but I doubt if many would understand this limit when experiments to improve the distance have been tried.

Here then, we have the answer to all those, for and against letters, which Editors have for so long had from, would be "Hams", and others.

No morse test, no inference with important services, no exams, just pay and keep to the rules.

Many years ago, experts had a very poor opinion of short waves, amateurs being given the use of them lead the way.

Pioneers, make light the way!

C. S. Burton,
Bulwell,
Nottingham.

Electronics Scouts

Sir—On 2nd, 3rd and 4th May 1969 a camp will be held at Polyapes Camp

Site, Oxshott (N.G.R. TQ131597) for all members of the Scout Movement who have an interest in any branch of electronics.

The full programme has yet to be finalised but it is hoped to include demonstrations, talks and discussions on the following: Hi-fi equipment, recording, model control, short wave listening, and amateur radio. In addition it is hoped to have experienced people with test equipment facilities to help the enthusiast with his home constructed projects.

For further details groups or individuals are invited to send a foolscap s.a.e. to:

J. A. Carter,
c/o Baden-Powell House,
Queensgate,
London, S.W.7.

Amorphous Devices

Sir—Further to R. F. Shaw's article on Amorphous Semiconductor Devices in February's edition your readers might like to know some of the history behind the, so called, "Ovionic" devices.

Mr. Shaw refers to the devices as a comparatively recent discovery. By semiconductor standards this is not altogether true. As long ago as 1962 Stanley Ovshinsky—President of Energy Conversion Devices Inc.—was working on specialised materials to form the basis of thermo-electric generators when he suddenly discovered that under certain electrical conditions an alloy of germanium and tellurium showed different apparent conductivity.

The same piece of material would for some apparent reason change from high to low resistance, and on further investigation he found that the material, when changing from a high resistance to a low resistance state, exhibited a characteristic very similar to a gas tube in that when a certain voltage across the material was exceeded it would "break down" and start to conduct. Unlike the gas tube the voltage drop across the material when conducting was very low, i.e. the resistance change was quite extraordinary changing from the order of 10 megohms to approximately 10 ohms. Another unusual phenomena was that which Mr. Shaw describes as the permanent memory out of circuit.

Although it was not known how the device actually worked Ovshinsky took out patents and proceeded to publish details of practical applications of such a device.

Readout—

A SELECTION FROM OUR POSTBAG

In 1963 a British firm obtained exclusive rights to exploit the device and started a research programme to try and evaluate the mechanism of the rather strange conduction characteristics.

At the same time a British Press Conference was called and representatives of most of the technical journals were given a demonstration of the prototype device. The demonstration was met with a widely differing reaction from wonderment to sheer scepticism.

Nevertheless a limited budget research programme was started and attempts were made to obtain government grants to subsidise the work which was progressing satisfactorily. All attempts to obtain such a grant failed—perhaps due to the risk of investing in such an unknown quantity—but the company continued its work and eventually exhibited a number of development devices at the 1964 IEA exhibition at Olympia. Two types of device were shown; the memory device using pure germanium telluride as a material and a threshold device—as described by Mr. Shaw—using germanium telluride with added quantities of arsenic.

In those days the devices were made from pellets of material with point contacts of beryllium copper forming the electrodes (see Fig. 1).

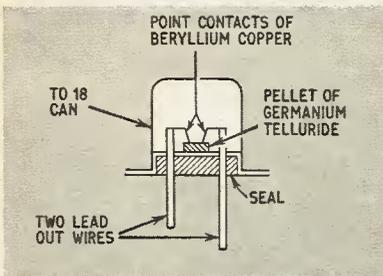


Fig. 1 Structure of the germanium telluride device of 1964

Unfortunately production devices were never made due to several artefacts in the development devices.

These problems all stemmed from the basic problem that the mechanism of conduction was not known. It was impossible to predict the all important breakdown (or threshold) voltage of the device and this could vary from batch to batch; typical values being anything between 20 and 100 volts.

Worse still this threshold voltage would vary for a single device throughout its life—which was comparatively short.

For some unknown reason the threshold voltage was load sensitive; for instance with a high resistance load the break-down could occur at voltages as high as 200 volts and with a large load drawing approxi-

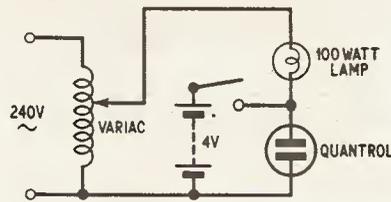


Fig. 2 Prototype test rig for the Quantrol device using a 4V battery for the high current pulse

mately 2 amps this would fall to the normal range of value (20 to 100 volts).

Fig. 2 shows the type of circuit in which the device operated. The device—at that time called Quantrol—would be connected in series with a load such as a 100 watt electric light bulb. The circuit was supplied from a variable transformer. Starting with the device in the non-conducting state and the applied voltage at zero the voltage would be increased to the threshold level and when this was reached the Quantrol would break down to a low resistance and the lamp would light. To turn the device off it was necessary to apply a comparatively high current pulse obtained from a low impedance. In the prototype test rig this was provided by a 4 volt battery and a push button switch.

Another disadvantage which is apparent from the above circuit was that the device was inherently a two terminal unit; isolated control as can be effected by a transistor, valve, or relay was impossible. It was suspected that the device worked by some type of field effect and attempts were made to introduce a third electrode using the material in a structure very similar to the present-day f.e.t.

All attempts to trigger the device by applied electric fields failed, and this led the researchers to believe that perhaps the device was operating by way of normal dielectric breakdown. The materials used were extremely easily oxidised—some of the alloys used were made by sintering in air which automatically oxidised the surface and others made by casting the molten alloy would not operate until the surface had been oxidised using strong nitric acid.

All the results indicated normal oxide breakdown (similar to that occurring with foil capacitors) and in many cases during the actual breakdown micro sparks could be seen at the junction between the electrode and the material. This effect adequately described the switch on characteristic, and switch off could be explained by the re-formation of an oxide under the surface of the contact by the thermal energy of the high current pulse. If this was the mechanism, the device was working on a physical destruction and reforming principle which would have been highly unreliable in practice. In all fairness, however, this was never conclusively proved and when the allocated research budget ran out further work stopped.

It is interesting to note that at about the same time an American company brought out a device exhibiting identical characteristics which was composed of two electrodes embedded in, but separated by a block of aluminium powder and epoxy resin. This device never reached full production due to the instability of its characteristics.

It seems rather strange that after a lapse of five years the identical device is again being exploited with virtually no change to its characteristics, and still considerable doubt as to its mechanism.

M. J. Hughes,
Westerham,
Kent.

Mr Michael J. Hughes' comments on amorphous semiconductor devices are most interesting and informative, but I would like to point out the fact that although the devices at present have similar characteristics to the older devices, they are vastly improved in their characteristics.

The new devices have very stable threshold voltages and other electrical characteristics providing one takes care to operate the devices within their prescribed parameters. The newer devices use both different glass alloys and physical device configurations arrived at by both empirical and theoretical considerations which resulted in their improved characteristics, stability, and reproducibility.

As Mr Hughes correctly pointed out, similar switching has been observed in oxide based devices, but there is now sufficient evidence to rule out this mechanism in the Ovshinsky devices described above.

The five year lapse since the first prototype does not seem unduly long for research and development in this field, since only at the present time has the theory of amorphous materials in general progressed to the state where we can make reasonable postulations as to their conduction mechanisms.—Robert F. Shaw.

NEW BOOKS

FEBRUARY

FET PRINCIPLES, EXPERIMENTS AND PROJECTS

by Edward M. Noll 40/- net

49 EASY TRANSISTOR PROJECTS

by Robert M. Brown and Tom Kneitel 16/- net

PHOTOFACT TELEVISION COURSE

by the Howard W. Sams Engineering Staff 40/- net

SERVICING DIGITAL DEVICES

by Jim Kyle 26/- net

MARCH

UNDERSTANDING ELECTRONICS UNITS AND STANDARDS

by Earl J. Waters 25/- net

USING SCOPES IN TRANSISTOR CIRCUITS

by Robert G. Middleton 32/- net

TRANSISTOR TV TRAINING COURSE

by Robert G. Middleton 35/- net

INDUSTRIAL TRANSISTOR CIRCUITS

by Allan Lytel 24/- net

APRIL

101 QUESTIONS AND ANSWERS ABOUT COLOUR TV

by Lee G. Sands 15/- net

HAVING FUN IN ELECTRONICS

by Lee G. Sands 25/- net

101 EASY AUDIO PROJECTS

by Robert M. Brown and Tom Kneitel 28/- net

PRACTICAL DESIGN WITH TRANSISTORS

by M. Horowitz 42/- net

FOULSHAM-SAMS TECHNICAL BOOKS

(W. FOULSHAM & CO. LTD.)

YEovil RD., SLOUGH, BUCKS, ENGLAND

VARIABLE VOLTAGE TRANSFORMERS



50 AMP



1/2 AMP



PORTABLE TYPE £9.5.0.

INPUT 230/240v. A.C. 50/60—
OUTPUT VARIABLE 0-260v.
BRAND NEW

Keenest prices in the country.
All Types (and Spares) from
1/2 to 50 amp. from stock.

SHROUDED TYPE

1 amp, £5. 10. 0. 2.5 amps, £6. 15. 0.
4 amps, £9. 0. 0. 8 amps, £9. 15. 0.
10 amps, £18. 10. 0. 15 amps, £21. 0. 0.
20 amps, £37. 0. 0. 37.5 amps, £72. 0. 0. 50 amps, £92. 0. 0.

OPEN TYPE (Panel Mounting)
1/2 amp, £3. 10. 0. 1 amp, £5. 10. 0.
2 1/2 amps, £6. 12. 6.

PORTABLE TYPE

1.5 amp. portable fitted metal case, voltmeter, lamp, switch, etc. £9.5.0. Similar to above 2.5 amp. £11.7.6.

L.T. TRANSFORMERS

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36 v. at 5 amps.	£4/5/0	6/-
2	30, 40, 50 v. at 5 amps.	£6/5/0	6/6
3	10, 17, 18 v. at 10 amps.	£4/10/0	4/6
4	6, 12 v. at 20 amps.	£5/17/6	6/6
5	17, 18, 20 v. at 20 amps.	£6/12/6	6/6
6	6, 12, 20 v. at 20 amps.	£6/5/0	7/6
7	24 v. at 10 amps.	£4/15/0	5/6
8	4, 6, 24, 32 v. at 12 amps.	£6/10/0	6/6

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250v. A.C. operation.

ECONOMY KIT. Flash rate 1-36 flash per second. All components including Unijunction, thyristor, tube and circuit. £5/5/0 plus 3/6 P. & P.

INDUSTRIAL KIT. Flash rate 1-80 f.p.s. Ideally suitable for schools, laboratories, etc. Incorporates double wound transformer which isolates both tube and timing circuit from mains. Stabilized timing circuit and high power tube. £8/8/0 plus 6/- P. & P.

6 1/2" POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 8/6 post paid. Regret not sold separately.


PARVALUX TYPE SD19 230/250 VOLTS A.C. REVERSIBLE GEARED MOTOR.

30 r.p.m., 40lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first class running order. A really powerful motor offered at a fraction of makers' price. 6 GNS, P. & P. 10/-.




BODINETYPEN.C.I GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, '38 amp.
(Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, '28 amp.
The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage for motor 115v. A.C. Supplied complete with transformer for 230/240v. A.C. input. Price, either type £2. 17. 6 plus 6/6 P. & P. or less transformer £2. 2. 6 plus 4/6 P. & P.

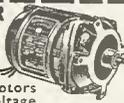

200/250v AC HORSTMANN 20A TIME SWITCH

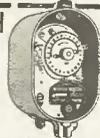2 on/off every 24 hours at any pre-set time. Fitted in metal case. 36 hr. spring reserve. Used but fully tested. Fraction of makers' price. £3.19.6 plus 4/6 P. & P. Available with solar dial on request.



INSULATED TERMINALS

Available in red, white, yellow, black, blue and green. New 17/- per doz. 2/- P. & P.

230/240v. A.C. SOLENOID
Heavy duty type, approx. 3 lbs. pull. Price: 17/6 plus 2/6 P. & P.

12/24v. D.C. SOLENOID
Approx. 8 oz. push. Price 8/6 plus 1/6 P. & P.



LIGHT SENSITIVE SWITCH


Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt D.C. op. price 25/- plus 2/6 P. & P. ORP 12 including circuit, 10/6 each, plus 1/- P. & P.



A.C. MAINS MODEL Incorporates Mains Transformer, Rectifier and special relay with 3, 5 amp mains c/o contacts. Price inc. circuit 47/6 plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING

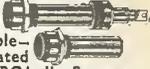Precision engineered light source with focusable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP. 12 or similar cell. Both units are single hole fixing. Price per pair £2.15.0 P. & P. 3/6.



UNISELECTOR SWITCHES

4 Bank 25 Way 24 v. D.C. operation £5.17.6 plus 2/6 P. & P.
8 Bank 25 Way 24 v. D.C. operation. £7.12.6 plus 4/6 P. & P.



MINIATURE UNISELECTOR SWITCH

Ex-Equipment
3 banks of 11 positions plus homing bank. 40 ohm coil. 24-36 v. D.C. operation. Tested. 22/4, plus 2/6 P. & P.



COPPER LAMINATE. Printed Circuit Board. Size 15 1/2" x 5 1/2" 3/9 each. 3 for 10/- Post paid.

RELAYS

Bulk purchase enables us to offer the following new SIEMENS, PLESSEY, etc. miniature plug in relays complete with base, at a fraction of makers' price.

Coil	Working Voltage	Contacts	Price
280	6-12	2 c/o	14/6
280	9-18	4 c/o	15/6
700	12-24	2 c/o	12/6
700	16-24	4 c/o	15/6
700	16-24	4M 2B	12/6
1250	20-40	2 c/o H.D.	12/6
2500	30-50	2 c/o H.D.	12/6
5800	50-70	4 c/o	10/-
9000	40-70	2 c/o	10/-

H.D. = Heavy Duty. POST PAID

SEALED RELAY

230 VOLT AC COIL
Two c/o 5 amp contacts. Plug-in I.O. Base. Price 14/6, incl. base. Post Paid. Three c/o Amp. contacts. 17/6 Incl. Base. Post Paid.



'AVO' METER MODEL 7

Supplied fully checked and tested on all ranges and in excellent condition. Complete with batteries and leads. Price £13.10. 0. P. & P. 7/6. Avo Leather Carrying Case 30/-. Regret not supplied separately.



'AVO' POWER AND DECIBEL EXTENSION UNIT

For Model 7 and 7X 'AVO' Meters. This resistance box will permit values from 500 to 1,500 ohms to be obtained. Supplied complete with leads. 42/6. P. & P. 4/6.

DRY REED SWITCHES

2 x 1 amp Dry Reeds (makes contacts). Mounted in 870 ohm 9-18 v. coil. Size 3" x 3 1/2" x 1/2". New. Price 8/6 per pair. Post Paid. Six of the above mentioned units (12 Reeds). Fitted in metal box. Size 4" x 3 1/2" x 1 1/2". Mfg. by Elliott Bros. New. 45/- each. Post Paid.

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
57 BRIDGMAN ROAD, LONDON, W.4 Phone 995 1560
SHOWROOM NOW OPEN CLOSED SATURDAY
Personal callers only
9 LITTLE NEWPORT ST. LONDON, W.C.2. Tel. GER 0576

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, WELLFIELD RD., S.W.16
Special 24 Hour Mail Order Service

AZ31	10/-	KT67	45/-	UOH81	7/-	12K8GT	8/-	2N2398	30/-	GEX54	2/6
BF100	5/6	KT81(7C5)	15/-	UCL82	7/6	12Q7GT	6/-	2N2904	10/-	GEX54	15/-
GC	20/-	KT81(7C5)	15/-	UCL83	10/-	20L1	20/-	2N2904	12/6	GEX54	3/-
CY30	12/6	KT81(7C5)	15/-	UF41	11/6	20P2	20/-	2N2926	5/3	G33M	3/6
DAF91	4/6	KT88	35/-	UF89	7/6	20P5	20/-	2N3819	13/6	G33M	3/6
DAF96	6/9	KT88	30/-	UL41	12/-	25Z4	6/3	2S002	20/-	G36M	3/6
DCC90	10/6	KTW61	8/6	UL94	7/-	25ZGT	8/-	2S003	12/-	G37M	3/6
DF91	4/-	KTW62	10/-	UY41	8/6	25Z6GT	8/6	2S004	11/-	HD967	4/6
DF96	7/6	ML14	17/6	UY85	6/6	30C15	15/-	2S005	48/-	HG5002	4/6
DB391	4/6	N78	11/6	VF48	23/6	30C17	15/-	2S006	20/-	JK9A	22/6
DE77	4/9	PC88	11/6	VR105/30	6/3	30C18	15/-	2S012	50/-	JK10A	15/-
DK91	6/-	PC88	11/6	VR105/30	6/3	30F5	17/-	2S012A	55/-	JK10A	16/6
DK92	9/-	PC97	8/9	W81	12/6	30FL1	16/-	2S013	20/-	JK18A	22/6
DK96	7/9	PC900	8/6	X78	32/6	30FL12	19/-	2S018	60/-	JK21A	12/6
DL66	25/-	PCC84	6/8	X81	45/-	30FL14	18/6	2S108	60/-	K886A	5/-
DL92	6/3	PC939	10/6	Z66	15/-	30L15	17/-	2S301	12/6	MAT101	8/6
DL94	6/3	PCC189	10/6	Z319	23/6	30L17	17/-	2S320	9/-	MAT120	7/9
DL96	7/6	PCF80	6/9	Z750	23/-	30P12	16/-	2S702	15/-	NKT128	6/-
DL810	12/6	PCF86	6/-	Z8031	12/-	30P19	15/-	45L	45/-	NKT142	8/-
DL816	30/-	PCF801	9/9	OA2	6/-	30P11	15/-	AC107	10/-	NKT211	6/-
DL819	30/-	PCF802	9/9	OB2	9/-	30P13	18/6	AC126	6/6	NKT214	4/6
EW450	7/6	PCF84	12/-	OC8	3/6	30P14	15/-	AC127	7/6	NKT216	7/8
DY86	6/6	PE82	7/9	OZ4	4/6	33L6	9/-	AC128	6/6	NKT216	6/6
DY87	6/6	PCL83	10/3	1B3GT	7/3	35L6GT	9/-	AC117	7/6	NKT217	8/6
E880C	12/-	PCL84	8/6	1CP31	46/3	35W4	4/6	AC119	5/3	NKT223	6/-
E180F	17/6	PCL85	9/3	IR3	6/-	35Z4GT	8/6	AC118	5/3	NKT223	6/-
E182CC	22/6	PCL86	9/3	2D21	6/6	50C5	6/3	AC119	6/6	NKT224	4/6
EABC80	6/6	PEN44	20/-	2B25	19/6	50C6GT	31/-	AC120	5/-	NKT225	3/6
EA42	10/-	PEN45DD	20/-	3E2	19/6	80	3/6	AD100	16/-	NKT225	3/6
EB91	9/-	PF200	14/-	3C45	65A	85A2	7/3	AD104	16/-	NKT265	9/6
EB33	8/6	PL36	10/9	4X150A	98/-	90AG	45/-	AD161	11/-	NKT274	5/-
EB041	9/9	PL41	8/6	5R4Y	10/6	90AV	45/-	AD114	6/6	NKT304	8/-
EB090	9/9	PL82	8/6	6/4	5/6	90C1	12/-	AP116	6/6	NKT350	8/-
EBF80	7/6	PL84	7/-	5V4G	4/6	90C6	25/-	AP116	6/6	NKT404	8/6
EBF89	9/6	PL500	14/6	5Y3GT	6/-	90CV	25/-	AP117	6/6	NKT452	12/6
EBF99	9/6	PL500	14/6	5Y3GT	6/-	90CV	25/-	AP117	6/6	NKT452	12/6
EBL21	12/-	PL500	14/6	5Y3GT	6/-	90CV	25/-	AP117	6/6	NKT452	12/6
EBL31	27/6	PL500	14/6	5Y3GT	6/-	90CV	25/-	AP117	6/6	NKT452	12/6
ECC33	15/6	PY33	10/9	6AK6	12/6	15B3	8/6	AP118	10/-	NKT676	5/-
ECC40	17/6	PY81	5/9	6AL5	3/7	30T	3/6	AP118	10/-	NKT676	5/-
ECC81	6/6	PY82	5/3	6AM6	3/6	811	35/-	AP119	12/6	NKT677	6/-
ECC82	5/9	PY83	7/-	6AN3	10/-	313	75/-	AS220	7/6	NKT777	8/-
ECC83	6/3	PY801	10/6	6AQ4	4/-	366A	3/-	AS221	12/6	OA5	3/-
ECC85	5/6	PZ30	10/6	6AS6	6/3	372A	57/6	AS223	30/-	OA7	4/-
ECC88	7/6	QV02/10	27/6	6AT6	4/9	3672	7/6	ATY10	39/6	OA10	3/-
ECP80	6/6	QV03/20	27/6	6AU6	5/-	3687	10/-	BC107	7/6	OA70	2/-
ECP82	6/6	QV04/15	8/6	6BA6	20/-	3691	25/-	BC108	5/-	OA79	2/6
ECP83	11/6	QV04/15	8/6	6BA6	20/-	3749	10/-	BCY31	13/6	OA85	2/8
ECH42	11/-	QV06/40	90/-	6B36	9/-	3842	65/-	BCY33	7/6	OA86	4/-
ECH81	5/9	QV06/40	90/-	6BJ6	9/-	3963	10/-	BCY34	6/6	OA200	3/3
ECH83	8/6	QV06/40	90/-	6BK4	21/6	6057	10/-	BCY40	12/-	OA202	4/3
ECL80	7/-	QV06/40	90/-	6BN6	7/6	6058	10/-	BCZ11	5/-	OA210	7/6
ECL82	7/6	QV06/40	90/-	6BR8	12/6	6061	12/-	BDY11	27/6	OA2200	11/-
ECL83	10/3	QV06/40	90/-	6BS7	25/-	6062	14/-	BDY12	32/6	OA2201	10/-
ECL86	9/-	QV06/40	90/-	6BW6	14/6	6063	7/-	BFY11	6/6	OA2202	8/6
ECL87	9/-	QV06/40	90/-	6BWW	13/6	6064	7/-	BFY12	6/6	OA2204	8/6
ECL88	9/-	QV06/40	90/-	6C6B	5/6	6067	8/6	BSY22	9/6	OA2208	9/6
ECL89	9/-	QV06/40	90/-	6C86	5/6	6067	8/6	BSY28	5/6	OA2222	9/6
ECL90	9/-	QV06/40	90/-	6CD6G	24/6	6080	25/-	BSY61	7/6	OA2224	10/-
ECL91	9/-	QV06/40	90/-	6CH6	7/6	6096	8/6	BSY63	7/6	OA2225	10/-
ECL92	9/-	QV06/40	90/-	6CL6	8/6	6146	27/6	BSY64	6/6	OA2242	4/8
ECL93	9/-	QV06/40	90/-	6CW4	12/6	3903	9/-	BSX82	40/-	OA2246	4/8
ECL94	9/-	QV06/40	90/-	6D4	18/-			BTY88	18/6	OA2290	9/6
ECL95	9/-	QV06/40	90/-	6D6	18/-			BTY5100R	140/-	OA2292	9/6
ECL96	9/-	QV06/40	90/-	6E26	9/6			OC18	20/-		
ECL97	9/-	QV06/40	90/-	6F23	16/-			OC19	7/6		
ECL98	9/-	QV06/40	90/-	6F24	14/-			OC20	10/-		
ECL99	9/-	QV06/40	90/-	6F25	15/-			OC22	10/-		
ECL00	9/-	QV06/40	90/-	6F28	14/-			OC23	11/6		
ECL01	9/-	QV06/40	90/-	6F36	4/6			OC24	15/6		
ECL02	9/-	QV06/40	90/-	6G7G	3/6			OC25	9/-		
ECL03	9/-	QV06/40	90/-	6J7G	6/6			OC26	7/-		
ECL04	9/-	QV06/40	90/-	6K7G	2/-			OC27	5/-		
ECL05	9/-	QV06/40	90/-	6K8G	3/6			OC29	16/6		
ECL06	9/-	QV06/40	90/-	6L6G	7/9	1252	4/3	CRS105	7/6	OC35	12/6
ECL07	9/-	QV06/40	90/-	6Q7G	6/6	2G210	12/6	CV102	3/6	OC36	12/6
ECL08	9/-	QV06/40	90/-	6S67	6/6	2G309	5/6	CV103	3/6	OC41	6/6
ECL09	9/-	QV06/40	90/-	6S7M	7/6	2G381	5/6	CV426	3/6	OC42	5/6
ECL10	9/-	QV06/40	90/-	6SL7GT	6/6	2G382	6/6	CV2226	20/-	OC43	9/-
ECL11	9/-	QV06/40	90/-	6SN7GT	5/6	2G401	5/6	CV2258	25/-	OC44	4/6
ECL12	9/-	QV06/40	90/-	6V6G	4/6	2G402	6/6	CV2290	5/6	OC44M	5/6
ECL13	9/-	QV06/40	90/-	6X4	4/6	2G403	10/6	CV2919	2/6	OC45	3/6
ECL14	9/-	QV06/40	90/-	6X5GT	4/6	2G414	6/6	CV2848	2/6	OC46M	4/6
ECL15	9/-	QV06/40	90/-	6X6GT	6/6	2G416	6/6	CV1782	30/-	OC46	5/6
ECL16	9/-	QV06/40	90/-	7B6	11/6	2G416	6/6	CV1783	30/-	OC47	7/6
ECL17	9/-	QV06/40	90/-	7B7	7/6	2G417	6/6	DD003	3/6	OC57	16/6
ECL18	9/-	QV06/40	90/-	7C5	15/-	2N247	9/6	DD190	9/6	OC58	17/6
ECL19	9/-	QV06/40	90/-	7C6	15/-	2N274	9/6	DD226A	7/6	OC59	18/6
ECL20	9/-	QV06/40	90/-	7H7	6/6	2N410	9/6	EW99	5/-	OC70	4/6
ECL21	9/-	QV06/40	90/-	7S7	12/6	2N416	12/6	ERT7	5/-	OC71	3/6
ECL22	9/-	QV06/40	90/-	7Y4	8/6	2N585	7/6	ERT8	8/-	OC72	5/6
ECL23	9/-	QV06/40	90/-	10P13	13/6	2N599	12/6	GET16	7/3	OC73	7/6
ECL24	9/-	QV06/40	90/-	11E3	70/-	2N696	10/-	GET20	10/-	OC74	6/6
ECL25	9/-	QV06/40	90/-	12AC6	10/-	2N697	12/6	GET88	5/-	OC75	6/6
ECL26	9/-	QV06/40	90/-	12AE6	9/6	2N700A	6/6	GET102	6/-	OC76	5/6
ECL27	9/-	QV06/40	90/-	12AT6	4/6	2N704	6/6	GET114	4/-	OC77	8/6
ECL28	9/-	QV06/40	90/-	12AT7	6/-	2N1301	6/6	GET116	15/-	OC81	3/6
ECL29	9/-	QV06/40	90/-	12AU7	5/9	2N1304	6/6	GET571	5/-	OC81D	3/6
ECL30	9/-	QV06/40	90/-	12AX7	6/3	2N2062	7/6	GET872	6/-	OC81DM	3/6
ECL31	9/-	QV06/40	90/-	12BA6	6/-	2N2068	20/-	GET874	5/-	OC81M	3/6
ECL32	9/-	QV06/40	90/-	12BC6	6/-	2N2147	12/6	GET875	6/-	OC81J	9/-
ECL33	9/-	QV06/40	90/-	12C15	20/-	2N2149	12/6	GET880	9/-	OC82	6/6
ECL34	9/-	QV06/40	90/-	12E1	20/-	2N2150	12/6	GET880	9/-	OC82	6/6
ECL35	9/-	QV06/40	90/-	12K7GT	7/-	2N2389A	4/6	GET855	5/-	OC82D	2/6


Postage 6d. valve, transistors plus GST

OPEN DAY TO CALLERS 9 a.m.—5.30 p.m. No early closing
C.W.O. No C.O.D. Tel. 01-769 0199 & 1649
SEND S.A.E. FOR FREE LIST OF 6,000 TYPES, VALVES AND TRANSISTORS

STEREOGRAM CABINET £19

An elegant Stereogram Cabinet in modern Veneered Mahogany and cloth covered Front Panel

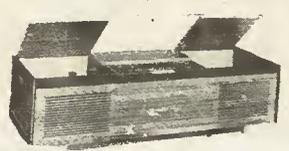BLACK LEATHERETTE SIDE PANELS
Dimensions: 52" x 17 1/2" x 12". Speaker positions for Twin 10" x 5" Speakers



SPEAKERS 6/6

2"—75Ω. 2 1/2"—35Ω. P. & P. 2/6.

ACOS MICS. 35/- STANDARD

STICK MIC. 2gns. P. & P. 3/6.

ASSORTED CONDENSERS

10/- for 50. P. & P. 7/6.

ASSORTED RESISTORS

10/- for 50. P. & P. 4/6.

ASSORTED CONTROLS

10/- for 25. P. & P. 7/6.

TRANSISTORS

MULLARD

PEAK SOUND


Aids to economical high fidelity

ES/10-15 BAXANDALL SPEAKER

*"A
thoroughbred"*

SAYS
RALPH WEST
HI-FI NEWS
OCTOBER, '68

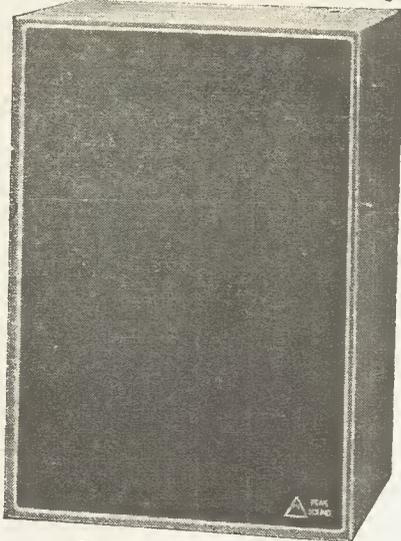"The immediate impression was of a thoroughbred speaker, smooth and effortless... voices were uncannily real. Once again we see the possibility of Rolls Royce standards... when you know how."



A revolutionary advance in design logic

We can only quote briefly from the report in *Hi-Fi News* which goes thoroughly into the merits of this remarkable loudspeaker. We supply the kit exactly to the specifications described by the designer, P. J. Baxandall in *Wireless World* (Aug. and Sept.). These designer-approved Peak Sound Kits come ready for instant assembly. Frequency range—60 to 14,000 Hz (100–10,000 Hz ± 3 dB); impedance—15 ohms; loading up to 10 watts R.M.S.; size 18" x 12" x 10". Here indeed is quality performance of a very high order for a very modest outlay.

Equaliser assembly 36/- (P/P 1/6);
Speaker Unit 38/- + 8/11 P. Tax (P/P
5/-); Cabinet assembly, teak finished.
£63.6 + 12/8 P. Tax (Carr. 8/6).
X-over for woofer if required 22/6 (P/P 3/6)

£9.17.6
+ 21/7 P. Tax
(Carr. in U.K. 11/6)

As specified for
P.W. Double 12
described in
Practical

Wireless

THE PEAK SOUND
PA/12-15 (12 watts
R.M.S. out into 15Ω)
is for the construc-
tor who appreciates
both sensible design



and genuine power and hi-fi performance. Available built or in kit form. Response 10 Hz – 45 KHz ± 0.5 dB Distortion at max. output –0.1% 43 dB neg. feed back. Size 5" x 3 3/4" x 1 3/4". With full instructions. Pre-amp. details available. (P/P for kit or built 2/6)

BUILT
AND TESTED

£5.19.6

Kit less
heat sink
and board

£3.19.6

Heat
sink 6/-
(P/P 1/6)

From your dealer or direct in case of difficulty.

PEAK SOUND (HARROW) LTD., 32 St. Judes Road,
Engfield Green, Egham, Surrey Telephone: EGHAM 5316

— TO PEAK SOUND —

Please send (post free)

for which I enclose £..... s..... d

NAME

ADDRESS

Block letters please

P.E.4

prepare now for tomorrow's world

Today there is a huge demand for technologists such as electronics, nuclear and computer systems engineers, radio and television engineers, etc. In the future, there will be even more such important positions requiring just the up-to-date, advanced technical education which CREI, the Home Study Division of McGraw-Hill Book Co., can provide.

CREI Study Programmes are directly related to the problems of industry including the latest technological developments and advanced ideas. The individual tuition given by the CREI panel of experts in each specialised field is comparable in technological content with that of technical colleges.

Take the first step to a better job now — enrol with CREI, the specialists in Technical Home Study Education.

CREI Programmes are available in:

Electronic Engineering Technology * Industrial Electronics for Automation * Computer Systems Technology * Nuclear Engineering * Mathematics for Electronics Engineers * Television Engineering * Radar and Servo Engineering * City and Guilds of London Institute: Subject No. 49 and Advanced Studies No. 300.



**CREI (London), Walpole House,
173-176 Sloane Street, London S.W.1.**

A Subsidiary of McGraw-Hill Inc.

Post this coupon today for a better future

To C.R.E.I. (London), Walpole House, 173-176 Sloane Street, London S.W.1.
Please send me (without obligation) details of your Educational Programmes

please tick

My interest is City and Guilds General

Name

Address

Electronics experience

PE17

Practical Electronics Classified Advertisements

The pre-paid rate for classified advertisements is 1/3 per word (minimum order 15/-), box number 1/6 extra. Semi-displayed setting £4.2.6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL ELECTRONICS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL ELECTRONICS, IPC Magazines Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

FOR SALE

£6,000 IN VOUCHERS GIVEN AWAY. See free Cat. for details. Tools, Materials, Mechanical, Electrical, thousands of interesting items. WHISTON, Dept. PVE, New Mills, Stockport SK12 4HL.

TIME SWITCHES, 14 day clock, once on once off every 24 hours, reconditioned and fully guaranteed. 5 amp Horstmann 32/6, 15 amp Venner 42/6. P. & P. 4/6. A. R. BATCHELOR (P.E. Dept.), 4 Park Road, Bromley, BR1 3HP.

RADIO CONTROL equipment/models/accessories. BILL, 3 Osterberg Road, Dartford, Kent. 27832.

FOR SALE due to pressure of other work. Complete stock of Mail Order Electronic Components Business including valuable test equipment. Approx. 15,000 items. 98% new, rest ex. eqt. Offers on £200. Trade enquiries invited. S.A.E. for details to Box 18.

**HIGH GLOSS METALLIC
HAMMERED ENAMEL
'MAKES FANTASTIC
DIFFERENCE TO PANELS'**

say hundreds of enthusiastic users. 'Crackle' pattern appears like magic on wood and metal. No under-coat. Air dries 15 min. to hard glossy finish. Heat, liquid and scratchproof. Bronze; Silver; Green; Black; Lt. and Dk. Blue. Send for Free list, or 8/- (+ 1/9 post) for trial 1/4 pt. TIN, colour samples and instructions. Send NOW. FINNIGAN SPECIALITY PAINTS Dept. P.E. STOCKSFIELD. Tel. 2280 Northumberland.



COMPUTER IN YOUR POCKET. Home, college, workshop. Pocket slide rules, 17/6, 10in desk/bench slide rules, 25/-. Full instructions. DEPT. PE, 19 Paynesfield Avenue, S.W.14.

COSSOR TWIN BEAM, Oscilloscope 'Scope Model 1049 Mk. IIIA. Complete with stand, in perfect working order, £55 or near offer. WADKINS, 177 Maesglas, Cardigan, West Wales.

AKAI XIV Mains/Portable Stereo Tape Recorder. Complete with tapes and earphones. All as new. £100. ALLEN, The Old Forge, Marston Magna, Nr. Yeovil, Som. Marston Magna 273.

MORSE MADE !! EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to: GSCHS/H, 45 GREEN LANE, PURLEY, SURREY

WANTED

NEW VALVES WANTED. Popular TV and Radio types. Best cash price by return. DURHAM SUPPLIES, 367F Kensington Street, Bradford 8, Yorkshire.

WANTED. Set Newnes R. & TV Servicing Volumes. NORMAN H. FIELD, 266 Broad Street, Birmingham 1. Please advise condition, price.

WANTED. Practical Electronics, November 1964 to date. Half price offered. G. GROVER, 42 Ditchling Rise, Brighton.

MISCELLANEOUS

RHYTHM MODULES. Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Rd., Ferndown, Dorset.

BUILD IT in a DEWBOX quality cabinet 21n x 2 1/2in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

GEARED MOTORS

Rectifiers, Potentiometers
6d Stamp for Catalogue

F. HOLFORD & CO.
6 Imperial Square, Cheltenham

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

ARTIFICIAL LIFE

Well almost, because the NEW range of projects include: an electronic 'animal' which "LEARNS", an Electro Chemical device capable of "REPRODUCING" itself! Other projects SURE TO INTRIGUE YOU are an audio transmitter/receiver which has quite an amazing range and requires NO LICENCE; also a machine which "recognizes" itself, and an electronic dog whistle, etc., etc. HOSTS OF EASY-TO-CONSTRUCT projects, for anyone with a basic knowledge of Electronics. SEND 2/6 for your list—NOW!

To: 'BOFFIN PROJECTS'

incorporating
BIONIC DESIGNS
4 CUNLIFFE RD.

STONELEIGH, EWELL, SURREY

MISCELLANEOUS (continued)

GREEN ELECTRONICS for coils and transformers wound to your specification, assembly and wiring of circuits. "TEMPLECOMBE", Cleveland Road, Worcester Park, Surrey.

PRINTED CIRCUIT for Practical Electronics RHYTHM GENERATOR. 14 1/2in x 5 1/2in undrilled, with layout plan, for simpler and neater construction. 29/6 including postage. Send cash with order to ALMARY DESIGNS, 12 Lattimore Road, Wheathampstead, Herts.

BOOKS AND PUBLICATIONS

MAKE YOUR OWN TALKIES. An introduction to electronic tape/film synchronisation, with an explanation of the "Carol" Cinesound system, modifying equipment, filming in sync., etc. Price 7/6, post free (refundable against purchase of your "Carol" Cinesound equipment). Contronics Ltd., Deepcut, Camberley, Surrey.

GOVT. SURPLUS WIRELESS EQUIPMENT HANDBOOK

This useful Handbook gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment, etc.; also contained are some suggested modification details and improvements for the equipment. Incorporated in this revised edition is a surplus/commercial cross referenced valve and transistor guide. This book is invaluable to radio enthusiasts, radio clubs, universities and laboratories. The latest edition priced at 35/- per volume plus 5/- P. & P. is obtainable from us at

GILTEXT (LEEDS) LTD

Dept. P.E., 24 Stansfield Chambers
Gt. George Street, Leeds 1
S.A.E. with all enquiries, please. Extra postage for all foreign orders.

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/6 P.P. 6d
1155 set Circuit and Notes	6/6 P.P. 6d
H.R.O. Technical Instructions ...	5/6 P.P. 6d
38 set Technical Instructions ...	5/6 P.P. 6d
46 set Working Instructions	5/6 P.P. 6d
88 set Technical Instructions	7/- P.P. 6d
BC. 221 Circuit and Notes	5/6 P.P. 6d
Wavemeter Class D Tech. Instr.	5/6 P.P. 6d
18 set Circuit and Notes	5/6 P.P. 6d
BC.1000 (31 set) Circuit & Notes	5/6 P.P. 6d
CR.100/B.28 Circuit and Notes	10/- P.P. 9d
R.107 Circuit and Notes	7/- P.P. 6d
A.R.88D. Instruction Manual	18/- P.P. 6d
62 set Circuit and Notes	6/6 P.P. 6d
52 set Sender & Receiver Circuits	7/6. post free
Circuit Diagrams 5/- each post free.	
R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26	
A.1134, T.1154, CR.300, BC.342, BC.312,	
BC.348, J.E.M.P. BC.624, 22 set.	
Resistor Colour Code Indicator	2/6 P.P. 6d


S.A.E. with all enquiries please.
Postage rates apply to U.K. only.
Mail order only to:

Instructional Handbook Supplies
Dept. P.E., Talbot House, 28 Talbot Gardens
Leeds 8

AIRCRAFT- PLUS GENERAL V.H.F. TELECOMMUNICATIONS BAND REC.

Listen to the thrills of Aircraft, Pilots, and Airports at work. Also Civil Depta., Fire and Ambulance services. Gas and Electricity Depta. Ideal for receiving 2 metre amateurs. Gives super reception within the range of all transmissions. A fully transistorised receiver covering 108-160 mc/s. VHF broadcast. Robust attractive finished metal cabinet size approx. 7 1/4" x 4". Operates from a 9 volt internal battery. Fitted internal speaker or headphone output. Available from us at £8.19.8. Carriage and insurance 10/6. C.W.O. or COD.

HEAT LIGHT SPEED CONTROL Unit

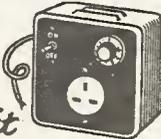

An electronic unit capable of controlling electrical equipment up to 3,000 watts capacity. Fingertip control of all a.c./d.c. electrical equipment. Suitable for all types of lighting arrangements. Incandescent lamps, spot lamps, are lamps, floodlights. Makes an ideal dimming unit. Ideal for controlling all types of electric drills and up to 2 h.p. electric motors for all applications. Ideal for all types of electric heaters. Suitable for lathes and power tools. Employs the latest electronic system. Size 6" x 6" x 2". Leaned metal case in pleasing hammer finish. Attractive front panel. Bargain price £8.19.6 p. & p. 10/-. C.O.D. if reqd.

AIR/SEA TRANS/REC. RESCUE

Compact V.H.F. Trans./Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over £50 each. Regulations state must not be operated in UK so please mention "For Dismantling purposes only" when ordering. Price £2.10.0 each, p. & p. 10/-. Two sets for £5.0.0, post free. Four sets £8, carriage free. Bulk sale of 10 sets £15, carriage £1. Export enquiries invited.



TRAWLER TOP BAND RECEIVER KIT

This wonderful little set will provide hours of listening pleasure. Super for listening to the Hams at work. A printed circuit layout makes it simple to build in a short time. Fully comprehensive instructions. Employs the latest components and transistors. Complete down to the last detail. An ideal project for beginners. Price 65/-, Post 5/-.


MINIATURE TRANSISTORISED B.F.O. UNIT
This is a miniature transistorised B.F.O. unit (tunable) that will enable your set to receive C.W. or S.S.B. reception. Compact. Single hole fixing. This small unit will fit anywhere. Ideal for all Ex-Govt. Communication Receivers and most Commercial Types. Complete with fitting instructions. 49/6, post free.

SCOOP PURCHASE TRANSFORMER SALE

Bulk purchase enables us to offer the following transformers at these ridiculously low prices. Made by a famous manufacturer and fully tested and guaranteed. Charger Transformers, 0-9-15V 2A. 9/6 each, p. & p. 2/6. Two for 17/6 post free. Transistor Power Pack Types, 6-3V at 2A, 7/6 each, p. & p. 2/6. 12V at 2A, 12/6 each, p. & p. 2/6.

GLOBE SCIENTIFIC LTD
DEPT. P.E.22 CAWOODS YARD,
MILL STREET, LEEDS 9

240 VOLT ELECTRICITY ANYWHERE

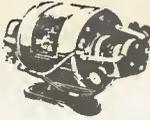

most brilliant performance ever from 12-volt Car Battery. BRILLIANT HEAVY DUTY 240 volt AMERICAN DYNAMOTOR with BIG 220 WATT OUTPUT. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and ALL UNIVERSAL AC/DC MAINS EQUIPMENT. Marvellous for Fluorescent lighting. Thousands of uses. Tremendous purchase of this model makes fantastically low price possible.

ONLY £4.19.6 each plus 10/6 delivery. C.O.D. with pleasure. MONEY BACK if not DELIGHTED. Please send S.A.E. for full illustrated details.

Dept. PE, STANFORD ELECTRONICS
Rear Derby Road, North Promenade
BLACKPOOL, Lancashire
Open 7 days a week

TAPE RECORDERS

TAPES TO DISC—using finest professional equipment—45 r.p.m. 22/-. S.A.E. leaflet. DERBY, High Bank, Hawk Street, Carnforth, Lancs.

SITUATIONS VACANT

A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

SERVICE ENGINEERS—we are an old established electronics company, but headed by a young management team, and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead, phone MICHAEL ADLER at 01-638 9606.

SERVICE SHEETS

SERVICE SHEETS (1925-69) for televisions, radios, transistors, tape recorders, record players, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

C. & A. SUPPLIERS SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, ETC.

Only 5/- each, plus S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

71 BEAUFORT PARK
LONDON, N.W.11

MAIL ORDER ONLY

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6. SHE 8441.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/6. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

TECHNICAL TRAINING by I C S IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the I C S trained man. Let I C S train YOU for a well-paid post in this expanding field.

I C S courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc.. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- * C. & G. ELECTRONIC SERVICING.
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- * RADIO AMATEURS' EXAMINATION.
- * P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how I C S can help YOU in your career. Full details of I C S courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

INTERNATIONAL CORRESPONDENCE SCHOOLS

A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!

International Correspondence Schools
(Dept. 152), Intertext House, Parkgate Road,
London, S.W.11.

NAME
Block Capitals Please

ADDRESS

4/69

EDUCATIONAL

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T/V, Telecoms., etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, 148 Holborn, London, E.C.1.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation. City & Guilds; R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for FREE Prospectus to ICS (Dept. 577), Intertext House, London, SW11.

RADIO OFFICERS see the world. Sea going and shore appointments. Trainee vacancies in Sept. and Jan. Grants available. Day and Boarding students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay, Wales.

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write: ICS, Dept. 561, Intertext House, London, S.W.11.

ENGINEERS. A technical certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B. and G.C.E. exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132-page guide. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

RECEIVERS AND COMPONENTS

ELECTRONIC STOCKMARKET kit of most parts; also "Reactalysr" and Waa-Waa pedal. S.A.E. for list. D.E.W. LTD., Ringwood Rd., Ferndown, Dorset.

L.S.T. ELECTRONIC COMPONENTS LTD.

PLEASE SEE
OUR DISPLAY ADVERTISEMENT ON
PAGE 247

PEAC OPERATIONAL AMPLIFIERS, ready built on printed circuit board. Tested and guaranteed. 34/- each, post free. WESTEK, P.O. Box 7, Rickmansworth, Herts.

RECEIVERS AND COMPONENTS (continued)

COMPONENTS AT GIVE-AWAY PRICES. Digital Counters, Rev Counters, Thyristors, Transistors, Valves, Tool Bags, Track Heads, Recording Tape, Aerials, Intercoms, Microphones, Micro Switches, Etc. 6d. stamp only, to DIAMOND MAIL ORDER PRODUCTS, Prospect House, Canal Head, Pocklington, York. NO4 2NW.

TRANSISTOR PANELS

New boxed, size 9in x 6in x 1½in with "Valvo" transistors type OC45 or similar, with full length leads, also an equal number of OA85 diodes, H/S resistors, etc. Built on perforated board in a metal frame.

Panel of 20 transistors, diodes, etc. 20/-
30 — 25/- 60 — 40/-
40 — 30/- 70 — 45/- Postage 2/- per panel.
50 — 35/- 80 — 30/-

TRANSISTOR CAPACITORS (ELECTROLYTIC)

500mF 4V	50mF 10V	10mF 25V
320mF 10V	30mF 10V	8mF 12V
250mF 4V	25mF 25V	6.4mF 64V
200mF 10V	20mF 12V	4mF 64V
100mF 12V	16mF 25V	2mF 12V
64mF 40V		1mF 25V

1/- each, 9/- per doz. Min. order 10/-
COMPUTER PANELS with 40 sil. pnp or npn transistors, Diodes and res., 22/6 Post Paid.

COMPUTER PANELS WITH SEMI-CONDUCTORS. Postage 6d per panel

8—OC42 or GET875 + 2—OA81	7/6
24—A1678 (V405A) 550 mc/s PNP + 24 Diodes	15/-
4—OC170 + 2—OC139 + 2—OC42	7/6
9—ASZ20 + 1—T2040 + 27 Diodes	7/6
4—OC42 + 6—GET875 + Diodes	7/6
2—OC170 + 1—G3036 + OC42	4/-
5—OC23 + 15—OA10	25/-
6—2N388 + 2—G2403 + 2—T2040	8/6
4—OC36 + 8—GET103 + 4—Z531A	25/-
8—ASZ20 + 80 Diodes	7/6
6—ASZ21 + 15—OA91	6/-
9—SB240 + 18—OA47	10/-
12—2G106 + 24 Diodes	9/6
8—OC72 + 8—OA10	10/-
6—OC44	5/-
6—2N388	7/6
8—OC76 + 8—OA10	7/6
12—2N388	10/-
12—A1678 (V405A) 550 mc/s PNP + 22 Diodes	10/-
36—OAS	6/-
6—GET872 + 8—OA10	5/-
4—OC42	3/-
12—ASZ20 + 80 Diodes	9/6
4—GET872 + 8—OA10	3 for 12/-
4—2G106 + 1—2N2410	4/-
2—OC42 + 8—OA47	3/-
2—GET872 + 4—OA10 + RF Chokes 3 for 10/-	6/-
24—Sil. h.f. Transistors	15/-
3—GET872 + 3—GEX541, ETC.	22/6
3—OC23 + 6—OA10 + 2—OAS	16/-

TEST CARDS. 6 transistors 20 for 20/-
ELECTROLYTICS 25,000 @ 12V, 16,000 @ 12V, 15,000 @ 10V, 10,000 @ 30V, 4,000 @ 60V, 3,000 @ 80V, 2,000 @ 50V, 1,200 @ 180V, 8/6 Post Paid.
ZENER DIODES—2.4, 2.7, 3.6, 4.75, 5.25, 5.75, 6.2, 6.8, 7.5, 13, 15, 16, 18, 20, 27, 30, 33 volts. 3/6 each, mostly 1 watt.
POLYSTYRENE CAPS. 125/350V, 270, 680, 820, 1,800, 2,200, 2,700, 6,800, 8,200, 1,200/125V, 3,900, 0.01, 0.012, 0.015 2/- doz., 4—40pf trimmers 4/- doz. Postage 1/-.
BRAND NEW BOXED CHASSIS containing 2—OC35, 2—OC29 12 VVW resistors 25/- Postage 1/6.

NEW CROSS RADIO
6 OLDHAM ROAD, MANCHESTER 4

BRAND NEW ELECTROLYTICS. 15 Volt, Long Wires, 2, 6, 8, 10, 15, 20, 30, 40, 50, 100 Mfda. 7/6 dozen, postage 1/- THE C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

ULTRASONIC TRANSDUCERS. Ideal remote control door alarms, etc. Operating frequency 40 ± 1Kc/s beam width @ 3dB Points 60°. 2 for 55/- or 30/- each. Post free. Circuit diagram available if required. THE DIAMOND STYLUS CO. LTD., Colwyn Bay, North Wales.

TAPE HEADS

BSR BRAD 39/6 pair 2 TRACK	MICHIGAN REC./PLAY HIGH IMP. 4-TRACK	45/-
BSR MALL 39/6 pair 4 TRACK	BOGEN ERASE UL218/8 4-TRACK	27/6
REITER — COLLARO ERASE 4-TRACK	COSMOCORD ERASE T.E. 2/9 4-TRACK	15/-

TRANSISTORISED FM TUNER
6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2½in S.I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.12.6

SUB-MIX. TRANSISTOR LW/MW/FM TUNER
Similar to above. Complete with aerial, tuners, dial and instructions. £14

TUNER/DULCI FMT78 STEREO £23

COMPACT TRANSISTOR FM TUNER
Oiled Walnut cabinet, brushed gold front panel, vertical styling, internal batteries. £12

FM MULTIPLEX STEREO ADAPTOR
Printed circuit biscuit, 4 trans. 6 diodes 9V with full instructions. £52.6

LOUDSPEAKERS

12" 20 watt, 15 ohm.	12" 25 watt, 15 ohm.
TWIN CONE £57.0	GUITAR SPEAKER 25-18K £57.0
FULL RANGE HIGH COMPLIANCE. 6" 16 ohm, 15 watt £518.0	10" 10 watt, 15 ohm, CERAMIC — 49/6
30-20K	MAGNET
6 1/2" 16 ohm, 10 watt, 30-18K £50.0	LOUDSPEAKERS. 2" 9/6
	40 ohm, 2 1/2" 80 ohm.
	12" TWIN CONE 10 watt PEAK 15 or 3 ohm.
4" 16 ohm, 5 watt, 40-16K £33.0	

TWEETER 3" 16 ohm, 10W CR/0.3kΩ, 18,000 c/s. £29/9

CROSSOVER NETWORK 14/-
3kcs, 16 or 3 ohm

REFLEX CONE TYPE WATERPROOF SPKR. 5 watt, 3 ohm. 300-16,000c/s PA and Music £3.10.0	MULTIMETERS from CHARGER TRANSFORMER. 4 Amp. 2 1/2/12 volt 3/- P/P
---	--

SUPER SILICON RECT. T.V., etc., 1,200 PIV 800mA, 5/-; or complete with instr. resistor, condenser, 6/8; 400 PIV HW 6A, 6/-; 200 PIV HW 6A, 6/- BY100 type, 6 for 10/-.

VHF AIRCRAFT BAND CONVERTER 75/-
Place within 1in. of MW radio

BURGLAR ALARM/FIRE ALARM DOOR BELL. LIST 37/6. OUR PRICE 7/6

CHANGER DECKS
U125 BSR with template, Mono. List 27.15.0
U125 BSR with template, Stereo. List 27.19.6
1025 Garrard with template, Mono. List 27.19.6
1025 Garrard with template, Stereo. List 28.5.0

PLINTH in simulated teak. Complete with Clearview rigid perspex cover for 1025. P/P on Decks, Plinth and Cover 7/6

SWITCH ROTARY RECIPROCATING 4 Position, 15amp. Single hole fixing, with instructions. List 14/7

C60 CASSETTE 12/6. C90 18/6

Stamped envelope for full selection and bargain offers in MULTIMETERS, RADIOS, BABY ALARMS, INTERCOMS, WALKIE-TALKIES, RECEIVERS, SINCLAIR, DULCI, and EAGLE Lists. UNDER 2/- P. & F. 6d., 21 to 23—1/6 over £3—2/6. C.O.D. 3/6. MAIL ORDER ONLY.

DURHAM SUPPLIES

367F, KENSINGTON STREET
BRADFORD 8, YORKSHIRE

Single channel Radio Control at a price you can afford

RADIO CONTROL PRODUCTS

EXCELLENT RANGE AND PERFORMANCE
TRANSMITTER—

- Crystal controlled tone Tx. 12v. operation. Silicon transistors. In smart blue anodised case with micro-switch.

Tx only £6 - 5 - 0



RECEIVER—

- Relayless weight 1½oz. Size 2½ x 1½ x ¾ in., working on 4.5 volts. In matching blue case.

Rx only £4 - 5 - 0

SUITABLE FOR MODELS OF ALL KINDS

ONLY £10 - 10 - 0 COMPLETE

Full off-the-shelf Guarantee, including crash damage, for 1 year

OBTAINABLE FROM

MODEL MART
3 COMBERTON ROAD
KIDDERMINSTER. Tel. 5879

OR DIRECT FROM

RADIO CONTROL PRODUCTS
38-FRANCHE ROAD
KIDDERMINSTER, WORCS.

R & R RADIO

51 Burnley Road, Rawtenstall
 Rossendale, Lancs
 Tel.: Rossendale 3152

VALVES BOXED, TESTED & GUARANTEED

BF80	3/-	EBC41	4/6	PY33	5/-
EBF89	3/6	PCC84	3/-	PY81	3/6
ECC82	3/-	PCF80	3/-	PY82	3/-
ECL80	3/-	PCF82	3/6	UI91	4/6
EF80	1/6	PCL82	4/-	6F23	5/-
EF85	3/-	PCL83	4/-	30F5	2/6
EY86	4/-	PL36	5/-	30L15	5/-
EL41	5/-	PL81	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/-

POST. ONE VALVE 9d. TWO TO SIX 6d.
 OVER SIX POST PAID.

TRANSISTOR BARGAIN!

High-gain low-noise npn planars
BUY NOW BEFORE PRICES RISE!

BC168B (hfe = 250 - 500 @ Ic = 2mA)
 BC168C (hfe = 450 - 500 @ Ic = 2mA)

BC168B is a smaller sized (TO 92) EXACT ELECTRICAL EQUIVALENT of BC148, and a likely direct substitute for BC108, BC171, BC183L, 2N2925, 2N2926 green, etc. These transistors have high audio gain at collector currents down to a few μ A. At normal currents they can be used from d.c. to v.h.f.

MAXIMUM RATINGS (both types)

VCE 30V; VCEO 20V; VEBO 5V.
 PC 220mW.

IC 100mA d.c. 200mA peak. Audio
 NF 2dB typ., 10dB max. ft=300MHz

Bulk purchase enables us to offer these superb modern silicon transistors at LESS THAN WHOLESALE PRICES. All mint, top grade, with makers' numbers and trade marks. Why buy unknown quantities when you can get the genuine articles at these prices? Send 6d. for full list.

EITHER TYPE OR MIXED:
5 for 10/-; 50 for 90/-; U.K. POST PAID

AMATRONIX LTD (PE)

396 Selsdon Road, South Croydon, Surrey, CR2 0DE

RELAYS, RELAYS

9V d.c. 60 ohm, 1C/O 3 amp (Magnetic Devices 703304), 2/6 each

24V d.c. 180 ohm, 2C/O 10 amp (B. & R. Relays Type 304), 4/6 each

110V d.c. 5,000 ohm, 1 Make, 1 Break, 3 amp (Londex), 5/6 each

35V d.c. 900 ohm, 3 Make, 3 amp (Magnetic Devices 695/TS.1427), 4/6 each

24V d.c. 400 ohm, 2C/O 3 amp Sealed, Octal Base (Allied Controls 828425 B/HX8), 10/8 each

24V d.c. 300 ohm, 1 Make, 1 Break, 10 amp (B. & R. Relays, Contactor), 5/6 each

6V d.c. 14 ohm, 2 Make, 15 amp (Magnetic Devices 703478), 7/6 each

110V a.c. 2 Make, 3 amp (Londex), 4/6 each

110V a.c. 4C/O, 2 amp (Londex), 7/6 each

Miniature moving coil 2 x 100 ohm, 1C/O, L/D sealed, 6in Fly Leads (Electro Methods 415), 10/8 each

6V d.c. 86 ohm, 1 Make, 3 amp (Magnetic Devices 100. 698/TS 1071), 3/- each

24V d.c. 860 ohm, 1 Make, 1 Break, 3 amp (Magnetic Devices TS1408/2), 4/6 each

24V d.c. 2 Make, 3 amp (CNZ.822006), 12/8 each

24V d.c. 150 ohm 2C/O, 10 amp (CNZ.B2792), 6/8 each

24V d.c. 400 ohm, 2C/O, 3 amp Sealed Octal Base (Forer & Brumfield 828428), 10/8 each

4V d.c. Stepping Solenoid (will take wafer switches), 3/6 each

Cut out Switch. Normal current 5 amp. At 10 amp Relay will operate and disconnect own supply. For series working (Marconi W9785 E.D.A.), 2/6 each

Carpenter Relays: 1,250 ohm + 1,250 ohm (SE 12TR), 130 ohm + 130 ohm (SE.38A), 1,040 ohm + 330 ohm (SE 12TR), 30 ohm + 110 ohm (3H.23), 2/6 each.

All Relays are in new condition. Please add 4/- in the £1 for Post and Packing. Minimum order 10/-.

K. G. SUPPLIES

10 Mallow Street, London, E.C.1

ELECTROVALUE

RAPID MAIL ORDER SERVICE

Unbeatable Value in SEMICONDUCTORS

80W BAILEY AMPLIFIER
 MJ481 and MJ491 matched pair output, 59/-; 40361 and 40362 matched pair driver, 30/3d; 40361 12/6; 40362 18/9; BC125 12/-; BC125 12/-; BC107 2/8; BC109 2/9. Main amp. PC board 12/6 each but FREE with each complete transistor set.
 Total for one channel £78.0 list with 10% discount, only **£68.18**. Total for two channels £14.16.0 list; with 15% discount only **£12.11.8**. Complete power supply kit **£4.5.0** list. Circuit reprints 1/- each.

G.E. 2N2926 PLASTIC RANGE
 Price reductions:
 Red spot = 55 to 110 2/3; Orange spot = 90 to 180 2/3; Yellow spot = 100 to 300 2/8; Green spot = 235 to 470 2/8.
 All the above brand new stock.

TEXAS SILENT RANGE
 30V 200mA npn: BC108 20V = 125 to 900 2/6
 2N3704 = 90 to 330 3/9 BC109 20V = 125 to 900 2/6
 2N3705 = 45 to 165 3/5 BC167 series (180mW 25V 200mA pnp: BC167 series (180mW 2N3702 = 60 to 300 3/6 300MHz ft, TO92): BC167 45V
 2N3703 = 30 to 150 3/3 BC168 20V = 125 to 500 2/3
 small signal npn: BC169 20V = 125 to 900 2/-
 2N3707 low noise 4/9 BC109 and BC169 are low noise.
 2N4058 low noise 4/9 BC167, BC168 and BC169 = 125 to 500 2/9 are plastic.
 Beta values for above, quoted immediately after type numbers.

FETs—Price reduced
 MPF105 25V max., gm = 2 to 6mA/V, low noise 7/6;
 2N3819 25V max., gm = 2 to 6mA/V, low noise 9/-.

MINI TRANSISTORS—Price Reduced
 2N4285 pnp hFE 35 to 150 @ 10mA IT 7MHz min., Veb 35V max.; 2N4286 npn 30V hFE over 100 @ 10mA to 1mA IT 280MHz typ.; 2N4289 pnp 60V hFE over 100 @ 100 μ A to 1mA IT 170MHz typ.; 2N4291 pnp 40V hFE over 100 @ 100mA, 2N3794 npn 40V hFE over 100 @ 100mA, complementary driver/output; 2N4292 npn 30V VHF N.F. 6dB max @ 100MHz, ft 670MHz typ.; B5041 Power 14.3W @ 100% base temp. 35V, hFE over 400 @ 0.5A. Insulated TO66 size mounting surface.
 Prices: 2N4285 to 2N4292 and 2N3794 2/11; B5041 13/8.

1,000V 1.5A GENERAL PURPOSE RECTIFIER type 1N6054 2/8 only.
1,000 0.75A miniature rectifier type TS1 1/9; 400V type TS4 2/3.

ZENER DIODES 3V to 27V 5% 400mW all preferred voltages, 4/6 each.

NEW TRANSISTOR BARGAINS
ALL POWER TYPES SUPPLIED WITH FREE INSULATING SETS.
 2N696 6/6 2N171 7/4 2N4060 4/3 BC148 3/6
 2N697 6/- 2N147 16/9 40250 15/- BC149 4/3
 2N706 3/5 2N269A 40406 16/8 BD123 24/3
 2N1132 18/- 40403 14/8 BF194 7/-
 2N1302 4/- 2N2646 9/6 AC126 6/6 BFX29 12/3
 2N1303 4/- 2N2924 5/- AC128 6/- BFX84 7/5
 2N1304 4/- 2N2926 5/8 AC176 11/- BFX85 8/3
 2N1305 4/- 2N3058 5/6 ACY17 8/- BFX88 7/9
 2N1306 6/9 2N3054 15/6 AD161 7/- BFY51 4/-
 2N1307 6/9 2N3056 16/6 AD162 7/- BSX20 4/6
 2N1308 8/8 2N3391A AF114 7/6 BSX20 4/6
 2N1309 3/9 5/8 AF124 7/6 NKT403
 2N1613 6/6 2N3706 3/8 BC147 4/3 14/10

ALL GOODS BRAND NEW—NO SURPLUS

1989 CATALOGUE now ready, full of most up to date information essential to every serious user. Send 1/6 for your copy
COMPONENT DISCOUNTS
 10% on total order over £3.0. 15% on total order over £10.0. *Unless stated otherwise*
POSTAGE AND PACKING on orders up to £1, add 1/-; over, post free in U.K.
OVERSEAS ORDERS WELCOMED Carriage charged at cost

ELECTROVALUE Dept. P.E.4

32A ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
 Telephone: EGHAM 5533 (STD 0784-3)

RESISTORS
METAL OXIDE type TR5 0.5W 2% tolerance. Very low noise, low temperature coefficient, low drift. A Professional resistor. All E24 preferred values 10 Ω to 1M Ω . Price: 1 to 11 10d; 12 to 25 8d; 25 up 6d.
CARBON FILM high stab low noise.
 W 10% 1 Ω to 33 Ω and W 5% 3.9 Ω to 1M Ω 1/10 doz., 14/6 100.
 W 10% 4.7 Ω to 10M Ω , 1/9 doz., 13/6 100.
 W 5% 4.7 Ω to 10M Ω , 2/2 doz., 17/- 100.
 W 10% 7.7 Ω to 10M Ω , 3/3 doz., 25/10 100.
 1/5 less per 100 if ordered in complete 100s of one ohmic value.
Beise state resistance values required.
Carbon Skeleton pre-sets: 100 Ω , 250 Ω , 500 Ω , 1k Ω , 2k Ω , 2.5k Ω , 5k Ω , 10k Ω , 20k Ω , 25k Ω , 50k Ω , 100k Ω , 200k Ω , 250k Ω , 500k Ω , 1M Ω , 2M Ω , 2.5M Ω , 5M Ω , 10M Ω . Vertical or horizontal mounting.
 Small high quality, 1/- each; Sub-mini, type 11d each.

PEAK SOUND PRODUCTS
 Peak Sound P.A.12-5 Power Amplifier has a maximum distortion level of only 0.1% at 11.5W, into 16 Ω . In kit form **£9.18.6**, plus 12/- for ready prepared heat sink and mounting board. Power supply ES.45 Kit **£4.10.0**.
 Pre-amp kit 27/- plus controls mono: 6/3; stereo 20/-.
 Active tone filter kit 18/- plus controls: mono 5/-, stereo 16/-.
 No discounts allowable on basic kits only.

ELECTROLYTICS
SUB-MIN.
 C426 range (μ F/V): 0.6/4, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4/40, 5/64, 6.4/64, 6.4/25, 8/4, 10/2.5, 10/16, 10/64, 12.5/25, 16/10, 16/40, 20/16, 20/64, 25/64, 25/25, 32/4, 32/10, 32/40, 32/64, 40/2.5, 40/16, 50/64, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/64, 125/4, 125/10, 125/16, 160/2.5, 200/64, 200/10, 250/4, 320/2.5, 320/64, 400/4, 500/2.5. **Price reduction 1/8 each.

MINIATURE (μ F/V):
 5/10, 10/10, 25/10, 50/10, 8d each, 25/25, 50/25, 100/10, 200/10, 1/- each; 50/50, 100/25, 1/6; 100/50, 25/25, 2/-.

LARGE ELECTROLYTICS (μ F/V):
 1000/50 7/-; 2000/50 8/3; 5000/50 17/6; 5000/25 10/3; 2000/64 15/-.
 Vertical clips for above types 9d each.

CAPACITORS
 Ceramic disc 20% 500V: 1,000pF, 2,000pF, 5,000pF, 50V: 0.01 μ F, 0.02 μ F, 0.05 μ F. Mylar film 10% 100V: 1,000pF, 2,000pF, 5,000pF, 0.01 μ F, 0.02 μ F, 0.05 μ F. Polystyrene 5%, 160V: 22pF preferred values to 820pF. ALL @ 5d each. Polyester 50V 20%: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1 μ F 7d each. 0.1 μ F 8d. 230V 10%: 0.16, 0.22 9d; 0.33 1/2; 0.47 1/6; 1 μ F 2/3; 2.2 μ F 4/-.

POTENTIOMETERS
 Price Reduced
 Short spindle 100 Ω to 10M Ω lin, 5K Ω to 5K Ω log, std. values. Only 2/- each.
 Long spindle 4.7k Ω 10k Ω , 22k Ω , 47k Ω , 100k Ω , lin or log. Only 2/6 each.
 Long spindle dual series: 10k Ω , 22k Ω , 47k Ω , 100k Ω , 220k Ω lin or log. Only 8/6 each.

RECEIVERS AND COMPONENTS

(continued)

50,000 TRANSISTORS to be cleared in lots of 50 for £1. Types available are germanium similar to OC44, and silicon similar to OC202. All transistors fully tested and guaranteed. Post free. WESTEK, P.O. Box 7, Rickmansworth, Herts.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS

2in x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price. 10 boards 10/-. P. & P. 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors.

100 boards 65/-. P. & P. 6/6. With a guaranteed minimum of 350 transistors.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-. P. & P. 2/-.

NPN GERMANIUM TOS 1 WATT POWER TRANSISTORS on small heat sink, on 2in x 4in panel. 5 for 10/-. P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 ex eqpt., 4 for 10/-. P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 on Finned Heat Sink (10D) 4 for £1, P. & P. 3/-.

LONG ARM TOGGLE SWITCHES ex eqpt. SPST 13/6 doz., DPST 15/- doz. P. & P. all types 2/- doz.

ORGAN BUILDERS' SPECIAL 500 TO18 TRANSISTORS on panels. £4, P. & P. 6/-.

OVERLOAD CUT OUTS. Panel mounting in the following values . . . 5/- each. 2, 3, 4, 5, 7, 8 amp. P. & P. 1/6.

MINIATURE GLASS NEONS, 12/6 doz. P. & P. 1/6.

150 PIV. 10 amp. **BRIDGE RECTIFIERS** on **FINNED HEAT SINK.** 12/- + 2/-. P. & P. ea.

LARGE CAPACITY ELECTROLYTICS 4 1/2in, 2in diam. Screw terminals. All at 6/- each + 1/6 each P. & P.

4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
6,600mF 45V d.c. wkg.
1,500mF 150V d.c. wkg.
16,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

Send 1/- stamps for list.

KEYTRONICS, 52 Earls Court Road
London, W.8. Mail order only

10W AMPLIFIERS

SSAR3. 10W push-pull output. TW99 output trans. 4 valve EF94, ECC81, Two EL90. Full chassis mounting. New and boxed. Complete with circuit drawings. £2.10.0. P. & P. 10/-.

19 set power unit, new with handbook, £3.10.0. P. & P. 10/-.

Mixer Units Type 18. H.F., M.F., L.F. Valve V885. 10/-. P. & P. 2/6.

Micro-Ammeters for Instrument Mounting, 0-100mA 30/-. P. & P. 2/6.

Micro-Ammeters Type Y 0-100mA, Heavy duty with leads. £3. P. & P. 5/-.

Flexible Metal Tubing, Galvanised: 1/2 int. dia. 35/- 100ft. P. & P. 7/6.

Field telephones Type F. 32/6. P. & P. 7/6.

CHASSIS UNIT. 7 valves ECC82 (3), EB91 (3), 6F33 (1). 45 Capacitors, Resistors, etc. Valve bases and cans. 20/-. P. & P. 4/6.

CABLE. Six core (75 yd approx.) and drum assembly. 25/-. P. & P. 4/6.

Resonance performance testers, S band, 0-25dB, 3,260-3,340Mc/s. £10. P. & P. 10/-.

SEND US YOUR TRANSFORMER REQUIREMENTS, 1,000 IN STOCK

S.A.E. FULL LIST.

STATUS SUPPLIES


STATUS HOUSE, WILKINSON AVE., BLACKPOOL

HOLIDAYS

HOLIDAY FOR BOYS 14/16 years August 1969, specialising in engineering, electronics, photography. Tuition, and practical work including go-karting. 11 days—£14.10.0. Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, 47 Marylebone Lane, London W.1.

PLEASE MENTION
PRACTICAL ELECTRONICS
WHEN REPLYING TO
ADVERTISEMENTS

HI-FI SOLID STATE AUDIO AMPLIFIER

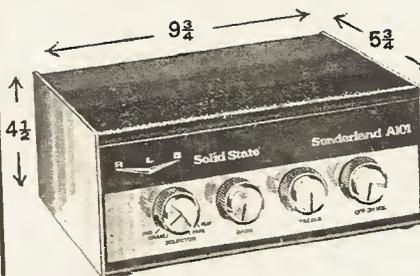

10 Watts continuous sine wave output. 15 Watts music power. Output 3-16 ohms impedance. Frequency response 15 Hz to 18 KHz-1dB.

Distortion at full power <0.15%.

This instrument comes to you complete with pre-amplifier, main amplifier and power unit. (A.C. Mains) in modern styled aluminium stelvite case.

Factory built and tested for the amazingly low price of 16 Gns. P. & P. 5/6.

SUNDERLAND ELECTRICS
48 Princess Street, Manchester 1

TRADE ENQUIRIES INVITED S.A.E. WITH ENQUIRIES PLEASE.

CRESCENT RADIO LTD.

(electronic component specialists)

For all regular components try
40 Mayes Road, Wood Green, N.22
For surplus components and Hi-Fi equipment try
11 Mayes Road, Wood Green, N.22

SOME COMPONENT BARGAINS

OC19 power transistor	5/- each
Model motor 6 to 12 volt, 9,000 rpm, 400 m/a	4/6 each
1 inch spun aluminium standard 1/2 inch spindle grub screw type knob. For a professional finish to all equipment	2/6 each
Double Pole Rotary on/off switch standard mains type	2/- each
Transistor radio cabinet ideal for your home built radio, 6 x 3 1/2 x 2 inch	3/- each
2 1/2 inch 80 ohm loudspeaker	5/6 each
Wearite Hyperloop Transformer type 210	3/6 each
120 volt 250 m/a tvl rectifier	1/- each
Car suppressor coil type	1/6 each
500 mfd 12 volt electrolytic capacitor	1/3 each
Toggle switch mains standard type	1/6 each
Connecting blocks, 4 way standard screw type	6d each 5/6 per doz.
Bargain boards, computer boards full of transistors, diodes and components—a real bargain for the home constructor	7 boards—10/-

With our new premises in Mayes Road we can now offer an even wider selection of components for the home constructor and enthusiast.

POSTAGE WITH ORDER PLEASE

P.S. Our new catalogue is now available at 1/6 per copy

The RADIO AMATEURS HANDBOOK 45/-

1969 Ed. by A.R.R.L. Postage 4/6

AUDIO AMPLIFIERS by Data. 10/6. P. & P. 1/-.

THE DESIGNERS GUIDE TO BRITISH TRANSISTORS by Kampel. 25/- . P. & P. 1/6.

HI-FI YEAR BOOK 1969 ED. 15/- . P. & P. 1/9.

UNDERSTANDING ELECTRONIC TEST EQUIPMENT by Risse. 30/- . P. & P. 1/6.

TRANSISTORS IN LOGICAL CIRCUITS by Altas. 16/- . P. & P. 1/3.

RADIO COMMUNICATIONS HANDBOOK by R.S.G.B. 63/- . P. & P. 4/6.

PRACTICAL OSCILLOSCOPE HANDBOOK by Turner 25/- . P. & P. 1/6.

F.E.T. PRINCIPLES, EXPERIMENTS & PROJECTS by Noll. 40/- . P. & P. 2/-.

49 EASY TRANSISTOR PROJECTS by Brown and Kneitel. 16/- . P. & P. 1/3.

SERVICING DIGITAL DEVICES by Kyle. 26/- . P. & P. 1/6.

TRANSISTOR CIRCUITS FOR RADIO CONTROLLED MODELS. 7/6. P. & P. 1/-.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2
(Leicester Square Tube Station)

Phone 01-437 4560

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 17/8. DAF96, DF96, DK96, DL96, 4 for 26/-.

OZ4	4/6	19BGG17/8	DL92	5/8	EL90	5/-	PEN44 12/8	UCC84	7/8	
1A7GT	7/6	20F2 13/8	DL94	5/8	EL95	5/-	PEN36C15	UCC85	6/8	
1H8GT	7/8	20F8 11/8	DL96	7/-	EM80	5/8	PFL20018/-	UCC80	8/8	
1N8GT	7/8	20P24 18/8	DY86	5/8	EM81	6/8	PL36	9/8	UCH42	9/8
1R4	6/8	20T4G11/8	DY87	5/8	EM84	6/8	PL81	7/8	UCH81	6/8
1S5	4/8	30C1 6/8	E44C80	6/8	EY11	7/8	PL82	6/8	UCL82	7/8
1T4	2/8	30C15 13/-	EAF42	8/8	EY61	7/8	PL83	6/8	UCL83	11/8
384	5/8	30C18 9/-	EB91	2/8	EY85	6/8	PL84	6/8	UL41	7/-
3V4	5/8	30F5 13/8	EBC33	7/8	EZ40	7/8	PL800 12/-	UF80	9/8	9/8
6Y4G	4/8	30FL1 12/8	EBC41	8/8	EZ41	7/8	PL504 12/8	UF85	6/8	7/-
6Z4G	7/8	30FL2 14/8	EBF80	6/-	EZ80	4/8	PL508 15/-	UF89	6/8	6/8
6Y3GT	5/8	30FL14 10/8	EBF89	6/8	EZ81	4/8	PL802 14/8	UL44	20/-	20/-
6S0L2	12/8	30L1 6/-	ECC81	8/8	EZ92	8/8	PY26 10/8	UL84	6/8	6/8
6AL5	2/8	30L15 14/-	ECC82	4/8	KT32	5/8	PY31 5/8	UM94	7/8	7/8
6AM6	3/8	30L17 13/8	ECC83	7/-	KT61	8/8	PY32 10/-	UY41	7/8	7/8
6AQ5	4/8	30P4 12/-	ECC84	5/8	KT66	16/-	PY33 10/-	UY85	5/8	5/8
6AT6	4/-	30P12 11/8	ECC85	5/-	ME140015/-	14/8	PY81 5/8	VP48	10/8	10/8
6AU6	4/8	30P19 12/-	ECC86	6/8	N78 14/8	8/8	PY82 5/8	VP121 21/-	21/-	21/-
6BA6	4/8	30PL1 12/8	ECC80 7/-	PCB80 7/-	PC86 9/8	PC88 9/8	PY83 5/8	Z77 3/8	3/8	3/8
6BE6	4/8	30PL13 14/8	ECC82 4/8	PC86 9/8	PC88 9/8	PC89 8/8	PY88 6/8	AC107	3/8	3/8
6B36	7/-	30PL14 15/-	ECC83 5/8	PC86 9/8	PC88 9/8	PC89 8/8	PY88 6/8	AC127	2/-	2/-
6B36	7/-	30PL14 15/-	ECC83 5/8	PC86 9/8	PC88 9/8	PC89 8/8	PY88 6/8	AD140	7/8	7/8
6B18	3/8	33L6GT 3/-	ECH42 10/8	PC90 8/8	PC92 8/8	PC93 8/8	PY801 6/8	AD140 18/-	18/-	18/-
6E14	9/-	35Z4GT 5/-	ECH81 5/8	PC97 8/8	PC99 8/8	PC99 8/8	R20 12/8	AF116 3/8-	3/8-	3/8-
6E23	18/8	6063 12/8	ECL80 6/8	PC98 9/8	PC98 9/8	PC98 9/8	R19 8/8	AF117 3/8-	3/8-	3/8-
6E7G	2/8	AZ31 9/-	ECL82 6/8	PC98 9/8	PC98 9/8	PC98 9/8	R20 12/8	AF124 7/8	7/8	7/8
6E8G	4/8	B729 12/8	ECL83 9/8	PC98 9/8	PC98 9/8	PC98 9/8	U26 12/-	AF125 3/8	3/8	3/8
6L18	6/8	CCH35 10/-	ECL86 8/8	PC98 9/8	PC98 9/8	PC98 9/8	U26 12/-	AF126 7/8-	7/8-	7/8-
6V6GT	6/8	CY31 6/8	EF59 3/8	PCF80 6/8	PCF80 6/8	PCF80 6/8	U47 18/8	AF127 3/8	3/8	3/8
6X4	3/8	DAC32 7/8	EF80 4/8	PCF82 6/8	PCF82 6/8	PCF82 6/8	U49 13/8	AF127 3/8	3/8	3/8
6X6GT	5/8	DAF91 4/8	EF85 5/8	PCF86 9/8	PCF86 9/8	PCF86 9/8	U52 8/8	OC25 5/8	5/8	5/8
7B6	10/8	DAF96 6/-	EF86 6/8	PCF80 13/8	PCF80 13/8	PCF80 13/8	U78 8/8	OC44	2/8	2/8
7B7	7/-	DF33 7/8	EF89 5/8	PCF80 13/8	PCF80 13/8	PCF80 13/8	U91 12/8	OC45 2/8	2/8	2/8
7C6	6/8	DF91 2/8	EF91 3/8	PCF80 2/8	PCF80 2/8	PCF80 2/8	U301 12/8	OC71 2/8	2/8	2/8
7Y4	6/8	DF96 6/-	EF94 3/8	PCF80 9/8	PCF80 9/8	PCF80 9/8	U801 18/-	OC72 2/8	2/8	2/8
10F1	15/-	DH77 4/-	EF183 6/-	PCF80 11/8	PCF80 11/8	PCF80 11/8	UABC90 6/8	OC75 2/8	2/8	2/8
10P13	15/8	DH31 10/8	EF184 5/8	PCF80 10/8	PCF80 10/8	PCF80 10/8	UB41 6/8	OC81 2/8	2/8	2/8
12AT7	8/8	DK32 7/8	EH90 6/8	PC182 7/8	PC182 7/8	PC182 7/8	UBC41 7/8	OC81D 2/8	2/8	2/8
12AUV	4/8	DK91 5/8	EL33 8/8	PC183 9/8	PC183 9/8	PC183 9/8	UBC81 7/8	OC81D 2/8	2/8	2/8
12AU7	4/8	DK92 9/8	EL34 8/8	PC184 7/8	PC184 7/8	PC184 7/8	UBF80 6/-	OC82 2/8	2/8	2/8
12AX7	4/8	DK96 7/-	EL41 6/8	PC185 8/8	PC185 8/8	PC185 8/8	UBF89 6/8	OC82D 2/8	2/8	2/8
12X8GT	7/-	DL35 5/-	EL54 4/8	PC186 8/8	PC186 8/8	PC186 8/8	UC92 5/-	OC170 2/8	2/8	2/8

READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.
Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage In Transit 6d. extra.

ERSIN



5 CORE SOLDER

for quick, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



SIZE 15 SOLDER DISPENSER

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



SIZE 12

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



BIB MODEL 8 WIRE STRIPPER AND CUTTER

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.

From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

MINIATURE RESISTORS LOW NOISE—CARBON FILM

- 1 watt 5% E24 Series 3/6 per doz.
- 1 watt 5% E24 Series 3/9 per doz.
- 1 watt 10% E12 Series 3/3 per doz.
- 1 watt 10% E12 Series 3/6 per doz.

Minimum order 1 doz.—mixed values

Free postage and packing but C.W.O.

ABRAHAM and PARTNERS
71 Kenley Road, London, S.W.19

BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 9v; 7 1/2v; 6v; 4 1/2v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17

SEND S.A.E. FOR NEW STOCK LISTS

WENTWORTH RADIO

104 SALISBURY ROAD, HIGH BARNET

01-449 3087

OA81 1/6
OA91 1/6
OC44 2/8
OC45 1/8
OC71 2/6
OC72 2/6
OC75 2/6
OC81 2/2
OC81D 2/3
OC170 2/9
OC171 2/9
OC201 2/3
BC107 2/3
BC108 3/9
BC109 4/9
BCY43 7/-
BCY70 5/-

BY100 4/6
BFY50 6/6
BFY51 4/-
BFY52 6/-
BFY53 4/9
AC126 4/6
AC127 5/-
2N404 5/-
2N696 5/-
2N697 5/-
2N706 5/3
2N1304 2/3
2N2923 4/-
2N2924 4/-
2N2925 5/-

2N2926 2/9
NKT121 8/6
NKT122 5/11
NKT126 6/3
NKT128 6/-
NKT213 6/-
NKT214 3/9
NKT215 4/9
NKT274 4/-
NKT275 4/-
NKT403 16/-
NKT405 14/9
NKT713 5/3
NKT773 4/9
NKT781 5/9
NKT16229 12/-
NKT20329 12/6

Cash with Order

P. & P. 1/-

BUILD YOUR CIRCUITS on VEROBOARD

—the Universal Wiring Board—obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants



AMAZING MINI-DRILL

FOR PRECISION MODEL WORK



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6 p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money Ref. Guarantee.

MERLIN SUPPLY CO.

Dept. PE3D, Nailsea, Bristol BS19 2LP

Silicon N.P.N. transistors. Similar to 2N2926. All individually tested. Gold plated leads for easy soldering. Unbeatable value at 1/6 each or £5 per 100.

12 VOLT TRANSISTORISED FLUORESCENT LIGHT.* 8 WATT 12in TUBE. Current drain only 700mA! Complete and tested £2/19/6 only! Or in kit form:

*Case	10/-	Transistor ..	10/-
Lamp holders— pair	5/-	Condensers, etc.	3/-
Transformer	13/6	Tub	8/-

*Post and Packing 3/-.

TRANSISTORS

OC200, OC203, OC204, all at 2/- each.
 ASY22, 2N753, BSY28, BSY65, 2G344A, 2G345A, 2G345B, 2G371A, 2G378A, all at 1/6 each.

Transistors similar to OC44, OC71 and OC72, all 1/- each. Unmarked, untested transistors, 7/6 for 50.

LIGHT SENSITIVE TRANSISTORS (similar OCP 71), 2/- each. 30 watt transistors (ASZ17), 10/- each.

ORP 12 Cadmium sulphide light-sensitive resistors 9/-.

RESISTORS

BY100, 800 p.i.v., 2/6 each, 24/- per doz., £7/10/- per 100, £50 per 1,000.
 BYZ13, 6-amp, 400 p.i.v., available on same terms.

MULLARD POLYESTER CAPACITORS FAR BELOW COST PRICE!

0-001µF 400 volts ..	3d	0-15µF 160 volts ..	6d
0-0015µF 400 volts ..	3d	0-22µF 160 volts ..	6d
0-0018µF 400 volts ..	3d	0-27µF 160 volts ..	6d
0-0022µF 400 volts ..	3d	1µF 125 volts ..	1/-
0-01µF 400 volts ..	3d		

VERY SPECIAL VALUE! Small Silver-mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. 10/- per 100.
PAPER CONDENSERS, MIXED BAGS, 0-0001 to 0-5µF. 12/6 per 100.

RESISTORS! Give-away offer! Mixed types and values. 1/2 to 1/2 watt. 6/6 per 100, 55/- per 1,000. Individual resistors 3d each. Also 1/2 to 3 watt close tolerance. Mixed values. 7/6 100, 55/- 1,000.

WIRE-WOUND RESISTORS. 1 watt to 10 watts. Mixed bags only. 16 for 10/-.

RECORD PLAYER CARTRIDGES

ACOS

GP 67/2 Mono.	15/- complete with needles.
GP 91/3 Stereo Compatible	£1/-
GP 93/1 Stereo Ceramic	£1/5/-
GP 94/1 Stereo Ceramic	£1/5/-

Small pick-up arms complete with cartridge and needle, 10/- only.

UNREPEATABLE OFFER!

GIANT SELENIUM PHOTO-CELLS
 PRODUCE UP TO 6ma FROM DAYLIGHT!
 67mm. diameter (29.2 sq. cm.) 10/- each
 50mm. x 37mm. (16.5 sq. cm.) 2 for 10/-

TRANSISTORISED SIGNAL INJECTOR KIT R.F./I.F./A.F. 10/-
TRANSISTORISED SIGNAL TRACER KIT 10/-
TRANSISTORISED REV. COUNTER KIT 10/-

VEROBOARD

2 1/2in x 1in 0-15in matrix	1/6	17in x 2 1/2in 0-15in matrix	11/-
3 1/2in x 2 1/2in 0-15in matrix	3/3	17in x 3 1/2in 0-15in matrix	14/8
3 1/2in x 3 1/2in 0-15in matrix	3/11	3 1/2in x 2 1/2in 0-1in matrix	4/2
5in x 2 1/2in 0-15in matrix	3/11	3 1/2in x 3 1/2in 0-1in matrix	4/9
5in x 3 1/2in 0-15in matrix	5/6	5in x 2 1/2in 0-1in matrix	4/7
		5in x 3 1/2in 0-1in matrix	5/6

Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6—3/6.

MULTIMETERS. 20,000 ohms per volt.

Ranges: a.c. 1,000V, 500V, 100V, 50V, 10V.
 d.c. 250mA, 2-5mA, 50µA
 d.c. 2,500V, 500V, 250V, 50V, 25V, 5V.
 Resistance: 0/60kΩ and 0/6MΩ. Special price £4 only.

ELECTROLYTIC CONDENSERS

0-25µF 3 volt	4µF 4 volt	10µF 25 volt	64µF 9 volt
1µF 6 volt	4µF 12 volt	20µF 6 volt	100µF 9 volt
1µF 20 volt	4µF 25 volt	25µF 6 volt	320µF 4 volt
1-25µF 16 volt	5µF 6 volt	25µF 12 volt	320µF 10 volt
2µF 3 volt	6µF 6 volt	25µF 25 volt	400µF 6-4 volt
2µF 350 volt	8µF 3 volt	30µF 6 volt	
2-5µF 16 volt	8µF 12 volt	30µF 10 volt	
3µF 25 volt	8µF 50 volt	50µF 6 volt	
3-2µF 64 volt	10µF 6 volt	64µF 2-5 volt	

All at 1/- each.
 20 assorted (our selection) 10/-.

SKELETON PRE-SET POTENTIOMETERS. 100Ω, 100KΩ, SLIDERS. 680KΩ. 6d each.

SMALL TRANSISTOR OUTPUT TRANSFORMERS 2/6 each.
SMALL TRANSISTOR DRIVER TRANSFORMERS 2/6 each.

TAPE RECORDER MICROPHONES 12/-.

Orders by post to:

G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/- Stamped addressed envelope must accompany any enquiries. For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

The most accurate pocket size CALCULATOR in the world




The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send 82/6 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. PE 22)
 54 Dundonald Road, London, S.W.19

FREE BOOKLET ON REQUEST

12in. DE-LUXE MKII £9

The exceptional quality and performance of the "De-luxe MKII" brings truly rich satisfying sound from a single loudspeaker, recreating the musical spectrum virtually flat ±5db. 25 to 16,000 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker "FERROBA" magnet assembly having a flux density of 14,000 gauss and a total flux of 150,000 Maxwells. Bass resonance 32-38 c.p.s. Rated 15 watts. Voice coils available 3 or 8 or 15 ohms. Suitable for any High Fidelity System. Design capability concept and programmed third generation hardware giving fantastically delightful sound.

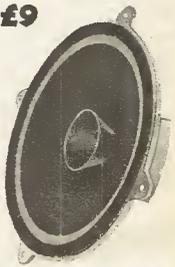

Further details and 48 page Enclosure Manual 5/9 post paid.

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

MARTIN IS HIGH FIDELITY

plus

ADD-ON-ABILITY
THRILLING POWER
DEPENDABILITY
GENUINE ECONOMY

How would you like to start with a simple amplifier, say, and add to it until it became a fully stereo twenty watt amplifier with FM tuner and facilities to take the most sensitive low output pickups ever made? With Martin Audiokits it's easy, for with these superbly engineered all-transistor prefabricated units, success is built in from the start and you build to your own preferred plan. IT'S A MONEY SAVING SCHEME, TOO.

Details from:—

● Trade enquiries invited.

MARTIN ELECTRONICS LTD., 155 High Street, Brentford, Middlesex. ISLeworth 1161

To MARTIN ELECTRONICS, 155 High Street Brentford, Middlesex

I have not had your leaflets before. Please send them on
 AMPLIFIERS FM TUNER RECORDKITS
 (Tick as required)

NAME.....

ADDRESS.....

PE 4

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

ELECTRONIC ENG.

Advanced Electronic Eng.—
Gen. Electronic Eng.—
Applied Electronics—
Practical Electronics—
Radar Tech.—
Frequency Modulation—
Transistors.

ELECTRICAL ENG.

Advanced Electrical Eng.—
General Electrical Eng.—
Installations—
Draughtsmanship—
Illuminating Eng.—
Refrigeration—
Elem. Elec. Science—
Elec. Supply—
Mining Elec. Eng.

CIVIL ENG.

Advanced Civil Eng.—
General Civil Eng.—
Municipal Eng.—
Structural Eng.—
Sanitary Eng.—
Road Eng.—
Hydraulics—
Mining—
Water Supply—
Petrol Tech.

RADIO & T.V. ENG.

Advanced Radio—
General Radio—
Radio & TV Servicing—
TV Engineering—
Telecommunications—
Sound Recording—
Automation—
Practical Radio—
Radio Amateurs' Examination.

MECHANICAL ENG.

Advanced Mechanical Eng.—
Gen. Mech. Eng.—
Maintenance Eng.—
Diesel Eng.—
Press Tool Design—
Sheet Metal Work—
Welding—
Eng. Pattern Making—
Inspection—
Draughtsmanship—
Metallurgy—
Production Eng.

AUTOMOBILE ENG.

Advanced Automobile Eng.—
General Auto. Eng.—
Auto. Maintenance—
Repair—
Auto. Diesel Maintenance—
Auto. Electrical Equipment—
Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A.,
A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG.,
CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Electronics, Radio, T.V., Etc.,
A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Electronics
Electronics Engineering
Practical Radio
Radio & Television Servicing
Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T.
NOW offers you a real laboratory training at home with practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy now—FREE and without obligation.



POST COUPON NOW!

TO B.I.E.T., 316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published about the 15th of the month by IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2, at the recommended maximum price shown on the cover. Printed in England by THE CHAPEL RIVER PRESS, Andover, Hants. Sole Agents—Australia and New Zealand: GORDON & GOTCH (A/sia) Ltd.; South Africa and Rhodesia: CENTRAL NEWS AGENCY LTD.; East Africa: STATIONERY & OFFICE SUPPLIES LTD. Subscription rate including postage for one year: To any part of the World £2 2s. 0d.

11 BREEZE

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE-HIGH FIDELITY

AUDIO EQUIPMENT

Mono or Stereo Audio. Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM **£15.5.0**

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately.

SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



Acclaimed by everyone MAYFAIR ELECTRONIC ORGAN

A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service.




Once built the 'MAYFAIR' will then provide years of enjoyable entertainment. **ONLY 99 Gns.**
Call in. See it and play it yourself.

ORGAN COMPONENTS: We carry a comprehensive stock of organ components for TRANSISTOR AND VALVE FREE PHASE designs. Ask for BROCHURE 9

Deferred terms available. COMPLETE KIT Deposit £29.19.0. 12 monthly payments of £7. TOTAL £113.19.0. EXPORT ENQUIRIES INVITED

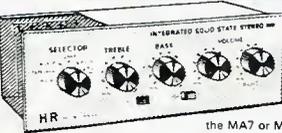BUILT AND TESTED Deposit £36.6.0 & 12 monthly payments of £9. Total £144.8.0. RHYTHM UNIT £59.10.0 pp. 10/-



INTEGRATED SOLID STATE TRANSISTOR POWER AMPLIFIERS

Complete with full Bass Treble, Volume and Selector Controls

MA66 12 WATTS STEREO
We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways being suitable for use with all types of PICK-UPS, TUNERS, DECKS and MICROPHONES—with fantastic power and quality with far greater adaptability with freedom for battery or mains operation. Output is from 3-16 OHMS. Whether you require a home or portable HI-FI installation, electronic guitar, P.A. System, Intercom.

the MA7 or MA66 will FILL THE BILL

for complete MA7 MONO **£8.10.0** OR THE STEREO **£16.10.0**

POST PACKING 5 EITHER MODEL Suitable for either model. OPTIONAL MAINS UNIT PS20 62 6d pp.4/-

Illustrated leaflets 12 and 14 FREE on request. Demonstrations Daily at our 309 Edgware Rd. Branch.

SINCLAIR EQUIPMENT

IC10 Integrated Circuit Amplifier 59.6
212 Amplifier 89.6
Micromatic (Kit) 48.6
Micromatic (Built) 59.6
P24 Power Unit 99.6
Stereo 25 £5.19.6
O14 Speaker System £7.19.6

All POST PAID. Delivery from stock.

DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.

TOTAL COST £6.19.6. P.P. 4/6
TO BUILD Send for Brochure 1

NEW MODELS NOMBREX TEST EQUIPMENT

MODEL	£	s.	d.	No.
22 Power Supply	14	0	0	22
30 Audio Generator	19	10	0	24
31 R.F. Generator	12	10	0	25
32 C.R. Bridge	10	10	0	26
33 Inductance Bridge	20	0	0	29

Send for descriptive illustrated Brochure.

QUALITY CAR RADIOS

A precision engineered car radio that's perfect company for long hours on the road. Has quick push-button operation for immediate station selection and choice of Medium or Long wave frequency. Output of 31 watts ensures crisp, top quality sound even at high motoring speeds. Includes full accessories and instructions.

POSITIVE/NEGATIVE EARTH PRICE £12.12.0 pp. 4/6
MANUAL as above £8.19.6. but with single MW/LW Push Button.

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses. Intercoms. Baby. Alarm. Guitar Practice. Telephone or Record Player Amplifier.

Optional Resene covered Wood cabinet 12 x 9 x 4 12.6. 7 x 4 in. speaker, 17/6. **45/-** pp. 2/6d.

Uses PPS battery. Ask for Leaflet 2

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK you need a MARTIN RECORDAKIT. This comprises a special high quality 8 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED

2 Track 36 gns. P.P. 22/6 either model
4 Track 39 gns. Today's ASK FOR BROCHURE 6 Value £60.

Kit comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1, 200 Ft. tape, spare spool. ALL UNITS AVAILABLE SEPARATELY.

VHF FM SUPERHET TUNER MKII

15 MULLARD TRANSISTORS & 4 DIODES - 300 Kcs BANDWIDTH - PRINTED CIRCUIT CONSTRUCTION - HIGH FIDELITY REPRODUCTION MONO AND STEREO

A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and, with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability, economically priced.

TOTAL COST £8.19.6. DECODER £5.19.6. (CABINET 20/- EXTRA) ASK FOR LEAFLET 3.

NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES

* RM12 1.35 volts 3600 mA/h OUR PRICE 5/- each Size 2" x 3" dia.
* RM25 10.35 volts 350 mA/h Pack of 6. Size 4" x 3" dia. OUR PRICE 10/- each

401
* RM25 10.35 volts 1.35v. cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITIES AVAILABLE.

GARRARD RECORD DECKS

BRAND NEW All below list price

MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY, SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES, coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY, WRITE TO US (on Company Headed Notepaper please) requesting our SEMI-CONDUCTOR BULLETIN. For TELEPHONE QUOTATIONS, PHONE (01) 723 1008/9 Extn. 4 (01) 723 0401 Extn. 4.

We purchase medium to large quantities of Transistors and Devices excess to Manufacturers and Distributors requirements.

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 TYPES. Send for your FREE COPY TODAY. (list 36)

S.C.R.'s from 5/-
Field Effect Transistors from 9/6
Power Transistors from 5/-
Diodes and Rectifiers from 1/6

	£	s.	d.
2025 Mono/Stereo	8	19	6
3000 DM with 9TAHC	9	19	6
SP25 Mk II	11	19	6
AT60 Mk II	13	10	0
3500 Mono/Stereo 9TAHC	12	19	6
401	28	10	0
AP75	19	0	0
SL55	11	19	6
SL65	14	14	0
SL75	29	0	0
SL85	39	10	0
A70 Mk II	12	12	0

Send for illustrated brochures 16, 17 Complete range of accessories available

HI-FI equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE RD.

for all leading makes AMPLIFIERS TUNERS DECKS SPEAKERS MICROPHONES TEST EQUIPMENT SYSTEMS

ALL WITH DISCOUNTS
Ask for Hi-Fi-Stock List Leaflet 16.17
IT WILL PAY YOU TO PAY US A VISIT!

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10/- worth discount vouchers FREE WITH EVERY COPY

- * 32 pages of transistors and semi-conductor devices, valves and crystals.
- * 210 pages of components and equipment.
- * 70 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS
320 BIG PAGES

Send today 7/6 Post etc 2/

HENRY'S RADIO LTD

OPEN MON-SAT. 9 a.m.-6 p.m. THURS. 9 a.m.-1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963