

PRACTICAL

ELECTRONICS

FEBRUARY 1970

THREE SHILLINGS



**SOUND
OPERATED
SWITCH**

ADCOLA

PRODUCTS LIMITED
(Regd Trade Mark)

THE RELIABLE SOLDERING INSTRUMENT!



SEND COUPON FOR LATEST LEAFLET


ADCOLA PRODUCTS LTD
ADCOLA HOUSE
GAUDEN ROAD
LONDON SW4
01-622 0291/3

NAME

ADDRESS

PE170

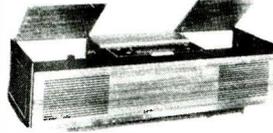STEREOGRAM CABINET £19
An elegant Stereogram Cabinet in modern Veneered Mahogany and cloth covered Front Panel
BLACK LEATHERETTE SIDE PANELS
Dimensions: 52" x 17½" x 12". Speaker positions for Twin 10" x 5" Speakers



SPEAKERS 6/6
2"—75Ω. 2½"—35Ω. P. & P. 2/6.
ACOS MICS. 35/- STANDARD
STICK MIC. 2gns. P. & P. 3/6.
ASSORTED CONDENSERS
10/- for 50. P. & P. 7/6.
ASSORTED RESISTORS
10/- for 50. P. & P. 4/6.
ASSORTED CONTROLS
10/- for 25. P. & P. 7/6.
TRANSISTORS
MULLARD MATCHED
OUTPUT KIT
9/- OC81D—2 OC81's.
P. & P. FREE.
FERRITE RODS 3/6
6", 8" x 3/8" complete with
LW/MW COILS. P. & P. FREE.

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E.12
Phone 01-478 6001-2-3
Stamp for Free List.

17in.—£11.10.0 Carr. 30/-
19in. SLIM-LINE
FERGUSON 24 gns.
TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS

FREE ILLUSTRATED
LIST OF TELEVISIONS
17"—19"—21"—23"



WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

RECORD PLAYER CABINET

49/6.
Cloth covered. Size 16½" x 14½" x 8"
Takes any modern autochanger.
P. & P. 7/6.

SINGLE PLAYER CABINETS

15/6. P. & P. 7/6.
TRANSISTOR CASES 19/6.
Cloth covered, many colours.
Size 9½" x 6½" x 3½". P. & P. 3/6.
Similar cases in plastic 7/6.


TWO-YEAR GUARANTEED
REGUNNED TUBES

70" & 90" 14in.—69/6, 17in.—
89/6, 21in.—99/6, 10" 17in.—
19in. & 21in.—99/6, 23" (not
bonded)—119/6. Exchanged
Bowls. Carr. 10/6.

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminated Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials 8W/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

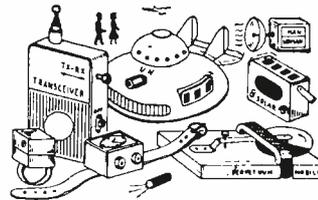

**EXPERIMENTER'S
PRINTED CIRCUIT KIT**

8/6

Po-tage & Pack. 1/6 (UK)

Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. (10) 3 Subminiature Radio Receivers based on the "Triplexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Sucking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.



YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

SINCLAIR IC

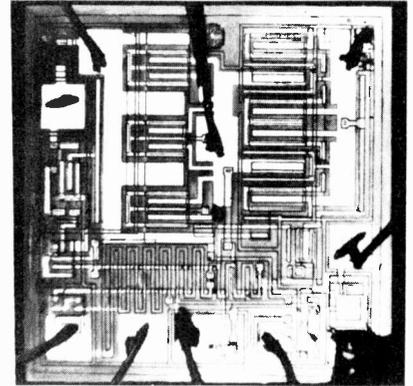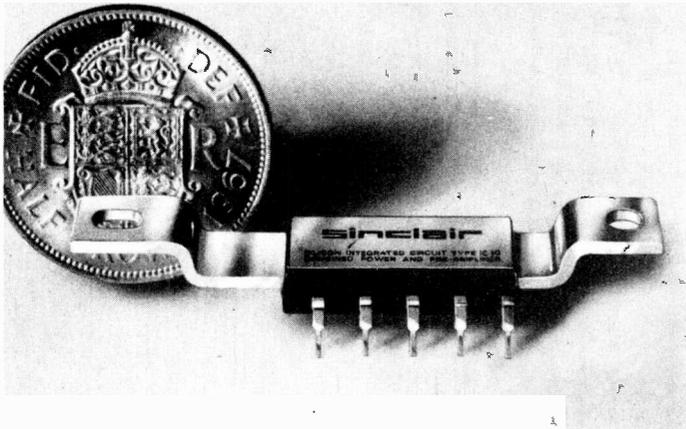MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMP



the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required for producing monolithic ICs are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. It also enables us to cover every IC-10 with the Sinclair guarantee of reliability.

■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz \pm 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.


SINCLAIR
IC.10 *with IC-10 manual* **59/6**

POST FREE

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD · CAMBRIDGE
Tel. 0223-52731

NEW

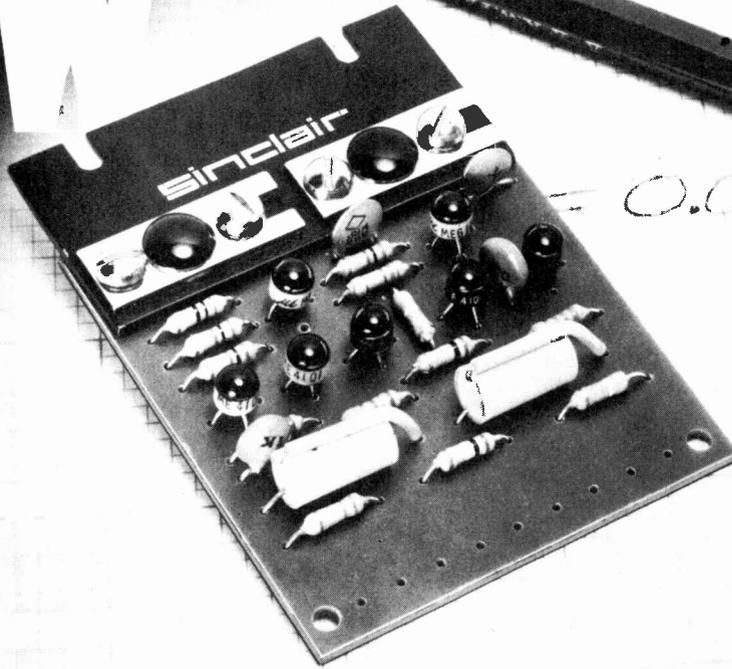

20 WATT
(40 WATT PEAK)

HIGH-FIDELITY
POWER AMPLIFIER


Z.30

THE WORLD'S LOWEST DISTORTION HIGH FIDELITY AMPLIFIER.

For four years, the Sinclair Z.12 dominated the constructor world, being the best selling unit of its kind this side of the Atlantic. Excellent as it was, the new Sinclair Z.30 is still better. Half the size of the Z.12, it has more than twice the power, very much greater gain and a level of distortion 50 times lower. This incredible figure results from using over 60dB of negative feed back with a constant current load to the driver stage obtained by incorporating a two transistor circuit in place of the more usual bootstrapping. 9 silicon epitaxial planar transistors are used to provide enormous power; up to 20 watts RMS sine wave (40 watts peak). The circuitry of this marvellous amplifier allows it to be operated from any voltage from 8 to 35 to perfection. At all output levels, distortion is only 0.02%. This puts true laboratory standards into the hands of every user of a Z.30. Two Z.30s and a new Stereo Sixty will make a stereo assembly of such perfection that it could not be bettered in its class no matter how much you spent. But the Z.30 has an enormous variety of applications, particularly where quality, precision and reliability are essential. It can also be used entirely on its own as an amplifier for an efficient economy record player.

APPLICATIONS

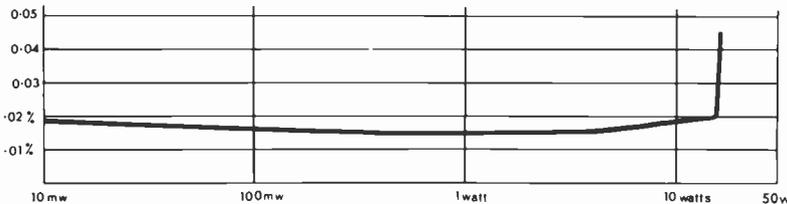Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work, etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



SPECIFICATIONS

Power output—15 watts R.M.S. into 8 ohms using a 35V supply; 20 watts R.M.S. into 3 ohms using a 30V supply.

Output—Class AB.

Frequency response—30 to 300,000 Hz \pm 1dB.

Distortion—0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.

Signal-to-noise ratio—better than 70dB unweighted.

Input sensitivity—250mV into 100k Ω .

Damping factor—> 500.

Loudspeaker impedances—3 to 15 ohms.

Power requirements—From 8 to 35V d.c. (The Z.30 will operate ideally from batteries if required.)

Size—3 $\frac{1}{2}$ x 2 $\frac{1}{4}$ x $\frac{1}{2}$ inches.


Built, tested and guaranteed, with circuits and instructions manual

89/6


sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET RD., CAMBRIDGE Tel: 0223 52731

NEW

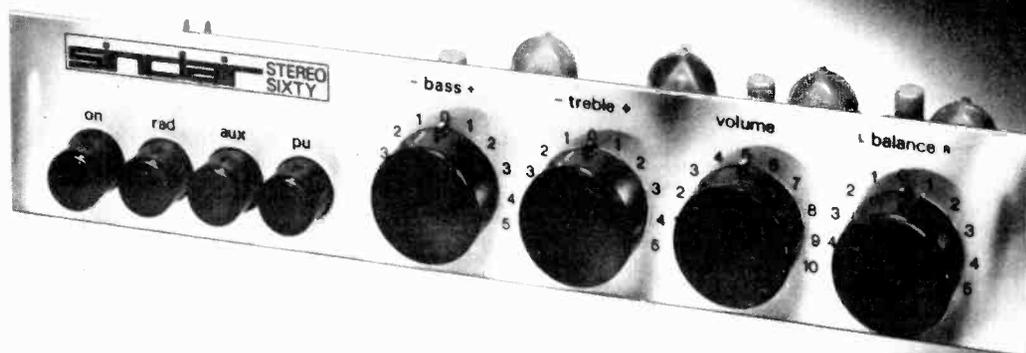

STEREO SIXTY PRE-AMP & TONE CONTROL UNIT

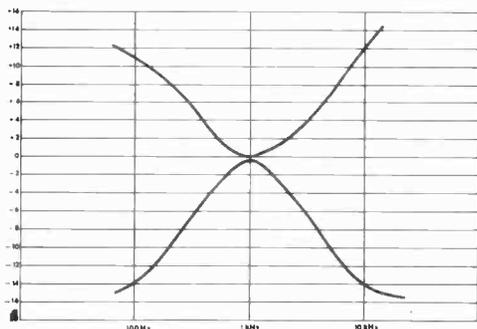

Curves to show bass and treble cut and boost

Ready built, tested and guaranteed with instructions

£9.19.6

This attractive and completely new unit is intended for use with two Z.30 amplifiers to provide the finest possible standards of stereo reproduction. Four press buttons and four rotary controls are used to provide on-off, three input selectors and Volume, Bass cut/boost, Treble cut/boost and Stereo balance. The on-off button also switches the power amplifiers. The front panel in brushed aluminium is flush mounted to the cabinet front, it being necessary only to drill holes to accommodate the controls. Rear adjustable brackets hold the chassis tight to the cabinet. The very latest ganged rotary controls are used to afford compactness and extra long working life free from noise.

The Stereo-60 may also be used with 2 IC-10's or any other high performance amplifiers.

SPECIFICATIONS

- Input sensitivities—Radio—up to 3mV Magnetic Pickup—3mV: correct to R.I.A.A. curve ± 1 dB; 20 to 25,000 Hz. Ceramic Pickup—up to 3mV: Auxiliary—up to 3mV.
- Output—250mV
- Signal-to-noise ratio—better than 70dB.

- Channel matching—within 1dB.
- Tone Controls—TREBLE —15 to +15dB at 10 KHz: BASS —15 to +15dB at 100 Hz.
- Power consumption 5mA.
- Front panel—brushed aluminium with black knobs and controls.
- Size 8 $\frac{1}{2}$ × 1 $\frac{1}{2}$ × 4 inches.

PZ.5 POWER SUPPLY UNIT

A new heavy duty mains power supply unit designed specially to drive two Z.30s and a Stereo Sixty. New compact design.

For AC Mains, 110-240V.

£4.19.6

USE THIS COUPON FOR Z.30, STEREO 60 AND P.Z.5.

Q.16 LOUDSPEAKER AND MICROMATIC ON NEXT PAGE

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
Please send

NAME

ADDRESS

For which I enclose cash/cheque money order


PE.270

sinclair

SINCLAIR

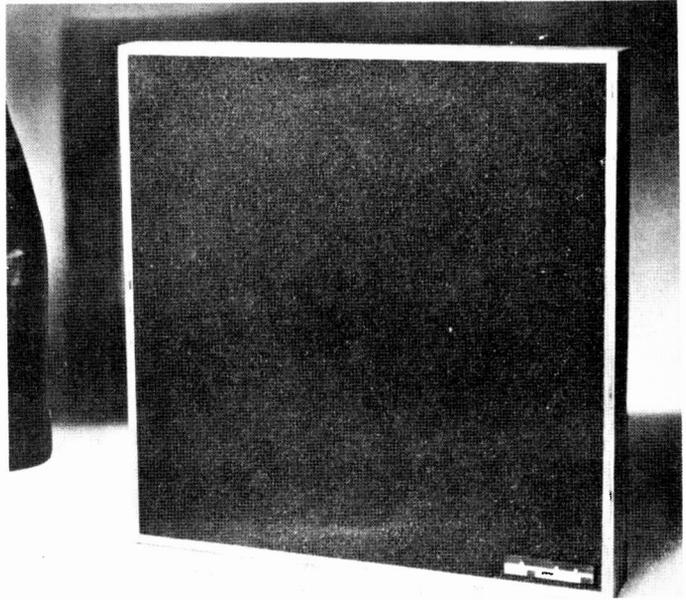Q.16

new elegance in an outstanding loudspeaker



All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design, the new Q.16 presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give.

The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000 Hz. with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: 9 $\frac{3}{4}$ " square \times 4 $\frac{1}{2}$ " deep from front to back.

£8.19.6
POST FREE

SINCLAIR MICROMATIC The world's most successful miniature radio



Specifications

Size: 1 $\frac{1}{2}$ " \times 1 $\frac{1}{2}$ " \times $\frac{1}{4}$ " (46 \times 33 \times 13mm).
Weight incl. batteries: 1 oz. (28.35gm) approx.
Tuning: Medium wave band with bandspread at higher frequency end.
Earpiece: Magnetic type.
Case: Black plastic with anodized aluminium front panel, spun aluminium dial.

Complete kit incl. earpiece, case, solder and instructions in fitted pack.

49/6

Inc. P/Tax

Ready built, tested and guaranteed, with earpiece.

59/6

Inc. P/Tax

Mallory Mercury Cell RM675 (2 required) each 2/9d.

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wristwatch, and dependable under the severest listening conditions.

SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

USE THIS COUPON FOR MICROMATIC AND Q.16 ORDERS

To: **SINCLAIR RADIONICS LIMITED, 22 NEWMARKET ROAD, CAMBRIDGE**
 Please send _____

 For which I enclose cash/cheque/money order. _____
 PE.270

NAME _____
 ADDRESS _____

sinclair
 SINCLAIR RADIONICS LIMITED
 22 NEWMARKET ROAD
 CAMBRIDGE Tel. 0223 52731

REDUCED IN PRICE

TRANSFORMERS

10-0-200-220-240
15-0-15 at 200mA
Shrouded. Flying leads colour
coded 12/6d each
0-200-220-240
0-24 at 0.5 amp-
48V at 50mA 7/6 each

RELAYS

S.T.C. Miniature Type 24
2p/c/o 8-24V D.C. 10/- each
S.T.C. Miniature Type 25
4/p/c/o 10-19V D.C. 10/- each

SEMI-CONDUCTORS

BF115 Mullard Transistor
4/- each

BFY52 Mullard Transistor

5/- each
1/6 each

OA70 Diodes

CAPACITORS

1,000pF Mullard. Poly. 6d each

SWITCHES

7-way Pushbutton Units
2/p/c/o per unit 7/6 each

ALSO IN STOCK

Relay Bases, Knobs, Resistors,
Capacitors, Pots, Plugs, Sockets,
etc., etc.

All components NEW

C.W.O. and add 3/- for P. & P.
Send for free catalogue

W.E.C. Ltd. (FE)

74 THE STREET, ASHTEAD, SURREY

ATB

SPRAGUE

Sprague low cost ATB features all welded connections, ultra low leakage, and stable life under severe conditions. 100 up Prices.

250 μ F	@	12v	10d
50 μ F	@	50v	7½d
10 μ F	@	100v	7½d
1000 μ F	@	6v	1¼d
500 μ F	@	15v	1¼d

More data from:

WEL Components Ltd

Dept. B, 5 Loverock Road, Reading, Berks. Tel.: Reading 500616-9 Telex 84529

Ministry of Technology approved distributor



AMAZING MINI-DRILL

FOR PRECISION
**MODEL
WORK**



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6 p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money Ref. Guarantee.

MERLIN SUPPLY CO.

Dept. PE 2D, Nailsea, Bristol BS19 2LP

Kinver for Components

LINEAR INTEGRATED CIRCUITS FOR ALL YOUR REQUIREMENTS

Sinclair Type IC-10 59/8 net.
Plessey SL403A 3W Audio Amplifier 49/6
G.E. Type PA230 Low Level Amplifier 21/-
G.E. Type PA234 1W Audio Amplifier 23/-
G.E. Type PA237 2W Audio Amplifier 34/-
G.E. Type PA246 5W Audio Amplifier 57/-
RCA Type CA3000 D.C. Amplifier 54/9
RCA Type CA3011 Wide Band Amplifier 20/-
RCA Type CA3020 1W Wide Band Amplifier 32/-
RCA Type CA3028A Differential Cascode Amp (120MHz) 20/-
RCA Type CA3029 Operational Amplifier 55/2
RCA Type CA3035 Ultra High Gain Amplifier 30/-
Mullard Type TAA263 A.F. Amplifier 15/9
Mullard Type TAA293 General Purpose Amplifier 21/8
Mullard Type TAA310 Record/Playback Pre-Amplifier 32/-
Mullard Type TAA320 MOS L.F. Amplifier 13/5
G.E. Type 2N5306 Darlingtion Pair 11/6
G.E. Type DI3T1 Programmable Unijunction Transistor 10/8

Add 1/- each to the above i.c.s. for data sheets if required. Data sheets may be purchased separately at 1/8 each, post free. Issued free with SL403A and IC-10 (Data not available separately for IC-10).

1 Watt Amplifier Module type PCM 1

This amplifier unit is a printed circuit module incorporating the popular and well tried PA234 i.c. amplifier. The unit is a COMPLETE AUDIO AMPLIFIER and requires no external components, you simply connect an 18V power supply and a 15 or 16 ohm speaker or headphone, even the supply smoothing capacitor and the output capacitor are included! The overall dimensions, including capacitors, are 2½in x 3in x 1½in. The input for 1W output at 1kHz is typically 300mV into 100kohms. This unit is available at only 38/- net, complete with descriptive leaflet or 70/- net per pair.

TRANSISTORS

ACY17	8/8	BC212L	3/9	OC26	9/-	2N1308	9/8
ACY18	4/5	BC213L	3/9	OC28	9/-	2N1309	9/8
ACY19	5/3	BC214L	4/-	OC35	9/-	2N2905	13/-
ACY20	4/6	BCY70	5/4	OC36	9/-	2N2924	4/4
ACY21	4/1	BCY71	10/4	OC71	3/-	2N2928	8/3
ACY22	2/10	BCY72	4/6	OC72	3/9	2N2928	3/-
ACY39	18/-	BD121	18/-	OC75	3/9	2N3053	6/8
ACY40	3/5	BF184	7/8	OC81D	3/-	2N3055	19/6
ACY41	4/4	BF194	7/-	OC170	3/9	2N3702	3/8
ACY44	6/2	BFY50	5/-	OC171	3/9	2N3703	3/3
ASY26	8/-	BFY71	4/6	2N696	4/9	2N3704	3/9
ASY27	8/-	BFY92	5/-	2N997	5/-	2N3705	3/4
ASY28	6/2	BSY95A	3/11	2N706	3/3	2N3707	4/-
ASY29	8/-	MJ481	27/3	2N1132	10/9	2N3708	2/5
BC107	3/3	MJ491	32/11	2N1302	3/11	2N3819	9/-
BC108	3/-	TIP31A	17/-	2N1303	3/11	2N3820	18/9
BC109	3/3	TIP32A	23/-	2N1304	5/-	2N3826	5/11
BC182L	3/2	T1844	1/9	2N1305	5/-	2N4058	4/8
BC183L	2/5	T1849	2/8	2N1306	6/5	2N4059	5/5
BC184L	3/2	T1850	3/9	2N1307	6/5	40408	14/11

2N2160 Unijunction 14/11

DIODES

AA119	3/-	OA91	1/3	1N82A	9/8	18134	5/3
AA111	2/6	OA202	2/-	1N87A	4/8	18940	1/2-
AAZ15	3/3	1N34A	4/-	1N914	2/-		
BAY38	3/9	1N60	4/-	1844	1/8		
OA47	2/-	1N64	4/-	18131	3/-		

VEROBOARD

2½in x 5in	0-1	0-15
2½in x 3½in	4/9	4/9
3½in x 3½in	4/2	3/5
3½in x 5in	5/6	5/6
3½in x 3½in	4/9	3/11
17in x 2½in		10/6
17in x 3½in		14/8

PLAIN VEROBOARD

(Uncoppered)
(0-15 in Matrix only)

2½in x 5in	3/8
2½in x 3½in	3/-
17in x 2½in	7/6
17in x 3½in	9/8
17in x 5in	14/8
Cutter	7/3
Pin Insertion Tool (0-1)	9/6
Pin Insertion Tool (0-15)	9/6
Packet of 36 pins (0-1)	3/11
Packet of 36 pins (0-15)	3/11

EDGE CONNECTORS FOR USE WITH VEROBOARD

16 way, 0-15in pitch	4/6
24 way, 0-15in pitch	6/9
24 way, 0-10in pitch	6/9
36 way, 0-10in pitch	8/7

INTERNATIONAL RECTIFIER HANDBOOKS

HB10 Rectifier Engineering Handbook	18/9
HB20 Zener Diode Handbook	18/9
HB30 Solar Cell and Photocell Handbook	18/9
HB40 SCR Handbook	20/-

PHOTOCELLS

1R CS-120	18/8
Mullard Type ORP12	9/-

ZENER DIODES

182030 Series (400mW 3-3V to 15V)	4/8
Z1100-C Series (1W 3-9V to 27V)	7/11

CARBON VOLUME CONTROLS (POTENTIOMETERS)

Linear or log function type are available in the following values 5k, 10k, 25k, 100k, 250k, 500k, 1M, 2M. Available in the following types: Single Pots 3/- each. Single Pots with DP switch 5/3 each. Ganged pots 8/6 each. Standard Skeleton pots, linear, horizontal or vertical mounting, available in the following values: 100, 220, 470, 1k, 2.2k to 47M. 1/- each.

COMPONENTS CATALOGUE 2/- post free (Inland) P. & P. 1/6 inland-overseas at cost (min. 10/-).

Cash with order please, discounts may be deducted as follows: order over £5, 10%, order over £10, 15%, excluding net items. Trade orders - net 30 days. Please send S.A.E. with enquiries, CALLERS WELCOME. Open 9.00 a.m.-12.50 p.m. 2.00 p.m.-5.00 p.m. Weekdays and Saturday Mornings 9.00 a.m.-12.50 p.m.

Kinver

STONE LANE KINVER
STOURBRIDGE WORCS
Telephone KINVER 2099

Complete stereo system — £29.10.0

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION— Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2½" tweeter. Teak finish 12" x 6½" x 5½", 4 guineas each. 7/6d. p. & p.
Type 2 as type 1. Size 17½" x 10½" x 6½". Incorporating 10½" x 6½" bass unit and 2½" tweeter. 3 ohms impedance 5½ guineas plus 15/- p. & p. 7/6d. p. & p.
 Garrard Changers from £7.19.6d. p. & p. 7/6d.
 Cover and Teak finish Plinth £4.15.0d. 7/6d. p. & p.

Duetto Integrated Transistor Stereo Amplifier **£9.10.0**
 plus 7/6d. p. & p.


The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION— R.M.S. power output: 3 watts per channel into 10 ohms speakers.
INPUT SENSITIVITY: Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.
CONTROLS: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.
STONE CONTROL: Treble lift and cut. Separate on/off switch. A pre- balance control.



These 5 items can be purchased together for £29.10 + £1.10 P. & P.

The Classic

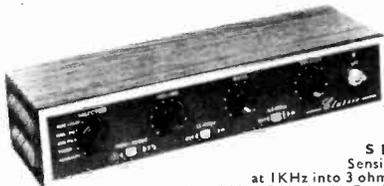

Teak finished case
£9
 Plus P. & P. 7/6

SPECIFICATION: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 3mV (at 3½ i.p.s.) Mag. P.U.: 2 mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output: 100mV. Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 13dB at 60Hz. Treble: ±14dB at 15KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½in long, 4½in deep, 2½in high. Built and tested.



The Viscount
 INTEGRATED HIGH FIDELITY TRANSISTOR STEREO AMPLIFIER
£14.5.0
 Plus P. & P. 7/6

SPECIFICATION: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monoral). Input: 6-position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner, Tape and Tape Rec. out. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency Response: 40Hz-20KHz ±2dB. Tone Controls: Separate bass and treble controls. Treble 13dB lift and cut [at 15KHz]. Bass: 15dB lift and 25dB cut [at 60Hz]. Volume Controls: Separate for each channel. A.C. Mains Input: 200-240V, 50-60Hz. Size: 12½ x 6in x 2½in teak-finished case. Built and tested. P. & P. 7/6.
Viscount Mark II for use with magnetic pick ups specification as above. Fully equalised for magnetic pick ups. Suitable for cartridges with minimum outputs of 4mV/cm/sec. at 1kc. Input Impedance 47k. 15 gns. plus 7/6 P. & P.



THE RELIANT Mk. II
 SOLID STATE GENERAL PURPOSE AMPLIFIER
£6.16.0 Plus P. & P. 7/6
 In teak finished case

SPECIFICATION: Output: 10 watts into a 3 ohms speaker.
 Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV) individual bass and treble control.
 Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ x 4½ x 2½in. Mike to suit (crystal): 12/6 plus 1/6 P. & P. 8 x 5in speaker 14/6 plus 3/- P. & P. Mk. I £5.15.0 plus 7/6 P. & P. Less teak finished case.

SPECIAL OFFER

Complete stereo systems comprising BALFOUR 4 speed auto player with stereo head, 2 DUO speaker systems size 12 x 6 x 5½in. Plinth (less cover) and the DUETTO stereo amplifier. All above items
£20 Plus P. & P. 20/-

NEW COMPLETE HI-FI STEREO SYSTEM **£39**

Comprising SP 25 Garrard Mk. II with diamond stereo cartridge, Viscount amplifier Mk. I, Two type 2 speakers, Plinth and cover. £39 plus £2 P. & P.

THE ELEGANT SEVEN Mk. III (350mW Output)



7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for fool-proof construction. **MAINS POWER PACK KIT**: 9/6 extra.

Price £49.6 Plus P. & P. 7/6.
 Circuit 2/6. Free with parts.

THE DORSET (600mW Output)




7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.
MAINS POWER PACK KIT: 9/6 extra.

Price £5.5.0 Plus P. & P. 7/6.
 Circuit 2/6. Free with parts.

QUALITY MAINS TRANSFORMER

Input 250V OUTPUT (All RMS values) 4 windings of 11-5V connected in series total 46V at 4.5 amps (conservatively rated). The following combinations may be used. 1. 23—0—23V; 2. 46V. Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- Plus P. & P. 7/6

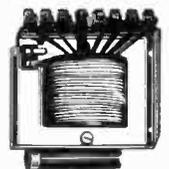

Also see opposite page





EXTRACTOR FAN

AC mains 230/250V, complete with pull switch. Size 6" x 6" x 4 in.

Price 27/6 Plus 7/6 P. & P.

X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp). Total Distortion at 1KHz, at 5 watts 0.35%, at rated output 1.5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V d.c. at 800mA (6-24V may be used).

Price 69/6 Plus 2/6 P. & P.


Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.

2. Treble: PRICE 5/-.

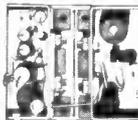3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.



Power Supplies for the X101:

P101 M (for mono) 35/- plus

4/6 P. & P.

P101 S (for stereo) 42/6 plus 4/6 P. & P.


CAR TRANSISTOR IGNITION SYSTEM

(by famous manufacturer)

For 6V or 12V positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.).

Price £4.19.6 (Post and Packing 5/- extra)

50 WATT AMPLIFIER A.C. Mains 200-250V

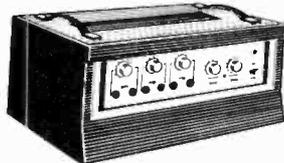

Price £28.10.0

Plus 20/- P. & P.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS
3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITY AND INPUT IMPEDANCES:

Channels 1 & 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 & 4 300 mV at 1m. Suitable for most high output instruments (gram, tuner, organ etc.). Input sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60 Hz/s. Bass Cut -13dB at 60 Hz/s. Treble Boost +11dB at 15 KHz/s. Treble Cut -12dB at 15KHz/s. With bass and treble controls central -3dB points are 30Hz/s and 20 KHz/s. POWER OUTPUT. For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz/s. Total distortion at 20 watts 0.15% at 1KHz/s. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEED BACK 20dB at 1KHz/s. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES. Adjustable from 200-250V. A.C. 50-60Hz/s. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.

THREE-IN-ONE HI-FI 10 WATT SPEAKER


A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20kc/s. Size 13½ x 8½ x 4½ inches. By famous manufacturer.

List Price £7. Our Price 74/6 Plus 5/- P. & P.

Similar speaker to the above without tweeters in 3 and 15 ohms 44/6 plus 5/- P. & P.

LIVINGSTONE LAB

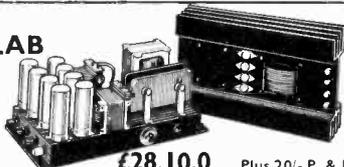50 watt RMS Base Transistor Amplifier. This amplifier is designed and manufactured by L.L. using the best quality components, thus making it extremely reliable and almost indestructible. Size (Power supply) 16 x 9½ x 6½ in. (Amplifier) 14½ x 9 x 4 in; sensitivity for rated output 1V.



£28.10.0

Plus 20/- P. & P.


TERMS C.W.O.

All enquiries

S.A.E.

RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7in to 10in or 12in. Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play.

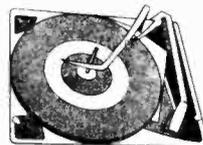

Only £5.19.6 Post and insurance 7/6 extra.


STEREO PRE-AMPLIFIER

Inputs—6 position rotary switch (3 position mono, 3 position stereo). Tuner 150 mV into 680k. Magnetic pick-up fully equalised and suitable for magnetic cartridges with minimising output of 4mV/cm/sec. Load 47k. Ceramic pick-up 150 mV into 680k. Sensitivities taken for 200mV output. Controls—separate volume controls for each channel. Twin ganged bass, 12dB lift and 15dB cut at 60c/s. Twin ganged treble, 10dB lift and 15dB cut at 10kc/s. Voltage required 23-30V D.C. at 5mA. Size 12½ x 3½ x 2½". In teak finished case, complete with front panel and knobs. Built and tested.

Price £7.7.0 Plus 5/- P. & P.

PYE CAR-RADIO PUSH BUTTON TUNING HEART

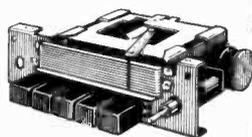This PRESTOLOCK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6½ x 4 x 2in. As illustrated but without knobs.



25/- Plus 3/- P. & P.

POCKET MULTI-METER



Size 3½ x 2½ x 1½ in. Meter size 2½ x 1½ in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods. battery and full instructions.

Price 42/6 Plus 3/6 P. & P.

FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

GARRARD TAPE MOTORS

Fast forward and fast re-wind motors, as used by famous manufacturer. Size 3 x 2½ x 2½ in. Spindle 5/16 in. A.C. Mains 250V.



39/6 per pair Plus 7/6 P. & P.

ADVANCE CONSTANT VOLTAGE TRANSFORMER



Output 7.5V at 1 amp and 30V at 100MA. Mains input 125V (2 can be used in series for 250V).

Price 22/6 Plus 7/6 P. & P.

40W FLUORESCENT LIGHT KIT



Incorporating GEC Choke size 8½ x 1½ x 1½ in, 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. 11/6

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½ x 1½ x 1½ in, 2 bi-pin holders, start and starter holder. P. & P. 6/6. 17/6

B.S.R. TD2 TAPE DECK

This tape deck takes 5½ in spools complete with two-track heads. Size 13½ in long by 8½ in wide.

Price £8.19.6 Plus P. & P. 7/6.

RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED

RADIO & TV COMPONENTS (ACTON) LTD.

21d High Street, Acton, London, W.3

Also at 323 Edgware Road, London, W.2

ALL ORDERS BY POST TO OUR ACTON ADDRESS

QUALITY COMPONENTS AND EQUIPMENT

NEW RANGES FOR THE AMATEUR AND PROFESSIONAL USER



* QUALITY PANEL METERS

3B Series. Face size 42 x 42mm (1 1/2 x 1 1/2 in). 50µA, 37.6; 100µA, 35; 200µA, 32.6; 500µA, 27.6; 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 25; each, 10V, 20V, 50V, 100V, 200V and 500V, 25; each, 1A and 5A, 25; each, "5" meter, 1mA, 29.6; VU meter, 37.6; 6S Series. Face size 86 x 78mm (3 1/2 x 3 in). 50µA, 62.6; 100µA, 52.6; 200µA, 47.6; 500µA, 37.6; each, "5" meter, 1mA, 42.6. Other ranges and sizes available. List on request with full details.



* 50,000 OHMS PER VOLT MULTIMETER

Recommended quality instrument with mirror scale and overload protection. 0/10/33/12/60/120/300/600/1200V d.c. (50KΩ/V), 0/3/30/120/300/600/1200V a.c. (10KΩ/V); 0/30/150/60/300mA, 0/12A; resistance 0/10KΩ/1/1/10/100MΩ. Meter movement 30µA. Polarity reversing switch. Complete with batteries, leads and instructions.




* SINE/SQUARE WAVE AUDIO GENERATOR



Provides audio output on 4 bands. Sine wave 20c/s to 20Kc/s; output up to 7V square wave 60c/s to 30Kc/s; 7V p-p. Distortion under 1%. Output impedance 1kΩ. Variable output amplitude control. Supplied with leads and instructions. A.C. mains operated.

TE22 Price £16.10.0.

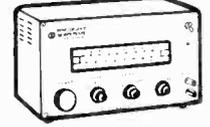* DELUXE SINE-SQUARE WAVE RC AUDIO GENERATOR



Weinbridge RC Audio oscillator featuring four overlapping scales covering 18c/s to 200 Kc/s. Output waveforms are sine, square and complex. Mirrored tuning control. Output 5 volts RMS or 10 volts P-P. Sine wave response ±3dB. Distortion under 1% at 1Kc/s. Stability ±1%. Accuracy ±2% 0/7 impedance under 30kΩms. Variable Attenuator. Mains operated. With Handbook.

ORC 27A Price £28.10 0pp/10c



* VACUUM TUBE VOLTMETER

Features low price for such an instrument. Large 6in full view scale meter. 28 ranges. D.C. volts: 0/1/5/15/50/150/500/1500 A.C. volts: 0/1/5/15/50/150/500/1500 r.m.s.; 0/1/4/14/40/140/400/1400/4000 p.p. Resistance: R x 10-100-1k-10k-100k-1M-10M. Range 0.2 ohm to 1000MΩ.

MODEL TE65 £17.10.0 p.p. 7/6 HV Probe 50/1 R.F. Probe 42/6



* 20,000 OHMS PER VOLT MULTIMETER

Popular model but with extra scale range, 20,000 ohms per volt. 0/5/25/50/250/500/2500V d.c. 0/10/50/100/500/1000V a.c. 0/50µA, 0/21/250mA. Resistance 0-6kΩ and 6MΩ. Also dB scales or capacitance.


Model 200H 77/6 pp2/- (Leather case, Price 15/- pp.2/-)



* PORTABLE OSCILLOSCOPE

Features 3in clear view tube, easy to use controls and good stability. Y amp. Sensitivity, 1V p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω. 25 PF. X amp sensitivity, 9V p-p/CM. Bandwidth 1.5 cps-800 KHz. Input imp. 2 meg Ω. 20 PF. Time base, 5 ranges 10 cps-300 KHz. Synchronisation, internal/external. Illuminated scale, 140 x 215 x 330 MM. Weight 15 lbs. 220/240V. A.C. Supplied brand new with handbook.

TO3 Price £35 p.p. 10/-

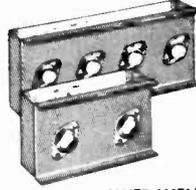

* TRANSISTOR POWER AMPLIFIERS

12 watt 3 ohm 100mV Input 24 volt supply. Model MPA 12/3 £4.10 p.p. 3/-
12 watt 12-16 ohm 100mV Input 40 volts supply. Model MPA 12/15 £5.5 p.p. 13/-
25 watt 8-16 ohm 180mV Input 50/60 volt supply. Model MPA 25 £7.10 p.p. 4/6
Power Supplies 24-40 volt 90/ p.p. 3/6
50-60 volt 97/6 p.p. 4/6
Model PAT 7 watt Amplifier 3 ohms O.P. 7mV Input, operates 12-18 volts D.C. Price 72/6 p.p. 2/6

* 100 WATT AMPLIFIER—details on request.

* GRID DIP METER

All transistor grid dip meter, absorption wavemeter and osc. detector. Frequency range 440kc/s to 280Mkc/s in 6 coils. Uses 3 transistors plus diode with 500µA meter. Internal battery.



TE15 Price £11.10.0 pp.3/6

* DC STABILISED POWER SUPPLY



Switched DC Stabilised Outputs UP TO 1AMP. 3.6-9 & 12 VOLTS. Indicator lamp for each voltage. Fully fused mains operated. Negligible ripple. Regulation 1%.

SE101A Price £8 15 0



* FIELD STRENGTH METER

5 Ranges 1-250 mc/s. Fitted 200µA meter. Earphone output. Calibrated tuning scales.

FL30HA Price 72/6 pp.2/- Also non-calibrated type peaking F/6 meter. FS1 Price 45/- pp.2/6

* TRANSISTORISED INTERCOMMS



Bellphone £4.10.0
2-station, £3.10.0; 3-station, £5.15.0;
4-station, £6.12.6 (2-station uses no wires) mains operated, £11.19.6.
Telephone amplifier, 59/6. p & p. 3/6

* SIGNAL INJECTOR



New model for checking all audio and RF up to VHF. Simple to use. Battery operated. Output approx. 1kΩ/s. 1-4V pp. Harmonics up to VHF.

SE250B Price 35/- p.p. 1/6

* MATCHING SIGNAL TRACER

SE500 Price 27/6 p.p. 1/6

Suppliers of quality components and equipment for over 25 years

AUDIO - HIGH FIDELITY

Complete range in stock to suit all Hi-Fi and Public Address requirements.

COMPONENTS


UK's largest supplier of components. EVERYTHING YOU NEED



* TRANSISTOR CHECKER

Complete capacity for checking all transistors npn and pnp for alpha, beta and German. Also diodes complete with leads and instructions. ZQM-2. Price £5.19.6, p.p. 3/6.

EXPERIMENTER'S MODULE

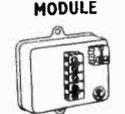

Terrific offer of brand new STC time delay electronic units. Adjustable 3-15 recs. 9-12V operated. Supplied complete with suggested uses circuits. STC Module Price 35/-.

9 VOLT 100 mA STABILISED SUPPLY

Size 3" x 2" x 1 1/2". Fused ready to use. U.K. made Transistorised. PRICE 45/- p.p. 2/6.

Transistors in stock for Industrial Price List.

Write for Industrial Price List. Includes all Types of Semiconductor Device.

PORTABLE GEIGER COUNTERS



FOR MEASUREMENT OF RADIO-ACTIVITY. Supplied complete with instructions, haversack, cables and probe. List price £70. OUR PRICE, NEW, TESTED COMPLETE WITH BATTERIES £7.10.0 POST 10/- SPARE BATTERIES 15/- PAIR POST 5/-

DOSIMETER POCKET-TYPE 0-50r/12/6



NOMBREX TRANSISTORISED Test Equipment

MODEL	£	s.	d.	No.
25a RF Gen.	21	0	0	35
28x Xtal RF Gen.	29	10	0	35
30 Audio Generator	19	10	0	24
31 R.F. Generator	12	10	0	26
32 C.R. Bridge	10	10	0	28
33 Inductance Bridge	20	0	0	29

STEREO HEADPHONES

Featuring soft Padded Headsets, wide frequency response. Adjustable Headbands. Fitted Jack plugs.



DHO 2/5 Recommended 20C/S-15KC/S ... £3.19.6
SE2B Built in Tweeters and Volume Controls ... £9.19.6
KOSS, KO727 £16.10.0. PRO-4A ... £23.0.0

CALL FOR DEMONSTRATION

Mono Switched 8/16 ohms and 4K ohms, Price £4.4.0

Stereo Headphone Amplifiers

Inputs for PU/Tuner, Battery Model Mains Operated High Quality

Eagle HA10 ... £8.19.6
Shure 5A2/E ... £18.18.0

GRAVINER FIRE DETECTOR UNIT

The Detector Unit consists essentially of a highly sensitive 931A photo-electric cell combined with a firing circuit. Incorporates a single cold cathode electronic relay, capacitors and resistors designed to fail to safety if external wiring is open or short circuited. Encapsulated in a resin which fully insulates the unit electrically and provides a high degree of mechanical and thermal shockproofing. Original price £74. OUR PRICE, BRAND NEW £38 each, with data sheet.



* SWR ALIGNMENT METER

Ideal for all transmitter alignment. Built-in field strength meter 100µA. Complete. Ready to use. SWR 1:1 to 1:3. SWR3 ... Price 69/6 p.p. 2/6



WELLER SOLDERING IRONS

8200 Gun & Iron ... 59/6
8200D PK Gun Kit ... 79/6
ANTEX CMI Iron ... 39/6
ANTEX Iron Kit ... 42/6

* MULTIMETER

Return of a popular model, 2000 ohms/V, 0/10/50/500/1000V a.c./d.c. 0/50µA, 0/10/250µA d.c. 0/10/100/1/10/100 resistance, dB and capacitance scales. Size 5in x 3 1/2in x 1 1/2in. Robust and easy to use. Complete with leads, batteries and instructions. THL 33A 82/6 p.p. 2/6. Leather case Price 22/6



CATALOGUES - TWO NEW EDITIONS NOW AVAILABLE SEE BACK COVER FOR DETAILS

Did you know we stock 1,000 Transistors and Devices? Ask for Latest FREE List (No. 36)

HENRY'S RADIO LTD.
303 & 309 Edgware Rd, London W2

'303' Components/Equipment/Organ Parts also
MAIL ORDER DEPT. 01-723-1008/9
'309' Test Gear/High Fidelity etc. 01-723 6963

ALL MAIL ORDERS TO '303'
SHOP HOURS 9 a.m. - 6 p.m. THURSDAY 1 p.m.
OPEN ALL DAY SATURDAY.

Brand New Fully Guaranteed TRANSISTORS & DEVICES


1N4001	2/-	2N3711	3/6	AF118	12/6	BSY66	5/-	OA95	1/6
1N4002	2/3	2N3730	10/-	AF124	6/-	BSY67	5/-	OA200	1/9
1N4003	2/6	2N3731	25/6	AF125	6/-	BSY95A	4/6	OA202	2/-
1N4004	3/6	2N3819	8/-	AF126	4/-	BSY95	4/-	OA210	9/6
1N4005	3/6	2N3820	19/6	AF127	4/-	HTY42	18/6	OA211	9/6
1N4006	4/-	2N3823	17/6	AF139	6/-	HTY79/400R	6/-	OA220	11/-
1N4007	5/-	2N4058	5/6	AF178	9/6		35/-	OA2201	10/-
1N4009	1/6	2N4061	4/-	AF181	8/6	BTY84	12/6	OA2202	8/6
1N4148	1/9	2N4286	3/-	AF186	9/6	BTY88	15/6	OA2203	8/6
1N4785	10/-	2N4288	8/-	AF239	8/6	BUY10	12/6	OA2204	8/6
2C210	12/6	2N4289	3/6	AFY19	22/6	BUY11	18/6	OA2205	8/6
2C240	49/6	2N4290	3/-	AFZ11	8/-	BY100	3/6	OA2207	9/6
2G301	4/-	2N4291	3/-	AFZ12	10/-	BY103	3/6	OA2207	9/6
2G302	4/6	2N4292	3/-	ASY26	6/6	BY114	5/-	OA2208	6/6
2G303	5/-	40361	12/-	ASY27	7/6	BY126	5/-	OA2209	6/6
2G306	7/6	40362	13/6	ASY28	6/6	BYX22/600	6/6	OA2210	6/6
2G308	7/6	28001	10/-	ASY29	6/6		5/3	OA2211	6/6
2G309	6/6	28002	10/6	ASY36	6/-	BYZ10	10/-	OA2212	6/6
2G339A	3/-	28003	9/6	ASY50	3/6	BYZ11	9/-	OA2222	6/6
2G371	4/6	28004	9/6	ASY51	8/-	BYZ12	8/-	OA2223	7/6
2G374	5/6	28005	15/-	ASY67	9/6	BYZ13	5/-	OA2224	7/6
2G381	5/-	28012	25/-	ASY83	5/-	BYZ15	20/-	OA2225	7/6
2G382	6/-	28012A	22/6	ASY86	6/6	BYZ16	12/6	OA2228	7/6
2G378A	4/6	28013	20/-	ASZ21	8/6	BZY88C3V3	4/-	OA2229	9/6
2G383	5/-	28013A	20/-	AU10	19/6	BZY88C4V7	4/-	OA2231	9/6
2C304	4/6	28014	15/-	AU101	30/-	BZY88C5V1	4/-	OA2232	7/6
2C305	5/-	28018	17/6	AM101	30/-	BZY88C5V1	4/-	OA2242	4/6
2N404	4/6	28020	50/-	B3M	19/6	BZY88C5V1	4/-	OA2244	4/6
2N456	15/-	28024	50/-	BA110	5/-	BZY88C6V8	4/-	OA2245	4/6
2N458	20/-	28025	60/-	BAY31	2/-	BZY88C7V5	4/-	OA2246	4/6
2N503	9/6	28026	100/-	BC107	3/-	BZY88C7V5	4/-	OA2247	4/6
2N599	12/6	28034	12/6	BC108	2/9	BZY88C8V2	4/-	OA2252	7/6
2N601	3/6	28036	10/6	BC109	3/-	BZY88C9V1	4/-	OC16	10/-
2N696	4/6	28102	10/-	BC113	6/6	BZY883V9	4/-	OC19	7/6
2N697	5/-	28103	12/6	BC116	8/-	BZY886V2	4/-	OC20	19/6
2N698	8/6	28104	12/6	BC118	7/6	BZY94C10	4/-	OC22	9/6
2N706	1/6	28131	7/6	BC134	7/6	BZY94C11	4/-	OC23	19/6
2N706A	2/6	28301	6/6	BC135	6/-	BZY94C12	4/-	OC24	12/6
2N707	12/6	28302	7/6	BC136	7/-	BZY94C13	4/-	OC25	7/6
2N708	3/6	28303	10/6	BC137	8/-	BZY94C13	4/-	OC26	5/6
2N711	7/6	28304	12/6	BC138	8/-	BZY94C14	4/-	OC28	12/6
2N711A	7/6	28305	15/-	BCY30	5/6	CP404	12/6	OC29	12/6
2N721	11/-	28320	9/-	BCY31	8/6	CR81/05	5/-	OC35	10/6
2N743	4/-	28321	6/-	BCY32	10/-	CR81/20	7/6	OC36	10/6
2N744	6/-	28322	7/6	BCY33	5/-	CR81/30	8/6	OC41	5/-
2N753	5/-	28323	10/6	BCY34	6/-	CR81/35	8/6	OC43	8/-
2N855	12/6	28324	7/6	BCY38	7/6	CR81/40	9/6	OC44	4/-
2N914	4/6	28501	8/6	BCY39	8/6	CR83/05	6/-	OC44M	4/-
2N916	4/6	28502	8/6	BCY40	10/-	CR83/10	6/-	OC45	3/6
2N918	7/6	28503	9/6	BCY42	5/-	CR83/20	7/6	OC45M	3/6
2N919	4/-	28512	9/6	BCY43	5/-	CR83/30	8/6	OC46	5/6
2N920	5/-	28701	8/6	BCY70	4/-	CR83/40	10/-	OC57	15/-
2N922	8/6	28702	11/-	BCZ11	7/6	CR83/025 AF	5/-	OC70	3/-
2N930	7/6	28724	50/-	BC147	3/6	CR825/025	5/-	OC71	3/-
2N1090	6/6	28731	8/6	BC148	2/9	CR825/025	15/-	OC72	5/-
2N1091	6/6	28732	8/6	BC149	4/-	DD006	3/9	OC73	6/6
2N1131	6/-	28733	9/6	BF152	6/-	DD058	6/6	OC74	6/6
2N1132	8/-	28743	50/-	BF182	6/6	DD190	12/6	OC75	5/-
2N829	4/6	28745A	30/-	BF194	3/6	DD226A	7/6	OC76	5/-
2N1303	4/6	AA129	4/-	BF195	3/-	DD262A	3/6	OC77	8/6
2N1304	5/-	AA178	8/6	BTY79/100R	15/-	DD281A	3/6	OC78	5/-
2N1305	5/-	AA178	8/6	BTY79/100R	15/-	DD3110	7/6	OC78D	2/6
2N1306	5/-	AA178	8/6	BTY79/100R	15/-	FST1/1	3/6	OC79	2/6
2N1307	5/-	AAZ12	4/-	BT102/800R	15/-	FST2/0	3/6	OC81	5/-
2N1308	6/-	AAZ13	2/6	BD119	12/6	FST2/1	3/6	OC81D	5/-
2N1309	5/-	AAZ17	2/6	BD124	12/6	FST3/0	3/6	OC81M	3/6
2N1420	18/6	AC126	5/-	BEN3000	5/-	FST3/8	6/-	OC81DM	3/6
2N1483	9/6	AC127	5/6	BF115	5/-	FST3/06 AF	3/-	OC82	5/-
2N1613	5/-	AC127Z	12/6	BF154	8/-	OC82D	6/-	OC83	5/-
2N2147	17/6	AC128	5/6	BF158	8/-	OC84	5/-	OC122	10/-
2N2160	15/-	AC154	3/-	BF159	12/-	OC123	10/6	OC139	5/-
2N2287	25/-	AC169	3/-	BF163	8/-	OC140	7/6	OC141	15/-
2N2297	9/6	AC153	4/-	BF167	5/-	OC169	5/-	OC170	5/-
2N2484	7/6	AC176	5/-	BF173	6/-	OC171	6/-	OC200	5/-
2N2646	10/6	AC187	5/-	BF180	7/6	OC207	15/-	OC201	9/6
2N2784	10/-	AC188	6/-	BF181	7/6	OC202	12/6	OC203	7/6
2N2900	6/6	AC192	5/6	BF190	5/-	OC204	8/-	OC205	12/6
2N2905	10/-	ACY18	4/-	BFN88	5/-	OC206	15/-	OC207	15/-
2N2925	4/-	ACY19	5/-	BFY17	6/-	OC208	19/6	OC208	19/6
2N2926	2/6	ACY20	4/-	BFY18	5/-	OC209	19/6	OC209	19/6
2N3011	7/6	ACY21	4/6	BFY19	5/-	OC210	19/6	OC210	19/6
2N3053	5/-	ACY22	3/6	BFY20	12/6	OC211	19/6	OC211	19/6
2N3054	12/6	ACY28	3/6	BFY50	5/-	OC212	19/6	OC212	19/6
2N3055	15/-	ACY34	4/-	BFY51	4/6	OC213	19/6	OC213	19/6
2N3133	6/-	ACY35	4/6	BFY62	5/-	OC214	19/6	OC214	19/6
2N3136	6/-	ACY39	9/6	BFY63	4/6	OC215	19/6	OC215	19/6
2N3142	7/6	ACY40	3/-	BFY64	8/6	OC216	19/6	OC216	19/6
2N3232	15/-	AD140	11/-	BLY10	20/-	OC217	19/6	OC217	19/6
2N3233	15/-	AD149	12/6	BLY11	22/6	OC218	19/6	OC218	19/6
2N3236	30/-	AD161	7/6	BPY10	19/6	OC219	19/6	OC219	19/6
2N3228	10/-	ADY32	7/6	BSN20	4/-	OC220	19/6	OC220	19/6
2N3238	9/6	ADY40	10/6	BSN21	5/-	OC221	19/6	OC221	19/6
2N3702	3/6	ADZ11	24/6	BSN76	4/-	OC222	19/6	OC222	19/6
2N3703	3/6	ADZ12	29/6	BSY27	4/-	OC223	19/6	OC223	19/6
2N3704	4/-	AEY11	10/-	BSY28	5/-	OC224	19/6	OC224	19/6
2N3705	3/6	AEY12	12/6	BSY29	5/-	OC225	19/6	OC225	19/6
2N3707	4/-	AF102	16/-	BSY50	5/-	OC226	19/6	OC226	19/6
2N3708	3/6	AF103	6/6	BSY51	5/-	OC227	19/6	OC227	19/6
2N3710	3/6	AF115	6/6	BSY53	5/-	OC228	19/6	OC228	19/6
2N3135	6/-	AF116	6/6	BSY54	5/-	OC229	19/6	OC229	19/6
2N3794	2/6	AF117	5/6	BSY65	5/-	OC230	19/6	OC230	19/6

Send for Free Copy of 1970
Transistor List (36) Today!
DISCOUNTS: 10% on 6-
16% on 12+ any one type.
QUANTITY PRICES: 100+
Phone: 01-723 0401. Ex. 3.
Post/Packing, please add 2/6 on
your order.

INTEGRATED CIRCUITS			
RP1010	29/6	PA230	22/6
CA3014	29/6	PA234	20/-
CA3018	22/6	PA237	37/6
CA3020	29/6	PA424	59/6
CA3028A	23/6	PA436	79/6
CA3036	18/6	PA246	52/6
IC10	59/6	MC1304	55/-
TA0100	45/-	TAA263	15/-
SL4003	49/6	UL900	10/-
UL900	10/-	UL910	10/-
UL910	10/-	UL914	12/6

HENRY'S RADIO

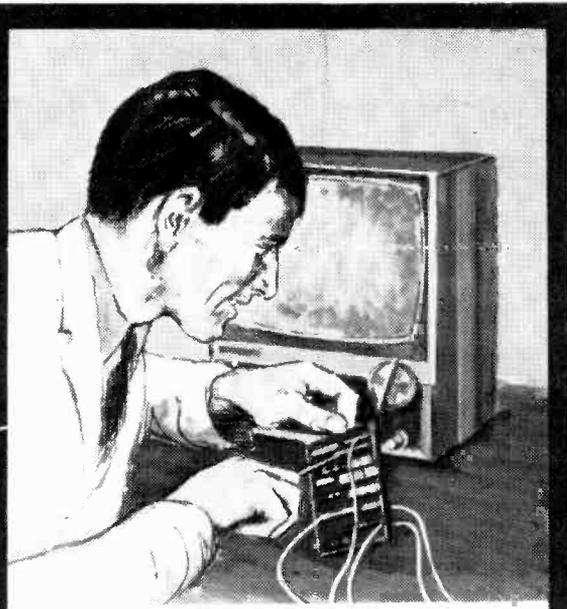303 EDGWARE ROAD
LONDON, W.2
(01) 723 1008/9
OPEN MON-SAT 9am-6pm THURS 9am-1pm



Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma Course which gives a thorough fundamental training for radio and television engineers, starts on 15th April.


The Course includes theoretical and practical instruction on Colour Television receivers and is recognised by the Radio Trades Examination Board for the Radio and Television Servicing Certificate examinations. College Diplomas are awarded to successful students.

The way to get ahead in this fast growing industry — an industry that gives you many far-reaching opportunities — is to enrol now with the world famous Pembridge College. Minimum entrance requirements: 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

To: The Pembridge College of Electronics (Dept. PE.2), 34a Hereford Rd., London, W.2
Please send, without obligation, details of the Full-time Course in Radio and Television.

NAME _____
ADDRESS _____


CAR LIGHT FLASHERS

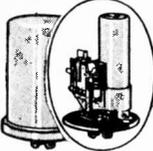

Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset.) Housed in strong plastic case. Flashing rate between 60-120 per minute. 12 volt DC operation. Maximum load 6 amps. Size 2 1/16" dia. x 4". Supplied brand new at a fraction of original cost. 6/9 each. P. & P. 2/6. (3 for 17/6. P. & P. 4/8.)

R209 MK II COMMUNICATION RECEIVER

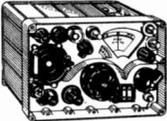11 valve high grade communication receiver suitable for tropical use. 1.20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, BFO. Aerial trimmer, internal speaker and 12 V d.c. internal power supply. Supplied in excellent condition, fully tested and checked. £15 Carr. 20/-.



TYPE 13A DOUBLE BEAM OSCILLOSCOPES




An excellent general purpose D/B oscilloscope. T.B. 2 c/s-750 kc/s. Bandwidth 5-5 Mc/s. Sensitivity 93 mV/cm. Operating voltage 0/100/200/250 V a.c. Supplied in excellent working condition. £22.10.0 or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.



MARCONI CT44/TF956 AF ABSORPTION WATTMETER
1 μwatt to 6 watts. £20. Carr. 20/-.

GEARED MAINS MOTORS

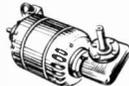

Paralux type 8D19 230/250V a.c. Reversible. 30 RPM. 40 lb in. Complete with capacitor. Excellent condition. 99/6. Carr. 10/-.

CLASS D WAVEMETERS




A crystal controlled heterodyne frequency meter covering 1-7.3 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. £5.19.6. Carr. 7/6, or brand new with accessories. £7.19.6. Carr. 7/6.

CLASS D WAVEMETERS No. 2


Crystal controlled. 1.2-19 Mc/s. Mains or 12V d.c. operation. Complete with calibration charts. Excellent condition. £12.10.0. Carr. 30/-.

TO-2 PORTABLE OSCILLOSCOPE

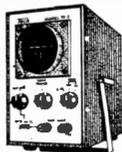A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 C/s-1 MHz. Input imp. 2 meg Ω. 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 230/240 V a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-.



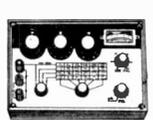TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω. 6 Ranges ±1%. L. 1 μH - 1 l HENRYS. C. 10pF ±11.1 nF d. 6 Ranges ±2%. TURNS RATIO 1.1/1000-1.1/100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 5/-.


UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built-in speaker and phone jack. Metal cabinet. Operation 230/240V. a.c. Supplied brand new, guaranteed with instructions. Carr. 7/6


13 gns.



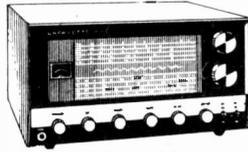TRIO JR-310 NEW AMATEUR BAND 10-80 METRE RECEIVER. In stock. £77.10.0.



LAFAYETTE SOLID STATE HAGOO RECEIVER
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 kc/s-400 kc/s and 550 kc/s-30 Mc/s FET front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 meter • 24in Bandsread • 230V a.c./12V d.c. neg. earth operation • EF gain control. Size 15in x 9 1/2in x 8 1/2in. Weight 18lb. EXCEPTIONAL VALUE. £45. Carr. 10/- S.A.E. for full details.

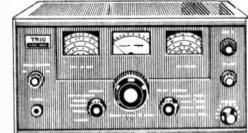

TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550Kc/s to 30Mc/s. continuous and electrical bandsread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 8SB-CW • ANL • Variable BFO • 8 meter • Sep. bandsread dial • 1F 445Kc/s • Audio output 1.5W. • Variable RF and AF gain controls. 115/250V A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42 Carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES** Normally £5.19.6. OUR PRICE £3.15.0 if purchased with above receiver.

TRIO JR-500SE 10-80 Metre AMATEUR RECEIVER £69.10.0

TRIO TS 510 AMATEUR TRANSCEIVER with speaker and mains P.S.U. £212

LAFAYETTE HA.800 SOLID STATE AMATEUR COMMUNICATION RECEIVER SIX BANDS 3.5-4, 7-7.3, 14-14.35, 21-45, 28-29.7, 50-54 Mc/s.

Dual conversion on all bands. 2 x 445 Kc/s mechanical filters. Product detector. Variable B.F.O. 100 Kc/s crystal calibrator. 8 meter. Huge slide rule dial. Operation 230V A.C. or 12V D.C. Size 15" x 9 1/2" x 8 1/2". Complete with instruction manual. £57.10.0. Carr. paid. (100 Kc/s Crystal 39/6 extra)




RCA COMMUNICATION RECEIVER AR88D

Latest release by ministry BRAND NEW in original cases. 110-250V a.c. operation. Frequency in 6 Bands. 635Kc/s-32Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £87.10.0. Carr. £2.


LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

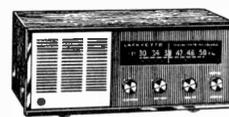A completely new transistorised receiver covering 132-174 Mc/s. Fully tuneable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 D. aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-.



TELETON MODEL CR 10T AM/FM STEREO TUNER AMPLIFIER

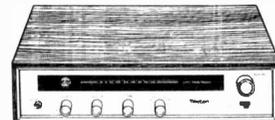A new model from Teleton. 31 solid state devices. 4+4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600 KHz FM 88-108 MHz. Automatic FM stereo reception. Stereo indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size: 13 1/2" x 3 1/2" x 9 1/2" approx. Price £34. Carr. 7/6.



CLEAR PLASTIC PANEL METERS




First grade quality Moving Coil panel meters. Type MR 38P. 1 1/2" square fronts.
500-0-500μA 27/6 50mA 27/6 150V. D.C. 27/6
1mA 27/6 100mA 27/6 300V. D.C. 27/6
1.0-10mA 27/6 150mA 27/6 500V. D.C. 27/6
2mA 27/6 200mA 27/6 750V. D.C. 27/6
5mA 27/6 300mA 27/6 15V. A.C. 27/6
10mA 27/6 500mA 27/6 50V. A.C. 27/6
750mA 27/6 3V. D.C. 27/6 150V. A.C. 27/6
1 amp 27/6 10V. D.C. 27/6 300V. A.C. 27/6
2 amp 27/6 20V. D.C. 27/6 500V. A.C. 27/6
5 amp 27/6 100V. D.C. 27/6 8 meter Im. 42/-
200μA 35/- 100V. D.C. 27/6 VU meter. 32/-
500μA 40/- Full range of other sizes in stock. Bend a.s.e. for leaflet.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, lin. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, 14/6. P. & P. 1/6.
50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, 21/-. P. & P. 1/6.
100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms, 27/6. P. & P. 1/6.

CRYSTAL CALIBRATORS No. 10

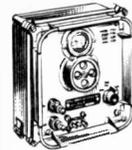

Small portable crystal controlled wavemeter. Size 7 1/2" x 4 1/2". Frequency range 500 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. 89/6. Carr. 7/6.

AVO 48A. Perfect order with set of shunts and resistances. £12.10.0. P. & P. 7/6.

T.E.40 HIGH SENSITIVITY A.C. VOLTMETER



10 meg. input 10 ranges: .01 / .003 / .1 / .3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s-1.2Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.10.0. Carr. 5/-.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500 Ω or 5K Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0. Carr. 10/-.

TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-. Additional Probes available: R.F. 35/-. H.V. 42/6.

COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.c. coupled. Band width 1kc/s. Perfect order. £25. Carr. 30/-.

AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 20-80Mc/s. AM C.W./F.M. Incorporates precision dial level meter. precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £25. Carr. 20/-.

PLESSEY SL 403A 3 watt Integrated Amplifier Circuit 49/6 POST PAID

EDDYSTONE VHF RECEIVERS MODEL 770R. 19-165 Mc/s. Excellent condition. £150.



TE-16A Transistorised Signal Generator. 5 ranges 400 KHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2 x 6 1/2 x 3 1/2. Complete with instructions and leads. £7.19.6. P. & P. 4/-.

FIELD TELEPHONES TYPE L Generator ringing, metal cases. Operates from two 1.5V. batteries (not supplied). Excellent condition. £4.10.0 per pair. Carr. 10/-.

SOLARTRON GD. 711S.2 OSCILLOSCOPES Double beam. D.C. to 9 Mc/s. Perfect order. £65. Carr. 50/-.

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.
150 W. £22.6. P. & P. 3/6
300 W. £219.6. P. & P. 4/6
500 W. £410.0. P. & P. 6/6
1,000 W. £810.0. P. & P. 7/6
1,500 W. £719.6. P. & P. 8/6
7,500 W. £1510.0. P. & P. 20/-

G. W. SMITH & CO (RADIO) LTD.
Also see oppos. page

ARF-100 COMBINED AF-RF SIGNAL GENERATOR



A.F. SINE WAVE 20-200,000 c/s. Square wave 20-30,000 c/s. O.P. HIGH IMP. 21V. P/P6000 3-8 V. P/P. TF 100 kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240 V a.c. £30.0.0. Carr. 7/6.

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120kc/s to 500Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal socket for calibration. 220/240V a.c. Size 140 x 215 x 170mm. Brand new with instructions. £15 Carr. 7/6.


TY75 AUDIO SIGNAL GENERATOR



Sine Wave 20c/s to 200kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts a.c. Size 210 x 150 x 120mm. Brand new with instructions. £16 Carr. 7/6.

MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. £20. Carr. 16/-.
LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER

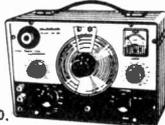2pF-2,000 mfd 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation. 200/250V a.c. Brand New £17.10.0. Carr. 7/6.



ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. **VM.76 VALVEMETER R.F.** measurements in excess of 100Mc/s and d.c. measurements up to 100V with accuracy of ±2% d.c. range 300 MV to 1kV a.c. range 300MV to 300V R.M.S. Resistance 0.02-500M Ω. Price £72.

VM.79 UHF MILLIVOLT METER. Transistorised. A.c. range 10MV-3V. D.c. current range 0.01µA-0.3mA. Resistance 1 ohm-10 megohms. Price £125.

H1B AUDIO SIGNAL GENERATOR. 15c/s-50kc/s. sine or square wave. Price £30.

J1B AUDIO SIGNAL GENERATOR. 15c/s-50kc/s. Price £30.

TT1S TRANSISTOR TESTER. £37.10.0. Carriage 10/- per item.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9967. B: 5-200. Ico: 0-50 microamps 0-5 mA. Resistance for diode 200 Ω-1M Ω. Supplied complete with instructions, battery and lead. £5.19.6. P. & P. 2/6.



TELLI DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0-1dB 10) + (1dB 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz (-3dB). Accuracy: 0-0.5dB. + indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.




SOLARTRON MONITOR OSCILLOSCOPE TYPE 101

An extremely high quality oscilloscope with time base of 10µsec to 20µsec. Internal Y amplifier. Separate mains power supply 200/250V. Supplied in excellent condition with cables, probe, etc., as received from Ministry. £8.19.6. Carr. 30/-.

Latest Catalogue

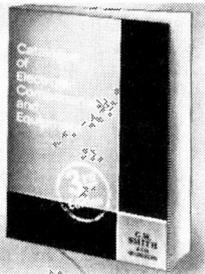The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT... Nearly 200 pages, fully illustrated and detailing thousands of items - many at bargain prices. FREE DISCOUNT COUPONS. VALUE 10/-.



SEND NOW-ONLY 7/6 P&P!

GARRARD

FULL CURRENT RANGE OFFERED, BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS

- *1025 Mono £6.19.6 SP25 MKII £11.19.6
- *1025 Stereo £8.19.6 *SL55 £11.19.6
- *2025 Stereo £7.19.6 A70 MKII £11.19.6
- *2025T/C £8.17.6 *SL55 £14.14.0
- *3000 Stereo £9.19.6 AP75 £17.17.0
- 401 £28. 7.6
- SL75 £28.10.0



Carriage/insurance 7/6 extra any model. WB4 Bases £3.19.6. Perspex covers £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carr. 5/- Full range of Garrard accessories available.

LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



19 transistors, 8 diodes, 11W music power, 30W at 8 Ω. Response 30-20,000 ± 2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16 Ω. Separate L and R volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/4 x 9 1/16 x 7 1/31/16in. Operation 115/230V. A.C. £28. Carriage 7/6.


MULTIMETERS for EVERY purpose!




TE-51. NEW 20,000 Ω VOLT MULTIMETER with overload protection and mirror scale. 0/6/30/120/1,200V a.c. 0/3/30/60/300/600/3,000V d.c. 0-60µA/12/300mA d.c. 0/60K/6 meg. ohm. £2/6. P. & P. 2/6.



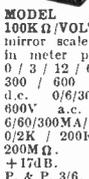TE-900 20,000 Ω VOLT GIANT MULTIMETER. 5in. full view meter. 2 colour scale, overload protection. 0/2.5/10/250/1,000/5,000V a.c. 0/2.5/12.5/10/50/250/1,000/5,000V d.c. 0/50µA/110/100/500mA 10A d.c. 20K/200K/20M Ω. £15. P. & P. 5/-.



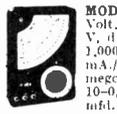
MODEL AS-100D. 100K Ω/VOLT. 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V a.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300mA/12 Amp. 0/2K/200K/2M/200M Ω. -20 to +17dB. £12.10.0. P. & P. 3/6.




MODEL TE-10A. 20K Ω/Volt. 5/25/50/250/500/2,500V. d.c. 10/50/100/500/1,000V. a.c. 0/50µA/2.5mA/250mA. d.c. 0/6K/6 megohms. -20 to +22dB. 10-0, 100 mfd. 1 0 0 100-0-1 mfd. 69/6. P. & P. 2/6.



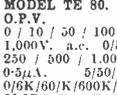MODEL TE-90 50,000 O.P.V. MIRROR SCALE OVERLOAD PROTECTION 0/3/12/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V d.c. 0-0.3/6/60/600mA d.c. 16K Ω/160K Ω/1.6/16M Ω. -20 to +63dB. £7.10.0. P. & P. 3/-.



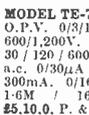MODEL TE 80. 20,000 O.P.V. 0/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V d.c. 0-3µA. 5/30/500mA/0/6K/60K/600K/6 Meg. £4.17.6. P. & P. 3/-.




MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V. d.c. 0/6/30/120/600/1,200V. a.c. 0/30µA/3/30/300mA. 0/16K/160K/1.6M/16megohm. £5.10.0. P. & P. 3/-.



MODEL TEL2. 20,000 O.P.V. 0/0.6/30/120/600/1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60µA/6/60/600mA. 0/1K/100K/1meg. 50P. 2 MFD. £5.19.6. P. & P. 3/6.



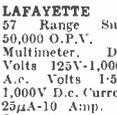MODEL PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA d.c. 0/100K Ω 39/6. P. & P. 1/6.



LAFAYETTE 57 Range Super 50,000 O.P.V. Multimeter. D.c. Volts 125V/1,000V. A.c. Volts 13V/1,000V D.c. Current 25µA-10 Amp. Ohms. 0-15 Meg Ω dB. -20 to +81dB. Overload Protection. £12.10.0. Carr. 3/6.

★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6 x 4 x 2 1/2in. 3 T.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM



Operative over amazingly long distances. Separate call, and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.9.6. P. & P. 3/6.



SINCLAIR EQUIPMENT Z30 20 watt amplifier, 99/6 PZ5 Power Supply Unit 99/6 PZ6 Power Supply Unit £7.19.6 Stereo 60 Preamp., £9.19.6 Q18 Speakers, £8.19.6 Micromatic Radio Kit, 49/6. Built 59/6

NEW IN STOCK IC/10 59/6 ALL POST PAID SPECIAL OFFER

Two Z30 Amps., PZ5 Power Supply, Stereo 60 Preamplifier, £22.

NEW SINCLAIR 2000 SYSTEM

35 watt Integrated Amplifier £29. Carr. 5/- Self powered P.M. Tuner. £25. Carr. 5/-.

PEAK SOUND PRODUCTS

Full range of Amplifiers, Kits, Speakers in stock.

ECHO HS-606 STEREO HEADPHONES



Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

HOSIDEN DH04S 2-WAY STEREO HEADSETS



Each headset contains a 2 1/2in woofer and a 2 1/2in tweeter. Built in individual level controls. 8 Ω imp. 25-18,000c/s. with cable and stereo plug. £5.19.6. P. & P. 2/6.

RECORDING HEADS

COSMOCORD 1-track heads. High imp. record/playback 65/- Low imp. erase 20/- **MARRIOTT** 1-track heads. High imp. record/playback 65/- Low imp. erase 20/- Post extra.

RACAL MA.168 TRANSISTORISED DIVERSITY SWITCH. Brand New Condition £15. Carr. 10/-.

AMERICAN TAPE

First grade quality American tapes. Brand new - Discount on quantities.

3in. 225ft. L.P. acetate	3/6
3 1/2in. 600ft. L.P. mylar	10/-
5in. 600ft. std. plastic	12/6
5in. 900ft. L.P. acetate	10/-
5in. 1,200ft. D.P. mylar	15/-
5 1/2in. 1,200ft. L.P. acetate	12/6
5 1/2in. 1,200ft. L.P. mylar	18/-
5 1/2in. 1,800ft. D.P. mylar	22/6
5 1/2in. 2,400ft. L.P. mylar	39/6
7in. 1,200ft. std. acetate	12/6
7in. 1,800ft. L.P. acetate	15/-
7in. 1,800ft. L.P. mylar	20/-
7in. 2,400ft. D.P. mylar	25/-
7in. 3,600ft. T.P. mylar	45/-


Postage 2/- Over £3 post paid.

MAXELL TAPE CASSETTES

C60. 10/3; C90. 14/3; C120. 19/6. Post extra.

G.W.SMITH & CO. (RADIO) LTD

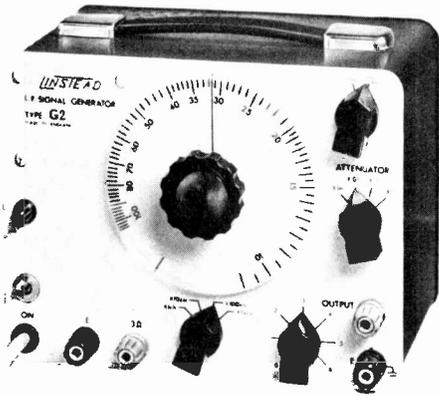All Mail Orders to - 147, Church Street, London, W.2 Tel: 01-262 6562 (Trade supplied)
3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)



Above Left


G.2. L.F. Signal Generator £26
 Frequency range 10 Hz—100 kHz
 Sine and Square Wave. Step
 Attenuator
 Total scale length approx. 40"

Above Right

M1 Voltmeter £26
 15 A.C. ranges 1mV to 500v
 3 D.C. ranges 0 to 400v
 Range increased by using
 A1 Amplifier which is powered by
 its own batteries

Linstead Electronics
 Roslyn Works, Roslyn Road, London, N.15
 Telephone 01-802 5144

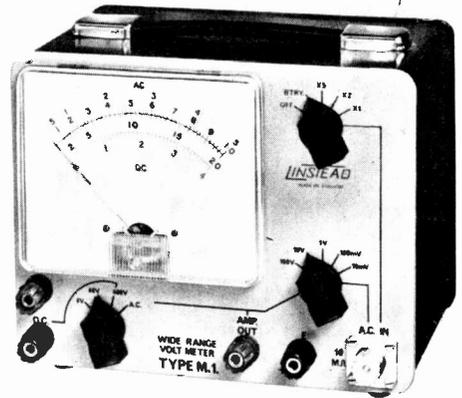
These
 Instruments
 were never
 meant for
 you...



Unless, of course, you are in science education. These instruments were designed and manufactured for education only with the in-built high quality that is necessary. Sales have been so successful that we have moved to a new factory and increased our production so that all users of signal generators and voltmeters can benefit. Illustrated leaflets available on request.

Linstead

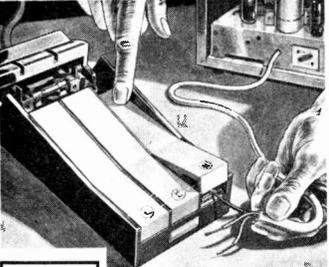MAINS Keynector
 A REVOLUTIONARY NEW PRODUCT
cuts out plugs




SAFEST & QUICKEST WAY TO CONNECT ELECTRICAL EQUIPMENT TO THE MAINS

No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. The Keynector casing is in two-tone plastic and measures 5 x 3 x 1 1/2 in. Please send for further information.

E.B. INSTRUMENTS
 DIVISION OF ELECTRONIC BROKERS LTD.
 49-53 PANCRAS ROAD, LONDON, N.W.1
 Telephone 01-837 7781

4-STATION INTERCOM

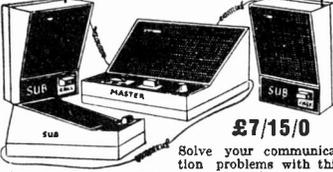

£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £10.10.6. P. & P. 8/6 extra.

INTERCOM/BABY ALARM



3 Gns.

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor TELEPHONE AMPLIFIER




59/6

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/3)
 189 KENSINGTON HIGH STREET, LONDON, W.8

DIMMASWITCH

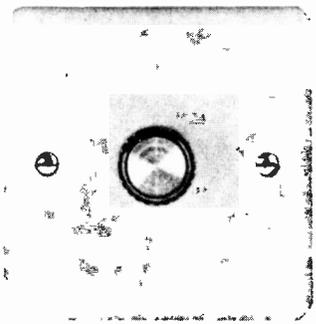


This is an attractive dimmer unit which fits in place of the normal wall light switch. The mounting plate is ivory to match modern fittings and the control knob is in bright chrome. An ON/OFF switch is incorporated to control up to 500 watts at mains voltages from 200-250 volts, 50 Hz.

These are normally sold at £4 19s. 6d.—our price is £3 5s. We also offer at £2 15s. a complete kit of parts with simple instructions enabling you to build this dimmer yourself.

The circuit uses the latest miniature RCA triac and new diac triggering device to give complete reliability. Radio interference suppression is included.

DEXTER & COMPANY
 ULVER HOUSE, 19 KING STREET
 CHESTER CHI 2AH
 Chester 25883

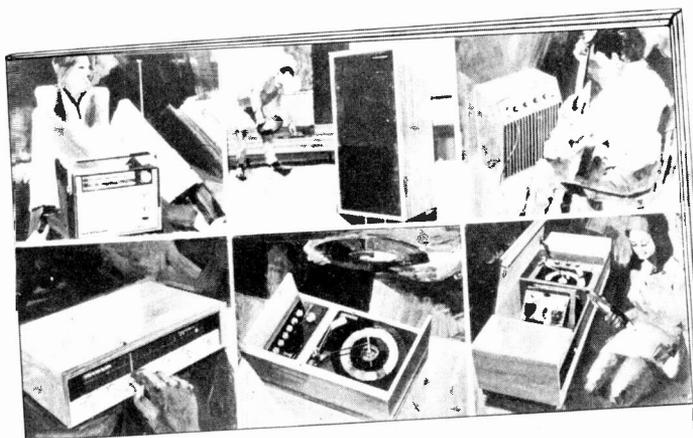
There's Something for Everyone in the NEW HEATHKIT CATALOGUE!



Look what's
new from

30^{NEW}
MODELS

HEATHKIT

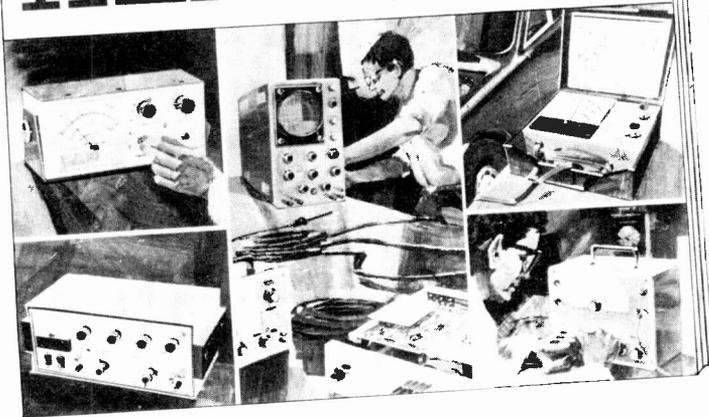

- GUITAR PRACTICE AMPLIFIER
- ELECTRONIC METRONOME
- AMBASSADOR SPEAKERS
- AUTO-TUNE-UP METER
- AIRCRAFT MONITOR RECEIVER
- CAR RADIO
- TECHNICIANS LOW-COST 'VVM'
- SEVERN AM/FM RADIO
- FABULOUS STEREO HI-FI COMPACTS
- STEREO RECORD PLAYER
- D.I.Y. SPEAKER SETS
- GENERATORS
- POWER SUPPLIES
- D.I.Y. RADIOGRAM PACK
- MANY OTHER MODELS TOO NUMEROUS TO MENTION

Leisure time takes on a new sparkle, a new interest when you add the creative fun you get from building a Heathkit model. Get the thrill of personal achievement when you switch on and realise that you've done something you doubted you could ever do. Your first step is FREE! just simply send for the latest Heathkit catalogue and see what a wide choice of models we offer. What ever your requirement, be it Hi-Fi, Audio, a Portable Radio, a Record Player, Amateur Radio, a SW Receiver, a Test Instrument or Educational Equipment . . . There is something for everyone. And we are adding to our wide range continuously.



DAYSTROM LIMITED
Gloucester GL2 6EE England
Tel.: Glos. 29451 Telex 43216

To: DAYSTROM LTD., GLOUCESTER
Please send me my free copy of the
1970 HEATHKIT CATALOGUE

NAME _____
ADDRESS _____
25/28

Lasky's

LASKY'S EXCLUSIVE TMK METER KITS

These two meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position; the Model 200 also has the range selector in position. The highest quality in components and 1% tolerance resistors are used throughout. Both offer professional standards of accuracy. Supplied complete with full constructional, circuit and operating instructions.

MODEL 200 20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3" x 2in meter. Full scale accuracy: DCV and current: $\pm 2\%$, ACV: $\pm 3\%$, resistance $\pm 3\%$. Special 0-6V DC range for transistor circuit measurements.

SPECIFICATION
 ● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV. ● ACV: 0-6-30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-60-600mA. ● Resistance: 0-10K-100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale). ● Capacitance: 0-002-0.2uf (AC 6V range). ● Decibels -20 to +63dB. ● Output: 0.05uf blocking capacitor. Uses two 1.5V (1.7 type) batteries. Black bakelite cabinet—size 5 1/2" x 3 1/2" x 1 1/2". Complete with test leads.



LASKY'S PRICE 85/- Post 3/6

MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is clearly indicated on the actual meter face. High speed rotary range selection knob; also features polarity reversal switch, shielded meter movement with overload protection circuit; Special uA and mA measurement ranges.

SPECIFICATION DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0-25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-0-25-125-500V at 5K/OPV. DCuA: 0-25uA at 125mA; 0-50uA at 250mA. DCmA: 0-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV. DC Amps: 0-5A at 125mV; 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0.1uF, 400V) in series with ACV ranges. Decibels: -20 to +81.5db. Operates on two 1.5V batteries. Black bakelite cabinet, size 5 1/2" x 6 1/2" x 2 1/2". Complete with test leads.




ALSO AVAILABLE READY BUILT AND TESTED £12.10.0. Post 5/-

**LASKY'S PRICE
£10.10.0** Post 5/-

Garrard

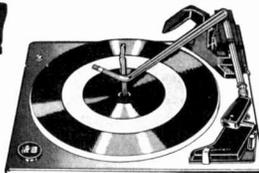SL.55
4-speed autochanger
with stereo cartridge



**LASKY'S PRICE
£11.19.6** Post 5/-
Complete with AD76K MAGNETIC CARTRIDGE £16.9.6

AUTOCHANGERS

1025 less cartridge .. 26 9 6
 1025 with GCM21 mono cartridge (Stereo Compat) .. 26 19 6
 2025TC with 9TA stereo diamond cartridge .. 26 17 6
 SL65B less cartridge .. 215 19 6
 AT60 Mk. II less cartridge .. 213 5 0
 SL75 less cartridge .. 228 10 0
 SL95 less cartridge .. 235 0 0
 A70 Mk. II less cartridge .. 213 19 6
 B.S.R. UA-47 less cartridge .. 25 9 6

Postage on all above 6/- extra


SINGLE PLAYERS

AP75 with AD76K magnetic cartridge .. 221 0 0
 AP75 less cartridge .. 218 10 0
 SP.25 Mk. II less cartridge .. 211 19 6
 SRP22 Mains model less cartridge .. 26 12 10
 SRP22 Battery model less cartridge .. 27 15 3
 TRANSCRIPTION DECK 401 228 10 0
GARRARD BASES:
 WB1 £2.8.11; WB4 Mk. II £5.8.11;
 WB5 £5.8.11.
CLEARVIEW PERSPEX COVERS:
 SPC1 £3.5.0 SPC4 Mk. II £4.6.6.

GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL
 16 colour pages in large 16x11in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test equipment, Components, etc., etc.
 Send 1/- for post only and inclusion on our regular mailing list. (5/- overseas)

DENSHI BOARD KITS EXPERIMENTAL AND EDUCATIONAL CIRCUIT SYSTEM

The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few minutes' study. DENSHI BOARD KITS come complete with an 80 page manual of circuits and data. Manuals are available separate at *4/6 post 6d. *Refundable if you purchase kit.

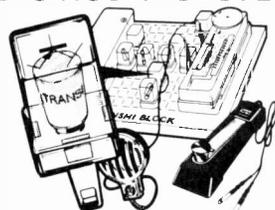

THESE ARE JUST A FEW OF THE CIRCUITS YOU CAN BUILD IN MINUTES: VARIOUS RADIO RECEIVERS, AMPLIFIERS, MORSE CODE PRACTICE DEVICE, CONTINUITY TESTER, SIGNAL INJECTOR, SIGNAL TRACER, WIRELESS MICROPHONE, ETC., ETC.

DENSHI BOARD KIT SR-1A comprises:

Base board; tuner block; 4 resistors; choke coil; transformer; 2SA transistor for RF; 2 diodes; 3 capacitors; battery block; Morse key; antenna lead; crystal earphone; various bridge and connecting pieces. This kit permits the building of 16 basic circuits.

LASKY'S PRICE £4.19.6 Post 3/6


DENSHI KIT SR-2A as SR-1A with these additional parts:

2SB transistor for AF; 2 resistors; 1 capacitor; crystal microphone; test probes; electrode; additional connecting pieces; 9V battery. This kit permits the building of 30 circuits.

LASKY'S PRICE £7.2.6 Post 3/6


SPECIAL HI-FI OFFER AD-86K STEREO MAGNETIC CARTRIDGE

The famous AUDIO DEVELOPMENT AD-86K high compliance stereo magnetic cartridge now at our "all time low" special price offers you the opportunity of obtaining magnetic pickup quality for your hi-fi at a price you can afford. Brief Spec: Diamond L.P. stylus Compliance 10×10^{-6} cm/dyne. Frequency response 20-20KHz. Channel separation 25dB. Output 5mV. Tracking pressure 3gm \pm 0.5gm. Standard j/m mounting. (Replacement stylus available.) Don't miss this great chance. List Price £8.2.8.

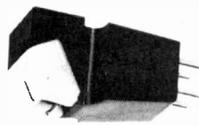

SPECIAL PRICE 69/6 Post 2/6
 Replacement diamond stylus EN308 39/6.

SKYROVER MK II

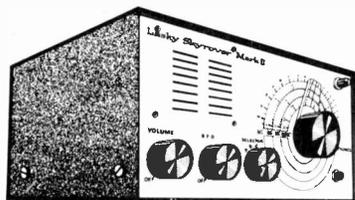

COMMUNICATION RECEIVER

A short wave receiver, exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain. Switch selected SW frequency range cover: 1.5 to 30Mc/s in three separate band-spread ranges and full AM medium waveband cover in one range 550-1,600Kc/s. Reduction drive tuning with hair line cursor. Power on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2" x 5 1/2" x 5 1/2". Complete with mains lead and full instructions.

Controls include volume on/off, BFO, Band selector. Power on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2" x 5 1/2" x 5 1/2". Complete with mains lead and full instructions.


**LASKY'S PRICE
£13.13.0** Post 5/-

Lasky's

NEW FOSTER "Criterion" Mk II

2 SPEAKER TWO WAY BOOK-SHELF SPEAKER SYSTEM

Another high quality sub-miniature book-shelf system from Foster. The "Criterion" Mk II is a sealed infinite baffle type enclosure using 5 1/2 in bass/mid-range woofer with rolled cloth edge and a 2 1/2 in HF cone type tweeter. The compact cabinet is constructed of 1/2 in laminate with handsome oiled walnut veneer finish and black woven acoustic gauze front panel with satin chrome edge insert. SPEC: Frequency range 90-20,000Hz. Power handling 10 watts. Impedance 8 ohms. HF crossover. Screw tag connections at rear. Size 12 1/2 x 7 1/2 x 6 1/2 in. The performance of the "Criterion" is superior to many larger and more expensive units and at Lasky's exclusive price offers absolutely unbeatable value.

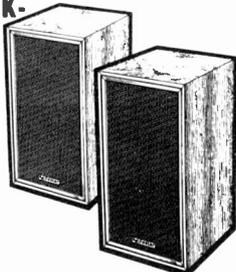


Post 1-7/6
2-12/6

LASKY'S PRICE **£9.10/-** or **£17.10/-**
2 for

TTC MODEL C-1000

A really tiny 1,000 O.P.V. pocket multi-tester with "big" meter performance. Precision 2 jewel meter movement. Hand calibrated to ±3% accuracy on full scale of DC ranges. 4% on AC ranges. 2 1/2 in square meter. SPECIFICATIONS AC/V ranges: 0-10, 50, 250 100V at 1K/O.P.V. DC currents: 0-1-100mA. Resistance: 0-150K/ohms (3,000 ohms centre scale). Decibels: -10 to +22dB. Operated on one penlight cell. Two colour buff/green case—size only 3 1/2 x 2 1/2 in. Click stop range selection switch. Ohms zero adjustment. Complete with test leads, battery and instructions with circuit data.

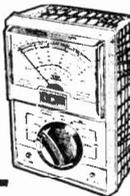


LASKY'S PRICE **39/6**

Post 2/6

TTC MODEL C-1051

20,000 O.P.V. pocket multimeter with mirror scale and built in thermal protection circuit. Exceptionally large easy to read meter with D'Arsonval movement. Colour coded scales. Single positive click-in, reversed selection switch for all ranges. Ohms zero adjustment. Range spec: A.C. volts: 0-6-30-300-1200V at 10K/ohms/V. D.C. volts: 0-3-15-150-300-12KV at 20K/ohms/V. Resistance: 0-66K-6megs. D.C. current: 0-50µA-300mA. Decibels: -20dB to +17dB. Hand calibration gives extremely high standard of accuracy on all ranges. Uses one 1 1/2 V penlight battery. Strong impact resistant plastic cabinet—size only 4 1/2 x 3 1/2 x 1 1/2 in. Two colour buff/green finish. Complete with test leads and battery. Original list price 59s.

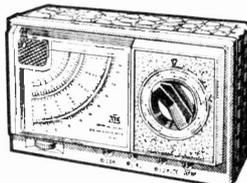

LASKY'S PRICE **75/-**

Post 2/6

TMK PL-436

20,000 O.P.V. Multitester for the amateur or professional. Features mirror scale and wood grain finish front panel. Spec: D.C./V ranges: 0-6, 3, 12, 30, 120, 600V at 20K/O.P.V. A.C./V ranges: 3, 30, 120, 600V at 8K/O.P.V. D.C. current: 50µA, 0-6, 60, 600mA. Resistance: 10K, 100K, 1M and 10M ohms end scale (65, 650, 6.5K and 65K ohms centre scale). Decibels: -20 to +37dB in four ranges. Operates on 2 x 1.5V U7 type batteries. Size: 5 1/2 x 4 1/2 x 2 1/2 in. Complete with test leads, batteries and instructions.




LASKY'S PRICE **£6.19.6**

Post 5/-

SCOOP! THE WORLD'S SMALLEST

6 TRANSISTOR TWO WAVEBAND RADIO RECEIVER

THE Astrad ORION

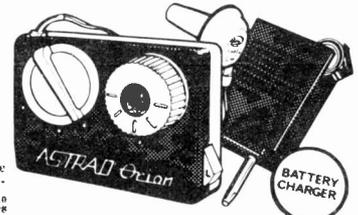

Made to the highest space-age standards—this remarkable micro-size set measures only 1 1/2 in x 1 1/2 in x 5/8 in, yet it contains 6 transistors and other components combined in a photo etched circuit, only 2 x 1/4 in: tuning capacitor, ferrite rod aerial, battery, wave band selection switch etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 160 kc/s, Long wave 150 kc/s to 408 kc/s. Sensitivity: 35mV max. Selectivity: -10dB (at 30 kc/s de-tuning). Power source: 1 x 1.4V Mercury battery.

The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic presentation/carrying case (matching the Orion). Never miss your favourite music, sport, news—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.

LASKY'S PRICE **ONLY 39/6**

Post 2/6
Extra re chargeable battery 3/6

*NOTE: The battery we supply with the Orion is a rechargeable type. Charger units are available enabling you to re-charge the battery from AC Mains 220/240V supply.

PRICE 19/6 extra. Post free with radio—otherwise 2/-

MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605Kc/s, 88 to 108Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 self powered by one 9V (PP3 type) battery is merely placed close to the receiving set and then tuned over 110 to 133Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 1 1/2 in. chrome telescopic antenna, size only 4 x 2 1/2 x 2 1/2 in. (inc. knobs). Complete with battery and full instructions.



LASKY'S PRICE **79/6**

Post Free

NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE at RECORD LOW PRICES

3in Message tape, 150ft	2 6	3in Standard play, 850ft PVC	11 6
3in Message tape, 225ft	3 9	3in Long play, 1,200ft Mylar	15 0
3in Message tape, 300ft	7 6	3in Triple play, 2,400ft Mylar	45 0
3in Triple play, 600ft Mylar	10 0	7in Standard play, 1,200ft Acetate	12 6
4in Triple play, 900ft Mylar	17 6	7in Standard play, 1,200ft Mylar	12 6
5in Double play, 1,200ft Mylar	15 0	7in Long play, 1,800ft Mylar	19 6
5in Long play, 900ft Acetate	10 0	7in Double play, 2,400ft Mylar	25 0
5in Standard play, 600ft PVC	8 8	5in Triple play, 1,800ft Mylar	35 0
5in Triple play, 1,800ft Mylar	22 6	7in Long play, 1,800ft Acetate	15 0
5 1/2in Long play, 1,200ft Acetate	12 6	7in Triple play, 3,600ft Mylar	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free. Special quotes for quantities.

NEW BUDGET PRICED CASSETTES from the U.S.A.

C.60—7/6 (6—42/6) C.90—12/6 (6—70/-) C.120—17/6

Post 1/- each. 4 and over Post Free. Special quotes for quantities.

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 8233

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1



Tel: 01-790 4821

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You **LEARN**—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
Dept. 371B, Aldermaston Court,
Aldermaston, Berkshire.

To: B.I.E.T., Dept. 371B, ALDERMASTON COURT,
ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name.....
address.....
age.....

POST THIS COUPON NOW!



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 90 ft. 18 gauge on plastic reel. Recommended retail price 15/-



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 202 ft. 22 gauge on plastic reel. Recommended retail price 15/-



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	2/6*
Size 5 (Illustrated)	Savbit	18	2/6*
15	60/40	22	3/-*

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIF WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

FREE LIST! SEND S.A.E. FOR BUMPER FLOG LIST

TECHNICAL TRADING

BARGAIN SPRING SALES AT ALL BRANCHES

- ★ LONDON (MUS 2639) 10 Tottenham Court Road
- ★ PORTSMOUTH (Tel. 22034) 350-352 Fraddon Road
- ★ SOUTHAMPTON 72 East Street (Tel. 25851)
- ★ BRIGHTON (Tel. 23975) 6 Queen's Road

All mail orders to DEVONIAN COURT, PK. CRES. PLACE, BRIGHTON (Tel 680722)

FANTASTICALLY POPULAR ★ JASON TAPE ★

We offer you fully tensilised polyester mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports **TRY ONE AND PROVE IT YOURSELF.**

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	12/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	Quadraple Play 3in. 600ft.	8/6


Postages 1/- reel. Post Free less 5% on three reels. Quantity and Trade enquiries invited.

BUILD YOUR CIRCUITS on VEROBOARD

—the Universal Wiring Board—obtainable from your local Retailer

Trade enquiries to: **NORMAN ROSE (ELECTRICAL) LTD.** 8 St. Chad's Place, Gray's Inn Road, London, W.C.1

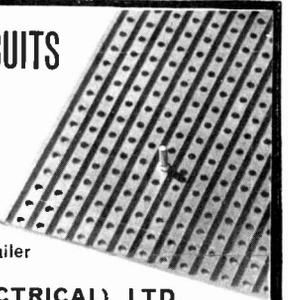
Technical enquiries to: **VERO ELECTRONICS LTD.** Industrial Estate, Chandler's Ford, Hants



LIND-AIR OPTRONICS LTD

See our vast range of Electronic Components and Accessories at our enlarged Component Centre 25 Tottenham Court Road

MAINS KEYNECTOR SAVES TIME—SAFELY!

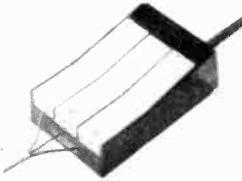

One mains "Keynector" instantly and safely connects electrical appliances to mains supply without the use of a plug. A number of appliances may be used simultaneously up to the full 13 amp rating of this device. A red light glows when "live". The "Keynector" is fused and has its own robust switch which is interlocked to prevent connections when "live".

Unavailable to handymen, servicemen, demonstrators, etc.

39/6 P. & P. 3/-

VHF AIRCRAFT BAND CONVERTER.

When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 108-135Mc/s. can be obtained. All transistor, 9V battery operation. Fully tunable 18jin. x 7 section telescopic aerial. Size 4 2/3 x 1 1/2in. 79/6. P. & P. 3/6



MODEL MAKER'S MOTOR

No. 15RN. Voltage 11.5V. Current 400mA. Torque 12g.cm. Body size 1 1/2" x long 7/8" dia. Shaft 3/8" long 3/16" dia. Ideal for small models and toys. 5/6 each. P. & P. 1/3. 3 for 15/- P. & P. 2/6.



DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. Only 59/6. P. & P. 3/6.



Battery Eliminator

Enables a transistor equipment to be operated from AC mains. 6/9 12V output selector switch and on/off switch. 100mA. Case size 4 2/3 x 2 1/2in. Complete with mains lead, connecting leads and instructions. 59/6. P. & P. 3/6.



SINCLAIR IC-10 INTEGRATED CIRCUIT



10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6. P. & P. 1/6.

SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250V. Output 15V at 0.5amps. 16/6. P. & P. 2/6.

HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY					
J1001	3"	Long Play PVC	2250ft	5/8	P. & P. 1/2
J1002	3"	Triple Play Poly	600ft	10/6	P. & P. 1/2
J1003	5"	Long Play PVC	900ft	10/-	P. & P. 1/8
J1004	5"	Double Play Poly	1200ft	15/-	P. & P. 1/8
J1005	5 1/2"	Long Play PVC	1200ft	12/6	P. & P. 2/-
J1006	5 1/2"	Double Play Poly	1800ft	22/6	P. & P. 2/-
J1007	7"	Standard-1 Play PVC	1200ft	12/6	P. & P. 2/6
J1008	7"	Long Play PVC	1800ft	17/6	P. & P. 2/6
J1009	7"	Double Play Poly	2400ft	25/-	P. & P. 2/6
J1010	7"	Triple Play Poly	3600ft	50/-	P. & P. 2/6



Visit our Brand New enlarged Hi-Fi Demonstration Room, Tape, Record Bar and Scientific Show of Microscopes, Binoculars, Telescopes and Watches at 18/19 Tottenham Court Road

TRANSFORMERS

AUTO WOUND TRANSFORMERS

All winding voltage ratings and tappings 0-115-200-220-240V, except MT113 0-115-210-240V

		Size	Weight	Price	
MT113	20W	2 1/4 x 1 1/4 x 1 1/2in	11oz	12/6	(P. & P. 2/6)
MT64	75W	2 1/2 x 2 1/2 x 2 1/2in	11b 14oz	21/9	(P. & P. 4/6)
MT4	150W	3 1/2 x 2 1/2 x 3in	31b	33/-	(P. & P. 6/9)
MT65	200W	3 1/4 x 4 1/4 x 4in	41b	39/6	(P. & P. 6/9)
MT66	300W	4 x 4 x 3 1/2in	61b 7oz	59/4	(P. & P. 9/-)
MT110	400W	4 1/4 x 4 1/4 x 4in	111b	85/-	(P. & P. 10/-)
MT67	500W	5 1/4 x 4 1/4 x 4in	121b 8oz	89/-	(P. & P. 10/6)
MT83	750W	4 1/2 x 5 1/2 x 4 1/2in	131b 4oz	95/7	(P. & P. 10/6)
MT84	1000W	4 1/2 x 5 1/2 x 4 1/2in	161b	142/2	(Carr. extra)
MT93	1500W	5 1/2 x 5 1/2 x 6 1/2in	281b 9oz	170/6	(Carr. extra)
MT94	1750W	5 1/2 x 6 1/2 x 6 1/2in	311b	195/-	(Carr. extra)
MT95	2000W	7 x 6 1/2 x 8 1/2in	401b	211/2	(Carr. extra)
MT73	3000W	6 1/2 x 7 1/2 x 8 1/2in	451b 8oz	300/-	(Carr. extra)

LOW VOLTAGE 12V RANGE

Primary 200-250V; secondary 12V					
MT111	0.5A	3 x 2 1/4 x 1 1/2in	12oz	15/3	(P. & P. 2/6)
MT71	2A	2 1/2 x 2 1/2 x 2 1/2in	11b	19/-	(P. & P. 3/9)
MT69	4A	3 x 2 1/2 x 2 1/2in	21b 4oz	28/-	(P. & P. 6/9)
MT70	6A	4 x 3 x 3 1/2in	31b 12oz	38/-	(P. & P. 6/9)
MT72	10A	3 1/4 x 4 1/4 x 4in	61b 3oz	51/-	(P. & P. 9/-)
MT115	20A	4 1/4 x 4 1/4 x 4in	111b 13oz	95/-	(P. & P. 9/-)
MT187	30A	5 1/4 x 4 1/4 x 4in	161b 12oz	180/-	P. & P. 13/6

LOW VOLTAGE 24V RANGE

Primary 200/250V; secondary 24V					
MT58	1A	2 1/2 x 2 1/2 x 2 1/2in	11b 7oz	23/9	(P. & P. 4/6)
MT114	3A	2 1/2 x 3 1/2 x 3in	31b 6oz	38/-	(P. & P. 6/-)
MT73	5A	4 x 3 x 3 1/2in	51b 12oz	53/10	(P. & P. 6/-)
MT17	8A	4 1/4 x 3 1/4 x 4in	71b 8oz	72/7	(P. & P. 9/-)
MT116	10A	4 1/4 x 4 1/4 x 4in	111b 13oz	95/-	(P. & P. 11/-)

LOW VOLTAGE 30V RANGE

Primary 200/250V; secondary tapped 12-15-20-24-30V					
MT112	0.5A	3 1/2 x 2 1/4 x 1 1/2in	11b 4oz	17/4	(P. & P. 3/9)
MT79	1A	2 1/2 x 2 1/2 x 2 1/2in	21b	23/-	(P. & P. 6/9)
MT29	3A	4 x 3 1/2 x 3 1/2in	41b 6oz	46/2	(P. & P. 6/9)
MT61	5A	4 1/2 x 3 1/2 x 4in	61b 8oz	60/9	(P. & P. 9/-)
MT88	8A	5 1/2 x 3 1/2 x 4 1/2in	91b 6oz	82/4	(P. & P. 9/-)
MT89	10A	5 1/2 x 4 1/2 x 4in	121b 2oz	105/6	(P. & P. 11/-)

LOW VOLTAGE 50V RANGE

Primary 200-250V; secondary tapped 19-25-33-40-50V					
MT102	0.5A	2 1/2 x 2 1/2 x 2 1/2in	11b 11oz	21/3	(P. & P. 6/-)
MT104	2A	4 x 3 1/2 x 3 1/2in	51b	45/8	(P. & P. 6/-)
MT106	4A	4 1/2 x 4 1/2 x 4 1/2in	91b 4oz	77/-	(P. & P. 9/-)
MT118	8A	5 1/2 x 4 1/2 x 4 1/2in	181b 9oz	132/-	(P. & P. 13/6)
MT119	10A	6 1/4 x 4 1/2 x 4 1/2in	191b 12oz	165/-	(P. & P. 15/6)

LOW VOLTAGE 60V RANGE

Primary 200/250V; secondary tapped 24-30-40-48-60V					
MT124	0.5A	3 1/2 x 2 1/4 x 2 1/2in	21b 4oz	24/-	(P. & P. 6/-)
MT127	2A	4 x 3 1/2 x 3 1/2in	51b 6oz	52/10	(P. & P. 6/-)
MT123	4A	4 1/2 x 3 1/2 x 4 1/2in	101b 8oz	99/-	(P. & P. 11/-)
MT122	10A	6 1/2 x 5 1/2 x 4 1/2in	231b 2oz	152/-	(Carr. extra)

MAINS H.T. RANGE

			Size	Price/P	
MT1AT	250-0-250V	80MA	6.3V 3.5A 5/6.3V 1A 3 1/2 x 3 1/2 x 3 1/2in	33/-	6/-
MT6AT	250-0-250V	100MA	6.3V 3.5A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	38/3	6/-
MT10	250-0-250V	120MA	6.3V 3.5A 5/6.3V 1A 4 x 4 x 3 1/2in	44/9	6/-
MT11AT	300-0-300V	100MA	6.3V 3.5A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	37/9	6/-
MT12AT	300-0-300V	120MA	6.3V 4A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	46/2	9/-
MT32AT	300-0-300V	150	6.3V 4A 5/6.3V 1A 4 x 4 x 3 1/2in	59/4	9/-
MT2AT	350-0-350V	80	6.3V 3.5A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	38/6	6/-
MT7	350-0-350V	100	6.3V 3.5A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	42/4	6/-
MT8	350-0-350V	120	6.3V 3.5A 5/6.3V 1A 4 x 3 1/2 x 3 1/2in	50/-	6/-

BATTERY CHARGER TYPES


Primary voltage 200-250V; secondary 6-12V (Rectifier not included)					
MT45	1.5A	2 1/2 x 2 1/2 x 2 1/2in	11b 9oz	21/9	(P. & P. 4/6)
MT46	2A	3 1/2 x 2 1/2 x 2 1/2in	21b 4oz	25/4	(P. & P. 6/-)
MT47	3A	4 x 3 x 3 1/2in	31b 8oz	28/4	(P. & P. 6/-)
MT5	4A	4 x 2 1/2 x 3 1/2in	31b 11oz	33/-	(P. & P. 6/-)
MT8	5A	4 x 3 1/2 x 3 1/2in	51b 4oz	42/6	(P. & P. 6/-)
MT86	6A	4 x 3 1/2 x 3 1/2in	51b 12oz	48/-	(P. & P. 6/-)
MT48	7A	4 x 4 x 3 1/2in	61b	56/7	(P. & P. 9/-)
MT146	8A	3 1/2 x 4 x 4in	61b 4oz	75/-	(P. & P. 9/-)
MT49	9A	4 1/2 x 3 1/2 x 4in	71b 8oz	99/-	(P. & P. 9/-)
MT147	10A	4 1/2 x 3 1/2 x 4in	91b 3oz	105/-	(P. & P. 9/-)
MT80	12.5A	5 1/2 x 4 1/2 x 4 1/2in	11b 14oz	125/-	(P. & P. 11/-)

Amperages are d.c. when used with nominal selenium bridge rectifiers

MAINS ISOLATING RANGE also available

TTC.C1001 MULTITESTER in leather case.

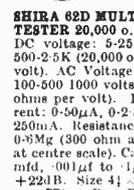
Overload protection. 20,000 ohm AC volts 10, 50, 250, 1,000V. DC volts 5-25, 125, 500, 2,500V. D.C. Current 0-50uA, 0-250mA Resistance 0-60K, 0-6 Megohm. Decibels -20 to +22dB. Size of meter 4 1/4 x 3 1/4 x 1 1/4in. 85/- P. & P. 3/6.



SHIRA 62D MULTITESTER 20,000 o.p.v.
DC voltage: 5-25-50-250-500-2.5K (20,000 ohms per volt). AC Voltage: 10-50-100-500 1000 volts (10,000 ohms per volt). DC Current: 0-50uA, 0-2.5mA, 0-250mA. Resistance: 0-6K, 0-5MG (300 ohm and 30K at centre scale). Capacitance: 10pf to 0.01 mfd, 0.01uf to 1uf. Decibels: -20 to +22dB. Size 4 1/4 x 3 1/4 x 1 1/4in. Complete with case 77/- P. & P. 3/6.



3-DeC BREAD BOARD

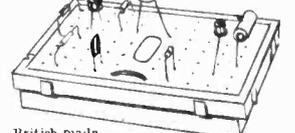

British made
Solderless breadboard panels, for fast reliable component connections. Control Single DeCs and One 8-DeC with Control Panel, Jigs and Accessories for solderless connections to controls, etc., with booklet "Projects on 8-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.
4-DeC KIT. Four 8-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on 8-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. 157/6. P. & P. 3/6.

GARRARD DECKS



SRP22 less cartridge	25.96
1025 Stereo/Mono with cart.	60.19.8
2025 Stereo/Mono with cart.	72.19.8
3000S Stereo/Mono with cart.	29.19.8
30001S Stereo/Mono with cart.	210.19.8
SP25 less cartridge	211.19.8
SP25 with Decca Deram cart.	217.4.8
SL55 less cartridge	211.19.8
SL55 with Decca Deram cart.	217.4.8
SL65 less cartridge	214.9.8
Covers for above	22.19.8
Bases for above	22.10.0
AP75 less cartridge	218.19.8
SL75 less cartridge	238.7.0
SL95 less cartridge	238.19.8
Bases for above	24.19.8

SPECIAL OFFER!
SP25 less cart., with base 113.10.9
P. & P. Deck/Cover/Base 17/-

MINIATURE SOLDERING IRON
British made and designed for use with transistor circuitry but ideal for many other uses. A.C. 240V, 18W. Length 8 1/2in. Slide on bit. Price 82/6. P. & P. 2/-.



LIND-AIR OPTRONICS LTD
18/19, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.
Telephone: 01-580 2255/4532/7679
Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

ALL MAIL ORDERS
To Dept. PE270
54a Tottenham Court Road
London, W.1

IF YOU HAVE

A HOME RADIO CATALOGUE

Ordering components is easier and quicker with our new

Credit Account Service



Just a
phone call
away

Our aim in life at Home Radio Components Ltd. is to make *your* life happier and less complicated! To this end we have recently introduced a Credit Account Service, one advantage of which is that you can order components by telephone *any time, any day*. If you phone out of shop hours a recording machine will take your message for us to deal with as soon as we open shop next day.

There are *other* advantages to the new Service—if you want to order by post we provide Order Forms and *Prepaid* Envelopes. You settle your account just once per month. We stipulate *no* minimum order value. Of course for ordering your components you first need our Catalogue, and after you have been in the Service 12 months we regularly send you an up-to-date catalogue—FREE!

For full details of our Credit Account service drop us a line or phone 01-648 8422.

IF YOU HAVEN'T...



Whether or not you want to use the Credit Account Service described above, you certainly need the Home Radio Components Catalogue if you construct or repair radio and electronic gadgets. The catalogue has 350 pages, lists 8,000 components and has over 1,500 illustrations. It contains 6 vouchers, each worth 1/- when used as indicated. Post the coupon with 12/- (8/6 plus 3/6 postage and packing) and we will send a catalogue by return of post. By the way, we supply *free* a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

Please write your Name and Address in block capitals

Name _____

Address _____



HOME RADIO (COMPONENTS) LTD., Dept. PE
234-240 London Road, Mitcham, Surrey, CR4 3HD

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES
Advertisement Manager D. TILLEARD

JUST THINK!

THE usefulness of electronics is surely limited only by our imagination. And amateurs no less than professionals have the power to extend this general usefulness in very many ways.

Consider the constructional projects featured in these pages. Broadly speaking, they can be divided into two classes. There are those designed right down to the final detail for some specific and exclusive purpose. There are also those not designed for just one particular or specific application, but having general utility or wide adaptability.

In this second category appear from time to time circuits that perform well defined functions, usually in response to external influences, though their adaptation to a practical task is generally left to the individual constructor. There is good justification for this. Designs such as these form the core of electronics, and are the basis around which the most elaborate of systems can be built up. They can also be likened to tools, to be applied with skill and imagination in solving problems and easing difficulties commonly experienced in everyday affairs. The circuit designer can suggest some applications, but it is beyond his powers to perceive all the multitude of needs which a particular circuit could likely meet.

Thus the exploitation of many circuits is very much a matter for individual enterprise. And devising an application is, in its own way, an achievement just as important and creative as the original circuit design. Of course, not only imagination, but a down-to-earth awareness of current problems and needs is desirable for this purpose, if the maximum benefit is to be extracted from electronics.

This month a design of the kind we have been referring to appears in our pages in the form of a sound operated switch. The function of this circuit is immediately evident, but its possible use perhaps less so. But it could initiate the thinking process, and that is no bad thing. One idea that has been brought to our attention certainly deserves serious thought, and we pass it on to our readers for due consideration. It is suggested that disabled and infirm persons, especially if bedridden or house bound, could find an alarm or signalling system based on this sound operated switch a boon. Anyhow, it is a thought.

Really, it is quite amazing what important roles even a humble circuit like this can assume, when you come to think about it.

F.E.B.

THIS MONTH

CONSTRUCTIONAL PROJECTS

RAINFALL GAUGE	116
P.E. ORGAN—10	134
SOUND OPERATED SWITCH	138
P.E. COMMUNICATIONS RECEIVER—5	144

SPECIAL SERIES

BASIC RADAR PRINCIPLES—1	121
DEMONSTRATION SWITCHING CIRCUITS—3	150

GENERAL FEATURES

CHESSBOARD COMPUTER	162
INGENUITY UNLIMITED	169

NEWS AND COMMENT

EDITORIAL	115
MARKET PLACE	130
SPACEWATCH	133
ELECTRONORAMA	142
BOOK REVIEWS	149
NEWS BRIEFS	154, 161
AUDIO TRENDS	157
READOUT	161

*Our March issue will be published on
Monday, February 16*

© IPC Magazines Limited 1970. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, 42s.


Editorial and advertisement offices: Fleetway House, Farringdon St., London, E.C.4. Phone 01-236 8080

RAINFALL GAUGE

By D. Bollen

Using digital readout this unit gives accurate measurement of rainfall with convenience of indoor monitoring

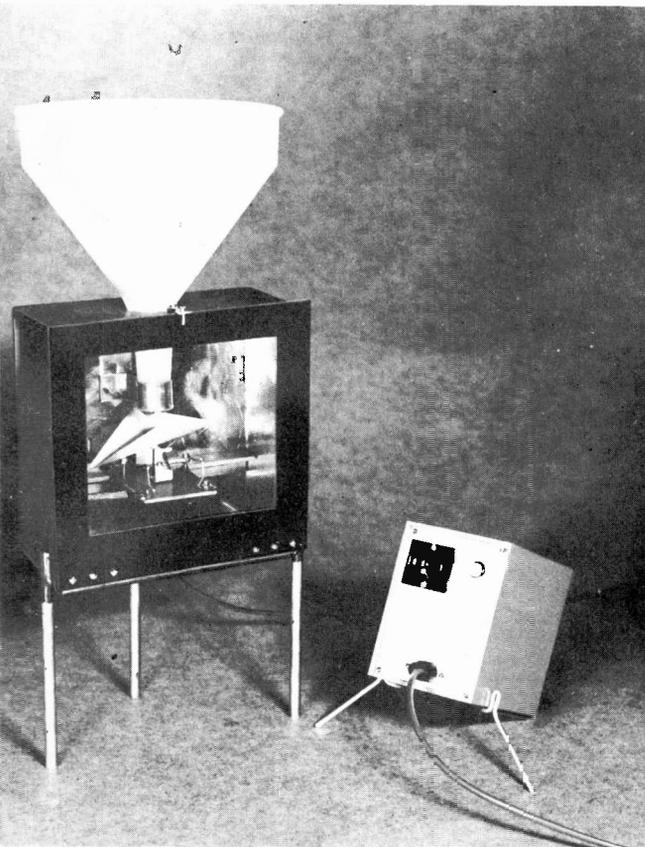THE main object of this rainfall gauge is that it should remove some of the outdoor discomforts of weather recording, by transmitting the desired information along wires to an indoor monitor. A metering accuracy of better than ± 1 per cent per inch of rain collected is desirable, while it should be capable of at least 6 months continuous operation on battery power.



RAIN GAUGES

A rain gauge which consists of a funnel and a graduated beaker is not a particularly convenient instrument for recording rainfall, because it involves direct measurement of water volumes.

More sophisticated gauges employ special bucket mechanisms to "digitise" the flow of water from a collecting funnel, and thereby give greater accuracy and convenience of measurement. However, where such instruments rely only on mechanical operation it is still necessary to go out of doors in all weathers to see how much rain has been recorded.

If the metering bucket is arranged to give an electrical pulse for every 0.01in increment of rainfall, it becomes a straightforward matter to record these pulses at some distance from the rain collecting funnel.

The prototype instrument uses such a system and, in fact, serves to demonstrate elementary analogue to digital conversion, and telemetry techniques.

BISTABLE BUCKET

It is quite often useful to consider the action of a mechanical device in terms of electrical circuit behaviour. The action of the "bistable" bucket can be related to that of a bistable multivibrator.

Looking at Fig. 1, the bucket has just attained one of its stable "states", and is in the process of discharging from the right-hand compartment while the left-hand compartment commences to fill. Note the "gating" action of the bucket partition; when the right-hand compartment is down the left-hand fills, and vice versa. Just at the point of tipping, when the weight of water has reached a pre-determined value, the bucket "flips" rapidly from one "state" to the other.

It is possible to adjust the amount of water discharged from each compartment by screwing up or down the bucket stop on the opposite side; this also provides a convenient method of levelling the bucket so that equal volumes of water are metered by each compartment.

The counting accuracy of the "bistable" bucket is mainly determined by the amount of frictional force exerted on the pivot shaft. If there is too much friction, the bucket will tend to tip varying amounts of water at each throw, or may not tip at all.

REED SWITCH PULSER

Fig. 2 shows how a low force switch of excellent reliability can be made from a small magnet and a reed switch. When the poles of the magnet are vertically aligned the reed switch contacts are open, but a small rotational movement of the magnet clockwise or anticlockwise causes the contacts to close.

It follows that, if the magnet is attached to the pivot shaft, the reed switch contacts will open briefly when the bucket "flips", and remain closed in the stable positions. The amount of friction imposed on the pivot shaft by this form of switch is very small indeed, and the enclosed contacts are not affected by humid conditions.

COUNTER CIRCUIT

The circuit in Fig. 3 shows an *npn-pnp* pair TR1 and TR2, which are held non-conducting when the contacts of S1 are closed; a small current due to R1 will flow along the line.

When the bucket tips, S1 contacts open briefly, R1 biases TR1 on, and the joint amplification provided by TR1 and TR2 causes a large current pulse to activate the electromagnetic counter.

Lamp LPI is included to show line discontinuities,

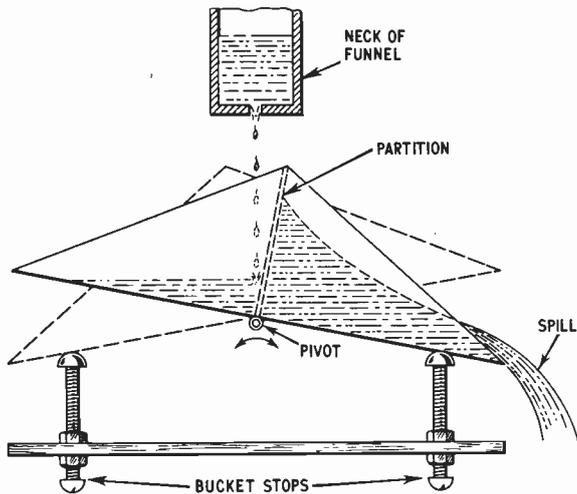


Fig. 1. Sectional view of the "bistable bucket" for metering liquid

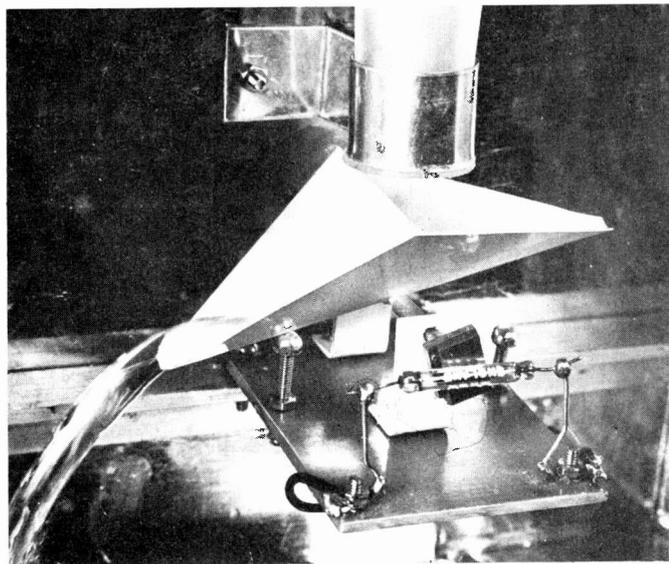


Fig. 2 (left). Low force magnet actuated reed switch operation


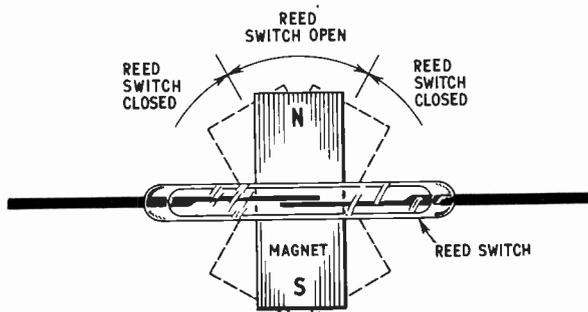


Fig. 3. Counter circuit and reed switch

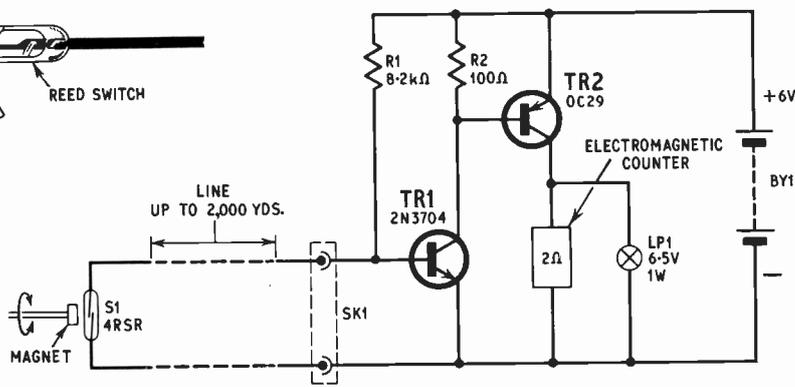

COMPONENTS . . .

Resistors

R1 8.2k Ω
R2 100 Ω
 $\pm 10\%$, $\frac{1}{2}$ W carbon

Transistors

TR1 2N3704
TR2 OC29

Switch

S1 Reed switch type 4RSR, 500mA contacts (Radiospares)
Short bar magnet 0.44in (Radiospares)

Lamp

LPI 6.5V 1W l.e.s. with l.e.s. lampholder

Socket and Plug

SK1 Non-reversible panel mounted, two-way

Battery

BY1 6V type 996

Miscellaneous

4 or 5 digit resettable electromagnetic counter (P.O. type meter)
Copper laminated s.r.b.p. 2in \times 3in \times $\frac{3}{32}$ in
Plain s.r.b.p. sheet 2 $\frac{1}{2}$ in \times 1 $\frac{1}{2}$ in
Aluminium sheet 18 s.w.g. 3in \times $\frac{1}{2}$ in
Brass rod 2in \times $\frac{3}{32}$ in dia.
Pillars $\frac{1}{2}$ in, 6 and 8B.A. nuts and bolts
Twin cable 14/0076 p.v.c. covered
Enamelled copper wire 26 s.w.g. for counter

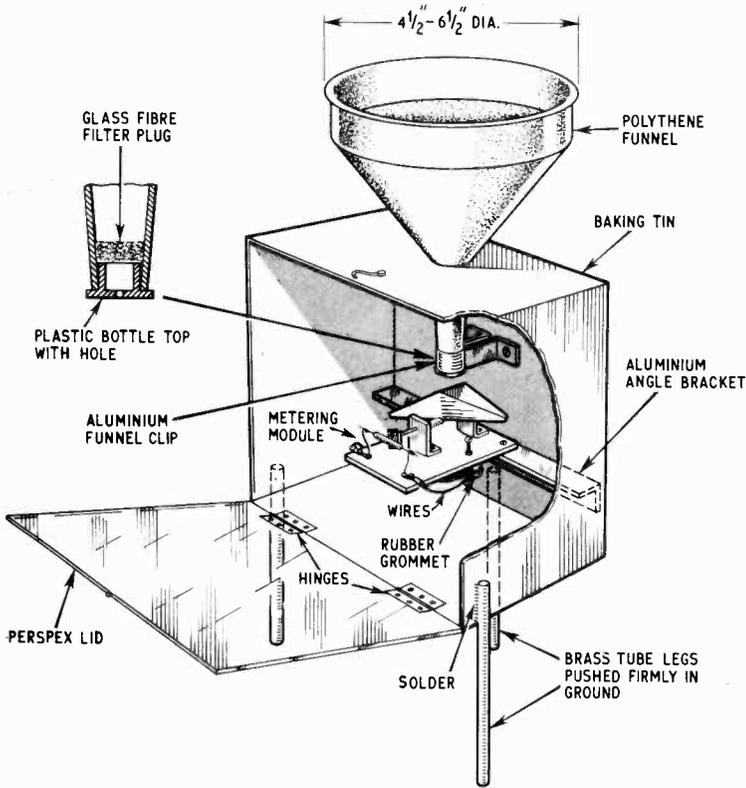


Fig. 4. Suggested layout for rain metering unit


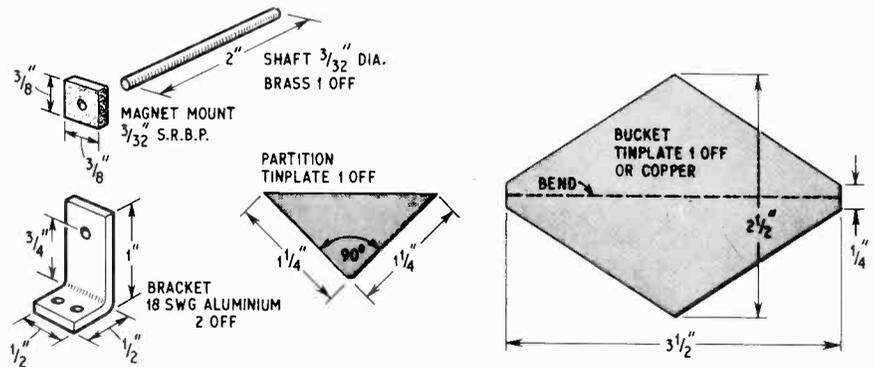


Fig. 5. Construction details of the liquid metering module

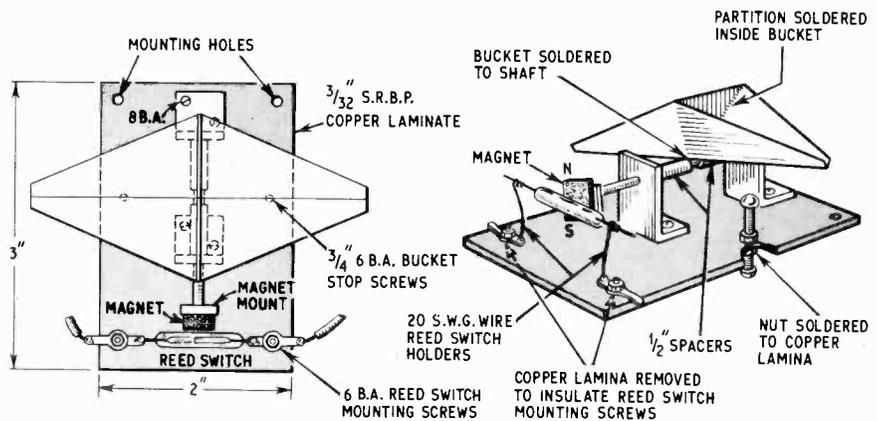

and gives a rough indication of the battery condition under full load, when the plug is removed from SK1.

The reason for not having an on-off switch in circuit is that it might be left inadvertently in the "off" position and thus falsify rainfall records. During a period without rain, circuit current drain is typically 1mA or less, most of which flows through R1.

At 1mA continuous, a 996 battery should give more than 10,000 hours' service, which is not much shorter than expected shelf-life. Although at the instant of pulsing, current rises to more than 2A, this will average out to less than 10mA equivalent continuous drain during periods of rainfall approaching the rate of 3in per hour.

LIQUID METERING MODULE

The metering module comprises a "bistable" bucket and a low force reed switch pulser mounted on a copper laminate panel. It is designed for use with plastic funnels from 4½in to 6½in diameter. A suggested housing for the module is shown in Fig. 4.

Module constructional details are given in Fig. 5. The bucket can be made up from tinfoil, cut from a can or tobacco tin. Resin cored solder and a 60W electric soldering iron are quite suitable for bucket joints provided that the tinfoil is thoroughly cleaned before soldering. After construction, remove surplus flux and paint the bucket with bitumen or similar proofing to prevent rusting.

When cutting and drilling the copper laminate panel, remove copper from around the holes where the reed switch mounting screws are situated. The 6B.A. nuts, to take the bucket stop screws, are soldered to the copper on the underside of the panel. Lock nuts may be fitted to the stop screws after final assembly.

Ensure that the pivot shaft moves freely in the bearing brackets with a small amount, but not excessive, "end float". To check correct switch action, listen for a closure "click" from the reed switch just before the bucket touches either stop. A rough test of bucket operation can be obtained by holding the module under a dripping tap.

INDOOR COUNTER UNIT

Component layout and underside wiring of the amplifier panel appear in Fig. 6, and a suggested layout of the complete indoor counter unit is shown in Fig. 7.

When wiring up the amplifier panel, avoid overheating TR2, as this might cause a permanent increase in leakage current, with a consequent shortening of battery life. LP1 tabs were soldered directly to the turret tags on the prototype amplifier panel.

Spring terminals on the 996 battery can make contact with small squares of tinned copper laminate which are glued to the front panel. The battery is held firmly against the contacts by the back of the counter box.

Having obtained an electromagnetic counter, it will almost certainly be necessary to rewind it for 6V operation, because the majority of this type of counter are intended for higher voltages. All of the existing winding should be removed from the coil first; it would not matter if the counter has a damaged coil to start with; it is not needed.

Where the electromagnet is mounted by a single stud, it is a simple matter to grip the stud in the chuck of a hand-drill, and then wind on 600 turns of 26 s.w.g. enamelled wire, maintaining even layer winding as far as possible.

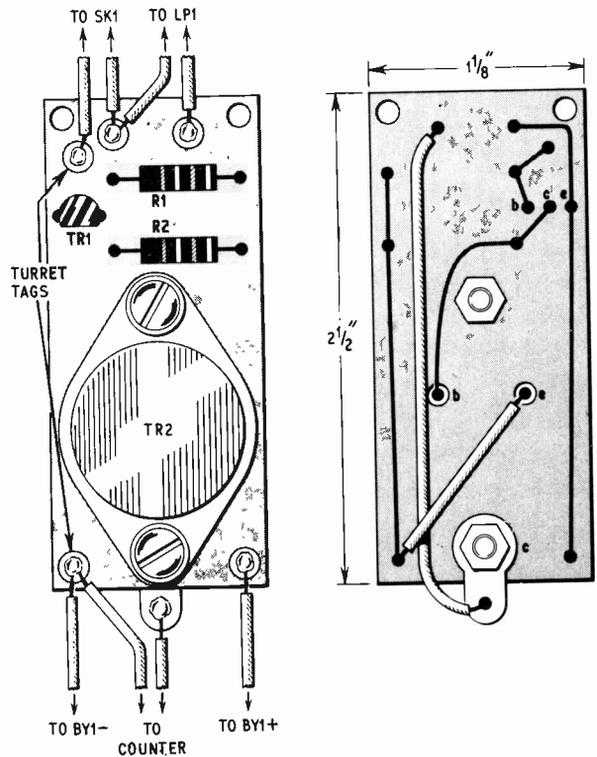


Fig. 6. Amplifier panel, components side and underside

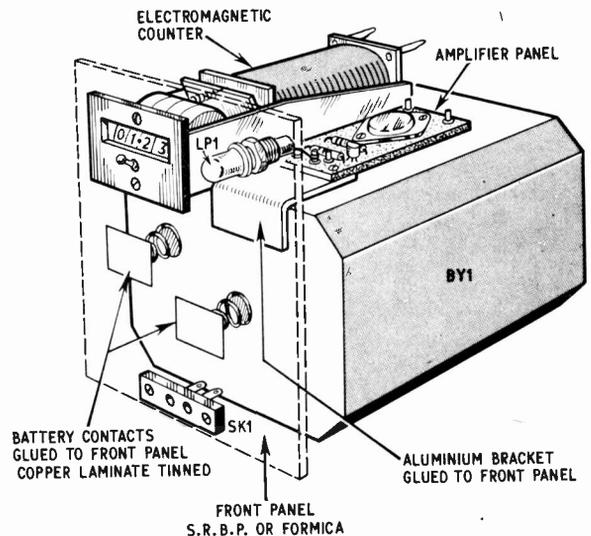


Fig. 7. Layout of the counter unit

There are many factors which affect radar operation: receiver noise, transmitter power, aerial beam shape, transmitter frequency, rain or cloud. For meteorological radar, signals reflected by rain or cloud provide valuable information, but for early warning enemy missile detection radar such echoes would be most unwelcome.

Each radar parameter has to be optimised for the specific application—marine, airfield, missile detection, and so on, but the principles to be described are common to all classifications.

Since radar echo signals are minute in comparison with the transmitted energy they must be detected in some manner which readily distinguishes them from the transmitted signal.

In pulsed radar this is done by turning off the transmitter for most of the time, so that any signals received during this "off" time can be recognised as echoes. This "off" to "on" duty period for the transmitter may be 1,000:1 or more. If the word radar is used without qualification then pulsed radar is almost always implied.

It is possible to recognise echoes even when the transmitter is operating and for specialised applications continuous wave radar may be used. Equipments where the transmitted signal is continuous or has a low duty cycle, typically 10:1, will be lumped into the category of c.w. radar.

Pulsed radar will be described first.

PULSED RADAR

The fundamental principles underlying the operation of a pulsed radar system are illustrated in Fig. 1.1. The transmitter is switched on for a short time (micro-seconds) to produce a burst or pulse of r.f. energy which is radiated from a directional aerial, much in the same way as a torch beam is directed.

If the energy encounters a target some of it is reflected back towards the receiver. ("Target" is the term used in the sense of the object to be located, rather than in the military sense.) This reflected energy is collected by the receiver aerial, amplified, and displayed on an indicator to show the radar operator that there is a target within range.

Although two aerials are shown in this diagram to aid the description, in practice a common aerial is usually used for both transmission and reception. To locate

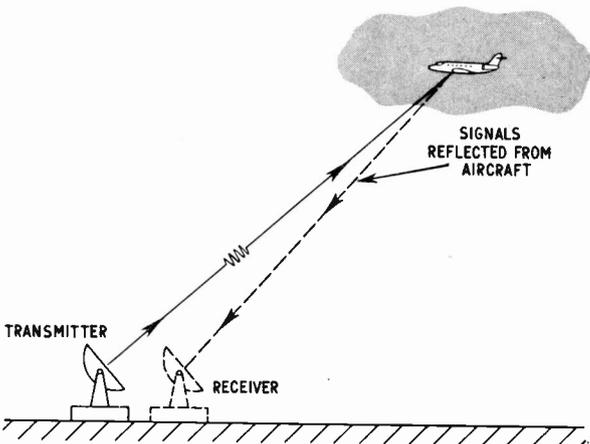


Fig. 1.1. The basic principle of a pulsed radar set

an object the radar must obtain three-dimensional information expressed as:

- (1) The bearing angle of the object with respect to ship track or north, or some other datum line.
- (2) The elevation angle of the object.
- (3) The range, or distance, of the object from the radar.

These three requirements are illustrated in Fig. 1.2.

RANGE MEASUREMENT

Radio waves travel through space at a velocity of 186,000 miles per second, but to avoid cumbersome units this figure may be converted to a scale more convenient for the application. For range measurement the time taken for a pulse to reach the target and return to the receiver is determined.

For the radio wave to travel 1,000 yards, the time taken would be $3\mu\text{s}$, so that for a target at 10,000 yards range, the pulse takes $30\mu\text{s}$ to reach it. The reflected energy travels another 10,000 yards back to the receiver. Therefore, the returned signal has travelled a total of 20,000 yards and has taken $60\mu\text{s}$ to do so.

The scales most commonly used to relate range and time delay are shown in Table 1.2.

Table 1.2. SCALES OF RANGE AND TIME DELAY

Range	Elapsed time between transmitted and received pulses
1,000 yards	$6.1\mu\text{s}$
1 mile	$10.7\mu\text{s}$
1 nautical mile	$12.4\mu\text{s}$

Range measured like this can be displayed on a cathode ray tube in a number of ways.

SIMPLE-RANGE DISPLAY

As the pulse is transmitted the sweep of a spot across the screen is initiated. When it has travelled its full sweep the spot flies back to the start and waits for the next transmitted pulse to trigger it again. A small sample of the transmitted pulse and the reflected signals are applied across the Y plates.


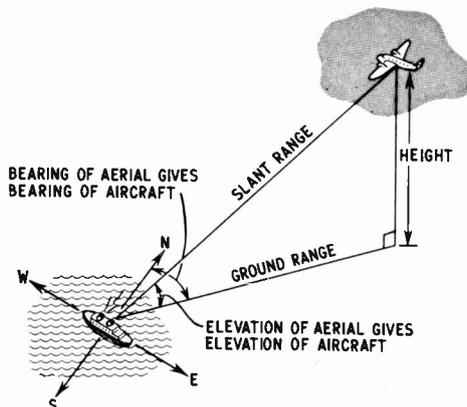



Fig. 1.2. The three information requirements for a radar set

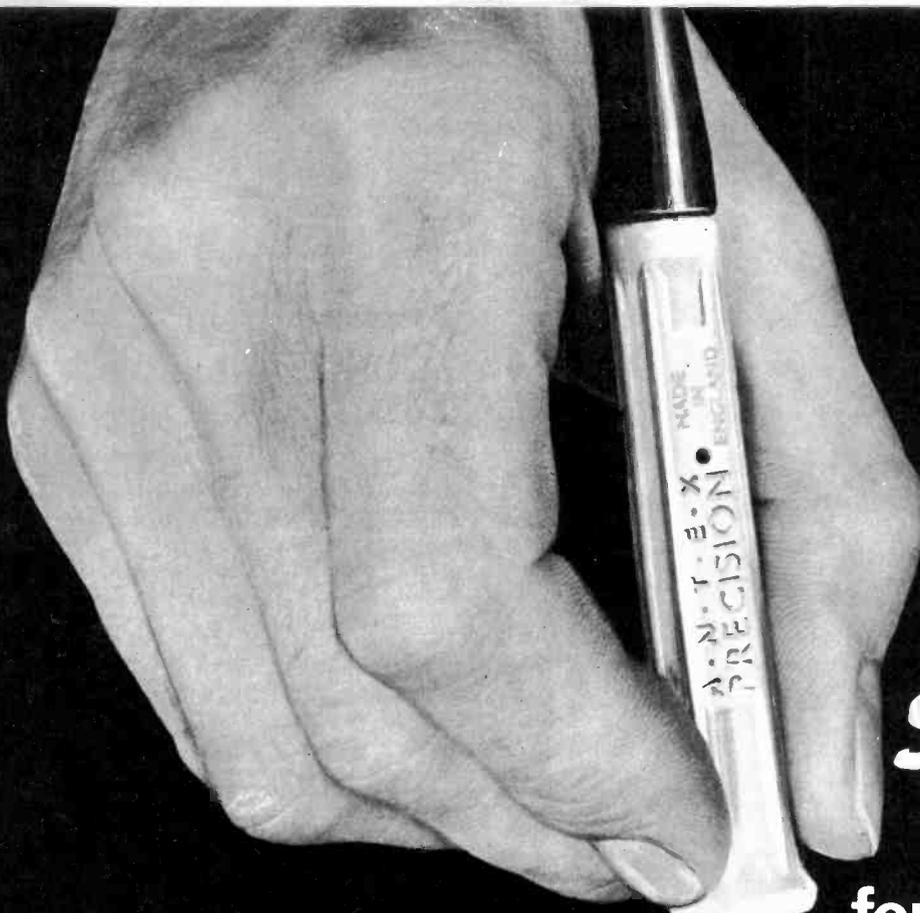

Sign here!!

**for your
miniature
soldering
iron.**

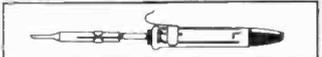CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 32/6**



G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-.



ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 35/-.



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6. Spare bits and elements for all models and voltages immediately available from stock.



Complete precision soldering kit

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box"—contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 3/32", 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31/-**



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

Please send me the Antex colour catalogue

Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....

I enclose cheque/P.O./cash value

NAME

ADDRESS


P.E.2

COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35

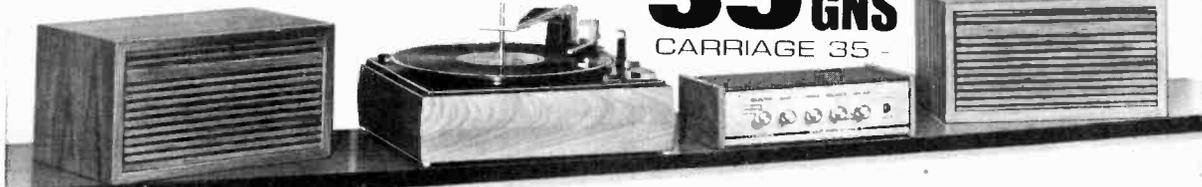

The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor Amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends. Size 12" x 5 1/4" x 3 1/4" high (Amplifier available separately if required £14.19.6. Carr. 7/6).

SPECIAL STEREO CARTRIDGES

SHURE	
M3D	List £8.10.6. Premier Price £8.19.6
M44-5	List £14.9.1. Premier Price £10.10.0
M44E	List £12.19.5. Premier Price £9. 9.0
M44E	List £17.8.4. Premier Price £13.19.6
M55E	List £20.15.1. Premier Price £15.15.0
M78-6	List £17.8.4. Premier Price £13.19.6
M75E	List £25.18.10. Premier Price £21.0.0

AUDIO-TECHNICA

AT78 Stereo	List £22.0.0 Our Price £15.0.0
AT7X Elliptical	List £25.0.0 Our Price £18.0.0

Post and Packing 1/6 each

"NOVA" TRANSISTOR STEREO AMPLIFIER

A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 10 watts per channel. Frequency response 40-20,000Hz ± 3dB. Inputs for Radio, P.U. Ceramic, P.U. Magnetic Tape. Separate bass and treble controls, Volume and Balance Controls. Mono/Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14 1/2 x 3 1/2 in., a.c. 200/250V.



WONDERFUL VALUE AT ONLY 25 gns. 10/-

"NOVA" 5 WATTS PER CHANNEL STEREO AMPLIFIER. Specification as above. £18.18.0. Carr. 10/-.

PICK-UP CARTRIDGES


AT MONEY SAVING PRICES!

GOLDRING G800 (Stereo)	£8.19.6
SONOTONE 9TAHC/D (Stereo)	£2.15.0
ACOS GP91/1SC (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94 (Stereo)	£2.14.8
B S R X3M (Mono compatible)	£1.18.5
B S R X3H (Mono compatible)	£1.18.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

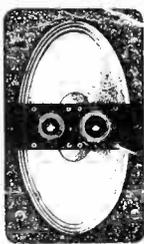All leading makes available including Rogers, Armstrong, Dulet, Wharfedale, Goodmans, Goldring, Shure, etc. etc.



E.M.I. 13 x 8in HI-FI SPEAKERS

Fitted two 2 1/2in tweeters and crossover network. Impedance 3 & 15 ohms. Handling capacity 10W. Brand new.

99/6

P. & P. 7/6

Also available without tweeters. 49/6

P. & P. 7/6



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft lead and stereo jack plug.

59/6

P. & P. 5/-

MONO HEADPHONES 2,000 ohm 14/6 P. & P. 2/6.

STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-.

MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-.

SAVE NEARLY £5!

Premier Stereo System with "NOVA" 10 watt Stereo Amplifier as above. 45 Gns. Carr. 35/-.

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone, low impedance microphones with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phono-plugs output. Attractive teak wood grain finish case.



Mono Model 59/6 Stereo Model 69/6

P. & P. 2/6.

'VERITAS' V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



34/6

P. & P. 1/6

JULIETTENA 5018 5 BAND 18 TRANSISTOR MAINS/BATTERY RADIO

Covers AM 540-1600Kc/s. Marine 1.6-4.6Mc/s. FM 88-108Mc/s. VHF 108-134Mc/s. PB 148-174Mc/s. Ferrite bar aerial for AM/MB. Telescopic aerial for FM/VHF/PB. 4" P.M. Speaker and B.F.O. Operates on AC 250V or DC by four 1.5V batteries. Size: 9 1/2" x 5 1/2" x 3 1/2".



PREMIER PRICE 39 GNS. P. & P. 10/-.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/8	LP6 5 1/2" 1200' P.V.C.	12/6
TT3 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/6
DT3 3 1/2" 600' POLYESTER	11/6	TT6 6 1/2" 2400' POLYESTER	37/6
SP5 5" 600' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	DT7 7" 2400' POLYESTER	25/-
DT5 5" 1200' POLYESTER	15/-	TT7 7" 3800' POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/9. TAPE CASES 5", 7" 2/6. Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/- (3 reels and over Post Free.)



MULTI TESTERS

"TEST 7". A really versatile instrument that makes a handy pocket size tool. Measures AC or DC voltage in three ranges 0-15-150-1000 volts. Resistance 0-100,000 ohms. Current 0-150 mA D.C. size only: 3 1/2 x 2 1/4 x 1 1/4 in. Complete with battery, test leads and instructions. 59/6 P. & P. 2/6.

POCKET SIZE MULTI TESTER With wide-angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt d.c. 10,000 ohms/volt a.c. 18 Ranges: 0-3-25-50-250-500-2,500 volts d.c. 0-10-50-100-500-1,000 volts a.c. 0-50µA-2.5mA-250mA d.c. 0-0.000 ohms-6 megohms. 10µF-0.001 mF-1 mF. -20 to +22dB. Complete battery, test lead and instructions. £4.19.6 P. & P. 3/6.

TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. 65/- P. & P. 4/-.



FOUR STATION INTERCOM. Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6. P. & P. 5/6.

"PREMIER" TAPE CASSETTES

C60 (60 min.)	7/6
THREE FOR 21/-	
C90 (90 min.)	12/6
THREE FOR 36/-	
C120 (120 min.)	17/6
THREE FOR 51/-	

P. & P. 1/-.

CASSETTE HEAD CLEANER
Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 11/6 P. & P. 1/-.

PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W1 Tel: 01-636 3451



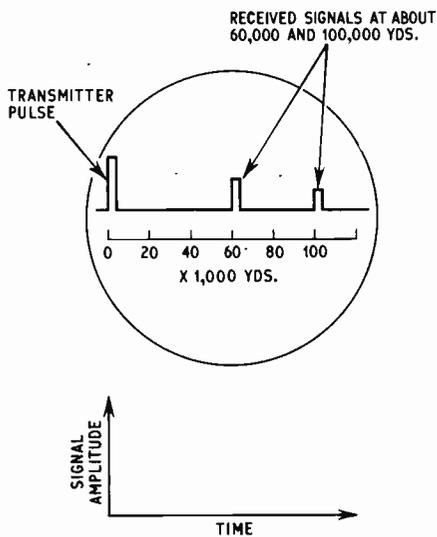


Fig. 1.3. "A" scope display of range

Since the pulse repetition frequency (p.r.f.) of the radar is high, typically 1kHz, the spot moves rapidly and the display appears continuous. This type of display is sometimes known as an "A" scope, Fig. 1.3.

If the radar p.r.f. is 1kHz then the spot could travel across the screen in 1ms. (Slightly less than 1ms in fact, because the spot cannot return to the start of the sweep instantaneously.) If the length of the sweep is 5in then each 1in represents $200\mu\text{s}$ or 20 miles.

The total length of scan represents the maximum attainable range of 100 miles since for targets beyond this range the reflected energy does not arrive back at the receiver before the next transmitted pulse. (A target at 110 miles could produce an indication as though it were at 10 miles, but the signal strength would be so low that it would be obvious that there was no real target at 10 miles.)

If the sweep speed is increased then the element of range represented on the screen is decreased, a sweep time of $200\mu\text{s}$ represents the first 20 miles of the available range. In this case the spot sweep is triggered by the transmitted pulse and takes $200\mu\text{s}$ to scan the screen. It then flies back to the start and waits for about $800\mu\text{s}$ during "dead time", until the next transmitted pulse again initiates the sweep.

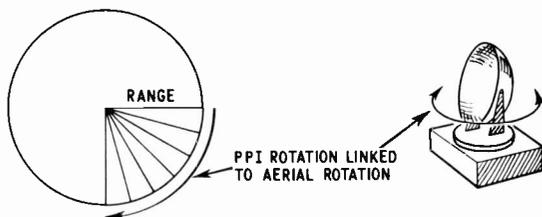


Fig. 1.4. The p.p.i. display principle for indicating both range and bearing

This "A" scope range display has the disadvantage that it can only display signals reflected from one direction at a time. This can be overcome by rotating the aerial and using a different form of display.

PLAN POSITION INDICATOR DISPLAY (P.P.I.)

For the p.p.i. display the spot sweep starts from the centre of a screen and moves outwards, so the distance between the centre of the screen and the circumference represents the range. Each sweep then rotates in step with the aerial, Fig. 1.4. The sweep from centre to circumference still occurs at the radar p.r.f. but the aerial rotation through 360 degrees occurs slowly due to mechanical limitations in moving the aerial mass.

The signals to be displayed are applied to the grid or cathode of the c.r.t. to "bright-up" the screen where a target appears. The screen is coated with a material having long afterglow properties so that the echo signals remain visible on the screen until the sweep has completed 360 degrees. The repeated rotational sweep brightens the display again.

A typical p.p.i. display is shown in Fig. 1.5, from which the range and bearings of all targets can be determined. The position of the transmitting and receiving aerial is normally indicated by the centre of the screen, but for some purposes such as ship navigation, it may be more

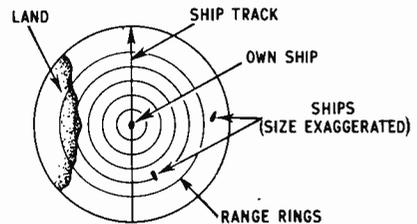


Fig. 1.5. A typical p.p.i. display for a ship

convenient to move the indication of the transmitter position to some other point on the screen, typically on the circumference.

HEIGHT MEASUREMENT

We have already seen how range can be determined by measuring the time it takes for a pulse to reach an object and return, and how bearing can be determined by rotating the aerial. For ship navigation purposes this is sufficient since all the ships, or land, are on the same plane as the transmitting ship, and the range measured is in this case the true ground range. However, for some applications, such as air traffic control, where the aircraft are not at a previously known elevation, it is important to determine height and ground range.

The elevation angle of an aircraft can be determined by allowing the aerial to "nod" up and down, and so locate the elevation at which maximum signal returns appear.

Once the target slant, range, and elevation have been determined, a straightforward trigonometrical calculation will give ground range and height, Fig. 1.6. In the early days of radar these computations for range and height were done mechanically, but now electronic methods are more reliable.

A "resolver" is provided with slant range and elevation information by an operator and produces height and ground range information which can be displayed as dial readings or on separate c.r.t.'s.

TYPICAL RADAR SYSTEM

The various sections of a radar installation are linked as, for example, in Fig. 1.7. The timing circuit generates a pulse at the radar p.r.f. which triggers the modulator at the required interval. Since the transmitter has to produce a very high power short pulse, it cannot be controlled by a normal electronic switch, and the modulator switches on the transmitter magnetron for the pulse duration required.

To avoid the need for two aerials, an electronic transmit-receive (t.r.) switch connects the transmitter to the aerial for the duration of the transmitted pulse and the receiver to the aerial for the intervals between pulses. This operation is not as simple as it sounds since, during the transmission of the high powered pulse, the receiver has to be protected from break-through which might damage it, and yet an instant later the receiver has to be ready to detect the very small signal returns.

These returns are mixed with the signal from a local oscillator to produce an output at the intermediate frequency. This i.f. signal is amplified and detected by

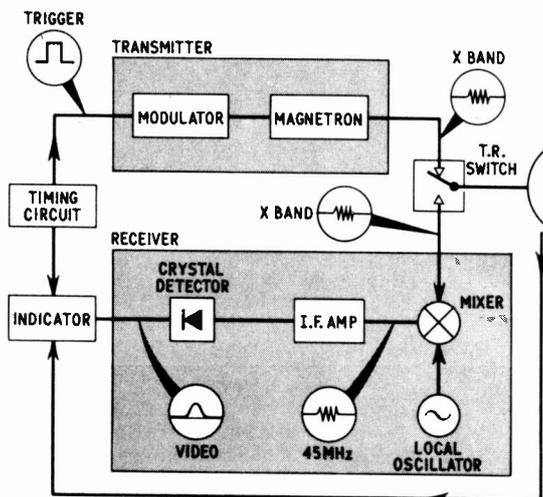


Fig. 1.7. The block diagram for a typical pulsed radar installation

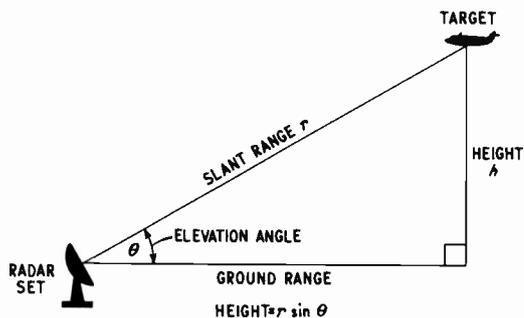


Fig. 1.6. Calculation of height from slant range and elevation information

a crystal detector and then applied as video information to the indicator display. The i.f. is typically 45MHz and these amplifiers are similar to those used in a television receiver.

On receive, the target information, aerial bearing, and elevation angles, are fed to the indicator unit, which displays the range, bearing, and height of all aircraft within range. An input from the timing circuit ensures that the c.r.t. can be synchronised to the transmitter p.r.f.

FACTORS AFFECTING PERFORMANCE

Each parameter of the radar will affect its maximum range and resolution; some are within the control of the designer and some remain the operator's responsibility. The designer can choose an aerial, receiver gain, transmitter power, p.r.f., pulse width, and display consistent with the application, while the operator may have to choose the location for transportable equipment. This must be sited so that it is not shielded by hills or tall buildings, and is well away from man-made electrical interference.

Some other interfering factors, such as target size and sea or weather conditions, may be beyond the control

of both designer and operator. These are as follows:

(a) *P.R.F.* The interval between transmitted pulses must be long enough for the pulse to reach a target at maximum range and return to the receiver, since if a second pulse is transmitted before the first has returned, the reflected pulse may be lost or at best, if displayed on the c.r.t. after the second pulse has been transmitted, could cause confusion to the operator.

To avoid this problem the radar p.r.f. is chosen so that there is ample time for a pulse to be reflected from a target at the maximum range of interest before a second pulse is transmitted. The sweep speed of the display is chosen so that only the range of interest is indicated.

A long range early warning search radar would have a low p.r.f. while an airfield local radar, with a maximum range of perhaps 10 miles, could have a high p.r.f. If the p.r.f. is made too low then the amount of information presented per second on an "A" scope or a p.p.i. is low, and performance will suffer.


This problem with a low p.r.f. may be partly overcome by using a storage tube display rather than p.p.i. In this system information is read on to the storage tube at the p.r.f. but retrieved by scanning at a faster rate and displaying the information on a conventional television type of tube.

(b) *PULSE WIDTH.* The pulse width affects two things, the minimum range and the resolution of the radar. Range measurement on an "A" scope is made from the leading edge of the transmitted pulse to the leading edge of the received pulse, if an object is so close that the echo pulse is received before the end of the transmitted pulse then it is impossible to interpolate the range on the screen.

If the transmitter has a pulse width of, say, $12\mu\text{s}$ then for a target at 1 mile the start of the echo signal would be received before the end of the transmitted pulse, Fig. 1.8a, and range cannot be measured. For a target at 1.5 miles the start of the echo pulse would be received shortly after the end of the transmitted pulse, Fig. 1.8b; in this case range can be measured.

In practice, pulse widths are normally shorter than the $12\mu\text{s}$ chosen for this example; $1\mu\text{s}$ is more common.

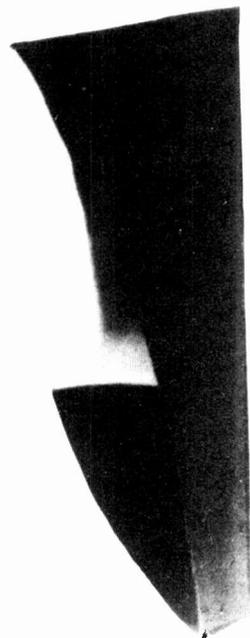2Watt and 3Watt Professional IC Audio Amplifiers now available



These Plessey general purpose integrated circuit audio amplifiers are being used by a number of major equipment manufacturers throughout the country.

Through large scale production Plessey can now make these devices available to home constructors at reasonable prices.

Each circuit incorporates a preamplifier and a class A-B power amplifier stage and needs only a minimum of external components.

Take a look at these specifications opposite!
These really outstanding Plessey IC audio amplifiers are immediately available off-the-shelf together with data/application brochures (Price 1s. 9d. each) which include PC board layouts for mono and stereo. Obtainable from:

Characteristic
Output power r.m.s.

Input impedance

Preamplifier
Main amplifier

Distortion

Preamplifier
Main amplifier

Frequency response

Lower—3dB point
Upper—3dB point

Operating voltage

Min. operating load

SL402A
2W

20 M Ω
100 M Ω

0.1%
0.3%

20 Hz
30 kHz

- 14 V

7.5 Ω

SL403A
3W

20 M Ω
100 M Ω

0.1%
0.3%

20 Hz
30 kHz

+ 18 V

7.5 Ω

Farnell Electronic Components Ltd
Canal Rd, Leeds LS12 2TU
Tel: Leeds 636311 Telex: 55147

SDS (Portsmouth) Ltd
Hillsea Industrial Estate, Hillsea, Portsmouth, Hants.
Tel: Portsmouth (0793) 62332 or 62180 Telex: 86114



PLESSEY microelectronics

Cheney Manor Swindon Wiltshire England Telephone: Swindon (0793) 6251. Telex: 44375

VARIABLE VOLTAGE TRANSFORMERS



INPUT 230/240v. A.C. 50/60—
OUTPUT VARIABLE 0-260v.

BRAND NEW
Keenest prices in the country.
All Types (and Spares) from
½ to 50 amp. from stock.

SHROUDED TYPE
1 amp, £5. 10. 0. 2.5 amps,
£6. 15. 0. 5 amps, £9. 15. 0.
8 amps, £14. 10. 0. 10 amps,
£18. 10. 0. 12 amps, £21. 0. 0.
15 amps, £25. 0. 0. 20 amps,
£37. 0. 0. 37.5 amps, £72. 0. 0.
50 amps, £92. 0. 0.



OPEN TYPE (Panel Mounting)
½ amp, £3.10.0. 1 amp, £5.10.0. 2½ amps, £6.12.6.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250v. A.C. operation.

EXPERIMENTERS' ECONOMY KIT
1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £5.5.0 plus 5/- P. & P.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor 1-80 f.p.s. Price 9 gns. 7/6 P. & P.

HY-LIGHT STROBE
This strobe has been designed and produced in response to wide public demand, for use in large rooms, halls and the photographic field. It has four times the light output at 30 f.p.s. and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Light output approx. 4 joules. Price £10.17.6. P. & P. 7/6.

7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 10/6. P. & P. 2/6 or Post Paid with kits.
Several types of Flash Tubes available from stock.

100 WATT POWER RHEOSTATS (NEW)

AVAILABLE IN THE FOLLOWING VALUES:
1 ohm, 10 a.; 5 ohm, 4.7 a.; 10 ohm, 3 a.;
25 ohm, 2 a.; 50 ohm, 1.4 a.; 100 ohm, 1 a.;
250 ohm, .7 a.; 500 ohm, .45 a.; 1 Kohm,
280 mA.; 1.5 Kohm, 230 mA.; 2.5 Kohm, 2 a.; 5 Kohm, 140
mA. Diameter 3½ in. Shaft length ¾ in., dia. ¼ in. All at 27/6
each. P. & P. 1/6.

50 WATT. 1/5/10/25/50/100/250/500/11/1/5/2/5/5 Kohm.
All at 21/- each. P. & P. 1/6.
25 WATT. 10/25/50/100/250/500/11/1/5/2/5 Kohm. All
at 14/6 each. P. & P. 1/6.

**VEEDER ROOT, 230V a.c. 50 cycle. 5-figure
counter (non-retractable).** 18/6. P. & P. 1/6.

MOTORIZED SWITCHING UNIT (EX-W.D.)
Powerful precision made Ex-W.D.
12V D.C. reversible motor, drives
multiple gear train with output
approx. 4 r.p.m. and 5 r.p.m.
Price 25/- Plus 4/6 P. & P.

EX-W.D. MINIATURE BLOWER UNIT
18-24V operation, overall length 3½"
blower 2½" by 2½". Price 20/- Plus
2/6 P. & P.

**PARVALUX TYPE SD19 230/250 VOLTS A.C.
REVERSIBLE GEARED MOTOR**
30 r.p.m. 40lb. ins. Position of drive
spindle adjustable to 3 different angles.
Mounted on substantial cast aluminium
base. Ex-equipment. Tested and in first
class running order. A really powerful
motor offered at a fraction of makers'
price. 6 GNS. P. & P. 10/-.

**R.C.A. Plastic Triac 400 PIV 8 amp. Price 25/6 R.C.A. Diac
for above, price 6/-.** Prices include data sheet and circuit.
G.E. P.U.T. D13 T1. 12/-. Texas F.E.T. 2N3819 7/6.

New plastic thyristor 400 PIV 8 amp, 18/6 incl. data sheet.
All above prices plus 1/6 P. & P.

VAN DE GRAAF ELECTROSTATIC GENERATOR
230V A.C. giving a potential of approx. 50,000V.
complete including accessories for carrying out a
number of interesting experiments, and full
instructions. This instrument is completely
safe, and ideally suited for School demonstra-
tions. Price £7.7.0, plus 4/- P. & P. L't. on req.

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cad-
mium Sulphide Photocell, Relay,
Transistor and Circuit, etc., 6-12
volt D.C. op. price 25/- plus 2/6
P. & P. ORP 12 including circuit,
10/6 each, plus 1/- P. & P.
A.C. MAINS MODEL. Incorporates
Mains Transformer, Rectifier and special
relay with 2.5 amp mains c/o contacts.
Price inc. circuit 47/6 plus 2/6 P. & P.

**LIGHT SOURCE AND PHOTO
CELL MOUNTING**
Precision engineered
light source with focusible
lens assembly and ventilated
lamp housing, to take MBC bulb. Separate
photo cell mounting assembly for ORP. 12
or similar cell. Both units are single hole
fixing. Price per pair £2.15.0. P. & P. 3/6.

RELAYS

New SIEMENS, PLESSEY, etc. mini-
ature relays at **COMPETITIVE PRICES**

Coil Ω	Working d.c. Volts	Contacts	Price
170	9-12	4 c/o H.D.	14/6
170	9-12	3 c/o + 1 H.D. c/o	12/6
280	6-12	2 c/o	1.8 14/6
700	12-24	2 c/o	1.8 12/6
700	16-24	4 c/o	1.8 15/6
700	16-24	4M 2B	1.8 12/6
2500	30-50	2 c/o H.D.	1.8 12/6
9000	40-70	2 c/o	1.8 10/-

H.D. Heavy Duty. **POST PAID**
I.B. = Including Base

MINIATURE RELAYS
9-12 volt d.c. 2 c/o 500 M.A. contacts.
Size 1 x ½ x ¾ in. Price 11/6 post paid.
30-36 v. d.c. 2 c/o 500 M.A. contacts. 3,200
ohm coil. Size 1 x ¾ x 1½ in. 8/6. Post paid.

230 VOLT AC RELAY LONDEX 4 c/o

3 amp contacts. 18/6 inc. base, post paid.

RING TRANSFORMER

Functional Versatile
Educational
This multi-purpose Auto
Transformer, with large
centre aperture, can be
used as a Double wound
current Transformer, Auto Transformer,
H.T. or L.T. Transformer, by simply hand
winding the required number of turns
through the centre opening. E.g. Using the
RT. 100 V.A. Model the output could be
wound to give 8V. @ 12amp, or 4V. @ 25amp,
or 2V. @ 50amp, etc.
Price: RT. 100VA 3.18 turns per volt, £2.5.0 +
3/6 p. and p. RT. 300VA 2.27 turns per volt,
£4.4.0 + 5/6 p. and p. RT. 1KV.A 1.82 turns per
volt, £6.10.0 + 6/6 p. and p.

SANWA MULTI RANGE METERS

New Model U50D Multi tester,
20,000 OPV, mirror scaled with overload
protection. Ranges—d.c. volts: 100mV,
0-5V, 5V, 250V, 1,000V; a.c. volts:
2-5V, 10V, 50V, 250V, 1,000V; d.c.
current: 5mA, 0-5MA, 5MA, 50MA,
250MA. Complete with battery and test
probe. £7.5.0 post paid.

34R SILICON SOLAR CELL

4 x 5 volt unit series
connected, output
up to 2V at 20mA
in sunlight, 30 times
the efficiency of selenium. 45/-, P. & P. 1/6.

LT TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price	Car.
1	30, 32, 34, 36V at 5A	£4.13.6	6/6
2	30, 40, 50V at 5A	£6.17.6	6/6
3	10, 17, 18V at 10A	£4.19.0	4/6
4	6, 12V at 20A	£6.8.9	6/6
5	17, 18, 20V at 20A	£7.5.9	6/6
6	6, 12, 20V at 20A	£6.17.6	7/6
7	24V at 10A	£5.4.6	5/6
8	4, 6, 24, 32V at 12A	£7.3.0	6/6

TRANSISTOR AUDIO AND RADIO CIRCUITS

for Radio Receivers, Radiograms, Record
Players, Tape Recorders and Hi-Fi Equip-
ment.

A Mullard Publication

30/- Postage 1/-

**PRACTICAL INTEGRATED CIR-
CUITS**, by A. J. McEvoy & L. McNamara.
18/- Postage 1/-.

**SCOPING WITH THE OSCILLO-
SCOPE**, by Gordon J. King. 28/- Postage
1/-.

**QUESTIONS AND ANSWERS
TRANSISTORS**, by Clement Brown. 10/-
Postage 6d.

COLOUR TELEVISION PAL SYSTEM,
by G. N. Patchett. 40/- Postage 1/-.

**RADIO COMMUNICATION HAND-
BOOK**, by Radio Society of Great Britain.
63/- Postage 4/6.

**TRANSISTOR SUBSTITUTION
HANDBOOK No. 9**, 18/- Postage 1/-.

S.C.R. MANUAL, by the General Electric
Company. 25/- Postage 1/6.

TRANSISTOR MANUAL, by the
General Electric Company. 21/- Postage 1/6.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
**19-21 PRAED STREET
LONDON, W.2**
Phone: PADDINGTON 4185
Closed Saturday 1 p.m.

NEW RANGE U.H.F. T/V AERIALS

All U.H.F. aerials now fitted with tilting bracket
and 4 element grid reflectors.

Loft Mounting Arrays: 7 element, 37/6.
11 element, 45/-; 14 element, 52/6. 18 element,
60/-; **Wall Mounting with Cranked Arm:**
7 element, 60/-; 11 element, 67/-; 14 element,
75/-; 18 element, 82/6. **Mast Mounting with**
2in. clamp. 7 element, 42/6; 11 element, 55/-;
14 element, 62/-; 18 element, 70/-; **Chimney
Mounting Arrays:** Complete, 7 element,
72/6; 11 element, 80/-; 14 element, 87/6; 18 element,
95/-; Complete assembly instructions with every
unit. **Low Loss Cable, 1/6 yd. U.H.F. Pre-
amps from 75/-.** State clearly channel number
required on all orders.

BBC · ITV AERIALS

BBC (Band 1). Telescopic
loft, 25/-; External S/D, 30/-;
"H", £2.15.0.
ITV (Band 3). 3 element loft
array, 30/-; 5 element, 40/-;
7 element, 50/-; Wall mounting,
3 element, 47/6; 5 element, 52/6.
Combined BBC/ITV. Loft
1+3, 30/-; 1+5, 50/-; 1+7,
60/-; Wall mounting 1+3, 57/6;
1+5, 67/6; Chimney 1+3, 67/6;
1+5, 75/-;
VHF transistor pre-amps,
75/-.

COMBINED BBC1-ITV-BBC2 AERIALS
1+3+5, 70/-; 1+5+9, 80/-; 1+5+14, 90/-;
1+7+14, 100/-; Loft mounting only. Special
leaflet available.

F.M. (Band 2). Loft S/D, 15/-; "H", 32/6, 3
element, 55/-; External units available. Co-ax.
cable, 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-.
Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D.
P. & P. 6/-. Send 6d. stamps for illustrated lists.

CALLERS WELCOME
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS (Dept. P.E.)
40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space
Dept. P.E. 57 BRIDGMAN ROAD, LONDON, W.4
SHOWROOM NOW OPEN CLOSED SATURDAY Phone 995 1560
Personal callers only
9 LITTLE NEWPORT ST.
LONDON, W.C.2. Tel. GER 0576

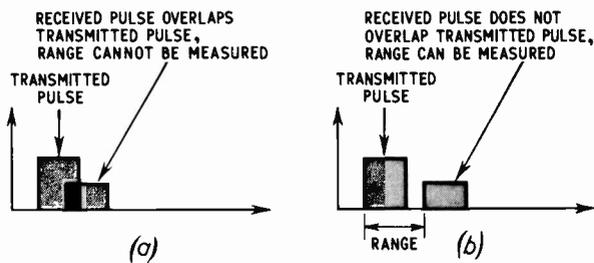


Fig. 1.8. Minimum range depends on pulse width

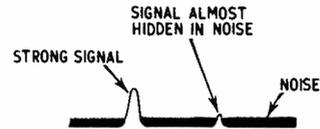


Fig. 1.9. The appearance of noise on an "A" scope

Even this is too long for some airborne interception applications since this represents a range of about 500ft.

If two targets in a direct line from the aerial are only separated by a short distance, then the front edge of the signal reflected by the furthest target will be combined with the trailing edge of the signal from the nearest target, and a "single" target indication would appear on the screen.

For very close ranges or for a high resolution, pulse widths of 0.1μs may have to be used. However, for a given peak amplitude a long pulse contains more energy than a short pulse, so that the short pulse requirements for a high resolution may have to be weighed against the maximum energy requirements for a long range.

(c) **TRANSMITTER POWER AND RECEIVER NOISE.** The maximum range of the radar will be limited by the ability of the receiver to detect the weakest echoes in the presence of noise. This noise input to the receiver is made up from atmospheric disturbance and thermal agitation in the receiver input stages. On an "A" scope display, the noise looks like "grass" which may hide the weak echoes, Fig. 1.9. The input to the receiver consists of signals plus noise in a specific ratio, and due to the extra noise contributed by the receiver itself, the signal to noise ratio at the output is smaller than the signal to noise ratio of the input signal.

The noise figure *N* of the receiver is defined as the ratio of "signal-to-noise ratio at the input" divided by "signal-to-noise ratio at the output". If the receiver were perfect and contributed no noise of its own, then this ratio would be 1 or 0dB. Since the receiver does contribute some noise power, then the noise figure may be 10dB at X-band unless special low noise techniques are used.

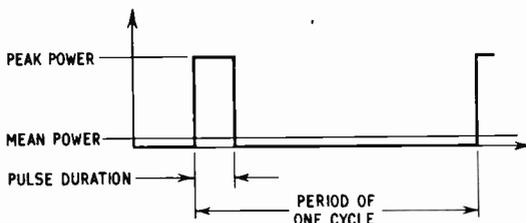


Fig. 1.10. The relationship between peak and mean power

Since the transmitter may have a pulse duration of 1μs and a p.r.f. of 1kHz the mean power developed may be low, while the peak power (which determines the strength of the echo signals) may be very high. So that the mean power ratings of the transmitter components can be lower than might be expected at first sight. One cycle of operation is shown in Fig. 1.10, where the power output remains at the peak level for only a small part of the complete cycle.

If the peak power is 100kW, the pulse width 1μs, and the p.r.f. 1kHz (1ms duration) then the mean power is given by:

$$\text{mean power} = \frac{\text{peak power}}{\text{duty cycle}} = \frac{100 \times 10^3}{1,000} = 100 \text{ watts.}$$

(d) **THE RADAR EQUATION AND MAXIMUM RANGE.** By considering the transmitter power, the gain of the directive aerial, and the effective radar cross-sectional area of the target, the maximum radar range can be determined.

$$R_{\text{max}} = \left[\frac{P_t G^2 \lambda^2 \sigma}{(4\pi)^3 S_{\text{min}}} \right]^{1/4}$$

where:

- P_t = transmitter power
- R_{max} = maximum detectable range
- G = aerial gain, using the same aerial for transmission and reception
- λ = wavelength
- σ = radar cross-section of the target
- S_{min} = minimum detectable signal.

This simplified version of the radar equation can only be used as a guide to expected performance since many factors, atmospheric conditions for example, have been omitted. It is difficult to make generalisations about performance from this equation alone since all the parameters are interdependent in a practical system.

However it can be seen that the maximum range is proportional to the fourth root of transmitter power, so that sixteen times the power is required to obtain twice the range. It may prove easier to improve the minimum detectable signal value by using low noise receiver techniques rather than attempt to increase the transmitter power.

Alternatively the maximum range is proportional to the square root of aerial gain, so that only four times the aerial gain will double the range.

Part of the art of system design consists of optimising conflicting parameters to achieve a required performance within a given size, weight, and complexity requirement.

To be continued

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

FLASH TUBES

Readers who like to construct their own photographic equipment will find the range of CD xenon filled flash tubes available from **W.E.L. Components Ltd.**, suitable for electronic flash gun construction experiments.

Three basic tubes are made. The CD10 is U shaped with wire ends and a light output rating of 50 joules. The tube operates from 500V but requires a minimum trigger voltage of 2kV. The maximum recycling time is 10 seconds.

The CD11 is similar to the CD10 but is mounted on an octal base. The CD14 uses the same xenon tube mounted on an octal base but incorporates a pulse transformer and integral reflector. Pulse transformers type PT56 are recommended for use with types CD10 and 11.

Further data, including an applications report giving details of a 50-joule flash unit, is available from **W.E.L. Components Ltd.**, 5 Lovelock Road, Reading. A small charge is made for posting and packing.

BATTERY TESTER

One of the many new ranges of **Eagle** products announced recently is a battery condition test meter type BT-15. The meter will test the condition of 1.5V to 90V dry cell batteries on load in 15 switched ranges.

On the switched ranges for 1.5V, 4.5V and 9V batteries there is a high and low position, which shows the battery condition for high and low current drain.

The meter scale is divided into three segments which read "replace" for less than 50 per cent efficiency; "useable" for between 50 and 80 per cent efficiency; and "good" for 80 to 100 per cent efficiency.

The BT-15 battery tester costs £9 and is housed in a plastics case, similar in appearance to a multimeter.

RESISTANCE BRIDGE

A robust general purpose bridge, type PW3, for d.c. resistance measurements with a range from 0.001 ohm to 10 Megohm is the latest product from **Croydon Precision Instruments**.


A transistor inverter, powered by seven 1½V dry cells, automatically

supplies the correct voltage for the bridge according to the range selected. The four measuring controls are connected in a form of Kelvin Varley potential divider network and a seven position range selection switch, for values of up to 1,000, 100, 10, 1, 0.1, 0.01 and 0.001, also incorporates a battery check position.

Under all conditions of measurement there is never less than 5,000 ohms in series with the galvanometer and Rx terminals. This gives a certain amount of protection to the meter when the battery key is opened while measuring the resistance of inductive circuits.

Another claimed feature of the bridge is that it has a true zero irrespective of range setting. There are no switch contacts in series with Rx, so eliminating any resistance variations due to contact resistances.

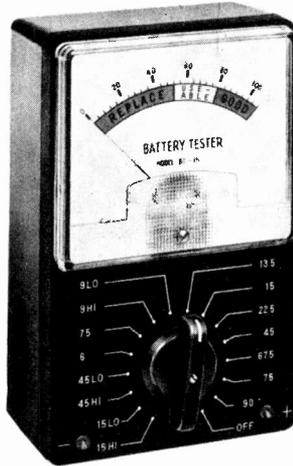The PW3 bridge is housed in an attaché style case and full details and cost can be obtained from **Croydon Precision Instruments Co.**, Hampton Road, Croydon, CR9 2RU.




Eagle Products battery tester



PW3 Resistance Bridge marketed by Croydon Precision Instruments

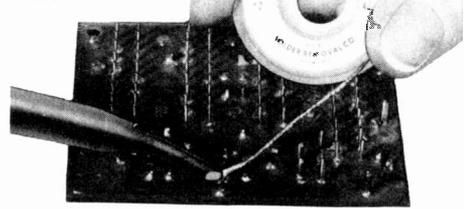Soder Wick from Southern Watch and Clock Supplies



DESOLDERING

Most desoldering products on the market consist of special soldering iron attachments and work on vacuum suction for removing solder. The "Soder Wick" from **Southern Watch and Clock Supplies**, is different in that it acts like "blotting paper" when applied to molten solder.

The joint to be desoldered is heated by any standard iron and as soon as the solder begins to melt the wick is applied directly to the joint, drawing the solder into itself. It is claimed that this method avoids any excessive heating and leaves the joint completely clean and ready for resoldering.

The wick, available in varying widths, can be used for all types of solder connections, from integrated circuits and printed circuit boards to electrical appliances or complex electrical apparatus.

The solder wick is supplied in 1½in plastics containers and there is approximately 60in of wick. Prices range from 18s to 20s per reel, according to width.

Further details can be obtained from **Southern Watch and Clock Supplies, Ltd.**, Industrial Tools Division, 48-56 High Street, Orpington, Kent.

LITERATURE

To save unnecessary costs and wastage, the **Mullard Technical Handbook** is now being issued as a series of three volumes. Each book deals with a particular section of Mullard manufactured components and is divided into several parts or chapters. The first part contains details of semiconductor and integrated circuit devices and is divided into six parts. The second contains five parts dealing with valves and tubes.

The final book deals with components and materials and is divided into three parts covering electrical components, ferrite, PXE, permanent magnets, and ferroxcube inductor cores.

As only certain sections will be of interest, according to particular requirements, each of the 14 parts can be purchased separately at 12s each, post free.

Further details and orders for the handbook should be addressed to **Central Technical Services, Mullard Ltd.**, Mullard House, Torrington Place, London, W.C.1.

4! brings you a mountain of components at manufacturers' prices

The serious amateur should never be without this comprehensive price list and guide to semiconductors and electronic components from RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold and others (together with manufacturers' application data) which you can buy direct from us at *manufacturers' prices* e.g. IN914 **1/3d.**

- IN916 **1/11d.** □ 2N697 **4/5d.** □ 2N706 **2/3d.** □ 2N706A **2/9d.** □ 2N929 **5/8d.**
- 2N1613 **4/8d.** □ 2N3011 **9/1d.** □ 2N3053 **6/2d.** □ 2N3053 **15/9d.** □ 3N140 **15/3d.** □ BFY50 **4/8d.** □ BFY51 **3/9d.** □ BSY27 **18/-** □ BSY95A **3/3d.** □ C407 **4/6d.** □ CA3012 **18/3d.** □ CA3014 **25/6d.** □ CA3020 **25/9d.** □ OA200 **1/9d.** □ OA202 **1/11d.**



Build the NEW Mainline Audio Amplifier kits - UP TO 70 WATTS

The result of the combined resources of SGS and RCA, these quasi circuits set new standards in quality and performance. Each kit is complete with circuit diagram, all semiconductors, resistors, capacitors and printed circuit board.

12A	£7. 0. 0.
25A	£8. 5. 0.
40A	£9. 0. 0.
70A	£10.10. 0.

Any two will make an outstanding stereo equipment.



To: Mainline Electronics Limited, Thames Avenue, Windsor, Berkshire

I enclose 4/-. Please send me your price list and guide

I am interested in Amp Mainline Audio Amplifier Kits. Please send me full data

I am interested in receiving data on preamplifier & power supply kits

NAME _____ ADDRESS _____

(A member of the ECS Group of Companies)

PE 270



Stentorian
**HIGH FIDELITY
SPEAKERS**
As used in the
**'Alan Douglas
Electronic Organ'**
featured in
this issue

Whiteley Stentorian Speakers incorporate 40 years of development in acoustic technology. Their frequency response is exceptionally wide, and their overall performance is outstanding. Few speakers can equal, and none can excel the superb reproduction of the high fidelity speakers in the Whiteley Stentorian range.



MODEL H.F.1016 MAJOR

10" Die-Cast Unit, incorporating 16,000 gauss magnet system and has a 15 ohms impedance speech coil. Handling capacity 10 watts. Frequency response 30-16,000 c.p.s. Bass resonance 39 c.p.s.



MODEL H.F.1012

10" Die-Cast Unit, incorporating 12,000 gauss magnet. Handling capacity 10 watts. Frequency response 30 c.p.s. to 14,000 c.p.s. Bass resonance 35 c.p.s. Fitted with cambric cone and universal impedance speech coil providing instantaneous matching at 3, 7.5 and 15 ohms.

Ask your dealer for full details of the Stentorian range or write to

WHITELEY ELECTRICAL RADIO CO. LTD


MANSFIELD · NOTTS · ENGLAND Tel: Mansfield 1762/5
London Office: 109 KINGSWAY, W.C.2 Tel: HOLborn 3074

FERRANTI
SEMICONDUCTORS

are specified by
PRACTICAL ELECTRONICS
for their
ELECTRONIC ORGAN

Supplies are available from
these FERRANTI Distributors:

- SOUTH** EDMUNDSONS ELECTRONICS LIMITED,
60-74 Market Parade, Rye Lane, Peckham,
LONDON S.E.15.
Tel: 01-639 9731. Telex: 887212.
- SEMICOMPS LIMITED,
Station Wharf Works, ALPERTON, Middlesex.
Tel: 01-903 3161. Telex: 935243.
- WEL COMPONENTS LIMITED,
5 Loverock Road, READING, Berks.
Tel: 0734-40616/9. Telex: 84529.
- MIDLANDS** COVENTRY FACTORS LIMITED,
Coronet House, Upper Well St., COVENTRY.
Tel: 0203 21051.
- SWIFT-HARDMANS ELECTRONIC AND
AUTOMATION DISTRIBUTORS,
Swift House, Hanley, STOKE-ON-TRENT.
Tel: 0782-24531. Telex: 36297.
- NORTH** SWIFT-HARDMANS ELECTRONIC AND
AUTOMATION DISTRIBUTORS,
P.O. Box 23, Hardale House, Baillie Street,
ROCHDALE, Lancs.
Tel: 0706-47411. Telex: 63237.
- SCOTLAND** SEMICOMPS NORTHERN LIMITED,
44 The Square, KELSO, Roxburghshire.
Tel: 2366-7/2369. Telex: 72192.

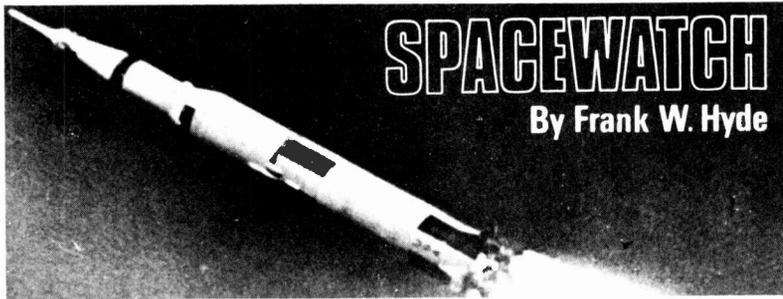

INTELSTAT IV

The largest communications satellite in the world is due to be launched in 1971. It has been designed for world wide communications and will be placed in a geostationary orbit at 22,300 miles above the earth. Almost 18ft high and 8ft in diameter, it will be capable of a number of combinations of voice and video transmissions. For example, it could carry 12 colour TV broadcasts or 6,000 two-way telephone conversations.

Intelstat, the International Telecommunications Satellite Consortium, owns the earlier Intelstat satellites which have already linked the countries of the world in a global communications service. There are now some 69 member countries of Intelstat. They jointly own the satellites but the terminals and land distribution systems are the property of the member governments or of private enterprise in the countries where they are installed.

The new generation of satellites for Intelstat described above will be built by the Hughes Aircraft Corporation of California. Of the four satellites to be built under this contract, two will be assembled in Europe by the British Aircraft Corporation, and then shipped to California for final testing.

POSITION FIXING BY SATELLITE

A system that can locate ships within five nautical miles has been developed by G.E.C. of America. Such an accuracy is as high as any system in use at the moment. If applied to the location of aircraft it would help to fit them into the airspace available with great precision and cut down congestion at the airports. Applied to ships it could be used where crowded harbours are involved with small and large vessels.

The NASA Applications Technology satellites I and II have been used for this purpose. A ground station sends out coded signals which are relayed by either of the pair of satellites. Coded signals are returned to the ground station from the vessel or aircraft taking part in the same way. In each case two signals, one from each satellite, are monitored by a computer at the ground station.

The positions of both satellites being known accurately, the timing of the returned signals can be used to calculate the position of the craft. As the computer does this in a few seconds, the fix is very fast.

Tests made of the system showed that all sorts of vehicles could be tracked. One test included a mobile van, a coast-guard ship, and two aircraft. The system was developed by Roy A. Anderson who points out that use of a higher frequency of operation would still further increase the accuracy by the reduction of the interaction of v.h.f. signals in the ionosphere. However its wider application is assured at the moment because the majority of installations have v.h.f. as standard equipment.

PIN POINT NAVIGATION

Still another system using very low frequencies has come into use. This is the accurate navigation system developed by the US Navy, which has been named OMEGA. It is swift and efficient in operation, virtually error proof, and should be of benefit to all seafaring nations.

The system consists of eight transmitters strategically set up round the world. Four of these have already been set up and are in operation. The remainder should be completed by 1972.

OMEGA began life 18 years ago when the US Navy were seeking a more efficient system covering long distances. Three stations were set up as a first experiment. After two years of tests the Navy ordered equipment to extend its use to surface and underwater craft. Now more than half of the world can be covered by the system and two of the largest commercial ocean going liners, the *Queen Elizabeth II* and *Challenge*, have been equipped.

When the world wide system is in operation there will be transmitters in Minnesota, Hawaii, Norway, Japan, Trinidad, Australia or New Zealand, Chile or Argentina, and La Reunion Island off Madagascar. These stations will cost less than £250,000.

VERY LOW FREQUENCY

The OMEGA transmitters use a very low frequency of operation, namely 10 to 15kHz. These low frequency waves are bounced continually

between the earth and the ionosphere and enable signals to be received at distances of more than 8,000 miles from the transmitter.

The basis of the fix is a comparison between two signals. The stations will each have a power of one kilowatt fed into a four wire aerial slung across a valley or fiord. The one installed at Bratland, Norway, spans 11,000ft across and has a mid-height of 1,435ft. The aerial at Trinidad spans 4,800ft and the midspan height is 800ft. The signal is continuously pulsed for one second out of ten seconds. Only one station transmits a given frequency at a given time. The pulses from each station differ slightly in length for identification purposes and the stations are synchronised by the use of "atomic" clocks. It is not expected that phase drift will exceed more than one micro-second per day.

There is a direct read-out on the front of the receiver and the time for a fix is about one minute. It is reported that underwater vessels down to 50ft can use the system.

THE RE-ENTRY BLACKOUT

The radio blackout that accompanies the entry of the space craft into the earth's atmosphere has been given some close attention. The radio silence lasts some four minutes and could be vital. In the event of space shuttles this period could be as long as 15 minutes. The Air Force Cambridge Research Laboratories at Hanscom Field, Massachusetts, are experimenting with a possible solution to the problem.

The plasma sheath formed by the ionised gas around the re-entry vehicle needs de-activation so that its transparency to radio waves may be accomplished. Past attempts have not been very successful. The Air Force Laboratories approach was an attempt to "mop up" as it were the free electrons with water or some other chemical sprayed out of the spacecraft. This was not satisfactory but an alternative and more novel approach is being tried.

If the plasma sheath could be raised to an even higher energy level it could result in the combination of the free electrons with the ions faster than they were disassociating. The reduction of the density of the electrons would allow the radio communication to continue.

The condition required can be accomplished by radiating r.f. power into the plasma sheath from the spacecraft. It was found that 20 watts of r.f. at 7MHz could neutralise the plasma. Experiments are being carried using this method backed up by spray methods using sulphur hexafluoride which absorbs more electrons. A space test was arranged to test the scheme under *Apollo* entry conditions. Doubtless the system will be incorporated in an early mission.

PE ORGAN PART 10

By Alan Douglas, Sen. Mem. I.E.E.E.

As we know, the manual voices of this organ are applied to one loudspeaker, the pedal tones to another. These units are external to the console, as this is the only way in which the sound can be properly heard.

CHOICE OF SPEAKERS

It is constantly claimed by loudspeaker manufacturers that their products reproduce everything equally well. This is no doubt largely true, but they do not all do it in the same way. Consequently we must accept the fact that loudspeakers have a voice of their own, and the use of "A" will not necessarily produce the same sound as the use of "B".

This factor assumes even greater importance with an organ, the power versus frequency distribution of which is quite different from broadcast programme music. Therefore we must decide on a specific type of loudspeaker and balance things up to suit this.

The organ was voiced on the WB.HF1214 for the manuals and the WB.HF1016 for the pedals. These were selected after comparative voicing tests with other loudspeakers.

ENCLOSURE CONSTRUCTION

The two loudspeakers are housed in a cabinet which makes the most of the space whilst completely separating the channels. Although of fair cubic capacity, it only occupies 24in by 15in floor space, and this is not thought excessive for an organ. Fig. 10.1 shows the principal details of the enclosure, which is constructed from $\frac{3}{4}$ in chipboard, which is cheap and very suitable acoustically as it is almost dead.

The box is divided as shown by a hardboard panel, the curvature and the small width making it quite rigid. At the one possible point of flexure, a 1in dowel is secured to prevent vibration.

SPEAKER POSITIONS

The upper loudspeaker is the manual one, HF.1214. This faces upwards, eliminating any noise. It speaks into the Leslie type rotor but the back wave is also used (unlike the usual concept) and this issues from a small slot just above the floor. It is very important that the battens supporting the box should allow about a 2in gap here.

The underside of the $\frac{3}{4}$ in chipboard mounting panel and the top 12in of the baffle have thick felt glued on—just a drop of glue at the corners, otherwise the absorbing power of the felt will be reduced.

The lower or pedal loudspeaker, HF.1016, is near the floor and faces outwards but away from the player. It has a vent equal to the cone area near the top of the box, and again felt is used behind this unit for 12in up the baffle and on the panel beneath the cone. Connections are brought out to a terminal block or sockets, where convenient.

Sealing at the top of the baffle is by one of the adhesive plastic tapes and along both sides of the baffle by Sealastik, a preparation which never fully hardens. This is quite easy to do if the bottom panel is fitted last. It is most important that the whole structure is airtight, otherwise we may get a weak bass and possible interference, since there is no way of phasing the two loudspeakers. In the prototype, all panel edges were glued by Evostik resin glue type W, which makes an extremely strong joint.

To match the console, the enclosure should be finished in Arborite Superdec Sapele laminate with a contrasting black gloss laminate for the top and supports. Contact adhesive is a suitable fixative.

EFFECT OF TREMULANT

We thus have two loudspeaker cabinets in one, as it were, and the distance between the top of the manual speaker and the floor vent produces subtle changes in phase when the tremulant is working since the floor vent signal is steady but the radiation from the top of the cone is modulated by the rotor.

A further valuable feature of the rotating device is that the sound appears to come from a much larger area than that of the loudspeaker cone, thus completely avoiding the "point source" effect, which is so undesirable in an organ.

Many instruments have two speeds for the rotor, but there are mechanical difficulties and, in general, one speed is quite acceptable. This rotor revolves at 360 r.p.m., and is driven by a standard tape recorder capstan motor.

ROTOR ASSEMBLY

To ensure easy starting the rotor is made from $\frac{1}{8}$ in thick balsa wood, and bent to the shape shown in Fig. 10.1 by steaming and careful shaping. This material is obtainable from any model aircraft shop.

The top, to which the rotor edge is glued, is made from $\frac{1}{4}$ in plywood with a centre hole of $\frac{3}{8}$ in diameter to take a Meccano spindle. To help in setting the rotor curtain, a rubber band can be fixed round it while the glue dries. The underside of the top plate is lined with typewriter felt glued on, which prevents vibration which at certain frequencies could cause spindle chatter.

To minimise acoustic cut-off and provide stiffness, we use a piece of $\frac{3}{8}$ in by $\frac{1}{8}$ in wall alloy angle to support the lower end of the spindle. This is shown in the figure and is held onto the top panel by two screws at each side.

The bottom bearing for the spindle is made from a little block of nylon, drilled halfway through. Note that this material tends to close in after drilling, so the drill must be larger than the spindle. Screw the block onto the angle with two 6B.A. screws tapped into the metal.

The upper mounting for the spindle is exactly the same, but of course the bearing hole is drilled right

LOUDSPEAKER & FINAL TUNING

through. Make the hole in the metal somewhat larger, so that the spindle cannot rub on it.

The top angle is supported from the speaker mounting board by two pieces of 1in dowel, glued and screwed into holes cut in the speaker support.

Now the rotor should spin round with the greatest ease and no noise. A trace of graphite where the spindle passes through the top bearing may be advantageous.

MOUNTING THE MOTOR

Hysteresis motors of the type specified hum or vibrate to some extent under load, due to magnetic slip. Therefore we must mount the motor on rubber. There are many ways of doing this, but two simple strips of foam rubber as in the figure will do very well.

These, as can be seen, are again mounted on two 1in dowelling pillars, to bring the height of the motor pulley in line with the spindle pulley. The diameters of these must be chosen to give the correct ratio, this depending on the actual motor speed. Such pulleys can often be standard Meccano types, held to the spindles by grub screws.

An ordinary rubber band about $\frac{1}{8}$ in wide will drive the very light rotor quite well, and to maintain the tension and align the motor spindle, we attach a light spring as shown to pull in the opposite direction. In any event, there must be no joints in the driving belt, but a metal spring type of belt is noisy. Plastic belts can be used, but are sometimes inclined to be stiff. The belt must be very flexible.



The final adjustment is for the height of the rotor above the speaker. Ideally the gap should be about $\frac{1}{16}$ in, but it may not be possible to get quite as close as this. A larger gap will not affect the higher frequencies, but will progressively reduce the lower ones. So some control over the modulation is possible.

ALL VOICES MODULATED

It is often said that only tibias and flutes can be treated by a rotating tremulant, but in fact we apply all the tonecolours in the organ and they are all effective—though naturally the lower notes are less modulated than the upper ones: but then, this is just what happens with pipes. The deepest tremulant is obtained when a re-entrant pipe enters the rotor, but this would be too much for some voices. It is felt that the arrangement outlined will suit most people.

There are other forms of Leslie device, such as rotating horns and rotating loudspeakers, but these either have special applications or are too complicated for our purpose.

As a matter of passing interest, the first rotating horn tremulant was patented by the late John Compton in 1932, but the original Doppler effect rotating paddle was in use over 100 years ago in reed organs. It was realised even then that both amplitude and frequency must cyclically change to produce the most pleasing effect.

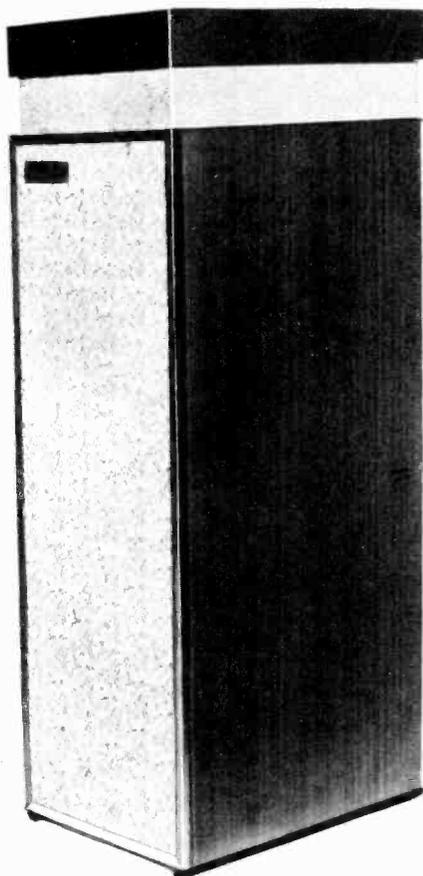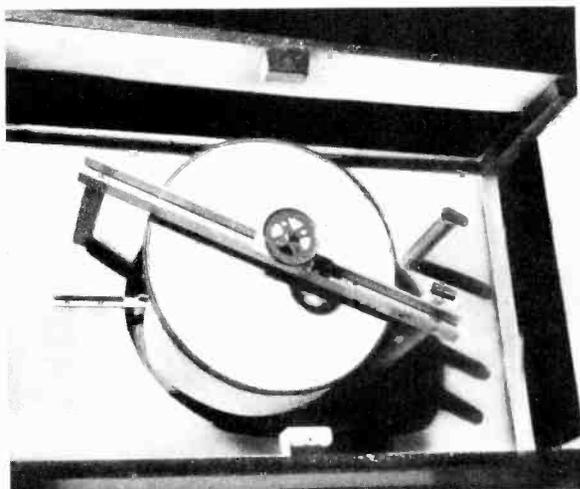

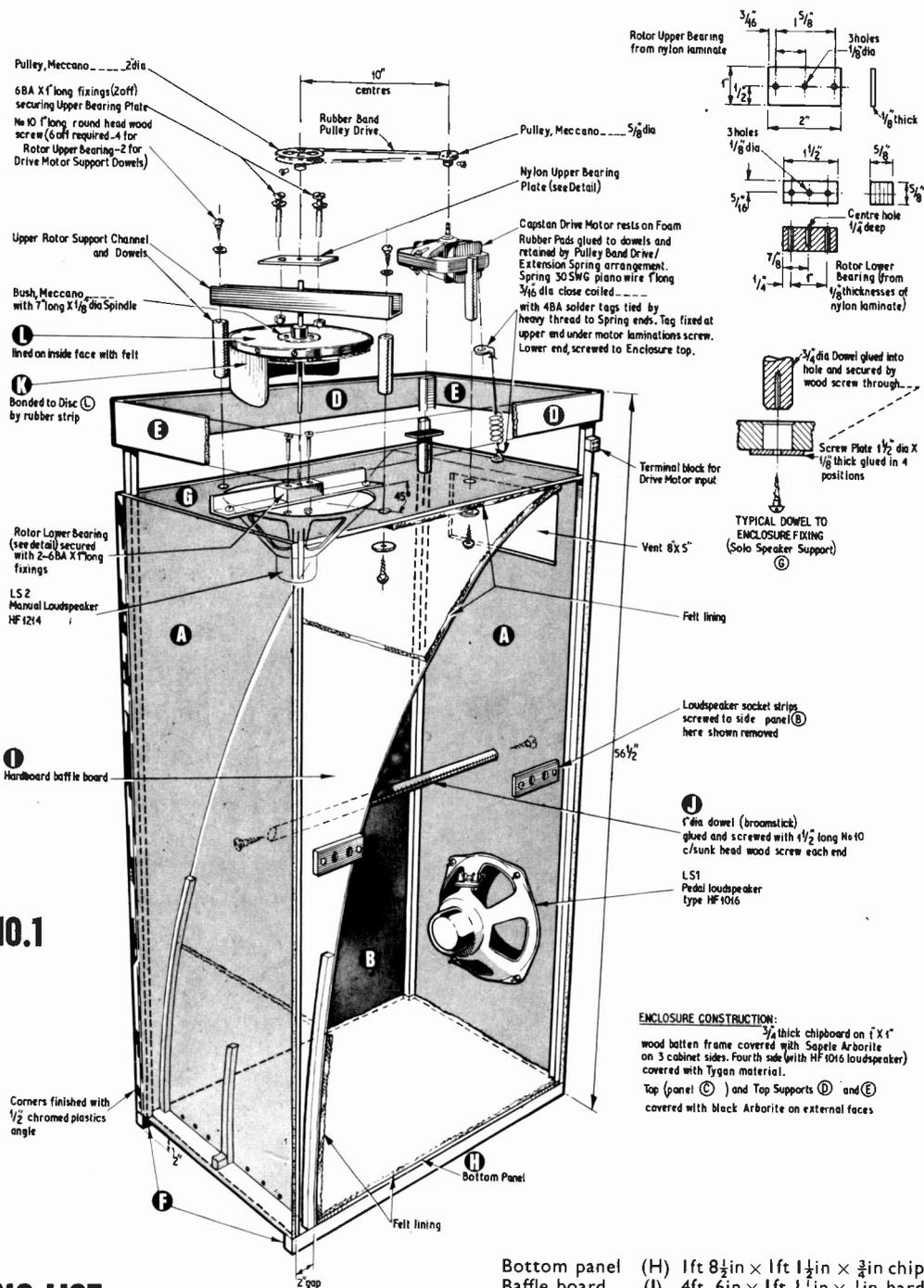


Fig. 10.1

CUTTING LIST

Enclosure			
Sides	(A)	(2 off)	3ft 1 1/2in x 1ft 1 1/2in x 3/8in chipboard
Sides	(B)	(2 off)	3ft 1 1/2in x 2ft x 3/8in chipboard
Top	(C)	(1 off)	2ft x 1ft 3in x 1/2in ply
Top supports	(D)	(2 off)	2ft x 3in x 3/8in chipboard
Top supports	(E)	(2 off)	1ft 1 1/2in x 3in x 3/8in chipboard
Feet	(F)	(2 off)	2ft x 2in x 1in hardwood
Solo speaker support	(G)	(1 off)	1ft 10 1/2in x 1ft 1 1/2in x 3/8in chipboard

Bottom panel	(H)	1ft 8 1/2in x 1ft 1 1/2in x 3/8in chipboard
Baffle board	(I)	4ft 6in x 1ft 1 1/2in x 1/8in hardboard
Baffle board dowel	(J)	1in dia. (length as required)

Rotor Assembly

Rotor baffle	(K)	18in x 4in x 1/8in balsa
Rotor top	(L)	11 1/2in x 11 1/2in x 1/4in ply
Rotor support dowels	(2 off)	5in x 1in dia.
Motor support dowels	(2 off)	4in x 1in dia.
Upper rotor support		1ft 3in x 3/8in x 3/8in duralumin channel
Lower rotor support		1ft 3in x 3/8in x 1/8in alloy angle

ENCLOSURE CONSTRUCTION:

3/4" thick chipboard on 1" x 1" wood batten frame covered with Sapelite Arborite on 3 cabinet sides. Fourth side with HF-1016 loudspeaker covered with Tygan material. Top (panel C) and Top Supports (D) and (E) covered with black Arborite on external faces.

MISCELLANEOUS PARTS

Meccano pulleys: 2in dia. (1 off); $\frac{3}{8}$ in dia. (1 off)
Meccano bush $\frac{3}{32}$ in dia. and 7in spindle to suit
Capstan drive motor 240V (1 off) (G. W. Smith & Co. Ltd)
4 way terminal block
2 way socket strip (2 off)
Foam rubber, felt lining, rotor bearing material (nylon or Perspex), plastics corner angle, spring and rubber band for motor.
Screws and nuts 6B.A. (4 off), screws, wood, No. 10 \times 1in (6 off).

POSITIONING OF ENCLOSURE

Although this organ should be completely free from hum, signal leakage or noise of any kind, it may well be that the most effective pedal sound is obtained when the pedal cone faces into a corner, about 3ft away. This perhaps will not be possible, in which case the cone should be parallel with the wall.

In small rooms, a frequency of 32Hz (wavelength 35ft) cannot be properly reflected, and if it is too near a wall some of the lower room resonances can be excited, giving rise to what appear to be changes in pitch as one moves about the room. So every effort should be made to avoid this effect by suitable placing of the unit in the room.

The worst results are always noticed in rooms of the same length, height and width, and in circular rooms.

TUNING THE ORGAN

The oscillators require careful tuning. It will be understood that as the dividers produce square waves, there will be many harmonics present, some of which are discordant. In such circumstances, if the organ is only slightly out of tune, these harmonics will beat with others.

Since the natural frequencies of the oscillators are high, it is more convenient to tune on a divider some octaves down. This is also in the range covered by the common type of tuning fork. Since one must have a standard for tuning, it is best to try and borrow a dozen forks covering the octave 261–523Hz, that is, middle C to the octave above. However, with care it is possible to tune by ear if we have one standard fork, C 261.62Hz.

TUNING PROCEDURE

In referring to the frequency chart given in Part Three, we can see that there is no top C 2ft therefore the lowest oscillator frequency starts at 4,186Hz which is the top C 4 ft.

The remaining oscillators run up to 2ft terminating at B, 7,902Hz.

The tuning capacitors listed are applied to each oscillator as shown. Note, however, that these values

B (7,902Hz)	21,600pF	F	23,200pF
A sharp	21,750pF	E	26,700pF
A	22,000pF	D sharp	27,000pF
G sharp	22,600pF	D	32,200pF
G	23,470pF	C sharp	39,190pF
F sharp	22,000pF	C (4,186Hz)	52,000pF

All polystyrene

are only approximate since the tolerances of the units used are not known exactly. Note also that the core of the Vinkers only allows a 7 per cent frequency adjustment.

These values should give a near enough approximation to the note required to allow fine tuning to commence. Again, the way the coils are wound and the tightness of the core clamp may alter some of the values shown. This is rather a tedious process, but it only has to be done once.

Having tuned middle C 261.6Hz exactly to the fork of this frequency so that no beat notes exist, hold the G above (note number 32 on the upper manual at 8ft pitch) with the tuned middle C and move the core of the G oscillator coil until there is no beat. The G is now flattened, or reduced in frequency, until there are 9 beats in 10 seconds.

With the G so tuned this is held with the D below (note number 27) and the oscillator of the latter adjusted for zero beat. This D is now flattened to produce 13 beats in 10 seconds.

Now D and A34 (note number 34 on upper manual) are adjusted for zero beat, then the A is flattened to 10 beats in 10 seconds.

This sequence is continued for A34 and E29, 15 beats. E29 and B36, 11 beats. B36 and F sharp (31), 17 beats. F sharp (31) and C sharp (26), 13 beats. C sharp (26) and G sharp (33), 9 beats. G sharp (33) and D sharp (28), 14 beats. D sharp (28) and A sharp (35), 11 beats. A sharp (35) and F30, 16 beats.

The second notes should always be flattened; the beats should never be obtained by sharpening the tuning.

If all that has gone before has been done carefully, then by holding C25 and F30, the beat rate should be 12 in 10 seconds. Very likely this will not come right the first time, but persevere until it is correct.

VOICE BALANCE AND ROOM SIZE

Readers will no doubt appreciate that electronic organs sound very different in different rooms, and this is in part due to the fact that the sound comes from a very small area, virtually a point source. Obviously this is a bad thing, since the area occupied by even the smallest assembly of pipes is some hundreds of times greater than that of the loudspeaker cones.

We have to remember also that the sound field changes with the frequency, lower notes spread out whilst higher ones concentrate more and more on the axis of the cone. All this means that the position of the loudspeaker in relation to the player will affect the balance of the sound spectrum. In fact, where extremely small rooms are concerned, it is practically impossible to obtain a correct balance for all stops, the more complex voices appearing to be shrill compared with flutes and the like.

STOP ADJUSTMENT

In this organ there is provision for regulating the loudness of such stops as might cause difficulties. The small adjustable pots in the tone networks can be set to give an agreeable balance for most conditions.

If the constructor still finds some voices too loud relative to the others, the particular resistor feeding the outlet busbar can be increased until the balance seems correct.

Next month: the concluding article in this series will discuss some additional circuits for various effects, and also organ playing technique.

- BABY ALARM
- PHOTOGRAPHIC TRIGGER
- SPORTS EVENT TIMER TRIGGER
- GARAGE DOOR CONTROL
- AID FOR THE DISABLED

THE sound operated switch described here incorporates a holding or locking action. The first sharp pulse of sound switches on the device, and after a short period of time the next pulse of sound will switch the device off. Thus this sound operated switch is different to others in that it only requires a sound to switch it on, and it will then remain switched on until a second sound turns it off.

CIRCUIT DESCRIPTION

A block diagram of the unit is shown in Fig. 1. A loudspeaker or microphone is used as a transducer, to pick up the sound which is applied to an audio amplifier (via a matching transformer in the case of LS1).

The amplified signal is then fed to a monostable circuit via a limiter. The monostable has a preset time constant to prevent it being switched more than once by a burst of sound. The output from the monostable is then fed to a bistable which switches the load via two further transistors.

The amplifier consists of a direct coupled *pnp-npn* transistor pair (TR1 and TR2 in Fig. 2) followed by a limiter (TR3). The base emitter junction of TR3 is in

effect a diode connected across R6; this means that any voltage above 0.7V will switch TR3 on. Thus when the high amplitude audio is applied to the base of TR3, the output across R7 is a series of pulses corresponding to the sharp audio peaks.

MONOSTABLE

These pulses are passed through the diode D1 to the monostable multivibrator. The monostable switches over on receipt of the first pulse and remains switched on for a preset period, determined by the time constant R10 C4, inhibiting the system and blocking any other sound from the bistable multivibrator.

A sharp sound (i.e. a "snap" of the fingers or a whistle) consists not of one single sound, but of a burst of sound, containing many separate pulses. Thus if this burst is amplified and then limited, a burst will appear across R7 containing a random number of individual pulses. If this burst was applied straight to the bistable, the multivibrator would "flip" backwards and forwards and have a fifty-fifty chance of staying in the original state, or of having changed state at the end of the burst.



SOUND OPERATED SWITCH

By J. E. KASSER

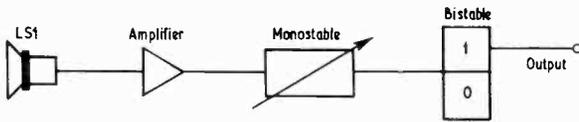


Fig. 1. Block diagram of the sound operated switch

COMPONENTS . . .

Resistors

R1	75k Ω	R13	8.2k Ω
R2	15k Ω	R14	15k Ω
R3	4.7k Ω	R15	1.2k Ω
R4	1.5k Ω	R16	8.2k Ω
R5	2.2k Ω	R17	15k Ω
R6	3.9k Ω	R18	15k Ω
R7	3.3k Ω	R19	8.2k Ω
R8	4.7k Ω	R20	1.2k Ω
R9	2.2k Ω	R21	100k Ω
R10	120k Ω	R22	15k Ω
R11	1.5k Ω	R23	10k Ω
R12	3.9k Ω		

All $\frac{1}{4}$ W, 10% carbon

Capacitors

C1	10 μ F elect. 12V
C2	10 μ F elect. 12V
C3	10 μ F elect. 12V
C4	20 μ F elect. 12V
C5	0.01 μ F
C6	0.01 μ F
C7	25 μ F elect. 12V

C4 can be adjusted to change the monostable delay time constant

Semiconductors

TR1, TR3-TR9 2N2926 or similar (8 off)
 TR2 OC201 or similar
 DI-D4 OA202

Miscellaneous

X1 Crystal microphone insert (can be used in place of T1 and LS1)
 T1 LT700 or similar push-pull audio output transformer. Connect loudspeaker to secondary and connect primary to input of amplifier
 LS1 3 Ω (miniature) loudspeaker
 BY1 9V battery
 S1 SPST toggle switch
 Case
 Foam rubber } see text
 Veroboard 5 $\frac{1}{8}$ in \times 1 $\frac{1}{8}$ in, 0.15in matrix

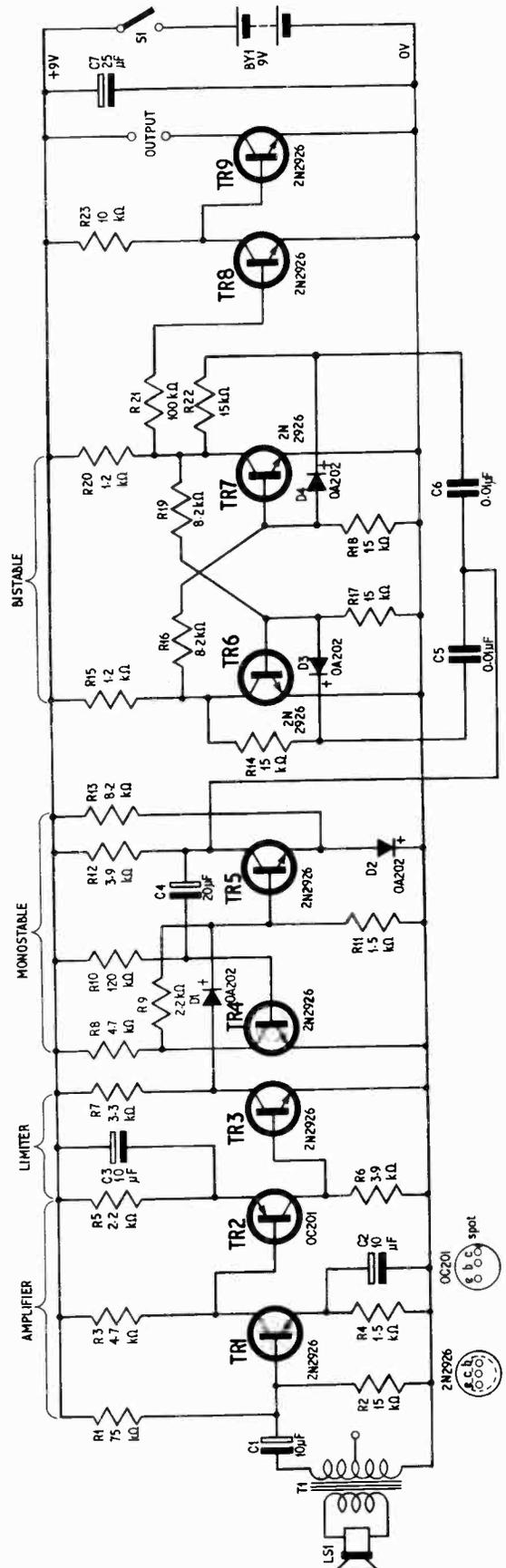


Fig. 2. Circuit diagram of the sound operated switch

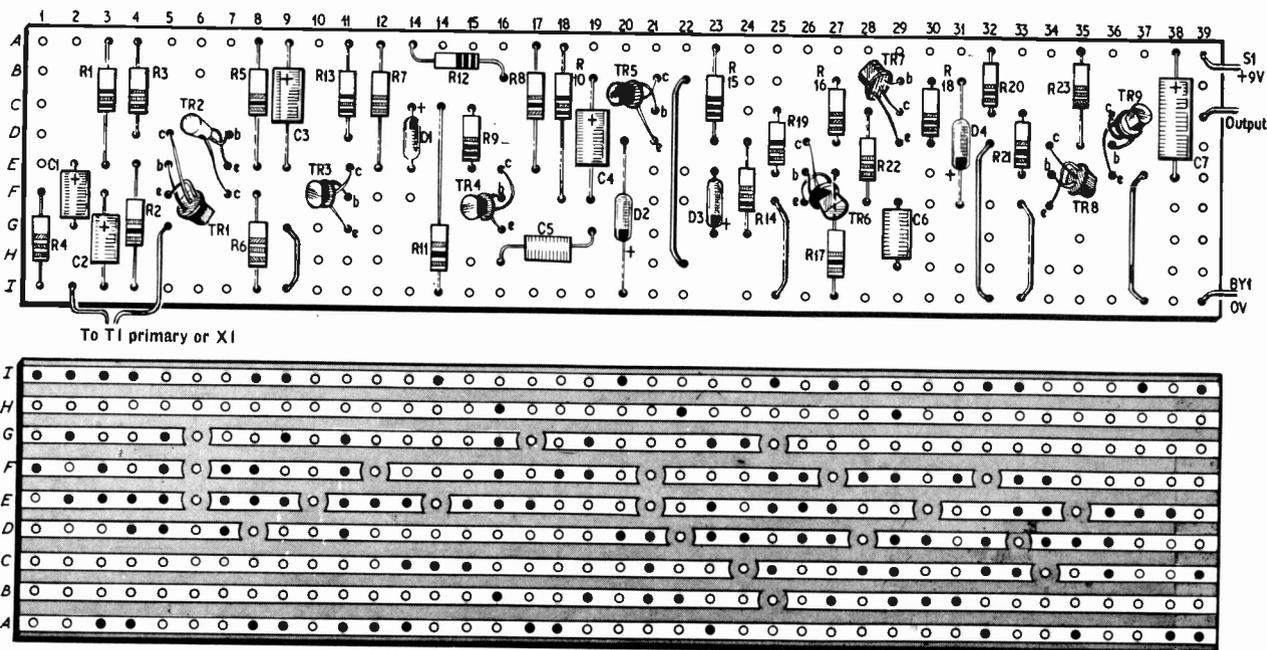


Fig. 3. Veroboard layout and wiring for the sound operated switch



Therefore, the monostable multivibrator acts on the first pulse of the burst, and can not flip back until after the whole burst has passed. The delay due to the time constant ($R_{10} C_4$) is set up to do this, and will also ensure that there is an inherent operating delay built in, so that a short period of time must elapse before a second change of state can take place.

BISTABLE

The output pulse from the monostable is passed to the bistable multivibrator, and is steered by the diodes to the correct transistor in order to change the state of the bistable. For when a pulse arrives at the input it finds one transistor switched on, the other off; thus one diode (D_3 or D_4) is reverse biased so that the pulse is steered through the other diode and switches over the multivibrator. The next pulse will find exactly the same situation, but the "roles" of the transistors and diodes will be reversed.

The current flowing in R_{21} due to the applied potential difference across it is the base current of transistor TR_8 . Thus when TR_7 is off, its collector is at a high potential, and current flows in R_{21} . When TR_7 is on, its collector is at earth potential and no current flows in R_{21} . When current flows in R_{21} , TR_8 is switched on, its collector falls to earth potential and switches off TR_9 , thus no current will flow in the load


connected across the output terminals. When the unit is in the other state TR_9 is switched on and current flows in its collector and load circuit.

CONSTRUCTION

Construction is straightforward, but is carried out in reverse, that is starting at the output stage and working back to the input. Build the bistable and output circuit first, and test this by momentarily shorting the junction of C_5 and C_6 to the negative line, when the switching action may be observed. Then build the monostable, connect it to the bistable, and test by momentarily touching the negative end of D_1 to the positive line. Finally, build the audio amplifier and limiter and test the complete unit. Sensitivity should be such that one can talk quite near the loudspeaker without switching the unit, but a snap of the fingers from across the room should operate the device.

Layout is not critical, and the unit may be built on Veroboard, tag board or on a printed circuit. Layout and wiring of the complete unit mounted on Veroboard is shown in Fig. 3.

The transistor types are not critical; TR_2 , the *pnp* type, can be almost any silicon transistor; an OC201 was used in the prototype. The *npn* types can be 2N2926, BSY27, ZTX300, or any similar transistor; the diodes used are all OA202.

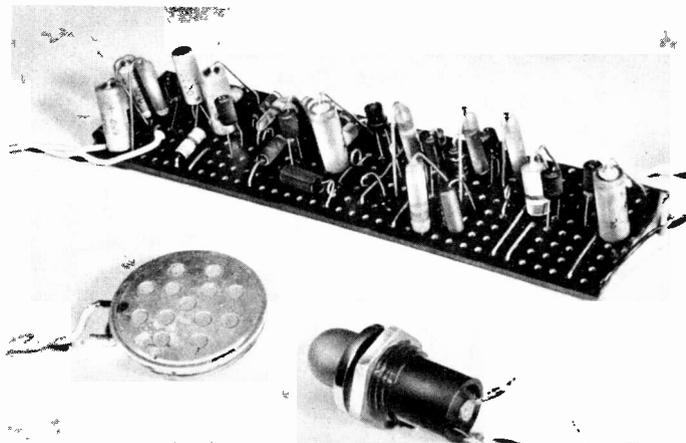

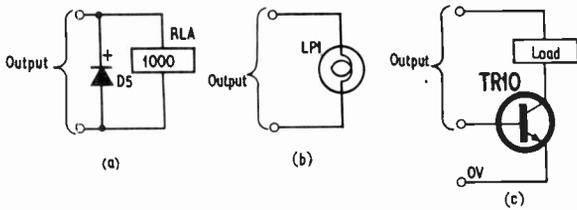


Fig. 4. Output load connections, (a) using relay to switch load, (b) miniature bulb as load, (c) power transistor used to switch load directly


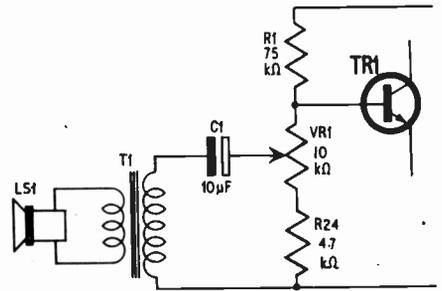


Fig. 5. Circuit for a sensitivity control

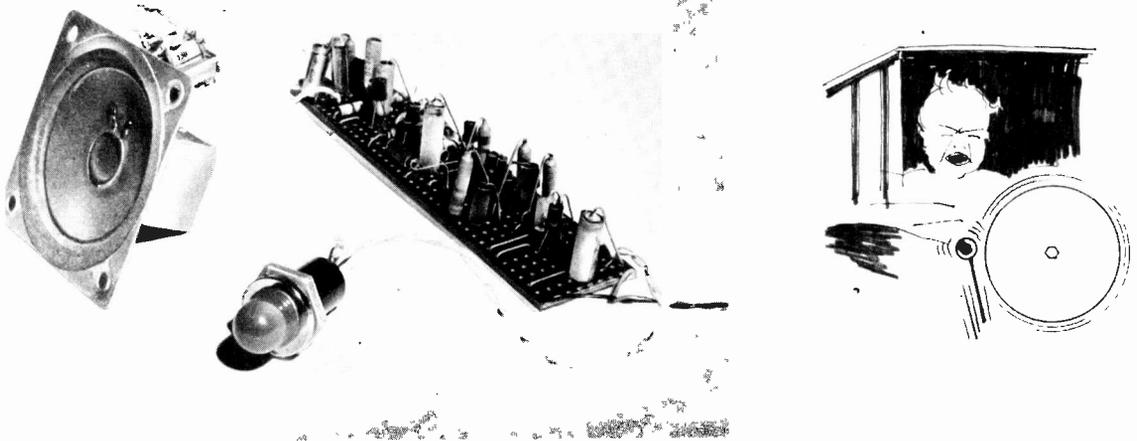

OUTPUT CIRCUITS

Having built the sound operated switch it must be connected to the load. The simplest way is shown in Fig. 4a, a relay coil (with a diode to remove any back e.m.f. generated) is connected across the output terminals. Almost any type of relay will do provided that it will operate on a 9V supply, at a current up to 40mA.

An alternative method of using the sound operated switch is shown in Fig. 4b. If a small bulb taking 60mA or less is connected across the output the sound signals will control the lamp directly. This may be used in the photographic dark-room to illuminate the light switch—just snap your fingers and the light will come on, enabling you to see the switch. The reason for using the small light and not controlling the main lighting directly is to prevent spurious sounds from turning on the main lights and thus ruining the film. The small bulb does not produce enough light to ruin papers and film, and the lamp can be shielded so that no direct lighting can fall on the working area.

A method of obtaining a greater load current is shown in Fig. 4c; this uses transistors TR9 and TR10 as a direct coupled current amplifier, and may thus control a load without the use of a relay. Transistor TR10 could be any *npn* power type such as a 2N3055, the size of the load will be limited by the power handling of this transistor.

INSTALLATION

Once the sound operated switch is working on the bench it may be noticed that extraneous noise or vibrations may trigger it. These unwanted effects can be countered in a number of ways.

The loudspeaker or microphone, which may be used remotely, can be mounted in sponge rubber. This

will effectively isolate the transducer from vibrations. The noise triggering level may be controlled by the simple addition of a sensitivity control as shown in Fig. 5, where R2 is replaced by a 10 kilohm potentiometer and 4.7 kilohm resistor in series.

The complete sound operated switch can be housed in any suitable cabinet; the loudspeaker may be mounted away from the circuitry if required.

USES

With a suitable delay period in the monostable the sound operated switch can be used to count the number of times a certain noise occurs. To do this the output may be fed to an electromagnetic counter.

The switch could also be used as a sound operated remote control unit to switch lights on or off; in the photographic darkroom as described earlier, or for room lighting. If a frequency sensitive amplifier is placed in the input circuit, the unit will only respond to tones of a given frequency, and may be used to switch almost any device on and off from a distance. (Suitable frequency sensitive amplifiers were described in PRACTICAL ELECTRONICS, January 1967 in the Remote Control Series—unfortunately we can no longer supply this issue—Ed.)

The sound operated switch can be used to help disabled persons as it can be connected to sound a bell or other call device. This application makes it possible for help to be summoned without the operator making any bodily movement. By using various frequency selective amplifiers and a number of switches, various operations may be activated by different sounds.

There are of course, other uses for the unit and no doubt many readers will find numerous interesting and useful applications for the sound operated switch. ★



I.T.N. Sound Equipment


I.T.N.'s new studios in Wells Street, London, were recently opened by Her Majesty, The Queen. The new studios were built for the new full colour transmissions.

Elcom (Northampton) Ltd., have provided the full sound facilities for the entire complex and the equipment consists of a 24 channel sound mixer and a grams desk for

each of the two studios, a dubbing mixer with an associated grams desk and a talk back system using the master to master technique covering all editorial locations.

Most of the equipment has been specially designed to I.T.A.'s requirements; the photograph above shows the grams unit (in the foreground), a 24 channel sound mixer, and the production desk in Studio 1 central control room.

ELECTRONORAMA

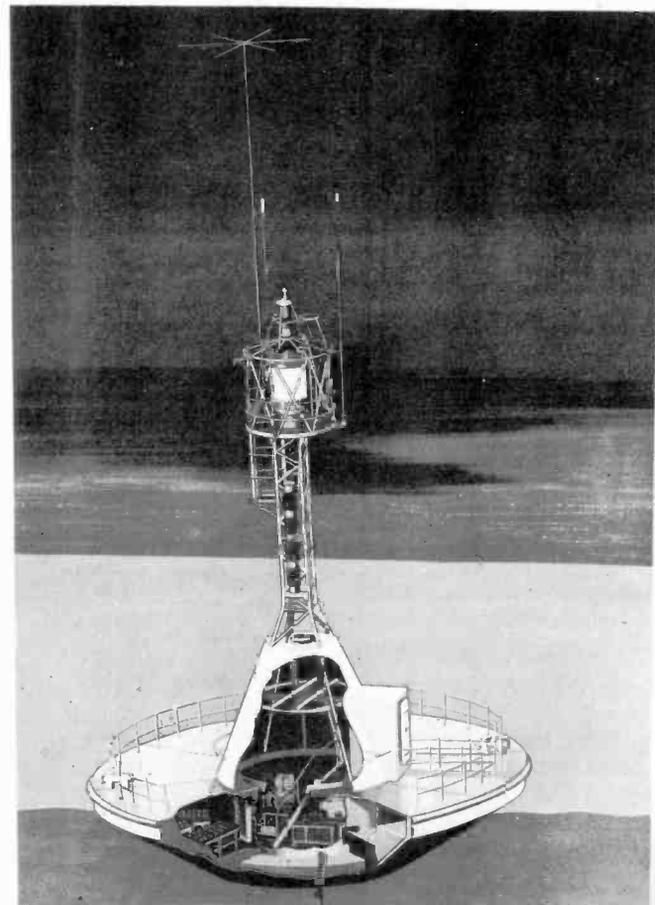

Navigation Buoy

A NEW navigational buoy, designed as an automatic replacement for a lightship, was recently handed over to Trinity House (the general lighthouse authority for England, Wales and the Channel Islands) by Hawker Siddeley Dynamics Ltd. The buoy is 40ft in diameter, 20ft from top to bottom, excluding the aerials, and weighs 84 tons.

Contained inside the buoy are three generating sets, logic and control equipment for the lights and fog signals. A u.h.f. control and monitoring link carries two-way data between the buoy and its shore station. Speech relay facilities are also included for use by servicing personnel. The radio equipment is duplicated to increase reliability and the standby equipment on the buoy has an automatic changeover.

The shore control station can monitor and control up to five buoys depending upon line-of-sight range. The buoys are completely automatic except for the operation of the fog signal. The telemetry system monitors each of the buoy's functions to check its operation and allows remote manual intervention should any automatic facility fail to operate. The buoy will be visited at six-monthly intervals for simple maintenance checks, refuelling and boosting the batteries. During maintenance periods, two exhaust fans ventilate the engine room, workshop and battery and electronic compartments.

"Lanby" (Large Automatic Navigational Buoy), as the new buoy is known, has been fitted with many safety facilities and is designed to operate in winds up to 100 m.p.h., waves up to 40ft high and tidal currents of 7 knots. The drawing on the left is an artist's impression showing a cutaway view of the new buoy; after full operational trials in the North Sea the Lanby buoy will be towed to its permanent site off Portland Bill to replace the Shambles lightship.

Electronics Aids Airlines



ELECTRONIC equipment is playing an ever increasing role in the running of airports and airlines. Aircraft have always been assisted by electronics but the systems are improving, giving greater reliability and speeding up many processes.

During the last few weeks there have been a number of additions and improvements to electronic equipment being used by the major airlines and large airports. Some of the recent additions are shown on this page.

The photograph at the top right-hand corner depicts a new type of aircraft power generating system test set. A range of these test sets have been developed by Kenure Holt and Company Ltd., and a typical test configuration for a Boeing 707, B.A.C. VC10 and B.A.C. One-eleven costs £6,000 to £9,000; much less than other test systems in use. The system, named "Kenair", can test up to four aircraft equipment panels simultaneously, thus reducing testing time and costs.

A data collection system for B.E.A.'s engine overhaul department at Heathrow has been installed for operation in conjunction with the B.E.A. computerised scheduling system for engine rework. In the initial installation the system, which was manufactured by Feedback Ltd., will accept information relating to movement of components from the outstations located in various work areas. Output data is transferred via punched tape to B.E.A.'s ICL 1903 computer; it is hoped that at a later date the punched tape stage will be eliminated. The centre and lower photographs on the right of this page show B.E.A. staff under instruction during a course with Feedback when they studied the new data collection hardware, and one of the outstations in use in the engine overhaul department.

The remaining photograph on this page shows a B.O.A.C. supervisor at Heathrow checking a VC10 before departure. The Multitone receiver in his breast pocket is part of a new u.h.f. paging system installed by B.O.A.C. for their maintenance division. The maintenance staff found that the v.h.f. equipped vans previously used were no longer adequate as a form of ground communication. Using the new system in conjunction with the old, a much more flexible network is obtained and staff can be called from any part of the airport, even inside an aircraft.

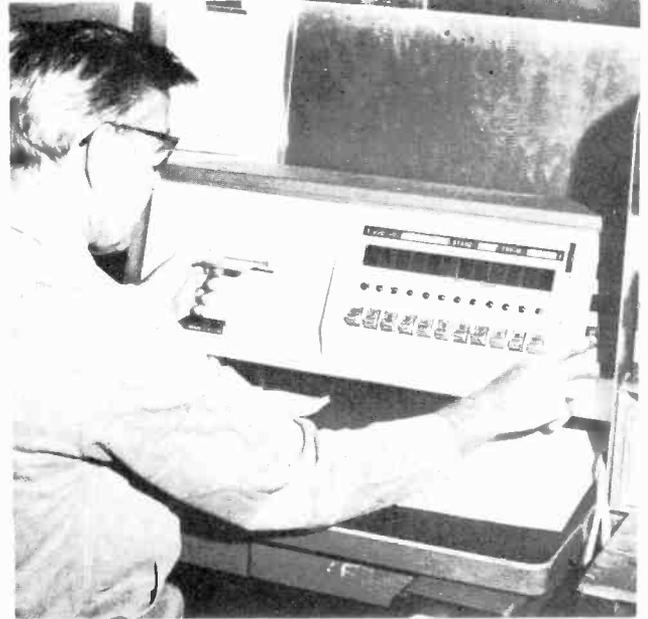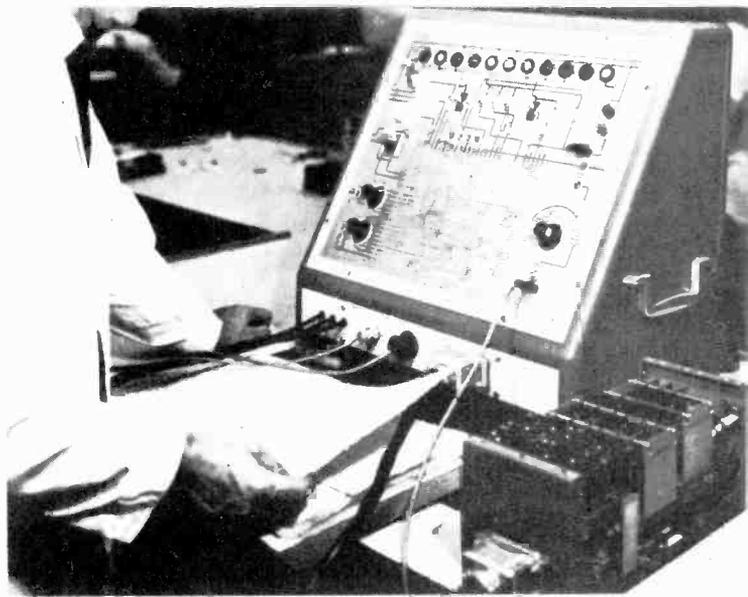

P.E. WIDEBAND H.F. COMMUNICATIONS RECEIVER

By R. HIRST S.T.C. LTD. PART FIVE SIDEBAND FILTER AND A.F. MODULES


Two further modules are described in this part, the modules are the Sideband Filter Unit and the A.F. Unit, and, as before, these were described briefly in the first part of the series.

The sideband unit can be broken down into three separate circuit configurations each of which performs a quite individual task.


CRYSTAL FILTER

Crystals X3 to X7 in conjunction with C70 to C75 act as a steep sided filter (Fig. 5.1) passing frequencies from 2.00075MHz to 2.001750MHz. Five crystals are the minimum quantity that can be used and they have been slightly staggered in frequency to get as wide a coverage as possible with the five crystals. The pass-band has some ripple in it as can be seen from Fig. 5.2.

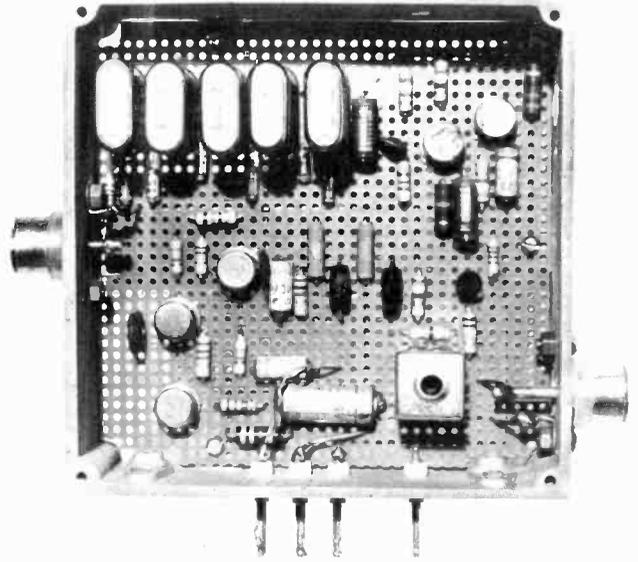The resultant audio bandwidth achieved with this number of elements is barely substantial but as the crystals are relatively expensive items it seems reasonable to indicate the minimum quantity that could be used. Should the constructor wish to improve the bandwidth it is quite easy to add another three crystals,



The Sideband Filter Unit module

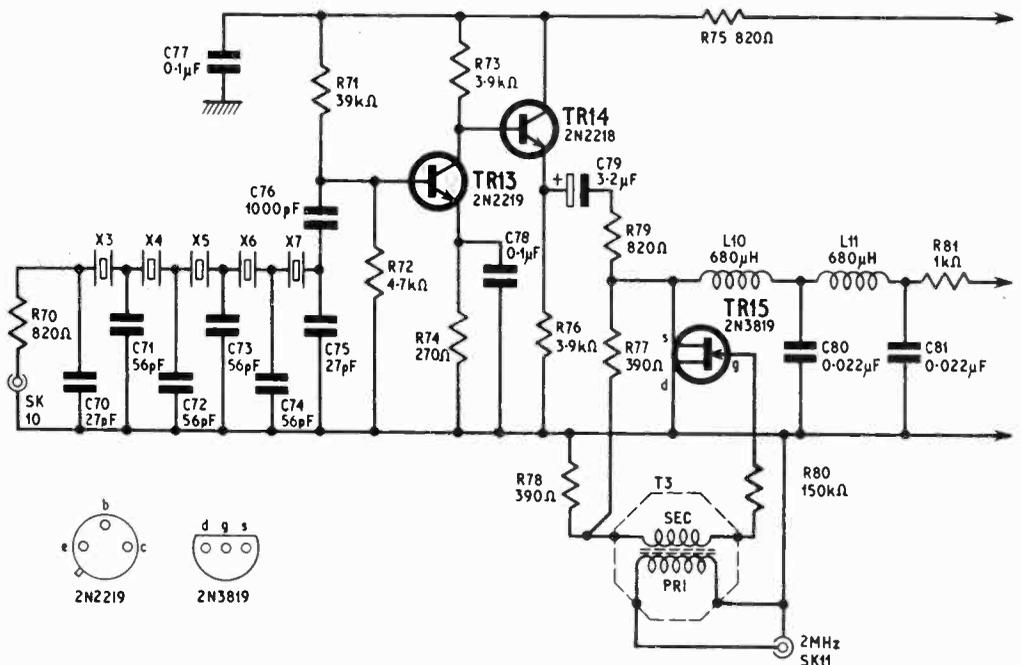

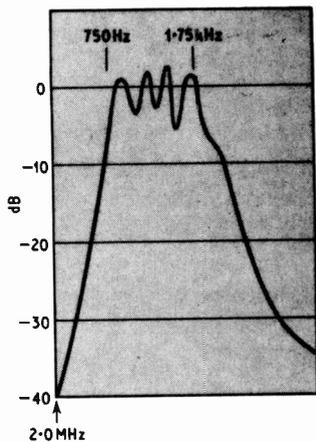


Fig. 5.2. Passband curve using the five stage filter

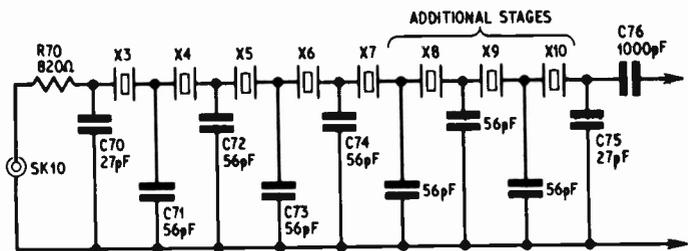


Fig. 5.3. Alternative eight stage crystal filter

as shown in Fig. 5.3, making a maximum total of eight in all.

With the alternative arrangement all the capacitors going from the junctions of the crystals down to earth can be adjusted slightly in value to compensate for individual crystal characteristics to give a reasonably flat bandwidth of 3kHz.

AMPLIFIER AND DEMODULATOR

Transistors TR13 and TR14 form a directly coupled amplifier where the signal is amplified by TR13 and transformed in impedance by TR14. The Field Effect Transistor TR15 is used as a demodulator in the following manner. The 2MHz switching frequency, which is derived from the 2MHz oscillator, is transformed up to approximately 7 volts by the transformer T3.

The f.e.t. which has been placed directly across the signal path goes alternately open and short circuit at the switching frequency thus producing an audio tone. This can be shown by subtracting from the signal frequency, which is from 2.000750MHz to 2.001750MHz, the switching frequency of 2.0MHz. Therefore if the sideband filter is wider in its passband, a greater audio range may be achieved. The r.f. is removed by the following low pass filter, L10, L11, C80, and C81.

PREAMPLIFIER

The resultant audio signal is now pre-amplified by TR16, TR17 and TR17A and is fed out to the audio gain control on the front panel of the receiver. The preamplifier uses three transistors in a directly coupled mode arranged so that the configuration is self temperature compensating by virtue of the d.c. negative feedback applied to the base of TR16 via R82. Capacitors C84 and C85 have been introduced to ensure that no r.f. signal gets through into the audio amplifier.

The preamplifier starts to cut off rapidly at approximately 4kHz but is very stable in its gain characteristics due to the considerable a.c. negative feedback applied via R82 to the base of TR16. This degree of negative feedback allows a wide spread in the tolerances of the transistors that may be used in all these stages. The audio output is taken from one of the pins at the base of the module via a screened lead to the gain control.

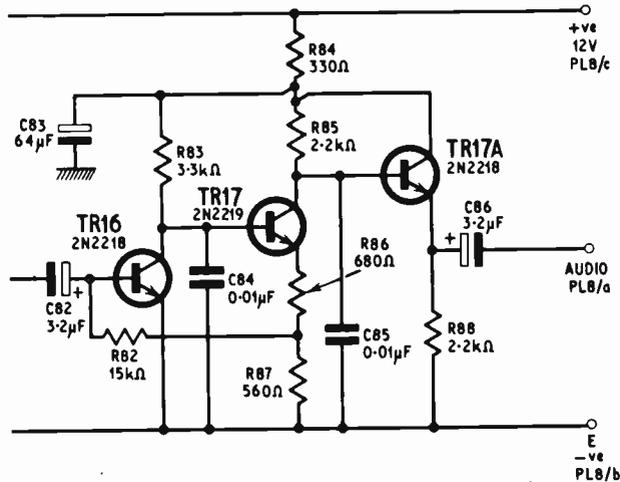


Fig. 5.1. Circuit diagram of the Sideband Filter Unit with a five stage crystal filter

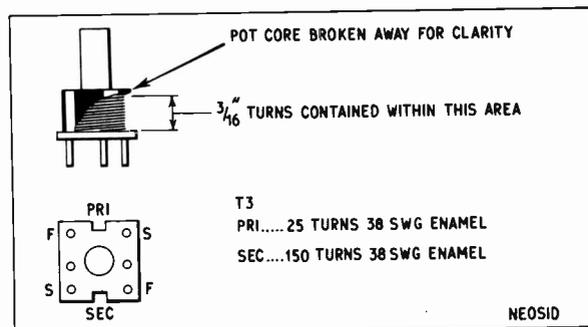


Fig. 5.4. Coil winding details for T3

COMPONENTS . . .

SIDEBAND FILTER UNIT

Resistors

R70	820Ω
R71	39kΩ
R72	4.7kΩ
R73	3.9kΩ
R74	270Ω
R75	820Ω
R76	3.9kΩ
R77	390Ω
R78	390Ω
R79	820Ω
R80	150kΩ
R81	1kΩ
R82	15kΩ
R83	3.3kΩ
R84	330Ω
R85	2.2kΩ
R86	680Ω
R87	560Ω
R88	2.2kΩ

Capacitors

C70	27pF	} polystyrene 2½%
C71	56pF	
C72	56pF	
C73	56pF	
C74	56pF	
C75	27pF	
C76	1,000pF	
C77	0.1μF polyester	
C78	0.1μF polyester	
C79	3.2μF elect. 12V	
C80	0.022μF polyester	
C81	0.022μF polyester	
C82	3.2μF elect. 12V	
C83	64μF elect. 12V	
C84	0.01μF ceramic	
C85	0.01μF ceramic	
C86	3.2μF elect. 12V	

Transistors

TR13	2N2219
TR14	2N2218
TR15	2N3819
TR16	2N2218
TR17	2N2219
TR17A	2N2218

Crystals

X3-7	2MHz fundamental (5 off—see text)
------	--------------------------------------

Inductors

T3	See Fig. 5.4
L10	680μH choke
L11	680μH choke

Miscellaneous

PL8/a, b, c, d insulated lead through connectors (4 off)
 SK10, 11 coaxial chassis mounted sockets (2 off)
 Plain perforated Veroboard
 3½in × 3½in, 0.1in grid

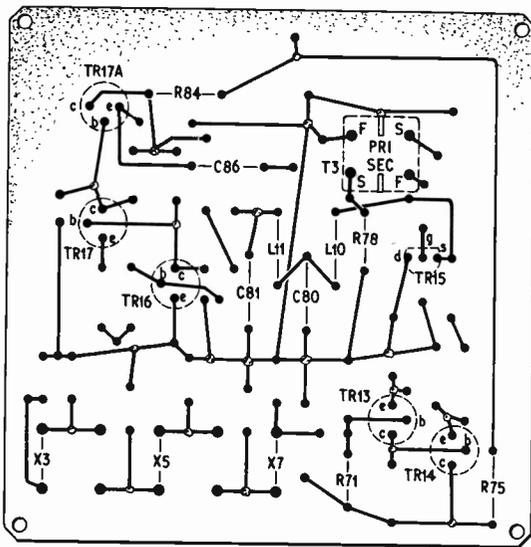
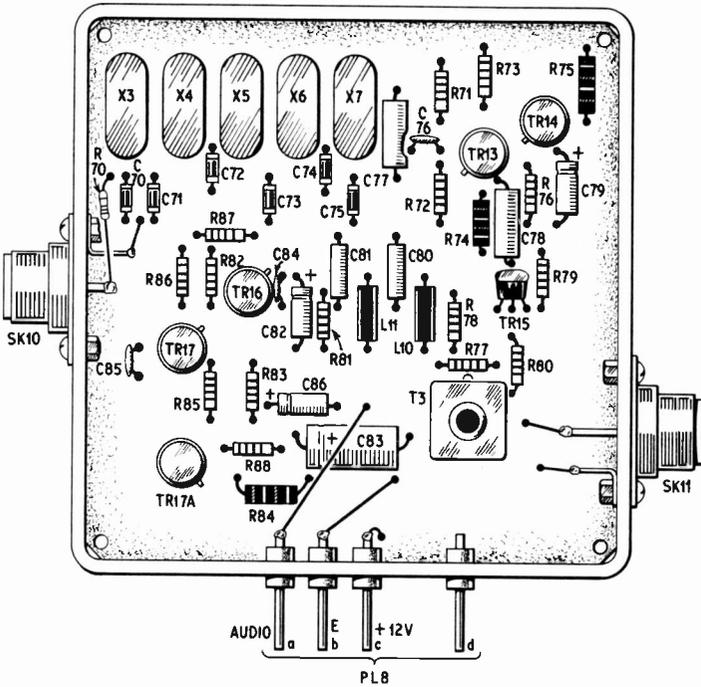


Fig. 5.5. Layout and wiring diagram of the Sideband Filter Unit

There is very little overall gain in the Sideband Unit due to the losses associated with the crystal filter and the mixer circuit, hence the following A.F. Unit has an input sensitivity in the order of 300 microvolts.

CONSTRUCTION

Winding details for T3 are given in Fig. 5.4; this coil should be wound before commencing construction of the module. It should be noted that the screw core used for this transformer is coded "grey" not violet as has been used previously; a cup core is also used for T3, see Fig. 5.4. Layout and wiring details are given in Fig. 5.5; this module is constructed along the same lines as previous modules using component leads for connecting up where possible. All components are mounted on a perforated board inside the module case described in the second part of this series.

SETTING UP INSTRUCTIONS

Equipment required:

- (a) Power supply 12 volts at 50mA.
- (b) Signal generator capable of supplying 2mV at 2MHz, variable plus or minus 6kHz from 2MHz; impedance 50 ohms.
- (c) Signal generator capable of giving out 1V at 2MHz; impedance 50 ohms.
- (d) Valve voltmeter with a sensitivity of 500 microvolts at audio frequencies; impedance greater than 100 kilohms.

PROCEDURE

Apply 12 volts in the correct polarity to the module. Check all the potentials at the base collector and

emitter of the transistors to ensure that they correspond with the values given in Table 5.1. If these levels are correct apply a signal at 1kHz above 2MHz (i.e. 2.001MHz) to the input SK10 at a level of 2 millivolts. Secondly, apply a signal at 2MHz, plus or minus 50Hz, to SK11 at a level of 800 millivolts; this measurement is taken in circuit with the amplifier switched on. The valve voltmeter can now be connected to PL8 where there should be an audio output in excess of 2 millivolts. It would be advantageous to connect an oscilloscope across PL8 at the same time to ensure that the waveform is undistorted and is free from r.f.

Table 5.1. SIDEBAND UNIT D.C. VOLTAGES

Stage		Voltage
TR13	Vc	5.4V
	Vb	1.2V
	Ve	0.4V
TR14	Vc	10.1V
	Vb	5.4V
	Ve	4.6V
TR16	Vc	3.1V
	Vb	0.65V
	Ve	0V
TR17	Vc	5.6V
	Vb	3.1V
	Ve	2.4V
TR17A	Vc	10.0V
	Vb	5.6V
	Ve	5.0V


A.F. UNIT

The Audio Frequency Unit simply consists of a pre-built audio package, purchased as a proprietary item, mounted in a module case. The 12 volt negative rail has been reduced to 8.2 volts within this unit by means of a resistor and Zener diode. The Zener has been shunted by a capacitor to ensure that the rail is adequately decoupled, see Fig. 5.6.

PERFORMANCE

The unit is capable of delivering, at minimum, 1 volt into a 25 ohm speaker for an input of 300 microvolts, giving an output of 40 milliwatts into the load. The audio amplifier type PC2 may be purchased from Newmarket Transistors Ltd., or one of their agents. The amplifier is entirely directly coupled except for the input stage thus ensuring, due to the large amount of d.c. negative feedback, a high degree of temperature stability.

The input signal has been brought directly to the input terminal of the package via a flying screened lead from PL8, to avoid any of the output current passing via the earth return of the input circuit therefore reducing the possibility of feedback being applied due to the common earth coupling. It is possible to get up to 100 milliwatts from this package if the speaker load is reduced to 15 ohms and the 56 ohm resistor in series with the negative rail is reduced to 39 ohms.

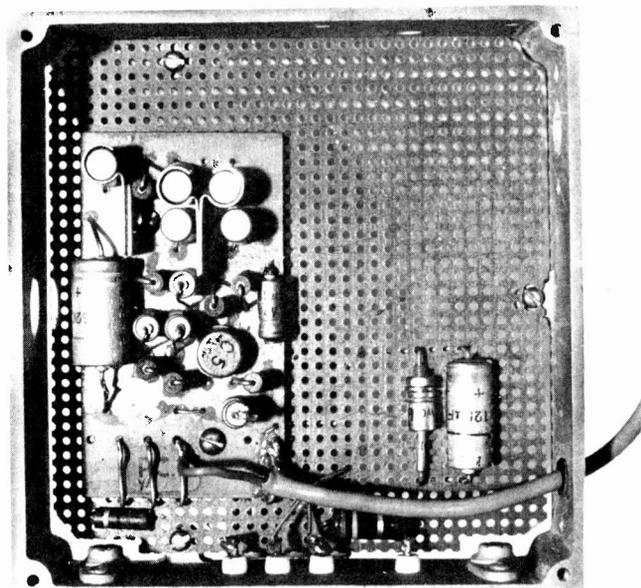

The A.F. Unit module

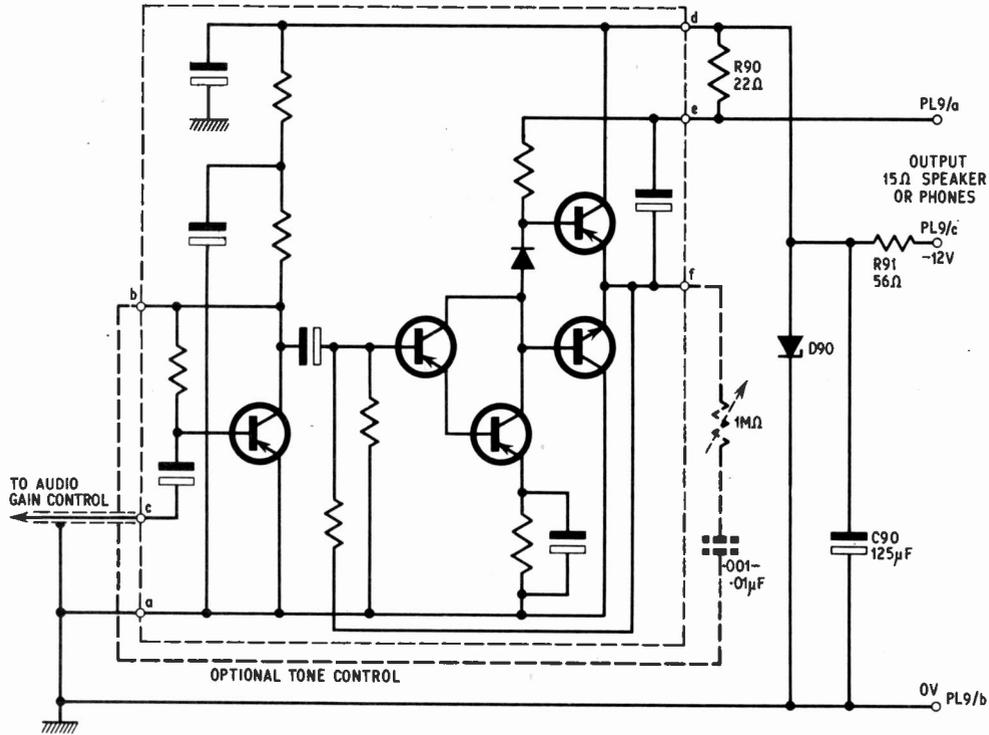


Fig. 5.6. Circuit diagram of the A.F. Unit

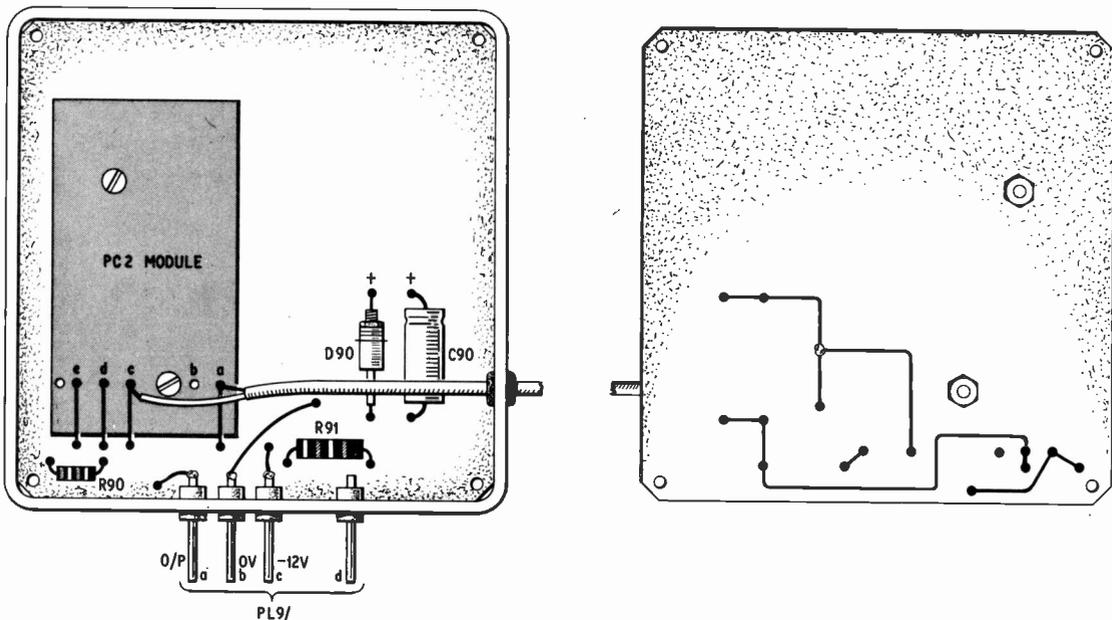


Fig. 5.7. Layout and wiring diagram of the A.F. Unit

CONSTRUCTION

As has been stated the amplifier is purchased as a complete module, this module is mounted on the perforated board using 6B.A. fixings and the power supply and output wiring is connected up. A layout and wiring diagram is shown in Fig. 5.7.

COMPONENTS . . .

A.F. UNIT

Resistors

R90 22 Ω $\frac{1}{2}$ W 10%
R91 56 Ω 1W 10%

Capacitor

C90 125 μ F elect. 10V

Zener Diode

D90 8.2V, 1.5W

Amplifier Package

Type PC2 (Newmarket Transistors)

Miscellaneous

PL9/a, b, c, d lead through connectors (4 off)
Veroboard, plain perforated 3 $\frac{1}{2}$ in \times 3 $\frac{1}{2}$ in, 0.1in grid
Screened audio lead (12in)

SETTING UP INSTRUCTIONS

Equipment required:

- Power supply 12V at 100mA.
- Signal generator capable of delivering up to 1mV in the frequency range 300Hz to 3kHz.
- Valve voltmeter covering the audio range with a sensitivity of 300 microvolts.
- Oscilloscope capable of measuring 1 volt at audio frequencies.

PROCEDURE

Apply 12 volts in the correct polarity to the power terminals of the unit and check that the voltage levels correspond with those given above.

Inject an input signal, via the flying lead, at a level of 300 microvolts at 1kHz and connect the valve voltmeter and the oscilloscope across a 25 ohm resistor placed across the output terminals. The level measured at the output point should not be less than 1 volt. The waveform should be examined on the oscilloscope to ensure that there is no clipping of the output waveform or any other form of apparent distortion.

Change the input frequency to 300Hz maintaining the input level at 300 microvolts and check to see that the output has not reduced or increased by more than 3dB. Repeat this last test with the input frequency changed to 3kHz.

Next month: R.F. Attenuator and Power Supply details



BOOK REVIEWS

ELECTRONICS

By Roland Worcester

Published by The Hamlyn Publishing Group Ltd.
159 pages, 7 $\frac{1}{8}$ in \times 4 $\frac{3}{8}$ in. Price 6s.

THE foreword to this book contains the following sentence in its final paragraph: "Hence the general reader owes it to himself to find out what electronics is all about, and this is one need that the book has been written to supply."

One would expect therefore that the book would be written with the beginner to electronics in mind, using simple terms to build up the knowledge of the reader. However, this is not the case and, in fact, some of the sentences and occasionally whole paragraphs just do not make complete sense. Descriptions of many circuit components are inadequate and could cause confusion.

Parts of the book have been written the wrong way around and it is not at all easy to follow. This point is illustrated by the explanation of capacitive reactance on page 19 although the capacitor is not described until page 28—presumably the reader is expected to understand reactance before he knows the basic operation of a capacitor!

"Electronics" has over 300 illustrations, nearly all of which are in colour; the book would have been greatly improved if some of the colour had been dropped and more care taken with the drawings—perhaps some photographs would assist the reader.

It is stated in the blurb that: "Roland Worcester is a pseudonym that conceals the identity of one of the leading authorities in Britain on the theory and applications of electronics." If this is true one wonders why the author's true name does not adorn the cover of this book.

M.K.

HI FI YEAR BOOK 1970

Edited by Colin Sproxtton


Published by IPC Electrical-Electronic Year
Books Ltd.

432 pages, 8 $\frac{1}{2}$ in \times 5 $\frac{3}{8}$ in. Price 20s.

THE casual purchaser of hi fi equipment has a vast range to choose from, which can be perplexing in deciding on the ultimate set-up. This annual publication (now under new management) is a great help in showing technical specifications and illustrations of almost all of the currently available hi fi equipments on the U.K. market. Prices at the time of going to press are those recommended by the manufacturers and may be adjusted due to the abolition of retail price maintenance.

The sections I found most interesting were the articles at the beginning (47 pages) by some well-known authors. John Borwick shows how to select equipment pieces to suit each other, and explains the different types so that the reader can begin to understand the specifications in the directory. R. C. Norris enlarges on speaker

continued on page 170

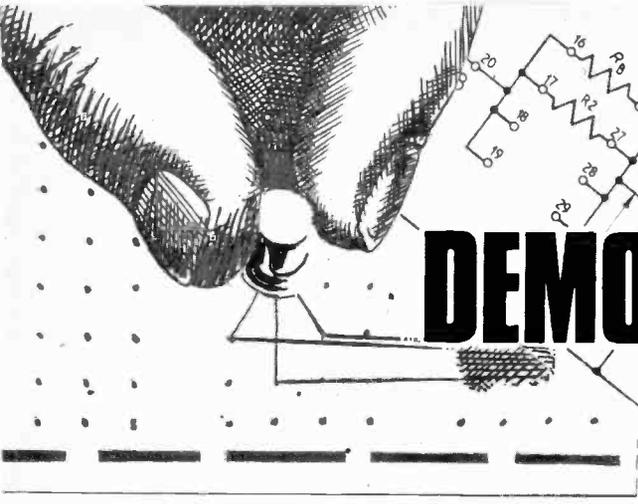

DEMO SWITCHING CIRCUITS

3

THE MONOSTABLE By B. Pounder

LAST month's article showed the effects of applying rectangular voltage pulses across a series CR network. Let us now apply these properties to a number of useful switching circuits, starting with the multivibrator series. There are three circuits of this type, the monostable, the astable and the bistable multivibrators. This article will deal with the first of these.

MONOSTABLE MULTIVIBRATOR

Fig. 3.1a shows a number of sharp trigger pulses that can be applied to the input of a monostable circuit; the output of the circuit is shown in Fig. 3.1b.

On receipt of a trigger pulse, the circuit switches from a stable state to a state of quasi-stability. The quasi-stable state persists for a time period τ , the length of which can be varied in the circuit design. Note that the fifth trigger pulse shown in Fig. 3.1 is ignored by the circuit as it has been applied during one of the quasi-stable periods.

The monostable acts as a pulse generator, an output pulse occurring after each trigger impulse applied during one of the stable periods. The circuit is often used as a "gate" which can be opened for a well defined interval of time.

CIRCUIT OPERATION

The basic monostable circuit is shown in Fig. 3.2 in which the d.c. conditions are indicated for the state in which TR1 is saturated, or on, and TR2 is cut-off.

To understand the operation of the circuit, it is necessary to recall from the first article that when a transistor is in saturation, the following approximations apply:

$$V_{be(sat)} = 0.8V \text{ (silicon transistors)}$$

$$= 0.3V \text{ (germanium transistors)}$$

$$V_{ce(sat)} = 0.2V \text{ to } 0.3V$$

These figures are valid for small general purpose or switching transistors. They will be assumed zero in the approximate analyses which follow.

When TR1 is on:

$$I_{c1} = \frac{V_{CC} - V_{ce1(sat)}}{R_1} \approx \frac{V_{CC}}{R_1}$$

$$I_{b1} = \frac{I_{c1}}{h_{FE}} = \frac{V_{CC} - V_{be1(sat)}}{R_3} \approx \frac{V_{CC}}{R_3}$$

$$= V_{ce1(sat)} \approx 0$$

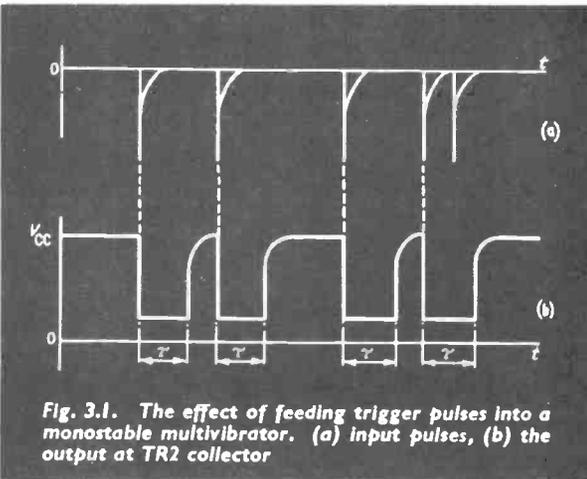


Fig. 3.1. The effect of feeding trigger pulses into a monostable multivibrator. (a) input pulses, (b) the output at TR2 collector

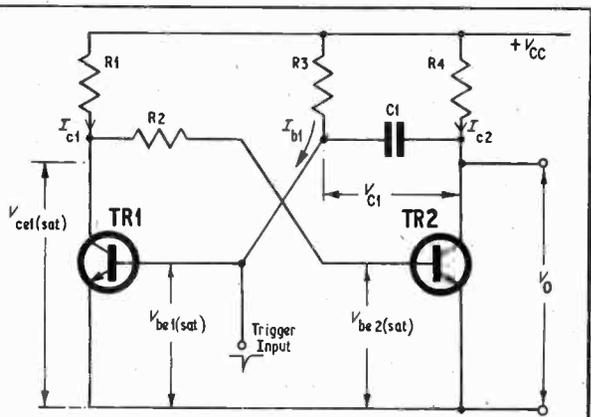


Fig. 3.2. Theoretical circuit of the monostable multivibrator

When TR2 is on:

$$I_{c2} = \frac{V_{CC} - V_{ce2(sat)}}{R_4} \approx \frac{V_{CC}}{R_4}$$

$$I_{b2} = \frac{I_{c2}}{h_{FE}} = \frac{V_{CC} - V_{be2(sat)}}{R_1 + R_2} \approx \frac{V_{CC}}{R_1 + R_2}$$

$$= V_0 = V_{ce2(sat)} \approx 0$$

Suppose that a negative trigger pulse is applied to the base of TR1. The transistor is driven towards cut-off and V_{ce1} rises towards the supply voltage V_{CC} . This rise in collector voltage causes an increase in the base current of TR2 which flows through R_2 , so TR2 begins to conduct and its collector voltage V_0 falls.

The voltage at the other side of the capacitor at TR1 base also falls, since the potential difference across the plates of a capacitor cannot change instantaneously. As TR1 base voltage falls, TR1 is held hard off.

The circuit therefore contains a regenerative feedback loop which causes the transistor driven towards cut-off to drive the other transistor into conduction and vice versa. The change of state to that in which TR1 is off and TR2 is on is rapid because of this regenerative action.

pass from negative to positive through zero. Soon after this happens, the base-emitter junction of TR1 becomes forward biased so this transistor begins to conduct once again. The collector voltage of TR1 now begins to fall; this fall, in being transmitted to the base of TR2, causes TR2 to turn off.

TIME FACTOR

The time period for which the circuit is in its quasi-stable state is easily found from equation (1). All we need do is substitute $t = \tau$ when the potential difference $V_{C1} = V_{CC}$. The result of such a substitution is that

$$\tau = 0.69C_1R_3 \quad (2)$$

Note that following the second switch-over, $C1$ completes its charging process through R_4 , having charged sufficiently to make $V_b = 0$. The equation for the final part of the charge process is therefore

$$V_{C1} = 2V_{CC}(1 - e^{-t/C_1R_4}) \quad (3)$$

The circuit conditions at the important instants during the operation period are illustrated in the approximate equivalent circuits shown in Figs. 3.3, 3.4,

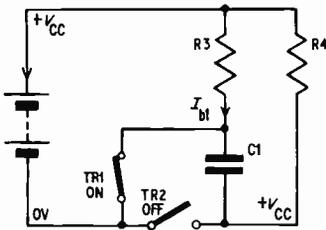


Fig. 3.3 TR1 on and TR2 off

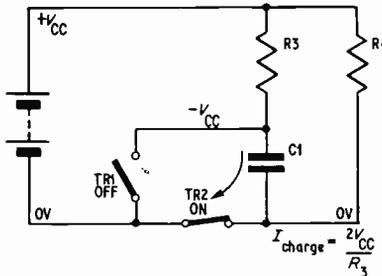


Fig. 3.4 TR1 off and TR2 on

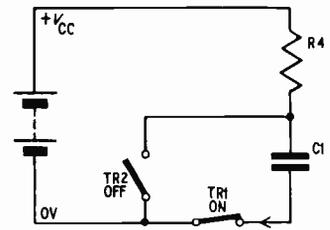


Fig. 3.5. Alternative configuration when TR1 is on and TR2 off

Equivalent passive circuits for illustrating certain instants in the operation of the circuit in Fig. 3.2

Just after the change of state has taken place, V_0 has dropped by almost V_{CC} to a value just greater than zero. V_{be1} therefore drops from its initial value of about zero by a similar amount, and finishes up at $-V_{CC}$.

The potential difference across R_3 at this instant is twice the supply voltage, or $2V_{CC}$, so a current $2V_{CC}/R_3$ commences to flow through R_3 . But this current cannot flow into TR1, for this transistor is cut-off. It therefore flows into $C1$ which commences to charge at an initial rate of $2V_{CC}/R_3$.

This current then falls exponentially on a time constant C_1R_3 . The series CR circuit reacts as though a potential difference of $2V_{CC}$ had been applied suddenly across it so the potential difference across $C1$ is given by

$$V_{C1} = 2V_{CC}(1 - e^{-t/C_1R_3}) \quad (1)$$

The circuit is in its quasi-stable state while $C1$ is in the first part of its charging process.

The rising potential difference given by equation (1) eventually causes the actual potential at TR1 base to

and 3.5. In each of these, the base-emitter junction of an *on* transistor is depicted as a closed switch, while the collector-emitter terminals of an *off* transistor are depicted as an open switch. Charge paths for the capacitor currents are also shown.

Equation (3) indicates that the circuit regains its initial state rapidly after the second switching instant. For example, if we substitute $t = \tau = 0.69C_1R_3$ and $V_{C1} = 0.98V_{CC}$ into the equation, we find that $R_3 = 5.7R_4$. Now R_3 is bound to be greater than this, unless a transistor with an abnormally low value of h_{FE} were used in the circuit. Thus in the time period τ following the period of quasi-stability, V_{C1} will have completed much more than 98 per cent of its total change.

CALCULATION OF COMPONENT VALUES

The circuit component values are calculated using the formulae which were used with Fig. 3.2 and equation (2).

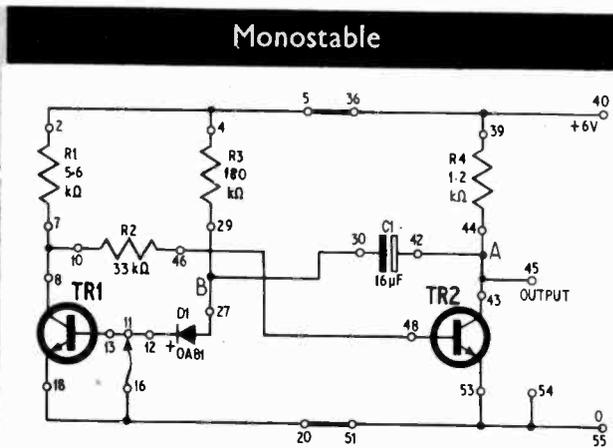
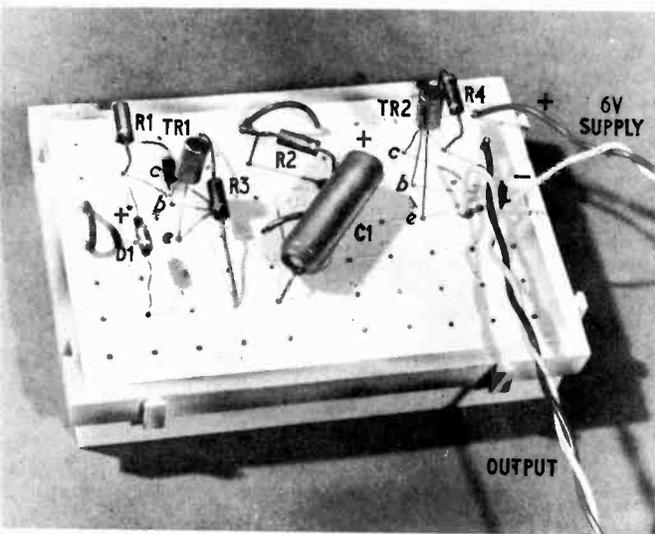


Fig. 3.6. Monostable circuit with hole numbers for S-Dec "breadboard"

The procedure is summarised as follows.

Design Procedure

- Step 1. Choose V_{CC} equal to the desired output voltage swing which is to appear across R_4 at the switching instants.
- Step 2. Choose a value for I_{c2} sufficiently large to meet the load requirements and calculate $R_4 = V_{CC}/I_{c2}$.
- Step 3. Calculate $(R_2 + R_1) = h_{FE}V_{CC}/I_{c2}$. If h_{FE} is the minimum value quoted for the particular transistor, this result will ensure that TR2 will saturate. If in doubt, take a value of 20 or 30 for h_{FE} .
- Step 4. Choose a small value for I_{c1} , but not so small as to cause a drop in h_{FE} . A value of about 1mA is often adequate, a current at which h_{FE} is very unlikely to be less than 30. Calculate $R_1 = V_{CC}/I_{c1}$.
- Step 5. Calculate $R_2 = (R_2 + R_1) - R_1$.
- Step 6. Calculate $R_3 = h_{FE}V_{CC}/I_{c1}$.
- Step 7. Calculate $C_1 = \tau/0.69R_3$. If R_3 is in megohms, C_1 will be in μF . If the value of C_1 is unsuitable, R_3 can be altered provided that Step 4 is repeated in order to allow for the resulting change in I_{c1} .

CIRCUIT EXAMPLE

Suppose the requirement is for the monostable output pulses to be of 6V amplitude across a 10 kilohm load.

- Hence $V_{CC} = 6V$. (step 1)
- If $I_{c2} = 5mA$, the circuit will be little affected by the load. Hence $R_4 = 6/5 = 1.2k\Omega$. (step 2)
- and $(R_1 + R_2) = 6 \times 30/5 = 36k\Omega$. (step 3)
- If $I_{c1} = 1mA$, $R_1 = 6/1 = 6k\Omega$. (step 4)
- so $R_2 = 30k\Omega$. (step 5)
- Also, $R_3 = 6 \times 30/1 = 180k\Omega$. (step 6)
- If we choose $\tau = 2$ seconds, a value long enough to

make demonstration of the circuit operation easy, then $C_1 = 2/(0.69 \times 0.18) \approx 16\mu F$. (step 7)

Of course, the values calculated do not always fall in line with preferred value components so the nearest types can be used. These are as follows:

R4	1.2kΩ	(step 2)
R1 + R2	39kΩ	(step 3)
R1	5.6kΩ	(step 4)
R2	33kΩ	(step 5)
R3	180kΩ	(step 6)
C1	16μF	(step 7)

The circuit is shown in Fig. 3.6 with S-Dec connections. It is triggered by momentarily connecting the base and emitter leads of TR1 together in order to turn this transistor off. The output voltage is observed with the aid of a high resistance voltmeter connected between the collector and emitter leads of TR2.

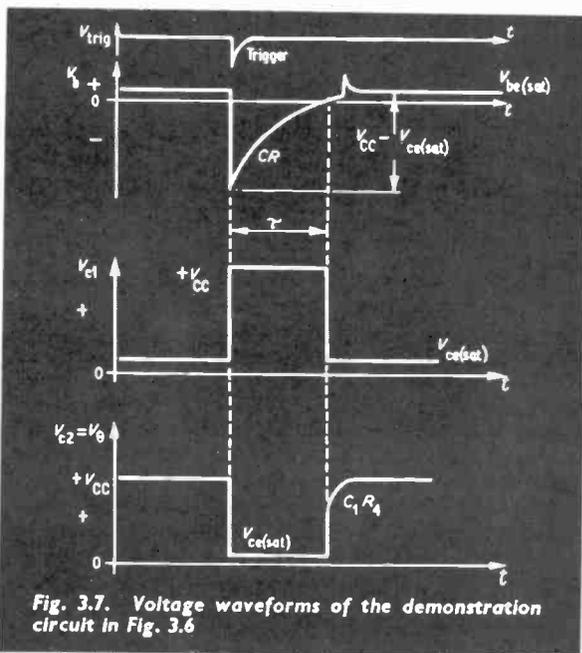


Fig. 3.7. Voltage waveforms of the demonstration circuit in Fig. 3.6

SUPER BARGAIN STOCKTAKING SALE!!!

Use the form below for your order. **CONDENSERS MUST BE ORDERED BY STOCK NUMBER ONLY.** If any sale item is "sold-out" when order received we shall substitute items of equal value.

ELECTROLYTIC CAPACITORS

Stock No.	Capacity	Voltage	Price	No. Req'd	£ s. d.	Stock No.	Capacity	Voltage	Price	No. Req'd	£ s. d.
1	1µF	6	4d			45	350	12	9d		
2	4µF	25	4d			46	20/4	275	1/-		
3	4µF	4	4d			47	250	50	2/-		
4	6µF	6	4d			48	500	25	1/6		
6	64µF	9	4d			49	400	15	1/-		
7	20µF	6	4d			50	400	2-5	3d		
11	8µF	6	4d			51	64	275	1/9		
16	32	150	9d			52	32/32	350	2/6		
17	64	2-5	3d			53	8/8/8	275	1/9		
18	100/200/200/50	275	7/6			54	500	6	6d		
19	50/80	300	3/-			55	64	275	1/3		
21	24	275	1/-			56	25	6	3d		
22	10	25	3d			57	100	9	6d		
23	125	2-5	3d			58	400	50	2/-		
25	16/32	350	2/6			59	400	30	1/6		
26	32	275	1/6			60	500	4	3d		
28	75/75/75/75	150	2/6			61	150	30	1/6		
30	12-5	40	9d			62	64/32/8	275	2/6		
32	3,000	35	7/6			64	40	6-4	3d		
33	3,000	15	3/-			67	30	6	3d		
34	3,000	30	7/-			68	100/100/50	275	3/-		
35	250	70	2/-			69	50/50/50	350	4/-		
36	2,500	9	2/-			70	40/40/20	275	2/-		
38	750	12	1/9			71	400	6-4	3d		
39	100µF	275	2/6			72	320	275	10	3d	
40	30µF	10	3d			73	32/32	275	2/6		
42	16µF	50REV	2/-								
43	16/16	275	2/-								
44	16	275	1/-								

Total:—

RESISTORS. EXCELLENT QUALITY. MAINLY 5%. 7/6 per 100 of any one value.

2/- per dozen of any one value. Smaller quantities 3d each.

Tick the values required.

13 ohms	220 ohms	1-5k Ω	3-6k Ω	7-5k Ω	22k Ω	39k Ω	62k Ω	130k Ω	560k Ω	1-8M Ω	7-5M Ω
22 ohms	470 ohms	1-8k Ω	4-3k Ω	10k Ω	24k Ω	43k Ω	75k Ω	360k Ω	620k Ω	3-6M Ω	8-2M Ω
36 ohms	560 ohms	2-2k Ω	4-7k Ω	16k Ω	27k Ω	47k Ω	82k Ω	430k Ω	1-2M Ω	5-1M Ω	9-1M Ω
47 ohms	750 ohms	2-4k Ω	5-6k Ω	18k Ω	30k Ω	51k Ω	91k Ω	470k Ω	1-5M Ω	6-2M Ω	10M Ω
91 ohms	1k Ω	3-3k Ω	6-8k Ω								

Total:

SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS. 10/- per 100 of any one value. 3/- per dozen of any one value. Smaller quantities 6d each.

As available. In following values. Tick those required.

2pF	5pF	12pF	25pF	50pF	80pF	135pF	180pF	250pF	680pF	1,000pF	2,500pF
3-9pF	6pF	15pF	27pF	58pF	82pF	140pF	190pF	330pF	800pF	1,100pF	2,700pF
4pF	8pF	18pF	30pF	62pF	100pF	158pF	200pF	500pF	820pF	1,500pF	3,000pF
4-7pF	10pF	22pF	39pF	72pF	125pF	170pF	240pF	600pF	900pF	2,200pF	6,200pF

Total:

COMPARE THESE PRICES!!

MULLARD POLYESTER CONDENSERS

1,000 pF 3d ea. 400V
1,500 pF 3d ea.
1,800 pF 3d ea.
2,200 pF 3d ea.
0-15 µF 6d ea. 160V
0-22 µF 6d ea. 160V
0-27 µF 6d ea. 160V
1 µF 1/- ea. 125V

No. Price

Total:

25% discount lots of 100 per type.
50% discount lots of 1,000 per type.

TRANSISTOR BARGAIN! THEY CAN'T GET ANY CHEAPER!!!

P.N.P. Audio, Untested, unmarked. MAINLY O.K., 10/- per 100.
N.P.N. Silicon, R.F. types, unmarked. ALL USABLE, 10/- per 50.
POWER OUTPUT (Similar OC35) ALL TESTED, 4/- ea; £2 doz.

SILICON PLANAR TRANSISTORS. ALL TESTED. NO LEAKS OR SHORTS

Gain of 20/50, 6d ea.; 50/100, 9d ea.; 100/200, 1/- ea.

LIGHT SENSITIVE TRANSISTORS. 2/- each.

LIGHT SENSITIVE DIODES. Can be used to control any transistorised device. 1/- each. 75/- per 100. £25 per 1,000.

THYRISTORS 400V BTY79, 7/6 ea. SCR51 (10A), £1 ea.

RECTIFIERS Latest type. All marked. 800V peak, 1A mean current type IN4006

2/6 ea. 24/- doz. £7/10/- 100.
S.T.C. 3/4 (400V), 2/6 ea. 24/- doz. £7/10/- 100.
BYZ 13 or 19 (6A), 2/6 ea. 24/- doz. £7/10/- 100.
BY127, 2/6 each. 24/- dozen. £7/10/- per 100. £50 per 1,000

RECORDING TAPE GIVE-AWAY!

ALL BRITISH MADE, BEST QUALITY!

5in Standard 7/6, 5 1/2in Standard 9/-, 5 1/2in Long-play 12/-, 7in Standard 12/-, 7in Long-play 16/3, 3in "Odd-ends" Mimmum 150ft 2/3.

MAINS DROPPER TYPE RESISTORS. Hundreds of types from 0-7 ohm upwards. 1V to 50V. A large percentage of these are Multi-tapped droppers for radiotelevision. Owing to the huge variety these can only be offered "assorted", 10/- per dozen.

GIANT SELENIUM SOLAR CELLS. Last few to clear at half price! Circular, 67mm diameter 5/- each. 50mm x 37mm. 3 for 10/-.

SKELETON PRESETS. Mixed. 6/- dozen.

VOLUME CONTROLS. 1/2MΩ, 1MΩ, with D.P. switch. 5k (no switch) all 2/-.

RECORD PLAYER AMPLIFIERS. All transistor. Complete with screened input lead, volume control and speaker leads. This excellent unit also has built-in rectifier and smoothing components enabling same to be used direct on 6 to 9V a.c. supply. Small number only. Cannot be repeated at this price! 30/- each.

TRANSISTOR RADIOS. Fantastic bargain! Tremendous value! Superb quality sound from large speaker! Excellent sensitivity! Complete with ear-piece, battery and plastic carrying case, all packed in a colourful presentation box. You would expect to pay £5—but our price due to huge purchase is only 37/6!!!

CO-AXIAL CABLE. Semi-air spaced. 8d yd 60 yd rolls 30/-, plus 4/6 postage.

CRYSTAL TAPE-RECORDER MIKES. 12/- each.

CRYSTAL EARPIECES WITH PLUG. 5/- each.

MAGNETIC EARPIECES. No Plug. 1/6 each.

THIN CONNECTING WIRE: 10 yds 1/-, 100 yds 7/6, 1,000 yds 50/-.

RECORD PLAYER CARTRIDGES

ACOS GP67/2, 15/- (Mono)
GP91/3, 20/- (Compatible)
GP93/1, 25/- (Stereo)
GP94/1, 30/- (Stereo, ceramic)
GP93/1 with diamond needle, 32/6
GP94/1 with diamond needle, 37/6

TRANSISTORISED FLUORESCENT LIGHTS. 12V.

BV, 12in tube, Reflector type, 59/6

15W 18 in tube, Batten type, 79/6

Complete with tube. Postage 3/-

TRANSISTORISED SIGNAL INJECTOR KIT 10/-

TRANSISTORISED SIGNAL TRACER KIT 10/-

TRANSISTORISED REV. COUNTER (CAR) 10/-

(State Positive or Negative earth)

VERO-BOARD

2 1/2 x 1 x 0-15in, 1/3 17 x 3 1/2 x 0-15in, 14/8
3 1/2 x 2 1/2 x 0-15 in, 3/3 3 1/2 x 2 1/2 x 0-1in, 4/2
3 1/2 x 3 1/2 x 0-15in, 3/11 3 1/2 x 3 1/2 x 0-1in, 4/9
5 x 2 1/2 x 0-15in, 3/11 5 x 2 1/2 x 0-1in, 4/7
5 x 3 1/2 x 0-15in, 5/6 5 x 3 1/2 x 0-1in, 5/6
17 x 2 1/2 x 0-15in, 11/-

Spot Face Cutter 7/-, Pin Insert Tool, 9/6.

Terminal Pins, 3/6 for 36.

Spot Face Cutter and 5 1/2 x 1in boards, 9/9.

These prices cannot be repeated. Order now. Don't forget to add your name and address! Please include suitable amount to cover post and packing. Minimum 2/-.

G. F. MILWARD - DRAYTON BASSETT - Nr. TAMWORTH, STAFFS - Phone TAMWORTH 2321

NEWS BRIEFS

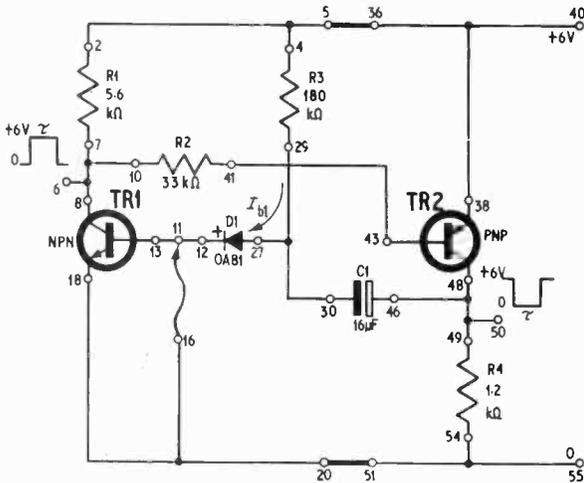


Fig. 3.8 Alternative monostable circuit using one npn and one pnp transistor

Note that the circuit includes a diode in the base lead of TR1. This shields the base from the drop in voltage to $-V_{CC}$ which occurs at the junction of R3 and C1 at the instant of switching and therefore eliminates the possibility of reverse bias breakdown of the base-emitter junction.

It is worth remembering that the base-emitter junctions of many modern silicon transistors can break down by the application of only a few volts reverse bias.

The important voltage waveforms are shown in Fig. 3.7, which includes the effects of finite values of $V_{be(sat)}$ and $V_{ce(sat)}$, ignored in the analysis above.

Interesting modifications can be made to the demonstration circuit if R_4 is replaced by a 6V, 100mA bulb or a 180 ohm relay, the design procedure being used to calculate the values of the other components. If the bulb circuit is tried, the transistor used for TR2 must be capable of operating safely at a 100mA collector current. Any npn TO-5 canned device should be suitable.

COMPLEMENTARY MONOSTABLE

In the previous circuit, npn transistors could be replaced by pnp transistors if the polarities of the supply and diode were reversed. If C1 is an electrolytic or tantalum capacitor, its polarity would also need reversing.

In addition to the straightforward circuits using either npn or pnp transistors, it is possible to use both types of device in the same circuit as shown in Fig. 3.8. This so-called "complementary circuit" is the same as Fig. 3.6 except that TR2 has been turned "upside down".

Note that in this circuit, when TR1 is on, receiving base current via R3 its collector voltage is approximately zero. The base voltage of TR2 is almost V_{CC} because V_{be} for TR2 is small. R2 therefore passes base current to TR2 so this transistor is on as well.

Both are switched off during the quasi-stable state of period τ . The calculation of component values is the same with this circuit as with the other and the formula for the period τ is again given by $\tau = 0.69CR$.

However, the recovery time constant is not C_1R_4 in this case (it is shorter in fact) because of the more complicated charging path for C1 after the second switching instant. The circuit is easily triggered by momentarily shorting the base of TR1 to the bottom rail by means of a jumper lead as before.

To be continued

Air Ionization

AN instrument that "negatively ionizes the air" has been produced by Medion Ltd. The instrument, named Airtone, has been designed with the needs of hay fever, asthma and migraine sufferers particularly in mind. It has been stated that "invigorating air is a balanced distribution of electrically-charged air molecules called ions. Unfortunately, present-day conditions result in air which is deficient in ions and in which the balance between those with a positive and negative charge is seriously disturbed." The Airtone has been designed to combat this situation.

Airtone is fully transistorised, incorporates a double probe radiation and focusing system and is claimed to be already well proven in clinical and other applications.

PLER Monitoring System

A NEW system called PLER after its location (at the Royal Canadian Air Force's Primrose Lake Evaluation Range) is now being used to track aircraft and measure their nose temperature or the structural stress on either wing while in flight.


The equipment is initially to be used in test programmes for ground weapons delivery systems and pilot training in bombing techniques. Ground radar units detect and record analogue signals from various sensing devices on the aircraft and convert them into digital signals for processing by a Honeywell DDP 516 computer. The results are projected on a circular plotting board and also retained on high speed magnetic tape as a permanent record.

More Reliable Meter

A TRANSISTOR controlled parking meter designed to run for 12 months from a single specially developed Mallory battery is now being used, for the first time, in West Germany.

The meter, called the Parkatron, is of completely new design and is controlled by two printed circuits. The relation between the value of the coin and the parking time can be programmed and the meter will automatically assess the value of up to three different coins.

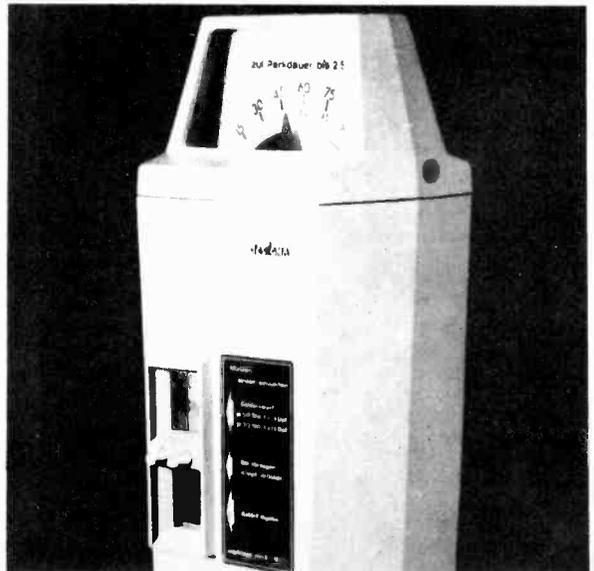The shape of the meter is slightly different from those in use in this country (see below) but perhaps we will soon see this type in Britain—unfortunately electronics brings improved reliability to everything!



AUDIO TRENDS

By F. C. JUDD

THE success or otherwise of the recent Audio Fair, held for the first time at Olympia and combined with the Photo-Cine Fair, is still a subject for discussion in hi fi circles. Many manufacturers claimed greater benefits despite the fact that the first scheduled day of the fair was rendered null and void by an industrial dispute.

At the moment, however, we are literally between "audio fairs" for, as reported in the last edition of *Audio Trends*, the Federation of British Audio Promotions Limited are running a hi fi exhibition in April 1970 at the Skyways Hotel, near the London Heathrow Airport.

Confirmed dates are now April 24 to 26 inclusive with the first day set aside for trade and press visitors only. For the remainder of the days the exhibition will be open to the public who will be admitted by ticket only, these being obtainable from local hi fi equipment dealers or from the Federation of British Audio Promotions Limited, 49 Russell Square, London, W.C.1.

NEW TUNER AMPLIFIER

Few manufacturers have yet exploited the possibilities of integrated circuits although many are now using field effect transistors. The new Japanese-made Akai AA-6600 stereo tuner amplifier, however, features both integrated circuits and f.e.t.'s.

The tuner front end employs f.e.t.'s for low noise and extra sensitivity followed by i.c.'s in the i.f. stages for high selectivity. The amplifier section caters for tape and pick-up and has a frequency response (according to

the maker's specification) of 20-50,000Hz \pm 3dB. The power output is rated at 37.5 watts r.m.s. (or 50 watts music power) per channel for an 8 ohm load.

Features include tape monitoring, loudness control, headphone jack and switchable double speaker connections, i.e. for two speakers per channel. The retail price of this new Akai stereo tuner amplifier was not available at the time of compiling this report but should by now be obtainable from the U.K. distributors—Rank Audio Visual Limited, P.O. Box 70, Great West Road, Brentford, Middlesex.

FIRST UHER STEREO AMPLIFIER

An interesting new stereo amplifier is the first ever from the German Uher company who are already well known for their tape recorders. The CV140 is rated at 35 watts r.m.s. per channel with a 4 ohm load (70 watts music power per channel) and has a frequency response of 20-20,000Hz \pm 1dB.

Six input sockets (DIN) provide for low impedance microphone, magnetic or ceramic pick-up, and tape recorder. All inputs are linked to a selector switch and all functions except volume, tone controls and balance are selected by push button.

A special feature of the CV140 is a front panel meter for monitoring the level of all input signals, which can




The Hydraulic Reference Turntable by Transcriptors Limited

be individually adjusted by preset controls. This amplifier is of course transistorised and retails at £166. Distributors are Bosch Limited (Uher Division), Rhodes Way, Radlett Road, Watford, Herts.


TRANSCRIPTION REFERENCE TURNTABLE

Perfect reproduction from records is the aim of most hi fi enthusiasts and a weak link in the hi fi chain could well be the record transcription unit. The "Transcription Hydraulic Reference Turntable" is an

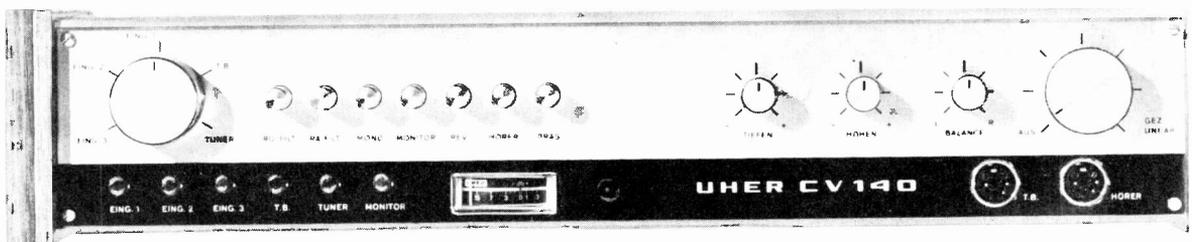The new Uher CV140 stereo amplifier has a built-in level meter for checking all input signals




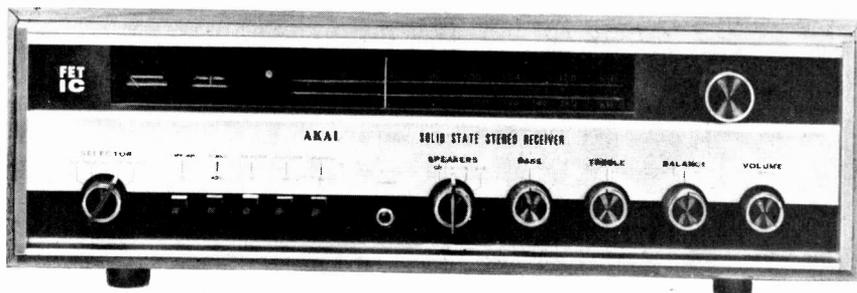The new Akai AA-6600 stereo tuner amplifier features integrated circuits and field effect transistors



attempt to offer what might be considered at the moment as the ultimate in record transcription units. It is a precision instrument designed to perform to a very rigid specification.

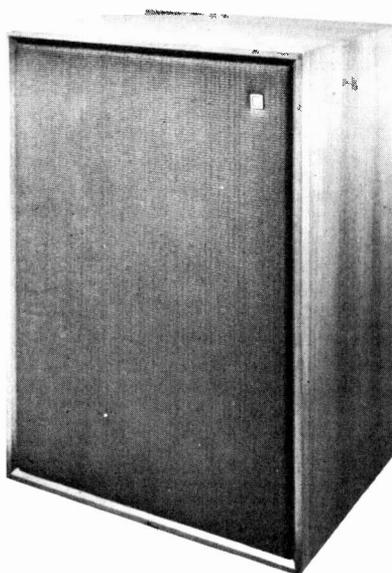The full technical details would take up the whole space devoted to this feature. The photograph, however, gives some idea of the complexity of this turntable which has a claimed total wow and flutter performance of only 0.06 per cent.



The Goodmans "Magister" loud-speaker

It operates at two speeds (33 and 45 r.p.m.) and has a built-in illuminated stroboscope. The makers claim that friction generated by the "unipivot" pick-up arm is so low in all planes as to defy measurement.

This instrument has a high performance, but is nevertheless very costly. The turntable unit costs £81 12s 6d plus £17 17s 6d purchase tax and the pick-up costs £19 2s 8d plus £3 13s 8d purchase tax. (These prices are subject to alteration.) For further details, write to Transcriptors Limited, 551 Holloway Road, London, N.19.

40 WATT "MAGISTER"

With transistorised amplifier outputs going up, and with the output impedance now reasonably firmly established at 8 ohms nominal, there is a demand for complementary matching loudspeakers.

The new Goodmans "Magister" fulfils the demand for it has a power handling capacity of 40 watts r.m.s. and an impedance of 8 ohms. It features a 15in bass speaker, a specially designed 5in mid-range speaker and two custom made treble units. The cabinet measures 27in x 20in x 14in and is available in teak or walnut finish, price £57. Details from dealers or Goodmans Loudspeakers Limited, Axiom Works, Lancelot Road, Wembley, Middlesex.

POCKET SIZED ELECTRONIC ORGAN

Many readers will no doubt have seen the "Stylophone" featured by Rolf Harris on television and although really unrelated to hi fi, it is worth mentioning for the benefit of those who feel the P.E. Electronic Organ a little too ambitious for them.

The "Stylophone" is a complete miniature 1½-octave electronic organ with a pleasing tone and vibrato. Despite its built-in 3in speaker it delivers a surprisingly large volume, enough in fact to play with say a piano accompaniment or the recorded accompaniment available on a 45 r.p.m. disc from the makers Dubreq Studios Limited, 275-281 Cricklewood Broadway, London, N.W.2.

It is a monophonic instrument with standard keyboard layout for the notes, but instead of pressing the keys, a pen-like stylus makes contact with them, thus producing the required notes. It has an output for direct connection to an external amplifier or a tape recorder.

The Stylophone retails at £8 10s and the accompaniment record complete with a tune book are available from the makers as above or musical instrument dealers. The record and tune book costs 10s plus 1s 6d purchase tax.

The "Stylophone" pocket sized electronic organ features a unique stylus contact keyboard system




LOOK!

PRACTICAL!

VISUAL!


EXCITING!

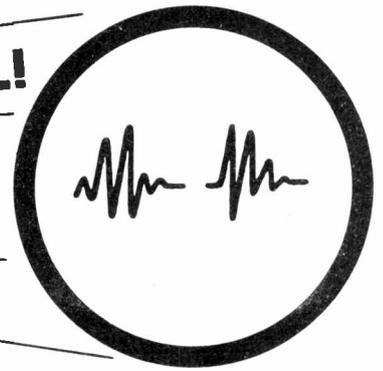

a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .


1 ▶ **OWN and HANDLE** a

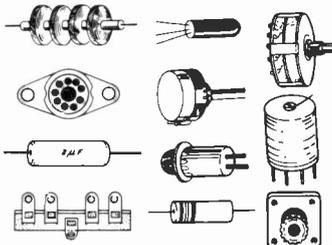complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ **BUILD and USE**

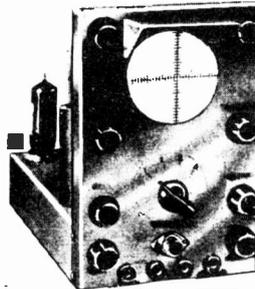a modern and professional **CATHODE RAY OSCILLOSCOPE**



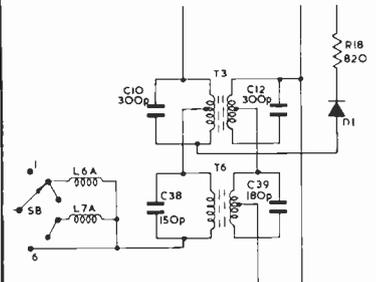3 ▶ **READ and DRAW and UNDERSTAND**
CIRCUIT DIAGRAMS



4 ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E.2

2 1/2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/4kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit **£3.15.0**. Post and ins. 7/6 or add up model **£4.15.0**. Post & ins. 7/6.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, resistor holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-efficient, mostly resin filled. Kit A—15-20w. 19/6. Kit B—30-40w. 19/6. Kit C—80w. 19/6. Kit E—65w. 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes, 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element, new plastic case 5/6 each, 3 heat model 7/6.



HIGH CAPACITY ELECTROLYTICS

Brand new, not ex equipment.
100 mfd 25v, 1/2 each, 12/- doz.
200 mfd 25v, 1/6 each, 15/- doz.
500 mfd 12v, 2/- each, **£1.1.0** doz.
1,000 mfd 12v, 3/- each, **£1.10.0** doz.
5,000 mfd 12v, 4/8 each, **£2.5.0** doz.
10,000 mfd 12v, 5/8 each, **£3.0.0** doz.
10,000 mfd 15v, 8/6 each, **£4.10.0** doz.
15,000 mfd 10v, 10/6 each, **£5.0.0** doz.
60,000 mfd 8v, 22/- each, **£10.0.0** doz.
70,000 mfd 13v, 40/- each, **£20.0.0** doz.

TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6.

TOGGLE SWITCH

3 amp 280v with fixing ring 1/6 each, 18/- doz.



80 OHM BALANCED ARMATURE EAR PIECE

Usable as microphone or loudspeaker 4/6 each.

MINIATURE EAR PIECE

As used with imported pocket radio 1/6 each 15/- doz.

ISOLATION SWITCH

20 Amp D.P. 250 volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on, 4/6, 48/- per dozen.



FLEX BARGAINS

Screened 3 Core Flex. Each core 14/0076 Copper PVC insulated and coloured, the 3 cores laid together and metal braided overall. Price **£3.15** per 100 yds. coil.

15 Amp 3 Core Non-kink Flex. 70/0076 insulated coloured cores, protected by tough rubber sheath, then black cotton braided with white tracer. A normal domestic flex as fitted to 3 kw. fires. Regular price 3/8 per yd. 50 yd. coil **£4.10.0**, or cut to your length 2/6 per yard.

10 Amp 3 Core Non-kink Flex. As above but cores are 26/0076 Copper. Normal price 2/6 per yd. 100 yd. coil **£7.10.0**, or cut to your length 1/9 yd.

6 Amp 2 Core Flex. As above, but 2 Cores each 20/0076 as used for Vacuum Cleaners, Electric Blankets, etc. 39/6 100 yd. coil.

15/20 AMP CONNECTORS

Polythene insulated 12 way strip 2/6 each 24/- doz.



13 AMP FUSED SWITCH

Made by G.E.C. for connecting water heater etc., into 13 amp ring main. Flush type 3/6 each, 30/- doz. Metal boxes for surface mounting, 1/6 each, 15/- doz.

REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types.

Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1 amp up to 300 volts. Price 2/6 each, 24/- dozen.

Standard. 2in. long x 3/16in. diameter. This will break currents of up to 1 amp, voltages up to 250 volts. Price 2/- each, 18/- per dozen.

Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp, 200 volts. Price 6/- each, 53/- per dozen.

Small ceramic magnets to operate these reed switches 1/8 each, 12/- dozen.

DIGITAL CLOCK

An imposing instrument ideal for modern reception centre or for Managing Director's office—definitely a showpiece to create interest and efficiency—mains frequency controlled so always keep right time without adjustment in black semi-matt perspex case—made up, tested and guaranteed—offer for only the cost of components **£29.10.0**, post and insurance 10/-.



MINIATURE EXTRACTOR FAN

Beautifully made by famous German Company. PAPST System, 230/240 A.C. Mains operated, size 3 1/2in. x 3 1/2in. x 2in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/-.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs. Supplied complete with 6 feet of heavy cable and 13 amp plug. Similar advertised at £5. Our price 39/6 in kit form + 4/6 P. & I. or 45/- + 4/6 P. & I. wired up.


Horstmann "Time and Set" Switch

(A 15 min Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6, p. & ins. 4/6.



24 HOUR TIME SWITCH

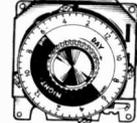Mains operated. Adjustable Contacts give on/off per 24 hours. Contacts rated 20 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 plus 3/6 postage and insurance, a real snip which should not be missed.




PROTECT VALUABLE DEVICES

FROM THERMAL RUNAWAY OR OVER-HEATING: Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by giving thermostats in strategic spots on the casing. Our contact thermostat has calibrated dial for setting between 90 deg. F. to 190 deg. F. or with the dial removed range setting is between 80 to 800 deg. F. Price 10/-.



BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4 1/2 volts. Supplied complete with 2 spools ready to install. Record, Replay and the sensitive M4 type intended for use with transistor amplifier. Price 79/6. Post and insurance 4/6.

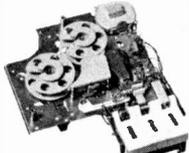


ATLAS SLIMLINE FLUORESCENTS THE TWENTYLITE

A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio frequency suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1 unit). Measures 2ft. long. Ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembly ready to install. 4ft. twin model 59/8. Postage and insurance 6/6 extra.

1 WATT AMPLIFIER & PREAMP

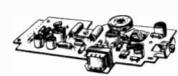5 transistors—highly efficient, made for use with tapehead G4 but equally suitable for microphone or pick up—limited quantity 29/6. Full circuit diag. also shows tape controls 5/-.



VARYLITE

Will dim incandescent lighting up to 800 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob **£3.19.6**.

FULL F1 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi loud and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specific 3 for 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in. 12in. over mounting lugs—Baffle hole 11in. Diam.—Mush plate, 4 holes—1in. diam. on pitch circle 11in. diam. Overall height 5 1/2in. A £6 speaker offered for only **£3.9.6** plus 7/6 p. & p. Don't miss this offer. 15in. 30 watt **£7.19.6**, 18in. 100 watt **£24.10.0**.



Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semiconductor add 1/- post. Over £1 post free. S.A.E. with enquiries please.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

AC FAN

Small but very powerful mains motor with 5 1/2in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient, 17/6, post 4/6. Mounts from back or front with 4BA screws.



750 MICRO AMP MOVING COIL METER

2 1/2in. ex. W.D. but brand new and unused 19/6.

0.0005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.

HEAT AND LIGHT LAMP

275W internally nipped bulb with b.c. end for plugging into lamp holder, 19/6 each, plus 4/6 postage and insurance.

COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above, 12/6 each, plus 4/6 post. 26 doz. post paid.

Battery Record Player. Made by Collaro. This is made up on a unit plate with speed selector and pick-up. The turntable is a heavy one and measures approximately 9 1/2in. Pick-up is fitted with the famous "Studio" cartridge. Price 69/6, postage and insurance 6/6.

E.H.T. Condenser. 28KV, 0.001mfd. Suitable for transmitting test conditions 6A at 300k/c. Bakelite case, 18/6 each.

55 Watt Tubular Element. Very well made unit. The element is wound on a porcelain former then encased in a brass tube terminated with beaded leads 12in. long. Normal mains voltage. Price 5/- each or 54/- per doz.

Press to Make Switch. Double pole, 5 amp contacts or can be used as single pole, 10 amp, contacts 250 volt working. Single hole fixing. 2/6 each, 24/- dozen.

Door Switch. Contacts open when plunger is depressed. Prevents lights being left on. 15 amp contacts. 230 volt working. Made by Arrow. 3/6 each, 36/- per dozen.

Rotary Appliance Switch. 16 amp, 230 volt on moulded ceramic base. Operated by pointer knob (not supplied). 2/- each, 18/- per dozen.

1/40th h.p. Motor. Made by the French (Casnor) Company. This is an excellent totally enclosed motor, powerful enough to operate small lathe, drilling machine, washing machine, etc. Its speed is 1,450 r.p.m. Made for normal 50 cycle, 230/250 volts mains, totally enclosed, size 2 1/2 x 3 1/2in. dia. with 1in. of 1/4in. spindle. Price 19/6 plus 4/6 postage and insurance.

THERMAL CUTOUT

A miniature device 1/4in. dia. on one screw fixing mount—can be used for motor overload protection—fire alarm—soldering iron switch off, etc.—15 amp contacts open with flame, radiant or conducted heat 1/6 each, 15/- doz. 25 100.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 1/6 plus 1/- post. Suitable box for wall mounting, 5/-, P. & P. 1/-.

Type "B" 15 amp. This is a 17in long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven kiln immersion heater or to make flame-stat or fire alarm.

Type "C". We call this the Ice-stat as it cuts in and out at around freezing point, 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/-.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid, particularly those in glass tanks, vats or sinks, thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—dechlorinators and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.

ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CRO 2TH

Also 102/3 Tamworth Road, Croydon

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

“Academic barrier”

Sir—In your thoughtful editorial last month, “The Non-Registered Engineer”, you expressed concern over the composite engineering register to cover chartered engineers, technician engineers and technicians which the Council of Engineering Institutions intends to set up in collaboration with over 40 organisations for “non-chartered engineers” and technicians of all disciplines.

It may not generally be understood that the award and registration of legally protected titles and designatory initials will not be dependent upon educational attainment alone. Evidence of practical training and experience will also be required, and one may feel sure that the circumstantial human aspects to which you have referred will not be overlooked by those now planning the registration arrangements.

Engineers and technicians whom you felt might be worried about the constraints such an “academic barrier” could impose upon ingenious minds, or be wondering whether ambition and progress might be frustrated for some, would be looking at registration in isolation, for it will be but the “end product”—the identification and status derived

from education, training, experience and responsibility.

Designers of proposed new education and training patterns are stressing the importance of ample opportunities being given for the inventive and other creative work that you mentioned. For instance, the recently published recommendations of the Engineering Industry Training Board, “The Training of Technician Engineers”, with their factors of basic training, general training, and then the objective training that is designed to develop expertise, should foster those opportunities.

The improved standing that registration could bring about, and the better opportunities for education and training now being developed, should combine to offer greater incentive to young people to seek a worthwhile career in industry where, it was authoritatively stated recently, a force of over one million technician engineers and technicians will be needed by 1975.

E. A. Bromfield,
Secretary,

The Institution of Electrical and
Electronics Technician Engineers,
London, W.C.2.

I have no doubt that the professional bodies make every attempt to assay the

practical qualities of candidates, in addition to examining their educational standards. The burden of my editorial was a different matter—concern for the large number of technicians and engineers usefully engaged in industry who, in the eyes of the Institutions, would be deemed “unqualified”.

For various reasons these technicians and engineers do not wish, or are unable, to undertake the study necessary in order to pass the examinations of the professional bodies. Perhaps it is a pity that they do not make this effort, but the point is that countless individuals are happy this way. Most of them no doubt enjoy their work and satisfy their employers. Status seeking is not their goal. Amongst their numbers are likely to be some really bright brains and—this is the crux of my argument—we cannot afford to jeopardise this source of novel and stimulating ideas.

—Ed.

Guildford group

Sir—An inaugural meeting of electronic enthusiasts was held on Saturday, November 22, at Chalklands, Hog’s Back, Seale, Farnham, when it was decided to form the Guildford and District Group of the British Amateur Electronics Club. Four members were present; there are in addition two other members in the group. Mr E. J. Phillips was appointed chairman and secretary.

Future plans of the group, which will hold monthly meetings, were discussed and it is anticipated that members will combine their efforts to produce some interesting projects after their next meeting.

If any inexperienced enthusiasts or experts wish to join they should apply to the secretary at the above address.

E. J. Phillips,
Farnham,
Surrey.

NEWS BRIEFS

New Research Centre

A NEW research centre is to be built for the Post Office on the former Martlesham Heath airfield near Ipswich, Suffolk. Construction of the new centre, said to be the finest of its kind in Europe, will commence in the near future and is expected to be complete towards the end of 1972.


The new centre will house the present Research Department stationed at Dollis Hill in North London; there will be plenty of space for expansion and for large scale field experiments. It is hoped that the new centre will attract graduates to a career in research to provide the best possible telecommunications and postal systems for Britain, thus maintaining her place as a world leader in the fast developing global communications system.


With a staff of up to 2,000 engineers, scientists and supporting technicians, the centre will bring increased spending power and new employment opportunities to the Ipswich area.

Solid State Lamps

A SERIES of new high power infrared solid state lamps have recently been introduced by the General Electric Company of the U.S.A. These small size lamps are particularly suited for use in computers and tape reading equipment. The high power output is obtained by a double lens construction. An inner plastics lens, covering the gallium arsenide chip, is surmounted by a conventional glass lens which hermetically seals the unit.

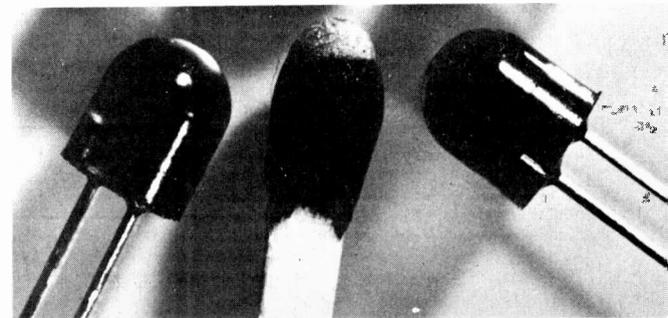The photograph below illustrates the size of the new lamps—their diameter is $\frac{1}{4}$ in.



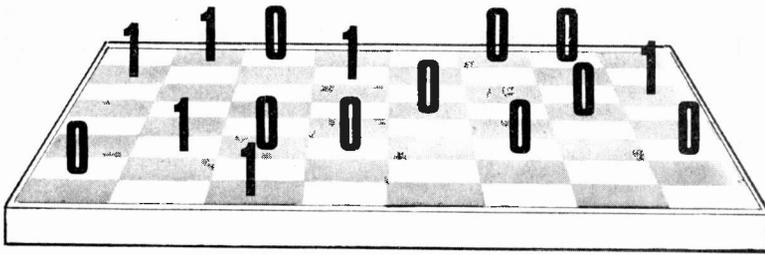

CHESSBOARD COMPUTER

By J. F. ROWLANDS

THIS demonstration of binary arithmetic was recorded by John Napier, the Scottish mathematician, and inventor of logarithm tables, as long ago as 1580 a.d.

As a matter of interest this kind of binary arithmetic is incredibly ancient—quite as old as the chessboard itself which is so archaic that no-one knows just when the first one was made—certainly it is more than 4,000 years ago. It was used long before the decimal system was perfected and quite apart from the binary computer it is used extensively today, maybe in ways that we do not readily recognise, such as the piano keyboard, in which an octave above a given note is exactly double the frequency of that note.

The binary system is essentially a *practical* system of arithmetic—given a simple conversion table you can do any calculation without any knowledge of multiplication tables, or how to “carry” in addition, or “borrow” in subtraction—it is used, unwittingly, by musicians, joiners and greengrocers as the most convenient method.

In radio circuitry, electrolytic capacitors are usually 1, 2, 4, 8, 16, 32, 64 μ F, a typically convenient binary series. Our system of balance weights (though soon to be replaced by the metric system) is another example: 1 dram, $\frac{1}{4}$ ounce, $\frac{1}{2}$, 1, 2, 4, 8 ounces, 1 pound.

Binary arithmetic is of interest today because the operations involved are closely analogous to the principle of the modern electronic binary computer. Those who are familiar with electronic switching circuits will recognise that the squares on a chess board could represent electronic switches. The placing of a counter in a square represents an impulse to the switch, and the presence or absence of the counter indicates ON or OFF respectively.

Other analogies will make themselves obvious later, but it must be realised that manual operation of binary arithmetic can be a very long and tedious process and quite impractical, but the comparatively simple rules, plus the fact that the numerous operations can be carried out electronically at fantastic speeds makes the system ideal for the modern computer.

It is not intended in this article to give details of the circuits of the electronic switches which the squares represent, but the on/off analogue will be grasped by those who are even slightly familiar with this aspect.

CONVERSION

The chessboard must have a fairly wide margin, and if this is not so the board must have strips of cardboard glued to three of its sides. The numbers of the binary series, 1, 2, 4, 8, 16, and so on, each number being twice the value of the previous one, is printed on it as shown in Fig. 1.

About two dozen counters of one colour are required, and about a dozen of a different colour for use as “markers” in division.

The first rule in binary arithmetic is: “All ordinary numbers must be expressed in terms of the numbers of the binary series.”

For the purpose of this demonstration, this can be done by subtracting from the ordinary numbers, and in turn from the remainders, the highest binary factor possible, until the remainder is nil.

For example, $136 - 128 = 8$, and $8 - 8 = 0$, so 128 and 8 are the binary factors of 136.

This method of extracting the binary factors, more often than not, requires more effort and arithmetic than that required to do the original calculation in the ordinary way, and Napier drew up a simple conversion table so that no ordinary calculation was called for.

In the electronic computer the conversion is done as a part of the process known as “programming”. The result is fed into the machine in the form of a punched

16384	8192	4096	2048	1024	512	256	128		
16384	8192	4096	2048	1024	512	256	128		
								128	128
								64	64
								32	32
								16	16
								8	8
								4	4
								2	2
								1	1
128	64	32	16	8	4	2	1		
128	64	32	16	8	4	2	1		

Fig. 1. Chessboard layout with margin numbers

ELECTROVALUE

Everything brand new and to specification • Large stocks • Good service

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/4W	5%	100 Ω-220k Ω	E12	18d	16d	15d
C	1/2W	5%	4.7 Ω-1M Ω	E24	2.5d	2d	1.75d
C	1/2W	10%	4.7 Ω-10M Ω	E12	2.5d	1.75d	1.5d
C	1/2W	5%	4.7 Ω-10M Ω	E24	3d	2.25d	2d
MO	1/2W	2%	18 Ω-1M Ω	E24	9d	8d	7d
C	1/2W	10%	4.7 Ω-10M Ω	E12	4d	3.25d	3d
WW	1W	10%	0.22 Ω-3.3 Ω	E12	15d all quantities		
WW	3W	5%	12 Ω-10k Ω	E12	15d all quantities		
WW	7W	5%	12 Ω-10k Ω	E12	15d all quantities		

CODES: C = carbon film, high stability, low noise. MO = metal oxide, Electrofil TR5, ultra low noise. WW = wire wound, Plessey.
VALUES: E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades. E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2.2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.
 Prices are in pence each for each ohmic value and power rating. (Ignore fractions of one penny on total resistor order.)

COLVERN 3 watt wire-wound potentiometers: 10 Ω, 15 Ω, 25 Ω, 50 Ω, 100 Ω, 150 Ω, 250 Ω, 500 Ω, 1k Ω, 1.5k Ω, 2.5k Ω, 5k Ω, 10k Ω, 15k Ω, 25k Ω, 50k Ω. Price only 5/6 each.

CARBON TRACK POTENTIOMETERS: Double wiper ensures minimum noise level. Long plastic spindles.

Single gang linear:	220 Ω, 470 Ω, 1k Ω, etc. to 2.2M Ω	each	Dual gang linear:	4k Ω, 10k Ω, 22k Ω, etc. to 1M Ω	each
Single gang log:	4k Ω, 10k Ω, 22k Ω, etc. to 2.2M Ω	2/6	Dual gang log:	4k Ω, 10k Ω, 22k Ω, etc. to 2M Ω	8/6
Any type with 1/2 amp double pole mains switch: extra		2/3	Log/Anti-log:	10k Ω, 47k Ω, 1M Ω only	8/6
			Dual anti-log:	10k Ω only	8/6

FETS n-channel. Low cost general purpose 2N5163, 25V, only 5/- each. Audio/r.f., Texas 2N3819 9/-, Motorola 2N5459 (MPP105) 9/6 each.

NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER, Type SL403A. Only 57/- each. Operates with 18V power supply. Sensitivity 20mV into 20M Ω, 3W into 7.5 Ω Application data with two or more P.E., Nov. 69, Stereo Amplifier kit less metalwork £11.18.2 net complete.

30 WATT BAILEY AMPLIFIER COMPONENTS

Transistors for one channel £7.5.6. list, with 10% discount only £6.11.0. Transistors for two channels £14.17.6. list, with 15% discount £12.7.5. Capacitors and resistors for one channel list £2. Printed circuit board free with each transistor set. Complete unregulated power supply kit £4.17.6. mono or stereo, subject to discount. Complete regulated power supply kit £9.5, subject to discount. Further details on application.

SINCLAIR IC10 Integrated Circuit Amplifier and Pre-amplifier. This remarkable monolithic integrated circuit amplifier and pre-amp is now available from stock. The equivalent of 13 transistor/18 resistor circuit plus 3 diodes and the first of its kind ever. It is d.c. coupled and applicable to an unusually wide range of uses as detailed in the manual provided with it. As advertised, post free 59/6 net.

CARBON SKELETON PRE-SETS. Small high quality, type PR. Linear only, 100 Ω, 220 Ω, 470 Ω, 1k Ω, 2k Ω, 4k Ω, 10k Ω, 22k Ω, 47k Ω, 100k Ω, 220k Ω, 470k Ω, 1M Ω, 2M Ω, 5M Ω, 10M Ω vertical or horizontal mounting, 1/- each.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/6 post free. Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC only 51/- post free.

LARGE CAPACITORS. All new stock. High ripple current types: 2,000μF 25V 7/4; 2,000μF 50V 11/4; 5,000μF 25V 12/6; 5,000μF 50V 21/11; 1,000μF 100V 16/3; 2,000μF 100V 18/9; 5,000μF 70V 36/-; 5,000μF 100V 58/3; 1,000μF 50V 8/2; 2,500μF 64V 15/5; 2,500μF 70V 19/6.

MEDIUM ELECTROLYTICS. Axial leads. Values (μF/V): 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 250/50 3/9; 500/25 4/-; 1,000/10 3/-; 500/50 4/6; 1,000/50 6/-; 2,000/25 6/-; Small electrolytics, axial leads: 5/10, 10/10, 25/10, 50/10, 1/- each; 25/25, 47/25, 100/10, 220/10, 1/3 each.

PEAK SOUND ENGLEFIELD KITS

Build it 12 + 12 or 25 + 25. Brilliant new styling and available in two forms: **STEREO 15 WATTS PER CHANNEL.** In kit form with complete amplifier and pre-amplifier modules and power supply. Output per channel into 15 Ω - 12W R.M.S. Price £38.9.0. net. **STEREO 25 WATTS PER CHANNEL.** As above but output per channel into 15 Ω - 25W R.M.S. Price £53.15.0. net. Brief specification: Total harmonic distortion 0.1%. Inputs: Magnetic, Ceramic, Tape, Radio, Signal to noise ratios: Better than 60dB all inputs. O/Load factor 28dB all channels. **ENGLEFIELD CABINET** to house either above assemblies (as illustrated) £5.0.0. net. Other peak sound products as advertised.

MULLARD SUB-MIN ELECTROLYTICS C426 RANGE.

Price 1/3 each. Axial leads. Values (μF/V): 0.6/4; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

WAVECHANGE SWITCHES: 1P 12W; 2P 6W; 3P 4W; 4P 3W long spindles, 4/9 each. Slider switches, double pole double throw, 3/- each.

BARGAINS IN NEW TRANSISTORS

All power types supplied with free insulating sets

2N696	5/6	2N5192	25/-
2N697	5/6	2N5195	29/3
2N706	2/9	40406	16/3
2N1132	9/9	40408	14/6
2N1302	4/-	AC126	6/6
2N1303	4/-	AC127	6/-
2N1304	4/6	AC128	6/-
2N1305	4/6	AC176	11/-
2N1306	6/9	ACY22	3/9
2N1307	6/9	ACY40	4/-
2N1308	8/9	AD140	19/-
2N1309	8/9	AD149	17/6
2N1613	6/-	AD161	
2N1711	7/4	AD162	16/- pr.
2N2218	10/6	AF118	16/6
2N2147	18/9	AF124	7/6
2N2369A	6/9	AF127	7/-
2N2646	10/9	BA102	9/-
2N2924	4/3	BC107	2/9
2N2925	5/3	BC108	2/6
2N2926R	2/6	BC109	2/9
2N2926O	2/3	BC147	4/3
2N2926V	2/3	BC148	3/3
2N2926G	2/3	BC149	4/3
2N3053	5/6	BC153	10/-
2N3054	14/3	BC154	11/-
2N3055	16/6	BC157	3/9
2N3391A	5/6	BC158	3/6
2N3702	3/6	BC159	3/9
2N3703	3/3	BC167	2/6
2N3704	3/9	BC168	2/3
2N3705	3/5	BC169	2/6
2N3706	3/3	BC177	6/3
2N3703	4/-	BC178	5/8
2N3708	2/9	BC179	6/-
2N3709	3/-	BD121	18/-
2N3710	3/3	BD123	24/3
2N3711	3/11	BF178	10/6
2N3904	7/6	BFX29	10/9
2N3908S	7/6	BFX85	8/3
2N3731	23/-	BFX88	7/9
2N3820	25/6	BFY50	4/6
2N3323	10/6	BFY51	4/3
2N3794	3/3	BSX20	3/9
2N4286	3/3	M1480	21/-
2N4289	3/3	M1481	2/-
2N4291	3/3	M1491	30/-
2N4292	3/3	P346A	5/9
2N4410	4/9	V405A	7/9

MAIN LINE AMPLIFIER KITS, as advertised. Prices net. Authorised dealer.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on net items).

POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

ELECTROVALUE

Dept. PE2, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
 Opening Hours: 9-5.30; Sat. 9 a.m. to 1 p.m. Tel.: Egham 5533 (STD 0784-3)

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



EST. 1891

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 151, Intertext House, Stewarts Rd., London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME.....

ADDRESS.....

2-70

INTERNATIONAL CORRESPONDENCE SCHOOLS

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 1R5, DAF96, DF96, DK96, DL96, 4 for 27/-

OZ4	4/8	12K9GT	7/3	DK91	5/9	EF184	5/8	PCL81	8/9	UBC41	9/9
1A7GT	7/8	12SN7GT	6/6	DK92	8/3	EH90	6/3	PCL82	7/-	UBF80	5/9
1H6GT	7/3	19BGG17	6/6	DK96	7/3	EL33	5/9	PCL83	10/-	UBF89	6/9
1N6GT	7/9	20F2	13/6	DL35	5/-	EL34	9/8	PCL84	7/8	UC92	5/8
1R5	5/9	20P3	11/9	DL92	5/9	EL41	10/6	PCL85	9/-	UC84	7/-
1B5	4/3	20P4	18/6	DL94	6/-	EL84	4/8	PCL86	8/3	UC85	7/3
1T4	2/9	26L6GT	5/-	DL96	7/3	EL90	4/6	PEN44	12/6	UCF80	7/8
3B4	5/9	28U4GT	11/8	DY86	5/9	EL500	12/6	PFL200	11/9	UCH42	12/-
3V4	6/-	30C1	6/6	DY87	5/9	EM80	7/6	PL36	9/9	UCH81	6/3
6Y3GT	5/9	30C15	13/-	EABCS90	6/6	EM81	7/6	PL81	7/9	UCL82	7/-
5Z4G	7/6	30C17	16/-	EAF42	10/-	EM84	6/9	PL82	6/6	UCL83	11/8
6J30L2	12/-	30C18	14/-	EB91	2/3	EM87	7/8	PL83	6/6	UF41	10/6
6AL5	2/3	30F5	18/-	EBC33	8/-	EY51	7/6	PL84	6/6	UF80	7/-
6AM6	2/9	30FL1	13/9	EBC41	9/6	EY86	6/6	PL500	13/-	UF85	6/9
6AQ5	4/6	30FL12	14/6	EBF80	6/9	EZ40	8/-	PL504	13/6	UF89	6/9
6AT6	4/-	30FL14	14/9	EBF89	6/3	EZ41	8/-	PL508	23/6	UL41	10/9
6AV6	4/6	30L1	8/6	ECC81	3/8	EZ80	4/8	PM84	7/6	UL44	20/-
6BA6	4/6	30L15	14/-	ECC82	4/9	EZ81	4/9	PX25	10/6	UL84	7/-
6BE6	4/9	30L17	15/6	ECC83	7/-	GZ32	8/9	PY32	10/6	UM84	6/6
6BJ6	8/6	30P4	12/-	ECC85	5/-	GZ34	9/9	PY33	10/-	UY41	7/6
6BW6	13/-	30P12	13/9	ECC91	3/-	KT61	8/9	PY81	5/3	UY85	5/9
6F13	3/6	30P19	12/-	ECC804	12/-	KT66	16/-	PY82	5/3	VP4B	10/9
6F14	9/-	30P19	13/9	ECC80	6/6	N78	17/8	PY83	5/9	W119	7/-
6F23	13/3	30P19	13/6	ECC82	5/9	PABCS0	7/-	PY88	6/9	Z77	2/9
6F25	13/-	30P14	15/6	ECC85	6/-	PC88	10/3	PY800	7/6	AC127	3/6
6J6	3/-	35L6GT	8/6	ECH42	13/6	PC88	10/3	PY801	6/9	AC127	2/8
6K7G	2/6	35W4	4/6	ECH81	5/9	PC96	8/6	R19	6/6	AD140	4/6
6K8G	2/9	35Z4GT	5/-	ECH83	8/3	PC97	8/6	R19	6/6	AF115	3/-
6L18	6/-	6063	12/6	ECH84	7/6	PC900	7/6	R20	12/6	AF116	3/6
68N7GT	4/3	AC/VP210	-	ECL80	7/-	PC84	6/6	U25	13/-	AF117	3/3
6V3	3/3	AZ31	9/6	ECL82	6/9	PCC85	6/6	U26	12/-	AF126	3/6
6V6GT	6/6	B2P9	12/6	ECL83	8/6	PCC88	10/3	U47	13/6	AF127	3/6
6X4	4/3	CCH35	13/6	ECL86	8/-	PCC89	10/6	U49	13/6	OC8	2/3
6X5GT	5/9	CL33	18/6	EF37A	6/6	PCC189	11/6	U78	4/3	OC45	2/3
7B7	7/-	CY31	6/9	EF39	4/9	PCF80	6/6	U91	12/6	OC71	2/6
7C6	6/9	DAC32	7/3	EF41	10/9	PCF82	6/6	U93	8/6	OC72	2/6
10F1	14/-	DAF91	4/3	EF80	4/6	PCF86	11/6	U91	14/6	OC75	2/6
10F18	7/3	DAF96	7/3	EF86	5/3	PCF200	13/6	U301	10/6	OC81	2/3
10P13	15/6	DF33	7/9	EF86	6/3	PCF500	13/6	U329	14/6	OC81D	2/3
12AT7	3/9	DF91	2/9	EF89	5/3	PCF801	6/9	U801	19/6	OC82	2/3
12AU6	4/9	DF96	7/3	EF91	2/9	PCF802	9/-	UABC80	6/6	OC82D	2/3
12AU7	4/9	DH77	4/-	EF94	4/6	PCF805	14/-	UAF42	10/3	OC82D	2/6
12AX7	4/9	DK32	7/6	EF183	5/9	PCF808	14/9	UB41	6/6	OC170	2/6

READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.

Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

PSYCHODELIC LIGHTING UNIT

3 Channel Colour — Organ; Operates from output of record player, tape recorder, etc. Drives up to 1.5 Kw. at 240 volts a.c. per channel. Suitable for the home or discotheque. Complete printed circuit assembly, built and tested. **14 gns.** plus 10/- carriage. Higher power units available on request.

Create 'PHASE' on your tape recordings, records, etc. Unique electronic circuitry enables you to create 'phase' effect at the turn of a knob. Complete printed circuit assembly built and tested. **65/-** plus 2/6 carriage. Battery operated.

SUPER 'FUZZ' UNIT, suitable for electric guitars, etc. Complete printed circuit assembly built and tested. Battery operated. **65/-** plus 2/6 carriage.

S.A.E. with all enquiries. Mail order only.

Electronic Products
98a, Lichfield Street
Walsall, Staffs.

card, or perhaps as a series of channelled impulses recorded on a magnetic tape.

Almost any simple mathematical process can be carried out by binary arithmetic on this chessboard. Details of the routine for addition, multiplication, subtraction and division, will now be given, with a few simple examples as illustrations.

ADDITION

Take, for example $23 + 54 + 87 = 164$

- (1) Convert all numbers to their equivalent binary factors:
 $23 = 16 + 4 + 2 + 1$
 $54 = 32 + 16 + 4 + 2$
 $87 = 64 + 16 + 4 + 2 + 1$
- (2) In the inner side margin place 13 counters in the squares appropriate to the above factors (Fig. 2).
- (3) A basic rule in this type of binary arithmetic is that no square must have more than one counter on it (obviously in an electronic circuit you cannot close a switch which is already closed).

In the example, several of the squares have more than one counter; the routine to rectify this is to remove any counters in excess of one, two at a time. For each pair so removed add one counter to the next higher square. Start by removing the two counters from square 1 and place one more on square 2—making a total of four in this square. Remove these, two at a time placing one for each pair on square 4 which will now have five counters. Remove two pairs of these, leaving one in place and place two counters in the empty square 8, and so on until you have three counters left: one in square 128, one in square 32 and one in square 4. The total is 164, the answer to $23 + 54 + 87$.

Any series of numbers can be added on a 64 square board, as long as the total does not exceed 32,767.

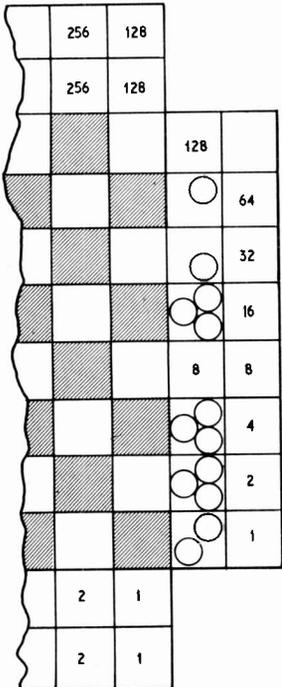


Fig. 2. Arrangement of counters at start of addition

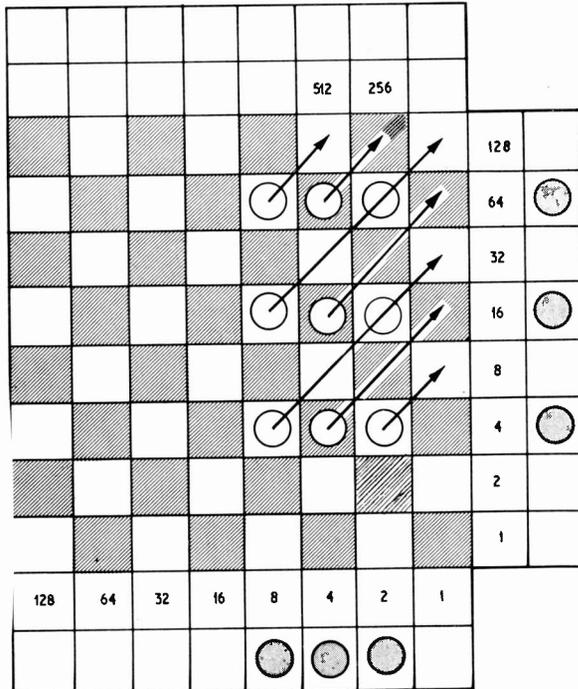


Fig. 3. Move (4) in multiplication

MULTIPLICATION

One example for multiplication could be $84 \times 14 = 1,176$.

- (1) Place markers in the outer side margin representing the binary factors of the larger number (i.e. at 4, 16, and 64 for 84) and in the outer lower margin for the smaller number (at 2, 4, and 8 for 14).
- (2) In the same horizontal row as the highest side marker (64). Place one counter in each square vertically above the markers at the bottom.
- (3) Repeat this in each horizontal row from the other side markers (16 and 4).
- (4) Move all the counters within the chess board diagonally up and right until they are all on the edges of the board next to the inner margins. See Fig. 3.
- (5) Some squares will now have more than one counter, so rectify this by following the method as in "addition".
- (6) The sum of the values of the counters after doing this will be 1,176.

The 64-square board limits the size of the numbers to be multiplied to 255×255 (i.e. a marker in all eight divisions of each margin and a total of 64 counters on the board before the diagonal move), and even this calls for a few imaginary squares to the left of 16,384.

If you can rake up enough counters it should be good practice in addition.

SUBTRACTION

- (1) Start by placing counters in the inner side margin representing the binary factors of the larger number, and similarly for the smaller number in the adjacent column of squares to the left Fig. 4.

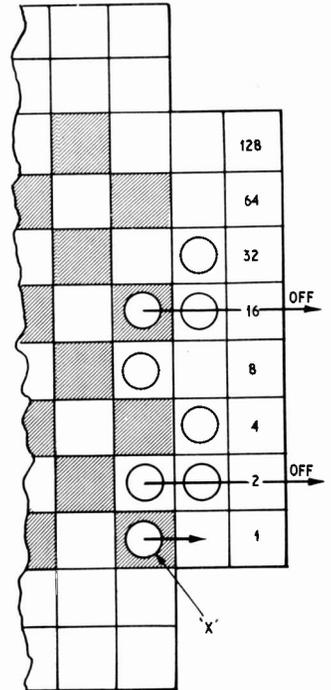


Fig. 4. Arrangement of counters at start of subtraction. Notice the position of the X counter

Table 1: MOVES FOR 54-27

Move	Counter X		Nearest counter above X			Fill in space(s)
	Left	Right	From	To	Remove at	
1		X	4	2	—	NIL
2	X		8	4	—	2
3		X	—	—	2	—
4	X		—	—	2	—
5		X	32	16	—	8, 4, 2
6	X		4	2	—	NIL
7		X	—	—	2	—
8	X		—	—	2	—
9		X	4	2	—	NIL

- (2) Remove any counters which occupy adjacent squares in both columns.
- (3) Move the lowest value counter from whichever column it is in, to the corresponding position in the other column. This counter, which we can call "X", has to be moved from one column to the other repeatedly. Each time it is moved to a different column the following routine has to be carried out with the nearest counter above it.
- (4) The nearest counter above has to be moved down one place, and the intervening empty places (if any) must be filled in with a counter in each. If the nearest counter above is in the *next* square remove it from the board.
- (5) Move counter "X" (Fig. 4) to the other column and repeat the above routine before returning it, and so on until the left-hand column is empty.

To make all this clear, Table 1 shows all the moves of counter "X", and the subsequent movement of the counter above it, required to subtract 27 from 54. Place counters at 32, 16, 4 and 2 in the inner side margin

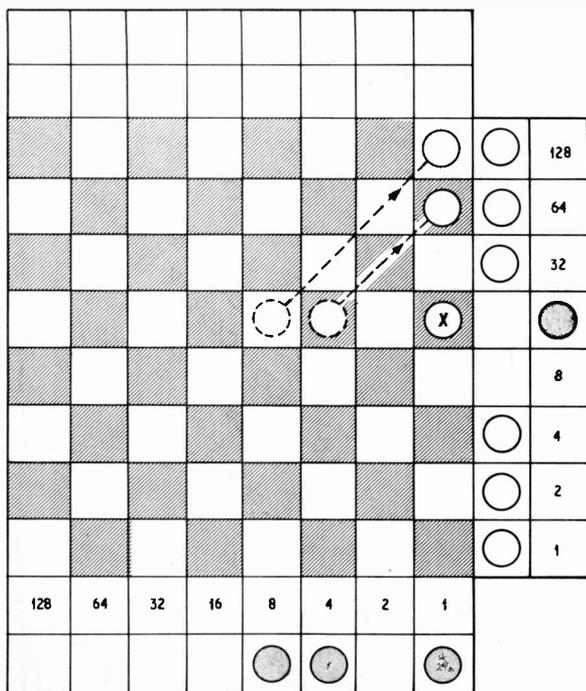


Fig. 5. Move (4) in division

and 16, 8, 2 and 1 in the squares on their left. Remove the "common" counters at 16 and at 2 and move the lowest ("X") counter to the right. Follow the sequences as in the Table.

The answer is the sum of the values of the counters in the margin, i.e. $16 + 8 + 2 + 1$.

Practice subtraction with various numbers, following this procedure exactly. After some practice it will be found that some moves can be "short cut", such as 3 and 4, and 7 and 8 in the chart, by removing both counters without moving X, and carrying on with the next move as though X had moved twice.

It is important to practise subtraction until you can do it confidently because it will have to be done under slightly different conditions in division and unless the principle is understood it can be confusing.

DIVISION

There is nothing difficult about division by binary arithmetic—in fact it is one of the most efficient of "mechanical" methods, the only snag being that the largest number that can be divided on a 64 square board is 255. Numbers up to 32,767 *can* be divided by a modified process, but the simplest solution is to make up a board with 16×16 squares (256). However, the main principles can be shown on the 64 square board with an example such as $231 \div 13$.

- (1) Place counters representing 231 (128, 64, 32, 4, 2, and 1) in the inner side margin, and "markers" of a different colour for 13 (8, 4, and 1) in the outer bottom margin.
- (2) Place a counter in the square to the left of the highest side counter (128) and move it down diagonally until it is in a square vertically above the highest bottom marker (8).
- (3) In the same horizontal row as this counter, place a counter in each square vertically above the other markers (4 and 1), and a marker in the outer side margin.
- (4) Now move the counters within the board diagonally up and right until they are adjacent to the margin. See Fig. 5.
- (5) Ignoring for the moment any counters below the side marker, subtract the counters on the left from those in the margin. In the example this is simple; after removing the "common" counters, the first move of X eliminates the counter at 32 and the subtraction is complete.
- (6) Place a counter in the square immediately next to the highest side counter 16 and repeat as at (2), (3), and (4) above. This time, however, you will be unable to subtract as above, since the values of the counters on the left are higher than those in the margin. The routine in cases such as this is to move each counter and the side marker down one square and try again. In this case it is now possible, but with larger numbers on a larger board it may be necessary to repeat the process more than once.
- (7) After subtraction you find you have a marker at 16 and at 1, the sum of which is 17 (the quotient), and counters at 8 and 2, the sum of which is the remainder (10).

A little consideration will show how to use the top margin for larger numbers, but you will have to keep a clear picture of what you are doing when it comes to "turning the corner" and the best solution is to use a larger board, which will also give you a bigger divisor.




The International Sound of the 70's


IS THE HEATHKIT 'COMPACTS' AND LOUDSPEAKERS



'COMPACT' AD27

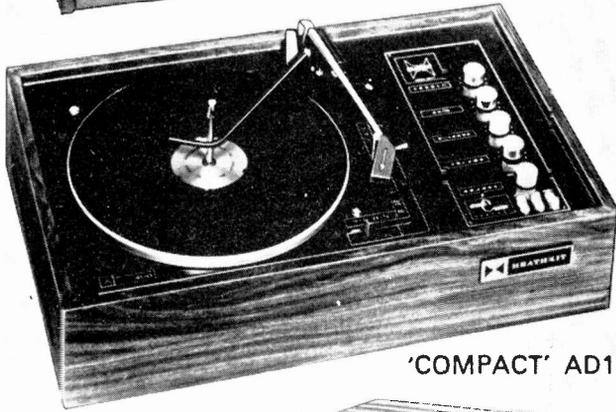

'COMPACT' AD17

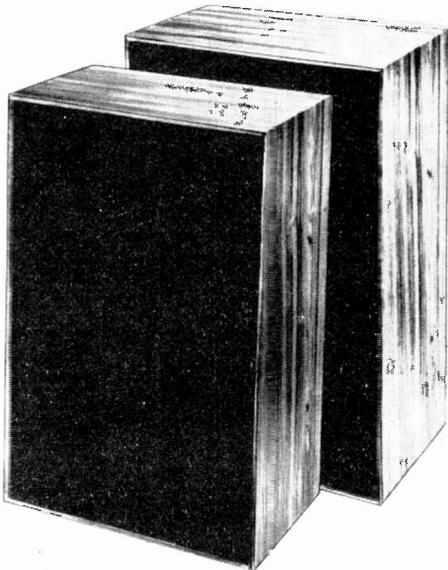

AMBASSADOR SPEAKERS

The fabulous Stereo 'Compacts'. Models AD-17 and AD-27 are setting the pace in hi-fi for the 1970's. They offer outstanding value and performance. The AD-17 comprises a BSR MA-65 Turntable/Shure M44-MB magnetic cartridge and a ten watt (RMS) per channel stereo amplifier all mounted on a teak or walnut plinth. Kit price £54. Carr. 13/-.

The AD-27 is similar but uses the MA-70 turntable and includes an FM stereo tuner. In this case the 'plinth' is better described as a small cabinet. It has the additional feature of a 'roller shutter' lid and is available in teak or walnut. Kit price £82. Carr. 13/-.

Heathkit offer many excellent loudspeaker systems. The new 'Ambassador' hi-fi loudspeaker is winning many friends. It's cabinet is supplied ready assembled and finished in selected teak or walnut veneers to harmonise with other current Heathkit hi-fi equipment. It uses three loudspeaker units, a 12in bass, 5in mid range and a 1in dome pressure tweeter. Excellent value at kit price £29.16.0. Carr. 15/-.

The complete Heathkit hi-fi range of stereo amplifiers, tuner/amplifiers, FM tuners, stereo 'compacts', loudspeaker systems and ancillary hi-fi equipment are all described and illustrated, many in full colour, in a wonderful free catalogue.

Send for the
FREE Catalogue
and see for
yourself ...
Today!

To: DAYSTROM LTD., GLOUCESTER GL2 6EE
Please rush me details of the
latest Heathkit Hi-Fi models

NAME _____
ADDRESS _____

25/2A



DAYSTROM LTD.


HEATHKIT DIVISION
GLOUCESTER GL2 6EE

Telephone: GLOUCESTER 2945

Telex 43216

MONO TRANSISTOR AMPLIFIER

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener. 6 transistor circuit with integrated pre-amplifier assembled on special printed sub-panel. AD161-AD162 operating in symmetrical complementary

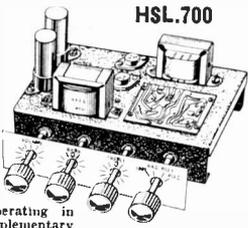

HSL.700

pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for a.c. mains 200-240v. Controls: bass, treble, volume/on/off. Function selector for PU1, PU2, tape, radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 x 4 1/2 in. High.

Sensitivity—PU1—50mV, 56K input impedance. PU2—110mV, 1 meg input impedance. Tape—110mV, 1 meg input impedance. Radio—110mV, 1 meg input impedance. Output power measured at 1Kc—6.2 watts RMS into 3 ohms, 5.8 watts RMS into 15 ohm. Overall frequency response 30c/s-18Kc/s; Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 10Kc/s.

The HSL.700 has been designed for true high fidelity reproduction from radio tuner, gramophone deck and tape recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, lens spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

OUR SPECIAL PRICE **£7.19.6p.** P. & P. 7/6.

LOUDSPEAKER BARGAINS

5in 3 ohm 18/-, P. & P. 3/-; 4in 3 ohm 21/-, P. & P. 4/-; 10 x 6in 3 ohm 27/6, P. & P. 6/-; E.M.I. 8 x 5in 3 ohm with high flux magnet 21/-, P. & P. 4/-; E.M.I. 13 1/2 x 8in 3 ohm with high flux ceramic magnet 42/-, (15 ohm 45/-), P. & P. 6/-; E.M.I. 13 x 8in, 3 or 15 ohm with two built-in tweeters and crossover network 4 gns. P. & P. 6/-.

BRAND NEW. 12in 16w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly 45.10.0, P. & P. 7/6. Guitar model: 25w 46.0.0, 35w 48.0.0. E.M.I. 3 1/2in HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohm 15/- each; 16 ohm 18/6 each. P. & P. 2/6.

12in "RA" TWIN CONE LOUDSPEAKERS. 10 watts peak handling. 3 or 15 ohm. 37/6, P. & P. 6/-.

35 OHM SPEAKERS

3 1/2in 14w. P. & P. 2/6; 7 x 4in 21/-, P. & P. 4/-; 10 OHM MOVING COIL SPEAKERS. High Flux Magnet 2 1/2" dia. 12/- each. P. & P. 1/6.

QUALITY PORTABLE TAPE RECORDER CASE.

Brand new. Beautifully made. Only 49/6. P. & P. 8/6.

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 18/6, P. & P. 1/6.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-, P. & P. 1/6.

HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity. 38/6, P. & P. 2/6.

PYE MICROSWITCHES S/P. C/O. Lever roller action. Rating 250v. AC at 5 amps. Size approx. 1" x 1" x 1 1/4". 4/- each. P. & P. 1/- (6 or more post free).

HONEYWELL MICROSWITCHES S/P. C/O. Push-button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2" x 1 1/2" x 5/8". 5/- each. P. & P. 1/- (6 or more post free).

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7' to approx. 56". Maximum diameter 1 1/2". 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6' to approx. 22 1/2". Maximum diameter 1 1/2". 5/- each. P. & P. 1/6.

TRANSFORMER BARGAINS!

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10, 20-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. Price 32/6. P. & P. 6/-.

MAINS TRANSFORMER. For resistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 11/-, P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 14/6, P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 12/6. P. & P. 2/6.

BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240v. AC Sec. 240v. at 50mA and 6-3v. at 1.5 amp. Stack size 2 1/2 x 2 1/2 in. 10/6. P. & P. 3/6. (Special quotations for quantities.)

BRAND NEW! PARMEKO MAINS TRANSFORMERS. Primary 110v-250v. Secondary 330-0-330v. 100mA and 6-3v. at 2 amps, 6-3v. at 2 amps and 6-3v. at 1 amp. Conservatively rated. Fully impregnated Electrostatic screen. Suitable for vertical or drop through mounting. Overall size 4 1/2 x 3 1/2 in. Weight 8 lb. Limited number only at 37/6, P. & P. 8/-.

Open all day Saturday
Early closing Wed. 1 p.m.

A few minutes from South Wimbledon
Tube Station

SPECIAL OFFER!!

Your opportunity to acquire a first class HI-FI LOUD-SPEAKER SYSTEM at an extremely moderate price! Beautifully made teak finish enclosure with most attractive Tegan front. Size 16 1/2" high x 10 1/2" wide x 8" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two E.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance. **OUR PRICE WHILE LIMITED 8 Gns.** Carriage STOCKS LAST 10/-

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response $\pm 3dB$. 20-20,000c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 0.6 amp. **PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0.** All Post Free. Also available STEREO 10 + 10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12. POWER PACK KIT £3.10.0.** Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).

Official stocks of all PEAK SOUND HI-FI EQUIPMENT

including the P.W. DOUBLE 12 STEREO AMPLIFIER as featured in Practical Wireless April, May and June issues. Component pack as specified. Total cost £23.5.6 plus P. & P. 11/-. (Excluding metalwork, knobs, plugs and sockets and fuses.)



SPECIAL PURCHASE!


E.M.I. 4-SPEED PLAYER

Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 V shaded motor (90 V tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 63/-, P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. PRICE 75/-, P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6, P. & P. 7/6.

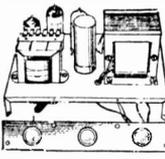DE LUXE QUALITY PORTABLE R/P CABINET MK II 5in. motor board size 14 1/2 x 12 1/2 in., clearance 2in. below. 4 unit. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP20). Size 18 x 16 x 8in. PRICE 79/6, P. & P. 9/6.



3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plate heavy gauge metal chassis size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 44.15.0, P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6, P. & P. 6/-.


BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NPN) 3/-.

Set of Mullard 6 transistors OC44, 2—OC45, AC128D, matched pair AC128 25/-; ORP12 Cadmium Sulphide Cell 10/6. All post free.

YNAIR and REXINE SPEAKERS AND CABINET FABRICS app. 6 1/2 in. wide. Usually 35/- yd., our price 15/- yd. length. P. & P. 3/6 (min. 1 yd.). S.A.E. for samples.

POWERFUL COMPACT MOTOR for 6-9v. Battery operation approx. 25mA. Made originally for "Staar" and "Greencoat" record player decks. Built in constant speed device. Ideal for models, etc. Overall size approx. 1 1/2" x 1 1/2". 7/6 each. P. & P. 1/6. (3 or more Post Free).

DE LUXE STEREO AMPLIFIER

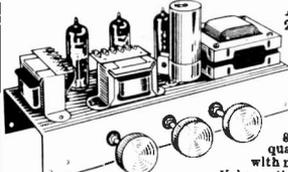

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2x ECL86 Triode Pentodes.

1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. Price 8 gns. P. & P. 8/-.


4-SPEED RECORD PLAYER BARGAINS

Mains models, All brand new in maker's packing. B.S.R. UA25 with latest mono compatible cart... £6.19.6 All plus Carriage and Packing 6/6. LATEST GARRARD MODELS. All types available 1925, 2025, SP25, 3000, AT60 etc. Send S.A.E. for Latest Prices! PLINTH UNITS cut out for Garrard Models 1025, 2025, 2000, 3000, AT60, SP25. With transparent plastic cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

SONOTONE 9TACH compatible Stereo Cartridge with diamond stylus 50/-, P. & P. 2/-.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. 30/-, P. & P. 2/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1
● Peak out in excess of 11 watts.
● All standard British components.
● Built on printed circuit panel size 6 x 3in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET114 or S1 Mullard AC 128D) and matched pair of AC128 at 9 volt operation.
● Everything supplied, wire, battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-, P. & P. 3/-.** Also ready built and tested, 52/6, P. & P. 3/-.

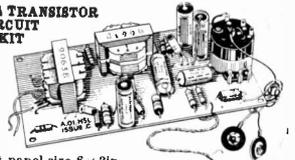


HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. FEW ONLY.

OUR ROCK BOTTOM BARGAIN PRICE **49/6** P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY £7.9.6, P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0, P. & P. 8/6.

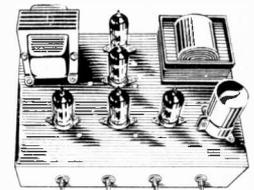


HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

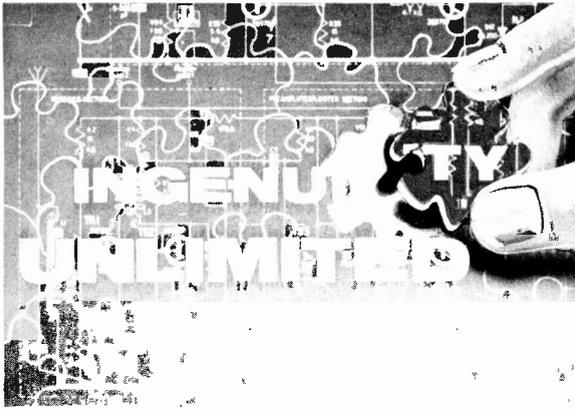PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

ADJUSTABLE LIGHT SOURCE

WHILST experimenting with various types of light operated switches, I found a need for an adjustable light source which would give a narrow beam of light without the use of complicated lens systems. The one here described was found to work extremely well and has been used to work quite a few types of circuits, both very sensitive and the more robust types.

The basic component consists of two cigar tubes, one of slightly larger diameter than the other. The larger of the two has the rounded end sawn off and the screw cap end left intact. The smaller tube has both ends sawn off to leave a tube of thin aluminium about 3in long, whilst the larger tube should be about 4in length when the cap is screwed on.

The two tubes are now made to slide together rather stiffly; this can be achieved by reaming out the end of the smaller tube until a firm fit is made. Any stray light that may escape around the joint can be eliminated by a snug fitting elastic band of fairly wide dimensions, fitted after completion. The assembly is shown in Fig. 1.

The choice of lens is not critical and the one that I used was taken from a vintage box camera. After removal from the body of the camera, the lens was fastened onto the smaller of the cigar tubes with contact adhesive, great care being taken to ensure a light proof fit. When finally set, the joint was covered with a single layer of black plastic tape to neaten the job.

The layout of the complete tube system is now built and tested for operation before the bulb assembly is made. This consists very simply of a hole in the screw cap of the larger tube with the bulb fastened in place with an ordinary m.e.s. lampholder.

Only one point is important in the choice of bulb used; the filament must be of the "spot" type and as small as possible. I tried quite a few types and makes before discovering that the ordinary 3.5V torch bulb was the most efficient. Before assembling the unit, drill or punch a few small holes for heat dissipation as near to the screw cap as possible (Fig. 1). The heat from even a small bulb in so confined a space is quite remarkable.

Strip aluminium was used to make the bracket which was jointed in the centre to allow for beam adjustment.

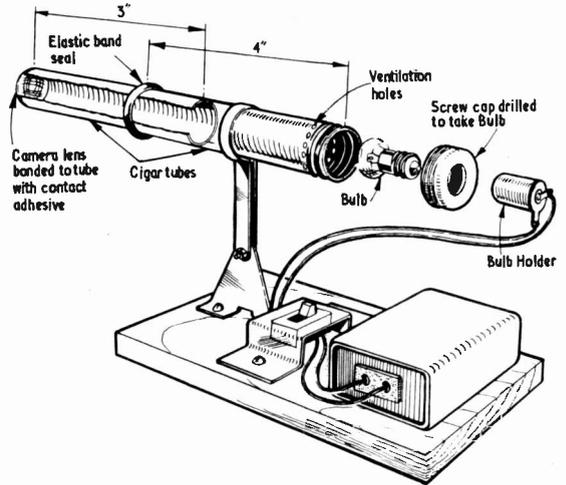


Fig. 1. Light source for light operated switch

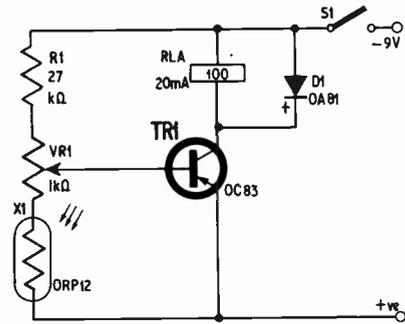


Fig. 2. Relay circuit

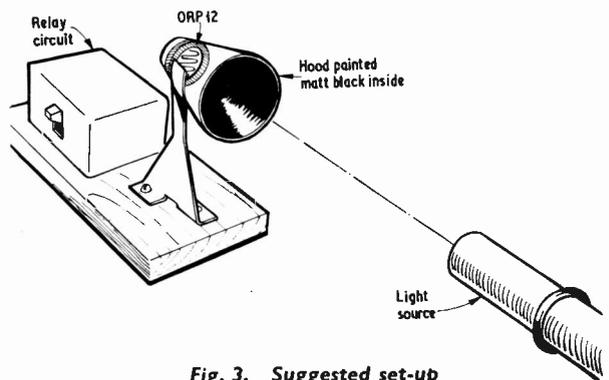


Fig. 3. Suggested set-up

As the completed unit is very light I did not find it necessary to wrap the aluminium strip right around the tubes, a very firm fit was obtained using only hand pressure. Care may be needed here to avoid distorting the thin aluminium.

The whole unit can be mounted on a board to suit individual requirements and a switch added to conserve battery drain.

The sliding tube assembly allows for a form of focus to be achieved but the light pattern will be found to be a

small circle of light easily adjusted to the dimensions of the ORP12 and providing ample illumination for distances up to 6ft. At distances greater than this some distortion of the pattern will be met but not too great and, providing the circuit used is sensitive enough, it will still be effective.

Fig. 2 shows a simple circuit controlling a relay RLA which can be of 100 ohms resistance or more and suitable for operation with a 9V battery and OC83 transistor. A typical set-up is shown in Fig. 3 which can be used to register objects breaking the light beam.

R. W. Lawrence,
6 Verdun Road,
Morton,
Manchester,
Lancs

IMPROVED SCHMITT TRIGGER

THE popular Schmitt trigger frequently occurs in constructional projects published in PRACTICAL ELECTRONICS. It would often be advantageous to reduce the hysteresis, or backlash, especially in those circuits which use a Schmitt to produce a square wave from a sine wave.

The circuit in Fig. 1 includes VR1, careful adjustment of which enables the hysteresis to be reduced to a very low level. This is because any unbalance in transistor characteristics is balanced out by the different amounts of VR1 which are included in each emitter lead.

It is usually convenient to set the hysteresis to 50mV or so. An input of 1kHz at a level of 120mV peak to peak (about 40mV r.m.s.) produces a square wave output with very fast rise and fall times—less than 5µs.

Component values are given here to suit the transistors quoted, but the modification shown will improve any existing Schmitt trigger by reducing the hysteresis as described.

VR1 can be set by adjusting it for a square wave output with successively smaller input signals until the required sensitivity is reached; attempts to reduce hysteresis to too low a value will result in the circuit oscillating.

J. N. Watt,
Camberley,
Surrey.


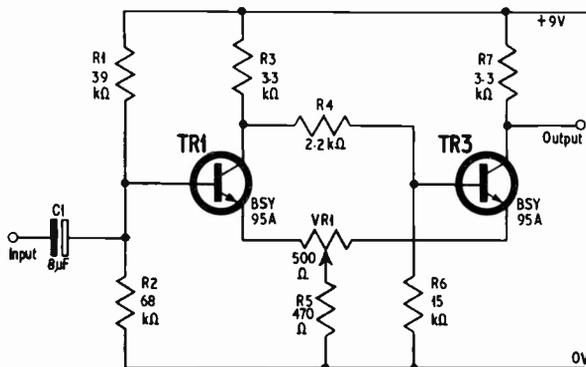


Fig. 1. Circuit diagram of the improved Schmitt trigger

LOGIC PROBE

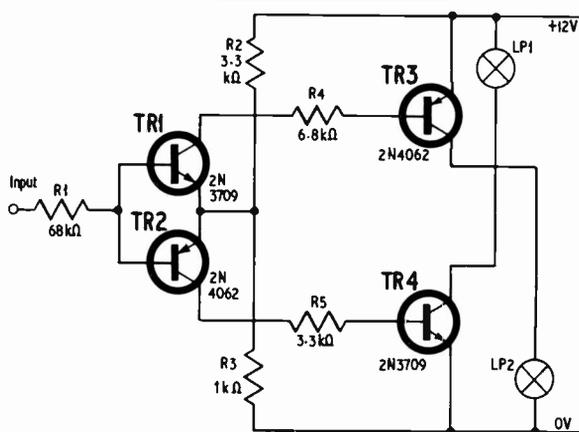

I AM enclosing a circuit diagram for a "0" and "1" logic test-probe which I have recently made. It is designed around a simple gating circuit. The probe operates from a +12V supply and has a threshold voltage of +3V at the input.

I designed it for use with 6V logic. Both lamps are normally off (indication of a disconnection). Lamp A glows for inputs of 2V; lamp B glows for inputs of 4V. The input impedance is adequately high. Threshold voltage may be selected by varying the values of R2 and R3.

The lamps I used were 12V 20mA types ex-G.P.O. signal lamps, but the circuit could easily be modified for higher power lamps by using suitable higher power transistors.

K. L. Spence,
London, N.W.7.

BOOK REVIEWS continued from page 149

enclosures, explaining the acoustic properties and the effects of resonances.

Anyone asked to suggest a list of recorded music, suitable for starting a collection, must have a difficult task; one man's meat may be another man's poison. W. A. Chislett has attempted to give micro-miniature reviews on more than 120 items, whilst admitting that "any great work is capable of more than one valid interpretation, which does not necessarily make one better than another".

Also included are chapters on Care and Storage of Records by A. C. Williams; Tape Recorders and Recording by H. W. Helyer; Stereo Radio—How it Works by Roy Prince; Radio Tuners by Gordon J. King.


This last article really illustrates how far advanced radio receiver techniques have become. It includes the description and use of f.e.t.'s and integrated circuits in f.m. tuners. Of the most recent techniques of improving selectivity, the use of d.c. controlled variable capacitance diodes for tuning and a.c. controlled feedback to them for a.f.c., really make one wish that these features had been invented some 14 years ago. An interesting experience described as the "Northampton Effect" just goes to show that the average listener places rather less faith in his tuner than perhaps is due. Here the BBC is not entirely blameless in providing the basis of 10kHz "burbling" on stereo.

Armchair shopping with this handbook can save headaches later, but do not expect it to give you all the answers to your problems.

M.A.C.

DE LUXE PLAYERS

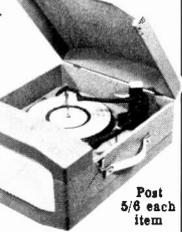PORTABLE CABINET Amplifier. To fit standard 75/- player or autochanger. RCS AMPLIFIER 3 WATT. Ready made and tested. This is a 2-stage unit using triode pentode condenser coupled valve, giving 8 watts output into a 3 ohm loudspeaker. Tone and volume controls mounted on panel. Supplied with knobs, loudspeaker and valves UCL82, UY85. Frequency response 50-12,000 cps. Sensitivity 200mV **59/6**



Post 5/6 each item

SINGLE PLAYERS MONO EMI Junior Mains £2.19.6 Garrard AP25 £18.10.0 Garrard SP75 MKII £12.19.6

AUTOCHANGERS MONO Balfour Princess 45.5.6 BSR Supralim UA25 £8.19.6 BSR Mini Changer 28.19.6 AUTOCHANGERS STEREO BSR Supralim 27.19.6 Garrard 1025 27.19.6 Garrard 3000 212.19.6

GARRARD TEAKWOOD BASE WB.1. Ready cut out for mounting 1025, 3000, SP25, AT80, etc. GARRARD PLASTIC COVER SP.1 for WB.1 BASE. Durable tinted attractive appearance. **65/-**

E.M.I. PICK-UP ARM. Complete with mono cartridge 29/6; XTAL GP67 17/6; Stereo Ceramic 35/-; ACOS LP 10/6

CRYSTAL MIKE INSERTS 1 1/2" dia. 6/6; ACOS 1 1/2" dia. 12/6. BMS, 1 1/2" dia. 9/6 QUALITY RIBBON MIKE WITH GOOSENECK £11.11.0 CRYSTAL HAND MIKE, HIGH OUTPUT 2/6

PORTABLE TRANSISTOR AMPLIFIER PLUS DYNAMIC MICROPHONE A self-contained fully portable mini p.c. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive rexine covered cabinet, size 12 x 4 1/2 in., with powerful 7 1/2 in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make. Only **90/-** Post Free



Only 90/- Post Free

WEYRAD P50 - TRANSISTOR COILS RA2W 6 in. Ferrite Aerial with car aerial coil 12/6 One. P50/LAC 5/4 I.F. P50/CC 270 kcs. 5/7 3rd I.F. P50/3CC 200/3C Telescopic Chrome Aerials 6in. extends to 23in. 5/- Ferrite Rods Only 8 in. 4/- 6 in. 5/-

VOLUME CONTROLS 80ohm Coax 8d. yd. Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. 1/5 3/-. D.P. 5/- STEREO L 8 10.6. D.P. 14/6 EDGE 5K. S.P. Transistor. 5/- Ideal 825 lines

WIRE-WOUND 3-WATT POTS. Type. Knurled Knob. Carbon 30 K to 2 meg. **4/6** WIRE-WOUND 3-WATT T. Type. STANDARD SIZE POTS. LONG SPINDLE. 10 OHMS to 100 K. **7/6**

VEROBOARD 0.15 MATRIX 2 1/2 x 5in. 3/8. 2 1/2 3 1/2. 3 1/2 3 1/2. 3 1/2 3 1/2. 5in. 5/2. EDGE CONNECTORS 16 way 5/-; 24 way 7/6. PINS 30 per packet 3/4. FACE CUTTERS 7/6. S.R.B.P. Board 0.15 MATRIX 2 1/2 in. wide 6d. per lin., 3 1/2 in. wide 9d. per lin.; 5in. wide 1 1/2/- per lin. (up to 17in.). S.R.B.P. drilled 1/4 in. Board 10 8in. 3/-

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 7 1/2 in. 6/-; 9 in. 7in. 8/6; 11 3in. 7/6; 11 7in. 9/6; 13 9in. 10/6; 14 11in. 14/6; 15 14in. 15/-; ALUMINIUM PANELS 18 s.w.g. 12 12in. 6/6; 14 9in. 5/6; 12 8in. 4/6; 10 7in. 3/6; 8 6in. 2/6; 6 4in. 1/6

Q MAX CHASSIS CUTTER Complete: a die, a punch, an Allen screw and key tin. 16/- tin. 17/6 1 1/2 in. 19/6 1 1/2 in. 24/- 2 1/2 in. 44/3 tin. 16/- 1 1/2 in. 19/6 1 1/2 in. 20/6 1 1/2 in. 29/6 2 1/2 in. 57/3 tin. 16/9 1 1/2 in. 19/6 1 1/2 in. 21/6 2in. 39/- tin. sq. 36/6 1 1/2 inch DIAMETER WAVE-CHANGING SWITCHES. 2 p. 12-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 38/- TOGGLE SWITCHES, sp. 2/8; s. 2/8; dp. 3/8; dp. dt. 4/6

ALL PURPOSE HEADPHONES H.R. HEADPHONES 2000 ohms Super Sensitive 35/- LOW RESISTANCE HEADPHONES 3-5 ohms 39/6 DE LUXE PADDED STEREO PHONES 8 ohms 79/6

"THE INSTANT" BULK TAP ERASER AND RECORDING HEAD DEMAGNETISER 200/250 v. A.C. Leaflet S.A.E. Post 2/6 **42/6**



Post 2/6 42/6

BARGAIN STEREO/MONO SYSTEM Attractive Slim PLAYER CABINET with B.S.E. Stereo Autochanger, 3 VALVE STEREO AMPLIFIER, two 8 in. LOUDSPEAKERS. (Only 4 pairs of wires £19.19.6 to join). Carr. 10/6. S.A.E. for details.

NEW TUBULAR ELECTROLYTICS CAN TYPES 2/350V .. 2/3 100/25V .. 2/3 8/600V .. 9/6 4/350V .. 2/3 250/25V .. 2/3 18/800V .. 12/6 8/450V .. 2/3 500/25V .. 4/- 16+16/500V .. 7/6 16/450V .. 3/- 8+8+450V .. 3/6 50+50/350V .. 7/- 32/450V .. 3/6 8+16/450V .. 3/6 80+100/350V .. 11/6 25/25V .. 1/9 16+16/450V .. 4/3 32+32+32/350V .. 8/6 50/60V .. 2/- 32+32/350V .. 4/6 100+50+50/350V .. 9/6

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-; CERAMIC 500V 1pF to 0.01mF 9d. PAPER 350V-0.1 9d, 0.2 8/-; 1mF 3/-; 2mF 150V 3/-; 500V-0.001, 0.002, 0.0047, 0.01, 0.02, 1/8, 0.047, 0.1, 2/8. SILVER MICA Colloids 1 1/2, 5-500V/1 1/2, 560-8,200V/2/-; 2,700-5,800V/3/6, 6,800V-0.01, mid 6/-; each TWIN GANG. "0-0" 208pF+176pF, 10/6; 365pF, miniature 10/6; 500pF standard with trimmers, 12/6; 500pF midget less trimmers, 7/6; 500pF slow motion, standard 9/-; small 3-gang 500pF 19/6. Single "0" 365pF 7/6. TWIN 10/6. SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF, 160pF, 200pF, 10/6 each.

TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF 150pF, 1/3; 250pF, 1/8; 800pF, 750pF, 1/8; 1000pF, 2/6. RECTIFIERS CONTACT COOLED 1/2 wave 60mA 7/6; 65mA 9/6. SILICON RY213 8/-; BY100 10/- Full wave Bridge 75mA 10/-; 150mA 19/6; 7V rect. 10/- NEON PANEL INDICATORS 250V, AC/DC Red, Amber 4/6. RESISTORS. Preferred values, 10 ohms to 10 meg. 1 w., 1/2 w., 20%, 30%, 1 1/2 w. 8d., 2 w. 1/-; 1 w. 10%, 6d. HIGH STABILITY. 1 w. 1%, 10 ohms to 10 meg., 2/-; Ditto 5%. Preferred values 10 ohms to 22 meg., 9d. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 2/- each; 3 watt, 0.5 ohm to 8.2 ohms, 2/-

BRAND NEW TRANSISTORS 6/- EACH. OCT1, OCT2, OCT3, OCT4, 4/6; AF1, AF2, 4/6; MAT 100 7/6; MAT 101 8/6; MAT 120 7/6; MAT 121 8/6. REPANO TRANSISTOR TRANSFORMERS. T445 Full Drive, 6.1 CT, 6.1, 11.5, 11.5, 3.5, 1.6, 1.6, T449. Interstage, 4.5-1, 6/-; T452 Output 3 ohms, 20.1, 6/-; T428/4 PAIR 10 watt Amp. Transformers and circuit 35/-

TRANSISTOR MAINS POWER PACKS. FULL WAVE 9 volt 500mA. Size 4 1/2 x 2 1/2 in. Metal case. **49/6** Circuit finish. Output terminals. On/off switch. 60Hz Half Wave 9 volt 500mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32.6 9 volt 500mA. TRANSFORMER ONLY. 2 1/2 x 1 1/2 in. 10/6

MAINS TRANSFORMERS Post 5/- each 250-0-250 50 mA, 6.3 v. 2 amps. center tapped 19/6 250-0-250 80 mA, 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/- 350-0-350 80 mA, 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/- 300-0-300 v. 120 mA, 6.3 v. 4 a. C.T.; 6.3 v. 2 a. 45/- MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 2 1/2 in. 12/6 HEATER 220 v. 4r. 2 1/2 in. 2 1/2 in. 12/6 HEATER TRANS. 6.3 v. 1 a., 8/6; 6.3 v. 4 a. 12/6 DiHo tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 1 1/2 amp. 12/6 GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 3 a. 35/- 1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 35/- AUTO TRANSFORMERS 0.115-230 v. Input/Output, 60w. 18/6; 150w. 35/-; 500w. 92/6; 1000w. 185/- CHARGER TRANSFORMERS. Input 200/250v for 6 or 12v., 1 1/2 amp., 22/-; 4 amp., 35/- FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 8/6; 2 amp. 11/3; 4 amp. 17/6.


COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE 2/- OUTLET BOXES. SURFACE OR FLUSH 4/6. BALANCED TWIN FEEDERS 1/2-10 ohms or 300 ohms. JACK SOCKET Std. open-circuit 2/6, closed circuit 4/6; Chrome Lead Socket 7/6. Phone Plugs 1/-; Phone Socket 1/-; JACK PLUGS Std. Chrome 3/-; 3.5mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 6-pin 2/-; DIN SOCKETS Lead 3-pin 3/6; 6-pin 4/6. DIN 3-pin 1/6; 6-pin 2/6. VALVE HOLDERS, 9d.; CERAMIC 1/-; CANS 1/-

T.S.L. LOUDSPEAKER CROSSOVER HLP2. 2-way crossover for 8 or 15 ohm speakers and tweeters, 3 phono input/output sockets. Made to suit OUR PRICE 22/6 at 42/- Post 2/6

Tape Spools 2/6. Tape Splicer 5/-. Leader Tape 4/6. Reuter Tape Heads for Collaro models 2 track 21/- pair. PHOTO-ELECTRIC RELAY SYSTEM. 240v. A.C. Exciter and relay unit with infra red filter. **£12** POST FREE For counting, door signals, alarms, etc.

MINI-MODULE LOUDSPEAKER KIT 10 WATT 65/- CARRIAGES- Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 in. Separate Bass, Middle and Treble Loudspeakers and crossover controller. The heavy duty 5 in. Bass Woofer unit is of high resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm. TEAK VENERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian 94/6 Post 5/- fluted front design for Mini-Module.

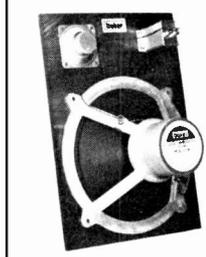ALL MODELS "BAKER SPEAKERS" IN STOCK BAKER MAJOR £8



30-14,500 c.p.s., Hi-Fi double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Base resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module kit, £8, 17,000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6.

BAKER "GROUP SOUND" SPEAKERS - POST FREE "Group 25" "Group 35" "Group 50" 12in 6gns. 15in 8gns. 15in 25 watt 35 watt 50 watt 18gns.

TEAK HI-FI SPEAKER CABINET. Fluted wood finish. For 10 or 12in round Loudspeaker £8.10.0. For 13 8in or 8in round Loudspeaker £4.14.6. For 10 8in or 8in round Loudspeaker £3.18.6. LOUDSPEAKER CABINET WADDING 18in wide, 2/6ft

Goodmans Tweeter 3 1/2 in 35m. EMI 2 1/2 in 8 ohm 17/6. Horn Tweeters 2-18kcs, 10W 15 ohm 29/6. Crossover 18/6. LOUDSPEAKERS P.M. 3 OHMS. 2 1/2 in, 3in, 4in, 5in, 5 x 3in, 7 x 4in, 17/6 each; 6 1/2 in 22/6; 8 x 5in, 21/-; 8 x 2 1/2 in 10/6. 10 x 6in, 30/-; 10in, or 12in. Double cone 3 or 15 ohm 39/6. E.M.I. Double Cone 13 1/2 x 8in, 3 or 15 ohm 10 watt 45/6. DITTO twin tweeters and X/over 3 or 8 or 15 ohm 10w. 79/6. SPECIAL OFFER! 8ohm, 2 1/2 in; 6 x 4 in; 8ohm, 2 1/2 in, 2 1/2 in. EACH 25 ohm, 6 in; 35 ohm, 3in 15 ohm, 7 x 4 in, 8 in. 8in LOUDSPEAKER UNITS each 27/6; 15 ohm 30/- ELAC 8 in. De Luxe Ceramic 3 ohm 45/-; 15 ohm 50/-; 5in LOUDSPEAKER. TWIN CONE 3 ohm 35/-; 15 in. WOOFER. 8 watts max. 20-10,000 cps. 8 or 15 ohm. 39/6. OUTPUT TRANS. EL84 etc. 4/6; MIKE TRANS. 50L 3/9. SPEAKER COVERING MATERIALS. Samples Large S.A.E.

THE FAMOUS "MULLARD 510" £16.19.6 Post 10/6



Main power, amplifier and 2 valve pre-amplifier. Silver grey facia panel. Volume, treble, bass controls. Function switch: Radio, Tape 1, Tape 2, Mic, Gram L.P. Gram 78. Tape output socket. Valves: 2 - EL84, 3 x EF86. 1 - EC68S, 1 - E281. Ultra linear Parmako output transformer. 20 db negative feedback. 10 watt rms mono, 3 and 15 ohm output. Brand new. Guaranteed.

ALL EAGLE PRODUCTS SUPPLIED AT LOWEST PRICES. 45-PAGE EAGLE CATALOGUE 5/- Post free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **79/6** BARGAIN DE LUXE TAPE SPLICER CUTS, trims, joins for editing and repairs. With 3 blades. **17/6** BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **59/6**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. Ready built. Printed Circuit. Calibrated slide dial tuning. Size 6 x 2 1/2 in. 9 volt. **£6.19.6** BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **69/6**

RADIO BOOKS (Postage 9d.) Practical Transistor Receivers 5/- Practical Radio Inside Out 4/8 Supersensitive Transistor Pocket Radio 3/6 Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 6 ea. 6/- C.T.V. Fault Finding 405/625 Lines 8/6 Shortwave Transistor Receivers 5/- Transistor Communication Sets 6/- Modern Transistor Circuits for Beginners 7/6 Sub-Miniature Transistor Receivers 5/- Wireless World Radio Valve Data 9/6 International Radio Station Guide 2/6 Receive foreign T.V. programmes by simple modifications. Valves, Transistors and Diodes equivalents Manual. 10/6

3 inch MOVING COIL METERS BRITISH MADE Various calibrations/movements. 500 Microamp. 1 Milliamm; 50-0-50 Microamp. etc. S.A.E. for list. **37/6**

BRAND NEW QUALITY EXTENSION LOUDSPEAKER Handsome plastic cabinet, 200c, lead and adaptors. For any radio, intercom, tape recorder, etc. 3 to 15 ohm. Size: 7 1/2" x 5 1/2" x 3". Post 2/6 **30/-**



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) List 1/-. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133 68 pass door, S.R. Stn. Selhurst. Tel. 01-684-1665

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



SUPPRESSOR CONDENSER TCC

1 mfd. 250v. A.C. working model with fixing lug. 1/9 each, 18/- per doz.



TUBULAR HEAT & LIGHT LAMP

600W. 29/6 plus 4/6 post and insurance.

BLANKET SIMMERSTAT


Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each we offer these while our stocks last at only 12/6 each.

DIAMOND H OVEN THERMOSTAT

Type 20 with capillary tube and sensor, 20 amp A.C. type as fitted to many cookers adjustable by control knob (not supplied) 12/6 each.

BLACK LIGHT

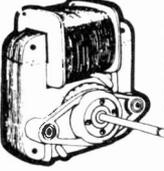G.E.C. tube for experiments and special lighting effects—40 watt 2ft tubes only. 18/6 each; holders and control gear 19/6, postage on single item 4/6 inc. Insurance, or both items ordered together postage 8/6 inc. insurance.




MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. 5/1p at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

INSTRUMENT MOTORS WITH GEARBOX

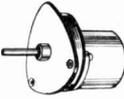Made by famous Smiths Company. Very powerful, although only quite small. Overall dimensions approx. 1 1/2 in. deep by 2 in. dia. Following models available please specify required speed. Revs per day, 2-8-12. Revs per hour, 1, 2, 4, 6, 12, 20, 30. Revs per minute, 1, 2, 3, 4, 6, 8, 15, 30, 60. 17/6 each.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions, 19/6 plus 2/6 post and insurance. Made up model 37/6 plus 2/6 p. & p.



SOLDER GUN

A must for every busy man. Gives almost instant heat; also illuminates job. 100 watt 220/240V, 39/6 (saves you over 30/- post and ins. 4/6. BIG JOB 250 watt model, 99/6 (saves you over £3.10), post and ins. 6/6.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6 plus 3/6 postage.

ERGOTROL UNITS

These units made by the Mullard Group are for operating and controlling d.c. Motors and equipment from A.C. mains.

Thyristors are used and these supply a variable d.c. resulting in motor speed control and operating efficiency far superior to most other methods.

The units are contained in wall mounting cabinets with front control panel on which are fuses—push buttons for on/off and the variable thyristor firing control.


4 models are available—all are brand new in makers cases:—

Model 2410 for up to	5 amps	£17.10.0
2411	10	£27.10.0
2413	45	£47.10.0
2415	80	£95. 0.0

Note: 2415 is a floor mounting unit.

RADIO STETHOSCOPE

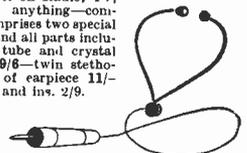Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stetho-ear instead of earpiece 11/- extra—post and ins. 2/9.



WAFFER SWITCHES TO YOUR REQUIREMENTS

Standard Size 1 1/2 waffer—silver plated 5 amp contact standard 1/4 in. spindle 2in. long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	7 way	8 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	10/6	10/6	10/6	14/6	14/6	22/6	22/6
6 poles	6/6	10/6	10/6	10/6	14/6	14/6	14/6	26/6	26/6
7 poles	6/6	10/6	10/6	14/6	18/6	18/6	18/6	30/6	30/6
8 poles	10/6	10/6	10/6	14/6	18/6	18/6	18/6	34/6	34/6
9 poles	10/6	10/6	14/6	14/6	22/6	22/6	22/6	38/6	38/6
10 poles	10/6	10/6	14/6	18/6	22/6	22/6	22/6	42/6	42/6
11 poles	10/6	14/6	14/6	18/6	26/6	26/6	26/6	46/6	46/6
12 poles	10/6	14/6	14/6	18/6	26/6	26/6	26/6	50/6	50/6

TANGENTIAL HEATER UNIT



A heater is coming but act today and you won't dismay. This heater unit is the very latest type, most efficient and quiet running. Is as fitted on Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2 kw element and 1 kw element allowing switching 1, 2 and 3 kw and with thermal safety cut-out. Can be fitted to any metal lined case or cabinet. Only needs on/off switch. 79/6, postage & insurance 6/6. Don't miss this.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semiconductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CRO 2TH
Also 102/3 Tamworth Road, Croydon



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-style drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

"I have looked at each book and must confess they are very good, everything is made so simple, which makes reading a pleasure." R.H.H.G., Blandford.

"I find the information contained very aptly illustrated and composed." D.G., Twickenham.

"I would like you to know once again that I have read parts of each volume and think they are excellent reading material. Easy to understand, easy to read and the subjects are not flooded with reams of unnecessary calculations which most electrical books delight in." P.B., New Malden.

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP
Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS

Prices include Postage and Packing.

Signature (If under 21 signature required of parent or guardian)

NAME

BLOCK LETTERS

FULL POSTAL ADDRESS

.....

SEMICONDUCTORS & COMPONENTS

BRAND NEW

(Saturday callers only 5% Discount)

GUARANTEED

TRANSISTORS

2G301	4/-	2N3053	6/6	25005	15/-	BC115	6/6	BFY76	6/-	NKT240	6/-
2G302	4/-	2N3054	11/6	25020	37/6	BC116	12/6	BFY77	11/6	NKT241	6/6
2G303	4/-	2N3055	15/-	25102	6/6	BC121	6/6	BFY90	12/6	NKT10419	6/6
2G306	8/6	2N3133	6/-	25103	6/6	BC122	4/-	BFV58	6/6	NKT10439	6/-
2G308	6/6	2N3134	6/-	25104	6/6	BC122	4/-	BFV59	6/6		
2G309	6/-	2N3135	6/-	25501	5/6	BC125	13/6	BFV60	6/6		
2G371	3/6	2N3136	6/-	25502	5/6	BC126	13/6	BSX19	5/6	NKT10519	6/-
2G374	4/6	2N3390	10/6	25503	5/6	BC140	11/-	BSX20	5/6		
2G381	4/6	2N3391	7/6	3N83	13/6	BC147	5/-	BSX21	8/6	NKT20329	6/-
2N404	6/6	2N3391A	6/-	3N128	18/6	BC149	4/6	BSX22	10/6		
2N696	5/-	2N3392	6/6	3N140	19/6	BC151	5/-	BSX23	10/6	NKT20339	6/6
2N697	5/-	2N3393	6/6	3N141	21/6	BC157	4/-	BSX24	10/6		
2N698	4/6	2N3394	5/6	3N142	16/6	BC158	3/6	BSX25	10/6	NKT80111	15/6
2N706	2/6	2N3402	7/6	3N143	19/6	BC159	4/-	BSX61	12/6		
2N708	4/-	2N3404	8/6	R.C.A.	24/-	BC160	12/6	BSX76	4/6	NKT80112	19/6
2N709	12/6	2N3405	12/6	40250	16/6	BC167	3/6	BSX77	6/6		
2N718	6/-	2N3414	5/6	40251	17/6	BC168	3/6	BSX78	6/6	NKT80113	22/6
2N726	5/-	2N3415	6/6	40253	8/6	BC169	3/6	BSY10	5/6	NKT80211	18/6
2N727	5/-	2N3416	7/6	40254	10/6	BC171	3/6	BSY24	4/-		
2N743	4/6	2N3417	11/6	40309	10/6	BC172	3/6	BSY25	4/-	NKT80212	18/6
2N744	4/6	2N3570	12/6	40310	13/-	BC182	4/6	BSY26	4/-		
2N753	5/6	2N3570	12/6	40311	10/6	BC183	4/6	BSY27	4/-	NKT80213	18/6
2N914	3/6	2N3605	5/6	40312	13/6	BC184	4/6	BSY28	4/-		
2N916	3/6	2N3606	5/6	40314	11/-	BC194	5/6	BSY29	4/-	NKT80214	18/6
2N918	6/-	2N3607	4/6	40315	11/-	BC195	5/6	BSY32	5/-		
2N929	5/6	2N3662	9/6	40316	12/6	BC192	5/6	BSY36	5/-	NKT80215	18/6
2N930	6/6	2N3663	10/6	40317	11/-	BCY30	7/6	BSY37	5/-		
2N937	10/6	2N3702	4/-	40319	14/6	BCY31	4/6	BSY38	4/6	NKT80216	18/6
2N1090	6/6	2N3704	5/6	40320	11/-	BCY32	7/6	BSY39	4/6		
2N1131	8/6	2N3705	4/6	40324	12/6	BCY33	5/6	BSY40	6/6	OC20	21/6
2N1132	8/6	2N3706	4/6	40326	10/6	BCY38	5/6	BSY51	10/6	OC22	8/6
2N1302	4/-	2N3707	4/-	40329	7/6	BCY39	6/6	BSY52	9/6	OC23	9/6
2N1303	4/-	2N3708	4/-	40334	8/-	BCY40	7/6	BSY54	6/-	OC24	7/6
2N1304	4/6	2N3709	4/-	40340	11/-	BCY42	3/-	BSY56	6/-	OC25	8/6
2N1305	4/6	2N3859A	6/-	40430	11/-	BCY43	3/-	BSY78	9/6	OC26	6/6
2N1306	5/6	2N3871	9/6	40361	12/6	BCY54	7/6	BSY79	9/6	OC28	8/6
2N1307	5/6	2N3872	9/6	40362	14/6	BCY58	4/6	BSY82	6/6	OC30	6/6
2N1308	6/-	2N3873	17/6	40467	16/6	BCY60	19/6	BSY85	13/6	OC36	6/6
2N1309	6/6	2N3874	5/6	40468	16/6	BCY71	9/6	BSY87	10/6	OC38	10/6
2N1420	7/6	2N3875	5/6	40469	16/6	BCY72	5/6	BSY90	11/6	OC42	4/6
2N1507	5/6	2N3876	5/6	AC107	6/-	BCY75	4/6	BSY95A	3/6	OC44	4/6
2N1525	7/6	2N3855A	6/-	AC126	5/-	BCZ11	17/6	BSW70	5/6	OC45	2/6
2N1526	7/6	2N3856A	6/-	AC128	4/-	BD121	17/6	BSW70	5/6	OC46	3/6
2N1527	7/6	2N3856	6/-	AC127	5/-	BD123	21/6	D16P1	7/6	OC70	3/6
2N1605	9/6	2N3856A	6/-	AC128	4/-	BD124	12/-	D16P2	8/-	OC71	2/6
2N1613	6/6	2N3858	5/6	AC154	4/6	BD125	12/6	D16P3	7/6	OC72	2/6
2N1631	8/6	2N3858A	6/-	AC176	6/-	BF115	5/6	D16P4	8/-	OC75	4/6
2N1632	8/6	2N3859	5/6	AC187	12/-	BF117	5/6	GET102	6/-	OC76	3/6
2N1637	8/6	2N3859A	6/-	AC188	12/-	BF169	7/6	GET103	6/-	OC78	3/6
2N1638	8/6	2N3860	6/-	AC17	5/6	BF173	7/6	GET114	4/-	OC81	4/6
2N1639	8/6	2N3877	9/6	AC19	5/6	BF177	11/6	GET114	4/-	OC82	3/6
2N1711	6/6	2N3877A	9/6	AC19	5/6	BF178	10/6	GET116	6/-	OC83	3/6
2N1889	8/6	2N3900	10/6	AC20	5/6	BF179	11/6	GET118	4/-	OC84	3/6
2N1893	8/6	2N3900A	11/6	AC21	5/6	BF180	7/6	GET119	4/-	OC85	3/6
2N2147	12/6	2N3901	19/6	AC22	4/6	BF181	6/6	GET120	6/6	OC87	3/6
2N2148	12/6	2N3903	8/6	AC23	4/6	BF184	7/6	GET120	6/6	OC88	3/6
2N2160	14/6	2N3904	8/6	AC24	4/6	BF187	5/6	GET123	6/6	OC89	4/6
2N2193	5/6	2N3905	8/6	AC24	5/6	BF185	5/6	GET123	6/6	OC92	4/6
2N2193a	5/6	2N3906	8/6	AC24	5/6	BF194	6/6	GET188	4/6	OC94	4/6
2N2194a	4/6	2N4058	6/6	AD140	8/-	BF195	5/6	GET189	4/6	OC123	4/6
2N2218	6/6	2N4059	5/6	AD149	11/6	BF196	5/6	GET189	4/6	OC139	6/6
2N2219	6/6	2N4061	5/6	AD150	15/6	BF197	5/6	GET189	4/6	OC140	6/6
2N2220	5/6	2N4062	5/6	AD162	7/6	BF198	5/6	GET189	4/6	OC170	6/6
2N2221	5/6	2N4244	9/6	AF106	11/6	BF224	6/6	MAT100	6/-	OC200	5/6
2N2222	5/6	2N4255	8/6	AF114	5/6	BF225	6/6	MAT101	6/-	OC201	5/6
2N2287	21/6	2N4255	7/6	AF115	5/6	BF237	6/6	MAT120	6/-	OC202	8/6
2N2297	6/6	2N4285	3/6	AF116	5/6	BF238	6/6	MAT121	6/-	OC203	5/6
2N2303	7/6	2N4286	3/6	AF118	12/6	BFX12	5/6	MJ400	21/6	OC204	5/6
2N2368	6/6	2N4287	3/6	AF119	12/6	BFX13	5/6	MJ420	22/6	OC205	7/6
2N2369	7/6	2N4288	3/6	AF117	12/6	MJ421	22/6	OC207	7/6	OC207	7/6
2N2369a	5/6	2N4289	4/6	AF124	5/6	BFX30	9/6	MJ430	20/6	OC271	10/6
2N2410	10/6	2N4290	3/6	AF125	5/6	BFX43	8/6	MJ440	19/6	ORP12	8/6
2N2411	6/6	2N4291	3/6	AF126	5/6	BFX44	8/6	MJ480	20/6	ORP60	10/6
2N2412	6/6	2N4292	3/6	AF127	5/6	BFX68	13/6	MJ481	27/6	ORP61	10/6
2N2483	5/6	2N4493	5/6	AF128	12/6	BFX84	13/6	MJ490	22/6	P346A	5/6
2N2484	5/6	2N4434	5/6	AF129	12/6	BFX84	8/6	MJ491	29/6	P346A	5/6
2N2539	4/6	2N4435	5/6	AF179	14/6	BFX85	10/6	MIE340	15/-	TIP32A	22/6
2N2540	4/6	2N5027	10/6	AF180	12/6	BFX86	8/6	MPF102	8/6	TIS34	16/6
2N2543	7/9	2N5028	11/6	AF181	8/6	BFX87	10/6	MPF103	7/6	TIS43	8/6
2N2614	7/6	2N5029	9/6	AF239	7/6	BFX88	5/6	MPF104	7/6	TIS44	3/6
2N2645	11/6	2N5030	8/6	AF279	13/6	BFX89	12/6	MPF105	8/6	TIS45	4/6
2N2646	11/6	2N5172	4/6	AF280	13/6	BFX92A	12/6	MP53638	6/6	TIS46	4/6
2N2696	6/6	2N5174	12/6	AF281	12/6	BFY10	4/6	NKT0013	8/6	TIS47	4/6
2N2711	8/6	2N5175	12/6	AS526	5/6	BFY11	4/6	NKT124	8/6	TIS48	4/6
2N2712	8/6	2N5176	13/6	AS527	8/6	BFY12	4/6	NKT125	6/6	TIS49	4/6
2N2713	9/6	2N5232	8/6	AS528	5/6	BFY18	4/6	NKT126	7/6	TIS50	5/6
2N2714	9/6	2N5232A	9/6	AS529	4/6	BFY19	4/6	NKT128	5/6	TIS51	4/6
2N2865	12/6	2N5245	12/6	AS536	5/6	BFY20	12/6	NKT135	5/6	TIS52	4/6
2N2904	8/6	2N5246	12/6	AS537	5/6	BFY21	8/6	NKT137	6/6	TIS53	6/6
2N2904A	8/6	2N5249	13/6	AS531	6/6	BFY24	10/6	NKT137	6/6	TIS56	6/6
2N2905	8/6	2N5249A	13/6	AS533	5/6	BFY25	5/6	NKT139	6/6	TIS57	6/6
2N2905A	8/6	2N5305	7/6	AS534	5/6	BFY26	4/6	NKT212	5/6	ZTX107	3/6
2N2906	8/6	2N5306	8/6	AS562	5/6	BFY29	10/6	NKT213	6/6	ZTX108	3/6
2N2906A	8/6	2N5307	7/6	AS563	3/6	BFY30	10/6	NKT214	4/6	ZTX109	3/6
2N2907	8/6	2N5308	7/6	AS572	5/6	BFY36	4/6	NKT215	4/6	ZTX300	4/6
2N2923	8/6	2N5309	6/6	AS583	5/6	BFY37	5/6	NKT216	6/6	ZTX301	4/6
2N2924	4/6	2N5310	8/6	AS586	6/6	BFY41	10/6	NKT217	8/6	ZTX302	5/6
2N2925	4/6	2N5354	5/6	AS520	7/6	BFY43	13/6	NKT219	6/6	ZTX303	5/6
2N2926	4/6	2N5355	5/6	AS521	7/6	BFY50	4/6	NKT223	6/6	ZTX304	7/6
.. Green	3/-	2N5356	10/6	AUY10	30/-	BFY51	4/6	NKT224	5/6	ZTX500	5/6
.. Yellow	2/9	2N5365	9/6	BC107	3/6	BFY52	4/6	NKT225	5/6	ZTX501	5/6
.. Orange	2/6	2N5366	10/6	BC108	3/6	BFY53	5/6	NKT229	6/6	ZTX502	6/6
2N3017	7/6	2N5367	11/6	BC109	3/6	BFY56A	11/6	NKT237	8/6	ZTX503	5/6
2N3014	7/6	2N5457	7/6	BC113	6/6	BFY75	6/6	NKT238	6/6	ZTX504	12/6

PANEL METERS
38 Series—FACE SIZE 42 x 42mm. All prices for 1-9 pieces.
50µA, 37/6; 100µA, 35/-; 200µA, 32/6; 500µA, 27/6; 50.0-50µA, 35/-; 100.0-100µA, 32/6; 500.0-500µA, 25/-; 1MA, 25/-; 5MA, 25/-; 10MA, 25/-; 50MA, 25/-; 100MA, 25/-; 500MA, 25/-; 1A, 25/-; 5A, 25/-; 10V, 25/-; 20V, 25/-; 50V, 25/-; 300V, 25/-; 500V, 25/-

SILICON RECTIFIERS

PIV	50	100	200	400	600	800	1000	12000
1A	2/9	3/-	3/3	3/6	3/9	4		

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service




NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3, and Trawler Band. Built in ferrite rod aerial for Medium and Long Waves. 5 section 22in chrome plated telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 x 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **£6.19.6** P. & P. 7/6

roamer seven mk IV

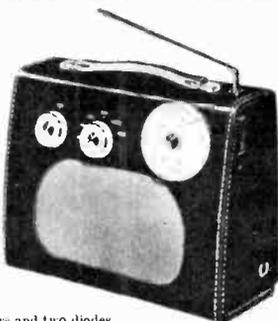


7 FULLY TUNABLE WAVE BANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts).

Total building costs **£5.19.6** P. & P. 7/6 Personal Earpiece with switched socket for private listening, 5/- extra.

NEW!

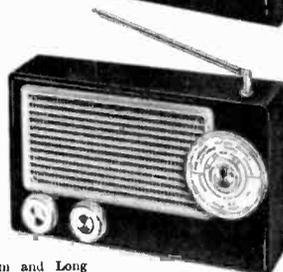transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER




Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **89/6** P. & P. 5/6 Earpiece with switched socket for private listening 5/- extra.

pocket five

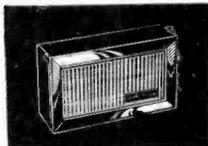MEDIUM WAVE, LONG WAVE AND TRAWLER BAND
PORTABLE
WITH SPEAKER AND EARPIECE



Attractive black and gold case. Size 5 1/2 x 1 1/2 x 5 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs **44/6** P. & P. 3/6

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND
PORTABLE
WITH SPEAKER AND EARPIECE




Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).

Total building costs **47/6** P. & P. 3/9

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

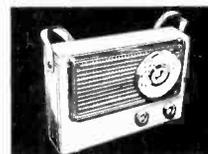

Attractive case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).

Total building costs **79/6** P. & P. 4/6

RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked
 ROAMER EIGHT ROAMER SEVEN
 TRANSEIGHT POCKET FIVE
 TRANSONA FIVE ROAMER SIX

Parts price list and plans for.....

Name.....

Address.....

PE14

* Callers side entrance Stylo Shoe Shop

* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Sonotone 9TA and 9TA/HC. Diamond Cartridge brand new, boxed in manufacturers' carton **49/6** plus 2/6 p/p. **Acos GP 91-1 and GP 91-3** stereo compatible cartridges, new in sealed manufacturers' cartons **22/6** plus 2/6 p/p.

BASF TAPE 25% OFF

5in 600ft. 14/- 900ft. 19/- 1200ft. 30/-
5½in 900ft. 19/- 1200 ft. 24/- 1800ft. 39/-
7in 1200ft. 24/- 1800ft. 35/- 2400ft. 57/-
P/P 2/- per reel—over £5 FREE

SPECIAL PURCHASE

12in 15watt HI-FI LOUDSPEAKERS

Made by famous British manufacturer to very high standards, heavy duty cast chassis, twin cone construction, smooth extended range, with very low level of distortion.—Response 35-17,500Hz.—impedance 15 ohms—flux, 11,000 gauss.

WALDON PRICE 97/6 each plus 6/6 P. & P.

E.M.I. HI-FI SPEAKERS

SET 450: 13×8 with two built-in tweeters and cross-over unit. **Our Price 69/6.** 3 or 15 ohm, 10W, 40-13,000Hz.

SET 850: 6in bass plus 3½in tweeter and cross-over unit. 8 ohm, 10W, 65-20,000Hz. **79/6.**

SET 250: 5in heavy duty bass plus 3in tweeter and cross-over unit. 8 ohm, 6W, 80-20,000Hz. **85/-**

Add 5/6 p/p for each speaker set.

TRIO Stereo Moving Magnet Cartridge Model AD76K. Diamond Stereo LP Stylus. Frequency response 20-20,000c/s output. 7mV tracking pressure 2 grammes ± 0.5 grm. Fully guaranteed. Price **85/-** p/p free.

GARRARD UNITS

	£	s	d
SP25 Mk. II	11	9	6
AP75	17	19	6
SL65	14	9	6
*3500	11	9	6

*Denotes including Sonotone 9TA-Stereo/Diamond Cartridge. Elegantly styled plinth and cover to suit the above units. From **5 gns.** Please add 10/-p/p each on all above items.

SPEAKER ENCLOSURES


Designed to accept the full range of E.M.I. loudspeakers. Beautifully styled in teak.

Prices from **89/6** each.

25 WATT GROUP SPEAKERS

Guitar group 25. 12in round, heavy duty cone, with solid aluminium chassis, 15 ohms imp. 12,000 gauss. Response 30-10,000c/s. **OUR SPECIAL PRICE**

£.5.9.6 plus 6/6 P. & P.

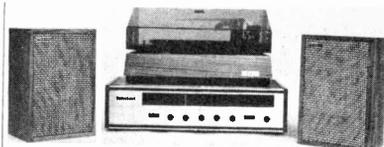

The greatest budget system available today—can't be beaten—price or quality anywhere—look at these great features—then compare:

Teleton FZ000 Mk. II. Tuner amp. Latest version with all the new features. Tuning indicator—fused circuit protection, AM-FM fitted multiplex, A.F.C. 2×5 watts per channel. A truly outstanding unit. £ s d 43 1 8

Garrard 3500 (Auto/single). Latest in the great new Garrard range, provides facilities and controls that are usually found only on much more expensive units 13 11 0

Teleton SA1003 matching speaker systems 10 0 0

Sonotone 9TA stereo cartridge with diamond styli—a perfect match 4 2 0

Plinth/Cover elegantly styled 7 0 0

Plugs and Leads all supplied 1 5 0

Normal Retail Price £78 19 8

Exclusively offered by **WALDON** +25/- at the remarkably low price of **63 gns** Carrg.

All items may be purchased separately.

WALDON ELECTRONICS, 707 Blackburn Road, Bolton, Lancs. Bolton 54280

PLEASE ENCLOSE 1/0 IN STAMPS WITH ENQUIRIES

ALL MOTORISTS ARE KEEN TO CUT COSTS 2,972,000

(National Readership Survey July '68 to June '69)

Do something about it. They read **PRACTICAL MOTORIST**

for some or all of the following reasons:

- ★ To keep their cars in as good a condition as a good garage can
- ★ To keep their cars in a better condition than a mediocre garage can
- ★ To save up to four-fifths of the garage bills
- ★ To guard against defects that keep running expenses up and resale value down
- ★ To save their own necks — they trust nobody but themselves with servicing and maintenance

PRACTICAL motorist the most widely read motoring monthly
START CUTTING COSTS. PLACE A REGULAR ORDER TODAY! 2/6

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
AC177	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AF117	3/6	2N1306-7	6/-
AF239	12/6	2N1308-9	8/-
AF186	10/-	2N3844A	5/-
AF139	10/-	Power Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	2/6	AUY10	30/-
OC45	2/6	2N3055	15/-
OC71	2/6	Diodes	
OC72	2/6	AA42	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/6	OA81	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

FREE!
PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

TRY OUR X PAKS FOR UNEQUALLED VALUE

XA PAK
Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1000
POST & PACKING 4/6 U.K.

XB PAK
Silicon TO-18 CAN type transistors NPN/PNP mixed lots with equivalents to OC200-1, 2N706A, BSY27/29, BSY95A.

PRICE £4.5.0 PER 500
PRICE £8 PER 1000
POST & PACKING 2/6 U.K.

XC PAK
Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £4.10.0 PER 1000
POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMICONDUCTORS. FREE PACKS SUSPENDED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries inc. Book of Instructions	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output. Pair	10/-
B81	10	Reed Switches, mixed types large and small	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	10/-
B92	4	NPN Sil. Trans. A06 = BSX20, 2N2369 500 MHz, 360mV	10/-
B93	5	GET13 Trans. equiv. to ACY17-21 PNP Germ.	10/-
B94	6	NPN Sil. Planar Epitaxial Trans. CS4 similar to BSY38 or BC108	10/-
B96	5	2N1336 PNP Sil. Trans. TO-18, HFE 100-300 I.C. 600mA, 200 MHz	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC136, OC81/2, OC71/2, NKT271, etc.	10/-
B99	200	Capacitors, Electrolytics paper, silver mica, etc. Post and packing, this Pak 2/6	10/-
H4	250	Mixed Resistors. Post and Packing 2/-	10/-
H7	40	Wirewound Resistors. Mixed types and values. Postage 1/6	10/-

RETURN OF THE UNBEATABLE P.I PAK. NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 10/-
2/- P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **20/- each**

FREE CATALOGUE AND LISTS FOR:-

**ZENER DIODES
TRANSISTORS, RECTIFIERS
FULL PRE-PAK LISTS
& SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS add EXTRA FOR AIRMAIL.

P.O. RELAYS 8 FOR
Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/- **20/-**

LOOK! TRANSISTORS ONLY 1/- EACH

TYPE A		TYPE B		TYPE C	
PNP	SILICON TO-5 CAN	PNP	SILICON PLASTIC ENCAPSULATION	NPN	SILICON TO-18 CAN
SPEC:-	ICER AT VCE=20v 1mA MAX. HFE 15-100	SPEC:-	ICER AT VCE=10v 1mA MAX	SPEC:-	ICER AT VCE=20v 1mA MAX
THESE ARE OF THE 2S300 TYPE WHICH IS A DIRECT EQUIVALENT TO THE OC200/205 RANGE		THESE ARE OF THE 2N3702/3 AND 2N4059/62 RANGE		THESE ARE SIMILAR TO THE BC108/109 TYPES	

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data and Circuits of types, supplied with orders	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can	10/-
B82	10	OC45, OC81D and OC81 Trans. Mullard glass type	10/-
B83	200	Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	10/-
B66	150	High quality Germ. Diodes. Min. glass type	10/-
B86	50	Sil. Diodes sub. min. 1N914 and 1N916 types	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes Mixed Voltages	10/-
H5	16	1 Amp. Plastic Diodes 50-1000 Volts	10/-
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	10/-



SPECIAL OFFER
12 VOLT STABILISED POWER UNITS
INPUT 110-250 V. AC.
OUTPUT 11-13V Stabilised AT 1 AMP.
Brand New makers surplus at the unrepeatable Price of £5 each
Post & Packing 7/6

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

R.S.T. VALVE MAIL ORDER CO.
BLACKWOOD HALL, WELLFIELD RD., S.W.16
SPECIAL EXPRESS MAIL ORDER SERVICE

1N21	3/6	28308	9/-	BCY54	7/3	GET116	6/-	OC20	17/6
1N21B	5/-	28501	5/-	BCY60	19/-	GET118	4/-	OC23	8/-
1N23	4/-	28703	12/6	BCY70	6/-	GET119	4/-	OC24	8/6
1N85	17/6	38148	19/-	BD11	6/-	GET120	6/6	OC24	9/-
1N293	10/-	A13759	4/-	BD121	19/-	GET587	8/6	OC25	7/6
1N296	10/-	AA129	5/-	BD123	22/6	GET872B	6/-	OC26	6/-
1N645	5/-	AA212	3/6	BD124	12/-	GET873	3/-	OC28	12/6
1N725A	4/-	AA213	3/-	BDY11	5/6	GET875	6/-	OC29	14/6
1N4007	4/6	AC107	5/6	BF115	5/6	GET880	8/9	OC30	8/-
18021	4/-	AC126	4/-	BF117	10/-	GET882	6/-	OC35	6/3
18113	3/-	AC127	5/-	BF167	6/6	GET885	10/-	OC36	8/6
18130	2/6	AC128	4/6	BF173	7/3	GEX35	4/6	OC38	10/3
18131	2/6	AC129	7/6	BF181	6/-	GEX3	1/6	OC41	4/6
2G220	12/6	AC187	11/-	BF184	7/6	GEX941	4/-	OC42	5/-
2G240	3/6	AC188	11/-	BF185	6/-	GJ3M	7/6	OC43	9/-
2G301	3/6	ACY17	4/6	BF194	6/3	GJ4M	7/6	OC44	4/-
2G306	8/-	ACY18	4/-	BF195	5/6	GJ5M	7/6	OC45	3/3
2G371B	4/-	ACY19	5/-	BF196	5/6	HG1005	10/-	OC46	3/-
2G381A	4/6	ACY20	5/-	BF197	5/6	MAT100	6/-	OC58	12/6
2G403	10/-	ACY21	4/6	BFX12	5/6	MAT101	8/3	OC59	17/-
2G414	6/-	ACY22	4/-	BFX13	5/6	MAT120	5/9	OC70	3/6
2G417	6/-	ACY27	5/-	BFX29	12/-	MAT121	6/-	OC71	3/6
2N214	8/6	ACX28	4/-	BFX30	8/6	MJ429	22/-	OC72	4/4
2N404	6/-	ACX39	12/6	BFX35	19/6	MJ421	22/-	OC73	7/3
2N247	9/6	ACX40	4/-	BFX43	8/3	NKT129	6/-	OC74	4/6
2N697	4/-	ACX41	5/-	BFX44	8/3	NKT135	5/3	OC75	4/6
2N698	4/6	ACX44	7/6	BFX68	13/-	NKT210	6/-	OC76	3/6
2N706	3/-	AD140	8/-	BFX88A	13/6	NKT211	6/6	OC77	4/-
2N706A	3/6	AD149	8/-	BFX85	10/-	NKT212	5/4	OC78	3/-
2N708	4/-	AD150	15/-	BFX86	9/6	NKT213	6/6	OC78D	3/3
2N709	12/6	AD161	7/6	BFX87	9/6	NKT214	4/4	OC79	5/3
2N711	7/6	AD162	7/-	BFX88	5/-	NKT215	4/6	OC81	4/-
2N987	10/6	AF106	10/6	BFY20	12/-	NKT216	6/4	OC81D	4/-
2N1090	6/6	AF114	5/-	BFY21	8/6	NKT217	8/4	OC81DM	4/-
2N1091	6/6	AF115	5/-	BFY24	9/-	NKT218	22/6	OC81M	5/-
2N1131	8/6	AF117	4/6	BFY41	9/6	NKT219	6/6	OC82	3/6
2N1132	7/6	AF118	12/-	BFY43	12/6	NKT221	5/6	OC82D	3/6
2N1303	4/6	AF118	12/-	BFY50	5/-	NKT223	6/6	OC83	4/6
2N1305	4/3	AF119	4/-	BFY51	6/-	NKT224	4/9	OC84	4/9
2N1304	4/9	AF124	5/-	BFY53	5/6	NKT225	4/9	OC114	7/6
2N1305	5/-	AF125	5/-	BFY77	12/-	NKT227	5/6	OC122	12/6
2N1306	5/-	AF126	5/-	BFY90	12/6	NKT229	5/9	OC123	4/4
2N1307	5/-	AF127	4/6	BXX27	10/-	NKT237	7/9	OC139	7/6
2N1308	6/-	AF139	7/6	BXX60	18/6	NKT238	5/9	OC140	7/6
2N1309	6/-	AF178	12/6	BSY61	12/-	NKT240	6/6	OC141	12/3
2N1420	7/3	AF179	11/-	BSY26	3/6	NKT241	6/6	OC169	6/-
2N1597	5/6	AF180	12/-	BSY27	4/-	NKT251	4/9	OC170	5/6
2N1626	7/6	AF181	8/-	BSY61	10/-	NKT261	4/6	OC171	6/-
2N1909	45/-	AF186	11/-	BSY78	9/3	NKT274	4/9	OC172	7/-
2N2147	16/6	AFY19	22/6	BSY79	9/3	NKT275	5/-	OC200	5/6
2N2148	12/-	AFZ11	6/-	BSY82	10/-	NKT277	4/9	OC201	8/6
2N2160	14/-	AFZ12	6/6	BSY83	11/-	NKT403	9/9	OC202	8/6
2N2193	5/6	ASX27	5/6	BSY84	12/-	NKT404	12/6	OC203	6/-
2N2287	20/6	ASX28	2/6	BSY85A	3/6	NKT678	6/-	OC204	5/6
2N2297	6/6	ASX28	5/6	BY100	12/-	NKT713	7/6	OC205	14/6
2N2369A	5/-	ASX29	5/-	BY213	5/-	NKT773	6/-	OC206	9/6
2N2410	10/6	ASX36	5/6	BYZ11	5/-	NKT777	7/6	OC207	7/6
2N2411	6/6	ASX60	5/-	BYZ11N	7/6	NKT8013		OC450	6/-
2N2412	6/6	ASX61	6/6	BYZ12	6/-	O78B	7/6	OC470	6/-
2N2483	5/6	ASX53	4/9	BYZ14	27/6	AS5	3/6	OCPT1	20/-
2N2484	5/6	ASX54	4/9	BYZ16	17/6	OAI0	3/-	PS144	4/-
2N2546	11/6	ASX55	6/-	C111	13/-	OA47	2/-	R19T	6/-
2N2696	6/3	ASX62	6/-	C20A	12/6	OA70	1/6	SAC40	5/-
2N2865	12/-	ASX86	6/6	CRS1/05	5/-	OA71	2/-	SFT308	7/6
2N2904	7/6	ASZ20	13/6	CS4B	37/6	OA73	2/-	SJ052F	7/6
2N2904A	8/-	ASZ21	7/6	CS10B	67/6	OA74	4/-	ST722A	5/-
2N2906	8/-	ASZ23	19/6	CV101	6/-	OA79	1/9	ST7231	12/6
2N2907	7/6	ASZ23	19/6	CV253	20/-	OA81	1/6	SX68	4/6
2N2926	3/-	AUY10	19/6	CV2154	32/6	OA85	1/6	SX68H	4/6
2N2924	4/6	BC107	3/6	CV2155	32/6	OA86	4/-	SX631	7/6
2N3014	7/6	BC108	3/6	CV2279	10/6	OA90	1/6	SX631CC	10/-
2N3054	11/-	BC109	3/6	CV2923	4/6	OA91	1/6	SX680T	4/-
2N3055	14/6	BC113	6/3	CV2923	4/6	OA95	1/6	SX634WK	8/-
2N3705	4/-	BC115	6/6	CV4073	3/-	OA95	1/6	SZ33C	12/-
2N3706	4/6	BC116	6/6	CV4074	3/6	OA200	2/-	V15/10P	15/-
2N3707	4/-	BC118	6/6	CV7108	80/-	OA202	2/-	V15/30P	15/-
2N3708	4/-	BC121	4/-	CV7109	75/-	OA210	6/6	V30/201P	9/6
2N3709	4/-	BC122	4/-	CV7183	30/-	OA211	10/-	XA122	6/-
2N3710	4/-	BC125	13/6	CV7312	10/-	OA2200	11/-	XA124	4/-
2N3819	8/-	BC126	13/6	CV7324	10/-	OA2201	10/-	XA142	5/-
2N3820	20/-	BC140	11/-	CV7341	6/-	OA2202	7/6	XA143	5/-
2N3823	17/-	BC145	15/-	CV7347	4/-	OA2203	8/-	XA152	5/-
2N3900	10/6	BC148	4/6	CV7361	12/6	OA2204	8/-	XA162	8/6
2N3900A	11/-	BC149	5/-	D246	7/6	OA2207	10/-	XB101	8/6
2N5027	10/6	BC157	4/-	DD006	6/6	OA2208	6/6	XB121	8/6
2N5028	11/6	BC160	12/6	DD007	8/-	OA2210	6/6	XB105	8/6
2N5029	7/6	BCY31	6/-	DD008	7/6	OA2222	9/6	XK518	6/-
2N5307	7/6	BCY32	7/6	GD3	6/6	OA2224	9/6	Z2A82CR	6/-
2N5308	7/6	BCY32	7/6	GD4	7/6	OA2225	7/6	ZR24	12/6
2N5309	11/-	BCY33	5/-	GD5	6/6	OA2242	4/6	ZS32A	6/-
28005	14/-	BCY34	5/-	GD6	6/-	OA2246	4/6	ZT21	6/-
28013	15/-	BCY38	5/6	GD8	5/-	OA2290	9/-	ZT43	8/-
28013A	16/6	BCY39	7/-	GET102	5/-	OC16	15/-		
28301	12/6	BCY40	7/6	GET113	5/-	OC18T	16/6		
28304	9/-	BCY42	3/-	GET114	4/-	OC19	8/6		

TRANSISTORS (POSTAGE, PACKING & INSURANCE) 1/3 PER ORDER

SEND S.A.E. FOR LIST OF 2,000 TYPES—
 VALVES, TUBES AND TRANSISTORS

TERMS OPEN DAILY TO CALLERS
 C.W.O. Mon.—Sat. 9 a.m.—5.30 p.m. Closed Sat. 1.30 p.m.—2.30 p.m.
 no C.O.D. Tel. 01-769 0199/1649

There is scope, variety and responsibility as a RADIO TECHNICIAN in Air Traffic Control

Join the National Air Traffic Control Service of the Board of Trade as a Radio Technician and you have the prospect of a steadily developing career in a demanding and ever-expanding field.

Entrance qualifications: you should be 19 or over with at least one year's practical experience in telecommunications. Preference will be given to those having OñC or qualifications in telecommunications.

Once appointed and given familiarisation training, you will be doing varied and vital work on some of the world's most advanced equipment including computers, radar and data extraction, automatic landing systems, communications and closed-circuit television. Work is based on Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

Salary: £985 (at 19) to £1,295 (at 25 or over); scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. Promotion prospects are excellent and ample opportunity and assistance is given to study for higher qualifications. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Send this coupon for full details and application form
 To: A. J. Edwards, C. Eng., M.I.E.E., M.I.E.R.E., Room 705,
 The Adelphi, John Adam Street, London WC2
 marking your envelope 'Recruitment'.

Name

Address

Not applicable to residents outside the United Kingdom. PE/A3

NATCS National Air Traffic Control Service

Practical Electronics Classified Advertisements

MISCELLANEOUS

HI-FI loudspeaker systems for the home constructor, cabinet kits, the new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding, speaker fabric (samples on request) and all other necessary components. Send 5d in stamps to: AUDIOSCAN, Dept. PE, 4 Princes Square, Harrogate, Yorks.

MUSICAL MIRACLES. Send S.A.E. for details of Rhythm Modules, Versatile Bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50µA meters 25/- post paid. HURRY! D.E.W. LTD. 254 Ringwood Road, Ferndown, Dorset.

ETCHED PRINTED CIRCUIT BOARD KITS. Full instructions. 19/6, c.w.o. CIR-CUITETCH, 12 Cambridge Rd., St. Albans, Herts.

A CORNUCOPIA OF COMPONENTS! Scarce Valves, selected TV Components, Educational and Projects kits, Speakers and Cabinets, Transistors, Resistors and valves, ½ watt, 3d each. State your requirements. S.A.E. for details. MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

NOTES ON USE OF TV for Aircraft or UFO Detection. Optical Detector Set and Instructions, 7/6 each. RADAR & ELECTRONICS PUBLICATIONS, 1 Stowmarket Road, Needham Market, Suffolk.

BUILD IT in a DEWBOX quality cabinet 21n x 2½n x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

BARGAIN PACK. 200 assorted springs, nuts, washers, screws. Popular sizes 7/6, including postage. COHAVEN, Industrial Estate, Ripley, Derbyshire.

SCRAP R.F. HEATING AND TRANSMITTING VALVES wanted. TY5-500, TY6-800, TY7-600, ESA1500, 3J202E. May be interested in other types. Good price paid for valves still under vacuum. ELECTRONIC HEAT CO. (01-654 7172).

MORE ROBOTS

Synthetic Animals with "BRAINS" of their own. The LATEST range of projects include: an electronic 'animal' which "LEARNS", and an Electro Chemical device capable of "REPRODUCING" itself! Other projects SURE TO INTRIGUE YOU are a transmitter/receiver which has quite a useful range and RADIATES WITHOUT USING R.F. also TEN new projects, one of which is an electronic dice machine. HOSTS OF EASY-TO-CONSTRUCT projects, for anyone with a basic knowledge of Electronics. DON'T WAIT. SEND 3/- for your list—NOW!

To: 'BOFFIN PROJECTS'

4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY
Designed by GERRY BROWN and
JOHN SALMON and presented
on T.V.

PHOTO ETCHED PRINTED CIRCUIT BOARDS for all P.E. projects. Electric fence, February 1969 4/-; Servoamplifier, September 1969 7/6. Send S.A.E. for full list. Your own circuit boards etched for 2d per square inch, plus postage. Boards made to your own design. CASTLE LABORATORIES, 32 Stapleton Close, Highworth, Wilts.

RATES: 1/3 per word (minimum 12 words). Box No. 1/6 extra.

Advertisements must be prepaid and addressed to Advertisement Manager,

"Practical Electronics"

IPC MAGAZINES LTD.,

Fleetway House, Farringdon Street,

London, E.C.4

MISCELLANEOUS (continued)

6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent, etc. Fully transistorised, low battery drain
Unbeatable at £2.19.6 post paid.
or in kit form 50/-

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 65/- POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

LONDON RADIO CONTROLLED SOCIETY. Meetings 2nd Thursday each month, 7.30 p.m. "The Rose and Crown", Park Lane, London, W.1 (between Piccadilly and Hilton Hotel). All aspects of Radio Controlled Models. Beginners and experts welcome; come along, or phone 369-3568 or 907-6271 for more information. Please note change of address.

JOURNAL OF PARAPHYSICS. Russian experiments: Telekinesis ("mind-over-matter"); brainwaves actuate electronic relays; transistor UFO detectors; finger-vision; hyperspace; time-reversal: tachyons ("Faster than light"), etc. S.A.E. for list. 20s. for back issues. Paraphysical Laboratory, Downton, Wilts.

ORGAN BUILDERS. Stocks of our Ex-Computer Divider boards are now exhausted and (apart from orders already reserved) we regret we are unable to meet further orders. ROGER ALLEN.

PRACTICAL ELECTRONICS ORGAN. Complete set of capacitors and resistors as listed in 2nd article (June issue). Also 12 Vinkor inductors and 12 printed divider boards. All new and unused. Bought for over £60. Offers: G. HIRST, 21 Westport Road, Cleethorpes, Lincs. Humberston 3619.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PP, New Mills, Stockport.

P.E. ODDS, any reasonable offers, send S.A.E.: BARR, 37 Woodcock Avenue, Naphill, Bucks.

MORSE MADE EASY !!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to: GSHBC (Box 19), 45 GREEN LANE, FURLEY, SURREY

SERVICE SHEETS

RADIO TELEVISION, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6. SHE 8441.

SERVICE SHEETS (1925-69) for televisions, radios, transistors, tape recorders, record players, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/6. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS

Only 10/- each, plus LARGE S.A.E.

(Uncrossed P.O.'s please, returned

If service sheets not available.)

FREE TV FAULT TRACING CHART OR TV

LIST ON REQUEST

C. CARANNA

71 BEAUFORT PARK, LONDON, N.W.11

MAIL ORDER ONLY

BOOKS AND PUBLICATIONS

SURPLUS HANDBOOKS

19 set Circuit and Notes 6/6 P.P. 6d
1155 set Circuit and Notes 6/6 P.P. 6d
H.R.O. Technical Instructions ... 5/6 P.P. 6d
38 set Technical Instructions ... 5/6 P.P. 6d
46 set Working Instructions 5/6 P.P. 6d
88 set Technical Instructions 7/- P.P. 6d
BC. 221 Circuit and Notes 5/6 P.P. 6d
Wavemeter Class D Tech. Instr. 5/6 P.P. 6d
18 set Circuit and Notes 5/6 P.P. 6d
BC.1000 (31 set) Circuit & Notes 5/6 P.P. 6d
CR.100/B.28 Circuit and Notes 10/- P.P. 9d
R.107 Circuit and Notes 7/- P.P. 6d
A.R.88D. Instruction Manual. ... 18/- P.P. 6d
62 set Circuit and Notes 6/6 P.P. 6d
52 set Sender & Receiver Circuits 7/6. post free
Circuit Diagrams 5/- each post free.
R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.
A.1134, T.1154, CR.300, BC.342, BC.312.
BC.348.J.E.M.P. BC.624, 22 set.
Colour Code Indicator 2/6 P.P. 6d
S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:

Instructional Handbook Supplies
Dept. P.E., Talbot House, 28 Talbot Gardens
Leeds 8

HOLIDAYS

HOLIDAY FOR BOYS. 14/16 years August 1970, specialising in engineering, electronics, photography. Tuition and practical work including karting. 11 days—£14 10s. Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, 47 Marylebone Lane, London, W1M 6AX.

HI-FI EQUIPMENT

RELIABLE GUIDE to best value in Hi-Fi. Audio Supply's seventy-five-page illustrated catalogue (6/6), 18 Blenheim Road, London, W.4.

EDUCATIONAL

GET INTO ELECTRONICS—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. A.M.I.E.R.E., R.T.E.B., City & Guilds, Radio, T.V., Telecoms., etc. For FREE 100-page book, write Dept. 856K, CHAMBERS COLLEGE, College House, 29-31 Wrights Lane, Kensington, London, W.8.

TECHNICAL TRAINING in Radio, TV & Electronics thro' world-famous ICS. For details of proven home-study courses write: ICS, Dept. 561, Intertext House, Stewarts Road, London, S.W.8.

ENGINEERS. A technical certificate or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.T., A.I.O.B. and G.C.E. exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto, Electronics, Radio, Computers, Draughts, Building, etc. For full details write for FREE 132-page guide. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

RADIO OFFICERS see the world. Sea going and shore appointments. Trainee vacancies during 1970. Grants available. Day and Boarding students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay, Wales.

SITUATIONS VACANT

A.M.I.E.R.E., A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

TRAINEE RADIO TECHNICIANS

A PROGRESSIVE CAREER IN THE FIELD OF RADIO AND ELECTRONICS

Applications are now invited for an intensive training course of two years, leading to appointment as a fully qualified RADIO TECHNICIAN, with further prospects of progression to the Telecommunication Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at 7 September 1970, on which date training commences.

Minimum educational qualifications required are passes at GCE 'O' Level in English Language, Mathematics and Physics (already held or expected to be obtained in the Summer, 1970). Equivalent passes in Scottish or Northern Ireland Certificates and CSE Grade I passes are also acceptable.

Closing date for receipt of applications 27 February 1970.

Apply for full details and application form to:—

**THE RECRUITMENT OFFICER (TRT/54)
GOVERNMENT COMMUNICATIONS
HEADQUARTERS
OAKLEY, PRIORS ROAD
CHELTENHAM, GLOS.
GL52 5AJ**

SITUATIONS VACANT (continued)

SERVICE ENGINEERS—we are an old established electronics company, but headed by a young management team, and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead, phone MICHAEL ADLER at 01-636 9606.

HENRY'S RADIO LTD.
303 EDGWARE RD., LONDON, W.2
HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION

SALES ASSISTANTS

Young man with good general knowledge of electronic components required for our retail sales Dept. Please Telephone 723-1008/9 Ext. 1.

SALES ASSISTANTS HI-FI DEPT.

Young man with a good general knowledge of HIGH FIDELITY EQUIPMENT required for our retail HI-FI SALES DEPT. Please contact MR. STEVENS Telephone 723-6963

RECEIVERS AND COMPONENTS

TO HELP THE HOME CONSTRUCTOR. Heathkit now make available our surplus Resistors, Capacitors, etc. at Bargain Prices. Send for lists. E. MOYLE, Daystrom Ltd., Gloucester.

BRAND NEW ELECTROLYTICS, 15/16V, 0.5, 1, 2, 5, 8, 10, 15, 20, 30, 40, 50, 100, 200mF, 8d. Carbon film resistors 1/4W, 5% E12 Series 10 ohms to 1 Megohm, 1/6 per dozen. Minimum order 7/6. Postage 1/-. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

RECEIVERS AND COMPONENTS

(continued)

EMC HOLDINGS & PRODUCTS

Building Your Own Organ, Amplifier etc. Stop tabs, rocker tabs (plain) 1/6 each. Bargain pack, 24 rocker or tab type 30/- Nylon T. Piece for retaining Kimber-Allen contact blocks. 1 required for two contacts, sample 1/- each. Quantity discounts, e.g., 5/- for 6, 9/- for 12, 16/- for 24. Single pole wafer type switch, 6-way, 2/6 each. Co-ax plugs, 1/- each, 10/- doz. Jack plugs, heavy duty, moulded cover virtually unbreakable. British made, 3/- each, 33/- doz. Jack sockets, open type, 2/2 each, 24/- doz. Recess plates for above sockets, black nylon. Designed to allow flush mounting on exterior cabinet. Also suitable for lamps, switches, etc., 1/- each, 10/- doz. Heavy duty foot switch, die cast body, single pole complete with rubber actuator and base plate, 18/6 each. Polystyrene capacitors 10,000pF, 20,000pF, 1/6 each. 100 ohm wire wound resistors 4.5W, 1/- each, 10/- doz. Output transformer suitable for Mullard 3W amplifier, 12/6 each. Including circuit for amplifier. **Superb offer.** 12in Goodman Speakers, heavy duty, 70 Hz. bass resonance, 15 ohm speech coil, 20W, R.M.S., £7.19.8. **Terms.** Cash with order and 2/- in the £ for postage and packing. Orders over £5 post free.

Trade Enquiries invited:

**E.M.C., Dept. P.E.2, 22 Norwich Road
Bournemouth BH2 5QZ**
S.A.E. for latest Price Lists of Organ and Electronic Components.

SL 402A and SL 403A

Before you buy these excellent I.C. Audio Amplifiers let us quote you a price for your quantity. If you require one or one thousand we assure you it will be worthwhile sending a S.A.E. to:

S.W.A. (Components), 13 Millways, Great Totham, Essex.

Send 2/6 for full details and application Brochure (post free).



TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

ESTABLISHED 1891

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students coached until successful.

NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-meter and valve volt meter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL
CORRESPONDENCE
SCHOOLS**

**A WHOLE WORLD
OF KNOWLEDGE
AWAITS YOU!**

International Correspondence Schools
(Dept. 152), Intertext House, Stewarts Road,
London, S.W.8.

NAME
Block Capitals Please

ADDRESS

270

RECEIVERS AND COMPONENTS
(continued)

TAPE HEADS

BSR BRAD. 39/6 pair REUTER — COLLARO
2-TRACK ERASE 12/6
4-TRACK
BOGEN ERASE
U1E18/8 25/-
4-TRACK
MICHIGAN REC./PLAY COSMOCORD ERASE
MED. IMP. 35/- T.E. 2/9
4-TRACK 12/6

TRANSISTOR LW/MW/FM TUNER CHASSIS
The most compact three-band Tuner chassis ever engineered. Output 50mV, exceptional sensitivity and selectivity on all bands. Operates from single 9 volt battery. Complete with aerials, 3-band tuning dial, mounting bracket circuit and 13 instructions. £13

TUNER DULCI FM/T7S STEREO £23
LIST £31 FEW ONLY AT
Sens. 14mV, O.P. 100mV, 88-108 mc, dim. 134 x 24 x 7".

COMPACT TRANSISTOR FM TUNER
Oiled Walnut cabinet, brushed gold front panel, vertical styling, internal batteries. Sensitivity: Better than 10uV. Audio Output: More than 500 mV (input level 25db). Signal to Noise Ratio: More than 35db (input level 25db). 6 Transistors, 3 diodes. £8.19.6

FM MULTIPLEX STEREO ADAPTER
Printed circuit biscuit, 4 trans. 6 diodes 9V with full instructions £4.19.6

LOUDSPEAKERS

GUITAR, P.A., or HI-FI
12" 25 watt, 15 ohm, 25-13K, Ceramic £5.7.0

10" 10 watt, 15 ohm, CERAMIC — 49/6 2" 40 ohm 6/6
MAGNET

SPEAKER CABINET £8
Takes 12" or 10" Speaker and a 4" or 3" Tweeter. Ht. 21", W. 15", D. 7 1/2". Polished Teak, matching ymair grille, list price £9.5.0.

CABINET Teak 231 x 131 x 91", contemp. 12" legs for Tape Recorder and Tuner or Amplifier, etc. 89/6
4 pole changerover, ideal for models.
1 1/2" x 1 1/2" x 7/8", 700 ohm 9-24V, 185 ohm 6-12V, 430 ohm 9-18V

RELAYS 10/-

TWEETER 19/6
3" 16 ohm, 10 watt crossover 3k Ohm, Horn type Hi-Fi 18,000 c/s

CROSSOVER NETWORK 15/-
3kc/s, 16 or 3 or 8 ohm.

CHARGER RECTIFIERS
F.W. 12 volt 1 Amp. 5/-
F.W. 12 volt 4 Amp. 10/6

CHARGER TRANSFORMER
250/12 volt. 3/- 3/P
1A 13/-, 2A 16/6
4 Amp 21/6

SUPER SILICON RECT. T.V., etc., 1,200 PIV 800mA, 4/8; or complete with instr. resistor, condenser, 6/-; 400 PIV HW 6A, 8/-.

MULTIMETERS from 32/-

TRANSISTORS
2N3638A 5/-, 2N3643 5/6, AC138 5/-, AC141 5/-, ACY20 3/8, ACY21 4/-, AF178 11/8, AF186 10/-, BC108 2/6, BCY33 4/8, BF181 7/-, NKT213 5/6, NKT226 5/6, OA81 1/6, OA2270 3/6, OC45 2/-, OC81D 2/3, OC82 4/-, OC200 3/3, GET103-113-118-119-887-889-890-896-7-8 3/-

SWITCH ROTARY RECIPROCATING 4 Position, 15amp. Single hole fixing, with instructions. List 14/7 C90 CASSETTE 7/6, C90 12/6, 3 Post free

Stamped envelope for full selection and bargain offers in MULTIMETERS, RADIOS, BABY ALARMS, INTERCOMS, WALKIE-TALKIES, RECTIFIERS, SINCLAIR, DULCI, UNDER £1 — P. & P. 6d. £1 to £3-1/6 over £3-2/6 C.O.D. 3/6. MAIL ORDER ONLY. U.K. ONLY

DURHAM SUPPLIES
367 KENSINGTON STREET
BRADFORD 8, YORKSHIRE

TOP PRICES PAID for new valves and components. Write **KENSINGTON SUPPLIES (B)**, 367 Kensington Street, Bradford 8, Yorks.

RECEIVERS AND COMPONENTS
(continued)

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semiconductor and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/-, P. & P. 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 55/-, P. & P. 7/6. With a guaranteed minimum of 350 transistors.

GIANT PANELS. 5 1/2in x 4in, min. 20 transistors, 9 x 56 uH inductors, resistors, diodes, etc. 3 for £1. P. & P. 2/-.

As above, only 21 transistors, 70 diodes, 62 min. 1/4W resistors. 3 for 25/-, P. & P. 2/-.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-, P. & P. 2/-.

TRIM POTS. On 2in x 4in boards + Ta caps and other components. Ideal for organ keyboard tuning, etc. 100u, 500u, 15K, 20K. Stacc requirements. 5 boards 10/-, P. & P. 2/-.

NPN GERMANIUM .T05 1 WATT POWER TRANSISTORS. On small heat sink, on 2in x 4in panel. 5 for 10/-, P. & P. 2/-.

POWER TRANSISTORS. Sim. to 2N174 ex-ect. On Finned Heat Sink (10D). 4 for £1. P. & P. 5/-.

DIODES. Ex eqpt., Silicon, 150 PIV, 10 amp. 4 for 10/-, 150 PIV, 20 amp. 4 for £1. Post free.

MINIATURE GLASS NEONS, 13/6 doz. **PAPST FANS.** Powerful Extractor/Blower fans. 4 1/2" x 4 1/2" x 2". 230/250V, 100 c.f.m., 2,800 r.p.m. Weight 2 lb. 12oz. 50/- post free.

SPRAGUE POLYESTER. 0.22uF 250V small capacitors. 5/- doz. P. & P. 1/-.

SPRAGUE ELECTROLYTICS. 4uF 150V. 5/- doz. P. & P. 1/-.

TANTALUM CAPS. 2.2uF 50V. 8/- doz. P. & P. 1/-.

NEW MIXED COMPONENTS. 150 High stab. Resistors 5% and better. 12/6. P. & P. 1/-.

250 mixed resistors. 1/4W + 1/2W. 12/6. P. & P. 1/-.

Large handful of mixed capacitors. 12/6. P. & P. 1/-.

LARGE CAPACITY ELECTROLYTICS. 4in, 2in diam. Screw terminals. 7/6 each post free. 4,000uF 72V d.c. wkg.

4 1/2" x 2". Plessey 1,500uF 150V d.c. wkg. 8/- each. 3" x 1" Plessey 2,000uF 25V d.c. wkg. 6/- each.

KEYTRONICS, 52 Earls Court Road London, W.8. Mail order only Tel. 01-478 8499

R & R RADIO

51 Burnley Road, Rawtenstall
Rossendale, Lancs
Tel.: Rossendale 3152
VALVES BOXED, TESTED & GUARANTEED

BF80	3/-	PCC84	3/-	PY81	3/6
EBF89	3/6	PCF80	3/-	PY82	3/6
ECC82	3/-	PCF82	3/6	UI91	4/6
ECL80	3/-	PCL82	4/-	6F23	5/-
EF80	1/6	PCL83	4/-	30F5	2/6
EF85	3/-	PL81	4/-	30L15	5/-
EY86	4/-	PL84	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/-
EBC41	4/6	PY33	5/-	50CD6G	7/6

Transistor Audio Pack, 2G339A, 2G381A, 2G371B 10/- each post 6d.
POST, ONE VALVE 9d. TWO TO SIX 6d. OVER SIX POST PAID.

RECEIVERS AND COMPONENTS
(continued)

TRANSISTOR PANELS

INTEGRATED CCT'S TAKEN FROM PANELS
A — Quad 2 1/2 P Gate 3/- With Pin Connections
B — Dual 4 1/2 P Gate 3/-
C — Dual 2 Level Gate 3/-
F — Single 1/2 P Gate 3/- Post Paid

EX GOVMT. RECEIVER R.209 covering 1-20 mc/s 12V D.C. Input £12.10.0 Post Paid (Tested).

50 VARIOUS TRANSISTORS on Panels 15/- Post Paid.
20—OC45 £1
20—OC76 £1
40—TK28c £1

COMPUTER PANELS with 40 sil. pnp or npn transistors, Diodes and res., 22/6 Post Paid.

COMPUTER PANELS WITH SEMI-CONDUCTORS. Postage 6d per panel
8—OC43 or GET875 + 24—OA81 7/6
24—A1678 (V405A) 550 mc/s PNP + 24 Diodes 15/-

4—OC170 + 2—OC139 + 2—OC42 7/6
9—ASZ20 + 1—T2040 + 27 Diodes 7/6
4—OC42 + 6—GET875 + Diodes 7/6
2—OC170 + 1—2G306 + OC42 4/-

5—OC23 + 15—OA10 25/-
8—ASZ20 + 80 Diodes 7/6
6—ASZ21 15—OA91 6/-
9—SB240 + 18—OA47 10/-

12—2G106 + 24 Diodes 9/6
8—OC72 + 8—OA10 10/-
8—OC76 + 8—OA10 7/6
12—A1678 (V405A) 550 mc/s PNP + 22 Diodes 10/-

36—OA5 6/-
6—GET872 + 8—OA10 5/-
4—OC42 3/-
12—ASZ20 + 80 Diodes 9/6

4—GET872 + 8—OA10 3 for 12/-
4—2G106 + 1—2N2410 4/-
2—OC42 + 8—OA47 3/-
2—GET872 + 4—OA10 + RF Chokes 3 for 10/-

24—Sil. h.f. Transistors 15/-
3—GET872 + 3—GEX541, ETC. 22/6
3—OC23 + 6—OA10 + 2—OA5 16/-

ELECTROLYTICS 25,000 @ 12V, 16,000 @ 12V, 15,000 @ 10V, 10,000 @ 30V, 4,000 @ 60V, 2,000 @ 50V, 1,200 @ 180V, 8/6 Post Paid.

ZENER DIODES—2.4, 2.7, 3.6, 4.75, 6.2, 6.8, 7.5, 13, 15, 16, 18, 20, 27, 30, 33 volts. 3/6 each, mostly 1 watt

POLYSTYRENE CAPACITORS. 125V, 18, 22, 120, 220, 270, 330, 390, 560, 820, 1,000, 1,200, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 2/6 doz. Post/Packing, 1/-.

BRAND NEW BOXED CHASSIS containing 2—OC35, 2—OC29 12 WW resistors 23/- Postage 1/6

NEW CROSS RADIO
6 OLDHAM ROAD, MANCHESTER 4

NEW FULL SPECIFICATION DEVICES.

Integrated Circuits complete with data:
GEPA230 Audio Preamp/ifier 18/6 each,
GEPA234 1W Audio Amplifier 17/6 each,
GEPA237 2W Audio Amplifier 32/6 each,
MEL11 Photo Darlington Amplifier 9/6 each,
High quality low cost plastic transistors:
GE2N5172 NPN 200mW Transistor 1/9 each,
ME0412 PNP 200mW Transistor 3/9 each.
Westinghouse guaranteed plastic rectifier:
IN4820 1-5A 400V Si Rectifier 2/6 each. C.W.O. P. & P. 1/- per order. JEF ELECTRONICS, York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only.

PRINTED CIRCUIT BOARDS FOR P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.
EXAMPLES
Waa-Vaa pedal Vol 4 No. 7 2/9d. ea. Audio Sig. Gen. (Sine and Square on one board) Vol 5 No. 10 8/6d. ea. Mic. Mixer (3 Boards) Vol 5 No. 4 12/-d. Set. Stockmarket Vol 4 No. 12. Central S.E. 6/-d. ea. Players 3/-d. ea. S.A.E. For List. Trade enquiries welcomed, P.H.E. ELECTRONICS, Industrial Estate, Sandwich, Kent. Tel. 2517.

RECEIVERS AND COMPONENTS

(continued)

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard Alloy Chassis

Width	Depth	4" Height £ s. d.	6" Height £ s. d.	7 1/2" Height £ s. d.
6 1/2"	3 1/2"	12 6	15 0	18 0
6 1/2"	4 1/2"	13 6	18 0	1 0 0
8 1/2"	3 1/2"	15 0	1 0 0	1 1 0
8 1/2"	6 1/2"	1 1 0	1 6 6	1 11 3
10 1/2"	7 1/2"	1 8 6	1 15 6	1 18 9
12 1/2"	5 1/2"	1 1 0	1 6 6	1 11 0
12 1/2"	5 1/2"	1 8 0	1 14 0	1 17 6
12 1/2"	8 1/2"	1 16 0	2 3 0	2 7 3
14 1/2"	3 1/2"	1 5 0	1 11 6	1 14 0
14 1/2"	9 1/2"	2 3 0	2 15 9	2 18 6
16 1/2"	6 1/2"	1 18 6	2 6 3	2 11 6
16 1/2"	10 1/2"	2 10 0	3 5 0	3 11 9

Cases—Post 4s. 6d. per order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

W. x D.	H.	W. x D.	H.	W. x D.	H.
6" x 3"	5 6	10" x 7"	8 6	14" x 3"	7 3
6" x 4"	5 6	12" x 3"	8 9	14" x 9"	14 6
6" x 3"	6 8	12" x 5"	7 9	16" x 6"	10 9
8" x 6"	7 9	12" x 8"	10 9	16" x 10"	16 0

Chassis—Post 3s. 0d. per order.
Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases
46 LOWFIELD ROAD
STOCKPORT, CHESHIRE
Tel. 061-480 2179

TERRIFIC TRANSISTORS!

Brand New. No seconds. No re-marks
Orders over 10/- UK post free.

AD161/2 high-gain (80-250) complementary audio power pair. SPECIAL OFFER: AD161 and AD162 WITH TWO INSULATING KITS, ONLY 12/-, UK post paid.
BC168B, high-gain (250-500), small-sized exact equivalent of BC148, only 2/3.
BC169C, high-gain (450-900) equiv. BC149, 2/6; **BC107**, 3/-; **BF167**, 5/3; **2N706**, 2/7. List 6d. Free with orders.



Mini Mains Trans. 1" x 1" x 1 1/4"

MT9, 9.0-9V, 80mA 12/6

MT6, 6.0-6V, 100mA 13/6

MT12, 12.0-12V, 50mA 13/6

Submin. bridge rect., 30Vrms, 150mA, 3/6

AMATRONIX LTD. (Mail order only)
396 Selsdon Rd., South Croydon, Surrey
CR2 0DE

TESTED UNMARKED, 2N706, 2N697, 2N1132, 2/- new; ECC82's 3/6. Post free. R. RAPHAEL, 70 Eileen Gardens, Birmingham, 37.

REVERBERATION UNITS, genuine GIBBS Hammond type with circuit and plugs **£7.12.6**; with printed circuit amplifier **£10.12.6**. **THORNHITHE LTD.**, 15 Mill Crescent, North Kessock, Inverness.

ELECTRICAL

240 VOLT ELECTRICITY ANYWHERE



BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY
Exclusive World Scope Purchase. The fabulous **Mk.2D American Heavy Duty Dynamotor** Unit with a Massive 220 watt output and giving the most Brilliant 200/240 volt performance all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested. Only **£4.19.6** + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.

Dept. PE, STANFORD ELECTRONICS
Rear Derby Road, North Promenade
BLACKPOOL, Lancashire

CRESCENT RADIO LTD.

(electronic component specialists)

For all regular components try

40 Mayes Road, Wood Green, N.22

For surplus components and equipment try

11 Mayes Road, Wood Green, N.22

BARGAIN COMPUTER BOARDS

Assorted Components mounted on boards all with long tags. Ideal for breaking down and experimenting with. Take advantage of bulk purchase

1 Board 2/- each
20 Boards 20/-

PRINTED CIRCUIT BOARD

8 x 6 inch One Sided Board ... 2/- each

TRANSISTOR RADIO PANEL

Incomplete Min. Radio Panel; I.F.T.s; Transistors; Resistors; Capacitors; All for 2/- per panel.

COMPONENT BARGAINS

S.P. Flick Toggle Switch, 2in. Dolly ... 3/6 each
250V 2 amp. Toggle Switch ... 1/6 each
4 Pin Transistor Holders ... 6d. each
1in. Spun Aluminium Knobs, 1/2in Spindle ... 2/6 each
OC19 Power Transistor ... 5/- each
Low Impedance Transistor Earpiece ... 1/6 each
2 1/2in 8ohm Loudspeaker ... 5/6 each
Continental Razor Adaptor Kit ... 7/6 each
100mF 6V d.c. Transistor Capacitor ... 9d. each
500mF 6V d.c. Transistor Capacitor ... 1/- each
6,800pF Mullard Capacitor 400V d.c. ... 6d. each

We have large stock of

Veroboard; Valves; Transistors; Loudspeakers; Auto-Changers; Recording Tape; Cable; Hi Fi

Send 1/6d for Our Catalogue

Postage with order please

P. & P. 1/-
Telephone
01-449 3087

WENTWORTH RADIO

104 SALISBURY ROAD
BARNET, HERTS.

New catalogue available. S.A.E. please. By return post all orders

AA120	5/-
ACY17	5/3
ACY18	4/6
ACY19	5/-
ACY20	3/6
ACY21	5/-
ACY22	3/9
ACY40	4/-
ACY41	4/6
AC126	4/-
AC127	5/-
AC128	3/6
AC176	5/6
AD140	8/-
AD161	8/-
AD162	7/6
AF114	4/6
AF115	3/9
AF116	3/6
AF117	3/6

AF118	8/-
ASV62	5/6
BC107	3/-
BC108	3/-
BF185	6/-
BFX12	5/6
BFX13	6/-
BFX29	8/6
BFX30	7/6
BFX43	8/-
BFX44	8/-
BFX68	12/-
BFX68A	13/-
BFX84	7/-
BFX85	12/-
BFX86	7/6
BFX87	12/-

BFX88	10/6
BFX92A	6/6
2N918	7/-
2N929	5/-
2N930	5/-
2N2926 Orange	2/3
2N2926 Yellow	2/6
2N2926 Green	3/-
2N3705	4/6
2N3706	4/6
2N3707	4/-
2N3708	3/6

SPECIAL OFFERS

BF180 6/6
BF184 4/6

Integrated Circuits. Mullard. All types Available. Enquire prices. Fairchild L900 9/6 L914 9/-

DIOTRAN SALES

P.O. BOX 5
WARE, HERTS
TEL.: WARE 3442

SIL. G.P. DIODES	
300mW	30
40PIV (Min.)	100
Sub-Min.	500
Fully Tested 1,000	£5
Ideal for Organ Builders.	£9

Post and Packing costs are continually rising. Please add 1/- towards same. **CASH WITH ORDER PLEASE. GIRO No. 30-102**

OVERSEAS QUOTATIONS BY RETURN SHIPMENTS TO ANYWHERE IN THE WORLD

OVER 3 MILLION SILICON ALLOY & GERM. TRANSISTORS AVAILABLE FOR IMMEDIATE DELIVERY

TRANSISTORS	Qty. Price	Qty. Price	Qty. Price	Qty. Price
Type and Construction	100	500	1,000	10,000
A 1 Germ. A.F. PNP T0-1 = AC127, NKT773, AC157, ASY86	£3.10	£15	£25	£200
A 2 Germ. A.F. PNP T0-5 = ACY17-21, NKT237-245	£1	£3	£5	£40
A 3 Germ. A.F. PNP T0-1 = AC128, NKT271, 2G381	£1	£3	£5	£40
A 4 Germ. R.F. PNP T0-1 = OC44-45, NKT72/125, ASY54	£1.10	£4.10	£7.10	£60
A 5 Germ. R.F. PNP T0-5 = 2N1303, NKT164-7, 2G301-3	£1.10	£4.10	£7.10	£60
A 6 Germ. V.H.F. PNP T0-1 = AF116-7, KNT667, 2G417	£3.10	£15	£25	£200
A 7 Assorted Germ. A.F.-R.F. PNP mixed cases, general purpose 15s.	£2.10	£4	£7	£32
A 8 Germ. A.F. 50-2 PNP = 2G371-89, ACY27-31, OC71-75	£2	£7.10	£12.10	£100
A 9 Sil. Alloy PNP T0-5 = 25301-5, BCY17-29, BCY30-34	£2	£7.10	£12.10	£100
A10 Sil. Alloy PNP 50-2 = 25321-325, OC200-205	£2	£7.10	£12.10	£100
A1 to A7 Guaranteed 80% Good usable Transistors ideal for low cost production work and experimental use. A8 to A10 are all perfect devices, factory tested, no open or short circuit Transistors in these lots.				

I/- each	TESTED TRANSISTORS ONE PRICE ONLY PNP, NPN. SILICON PLANAR 1/- EACH				I/- each
BC108	2N696	2N1132	2N2220	2S733	
BC109	2N697	2N1613	2N3707	2N3391	
BFY50	2N706	2N1711	2N3711	T1544	
BFY51	2N708	2N2904	25102	2N2906	
BFX84	2N929	2N2905	25103	2N2907	
BFX86	2N930	2N2924	25104	2N2696	
BFX88	2N1131	2N2926	25732	2N3702	

From Manufacturers' Over-runs—Unmarked Plastic and Metal cases. Devices similar to above Nos.

BRAND NEW FULLY TESTED EPOXY CASE UNIJUNCTION TRANSISTORS. Type T1543 and BEN 3000 and replacement for 2N2646. Full data available. **LOWEST PRICE AVAILABLE ANYWHERE. 100 off 4/- each = £20; 500 off 3/6 each = £87.10; 1,000 off 3/- each = £150.** Sample devices 7/- each on request.

PLASTIC PNP SILICON TRANSISTORS. Manufacturers' seconds from 2N3702-3 family. Ideal cheap trans. for manufacturing, etc. £8.0.0.—500, £13.10.0—1,000 pieces.

HIGH QUALITY SILICON PLANAR DIODES. SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, OA202, BAY38, 15130, 15940. 200,000 to clear at £4 per 1,000 pieces. **GUARANTEED 80% GOOD.**

PLASTIC NPN SILICON TRANSISTORS. Manufacturers' seconds from 2N3707-3711 family. Ideal cheap trans. for manufacturing, etc. £7.10.0—500, £12.0.0—1,000 pieces.

SILICON PLANAR PLASTIC TRANSISTORS. 2N3708A VcB30 Hfe 20-60. All marked, fully tested and guaranteed. 1 off 1/6 each; 100 off 10d. each; 500 off 9d. each; 1,000 off 7½d. each.

TO-18 METAL CAN SILICON PLANAR TRANS. Very high quality, 99% good. Type 2N706, BSY27. £8 per 500 pieces. £13 per 1,000 pieces.

TO-5 METAL CAN SILICON PLANAR TRANSISTORS. VERY HIGH QUALITY 99% good type. 2N697, BFY51, 2N1893, £8 per 500 pieces. £13/0/0 for 1,000 pieces.

TOP HAT RECTIFIERS. All good. No short or open circuit devices. Voltage range 25-400PIV, 750mA. £3 per 100, £12.10.0 per 500.

GERM. PNP AND NPN TRANSISTORS FULLY TESTED, UNMARKED SIMILAR TO 1/6 EACH							
AC125	ACY22	ACY36	NKT677	OC81	2S738		
AC126	ACY27	NKT141	NKT713	OC82	2G382		
AC127	ACY28	NKT142	NKT773	2G301	2G399A		
AC128	ACY29	NKT212	OC44	2G302			
AC130	ACY30	NKT213	OC45	2G303			
ACY19	ACY31	NKT214	OC71	2G308			
ACY20	ACY34	NKT215	OC72	2G371			
ACY21	ACY35	NKT271	OC75	2G374			

BACK IN STOCK

EX-COMPUTER PANELS I.B.M. Size 2 1/2" x 4 1/2" with TRANSISTORS, DIODES, RESISTORS, CAPACITORS, etc. Over 1/2 million already Sold out to the Trade, at our Ridiculous Price of £3 per 100 panels or £28 per 1,000 panels. Plus carriage 6/-.

TRANSISTOR EQVT. BOOK

2,500 cross references of transistors—British, European, American and Japanese. A must for every transistor user. Distributed by DIOTRAN SALES. 15/- EACH.

TEXAS 2G371 A/B Eqvt. OC71 Germ. Gen. Purpose Trans.

1-99	Each
100-499	1/6
500-999	1/3
1000 up	1/2
	9d.

All Brand New and Coded.

Vast mixed lot of subminiature glass diodes. Comprising of Silicon, Germ., Point Contact and Gold Bonded types plus some Zeners, 500,000 available at Lowest of Low Price. 1,000 pieces £3.0.0, 5,000 pieces £13.10.0, 10,000 pieces £23.

CITY AND COUNTY OF BRISTOL BRISTOL POLYTECHNIC CAREERS IN RADIO AND RADAR

Marine Radio Officers

2-year full time course leading to the Second and First Class P.M.G. Certificates and the B.O.T. Radar Maintenance Certificate.

Conversion Course (Second Class to First Class).

R.T. Licences (Full or Restricted).

Courses for Qualified Marine Radio Officers

Single Side Band Techniques (2 weeks).

Marine Electronics Diploma Course (3 months).

Advanced Marine Electronics Diploma Course (3 months).

Training is given on the latest types of Marine and Aircraft equipment in approved Laboratories at THE SCHOOL OF RADIO AND RADAR.

Senior Lecturer-in-Charge: F. E. Barltrop.

For further information, apply:

**Chief Administrative Officer
Bristol Polytechnic
Ashley Down BS7 9BU**

Licensed Aircraft Radio Engineers

2-year full-time course covering the Aircraft Radio Engineers Licences categories A & B, issued by the Board of Trade (Civil Aviation) followed by a six-months course for Radar Rating (A & B) in association with the above.



BAKER MAJOR £8

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker magnet assembly Alcomax II having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module as illustrated 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6.

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665

LOW COST SEMICONDUCTORS!!!

RETURN OF POST SERVICE

BC108, BC108, BC109, 2N706, OC71-5, OC81, OC44/45 11d each (10/- dozen)

(All semiconductors are supplied on a true-to-spec money back guarantee. Type Nos. listed are for description. Goods are individually selected from over-runs)

1/4W resistors, any preferred value. 4-7Ω to 10MΩ, ±10%. 1 1/2 d each, 1/3 dozen of any one value, 10/- hundred.

5% high stability resistors, fully insulated, 1/4W 4d, 1W 7d, 2W 10d. Open circuit jack sockets 2/6, closed circuit 3/3.

4000µF/72V electrolytics, 7/-, 10µF/16V Mullard 11d. 16µF/10V, 25/25, 25/16, 11 1/2d. 100µF/140V, 160/25, 64/64, 2/3. 0.1µF/400V. 10d each.

LET US KNOW YOUR REQUIREMENTS FOR P.E. KITS. FOR A COMPETITIVE QUOTATION

Min. order 10/-, plus 1/- post. Please deduct 7 1/2% for order of over £3.

**NEWBURY SOUND EQUIPMENT (Retail Dept.)
9 Upper Grove, S.E.25 (callers by appointment)**

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

ELECTRONIC ENG.

Advanced Electronic Eng.—
Gen. Electronic Eng.—
Applied Electronics—
Practical Electronics—
Radar Tech.—
Frequency Modulation—
Transistors.

ELECTRICAL ENG.

Advanced Electrical Eng.—
General Electrical Eng.—
Installations—
Draughtsmanship—
Illuminating Eng.—
Refrigeration—
Elem. Elec. Science—
Elec. Supply—
Mining Elec. Eng.

CIVIL ENG.

Advanced Civil Eng.—
General Civil Eng.—
Municipal Eng.—
Structural Eng.—
Sanitary Eng.—
Road Eng.—
Hydraulics—
Mining—
Water Supply—
Petrol Tech.

RADIO & T.V. ENG.

Advanced Radio—
General Radio—
Radio & TV Servicing—
TV Engineering—
Telecommunications—
Sound Recording—
Automation—
Practical Radio—
Radio Amateurs' Examination.

MECHANICAL ENG.

Advanced Mechanical Eng.—
Gen. Mech. Eng.—
Maintenance Eng.—
Diesel Eng.—
Press Tool Design—
Sheet Metal Work—
Welding—
Eng. Pattern Making—
Inspection—
Draughtsmanship—
Metallurgy—
Production Eng.

AUTOMOBILE ENG.

Advanced Automobile Eng.—
General Auto. Eng.—
Auto. Maintenance—
Repair—
Auto. Diesel Maintenance—
Auto. Electrical Equipment—
Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? A.M.I.E.R.E., B.Sc.(Eng.), A.M.S.E., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Ex., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
D9, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Electronics, Radio, T.V., Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Electronics Electronics Engineering Practical Radio Radio & Television Servicing Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy now—FREE and without obligation.



POST COUPON NOW!

TO B.I.E.T., D9, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published approximately on the 15th of each month by ICP Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by The Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia, Malawi and Zambia—Kingstons Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2 2s. 0d. Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES

BUILD A QUALITY 4 TRACK TAPE RECORDER



To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board - in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL, MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises Deck, Amplifier, Cabinet and speaker, with microphone, 7 1200 H tape, and spare spool. ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY

SCOOP! STAAR RECORD PLAYER

Deck plays 33, 45, 78, R.P.M. records. 9 volt operated, with mono cartridge. BRAND NEW as illustrated



PRICE 59/6.
p.p. 3/6.
Send for leaflet
No. 2




MULLARD 1 WATT AMPLIFIER

Portable Transistor Unit ideal for Intercoms, Baby Bells, Telephone, Record Players or Guitar Practice. 9 Volt 5 transistors with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK. PRICE 45/- p.p. 2/6.

OTHER ITEMS: Suitable 7 x 4 inch, 3 ohm speaker 17/6 p.p. 1/6. Revox covered cabinet 12 x 9 x 4 12/6 p.p. 2/6. P.P. 9 Volt battery 3/9. Write for leaflet No. 2.

GARRARD RECORD DECKS

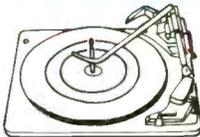

All the latest models BRAND NEW and guaranteed - TERRIFIC SAVINGS!

- *2025 STEREO £ 7 19.6
- *2025TC DIAMOND 9TAH.C £ 9 19.6
- *3000 STEREO 9TAH.C £ 9 19.6
- *SP 25 Mk.II £11 19.6
- *SL 55 £12 10.0
- *A70 Mk.II £13 10.0
- *AT 60 K.II £13 10.0
- *SL 65 £14 14.0
- *AP 75 £15 0.0
- *401 £28 7.6
- *SL 75 £29 0.0
- *SL 95 £35 0.0
- *GL 75 GOLDRING £33 0.0
- *GL 75 P £46 15.0

ALSO IN STOCK - THORENS - LENC0 - B.S.R. Carriage/Insurance 7/6 extra on any model. WBA BASES £3.19.6. PERSPEX COVERS £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carriage 5/- Complete range of Cartridges/Plinths/Covers. SEND FOR 8 PAGE BROCHURE 16/17 TODAY.

BUILD YOURSELF A QUALITY RADIO



New printed circuit design with full power output. Fully tuneable on both mw/lw. bands. 7 Mullard transistors. Fitted 5" speaker. Room Filling Power. Easy to build with terrific results. All local and continental stations. Complete detailed instructions.

TOTAL COST £6.19.6. p.p. 4/6.
Ask for Leaflet No. 1.

TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW 1969 LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36). Whether you require one or 1000, devices we can fulfil your order from stock! For quantity quotations telephone (011 723 0401) Ex. 4 or (01) 402 6823.

HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Mike, Tuners.

16 transistor mains operated. Output 5.5 watts for 8 15 ohm speakers. Black, silver and wood finish, size 13" x 3" x 6".

PRICE £13.10.0. p.p. 7/6. (Leaflet on request)

Complete Stereo System 5-5. Garrard 2025 stereo, 5.5 Amplifier, Plinth/Cover, Two 10 watt speakers with tweeters in polished cabinets.

Usual price £47.0.0. OUR PRICE £39.10.0. p.p. 20/- ASK FOR BROCHURE 13



SINCLAIR EQUIPMENT

The SINCLAIR IC-10 is the worlds first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself has an output power of 10 watts, yet with an overall size of 1 x 0.4 x 0.2 in.

IC 10 Integrated Circuit Amplifier	59/6	OTHER TYPES OF INTEGRATED CIRCUITS	52/6
730	89/6	RCA CA3014	20/6
Stereo 60	£9 19.6	RCA CA3018	22/6
P25 Power Supply	£4 19.6	RCA CA3020	29/6
O16 Loud Speaker	£8 19.6	RCA CA3026	19/6
213 Amplifier	89/6	Sinclair I.C.10	59/6
PZ 4 Power unit	99/6	G.E. PA230*	22/6
Stereo 25	£9 19.6	G.E. PA234*	20/0
O16 Speaker system	£7 19.6	G.E. PA237*	37/6

All post paid, delivery from stock.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS. 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound.

PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3. (FOR STEREO)



HENRY'S RADIO Fully Illustrated CATALOGUES

ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

COMPREHENSIVE CLEAR CONCISE CATALOGUES
A Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers 10/- value, for use with purchases.

ORDER AS CATALOGUE A PRICE 7/6. p.p. 2/-

B New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher.

ORDER AS CATALOGUE B. PRICE 7/6. p.p. 1/-

WHY NOT SEND AWAY TODAY!


AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. 11 - each unit or system will compare favourably with other professional equipment selling at much higher prices.

£11.12.6. to £38.17.6. (all units available separately).

THE FINEST VALUE IN LOW COST HIGH FIDELITY - CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS.

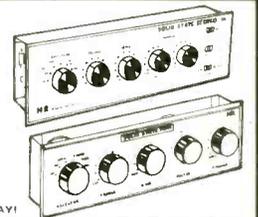SEND FOR BROCHURES No. 12/14 and 21 TODAY!



Hi-Fi equipment to suit EVERY POCKET

HIGH FIDELITY AUDIO EQUIPMENT CATALOGUE 5/ p.p. 1/-



VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of - AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS - IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40 - £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

ELECTRONIC ORGANS

COMPLETE KITS FOR THE HOME CONGRAN

STAR FEATURES
*ALL TRANSISTOR PRINTED CIRCUIT DESIGNS.
*BRITISH DESIGN *STEP BY STEP DETAILED INSTRUCTIONS. *SAVES UP TO 50% ON COMMERCIAL EQUIVALENT *EVERYTHING SUPPLIED DOWN TO THE LAST ITEM *FULL AFTER-SALES SERVICE & ADVICE. *CREDIT SALE & H.P. TERMS AVAILABLE

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music - to a two manual five octave deluxe model with OAK CONSOLE from £285 for the serious musician

These kits are the result of 25 years of research and design and offer the best that is essential to good organ designs, coupled with excellent value are within the reach of most pockets. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals will produce an instrument that will be a delight to own and use and will give years of trouble free entertainment for the whole family.

SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON CALL IN SEE, HEAR, PLAY FOR YOURSELF

Organ Demonstration Room 1st Floor

PRACTICAL ELECTRONICS ORGAN ORGAN COMPONENTS

We are able to supply all items for this series, details on request.

Start building for as little as £10

MODELS FROM £99 - £350.



ILLUSTRATION OF GROSVENOR ELECTRONIC ORGAN

Built models available from £124

HENRY'S RADIO LTD.

Mail Order Dept., Components, Organ Dept.
303 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 1008/9

High Fidelity and Equipment Centre
309 EDGWARE ROAD, LONDON W.2.
Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS 9am-1pm